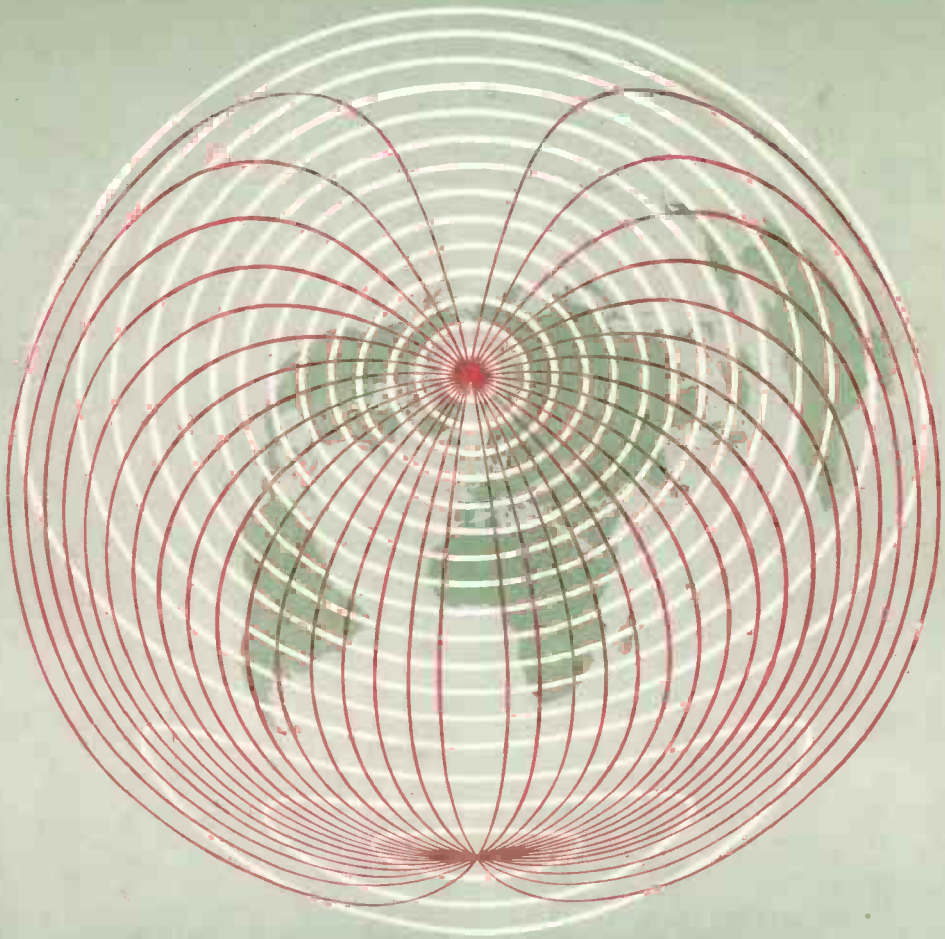


Wireless World

DECEMBER 1951

TWO SHILLINGS



RADIO, TELEVISION AND ELECTRONICS



As the smallness of the ingeniously designed BICC Multicore Camera Trailing Cable is made possible by the use of solid conductors, this moulded-on coupler was developed mainly to overcome end breakage, which otherwise would be a serious problem with this type of cable. But the unique design of this coupler presents other advantages—it ensures reliable contact, adequate screening and great mechanical strength, leading to a long and trouble-free life.

BICC T/V Camera Cables with moulded-on couplers have satisfactorily withstood arduous service on BBC T/V Cameras.



POLYPOLE CABLE COUPLER

BRITISH INSULATED CALLENDER'S CABLES LIMITED
NORFOLK HOUSE, NORFOLK STREET, LONDON, W.C.2

Wireless World

RADIO, TELEVISION
AND ELECTRONICS

41st YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK, M.I.E.E.

Editor: H. F. SMITH

DECEMBER 1951

In This Issue

| | |
|---|-----|
| EDITORIAL COMMENT | 479 |
| RADIO FEEDER UNIT. By <i>J. F. O. Vaughan</i> | 480 |
| CONTINENTAL GRAMOPHONE RECORDS | 485 |
| DESIGN FOR AN F.M. RECEIVER—2. By <i>J. G. Spencer</i> | 487 |
| SHORT-WAVE CONDITIONS. By <i>T. W. Bennington</i> | 490 |
| RADIO FOR TAXIS | 491 |
| POTTED CIRCUITS | 493 |
| R.F. CHOKES. By " <i>Cathode Ray</i> " | 494 |
| LETTERS TO THE EDITOR | 499 |
| WORLD OF WIRELESS | 501 |
| VALVE CATHODE LIFE. By <i>C. C. Eaglesfield</i> | 505 |
| OSCILLOSCOPE "HUM". By <i>W. Tusting</i> | 507 |
| ELECTROLYTIC CAPACITORS. By <i>G. W. A. Dummer</i> | 510 |
| RINGING-CHOKE E.H.T. SYSTEMS—2. By <i>W. T. Cocking</i> | 513 |
| WIDE RANGE SQUARE WAVE SHAPER. By <i>J. E. Atew</i> | 517 |
| MANUFACTURERS' PRODUCTS | 519 |
| RANDOM RADIATIONS. By " <i>Diallist</i> " | 520 |
| UNBIASED. By " <i>Free Grid</i> " | 522 |

PUBLISHED MONTHLY: Price 2/- (last Tuesday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. Telephone: Waterloo 3333 (60 lines). Telegrams: "Ethaworld, Sedist, London." Annual Subscription: Home and Overseas, £1 7s. 0d. U.S.A. \$4.50, Canada \$4.00. BRANCH OFFICES: Birmingham: King Edward House, New Street, 2. Coventry: 8-10, Corporation Street. Glasgow: 26B, Renfield Street, C.2. Manchester: 260, Deansgate. 3

VALVES...and their Applications

INDIRECTLY-HEATED VALVES FOR BROADCAST RECEIVERS

The Detector And A.F. Amplifier Stages

In the conventional 4-valve superheterodyne receiver the I.F. amplifier is usually followed by a double diode triode in which one diode serves as detector, the other as A.V.C. rectifier, and the triode as an A.F. voltage amplifier.

The Mullard valves for this application are the EBC41 and the UBC41, the former having a 6.3-volt heater and the latter a 0.1-amp. heater for series operation.

In each case the triode section has an amplification factor of 70 so that, as a resistance-capacitance coupled amplifier, it is capable of a gain of from 40 to 50.

In D.C./A.C. receivers the heater of the UBC41 should be connected at the earth end of the heater chain, with pin No. 1 (one of the heater pins) connected to chassis in order to keep hum to a minimum; a'd (pin No. 5) should then be used as the signal diode, and a'd (pin No. 6) as the A.V.C. rectifier.

The triode section of the EBC41 or UBC41 may be operated either with cathode bias or with grid-current bias via a grid leak of the order of 10 MΩ. The gain and maximum output voltage for a given distortion will be practically the same for either arrangement. With 20MΩ grid leak and no standing bias the input impedance for small signals will be in the order of 2 MΩ.

Negative feedback may be applied to the A.F. amplifier if desired. When doing so, however, care must be taken that the feedback voltage is not applied to the diodes; otherwise distortion will result.

For minimum hum it is desirable to keep the impedance from cathode to earth as low as possible.

DOUBLE DIODE TRIODES

TYPE EBC41 for A.C. Mains and Car Radio Sets.

TYPE UBC41 for D.C./A.C. Mains Sets

Heater

| | EBC41 | UBC41 |
|-------|-------|--------|
| V_h | 6.3 | 14.0 V |
| I_h | 0.23 | 0.1 A |

Characteristics

| | EBC41 | UBC41 |
|-------|-------|-----------|
| V_a | 250 | 170 V |
| V_g | -3 | -1.6 V |
| I_a | 1.0 | 1.5 mA |
| μ | 70 | 70 |
| g_m | 1.3 | 1.65 mA/V |
| r_a | 54 | 42 KΩ |

Limiting Values

Triode Section

| | EBC41 | UBC41 |
|------------------------|-------|--------|
| $V_{a(b)}$ max. | 550 | 550 V |
| V_a max. | 300 | 250 V |
| p_a max. | 1 | 1 W |
| I_k max. | 5 | 5 mA |
| V_g max. | | |
| ($I_g = +0.3 \mu A$) | -1.3 | -1.3 V |
| R_{g-k} max. | | |
| (cathode bias) | 3.0 | 3.0 MΩ |
| V_{h-k} max. | 100 | 150 V |
| R_{h-k} max. | 20 | 20 KΩ |

Diode Sections

| | EBC41 | UBC41 |
|-------------------|-------|--------|
| $V_{ad(pk)}$ max. | 200 | 200 V |
| I_{ad} max. | 0.8 | 0.8 mA |

THE COMPLETE SERIES

| | FREQUENCY CHANGER | R.F. OR I.F. AMPLIFIER | DET., A.F. AMPLIFR. & A.V.C. DIODE | OUTPUT PENTODES | RECTIFIERS |
|--------------|-------------------|------------------------|------------------------------------|-----------------|------------|
| 6.3V Heater | ECH42 | EF41 | EBC41 | EL41; EL42 | EZ40; EZ41 |
| 0.1 A Heater | UCH42 | UF41 | UB41 | UL41 | UY41 |

Reprints of this article together with additional data may be obtained free of charge from the address below.



MULLARD LTD., Technical Publications Department, Century House, Shaftesbury Avenue, W.C.2.

Wireless World

DECEMBER 1951

VOL. LVII. No. 12.

Encouraging Technical Writers

THERE can be no doubt that the prestige of British radio was gravely harmed when, during the period immediately following the end of the war in 1945, publication of information on wartime developments was deliberately delayed by concerted official and semi-official action. The whole technical world was hungry for details of the developments, but, for a year or more, all the information released came from non-British sources. As an indirect result of this "hangover" from wartime censorship, technical writers were discouraged; indeed, the impression became current—and is to some extent still current—that it was almost improper to write on any subject that was not already safely in the textbooks. These feelings, coupled with a widespread idea that technical writing was mildly frowned upon by employers in industry, has certainly restricted, or, at the best, delayed, publication of information on many important British developments. All too often, detailed information is released so late that it is no longer topical.

Wireless World hopes and expects that these harmful ideas will be dispelled by the wise and generous action of the Radio Industry Council in establishing a "premium" scheme for the active encouragement of technical writing. Starting from 1st January, 1952, the R.I.C. will award premiums of 25 guineas each, up to an average of six per year, "to the writers of published articles which, in the opinion of a panel of judges, deserve to be commended by the industry." Eligibility is restricted to articles by any non-professional writer published in papers or periodicals which can be bought by the public from bookstalls or by subscription. Journals of learned or professional societies and those circulating exclusively to members of a trade are barred.

In broad principle the scheme seems entirely commendable, and wisely no attempt has been made at this stage to fill in all the details. That can be done as the scheme develops; what really matters is that it has now been made clear that the industry as a body looks on technical writing by its employees and others as meritorious and worthy of reward. The

judges "are to be given the greatest possible freedom in choosing articles for awards, but they will be asked broadly to take into consideration: Value of the article in making known British achievements in radio and electronics; originality of subject, technical interest; presentation and clarity."

We hope that an incidental result of the premium scheme will be to establish the principle that there is merit in exposition of the work of others. Not all those responsible for technical developments have cultivated the art of clear writing; sometimes, too, they tend to be unsympathetic towards non-specialist readers with less knowledge of their subject than themselves.

Propaganda—and the Reverse

Obviously, it is not the object of the R.I.C. premium awards to encourage the writing of tendentious propaganda; that would spell failure from the start. But equally we think it is desirable that technical writers should realize that most foreign readers do not understand our queer national characteristic of denigrating the British way of life in all things. A particularly bad example of this appeared in the American journal *Audio Engineering* for October, where a British author, H. A. Hartley, paints a gloomy, misleading and damaging picture of the backwardness of this country, especially in the field of sound reproduction. The author is entitled to air his opinions, but should verify the facts purporting to support them. As it is, all too many of the points capable of verification are wrong. One example will serve: in the very first paragraph, Mr. Hartley, deploring what he considers to be the loss of British leadership in television, cites the arrival of the 12-in tube as the feature of this year's radio show. He is more than a year behind the times; even at the 1950 show there were more 12-in tubes than smaller ones. At this year's show the 12-in tube was commonplace, with many of 15 and 16in. And, going back to the pre-austerity era, the sight of a 12-in tube was not a matter for amazement even in 1937.

RADIO FEEDER UNIT

High Quality Pre-tuned Receiver with Gramophone Pre-amplifier

By J. F. O. VAUGHAN

THIS feeder unit is intended to provide an output of the high quality necessary to do justice to the several new amplifiers which have been described in *Wireless World* in the past few years. It provides switched selection of four stations (normally local ones), three on the medium waveband and one on the long, and an input for gramophone of sufficient gain for light-weight low-output pickups.

Except for the rectifier, which is a standard type on an octal base, B7G-type valves are used. This is done largely because of the convenience of single-ended valves for the r.f. stages from the point of view of screening. Apart from the miniature types most single ended valves are either obsolescent or have unsuitable characteristics.

From the circuit diagram it can be seen that there are two r.f. stages, V_1 and V_2 , a diode detector, V_3 , an a.f. amplifier, V_3 , to compensate for the loss caused by the tone control circuits, and a separate amplifier, V_4 , for gramophone input. A.g.c. is not provided as it is difficult to arrange a simple system which is quite free from distortion; the unit is intended primarily for the reception of local stations, where fading is negligible, and so the absence of a.g.c. should be no disadvantage.

The local stations will not, of course, be received all at the same strength and for this reason provision has been made for adjustment of the r.f. gain at each


position of the station-selector switch. Four pre-set resistors, R_1 — R_4 , one for each switch position, are provided in the cathode circuit of V_1 to enable the output from the four stations to be made the same. The resistor R_8 from the switch S_8 to h.t. + provides additional biasing current through these resistors, so increasing the range of gain variation available. R_5 biases V_1 when the gramophone input is in use. The switch S_8 is a make-before-break type so that at no time is the cathode of V_1 subjected to full h.t. potential.


The tone control circuit is the one in this year's *Wireless World* Diary and was designed to avoid the use of inductors. The pickup input circuit gives bass compensation of 6 db per octave and is intended for pickups with a fairly level bass response. Most special pickups require a particular form of compensation and the circuit recommended by the makers can be substituted for the one shown.

The detector circuit is straightforward and it will be found that even with a value of only $1\text{ M}\Omega$ for the volume control the a.c. load resistance is quite high enough compared with the d.c. load resistance to avoid appreciable distortion. (See "Diode Detector Distortion" by W. T. Cocking in the May 1951 issue of *Wireless World*.)


The high gain obtainable from the two r.f. stages makes the mechanical layout of this part of the circuit

Complete circuit diagram of the unit.

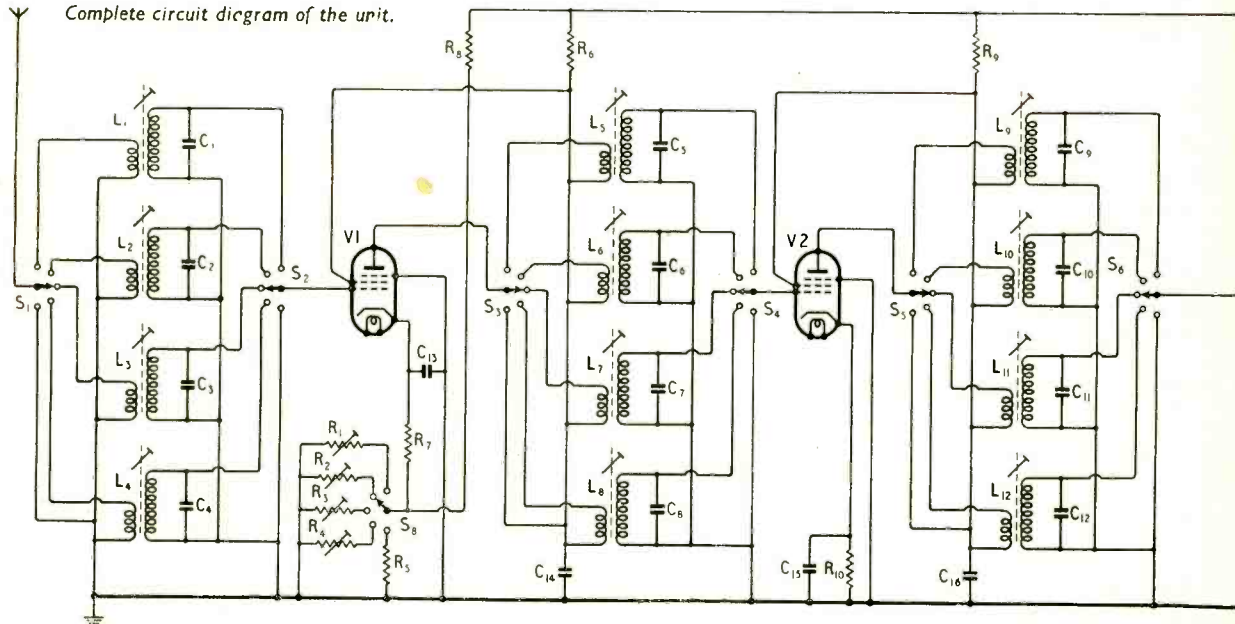

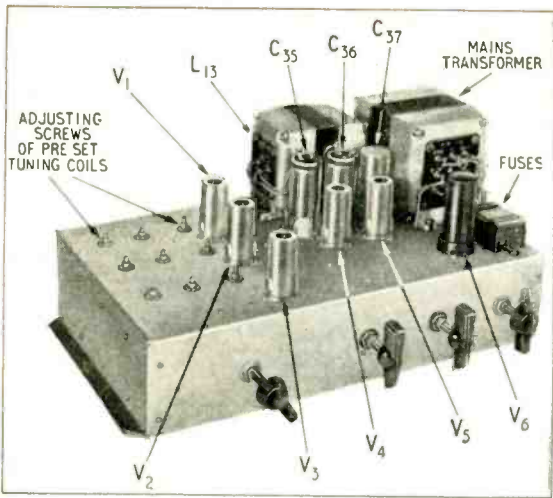

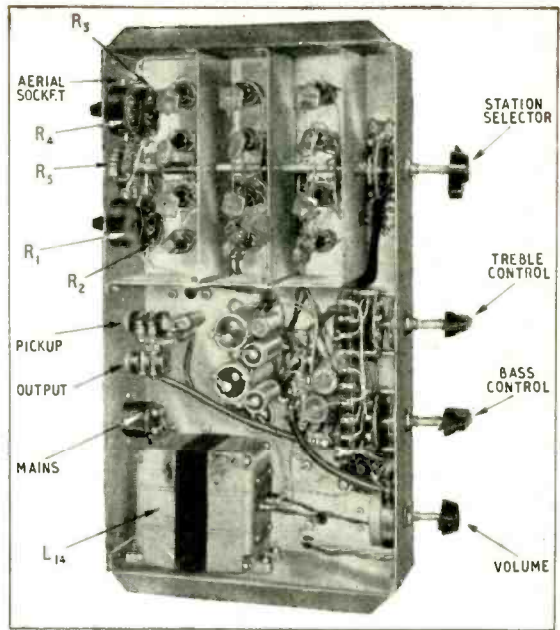Top view, showing the adjusting screws for the pre-set tuning coils.




Right: General underside view of the unit.

very difficult if stability is to be achieved. The photographs show that each set of coils and associated switch wafer is mounted on a separate sub-chassis. The sub-chassis are like inverted boxes having only two sides. They nest together, the other two sides being formed by the adjacent sub-chassis and the main chassis. They are mounted "bottom" upwards against the top of the main chassis. The coils are mounted on the "bottom," the main chassis having clearance holes for the coil-fixing nuts. One side of each sub-chassis forms a screen across the holder of the appropriate valve, except in the case of the detector. These screens and the rear of the main chassis must have holes large enough to prevent the switch shaft

from being able to touch them where it passes through them. This has a very considerable effect on stability.

The switch shaft consists of sections in convenient lengths joined by couplers—these are made of copper sheet rolled to the shape of the shaft and soldered and are fixed to the shaft by 6 B.A. screws tapped into it. Copper was chosen because it can be soldered and because it provides a slight degree of flexibility. It is not known whether it will prove too soft for continual use, but it has not yet given trouble after many operations. Standard $\frac{1}{4}$ -in flexible shaft couplers are too big and they do not line up the shafts with sufficient accuracy. Wafer switches are normally purchased assembled on rods and must, of course, be dismantled

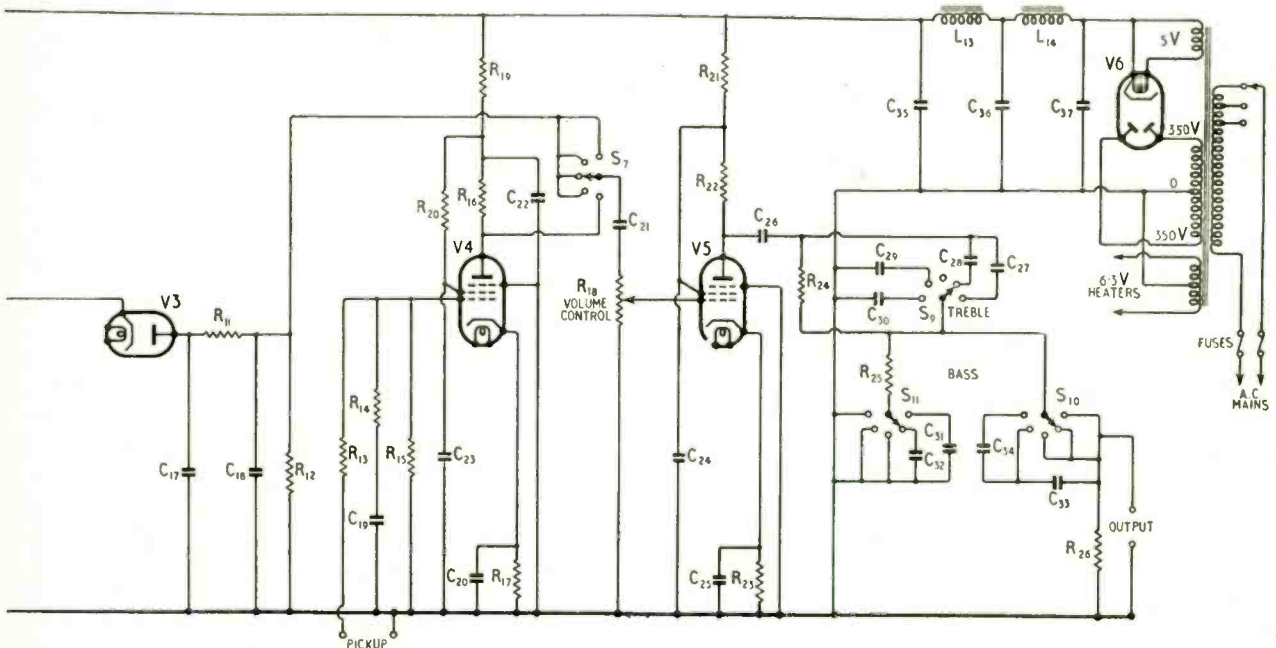


for this particular application. It is essential to line up the wafers on the various screens very accurately before inserting the shaft, as otherwise contacts will be damaged and the life of the switch will be greatly reduced.

Each sub-chassis is wired up as a separate unit, leaving only three leads to be connected when it is fixed to the main chassis. These are: (a) the lead which goes to the screen-grid pin on the valve-holder (to earth in the case of the aerial coils), (b) the lead to the valve anode (to the aerial socket in the first stage), and (c) the lead to the grid of the next valve (to the detector cathode in the third stage).

The valveholder wiring for the first and second stages is arranged so that it does not interfere with the insertion and removal of the sub-chassis. The only components on the holder are cathode and screen-cum-anode by-pass capacitors, for which metallized types are used to save space, and the cathode-bias and h.t. decoupling resistors.

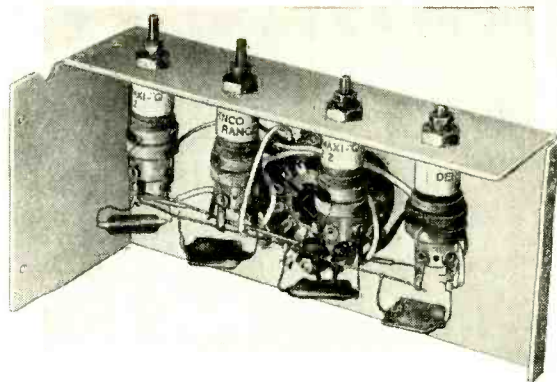The tone-control components are also assembled on to a separate unit. In this unit two switches are used, each having 2-pole 5-way contacts. In the case of the treble control, only one half of the wafer,



One of the sub-chassis taken out of the unit, showing the tuning coils and capacitors and the switch wafer.

shown as S_9 in the diagram, is used. The circuit for the bass control demands the use of the whole wafer, shown as S_{10} and S_{11} . The two halves must be wired so that when the wiper of S_{10} is at the top, so is the wiper of S_{11} ; i.e., either C_{31} - C_{32} is in circuit or

LIST OF COMPONENTS

Capacitors

| | | |
|-----------------------|---|----------|
| C_1 to C_{12} | tuning capacitors, protected silvered mica; see text. | Hunts |
| C_{13} to C_{16} | 0.01 μ F metallized paper | Dubilier |
| C_{17} and C_{18} | 500pF silvered mica | Hunts |
| C_{19} | 0.02 μ F paper | " |
| C_{20} | 50 μ F electrolytic, 12V working | " |
| C_{21} | 0.01 μ F paper | " |
| C_{22} | 8 μ F electrolytic, 450V working | " |
| C_{23} | 0.1 μ F paper | " |
| C_{24} | 8 μ F electrolytic, 450V working | " |
| C_{25} | 50 μ F electrolytic, 12V working | " |
| C_{26} | 0.15 μ F paper | " |
| C_{27} | 0.001 μ F mica, moulded | " |
| C_{28} | 250pF mica, moulded | " |
| C_{29} | 500pF mica moulded | " |
| C_{30} | 1,500pF mica, moulded | " |
| C_{31} | 0.05 μ F paper | " |
| C_{32} | 0.15 μ F paper | " |
| C_{33} | 1,500pF mica, moulded | " |
| C_{34} | 0.001 μ F mica, moulded | " |
| C_{35} to C_{37} | 16 μ F electrolytic, 450V working | " |

Resistors

| | | |
|----------------|-------------------------------|----------|
| R_1 to R_4 | 10k Ω pre-set | Colvern |
| R_5 | 10k Ω $\frac{1}{2}$ W | Erie |
| R_6 | 3.3k Ω $\frac{1}{2}$ W | " |
| R_7 | 220 Ω $\frac{1}{2}$ W | " |
| R_8 | 0.1M Ω $\frac{1}{2}$ W | " |
| R_9 | 3.3k Ω $\frac{1}{2}$ W | " |
| R_{10} | 470 Ω $\frac{1}{2}$ W | " |
| R_{11} | 50k Ω $\frac{1}{2}$ W | " |
| R_{12} | 220k Ω $\frac{1}{2}$ W | " |
| R_{13} | 220k Ω $\frac{1}{2}$ W | " |
| R_{14} | 22k Ω $\frac{1}{2}$ W | " |
| R_{15} | 1M Ω $\frac{1}{2}$ W | " |
| R_{16} | 220k Ω $\frac{1}{2}$ W | " |
| R_{17} | 1.8k Ω $\frac{1}{2}$ W | " |
| R_{18} | 1M Ω variable, tapered | Reliance |

| | | |
|----------|--------------------------------|------|
| R_{19} | 47k Ω $\frac{1}{2}$ W | Erie |
| R_{20} | 1.2M Ω $\frac{1}{2}$ W | " |
| R_{21} | 22k Ω $\frac{1}{2}$ W | " |
| R_{22} | 10k Ω $\frac{1}{2}$ W | " |
| R_{23} | 330 Ω $\frac{1}{2}$ W | " |
| R_{24} | 0.15M Ω $\frac{1}{2}$ W | " |
| R_{25} | 10k Ω $\frac{1}{2}$ W | " |
| R_{26} | 1M Ω $\frac{1}{2}$ W | " |

Valves

| | | |
|-------|------|---------|
| V_1 | EF92 | Mullard |
| V_2 | EF91 | " |
| V_3 | EF91 | " |
| V_4 | EF92 | " |
| V_5 | EF91 | " |
| V_6 | 5Z4 | Cossor |

Coils and Chokes

| | | |
|-----------------------|----------------|--------------|
| L_1 to L_3 | Range 2 blue | Denco Maxi Q |
| L_4 | Range 1 blue | " |
| L_5 to L_7 | Range 2 yellow | " |
| L_9 to L_{11} | | |
| L_8 and L_{12} | Range 1 yellow | " |
| L_{13} and L_{14} | 20H at 60mA | Woden |

Switches

| | | |
|-----------------------|-----------------------------|--------|
| S_1 to S_8 | 5 wafers, each 2-pole 5-way | N.S.F. |
| S_9 | 1 wafer, 2-pole 5-way | " |
| S_{10} and S_{11} | | |

Mains Transformer

| | | |
|--------------|---------------------|-------|
| Primary: | 10-0-200-220-240V | Woden |
| Secondaries: | 350-0-350V at 80 mA | |
| | 5V at 2A | |
| | 6.3V at 3A | |

Chassis Fittings

| | |
|---------------------------------|-------------------|
| 2 telephone jacks, 2-point | Igranic or Bulgin |
| Mains connector | Bulgin |
| Twin fuseholder | " |
| 1 octal valveholder | " |
| 5 B7G valveholders with cans | Belling & Lee |
| 2 telephone-type plugs, 2-point | Bulgin |
| Aerial socket and plug | Belling & Lee |


C₃₂-C₃₄—not, for instance, C₃₂ and C₃₃ together. These switches are often fitted with earthing strips which short-circuit some of the contacts not in use. If these are fitted they must be removed, as they upset the tone-control connections.

To assemble the unit the spacer tubes on the screws holding the switch wafers to the click-plates are removed, sawn in half and replaced with the switch wafer between the halves. The ends of the screws in question are then passed through holes in a suitable tag-board and the nuts replaced. The components are mounted on the tag-board and wired to the switches and the whole is then fixed to the main chassis by the panel-fixing nuts. As the switches are rigidly fixed to each other by the tag-board, the locating tags provided to prevent rotation on the panel need not be used. C₂₆ and R₂₆ are also mounted on the tag-board, so the only connections to this unit are from the anode of V₅ and from the output jack. This latter lead should be screened and the screening joined to the jack sleeve terminal and earthed at one point only. The earth connection on the unit is taken to one of the screws holding the switches to the tag-board.


The r.f. coils are tuned by dust-iron cores, suitable fixed capacitors being chosen to bring the desired frequency within the range of adjustment. The whole range can be covered by preferred values of capacitance with a selection tolerance of $\pm 10\%$. The two curves for the medium and long wavebands show frequency versus capacitance for the upper and lower limits of inductance and give preferred values of capacitance assuming 40pF strays. In the present case the values selected are 47pF for the 1,214-kc/s Light Programme (C₁-C₅-C₉), 82pF for the 908-kc/s Home Service (C₂-C₆-C₁₀), 220pF for the 647-kc/s Third Programme (C₃-C₇-C₁₁) and 220pF for the 200-kc/s long-wave Light Pro-


gramme (C₄-C₈-C₁₂), and have all been found to tune in the station without difficulty.

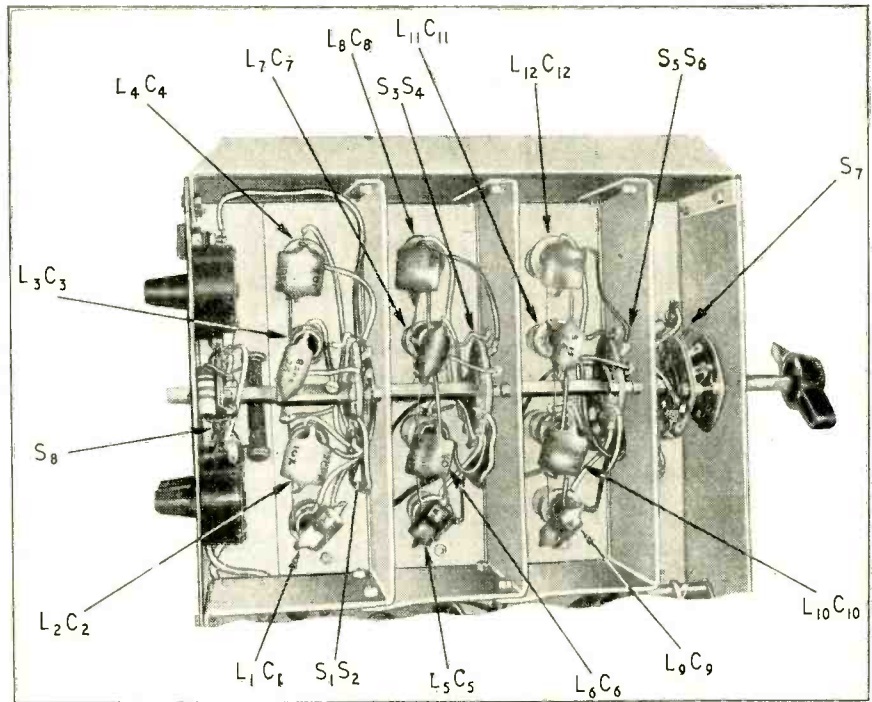The three circuits for each station are normally tuned for maximum signal, but the sensitivity is such



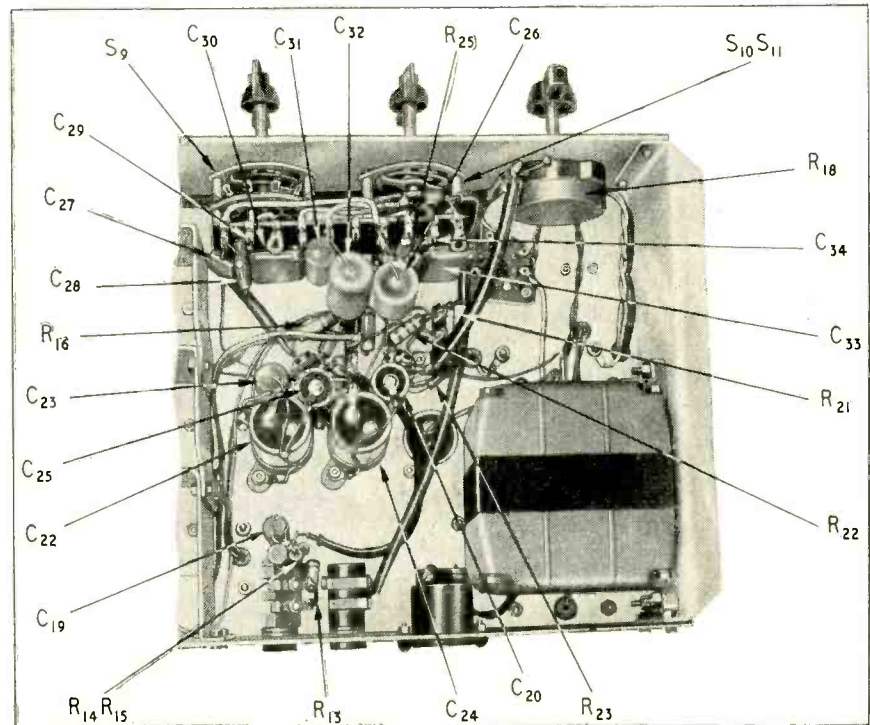Underside of the r.f. end (above) and a.f. end (below) of the chassis



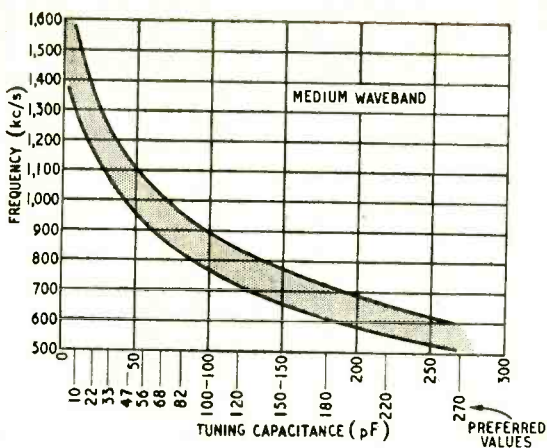


These two curves enable preferred-value capacitors to be selected for tuning on the medium waveband. They represent the upper and lower limits of inductance of the adjustable tuning coils, so the shaded area between indicates the range of adjustment.

that the improved bandwidth obtained by staggering-tuning can be taken advantage of, provided that interference from neighbouring stations is not troublesome. It may, in fact, be found that the circuits cannot be aligned exactly without trouble from instability, particularly where the tuning capacitors are small and there is a very high circuit Q. In the first stage this can be overcome by adjustment of the appropriate pre-set resistor in the cathode circuit of V_{11} , but if the second stage is unstable it may be necessary to increase the value of R_{10} . It must be pointed out that small changes in layout have a very considerable effect on stability and each separate case will need different treatment.

Adjusting the Coils

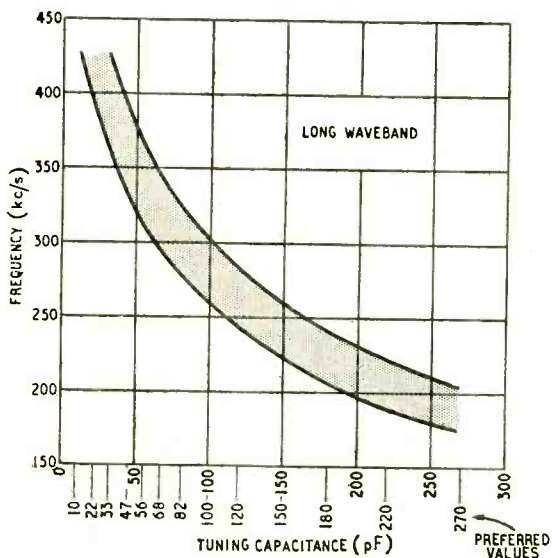If stations other than those mentioned above are better received in a particular locality, the capacitance values for them can be selected from the curves—



Curves for tuning by preferred values on the long waveband.

and of course there is no reason why two stations should not be on the long waveband and two on the medium; alternatively the long waveband can be cut out altogether and all four stations selected from the medium waveband.

Incidentally, the coils as supplied do not have any means of locking after adjustment and there is a danger of the cores shifting and so upsetting the tuning. This can be avoided by securing the adjusting screw of each coil with a 4 B.A. brass lock-nut. The best way to do it is to slide the nut on to the shaft of a thin screwdriver, use this for adjusting the coil, then, holding the adjusting screw steady with the screwdriver, run on the nut and finally tighten it against the coil-fixing column. This method ensures that the tuning is not disturbed when the lock-nut is tightened.

A separate power-pack is included in this unit to avoid the difficulties which might arise in obtaining h.t. and l.t. from the amplifier with which it is to be used. The mains transformer has a 350-0-350-V winding because, although such a high voltage is not really necessary, its use is no disadvantage and it enables a standard transformer to be used. Two stages of smoothing are incorporated to keep hum to a minimum. No mains switch is fitted as it is assumed that the supply to the whole equipment will be controlled by one switch.

COMPONENT SPECIFICATIONS

TWO new specifications covering air and mica dielectric pre-set capacitors have recently been issued by the Radio Industry Council. In common with other specifications of this kind the components are classified into three main groups, red, yellow and green respectively, which indicate the climatic conditions, in this descending order of severity, for which they are suitable. The specified tests are also based on this colour classification.

Sections 1 and 2 only are available covering performance requirements and production tests for all three groups. Section 3 of each dealing with types, values and sizes will follow later.

Specification RIC/143 deals with variable pre-set mica dielectric capacitors and covers single- and multiple-plate types. It is specified that the single-plate type shall be variable between limits of 2-15 pF, 3-30 pF or 4-40 pF. Actual values of the multiple-plate type will be defined in section 3 when issued, but the largest capacitance has been fixed at 3,000 pF. The maximum working voltage is 150 d.c.

Variable pre-set air dielectric capacitors are dealt with in RIC/142 and covers rotary flat-plate and concentric-vane types. Ranges, values and voltage ratings will be given in section 3 when issued.

Now available is section 3 of RIC/131 covering paper dielectric tubular capacitors. Four varieties are listed, type C, ceramic cased; type M, metal cased; type S, metal cased with one terminal connected to case and type W, wax coated.

Intended for use within the radio industry, copies of these specifications are obtainable from The Radio Industry Council, 59, Russell Square, London, W.C.1, and they cost 7s 6d for sections 1 and 2 of RIC/142 and 5s for RIC/143, sections 1 and 2. Section 3 of RIC/131 costs 2s. All prices include postage.

Continental Gramophone Records

*New Long-playing and
Variable Groove Pitch Types*



From a
Correspondent

IF an analysis were made of the amount of research into the various aspects of gramophone recording and reproduction, it would probably be found that the time devoted to the economics of record production and material cost is very much less than that of any other aspect of the art. It is only within the last few years that any serious attempt has been made to overcome the large bulk and high cost of records, notable examples being the American R.C.A. 45-r.p.m. records, giving a playing time of approximately five minutes on a 7-in disc, the American Columbia L.P. and the British Decca, 33 $\frac{1}{3}$ -r.p.m., giving playing times of over 20 minutes on a 12-in disc, against approximately five minutes for the 78-r.p.m., 12-in disc. The long-playing records have the added advantage of greater signal-to-noise ratio, but unfortunately the higher cost of the vinyl resin compared with shellac does militate against the use of low-noise unloaded resins for 10-in or 12-in, 78-r.p.m. discs.


The long-playing record at 33 $\frac{1}{3}$ r.p.m., using a 0.001-in radius stylus, has been available in this country for some time, and is now finding ready acceptance among enthusiasts. Philips of Holland have recently announced long-playing records with the same characteristics as the American Columbia L.P.s. On these records the pre-emphasis above 3 kc/s is somewhat greater than the British Decca. They are pressed from the same type vinyl resin as the American and British records.

The long-playing records just mentioned require a turntable speed other than the standard 78 r.p.m., and this considerably increases the cost of the gramophone turntable system, apart from special compensating networks for a different type of recording characteristic. One solution to the economics of the situation is provided by the new 7-in "Minigroove" records produced by Philips of Holland. These are 78-r.p.m. vinyl pressings with a fine-groove recording, requiring a 0.001-in radius stylus. They give a playing time of approximately 4 $\frac{1}{2}$ minutes, and are cut to effectively the same characteristics as the standard 78-r.p.m. records produced in this country. The diameter of the inner groove is only 3 $\frac{1}{4}$ -in, but in view of the small stylus diameter (0.001-in) and the high lateral groove speed, tracing distortion is no worse than the best 78-r.p.m. standard records. The recordings sound very clean, and the absence of background noise is a decided advantage over the shellac pressings. The recording level is about 3 to 6 db lower than standard commercial records available

in this country, but is usually sufficient to load fully the average radio receiver or amplifier. One disconcerting feature of the small-diameter inner groove is that on some record players the automatic stop mechanism trips before the end of the record, and in a few cases, where a positive stop is provided for the tone arm, the unfortunate groove gets chewed up! In spite of the high cost of the vinyl plastic, the small size of the record results in the selling price being no greater than that of a 12-in shellac record of the same playing time.

It has been contended that space is wasted on normal recording systems because the groove pitch must be such that no over-cutting occurs in the loudest passages, which occur only for a small fraction of the total playing time. One solution is to use a vari-

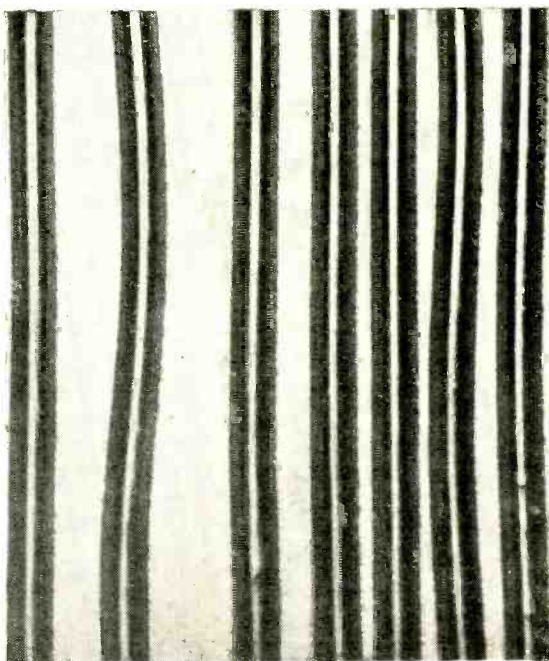Photomicrograph showing variable groove pitch in a Deutsche Grammophon Gesellschaft recording of a violoncello sonata. (Photo by C. E. Watts.)



able groove pitch, with the grooves close together on soft passages and wider apart on loud passages.

In order to obtain a variable groove pitch which is dependent on the amplitude of the recording, two requirements must be fulfilled: (a) an infinitely variable gear ratio (giving pitches between 90 and 300 grooves per inch) between the turntable and lead screw, and (b) a means of anticipating high recording amplitudes by at least one revolution of the turntable.

In the simplest system, the gear ratio is varied manually, together with the master gain control in such a manner that on crescendos and loud passages, the groove pitch is increased. This requires that the control engineer has a score, is able to read it, and has an extra knob to twiddle in anticipation of the loud passage. In an ideal automatic system, the variable gear ratio should be controlled directly from the signal current by means of a servo system with some electronic or mechanical means for anticipating the variations in signal strength. The practical interpretation of a system is to record on magnetic tape and to use two playback heads, spaced in time one revolution of the record apart, the first playback head providing the control current of the servo system operating the variable gear ratio (and thus the groove pitch), and

the second head providing the recording signal with the necessary delay.

As most of the original recording is now done on tape and then dubbed on to the disc, this system is not really so complicated as may seem at first sight, the only extra apparatus required on the tape reproducer being one playback head together with the necessary amplifier and servo system.

Two Continental series, "Deutsche Grammophon Gesellschaft" and "Archiv," are being recorded with variable groove pitch, and a playing time of $7\frac{1}{2}$ minutes is obtained for a dynamic range of 36 db with 12-in discs. These records have some pre-emphasis approaching the Decca "ffrr" characteristic. They are pressed on shellac, which unfortunately is not always of the high quality to which we are accustomed in this country, and some of the pressings exhibit a rather high surface noise.

One useful feature with the "Archiv" discs is the information sheet which is supplied with each record, giving all details of the particular record. It is a procedure which, if extended to give technical details, such as pre-emphasis, top "roll-off," dynamic range, maximum level, etc., can be commended to the British record companies.

LONG-DISTANCE RADIO JUBILEE

FIFTY years ago this month the possibility of long-distance radio communication was proved by the success achieved by Marconi in the first transatlantic wireless transmission. It was on December 12th, 1901, that young Guglielmo Marconi, then only 25 years old, received in Newfoundland, with the simplest possible apparatus, single-letter signals transmitted from Poldhu, Cornwall.

The story is so well known that it hardly needs repeating—the building of the 12-kW station at Poldhu (many times more powerful than that used in earlier experiments), the wrecking of the transmitter aerial by a gale shortly before the experiment, the kite receiving aerial at Signal Hill, Newfoundland, and the reception of the prearranged signal, the letter "S" in morse.

Marchese Luigi Solari, who is believed to be the only survivor of Marconi's original band of collaborators, has sent us some interesting reminiscences of the


experiments, during which he was present at Poldhu. It was, in fact, a Solari mercury coherer, connected in series with a telephone and the aerial, which was used by Marconi for the reception of the signals.



It has often been asked why the letter "S" was used as a test signal for the experiments instead of the letter "V," which is normally employed as a test signal. According to the Marchese, the consecutive dots were more readily distinguishable from the atmospherics, which produced sounds "like that of long dashes."

Within a few weeks of Marconi's initial success he received on board the American liner *Philadelphia* complete messages transmitted from Poldhu at a distance of 1,551 miles and of single letters up to 2,099 miles. He was then on his way to Canada to erect the Marconi Wireless Telegraph Co.'s station at Glace Bay, which was used for the first commercial transatlantic service. Incidentally, Marconi's experi-

ments at Signal Hill came to an abrupt end when, to quote from his article in *Wireless World* on the 25th anniversary of his successful experiments, "I was notified on behalf of the Anglo-American Telegraph Company that, as they held a charter giving them the exclusive right to construct and operate stations for telegraphic communication between Newfoundland and places outside the Colony, the work upon which I was engaged was a violation of their rights."

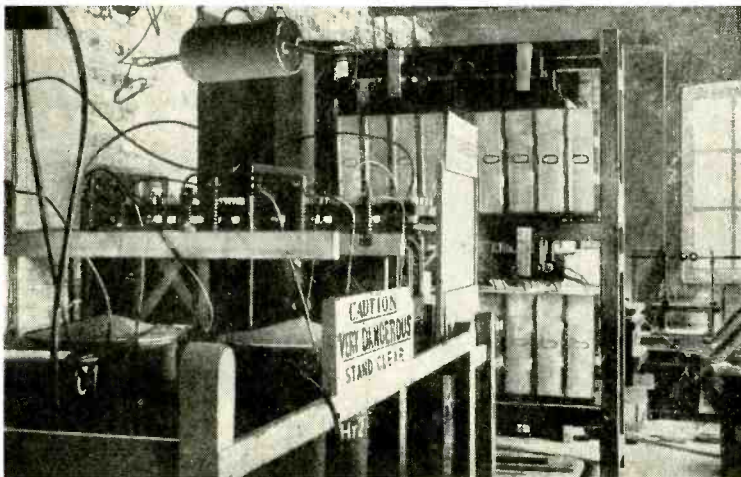POLDHU. Some of the early apparatus at the Marconi station at Poldhu. On the extreme left are the transformers; the banks of condensers are carried in metal containers in the wooden rack and the spark gap consisting of two steel spheres mounted on insulating rods is visible on the right.



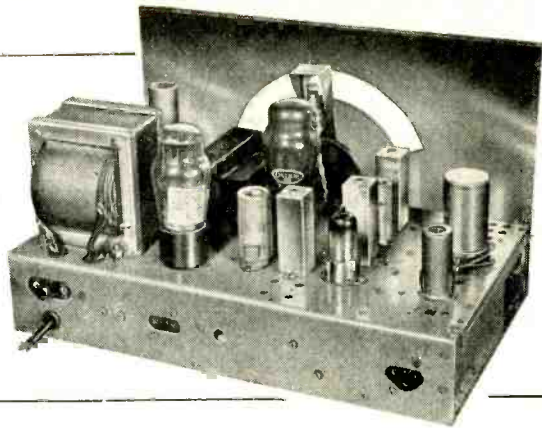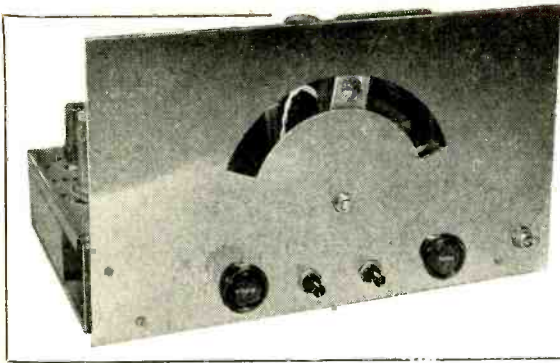

DESIGN FOR AN

(Concluded from page 444 of previous issue)

F.M. Receiver

By
J. G. SPENCER*

2.— Circuit Alignment and Performance Specification

A DESCRIPTION of the receiver and details of the coils and transformers having been given in the first part of this article, attention can now be turned to the important subject of aligning the various circuits.

Alignment of the I.F. Amplifier.—The nominal intermediate frequency is 8.2 Mc/s but this is not critical and any value between 8.0 Mc/s and 8.5 Mc/s is satisfactory. The two i.f. transformers are adjusted for critical coupling and this should be obtained with the coil spacing given in the winding data. It is possible that with slight differences in chassis wiring the stray external coupling capacitances will differ and it is worth checking the response curve of each transformer to ensure that the coupling is correct.

For the i.f. output meter the most suitable device is a microammeter connected in series with R_{15} at its earthy end, but if no meter sufficiently sensitive to give an accurately readable deflection on 10 μ A is available, the output valve can be pressed into service as a d.c. valve voltmeter. To do this, remove V_5 and connect the grid of V_6 to the junction of R_{13} and R_{14} . The i.f. output can then be measured with a voltmeter connected across R_{29} .

When using V_6 in this way it is advisable to keep the input voltage within the range of ± 4 V, in order that the cathode voltage shall be linearly proportional to the input. A change of grid voltage of 4 V gives a change of cathode voltage of approximately 1.8 V.

Disconnect C_7 at its junction with R_5 and connect a 1,000- Ω resistor between the control grid of V_2 and earth. Connect the output of the signal generator across this resistor.


Set the signal generator to a frequency of 8.2 Mc/s and adjust the cores of L_6 , L_7 , L_8 and L_9 for maximum output.

Then connect a 2.2-k Ω resistor across L_6 and a similar resistor across L_7 , this will damp these circuits to such an extent that they are substantially flat over the pass band, increase the signal generator output until a readable output-meter deflection is obtained

and plot the response curve of the second i.f. transformer.

If the coupling between L_8 and L_9 is correct the curve of Fig. 4(A) will be obtained, substantially flat topped and 3 db down at approximately ± 120 kc/s. If the coupling is too great the curve will be wider and will show two "humps," conversely if the coupling is too weak the curve will be narrower. If any adjustment of the spacing between L_8 and L_9 is necessary

Fig. 4. I.F. response curves centered on 8.2 Mc/s. Curve A is response of one transformer (L_8 , L_9); curve B is overall response when correctly aligned.

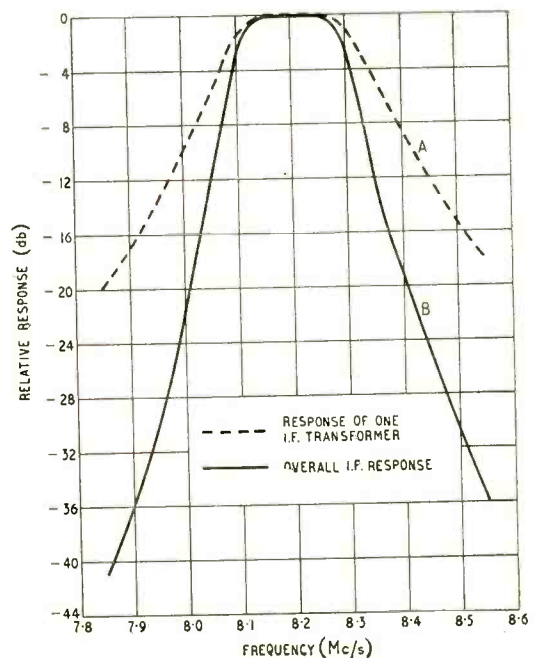

*Research Department, B.B.C.

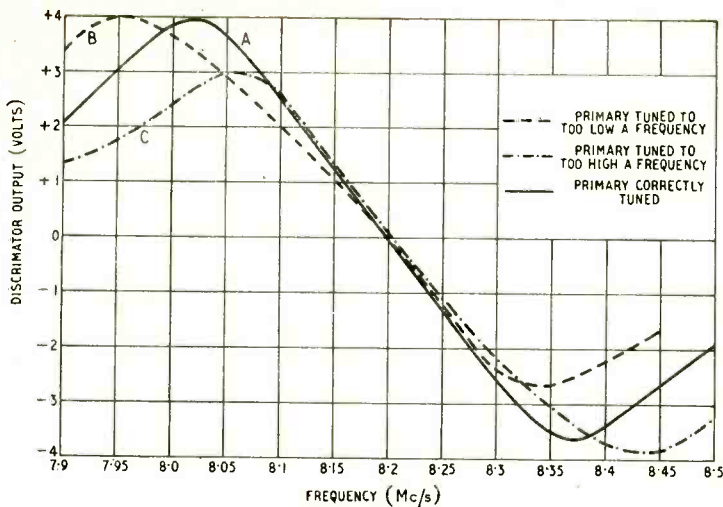


Fig. 5. Form of curves produced by various adjustments of discriminator transformer (L_{10} , L_{11}). Curve A shows correct tuning, Curves B and C mistuning of secondary circuit.

both circuits should be retuned after such adjustment. This process should be repeated for the first i.f. transformer with L_8 and L_9 each damped with 2.2 k Ω .

For this part of the alignment the d.c. output from the grid of V_4 should not be more than figure 1 V to avoid overloading V_3 . The response curve obtained should be similar to that for the second i.f. transformer.

Finally, remove the damping resistors and plot the i.f. overall response curve. This should be ± 100 kc/s wide at the 3-db down points as shown in Fig.4(B). *The Discriminator.*—(1) Disconnect C_{26} from L_0 and connect signal generator output between the free side of C_{26} and earth. Set signal generator to 8.2 Mc/s and output to figure 1 V.

(2) Disconnect h.t. supply to V_5 and short circuit R_{26} .

(3) Connect voltmeter across R_{29} .

(4) Connect junction of R_{21} and R_{22} to grid of V_6 through a 500-k Ω resistor.

(5) Adjust trimmer of L_{10} for maximum downwards deflection of voltmeter.

(6) Remove 500-k Ω resistor from junction of R_{21} and R_{22} and connect to junction of R_{21} and R_{23} .

(7) Adjust trimmer of L_{11} for zero output (i.e., earthing the grid of V_6 gives no change of voltmeter reading).

(8) Repeat steps 4 to 7 once more.

The discriminator response curve of output against frequency should now be plotted and if the alignment is correct it will be similar to that shown in Fig. 5(A) linear over a range of ± 120 kc/s and with the positive and negative peaks of approximately equal amplitudes situated ± 170 kc/s from the centre zero. If the bandwidth is narrower than this the coupling between L_{10} and L_{11} should be increased and vice versa.

The effect of primary mistuning is to shift both peaks of the curve in the same direction, so that they are unequally spaced from the zero point, and also to make their amplitudes unequal. This effect is shown in Fig.5(B) and (C). Mistuning of the secondary will shift the frequency of zero output.

R.F. and oscillator circuits.—To check that the oscillator is functioning insert a milliammeter between the low potential end of R_8 and the cathode of V_2 and measure the oscillator grid current. This should be of the order of 40 μ A. If no grid current is observed check that L_4 is connected in the correct sense and

reverse the connections if necessary. A signal generator covering the 90-Mc/s band will facilitate the r.f. alignment but it is not essential as almost any generator whose oscillator fundamental frequency goes up to 10 Mc/s or above will generate harmonics in the required range and of sufficient amplitude for the purpose.

First set C_{17} to mid scale and C_{18} to minimum capacity, adjust the cores of L_2 and L_3 to the middle of their travel and switch the receiver to a.m.

If the harmonic method is used set the signal generator to the highest available integral sub-multiple of 91.2 Mc/s, switch on modulation and adjust the

oscillator trimmer, C_{18} , until the signal is heard. Then adjust L_2 and L_3 for maximum output, reducing the signal generator output if necessary to prevent the action of a.g.c. from masking the effect of the tuning adjustments.

If a low frequency fundamental is being used it may be possible to align the receiver on the wrong harmonic and to check this rotate the signal generator tuning until the next harmonic response is heard. Note the frequencies at which these two adjacent responses occur. Let these two frequencies be f_1 and f_2 and the frequency to which the receiver is tuned be f_0 , then

$$f_0 = \frac{f_1 \times f_2}{f_1 - f_2}$$

Two points must be borne in mind when aligning on harmonics. In the first place only the fundamental ranges of the signal generator should be used. It is quite common practice for the highest range to be on a harmonic of the fundamental oscillator frequency and if this is employed the formula given will not hold good.

Secondly, care must be taken to avoid confusion from image responses in the receiver, the local oscillator frequency is below that of the carrier and the image frequency is therefore 16.4 Mc/s lower than the signal.

When the r.f. circuits are lined up there is little possibility of error since they attenuate the image frequency by some 30 to 40 db, but if the r.f. circuits are off tune in the initial stages of alignment the image response may be comparable in amplitude with that of the primary signal.

Aerials.—The B.B.C. experimental v.h.f. transmitter at Wrotham radiates f.m. and a.m. on frequencies of 91.4 Mc/s and 93.8 Mc/s respectively, both transmissions being horizontally polarised. It has a nominal service area of approximately 60 miles radius, but at these frequencies the intensity of the field at any point is greatly influenced by local topography and areas of low field strength may occur within this distance.

Generally speaking, however, a horizontal dipole, 5 ft. 1 in long, erected at roof height and broadside on to the transmitter should give an adequate input to the receiver, even at the edge of the service area. If any difficulty is experienced, the aerial should be tried in different positions, since the field strength can


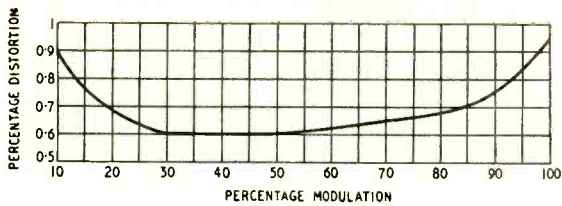


Fig. 6. Curve showing harmonic distortion with depth of modulation.

Fig. 7. Curve showing modulation frequency response when corrected for pre-emphasis.

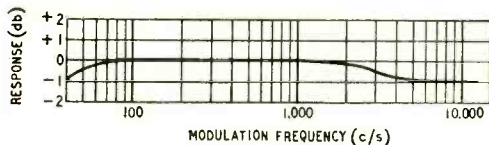

differ considerably between points only a few feet apart.

In many cases there will be no need for more than a simple indoor aerial, such as a length of twin flex connected to the receiver and opened out at the far end to form a dipole, which can be laid along the picture rail or on the floor.

At a receiving site rather more than 20 miles from the transmitter the receiver has been found to work quite satisfactorily with a length of wire 30 in long connected to one aerial socket and hanging vertically downwards. In view of the complex standing wave pattern set up inside a building at v.h.f. it is even more important with indoor aerials than with those erected in the open to try the effect of varying the position of the aerial.

Test Instruments.—The essential test instruments required for aligning the receiver are a d.c. voltmeter reading 0-10 volts and a signal generator covering the intermediate frequency of 8.2 Mc/s.

The absolute frequency accuracy of the latter instrument is not important but it must be capable of being adjusted in small increments of frequency, not more than 50 kc/s, with a fair degree of accuracy. This facility is essential for taking response curves of the i.f. transformers and discriminator.

A microammeter with a full-scale deflection of the order of 100 μ A and a signal generator covering the 90-Mc/s band are of great assistance if available but

they are not essential provided harmonics in this band can be obtained from the signal generator used for the i.f. alignment.

Performance Specification

The following results of performance tests made on the prototype receiver will be of interest as a final check on performance. All measurements of signal-to-unwanted-response ratio were made with a square-law meter preceded by an aural weighting network, a method which has been found to give results in close agreement with subjective assessments†.

Absolute sensitivity.—Carrier input required with 40 per cent modulation to produce 50 mW output = 19 μ V.

Maximum deviation sensitivity for 10 per cent harmonic distortion.—Carrier input required to produce 10 per cent distortion with 100 per cent modulation at 400 c/s and with 50 mW output = 60 μ V.

Sensitivity for 40 db signal to noise ratio.—Carrier input required with 40 per cent modulation to produce 40 db output signal to noise ratio = 40 μ V.

The three foregoing sensitivity measurements were all made at the mid-band signal frequency and will be some 6 db worse at the limits of the tuning range due to the drop in response of the r.f. circuits.

Signal to hum ratio.—Modulation depth required to produce 40 db signal to hum ratio with a carrier input of 10 mV = 0.9 per cent.

Harmonic distortion, variation with modulation depth.—See curve Fig. 6. For this test the gain control setting is fixed at a level which gives 50 mW output with 40 per cent modulation.


Maximum output power for 10 per cent harmonic distortion.—Carrier modulation 100 per cent at 400 c/s = 2.0 watts.

Modulation frequency characteristics.—(Output level of 50 mW.) See curve Fig. 7.

Adjacent channel suppression ratio.—Ratio of amplitude of interfering carrier, modulated 40 per cent, situated on the adjacent channel to that to which the receiver is tuned, i.e. spaced by ± 200 kc/s which produces a signal to interference ratio of 40 db to the wanted carrier, latter modulated 40 per cent: — + 200 kc/s = - 10 db; - 200 kc/s = + 3.5 db.


Second and third channel suppression ratio.—As

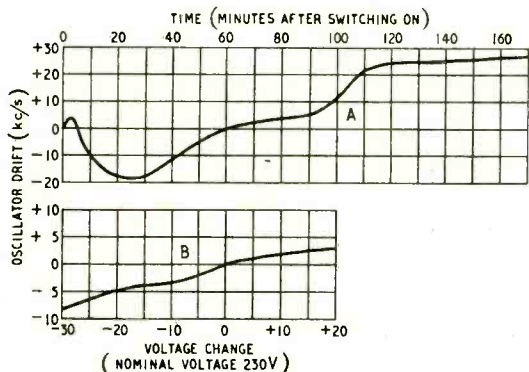† "Electrical Noise"; Maurice, Newell and Spencer. *Wireless Engineer*, January, 1950.



Left: Fig. 8. Local oscillator frequency stability; curve A initial drift with temperature compensation; curve B drift due to mains fluctuations.

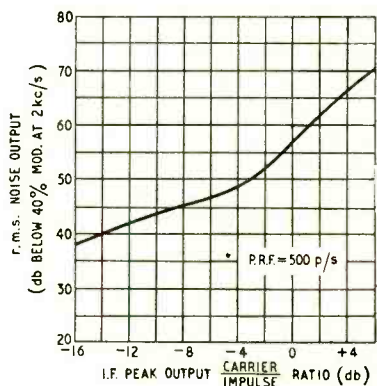Right: Fig. 9. Impulse interference performance curve.



above but with the interfering carrier spaced ± 400 kc/s and ± 600 kc/s from the wanted carrier:—

- + 400 kc/s = + 14.5 db
- 400 kc/s = + 23.5 db
- + 600 kc/s > + 30 db
- 600 kc/s > + 30 db

Image channel suppression ratio.—As above but with interfering carrier at image frequency = + 13 db.

Intermediate frequency suppression ratio.— as above but with interfering carrier at i.f. = + 29.4 db.

Spurious frequency suppression ratio.—As above but with interfering carrier at any frequency likely to produce a spurious response, e.g. by beating with local oscillator harmonics etc. Two spurious responses were found, at signal frequency plus and minus intermediate frequency respectively and both required

the interfering carrier to be + 22 db relative to the wanted carrier.

Local oscillator drift.—See curve (A) Fig. 8.

Dependence of local oscillator frequency upon mains voltage.—See Curve (B) Fig. 8.

Co-channel suppression ratio.—As for adjacent channel but with interfering carrier adjusted to within ± 1 kc/s of the wanted carrier = - 11 db.

Amplitude modulation suppression.—Ratio of output due to f.m. to output due to a.m. when the receiver is tuned to a carrier simultaneously amplitude and frequency modulated to depths of 40 per cent = 30 db.

Impulsive interference performance.—See curve Fig. 9 in which the output signal-to-noise ratio is plotted against the peak impulse to carrier ratio at the output of the i.f. amplifier.

SHORT-WAVE CONDITIONS

October in Retrospect : Forecast for December

By T. W. BENNINGTON*

DURING October the average maximum usable frequencies for these latitudes increased considerably during the daytime, and decreased considerably by night, which variations were in accordance with the normal seasonal trend.

Daytime working frequencies were fairly high, 22 Mc/s being consistently usable over east/west paths under undisturbed conditions. On very few occasions, however,

were higher frequencies than this usable. Over north/south paths frequencies up to 26 Mc/s were usable during undisturbed days. At night 7 and 6 Mc/s were generally the highest usable frequencies after midnight.

There was a further small decrease in the amount of sporadic E recorded.

There was a considerable decrease in the average sunspot activity during the month. Since the big decrease in the general level of sunspot activity which occurred in the autumn and winter of 1950, the decrease has been much more gradual, with the result that the level of activity is not very greatly lower than it was at this time last year.


Though less disturbed than September, October was yet a very disturbed month. The ionospheric storms were accompanied by severe magnetic storms and by auroral activity in this country, and "great magnetic storms" were recorded on 17th and 28th. The most disturbed periods for short-wave conditions were 8th-11th, 13th-14th, 16th-23rd, and 28th-29th. No Dellinger fadeouts have, as yet, been reported.

Forecast: During December a small decrease in the daytime m.u.f.'s for these latitudes is to be expected, as compared with those for November. At night there should be a further considerable decrease in m.u.f.'s, and perhaps the lowest values for the coming winter season will occur during the month.

Working frequencies should, therefore, be reasonably high during the peak day period and very low by night, whilst over a considerable part of the daily period only medium-high frequencies will be usable. On east/west circuits frequencies up to about 20 Mc/s should be regularly usable, and those a few megacycles higher sometimes so. At night low frequencies will be necessary, and after midnight even 6 Mc/s may be often too high. Over north/south circuits frequencies up to 26 Mc/s should be regularly usable during the daytime, and 7 Mc/s be about the highest usable frequency after midnight.

Sporadic E capable of propagating very high frequencies is unlikely to be prevalent, and medium-distance communication on high frequencies is, therefore, unlikely to occur.

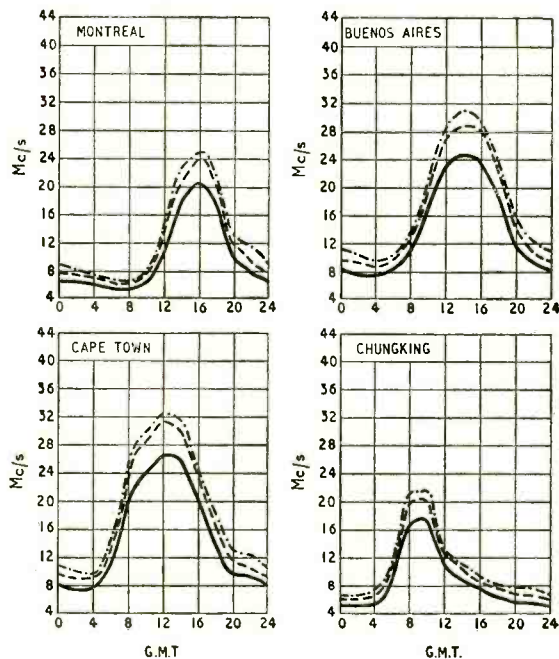The curves indicate the highest frequencies likely to be usable over four long-distance circuits from this country during the month.



— FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE ON ALL UNDISTURBED DAYS
 - - - PREDICTED AVERAGE MAXIMUM USABLE FREQUENCY
 - · - · FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE FOR 25% OF THE TOTAL TIME

*Engineering Division, B.B.C.

Radio for Taxis


Ambitious Scheme for the London Area

THE use of radio-telephones in private hire vehicles is not a new departure, neither is its extension to taxicabs, but installations of this kind can often provide some interesting technical problems. A case in point is the somewhat ambitious scheme launched recently for fitting a large number of London's taxicabs with two-way v.h.f. radio-telephones. An initial target of 1,000 cabs is visualized, with a single radio centre handling all line and radio traffic. The scheme is well under way and taxis participating in it can be identified by the short vertical aerial, little more than a foot in length, mounted well forward on the roof of the cab.

Radio equipment for this scheme is supplied by Pye Telecommunications, but it was not necessary to design equipment especially for the purpose as their existing v.h.f. mobile sets Type PTC115, with a few modifications, meet the requirements of the taxis and the Type PTC704 that of the radio centre.

These two equipments are for operation in the band 100-184 Mc/s, the actual frequencies employed being 172.8 and 182.8 Mc/s. Although two frequencies are available a duplex system is not used since all messages are brief.

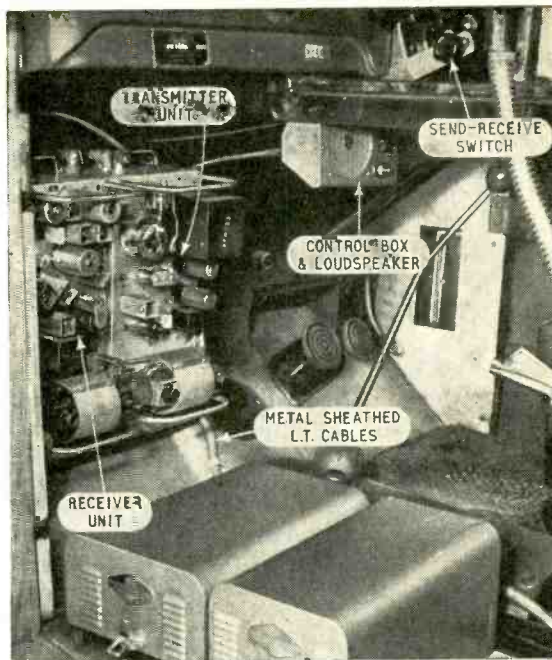Despite the use of such a high carrier frequency no difficulty has been experienced from attenuation in the vast built-up area of London and although the scheme has now been in operation for several months not a single blank area has so far been encountered. One transmitting site only is used, but it is located on very high ground on the northern outskirts of the metropolis.



Early stage in fitting Pye Type PTC115 v.h.f. radio in one of London's taxis. Covers are not yet in place and the partition between driver and luggage space has not yet been replaced. Below: Experimental corner reflector type aerial under test for standing wave ratio on feeder. A slotted section of feeder is used.

Amplitude modulation is employed and the r.f. power output from the fixed and mobile equipments is approximately 12 watts. This gives a good solid signal anywhere in the London area and quite sufficient to override all traffic noises in the taxis, which have to be fitted with loudspeakers in order that the driver's attention should not be distracted from his primary function of driving, which might well be the case if a calling device in the form of a buzzer or lamp were used and the driver required to search for and pick up a hand telephone set.

This requirement gave rise to two other problems; one was how to operate the send-receive switch without removing the hand from the driving wheel, and the other the positioning of the microphone. These two are really a single problem as in most mobile equipments using hand telephone sets the send-receive switch is embodied in the handgrip when a simplex system is used.

Speaking into the microphone from any distance is quite impractical on the road as the voice will more often than not be drowned by the noise of passing traffic. A little ingenuity was required to avoid the necessity to pick up the microphone and at the same time have it sufficiently close to the mouth.

In the case of these radio-equipped taxis the microphone is carried by a horizontal swivelling arm attached to a vertical rod mounted on the glass



partition which divides the drivers' compartment from the luggage space. This arm can be moved up or down and clamped in any position and also swung to or away from the glass partition. In the operating position it is adjacent to the driver's mouth and slightly to his left. He can speak into it without actually turning his head and taking his eyes off the road.

The difficulty of the change-over switch was overcome by mounting a press-to-talk switch on an arm extending out from the instrument panel in the driver's compartment and terminating just below the rim of the steering wheel on the left-hand side. The knob of the switch projects outward, that is, to the left, and by extending the first two fingers of the left hand it is quite easy to operate the switch without relaxing the grip on the wheel.

As the equipment is remotely controlled, it is possible to accommodate the bulk of it anywhere in the vehicle. The only items that must be convenient to the driver are the remote-control box (with built-in speaker), send-receive switch and microphone.

The taxis we saw fitted were Austins and the radio transmitting and receiving units are mounted in a small recess in the front part of the luggage compartment. Owing to its awkward position and shape it is not very useful for luggage, so that fitting the radio here leads to no worth-while loss of luggage capacity. The space is just large enough to take the two radio units and their anti-shock cradle mounted on end, as shown in one of the illustrations, and it is then enclosed by a stout metal panel to protect the sets from possible damage. This had not been fitted when the photographs were taken, neither had the partition between the driver's cab and luggage compartment been reinstated as it was desired to show as much of the apparatus as possible. For example, the control unit is included and so is the arm carrying the send-receive switch, also the armoured cable connecting the radio units to the battery, which in these taxis is accommodated below the driver's seat.

With a 12-volt supply the receiver consumption is

about 4.5 A; current rises to 6 A when the transmitter valve heaters are switched on; that is to say, when the whole equipment is in the "stand-by" condition and ready for immediate use. With the transmitter in operation the consumption rises to 14 A, but this latter demand is for only very short periods. Nevertheless, a larger-capacity battery than usual is desirable and so is a dynamo giving a somewhat greater charging rate.

The receiver of the PTC115 is a double-super-heterodyne having 11 valves in all. They are miniature types, and so the sets can be kept reasonably small; the two units together measure 16½ in wide, 15½ in deep and 8 in high, and the total weight is 40 lb. The valve arrangement of the receiver is, briefly: one r.f. stage; first mixer with local oscillations fed from the frequency multiplier of a crystal oscillator; second mixer with local oscillations fed in from the crystal oscillator stage; two i.f. stages with eight tuned circuits at about 3 Mc/s (2nd i.f.); signal detector and a.g.c.; noise limiter, a.f. and output stages. Grid bias for all valves is taken from a resistor connected in the h.t. negative lead in preference to separate cathode resistors. This is a widely used system in commercial radio equipments, and also in many Service sets, and no doubt the saving effected in cathode resistors and capacitors, especially where a fairly large number of valves is used, accounts for its popularity.

A signal to noise-operated muting circuit with three valves and a relay, for suppression of all receiver noise in the absence of a carrier, can be included in the receiver if required.


In the companion transmitter there are seven valves, in this case a mixture of octal, miniature and special types. The first stage is a crystal oscillator and combined frequency doubler, the second is a frequency tripler, the third (two valves) a push-push (anodes parallel, grids push-pull) doubler and the fourth a push-pull r.f. power amplifier, the valve used here being a double tetrode, the American type 832. The remaining two valves are a pair of 6V6s operated as a push-pull modulator with the microphone output applied to their grids via a step-up transformer. There is no intermediate amplifier.

High tension for both units is supplied by small rotary generators, one machine being used for the receiver and part of the transmitter, and the other for the remaining valves in the transmitter.

A point of interest regarding the installation in the taxi is that all permanent wiring for the radio, such as l.t., microphone input, loudspeaker output, and relay circuits, terminates at the anti-shock cradle. The "take-off" from the cradle to the transmitter and receiver units is by means of self-aligning plugs and sockets, so that either unit can be easily removed for replacement in the event of a fault, or for a routine check-up in the maintenance department without disturbing a single wire with the exception of the aerial cable.

The fixed station (Pye Type PTC704) is entirely automatic in operation and is controlled over Post Office lines from a radio centre near King's Cross. Transmitter and receiver are duplicated and should a fault develop the stand-by set comes into operation immediately. As a further insurance against breakdown, a stand-by set is installed at the radio centre with an aerial on a 100-ft mast.

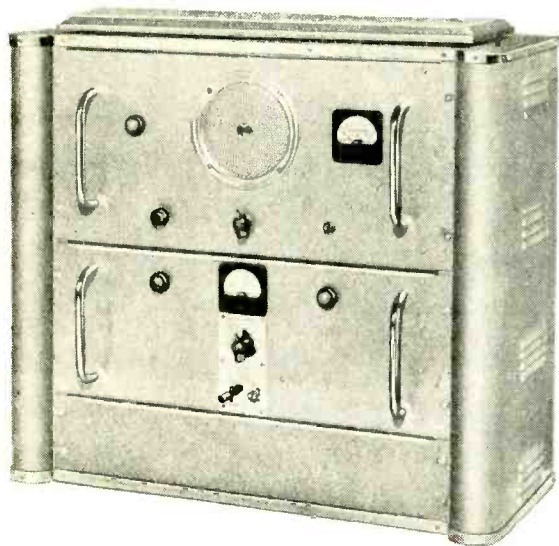Circuit layouts are very similar to those of the respective mobile equipments, with the exception that as the whole station is operated from the a.c. mains,




One of the Pye Type PTC704 v.h.f. radio telephone equipments used at the fixed station and as stand-by at the radio control centre.

size, weight and consumption are not important and several refinements can be included. For example, a moving-coil microphone is used which demands a few extra audio stages in the modulator, a signal-noise operated muting circuit is permanently built-in and not optional and the receiver is capable of giving a larger audio output.

It is expected that before very long the amount of radio traffic to be handled will exceed the capacity

of a single transmitter and that some form of multiple-station operation for the London area will have to be adopted. Some investigation has been carried out along these lines and the possibilities of limited-coverage aerials are also being studied. One of the illustrations here shows a corner reflector aerial being lined up by measuring the standing wave ratio on a slotted section of transmission line. The dipole is not visible, but it is in the angle of the reflectors.

Potted Circuits

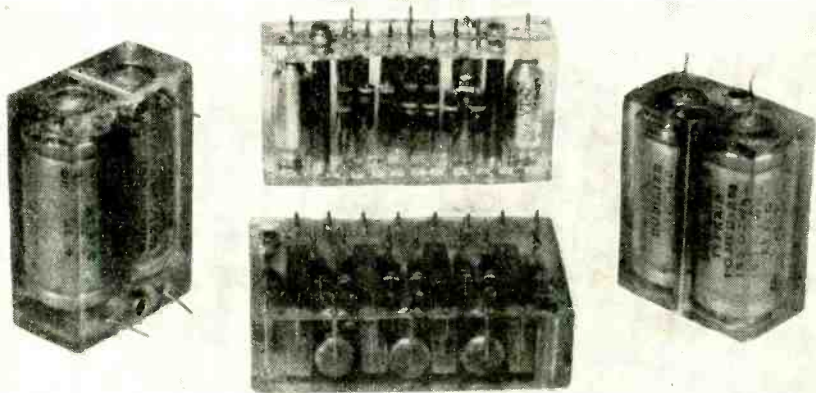

New Development in Miniaturization of Equipment

THE technique of prefabrication has been applied to a good many unlikely things, including houses and pork pies, but one would never have thought it could enter into anything so complex as the manufacture of radio circuitry. Component sub-assemblies were probably the first move in this direction, then followed printed circuits, and now another important advance has been made in the sub-assembly idea. This is the breaking-down of apparatus into groups of wired-up components and embedding them in blocks of protective resin. The process is known variously as "potting," "moulding," "packaging," or—to be really highbrow—"encapsulating," and is the outcome of work done by the Telecommunications Research Establishment of the Ministry of Supply. At the moment it is largely confined to equipment being made for the Services.

The technique has two main advantages. First, it permits quick and easy servicing in the field by unskilled men—when a fault develops the cube in question is simply taken out, thrown away and replaced by another one. Secondly, equipment can be made much smaller and lighter. Not only are tag-strips and other fixing devices unnecessary, but the components can be sealed off and protected *en bloc* in much less space than if they were treated individually—there is no need for cumbersome devices such as pressurized boxes. As an example, 38 components have been enclosed in a block measuring only $2\frac{3}{4}$ in \times $1\frac{1}{4}$ in \times $\frac{1}{8}$ in.

Potting is quite a simple affair and no special equipment is required. The components are assembled—sometimes between two plates of Perspex—and placed in a mould, then the resin is poured in and allowed

to set. The resin (known as "Marco," and made by Scott, Bader & Co.) is already in liquid form, so it does not have to be melted and there is no danger of damaging the components by heat. It does, however, require a catalyst to make it set and an accelerator to speed up the process, and these are added just before use. When finished, the blocks are proof against temperature and pressure changes, moisture, fungi and heat (they cannot be melted away). Months of immersion in water has no ill effect on them. They are also very rigid and there is little danger of anything shaking loose as a result of mechanical shock or vibration.

One difficult problem in the technique is getting rid of the heat generated internally by the components. Various methods have been tried, but the most convenient seems to be to load the resin with mica (25 per cent proportion) as this increases the thermal conductivity. The mica also improves the dielectric strength of the resin and lowers its coefficient of linear expansion which is, unfortunately, rather high. T.R.E. do not favour the American practice of encapsulating the valves as well since they only make matters worse—not to mention the extra expense when faulty units are thrown away.

In practice a single potted circuit usually accommodates three or four sub-miniature valve stages, or the equivalent. All the connections are brought out on one face so they will be easily accessible when the blocks are packed together and into the chassis. For fixing purposes a couple of tubes are embedded into the resin to take fixing screws. Incidentally, the resin can be coloured, and this provides a very convenient means of identifying the circuits.

R. F. Chokes

"They are most interesting little components . . ."

says "CATHODE RAY"

ALTHOUGH r.f. chokes are not so conspicuous as they once were, they do have their uses, so it is as well to know how they work. From the almost total absence of detailed information on them the reader might suppose that there is not much to it. He would be making a great mistake. They are most interesting little components, quite capable of exercising the inquiring mind. It is usual, for example, for the manufacturer of an r.f. choke to claim that it is "all-wave"; that is to say, that it is effective as an r.f. rejector over such a wide band as 150—20,000kc/s. Yet if the same manufacturer produces tuning coils he will probably claim for them just the opposite, that they tune very sharply! Does then the construction of a choke coil differ fundamentally from a tuning coil's, and if so how? What and why are the dead-spots one may have heard of? Why is it sometimes an advantage to put a short-wave choke (which is a low-inductance coil) in series with a long-wave one (which has a high inductance)? Could not the slight increase of inductance be obtained equally well and much more conveniently by winding a few more turns on the bigger coil? Why have so many different shapes and styles been put on the market? Which is the best type of winding? What decides the right inductance for the job? And so on.

The ideal r.f. choke would act as a complete open-circuit at all radio frequencies, and a short-circuit at zero (and perhaps audio) frequency. Since it consists of an inductive coil of wire, one might expect it to act like a tuning coil and respond more or less sharply to a particular frequency. And in fact it does do so at some frequency or other. The essential difference between a tuning coil and a r.f. choke is that the resonant frequency of the tuning coil (by itself) is higher than any of the working frequencies, whereas the resonant frequency of a r.f. choke is lower than any (or most) of the working frequencies. To appreciate what this means we have to be clear about the meaning of "resonant frequency (by itself)," which I shall denote by f_s .

Elementary theory teaches us that resonance takes place when the inductive reactance is matched by an equal capacitive reactance. So tuning coils, which are designed to provide the inductance, are used in conjunction with tuning capacitors, which are designed to provide the capacitance. Sometimes the inductance is fixed and is tuned by a variable capacitor; sometimes (especially in i.f. circuits and others for working on one fixed frequency) the capacitance is fixed and is tuned by a variable inductor—e.g., screwing an iron-core in or out. Even when there is no visible capacitor, there is inevitably a certain amount of

capacitance in parallel with the coil, due to the wiring valve electrodes, etc. Even if you were to disconnect the coil altogether, so as to remove all such added capacitances, you would still find that it would resonate at a particular frequency, detected by the sudden increase in absorption from a tunable circuit very loosely coupled to it. That particular frequency could then reasonably be called the resonant frequency of the coil by itself. Knowing the inductance of the coil, you could use the usual formula to calculate the capacitance that it needed to tune it to that frequency (f_s) and the result would be what is called the self-capacitance of the coil, C_s . So any isolated coil can be represented theoretically as in Fig. 1. For most r.f. coils C_s is between 1 and 15pF. If you like you can add a resistance in series with L to represent the resistance of the wire and any other losses at the resonant frequency.

Note that we are not entitled, merely on the strength of the foregoing experiment, to represent the coil in this way, with the same value of C_s , at any other than the resonant frequency. If we use the coil in any practical tuning circuit, there is bound to be some added capacitance due to the circuit wiring, etc., and probably a tuning capacitor as well. So the working resonant frequency or frequencies are bound to be lower than f_s . Seeing that the self-capacitance is not really a single lump, as in Fig. 1, but is distributed in and mixed up with the inductive turns of wire, it is perhaps surprising that if we make very careful measurements of added capacitances and resulting resonant frequencies we find that at frequencies below f_s the coil does continue to behave as if its self-capacitance were one practically constant lump.

We know that at the resonant frequency a parallel combination of L and any C (a rejector circuit) behaves as a high resistance; so that is an alternative to Fig. 1 as a representation. The lower the actual (series) resistance of the coil, the higher this representative resistance. No inductance or capacitance appears because they have balanced one another out. But unlike Fig. 1 this resistance representation does not hold even approximately good at other than the resonant frequency. The inductance of the coil has a reactance increasing steadily from zero at zero frequency. And the reactance of the capacitance in parallel with it decreases from infinity at zero frequency, as shown in Fig. 2. The resonant frequency is that at which the two reactances are equal. At any other frequency, either inductance or capacitance prevails. Since we are considering them in parallel, the prevailing element is the one that offers the lower reactance, because most of the current goes that way. At

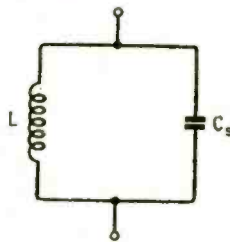


Fig. 1. Approximate theoretical equivalent of a choke or other coil, neglecting resistance.

frequencies below resonance the combination is, on balance, inductive; and at higher frequencies is capacitive. Calculating the combined reactance at various frequencies we get graphs like Fig. 3. Note that at frequencies far from resonance they are much the same as in Fig. 2. (I hope the more knowledgeable readers are not getting too bored with all this familiar stuff, but the recapitulation is just about over.)

Fig. 3, with its reactance curves disappearing into infinity, is not perhaps very helpful or convincing to the practical man; but we can express the same thing in more easily graspable terms as the capacitance which, on its own, would produce the same reactance (Fig. 4). The inductive reactance is covered by this representation; it appears as a negative capacitance. Exactly at resonance, the infinite reactance is very conveniently represented by zero capacitance.

If you have been following this you will see that at frequencies very much higher than resonance the reactance of L is so much greater than that of C that it is more or less negligible as a path, and it is fair to represent the whole outfit by the capacitance alone. The higher the frequency above resonance, the fairer. So we see that by making the inductance of a coil large enough to put the resonant frequency well below any of the working frequencies, the coil behaves at all those working frequencies as if it were nothing but C_s , which as I said is normally only a few pF, so can be relied upon to offer a pretty high impedance, and in some circuits merges into the general circuit capacitance without making much difference. At lower frequencies, down to and slightly below resonance, the equivalent capacitance is even smaller. Being negative below resonance, it begins to neutralize the circuit capacitance, and only after it has done so completely does the circuit as a whole become inductive and its reactance start to fall. So we see that over a very large frequency range, from something below resonance to an indefinite amount above, a choke coil can behave almost as an open circuit—at worst, as a slight increase in the stray capacitance. A tuning coil, on the contrary, generally has a relatively low inductance, and is shunted by a relatively large capacitance, so that except at or near the resonant frequency either L or C provides a low-reactance path.

In practice there are also r.f. losses. They are represented in Fig. 5 by R, which is preferably too large to form much of a path. C is the imaginary variable capacitance shown in Fig. 4, comprising L and C_s .

So far, then, we conclude that the aims in an r.f. choke design are to make its inductance high enough to put f_s somewhere near the low end of the working frequency range, and (notwithstanding this) to make C_s as small as possible. Minimizing C_s is not only desirable for its own sake, by raising the reactance, but also because it generally raises the resistance R. An "all-wave" choke is evidently satisfactory if f_s is about 200 kc/s; and if C_s is as low as 3pF that means L has to be over 200,000 μ H. The more successful one is in keeping C_s low, the higher L must be to keep f_s right. So the problem appears to be one of getting a high inductance with a very low self-capacitance. There are various well-known ways of promoting this object, such as winding the coil narrow and deep, or lattice-wise, and perhaps dividing it into several sections.

Judging from many of the r.f. chokes I have come

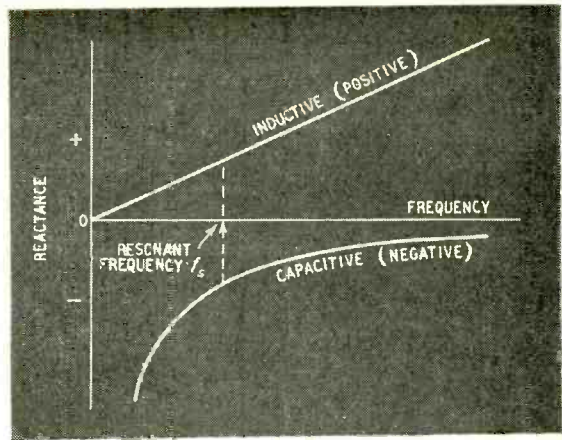


Fig. 2. Reactance graphs of inductance and capacitance such as those of a coil (Fig. 1) showing how their magnitudes are equal at one (the resonant) frequency.

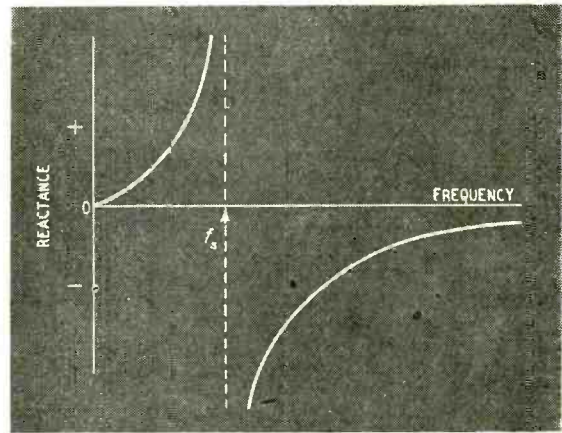


Fig. 3. Combined reactance of the two in parallel showing how it goes to infinity at the resonant frequency.

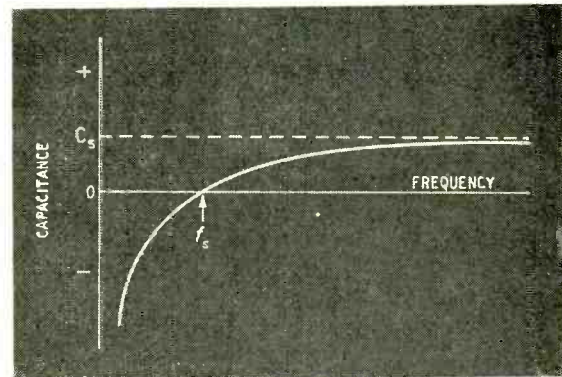


Fig. 4. If the reactance of the Fig. 1 combination were supposed to be due entirely to a capacitance, that capacitance would have to vary with frequency in the manner shown here. At the highest frequencies, it would be practically equal to C_s .

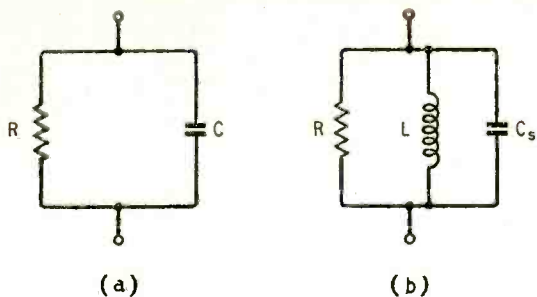


Fig. 5. The variable C in Fig. 4 can be assumed to account for the reactance of a choke (a): it represents the more or less fixed L and C_s in Fig. 1, (b). In both, the resistive component can be represented by a parallel resistance R .

across in my time, their designers must have imagined that the matter was as simple as that. Unfortunately it is not. The mistake is to assume that Fig. 1 holds good at frequencies above resonance as well as below. One way of seeing how this is unlikely to be so is to consider Fig. 4. At a given frequency, a coil large enough for its f_s to be lower is equivalent to a small capacitance—rather smaller than its C_s . At the same frequency, a coil small enough for its f_s to be higher is equivalent to an inductance. Now consider any point near one end of the winding of an r.f. choke, such as p in Fig. 6(a). It divides the choke into two unequal parts, one of which can be regarded as the large coil just mentioned and the other the small coil. Their single equivalents are therefore respectively a capacitance and an inductance, as in Fig. 6(b). It may well happen that there exists a point and a frequency such that the reactances of these two are not only opposite but equal. If so, they form a tuned acceptor circuit, which is precisely what is not wanted, for it means that the choke offers an impedance consisting of nothing more than the series r.f. resistance of the two parts.

If you test a choke over a wide range of frequency

above f_s the odds are in favour of your finding several such frequencies where the resistance R dips downwards. At the same frequencies the measured capacitance C fluctuates from the smooth and almost level curve at the right-hand end of Fig. 4. Some chokes I have tested dip as low as $10,000\ \Omega$ (from a normal level of perhaps $250,000\ \Omega$), and since a usual position for an r.f. choke is in parallel with a tuning circuit it is not hard to imagine why such occurrences are called "dead spots"! The damping effect on a high- Q circuit is of course catastrophic. If a medium-wave tuning circuit by itself had a Q at 1Mc/s of 180, a choke resistance of $250,000\ \Omega$ would reduce it to 105, and a $10,000\ \Omega$ resistance to 9.5! The associated violent fluctuation in equivalent capacitance is likely to be very upsetting, particularly if the tuning is supposed to be ganged.

These statements may be more convincing if backed by some actual examples. And it may be as well to say something about the method of measurement. One way of measuring the values of R and C is by means of a bridge, but a bridge covering a wide range of radio frequencies is a rare and expensive thing. Humbler experimenters can get the results by making up a special oscillator with carefully arranged tuning and oscillation controls. The effect of putting capacitance in parallel with an oscillator tuning circuit is to shift the frequency and if it is brought back again by reducing the capacitance of a parallel tuning capacitor calibrated in pF the value of the added capacitance can be read off. The effect of putting resistance in parallel is to shift the point on the oscillation control at which oscillation just stops or starts, and by making a preliminary trial with a number of known resistors the control can be calibrated in resistance at each frequency. So the drill is to set the oscillator so that it just oscillates, with the calibrated capacitor at zero on its scale. The choke is then clipped across the tuned circuit terminals and the oscillation control reset to restore oscillation (the amount of the adjustment showing the choke resis-


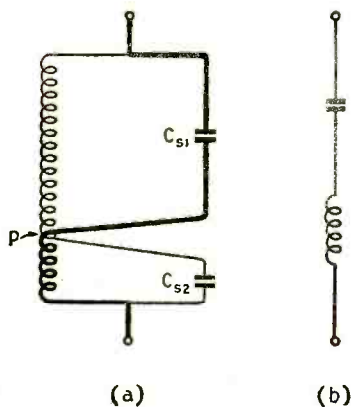


Fig. 6. Showing how at a certain frequency one part of a coil can be capacitive and another inductive (a), forming a series resonant circuit (b).

Fig. 7. Equivalent resistance and capacitance, R and C in Fig. 5 (a), graphed for three actual r.f. chokes over a wide range of frequency.

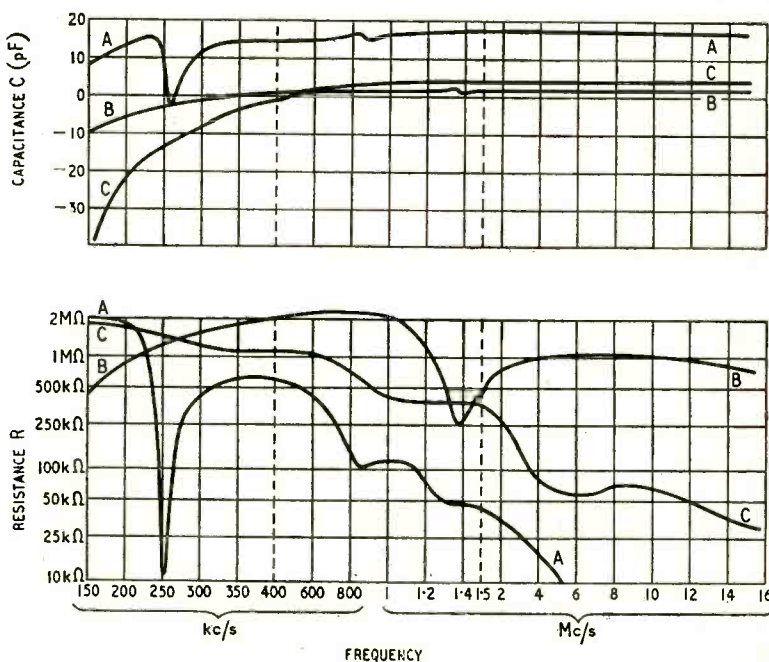

tance), and the calibrated capacitor is reset to restore the original frequency (the amount of the adjustment showing the choke capacitance). The test is then repeated at sufficient frequencies to provide data for a graph. To cope with both positive and negative capacitance the calibrated capacitor should have a centre zero, reductions in its capacitance being marked positive and increases negative.

One of the misconceptions about r.f. chokes is to suppose that dead spots are necessarily caused by the separate sections of divided windings resonating on their own. As a matter of fact the worst offenders are usually single-section types. "A" in Fig. 7 is an example; $\frac{1}{2}$ in internal diameter, 1 $\frac{1}{2}$ in external diameter, $\frac{1}{4}$ in wide. It has an inductance of about 150,000 μ H which, with such a large C_s as this choke has, is enough to bring its rejector resonance well below the measured range of frequency. As you see, there is a violent acceptor resonance at 250kc/s. You can imagine what would happen to a parallel-fed tuned circuit in which this choke was used as the feed path! Note the accompanying fluctuation in capacitance. And the very low resistance and large capacitance at high frequencies.

I checked the Fig. 6 theory in a rather interesting way by feeding a choke at a pronounced dead-spot frequency from a powerful oscillator. After keeping it on for some time I found that a comparatively small part of the winding had become hot while the rest was cool. The hot section was, of course, the one forming the inductance, through which the full r.f. current had flowed.

While narrowing a single coil is some help by reducing C_s , a serious long-wave dead spot is likely to persist unless the winding is divided into sections. Doing this does not in itself guarantee that there will be no appreciable series resonances. Design by theory is so difficult that most of us work by trial and error. Obviously one takes care about such things as keeping the terminal leads from running close together, as that would quite unnecessarily increase C_s . Apart from dodging dead spots, the main difficulty is that success in reducing C_s brings f_s higher, so that the steep negative fall-off in Fig. 4 comes into the working range of frequency and it is necessary to raise the inductance. This means more turns, more series resistance, and more inductive coupling and risk of introducing hum and undesired feedback.

With the object, presumably, of reducing inductive coupling, it was once a practice to enclose chokes in screening cans. But these, while possibly of some value for cutting out *capacitive* coupling, are almost completely ineffective as magnetic screens at power or even audio frequencies. And at the working (radio) frequencies, at which the screening might be effective, the choke does not act as an inductance anyway. Moreover the screen largely spoils the performance of an otherwise good choke, by increasing C_s and reducing R and L.

Another scheme is to have two oppositely-wound coils side-by-side—the so-called binocular choke. This is very effective in directions equidistant from the two halves of the choke, but much less so where one half is nearer than the other (Fig. 8(a)). Personally I prefer to have the two halves end-to-end on the same axis, as in Fig. 8(b).

In these anti-coupling schemes each half of the choke opposes the other, reducing the inductance. So by now the number of turns required is becoming really formidable, unless one eases the situation by


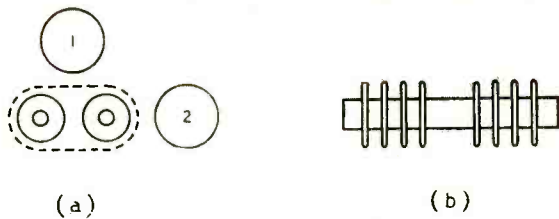


Fig. 8. At (a), coupling between a binocular choke and a coil in position 1 may be zero, but in position 2 can be quite considerable. An alternative method of winding two halves of a choke to counteract coupling is end-to-end, as at (b).

Fig. 9. Parallel-feed intervalve coupling circuit. The detuning effect of the choke has to be counteracted by trimming L_1 as well as C_1 .

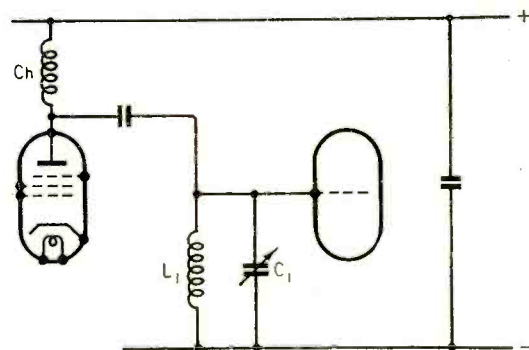

using an iron core (or a pair of them for a twin choke). Fortunately the effectiveness of the core at the higher radio frequencies is unimportant—if anything it would be an advantage if it fell right off—so one is free to choose a grade that has a high permeability in the region of 150kc/s (assuming that to be the lowest working frequency). The core is likely to increase C_s , but with suitable design it need only be very slightly; and the increase may well be more than wiped out by the reduction in the size of winding due to the core.

Type A in Fig. 7, a one-time commercial model, is an example of how bad a choke can be. Curves B refer to an experimental attempt to show how good a choke can be. No doubt even this could be improved upon, for it dates from a time when suitable iron-dust cores were not readily available, and they were in fact made of thin rolled-up iron tape, one in each end of a Fig. 8(b) pair. The fall-off is decidedly in evidence at 150kc/s, and there is one rather nasty dip in the resistance at about 1.4Mc/s.

The third example, C in Fig. 7, is a present-day type of simple and inexpensive construction, without the anti-coupling (or astatic) feature. It is remarkably free from violent series resonances. The inductance is rather on the low side, so that if it were used in parallel with one tuned circuit in a gang it would upset the tuning at the low-frequency end unless suitable precautions were taken. Fig. 9 shows the elements of a tuned r.f. intervalve coupling (L_1 and C_1) parallel-fed via an r.f. choke Ch. So far as r.f. is concerned, Ch is in parallel with L_1C_1 , which is not only damped by R in Fig. 7 but detuned by the varying C. If C

consisted solely of C_s (L being infinitely large), then the detuning due to the choke would be removable by adjusting the trimmer capacitor in parallel with C_s , reducing its capacitance by an amount equal to C_s . But since any real choke has a finite inductance L , which causes an effect equivalent to the imaginary varying C in Figs. 4 and 7, something more is needed to counteract the detuning effect of Ch . Putting L in parallel with L_1 is equivalent to reducing L_1 . So we need only increase L_1 by that amount to bring it to the correct value.

The rule for calculating inductances in parallel is the same as for resistances. Let us denote the increased tuning-coil inductance by L_1' . To get things right, the inductance of L_1' in parallel with L must be equal to the original L_1 . Putting it in algebra:

$$\frac{1}{L_1'} + \frac{1}{L} = \frac{1}{L_1}$$

With a little manipulation this can be worked around to

$$L_1' = \frac{LL_1}{L - L_1}$$

For instance, if L_1 , the normal tuning coil inductance, is $2,200\mu\text{H}$, and L , the choke inductance, is $50,000\mu\text{H}$, the adjusted tuning coil inductance must be $2,200 \times 50,000$ divided by $50,000 - 2,200$, which is $2,300$ —a rise of about $4\frac{1}{2}\%$. If the tuning coil is fitted with an adjustable iron core this should be easy.

I hope that by now most of the questions at the beginning may be deemed to have been answered, directly or indirectly; but there is perhaps one

exception—the question about putting a short-wave choke in series with an “all-wave” type to make it rather more all-wave than it would otherwise be. This question chiefly concerns the self-capacitance, C_s . If the choke is in parallel with other capacitances, as in Fig. 9 for example, then a picofarad more or less is neither here nor there, because it can be taken up on the trimmer. The main object in keeping C_s low in such circumstances is as a means of keeping R high. But if the purpose of the choke is to prevent r.f. currents from taking a certain path, then C_s becomes vital on its own account at the higher frequencies. A value of, say, 5pF would be generally satisfactory at low r.f. (reactance $160,000\Omega$ at 200kc/s) and perhaps fair enough at medium r.f. ($32,000\Omega$ at 1Mc/s). But at 20Mc/s it is down to $1,600\Omega$, so it would be pointless to strive to keep R up in the megohm region. By winding a comparatively few turns of small diameter in one of the low-capacitance styles, it is possible to keep C_s down to less than 1pF , with great advantage at the high-frequency end. But of course the inductance would be quite inadequate for low r.f. So if both have to be covered, both chokes can be connected in series and placed so as not to couple with one another. At the h.f. end we have perhaps 0.7pF in series with 5pF . This is not at all the same thing as a few more turns on the big choke, where they would couple closely with the others and the type of winding (being designed for high inductance) would be unsuitable for very low capacitance. At low r.f. the small choke would hardly influence the situation at all; it would merely be a relatively small series inductance.

BUSINESS RADIO

A Review of the Present Position

CONSIDERABLE criticism has recently been levelled against the Post Office from certain quarters for its so-called tardiness regarding the development of Business Radio. This criticism is, we believe, largely due to a misinterpretation of the facts and also to the reluctance of the Post Office to give undue publicity to the Service for fear of an avalanche of requests for frequencies for “frivolous” purposes. We are, therefore, grateful to the officers of the Overseas Telecommunication Dept. (the section of the Post Office responsible for the licensing of Business Radio) for facts regarding the Service.

It will be recalled that, as stated in our September issue, the P.M.G. announced in the House that 400 licences, covering 392 fixed and 1,902 mobile stations, had been issued by the Post Office for mobile radio services (excluding police and fire) at the end of July. This tells only half the story. Whilst this is, of course, the correct number of licences in force, no mention was made of the hundreds of applicants to whom frequencies had been allocated, but whose licences were held up until equipment was delivered. Had these been added to the totals they would have been increased by some 50 per cent. In fairness to the Post Office it should, moreover, be stated that every application for a mobile Business Radio licence has been met—except, of course, where it was considered the line telephone service met the need.

It is perhaps worth commenting on the relative

positions in this country and the United States. In the U.S. Business Radio is largely confined to taxi and car-hire services, and, as they have only four channels below 450Mc/s , as many as 400 taxis operate in the same channel in some of the larger cities. In this country any applicant—from bookmaker to builder, doctor to dairy farmer, and taxi-owner to towage company—is accommodated within one of the existing Business Radio bands.

With, however, the growth of the demand for this service, the available channels in the 71.5-88 and 156-184 Mc/s bands are, so far as London is concerned, liable to become overcrowded. There is, of course, the 460-470 Mc/s band, but the utilization of this band is hampered by the lack of suitable equipment.

Readers may like to have exact details of the bands in which Business Radio is accommodated:—(a) 71.5-72.8, (b) 76.7-78.0, (c) 85-88, (d) 156-184, and (e) 460-470 Mc/s .

Frequencies in (a) and (b) are paired with those in (c) for duplex operation. Channels are 50kc/s wide in (a), (b) and (c), and 100kc/s wide in (d). So far, of course, there is no service in this country comparable with the American “Citizen’s Radio”—a mobile radio-telephone service for John Citizen. Provision has, however, been made by the Post Office for the operation of land mobile services in the 460-470 Mc/s band, where the Post Office point-to-point service is also accommodated.

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents.

Pulse Power

IN his article "Mystery Broadcasting" your contributor Thomas Roddam refers in your October issue to a transmitter of 1-kW mean power sending 1- μ s, 33-kW pulses 30,000 times per second and states that this would be received as a 33-kW transmitter.

This is erroneous, since the signal-to-noise ratio, the proper basis of comparison, would be no better than in the 1-kW condition. Let us take, for example, a transmitter sending pulses of a certain duration. These pulses are then reduced to one-fourth of their former length and, for the same mean transmitter power, the pulse power can be increased four times. This doubles the signal voltage in the receiver, but to handle these shortened pulses, the receiver bandwidth must be increased four times. Since the noise voltage is proportional to the square root of the receiver bandwidth, it is now double its former value, so that there is no net gain; signal volts and noise volts having increased equally. There is no way round this problem which is fundamental to all pulse systems; any attempt to reduce noise by increased selectivity would only deform the shape of the signals and sacrifice the pulse energy residing in that part of its sideband spectrum which lies outside the pass-band of the receiver.

These points are not made to discredit pulse transmission systems which, as your contributor correctly states, afford substantial signal-to-noise ratio improvements, but to demonstrate that altering the duty cycle of the transmitter cannot, in itself, affect the signal-to-noise ratio of the system as a whole. Basically, pulse modulation gets its advantage by sending all audio levels at full power in the manner explained by your contributor "Cathode Ray" in another part of the same issue. S. COOK.

Taunton, Somerset.

Earls Court Television

WHILE watching the various television demonstrations at Earls Court, it occurred to me that it is possible for many prospective buyers of television sets to be sadly disappointed when they compare the picture they will be shown in their local dealer's shop with the one they saw at the Show.

In Earls Court a high level television signal, amplitude 1mV \pm 3db in 70 Ω , was available at each outlet from the feeder system. This signal was completely free both from fading and interference and hence any television set should be capable of being set up to resolve it into a nearly perfect picture. Except in localities very close to the television transmitting stations nothing like such ideal conditions could possibly exist, since:—

(a) According to the field strength diagrams published by the B.B.C., the high signal level of 1mV/metre is only found within a radius of some 25-30 miles of Alexandra Palace or 40-50 miles of Sutton Coldfield.

(b) As soon as a metre-wave radio broadcast path is employed, interference becomes apparent, its effect on signal-to-noise ratio being normally dependent on the distance from the receiver to the transmitting station, though it may often be sufficient to spoil the picture in an area of nominally high signal level.

Surely, therefore, for demonstration purposes, it would be better to employ a signal which approximates more nearly to the one met with in practice, that is to say, one which is subjected to fading, aeroplane effect and a varying amount of man-made and atmospheric static. I would suggest for the latter a suitable interference level would be equivalent to that obtained in a suburban area fairly close to a main road. Such a test signed would be a check both of the efficiency of the receiver and of any interference

suppression circuits incorporated therein, which is surely the purpose of a competitive demonstration such as that in "Television Avenue." I. G. BENBOUGH.
Reading, Berks.

Redundant Word?

AS one of the technical people whose education has been advanced by reading *Wireless World* may I point out to R. L. Hackworth (November issue, p. 458) that when we speak of voltage, amperage and wattage we are conveying something more than the simple ideas of p.d., current and power; namely, the order of magnitude of the quantities, and the units in which they are measured. One does not speak of the "service obtainable from a motor tyre in terms of the distance traversed in miles" but of the mileage (milage)—a word Mr. Hackworth can look up in the Oxford Dictionary: at the same time I suggest he also looks up the definition of another word with the same termination, i.e., verbiage.

Hindhead.

HENRY MORGAN.

Legitimizing the "Puff"

WHILST Mr. Mayes' proposal to introduce a prefix for 10⁻⁹ (October issue) is logically sound on a broad basis and would go a long way towards easing the situation, the fact remains that the farad is an inconveniently large unit from a practical aspect. It seems unfortunate that having at last been presented by Giorgi with a much-improved system of absolute/practical units, we still cannot use the unit of capacitance as it stands and must, in effect, take 10⁻⁶ absolute units as our practical unit (i.e., the microfarad). Furthermore, we find it necessary to invent new prefixes to avoid decimal points and long strings of noughts. I suspect that "pico-" was born solely to help with the unit of capacitance, whilst we are now considering a prefix for 10⁻⁹ and it seems unlikely that these prefixes will have much use elsewhere (unless, for instance, we can persuade the physicists to abandon the angstrom—10⁻¹⁰ metres—and use instead the picometre, with appropriate numerical adjustments!)

Incidentally, it may be of interest to observe that the original value of the farad, as specified as a practical unit by the British Association for the Advancement of Science between 1861 and 1867, was equal to what we now call the microfarad. The latter was considered a convenient size for practical purposes in the telegraph field (at that time virtually the only practical application of electrical science).

I do not regard the "puff" as a new practical unit, having an arbitrary relationship with the absolute unit, in the way that the ampere is fixed at 10⁻¹ absolute c.g.s. units, but rather as a re-naming of an existing sub-multiple of the absolute (and practical) unit of the m.k.s. system. Splitting hairs, perhaps, but the "puff" is already used fairly widely (and unofficially) and would no doubt remain even if a new sub-multiple were introduced.

Mr. Mayes' specification for metric prefixes is sound, but should include the requirement that the prefix be not liable to ambiguity in conjunction with contractions of the names of units. The suggestion is that 10⁻⁹ farad could become 1 lillifarad or 1IF—by the way, Mr. Mayes, may we please at least have consistency as to capital or lower-case letters—but let us not overdo the humour by coining a prefix which, if the small letter is used (as it should be), stands an excellent chance of being misread for the figure "1," whilst the capital letters form a common abbreviation! Quite apart from the phonetic similarity between "lilli-" and "milli-."

If we must have a 10⁻⁹ prefix, then "nano-" referred

to in the editorial footnote to Mr. Mayes' letter, seems to meet the specification.

I am pleased that "Diallist" is apparently not horror-stricken at the thought of a "new" unit, but I disagree that the "puff" would be too small. Certainly a larger unit (replacing the microfarad) would be nearly as good, but the "puff" would be quite big enough for ordinary purposes and has the advantage of current usage. It is agreed that a "micro-puff" is unlikely to find a wide use, but so is a "micro-ohm." As to the typing of μ , I know that a "u" with a manually-added tail gives the right answer, but it tends to be overlooked when it occurs many times in a draft, and "uuF" looks wrong. Besides, a typist will often try to fabricate the thing from a "u" plus a displaced oblique stroke, with (usually) awful results!

Brookmans Park, Herts.

A. C. KAY.

"Decentralized" Broadcasting

I DO not think *Wireless World* need apologize for venturing to put its nose outside the field of pure technology—alluding to the first two paragraphs of the November editorial—in a matter which is so closely associated with radio as the content of what is broadcast. Taking the liberty of a correspondent to go a little farther than editorial etiquette permits, I should like to say that, although I grumble a good deal at B.B.C. programmes, I know, underneath, that they are far better than the mercenary and small-minded drivel which local magnates would inflict on us if they could get at the microphone—and the dangerous rubbish they would pour out at times of social unrest and national danger. Neither financial ability to hire a broadcasting station and its technical personnel, nor success in vote-catching, are proofs of good taste, intelligence, or even sense of social responsibility. May we be saved from the boring nonsense sponsored by sales departments and local provincial big-wigs, which is such a feature of broadcasting in the U.S.A. and in the less "free" countries of Europe and Asia!

Huntingdon.

W. H. CAZALY.

"Jointing Aluminium"

IN reply to P. A. Raine's letter (October issue), I would emphasize the following facts.

The scratch brush method can, of course, produce a semblance of a completely tinned surface, but if the aluminium is reheated and the surface wiped it will be found that a series of fine scratches have been produced in the oxide layer in which the solder has bonded to the aluminium. The continuous film of solder then floats over the surface of the remaining oxide and is keyed by the bonding achieved in the scratches.

Ultrasonic abrasion caused by cavitation in the molten solder occurs on a semi-molecular scale and after tinning by this means the wiping of the metal will reveal an unbroken surface of solder.

While I do not wish to cast any reflection on the scratch brush method advocated by Mr. Raine, it will be realized from these comments that the ultrasonic method will produce a stronger joint with better electrical properties. In the jointing of cable sheaths, no great strength of joint is required nor are its electrical properties of interest. There are, however, many operations where these factors are of the utmost importance and mechanical abrasion cannot be considered satisfactory in these cases.

Mullard Ltd.

A. E. CRAWFORD.

London, W.C.2

Bad Radio Teaching

"DIALLIST" (*Wireless World*, August number) will find that Prof. Sandiford has devoted a chapter to the teaching and learning of elementary mathematics (the

root of the trouble about "maths") in his "Educational Psychology" (Longmans, Green and Company). The trouble is that very few teachers know enough about psychology either to perceive the use it can be to them or to apply it intelligently and efficiently in their work; most of them drift into teaching as a means of livelihood on the strength of their technical exam-passing abilities and regard teaching as a fairly easy job requiring only that they "say it very loud and clear."

Not only the teaching of mathematics, but the teaching of that group of subjects lumped under the heading of "radio" is so badly done, by people who may know something about radio but practically nothing about teaching, especially the teaching of radio, and, moreover, have resentment, probably arising out of their ignorance of what teaching means and conceit about their small fund of specialized technical skill, against being told what bad teachers they are, that there need be no surprise or mystery about the shortage of really well-trained younger radio technicians to-day.

It is usual to blame the youngsters and dub them stupid. In fact, only the native wits, as good as ever they were, and the pathetic keenness of intelligent youngsters to grasp the "go" of some of the exciting stuff of their modern electromechanized civilization, prevents radio, amongst much else, becoming a kind of magic beyond the comprehension of any but wizardlike creatures muttering mathematical mumbo-jumbo, in the view of the average citizen. If the technical experts would be content with a little less attention to erudition and a little more to the psychology of explanation, we should soon find the shortage of good technicians markedly lessening.

MARK OWNEY.

Valve Standardization

I CANNOT believe the majority of your readers will agree with Mr. J. R. Hughes who, in your report of the Brit. I.R.E. Convention, is stated to have said that "the main obstacle to standardization is the valve user." I would remind him of the side-contact base series, the Mazda Octal series and that recent "achievement" the B8A series—all of which were "sold" to the user by the valve makers themselves. And, of course, history usually repeats itself!

Broxbourne, Herts.

T. L. FRANKLIN.

Crystal Menace?

REFERRING to the recent correspondence on the radiation of harmonics from crystal sets, surely there is no disadvantage in transposing the aerial series capacitors and their associated inductances. The theoretical 6db reduction per number of harmonic is worth having.

Reading, Berks.

F. A. RUDDLE.

Diathermy Interference

H. WILLAN CRITCHLEY, in your November issue, "doubts if diathermy is the source of the interference" (causing herring bone or oak-grain bands on Holme Moss Television transmissions). May I say that my tests have established that it definitely is the cause. In this area we have been in touch with the hospital engineer, and have, with his co-operation, watched a television receiver while the diathermy equipment was switched on and off. The interference band only appeared when the equipment was in use, and disappeared immediately on switching off the equipment.

The variation of the pattern is most probably due to the different applications of the diathermy.

P. L. EVERETT.

Chester-le-Street, Co. Durham.

WORLD OF WIRELESS

U.K. Frequency Standards ♦ Aeronautical Radio Aids ♦ Mobile
Television Stations ♦ B.B.C. Expenditure ♦ December Meetings

Standard Frequencies

AN experimental service of standard frequency transmissions from the Rugby station MSF was inaugurated under the auspices of the National Physical Laboratory some twenty months ago. Various changes having recently been introduced in the schedule, we give below revised details of the transmissions.

The frequencies, which are maintained within two parts in one hundred million of their nominal value, are monitored at the N.P.L., Teddington, Middlesex, to which all correspondence relating to the transmissions should be sent. The transmitter has a power of 10 kW.


The revised schedule (G.M.T.) is 0544-0615 on 5 Mc/s; 0629-0700 on 10 Mc/s; and 1029-1130 and 1429-1530 on 60 kc/s. The first minute of each transmission period is devoted to the call sign in slow morse and a speech announcement; then the following fifteen-minute cycle is repeated: carrier modulated with 1,000 c/s for five minutes, one cycle-per-second timing pulses for five minutes, the carrier unmodulated for four minutes and the call sign and announcement for one minute.

The low-power transmissions on 2 Mc/s from the Royal Observatory station (GMT) at Abinger, Surrey, which were introduced as an interim measure in 1948, have been discontinued for some time.

Television Exhibition

THE annual exhibition of the Television Society, which is expected to be on a larger scale than in past years, will be held at the invitation of Mullards in the basement of Century House, Shaftesbury Avenue, London, W.C.2, on December 28th and 29th. On the first day it is open to members only from 6.0 to 9.30 p.m., but on the following day the public will be admitted by invitation ticket from 10.30 a.m. to 5.0 p.m.

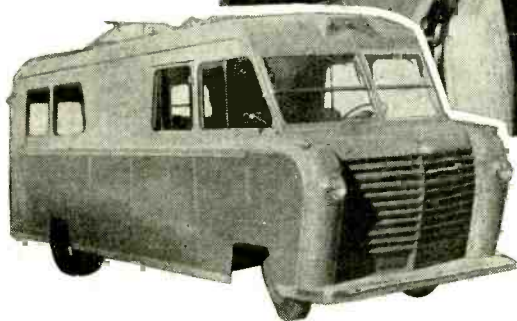COMPLETE mobile television station. Above the four control monitors is the receiver monitoring the radiated picture.



Exhibitors will be limited to members of the Society, and a number of manufacturers invited by the Society. All exhibits will be associated with some phase of television engineering or production. Some of the manufacturers will be exhibiting equipment for which a member of the Society has been responsible, either in design or production.

Further particulars are available from the Society's lecture secretary, G. T. Clack, 10, Tantallon Road, London, S.W.12.

Teaching Teachers

PREPARATORY to the commencement of the scholastic year, a week's course for full-time and part-time teachers of radio and television servicing was held at the Regent Street Polytechnic in September under the direction of H. W. French, B.Sc., H.M. Inspector of Schools.

Organized jointly by the Ministry of Education and the Radio Industry Council, the course was particularly valuable for the interchange of ideas between those concerned with technical education and representatives of the radio industry.


Flight Log Navigation

FOLLOWING a recommendation by the International Civil Aviation Organization, the Ministry of Civil Aviation has recently undertaken a series of trials with the Decca flight log navigational aid. This automatic device, described in our April, 1951, issue (p. 143), is an adjunct to the ordinary Decca system, giving a continuous plot on a map of the exact position of the aircraft.

According to the Ministry, the results so far obtained suggest that the Decca system and flight log may be able to provide European air routes with a better navigational service than any at present in use or contemplated, and at much lower cost than for any comparable system. It is thought, too, that the flight log will be of particular value for navigation in jet aircraft. Representatives of European civil aviation have been collaborating in the trials.

Television O.B. Units

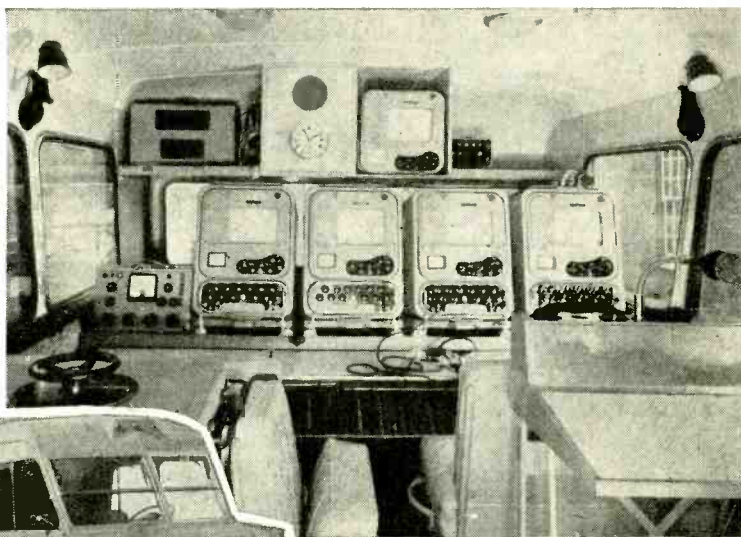WE recently had an opportunity of inspecting one of the two mobile O.B. television units which Marconi's are supplying to the Canadian Broadcasting Corporation.



Each vehicle is a self-contained three-camera station with its own microwave radio link, the parabola for which is stowed on the roof. As will be seen in the interior view reproduced, four monitors are provided—one for each camera, and that

on the right as a master control and mixer. These monitoring units are designed for ease of servicing—the camera control unit (the lower section of the monitor) can be withdrawn revealing all the wiring, which, incidentally, is on the topside of the chassis.

Intercommunication between members of the crew is a major problem in O.B. units and provision is made so that all members can hear, in their headphones, both the transmitted programme and, superimposed, all instructions. Camera operators can speak to the camera control positions and the producer, whilst the latter (whose desk is on the right in the photograph), and the technical director, can speak to all the crew.

Commemorative Plaques

DURING the recent unveiling of the commemorative plaque to Baird on the wall of 22, Frith Street, Soho, where he first demonstrated television, reference was made to the proposal to commemorate the London residence of Marconi. It appears, however, that two difficulties arise. First, Marconi lived in a number of houses in London, and secondly, will the L.C.C. again break its rule that plaques are not erected until at least twenty years after the death of the celebrity they wish to honour—Marconi died in July, 1937.

Having broken away from usual practice in the case of Baird, it would be unreasonable for the Council to adhere to the rule in the case of Marconi, upon whose foundation Baird built. December 12th, the fiftieth anniversary of the spanning of the Atlantic, would have been an ideal date for the dedication.

International Television

THE first issue of the *Bulletin* of the Comité International de Télévision has recently been received. In it is outlined the constitution of the C.I.T. which was set up in 1947 for the purpose of encouraging international collaboration in the field of television technique. The 182-page *Bulletin* includes a number of papers—in English, French, German and Italian—read at the Milan International Television Congress.

Among the British radio personalities on the Study Committees are Dr. R. C. G. Williams (chief engineer, Philips Electrical), vice-president of the Commercial Committee, and T. M. C. Lance (chief engineer, Cinema-Television), president of the committee responsible for organizing congresses and exhibitions.

The headquarters of the C.I.T. are at 41, Gloriosastrasse, Zurich, 6, Switzerland, and the general secretariat at 92, Avenue Champs-Élysées, Paris, France, from whom details can be obtained of the journal.


Electronics and Films

A NEW company, High Definition Films, Ltd., of which Norman Collins (at one time B.B.C. Controller of Television) is chairman and managing director, has been formed to develop the use of electronic apparatus in the film industry. An advantage of the electronic film camera is that it enables the film director and technicians to see on monitors during the filming the shots exactly as filmed and, moreover, it is more sensitive.

T. C. Macnamara, technical director of Scopony-Baird, will be in charge of the company's technical operations, which will be conducted at Cambridge in collaboration with Pye. Other directors of the company, the address of which is 24, Old Bond Street, London, E.C.2, are Sir Robert Renwick and C. O. Stanley (chairman of Pye Radio).

Comparative Costs

FROM a perusal of the financial statements published in the "B.B.C. Yearbook, 1952," some interesting conclusions can be drawn. It is particularly interesting to note that, whereas in the Home "sound" services the revenue expenditure on engineering and programmes is respectively 23.5 and 57 per cent of the total; in television it is 35.5 and 44.6 per cent respectively. Plant maintenance in television accounts for 10 per cent compared with 2 per cent for sound, despite the fact that the hours of operation are vastly different—television 6,610 hours, Home "sound" 203,178 hours in 1950.

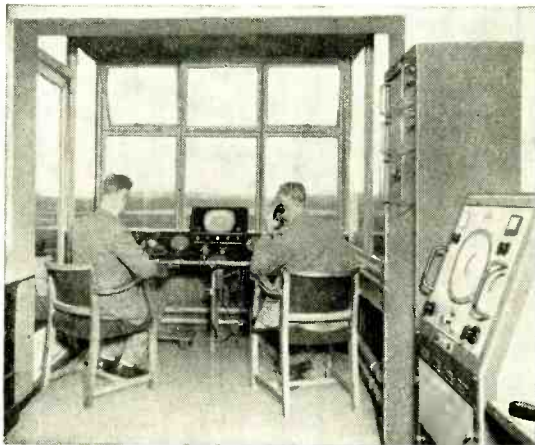

V.H.F./D.F. installation in the control tower at the de Havilland airfield, Hatfield. Master control console and twin receivers are on the right with the remote bearing indicator on the control desk.

So far as the Overseas Services are concerned, which were on the air for 166,830 hours in 1950, the expenditure on engineering was 26.3 per cent and programmes 55.9.

The rate of depreciation of television gear, compared with sound equipment, is considerably higher, when the hours of operation are taken into account. For the year 1950/51, the figures are "sound" £108,000; television £74,000.

On the revenue side the income from "sound only" licences was £10,680,906, and from television fees £1,413,292, whilst the expenditure on the Home "sound" service was £7,860,883 and on television £1,718,578. The Corporation's income from publications was £955,230.

Radio and Power Cuts

IN our last issue reference was made to the use of broadcasting as a means of conveying warnings of impending load-shedding to consumers. The B.B.C. has since issued detailed plans which, as suggested by our contemporary *Electrical Review*, include the transmission of a 1,000c/s tone for three seconds preceded by the word "caution." These warnings will be transmitted on 1,500 metres between 7.30 a.m. and 12.30 p.m., and from 3.0 to 6.0 p.m. on Mondays to Fridays.

The B.B.C. is further co-operating in the fuel economy campaign by delaying the start of the children's television programme on week-days until 5.30, as was suggested by our contributor, M. G. Scroggie.

V.H.F. Direction Finder

A NEW v.h.f. direction finder, incorporating a number of novel features, has been developed by the Marconi Company for the 118-132-Mc/s band used by civil aviation. It is the Type AD200 and is capable of giving a first-class "sensed" bearing immediately on request, a valuable feature in view of the high speeds now attained by jet-engined aircraft.

The direction finder is largely automatic in operation and can be controlled either locally or from a distance of up to 30 miles over ordinary telephone lines.

Two d.f. channels, each with its own display units, may be operated simultaneously from a single aerial system, one pair of telephone lines being required for each when remotely controlled. Bearings are automatically corrected for sense and are read off an 8-in circular meter scaled directly in degrees.

In addition to local and remote d.f. consoles, desk-type bearing repeater units are available for extending the

d.f. information to points such as a control tower where space may be limited.

PERSONALITIES

N. C. Robertson, M.B.E., will be responsible for the production of all radio, radar, telecommunication and electronic equipment as Director-General of Electronics Production in



N. C. ROBERTSON, M.B.E.

the Ministry of Supply—an honorary post. The creation of this Directorship was announced in the House of Commons in July. Mr. Robertson, who is 43, and has been in the radio industry since 1924, joined E. K. Cole, Ltd., in 1930. He has been successively chief inspector, production manager, works manager and since 1945 deputy managing director in the company. He is an Associate of the I.E.E. and was made an M.B.E. in 1944.

S. S. C. Mitchell, C.B., O.B.E., M.I.Mech.E., the new Controller of Guided Weapons and Electronics in the Ministry of Supply, will be in charge of all work in research, development and production of guided weapons in Britain. He will also undertake the responsibility for the direction of the Ministry of Supply's work on electronics research, development and production. During his naval career he specialized in gunnery. Since 1945 he has been Chief Engineer, Armament Design, at the Ministry of Supply. He is 49.

G. E. Condliffe, O.B.E., B.Sc., M.I.E.E., who has for some time been managing director of Emitron Television, Ltd., has been appointed to a similar post with the associated concern, E.M.I. Research Laboratories, Ltd. He joined the research laboratories of the Gramophone Co. in 1929, and during the war was concerned with Government radar projects.

S. A. Hurren, Head of the Department of Radio and Musical Instrument Technology at the Northern Polytechnic, Holloway, London, N.7, since 1935, is retiring at the end of the year. Mr. Hurren, who has spent 32 of his 44 years of teaching at the Northern Polytechnic, has been chairman of the Radio Trades Examination Board since its inception, and is a past president of the Brit.I.R.E.

John C. G. Gilbert, Assoc. I.E.E., M.Brit.I.R.E., who has been lecturing at the Northern Polytechnic, Holloway, since 1934, and for the past year has

been senior lecturer in the Department of Radio and Musical Instrument Technology, has been appointed Head of the Department in succession to S. A. Hurren.

IN BRIEF

Receiving Licences.—If the rate of increase in television licences recorded during September (25,450) has been maintained during the following two months, the number will have reached a million by the time this issue appears. The September figure was 958,500. The total number of broadcast receiving licences (sound and vision) in force in the U.K. at the end of the third quarter was 12,391,350, which was a reduction of 52,500 on August.

Faraday Lecture.—This year's I.E.E. Faraday Lecturer is Dr. G. F. Dutton, of E.M.I. Engineering Development, Ltd., who has chosen as his subject "Sound Recording—Home, Professional, Industrial and Scientific Applications." The lecture will be delivered first at the Town Hall, Birmingham, on December 18th, and subsequently on December 19th at Leicester; January 10th, Cardiff; February 12th, London; March 11th, Newcastle-upon-Tyne; March 13th, Leeds; March 17th, Liverpool; March 20th, Belfast; April 7th, Southampton; April 22nd, Glasgow; April 24th, Aberdeen.

Amateur Show.—The R.S.G.B. Amateur Radio Exhibition opens at the Royal Hotel, Woburn Place, London, W.C.1, at 11.0 a.m. on November 28th, although the official opening ceremony by Charles I. Orr-Ewing, O.B.E., M.P., is not until noon. Admission to the exhibition, which will be open from 11.0 to 9.0 p.m. daily until December 1st, is sixpence.

Patent Office Library.—It has been decided to continue the extended hours of opening of the Patent Office Library at 25, Southampton Buildings, Chancery Lane, London, W.C.2, until December 28th. The hours are 10 a.m. to 9 p.m. Monday to Friday, and 10 a.m. to 5 p.m. Saturday.

Photos for Publication.—Whilst not of direct interest to readers of *Wireless World*, the book "Cash From Your Camera," issued by our associate journal, *Amateur Photographer*, will be found extremely useful by those who aspire to take photographs with a view to publication. It has 140 pages and costs 7s 6d, or by post from our publisher, price 7s 10d.

Technical Register.—The office of the Technical and Scientific Register of the Ministry of Labour and National Service is now at Almack House, 26-28, King Street, St. James' Square, London, S.W.1 (Tel.: Trafalgar 7020).

Training Courses for service technicians have been started by E.M.I. in Scotland. Particulars of the ten-day courses, which will cover basic television theory as well as specialized receiver circuitry, are obtainable from A. J. Lillicrap, Training Division, E.M.I. Sales & Service, Sheraton Works, Wadsworth Road, Greenford, Middx.

"**Facts and Figures**" is the title of a 20-page extract from the B.S.R.A. Diary giving basic data and useful formulae relating to recording on disc, magnetic tape and film. It is available from the Hon. Librarian, British Sound Recording Association, 8, Stanton Road, London, S.W.20, price 1s 3d.

Grommets.—Minimum physical test requirements and dimensions for a standard range of grommets for use in various industries, including telecommunications, are given in BS.1767:1951, "Grommets for General Purposes." This British Standard, which costs 2s, is confined to rubber, synthetic rubber and rubber-like materials such as P.V.C.


Finland.—A booklet has been issued by the Finnish Association of Technical Traders giving the names and addresses of member firms in various branches of industry with whom manufacturers wishing to market their products in Finland are invited to communicate.

"**Toute la Radio**," our Paris contemporary, has produced another overseas edition (November), in which summaries of the main articles are given in English and Spanish.

E.I.B.A. Ball.—Manchester's Annual Electrical Industries Ball, in aid of the Electrical Industries Benevolent Association, will be held on December 7th at the Midland Hotel at 7.15. Applications for tickets should be made to Claude Brookes, Salford Electrical Instruments, Ltd., Peel Works, Silk Street, Salford, 3.

Aerial "Whys and Wherefores."—Preparatory to the opening of the Kirk O' Shotts television station, Belling and Lee are arranging three meetings for dealers at which there will be talks on the "whys and wherefores" of different types of aeriels. Details of the meetings, which will be held in Edinburgh

AIRPORT CONTROL

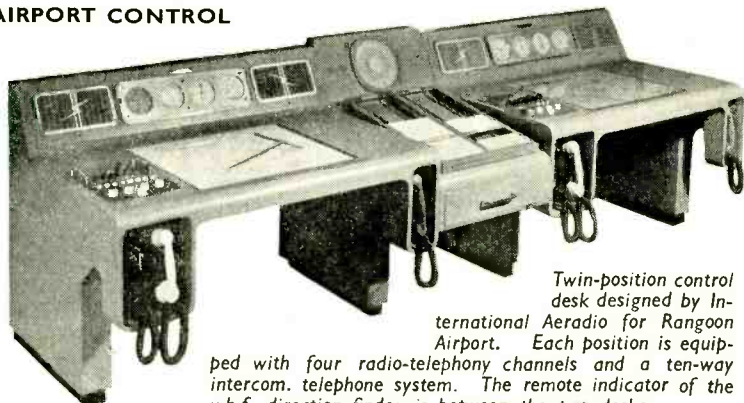

Twin-position control desk designed by International Aeradio for Rangoon Airport. Each position is equipped with four radio-telephony channels and a ten-way intercom. telephone system. The remote indicator of the v.h.f. direction finder is between the two desks.

(December 10th), Dundee (12th) and Glasgow (14th), are obtainable from Belling and Lee, Cambridge Arterial Road, Enfield, Middx.

"A Guide to Plastics" by C. A. Redfarn, B.Sc., Ph.D., F.R.I.C., which is issued by our associate journal *British Plastics*, price 7s 6d, deals with the subject of plastics from the basic raw material, through the stages of manufacture to finished products.

Plastics Exhibition.—The success of the Plastics Exhibition and Convention held at Olympia in June has prompted the organizers, *British Plastics*, to make preparatory arrangements for a similar exhibition in 1953.

Antipodean Radio-telephony.—The Hong Kong-Australia radio-telephone service has now been extended to New Zealand.

INDUSTRIAL NEWS

Tannoy sound-reinforcing equipment, similar to that installed in both Houses of Parliament and Church House, Westminster, has been provided in the Parliament Chamber, New Delhi. The installation, which includes sixteen microphones and over 400 reproducers, was undertaken by Union Radio and Appliances, Ltd., New Delhi, India.

E.M.I. Service Depot for the Northern television area has been opened by E.M.I. Sales & Service at Regent House, Cannon Street, Manchester (Tel.: Deansgate 2315). H. A. H. Kelsey, previously with the organization at Perivale, has been appointed manager of the depot.

Londex, Ltd., have opened a third factory—in Croydon. The main offices and research section remain at the Anerley Works, Anerley Road, London, S.E.20 (Tel.: Sydenham 6258), and the Progress and Buying Departments at Howard Road, S.E.20 (Tel.: Sydenham 2431).

Edison Swan Electric Co. announce that they have ceased to handle Plessey components suitable for the "Viewmaster" television receiver.

Grampian Reproducers, Ltd., announce that G. Fidler, who was in charge of their experimental department, has resigned. He has joined Avimo, Ltd., of Taunton, as chief engineer.

Altron is the trade name adopted by Allied Electronics, Ltd., of 28, Upper Richmond Road, London, S.W.15 (Tel.: Vandyke 1856), manufacturers of communications and industrial electronic equipment. They previously traded under the name of British Electronic Industries.

Osmor Radio Products, Bridge View Works, Borough Hill, Croydon, Surrey, manufacturers of coils and coil assemblies, have changed their telephone number to Croydon 5148.

Barker Loudspeakers.—Owing to the loss of a quantity of correspondence received between October 1st and 12th, Barker's ask correspondents to write again should they not receive a reply.

MEETINGS

Institution of Electrical Engineers

Radio Section.—"An Investigation into the Mechanism of Magnetic-Tape Recording" by P. E. Axon, O.B.E., M.Sc., on December 5th.

Informal Lecture on "What Practical Benefits can Communication Engineers expect from the Modern Information Theory?" by E. C. Cherry, M.Sc. (Eng.), on December 17th.

Ordinary Meeting.—"Technical Colleges and Education for the Electrical Industry" by H. L. Haslegrave, M.A., Ph.D., M.Sc.(Eng.), on December 6th.

Education Circle.—Discussion on "Activity Methods in Technical Education"; opener R. D. Watts, B.Sc., at 6 on December 12th.

The above meetings will be held at 5.30 (except where otherwise stated) at the I.E.E., Savoy Place, London, W.C.2.

East Midland Centre.—Faraday Lecture on "Sound Recording—Home, Professional, Industrial and Scientific Applications" by G. F. Dutton, Ph.D., B.Sc. (Eng.), at 7.15 on December 19th at De Montford Hall, Leicester.

Cambridge Radio Group.—Informal Lecture on "What Practical Benefits can Communication Engineers expect from the Modern Information Theory?" by E. C. Cherry, M.Sc.(Eng.), at 8.15 on December 4th at the Cavendish Laboratory, Cambridge. (Joint Meeting with the Cambridge University Wireless Society.)

Mersey & North Wales Centre.—"The London-Birmingham Television-Cable System" by T. Kilvington, B.Sc. (Eng.), F. J. M. Laver, and H. Stanesby, at 6.30 on December 3rd at the Liverpool Royal Institution, Colquitt Street, Liverpool.

North Eastern Radio Group.—"The Life of Oxide Cathodes in Modern Receiving Valves" by G. H. Metson, Ph.D., M.Sc., S. Wagener, Dr.Phil., M. F. Holmes, B.Sc., and M. R. Child, at 6.15 on December 3rd at King's College, Newcastle-upon-Tyne.

North Midland Centre.—Discussion on "The Devising of Examination Questions"; opener Prof. G. W. Carter, M.A., at 6 on December 4th at the Lighting Service Bureau, 24, Aire Street, Leeds.

North Western Centre.—"Technical Colleges and Education for the Electrical Industry" by H. L. Haslegrave, M.A., Ph.D., M.Sc.(Eng.), at 6.15 on December 4th at the Engineers' Club, Albert Square, Manchester.

South Midland Centre.—"The Sutton Coldfield Television Broadcasting Station" by P. A. T. Bevan, B.Sc., and H. Page, M.Sc., and "The Vision Transmitter for the Sutton Coldfield Television Station" by E. A. Nind, B.Sc. (Eng.), and E. McP. Leyton, at 6 on December 3rd at the James Watt Memorial Institute, Great Charles Street, Birmingham.

Faraday Lecture on "Sound Recording—Home, Professional, Industrial and Scientific Applications" by G. F. Dutton, Ph.D., B.Sc.(Eng.), at 6 on December 18th at the Town Hall, Birmingham.

Western Centre.—"The Life and Work of Oliver Heaviside" by Prof. G. H. Rawcliffe, M.A., D.Sc., at 6 on December 10th at the South Wales Institute of Engineers, Park Place, Cardiff.

British Institution of Radio Engineers

London Section.—"Electronic Analogues of Physiological Processes" by W. Grey Walter, M.A., Sc.D., and H. W. Shipton (Burden Neurological Inst.) at 6.30 on December 13th at the London School of Hygiene and Tropical Medicine, Keppel Street, W.C.1.

Scottish Section.—"Automatic Precision Temperature Recorders incorporating the Electronic Potentiometer" by C. H. Oford (Honeywell, Brown & Co.) at 7 on December 6th at the Institute of Engineers and Shipbuilders, Glasgow.

Merseyside Section.—"Multi-Station V.H.F. Communication Systems using Frequency Modulation" by W. P. Cole, B.Sc., and E. G. Hamer, B.Sc. (G.E.C. Research Laboratories) at 7 on December 6th at the Electricity Service Centre, Whitechapel, Liverpool.

South Midlands Section.—"Improvements in and relating to Loudspeaker Design" by R. T. Lakin (Whiteley Electrical) at 7.15 on December 12th at the Corporation Street Civic Restaurant, Coventry.

West Midlands Section.—"Design and Application of Industrial H.F. Heaters" by F. W. Budge at 7 on December 18th at Wolverhampton and Staffordshire Technical College, Wolverhampton.

Institution of Electronics

N. Western Branch.—"The Use of Cathode-Ray Tubes in Digital Computing Machines" by T. Kilburn, M.A., Ph.D., A.M.I.E.E., at 7 on November 30th at the College of Technology, Manchester.

Southern Branch.—"Germanium Crystal Valves: Their Characteristics and Applications" by B. R. Bettridge (G.E.C.), at 6.30 on December 5th at Southampton University College.

"Ionization and Nuclear Bombardment" by Inst. Lt. Cdr. R. E. Ward, A.C.G.I., Wh.Sch., R.N., at 7 on December 12th at H.M.S. Phoenix, Portsmouth.

Television Society

"Television Receiver Design for British and European Systems—a Comparative Study" by Bryan R. Overton, B.Sc., (Mullard Research Labs.) at 7 on December 6th at the Cinematograph Exhibitors' Association, 164, Shaftesbury Avenue, London, W.C.2.

Leicester Centre.—"Wide - Angle Scanning Circuits," by A. J. Thoroughgood, at 7 on December 3rd at the Leicester College of Technology (Room 104), The Newarke, Leicester.

British Sound Recording Association

London Section.—Members' Night: Short papers given by members on Hot stylus technique, Pickup design, Pickup tracking and Magnetic tape problems, at 7 on December 21st at the Royal Society of Arts, 6, John Adam Street, London, W.C.2.

Portsmouth Centre.—"Building High-Fidelity Amplifiers" by S. Goodsell, at 7.30 on December 20th at the Central Library, Guildhall Square, Portsmouth.

Radio Society of Great Britain

Annual general meeting at 6.30 on December 18th at the I.E.E., Savoy Place, London, W.C.2.

Engineers' Guild

Metropolitan Branch.—Films: "Voices under the Sea" (Cable & Wireless), and "The Port of Manchester," at 6 on December 6th at Caxton Hall, London, S.W.1.

Institution of Works Managers

Glasgow Branch.—"Electronics" by a representative from Ferranti, at 7.15 on December 17th at the Institution of Engineers and Shipbuilders in Scotland, 39, Elmbank Crescent, Glasgow, C.2.

VALVE CATHODE LIFE

By C. C. EAGLESFIELD, M.A. A.M.I.E.E.*

New Explanation for Apparent Deterioration—and a Remedy

IT is generally supposed that the lives of oxide-coated cathodes are only moderate; it may therefore come as a surprise that, in an investigation of the life records of repeater valves made by Standard Telephones and Cables, no evidence could be found to put a definite term to the cathode lives. The conclusion seems to be that the emission continues indefinitely.¹

However, an effect has been found that could easily be mistaken for a drop in the emissivity. This is the formation of a resistive barrier between the cathode core and the coating, which causes a feedback and thereby a change in the measured characteristics. The effect seems to occur so universally that the study of cathode life almost becomes a study of this resistance. When the life history of a valve shows a deterioration in working current, bias, or mutual conductance, it is perfectly feasible to postulate such a cathode resistance of sufficient magnitude to explain the change. If this be done, one would expect the required resistance to be inversely proportional to the cathode area.

In Fig. 1 is shown the life history of three valve types in terms of such a cathode resistance. The resistance is brought on to a common basis, i.e., for a cathode area of one square centimetre, and is derived from the observed change of mutual conductance during life. Two of the types are small r.f. pentodes and the third is an r.f. pentode of somewhat greater rating—it has a 5-W cathode (triple-carbonate on 0 nickel) and a mutual conductance of 6.5 mA/V at its usual working anode current of 38 mA. All three can be regarded as normal receiving-type valves.

It will be seen that the resistance builds up to a saturation value of about 40 ohm-square-centimetres for all three types, with a surprisingly sharp angle where the rise meets the saturation level.

The resistance grows in a similar way for many other types; the three valves shown have been chosen because it happens that the tests have been continued long enough to show the saturation level clearly. All the life histories that have been examined can be explained by the hypothesis that a cathode resistance builds up to 40 ohm-square-centimetres and then stays constant.

It is important to realize that the suggestion is that no change takes place in the emissivity of the cathodes, but that in all valves the resistance grows to a certain value and then stays constant. It may, or may not, change the measured characteristics appreciably, according to the design of the valve. But all valves grow the resistance and then stay without change indefinitely.

Are there any reasons for supposing that such a resistance exists physically?

A way of detecting it is to measure the mutual conductance at a high frequency (greater than about 5 Mc/s) as well as at a low frequency (less than about 50 kc/s). With a new valve, there is no difference but with an aged valve the high-frequency mutual conductance is the greater. Such a difference is only to be explained by a resistance shunted by a capacitance having been formed at the cathode.

The double-frequency method has been used to measure the cathode resistance of a number of valves that had deteriorated during life, supposedly for a drop in emission. In every case, a resistance was found and the resistance was approximately that required to explain the change in characteristics.

Growth of Cathode Resistance

Two possible causes have been suggested for the growth of the resistance: a mechanical theory by Raudorf and a chemical theory by Eisenstein.

Raudorf's theory² is that with age the coating shrinks away from the core, leaving contact between coating and core only at minute discrete spots. The reduction of contact area explains the resistance, which is localized round the contacts, and the high capacitance is explained by the close spacing between the core and the body of the coating. Raudorf associated the shrinking of the coating with a network of fine cracks that he observed on the outer surface of the coating of aged cathodes, and stated that he found flat cathodes much superior to round cathodes.

Eisenstein's theory³ is that a resistive film is formed at the interface of core and coating by the formation of compounds of barium and core impurities. These impurities are deliberately included in the core metal as reducing agents to promote activation: the most usual are silicon and magnesium and their effect is to

* Standard Telephones and Cables.
² W. Raudorf, *Wireless Engineer*, October, 1949, pp. 331-337, and May, 1950, p. 164.
³ A. Eisenstein, *Wireless Engineer*, March 1950, pp. 100-101.

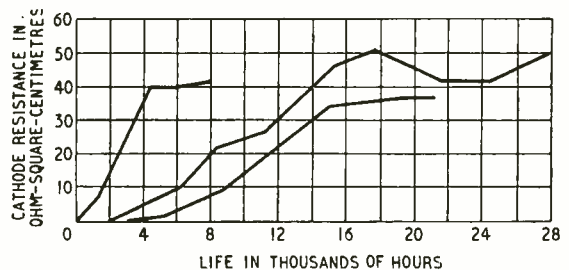


Fig. 1. Growth of cathode resistance during life for three types of valves.

C. C. Eaglesfield, *Electrical Communication*, June, 1951, pp. 95-102.

release free barium. Eisenstein regards barium-orthosilicate as the most important cause of the resistance.

To the writer it seems that Eisenstein's theory is more probable and contains fewer inconsistencies.

It is doubtful whether the resistance could be cured in the manufacturing process—and in any case every trial experiment would take many thousands of hours to complete, as can be seen from Fig. 1. This being so, it is worth while considering what can be done in the design of apparatus to reduce the effect of the resistance, on the assumption that all present valves have it and all future valves will have it, for an indefinite time ahead.

The known facts can be summed up by saying that within six months to two years running, valves will change from their initial state to a final state in which they have a cathode resistance shunted by a capacitance.

Remedy in Circuit Design

Measurements on valves in their final state suggest average figures of 40 ohm-square-centimetres for the resistance and 0.005 μ F per square centimetre for the capacitance. It has been verified that the resistance is linear up to a loading of 40mA per square centimetre. The resistance is temperature dependent, but as there is little difference between the cathode temperatures of one valve type and another, this need not concern the user.

The user will probably not know the coated area of the cathode of any particular type of valve, but he may estimate it from the rated heater power, on the basis of 3W per square centimetre.

The easiest way to deal with this problem is to concentrate on the two states of the valves: if the apparatus is satisfactory for both states, it seems a fair deduction that it would be satisfactory during the period of growth. The designer may proceed with a trial design, based on the valves in their new state. He then estimates the resistance and capacitance that will grow at each cathode and, by experiment or calculation, tests whether the design is still satisfactory.

It is hardly possible to give very general instructions on how to choose circuits that will prove satisfactory: each case must be considered on its merits. However, consideration suggests that a liberal use of feedback gives the best chance of success. The reason is that the feedback produced by the life-impedance depends on the valve's effective mutual conductance and a permanent feedback effectively reduces the mutual conductance. A rough rule is that the permanent feedback should swamp the life-impedance feedback.

Take, first of all, a rather simple case, a single valve used for Class A amplification at high radio frequencies. Since the life-resistance is adequately bypassed by the life-capacitance, it will cause no feedback, but will only alter the bias conditions. This is easily allowed for by using a cathode resistor large compared with the life-resistance to provide bias. This usually gives excess grid bias, so the grid is returned, not to earth, but to a positive point. By this very simple device the valve's running conditions can easily be kept almost the same for its two states.

Now consider an amplifier for audio frequencies. It is not likely that the valves for this service will show particularly large changes during life, as there is little need for a high ratio of mutual conductance to heater power. The feedback due to the life-impedance will be constant over the audio-frequency band. To reduce

distortion, it is customary to provide a strong feedback from the output of the amplifier to an early stage and this would probably swamp the life-feedback. It seems likely that little modification would be needed to most audio-frequency amplifiers to make them satisfactory.

It thus seems that where the application involves frequencies either very high or very low there should not be any great trouble. A more difficult case is the video-frequency amplifier, partly because the life-feedback then varies over the band and partly because the valves likely to be used are just those most susceptible to the effect.

Such amplifiers are normally required to have a flat frequency characteristic, and it is therefore necessary to compensate for their natural tendency to fall off at the higher frequencies. This is often done by increasing the effectiveness of the inter-stage coupling at the higher frequencies, but another way is to provide a frequency-dependent feedback, and this seems a better way for our present purpose.

Considering a single stage, the compensating feedback may be a resistance and capacitance in shunt in the cathode lead. Now there is usually a range of feedback for which the overall result is much the same, i.e., the same stage gain and frequency characteristic can be got by using high forward gain and high feedback or low forward gain and low feedback. It may thus be possible to swamp the life-feedback.

Where there are a number of stages, it must be considered whether to use feedback over several stages, at each stage, or a combination of both.

If great linearity is required in the input-output voltage characteristic, then feedback will be needed for this purpose. Such a requirement arises in multi-channel carrier amplifiers. For this case, it may prove best to use frequency-dependent feedback at each stage and frequency-constant feedback over the whole chain.

STANDARDS FOR DRY BATTERIES

A NEW British Standards specification, BS1766, dated 1951, recently issued, prescribes the dimensions and performance of dry batteries for use in domestic radio receivers. The performance tests recommended are for their use in a temperate climate, such as prevails in the United Kingdom, and will not be applicable to tropical or arctic conditions. The need for this specification has arisen as experience has shown that the provisions in BS397, "Leclanché-type Primary Cells and Batteries" do not fully meet the present-day requirements for domestic radio batteries. To avoid misunderstanding, definitions are given of the type of primary cell covered by the specification.

In the section devoted to tests it is laid down that for h.t. batteries the end-point, which determines the life of the battery, shall be at 55 per cent of the nominal voltage, and for l.t. batteries when the voltage per cell falls to 1.0V. An alternative of 1.1V is mentioned also.

Provisions are made, *inter alia*, regarding "shelf life" and the types of terminal connections, sockets and otherwise, to be used and their position.

Copies are obtainable from the British Standards Institution, 24, Victoria Street, London, S.W.1, and the price is 2s, including postage.

Oscilloscope "Hum"

Some Power-supply Troubles

By W. TUSTING

IN the course of constructing an oscilloscope the writer met with considerable difficulty from mains hum of a kind which is rarely referred to in print, and it is thought that an account of the steps which led to its removal may be of value to other experimenters. The difficulty arose out of the stray field of the mains transformer and, in spite of the presence of a well-made screen around the tube, an unwanted deflection of no less than 0.75 in was found! It is, of course, very well known that the leakage field of a mains transformer is liable to cause such an unwanted deflection and it is commonly stated that it is necessary either to space the transformer widely from the cathode-ray tube or to fit the tube with a mumetal screen. The phrasing usually adopted leads one to believe that if a mumetal screen is used the position of the transformer is unimportant. There is, too, an idea existing that all tube screens are mumetal or its equivalent.

The oscilloscope was built on the stripped chassis of an ANP4 Loran Indicator Unit using the 5CP1 tube of this unit with its screen. This tube is a 5-in type with a post-deflection accelerator. It is rated for 2kV on the final anode and an additional 2kV on the post-deflection electrode. However, in this instance the final anode and the post-deflection electrode were joined together and operated at a little under 2kV, since this was found to give adequate brightness.

An h.t. supply of some 350 V was needed for amplifiers, time bases, etc., and as a suitable transformer was available it was decided to take the e.h.t. supply from this also, through a voltage-multiplying circuit using metal rectifiers. This saved the provision of a separate e.h.t. transformer or, the alternative, re-winding the general transformer to include an e.h.t. winding.

The basic circuit of the power-supply unit is shown in Fig. 1 and is of a type discussed by A. H. B. Walker.¹ Since it was intended to use direct coupling between the amplifiers and the deflector plates the final anode of the tube had to be taken to a point about 250 volts above earth. The total voltage available for the tube is thus about 250 volts more than the output of the voltage-multiplying rectifier.

The chassis of the Indicator Unit takes the form of a steel tray of 2 in under-chassis depth. There is a steel front panel carrying the mounting for the front end of the tube and two upper sub-chassis. These are at about 1 in below the level of the tube axis and one on each side of it. They are shaped roughly to the tube contour on one side and have attached vertical pieces which bolt to the lower chassis. At the rear they carry the back tube mount. The tube has a metal screen fitting it which is quite elaborately and

solidly constructed. The general form of the chassis is sketched in Fig. 2.

In view of this screen no hum trouble was expected, but as a precaution the mains transformer was mounted as far from the tube as possible. A rectangular hole was cut in the lower chassis at the back and the transformer mounted beneath the chassis with only the upper half of the bobbin projecting through. The clearance between the bobbin and the underside of the c.r. tube was about 4 in.

Initially, the tube was operated at 1.75 kV and a vertical deflection of 0.75 in was found and was due solely to the external field of the mains transformer. It is very easy to determine whether or not a deflection is produced by a magnetic field. If the deflection is unaffected by rotating the tube it is due to a magnetic field, whereas if it rotates with the tube it is caused by a voltage on the deflector plates. Of course, if the screen around the tube is not symmetrical and it is rotated with the tube the pattern will vary somewhat even when only a magnetic field is present.

A spurious deflection of 0.75 in is, of course, intolerable. The most that could be allowed would be about 1 mm, and even this is too great.

Operation with no tube screen at all was tried. The deflection was then 1.35 in. The screen was thus giving only 2.5 db attenuation of the stray field and was, practically speaking, useless. A mumetal screen was then tried. This was one made for a VCR97 tube and did not fit the 5CP1 properly. However, it covered the tube from the base up to the side-con-

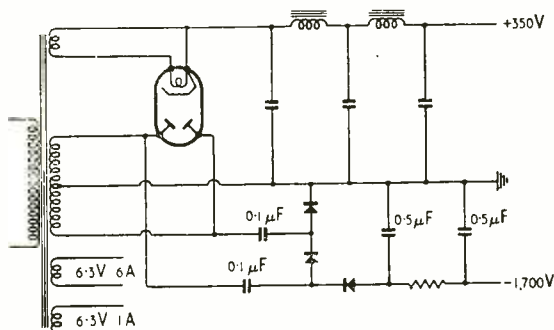


Fig. 1. Circuit of power supply unit.


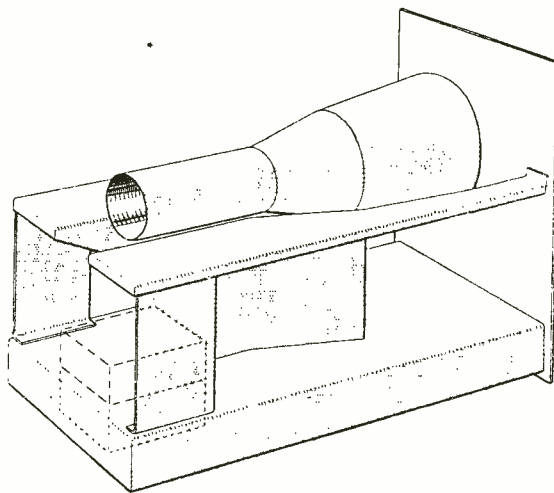
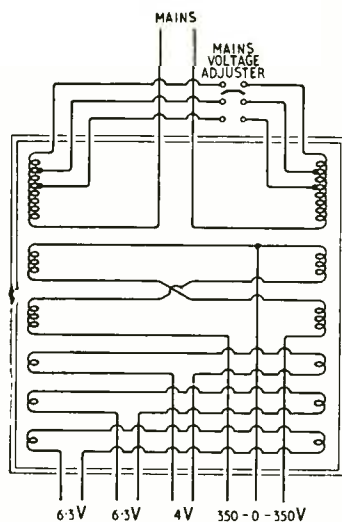


Fig. 2. General form of oscilloscope chassis.

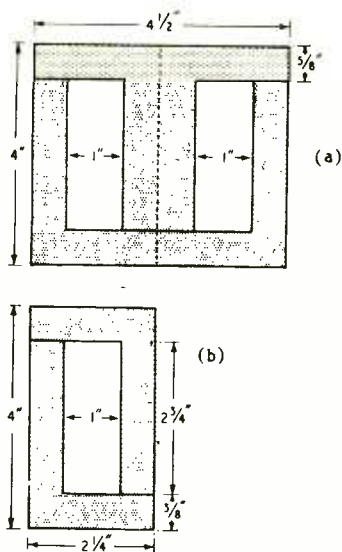¹ "Television E.H.T. Supply," *Wireless World*, April and May 1948, pp. 120 and 169



Left: Fig. 3. Transformer laminations (a) T and U pieces; (b) cut into L pieces. Right: Fig. 4. Connections of astatic transformer.

necter on the flare. This brought the deflection down to $\frac{1}{8}$ in only, making its attenuation about 23 db.

This screen is made in two pieces, as two half-cylinders with attached flares. The two halves overlap for about $\frac{1}{2}$ in, but it was found that the joints affected the screening and that the screening was best when the two joints were in the horizontal plane. This is reasonable, because with a vertical spurious deflection the magnetic field is horizontal.

The enormous difference between the two tube screens made it obvious that the original one was not mumetal at all, and that it was quite useless for screening against a 50-c/s field. A second mumetal screen was obtained and fitted outside the first one in the hope that the deflection would again be reduced by a factor of the same order. However, this merely gave an improvement of some 25 per cent and reduced the deflection to $\frac{3}{32}$ in.

There were indications that some field was passing through the unscreened part of the tube in front of its side-connector. A screen for this was, therefore, fabricated out of a VCR97 screen. This was cut with shears and a flare made from four overlapping pieces. These were held together by narrow strips of mumetal passed through pairs of holes and turned over, rather like the wire staples used for holding papers together. The new flare was held on to a normal VCR97 screen by six screws and nuts.

This screen gives almost complete coverage of the tube, save, perhaps, for an inch back from the screen. It is probably not as effective as one made for the job because of the number of joints. Also mumetal needs heat treatment after working. It was thought, however, that the small amount of gentle bending, cutting with shears and drilling which the metal received would not seriously affect its properties.

This new screen reduced the deflection to $\frac{1}{16}$ in, some 29 db less than that with no screen; the screen was 26.5 db better than the original one. This was a great improvement and brought the oscilloscope to the state of being usable although the deflection was still too great to be satisfactory. It was estimated that a further reduction by a factor of at least 5 was necessary.

In view of the fact that some other oscilloscopes were free from this trouble, in spite of there being no greater spacing between the tube and transformer, it was thought that the particular form of the chassis might be responsible. The two sub-chassis on either side of the tube were of steel and connected through vertical steel supports to the main chassis on either side of the transformer. The erection resembled a pair of pole pieces and it was thought that they might be acting as such. However, their complete removal and also the removal of the front panel made no measurable difference.

It was now evident that something would have to be done to the transformer. Experiment was made difficult by the fact that no alternative tube supply was available and, since trouble had not been expected, all the other components had been mounted on the chassis around the transformer.

The original mounting was with the laminations horizontal and in contact with the chassis, the core lying fore-and-aft. With some trouble the transformer was turned through a right angle so that the core lay across the chassis. The only effect of this was to turn the deflection from a vertical to a horizontal trace, the magnitude being hardly altered.

Transformer Stray Field

The puzzle of why this unwanted deflection did not occur in other oscilloscopes remained and one of them was examined in some detail. This oscilloscope had two transformers, one for the h.t. and the other for the e.h.t. supplies. They were similar in size and symmetrically disposed with regard to the tube. It occurred to the writer that their external magnetic fields might be in opposition in the region of the tube and the experiment of reversing the primary connections of one of the transformers was tried. This at once produced a spurious deflection of the same order of magnitude as that in the other equipment.

It is clear, therefore, that with transformers of normal construction it is better to use two than one and to pole their primaries so that their external fields are in opposition. It is clear, too, that for maximum effect the two transformers should be physically as alike as possible and have equal magnetizing currents, but the secondary turns need not be the same. The transformers should be mounted symmetrically with regard to the tube and as close together as possible.

The use of two transformers instead of one bigger one is definitely an advantage from the point of view of hum from their magnetic fields. Even with identical transformers, however, complete cancellation of the field cannot be obtained unless they occupy the same physical position and this is impossible.

In practice, the use of two identical transformers (identical save for their actual secondary turns) is inconvenient and usually takes up a great deal of space. If the transformers are dissimilar the hum reduction is less and their placing may be critical.

It is better, therefore, to use a so-called astatically wound transformer. This has a rectangular core with

a single window and is built up from L laminations instead of the usual T and U or E and I pieces. The windings are in two bobbins on opposite limbs of the core and all windings are split equally between the two. They are connected in series to be series-aiding around the core, but the external fields are in opposition.

The properties of such a transformer are obviously better than those of two ordinary ones because the two sets of windings can be much closer together. Moreover, the total volume required is less. It was decided, therefore, that the proper thing to do was to make an astatic transformer in spite of the labour involved. No suitable laminations were found in the lists—the nearest would have made the transformer at least an inch too big for the available space. It was decided, therefore, to use the existing laminations (M. & E. No. 60) cut in half. They are as shown in Fig. 3(a) and by cutting along the dotted line a set of L pieces (b) is obtained. The cut edges all come on the outside and so any irregularities do not affect the joint in the magnetic circuit.

The stack height is double that of the existing transformer so that the volume of iron is unchanged as are also the length of the magnetic path and the core area. The same turns per volt are thus needed for the same flux density in the core. The window area is unaltered, so that the same turns can be accommodated. However, with two bobbins instead of one there is rather more waste space needed for insulation between coils and between coils and the iron.

The existing bobbins had rather a large clearance between the outside of the coil and the iron, however, and being wound in sandwich form there was a lot of waste space from the end cheeks of sections. It was felt, therefore, that there would be no difficulty in accommodating the turns. The mean length of turn came out somewhat greater and was reflected by an increase of the copper losses. This would tend to increase the working temperature, but to offset this the surface area of the windings was rather greater.

The transformer was rewound on these lines, there being two identical bobbins with the primary on the inside and the h.t. secondary outside this and the l.t. windings outside the lot. The h.t. winding in each

bobbin was split into two sections. Since the two halves of a 350-0-350 V winding carry current alternately and not simultaneously a balance in the external field is only obtained if each half is split into two sections of which one is on each bobbin. (See Fig. 4.)

Both bobbins were wound identically and one was turned around in assembling them on the core so that the coils were in series-aiding when the outer of one winding on one bobbin was joined to the outer of the corresponding winding on the other bobbin.

From the point of view of stray field this transformer was completely successful. With the mumetal screen there was no observable deflection of the spot. Without any screen around the tube at all the deflection was only about $\frac{1}{2}$ in high.

The form of the hum on the screen was not the same with the two transformers, however. With the original one it took the form of a vertical or horizontal line according to the position of the transformer. With the astatically-wound component it formed a rectangle about 4 mm high and 1.5 mm wide. This is obviously due to two fields in different directions with a phase displacement between them, the rectangular picture being due to waveform distortion. The precise mechanism is a little obscure.

Taking the diagonal, 42.5 mm = 0.168 in, as a measure of the hum amplitude, the improvement due to the astatic transformer is $1.35/0.168 = 8$ times, or 18 db. As compared with the starting point a total improvement of 44.5 db in the hum level had been achieved—26.5 db from replacing the original tube screen by one of mumetal and 18 db by replacing the original transformer by one wound astatically. The hum deflection, which is too small to measure, should thus be 44.5 db below 0.75 in, or $0.75/168 = 0.0045$ in = 0.1 mm. This is considerably less than the spot size and is entirely satisfactory.

Although not strictly relevant to the subject of this article it may be worth mentioning that considerable difficulty was experienced from leakage between the heater winding for the c.r. tube and other windings. The full e.h.t. voltage exists between them and as the e.h.t. supply is of high impedance quite a small leakage reduces the voltage greatly. It was found essential to impregnate the windings to keep down the leakage.

MANUFACTURERS' LITERATURE

Ediswan Valve Manual in two loose-leaf books; Volume I for Mazda receiving valves and cathode-ray tubes, Volume 2 for transmitting, industrial and special types. Available from the Edison Swan Electric Co., Ltd., 155, Charing Cross Road, London, W.C.2, at 7s 6d complete.

Industrial Timers described in leaflets from Allied Electronics, Ltd., 28, Upper Richmond Road, Putney, London, S.W.15.

Holme Moss Mast; constructional details given in an illustrated brochure from British Insulated Callender's Construction Co., Ltd., 21, Bloomsbury Street, London, W.C.1.

Coin-operated Radio equipment for hotels, blocks of flats, etc., outlined briefly in a leaflet from Hadley Sound Equipments, Ltd., Cape Hill, Smethwick, Staffs.

Geiger Counter and **Oscilloscope** tubes; technical details in a leaflet from 20th Century Electronics, Ltd., Dunbar Works, Dunbar Street, West Norwood, London, S.E.27.

Quartz Crystals in evacuated glass envelopes; a leaflet giving brief details of the types made by Standard Telephones & Cables, Ltd., Connaught House, Aldwych, London, W.C.2.

Aluminium Wire data sheets in a folder from Aluminium Wire & Cable Co., Ltd., 37, Thurloe Street, South Kensington, London, S.W.7.

Time Switch with electrically wound spring giving eight hours' running, described in a leaflet from Venner Time Switches, Ltd., Kingston-By-Pass, New Malden, Surrey.

Soldering Irons and Crucibles, with elements claimed never to need replacement, described in a brochure from The Automatic Coil Winder & Electrical Equipment Co., Ltd., Winder House, Douglas Street, London, S.W.1.

Aerials for sound, television and car radio in a 1951-52 catalogue from Aerialite, Ltd., Castle Works, Stalybridge, Cheshire.

Meter Making illustrated in a booklet published to mark the Golden Jubilee of Everett Edgcombe & Co., Ltd., Colindale Works, London, N.W.9.

Car Aerial, telescopic turret type, described in a leaflet from E. K. Cole, Ltd., Ekco Works, Southend-on-Sea, Essex.

"How to Choose a Television Set," a booklet intended for non-technical would-be viewers, from The Edison Swan Electric Co. Ltd., 155, Charing Cross Road, London, W.C.2.

Electrolytic Capacitors

Principles of Operation and Some Recent Developments

By G. W. A. DUMMER, M.B.E., M.I.E.E.

IT is strange to think that it is nearly seventy years since the first electrolytic capacitor was made in Germany and nearly ninety years since the principle was first noticed. The outstanding advantage of the electrolytic capacitor is its large capacity in a small volume. Looking at a modern compact electrolytic capacitor, a capacity of $8\mu\text{F}$ at 450 volts (working) in a container $\frac{3}{4}$ in diameter and $2\frac{1}{4}$ in long seems incredible when the paper equivalent is considered, and

at low voltages the capacity comparison is many times greater. Even this does not compare with results now being obtained on new developments such as the tantalum electrolytic capacitor described later in this article.

The large capacity comes from the very thin film of dielectric used—of the order of 10^{-5} cm (or a few millionths of an inch). Capacity is determined by the well-known formula:

$$C = 0.0885 \frac{KA}{T} \mu\mu\text{F} \text{ (for a flat plate capacitor)}$$

where K = dielectric constant (about 12 for electrolytic capacitors)

A = area of one plate in sq cm.

T = distance between plates in cm.

Hence if T is very small the capacity will be very large. The method of making this thin film is by anodic oxidation. Certain metals, notably aluminium, tantalum, vanadium, magnesium, bismuth and antimony are readily coated with a film of dielectric by an electrolytic "forming" process. If an aluminium electrode is placed in a solution of ammonium borate and a constant voltage applied, the initial current will be high but will gradually drop as the dielectric film forms (see Fig. 1).

The forming process consists of the deposition of a thin film of aluminium oxide on the surface of the plate. In modern practice the anode foil enters a tank of electrolyte with a constant voltage applied and continues passing through the tank until the required thickness of film is produced.

The strength of the film is remarkable. A p.d. of 100 volts across a film of 10^{-5} cm represents a dielectric strength of 10 million volts per cm, which is beginning to approach the theoretical strength predicted by the ionic theory of crystals, which otherwise has never been approached in practice. The maximum capacity obtainable with a given anode surface area is inversely proportional to the voltage used in the forming process, i.e. the film thickness depends on the forming voltage. Low-voltage capacitors have thinner films and therefore a higher capacity/volume ratio than high-voltage capacitors. The thickest film is formed at about 600 volts, which sets a limit to the maximum working voltage obtainable of about 500 to 550 volts (at room temperature), as the working voltage is approximately 90 per cent of the forming voltage. Ripple voltage must be included in this where the capacitor is being used for rectifier smoothing. It can also be seen from this that the surge voltage is limited in this type of capacitor.

Present Types

There are three main types of dry electrolytic capacitor in use today, those using a plain foil anode.



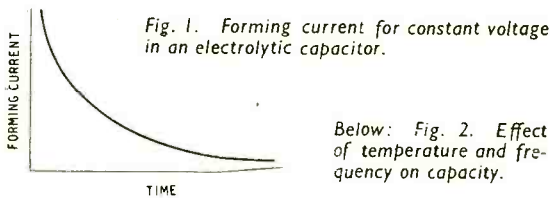


Fig. 1. Forming current for constant voltage in an electrolytic capacitor.

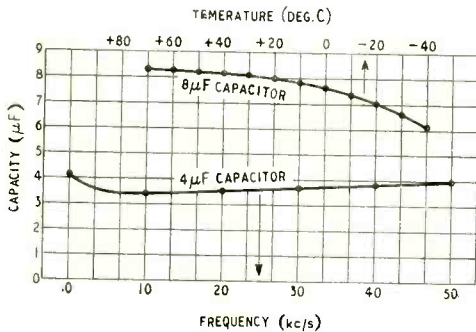Below: Fig. 2. Effect of temperature and frequency on capacity.



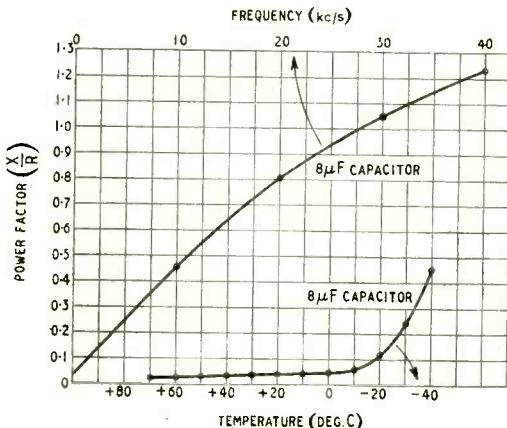Below: Fig. 3. Variation of power factor (ratio of reactance to parallel resistance) with temperature and frequency.



those with an etched foil anode and those with a sprayed gauze anode. The latter two have greater capacity in the same volume because the anode surface is roughened, thus providing greater area. The essential parts of an electrolytic capacitor are:—

1. The aluminium foil—Positive or anode.
2. The oxide film—Dielectric.
3. The electrolyte (usually a paste of glycol and ammonium tetraborate—Negative or cathode.
4. Spacers—Necessary to separate the negative electrode and anode film from direct contact.
5. A second aluminium foil—A contact electrode to the electrolyte.

A plain-foil dry electrolytic capacitor is made by first forming a coating of aluminium oxide on both sides of an aluminium foil about 0.002in thick. Two strips of aluminium foil are used (the formed foil as anode and the plain as contacting electrode for the electrolyte cathode) separated by two layers of porous paper soaked with electrolyte. This assembly is rolled up, the ends closed with wax and then sealed into a metal container.

Reversible electrolytic capacitors are also made by pre-forming both the aluminium foils and bringing out separate contacts. Each film is effective during the half-cycle that the other is ineffective.

The etched foil type is similar in construction, but the anode foil is mildly acid-etched before forming. This increases the surface area, and as the electrolyte is a paste it can adhere closely to the anode contour. It is essential to control the etching process closely so that "thin" spots are not left on the foil and also to ensure that no acid is left which might contaminate the foil.

The sprayed gauze anode type consists of a fine cotton gauze on which is sprayed pure aluminium from a metal spraying pistol. The effective area is still further increased by this method, but again careful control is needed.

The principal characteristics may be considered as:—

1. Capacity and the effect of temperature and frequency.
2. Power factor and the effect of temperature and frequency.
3. Leakage current and the effect of time, temperature and voltage.

Taking a typical capacitor, Fig. 2 shows the variation in capacity due to temperature and frequency. It is interesting to compare this curve with that given later for a tantalum capacitor (Fig. 6).

The safe working voltage of the capacitor is determined by the leakage current/voltage characteristic. It will be seen from Fig. 4 that the limit of safe working occurs at about 400/450 volts in this case. Over this voltage the leakage current rises rapidly and breakdown soon sets in.

The leakage current also increases with increase of temperature and becomes very large as breakdown is approached. The leakage current/temperature curve is similar in shape to the leakage current/voltage curve.

In general, the disadvantages of electrolytic capacitors may be summed up as the high power factor (about 10 times that of an average paper capacitor), the variation in capacity (selection tolerances of -20% to +50% of the nominal value may be possible) the small safety factor, and the high leakage current.

The great advantage of electrolytic capacitors is, of course, the very high capacity/volume ratio and for

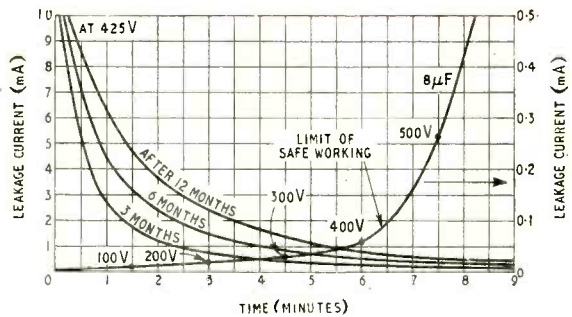


Fig. 4. Leakage current-variation with time and applied voltage.

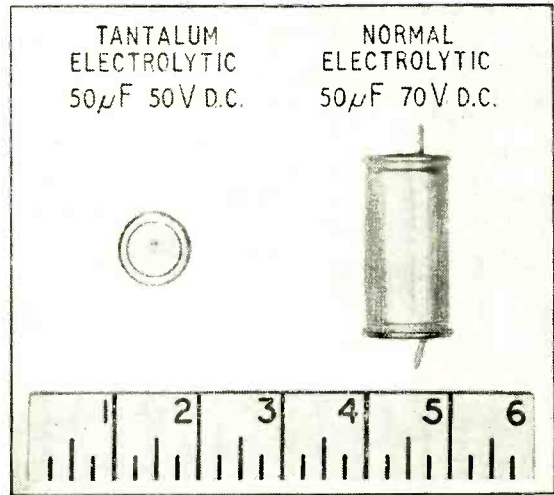


Fig. 5. Comparative size of conventional and tantalum electrolytic capacitors. (Plessey Company.)

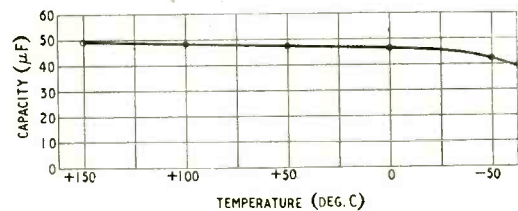


Fig. 6. Capacitance-temperature curve for the tantalum capacitor.

smoothing, decoupling and bypass capacitors this advantage may outweigh all the disadvantages.

New Developments

During the last few years considerable experimental work has been done in obtaining greater surface area on the anodes and on the use of new anode materials and new electrolytes. It has been known for some time that an increase in the purity of the aluminium foil used would improve the life of the capacitor, but the effect of the various impurities present in the metal has yet to be fully investigated.

One of the most promising new developments is the tantalum electrolytic capacitor. A photograph of one of the units is shown in Fig. 5 showing a comparison with a modern electrolytic capacitor of similar

capacity. The capacitor is made by vacuum sintering a capsule of pressed powdered tantalum and mounting it inside a silver cup containing sulphuric acid as electrolyte. These capacitors are therefore essentially "wet" electrolytic capacitors. The tantalum is the anode and the silver cup the cathode. The unit is sealed by pressing cathode and anode together over a ring of polytetrafluorethylene (P.T.F.E.), which serves as an insulating washer. P.T.F.E. is necessary owing to the very wide working temperature range of the capacitor, ordinary plastics would freeze or melt at the temperatures at which this capacitor is capable of working. The capacity/temperature characteristic is given in Fig. 6 and it is interesting to compare this with Fig. 2.

The power factor is approximately 0.08 and the leakage current is very small indeed, of the order of

10 μ A at room temperature. They should not normally need reforming during their life. The price of the capacitors will necessarily be high owing to the high cost of tantalum.

Dry tantalum capacitors (using tantalum in foil form) are now available commercially in the U.S.A. They are rated at 150 volts and are made in values from 0.02 μ F to 1.0 μ F. They are extremely small (1.0 μ F is $\frac{3}{8}$ in dia. by 1.0in long) and they have an operating temperature range of -55° to +85° C.

There is no doubt that both these capacitors represent an outstanding advance in technique, but it will be some time before prices become comparable with normal types, if ever! There are, however, occasions when extremely small, efficient and reliable capacitors must be used and it is in these fields that the tantalum capacitor will become indispensable.

PHONETIC ALPHABETS

IN view of the introduction by the International Civil Aviation Organization on November 1st of a new phonetic alphabet for use in aeronautical radiotelephony, we feel readers will be interested to be able to compare this with those used in the Services and that agreed at Atlantic City for the maritime mobile radio-telephone service.

The pronunciation of the words in the new word-spelling alphabet, which is the first listed below, is generally as in English, but, as is indicated by heavy type, in one or two cases the stressed syllable differs from normal practice. Where the pronunciation differs from normal English it is shown in parentheses.

This list replaces in civil aviation the well-known Able-Baker list (shown in the second column) which, incidentally, may still be used on request by aircraft until next October. It will be recalled that these spellings, which differ slightly from those used before 1939,

were employed by the Allied Forces during the war and have since been approved by the North Atlantic Treaty Organization. The Able-Baker list is, of course, that authorized for use between British ships and coast stations and, for that matter, all "wireless installations licensed by the P.M.G." It should be pointed out that the Atlantic City Convention permits stations of the same country to use "when communicating between themselves, any other table recognized by their administration."

There is also a third variation—that agreed at the 1947 Atlantic City Conference for international use in radiotelephony when it is necessary to verify a letter by analogy, and this is given in the last column.

One change from existing practice in the pronunciation of numbers is introduced in the new I.C.A.O. procedure. The number 3 is to be pronounced "tree" instead of "thuu-ree."

| | I.C.A.O. | Services | Atlantic Cy. |
|---|--------------------------|----------|--------------|
| A | Alfa | Able | Amsterdam |
| B | Bravo | Baker | Baltimore |
| C | Coca | Charlie | Casablanca |
| D | Delta | Dog | Danemark |
| E | Echo | Easy | Edison |
| F | Foxtrot | Fox | Florida |
| G | Golf | George | Gallipoli |
| H | Hotel | How | Havana |
| I | India | Item | Italia |
| J | Juliett | Jig | Jerusalem |
| K | Kilo (Kee-lo) | King | Kilogramme |
| L | Lima (Lee-ma) | Love | Liverpool |
| M | Metro | Mike | Madagascar |
| N | Nectar | Nan | New York |
| O | Oscar | Oboe | Oslo |
| P | Papa | Peter | Paris |
| Q | Quebec (Kibbeck) | Queen | Quebec |
| R | Romeo | Roger | Roma |
| S | Sierra (See-erra) | Sugar | Santiago |
| T | Tango | Tare | Tripoli |
| U | Union | Uncle | Upsala |
| V | Victor | Victor | Valencia |
| W | Whiskey | William | Washington |
| X | Extra | Xray | Xanthippe |
| Y | Yankee | Yoke | Yokohama |
| Z | Zulu | Zebra | Zurich |

TELESCRIBE IN CIVIL AVIATION

THE experimental air traffic control unit, established by the Ministry of Civil Aviation at London airport to try out new ideas in handling aircraft movement information, is investigating the possibilities of the Mullard Telescribe system for this purpose.

A rapid and accurate means of transmitting details of the movement of aircraft between units of a control organization such as exists at London airport is essential for the efficient operation. Owing to the density of air traffic, telephones are becoming too slow and alternative methods are being sought.

The advantage of the Telescribe is that written messages, printed matter, plans, photographs or sketches can be transmitted with equal facility to a distant point and reproduced on a cathode-ray tube, or tubes.

The material to be transmitted is written, or placed, on a sheet of glass which is scanned from below by a spot of light projected from a small c.r. tube in conjunction with an optical system. The light reflected from anything placed on the glass screen is picked up by a photocell, and the electrical signals produced are amplified and passed to the distant point where they are used to modulate a television-type receiving tube and so reproduce an exact replica of the original. Written messages are actually transmitted letter by letter as they are written on the glass. Speed and accuracy are assured. Synchronized, or common, time bases are used for both c.r. tubes.

Ring-ing-Choke E.H.T. Systems

Part 2 — Voltage Doublers and Regulators

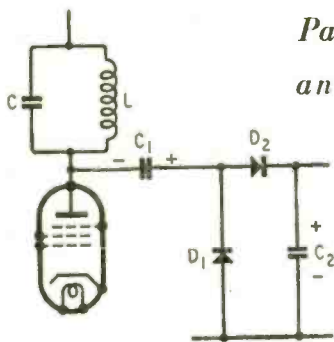


Fig. 6. Voltage-doubler rectifier connected to a ringing choke.

IT appeared in Part 1 that, using a half-wave rectifier and for a given required voltage regulation, the input power needed is proportional to the output power. When good basic regulation is required, the ratio of stored energy to output energy per cycle must be large. In addition, on account of the unavoidable circuit capacitance the stored energy is proportional to the square of the output voltage and at a high voltage may become greater than is necessary for the required regulation.

An economy of input power can then be achieved by using a voltage-multiplying rectifier. With a doubler, for instance, and the same circuit capacitance, the stored energy need be roughly one-quarter only of that with the half-wave rectifier. The regulation will, of course, be four times as bad, but this may or may not be important. If it is, a voltage-regulating circuit can be provided with any form of rectifier.

The use of a regulator has the advantage of permitting the design to be carried out for maximum economy without regard to the basic regulation. It is not suggested, however, that the use of a regulator is always necessary or advisable. It necessarily contains quite a few components and so increases not only the cost but the chances of a fault. If the basic regulation is nearly good enough, therefore, it may be better to improve it by increasing the input power.

The basic circuit of a doubler is shown in Fig. 6 connected to the ringing-choke circuit. As before, we assume that the rectifiers are perfect and that C_1 and C_2 are infinitely large; these capacitors are charged in operation to the steady voltages V_1 and V_2 with the polarities indicated on the diagram. As in Part 1, the peak voltage on the tuned circuit is V_m and the circuit has stored energy $W_s = \frac{1}{2}Li_p^2 = \frac{1}{2}CV_m^2$.

The right-hand side of the diode D_2 is above earth by V_2 . The left-hand side is above earth by the tuned-circuit voltage plus V_1 ; D_2 conducts when the two become equal; that is, when the voltage across C reaches $V_2 - V_1$. The energy then stored in C is $\frac{1}{2}C(V_2 - V_1)^2$ and so the energy lost by L to the capacitors of the rectifier circuit is

$$\frac{1}{2} C [V_m^2 - (V_2 - V_1)^2]$$

This is on the first positive half-cycle and C is left with energy $\frac{1}{2}C(V_2 - V_1)^2$ when D_2 ceases to conduct and the voltage falls because L has lost all its energy. The energy in C is transferred to the inductance and then back to C again, this time charging it negatively for the first negative half-cycle of oscillation. When

By W. T. COCKING, M.I.E.E.

the voltage reaches $-V_1$ the diode D_1 conducts. The energy then stored in C is $\frac{1}{2}CV_1^2$ and the energy in L , which is

$$\frac{1}{2}C[(V_2 - V_1)^2 - V_1^2]$$

passes to C_1 . The total energy passed to the reservoir capacitors is the sum of the two; that is,

$$\frac{1}{2}C(V_m^2 - V_1^2)$$

The load takes current i_o at voltage V_2 for the time τ , so we have

$$\frac{1}{2}C(V_m^2 - V_1^2) = i_o V_2 \tau$$


This leads to the expression

$$\frac{V_1}{V_m} = \sqrt{1 - \frac{W_o}{W_s}} \quad \dots \quad (7)$$

which is the same as equation (3) for the half-wave rectifier, except that V_1 is no longer the output voltage but is merely the voltage across C_1 . As before, W_o and W_s are the output and stored energies.

We have now to find the relation between V_2 and V_1 , or between V_2 and V_m , whichever is the more convenient. We do this by considering the charge q

Fig. 7. Variation of V_1/V_m , V_2/V_m with W_o/W_s . The curves for $\Delta V_1/V_m$ and $\Delta V_2/2V_m$ represent the fractional voltage regulation of V_1 and V_m . The curves for V_1 apply also to a half-wave rectifier.

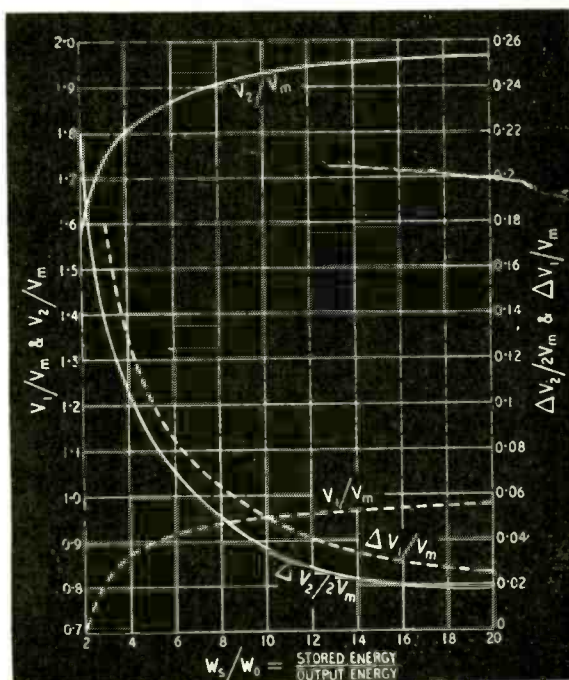

conveyed around the circuit. The energy supplied to C_1 is $\frac{1}{2}CV_2^2(1 - 2V_1/V_2)$ and is equal to qV_1 (see Appendix); therefore

$$q = \frac{1}{2}CV_2(V_2/V_1 - 2)$$

This charge is conveyed into C_1 when D_1 conducts and removed from it to C_2 when D_2 conducts. The load energy W_o is equal to the supply to C_2 and this is qV_2 and so

$$W_o = \frac{1}{2}CV_2^2(V_2/V_1 - 2)$$

Re-arranging and substituting from (7) we get

$$\frac{V_m^3}{V_2^3} \cdot \frac{W_o}{W_s} + 2 \frac{V_m}{V_2} - \frac{1}{\sqrt{1 - W_o/W_s}} = 0 \dots (8)$$

Being a cubic this equation is an awkward one and we cannot easily see the relation between $V_2/2V_m$ and W_o/W_s . However, if the latter term is very small the relation is approximately

$$\frac{V_2}{2V_m} = 1 + \frac{1}{2} \frac{W_o}{W_s} \dots \dots \dots (9)$$

so that on light loads the regulation is the same as that of the half-wave rectifier.

Voltage-Doubler Regulation

The precise relation of equation (10) is shown in Fig. 7, where the solid-line curves show $\Delta V_2/2V_m$ and V_2/V_m as functions of W_s/W_o , while the dotted-line curves show $\Delta V_1/V_m$ and V_1/V_m . These apply for the half-wave case and also for the voltage across C_1 for the doubler.

The term ΔV_2 is defined by the relation $V_2 + \Delta V_2 = 2V_m$ and represents the difference between the output voltages on load and on no load. Examination of these curves reveals what seems at first a surprising thing. The regulation of the doubler is better than that of the half-wave rectifier. The reason for this is that the energy is withdrawn from the tuned circuit during two half-cycles of oscillation instead of only during one. The regulation of the voltage V_1 across C_1 is precisely the same as in the half-wave case for it is fed from the tuned circuit under conditions dictated by the maximum energy loss. When D_2 conducts to transfer charge to C_2 , however, the tuned circuit has

to supply only part of the total energy and the regulation here depends on this part only and must be better than in the case of V_1 . The total regulation is therefore better.

Let us now see how the voltage-doubler fits into the design of a regulated supply for 10 kV at 100 μ A; as before, $\tau = 100 \mu$ sec and we aim at a regulation of 2%. Let us assume that without the regulator a regulation of 10% will suffice. Reference to Fig. 7 shows $W_s/W_o = 4.3$ and $V_2/V_m = 1.81$ while equation (7) gives $V_1/V_m = 0.88$.

At full load ($W_o = 10^{-4}$ joule) $V_m = 10/1.81 = 5.5$ kV and $V_1 = 4.84$ kV and the stored energy is $W_s = 4.3 \times 10^{-4}$ joule. The capacitance C should, therefore, be $2W_s/V_m^2 = 8.6 \times 10^{-4}/5.5^2 \times 10^6 = 2.86 \times 10^{-11}$ F = 28.6 pF. The inductance L is $2W_s/i_n^2 = 8.6 \times 10^{-4}/0.15^2 = 3.82 \times 10^{-2}$ H = 38.2 mH. Let us make $E_{HT} = 250$ V and taking 90 V for the minimum permissible anode voltage, we can make $E_L = 160$ V = Li_n/τ_c ; therefore,

$$\tau_c = 38.2 \times 0.15 \times 10^{-3}/160 = 3.59 \times 10^{-5} \text{ sec} = 35.9 \mu\text{sec.}$$

Therefore $i_a = 75 \times 35.9/100 = 26.9$ mA. The input power is $250 \times 0.0269 = 6.7$ W of which $6.7 - 4.3 = 2.4$ watts is anode dissipation in the valve.

These conditions are much more satisfactory than those for the half-wave rectifier. The capacitance needed is practically large and because of the lower value of V_m the input power needed is quite small. The regulation is poor, however, so that we now have to consider how a regulator may be provided to improve it.

For simplicity, we first of all consider the half-wave case, although most of what is said applies equally to the doubler.


One form of regulator is shown in Fig. 8 added to the circuit of Fig. 4. The coil L has an additional winding L_1 and ideally the voltage across L_1 is $1/m$ of the voltage across L . This voltage is applied to the diode V_2 which acts as a peak rectifier and produces across its load circuit R_2C_2 a mean voltage nearly equal to V_1/m . In polarity the voltage makes the diode anode negative to its cathode. This cathode is returned through L_1 to earth, but in practice it may be necessary to return it to some fixed point above or below earth to obtain the correct mean grid bias on V_1 .

The grid leak R_1 of V_1 is returned to the diode anode. Therefore, the grid-cathode voltage V_{gk} of V_1 is negative by V_1/m . Now V_1 depends on the load on the e.h.t. circuit. Increasing the load makes V_1 fall and as a result V_{gk} becomes less negative. If the input drive to V_1 is fixed, the instantaneous peak grid voltage also becomes less negative and the peak anode current rises. In its turn this increases the stored energy and so V_m . Although V_1 is still a smaller fraction of V_m than at a lighter load the increase of V_m makes the fall of V_1 smaller than it would be without the regulator. The circuit is in its essentials an a.g.c. circuit.

Now let us consider the precise effect of varying the grid bias on V_1 . In Fig 9(a) the lines v_0 and v_c represent the zero and the cut-off grid-bias voltages. If the input saw-tooth wave is ABC applied about a grid bias v_3 the valve conducts only for the period for which the wave is above the dotted line v_c and the peak current corresponds to B. The anode-current wave is shown in Fig. 9(b) by 1.

Now if the bias is reduced and becomes v_2 the whole grid-voltage wave is moved upwards in (a) and becomes DEF. The valve conducts for a longer period

Fig. 8. Half-wave rectifier circuit with the basic form of a voltage regulator.

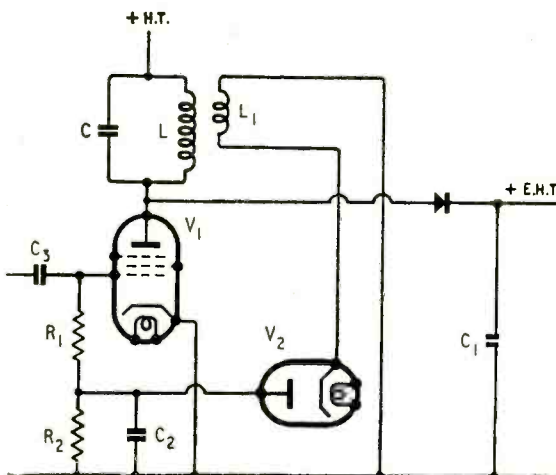

and the peak current at E is greater. The current wave in (b) is 2.

The mean anode current is $i_a = \frac{i_p \cdot \tau_c}{2 \cdot \tau}$ where i_p

is the peak current, τ_c is the conduction period and τ is the duration of one cycle of the input waveform. Because τ_c increases as well as i_p , i_a rises more quickly than either. In fact, τ_c is proportional to i_p and hence i_a is proportional to the square of i_p .

This goes on with reducing bias until the valve runs into grid current or bottoms or both. The first is shown by GHKL in Fig. 9(a) and the resulting anode current by 3 in (b). Once the flattening of the top of the current wave occurs no further reduction of bias can increase i_p and the regulator will cease to function. Reducing the bias then merely shifts the region of changing current to the left and increases the width of the flat top. The mean current, however, increases rapidly. If τ_1 and τ_2 represent the regions of increasing and constant current, the mean anode current is

$$i_a = \frac{i_p \cdot \tau_1}{2 \cdot \tau} + i_p \frac{\tau_2}{\tau}$$

Reducing the bias beyond a certain point thus has the effects of making the regulator cease working and making the anode current very large.

It is not difficult to work out the improvement due to the regulator. As before, let V_1 be the output voltage on full load, W_0 and W_s be the stored energy, while V_m is the peak voltage on no load with that same stored energy (that is, the no-load peak voltage without the regulator). The peak anode current will be i_p . On no load with the regulator in action let the output and peak voltages both be V_m' and the peak anode current i_p' . Let the mutual conductance of the valve be g_m , and let m be, not simply the turns ratio of the transformer, but the ratio of the peak voltage across C_1 to the regulator-diode mean output voltage. Ideally, this would be the same as the turns ratio, but in practice the value of m is always larger than the turns ratio, partly because of leakage inductance and partly because of rectifier losses.

The change of output voltage from no load to full load is $V_m' - V_1$ and this causes a change of regulator-diode output voltage of $-(V_m' - V_1)/m$ and this is the change of grid voltage. The resulting change of anode current is

$$i_p' - i_p = -g_m(V_m' - V_1)/m$$

Now $i_p = \sqrt{V_m \sqrt{C/L}} = V_1 \sqrt{C/L} / \sqrt{1 - W_0/W_s}$ and $i_p' = V_m' \sqrt{C/L}$.

Making the substitutions and collecting terms we get

$$\frac{V_1}{V_m'} = \frac{g_m + \sqrt{C/L}}{g_m + \sqrt{C/L} / \sqrt{1 - W_0/W_s}}$$

Let $\frac{V_m' - V_1}{V_m'} = \frac{\Delta V_1'}{V_m'} = 1 - \frac{V_1}{V_m'}$, and from equation

$$(3) \frac{V_1}{V_m'} = \sqrt{1 - \frac{W_0}{W_s}}$$

then $\frac{\Delta V_1'}{V_m'} = \frac{\Delta V_1}{V_m} \cdot \frac{1}{1 + g_m \sqrt{L/C} \left(1 - \frac{\Delta V_1}{V_m}\right) / m}$ (10)

The new regulation is equal to the old regulation

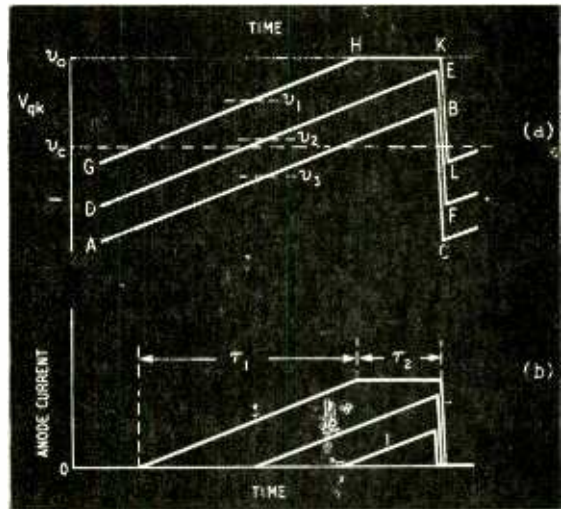


Fig. 9. The effect of varying the grid bias of the driving pentode is shown here. The relation between the driving wave and the cut-off voltage appears in (a) and the anode current waves in (b).

divided by the denominator of the second term. This term

$$1 + g_m \sqrt{L/C} \left(1 - \frac{\Delta V_1}{V_m}\right) / m \dots \dots (11)$$

is the improvement factor of the regulator.

For the doubler under the conditions developed earlier we have a basic regulation $\Delta V_1/V_m$ of 0.1 and we require the final regulation to be 0.02. The improvement factor is thus to be 5. So from (11)

$$m = \frac{g_m}{4 \sqrt{L/C}} (1 - 0.1)$$

which leads to $m = 8.3 g_m$ (mA/V). If g_m is 14 mA/V, therefore, $m = 112$.

The bias voltage developed by the regulator is thus $5100/112 = 45.6$ V on no load and $4840/112 = 43$ V on full load. The change of grid voltage is thus 2.6 volts.

Safety Devices

At this stage in a practical design it would be necessary to refer to the valve curves in order to determine the mean grid bias required. We found τ_c earlier to be 35.9 μ sec and as $i_p = 150$ mA, if we take $g_m = 14$ mA/V, the change of grid voltage during τ_c must be $15/14 = 10.7$ V. The peak-to-peak sawtooth input voltage needed is $10.7\tau/\tau_c = 10.7 \times 100/35.9 \approx 30$ V. From the valve curves the grid bias corresponding to i_p must be determined (say it is -4V). The mean bias must be this value plus one-half of the peak-to-peak input or -19 V.

The regulator develops -43 volts and so the diode circuit must be returned to $43 - 19 = 24$ volts positive to obtain the proper bias. The final arrangement is shown in Fig. 10. The positive bias is obtained from the potential divider R_3, R_4 and R_5 .

The cathode bias to V_1 and the diode V_{2B} are points that need explanation. They are safety devices and are not otherwise necessary. If they are omitted a failure in the drive to V_1 will result in the grid potential

of V_1 rising to about zero volts and the resulting anode current will be excessive. To counter this, the cathode-bias resistor R_1 is included to limit the current to a safe value if the grid rises to earth potential.

Since the regulator V_{2A} is returned to a point

TABLE 1

| | Calculated (1) | Measured (2) | Calculated and corrected for i_p (3) | Calculated and corrected for C (4) | Calculated and corrected for τ_c (5) |
|------------------------------|-------------------|-----------------|---|---------------------------------------|--|
| L (mH) | 63 | 63 | 63 | 63 | 63 |
| C (pF) | 36 | 40 | 36 | 40 | 40 |
| τ_c (μ sec) | 45.5 | 49.5 | 43.7 | 43.7 | 49.5 |
| i_p (mA) | 130 | 125 | 125 | 125 | 125 |
| i_a (mA) | 29.5 | 39 | 28.4 | 28.4 | 32.2 |
| V_0 (kV) at $i_0=100\mu A$ | 10 | 7.9 | 9.6 | 9.1 | 9.1 |

positive to earth it is necessary to include V_{2B} to prevent the grid of V_1 rising appreciably above earth if the drive fails. In normal operation V_{2B} is kept cut-off by the voltage developed across R_2 by the regulator.


The cathode-bias resistor has one adverse effect. It reduces the effective mutual conductance of V_1 in so far as the regulator action is concerned. If the resistor is $100\ \Omega$ and g_m is $14\ \text{mA/V}$ the effective value becomes $14/(1 + 14 \times 0.1) = 5.8\ \text{mA/V}$ only, so that m must be reduced to $1/2.4$ times; in the example from 112 to $112/2.4 = 47$. In its turn this affects the positive bias needed from R_1 .

As has already been pointed out, m is not the turns ratio of L to L_1 , and because of leakage inductance and rectifier efficiency the actual turns ratio may well have to be determined experimentally. If L is air-cored, and m is around 50 , the actual turns ratio may well be around $25:1$.

It should be pointed out that when a voltage-doubler is used the regulator diode should be so connected that it operates on the first *negative* half-cycle, since the amplitude of this is more affected by the load than that of the first positive half-cycle. With the circuit of Fig. 10, this is obtained if both windings are in the same direction and their starts are both made their earthy ends.

Reverting to the basic circuit itself, some measurements have been made in order to find out how well the very simplified theory given here agrees with actual practice. Close agreement cannot, of course, be expected. Some of the discrepancies are due, not to the method of calculation, but to the practical values being rather different from those assumed for the calculation. In Table 1, column 1 represents the

Fig. 10. Circuit of a practical ringing-choke e.h.t. unit with regulator and voltage doubler e.h.t. rectifier.

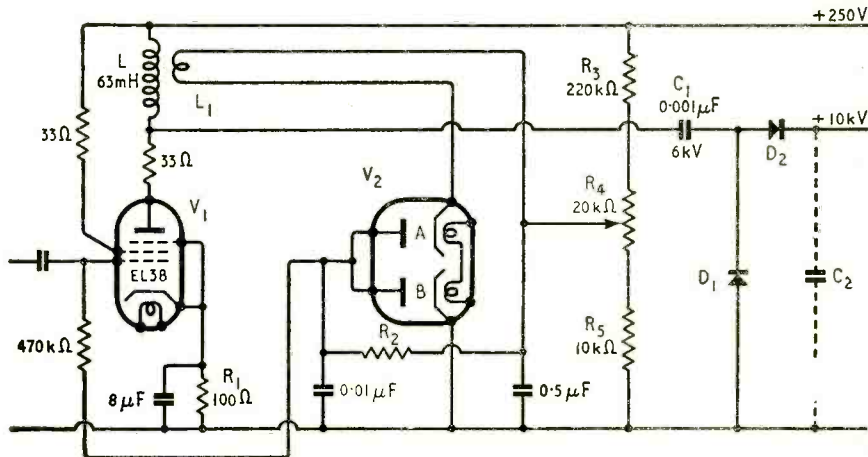

design figures, in which C was an initial guess. Column 2 represents the performance of the supply unit as built and the figures are, of course, subject to measurement errors.

As it turned out, the drive was not quite enough to provide $130\ \text{mA}$ peak current and it was rather difficult to increase it. Column 3 shows the figures of column 1 corrected for a peak current of $125\ \text{mA}$ only and column 4 shows them further corrected for the actual capacitance of $40\ \text{pF}$ instead of $36\ \text{pF}$. Column 5 shows a further correction for the practical value of τ_c .

The remaining discrepancies between measurement and calculation, columns 2 and 5, are only in i_a and V_0 . The current is in practice 17% higher than theory indicates and the voltage is 13% lower. The voltage agreement is remarkably good in view of the simplifications that have been made in calculation. The difference of current is more surprising, but may well be largely due to errors of measurement, for it is not easy to determine precisely the point at which the driving valve starts to conduct.

It should be noted that no attempt was made to adjust the drive and bias voltage of V_1 precisely. There is little doubt that had more drive and more bias been used τ_c would have been smaller and, in consequence, i_a would have been less.

On the basis of these results, and certain others which are not quoted here, it is considered that the method of design described in this article is a satisfactory one for practical purposes. In order to allow for losses in the coil and in the rectifier it seems that one should design for an output voltage about 15% greater than is actually needed.

APPENDIX

Let charge δQ be added to a capacitance C which already carries a charge Q , so that the charge becomes $Q + \delta Q$.

The initial potential difference is $V = Q/C$ and the final is $V + \delta V = (Q + \delta Q)/C$; therefore, $\delta V = \delta Q/C$.

The stored energy is initially $\frac{1}{2}QV$ and finally $\frac{1}{2}(Q + \delta Q)(V + \delta V)$.

$$= \frac{1}{2}(QV + Q\delta V + V\delta Q + \delta V\delta Q).$$

The increase of energy is, therefore,

$$W = \frac{1}{2}(Q\delta V + V\delta Q + \delta V\delta Q) \\ = \frac{1}{2}(CV\delta V + V\delta Q + \delta V\delta Q) \\ = \frac{1}{2}(2V\delta Q + \delta V\delta Q) \\ = \delta Q(V + \delta V/2)$$

$$\therefore \delta Q \approx W/V \text{ if } V \gg \delta V/2$$

When $C \rightarrow \infty$, $\delta V \rightarrow 0$ and so, if C is large enough, the relation $\delta Q = W/V$ holds for any magnitude of δQ , provided only that V is not itself infinitesimal.

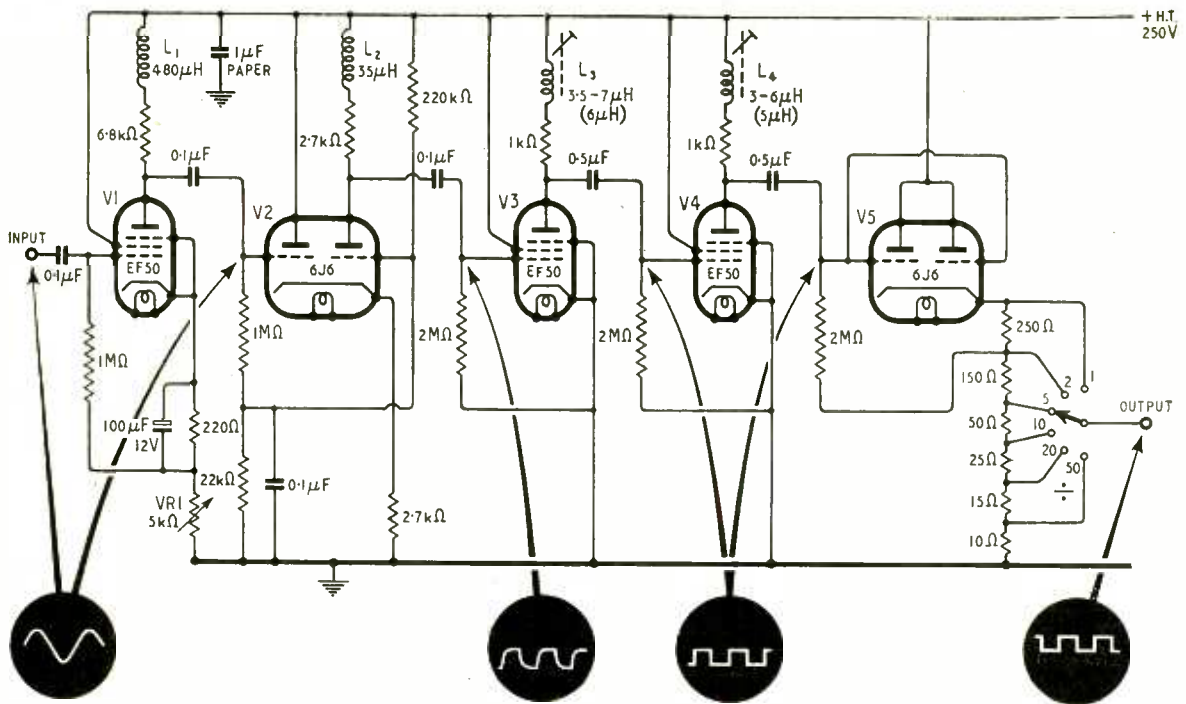


Fig. 1. Circuit of square-wave shaper, showing waveforms at various points.

Wide Range Square Wave Shaper

A Unit Giving Fast Rise Time for Video Amplifier Testing

By J. E. ATTEW

THE writer has recently designed a square wave generator for use in the testing of video amplifier chains for flying spot scanning experiments. The aim was to produce a square wave of frequency from 20c/s to 300kc/s at least, with as small a rise time as possible, and an output of approximately 10 volts peak-to-peak.

The first method tried was a multivibrator using pentodes, with a clipper stage, but this was found to be inconvenient in use, due to synchronizing troubles and to the large number of controls.

Finally it was decided to shape sine waves from an audio oscillator for low frequencies and from an r.f. signal generator for higher frequencies. This allowed precise frequency setting and there were only two controls.

The Circuit

In Fig. 1 the first valve V1 is a pre-amplifier with a gain of approximately 40 up to 1Mc/s. VR1 controls the output into V2, the squaring stage, which requires approximately 24 volts r.m.s. to produce a square wave of unity mark/space ratio, across the anode load. Choke L_2 is for high-frequency compensation. This method of squaring was described by J. McG.

Sowerby in *Wireless World*, August, 1948 issue. The output signal passes through two overdriven clipping stages V3 and V4, each progressively increasing the rise time. Both stages are shunt compensated for higher frequencies by chokes, which are of the value $L = mR_p^2 C_0$, where L = inductance in μH , R_p = anode load in $k\Omega$, C_0 = valve and circuit capacities across R_p , in pF and $m = 0.25$, a value which produces no overshoot but increases the high-frequency response by 1.4 times the original -3db value. These two chokes have been made adjustable to give precise settings and are adjusted to the value where no overshoot occurs at 500kc/s square wave output.

As $f_{-3\text{db}}$ is the frequency where the value of R_p equals the reactance of C_0 , and C_0 in the last stage is approximately 16pF (valve capacities + 10pF strays), then $f_{-3\text{db}}$ equals approximately 10Mc/s. and, with compensation, 14Mc/s.

$$\text{Rise time is given as } \nu = \frac{0.35}{f_{-3\text{db}}} \mu \text{ secs.}$$

$$\therefore \nu = \frac{0.35}{14} = 0.025 \mu \text{ secs.}$$

The measured rise time does approach this value,

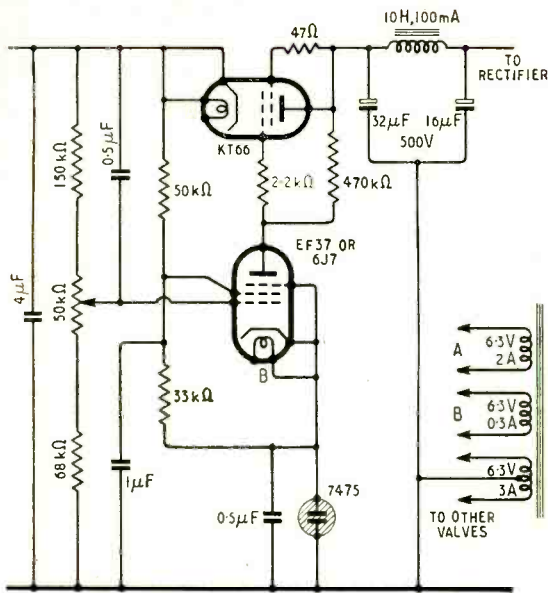


Fig. 2. Stabilizing section of power pack. Mains transformer, 350-0-350V, 80mA.

being of the order of 0.034; fall time 0.038, with 75pF across the output.

A cathode follower V6 consisting of a 6J6 with the two halves in parallel was used, as this combination gives a high mutual conductance of approximately 10mA/V (so a low output impedance) and a large initial current which preserves the decay or fall time of the square wave. If the cathode is looking into a comparatively large capacitive circuit, it may not follow the grid voltage when a rapidly increasing negative voltage is applied. The valve would then cut off, and the output time constant would be $R_k C_0$ and not $R_0 C_0$ (where R_k = cathode resistance, C_0 = capacity across output and R_0 = output impedance). Therefore, the decay time would increase. The rise

and fall times are approximately equal with this output circuit, and the output impedance is of the order of 85 ohms in maximum output position.

A step attenuator is fitted, the highest output impedance occurring in the $\div 2$ position, where it must be used with caution when producing high-frequency square waves if large circuit capacities to earth are present.

The low-frequency response is taken care of by large coupling time constants and a stabilized power supply (Fig. 2), so preventing any droop of the square wave. 20c/s square waves show negligible droop. The regulated power supply could possibly be replaced by a supply with a 10) to 200μF capacitor or more across the output, but this has not been tried.

L_3 and L_4 consist of 16-17 turns of 36 s.w.g. on an "Aladdin" former type F804 with dust core. L_2 consists of 55 turns of 36-38 s.w.g. on a $\frac{3}{8}$ in diameter former.

The final unit was built in the form of a strip similar to the vision chain of a television set. Screens were fitted between each stage across valveholders, and coupling components mounted on valveholder tags, as is good practice for wideband construction to keep circuit capacities to a minimum.

A particular make of condenser used to couple V3 to V4, produced a pronounced ringing effect at high frequencies, no doubt due to it having an inductive component. This, although it was marked N.I., was replaced by a more suitable type.

The required minimum input for a good square wave is 0.6 volt r.m.s., but the sensitivity could be increased by the addition of another stage similar to V1 between V1 and V2. Maximum output voltage is 11.5 volts peak-to-peak.

As a point of interest it is possible to produce a pulse output by replacing L_2 with a larger inductance, the repetition frequency being dependent on the input frequency, and the pulse width on the value of inductance.

The excellence of the square wave from the unit has been found more than adequate for the original purpose, and good square waves up to 1Mc/s can be produced.

CLUB NEWS

Brighton.—The programme for the December meetings of the Brighton & District Radio Club, which are held at the Eagle Inn, Gloucester Road, Brighton 1, on Tuesdays at 7.30, includes demonstrations of Pye telecommunication gear, by W. E. Rees, of Business Radio, Ltd., (December 4th) and of a home-constructed tape recorder. The club transmitter, G3EVE, is on the air on 80 metres c.w. one Tuesday a month. Sec.: R. T. Parsons, 14, Carlyle Avenue, Brighton 7, Sussex.

Cleckheaton.—"Police Radio" is the subject of the talk to be given by Supt. Dewhirst of the Bradford City Police to members of the Spen Valley Radio & Television Society on December 5th. The club meets at 7.30 on alternate Wednesdays at the Temperance Hall, Cleckheaton. Sec.: N. Pride, 100, Raikes Lane, Birstall, Nr. Leeds, Yorks.

Exeter.—Meetings of the Exeter Radio & Television Club (previously the Exeter & District Radio Society) are held on Thursdays at 7.30 in the Exeter Hobbies Association Hut, Haldon Road, Exeter. On December 6th the club will hold a servicing competition and on the 13th there will be a demonstrated talk on "The A.F. Amplifier Stage." Sec.: L. R. Jenkin, 16, South Avenue, Exeter, Devon.

Harrogate.—With the opening of the Holme Moss television station, it has been decided by the Harrogate Radio Society that at the monthly lecture meeting at the Y.M.C.A., the emphasis will be on television. Sec.: J. Coleby, 19, St Winifreds Avenue, Harrogate, Yorks.

Ilford.—At the December meeting of the Ilford & District Radio Society Mr. Pratt (Avo) will talk on "Instruments." Meetings are held every Thursday in St. Albans Church Hall, Albert Road, Ilford, at 8.0. Vice-president and Sec.: H. T. Stott, 10, Gordon Road, Chadwell Heath, Romford, Essex.

Two Calls—Details of the British Two-Call Club, membership of which is open to amateurs who have operated under an overseas call-sign and one in this country, are obtainable from G. V. Haylock (G2DHV), 63, Lewisham Hill, London, S.E.13.

World Friendship Society of Radio Amateurs will have an information stand at the exhibition, organized by Mullards, to be held at the Church Hall, Bellwood Road, Waverley Park, London, S.E.15, on December 1st. During the evening a selection of Mullard film-strips will be shown. Tickets are obtainable from A. H. Bird, G6AQ, 35, Bellwood Road, London, S.E.15.

Manufacturers' Products

New Equipment and Accessories for Radio and Electronics

Multi-range Meter

THE new multi-range meter produced by Taylor Electrical Instruments, model 77A, is notable for its good mechanical design and satisfying appearance. The movement is fitted with sprung jewels to give resistance to shock and postpone the onset of sticking and has been generally designed to reduce sluggishness—it has a sensitivity of 41 μ A. Silver-plated contacts are used in the single range-switch, which has a firm and definite action.

On the switch there are five voltage ranges (both both d.c. and a.c.), five d.c. current ranges, two resistance ranges going up to a maximum of 5 M Ω , and a position which puts an internal buzzer and battery in series with the test prods. There are also two extra d.c. ranges, 0-3,000 V and 0-15 A and provision for measuring a.c. output voltage.

The meter is available from the makers at 419-424, Montrose Avenue, Slough, Bucks, price £16.





Taylor multi-range meter

Television Signal Generator

THE thing that strikes one most about the new W90 television signal generator recently introduced by Waveforms, Ltd., is its unusual versatility. First of all it has two variable r.f. oscillators (40-70 Mc/s), one for vision and the other for sound, then both of these can be modulated in a variety of different ways. The v.f. modulation, which is available also at a separate output, has the usual sync and blanking pulses and provides eight different patterns which can themselves be combined to give complex patterns. In addition the complete sync waveform is brought out separately. The

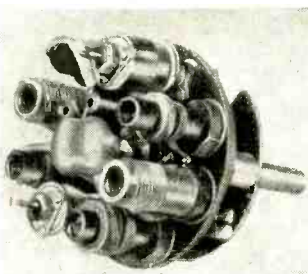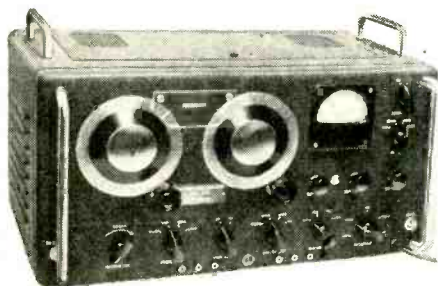Waveforms television signal generator and (right) miniature coil turret for 3-band superhet obtainable from Stern Radio.



r.f. output for sound can be internally modulated (400 c/s), externally modulated, or used without modulation. Each of the two outputs, vision and sound, has its own amplitude control but after the two are combined they go through a common stepped attenuator.

The W90 is available from the makers at 26, Oakleigh Road, New Southgate, London, N.11.

Miniature Coil Turrets

MORE than usual interest attaches to the introduction by Denco of a range of miniature coil turrets. This method of coil switching is probably the most efficient as unused coils are completely removed from the circuit.

These turrets measure 2 in in diameter and 1 $\frac{1}{2}$ in deep and are intended for use in small superhets. The type CT10 is for a 3-band receiver and it covers 150-410 kc/s, 520-1560 kc/s and 6-9 Mc/s respectively when tuned by a 2-gang capacitor of 534 pF and using an i.f. of 465 kc/s.

The other unit (type CT9) is also for a superhet and provides the choice of four pre-tuned stations, three in the medium and one in the long waveband.

Dust cored coils are used throughout with provision for inductance as well as capacitance trimming. Each turret is accompanied by full instructions for fitting, wiring and alignment, also by a circuit diagram of a suggested receiver. Alignment instructions are very well prepared.

The turrets are obtainable from Stern Radio, Ltd., 109-115, Fleet Street, London, E.C.4, and cost 52s for the CT10 and 39/6 for the CT9, including U.K. purchase tax.

New TRIX Quality SOUND EQUIPMENT



ENCLOSED RACK EQUIPMENT

For medium powered installations, incorporating 20 to 30 watt amplifier unit, radio receiver with monitor speaker, and gramophone unit. Provision for microphone input and multiple speaker matching.



HIGH FIDELITY MICROPHONE

Model G7808, moving coil type. New design, neat and unobtrusive, in die-cast alloy casing. Fitted with switch and plug and socket connection.

Send for latest catalogue and price lists of the Trix range of Sound Equipment.

THE TRIX ELECTRICAL CO. LTD.
1-5 Maple Place Tottenham Court Road,
London, W.1. Phone: MUSeum 5817.
Grams & Cables: "Trixadin, Wesdo, London"

AMPLIFIERS • MICROPHONES • LOUDSPEAKERS

RANDOM RADIATIONS

By "DIALLIST"

International Standardization

A READER TELLS ME that soon after reading my note on the lack of standardization that prevails even in mathematical signs he was able to ask a Danish friend about the use of \ominus for minus in his country. He confirmed that it was so used, but added that the practice was confined to text books (I've seen it in others, nevertheless) and that in the ordinary way Danes use "—" just as we do. The Danish division sign is a colon, which I have come across in French books as well. There is a relic of this in our old "rule of three" signs, for $3:4:6:8$ amounts to $3 \div 4 = 6 \div 8$. It seems queer that we cannot reach international agreement in a matter so apparently simple and straightforward as the signs associated with elementary arithmetic—but there it is. I am waiting for a reader to tell me that in the course of his travels in Yugotobrazia, or Lunibinia or some such land, he has found that \times indicates division, \div multiplication, $-$ addition, and $+$ subtraction! Do you know, by the way, how the plus sign was evolved? It was at first a handwriting sign, the cursive form of the printer's "ampersand" (and *per se* and), which was itself a contracted outline of the Latin *et*; the same sign, in fact, with a vertical downstroke and a looped cross-stroke that most of us use for "and" to save time in writing notes or letters. It was used by early mathematicians to mean "added to," and, when the printers came to setting their manuscripts in type, they evolved the $+$ sign to represent it.

Nation-wide Television

THOUGH WE HAVE HAD a regular television service for some fifteen years now (except for the wartime gap), it was a rather restricted one until Holme Moss came on the air. The population of these islands being concentrated, as it is, perhaps unfortunately, round the "Great Wen" of London, the Alexandra Palace station (of modest power by to-day's British standards) serves more than a quarter of our people. Sutton Coldfield added about another eighth of them and Holme Moss something like a further quarter to the total of

those within range of a television transmitter. Reception has thus become possible in about eight million homes. Though we had a lot of leeway to make good when the war ended, the problem has been so well and so energetically tackled that we have already achieved a television service which covers a higher percentage of homes than that of any other country.

Viewing Hours

WE CANNOT, of course, compete with the United States in the number of hours each day in which televiewing is possible, or in the matter of alternative programmes, but I am not at all sure that we should benefit greatly, could we do so. Take the question of alternative programmes. There seems to be only one way of making these available, by getting advertisers to sponsor them—and that, so the many American friends from whom I hear assure me, is a blessing so mixed that it ceases to be a blessing. Since, for a variety of reasons, a television programme costs many times as much as one of the "sound only" kind, there is no other way of providing them here at the present time (short of a £10 television receiving licence, which is unthinkable). And what of the number

of hours each day during which reception is possible? We must, I feel, realize that viewing by wireless is a much more expensive pastime than listening by wireless. Until a system has been invented and developed which uses receiving gear that is much less expensive to buy, operate and maintain, television reception must remain something of a luxury; that is why I do not feel that any great increase in the number of programme hours would be justified. Not everyone, though, will agree with that view!

Australia's "Pedal Wireless"

UNTIL I READ "Flying Doctor Calling," by E. Hill, I had not fully realized how vast a land Australia is (nearly as big as the whole of Europe this side of the Urals) or how completely isolated settlements can be in the "Outback." Or rather, how isolated they could be, until the advent of the pedal radio set. It was this transceiver, with its pedal-operated generator, that made it possible for the "flying doctor" service, founded by the Very Rev. John Flynn, O.B.E., to develop into the marvellous system which now covers all of those huge lonely tracts. Until quite recently, days or even weeks of travelling might be needed to reach the nearest place where medical help was available. Now any dweller in the outback who invests £40 or so in one of these sets and makes a landing-strip near his home has the flying doctor service available in emergencies com-



"WIRELESS WORLD" PUBLICATIONS

| | Net Price | By post |
|---|-----------|---------|
| FOUNDATIONS OF WIRELESS. M. G. Scroggie, B.Sc., M.I.E.E. Fifth Edition. | 12/6 | 13/- |
| RADIO VALVE DATA: Characteristics of 2,000 Valves and C.R. Tubes. 2nd Edition. | 3/6 | 3/10 |
| TELEVISION RECEIVING EQUIPMENT. W. T. Cocking, M.I.E.E. 3rd Edition. | 18/- | 18/8 |
| SHORT-WAVE RADIO AND THE IONOSPHERE. T. W. Bennington. 2nd Edition. | 10/6 | 10/10 |
| WIRELESS SERVICING MANUAL. W. T. Cocking, M.I.E.E. 8th Edition. | 12/6 | 12/11 |
| RADIO LABORATORY HANDBOOK. M. G. Scroggie, B.Sc., M.I.E.E. 5th Edition. | 15/- | 15/6 |
| BASIC MATHEMATICS FOR RADIO STUDENTS. F. M. Colebrook, B.Sc., D.I.C., A.C.G.I. 2nd Edition. | 10/6 | 10/10 |
| WILLIAMSON AMPLIFIER: Articles on Design of a High-quality Amplifier. | 3/6 | 3/9 |
| RADIO DATA CHARTS. R. T. Beatty, M.A., B.E., D.Sc., 5th Edition—revised by J. McG. Sowerby, B.A., M.I.E.E. | 7/6 | 7/11 |

A complete list of books is available on application

Obtainable from all leading booksellers or from

LIFFE & SONS LTD., Dorset House, Stamford Street, London. S.E.1.

pletely free of charge. The operator at the medical centre nearest his home listens for calls at a certain number of minutes past every hour of the twenty-four. Any urgent call is put through to the doctor, who tells the caller what immediate treatment he should give. "Got a landing-strip?" asks the doctor; "Good; I'll be with you about . . ." and he names a time. The flying doctor comes in an ambulance 'plane and within a few hours of the pedal wireless call the patient is lying in a comfortable hospital bed. A magnificent service. What a different world it would be if man always used wireless and the gifts that he receives from other branches of science for such worthy purposes!

Fine Abrasives

A KIND READER, who read my note a month or two ago on cleaning rotary switches of the leaf-contact type by treating them with fine abrasive paper, has sent me sheets of two grades of crocus paper and of rouge paper. It is invaluable not only for the job I described, but for cleaning up the travelling arms of wire-wound potentiometers and variable resistors, valve pins, the bared ends of fine wires, the tips of terminal binding screws and a whole lot of other electrical contacts which may give trouble by becoming dull or dirty. Other readers may care to have particulars of them, so here they are. The two crocus papers are made by Huber, of Paris. They are marked No. 1 and No. 2 and the latter is a good deal the finer. The rouge paper is made by W. Canning & Co., of Birmingham.


B.B.C. ACTIVITIES

UNDER the most favourable conditions the change [from m.w. to centimetre-wave broadcasting] must inevitably be gradual. But the sooner it can be begun the better," writes the Director-General in his article on the "Fourth Decade" in the "B.B.C. Yearbook, 1952."*

Among the articles of technical interest in the Yearbook are "Engineering Research," by H. T. Greator, "Television Goes Further Afield," by M. J. L. Pulling, and a review of the work of the Engineering Division. The Reference Section of the Yearbook will be found particularly useful giving, as it does, details of the services provided by the B.B.C.

* Published by the B.B.C., price 3/6.


Quality Switches

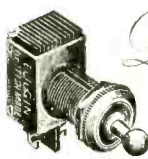


BULGIN Quality switches are known the world over for their reliability and long trouble-free life. They are robust and withstand shocks and rough usage that would damage many other types. The extensive range of Bulgin switches includes hundreds of different types, and Toggle and Lever action, push and pull, Key, Rotary and Semi-rotary types, Double and Single Pole.



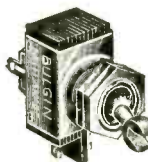
LIST No. S.400. Long-bush, single-pole Q.M.B. toggle-switch fitted with silver-plated solder-tags of new design making for easier and speedier soldering.



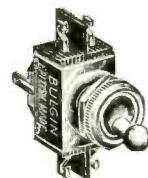
LIST No. S.467. Semi-Rotary switch, designed with long bush for uses where panel is of more than normal thickness. Many similar models available.



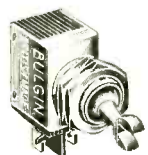LIST No. S.267/SD. Single-pole switch with slotted dolly. Ideal for use with time switches, record auto-changers, and many other mechanical operations.



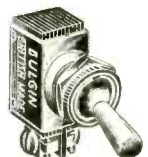LIST No. S.270. Double pole, compound roller-action, change-over switch. Designed for use with 6-250V. circuits, a.c. or d.c. Tested at 1,000 V. peak (-4 times working V.).




LIST No. S.263/SD. Long-internal-earth-path construction for low- Ω earthing. Fitted with slotted dolly for mechanical operation. Highest-grade insulation throughout.



LIST No. S.271/PD. Single-pole switch with pear dolly. Biased to off. Highly plated screw terminals for connection and best grade S.R.B.P. insulation.

LIST No. S.290. Low-voltage, low Ω , Q.M.B. Toggle switch, single-pole, change-over type. For all low-potential requirements, to ensure unfauling low- Ω circuiting.

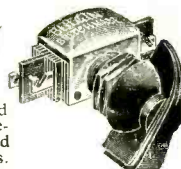LIST No. S.354. These famous snap-action Q.M.B. toggle switches have insulated leads for connections. With ball dolly as standard, but "pear" or "slotted" dollies are available to quantity orders.



LIST No. S.254. Semi-rotary switch, single-pole change-over type. Fitted with standard bush for panels up to 1/4 in. max. thickness. Many other models available.



LIST No. S.53. Heavy-duty Lever switch, suitable for all types of electrical appliances. Cadmium-plated steel frame with glazed porcelain body.




LIST No. MP.1-3. General-duty small push for "on" (spring-return) switch with 1 pole the fixing bush. Colour coded for easy identification.


LIST No. S.377. Lever-action Q.M.B. appliance switch, suitable for various electrical appliances, loads of 1-0.7 p.f. for 6-250V. circuits. Strong bakelite frame.



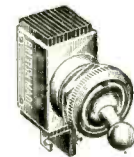LIST No. S.469. A new range of dust-proof single-pole switches of easy operation, for application especially on automobile circuits. 6-250 V. working.



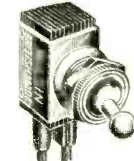LIST No. S.357. Change over type switch of the press button type, designed for use with refrigerators, cupboards, etc., for automatic change-over switching.



LIST No. S.259. Standard type switch for panels up to 3/16 in. thickness. Q.M.B. roller contact action. New style silver-plated solder-tags, highest grade insulation throughout.

★ SEND FOR NEW CATALOGUE No. 190 W.W. Price 1/- post free.

"The Choice of Critics"



regd. trade mark.

MANUFACTURERS OF RADIO AND ELECTRONIC COMPONENTS

BULGIN
Components

A. F. BULGIN & CO. LTD
BYE-PASS ROAD BARKING

TELEPHONE Ripplewa 3474 (5 lines)

UNBIASED

By FREE GRID

Cavalcade of P.A.

IT is a thousand pities that no attempt ever seems to be made by inventors and other pioneers to make some sort of public record when any particular thing is done and exactly what it is that is being done; if they did so the task of historians would be made so much easier. I have been endeavouring to piece together a history of radio and its offshoots and very hard going I have found it.

At present I am engaged on p.a. and let me forestall the flood of letters by saying that I am perfectly well aware that it is not an offshoot of radio but existed in the form of the megaphone long centuries before Marconi was born. But all the same, I intend to include it in my proposed history of radio, for nobody can deny that it is the a.f. technique developed by radio designers that has brought home to us the full horror of unbridled invention.

I am at the moment seeking to find out when and by whom p.a. was first used in an election and who first coined the term "Public Address." I am, of course, acquainted with the fact that regular broadcasting in this country began by the reading of election results on November 14th, 1922. I am aware, also, that a monstrous stentorphone, using air-blast technique in more senses than one, was installed long before that date on New Brighton Pier by one of our great dailies. It was, as a matter of fact, used in August, 1921, for election purposes—actually the choice of a Beauty Queen. I can personally vouch for the accuracy of this, as I was roped in as a member of the electoral college—at that time I had some reputation as a judge at fat



Election of a Beauty Queen.

stock shows. But my line of enquiry at present is directed to finding out when a parliamentary or municipal candidate first used a microphone, amplifier and loudspeaker to bludgeon his views into the addled and sound-drunk pates of his befuddled audience.

One of the pioneers in the use of p.a. for election purposes was, of course, Sir Ian Fraser, but I doubt if he was the first. I should be very surprised if p.a. were used even in rudimentary form in the General Election at the end of 1918, while I am quite sure it wasn't used in the previous one, which was at the end of 1910. Subsequent to 1918 we had general elections in 1922, 1923 and 1924, but don't forget the bye-elections. By 1928 p.a. was well established on a commercial basis and was extensively used in that year at a local election in St. Marylebone, as I well remember.

In the U.S.A. they used it much earlier than we did over here and I recall standing in Fulton Street, New York, in November, 1920, gaping in wonderment at the meaningless and mumbled mouthings coming from a loudspeaker which an interpreter informed me were in support of the presidential candidature of Harding; despite this handicap, he was elected by a large majority.

If, therefore, any of you know of any outstandingly early and well authenticated instances of the use of p.a. at an election in this country, I hope you will let me have them.

Receiver of the Future

DOES it ever occur to any of you what sort of broadcast receiver we shall all be using in a few years' time? Until recently I had seriously thought that we should all be back to the crystal set as, according to the modern disciples of James II, power cuts are going to get more and more severe as the years go on. It is quite useless thinking of the popular mains/battery set as a solution. The gaps in the power supply cannot be filled in that way, for the same "Dismal Jimmies" tell us that there will not be enough raw material to spare for making batteries in sufficient quantities for listeners' needs.

However, after reading the informative article by R. W. Hallows in the October issue, it is obvious that we are saved. It will only be necessary to get one of the battery reactivation units he mentions and



"Intelligent use of a tin-opener"


remove the gaseous sludge which gathers around the positive element and clogs up the works, thus bringing our dry cells to a premature end. Incidentally, I was surprised that he was content merely to hazard an intelligent guess at the *modus operandi* of this device and did not confirm it by the equally intelligent use of a tin opener, as, of course, I did immediately I read his article.

Of course, these "reactivators" cannot remain as untidy units outside our receivers; they must eventually become an integral part of set design. There must also be an automatic switch to put the batteries "on activation" for the correct period of time after each bout of listening. Such a device should not be a tame time-switch but should depend for its functioning on the internal resistance of the batteries and keep the latter coupled to the rejuvenator unit until this falls to the correct fraction of an ohm.

Transoceanic Jubilee

IT is exactly half a century (December 12th) since Marconi first spanned the Atlantic by wireless and was, for his pains, called by many an impractical visionary. He had been called that when he first mooted the idea in 1899. It is somewhat surprising, however, to learn that Sir William Preece, the famous Chief Engineer of the G.P.O., who had taken such a great practical interest in young Marconi's experiments and helped him so much, had little faith in the commercial future of the inventor's work.

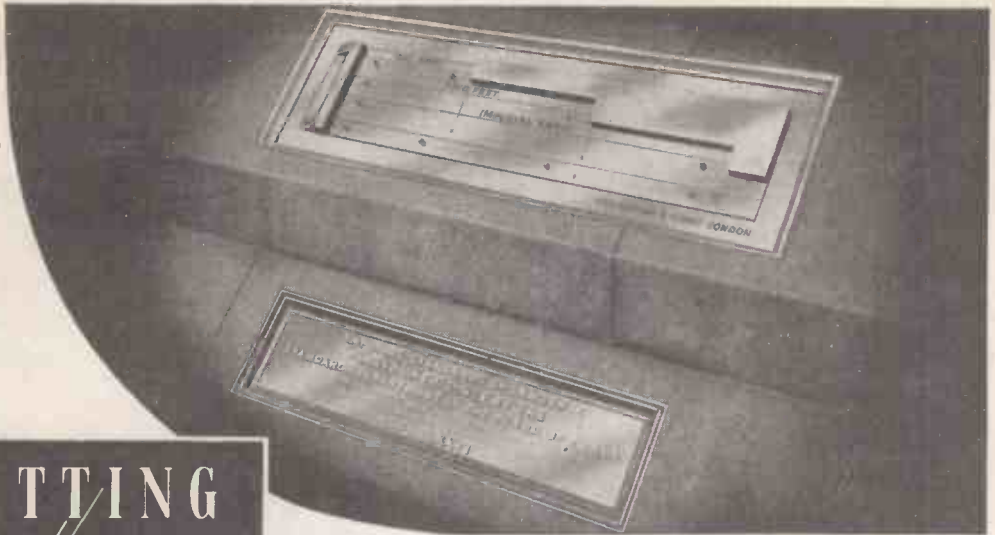According to the late R. D. Blumenfeld, one of the most famous figures in Fleet Street's Valhalla and an erstwhile editor of the *Daily Express*, Sir William Preece stated unequivocally that "Wireless telegraphy is not and cannot be a commercial success. It may be used under exceptional circumstances by the Army and Navy, but commercially it is impossible."



Imperial Standards of Length
— Trafalgar Square, London.

SETTING *the* STANDARD

In every branch of industry, in laboratories and scientific research establishments, in the services and, in fact, wherever electrical maintenance and measurement are of prime importance, "AVO" Electrical Testing Instruments maintain a reputation unexcelled for robustness and dependable accuracy. They are frequently used as a standard by which other instruments are judged.



AVOCET



The model 7 Universal AvoMeter is a typical example of a modern "AVO" multi-range meter. It is a combination AC/DC instrument providing on a 5-inch hand calibrated scale 50 ranges of readings of Current, Voltage, Resistance, Capacitance, Power Output and Decibels. The total resistance of the instrument is 500,000 ohms, and its small power consumption and precision accuracy make it the choice of radio, television, and electrical engineers throughout the world.

Write for a **FREE** copy of the Comprehensive Guide to "Avo" instruments

THE STANDARD OF *Dependable* ACCURACY



THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
WINDER HOUSE • DOUGLAS STREET • LONDON • S.W.1 • Telephone: VICTORIA 3404/9

GOODSELL

RECEIVERS AND HIGH-FIDELITY AMPLIFIERS

NOTE THESE FEATURES

- ★ Impregnated grid coupling condensers.
- ★ Paper Condensers on the H.T. supply line.
- ★ Matched or close tolerance resistors, where balance is important.
- ★ Steel chassis.
- ★ Model D.P.S. with separate H.T. supply incorporated on the same chassis for use with multi-stage pre-amplifiers.

Williamson Amplifier Type K.T.66 D.P.S. to specification. Illustrated is the dual power supply model with Partridge output transformers, large paper condensers and B.V.A. valves.

Price £32/10/-


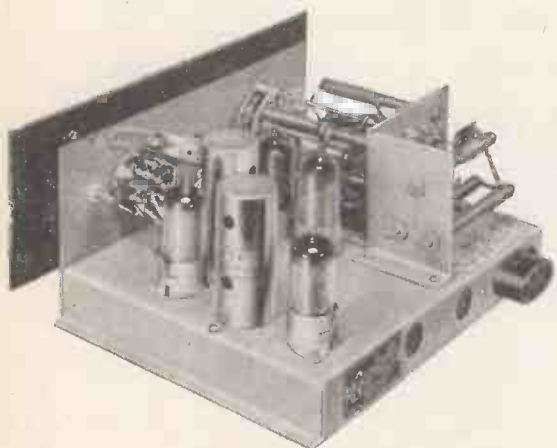


Illustration shows our Model SP2 Tuner Unit which includes such refinements as an R.F. stage, variable selectivity I.F. stage and a special high-quality detector. Valves—EF41, ECH42, EF41 and ECC40. Prices from £10/10/0 plus Tax.

For use with above equipment:—

Wide range four-stage tone control and equaliser for L.P. and Standard records, with microphone and radio input. Complete with engraved Perspex panel, £8/8/0.

With Low-pass filter, £11/11/0.

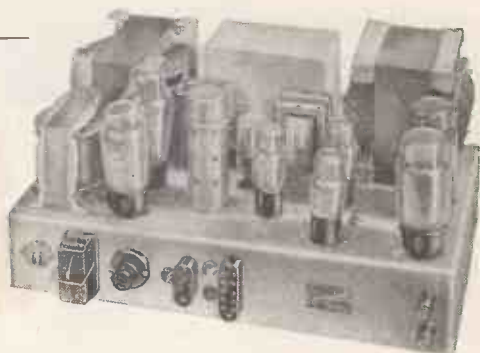

DEMONSTRATION ROOM AND SALES OFFICE

B.K. PARTNERS LTD., 229,231 Regent Street, W.1. (Sole Distributors for United Kingdom) Regent 1267

MANUFACTURED BY

GOODSELL LTD., 40 GARDNER STREET, BRIGHTON, 1

Phone: Brighton 2673

ACTUAL SIZE

A High-Slope Low-Noise R.F. Pentode with low power consumption



The combination of good slope to capacity ratio, low noise factor, and low power consumption makes this new Mullard R.F. pentode an ideal valve for use in all types of communications equipment operating at V.H.F. Its slope to capacity ratio approaches unity, and this makes it specially suitable for use in Wide Band Amplifiers.

Used as a neutralized triode, and followed by a grounded grid stage (cascode), the EF95 has a typical noise factor of 3.5 when operated at 180 Mc/s.

With a heater current of only 0.175A., this valve shows a large saving in power consumption over previous valves of a similar class. This saving in power is emphasized in applications where large numbers of R.F. stages are involved.

The EF95 has identical characteristics to the American 6AK5 and may be used as a direct replacement for this valve.

For full technical information on this and other valves in the Mullard range please write to the address below.

| | | | |
|------------------------|----------------|------------------------|-----------------|
| Heater | | Capacitances | |
| V_h | 6.3 V | C_{in} | 4.0 $\mu\mu F$ |
| I_h | 0.175 A | C_{out} | 2.8 $\mu\mu F$ |
| Characteristics | | C_{a-gl} | 0.02 $\mu\mu F$ |
| V_a | 120 V | Limiting Values | |
| V_{g2} | 120 V | V_a max. | 180 V |
| V_{g1} | -2.0 V | p_a max. | 1.7 W |
| I_a | 7.5 mA | V_{g2} max. | 140 V |
| I_{g2} | 2.5 mA | p_{g2} max. | 0.5 W |
| g_m | 5.0 mA/V | I_k max. | 18 mA |
| r_a | 0.34 $M\Omega$ | | |
| Base B7G | | | |



MULLARD LTD . COMMUNICATIONS AND INDUSTRIAL VALVE DEPARTMENT . CENTURY HOUSE . SHAFTESBURY AVENUE . LONDON . WC2


GOODMANS

**HIGH FIDELITY—12" P.M.
TWIN CONE AXIOM 150**

This 12" high fidelity unit has a twin curvilinear diaphragm, (Patent No. 451754). A carefully designed magnet assembly using anisotropic material provides a total flux of 158,000 maxwells on a 1 1/2" pole. The back centring device is a dustproof bakelised linen disc with concentric corrugations.

The combination of these features gives this precision-built instrument an outstandingly wide coverage from 40 to 15,000 c.p.s. free from bass modulation effects.

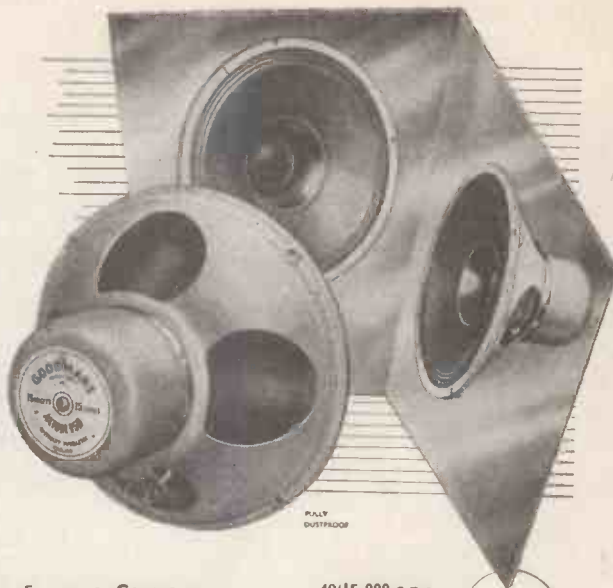An ideal high fidelity reproducer for the record enthusiast and the connoisseur of wide range musical reproduction, it gives exceptionally fine transient and frequency response.



Frequency Coverage 40/15,000 c.p.s.
Overall Diameter 12 1/2"-31.3 cms.
Overall Depth 6 1/8"-17.6 cms.
Fundamental Resonance 55 c.p.s.
Voice Coil Diameter 1 1/2"-4.4 cms.
Voice Coil Impedance 15 ohms at 400 c.p.s.
Maximum Power Capacity ... 15 Watts Peak A.C.
Flux Density 14,000 gauss
Net Weight 12 lbs. 13 oz.-5.8 kg.
Finish Grey Rivelling Enamel

£10.56
LIST



For use with this model we recommend Goodman's High Fidelity Heavy Duty Output Transformer Type H.4. Net Weight 5 lbs.—2.3 kg



A Bass Reflex Cabinet measuring approximately 30"x23"x16" and a corner cabinet have been specially designed for this loudspeaker and working drawings are available

GOODMANS INDUSTRIES LIMITED
Lancelot Road, Wembley, Middlesex. WEMBLEY 1200

MAGNETIC RECORDING MADE EASY!

Today, a great number of people own high-quality amplifiers capable of reproducing a frequency band far in excess of that required for tape recording. The Berry Magnetic Recording Amplifier Units MRU1 and 2, effectively convert existing amplifiers without internal modification to enable tape recording and playback to be done. Unit MRU3 is a complete recording amplifier.

Included in the units are a pre-amplifier with frequency-compensating networks and a 45 kc/s. oscillator providing the requisite bias and erase voltages at their correct amplitudes.

MRU1 UNIT. PRICE of complete kit of parts including full instructions, theoretical circuit, practical layouts, etc. Chassis size 8in. x 6in. x 2 1/2in. Power required from main amplifier 60 m/A. at 250 volts... **£9 0 0**

MRU2 UNIT. Identical in specification to the MRU1 with the addition of a power supply (200-250 volts A.C.) making this unit completely independent of the main amplifier. Chassis size 11in. x 6 1/2in. x 2 1/2in. PRICE of complete kit of parts including full instructions, etc. **£12 10 0**

MRU3 UNIT. For those who require a COMPLETE RECORDING AMPLIFIER this is available and comprises the MRU2 Unit with an additional two-stage amplifier on the same chassis (11in. x 6 1/2in. x 2 1/2in.) terminating in a 3.5 watt tetrode with negative feedback. PRICE of complete kit of parts including full instructions, etc. **£15 10 0**

A charge of five shillings is made for the complete instructions if sold separately to the kits but this amount will be refunded against purchases to the minimum value of Three pounds. List MTR1 contains full technical details of these kits and also information about available accessories for magnetic tape recording. It will be sent on receipt of threepence in stamps.

AMPLIFIERS

LEAK "Point One" **£27 7 0**
Pre-amp. **£9 9 0**
Tuner Unit. **£37 4 6**
ACOUSTICAL "QUAD" **£35 0 0**
Tuner Unit. **£26 0 0**
BERRY'S 10 w. 5 valve. **£15 15 0**

ARMSTRONG CHASSIS

EXP 73, 7 valves, 3 wave-bands. **£26 0 8**
EXP 125/3, 14 valves, 5 wave-bands **£53 0 10**

CRYSTALS

BROOKES & QCC **£1 12 6**

DENCO

Chassis mtg. coils. **3 9**

LABGEAR

Wide Band Couplers. **£1 1 0**
Transmitting coils all freq.

MICROPHONES

ACOS Xtal. **£6 6 0**
GRAMPIAN M.C. **£8 8 0**
RESLO Ribbon. **£7 10 0**
ROTHERMEL D.104. **£5 5 0**
TRIX M.C. **£8 0 0**
VITAVOX M.C. **£6 15 0**

MOTORS

CHANCERY Long Playing attach. **£3 12 6**
COLLARO and Pick-up. **£6 10 10**
CONNOISSEUR 2-speed. **£20 19 3**
DECCA 2-speed Rec. Plyr. **£12 1 6**
DECCA 3-speed motor. **£7 3 4**
PLESSEY 3-speed changer. **£23 13 0**

IN STOCK

"Q-MAX"

B4/40 Transmitter. **£75 0 0**
Chassis Cutters—all sizes.
Absorp. Wvmtr. **£1 15 0**
Grid Dip Oscillator. **£11 4 0**
"S" Meter. **£3 3 0**

RAYMART

Plug-in coils from 11-350 metres. Plain and ribbed formers.

SPEAKERS

BARKER 148a. **£15 15 0**
BARKER 150a. **£18 18 0**
GOODMAN 15in. **£18 10 0**
W.B. Con. Duplex 10in. **£6 6 0**
WHARFEDALE
Super 5CS/AL. **£4 12 6**
Super 8CS/AL. **£4 12 6**
Golden 10. **£5 2 6**
Super 12CS/AL. **£15 0 0**

TELEVISION

Full range of components for VIEWMASTER AND ELEC. ENG.

T.C.C.

Full range of Condensers.

WEARITE

All "P" Coils in stock. **3 0**

WILLIAMSON

All components available including precision resistors and condensers, and Partridge or Vortexion Output, and Mains Transformers, Chokes, etc.


Send sixpence in stamps for a copy of our General Catalogue giving details of many of our stock lines.

BERRY'S
(SHORT WAVE) LTD.

25, HIGH HOLBORN, LONDON, W.C.1
TEL: HOLBORN 6231

RELIABILITY SPECIFIED

for the

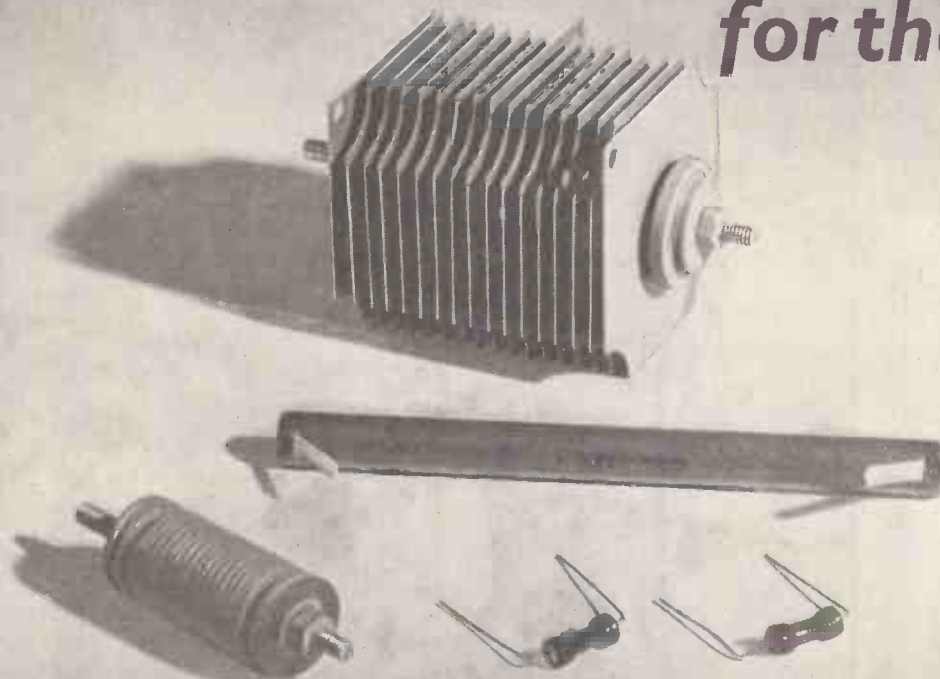

“VIEW MASTER”

MODEL ‘C’

FOR HOLME MOSS RECEPTION



METAL RECTIFIERS

Westinghouse metal rectifiers, because of their outstanding efficiency and reliability, are used extensively in commercial television receivers. It is little wonder, therefore, that they should be specified for the “View Master,” a receiver that incorporates only the best of components. The 14A86 for H.T. supply, 14D36 for H.T. boost and 36EHT100 for E.H.T. supply assembled with “Westalite” discs, and the “Westectors” WX3 and WX6 for sound and vision interference suppression containing the well-known copper-oxide elements, are the five rectifiers used in this easy-to-build television receiver. Send 5/- to the address below for an instruction envelope and build yourself a really good set.

DEPT. W.W.12

WESTINGHOUSE BRAKE & SIGNAL CO. LTD.
82 YORK WAY, KING'S CROSS, LONDON, N:1

That's why **MY**
TELEVISION IS
SO GOOD!



a **TELECRAFT**
AERIAL
of course!

" I insisted on TELECRAFT because I knew that it was designed and constructed by a team of engineers with 14 years practical experience in the design and erection of vision aerials.

"My dealer agreed with me, and added that quite apart from providing perfect television, a TELECRAFT AERIAL was a permanent fixture, being absolutely storm and weatherproof. . . ."

I always tell my friends, "Instal a TELECRAFT and see for yourself!"

There is a TELECRAFT AERIAL for every contingency—indoors or out.

BETTER THAN ANY—CHEAPER THAN MOST.

Ask your Dealer about TELECRAFT.

Contact your
 Dealer
 and insist on



Send for
 Descriptive
 Literature

THORNTON HEATH, SURREY

Tel. : THORnton Heath 1191-2-3.

Depots:—BIRMINGHAM,
 BRISTOL, MANCHESTER,
 WORTHING, STOKE-ON-TRENT,
 GLOUCESTER.

SCOTTISH ENQUIRIES :
 LOUIS GRACE, 28, Langside Place,
 Glasgow, S.1
 Langside 4633

The New

MAGNAVISTA

*Filtachromatic
 Television
 Lens*

**MORE TO SEE!
 MORE CAN SEE IT!**

Everyone gets a look in—and everyone sees more when you fit a Magnavista. Even the smallest sets give you **BIG PICTURE** enjoyment with this scientifically computed lens. You get daylight viewing too, and the filter inside the lens allows you to use a normal brilliance setting, and avoids overworking the tube.

There is a Magnavista model specially computed for every set—each one guaranteed for 12 months.

PRICES

There are over 18 different Magnavista models at prices ranging from £5/5/- upwards.


a product of

METROPEX LTD

42a DENMARK HILL, LONDON, S.E.5.

In Constant Demand

by **MUSIC LOVERS**
THE WORLD OVER

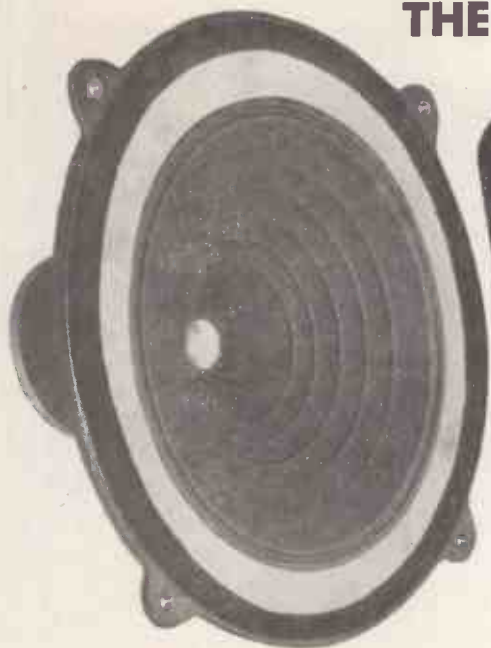

The **BAKERS 12"**
"TRIPLE CONE"
SPEAKER

| | |
|---|----------------------|
| Cone type..... | "Triple" |
| Effective cone dia..... | 9in. |
| Suspension | Cloth |
| Voice coil dia. | 1½in. |
| Coil impedance (to order) Standard..... | 15 ohms |
| Flux density | 15,000 lines sq. cm. |
| Frequency range | 20/15,000 c.p.s. |
| Natural resonance | 35 c.p.s. |
| Max. peak input | 10 watts |

Price £8 : 5 : 0



**EXPORT
 ENQUIRIES
 INVITED**

A few
 Overseas Agencies
 still open.

This amazing Reproducer, known the world over, requires little introduction. The unique diaphragm assembly is comprised of three cones which, used in conjunction with an extremely powerful magnet system, control completely the brilliant upper register down to the lowest note of the organ, with perfect ease. This enables a class of reproduction to be obtained which will delight and thrill the heart of every music lover. If you are not fully conversant with all the ingenious constructional details of this High Grade Reproducer, you should write without delay for Descriptive Leaflets—or better still call for an audition of: "BAKERS" SPEAKERS, RECEIVERS and AMPLIFIERS, the combination of which offers the highest possible QUALITY REPRODUCTION obtainable.

Also Available :

12" Single Cone and 18" Duplex Speakers, High Class Amplifiers and Receivers for Home use and Public Address.

A Limited Number of the Latest Type Record Changers and Players fitted with High Fidelity Pickups in stock.

BAKERS
'Selhurst'
RADIO

EQUITABLE HOUSE, Dingwall Rd., CROYDON. Telephone : CROYDON 2271/2

Pioneer Manufacturers of Moving Coil Speakers since 1925



The
EDDYSTONE "680X"
COMMUNICATION
RECEIVER

A high grade instrument fulfilling professional requirements

The model "680X" has been developed from the well-proven "680". The full vision straight line tuning scales are considerably increased in area. An improved vernier bandsread device is incorporated. The receiver uses a total of fifteen valves and gives a high performance over a continuous range of 30 megacycles to 480 kilocycles. Operation from AC mains 110 and 200/240 volts, 40/60 cycles.

An exceedingly durable polychromatic finish has been adopted for the exterior and some interior parts. Of robust construction and first-class workmanship throughout, the "680X" will give reliable service in any climate.

Please write for full specification to the manufacturers
STRATTON & CO. LTD., WEST HEATH, BIRMINGHAM 31



Precision **INSTRUMENTS**

SIFAM Portable Instruments

Moving Coil 6" Scale
Type M601.



Moving Coil 8" Scale
Type M801.

SIFAM Portable instruments are used by discriminating engineers. Their robust construction and high-grade finish ensure accurate readings for many years. All portable instruments are fitted with knife-edge pointers and mirror scales.

The case is mahogany, with wax polish finish.

Accuracy either B.S. First Grade or Sub-standard.

These portables are also available as Pyrometers, complete with external Thermo-couples to meet any special requirements.



● Write for Catalogue giving full details of the complete SIFAM range.

SIFAM ELECTRICAL INSTRUMENT CO. LTD., Leigh Court, Torquay.

Telephone 4547/8.



Twin-channel airfield racks


For Ground to Air V.H.F. R/T communication
and Ground Radio Links.

Remote control operation over telephone lines
is available for distances up to 15 miles.

A two-channel system is illustrated but additional
channels may be added as required.

All Pye V.H.F. equipment is fully tropicalised and
normally operates in the band 60-184 Mc/s.

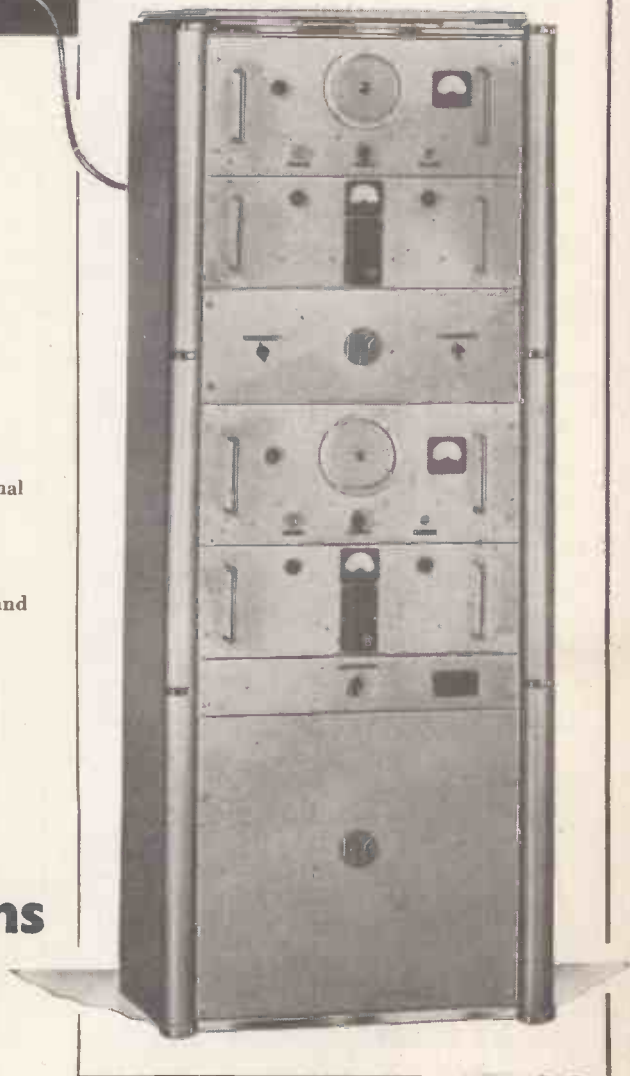Pye V.H.F. equipment is officially approved.



Telecommunications

CAMBRIDGE



ENGLAND

Overseas Enquiries to:—

EXPORT DEPARTMENT · PYE LIMITED · CAMBRIDGE · ENGLAND

ACE Radio Chassis

This range of High Quality Radio Chassis designed and built to exacting specification by skilled engineers is

now available from

**MAJOR
DISTRIBUTORS LTD.**

Model 600

9 valve, 9 waveband bandsread receiver covering the following ranges: 11, 13, 16, 19, 23, 31, 41 and 49 metre bands on 7 bandsread ranges. Also either medium wave 180-550 metres and long wave 800-2,000 metres, or medium wave and trawler band (60/150 metres). 10 watts push-pull output feeding twin 10in. speakers. Magic eye tuning indicator, employs Octal range of valves, RF stage on all bands. A.C. mains only **£36.2.4** 200/250.

Model T875

8 valve, 7 waveband bandsread receiver covering 11, 13, 16, 19, 23, 31, 41 and 49 metre bands on 5 bandsread ranges and medium and trawler bands in 2 ranges from 130.570 metres, no long wave. This receiver, by utilising the ingenious Ace selector system of splitting the medium band, gives a much better medium wave performance than that of competitive receivers covering 180/550 on the one band. Magic eye tuning indicator, push-pull output, 10 watts feeding twin 8in. speakers, employs the latest type miniature valves. A.C. **£28.17.8** mains only 110/250.

Model T845

8 valve, 4 waveband receiver covering 1,000/2,000 metres, 270/570 metres, 130/275 metres and 16/33 metres. Medium wave performance is similar to Model T875. 10 watts push-pull output feeding twin 8in. speakers. Magic eye tuning indicator, and employs the latest type miniature valves. A.C. mains only **£23.10.2** 110/250.

Model T675

6 valve, 7 waveband receiver, waveband coverage and specifications exactly as T875 except that push-pull output is not used and one 8in. speaker is employed. 3.5 watts output, A.C. mains only **£23.10.2** 110/250 v.

Model U675

Specification as Model T675 but for AC/DC mains operation, 200/250 volt. **£23.10.2**

Model T645

6 valve, 4 waveband receiver, waveband coverage and specifications exactly as Model T845 except that push-pull output is not used and one 8in. speaker is employed. 3.5 watts output. **£18.1.0**

Model U645

Specification as Model T645 but for AC/DC mains operation, 200/250 volt. **£18.1.0**

We can give immediate delivery on all of the above models.

All prices nett ex works, packing and transport extra

**MAJOR
DISTRIBUTORS LTD.**

TOWER WORKS, POUND LANE, LONDON, N.W.10
Telephone: WILlesden 8713.


PROFFITTS of BOLTON

The leading suppliers of Magnetic Recorders

MAGNETIC RECORDERS. The popularity of the magnetic recorder has enabled more and more manufacturers to produce and offer instruments of all types—and at widely differing prices. Before making a decision as to the type of machine you may require we would respectfully advise you to consult us—having had many years of experience in the recording sphere we are able to offer expert and unbiased advice; we do not stock and sell instruments unless they are thoroughly tested and eventually approved by us. May we, therefore solicit and look forward to the receipt of your esteemed enquiry? All letters answered by return mail.

A comparatively recent introduction this tape recorder represents most excellent value for money and the sound quality is really outstanding. Fitted in a beautifully constructed walnut veneer cabinet, highly polished, the recorder uses the standard plastic tape and gives 33 minutes playing or recording time at 7½ inches per second. A neon lamp modulation level indicator is provided and inputs for gram/radio and mike.

Simple to thread and operate—there are three controls only, viz.: **SOUND, VOLUME and MOTOR.** Erasure is accomplished with a permanent magnet. Sound output is approximately three watts. Price (exclusive of mike), £48, or £9/12/- deposit, 24 monthly payments of £1/15/6. A crystal mike is recommended for use with this recorder and can be supplied by us as an extra. Telephone attachments for recording two-way phone conversation, £3/3/- extra.

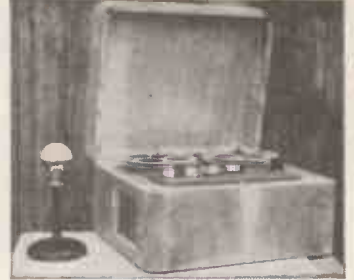

THE S.R. RECORDER.



THE SOUND-MIRROR RECORDER.

British enterprise gives you this really superb example of a quality recorder: note these attractive features: ● One single knob control provides for play/record, rewind (two positions), fast forward enabling any given recording on the tape to be selected with ease. ● Automatic erasure as each new recording is made. ● Perfect fidelity without scratch or extraneous noises. ● Frequency response 80 to 8,000 cycles, output 3½ watts in push-pull. ● 8 inch P.M. speaker. ● Magic eye modulation level indicator. ● Input channels for mike, gram. or radio. ● Power supply 200/250 A.C. only. (A six or twelve-volt rotary converter is available.) ● Crystal (Acos) omni-directional mike. ● Tone control. ● Separate panel controls for mike and gram. inputs. ● Simple threading and extremely quiet running.

PRICES. Standard model fitted in handsome polished veneer cabinet—a distinctive piece of furniture, £76/6/6, or deposit £15/5/3, balance 24 months. Portable model same tape deck and amplifier as above but with six-inch speaker and fitted in crocodile skin covered case with carrying handle, £86/6/6, or £17/5/3 deposit, balance 24 months. N.B.—Both the above prices include crystal mike and one reel of tape.

SCOPHONY BAIRD HOME RECORDER.

A self contained portable recording instrument of British manufacture using standard plastic tape. Special features:

● Simplicity of operation—us rewind, stop and forward drive for recording or play-back operated from one control. ● Very portable equipment contained in neatly designed carrying case weight 30lb., imitation crocodile skin covered, stowage for mike. ● Records through appropriate input channel from mike, radio or gram.—frequency response 50 to 5,000 cycles at 7½ inches per second. ● Output—about 8 watts in push-pull. ● Distortion less than 2% at maximum level.

● Power supply 200/250 A.C. only. ● Pea-nut input level indicator: red and green warning lights for recording and playback respectively.

PRICE. Inclusive of moving coil or crystal mike (as supplies permit) and one reel of tape, £58/5/6, or £11/13/- deposit balance 24 months. We are also stockists (when supplies are available) of the Simon, Clifton Wirek (Magnigraph) and other Recorders. Descriptive leaflets and information relative to our Easy Payment terms, with pleasure.

SPECIAL OFFER

ONE ONLY M.S.S. DISC RECORDER PORTABLE MODEL PR.6. Complete with separate speaker, amplifier and control panel, microphone, monitoring headphones, record blanks. A super recorder in brand new condition—offered at £210, or £42 deposit, balance 24 months.


R. W. PROFFITT LTD. (Radio and Electrical Engineers)

49/51 KNOWSLEY STREET, BOLTON

Phone: BOLTON 4422

Grams: ELECTRA, BOLTON

Valve book of the year!

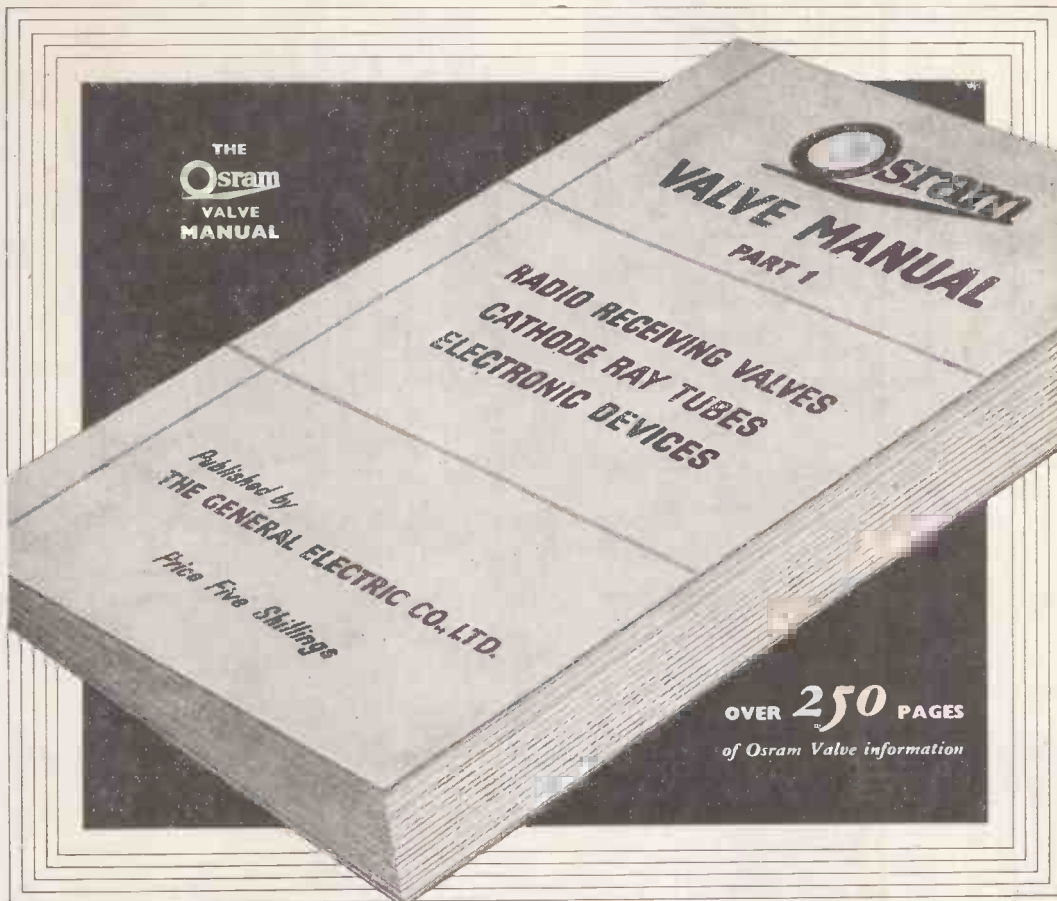

CHARACTERISTICS OF RECEIVING VALVES
ELECTRONIC DEVICES . CATHODE RAY TUBES
PHOTO CELLS . GERMANIUM CRYSTALS
COMPARATIVE AND REPLACEMENT TABLES
COMPREHENSIVE REFERENCE to G.E.C. television,
 radio and communication equipment with valve combinations.
TYPICAL VALVE CIRCUITS

PRICE

5/-

Plus 9d. for postage and packing.


Apply to your
radio retailer
for your copy.

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY LONDON, W.C.2.

Recognised as the Most Reliable Valveholders


Now in full production
NOVAL and B7G
 Valveholders
 of all types in
NYLON LOADED
BAKELITE

B9A-NOVAL

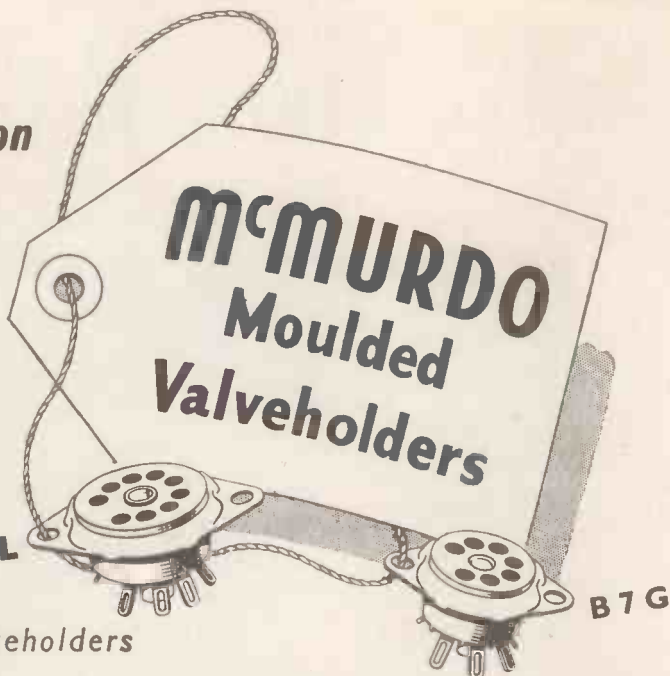

We make all types of Valveholders

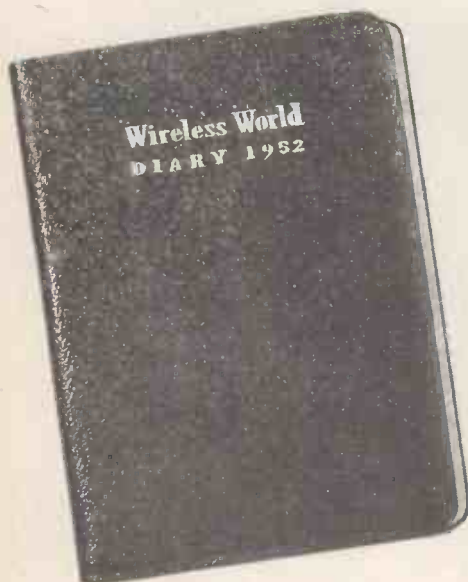Wholesale Enquiries:—CYRIL FRENCH LTD., HIGH STREET, HAMPTON WICK, MIDDLESEX · KIN. 2240
 Manufacturers' Enquiries:—THE McMURDO INSTRUMENT CO. LTD., VICTORIA WORKS, ASHTEAD, SURREY
 ASHTEAD 3401



A week-to-an-opening diary *PLUS*
 80 pages of reference material

Wireless World DIARY, 1952

The reference pages of this invaluable diary contain the kind of information that every reader of WIRELESS WORLD must have. Well produced, compact and easy to use, its data is essential to all who make, maintain and use radio and television equipment. Diary pages show one week to an opening, with ample space for notes.

Morocco grained leather : 6s. 1½d. (incl. P.T.)

Rexine : 4s. 3½d. (incl. P.T.)

Obtainable from all Bookseller and Stationers

ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD ST. S.E.1



CONTENTS INCLUDE: Formulae : Design Data ; Circuit Diagrams ; Valve Base Connections ; Licence Regulations ; Mathematical Signs ; Resistor and Capacitor Markings ; Wire Tables ; Waveband Classification ; International Organizations ; Abacs ; Standard Time, etc.

And now —
 the **Simphonic** TAPE RECORDER
 Model 1A



SIMPSONIC
 Recorders are used by:

- UNIVERSITIES
- SCHOOLS
- ELOCUTIONISTS
- HOSPITALS
- CLINICS
- RESEARCH LABORATORIES
- COMMERCIAL UNDERTAKINGS
- BUSINESS HOUSES
- RECORDING STUDIOS
- ACTORS, SINGERS & MUSICIANS

- TAPE SPEEDS
- RECORDING TRACKS
- PLAYING TIME
- FREQUENCY RESPONSE
- OUTPUT POWER
- OUTPUT IMPEDANCE
- LOUDSPEAKER
- INPUT CHANNELS
- POWER SUPPLY
- POWER CONSUMPTION
- SIZE AND WEIGHT

3½ and 7½ inches per second
 Two—side by side
 60 minutes per track at 3½ ins./sec.
 30 minutes per track at 7½ ins./sec.
 50 to 9,000 c/s. at 7½ ins./sec. ±2db.
 8 watts
 15 ohms. for external speaker
 6½ inch built-in monitor speaker
 High impedance for microphone
 Low or high impedance for radio
 200/250 volts 50 cycles A.C.
 100 watts approx.
 18 ins. x 15 ins. x 10 ins.—40 lbs. approx.

★ The well-known
SIMPSONIC MODEL 2B
 is still available for
 early delivery ★

SIMON SOUND SERVICE

RECORDER HOUSE, 48/50, GEORGE STREET, PORTMAN SQUARE, LONDON, W.1. ENG.

Telephone : Welbeck 2371 (5 lines). Telegrams : Simsale, Wesdo, London. Cables : Simsale, London,


H.F. CHANNELISED TRANSMITTERS

(H.C. 100 SERIES)

- ▶ **Output:** 400 watts for all transmissions.
- ▶ **Frequency Range:** 2 Mc/s to 27.5 Mc/s.
- ▶ **Transmission:**
Telephony, (high level modulation).
Telegraphy:—C.W. on/off. M.C.W.
Frequency Shift.

The Series comprises nine standard editions offering:—

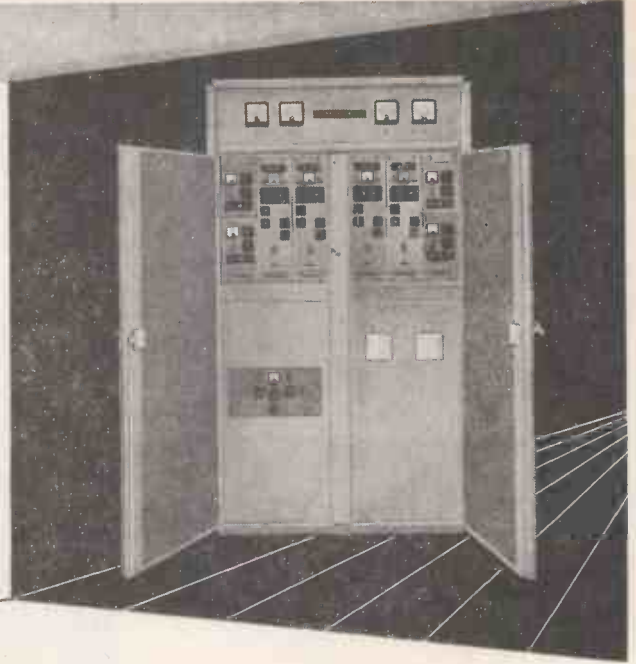
- ▶ **Simultaneous Operation** on 2, 3 or 4 pre-selected frequencies, depending on the types of transmission chosen.
- ▶ **Local or Remote Control** of each channel.



MARCONI COMMUNICATION SYSTEMS

SURVEYED · PLANNED · INSTALLED · MAINTAINED

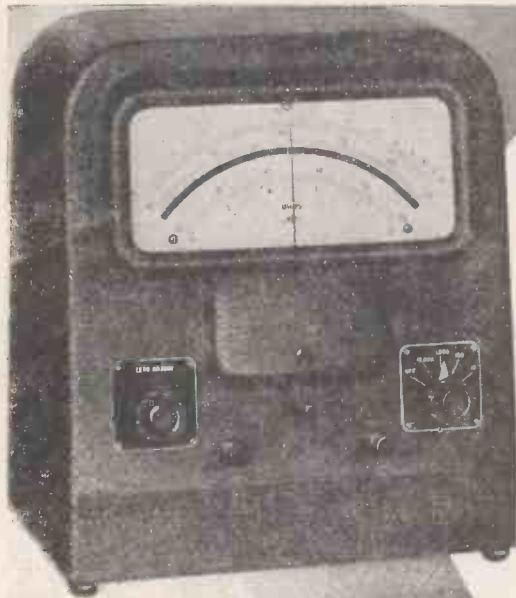MARCONI'S WIRELESS TELEGRAPH CO. LTD · MARCONI HOUSE · CHELMSFORD · ESSEX



Rapid

PRODUCTION TESTING

With its almost linear 8" scale the Pullin Bench Ohmmeter is the ideal instrument for rapid production testing of a wide range of resistance values.

A selector switch gives an immediate choice of 4 range-scales on the one instrument, 0-10, 0-100, 0-1,000, 0-10,000.

Calibration accuracy on all scales being plus or minus 1% full-scale deflection.

Pullin industrial bench type Ohmmeter gives accurate readings independent of supply voltage variations of plus or minus 20%.


**PULLIN BENCH TYPE
OHMMETER**
MEASURING INSTRUMENTS (PULLIN) LTD.

Electrin Works, Winchester Street, W.3.

Acorn 4651

A.T.M.


WIDE BAND MATCHING UNIT

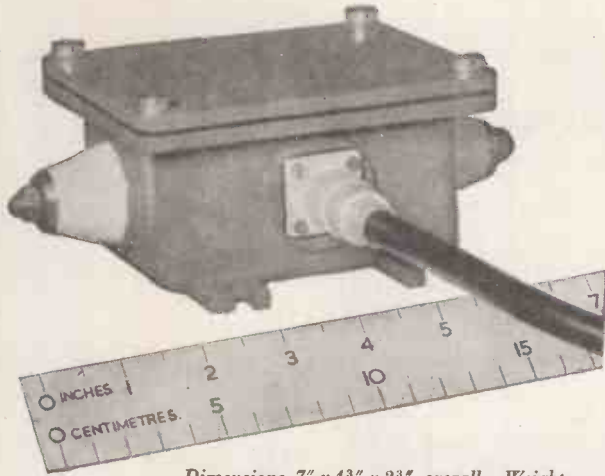

Dimensions 7" x 4½" x 2½" overall. Weight 4½ lb. approx. Construction complies with climatic and weather-proof requirements of the relevant Inter-Service specifications.

The "A.T.M." wide band matching unit is designed to meet the need for matching different impedances over an extensive frequency range. The type shown here is for matching a 600-ohm balanced open-wire feeder from a receiving aerial to a 75-ohm unbalanced coaxial cable. Alternative types can be provided for matching other impedance values, either balanced or unbalanced according to individual requirements. The units are compact and light in weight.

Please write for full details.

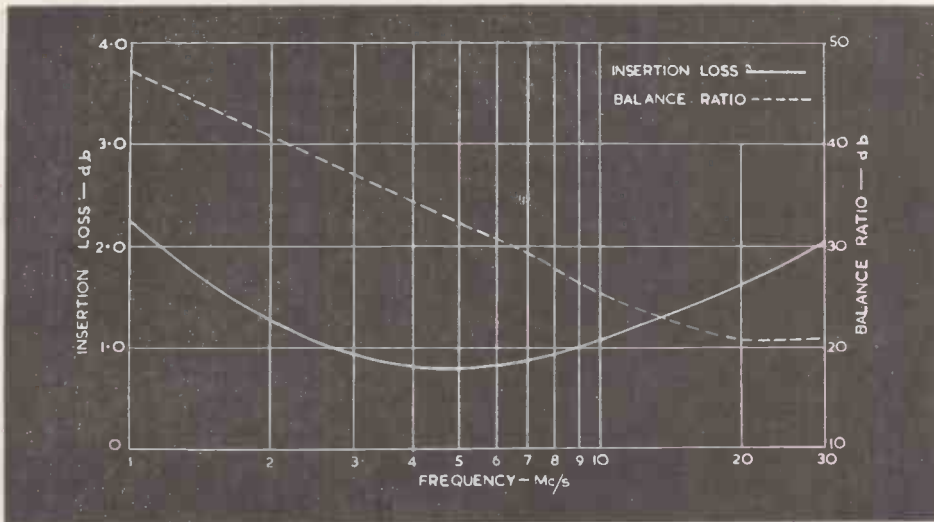

Characteristics of Wide Band Matching Transformer.
600Ω Balanced: 75Ω Unbalanced. Power rating: 1 watt.

AUTOMATIC TELEPHONE & ELECTRIC CO. LTD.

(RADIO & TRANSMISSION DIVISION)


Strowger House, Arundel Street, London, W.C.2

Telephone: TEMple Bar 9262

Telegrams: Strowgerex, London



**Three heads
are better
than one!**

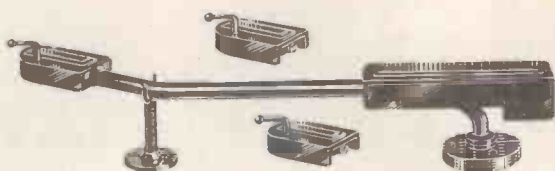

For Standard and Microgroove Recordings

Green Spot with .001" radius sapphire for micro-groove recordings.

Red Spot with .0025" radius sapphire for modern standard recordings.

Yellow Spot with .003" radius sapphire for older standard recordings.

These pickup heads are fitted with an easily replaceable armature system complete with a semi-permanent sapphire. Armature mass 20 mg.

Extremely low mass at needle point (4/5 mg. only), allowing for reduction in downward pressure to 10/12 grams for standard recordings and 7/9 grams for microgroove recordings.

Prices: With one head £4 10 0 plus £1 19 0 Purchase Tax. Extra heads each £2 10 0 plus £1.1 8 Purchase Tax. Spare armature system with sapphire 14/8 including tax.

Licensed under Letters Patent No. 586900 and/or 615424.


a **Connoisseur** *product*

Tel. : HALIFAX 69169.

Manufactured by A. R. SUGDEN & CO. (ENGINEERS) LTD., Well Green Lane, Brighouse, Yorks.

FREE!

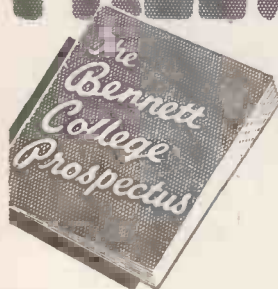to those who wish to Qualify in any of these subjects*



Now where does your career lie?

Applied Mechanics * Aviation—Engineering and Wireless * Book-keeping * Commercial Art Draughtsmanship—Electrical and Mechanical * Electrical Engineering—A.M.I.E.E. subjects * General Certificate of Education Journalism * Languages Mathematics * Mechanical Engineering—A.M.I.Mech.E. Physics * Plastics * Press Tool Work * Public Speaking * Radio Service Engineering * Salesmanship Telecommunications (C and G) Television * Viewers, Gaugers and Inspectors * Workshop Practice Works Management and many others

* BY POST, specialized Tutors in these and many other subjects give individual and understanding attention to Bennett College Students to whom Books are free. Tuition is guaranteed until you qualify. State your subject. Send coupon for prospectus as it applies to you.

This book costs you nothing. But it offers you success in terms of your career.

TEAR OUT


To the Governor, Dept. L41
The BENNETT COLLEGE
Sheffield, England. Send me the free book on how I can qualify in.....(subject)

NAME
ADDRESS
..... AGE (if under 21).....
PLEASE WRITE IN BLOCK LETTERS

You can start on a **BENNETT COURSE FOR ONLY 30/-** and monthly instalments of **15/-**

CELESTION

The Foremost Name in Sound Reproduction

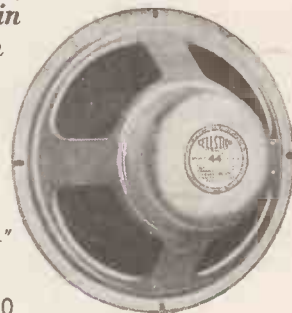


MODEL P44.

- Overall Diameter 12 $\frac{3}{16}$ "
- Voice Coil Impedance ohms 3.0
- Magnet Pole Diameter 1 $\frac{1}{2}$ "
- Flux Density (Gauss) 10,000
- Total Gap Flux (Maxwells) 60,000
- Peak Power Capacity 10W

The General Public should please order through their Local Dealers.

Manufacturers are invited to write for details of the full range of Celestion speakers.

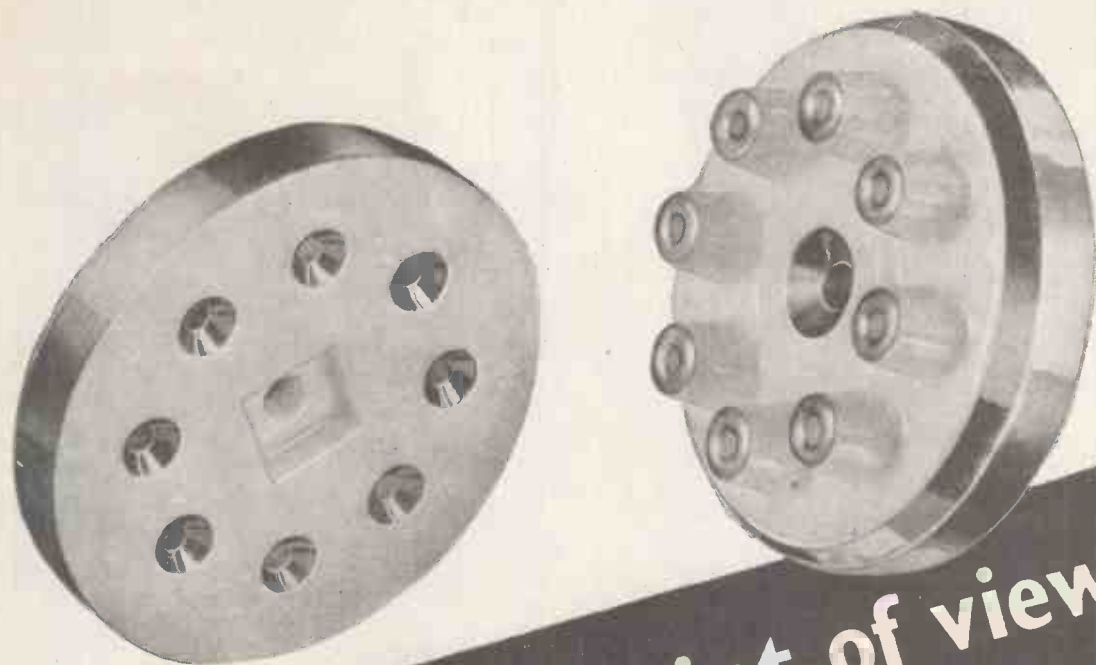ROLA CELESTION LIMITED,
SUMMER ROAD, THAMES DITTON, SURREY
Telephone : EMBERBROOK 3402-5



from every point of view



Frequentite is the most suitable insulating material for all high frequency applications. Seventeen years ago we introduced the first British-made low-loss ceramic, and consultation with us before finalising the design of new components is a wise precaution.

STEATITE & PORCELAIN PRODUCTS LTD.



Head Office : Stourport-on-Severn, Worcestershire. Telephone : Stourport III. Telegrams : Steatite, Stourport

S.P.72

MAINS TRANSFORMERS

FULLY INTERLEAVED. SCREENED AND IMPREGNATED. ALL GUARANTEED. ALL PRIMARIES ARE 200/250 v. Half Shrouded.

HSM63. (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps. 18/-
 HS63. Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps. 18/6
 HS40. Windings as above. 4 v. at 4 amps., 4 v. at 2 amps. 18/6

Output
 HS2. 250-0-250 v. 80 m/a. 21/-
 HS3. 350-0-350 v. 80 m/a. 21/-
 HS2X. 250-0-250 v. 100 m/a. HS75. 275-0-275 v. 100 m/a. 23/-
 HS30X. 300-0-300 v. 100 m/a. HS3X. 350-0-350 v. 100 m/a. 23/-

Fully Shrouded
 FSM63. (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps. 18/6

Output
 FS2. 250-0-250 v. 80 m/a. 23/-
 FS30. 300-0-300 v. 80 m/a. FS3. 350-0-350 v. 80 m/a. 23/-
 FS2X. 250-0-250 v. 100 m/a. FS75. 275-0-275 v. 100 m/a. 25/9
 FS30X. 300-0-300 v. 100 m/a. FS3X. 350-0-350 v. 100 m/a. 25/9

All the above have 6.3-4-0 v. at 4 amps., 5-4-0 v. at 2 amps.
 FS43. Output 425-0-425 v. 200 m/a., 6.3 v. 4 amps., C.T. 6.3 v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded 51/-

FS50. Output 450-0-450 v. 250 m/a., 6.3 v. 2 amps., C.T. 6.3 v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded 75/-

F30X. Output 300-0-300 v. 80 m/a., 6.3 v. 7 amps., 5 v. 2 amps. Framed. Flying leads 31/9

F35X. Output 350-0-350 v. 250 m/a., 6.3 v. 6 amps., 4 v. 8 amps., 4 v. 3 amps., 0-2-6.3 v. 2 amps. Fully shrouded 71/6

FS160X. Output 350-0-350 v. 160 m/a., 6.3 v. 6 amps., 6.3 v. 3 amps., 5 v. 3 amps. Fully shrouded 45/-

FS43X. Output 425-0-425 v. 250 m/a., 6.3 v. 6 amps., 6.3 v. 6 amps., 5 v. 3 amps. Fully shrouded 69/-

HS6. Output 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. For receiver RI355. Half shrouded 29/3

HS150. Output 350-0-350 v. 150 m/a., 6.3 v. 3 amps., C.T. 5 v. 3 amps. Half shrouded 30/9

F36. Output 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. Half shrouded 30/9

FS120. Output 350-0-350 v. 120 m/a., 6.3 v. 2 amps., C.T. 6.3 v. 2 amps., C.T. 5 v. 3 amps. Fully shrouded 33/-

FS256. Output 250-0-250 v. 80 m/a., 6.3 v. at 6 amps., 5 v. at 3 amps. Fully shrouded 30/9

PR1/1. Output 230 v. at 30 m/a., 6.3 v. at 1.5/2 amps. 23/-

FS150. 350-0-350 v. 150 m/a., 6.3 v. 4 amps., 5 v. 3 amps. 34/9

FS150X. Output 350-0-350 v. at 150 m/a., 6.3 v. at 2 amps., C.T. 6.3 v. at 2 amps., C.T. 5 v. at 3 amps. Fully shrouded 34/9

The above have inputs of 200/250 v.

FILAMENT TRANSFORMERS

F4. Output, 4 v. 2 amps. F6. Output, 6.3 v. 2 amps. 9/-
 F12X. Output, 12 v. at 1 amp. 9/- F6X. Output, 6.3 v. 0.3 amps. 6/-
 F12. Output, 12.6 v. tapped 6.3 v. at 3 amps. 18/6
 F24. Output, 24 v. tapped 12 v. at 3 amps. 26/-

F12 and F24 framed with Flying Leads
 FU6. Output, 0-2-4-4-6.3 v. at 2 amps. 11/-
 F29. Output, 0-2-4-5-6.3 v. at 4 amps. 20/9

FU6 and F29 clamped with Flying Leads.
 F5. Output, 6.3 v. at 10 amps. or 5 v. at 10 amps. or 12.6 v. at 5 amps. or 10 v. at 5 amps. 37/9

F6/4. Output, four at 6.3 v. tapped at 5 v. at 5 amps. per winding, giving by suitable series and parallel connections 24 v. at 5 amps., 20 v. at 5 amps., 18 v. at 5 amps., 15 v. at 5 amps., 12.6 v. at 10 amps., 10 v. at 10 amps., 6.3 v. at 20 amps., 5 v. at 20 amps. 57/-

F5 and F6/4 framed with Flying Leads.
 FU12. Output 0-4-6.3 v. 3 amps. FU24. Output 0-12-24 v. 1 amp 19/6

OUTPUT TRANSFORMERS

MOPI. Ratios 26, 46, 56, 66, 90, 120-1 50 m/a max. current. C.T. for Q.P.P. Class B., etc. Secondary 2/4 ohms. Top panel and clamped, each 6/-

OPI. Midget Power Pentode, ratios 30, 60, 90-1, 40 m/a. Secondary 2/3 ohms, each 4/-

OP2. Midget Pentode, ratios 45-1. Secondary 2/3 ohms, 40 m/a, per doz. 39/6

OP10. 10/15 watts output. 20 ratios on Full and Half primary OP30. 30 watts output, 20 ratios on Full and Half primary 19/9

Williamson's O.P. Transformer to Author's specification 28/5
 Chokes for Williamson's Amplifier. 30H. at 20 m/a 44/3/6
 10H. at 150 m/a 15/6
 Choke C4. 60 m/a, approx. 8H., 350 ohms 5/-
 Choke C5. 40 m/a, approx. 5H., 350 ohms 4/-
 Choke C6. 50 m/a, 50H., 1,500 ohms 22/-

CD. 360 Micro henries clamped, 5/3. C7 90 m/a, 180 ohms, clamped 6/3
 Belling-Lee Co-Axial Plugs. Type 642/F, each 1/3
 Belling-Lee Co-Axial Sockets. Type 604/S, each 1/3
 Quotations, etc.—stamped addressed envelope please.
 C.W.O. (add 1/3 in £ for carriage all orders over £2 carriage paid. Trade and also Export enquiries invited.

H. ASHWORTH (Dept. WW),
 676, Gt. Horton Road, Bradford, Yorks.

Make "PYROBIT"

ELECTRIC SOLDERING IRONS

Your CHOICE


THEY ARE USED BY EXPERTS ALL OVER THE WORLD!



Delivery from Stock, ask for Leaflet

The ACRU ELECTRIC TOOL MFG. Co. Ltd.
 123 Hyde Road, ARDWICK, MANCHESTER

Have you "A.A."?*

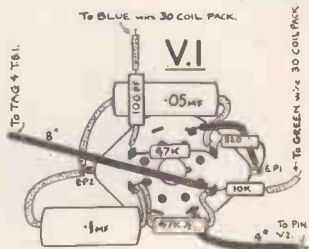

This small reproduction of a SUB-ASSEMBLY taken from one of our series of unique LIFE-SIZE, "EASY AS A.B.C." CONSTRUCTION SHEETS illustrates how really simple radio assembly for the Home Constructor can be! IF YOU have average ability ("A.A.") and could wire this simple unit then you can tackle any, or all, of the TWELVE GUARANTEED OUTFITS given in our HOME CONSTRUCTOR'S HANDBOOK, knowing that with OUR sheets failure is impossible!


Our world-famous publication has ONCE AGAIN BEEN ENLARGED and now contains the following FULL PAGE circuits, with illustrations, descriptions, full parts lists and details, as well as a host of extremely useful information, data, formulae, etc.

- 3 Valve 3 wave FEEDER
- 4 Valve 3 wave FEEDER (with "hi-fi" switching for high quality on locals)
- 5 Valve 3 wave AC SUPER
- 5 Valve 3 wave AC/DC SUPERHET.
- FEEDER AMPLIFIER and Power Pack
- 6 Valve 3 wave A.C. SUPERHET
- 6 Valve 3 wave AC/DC SUPERHET
- SIGNAL TRACER
- 4 Valve BATTERY SUPER
- 5 Watt quality AMPLIFIER
- 10 Watt quality AMPLIFIER
- SIGNAL GENERATOR

(† All Parts are obtainable from us by mail and are clearly marked and identified with our Construction Sheets.)

The price 2/6 Only which makes this Book just about the best value-for-money obtainable anywhere to-day!! Many thousands of Constructors like yourself are using our splendid circuits, so SEND NOW FOR YOUR COPY The 1951/2 ISSUE is obtainable by mail ONLY FROM:

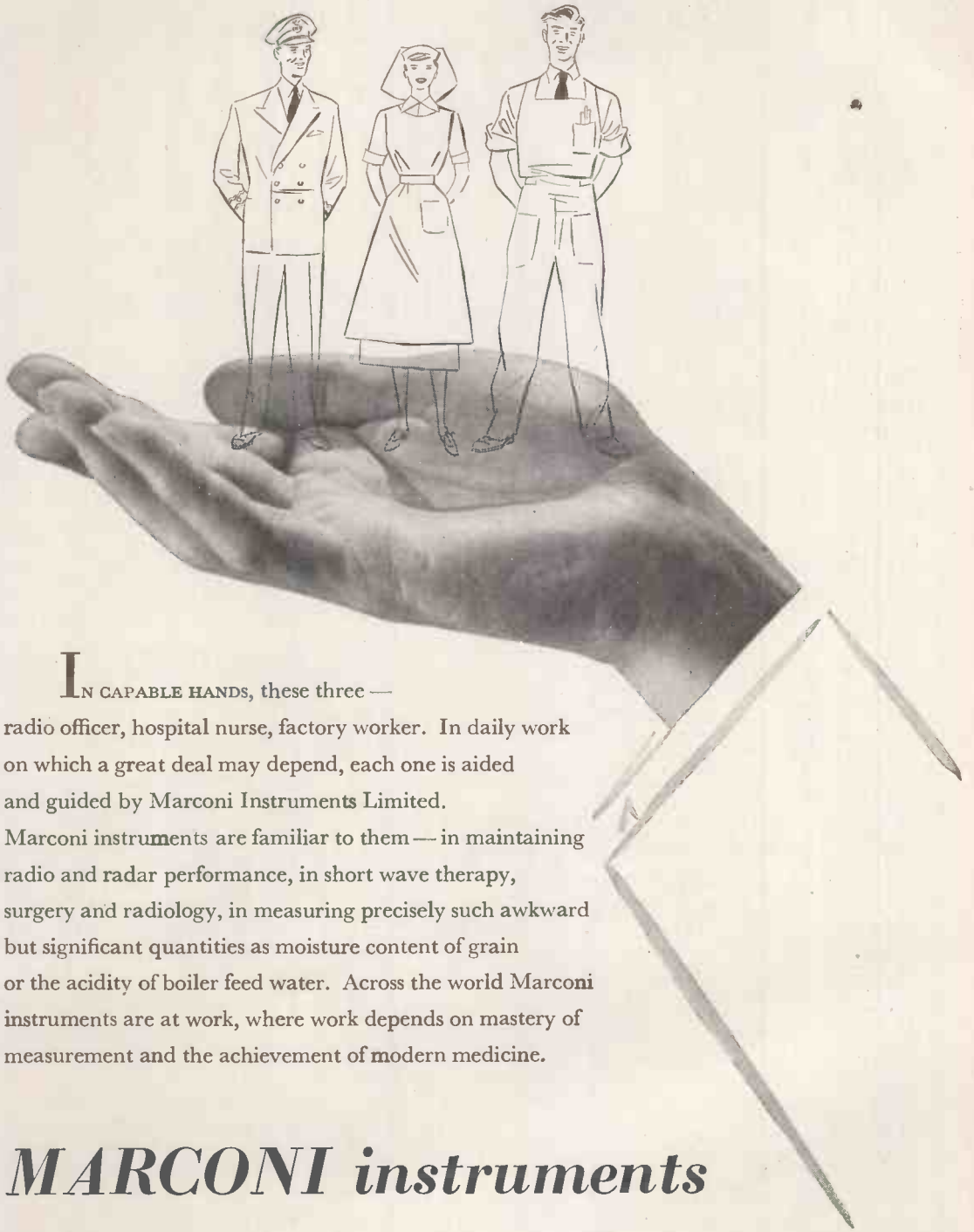RODING LABORATORIES (Dept. W.D.)
 694, LEA BRIDGE ROAD LONDON, E.10



IN CAPABLE HANDS, these three — radio officer, hospital nurse, factory worker. In daily work on which a great deal may depend, each one is aided and guided by Marconi Instruments Limited. Marconi instruments are familiar to them — in maintaining radio and radar performance, in short wave therapy, surgery and radiology, in measuring precisely such awkward but significant quantities as moisture content of grain or the acidity of boiler feed water. Across the world Marconi instruments are at work, where work depends on mastery of measurement and the achievement of modern medicine.

MARCONI *instruments*

MARCONI INSTRUMENTS LTD · ST. ALBANS · HERTS · Telephone: St. Albans 6161/7

London Office: Marconi House, Strand, W.C.2. Midland Office: 19 The Parade, Leamington Spa. Northern Office: 30 Alblon Street, Hull.

MUREX are now making


ZIRCONIUM

ROD · WIRE · SHEET

in commercial quantities

In addition to Tungsten, Molybdenum and Tantalum we are now making ZIRCONIUM ROD, WIRE and SHEET in commercial quantities. We shall be pleased to have details of your requirements. Technical literature available on request.

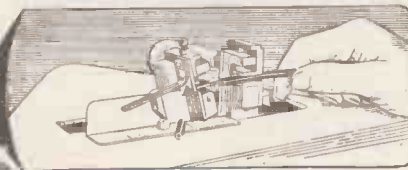
MUREX LTD. (Powder Metallurgy Division) · Rainham · Essex Tel.: Rainham, Essex, 240
LONDON SALES OFFICE: CENTRAL HOUSE, UPPER WOBURN PLACE, W.C.1. Tel.: EUSon 8265



The new HYDE foot operated WIRE STRIPPER

These two machines will, between them, strip with speed and accuracy practically all types of Insulated Wires and Cables from Small Wires and Flexes up to Cables of $\frac{1}{2}$ " diameter. HYDE Stripping Machines are cutting the costs and speeding the production of many world famous manufacturers. SEND SAMPLES OF WIRES AND CABLES USED, FOR FULL REPORT.

... and the
BENCH MODEL

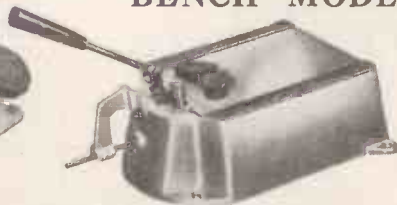

Telephone : Wythenshawe 2850

J. B. HYDE & CO. LTD., Wythenshawe, Manchester

Preliminary Announcement! In accordance with our declared policy of manufacturing only the finest and most modern equipment,

PANDA PROUDLY PRESENTS THE PR-120-V

The FIRST Table Top Tx to incorporate the following desirable features:—

* **T.V.I.**—Incorporating the absolute latest in T.V.I. proofing. You can now live with T.V.

* **FLEXIBILITY.**—Band-switched 3.5, 7, 14, 21 and 28 Mc/s.

* **THE COMPLETE "TABLE TOPPER"** Speech Amplifier, modulator and all power supplies built into one modern table top cabinet.

* **QRO.**—120 watts of 100 per cent. modulated phone and 150 watts of C.W.

* **VERSATILE.**—High stability calibrated V.F.O. incorporated.
* **Harmonic Check facility.** Fully metered. H.T. interlock and full safety precautions. Embodied variable excitation control, Break-in facilities provided. Output impedance 50—100 ohms unbalanced line.



In fact, IT HAS EVERYTHING!

With a key, mike and power plug you can work WHO you want WHEN you want with the PR-120-V.

The PR-120-V is now in production. Price £125. Delivery to commence December and all orders will be dealt with strictly in rotation. Export inquiries will command priority. The PR-120-V is the latest product of the PANDA organisation and is another "first." A new piece of "PANDA" (Regd.) Equipment.

PANDA RADIO CO., 58 School Lane, Rochdale

Tel. : 47861. Grams : PANDA, ROCHDALE

**THE WORLD
RENOWNED**

Plus-a-Gram
Regd

**MAKES YOUR SET
A RADIOGRAM**



TABLE AUTO-CHANGER MODELS

MODEL J/T/AUTO. Table Model, fitted with Garrard Automatic Record Changer, playing 8-10" or 8-12" records. **£25-12-4**

MODEL T/3S/AUTO (3 SPEED). Table Model, fitted with 3-speed Garrard Automatic Record Changing Unit, playing 8-10" or 8-12" records and fitted with dual pick-up head suitable for standard or long-playing records (for A.C. mains). **£31-3-6**



CONSOLE AUTO-CHANGER MODELS

MODEL C/J/AUTO. Console Model fitted with Garrard Automatic Record Changer, playing 8-10" or 8-12" records (for A.C. mains). **£37-14-0**

MODEL C/3S/AUTO (3 SPEED). Console Model, fitted with 3-speed Garrard Automatic Record Changing Unit, playing 8-10" or 8-12" records and fitted with dual pick-up head suitable for standard or long-playing records (for A.C. mains). **£43-5-2**

PRICES ARE INCLUSIVE OF PURCHASE TAX.



PORTABLE MODELS

MODEL P.S.L. Portable Model, in Figured Walnut Case, fitted with Garrard A.C. Rim-Drive Motor. **£12-13-9**

MODEL P.M.3 (3 SPEED). Portable Model, in Figured Walnut Case, fitted with 3-speed Garrard Motor and dual pick-up head suitable for standard and long-playing records (for A.C. mains). **£17-10-5**

CABINETS. Handsome design, finished in Walnut, following the modern trend, the simple but effective style of the Cabinet is a welcome addition to any room. The Console models have ample record storage accommodation.

Patent No. 404,373.

Registered Nos. 789,034 and 833,875, etc.



TABLE MODELS

MODEL J/T. Junior Table Model fitted with Garrard Rim-Drive Motor. **£14-19-8**

MODEL T/M. Standard Table Model, fitted with Centre Drive Motor. **£17-17-8**

MODEL T/M/U. Standard Table Model available for A.C./D.C. mains (universal). **£21-15-0**

MODEL T/3S (3 SPEED). Table Model, 21" wide, fitted with Garrard 3-speed Motor and dual pick-up head, suitable for standard and long-playing records (for A.C. mains). **£19-18-9**



CONSOLE MODELS

MODEL C/J/21. Console Junior Model, 21" wide, fitted with Garrard Rim-Drive Motor. **£26-2-0**

MODEL C/M/21. Standard Console Model, 21" wide, fitted with Centre Drive Motor. **£29-0-0**

MODEL C/M/U/21. Standard Console Model, 21" wide, available for A.C./D.C. mains (universal). **£32-17-4**

MODEL C/3S (3 SPEED). Console Model, 21" wide, fitted with Garrard 3-speed Motor and dual pick-up head suitable for standard and long-playing records (for A.C. mains). **£30-9-0**

Wolf



puts **HIGH SPEED**
into **SOLDERING**

SOLDERGUNS

Built to increase output and cut costs over the whole field of soldering from fine instrument work to heavy industrial soldering. Only Wolf Solderguns have all these outstanding advantages.

- OFF-STRAIGHT EASY-GRIP HANDLE
- PERFECT CONTROL
- LOW CURRENT CONSUMPTION
- QUICKER HEAT-UP
- MAINTAINS CORRECT HEAT
- LOCALISED HEAT
- MODELS FOR EVERY PURPOSE FROM FINE INSTRUMENT TO HEAVY INDUSTRIAL SOLDERING



TYPE 21

4

OTHER MODELS TO CHOOSE FROM



TYPE 31



TYPE 41




TYPE 71



TYPE 81

HAVE YOU TRIED AUTOMATIC SOLDERING?

Win new efficiency and economy with Wolf Automatic Soldergun. Its auto-feed, trigger solder-feed action and perfect balance make it indispensable to all modern assembly.

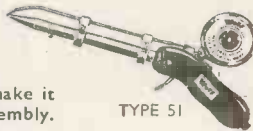

TYPE 51

SOLDERING IRONS



TYPE 32



TYPE 42



TYPE 22

For all who, for special reasons, prefer the conventional straight type handle. Identical as regards elements and bits to Wolf Solderguns but with round hard wooden handle with heat deflecting skirt.

Wolf

It pays to Solder with

ELECTRIC SOLDERGUNS & SOLDERING IRONS

* Obtainable from all high-class stockists and ironmongers.

WOLF ELECTRIC TOOLS LTD.

PIONEER WORKS, HANGER LANE, LONDON, W.5
Telephone: PERivale 5631-4. BRANCHES: BIRMINGHAM · MANCHESTER · LEEDS · BRISTOL · GLASGOW

Good music deserves FIDELITY in recording and in reproduction

A world-famous Orchestra—playing the loveliest work of a renowned composer—beautifully recorded by the most modern technique—all those amount to very little unless the sound equipment is capable of reproducing the original music with a high standard of fidelity. Specially developed to meet the exacting requirements of music lovers, the GRAMPOLA Model S.50 Amplified Electric Gramophone



is an instrument which gives equal satisfaction to the musician and technician alike. Weighing only 21 pounds, it is readily portable, and the two simple controls are fitted on the outside of the case, so that the lid can be closed during playing, eliminating surface noise.

GRAMPOLA Model S.50
Price £24.12.8 (inc. P.T.)
Amplified Electric Gramophone for A.C. Mains, 50 cycles 200/250 volts.
Weight 21 lb.
Size 14½" x 13½" x 9".

Get full details without delay from:

GRAMPIAN REPRODUCERS LTD

9, HANWORTH TRADING ESTATE, FELTHAM, MIDD^X
Telephone: Feltham 2657 Telegrams: Reamp, Feltham

M.R. SUPPLIES Ltd

Offer from stock the following brand new (or otherwise perfect) material. All prices nett. Immediate despatch.

- HIGH DUTY RECTIFIER UNITS (S.T.C.)** Input 220/240 v. 50 c. 1 ph. Output 36 volts 50 amps. Made to rigid specification for ambient of 122 deg. F. Metal rectified, fitted switch and fuses. Average size: 4ft. x 20in. x 2½in. weight approx. 2 cwt. New or as new, £28 ex here, or can be despatched England, 25/-, Scotland/Wales, 30/- Also very few, 200/250 v. 50 c. 1 ph. output 30 v. 28 amps., switched and fused and smoothed, £21 (despatched England, 15/-).
- SELENIUM RECTIFIERS.** High-duty Industrial type, funnel-cooled without forced draught. All full-wave. Remarkable offer of these brand new units from stock, under half list price. 30 v. 20 amps, 60 v. 10 amps, either £4.15/- (despatch 3/6). Two in bridge 30 v. 50 amps., 60 v. 20 amps., 130 v. 10 amps., any pair £9 (des. 9/). Also four in bridge to deliver up to 240 v. 10 amps., £18 the four (des. 12/6). Also single unit, 12 v. 50 amps., £5/5/- (des. 3/6). Also 24 v. 3 amps. full-wave, 32/6 (des. 1/-); 12 v. 3 amps., 20/- (des. 9d.).
- PRECISION MAINS VOLTAGE METERS (B.P.L.)** Rectified moving coil, 0/300 v. A.C. 3½in. Bush panel mount, 77/6 (des. 1/6).
- ROTARY CONVERTERS.** Input 24 volts D.C. output 230 v. 50 c. loading up to 120 watts. Mounted in portable metal case with switch and sockets. Ideal for mobile, boat and caravan use. Perfect order, £4/10/- (des. 3/6).
- VOLTAGE CHANGING TRANSFORMERS.** 100/110-200/250 v. (and vice versa) (A) loading 500 va. In cylindrical steel housing with conduit entries, £4/10/- (des. 3/6) (B) Loading 1,250 va. in portable housing with handle £8/15/- (des. 5/-) (C) Same rating as (B) but with 10 v. tap selector switch, 200/250 v., and 0/120 v. meter, for accurate step-down from varying mains inputs, in portable case with handle, £8/17/6 (des. 6/-).
- PUMPS.** Immediate delivery of the following: Stuart, 220/250 volt A.C. Motor/Pump Units, with capacitor/induction motor, high duty, direct starting, minimum maintenance, No. 21 (1 h.p.) 1,000 g.p.h., £20, (des. 6/6); No. 22 (1 h.p.) 2,000 g.p.h., £25 (des. 7/6). Both centrifugal. Also Rotary Vane Pumps, positive displacement (last few) up to 3,000 g.p.h. Power required 1 h.p. (minimum), all bronze construction, £8/15/- (des. 4/6). Also Gerotor Liquid Pumps by May Oil Burner Corp., power required ½ h.p. (min.) up to 2,000 g.p.h., 57/6 (des. 3/6). Also Immersion Pumps (self-priming)—as R.A.F. but German version. Can be immersed up to 30in. approx. 300 g.p.h. Rated for 24 v. D.C., suitable for 12 v. D.C. or intermittent use on 15/24 v. A.C. 37/6 (des. 2/6).
- GEARED MOTORS.** precision made. Motor rated for 48 v. D.C. fitted with 45/1 reduction gear box, motor shaft 920 r.p.m.. 2-ended final shaft approx. 20 r.p.m., 47/6 (des. 2/-). Further details on request.
- FOOT SWITCHES.** fitted ball-top plunger, each depression closes one and opens one circuit, capacity 10 amps at 200/250 v., 6/6 (des. 1/-).
- LIGHTING DIMMERS.** full-bright to blackout at 220/240 volts, with "off" position: 100-watts, 32/6, 200-watts 37/6, 500-watts, 50/- (des. 2/-), 1,000-watts £5 (des. 3/6). And higher ratings—please enquire.
- THERMOSTATS.** Immersion type (Sunvic) 90/190 deg. F. 15-amps., 200/250 v. A.C. use 10in. long 25/6 (des. 1/3). Also ex-A.M. frost protection type, on at 32 deg. F. off at 49 deg. F., capacity 1.5 amps, 4/6 (des. 8d.). Capsillary type, tube 3in. long, with 8in. pinial range 55/80 deg. F., capacity 5 amps., for air or immersion, 17/6 (des. 1/3).
- MINIATURE MOTORS** 12 v. D.C. (up to 20 v. A.C.). Note the small, size 2½in. long, 1½in. dia. fitted removable pulley, with internal adjustable governor, approx. 3,000 r.p.m. Good power, 12/6 (des. 9d.).
- EXTRACTOR FANS,** 200/250 v. A.C. 8in. impeller, fitted grille 82/6 (des. 1/6). Also Hoover 12/24 v. A.C. D.C. model, 17/6 (des. 1/6).
- JEWEL-TIPPED GRAMO NEEDLES** (permanent) Miniature or standard shank (Please state which) 2/6.

M.R. SUPPLIES Ltd., 68 New Oxford Street, London, W.C.1
Telephone: MUSeum 2958

There's a place for YOU



... in the

part-time

R.A.F

The Royal Air Force urgently needs a trained reserve it can count on in an emergency. And it is men and women like *you* who must form that reserve — people who are ready to give up a small part of their spare time to training: either to continuing to fly or to doing equally important jobs on the ground. Your close association with the Royal Air Force will bring you new experience and fresh companionship. Moreover, by volunteering now, you will be showing the world that you at least are ready to face up to whatever the future holds. Post the coupon below for full details.

TO: ROYAL AIR FORCE (W.D.69A), VICTORY HOUSE, LONDON W.C.2


Please send particulars of part-time service with the R.A.F. (*Applicants from British Isles only.*)

NAME.....


ADDRESS.....

(*If ex-R.A.F. or W.A.A.F. please give rank, trade and number*)

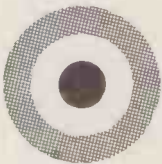
★ If you are between 14 and 17 — and keen — join the Air Training Corps ★



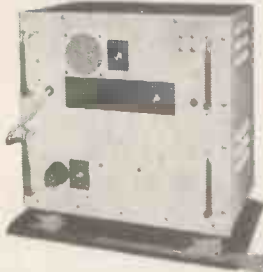ISOLATE that **VIBRATION** through **EQUIFLEX** THE ALL-METAL SPRING MOUNTING



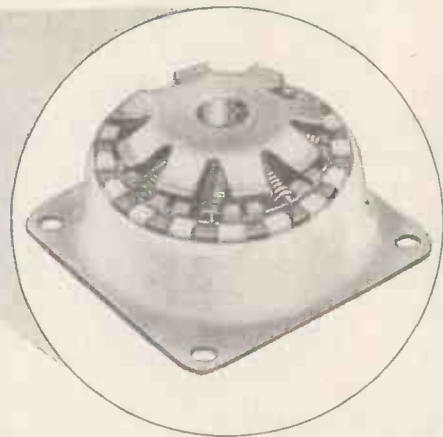- EQUAL FLEXIBILITY IN ALL DIRECTIONS
- CAN BE LOADED IN ANY DIRECTION
- UNAFFECTED BY CLIMATIC CONDITIONS
- VARIOUS TYPES FROM 1-35 lbs PER UNIT
- VIBRATION IS BOTH DANGEROUS AND COSTLY



Write for Catalogue and Price List to
A. WELLS & CO. LTD.
STIRLING RD WALTHAMSTOW, LONDON E.17.

M.O.S. TYPE APPROVED. PATENT NO 571026
FOREIGN PATENTS GRANTED

ICS HOME STUDY backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an ICS Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and, if necessary, television, include the following:

Complete Radio Engineering . Radio Service Engineers . Radio Service and Sales . Advanced Short-Wave Radio . Elementary Electronics, Radar and Radio . Television Technology.

And the following Radio Examinations

British Institution of Radio Engineers . P.M.G. Certificates for Wireless Operators . City and Guilds Telecommunications Wireless Operators and Wireless Mechanics, R.A.F.

Students intending to sit for the above Examinations should enrol NOW for preparatory Courses.

Using a specially prepared study programme, students study at their own pace, in their spare time and, with time for revision, sit with full confidence of success.

(I.C.S. Students are coached until successful)

Write today for our FREE "RADIO" booklet which fully describes the above ICS Courses and the facilities for the complete study of Radio and/or Television technology. The ICS Advisory Department will also give free and impartial advice on the need for and the means of instruction.

GENEROUS DISCOUNT GRANTED TO ALL MEMBERS OF H.M. FORCES.

International
CORRESPONDENCE SCHOOLS

Dept. W.L.29. International Buildings, Kingsway, London, W.C.2.

FRITH RADIOCRAFT LTD for GRAM EQUIPMENT

These items available from stock:

COLLARO 3-RC-511 three-speed AUTO-CHANGERS. 33-45-78 R.P.M. Play 10 7in., 10in. or 12in. standard or microgroove records unmixed. Hi-Fi dual purpose head fitted with ACOS cartridge and sapphire. Complete in open type metal case suitable for rack or cabinet installation. Price £18/15/-.

PLESSEY multi-speed AUTO-CHANGERS to play 8-10 records 10in. and 12in. MIXED at 33 or 78 R.P.M. or 8-10 records 7in. only at 33 or 45 R.P.M. ACOS dual sapphire head for standard or microgroove records. Price £23/13/-.

RICHARD ALLAN portable case record player, incorporating Collaro 3-514 3-speed unit for 33, 45 and 78 R.P.M. Dual purpose ACOS pickup head with sapphire. Auto-stop. De Luxe walnut finish cabinet. Price £21/5/4.

CONNOISSEUR de luxe 2-speed motors with heavy lathe-turned 12in. turntable. Speeds 33 and 78 R.P.M., suitable for standard, transcription or microgroove records. Complete on mounting plate, 13 1/4in. x 15 1/2in., ready drilled for the Connoisseur pickup. Price £22/18/8.

CONNOISSEUR super lightweight pickups. Twin heads, both with sapphires, £10/0/8.

DECCA XMS Hi-Fi pickups, with "C" and "D" heads, £7.

ACOS GP-20 pickups, £3/11/5. Extra GP-19-LP head, £2/3/4.

STROBOSCOPES, printed on robust xylonite for 33 and 78 R.P.M. at 50 and 60 c/s., 3/11.

DECCA turnover crystal pickups with twin sapphires, £3/19/4.

MARCONI 14 lightweight pickup with matching transformer, £2/8/4.

B.S.R. MU-10 motors with 10in. turntable 33 or 78 R.P.M. for 100-250 v. 50 c/s., £3/15/-.

B.S.R. MU-14 gram. motors with Rotacam instant speed change or 33, 45 or 78 R.P.M., £7/3/4.

FRITH RADIOCRAFT LTD

69-71 CHURCH GATE, LEICESTER

Phone 58927



SPECIAL CELLS

FOR SPECIAL PURPOSES

Included in the wide range of "CINTEL" photo-electric cells you will probably find the very one suited to your own particular requirement; but if your problem calls for a cell of special properties, then we are prepared to make it for you.

With over 70 different types in our range, and equivalents for most other manufacturers' cells, we are in a position to solve your photo-cell problem.

Full technical information is available on application to:—



TYPE VA 39
FOR
ACCURATE
PHOTO-
METRIC
WORK



TYPE QVA 39
QUARTZ
ENVELOPE
SENSITIVE
DOWN TO
1900 AU.

CINEMA-TELEVISION LIMITED

A Company within the J. Arthur Rank Organisation

WORSLEY BRIDGE ROAD · LONDON · S E 2 6

Telephone: HITHer Green 4600

SALES AND SERVICING AGENTS

F. C. Robinson & Partners Ltd., H. Hawnt & Co., Ltd., Atkins, Robertson & Whiteford Ltd.,
287, Deansgate, Manchester, 3 59, Moor St., Birmingham, 4 100, Torrissdale Street, Glasgow, S.2



REGISTERED TRADE MARK

SPECIAL PURPOSE ALLOYS

TELCON THERMOSTATIC BIMETALS

A range of precision bimetals noted for their stability and suitable for all applications involving temperature control, indication or compensation.

| TYPE | COMPOSITION | | Deflection Constant per °C. (d) | Resistivity microhms/cm. cube at 20°C. | Maximum Working Temp. °C. |
|-------------|--------------------|---------------------|---------------------------------|--|---------------------------|
| | Low Expansion % Ni | High Expansion % Ni | | | |
| BIMETAL 140 | 38 | 20 | 14.0x10 ⁻⁶ | 75 | 300 |
| BIMETAL 400 | 42 | 20 | 11.0x10 ⁻⁶ | 70 | 400 |
| BIMETAL 15 | 36 | 100 | 9.7x10 ⁻⁶ | 15 | 200 |

Our Representative will call, or full technical data will be sent on request.

TELCON METALS



THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD.

Head Office: 22 OLD BROAD STREET, LONDON, E.C.2. Telephone: LONDON Wall 7104
Enquiries to: TELCON WORKS, GREENWICH, S.E.10. Telephone: GREENWICH 3291

Widney-DORLEC

REGISTERED TRADE MARKS

CABINETS



We are now able to accept **ORDERS** for small or large quantities to any specified design

Technical Adviser:
C. H. DAVIS
59, BROMPTON ROAD
LONDON S.W.3

If you do not already know about this unique cabinet system, write for details.



MANUFACTURERS

HALLAM, SLEIGH & CHESTON LTD
WIDNEY WORKS · BIRMINGHAM · 4

Phone: Aston Cross 0916 (4 lines) · Grams Superfine, Birmingham, 4

BRADMATIC

MAGNETIC TAPE RECORDING EQUIPMENT

Bradmaster Model 5 Tape Desk

- Built to professional standards.
- Two speeds—3½ and 7½ inches per second.
- Easily adjusted for single or twin track recordings.
- Fast wind and rewind—full reel rewound in 1½ minutes.
- Heavy alloy flywheel. Freedom from "wow" and "flutter."
- Double servo brakes on each hub.
- Push Button control.
- Three heavy duty motors.
- Three shielded Bradmatic heads.
- Size: 13½in. x 15½in. x 6½in. deep.

Price **£41** (fitted with 5 R.P. heads)

or with 6 R.P. heads **£42**

| | |
|--|-------------|
| Hi-fidelity magnetic sound heads: | |
| type 5 R.P. (record/play head) | £3 5 0 each |
| type 5 E (erase head) | £3 5 0 .. |
| Super fidelity magnetic sound head, type 6 R.P. (record/play head) | £3 15 0 .. |
| Composite screening cans (constructed of steel and mumetal) | 4 6 .. |
| Oscillator coils | 8 0 .. |
| Oscillator coil type I.B. | 9 0 .. |
| Plate coil type I.B. | 9 0 .. |
| Tape on 7in. reels, 1,200ft.: | |
| Emitape type 65 Low Coercivity | £1 15 0 .. |
| Emitape type H.60 High Coercivity | £1 15 0 .. |
| G.E.C. Grade "A" | £1 10 0 .. |
| Scotch Boy (Durex) MCI-III | £1 15 0 .. |
| Amplifiers and Microphones supplied. | |

Trade Supplied.

Send for Lists to the Sole Manufacturers.

BRADMATIC LIMITED

STATION RD. ASTON BIRMINGHAM 6

Phone: EAST 0574. Grams: Bradmatic, Birmingham

We recommend this tube

because

It has a specially flat face.

**It gives a bright,
pleasantly coloured
image.**

**Ferranti reliability
ensures long life.**

**It gives freedom
from ion burns.**


The price is reasonable.



FERRANTI CATHODE RAY TUBES

**There's a keen demand for this Ferranti T12/44 12" Television Tube, so place your order NOW!
FERRANTI LTD MOSTON MANCHESTER 10; & 36 KINGSWAY LONDON WC2**

STRICTLY EXPORT ONLY

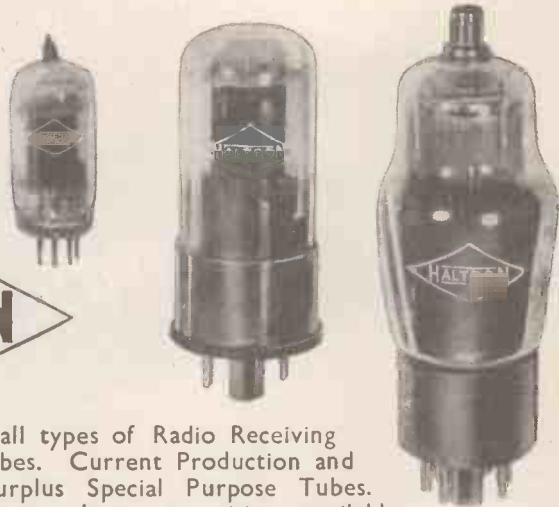

Leading Exporters of all types of Radio Receiving and Transmitting Tubes. Current Production and Ex-Government Surplus Special Purpose Tubes. Over 400 types in large quantities, available Ex-Stock. Suppliers to Foreign Governments, Airlines, etc.

HALL ELECTRIC LTD

89, CHARLOTTE ST., LONDON, W.1.

Phones: MUSEUM 9661 (5 lines)
Cables: HALLECTRIC, LONDON

"Cyldon" Variable CAPACITORS

From MINIATURE TRIMMERS to HIGH VOLTAGE TRANSMITTER CAPACITORS

Here are shown just two examples from the comprehensive "Cyldon" range. For precision, stability, and long life, "Cyldon" superiority is recognised by all designers and users of electronic equipment.

No. 19
Miniature Mica Compression Trimmer

The 3 forms in which this compact variable capacitor is available make it useful as a miniature I.F. trimmer for use in small coil packs, etc. No. 19, illustrated, is a dual trimmer on a common base. No. 19a is a dual trimmer with a steel strip tapped 8 B.A. for mounting. No. 19g is a multi-way trimmer in 2, 4, or 8 sections, banked in mixed capacities to customers' specifications. Each is tested for insulation breakdown throughout its capacity range at 250 v. D.C.

No. 25
Mica Compression Trimmer

Although suitable for very small equipment, its range of maximum capacities—up to 750pF.—gives it wide application. No. 25, illustrated, is for chassis mounting or wire suspension. (Illustration is of under side.) No. 25g is a multi-way assembly for coil packs, fixed station trimming, etc., on a mounting plate pierced for chassis or stand-off mounting. In units of mixed capacities to a maximum of six banks.

• Enquiries invited from Equipment Manufacturers and Wholesale Trade only. Full details of the complete "Cyldon" range and list of Agents for Home and Overseas available from the manufacturers:

SYDNEY S. BIRD & SONS, LTD.

CAMBRIDGE ARTERIAL ROAD, ENFIELD, MIDDX.
Phone: Enfield 2071-2. Grams: Capacity, Enfield.

- RADIO MANUFACTURERS
- RESEARCH LABORATORIES
- GOVERNMENT DEPARTMENTS
- OVERSEAS BUYERS

Should pass their enquiries to the people who set out to "deliver the goods"—no matter how difficult the supply position. People who are not content to try only the regular sources of supply, but keep on trying

Radio Components by all the well-known manufacturers can be supplied in both large and small quantities.

Principal stockists and exporters of the renowned ELSTONE TRANSFORMERS AND CHOKES.


UNCLES, BLISS (Export) Ltd.,

139, Cherry Orchard Road, East Croydon, Surrey.
Telephones: CROYdon 3379/6390.

"An unusually versatile and enterprising organisation."

DEPTH PERSPECTIVE..

The ability of a reproducer in separating the instruments of an orchestra is dependant among other factors upon the area from which the sound appears to emanate. Many experimenters will have found that a larger area appears to improve orchestral analysis but that it detracts from the realism of solo instruments and the human voice. In the Corner Ribbon Loudspeaker, the sound source is small and forward, but it radiates a proportion of sounds in nearly all directions, including upwards and to the rear. The sound pattern reproduced from solo instruments is very similar to that obtained in nature and it is probably the only loudspeaker which can be used in direct comparison laboratory tests to give a complete illusion of most instruments to a critical audience. With an orchestra, the larger microphone distances influence the acoustics of the recording so that the apparent sound source in the loudspeaker recedes. Reflections from the back radiation add to the area of sound so that it now appears to emanate from an opening of eight to ten square feet. The above is just one of the reasons why the Corner Ribbon Loudspeaker gives an analysis of sound in natural perspective.


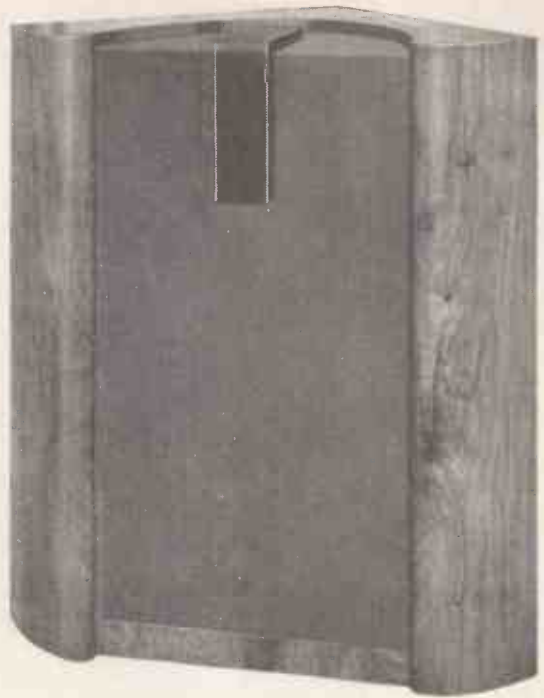


THE
CORNER RIBBON
LOUDSPEAKER

£83

controlled sale

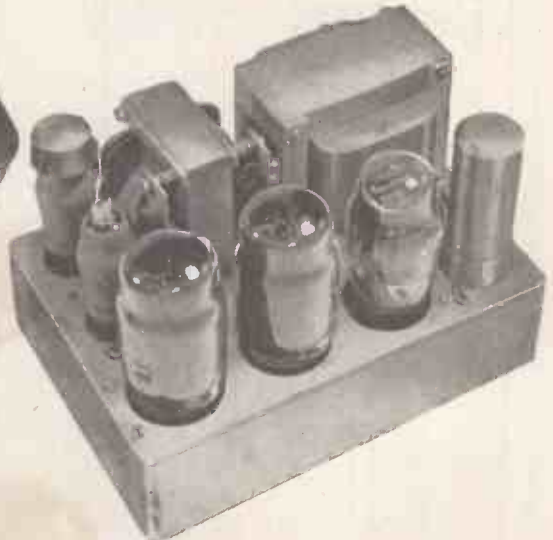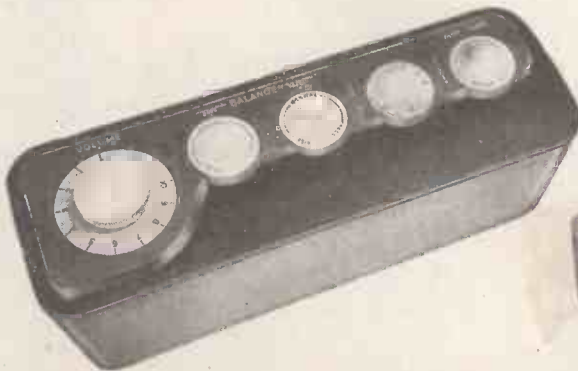A booklet describing the development of this loudspeaker is available on request



It is important to remember that a good loudspeaker will give you music, noise and distortion, all faithfully reproduced. The QUAD amplifier used with a good loudspeaker will give you the closest approach to the original sound.

THE Q.U.A.D. AMPLIFIER
in two units as illustrated

£35

ACOUSTICAL
MANUFACTURING CO LTD
HUNTINGDON · HUNTS · TEL: 361

FIELDEN


PROXIMITY METER



In most applications it is unnecessary to establish physical contact with the specimen.

An indispensable tool for laboratory and workshop investigation of physical, chemical and mechanical phenomena which may be resolved into changes of electrical capacitance. At maximum sensitivity, full scale deflection can be obtained for a 0.2% change in terminal capacity. For example, dimensional displacements, vibrations, strains, surface irregularities, dielectric properties of solids and liquids, certain moisture content and coating thickness problems.

fielden
INSTRUMENTATION

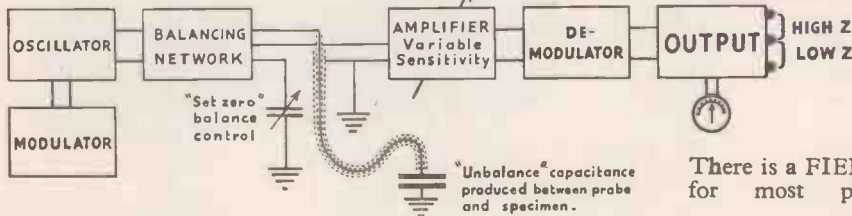

There is a FIELDEN INSTRUMENT for most physical measurements.

Full details by return post from
FIELDEN (ELECTRONICS) LIMITED, "H" Block, Paston Road, Wythenshawe, Manchester
Also at LONDON, PENNSYLVANIA and MELBOURNE.

These
Richard Allan
Bafflettes




Major
£3/15/-

Minor
£3/3/-

Baby
£2/7/6

are fitted with
LARGER Loudspeakers
than ANY similarly priced
extension loudspeakers!

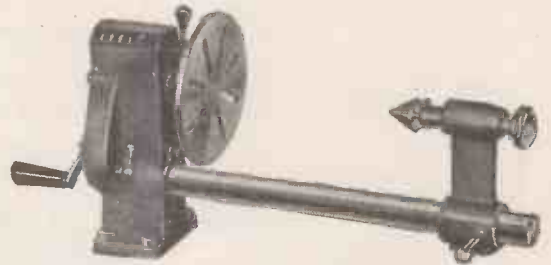Obtainable from all good Radio Dealers
Richard Allan Radio Ltd., Bafflette House, Batley, Yorks



TYPE H/1 HAND COIL WINDING MACHINE

This machine is of sturdy construction and will handle wire gauges from 16—45 S.W.G. Alternative winding ratios of 1—1 or 3½—1 are provided. The tailstock supporting bar is quickly detachable to allow large diameter coils to be wound. The Type H/1 machine can be used as an Armature winder with the addition of our Type A.W./1. armature winding head. We can supply 6" or 12" Face plates, 0—¼", self centring Chuck and a suitable Reel Holder for use with the Type H/1 machine.

Please write for illustrated leaflets to

KOLECTRIC LTD


73. UXBRIDGE ROAD, EALING, LONDON, W.5

Telephone: EALing 096

HIGH STABILITY RESISTORS

- * High intrinsic stability of resistance value.
- * Low temperature coefficient of resistance.
- * Negligible voltage coefficient.
- * Very low noise level.
- * Inductive phase angle negligible.
- * Rigid metal end-cap contacts with integral connection wires.
- * Available in two types — Normal and Insulated (with neoprene sleeve). Supplied in preferred values.

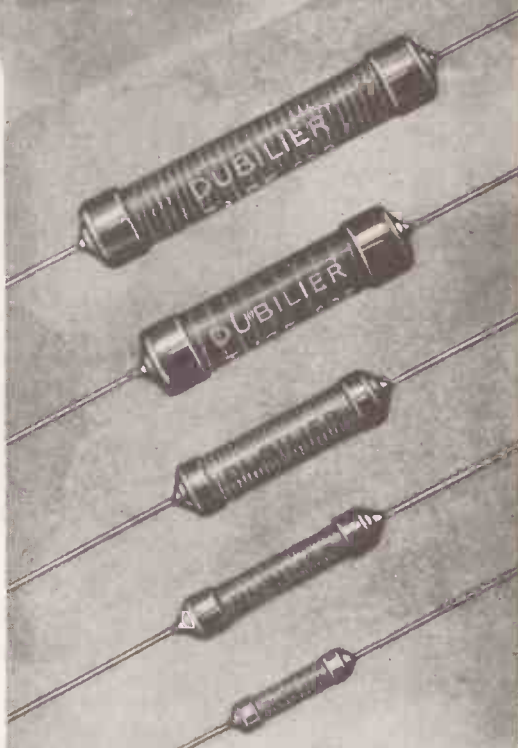The Dubilier High Stability Resistor owes its acknowledged world-wide superiority to the most modern process of manufacture backed by long experience and intensive research in this specialised field of resistor engineering.



DUBILIER

RESISTORS

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA RD., N. ACTON, LONDON, W.3, ENGLAND
Phone : Acorn 2241 (5 lines). Grams : Hivoltcon, Wesphone, London. Cables : Hivoltcon, London, Marconi International Code

FERROXCUBE

FERROMAGNETIC FERRITE

FOR TELEVISION

THE improvement in television components, with their smaller size and greater efficiency, is largely due to Ferroxcube, the new Mullard magnetic core material.

The uses of Mullard Ferroxcube in the production of TV components fall into these three main groups:

LINE OUTPUT TRANSFORMER COILS


Since the advent of wide-angle television tubes, with the accompanying demand for increased E.H.T. supplies, the need for line output transformers of the highest possible efficiency has been greater than ever. Mullard Ferroxcube, with its low iron losses, completely fulfils this need — also facilitating the assembly of small, compact transformer units by means of solid, non-laminated U-shape cores.

DEFLECTION COIL YOKES

Mullard Ferroxcube cores in ring form are ideal for producing the magnetic circuit around deflection coils. Used in this way, Mullard Ferroxcube makes possible the construction of efficient deflector coils with a high Q factor. In order to simplify assembly problems, these ring cores are supplied either in the form of a complete circle, as two semi-circles, or as castellated yokes.

LINEARITY AND PICTURE WIDTH CONTROLS

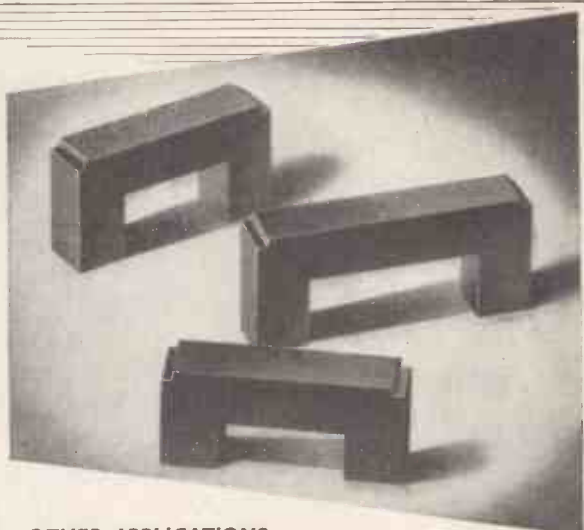Mullard Ferroxcube can very conveniently be extruded into rods and tubes. In this form it is ideal for use in linearity and picture width controls, providing a smooth control in a compact assembly.



OTHER APPLICATIONS

In addition to its uses in television receivers, Mullard Ferroxcube is also being widely employed in line communications, radar, and other specialised electronic equipments. The purposes for which it is already being most successfully applied in such equipments include filter networks, wide band transformers, magnetic amplifiers, and pulse transformers.

PLEASE WRITE FOR FULL DETAILS



Mullard FERROXCUBE

FERROMAGNETIC FERRITE

MULLARD LIMITED · CENTURY HOUSE · SHAFESBURY AVENUE · LONDON · W.C.2. (MF376)

If you must have a fit...

fit an

OSMOR 'Q' COILPACK

—for easy assembly

and whistle-free reception. No complicated wiring circuits — just five simple connections for the OSMOR pre-aligned Coilpack to be installed — and you're all set for receiving 'Loud and Clear.' All types available for battery and mains, with full instructions and circuit diagrams.

end Sd. (stamps) for complete receiver circuits, also lists of Coils Coilpacks and all Radio Components.

As specified for conversion of the Type 25 unit of the T.R.1196, also Type 18 and wartime utility receiver, etc.

OSMOR RADIO PRODUCTS LTD. (Dept. W.25)
BRIDGE VIEW WORKS, BOROUGH HILL CROYDON SURREY

Telephone: CROYDON 5148/9

QUALITY REPRODUCTION

Where High Sensitivity is desired it is definitely obtainable when you choose and use S. G. BROWN Type "F" (Featherweight) Headphones. D.C. Resistance 4,000 ohms.

Impedance 14,000 ohms at 1,000 c.p.s. Weight 9 ozs.

High quality Reproduction is one of the outstanding characteristics of S. G. BROWN Type "K" Moving Coil Headphones. Excellent for DX work, laboratory purposes, monitoring, etc.

D.C. Resistance 47 ohms. Impedance 52 ohms at 1,000 c.p.s.

Write for Brochure "W". It gives details of all types of S. G. Brown headphones.

S.G. Brown, Ltd.

SHAKESPEARE STREET, WATFORD, HERTS



The Advance type H1 Audio Signal Generator completely covers the unusually wide range of 15 c/s to 50,000 c/s. It is characterised by its extremely low distortion and level output over the entire range; provides both sine and square wave output. A robust, reliable and accurate instrument for the discriminating service engineer ● Accuracy $\pm 1\%$, ± 1 c/s. ● Distortion less than 1% at 1,000 c/s. ● Output from 200 microvolts to 20 volts with accuracy of ± 1 db. ● Weight 14 lb. ● Size 13½" x 10½" x 8"


The Advance range covers
15 c/s to 310 Mc/s.

FULL TECHNICAL DETAILS AVAILABLE
IN FOLDER S16/w

Advance
AUDIO GENERATOR

ADVANCE COMPONENTS LTD., BACK ROAD, SHERNHALL STREET, LONDON, E.17

'Phone: LARKSwood 4366/7/8

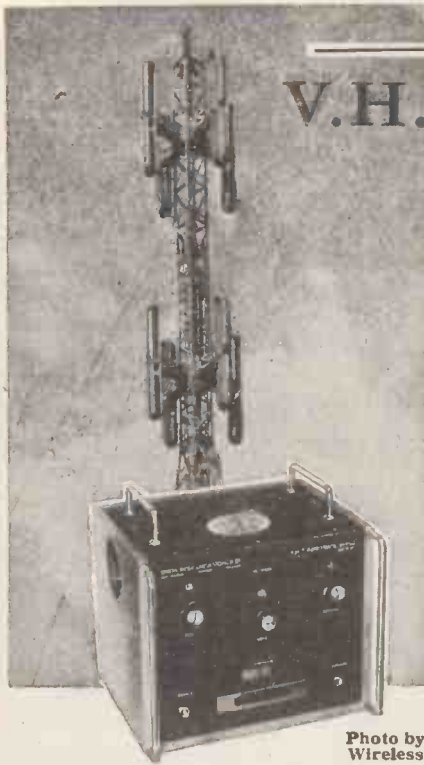

V.H.F. Bridges

Balanced measurements up to 100 M/cs
Unbalanced measurement up to 250 M/cs

DURING the last few years a number of techniques have been developed for making V.H.F. impedance measurements with an accuracy of 1% or 2%, so that a V.H.F. Bridge is no longer a novelty. It is still, however, comforting to have a bridge with which parasitic capacities do not cause serious errors in measurement. Wayne Kerr bridges avoid the difficulties arising from parasitic capacities by the use of transformer ratio arms, which give extremely low impedances between the bridge terminals and from the bridge terminals to ground. These V.H.F. bridges are as stable and as simple to use as an audio frequency bridge.



Photo by courtesy Marconi's Wireless Telegraph Co. Ltd.

THE WAYNE KERR LABORATORIES LTD., NEW MALDEN, SURREY Tel: MALden 2202

FOR GREATEST EFFICIENCY
AT
THE HIGHER FREQUENCIES

SILVERED



CERAMIC

PRECISION CAPACITORS

FOR TELEVISION, F.M., AND ALL U.H.F. APPLICATIONS

Constructors', service replacement, and all kit types.

High precision and laboratory types.

INQUIRIES INVITED

SPHERE RADIO LIMITED,
HEATH LANE, WEST BROMWICH.

MODERN ELECTRICS LTD.,

164, Charing Cross Road,
London, W.C.2 'phone TEMple Bar 7587

Immediate delivery from stock

Export enquiries welcomed. Prompt attention to post orders.

| TAPE RECORDERS | | TAPE | |
|---|-----------|--|----------|
| SOUNDMIRROR | | Soundmirror Tape ... | £1 5 0 |
| Table Model | £69 10 0 | E.M.I. Medium and High Coercivity ... | £1 15 0 |
| Portable Model ... | £79 10 0 | Scotch Boy (Durex) MCI-III | £1 15 0 |
| SIMPHONIC | | Philips Tape | £2 0 0 |
| 2B, complete | £60 0 0 | E.M.I., G.E.C. and Durex spools..... | 4 0 |
| 1A, (now booking for January delivery) | £76 0 0 | "Magnetic Recording" by S. J. Begun, post free | £1 6 0 |
| SCOPHONY-BAIRD | | | |
| Complete with Microphone | £58 5 6 | | |
| | | TEST GEAR | |
| CONNOISSEUR | | AVO | |
| 2-speed Motors ... | £22 18 8 | Models 7, 8 | £19 10 0 |
| CONNOISSEUR | Pick-ups. | D.C. Minor | £5 5 0 |
| Std. and Micro-groove | £10 0 8 | Unimirror | £10 10 0 |
| Standard | £4 11 5 | Electronic Test Meter | £40 0 0 |
| ACOS L.P. and Std. heads | £2 3 4 | Wide Band Sig. Gen. | £30 0 0 |
| DECCA Pick-up ... | £3 15 4 | Valve Tester | £50 0 0 |
| DECCA Crystal, L.P. and Std. heads | £3 19 2 | Univ. Bridge | £26 0 0 |
| DECCA XMS Mag., interchangeable heads | £7 0 0 | PIFCO | |
| DECCA MOTORS, | | Radiometer | £1 7 6 |
| 33½ and 78 r.p.m.... | £3 14 4 | TAYLOR | |
| 33½-45 & 78 r.p.m. | £7 3 4 | ALL TAYLOR TEST GEAR IN STOCK. Still available on H.P. Send S.A.E for catalogue and terms. | |
| PLESSEY 3 speed Auto-Changer unit | £23 13 0 | | |
| COLLARO 3-spd. Auto Changer unit with 2 heads..... | £17 16 2 | | |


The EDISWAN ES 85

The Ediswan ES85 is a directly heated thoriated tungsten filament triode designed primarily for use as a class B power amplifier or modulator.

When used as an amplifier a pair of ES85's will deliver approximately 250 watts of power at audio frequencies.

They are, therefore, suitable for use in large public address systems, wired wireless networks or as A.F. modulators in transmitting equipment.

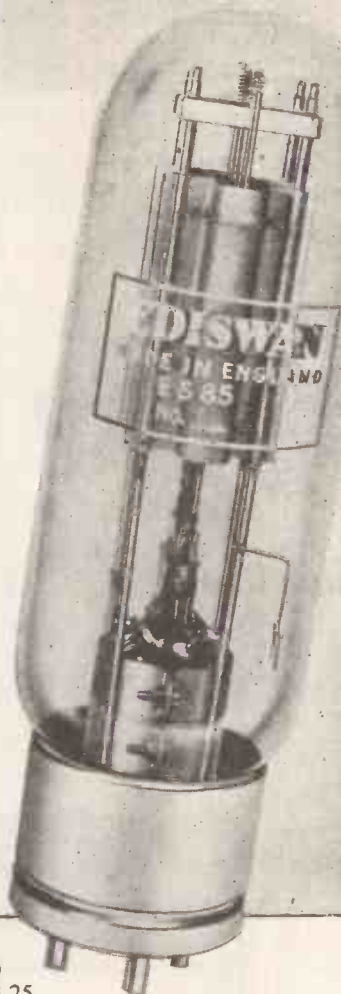The ES85 may also be employed in R.F. equipments providing the frequency does not exceed 6.0 mcs.



rating

| | | |
|---|----------|-------|
| Filament voltage (volts) | Vf | 10 |
| Filament current (amps) | If | 3.25 |
| Maximum Anode voltage (kv) | Va (Max) | 1.25 |
| Maximum Anode Dissipation (watts) | Wa | 85 |
| Mutual Conductance (mA/V) | gm | 4 |
| * Amplification Factor | | 12.5 |
| Anode Impedance (ohms) | | 3,100 |
| Maximum Operating Frequency at full rating (mcs) | | 6 |
| Maximum Audio Output 2 valves (watts) W out (Class B push pull) | | 245 |

* Taken at Va = 1 kV. Vg = -55v.

Further details of this and other Ediswan Valves are available on request.

EDISWAN
SPECIAL PURPOSE
VALVES

THE EDISON SWAN ELECTRIC COMPANY, LTD., 155 CHARING CROSS ROAD, LONDON, W.C.2

Member of the A.E.I. Group of Companies

EV83

VALVES!!**TUBES!!**

RECEIVING. TRANSMITTING. MAGNETRONS. KLYSTRONS.
CATHODE-RAY TUBES. PHOTOCELLS. ETC.

First Grade Quality - British and American Make - No Dollar Expenditure Involved

**LARGE QUANTITIES & GREAT VARIETIES
IMMEDIATE DELIVERIES FROM STOCK**

Write or Phone:-

S. Szymanski
(pronounced SHE-MAN-SKEE)

**ELECTRONIC
ENGINEER & STOCKIST**

95, STRODES CRESCENT, STAINES, MIDDLESEX

Telephone: STAINES 3971


Telegrams: "Shemanskee" Staines.

PROBABLY THE LARGEST ACTUAL STOCKIST IN ENGLAND

WHOLESALE & EXPORT ONLY

CABINETS

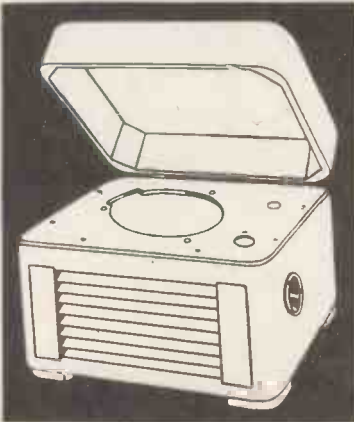Beautifully polished Walnut with Rumanian Birch grille and feet. Lid interior felted. Top plate cut out for gramophone unit. Recessed escutcheon plate fitted in side for volume control. Access trap-door in base. Rubber non-scratch feet. Sub-baffle for 6in. loud-speaker. External 16 x 14 x 12in. deep. Internal 15 x 13 x 7in. below top plate, 3in. above to lid. Solid and finely built.



£3. 10. 0.

Each, incl. Purchase Tax
Packing & carriage extra

GRAMOPHONE UNITS FOR TOP PLATE AVAILABLE

Send details of your requirements to


N. MIERS

& CO. LTD.

115 Gower Street, London, W.C.1

Phone: EUSton 7515.

Grams: Miersco. Westcen

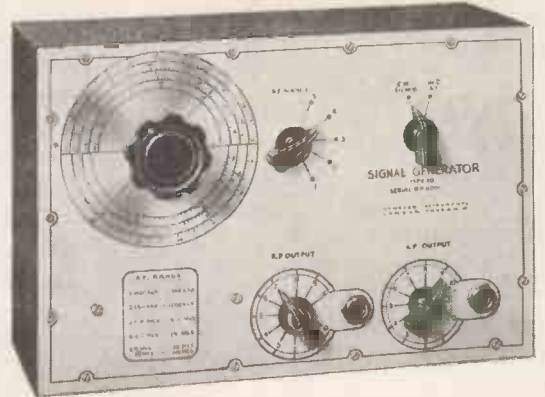

SIGNAL GENERATOR TYPE 10. 100 Kc/s-100 Mc/s

Price £7. 10. 0

The accuracy, reliability and comprehensive specification, are some of the reasons why the TYPE 10 has achieved such outstanding success.

• 100 Kc/s to 100 Mc/s • Modulated or unmodulated carrier • Direct calibration • Adjustable 400 c.p.s., AF signal • Stable RF oscillator Large, easily read scale • AC mains operation.

New instruments now available include the HOMELAB CHECKTEST, price 37/6d., and a range of accurately calibrated variable condensers, 100pf., 500pf., and 1000pf., price 42/- each.

Obtainable only direct from the manufacturers. Send or full technical details or call at address below.

HOMELAB INSTRUMENTS LTD.,


68a, COBDEN ROAD, LONDON, E.11

Telephone: LEY 5651

- Finger-tip selection
- Positive segregation
- Carries complete range in minimum of space

700 LABpak'd RESISTORS

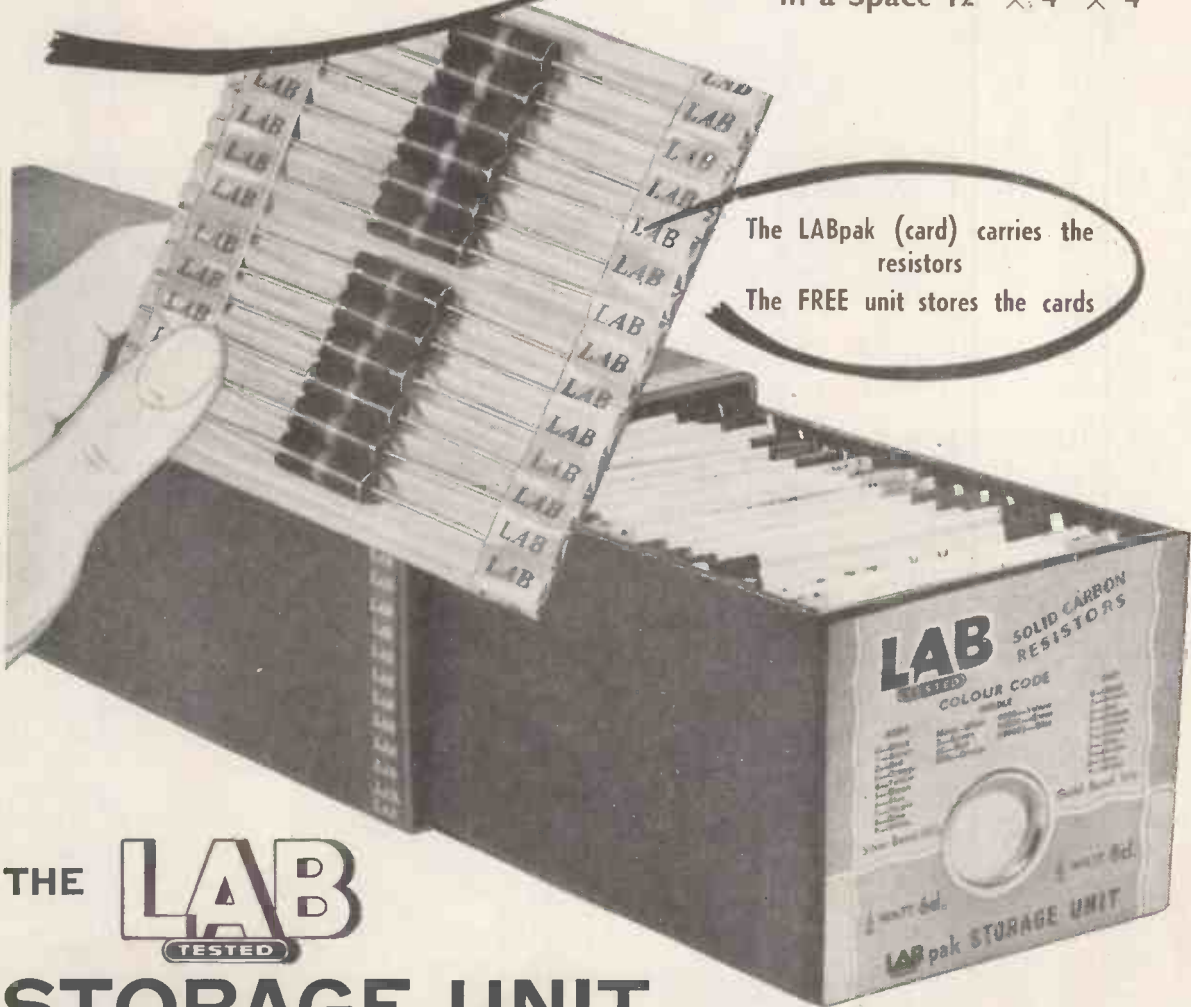10 ohms — 10 megohms
in a Space 12" × 4" × 4"



The LABpak (card) carries the resistors
The FREE unit stores the cards

THE **LAB** TESTED STORAGE UNIT

is designed to provide a comprehensive range of resistors for research and experimental laboratories and small production units. It is supplied free with an initial purchase of

180 Type R Resistors (Order LSUC $\frac{1}{2}$)
or 240 Type T Resistors (Order LSUC $\frac{1}{4}$)

Alternatively you may specify your own Ohmic values from the preferred range. Thereafter replacements and additions, ready carded, are always available from stock.

For further information

● please send to:

THE RADIO RESISTOR COMPANY LTD.,
50, Abbey Gardens, London, N.W.8. Tel.: Maida Vale 5522


RESISTOR SPECIFICATION

| Ref. | Type | Loading | Max. Volts | Range | Dimensions |
|------|---------------------|---------------------|------------|------------|----------------------|
| T | $\frac{1}{4}$ -watt | $\frac{1}{2}$ -watt | 250 | 10 ohms to | 3" × $\frac{1}{2}$ " |
| R | $\frac{1}{2}$ -watt | 1-watt | 500 | 10 megohms | 3" × $\frac{1}{2}$ " |

Tolerance available $\pm 20\%$, $\pm 10\%$ $\pm 5\%$



G.E.C.
QUARTZ CRYSTAL
UNITS

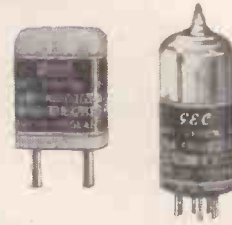

for reliable Radio Communications

YOU CAN'T BUY BETTER!

A COMPREHENSIVE RANGE OF UNITS
IS AVAILABLE COVERING ALL COMMUNICATION
REQUIREMENTS. ASK FOR LEAFLET GC5012.

Be sure that the Quartz Crystal Units in your radio equipment are the best obtainable, for they are the most critical components.

SALFORD ELECTRICAL INSTRUMENTS LTD · SALFORD 3 · LANCs
A SUBSIDIARY OF THE GENERAL ELECTRIC CO. LTD. OF ENGLAND

PHIDELITY

Endless-Loop

MAGNETIC TAPE MECHANISM

For Sales announcements,
Automatic verbal warnings,
Language training, Wave form analysis,
Film dubbing, etc.

Here is a magnetic tape driving mechanism which, utilising 1" magnetic tape, provides unlimited repetition or interchange of recorded announcements.



The recording medium is contained in a detachable cassette (maximum capacity 30 minutes' playing time). Switch-off and switch-on timings are remote controlled by push-button or time-switch. A unique contactor arrangement and a mechanical counter ensure rapid selection, at a fast forward speed, of any part of the 600ft. tape loop. Light in weight; compact in design, size 10in. x 6in. Available in two models: (a) 3½in. per sec., giving 30 minutes recording; (b) 7½in. per sec., giving 15 minutes recording. **PRICE £24. 0. 0.**

For further particulars write to:—

PHIDELITY MAGNETIC PRODUCTS LTD.
65-66 CHANCERY LANE, LONDON, W.C.2.

Telephone: CHAncery 4342.



With this Book
you can
WIN £25

All you do is purchase a copy of **PIANOS, PIANISTS & SONICS** by G. A. Briggs, for 10/6 from your local book seller or dealer and write an essay of not more than 300 words on one of the two following subjects:—

- (a) Which in your opinion is the most interesting chapter in the book, and why?
- (b) Which chapter do you find the least interesting in the book, and why?

10/6
11" POST FREE

Entry forms will be supplied with your purchase, or if you have already made your purchase apply to your bookseller or to the publishers for an entry form. Thirteen prizes will be awarded for essays in each section. Mr. J. Raymond Tobin, B Mus. (Editor of "The Music Teacher") has kindly consented to act as adjudicator.

RULES

This competition is open to readers in any country. The adjudicator's decision is final. **NO CORRESPONDENCE** can be entertained. **ENTRIES** will not be acknowledged or returned. The Publishers, Wharfedale Wireless Works reserve the right to use or reprint any of the prize-winning essays. No employee of Wharfedale Wireless Works nor anyone connected with the production of the book is eligible to compete. Closing date of competition January 31st, 1952. Winners will be announced in the **MUSIC TEACHER & WIRELESS WORLD**. All entries must be sent postage paid direct to:—

PRIZES IN EACH SECTION

| | |
|-----------------------|---|
| 1st Prize | £25 . 0 . 0 |
| 2nd Prize | £10 |
| 3rd Prize | £5 |
| 10 Consolation Prizes | of £1 each making a total of £100 that must be won. |

WHARFEDALE WIRELESS WORKS
BRADFORD ROAD, IDLE, BRADFORD, YORKS.

Telephone: IDLE 461.



An Announcement...

DUREX ABRASIVES LTD. wish to announce that as from June 14th, 1951, the name of the Company has been changed, and is now the MINNESOTA MINING & MANUFACTURING COMPANY LTD. Identification will be as before, except that the words "Scotch Boy" will be used instead of "Durex" as a prefix to the name of the material, e.g., "Scotch Boy" Magnetic Recording Tape instead of "Durex" Magnetic Recording Tape.


Existing high standards in the quality of the products will be maintained, the change is in name only.

'SCOTCH BOY'
Magnetic Recording
TAPE



ANOTHER **3M** COMPANY PRODUCT

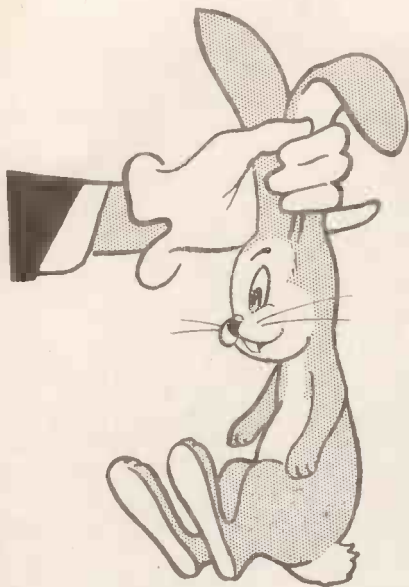Manufactured by :—
MINNESOTA MINING & MANUFACTURING COMPANY LTD
167, STRAND - LONDON - W.C.2 - AND SLOUGH



Not magic

... it's the result of
intensive engineering research

There's no magic in the design of Vitavox loudspeakers, there are no short cuts to perfection. The magician's approach to loudspeaker design has produced many a red herring out of the hat by mistake and the years of steady development work which we have undertaken show that it's not all done by mirrors.

A typical example of Vitavox design for sound, Bitone Reproducers are intended for quality reproduction in small halls, the use of multicell horns in the high frequency channel ensuring maximum fidelity over a wide area.



VITAVOX

LOUDSPEAKERS AND MICROPHONES

VITAVOX LIMITED • WESTMORELAND ROAD •
LONDON, N.W.9 Telephone: COLindale 8671-3

Bitone Reproducer, Model 6201. Please write for more details if you are interested.

Why do it the Hard Way?

*If you are building a
prototype or doing
a pilot run —
YOU'LL NEED*

CONDENSERS - RESISTORS - VALVES
METERS - CHASSIS - PANELS - JACKS
PLUGS - SOCKETS - WIRE - SLEEVING
COAXIAL CONNECTORS - HI. STAB -
VITREOUS RESISTORS - ETC. - ETC.

**BUY IT ALL UNDER ONE ROOF and
CUT OUT PAPER WORK AND DELAY**

TELE-RADIO (1943) LTD.

177, EDGWARE ROAD, LONDON, W.2

Phone: PAD. 5606
PAD. 6116

Shop Hours:
Mon.-Sat. 9 a.m.—6 p.m.
Thursday 9 a.m.—1 p.m.



ONLY
25/6
POST FREE

**A
workshop
in your
pocket!**



THE TELEVISION AND
RADIO SERVICE ENGINEER'S
MASTER TRIMMER KIT

Contains:

- 1 End Trimmer.
- 1 Side Trimmer.
- 1 Yaxley Switch Contact Adjuster.
- 1 Low Capacity Trimmer.

- 1 Screwdriver.
- 1 Set of Feeler Gauges.
- 1 Set of six Box Spanners from 1 to 8 B.A.
- 1 Set of four Spanners from 0 to 8 B.A.

in durable black crackle finish metal case.

Export enquiries invited

SEND YOUR ORDER TO:
J. & S. NEWMAN LTD.

100 HAMPSTEAD RD., N.W.1
Tel.: EUSton 5176/7

PREMIER RADIO COMPANY

B. H. MORRIS & CO. (RADIO) LTD.

HEAD OFFICE AND MAIL ORDER (DEPT. W.W.)

207 EDGWARE ROAD, LONDON, W.2

Open every day until 6 p.m., including Saturdays. Closed 1 p.m. Thursdays.
 TERMS OF BUSINESS:—CASH WITH ORDER OR C.O.D. OVER £1.

Please add 1/6 for post orders under 40/-, 1/- under 20/-.

Phones:
AMBassador 4033
PADddington 3271
PADddington 3272

BRAND NEW R1155 RECEIVERS
 In original cases, complete with 10 valves, £12/10-7/6 packing and carriage.

BRAND NEW R1355 RECEIVERS
 In original cases, as specified for the "Inexpensive Televisor," complete with 11 valves, £2.15/-, 7/6 packing and carriage.

HEADPHONES
 Balanced Armature Low resistance.
 Type 1, 5/11 set; Type 2, 7/11 pair.

High Resistance, 12/6 pair.
 Moving Reed Type 3, 8/11 pair.
 Lightweight High Resistance, 14 6 pair.

TRANSMITTER RECEIVER TYPE TR9H
 Consists of Transmitter type T1396 and Receiver R1139 in one case. This is a 9 valve Battery operated Unit covering 4.3 Mc/s to 6.6 Mc/s. Crystal controlled, complete with valves. 50/- plus 7/6 packing and postage.

TANNOY HAND MICROPHONES
 With switch in handle. 4/11, plus pack, post and insurance 2/-.

ADJUSTABLE BENCH LAMP
 Complete with flex, lampholder, and reflector. 25/-, Post and insurance 2/-.

POST OFFICE DESK TELEPHONES
 Complete with screened lead and plug. Brand new in maker's carton 12/6, post and insurance 1/6. Special quotations for quantities.

BURGOYNE SOLDER GUNS, 75/-.

THREE-PIECE AERIAL
 Ex-U.S.A. copper-plated steel, highly flexible with non-stick screw joints, tapering 1in. to 1in. Brand new in container, 6/9, packing and carriage 1/6. Insulated Base, 2/6.

MAINS NOISE ELIMINATOR KIT
 Two specially designed chokes with three smoothing condensers with circuit diagram. Cuts out all mains noise. Can be assembled inside existing receiver, 6/- complete.

PREMIER TELEVISOR CABINET FOR 12in. TUBE TELEVISOR



A handsome walnut finished cabinet. Primarily designed for our own Kits. They are quite suitable for most of the kits published in the various Radio periodicals. For this reason the holes for control knobs have not been drilled. A baffle board suitable for a 10in. Loudspeaker is provided. Outside dimensions 33in. high, 20in. deep, 16in. wide £9/9/- plus 7/6 packing and carriage.




BUILD A PROFESSIONAL LOOKING RADIO AT LESS THAN HALF TO-DAY'S PRICE

- We can supply all the parts to help you.
- Bakelite Cabinet (Brown or Ivory) 17/6
 - Packing and insurance 2/6
 - Punched chassis, 3-valve plus rectifier T.R.F. 3/9
 - Engraved Glass Dials, 180-550 and 800-2,200 m. 1/-
 - With station names, new wavebands. T.R.F.
 - Coils, 180-550, 800-2,200 metres, pair 6/6
 - Drum (2 1/2 in. diam.) 1/-
 - Driving head 1/-
 - Double pointer 4d
 - Spring 3d
 - Nylon cord (yard) 6d
 - Dial Front Plate 2/6
 - SEND 1/6 FOR EASY TO FOLLOW POINT TO POINT DIAGRAMS AND CIRCUIT DIAGRAM which shows you how YOU can build the Receiver illustrated above.

THE COMPLETE KIT
 to construct a 3 valve plus rectifier TRF Receiver for use on 200/250 v. A.C. mains can be supplied at £8/9/6 plus 2/6 packing and carriage.
 Each Kit is complete in every detail, nothing has to be made or improvised. Easy to follow, point to point diagrams are supplied, making construction very simple. The Dial is illuminated and the Receiver housed in a Bakelite Cabinet size 12in. x 5in. x 6in. presents an attractive appearance. The valve line-up is
 717A—H.P. Pentode.
 VRI10—Detector.
 ATP4—Output and Metal Rectifier.

Waveband coverage 15 for the medium and long bands. Choice of Walnut or Ivory coloured Cabinet.

SENSATIONAL OFFER

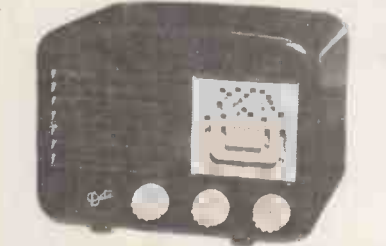

The famous Dulc Midget Receiver for use on either A.C. or D.C. mains, 200/250 volts. This is a 2-waveband 4 v. Superhet Receiver covering the short waveband from 13.6 metres to 50 metres, and the medium waveband from 200-550 metres. Can be supplied in either ivory or brown bakelite cabinet.
 Size 7 1/2 in. length.
 6 in. height.
 5 1/2 in. depth.

This receiver is fully covered by the manufacturer's guarantee.
 Price £8/15/-, carriage paid.
THIS OFFER CANNOT BE REPEATED

BATTERY CHARGER KITS
 All incorporate metal rectifiers. Transformers are suitable for 200/250 v. A.C. 50 cycle MAINS.
 Cat. No. 2002 Charges 6 volt accumulator at 1 amp. Resistance supplied to charge 2 v. accumulator £1 2 6
 2003 Charges 12 volt accumulator at 1 amp. £1 7 6

SUPER QUALITY TELEVISION MAGNIFYING LENS

To suit 5in., 6in., or 7in. Tubes. Increase picture size considerably. 25/- each.



SPECIAL OFFER OF PLESSEY GRAMOPHONE UNITS at almost half price
 The Motor, Tone arm, and Magnetic Pick-up is in one Unit, with Automatic stop and start.
 For use on 200/250 v. A.C. mains 50 cycles. Limited quantity only. £4 19/6, plus 5/- packing and carriage.

BRAND NEW CAR BATTERIES



Delco-Remy in original cases.
 6 v. 90 a.s. £4/15/-, plus 7/6 carriage and packing.
 6 v. 100 a.s. £4/17/6, plus 7/6 carriage and packing.
 6 v. 140 a.s. £5/10/-, plus 7/6 carriage and packing.
 12 v. 85 a.s. British made, £5/10/-, plus 7/6 carriage and packing.
 6 v. 170 A., in teak case, £5/10/-, plus 7/6 carriage and packing.
 6 v. 11-plate British made, £3/17/6, plus 7/6 carriage and packing.

GRAMOPHONE UNITS

- Connoisseur 2-speed Gram Unit, less pick-up £20 19 3
- Pick-up and 2 heads for above £9 6 4
- Conral Rim Drive Gram Unit, less pick-up
- 78 r.p.m. £4 3 10
- Conral Rim Drive Gram Units, 33 r.p.m. £4 7 5
- Decca 3-speed Rim Drive Gram Unit, less pick-up £7 3 4
- Decca single-speed Rim Drive, less pick-up £3 14 4
- Collaro auto-changer 3-speed unit with crystal for long playing and standard recordings £18 14 1
- Collaro single speed auto-changer unit, 78 r.p.m. maghead mounted on metal stand £16 10 0
- Plessey auto-changer unit, 3-speed maghead, plays mixed records £23 13 0
- Collaro rim drive unit, maghead 78 r.p.m. £6 11 4
- Please add 5/- extra for packing, carriage and insurance charges on gramophone units.
- All the above are for use on A.C. mains only.

T.V. WHITE RUBBER MASKS (CORRECT ASPECT)

We can supply a specially designed White Rubber Mask for 6in. C.B. tubes at 8/6 each.
 9in. White Masks, 9/6. 12in. White Masks, 16/11. Round or flat faced.

SORBO RUBBER MASKS, GREY FELT FINISH (NEW ASPECT RATIO)
 9in., 5/-; 12in., 9/6.

P.M. MOVING COIL LOUDSPEAKERS
 (3 ohm voice coils)

- 2 1/2 in. Goodmans 15/-
- 3 in. Plessey 15/-
- 5 in. Plessey 12/6
- 6 in. Truevox 12/6
- 5 in. Rola 13/6
- 5 in. Truevox 12/6
- 6 in. Plessey 14/6
- 10 in. P. R.C. 27/6
- 12 in. Truvox 70/-

ACCUMULATORS
 By world-famous maker, 2 volt 10 a., 4 11.

"Important announcement: Premier Radio Co. no longer have a branch at Fleet St., London, E.C.4. Premier products can be obtained at our only address, 207, EDGWARE ROAD, W.2."
 "We cannot accept responsibility for, or guarantee of any kit or component sold as a Premier product by firms other than ourselves."


Listen to the radio in **EVERY** room

— for as little as 42/-



ONE Stentorian Speaker will enable you to enjoy perfect listening in every room. Simple wiring and a 2 amp. socket in each room, easily and cheaply fixed, mean a Stentorian can become your portable radio, providing entertainment in any room in the house, for as little as 42/-. Reproduction is, in most cases, better than that given by the set itself.

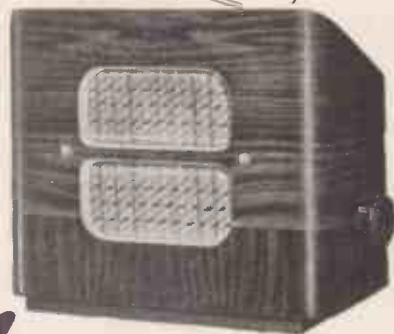Send for leaflets or, better still, ask your usual dealer to demonstrate.



● Illustrated here is the Bude, price 42/-. Other models include the remote control button which, in conjunction with the 'Long Arm' Remote Control, enables the Radio to be switched on or off from any room in the house.

Stentorian EXTENSION SPEAKERS

WHITELEY ELECTRICAL RADIO CO. LTD MANSFIELD NOTTS

made to measure . . .



The man who knows exactly the state of his insulation at any time—is wise.

But one who uses a "Record" Insulation Test Set is wisest. It is made to measure—**ACCURATELY**, by those who were pioneers in this field and who have kept ahead.

RECORD

MAKERS OF MANY OTHER
FINE INSTRUMENTS.

THE RECORD ELECTRICAL CO LTD

BROADHEATH · ALTRINCHAM · CHESHIRE

Phone: Altrincham 3221/2/3 Cables and Grams: "Circscale" Altrincham
London Office: 28 Victoria Street, London, S.W.1 Phone: Abbey 5148 & 2783
Grams: "Circscale" Sowest, London. Cables: "Circscale" London

Hear yourself speak on the S.R. MAGNETIC TAPE RECORDER

£48 COMPLETE

Enjoy the thrill of recording your own and friends' voices on all entertaining and exciting occasions on the S.R. Magnetic Tape Recorder. You can have 30 minutes of non-stop recording of any audible sound with immediate playback. The tape can be erased and re-used indefinitely.

Capture your favourite Radio programme or Commentary for playing back at your convenience.

This beautifully made instrument in its craftsman-built veneered Cabinet is available for delivery in approximately 5 weeks from date of order at £48, plus 15/- for packing and carriage—but please order early as we anticipate a large response in view of the quality and low price of this model.



TRADE & EXPORT ENQUIRIES INVITED.

Terms of Business: Cash with Order or against Pro-Forma invoice.
Suitable only for A.C. mains 200/250 volts.

MADE BY


SOUTHERN RADIO
(WORTHING) LTD.

DOMINION ROAD, WORTHING, SUSSEX

Tel.: Worthing 2507

POINTERS

SUPREMACY

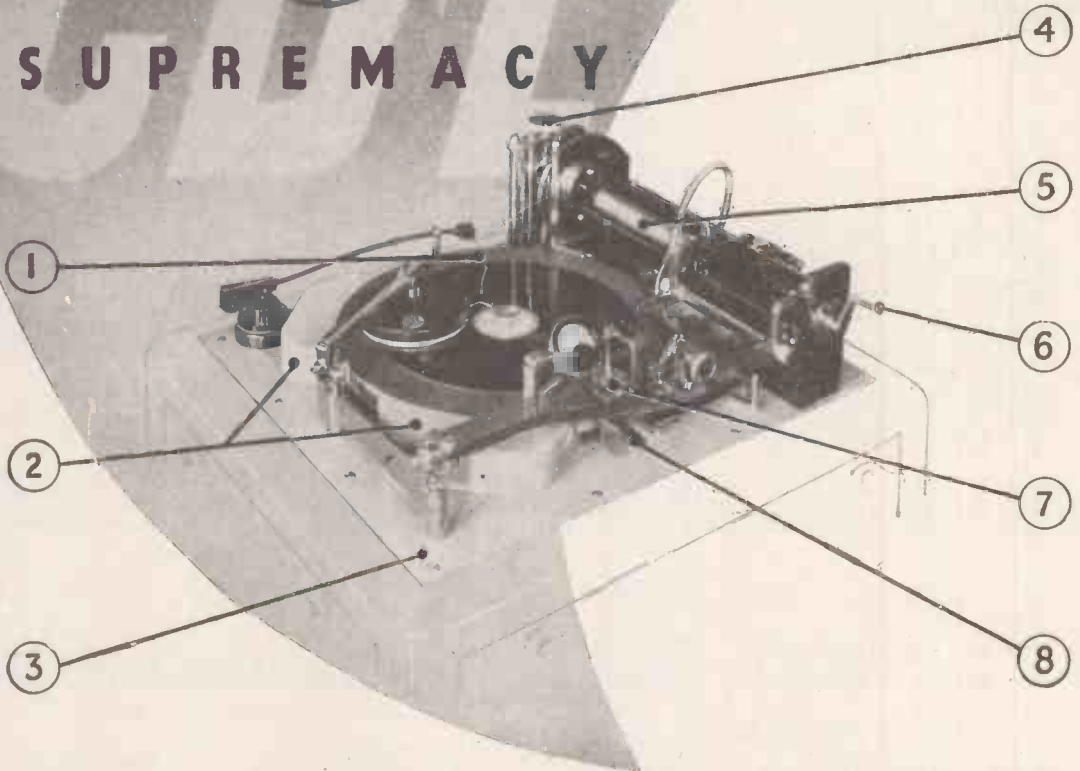

DIRECT RECORDING ON DISK


Some points about the CB/E which have made this machine the considered choice of many discriminating broadcasting concerns throughout the world.

- | | |
|---|---|
| (1) HEAVY CAST IRON TURNTABLE , accurately balanced, ensures freedom from 'wow.' | (5) GROUND STEEL LEADSCREW HOUSING TUBE provides a generous cutterhead arm bearing free from side-play. |
| (2) TWIN DUAL SPEED FRICTION DRIVES designed to reduce vibration and ground noise to a minimum. | (6) HAND OPERATED TRAVERSING CONTROL provides easy scrolling off and scrolling on. |
| (3) ROBUST MILD STEEL BASE PLATE $\frac{1}{2}$ " thick ensures rigidity, stability and freedom from vibration. | (7) PATENTED ELECTRO MAGNETIC CUTTERHEAD with built in equaliser, possessing exceptionally stable characteristics. |
| (4) GROOVE SPACING CONTROL gives continuous adjustment of pitch when cutting outside/in or inside/out. | (8) CHANGE SPEED LEVER provides instantaneous change to either 78 r.p.m. or 33 $\frac{1}{3}$ r.p.m. |

Full details and technical data on request.

M · S · S · RECORDING COMPANY LTD
 POYLE CLOSE · COLNBROOK · BUCKINGHAMSHIRE · TELEPHONE · COLNBROOK 284

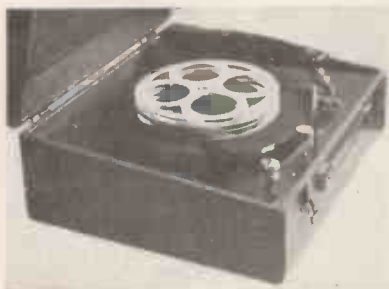FIRST AGAIN! ★★★★★★★★★★★★★★★★★★★★ Here is Your Two-Valve Translator




You can magnetically record, using your gramophone motor as a drive and the amplifier within your radio as the tape amplifier. Conversion Kit (readily detachable) containing all necessary parts and instructions, £7, includes postage, etc.

- ★ 1948 We gave you wire recording utilising a gramophone motor
- ★ 1949 We gave you talking books for the blind
- ★ 1950 We gave you tape recording utilising a gramophone motor
- ★ 1952 We give you now for the FIRST TIME in MAGNETIC RECORDING

A Two-Valve Translator

By clever circuitry we have produced for you a 2-valve translator which supersedes costly amplifiers and saves you needless expense. This unique translator will magnetically record from any microphone or pick-up. This unique translator will playback from any make of recorder. It will (without electrical connection to telephones) record 2-way conversations. It will playback into business intercom systems. It will playback into cinema or wireless relay systems.

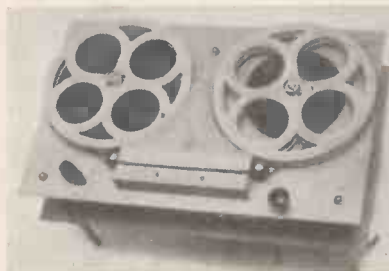The translator has both audio and a radio frequency outlet so that any radio receiver tunable to say 900 metres can boost the output to greater volume if desired. This wonderful new TWO-VALVE TRANSLATOR CHASSIS costs only £12/10/- ready for use on 230 A.C. Other voltages to order.



The Diamond Tape Recorder.
Two speeds (Diction 2 hours, Music 1 hour). Twin tracks. Fast forward wind and fast rewind. Strongly built for hard work. Can be used with any conventional amplifier or the translator. £25, including choice of tape, Diamond, Scotch Boy, E.M.I., G.E.C.

Recording/playback and erase heads for home assembly. Bandeau Type 7/6 pair. Record/playback and erase. Kit contains all parts and instructions. **Cassette Type 30/-.** Contains both record/playback and erase heads in one housing. The heads can be changed about according to tape direction (erase should precede record head). Gaps are adjustable. Cores are stacked mumetal half width for 2-way tracking. Bobbins ready wound Hi or Lo impedance to choice.

Oscillator coils 6/6. For generating 45Kc supersonic bias current and erase current. Primary and secondary windings for Hi or Lo Impedance heads.

PARK RADIO OF MANOR PARK

DISTRIBUTORS FOR JUDGE INDUSTRIES
783 ROMFORD ROAD, LONDON, E.12

Phone 1LF 2066
for demonstrations by appointment only

B.P.L. TEST SETS

NOW AVAILABLE

AT NET PRICES

B.P.L. UNIVERSAL TEST SET

£5 - 18 - 6

B.P.L. SUPER RANGER 1,000 Ω/v.

£13 - 10 - 0

B.P.L. SUPER RANGER 20,000 Ω/v.

£15 - 10 - 0

Prices include postage and packing and are applicable to Home Market only.

Send your order direct to:

**BRITISH PHYSICAL LABORATORIES
HOUSEBOAT WORKS, RADLETT, HERTS**

Tel. : Radlett 5674-5-6

The WILLIAMSON AMPLIFIER

(MODEL D)

Individually built by craftsmen to laboratory standards, our latest version of this already firmly established design sets new standards of workmanship and reliability, which, together with an unsurpassed performance, make it, we believe, the World's finest audio amplifier.

To match its exceptional performance we have designed a new pre-amplifier/tone compensation unit of extreme versatility, which features accurate compensation for all types of recordings.

PRICES :

"RD Williamson amplifier — Model D" £29 0 0

"RD Williamson pre-amplifier/tone compensation unit" £9 17 6

(Engraved control panel, 10/-)

Detailed specifications of both units will be forwarded on request. TRADE AND EXPORT ENQUIRIES INVITED. (Details of semi-tropical units available).

ROGERS DEVELOPMENTS Co.

"Rodevco House," 116 Blackheath Road,
GREENWICH, S.E.10.


Telephone : TIDeway 1723.

GOVERNMENT SURPLUS

LONDON CENTRAL RADIO STORES

DELIVERY FROM STOCK

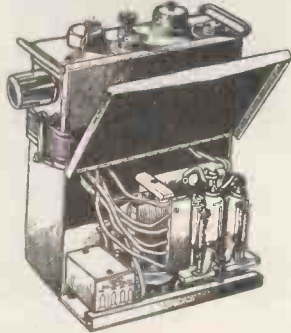TELESONIC 4-VALVE BATTERY PORTABLE
(Fixed Range). Type YA4915



Includes three XH and one XP Hivac midget valves. Can be adapted for Deaf Aid or Midget Receiver, but we do not supply information on this point. Batteries required 3 v. L.T., 97 v. H.T. In metal case, size 5½ x 7 x 2in. Weight 4lb., less batteries. Carr. and 45/- packing 2/6.
(Illustration shows chassis partly removed from cabinet.)

NEW NIFE ACCUMULATORS. 2.5v. 2½ amp./hours for 8 hours. Size 3 x 4½ x 1½in. (Flat) 6/6. Post and packing 9d.



A Fine Opportunity!
New INERT CELL ACCUMULATORS

Everlasting. No acid or charging required. Suitable for battery sets, electric bells, etc. 1.5 v. 2/10 each. Post free.

VIBRATORS

2-volt, Type R76C. 7-pin self-rectifying. Output 200 v. at 60 mA. Made by Electronic Laboratories Inc., 7/6.

Mallory, Type 650, 6-volt 4-pin American base, 7/6.

Mallory, Type G629C. 12-volt, 4-pin American base, 7/6.

COSSOR DOUBLE BEAM 'SCOPE
£47.10.0 Carr. Paid.

UNISELECTOR SWITCHES



4-bank, full wipers, 37/6.
6-bank, half-wipers, 27/6.
3-bank, full wipers, 19/6.

Have various applications, including automatic tuning circuit selection, etc. Operates on 25-50 v.

EX-R.A.F. VISION UNIT No. 62

Complete with VCR97 Tube, 3 VR05, 13 CV118, 1 CVR54, 1 EA50, 2 VR92 valves.

67/6 Carr. and pkg. 7/6

RECEIVER UNIT Type 160

Contains 4 valves: 136, 137, 91, 66 also Selector Switch, Resistors, etc. 22/6

Special Offer!

PHILCO 5-VALVE Reconditioned SUPERHET RECEIVERS

— Note Price Reductions —

We have been fortunate in purchasing a large stock of Philco Radios and each one is carefully tested before despatch. The circuits are of high gain and every set is fitted with pick-up sockets feeding a high gain L.F. valve which in turn drives an output valve usually delivering about 4 watts of audio to the speaker. All sets will take one or more extension speakers and are available in 200-250 v. A.C. or A.C./D.C. The prices quoted below are less than one-third of comparative sets on the market today. All have tone controls.

174/- ALL-WAVE TABLE MODEL incorporating two-speed tuning and provision for normal aerial or dipole. Medium or dark walnut cabinet, size 18½ x 20 x 9½in. Really excellent performance.

115/- LARGE TABLE MODEL in light walnut cabinet only, size 19 x 16 x 10½in., large dial in metres and frequency. Exceptional high gain using high "Q" IF transformers and special aerial circuit. Normal or dipole aeriels may be used.

132/- JUNIOR DE LUXE TABLE MODEL in light walnut with dark walnut banding, size 17 x 14 x 10½in., and attractive bronze metal speaker grille. Extremely selective, brightly illuminated semi-circular dial with station names. Normal aerial input. Lovely appearance.

110/- MEDIUM TABLE MODEL, known as the "Cathedral Model," receiving all British and European stations with great clarity and freedom from interference. Normal or dipole aerial input. Available in light or dark oak. Cabinet size, 19 x 14 x 10in.

95/- STANDARD TABLE MODEL. Rectangular cabinet, size 18 x 14½ x 10in. Available in either light or medium oak. Very nice tone. Receives all British and European stations. An absolute gift at only 95/- each.

Plus 10/6 per set, carriage and packing. A.C./D.C. models are 5/- less than above prices.

These sets use normal valves obtainable anywhere. Whilst it will be many years before you will require any replacements, we can supply spare valves from stock at normal retail price.

WESTINGHOUSE BATTERY CHARGERS

Size 16 x 16 x 22in. A.C. 200-250v. 50 cycles. Output 6-8v. D.C., 32 amp. Weight approx. 140lb. Price Carr. and Pkg. 20/- **£20.0.0**

Size 16 x 14 x 12in. A.C. 200-250v. 50 cycles. Output D.C. 185v. 0.75 amp. Weight approx. 50lb. Price Carr. and Pkg. 15/- **£8.15.0**

WANTED

GOOD NEW or USED EQUIPMENT

AR88's

D.B. 'SCOPES

METERS

and all kinds of

TEST GEAR,


CONVERTERS, ETC.

PHOTO ELECTRIC CELLS,
Type CV143

Small infra-red image glass converter, tube, 50-100v. Suitable for all purposes.

14/6

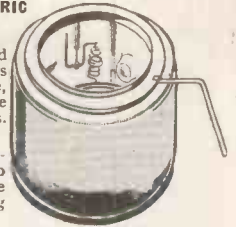N.B.—We cannot enter into correspondence regarding these cells.



MARCONI De Luxe 8-VALVE
Motor Tuning Press Button
ALL-WAVE TABLE RADIO SUPERHET

Output 8 watts from 6L6 and High Gain Pick-up input. In use with the latest high fidelity types. Together with a host of Push-Button Stations this makes a most useful receiver. You can cruise round the dial on the motor tuning.

This type of set is not available on the Home market and we are fortunate in being able to offer it to readers.

Complete with makers Inspection Book. Price **£28.0.0**

Plus 27/6 carriage and packing.



MAP READING TORCH. Powerful magnifying lens, 3in. diam. In bakelite case. Fitted with dimmer switch. Takes two U2 cells. With bulb, less batteries. **22/6**

NEW MOVING COIL MICROPHONE AND HEADPHONES, 14/6.

SELENIUM FULL-WAVE RECTIFIER
80 v. 20 amp. Size 11 x 6 x 6in. Weight approx. 12 lb. **60/-**

4-VALVE (Used) SUPERHET
UTILITY RECEIVERS

Medium Waveband Only



Four valves, P.M. Speaker, complete in pine wood cabinet size 13½ x 12 x 6½in. A.C. mains 200/250 volts. In good working order. Plus 7/6 carr. and pkg. **£4.10.0**

Please Note: All carriage charges relate to Inland Orders only • We do not issue lists or catalogues

LONDON CENTRAL RADIO STORES, 23 LISLE ST. (GERrard 2969) LONDON, W.C.2

Closed Thursday 1 p.m. Open all day Saturday and weekdays 9 a.m.—6 p.m.

RIALTON RADIO

AMAZING VALUE!

**COMPARE
OUR
PRICES**



Brand new 5 valve 3 waveband radiogram, marvellous walnut cabinet, 10" speaker, automatic record changer, 10-10" or 12" records, record storage compartments, £42 16s. 9d. while stocks last.



5 valve 3 waveband chassis for A.C. or A.C./

D.C. Not a kit, fully tested, complete with valves and 8" speaker. £9 17s. 6d.

5 valve 3 waveband table model, 4 watts output, 8" speaker. Few only, A.C. and A.C./D.C. Full size walnut cabinet, £15 16s. 6d.

- ALL MODELS ● FULLY GUARANTEED FOR ONE YEAR
- 7 DAYS' FREE TRIAL
 - MONEY BACK IF NOT SATISFIED
 - MADE BY WORLD FAMOUS MANUFACTURER

Send for complete illustrated catalogue of hundreds of cut price radio and television components.

TERMS—Cash with order, carriage free London Area. Provinces 5/- extra, chassis or table model ; 15/- radiogram.




DON'T WASTE TIME—JOIN OUR MAILING LIST
75 BELLENDEN RD., PECKHAM, S.E.15 Phone: RENown 4904

The BIJOU

This ever popular Wharfedale speaker combines attractive appearance, handy size and moderate price. Fitted with the Standard 8" Unit. Handles 3 watts.

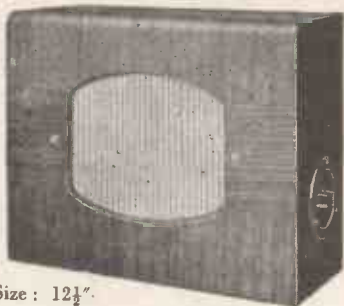Hand polished Walnut and fitted with volume control and 5' of P.V.C. flex. Weight 5½lbs. Size: 12½" x 10" x 5½".



ALSO AVAILABLE IN LIGHT MAPLE VENEER AT SAME PRICE

90/-

Wharfedale
WIRELESS WORKS

BRADFORD RD., IDLE, BRADFORD, YORKS

Telephone: IDLE 461

EXPORT & WHOLESALE

Valves Receiving ★ Valves Transmitting

Tubes Cathode Ray

Both British and American makes. Govt. surplus and regular types, including special purpose tubes. No dollar expenditure involved. We can offer rapid delivery from our ample stocks. One of the largest in England.

Large stocks of:—

P.M. Speakers Transformers
Condensers, etc.



V.E.S. WHOLESALE SERVICES LTD.

11, GUNNERSBURY LANE, W. ACTON, W.3.

Telephone: ACOrn 5027 (3 lines).

THE *New* WINDSOR

TEST METER

20,000 o.p.v.

MODEL 77A



An entirely new instrument incorporating the latest improvements in manufacturing technique. Refinements include shockproof moulded case, clear and easy to read scales and many other features.

Price **£16 . 0 . 0** LIST PRICE

SENSITIVITY

20,000 ohms per volt D.C.

5,000 ohms per volt A.C.

OVERLOAD PROTECTION

Meter movement has instantaneous overload protection, effective on all ranges.

BUZZER

A Buzzer is fitted internally for quick continuity testing.

METER

Precision engineered moving coil, fitted with 5" scale and knife-edge pointer.

SWITCHING

One switch selects both circuit and range. Heavily silver plated beryllium copper switch contacts ensure low loss and trouble-free operation. Large 2" milled knob for easy handling.

RANGES

VOLTS D.C. 0-7.5-30-75-300-750-3,000

VOLTS A.C. 0-7.5-30-75-300-750

RESISTANCE 10 ohms-5 megohms in two ranges, self contained.

MILLIAMPS D.C. 0-15-15-15-150-1500

AMPERES D.C. 0-15.

OUTPUT. As for A.C. volt ranges except 3,000 v., via a condenser.

Please write for illustrated leaflet featuring our new range of radio and television test gear.

TAYLOR ELECTRICAL INSTRUMENTS LTD.

419-424 MONTROSE AVENUE, SLOUGH, BUCKS.

Phone: SLOUGH 21381



EXCEPTIONAL OFFER ! (EXPORT ONLY)

UNUSED U.S.A. RADAR EQUIPMENT

TYPE S.Q.
TYPE S.G.A.
TYPE S.G.I.

All equipment is tropical packed.
Complete range of Equipment, Stock and
Tender Spares ; large stocks available.

A.M. RADAR EQUIPMENT

TYPE H2S.

Reconditioned, with A.I.D. Certificates.

INSTALLATION AND MAINTENANCE SERVICE AVAILABLE

SALWAY MORGAN & CO. LTD.

PHONE 840, 841, 842. POOLE DORSET
GRAMS SERVICES, POOLE

“You’re **CERTAIN** to get
it at **ARTHURS!**”

★ **VALVES** : We have probably the largest stock of
valves in the country. Send your enquiries.

AVO METERS IN STOCK.

| | |
|------------------------------------|----------|
| Avo Model 7 | £19 10 0 |
| Avo Model 8, high resistance | £19 10 0 |
| Avo Model 40 | £17 10 0 |
| Heavy Duty | £13 13 0 |
| Avo Minor, AC/DC model | £10 10 0 |
| Electronic Test Meter | £40 0 0 |
| Signal Generator | £30 0 0 |
| Valve Characteristic Meter | £50 0 0 |
| Universal Bridge | £26 0 0 |

★ **Cossor Oscillograph Model 1035** £85.0.0

VALVE MANUALS

Mullard 5/- ea.
Mazda : Part 1, 1/-, Part 2, 2/-
Brimar Teletube and 4/-
Radio Mullard Valve Replacement Guide 1933-49, 2/6
Post 6d. each extra.
Send for catalogue.

TAYLORS METERS. List on request.

| | |
|---------------------------|---------|
| DECCA PICK-UPS | £3 15 5 |
| DECCA HEAD | £2 19 2 |
| ADAPTOR for Gerrard | 3 8 |

All goods offered subject to price alterations and being unsold.

LONDON'S OLDEST LEADING RADIO DEALERS

Arthur's


EST. 1919

PROPS: ARTHUR GRAY, LTD. Terms C.O.D. or cash with order

Our Only Address. Gray House, 150/152 Charing Cross Rd., London, W.C.2
TEmple Bar 5833/4 and 4765
ELECTRICAL, TELEVISION & RADIO ENGINEERS

HIGH GRADE LABORATORY EQUIPMENT

REBUILT AND GUARANTEED AS NEW

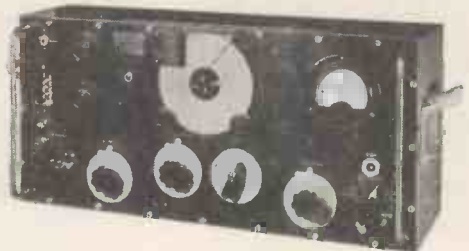

SIGNAL GENERATOR TYPE T.F.144G

WE HAVE A COMPREHENSIVE STOCK OF WHICH THE FOLLOWING IS A SMALL SELECTION

| | |
|--|------------------------------|
| Valve Voltmeters Type TF428B | Signal Generator Type TF144G |
| Oscilloscope Type 208 Dumont | " " " TF517F |
| Oscilloscope Type 224 Dumont | " " " TF390G |
| Frequency Meter BC221AK | " " " 804B |
| G.R. Standard Air Condenser Type 722-F85 | |

For further particulars of this and other high-grade electronic instruments, write to :—

HATFIELD INSTRUMENTS
175 UXBRIDGE RD., HANWELL, LONDON, W.7
Telephone: EALING 0779


YOU'LL FIND THE GEAR YOU NEED AT THE RADIO CENTRE!

Last month we issued a comprehensive list of hire purchase facilities available on our varied stock. Additional items are detailed below, as well as the latest releases available.

INTRODUCING THE LATEST M.O.S. 'EASY-TO-BUILD' KIT:

THE QUALITY GRAND AMPLIFIER

- Frequency Response \pm 0.5 db
- 30 c/s—12 kc/s.
- Distortion 0.45% total at 1,000 c/s for 8 watts.
- Maximum power output 10 watts.
- High gain input.
- Low gain input.
- Bass boost/cut.
- Treble boost/cut.
- Negligible phase shift.
- 20 db. Negative feed back.
- 3, 7.5 and 15 ohm outputs.
- Neg. feed back loop incorporates output transformer, p.p. output stage, phase inverter and driver.
- For A.C. mains.

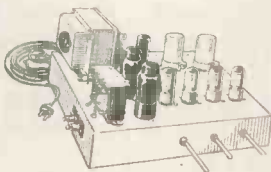

Complete in kit form with all valves and components, pre-drilled chassis, down to nuts, bolts and solder, etc. Supplied with comprehensive illustrated construction manual.


A 7-valve amplifier designed for the connoisseur and comparable in performance to amplifiers costing several times the price of the Quality Grand. Send for instruction manual to-day! (Cost credited if kit is eventually purchased.) Better still, call and see the Quality Grand demonstrated without obligation in our showroom.

Suitable associated equipment is advertised below.

£9:19:6
complete carriage paid.

H.P. terms: £3 down and 12 monthly payments of 15/-. Instruction manual only 4/6, post free.

RADIO FEEDER—TYPE RF1

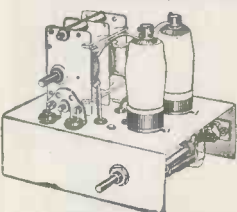

Designed for use with A.C. operated amplifiers, the Radio Feeder RF1 employs a two-stage T.R.F. circuit giving a high quality output. By the use of high-gain pentode valves, sensitivity is such that the unit can be operated in areas of only moderate signal strength. Like all M.O.S. kits, the instructions are simple to follow, the instruction manual being liberally illustrated with precise diagrams. The kit itself is complete in every detail from a pre-drilled chassis, valves, coils, etc., to nuts and bolts and solder.

Instruction Manual (containing full details) 2/-.
RF1 Feeder Unit Kit with Manual **£2 12 6**

LOUDSPEAKERS

| | Cash | H.P. Deposit | 12 Monthly Payments |
|--|----------|------------------|---------------------|
| MILNES | | | |
| Super 10in. Chassis | £12 12 0 | £3 12 0 | 18 4 |
| EXTENSION SPEAKERS | | | |
| RM in plastic cabinet with volume control | £1 19 11 | (plus 2/6 carr.) | |
| EKCO ES 115 in plastic cabinet. Various colours. | £2 17 6 | (plus 2/6 carr.) | |
| BAKERS | | | |
| 12in. Triple Cone | £8 5 0 | £2 15 0 | 12 6 |
| 18in. Duplex | £12 12 0 | £4 12 0 | 16 8 |
| 12in. Single Cone | £6 15 0 | £2 15 0 | 10 0 |
| VITAVOX | | | |
| K12/10 | £8 10 0 | £3 0 0 | 12 6 |
| WHARFEDALE | | | |
| Super 8 cs | £4 7 6 | — | — |
| Bronze 10in. (3 or 15 ohm) | £3 2 6 | — | — |
| W.B. STENTORIAN | | | |
| Duplex with trans. | £7 15 0 | £2 5 0 | 12 6 |
| GOODMANS | | | |
| Audiom 60 | £8 12 6 | £2 12 6 | 13 4 |

ELECTRIC TOOLS

Accredited dealers for Wolf and Handy Utility. We can supply any type on hire purchase terms.

MOS MAIL ORDER SUPPLY
THE RADIO CENTRE
(Dept. WW12)
33 Tottenham Court Road, London, W.1

The Latest in Gramophone Equipment!

- THE PLESSEY MULTI-SPEED AUTO. CHANGER**
£23/13/0 or £7 DOWN and 12 monthly payments of 31/6.
This unit can be supplied mounted on desk of handsome walnut for £25/5/2 or £8 DOWN and 12 monthly payments of 32/6.
 - THE COLLARO RC5II SINGLE SPEED AUTO. CHANGER**
A non-mixing changer for 78 R.P.M., complete with pick-up, £11/18/4 or £4 down and 12 monthly payments of 16/8. Similar model mounted on desk £16/10/0 or £5 down and 12 monthly payments of 22/6.
 - THE COLLARO 3 RC5II 3-SPEED AUTO. CHANGER**
Complete with pickup and dual purpose head and mounted on a handsome metal desk enclosing the motor, £18/10/0 or £6/10/0 down and 12 monthly payments of 23/4.
 - THE COLLARO MICROGRAM DE LUXE 3-SPEED AUTO.**
A complete player with amplifier. £36/3/10 or £12 down and 12 monthly payments of 45/-.
 - THE COLLARO MICROGRAM DE LUXE 1-SPEED AUTO. OR 3-SPEED NON-AUTO.**
£31/3/6 or £10 down and 12 monthly payments of £2.
 - THE DECCA MU10.** 75/- or 20/- down and 12 monthly payment of 7/9.
 - THE DECCA MU14.** £7/3/4 or 43/4 down and 12 monthly payments of 11/8.
 - THE DECCA 348C.** 3-speed unit in handsome case, £22/1/0 or £7 down and 12 monthly payments of 29/-.
- * All other players and motors as previously advertised are still available from stock.

The Latest in Magnetic Recording!


- THE LANE TAPE DECK.** £16/10/0 or 130/- down and 20/- per month (12).
- THE QUALTAPE DECK.** £13/13/0 or 73/- down and 20/- per month (12).
- THE SIMON TAPE RECORDER "SIMPHONIC."** £60 or £20 down and £3/15/0 per month (12).

MOTORS by BSR

Type FP10 38/-. SRI 32/-. SR2 25/-.

MOTORS by Collaro

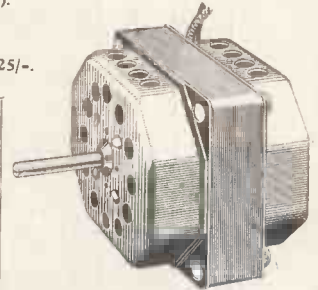with cooling fan. 42/- or matched pair 84/-.



INCREASED RANGE OF TAPES!

- E.M.I. 1,200ft. high or low coercivity 35/- reel. 600ft. low coercivity 21/- reel.
- G.E.C. 1,200ft., 30/- per reel.
- SCOTCH BOY. 1,200ft., 35/- per reel.
- PHILIPS (homogeneous). 40/- per reel. Spare 1,200ft. spools 4/6.

OSCILLATOR UNITS

Lane type OC/1 Erase and bias generator unit 70/-.
OC/2 Oscillator coils, 10/-.
Tamsa Oscillator coils, 10/6.
The well known TAMSA heads are still available at £2/19/6 for any type, i.e., Playback, Record/Playback or Erase.

MANUALS

"Magnetic Tape Recording," by Begun, 25/-.

MICROPHONES

ACOS M.I.C. 22-2, £6/6/0 or 36/- down and 12 monthly payments of 10/10.
RESLO RIBBON. £7/10/0 or 50/- down and 12 monthly payments of 11/6.

VALVES AND CRTs

- 9in. Mullard or Mazda C.R.T. £5 deposit, 12 monthly payments of 18/-.
 - 12in. Mullard or Mazda C.R.T. £5/4/10 deposit, 12 monthly payments of 25/-.
 - 12in. Brimar C12B. £5/7/8 deposit, 12 monthly payments of 27/-.
- Cash price £19/7/8.
Quotations given on request for tubes not listed.

ALL TYPES OF B.V.A. VALVES CAN BE SUPPLIED ON H.P. TERMS PROVIDED THAT THE TOTAL CASH PRICE EXCEEDS £10 BASED ON CURRENT B.V.A. LIST PRICES. ENQUIRIES FOR QUOTATIONS INVITED.

For IMMEDIATE DELIVERY From OUR LARGE STOCKS

VARNISHED COTTON SLEEVING various colours $\frac{1}{2}$ m.m.—20 m.m.

RESISTORS

HIGH STABILITY, close tolerances $\frac{1}{4}$, $\frac{1}{2}$, 1 and 2 watt.

All values up to 2 meg. also 8, 13 and 30 meg.

CARBON—2 watt and 5 watt.

Standard Car Suppressors 15,000 ohms.

CAPACITORS

Block Paper, Silvered Mica, Mica and Ceramic
also .1 MF SUPPRESSORS with Flying Lead.

SWITCHES

OAK, YAXLEY, WAFERS and LOCATORS

LAMINATIONS

RADIOMETAL 30, 31, 39 and 40

MU-METAL 35

WIRES

DOUBLE RAYON REGENERATED CELLULOSE
28 gauge

PLAIN COPPER DOUBLE REGENERATED
CELLULOSE 7/35 S.W.G.

PLUGS AND SOCKETS

PYE PLUGS and SOCKETS

JONES PLUGS and SOCKETS, 4, 6, 8, and 10-way

See also our November advertisement page 18 for CINCH COMPONENTS
WHOLESALE, MANUFACTURERS AND EXPORT ENQUIRIES ONLY

RADIO TRADERS LTD

23 WARDOUR ST., LONDON, W.1

Phone: GERrard 3977/8

Grams: "Radiotrade"

CONSTANT VOLTAGE POWER SUPPLY UNITS

MODEL 101-C

Output: 250/400v. 0.250mA max.
Stability: Better than 0.1%.
Output Impedance: Less than 1 ohm.
Output Ripple: Less than 2mV. R.M.S.
Mains Supply: 200/250v. 45-60c/s.
Regulation down to zero load.



DETAILS ON REQUEST.

ALL-POWER TRANSFORMERS LTD.

CHERTSEY ROAD, BYFLEET, SURREY.

Tel: Byfleet 3224/5.

ALL the A.C. power you require
from your D.C. supply

with a

Valradio



D.C./A.C. CONVERTER

Models for Electric Gramophone from £8, plus 10%

Models for

- Radio-grams and Autochange Radio-grams (inc. 3-speed motors)
- Radios
- Televisions, etc., from £10.15.0, plus 10%

Input, 6, 12, 24, 32, 50, 110 or 200/250V. D.C.
Output 230V. 50 or 60 c/s.

Valradio

Descriptive literature W.W. 10 from the manufacturers:-
NEW CHAPEL ROAD, HIGH ST., FELTHAM, MIDDX.
Tel.: FELtham 4242.

Service Dept.: 57 Fortress Road, London, N.W.5. Tel.: GULLiver 5165.

Overseas Enquiries to nearest E.M.I. Organisation Depot.

Let's have
"THE GONDOLIERS"
AGAIN!



Whatever your favourite piece of music, the Soundmirror will record it and play it back for you again and again. There is no end to the thrills which this new magic entertainer can bring. It will record the humorous patter of your favourite comedian, the art of the orator, the fun of a party or important family occasions like weddings. It will play them back with perfect fidelity immediately it is recorded and as often as you wish. Unwanted recordings are automatically erased as new ones are made and the magnetic tape used time and time again.

MODELS FROM £69, 10.0 exclusive of microphone.

Manufactured under agreement with the Brush Development Co., of the U.S.A. Licensed under the Brush Development Co., the Brush Crystal Co., Magnetone Inc., and Thermionic Products Ltd. Patent No. 454595 and others; and patents pending in all the principal countries of the world.

THE
Soundmirror
MAGNETIC TAPE RECORDER

Now available in England—the book "Magnetic Recording" by Dr. S. J. Begun. A comprehensive treatise. Price 25/-, postage 9d. extra

Call on your local radio dealer and hear your own voice recorded or write for literature or a demonstration by appointment to the manufacturers.

THERMIONIC PRODUCTS LTD.


(Division SM/WW), Hythe, Southampton. Phone: Hythe 3265

London Showrooms: **Morris House, Jermyn Street, S.W.1**

Telephone: Whitehall 6422 (5 lines). Sales and Service Centres: Manchester Birmingham, Bristol, Leeds, Newcastle, Glasgow, etc.

Cold Cathode Diode

NT 2

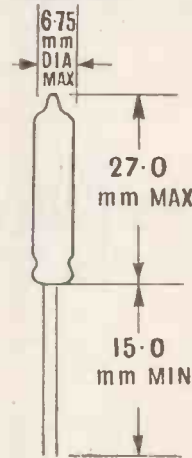

The NT2 is a very small cold cathode diode of wide application: e.g., in counters, storage circuits, low current stabilisers and so on.

It is moreover an ideal indicator tube giving a clear bright indication with currents as low as 0.3 mA.


RATINGS

| | |
|---|---------------|
| Nominal strike voltage .. | 80 V. |
| Nominal maintaining voltage at 0.5 mA. .. | 60 V. |
| Maximum power dissipation | 0.06W. |
| Maximum current for continuous operation | 1mA. |



**GREENHILL CRESCENT
HARROW-ON-THE-HILL, MIDDX.**

Telephone: HARrow 2655

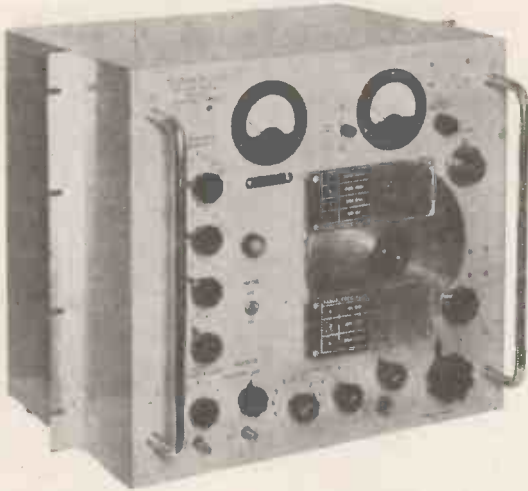

Power supplies :
200 — 250 Volt. 50 c/s

Range of measurements;
through levels + 10 db to - 61.5 db
or terminated levels + 10 db to - 81.5 db
referred to 1mW in 75 ohms

SELECTIVE TRANSMISSION MEASURING SET MODEL RP 3110

Designed and manufactured for G.P.O.

This is a precision instrument for measurements on multi-circuit coaxial cable carrier systems by means of a comparison with locally generated signals of known frequency and level.

Frequency coverage; 60 Kc/s—3 Mc/s in 7 ranges.

Calibration accuracy: below 0.2% or 2 Kc/s whichever is the greater.

BRITISH COMMUNICATIONS CORPORATION LTD.

GORDON AVENUE, STANMORE, MIDDX.

Telephone : GRIMSDYKE 2266

Cables : DISC, STANMORE

GEE Pros. RADIO Ltd.

Belling-Lee 5, 7 and 10-pin plugs and sockets.
465 k/c. I.F.T.'s standard and semi-midget sizes.

Systoflex and P.V.C. sleeving.

813 Ceramic valve holders.

H.T. and L.T. metal rectifiers.

12-100 watt W.W. Porcelain resistors.

Photo-Electric Multipliers 931A

C.R.T.'s and special purpose valves.

12in. Table model T.V. Cabinets.

12 v. D.C. to 230 v. A.C. Rotary Convertors.

Tropical Carbon Potentiometers.

Magnetic throat-microphone capsules.

Mansbridge paper capacitors.

2½in. Round flush mounting 0-20 amp. A.C. meter.

R.C.A. 100 K.C. Crystals.

Wavemeter Class D, I-Mk. II.

Etc., etc., etc.

May we have your enquiries. Delivery ex-Stock.

We carry a very large stock of good clean and unused material, and can quote keen and competitive prices to manufacturers, and wholesale and export buyers.

15 LITTLE NEWPORT ST., LONDON, W.C.2
GERrard 6794/1453

BRIERLEY DIAMOND MICROARMATURE PICK-UP

This new pick-up has many noteworthy characteristics, some of which are listed below :—


1. The mass of the moving parts is less, we believe, than in any other pick-up of any type—other than our own Ribbon which is, of course, unique.
2. The output voltage—about 1/25th v.—is high enough to cause no trouble.
3. It is sufficiently robust to be used by any reasonably intelligent and careful family.
4. The use of a diamond point has, *inter alia*, the enormous advantage that a very large number of records may be played with negligible point wear. This results in a sustained "new" performance together with the elimination of that mental irritation at the gradual and perceptible "falling off" unavoidable with less wear-resistant points.
5. Organised production on a reasonable scale should give us a satisfactory "spares" and repair service and has enabled us to produce this pick-up at a price which many may at first have believed to be either a mistake or a printer's error.

Pick-ups, types JB/P/A/1D (78) and JB/P/A/1MD (LP) £6/0/0. Purchase Tax, £2/12/-

Mumetal Coupling Transformer, type JB/T/A, £1/5/-.

Full details sent on request.

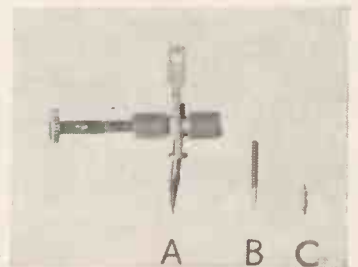J. H. BRIERLEY (Gramophones and Recordings) LTD.
KIRKBY TRADING ESTATE . LIVERPOOL



Photograph of A. Standard Needle, B. Miniatur Needle and C Brierley Microarmature.

HOLLEY'S Radio



H. J. Leak Amplifier

RC/PA/U



Q.U.A.D. Amplifier



Wharfedale
Super 5 CS/L

NOW IN STOCK

LEAK "POINT ONE" AMPLIFIERS. Price 27 Guineas. **RC/PA/U.** 9 Guineas. **SUPERHET RADIO TUNER,** £25/10/-. Plus Purchase Tax. **ACOUSTICAL Q.U.A.D. AMPLIFIER.** Price £35. **Q.U.A.D/R.** Radio Tuner Unit, £26, incl. tax.

SOUND SALES "A-Z" AMPLIFIER with **TONE COLOUR** tone control unit Price £32/10/-. New model **"TONE-MASTER" AMPLIFIER** with **TONE COLOUR** control unit. Price £25/10/-. New improved version of **"DX PLUS ONE" RADIO TUNER** also available.

WILLIAMSON AMPLIFIER. Junior version by **GOODSELL Ltd.** Price £22/10/-. **PRE-AMP** for **WILLIAMSON,** fitted with tone control and low pass filter. Price 11 Guineas.

ROGERS "BABY DE LUXE" amplifier, complete £17/10/-. **"RD JUNIOR DE LUXE"** amplifier (KT66), £.5.

ARMSTRONG Model 73 All wave Chassis and Model 104.

Recommended SPEAKERS

VOIGT DOMESTIC CORNER HORN (in white), £47/10/.

P.M. UNIT, £40.

TANNOY DUAL CONCENTRIC, £27/10/-. 12in. model.

WHARFEDALE SUPER TWELVE C.S.A./L, £15, also **SUPER FIVE C.S.A./L.** **DECCA CORNER SPEAKER.** Price £21/10/-.
BARKER 150 SPEAKER UNIT. 18 Gns.

Other items in limited numbers.

CONNOISSEUR TWO SPEED MOTORS, £20/19/3.

THREE SPEED AUTOCHANGE UNITS. Prices from £15/11/9.

RADIOGRAM CABINETS, from £12/10/-.
DECCA XMS Pick-ups, £7. **ACOS GP20,** £3/11/5. **CONNOISSEUR Super Lightweight,** £10/0/8.

Side by side demonstrations of the above equipment any time during business hours 9.30 a.m.—1 p.m. 2—6 p.m. Thursday 9.30 a.m.—1 p.m.

HOLLEY'S RADIO STORES

285, CAMBERWELL ROAD, LONDON S.E.5

Open all day Saturday - - - - Callers only

Telephone : RODney 4988



CLEAR PICTURES in "poor reception" areas

The models 63 and 63A have been designed for maximum performance in fringe and difficult reception areas. Since the reception of your TV receiver is wholly dependent on the efficiency of the aerial system, the Aerialite features of greater gain, broader bandwidth and sharper directivity are very worthwhile. There is every reason why you should specify Aerialite for your TV aerial if you wish to ensure strong, clear and interference-free pictures. The models 63 and 63A are priced at: £12.15.0 and £13.5.0 respectively, complete with 10ft. masts, lashings, etc. Models with 14ft. masts are available at 17/- extra. Aerialite are manufacturers of a comprehensive range of TV and radio aerials as well as coaxial and R.F. cables.



Aerialite LTD.
CASTLE WORKS STALYBRIDGE CHESHIRE

The Picture
can ONLY
be as good
as the
AERIAL -
be sure with



Telerection
specially for Fringe Areas
Antenna Works, St. Paul's
CHELTENHAM Telephone Cheltenham 55960

**TO HAMS & DEALERS
WE WANT TO BUY**

**AMERICAN SURPLUS
EQUIPMENT OF EVERY KIND
FOR RADIO HAM SHACK -
NEW YORK'S LEADING DEALERS**

**RECEIVERS TRANSMITTERS
TEST SETS SIG GENS
EVERYTHING ELECTRONIC**

We are interested in any quantity, from one upwards.
Phone us immediately, transfer charge.

**ALTHAM RADIO CO BRAZENOSE ST
MANCHESTER 2 Tel: DEAnsgate 5387**



Dept. W.W.
**18 TOTTENHAM
COURT ROAD,
LONDON, W.1**
Tel.: MUSEum 2453/4539

Shop Hours: Monday-Friday 9—5.30 Saturday 9—1

RELAYS

D.C. COIL RESISTANCE

3,000 TYPES: 1.9Ω to 80,000Ω
600 TYPES: 0.4Ω to 9,200Ω.

ALSO LARGE STOCKS OF
DOUBLE & TRIPLEWOUND
AND SLUGGED COILS.


CONTACTS

3,000 TYPES: up to 8 sets.
600 TYPES: up to 4 sets.


3,000 TYPES: Make (M), Break (B),
in Twin-silver, Twin-platinum, Dome-
silver (2 amp.), Tungsten (5 amp.),
and Flat-silver (8 amp.). Change-
Over (C), in all but Tungsten; Make-
Before-Break (K), in Twin-silver and
Twin-platinum.

600 TYPES: (M), (B) and (C), in
Twin-silver and Twin-platinum.

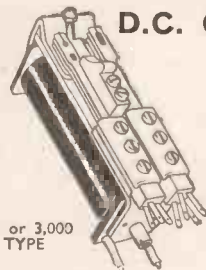SPECIAL
S.T. & C. Type Polarised Relays:
6 Coils—180 ohms + 180 ohms + 180
ohms + 180 ohms + 115 ohms + 115
ohms on same bobbin.
Contacts—Single change-over:
Dimensions: — 3½in. x 3½in. base.
6½in. overall height.



600 or 3,000
TYPE

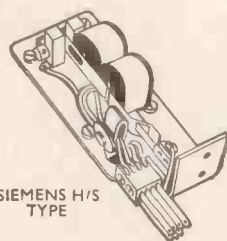


SIEMENS H/S
TYPE

COLLARO

QUALITY PRODUCTS

The Collaro 3RC521 Record Changer

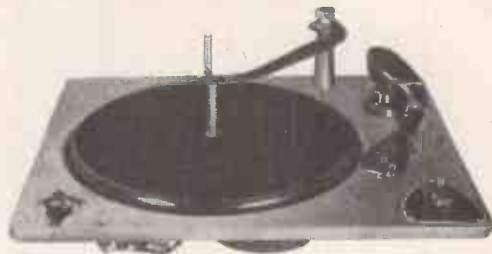A completely automatic three-speed changer designed to play 33 $\frac{1}{3}$, 45 and 78 r.p.m. records—with a minimum need for adjustments. Fitted with a pickup arm, suitable for all types of Collaro Plug-in heads. Beautifully made and completely foolproof.



The Collaro 3/514 Gramophone Unit

A brilliant three-speed unit which incorporates all the accepted Collaro features... patented 3-speed drive... spring suspension... plug-in pickup heads.




Both models mentioned are suitable for A.C. Supplies.

They're three-speed. They "Take all Records!"

COLLARO LIMITED

MAKERS OF FINE QUALITY GRAMOPHONE COMPONENTS, RECORD CHANGERS AND GRAMOPHONE UNITS, PORTABLE ELECTRIC GRAMOPHONES, INDUCTION MOTORS, PICKUPS AND PLUG-IN HEADS.

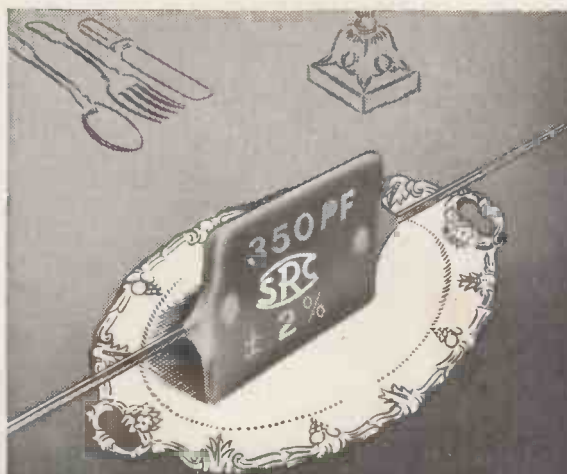RIPPLE WORKS · BY-PASS ROAD · BARKING · ESSEX
 Phone : Rippleway 3333 Telegrams : Korllaro, Barking



Precious Silver

In these days of steadily rising raw material prices precious Silver has become even more precious. For Silver, however, there is no substitute; Electrodes of our Capacitors are made from pure Silver; Contact Foils and Wire Ends are Silver plated.

The specialists for Silver Mica Capacitors

STABILITY RADIO COMPONENTS LTD.

COMMERCE ESTATE, WOODFORD AVENUE, LONDON, E.18.

BUCKHURST 6501/2

with confidence, as only OKERIN Waxes are used.

Yours faithfully,

J. Power Factor

A. M. I. E. E.

P.S. Waxes are small in bulk, but bulk large in importance, - they must be just right for the job, and reliable. Always Specify OKERIN.

Sales Department

ASTOR BOISSELIER & LAWRENCE LTD.

9, SAVOY STREET · STRAND · LONDON · W.C.2

Works and Laboratories · WEST DRAYTON · Middlesex

McELROY-ADAMS MFG. GROUP LTD.

(Sole concessionaires U.K. for Hallicrafter communication equipment)

46 GREYHOUND ROAD, LONDON, W.6.

SPECIAL PURPOSE AND TRANSMITTING VALVES.

| | | | |
|---------------------|------------|----------------------|-----------|
| Eimac 304 T.H. | 130/- each | Taylor T200 | 60/- each |
| Hytron H.Y. 65 ... | 90/- .. | R.C.A. C.R.C. 860... | 15/- .. |
| Raytheon R.K.28A... | 90/- .. | H.K.257B | 70/- .. |
| P.T.15 | 10/- .. | R.C.A.8308 | 20/- .. |

PANORAMIC ADAPTOR.

Model R.B.W.2. Suitable for use with the Hallicrafter receivers 527 and 536 or any communication receiver having an intermediate frequency of 5.25 megacycles. Price £45 each.

TRANSMITTER ARMY No. 12.

Frequency Coverage 1-17.5 Mc/s in four switched bands. C.W. and Phone built in modulator. Watts output 25. Operated from A.C. mains 100-250 Volts and complete with all tubes and delivered £25 each, carriage paid.

TRANSMITTER 1154.

Three band transmitter with all valves and in transit case. Bands, 200-500 Kc/s, 3.0-5.5 Mc/s, 5.5-10 Mc/s. £5/10/- each, carriage paid.

TUNING UNITS B.C.375E.

T.U.5, T.U.6, T.U.7, T.U.9, T.U.10, T.U.26. All 22/6 each.

SPEECH AMPLIFIER.

For use with R.C.A. Transmitter E.T.4336, complete with all valves. (British made). £24/10/- each, carriage paid.

Cables : Hallicraft, London.

Phone : FULham 1138/9.

G2AK This Month's G2AK Bargains

R.C.A. 100 Kc/s. 3-pin sub standard Xtals, £1 each.

C.R. TUBES Type 5CPI brand new in cartons 17/6 each, plus 1/6 postage.

T.V. TUBE MASKS. 12in., New Ratio, brand new, 15/- each, post free.

MOVING COIL HEADPHONES with moving coil microphone. Price 6/-. Post 1/-. Transformer to match 2/-. Balanced Armature L.R. Phones, 9/6 per pair.

TWIN RIBBON FEEDER. Heavy duty 300 ohm. 5d. per yd Standard K25 300 ohm ribbon, 9d. per yd. Co-ax. cable, 1/2 in. dia 70 ohm., 8d. per yd. 1/2 in. dia., 1/3 per yd 7ft. length 1/2 in. dia. Co-ax. with Pye plug one end, 1/6, post free. All other Co-ax., and feeder, plus 1/6 post any length.

POTENTIOMETERS. 5 watt wire-wound 20 k., 25 k., 2/- Carbon Type Potentiometers, 50 k., 100 k., 1 meg., 2 meg., 1/6.

TRANSMITTING TUBES. Type 807, 10/- ea. Type 813 New and Boxed £3/10 each. 723 A/B Klystron £3 ea. Type 866A, 17/6 each. Few only.

METERS. 2 1/2 in. Flush mounting M.C. 100 mA., 500 mA., and 20 mA. 12/6 each. 2 in. Flush M.C. 500 Microamp, 10/- 5 mA., 7/6, 2 0.5 Amp. Thermo, 5/-. Special Offer 2 1/2 in. Flush 0-1 mA Rectifier meter, scaled 0-10 volts, 22/6 each. Few only.

CERAMIC 2 Bank, 4 Pole, 4 Way Switches, 3/9 each. Post free. CERAMIC COIL FORMERS. 5 1/2 in. long by 2 1/2 in. diameter ; threaded 24 grooves, 4/6 each, post free.

JONES PLUGS. 8 pin, male and female 1/6 per pair, 12/- per dozen pairs.

Carriage paid on all orders over £1 except where stated. Please include small amount for orders under £1.

Please print your name and address.

CHAS. H. YOUNG, G2AK

All Callers to 110 DALE END, BIRMINGHAM

Phone : CENTRAL 1635.

Mail Orders to 102 HOLLOWAY HEAD, BIRMINGHAM

Phone : MIDLAND 3254.

Good Points of *Superspeed* **ACTIVATED** COLOURED ROSIN CORED SOLDER

- ★ Coloured Core provides coloured rosin residue for ready identification.
- ★ Choice of red, blue, green, purple or yellow core.
- ★ Stellate Core cross-section for quick melting and fluxing.
- ★ Activated Rosin Core for fast working and absence of corrosion.
- ★ Identical—except for colour—with the famous Superspeed White Flash Cored Solder.
- ★ Residue solidifies to a hard, semi-transparent film of high dielectric strength.

Let us send you full technical details of the new Coloured-core Solder.

We are established specialists in the production of solders and fluxes for every type of pre-tinning, dipping and soldering in electrical, radio and similar jointing and assembly work. If you are engaged in manufacture in this field it is almost certain that we can be of service to you. Make an appointment for a member of our Technical Sales staff to call on you.

H. J. ENTHOVEN & SONS LTD

ENTHOVEN HOUSE,
89 UPPER THAMES STREET, LONDON, E.C.4

Telephone : MANsion House 4533
Telegrams : Enthoven, Phone, London.

Works :
CROYDON, ROTHERHITHE & DERBYSHIRE

Estd.

L.R.S.

1925

For **PROMPT** and **EFFICIENT SERVICE**

CASH or **EASY TERMS**

We have a limited stock of the following equipment available for immediate delivery.

ARMSTRONG ALL-WAVE CHASSIS

MODEL EXP. 73. Cash £25/12/4 or £7/15/- with order and 10 monthly instalments of 40/-.

MODEL RF. 103. Cash £28/16/- or £8/15/- with order and 11 monthly instalments of 40/-.

MODEL RF. 104. Cash £34/12/10 or £11/10/- with order and 13 monthly instalments of 40/-.

Passenger carriage 10/- extra payable with deposit.

W. B. CONCENTRIC-DUPLEX LOUDSPEAKERS

The unit for the Connoisseur. Each unit constitutes two separate loudspeakers, concentrically mounted and having its own speech coil, gap and diaphragm. Should not be confused with the twin-cone type.

10in. MODEL. Cash £7/7/- or £2 with order and 6 monthly instalments of 20/-.

12in. MODEL. Cash £18/18/- or £5/5/- with order and 8 monthly instalments of 40/-.

Both the above complete with transformer and Cross-over Network.

Specification of any of the above on request

TEN FREE SHAVES

with the

NEW SUPER REMINGTON

'CONTOUR

6'



ELECTRIC SHAVER

will convince you that it really does give a better, more pleasant and far quicker shave. Once you have tried this remarkable new shaver, we feel confident you will agree.

TEN DAYS' FREE TRIAL

on receipt of 50/- deposit (returnable if shaver not entirely satisfactory) with 7 monthly instalments of 20/- AC/DC 209/250 v.

CASH PRICE £8.19.5

Other voltages available. Every shaver is **BRAND NEW** and despatched in superb silk-lined presentation case per reg. post. Prompt despatch guaranteed.

Write for detailed Brochure.

The L.R. SUPPLY COMPANY Ltd.

(LONDON RADIO SUPPLY CO.)

BALCOMBE - - SUSSEX

Telephone : Balcombe 254

A QUESTION FOR DESIGNERS



Circuits progress ; new cases will evolve from new materials and techniques—but the one outstanding feature of tomorrow's battery radio is here today—


VENNER

Lightweight Accumulators

One third the weight and half the size of standard accumulators of comparable capacity, these revolutionary miniature storage batteries maintain a steady 1.5 volt output on load throughout their discharge period.

Thus they eliminate the need for constant replacement due to voltage drop, which is the failing of all other conventional L.T. batteries. In addition, Venner Lightweight Accumulators are completely

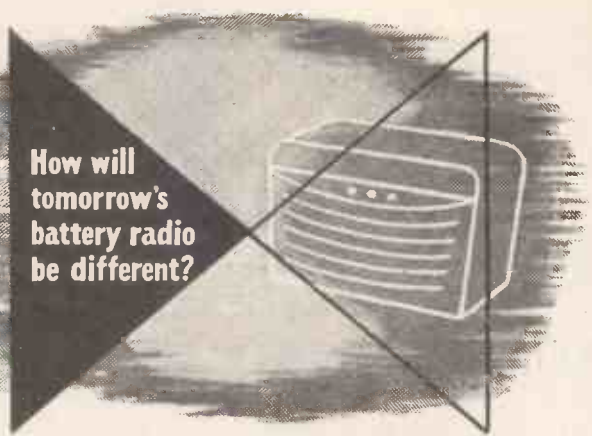How will tomorrow's battery radio be different?



non-spillable, are unharmed by high charge and discharge rates and may be left in discharged condition without damage.

The services of our technical department are freely at your disposal in investigating the many operational advantages of these accumulators.

VENNER

For full technical data please write for leaflet VAO11/WW.
ACCUMULATORS LTD


Distributors for London and Home Counties:—
David & Solf Ltd., 173, Sloane Street, S.W.1. Tel.: SLOane 8532.

KINGSTON BY-PASS, NEW MALDEN, SURREY Telephone: MALden 2449

AMBASSADOR

created
the first
Television
Corner
Console

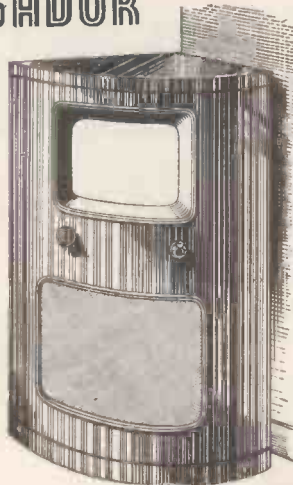Although imitated it is unequalled in performance, style or price. The best costs you less—see your nearest AMBASSADOR dealer.



The T.V.A.
12" Corner Console
in Walnut


YOU'LL NEVER REGRET
BUYING AMBASSADOR TELEVISION

AMBASSADOR RADIO & TELEVISION, BRIGHOUSE, YORKSHIRE

PRATTS RADIO

1070 Harrow Road, London, N.W.10
(Nr. SCRUBBS LANE)

Tel. LADbroke 1734

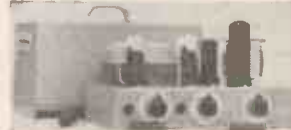

MODEL AC10E £9/18/6

AMPLIFIERS. College general purpose units. MODEL AC10E. 4 valve 10 watts. Neg. feedback, £9/18/6. MODEL AC18E, 6 valve; 18½ watt P/P output. Feedback over 3 stages, £14/14/-. MODEL AC32E. 32 watts P/P output. Feedback over 3 stages. £18/18/-. MODEL U10E, for DC/AC mains, 6 valve 10 watt P/P output. Feedback over 3 stages. £12/12/-. All are complete with cases and chrome handles. They have a separate microphone stage. Separate inputs for mike and gram., allowing individual mixing, etc. Outputs match 3, 8 or 15 ohm speakers. Max. input volts required for full stated output average Mike .005, Gram. .3%. MODEL AC3C, 6 valve P/P 8-10 watt unit for records, radio, etc. Feedback over 3 stages. Output to 3, 8, 15 ohms. £9/18/6. MODEL AC4C, 3 valve record/radio amplifier, 4 watts to .3 ohms, £5/9/6. Ditto U4C for DC/AC mains, £5/9/6. Stamp for list. Full range of accessories available, including: Rothermel Crystal Mikes, 105/-; Goodmans 12in. P.M. speaker, £8/12/6; Colliaro A.C. Record Players, rim drive, magnetic model, £8/9/-. Crystal, £8/15/-. Jack plugs 1/6 each extra.
Nearest Station: Kensal Green.

A MINIATURE MAGNETIC LIGHTWEIGHT EARPHONE




The new Amplivox E.4 Earphone has been primarily developed for use with office dictating machines, industrial equipments and hearing aids where a highly sensitive, lightweight, miniature receiver is needed.

Available in D.C. resistances: 2-2000 ohms; frequency 100-4000 c.p.s.; diameter .835", depth .420"; weight ¼ oz.

AMPLIVOX LTD.
2 Bentinck Street, London, W.1

R & A - Alpha and Omega

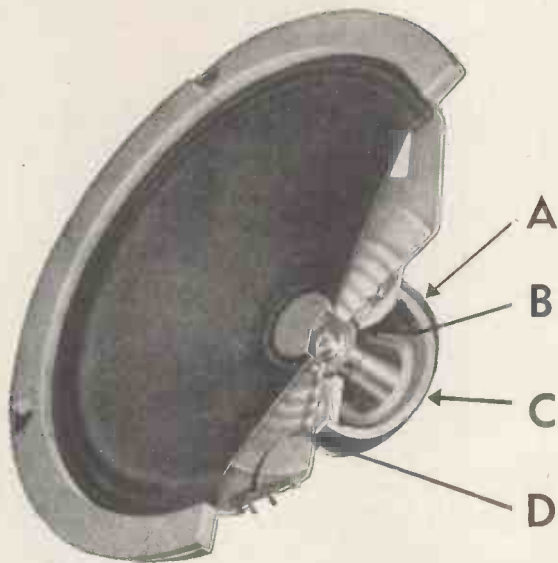


IN RECENT ADVERTISEMENTS we have talked about some of the key features in the design and construction of R. & A. Reproducers, notably—

- Totally-enclosed, high efficiency magnet systems (A)
- Permanent voice-coil alignment due to Co-axial Construction (B)
- Zero external field (C)
- Voice-coil leads moulded into centring member (D)
- Full tropical protection

Taken separately, these are our particular solutions to common problems. Their combined effect on the reliability, performance and value of the finished product is best shown by the continuing and growing demand made upon us by leading set-makers here and in other countries. We will gladly provide every opportunity for you to make your own independent judgment.

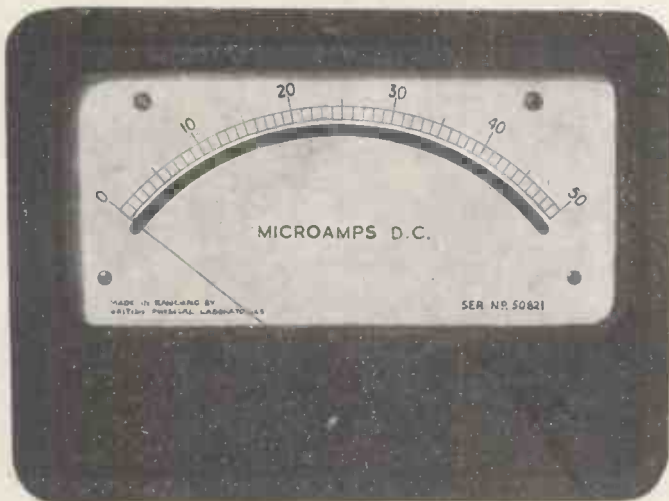REPRODUCERS AND AMPLIFIERS LIMITED
WOLVERHAMPTON · ENGLAND
 Telephone: Wolverhampton 22241 (5 lines). Telegrams: Audio, Wolverhampton



| SIZE | 2½" | 3½" | 5" |
|-------|------|------|------|
| RANGE | 25µA | 10µA | 10µA |
| | to | to | to |
| | 50A | 50A | 50A |

(Prices on application)

S.50 type Microammeters are stocked by Messrs. M. R. Supplies at New Oxford Street, London, W.1.

All sizes available with
MIRROR SCALE
 1st Grade Accuracy

SENSITIVE PANEL MOUNTING METERS

For particulars of these and our full range of measuring instruments write to :—

BRITISH PHYSICAL LABORATORIES

HOUSEBOAT WORKS · RADLETT · HERTS · Telephone : RADlett 5674-5-6

RADIO SUPPLY CO.

15, WELLINGTON ST., LEEDS, 1.

Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/3 charged on orders under £3. Open to callers 9 a.m. to 5.30 p.m. Saturdays until 1 p.m.

R.S.C. MAINS TRANSFORMERS

Fully Guaranteed, Interleaved, and Impregnated. Primaries 200-230-250v. 50 c/s. Screened.

DROP THROUGH TYPES, TOP SHROUDED

| | |
|--|-------|
| 260-0-260 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a. | 12/11 |
| 260-0-260 v. 80 ma., 6.3 v. 3 a., 5 v. 2 a. | 14/11 |
| 350-0-350 v. 80 ma., 6.3 v. 2 a., 5 v. 2 a. | 14/11 |
| 350-0-350 v. 80 ma., 0-4-6.3 v. 2 a., 0-4.5 v. 2 a. | 18/9 |
| 260-0-260 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a. | 19/9 |
| 350-0-350 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a. | 19/9 |
| 250-0-250 v. 100 ma., 6.3 v. 4 a., 5 v. 3 a. | 21/9 |
| 250-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., for R1355 conversion | 23/11 |
| 350-0-350 v. 100 ma., 6.3 v. 4 v. 4 a. C.T. 0-4.5 v. 3 a. | 21/11 |
| 350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a. | 25/9 |
| 350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a. | 27/11 |

CLAMPED UPRIGHT MOUNTING

| | |
|--|------|
| 350-0-350 v. 100 ma., 6.3 v. 3 a., 5 v. 3 a. | 21/6 |
| 350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a. | 27/9 |

FULLY SHROUDED, UPRIGHT

| | |
|--|-------|
| 250-0-250 v. 60 ma., 6.3 v. 2 a., 5 v. 2 a., Midget type 2 1/2-3-in. | 16/9 |
| 350-0-350 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a. | 18/9 |
| 250-0-250 v. 100 ma., 6.3 v. 4 v. 4 a. C.T. 0-4.5 v. 3 a. | 23/9 |
| 250-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., for R1355 conversion | 26/9 |
| 300-0-300 v. 100 ma., 6.3 v. 4 v. 4 a., C.T., 0-4.5 v. 3 a. | 23/9 |
| 350-0-350 v. 100 ma., 6.3 v. 4 v. 4 a. C.T., 0-4.5 v. 3 a. | 23/9 |
| 350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a. | 27/9 |
| 350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a. | 29/11 |
| 350-0-350 v. 250 ma., 6.3 v. 6 a., 4 v. 8 a. 0-2.6 v. 2 a., 4 v. 3 a., for Electronic Eng. Televisor | 63/- |
| 425-0-425 v. 200 ma., 6.3 v. 4 v. 4 a. C.T. 6.3 v. 4 v. 4 a., C.T., 0-4.5 v. 3 a., suitable Williamson Amplifier | 48/9 |
| 325-0-325 v. 20 ma., 6.3 v. 0.5 a., 6.3 v. 1.5 a. for Williamson Preamplifier | 17/6 |

FILAMENT TRANSFORMERS

| | |
|--|------|
| All with 200-250 v. 50 c/s. primaries: 6.3 v. 2 a., 7/6; 0-4-6.3 v. 2 a., 7/9; 12 v. 1 a., 7/11; 6.3 v. 3 a., 10/11; 6.3 v. 6 a., 16/9; 0-2-4.5-6.3 v. 4 a., 16/9; 12 v. 3 a., or 24 v. 1.5 a. | 16/9 |
|--|------|

CHARGER TRANSFORMERS

| | |
|--|------|
| All with 200-230-250 v. 50 c/s. Primaries: 0-9-15 v. 1.5 a., 12/9; 0-9-15 v. 3 a., 15/9; 0-9-15 v. 6 a. 21/9; 0-4-9-15-24 v. 3 a., 21/9; 0-9-15-30 v. 3 a. | 22/9 |
|--|------|

SMOOTHING CHOKES

| | |
|--|-----|
| 200 ma. 5 h. 100 ohms | 7/6 |
| 100 ma. 10 h. 100 ohms | 7/6 |
| 90 ma. 10 h. 100 ohms | 5/9 |
| 80 ma. 10 h. 350 ohms | 5/6 |
| 50 ma. 50 h. 1,500 ohms. (Williamson Amp.) | 8/6 |

AUTO TRANSFORMERS

| | |
|------------------------------|------|
| 100 watts 110-200-230-250 v. | 19/9 |
|------------------------------|------|

ELIMINATOR TRANSFORMERS

| | |
|--|--------------|
| Primaries 200-250 v. 50 c/s. 120 v. 40 ma. 120-0-120 v. 30 ma. 4 v. 1/2 a. | 7/11 12/9 |
|--|--------------|

OUTPUT TRANSFORMERS

| | |
|---|-------|
| Midget Battery, Pentode 66: 1 for 354, etc. | 3/6 |
| 5 small Pentode, 5,000 ohms to 3 ohms | 3/9 |
| Standard Pentode 8,000 ohms to 3 ohms | 4/9 |
| Pentode 8,000 ohms tapped 5,000 ohms to 3 ohms (50 ma.) | 4/11 |
| Multi ratio 40 ma., 30: 1, 45: 1, 60: 1, 90: 1 Class B Push-Pull | 5/3 |
| Push-Pull 8 watts 6V6 to 3 ohms | 9/6 |
| Push-Pull 10-12 watts 6V6 to 3 or 15 ohms | 15/11 |
| Push-Pull 10-12 watt to match 6L6, PX4, 6V6, etc., to 3-5-8 or 15 ohm speaker | 15/11 |
| Push-Pull 15-18 watts to match 6L6, etc., to 3 or 15 ohm speaker | 21/9 |

SPECIAL OFFERS. Mains Trans.

| | |
|---|------|
| 200-230 v. Primaries. 6.3 v. 1.5 a. small ... | 5/6 |
| 300-0-300 v. 70 ma. 6.3 v. 3 a., 4 v. 2 a. | 11/6 |
| Auto 0-200-230-320 v 70 ma. with 6.3 v. 3 a. L.T. | 7/6 |

| | |
|-------------------------------------|-------|
| SPEAKERS P.M. 5in. 2-3 ohms | 12/11 |
| M.E. Bin. 2-3 ohms (Field 600 ohms) | 12/9 |

RECEIVER CHASSIS, 16 s.w.g., aluminium 10-5 1/2-in., 3/6; 11-6-2 1/2-in., 3/11; 12-8-2 1/2-in., 4/11; 16-8-2 1/2-in., 6/9; 20-8-2 1/2-in., 7/11.

AMPLIFIER CHASSIS, 16 s.w.g. aluminium, 12-8-2 1/2-in., 7/11; 16-8-2 1/2-in., 10/11; 20-8-2 1/2-in., 13/6.

MISC. ITEMS. Ex.-Govt. chokes 100 ma., 10 h., 100 ohms. Tropicalised, 4/3. Ex.-Govt. Selenium rectifiers, 600v. 30 ma., 6/9; 120-0-120 v. 60 ma. 4/6; New, 150 v. 60 ma., H.W., 3/9; Vol. Controls, 200 k. long spindle, 1/3 ea., 12/6 doz. 0.1 mfd. 1,000 v. Tubulars, 4/11 doz. Ex-Govt. Receiver Units, type 71, less valves, 1/9; E.H.T. Smoothers. 0.5 mfd., 3,500 v., 1/9; 4 mfd. 600 v. Blocks (ex new equip.), 2/9. Ex-Govt. R1124 Units, less valves, 10/9. New 2,000 mfd. 12 v. Blocks, 4/6.

ELECTROLYTICS, Tubular 8 mfd. 350 v. 1/11, 8 mfd. 450 v. 2/3; Can 16 mfd. 450 v. 2/11; 8-8 mfd. 500 v. 4/6; 8-16 mfd. 450 v. 4/6; 12-12 mfd. 350 v. 3/3; 16-16 mfd. 450 v. 5/3; 32 mfd. 350 v. 4/3; 32 mfd. 450 v. 5/3; 32-32 mfd., 350 v. 6/6; 32-32 mfd. 450 v. 7/6.

FULL RANGE OF STANDARD COMPONENTS AVAILABLE AT KEEN PRICES. ALL GOODS GUARANTEED AND NEW UNLESS OTHERWISE STATED. QUANTITY QUOTATIONS GIVEN FOR STANDARD TYPES OR SPECIALS. S.A.E. PLEASE WITH ALL ENQUIRIES FULL STOCK LIST 4d. SPECIAL LIST FOR TRADE, 4d.

1 KW TELEGRAPH TRANSMITTERS. Two HF 300's output. Operation 3.5 mc to 16 mc.

RCA TRANSMITTERS. Type ET-4336. Complete with matched speech amplifier, crystal multiplier and VFO units. Brand new.

LM-300 TRANSMITTERS (U.S.A.). 140 kc to 400 kc and 650 kc to 1,600 kc. 300 watt output.

No. 12 TRANSMITTERS. With coupling units, remote control etc.

AR.77's, AR.-88's, NC200, NC45, HRO and others.

AUTOMATIC HIGH SPEED TELEGRAPH EQUIPMENT. "BOEHME" (U.S.A.) Up to 400 signs per minute on line and wireless

NAVY MODEL TBY-8 TRANSMITTING-RECEIVING EQUIPMENT. Output 0.75 watts on M.C.W. telegraphy and 0.5 watts on telephony. Frequency range 28-80 mc.

All above items in excellent working condition.

Working demonstration upon request

TX VALVES 805, 807, 814, 861, 866A, DET-16 and many others.

Large stock of Tx condensers, crystals and other components Alignment and repair of communication receivers and all other short-wave equipment undertaken

P.C.A. RADIO

Transmitter Division :—
The Arches, Cambridge Grove,
London, W.6. Tel. RIV 3279

Receiver Division :—
170 Goldhawk Road,
London, W.12.
Tel. SHE 4946

TELEVISION INTERFERENCE Suppressors!

For the alleviation and cure of this interference with Television, from motor cars, lorries, vans, etc.

Fit in a second!

A.F. BULGIN & CO. LTD.
BYPASS ROAD, BARKING,
ESSEX RIPLEYWAY 3474-9



RADIOMENDERS LIMITED

FOR SPECIAL TRANSFORMERS AND REWINDS

We specialize in
AMATEURS' WINDINGS, TRANSFORMERS
ALL TYPES, CHOKES, PICK-UP COILS,
INSTRUMENT COILS, Etc.

Highest Workmanship ★ Good Delivery

RADIOMENDERS LTD.,
Television and Radio Apparatus. Transformer and Coilwinders.
123-5-7 Parchmore Road,
THORNTON HEATH, SURREY.
LIV 2261. Trade enquiries invited. Established 16 years.

WEBB'S *Radio*

EDDYSTONE '740'

Communications Receiver

We are pleased to say supplies are again available of the popular "740," the communications receiver giving high performance at a reasonable price. The comprehensive specification includes:—

- A.C. operation 110 and 220/250 volts, with 6 volt operation from external vibrator unit.
- Eight modern valves, all B8A bases.
- Four bands cover 30.6 mc/s to 1.4 mc/s continuous (9.8 to 214.3 metres) and 205 to 620 metres.
- Beat Frequency Oscillator, Noise limiter, R.F. stages.
- Precision tuning 140/l with auxiliary scale giving equivalent tuning length of 60" for each band.
- Provision for plugging in external "S" meter.

EDDYSTONE '740' COMMUNICATIONS RECEIVER £38.15

Makers' details of this GUARANTEED RECEIVER available on request. Can also be supplied under Webb's Extended Payment Scheme if desired.

HIGH FIDELITY

Despite the prevailing shortage we can still give immediate delivery on most leading makes of amplifiers, pick-ups, loud-speakers and kindred apparatus. What is more we back our supplies with an efficient after-sales service, while our advice is always available gratis.

Some of the world-famous reproducers to be heard in our Demonstration Room include—

The "MORDAUNT" CORNER HORN, the "KLIPSCHORN" and the "VOIGT"

playing with amplifiers by

ROGERS * ACOUSTICAL
SOUND SALES * LEAK



14 SOHO ST., OXFORD ST., LONDON, W.1


Phone: GERrard 2089. Shop Hours: 9 a.m.—5.30 p.m. Sats. 9 a.m.—1 p.m.

ANTIFERRENCE *Specialisation*

Aerials and aerial equipment have always been the exclusive concern of Antiferrence Ltd. From the early days of television Antiferrence research and development have pioneered the way in aerial design and technique. From this specialised endeavour has been built a range of Radio and Television aerials and equipment acknowledged second to none. Below are briefly described two models that have been produced to fulfil very specific requirements. The full Antiferrence range includes aerials to meet every possible need.

TYPICAL TELEVISION AERIALS

The "4-WAY" INDOOR AERIAL

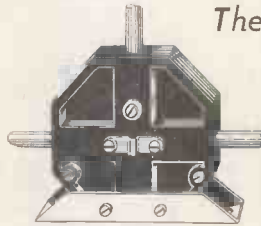


MODEL '4-WAY'/*
LIST PRICE 27/6

Where signal strength permits, the "4-Way" provides the ideal indoor aerial, and can easily be adapted to suit individual locations. Gives full picture definition, installed in a few minutes with either balanced twin feeder or co-axial cable.

In many instances the "4-Way" aerial can be used with two rods only and spare "4-Way" insulators are available as separate items for making surplus rods into complete aerials.

The "2-WAY" OUTDOOR AERIAL

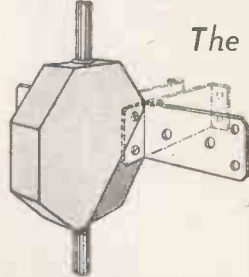

MODEL '2-WAY'/*
LIST PRICE 24/6

A wall-mounting model that provides exceptional efficiency at very low cost. The moulded insulator receives the screwed-in rods, and a two-position bracket gives up to 3in. wall clearance. Connections protected by weatherproof cap.

* Add suffix for channel required:—
/1 for London: /2 Holme Moss: /3 Kirk-o-Shotts:
/4 Midlands: /5 Wenvoe.

And, of course, the "ANTEX"
of the famous "X" array, is another example of Antiferrence leadership. The "Antex" is available in four models.

| | |
|---|------------|
| | LIST PRICE |
| MODEL X2P/* Pole Mounting | 57/- |
| MODEL X2W/* 5ft. Mast mounting (wall fitting) | 75/6 |
| MODEL X2L/* " " (chimney flashing) | 88/6 |
| MODEL X2M/* 10ft. " " " | 123/6 |

ANTIFERRENCE LIMITED
67 BRYANSTON STREET, LONDON W.1

PHILIPS announce
a wide extension to their range of
ELECTRONIC INSTRUMENTS
by the introduction of instruments for the
RADIO and ALLIED INDUSTRIES

The range includes :

Standard Condensers

Oscilloscopes

H.F. Oscillators

A.F. Oscillators

Measuring Bridges

Valve Voltmeters

Electronic Switches

Electronic Relays

Power Supplies

Television Pattern Generators

Variable Transformers

Electronic Test Meters



PHILIPS ELECTRICAL LTD.

CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2. (P1973)

RADIO EXCHANGE CO.

BRAND NEW ACCUMULATORS in transparent, unspillable, plastic cases. 7 A.H. 2 v., 6/6 ; 20 A.H. 2 v. (ex-58 set) with built-in hydrometers, 15/-.

RECEIVER P40. Complete with valves, tuning 85-95 mc/s. these are ideal for Wrotham or "2" metre conversion. Housed in attractive robust grey cases these contain 4 EF54's (RF, mixer, Xcal multipliers), EC32 (Xcal oscillator), 2 EF39's (2.9 mc, s IF's), EB34 (det), 6J5 and 6V6 (audio). In original cartons, complete with circuit, 69/6 Circuit only 1/3.

TRANSMITTER 21. Sending CW, MCW or speech on 4.2-7.5 and 18-31 mc/s these are complete with valves, circuit, control box, key and front panel. Wire (not formers) from PA coils, and relays, have been stripped by the M.O.S. but may easily be replaced with the aid of our circuit and data in excellent condition, 25/-.

RECEIVER 1225. Ideal for 2 metres, these are complete with 5 EF50's, 2 EF39's and EB34 ; the crystal controlled oscillator and RF's may be set to 4 pre-tuned frequencies. ONLY 39/6 (post 1/6).

POWER UNIT S441B with separate individually controlled HT and LT transformers, jewelled indicator lights, attractive appearance and modest size (14 in. x 7 1/2 in. x 7 in.) these deliver 300 v. at 200 mA., fully smoothed, 12 v. at 3A, AC and 5 v. DC. from 200/250 v. 50 cps. In ORIGINAL CARTONS. Only 65/- (carr. 5/-).

VIBRATOR UNIT 21. 6 v. input, approx 160 v. at 40 mA smoothed DC output ; designed for the Tx/Rx 21. ONLY 15/6.

POWER UNIT S532. With 5Z4 rectifier, SU2150 (5 KV), EHT rectifier, choke, relay, condensers, transformers, etc., our conversion will produce a fine little HT or EHT unit for mains input. ONLY 17/6 (carr. 2/3).

CARRIER LEVEL METERS. Brand New in original cartons, scaled, 10/0 ; 2 mA F.S.D., 7/6 (post 6d).

NEW 1355 CONVERSION data for all 5 TV channels, 3/-.

MIDGET AMPLIFIERS with two 12SH7's, one 12SJ7, these measure 5 in. x 3 1/2 in. x 3 in. OUR PRICE 13/6 (carr. 1/6).

TRANS/REC INSTALLATIONS suitable for taxi/business radio equipments ; prices on application.

BARGAINS FOR CALLERS . . . quantities too small to advertise, such as wavemeters, receivers, transmitters, test sets etc., etc

9 CAULDWELL STREET, BEDFORD

Phone : 5568.

"ADCOLA" SOLDERING INSTRUMENTS

Reg. Trade Mark



Rev. Design, 860702

Designed for Wireless Assembly and Maintenance.

SUPPLIED FOR ALL VOLT RANGES FROM 6.7v to 230/50v.

The three Adcola Models cover the requirements of the Television, Telecommunication and Radar Engineers and assure thorough jointing.

3/8 in. dia. Bit. Standard Model— 22/6
 1/2 in. dia. Bit. Standard Model— 25/-
 5/8 in. dia. Detachable Bit — 30/-

Patented in England and Abroad.

Sole Manufacturers :

ADCOLA PRODUCTS LIMITED
 General Offices & Works: CRANMER COURT, CLAPHAM HIGH STREET, LONDON, S.W.4. Tel.: MACaulay 4272.

COILS • COILS • COILS


T.R.F. • SUPERHET • FILTERS • PACKS
 TELEVISION COILS • I.F. TRANSFORMERS

FOR DEPENDABLE COMPONENTS CONTACT

OLYMPIC RADIO COMPONENTS

COIL WINDING SPECIALISTS & MANUFACTURERS
 224, HORNSEY RD., N.7. NORTH 2914

the new
A.D.C.
speaker

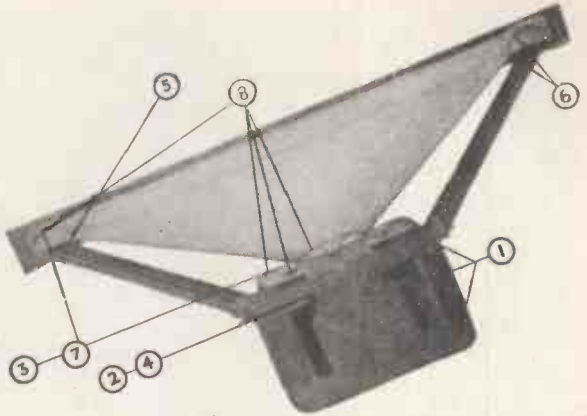

A BRITISH INVENTION

**PERFECT & NATURAL
REPRODUCTION**

Manufactured by:-

AUDIO-ACOUSTIC DIFFUSEURS LTD.
BROOK HOUSE, PARK LANE, LONDON, W.1

Factory: Tarrant Street, Arundel.

The A.D.C. Speaker Design.

1. Magnetic assembly. Metal plates of ample dimensions. High value B. H. Ticonal magnet is employed. 2. Voice coil. Spaced windings and designed to prevent distortion through inhomogeneity of the flux density. 3. The Cone assembly is suspended so as to have movement parallel to the axis of motion. The design also fulfils the requirements of insulating acoustically the front and rear of the assembly. 4. The Voice Coil is of a special design being of high efficiency, both windings operate in an undistorted field. 5. The suspension is such that the terminating periphery of the actual Cone is not a free edge. 6. The Cone and supporting member do not constitute a change of medium at their junctions. 7. The parallel motion (3) does not give rise to distortion of the supporting surround. 8. The suspension system will offer constant friction resistance to motion.

Technical Details.

Resonant Frequency—Nil smooth sinusoidal base wave form. No phase change or voltage generated in voice coil. **Decay Time**—Open voice coil circuit, critical non oscillatory. **Cone Damping**—Resistance at all frequencies. **Cone Movement**—Linear at all frequencies. **Air Loading**—Both sides radiating 20 grams. **Motion Modulation**—Electrical, non-mechanical. **Transient Response**—Transients are free of basic resonance and reverse modulation throughout the frequency scale. **High Frequency**—Low ambient noise level, wide angle 70° of axis at 10,000 cycles. **Reproduction**—The tone is without colouration and hardness, therefore the colour-tone of any musical instrument is not altered by the addition of colour-tone from the Speaker. Write for illustrated Brochure.

FOR HIGH-FREQUENCY INSULATION

specify

'FREQUELEX'

The Inductance shown is supported by our "FREQUELEX" Ceramic Rods and forms part of a 100 k.w. Radio Transmitter.

This is only one of many applications where Rods made to close limits are required.


We specialise in the manufacture of Ceramic Rods and Tubes of various sections in several classes of materials over wide dimensional ranges.

The Principal Materials Are:—

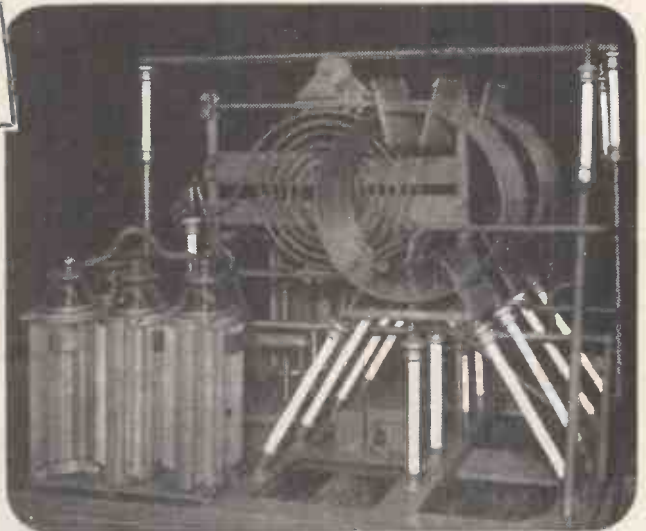1. Porcelain for general insulation.
2. Frequelex for High Frequency Insulation.
3. Permallex and Templex for Capacitors.

The degree of accuracy depends on the size of the Rod or Tube, but the standard degree of accuracy is outlined in the Inter-Service Component Manufacturer's Council—Panel R Specification embodied in our Catalogue of Radio Frequency Ceramics, copy of which will be sent on request.

Large Rods up to 44" long and 1½" square are used as supports for Tuning Coils, etc.



We shall be pleased to have your enquiries for all sizes of Tubes and Rods. Prompt deliveries can be given for most sizes.

Photograph by permission of The Marconi Wireless Telegraph Company Ltd., Chelmsford.



Bullers **LOW LOSS CERAMICS**

BULLERS LIMITED, 6 Laurence Pountney Hill, E.C.4. Phone: MANsion House 9971 (3 lines). Grams: 'Bullers, Cannon, London'

Announcing
 THIS COMPLETE RANGE — NOW OBTAINABLE...

GU4

A beautifully styled three speed gramophone. Complete with ingenious automatic stop and light weight crystal pickup fitted with two permanent sapphire styli.



MU14

A de luxe three speed turntable unit which can be used with the buyer's own choice of crystal or magnetic pickup.



MU10

A high performance two speed turntable unit designed for easy conversion from 78 r.p.m. to 33½ r.p.m.



MU15

A turntable unit for operation at 78 r.p.m. It is fitted with an 8" diameter turntable and is ideal for use where space is a consideration.



The introduction of these units sets a new standard of quality. Advanced design and modern factory methods make the manufacture of such units possible.

BIRMINGHAM SOUND REPRODUCERS LTD.

BSR

Old Hill, Staffs. Tel. Cradley Heath 6212/3, Grams: 'Electronic Old Hill, Cradley Heath.'

Wireless World

RADIO, TELEVISION
AND ELECTRONICS

41st YEAR OF PUBLICATION

Managing Editor: HUGH S. POCKOCK, M.I.E.E.
Editor: H. F. SMITH

DECEMBER 1951

In This Issue

| | |
|---|-----|
| EDITORIAL COMMENT | 479 |
| RADIO FEEDER UNIT. By <i>J. F. O. Vaughan</i> | 480 |
| CONTINENTAL GRAMOPHONE RECORDS | 485 |
| DESIGN FOR AN F.M. RECEIVER—2. By <i>J. G. Spencer</i> | 487 |
| SHORT-WAVE CONDITIONS. By <i>T. W. Bennington</i> | 490 |
| RADIO FOR TAXIS | 491 |
| POTTED CIRCUITS | 493 |
| R.F. CHOKES. By " <i>Cathode Ray</i> " | 494 |
| LETTERS TO THE EDITOR | 499 |
| WORLD OF WIRELESS | 501 |
| VALVE CATHODE LIFE. By <i>C. C. Eaglesfield</i> | 505 |
| OSCILLOSCOPE "HUM". By <i>W. Tusting</i> | 507 |
| ELECTROLYTIC CAPACITORS. By <i>G. W. A. Dummer</i> | 510 |
| RINGING-CHOKE E.H.T. SYSTEMS—2. By <i>W. T. Cocking</i> | 513 |
| WIDE RANGE SQUARE WAVE SHAPER. By <i>J. E. Attew</i> | 517 |
| MANUFACTURERS' PRODUCTS | 519 |
| RANDOM RADIATIONS. By " <i>Diallist</i> " | 520 |
| UNBIASED. By " <i>Free Grid</i> " | 522 |

PUBLISHED MONTHLY: Price 2/- (last Tuesday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. Telephone: Waterloo 3333 (60 lines). Telegrams: "Ethaworld, Sedist, London." Annual Subscription: Home and Overseas, £1 7s. 0d. U.S.A. \$4.50, Canada \$4.00. BRANCH OFFICES: Birmingham: King Edward House, New Street, 2. Coventry: 8-10, Corporation Street. Glasgow: 26B, Renfield Street, C.2. Manchester: 260, Deansgate. 3

VALVES...and their Applications

INDIRECTLY-HEATED VALVES FOR BROADCAST RECEIVERS

The Detector And A.F. Amplifier Stages

In the conventional 4-valve superheterodyne receiver the I.F. amplifier is usually followed by a double diode triode in which one diode serves as detector, the other as A.V.C. rectifier, and the triode as an A.F. voltage amplifier.

The Mullard valves for this application are the EBC41 and the UBC41, the former having a 6.3-volt heater and the latter a 0.1-amp. heater for series operation.

In each case the triode section has an amplification factor of 70 so that, as a resistance-capacitance coupled amplifier, it is capable of a gain of from 40 to 50.

In D.C./A.C. receivers the heater of the UBC41 should be connected at the earth end of the heater chain, with pin No. 1 (one of the heater pins) connected to chassis in order to keep hum to a minimum; a'd (pin No. 5) should then be used as the signal diode, and a'd (pin No. 6) as the A.V.C. rectifier.

The triode section of the EBC41 or UBC41 may be operated either with cathode bias or with grid-current bias via a grid leak of the order of 10 M Ω . The gain and maximum output voltage for a given distortion will be practically the same for either arrangement. With 20M Ω grid leak and no standing bias the input impedance for small signals will be in the order of 2 M Ω .

Negative feedback may be applied to the A.F. amplifier if desired. When doing so, however, care must be taken that the feedback voltage is not applied to the diodes; otherwise distortion will result.

For minimum hum it is desirable to keep the impedance from cathode to earth as low as possible.

DOUBLE DIODE TRIODES

TYPE EBC41 for A.C. Mains and Car Radio Sets.

TYPE UBC41 for D.C./A.C. Mains Sets

Heater

| | EBC41 | UBC41 |
|-------|-------|--------|
| V_h | 6.3 | 14.0 V |
| I_h | 0.23 | 0.1 A |

Characteristics

| | | |
|-------|-----|---------------|
| V_a | 250 | 170 V |
| V_g | —3 | —1.6 V |
| I_a | 1.0 | 1.5 mA |
| μ | 70 | 70 |
| g_m | 1.3 | 1.65 mA/V |
| r_a | 54 | 42 K Ω |

Limiting Values

Triode Section

| | | |
|------------------------|------|----------------|
| $V_{a(b)}$ max. | 550 | 550 V |
| V_a max. | 300 | 250 V |
| P_a max. | 1 | 1 W |
| I_k max. | 5 | 5 mA |
| V_g max. | | |
| ($I_g = +0.3 \mu A$) | —1.3 | —1.3 V |
| R_{g-k} max. | | |
| (cathode bias) | 3.0 | 3.0 M Ω |
| V_{h-k} max. | 100 | 150 V |
| R_{h-k} max. | 20 | 20 K Ω |

Diode Sections

| | | |
|-------------------|-----|--------|
| $V_{ad(pk)}$ max. | 200 | 200 V |
| I_{ad} max. | 0.8 | 0.8 mA |

THE COMPLETE SERIES

| | FREQUENCY CHANGER | R.F. OR I.F. AMPLIFIER | DET., A.F. AMPLIFR., & A.V.C. DIODE | OUTPUT PENTODES | RECTIFIERS |
|--------------|-------------------|------------------------|-------------------------------------|-----------------|------------|
| 6.3V Heater | ECH42 | EF41 | EBC41 | EL41; EL42 | EZ40; EZ41 |
| 0.1 A Heater | UCH42 | UF41 | UB41 | UL41 | UY41 |


Reprints of this article together with additional data may be obtained free of charge from the address below.



MULLARD LTD., Technical Publications Department, Century House, Shaftesbury Avenue, W.C.2.

ready now!

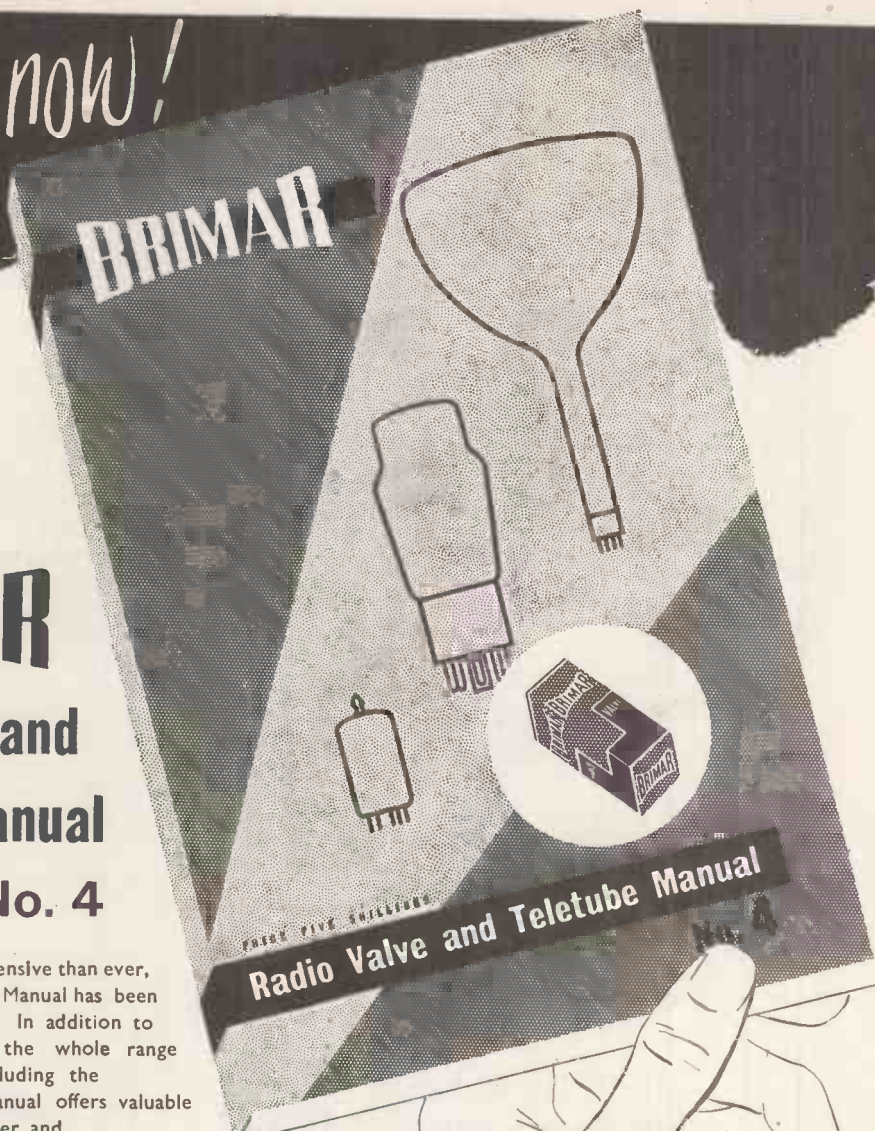The
BRIMAR
radio valve and
teletube manual
No. 4



Bigger . . . more comprehensive than ever, this indispensable 224-page Manual has been brought right up to date. In addition to comprehensive data on the whole range of current valve types, including the Trustworthy series, the Manual offers valuable material for Service Engineer and competent amateur.

C O N T E N T S

- | | |
|--|---------------------------|
| Valve Ratings | Substitution List |
| Classified List of Current Equipment Types | Formulae |
| Valve Types (inc. 'Trustworthy' Range) | Output Transformer Ratios |
| Cathode Ray Tubes | ABAC |
| Metal Rectifiers | Conversion Table |
| Brimistors | Colour Codes |
| Brimarizing | Circuits |
| | Equivalents |
| | Price List |

Standard Telephones and Cables Limited

RADIO RECEIVER VALVE DIVISION

FOOTSCRAY, SIDCUP, KENT FOOTscray 3333


From
your usual
Wholesaler

PRICE
5/-

NOW is the time to BRIMARIZE!



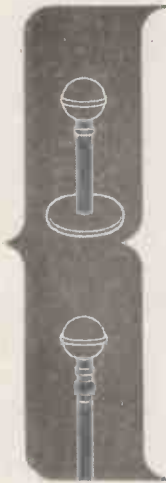high fidelity MICROPHONES
FOR PUBLIC ADDRESS : RECORDING : AMATEUR RADIO



TYPE MIC 22

This model incorporates the famous Acos "Filtercel" insert giving extreme sensitivity and high fidelity. Response is substantially flat from 40-6,000 cps. The microphone is vibration and shock proof and is not affected by low frequency wind noises. Two alternative mountings are available for the MIC 22 head :

MIC 22-2 is supplied as a complete unit incorporating an attractive desk stand with cable side entry.

MIC 22-1 is for fitting to any British or American type standard floor stand and can also be used as a hand microphone.

PRICE £6 · 6. (Either Model)

TYPE MIC 16

Incorporates the Acos Floating Crystal Sound Cell giving a response substantially flat from 30-10,000 cps. Performance is unaffected by vibration or shock and low frequency wind noises. As in the case of the MIC 22, two alternative mountings for the MIC 16 head are available :

MIC 16-2 is a complete desk stand unit with side cable entry.

MIC 16-1 is ready for fixing to either British or American type floor stands by means of a knurled ring.

PRICE £12 · 12. (Either Model)



COSMOCORD LIMITED

ENFIELD, MIDDX.

P.S. As you probably know, we make good pick-ups too, in large numbers. But even larger numbers of people want them. Although, therefore, we expect to be producing still more and still better pick-ups soon, just now we don't advertise pick-ups at all.

THE "BELLING-LEE" PAGE

Providing technical information, service and advice in relation to our products and the suppression of electrical interference



Holme Moss Received at Radio Show, London.

T.V. signals from Holme Moss were received on the roof at the Radio Show, Earls Court, London. The test was carried out by two exhibitors in the Show—a receivers manufacturer (E. K. Cole) and an aerials manufacturer (Belling & Lee).

"The long-distance claims for Holme Moss were confirmed by this test," said Mr. Walter York, of E. K. Cole, "but as always with 'freak' reception, local interference can considerably mar the entertainment value."

Just because a "Multirod" brought in Holme Moss at Earls Court, it does not mean that henceforth we advertise reception at 200 miles. Nevertheless we are pleased that our aerial was chosen for the test.

The dipole has its limits.

There will always be places within a few miles of a television transmitter where an "H" type aerial will be necessary. In such cases the "H" type is being used to give a better signal-to-noise ratio, i.e., to reduce the effect of interference and/or "ghosts." In a location free from these distractions, but many times the distance from the transmitter, a simple dipole, even an indoor "Doorod" might be expected to give satisfaction. The very great area served by Holme Moss results in the simple dipole giving an adequate signal over far greater distances than with Sutton Coldfield or Alexandra Palace, but the vast area covered contains many great hills and deep valleys, resulting in reflections, double images,

"ghosts" or what-not in greater confusion than ever before. Further, the densely industrialised towns and their suburbs, with their mills, chimneys, cooling towers gas-holders, etc., all tend to confuse the picture on the screen. The simple dipole just cannot cope with these conditions. Where they occur, the problem must be appreciated and faced, and more elaborate aerial arrangements must be provided. So—if your dealer suggests that with his experience such and such an aerial is necessary, remember, he has had the opportunity of "looking in" at more houses than most other people. He generally knows the peculiarities of his own district. It is however, as well to remember that reception conditions can vary tremendously between two points quite close to each other. Don't insist on a dipole if an "H" is necessary, but...

... Don't be an "H" type Snob.

The astoundingly successful coverage of Holme Moss resulted in several comments at the Radio Show, hinting that fewer "Multirods" and "H" aerials would be required. This is not so. There will always be a "fringe" but it will be further away. The further away it is, the greater the circumference and the longer the "fringe" and the greater the number of "Multirods" and "H" type aerials that will be required. In fringe areas a simple aerial or an indoor aerial will not do, don't waste precious materials. Don't use an "H" when a dipole will suffice. Don't be an "H" Type Snob.

Is it the Car or is it the Suppressor?

From time to time we hear that after the fitting of a suppressor, the performance of the car engine deteriorates. We agree that this will happen in some cases, but only when the engine already has faults which affect its efficiency and which are "brought to the surface" as it were, by the fitting of a suppressor.

A good illustration of this point is given in some recent exchanges of correspondence from which we quote the following extracts:

"I am interested in your statement that an ignition suppressor does not affect engine performance, for this is not my experience, and I am carrying on some experiments in order to use one on my own car. I find, so far, that both the

slow running and smooth acceleration are adversely affected, but it may be that the setting of the various ignition components are more critical when a suppressor is fitted."

In reply we said:

"We have known of cases where fitting an ignition suppressor has affected the performance of an engine, but in all cases we have investigated, we have found that the initial cause is in the engine itself. For example, if there is any tendency for the plugs to 'oil up'; then when a suppressor is fitted, which will reduce the temperature of the spark, the oil is not burnt off as it would be with no suppressor fitted. On an engine which is in good condition, the reduction in spark intensity has no effect on the performance and does in fact, tend to prolong the life of the sparking plugs.

We do not, of course, know all the facts in your particular case, but if further information becomes



"Belling-Lee" Distributor Suppressor L.630.

available in the light of experience, we shall be pleased to receive this."

After some time we received the following:

"I have now obtained satisfactory results with a T.V. ignition suppressor on my car, and I thought that you might be interested in the cause of unsatisfactory running when I wrote to you.

(1) The ignition coil was found to be faulty, giving a weak spark. It was apparently just adequate under normal conditions but failed to pass the normal coil test at my garage.

The manufacturers credited me in full and it has been replaced with a sports coil, which seems to be very satisfactory.

(2) The carburettor tuning was over-rich in the idling position. The manufacturers have adjusted it with good results.


I am now unable to tell from the car performance whether the suppressor is 'in or out' and I shall continue to use it, no doubt with considerable reduction in TV interference."

BELLING & LEE LTD
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDD., ENGLAND



rectifiers

for the radio industry

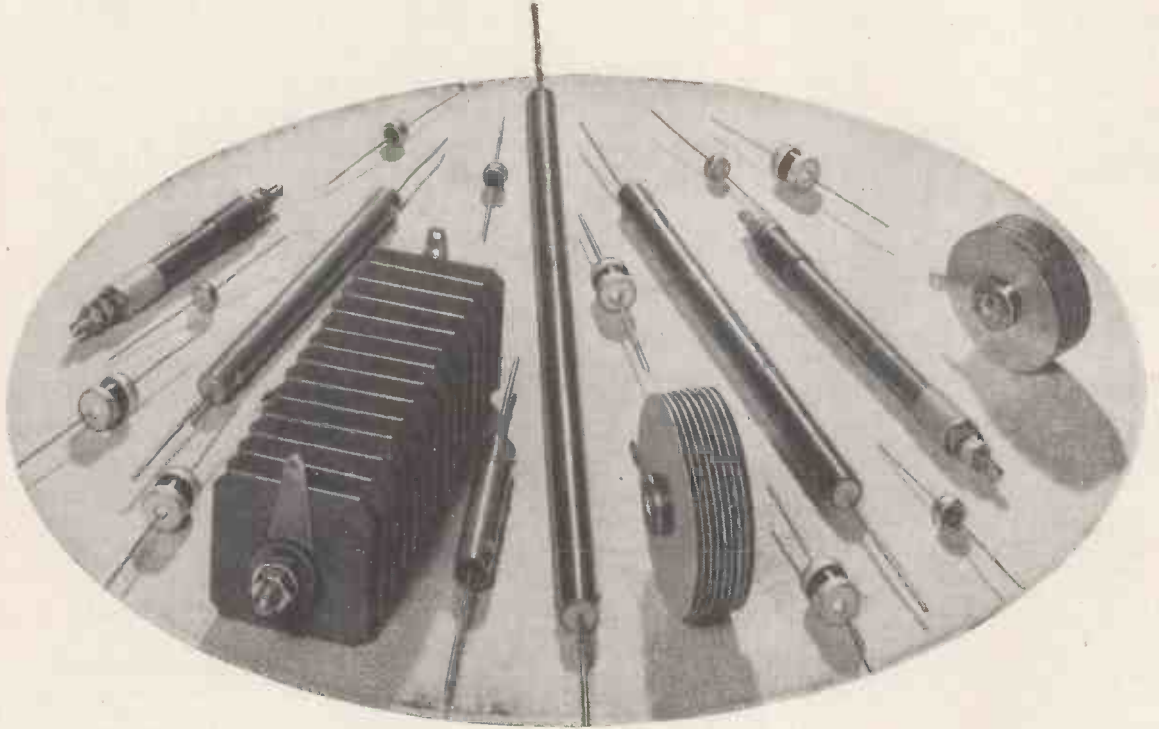

WHEREVER a radio or television diagram shows a rectifier operating at 0.5 Volts or higher, at a frequency below 5 mc/s there is almost certain to be a SenTerCel Selenium Rectifier which will do a better job because it:

Please write for leaflets **F/SRL9, 9a, 10 & 11**

- Saves space and weight
- Reduces wiring
- Withstands an unlimited instantaneous overload
- Reduces heat dissipation
- Needs no "warming-up" period
- Saves the cost of a valveholder
- Is practically indestructible in service
- Imposes no limit on the size of the reservoir capacitor
- Is low in cost

Standard Telephones and Cables Limited

Registered Office: Connaught House, Aldwych, London, W.C.2

RECTIFIER DIVISION WARWICK ROAD, BOREHAM WOOD, HERTS.

Elstree 2401 Telegrams: Sentercel Borehamwood

VORTEXION

High Quality Reproduction



"FIFTY and THIRTY WATT" CINEMA AMPLIFIERS as illustrated for single or double P.E.C. input with separate adjustable bias. Full range of tone controls to suit all needs with built-in Exciter Supply if required.

TYPE C.P. 20A AMPLIFIER For AC Mains and 12 volt working giving 15 watts output, has switch change-over from AC to DC and "Stand-by" positions. Consumes only $5\frac{1}{2}$ amperes from 12 volt battery. Fitted with mu-metal shielded microphone transformer for 15 ohm microphone, provision for crystal or moving iron pick-up with tone control for bass and top. Outputs for 7.5 and 15 ohms. Complete in steel case with valves.



FOUR-WAY ELECTRONIC MIXER This unit has 4 built-in balanced and screened microphone transformers, normally of 7.5-30 ohms impedance. It has 5 valves and selenium rectifier supplied by its own built-in screened power pack consumption 20 watts. Suitable for recording and dubbing, or large P.A. Installations since it will drive up to six of our 50 watts amplifiers whose base dimensions it matches. The standard model has an output impedance of 20,000 ohms or less and any impedance can be supplied to order.



OTHER MODELS IN OUR RANGE OF AMPLIFIERS ARE

"SUPER-FIFTY WATT"


"THIRTY WATT"

"10-15 WATT RECORD REPRODUCER"

These are fitted in well ventilated steel cases with recessed controls, as illustrated.

Full details upon request.

Export enquiries invited.

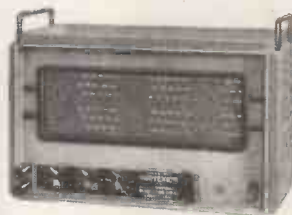

VORTEXION LTD.,

257-261 THE BROADWAY, WIMBLEDON, LONDON, S.W.19

Telephones: Lib 2814 and 6242-3 Telegrams: "Vortexion, Wimble, London."

Can this Instrument solve a problem for YOU?



Here, in the Physics Laboratory of the British Iron and Steel Research Association, is a COSSOR Double Beam Oscillograph in use. Many other industries, ranging from nylon spinning to the manufacture of jet engines, now use this versatile instrument. Typical everyday applications are the tracing of noise, strain and vibration; and the answer to long-standing industrial problems is often provided. Our technical advisory staff will quickly let you know whether the Oscillograph can help with *your* problems.

Here are some details: The Double Beam Tube presents two simultaneous independent traces over the full diameter of a 90 mm. screen, and provision is made for the measurement of both input voltage and time upon the calibrated dials. Permanent photographic records may be made using the Cossor Model 1428 Camera.

COSSOR

Double Beam OSCILLOGRAPHS

Please address enquiries to:—

A. C. COSSOR LTD., INSTRUMENT DIVISION · (Dept. No. 1) Highbury Grove · London, N.5



No 10. Multi-Range Testing Instruments

Best known of all instruments for the testing and servicing of radio and television equipment is undoubtedly the Weston Model E.772 Analyser, a first-class portable instrument with a sensitivity of 20,000 ohms per volt on all D.C. ranges and 1,000 ohms per volt on all A.C. ranges. The additional features of wide range coverage, robust construction and simplicity in operation contribute toward making the E.772 ideal also for laboratory and research work. Full details of this instrument and also of the Model S.75 — a Test Set covering 53 ranges — will gladly be supplied on request.

THE WESTON E772

Super Sensitive Analyzer

SANGAMO WESTON LIMITED

Enfield, Middlesex

Tel.: Enfield 3434 (6 lines) and 1242 (4 lines)

Grams: Sanwest, Enfield

Branches: Glasgow, Manchester, Newcastle-on-Tyne, Leeds, Liverpool, Wolverhampton, Nottingham, Bristol, Southampton and Brighton.


— towards perfection — from every point of view

The **LOWTHER P.M.4 UNIT**
(for horn loading)
The most outstanding and efficient of its kind

NATIONAL PHYSICAL LABORATORY REPORT

ON. TESTS OF LOUDSPEAKER DRIVE UNIT
SERIAL No. 401/B21

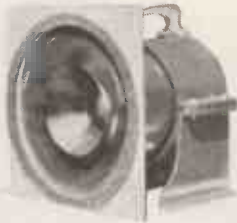Tested for :—
The Lowther Manufacturing Co.
Reference :
Order No. 4935, dated 20.9.51



The unit was tested for average flux density over the gap area and for maximum flux density. The results obtained were :—

Average flux density = 23 800 gauss
Maximum flux density = 24 100 gauss

These values are based on an assumed mean diameter of air-gap of 3.9cm.

Date 5th October, 1951 Reference E.470.58


Further details gladly sent upon request :—

THE LOWTHER MANUFACTURING CO.
(The Laboratory Production unit)
LOWTHER HOUSE, ST. MARK'S ROAD,
BROMLEY, KENT. Phone : RAV 5225



The Greatest Advance towards Perfect Reproduction
The NEW "TONE COLOUR" UNIT Plus the

AMAZING

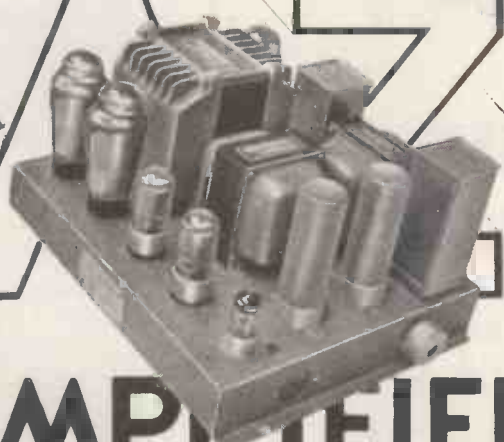

Owners of "Sound Sales" Equipment can always obtain a circuit diagram if they care to apply, quoting serial number. Full connecting instructions are despatched with each unit.

TYPE A-Z
£32.10.0
Complete

AMPLIFIER

SOUND SALES LIMITED



DEMONSTRATIONS at our London Showroom:

LLOYDS BANK, CHAMBERS, 125 OXFORD STREET, W.1 (ENTRANCE IN WARDOUR ST.) Telephone: GERrard 878;
(Works: West Street, Farnham, Surrey. Telephone: Farnham 6461)



ON 12TH DECEMBER 1901 Marconi did what many distinguished scientists said was impossible. He transmitted a wireless signal across 2,000 miles of ocean, from Poldhu in Cornwall to St. John's in Newfoundland. In a prophetic report *The Times* called this an event "the importance of which it is impossible to over-value".

MARCONI serves mankind

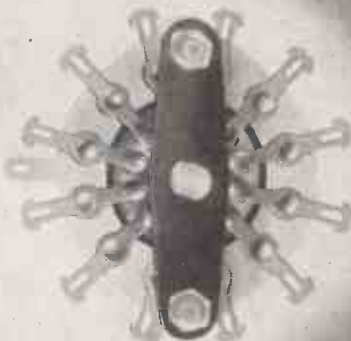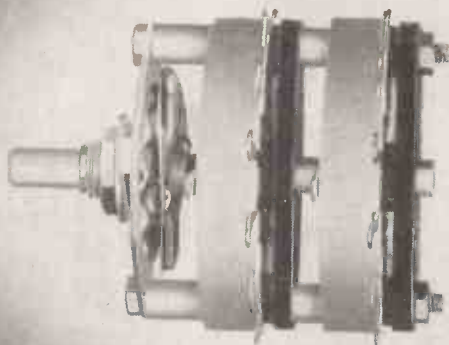

CERAMIC SWITCHES

For applications where only the best is good enough. Stators and rotors of "Frequentite" ceramic. All contact members of silver alloy.

Wright and Weaire Limited

138, SLOANE ST. · LONDON · S.W.1 TEL SLOANE 221415 FACTORY: SOUTH SHIELDS, CO. DURHAM

SUCCESS?

In Radio, Television, and Electronics, there are many more top jobs than engineers qualified to fill them. Because we are part of the great E.M.I. Group we have first-hand knowledge of the needs of employers, thus our Home Study courses are authoritative and based upon modern industrial needs. Alternatively, our courses will prove equally valuable to you in furthering your hobby.

START
HERE

POST THIS COUPON NOW

E.M.I. INSTITUTES, Postal Division, Dept. 16,
43, GROVE PARK ROAD, CHISWICK, LONDON, W.4.
Please send, without obligation, your FREE BROCHURE.
I have marked the subjects which interest me.

Mechanical Eng. Electrical Eng. Draughtsmanship.
 Radio. Television. Production Eng. Automobile
Eng. Aeronautical Eng. General Cert. of Education
 (Matric). Civil Service.

Also Courses for A.M.I.Mech.E., A.M.I.C.E., A.M.Brit.I.R.E.,
A.F.R.Ae.S., CITY and GUILDS EXAMS, in
Mech. Eng., Elect. Eng., Telecommunications, etc.

Other Subjects

NAME

ADDRESS



E.M.I. INSTITUTES — The College backed by an Industry

L.35a



*The Finest Needle
for your Radiogram*

**THE GOLDRING
ACOUSTIC-
FILTERED
TYPE S6**


- Eliminates Needle Changing
- Gives better reproduction
- Filters out surface noise
- Increases life of records

Goldring "Acoustic-filtered
Needles" suit any Standard
Pick-ups.

*Look for the
Display Card
at your Dealers*



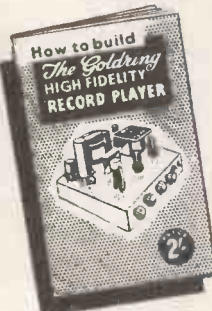Goldring
Needles cost
10/6 inclu-
ding P Tax



The Radio Press acclaim this instruction
book to build a Record Player of the
highest quality. Price 2/-, post free.

**ERWIN SCHARF
GOLDRING PRODUCTS**
49-51a De Beauvoir Road,
London, N.1 Tel.: Clissold 3434/6

Is your amplifier good enough for use

by the B.B.C. and many Commonwealth and foreign broadcasting Corporations in Monitor systems and as a driver amplifier in the speech modulator chain of broadcast transmitters?

by famous record manufacturers for disc recording?

Professional audio engineers have chosen the TL/12 amplifier for the above applications to help bring to you the music on which you rely for your pleasure.


This is a unique distinction for an amplifier available to the general public.

Used with the RC/PA/U pre-amplifier and the best available complementary equipment the TL/12 power amplifier gives to the music-lover a quality of reproduction unsurpassed by any equipment at any price.

These amplifiers are built to a tropical specification and they are distributed throughout the world. During 1951 to date orders totalling over 2,000 have been received from the U.S.A. for RC/PA/U and TL/12 amplifiers for high quality radio/gramophone reproducers for the home.



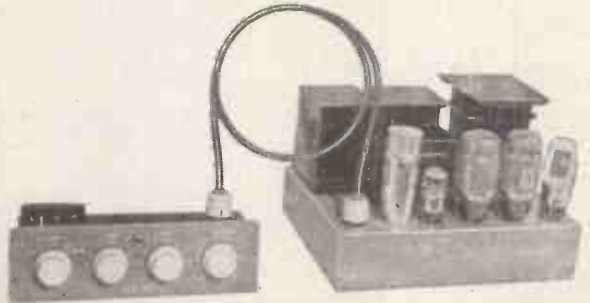This illustration shows the RC/PA/U pre-amplifier mounted in a console cabinet designed for armchair operation. The TL/12 amplifier is mounted in the base of the cabinet. The Leak Dynamic pick-up and Leak radio unit are also incorporated. This console was presented to Harold Rawlinson, Esq., conductor of the Insurance Orchestra Society, on the occasion of the Society's Silver Jubilee.



| | |
|------------------------------|--|
| RC/PA/U | "POINT ONE" TL/12 |
| REMOTE CONTROL PRE-AMPLIFIER | TRIPLE LOOP FEEDBACK 12 WATT AMPLIFIER |
| PRICE 9 GUINEAS | PRICE 27 GUINEAS |

Craftsmanship is apparent on inspection. Performance is certified by the N.P.L.

★ A 28-page illustrated booklet describing these amplifiers and containing much information of interest to music lovers seeking the highest standard of reproduction is available free on request. ★

H. J. LEAK & CO. LTD. (Established 1934)

BRUNEL ROAD, WESTWAY FACTORY ESTATE, ACTON, W.3

Phone: SNEpherds Bush 1173

Telegrams: Sinusoidal Ealux. London

Foreign: Sinusoidal, London

ELPREQ PAGES




EXTENSION SPEAKER IN METAL CABINET

This has a 6in. P.M. Goodman's Speaker, heavy magnet type, complete with an output transformer. It is fitted in grey steel case with perforated front and back, ideal for P.A. work in canteens, clubs, etc. 27/6 each.

TWO-VOLT ACCUMULATORS

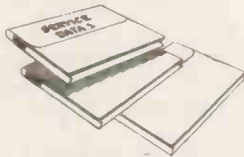Made for the Forces by one of the most famous firms in the world. 15 amp.-hour size approx. 6in. x 1 1/2in. square in ebonite case, pre-charged, only need filling with acid, 5/9 each, plus 1/3 post and insurance. Six or more post free.



SERVICE DATA

100 service sheets, covering British receivers which have been sold in big quantities, and which every service engineer is ultimately bound to meet. The following makers are included: Aerodyne, Alba, Bush, Cossor, Ekco, Ever-Ready, Ferguson, Ferranti, G.E.C., H.M.V., Kolster Brandes, Lissen McMichael, Marconi, Mollard, Murphy, Philco, Philips, Pye, Ultra. Undoubtedly a mine of information invaluable to all who earn their living from radio servicing. Price £1 for the complete folder.


Our folder No. 2 consists of 100 data sheets covering most of the popular American T.R.F. and superhet receivers "all dry" etc., which have been imported into this Country. Names include Sparton, Emmerson, Admiral, Crossley, R.C.A. Victor, etc. Each sheet gives circuit diagrams and component values, alignment procedure, etc., etc. Price for the folder of 100 sheets if £1. Post free.

MISCELLANEOUS BOOKLETS

These give circuit diagrams and details of Ex-Government receivers and equipment. In practically all cases the information has been extracted from official publications. Separate booklets for each piece of equipment. Booklets available covering the following:—R1155, R208, R109, TR1196, TR18, BC348, BC312, R1116, R107, R103, BC221, BC342, Pre-Amp. from RF27, Pre-Amp. from Unit 208A, T.V. Receiver from 3170, etc. T.V. receiver from 194 strip. Dual band T.V. receiver. Price of any of these booklets is 1/6 each—all post free.

GIVE A RADIO YOU HAVE MADE

You will find that the building of our all mains radio receivers is simplicity itself, and the more you make the less time each takes, everything down to the last nut and bolt is supplied and everything fits together in a professional manner. When finished the receiver looks and plays as well as those being offered in radio shops at anything between £10 and £14. So why not give one as a present to someone dear to you this Christmas.

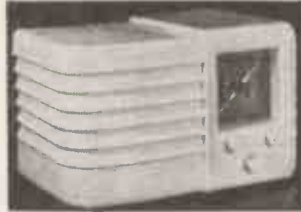


The one illustrated above we call "The Occasional" in a choice of colours, ivory, walnut or green, and the T.R.F. costs just less than £6 to make while the superhet costs approximately £8.

The other radio illustrated we call "The White Lady," this is an extra fine cabinet of pure white. The complete T.R.F. receiver costs about £6/5/- to build, and the superhet receiver cost about £8/5/0 to build.

EXCELLENT XMAS PRESENT

Novelty radio in coloured plastic cabinet only 6in. high, ideal for a nursery or bedroom, complete with built-in moving coil speaker, 2-gang tuning condenser, volume control and ON/OFF switch, all wired up ready to operate as soon as valves are fitted. Works off dry batteries. Valves required are three of type IT4 and one of 3S4. Because of a frustrated export order, we are able to offer these sets brand new and perfect, complete except for valves, at the remarkable price of 49/6 each, postage and insurance 2/6 extra. Don't delay—send your order to-day.

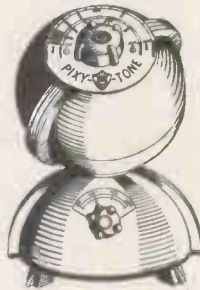

EXCELLENT CHRISTMAS PRESENT FOR MOTHER OR MARRIED SISTER

The "Lectross" is a convector room heater which can be a clothes drier on washing days. It will make life easier in any home, but is an extra boon in flats and where washing is done in the evening. It is also ideal in hairdressing salons as it keeps the towels dry and heats the shop.


We have sold a lot of these, and all purchasers have been delighted. In fact they find it difficult to believe we can supply at such low a price. We could not, but for the fact that the "Lectross" manufacturers were forced into bankruptcy by a cancelled export order. We are able to offer them to you at less than half the original price, and only quarter of what the price would be if they were made to-day. We also bought all the spare parts, so you need have no fears about repairs, in fact we guarantee always to be able to supply spares.

The size of the "Lectross" is 3ft. wide, 3ft. high x 5in. deep. It has four chrome plated rails and works off A.C. or D.C. mains consuming 750 watts, i.e., just less than one Unit. Price £5/19/6, plus 7/6 carriage—please state your mains voltage.



ELECTRONIC TIMER

With this instrument processes which operate over a specified time can be controlled automatically, e.g., in photography use it to control exposures, etc. The instrument can be set to any length of time from a fraction of a second up to three minutes, and it can be made to switch the appliance on or off. Circuit diagram and instructions. 2/3. Complete kit of parts including valves, mains transformer, power pack, sensitive relay, potentiometer and metal case, 69/6.

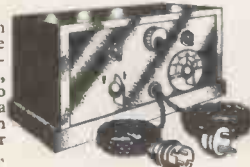

BRASS CASED PLUGS




Seven way brass cased plug ideal for portable apparatus. Price 2/3 each half. Bin D33BR and D33BL.



EX-ROYAL NAVY SOUND POWERED TELEPHONE

These require no batteries, and will go for long periods without attention. Complete with generator and sounder which gives a high pitched note, easily heard above any other noise. Also fitted with an indicator lamp which in quiet situations can be used instead of the sounder, or where several 'phones are used together will indicate which one is being called. Size 7 1/2in. x 9in. x 7 1/2in., wall mounting, designed for ships' use, but equally suitable for home, office, warehouse, factory, garage, etc. Price 37/6 each, plus 3/6 carriage.

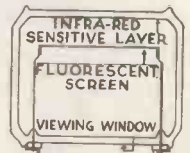

"SNIPERSCOPE"

Famous wartime "cats eye" used in conjunction with a lens system and h.t. for seeing in the dark. This is an infra-red image converter cell with a silver caesium screen which lights up (like a cathode ray tube) when the electrons released by the infra-red strike it. It follows that as light from an ordinary lamp is rich in infra-red these cells will work: burglar alarms, counting circuits, smoke detectors and the hundred and one other devices as will the simpler type of photo cell. Here then is a golden opportunity for some interesting experiments price 9/6 each, or six for 52/6. Data will be supplied with cells if requested.





SHEET PAXOLIN

Invaluable for when you are experimenting. Size 6in. x 6in., 1/-. Size 12in. x 8in., 2/-. Size 12in. x 12in., 3/6. Size 24in. x 12in., 6/-.

RELAYS

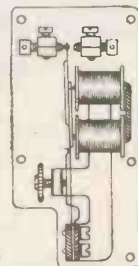Extra light weight extra sensitive for high speed or radio control work, weight only 1 1/2 oz., closes on 2 mA., solid, platinum change-over contacts, adjustable pressure. Price 13/6.



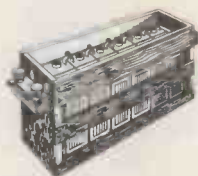


12-CELL ACCUMULATOR

This accumulator can be coupled up to give 24 v. with all cells connected in series or 12, 6 or 2 volts by series parallel arrangements. They were originally made for the Admiralty by a leading manufacturer, have never been filled, and are in excellent condition. Each is contained in a wooden crate as illustrated. Price 27/6 each. Postage and insurance 5/-.




TUNING UNITS

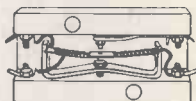American made units, available are TU5B, TU6B, TU9B, TU10B, TU13A, TU17A, TU25A, TU47, TU48, TU49, TU51, TU52, TU54, TU60. All 19/6 each, plus 3/6 carriage.



REPLACING THE U.U.8

You can overcome the shortage of high current indirectly heated rectifiers by using a Thermal Delay Switch. You simply connect this across the heaters of a directly heated rectifier such as FW 4/500 and the H.T. will not be switched on until the other valves have had ample time to warm up. The delay switch is as illustrated, with the addition of a protective cover, Price 3/9 each, the heater voltage is 4, but of course this can be used on higher voltages with a limiting resistor.

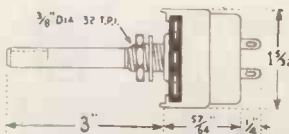

VOLUME CONTROLS

We carry a full range of standard-size volume controls from 2K, to 2 meg. Prices are: less switch, 3/-: Single pole switch, 4/-: double pole switch, 5/-: We can also supply midget-type controls, less switch, 4/-: single pole switch, 5/9: double pole switch, 6/6. Each of these midget controls has a serial number and carries a 12-month guarantee by the makers; they are made on the new moulded track principle and really do perform well.

CONTINUOUSLY VARIABLE MAINS TRANSFORMER
As described in the "Wireless World," August 1951 issue, this has a primary tapped at 81 v. and four secondaries of 1 v., 3 v., 9 v. and 27 v. respectively.
By suitable selection of windings, voltage in steps of 1 v. up to 40 v. can be obtained with isolation from the mains at 100 watt rating, e.g., 20 amps at 5 v. and 2 1/2 amps at 40 v. By adding the primary the voltage can be varied in steps of 1 v. up to 280 v.
This is undoubtedly an essential piece of equipment in all experimental laboratories. Price £3/10/0 each.
NOTE.—The switch in the text is not fitted.

SPECIAL PERSONAL SET OFFER



Resulting from the changeover of a famous manufacturer to important work we are able to offer practically all the parts for the really neat personal radio illustrated.

The most important thing, of course, is the cabinet, and for this we can offer a complete kit of parts, which includes cream plastic lid, base and escutcheon, cracked metal body and all accessories such as knobs, hinges, lid arm, clips, etc. Price 22/6, but remember this brings the complete cabinet size 7in. x 4in. x 3 1/2in. Other items available are:—Metal Chassis, five-part assembly comprises the main chassis and sections for holding the batteries and the loudspeaker. Price 4/6: Frame Aerial, 3/6: Frame


Aerial Cover, 1/6: Oscillator Coil, 3/6: L.F. Transformers "Wearite" midget, per pair, 17/6: Volume Control, 1 meg midget, 3/6: Speaker, midget "Plessey" 3in., 14/6: Output Transformer to match, 5/-: ON/OFF Switch, lid operated, 1/6: Resistors, miscellaneous, total 8, 4/-: Condensers, miscellaneous, total 9, 4/6: B7G Amphenol Valve Holders, each, 8d.: Battery Stud Conectors, per pair, 9d.: Tuning Condenser, 8/6: Assembly Instructions, including wiring diagram and alignment data, 2/6.

NOTE.—All these parts are offered separately. Valves required are 1R5, 1T4, 1S5, 3S4, or 3V4, all available.

10,000 B.V.A. VALVES AT PRE-BUDGET PRICES


MULTI-SPEED MOTORS

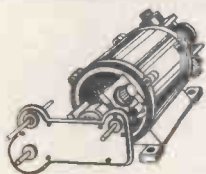You can adjust this motor to almost any speed you want, it will work directly off A.C. mains, or if you require greater power or greater speed work it through a metal rectifier. This motor is fitted with a gear box enabling speeds down as low as 1 r.p.m. to be obtained. Price 14/6, postage and packing 1/6 extra.



THIS MONTH'S SNIP.

Really beautifully made transformers, fully shrouded upright mounting, with plated and polished shrouds. Type 1—Primary 10-0-200, 220, 240, H.T. secondary 350-0-350 v. at 250 mA. L.T. 4 v. at 6 to 8 amps, and 4 v. at 3 to 4 amps. Dimensions are 4 1/2in. x 4in. x 4 1/2in. Price 27/6, plus 2/6 postage and packing. Type 2. Primary as type 1, H.T. Secondary 300-0-300 v. L.T., 7.5-0-7.5 v. at 3 amps, and 4 v. at 3 to 4 amps, Dimensions 4 1/2in. high x 4in. x 3 1/2in. Price 17/6, plus 2/- postage and packing.

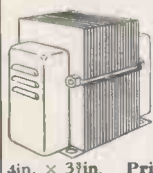

6-VOLT AMERICAN HEAVY-DUTY BATTERIES

Made by one or other of the most famous American battery companies. For reliability and long service between charges these are in a class of their own. Capacity rating is 140 amp-hour. We have a limited quantity of these batteries available, unused—in fact they have never been filled with acid, and the price is £5/10/-, carriage extra at cost depending upon your locality



Orders by post are dealt with by our Ruislip depot. To avoid delay address to—E.P.E. Ltd., Dept. 2 Windmill Hill. Ruislip, Middx.



2-GANG .00035 TUNING CONDENSER


Complete with perspex dust cover and built-in trimmers. Super job for tuning personal receivers, 8/6 each.

A MILLIBAR BAROMETER

If you are interested in meteorology, then you will be interested to know that an article appeared in one of the leading meteorological journals showing how the Ex-R.A.F. Sensitive Altimeter can become a first-class highly sensitive yet robust aneroid barometer. We offer the sensitive altimeters in good condition with instructions at 17/6 plus 1/- postage.



RINGING SPEECH TRANSFORMER

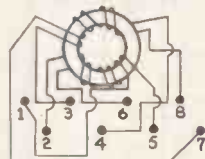

Totally enclosed in round black case. 2in. high, diameter approximately 3 1/2in. Circuit as per diagram, 6/6 each.

METAL DIVIDERS



Really well made for Government workshops. Ideal for marking out on metal chassis. Price 3/6.

PYREX AERIAL INSULATORS

Ideal for aerial connections through cabin walls or through panels. Consists of glass dome with threaded rod and terminal ends and metal fixing flange. Price 2/- each.



MINIATURE FLEX CONNECTORS

Plug and socket complete, ebonite, non-reversible. Ideal for toys razors, etc. 2 pair rating. 9d. pair. Bin D32B.



CLIX 15-AMP FOOT SWITCH PLUG

Made to B.S.S. specification, shuttered in moulded bakelite case, 8/6 each.



Orders under £2 add 2/6. under £1 add 1/9. Postable items can be sent C.O.D. additional charge approx. 2/6. Lis: fd Early closing days: Wednesday. Ruislip: Saturday. City.



PRECISION EQUIPMENT

WINDMILL HILL, RUISLIP, MDX, Phone: RUISLIP 5780
152-153 FLEET STREET, E.C.4. Phone: CENTRAL 2833

ELPREQ PAGES



ENAMELLED WIRE (On wooden reels)


| S.W.G. | 2 oz. Reel. | 4 oz. Reel. | 8 oz. Reel. |
|--------|-------------|-------------|-------------|
| 16 | 1/3 | 1/10 | 3/9 |
| 18 | 1/3 | 2/- | — |
| 20 | 1/4 | 2/2 | 3/9 |
| 22 | 1/5 | 2/4 | 4/2 |
| 24 | 1/6 | 2/6 | 4/2 |
| 26 | 1/7 | 2/8 | 4/6 |
| 27 | 1/8 | 2/9 | 4/6 |
| 28 | 1/8 | 2/10 | 4/6 |
| 30 | 1/9 | 3/- | 4/8 |
| 31 | 1/10 | 3/1 | 4/11 |
| 32 | 1/10 | 3/2 | 4/11 |
| 33 | 1/11 | 3/3 | 4/11 |
| 34 | 1/11 | 3/4 | 4/11 |
| 36 | 2/- | 3/6 | — |
| 38 | 2/2 | 3/10 | — |
| 40 | 2/4 | 4/2 | 7/6 |

TINNED COPPER WIRE.

| S.W.G. | 2 oz. Reel. | 4 oz. Reel. | 8 oz. Reel. |
|--------|-------------|-------------|-------------|
| 16 | 1/3 | 1/10 | 3/7 |
| 18 | 1/5 | 2/- | 3/11 |
| 20 | 1/4 | 2/2 | — |
| 22 | 1/5 | 2/5 | 4/- |

DOUBLE SILK COVERED WIRE.

| S.W.G. | 2 oz. Reel. | 4 oz. Reel. |
|--------|-------------|-------------|
| 16 | 1/3 | 1/10 |
| 18 | 1.3 | 1/11 |
| 19 | 1/5 | 2/3 |
| 20 | 1.6 | 2/6 |
| 22 | 1/8 | 2/10 |
| 23 | 1/9 | 3/- |
| 24 | 1/9 | 3/- |
| 26 | 1/11 | 3/4 |
| 27 | 2/- | 3/6 |
| 28 | 2.1 | 3/8 |
| 29 | 2/2 | 3/10 |
| 30 | 2/3 | 4/- |
| 31 | 2/4 | 4/2 |
| 32 | 2/6 | 4/6 |
| 33 | 2/9 | 5/- |
| 34 | 2/10 | 5/2 |
| 35 | 3/- | 5/6 |
| 36 | 3/2 | 5/10 |
| 38 | 3/6 | 6/6 |
| 39 | 3/9 | — |
| 40 | 4/- | 7/6 |
| 41 | 2/3 | — |
| 42 | 2/6 | — |

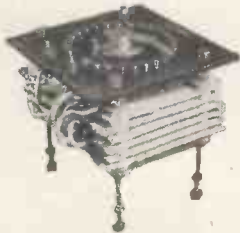

DIMMER RESISTANCE.


25 steps up to 60 ohms, maximum current 10 amp, minimum 1 amp. Size 8" x 8" x 7" deep. Complete with handle, rather soled but in good working order. Price 27/6, plus 5/- carriage and packing.

CRYSTAL OVENS.

Thermostatically controlled work off 230 v Price £4/10/-.


GROMMETS.

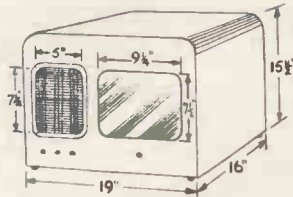1/8", 3/16", 1/4", 5/16", 3/8", 1/2", 5/8", 3/4", 1d. each.
3/8", 1", 1 1/4", 1 1/2", 1d. each.
Servicemar's packet of 24 assorted sizes, 2/-.



T.V. CABINETS.

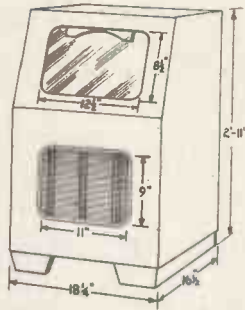Suitable for "Viewmaster," etc., well made and nicely finished, veneered and polished. Console Model £10/19/6. Table Model £6/19/6.



RADIOGRAM CABINET. A full size console type, walnut finish, takes standard type auto-change unit £12/10/-. Except where you can collect, these are available only with the delivery area of our own van, e.g., 50 miles from London. Delivery charge will depend upon distance.

BASIC ELECTRICITY EXPERIMENTER'S OUTFIT.

If you want to help someone with their electrical studies, this is an ideal gift. Made pre-war, this contains an assortment of over 50 bits and pieces including switches, galvanometer, resistance wire for making motors, Wheatstone bridge, meters and an instruction book detailing 31 experiments which cover the course up to Matriculation standard. This outfit if made to-day must cost £4 to £5. Limited quantity at 19/6, plus 2/6 postage and packing.



HIGH CYCLE MOTOR ALTERNATOR.

TYPE 1. Has a motor 230 v., 50 cycle single phase 2,800 r.p.m. coupled to a generator output 250 v., 1,728 cycles at .24 amps. Good condition with wiring diagram, £3/10/-, plus 7/6 carriage.
TYPE 2. Has a motor 230 v. 50 c. single phase coupled to an alternator, output 250 v. 625 cycles .24 amps. Price £3/10/-, p.us 7/6 carriage.




MORSE PRACTICE OUTFIT.

Consists of nicely balanced key mounted on base board with variable note buzzer with terminals and room for battery (Ever-Ready Type 1215, or can be fixed up for twin cell as illustrated). Ideal Christmas present for Scout or Air Cadet, Price 6/6 ess battery, plus 1/- postage and packing.

TRANSMITTER 1154.

This world famous Transmitter uses the P.A. stage of two PT15 driven by an ML6 as on Hartley Oscillator, sidetone being provided by a further ML6. Frequency coverage in three ranges 10 to 5.5 mc/s, 5.5 to 3 mc/s, 200 to 500 kc/s. Special mechanism for holding to and returning to frequencies. Complete with switches, tuning condensers, meters and a host of other parts. Worth £20 to £30. We have a few of these units left in good condition. Price 59/6 each. Carr. etc. 25/-, partly returnable. Don't miss this bargain.

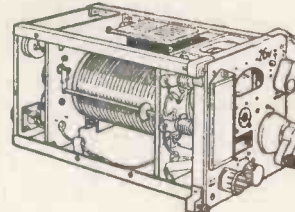


TUNING UNIT 126.

For matching transmitter to long wire aerial. Consists of a coil driven by a handle with roller contactor and revolution counter to show position of wheel on wire. Numerous subsidiary components. This is a continuously variable inductance which can be locked at any position. Price 17/6, plus 2/- post.

RADIO STETHOSCOPE.


A novel device aptly called - Radio Stethoscope is described in a recent edition of the "Radio Constructor," this is compact and can be slipped into the pocket rather like a fountain pen. With it in most districts a receiver can be checked from the grid of the first valve right through to the output without a signal generator, the stethoscope will operate in both L.F. and R.F. circuits without alteration. It is a complete fault finder.

The only parts needed to make the simple circuit tracer are a pair of crocodile clips, a germanium crystal, and a paper tubular condenser and we will supply whole outfit for 6/6 post free, and with each outfit we will give re-print of the article as it appeared in the "Radio Constructor." **NOTE.**—If you wish to make it up as a pocket unit then you will need a few other odds and ends, solder tags, etc., from your spares box.

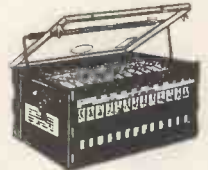

MILNES H.T. UNITS.

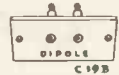120 volts 60 m.A., you charge these from a 6 v. car battery. Price 67/6 each—callers only or carriage at your risk.



SOCKET STRIPS. Paxolin mounted.

- Two socket engraved L.S. 6d. each. Bin. C16B.
- Two socket engraved A.E. 6d. each. Bin. C18A.
- Two socket engraved P.U. 6d. each. Bin. C19B.
- Two socket engraved Dipole 6d. each. Bin. C19B.
- Two socket plain. 5d. each. Bin. C18B.
- Three socket engraved DIP and E. 9d. each. Bin. C16D.
- Three socket engraved A1, A2 and E. 9d. each. Bin. C19D.
- Four socket engraved A.E. Pickup, 9d. each. Bin. C19E.
- Four socket engraved P.U. Ext. L.S. 9d. each. Bin. C16E.
- Five socket plain. 9d. each. Bin. C16C.

TAGSTRIPS. Paxolin mounted.

- Two lugs, one earthed, 3d. each. Bin. C17A.
- Three lugs, centre earthed, 4d. each. Bin. C17B.
- Four lugs, one end earthed, 5d. each. Bin. C17C.
- Six lugs, two ends earthed, 6d. each. Bin. C17E.



GROUP PANELS. Paxolin mounted.

- 5 components (10 lugs), 7d. each. Bin. C18CL.
- 6 components (12 lugs), 8d. each. Bin. C18CC.
- 11 component* (22 lugs), 1/- each. Bin. C18CR.

TERMINALS




Earthing screw terminals, 2BA, also used for connecting two spades (as C20A) together, 9d. each. Bin. C20C.

Screw down terminal 4 B.A. with plain insulated head. 5d. each. Bin. C50F.

Screw down terminal all metal. 6 B.A., 4d. each. Bin. C21C.

YAXLEY TYPE SWITCHES.

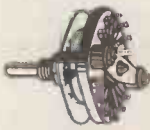

A.1 popular types and sizes in stock. Two Specials this month: Ceramic 3 pole 3 way, price 2/6 each. 6 pole 3 way, Price 2/6 each.

12in. TRUVOX SPEAKERS.

We have been out of stock of these grand reproducers for some months, but we have just had a delivery so now is your chance. Price £3 each.

AIR COOLED CHOKES.

No D.C. resistance, size 5 1/2" x 4" x 5" high, superior manufacture. Two types available (a) 6 milli-henries, (b) 85 milli-henries. Price 12/6 each.

OCTOPUS CLIPS.



An ideal clip for fixing anything to a rod or pole, this is self adjusting from 1 1/2" to 4 1/2". Price 1/- each.

CO-AXIAL CABLE.

70 to 80 ohms for T.V. by one of our leading manufacturers, medium thickness Price 1/2 per yard.

MORSE OSCILLATOR.

With variable note and variable output fitted with jack for external modulation Complete with valves. Price 15/-, postage and packing 2/-.



KLAXON.
Strap operated, soiled, but in good working order. Price 12/6.

UNIT TYPE RDFI

As suggested by "Practical Television" October as suitable for a home built Television, but with the complete set of 14 valves instead of 11, e.g., 5 of SP61, 2 of P61, 3 of EA50 and 1 each of CV63, EB34, EC53, 5Z4. Price 49/6, plus 5/- post.


194 STRIP.

Also described in the October "Practical Television," contains 8 valves and really does give superior results. Price 45/-, plus 2/6 postage.



1/3 HORSEPOWER ELECTRIC MOTORS.

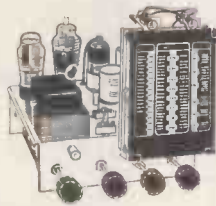
Solid cast body, well wound and impregnated. Heavy duty continuous rating. Price £5/15/-, carriage 7/6 extra.




3 WAVE-BAND 5 VALVE SUPERHET CHASSIS

Brand new, tested, and ready for immediate operation, full vision scale size 6" x 8" covering the long wave 200-500 metres, medium wave 37-100 metres, and short wave 13-37 metres. First class parts, Parmeko mains transformer, Eric resistors, Hunts condensers, etc. Special points include (1) Flywheel tuning. (2) Dust. (3) Cored I.F.'s. (4) Sockets for extension speaker and pick-up. (5) 4 watts output. (6) Coil speaker, £10/10/-, carriage, packing and insurance 7/6 extra.

BATTERY CHARGERS.

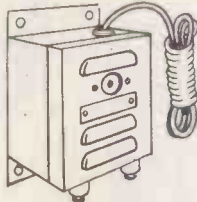

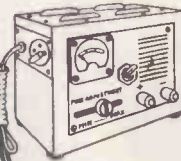Motorists you should have one of these, it will repay its cost the first night you leave your ignition switched on or otherwise run down your battery. Madison type charging 6 or 12 v. at 1 amp. Price 59/6. Amplion type charging 6 or 12 v. with ammeter and variable charging rate up to 2 amps. Price £6/6/-.



2V VIBRATOR UNIT (Battery Superseder).

American made for type 58 Walkie Talkie. Output 1.4 v. L.T. and 90 v. or 180 v. H.T. Price 49/6.



110 v. 2 1/2 AMP. RECTIFIER UNIT.

This is an excellent unit suitable for driving 110 v. D.C. equipment from 230 v. A.C. mains or for charging batteries for stand-by lighting, etc. Made for the Government—new and unused, with switchgear. Price £27/10/- each.


CARTRIDGE FUSES.

All types 6d. each, accurately rated, packets of one dozen. Available in the following sizes and amperages—

| 1/2" length | 3/16" length | 1" length | 1 1/4" length |
|-------------|--------------|-----------|---------------|
| Diameter | Diameter | Diameter | Diameter |
| 3/16" | 3/16" | 3/16" | 3/16" |
| 60 m.A. | 200 m.A. | 250 m.A. | 60 m.A. |
| 150 m.A. | 500 m.A. | 500 m.A. | 100 m.A. |
| 1 amp. | 1 amp. | 1 amp. | 150 m.A. |
| 2 amp. | 2 amp. | 2 amp. | 250 m.A. |
| | 5 amp. | 5 amp. | 500 m.A. |
| | 10 amp. | 10 amp. | 750 m.A. |
| | 15 amp. | 15 amp. | 15 amp. |

EQUIP YOUR LABORATORY.

You many times have felt the need of a device which would enable you to put resistance or capacity or a combination of these two quickly into a circuit. We have a small quantity of resistance capacity boxes which, by the simple manipulation of plugs, will enable you to do this. With these boxes you can put in 1 ohm, 2 ohms, 3 ohms, 4 ohms, and so on, in steps of 1 ohm, right up to 6,000 ohms. In a similar way capacity can be put into circuit by small amounts, thus making it simple for you to find optimum working conditions. These boxes made for Government Laboratories are available while they last at 19.6 each, plus 1/6 post and packing. Don't delay—order by return.

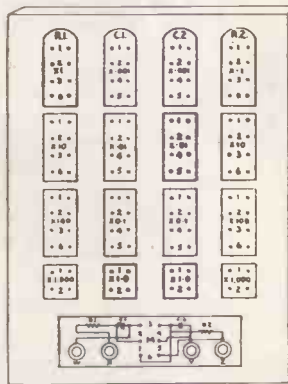

Orders by post are dealt with by our Ruislip depot. To avoid delay address to Electronic Precision Equipment, Ltd., Dept. 2, Windmill Hill, Ruislip, Middlesex.



500W PORTABLE HEATER.

Made by G.E.C. for the Navy, waterproof and almost indestructible, safe in the garage or other inflammable atmospheres. Price 19/6, plus 2/6 postage and packing.

SPEMET.

Made from polished aluminium, an excellent material for fronts of cabinets or for special cabinets you are making, and for air conditioners, etc.

Close mesh 8 holes to the inch. 24" x 12", 10/-, 12" x 12", 5/3. 6" x 6", 1/9. Wide mesh 4 holes to the inch. 24" x 12", 9/-, 12" x 12", 4/9. 6" x 6", 1/6. Postage and special packing 1/6 extra for any quantity up to 12 sheets. Over 12 sheets post free.

SLIDER RESISTORS.

Heavy duty type size. Size 7" x 1 1/2", 1.2 ohms 15 amps. Price 15/-.

TUNING ASSEMBLY.

Comprises 2 gang condenser, 6 iron cored coils, dial, wave-change switch and trimmer assembly for superhet covering 13-500 metres. Price 27/6.

COIL PACK.

Covering same range as above, aligned for 465 kc/s I.F. Price 25/-.

HARDWARE.

Serviceman's 3 gross assorted nuts, bolts and washers all useful sizes. Price 6/6. We endeavour to maintain stocks of wood screws, steel and brass round head and counter sunk, Parker Kalon self cutting screws, washers and studding. Send us your orders and enquiries.

U.S. HEADSETS.

Type HS30—Lightweight ear fitting type. 27/6 per pair.



ELECTRIC BELLS.

Loud ringing with double gong, operate off hand magneto or A.C. mains. Price 25/-.

Ex-equipment small round type, e.g. all the works under the dome for operation from dry batteries. Price 3/6 each.

Similar ditto, but for use on A.C. mains or magneto. Price 3/6.

Orders under £2 add 2/6, under £1 add 1/9. Postable items can be sent C.O.D., additional charge approx. 2/6. Lis. 6d. Early closing days: Wednesday Ruislip: Saturday, City.

WINDMILL HILL, RUISLIP, MDX, Phone: RUISLIP 5780
152-153 FLEET STREET, E.C.4. Phone: CENTRAL 2833



BUILD A PROFESSIONAL RADIO OR AMPLIFIER AT LESS THAN HALF TODAY'S PRICE

A MAINS OR BATTERY PORTABLE KIT



A Midget 4-valve Superhet Portable Set covering medium and long wavebands.

Designed to operate on A.C. mains 200/240 volts, or by an "Alldry" battery. The set is so designed, that the mains section is supplied as a separate unit which may be added at any time. The Kit therefore can be supplied (a) as an "Alldry" Battery Superhet Personal Set, which can then be accommodated in the Attache Case as illustrated above (size 9 1/2 in. x 4 1/2 in. x 7 1/2 in.). This is attractively finished in Dark Green or Blue Rezinex (b) or as a Combined Mains/Battery Superhet Portable Receiver, for which a polished Wood Cabinet is available to accommodate both Mains Unit and Batteries together. Circuit incorporates delayed A.V.C. and Pre-selective Audio Feedback. Kit is complete in every detail and includes ready wound frame aeriols, fully aligned I.F. Transistors, and drilled chassis etc. Overall size of assembled chassis 8 in. x 4 in. x 2 1/2 in.

We can supply the set either as a complete Kit of Parts for £8/16/9 (incl. P.T.), (plus Cabinet and Mains Unit), or by supplying the components separately. The complete Assembly Instructions, which include full price details (including prices of individual components), Circuit and Component Layout, etc., are available for 1/9 incl. postage.

A T.R.F. BATTERY "PERSONAL" KIT



A complete Kit of Parts to build a Midget 4-valve Alldry Battery Portable Set, covering medium waveband.

Consists of Regenerative T.R.F. circuit, employing Flat Tuned Frame Aerial with Denco Iron Dust Coiled Coil. Valve line up, two I.T.4's (R.F. Ampl. and Det.), 1B5 and 3SA output.

Kit is complete in every respect and includes drilled chassis, and latest type Bolo 3 in. P.M. speaker. Overall size of assembled chassis 4 1/2 in. x 2 1/2 in. x 3 1/2 in.

We can supply the Complete Kit (less cabinet) for £6/4/8 (inc. P.T.) or by supplying the components separately. The Complete Assembly Instructions, including individual component prices, Circuit and Component Layout, etc., is available for 1/-, incl. post.

A KIT OF PARTS

Complete in every detail, to build a 3-valve Amplifier for A.C./D.C. mains 200-250 volts.

Has an output of 3 watts, and incorporates a Tone Control. Valve line up, 25A6, 6J7, U81.

Our price of £4/12/6 for complete kit, includes a matched 6 1/2 in. P.M. speaker.

This Amplifier can also be supplied assembled and ready for use for £5/12/6.

You're SURE to get it at STERN'S ESTABLISHED 25 YEARS

A MIDGET 4-STATION "PRE-SET" RECEIVER

A complete Kit to build a 4-Station "Pre-Set" Superhet Receiver for A.C. mains operation. The Set is designed to receive any three stations on medium waveband and one on long waves, each station being received by the turn of a Rotary Switch—No Tuning being necessary.

It is of midget size, being 9 1/2 in. x 4 1/2 in. x 7 1/2 in. high, and has the performance of a far more expensive ready made set, but can be built for half the price.



Price of complete Kit or Parts (including aligned I.F. Transistors, and drilled chassis, etc.), £9 2/6 (incl. P.T.), (plus Cabinet 25/6), or the components can be purchased separately. The complete Assembly Instructions including Individual Component Price List, Circuit and Component Layout etc., is available for 1/9.

STERN'S "RADIO TUNER MANUAL" Price 2/6. (Plus 3d. Post). Contains complete and detailed assembly instructions showing how to make:—

A 1 Valve T.R.F. Tuning Unit, covering Long and Medium Wavebands.

A 4 Station "Pre-Set" Superhet Tuning Unit, producing 3 Stations on Medium Waveband and 1 on Long Waves.

A 2 Valve Superhet Tuning Unit, covering Short, Medium and Long Wavebands.

Each Tuner is for A.O. Mains operation. Circuit Diagrams and Practical Component Layouts are shown, together with complete component Price Lists.

THE WIRELESS WORLD MIDGET A.C. MAINS 2-VALVE RECEIVER

We can supply all the components to build this set, including Valves and Moving Coil Speaker for £3/10/-, including Designer's complete building instructions (these are available separately for 9d.).

THE "SUMMER ALLDRY" BATTERY PORTABLE

As published in June issue of "Practical Wireless." We can supply, from stock, all the components to build this Midget 3-valve Portable for £2/19/6 (less valves). This also includes dial, top panel and aly sheet for chassis. The complete article and circuit, including Practical Layout and Price List, is available for 9d.

PICK-UPS

Cosmoord "G.P.20." for standard records, £3/11/5; Interchangeable (G.P.19) Head for L.P. records, £2/3/4. Decca lightweight "turnover Head" type, for L.P. and standard records, £3/19/2.

Marconi, Standard, lightweight Magnetic, £1/15/10

Marconi Matching Transformer, 7/6.

Golding, Standard, lightweight, Magnetic, 29/6.

ALL KITS INCLUDE "EASY TO FOLLOW" POINT-TO-POINT WIRING DIAGRAMS

THE WIRELESS WORLD 3-VALVE SET



A Midget 3-valve T.R.F. Receiver for operation on A.C. mains, covering long and medium wavebands.

We are able to supply all of the components to build this set, as designed, and specified in the Feb. 1950 issue including the drilled chassis, valves, and moving coil speaker, etc., at the following prices:—


To construct complete chassis, less dial and drive assembly, £5/17/9. Ditto including dial and drive assembly, £5/12/8.

To construct the complete Set, including dial and drive assembly and cabinet, £6/14/3.

Overall size of cabinet is 7 1/2 in. x 5 1/2 in. x 11 1/2 in.

A reprint of the designer's article, giving Circuit and Assembly Instructions (this is available separately for 9d.), together with a Practical Component Layout is included with each of above assemblies.

BATTERY CHARGER KITS

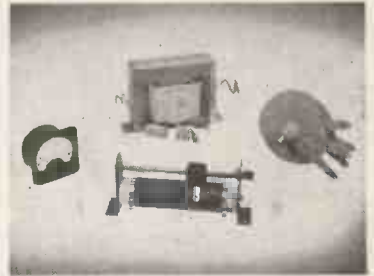

All Kits incorporate Metal Rectifiers, and are for use on A.C. mains 220-250 volts. All Kits include an easily followed Wiring Diagram.

For charging 6 v. battery at 1 1/2 amps., £1/3/9.

For charging 6 volt. battery at 1 1/2 amps., with Variable Resistor and Meter, £2/4/3.

For charging 12-volt battery at 1 1/2 amps., £1/6/9.

For charging 12-volt battery at 1 1/2 amps., with Variable Resistor and Meter, £2/7/6.

For charging 6 or 12 volt battery at 3 amps., £1/19/0.

For charging 6 or 12 volt battery at 3 amps., with Variable Resistor and Meter £3/1/6.

THE WIRELESS WORLD MODERN CRYSTAL SET

Designed for the Pre-selection of THREE STATIONS to suit local conditions, each station being received by the turn of a rotary switch. We are able to supply all components including drilled chassis to build this new type of Receiver, to the designer's specification, as published in October issue, for 36/3 (plus cost of selected coils). A reprint of the designer's article (available separately for 9d.), together with a practical component layout make the assembly very easy.


★ Send 6d. P.O. for our STOCK LIST, it shows "hundreds" of Wireless

When ordering please include

STERN RADIO LTD., 109

Tel.: CENTR

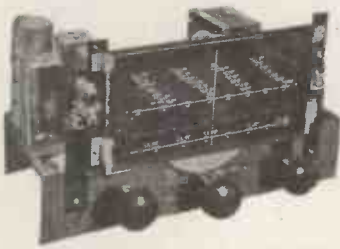AN A.C. MAINS "ALL-WAVE SUPERHET" CHASSIS



A completely assembled chassis for A.C. mains 200-250 volts, designed for good selective and quality reproduction, and serves as an ideal replacement chassis for that "old radiogram, etc."


Incorporates in addition to the three controls shown above, a Tone Control and a Radio-Gram Switch. These two are left on "floating leads" to enable them to be placed in any position on cabinet.

The set employs a modern 5-valve line up, and covers three wavebands, 16-50, 190-550 and 800-2,000 metres. Fly-wheel tunings incorporated.

Overall size of assembled chassis, 13 1/2 in. x 6 in. x 8 1/2 in. high. Dial size 9 in. x 4 1/2 in.; an attractive Dial Escutcheon Plate is supplied.

Price of complete chassis, wired and ready for use £14/19/6.

A QUALITY "PUSH-PULL" AMPLIFIER KIT

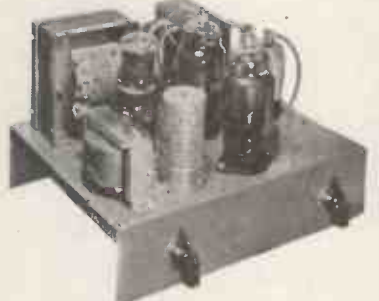

A Kit of Parts to build a 6-8-watt Push-Pull Amplifier for operation on A.C. mains 200-250 volts. Incorporates a simple arrangement to enable either a magnetic, crystal, or light-weight pick-up to be used. A 10-watt Output Transformer is designed to match from 2 to 15 ohm speakers. Tone control is incorporated. The overall size of the assembled chassis is 10 in. x 8 in. x 7 1/2 in. high. Price of kit, complete in every detail, including drilled chassis and valves, £6/5/-. Component layouts supplied.

Price of assembled chassis, supplied ready for use, £7/10/-.

"PERSONAL SET" BATTERY ELIMINATOR

A complete kit of parts to build a Midget "Aldry" Battery Eliminator, giving approx. 69 volts and 1.4 volts. This Eliminator is for use on A.C. mains and is suitable for any 4-valve Superhet Receiver requiring H.T. and L.T. voltage as above or approx. to 69 volts



The kit is quite easily and quickly assembled and is housed in a light aluminium case, size 4 1/2 in. x 1 1/2 in. x 3 1/2 in. Price of complete kit, with easy to follow assembly instructions, 42/6.

In addition we can offer a similar COMPLETE KIT to provide approx. 90 Volts and 1.4 Volts. Size of assembled Unit 7 in. x 2 1/2 in. x 1 1/2 in. Price 47/6.



TWO NEW Denco ULTRA MIDGET SUPERHET COIL TURRETS
Both having a Rotary Turret Action

- (a) The O.T.9. Turret consists of 4 STATION "PRE-SET" UNIT, from which any three Stations on Medium Waveband and one on Long Waves can be received by a turn of the Turret Switch.
- (b) The O.T.10 Turret being a 3 Waveband Coil Pack, incorporating a fourth switch position providing for completely switching out Radio when using gram. The complete coverage is Long Waveband 700 to 2000 metres; Medium Waves 190 to 570 Metres and Short Waves 15 to 50 Metres.



The outstanding advantages these units have over other similar units can be readily seen, the main features being (a) Neat and Compact, the overall size being only 2 1/2 in. dia. x 1 1/2 in. deep.

- (b) Fitting is simplicity itself, each Turret having one hole fixing and requiring only four connections.
- (c) The Rotary Turret design switches the actual Coils, which incorporate variable iron dust cores, on to positive contacts, thereby reducing stray capacities to the absolute minimum.
- (d) They are supplied Factory wired and aligned and have been designed to operate with any conventional circuit arrangement of 465 kc/s, and due to their unique design are extremely sensitive and efficient.

Price - O.T.9. Turret 39/6. O.T.10 Turret 52/-. A complete Receiver circuit together with headset containing all necessary data is included with each Turret. These can be supplied separately for 6d.

THE FAMOUS W.B. "STENTORIAN" RANGE OF P.M. SPEAKERS

| Size | Impedance | Watts | Price |
|-----------|-----------|-------|-------|
| 2 1/2 in. | 2-3 ohms | 1 | 18/6 |
| 3 1/4 in. | 2 | 2 | 19/6 |
| 5 in. | 2 | 4 | 21/- |
| 6 in. | 3 | 3 | 24/6 |
| 7 in. | 3 1/2 | 3 | 23/6 |
| 8 in. | 5 | 5 | 32/6 |
| 9 in. | 7 | 5 | 44/6 |
| 10 in. | 10 | 10 | 49 |
| 12 in. | 16 | 15 | £9 |

New Mfrs. Surplus Speakers. All 2 1/2 ohms. 2 1/2 in. 15/-; 3 1/4 in. 14/6; 5 in. 14/6; 6 in. 15/6; 8 in. 16/9; 10 in. 19/6; New Type Rols. 3 in. 21/-; 4 in. 22/6.

Output Transf. Midge 600 (or 90-1) in. x in. x 1 1/2 in. 3/9. 5-watt Multi-ratio, 12 tapplings between 24-1 and 114-1 (some O.T.), 8/6. Wharfedale, 12 watt, push-pull, multi-ratio, 25/-; P/pull, 20 watt, multi-ratio, 37/6, and many others.

Ext. Speaker Volume Control, 2/6. New Electrolytic Condensers. Not Ex-Govt. All 450/500 volts, 8 mfd. (1 1/2 in. x 1/2 in. dia.), 3/-; 8 mfd. (1 1/2 in. x 1/2 in. dia.), 4/9; 16-8 mfd. (1 1/2 in. x 1/2 in. dia.), 5/6; 16-16 mfd. (1 1/2 in. x 1/2 in. dia.), 5/9; 32-32 mfd. 350 volt, 5/9; Cardboard Tubular (1 1/2 in. x 1/2 in. dia.), 3/6; 8 mfd. 500 v. 4/-; 16 mfd. 500 v. 5/9. Can. Standard size all 500 volts, 4 mfd. 3/6, 8 mfd. 4/3; 8-8 mfd. 5/9; 16 mfd. 5/6; 16-16 mfd. 7/9; 32 mfd. 9/9.

Denco I.F. Liser, for accurately lining 465 K/c. and 1.6 m/c. I.F. channels, and associate circuits. Battery operated - small and completely self-contained, 47/6.

Potentiometers. New, not Ex-Govt. 2K, 5K, 10K, 25K, 50K 100K, 250K, 1 and 2 meg. Price, less switch, 3/9. Price with S/Pole switch, 5/9. Price with D/Pole switch, 6/6.

Surplus Potentiometers. All standard with extended splines, 5K, 10K, 15K, 20K, 25K, 50K, 100K, 1 and 2 meg., 2/- each.

Coils, Denco "Maxi Q," midget size, Litz wound on Polystyrene Formers, with adjustable iron cores. Available for Aerial H.F. and Oscillator 465 K/c. or 1.6 M/c. 3/9, each, or with reaction winding 4/9. Denco Matched pair T.R.F. Coils for long and medium waves, 6/6 pr. Weymouth matched pairs of coils, for T.R.F. covering long and medium waves, 10/6 pr. or for Superhet covering Long, Medium and Short Waves, 11/6 pr. All types of Wearite "P" coils in stock at 3/9.

Coil Packs. Osmer Midget Coil Pack. Size 3 1/2 in. x 2 1/2 in. 1 1/2 in. covering S. M. and L. waves. Coils wound on Polystyrene Formers with adjustable iron cores, ensure efficient performance. Factory wired and aligned. Price including full circuits for Superhet 465 K/c. Unit 52/- (incl. P.T.). This Denco Coil Pack is also available for Midget Superhet BATTERY Portable sets including a matched ready wound Frame Aerial. Price 54/2 (incl. P.T.). Weymouth Midget 3 1/2 x 2 1/2 in. covering S.M.L. w/bands, for 465 Kc/s., employing Matched Iron Core Coils on each w/band, 51/6.

Wearite Pack 4 1/2 x 3 1/2 x 1 1/2 in. Type 706 covers two short w/bands and medium w/band and Type 705 covers short-medium-long waves. Both for 465 kc/s. Incorporates gram. position, and employs adjustable core coils, 53/4.

All the above Coil Packs include Switching, Padding and Trimmer Condensers. L.F. Chokes. Midget 10 henry 250 ohms 40 mA., 3/6. 20 henry 250 ohm 60 mA., 6/6; 20 henry 300 ohm 100 mA., 12/9; 5 henry 60 ohm 250 mA., 28/6; 20 henry 250 ohm 150 mA., 15/6; 8 henry 250 ohm 120 mA., 8/6; 18 henry 20 x 7 x 2 1/2 in., 250 mA., 26/6.

I.F. Transformer, 465 K/c. New well-known manufacturer's surplus 1/2 in. x 1/2 in. x 1 1/2 in. Iron Core, 3/- each. Denco Iron Core, 465 K/c. or 1.6 m/c., 1 1/2 in. x 1 1/2 in. x 3 1/2 in. 16/6 pair. Wearite Stand Cap. Tuned 465 K/c. 20/- pr. New Surplus 465 K/c. Iron Core, 4 in. x 1 1/2 in. sq., 10/- pr. Transformers. (a) Input 230 volt, output 200 v/4 amp. and 6.3 v., 9 amp., 11/-; (b) Input 230 volts, output 250 volts 30 mA., and 6.3 volts 1 amp., 13/9.

E.H.T. Transformer. Prim. 230 v. Sec. 5 Kv. and 4-volt tapped 2 volt, 59/6. Do. but 4 kv., 54/-. Heater Auto Transformers. (a) Tapped 2 v., 4 v., 5 v., and 6.3 volts 3 amp., 9/6; (b) 4 v., 3 amp., to 5 v., 3 amp. Reversible, 6/6; (c) 4 v., 3 amp. to 6.3 v., 2 amp. Reversible, 6/6.

NEW SURPLUS FOSTER TRANSFORMERS. Primary 230 volts. Secondary 12 volts 3 amps., 21/-.

Filament Transformer. Input 230 volts, output 6.3 v., 1 1/2 amp., 8/3; 4 v., 1 1/2 amp., 7/6; Input 200/250 v. output 4 v. (O.T.), 1 1/2 amp., 4 v., 2 amp., 6.3 v., 2 amp., 10/6. Input 230 v. output 6.3 v. (O.T.) 4 amp., 17/6.

Ictal Chassis, substantially made with four sides, 7 in. x 4 in. x 2 in., 3.11.9 x 5 x 2 1/2 in. 5.3, 10 x 8 x 2 1/2 in. 6/-, 10 x 7 x 2 1/2 in. 4.6, 12 x 9 x 2 1/2 in. 7/9, 14 x 4 x 2 1/2 in. 8.3, 16 x 8 x 2 1/2 in. 9/-.

Mains Transformers. All New Stock with Primaries tapped for 200-250 volts. Secondaries (a) 250-0-250 volt, 80 mA., 6.3 v. (tapped 4 v.) 4 amp. and 5 v. (tapped 4 v.) 2 amp., 18/6 (also available with 350-0-350 volt at 18/6). Sterco's 350-0-350 volt, 150 mA., 4 v. (tapped 4 v.) 4 amp. and 5 v. (tapped 4 v.) 2 amp., 18/6; (c) 350-0-350 v. 250 mA. 4 volt, 8 amp., 4 v., 3 amp., 6.3 v. (tapped 2 v.) 2 amp. and 6.3 v., 8 amp., 84/-, and many other ratings.

Westinghouse Rectifiers. (a) H.T. 61. Rated 350-0-350 volts, 100 mA., 35/-; (b) H.T. 52. Rated 350-0-350 v., 200 mA., 37/6; (c) H.T. 53. Rated 500-0-500 v., 200 mA., 50/-.

Types, 14D36 11/3; 16HT28, 12/6; 16 EHT56, 17/9; 36EHT25, 13/10; 36 EHT35 18/2; 36EHT40, 20/6; 36EHT45, 22/6; 36EHT50, 24/10; 36EHT60, 25/6; 36EHT100, 25/-; 36EHT114, 7/9.

F. Wave Bridge Rectifiers. For charging 2, 4 or 6 volt at 1 1/2 amp. 8/6 For charging 6 or 12 volt at 1 1/2 amp. 12/6 For charging 6 or 12 volts at 3 amps. 21/6 For charging 6 or 12 volts at 5 amps. 28/10 For charging 12 or 24 volts at 3 amps. 25/9

A Variable Resistor for control of Charging Equipment (or Models) up to 3 amps., 15/-.

Suitable Charger Meter, max. 4 amps. 7/6. Meter Rectifiers, Westinghouse 250 microamp., 11/6; 1 m.A., 10/6; 5 m.A., 6/6.

Selenium Rectifiers. H.T./H.E. wave. 250 v. 30 mA., 5/6; 350 v. 100 mA., 7/6. 260 v. 170 mA., 13/9.

Charger Transformers. Suitable for use with preceding Rectifiers. Eac. has input of 230 volts. Outputs (a) 30 volts tapped 15 v. and 9 v. at 3 amps., 25/6; (b) 30 volts tapped 15 v. and 9 v. at 3 amps., 26/3; (c) 15 volts tapped 9 v. at 3 amps., 19/6; (d) 12 volt-1 1/2 amp., 12/3; (e) 15 volts tapped 9 v. at 6 amps., 24/3; 15 volts tapped 9 v. at 1 1/2 amp., 15/3 12 volt-1 amp., 7/6.

A Battery Charger Wiring Diagram is included with purchase of Charger Transformer and Rectifier.

Adjustable Mains Droppers, 1 1/2 in. dia. x 2 1/2 in. (a) 15 amp. 1,500 ohms, 5/-; (b) 2 amp., 1,000 ohms, 4/-; (c) 3 amp., 800 ohms, 5/-.

Television. We keep a very complete catalogue of TV components. The Viewmaster TV Assembly Instructions showing Practical Layout and Price List in stock, price 5/6 (incl. post). We can supply all the specified components for the TV, ex stock, either by way of individual components or by the published stage.

9" Max Chassis Cutters. The quickest and also simplest method of Chassis cutting, consists of a die, punch, and Allowance.

To cut 1/2 in. dia. (B7C) 10/6 To cut 1/2 in. dia. (B8A) 10/6 To cut 1/2 in. dia. (Octal) 13/6 To cut 1 1/2 in. dia. (English) 13/6 To cut 1 1/2 in. dia. (EF30) 14/6

Key for any of above 1/- Adjustable Chassis Cutter for holes from 1/2 in. to 2 1/2 in. dia. (used with hand brace), 7/6.

The Handy-Utility 7 1/2 in. Portable Electric Drill for use on A.C. or D.C. mains. A powerful and robust drill that will drill wood, metal, and almost anything, can also be used for grinding, buffing and wire brushing, etc. Employs instant release trigger switch. Price £6/10/-.

Describe leaflet is available. With instrument type kit for use on A.C. or D.C. mains. 22-1. Spare elements and bits always in stock.

Ex-Govt. complete set of Moving Coil Headphones and Microphone with headset, 10/6.

Components and many KITS OF PARTS for both Sets and Battery Chargers. Approx. cost of Post & Packing.

& 115 FLEET STREET, E.C.4

5814 and 2280

OUR 16TH YEAR.

MONEY SAVING OFFERS



CONTROL UNIT 499. Size $5\frac{1}{2} \times 5 \times 3$ in. Slow motion drive, switches and useful parts. 5/-, post paid.



CONTROL UNIT 410. Size $5 \times 3\frac{1}{2} \times 3$ in. Brand new. 25 k. pot, 2 S.P.D.T. switches, one 3-way switch, 1 D.P.S.T. jack push switch. Neat case. 5/-, post 1/-.




CONTROL UNIT. Ex-R.A.F. type 88a, ref. 10L/137. Brand new. Mahogany case with sloping grey enamel panel size 12×7 in. Overall size of case: base, 12×9 in.; top, 12×4 in.; Height, 7 in. Fittings include red and green calling lights, R.T./W.T. switch, send/

receive switch, sidetone control, 1 mike, 2 telephone and 1 key jack sockets. Interior chassis size L. 11 in., W. 8 in., D. 1 in. Components include VT20 (2ZOP) valve, 3 L.F. transformers, various first-grade resistors and condensers, outlet cable of 10 way $\frac{1}{2}$ in. screened lead (detachable), terminating in 10 way Jones plug, 2 additional outlets terminating 1 with miniature 2-pin socket and 1 with standard jack plug. A magnificent control unit for your amateur radio station. Price while they last, 25/- each, carr. paid



G.E.C. Ex-GOVT. TRANSMITTER/RECEIVER. M.R. series. 10 valves. 1 Det. 19, 1 L63, 1 H63, 1 D63, 3 KTW63, 1 KT63, 2 EF50 (value of valves exceeds £10 at current prices), 2 westectors, etc. Grey enamel case size $10 \times 8 \times 7$ in., weight 22 lbs. All valves guaranteed. Operating frequency around

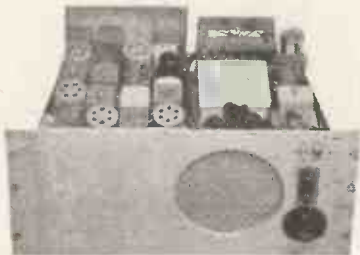90 mcs. We regret we have no precise technical data on this instrument. Apparently designed for mobile work with crystal control (no crystals included). An outstanding bargain at £3/19/6, plus 5/- packing and carriage. Condition as new.



G.E.C. TRANSMITTER/RECEIVER, with power pack. Same specification as M.R. series illustrated on this page, with the addition of A.C. power pack. This incorporates heavy duty mains transformer and choke 5u4G rectifier valve, smoothing condensers, circuit breaker, 6in. P.M. speaker, H.T. switch, mains switch, jewel light, output attenuator. Front panel size 19×8 in., grey enamel finish. Front to back width, 12 in.; weight, 60 lbs. First-class condition. Bargain price 6 gns., plus part packing and carriage 12/6



JUNCTION BOX. Type 204 Ref. 10A/16002. Length $7\frac{1}{2} \times 3 \times 3$ in. 5 4-pin outlets, 2 2-pin outlets, grey enamel. Brand new. Weight 2 lbs. Useful round the shack. 2/- each, post 6d. As illus.



TELEVISION PRE AMPLIFIER. Just the thing you have been looking for. This ex-Govt. 1-valve pre-amplifier is extremely sensitive and stable. It makes an amazing improvement in both vision and sound reception in all fringe areas. Available for London (type A), Birmingham (type B), Holme Moss (type H).

Very small dimensions. Length, 4 in. Width, 3 in. Chassis depth, 1 in. Overall depth from top of valve, 4 in. Fitted with EF50 valve. Ready for use. Power requirements 6.3 v. L.T. 200/275 v. H.T. Coax. Input and Output sockets. Ideal for "The Viewmaster" "The Inexpensive Television Set." Electronic Engineering Telesov, and any commercial set with suitable power supply. Unique value at the price of 15/- (post paid)

EDDYSTONE 358J COMMUNICATIONS RECEIVER (4 only). Grey cabinet with chrome handles. Size L19, W13, D11, 7 valves. EF39 (4), ECH35, EL32, EBC33. Valve check meter switched to all valves. Controls; H.F. gain, H.T. on/off, 120 ohm and 2,000 ohm phone jacks. B.F.O. switch, A.V.C. switch, L.F. Gain, B.F.O. Control, Tone, main tuning with micrometer indicator. Each set is complete with Eddystone 230 v. A.C. Power Unit incorporating 524 rectifier with heavy duty smoothing chokes. Separate power switch. Grey case size $11\frac{1}{2} \times 6\frac{1}{2} \times 3\frac{1}{2}$ in. loud speaker in grey enamel cabinet 8 in. unit with high and low impedance connections. Nine Eddystone coils giving continuous coverage from 90kcs. to 31mcs. Everything for a complete station. These ex-Govt. receivers have been used, but are in ex. cond. Really outstanding value at £25 each carr. paid per pass. train.

R1224A 5-VALVE BATTERY RECEIVERS. A few only. These very scarce 3 waveband battery superhets, tune 30-300 metres. Valves: 2 VP23's, FC2A, HL2, PM2A included. IF 470 kcs. Has R.F. stage, Muirhead diodes, 2 output jacks, Air Force grey cabinet. Requires 120 v. H.T. and 2 v. L.T. Outstanding performance. Price £7/10/- carr. paid.

CRYSTAL MULTIPLIERS for the ET4336 Transmitter. New condition. Less valves and M.A. meter. 30/- each, carr. 3/6.

CAY TUNING UNITS 4715A. 800-1,500 kcs. Brand new in metal case with lid, 3 slow motion dials, 4 switches. Many fine components. 15/-, or without case 10/-, carriage 2/6.

SECTIONAL AERIAL MASTS. Approx. 30ft. Seasoned timber. 10 metal sleeved sections. Store soiled but absolutely sound. 30/- each, carr. 5/-, Last few.

C/3 VOLTAGE CONTROL UNIT. Ref. No. 5U/1269. Contains on/off switch, pilot light, 6 bank fuse panel, 5 plus 3 mfd. Heavy duty fully filtered mains suppressor. Handsome case. Size $11 \times 8 \times 7\frac{1}{2}$ in. 10/- each, carr. 2/6.

PAMPHONIC P.A. SPEAKERS. 10in. high flux unit (not surplus). Handsome maroon cellulose metal cabinet $20 \times 9 \times 13$ in., impedance 3 ohms. New and unexpected delivery enables us to repeat this popular item. Price 55/-, carr. 4/-.

CONTROL UNIT 454A. Brand new in sealed packing. Size $8\frac{1}{2} \times 6\frac{1}{2} \times 3\frac{1}{2}$. Fitted with 0-1 mA. meter, four 50k pots., 1 5k pot., 1 250k pot., 1 D.P. toggle switch, 3 jewel light jacks, 1 G.P.O. type 2 pole switch, 1 Yaxley-5-pole switch. Suitable as basis for a good test meter. Price 30/-, carr. paid.

RECEIVER TYPE 25 (TR1196). Easily converted to all wave superhet. Data supplied. 6 valves: EF36 (2), EF39 (2), EK32, EBC33. New condition. Last few. 39/6, post and packing 2/-.

TELEVISION AERIALS. Birmingham Frequency H. Type. Famous Aeriatec manufacture. Complete with 8ft steel mast, masthead bracket, lashing, bracket and thimbles, etc. While they last 100/- each, carr. paid. Current list price £6/5/0. These are perfect for Holme Moss within 40 miles.

AMPLIFIER A1271. Brand new. Size 5in. cube. Fitted VR56 (EF36) D.P.D.T. switch. Relay. 2 mfd. potmeter, 2 trans. Neat case Unique value. 10/- each, post 1/6.



AIR MINISTRY COMMUNICATIONS RECEIVER R1155. Brand new in transit cases. We mean BRAND-NEW. These sets are unique and have never been used. Price, unfortunately, is a little higher than usual, but having regard to their condition would be cheap at £20. Supplied complete with "Wireless World" 12-page data sheet. These sets cover the following frequencies: 18.5-7.5 mcs., 7.5-3 mcs., 1,500-600 kcs., 500-200 kcs., 200-75 kcs., 9 valves and Magic Eye. Price 14 gns., carr. paid.

1155 POWER PACK AND OUTPUT STAGE, complete with U50 and KT63 valves (not surplus). Black crackle case $12 \times 8 \times 5$ in., built in 5in. P.M. speaker and phone jack Operates on 200/250 v. A.C. Connections terminate in Jones plug which enables instant operation of receiver without any modifications whatsoever. Made to "Wireless World" specification. Matches in appearance with receiver. Price £6/10/-, plus carriage 3/6.

SATISFACTION GUARANTEED AS ALWAYS

ITEMS OVER 15 lbs IN WEIGHT CANNOT BE SENT C.O.D

H.P. RADIO SERVICES LTD.

BRITAIN'S LEADING RADIO MAIL ORDER HOUSE

55 COUNTY ROAD, LIVERPOOL 4. Est. 1935. Tel. A14/12448.



TELEVISION CONSOLE CABINETS DE LUXE BEAUTIFUL WALNUT VENEER

BOOST E.H.T. KIT. Comprises one selenium rectifier, one 2-meg. resistance and two T.C.C. .001 mfd. 6 kV. condensers. For converting 9in. T.V. receivers to 12in.

10 in. CONVERSION KIT

Comprises 10in. Cossor cathode ray tube type 108K, line fly-back E.H.T. transformer, EY51-EHT rectifier, scanning coils, 10in cream mask and armour plate glass.

YOURS FOR £15.10.0
Carriage and insurance 25/- extra.

12 in. CONVERSION KIT

Comprises 12in. cathode ray tube (by either Brimar, Mullard or Mazda), Boost EHT Kit, 12in. mask and armour plate glass. Inductance width control.

YOURS FOR £20.18.4
Carriage and insurance 25/- extra.

For 12in. cathode ray tubes. Beautiful figured medium walnut finish, with high polish. Fitted with shelf for receiver, glass, speaker baffle and fret, and castors for easy movement. Undrilled. Suitable for use with the Viewmaster. "Practical Television," "Practical Wireless," and "Wireless World" televisions.



LASKY'S PRICE £8.10.0

Carriage 12/6 extra.

Outside dimensions of cabinet: 17½in. x 16½in. x 32in.

Why not convert your table receiver to a console?

Adaptor frames for fitting 9in. or 10in. C.R. tubes available if required.

LASKY'S 20/- Postage 1/- extra.

FRAME BLOCKING OSCILLATOR TRANSFORMERS. LASKY'S PRICE 4/6 each. Post 4d. extra.

BRAND NEW AND UNUSED. CATHODE RAY TUBES. COSSOR 108K. 10in. Magnetic tube. Uses a special ion trap which prevents screen burn. **LASKY'S PRE-BUDGET PRICE £12.12.0** Carriage and insurance 22/6 extra.

CATHODE RAY TUBES. All types and sizes available from stock. Brand new and fully guaranteed.

12in. from £18 4 10
15in. from £22 16 10
16in. from £24 6 5

CO-AXIAL CABLE. Standard impedance. Single screened, 1/- per yard. Twin screened, 1/6 per yard. Twin balanced feeder, 7/1d. per yard. Post extra. Any length cut to your requirements. 10% discount on 50 or more yards.

EVERYBODY IS BUILDING THE VIEWMASTER

The television set you can build at home from standard parts. Holme Moss, Sutton Coldfield and Alexandra Palace operation. Brilliant high definition black and white picture.


Superb reproduction. Uses 9in. or 12in. Cathode Ray Tube.

Table or Console Model. Incorporates all the latest developments.

Television for the home constructor at its finest.

Send to-day for the **CONSTRUCTION ENVELOPE**, a 32-page booklet crammed with top-rate information and all the necessary data, also 8 full-size working drawings and stage by stage wiring instructions. Model "A" for use in London and Home Counties. Model "B" for use in Sutton Coldfield Area. Model C for Holme Moss.

PRICE 5/- per copy Post free.

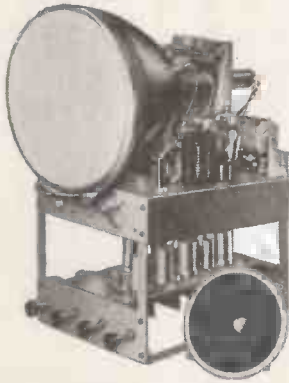

ALL COMPONENTS IN STOCK AND SOLD SEPARATELY

8in. CLOSED FIELD LOUD-SPEAKERS. Ideal for television receivers. Less of/trans. 3 ohms. Will not affect your C.R. tube.

LASKY'S PRICE 17/6 Post 1/6 extra.

T.C.C. VISCONOL HIGH VOLTAGE CONDENSERS (Cathodray).

.001 mfd. 6 kV. Price 4/6 each.
.001 mfd. 12.5 kV. Price 7/6 each.
.1 mfd. 7 kV. Price 15/- each.
.1 mfd. 6 kV. Price 10/- each.
All post extra.

ENGRAVED KNOBS. 1½in. diameter. ¼in. Spindle. For television, radio and amplifiers. All types. (Brilliance, tone, etc.). **PRICE 1/6** each. Post extra.

WIREWOUND COLVERN POT/METERS. Most values. **LASKY'S 3/6** each. **PRICE** Post extra.

TELEVISION VALVES. MOSTLY AT PRE-BUDGET PRICES. EL38, EL33, 6P28, 6K25, EY51, 62B7, 7C5, PL38, P230, GZ32. Etc. **NO SHORTAGE AT LASKY'S.**

CATHODE RAY TUBE MASKS
9in., with fitted armour plate glass 10/6
less glass 7/6
10in. 9/6
12in., soiled white... 10/-
Brand new white Special for flat face tubes..... 22/-
Postage 1/6 each extra.

ARMOUR PLATE SAFETY GLASS. For 9in. tubes 3/11, 12in. 4/11 per piece. Post 1/- each.

TINTED SCREEN FILTER PLATES. 9in.-10in., 18/6; 12in., 25/- Postage 1/- each extra.

CATHODE RAY TUBE SCREEN ENLARGERS. 6in. clear, 25/-; filter 27/6, carriage and ins. 3/6 extra. 9in.-10in. clear 55/-; 12in. clear 75/-; filter 80/-, carriage and ins. 7/6 extra.

LONDON, MIDLAND AND HOLME MOSS TELEVISION AERIALS. By K. A. Ltd. Single dipole. Price 33/- H Type 66/- CARRIAGE FREE.

RECEIVER UNIT TYPE 153. (45 Mc/s. Pye Strip), BRAND NEW AND UNUSED. Contains 4RF stages, detector, video amplifier and phase splitter. Uses 6 EF50 and 1 EA50. Stripped from brand new equipment. Supplied with all 7 valves. Full circuit and data free with each unit. **LASKY'S PRICE 63/-** Post Free.

MONEY BACK GUARANTEE. Everything ordered from Lasky's, is guaranteed as advertised. If you are not more than satisfied, return goods for cash refund.

LASKY'S RADIO

370 HARROW ROAD, PADDINGTON, LONDON, W.9

(Opposite Paddington Hospital)

Telephones: CUNningham 1979 and 7214

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m., Thurs. half day 1 p.m. Send 2½d. stamp with your name and address (in block letters please) for a copy of our current stock list giving details of our supplies of new manufacturers' surplus equipment and ex-government radio, radar and valves, etc.




RED HOT VALUE AN ALL WAVE RECEIVER CHASSIS AT HALF PRICE

NOT A KIT, BUT A FACTORY BUILT JOB.
FULLY ASSEMBLED, ALIGNED AND TESTED.

Made by a well-known manufacturer. 5 valve
superhet, 3 wavebands, long, medium and short.
For A.C. mains, 200-250 volts.

HIGHEST QUALITY COMPONENTS USED
THROUGHOUT.

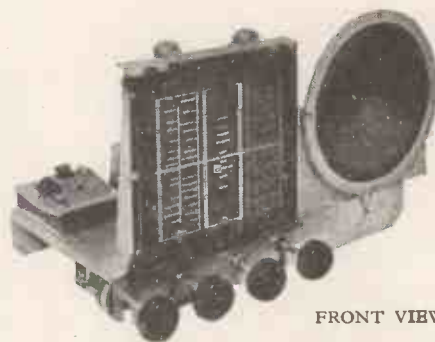Size of chassis :—15½" wide, 8" deep, 2¼" high.



FRONT VIEW

**A BRAND NEW
FULL SIZE
RADIO**

LASKY'S
PRICE


£10 . 19 . 6

Complete with
5 valves
and speaker.

Carriage and insurance 10/6 extra.

LOOK AT THESE FEATURES

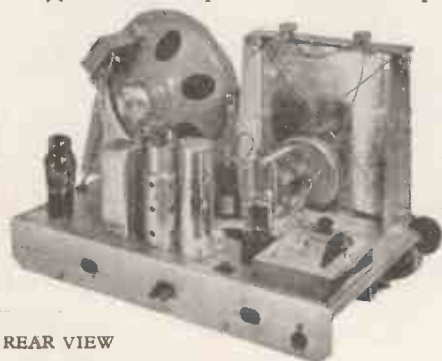- ★ 5 New Brimar valves
- ★ 8" Elac p.m. speaker
- ★ Variable tone control
- ★ Large edgelit dial, 7½" square
- ★ 2-speed tuning with nylon drive
- ★ 4 watts output
- ★ Sockets for p.u. and extension speaker
- ★ 465 Kc/s I.F.
- ★ A.V.C.
- ★ Circuit diagrams



REAR VIEW

A beautiful walnut plastic
cabinet, size :—19" wide,
10" deep, 12½" high as
illustrated. (Knobs extra).



LASKY'S PRICE 25/-

Carriage, packing and insurance 10/- extra.

If you need further details, please write. Circuit diagrams supplied separately for 1/6.
Better still call and hear it yourself.

SOLD ONLY BY —

LASKY'S RADIO

370 HARROW ROAD, PADDINGTON, LONDON, W.9

(Opposite Paddington Hospital)

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m., Thurs. half day 1 p.m. Send a 2½d. stamp with your name and address (in block letters please) for a copy of our current stock list giving details of our supplies of new manufacturers' surplus equipment and ex-Government radio, radar and valves, etc.

Telephones: CUNningham 1979 and 7214

WEARITE I.F. TRANSFORMERS. Type 550

Permeability tuned, 445-520 Kc/s. Type 551. Critically coupled, with top grid connection. Type 552. Closer coupling for feeding drive circuit. Q115. Inductance 700 microhenries, at 465 Kc/s. Band width of each of the above transformers is 7-20 Kc/s at 2-20 Dbs. Size: -3 1/2 in. high, 1 1/2 in. square. Supplied with fixing screws and nuts.

LASKY'S PRICE 6/6 each. 12/6 per pair.

ALL YOUR RADIO VALVE REQUIREMENTS AT LASKY'S

CARBON POT/METERS

All with long spindle, 1, 1, 1 and 2 meg. LASKY'S PRICE, less switch 3/3 each. With switch 4/3 each. All post extra.

SMOOTHING CHOKES

Table with 2 columns: Type and Price. Includes items like 20 M/a. 40 H., 40 M/a. 8 H., 40 M/a. 10 H., 75 M/a. 150 H., etc.

SPEAKER FRET

Metal, one side finished gold, other side silver. Size: 12in. x 12in. LASKY'S PRICE 4/3 per piece. Post 6d. extra.

RADAR INDICATOR UNITS TYPE 162C

BRAND NEW IN MAKER'S ORIGINAL WOOD CASE. Contains 2 cathode ray tubes, one 6in. VCR517 and one 3in. VCR139. Also the following valves: three 8P61, one 6J5, three EA50, one D1. Dozens of components, coils, resistance, condensers, seven pot. meters, etc. Enclosed in metal case, size 12in. x 9in. x 19in. Weight 40 lb.

LASKY'S PRICE 79/6 Carriage 7/6 extra.

METAL RECTIFIERS

Type RML. 125 volts at 60 m.a. Price, 3/11. Post 4d. Type RME. 125 volts at 100 m/a. Price, 4/3. Post 4d. Any number can be used together, either in series or parallel.

P.M. LOUDSPEAKERS

New and unused. First quality. All less o/trans. 8in. 12/11 8in. 25/6 6in. 13/6 12in. 75/-

Postage extra on each speaker.

ALL THE BEST MAKES AT THE BEST PRICES.

EX-A.M. RECEIVERS

TYPE R1481

IN ORIGINAL WOOD CASES. Frequency coverage: 66-86 Mc/s. Description: Contains 11 valves: 1 VR65, 1 VR66, 4 VR25, 2 VR64, 1 6J5, 1 VR70, 1 VR57. Large tuning scale with slow motion drive, 0.5 m/a. tuning meter, R.F. and L.F. gain controls, jack sockets for line and 'phone. Totally enclosed in metal case, grey enameled, with plated handles. Size 18in. x 10in. x 11in. Weight packed, 54lb. Supplied complete with circuit and calibration chart. Soiled condition LASKY'S PRICE 69/6 each. Carriage 10/- ex.

RECEIVER UNITS TYPE 25

The receiver section of the TR1196 equipment. Easily converted to an all-wave receiver 6 valve superhet. Valve line up: two EF36, two EF39, one EK32, one EB033. Full details and circuits supplied free with each receiver. Slightly soiled but unused. LASKY'S PRICE 35/- Carriage 3/6 extra. The Receiver 25, less valves. LASKY'S PRICE 8/6 Carriage 3/6 extra.

ANTENNA RELAY UNITS

TYPE CBV/29125

BRAND NEW AND UNUSED. IN ORIGINAL CARTONS American Air Corps equipment. Contains an 0.5 m/a. moving coil meter, also relay, insulators, 0.75 amp. heating element, switch, etc. A 50 pf. vacuum condenser 5 kv. working. Fitted in black metal case, crackle finished, size 4 1/2 in. x 5 in. x 3 1/2 in.

LASKY'S PRICE 12/6 Postage 1/6 extra.

CONDENSER CORNER

Table with 2 columns: Type and Price. Includes items like 8 mfd. 500 v.v., 8 mfd. 450 v.v., 8 x 8 mfd. 500 v.v., etc.

EPICYCLIC DRIVES

For 1/2 in. spindle. Standard reduction. LASKY'S PRICE 1/6 each. Post 4d. extra.

A GENUINE MINIATURE 2-GANG TUNING CONDENSER

.0005 mfd. Size: 1 1/2 in. deep, 1 1/2 in. high, 1 1/2 in. wide. 1/2 in. spindle. With fixing feet. LASKY'S PRICE 6/6 each. Post 6d. extra.

COIL PACK SCOOP

No. 1. 3 Wavebands. 12-35 metres, 35-100 metres; 200-550 m/cycles. 1/2 in. spindle, 1 1/2 in. long wavechange switch. Completely assembled and wired. Size: 4in. x 4in. x 3in. BRAND NEW. LASKY'S PRICE 19/11 Postage 1/- extra. Circuit available price 1/-.

No. 2. Midget Coil Pack. 3 wavebands. Standard long, medium and short. 1/2 in. spindle, 2in. long wavechange switch. Completely assembled and wired. Size: 3 1/2 in. x 1 1/2 in. x 2 1/2 in. BRAND NEW. LASKY'S PRICE 27/6 Postage 1/- extra. Circuit available, price 1/-.

ALL OTHER TYPES AND MAKES OF COIL PACKS AVAILABLE

Osborn, Weymouth, Wearite, etc., etc.

BRAND NEW RADAR UNITS

Supplied in Wood Transit Case. Containing 23 brand new valves: 15 EF50; 2 VR65; 3 EB34; 1 VR55; 1 VR58; 1 EA50. Also a removable 45 Mc/s. I.F. Strip (Receiving Unit Type 153). Hundreds of components Resistances, Condensers, 12 Pot/Meters, Relays, Ceramic and Amphenol valve holders, etc. Totally enclosed in metal case, black finish. Overall dimensions 7 1/2 x 13 x 2 1/2 in.

LASKY'S PRICE £5/19/6 Carriage 7/6 extra.

TYPE J/RA/1. 30 WATTS HEAVY DUTY AMPLIFIER

Rack mounting, grey crackle finished. Uses KTZ63 and L63, feeding 2 KT66s in push-pull. Rectifier type U52. Meter and switch for checking all current readings. Panel light, bass brilliance and gain controls. Size: 19in. x 12in. x 12in. on a chassis 4 1/2 in. high.

LASKY'S PRICE £13/19/6 Carriage and packing 25/- extra.

J/RA/2. 10-12 WATTS CHASSIS AMPLIFIER

Uses an L63 feeding 2 KT66s in push-pull. Rectifier type U50. Size: 6in. x 17in. on 2in. chassis.

LASKY'S PRICE £7/19/6 Carriage and packing 10/- extra.

Send 3d. stamp for further details of J/RA/1 and J/RA/2 Amplifiers.

OUTPUT TRANSFORMERS

Table with 2 columns: Transformer Type and Price. Includes items like Miniature Pentode (184, 384), Midget Pentode, 40 M/a., Multi-Ratio Standard, etc.

Standard Pentode. 60m/a. Postage extra.

FILAMENT TRANSFORMERS

All primaries 230 volts 50 c.p.s.

Table with 2 columns: Transformer Type and Price. Includes items like FIL 2, 6.3 v. 1.5 a., FIL 3, 6.3 v. 3 a., etc.

MAINS TRANSFORMERS

All 200-250 volts 50 c.p.s. primary. Finest quality, fully guaranteed.

Table with 2 columns: Transformer Type and Price. Includes items like MBA/8, 350-0-350 v. 80 M/a., MBA/5, 350-0-350 v. 125 M/a., etc.

AUTO TRANSFORMER. TYPE AT/3

0.10-120-200-230-250 volts. 100 watts. LASKY'S PRICE 19/6 Postage 1/6.

ANTENNA ROD SECTIONS

Each section is steel heavily copper plated. 12in. long and 1/2 in. in diameter. Any number of sections can be fitted together. LASKY'S PRICE 2/6 per doz.; 8/- for 3 doz.; 11/- per half gross; 20/- per gross. Post free.



DUAL WAVE COILS

M. & L. T.R.F. AE. and HF.

LASKY'S PRICE 5/11 Per pair. Post 6d. extra.

EX-A.M. COMMUNICATION RECEIVER TYPE R1155

BRAND NEW IN WOOD TRANSIT CASE. Aerial tested before despatch. Supplied complete with 10 valves. Circuit: B.F.O., A.V.C., R.F. Amp., two I.F. stages, magic eye, etc. 5 frequency ranges: 1.8-7.5 Mc/s.; 7.5-3.0 Mc/s.; 1.300-600 kc/s.; 600-200 kc/s.; 200-75 kc/s.

LASKY'S PRICE £12/10/-

Carriage (in wood case) 7/6 extra. Full modification data and circuit details supplied.

CRYSTAL DIODES

Wire ends Supplied with circuit

LASKY'S PRICE 3/11 each. Post 3d. extra.

VIBRATOR PACKS

For use with the P.C.R. Philips Communications Receiver. 12-volt input. Supplied complete with vibrator and metal rectifiers, etc.

LASKY'S PRICE 39/6 Carriage 5/- extra.

TABLE MICROPHONE STAND

Two sections, chrome plated. Crackle finished base.

LASKY'S PRICE 17/6 Post. packing 2/6 extra.

LASKY'S OWN TEST PRODS

Made for safety.

Fused test prods. Fully insulated pencil type with retractable point. Contacts only made when desired by pressing top. Each prod. contains a cartridge type fuse and spring.

LASKY'S PRICE 4/11 per pair (one red, one black). Post 6d. extra.

TOGGLE SWITCHES

Single pole, double throw. Ex-Govt., brand new. Black plastic finish.

LASKY'S PRICE 1/- each. 10/- Per doz. Post extra.

CATHODE RAY TUBES TYPE 3BP1

American. Fitted in adjustable viewing tube, with green calibrated perspex filter plate, mu-metal shield, base and connecting cable. BRAND NEW. Black crackle finish.

LASKY'S PRICE 29/6 Carriage 3/6 extra.

CAR BATTERIES

By DELCO-REMY. Ex-American Army. Absolutely perfect, brand new and unused, in maker's original packing. No. 1. 6-volt 140 A.H. approx. Size: 7in. deep, 13in. wide, 8 1/2 in. high. In genuine hard rubber case.

LASKY'S PRICE £4/19/6 Carriage 7/6 extra.

No. 2. 6-volt 90 A.H. Size: 9in. wide, 7in. deep, 8in. high. In genuine hard rubber case.

LASKY'S PRICE 87/6 Carriage 7/6 extra.

MAINS DROPPERS

All types from 2/6 each. 12 assorted, 25/- Post free.

MIDGET YAXLEY SWITCHES

4 pole 2 way. Long spindle.

LASKY'S PRICE 2/11 Postage 3d. extra.

LARGE STOCKS OF RESISTANCES ALWAYS AVAILABLE


All values. Prices: -1/10th and 1/8th watt, 7d. each; 1/4 and 1/2 watt, 4d. each; 1 watt, 8d. each. Postage extra.

MONEY BACK GUARANTEE

Everything ordered from Lasky's is guaranteed to be as advertised. If you are not more than satisfied return goods for cash refund.

GARLAND BROS. LTD

LANE PRECISION BUILT TAPE TABLE.

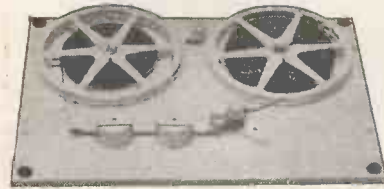


High fidelity high impedance record-playback and erase heads in mumetal shields. Heavy balanced flywheel giving freedom from "wow" and "flutter." Fast rewind. Heads are half-track, giving one hour's playing time with 1,200-foot reel of tape. £16/10/-, plus carriage, etc., 10/-.

DEMONSTRATIONS at Deptford and Lewisham.

TAPE DECK AMPLIFIER UE6. A six-valve record-playback amplifier suitable for use with high impedance heads. Features include variable bass and treble lift, recording level indicator and built-in oscillator supplying h.f. bias and erase sufficient for the highest coercivity tapes. Supplied in kit form, with punched chassis, all valves, components, circuits and full instructions. £10/10/-, plus carriage 5/-.

TAPE DECK AMPLIFIER HNES, a five-valve record-playback amplifier suitable for use with high impedance heads. With built-in oscillator supplying h.f. bias and erase. Supplied in kit form, with punched chassis, all valves and components, circuits and full instructions. £7/10/-, plus 5/- carriage.

AMPLIFIER ACIII.

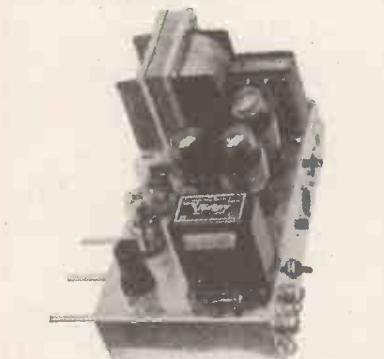

7 valves (including rectifier). 10 watts push-pull output to 3 ohm or 15 ohm speaker. Supply available for tuner unit, etc. High and low gain inputs. Separate Bass and Treble controls. Negative Feedback. Varley mains and output transformers. Complete kit, with circuits and instructions, including circuit of suitable local-station quality tuner. £8/19/6, plus carriage 5/-.

MODIFICATION KIT UE2. Enabling the use of Amplifier ACIII as a high-quality tape record-playback amplifier, for use with high impedance heads. Incorporating pre-amplifier, oscillator supplying h.f. bias and erase sufficient for the highest coercivity tapes and recording level indicator. In kit form, with all valves, components, punched chassis circuits and full instructions. £4/4/-, plus 5/- carriage.

MAGNETIC RECORDING TAPE. Emitape, Grade A, 600ft., 21/-; 1,200ft., 35/- Scotch Boy (Durex), 1,200ft., 35/-.

SPARE TAPE REELS. 7in. (1,200ft.) plastic, 4/- each.

MAGNETIC RECORDING HEADS. High impedance half track heads, in mumetal shields. Record-playback, £2/10/-.

LUSTRAPHONE MOVING COIL MICROPHONES. Type C51. Response substantially flat to 8 kc/s. Impedance 20 ohms. Fitted with switch, £5 each. Type C51/Z. As above, but impedance 200,000 ohms, £5/12/6 each.

AMPLIFIER II/66. For those who desire good quality reproduction at low cost. Valve line-up is 6J5-6J5-KT66-5Z4. Output 5 watts. Volume tone and variable feedback controls. High grade output transformer. Chassis completely isolated from mains. Complete kit, including punched chassis, all valves and components, with circuits and instructions, £5/2/6. Amplifier wired and tested, £6/2/6.

PLUGS AND SOCKETS. Pye angle, 1/-; Pye straight, 1/3; B. & L. 5-pin, 1/6; B. & L. 7-pin, 1/9; B. & L. 10-pin, 2/3; Jones 6-way, 1/6; Jones 8-way, 1/9; E.H.T. Single, 1/-; the above prices include plug and socket in all cases. Pye T-pieces, 9d. Pye connectors, 9d. Pye Angle P. & S. to fit 3/16 in. cable, 1/3 complete.

MUIRHEAD SLOW MOTION DRIVES. As used on G-units and R.1224A. Precision-made and incorporating a slow-motion drive of the order of 50 or 60 to one; ideal for tuning or test equipment, 6/6 each.

MAT RESISTORS. 300 ohm, 250 watt, 2/3 each, 21/- per doz.

ACCUMULATORS. 2 v. 10 A.H. In black moulded bakelite case, unfilled but charged, 4/9 each.

WAFFER SWITCHES, SP 10 w., 1/9; SP 11 w., 2/-; 4 p. 2 w. midget, 2/-; SP 3 w., 1/3.

TOGGLE SWITCHES. Arrow, D.P.D.T., Q.M.B., rating 250 v. 3 a., plated dolly and bush. Brand new, 3/- each; 33/- per doz. Ditto S.P.D.T., 2/3 each, 24/- per dozen. Black bakelite D.P.D.T., 250 v. 3 a., 2/6 each, 27/- per dozen. Ditto S.P.D.T., 1/9 each, 18/- per dozen.

BRIGHT ZINC PLATED CHASSIS. Two sided with fixing flanges, 13 1/2 x 6 x 2 1/2 in., drilled for five-valve superhet, 2/9 each. Two-sided, 11 x 5 1/2 x 2 in., drilled with seven octal (1 1/2 in.) holes, 2/9 each.

TINPLATE CHASSIS. Two-sided, 10 1/2 x 4 1/2 x 2 in., undrilled, 2/9 each.

SPECIAL PURPOSE VALVES. VR116, 5/-; CV73, 4/-; 9003 5/-; 954, 3/-; VU1141, 6/6; CV66, 6/6; VR136 (EF54), 7/6; VU111, 5/-; VU133, 3/6; CV54, 3/6; E1148, 3/6; VU33, 3/6; CV265, 3/6; VU134, 9/6; VR65A, 4/6; MS/Pen, 4/6.

SPECIAL OFFER. EL50 6.3 v. 8 watt output pentode, 5/- each; 55/- per doz. Side contact valveholders to suit, 9d. each.

A REMINDER. In addition to the items listed here, may we mention that we also carry large and comprehensive stocks of radio, television and electronic equipment and components by Acos, Avo, Belling & Lee, Bulgin, B.S.R., Collaro, Colvern, Connoisseur, Decca, Ediswan, Erie, Morganite, Osrom, Partridge, Radiospares, S.T.C., Taylor, T.C.C., Varley, Vortexion, Westinghouse, Whiteley, Wright & Weaire and other famous manufacturers—and, of course, a wide range of B.V.A. and Tungram valves and cathode ray tubes at current prices.

PLESSEY 3-SPEED AUTO-CHANGERS.



Plays eight 78 R.P.M., ten 33 1/3 R.P.M. or 45 R.P.M. records. Replaceable double-pointed sapphire stylus, £23/13/-.

DECCA THREE-SPEED GRAM MOTORS. For 33 1/3, 45 and 78 r.p.m. Instant single-lever speed selection. For A.C. only, 100-250 v. 50 cycle operation. Price (incl. P.T.), £7/3/4.

DECCA TURNOVER PICKUP. A high fidelity crystal pickup with turnover head (two sapphires) for use on the above or other multi-speed motors. Price (incl. P.T.), £3/19/4.

MAINS TRANSFORMERS. MT1, 250-0-250 v. 80 m/a., 0-4-6.3 v. 4 a., 0-4-5 v. 2 a., 18/6 each; MT2, 350-0-350 v. 80 m/a., 0-4-6.3 v. 4 a., 0-4-5 v. 2 a., 18/6 each; MT3, 0-30 v. tapped to give 13 different voltage outputs at 2 a., 18/6 each; 300-0-300 v. 120 m/a., 6.3 v. 3 a., 5 v. 2 a., 22/6 each. All above transformers tapped 200-220-240 v. 100 w auto., 0-10-120-200-230-250 v., 18/6 each.

I.F. TRANSFORMERS. 465 kc. standard size, 3 1/2 in. x 1 1/2 in. x 1 1/2 in., 12/6 per pair. Small size, 2 1/2 in. x 1 1/2 in. x 1 in., 13/6 per pair. Made for us by a leading manufacturer.

WIRELESS WORLD DIARY 1952. Containing 80 pages of invaluable technical data. Get your copy now, and avoid disappointment. With leather covers, 6/11d. each, with rexine covers, 4/3 1/2d. each. (We also carry a full range of W/W publications and reprints.)

TRF KITS.



Complete with cabinet in ivory or brown bakelite, three valves and metal-rectifier, chassis, loud-speaker and all components and accessories. For medium and long waves. A.C. only, 200-250 v. With circuits and instructions. Limited number only. £5/15/-.

CONDENSERS (pFs). 2, 4, 10, 15, 20, 30, 50, 75, 100, 150, 200, 6d. each, 5/6 doz. 220, 300, 330, 500, 1,000, 2,000, 4,000, 4,500, 4,700, 9d. each, 7/6 doz.

HIGH-CAPACITY PRECISION MICA CONDENSERS. By leading manufacturers. Accuracy plus or minus 0.5 (point five) per cent of stated value. Pure mica and copper foil.

(c) 0.035020µF, 1/6; (d) 0.040710µF, 1/6; (f) 0.065350µF, 1/6; (ff) 0.082910µF, 1/6; (g) 0.087450µF, 1/6; (h) 0.108435µF, 1/9; (i) 0.123750µF, 1/9; (j) 0.147000µF, 1/9; (k) 0.205276µF, 2/-.

No further stocks (a), (b), (bl) or (e). Many close tolerance standard values may be made up by parallel or other combinations of above, e.g.: 4j + 2k = 1µF; 2k + g = 0.5µF; c + f = 0.1µF (A table of over 150 series and parallel combinations of these condensers, invaluable on calculating filter networks, etc., is available on receipt of 2d. stamp.)

CLOSE TOLERANCE SILVER MICA CONDENSERS. 10,000pF (0.01µF) plus or minus 2% ideal for service bridges, etc., 1/- each, 9/- per doz., £4/10/- per gross. 1,000pF (0.001µF), ± 1%, 1/3 each. 100pF (0.0001µF) ± 1%, 9d. each.

HIGH STABILITY RESISTORS. 1% 1/2 w.: 1.5k, 8k, 9d. each; 1% 1/2 w.: 10k, 25k, 50k, 100k, 500k, 1/- each; 1% 1 w.: 1m., 1/3 each; 2% 1/2 w.: 4k, 10k, 13k, 45k, 55k, 250k, 1m., 9d. each; 2% 1 w.: 120k, 1m., 1/- each; 5% 1/2 w.: 3.9k, 10k, 39k, 75k, 130k, 600k, 8d. each; 5% 1 w.: 5k, 8k, 510k, 910k, 1.8m, 2m, 9d. each; 5% 2 w.: 10m, 11m, 12m, 14m, 50m, 100m, 1/3 each. We have at press date large stocks of many of these values.

SMALL-SIZE PAPER CONDENSERS. 2µF 100 v. wkg., dimensions 1 1/2 in. x 1 1/2 in. x 1/2 in. Ideal for cross-over networks, etc., 4/6 per doz., 45/- per gross, £14/10/- per thousand.

PAPER CONDENSERS. 1µF 500 v. wkg., 2 1/2 in. x 2 in. x 1/2 in. Inverted mounting, 1/- each, 9/- per doz., £3/12/- per gross. 1µF 600 v. wkg., 2 1/2 in. x 1 1/2 in. x 1 in. Upright mounting, 1/6 each, 15/- per doz., £7 per gross.

HIGH VOLTAGE MICA CONDENSERS. 0.1µF 1,500 v. wkg., by a leading manufacturer. Bakelite cased upright mounting, 3in. x 2 1/2 in. x 1 1/2 in. overall. Price 2/- each, 21/- per doz.

EXTENSION SPEAKERS.



In tasteful brown bakelite louvered cabinet and incorporating an Flac 5in. P.M. speaker (commended editorial columns this journal), and volume control, £11/7/6.

| EX-GOVT. POTENTIOMETERS | | | | |
|-------------------------|----------------------|----------|----------------|-------|
| Value | Track | Watt-age | Spindle length | Price |
| 50Ω | W/W | 5 | Preset | 2/6 |
| 100Ω | W/W | 1 | Preset | 1/9 |
| 500Ω | W/W | 1 | 5/16in. | 1/9 |
| 1kΩ | W/W | 3 | 1/2in. | 2/6 |
| 1kΩ | W/W | 5 | 1/2in. | 2/6 |
| 2kΩ | W/W | 3 | Preset | 1/9 |
| 2kΩ | W/W | 6 | " | 2/6 |
| 2kΩ | W/W | 5 | 1/2in. | 3/- |
| 3kΩ | W/W | 6 | Preset | 2/6 |
| 3kΩ | Carbon Trop. | 2 | 1/2in. | 1/9 |
| 5kΩ | W/W | 1 | Preset | 1/9 |
| 5kΩ | W/W | 2 | 1/2in. | 2/6 |
| 5kΩ | W/W | 5 | 1/2in. | 3/- |
| 5kΩ | W/W | 5 | 1/2in. | 2/6 |
| 8kΩ | W/W | 5 | 1/2in. | 2/6 |
| 10kΩ | W/W | 4 | 1/2in. | 2/6 |
| 10kΩ | Carbon Trop. | 2 | 1/2in. | 2/- |
| 10kΩ | Carbon | 1 | Preset | 1/3 |
| 20kΩ | W/W | 3 | Preset | 2/- |
| 20kΩ | W/W | 5 | 1/2in. | 3/- |
| 20kΩ | Carbon Trop. | 2 | 1/2in. | 1/9 |
| 50kΩ | W/W (earthed slider) | 3 | 1/2in. | 2/6 |
| 50kΩ | Carbon Mini. | 1/2 | 1/2in. | 1/6 |
| 100kΩ | Carbon Mini. | 1 | 1/2in. | 1/6 |
| 200kΩ | Carbon | 1 | 1/2in. | 1/9 |
| 500kΩ | Carbon Trop. | 2 | 1/2in. | 1/6 |
| 500kΩ | Carbon Trop. | 2 | 1/2in. | 1/9 |
| 500kΩ | Carbon Mini. | 1 | 1/2in. | 1/6 |
| 1MΩ | Carbon | 1 | 1/2in. | 2/- |

All new and unused. Spindle diameter 2in. in all cases. Quantity prices on application.

SLEEVING. 2 mm. oiled silk, etc., 3/6 per 24 nominal yard lengths, assorted colours, 33/- per two gross disto.

METERS. All 2in. 0-4 a. D.C., 9/6; 0-8 a. D.C., 9/6; 0-20 a. D.C., 7/6; 0-50 v. D.C., 7/6; 0-300 v. D.C., 8/6; 0-500 mA. TH/C, 7/6.

SWITCHBOARD VOLTMETERS. First grade M.I. Meters in robust metal case. 0-5 v. A.C. or D.C. (separate calibration for A.C.). Scale length approx. 6 1/2 in. Few only, 37/6 each.

PAXOLIN COIL FORMERS. 1 1/2 in. long by 5/16 in. diameter. Also suitable for metal rectifier sleeves. Approx. 50,000 available. £1 per thousand.

AERIAL RODS. Copper plated steel. Fit into each other to make up any length aerial. Per doz., 2/-; per gross, 18/-; per thousand, £4/10/-.

METAL CUTTING SHEARS. A robust tool, one-inch blades, will cut up to 16 s.w.g. aluminium. Per pair, 2/-; per doz. pairs, 21/-; per gross pairs, £11.

GERMANIUM DIODES. Latest sub-miniature wire-ended glass-enclosed type, by a leading manufacturer. Minimum life 10,000 hours, low shunt capacity, no heater supply required. Special offer at 5/6 each, or £3 per dozen.

LAMINATION AND COPPER SHORT-AGE. Small manufacturers and others with winding facilities might profitably get in touch with us, as we have a quantity of 500-2,000 cycle transformers of all types, ideal as cores for rewind.

ROTARY TRANSFORMERS. Input 14 v. D.C., output 600 v. 140 mA. D.C., 22/6 each. Input 24 v. D.C., output 300 v. 150 mA. and 150 v. 30 mA. D.C., 17/6 each.

BLOWER MOTORS. American make. Nominal input 27 v. D.C. Shunt wound, with field and armature windings brought out separately, so can be put in series for higher voltages. Will also work on A.C., 12/6 each. Tested ex-equipment.

CARBON HAND MICROPHONES. Type No. 3. With G.P.O. type carbon insert, press switch in handle, lead and jack plug. New and unused, 5/- each.

L.F. CHOKES. 8H 120 mA American made, 13/9 each. American potted type, 1.28H 130 mA., tested ex-equipment, 3/6 each.

PULLIN MOTORS. Type A/3R. For 24 v D.C. 3 1/2 in. x 2 1/2 in., 8/6 each.

TRIMMERS. Miniature ceramic air-spaced 3-30pF, 6d. each. Philips concentric type 3-30pF, 8d. each. Standard size ceramic air-spaced trimmers, 30pF, 1/-; 50pF, 1/-; 75pF, 1/3; ceramic compression type trimmers, 50pF, 6d.; 100 + 100pF, 1/-; 200 + 500pF, 1/3; 1,000pF, 9d.

T.R.F. COILS. For long and medium waves. With reaction winding, 6/- per pair. Without reaction winding, 6/- per pair.

METAL RECTIFIERS. Type RM2, 125 v., at 100 mA. Two in series required for mains voltage. Price 4/- each; 6 v. 1 a. half-wave (or full wave with C.T. transformer), price 5/- each; 12 v. 1 a. bridge, 8/6 each.

ROTARY SELECTOR SWITCHES. Type 10D/373-374. Sometimes described as impulse relays. 24 v. Solenoid. 52 pulses for one rev. Four position. Single stroke or continuous operation. Platinum contacts. 3/- each, or 15/- per half-dozen.

STABILVOLTS: Type NSI. Voltage stabiliser and divider. Operating voltages 280 v., 210 v., 140 v., 70 v.; max. electrode current, 80 mA. Each 10/-.

STABILVOLT TYPE VS68. Similar to STV280/40. Operating voltages 280, 210, 140, 70 v. Max. electrode current 60 mA. 7/6 each, or 78/- per doz.

BAKELITE-CASED IGNITION SWITCHES: type 5C/547. Will switch substantial currents at low voltage; many useful applications. 1/3 each, 13/- per dozen, 66/10/- per gross.

MINIATURE TANDEM POTS: 30 k, plus 1.5 k, with S.P. switch. Spindle diameter 1/2 in., spindle length 1/2 in. from end of bush. 2/6 each.

VALVE HOLDERS: Ceramic: UX5 (807, etc.), 1/- each, 10/- doz.; UX7 medium (1625, RK34, etc.), 1/- each, 10/- doz.; B9G (EF50, etc.), 9d. each, 7/6 doz.; Amphenol: Int. lctal, 9d. each, 7/6 doz.; Br. 7p, 9d. each, 7/6 doz.; Br. 5p, 9d. each, 7/6 doz.; UX7 med., 9d. each, 7/6 doz.; UX5, 9d. each, 7/6 doz. Paxolin: Br. 5, Br. 7, UX4, UX5, UX6, UX7, 6d. each.

AMPLION TESTMETER: 10 Ranges A.C. and D.C. Up to 500 v. A.C. and D.C. Resistance up to 200,000 ohms, 1,800 ohms per volt A.C. and D.C. Price £5.

P.O. TYPE JACK SOCKETS: 2 way shorting type Ref. No. 10H/1739, special offer at 1/- each, 9/- per doz.

FLEX CONNECTORS: Ref. No.'s 5c/455 plug, 5c/591 socket. Overall dimensions when joined 2 1/2 in. x 1/2 in. For joining two lengths of flex or cable. Price complete (plug and socket) 1/3 each, 12/- per doz., £6 per gross.

CATHODE RAY TUBES. SCPI, Electrostatic intensifier-type C.R.T., diameter 5in. max. second anode voltage 2 kv., max. intensifier anode voltage 4 kv., medium persistence screen. Brand new in original crate or carton, 22/6 each.

OIL AND RADIATOR TEMPERATURE INDICATORS. By leading aircraft instrument makers. These are sensitive moving coil instruments, with centre-tapped moving coil. Each 3/9.

TELEVISION MAGNIFYING LENS. 9in. clear, 55/-; 9in. filter, 60/-; 12in. clear, 75/-; 12in. filter, 80/- Carriage and packing 5/- each, all types.


TECHNICAL BOOKS: Television Receiving Equipment, by Cocking, 18/6. Radio Data Charts, abacs for receiver design, 8/- Magnetic Tape Recorder, design and construction, by Chessman, 3/9. Cathode Ray Tube Traces, by Moss, 11/-.

Electrophysiological Technique, by Dickinson, 13/- Radio Charts No. 1, a modern superhet for A.C./D.C. mains, 2/9. Radio Charts No. 2, a high fidelity push-pull amplifier for A.C., 2/9. Audio Handbook No. 1, amplifiers, test and servicing, 3/9. The Williams Amplifier, 3/9. Brimar Valve Manual, 5/3. Ediswan—Mazda Valve Manual, 1/3. Mullard Valve Manual, 5/3. Marconi Osram Valve Manual, 5/3. Television Explained, by Miller, 5/6. Television Servicing Manual, 4/9.

A Comprehensive Radio Valve Guide, by May, 5/3. W/TV Radio Valve Data, 3/9. The De-Luxe Home Built Televisor and Radiogram, by Flack, 6/9. Radio Circuits, step by step survey of superhet receivers, by Miller, 5/6. W/W Guide to Broadcasting Stations, 2/3. Above prices include postage in all cases.

CARBON RESISTORS: Large and comprehensive stocks at following prices: 1/4 w., 4d.; 1/2 w., 5d.; 1 w., 6d.; 2 w., 9d.; 4 w., 1/- each. Among the values available at press date are the following: 1/4 w.: 10, 20, 22, 33, 39, 43, 51, 56, 68, 82, 100, 150, 180, 220, 270, 300, 330, 390, 430, 450, 470, 560, 680, 700, 1 k, 1.5 k, 2.2 k, 2.4 k, 2.7 k, 3.2 k, 3.3 k, 3.9 k, 4.4 k, 4.7 k, 5.6 k, 6.2 k, 6.8 k, 8 k, 10 k, 12 k, 15 k, 18 k, 20 k, 22 k, 25 k, 24 k, 27 k, 30 k, 33 k, 36 k, 39 k, 40 k, 47 k, 50 k, 56 k, 60 k, 62 k, 68 k, 100 k, 220 k, 270 k, 330 k, 350 k, 390 k, 470 k, 500 k, 560 k, 600 k, 680 k, 750 k, 820 k, 1 m, 1.5 m, 2 m, 2.2 m, 3.3 m, 4.7 m, 6 m; 1/2 w.: 10, 12, 13, 20, 22, 27, 30, 43, 68, 100, 120, 130, 150, 270, 300, 390, 400, 470, 500, 560, 680, 750, 1 k, 1.5 k, 2 k, 2.2 k, 2.4 k, 3.2 k, 3.9 k, 4.7 k, 5.1 k, 6.2 k, 7.5 k, 8.2 k, 10 k, 12 k, 13 k, 15 k, 16 k, 18 k, 20 k, 25 k, 39 k, 40 k, 50 k, 60 k, 100 k, 350 k, 400 k, 470 k, 500 k, 560 k, 600 k, 680 k, 820 k, 1 m, 1.5 m, 2 m, 2.2 m, 2.7 m, 4.7 m; 1 w.: 20, 27, 33, 50, 56, 68, 82, 120, 240, 330, 470, 750, 820, 1 k, 1.2 k, 1.5 k, 1.8 k, 2.2 k, 2.4 k, 3 k, 3.9 k, 4.7 k, 6.8 k, 8.2 k, 10 k, 18 k, 20 k, 24 k, 30 k, 33 k, 50 k, 68 k, 70 k, 80 k, 100 k, 330 k, 470 k, 680 k, 750 k, 1 m, 1.2 m, 1.8 m, 3.3 m; 2 w.: 47, 220, 250, 270, 470, 600, 680, 1 k, 1.5 k, 3 k, 3.3 k, 4.3 k, 4.7 k, 6 k, 6.8 k, 8.2 k, 10 k, 18 k, 22 k, 27 k, 30 k, 47 k, 50 k, 68 k, 680 k; 4 w.: 2.7 k, 20 k, 40 k, 56 k, 68 k, 240 k, 470 k.

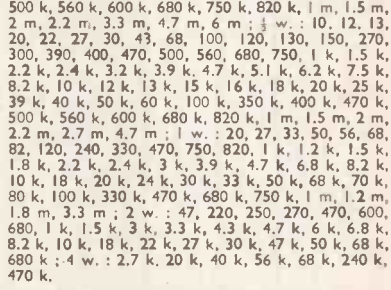JUNERO MULTI-POSE TOOL WITH XACTO SLIDE GAUGE.



Some months ago we offered you a free supply of strip and rod to enable you to try the above, which is priced at £1/7/6; we also offered to refund the cost if after one week's trial you did not think it worth the price. We are pleased to be able to state that most one of the many purchasers asked for a refund. We now repeat the offer. Among the other Junero items, of which we carry a complete range, are the Engraving Tool, for A.C. 200-240 v., for engraving on metals, plastics, etc., at 12/6; and the Punching and Rivetting Jig, at 7/6.

*We wish our many friends
at home and overseas a Happy
Xmas and a Prosperous and
Peaceful New Year*

S.W. TUNING CONDENSERS. 50p F max., 3-hole fixing, spindle diam. 1/2 in., spindle length 1 1/2 in., 1/6 each. 160p F (0.00016μF) max., upright mtg., with 4 fixing feet, spindle diam. 1/2 in., spindle length 1 1/2 in., 2/3 each.

TWO-GANG CONDENSERS. .0005μF, with fixing feet. Size 2 1/2 in. x 2 1/2 in. x 1 1/2 in. Spindle diameter 1/2 in., spindle length 1 1/2 in., 7/9 each. Midget two-gang condensers .0005μF with trimmers. Size 1 1/2 in. x 1 1/2 in. x 2 1/2 in. Spindle diameter 1/2 in., spindle length 1 1/2 in., 8/6 each.

HEATER TRANSFORMERS. Pri. 230 v., Sec. 6.3 v. 1.5 a., 7/6; Pri. 230 v. Sec. 12 v. 1 a., 7/6.

POTTED TRANSFORMERS. Pri 230v 50cps Sec. 0-325v 60mA. 0-6.3v 500mA. Size 3in. x 3in. x 2 1/2in., upright mounting, 12/6 each. Ex unused equipment.

ALL GOODS NEW AND UNUSED OTHERWISE STATED. GOODS SHOWN AS EX-EQUIPMENT HAVE BEEN FULLY TESTED AND ARE IN GOOD WORKING ORDER. PLEASE ADD POST OR CARRIAGE ON ALL ITEMS. KINDLY PRINT NAME AND ADDRESS. POST ORDERS TO OUR DEPTFORD ADDRESS. EARLY CLOSING THURSDAY, OPEN ALL DAY SATURDAY

GARLAND BROS. LTD
CHESHAM HOUSE, DEPTFORD 5 OBELISK PARADE, LEWISHAM,
BROADWAY, S.E.8 S.E.13
TELEPHONE: TIDEWAY 4412/3 TELEPHONE: LEE GREEN 4036

Best Buy at Britain's

CHARLES BRITAIN (RADIO) LTD.

11, UPPER SAINT MARTIN'S LANE, LONDON, W.C.2

(Three minutes from Leicester Square Tube Station up Cranbourne Street)

Telephone: TEMple Bar 0545

Shop hours 9-6 p.m. daily (9-1 p.m. Thursday).

Open all day Saturday

ERSKINE OSCILLOSCOPE TYPE 1/B. A few of these excellent little scopes as advertised previously, still available. Contained in a neat black metal case size 7½ in. x 5½ in. x 11 in., complete with tube and valves and ready for operation on 200/250 volt A.C. mains. All brand new and boxed. They should be invaluable to the service engineer, experimenter, schools, etc. As the price is only £10/10/0, plus 5/- carriage and packing. Full details available on receipt of 5 A.E.

COMMUNICATIONS RECEIVER R.1155. A first rate superhet. communications receiver capable of giving good quality reproduction of local stations as well as being ideal for reception of that elusive DX short wave station. Full circuit and operational details as well as conversion to A.C. mains operation are contained in the revised and enlarged "Wireless World" leaflet which is supplied with each set or available separately at 1/3, post paid.

The receivers are in brand new condition and perfect working order and are moderately priced at £11/19/6, carriage and packing in original transit cases 10/6. Any set gladly demonstrated to callers.

R1155 POWER PACK AND OUTPUT STAGE. Enables this receiver to be operated direct from A.C. mains. Just plug in and connect low impedance speaker. (Note—speaker not supplied), £3/19/6, carriage paid. This unit is manufactured by ourselves from new components and valves and assembled in a neat black A.M. case, size 8½ in. x 6½ in. x 4 in. All the necessary leads and plugs are supplied and included in the price.

BAKELITE EXTENSION SPEAKER. Cream cabinet, size 6½ in. x 6½ in. x 3 in. Containing a 5 in. Rola speaker, 2/3 ohms. Brand new and boxed, 22/6. For callers only.

DE LUXE MODEL EXTENSION SPEAKER. Walnut cabinet containing a 6 in. Rola speaker and fitted with volume control. Size 12 in. x 10½ in. x 6 in. Price only 35/-, plus 2/6 carriage and packing.

MAINS TRANSFORMERS. Three types, all standard primaries. Universal mounting. Size 12 in. x 10½ in. x 6 in. Price only 35/-, plus 2/6 carriage and packing.

SPECIAL OFFER. Manufacturers surplus transformers—standard tapped primary. 375-0-375 v. 200 m.a., 6.3 v. 8 a., 5 v. 3 a., 4 v. 2 a., 4 v. 2 a. Size 4½ in. x 4½ in. x 5 in. Semi-shrouded drop-through type. A bargain offer at 39/6, plus 1/6 post and packing.

FILAMENT TRANSFORMERS. 230 volts 50 cycles primary. Secondary 6.3 v. 1.5 amps, price 7/6, post paid.

MANSBRIDGE CONDENSERS. 10 mfd. 1,000 volt test. Size 3½ in. x 3 in. x 2 in. Will work at 600 v. D.C. Price 3 for 10/6, post paid. These are brand new and boxed.

TROPICALISED MANSBRIDGE CONDENSERS. 10 mfd. 1,000 volt test, 600 v. working. Similar to above, but superior finish. Price 3 for 15/-, post paid. Brand new.

ELECTROLYTIC CONDENSERS. 16 mfd. at 500 v. working, 600 v. surge. 3 for 11/6, post paid. These condensers are tall can type, single hole fixing. Minimum quantity by post is three.

MULTIPLE BLOCK CONDENSERS. Electrolytic, 8 x 16 x 4 x 4 x 6 mfd. All 450 volt working. 4/9, plus 9d. post or two for 10/-, post paid.

BLOCK CONDENSERS. Electrolytic 8 mfd. 500 v. working. Three for 9/-, post paid.

BIAS CONDENSERS. 20 mfd. 50 v. D.C. working, small can type, single hole fixing at

10/6, per dozen. 50 mfd. 25 v. single hole fixing can at 10/6 per dozen. 25 mfd. 25 v. wire end cardboard tubular, 15/- per dozen. All brand new. Minimum quantity 1 dozen.

ELECTROLYTIC CONDENSER. 16 mfd. 350 v. working, metal can type, well known make, type CE26L. Brand new at 4 for 10/6, post paid. Minimum quantity is four. 12-12 mfd. 350 v. working, CE34LF, small tubular aluminium can type at 3 for 10/6, post paid.

PORTABLE TESTING INSTRUMENT. These multimeters are perfect, brand new and contained in manufacturers original boxes. The instrument is a moving coil, volt, ohm, milliammeter, complete in an attractive carrying case with handle. The dial is calibrated for readings of 0-1.5 v., 0-3 v., 0-60 m.a. and 0-5,000 ohms. Further ranges may be added as desired. A range switch is incorporated and the basic movement is 6 m.a., 250 ohms resistance. Our price is 15/-, plus 1/6 post and packing.

SIMPSON DUAL-RANGE OHM-METER. Brand new American instruments. Incorporates 2½ in. moving coil meter, ranges 0-2000 and 0-200,000 ohms, 52/6, post paid.

CAR BATTERY. American made by Reading, 6 v. 90 AH., 7½ in. x 8½ in. x 7 in. Brand new and in original packing, 79/6, plus 5/- carriage.

BATTERY CHARGER. Contained in black crackle case size 6 in. x 7 in. x 12 in. Includes a heavy duty transformer, metal rectifier, 0-5 ammeter, on/off switch and two Sloydlock fuses. 230 volts 50 cycles input, output 4 amp. 6 or 12 volt battery. The transformer, etc., is conservatively rated and the whole unit is of sturdy construction and super quality. Made to a very stringent specification this equipment is well worth the price of £4/19/6, plus 5/- carriage and packing. In Brand New Unused condition.

with circuit diagram. Price (less dynamotor), £4/10/0, carriage paid. In brand new condition and contained in black crackle cases.

RECEIVER TYPE 21. A battery operated superhet. covering 4.2-7 mc/s. and 19-31 mc/s. Operates as a double superhet on the 10 metre band. Complete with nine valves and circuit diagram. In new condition. Only 45/-, carriage paid.

45 M/C.S. "PYE" STRIP. A ready made vision receiver for the London frequency. Use six EF50 valves and an EA50. Circuit data provided. Less valves 37/6. With all valves, 57/6, plus 1/6 post and packing.

24 VOLT EXTRACTOR FAN. For operation from 24 volt A.C./D.C., but will function from the mains when fitted with a suitable dropper resistance. Has many uses: ventilation purposes, as a hair dryer, etc. As new, only 12/6, plus 1/6 post and packing.

EX-R.A.F. U.H.F. ANTENNA. This consists of an EA50 untuned detector stage mounted on a moulded streamlined base. The copper antenna measures 22.5 cm. All connections are brought out to a 3-pin screened connector. These units are brand new and boxed. Only 5/-, post paid.

METAL RECTIFIERS. 12 v. 2 a., full-wave bridge, 12/6, plus 6d. post. Miniature H.T. rectifiers type RM2, 125 v. 100 m.a., 4/3 each, or 2 for 8/-, RM3, 125 v. 120 m.a., 5/- each, or 2 for 9/6, plus 6d. post on one or two. Selenium rectifiers, 150 v. 40 m.a., 3 for 10/-, post paid. 230 v. 60 m.a. at 2 for 9/-, post paid.

EF50 (VR91). Red American Sylvania types at 8/6 each. Brand new. British types also available at 5/- each tested.

SPECIAL PURPOSE VALVES. VT501 (TT11) 5/-, 954, 2/6. VR136 (EF54), 6/6. E1148, 2/6

VR65a (SP41), 3/-. Hundreds of others types in stock. Post 6d. for 1-4 valves

SPARE C.R.T.s. For Erskine 'Scope Type 1/B as advertised by us. G.E.C. Type E4103/4. Brand new and boxed only, 22/6 each, post paid.

Mu-metal Shield for above tube 3/6 extra. Holder for same 1/-. These two items only supplied with tube.

EX-GOVT. CHOKES. 20 H. 80 m.a. 350 ohms, 6/6. 30 H. 100 m.a., 12/6. Both types are upright mounting and very conservatively rated. 1/- each postage.

6 in. MAGNIFYING LENS. Super quality oil filled perspex. Enables you to have a large picture with the VCR97, VCR517 and SCPI, etc., tubes. Special price only 22/6 each, plus 1/6 post and packing.

DIFFERENTIAL MILLIAMMETER. Moving coil 15-0-15 m.a. Centre zero 2½ in. Bakelite case. Brand new and boxed, 10/6, post paid.


DECCA THREE-SPEED GRAM MOTORS. For 33, 45 and 78 r.p.m., A.C. only, 100-250 v. 50 cycles. Price £7/3/4.

USEFUL PUBLICATIONS. "Inexpensive Television" gives all the "gen" on 6 in. televisions and the "Easybuilt" Television gives the "gen" on 9 in. and 12 in. magnetic televisor. Both publications 2/9 each, post free.

R.C.A. WAVEMETERS. We have just a few of these which we are offering to callers only at £4/19/6. These are without valves, but complete with precision 1 mc/s crystal. The frequency range is 2.5-5 mc/s. on fundamentals, and the dial is calibrated every kilocycle.

INDICATOR UNIT CHASSIS, various types, all filled with pots, valve and tube holders, resistors and condensers, etc. For callers only at 12/6 each. A real snip.

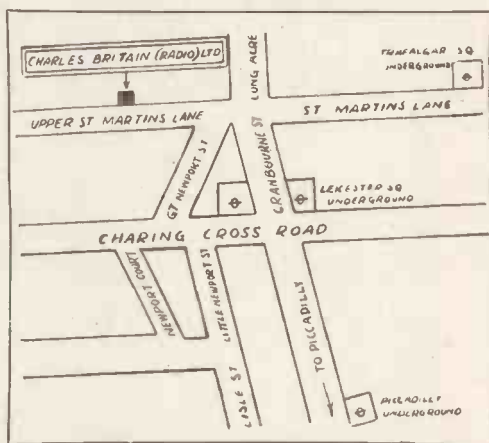TWO-VALVE T.V. PRE-AMP. CHASSIS, two valve EF50s, less valves at 7/6, plus 1/- post and packing.



NEW EXIDE ACCUMULATORS. 2 volt 15-20 AH, in black bakelite case, size 6 in. x 1½ in. square. Brand new at 4/6 each, plus 9d. post.

PHILCO CAR RADIO. 200-550 metres. For 6 volt operation. Valve line up: two of EF39, one of ECH35, one of EBC33, one of EL32, one of 6X5 and a 6 volt vibrator. Unusually powerful and selective, as an R.F. stage is incorporated. A built in 6½ in. speaker is included. Our price £10/10/0, plus 5/- carriage and packing. In perfect working order.

SHIPPING AND TOP BAND. Listeners to these bands will be pleased to hear that we can once again offer a Command Set with a frequency coverage of 1.5 to 3 mc/s. (100-200 metres). These follow the same specifications as the other types of Command Receivers and are complete

Personal Callers should note that it is impossible to convey in this advert, the enormous range of components, valves, C.R.T.'s test equipment and other gear which we have in stock. When in town pay us a visit and you will be surprised and delighted at the astonishing variety of goods we have to offer at keen competitive prices.



CHARLES BRITAIN (Radio) Ltd.
11, UPPER SAINT MARTIN'S LANE,
LONDON, W.C.2
TEMple Bar 0545

MAINS TRANSFORMERS

These transformers are all famous radio manufacturers' surplus and are fully interleaved, impregnated and guaranteed.

Primary 200-250 v. P. & P. on each 1/6 extra.
 300-0-300, 100 mA, 6 volt 3 amp, 5 volt 2 amp., 17/6.
 320-0-320, 100 mA, 6 volt 3 amp., 5 volt 2 amp., 17/6.
 320-0-320, 120 mA, 6 volt 4 amp, 5 volt 2 amp, 25/-.
 280-0-280, 120 mA, 6 v. 6 amp., 5 v. 2 amp. Less fixing clamps, 18/6.

250-0-250, 100 mA, 6 v. 3 amp., 4 v. 3 amp., 4 v. 3 amp, 17/6.

250-0-250, 60 mA, 6 v. 4 amp. (to be used on common heater chain with 6 X 5 rectifier), 13/6.

280-0-280, 80 mA, 6 v. 3 amp, 4 v. 2 amp, drop-through, 14/-.

Drop thro', 350-0-350 v. 70 mA, 6 v. 2.5 amp, 5 v. 2 amp, 14/6.

Semi-shrouded, drop-thro' or upright mounting 280-0-280 80 mA, 4 v. 6 amp, 4 v. 2 amp, 12/6.

Auto-wound H.T. 280 volts at 360 mA, 4 v. 3 amp, 2 v. 3 amp, or 6 v. 3 amp. Separate 4 v. 3 amp rectifier winding (upright or drop-through), 10/6.

350-0-350, 120 mA, 4 v. 6 amp, 4 v. 3 amp, drop-through, 21/-.

Auto-transformer, various combinations of voltages including 110 v. 70 watt, and 3/4 volts windings at 1 amp, 2 volt 1 amp, drop-through or upright mounting, 10/6.

Heater Transformer Pri. 200-250 v., 6 v. 1 1/2 amp, 6/-; 13 v. 1 1/2 amp, 6/-; 2 v. 2 1/2 amp, 5/-.

P. & P. each 9d.

ELECTROLYTIC CONDENSERS

16 + 16 mfd. 450 v. wkg., 5/6.

50 mfd. 25 wkg., 1/9.

100 mfd. 12 v. wkg., 1/3.

50 mfd. 12 v. wkg., 1/6.

25 mfd. 25 v. wkg., 1/2.

16 x 8 mfd., 450 wkg., 4/-.

8 mfd. 450 v. wkg., 2/6.

250 mfd. 12 v. wkg., 1/3.

16 mfd. 500 v., 4/-.

8 mfd. 500 v., 3/-.

8 x 8 mfd. 450 wkg., 3/6.

32 mfd. 350 wkg., 2/6.

32 + 32 mfd. small tube tag ends 200 v. wkg., 2/-.

16 + 8 mfd. 350 wkg., miniature tag end, 3/-.

P.M. SPEAKERS

with less trans. trans.

3 1/2 in. 11/6

5 in. 15/6 12/6

6 1/2 in. 14/6 11/6

8 in. 17/- 14/6

10 in. M.E. Speaker Field Coil, 1,100 ohms, speech coil 2-3 ohms, 17/6.


P. & P. on each of the above 1/- extra.

Constructor's Parcel. Comprising chassis 10 1/2 x 5 1/2 x 2 in. with speaker and valve holder cut-outs, 5 in. P.M. speaker with transformer, twin gang with trimmers, pair T.R.F. coils long and medium iron cored, four valve holders 20K volume control and wave-change switch. Post paid 21/-.

Volume Controls, by famous manufacturer. Long spindle less switch, 5 k., 50 k., 500 k., 1 meg. 2/6 each. P. & P. 3d. each.


Frame Blocking Oscillator Transformer, 4/6.

D. COHEN
 RADIO & TELEVISION COMPONENTS

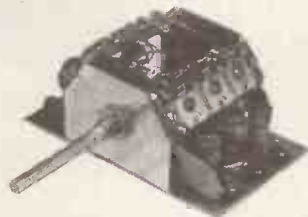

Three Wave-Band Coil Pack, iron cored coils, 16-50, 180-550, 1,000-2,000 metres. I.F. frequency 465 Kc. Size, 4 1/2 in. X 1 1/2 in. X 2 1/2 in., 24/-, post paid. Double ended perspex trimming tool given free with each pack.

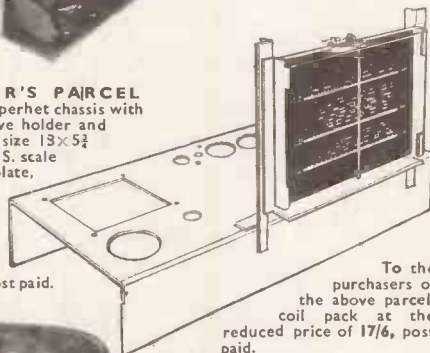CONSTRUCTOR'S PARCEL comprising 5-valve superhet chassis with transformer I.F., valve holder and transformer cut-outs, size 13 x 5 1/2 x 2 1/2 in., with L.M. & S. scale size 7 x 5 in. Back plate, two supporting brackets, drive drum pointer two speed spindle, spring, three pulleys and five international Octal valve holders, 11/6, post paid.



To the purchasers of the above parcel, coil pack at the reduced price of 17/6, post paid.



Pensold 6 volt Light Weight Soldering Iron, weight 3 1/2 ounces complete with 1 1/2 yards circular flex, 8/6. Post & pack. 1/-.

Complete with suitable heater transformer Primary 230/250 volts, 10/6. Post & pack. 1/9.

Transformer not sold separately.

P.M. Focus Unit. For any 9 in. or 12 in. tube, except Mazda 12 in., state tube, 12/6.

P.M. Focus Unit. For Mazda 12 in., 15/-.

T.V. Chassis. Size 9 1/2 x 9 1/2 x 3 1/2 in., 3/-.

Standard 465 Kc. I.F.'s. Q. 120 iron cored, 3 1/2 x 1 1/2 x 1 1/2 in., per pair, 10/6.

MAINS or BATTERY SUPERHET PORTABLE COILS. Comprising medium wave frame aerial and long wave loading coil, used as aerial coils. Midget iron cored screened L/M osc. coils, complete with circuit I.F. frequency 465 Kc., 9/6.

IRON CORED LONG, MEDIUM and SHORT SUPERHET COILS coupling winding on all bands, 13.5-50, 180-550, 1,000-2,000 metres, complete with circuit, 8/6.

METAL RECTIFIERS, 250 v. 60 mA, latest midget Selenium type, 6/6 post pd.

OUTPUT TRANSFORMERS. Standard type 5,000 ohms imp., 2 ohms speech coil, 4/9; Push-Pull 6 v. 6 matching 10 watt 2 ohms speech coil, 6/9.

42-l speech coil 2 ohm with extra feed back winding, 4/3; Miniature 42-l 2 ohm speech coil, 3/3.

SET OF 3 BROWN KNOBS marked "wave change," "tuning," and "volume," 1/6.

6-pin 6 volt synchronous vibrator 8/6

6 volt standard 4-pin vibrator 8/6

Vibrator transformer 250-0-250 80 mA. 6 volt. Pri. 8/6

EXTENSION SPEAKER CABINET

Polished in a pleasing light and dark shade. Complete with an 8" P.M. Rubber feet and back. Size 10" x 10" x 4 1/2", 22/6 post paid.

TELEVISION MASKS

White Rubber. 9 in. with glass, 10/6. White Rubber. 12 in. with glass, 15/-. 15 in. white rubber mask, soiled, 12/6, plus 1/- P. & P.

Midget Components. Twin gang 3/4 in. diameter, 2 in. long. (The dimensions of this gang are slightly deeper than a standard volume control). Pair Medium and Long iron cored T.R.F. Coils 3/4 in. long X 3/4 in. wide complete with a 4-valve all-dry circuit, tuning scale and pointer knob. All the items 10/- post paid.

All - Dry A.C. Mains Supply Unit, size 3 1/2 in. long X 2 1/2 in. wide X 1 1/2 in. deep. We can supply a complete all-dry circuit, using the above Midget Components to incorporate the above Power-Unit, 19/6, post paid with circuit.

Midget Bakelite Cabinet. 7 in. X 5 1/2 in. X 5 in. c/w 5-valve 5/4h. chassis med./long wave scale and back (takes std. twin gang condenser and 3 1/2-in. speaker). 15/- P. & P. 1/6.

Line and Frame Coil Assembly. Frame coils wound but not fitted (full instructions supplied). High impedance frame; low impedance line, matching 5-1, 8/6.

Wave Change Switches. 6-pole 3-way, 2/-; 4-pole 3-way, 1/9; 5-pole 2-way midget, 1/9; 5-pole 3-way, 1/9; 3-pole 3-way, 1/9; 2-pole 1-way midget, 1/3; 2-pole 1-way, 1/3; 9-pole 3-way, 3/6. P. & P. 3d. each.

Pre-Aligned Midget 465 Kc. Q. 120, 9/- per pair, post 6d. **Miniature 465 Kc. I.F.s. Q. 120,** per pair, 10/-.

465 Kc. Midget I.F.s. Q. 120, size 1 1/2 in. long, lin. wide, 2 in. deep, by very famous manufacturer. Pre-aligned adjustable iron dust cores, per pair, 12/6.

Iron Cored 465 Kc. Whistle Filter, 2/6.

Valve Holders. Paxolin international octal, 4d. each. Moulded international octal, 7d. each. EFSO ceramic, 7d. each. Moulded B7G slightly soiled, 6d. each.

Line Cord. 3-way 0.3 amp., 180 ohms per yard, 1/3 per yard. **Ceramic P.F.S.** 3 each of the following: 330, 220, 180 and 82, 2/6.

Trimmers. 5-40 pf., 5d.; 10-110, 10-250, 10-450 pf., 10d. Three bank, 50 pf., 1/3. Four bank, 50 pf., 1/8.

Twin Gang .0005 Tuning Condenser, 5/-. With trimmers, 7/6. Post and packing 6d.

Twin Gang Midget .00037 with perspex dust cover and trimmers, 8/6. Post and pkg. 6d.

Mains Droppers. 0.3 amp. 460 ohms, tapped 280 and 410, 1/6; 0.2 amp. 717 ohms, tapped at 100 ohms, vitreous, 1/6; 0.3 amp. 950 ohms, tapped 700 and 825, 2/6; 0.2 amp. 1,000 ohm, vitreous, tapped, 2/6.

P. & P. on each 3d.

Volume Controls by famous manufacturer. Long spindle and switch 1/2, 1 and 2 meg., 4/- each; 20, 25 and 50 kt, 3/6 each. Post and packing 3d. each.

THIS MONTH'S OUTSTANDING OFFER

Volume Control. Removed from chassis with mounting bracket 1/2 meg. with switch, 2/-, post paid.

Terms of business: Cash with order. Dispatch of goods within 3 days from receipt of order. Where post and packing charge is not stated please add 6d. up to 10/-, 1/- up to £1 and 1/6 up to £2.

23 HIGH STREET (Opposite Granada Cinema,) ACTON, W.3

Hours of Business: Saturdays 9-6 p.m. Wednesday 9-1 p.m. Other days 9-4.30 p.m.

Telephone: ACOrn 5901

CLYDESDALE

Bargains in Ex-Service Radio and Electronic Equipment

ELECTRIC IGNITION TESTER TYPE V.E.D. PATT. 56352, MADE BY ENGLISH ELECTRIC

A cathode ray tester employing an entirely new technique in ignition testing of internal combustion engines. Enables the electrical performance of the entire ignition system to be observed on the screen of the Cathode Ray Tube, while the engine is running. Will operate from 6, 12 and 24 volts D.C. or 230 v. A.C. Built into a black crackle case with hinged front and carrying handle. Dim.: 15½ x 8½ x 11½ in.

CLYDESDALE'S PRICE ONLY **£35** **CARRIAGE PAID**

Ex-U.S.A.A.F. in original carton COMBINED PRESSURE AND VACUUM PUMP

137J/3798, made by G.M.C./Delco (U.S.A.). 24 v. D.C. 11.2 a., 6,600 r.p.m., ½ h.p. motor, with vacuum and pressure pumps, whole assembly 12 x 7½ x 7 in. Shock mtd. on board 14½ x 6½ x 1½ in. Accessories include conn. nozzles and Schween regulating valve.

CLYDESDALE'S PRICE ONLY **£4.4.0** **CARRIAGE PAID**

COOLANT PUMP BY PACKARD U.S.A.

A turbine type pump, directly driven from semi-ball joint-spline socket (by motor not supplied) clockwise rotation with safety valve, sludge vent, etc.

Dia. of turbine 6 in., dia. of pump chamber 8 in., depth 2 in. Inlet and outlet dia. 1½ in. Overall dim.: 11½ x 7½ x 13 in.

CLYDESDALE'S PRICE ONLY **49/6** **CARRIAGE PAID**

FEATHERING PUMP 5U/402

Driven by a 24 v. D.C. motor type C2801, through 2:1 reduction gear, fluid moved by two 12-tooth wheels. Safety valve fitted. Overall dimensions 12½ x 6 x 6 in. Pumping rate, lubricating oil 2 gals. per min. approx. Air pressure, 40 lbs. per sq. in. Oil pressure, over 100 lbs. per sq. in. Inlet ½ in. Outlet 1 in.

CLYDESDALE'S PRICE ONLY **£2.10.0** **CARRIAGE PAID**

PUMP DESSICATOR ADM. PATT. 12128 FOR TELESCOPES AND BINOCULARS

Hand operated complete with spare gel cell and conn. tubes. Stroke cap. 480 ccs. fitted humidity gauge, reads 10/100 per cent., vacuum gauge 0/30 in. In wood transit case 19½ x 12 x 9 in.


CLYDESDALE'S PRICE ONLY **£5.10.0** **CARRIAGE PAID**

HAND GENERATOR 10 WATT Mk. II

Designed for V3.48 and V3.18 driven by two handles, complete with operator's seat. Speed should be 50/70 r.p.m. Smoothed outputs: 162 v. 60 mA., 3.1 v. 3 a. and 12 v. Generator Dim.: 5½ x 5½ x 6½ in., wgt. 13 lbs. Leg v/seat dim.: 33 x 6 x 2½ in., wgt. 5½ lbs. Legs (2) dim.: 25 x 2 in.

CLYDESDALE'S PRICE ONLY **45/- each** **CARRIAGE PAID**

BATTERY CHARGER

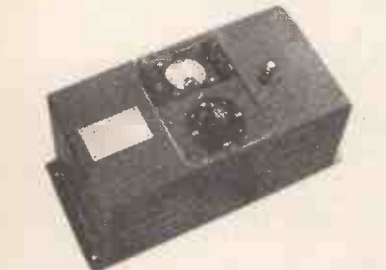

Rectifier type 42A. Ref. 10DB/1630. A compact battery charger, output 4 amps. at 6 or 12 volts D.C. Input 230 v. A.C. 50 cfs. with ammeter, removable fuses, control switch for each circuit, input and output points, contained in well ventilated black crackle metal case, for wall or bench mtg. Dim.: 12 x 8 x 6 in.

CLYDESDALE'S PRICE ONLY **£5.19.6 each** **CARRIAGE PAID**

TEST EQUIPMENT

Common series test gear with 3 antennas, 3 test units, mod. BC-456-B (or E) with dynamotor, antenna relay, 2 radio control boxes, 2 racks, 6 mountings, I.F. shunt unit, control unit NC-237 and 17 cable assembly.

CLYDESDALE'S PRICE ONLY **£22.10.0** **CARRIAGE PAID**

COND. NO. 9 SET, Mk. I, RECEIVER UNIT WITH POWER SUPPLY UNIT

A 10-valve 7/ARF3, 2/129C7, 12Y4, band-pass, superhet receiver, frequency range 2 to 5 mcs., with built-in calibrator, switched H.T. and "S" meter, H.F. and L.F. gain B.F.O., etc., etc.

Separate power unit operated from 12 v. D.C. 115 v. A.C. or 230 v. A.C. OZ4 cold cathode rectifier, with spares kit, all valves, aerial, insulators, headphones, packed in wood case, 24 in. x 22 in. x 3 1/2 in.

CLYDESDALE'S PRICE ONLY **£10** **CARRIAGE PAID**

FOR EXPORT ONLY WIRELESS SET NO. 38 Mk.2 BRAND NEW

A haversack type transmitter, range up to 5 miles. Frequencies 7 to 9 mcs. 5 valves: 4/ARP12, ATP4, operated from dry batteries (not supplied), complete with headphones, throat microphones, aerials, junction box spares, satchel and instruction card. Four complete units packed in wood case, 57½ x 14 x 14 in.

PRICE ON APPLICATION.

WS.18 RECEIVER SECTION

Superhet chassis with 4 valves: 3/ARP12, AR8, range 6-9 mcs. = 50-33.3 metres, etc., etc., on 8½ x 6 in. chassis with 9½ x 5½ in. front panel.

CLYDESDALE'S PRICE ONLY **25/-** **POST PAID**

Circuits, 2/3.

Also available with partly stripped (M.O.S.) Tx section, no valves or meter, with metal carrying case. Dim.: 11 x 10 x 17 in.

CLYDESDALE'S PRICE ONLY **37/6** **CARRIAGE PAID**

Circuits, 4/6.

U.S.A. PATT. MORSE KEY TYPE CJB



Enclosed contact type as made by J. H. Bunnell and Co., and used in American aircraft. Finish black crackle, complete with contact and tension adjusting screws. Dim.: 8½ x 11 x 2 in.

CLYDESDALE'S PRICE ONLY **12/6** **POST PAID**

NEW LIST NO. 8

Giving details and illustrations of ex-services items and cancelling all previous lists and supplements.

Now Ready—Price 1/6.

Price credited on first purchase of 10/- or over.

I.F./A.F. AMPLIFIER UNIT R1355

The popular TV unit, 5 I.F. stages, 10 valves: 8/VR65 (SP61), 5U4G, VU120A, etc., etc. In metal case, 18 x 8½ x 7½ in.

CLYDESDALE'S PRICE ONLY **67/6 each** **CARRIAGE PAID**

R.F. UNIT TYPE 27

In original carton. The ideal S.W. Converter for TV, variable tuning. Range, 85-65 mcs., 2/VR136 (EP54), VR136 (EC52), etc. Output, 7-8 mcs. In metal case, 9½ x 7½ x 4½ in.

CLYDESDALE'S PRICE ONLY **63/- each** **POST PAID**

Special offer: R1355 UNIT, plus R.F.27 UNIT, for £5/17/6, carriage paid.

INDICATOR UNIT TYPE 217A

Containing 100 microamp (sd. 2½ in. flush mtg. meter, dial calibrated in yards; vol. controls, toggle sw., etc., in metal case 6 x 4½ x 2 in.

CLYDESDALE'S PRICE ONLY **25/-** **POST PAID**



A table type field telephone in bakelite moulded case, with bell and magneto generator, operated from internal 3-volt "2" or "7" coil battery (not supplied). Suitable for two-way communication up to a mile distance when used in pairs. Overall dimensions: 9½ x 6½ x 5½ in.

CLYDESDALE'S PRICE ONLY **£3.19.6 each** **POST PAID**

FLUXMETER WY.0023

Designed to calibrate the field of magnets within the range of 500 to 4,000 gauss and to determine their polarity. Complete with probe unit and contained in a hardwood case with hinged lid and handle. Instructions on lid. Dim.: 12½ x 9 x 6 in.

CLYDESDALE'S PRICE ONLY **£5** **CARRIAGE PAID**

JEFFERSON TRAVIS UF-2 TRANSCEIVER CHASSIS

Partly stripped by the M.O.S., less valves, tuning inductance sec. connections, but otherwise fairly intact. A fine basis for a transportable type two-way radio. Original frequencies 60-75 mcs. Valve types 2/6Y7, 12J5. The unit comprises two chassis, with controls and speaker mounted on chrome plate etched steel panels, housed in cabinet finished black crackle. Dim.: 15½ x 18½ x 8½ in.

CLYDESDALE'S PRICE ONLY **£2** **CARRIAGE PAID**

JEFFERSON TRAVIS UF-I POWER SUPPLY

Complete self-contained vibratorpack. Input 12 volts. Outputs 200/150 v. D.C., 30/50 mA. Choke capacity smoothed and 2 L.T. taps. Unused but vibrator contacts stuck due to long storage. Complete with synchronous vibrator, smoothing coils, etc. in metal case. Dim.: 7 x 3 x 4 in.

CLYDESDALE'S PRICE ONLY **25/-** **CARRIAGE PAID**

S-440-B V.H.F. TRANSMITTER CHASSIS

Partly stripped by the M.O.S., less valves, tuning coils and crystal, but otherwise fairly intact. A fine basis for ideas in V.F.O. or Tx. Original frequencies 85-98 mcs. valve types 3/RK34, 2/6N7, 6V6. Housed in louvred case finished grey crackle. Dim., 14 x 8 x 7 in.

CLYDESDALE'S PRICE ONLY **27/6** **POST PAID**

COMMAND TRANSMITTER CHASSIS

Partly stripped by the M.O.S., less valves, coil winding, crystal and dynamotor, but otherwise fairly intact. A fine basis for ideas in V.F.O. or Tx. Models BC-457 to BC-459 components identical, valve types 2/1625, 1626, 1629. Conversion suggestions and circuits supplied. In aluminium case. Dim., 7½ x 5 x 8½ in. Wgt., 8½ lbs.

CLYDESDALE'S PRICE ONLY **15/-** **POST PAID**

SPEECH MODULATOR BC-456

Command Modulator unit with valves, 1625, 12J5, VR150/30 less dynamotor, otherwise complete in metal case 10½ x 7½ x 4½ in., chassis depth 2½ in.

CLYDESDALE'S PRICE ONLY **19/6** **CARRIAGE PAID**

BC-625-A TRANSMITTER CHASSIS

Less Valves. Partly stripped by the B.O.T., but contains many useful parts. R.F. section in good order, less valves, crystal switch and crystals, separate modulation transformer and choke supplied. Dim.: 15½ x 7½ x 6 in.

CLYDESDALE'S PRICE ONLY **29/6** **CARRIAGE PAID**

DINGHY TELESCOPIC MAST

A lightweight (4 oz.) mast for many uses, car aerial, camera tripod, fishing rod, etc. Made of aluminium, 7 sections. Closed, 14½ in.; extended, 7 ft. 6 in. Diam., base ½ in., top 7/16 in.

CLYDESDALE'S PRICE ONLY **6/-** **POST PAID**

AERIAL INSULATORS 10A/1275

Black plastic chain insulators, 3 links each. 3½ in. long, 1½ in. wide. Total length, 7 in.

CLYDESDALE'S PRICE ONLY **1/6 per pair** **POST PAID**

Order direct from:—

CLYDESDALE

Phone: South 2706/9 Branches in Scotland, England and Northern Ireland

SUPPLY 2 BRIDGE STREET CO. LTD. GLASGOW · CS

UNIVERSITY RADIO LTD.

Offer Guaranteed Used Equipment at Attractive Prices

| | | | | | |
|---|----------|---|----------|---|----------|
| Evershed's 500 volt Wee Megger, in leather case..... | £10 10 0 | Avo 1949 Capacity and Resistance Bridge, as new | £6 10 0 | Wharfedale Super 8/CS, as new | £3 7 6 |
| Avo 1948 Signal Generator, as new | £12 10 0 | R.C.A. Volt-Ohm-Ammist Junior Valve Voltmeter, as new with manual | £16 10 0 | Wharfedale Bronze 10in. Speaker | £2 5 0 |
| Cossor Double-Beam Oscilloscope, model 339, as new | £45 0 0 | Shaftesbury Ribbon Mikes, as new | £6 0 0 | Wharfedale Corner Cabinet, fitted with 12in. Wharfedale Speaker. All as new | £19 0 0 |
| Cossor, as above, model 3339 | £36 10 0 | Rothermel Crystal Mikes, as new | £2 2 6 | Wharfedale Twin Speakers, in Wharfedale Corner Cabinet, as new | £30 0 0 |
| Triplet Combination Tester, model 1183-SC, complete with leads etc. As new | £13 10 0 | Voigt Light Twin Speaker Unit, mains energised, complete with mains-energising unit, as new | £16 10 0 | E.M.I. 30 watt Amplifier, AC 200-250 volts. Mike and Gram. Input. Rack-mounting. 2 KT66's in push-pull. Variable impedance speaker-output. Metered. With valves. As new | £19 10 0 |
| Taylor Valve-Tester, model 47A, with several extra valve-adaptors, charts, etc. Complete and as new | £20 0 0 | Voigt Latest Model PM Unit, in Voigt corner cabinet, unpolished. (Not Home Constructor Cabinet) Listed £90, our price, as new | £70 0 0 | R-107 Receiver, with all valves, less metal case. New condition | £13 0 0 |
| Taylor 120A AC/DC Test-Meter, as new | £6 10 0 | Wharfedale W-10/CS Speaker, 2-3 or 15 ohms, as new | £7 0 0 | Garrard Auto-changer, model RC70A, in portable rexine case, as new, 78 r.p.m. | £15 10 0 |
| Avo Minor, AC/DC, as new | £7 10 0 | Wharfedale W-12/CS, as new | £7 0 0 | | |
| Avo Model 7, as new | £14 10 0 | | | | |
| Avo Model 40, as new | £12 10 0 | | | | |
| Eddystone 640, as new | £23 10 0 | | | | |

WE NEED GOOD USED EQUIPMENT URGENTLY PLEASE SEND, BRING OR PHONE FOR OFFER

| | | | | | |
|--|----------|---|----------|---|----------|
| Trixette 3-speed Record Player, with built-in amplifier and speaker, as new, A.C. 200-250 volts | £32 0 0 | Ex-W.D. B2 TX/RX, in portable case. A.C. and battery power-unit. Coils, phones, key, etc. As new | £17 10 0 | Marconi-Ekco Signal Generator Type TM2571. Coverage 3.5 to 150 Megs. A.C. 200-250v. With calibration charts, etc. Perfect | £40 0 0 |
| Decca Long-playing Record Unit, in portable Rexine case, as new | £8 10 0 | Evershed & Vignoll's 500 volt Constant Pressure Megger, in leather case, as new | £19 10 0 | Transmitter Type 12, A.C. 200-250 volts, 2.6 to 17.5 Megs., complete with valves and perfect | £20 0 0 |
| Decca Record-playing Unit, 78 r.p.m., as new | £6 10 0 | As Above, 100 volt | £12 0 0 | Ex-W.D. TX/RX Type A Mill, in small portable attache case, with built-in A.C. Power-pack 100-250 volts or D.C. 6 volts. Complete with key, etc., as new | £12 10 0 |
| Sound Sales Combined Amplifier and Tuner Unit, with tone-control etc. A.C. 200-250 volts, 3 wave-bands. Variable selectivity. 2 PX4's in p-p. As new | £22 10 0 | Cambridge Unipivot Galvanometer, patt. "L," 0-120 milli-volts 6" scale, as new | £8 0 0 | Ward Rotary Converter, 24 volt D.C. to 230 A.C., 50 cycles, 250 watts, with built-in filter-unit. As new | £12 10 0 |
| Acoustical 30 watt Amplifier, with M/C Mike and Gram. inputs, A.C. 200-250 volts. Complete in metal case, as new | £16 10 0 | Newton Bros. Carbon Pile Auto Voltage-Control Regulator, 600 watts. As new | £10 10 0 | E.D.C. Rotary Converter, 110 D.C. to 230 A.C., 350 watts. As new | £18 10 0 |
| | | Ex-U.S. Navy H.R.O. Receiver, with 5 coils, 550 KC's to 30 megs. Complete with AC Power-pack. As new | £22 0 0 | B.S.R. Disc-Recording Amplifier, type AR15 in portable metal case. As new | £38 10 0 |
| | | Decca (1949) Decallian, non-auto record player, with built-in Amplifier and Speaker. In portable case. As new | £19 10 0 | | |

WE NEED AR 88's - BC 221's - 348's - 342's ALSO COSSOR DB'SCOPIES 339a OR 3339 Etc. WE WILL PAY WITHIN £2.0.0 OF THE MARKET PRICE

| | | | | | |
|--|----------|--|----------|--|----------|
| B.S.R. Disc-Recording Unit, in portable case, as new | £70 0 0 | Weston (U.S.A.) A.C. D.C. Test-meter, model E772, 20,000 o.p.v. In portable case. As new | £15 0 0 | General Electric (U.S.A.) Tube Checker in portable case. 110 A.C., as new | £11 10 0 |
| Rogers Williamson Amplifier and Tone-Control Unit, complete with all valves. As new | £34 0 0 | R-107 Receiver, complete and perfect | £14 0 0 | E.D.C. Rotary Converter, D.C. 220-240, A.C. 220-240, 50 cy. 120 w., in metal silencing case, complete with filter-unit. As new | £16 10 0 |
| Eddystone 358X, with 8 coils. 31 meg. to 100 kc's with A.C. power-pack. As new | £22 10 0 | Thrush Capacity and Resistance Bridge, as new | £7 10 0 | As above, 110 volts to 230-50 A.C. 100 watts with filter unit, as new | £10 10 0 |
| Vortexion 50 watt Amplifier, chassis and valves with moving-coil mike and gram. inputs etc. A.C. 200-250 volts. As new | £18 10 0 | Webb's Triple Cross-over Unit, type CE, as new | £4 0 0 | Avo Electronic Valve-Tester. Latest model, as new | £45 0 0 |
| Taylor 313C Capacity and Inductance Adaptor, as new | £3 17 6 | Venner 50 amp. Clockwork Time-Switch, as new | £7 10 0 | Avo Wide-Range Signal Generator, as new | £23 10 0 |
| Taub (U.S.A.) Short-wave Receiver, chassis and valves, 1.5 to 30 megs. A.C. 200-250 volts. With matching PM speaker | £11 10 0 | 3-circuit Charger by Newton's of Taunton. 50 volts at 1/2 amp., 50 volts at 2 amps. and 50 volts at 6 amps. A.C. 200-250 volts. In perfect working order | £10 10 0 | We have in stock several of the latest models of Marconi Signal Generators etc. | |
| | | Valradio Convertors, 200-250 D.C. to 200-250 A.C., 50 cycles, 200 watts. As new | £10 10 0 | Mullard Oscilloscope, type GM-3152, as new | £30 0 0 |
| | | | | S.T.C. Oscilloscope, type 74340, complete and as new | £30 0 0 |



We have a large selection of British and U.S.A. Valve Testers, Test-Meters and Signal Generators, etc. Your enquiries are welcome. S.A.E. please.

THESE ITEMS ARE ONLY A SMALL SELECTION FROM OUR STOCK OF EQUIPMENT. YOUR ENQUIRIES FOR ANYTHING THAT YOU MAY NEED WILL BE WELCOME. WE HAVE OTHER EQUIPMENT ARRIVING DAILY!

CASH OR CHEQUE WITH ORDERS.

ALL ITEMS ARE CARRIAGE EXTRA.

22 LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2

OUR BRANCH AT 39a (opposite) IS OPEN ALL DAY THURSDAY.

Phone: GERrard 4447, 8582 and 5507. Hours 9 to 6. Thursdays 9 to 1.

Henry's

RADIO COMPONENTS
ELECTRONIC
& TELEPHONE
EQUIPMENT

RECEIVER TYPE 25. The receiver portion of the T/R 1196. Covers 4.3-6.7 Mc/s and makes an ideal basis for an all-wave receiver, as per "Practical Wireless," August, 1949, issue. Complete with valves types EF36(2), EF39(2), EK32 and EBC33. Supplied complete with necessary conversion data for home use. 35/-; new condition. Chassis only 8/6.

CATHODE RAY TUBES. VCR97 6in. Guaranteed for Television use, full picture 45/- plus 7/6 carr. and packing. SCPI (U.S.A.) 25/- 3BP1 3ins. Tube complete with base, holder and shield in metal case, 25/-.

MOVING COIL METERS, 2in. SCALE. 0-50 mA., panel mounting, 7/6; 0-40 volts, panel mounting, 7/6; 0-20 amps., round projecting type, 7/6; 0-40/120 mA., double reading, round projecting type, 12/6; 0-100 v. A.C. Rectified 1000 o.p.v. 2 1/2in. scale 25/-.

5KV ELECTROSTATIC VOLTMETER. 0-5 kV, panel-mounting, 3 1/2in. scale, brand new. 50/- each.

A SIGNAL TRACER at minimum cost. An easy-to-build unit that can be used for R.F., I.F., and Audio signal tracing, without any switching or tuning. Highly sensitive, easy-to-build, responds to signals picked up from an ordinary receiving aerial. The circuit is that of a high-gain 3-stage resistance-coupled audio frequency amplifier, with a 5-in. speaker in the Output of the Power Amplifier stage.

We shall be pleased to supply a complete kit for the construction of the above, right down to the last nut and bolt, for the low price of £2/18/6. Concise instructions and circuits are supplied. If preferred, circuit and instructions only can be supplied for 1/6 post free. All items may be purchased separately. This is a highly efficient instrument, and a MUST for every radio man. Completely assembled and tested, ready for use, £5/5/-.

NO. 38 "WALKIE-TALKIE" TRANS/RECEIVER. Complete with throat mike, phones, junction box and aerial rods in canvas bag. Freq. range 7.4 to 9 Mc/s. All units are as new and tested before despatch. As supplied to Overseas Police Forces. £4/19/6, carriage 2/6.

PLESSEY, 3in. P.M. SPEAKER with miniature Output Trans. 17/6. W.B. 2 1/2in. P.M. 3 ohms, less trans., 15/-.

VR91 (EF50) RED SYLVANIAN. Brand new and boxed, 10/- Brand new (British), 8/6.

Ex-Units (but guaranteed), 6/-.
GERMANIUM CRYSTAL DIODES, complete with full wiring circuit and diagram, 4/6.

METAL RECTIFIERS. S.T.C. 200 volts, 75 mA, 6/-; G.E.C. 6 volts, 1 amp., 4/-; Westinghouse 12 volts, 2 amp., 12/6; 12 V. 3 1/2 amps., 17/6; Pencil Type E.H.T. 600 v. 1 mA., 4/7; Pencil Type E.H.T. 1,000 v. 1 mA., 6/-.

W.6 and WX6, 1/6.
FILAMENT TRANSFORMERS. All inputs 200/50 A.C. 6.3 v. 1.5 amp., 7/6; 6.3 v. 2 1/2 amp., 10/-; 6 v. or 12 v. 3 a., 15/-; 6.3 v. 12 a., 37/6.

R.3515 I.F. STRIP. A complete I.F. Unit, comprising 6 SP61 I.F. Stages, tuned to 13.5 Mc/s, 1 EA50 diode detector, and 1 EF35 or EF39 output on video stage. A few modifications only are required to adapt this unit, which will give pictures of extremely good quality. Price, complete with valves, and foolproof modification instructions, is 45/-, plus 5/- carriage and packing. Limited quantity only.

R3547 RECEIVERS. Absolutely brand new, in sealed manufacturers' packing cases. Incorporating 15 valves type EF50, 2 of SP61, EF36, EBC33, 3 of EB34. Complete 45 Mc/s I.F. Strip, motor dial and drive, pots, etc., £6 only, plus 10/- packing and carriage. Whilst they last!

RECEIVER R.1335, as specified for "Inexpensive Television." Complete with 8 valves VR65, and 1 ea. 5U4G, VUI20, VR92, and a copy of "Inexpensive T.V." ONLY 55/- (carriage, etc., 7/6).

FREQUENCY CONTROL CRYSTALS. By American G.E. Co. Octal base fixing. Following frequencies only: 2,500 kc/s, 3,500 kc/s, 4,600 kc/s, 6,200 kc/s, 8,000 kc/s, 7/6 each.

MIDGET .0005 mfd. TWO-GANG TUNING CONDENSERS. Size only 2 1/2in. x 1 1/2in. x 1 1/2in. Capacity guaranteed, standard length 1/2in. spindle, complete with mounting bracket, less trimmers, 6/6 or, complete with "built-in" trimmers, 7/6 each plus 6d. post.

VIBRATOR POWER UNITS, 2 volt. As for Canadian 58 set. Completely smoothed, output 1.5 v. L.T. and 90 v. and 180 v. H.T. at 35 mA. Complete in grey metal box. Size 8 x 3 1/2 x 4 1/2in., 50/- only.

PUSH-PULL OUTPUT TRANSFORMER. U.S.A. dotted type primary 10,000/5 Sec. 20, 80, 150/20 watts, 21/-.

TWO-GANG .0005 CONDENSER. Complete with 4-way push-button assembly. Size 3 1/2in. x 3in. x 3in., 8/6 each.

NEW 28-PAGE CATALOGUE NOW AVAILABLE PRICE 3d.

5, HARROW ROAD, LONDON, W.2

PADDington 1008/9 and 401

DECEMBER OFFERS

BATTERY SUPERSEDER. Will save battery users pounds. Operates from a 2-volt ACCUMULATOR and delivers constant H.T. of 67 volts at 4.7 mA, 130 volts at 13-25 mA, and 1.4 v. L.T. if required. American made, and originally intended for Walkie Talkie equipment, this unit is easily adapted for use with any battery set, and full illustrated details are supplied. ONLY 60/- (postage etc., 2/-).

I.F. STRIP TYPE 194. An easily modified I.F. Strip recommended for T.V. constructors who want good results at moderate cost, or for those who have built televisions but are having trouble in the vision or sound receivers. Can also be modified for 2 Channel working as per details in "Practical Television" October issue. This 6-stage strip measures 18in. x 5in. x 5in. and contains 6 valves: VR65, 1 of VR92, and 1 of VR53 or VR56. Mod. data supplied. BRAND NEW. ONLY 45/- (postage, etc., 2/6).

RECEIVER R.1355. The unit specified for "Inexpensive Television." Complete with 8 valves: VR65, and 1 ea. 5U4G, VUI20, VR92, and a copy of "Inexpensive T.V.," which gives full constructional details.

RDF 1 RECEIVER. A very powerful 14-valve receiver with 4 I.F. stages of 12 mcs. with 4 mcs. bandwidth. Will convert into a first-class T.V. receiver for 2 Channel working as described in "Practical Television," October and November issues, a reprint being supplied. Valve line up: 5 of SP61, 2 of P61, 3 of EA50, and 1 ea. CV63, EB34, EC52, 5Z4G. ONLY 49/6 (carriage, etc., 5/-).

10-VALVE 1 1/2-METRE SUPERHET ZC8931. For long-distance T.V. results. Valve line up is 6 of VR65, 2 of VR92, and 1 ea. VR136 and VR137, and the 12 mcs. 6-stage I.F. Strip gives tremendous amplification with ample bandwidth of 4 mcs. Easily modified. Full details supplied. ONLY 59/6 (carriage 5/-).

6046/6050 AMPLIFIER. An ideal unit for conversion into a high gain T.V. pre-amplifier, full details being supplied. Complete with 2 valves EF50. ONLY 22/6 (postage, etc., 1/6).

R.F. UNIT TYPE 24. For use with the R.1355 Receiver for Sutton Coldfield T.V. (mod. data supplied) or as a pre-amplifier as per "Practical Television" December 1950. ONLY 17/6 (postage 1/6).

SECTIONAL TELESCOPIC AERIAL, comprising 16 sections each 16in. in length, and colour-coded for ease of assembly. Complete in web case. BRAND NEW. ONLY 9/6 (postage 1/-).

WALKIE TALKIE CHASSIS TYPE 38. A beautifully made chassis, ideal for the enthusiast, or as a source of components. As used by the Forces, with the exception of certain transmitting components removed by the Ministry of Supply. ONLY 9/6 (postage 1/6).

HEADPHONES DLR NO. 2. Low resistance phones fitted with solid type head band, and 6ft. lead terminating in jack-plug. As used on type 18 receiver, etc. BRAND NEW. ONLY 6/6 (postage 1/-).

MUIRHEAD SLOW MOTION DRIVE. A really precision product of this famous maker. 3in. in diameter with edge marked 0-180. Complete with cursor. BRAND NEW IN MAKER'S CARTONS. ONLY 8/6 (postage 1/-).

CONDENSERS. Paper metal cased. 1 mfd. 3,000 volts, 4/6; electrolytics (cans unless stated), 8 mfd. 450 v., 2/6; 8 x 8 500 v., 4/9; 8 x 16 450 v., 5/9; 16 500 v. cardboard, 6/-; 16 450 v. can, 5/6; 16 x 16 500 v., 7/-; 24 350 v. cardboard, 4/6; 25 25 v., 1/6; 32 350 v., 2/9; 50 12 v. can or card, 1/8; 32 x 16 450 v., 6/9 (postage 1/- please on orders under £1).

CHOKES. 20 H.80/120 mA, 6/6; 5 H.200/300 mA, 6/- (postage 1/-).

GERMANIUM CRYSTAL DIODES, 4/6.
VR91 (EF50), ex New Equipment, and tested, 6/6; American Red Sylvanias, 8/6.

MAINS TRANSFORMER. Standard primaries. Universal mounting, 350-0-350 v. 80 mA, 0.4-6.3 v. 4 a., and 0.4-5 v. 2 a., 18/6 (postage 1/6).

TRAIN TRANSFORMER. 200/240 v. input, output 30 v. 2 a., tapped 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v., 19/6 (postage 1/6).

EHT TRANSFORMER, for VCR97 tube, with 4 v. for tube heater, and 4 v. tapped 2 v. for EHT rectifier, 37/6 (postage 1/6).

6in. MAGNIFYING LENS FOR VCR97 TUBE. First-grade oil-filled. ONLY 25/- (postage 1/6).

PENTODE OUTPUT TRANSFORMER, for 3 ohm speakers, 5/3.

WHARFEDALE OP3, with ratios of 30, 60, and 90, 6/6 (postage per trans. 4d.).

6.3 v. FILAMENT TRANSFORMER, rated 1 1/2 amps., 7/6 (postage 4d.).

CO-AXIAL CABLE, 75-80 ohms, thin type, 1/3 per yard (post paid 12 yards or more).

VOLUME CONTROLS. New, manufacturer's surplus. Less switch, from 2 k. to 3 megs., 3/-; with switch from 1 k. to 2 megs., 4/6 (postage 3d.).

HAND MICROPHONE, with carbon granule insert and switch in handle, 3/6 (postage 1/-).

INTERNATIONAL OCTAL PLUG. Fits into I.O. valve-holder, 2/- (postage 3d.).

VIBRATORS. Mallory type 650 4 pin, 7/6 (postage 6d.).

VALVE HOLDERS. Amphenol I.O. or M.O. 7d., 6/- per doz. Ceramic Brit. 5 pin, 1/-, 10/- doz. Diode, 6d., 5/- doz. VCR97 holder, 2/6, 24/- doz. (post paid 1 doz. or more).

Cash with order please, and print name and address clearly. Amounts given for carriage refer to inland only.


U.E.I. CORPORATION

Radio Corner, 138 Gray's Inn Road, London, W.C.1. Phone: TERMINUS 7937.

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross)

Recognised as the Most Reliable Valveholders

Sub-Miniature Valveholders

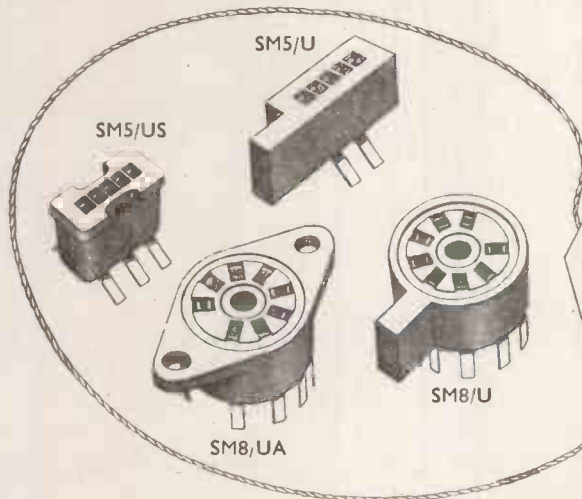

All Moulded in Silica-loaded Polystyrene

- B5A TYPES** { SM5/U. Panel Mounting
SM5/US. Chassis Mounting
- B8D TYPES** { SM8/U. Panel Mounting
SM8/UA. Chassis Mounting

Wholesale Enquiries:—CYRIL FRENCH LTD., HIGH STREET, HAMPTON WICK, MIDDLESEX · KIN. 2240
Manufacturers' Enquiries:—THE McMURDO INSTRUMENT CO. LTD., VICTORIA WORKS, ASHTEAD, SURREY ASHTEAD 3401

GALPIN'S ELECTRICAL STORES

408 High Street, Lewisham, London, S.E.13

Telephone: Lee Green 0309

Near Lewisham Hospital

Terms:

CASH WITH ORDER. NO C.O.D.

EARLY CLOSING DAY THURSDAY

ALL GOODS SENT ON 7 DAYS' APPROVAL AGAINST CASH

MAINS TRANSFORMERS (new). Input 200-250 volts in steps of 10 volts. Output 350-0-350 volts 300 m/amps., 6.3 volts 8 amps., twice, 4 volts 4 amps., 5 volts 4 amps., 65/- each, carriage 3/6. Ditto, 450-0-450 volts 250 m/amps., 6.3 volts 8 amps. twice, 4 volts 4 amps., 5 volts 4 amps., 65/- each, carriage 3/6. Another, input as above. Output 500-0-500 volts 250 m/amps., 6.3 volts 8 amps. twice, 6.3 volts 4 amps., 4 volts 4 amps., 5 volts 4 amps., 70/-, carriage 3/6. Another, wound to (electronic) specifications, 350-0-350 volts 250 m/amps., 4 volts 8 amps., 4 volts 4 amps., 6.3 volts 8 amps., 0-2-6.3 volts 2 amps., 63/6 each, carriage paid. Another, input as above. Output 500-350-0-350-500 volts 250 m/amps., 6.3 volts 6 amps., 0-2-6.3 volts 2 amps., 0-4-5 volts 4 amps. twice, 67/6 each, carriage 3/6.

PRE-PAYMENT 1/- SLOT METERS. 200-250 volts A.C., 50 cycles, 1 phase, set at 3d. per unit, 60/- each, carriage 5/-. Ditto for D.C. mains, 45/- each, carriage 5/- (all 20 amp. load).

SWITCHBOARD METERS. 4in. scale, moving coil (D.C.) only, 0 to 14 amps., 17/6 each, post 1/6. Ditto, A.C./D.C., 22/6 each, post 1/6. Another 0 to 30 amps., A.C./D.C., 25/-, post 1/6.

MAINS TRANSFORMERS (new). Input 200-250 volts in steps of 10 volts, output 350-0-350 volts 180 m/amps., 4 volts 4 amps., 5 volts 3 amps., 6.3 volts 4 amps., 39/6 each, post 1/6. Another, 350-0-350 volts 180 m/amps., 6.3 volts 8 amps., 0-4-5 volts 4 amps., 39/6 each, post 1/6. Another, 500-0-500 volts 150 m/amps., 4 volts 4 amps. C.T., 6.3 volts 4 amps. C.T., 5 volts 3 amps., 42/6 each, post 1/6. Another, 425-0-425 volts 160 m/amps., 6.3 volts 4 amps. C.T. twice, 5 v. 3 amps., 42/6 each, post 1/6.

DOUBLE-WOUND VOLTAGE CHANGER TRANSFORMERS. 3,000 watt, 110 to 240 volts or vice versa, weight 100 lb., £10/10/- each, carriage 10/-.

EX-W.D. SURPLUS METERS. 2in. scale, 0 to 20 volts, 6/6 each, post 6d.; 0 to 40 volts, 7/6 each, post 6d. (both moving coil). Thermo coupled 0 to 350 m/amp., 7/6 each, post 6d.

SWITCHBOARD. 4in. scale Amp. meters; moving coil meters, 100 to 250 amps., complete with shunt, 30/- each, post 1/6.

EX-RADAR MAINS TRANSFORMERS. 230 volts input, 50 cycles, 1 phase. Output 4,500-5,500 volts approx., 30 m/amps., 6.3 volts 2 amps., 4 volts 1 1/2 amps., 2 volts 2 amps., these transformers are new, immersed in oil. Can be taken out of the oil and used as television transformers, giving an output of 10 m/amps.; overall size of transformers, separately, 5 1/2 x 4 1/2 x 4in. and 3 x 3 x 2 1/2in., price £3/10/- each, carriage paid.

ROTARY CONVERTERS. 24-28 volts D.C. Input, 1,200 volts 70 m/amps. D.C. Output, 10/- each, post free.

AUTO-WOUND VOLTAGE CHANGER TRANSFORMERS. Tapped 0-110-200-230 volts 350 watts, 48/6 each, post 1/6. As above, but 500 watts, 62/6 each, carriage 3/6. As above, 200 watts, 35/- each, post 1/6. 1,600 watts, tapped 0-110-150-190-230 volts, £5/5/- each, carriage 5/-.

TYPE 101 R.F. UNITS (new). Containing 6 valves, including grounded grid triode F.H.P., 24-volt universal motor, numerous resistances and condensers, etc., 35/- each, carriage 3/6.

RECTIFIERS (new). D.C. output 36 volts at 50 amps., complete with mains transformer, 230 volts A.C. Input 50 cycles, 11 phase. Output to match the required voltage for the rectifier, £15 per set, carriage 10/-.

MAINS TRANSFORMERS (new). Suitable for spot welding. Input 200-250 volts in steps of 10 volts. Output suitably tapped for a combination of either 2-4-6-8-10 or 12 volts at 50-70 amps., 87/6 each, carriage 7/6.

EX-NAVAL ROTARY CONVERTERS. 110 volts D.C. input. Output 230 volts A.C., 50 cycles, 1 phase, 250 watts, capable of 50 per cent. overload, weight 100 lb., price £10/10/- each, carriage forward.

ELECTRIC LIGHT QUARTERLY TYPE CHECK METERS. All for 200-250 volts A.C., 50 cycles, 1 phase, 5 amp. load, 17/6 each, post 1/6; 10 amp., 21/- each, post 1/6; 20 amp. load, 25/- each, post 1/6.

MAINS TRANSFORMERS (new). 200-250 volts input, in steps of 10 volts. Output 0-6-12-24 volts 6 amps., 37/6 each, post 1/6. Another as above, but 10-12 amps., 48/6 each, post 1/6. Another as above, but 25-30 amps., 70/- each, carriage 1/6. Another, input as above, output 0.3-18-30-36 volts 6 amps., 42/6 each, post 1/6.

PRE-PAYMENT 1/- SLOT METERS, by well-known makers, 200-250 volt A.C., 50 cycles, 1 phase, 20 amp. load. Set rating of 8d. or 9d. per unit, bakelite case, 37/6 each (for shop clients only).

EX-R.A.F. ROTARY CONVERTERS. 24 volts D.C., input 50 volts, 50 cycles, 1 phase at 450 watts output, complete with step-up transformer 50 to 230 volts, £9/10/- each, carriage 10/-.

EX-U.S.A. W.D. ROTARY TRANSFORMERS, 12 volts D.C. input, 500 volts, 50 m/amps; 275 volts, 100 m/amps. D.C. output, complete with smoothing switches, fuses, etc., as new, 17/6 each, carriage 2/6, can be run on 6 volts giving half the stated output.

EX-R.A.F. ROTARY CONVERTORS, 12 volts D.C. input, 230 volts, 100 watts, 50 cycles, 1 phase A.C. output, £4/10/- each, carriage 7/6.

OUTSTANDING OFFERS FOR EXPORT ONLY

U.S.A. Radio & Radar Equipment
RCA TRANSMITTERS, Type ET-4336-B, H, K, L.
Westinghouse AIRCRAFT TRANSMITTERS, Model GO-9.

TRANSMITTERS/RECEIVERS SCR-536.
TEST EQUIPMENT IE-46 (Signal Generators I-196-B,
Frequency Meters BC-906-D, Radio Receivers
BC-1066-B).

AN/TRC EQUIPMENT,
SCR-399.

RADAR Mk.26 (Models 3 and 4).
INTERGATORS-RESPONSORS BM-1 (and BN-1)
REPEATER-INDICATORS AN/APA-1.

RADAR INDICATING EQUIPMENT, Model VF.
AIRCRAFT RADAR EQUIPMENT AP5-3, 4 and 6.

TEST UNITS AN/UM.
GISHOLT-BALANCING METERING UNITS
(complete).

Spares (Radio & Radar—U.S.A.)
Full range of spares for AN/JAPN-3.
Spares for most models of U.S.A. Naval and Aircraft
RADAR UNITS.

Spares for most AMERICAN TRANSMITTERS.
Brand new Klystrons (RAYTHEON) 2 K-33.
CRYSTALS (for SCR-610, etc.)

Complete Operations Center AN/TTC-1
(Full installation for Wing Filter or Operations Room, or Combined
Filter-Fighter Control Area Operations Room.)

Power Units, Motor Generators, Dynamotors
and large quantities of various components

Aircraft Instruments and Accessories
Large selection of Bendix Instruments.
Aircraft Generators and Motor Assemblies.

Individual Test Certificates and A.I.D. Certificates can be supplied
upon request.

Enquiries to

BRITISH SAROZAL LTD.

(Export Branch)

1 BRISTOL HOUSE, SOUTHAMPTON ROW, LONDON, W.C.1

Telephone: HOLborn 6763/4/5 Cables: Sarozal, London

OVERSEAS BUYERS ARE CORDIALLY INVITED TO VISIT OUR
WAREHOUSES, SHOWROOMS AND LABORATORY.

C. MARKS & CO.

B38 COMMUNICATION RECEIVERS. By Marconi. A nine valve Superhet
with Coil Turret. 1 to 20 mc/s. in 4 bands. Sensitivity for 10 db. Sig/noise
ratio less than 1 μ volt on all bands. Built-in Output Meter and Filament
Transformer. Needs 200 v. D.C. (preferably stabilised) for immediate use.
Standard valves used, KTW81, KTW63, X66, KT61, etc. The greatest bargain
ever offered. 125 valves. Price 2/12, carr. paid 1/2.

RECEIVERS TTP1 161. Containing CV96, Grounded Grid Triode, 2 VR136
Pentodes (EF34) and VR137 (EC52) valves. A four-position coil turret. With
magnetic pawl and ratchet motor included. Covers 170 to 230 meg. 45 meg. IF
output. Outstanding value at 19/6 each, plus post 1/6.

AMPLIFIER UNIT TYPE A1271. Containing VR56, 500 ohm relay multi-
contact, mike and line valve transformer, potentiometers, resistors, condensers,
etc. In black metal box. As advertised at 16/-, price 8/6 each. Brand new
SELENIUM RECTIFIERS, HALF WAVE. 12 v. or 6 v. at 3 a. 10/6 each.
12 v. or 6 v. at 5 a. 12/6 each, 24 v. or 12 v. at 4 a. 15/6 each, 24 v. or 12 v. at
6 a. 18/6 each, 36 v. or 24 v. at 4 a. 18/6 each, 24 v. or 12 v. at 5 a. 32/6 each.

WAVE BRIDGE. 12 v. at 1 amp. 7/6 each, 24 v. or 12 v. at 5 a. 32/6 each,
24 v. or 12 v. at 10 a. 39/6 each. Please add 1/6 carr.

38 SETS WALKIE-TALKIE. 7.4 to 9 mc/s. Containing 4 VP23 valves, but
partly stripped by the Ministry of the Send/Rec., Switch and ATP4 valve.
These items are included to make a complete set. Price 25/-.

ACCUMULATORS. 10 a.H. 2 volt Lead Acid. Manufactured by Exide. Brand
new and boxed at 3/9 each, plus 1/6 post.

"NIFE" AGES. 2.5 v. 15 a.H. (Twin Cell) Nickel Alkali Type. Almost
Indestructible. In sealed but guaranteed serviceable condition. 6/6 each.
66/- per doz.

CONDENSERS. BY WELL-KNOWN MANUFACTURERS. 4 μ F 600 v. wkg.,
oil filled, 3/- each. 10 μ F Paper 450 v. wkg. at 3/6 each, 2 mfd. 3 kv. wkg. at
10/6 each. 1.25 μ F at 6 kv. 12/6 each. Bathub 1 μ F 600 v., .25 μ F 600 v.,
1 - 1 μ F 400 v. at 1/- each. Oil filled, .05 μ F 6 kv. at 5/6 each, .01 μ F 5 kv.
Tubular at 1/6 each. .01 μ F 4 kv. and .001 μ F 4 kv. (Bakelite), 9/- doz.

EARPIECES. 8.2 Ω and 1620 Ω . Types Nos. 13486, 12401 and 12443. All at
1/6 each, 15/6 doz., or 144/- per gross.

SLOW-MOTION DRIVES. 11 set types. Spiral calibration. New and un-
calibrated. Price 7/6 each.

POTENTIOMETERS. 100 K and 6 K. By De Jeun Amisco. High wattage
precision type. At 7/6 each, 1 meg. 2 bank at 2/6 each.

MAINS TRANSFORMERS. Ideal for test gear, tuners or small sets. When used
in power pack will give 200 v. at 50 m.a. D.C., 6.3 v. A.C. tapped 5 v. at 1.5 amp.
Amazing value at 7/6 each.

YALEY SWITCHES. Single pole 11 pos. 2 bank, 3 pole 3 pos. 3 bank, 2 pole
4 pos. 2 bank, at 1/6 each, plus 6d. post.

METAL RECTIFIERS. 200 v. at 40 m.a. Suitable for AC/DC Type power
packs. 2/6 ea.

VITREOUS RESISTORS (10W/9824) 150 watt 20 K. Individually boxed and
brand new. 2/6 each, 24/- doz.

VALVE BASES. 813 bases. Ceramic. Brand new 5/- each. VR92 3/6 doz.

JUMBO BASES. 4 pin ceramic, at 3/6 each.

BELLING 7-PIN PLUGS AND SOCKETS, at 2/- pair, or 18/- per doz. pairs.

IRON DUST CORED COILS. 1 in. dia. contain standard size core. 2/6 doz.

COLLINS MIKE TRANSFORMERS. Ratio 41:1. Potted. 5/- each.

MORSE KEYS. Army Type. Enclosed. 1/6 each, post 1/-.

MAINS DROPPERS. Standard makes, 2 and 3 amp, 3/6 each.

88, COMMERCIAL ST., NEWPORT, MON. Tele. 4711

also at 25, Wyndham Arcade, Cardiff

All mail orders and enquiries to Newport branch please

WALTON'S of WOLVERHAMPTON

The leading Midland dealers in ex-Government and other radio and
electrical equipment. We specialize in high grade goods at really
competitive prices. Prompt attention to all mail orders, large or
small. Special offer this month:—

8in. Heavy Duty P.M. SPEAKERS, brand new in maker's sealed
boxes. 25/-, post 1/-.

Boxes of assorted nuts, bolts, washers, etc., mainly B.A.,
approx. 1,000 items per box. 3/6 box, postage 1/-.

Rivets. 3/6 box, postage 9d.

Polythelene DIPOLE INSULATORS. 5/- each, postage 1/6.

HOLME MOSS DIPOLE AERIALS. 15/- each, carriage 2/6.

SUTTON COLDFIELD DIPOLE AERIALS. 15/- each, plus
carriage 2/6.

TELEVISION MASTS. 5ft. 6in. sections, 2in. o/d. 11ft. (2 secs.),
12/6, carriage 2/6. 22ft. (4 secs.), 22/6, carriage 3/6.

Send s.a.e. for special clearance list.

WALTON'S WIRELESS STORES

48 STAFFORD STREET, WOLVERHAMPTON

LYONS RADIO Ltd.

TEST METERS. Make yourself some useful test gear from the two
sensitive meter movements contained in VISUAL INDICATOR TYPE 3
as fully described in the September issue of "Wireless World."
PRICE 5/- each, postage 1/6 or 3 for 15/- post free.

ACCUMULATORS. 24 v. 11 amp-hour (at 5 hr. rate). Case size
8 x 7 $\frac{1}{2}$ x 7 $\frac{1}{2}$ ins. with terminal cover projecting on one side 3 $\frac{1}{2}$ ins. These
are in brand new unused condition manufactured by leading U.S.A.
makers. PRICE 52/6, carriage 10/6 (5/- returnable on crate).

OSCILLATOR UNITS TYPE 76. Simple signal generators providing
a test signal over a frequency range of 98 to 152 Mc. CW. or
MCW. Valves employed are one each of VR66 and VR67. H.T. required
for operation is about 60 v. D.C. and L.T. 6 v. or 6.3 v. A.C. or D.C.
Built in metal instrument cases approx. 9in. cube. In good working
order, tested before despatch. PRICE 55/-, carriage 3/6.

AUDIO HANDBOOK. Prepared to help constructors solve the
problems arising when a piece of equipment has been built but doesn't
work, particularly relating to audio amplifiers. PRICE 3/9, post paid.
L.T. MAINS TRANSFORMERS. Primary 200/250 v. 50 cps.
Secondaries: 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 v. at 2 amps.
total loading. Brand new and guaranteed. PRICE 18/6, post 1/6.

3, GOLDHAWK RD. (Dept. M.W.), SHEPHERDS BUSH, LONDON, W.12
Telephone: SHEpherds Bush 1729

HOLME MOSS CONVERSION

Type AC/4 Converter unit for use with Sutton Coldfield receivers.
Optimum picture detail and Sound reception without retuning or
alterations. Incorporates power supply unit, R.F. stage and the highly
successful double mixer stage ensuring freedom from noise and correct
reception of the new single side band transmitters: Price complete
with 5 valves, etc., 15 gns. On approval 7 days.

Holme Moss models of the type AC/3 neutralized triode Pre-
Amplifier are also available. A well designed and proved unit giving
the best possible results for 'Fringe' viewers. Our confidence in
the unit is revealed by our 7 days approval offer. C.O.D. if desired
or by arrangement through your Dealer. Illustrated leaflets and
details, etc., available on request.

SPENCER WEST QUAY WORKS, GT. YARMOUTH

Phone: Gt. Yarmouth 3009

POLYTHENE H. F. EQUIPMENT

(AMBYTHENE BRAND)

COIL FORMERS
CHOKES
STAND-OFFS
FEED-THROUGHS

Send for Particulars and Samples

AMPLEX APPLIANCES (KENT) LTD.

19, DARTMOUTH ROAD, HAYES, BROMLEY, KENT
(RAVensbourne 5531)

Wireless World Classified Advertisements

Rate 7/- for 2 lines or less and 3/8 for every additional line or part thereof, average lines 5 words. Box Numbers 2 words plus 1/-. (Address replies: Box 0000 c/o "Wireless World" Dorset House, Stamford St., London, S.E.1.) Trade discount details available on application. Press Day: January 1952 issue, Thursday, November 29th. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components which may be offered for sale through our columns carry no manufacturers' guarantee. Many of these components will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such components purchased.

NEW RECEIVERS AND AMPLIFIERS

BERNARD'S—Manufacturers of television, radio and amplifying equipment, can now offer good deliveries of hand-built equipment, let us quote you and save yourself £££££ by buying direct from actual manufacturers; 12 months' written guarantee; we supply complete television receivers; time-bases, vision strips, amplifiers 5-1,000 watts, radio receivers; quotations by return post.
BERNARD'S—295, Munster Rd., Fulham, S.W.6. [0097]

UNIVERSAL ELECTRONIC PRODUCTS, 36 Marylebone, High St., London, W.1. Welbeck 4058.

SPECIALISTS in the design and manufacture of high fidelity reproducing equipment from 5-100 watts for domestic or industrial purposes. Our new twin channel amplifier (type U.E.57) with independent bass and treble outputs, provides the most satisfying standard of reproduction we have yet experienced. It is now being demonstrated in our showrooms daily (we close Thursday 1 p.m., Saturday 4.30 p.m.), and we invite those who seek perfection from recorded music to hear this superb instrument. We also offer tuning units or complete chassis designed and constructed to individual requirements.

12 treble boost; £12/15; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [0065]

MIDLAND RADIO COIL PRODUCTS offer a service for the production of high quality amplifiers and radio equipment to specification; list of standard products is available; suppliers of audio and radio equipment to the Northamptonshire Education Authority.—Enquiries to 28, Winstantly Rd. in our showrooms, 1635.

J.R. ELECTRICAL & ELECTRONIC DEVELOPMENT, Ltd., Hubert St., Birmingham, 6 (Aston Cross 2440), the Midlands specialist manufacturers of high fidelity sound reproduction equipment, for the world-famous Williamson amplifier and associated accessories including tone control stages, loudspeaker crossover units, distortionless contrast expanders and radio feeders; send for details and prices. [0105]

TELRAD ELECTRONICS, 70, Church Rd., Upper Norwood, London, S.E.13.—Designers and manufacturers of Telrad quality amplifiers; established as the most outstanding value in high-quality amplifiers, thanks to faithful reproduction at unrivalled price, these unique amplifiers are the first choice of the enthusiast; built to satisfy the discriminating ear; bass and treble independent controls, providing widest possible variation to suit all recordings and varying acoustic properties of one room with another; full details on request.—Write, call or phone Livingstone 4879.

RECEIVERS, AMPLIFIERS—SURPLUS AND SECONDHAND

EDDYSTONE communications receiver model 740, good working order; £25.—Box 4956.

G.E.C. BRT.400B, communications receiver and 10in Golden Wharfedale July, 1951, perfect; £96 or near offer.—Box 4960. [7706]

SCOTT Philharmonic 30-valve fidelity set, 4-2,000 mtrs., in Warwick cabinet; £125.—A.C.S. 34, Widmore Rd., Bromley, Kent. [7736]

SPENCER WEST 3-valve A.C. D.C. pre-amplifier, Midland; new; £8/8, with valves.—George Hill, 7, Wharfedale Crescent, Tadcaster.

T23 Baird television, new tube, recently overhauled, but low vision gain; £30 or offer.—After 8 p.m., 8, Roseway, Turney Rd., S.E.21.

RUO 9-waveband feeder unit, 15 watt amplifier, twin Goodmans 12in speakers and Garrard RC65 changer in walnut cabinet; £85 or offer.—Box 4966. [7715]

HERO Rx's and coils in stock, also Amps EC3439, CR100 etc.—Requirements please to R.T. & I. Service 254, Grove Green Rd., London, E.11. Ley. 4986. [0053]

LOUDSPEAKERS—SURPLUS AND SECONDHAND

GOODMAN'S Axiom 12, unused, in original carton;—Box 496

BASS Reflex cabinet for 12in speaker, 1 1/2 in oak; 78/-.—Box 4969. [7724]



Partridge News

Pointers to PARTRIDGE PRECISION

TRANSFORMER SERVICE

● "Standard" and "to Specification" types available in over 100 Models in 5VA to 100kVA range.

● Available for EARLY DELIVERY.

● Wide Range of hermetically sealed types including the new inter-service approved type 'C' Admiralty type (as illustrated).

● ALL WILLIAMSON Amplifier components immediately available from stock.

● An advisory and design service for the production of "to Specification" types—this specialist facility is used by the B.B.C., the Post Office, Government Research Stations, and leading Industrial concerns.



PARTRIDGE TRANSFORMERS LTD

ROEBUCK ROAD, KINGSTON BY-PASS
TOLWORTH SURREY
Telephone: ELMbridge 6737-8

VOIGT unit and corner horn; £20.—144, Sidcup Hill, Sidcup, Kent. [7749]

BARKER natural reproducer No. 1484, 17749 new; £9 or nearest.—Box 4964. [7712]

GOODMANS Axiom 22, practically unobtainable, as new, boxed; £11.—Box 5017. [7716]

BARKER 148 model, £10/10, or with R.D. cabinet £21; perfect condition.—Snelgrove, 516 Canford Lane, Westbury-on-Trym, Bristol, Tel. 82940. [17774]

NEW TEST EQUIPMENT

TOROIDAL coils; your network problems at all frequencies can be solved by these versatile and increasingly popular inductors; harmonic selection and filtering, sideband suppression, admission; crossover networks; tele-metering; cuts of 50db within lincs at 50kcs possible; very high Q, low C allows tune over wide ranges; 25mH to 2.0H, many values from stock; decade boxes 0.1H to 0.4H for early delivery; also 05% silver mica condensers; on Govt. and G.P.O. lists. **BEL SOUND PRODUCTS** Co., Marlborough Yard London Archway, N.19 Tel. Arc. 5078.

TEST EQUIPMENT—SURPLUS AND SECONDHAND

COSSOR 339A D/E scope J tube, £26, or less tube £21; Recorder Minor ins. tester, 500-volt, £8, as new.—Box 5018. [7767]

MULLARD Master valve tester, complete with 640 cards, test valves, ohms, amps, volts, cap, in good working order; £25 or nearest offer.—Hugos, Tanning St., Lowry, Bristol. [7680]

MATEUR selling equipment at bargain prices, wavemeter, oscilloscopes, signal generators, receivers, etc.; send stamped addressed envelope for list.—Gifford, 22 Pembury Rd., Tonbridge.

A.S. new Taylor model 85A multi-test meter 20-100 p.v. £16; Taylor model 65C signal generator, £15.—Renfree, 86, Fitzharris Ave., Bournemouth. [7695]

SIGNAL generators, oscilloscopes, output meters valve voltmeters, frequency meters, multirange meters in stock, your enquiries are invited.—Requirements to R.T. & I. Service 254, Grove Green Rd London, E.11 Ley 4986

BC221 frequency meter (modulated), complete with mains unit, service manual, etc. new, one only, £40, callers preferred; Tinsley's condenser microphone tester, VHF receiver R1294, 500-3,000mc/s, as new, with manual. £15.—Haynsons, 14, St. Mary's, Bedford, Tel. 4568.

NEW DYNAMOS, MOTORS, ETC. BATTERY chargers, 2-6-12volts, lamp, a.c. mains operated, ammeter fitted, guaranteed; 52/6 (despatch 2/6)—Thames Valley Products, 28, Camden Ave., Farnham, [7654]

BATTERY chargers, 4 models, 2-6-12v, 1-2-4 amp D.C.; acy mains voltage; also larger types special transformers, chokes, test gear, interior car heaters, etc.—The Banner Electric Co., Ltd, Hoddeston, Hertford. [0122]

ALL types of rotating electrical machinery up to 20kva available, including rotary converters, rotary transformers, motors, petrol and diesel-engined generating plants, alternators and d.c. generators. We are also in a position to quote for power transformers; as actual manufacturers we will be glad to quote for any quantity for home or export.

DIESEL Electric generating plants, 3kva, 250v with push-button remote control, starting equipment, ready for use; £240

ROTARY transformers, input 20v d.c., outputs 6.5v d.c. and 300v d.c., permanent magnet field, 20/-; ditto, input 28v d.c. and 1,200V 70ma d.c. output; energised field, 35/-; ditto, input 12v d.c. output 500v, 90ma d.c., energised fields 35/-; reasonable delivery.

CHAS. F. WARD, Lordscroft Works Haverhill, Suffolk, Tel 253 [0039]

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND

PLEASE see "W.W." Nov., page 92, as only the following items can be supplied:—

NEW model diesel alternator plant, on steel frame, 230/150+32v 15amp d.c. Petters latest type A.V.I. engine, air- or water-cooled, alternator belt driven, self-energised, automatic voltage control by winding on stator, at 1,500-rpm, also a d.c. output for charging starter battery up to 15amps, battery can supply few lights when main plant is not in use, "start and stop" by remote control, "press-buttons," complete with heavy battery cables and charged heavy duty 24v 120amp/hr lighting and starter battery, engine covered by Petters' inspection service, free delivery 100 mls. London, £250; a few from stock, others good delivery; concrete beds supplied.

ALTERNATORS as fitted in above plant, 3k.v.a. £61 6k.v.a. £81, delivered; 3k.v.a. £66, 6k.v.a. £87/10, c.o.d. London Docks, kindly state direction of rotation at pulley end.

THE above are not surplus, but current products of British manufacturers.

6v BATTs., 100-125amp/hr. £5. del.; rotary converters, 24v d.c. to 250/150 80-100watts; switch, metal box, tested, £3/17/6 del.; shunt dyno 32v 9a. £6/5; with good, 90/- del.; sliding res. Zenith 20 16a, 50 10a, 19/6 del.; battery chargers, 12 and 24v, also H. flexible cable; see "W.W." August, p. 74.

PLEASE see displayed advert., page 113, for S.T.C. selenium rectifiers, terms c.w.o. proforma invoice, c.o.d. (post goods only).

T. W. PEARCE, 66, Great Percy St., W.C.1 (near Angel). [0014]



THOUGHTS ON THE AUDIO FAIR

The Audio Fair is an annual New York institution at which appears all that is best in the American world of sound reproduction. So far as we know we are the only British manufacturer appearing under his own colours. Some British audio products are sold in the U.S.A. through the medium of various distributors, but our distribution is done by ourselves for the simple reason that ever since we started in business so many years ago we have felt the necessity of preserving that personal touch which is so desirable in merchandise of the highest quality. The intervening Atlantic Ocean calls for no change in that policy.

Our speakers are used and very greatly appreciated all over the U.S.A., and our presence at the Audio Fair is not so much concerned with getting new business as with establishing personal contact with many of our friends whom we only know by correspondence as satisfied customers. But in addition H. A. Hartley has been invited to meet many technical bodies seriously interested in bettering sound reproduction technique. These invitations, so we gather, are the result of the performance of the 215 speaker as compared with the very expensive American units, and of his unusual but admittedly rational approach to and solution of the problems involved in the well-worn words "high-fidelity."

As to that, he may have something to tell the Americans, but he is also interested in the likelihood of the Americans having something to tell him. In art and science true internationalism does exist, and nothing but good can emerge from the experts of two nations getting together for mutual benefit. We foresee being able to make some very interesting additions to our range of high-fidelity products.

Our catalogue will be sent free on request (a 1/2d. stamp will be appreciated) to everyone who feels he has not yet got the last word in undistorted sound reproduction, and a request for this catalogue will result in supplements being posted as they appear. All who have already asked for lists will also receive this new information.

There will be no change in the 215 speaker. Its performance is so advanced that change is hardly necessary, and at £10.10.0 we cheerfully put it up against any other speaker at any price.

Send for your catalogue to-day, and don't forget that our now world-famous L.P. record service will bring you guaranteed mint copies of L.P. records at the same cost as buying them locally. We will even advise you on what not to buy, for our whole effort is concentrated on giving you the utmost satisfaction in every way.

Subscribers to our R.L.P. service will receive a complete L.P. review in a few weeks.

H. A. HARTLEY Co. Ltd.,
152, HAMMERSMITH ROAD, LONDON. W.6
Phone: RIV. 7387

TRANSMITTING EQUIPMENT
VALVES.—A quantity of 801A's and 830B's, new and boxed.—Offers to Box 4954.
TRO sets, complete with a valve, not guaranteed, 20/- post paid; trade enquiries invited.—Autorex, New Whittington, Chesterfield.
MAGSLIP transmitters from 10/-: ideal for remote control of radio apparatus, including Antenna direction indication; stamp for details.
ENGINEERING FACILITIES LTD., 29, Rea St., Birmingham, 5 [7507]

NEW GRAMOPHONE AND SOUND EQUIPMENT
FRITH RADIOCRAFT Ltd., offer from stock:—
SOPHONY-BAIRD magnetic tape recorders, complete in luxury portable case with m/c mixer; £58/5/6.
EDDYSTONE communication receivers; 740 £34/15. 750 £68.
PHILIPS 12-volt Motoradio model 574V, three only; at pre-bought price £29/6/4.
FULLIN series 100 multirange meters, 10,000 ohms per volt, 21 ranges; £1/7/1.
SKYWAY "Junior" amplifiers, 2XEL32 push-pull output, high impedance PD input only; £8/15.
SKYWAY "Baby Grand" amplifiers, 2X6V6 push-pull output, de luxe type with Woden "Potted" transformers, treble and bass controls, inputs for 50 and 500 mv; £14/14.
RECORDING tape EMI 65A, 65B or H60. 35/-: Scotch Boy (Durex), 35/-; Philips, £2: all 1,200 ft. reels; spare spools, 10/-.

RECORDING motors BSR SR1, 32/-; SR2, 25/-; FP10, 38/-; Collaro clockwise or anticlockwise, 42/-.
WHARFEDALE "Golden" 10in speakers, 3 or 15 ohms; £5/2/6.
W. B. SPEAKERS, 9in PM "Stentorian," 3 ohms; £1/16/9.
CELESTION speakers, 12in PM, 3 ohms; £4/5.
ACOS microphones, MIC 22/1 or 22/2, for floor or desk stand fitting, £6/6; table stands, 21/-; 3-section folding floor stand, £3/7/6.
COLLARO RC500 auto changers, 78 r.p.m., play ten 10in or 12in records unmixed, lightweight p.u. for "99" needles; £11/16/9.
EKCO moulded plastic speaker grille, 16 1/2in x 12in, cream or gold, entirely free from resonance; 6/6 plus 1/3 post; sample on request.
ESCUTCHEON moulding flexible cream plastic, 1/4-in U section; 1/6 per yard.

NEW type and scarce valves; EF37A 25/2, PZ30 21/6, DUB 21/6, ECL80 26/8.
FRITH RADIOCRAFT, Ltd., 69-71, Church Gate, Leicester, Tel. 58927. [0024]


WILLIAMSON tuner trf coils, pair mw or lw, very high Q 8/6, wound to your station choice 10/-.
FILTERS steep cut 7/12kes, pair high mu permalloy toroids with C in core, 70/-; low R crossover, L=5mH, ferramic core, each 45/-; 9Kcs whistle filter, toroidal, over -40db @ 180cps bandwidth, canned, 40/-; zero hum input transformers to order.
POTTED latest ferramic inductors, ultra high Q, optimum 7=200Kcs, trade supplied; no general list, please make specific inquiries.
BEL SOUND PRODUCTS Co., Marlborough Yr.1, London N.19, Arc 5078 [0187]

TAPE recorder motos, 230v a.c., powerful, quiet brand new, 13/11; post, etc., 1/1.—K. W. Logan, Westalley, Hitchin, Herts. [6469]
MAGNETIC tap; new high coercivity Emitape 35/- spool 1,200 feet tape decks, blank recording discs. 10in. 3/- from stock; full trade terms.

SOUND DISCS (SUPPLIES) LTD., 178 Bishop Rd., Southport, Lancs. Tel. 88153. [7765]
MAKE your own m.c. pick-up, first-grade instrument response to 14kc-11db; components supplied.—S.a.g. for details to Pollock, 51, Brooklawn Drive, Manchester, 20. [7689]
CINE-VOX disc recording equipments, type C7J for high-quality recordings from existing microphone equipment, price from 28gns; also available as a complete channel inclusive of mic., amplifier and playback equipment, at 70gns; type C7, for highest quality professional requirements—recorder mechanism at 48gns, or complete channel at 110gns; demonstrations arranged in London.

PLEASE write for details to K.T.S., Ltd., 60, Aylward Rd., London, S.W.20. (Liberty 2261.) Callers by appointment only. [0209]
MAGNETAPE recording panels designed for the connoisseur, 2 speeds 7.5 and 15 i.p.s., selected by 2-position switch, automatic braking, rewind, tape lifting and tensioning mechanism all interlocked to 3-position switch, simple to operate, no tape spills, no unclenching of tape for rewind, tape can be inched or shuttled in either direction with instantaneous stop and start for easy editing and cueing; erase and hi-fidelity record/play heads using full width track for low noise recording; frequency range 30 to over 12,000 c/s, panel size 19in x 12in in black perspex and is symmetrical in layout, heads and mechanism enclosed in moulded perspex cover; price £28.—Stamp for details to Electromechs, Euston Chambers, Morecambe, Lancs. [7615]

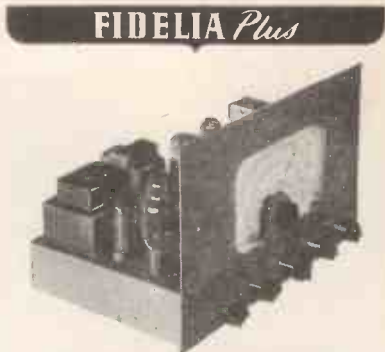GRAMOPHONE AND SOUND EQUIPMENT
—SURPLUS AND SECONDHAND
BARGAIN, as new, Simon tape recorder; cost £60 accept—£45.—Box 4951. [7633]
EMITAPE type 65, used but perfect; £1 per £1,200ft reel. Wanted, high coercivity tape.—Box 4967. [7716]



FIDELIA Plus

The whole range of Fidelity receivers has variable selectivity; wide-range tone control circuit with separate Bass and Treble controls; audio response of 20-20,000 cycles; triode-operated output stages. The range includes: Fidelity Standard 7 valve model, £21/15/-; Fidelity Plus (illustrated above), £24/5/-; Fidelity De Luxe 9 valve model, with 7-watt push-pull output stage, £25/5/-; Fidelity Major 10 valve model, £31/10/-; Data sheets free on request.

By the time this copy appears, we should have moved our offices—please note our new address below. Our new "home" faces the main Brighton-Newhaven road. We shall be very pleased to demonstrate any of our equipment by appointment. This includes west ends, should you be visiting the coast, provided you let us know in advance.

ELECTRO Acoustic DEVELOPMENTS

2 Amburst Road, Telscombe Cliffs, Sussex

SOLONS FOR ESSENTIAL JOBS!

Use SOLONS for the jobs that matter—this modern precision tool makes soldering speedier, simpler and more reliable. 5 models: 65 watt with oval tapered and round pencil bit; 125 watt with oval tapered and round pencil bit; 240 watt with oval tapered bit; each with 6 feet 3-core Henley flexible. Voltage ranges from 100 to 250.

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.
51-53 Hatton Garden London, E.C.1

HENLEY SOLON ELECTRIC SOLDERING IRONS
FOR INDUSTRIAL USE

Write to Folder Y 10



DEPT. W.W. 18 TOTTENHAM CT. RD
LONDON, W.1. MUSEUM 4539/2453

MAINS TRANSFORMERS (all upright mounting):
Pri. 200-240 v., sec. 350-0-350 v. 80 mA., 0-4 v. 5 a., 6.3 v. 4 a., 0-4-5 v. 2 a. Price 21/-, plus 1/- post.
Pri. 200-240 v., sec. 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v., 30 v., 2 a. Price 19/6, plus 1/- post.
Pri. 200-240 v., sec. 250-0-250 v. 60 mA., 6.3 v. 3 a., 5 v. 2 a. Price 21/-, plus 1/- post.
Pri. 200-240 v., sec. 350-0-350 v. 80 mA., 6.3 v. 3 a., 5 v. 2 a. Price 27/6, plus 1/- post.
Pri. 200-240 v., sec. 250-0-250 v. 120 mA., 6.3 v. 7 a., 5 v. 3 a. Price 25/6, plus 1/- post.
Pri. 200-240 v., sec. 350-0-350 v. 120 mA., 6.3 v. 5 a., 5 v. 3 a. Price 37/6, plus 1/- post.
Pri. 200-240 v., sec. 300-0-300 v. 100 mA., 6.3 v. 3 a., 5 v. 2 a. Price 31/6, plus 1/- post.
Pri. 200-240 v., 6.3 v. 1.5 a. Price 7/6, plus 6d. post.
Pri. 200-230 v., 4 v. 2 a. Price 7/6, plus 6d. post.
40 Watt Auto Transformer 18/9
60 Watt Auto Transformer 18/9
75 Watt Auto Transformer 20/-
100 Watt Auto Transformer 22/6
Plus 1/- post.

CHOKES:
20 Hy. 10 mA. 1,000 ohms 5/6
50 Hy. 20 mA. 1,000 ohms 6/6
50 Hy. 30 mA. 1,000 ohms 6/6
15 Hy. 60 mA. 300 ohms 5/6
20 Hy. 60 mA. 500 ohms 9/6
10 Hy. 100 mA. 300 ohms 11/6
10 Hy. 150 mA. 200 ohms 15/-
15 Hy. 150 mA. 170 ohms 17/9
5 Hy. 250 mA. 80 ohms 18/-
Postage and packing, 9d. extra.

OUTPUT TRANSFORMERS:
Wharfedale OP3. Ratios, 30, 60 and 90: 1, at 7/-, Wharfedale type P. Ratios, 30, 60, 45 and 90: 1, at 8/6.
Wharfedale type GP8. Ratios, 12, 18, 24, 30, 36, 48, 60 and 72: 1, at 12/6.
Wharfedale Universal. Ratios 40 CT., 60 CT. and 80: 1 CT., at 14/6.
Wharfedale W.12. Ratios 15, 25 and 45: 1, 25/-, Post 9d. extra.
Midget-output. Ratio 42: 1 only, at 5/3, plus 3d. post.
60-1 Ratio Microphone Transformer, at 8/3, 1/- plus 6d. post.
100-1 Ratio Microphone Transformer, at 9/-, plus 6d. post.

WIREK model B wire recorder, good as new; £45 or near offer. Box 4991. [7755]
SIMPHONIC tape recorder, model 2A, almost new, with microphone and tape, perfect; £45 or nearest offer.—Box 4976. [7735]
DISC recorder, B.S.R., type DR33M and AR15C, ribbon and m/coil mics., stock of blanks, condition as new; £120.—Box 4959. [7670]
SCOPHONY-BAIRD magnetic type home recorder, three 1,200ft reels tape, complete, hardly used; £60.—Underwood, Hambleton, Bucks.
LOWTHER normal speed moving-coil pick-up and mu-metal transformer, perfect condition; £5.—Palmer, 8, Burnt Ash Hill, Lee, S.E.12.
20 Watt cinema type high fidelity P.A. horn speaker; 2 calibrated 4021C mics.; Goodman's R22 (20w) in baffle; Brown K phones; V.I. meter; large A.F., power transformers; hundreds other A.F. components; entire experimenter's stock; cheap.—Box 4510. [7598]

NEW COMPONENTS RECTIFIERS.

B.T.H. MERCURY vapour valve, type U 150/1,100 half-wave, capable of supplying d.c. output current of 150 milliamps at 1,000 volts Edison screw base, anode top cap, directly heated cathode, 2 volts at 5 amps; brand new, boxed in large quantity; price 10/- each; porcelain holder 2/6.

T. KIRKLAND & Co. (ENGINEERS), Ltd., 30, Lower Byrom St., Liverpool Rd., Deansgate, Manchester 5. [7599]

TELEVISION COILSETS (t.r.f.), EE PW view/mast, boxed, labelled.

BELSOL doped, with video chokes, Lond. 16/6. Midland 18/6, Holme Moss 21/-, Scotland 25/- (superhet), Wireless World, set of 20, 42/6 FT. set 12 to order; improved definition with 100 and 2.5Mc boost chokes 5/-; linearity/width controls 5/-.

WIRELESS WORLD chassis sets, line mains and blocking transformers, focus and defn. coils, EHT Westhef, treble units, this set remains among the leaders; formers, 1/4in. 1/4in polystyrene, tagged with cores, 10d. 1/-; latest 3/4in canned core formers, 2/- (wire and wdg data TV IF 2/6 extra); 1/4in poly rod, poly cement, 3/4in. 1/4in. 3/4in pax tube 1/6it; trade supplied.

BEL SOUND PRODUCTS Co., Marlborough Yard, London, Archway, N.19. [0183]
CRYSTAL microphone inserts (Cosmocord Mic-6); guaranteed brand new; 15/6 post free.

RADIO-AID, Ltd. (Retail Dept.), 29, Market St., Wretford. [0036]
500 Watt auto transformers, 110/230 tapped, in steel cases with carrying handle; 70/-, carr. 3/-.—Champion Products, 43, Uplands Way, N.21. [0100]

FM receiver, November issue, coilset of 6 pieces, ex to spec with induct. condensers 45/6, or majority of parts rec drilled chassis, coils, valves, £20; wobulator coils 7/6 pair.

BEL, Marlborough Yard, London, Archway, N.19.
YOU are bound to try an Osmer "Q" Coil-pack eventually and be delighted with the results, why not save time and money now? Send a stamp for free circuits and latest lists of coils, coilpacks, dials, etc., etc.
OSMOR RADIO PRODUCTS, Ltd. (Dept. W.C.A.), Borough Hill, Croydon, Surrey. (Tel. Croydon 5148/9.) [0046]

EVERYTHING for home constructor, chassis, E condensers, coils, valves, resistors, gram units, speakers, test gear, Viewmaster kits, etc., cash or H.P.; stamp for lists; quick service, no Govt. surplus offered.—James H. Martin & Co., BCM/EDHWA, London, W.C.1. [7699]
18/-—For this modest sum you can build a first-class 2-waveband plus gram superhet coil pack; all components supplied complete with full constructional details and suitable circuit diagram; stamp for illustrated catalogue of all our products. See also our display advertisement.

SUPACOILS, 98, Greenway Ave., London, E.17.
MINICOILS, midget size, 1in high, 1/4in diam., high Q, iron-cored, two-hole fixing, all coils wound on polystyrene formers, fitted 4-way tap-pans; ranges, LW, MW, SW (15-45m); types, H.P. AE, OSC; I.F. 455kc, 3/6 each; 465kc I.F. rejector 4/3 each; each coil boxed, with connection data, etc.

SUPERHET coilpack kits, comprising LW, MW, SW, AE and OSC coils, 4P 4w w/c switch, all padders and trimmers, 465kc I.F. rejector, 35/-.
"HIGH Q" TRF coil, LW and MW with reaction, inc. circuits, 5/-; replacement P.U. bobbins, 4,000Ω, 7/6; other valves stocked; midget TRF 3-station coilpack kits, 16/6; midget relays, 5,000Ω, coil, weight 1oz., 1/-; "Viewmaster" TV pre-amp kits, complete, inc. valve, 42/-, deliveries by return; all c.w.o.; trade supplied.

A. P. CRETTON (W), 349, Copnor Rd., Ports-mouth. [7397]

COMPONENTS—SURPLUS AND SECONDHAND

C. J. EMMS, Ltd.
RECTIFIERS, full wave bridge type, as follows:
1 amp, 12 or 6v, 5/6; 3 amp, 12 or 6v, 12/6;
1 amp, 12 or 6v, 15/-; 5 amp, 12 or 6v, 17/6;
1 amp, 6 or 12v, 22/6; 24v 1 amp, 11/-; 24v 3 amp, 25/-; 24v 4 amp, 30/-.
New sliding resistance sets from 1 to 4 amp 14Ω to 12 amp 1Ω, 7 in all, 30/- per carton.—268, Colherne Mews, London, S.W.10. Fre-mantle 8941. [0201]

PLESSEY new surplus 0005 three-ganged Trimmers tuning condensers, 8/6 each.—36, Wellington Rd., Wokingham. [7723]

CASE and chassis 1/6; 2v triodes, solder 1/-; 8/275, VCR7 holders 6d; crystals 3d; mikes, sd; mike trans. 1/-; phones, s.a.e. list, post extra.
ANNAKIN, 25, Ashfield Place, Otley, Yorks.

The House for Quick Delivery

The following Goods Ex-Stock.
Cash with Order, or C.O.D.

PLESSEY Multi-Speed Auto Record Changer, 10in.-12in. at 78 r.p.m., 10in.-12in. at 33 1/2 r.p.m., 7in. at 33 1/2 r.p.m., 7in. at 45 r.p.m. Virtually no needle changing. Simple in design and construction, extremely easy to operate.
Price including Tax at £23 13 0

B.S.R. G.U.4 Three-speed Gramophone Unit complete with lightweight Pick-up, and high fidelity crystal head.
Price including Tax at £9 19 11

G.E.C. Multi-beam Loudspeakers. Designed for use in Theatres, Assembly Halls, works, canteens, etc., where it is necessary to ensure that the full frequency range of speech and music is evenly distributed over a wide area. The Multi-beam Assembly has a bank of nine specially matched speaker units, are mounted so as to give a correct frequency balance over a horizontal angle of approximately 60 degrees. The effect when used with a good quality amplifying system is most impressive, being characterised by a clean and well maintained response in the upper register and a strong true base.

Provision is made on each assembly for wall or bracket mounting, or for chain suspension. The Multi-beam Speaker Assembly is sensitive to inputs of one or two watts, but a single assembly can accommodate inputs up to 30 watts without distress. High impedance matching is provided, the transformer having tapings at 750, 1,500, and 3,000 ohms, giving a power input of approx. 20, 10, and 5 watts from a 120-volt loudspeaker line. In halls of average dimensions it will usually be found that comprehensive sound coverage can be achieved with two assemblies, one each side of the stage, or with four assemblies if balcony and gallery areas exist.

- List Price £35 0 0
- New in original packing.
- My Price £10 10 0
- Carriage extra.
- DECCA** 3-speed Motors with Turntable, ready for mounting, at £7 3 4
- ACOS G.P.20**, complete with either Standard or L.P. Heads at £3 11 5
- ACOS** Heads, Standard or L.P. ... £2 3 4
- GARRARD** Standard Playing Unit, with Pick-up £6 3 2
- COLLARO** Standard Playing Unit, with Pick-up £6 10 6
- LEAK TL/12-watt "Point One"** Feedback Amplifier £28 7 0
- LEAK RC/PA/U** Remote Control Pre-Amplifier £9 9 0
- LEAK V.S.** Superhet Tuner Unit, complete with Valves £37 2 4


Send me your order for all your Wharfedale Speakers. Test Meters—Avo, Taylor, Advance. Valves. Components.

Please note these prices are subject to any increase by the makers due to rises in costs.

A. ERNEST BUCHAN (M.O. Dept.)

28, BELMONT ST., ABERDEEN Telephone 23579

CABINETS & CHASSIS

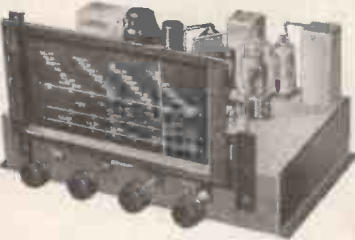

A.C. 5 valve 3 W/B Superhet Radiogram chassis. Absolutely complete kit of parts including detailed wiring diagram £10/15/0 Or fully wired and tested ... £12/10/0

CABINETS OF DISTINCTION

Send 6d. for our new illustrated cabinet catalogue.

AMPLIFIERS :

4 to 15 watts ... from £3/19/6

Full details from:—

LEWIS RADIO CO.

(Dept. 1251)

322 HIGH RD., WOOD GREEN, LONDON, N.22.

Callers to:—

120 GREEN LANES, PALMERS GREEN LONDON, N.13 (near Bowes Road)

Phone: Bowes Park 6064

RADIO CLEARANCE, Ltd.

TELEVISION! Set of 3 components, comprising line output trans., with E.H.T. winding to give 7 kV, using EY51 (heater winding for EY51 also included), and fitted with width control scanning coils, low impedance line and frame, focus coil (res. 10,000 Ω), current approx. 20 mA; the set of 3 for 42" plus 1/6 post, diagram of line trans. supplied.

MINIATURE iron cored coils, former size 1 1/2" x 3/4" adjustable core, set of 4 coils. M.W., AE and OSC. S.W., AE and OSC. 5/11, post 6d; mains dropping resistors for .15a valves, 920 Ω , tapped at 850 and 700 Ω , small size (3 1/2" x 1/2"), 2/3.

A.C./D.C. amplifiers, complete kit for construction of 20w, 8v amplifier by McMurdo, all first-class components by Partridge, Gardner, etc., valves 4XCL33; 2XEF57, 2XUR5C, black crinkle chassis and case, isolated from mains, and drilled, circuit diagram supplied, everything complete, £10/10/6, carr. paid.

PERSONAL receivers. 3 valve T.R.F. using IT4s, contained in handsome bakelite case with lift-up lid, size 7x5 1/2 x 5 1/2 in with lid closed, plastic carrying handle, frame AE in lid, these receivers cover the medium waveband and operate from self-contained dry tabs., standard types. W145 and U2, output to a pair of lightweight 'phones (H.R.) controls, SM tuning and reaction, opening lid switches on, supplied brand new with valves, batteries, 'phones, an ideal set for invalids, hosp. patients, etc., these receivers are not Govt. surplus and are offered ready to play; carr. paid 24/4

CLASSIC steel 24x14x1 1/2 in drilled 3 button base holes 1/9, 5x3x1 1/2, drilled 5 button base holes. 2/3; all. 17x9 1/2 x 2 1/2, drilled 7 int. octal and square, open ends 3/-. all. 14 1/2 x 10 x 2 1/2 drilled 10-BBA, 5 int. octal. ex. T.V. 4/3; primary 0-110-210 240v 50c/s, secs 300-0-300v 80ma. 4w 2a, 6.3v 2.5a, 15/6. Heater trans., auto wound 200/250v 50c/s to 6.3v 3a, 8/-; smoothing chokes, 5H, 200ma 1000 5/6, 8H 250ma 500 size 4x5x5 potted 10/6 post paid; electrolytics 32mf 350v card 2/-, 32-350v can 2/6, 16-450v can 2/6, 2-4 450v can, small 8/3, 8+4 275v 2/-, 4-450v 1/6; switch standard Yaxley type, 2p 4w 1b with shorting wafers 2/-; superhet coils 1 1/2 x 1 1/2, formers M. wave H.F., A.E. Osc, L, wave H.F., AE, Osc, 1/9 per coil; I.F. trans. 465kc/s 1 1/2 x 1 1/2 x 4in iron cored 8/- pair; meters 2 1/2 square bakelite cased, 0/5ma 6/6 0/50ma 7/6 0/300v d.c. with series res. 7/6, bakelite cased 2 1/2 in circular 0/200ma 9/6; Rotary power units type 104, p.m. rotary mounted on chassis with supp. input 12v d.c. output, 250v 60ma, 6.5v 2.5a d.c. 7/-, type 87 24v input, outputs as 104 6/6 post paid; and sockets, bakelite with keyway 5/-, 1/6 pair; extension speaker controls 10 Ω wire wound, 1/4 in spindle 9d; "Pye Strips" the well-known 45mc/s vision strips, brand new, less EF50s, with EA50, perfect condition, 39/6, plus 1/6 post; focus coils, low res., 200 Ω standard TV 8/6 can be used as alternative with kit, if required; 6 1/2 in loudspeakers, p.m. less trans., boxed, 12/6 post paid; Mansbridge conds., 4mf 1,000v wkg. 3/-; v.c. with sp switch long spindle 25k. 50k. 100k. 2m -/-.

SMALL size iron cored I.F.s, 465kc/s, size 1 1/2 x 1 1/2 x 2 1/2 in, 8/6 pair; frame aerials for personal sets, etc., medium wave, rectangular winding, size 6 1/2 x 4 1/2 x 1 1/2 in, wound round 4 wooden bobbins mounted at the corners of an all. plate, tabs for connector 2/6, 2 1/2 in output tabs, 5.000/3.750, 2/11; valveholders, Amphopol. int. octal 7d. ceramic int. octal 10d.

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188.

B ENDIX BC.221 frequency meters complete: £30.
S.C.R. 522 frequency 100-156 mcs complete transmitter/receiver, in new condition, with all tubes; £30.
EIMAC 100th transmitting valves; 55/-
TAYLOR T200 transmitting valves; £6.
THROAT microphones, new and boxed; 4/6.
PLUG and key assembly No. 3 with send/rec. switch; 5/6.
LEACH relay heavy duty 24 VDC, res. 250 ohms; 7/6.
CLARKE keying relays; 17/6.
PAPER condenser, 4mf 300v wkg., 6/6; paper condenser, 0.25mf 1,200v wkg., 4/-; paper condenser, 0.05 mf 0.05, 2,000v, 4/-.

SMALL porcelain jumbo, 4-pin bases; 4/- each.
LARGE porcelain jumbo, 4-pin bases; 6/6 each.
McEIROY-ADAMS MFG. GROUP, Ltd., 46, Greyhound Rd., Fulham, W.6. Tel. Fulham 1802. Cable: Hallcraft, London. F0196

OUR latest clearance list now available; send 6s. & 10-day for your copy.
WALTON'S WIRELESS STORES, 48, Stafford St., Wolverhampton. F0061

MAGSLIPS at 1/10 to 1/20 of list prices. huge stocks, please state requirements.
K LOGAN Westley, Hitchin, Herts. F6369
G. and T.V. console cabinets (pre-war).
R quality amplifier, r.f. unit, t.v. chassis for e.m. deflexion (professionally built); A.V.O. "W.W." from 1945. (London).—Box 4970.

RESISTANCES, vitreous, wirewound. 30-watt 800 ohm tapped, 2/-, 2,000 1/3, 15-watt 1,500 10d, 6-watt 50 200, 3,000, 5d; 3-watt 25, 1000 1500 4d; 2-watt 45, 1,000, 3d; sliding rheostats, 12 amp 1 ohm, 6/-; 6 amp 4 ohm, 7/6; meters, 0-15v MI, 5/-; 0-250 micro A (temperature scale), 15/-; sturdy motors, 24v 3 ph 50w (run 1ph with condenser), 5/-; rectifiers, FV (rv 1a, 5/6; 12v 5a, 7/6; 12v 8a, 23/-; LW 250v 200 mA, 12/6; other sizes available; rectangular bicycle transformers, suitable audio 800/3 ohms, or set of 6 give multitapped 20v 4a from mains 2/6; 3kw 50c transformers, various outputs, 25/-; various converters; details on request; technical queries welcomed; terms c.w.o. or c.o.d.; orders over 3/- carriage paid U.K.

PARKER, 68, Station Rd., Petersfield. T7557

DUKE & CO.

RADIO CONTROL UNIT, 12/6, incl. 3 1/2 in. tweeter speaker; 25 resist. wirewound; I.F. trans.; various Conds.; instr. fuse; 8 internal octals, ceramic, 3 Acorns ceramic, 7 v/controls. Relay, 2 co-ax. connectors, all usual parts, etc. Clean chassis and cabinet. Ideal amplifier or receiver, etc. Post 2/- extra.

CLOCKWORK MECHANISM. Just in, 8/6 each. Beautifully made in solid brass, small, but each piece engineering perfection. TYPE R.O.F. (B) 4551. Full instructions on manufacture of timepieces and photographic exposure timing units supplied free. Just the job for an amateur mechanic with ideas.

MIDGET RECEIVERS in bakelite plastic cabinet, walnut green or ivory. 4-valve T.R.F. Universal or A.C. for only 25/12/6. Assembled 35/- extra. New and improved circuits. THE ONLY set now available at this price. Post and packing 2/6.

SHORT-WAVE SUPERHET, 15/6. Number 19 set. receiver. FREE INSTRUCTIONS for conversion to all-wave and circuit. Diagram incl. NOTE set with a little alteration makes first-class portable or car radio. I.F.'s 465. Post 2/- extra.

AERIALS, 200ft., on winch 2/9, or 12ft. in three sections 4ft. each, tubular copper-plated steel, 7/- only. Carr. 2/- extra. Also Bases for 12ft. Aerials, tough rubber, spring mounted, 1/6, post 1/2.

NEW SPEAKERS, 2 1/2 in. and 3 in., perfect, 16/6 with transformer, or less trans., 13/6.

MOTORS, 160-250 volts and 100-110 volts, 3,000 r.p.m. Approx. 1/16 h.p. Made by Croydon Manufacturing Co. Silent running, fan cooled, Universal shaft 1 1/2 x 5/16 in. Dimen. outside, 6in. x 4in. Ideal for sewing machines, hobbies, etc. 39/6.

NICKEL CHROME WIRE, 60 yd. spools of .014 wire for only 4/6, or 25 yds., .032 same price. These prices are a fraction of to-day's prices (if you can buy it).

T.V. INTERFERENCE SUPPRESSOR TRAP. This is a small ex-W.D. aerial interference suppressor, and has proved to be an efficient trap for most types of interference. Price 1/6.

INSTRUMENT STORAGE CASES. 1 1/2 in. laminated plywood, with heavy quality steel hinges and locking device, in as new condition, two sizes, large, 9in. x 9in. x 7 1/2 in., 3/6. Small, 7 1/2 in. x 6 1/2 in. x 6 1/2 in., 2/6. In metal, 10 1/2 in. x 8 1/2 in. x 5 1/2 in., with strap, 2/-, plus post. Money back guarantee. Cash with order, please, or C.O.D. Stamps ONLY for Lists.

Mail orders: 621 Romford Road, Manor Park, London, E.12. GRA. 6677

Retail Sales: 219 ILFORD LANE, ILFORD, ESSEX ILF. 0295

OPPORTUNITIES IN RADIO



Get this FREE Book!

'ENGINEERING OPPORTUNITIES' reveals how you can become technically qualified at home for a highly paid key-appointment in the vast Radio and Television Industry. In 144 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study courses in all branches of TELEVISION and RADIO, A.M. Brit. I.R.E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency, and General Wireless Courses.

We definitely Guarantee

"NO PASS—NO FEE"

If you're earning less than £14 a week this enlightening book is for you. Write for your copy today. It will be sent FREE and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



3888 SHAKESPEARE HOUSE, 17/19 STRATFORD PLACE, LONDON, W1



"DEMOBBED VALVES" MANUAL
2/9 POST FREE

giving equivalents of British and American Service and Cross Reference of Commercial types, with an appendix of B.V.A. Equivalents and comprehensive Price List. We have still some valves left at PRE-BUDGET rates which actually sold at the old

price. There is a space free for YOU on our mailing list.

EXPORT to all parts of the Commonwealth and beyond—safely packed, fully insured (no C.O.D.) and free of tax.

ELECTROLYTIC SUPER QUALITY CONDENSERS

Special offer
Cardboard tubular, wire ends, 500 v.

| | Dimensions | |
|---------------------|-----------------|-----|
| 8 mfd. 500 v. | 2 1/2" x 3 1/2" | 2/9 |
| 16 mfd. 500 v. | 2 1/2" x 3" | 3/6 |
| 20 mfd. 25 v. | 1 1/2" x 1 1/2" | 1/9 |
| 50 mfd. 50 v. | 1 1/2" x 1 1/2" | 2/- |

CANS, single hole fixing, screw ends:

| | | |
|--------------------------|-----------------|-----|
| 8 x 8 mfd. 500 v. | 2 1/2" x 1" | 5/6 |
| 8 x 16 mfd. 500 v. | 2 1/2" x 1" | 6/6 |
| 16 x 16 mfd. 500 v. | 2 1/2" x 1 1/2" | 8/- |

Postage extra.

GERMANIUM CRYSTALS as specified in "Wireless World" Spt., page 338, 4/6.

COILS, HH4, HH3, HH2, at 3/9 each. Capacitors, 10d. each.

HOLME MOSS VIEW MASTER TELEVISION MODEL C, 5/3, complete plans.

C.R.T. 3-inch E.M.I. Type 4/1. Brand new in cartons, 17/6, plus 2/6 post.

CONDENSER TESTERS and Rectifier Units. Plugs straight into A.C. mains, 200/240 v., and is indispensable for examination of condensers. Very slight and intermittent leakages which cannot be discovered by conventional instruments can be traced by this unit. Complete, 39/6. Post 1/-.

SERVICE SHEETS. The one you require enclosed if available in a dozen, our choice, 10/6.

ADCOLA 3/16in. DIA. BIT SOLDERING INSTRUMENT. Miniature type to meet every requirement for Radio, Television, etc., 22/6. Post 1/4.

FABRIC for speakers, 1 square foot, 4/-. **TAYLOR ON EASY TERMS.** EASY TERMS up to 10 months—and very near Cash Price on All TAYLOR METERS.

THE "Q-MAX" CHASSIS PUNCH.

| 1 1/2" | 1 1/4" | 1 1/8" | 1" | 3/4" | 1/2" |
|---------|--------|---------|------|---------|------|
| 10/6 | 11/6 | 13/6 | 16/6 | 27/6 | 21/- |
| Key 9d. | | Key 1/- | | Key 1/6 | |

JUNEERO PATENT MULTI-PURPOSE TOOL

It punches, bends, shears and threads. Specially designed for Model Making, Metal Working and Home Repairs, 20/-. With "Xakto" slide gauge, 27/6. **JUNEERO ENGRAVING TOOL**, for Metals, Plastics, etc. A.C. Model 12/6.



Just published: Our new complete illustrated 28 page catalogue, 5d. stamps. (Kindly mark envelope W.W.12)

RADIO BULLS VALVES
246 HIGH ST. HARLESDEN NW10

MEISSNER de luxe signal shifter, £20; Hall-crafter Skyrider Model 23, perfect. **EDDYSTONE** 640, 1145, transmitters, communication receivers in stock. Hammerlung Super Pro. H.R.O. Semors C.R. 100. A.R. 2810. A.R. 88L.F., etc. all in perfect order. R.1155 receivers in new condition; your enquiries are invited for rotary converters and electric motors, most sizes and types available from stock; motor alternators, 110v d.c. input 230v a.c., 50 cycles, 250 watt output, special clearance of F.H.P. electric motors, 35/-, 110v-250v a.c. **UNIVERSAL** a.c./d.c. motors, suitable for sewing machines, 40/- each; 12v-15v a.c./d.c. motors with extended spindle, suitable for models, etc., 9/5; 20 watt P.A. rack mounting amplifier, new and complete, with heavy duty a.c. power pack; 200/250v, PX25 P.P. output, £5/10, less valves; new moving coil microphones, hand type, heavy duty and complete with 12yd screened cable, £3/15; 20ft telescopic tubular T/V mast, 18/6 each; large selection of test equipment, multi-range meters, valve testers, signal generators, oscilloscopes, bridge meggers and meggers, etc., all at reasonable prices; hand bearing prismatic compasses with provision for battery in handle, perfect, 40/- each; very large stocks of transmitting valves, Klystron, of all types, send us your requirements; special offer of new, not ex-W.D., mains transformer, semi-shrouded 200/250v tapped primary, 250-0-250, 100ma, 5v 3amp, 6v 4amp, 20/- each; large stocks of L.T. transformers, special sizes and ratings wound to specification; auto-record changers in stock from £10/15; switchboard mounting voltmeters, ampmeters, various ranges a.c. and d.c. available at cheap prices to clear; large stocks of enamelled wire, 28 s.w.g., 18 and 20 s.w.g., D.S.G. No. 15 U.K. base, American valves available. Special offer, H.R.O. coils, 40/6 mfd and 160-430 k/f, 45/- each, quantity of Itz and nickel chrome wire available; type 74 indicator units, complete with tube, as new, £6 each; prices do not include postage; American Dingley transmitter, type SCR578, 500 k/v M.C.W. large stock electric exhaust fans, many types. Hallcrafter Sun, Sky-rider 5X28 in stock. Evershed bridge megger, 500v 1 1/2 kw. e.d.c. rotary converter, 220 d.c./230 a.c., complete with Igranic starter, £28. Large selection of American Pyranch high-voltage working condensers; 0-5 mfd meter rectifiers 6/3 ea.

SERVICE RADIO SPARES, 4, Lisle St., W.C.2. Gerrard 1734. 10188

SOUTHERN RADIO SUPPLY, Ltd., 11, Little Newport Street, London, W.C.2. See our displayed advertisement, page 1008.

CUPERTON RADIO, 74/6, Romford Rd., Manor Park, London, E.12. Tel. II. 1260. Est. 17 years. Latest bargains at the right price.

TWIN gang 0.0005 mfd T/cond., with fixing bracket, less trimmers, 7/6 ea.; standard size, 465 k/c.s., 1F/TS, 8/6 pair; 28-way ag strips, 1/- ea.; 5ma Bridge type meter rectifiers, 5/6 ea.

CARBON Vol/controls, 100K ohms, long spindle with S/P switch 2/6 each; 100K ohms v/cont., less switch, 1/3; 0.25 meg v/cont., less switch, 2/6 ea.; 50K ohms heavy duty carbon, v/cont. and also 20K ohm w/wound vol/cont., 2/3 ea.; 3 meg. carbon vol/cont., 7/4d ea.

L.F. CHOKES, 60 ma. 4/3 ea.; 4B.A. brass nickel-plated terminals, 2/3 doz.; electrolytic condensers, 32-32 mfd, 350v cap type, 5/9 ea.; 16-32 mfd, 350v small can cond., 4/9; 32 mfd 500v tub. cardboard wire-end cond., 5/6 ea.; 50 mfd 50v cardboard bias cond. or 50 mfd 12v meta. tag end cond., 1/- ea.


WESTINGHOUSE type metal rectifiers, 250 R.M.S., 65 mfd 5/6 g. g. coils, 6/4d x 4 1/2 in. lengths, in 3 colours, 3/6 ea.; metal escutcheon for same, 2/6; pointer, 10/-; drop-through type mains trans., primary 0-250v tapped on voltage panel, sec. 275-0-275v, 80 ma. 5/3v 2 amp, 5v 2 amp, 15/1; L.T. heater trans., 0-200-230v, 6.3v 1.5 amp, 6/9 ea.; flat-type mains dropper tapped 200-250v, 630 ohm, at 0.2 amp 1/6 ea.; valve holders, moulder, BTG v/hdrs., 10d ea.; int/ota amp. type, 7d ea.; 2-pole, 2-way small rotary switches, 8d ea.; 4-pole, 3-way small, with medium spindle, 2/11 ea.; 0.001 mfd 600v tub. cardboard cond., 2/6 doz.

MANY other bargain lines in stock; let us quote you.

TERMS: c.w.o., no e.o.d.; send 6d extra for postage orders under £5; 2 1/2d s.a.e. all enquiries and list. 10021

G. A. RYALL, "Utopia," Mayfield Rd., Herne Bay, Kent, offers post free bargains, all new or as new; switches, standard Vaxley type, 3B, 2P, 9w, 1/8; 2B, SP, 6w, 1/6; smaller type, 3B, 2P, 6w, total 5P, only 2/4; miniature instrument switch circular, SB, 2P, 6w, 1/6; one type 2B, 3w 3P., coloured high voltage leads, 2/-; and one type soldered tag, 2B, 4w, total 5P, having one double bank, 1/6; Paxolin special offer quarter inch 12in x 8in, 3/9; meters, brand new, in makers' boxes, British made, 2 1/2 in (3 1/2 in) overall, 0-30ma, circular flush with front fixing and 2in square front voltmeter, 0-300v FSD, 1ma, and square front 2in 0-5ma fine opening by best maker, all 6/9 each; high resistance headphones with good type microphone, padded double headbands, and sponge type ear-caps, all wired into large 4-cleft plug as per R.A.F. adverts, 8/10, as new; four resistance panels with thirty 1/4-1/2-1-2 watt, colour coded carbon resistors, best makes at 4/6 lot; three 2in high stability vitreous resistances on panel with bolts for mtg. two 25,000 and one 150ohms, 1/9; pairs 25mfd 50v, 1/9; light twin cable, 3 pairs, 1/3; triple, 1/6; twin plug and jack, 1/4; triple, 1/6; twin screened, 7d; 7 pin lengths, 1/4; Bakelite toggle switches, 2P, ST., 1/3; 250v and 2P, DT, G.O., 1/9; miniature red lamp-holders, panel mtg., 12v bulb cap cover, brass, 1/9 complete. 10205

Armstrong
THE CHASSIS PEOPLE

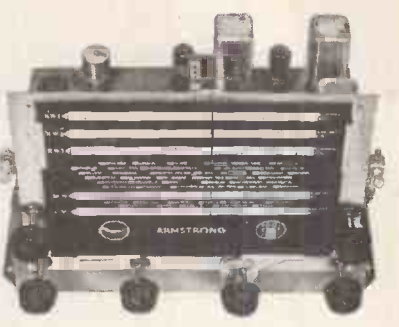

The prestige of Armstrong chassis is firmly based upon many years of constant endeavour to produce reliable and efficient receivers at an economical price. Our present range of chassis will even further advance the already high reputation enjoyed by our receivers. We are delighted to give demonstrations in our showroom and our illustrated catalogue will be sent on request.

MODEL EXP 125/3 14-VALVE ALL-WAVE RADIOGRAM CHASSIS

5 Wave Bands covering from 10.9 to 550m and 800 to 2,000m. R.F. Pre-Amplifier. Two i.F. Stages with Variable Se-selectivity. Bass and Treble Controls. 15-Watt Push-Pull Output. For A.C. Mains. £36.15.0. plus P.T.

MODEL RF 104 10-VALVE ALL-WAVE RADIO CHASSIS

4 Wave Bands. R.F. Pre-Amplifier Two i.F. Stages with Variable Selectivity. 10-Watt Push-Pull Output. For A.C. Mains. £24.0.0. plus P.T.

MODEL EXP 73 8-STAGE ALL-WAVE RADIO CHASSIS

3 Wave Bands. Variable Selectivity. Fly-Whew Tuning. 8-Watt Push-Pull Output with Negative Feed Back. For A.C. Mains. £17.15.0. plus P.T.

TELEVISION

The new **ARMSTRONG TELEVISION CHASSIS, model TV. 15**, incorporating a 12" C.R.T., is now available for distribution.
PRICE: 53 GUINEAS TAX PAID

Unfortunately, owing to the limited supply of material, the Chassis is at present available only for the London Service Area. Please send for full details.

ARMSTRONG WIRELESS & TELEVISION CO. LTD.
WALTERS ROAD, HOLLOWAY, LONDON, N.7
Telephone: NORTH 3213

THE MODERN BOOK CO.

Encyclopedia on Cathode Ray Oscilloscopes. By Rider and Usan. 75s. Postage free.

Mathematics for the Million. By L. Hogben. 20s. Postage 1/-.

Radio Circuits. By W. E. Miller. 5s. Postage 4d.

Radio Servicing Equipment. By E. J. G. Lewis. 25s. Postage 9d.

Television Receiving Equipment. By W. T. Cocking. 18s. Postage 6d.

Magnetic Recording. By S. J. Begun. 25s. Postage 9d.

Industrial High Vacuum. By J. R. Davy. 25s. Postage 9d.

Sound Reproduction. By G. A. Briggs. 10s. 6d. Postage 6d.

Radio Engineers' Handbook. By F. E. Terman, Sc.D. 50s. Postage 9d.

Radio Engineering. By E. K. Sandeman. Vol. 1. 45s. Vol. 2. 40s. Postage 1/-.

"Practical Wireless" Encyclopaedia. By F. J. Camm. 21s. Postage 9d.

Brimar Radio Valve and Teletube Manual No. 4. 5s. Postage 3d.

Osram Valve Manual. Part one by G.E.C. 5s. Postage 4d.

Radio Valve Data. Compiled by "Wireless World." 3s. 6d. Postage 3d.

We have the finest selection of British and American Radio Books. Complete list on application.

19-21 PRAED STREET
(Dept. W.12)
LONDON, W.2
PADdington 4185

WILCO ELECTRONICS

METAL RECTIFIERS.—12 v. 1 amp., 12/6; 6 v. 1 amp., 10/6; 48 v. 150 m/a., 10/-; All Bridge type. Post 1/-

ACCUMULATOR CHARGERS in black crackle case with fuses and meter. 6 and 12 volts at 4 amps. Bargain price, £4/19/6. Pkg. and carr., 5/-.

SLOW-MOTION DIALS. 6in. Scaled 0-100, reduction 200 to 1 or direct, ideal for wavemeters, signal generators, etc. Our price, while they last, 5/6 each, post 1/-.

"ELF" CIRCUIT BREAKER, 220 volts-2 amps., size 3 inches round, 10/6, post 1/-.

KLAXON GEARED MOTORS No. IK55B3-W7. Torque 15 lbs./in., r.p.m. 175. Motor r.p.m. 1,400 at 230 v. A.C. Split phase induction type, £10 each.

KLAXON CAPACITOR INDUCTION MOTORS with 4in. fan, 1/40 h.p., 200/240 v. A.C., 2,700 r.p.m. No. EM5CB2 with condenser, 55/- each.

24-VOLT D.C. MOTORS with double ended shaft 2in. x 3in., 8/6, postage 1/-.

THERMOSTAT SWITCH.—Bimetal type in sealed glass tube, 2 1/2in. x 3in. 30 deg. Cent. Ideal for Aquariums, Wax and Oil Baths, Gluepots, etc. Will control 1 amp. at 240 v., 5/- each.

THERMOSTAT. Satchwell 12in. stem, 0/250 v. A.C./D.C., 15 amp. 10 to 90 deg. Cent., 35/-.

CUTTER HEADS.—"Recording" high impedance. Amazing bargain at 55/- each. Post 1/-.

CUTTERS STYLII, 6/- per doz., large quantity available at special rates.

0/50 MICROAMMETER 2 1/2in. Flush type contained in Test Set 28. A very sensitive meter only 50/-.

AIRCRAFT CLOCKS with splendid 8-day jewelled movement. Flange type, made to stringent Govt. specification. Brand new, guaranteed. Ideal for car, study, bedroom, etc. Special offer, 65/- each. Post free.

204 LOWER ADDISCOMBE ROAD, CROYDON.

OVERSTOCKED, price slashed to below cost: P.M. speakers, 5in, 11/6; 8in, 12/-; 10in, 26/-; all 2-3ohms; O/trans., Pent, 3/6; H/duty, 5/6; 80ohms Co-ax., 12/- dozen yards; mains trans., 300-0-300, 49/2a, 100ma, 17/6; 450v condensers, 4mf, 1/6; 8, 2/6; 16, 2/9; 8X16, 4/-; 32X32, 6/3; 500Vw, 8mf, 3/-; 16, 4/3; 3-way tag strips, 5/- 100; hundreds other bargains; s.a.e. list.—Radio Unlimited, Elm Rd., London. E.17. Tel. Key 4813. [0062]

BRITISH SOUND RECORDING ASSOCIATION. MEMBERSHIP of the Association is essential to all actively engaged or keenly interested in high-quality sound recording and reproduction. The 1951-52 Lecture Season has commenced and an exceedingly interesting series of papers and lectures, many with demonstrations, has been arranged for the benefit of members. Additions have again been made to the publications of the Association and there are also the very special and exclusive test disks. Full information is contained in the latest Publications List, P.104, and this, together with the new brochure giving full information of the work of the Association and the benefits conferred by membership, with a Membership Application Form, may be obtained from the Membership Secretary at 48, Mount View Rd., North Chingford, London. E.4. England. [0119]

WANTED, B.S.R. mixer-recording control amplifier.—Box 497A, also L050A oscilloscope type 339A, also L050A oscilloscope.

LESLIE DIXON & Co., 214, Queenstown Rd., Battersea, S.W.8. Macaulay 2159. [0176]

ENAMEL wires, 24 to 30swg, toroidal cores, best only, bios, toroidal wdg machines, Bel, Marlborough Yard, N.19. Arc 5078. [0191]

WANTED, 6, 8 and 12 way Jones' plugs, sockets with or without shrouds; quote price per 1,000.—B.E.A., Ltd., Rugeley, Staffs.

WANTED, laboratory test equipment, including standard signal generator, watt meter, oscilloscope, bridges, recorders; send price and details to: HATFIELD INSTRUMENTS, 175, Uxbridge Rd., Hanwell, W.7. Tel. Ealing 0779. [0037]

WANTED, HRO colls. Rxs, etc. AR88s, BC348s, S27s, etc.—Details to R.T. & I. Service, 254, Grove Green Rd., London. E.11. Ley. 4986. [0163]

WANTED, RCA speech amplifiers, type MI-11220 J or K; offers, stating quantity and price, to PCA Radio, The Arches, Cambridge Grove, W.6. [0080]

WANTED, all types of radio equipment, test instruments, radio receivers, personal sets, television, components, etc.; call, write, send or phone.

MILLER'S RADIO, 38a, Newport Court, Charing Cross Rd., London. [7010]

WANTED, set manufacturers' or ex-Government radio equipment, large or small quantities of valves, electrolytics, speakers, meters, also components.

LOWE BROS. 199 Mile End Rd. London, E.1. Ste 2579. [16554]

WANTED, mild steel rod, freecutting, bright, 3/4in, 1/2in, 1/4in, 3/16in, and 1/8in diameters.—Mr. Livemore, L.M.K. Manufacturing Co. Ltd., Ealing 1858. [7645]

WANTED, BC-610 Hallicrafters, RCA ET-4356 transmitter, SX-23, AR-88, S-27, HRO receiver and spare parts for above; best price.—Write Box 864, c/o Spiers Service, 62, Centurion Rd., Brighton, Sussex. [0081]

WANTED, AN/AR-4 receiver, any units; any other good quality U.S. surplus radio and radar, tubes, test sets; laboratory equipment, etc.; give condition and price in first letter.—Littell Farhills, Box 26, Dayton 9, Ohio, U.S.A. [16346]

URGENTLY required for marine radio manufacturer, surplus 6-pin and 4-pin plug and sockets, type No. 10H/1291 plugs with 10H/403 sockets, and 10H/391 plugs with 10H/1599 sockets; original manufacturer's name or details of price and stock.—Woodsons, 76, Regent Quay, Aberdeen. [7699]

REPAIRS AND SERVICE

BERNARD'S. TELEVISION, radio and amplifier repairs, conversions and modifications; home-built receivers aligned; commercial radios rebuilt; send equipment with full instructions for quotation by return post; 12 months' guarantee on all work done.

BERNARD'S.—295, Munster Rd., Fulham, S.W.6. [0099]

MAINS transformers rewound, new transformers to any specification.

MOTOR rewinding and complete overhauls; first-class workmanship, fully guaranteed.

F.M. ELECTRIC Co., Ltd., Potters Bldgs., Warser Gate, Nottingham. Est. 1917. Tel. 3855.

LOUDSPEAKERS repaired promptly.—Model Loudspeaker Service, 34a, Bullingdon Rd., Oxford. [6819]

SPEAKER repairs, cones fitted, fields and clock coils wound, prompt service, guaranteed satisfaction.

L. S. REPAIR SERVICE, Pluckley, Ashford, Kent. [0110]

MAINS transformers rewound or constructed to any specification; prompt delivery.

Bede Transformer Co., Ltd., Bedesway, Bede Trading Estate, Jarrow. [3198]

REPAIRS.—E.H.T., mains and O.P. transformers, field coils and chokes; also armatures and motors; new transformers designed to any specification; all work fully guaranteed.

WILLESDEN TRANSFORMER Co., Ltd., 20a, Church Lane, Church Rd., N.W.10. Tel. Willesden 7093. [70076]




They all say "Thanks"

"... I have recently purchased your output transformer type 2B36B and find it perfection in itself for sound quality..." W: Ontario.

SAVAGE TRANSFORMERS LTD. NURSTEED ROAD • DEVIZES • WILTS
Tel.: Devizes 536

PHILIPS

FOR SOUND INSTALLATIONS



TRADE MARK, PHILIPS ELECTRICAL LTD.

All enquiries to:

PHILIPS ELECTRICAL LTD.
DEPT. ELA AMPLIFIERS

Century House • Shaftesbury Ave.
London • W.C.2.

OR

C. W. CAMERON LTD.
(Sole Distributors for Scotland)

57, Oswald Street • Glasgow • C.I.

(A870)

JOHN FARMER

24. **AMMETERS.** Hot wire, 0.9 amps. A.C./D.C., 3/4in. dia., 2 1/4in. scale, to fit 2 1/4in. dia. hole, flush panel mounting, brand new, boxed, 10/- each, post 6d. 90. **TOGGLE SWITCHES.** 250 v. 2 amp. single pole, panel mounting, 9d. each, post 3d.; 7/6 per doz., post 6d.; 72/- per gross, post 1/6. 124. **VOLTMETERS.** 0-100 volts, A.C., moving coil, internal rectifier, 1 m/a., scaled 0-20-40-60-80-100 with 1/10th sub-divisions, 2 1/2in. scale, flush panel mounting, new, 20/- each, post 6d. 138. "PYE" 45 Mc/s I.F. STRIPS, complete with six EF50's and one EA50, new, unused, 60/- each, post 1/6. 169. **ANTI-VIBRATION MOUNTINGS.** 10 lbs., centre part floats on 16 coiled springs, with hole to take up to 1/2in. bolt, base 2 1/2in. square, overall height 1 1/2in. Anodised steel. Ideal for all radio units. Brand new, post 1/6 for four, post 6d.; 4/- per doz., post 10d. 211. **SUPPRESSORS,** mains type, 4 section metal case with cover, dust cored coils and condensers, two input and output leads, size 4in. x 3 1/4in. x 1 1/4in., 3/6 each, post 10d. 215. **MASTER CONTACTORS** a high-grade clockwork movement running approx. 6/8 hours and providing 2 impulses per second, complete with suppressor, stop/start device, winding key, thermostat, etc. brand new, at fraction of original cost, 15/- each, post 1/-. 224. **RUBBER GROMMETS,** fit 1/4in. hole, admit up to 3/4in. cable, 8d. per doz., post 3d.; 6/- per gross, post 6d. 236. **THERMAL DELAY SWITCHES.** Ref. 10F/8077. Also useful as overload cut-out, periodic flasher, etc. 5.P. change-over robust platinum contacts, variable screw adjustment, normally set to cut out at 50 m/a., A.C., heater 50 ohms, bracket mounted, new, unused, 5/6 each, post 4d. 249. **AMPLIFIER UNITS,** type 165. Five valves (two VT52, two VR55, one VR55). Chassis mounted with protection frame size 7 1/2in. x 7 1/2in. x 4 1/2in., 20/- each, post 1/8. We have also Amplifier Units type 18, which are identical to the 165 and are the same price. 256. **ROTARY TRANSFORMERS,** type 93 (limited stock), brand new, boxed and tropicalised, 15/- each, post 1/8. 266. **MUIRHEAD VERNIER DRIVES,** type "D," ratio 40-1, marked 0-180 degrees, illuminated cursor, easy panel fitting for 1/4in. dia. shafts, new, 8/6 each, post 6d. 270. **CIRCUIT BREAKERS,** TYPE 10F/508. Electro-magnetic overload. In ironclad cases, size 6 1/2in. x 3 1/2in. x 2 1/2in., large ivory on/off switch, no rating details except pointer with 1.75 and 2-amp. A.C. graduations, 2 terminals for simple series connection, 12/6 each, post 1/-. 271. **POWER TRANSFORMERS,** single phase, 50 cycles, input 200-220-240 volts plus 10 v. Bakelite panel attached with secondary leads to U17 and RZ1/150 valve bases, also neg. 700 v. pos. D.C. terminations. Size 6 1/2in. x 6 1/2in. x 5 1/2in., new, in wooden cases, 35/- each, carriage 3/6. 272. "RECORD" BOND TESTERS, 0 to .1 ohms, 2 1/2in. scale, battery compartment, in brown bakelite cases, size 6 1/2in. x 6 1/2in. x 4 1/2in., with shoulder straps, new, unused, 20/- each, post 1/6. 277. **ELLIOT D.C. VOLT/AMMETERS,** type M.S.C. M/c meter, triple scale, 0-3, 0-30 and 0-300 v., complete with 4 massive high-grade shunts all 50 m.v. 0-3, 0-30, 0-300 and 0-600 amps., with resistance leads. In sectional baize-lined leather cases, size 1 1/2in. x 6in. x 5 1/2in. New, unused condition, £5/10/0 each, post 1/8. 280. **TEST LEADS,** consist of insulated panel mounting socket, plug fitted 1 yd. rubber flex with crocodile clip, 1/3 each, post 3d.; 12/- per doz., post 6d. 311. **TIME SWITCHES,** clockwork movement, setting dial up to 36 hours, fitted 3-pin 2-amp. plug, requires 3/32in. square winding key. Brand new, 30/- each, post 6d.

The above are a few items from our lists obtainable now from :

JOHN FARMER (DEPT. A.1.),
194 HARBORNE PARK RD.,
HARBORNE, B'HAM, 17

Tel. : HARborne 1309

METROPOLITAN RADIO SERVICE regret to advise that their transformer rewind service is temporarily suspended.—75, Kilburn Lane, London, W.10. 10130
"SERVICE with a smile"—Repairers of all types of British and American receivers; coil rewinds; American valves, spares, line cord.—F.R.I. Ltd., 22, Howland St., W.1. Museum 5675. 10112
ELECTRICAL measuring instruments of every make, multi or single range, repaired and standardised; prompt attention.—The Electrical Instrument Repair Service, 329, Kilburn Lane, London, W.9. Tel. Lad. 4168. 13715
24-HOUR service 6 months' guarantee, any 24 transformer rewind, mains outputs and i.f.s., etc.; all types of new transf., etc., supplied to specification; business heading or service card for trade prices.—Majestic Winding Co., 180, Windham Rd., Bournemouth. 16520

MISCELLANEOUS
EMIDICTA with desk mic., etc.; best offer secured.—Box 4974. 17732
METALWORKS; all types cabinets, chassis racks, etc., to your own specifications. **PHILPOTT'S METAL WORKS** Ltd. (G4B1). Chapman St., Loughborough. 10206
WALNUT radiogram cabinets, stamp leaflets.—Cabinetware, 1a, Heyes St., Blackburn. 13715
WALNUT radiogram cabinets, stamp details.—E. Wisker, 501, Hale End Rd., Highams Park, E.4. 16942

WALNUT radiogram and television cabinets, soundly constructed, stamp details.—R. Shaw, 69, Fairtop Rd., Leytonstone, E.11. 17435
EUREKA nichrome, silk and cotton covered copper wires wanted, top price paid.—Doyle, 144, St. John St., E.C.1. C/e 7723.
"PANL" the air drying black crackle finish, is applied like ordinary paint; details: L. Miller, 2, Kenton Park Cres., Kenton, Middx. 17435
NICKEL chrome wires, 65/15 quality gauges 32, 34, 35, 44, 46; 80/20 quality gauges 30, 31, 40.—Doyle, 144, St. John St., London, E.C.1. C/e 7723. 17435

MANUFACTURERS, wholesalers, please note; we can handle TV and home construction. TV coils wound; sliding quantity terms.—Bel. Marlborough Yard, N.19. Arc. 5078. 10190
IMPREGNATOR for wax or varnish 1 1/2in. dia., 1 1/4in. deep, arranged for heating to 120 degrees C; complete with pulsometer vacuum pump.—V.C.A., 505, Lordship Lane, London, S.E.22. 17627

ENGRAVING.—On all metals and plastics. Engrave name plates, panels, dials, instruction panels, advertising novelties etc., etc.; trade enquiries invited.—E. Reddish, 17, Standard St., New Kent Rd., S.E.1. Hop. 0505. 17632
ENGRAVING, amateurs and trace could take the opportunity of engraving problems in the future by setting in touch with A. G. Engraving, 13a, Windmill Rd., London, S.W.18. Brass, bronze, eroid, Perflex dials; one knob or retention equa'y entertained. 10034

ALLSCREWS Ltd. for B.A. screws, nuts washers studding, grub-screws, bolts, soldering tags, woodscrews, etc. plain or nickel, or cadmium plated, one-gross packets or large quantities, stamp for lists.—270a, King St., Mammersmith, W.6. Riv. 7762. 15426

EX-W.D. unused fluorescent lighting sets for 12 and 24 volts d.c. input, 230 v a.c. output, rotary converter, choke, P.F. condenser, leak transformer for 85 watt sodium lamps, the whole enclosed in metal box, £5 to clear.—A. J. Philpott, Fountain Sq., Fenton, Stoke-on-Trent. 17496

COPPER wires enamelled, tinned, Litz, cotton, silk covered, all gauges; B.A. screws, nuts, washers, soldering tags, eyelets, ebonite and laminated bakelite panels, tubes, coil formers; Tufnol rod; headphones, flexes, etc.; latest radio publications, full range available; list, s.a.e.; trade supplied.—Post Radio Supplies, 33, Bourne Street, London, W.1. 17435

FLUORESCENT 80watt chokes, tapped 200-250v a.c., 25/8; 80watt control ballast, wired, tested, tapped, with glow starter and lamp holders, 49/3; metal rectifiers, 12v amp. full-wave, 16/6; rotary converters, 12v d.c. in, giving 250v 50m.a., 6.3v 2 1/2amps, 8/9.—Malden Transformer Supplies, 200, Cambridge Rd., Kingston-on-Thames. 10038

TV-ITIS.—A complaint suffered by many who have no black screen; our conversion kit will change your ordinary television set into a black screen set; price 9/6 post free; will fit any size of set from 12in tube downwards; no suckers, no screws, no glue, and can be removed and replaced at any time; trade enquiries invited.—Unit Light Manufacturing Co., 19, Queen St., Blackpool. 17635

WORK WANTED
DRAUGHTING, tracing and photoprinting services; estimates free; contractors to the Ministry of Supply and the Admiralty for drawing and tracing work to their requirements and specifications; sub-contracting work of this nature undertaken.

DRAWING & TRACING Ltd., 456a, Ewell Rd., Tolworth, Surbiton, Tel. Elbridge 7406. 15975
INSTRUMENT company, established, with 4,000 sq ft space, male and female labour, experienced supervision, own machine shop and sheet-metal dept., seek assembly, repair or manufacture radio or electrical work, A.I.D. standard; conversant commercial radio service Padar, v.h.f. systems, etc.—Box 4316. 17518

SITUATIONS VACANT
EXPERIENCED radio and television engineer required; permanent position, good wages.—Apply Maxwell & Sons, Ltd., 45, Hill Rd., Wimbledon. 17656
RADIO and television engineer, experienced, all leading makes; able to drive; permanent position.—Collers (Estd. 1852), 429-431, Brixton Rd., S.W.9. 17634

DEMAND FOR CHRISTMAS



FOUR MARKS TO GO—JUST TIME TO ORDER AND GET DELIVERY OF YOUR BARKER SOUND UNIT TO DELIGHT YOU AT XMAS AND FOR MANY YEARS

The intrinsic value for money in a Barker unit is the highest obtainable, as a long term sound investment. For the most critical owner of first-class gear the 150 with its 17,000 lines/sq. cm. will be ideal. Close behind it is the famous 148a, used all over the world by high quality enthusiasts.

Both are full 12in. units with 90° corrugated linen cones and the unique dual drive with built-in crossover and feed-back. Both cover from 30 to over 15,000 cps. Both are so highly damped that there is no perceptible resonance anywhere. Both take 15 watts peak input.

The 150 has a slightly flatter and smoother middle register, with a better grip of transients owing to its big magnet; but many people still prefer the more forward effect given by the 148a. If you live abroad (Barker Units are to-day used in 26 countries) then the fact that 148a will go by post is important.

We supply through your radio dealer, or direct for cash or on hire purchase. Write NOW to :

BARKER NATURAL REPRODUCERS

3 NEWMAN YARD, LONDON, W.1

THE BRITISH NATIONAL RADIO SCHOOL

ESTD. 1940

NOW IN OUR TWELFTH
YEAR AND STILL

NO B.N.R.S. STUDENT HAS EVER FAILED

to pass his examination(s) after
completing our appropriate study
course.

INCENTIVE AND REWARD

is now assured so

AIM HIGH—GO FORWARD
with the B.N.R.S.

**A.M.Brit.I.R.E. and
CITY and Guilds Radio and
Telecommunications Exams., etc., etc.**

Introductory offer, six lessons with questions,
model answers and full coaching services, 30/-

Please mention this advert. and send for free
booklet, which gives details about all our study
courses, to:—

STUDIES DIRECTOR

BRITISH NATIONAL RADIO SCHOOL

68, ADDISCOMBE ROAD, CROYDON

Phone: Addiscombe 3341

"AUTOMAT" HOME CHARGERS, SELENIUM RECTIFIERS, CHARGER KITS

All New Goods with Full Guarantee



"AUTOMAT" HEAVY
DUTY HOME CHARGER,
for car or radio cells. Vir-
tually unbreakable. Se-
lениum rectification. Im-
pregnated transformer of
large size. Fine workman-
ship and appearance. 12
months' guarantee. For
A.C. mains only. Standard
model 6 v./12 v. 2 amp.
output, 8 1/2 lb. wt., 59/6,
post 2/-. Minor 1 amp.
model, wt. 7 lb., 50/-, post

2/-. 5 amp. truck or large car model, 26, carr. 5/-.
Minor model for 6 v. only at 2 amp., 52/6, post 2/-.
ELIMINATOR KIT. Transformer, selenium, h.t.
rect., 1:1 rect., 2 x 15 mfd. condensers for 120 v.
20/30 mA. eliminator with trickle charge, 35/-, or
with handsome steel case, 43/-, post 1/2.
FOOLPROOF CHARGER KITS. Standard model,
45 watts trans., triple tapped, large 12 v. 2 amp.
selenium rectifier, ballast/indicator bulb for 2 v., 6 v.,
12 v. charger, simple and foolproof, 38/6, post 1/4/-,
or with handsome steel case, screws grommets, 52/6.
Ditto kit, but 60-watt trans. and 12 v. 3 amp. rectifier.
45/-, weight 8 lb., or with case, 58/-, Junior kit, 6 v.
1.5 a. rect., 40 w. trans., ballast bulb, case, screws,
for 6 v. 1.5 a. charge, 42/-, wt. 7 1/2 lb., ditto but 6 v./12 v.,
46/-, post 1/2. Heavy duty kit for 6 v./12 v. 6 amps.
100 watt trans., 12 v. 6 amp. rectifier, giant finned
type, slider resistance 8 ohms, ammeter, 24/12/6,
post 3/4, 16 lb. Ditto but 4 amp. output max., 23/12/6,
post 1/8. Trickle charger kit, 2 v. 0.5 amp. rectifier
and high-grade transformer with ballast resistor,
12/6, post 6d.

SELENIUM RECTIFIERS. New stock not surplus,
12/15 v. 2 amp., 13/6; 6 v. 2 amp., 9/-, post 6d.
12 v. 1 amp., 12/6; 12 v. 3 amp., 15/9; 6 v. 4 amp.,
16/6; 12/15 v. 5 amp., 27/-, post 9d. Giant finned
type, 12 v. 6 amp., 35/-, post 1/3; 24 v. 4 amp., 54/6;
24 v. 6 amp., 67/-; 24 v. 2 amp., 27/6. Small space
H.T. rectifiers, selenium, 250 v. 60 mA., 7/6; 110 v./
135 v. 60 mA., 6/6; 250 v. 100 mA. bridge, 13/6. All
6d. extra postage. Small 40 mA. type for relays, 2/10.
"RENEWBAT," battery desulphator and conditioner
1/9, post 3d. Car size, 3/-, post 4d.

CHAMPION PRODUCTS
43 Uplands Way, London, N.21. Phone LAB 4457

ADMIRALTY.

APPLICATIONS are invited from engineering
electrical and ship draughtsmen for temporary
service in Admiralty Departments at Bath.
CANDIDATES must be British subjects of 21
years of age and upwards, who have had practical
workshop and drawing office experience.

SALARY will be assessed according to age qual-
ifications and experience within the range £320-
£545 per annum.
APPLICATIONS, giving age and details of techni-
cal qualifications, apprenticeship (or equiva-
lents) workshop and drawing office experience,
should be sent to Admiralty (O.E. II, Room 88),
Empire Hotel, Bath. Candidates required for
interview will be advised within two weeks of
receipt of application. 16952

ADMIRALTY.

TEMPORARY assistant overseers experienced in
electrical engineering techniques are re-
quired for temporary service in the overseer's
service of the electrical engineering dept.,
Admiralty; vacancies exist at London, Belfast,
Birmingham, Birkenhead, Barrow, Bishop
 Auckland, Hull, Leeds, Liverpool, Manchester,
Newcastle and Sheffield; candidates must be
British subjects of 21 years of age and upwards
who have served an apprenticeship or had
equivalent practical workshop experience and
possess some technical qualifications.
SALARY will be assessed according to age, qual-
ifications and experience on a range with a Lon-
don maximum of £675 p.a.; for candidates of
30 years of age salary will normally be related
directly to that age, £370 p.a. (London) and for
younger candidates will be approximately £20
p.a. less than the age 30 rate for each year of age
they are under 30.

THE London rates are reduced from £10 to £15
p.a. at Belfast, Birmingham, Birkenhead, Hull,
Leeds, Liverpool, Manchester, Newcastle and
Sheffield, and by from £20 to £30 p.a. at other
towns in the provinces.

APPLICATIONS, stating age, details of techni-
cal qualifications and apprenticeship (or equiva-
lents) and workshop experience, should be sent to
the Admiralty, Empire Hotel, (O.E. II, Room 83),
Bath; candidates will be interviewed locally as
soon as possible after receipt of their applica-
tions. 17770

GOLDEN opportunity.

SMALL, growing, electronic laboratory and
manufacturing plant on eastern United States
coast requires several degree engineers in elec-
tronics, at least five years' experience in radar
or communications systems preferred; plant now
employs 500 personnel; salaries extremely good;
contract for one year renewable by both parties;
fare paid to States and return after one year if
not satisfactory; give complete resume and en-
close recent snapshot.—Box 4972. 17728

UNIVERSITY OF DURHAM.

KING'S College, Newcastle-upon-Tyne.
TECHNICIAN required in the Department of
Agricultural Engineering for work on electronic
stress measurement and other instrumentation.
Candidates should have considerable telecom-
munication experience or experience of compar-
able stress measurement techniques; they should
also either hold Telecommunications Certificates
1, 2 and 3, or have completed the Armament
Artificer (Telemach or Radar) or an equivalent
course.

SALARY on Grade C (£375×£15 to £435).
APPLICATIONS should be addressed to the Pro-
fessor of Agricultural Engineering so as to reach
him not later than ten days from the appearance
of this advertisement.

G. R. HANSON,

Registrar of King's College.
Physicist or engineer (radar).

DOMINION Physical Laboratory, New Zealand.
APPLICATIONS are invited from suitably qual-
ified persons to fill the vacancy for a physicist or
engineer in the Radar Laboratory, Lower Hutt,
New Zealand.

COMMENCING salary, according to qualifications
and experience, will be up to £860 N.Z. per annum
plus 15% general wage increase.
APPLICANTS should possess first- or second-class
honours in physics or engineering. The appointee
will be required to work on decimetre-wave
apparatus in the field or radar laboratory. Pre-
vious experience in this type of work is desirable.
APPLICATION forms and conditions of appoint-
ment may be obtained from:—

THE High Commissioner for New Zealand, 415,
Strand, London, W.C.2. mentioning this paper
and quoting reference No. AS/64/107. Completed
applications should be lodged not later than the
8th December, 1951. 17717

THE Telecommunications Division of The
Plessey Company

REQUIRES for work in its laboratories at Ilford,
a limited number of experienced electronic
engineers.

THE vacancies are for work on long term pro-
jects in connection with important defence and
other contracts in the radio communication field.
THE successful applicants will be required to
take charge of portions of major projects under
the direction of the principal project engineers.
AGE is not important but the minimum qual-
ifications are either a degree in physics or
engineering or at least six years' experience of
advanced development work in radio communi-
cation; applicants should be of British birth.
THE posts are permanent and pensionable and
very adequate salaries are available for the right
men.

Write in confidence to the Personnel Manager,
The Plessey Co., Ltd., Ilford, Essex, marking
letter "A" for the attention of the Chief Engineer.
—Telecommunications Engineering Laboratories."

A Variety of Useful Electradix Bargains

HIGH GRADE COMMUNICATION RE-
CEIVERS A.R.88D £65, and 5.27 £38, carr. extra.
All in excellent condition.

TRANSFORMERS. B.T.H. 230 volts to 40
volts 2 amps. 25 x, 230 volts to 53 volts 15 amps., 6
volts 5 amps., 30 volts 1 amp., 60 volts 1 amp. £5.

Soil Warming Transformer 230 volts 50 c/s. input,
10-20-30 volts 1500 watts output, shrouded £4/10/-.

SUN LAMPS. Unused Hanovia Alpine Clinical
Model 110 volts on adjustable stand, Quartz
lamp 1/4 in. dia. 7 1/2 in. long housed in chrom. plated
reflector 12 in. x 12 in. The whole equipment
mounted on ball bearing casters for easy move-
ment £18/10/-. Auto Transformer for use on
230 volts A.C. £5.

FREQUENCY TUNING FORKS for operating
L.F. Phonic Motors, fork tines of mild steel,
constancy of frequency 1 in 2,000 with ordinary
room temperature changes £37/10/-. Low
Frequency Phonic Motor designed for use with the
above Fork £15/10/-. Send for descriptive
leaflet.

HOUSE OR OFFICE TELEPHONES.
Ex G.P.O. Wall type constructors parts compris-
ing Mag. bell in pol. wood case 8 in. x 6 in. x 3 in.
fitted Transformer, condenser, Switch hook and
contacts, Microphone, G.P.O. bell type receiver,
hand magnet Generators and wiring diagram
35/- per pair, carr. Eng. & Wales 5/- extra.

CONDENSERS. Paper 1 + 1 Mfd. 7 1/6 doz.,
hermetically sealed, 2 mfd. 400 VDC 10/6 doz.
Other sizes in stock, send for list.

CRYSTAL SETS. The "Lesdix" Festival
Model in black bakelite case, fitted variable con-
denser, wire wound coil, diode detector, phone
transformer and terminals, headphones with
headband cord and plug. All aerial tested 30/-,
postage 1/6.

Morse Keys, Buzzers, Vibrators, Thermostats,
Microphones, Relays, Switches, Dynamos, Motors,
Alternators, Lighting Plants, Battery Chargers,
etc. Send us your enquiries.

ELECTRADIX RADIOS

214 Queenstown Road, London, S.W.8

Telephone: MACaulay 2159

WANTED TRANSFORMER LAMINATIONS COPPER WIRE

TOP PRICES PAID

Write • Wire • Phone

PORCHESTER ELECTRICAL SUPPLY CO. LTD.

47 GERRARD ST., LONDON, W.1

Telephone: GERard 7676

Telegrams: Porcos, Lesquare, London



**A WINDOW WORTH
LOOKING INTO**

Television Coil Formers. With iron stud cores, Polystyrene, lin. x 3/16 in. with single hole 6ba fixing, 6d. each, 5/6 per dozen.

Television. Amplifiers, type 208a, 45 Mc/s. can be rewound for 56 Mc/s complete with 2 EF50 valves, 14/6 each.

Television. .1 mfd. high voltage Condensers, Mansbridge type, 5,000 volt, "NO TROUBLE," very limited number now left, 2/- each.

Television. EF50 (VR91). Boxed, brand new, 7/6 each.

Television. Diode Holders, 3d. each. Cradle type, 6d., ditto Polystyrene, 8d. each.

Television. High voltage Pots. Ex-W.D., most sizes available, 1/9 each.

Television. Wire wound Pots., from 1 ohm to 50K, 2/- each.

Television Dural Aerial Masts, 7 feet long, ideal for making your own aerial, 4/6 each.

Television Transformers. 230 volt primary, secondary 1,800 volts, 20 M/a, 22/6 each. Ex-W.D., not rubbish.

Television. Chassis. 4 stage. EF50 and diode holders mounted with coils and coupling condensers and resistors, each stage separately screened, wonderful bargain, 8/6 each.

Aerial Coupling Units, with silver plated tank coil, 3in. in diameter with 37 turns of 12 SWG, complete with 0-1 amp. thermometer, brand new, 14/6 each. The coils have a variable selector with dial.

Meters. Thermo 0-350 M/as 2in. round flush mounting, brand new, 5/6 each.

Meters. 0-1 1/2 M/a 2in. round flush mounting Brand new and boxed, 6/6 each.

Auto Transformer. Ex-W.D. 100/250 volt at 100 watts, 15/6 each.

Micro Switches. Several types available, large stocks, please let us have your requirements.

Ex-W.D. 2 Valve Battery Amplifiers. Complete with 2 volt driver and Q.P.P. output valve, brand new. Ideal for Mic. or Gramo, 12/6, valves alone are worth this.

Switch. Suitable for "Williamson," single pole 8 way 5 bank, 3/6 each. Limited number only.

Rectifiers. LT 12 volt 1 1/2 amp., bridge, 10/6 each.

Rectifiers. LT 6 volt 1 amp., 4/6 each.

Cable. Heavy duty twin, ideal for garage extension. Ex-W.D., 1/- per yard, worth double, minimum 12 yards.

Special Offer. Condensers. 16 x 16 x 16 mfd., 450 volt working, brand new, 3/6 each.

Amplifiers Type A1271. With new VR56, also 400 ohm relay 4M 2B, with host of useful spare condensers, volume control and resistors, 9/6 each.

Open all day Saturday,

G. W. SMITH & CO.

(RADIO) LTD

3, LISLE STREET, LONDON, W.C.2

Telephone : GERrard 8204/9155

CROWN AGENTS FOR THE COLONIES.

WIRELESS Station Superintendent required by the Government of Nigeria for the Posts and Telegraphs Department for one tour of 18 or 24 months in the first instance with prospect of permanency. Salary (including allowances) between £711 and £1,042 a year according to qualifications and experience. Outfit allowance £50. Free passage for officer and wife and assistance towards cost of children's passages or their maintenance in this country. Liberal leave on full salary. Candidates (under 40 years) must have had wide practical experience of modern radio techniques and equipment, in particular V.H.F. equipment, and preferably also V.H.F. multi-channel equipment. Preference will be given to candidates possessing a First Class Radio Telegraphy Operator's Certificate, Associate Membership of the British Institution of Radio Engineers, or equivalent. Apply at once by letter, stating age, full names in block letters and full particulars of qualifications and experience, and mentioning this paper, to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting, on letter, M.28927B. The Crown Agents cannot undertake to acknowledge all applications and will communicate only with applicants selected for further consideration.

ROYAL AIR FORCE, Education Branch.

APPLICATIONS are invited for permanent commissions (age limit 23-35 years) or for short service commissions for 3, 4 or 5 years from university graduates in electrical, electronic or radio engineering; candidates for permanent commissions should normally be first- or second-class honours graduates; starting point on the progressive pay scale depends on qualifications, experience and war service; an honours graduate aged 25 may receive pay of £529 a year with marriage allowance of £538; single officers receive free quarters accommodation; all officers draw rations in kind or a tax-free allowance of £60 a year in lieu; there is time promotion to squadron leader in which rank pay and marriage allowance rise to £1,232; promotion to higher rank is by selection; some short service officers will be selected annually for permanent commissions.

W.R.A.F. Vacancies exist in the Women's Royal Air Force for candidates with similar qualifications; conditions are as for men except that pay rates are about three-quarters of those for men.

FULL details including rates of retired pay and terminal grant for permanent officers and gratuities for short service officers may be obtained with application forms from Air Ministry (A.R.1), Kingsway, London, W.C.2 7637

CROWN AGENTS FOR THE COLONIES.

ASSISTANT Inspecting Engineer (Electronic) requires for duties in the United Kingdom to visit manufacturers to advise and assist in maintaining required standards and to carry out inspection and acceptance tests in connection with contracts covering a wide variety of radio and electronic products. Applicants should have served an apprenticeship with a firm manufacturing radio and associated equipment and have had subsequent experience on the manufacturing and technical side of the industry. They should preferably be corporate members of the Institution of Electrical Engineers or be in a position to obtain this within two years.

THE salary scale is £475-£225 to £650. The £475 minimum is linked to entry age at 25 with an addition of £25 for each year above that age up to £600. Extra duty allowance of 8% of annual salary is also payable at present. Travelling expenses and/or car mileage allowance, with appropriate subsistence allowances, are paid.

ENGAGEMENT will be on unestablished terms with a prospect, after satisfactory service and as vacancies occur, of appointment to established and pensionable staff and promotion to a higher grade.

Apply at once by letter, stating age, full names in block letters, and full particulars of qualifications and experience and mentioning this paper to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting M.25691.B on both letter and envelope. The Crown Agents cannot undertake to acknowledge all applications and will communicate only with applicants selected for further consideration. 17631

CROWN AGENTS FOR THE COLONIES.

RADIO Officer required by the East Africa High Commission for the Director of Civil Aviation for one tour of 48 months in the first instance; commencing salary according to age and experience in scale £550 rising to £715 a year; cost of living allowance of 15% of salary; gratuity of 13 1/2% of total salary received is payable on satisfactory completion of service; outfit allowance £30; free passages; candidates under 40 should hold a first-class certificate of proficiency in radio telegraphy issued by the Ministry of Civil Aviation; or alternatively, hold the provisional aircraft W/T operators licence and have had not less than 1,000 hours flying experience in civil aircraft; apply at once by letter stating age, full names in block letters, and full particulars of qualifications and experience and mentioning this paper to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting M.25107.B, on both letter and envelope; the Crown Agents cannot undertake to acknowledge all applications and will communicate only with applicants selected for further consideration. 17703

EXPERIENCED TV radio engineer required for bench and outside service work, age 25-35 years, competent driver.—Direct Sales, 59-52, The Broadway, Stanmore Mddx. 17756



Introducing...
COIL PACK

Model 320

5-waveband coil unit.

A comprehensive pre-aligned assembly consisting of switch, complete set of aerial, H.F. and oscillator coils and all associated trimming and padding condensers for 5-waveband operation with tuned H.F. stage on all bands. All coils have dust iron cores for inductance adjustment. A six position switch is used with provision for pick up connections and H.F. muting on the sixth position. For use with any of the standard frequency changer valves (6K8, ECH35 etc.) and an I.F. frequency of 470 Kc.

Ranges : 1, 13-40. 2, 30-100, 3, 80-200. 4, 200-550. 5, 900-2000 metres.

All parts for the above can be supplied separately if required.

TELEVISION COMPONENTS

"Electronic Engineering"—

- Focus Coil
- Deflector Coils
- Line Output Transformer
- Deflector Coils and Line Output Transformers suitable for other Kits are also available.

I.F. TRANSFORMERS Iron Core Tuned 472Kc. Per pair, 15/-

We also manufacture:—

- 3- and 6-BANK TRIMMERS
- MAINS TRANSFORMERS
- OUTPUT TRANSFORMERS

ALL COMPONENTS ARE MANUFACTURED IN OUR OWN WORKS

**ALLEN
COMPONENTS LTD**

GROWN WORKS,
197, LOWER RICHMOND ROAD,
RICHMOND.

'Phone: Prospect 4463

ALPHA OFFERS:-

BELLING-LEE TYPE, 5-pin chassis mounting socket with flexible plug, 2/- each. 7-pin chassis mounting plug with flexible socket, 2/- each. 2 1/2 M.M. steevings, various colours, 2d. yard.

CONDENSERS. .001 mfd. 1,000 v., .25 mfd. 350 v., 4/- doz.; Standard output transformers, 4/6 each; .00035 midget two-gang with dust cover and trimmers, 9/- each; .3 amp. mains dropper. Vitreous Type, 717 ohms with tap at 600 ohms, 1/3 each; Focus units, R171, 12/6 each; 3-way mounting, mains transformer 200-220-240 v. Primary 350-0-350 v. 80 mA., 0-4-5 v. 2 amp. 0-4-6.3 v. 4 amps, 16/- each; VR92, 2/- each; B30 Holders, 3/6 doz.; VR137, 5/9; B90 Valve Holders, 6/- doz.; 1934 Minivatt 4-pin type, 3/- each. Resistors: 1 watt all insulated, well known makers; 20 ohms, 47 ohms, 270 ohms, 1,500 ohms, 5K ohms, 10K ohms, 30K ohms, 33K ohms, 330K ohms, 200 ohms, 1.8m ohms, some close tolerance, 3/6 doz.; 75 ohms co-axial cable, 1/2 yd. Microphone cable, stranded flex, lined copper screening, stout P.V.C. outer sheath, 1/- yd.

METAL RECTIFIERS, L.T. 12 volt 1 amp., 1/- each, L.T. 2 volt 1 amp., 5/- each. L.T. 12 volt 3 amp., 18/6 each. L.T. 12 volt 4 amp., 19/6 each. H.T. 300 volt 80 mA., 5/9 each. H.T. 350 volt 75 mA., 6/3 each. H.T. 250 volt 60 mA., 4/9 each.

CHASSIS. 4 sides, 16 S.W.G. Aluminium, 20" x 8" x 2 1/2", 9/6 each. Cad'm Plated Midget Chassis, Valve Holders, etc., etc., cut out ready, 1/- each.

TOGGLE SWITCHES, etc. 4 Pole on/off Rotary Toggle, 2/6 each. Single Pole Toggle, 1 hole fitting, with slotted dolly, 1/- each. Arrow Roller Type Switch with white or black handle, 5 amp., 1/6 each. A.B. Switch suitable for Hoover Vacuum Cleaners, 1/6 each.

The following have been removed from ex-Gov. equipment but guaranteed serviceable: Igranite Two-way Jack socket, 1/- each; two metal rectifiers mounted on brackets, 200 volts, 30 mA. each section, 4/- each. Wax dipped chassis mounting. Mains transformer, 350-0-350 v. 120 mA., 5 v. 3 amp. and 2.63 v. 3 amp. secs. 200/250 Primary, 25/6 each. B90 (EP50) Ceramic Valve Holders with Screw Retainer Rings, 10d. each. .01 mfd. 5KV. bakelite case tubular condensers, 1/8 each. .01 mfd. .5KV. tall can type, 2/- each. .02 mfd. 8KV. tall can type, 2/6 each. Wire wound Volume Controls, 5 ohms, 200 ohms, 1/- each. Carbon volume controls, 500 ohms, 10K ohms, 20K ohms, .00k ohms, 700K ohms, 1/- each. **POST ORDERS ONLY**, **W.O.O. O.O.D. POSTAGE EXTRA UNDER £2.** New list available. Send 3d. stamp.

ALPHA RADIO SUPPLY CO.,
5/6, VINCES CHAMBERS,
VICTORIA SQUARE, LEEDS, 1.

MAGNETIC TAPE

Recording equipments and Components

MAGNETIC HEADS. A new series of 1/4-track totally enclosed heads are now offered having a wide frequency range and high efficiency. These heads are considered the best available today. The frequency response obtainable is better than 1 kc/s per inch of tape speed with simple correction equipment. Consistency is maintained by employing optical finishing techniques.

RECORD/REPRODUCE HEAD. Employs the smallest effective gap obtainable. Available in low impedance (2.4 mH. 15 ohms at 1 kc. approx.), and high impedance (200 mH. 1,250 ohms at 1 kc. approx.), Price £3/3-.

ERASE HEAD. Available in medium impedance. Price £3/1-.

TRANSFORMER. Suitable for low-impedance head to grid step-up. Price £1/1-.

TRANSFORMER. As above, but enclosed in 16 s.w.g. metal can. Price £2/1-.

OSCILLATOR COIL ASSEMBLY. Comprises high-Q coil and condenser tuned to 45 kcs. Specially designed to provide highly symmetrical sine wave output for low tape noise. Price 10/6.

OSCILLATOR UNIT. Constructed on small chassis suitable for sub-assembly, provides r.f. for erase and bias at 45 kcs. Requires 250 v. h.t. and 6.3 v. for operation. Complete with 6V6 valve. Price £3/1-.

AMPLIFIERS. A range of amplifiers have been developed specifically for use with tape. Please send for further details.

CABOT RADIO COMPANY LIMITED
Electronic Equipment Manufacturers
28, BEDMINSTER PARADE, BRISTOL, 3.
Telephone 64314.
Available also from:-
WILL DAY LTD., 19 LISLE ST., LONDON, W.C.2.

NO. 4 Central Workshops R.E.M.E., Donnington, Shropshire.
APPLICATIONS are required from candidates for technical electrical and electronic engineering grade appointments (salary scale up to approximately £800 per annum).
APPLICANTS must have experience of either design, manufacture or repair in one or more of the following branches: (a) electronic servo or computing equipment; (b) modern communication equipment; (c) electrical and electronic test equipment and measuring devices; (d) service radar equipment.
APPLICATIONS are also invited for other vacancies with prospects to transfer to technical grades for persons—male or female, age 18 upwards—having the following academic qualifications but little or no practical experience: national engineering certificate, higher national engineering certificate, higher school certificate.
ASSISTED travel facilities available in approximately a 40-mile radius of Donnington; staff midday meal service; 5-day week; annual entitlement of leave on starting, lower grades 16 days per annum, higher grades 20 days per annum for the technical vacancies.
APPLICANTS can apply in person or in writing in the first instance to C.E.P.O. No. 4 Central Workshops R.E.M.E., C.O.D., Donnington, Shropshire. 17576


PHYSICISTS required for interesting work in the following fields:-
(1) Application of new materials to electronic engineering.
(2) Cathode ray tube development.
(3) Properties of magnetic materials and applications to magnetic tape recording.
(4) Electronic engineering problems, including microwave applications.
THE posts are for permanent pensionable staff, and carry good salary and prospects. Applicants should have a sound theoretical training with a degree or equivalent and experience in one of these fields, and should write giving full details and quoting ED/35, to Personnel Department, E.M.I. Engineering Development, Hayes, Middx.
MANUFACTURERS of domestic radio and television in London, W. have two laboratory vacancies:
(A) **QUALIFIED** electrical or radio engineer (B.Sc. (Eng.) preferred); experience not essential.
(b) **LABORATORY** assistant; some experience required; an evening class student could leave early once or twice a week.
BOTH these will be supervised by an experienced engineer.

THE laboratory carries out design, development and testing of a wide range of miscellaneous duties; versatility, manual dexterity and some small knowledge of draughtsmanship are an advantage to applicants; write stating qualifications, experience & salary reqd.—Box 4973, 17731
TELEVISION and radio engineer urgently required, good refs. essential (Cobham, Surrey area)—Box 4977, 17743
RADIO and television retail manager required. A good salary to capable man.—Polchar's, 85, Rushey Green, S.E.6. Htt. 2134, 17742
E.M.I. ENGINEERING DEVELOPMENT, LTD. offer interesting and progressive positions connected with the development of:-
(a) Small electric motors, and their application to gramophone equipment.
(b) Radio transformers and other components.
(c) Stabilised power packs for airborne equipment.

QUALIFICATIONS: age 23-28, training in physics or engineering, experience in the above field an advantage; salary according to age and qualifications; applications should be sent to Personnel Department (ED/53), E.M.I. Engineering Development, Ltd., Hayes, Middx.
THE following vacancies exist in the design department of a company operating a large number of wire broadcasting systems:
1. **SENIOR** engineer to take charge of radio frequency section; must have a degree and have had at least three years' practical experience of television design.
SALARY: £800 to £1,000 per annum, according to experience.
2. **JUNIOR** engineers age 20 to 25 with degree or graduateship of I.E.E. or I.R.E.
SALARY: £400 to £500 per annum.
3. **LABORATORY** assistants capable of wiring and testing radio equipment under supervision.
SALARY: 28 per week.—Please send full particulars to Box 4314. 17511

SERVICE Engineer required for television and radio relay. Successful applicant will receive television training. Apply Box 4945, 17625
EXPERIENCED engineers required to fill the following vacancies in the electronics laboratories of a company situated near London.
1. **DEPUTY** Section Leader of Microwave and R.F. Laboratory. Applicants should hold an honours degree or equivalent in either physics or maths plus some industrial experience.
2. **DEPUTY** Section Leader of Circuits Laboratory. Applicants should hold an honours degree or equivalent and have extensive experience of electronics generally and pulse techniques in particular.
3. **DESIGNER** Draughtsmen to work on light mechanical devices associated with electronics generally. Applicants should hold a Higher National Certificate or equivalent, preferably in mechanical engineering.
THESE posts qualify for the company's pension scheme. The work is both novel and interesting and involves the development of new techniques but not original research. Successful applicants will, after a probationary period, be expected to carry the full design responsibility of a particular project.
APPLY giving details of age, experience and salary required to:-
THE Personnel Department, Kelvin & Hughes, Ltd., New North Rd. Barking, Ilford, Essex.

POTENTIOMETERS

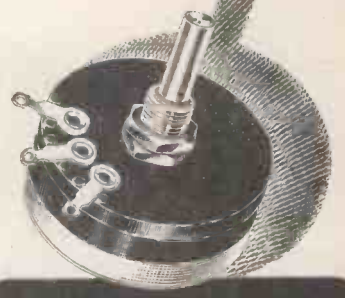

Wire-wound and Composition types. Single, Ganged, Tandem Units. Characteristics: linear, log., semi-log., non-inductive, etc. Full details on request.

RELIANCE

RELIANCE MFGG., CO. (SOUTHWARK), LTD.
SUTHERLAND ROAD, HIGHAM HILL,
WALTHAMSTOW, E.17.
Telephone: Larkwood 3245



JEWEL NEEDLES

★ **SAPPHIRE 9/11** including tax.
GEMTIPT straight and trailer for crystal and magnetic pick-ups. **SAPPHIRE** STYLUS for light weight pick-ups.
★ **DIAMOND 7 gns. plus 62/11 tax.**
To fit most light weight pick-ups.
Pick-ups with removable arnatures or fixed point, fitted at 27.13.11 plus 65/11 tax; L.P. at 28.14.11 plus 74/11 tax.
These unique needles are unimpaired by years of use. 90 times harder than sapphire and more shock-proof.
STARR NEEDLES are stocked by Webb's Radio, Keith Prowse, Quality Mart and other good dealers. In cases of difficulty write direct.

STARR BRITISH PRODUCTS

8 DARTMOUTH PARK AVENUE,
LONDON, N.W.5 2nd. GULiver 1131
Export Enquiries:
General & Overseas Trading Corp., Ltd.,
6 Duke Street, St. James's London, S.W.1

SURPLUS Bargains

MANUFACTURERS' & BANKRUPT STOCKS LIMITED SUPPLIES ONLY

SUPPLIES ARE GETTING SHORT

-BUY NOW-


VISIT OUR SHOWROOM ALWAYS SOMETHING NEW

We can offer for immediate delivery

EX-W.D.

AERIALS
CAN ALSO BE USED AS
FISHING RODS

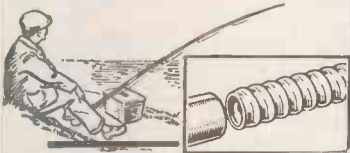12ft. Light Steel Aerials in 3 screw-in sections of 4ft.



Charging Control Boards with Auto. cut out, 3 amp. 220 v.

Yaxley Type Switches, Mansbridge Condensers (Oil filled and Jelly), Burgoyne Solder Guns, Tannoy Handmikes, Dinghy Transmitter Sets, Adhesive Tape, Coaxial Cable, Magnifying Lenses, Rubber Masks, Speakers, Coaxial Plugs and Sockets, Belling Fuse and Sockets, Vibrators, Belling Fuseholders, Meters, Mica Condensers, Electrolytic Condensers, Volume Controls, Valve Holders, Output Transformers, Mains Transformers, Chokes, Headphones, Valves Type CV 101, etc., etc.

Receivers: R1155, 1355 and 184 Brand New in original cases. Dinghy Radio Transmitter SCR 578.

SPECIAL OFFER NOW AVAILABLE

—DIRECT FROM M.O.S. STORAGE AND STARTER BATTERIES



6 volt. 90 Amp. 15 plate "Reading" U.S.
6 volt. 100 Amp. 15 plate "Delco Remy"
6 volt. 140 Amp. 21 plate "Delco Remy"
12 volt. 9 plate.
12 volt. 14 Amp. In METAL CARRYING CASE.

All Brand New in original cases.

Your enquiries are invited

WHOLESALE AND EXPORT ONLY

For further bargains call at our Counter or write for NEW bulletin

RADIO MERCHANDISE COMPANY LIMITED

65, Farringdon Road, London, E.C.1
Telephone: HOLborn 6377 Quote Dept. W.W.

YOUNG man (20-25), with good A.F. and mech. knowledge. for mobile projectionist/service engineer; clean licence; perm. post.

JOHN KING (FILMS) Ltd., 7-9, Centworth St., 1 mile Baker St. Stn. Welbeck, 1157. (7524)

BUSH RADIO, Ltd., require a number of engineers and physicists for new research and development laboratories which are being formed at Plymouth.

(a) A QUALIFIED senior engineer for a responsible position. The applicant should have a university degree in physics or electrical engineering, or have passed the graduateship examination of the I.E.E. He will be required to make preliminary theoretical investigations to initiate experimental work, and to direct assistants.

(b) A SENIOR engineer—preferably with a good theoretical background. A successful applicant will be required to carry through to the production stage, design and development of radar and similar equipment.

(c) A TRANSFORMER designer. The applicant should be experienced in the design of small power transformers (less than 0.5 kva), chokes, audio transformers and pulse transformers, and will be expected to carry through to the production stage the design of power supplies and other associated equipment. Experience of servomotors and generators would be useful, but is not essential.

(d) A RESEARCH physicist or engineer. The applicant should have a university degree in physics or electrical engineering. Ability to apply mathematics to electrical problems is required, as well as a flair for experimental work in the field of electronics. Previous experience is not essential.

CANDIDATES for posts (a) and (b) above should have had at least five years' experience in the design of electronic equipment, especially in the following fields: Pulse techniques, C.R.T. displays, telemetering equipment, microwave equipment and aerials, servo-mechanisms.

THE Laboratory is situated in pleasant surroundings on the outskirts of Plymouth, and there is a pension scheme in operation. Candidates should write giving full details and salary required to the Chief Engineer, Bush Radio, Ltd., Power Rd., Chiswick W 4. (7489)

DEVELOPMENT engineers. Applications invited for the undermentioned positions by a rapidly expanding organisation situated at Hythe, Southampton.

A.—SENIOR development engineers, electrical, with several years' experience in research and/or development and design in light engineering, electronic and mechanical projects, such as magnetic recording, telecommunication, and audio frequency equipment, etc., for work on interesting new projects; applicants should have experience in the supervision of a small group; assistance given to successful applicants to obtain suitable accommodation; Degree desirable.

B.—SENIOR mechanical development engineer, with considerable experience in the design of the mechanical details relating to such apparatus as described above (or similar); applicants should be capable of progressing the design through the prototype stage to finality; used to the control of a model room and all types of machinery; also limited production of the parts designed, by temporary tools if necessary.

C.—JUNIOR engineers with experience in research, design and development of prototypes in connection with projects such as above, preferably with Higher National Certificate.

D.—DRAUGHTSMAN, accustomed to the design and layout of small mechanical projects.

SALARIES in accordance with qualifications and experience. Please give full details in chronological order with age, and salary desired.—Box 4978. (7744)

RADIO and television, capable man wanted to take charge of service and sales; in addition a service engineer.—The Truman Electrical Co., 40-42a, Bridge St., Walsall, Staffs. (7753)

THERMIONIC technical assistant; must be keen on industrial electronics; some experience of audio equipment.—Please apply The Rover Co., Ltd., Lode Lane, Solihull. (7659)

RADIO engineer required accustomed to layout and design of chassis.—Apply to Employment Manager, Vickers-Armstrongs, Ltd. (Aircraft Section), Weybridge, Surrey. (7426)

EXPERIENCED and conscientious trouble-shooter required for sub-miniature electronic equipment; Victoria area; write full details, experience & salary reqd.—Box 4962.

ELECTRICAL Inspector's required for sub-miniature electronic equipment; Victoria area; previous experience essential; write full details, experience & salary reqd.—Box 4963

FERRANTI, Ltd., Weston Works, Manchester, have staff vacancies in connection with special electronic valve development and manufacture in association with an important radio tele-control project.

(1) SENIOR valve engineers to take charge of research and development work.

QUALIFICATIONS include a good degree in physics or electrical engineering and extensive experience in charge of development work. SALARY according to qualifications and experience in the range of £1,100—£1,600 per annum; please quote Ref. S.V.E.

THE company has a staff pension scheme, and will give housing assistance in special cases.—Application forms from Mr. R. J. Hebbert, Staff Manager, Ferranti, Ltd., Hollinwood, Lancs. (7668)

TELEVISION development engineer required in a senior capacity in a research laboratory. The position requires considerable experience and ability to undertake design work unaided. Applicants possessing suitable academic and practical qualifications should apply in first instance to Box 4957. (7668)

Come to Classic for

"The Classic Service"

Our Motto is: "Nothing is too much trouble"

We will ship to any part of the British Isles or abroad.

TAPE RECORDING EQUIPMENT Delivery Price

| | | |
|------------------------------|-------|----------|
| Simon Simphonice, Model IA | Soon | |
| Sound Mirror, Table model | Stock | £69 10 0 |
| Sound Mirror, portable model | Stock | £79 10 0 |
| Scophony, portable mod. | Stock | £58 10 0 |
| Bradmaster Tape Desks | Stock | £42 10 0 |
| Microphones | Stock | £6 16 6 |
| Tapes from stock | | £1 5 0 |

AMPLIFIERS AND HI-FI EQUIPMENT

| | | |
|--|-------|----------|
| Leak T12 Amplifiers, with control unit | Stock | £37 16 0 |
| Williamson (Goodsell), with control unit | Stock | £40 15 0 |
| Quad Amplifier with control unit | Stock | £35 0 0 |
| Quad Radio Feeder Unit | Stock | £26 0 0 |
| Leak Radio Feeder Unit | Stock | £37 2 4 |

MOTORS AND PICK-UPS

| | | |
|---|-------|----------|
| Connoisseur 2-speed Motor | Stock | £22 18 8 |
| Connoisseur Super lightweight Pick-up | Stock | £4 10 5 |
| Garrard Auto-changer Unit and single-speed 8 record | Stock | £12 12 0 |
| Plessey Auto-changer Unit, 3 speed, 7in., 10in. and 12in. mixed | Stock | £23 13 0 |
| Collaro Auto-changer Unit, 3 speed, 8 record | Stock | £18 14 1 |
| Decca 2-speed Motor and Pick-up | Stock | £9 19 6 |
| Decca dual Head Pick-up | Stock | £3 10 0 |
| Leak Pick-ups, standard or L/P | Stock | £8 8 0 |
| Trix Autogram 3-speed Garrard Unit | Stock | £44 0 0 |

QUALITY SPEAKERS. UNITS

| | | |
|--------------------------------|-------|----------|
| Bakers, 12in. triple cone unit | Stock | £9 15 0 |
| Barker's 148A Unit | Stock | £15 15 0 |
| Barker's 150 Unit | Stock | £18 18 0 |
| Tannoy Duo Concentric, 12in. | Stock | £27 10 0 |
| W.B. 10in. Duo Concentric | Stock | £6 6 0 |
| W.B. 12in. Series gap 15 watt | Stock | £8 10 0 |
| Wharfedale Units, wide range | | £4 14 6 |

QUALITY SPEAKERS. CABINET TYPE

| | | |
|---|-------|----------|
| Leak, 2 unit, 400 cyl. crossover, in walnut cabinet | Stock | £57 10 0 |
| Decca Corner Speaker, 3 or 15 ohms. | Stock | £21 0 0 |
| W.B. 10in. Duo Concentric Corner | Stock | £13 16 0 |

COMPONENT AND KITS

| | |
|---------------------------------|-------------|
| Williamson Amplifier Kits Comp. | £20 10 0 |
| Viewmaster Tele. Kits | £27 10 0 |
| Germanium Crystals | Stock £ 3 9 |
| 16 ft. Portable Aerial | £1 12 6 |

All goods despatched by post or passenger train. Please include carriage.

Send Stamps for list. All Enquiries to

The Classic

Electrical Co. Ltd.

"THE HI-FI TELEVISION SPECIALISTS"
352/364 Lower Addiscombe Road, Croydon, Surrey. Telephone: Addiscombe 6061/2.

SUCCESSFUL SALES! **SATISFIED CUSTOMERS!**

Pennine RADIO

THE ALL SEASON SENSATION. ACCLAIMED THE COUNTRY OVER. THE INTIMATE RECEIVER WHICH COMBINES APPEARANCE AND PERFORMANCE. HOUSED IN A BEAUTIFUL WALNUT CABINET. EACH SET FULLY GUARANTEED.

HEIGHT 10", WIDTH 12", DEPTH 5 1/4"
4 Valve SUPERHET

THE SET THAT SELLS ITSELF!

UNBEATABLE VALUE
£15 0 2
INC. TAX.



"THE ROVER"

SUPPLIED ONLY THROUGH SELECTED WHOLESALE. ILLUSTRATED LEAFLETS AND ATTRACTIVE DISPLAY CARDS.

PENNINE AMPLIFIERS
ELLAND YORKS ENGLAND
TEL. ELLAND 2107

IT'S WORTH WHILE

Sending for the

CANDLER BOOK OF FACTS

if you're interested in

MORSE CODE TRAINING

Read these extracts from letters which Candler students have sent us:

Re. JUNIOR COURSE

"I simply must congratulate you on having such an easy way of teaching code. Frankly, I'm amazed at the speed with which I've been able to progress with your course. I can now send at 15 w.p.m. and receive at 8 w.p.m. This was accomplished with only 4 hours study per week." J. S.

Re. SPECIAL COURSE

"So far I have found your Special Course for securing an Amateur Transmitting Licence very beneficial in learning the Morse code, since I am practising on my own. I am now able to copy at approximately 10-12 words per minute. My sending speed is approximately 13-15 words per minute with comfort." O. F. S.

Re. ADVANCED COURSE

"With regard to code work, I can send at a comfortable 30 w.p.m. and can read quite long sentences at a speed just under that. . . I have a smoother sending action, and get off 'reversals' at a fairly high speed with good spacing and accuracy." J. C. B.

Send for the "Book of Facts"—it gives details of all the above Courses.

THE CANDLER SYSTEM CO.,
(55W) 52b, ABINGDON RD., LONDON, W.8
Candler System Company, Denver, Colorado, U.S.A.

DEVELOPMENT engineer required by A. H. F. Ltd., Shepherds Bush; preference given to man with experience of high frequency induction heating equipment; good salary to right man.—Tel. 1151.

DEVELOPMENT engineer required for well-known firm of electrical instrument makers situated North London. Man with good technical and mechanical knowledge for experimental work.—Box 4512.

APPPLICATIONS are invited by the Ministry of Supply for vacancies in the experimental officer class at the Atomic Energy Research Establishment, Harwell, Berks, for work in the following fields:—

PHYSICS, electronics and scientific computing (Ref. A309/51/ABL), and chemistry (other than organic chemistry), chemical engineering and metallurgy (Ref. F777/51/A/BL).

THESE posts offer a wide variety of experimental work in connection with the development of atomic energy and the opportunity for a career in an increasingly important branch of science. Candidates should possess at least Higher School Certificate or Higher National Certificate in a relevant scientific subject or mathematics or equivalent qualifications; higher qualifications will be an advantage.

APPOINTMENTS will be made according to qualifications, experience and age within the following salary ranges. experimental officer (male) £545—£695 per annum; assistant experimental officer (male) £240 (at age 18)—£505 per annum; rates for women somewhat lower. APPLICATION forms obtainable from Ministry of Labour and National Service, Technical and Scientific Register, Almack House, 26, King St., London, S.W.1.

INSTRUMENT assemblers with some electrical knowledge required, also test room assistants, for well-known instrument company situated in North London, good working conditions and canteen.—Apply Box 4511.

RADIO and radar design draughtsmen (experienced) required.—Apply stating age, experience and salary required, to the Personnel Department, Kelvin & Hughes, Ltd., New North Rd., Barking, Essex.

PLANNING engineers with jig and tool design and estimating experience required for electronics division of E. K. Cole, Ltd., Malmesbury, Wilts.—Apply Personnel Manager stating age, experience and salary required.

THE Research & Armament Development Division of the Fairey Aviation Company, Limited, is engaged in a Guided Weapon Project which offers work of exceptional interest and opportunity to the following:—

ELECTRONIC Engineers experienced in micro-wave, pulse or communication techniques. There are both senior and junior vacancies and though a degree or equivalent is normally required, applicants who lack such a qualification but who have considerable experience will also be considered.

A SENIOR Electro-Mechanical Engineer for servo-mechanism analysis and automatic control design; electro mechanical, hydraulic or pneumatic.

ACCOMMODATION Assistance will be given in selected cases. Pension scheme good salaries. British-born applicants should send full details to the Manager, Dept. W., The Fairey Aviation Company, Limited, Research and Armament Development Division, Heston Aerodrome, Hounslow, Middlesex.

TELEVISION engineer required, first-class rates and excellent working conditions. Candidates stating age, qualifications, experience and salary required, to British Relay Wireless, Ltd., Services Department, 397, Albany Rd., S.E.5.

CALIBRATION engineer required to supervise and maintain test gear of valve manufacturing plant; 40-hour week, salary up to £475 per annum; West London area; write giving age and fullest details of experience.—Box 5016.

SERVICE engineer for television and tele-communications equipment required, good wages paid to right man; write stating experience and wages required.—Gurney's (Radio), Ltd., 109, Broadway, Southall, Middx. 17730

ADMIRALTY.—Vacancies exist for electrical and/or mechanical engineering draughtsmen in Admiralty Research and Development Establishments located in the vicinity of Weymouth, Portsmouth, Teddington (Middlesex) and Baldock, Herts.

DRAUGHTSMEN experienced in light current, electro-mechanical, precision mechanical and electronic equipment are particularly needed.

CCANDIDATES must be British subjects of 21 years of age and upwards who have had practical workshop experience (preferably an apprenticeship) together with drawing office experience.

APPOINTMENTS will be in an unestablished capacity, but opportunities may occur for qualified staff to compete for established posts. THE salaries offered, depending on age, experience, ability, and place of duty, will be within the range £200-£360 per annum.

HOSTEL accommodation is available at some establishments.

APPPLICATIONS, stating age and details of technical qualifications, apprenticeship (or equivalents) workshop and drawing office experience, should be sent to Admiralty (G.E.H. Room 88), Empire Hotel, Bath, quoting DM/R.D. Original testimonials should not be forwarded with application. Candidates required for interview (at London or Bath whichever is nearer) will be advised within two weeks of receipt of application.

SENIOR laboratory engineer with experience for television development, all circuit design work, of high national importance; excellent prospects and conditions.—Write, call or phone Personnel Manager, Peto-Scott Electrical Instruments, Ltd., Weybridge Trading Estate, Weybridge 4271.

SOUTHERN RADIO'S WIRELESS BARGAINS

WALKIE-TALKIE (TRANSMITTER-RECEIVER). Type 38 Mark II. Complete with 5 valves, Throat Microphone, Headphones and Aerial. 7 mc/s Amateur Band suitable for field use. Powerful Superhet Receiver. Modulated Transmitter. Guaranteed ready for the Air, less batteries, £3/10/-.

R.3515 TELEVISION UNITS. Complete with 21 valves. 6 Stage 14mc/s I.F. Strip. Ideal for T.V. Conversion. Brand new in original wooden cases, £3/10/-.

LUBBRA HOLE CUTTERS. Adjustable from 1/4 in. to 3/4 in. for use on Wood, Metal, Plastic, etc.

5/9. LUBBRA FLY CUTTERS, 14/6.

LIONEL "BUG" KEYS. Genuine U.S.A. Automatic Morse Key, Type J36. Few only, £3/7/6.

THROAT MICROPHONES. Magnetic type complete with long lead and plug, 4/6.

HAND GENERATORS. 6 volts at 5 amps. With Crank, 21/-.

PLASTIC TRANSPARENT MAP CASES, 14 inches by 10 1/2 inches. Ideal for Maps, Charts, Display, Photographs, etc., 5/6.

STAR IDENTIFIERS. With Hydrographic Office Modifications A-N Type 1. Complete in case, 5/6.

MOVING COIL D/C METERS. Brand new, 2 in. 0-2 mA., 0-5 mA., 0-30 mA., 0-20 volts, 9/6 ea.

WESTECTORS. Type WX6 and W112, 1/- ea., 11/- doz.

VALVES. Brand new 805 U.S.A. in original cartons, each 32/6. A.T.P.4 for use on Transmitting section of Type "38" Walkie-Talkie, 7/6, 6K7, 7/6. Allbrand new.

MARCONI AERIAL FILTER UNITS. Type "916" in conformity with P.O. Specification. Full instructions for fixing, 4/-.

CONTACTOR TIME SWITCHES. 10-hour movement, 2 impulses per second. Thermostatic Control in soundproof Cases, 11/6.

VISUAL INDICATOR UNIT Type 3 (10Q/4). Contains two Moving Coil movements, two Neons, etc. Easily convertible to very efficient M.C. Meters, 11/-.

Conversion fully described in "W.W." Sept. 1951.

Full list of Radio Publications, 2/4d.

SOUTHERN RADIO SUPPLY LTD.,
11, LITTLE NEWPORT STREET, LONDON
W.C.2. GERARD 6653

"Quixo" Radio Cell Tester

Accurate tests
High, Low and Grid
Bias Batteries.
Write for leaflet 30M

RUNBAKEN MANCHESTER 1

ODDIE FASTENERS

PAT 507249

THE FASTENER WITH ENDLESS APPLICATIONS—SIMPLE—POSITIVE SELF-LOCKING. MADE IN A VARIETY OF TYPES AND SIZES. SPECIAL FASTENERS TO SUIT CUSTOMERS REQUIREMENTS. WIDELY USED IN THE RADIO INDUSTRY.

Illustrated brochures and other information will be gladly sent on request.

Oddie, Bradbury & Cull Ltd., Southampton
Tel.: 55883 Cables: Fasteners, Southampton

THIS IS
REOSOUND
REGISTERED TRADE MARK

DE LUXE INSTRUMENT CASE



12in. x 8in. x 5in. in 18G. Steel with Radused Top Corners, Louvred Back and fitted with Chromium Plated Handle, and four P.V.C. feet. Finished in Black, Grey, or Brown Wrinkle Enamel. 18G. Steel front panel, £1/8/3 With front panel in 16G. Aluminium, £1/7/6 Small steel chassis with angle brackets to fit, Black 5 8 Ditto, in 16G. Aluminium, self-colour... 7 6

Postage and Packing 2/-
Carriage Paid on Orders over £5.
Illustrated Lists on request.
All List Prices now plus 25%.
Trade Terms on application.

REOSOUND ENGINEERING & ELECTRICAL COMPANY, "Reosound Works," Coleshill Road, Sutton Coldfield.
Grams: Reosound, Sutton Coldfield.
Tel. SUT. 4685.

SENIOR and junior draughtsmen, with experience in sheet metal work and general radio engineering, urgently required by well-known engineering firm in East Anglia; replies treated in confidence.—Apply Box 4968. [7721]

BOYD, Ltd. require radio and TV engineers for their Central Service, Chatham, Dunbridge and Bexley Heath branches, owing an advantage; good wages and prospects.—Reply, Service Supervisor, 18, Crown Place, N.W.5.

WANTED immediately, experienced car radio mechanic with knowledge of automobile electrical equipment; permanent situation for right man.—Apply T. J. Nice & Co. Ltd., Motor Engineers, Abbeygate St., Bury St. Edmunds. Tel. 601-2. [7665]

RADIO mechanic required for radio service work at S. Smith & Sons (England), Ltd., Great West Road, Factory, Brentford; experience essential; high starting wage.—Apply in person to Personnel Manager or Tel. Ealing 8071 ext. 25. [7454]

ARTTECH, Ltd., Aylesbury and Thame Airport, Haddenham, Bucks, urgently require radio and radar mechanics; excellent long-term prospects and pay with opportunities for good bonus earnings.—Apply immediately, Personnel Superintendent. [7667]

LICENSED aircraft radio maintenance engineers are required for service in the North and South of England; applications in confidence.—Technical Manager, Lancashire Aircraft Corporation, Bovington Airport, Hemel Hempstead, Herts. [7702]

RADIO development engineer required by leading manufacturer to undertake work in a senior capacity in a research laboratory. Applicants with suitable qualifications to undertake design work unaided should apply in first instance to Box 4958. [7669]

EXPERIENCED sound engineer for electrical and acoustic measurements on production batches of audiometers; permanent position for steady man.—Amplivox, Ltd., Abbey Manlg. Estate, Mount Pleasant, Wembley, Tel. Wembley 3906. [7753]

NUMBER of vacancies exist for draughtsmen and designer draughtsmen in various sections of the Pye group of companies.—Please reply giving details of age, experience and salary required to Personnel Department, 37, Andover Rd., Salisbury, Wilt. [7437]

E. K. COLE, Ltd., have vacancies for testers at their Electronics Division; experience in the testing of radar, communications or electronics equipments to Ministry specifications essential.—Full details writing to the Personnel Manager, Aylesbury, Wilts. [7340]

DRAUGHTSMEN, senior, required with electrical or radio experience and knowledge of Ministry specifications; salary up to £600 per annum; location, Bedfordshire.—Write, giving full details of qualifications and experience, mentioning ref. ADD, to Box 4197. [7488]

ASST. BUYER required by large manufacturing company in S.E. London. Thorough knowledge of electrical and engineering markets. Position offers scope for advancement. Pension scheme.—Applications, giving full details of age, experience and salary required, to Box 4947.

ELECTRICAL transformer designer required with experience of transformer design up to 500KVA; able to take full responsibility; apply giving full details of experience and salary anticipated to Woden Transformer Co., Ltd., Moxley Rd., Bilsington Station, Bilsen, [7493]

TECHNICAL assistant required for work in materials application division. Qualifications: Inter B.Sc. or equivalent, with interest in metallurgy.—Apply giving age and fullest details of experience to Personnel Department (ED/55), E.M.C. Engineering, Limited, Hayes, Middx.

SENIOR Television Engineer, able to take charge of television development is required by large company in S.E. London. Staff pension scheme.—Applications, giving full details of age, experience and salary required, to Personnel Manager, Burntup, Limited, West Street, Erith. [7620]

ELECTRONIC assistant required for construction and wiring of test-gear in engineering laboratory; interesting work 5-day week.—Write, stating age and giving full details of previous experience and salary required, to the Personnel Officer, The de Havilland Engine Co., Ltd., Stag Lane, Edgware, Middlesex. [7550]

A NEW defence project of National importance being undertaken by a well-known aircraft company located in the northern outskirts of London offers highly paid and interesting posts for suitably qualified applicants; vacancies exist in senior (salaried grades) and for junior engineers in various categories:—
(a) **PHYSICISTS** with experience in electronic problems.
(b) **PHYSICISTS** with experience in optical work.
(c) **ELECTRONIC** engineers with Servo-mechanism experience.
(d) **ELECTRONIC** engineers with experience of low frequency work and measuring systems.
(e) **ELECTRICAL** engineers with experience in small motor design and development.
APPLICANTS for senior posts should possess a good University degree and preferably should have some industrial experience. **APPLICANTS** for junior posts should have a good industrial experience, be qualified either by City & Guilds Certificate or by Inter B.Sc. **WRITE** full details, qualifications, experience, age, salary sought, to—Box A.C.65488, Samson Cards, 57/61, Mortimer St., W.1.

A NUMBER of senior and junior vacancies for a radio, radar, electronic, television, etc., development, service engineers, draughtsmen, wiremen, testers, inspectors, etc.; urgently requiring 30 television service engineers.—Write in confidence, Technical Employment Agency, 179 Clapham Rd., S.W.9. (Brixton 3487.) [1013]

NUSOUND PRODUCTS

136 WARDOUR STREET, LONDON, W.1 (Oxford Street End) Tel: GERtard 8845

NUSOUND FIDELITY-TEN. The latest super quality Amplifier. All Triode line up. P-Pull PX4 output. Frequency response 20-25 kcs. ± .6 d.b. and continuing up to 50 kcs. ± .9 d.b. Sensitivity 120 mv for max 10 w. output. Total harmonic distortion 1% per cent. at 1,000 c.p.s. at 6 watts. 20 d.b. neg. feedback. Independent Treble and Bass controls. Chassis size: 14 x 9 x 7 1/2 in. high. A.C. model only, £26.

A NEW FEEDER UNIT. This is our latest addition to our range, and employs a 5/het c.c.t. with two I.F. stages and variable selectivity controls giving bandwidths of 7-10 and 14 kcs. The unit covers the medium-long and short wavebands and has a large illuminated dial. Price 17 gns. inc.

RETAIL TRADE ENQ. ON ABOVE ITEMS. PLEASE SEND STAMP FOR LEAFLETS.

NUSOUND QUALITY AMPLIFIERS.
8 1/2-WATT OUTPUT.—PP 6V6s—dependent bass and treble boost and cut—switch for L.P. records—neg. feedback—provision for radio feeder unit—freq. response 23 to 20,000 c.p.s.—± 1/2 d.b.—hum 80 d.b. down at 6.5 watts—feedback 14 d.b.—sensitivity .05 volt. Price only £15/17/6. Also available with remote control unit. Price £17/10/-.

NUSOUND REFLEX CABINETS.—For Wharfedale speakers—10in., £9/9/-; 12in., £10/10/-. Veneered polish finish mahogany or oak.
Please send stamp for list of all our products. Our other products inc. 4 1/2 watt Amp.—A.C. Model £11/10/-; A.C./D.C. £12; T.R.F. Pre-set Feeder, 3 station, £7/12/6; 3 station Pre-set S/Het, £8/18/-; two-band variably tuned S/Het, £11/5/-.
Remote control pre-amp. Unit, inc. tone controls, £5/7/6.

GRAMOPHONE EQUIPMENT
Decca 33 or 78 r.p.m. motor, £3/14/4, inc. Connoisseur P/ups, Std. L/weight, £4/11/8. Trans. 13/-, Super L/weight, one head, £6/9/-, LP Head 7/18. Trans. 15/-, Fibre P/up £4/3/2. Trans. 25/-, Two-speed Stroboscope 3/11. Garrard Heads: Standard 25/3. Miniature 59/11. High 56/-, Type A Adapter 7/7. Decca Mag. Heads 59/2. Decca XMS P/up £7 complete. Chancery Attachment 7/6. Decca 3-speed motor £7/3/4. Connoisseur 2-speed motor £22/18/8. Chancery Xcal P/up (LP20 insert) 53/-. Spare insert, LP 3/6. Garrard AC6 motor, speed controlled, 12in. table £6/15/10. Collaro A.C. 514MB motor and P/up £6/10/5. Collaro A.C./D.C. motor, 12in. table £12/2/7.
(We stock a full range of Wharfedale & Goodmans speakers and accessories.) TV and Gram. list 4d. (Please Add Postage.)



RAINBOW
Radio & Television

10 minutes, is the time taken to change over SUTTON COLDFIELD tuned T.V.s to receive HOLME MOSS with our HM.2. Frequency Converter unit.
Retail: **£8-0-0**
And for "long range" reception our T.V. Pre-Amplifiers are still "Pre-Eminent." Retail at: **£5-17-6 and £7-10-0**

Obtainable through your dealer or direct:—
RAINBOW RADIO MFTG. CO. LTD.
Mincing Lane, Blackburn, Lancs


EX GOVERNMENT BARGAINS

New and Used Equipment

Telephones. Ex-G.P.O. wall telephones, brand new, in maker's wrappings, complete in teak case with battery and hand generator ready to use, only 4 1/2 v. bellset required, 90/- pair, carriage 5/-.
Uniselector Switches. 3 banks of 25 contacts per bank. New condition, 21/6. postage 1/3.
Moving Coil Earphones. Impedance 30 ohms, in used condition. 5/- per pair postage 1/6.
Vibrator Packs. 12 volt input. 250 volts at 50 millamps output, complete with smoothing and GZAA valve, ex No. 19 Equipment, 15/6, postage 2/3.
Camera Control Units. Consisting of 24-volt motor geared to clockwork mechanism with 1-50 second timing device. Used for exposure timing, etc. Complete with control knobs, indicators, signal lamps, etc., in metal case, 8in. x 5in. x 3in. in solid condition, 12/6, postage 1/6.
Bomb Release Controls. Containing 4 relays, toggle switch, indicator lamp, selenium rectifier, 32 mf. condenser, Xaxley switch, thermal switch and various small condensers and resistances, all contained in metal box black crackle finish. a good experimenter's lot, also useful as a process timer, will give 20 different speeds, 16/6, postage 7/6.
A.E. Balls. Will operate direct from 230 volt A.C. mains, 4/6 each, post 9d.
Microphones. Tannoy sound power type in metal case with handle, 9/8. Moving coil type in bakelite case with handle, 6/9. Carbon type in bakelite case with handle, 3/-. Postage 9d. each 1/6.
Steel Chassis. Clean 9in. x 5 1/2in. x 3 1/2in. drilled for 5 valves, volume control, switch, etc., drop-through transformer, 2/-, postage 6d.
Rotary Converters. Delco 12 and 24 volt. 265 volts at 120 milliamperes, and 840 volts at 26 milliamperes output. New condition, 19/-, post 2/-.
Ohmiv Wire Wound Pots. Vitreous 100 ohm 25 watt, 350 ohm 25 watt, 3/6. Postage 8d.
Relays. Low Resistance. 30 ohms. Double pole brake contacts with 4-pin Jones socket and 5 ohm resistor, brand new condition, 3/-, post 9d.
Magnetic Counters. Will operate on 12-24 volts D.C. reading 0-9999. 6/-, postage 1/-.
V.F. Telegraph Units. Simplex No. 3, for use with teleprinters, etc. Complete in case with power unit and 4 ARP9 valves and instruction booklet. Brand new condition. 65/-, carriage 7/6.
New List No. 7. Containing 800 Ex-Government items. 6d. post free. 1/6 overseas Air Mail.

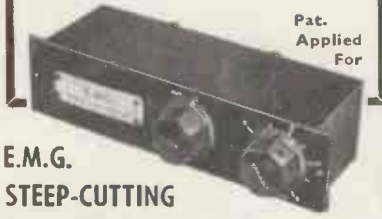A. T. SALLIS
93, North Road, Brighton, Sussex
Phone: Brighton 25806

A REMARKABLE ACHIEVEMENT IN FILTER DESIGN



E.M.G.
STEEP-CUTTING
INFINITELY VARIABLE FILTER

- Cuts at any selected frequency between 4,000 and 8,000 c.p.s.
- Average steepness of cut 30 db. per octave.
- Connects between secondary of output transformer and speaker (15 ohms. rated impedance)
- Specially valuable for use with new microgroove records
- Greatly reduces needle-hiss on ordinary records with minimum high note loss, and suppresses high pitched interferences on radio.
- No distortion, and no appreciable loss of volume.
- Leaflet available from the manufacturers.
- Novel circuit, patents pend. u.

£4 - 10 - 0
 Trade Enquiries invited

E.M.G. HANDMADE GRAMOPHONES, LTD.
 Newman St., Oxford St., W.1.
 Telephone: Museum 9971-2-3

TELECRAFT AERIALS ENSURE THE BEST TELEVISION TRY ONE AND SEE FOR YOURSELF

G.E.C. GERMANIUM CRYSTAL DIODES

LATEST, SMALLEST, SUPREME CRYSTAL DETECTOR
 Midget Size, 5/16in. x 3/16in.
 Wire Ends for Easy Fixing.
 4/6 each, postage 2jd.

Technical Details and Selected Types available.
SILICON DIODES, 3/6. Postage 2jd.
 Fixing Brackets, 3d. pair.

COPPER INSTRUMENT WIRE
 ENAMELLED, TINNED, LITZ,
 COTTON AND SILK COVERED
 Most gauges available.

B.A. SCREWS, NUTS, WASHERS,
 soldering tags, eyelets and rivets.
EBONITE AND BAKELITE PANELS,
TUFNOL ROD, PAXOLIN TYPE COIL
FORMERS AND TUBES, ALL DIAMETERS.

Latest Radio Publications.
 SEND STAMP FOR LIST.
 TRADE SUPPLIED.

POST RADIO SUPPLIES
 33 Bourne Gardens, London, E.4

TECHNICAL assistants required for interesting laboratory and field work connected with guided missiles project; applicants to be between 20 and 35 years of age, with at least National Certificate (Electrical) or equivalent; experience of R.F. technique up to 500mc would be an advantage.—Full particulars to Box 4522. (7540)

RADIO mechanics required for work on electronic equipments at Stanmore; previous experience essential; progressive staff positions; 5-day week.—Write, giving full details of age, experience and qualifications, to the Staff Manager (Ref. GBL/C/43), Research Laboratories of the General Electric Co., Ltd., Electricity Division, S.E. London

A PROGRESSIVE manufacturing company in S.E. London is desirous of appointing a chief inspector with electrical and mechanical experience and knowledge of radio and television. Staff pension scheme.—Application in confidence, should give full details of age, qualifications, experience and salary, to Box 4948.

A SENIOR test engineer is required by a well known Midland electrical firm; the successful candidate will be responsible for all testing of industrial electronic equipment and for this type of work is essential; applicants should write giving the fullest particulars of qualifications & exp. quoting IDB.—Box 5014.

MURPHY RADIO, Ltd., require a foreman inspector for the prototype manufacturing section of the electronics division; experience with communications and radar equipment built to service standards and procedure is essential.—Apply, giving full particulars to Personnel Department, Murphy Radio, Welwyn.

A LABORATORY ASSISTANT required, capable of taking charge of electrical and electronic equipment for a guided missiles project; duties will include calibration and minor repairs of instruments; applicant with the necessary experience will also control sub-standards and undertake design of laboratory equipment.—Full particulars to Box 4521.

ENGLISH ELECTRIC VALVE CO., Ltd., L. Chelmsford, require a young engineer for testing and development of prototype microwave klystrons; suitably experienced and qualified applicants should write, giving full details and quoting ref. 419C. to—Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., London, S.W.1. (7642)

MURPHY RADIO, Ltd., have vacancies for senior mechanical designers in their electronics division; a full and varied programme ensures opportunity of widening experience with excellent prospects; application giving particulars of training and experience should be made immediately to—Personnel Dept., Murphy Radio, Ltd., Welwyn Garden City. (7408)

MULLARD EQUIPMENT, Ltd., S.W.18. Designers.—Electro-mechanical designers of degree standard required for interpreting laboratory electronic devices into production designs; permanent, pensionable posts; salary according to qualifications and experience.—Apply Personnel Department, Mullard Equipment, Ltd., Brathway Rd., Wandsworth, S.W.18. (7525)

A SENIOR designer required to undertake development work on low-frequency iron-cored components. Previous experience in this subject is essential, and a degree or equivalent would be an advantage. The salary will be in accordance with qualifications and experience.—Apply in writing to Advance Components, Ltd., Back Rd., Sernhalp St., Walthamstow, E.17.

TELEVISION service engineers or good radio service engineers for training in television required by large company for the Bristol area; applicants must be prepared to work in the London area for the period of training, and return to the Bristol area with the opening of the new transmitter.—Give details of experience, age and salary required to Box 4955

ELECTRONIC circuit engineer/draftsman required with sound knowledge of circuitry and component specifications, to work at Luton. Graduate Brit. I.R.E. or equivalent an advantage. Applications from engineers with limited draughting experience will be considered.—Apply to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1.

ASSISTANT chief inspector required with not less than five years' experience on the inspection of electronic apparatus to ministry requirements; should preferably possess a degree or Associate Membership of the Institute of Electrical Engineers; this post is permanent and pensionable; excellent salary to suitable applicant; N. London area; fullest particulars.—Box 5015 (7776)

Physics student required for development work on electronic components in laboratory of large company situated in country area of Essex; suitable applicant should have degree in physics and should be interested in development work, previous experience being an advantage; accommodation will be made available for full-time applicant.—Kindly state details to Box 4965. (7714)

HIGH power rf dielectric heating equipment.—Engineer required to supervise installation and acceptance tests; experience on either large rf heating equipment or radio transmitter employing water-cooled valves is essential; this position has particularly interesting prospects; write, stating full experience, age and salary required.—Radio Heaters Ltd., Wokingham.

NUMBER of vacancies exist for electro-mechanical designers with a good degree in mechanical and electrical engineering, or similar qualification, and several years experience in a laboratory or factory design department. Successful candidates will be expected to work in laboratory teams or in laboratory/factory teams on interesting and varied projects, and to be responsible for the mechanical design of equipment; the posts are permanent and pensionable; salary according to qualifications and experience and consistent with present day levels.—Application form from Personnel Officer, Ford Research Laboratory, Cross Oak Lane, Salfords, nr Redhill Surrey. (7378)

"You can rely on us"

FOR CLEAN COMPONENTS AT COMPETITIVE PRICES

IMMEDIATE DISPATCH

MIDGET COIL-PACKS

These are an ideal miniature Coil-Pack especially suited where space is limited. They consist of iron-cored miniature coils for both Aerial and Oscillator stages, built-in Wavechange switch and midget trimmers. They are intended for an I.F. of 465 Kc/s. and I.F. Transformers type RS/GB 465 (12/6 per pair) are the ideal companions for a trouble-free superhet.

TYPE "R"
 MW/LW GRAM. Ranges: 200-550 metres, 800-2,000 metres.
 SIZE: Length 2 1/2 in. Width 1 1/2 in. Depth 1 1/2 in.

TYPE "S"
 MW/SW GRAM. Ranges: 200-550 metres, 17-50 metres.
 SIZE: As Type "R."

TYPE "C"
 LW/MW/SW. Ranges: 800-2,000 metres, 200-550 metres, 17-50 metres.
 SIZE: Length 3 1/2 in. Width 1 1/2 in. Depth 1 1/2 in.

TYPE "R" and **"S"** each 28/- **TYPE "C"** each 32/6. Post 6d.

All coils enclosed—all iron-dust cores adjustable. Completely wired, only five connections needed to external circuit.

Catalogue with Data, 6d.

AERIAL FILTERS 465 Kc/s, 6/3. Post 3d.


RADIO SERVICING Co.

444 Wandsworth Road, London, S.W.8

Phone: MACaulay 4155

77, 77A Bus, 28 Tram. Wandsworth Rd. S.R. Station
 Open till 8.30 p.m.

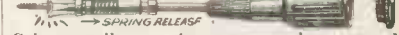GRIPS the SCREW AND DRIVES IT HOME INTO THAT AWKWARD SPOT SO QUICK SO EASY!



Grips smallest grub screw or large wood screw, firmly, instantly, drives quickly home! Saves time and labour!

POST 4/- MAILEX SUPPLY CO. (W), PAID 70 Poynters Rd., Dunstable, Beds.

Convert that old Gramophone

OR OBSOLETE RADIOGRAM

into a **MODERN ALL-WAVE**

RADIOGRAM

OR POWERFUL RECORD PLAYER

Our "SKYWAY DESIGNS" Book gives full details on how to build FOUR first-class Amplifiers and Radiogram chassis. No radio experience is required to understand the clear circuit diagrams and stage by stage wiring plans.

2/6

POST FREE

All parts and materials are easily obtainable, mostly without purchase tax. Performance equal to radiograms costing over £100.

only from **Frith RADIOCRAFT Ltd.** 99-71 CHURCH GATE-LEICESTER

PHONE 58927

THE VENTEX COLUMN REPRODUCER



A loudspeaker with all the qualities required for **WIDE RANGE** reproduction in the home.

- 1 sq. ft. Floor Space
- 360° high note radiation
- Built-in Diffuser
- Response 30-20,000 c.p.s.
- Sound Source from natural height
- Beautifully styled for the home
- Hand French polished

PATS. PENDING

Supplied with **TANNOY DUAL-CONCENTRIC** unit complete with Cross-over filter.

Available in Mahogany, Walnut, or Oak.


at 45 Gns. ex works.

MANUFACTURERS OF TUNER UNITS

C. T. CHAPMAN (Reproducers) LTD.

RILEY WORKS, RILEY STREET, CHELSEA, S.W.10. FLAXman 4577/8

Demonstrations at **WEBB'S RADIO.**

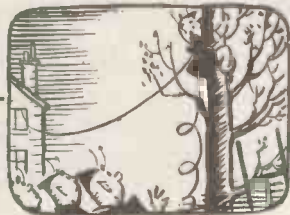

THE "FLUXITE QUINS" AT WORK

"Our T.V.'s. all set for to-night, Thanks to solder and Good old **FLUXITE**

"So why shin that tree?"

"New aerial!" bawled **E.E.**

"We shall see miles more from this height!"

See that **FLUXITE** is always by you—in the house — garage — workshop — wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all Iron-mongers—in this from 1/- upwards.

TO CYCLISTS! For stronger wheels that will remain round and true, here's a time tested tip. Tie the spokes where they cross with fine wire **AND SOLDER.** It's simple — with **FLUXITE** — but **IMPORTANT.**

The **FLUXITE GUN** puts **FLUXITE** where you want it by simple pressure. Price 2/6, or filled, 3/6.

FLUXITE SIMPLIFIES ALL SOLDERING

Write for Book on the Art of "SOFT" Soldering and for leaflet on **CASE-HARDENING STEEL** and **TEMPERING TOOLS** with **FLUXITE.** Price 1d. ea.

FLUXITE LTD. (Dept. WW), BERMONDSEY STREET, LONDON, S.E.1.

LABORATORY assistants required for development on laboratories engaged on the design of experimental and prototype electronic equipment; applicants should have a wide experience of the maintenance and installation of radio, television and radar, and should write, giving full details, to Personnel Department (ED/51), E.M.I. Engineering Development, Hayes, Middx.

TECHNICAL Librarian/information officer to form and operate library of monographs, periodicals, internal reports, trade literature, etc., covering radio, electronic and allied interests and run information services; to have both technical and library qualifications and prepared to take live interest in firm's activities.—Write to Box WW297, L.P.E., 110, St. Martin's Lane, W.C.2. [7719]

EXPERIENCED telecommunications draughtsmen required by the Plessey Co., Ltd., permanent and progressive positions are offered to men having experience of line communications equipment or radio communications equipment; positions offer varied and interesting jobs with usual staff privileges.—Applicants should state full details to Personnel Manager, The Plessey Co., Ltd., Ilford, Essex. [7682]

COMMUNICATIONS engineer, familiar with circuit design, is required for work on H/F quartz crystal circuits; candidates should preferably have a university degree and 2-3 years experience in experimental work.—Applicants should be sent to the Staff Manager (Ref. GBLC/O/177), Research Laboratories of The General Electric Co., Ltd., Wembley, Middlesex, stating age and record. [7690]

RADIO/Radar mechanics required by progressive and expanding company for work on aircraft radio/radar equipment, although experience in this type of work would be preferable; applicants having a sound basic knowledge of radio maintenance may be acceptable; remuneration based on experience and ability; licensed personnel will receive prior consideration.—Box 4952. [7636]

A FEW interesting vacancies exist for graduates in physics or electronic engineering preferably with first- or second-class honours; the work relates to Government Development Contracts connected with frequency control systems.—Apply Personnel Manager, Standard Telephones & Cables, Ltd., North Woolwich, E.16, giving summary of experience and qualifications and enclosing references. [7720]

ENGINEERS required for interesting work on the development of radio transformers and similar components. The work involves investigation of the application of new magnetic materials to transformer design.—Applicants should write, giving full details of experience, etc., and salary required, to the Personnel Department (ED/50), E.M.I. Engineering Development, Ltd., Hayes, Middlesex. [7674]

ENGINEERS required for liaison between development team and users of special electronic equipment; applicants should have a degree or similar qualification with a sound general experience in the field of electronics.—Application should be made, giving full details of experience, etc., and quoting ED/52, to the Personnel Department, E.M.I. Engineering Development, Ltd., Hayes, Middlesex. [7687]

E.M.I. ENGINEERING DEVELOPMENT, Ltd., have a number of vacancies for engineers and senior engineers on interesting development work in various electronic engineering projects. The posts are for permanent pensionable staff, and offer good prospects. Qualifications: a degree in Physics or Engineering or equivalent, together with several years' design or specialised experience in the following fields:—

- (a) L.F. equipment.
- (b) Television equipment.
- (c) Microwave techniques.
- (d) Pulse techniques.
- (e) Servo techniques.
- (f) Test gear designs.
- (g) Inspection.

APPLICANTS should write, giving full details of experience and type of work required, and quote ED/35 to Personnel Department, E.M.I. Engineering Development Ltd., Hayes, Middlesex.

JUNIOR engineers to assist in the design, construction and test of laboratory models of special electronic circuits; some experience of similar work desirable and a knowledge of radar circuits, design and operation an advantage; salary up to £600 per annum.—Please write, giving full details and quoting ref. 815c, to Central Personnel Services, English Electric Co., Ltd., 24-30 Chillingham St., London, S.W.1.

EXPERIENCED telecommunications draughtsmen required by the Plessey Company, Limited. Permanent and progressive positions are offered to men having experience of line communications equipment or radio communications equipment. Positions offer varied and interesting jobs with usual staff privileges.—Applicants should state full details to Personnel Manager, The Plessey Co., Ltd., Ilford, Essex.

TECHNICAL writers (male or female) required to prepare and edit reports and handbooks for publication; qualifications, a good general training in electronics with wide practical experience of electronic equipment, marked critical faculty (form and content) and ability to write clear English.—Applicants should write, giving full details, to Personnel Department, ED/42, E.M.I. Engineering Development, Hayes, Middx.

EADING aircraft instrument manufacturer has a vacancy for an electronic engineer with a good knowledge of aircraft engines and the application of electronic analysis systems; engagement will be on a monthly basis and successful applicant will be required to travel; commensurate salary according to qualifications and experience, but not less than £450 p.a.; superannuation scheme.—Application to Box A.C.66507, Samson Clarks, 57/61, Mortimer St., London, W.1. [7639]

SUPACOILS

OFFER THE LATEST EDITION OF THE HOME CONSTRUCTOR'S HANDBOOK

If you wish to build Superhets, Feeder Units, Amplifiers, etc., etc., you **MUST** have this Handbook. In addition to a considerable number of reliable and tested circuits it contains:

- Pages of servicing and constructional information which will assist you in **YOUR** radio problem.
- Complete resistance colour code.
- A considerable amount of invaluable general Radio information.
- A comprehensive catalogue.
- Above all it is profusely illustrated with half tone blocks and costs 2/- only or a copy will be given **FREE** with every order for £1 or more.

We also offer the following selection from our stocks of quality components:

- **COILS.** Our standard High Q variable iron dust cored coils (as recommended for the P.W. 9 valver) in wavelengths 10-30, 16-50, 30-75, 75-200, 190-550 and 800-2,000 metres; Aerial, H.F. or Oscillator 3/- each.
- **COIL GROUPS.** Our very popular coil groups are being used by more and more constructors for set building. Coil Group "A" consists of 6 of the above coils (your own selection), 1 Miniature 4p. 3w. rotary switch, 2 fixed padders (to suit coils selected), 6 variable trimmers. Complete group. £1 9 0
- Coil Group "B" consists of 9 of the above coils (your own selection), 1 rotary 7p 4w switch (3 w/bands and gram.), 2 fixed padders (to suit coils selected), 9 variable trimmers. Complete group. £2 7 6
- **SPECIAL.** We have recently introduced a new range of miniature iron-dust cored coils, waveband coverage as for our standard coils. Price 3/6 each (full descriptive leaflet and quantity terms on application).
- **I.F. TRANSFORMERS.** Iron dust cored, pre-aligned to 465 Kc/s. 16/6 pair.
- **T.R.F. COILS.** Iron cored. Medium Wave only, grid coil Litz-wound, Aerial and H.F. 7/- pair.
- **T.R.F. COILS.** Air cored. Long and Medium Wave on one former with coupling coil. Aerial and H.F. (M.W. Grid Coils Litz-wound). 8/- pair.
- Large stock of coil packs and all components. Stamp for complete catalogue. Export enquiries for all our products cordially invited.

SUPACOILS MAIL ORDER OFFICE
98, Greenway Ave., London, E.17

B. & H. RADIO EAST STREET, DARLINGTON


BASS & TREBLE SEPARATOR
Enables the use of separate speakers for Bass and Treble. Permits adjustment of treble and matches up speakers of different impedance. Kit of Parts £1 13 6

SCRATCH FILTER
Easily fitted to pick-up and gives marked reduction of scratch 17 6

WHISTLE FILTER
is very simply inserted in speaker wiring and completely eliminates 9 Kc/s. whistle..... £1 15 0

A.F. and R.F. COILS rewound or wound to specification.

**THE HAYES RG/135
RADIOGRAM CHASSIS**

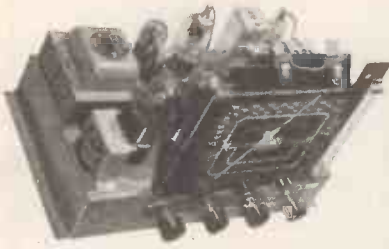

Combining advanced design with a high standard of construction, the RG/135 7-valve circuit includes a 6 watt output stage with negative feedback, and a new tone control system. Price £18 complete. Write for full details of this chassis and also of our popular RG/120 5-valve model, price £14 complete.

THE HAYES COMPANY
1 Alcester Road, Birmingham 13

Telephone South 0202

AUTOMATIC SWITCHES

(RECONDITIONED)
ELECTRIC CLOCKWORK
1 to 100 AMPS. 7 to 35 DAYS

From **35/-** EACH

All guaranteed for a year.

Write for Illustrated Hds.:

**DONOHUE'S (Timers), 6, GEORGE ST.,
NORTH SHIELDS, NORTHUMBERLAND.**

**CABINETS
FOR THE RADIO INDUSTRY**

Designed and Manufactured

THE CHAFFEY CABINET CO.

(FORMERLY CHAFFEY-CONSOLE)

6, SEFTON RD., PETTS WOOD, KENT
Telephone : Orpington 3559

**SAMSONS
SURPLUS STORES**

BRAND NEW EX-GOVERNMENT VALVES
813. £3/10/-; VT90. 17/8; U18. 8/8; 5T4G.
9/6; VU138. 7/6; 024. 7/6; HL1320. 7/6;
Carr. all types 6d.

Special offer of HEAVY DUTY TRANSFORMERS.
Prim 180-230 v. 50 cy. Sec. 14-20 v. 20 amps.
47/6, carr. 3/6. Prim. 180-230 v. 50 cy. Sec.
4.2 v. + 4.2 v. 10 amps. 25/-, carr. 2/6. Prim.
200-230 v. 50 cy. Sec. 6.3 v. 15 amps. 17/6.
Carr. 1/6. Prim 200-240 v. 50 cy. Sec. 5 v. 7 1/2
10 v. 5 A. 22/6, carr. 1/6.

DS SINGLE TELEPHONE CABLE, 1 mile drums,
55/-, carr. 7/6.

HEAVY DUTY W.W. POTS, 20 watts 17K and
20K, 10/6 each, carr. 1/-.

S.T.C. ATTENUATORS, 5K in 75 ohms steps,
9/6, carr. 1/-.

5 PIN CERAMIC COIL BASES for Eddystone in-
duction coils. 2/-, postage 6d.

30FT. COILS CO-AXIAL CABLE with Pye sockets
on each end, 8/6, postage 1/6.

VARIOMETER INDUCTANCES for the No. 19
variometers, 3/6, post 9d.

169/171 Edgware Road
London, W.2. Tel. PAD. 7851
125 Tottenham Court Road, W.1
Tel. EUS. 4982

All orders and enquiries to our Edgware Road
branch, please. Open all day Saturday at the
Edgware Road Branch.

MURPHY RADIO, Ltd. have vacancies in the
electronics division for qualified engineers
with factory test experience on service equip-
ment; duties will consist of the testing of
development models, the preparation of test
data for the factory and the instruction of
test department personnel in the handling of
new equipment.—Apply giving full particulars,
to Personnel Dept., Murphy Radio, Welwyn. 17648

BUSH and Murphy dealer requires first-class
radio and television engineer; must be
thoroughly conversant with service of all leading
makes of TV and able to get quick results in
well-equipped workshop; in exchange for these
qualifications a permanent post with good salary
and a newly furnished flat in beautiful country
district is offered.—Send full details in first
instance to Stute Pinnington, Old Hall, Wel-
wyn, Herts. [7747

JUNIOR radio engineer required for installa-
tion and testing of aircraft radio equip-
ment; duties will involve test flying; current
M.C.A. operator's licence an advantage, but
consideration will be given to suitable applicant
prepared to obtain licence during probationary
period.—Application should be made in writing,
giving details of experience and salary required,
to the Personnel Manager, The de Havilland
Aircraft Co. Ltd., Hatfield. [7500

EX-SERVICE urgently required for interest-
ing work West Middlesex area. Well-paid jobs
await those accepted for preliminary training in
central London. Three-quarters full union rate
paid during three months' training. Contracts
offered suitable applicants. This is a genuine
offer of employment by one of the largest elec-
tronic organisations. Write for particulars and
application form.—Box 4195. [7486

AN electronic engineer required, by firm
in the Guildford area, for development work
on aircraft instruments and electronic equip-
ment; applicants should possess a University
Degree, Higher National Certificate or equivalent
qualifications, and preferably have had labora-
tory experience in physics, electrical engineering
or instrument technology.—They should apply,
giving details of qualifications, experience and
desired salary, to Box 4953. [7638

ENGLISH ELECTRIC have a limited number
of vacancies at Hatfield for senior draughts-
men with first-class experience of switchgear or
industrial electronics. Some assistance with
regard to living accommodation may be given
to suitably qualified married men.—Write giving
full details of qualifications and experience to
noting Ref. 141/356 to Central Personnel Ser-
vices, English Electric Co., Ltd., 24-30,
Gillingham St., London, S.W.1. [7652

REQUIRED by an old-established firm at
their research laboratories, Borehamwood,
senior draughtsman for design of special
electronic equipment or mechanical and elec-
trical precision devices; sound general engin-
eering and practical experience, Higher National
Certificate standard preferred; must be capable
of undertaking design work calling for original-
ity and initiative; salary up to £625; five-day
week of 39 1/2 hours. Apply—Box 4185. [7448

BELLING & LEE, Ltd., Cambridge Arterial
Rd., Enfield, Middlesex, require research
assistants in connection with work on electronic
components, fuses, interference suppressors and
television aerials; applicants must be graduates
of the I.E.E. or possess equivalent qualifications
together with similar laboratory experience;
salary will be commensurate with previous ex-
periences; applications must be detailed and
concise, and will be treated as confidential.

ENGLISH ELECTRIC invite applications from
design engineers with radio or electronic
and allied mechanical experience to supervise
small teams of draughtsmen engaged on ex-
perimental radar equipment; must be familiar
with drawing office methods, and should have
qualifications to H.N.C. or Brit. I.R.E.—Apply,
giving full details and quoting ref. 819B to
Central Personnel Services, English Electric Co.,
Ltd., 24-30, Gillingham St., London, S.W.1.

SENIOR circuit engineer is required by the
English Electric Co. for employment in the
London area; experience of designing time bases,
stabilized power packs and cathode ray monitor-
ing circuits is essential; a degree and an interest
in production development is desirable; a good
salary will be paid to the right man for this
responsible position.—Write, giving full details,
quoting ref. 921, to Central Personnel Services,
English Electric Co., Ltd., 24/30, Gillingham St.,
London, S.W.1. [7679

SENIOR technical writer to start and take
working charge of technical literature sec-
tion, and originate instruction booklets, service
manuals, etc., on radio communication equipment
and allied electronic instruments, scope for
initiative, organising ability and good prospects
for energetic man with technical qualifications,
writing experience and willing to take responsi-
bility; salary £700-900 depending on experience.
etc.—Write to Box WW296, L.P.E., 110, St. 77118

SEVERAL electronic engineers or physicists are
required who have graduated in physics or
telecommunications and have two or three years'
radar experience, to take charge of the develop-
ment of particular sections of a project involving
radar.—The work includes design of pulse
generators, timing wave form oscillators, elec-
tronic computers, V.H.F. transmitters and
receivers and servo systems. In addition tech-
nical assistants are needed with H.N.C. or
equivalent qualifications.

ALL the positions available are for work of high
interest in a new and expanding field.
APPLICATIONS, which will receive prompt
attention, should give the fullest details of edu-
cation and professional experience with appro-
priate dates.

APPLY Employment Manager, Vickers-Arm-
strongs, Ltd. (Aircraft Section), Werbridge. 17752

WEST END RADIO LTD.
Estd. 20 YEARS
FOR RADIO BARGAINS

Electronic Stethoscopes as used for the
detection of bomb fuses. Containing the
following:—2 crystal microphones on mag-
netic bases (one under water type), 3 valve
battery amplifier, 'phones, etc., packed in
metal case, 11 x 7 x 5in. Brand nsw, 59/6.
Magnetic Cathode Ray Tubes, type 516,
4-volt heater, blue trace, semi-persistent,
9in. New and unused, 47/6 each.
R.A.F. Engine-drive Generators (will
wind drive) giving 12 v. D.C. 500 watts, 27/6.
Ex-Govt. Motorized Pumps. 24 v. D.C.
Hydraulic type, 27/6 each.

THIS MONTH'S SPECIAL

The Famous C.R. 100. Navy Communi-
cation Receiver. 11 valves 6 ranges with
B.F.O. and Bandpass. 200-250 v. A.C. mains
operation. Reconditioned in our own work-
shops, £29/10/-. Send 6d. for Illustrated
Brochure.

Thousands of bargains for callers. Please
enclose postage with order

WEST END RADIO LTD.
14, LILE ST., LEICESTER SQUARE,
LONDON, W.C.2. Phone GER 9541
OPEN ALL DAY SATURDAY.
NO LISTS AT PRESENT.

RADIO G200 OFFERS

WESTINGHOUSE RECTIFIER UNITS, input
200/250V—50 c.p.s. 40

TYPE 28A. 50v. 0.75 amps. D.C. Price 75/-

TYPE 28B. 50v. 1 1/2 amps. D.C. Price 95/-

TYPE 28C. 50v. 3 amps. D.C. Price 135/-

TRADE & OVERSEAS INQUIRIES INVITED

ARTHUR HOILE 55 UNION STREET,
MAIDSTONE, KENT
Phone 2812

TANNOY
PRODUCTS
SOUND EQUIPMENT
"clearly the best for
all occasions"
WEST NORWOOD S.E.27. Tel. GIPsy Hill 1131 (7 lines)

100 kcs.
**QUARTZ
CRYSTAL
UNIT**
Type
Q5/100

for Secondary Frequency Standards

★ Accuracy better than 0.01%. ★ Temperature
coefficient 2 parts in a million per degree Centri-
grade temperature change. ★ Gold electrodes
applied by cathodic sputtering direct to the faces
of the crystal, giving permanence of calibration.
★ Simple single valve circuit giving strong harmonics
at 100 kcs. intervals up to 20 Mcs. ★ Octal based
mount of compact dimensions. PRICE 45/- Post Free

Full details of the Q5/100 including circuit
are contained in our leaflet Q1. Send stamp
to-day for your copy.

THE QUARTZ CRYSTAL Co. Ltd.
63-71 Kingston Road,
NEW MALDEN, SURREY
Telephone : MALden 0334

AMC

TELEVISION

Manufactured to
"ELECTRONIC ENGINEERING"
TELEVISOR SPECIFICATION
LINE OUTPUT TRANSFORMERS

FOCUS COILS

P.M. Focus Ring R.17. (all Mullard Tubes).
P.M. Focus Ring R.20 & R.25. (all other tubes).

LINE AND FRAME SCANNING COIL ASSEMBLIES

All Steel Cadmium Plated Power and Time Base Chassis valve-holders, 3-point and single socket and all necessary cut-outs. Sound Panel Chassis Assembly, fitted with Screens, valve-holders, formers and dust covers. Vision Panel Chassis Assembly, fitted with screens, valve-holders, formers and dust covers 9in. and 12in. C.R. Tube Support for mounting on top of Gantry assembly. Smoothing Choke (Ch. 9) 5 H., 250 m/A. 5-valve Superhet Radio Chassis. Drilled and fitted with 5 Amphenol Octal valve holders, aerial, earth and gramophone sockets, necessary cut-outs for all control mountings, mains transformer and tuning gang condenser. Complete with 2 steel fixing feet. Cadmium plated.

Full Vision Drive Assembly. Fitted with unbreakable Perspex 3-coloured scale for long, medium and short wave-bands. Calibrated in metres, kilocycles and station names. I.F. Transformers High Q 465 k/c/s.

ALBERT MANUFACTURING CO.
5 SHAKESPEARE ROAD, FINCHLEY, N.3
Telephone: FINchley 2188

SENIOR draughtsmen: Metropolitan-Vickers Electrical Co., Ltd., require for their Trafford Park works a number of senior draughtsmen, preferably with experience in radio and radar equipment; for qualified men these jobs are permanent, five-day week under good conditions.—Apply in writing stating age, experience, qualifications, salary required, etc., marking envelopes "Rad'o D.O.," to Personnel Manager, Metropolitan-Vickers Electrical Co., Ltd., Trafford Park, Manchester, 17. [7424]

MARCONI'S WIRELESS TELEGRAPH Co., Ltd., require engineers for their marine development group for work on radar and echosounding equipment. Applicants should have good academic qualifications and preferably have had experience in one of the above or kindred subjects. A short period training will be given if necessary. Five-day week. Good pension scheme.—Please apply quoting Ref. No. 848A to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [7655]

THE General Post Office has vacancies for radio operators at its coast radio stations and applications are invited from men between 21 and 28 years of age who hold the Postmaster-General's First and Second Class Certificate of Proficiency in Radiotelegraphy. Selected candidates who hold or obtain the First Class Certificate will be considered later for permanent pensionable posts.—Early application should be made to the Inspector of Wireless Telegraphy, G.P.O. Headquarters, London, E.C.1, who will supply particulars. [7476]

B.C.C. requires instructor in engineering training department at Evesham, Worcester; candidates should have degree or equivalent qualification in physics or electrical engineering; knowledge of any branch of radio or broadcast engineering (sound or television) and teaching experience are desirable; salary £655 (may be higher if qualifications exceptional) rising by 5 annual increments to £840 p.a. maximum.—Applications to reach Engineering Establishment Officer, Broadcasters' House, London, W.1, within 7 days. [7741]

RADAR and electronic technicians are required for repair and maintenance of radar and electronic control and computing equipment in the Glasgow and Edinburgh areas. Applicants should have a qualification comparable with the standard of Armament Artificer (R.E.M.E.) or hold National Certificate in Electrical Engineering, or equivalent qualifications. Salary in Scale £437 (at 26), by £20 to £545. Applications should be addressed to A.D.M.E., H.Q. 3 A.A. Group, Riccarton House, Currie, Midlothian, giving details of exp., qualification and age. [7671]

MITCHAM WORKS, Ltd., require a Senior Mechanical Designer; applications are invited from men with Higher National Certificate or equivalent qualifications with workshop plus several years' design experience in the mass production of electronic test equipment to commercial and service requirements. The man required for this position must be capable of taking full responsibility for the projects assigned to him. Salary not less than £650 per annum to the Right man.—Apply to Personnel Officer, Mitcham Works, Ltd., New Rd., Mitcham Junction, Surrey. [7666]

SENIOR and junior development engineers required in the components laboratory of the Plessey Co., Ltd. Vacancies are in connection with the design and development of components mainly for radio and television; for the senior positions a degree in engineering or physics, or equivalent qualification is required, and for the junior positions Inter B.Sc. or Higher National Certificate; salaries in accordance with qualifications and industrial experience.—Applicants should state fullest details of experience to Personnel Manager, The Plessey Co., Ltd., Ilford, Essex. [7683]

SEVERAL vacancies exist in the development laboratory of the General Electric Co., Ltd., Witton, for development engineers in the electronics, electrical machines and protective gear sections; applicants should preferably possess a degree or Higher National Certificate in electrical engineering, but those taking their final examination this year will also be considered; salaries will depend upon qualifications, age and experience.—Apply in writing, giving full particulars and quoting "Development Laboratory," to Staff Manager, General Electric Co., Ltd., Witton, Birmingham, 6. [7691]

E.M.I. ENGINEERING DEVELOPMENT, Ltd., require experienced electronic engineers, including team leaders, for the development and design of radar equipment; applicants should have a sound technical training with a degree, or equivalent qualification, and several years' experience in this field, a thorough knowledge of microwave technique and ability to originate circuitry is essential; the appointments are for permanent pensionable staff and carry a good salary and excellent prospects.—Applicants should write quoting ED/34 and give full details to Personnel Department, E.M.I. Engineering Developments, Ltd., Hayes, Middlesex. [7697]

THE GENERAL ELECTRIC Co., Ltd., Brown's Lane, Coventry, have vacancies for development engineers, senior development engineers, mechanical and electronic for their development laboratories on work of national importance; fields include microwave and pulse applications; salary range £400-£1,250 per annum; vacancies also exist for specialist engineers in component design, valve applications, electro-mechanical devices and small mechanisms; the Company's laboratories provide excellent working conditions with social and welfare facilities; remuneration scheme in assistance with housing in special cases; apply by letter stating age and experience to—The Personnel Manager (Ref. CEO). [7705]

OUTSTANDING VALUE IN BRAND NEW EQUIPMENT

HEARING IS BELIEVING! You are cordially invited to call and hear this new equipment which is commanding increasing interest... and saving people money. Open daily, incl. Sats., 9 a.m. till 6 p.m. If you just cannot call, send two 2d. stamps for full Catalogue and Bargain Supplement. Terms: C.W.O. or C.O.D.

SYMPHONY No. 1 (AMPLIFIER) by N.R.S. The most versatile domestic Audio Amplifier on the market to-day. Independent control of Bass, Middle and Top, separate Scratch Cut, negative feedback. For A.C. 200-250 v., input for magnetic, crystal and hi-fi pick-ups, and Tuner. 5-watts output. Price: 3 ohm model, 9/6; 15 ohm model, £10/7/6, carriage 5/-.

SYMPHONY No. 2 MARK II. New model with 10 watts push-pull triode output, breathtaking realism, hum level negligible—90 db down. Wooden mains transformer, choke and output transformer for 3, 7.5 and 15 ohms. Input for ordinary and hi-fidelity pick-ups. Tone control system same as No. 1. A truly magnificent instrument for only 15 gns., carriage 5/-.

No. 2 PUBLIC ADDRESS AMPLIFIER. Same chassis and power parts as No. 1 Symphony but simple one knob tone control. 15 watts push-pull output. 2 inputs with separate volume controls for fading mike and gram. Complete kit 10 gns. Ready built, £11/19/6.

QUALITY LOUDSPEAKERS: Wharfedale Super 5 C.S. AL Tweeter, 9/2/6, Super 8 C.S. AL. 9/2/6; Golden 10 CBS, 10/7/6; W12 (12in.), 17/0/-; Grampian 12in. 15 watt, £7; Vitavox K12/10 12in. 10 watt, 17/0/-; Wharfedale Super 12 C.S. AL. 29/0/-.

BASS-REFLEX CABINET KITS give superb bass response and top (pat. patent timber). Full instructions supplied. 8in. speaker model 2ft. 6in. high x 1ft. 3in. x 1ft. deep. Price 85/-; 10in. speaker model, 30in. x 16in. x 13 1/2in., 97/6; 12in. speaker model, 30in. x 17in. x 16, 107/6. Any of above ready built for 7/6 extra. Carr. in any case 7/6.

FOR CALLERS ONLY. Above B/R Cabinets also now available, finished in high class veneers to match customers' individual furnishing schemes. Examples on view.

RECORD PLAYER CASES, well made, measure 15 1/2in. x 13 1/2in. x 7in., beautifully covered in brown Rexine, fitted hinged lid, clasps and sprung carrying handle. Price complete with uncut motor board, 57/6, Post 2/6.

DECCA THREE-SPEED GRAM. MOTOR and substantial turntable, fitted precision switch, giving 33 1/3, 45 and 78 r.p.m. Our special offer, £7/3/9, plus 2/6 post.

DECCA LIGHTWEIGHT PICK-UP to match, complete with Acos (78) and Acos (33 1/3) plug-in cartridges with permanent sapphire, £4/4/6; or with either one head only, £2/13/6, post 1/6. Spare heads, 32/6.

ABOVE MOTOR AND PICK-UP with 2 heads fitted in de Luxe leatherette-covered portable case, 15 gns.

NORTHERN RADIO SERVICES
16 Kings College Road, London, N.W.3
Phone: PRImrose 8314

NEW S.T.C. SELENIUM RECTIFIERS. Largest L.T. range in Great Britain. Current products. NOT SURPLUS. E.H.T. H4/200 W.W. Televisor replaced by N2/100, 17/-; for VR97, N2/50 12/-, Post 6d.

NOTE REVISED PRICES 1st JUNE, 1951

HALF WAVE HEAVY DUTY 7 1/2in. SQUARE COOLING FINS. 16 v. 5 a., 26/-; 10 a., 29/-; 16 a., 53/-; 30 v. 5 a., 41/6; 8 a., 47/-; 48 v. 2.5 a., 31/-; 5 a., 56/-; 8 a., 65/-; all post 1/-.

BRIDGE CONNECTED FULL WAVE. 17 v. 1.25 a., 14/2; 1.7 a., 22/9; 2.5 a., 25/-; 3 a., 26/-; 4 a., 30/-; 5 a., 32/6; all post free 33 v. 7 a., 21/-; 1 a., 24/3; 1.5 a., 39/-; 2 a., 44/-; 3 a., 45/-; 4 a., 54/-; 5 a., 58/-; all post 11d. 54 v. 1 a., 33/6; 1.5 a., 54/-; 2 a., 60/-; 3 a., 61/-; 5 a., 81/-; 72 v. 1.5 a., 68/-; 2 a., 79/-; 3 a., 80/-; 5 a., 106/-; 100 v. 1.5 a., 97/-; 2 a., 112/-; 5 a., 152/- all post 1/1

BRIDGE CONNECTED HEAVY DUTY 7 1/2in. SQUARE COOLING FINS. 17 v. 6 a., 43/-; 10 a., 49/- post 1/6.

BRIDGE CONNECTED HEAVY DUTY Funnel Cooled, also

7 1/2in. SQUARE COOLING FINS. Revised price, same both types. 17 v. 12 a., 88/-; 20 a., 102/-; 30 a., 142/-; 50 a., £11; 33 v. 6 a., 79/-; 10 a., 91/-; 12 a., 146/-; 20 a., 164/-; 54 v. 6 a., 104/-; 10 a., 124/-; 72 v. 6 a., 134/-; 10 a., 154/-; 100 v. 6 a., 192/-; 10 a., £11 all post 1/8.

SOME G.E.C. & "WESTINGHOUSE" RECTS. NOW STOCKED.

VERY SLOW DELIVERY OF MANY RECTS. WILL DO OUR BEST! HOSPITALS, RESEARCH LABS. AND GOVERNMENT CONTRACTS GIVEN PRIORITY.

Wholesale & Retail

T. W. PEARCE (Est. 20 yrs.)
66 GREAT PERCY STREET, LONDON, W.C.1
Off Pentonville Rd. - Between King's Cross and Angel

ENGINEERS!

Whatever your age or experience, you must read "ENGINEERING OPPORTUNITIES". Full detail of City & Guilds (Electrical, etc.), MATRIC, i.e., "NO PASS—NO FEE" terms and details of Courses in all branches of Engineering—Mechanical, Electrical, Civil, Auto., Aero., Radio, etc., Building, etc. If you're earning less than £14 a week, tell us what interests you and write for your copy of "ENGINEERING OPPORTUNITIES" today—FREE!

B.I.E.T.
887 Shakespeare Hse.,
17-19, Stratford Place,
London, W.1.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Come to
SMITH'S of EDGWARE ROAD,
 the friendly shop,
 for all radio components

We stock everything the constructor needs—our 25 years' experience of handling radio parts and accessories enables us to select the best of the regular lines and the more useful items from the surplus markets in:—

- | | |
|-------------------------|---------------------------|
| Loudspeakers & Phones | Capacitors & Resistors |
| Transformers & Chokes | Coils & Sockets |
| Meters & Test Equipment | Plugs & Formers |
| Pickup & Turntables | Aerials & Insulators |
| Switches & Dials | Motors & Generators |
| Metalwork & Bakelite | Wires & Cables |
| Books & Tools | Panel Lights & Fuses |
| Valve Holders & Cans | Sleeving, Nuts & Bolts, |
| Metal Rec.ifiers | Tags, Clips, Grommets & |
| Cabinets & Cases | all other bits and pieces |

NOTHING TOO LARGE—NOTHING TOO SMALL

We have one of the largest stocks of B.V.A. Valves & C.R.T.s. (No general catalogue available.)

H. L. SMITH & CO. LTD.
 287/9, EDGWARE ROAD, LONDON, W.2
 Tel. Paddington 5891. Hours 9 to 6 (Thursday 1 o'clock)
 Near Edgware Road Stations, Metropolitan and Bakerloo

EXCEL SOUND SERVICES LTD.

are pleased to announce that they are now accepting orders for their Tape Recorders.

Trade enquiries invited

49, BRADFORD ROAD, SHIPLEY, YORKS.
 Telephone: Shipley 55779 & 51291

TESTSCOPE Mains Tester

For high & low voltage testing:—
 1/30 & 100/850 volts A.C. or D.C. Write for interesting leaflet 30F



RUNBAKEN · MANCHESTER I

TELEPHONE EXCHANGES. Suitable factory office, etc. Contains 18 jacks, five 1,000-ohm relays, terminal board, five Channels, indicators, switches, etc., jack plugs, 1/- each, extra, price 35/-. carriage 2/6.
TELEPHONE SETS. Consists two balanced phones connected 25ft. flex, gives efficient speaking communication to 100ft., no batteries required, price 8/6, post 8d.

Relays, 10/42,000 ohm. Send for list.
 L. O. NORTHALL, 16 Holly Rd., Quinton, B'ham, 32
 Retail: 418 High St., Smethwick. Phone: WOO 3186

TRANSFORMERS

FOR ALL PURPOSES
 SINGLY OR IN QUANTITIES
 FROM OUR STANDARD RANGE
 OR TO YOUR SPECIFICATIONS
GOOD DELIVERIES
REASONABLE PRICES

We have also a department for rewinds giving you a 24 hour service and a better job. Please label all burnt-outs with your name and address when despatching.

P. HOWORTH
 51 POLLARD LANE · BRADFORD

Tel.: 37030

ELECTRONIC engineers are invited to apply for an interesting position in the telecommunications research laboratory of British Insulated Callender's Cables, Ltd., situated at Kirkby, nr. Liverpool; duties include the design and development of electronic instruments for use in connection with cable research and manufacture the minimum qualifications required are a degree in physics or light current electrical engineering and experience in electronic instrument design.—Applications, in writing, should be submitted to The Staff Officer, B.I.C.C. Ltd., Grosvenor Lane, Liverpool, L7 2EN

SENIOR and Junior Development Engineers required in the components laboratory of the Plessey Co., Ltd. The vacancies are in connection with the design and development of components mainly for radio and television. For the senior positions a degree in engineering or physics, or equivalent qualification is required, and for the junior positions Inter. B.Sc. or higher national certificate. Salary will be in accordance with qualifications and industrial experience.—Applications should state full details of experience to Personnel Manager, The Plessey Co., Ltd., Ilford, Essex. [7625]

THE PLESSEY Co., Ltd., Vicarage Lane, Ilford, have an immediate vacancy for a graduate engineer between the ages of 25 and 35 with an interest in light electro-mechanical devices, and another for an electronic circuit designer; applicants must be British born, and should preferably have had some experience in design work in these fields; the posts are progressive and desirable member of a well formed division of the company; salaries will be in accordance with age and experience.—Application should be made, in writing, to the Personnel Manager, quoting reference G.C. [7684]

B.C.C. requires technical assistants, class II (aged 21 or over) for work on an advanced department for service at transmitter, studio, and recording and television centres anywhere in U.K.; knowledge of mathematics and science to school certificate standard and lively interest in radio/television essential, experience in electrical or radio engineering an advantage; starting wage £6/19 with 5 annual increments to £9/0/6; prospects of promotion.—Write to Engineering Establishment Officer, Broadcasting House, London, W.1 (enclosing addressed foolscap envelope) for application form. [7697]

EX R.N. electrical and communications ratings wanted now for Royal Australian Navy; engagement 6 years, excellent conditions and good chances of promotion; free passage for whole family, but remember the housing situation is still critical; Australia has a fine sunny climate, plenty of good unrationed food, low taxes and full social services; basic daily pay, general scale: P.O., 35/-; leading ratings, 29/-; able rate, 26/-; Basic daily pay, artificers scale: 1st class, 36/3; 2nd class, 35/6; 3rd class, 34/9; 4th class, 32/-; General allowances, marriage, 6/-; uniform, 1/9; each G.C. Badge, 4d. Vacancies for ex-ratings: (a) of leading rate and above (electrical); (b) below G.P.O. (communications) discharged from R.N. not more than 5 years ago and not more than 39 years old (44 for artificers); write for full details, stating whether married or single and enclosing R.N. Service certificate, to—R.A.N. Liaison Officer, Dept. W.W., Canberra House, 87, Jermyon St., London, S.W.1.

TECHNICAL grades II and III required by Ministry of Supply establishment in Norfolk; duties: preparation of schedules of radio and radar equipments and installations involving the breaking down into assemblies, sub-assemblies and components for provisioning action; instructional memoranda on the installation of radio and radar equipment in service aircraft; qualifications: British, of British parentage; recognised apprenticeship followed by a few years' experience in an appropriate trade and preferably possess the Higher National Certificate (Ordinary National Certificate for Technical Grades II) or City and Guilds Certificate in relevant subjects; should be able to interpret drawings, circuit diagrams and specifications; knowledge of Component Standardisation Committee specifications and procedure an advantage; salaries: technical grade II £540—£645 p.a. (one post), technical grade III £437—£545 p.a. (two posts); unestablished opportunities for establishment may arise.—Application forms from Ministry of Labour and National Service, Technical and Scientific Register (K), York House, Kingsway, W.C.2, quoting reference No. D454/51A. Closing date December 11, 1951. [7646]

SITUATIONS WANTED
WIDELY-experienced engineer (39) production, trouble-shoot, depot and field service, radio, television, radar, accustomed control labour and handle technical correspondence, present responsible post in southern England; requires salary £570, not interested in less.—Box 4975.

BUSINESSES FOR SALE AND WANTED
LONDON N.W.7. — Magnificently situated wireless and television business for disposal as a going concern, advantageous terms of lease, and excellent annual turnover; price for lease and goodwill £2,000; s.a.v.—Gladling Son & Wing, Chartered Surveyors, 8-11, Pavilion Buildings, Brighton. [7698]

PAINTS, CELLULOSE, ETC.
PAINT spraying handbook 5/6, post free; cellulose and synthetic paints and all spraying requisites supplied; catalogue free.—Leonard Brooks, 53, Harold Wood, Romford. [70207]

TECHNICAL TRAINING
CITY & GUILDS (Electrical, etc.) on "No Pass—No Fees" terms. Over 95% success for full details of modern courses in all branches of Electrical Technology send for our 144-page handbook, free and post free.—E.I.E.T. (Dept. 388A), 17, Stratford Place, London, W.1.

WILKINSON'S of CROYDON

AUTO TRANSFORMER. 230/115 volts 500 watts 50 cycles, fully shrouded, new. Made by Met. Vic. £4/10/- each.
RECTIFIERS SELENIUM. ½ wave 12 v. 200 mA. 2/6 each; 444 v. 40 mA., 9/3 each; Voltage Doubler, 168 v. 40 mA., 7/6 each; Bridge type 24 v. 75 mA., 3/4 each; 36 v. 2.5 amp. 27/- each; 48 v. 75 mA., 5/7 each; 48 v. 150 mA., 6/10 each; 96 v. 600 mA., 31/- each; 96 v. 2.5 amp., 66/- each.

ELECTRONIC IGNITION TESTER. Type U.E.D. English Electric, Incorporating Cathode Ray Tube giving a visual trace of the complete ignition cycle enabling the electrical performance of the entire system to be observed whilst the engine is running. Operates on 230 Volts A.C. also 6, 12 and 24 volts D.C. Brand New. £35.

TEST SET 205. Wavemeter range. 3.05 to 3.35 centimetres, built-in oscillator with 9 valves including Klystron type CV.129, etc., in good condition. £20.

PHOTOMULTIPLIER NO. 931A. With network. Contained in transmitting unit APQ9. £5. Cge. and pkg. 10/-.
 We hold very large stocks of RELAYS, CONDENSERS, RACKS FOR 19in. PANELS, SLIDLOCK FUSES, SANTON AND ARROW SWITCHES.

19 LANSDOWNE ROAD, CROYDON
 CR0 0B39.

MAGNETIC TAPE RECORDERS and COMPONENTS

from
WILL DAY, LIMITED

19 Lisle Street, London, W.C.2.
 GERrard 7105 and 4476

SEND 1d. STAMP FOR LIST — SENT BY RETURN

LOCKWOOD

makers of
Fine Cabinets
 and woodwork of every description for the Radio and allied trades

LOCKWOOD & COMPANY

Lowlands Rd., Harrow Middlesex. Byron 3704

The VOIGT Loudspeaker is still ahead of all others. P.M. Unit with 23,000 line gap flux 240 ex works.

Order from
VOIGT PATENTS LTD.
 Sydnam, S.E.26 SYD 5666
 Sole makers of VOIGT Products

ANOTHER OF BROOKES FAMOUS CRYSTALS

TYPE "SM"
 Range 3 to 17 mc/s.
 Hermetically sealed metal can 1.125" high under pins, 0.825" wide, 0.457" thick, with 3/32" diameter pins at 0.490" centres.

BROOKES CRYSTALS LTD.
 10, Sockwell St., Greenwich, London, S.E.10.
 Phone: GREENwich 1828. Cables: Xtals London.
 Grams: Xtals Green London.

TELEVISION

THE GOTHIC TELEVISION SCHOOL, devoted exclusively to training in television, prepares students to Brit.I.R.E., and R.T.E.B. examination standards; correspondence course prospectus from the Principal, Gothic Television School, 13, North Avenue, London, W.15. [0051]

RADIO training—P.M.G. exams. and I.E.E. Diploma; prospectus free.—Technical College, Hull. [0111]

WIRELESS operating; attendance and postal courses.—Stamp for reply to Manager, The Wireless School, Manor Gdns, London, N.7.

NOTHING succeeds like success! What we have done a thousand times we can do again, for you.—See the B.N.R.S. advt., page 104.

SEE the world, 600 Radio Officers required; send 2d stamp for prospectus to Britain's leading college; we train most, in shortest period, at lowest cost.—Wireless College, Colwyn Bay.

A.M.I.Mech.E.—A.M.Brit.I.R.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams and courses in all branches of engineering, building, etc., write for 144-page handbook—free.—B.I.E.T. (Dept. 327B), 17, Startford Place, London, W.1. [0118]

TELEVISION postal course for radio trades Examination Board's diploma; also postal courses for P.M.G. 2nd and 1st class Certificates and Amateur Radio Transmitting licence.—Apply British School of Telegraphy, Ltd., 179, Clapham Rd. London, S.W.9. (40 years' experience in coaching students in wireless telegraphy and allied subjects.) [0124]

YOUR METER DAMAGED?



Leading Electrical Instrument Repairers to the Industry

Contractors to The Ministry of Supply. Repairs by skilled craftsmen of all makes and types of Voltmeters, Ammeters, Microammeters, Multirange Test meters, Electrical Thermometers, Recording Instruments, Synchronous Clocks, etc. Quick deliveries—for speedy estimate send defective instrument by registered post to:—

L. GLASER
Electrical Instrument Repairers
341 CITY ROAD, E.C.1
Tel. Terminus 2489

WANTED

Post Office Relays, all types.
P.O. Hand Generators, type C.
Impulse Switches, any condition, large or small quantities.

BOX 4657, c/o "Wireless World"

QUALITY TELEVISION COMPONENTS

Scanning and Focus Coils
P.M. Focus Units
5/10 Kv. R.F. E.H.T. Units
E.H.T. and Output Transformers
Line By-back E.H.T. Units
"TELEVISION CIRCUITS"
3rd Edition, 2/6
HAYNES RADIO LTD.
Queensway Enfield Middlesex

TAMSA
TAPE & WIRE RECORDING
We supply ALL RECORDING COMPONENTS. Write for Latest Price List of:—
TAPE MECHANISMS, TAPES, WIRES and SPOOLS, HEADS, AMPLIFIERS, OSCILLATOR COILS and UNITS.
NOW AVAILABLE—The New Type HIGH COERCIVITY EMITAPE TOPHET M. High Quality Recording Wire.
Constructors' Envelopes. Books on Tape Rec'd'g.
Manufactured by
AUDIGRAPH LTD.
Dept. MR3, 74, Great Hampton Street, HOCKLEY, BIRMINGHAM, 18

THE Institute of Practical Radio Engineers have available home study courses in every phase of radio and television engineering specialising in the practical training of apprentices in the retail trade; enrolments limited, fees moderate.—The Syllabus of Instructional Text may be obtained post free from the Secretary, I.P.R.E., Fairfield House, 20, Fairfield Rd., Crouch End, London, N.8. [0088]

FREE! Brochure giving details of home study training in radio, television and all branches of electronics, courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E. City and Guilds Telecommunications, R.T.E.B., and other professional examinations; train with the college operated by Britain's largest electronic organisation, moderate fees.—Write to E.M.I. Institutes, Postal Division, Dept. W.W.28, 43, Grove Park Rd., London, W.4, Chiswick 4417. (Associated with H.M.V.) [0001]

BOOKS, INSTRUCTIONS, ETC.
"RADIO Servicing" by Abraham Marcus. A practical guide to the methods of finding faults together with a complete technical background of theory and practice; 36/- (post free).—Write to Allen & Unwin, 40, Museum St., W.C.1, for descriptive leaflet. [7779]

I.P.R.E. Technical Publications; 5,000 alignment peaks for superheterodynes, 4/9 post free; The Practical Radio Engineer, quarterly publication of the Institute, same as copy 2/- post free; membership and examination data 1/- post free.—Secretary, I.P.R.E., 20, Fairfield Rd London, N.8. [0089]


BRASS, COPPER, DURAL, ALUMINIUM, BRONZE
ROD, BAR, SHEET, TUBE, STRIP WIRE.
3,000 STANDARD STOCK SIZES

No Quantity too Small. List on application.
London: H. ROLLET & Co. Ltd. Liverpool: 6, Chesham Place, S.W.1. Kirby Estate, W.C.1 Oanc 3463 SIMONSWOOD 3271/3

TOROIDAL WINDING CAPACITY AVAILABLE

BEL SOUND PRODUCTS CO.
Marlborough Yard, London, N.19
Tel: ARChway 5078

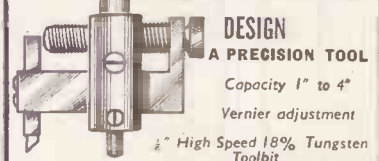PARALEX ADJUSTABLE HOLE CUTTER
Selected by the COUNCIL of INDUSTRIAL DESIGN



A PRECISION TOOL
Capacity 1" to 4"
Vernier adjustment
1/2" High Speed 18% Tungsten Toolbit
P.L. round parallel shank 16/- each (incl. post) essential parts case-hardened
Wholesale and Export Enquiries solicited
ALFA PRECISE INSTRUMENT CO.,
111, Greencroft Gardens, London, N.W.6

ELECTRONICS DUPLEY LTD.
CRANMER AV. EALING, W 13.

Transformer and Coil Manufacturers to the Trade
Telephone: EALing 5638

TRANSFORMERS & COILS TO SPECIFICATION.

MANUFACTURED OR REWOUND
Filter Coils ± 1% a Speciality.
JOHN FACTOR LTD.
9-11 EAST STREET, TORQUAY, DEVON
Phone: Torquay 2162

• Radiospares • Quality Parts

THE SERVICE ENGINEER'S FIRST CHOICE

| | |
|---------------------------|------------------------------------|
| CONDENSERS | Silver Mica · Tubular · Mansbridge |
| CRYSTALS | American · British |
| HEADPHONES | High and Low Impedance |
| METERS | Thermo · Moving Coil · Moving Iron |
| PLUG & SOCKETS | All Types |
| RESISTORS | Carbon and wire wound |
| VOLUME CONTROLS | Carbon and wire wound |

We hold large and comprehensive stocks of new components and units, both Government and Manufacturers' Surplus

No. 19 Set, Equipment Available.
Wholesale and Export Only.

ANDERS RADIO LTD.
167, HAMPSTEAD ROAD, LONDON, N.W.1
EUS.: 1639 EST. 1928

RADIO DEALERS & SERVICE ENGS. ONLY EXPORT AND IN THE U.K.

Invited to write for our 1951 Complete Price List. Full details of A.W.F. speaker cone assemblies give you fast, cheap, speaker repairs in your own workshops. A.W.F. Transformers and chokes for almost all replacements. A.W.F. Repair Department for repairs to speakers, transformers, Gram. motors, Vac. motors, etc. Current stocks of Tungram Valves, T.C.C. and Dubilier capacitors. Erie Resistors and pots, Components and Cabinets for 'Viewmaster' and 'E.E.' Televisors, and hundreds of other lines.

ENCLOSE POSTAGE 3d. inland, 2/- Overseas Air Mail:

A.W.F. RADIO PRODUCTS
TATLER CHAMBERS · THORNTON ROAD
BRADFORD · YORKS
TEL: 24009 GRAMS & CABLES: "TESTPROD"

INDEX TO ADVERTISERS

| | PAGE | | PAGE | | PAGE |
|---|----------------|--|------------|---|-----------|
| Acoustical Mfg. Co., Ltd. | 29 | Ferranti, Ltd. | 27 | Proffitt, R. W., Ltd. | 10 |
| Acro Electric Tool Mfg. Co., Ltd. | The 18 | Flaiden (Electronics), Ltd. | 30 | Fye Telecommunications, Ltd. | 9 |
| Adcola Products, Ltd. | 62 | Fluxite, Ltd. | 11 | | |
| Advance Components, Ltd. | 33 | Frith Radiocraft, Ltd. | 24, 110 | Quartz Crystal Co., Ltd. | 112 |
| Aerialite Ltd. | 53 | | | | |
| Albert Manufacturing Co. | 113 | Galpins | 95 | Radio Exchange Co. | 62 |
| Alfa Precise Instrument Co. | 115 | Garland Bros. | 88, 89 | Radiomenders, Ltd. | 60 |
| Allan, Richard, Radio, Ltd. | 30 | Gee Bros. Radio, Ltd. | 52 | Radio Merchandise Co., Ltd. | 107 |
| Allen Components, Ltd. | 105 | General Electric Co., Ltd. | 11 | Radio Resistor Co., Ltd. | 37 |
| All-Power Transformers, Ltd. | 50 | Glaser, L. | 115 | Radio Servicing Co. | 110 |
| Alpha Radio Supply Co., The | 106 | Goodmans Industries, Ltd. | 4 | Radiospares, Ltd. | 115 |
| Altham Radio Co. | 54 | Goodsell, Ltd. | 2 | Radio Supply Co. | 60 |
| Ambassador Radio | 58 | Gram-pan Reproducers, Ltd. | 22 | Radio Traders, Ltd. | 50 |
| Amplex Appliances (Kent), Ltd. | 96 | Gray, Arthur, Ltd. | 48 | Rainbow Mfg. Co., Ltd. | 18 |
| Amplivox, Ltd. | 58 | | | Record Electrical Co., Ltd., The | 109 |
| Anders Radio, Ltd. | 115 | Hall Electric, Ltd. | 28 | Reliance Mfg. Co. (Southwark), Ltd. | 106 |
| Antiference, Ltd. | 61 | Hallam, Sleigh & Cheston, Ltd. | 26 | Reosound Engineering & Electrical Co. | 109 |
| Armstrong Wireless & Television Co., Ltd. | 101 | Hartley, H. A., Co., Ltd. | 98 | Reproducers and Amplifiers, Ltd. | 59 |
| Ashworth, H. | 18 | Haves Co., The | 112 | Rialton Radio | 46 |
| Astor Boisselier & Lawrence, Ltd. | 56 | Haynes Radio, Ltd. | 115 | Roding Laboratories | 18 |
| Audigraph, Ltd. | 16 | Henley's, W. T., Telegraph Works Co., Ltd. | 94 | Rogers Developments Co. | 44 |
| Audio-Acoustic Diffusers, Ltd. | 65 | Henry's | 98 | Ro-a Celestion, Ltd. | 16 |
| Automatic Coil Winder & Electrical Equipment Co., Ltd., The | 15 | Hivac, Ltd. | 98 | Rollet, H. & Co., Ltd. | 115 |
| Automatic Telephone & Electric Co., Ltd. | 1 | Holle, Arthur | 112 | Royal Air Force, The | 23 |
| A.W.F. Radio Products | 115 | Holley's Radio Stores | 36 | Runbaken Electrical Products | 108, 114 |
| | | Home-lab Instruments, Ltd. | 56 | | |
| Bakers "Selhurst" Radio | 7 | Howarth, P. | 114 | Salford Electrical Instruments, Ltd. | 38 |
| B. & H. Radio | 111 | H.P. Radio Services, Ltd. | 84 | Sallis, A. T. | 109 |
| Barker Natural Reproducers | 103 | Hyde, J. B. & Co., Ltd. | 20 | Salwey Morgan & Co., Ltd. | 112 |
| Bel Sound Products Co. | 115 | | | Samsons Surplus Stores | 48 |
| Belling & Lee, Ltd. | 69 | Iliffe & Sons Ltd. | 12 | Sangamo Weston, Ltd. | 105 |
| Bennett College, Ltd., The | 16 | International Correspondence Schools | 24 | Savage Transformers, Ltd. | 107 |
| Berry's (Short Wave), Ltd. | 4 | Kolestric, Ltd. | 30 | Scharf, Erwin | 76 |
| Bird, S. S. & Sons, Ltd. | 28 | | | Sifam Electrical Instruments Co., Ltd. | 8 |
| Birmingham Sound Reproducers, Ltd. | 64 | Lasky's Radio | 85, 86, 87 | Simon Sound Service | 13 |
| Bradmatic, Ltd. | 26 | Leak, H. J. & Co., Ltd. | 77 | Smith, G. W. (Radio), Ltd. | 105 |
| Brierley, J. H. (Gramophones & Recordings), Ltd. | 52 | Lewis Radio Co. | 100 | Smith, H. L. & Co., Ltd. | 114 |
| British Chm. (Radio) Ltd. | 90 | Lockwood & Co. | 114 | Sound Sales, Ltd. | 74 |
| British Communications Corp., Ltd. | 52 | London Central Radio Stores | 74 | Southern Radio Supply, Ltd. | 108 |
| British Institute of Engineering Technology | 100, 113 | Lowther Mfg. Co. | 45 | Southern Radio (Worthing), Ltd. | 42 |
| British Insulated Callender's Cables, Ltd. | Cover 11 | L.R. Supply Co., Ltd. | 96 | Spencer-West | 96 |
| | | Lyons Radio | 96 | Sphere Radio, Ltd. | 34 |
| British National Radio School | 104 | Mail Order Supply Co. | 49 | Stability Radio Components, Ltd. | 55 |
| British Physical Laboratories | 44, 59 | Mallex Supply Co. | 110 | Standard Telephones & Cables, Ltd. | 67, 70 |
| British Sarozal, Ltd. | 96 | Major Distributors | 10 | Starr British Products | 106 |
| Brookes Crystals, Ltd. | 114 | Marconi Instruments, Ltd. | 19 | Steatite & Porcelain Products, Ltd. | 17 |
| Brown, S. G., Ltd. | 36 | Marconi's Wireless Telegraph Co., Ltd. | 14, 21 | Stearn Radio, Ltd. | 82, 83 |
| Buchan, A. E. | 39 | Margolin, J. & A., Ltd. | 96 | Stratton & Co., Ltd. | 8 |
| Bulgin, A. F. & Co., Ltd. | 60, Edit. 521 | Marks, C. & Co. | 21 | Studen, A. R. & Co. (Engineers), Ltd. | 18 |
| Bull, J., & Sons | 101 | McElroy-Adams Mfg. Group, Ltd. | 56 | Supacolis | 111 |
| Bullers, Ltd. | 63 | McMurdo Instruments Co., Ltd. | 12, 95 | Szymanski, S. | 36 |
| | | Measuring Instruments (Pullin), Ltd. | 14 | | |
| Cabot Radio Co., Ltd. | 106 | Metroplex, Ltd. | 6 | Tannoy Rentals, Ltd. | 112 |
| Candler System Co. | 108 | Miers, N. & Co., Ltd. | 36 | Taylor Electrical Instruments, Ltd. | 47 |
| Chaffey Cabinet Co., The | 112 | Minnesota Minink & Mfg. Co., Ltd. | 39 | Telectronics, Ltd. | 6, 110 |
| Champion Products | 104 | Modern Book Co. | 102 | Telegraph Condenser Co., Ltd. | Cover 11 |
| Chapman, C. T. (Reproducers), Ltd. | 111 | Modern Electric, Ltd. | 34 | Telegraph Construction & Maintenance Co., Ltd., The | 26 |
| Cinema-Television, Ltd. | 107 | M.R. Supplies, Ltd. | 22 | Tele-Radio (1945), Ltd. | 40 |
| Classic Electrical Co., Ltd. | 25 | M.S.S. Recording Co., Ltd. | 43 | Telsat, Ltd. & Co., Ltd. | 54 |
| Clydesdale Supply Co. | 92 | Milard, Ltd. | 3, 32, 66 | Thermionic Products, Ltd. | 51 |
| Cohen, D. | 91 | Multicore Solders, Ltd. | Cover 19 | Trix Electrical Co., Ltd. | Edit. 519 |
| Collaro, Ltd. | 55 | Murex, Ltd. | Cover 20 | | |
| Cosmocord, Ltd. | 68 | | | Uncles, Bliss, & Co., Ltd. | 28 |
| Cossor, A. C., Ltd. | 72 | Newman, J. & S., Ltd. | 40 | University Electrical Instruments Corp. | 94 |
| | | Northall, L. C. | 113 | University Radio, Ltd. | 93 |
| Davis, Alec, Supplies, Ltd. | 54, 99 | Northern Radio Services | 109 | | |
| Davis, Jack (Relays), Ltd. | 116 | Nusound Products | 109 | Valradio, Ltd. | 50 |
| Day, Will, Ltd. | 114 | | | Venner Accumulators, Ltd. | 58 |
| Donohoe's (Timers) | 112 | Oddie, Bradbury & Cull, Ltd. | 108 | V.E.S. Wholesale Services, Ltd. | 46, 116 |
| Dubilier Condenser Co. (1925), Ltd. | 100 | Olympic Radio Components | 62 | Vitavox, Ltd. | 40 |
| Duke & Co. | 31 | Osmor Radio Products, Ltd. | 32 | Voice Patents, Ltd. | 114 |
| Dupley Electronics, Ltd. | 115 | | | Vortexion, Ltd. | 71 |
| | | Panda Radio Co. | 20 | | |
| Ede's Studios | 100 | Park Radio, Ltd. | 44 | Walton's Wireless Stores | 96 |
| Edison Swan Electric Co., Ltd. | 104 | Partridge Transformers, Ltd. | 97 | Wayne Kerr Laboratories, Ltd., The | 30 |
| Electradix Electrical Co. | 98 | P.C.A. Radio | 60 | Webb's Radio | 61 |
| Electronic Acoustic Developments | 98 | Pearce, T. W. | 113 | W.E. & Co., Ltd. | 24 |
| Electronic Precision Equipment | 78, 79, 80, 81 | Pennine Amplifiers | 108 | West End Radio, Ltd. | 5 |
| E.M.G. Handmade Gramophones, Ltd. | 110 | Phidelity Magnetic Products, Ltd. | 108 | Wharfedale Wireless Works | 38, 46 |
| E.M.I. Institutes | 76 | Philips Electrical, Ltd. | 62, 102 | Whiteley Electrical Radio Co., Ltd. | 42 |
| Enthoven, H. J., & Sons, Ltd. | 57 | Porchester Electrical Supply Co., Ltd. | 104 | Wilco Electronics | 102 |
| Excel Sound Services, Ltd. | 114 | Post Radio Supplies | 110 | Wilson Patents, Ltd. | 114 |
| | | Pratts Radio | 58 | Wolf Electric Tools, Ltd. | 22 |
| Factor, J., Ltd. | 115 | Premier Radio Co. | 41 | Wright & Wearle, Ltd. | 76 |
| Farmer, John | 105 | | | Yuden, C. H. | 56 |



RELAYS AND KEY SWITCHES

LARGEST EX-GOVT. STOCK IN GT. BRITAIN

Types 600-3000 Relays—Siemens High Speed
Also A.C. 400 volts 50 cycles

Uniselector Switches, Telephone Switch-boards, Telephone Components, Plugs, Jacks, Handsets — Government Contractors.

JACK DAVIS (RELAYS) LTD. (DEPT. W.)
36 PERCY STREET, LONDON, W.1
Phones: MUSeum 7960 LANgham 4821

DEALERS & SERVICE ENGINEERS

HOME AND OVERSEAS TRADE

Large stock of servicing accessories for Radio and Television Receivers.

COILS — POTENTIOMETERS — RESISTORS — LOUDSPEAKERS
CONDENSERS — MAINS TRANSFORMERS — CHOKES

Many other useful, low-priced items.

Send for our monthly bulletin, which always announces special bargain lines.

Trade only supplied.



V.E.S. WHOLESALE SERVICES LTD.,
11, GUNNERSBURY LANE W ACTON W.3.
Telephone: ACORn 5027.

Condenser leadership -from the inside!

Unique wire and eyelet assembly ensuring complete mechanical and electrical connection.

Robust outer aluminium casing.

Synthetic rubber bungs giving full hermetic seal.

Heavy gauge aluminium wire secured to the foils.

Pure aluminium foil and paper element.

"All-aluminium" non-corrosive internal construction.

Viscous electrolyte.



T.C.C. "Picopacks" feature a unique yet simple construction which alone makes possible the manufacture of these miniature electrolytic condensers. In keeping with the famous T.C.C. "Micropack" and "Lectropack" ranges, they embody the "ALL-ALUMINIUM" technique using specially developed viscous electrolytes giving good characteristics at high and low temperatures. A range covering working voltages from 6 to 350 D.C. has been standardised, having numerous applications in such small assemblies as are found in car radios, mobile transmitters, hearing aids, etc.



'PICOPACK' ELECTROLYTIC CONDENSERS

(REGD.)

THE TELEGRAPH CONDENSER CO. LTD · RADIO DIVISION · LONDON · W.3 · Tel: Acorn 0061 (9 lines)

THE FINEST CORED SOLDER IN THE WORLD

proved in use over 12 years

BY LEADING MANUFACTURERS OF

Electronic Equipment

During 1939-45, more Ersin Multicore was made and used in the manufacture of electronic equipment for the Services than any other activated, non-corrosive, flux-cored solder in the world.

During 1946-51, the demand for Ersin Multicore increased to such an extent that regular supplies were exported to more than 48 overseas countries—even to the U.S.A., where many home-produced brands can be obtained at a lower price.

HERE ARE SOME OF THE REASONS WHY ERSIN MULTICORE HAS ATTAINED SUCH WORLD-WIDE POPULARITY:—

- The 3-cored construction guarantees flux continuity and prevents "dry" or H.R. Joints.
- Multiple core composition means thinner walls of solder, which result in instant melting.
- The correct proportion of flux to solder is always assured—no extra flux is required.
- Ersin Flux reduces surface tension of molten solder, causing it to wet metals rapidly. It also cleans oxidised metallic surfaces.
- Soldered joints made with Ersin Multicore remain free from corrosion even after prolonged exposure.
- The flux residue is impervious to moisture, hard, non-sticky, non-toxic and avoids accumulation of dirt.
- For more than 12 years, the same unvarying and consistently high quality has been maintained.
- Fully approved by A.I.D., A.R.B., and G.P.O. and complies with U.S. Govt. specifications, B.S.S. 219 & 441 and M.A.P., D.T.D. 599.

Ersin Multicore is now available in 377 different packings, 2 flux percentages, 8 alloys and 9 gauges. We will be pleased to send to manufacturers, without charge, new technical literature and bulk prices. Service engineers and radio enthusiasts can obtain Size 1 cartons from most radio and electrical shops.

7lb. reel for factory use, Size 1 Carton for Service Engineers.



Ersin Multicore being used in servicing a modern aircraft transmitter-receiver at Airwork's Maintenance Workshops, Gatwick



Assembling television receivers at the DuMont Factories, Newark, U.S.A., with British-made Ersin Multicore Solder



Considerable quantities of Ersin Multicore are used at the factory of the Amalgamated Wireless (Australia) Ltd., Sydney, Australia

SIZE 1 CARTONS 5/- RETAIL

| Catalogue Ref. No. | Alloy Tin/Lead | S.W.G. | Approx. Length per Carton |
|--------------------|----------------|--------|---------------------------|
| C 16014 | 60/40 | 14 | 13 feet |
| C 16018 | 60/40 | 18 | 37 feet |
| C 14013 | 40/60 | 13 | 13 feet |
| C 14016 | 40/60 | 16 | 26 feet |

Ersin Multicore Solder

MULTICORE SOLDERS LTD.,

MELLIER HOUSE, ALBEMARLE STREET, LONDON, W.1 • REGent 1411