

wireless world

OCTOBER 1982 80p

**Electronic
compass**

**Satellite
dish
antennas**

V.d.us

Modular preamplifier

Australia A\$ 2.70
Canada C\$ 3.25
Denmark DKR 33.25
Germany DM. 7.00
Greece DRA 190.00
Holland DFL 8.50
Italy L 3700
New Zealand NZ\$ 3.00
Norway NKR 26.00
Singapore M\$ 5.50
Spain PTS 275.00
Switzerland FR. 7.00
U.S.A. \$ 3.75



Autostore.

Low-cost voice-logging for people with more important things to do.

The problem: logging telephone and radio messages without spending a fortune on equipment or hiring an expensive technician to operate it.

The solution: the new Racal Recorders Autostore.
SIMPLICITY

With its automatic cassette-loading and fully automatic changeover from one deck to another, Autostore can—quite literally—be operated by whoever happens to be around.

And it provides over 24 hours of unattended continuous recording on eight channels.

VERSATILITY

Able to log radio and telephone messages simultaneously, Autostore can form part of a new system—or fit just as easily into an existing one.

And its uses vary from ambulance, fire, police and security applications to the recording of financial transactions, conferences, oil installation communications and taxi services.

Racal Recorders

Racal Recorders Limited, Hardley Industrial Estate, Hythe, Southampton, Hampshire SO4 6ZH, England.
Tel: (0703) 843265 Telex: 47600



RELIABILITY

Available in 4 or 8 channel versions, and with integral micro-processor controlled automatic Timesearch capability to enable rapid message retrieval, Autostore is engineered to the very highest standards by the company which pioneered air traffic control recording techniques.

FULL DETAILS

For full details of Autostore send off the coupon today.



I am interested in recording my communications accurately and reliably. Please:

- send me full details of Autostore
- arrange for a demonstration at my own premises

Name _____

Position _____

Company _____

Address _____

Tel: _____

Racal Recorders Limited, Hardley Industrial Estate, Hythe, Southampton, Hampshire SO4 6ZH, England.

ww



Front cover is John Linsley Hood's new preamplifier, shown on the power amplifier featured in June, July and August: Photograph by Alan McFaden and Alan Kerr.

NEXT MONTH

Two-metre transceiver. Six-mode design with microprocessor control for mobile use. Nine frequency memories are committed by push buttons.

Robin Howes explores the theme that many thoughtful people in responsible positions are concerned about the way industrial societies are going in a two part article on engineers and social responsibility.

Instead of trying to ignore Planck's quantum hypothesis suppose we afford it more than lip service; what then? Dr Murray continues Heretics Guide to Physics by discussing the new situations that would arise.

J. H. Bujs analyses reproduction of binaural recordings via loudspeakers and gives a circuit that also improves headphone reproduction of stereo programmes.

Current issue price 80p, back issues (if available) £1, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hopton Street, London SE1. Available on microfilm; please contact editor.

By post, current issue £1.23, back issues (if available) £1.80, order and payments to EEP General Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Telephones: Editorial 01-661 3500. Advertising 01-661 3130.

Telegrams/Telex: 892084 BISPRS G.

Subscription rates: 1 year £14 UK and £17 outside UK.

Student rates: 1 year £9.35 UK and £11.70 outside UK.

Distribution: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telephone 01-661 3500.

Subscriptions: Oakfield House, Perry-mount Road, Haywards Heath, Sussex RH16 3DH. Telephone: 0444 59188. Please notify a change of address.

USA: \$39 surface mail, \$98.30 airmail. US subscriptions from IPC B.P., Subscriptions Office, 205 E.42nd Street, NY 10017.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd class postage paid at New York.

© IPC Business Press Ltd. 1982 ISSN 0043 6062.

ELECTRONICS
BROADCASTING
AUDIO
OCTOBER 1982

wireless world

COMMUNICATIONS
COMPUTING
VIDEO

Vol 88 No 1561

31 VISION OF THE FUTURE

32 MODULAR PREAMPLIFIER
by J. L. Linsley Hood

37 THE ETHER — AN ASSESSMENT
by H. Aspden

40 COMMUNICATIONS

42 CIRCUIT IDEAS

44 FAULT-FINDING IN MICRO-BASED SYSTEMS
by S. Day

49 ELECTRONIC COMPASS
by N. Pollock

55 INTRODUCTION TO V.D.Us
by C. P. Aidworth

59 AUDIO OSCILLATOR WITH TONE-BURST
by J. T. Tierman

63 LETTERS

67 PARABOLIC ANTENNA DESIGN
by M. L. Christieson

69 PROGRAMMABLE GPIB-TO-SERIAL INTERFACE
by C. Jay

73 EPROM EMULATOR
by P. Nicholls

74 NEWS

77 IMPACT OF THE PHOTON
by W. A. Scott Murray

80 FLOPPY-DISC DRIVES
by J. R. Watkinson

83 METEOSAT HIGH-RESOLUTION IMAGES
by M. L. Christieson

85 SIDEBANDS: PAST, PRESENT AND FUTURE
by D. A. Bell

87 NEW PRODUCTS

ADCOLA

(Regd Trade Mark)

SOLDERING TOOL

TYPE 444

with

Electronic Temperature Control Circuit

contained within the handle



ADCOLA
TYPE 444

DESIGN FEATURES

- NO MOVING PARTS
- NO MAGNETIC EFFECT
- NO MAINS SPIKING

- MINIMAL MAINTENANCE
- FULL RANGE OF PUSH IN SOLDERING TIPS
- FAIL SAFE CIRCUITRY

The Adcola 444 operates from 24VAC. 50 VA. 50/60Hz. supply. Temperature range normally factory set at 360°C is fully variable between 220°C - 420°C. The control circuit is based on a specially designed integrated circuit and uses a thermocouple temperature sensor.

Full specifications and prices from

ADCOLA

(Regd Trade Mark)

ADCOLA PRODUCTS LIMITED

ADCOLA HOUSE, GAUDEN ROAD, LONDON SW4 6LH.
Telephone: 01-622 0291/4 Telex 21851 ADCOLA G

WW - 049 FOR FURTHER DETAILS

PRINTED CIRCUITS

FOR WIRELESS WORLD PROJECTS

Audio compressor/limiter—Dec. 1975—1 s.s. (stereo)	£4.25
Cassette recorder—May 1976—1 s.s.	£5.00
Audio compander—July 1976—1 s.s.	£4.25
Audio preamplifier—November 1976—2 s.s.	£8.50
Additional circuits—October 1977—1 s.s.	£4.00
Stereo coder—April 1977—1 d.s. 2 s.s.	£8.50
Low distortion disc amplifier (stereo)—September 1977—1 s.s.	£2.00
Low distortion audio oscillator—September 1977—1 s.s.	£3.50
Synthesized f.m. transceiver—November 1977—2 d.s. 1 s.s.	£12.00
Morsemaker—June 1978—1 d.s.	£4.50
Metal detector—July 1978—1 d.s.	£3.75
Oscilloscope waveform store—October 1978—4 d.s.	£18.00
Regulator for car alternator—August 1978—1 s.s.	£2.00
Wideband noise reducer—November 1978—1 d.s.	£5.00
Versatile noise generator—January 1979—1 s.s.	£5.00
200MHz frequency meter—January 1979—1 d.s.	£7.00
High performance preamplifier—February 1979—1 s.s.	£5.50
Distortion meter and oscillator—July 1979—2 s.s.	£5.50
Moving coil preamplifier—August 1979—1 s.s.	£3.50
Multi-mode transceiver—October 1979—10 d.s.	£35.00
Amplification system—Oct. 1979—3 preamp 1 poweramp	£4.20 each
Digital capacitance meter—April 1980—2 s.s.	£7.50
Colour graphics system—April 1980—1 d.s.	£18.50
Audio spectrum analyser—May 1980—3 s.s.	£10.50
Multi-section equalizer—June 1980—2 s.s.	£8.00
Floating-bridge power amp—Oct. 1980—1 s.s. (12V or 40V)	£4.00
Nanocomp 6802 or 6809—Jan., July, 1981—1 d.s. 1 s.s.	£9.00
Cassette interface—July, 1981—1 s.s.	£1.50
Eprom programmer—Jan., 1982—1 d.s.	£4.50
Logic probe—Feb., 1981—2 d.s.	£6.00
Modular frequency counters—March, 1981—8 s.s.	£20.00
Opto electronic contact breaker (Deico)—April, 1981—2 s.s.	£4.00
CB synthesiser—Sept.—1 d.s.	£6.00
Electronic ignition—March, 1982—1 s.s.	£4.00

Boards and glassfibre roller-tinned and drilled. Prices include VAT and UK postage. Airmail add 30%, Europe add 10%. Insurance 10%. Remittance with order to:

**M. R. SAGIN, NANCARRAS MILL, THE LEVEL
CONSTANTINE, FALMOUTH, CORNWALL**

WW - 016 FOR FURTHER DETAILS

PRODUCTION TESTING

DEVELOPMENT

SERVICING

POWER UNITS

Now available with
3 OUTPUTS



Type 250VRU/30/25

OUTPUT 1: 0-30v, 25A DC

OUTPUT 2: 0-70v, 10A AC

OUTPUT 3: 0-250v, 4A AC

ALL
Continuously
Variable

Valradio

VALRADIO LIMITED, BROWELLS LANE, FELTHAM
MIDDLESEX TW13 7EN
Telephone: 01-890 4242/4837

WW - 017 FOR FURTHER DETAILS



THE SOURCE.... of all good used test equipment

Electronic Brokers are Europe's leading Second User Equipment Company. We carry large stocks of the very latest test equipment which is refurbished in our own service laboratories and calibrated to meet the manufacturer's sales specifications. When you buy used equipment from Electronic Brokers, it can be yours in just days. No waiting for manufacturers lengthy production schedules. All equipment is fully guaranteed.

ANALOGUE VOLTMETERS

Bruel and Kjaer
2409 TRUE RMS. Average and Peak 2Hz-200KHz. £250.00

Fluke
845AB Null Detector £810.00
883A AC/DC Differential Voltmeter £815.00

Hewlett Packard
3400A True RMS 1mV-300V 10Hz-10MHz £800.00
3406A 1mV-3V FSD 10KHz-1.2GHz £850.00

Marconi
TF2600A 1mV-100V FSD 10Hz-10MHz £245.00

Racal
9301A RF Millivoltmeter £525.00

Rohde & Schwarz
URV RF-DC Millivoltmeter DC 50 μ V-1050V RF 10KHz-2GHz £950.00

ANALYSERS

Hewlett Packard
3580A Spectrum Analyser 5Hz-50KHz £2950.00

141T/8552B/8555A 10MHz-18GHz £9750.00

332A Distortion Meter 5Hz-600KHz £495.00

8407A/8412A Network Analyser £1950.00

Marconi
TF2331 Distortion Meter 20Hz-20KHz £475.00

Solartron
1172 TFA. £4000.00

Tektronix
7DD1/F2 Logic Analyser in 7704A Mainframe £4950.00

BRIDGES

Marconi
TM4520 Set of Inductors £350.00

Rohde & Schwarz
LRT (BN6100) Inductance Meter. 1pH-100 μ H. 2-285KHz. £395.00

Wayne Kerr
8642 LCR 0.1% £795.00
SR 268 Source & Detector £875.00

DVM's AND DMM's

Fluke
8300A 5 $\frac{1}{2}$ Digit DC only 1 μ V sensitivity 5 ranges to 1100V. £750.00

Philips
PM 2523-01 LED 3 $\frac{1}{2}$ Digit DMM £95.00

Solartron
7055 Microprocessor DMM. Scale Length 20,000. AC/DC volts, resistance. 1 μ V resolution. £495.00

FREQUENCY COUNTERS

Fluke
1920A with Option 13 9 Digit 1GHz £750.00

Hewlett Packard
5340A 8 Digit 10Hz-18GHz £3750.00

OSCILLOSCOPES

Marconi
TF2213/1 + TK2214 X-Y Display and memory £550.00

Philips
PM 3234 True Dual Beam Storage Oscilloscope 10MHz New CRT. £1750.00
PM 3244 50MHz 4 Channel Delay T'Base £1500.00

Tektronix
475 Dual Trace 200MHz Portable £2000.00
7313 100MHz Storage Mainframe £2225.00

7603 100MHz Mainframe with 7A18N and 7B53N £3000.00
7704A 200MHz Mainframe c/w 7A22 Diff. Amplifier, 7A26 Dual Channel, 7B80 Timebase and 7B85 Delaying Timebase £4810.00

7904 500MHz Mainframe £4500.00
S1 Sampling Head. As New £4500.00
7D14 Digital Counter plug-in 525MHz £950.00

434 Option 01 Storage Oscilloscope 25MHz £2250.00
P6015 HV Probe £295.00

Tequipment
DM63 Storage Oscilloscope Fitted with 2 x V4 Plug-ins to give 4 Trace 15MHz £1350.00
CT 71 Curve Tracer £450.00

Texscan
DU120 12" Display £425.00

RECORDERS

Hewlett Packard
7045A X-Y Plotter T'Base Metric £1150.00

Watanabe
MC641 6 Channel 250mm Chert Recorder £1495.00

Yokogawa
3047 2 Channel 2 cm/HR - 60cm/MIN £550.00

SIGNAL SOURCES

Hewlett Packard
4204A Decade LF Oscillator. 10Hz-1MHz. 1mV-10V into 600 Ω . £695.00

606B AM Signal Generator. 50KHz-65MHz. AM 0-95% £850.00

608F 10-455MHz AM/PCM Modulation 0.1 μ V-1V output. £800.00

616B 1.8-4.2GHz int or ext PCM/FM 0.1 μ V-0.224V £1000.00

651B Test Oscillator. 10Hz-10MHz. 0.1mV-3.16V £415.00

3320A Frequency Synthesizer. 0.01Hz-13MHz £995.00

8616A Signal Generator 1.8 - 4.5GHz £2000.00

8620C + 86250B Sweep Oscillator 8-12.4GHz P.O.A.

Marconi
TF144H/4 AM Signal Generator. 10KHz-72MHz. 2 μ V-2V £750.00

TF2002B AM/FM 10KHz-98MHz £1200.00

TF2170B Synchronizer for TF2002B £450.00

TF995B/2 AM/FM 200KHz-200MHz £695.00

TF2005R2 Tone Signal Source. 20Hz-20KHz. 0-111dB in 0.1dB steps £295.00

TF2008 AM/FM 10KHz-510MHz built in sweeper. Output 0.2 μ V-200mV £3500.00

TF2016 + TF2173 Synchroniser AM/FM 10KHz-102MHz £2000.00

TF2169 Pulse Modulator for use with TF2015 or TF2016 £200.00

TF 2000 AF Signal Source £365.00

TF 2015 + TF2171 Generator & Synchroniser £1850.00

Philips
PM6456 Stereo Generator. £250.00

Radiometer
SMG1 Stereo Generator £375.00

Telonic
1006A Sweep Oscillator 450 - 850MHz £750.00

TRANSMISSION MEASURING EQUIPMENT

Siemens
D2072 + W2072 Level Meter and Oscillator 50KHz-100MHz £2200.00

W2006 + D2006 Carrier Level Test Set. 10KHz-17MHz. -100 to +10dB £1650.00

W2007 + D2007 Carrier Level Test Set. 6KHz-18.6MHz. -120 to +20dB £1800.00

Wandel and Goltermann
PF-1 Digital Error Rate Measuring Set. Consisting of PFM-1 Digital Error Rate Meter and PFG-1 Pattern Generator £2490.00

SPM-6 and PS-6 Level Measuring Set. 6KHz-18.6MHz. -110dB to +20dB. Mains / battery operation £2150.00

MISCELLANEOUS

Bruel & Kjaer
2209 Sound Level Meter £975.00

Dymar
2085 AF Power meter 20Hz-30KHz 10 μ V-50W input imp 1.2-1000 Ω . £250.00

Ferrograph
RTS 2 Test Set. £355.00

Fluke
3010A Logic Tester: Self Contained Portable. Full Spec. on Request £8500.00

Hewlett Packard
8403A Modulator Fitted With 8732B PIN MDCULATDR £1500.00

8412A Phase Magnitude CRT display for network analyser £1600.00

8482H Power Sensor 100KHz-4.2GHz. AS NEW £250.00

8745A S Parameter Test Set. Fitted with 11604A Universal Arms 0.1-2GHz £2750.00

59308A HP-IB Timing Generator. £300.00

Marconi
TF2162 M.F. Attenuator: 0-111dB £135.00

TF 2502 RF Power Meter DC - 1GHz 10W £525.00

TF2331 AF Distortion Meter £475.00

TF2500 AF Power Meter. 7 ranges 100 μ Watts to 25 watts £275.00

TM8339 AC/DC mixer for use with TF2702 £250.00

Rohde and Schwarz
MSC Stereo Coder. 30Hz-15KHz £500.00

Schaffner
NSG 509 Pulse Test Generator £785.00

Shackman
Super 7 MKII Camera £275.00

Tektronix
141A PAL Test Signal Generator £1750.00

1481C PAL TV Waveform Monitor £2375.00

191 Constant Amplitude Sig. Gen. 350KHz-100MHz 5mV-5.5V £250.00

106 Square Wave Generator 1nS risetime 10Hz-1MHz without accessories £175.00

284 Pulse Generator 70pS risetime £950.00

1502 TOR £3500.00

2901 Time-Mark Generator £195.00

Please note: Prices shown do not include VAT or carriage.



Electronic Brokers Limited
61/65 Kings Cross Road
LONDON WC1X 9LN
Telephone: 01-278 3461
Telex: 298694 Elebro G

Latest Second User Test Equipment Catalogue now out. Send for your FREE copy



See us at **TESTMEX'82** Stand J7

WW - 200 FOR FURTHER DETAILS


PORTABLE MAINS DISTRIBUTION NOW WITH EARTH LEAKAGE

OLSON

**FOR INSTANT MAINS DISTRIBUTION IN
OFFICES, LABORATORIES, WORKSHOPS
AND FOR MAXIMUM SAFETY**



BEL 5SW
£61, £2.25 P&P + VAT

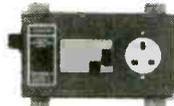

PEL 1
£44.50, £1.50 P&P + VAT




N13A/6
£23.40, £1.50 P&P + VAT



13A/4SW
£22.40, £1.50 P&P + VAT



13A/5/R £25.30, £1.50 P&P + VAT

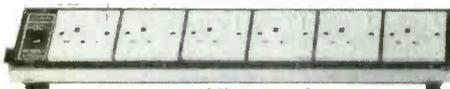

13A/6SW Sloping
£26, £1.50 P&P + VAT




PEL 3
£65, £2.25 P&P + VAT



WEL 2
£52.80, £2.25 P&P + VAT



T13A/5
£21.75
£1.50 P&P + VAT

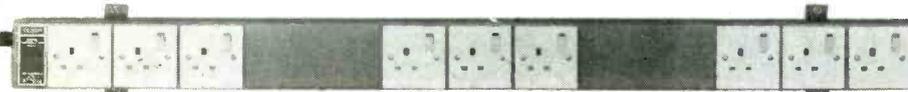

TR9 £38.75, £2.50 P&P + VAT



N13A/3
£16.77, £1.50 P&P + VAT


DELIVERY EX-STOCK

OLSON Electronics Ltd. FACTORY NO. 8, 5-7 LONG STREET
LONDON E2 8HJ Tel: 01-739 2343



WW - 029 FOR FURTHER DETAILS

METER PROBLEMS?

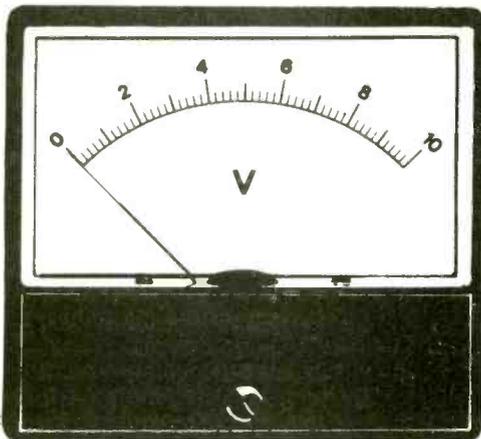

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

HARRIS ELECTRONICS (London)

138 GRAY'S INN ROAD, W.C.1. Phone: 01/837/7937

Telex: 892301 HARTRO G.

WW - 018 FOR FURTHER DETAILS

Time's running out...
for Ni-Cads!

**NEW
NEC
SUPERCAPS**



Available from stock NOW!

1.0 FARAD

SUPERCAP

5101

**C.MOS
R.A.M.**

1 MONTH

1.0 FARAD

SUPERCAP

1703

**Programmable
Tuner Chip**

1 WEEK

1.0 FARAD

SUPERCAP

7507

**C.MOS
Microcomputer**

1 DAY



**Only part of the
Anglia range of
NEC components**

Anglia

COMPONENTS



**THE PARTS YOU NEED
- fast!**

Burdett Road, Wisbech,
Cambs, PE13 2PS
Telephone 0945 63281
Telex 32630 ANGLIA G

WW - 046 FOR FURTHER DETAILS



Hilomast Ltd

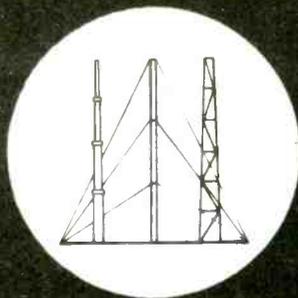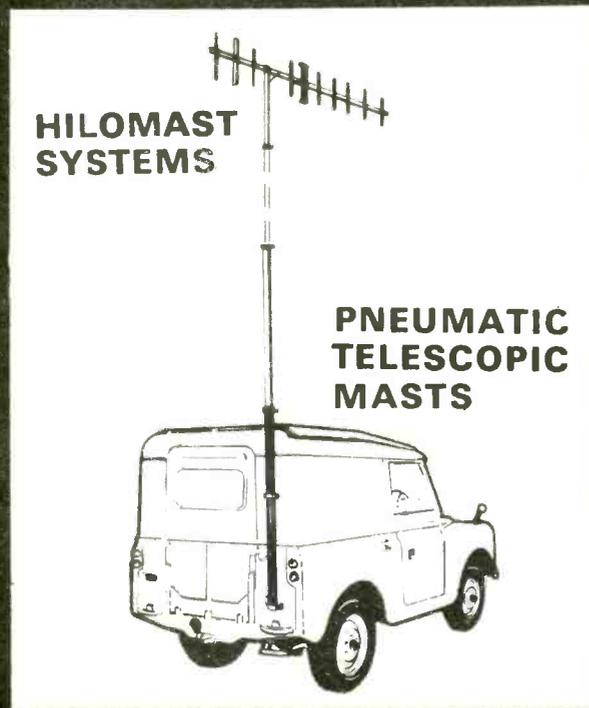

HILOMAST LIMITED
 THE STREET HEYBRIDGE — MALDON
 ESSEX CM9 7NB ENGLAND
 Tel. MALDON (0621) 56480
 TELEX NO. 995855


WW - 043 FOR FURTHER DETAILS

WIRELESS WORLD OCTOBER 1982

New Fluke 4½ Digit Hand-held D.M.M.s

See us at
TESTEX '82
 Stand J4

Now in Stock

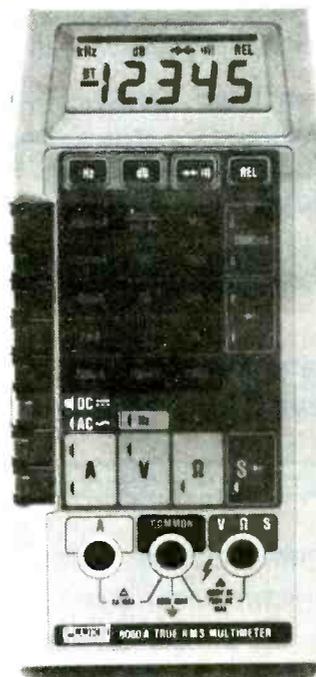

Basic dc accuracy 0.04%; 10 μV, 10 nA and 10 mΩ sensitivity.
 Display annunciators for low battery (BT) and special functions: frequency (kHz), dB, continuity (→←) and relative reference (REL).
 Autoranging M Ω measurements from 2 M Ω to 300 M Ω.
 Conductance functions for resistance measurements to 10,000 M Ω.
 Separate constant-current source diode-test function for checking semiconductor junctions.
 Full range capability for voltage, current, resistance (200 μA, 200 mV and 200 Ω ranges).
 Wideband True RMS AC measurements to 100 kHz.
 Overload protection to 750 VAC or 1000 VDC on voltage inputs and 500 V on resistance. Protection on current inputs provided by a 2A/250V fuse in line with a heavy-duty 3A/600V fuse.
 Sophisticated self-diagnostics provided for all range and function selections plus LCD display, battery and CMOS circuitry.
 Fluke's 8062A makes many of the same measurements as the 8060A, at a lower price.
 Continuity and relative reference functions identical to 8060A.
 True RMS measurements to 30 kHz.
 Basic dc accuracy 0.05%; 10 μV, 10 nA and 10 mΩ sensitivity.

Fluke 8060A £275.00
 Fluke 8062A £210.00

Fluke 8022B With 2 year warranty	£95.00
Fluke 8021B With 2 year warranty	£105.00
Fluke 8020B With 2 year warranty	£135.00
Fluke 8024B With 2 year warranty	£165.00
Fluke 8050A	£305.00
Fluke 8012A	£270.00
Fluke 8010A	£215.00

Mains Model £275.00 Mains Battery £305.00
 Mains Model £245.00 Mains Battery £270.00
 Mains Model £185.00 Mains Battery £215.00

ACCESSORIES

A81-230 Battery eliminator	£15.00
C90 Carry case for hand held	£11.00
801-600 Amp clamp	£75.00
80J-10 Current shunt 10A	£24.00
80K-40 H.V. probe 40kV	£62.00
80K-6 H.V. probe 6kV	£44.00
80T-150 Temperature probe	£79.00
80T-H Touch hold probe	£40.00
83RF R.F. probe 100MHz	£44.00
85RF R.F. probe 500MHz	£76.00
Y8102 Thermocouple probe	£45.00
Y8103 Bead thermocouple	£20.00
Y8104 K type thermocouple termination	£9.00
Y8133 Deluxe test leads	£15.00

Full Specs. on Request.
 The above prices do not include carriage or VAT (15%).



Simply Phone or Telex your order for Immediate dispatch.

Electronic Brokers Ltd
 61/65 Kings Cross Road
 London WC1X 9LN
 Telephone: 01-278 3461
 Telex: 298694 Elebro G
 WW - 201 FOR FURTHER DETAILS




CX80 COLOUR MATRIX PRINTER

New low price
£795 + V.A.T.

At last a low-cost Colour Matrix Printer for Text, Graphics, Histograms, Colour VDU Dumps, etc.

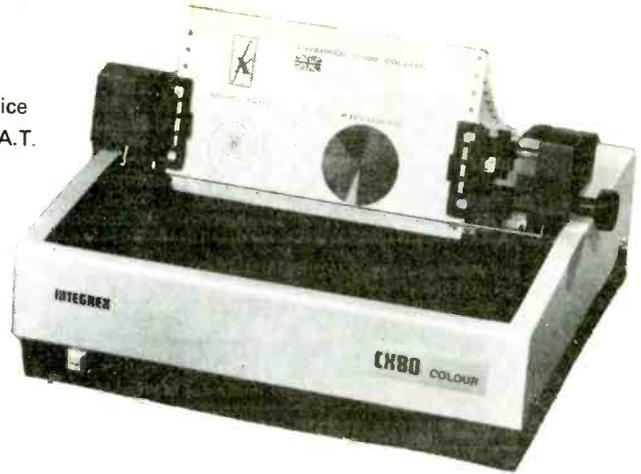Colour printout is quickly assimilated, makes graphics more understandable and is an ideal medium for the presentation of complex data or concepts.



Compatible with most microprocessors, prints in 7 colours – sophisticated internal programme makes the CX80 easy to use.

Dot Addressable + 15 user programmable characters, 96 ASCII and 64 graphics characters in rom. Centronics interface with RS232 and IEEE488 options. Apple II interface gives dot for dot colour dump. New viewdata interface prints out two pages side by side in full colour. See Prestel 200650.

The CX80 is a product of our own design and development laboratories. It represents a British breakthrough in colour printer technology. Colour brochure on request. OEM pricing available.

INTEGREX LIMITED

Portwood Industrial Estate, Church Gresley
Burton-on-Trent, Staffs DE11 9PT
Burton-on-Trent (0283) 215432. Telex: 377106

IN VIEW OF THE EXTREMELY RAPID CHANGE TAKING PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTITIES OF COMPONENTS BECOME REDUNDANT. WE ARE CASH PURCHASERS OF SUCH MATERIALS AND WOULD APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE. WE PAY TOP PRICES AND COLLECT.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho corner
Telephone 445 2713/0749 (9461)

WW - 071 FOR FURTHER DETAILS

RADIATION DETECTORS

BE PREPARED

VIEW THRU LENS

Ideal for the experimenter

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH
- 0-5 R

British design & manufacture
Tested and fully guaranteed. Ex-stock delivery.
As supplied to Fire Services/Civil Defence

HENRY'S

01-723 1008/9

CALLERS: 404 EDGWARE ROAD, LONDON W2 1ED
Mail Orders/Export Enquiries to: 11-12 Paddington Green, London W2

FREE RECHARGE SERVICE AFTER PURCHASE

£6.95

Add. VAT, Post & Packing

COMPLETE WITH DATA

Official Orders welcome



NEW OFF THE SHELF QUALITY ENCODER DISCS

Veco Electroforming Photo-etching Limited, one of the largest European suppliers of custom-designed electroformed and photo-etched components is now offering a range of "off the shelf" encoder discs.

These will enable small users to purchase at highly competitive prices and larger users to carry out initial development work and prototype manufacture prior to purchase of production quantities. In addition, these "off the shelf" designs can also be supplied in larger quantities for production with a relatively short delivery time.

The initial range is as follows:

1. Diameter 30mm 120 slots – Price 1-5 off £5 each
2. Diameter 60mm 120 slots – Price 1-5 off £7 each
3. Diameter 60mm 240 slots – Price 1-5 off £9 each
4. Diameter 60mm 360 slots – Price 1-5 off £12 each

Price reductions available according to quantity.

Specification:

Material Hard Nickel 0.08 to 0.09mm thick.

Centre Hole 10mm ± 20 microns.

Slot Width Tolerance ± 7 microns.

Mark Space ratio 1 to 1.

Angular Tolerances ± 20 seconds.

General Tolerances ± 20 microns.

Delivery is from stock.

Contact: VECO ELECTROFORMING/PHOTO-ETCHING LTD

36 Essendene Road

Caterham, Surrey CR3 5PA

Tel: Caterham (0883) 46062

Please send further details without obligation to:

Name _____ Job Title _____

Company Name and Address _____

Tel. No. _____

WW - 051 FOR FURTHER DETAILS



Bigger and Better for 1982
the colourful Wilmslow Audio brochure
— the definitive loudspeaker catalogue!

Everything for the speaker constructor — kits, drive units, components for HiFi and PA.

50 DIY HiFi speaker designs including the exciting new dB Total Concept speaker kits, the Kef Constructor range, Wharfedale Speakercraft, etc.

Flatpack cabinet kits for Kef, Wharfedale and many others.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our ★
two listening lounges
(Customer operated demonstration facilities)
- ★ Ample parking ★

Send £1.50 for catalogue
(cheque, M.O. or stamps — or phone with your credit card number)

- ★ Access — Visa — American Express accepted ★
- also HiFi Markets Budget Card.



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



WW — 061 FOR FURTHER DETAILS

AUCTION

Appointed by the plant management we are auctioning modern production equipment of the Color-TV-Tube Manufacturing Plant of Messrs.:

VIDEOCOLOR GMBH
D-7900 ULM-DONAUAL, Graf Arco St. 3

Tuesd. Sept. 28, '82
Wednesd. Sept. 29, '82

starting from 9.30 A.M. each day

The following will be auctioned:

approx. 700 measuring and testing units electrical and mechanical, laboratory agitators, measuring devises, degreasing plants, ultra-sonic washing plants, kiln systems, automatic welders, continuous reduction furnaces, AEG-make, planishers, UNGERER RM 900 1/23, hydraulic drawing presses, continuous annealing furnaces, automatic coating machines, automatic foil applicators, vacuum pump units, automatic color-TV picture tube testers, solder applicators, rotary conveyors, foil and acetone reclaiming machines, fully automatic media preparation and mixer systems, neutral ization plant, laboratory equipment, centrifuges, goods wagons, lifting platform, palletizing and racking systems, office furniture and office machines, automatic lathes, machine tools, EDV-system AEG 8020/4 type and many other items. Inspection: on Monday September 27, 1982 from 10 A.M. to 6 P.M. on auction days from 8 A.M. to 9.45 A.M. Preliminary inspection of large plant and equipment can be arranged subject to prior agreement.

Please ask for our detailed catalogue.

HORST F.G. ANGERMANN
HAMBURG VEREIDIGTER U. ÖFFENTLICH
BESTELLTER VERSTEIGERER
SCHÄTZER FÜR
IMMOBILIEN, MASCHINEN UND INDUSTRIEANLAGEN
D-2000 Hamburg 11 · Mattentwiete 5
Telefon (040) 36 76 91-93 · Telex 02-13 303 · 02-15 272

WW — 079 FOR FURTHER DETAILS

We supply HAMEG for Industry

See us at
TESTIMEX '82
Stand J4



HM 307 OSCILLOSCOPE

Single trace DC to 10MHz Rise time 35ns 5mV/cm to 20V/cm Timebase 0.5µs-0.25 Built in component tester LPS technique provides stable and reliable triggering up to 30MHz **£138.00**



HM 203 PORTABLE OSCILLOSCOPE

Dual Trace DC to 20MHz 8 x 10cm display Risetime 17 5nS Sensitivity 5mV/cm-20V/cm Timebase 0.5µs-0.25 x 5 magnifier X-Y operation Auto or variable trigger Channel 1. Channel 2. line and external. Coupling AC, or TV low pass filter Weighs only 6Kg Size (m.m.) H 145. W 285. D 380 **£220.00**



HM412-5

Dual Trace DC to 20MHz 8 x 10cm display with internal graticule Rise time 17 5nS Variable input 2mV-20V/cm. Add and invert modes Timebase 0.5µs-0.25 with sweep delay 100ns-1S x 5 expansion X-Y operation Z modulation Trigger CH1. CH2. CH1/2. Line or EXT **£350.00**



HM705

Dual Trace DC 70MHz 8 x 10cm display with internal graticule Rise time 5nS Variable input 2mV-20V Add and invert modes 95nS Signal Delay Line Timebase 50ns-1S/cm with Sweep delay 100ns-1S x 10 expansion XY operation Z modulation Trigger CH1. CH2. CH1/2 line or EXT **£580.00**

The above prices do not include carriage or VAT (15%).

Simple Phone or Telex your order for immediate dispatch.

Electronic Brokers Ltd
61/65 Kings Cross Road
London WC1X 9LN
Telephone: 01-278 3461
Telex: 298694 Elebro G

WW — 202 FOR FURTHER DETAILS




Electronic Brokers



AMCRON INDUSTRIAL MUSCLE

- ★ POWER RESPONSE DC - 45KHz ± 1dB.
- ★ OUTPUT POWER IN EXCESS OF 1.5KW INTO 2.75 Ohm LOAD: (CONTINUOUS R.M.S.)
- ★ D.C. OUTPUT 20 AMPS AT 100 VOLTS OR 2KVA.
- ★ HARMONIC DISTORTION LESS THAN 0.05% DC-20KHz AT 1kW INTO 6 OHMS.
- ★ PLUG-IN MODULES: CONSTANT VOLTAGE/CURRENT, PRECISION OSCILLATORS.
- ★ UNIPOLAR AND BIPOLAR DIGITAL INTERFACES, FUNCTION GENERATORS, AND MANY OTHERS.
- ★ OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD.
- ★ FULL OPEN AND SHORT CIRCUIT PROTECTION GUARANTEED STABLE INTO ANY LOAD.
- ★ TWO UNITS MAY BE CONNECTED TO PROVIDE UP TO 4kW.
- ★ INTERLOCK CAPABILITY FOR UP TO EIGHT UNITS.
- ★ 3-YEAR PARTS AND LABOUR WARRANTY.
- ★ UNITS AVAILABLE FROM 100VA-12KVA.

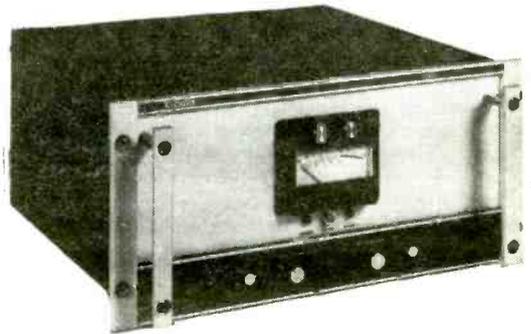

Model - M600

For full details on all Amcron Products write or phone Chris Flack

P.O. BOX 3
ATTLEBOROUGH
NORFOLK NR17 2PF
Tel: 0953-452477

Analogue Associates

PROFESSIONAL INDUSTRIAL ELECTRONICS

WW - 027 FOR FURTHER DETAILS



MICRO-PROFESSOR

YOUR GUIDE TO THE WORLD OF MICROPROCESSORS

A low cost tool for learning, teaching & prototyping.

Micro-Professor is a low-cost Z80 based microcomputer which provides you with an interesting and inexpensive way to understand the world of microprocessors and utilise their unlimited potential.

Micro-Professor is a complete hardware and software system whose extensive manual gives you detailed schematics and examples of programme code. A superb learning development tool for students, hobbyists and microprocessor engineers, as well as an excellent teaching aid for instructors of electrical engineering and computer science courses.

Technical specification

Z80 CPU, 2K RAM, 2K monitor, 24 I/O lines, LED display, cassette interface, CTC/PIO facility, 2.25" speaker, three manuals, 36 keyboard. Options include: EPROM board, speech board and printer board.

Please send or telephone for full details.



(by phone or post)

Complete the coupon today!

Please allow 28 days for delivery.

Please send me:	Price	Qty	p&p
Micro-Professor	£79.95		£2.95
SSB-MPF board	£69.95		£2.95
EPB-MPF board	£84.95		£2.95
PRT-MPF board	£74.75		£2.95
	Total		

I enclose cheque/P.O. for £.....

Name

Address

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

£79.95 + p&p

Now includes 2K BASIC

FLIGHT ELECTRONICS LTD. Flight House, Quayside Rd, Southampton, Hants SO2 4AD. Tel: (0703) 34003/27721. Telex: 477793.

Mail order only • Trade enquiries welcome • Bulk order discounts • Prices include VAT


WW - 005 FOR FURTHER DETAILS

ambit[®] INTERNATIONAL

THE MOST COMPREHENSIVE RANGE OF COMPONENTS, KITS AND MODULES IN THE WORLD & THERE'S ONLY ROOM FOR A FRACTION HERE, GET THE CATALOGUE AND FIND THE BEST.

BAND 2 TUNERHEADS (Varicap Tuning)

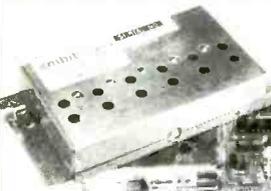EF5804
2 MOSFET of stages MOSFET mixer, JFET IF preamp, with internally amplified PIN diode AGC. Tuning voltage for 88-108MHz is 2.8V. Buffered LO output. AGC input.
145 x 70 x 24mm.
Stock No. 1-24 25+
40-05804 Bit 24.95 19.65



7255 The latest complete FM tunerhead from RF input to stereo output. MOSFET RF stages, HA11225 IF and PLL IC. 7255 special offer price: £30.00 plus VAT




911225A The 911225A is the 7230 "edited" and shrunk into a screened metal case, 97 x 56 x 24mm. The unit is ideally suited to use with synthesised tuner systems.
Stock No. 1-24 25+
40-91225 Built 20.82 16.25

944378 'Hyperfl' series decoder module with the TOKO KB4437 pilot cancel PLL IC birdy filter and the KB4438 muting stereo audio preamp with 26/38kHz pilot tone filtering.
Stock No. 1-24 25+
40-04378 Built 19.95 18.05



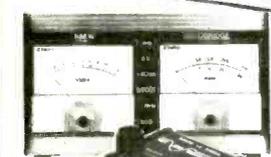DFCM500 Wide range digital frequency/capacitance meter. Frequency ranges: 0-1MHz, 50MHz and 80-500MHz. 8 digit LED display, mains or Ni-Cad battery operation.
Stock No. 1-24 25+
40-01500 Kit 95.95 86.50



AUTOBRIDGE
An automatic power tracking VSWR and self-ranging power meter. Complete Kit: All PCBs, board mounted components, meters, case (lunrilled), transformer etc.
Stock No. 40-40400 £52.86 + £1.50 P&P




FET DIP OSCILLATOR
An essential piece of test equipment for the RF constructor. GDO or WM function covering 1.6-215MHz in five ranges. Audio and meter indication. Kit includes, fibre glass PCB, all components, all hardware, punch, painted and screen printed case, wire etc. for coils and printed scale.
Stock No. 1-24 25+
40-16215 Kit 17.90 16.20



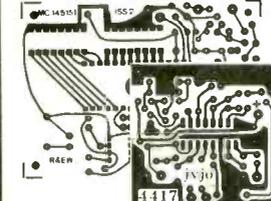10.MHz SSB GENERATOR
PCB, All components, eight-pole crystal filter.
Stock No. 40-10700 Price £29.65

R&E.W PROJECT AND DATABRIEF PCBs

High quality glass fibre printed circuit boards for projects and Databriefs published in Radio & Electronics World.
27MHz Deviation Meter £1.98
PA105 £3.39
TV Pattern Generator £5.70
MC145151 £2.57
2m Pre-amp £0.97
KB4417 (Undrilled) £0.60
0-30V PSU £3.92
2m PA Mk II £5.14
ULN3859 (Undrilled) £0.84
SSB Exciter £3.37
HA12017 £2.16
Up Converter £4.75



2m PRE-AMP
Very compact low-noise MOSFET 2m pre-amp. Gain 22dB. Noise figure, less than 1.5dB. i/p and o/p impedance, 50 ohm size, 34 x 9 x 15mm. From April '82 R&E.W.
Stock No. 1-24 25+
40-14400 Kit 2.55 2.30



70cm PRE-AMP
Compact low-noise pre-amp. Gain at 433MHz: 13dB. i/p and o/p impedance 50ohms. Size 50 x 10 x 17mm. From March '82 R&E.W.
Stock No. 1-24 25+
40-07000 Kit 3.90 3.60



2m POWER AMP
20 watt 144MHz linear power amplifier. 10dB gain, 2W input - 20W output. Automatic switched relay. Bypasses power amp in receiver mode. Developed from original class C version in Dec 81. R&E.W. High power output relay. Pre-drilled heatsink, optional RX pre-amp. Kit only.
Stock No. 1-24 25+
40-14421 Less Preamp 28.50 25.65
40-14422 With Preamp 30.40 27.36

AND THERE'S PLENTY MORE IN THE CATALOGUE 70p inc.

RETAIL SHOP OPENING HOURS

Monday to Thursday 8.30-6.30
Friday 8.30-8.30 Saturday 9.00-6.30
(Access + Barclaycard orders accepted)

NOW IN STOCK

MF10 - National's new Dual Switched - Capacitor Filter.
Price £5.05

ALL PRICES SHOWN EXCLUDE VAT. P&P 50p per order.

AMBIT INTERNATIONAL DEPT. WW
200 North Service Road, Brentwood, Essex
TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

WW - 048 FOR FURTHER DETAILS

WIRELESS WORLD OCTOBER 1982

Electronic Brokers

DEC SALE

a selection from our huge stocks

All items reconditioned unless otherwise stated

WORD PROCESSORS

SPECIAL PURCHASE OF THE BEST-SELLING DEC WS78 WORD PROCESSORS

- * VT78 32KB Video Data Processor
 - * RX01 Dual Floppy Disk Drive
 - * Diablo Letter Quality Printer
 - * Mounted in mobile unit with storage cupboard
 - * Includes complete WP Software package
- £2,850**

SYSTEMS

PDP11V03 SYSTEM

11/03 32KB Processor including Console Interface
RXV11 Dual Floppy Disk Drive and Control
Low Cabinet on Castors
RT11 Licence

£1,525

PDP11/34A SYSTEM

11/34A 128KB Processor
RK611 14MB Disk Drive and Control
RK05 Add-on Disk Drive
LA36 Console
H967 Rack Cabinet

£11,750

PDP11/70 SYSTEM (NEW)

11/70 CPU 512KB MOS
Dual Data System Cab.
RWM03 67MB Disk Drive and Ctl
LA120 Console Printer

£55,000

PROCESSORS

- PDP8A-205 32KW MOS (NEW) £1,750
- PDP8A-400 8KW Core £1,500
- PDP11/04 10 1/2" 32KB MOS £3,625
- PDP11/34A 128KB MOS £5,000
- PDP11/34A 256KB MOS £6,250
- PDP11/40 96KW Core, KT11D £4,650
- PDP11/44 256KB MOS £11,500
- PDP11 X44-CB 256KB TU58 £12,750
- PDP11/7051 2KB MOS (NEW) £43,000
- KMC11A Auxiliary Processor £875

PRINTERS/TERMINALS

- LA36 DECwriter II 20mA £295
- LA36 DECwriter I RS232 £325
- LA34 DECwriter IV £425
- LA180-PD Parallel DECprinter (NEW) £495
- LA180-ED RS232 DECprinter (NEW) £670
- VT50 DECscope 20mA £199
- VT50 DECscope RS232 £225
- VT55 Graphics DECscope £495

INTERFACES

- DL11W Asynchronous I/F £395
- DU11 DA Synchronous I/F £525
- DUP11 DA Synchronous I/F £750
- KL8E Asynchronous (BE) £175
- KL8JA Asynchronous (BE, BA) £275
- M7258 Printer I/F (PDP11) £325
- M8207 Printer I/F (LS11) £175
- M8342 Printer I/F (BE, BA) £225

PDP8A


- PDP8A-205 Processor 10 1/2" 32KW MOS (NEW) £1,750
- PDP8A-400 Processor, 8KW Core, KMBAA, OKCBAA £1,500
- KCBAA Programmers Console £275
- KMBAA Option Module £275
- MMBAA8KW Core Memory £500
- MMBAB 16KW Core Memory £995
- MS8CB 32KW MOS Memory £750
- RX8E Dual Floppy & Ctl (NEW) £995
- RX28 Dual Floppy and Ctl (NEW) £1,450

OPTIONS

- AR11 16 channel A/D £750
- BA11 FE expander box £995
- BA11KF expander box £1,325
- BA11LF expander box £825
- DH11 AC Multiplexor £3,250
- DH11 AO Multiplexor £4,000
- DJ11 AA Multiplexor E1A (NEW) £1,250
- DL11 Serial Interface £250
- DL11W Asynchronous Interface £395
- DM11 DA Line Adaptor £525
- DR11K Digital I/O £425
- DU11 DA Synchronous Interface £525
- DUP11 DA Synchronous Interface £750
- DZ11 A Multiplexor £1,385
- DZ11 B Multiplexor £985
- FP11 A Floating Point £1,500
- FP11 E Floating Point (11/60) £1,975
- H720 Power Supply £175
- H744 Power Supply £125
- H745 Power Supply £90
- H754 Power Supply £175
- H755BB Battery Back-up £485
- H755CB Battery Back-up (11/34) £685
- H755DB Battery Back-up (11/44) £685
- KE11 A Extended Arithmetic £625
- KE11 B Extended Arithmetic £595
- KG11 A CRC module £485
- KIT11 H Bus Interface £250
- KK11 A Cache Memory £1,500
- KT11 D Memory Management (NEW) £750
- KW11 L Real Time Clock £150
- KW11 P Programmable Clock £345
- LP11 Printer Control module £325

DAISY WHEEL PRINTERS

NEW LOW PRICE

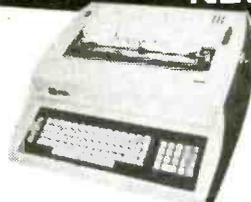

Scoop purchase of factory refurbished Anderson Jacobson AJB32 daisy wheel printers complete with full keyboard, integral stand, and RS232 interface. Utilising the famous QUME Printer Mechanism.

NOW ONLY £750

HAZELTINE VDUS

SAVE UP TO 51%



- HAZELTINE 1510** [MLP £880]. Only **£550**
- HAZELTINE 1520** [MLP £1050]. Only **£625**
- HAZELTINE 1552** [MLP £800]. Only **£395**
- HAZELTINE 1410** [MLP £475]. Only **£295**
- HAZELTINE 1420** [MLP £515]. Only **£350**

Manufacturer's surplus - ALL BRAND NEW BOXED

New Autumn '82 Catalogue now out. Send for your FREE copy now.


ADD 15% VAT TO ALL PRICES

Carriage and Packing extra

Electronic Brokers Ltd., 61/65 Kings Cross Road, London WC1X 9LN. Tel: 01-278 3461. Telex 298694



WW - 203 FOR FURTHER DETAILS

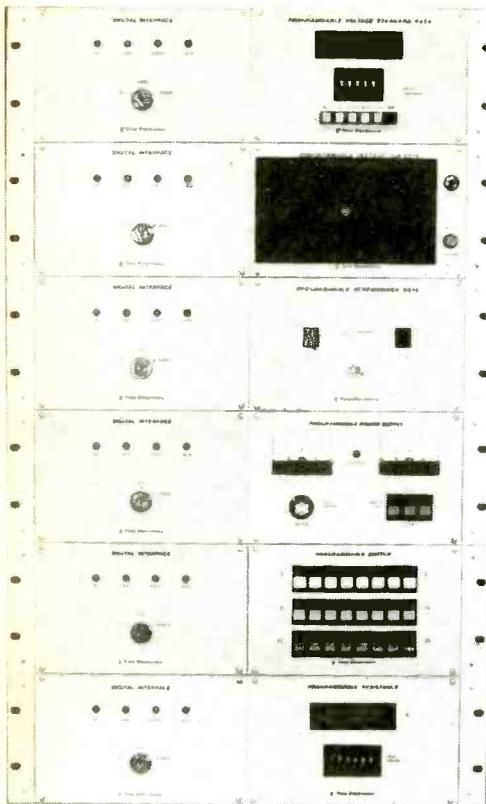

IEEE PROGRAMMABLES from TIME

9814 IEEE PROGRAMMABLE VOLTAGE STANDARD

A higher performance voltage standard with 4 ranges from 0.1 volt to 10 volt output. Accuracy is 0.01% and the resolution of setting is 1 in 200,000. Output resistance is less than 0.01 ohms, and output current adjustable 20mA-200mA. Temperature coeff is less than 20ppm/°C and long term stability better than 50ppm per year. Full manual control is available via front panel controls. Available for benchtop use or 19" rack mounting.

9816 IEEE PROGRAMMABLE VOICE

A high quality speech synthesizer which has a 280 word vocabulary. By suitable programming via the IEEE bus it is possible to output single words, phrases and sentences. The vocabulary has been chosen to be applicable to many ATE applications.

9815 IEEE PROGRAMMABLE SCREWDRIVER

The unit has been designed to overcome the problems of adjusting large numbers of multi-turn trimmers in ATE systems. The screwdriver is fully programmable via the IEEE bus with 3 speeds of rotation and 2 selectable torque values available. The unit is supplied complete with a flexible drive shaft and drill chuck into which various adjusting tools can be located.

9810 IEEE/PROGRAMMABLE POWER SUPPLY

0-33V in 0.1V steps. Local or remote (IEEE) operation. Fully programmable on the IEEE bus with 3 settable current limits 1mA, 10mA and 1.1A. A dual version of the 9810 is also available. The unit is 3 Euro units high and standard 19" rack mounting width.

9812 IEEE PROGRAMMABLE SWITCH

24 double pole changeover switches are available with full IEEE control. Each switch is rated at 1 Amp, 30V dc or 100V ac. Thermal emfs have been minimised to less than 1µV per switch. All outputs are on the rear panel along with the IEEE address selector switch and bus connector. Manual control of the switches is also provided via a set of front panel switches which also incorporate LED indicators.

9811 IEEE PROGRAMMABLE RESISTANCE

0-1 Megohm in 1 Ohm steps, fully programmable via the IEEE bus. Accuracy is 0.1% over most of the resistance range. Resistors are rated at 1 watt each. An attractive feature is the option to switch to local operation when the output resistance can be set up manually via front panel switches.




TIME ELECTRONICS LTD, Botany Industrial Est., Tonbridge, Kent, England TN9 1RS. Tel: (0732) 355993. Telex: 95481



WW - 086 FOR FURTHER DETAILS

Toroidal Transformers

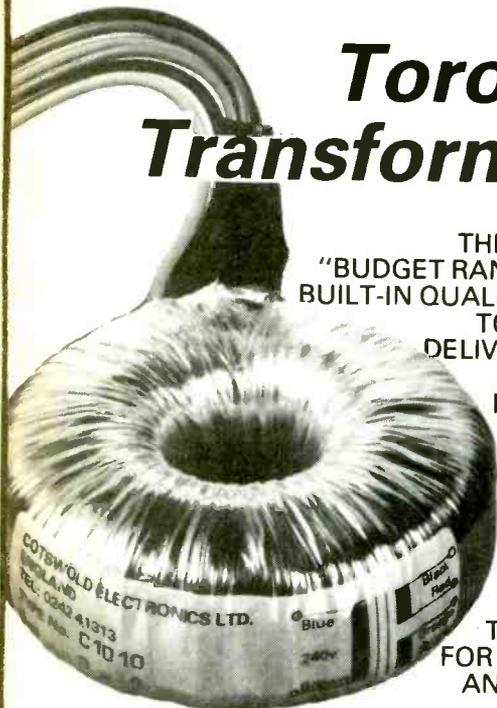

THE COTSWOLD "BUDGET RANGE" OFFERS BUILT-IN QUALITY COUPLED TO A RELIABLE DELIVERY SERVICE MOST TYPES FROM STOCK

IEC 65
VDE 0550
BS 415
TO ORDER

PHONE
TELEX, WRITE
FOR DATA SHEET
AND PRICE LIST

Budget Range Stockist
BARRIE ELECTRONICS LTD.
3 The Minories, London EC3N 1BJ. 01-488 3316

Cotswold Electronics LTD.

Unit T1, Kingsville Road, Kingsditch Trading Estate, Cheltenham GL51 9NX

Tel: 0242-41313

Telex: 897106

WW - 045 FOR FURTHER DETAILS

STABILIZER 4



The Stabilizer is a high quality frequency shifter for howl reduction on speech and music. It offers variable shifts either up or down between 1 and 10 Hertz so allowing choice of the optimum shift for the particular acoustics and sound sources involved in each installation. Rack and box versions.

+5 Hz FIXED SHIFT CIRCUIT BOARDS as WW July 1973 article but improved noise level, lower distortion, adjustment-free oscillator and IC sockets: Mark 4. Small enough to be built inside the cabinets of many amplifiers. Complete kit and board £40. Board built and aligned £56 including psu and mains transformer. DESIGNER APPROVED. C.W.O. loss 5% + V.A.T. 15%.

Stereo Disc Amplifier 3 and 4. 10 Outlet Distribution Amplifier * PPM2 and PPM3 Drive Circuits and Ernest Turner Movements * Illuminated PPM Boxes * Peak Deviation Meter * Programme and Deviation Chart Recorders * Moving Coil Preamplifier * Broadcast Monitor Receiver 150kHz-30MHz.

SURREY ELECTRONICS LTD., The Forge, Lucks Green, Cranleigh, Surrey GU8 7BG
Telephone: 0483 275997

TV TUBE REBUILDING

Faircrest Engineering Ltd. manufacture a comprehensive range of equipment for processing all types of picture tubes, colour and mono. Standard or custom built units for established or new businesses. We export world-wide and have an excellent spares service backed by a strong technical team.

Full training courses are individually tailored to customers requirements.

For full details of our service contact Neil Jupp

FAIRCREST ENGINEERING LTD.

4 Union Road, Croydon, CR0 2XX
01-684 1422/01-684 0246

WW - 056 FOR FURTHER DETAILS

HANDSOME!

First there was the 130. A handheld D.M.M. which still sets the standards our competitors strive to match.

Next came the 131. The introduction of the 135 saw 4½ digits on a handheld D.M.M. for the very first time.

And that same commitment to innovation has resulted in the latest additions to the range. The Keithley 128 D.M.M. with audio-tone and 870 Digital Thermometer with centigrade and fahrenheit readout.

The result is an unrivalled selection of handheld measuring devices. Each specification carefully matched to a given need. With performance that looks pretty good on paper. And even better in the field!



Model 870 ● 0.025% accuracy ● Centigrade and fahrenheit readout ● Measures up to 1370°C

● C. 1° resolution up to 200°C

Model 128 ● Audio-tone with adjustable threshold ● 25 ranges: 5 functions ● 10 amp span

Model 135 ● 0.05% accuracy ● Full overload protection ● ACU bandwidth to 20 KHz

Model 131 ● 0.25% accuracy ● 25 ranges: 5 functions ● 10 amp span

Model 130 ● 25 ranges: 5 functions ● 10 amp span ● 0.5% accuracy

All models are guaranteed accurate for one year. And built to the high standards of quality expected of the Keithley name.

For more information simply fill in the coupon.

And learn about a range which will serve you . . . handsomely!

KEITHLEY

Keithley Instruments Ltd

1 Boulton Road Reading Berkshire RG2 0NL

Telephone (0734) 861287

Telex 847047

Also available from


I.T.T. Instrument Services, Tel. Harlow 29522

WW - 083 FOR FURTHER DETAILS

I would like to know more about your Handheld Units.
Please send me details on D.M.M.'s 870 Thermometer

Name _____ Position _____
Company _____
Address _____
Telephone _____

www/10/82

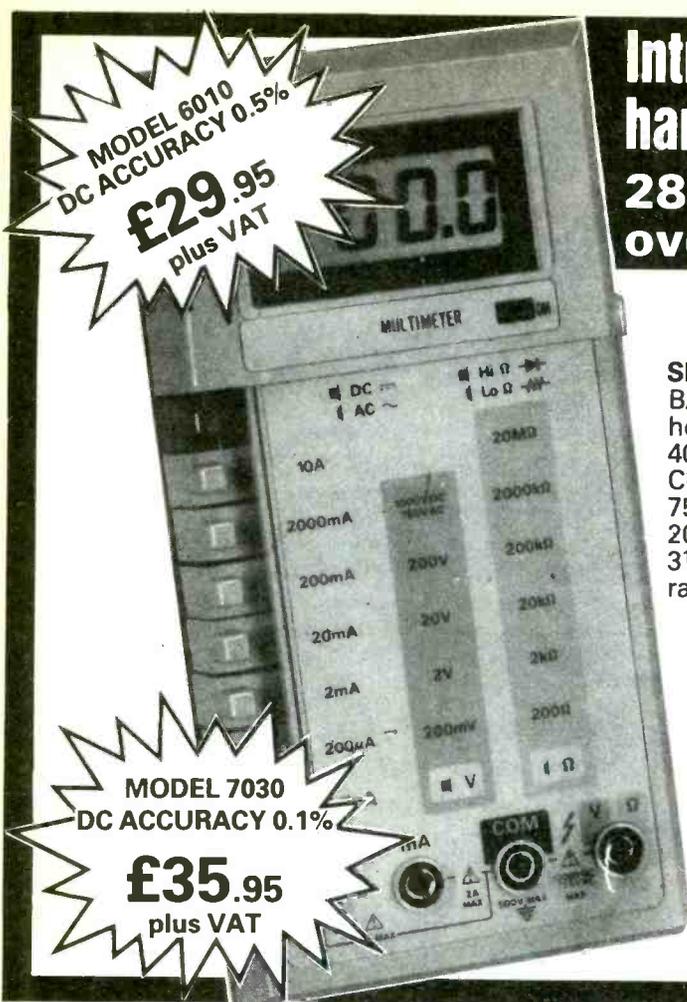

MODEL 6010
DC ACCURACY 0.5%
£29.95
plus VAT

MODEL 7030
DC ACCURACY 0.1%
£35.95
plus VAT

**Introducing two new
hand-held digital multimeters**
**28 Ranges, each with full
overload protection**

10 amp AC/DC

SPECIFICATION 6010 & 7030

BATTERY: Single 9v dry cell. BATTERY LIFE: 200 hours. DIMENSIONS: 170 x 89 x 38mm. WEIGHT: 400g inc. battery. MODE SELECT: Push button. AC DC CURRENT: 200 μ A to 10A. AC VOLTAGE: 200mV to 750V. DC VOLTAGE: 200mV to 1000V. RESISTANCE: 200 Ω to 20M Ω . INPUT IMPEDANCE: 10M Ω . DISPLAY: 3½ Digit 13mm LCD. O/LOAD PROTECTION: All ranges.

OTHER FEATURES:

Auto polarity, auto zero, battery-low indicator, ABS plastic case with tilt stand, battery and test leads included, optional carrying case.

Please add 15% to your order for VAT. Postage and packing is free of charge.

Trade prices available on application.

ARMON ELECTRONICS LTD.

Cottrell House, 53-63 Wembley Hill Road
Wembley, Middlesex HA9 8BH, England
Tel. 01-902 4321 (3 lines). Tlx: No. 923985



WW - 055 FOR FURTHER DETAILS


Double Top

This new addition to the Eddystone range of diecast boxes is supplied with interchangeable deep or shallow, close-fitting flanged lids giving flexibility of application with minimum stocking.

Please write or telephone for details of the new, versatile 10758P box. And ask about the whole Eddystone range of strong, lightweight, corrosion-resistant, diecast aluminium boxes, water-resistant boxes and moulded ABS plastic boxes, in a range of sizes to meet a thousand applications.

STOP PRESS!

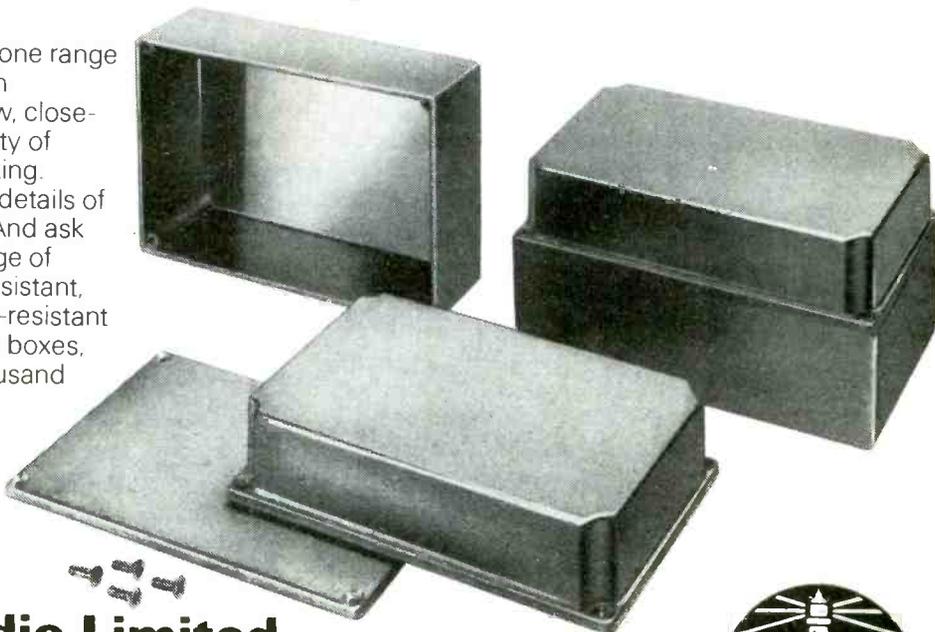The flexibility of deep/shallow and base lids has now been extended to a number of standard sizes.



Eddystone Radio Limited

Member of Marconi Communication Systems Limited

Alvechurch Road, Birmingham B31 3PP, England
Telephone: 021-475 2231 Telex: 337081

A GEC Marconi Electronics Company



WW - 053 FOR FURTHER DETAILS

BUILD A PAIR OF MICRO MONITORS!

Just a few hours easy and interesting work and you'll have a superb pair of compact loudspeakers for about half the price of equivalent 'assembled' models.
The Wilmslow Audio Micro Monitor will stand comparison with any speaker of similar size (at any price!). Don't take our word for it - call for a demonstration!



The Micro Monitor kit contains all the components needed - a pair of cabinets in flat-pack form - accurately machined for easy assembly, all drive units, crossover networks, acoustic wadding, grille foam, velcro, nuts and bolts, etc. No electronic or woodworking knowledge required - simple, foolproof instructions supplied. The cabinets can be stained, painted or finished with iron-on veneer. Dimensions of assembled cabinet: 32x24x20cms. Suitable for amplifiers of 20 - 50 watts.

Price: **£112.95** per pair including VAT. Carriage and insurance £5.50



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS

1982 Catalogue - £1.50 post free

Lightning service on telephoned credit card orders!

WW - 020 FOR FURTHER DETAILS

The new CES micropad



The microphone for mobile radio, with DTMF signalling and optional ANI, brings greater system flexibility to your telecom network.

Interface
Quartz
Devices
Limited

For further information contact the sole agents

IQD

29 Market Street
Crewkerne
Somerset TA18 7JU

Crewkerne (0460) 74433
Telex 46283 infacex g

WW - 019 FOR FURTHER DETAILS

WIRELESS WORLD OCTOBER 1982

MIDWICH HAS MOVED! OUR PRICES HAVE TOO - DOWN!

In order to maintain our standard of service and house our ever growing range of stock, we've moved to larger premises. You can still use our old telephone number for a limited period, but please make a note of our new one and our address.

To celebrate the move we have reduced our prices still further. We know this will displace our competitors, but we'd rather please our customers.
NB - NO SURCHARGE ON CREDIT CARD ORDERS.

Be happy - move with Midwich. And remember, we always try to give you the best deal and the best service. If we fall just let us know - we will always try to make amends.

MEMORIES ** NEW LOWER PRICES **

*2114 Low Power 200ns	0.80	*2732 350ns	4.40	*4164 200ns (T0)	4.85
*2716 450ns (5V)	2.10	*2532 450ns	3.60	*4816/4516 100ns	3.25
*2716 350ns (5V)	3.50	*4116 200ns	0.70	*5516 200ns	9.38
*2716 450ns (3 rail)	5.95	*4116 150ns	1.10	*6116P3 150ns	4.30
*2732 450ns	3.90	*4118 150ns	3.38	*6116LP3 150ns	5.75

BBC MICRO UPGRADE KITS ** NEW LOWER PRICES **

BBC1	4516/4816 X 8 100ns	25.50	BBC21	Printer cable complete	13.00
BBC2	Printer/User I/O kit (IC69,70 + PL9,10)	8.00	BBC22	Connector for user port with 36" cable	2.00
BBC4	Analogue input kit (IC73, 77 + SK6)	8.70	BBC55	Analogue input plug with cover 5 and 6 pin DIN plugs for Serial I/O and RGB input	2.25
BBC5	Serial I/O and RGB kit (IC74,75 + SK3,4)	11.45	BBC66	Connector for bus port with cable	3.50
BBC6	Expansion bus and tube kit (IC71, 72, 76 + PL11, 12)	8.25			

MOST KITS ARE NOW EX-STOCK!

*** We've done it again! Massive price reductions on LPS and CMOS ***

Device	Price	Device	Price	Device	Price	Device	Price	Device	Price
*Z80 FAMILY		*WD1391 KIT	45.50	CRYSTALS		09	0.11	245	0.88
*Z80CPU	3.15	*WD1393 KIT	45.50	1MHZ	2.00	10	0.11	251	0.29
*Z80ACPU	3.50	*WD1395 KIT	45.50	1.008MHZ	2.00	12	0.11	257	0.34
*Z80CTC	2.75	*WD1397 KIT	45.50	1.8432MHZ	2.20	13	0.15	259	0.57
*Z80ACTC	2.95	(KITS INCLUDE		3.6864MHZ	2.95	14	0.33	266	0.19
*Z80ADART	5.70	FD179X + WD2143		4MHZ	1.45	15	0.12	273	0.58
*Z80ADMA	11.95	+ WD1691)		6MHZ	1.45	20	0.12	279	0.58
*Z80PIO	2.75			8MHZ	1.70	21	0.12	283	0.39
*Z80ASIO-0	11.99					26	0.12	365	0.29
*Z80ASIO-1	11.99	MISC SUPPORT		CMOS 4000'S		27	0.12	366	0.29
*Z80ASIO-2	11.99	CHIPS		SERIES		28	0.12	367	0.29
*MK3886	11.00	*AY3-1015	2.99			30	0.12	368	0.39
*MK3886-4	14.47	*AY3-1270	7.95	4001	0.10	32	0.12	373	0.58
		*AY3-8910	5.99	4002	0.12	37	0.12	374	0.84
		*AY5-1013	2.99	4007	0.15	38	0.12	377	0.88
		*AY5-3762	7.95	4011	0.11	40	0.12	390	0.60
		*AY5-2376	5.99	4012	0.15	42	0.12	393	0.44
		*DP8304	4.50	4017	0.15	47	0.12	399	0.44
		*MC1488	0.55	4013	0.24	51	0.14		
		*MC1489	0.55	4015	0.49	54	0.14		
		*MC3446	2.95	4016	0.19	51	0.14		
		*MC3448A	4.25	4017	0.37	74	0.16		
		*MC3480	7.95	4020	0.49	75	0.19		
		*MC3487	2.95	4023	0.15	76	0.17		
		*MC4411	8.94	4024	0.31	83	0.34		
		*MC14412	7.99	4025	0.16	85	0.51		
		*R03-2513L	9.99	4027	0.23	86	0.15		
		*R03-2513U	5.99	4028	0.49	90	0.28		
				4040	0.49	92	0.31		
				4042	0.44	93	0.25		
				4046	0.84	109	0.27		
				*ZM450E	7.61	122	0.35		
				*ZM450 KIT	17.35	123	0.35		
						125	0.24		
						126	0.44		
						132	0.50		
						136	0.59		
						138	0.29		
						139	0.15		
						148	0.14		
						151	0.14		
						153	0.14		
						155	0.29		
						156	0.34		
						157	0.34		
						158	0.25		
						161	0.44		
						163	0.44		
						164	0.39		
						165	0.49		
						166	0.54		
						173	0.89		
						174	0.54		
						175	0.40		
						191	0.44		
						192	0.44		
						193	0.44		
						194	0.34		
						195	0.54		
						221	0.11		
						240	0.11		
						241	0.11		
						242	0.11		
						243	0.11		
						244	0.11		

QUANTITY PRICING

Special prices available for bulk purchases. Tel 0379-898751 for an instant quote. Large stocks held on many items!

FLOPPY DISC CONTROLLERS *FD1771 17.12

Data sheets available on asterisked items. Please telephone for prices and details.

VISA

24 Hour Telephone order service for credit card holders. All prices exclude VAT and carriage (0.75 on orders under £10 nett). Official orders from educational and government establishments, and public companies accepted. Credit accounts available to others (subject to status). All orders despatched on day of receipt. Out of stock items will follow on automatically at our discretion or a refund will be given if requested. **NO SURCHARGE FOR CREDIT CARD ORDERS**

MIDWICH COMPUTER CO LTD


Dept WW, Rickinghall House, Rickinghall, Suffolk IP22 1HH
Telephone (0379) DISS 898751

Please make a note of our new address & telephone number

WW - 007 FOR FURTHER DETAILS

moulded nylon **TRANSIPILLARS**[®]

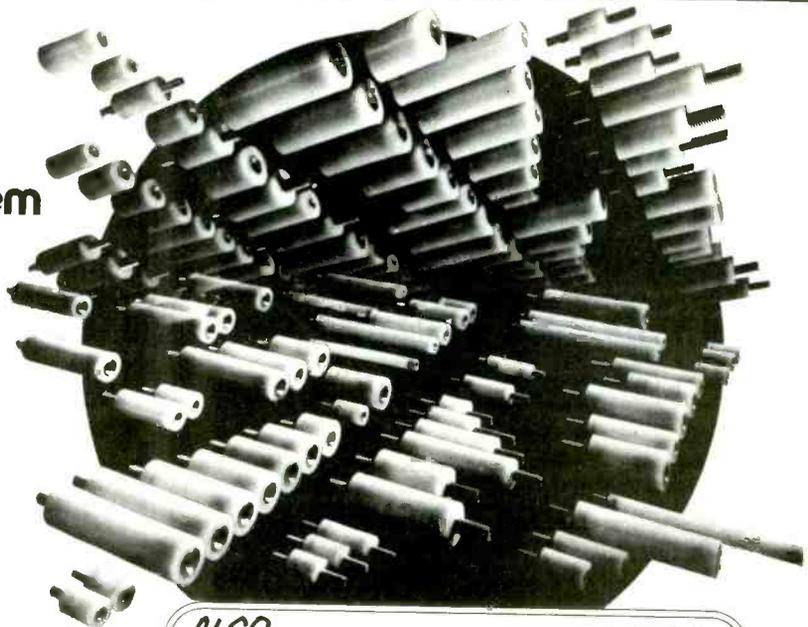probably the most versatile and rugged insulating mounting system ever developed



Transipillar insulating mounts hold heavy sub-assemblies totally secure. Because they're precision moulded from very tough Nylon.

Metric or Imperial versions are available, with insulator lengths from 1/2 in to 2 3/4 in, and a choice of metal screw or threaded insert end fittings from 0 to 6BA.

If one of the preferred sizes won't suit your application, the chances are we can make one that will.

Write today for samples, full technical details and prices of TRANSIPILLARS.

WK ELECTRONICS LTD
 Napier Road Bromley Kent BR2 9JA
 Telephone: 01-464 4346 Telex: 896691 Extn WKE.

ALSO **TRANSIBLOCK**[®]

the patented insulating mount for 1/8 in thick heatsinks. Eliminates the need for power transistor mica washers.



WW - 063 FOR FURTHER DETAILS

WRONG TIME?

MSF CLOCK is ALWAYS CORRECT - never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST, leap year and parallel BCD (including WEEKDAY) output, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, GET the RIGHT TIME, £69.60.

60KHZ RUGBY RECEIVER, as in MSF Clock, serial date output for computer, etc., decoding details and ZX81 listing for local, GMT and SIDEREAL time, £22.20.

Tunable Audio Notch Filter £16.40, **Speech Compressor** £15.30, **Antenna Noise Bridge** £18.60, **10-150KHz Receiver** £19.40.

Each fun-to-build kit (ready made to order) includes all parts, printed circuit, case, postage, etc., instructions, money back assurance so GET yours NOW.

CAMBRIDGE KITS

45 (WK) Old School Lane, Milton, Cambridge. Tel: 860150

LAST CHANCE AT THIS PRICE. METALFILM RESISTORS 1% Tolerance, 1/4 Watt

100R	1k	10k	100k
110R	1k1	11k	110k
120R	1k2	12k	120k
130R	1k3	13k	130k
150R	1k5	15k	150k
160R	1k6	16k	160k
180R	1k8	18k	180k
200R	2k	20k	200k
220R	2k2	22k	220k
240R	2k4	24k	240k
270R	2k7	27k	270k
300R	3k	30k	-
330R	3k3	33k	330k
360R	3k6	36k	-
390R	3k9	39k	-
430R	4k3	43k	-
470R	4k7	47k	470k
510R	5k1	51k	-
560R	5k6	56k	560k
620R	6k2	62k	-
680R	6k8	68k	680k
750R	7k5	75k	-
820R	8k2	82k	820k
910R	9k1	91k	1M

ONLY 3p EACH

High Quality High Stability. Huge Strength.

Minimum order £20
 89 Values (£24)

VAT, p&p inclusive.

SPECIAL OFFER
 10 PCS of EACH (890 RESISTORS)
£23.00

ORION SCIENTIFIC PRODUCTS LTD. 4 GOLDEN SQ LONDON W1

WW - 057 FOR FURTHER DETAILS

THE TL100 HAS BEEN DESIGNED FOR THE PROFESSIONAL ELECTRONICS, TV OR INSTRUMENT TECHNICIAN. CONSTRUCTED FROM HARD-WEARING ABS WITH STRONG ALUMINIUM FRAMES, TWIN HANDLES AND TOGGLE LOCKS. A MOULDED TRAY IN THE BASE, A COMPREHENSIVE 2-SIDED TOOL PALLET THAT IS REVERSIBLE WITH SPACE FOR OVER 40 TOOLS. THERE IS SPACE FOR DOCUMENTS AND A HEATSINK FOR A HOT SOLDERING IRON.

ALSO AVAILABLE IS THE TL99 17in. x 12in. x 6in. £39.90

* DISCOUNT STRUCTURE FOR MULTIPLE USERS ONLY

SIZE TL100 19in. x 14in. x 6in.



£43.70




Telesman Products Ltd
 "Wychwood", 2 Abbots Ripon Rd., Sapley, Cambs. PE17 2LA. Tel: (0480) 57758
 Please send TL100 Professional Toolcases at £43.70 each
 TL99 £39.90. Both inc. VAT (P&P £2.60 extra)

Enclosed my cheque for £.....
 Name.....
 Company.....
 Address.....

WW

The Professional Choice

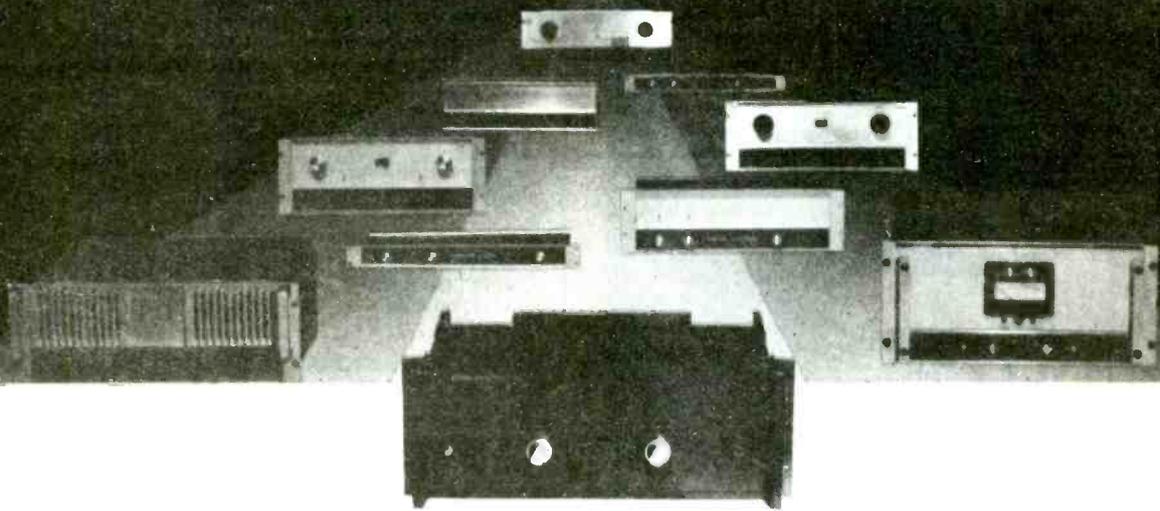

AMCRON 

Since the introduction of the DC300 in 1967, AMCRON amplifiers have been used worldwide – wherever there has been a need for a rugged and reliable amplifier. Their reputation amongst professional users, throughout industry, has made the name of AMCRON synonymous with power amplification. For power you can depend on - choose AMCRON, the professional choice.

For further details contact the UK Industrial distributor:

GAS

G.A.S. ELECTRONICS

16, ST. ALFEGE PASSAGE, LONDON SE10

TELEPHONE: 01-853 5295

TELEX: 923393 LASER G

WW - 025 FOR FURTHER DETAILS

The lightweight mast with 101 applications

25
years in this
specialist field



The smoothly operated QTM Mast comes fitted with handpump or can be vehicle mounted with 'Power Pack' for extension and retraction. Available in a range of heights up to 15 metres, the QTM mast can provide the ideal answer for:

- Mobile Radio Telephone
- Police Mobile HQ (UHF)
- Field Telecommunications
- Floodlighting
- Anemometer and Wind Measurement
- Environmental - gas sampling collector
- High level photography
- Meteorology
- And a host of other uses

CLARK MASTS

Find out more about the QTM series by writing or phoning:-

<p>U.K. CLARK MASTS LTD. (W.W.) Evergreen House, Ringwood Road, Binstead, Isle of Wight, England PO33 3PA Tel: Isle of Wight (0983) 63691 Telex 86686</p>	<p>EUROPE GENK TECHNICAL PRODUCTS N.V. (W.W.) Woudstraat 21, 3600 Genk, Belgium. Telephone 011-380831 Telex 39354 Genant B.</p>
--	--

WW - 028 FOR FURTHER DETAILS

EV88 - A low-cost evaluation system for the 8088 microprocessor

EV88 is a single board microcomputer that is ideal for evaluating the 8088 8-bit/16-bit microprocessor. EV88 can also be used as a powerful controller, and, with a suitable cross-assembler running on a standard microcomputer, and an EPROM programmer, for low-cost development of 8088-based systems.

EV88 is supplied fully assembled and tested, with comprehensive documentation, and a copy of The 8086 Book, by Rector and Alexy. All you need is a 5V 1A power supply and a terminal or a suitable microcomputer.

- ★ 8088 microprocessor in minimum mode (software compatible with the 8086 16-bit microprocessor).
 - ★ Comprehensive monitor in 2K EPROM.
 - ★ 2K CMOS RAM.
 - ★ Cassette interface.
 - ★ 24 lines of I/O.
 - ★ Eight levels of interrupt.
 - ★ RS-232 compatible serial interface (300 baud to 9600 baud).
 - ★ Three-channel counter/timer.
 - ★ Buffered data, address and control lines.
 - ★ Double Eurocard.
 - ★ On-board expansion to 16K EPROM/RAM (sockets provided).
 - ★ Breadboarding area.
 - ★ All bus signals available on 64-way DIN 41612 connector.
 - ★ Single 5V supply.
 - ★ Price £300 plus VAT. Includes delivery.
- 8088/8086 design service available (software and hardware).

LFH Associates Ltd.
40A High Street
Stony Stratford
Milton Keynes
(0908) 564271

WW - 034 FOR FURTHER DETAILS

GREENWELD 443G Millbrook Road, Southampton, SO1 0HX

BULK BARGAINS

All goods new full spec. Prices are for 100 or 1k of one type. Add £1 carriage and V.A.T. to all orders. Send s.a.e. for bulk buyers lists, or 75p for full catalogue (free to schools, etc.).

1/4W 5% Carbon Film Resistors - The following values only: 4R7 5R1 6R2 6R8 8R2 13R 18R 27R 33R 39R 56R 68R 100R 180R 220R 270R 470R 1k 2k7 3k 4k7 12k 18k 22k 30k 33k 36k 39k 75k 200k 220k 240k 390k 500k 620k 680k 1M5 - all at £31/1000.
ALSO: 7 million 1/4W 5% resistors, carbon/carbon film for sale as one lot - £3000.

DIODES		BRIDGES		CMOS		TL	
Type	100+ 1k+	Type	100+	Type	100+	Type	100+
AA132	.04 02	WO1	.15	4520B	.39	7400	.08
133	.04 02	WO2	.16	4528B	.47	7401	.08
BA130	.04 02	WO4	.17	4582	.60	7405	.09
155	.04	WO6	.19	40014	.32	7408	.10
BYX94	.06 04	SO2	.19	74C00	.18	7409	.10
BY127	.07 06	SO4	.22			7410	.10
BY196	.07	SO6	.28			7411	.15
BY197	.07	PW005	.39			7417	.18
BY198	.08	15A100V	1.20			7420	.10
CG50H	.01	12A200V	.65			7426	.20
DK14	.04 02	B80C600	.14			7427	.20
FA2008	.05					7430	.08
FA2001	.05					7437	.19
HG5085	.04					7440	.11
OA2201	.04					7442	.30
OA2208	.04					7445	.30
SX632	.04 03					7447	.32
SX753	.40					7450	.10
IN446	.04					7454	.10
458	.04					7460	.10
459	.04					7472	.18
627	.04					7473	.20
643	.04					7474	.15
3062	.05					7483	.40
3890	.35					7485	.45
4001	.03 02					7490	.20
4002	.03 02					7491	.36
4003	.032 022					7493	.18
4005	.04 027					7496	.39
4006	.044 030					74107	.16
4007	.048 032					74109	.28
4148	.02 013					74121	.22
4149	.03 018					74123	.25
4447	.03 018					74150	.45
4448	.03					74152	.28
4154	.03 018					74179	.65
4742A	.06 045					74180	.45
5243B	.06					74181	.80
5279	.05					74182	.50
5402	.08					74190	.40
5403	.09					74194	.50
5404	.10 .085					74366	.40
5405	.11						
5406	.12						
IS101	.05						
410	.10						
423	.25						
921	.05 032						
IS4402A	.07 .05						
5056A	.07						
25G10	.97						

Tant Beads: 2.2/16 .04; 10/35 .16; ITT PMT POLYESTERS: .01/400 02; 22/100 .023; 33/100 .025; 47/100 028; 68/100 .04; 1/100 .055.

400mW Zeners, 5%: All E24 values from 2V4 to 36V and 75V at .035; 1k (mixed 100s) 029.
1.3W 5% Zeners: 3V6 3V9 4V3 7V5 11V 12V 13V 16V 18V 30V 56V 75V 110V 180V at .06; 1k (mixed 100s) 045.

TRANSISTORS

AC 127	.16	BD132	.26
AC128	.16	BD246	.30
AD161/2	.45	BD433	.28
BC107	.08	BD695A	.45
BC108C	.08	BD696A	.45
BC109C	.09	BF173	.16
BC182B	.05	BF181	.18
BC182L	.05	BF195	.06
BC183	.05	BF258	.20
BC183L	.05	BFV50	.17
BC184	.05	BFV51	.15
BC212B	.05	BFV52	.15
BC213	.05	BRV46	.17
BC214B	.05	BU206	.70
BC214L	.05	BU208	.92
BC308B	.05	OC35	.70
BC327	.05	PBC108	.05
BC328	.06	TIP31A	.21
BC338	.06	TIP32A	.21
BC547	.05	TIP41C	.32
BC548	.05	2N1132	.16
BC549	.05	2N2222	.10
BC557	.05	2N2369	.12
BC558	.05	2N2646	.40
BC559	.05	2N2926R	.05
BCY70	.12	2N3053	.16
BCY71	.12	2N3055	.30
BCY72	.12	2N3072-10	.05
BD131	.26		

WW - 022 FOR FURTHER DETAILS

AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

RETAIL-MAIL ORDER-EXPORT INDUSTRIAL-EDUCATIONAL

TEST EQUIPMENT CENTRES

CALL IN AND SEE FOR YOURSELF OPEN SIX DAYS A WEEK ALL MODELS ON DISPLAY



DIGITAL MULTIMETERS

- All models complete with leads and batteries
- Hand Held Models** 3 1/2 digit LCD (UK C/P 65p)
- KD25C 13 range 0.2A DC with carry case **£26.50**
 - KD30C 26 range 1A AC/DC 200 Meg Ohm with carry case **£37.50**
 - KD55C 28 range 10A AC/DC version of above **£41.50**
 - 2033A 26 range push button 2 amp AC/DC **£36.50**
 - 188m/6011A 15 range + Hfe tester plus 1 button 10A DC **£43.50**
 - 189m 30 range plus Hfe tester. Rotary switch 10A AC/DC **£69.95**
 - 2037A 28 range 0.1% 2A AC/DC + 2 temp ranges push button **£77.00**
 - 129 25 range 0.8% basic 10A AC/DC rotary switches (Keithley) **£79.35**
 - 130 As model 129 but 0.5% basic **£102.35**
- Bench Models** 3 1/2 digit LCD unless stated (UK C/P 90p)
- 2010A LED 31 range. 10A AC/DC basic 0.1% (Sabtronics) **£81.50**
 - TM353 LCD 27 range 2A AC/DC basic 0.15% (Sinclair) **£86.25**
 - 2015A LCD 31 range 10A AC/DC basic 0.1% (Sabtronics) **£89.50**
 - TM351 LCD 29 range 10A AC/DC basic 0.1% (Sinclair) **£113.85**
 - 2001 LCD 28 range plus 5 range capacitance meter 10A AC/DC Basic 0.1% (Pantec) **£108.00**
 - TM451 4 1/2 digit 0.03% basic all facilities (Sinclair) **£171.00**
 - 1503A 4 1/2 digit LCD 30 ranges 10A AC/DC 4 MHz counter. 4 KHZ osc. 0.05% basic (Thurlby) **£171.00**
 - 1503HA As above but 25A and 0.03% basic **£189.75**
- ACCESSORIES**
- AC Adaptors (2010A & 2015A only) **£5.69**
 - Cases TM351/353 **£6.84**
 - 2001 **£7.50**
 - 1503 **£20.45**
 - Touch and hold probe THP20 **£14.95**




OSCILLOSCOPES

- (UK C/P Single trace £3 ea. Safgan £3 ea. Dual trace £4 ea. SC110 £10.00)
- TRIO CS1566A** 20 + 20 MHz dual trace triggered sweep. 5mV/0.5 us/CH2 InV/x 10 mag. 19 sweep ranges. Limited offer **WAS £363.40 NOW £320.00 (UK C/P £4.00)**
- HM307** Single trace 10 MHz 5mV/0.5 micro sec. Plus built in component tester 6 x 7cm display (HAMEG) **£158.70** Optional case **£18.40**
- 3030** Single trace 15 MHz, 5mV/0.5 micro sec. Plus built in component tester. 95mm tube. Trig. to 20 MHz (CROTECH) **£172.50**
- 3035** Single trace 15 MHz, 5mV. Trig to 20 MHz plus built in component tester 0.2 µSec. 130mm Tube (CROTECH) **£189.75**
- HM203** Dual 20 MHz. Trig to 30 MHz 5mV/0.5 micro sec. 8 x 10cm display (HAMEG) **£253.00**
- CS1562A** Dual 10 MHz 10mV 1 µSec. 140mm tube (TRIO) **£267.95**
- 3131** Dual trace 15 MHz trig. to 35 MHz 5mV. 0.5 micro sec. 130mm tube. plus component tester **£276.00**
- CS1575** Dual 5 MHz 1mV 0.5 µSec. 140mm tube. Phase display audio scope. (TRIO) **£312.80**
- CS1560AII** Dual 15 MHz 10mV. 0.5 µSec. (TRIO) **£341.55**
- 3034** Battery-mains dual trace 15 MHz. Trig to 20 MHz built in. Nicade. 5mV. 0.5 micro sec. (CROTECH) **£414.00** (Eliminator charger optional) **£36.80**
- HM412-5** Dual 20 MHz delayed sweep. Trig to 40 MHz. 5mV 0.1 micro sec 8 x 10cm display (HAMEG) **£402.50** (Optional case £21.85)
- SC110A** New Model 10 MHz battery portable. 10mV 0.1 µSec. 2 trace. All facilities (THANDAR) **£171.00** (Options: Carry case **£6.84**, AC Adaptor **£5.69**, Nicade **£12.65**)
- CS1820** Dual 20 MHz 2.5mV 0.1 µSec. Delay sweep. 140mm tube (TRIO) **£483.00**
- CS1577A** Dual 35 MHz 2mV. 0.1 µSec. Single sweep facility. 140mm tube (TRIO) **£523.25**
- CS1830N** Dual 30 MHz 2mV 0.2 µSec (Hitted delay line) Delay sweep 140mm tube (TRIO) **£626.75**
- HM705** Dual 70 MHz delayed sweep. Single sweep. Delay line Trig to 70 MHz. 2mV. 0.1 micro sec. 8 x 10cm display (HAMEG) **£667.00**
- Range of low cost Dual Trace Scopes mains operated. Made in UK to exacting standards. Available as 10 MHz, 15 MHz or 20 MHz All feature 5mV sensitivity, 0.5 micro sec. 6.4 x 8cm display (SAFGAN)
- OPTIONS** HM203/412/705 View Hoods **£6.90** Component Tester **£28.75** OT410 Dual 10 MHz **£205.85** OT415 Dual 15 MHz **£217.35** OT420 Dual 20 MHz **£228.85**
- Scope probes all models - see below

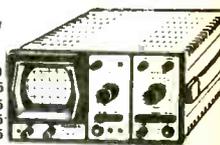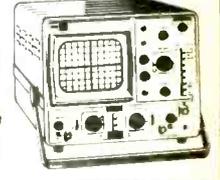

GENERATORS

- R-C Pulse: RF Function: audio (UK C/P £1)
- All models 220/240 V AC
- AUDIO** 4 band Sine/SQ output
- TE220 Max distortion 1% 20Hz/200KHz **£69.95**
 - LAG27 Max distortion 0.5-1% (LEADER) 10Hz-1MHz **£86.25**
 - AG20A Max distortion 0.5% (TRIO) 20Hz-200KHz **£78.20**
 - LAG120A 5 band 10 Hz - 1MHz. Sine/SQ 0.05-0.8% dist. **£46.00**
- LAG125** As LAG120A but 0.02% dist. (LEADER) **£273.00**
- AG203** 10 Hz - 1 MHz 5 band 0.1% Sine/SQ (TRIO) **£126.50**
- RF** (All with Int/Ext mod. variable output)
- TE20D 100 KHz - 100 MHz 6 band (300 MHz harm) **£59.95**
 - LSG17 100KHz-150MHz (450MHz harm) LEADER **£71.30**
 - SG402 100 KHz - 30 MHz 6 band (TRIO) **£68.00**
- FUNCTION** (All sine/SQ/Triangle/TTL etc.)
- 5020A 1 Hz - 200 KHz (SABTRONICS) **£90.00**
 - TG100 1 Hz - 100 KHz (THANDAR) **£90.85**
 - TG102 0.2 Hz - 2 MHz (THANDAR) **£166.75**
- PULSE**
- TG105 5 Hz - 5 MHz Various outputs (THANDAR) **£97.75**
 - 4001 Ultra-variable 0.5Hz-5MHz (GSC) **£113.85**

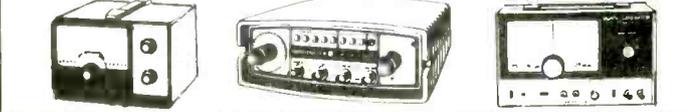

FREQUENCY COUNTERS

- (All models battery operated)
- (UK C/P £1)
- PFM200A Pocket 8 digit LED 200 MHz 10 mV (THANDAR) **£67.50**
 - Max 50 50 MHz 6 digit LED Pocket (GSC) **£56.35**
 - Max 550 6 digit LED Pocket (GSC) **£97.75**
 - 8110A 8 digit LED 2 range 100 MHz Bench (SABTRONICS) **£77.00**
 - 8610A 8 digit LED 3 range 600 MHz Bench (SABTRONICS) **£94.00**
 - Max 100 5Hz-100MHz 8 digit bench LED (GSC) **£97.75**
 - 8610B 9 digit LED 3 range 600 MHz Bench (SABTRONICS) **£113.85**
- 8000B 9 digit LED 3 range 1000 MHz Bench (SABTRONICS) **£178.00**
 - TF040 8 digit LED 40 MHz (600 MHz with TP600) (THANDAR) **£126.50**
 - TF200 8 digit LED 2 range 200 MHz (600 MHz with TP600) (THANDAR) **£166.75**
 - TP600 600 MHz prescaler (THANDAR) **£43.13**
 - TP1000 1GHz prescaler **£74.75**
- OPTIONS**
- TF series carry case **£6.84**
 - AC adaptors **£5.69**
 - 8 series AC Adaptors **£5.69**
 - All models probe kits **£7.95**



INSULATION AND CLAMP METERS

- Multi-range clamps all with resistance range, carry case and leads. Also digital and DC clamp in stock (UK C/P 75p)
- ST300 300A 6000V AC. 9 ranges **£28.95**
 - K2606 300A 6000V AC. 8 ranges. (Optional temp probe ET3 80) **£49.50**
 - K2903 900A 750V AC. 9 ranges **£77.50**

ELECTRONIC INSULATION TESTERS

- Battery operated complete with carry case
- YF501L 500V/100 Meg Plus 0.100 ohm (UK C/P £11) **£65.00**
 - K3103 600V/100 Meg Plus 0.2 6K ohm **£109.00**
 - K3106 500V & 1000V 1000 & 2000 Meg **£119.00**
 - K4101 Earth resistance tester **£149.00**
 - M500 Hand cranked insulation tester 500V/100 Meg **£79.50**
 - K8031 110V/600V phase tester **£23.50**

AMATEUR RADIO AND CB TESTING

- (Full lists send S.A.E.)
- KDM6 1.5 to 250 MHz 6 range DIP meter (illus) **£47.95**
 - PC1000 3 meters 0/10/100/1000 watts. SWR etc. 150 MHz max. (illus) **£45.00**
 - CB20 SWR/Power twin meter to 30 MHz. 1KW (illus) **£8.95**
 - HM20 20K/Volt multirange multimeter Plus SWR/Power meter 150 MHz Detachable Coupler **£22.95**
 - LPM880 RF Power meter 5/20/120W 1.8 - 500 MHz **£84.00**
 - LPM885 SWR/Power 20/200/1000W 1.8 - 54 MHz (illus) **£54.00**

HAVE A BANANA!

- Low cost reliable meters (All supplied with batts/leads) (UK C/P 55p)
- BANANA 15 range pocket 20K/Volt plus cont. buzzer (illus) **£20.84**
 - NH55 10 range pocket 2K/Volt **£5.50**
 - STS 11 range pocket 4K/Volt **£6.50**
 - NH56R 22 range pocket 20K/Volt **£9.95**
 - YH360TR 19 range plus Hfe test 20K/Volt **£12.95**
 - KRT5001 16 range 10 amp DC range double 50K/Volt **£16.50**

VARIABLE POWER SUPPLIES

- Mains input - Volts/Amps meter (UK C/P £1)
- PP241 0/12/12/24 Volt. 0/1 amp **£35.00**
 - PP243 0/12/12/24 Volt. 0/3 amp **£59.95**
 - PS13075 twin meter 8-15V 2-7A **£35.95**
- ST303TR** 21 range plus Hfe test 20K/Volt **£16.95**
- AT1020** 18 range Deluxe 2KV & Hfe Tester **£17.50**
- TMK500** 23 range plus 12A DC plus cont. buzzer 30K/Volt **£21.50**
- 168m** 36 range large scale 10A AC/DC 50K/Volt **£28.50**
- AT21D** 21 range 12A AC/DC 100K/Volt **£29.50**
- 360TR** 23 range large scale 10A AC/DC Hfe test 50 meg ohm. 1KV AC/DC 100K/Volt **£34.95**
- Choose from UK's largest range

TOP QUALITY ANALOGUE MULTIMETERS

- (UK C/P £1.20)
- All featuring AC/DC Volts/Current and Ohms ranges
- MAJOR 20K 29 range 20K/V. 2 1/2 AC. 12 1/2 A AC (PANTEC) **£33.90**
 - MAJOR 50K 29 range 50K/V. 2 1/2 AC. 12 1/2 A AC (PANTEC) **£40.25**
 - PAN3001 34 range 40K/V. 5A AC/DC. 50 Meg (PANTEC) **£59.80**
 - Also 500KHz - 500 MHz signal injector and 3 range cap. meter **£66.70**
 - PAN3003 32 range 1 Meg/V. 5A AC/DC. 1 µF. FSD (PANTEC) **£66.70**
- (NOTE 3001 & 3003 Electronic Protection Mirror Scales)
- K1400 26 range large scale 20K/Volt. 10A AC/DC. 20 Meg ohm. 5KV AC/DC **£95.00**
 - K2000 39 range 10 Meg. ohm input 25 Hz - 1 MHz **£105.00**
 - M1500 43 range 20K/V. 9 range AC. 10A 12 range DC. 10A **£67.50**

DIRECT READ HV PROBE

- (UK C/P 65p)
- 0/40 KV. 20K/Volt **£18.40**

OSCILLOSCOPE PROBE KITS

- (UK C/P 50p per 1 to 3)
- BNC plug X1 **£7.95**
 - X1 - X10 **£9.45**
 - X10 - X100 **£10.50**
 - X100 **£19.95**

DECADE BOXES

- RSB2 32 value Resis. box. 1 ohm to 4 Meg. **£18.50**
- CSB20 20 Value Cap. box. 470 pF to 1 µF **£21.00**

PORTABLE TV COLOUR GENERATOR

- MC101
- 8 patterns/dots/lines etc. Built in nicade. Pat B UHF only. Complete with charger, case and leads. **£162.50**

DIRECT READ TEMPERATURE

- TH301 -50°C to +750°C. LCD readout. Complete with battery and thermocouple **£68.43**

LOGIC PROBES/MONITOR

- Sabtronics LP10 10 MHz probe **£28.50**
- GSC LP2 1.5 MHz probe **£19.95**
- LEADER LP076 50 MHz (with case) **£56.90**
- GSC LM1 monitor (8 to 16 pin IC's) **£33.00**
- GSC OPI Digital pulser. Single/100 pps **£58.50**

AUDIO ELECTRONICS CUREGATE LIMITED

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TEL 01-724 3564

ALSO AT HENRY'S RADIO, 404/406 EDGWARE ROAD, LONDON W2

WE ARE OPEN 6 DAYS A WEEK - CALL IN AND SEE FOR YOURSELF!

Order by Post with CHEQUES/ACCESS/VISA or Telephone your order

Allow up to 10 days for delivery (unless advised)

Send large SAE (20p UK) Schools, Companies, etc. Please write in.

FREE CATALOGUE

ALL PRICES INCLUDE VAT

WW - 011 FOR FURTHER DETAILS

Sinclair ZX Spectr

**16K or 48K RAM...
full-size moving-
key keyboard...
colour and sound...
high-resolution
graphics...**

**From only
£125!**



First, there was the world-beating Sinclair ZX80. The first personal computer for under £100.

Then, the ZX81. With up to 16K RAM available, and the ZX Printer. Giving more power and more flexibility. Together, they've sold over 500,000 so far, to make Sinclair world leaders in personal computing. And the ZX81 remains the ideal low-cost introduction to computing.

Now there's the ZX Spectrum! With up to 48K of RAM. A full-size moving-key keyboard. Vivid colour and sound. High-resolution graphics. And a low price that's unrivalled.

Professional power— personal computer price!

The ZX Spectrum incorporates all the proven features of the ZX81. But its new 16K BASIC ROM dramatically increases your computing power.

You have access to a range of 8 colours for foreground, background and border, together with a sound generator and high-resolution graphics.

You have the facility to support separate data files.

You have a choice of storage capacities (governed by the amount of RAM). 16K of RAM (which you can update later to 48K of RAM) or a massive 48K of RAM.

Yet the price of the Spectrum 16K is an amazing £125! Even the popular 48K version costs only £175!

You may decide to begin with the 16K version. If so, you can still return it later for an upgrade. The cost? Around £60.

Ready to use today, easy to expand tomorrow

Your ZX Spectrum comes with a mains adaptor and all the necessary leads to connect to most cassette recorders and TVs (colour or black and white).

Employing Sinclair BASIC (now used in over 500,000 computers worldwide) the ZX Spectrum comes complete with two manuals which together represent a detailed course in BASIC programming. Whether you're a beginner or a competent programmer, you'll find them both of immense help. Depending on your computer experience, you'll quickly be moving into the colourful world of ZX Spectrum professional-level computing.

There's no need to stop there. The ZX Printer—available now—is fully compatible with the ZX Spectrum. And later this year there will be Microdrives for massive amounts of extra on-line storage, plus an RS232/network interface board.



Key features of the Sinclair ZX Spectrum

- Full colour—8 colours each for foreground, background and border, plus flashing and brightness-intensity control.
- Sound—BEEP command with variable pitch and duration.
- Massive RAM—16K or 48K.
- Full-size moving-key keyboard— all keys at normal typewriter pitch, with repeat facility on each key.
- High-resolution—256 dots horizontally x 192 vertically, each individually addressable for true high-resolution graphics.
- ASCII character set—with upper- and lower-case characters.
- Teletext-compatible—user software can generate 40 characters per line or other settings.
- High speed LOAD & SAVE—16K in 100 seconds via cassette, with VERIFY & MERGE for programs and separate data files.
- Sinclair 16K extended BASIC—incorporating unique 'one-touch' keyword entry, syntax check, and report codes.

um



The ZX Printer – available now

Designed exclusively for use with the Sinclair ZX range of computers, the printer offers ZX Spectrum owners the full ASCII character set – including lower-case characters and high-resolution graphics.

A special feature is COPY which prints out exactly what is on the whole TV screen without the need for further instructions. Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your ZX Spectrum. A roll of paper (65ft long and 4in wide) is supplied, along with full instructions. Further supplies of paper are available in packs of five rolls.



The ZX Microdrive – coming soon

The new Microdrives, designed especially for the ZX Spectrum, are set to change the face of personal computing.

Each Microdrive is capable of holding up to 100K bytes using a single interchangeable microfloppy.

The transfer rate is 16K bytes per second, with average access time of 3.5 seconds. And you'll be able to connect up to 8 ZX Microdrives to your ZX Spectrum.

All the BASIC commands required for the Microdrives are included on the Spectrum.

A remarkable breakthrough at a remarkable price. The Microdrives are available later this year, for around £50.



RS232 / network interface board

This interface, available later this year, will enable you to connect your ZX Spectrum to a whole host of printers, terminals and other computers.

The potential is enormous. And the astonishingly low price of only £20 is possible only because the operating systems are already designed into the ROM.

How to order your ZX Spectrum

BY PHONE – Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day. BY FREEPOST – use the no-stamp needed coupon below. You can pay by cheque, postal order, Access,

Barclaycard or Trustcard. EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

ZX Spectrum

Available only by mail order and only from

sinclair

Sinclair Research Ltd,
Stanhope Road, Camberley,
Surrey, GU15 3PS.
Tel: Camberley (0276) 685311

To: Sinclair Research, FREEPOST, Camberley, Surrey, GU15 3BR. **Order**

Qty	Item	Code	Item Price £	Total £
	Sinclair ZX Spectrum – 16K RAM version	100	125.00	
	Sinclair ZX Spectrum – 48K RAM version	101	175.00	
	Sinclair ZX Printer	27	59.95	
	Printer paper (pack of 5 rolls)	16	11.95	
	Postage and packing: orders under £100	28	2.95	
	orders over £100	29	4.95	
			Total £	

Please tick if you require a VAT receipt

*I enclose a cheque/postal order payable to Sinclair Research Ltd for £ _____

*Please charge to my Access/Barclaycard/Trustcard account no. _____

*Please delete/complete as applicable _____

Signature _____

PLEASE PRINT


Name: Mr/Mrs/Miss _____

Address _____

WRW 810

FREEPOST – no stamp needed. Prices apply to UK only. Export prices on application.

Testing... Testing... Testing...

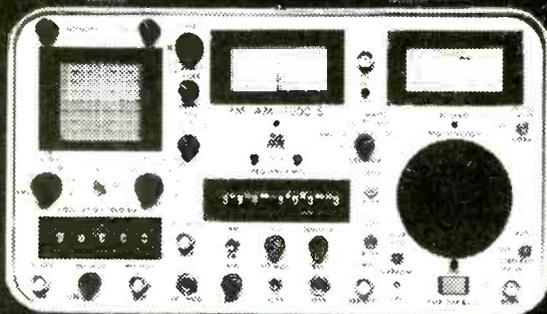

anywhere!

FM/AM 1000s with Spectrum Analyser — we call it the SUPER — S

A portable communications service monitor for IFR, light enough to carry anywhere and good enough for most two-way radio system tests.

The FM/AM 1000s can do the work of a spectrum analyser, oscilloscope, tone generator, deviation meter, modulation meter, signal generator, wattmeter, voltmeter, frequency error meter — and up to five service engineers who could be doing something else!

A PRACTICAL TOP UP! MM-100 MULTI-METER

Simply replaces the protective lid of the FM/AM 1000s. It includes a modified probe, PB-114, and a built in speaker unit with independent volume control for audible response to signal measurement. This practical 'top up' will perform the following functions.

Sinad: Measurements for 1 kHz tone (± 20 Hz)

Distortion: To 30%

DC Volts: Up to 300 volts and up to 800 volts when the X10 probe is used

AC Volts: 600 VRMS maximum for frequencies between 25 Hz and 25 kHz

Ohms: Using the modified probe, part number PB-114.

Ohms can be measured on scales X1 to X10 K
% AM Measured on the RF signal applied to the FM/AM-1000 unit

OPTIONAL ACCESSORIES

A choice of R.F. power attenuators and protective carrying cases.



For further information contact Mike Taylor



**Fieldtech
Heathrow**

Fieldtech
Heathrow Ltd.
Huntavia House
420 Bath Road
West Drayton
Middlesex UB7 0LL
Tel 01-897 6446
Telex 23734
FLDTEC G

IFR precision simulators

WW - 064 FOR FURTHER DETAILS

VALVES

		Minimum Order £1	VALVES VAT IS INCLUDED
A1065	1.40	EL821	8.20
A2293	8.00	EL822	9.95
A2900	13.75	EM80	0.85
AR8	0.75	EM87	1.30
ARP3	0.70	EY51	0.95
ATP4	3.90	EY81	0.85
B12H	1.40	EY86/87	4.20
CY31	0.70	EY88	0.65
DAF96	0.70	EZ80	0.70
DT22	28.85	EZ81	0.70
DF96	0.70	GM4	5.90
DH76	0.75	GY501	1.30
DL32	0.90	GZ32	1.05
DY86/87	0.85	GZ33	4.20
DY802	0.70	GZ34	2.75
E55L	14.90	GZ37	3.95
E88CC	1.80	KT66	6.30
E88CC/01	3.10	KT88	9.20
E92CC	2.90	KT88	9.95
E180CC	4.20	KT88	13.90
E180F	7.70	MH4	2.50
E182CC	6.25	ML6	2.50
EA76	2.25	MX10/01/21	5.00
EABC80	0.80	N78	9.90
EB91	0.80	OA2	0.70
EBCC33	1.15	OB2	0.80
EBCC30	0.90	PABC80	0.80
EBF80	0.80	PC85	0.75
EBF83	0.80	PC86	0.85
EBF89	0.80	PC88	0.90
EC52	0.85	PC97	1.25
EC81	4.40	OB2	0.80
EC82	0.85	PCC84	0.80
EC881	0.85	PCC89	0.85
EC882	0.80	PCC189	0.85
EC883	0.85	PCF80	0.80
EC884	0.80	PCF82	0.70
EC885	0.80	PCF84	0.75
EC886	1.70	PCF86	1.50
EC888	0.80	PCF87	0.50
EC889	0.35	PCF200	1.45
EC8804	0.90	PCF201	1.85
ECF80	0.85	PCF800	0.50
ECF82	0.85	PCF801	1.75
ECF801	1.05	PCF802	0.70
ECH34	2.25	PCF806	1.20
ECH35	1.70	PCF808	1.45
ECH42	2.10*	PCH200	1.35
ECH81	1.20	PCL81	0.75
ECH84	0.70	PCL82	0.95
ECL80	0.70	PCL86	0.75
ECL82	0.75	PCL805/85	0.95
ECL83	1.40	PD500/510/4.30	
ECL85	0.90	PFL200	1.10
ECL86	0.85	PFL200	2.90*
EF37A	2.15	PL36	1.10
EF39	1.25	PL81	0.85
EF80	0.85	PL82	0.70
EF83	1.75	PL83	0.80
EF85	0.80	PL84	0.95
EF86	0.75	PLS04	1.00
EF89	1.95	PLS08	1.95
EF91	1.50	PLS09	3.20
EF92	2.90	PLS19	5.65*
EF95	0.85	PL519	3.95
EF96	0.80	PL502	6.10*
EF183	0.80	PL802	3.20
EF184	0.80	PY32	0.70
EF812	0.75	PY80	0.70
EF1200	1.85	PY81/800	0.85
EH90	0.85	PY82	0.85
EL32	1.10	PY83	0.80
EL34	1.80	PY88	0.80
EL81	2.45	PY809	6.45
EL82	0.70	PY801	0.80
EL84	0.80	QV03/10	7.50
EL86	0.85	QV03-20A	6A65
EL90	1.90	QV03-25A	6A65
EL91	4.20	QV03-25A	6AK5
EL95	0.80	QV03-25A	36.50
EL504	1.70	QV06/40A	6AL5
EL803	6.90	QV13-12	16.10
EL509	3.95	QV13-400	4.20
EL802	1.70	SC1/600	4.50
SC1/600	4.50	SC1/600	4.50
6AN8A	2.50	6AN8A	2.50
6AQ5	1.00	6AQ5	1.00
6AQ5W	1.80	6AQ5W	1.80
6AS6	1.15	6AS6	1.15
6AT6	1.15	6AT6	1.15
6AU6	1.15	6AU6	1.15
6AV6	0.85	6AV6	0.85
6AX4GT	1.30	6AX4GT	1.30
6AX5GT	1.30	6AX5GT	1.30
6BA6	0.55	6BA6	0.55
6BE6	0.60	6BE6	0.60
6BG6G	1.80	6BG6G	1.80
6B16	1.30	6B16	1.30
6BQ7A	0.85	6BQ7A	0.85
6BR7	4.80	6BR7	4.80
6BW6	6.20	6BW6	6.20
6BW7	1.75	6BW7	1.75
6CA	0.80	6CA	0.80
6CB	0.70	6CB	0.70
6CH6	1.30	6CH6	1.30
6CL6	2.75	6CL6	2.75
6CX8	3.80	6CX8	3.80
6CY5	1.15	6CY5	1.15
6D6	0.70	6D6	0.70
6E6	1.60	6E6	1.60
6F6GB	1.10	6F6GB	1.10
6F7	2.80	6F7	2.80
6F8G	0.85	6F8G	0.85
6F12	1.50	6F12	1.50
6F14	1.15	6F14	1.15
6F15	0.90	6F15	0.90
6F17	3.20	6F17	3.20
6F23	0.75	6F23	0.75
6F24	1.75	6F24	1.75
6F33	10.50	6F33	10.50
6F8H	4.20	6F8H	4.20
6G5AB	0.85	6G5AB	0.85
6G8BA	0.35	6G8BA	0.35
6H6	1.80	6H6	1.80
6J4	1.35	6J4	1.35
6J4WA	2.00	6J4WA	2.00
6K5	2.30	6K5	2.30
6J5GT	0.90	6J5GT	0.90
6K11	1.10	6K11	1.10
6K12	1.15	6K12	1.15
6K13	1.25	6K13	1.25
6K14	2.45	6K14	2.45
6K7	0.80	6K7	0.80
6KD6	3.35	6KD6	3.35
6L6M	2.80	6L6M	2.80
6L6G	2.50	6L6G	2.50
6L6GC	1.10	6L6GC	1.10
6L7	1.25	6L7	1.25
6L7G	0.85	6L7G	0.85
6L8	0.70	6L8	0.70
6L9	2.95	6L9	2.95
6M2	0.70	6M2	0.70
6M2A	1.70	6M2A	1.70
6M7	1.00	6M7	1.00
6M8	1.15	6M8	1.15
6M9	1.90	6M9	1.90
6M10	1.05	6M10	1.05
6M11	1.10	6M11	1.10
6M12	1.15	6M12	1.15
6M13	1.20	6M13	1.20
6M14	1.25	6M14	1.25
6M15	1.30	6M15	1.30
6M16	1.35	6M16	1.35
6M17	1.40	6M17	1.40
6M18	1.45	6M18	1.45
6M19	1.50	6M19	1.50
6M20	1.55	6M20	1.55
6M21	1.60	6M21	1.60
6M22	1.65	6M22	1.65
6M23	1.70	6M23	1.70
6M24	1.75	6M24	1.75
6M25	1.80	6M25	1.80
6M26	1.85	6M26	1.85
6M27	1.90	6M27	1.90
6M28	1.95	6M28	1.95
6M29	2.00	6M29	2.00
6M30	2.05	6M30	2.05
6M31	2.10	6M31	2.10
6M32	2.15	6M32	2.15
6M33	2.20	6M33	2.20
6M34	2.25	6M34	2.25
6M35	2.30	6M35	2.30
6M36	2.35	6M36	2.35
6M37	2.40	6M37	2.40
6M38	2.45	6M38	2.45
6M39	2.50	6M39	2.50
6M40	2.55	6M40	2.55
6M41	2.60	6M41	2.60
6M42	2.65	6M42	2.65
6M43	2.70	6M43	2.70
6M44	2.75	6M44	2.75
6M45	2.80	6M45	2.80
6M46	2.85	6M46	2.85
6M47	2.90	6M47	2.90
6M48	2.95	6M48	2.95
6M49	3.00	6M49	3.00
6M50	3.05	6M50	3.05
6M51	3.10	6M51	3.10
6M52	3.15	6M52	3.15
6M53	3.20	6M53	3.20
6M54	3.25	6M54	3.25
6M55	3.30	6M55	3.30
6M56	3.35	6M56	3.35
6M57	3.40	6M57	3.40
6M58	3.45	6M58	3.45
6M59	3.50	6M59	3.50
6M60	3.55	6M60	3.55
6M61	3.60	6M61	3.60
6M62	3.65	6M62	3.65
6M63	3.70	6M63	3.70
6M64	3.75	6M64	3.75
6M65	3.80	6M65	3.80
6M66	3.85	6M66	3.85
6M67	3.90	6M67	3.90
6M68	3.95	6M68	3.95
6M69	4.00	6M69	4.00
6M70	4.05	6M70	4.05
6M71	4.10	6M71	4.10
6M72	4.15	6M72	4.15
6M73	4.20	6M73	4.20
6M74	4.25	6M74	4.25
6M75	4.30	6M75	4.30
6M76	4.35	6M76	4.35
6M77	4.40	6M77	4.40
6M78	4.45	6M78	4.45
6M79	4.50	6M79	4.50
6M80	4.55	6M80	4.55
6M81	4.60	6M81	4.60
6M82	4.65	6M82	4.65
6M83	4.70	6M83	4.70
6M84	4.75	6M84	4.75
6M85	4.80	6M85	4.80
6M86	4.85	6M86	4.85
6M87	4.90	6M87	4.90
6M88	4.95	6M88	4.95
6M89	5.00	6M89	5.00
6M90	5.05	6M90	5.05
6M91	5.10	6M91	5.10
6M92	5.15	6M92	5.15
6M93	5.20	6M93	5.20
6M94	5.25	6M94	5.25
6M95	5.30	6M95	5.30
6M96	5.35	6M96	5.35
6M97	5.40	6M97	5.40
6M98	5.45	6M98	5.45
6M99	5.50	6M99	5.50
6M100	5.55	6M100	5.55
6M101	5.60	6M101	5.60
6M102	5.65	6M102	5.65
6M103	5.70	6M103	5.70
6M104	5.75	6M104	5.75
6M105	5.80	6M105	5.80
6M106	5.85	6M106	5.85
6M107	5.90	6M107	5.90
6M108	5.95	6M108	5.95
6M109	6.00	6M109	6.00
6M110	6.05	6M110	6.05
6M111	6.10	6M111	6.10
6M112	6.15	6M112	6.15
6M113	6.20	6M113	6.20
6M114	6.25	6M114	6.25
6M115	6.30	6M115	6.30
6M116	6.35	6M116	6.35
6M117	6.40	6M117	6.40
6M118	6.45	6M118	6.45
6M119	6.50	6M119	6.50
6M120	6.55	6M120	6.55
6M121	6.60	6M121	6.60
6M122	6.65	6M122	6.65
6M123	6.70	6M123	6.70
6M124	6.75	6M124	6.75
6M125	6.80	6M125	6.80
6M126	6.85	6M126	6.85
6M127	6.90	6M127	6.90
6M128	6.95	6M128	6.95
6M129	7.00	6M129	7.00
6M130			

THE HEADSET THAT'S WAY AHEAD OF ITS TIME.



THE DANAVOX HMT 808.

The Danavox HMT 808 is the most advanced headset of its kind that you can buy today. Employing Danavox expertise and quality throughout, it offers many unique features at a remarkably low price.

- Lightweight. Weighs only 35 grams
- Comfortable and hygienic. Does not go in the ear so it can be comfortably positioned in seconds
- Versatile. Can be worn under the chin or over the head using single ear or binaurally
- Multiple version microphone. Available with either magnetic microphone or electret with noise cancelling feature and pre-amplifier for matching into telephone systems

- Technically advanced. Pre-amp employs latest thick film technology
- Easy servicing and repairs. Quick changing of earphones, cords, earpieces and switches
- Realistically priced
- Danavox quality engineering and guarantee.

For full details contact
John Carter at Danavox.




danavox

DANAVOX (Gt. Britain) Ltd.,
1 Cheyne Walk, Northampton NN1 5PT
Tel: (0604) 36351 Telex 312395

WW - 012 FOR FURTHER DETAILS

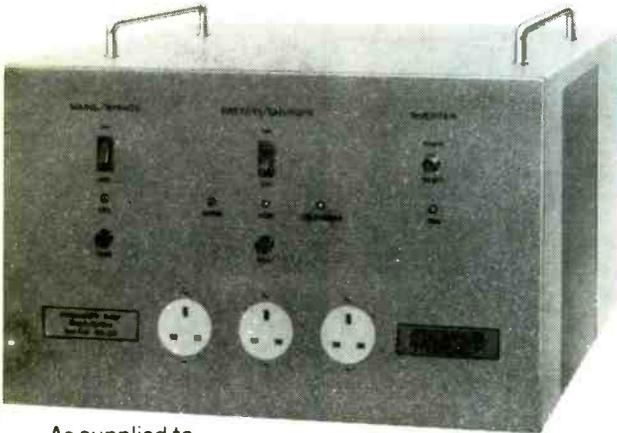The simple answer to all your power supply problems.



As supplied to International Telecommunications Companies
Uninterruptible Power Supplies - UPS CVT Reliability
 125va to 50kva, 50 or 60hz.

- **STANDBY POWER.** Invaluable for winding down a computer programme on mains failure and wherever continuous power is essential.
- **STABILISATION.** $\pm 5\%$ Vital to combat mains voltage fluctuations and ensure the operation of equipment at peak efficiency. Frequency stabilised $\pm 0.1\%$ 47 to 65Hz.
- **TRANSIENT ATTENUATION.** Provides suppression of mains born interference (spikes).

An unbeatable power package at a price to suit all budgets from Galatrek International, UPS are DOWN to unbeatable prices.

For more information, cut the coupon.
 Galatrek International, FREEPOST, Scotland Street, Llanrwst, nr. Llandudno, Gwynedd LL26 0AL, BRITAIN,
 Tel No: 0492-640311/641298, Telex: 617114 A/B Galahu.
 Made and Designed in Britain by Galatrek.



- Please send me full details of your range of voltage stabilisers, filters, cut outs, generators and CVT's
- Please send me full details of UPS
- Please send me a requirement check sheet
- Consultation with Galatrek Engineer

Name _____
 Position _____
 Company _____
 Address _____

Tel No _____ Telex _____
 Trade OEM (please tick where appropriate) WW 2/10

WW - 010 FOR FURTHER DETAILS

D.I.L. MINIATURE ON-OFF SWITCHES Gold-plated contacts. Sealed base ideal for programming. 6-position at less than half manufacturer's price. ONLY 75p Will fit into 14-pin di socket Ten at 65p ea. per 100 55p ea.	HONEYWELL PROXIMITY DETECTOR integral amplifier. Bv D.C. £3.50 ea PHOTO CONDUCTIVE CELL. £1.25. High-power CdS cell. 800mW. for control circuits. Resistance 800 ohm to 4K Max. volts 240. Size 1/2 x 1/2in RIBBON MICROPHONE with pre-amp on chassis. £1.75.	MULLARD MODULES LP1171 AM FM 1/4 Strip Front end Pair £5.75 Complete with Data LP1186 LP1157 varicap Med. & Long Tuner £2.50 £5.00	ULTRA SONIC TRANSDUCERS 40KCS. Complete on 18in. Screened cable, each pair £2.95 ULTRA SONIC TRANSMITTER. Complete unit (uncased requires 15V). £3.25 FOSTER DYNAMIC MICROPHONES. 200 ohm impedance. Moving coil. Complete on chassis. £1.75 pair.
U.H.F. MODULATORS Latest type, adjustable, ideal for computers, with data circuit. Size 3x2 1/2 x 1 inch. Only £2.50 In screened case	LM380 Amplifier..... 85p LM318N Hi-Slew Op Amp..... £1.50 LM323K, 5v. 3-amp. reg..... £3.50 LM310N Volt. Follower Amp..... £1.20 LM311H High Perf. Volt. Comparator..... £1.00 LM384N, 5-watt Amp £1.20 LM393N Dual Com..... £1.00 7905 Reg. -5v..... 75p	MINIATURE HIGH-QUALITY FANS "Whisper Model" by Roton. Low-power consumption (less than 10 watts). Silent running. 115v. (two in series for 230v) 50-60Hz. Size 4 1/2 x 4 1/2 x 1 1/2in. ONLY 65.50 EACH incl. V.A.T. BRAND NEW 50% less than manufacturer's price.	STEREO CASSETTE Mechanisms 6 or 12 volt. Complete with Heads + Erase and Solenoid. Brand new..... £3.90 ea.
MINIATURE EDGE INDICATOR METER With illuminated dial scale 0-10 F.S.D. 100 microamp. Size 1 1/2 x 1 1/2 x 1/2 deep. Only £1.65.	MONSANTO Half-inch + 1 Display High Intensity £1 each set of 4 £3.50 Common anode 14 Pin Dii Package	STEREO CASSETTE TAPE HEADS. Quality replacement for most recorders with mounting plate. Record/Replay £2.80 MARRIOTT TAPE HEADS Quarter track. Type XRPS18 Record/Replay (each) £2.00 XRPS36 Record/Replay (each) £3.00 XES11 Erase (each) £1.00	TV CENDERGENCE POTS (LVI) 50 ohm ALL 100. 200. 5K 5p ea.
BRIDGE RECTIFIER 800 PIV 35 amps. 1 1/2 x 1 1/2 x 1/2in. £3.50	NATIONAL P.8080A Chips £2.95 8216..... £1.75 1N4148 DIODES Full spec. but no polarity band. Per 1000..... £10 MINIATURE M.P.C. POTENTIOMETERS. Model M2. High-quality, 5% tolerance, 2-watt, with lin spirals. All values, 47 ohms-47k, only 60p each per 10. 50p each per 100. 40p each.	RECHARGEABLE BATTERIES VARTA 3.6 volts DEAC. 1MAH 225..... £1.50 DRYFIT 6-volt, 4.5 amp..... £7.50 XTAL FILTER 10.7 mc/s. 12.5DB separation. 1 1/2 x 1 1/4 x 1 inch £7.00 100KC/S + 1 meg 3-pin	HEWLETT-PACKARD DISPLAYS 5082-7650 HIGH EFFICIENCY AND VERY BRIGHT. Only £1.00 each Set of 6 for £5 Half-inch red common anode will replace 0L70/14-pin Di.
"CHERRY" ADD-ON KEYPAD A compact 12-button keypad suitable for use with keyboard extend its functions plus four extra keys. Supplied brand new LIST PRICE £22.00 OUR PRICE ONLY £7.50 incl. V.A.T.	QUANTITY DISCOUNTS on ALL items (unless stated), 15% per 10, 20% per 50, 25% per 100. All items BRAND NEW (unless otherwise stated). DELIVERY from stock - Add post 35p per order.		

Henry's EXPORT enquiries invited TELEX 262284 Transonics Mono 1400

01-723 1008/9

Callers to: 404 EDGWARE ROAD, LONDON W2 1ED
 ALL MAIL ORDERS/EXPORT ENQUIRIES 11/12 PADDINGTON GREEN, LONDON, W2

ORDER YOUR FAVOURITE AUDIO ACCESSORIES BY MAIL

SEND FOR YOUR FREE COPY OF OUR 1982 CATALOG

OVER 250 ITEMS
 INCLUDING DIRECT BOXES, MIC-SPLITTERS, SIGNAL PROCESSING, AUDIO MODULES, TRANSFORMERS & MANY OTHER ACCESSORIES
WITH TECHNICAL DATA & USE DIAGRAMS

We Ship the fastest & most convenient way for you! Most Shipments From Stock

SESCOM SESCO, INC. RETAIL SALES DIVISION
 1111 Las Vegas Blvd. North (702)384-0893
 Las Vegas, NV 89101-1197 U.S.A. (800)634-3457 TWX (910)387-6996

WW - 037 FOR FURTHER DETAILS

INSTANT PRINTED CIRCUITS!!

Make your own - to professional standards - within minutes using either "Fotolak" Light-sensitive Aerosol Lacquer or Pre-coated board. No Darkroom or Ultra-violet source needed!

Fotolak aerosol..... £2.50 (30p)	Developer..... £0.30 (15p)
Ferric Chloride..... £0.60 (45p)	Acetate Sheet..... £0.15 (15p)

Copper-clad Fibre-glass Boards: Single-sided..... £2 ft. sq. (45p)
 Double-sided..... £2.25 ft. sq. (60p)

Pre-coated Fibre-glass Board:
 8"x4 1/2"..... £1.75 (25p) 16"x9"..... £7 (60p) 24"x18"..... £18 (£1.70)
 8"x9"..... £3.50 (45p) 24"x12"..... £13 (£1.20) Eurocard £1.25 (25p)

Double-sided Board (all sizes) add 20%
 Postage individual items in brackets. Maximum charge £2 per order.

WHITE HOUSE ELECTRONICS
 P.O. Box 19, Praa Sands, Penzance TR20 9TF
 Telephone: Germoe (073-676) 2329



Constructor Series Speakers

IT'S
SO
EASY

Have fun, save money, building a Kef design with a Wilmslow Audio CS Total kit.

No electronic or woodworking knowledge necessary and the end result is a proven top-quality design that you'll be proud of.

Each kit contains all cabinet components, accurately machined for easy assembly, speaker drive units, crossovers, wadding, grille fabric, terminals, nuts, bolts, etc.

The cabinets can be painted or stained or finished with iron-on veneer or self adhesive woodgrain vinyl.

Easy foolproof assembly instructions supplied. Set of constructor leaflets sent free on receipt of large S.A.E.



Prices: CS1 (As 101)	£110 pr. inc. VAT, plus carr./ins. £ 5.50
CS1A (s amplified LS3/5A)	£103 pr. inc. VAT, plus carr./ins. £ 5.50
CS3 (as 103.2)	£129 pr. inc. VAT, plus carr./ins. £10.00
CS5 (as Carlton II)	£192 pr. inc. VAT, plus carr./ins. £15.00
CS7 (as Cantata)	£250 pr. inc. VAT, plus carr./ins. £18.00



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS

1982 Catalogue — £1.50 post free



Lightning service on telephoned credit card orders!



RADIOCODE CLOCKS

are powerful and comprehensive instruments which receive, decode and analyse time-coded standard frequency transmissions to provide accurate, secure and completely automatic time/calendar or synchronisation systems.




Applications

- Automatic master clock and slave controller.
- Synchronisation of separate equipment and events.
- Programmable energy management system.
- Computer clock/calendar with battery backup.
- Data logging and time recording.
- Process and equipment control.
- Broadcasting, Astronomy, Navigation.
- Satellite tracking.

If you have a time or synchronisation problem, write or phone for further details of our portable and new microcomputer-controlled Radiocode Clocks.

Circuit Services, 6 Elmbridge Drive
Ruislip, Middlesex. Ruislip 76962

WW - 015 FOR FURTHER DETAILS

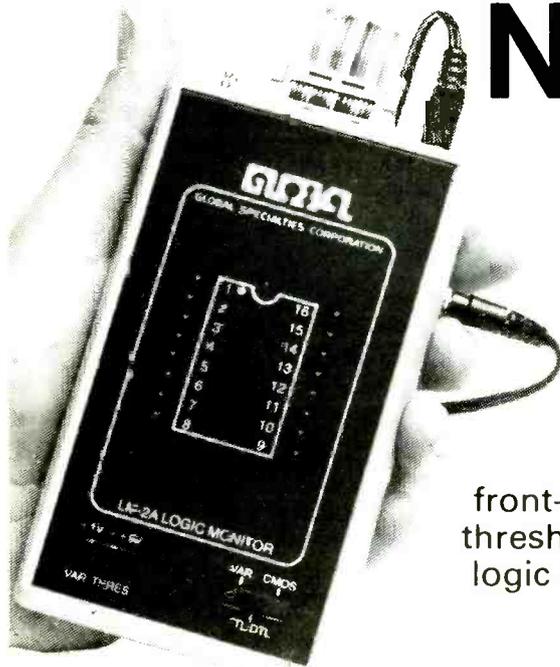

Now, really reason with IC's

With the new LM2A logic monitor from GSC, you can see just what's going on in an integrated circuit for only £75.*

The LM2A's sixteen LED indicators show the static and dynamic logic states of all the pins on 14 or 16-pin IC packages, and GSC's unique Proto-Clip provides rapid, reliable contact with the circuit.

You can use the LM2A with different logic families, too. A front-panel switch lets you select TTL or C-MOS, and a variable threshold control covers any voltage from +1V to +9V for other logic levels. It's small and light enough to hold in the hand, and operation is simplicity itself.

Take the logical course of action - fill in the coupon now.

* Price excluding P&P and 15% VAT.

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited, Dept. 7L
Unit 1, Shire Hill Industrial Estate
Saffron Walden, Essex CB11 3AQ
Telephone: Saffron Walden (0799) 21682
Telex: 817477

G.S.C. (UK) Ltd., Dept. 7L, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

Model LM2A	LOGIC MONITOR	Unit price inc. P & P 15% VAT £88.55	Qty. Reqd.
------------	---------------	--------------------------------------	------------

Name _____
Address _____

I enclose cheque/P.O. for £ _____ or debit by Barclaycard/Access/
American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION - The G.S.C. 24 hour, 5 day a week service.
Telephone (0799) 21682 and give us your Barclaycard, Access, American
Express number and your order will be in the post immediately

For FREE catalogue tick box

EP4000 EPROM EMULATOR PROGRAMMER



The microprocessor controlled EP4000 will emulate and program all the popular EPROMs including the 2704, 2708, 2716(3), 2508, 2758, 2516, 2716, 2532 and 2732 devices. Personality cards and hardware changes are not required as the machine configures itself for the different devices. Other devices such as bipolar PROMs and 2764 and 2564 EPROMs are programmed with external modules.

The editing and emulation facilities, video output and serial/parallel input/output provided as standard make the EP4000 very flexible to allow its use in three main modes:

- As a stand alone unit for editing and duplicating EPROMs.

Items pictured are: ● EP4000 Emulator Programmer - £545 + £12 delivery; ● BSC buffered simulator cable - £39; ● MESA 4 multi EPROM simulator cable - £98; ● 2732A Programming adaptor - £39; ● 2764 Programming adaptor - £64; ● 2564 Programming adaptor - £64; ●

- As a slave programmer used in conjunction with a software development system or microcomputer.
- As a real time EPROM emulator for program debugging and development (standard access time of the emulator is 300ns).

Data can be loaded into the 4k x 8 static RAM from a pre-programmed EPROM, the keypad, the serial or parallel ports and an audio cassette. Keypad editing allows for data entry, shift, move, delete, store, match and scroll, and a 1k x 8 RAM allows temporary block storage. A video output for memory map display, as well as the built-in 8 digit hex display allows full use of the editing facilities to be made.

BP4 (TEXAS) Bipolar PROM Programming module - £190

Also available (not shown): ● VM10 Video monitor - £99; ● UV141 EPROM Eraser with timer - £78; ● GP100A 80 column Printer - £225; ● PI100 interface for EP4000 to GP100A - £65.

VAT should be added to all prices

DISTRIBUTORS REQUIRED

EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

P8000 — THE PRODUCTION PROGRAMMER THAT HANDLES ALL NMOS EPROMS



**NEW
PRODUCT**

- Checks, Programs, Compares up to 8 devices simultaneously
- Handles all NMOS EPROMS up to projected 128K designs with no personality modules or characterisers — See list
- Easy to use, menu driven operation for blankcheck, program, verify, illegal bit check, checksum, self-test
- Constant display of device type, mode and fault codings
- Individual socket LED indicators for EPROM status
- Comprehensive EPROM integrity checks — Illegal bit check, data and address shorts, constant power line monitoring
- Full safeguard protection on all sockets
- Automatic machine self-test routine
- Powered down sockets
- Cost effective price — £695 + VAT
- Available from stock

**2704
2708
2716(3)
2508
2758A
2758B
2516
2716
48016
2532
2732
2732A
68732-0
68732-1
68766
68764
2764
2564
MK2764**

Write or phone for more details

DISTRIBUTORS REQUIRED

EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.


Tel: Plymouth (0752) 332961
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

WW — 024 FOR FURTHER DETAILS

Marconi Type R1020 Hinged Antenna Column.

Easy to raise
Easy to lower

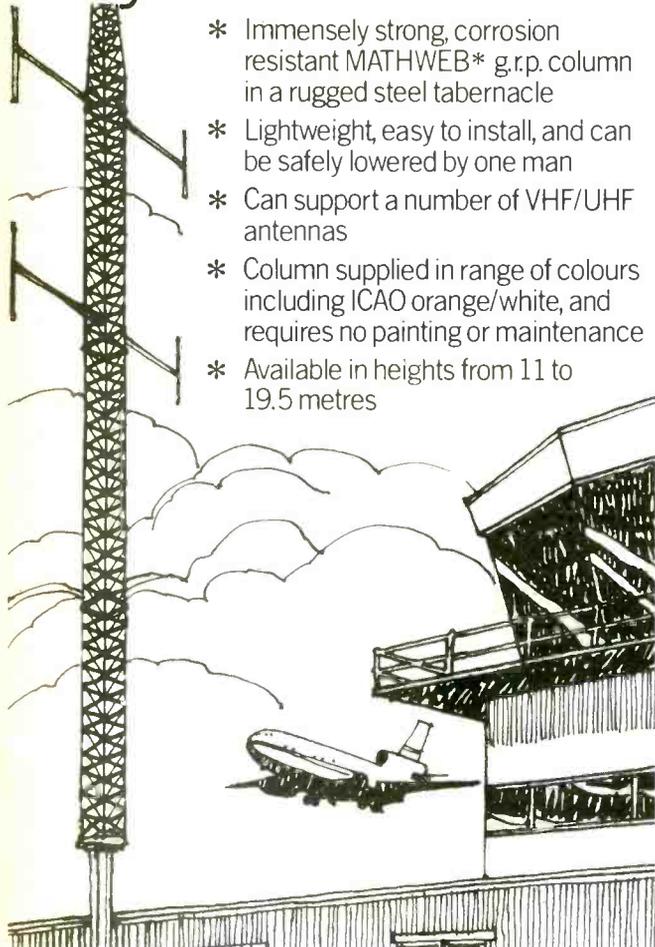

- * Immensely strong, corrosion resistant MATHWEB* g.r.p. column in a rugged steel tabernacle
- * Lightweight, easy to install, and can be safely lowered by one man
- * Can support a number of VHF/UHF antennas
- * Column supplied in range of colours including ICAO orange/white, and requires no painting or maintenance
- * Available in heights from 11 to 19.5 metres

OTHER MARCONI SUPPORT STRUCTURES

Include the MATHWEB* Lattice Antenna Mast Type R1010, and the Triangular Section Tubular Steel Self Supporting Tower Type R1060.

For more information talk to Chris Pettitt, Marketing Manager, Antenna Systems Division.

* MATHWEB is a registered trademark of the BP Group

Marconi
Communication Systems



Antenna Systems Division
Marconi Communication Systems Limited,
Lane Works, Waterhouse Lane, Cheimsford CM1 2QX, England
Tel: 0245 353221 Telex: 99108

A GEC-Marconi Electronics Company

WW - 008 FOR FURTHER DETAILS

POPULAR FRONT IN POWER



Probably Europe's most popular bench power supply range. More than 50,000 in use. Nine models to choose from (most with NATO stock numbers).

The Farnell L series feature large recessed meters, constant voltage or constant current, overload and short circuit protection, coarse and fine controls, a separate output switch and LED indicators for mains on and current limit.

THEY'RE EX-STOCK TOO!

Models available:

L50-05	0-50V, 0.5A
L30-1	0-30V, 1A
L10-3C*	0-10V, 3A
L30-2	0-30V, 2A
L30-5	0-30V, 5A
L12-10C*	0-12V, 10A
LT50-05 (twin)	2 x 0-50V, 0.5A
LT30-1 (twin)	2 x 0-30V, 1A
LT30-2 (twin)	2 x 0-30V, 2A

* with adjustable overvoltage protection

For quick delivery or specs. and prices contact



FARNELL INSTRUMENTS LIMITED
WETHERBY · WEST YORKSHIRE LS22 4QH · TELEPHONE 0937 61961
TELEX 557294 FARIST G
or Harpenden (05827) 69071

WW - 088 FOR FURTHER DETAILS

ONLY HB ELECTRONICS OFFER SUCH A HIGH QUALITY RANGE AT SUCH UNBEATABLE PRICES

Whatever your requirements in soldering and desoldering equipment, you won't find better value at such competitive prices.

Just take a look at these:

UNGARmatic
24V TEMPERATURE CONTROLLED SOLDERING IRON
UNBEATABLE PRICE
£16.00 ONLY
Inc Heater & Tip (+ £2.40 VAT)

SOLDERING ACCESSORIES

HANDLE (71)



with heat resistant secondary cord. **£5.85 EACH** (+ 88p VAT)

HEATER (76/77/78)



£11.43 (+ £1.72 VAT)

Temperature Ranges 77 370°C (700°F)
76 315°C (600°F) 78 430°C (800°F)

TIPS Long Life Interchangeable

Iron-clad, chrome plated and pre-tinned.

£1.30 EACH (+ 20p VAT)

	80. Long Screwdriver	3.17mm
	81. Screwdriver	5.95mm
	82. Spade	.79mm
	83. Screwdriver	2.38mm
	84. Long Screwdriver	1.98mm
	85. Stepped Spade	1.19mm
	86. Needle Tip	1.19mm
	87. Screwdriver	1.59mm
	88. Long Screwdriver	1.19mm
	92. Screwdriver	3.17mm
	93. Screwdriver	.79mm
	94. Short Conical	.79mm
	95. Adaptor	

DESOLDERING SYSTEMS & ACCESSORIES

DESOLDERING PUMP (7872)

DESOLDERING PUMP
£5.99
(+ 90p VAT)

Lightweight Anodised Aluminium

Designed for operation with one hand.

DESOLDERING KIT (50DK)

Kit Includes: 95 Tip Adaptor 6948 Slotted DIP desoldering bar tip
6982 Spring loaded extractor 5013 Super-Wick T.M. desoldering braid.

4000E DESOLDERING STATION
£285
(£42.78 VAT)

DESOLDERING KIT
£9.43
(+ £1.42 VAT)

HEAT GUN (6966G)

240 V HEAT GUN
£44.00
(+ £6.60 VAT)

Lightweight Heat Gun complete with stand and set of 4 push-on baffle adaptors

ORDER TODAY - 24 HOUR DESPATCH



For further details and comprehensive literature on all our products contact this number today 0204 386361 or fill in the coupon.

HB Electronics

CANNING
THE W. CANNING GROUP

Lever Street, Bolton, Lancs.

Please add VAT to prices shown

Post to HB Electronics (DEPT D.S.) Lever St, Bolton, Lancs.

QUANTITY	PRODUCT NO.	UNIT PRICE	TOTAL PRICE


CHEQUE POSTAL ORDER TOTAL

NAME _____

ADDRESS _____

ALL PRICES INCLUDE POST AND PACKING

WW - 042 FOR FURTHER DETAILS

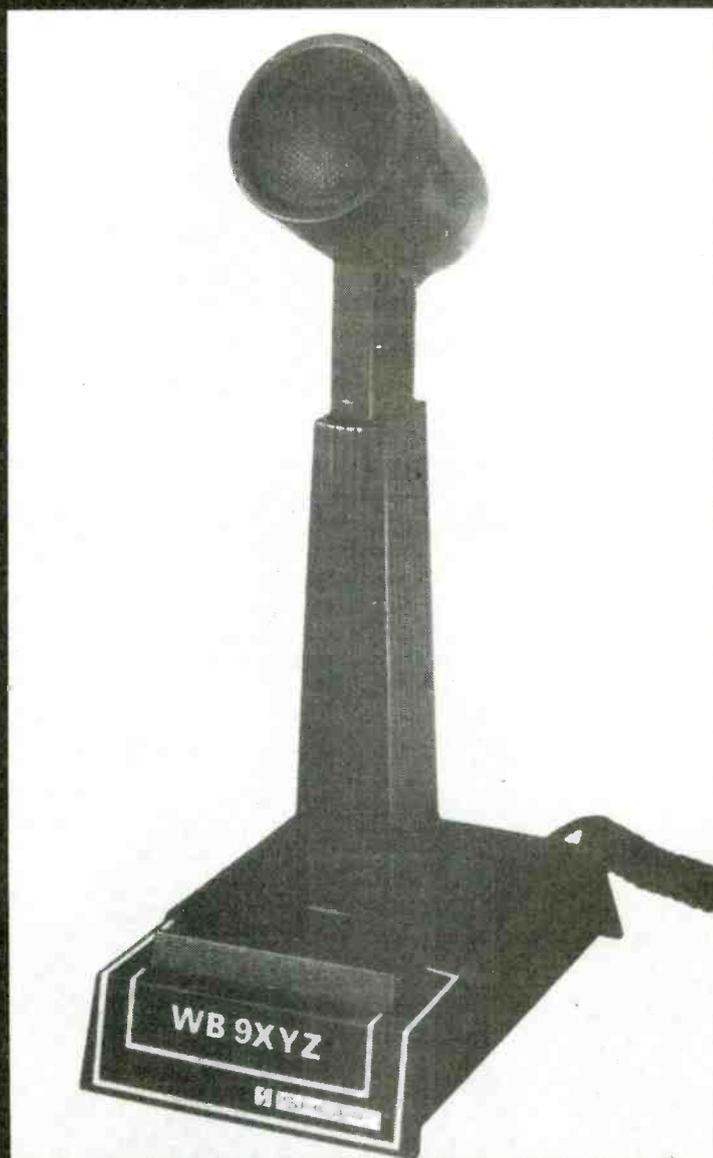

The over and outperformer

SHURE

You simply can't make it
any clearer.

For the address of your nearest dealer together with full details of the Shure Microphone range, write to:
Shure Electronics Ltd., Eccleston Road, Maidstone ME15 6AU or telephone: 0622 59881.

WW - 082 FOR FURTHER DETAILS

Editor:
PHILIP DARRINGTON

Deputy Editor:
GEOFF SHORTER, B.Sc.
01-661 8639

Technical Editor:
MARTIN ECCLES
01-661 8638

News Editor:
DAVID SCOBIE
01-661 8632

Drawing Office Manager:
ROGER GOODMAN

Technical Illustrator:
BETTY PALMER

Advertisement Manager:
BOB NIBBS, A.C.I.I.
01-661 3130

BARBARA MILLER
01-661 8640

Northern Sales:
HARRY AIKEN
061-872 8861

Midland Sales:
BASIL MCGOWAN
021-356 4838

Group Classified Manager:
BRIAN DURRANT
01-661 3106

IAN FAUX
01-661 3033

Production:
BRIAN BANNISTER
(Make-up and copy)
01-661 8648

Vision of the future

Viewed dispassionately, broadcasting information between fixed points on the earth seems to be a nonsense – a little like throwing a bowlful of sugar in the air in the expectation that some of it will fall into one's cup of coffee.

The UK is about to take the step of laying broad-band cables (optical-fibre and copper coax.) to provide more television, radio and interactive information services in the home, at a cost of several thousand million pounds. This use of cable is greatly to be applauded – not necessarily because yet more television will be provided, but because it at least makes possible the eventual use of the radio spectrum at v.h.f. and u.h.f. up to 1GHz for communication between mobile stations, which cannot use alternative means.

But there is some doubt, at least, that cable, used in the way recommended by the Information Technology Advisory Panel, is the best way of going about it. Thirty channels, twenty of them for entertainment, are proposed for the main network of optical fibre, but a reversion to copper in the form of coaxial cable for each group of users will reduce the bandwidth to around 35MHz – say four tv channels and interactive information for banking, shopping, alarms, etc.

There seems little need to institute a new programme of cable laying to provide not much more in the way of facilities than already exists, particularly when the new Telecom digital telephone network will be able to handle the two-way information – teletex, and the rest – quite adequately. If there is a real need for tens of channels of television – a need felt by viewers, not that experienced by those hoping to see the first Lord Thomson of Fleet's remarks about commercial television revived – then a direct-broadcasting satellite is the answer.

Given a commercial incentive, it seems more than likely that small dish aerials and down-converters could be manufactured at a reasonable cost, and the compromise solution, microwave distribution of

satellite broadcasts, would possibly be somewhat cheaper.

British Telecom are, after all, in the business of cables, and have been since the telephone; they would therefore seem to be the best people to instal, and supervise any system of communications using cable as a medium. The BBC and IBA have unrivalled reputations in the production of programmes and in the technical business of broadcasting. Who better, then, to continue to do so?

The 'nonsense' of broadcasting may not, therefore, be quite as nonsensical as it seems, so long as it can be kept well away from those users who need radio communication for other than entertainment purposes – the real users of radio.

The rush of information technology to the head evidently being experienced by the government could, if not regulated by wise counsel, undo the years of effort by broadcasters to provide superbly well-engineered and programmed services. There is no need for national cable television: its popularity in the US is only in part due to the proliferation of channels it affords. US television suffers from two handicaps vis-à-vis its UK counterpart – its use of the NTSC standard and its infestation with 'sponsorship'. NTSC does not take kindly to the kind of terrain US cities provide – phase errors more or less ignored by PAL create chaos in NTSC – and the kind of programmes Americans receive from broadcast transmissions are not of the highest quality in the first place. And yet only about a third of US homes are connected to a cable. In the UK there would be even less point in taking cable signals, where almost everyone can receive good signals and reasonably good programmes.

Why the need for haste? It seems unlikely that the increased export market for programmes and services anticipated by Kenneth Baker at Communications '82 would materialize, and a sudden Cabinet fascination with IT is not a good reason for impetuous change in the name of progress.

MODULAR PREAMPLIFIER



A matching unit to the 80-100W power amplifier described in the June, July and August issues of Wireless World. Each circuit in the design is separate, and can be included or omitted, as desired, or switched in and out from the front panel. The design includes a noise blanker and image-width control

In the July 1969 issue of *Wireless World*, and in a subsequent postscript in December 1970, I described a 'Modular pre-amplifier' which I had built to drive a Williamson (valve-operated) audio power amplifier (subsequently replaced by a pair of 10 watt, class 'A' transistor-operated power amps).

This preamplifier was of modular form almost by accident, in that it was intended to fit, with the minimum of inconvenience, into odd corners within the massive antique oak 'radiogram' cabinet which currently housed the Williamson power amplifier, the turntable, a home-made communications receiver, and the existing valve preamplifier - together with a short exponential-horn loudspeaker unit! To remove the valve preamplifier was too difficult a task, since it was integral with the demodulator and i.f. stages of the radio receiver, so its replacements would have to fit in where they could. This necessitated the assembly of the pre-amp. circuit from a series of modules having a low output impedance and a high input impedance, so that they could be interconnected as re-

by J. L. Linsley Hood

quired by lengths of screened cable without the need to worry about any audible degradation of frequency response.

In the event, it became clear that a modular design of this type had many attractions for potential constructors, in that they could use those bits which fitted their needs, and ignore those for which they had no requirement. The attractiveness of this approach has remained with me, and was very much in my mind when I considered what type of signal conditioning stages I should use to precede the 80-100 watt power amplifier, if these were to be of interest to anyone other than myself.


However, much has changed since 1969, and it was apparent that in the fiercely competitive and highly demanding world of 'Hi-fi' of the 1980s, much more was

necessary than the types of circuit block which were merely a large improvement on a rather off-colour 1950 d.i.y. hotch-potch. I have, therefore, tried to take a new look at what could or should be provided in the way of signal amplification and conditioning prior to the main power amplifier stage, and to put together circuits which would meet these requirements with the greatest economy in circuit design consistent with the type of performance now expected from such equipment.

The task of the circuit designer in this field has been enormously assisted by the availability of low-noise, low-distortion integrated circuit operational amplifiers of the Texas Instruments 'TL071-TL072' series, and its equivalents such as the NS 'LF351-LF353'.* Under proper conditions of use, these can give a total harmonic distortion, over the whole effective audio bandwidth, of the order of 0.01% at 10 volts r.m.s. output, and with an effective input noise resistance of the order of 2000 ohms or less. This makes it a

* An article by J.L.L.H. on these integrated circuits appeared in *WW*, September, 1982.

Fig. 1. Layout of modules in preamplifier assembly, shown in the mode adopted for normal input from a good quality record.

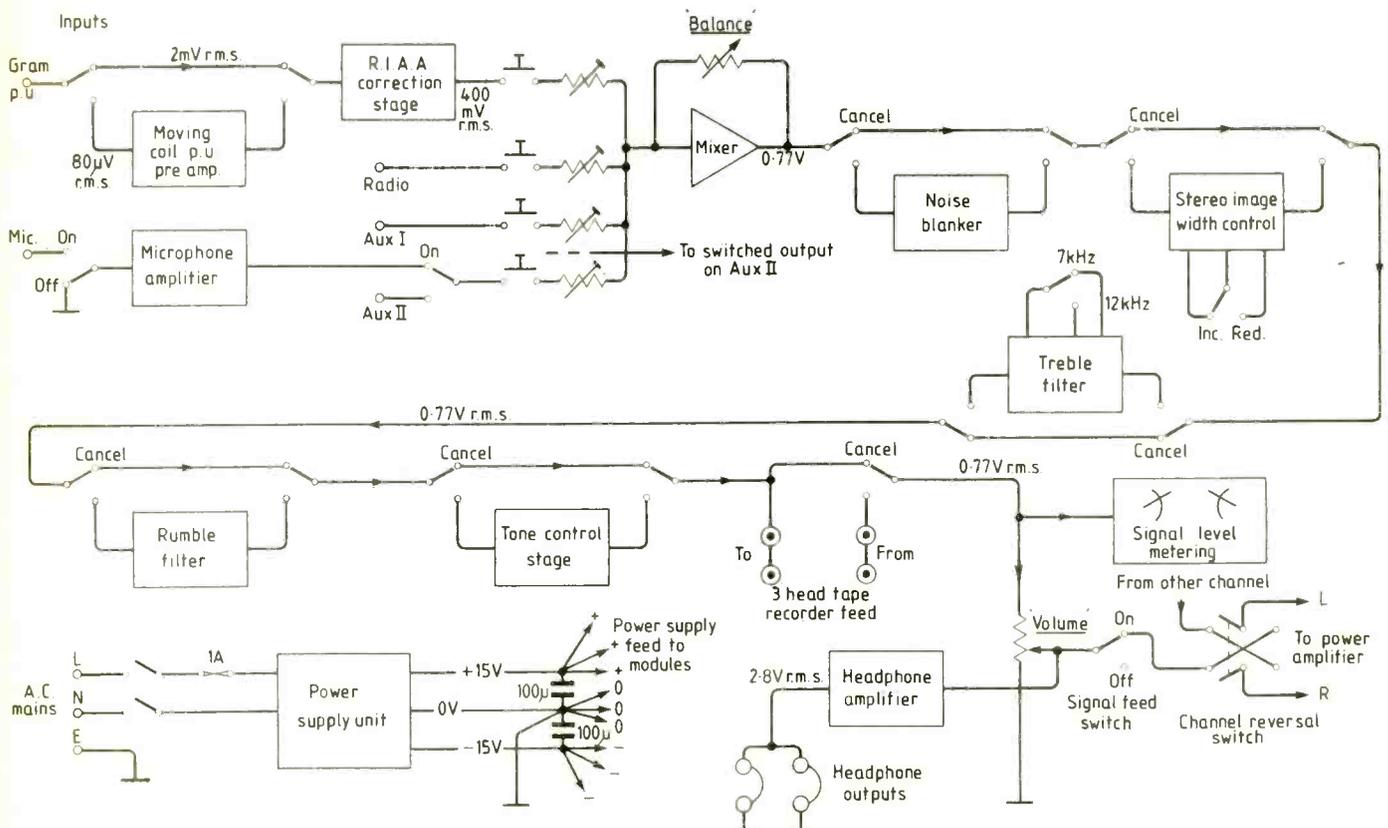

sensible proposition to envisage the pre-amplifier modules operating at the 0dB level (referred to 0.774V r.m.s. in 600Ω), employing this type of op. amp. gain block, to give both an adequate overload margin and a negligible contribution to total circuit noise and distortion. (The gain characteristics of the power amplifier unit were chosen to give maximum output at 0.774 V r.m.s. input).

I should, perhaps, explain at this point that my decision to use conventional 'audio-oriented' operational amplifiers, rather than the many, often equally good, special-purpose 'consumer' circuit blocks which are readily available, is due mainly to inward doubts on my part as to whether such consumer ICs, with their special circuit applications and their unique package and pin configurations, have an adequate guarantee of availability. Certainly some of these introduced during the 1970s have long since vanished, while the 8-pin dil or T099-based 741 and its successors have gone from strength to strength, as process or technology improvements have been incorporated into 741 pin-compatible designs — such as the TL071!

Basic design philosophy

The intention of the design is to handle the signal, at all stages after the input-signal amplification, at a low impedance — say 600 ohms — and a peak signal level not greatly in excess of 0.774 V r.m.s. through a series of optional, unity-gain, non-inverting conditioning modules (there is one exception to this, to which I shall refer later). They can be included or omitted as required without design problems, or indeed — as in the case of the prototype — included physically but omitted or selected by means of a switch. This allows the signal handling chain to have as few elements in its sequence as is necessary, while allowing the inclusion of other stages as and when these are thought to be useful. The modules I have included in this design are: a microphone amplifier; a low-noise, low-impedance head-amplifier intended specifically for use with moving-coil pickups; a two-stage 'series-shunt' RIAA-characteristic pick-up input amplifier; and a four-input, virtual-earth mixer stage. The output signal level from this stage is at a nominal 0.774V, 600 ohms impedance, and the subsequent stages operate at this level. These are: a noise-blanker stage to minimize the annoying intrusion of 'clicks' due to scratches on records; a stereo 'image-width' control stage; a two-frequency, variable-slope treble filter; an eight-octave $\pm 3\text{dB}$ additive lift or cut tone-control stage; a rumble filter having a steep cut (approximately -22dB/octave) below 30Hz; and a signal strength display meter.

For convenience in the use of the pre-amplifier when recording on to tape from the microphone inputs, I have also included a separate, twin-output headphone amplifier, in parallel with the switchable output to the main amplifier. This allows the preamplifier to be used on its own as a very high quality system for private headphone listening.

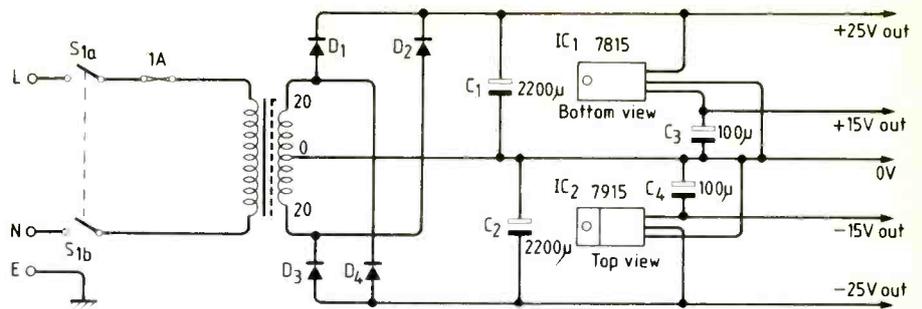


Fig. 2. Circuit diagram of power supply. Toroidal transformer from RS Components.

These stages are all based, where practicable, on the use of dual fet-input, low-noise operational amplifiers (TL072 or equivalent) operated from $\pm 15\text{V}$ d.c. supply lines, which are derived from a conventional bridge-rectifier power supply via a pair of positive and negative output integrated-circuit voltage stabilizers (7815/7915 series). This gives a signal line which normally resides within 15mV of the 0V centre-line potential, and eliminates clicks when stages are switched in or out of circuit.

I have shown the layout of the prototype preamplifier, in block diagram form, in Fig. 1, though I expect that most potential users would wish to employ a simpler combination of these component modules.

With this last thought in mind, I have described the modules, not in the sequence in which they have been listed above, but in their order of practical importance from the point of view of the user wishing to build the simplest of the possible useful combinations.

Power supply unit (Fig. 2)

This is of simple and conventional form, using a small, 10VA 20-0-20 volt p.c.b.-mounted toroidal transformer, a bridge connected rectifier, and a pair of integrated-circuit voltage regulators giving a smooth, reasonably ripple-free pair of 15V

supply lines. In addition, a pair of less well smoothed 25V lines are provided for the headphone amplifier circuit, to avoid the possible intrusion of undesirable high-current signal components into the voltage supply lines used to power the early, small signal, stages.

Although small toroidal transformers are substantially more expensive than their 'E' and 'I' cored counterparts, the very low external magnetic field associated with these toroids make it very much easier to incorporate a power supply on to the pre-amp. chassis, without hum problems. Even so, care should be exercised in the disposition of the wiring associated with the inputs to the microphone amp., the RIAA stage, and, particularly, with regard to the moving-coil head amplifier. All in all, I think the extra cost of the toroidal transformer is amply justified.

Mixer stage (Fig. 3)

Although most normal usage of any pre-amplifier will not require any form of signal mixing, nevertheless some form of input amplification and impedance transformation will be needed for most likely external input sources if it is intended to handle the signal through the remaining stages of the preamp. at 0.77V r.m.s. and a nominal 600 ohms line impedance. Nothing will be lost, therefore,

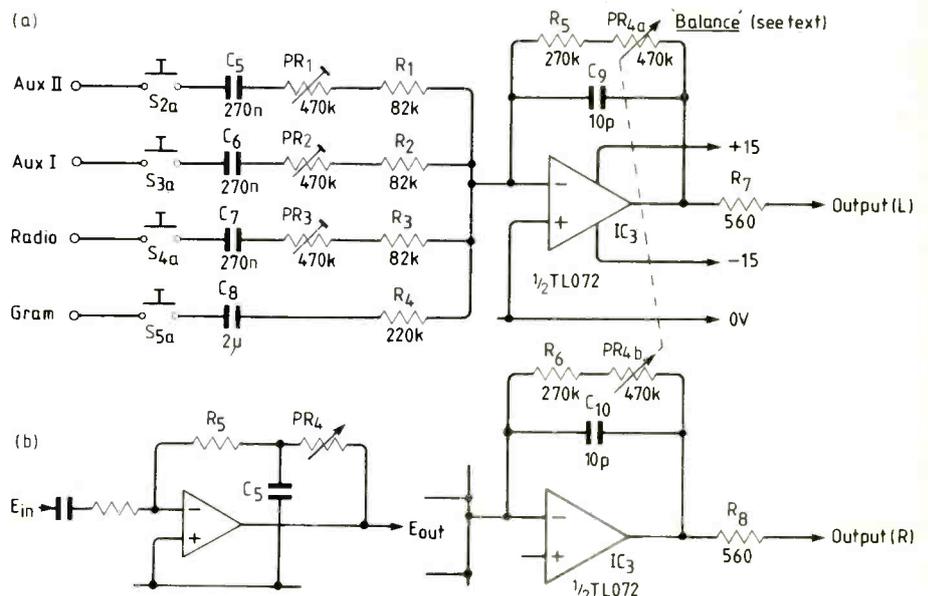


Fig. 3. Input mixer and buffer stage is at (a) Careless wiring of balance control could introduce stray capacitance, resulting h.f. lift configuration at (b).

in economy or simplicity, if the input buffer amplifier is arranged as a 'virtual-earth' mixer stage, which can operate equally well with a single or with multiple inputs.

A minor inconvenience does arise, however, in this context, due to what I think of as the absurd DIN convention for signal outputs from such things as radio receivers and tape recorders. This stipulates an output operating effectively as a constant-current source, giving an output voltage of 1mV for each 1kΩ of load resistance. This cannot give a decent signal to noise ratio at load impedances much less than some 100kΩ, and at this value or above, care must be taken to avoid electrostatically induced 50Hz ripple. The need to cater for inputs of this type has forced the adoption in this circuit of component resistor values which are much higher than I would otherwise have preferred. If the user intends only to use the circuit with signal sources having output impedances of 10kΩ or lower, all of the resistor values in the circuit can be reduced, with advantage, by a factor of 10, which will much reduce 'hum' pick-up and similar problems. If this is done, however, the capacitor values, with the exception of C₉ and C₁₀ should be proportionally increased.

Only one channel is fully drawn in Fig. 3(a): the other channel is identical with the exception of the connexions to the 'balance' potentiometers (PR_{4(a)} and PR_{4(b)}) which are reversed, so that one half will increase in value as the other is reduced. One point should be noted, however, in wiring this potentiometer - screened cable should only be used for this as a last resort, if the siting of the mixer circuit board makes it essential, since the effect of stray capacitance will be to form the circuit shown in Fig 3(b), which operates as an h.f. 'lift' configuration. The purpose of the

small capacitors (C₉ and C₁₀), of 5-10pF value, is to preclude possible instability due to this type of stray capacitance. An ideal embodiment of this circuit would be to enclose it within a small metal box, within which the balance pot. could be fixed, and short, unscreened leads used in its wiring.

On setting up, the input potentiometers (and the gain pots within the RIAA stage) should be set so that the signal levels on all the inputs peak at about the 1V level (0dB+3dB).

Series-shunt RIAA equalizing stage (Fig. 6)

Few aspects of audio engineering have generated so much debate as that concerned with the niceties of the frequency response correction required for the reproduction of RIAA-standard gramophone recordings. This debate is, I think, fully justified since so many of the circuit configurations employed to achieve this aim, even when apparently quite well designed, can be shown by mathematical analysis, when all the appropriate circuit parameters are included, to perform relatively badly.

The basic RIAA replay specification sti-

pulates the response curve generated by three time constants - 3180, 318 and 75 microseconds. This leads to the well-known curve shown in Fig. 4(a) in which the 3dB break points occur at 50.05Hz, 500.5Hz and 2122.1Hz, and in which the response at 21.221kHz and the l.f. asymptote below 20Hz are respectively -20dB and +20dB with respect to 1kHz. Part of the performance shortcomings of even well-known and prestigious commercial units stem from the almost universal adoption of the equalization circuit arrangement shown in Fig. 5(c), which employs series-connected feedback. This is done because it allows a lower apparent input noise component when measured under input short circuit conditions, although this advantage is lessened when measured with pick-up cartridge inductance in circuit. The snag with the arrangement of 5(c) is that it has a gain characteristic which tends to unity at high frequencies, as shown in Fig. 4(b), which gives a transient response to the system which is significantly different from that ideally required, and this difference is, in my experience, quite audible.

The possible configurations which can

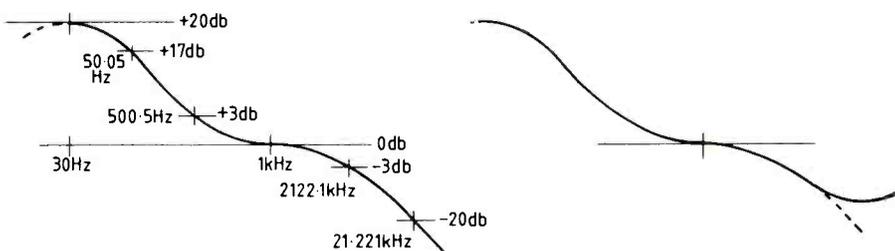


Fig. 4. RIAA recommended equalization characteristic (a). Curve at (b) shows response of series-feedback circuit seen at Fig. 5(c).

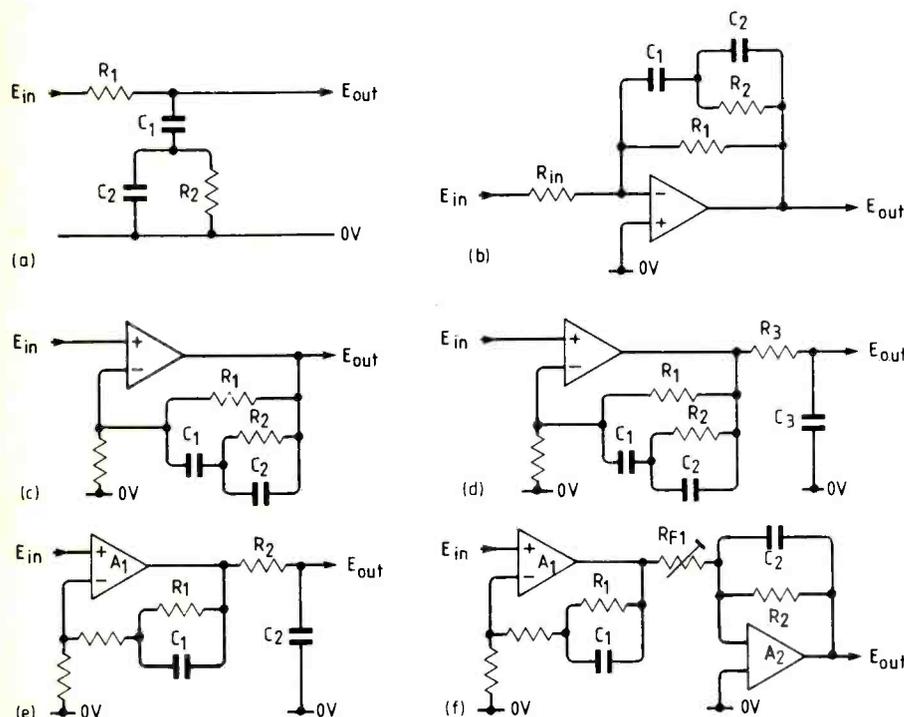


Fig. 5. Possible RIAA correction circuit arrangements: passive circuit (a); shunt feedback (b); series feedback (c); series feedback with h.f. correction RC; series plus passive network; series/shunt feedback.

be used to provide the RIAA characteristic compensation are shown in Fig. 5. An almost perfect approach to the required curve is possible with the passive network of (a) and the shunt feedback system of (b). The difficulty in the case of (a) is that some form of input buffer amplifier stage is necessary, and this will work under non-ideal conditions of high signal inputs at high frequencies, leading to problems of overload margins. For this reason it is seldom employed commercially. The somewhat less good overall noise figure associated with the circuit arrangement of (b) has also ensured its neglect in commercial designs, even though it has the merits of simplicity and accuracy of frequency and transient response. The inherent unity gain at h.f. characteristic of (c) presents the circuit designer with a problem, in that the unwanted h.f. break-point depends on the feedback factor. If a low closed-loop gain is used, to allow a high measure of n.f.b. in the interests of circuit linearity and constancy of input impedance, the upper break point will occur at a lower, and more intrusive, part of the frequency spectrum. On the other hand, a high closed-loop gain may not offer adequate circuit performance.

A solution to this dilemma may be found in the addition of a supplementary CR time-constant, as shown in (d), to straighten out the unwanted h.f. break-point due to the amplifier reverting to

Table 1
Gain of RIAA stage as a function of signal frequency

F_m (Hz)	Gain (dB)	
10	60.33	due to input coupling capacitor and feedback d.c. blocking capacitor (C_{11} and C_{114})
20	61.25	
30	60.64	
50	58.95	
100	55.05	
200	50.06	
500.5	44.47	
1k	41.63	
2122.1	38.81	
3k	36.89	
5k	33.41	
10k	27.89	
21.221k	21.67	

Note. The recent amendment to the RIAA recommended curve below 30Hz is intended to take recognition of unwanted v.l.f. components of signal output and is redundant where ancillary rumble filtering is available.

unity gain. This, however, leaves the query as to why, if a passive h.f. integrating time-constant is to be employed at all, this should not have the 75 μ s characteristic called for by the RIAA specification, leading to the system of (e), which has been used for some years by one or two of the more thoughtful manufacturers. This can have an almost ideal frequency and transient response, and its only snag is that the inherent attenuation of the output integration network requires that the output of the amplifier A_1 must be fairly large at h.f., which lessens the possible overload margins of the system.

This difficulty can be removed if the passive integration network is replaced by an active stage, as shown in (f), which results in a very satisfactory solution to the various conflicting requirements of this stage, and, in view of the ready availability of high quality i.c.s, having a satisfactorily low noise component at the signal levels associated with this second stage, does not

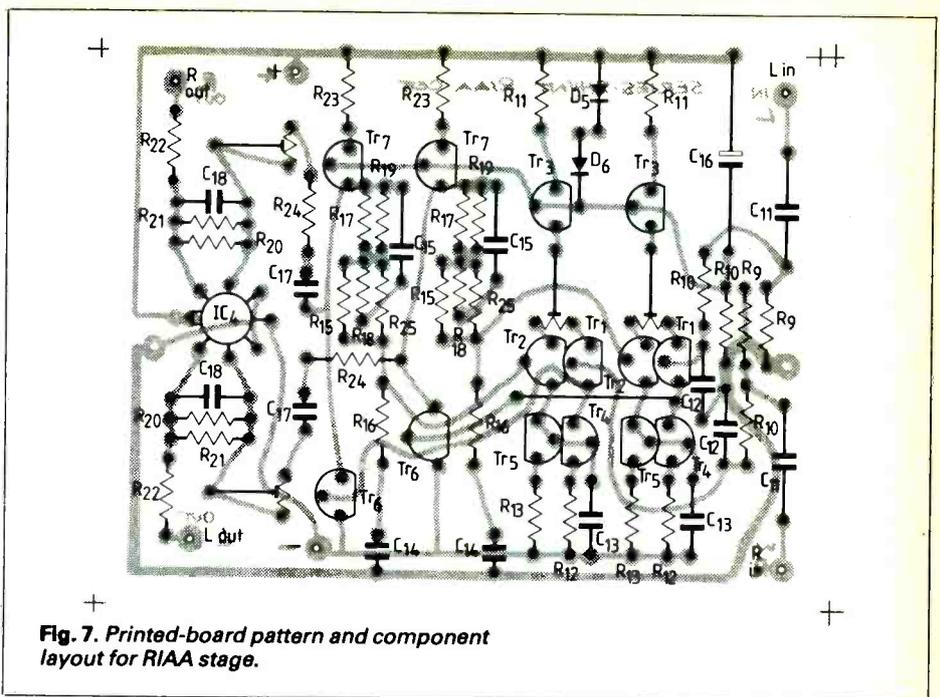


Fig. 7. Printed-board pattern and component layout for RIAA stage.


substantially increase the cost of the system in comparison with that of (e). Moreover, the independence of the overall performance, apart from gain, of the circuit in respect of the value of R_{f1} allows this to be used to set the overall RIAA stage gain. In view of these many advantages I have used this 'series-shunt', two-stage configuration as the RIAA input stage in this design. Because the target noise resistance, referred to the input, was 500 ohms, which is lower than can be obtained from currently available i.c. operational amplifiers, I have used a discrete component design for the input stage. The circuit of this is shown in Fig. 6.

This is of conventional form, employing an input long-tailed pair of low-noise p-n-p transistors (Tr_1 , Tr_2) driving a current-mirror load (Tr_4 , Tr_5). Transistors Tr_3 and Tr_7 are constant-current sources for the

input long-tailed pair and the output class A amplifier stage (Tr_6). The RC network C_{14} , C_{15} , R_{15} , R_{16} , R_{17} , R_{18} , R_{19} and R_{25} provides the required frequency response adjustment for the 10Hz-1kHz part of the RIAA curve, while the network C_{18} , R_{20} and R_{21} gives the necessary 75 μ s de-emphasis to generate that part of the curve from 1kHz upwards.

The input integration network R_{10} and C_{12} lessens the possibility of radio signal breakthrough, and the potentiometer PR_5 allows the output signal voltage to be adjusted to a level adequately close to 0V, if it is desired to operate the amplifier in a completely direct-coupled mode to minimize v.l.f. phase-shifts. The calculated frequency response of the RIAA stage, for all the component values shown, is given in Table 1. In this the l.f. open-loop gains of the two amplifier stages are assumed to be 100,000 (which is close to

Fig. 6. Final series/shunt RIAA equalizing stage of one preamplifier channel.

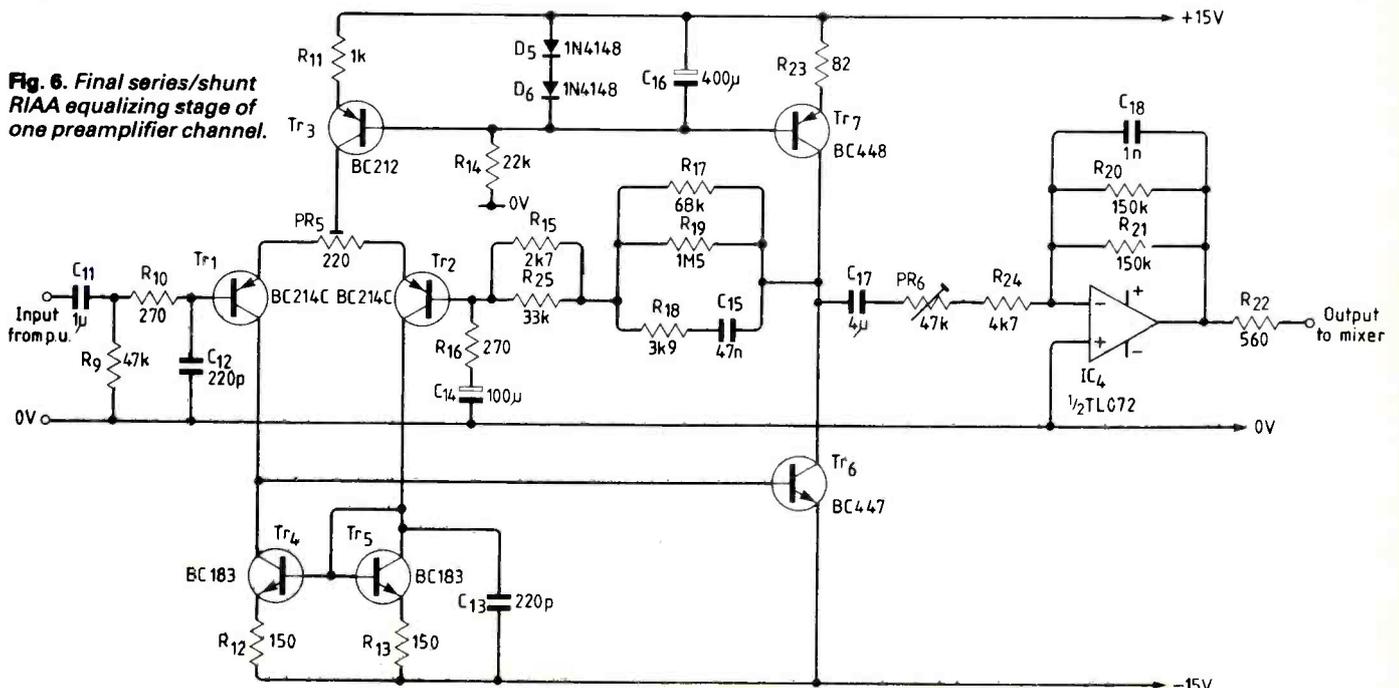

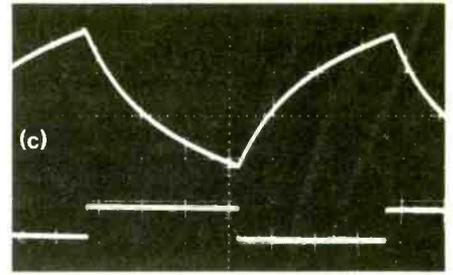
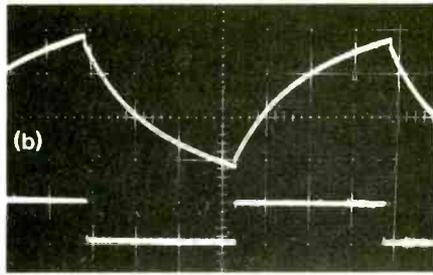
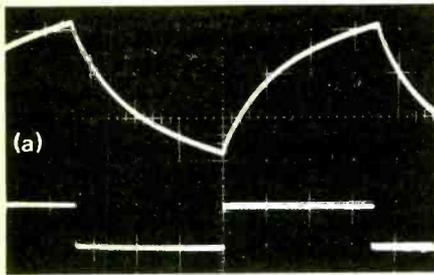


Fig. 8. Response of equalizing circuits to square-wave input. Passive circuit of Fig. 5(a) produces curve (a); curve (b) is output of system when conventional series-feedback equalizer is used; series/shunt circuit chosen and shown in Fig. 6 produces trace at (c).

Table 2 Performance of RIAA stage

Maximum output voltage swing	10V r.m.s.
Distortion at 10V r.m.s. and 1kHz	0.01%
Distortion at 10V r.m.s. and 20kHz	0.018%
Current consumption (two channels)	17mA
Distortion at 0.774V r.m.s. and 1kHz	0.003%
Input noise resistance	450 ohms
(Measured with first stage only, and with feedback network adjusted to give a flat response gain of 100x. Input s/c, measurement bandwidth 250kHz, temperature 20°C.)	
Mains hum components (50 and 100Hz)	-100dB ref. 0.774V
when fed from recommended power supply.	

the expected value), and a value of 10kΩ is assumed for the total value of PR₆+R₂₄ — this will only affect the gain, not the frequency response. The conformity of the frequency response to the RIAA standard, using preferred-value resistors and capacitors, is within 0.2dB over this frequency range. In view of likely component tolerances it does not seem profitable to aim for a closer fit than this. The other performance characteristics of the circuit are listed in Table 2.

Since the layout of the circuit may be critical to its performance, I am showing the p.c.b. layout employed in the prototype in Fig. 7. Measurements on the performance of this showed agreement with the calculated results within the 0.5dB level of confidence in the accuracy of test instruments and signal sources.

To illustrate the differences in the transient response given by the various possible types of RIAA equalizing stage, Fig. 8 shows the output given by the system

when it is driven by an input 1kHz square wave. That of a passive RC equalizing network is shown at (a), that from a conventional series-feedback system with an upper gain asymptote of 25kHz at (b), and that from the series-shunt feedback system adopted in Fig. 6 in that of (c). This is very similar in shape to that given by the passive network.

Overload margin

An important design characteristic in any input stage, where this precedes any signal level control, is its ability to avoid input overloads. Typical moving-magnet and

variable-reluctance cartridges have output signal levels in the range 0.5-2mV/cm/s recorded velocity. The highest modulation levels capable of being traced by the best of modern cartridges are of the order of 40cm/s, but, in general, the maximum groove velocities will be a good bit less than this. These very high modulation levels also only occur at frequencies in excess of 1kHz — since at lower frequencies there would be a substantial risk of groove breakthrough. The first stage gain at 1kHz is 28.58dB (26.85x) which would give a worst possible output voltage of 2.15V at the collector of Tr₆. The clipping level at this point is 10.2V r.m.s., which gives an adequate margin for overload avoidance. The gain of the second stage can be made as low as necessary by adjustment to PR₆. The 47kΩ value suggested is likely to cover all practical cartridge requirements.



Practical preamplifier system

Although the complete preamplifier, in its prototype form, contains more modules than this, a very satisfactory performance will be given, under most normal conditions, by the relatively simple system built up from the units described above, comprising the RIAA input stage, the mixer module, and the ±15 volt d.c. power supply unit, with the power amplifier stage fed directly from a 10kΩ log. dual-gang pot connected to the output of the mixer module, as shown in Fig. 1. Indeed, for the bulk of my own listening, this is all I leave switched into circuit.

The remaining modules and some constructional notes will be given in the following parts of this article.

WW

THE ETHER — AN ASSESSMENT

Does the ether exist? Dr Aspden shows that Oliver Heaviside's insight could have pre-empted Einstein's success with the General Theory of Relativity and encouraged investigations into the properties of the ether.

by H. Aspden*

Ph.D., B.Sc., F.I.E.E.

Though relativity has very little bearing upon the practical problems of radio transmission, it does preclude belief in the ether and wave propagation as contemplated by Maxwell, leaving us with no tangible alternative. Until we have a better understanding of the vacuum medium and the way in which it regulates electromagnetic wave motion, it is likely that Einstein's ideas will be questioned.

Essex, writing about relativity and time signals (*Wireless World*, October 1978), and Wellard, writing about the work of James Clerk Maxwell (*Wireless World*, March and May, 1981), both evoke this controversy.

In fact, special relativity, which dates from 1905, has very dubious support, because alternative explanation of $E = Mc^2$ and mass increase with speed is available from textbooks on classical electromagnetism¹. Besides, the transmutation of mass and energy, the basis of $E = Mc^2$, was recognized by Jeans, writing in 1904, one year before Einstein introduced his theory². How, then, can we have confidence in relativity, when Essen demonstrates so convincingly the absurdity of expecting time to pass at a different rate when perceived by different observers in relative motion?

Einstein's theory really depends, for its acceptance, principally upon the success of the later 1916 General Theory of Relativity, which brought a slight modification to Newton's Law of Gravitation. The successive elliptical orbits of the planet Mercury were known to have a progressive advance, part of which was anomalous, as judged from Newton's Law. Einstein's Law gave the right answer and relativity was thereby acclaimed.

Einstein made no reference to an earlier paper by Gerber³, entitled 'The Space and Time Propagation of Gravitation'. It appeared in 1898, eighteen years before Einstein wrote on the subject, and gave precisely the same formula for the advance of Mercury's perihelion as that presented by Einstein. Gerber's paper explained how the anomalous perihelion motion of the planet could be explained by recognizing that gravitation propagated at the speed of light. When Einstein's paper appeared in *Ann. d. Phys.* in 1916, a colleague of Gerber arranged for the publication of an updated version of Gerber's work in the 1917 issue of this same journal. However,

Gerber, then deceased, was unable to defend his theory against attack. It was in error; the direct propagation of gravitational action between sun and planet at the speed of light only gives a partial account of the anomaly.

Meanwhile, as we may read from the opening passage of Leon Brillouin's book 'Relativity Reexamined'⁴, Heaviside, in 1893, had pointed out that 'to form any notion at all of the flux of gravitational energy, we must first localize the energy'. If this is taken to heart, it leads us to recognize that the flow of gravitational energy is not directly along the line between sun and planet, but is, of necessity, via a longer route. The energy must flow from one of these bodies to the surrounding field and then from the field to the other body. This modifies the resulting retardation of gravitational action and affects the perihelion motion accordingly. The result, as the author⁵ has shown, is in exact accord with that originally predicted by Gerber. Einstein's Law of Gravitation, the only significant consequence of his general relativity theory, can be deduced by a simple classical analysis, which exploits the intuitive remark of Oliver Heaviside dating from 1893.

This, in itself, does not prove that Einstein's theory is wrong. We do, however, have viable alternative theory which is quite simple, and one must wait for the experimental evidence to direct us on the right course. This evidence is likely to come from measurements evidencing the properties of the ether. Already, in 1980, we have the experimental data of Graham and Lahoz⁶ showing that the ether can exert a force, and supporting Maxwell. Burrows (Letter to the Editor, *Wireless World*, October 1981) asserts that this is a one-off measurement needing verification. It is nevertheless backed by the discovery that the Earth's cosmic motion through space at a speed of some 400 km/s can be detected by measuring anisotropy in the intensity of the 3K background radiation. (See article entitled 'The Cosmic Background Radiation and the New Aether Drift' in *Scientific American*, May 1978). Furthermore, as we shall see below, it is supported by other evidence on electromagnetic-wave

propagation suggesting that the Earth's West-East motion due to its rotation can be directly measured as a linear velocity by optical techniques.

On such a course, the ether is destined for reacceptance and Einstein's theory may have to yield ground. There is, therefore, purpose in reassessing the ether and its properties, and in this quest we will again be mindful of Heaviside. It is to his great credit that he discovered how to design a telegraph line capable of propagating signals without distortion. The inductive and capacitive properties of a telegraph line cause the speed of propagation to depend upon frequency. By appropriate matching of these properties, as well as resistance and leakage, the attenuated signal can propagate without distortion. Now, electromagnetic waves propagate through the ether without distortion and, though the ether is not subject to resistance and leakage, it does have inductance and capacitance, because there are magnetic fields and electric fields in the vacuum.

Nature, anticipating Heaviside's contribution to telegraphic communication, has provided that extra something in the ether to secure distortionless signal propagation. This becomes an important clue in our quest to understand more about the ether.

According to its dictionary definition, 'ether' is 'a medium, not matter, that has been assumed to fill all space and transmit electromagnetic waves'. With such definition, the 'ether' remains valid terminology. The problem which some scientists have in accepting the existence of the ether arises from a further assumption that the ether cannot adapt to its environment and so must regulate the constancy of the speed of light in a universal frame of reference. When motion of the Earth about the sun could not be detected by speed of light measurements in the laboratory frame, the very existence of the ether came under challenge. Yet what logic is there in saying that A is believed to have property B, but we cannot detect property B, so A does not exist? Surely, the only valid conclusion is that A may still exist but it appears not to have property B.

Why bother? We have Maxwell's equations and we have relativity. The latter tells us not to expect to detect anything at all except according to physical laws which adapt to the reference frame of an observer. Without an observer, whether real or hypothetical, there can, in

*IBM United Kingdom Ltd.

relativity, be no definitive physical phenomena. Hence we are supposed to live in a somewhat abstract world and are encouraged not to seek to understand the universal and uniform nature of whatever it is that permeates the vacuum and regulates electromagnetic wave propagation.

I have good reason for believing that a great deal of opportunity is being missed in scientific and technological research by accepting doctrinaire theory and not keeping an open mind on this ether question. For example, it is to the credit of those engaged in precision measurement in fundamental physics that some constants can now be determined to a few parts in 10^{12} . Such precision defies imagination if related to the measurement tasks we undertake domestically or in industry. Yet, what is really fascinating is that Nature is actually able to regulate physical quantities universally and hold them stable to such accuracy, notwithstanding environmental fluctuations, wherever we look in the universe. This surely suggests a fundamental mechanism and a reference or control medium, having a universal metric binding all matter together as part of a common system. To me, this is the primary role of the so-called ether, with the light propagation characteristic assuming secondary importance.

By postulating an electric but neutral medium of the simplest possible kind and analyzing its structure, as if it were a kind of invisible and elusive crystal extending throughout space, the author⁷, in collaboration with Dr Eagles of the National Standards Laboratory in Australia, has found it possible to deduce fundamental constants (notably $\alpha = 2\pi e^2/hc$) to the measured accuracy of less than one part per million. It is this that has committed me to a course of scientific enquiry founded upon a positive belief in the ether rather than a passive acceptance of a rather sterile theory of relativity.

In the above expression, e is the electric charge of the electron, h is Planck's constant and c is the speed of light *in vacuo*. Hence the dependence of α upon the metric of the ether medium is very closely related to electromagnetic wave propagation, because $E = hv$, Planck's radiation law, signifies the energy of quanta propagated as electromagnetic disturbances at the speed of light and at frequency ν .

It is a relatively simple task to show that this structured vacuum medium can accommodate to the propagation properties of electromagnetic waves, and particularly on two basic counts. These are: (a) the fact that the speed of propagation is referred not to an absolute frame but to one which can adapt to the reference frame of an Earthly observer and (b) the equally important fact that light travelling in true vacuum suffers no dispersion resulting from its speed varying with frequency.

From the optical characteristics of ionic crystals it is known that there is dispersion, significant at frequencies in the vicinity of the natural resonant frequency

of the crystal. One should than bear in mind that energy quanta of sufficient strength can induce the creation of electron-positron pairs in the vacuum. This suggests that the ether sets a critical frequency threshold ν_0 and so may have an electrical structure conforming with this resonant frequency. Thus, in proposing a kind of crystal structure for the vacuum medium and establishing, as I have⁷, that it has a natural frequency ν_0 given by mc^2/h , the Compton frequency of the electron of mass m , one is led directly into the question of dispersion.

Before dealing with this, consider first the other problem. Michelson's experiments towards the end of the 19th century have shown that the Earth itself determines the local frame in which light has a speed c independent of direction. This is not in the least surprising if we admit the vacuum medium to be electrically-structured. Lorentz has shown that, according to classical electron theory, the speed of light in matter depends upon electron density and the oscillation period of such electrons in material media. Electron density does not depend upon rotation, nor is it a vector. Therefore, the speed of light (as opposed to its direction) should be unaffected by rotation. Hence, if there is any theoretical connexion or analogy between this situation in matter and what may govern the speed of light in vacuum, the expectation must be that, in the laboratory vacuum, the speed of light is referred to the Earth's inertial (non-rotating) frame. An experiment aimed at detecting the Earth's rotation using optical techniques referred to the vacuum should give a positive result.

Such an experiment was performed by Michelson in 1925, confirming the classical expectation from ether theory by sensing the Earth's rotation. Earlier, Sagnac had sensed the rotation of optical apparatus by speed of light measurement, a technique now applied in the ring-laser gyro. It is assumed that detection of speed of rotation accords with relativity, owing to parts of the rotating apparatus having motion relative to other parts. On the

other hand, if such experiments permit comparison of the speed of light East-West versus West-East and afford a measure of linear speed difference, it is relativity that is in difficulty. With the advance of optical measurement techniques, it should soon be possible to resolve this question.

For translational motion with the Earth, the vacuum structure acquires a linear displacement. Clearly, any displacement of electric charge in the vacuum must be transitory and oscillatory, unless it is balanced by a matching counterflow or reverse displacement of some of the charge present. Otherwise there would be a steady build-up of charge and an ever-increasing electric field. One may, therefore, visualize the vacuum as having two charge structures capable of moving through one another in opposite directions. This is quite possible because there are no rigid bonds between the charges, just electric field interactions.

It is this dual structure for charge displacement that is the key. The primary structure moves forward with the Earth. The secondary structure moves through the primary structure in the reverse direction and, by analogy with an optical effect named after Fresnel, we expect this reverse flow to affect the speed of light through the primary structure. Fresnel's theory explains why the speed of light increases in proportion to $u(1-1/\mu^2)$, where u is the velocity of the disturbing medium and μ is the applicable refractive index. This can be deduced from electron theory, but it has been verified by experiments in which the speed of light through moving water is measured.

Applying this same theory to the vacuum itself, and recognizing the counter displacement, it is an easy matter to arrive at the result discovered experimentally by the Michelson-Morley observations.

Let there be N like charges, e , per unit volume within an electrical continuum of uniform but opposite charge density σ . Then:

$$Ne = \sigma \quad (1)$$

Let N_1 and N_2 denote the population



'Being a physicist, Nurse, he may be allergic to ether, but ask him if he wants our high-speed rejuvenation treatment. Oh, and the nearest Relativist to contact if it fails.'

density in the primary structure and the secondary structure, respectively. Then:

$$N = N_1 + N_2 \quad (2)$$

On electron theory, the propagation velocity is proportional to $(ne^2/m)^{1/2}$, where there are n charges e of mass m per unit volume, also having a resonant mode at frequency given by the angular velocity ω :

$$\omega^2 = 4\pi ne^2/m \quad (3)$$

From the properties of matter, we know that the propagation velocity in a structured medium is given by $(P/\rho)^{1/2}$, where P is the pressure modulus of the medium and ρ its mass density.

These considerations guide us to the formula:

$$c_1 = (P/N_1 m)^{1/2} \quad (4)$$

for the speed of light c_1 set by the primary vacuum structure, where ρ becomes $N_1 m$. P becomes the pressure or energy density modulus of this primary structure.

Let v denote the velocity of the primary structure and u the velocity of the secondary structure in reverse flow. The linear momentum of the vacuum has to be zero unless there is a steady build-up of electric field. Hence:

$$vN_1 + uN_2 = 0 \quad (5)$$

Even in the absence of matter, the vacuum has a refractive index μ referenced on the primary structure and attributable to the disturbing effect of the secondary structure. This is simply:

$$\mu = c/c_1 \quad (6)$$

The speed of light in the frame of reference set by (5), the rest frame, then becomes c , the value set by the combined effect of the primary and secondary vacuum structures, augmented by the Fresnel drag of $u(1-1/\mu^2)$ caused by the disturbance of the secondary structure.

From (4) and (6), μ^2 becomes proportional to N_1 , with P constant, so that, from (2), μ^2 is $1-N_2/N$ and $1-1/\mu^2$ is $-N_2/N_1$. We then see from (5) that $1-1/\mu^2$ becomes simply v/u . Thus the Fresnel drag in the vacuum, which is $u(1-1/\mu^2)$, is the velocity v of the primary structure, proving, from simple classical electron theory, that the speed of light will be referenced on the vacuum structure moving with the Earth, as was found by Michelson.

We do not need to appeal to relativity for an explanation of this basic observation. The Michelson-Morley experiment verifies that Maxwell's electric displacement can be a dual and reciprocal phenomenon. Oscillations of the electrical structure of the vacuum can occur at the resonant frequency ν_0 with no reverse motion of the secondary structure or counter-displacement. However, we may expect light propagation at lower frequencies to involve counter-displacement and it is this that brings a new and important dimension to Maxwell's theory. With it comes a solution to the dispersion problem.

Note that the frequency of an electromagnetic wave has no meaning at a point in space and time. Frequency concerns rate of change and this



The Author

Following electrical engineering studies at Manchester University and two years of graduate training in industry, Harold Aspden did Ph.D. research on magnetism at Trinity College, Cambridge. Shortly after embarking on a career in the patents profession, some 29 years ago, he had an idea on electromagnetic reaction which intrigued him and led to a firm belief in the need for an ether. Dr Aspden has had success in his chosen career, having directed IBM's European Patent Operations for the last 18 years, but his ambition is to achieve success in his private quest to bring the ether back into favour. The very substantial scientific potential which Dr Aspden sees in an ether revival is evident from his book 'Physics Unified', published in 1980.

information implies comparison of signal strengths at two points in time or two points in space. However, given dual displacement at a point in space, as we now have in the theory just presented, the frequency can be codified by the relative strengths of the two displacement parameters.

The frequency of the signal is, in fact, preserved in transit through the vacuum medium, because the medium propagates two electric displacement signals in anti-phase, and the relative amplitude of the signal strengths determines the frequency. As we shall now see, this involves the vacuum adjusting to the signal in transit to adopt a locally-tuned condition having the resonant frequency of the signal. The frequency ν_0 at which electron-position pair creation occurs is the limit frequency beyond which there is no counter-displacement. However, the interesting point is that there is no forced oscillation and so no dispersion characteristic in the vacuum, since the vacuum adapts to any frequency and exhibits the properties of a tuned LC system.

It is easily shown how the capacitance and inductance of unit volume of the vacuum can be evaluated. The capacitance per unit volume is $1/4\pi$ and the inductance per unit volume is frequency-dependent and proportional to ρ/σ^2 , where $\rho = Nm$ and $\sigma = Ne$.

The presence of an electric field of strength V signifies imbalance between displacement and counter-displacement, represented by a displacement distance x ,

where x is $x_1 + x_2$, x_1 and x_2 being the respective displacements of the primary and secondary structures and x_2 being a negative quantity. The restoring force on charge e is then:

$$Ve = 4\pi\sigma ex \quad (7)$$

The energy stored by this displacement is $2\pi\sigma ex^2$, owing to the linear force rate, and, in energy density terms, this becomes $2\pi\sigma^2 x^2$, which, from (7), is $V^2/8\pi$, as expected. This is also $1/2 CV^2$, where C is the capacitance per unit volume, and so C is $1/4\pi$.

Under dynamic conditions, we can equate the force given by (7) with mx_1 to find a resonant angular frequency ω . (7) becomes $4\pi\sigma ekx_1$, where kx_1 is x . Thus, from (1):

$$\omega^2 = 4\pi Ne^2 k/m \quad (8)$$

At the threshold angular frequency $2\pi\nu_0 = \omega_0$ and this applies for the zero counter-displacement condition for which $x = x_1$ and $k = 1$. Thus, since k is $1 + x_2/x_1$, $(\omega/\omega_0)^2$ becomes $1 + x_2/x_1$, showing how the frequency ω is codified by the ratio of the displacements. (x_2 is negative.)

The value of the inductance L per unit volume is readily found from (8), because ω^2 is $1/LC$ and C is $1/4\pi$. We find that L is $(\rho/\sigma^2)/k$.

Such analysis assures us that the vacuum medium does not forcibly respond to the dynamic frequency characteristics of a signal. It propagates the primary and secondary displacements and the local vacuum resonates at the optimum frequency set by these displacements. In this way the signal frequency is preserved over vast distances.

The dual electrical displacement suggested above greatly strengthens the basis on which one can develop a phenomenological ether theory supporting Maxwell's equations. More important, however, it opens the path for new avenues of research into the effects of energy absorption from electromagnetic waves and their mutual interference. Meanwhile, note that Einstein's $E = Mc^2$ law, the keystone of special relativity and his law of gravitation, the basis of his general relativity, have both succumbed to alternative explanation⁵⁻⁸.

It is likely to be in the optical measurement field, involving speed of light tests in relation to Earth rotation, that we may see the determining experiments, crucial to relativity. The ether will surely survive. WWW

References

1. H. A. Wilson, 'Modern Physics', 2nd., Blackie, 1946.
2. H. H. Jeans, *Nature*, 70, 101 (1904).
3. P. Gerber, *Zeitschrift f. Math. u. Phys.*, 43, 93 (1898).
4. L. Brillouin, 'Relativity Reexamined', Academic Press, 1970.
5. H. Aspden, *J. Phys. A: Math. Gen.*, 13, 3649 (1980).
6. G. M. Graham and D. H. Lahoz, *Nature*, 285, 154 (1980).
7. H. Aspden and D. M. Eagles, *Physics Letters*, 41A, 423 (1972).
8. H. Aspden, *Int. Jour. Theor. Phys.*, 15, 631 (1976).

COMMUNICATIONS

Falklands electronics

The fierce media criticism of inconsistent censorship and the absence of any video link with the British Task Force in the South Atlantic (at least until the despatch of Gresham Lion digital slowscan tv equipment) has been followed by many revelations of the improvisations that were necessary to overcome operational problems and the absence of airborne early-warning radar.

The satellite-carried speech links made available to the reporters, but also presumably used for encrypted Service traffic, certainly provided reliable and reasonably good-quality communications (though this would not necessarily be the case against an enemy with more sophisticated jamming or anti-satellite systems). Nevertheless it has been alleged that there remains a serious e.m.c. problem that required radar to be turned off during satellite transmissions. It has also come as a surprise to find the extent to which missile countermeasures still depend on the use of vast amounts of "chaff" – the "window" technique of World War 2 – with *Aviation Week* reporting that Plessey Aerospace were working a 24-hour-day, 7-days-a-week producing the stuff. Chaff and helicopter decoys seem to have proved moderately effective in diverting some Exocet missiles away from their intended targets – though one that was deflected from an aircraft carrier promptly locked on to the ill-fated Atlantic Conveyor. There have been rumours of attempts to recover nuclear weapons from some sunken Royal Navy vessels, though it is equally possible that the work is aimed at recovering cryptographic or other sensitive material. Equally alarming are the reports that two Russian Cosmos ocean surveillance satellites launched during this period were carrying nuclear electric-generators for the radars and were similar to the nuclear-powered satellite that caused so much public concern when it came down over Northern Canada on January 24, 1978. If the Falklands have underlined anything it is that we live in an extremely dangerous world – to which advanced electronics and communications contribute. It can be claimed that the British electronics systems were used defensively as well as offensively, and mostly worked, though in some cases not without considerable last-minute improvisation.

Manpack satellite

The Special Air Service had its own communications links back to the UK as well as what was clearly a considerable number of clandestine infiltration links between the Task Force and the SAS reconnaissance and intelligence-gathering parties.

There has been no public information given on whether these communications were effected via satellite or on h.f. or a mixture of both. But at least one British firm, Ferranti Electronics, has recently announced the development of a manpack portable satellite terminal "Mansat" that has a shallow-reflector aerial built into a rigid carrying module. It could, one imagines, be used for infiltration communications. This equipment, working on about 7.5 GHz, can provide a duplex telephony link and a 50 bit/sec telegraphy link using a standard QWERTY-type keyboard. It works from internal batteries, and GaAs field-effect transistors are used in both the receiver and transmitter chain. Microprocessors take care of message storage, encoding, display and alarm monitoring. It is claimed that the equipment can be positioned and in contact within two minutes. But I rather doubt if such equipment was used in the South Atlantic, and "old-fashioned" h.f. may have provided the intelligence.

Wideawake Ascension

Back in 1967 I was lucky enough to be one of a small party of journalists forming possibly the only press trip ever made to Ascension Island. It was at the time of the opening of the Cable and Wireless earth station built by Marconi on the island as part of the elaborate NASA Apollo communications system. The island, even then, was an amazing contrast between modern communications, missile tracking aeriels, a BBC overseas relay station with four 250 kW transmitters and an old-style brass-instrumented telegraph cable station (this was before the South African telephone cable), giant turtles coming ashore to lay their eggs and millions of wideawake terns, all to a backdrop of a desolate, crater-pitted, near lunar landscape. Water was in short supply but whisky was 60p a bottle, gin 25p and the temporary residents paid no income tax! And though I recall well the computerized, air-conditioned NASA tracking station and the large futuristic "aerial farms" what really remains in the memory is the pleasant English farm at the top of Green Mountain where, on behalf of Cable and Wireless, a Somerset farm-manager looked after 2000 sheep, 300 pigs and 35 milking cows! The island has been a natural communications centre since the days when it was garrisoned by the Royal Navy and Royal Marines. Sadly, there are still the graves of young sailors put ashore with yellow fever in the nineteenth century. Landing a large Britannia aircraft at Wideawake Airport was quite an event for the island and one wonders how much it has all been changed by the furious burst of activity this year.

Whose light pipe?

British Telecom do not believe in hiding their light under a bushel or burying their talents in a napkin. Not only have they instituted a prestigious Martlesham Medal to give recognition to their own research engineers but they recently put out a 1500-word, seven-page press release to mark the second such award to Dr George Newns and Dr Keith Beales. This was for their development of the double crucible production process for optical fibres. I am all for giving medals to engineers and full credit to those whose work is seldom in the public eye. But BT's publicity boys do lay it on a bit thick. Was it really BT who, to quote the press release, "first took up the challenge (of optical fibres) and began devoting time and resources to the enormous problems of translating theory into practice"?

It is evident from the release that BT set up its research team for optical fibres during 1968. Yet I recall talking to Dr Kao at STL at Harlow, early that year. He showed me some of his continuing work on optical fibres which had obviously been started many months earlier. It was devoted to the very practical problem of producing low-attenuation glass. He was convinced this was possible and outlined to me the role optical fibres could play in telecommunications.

BT's press release also recalls that the first Martlesham Medal went last year to Dr Tommy Flowers "the man who invented Britain's and possibly the world's first computer . . . Collossus (sic)". Again Tom Flowers deserves the highest praise for his important pioneering work on the Bletchley Park cryptographic computers but it would have been nice if BT's publicity boys had included just a passing reference to Alan Mathison Turing – but then Turing owed his allegiance to GCCS and "C" of the Secret Service and not to the inventive British Post Office!

Stormy ionosphere

Solar storms, sudden ionospheric disturbances and blackouts, high levels of polar cap absorption and intense auroral conditions continued to dominate the h.f. scene in July. In fact July 12-18 witnessed one of the biggest proton flare events for many years. A blackout on h.f. on July 12 lasted four hours. While this resulted in generally poor h.f. conditions, v.h.f. operators were able to take advantage of the near-sensational auroral conditions which unusually extended as far south as the Mediterranean area. British and Irish stations, for example were able on 144 MHz to contact F6KAW/EA6 in Minorca.

Although it is possible to trace a link between solar storms and auroral conditions, there still remains no positive way of

predicting "sporadic E" openings which are linked to wind shears in the upper atmosphere. However Jim Stewart, WA4MV1 has recently confirmed in a letter to *QST* the growing belief that a link can be shown between Sporadic E and certain types of severe weather, particularly severe thunderstorms. He notes that apart from heavy rain and turbulence, some thunderstorms appear to produce wind shears and large static-electric charges that play a significant part in the process. Examination of hundreds of weather maps and other data have convinced the American that there is very often a severe weather area roughly midway between stations linked by sporadic E propagation. Storm activity above 60,000ft could result in 144 MHz openings, whereas storms at around 40,000 ft tend to result in 50 MHz openings. While his results may apply primarily to the large land area of the United States, it is one of the few ideas so far advanced that could lead to prediction of Sporadic E openings.

AMATEUR RADIO

Amateur satellites

So far attempts by Stanford University, using a large dish aerial, to regain control of the British UoSAT OSCAR satellite, built by the team at the University of Surrey — appear to have failed. As reported earlier a "one-in-a-million" software error caused both beacon transmitters to be switched on simultaneously with consequent desensitizing of the on-board receivers. At the time of writing it is still hoped that control can be regained by a strong command signal but hopes are fading, and this experimental scientific satellite remains virtually out of action.

A low-orbit Russian amateur radio satellite "Iskra Two" which was ejected from the manned Salyut/Soyuz orbiting space station on May 17 re-entered the earth's atmosphere early in the morning of July 9. Although it carried an h.f. transponder this was activated only for a brief period.

Amsat-UK (94 Herongate Road, Wanstead Park, London E12 5EQ) has published a new edition of its useful 16-page booklet "Guide to Oscar Operating" providing the basic information needed by amateurs who wish to have a go at making contacts through Oscar satellites and background information and practical experiences since the first amateur satellite was launched in October 1961.

Here and there

I.A.R.U. statistics now put the total number of licensed amateurs at over 1.1-million of which about 200,000 are in Region 1 (Europe/ Africa), about 480,000 in Region 2 (North and South America) and about 470,000 in Region 3 (Asia and Oceania). Japan heads the table with around 450,000, U.S.A. 390,000, West Germany 42,000, U.S.S.R. and Argentina each 26,000. Then comes the U.K. with around 25,000 followed by Canada 21,000, Italy 17,000, Brazil 14,000 and Australia 13,000 though these figures may already be a little out-of-date.

A Dutch enthusiast, Ryn Muntjewerff is now known to have received 435 MHz amateur television pictures in November 1979 from F1AJD, Angouleme, France over a distance of about 1000 km, thought to be a record for this band. Among the journals and newsletters devoted entirely to amateur television are: *CQ-TV* of the British Amateur Television Club, "*A5 Amateur Television Magazine*" (USA monthly), "*The ATVer*" (Australia), *NBTV* (Narrow Bandwidth Television Association, UK) and "*Der TV Amateur*" (West Germany).

Aerial pioneers

Two names that have become almost part of the language of aerials — Beverage and Kraus — have recently been reflecting in the columns of *QST* on the continued value of designs put forward in 1922 and 1937 respectively. Harold Beverage, ex-W2BML first developed and described his very long but low aerials 60 years ago when working for RCA. He has revealed that after becoming interested in radio as early as 1912 he had two job offers on graduating from college: playing trombone at Loews Theatre for £2 per week or working for General Electric for \$11.20 a week. Such was his enthusiasm for radio that he opted for G.E.! Apart from the still famous Beverage aerial, he was co-inventor with H. O. Pearson of the "diversity reception system" for combatting fading on h.f. Curiously the most complex diversity systems these days — quadruple diversity — are usually at much higher frequencies for troposcatter or long microwave links across sea paths.

Professor John Kraus, W8JK — for many years a leading figure among American radio astronomers — made his name initially when he adapted Dr George Brown's work on close-spaced medium-wave aerials in order to produce the first effective bi-directional rotary h.f. beams in 1937. This was a few months before another leading amateur, Van Roberts, similarly adapted Brown's work on close-spaced parasitic arrays to come up with the aerial that has made Yagi's name famous throughout the amateur radio world. John

Kraus shows that a special attraction of the original W8JK-type of array is that it can work effectively over a continuous frequency range of more than 3 to 1 without traps or loading coils and with non-critical dimensions. The availability (so far in some countries only) of 18 and 24MHz bands makes the W8JK design particularly attractive and its may well be heading for a revival.

So far American amateurs have not been able to make use of any of the new h.f. bands (10, 18 and 24MHz) since the USA have not yet ratified the WARC 1979 agreements. Japanese amateurs were authorized to use the 10MHz band from April 1, 1982. Maximum power is 500 watts for stations having a frequency measuring instrument and 10 watts for those without!

Heavy guns

The American FCC have been firing some heavy guns recently in its efforts to stamp out abuses of the American radio regulations. A former Californian amateur indicted of operating a station without a licence and using obscene, indecent and profane language has been facing, if found guilty, a possible maximum sentence of 10 years imprisonment and a fine of up to \$70,000. Another Californian lost his amateur licence after taking a licence examination on behalf of a candidate. The FCC has refused to renew the licence of a former amateur who two years ago was found to have deliberately jammed an amateur repeater. Unlicensed operators facing charges of putting out broadcast transmission on 7040kHz from Miami directed at Cuba have been referred to the U.S. Department of Justice with a request for criminal prosecution which could result in a \$10,000 fine and/or a one year prison sentence.

In brief

A reminder that many local adult centres are starting RAE classes in the second half of September. In Beckenham, Kent the demand for morse classes in the London area has caused a switch from RAE classes to morse training Date of the Midlands v.h.f. convention has been changed to October 9 at The Polytechnic Wolverhampton. Reminder that Welsh Amateur Radio Convention is at Oakdale Community Centre, Blackwood, Gwent on September 26 . . . There are hopes that amateur radio activities may be permitted again soon in Poland. . . A "congress of radio amateurs connected with the railways" (FIRAC — Federation International Radio Amateur Cheminot) is to be held at Gunton Hall, Lowestoft from October 4 to 8 (details G. Sims, G4GNQ, 85 Surrey Street, Glossop, Derbyshire SK13 9AJ).

PAT HAWKER, G3VA

CIRCUIT IDEAS

Static b.c.d.-to-binary converter

Converters such as those used in synthesizers, where a decimal channel number might have to be changed into binary form to drive a p.l.l., might be in the form of a relatively expensive and, perhaps inconvenient prom, or as binary and decimal up/down counters in parallel, which can give carry and synchronizing problems, or they may be made up using shift registers with correction networks like the 74184. The following is a static cmos converter on similar lines.

For digits zero to nine, both binary and b.c.d. forms are the same but the first decimal carry, at 10, leads to problems at the 'tens' A input, resulting in a binary 16 being interpreted. Therefore, six has to be subtracted to return the original value, 10. At the next carry, b.c.d. 20, binary 32 is interpreted, and must be corrected by


Decoded output IC ₁	Equiv decimal range	Subtraction value	Added complement								
			IC ₃				IC ₂				
			(B ₄) (128)	B ₃ 64	B ₂ 32	B ₁ 16	B ₄ 8	B ₃ 4	B ₂ 2	B ₁ 1	
0	0 - 9	%	X	L	L	L	L	L	L	L	L
1	10 - 19	5	X	H	H	H	L	L	L	L	L
2	20 - 29	11	X	H	H	H	L	H	H	L	L
3	30 - 39	17	X	H	H	L	H	H	H	L	L
4	40 - 49	23	X	H	H	L	L	L	L	L	L
5	50 - 59	29	X	H	H	L	L	L	L	H	L
6	60 - 69	35	X	H	L	H	H	H	H	L	L
7	70 - 79	41	X	H	L	H	L	H	H	L	L
8	80 - 89	47	X	H	L	H	L	L	L	L	L
9	90 - 99	53	X	H	L	L	H	L	L	H	L


X = don't care

subtracting twice 6, and so on for each successive decade. Here, rather than carrying out subtractions, two's complements implemented by diode matrices are added using two 4-bit full adders. A one-out-of-10 decoder chooses the correction value as represented in the table. B₄ of the second

adder is not used, but should be tied to either rail. Nine of the 33 diodes may be replaced by the inverter as shown. Expansion of the circuit is possible.

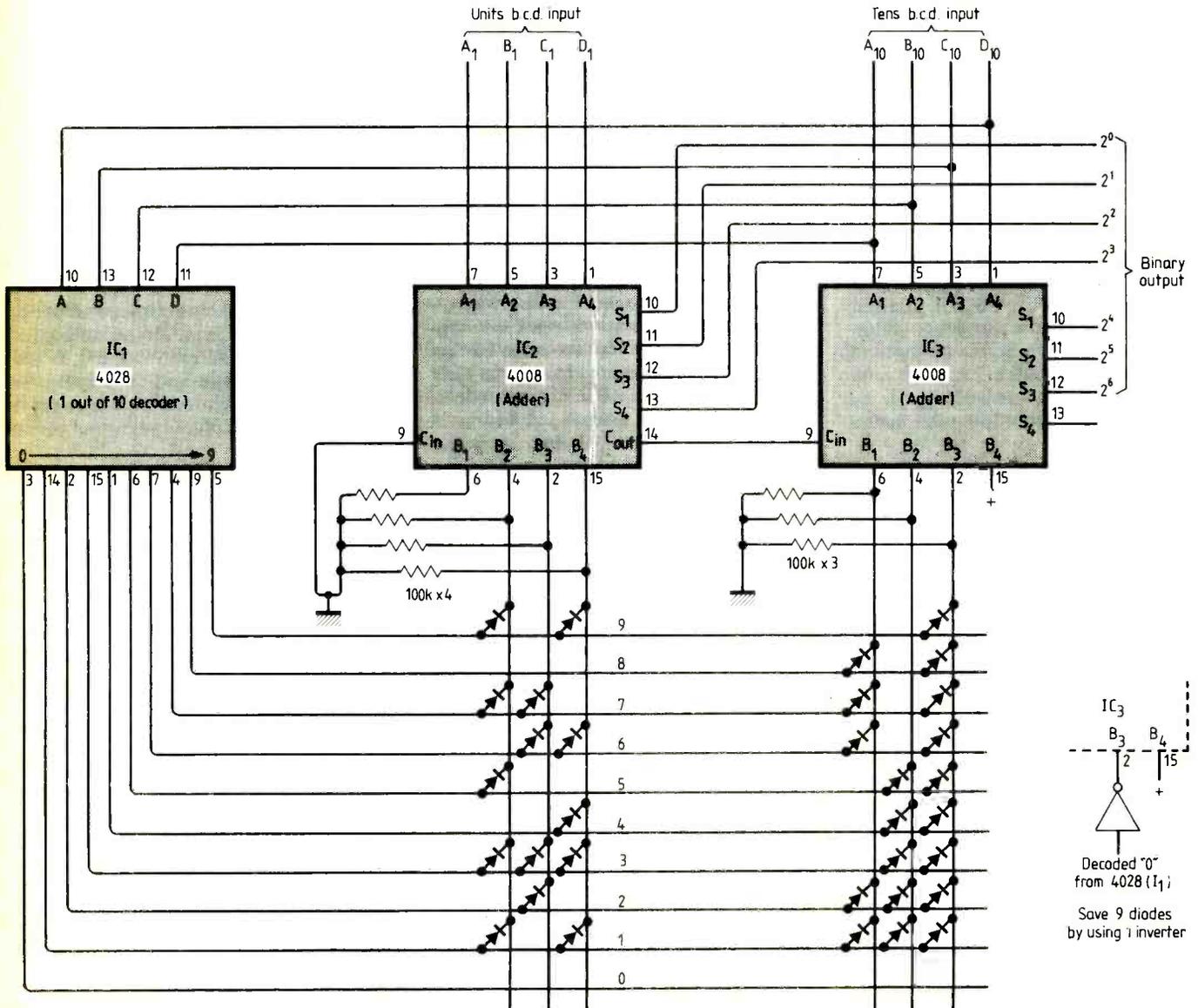Falko Kuhnke
Institut für Geophysik und Meteorologie
Braunschweig



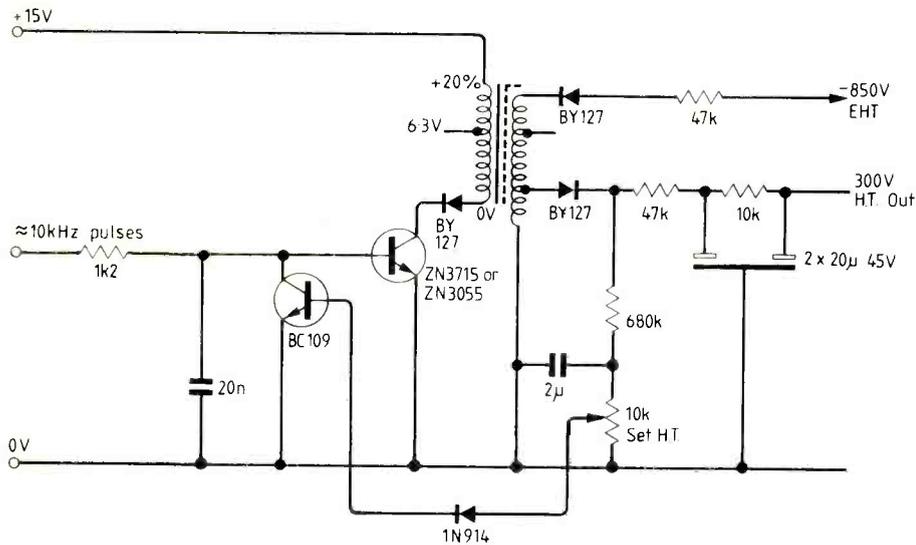

Oscilloscope supply

Circuit shown provides around 850V at 75µA and 300V at 2mA from a 15V supply. Insulation of the output transformer (an RS196 224) is flash tested to 5kV but one could be specially wound using, say, a Mullard FX2243 or Siemens 631 N 27. The prototype was driven by a uni-junction transistor oscillator and buffer circuit.

G. V. Whitney
Sale
Cheshire


Minimum-parts sequencer

Combining a cmos decade counter with the 555 timer yields a simple yet versatile adjustable-delay sequencer. Buffered outputs 1 to 9 are activated in succession as the 4017 counter is clocked. Each output remains on for a duration proportional to the values of R_1 to R_9 respectively.

A momentary high level on the start input resets the counter, activates output 1 and starts charging C_1 through R_1 , D_1 and R_{10} . As C_1 charges, the timer output goes high, causing a negative transition, due to the inverter, on the counter's clock input, which is ignored. When C_1 reaches $2/3 V_2$, the timer output goes low, clocking the counter, enabling output 2, setting R_1 low while pulling R_2 high, and enabling another charge cycle on completion of discharge through R_{10} .

The sequence continues until the ninth count, when inhibit input (pin 13) is activated, preventing further clocking. Since all charging resistors are deactivated, the system remains inactive until start is pulsed. A more elegant approach would be to connect an extra inverter between the junction of the 9 and inhibit outputs of the counter and the reset (pin 4) input of the timer. Keep in mind that upon power-on or after the timer has been reset (low on pin 4), the first timing period will be approximately twice as long as the reset, due to the capacitor having to charge from ground instead of $1/3 V_s$.

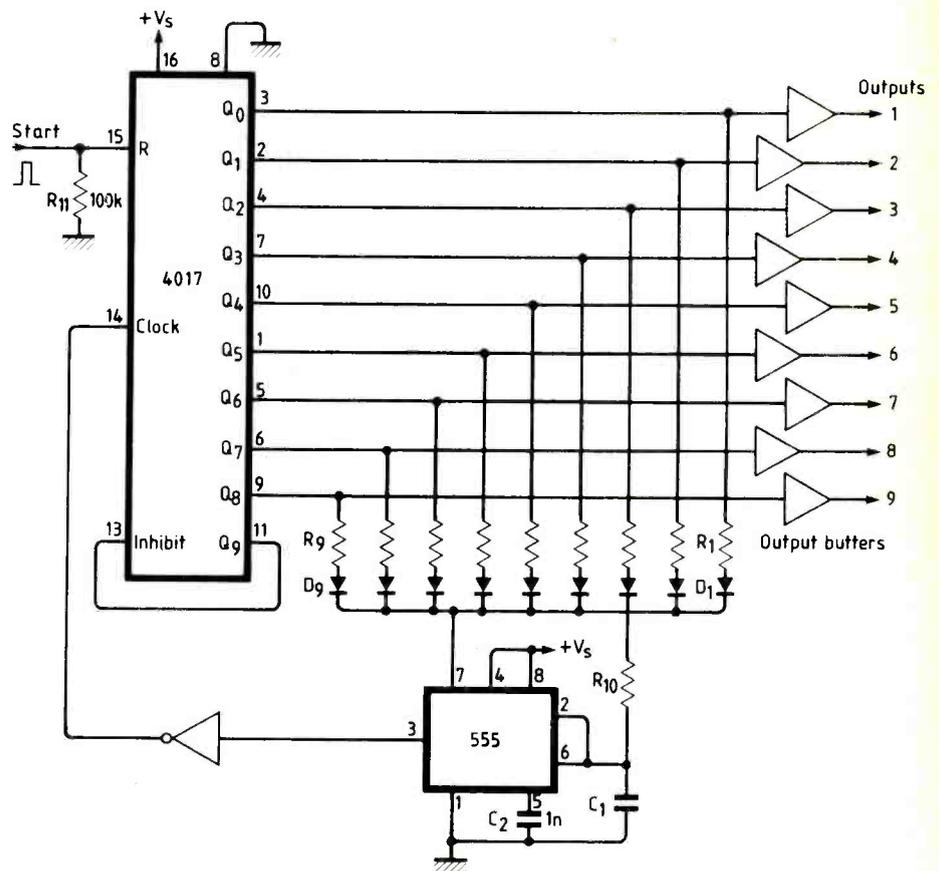Many variations are possible. For example, repetitive sequences of up to 10 steps can be obtained by grounding the counter's inhibit input and connecting an extra resistor and diode to timer pin 7 from the counter's 9 output. A 4-bit binary counter feeding a 4-to-16 converter (e.g. cmos 14515) will provide up to 16 lines.



Pin 5 of the timer, shown de-coupled to ground through C_2 , can be used as a modulation input to compress or expand all output times simultaneously, i.e. scale factor. Output buffers can be selected according to requirements or omitted entirely if driving other cmos logic.

Values of resistors R_1 - R_{10} should be kept as large as possible to minimize loading of the cmos output stages during

charging. If potentiometers are used to trim timing, R_{10} should be at least 4.7kΩ to minimize inrush current, should any pot be turned to zero resistance. The time delay caused by the combination of R_{10} and C_1 adds a constant to the time that each output remains high.

V. Labuc
Noranda Research Centre
Quebec

FAULT-FINDING IN MICROPROCESSOR-BASED SYSTEMS

The complexity of some systems aggravates the problem of fault location. Techniques include the use of special equipment and the ability of the processor to diagnose itself. The author discusses some of the available equipment and techniques.

During the last decade electronic systems have changed substantially in conception and complexity due to the introduction of microprocessors and their accompanying devices. Previously, such systems were designed using families of integrated circuit logic elements, the most complex of which would probably have been a four-bit synchronous updown counter. Fault finding in sequential random logic systems involved the use of logic diagrams annotated with waveforms and timing sequences, and required that the fault finder had a detailed understanding of the system operation. The equipment required would be a two-channel oscilloscope with various trigger and sweep facilities, and possibly a special test rig to provide signals to stimulate the printed circuit board, if it were being tested remote from its system. The time required to find a fault would depend largely on the skill of the test or service engineer. Equipment in service could be repaired quickly by module or PCB replacement, but ultimately, fault finding down to component level had to be undertaken in the manner described above.

Systems designed around microprocessors are conceptually different in that they are bus structured with data being transferred around the system in parallel. In general, input data is read and processed in the CPU to produce the output under the control of the system software. When debugging or fault finding on this type of system, many lines need to be monitored simultaneously and in synchronism with some derivative of the system clock. 'Glitches' and undefined levels on tri-state busses at other times are of no consequence.

Currently systems are being designed using the fourth generation of microprocessors with 20-bit address busses and 16-bit data busses. Clock rates are up to 11 MHz; and multiprocessor systems, with bus access time division multiplexed between processors under the control of a master, are being implemented as solutions to the demands of more processing power. All these advances in technology and system complexity aggravate the problems of fault location. To assist the designer and test technician in overcoming these problems various techniques can be used, some requiring special equipment and some utilising the power of the proces-

by **Stephen Day**

sor in self-diagnosis of faults. It is the purpose of this paper to discuss the current state of the art equipment and techniques and indicate how they are applicable to fault finding from design and development through assembly and test to in-field service.

Logic analysers


The logic analyser was the first of a range of equipments designed specifically for data domain analysis and was initially produced as an instrument for use in the laboratory during the development phase of a microprocessor implementation project. Its appearance was similar to an oscilloscope but having multiline data probes. The data on each probe line could be sampled under control of a system clock which could be qualified typically to sample once every processor instruction cycle. The samples were stored in an internal memory with a capacity of up to 16x16-bit words, and the trigger word, from which sampling was initiated, was set up on a bank of switches.

More recently the ergonomics of logic analysers have been significantly improved and memory size has been increased up to 1000x20-bit words. The options available for setting up the equipment are displayed as a menu on the screen, with a cursor to indicate the next input required. The keyboard is used to enter the information to give the required operating sequence. Typical of the options for trigger selection are: clock source, edge polarity, trigger word, clock cycles delay, trigger start or end, block pattern recognition etc. Possible data display modes on the screen are: (a) Table. A listing of the sampled data states in binary or to some other numerical base such as hexadecimal (Fig. 1a) (b) Timing. Data is displayed across the screen as several channels showing the HI-LO activity (Fig. 1b). (c) Graph. The horizontal axis represents analyser store addresses and the vertical axis the numerical value of the stored data (Fig 1c). (d) Map. Each 16-bit sample is divided into its upper and lower 8-bit bytes. The values of these produce the vertical and

horizontal deflection. (1d). The top left of the display is address 0000 and bottom right is FFFF. The map display will assume some unique pattern depending on the frequency of access of the various address locations being accessed by the program being executed.

When monitoring the data on a microprocessor bus it is possible to reconvert the binary data back into its mnemonic assembly language from automatically and this feature, known as disassembly, has been built into some instruments. The analyser has a personality module according to the microprocessor in the system under development and the table display can then be a list of assembly language statements which are more readily interpreted for program debugging.

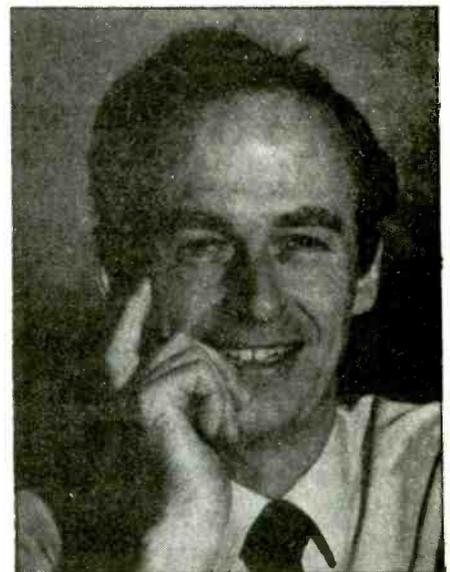Remote access for initialisation and interrogation can also be provided by



The Author

Stephen Day, BSc, CEng, MIEE, graduated from Manchester University during his student/graduate apprenticeship with the UKAEA at Aldermaston. Later he moved to Godwin Warren Engineering as Senior Design Engineer. In 1974 he joined the IBA as a Senior Engineer and is at present working there as Project Leader for enhanced teletext.



connection to an instrumentation bus.

A further development of the logic state analyser is the logic timing analyser. This device samples the data input lines with a clock which is asynchronous with the system under test. In this way it is possible to trap random events or 'glitches' as small as 5 ns wide by using clock frequencies up to 20 MHz. The display is usually presented as a timing diagram. One particularly useful application for this type of instrument is in trapping intermittent faults. The technique is known as 'babysitting'. Having established what trigger condition to use, a set of normal data is sampled and transferred to the secondary or reference memory. The user can now leave the instrument to monitor the system under test and it will acquire new data each time the pre-selected trigger point is encountered. Any difference between the new data and the reference data will cause the analyser to stop sampling and indicate where the difference has occurred. On return the user can step through the logic timing diagram on the display and draw conclusions for further investigation of the fault.


In circuit emulation (ICE)

This is a technique for using a microprocessor development system to debug both hardware and software during the developmental phase of a project. Early microprocessor development systems were essentially for software development. They had the usual suite of routines for editing and assembling programs and it was possible to partially debug the software by limited execution within the development system. It was then necessary to commit the software to eprom in order to transfer it to the hardware of the system being developed. For further debugging use was made of a logic analyser to find out why programs operated incorrectly or whether the fault was in the hardware.


In-circuit emulation is created by additional hardware which allows the microprocessor in the target system to be emulated by a similar microprocessor in the development system. The ICE module connects to the target system by multi-way umbilical cable terminated with a plug which is inserted into the socket where the microprocessor would normally reside. In this way the resources of the development system are extended to the prototype in order to facilitate the hardware/software integration. Figure 2 shows a typical microprocessor development system with ICE. Resource allocation is extremely flexible in all modes of operation and will depend to some extent on the state of development of the prototype hardware. The development system mass storage medium, usually floppy disc, is used to store the target system software in both source and object form. Loading is quick and errors can be patched out in the object code to try modifications. These changes can then be incorporated in the source code and rapidly reassembled. Random access memory and i/o facilities of the development system can be used as though they are local memory and i/o of the prototype system even before this part of the hardware is built.

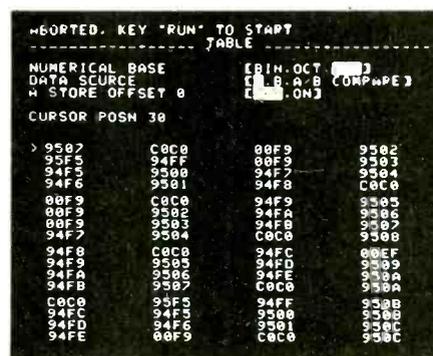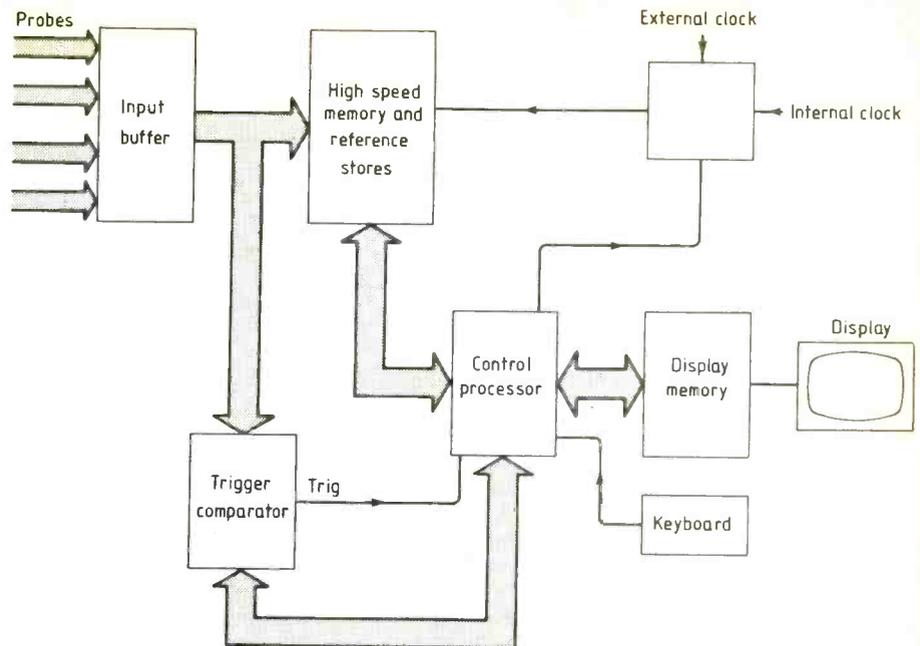


(a)

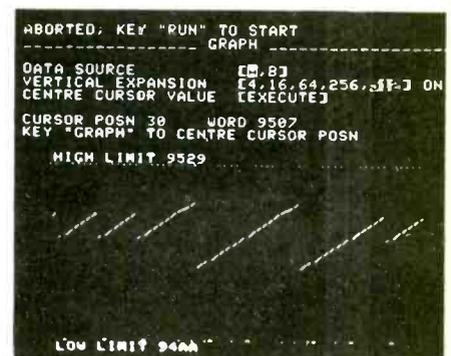

(b)

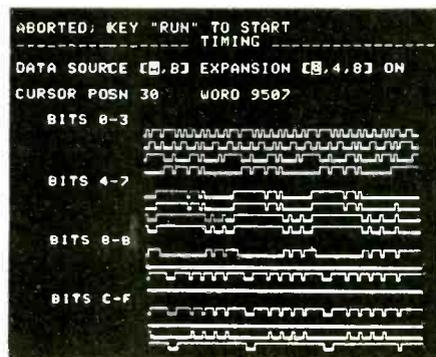

(c)

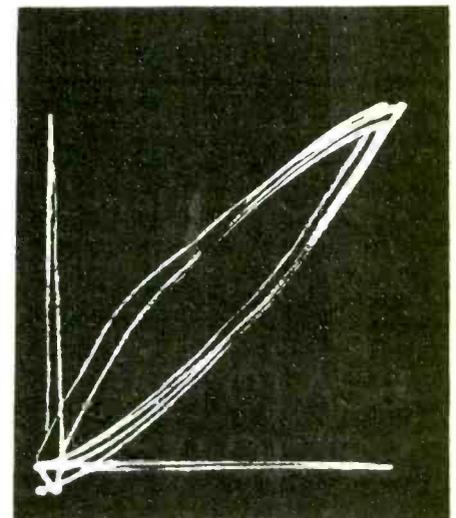

(d)

Fig. 1. Block diagram of a logic analyser. Its various modes of display are: a. a table; b. a timing chart; c. a graph; and d. a map (see text).

During emulation a breakpoint can be specified which can be conditional on a number of different factors such as memory read, memory write, instruction fetch or i/o operation at selected addresses. When the breakpoint has been encountered the internal registers of the processor and any memory locations can be interrogated and modified as necessary before re-starting emulation. It is also possible to display the contents of the trace memory to check the instruction sequence before the breakpoint.

Another possible mode of operation is single stepping. In this way more detailed

information can be acquired by the trace memory as the program is executed one instruction at a time.

Probably the most important advantage of ICE is the simple connection into the prototype system. One cable is all that is required with no need for circuit modifications or temporary jumpers. Early development and debugging of the software enables completion of the total system integration in the shortest possible timescale. Finally, the time consuming procedure of using eproms to transfer programs under development to the target system is eliminated.

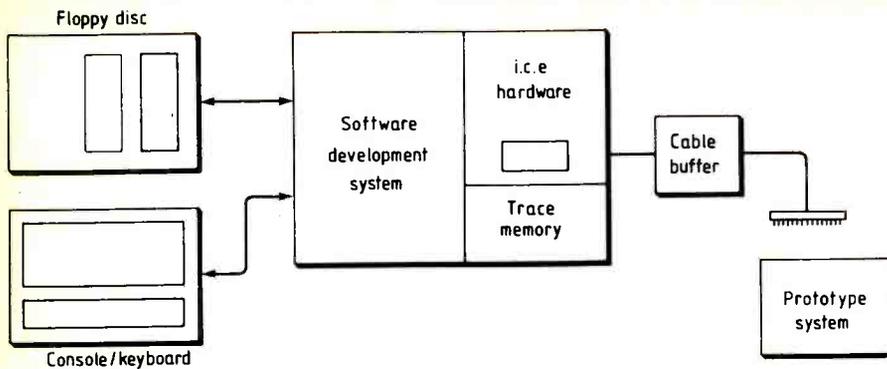


Fig. 2. In-circuit emulation system.

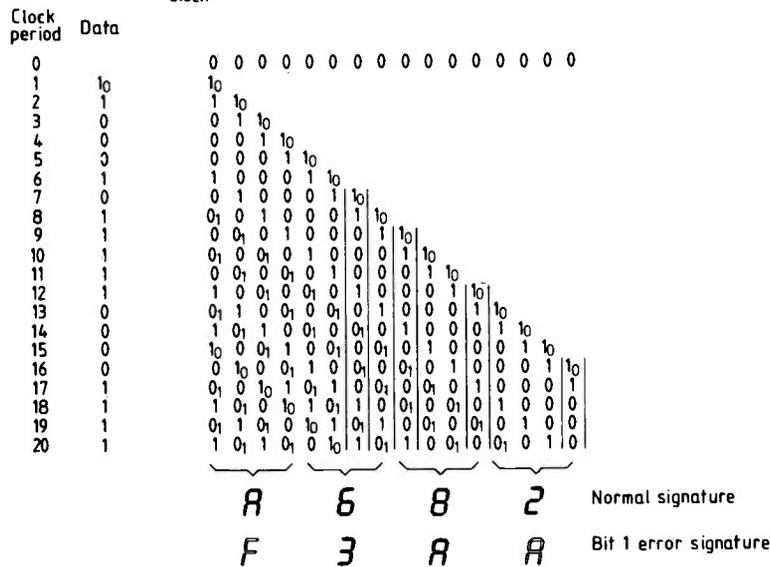
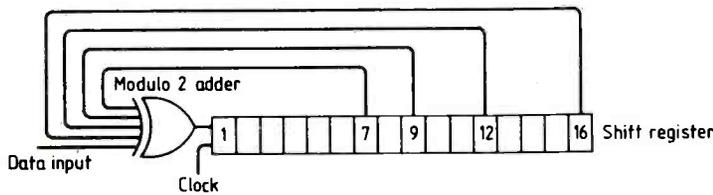
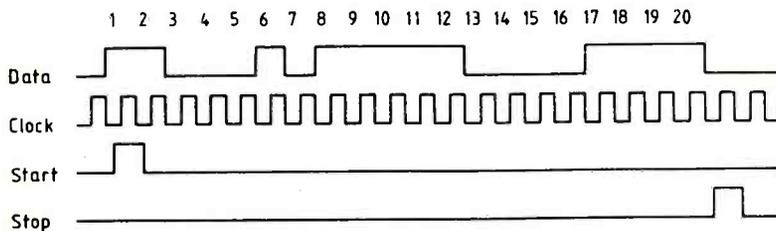


Fig. 3. Derivation of signature from data stream.

Signature analysis

If a piece of equipment is made to repetitively execute a certain sequence of instructions then it should be possible to identify correct operation by monitoring the changing logic levels at each node in the circuit. This would produce a mass of information which would be completely un-manageable in a test situation. In order to compress this information into a more useful form a technique known as signature analysis was developed by Hewlett Packard Ltd. The data appearing at a given node is sampled for a known period, between start and stop signals, by clocking it with the system clock into a feedback shift register. The residue at the end of the sampling period is a characteristic of the activity at that node.

Using a 16-bit shift register and arranging the feedback such that a maximal length sequence is produced will give 65 536 possible residual states. The parallel 16-bit output from the register is used to drive four hexadecimal displays and the resulting number is termed the 'signature' of that node. Errors in the data stream will normally cause a different signature to be displayed. It is possible to show¹ that all single bit errors will change the signature and that the probability of multiple bit errors being missed is less than 0.002%. This is far better than the performance of other techniques such as bit or transition counting.

An example of how a signature is derived is shown in Fig. 3. The data signal is gated with the four feedback bits in a gate

which produces a logic one output only when the modulo two sum of the inputs is one. The clock is enabled during the window between the start and stop pulses and in this case samples the data 20 times. The chart shows how the bits propagate through the shift register and the resulting signature is A682. Superimposed on the chart is the result of introducing a single bit error in the first bit. The signature changes to F3AA. In a similar way it could be shown that the signature would be 8E92 for an error in bit 8 and 2682 for an error in the last bit. Thus it can be seen that a single bit error even in such a short sequence will produce quite a dramatic change in the readout from the signature analyser. In a practical situation the window period would be considerably more than 20 clock periods and can be more than 2^{16} (the cycle length of the register) if appropriate.

Signatures for a given circuit are not designed or calculated. What must be decided at the design stage is how start and stop signals can be produced and what hierarchy of tests is required to fully validate each node. This may involve the use of special test sockets to break feedback loops and isolate parts of the circuit under test. Finally, when the design is complete, the test routines are executed and the signatures at each node in the equipment are recorded. Documentation is completed by adding the signatures to the circuit diagram an example of which is shown in Fig. 4. The handbook should detail the sequence of tests and fixtures, switches or jumpers that are required.

After proving the operation of the system kernel a series of tests are run which successively introduce a larger percentage of the system until a signature fault is found. Faulty components can be located by backtracking until a device with a correct input signature but erroneous output signature is found.

Signature analysis is a very powerful service aid and is also useful for final assembly testing. The equipment is relatively inexpensive and the extra design work is minimal. Retrospective design into existing systems is also an attractive proposition.

Automatic test equipment (ATE)

This is the name given to usually large equipment sets which allow the user to test, thoroughly and quickly, complex circuit boards. They represent a considerable capital investment and are essentially fixed. Usually they can be justified only in a production situation with a high throughput although sometimes there is a case for them in a repair and maintenance department.

A typical ATE system is shown diagrammatically in Fig. 5. User communication with the system is via the console keyboard and v.d.u. Test routines are stored either on floppy or rigid discs. The processor controls setting up and running of the tests. It communicates with the unit under test (u.u.t) via the digital control unit and the high speed read/write memory. Connection to the u.u.t is made in a number of ways including via its edge

connector, through a bed of nails fixture and through test clips and probes.

The usual test procedure involves the stimulation of the input nodes of the u.u.t with data in the form of arrays of sequential test patterns. The u.u.t is clocked at its normal operating speed and response data at all outputs and internal nodes is captured in the memory for comparison with the correct response pattern. Input sequences up to 4000 bits long are used and the output comparison is done either on a bit for bit basis or the response data is compressed into a signature for each node and then compared with stored signatures.

The input test patterns are usually algorithmically generated by the test procedure in order to simulate some functional response. Another possibility is to use pseudo-random binary sequences as input data providing a more exhaustive though lengthy test. The correct response patterns are assessed either by emulation or heuristically. In the first case it is necessary for the ATE to have detailed circuit information of the u.u.t and also to store a library of device models so that the correct response can be calculated. Functional models of complex l.s.i devices such as microprocessors are therefore required. In the second case a known good unit is monitored through all the tests and the correct

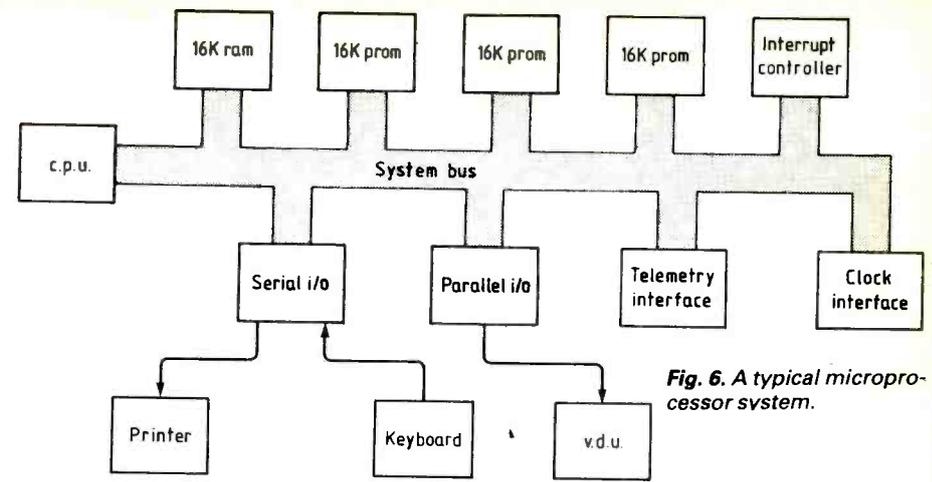


Fig. 6. A typical microprocessor system.

responses are learnt and stored for later use.

The result of this initial testing is that the unit is either good or faulty, and in the latter case there is no information concerning the possible fault location. A second series of diagnostic tests then has to be executed and these will involve the operator following a set of simple instructions displayed on the v.d.u. The operator is guided through the circuitry applying either current or voltage probes until a faulty component is found. A label is then

printed which can be attached to the unit for return to assembly.

Thus an ATE system is very comprehensive in its ability to fault find large numbers of different circuits by having different bed of nails configurations and storing its programs and responses on disc.

It does suffer from the drawback that, although the operator requires little skill or training, it is necessary to program the system in some considerable detail for each new board. Special high level languages have been developed to make programming easier, but there is no standard, and usually a skilled ATE programmer is required.


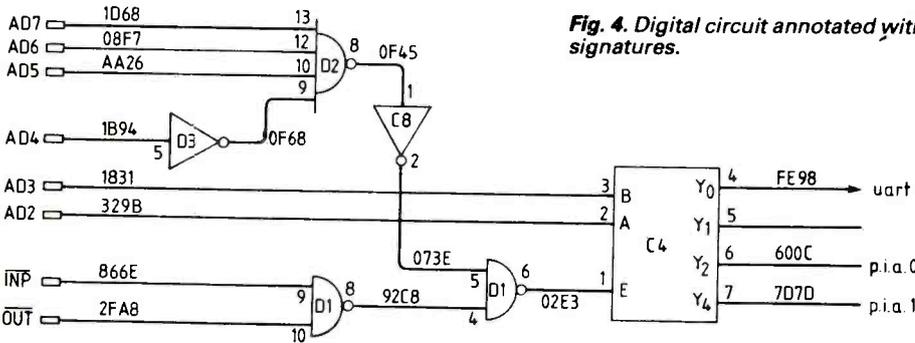


Fig. 4. Digital circuit annotated with signatures.

Fig. 5. An automatic test equipment layout.

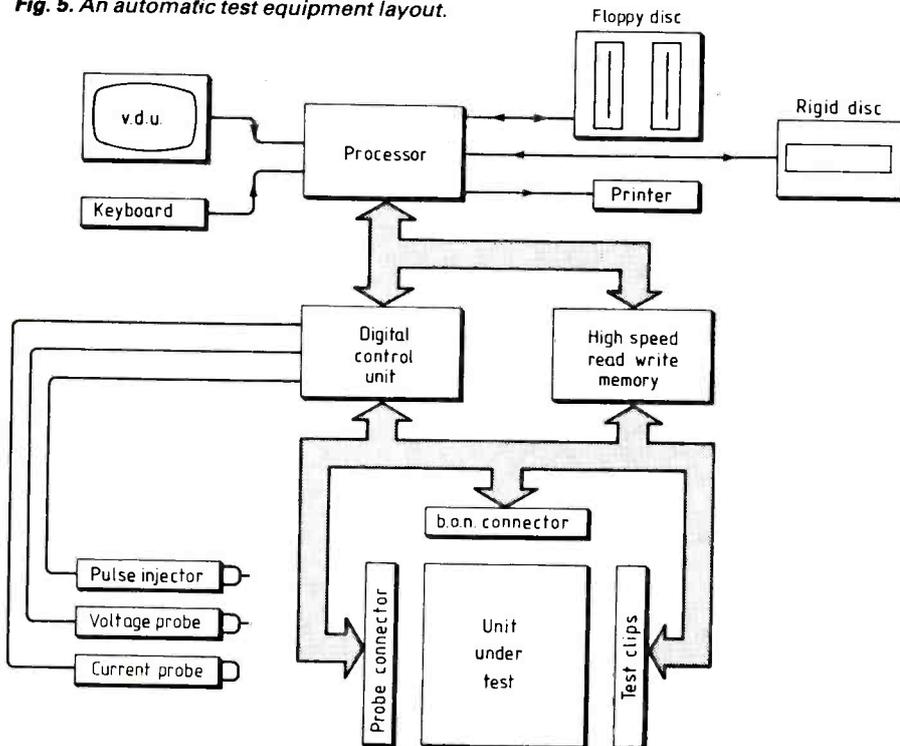

Portable diagnostic test sets

A diagnostic tester designed to fault-find and validate a specific microprocessor system can sometimes prove to be a cost effective solution to provision of field service maintenance equipment. It is portable and versatile and is used to perform automatic functional tests on the equipment within its normal operating environment.

A typical microprocessor system is shown in Fig. 6. It comprises 10 printed circuit cards with connection to various peripherals. The tester has access to the system bus and the i/o sockets. One convenient form of implementation is therefore an extra circuit card which plugs into a spare socket in the system rack and connects to a hand held controller with an alphanumeric display. The components necessary for such a test set are shown in Fig. 7.

The test programs are stored in prom on the test card and the small ram is used as stack, display buffer and workspace, so that the main system ram need not be operational. The u.s.a.r.t with its clock divider chain producing clock rates for 110 and 1200 baud is used to test the serial links. One p.i.a controls the display and reads the keypad and the other is used to test the interrupt system and the parallel i/o. The most convenient address at which to locate the test routine will normally be zero so that system reset will initiate the test sequence. It will probably therefore be necessary to have a switch on the main system which will disable memory at overlapping addresses while the test routines are executing.

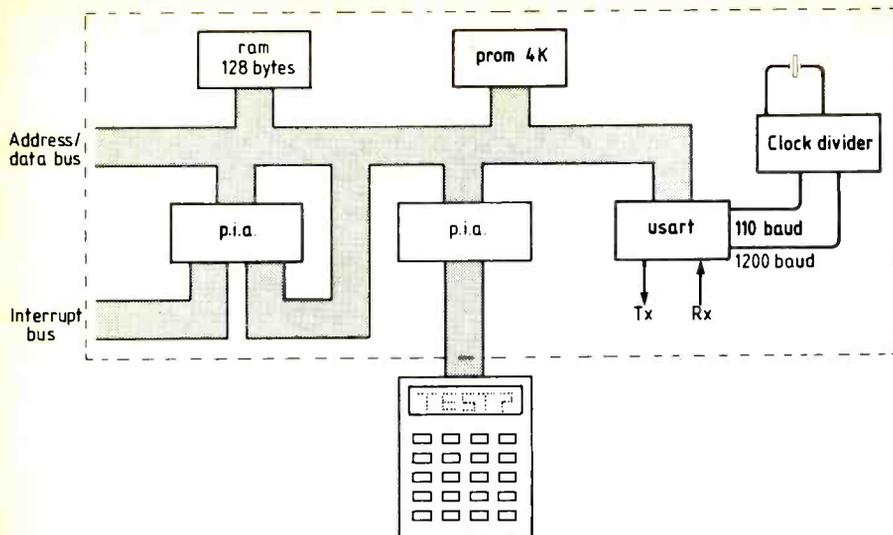


Fig. 7. A test set consisting of a p.c.b. and a control module.

Fault finding follows a logical sequence of building up confidence in the operation of the system components. The c.p.u of the main system is used as the processor to execute the tests. The address and data busses and the c.p.u are confirmed as operational if the tester initialises correctly. Memory tests consist of write-read pattern checks on ram and checksum test on prom. The serial inputs are tested by lopping to the tester serial output. The serial outputs are looped to the tester serial input and known data sequences can be sent out to assist with fault finding at the peripherals. The tester displays diagnostics for each test to indicate success or mode of failure. In the case of proms and

rams the actual faulty chip can be indicated. The fault, when located, can be rectified by changing a circuit card; or a series of lower level test can be executed in order to fault-find down to component level with the aid of scope and logic analyser.

In many systems validation routines are an integral part of the software and are run at initialisation. However, they cannot perform such comprehensive tests as this type of portable test set with interaction of a maintenance engineer. The operation of the tester is straightforward and requires minimum documentation. It is also readily acceptable as part of the maintenance engineer's kit.

Conclusions

Several techniques have been discussed in this paper which make fault analysis in the data domain a practical proposition. In a design and development laboratory, use is made of logic analysers and microprocessor development systems with in circuit emulation. In production and field maintenance the choice is less straightforward. ATE for assembly use appears to be the best technique for thorough testing but is costly both in initial equipment and in programming. Equipment for service use can be selected only when a maintenance philosophy has been evolved depending on the type of equipment, numbers in service, ability and availability of field personnel, acceptable down time etc.

Future developments will see the introduction of 32 and 64 bit microprocessor systems which will require even more sophisticated techniques for fault finding. Designs will become fault tolerant by the introduction of both chip and peripheral hardware redundancy. In the field there will be greater use of remote fault analysis. Faulty systems will be connected by telephone lines to central installations, the test routines being down loaded and results fed back for analysis.

There will therefore be a continuing trend towards improved system reliability by increasing MTBF and minimising down time on the occurrence of a fault.

WV

References

1. Frohwerk, R. A. 'Signature analysis: a new digital field service method'. HP Journal, May 1977.

Reprinted from *IBA Technical Review*, No. 15, 1981.

BOOKS

Regulated Power Supplies, (3rd ed.),

by I. M. Gottlieb

423 pp., paperback

Prentice-Hall International, £13.95. ISBN 0-672-21808-9

AN expansion of the earlier works, dealing in an extremely thorough manner with a subject which is not often treated in isolation. Practice, rather than theory is the approach, from a description of basic requirements to the implementation of linear and switching-type voltage and current regulators. The author not only provides an exceptionally detailed treatment of the subject, but does it in a literate manner.

Computing

Mastering Computer Programming

by P. E. Gosling

212 pages, hardback/paperback

MacMillan £8.95/£2.95

The title of this book is one result of its forming part of the Master series, but the author lays no claim to omnipotence. He has produced a very 'accessible' description of the processes involved in writing programs, with a useful chapter on

errors and a piece on Fortran, Cobol and Pascal - Basic is used in the body of the book. The writing is direct and easy to read.

Microprocessor Development and Development Systems

Edited by Vincent Tseng

202 pages, hardback

Granada, £16.00

In the development of most applications using microprocessors, a 'development system' to aid programming and testing is of great benefit. The book, written by several authorities in the field, describes a number of such systems and their use and includes a chapter on emulators. There is also a section on managing without a d.s. The style is descriptive and 'readable'.

Microcomputer Design and Troubleshooting

by Eugene M. Zumchak

350 pages, paperback

Prentice-Hall, £12.55

A rather more down to earth treatment of the practicalities of design with micros than is usually found at this level. A home-built development system is described and further chapter headings include read/write timing, interfacing, hardware testing and software design.

Circuit Design Programs for the Apple II

by Howard M. Berlin

132 pages, plastic bound.

Prentice-Hall, £11.15

One of the Blacksburg series, this is a set of Basic programs intended to take the labour out of circuit design calculations, graph plotting and signal analysis, including average and r.m.s. values and Fourier series. Equipment needed to use the programs is either an Apple II Plus or Apple II with Applesoft card. A minimum of 32K ram is required, 48K being preferable.

Amateur radio

Amateur Radio Equipment Fundamentals

by A. D. Helpick, K2BLA

248 pp., hardback

Prentice-Hall International, £14.20. ISBN 0-13-023655-1

The tradition of home-built amateur radio equipment has largely given way to the operation of commercial gear. In an attempt to offset this trend, Mr Helpick has provided a course of instructions in the basics of design and construction of transmitting and receiving equipment, and has included two chapters of designs for receivers, transmitters and a 100W linear amplifier.

ELECTRONIC COMPASS USING A FLUXGATE SENSOR

A device to fill the gap between the old-fashioned compass and expensive gyro-based navigation systems – an all-solid-state, high-resolution magnetic sensor.

With the ready availability of micro-computers, simple dead reckoning navigation systems for boats and cars can be constructed, if suitable distance and direction inputs are available. A 'distance-travelled' signal can usually be obtained quite easily, but the provision of a digital magnetic heading is more difficult. It would be possible to arrange a servo pointer follower and angle digitizer attachment for a conventional moving magnet compass, but this would be mechanically complex and unattractive for amateur construction. An inherently digital solid-state compass is a much more elegant solution. A compass of this type would be valuable in any application where multiple output displays are needed, a computer readable output is required or where the sensor will be subject to high vibration or accelerations. In addition, the electronic nature of the sensor permits its location far from large metallic masses which can locally distort the field.

All solid-state compasses operate by sensing two or three resolutives of the horizontal component of the earth's magnetic field and then perform appropriate trigonometry with these resolutives to obtain the resultant magnetic flux direction. Using Hall-effect sensors, it is possible to produce very simple arrangements¹. Unfortunately, during preliminary testing none of the low-cost, commercially available Hall-effect probes, including those with integral ferrite flux-concentrators, were found to have sufficient accuracy at magnetic field levels appropriate for compasses. Even when extra flux-concentrators formed by 2cm long Mumetal strips attached to each side of the sensor were added, increasing their output from microvolt to millivolt levels, the temperature drifts were of similar magnitude to the output produced by the earth's field. The disappointing results obtained with Hall-effect sensors forced the adoption of a fluxgate sensor with its inherently greater circuit complexity.

The theory of fluxgate magnetometers and compasses is beyond the scope of this paper and interested readers are referred to References 2 and 3. For a brief description of the principle of operation, see box.

An initial prototype of a fluxgate sensor used magnetic cores cut from Mumetal sheet, but an inconvenient post-fabrication annealing operation in a hydrogen atmosphere was required to obtain the desired magnetic properties. To overcome this dif-

by Neil Pollock

ficulty, attention was directed to magnetometer designs which could be constructed using readily available commercial ferrite components.

Circuit

The arrangement finally chosen (based on a design intended for sounding rockets⁴), uses a 14mm diameter Philips ferrite toroid type number 4322-020-97140 (grey coating) or the equivalent uncoated toroid 4322-020-31390. Notes on adapting the design to use other toroid types are included later.

The circuit diagram and coil winding details are shown in Figs 2 and 3. The toroid is driven into saturation in alternate directions at about 10kHz by a magnetic multivibrator circuit of the type often used in inverters.

Windings P₁ and P₂ are the drive primaries while P₃ and P₄ provide the necessary

feedback to maintain oscillation. The two secondary coils S_x and S_y are arranged so that in the absence of an applied external magnetic field they, at least in theory, experience no induced voltage. In practice, due to imperfections in the toroid and coils, voltage spikes are induced in the secondaries as the toroid goes into and out of saturation. These spikes have amplitudes varying from barely detectable to over one volt for different coil assemblies (Fig. 4).

When an external field is applied in the plane of the toroid some initial magnetization is induced in it. This initial magnetization results in one part of the toroid being driven into saturation before the part 180° away from it during one half of the oscillator cycle and the reverse situation occurring during the other half cycle. This non-symmetrical saturation of the core produces a flux unbalance and an induced voltage in the secondary windings. The magnitude of this induced voltage is closely proportional to the applied flux

Fluxgate magnetometers

There are very few means of measuring absolute values of magnetic fields. The most popular one is the Hall effect sensor, but most commercial units are designed for relatively high values of field.

The fluxgate configuration can measure very low field magnitudes by using the chopper-amplifier principle. Briefly, it is based on the fact that all parts of a uniformly excited toroidal magnetic circuit would be equally magnetized in the absence of external magnetic fields and therefore no voltage would be induced into a coil encompassing the whole magnetic circuit.

The introduction of external field in the plane of the toroid would result in a slight unbalance between the two halves of the magnetic circuit (see Fig. 1).

The flux at point A equals $\phi_A = \phi_0 + \phi$, whereas point B, situated 180° away would correspond to a flux $\phi_B = \phi_0 - \phi$. Where ϕ_0 is due to local toroid excitation and ϕ , to the external field.

Although the unbalance is very slight, it can be measured through one of its side effects: If we cyclically change the local excitation so as to switch the toroid between its two magnetic saturation points, we find that due to the unbalance, one half would be driven

into saturation a short time before the opposite half and the toroid as a whole would, for a short period of time act as a small magnet. The net result is that a coil encompassing the complete magnetic circuit would pick up an induced voltage impulse, proportional to the external field.

By mounting two such coils perpendicularly to each other onto the same toroid, we can resolve any external field into its X and Y components in the toroid plane.

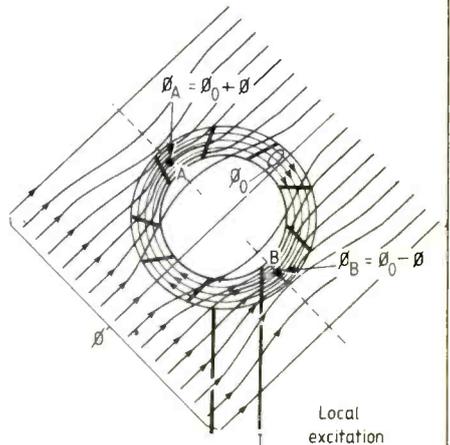


Fig. 1. Flux interference pattern.

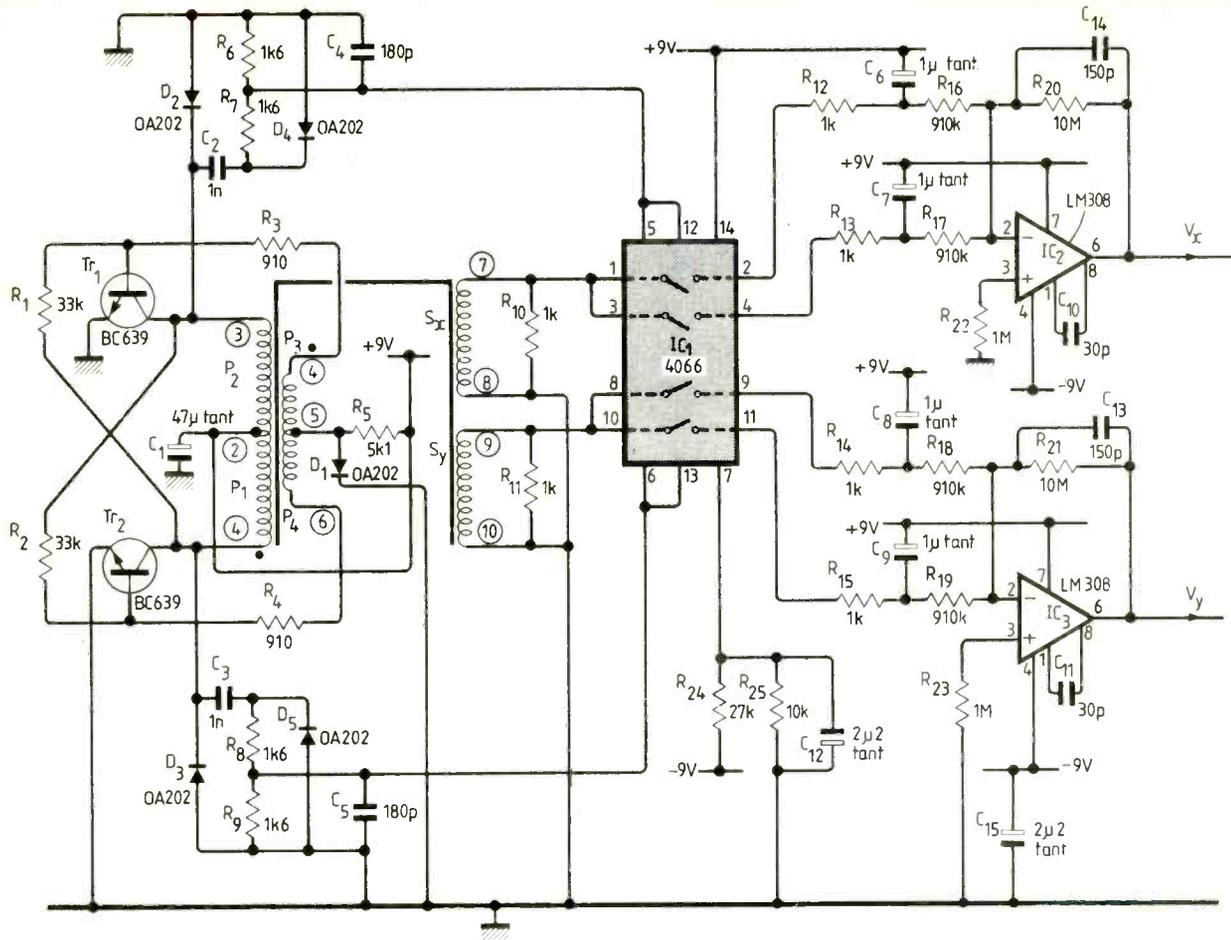


Fig. 2. Fluxgate sensor circuit diagram.

component perpendicular to the plane of the appropriate secondary coil. In practice, the effect of applying an external field is to change the amplitude of the pre-existing secondary voltage spikes. The amplitude of these spikes is also quite strongly temperature dependent. Figure 5 illustrates how the effect of an applied field is separated from the effect of temperature.

To perform the necessary arithmetic on spike amplitudes, a phase sensitive detector and summing amplifier is used for each secondary. The detector control signals (Fig. 6) are generated by differentiating, half wave rectifying and attenuating the primary drive voltages. The phase detector outputs are summed and the resulting

mean voltages (outputs V_x and V_y) are proportional to the sine and cosine of the angle between the applied field and the plane of the S_x coil. In principle the compass output is simply the arctangent of the output voltage ratio. It is essential that the coil assembly and the associated electronics be located on the same circuit board because the zero offset is very sensitive to the relationship between the wires connecting the coil to the electronics.

Construction details

The coils are the heart of the device and, although they are relatively non-critical, an effort applied to winding them carefully and neatly will be well repaid. The primary drive windings P_1 and P_2 are wound on the toroid first and fill it about $1\frac{1}{2}$ layers deep. These two coils are bifilar wound, that is they are wound with two wires side by side to produce two closely identical windings. The feedback windings P_3 and P_4 are bifilar wound on top of P_1 and P_2 . The two secondary windings can either be wound on a tubular former with notches at 90° intervals, which fits around the pre-wound toroid (Fig. 7) or wound separately and then glued in place. If the latter method is adopted it is suggested that each secondary be wound around a 6mm by 16.5mm rectangle formed by four pins. On removal of the pins the preformed rectangular coil should be bound with another piece of coil wire (taking care not to create a shorted turn) so that it is bundled together. The two secondaries can then be


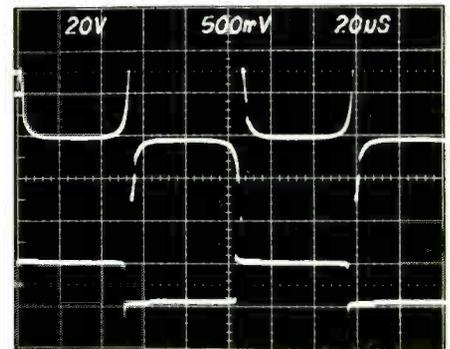


Fig. 4. Primary drive voltage (lower trace) and resulting secondary (S_x) voltage spikes (upper trace).

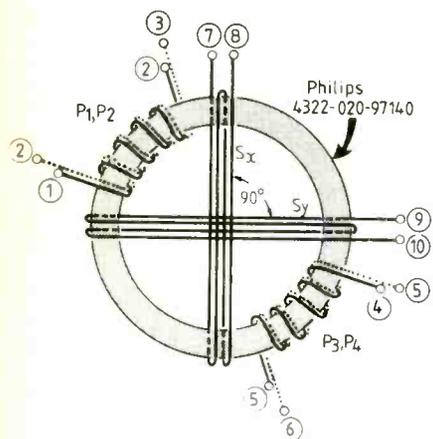

P_1, P_2 - 2×50 turns 30 Swg enamelled cu. wire
 P_3, P_4 - 2×10 " 30 " " " " "
 S_x, S_y - 100 " 40 " " " " "

Fig. 3. Toroid windings.

placed around the toroid and secured with quick-setting epoxy glue. However the secondaries are wound, it is essential that they are a neat fit and closely coupled to the toroid. On completion of the windings the toroid assembly should be glued to the circuit board and the leads connected, being careful to observe the correct hand of the P_1, P_2, P_3 and P_4 windings. All windings should be securely glued to prevent any relative movement between them.

The remainder of the circuit is straightforward and a board layout and component positions are reproduced in Figs. 8 and 9. The use of metal-can transistors and integrated circuits should be avoided, since they could distort the applied magnetic field.

If it is desired to use a toroid other than the one specified, the following procedure

is recommended. If necessary, change the number of turns on the primary windings, keeping the same ratio between drive and feedback windings, so that the operating frequency is in the range 5kHz to 50kHz. Change the value of C_2 and C_3 so that the phase sensitive detector control pulses are similar in length to the secondary spikes. Alter the value of R_{20} and R_{21} to obtain the desired overall sensitivity. Although they have not been tried, their specifications suggest that the following toroids could be used with only minor component value changes: Philips 4322-020-97060 (blue coating); Philips 4322-020-31390 (uncoated); Siemens B64290-K0045-X026 (coated); Siemens B64290-A0045-X026 (uncoated).

Performance

To facilitate calibration, the sensor board should be taped to a 360° plastic protractor which can be rotated inside a circle drawn on a piece of paper placed on a wooden table top. Care must be taken not to move any ferrous or magnetic objects near the compass sensor during calibration. The author experienced inconsistent results which were eventually traced to the effect of his metal belt buckle. A typical calibration chart is shown in Fig. 10. The V_x and V_y outputs are usually within $\pm 1^\circ$ of best fit sine curves with zero offsets in the range ± 2 volts. A peak-to-peak amplitude of about 1.2volts was produced by a horizontal flux density of 2.2×10^{-5} tesla (weber/m² - the value for Melbourne, Australia). Similar outputs should be obtained

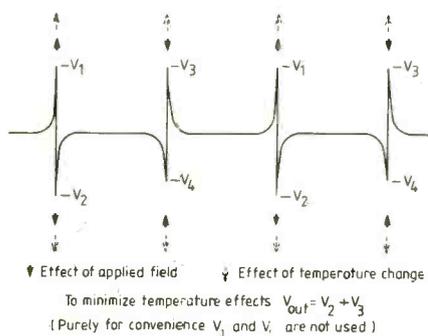


Fig. 5. Effects of temperature versus applied magnetic field on secondary waveform.

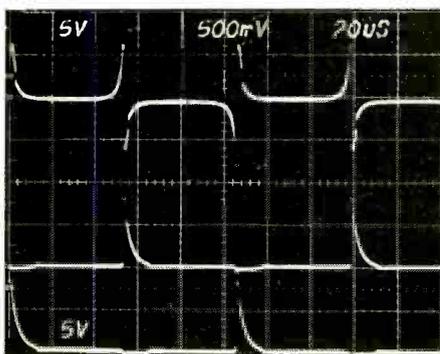


Fig. 6. Secondary output (S_x - IC1, pin 1 - upper trace) and phase sensitive detector's control signals: middle trace: IC1, pin 5. lower trace: IC1, pin 6

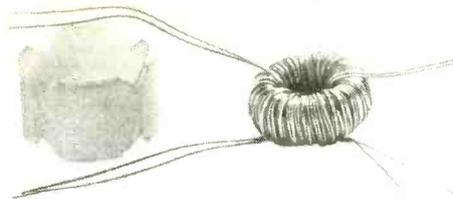


Fig. 7. Toroid with primary windings and former for secondaries.

in Europe and the USA. In other parts of the world the horizontal flux density varies from zero at the magnetic poles to 4.13×10^{-5} tesla in the Bay of Bengal. If the sensor is not horizontal, total flux densities exceeding 6×10^{-5} tesla may be found. The sensor peak-to-peak output voltages are directly proportional to the field strength in the plane of the toroid. For carefully wound coils the phase angle between the two output voltages will be within a few degrees of the desired 90°. It is suggested that any departure from 90° is treated as a correction in the angle computation, but if desired the coils can be bent by trial and error prior to final glueing to produce the desired angle between them.

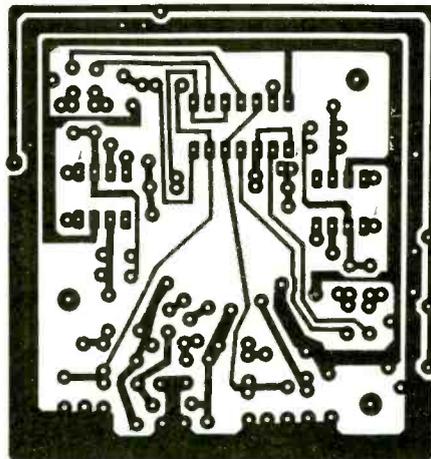


Fig. 8. Fluxgate sensor p.c.b. layout.

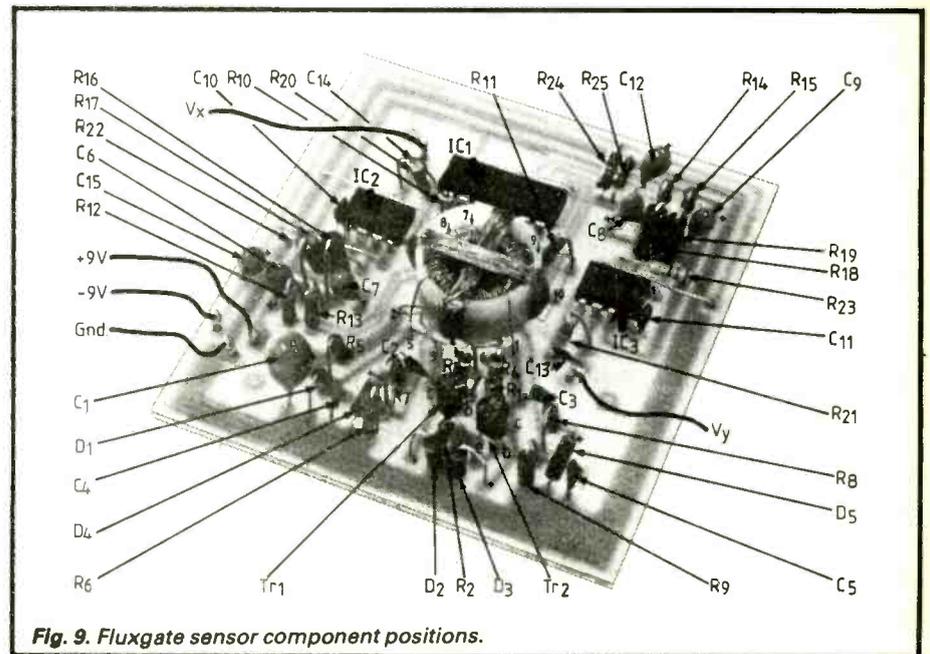


Fig. 9. Fluxgate sensor component positions.

The sensitivity of the sensor is quite strongly temperature dependent (about 5% per °C) but since both outputs are affected equally the indicated angle is unchanged. The zero offsets vary by about 10mV/°C and for operation in environments which are not temperature controlled, these changes would have to be corrected for, if maximum accuracy was required. The repeatability of the sensor calibration is excellent with no measurable change over a one month test period, and presumably for much longer periods since there is no obvious mechanism for long term drifts. The sensor is very sensitive to temperature gradients in the ferrite core and it is essential that it be protected from draughts. The sensor board draws 17mA from the +9volt supply and 2mA from the -9volt supply.

Installation

The sensor must be mounted in a horizontal attitude if accurate results are to be obtained. In a boat, where large attitude changes are often experienced, the sensor would have to be mounted on a set of gimbals. In a land vehicle subject to large accelerations but normally operating on an approximately level surface, it may be better to rigidly mount the sensor. If mounted near large ferrous objects or sources of magnetism, the sensor must be compensated as for a normal compass³. Fortunately with the freedom to remotely mount the sensor it is often possible to find a location where compensation is not required and the small residual errors can be treated as part of the calibration. If very long connecting leads are to be used between the sensor board and readout electronics, it may be necessary to include 1kΩ resistors in series with the V_x and V_y outputs to decouple the operational amplifiers from the cable capacitance.

Microprocessor readout system

In a microprocessor-based system the sensor outputs V_x and V_y would be multiplexed into an analog-to-digital

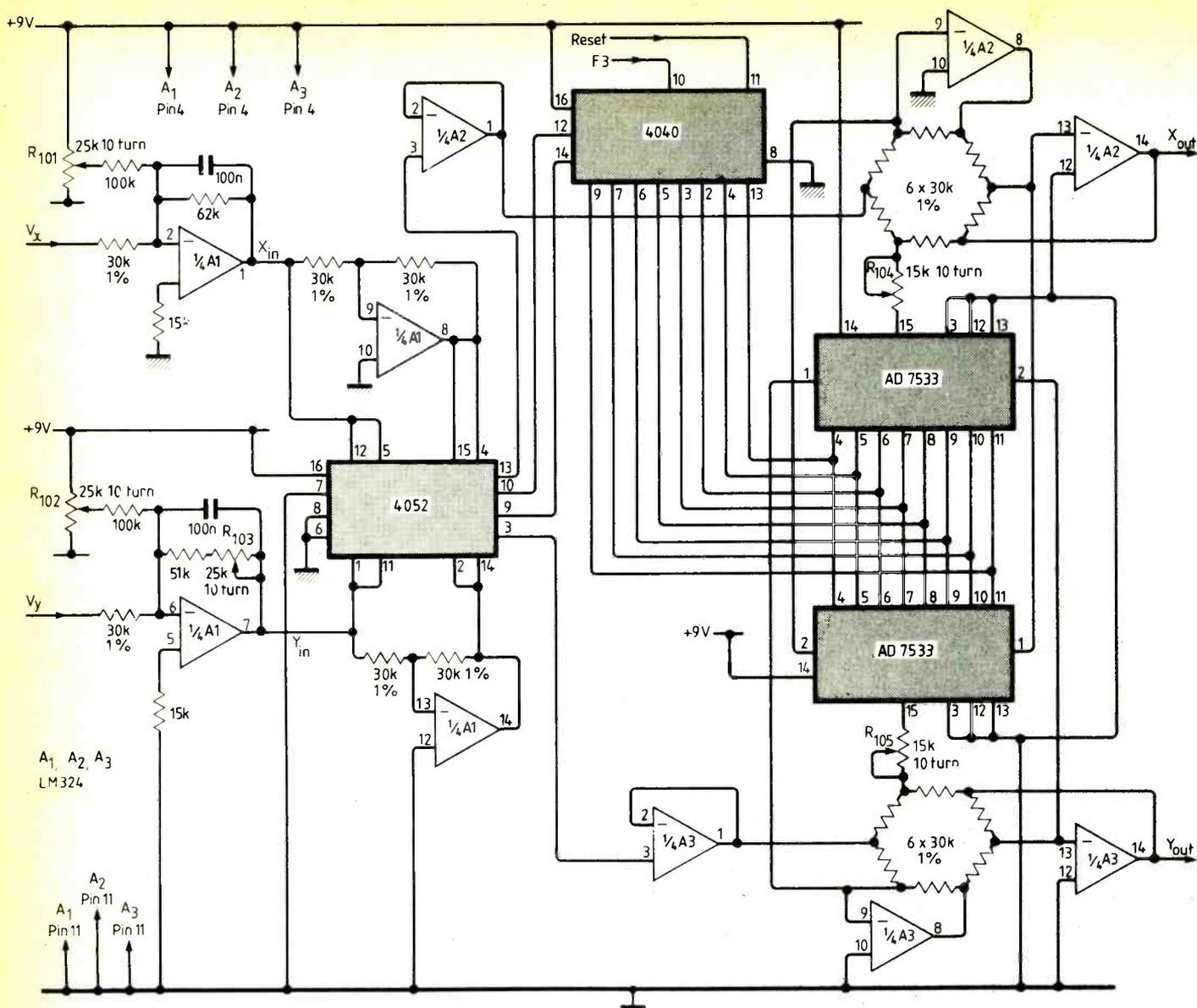


Fig. 12. Angle decoder: input circuitry and vector rotator.

dedicated hard wired readout system. A relatively simple, low cost, arrangement which was used during the development of the sensor is shown in block diagram form in Fig. 11. The operation of this system depends primarily on a vector rotator

which has as inputs two analogue voltages X_{in} and Y_{in} which are taken as the X and Y components of an input vector and a digital angle θ (0 to 1024 for 0 to 360°). The outputs X_{out} and Y_{out} are the X and Y components of the input vector rotated through the angle θ . The heading angle is given by the value of θ which reduces the X output to zero (ie. the angle through

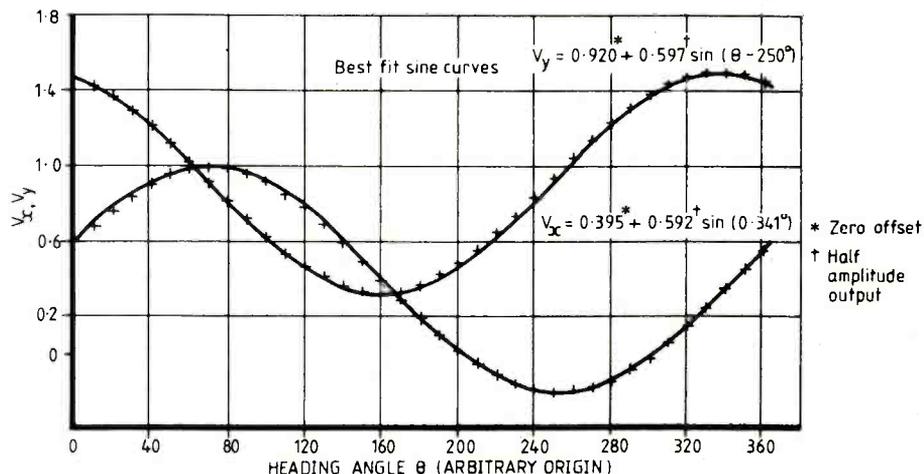


Fig. 10. Typical calibration chart.

converter with a useful resolution of at least 10 bits. An a. to d. converter like the Intersil ICL7109 would be the first choice in this application since it could be simply interfaced to most microprocessors using parallel or serial data transfer. When the digital values of V_x and V_y were read in, the ratio $R = (V_x - V_{x0}) / (V_y - V_{y0})$ should be calculated, where V_{x0} and V_{y0} are the zero offsets which should be varied with the measured sensor temperature unless it is placed in a temperature-controlled enclosure. Using the value of R and the signs of $V_x - V_{x0}$ and $V_y - V_{y0}$ it would be possible to construct a look up table to give the heading angle with 1° resolution. The actual sensor will resolve heading changes of much less than 1° but when all sources of error are considered there is little point in aiming for greater overall resolution. Alternatively, if a dedicated arithmetic chip like the National Semiconductor MM57109 was available, it may be more efficient to take the arctangent of R and apply any necessary corrections to the computed heading later.

Hard-wired logic readout

In applications where a microprocessor is not available, it may be desired to have a

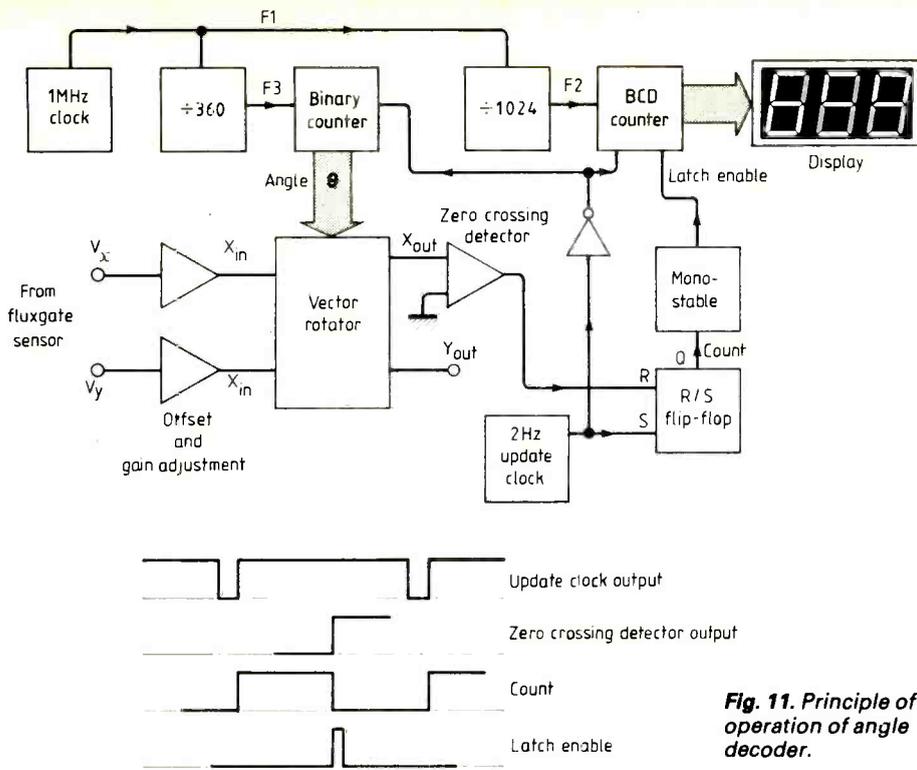


Fig. 11. Principle of operation of angle decoder.


which the input vector must be rotated, to align it with the system Y axis).

When a reading is initiated by the 2Hz update clock, the binary and b.c.d. counters start counting from zero. When X_{out} passes through zero in a negative going direction, a latch enable pulse is generated which gates the current b.c.d. counter contents into the display. The RS flip-flop is needed to ensure that only the first zero-crossing in each update clock cycle produces a latch-enable pulse. The 360/1024 ratio between F_2 and F_3 produces an output in degrees. Outputs in other units, eg. tenths of degrees or grads, could be produced simply by changing this ratio. For this system to work correctly, the X_{in} and Y_{in} inputs must have the same sensitivity and no offsets; this is achieved with a pair of offset and gain adjustment amplifiers.

The circuit which is designed around a simple vector rotator⁵, using a pair of Analog Devices AD7533 low-cost multiplying digital to analog converters, is presented in Figs. 12 and 13. This circuit, which has an overall decoding accuracy of about $\pm 1^\circ$, draws 15mA from the +9volt supply, 7mA from the -9volt supply and 170mA from the +5volt display supply.

The set up procedure, which consists of adjusting offsets, sensitivities and balance is as follows: with the sensor board not connected, adjust R_{101} and R_{102} to set $X_{in} = 5$ volts and $Y_{in} = 0$. Remove the 4040

Fig. 13. Angle decoder: control logic and display.

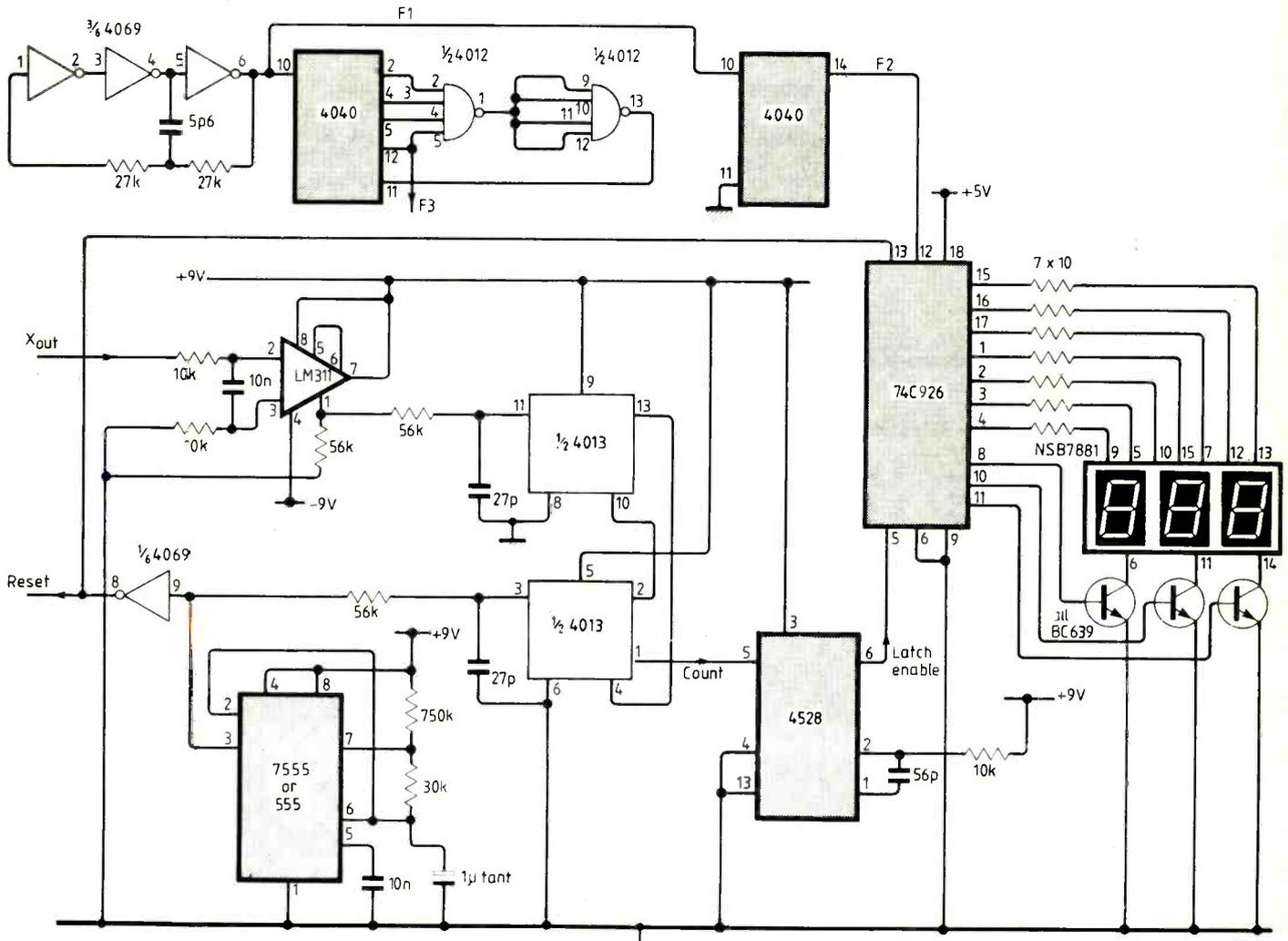

counter and ground its socket's pins 2-7, 9 and 12-14. Adjust R_{104} and R_{105} to set $X_{out} = -Y_{out} = 5/\sqrt{2} = 3.54$ volts. Readjust R_{101} and R_{102} to obtain $X_{in} = 0$ and $Y_{in} = 5$ volt. Check that $X_{out} \approx Y_{out} \approx 3.54$ volts. This set up procedure for R_{104} and R_{105} is sufficiently accurate for most applications, but if maximum accuracy is needed an iterative procedure⁴ should be adopted. Replace the 4040 and connect the sensor board. While rotating the sensor board through 360° set R_{101} to remove the V_x zero offset so $X_{in,max} = -X_{in,min}$. Set R_{102} to remove the V_y zero offset so $Y_{in,max} = -Y_{in,min}$ and finally set R_{103} to equalize X and Y sensitivities so that $X_{in,max} = Y_{in,max}$. Since this circuit was developed primarily for bench testing, no compensation for changes in X and Y zero offsets with temperature is provided. An enthusiastic analog circuit designer could perform this compensation with thermistors in resistor networks around the input amplifiers.

Power supply

Since this system will normally be used in mobile applications, it is desirable that it should operate off a 12volt supply. A regulated power supply suitable for this purpose is shown in Fig. 14. Two alternative methods, (1) or (2) of generating the -9volt supply are shown. The Fairchild $\mu A78S40$ universal switching regulator was used for most of the development of this project. However quite recently the Intersil ICL7660 voltage converter became available and proved to have equal performance in this application with a considerably simpler circuit.

Magnetic compasses and the precautions required for their effective use are complex and it is strongly recommended that potential users read Ref. 3 and thoroughly check the accuracy of their own installation before relying on it in circumstances where life or property might be at risk. **WW**

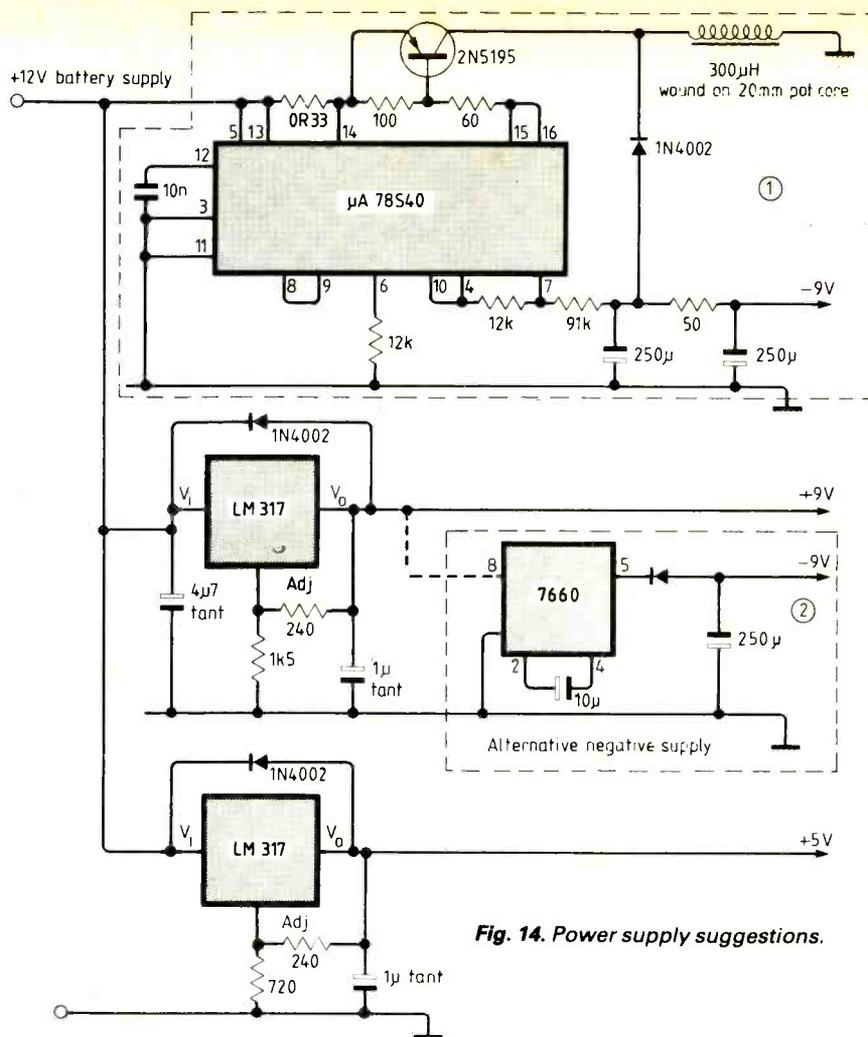


Fig. 14. Power supply suggestions.

References


1. Steinbaugh, G. Hall Compass Points Digitally to Headings. Electronics, Dec. 18, 1980, pp. 112-114
2. Stuart, W. F. Earth's Field Magnetometry. Reports on Progress in Physics, Vol. 35, 1972, pp. 803-881
3. Hine, A. Magnetic Compasses and Magnetometers. Adam Hilger Ltd. London, 1968
4. Acuna, M. H. and Pellerin, C. J. A Miniature Two-Axis Fluxgate Magnetometer. IEEE Transactions on Geoscience Electronics, Vol. GE-7, No. 4, Oct. 1969, pp. 252-260.
5. Mayer, A. Low-Cost Co-ordinate Converter Rotates Vectors Easily. Electronics, Sept. 22, 1981, pp. 133-135

M. G. Scroggie – Fifty-nine years a WW author

There can be very few electronic engineers, from this country or abroad, to whom the nom de plume Cathode Ray is not part of their education. For nearly sixty years Marcus Scroggie has contributed articles on wireless and other manifestations of the mobile electron which have instructed, entertained and humiliated more readers than would probably care to admit to it.

His technique has often been to take a 'simple' circuit and concede that nothing could be easier. The next step in the process, to demonstrate that the apparent simplicity is a snare and a delusion, would possibly have reduced the number of engineers to a dangerous level had he not quickly moved on to show that, if approached in the proper manner, the circuit was unlikely to bite.

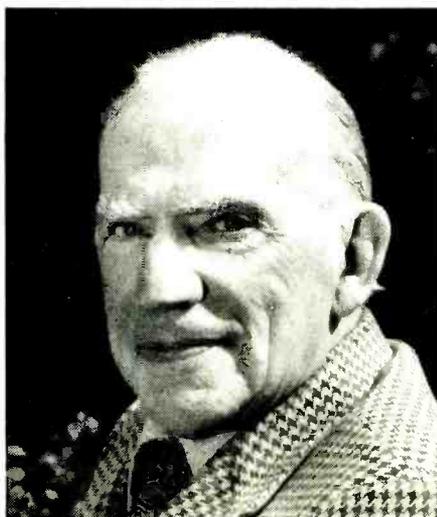M. G. S. is not adverse to an argument, the most notable perhaps being the Affair of the Arrow, his contention being that to



put arrows on both ends of a vector/phasor was akin to not knowing whether the voltage is coming or going. He has also, on occasion, been a touch professorial with those who approach the Queen's English with evil intent. The editorial people in WW have long been terrified of writing 'd.c.' (meaning zero frequency) or phrases such as decoupling to earth' in case M. G. S. saw the piece and fired a broadside.

The first WW article under the name of Marcus Scroggie appeared in the issue for August 15, 1923 – a method of raising 800V for a valve transmitter, M. G. S. being also amateur operator 5JX. But the pieces which have contributed most to the stature of WW since the first article appeared in 1934 are the articles by Cathode Ray, for which tens of thousands of engineers have cause to thank him.

On his 81st birthday, we wish Marcus Scroggie well.

INTRODUCTION TO VDUs

A simple explanation for newcomers to computing of the characteristics of visual display units, their method of working and control, and a description of some integrated-circuit video-display controllers.

by Colin Carson

In the world of computers, the word 'monitor' has an unfortunate double meaning. A software monitor is a program, permanently resident in a computing system, which can be used to test peripherals or memory on that system and perform simple program debugging. An electronic monitor is almost a television set without the receiver and loudspeaker: essentially it is the tube, sometimes the power supply, and the electronics required to produce a picture. Instead of the aerial being the signal source, an unmodulated signal has to be provided — either composite video or direct drive. The former is a single line, whereas the latter is made up from three lines — a video line, horizontal sync. and vertical sync. lines.

Composite video

Figure 1 shows some sample video waveforms. In the composite video signal, the quiescent level is usually 0.3V, which corresponds to black level on the screen. Synchronizing pulses are superimposed on this black level, the short pulses forcing a horizontal retrace and the long ones vertical retraces. The majority of the time between horizontal sync. pulses can be used for the display, the remaining time from just before to just after the sync. pulses being the blanking period, during which the tube does a retrace. During blanking, the signal must not exceed the black level, or the retrace will be seen on the screen. The composite video signal rises to 1V, the 'white level' or brightest white on a white monochrome set: since the signal varies between 0.3V and 1V, the picture increases in intensity through levels of grey. The waveform shown would produce a bright white dot at the left-hand end of that scan line. A line impedance of 75 ohms is normally associated with composite video signals.

Direct drive

The direct-drive waveforms, also seen in Fig. 1, should produce the same visible results as the composite waveform shown above them. Direct-drive voltage levels are not as well defined as composite video — some monitors take signals from t.t.l. buffers, while others need 1V signals.

Direct drive has the advantage that all the drive signals are, normally, readily available from the circuitry generating the video signal; however, it is difficult to send these signals over long lengths of cable. This problem is avoided with composite video, which can be transmitted down metres of coaxial cable without much of a problem. Direct-drive signals can be converted to composite video with a

handful of components, but the reverse procedure is not so easy. Generally, there are more direct-drive t.t.l. monitors on the market than the composite-video type and the price of the former is normally slightly lower.

Of course, a monitor is not essential: a low-resolution picture can easily be produced on a television set, by connecting a composite-video signal to a u.h.f. modulator. The modulated signal is fed down coaxial cable to the aerial socket on the television receiver, which is then tuned to the new signal on a spare channel.

Bandwidth

The picture is made up from discrete dots, which merge together when viewed from a distance. Only a finite number of dots can be fitted into the display time available and this number is limited by the bandwidth of the monitor or television. If a monitor possesses a bandwidth of 10MHz ($1/f = 100\text{ns}$), then the minimum width of a dot must at least be equal to $1/f$ and preferably double — that is 100 to 200ns. If this constraint is not met, then the monitor will be unable faithfully to interpret the video waveform. Having decided upon a dot width, its inverse is termed the dot-clock frequency and is usually the highest frequency needed in a system. When incorporating a video display into a system it is always desirable to generate dot-clock, processor clock and band rate from dividers driven from a single crystal oscillator — although this is not always possible.

Suppose a dot clock frequency of 10MHz is used with a monitor having a horizontal scan rate of 15.625kHz (64 microseconds) with 48 microseconds of that allowed for display, then it would be possible to display x dots on each horizontal scan line, where x equals the available

time (48) divided by the dot width (0.1) — that is 480 dots.

A domestic television set has a bandwidth of between 4 and 8 MHz, whereas monitors commonly have bandwidths up to 20MHz, some up to 65MHz.

Horizontal scan rates

The television standard of 15.625kHz has the disadvantage that, to much of the population, it is audible. There is a growing trend to increase this frequency so that it cannot be heard, 18 to 20kHz being common. Obviously, as this frequency increases, so does the bandwidth necessary to display the required number of dots.

Vertical scan rate/refresh rate

In the UK, the vertical scan rate is nearly always 50Hz, although an increase of 5Hz or so can be useful for reducing screen flicker. As soon as a monitor is run at anything but 50Hz, care must be taken to avoid hum loops.

Knowing the vertical and horizontal scan frequencies, the maximum number of horizontal scan lines can be calculated. A frequency of 50Hz corresponds to 20 milliseconds between vertical sync. pulses, of which one millisecond might be needed for vertical blanking. The remaining 19 mil-

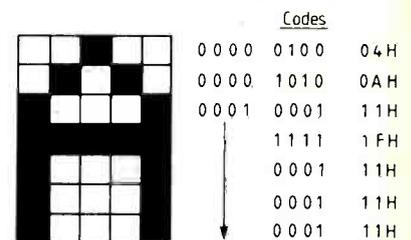


Fig. 2. Capital A formed in a 7 × 5 matrix, with matrix patterns obtained from character generator and hex. equivalents.

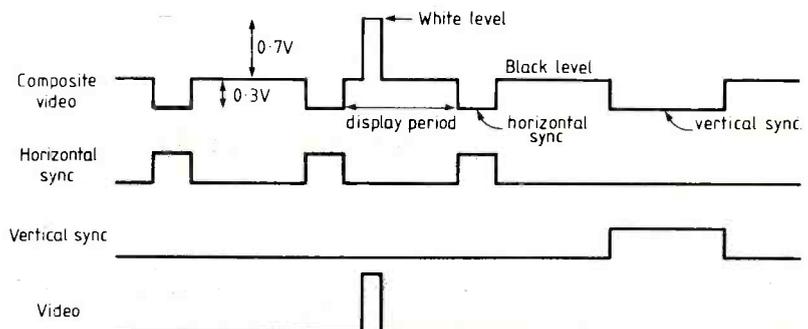


Fig. 1. Video waveforms. Top is composite-video signal, while other three waveforms,

fed separately, form the direct drive.

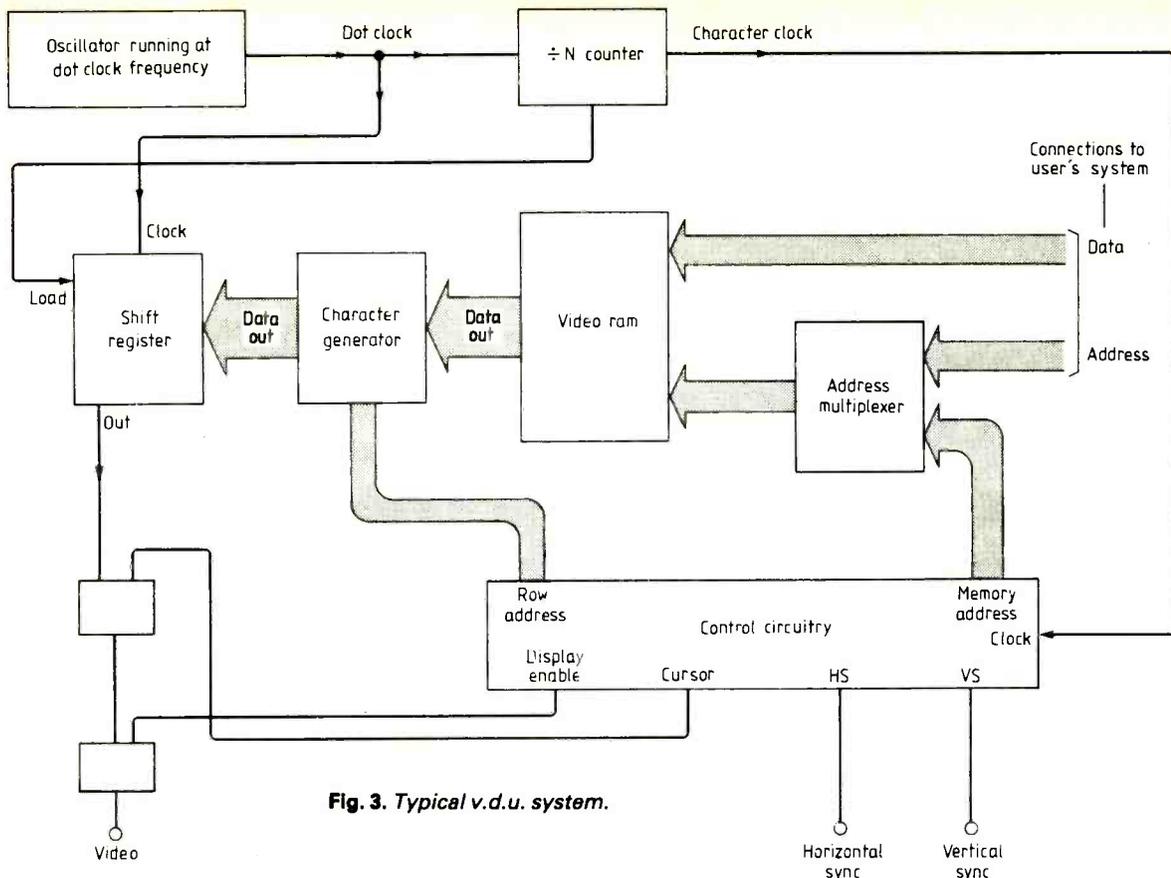


Fig. 3. Typical v.d.u. system.

liseconds is available for horizontal scan lines, the number of which is calculated by dividing this period by the horizontal scan time, i.e. $19000/64 = 296$ scan lines.

Characters

A character can be displayed on the screen by illuminating specific dots within a small matrix, 5×7 and 7×9 being common matrix sizes. Figure 2 shows an upper case 'A' formed in a 5×7 matrix, which is adequate for low-bandwidth applications. Larger matrices improve character resolution, provided the monitor has sufficient bandwidth. With a 5×7 matrix, an inter-character spacing of one dot is acceptable, so a scan line supporting 480 dots could handle $480/(5 + 1) =$ i.e. 80 characters horizontally.

The matrix patterns for each character displayable by a video system are stored in a prom or rom character generator and make up what is known as the character set. Each pattern has to be coded into binary, using a 1 where the matrix is to be illuminated and 0 elsewhere. Each horizontal bit pattern in Fig. 2 is converted to a byte and stored, scan line by scan line, in the character generator, which is often a prom, so that the character set can be changed at will.

If 296 horizontal scan lines are available, and a 5×7 matrix is being used with three scan lines free between each row of characters, then 29 rows of characters could be fitted onto that screen. This would not be very readable and would not allow for lower-case letters with descenders such as 'g' or 'y'. They are accommodated by in-

creasing the depth of the matrix or by raising them into the matrix, which can be strange visibly.

The character clock indicates the rate that characters appear on the screen. If dot clock is 100MHz and each character is $5 + 1$ dots wide, then the character clock rate is $10/(5 + 1) = 1.67$ MHz.

Cursor

The cursor is a block or bar of light, often flashing, which moves around the screen indicating the position where the next character is to appear. As the screen is filled with text, so the cursor moves along covering each line in turn: carriage return sends the cursor to the start of the next line down. When the cursor reaches the end of the bottom line on the screen, it is common for the text to scroll, which means that each line of text moves up the screen one line and the top line disappears.

Video ram

Figure 3 shows a typical, minimum visual-display system.

Screen information is stored in an area of ram known as video ram: in older designs, this ram often has separate data input and output pins. Each byte in the video ram corresponds to a position on the screen; for example, a screen having 16 rows of characters with 64 characters in each row requires 16×64 , i.e. 1024 contiguous bytes of video ram. The first byte corresponds to the first character on the first row, the second to the second character on the first row . . . the 65th byte to the

first character on the second row and so on until the 1024th byte which corresponds to the last character in the last row.

A code has to be stored in each location to define what character will appear at the allocated position on the screen. This code is usually an ASCII seven-bit code; the character generator is coded similarly. As the video ram is likely to be eight bits wide, and the ASCII code only seven, the spare bit can be used for other purposes.

The video ram is accessible by both the video control circuitry and the user's system — the latter may well want to read the video ram as well as write to it. Exactly how the circuitry arbitrates between the two interested parties is a matter for some care. In Fig. 3 a multiplexer is fitted to the address lines feeding the video ram so that they can be switched between the user's system and the video control circuitry, which issues a series of 64 sequential video ram addresses. At the top of the screen, the first address issued is 000H, as this corresponds to the first byte on the first row, the next 001H and so on up to 03FH. Suppose that 41H is stored in location 000H; shortly after the issue of that address by the control circuitry, 41H appears data output pins and this code is presented at the input of the character generator. The control circuitry also issues a row address for the character generator, which increments for each scan line of the character. The display-enable line is active except during blanking and the cursor line at the time it is present on the screen.

Continued next month



No hangover!

Hangover, a rather loose term to describe the stored energy resonance in a loudspeaker, the principal cause of colouration that immediately tells you you're listening to a loudspeaker.


Take it away and there's a new world – the loudspeakers have nothing more to say – instead there's just the orchestra and the magic of the music.

If music is an important part of your life, then a pair of ESL-63 loudspeakers could be the best investment you've ever made.

Perhaps even something to celebrate about.



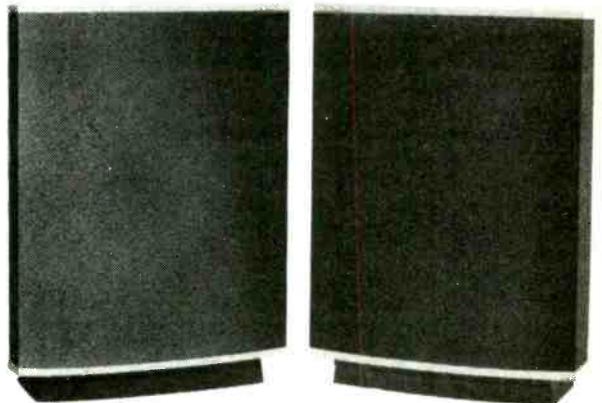For further details and the name and address of your nearest Quad ESL-63 retailer write or telephone The Acoustical Manufacturing Co. Ltd., Huntingdon, Cambs., PE18 7DB. Telephone: (0480) 52561.



QUAD 
for the closest approach
to the original sound

WW - 013 FOR FURTHER DETAILS

Better by design



The best ref. for the low power game.

What makes the new Ferranti ZNREF Series such a sharp-eyed reference source in the lower power field?

A minimum operating current of 150 μ A. Voltages from 2.5V to 10V. Excellent temperature stability. Low dynamic impedance. Trimmable output. A choice of initial voltage tolerances. And the ability to control the game over a wide range of currents and temperatures.

Whatever league you're in—data

acquisition systems, portable instrumentation, codec systems or digital voltmeters, put the whistle in the hands of one of our ZNREF Series and win the game.

Send for data or contact,

Ferranti Electronics Limited,
Fields New Road, Chadderton,
Oldham OL9 8NP.
Tel: 061-624 0515/6661
Telex: 668038

FERRANTI

Semiconductors

WW - 0% FOR FURTHER DETAILS



Distributors: Celdis, Reading, Tel: 0734 585171 • Farnell Electronic Components, Leeds, Tel: 0532 636311 • Intel Electronics, Henlow, Tel: 0462 812505 • ITT Electronic Services, Harlow, Tel: 0279 26777 • Midwich Computer Co., Bury St Edmunds, Tel: 0284 701321 • Semicomps, Keighley, Tel: 0535 65191 • Semicomps, Kelso, Tel: 0573 24366 • Swift-Sasco, Crawley, Tel: 0293 28700.

AUDIO OSCILLATOR WITH TONE BURST

An audio signal generator, providing both sine and square outputs from 10Hz to 250kHz. Switch-controlled logic circuitry provides a variable mark/space-ratio tone burst, and the output can be switched to include a RIAA network

This article describes the design and construction of a signal generator capable of producing both sine and square waves in the range 10Hz-250kHz. Comprehensive tone-burst generation facilities are also provided. The oscillator section is a conventional Wien-bridge configuration, using an RA53 thermistor for amplitude stabilization; and for those who have no requirement for tone burst facilities, the oscillator, associated attenuator, and output amplifier may be used as the basis for a good general-purpose sinewave generator. The sine-wave distortion has not been measured, but the distortion figure for this type of circuit is usually claimed to be 0.5 - 1.0% over the 20Hz - 20kHz range. Also included in the oscillator section is an octave switching arrangement (very convenient for checking filter slope rates) and an RIAA pre-emphasis network, which may be used for testing the performance of magnetic pickup preamplifier inputs.

Circuit description

The oscillator, shown in Fig. 1 employs a Wien-bridge network to determine frequency and the oft-used R53 thermistor stabilizes the oscillator output at about 1V r.m.s. It is the simplest (and most reliable) form of stabilization, its main drawback being a relatively long thermal time constant which gives rise to some output-amplitude bounce on changing frequency.

Variation of R_A/R_B and/or C_A/C_B control output frequency: R_1 and R_6 set the maximum frequency for a given value of C ; minimum frequency is determined by the

by J. T. Tiernan,
F.S.E.R.T.

maximum value of R_A/R_B (plus, of course, R_1 and R_6). In practice, the value of C_2 also affects the lowest frequency that can be obtained - the larger the value of C_2 the lower you can go.

A CA3140 op-amp is used as the active element in the oscillator, with R_7 included to help it sink current to the 0V line. With out R_7 , there is noticeable clipping of negative half cycles of the output sinewave. A 741 may be substituted directly for the 3140, but the 741's poor slew-rate performance will limit the upper frequency obtained to around 50kHz.

Frequency determination. Many signal generators have frequency bands spanning the 15-200 range; but that is not always convenient, and this design works in bands of 10-150 via the selection of CA_{1-4} and CB_{1-4} (Fig. 2). An additional and useful feature is provided by capacitors CA_{11-44} and CB_{11-44} in conjunction with S_7 , operation of which effectively halves the value of the selected capacitors and causes the output frequency to be exactly doubled. It allows for quick and convenient checking of filter roll-off slopes.


The bandwidth of a given effect is usually proportional to its centre frequency, and this implies that it would be appropriate to give more dial space to the

lower frequencies in order to keep bandwidth vs frequency in proper perspective. Many commercial signal generators for serious audio work give approximately equal space on the dial scale for each octave of frequency covered, and the (nearly) ideal component for R_A/R_B is a dual square-law potentiometer. Such components are available but, besides the expense, they are wirewound, rather large, and not well suited to high-frequency operation. However, shunting the active section of a log-potentiometer, as shown in Fig. 2 (R_{32} and R_{33} across R_A and R_B) produces a very acceptable result. Frequency calibration holds good up to about 50kHz, but above that there is a gradual divergence leading to a -15% error at the maximum output frequency.

The output from the oscillator at points E and F of Fig. 1, is about 1V r.m.s. and is fed to the tone-burst section (to be eventually returned to point G for output conditioning). Those who wish to make use of the oscillator section only may link points E and G directly.

Attenuator. Resistors $R_8, 9, 10$, in conjunction with S_2 and P_1 , form a simple decade attenuator. The decade divisions are not exact owing to the finite input impedance (47k) of the output amplifier. The attenuator is placed before the amplifier in order to realise minimum output impedance, and hence maximum drive capability at the output terminal. If 600 ohm output impedance is required it can be achieved by bridging points M and N with a 600 ohm resistor.

Fig. 1. Wien-bridge oscillator circuit with output amplifier. Frequency determining network shown in Fig. 2.

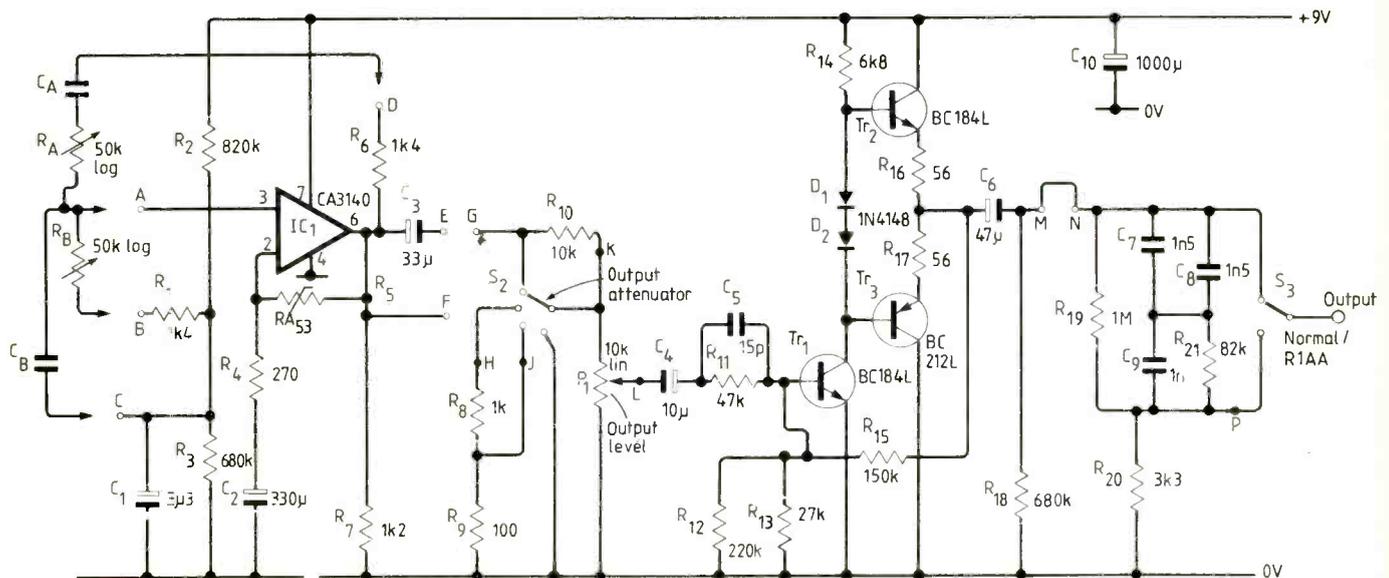

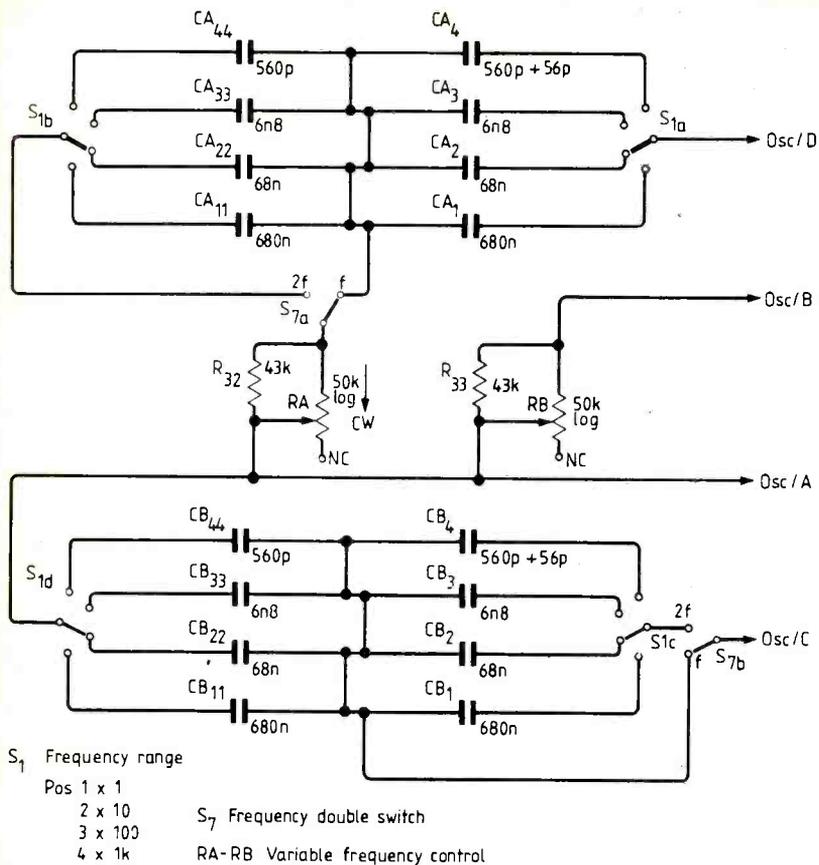


Fig. 2. Components shown as CA , RA , etc in Fig. 1. Frequency is switched in decade steps and S_7 doubles frequency.

Output section. The output amplifier is a simple class B design with a gain of about 2.5, and it is capable of driving output loads as low as 10 ohm (but at reduced output, about 300mV maximum). There are no discernible crossover effects and its performance is far superior to that which could be obtained by using, say, another 3140 op-amp. The d.c. levels have been chosen to allow operation down to +7.5V supply voltage (the lowest value at which the battery supply can be considered usable) at which the amplifier will deliver 2V r.m.s. before the onset of clipping. This approach restricts the maximum potential output which could be realised for supply voltages above 7.5V, but it should prove adequate for most test applications. With the amplifier gain value chosen it will always be possible to provide slight overdrive at the maximum settings of S_2 and P_1 ; and the short circuit output current is limited to 50mA r.m.s. with $R_{16}=R_{17} = 560\text{ohms}$. Output rise and fall times (square-wave input with $C_{12} = 18\text{pF}$) are symmetrical and surprisingly good for so simple a design.

The final bit of output circuitry is a passive RIAA pre-emphasis network, accurate to within 1dB, and useful for carrying out equalization checks on magnetic pickup preamplifiers. The attenuation factor of the network measures 31dB, and output impedance 3k3 ohms, at 1kHz.

Tone burst generator

The ability to generate short but precisely defined bursts of signal is a very useful attribute for a piece of audio test equipment; audio systems can be fed with test

inputs which approximate to the real-life situation, and the following applications spring immediately to mind:

- amplifier peak power determination;
- visual inspection of amplifier transient behaviour;
- measurement of noise reduction circuitry performance; (attack/release times and frequency sensitivity)
- loudspeaker tone burst testing.

In the circuit to be described, c.m.o.s. logic i.cs are used to generate the tone-burst control signals. The design uses four i.cs, and tone-burst timing is controlled by the outputs of a single 12 bit counter, clocked at the oscillator signal frequency. An oscilloscope pre-trigger is produced one half cycle before the start of a tone burst.

Logic description. The circuit diagrams for the control logic are given at Figs 4 and 5, but to aid understanding, an equivalent-function logic version, with associated waveforms, is given at Fig. 3. (The waveforms assume selection of the Q_1 and Q_2 outputs - points G and H - from the counter, to set the number of cycles in the burst and the total sequence period respectively.)

Referring to Fig. 3; the counter is running constantly, clocked via a squaring amplifier and Schmitt trigger (note that the counter advances on the negative transition of the clock signal). Every time


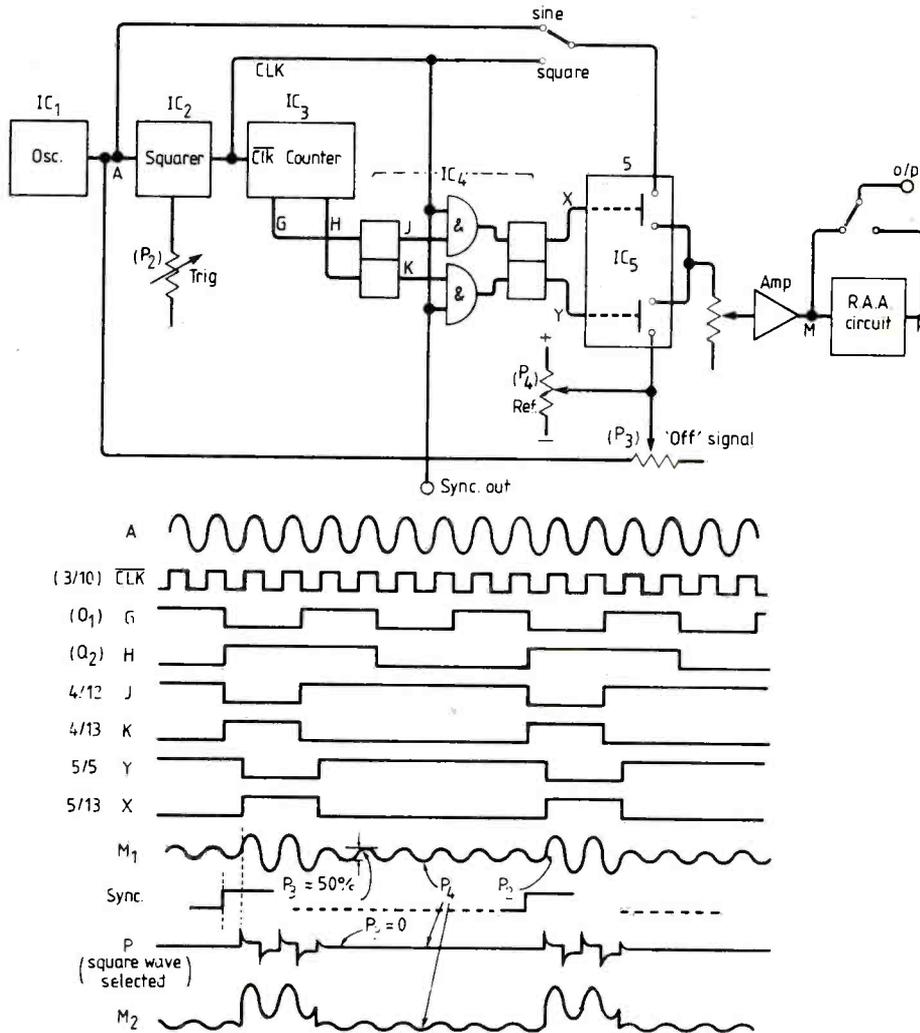


Fig. 3. Basic circuit of tone-burst switching, with waveforms.

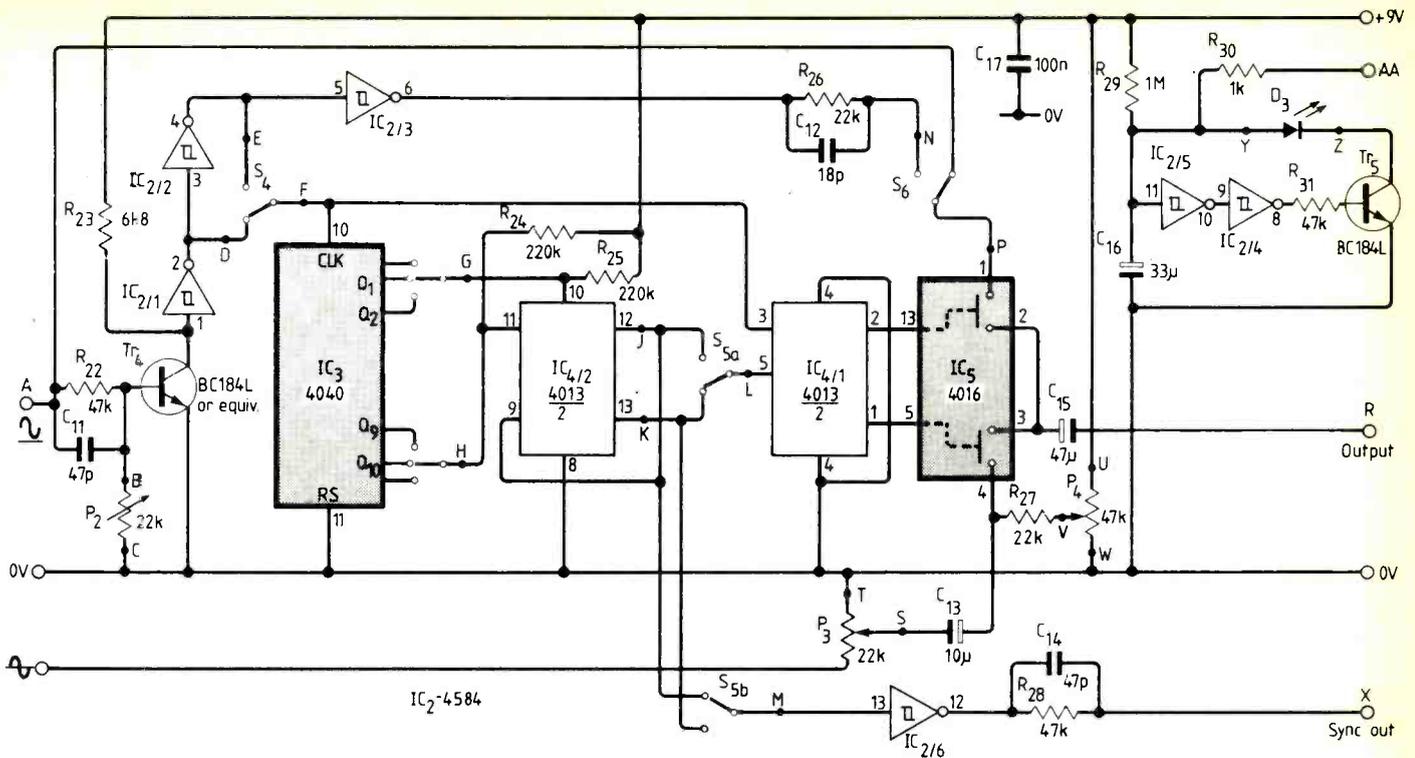

IC₂-4584

G goes positive it will either set or maintain toggle output J at logic 1. Each positive transition of H will reverse the status of the first toggle, but reset will occur as soon as there is a positive transition at G.

Since the counter advances on the negative clock transition, the states of J and K will not be transferred to X and Y until half a cycle after they (J and K) have changed: this system ensures there will be no odd triggering effects due to counter propagation delays, but it will provide a convenient (and necessary, for some 'scopes) sync. waveform half a cycle before the analogue gate IC₅ is opened for a tone-burst transmission. During the X 'on' period, the upper gate of IC₅ transmits the input signal to the output attenuator: during the Y 'on' period it will pass whatever is present at the input of the lower gate, which is a d.c. level set by P₄ (usually to the centre level of the signal waveform on the upper gate) on which may be superimposed the input sine wave from point A, at an amplitude determined by the setting of P₃. The trigger control, P₂, sets the mark/space ratio of the Schmitt-derived square wave, and hence either (a) the duty cycle of the output waveform (square-wave output selected) or (b) the point on the sine wave at which the tone burst starts. Wave-

Fig. 4. Tone-burst gating. Inputs from circuit of Fig. 1. (E and F) and output to G in Fig. 1.

forms M₁, M₂ and P give some idea of the effects of P₂, P₃, and P₄. Note that the waveform lettering is correct in relation to Figs 4 and 5 except those noted arbitrarily as X and Y at the inputs to the analogue gates.

Taking the real-world circuits and dealing first with Fig. 4, Tr₄ takes the input sinewave, plus a 4.5V d.c. level, from point F in the oscillator section and raises it to a level suitable for operating the Schmitt trigger IC_{2/1}. Variation of P₂ allows variation of the m/s ratio of the resulting square wave between 0 and 100%. The Schmitt circuits invert the input waveform, and thus S₄ will select a

clock-pulse train which may be either in phase or 180° displaced from the input sinewave. The setting of S₄ (INVERT) determines the polarity of the output tone burst, i.e. 'n' cycles, starting with a positive half cycle, or 'n' cycles starting negative. A third Schmitt, IC_{2/3}, is used to invert and buffer the square wave for input to the analogue gate, and R₂₆/C₁₂ attenuate it to approximately the same pk-pk amplitude as the sinewave (but only at V_{supply} = 9V; the square wave amplitude will vary according to the actual supply voltage).

The square wave at point F clocks the counter to produce division ratios 2, 4, 8, 16 . . . 2048, 4096 at the Q₀ . . . Q₁₁ terminals, and the selected Q points are fed to the 'set direct' and clock inputs of IC_{4/2} (a D-type flip-flop with the D input on pin 9) - refer back to Fig. 3 for the

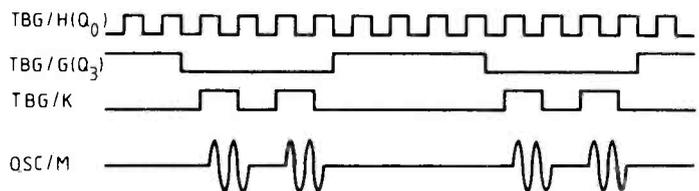


Fig. 6. Setting S₈ in Fig. 5 to "PATTERN" produces this type of output.

waveforms. Either the J or K output may be selected to feed the D input of IC_{4/1}, and the position of S₅ determines the tone-burst /space relationship of the output sequence. For G=Q₂, H=Q₇, S₅=K, the output will consist of sequences of eight cycles of signal followed by 248 (=256-8) cycles of 'space'. With S₅ = J and Qs unchanged, the output sequence will be reversed to 248 cycles of signal and eight cycles of 'space'.

For constant sine or square-wave output (S₆) the Q selection switches (Fig. 5) are all set to 'off' (J = 1 via R₂₅) and S_{5(a)} is set to select K (REVERSE).

The sync. output is taken from either J or K via S_{5(b)} and buffered out via IC_{2/6}

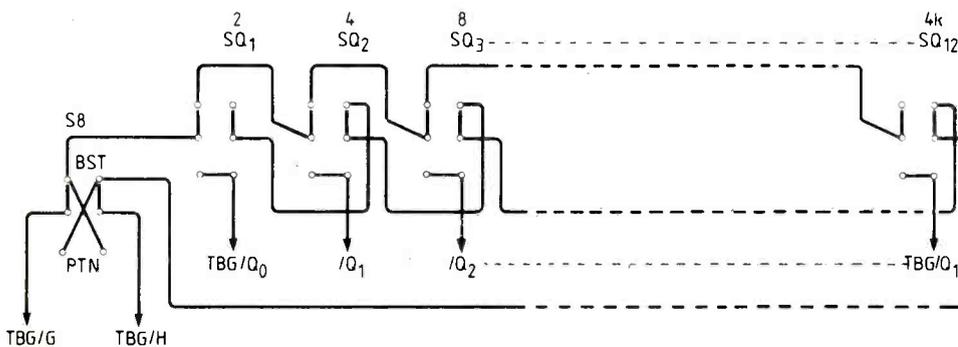


Fig. 5. Switching for tone-burst gating. Circuit connects to G and H in Fig. 4.

and R_{28}/C_{14} . In practice, point M can be connected directly to point L; $S_{5(b)}$ is only required if your oscilloscope 'prefers' triggering from a particular polarity waveform when $S_{5(b)}$ can be wired accordingly.

Q switching (Fig. 5). It is appropriate to look at the counter switching arrangements at this point rather than going immediately to the circuitry around $IC_{2/4}$ and $IC_{2/5}$. There are 12 Q switches, one for each of the counter outputs $Q_0 - Q_{11}$, and the interconnexions are such that, regardless of the total number of switches in the 'on' position, only the outer two are effective and feeding Q signals to S_8 . With S_8 in the BURST position, the generated control signals are as depicted in Fig. 3. The time period contribution of an 'effective' Q switch depends on whether it is the first (feeding G) or the last (feeding H); the last switch sets the overall sequence time period in accordance with the normal binary weighting of its Q input, i.e. $Q_0 = 2, Q_2 = 4, Q_2 = 8$ etc. The first switch sets the burst-time period within the overall sequence at a value equal to half its binary weighting ($Q_0=1, Q_1=2$, etc). Waveforms G, H, J make the relationship clear.

When S_8 is in the PATTERN position, the situation is rather different and the operation cannot be seen from the simple representation at Fig. 3. The waveforms given in Fig. 6 show what happens when $G=Q_3$ and $H=Q_0$. When, say, $G=Q_6$ and $H=Q_2$, the output will consist of 128 cycle sequence periods, within which there will be four bursts of eight cycles spaced at eight-cycle intervals. This option may have no useful application, but the result is too pretty to ignore, and it is the only option which can produce 1:1 mark-space ratio in tone-burst mode.

Turning now to the last two elements of IC_2 ($IC_{2/4}$ and $IC_{2/5}$); these are used to form a 'battery saver' circuit feeding a front panel led 'on' indicator (D_3). With the component values specified, C_{16} charges (via R_{29}) and discharges (Tr_5 and D_3) on a three-second cycle, causing the led to flash appropriately. But with the led buried in a plastic bung for panel mounting, and in a well-lit room, the effect is, frankly, disappointing; the led needs to be reasonably openly mounted, and angled upwards, for it to be worthwhile.

The resistor R_{30} and terminal AA are provided to give constant led operation when the generator is fed from an external supply (see Fig. 7); but if a rise to 16mA on battery operation can be tolerated, terminal AA may be connected permanently to the +9V supply line.


Finally, in this description of the tone-burst logic, a couple of points about the nature of the input to terminal A should be mentioned. In order to exercise smooth control of the m/s ratio to the square wave out of $IC_{2/1}$, the input circuitry for Tr_4 has been designed to accept a sinewave input of about 1V r.m.s. with a d.c. component of about +4.5V. It is also worth mentioning that shunting P_2 (22k) with a 33k resistor gives smoother control than the potentiometer on its own. The signal inputs to

Specification	
All measurements taken with battery supply, $V=9.5V$	
Frequency range	10Hz-250kHz in four overlapping bands. 10-150 nominal band scale plus octave multiplier.
Output waveforms	<ol style="list-style-type: none"> 1. continuous sine wave 2. continuous square wave with variable m/s ratio and symmetrical rise/fall times: to 70% 60ns to 90% 250ns at 7V pk-pk output and 10k Ω load. 3. Sine-wave burst: any binary figure (1,2,4,8 etc) between 1 and 2048 cycles within an overall timing sequence selectable between 2 and 4096 cycles. 4. Square-wave burst, as for 3. 5. Either 3 or 4, but with variable-amplitude sine-wave, interposed between the main burst signals. 6. Group burst patterns 7. All the above but with RIAA pre-emphasis.
Maximum output signal (1KHz sine wave)	$R_L=10k \Omega$ 2.5Vr.m.s. $R_L=600 \Omega$ 2.25Vr.m.s. (+9dBm) $R_L=100 \Omega$ 1.5Vr.m.s. $R_L=10 \Omega$ 300mVr.m.s.
Amplitude/frequency stability	+0.5 -1.0dB, 10Hz-250kHz (ref. 1kHz, 2V r.m.s.)
*Square wave amplitude	Variable up to 7V pk-pk
Short-circuit output current	Limited at 50mA r.m.s.
Supply requirement	7.5-9.5V at 10mA (internal batteries) or 7.5-12V at 12-20mA (ext. supply)
*set approximately equal to sine wave pk-pk output (with 9V supply)	


the analogue gates (IC_5) must not go outside the limits bounded by the power supply feeds to the i.c. Slight overdrive will result in clipping of the output and severe overdrive may cause permanent damage to the device. The output from Point F on the oscillator fulfils both the above, and if anyone wishes to make up the tone-burst logic only, to be driven from a generator with an earth-referred output, a coupling network similar to that

at Fig. 8 must be used for coupling to point A (TBG/A) in the tone-burst logic.

continued on page 86

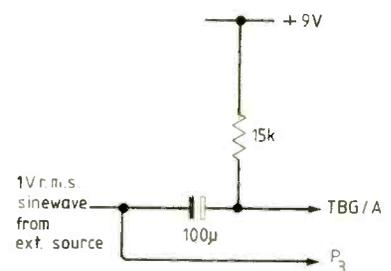

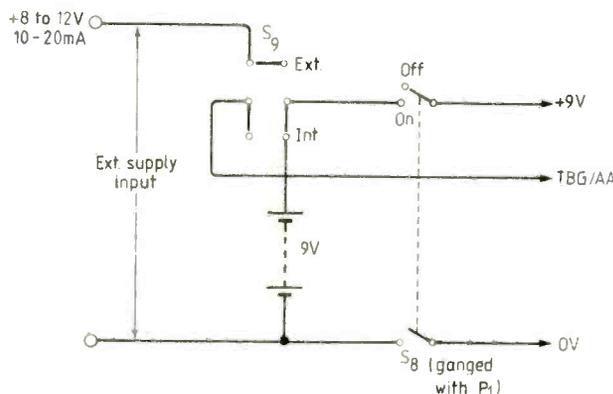▲ Fig. 8. Circuit to allow the use of the tone-burst generator alone.



◀ Fig. 7. Power supplies. See text for recommendations.

LETTERS

TAPE VOICES

It is now more than eleven years ago that Konstantin Raudive's book, "Breakthrough" announced the discovery of the tape-voice phenomenon to the English speaking world. The publication started what at that time was expected to become the greater challenge in the field of parapsychology and electronics.

Wireless World also carried a detailed review of the book "which I strongly commend to your attention" (Vector, June 1971), and the comment that "the problem cries out for investigation". For the sake of truth, it must be admitted that some interesting investigations indeed was carried out, and the results of some very convincing tests (by Pye, Belling-Lee, and others) were published. Also, a lot of articles, radio and television programmes dealt with the matter. But after a short time, the interest decreased, and today (to my best knowledge) all research is done outside Britain.

Can it really be true that British engineers and technicians (I mean, of course, real technicians and not modern black-box manipulators with digitalized brains) have completely given up this, "the greatest challenge"? I can't believe that this should be the case.

Anyhow, if there is somebody working on the technical aspects of this matter, I should be very glad to hear of it.

Peter Stein
3400 Hilleroed
Denmark

LM 109

In Appendix 1 of the interesting article "LM 109 three-terminal voltage regular" (March 1982), J. L. Linsley Hood sounded hardly convincing when he neglected the last two terms of equation (1), as these are strongly temperature-dependent. I would like to propose a simpler, but more credible solution.

The voltage across a forward-biased emitter junction in silicon is approximately 0.6V and decreases by 2mV per degree Centigrade. Therefore $V_{BE}=0.6$ and $\partial V_{BE}/\partial T=-0.002$. On the other hand,

$$V_{BE} = \frac{kT}{q} \ln \left(1 + \frac{I_E - \alpha_1 I_C}{I_{EO}} \right)$$

where α_1 is the inverted common-base current gain. As I_E and I_C are much greater than the leakage current I_{EO} and α_1 is in the order of 0.5, it is reasonable to assume that

$$\frac{I_E - \alpha_1 I_C}{I_{EO}} \gg 1$$

$$V_{BE} \approx \frac{kT}{q} \ln \left(\frac{I_E - \alpha_1 I_C}{I_{EO}} \right)$$

Imposing the condition $I_{C1}=10I_{C2}$ for two identical transistors at the same temperature,

$$\frac{I_{E1}}{I_{E2}} = \frac{I_{C1}}{I_{C2}} = \frac{I_{E1} - \alpha_1 I_{C1}}{I_{E2} - \alpha_1 I_{C2}} = 10$$

$$\Delta V_{BE} = \frac{kT}{q} \ln \left(\frac{I_{C1}}{I_{C2}} \right)$$

which is equation (3) in the article.

$$\frac{\partial}{\partial T} \Delta V_{BE} = \frac{k}{q} \ln \left(\frac{I_{C1}}{I_{C2}} \right) = \frac{\Delta V_{BE}}{T}$$

The reference voltage should be independent from temperature:

$$V_{out} = V_{BE} + \delta \Delta V_{BE}$$

$$\frac{\partial}{\partial T} V_{out} = \frac{\partial V_{BE}}{\partial T} + \delta \frac{\partial \Delta V_{BE}}{\partial T}$$

$$= -0.002 + \frac{\delta \Delta V_{BE}}{T} = 0$$

$$\delta \Delta V_{BE} = 0.002T = 0.6 \text{ volts for } T = 300^\circ\text{K.}$$

Finally,

$$V_{out} = V_{BE} + \delta \Delta V_{BE} = 0.6 + 0.6 = 1.2V,$$

which is the "band-gap" potential for silicon.
W. Falcone,
Department of Pharmacology
Leeds University.

CALCULATING V.S.W.R.

I have stumbled upon a quick method of calculating v.s.w.r. when the reflection coefficient is known and vice versa, which may be of interest to *Wireless World* readers. This method is especially helpful for use with a scientific pocket calculator. The theory behind this method is as follows:

$$v.s.w.r.(s) = \frac{1+|r|}{1-|r|}$$

where r is the reflection coefficient. This function has a minimum value of 1 when $|r|=0$, and a maximum value of infinity where $|r|=1$.

A function with identical properties is $\tan(45^\circ + |x|)$ which is 1 for $|x|=0$ and infinity for $|x|=45^\circ$. Expanding,

$$\tan(45^\circ + |x|) = \frac{\tan 45^\circ + \tan |x|}{1 - \tan 45^\circ \tan |x|} = \frac{1 + \tan |x|}{1 - \tan |x|}$$

This leads to the conclusion that if

$$s = \tan(45^\circ + |x|), \quad |x| = \tan^{-1}|r|$$

$$\therefore \tan^{-1}s = 45^\circ + \tan^{-1}|r|$$

The method of calculating $|r|$ from s is therefore to convert s into an angle by taking the inverse or arc tan on the calculator, subtract 45° and then take the tan of the difference.

A. Marshall
Teddington
Middlesex.

DOUBLE-BLIND LISTENING TESTS

IT would seem that the double-blind listening test (d.b.l.t.) method has been primarily concerned with measurement oriented methodology. Little, if any, consideration has been given to the hearing processes and the listening behaviour involved in the design of the test method. I believe there is reasonable cause to doubt the results of this test method.

The A-B d.b.l.t. is conducted in conditions which do not represent the situation in which we normally experience reproduced music. Perhaps a test that more closely parallels conditions in which audiophiles say they've heard

differences would be a step in the right direction. Those conditions include but, are not limited to: aural familiarity with the equipment; aural familiarity with the room; and both of the above achieved through listening periods of an extended length of time.

Consequently, for a valid listening test, the person doing the test needs to be very familiar with the system; all of its components together in the particular room in which the test is being conducted. This would probably be the home system of the person doing the test. A d.b.l.t. which ignores the normal listening conditions should be suspect.

Differences seem most noticeable (after long familiarity with one unit) the first few moments after a change is made. After changing to the unit on which one heard a difference, the longer one is exposed to only this new unit the less one is struck by the difference between the two. Long term listening periods (familiarity) are necessary to hear differences that are most noticeable when initially changed to another unit.

Shortening the listening period (as d.b.l.t. are now conducted) does not seem to lead to the same degree of noticeable difference. It seems that as we shorten the listening period between units the more alike they tend to sound. Carried to extreme, if we switched between the two units under test very rapidly there would be no perceived difference at all. We hear a composite of the two. Such qualities as imaging and related sound field perceptions require careful long term listening. In many cases only long term listening comparisons will clearly reveal a difference between the two and what that difference is.

Audiophiles spend many hours listening to music via their own systems and develop a high degree of sensitivity with those particular systems. In many cases the equipment used compliments their perceptual biases, which increases the person's enjoyment and sensitivity to certain interests. Equipment changes are more likely to be noticeable in this environment, and it is in just this kind of environment that many audiophiles say that they hear differences.

The process of subjecting an individual, or worse, a panel of listeners, to only an evening of d.b.l.t. in an unfamiliar acoustical environment, with unfamiliar equipment and adding a randomizing procedure to the testing, results in just what one would expect - insensitivity and aural confusion. Such testing to date has been rather like an experiment where we design instrumentation to measure very accurately certain parameters but we don't understand the experiment and therefore gather accurate garbage.

No method exists that can "prove" either the existence or non-existence of a given perceptual phenomenon. Thus the astute audiophile will note the claims and counter-claims and the conditions that produced them, and will attempt for himself to hear (or not hear) what was claimed. He would be better served to listen for himself rather than accept others' biases and perceptions or the results of d.b.l.t.s. As long as there continues to be an interest in listening tests, inquiry into the nature and behaviour of the listening and hearing processes must be sought, understood and appropriately incorporated.

Richard N. Marsh
Livermore
California, USA.

TELETEXT DECODER

Mr Alan Pemberton's letter on p.49 of February 1982 *WW* points out why the original erase page circuitry does not work correctly with interleaved magazines, as currently used on 'Oracle'.

Unfortunately, I found that the circuit he suggested, while working fine on Oracle, caused the loss of the first 4 rows of Ceefax pages (following the header) on my decoder. In his modified circuit, when 77,1 is high, the negative strobe pulses from 71,3 pass through 77,6 and clock IC₇₈ on their positive going back edges. When 77,1 is low, 78,11 is held low regardless of 71,3.

However, as 71,3 is normally high, IC₇₈ will also be clocked when 71,5 goes high, and I suspect that I was encountering unwanted loading of IC₇₈ at this point.

The modification can be simplified by leaving the feed to 78,12 unchanged from the original design, while And gating 71,3 with Q (78,8) instead of 71,5; so that once IC₇₈ is set, the clock is disabled until the bistable is cleared by the next field sync. on pin 13.

As my decoder uses the whole of IC₇₇ for other purposes, the And gating was achieved by inserting a germanium diode between 71,3 and 78,11 (cathode to 71,3); and adding a second one from 78,11 to 78,8 (cathode to 78,8).

For the correct operation of the decoder with interleaved magazines, it is essential to break the link from 5,9 to 21,1; and to carry out the modifications described on p.60 of February 1977 *WW*, which check the magazine number of every row.



J. H. Hinton
Cambridge

I have received details from Humphrey Hinton of his own modification, and now see the reason for the odd behaviour of my modification in his decoder. An earlier obscure modification of my own had resulted in IC₇₈ being clocked by positive-going pulses, and not negative-going as in the original design.

A simple re-arrangement of the gates of IC₇₇ will ensure that 'standard' decoders will function correctly on both Oracle and Ceefax.

I thank Mr. Hinton for bringing this to my attention and apologise to constructors who have tried the modification without success.

Alan Pemberton
Sheffield

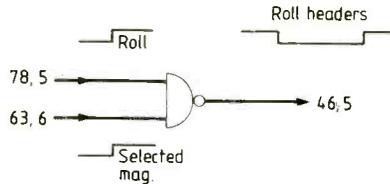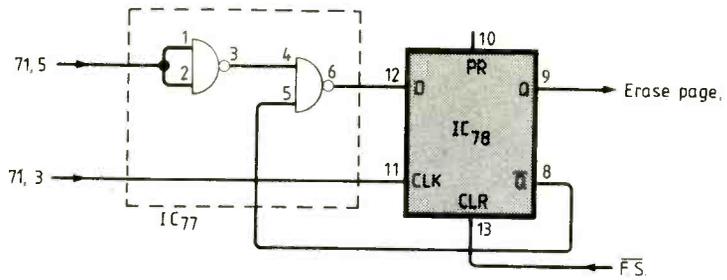

I was pleased to see in the Letter Column (*WW* February 1982) that an interest on the *WW* Teletext decoder still prevails. I was encouraged by Mr. Pemberton's letter to modify the clear page detection circuit enabling the decoder to work with interleaved magazines. Alas, I could not get it to work satisfactorily so I reconfigured the two spare gates as shown below.


This works upon the simple strategy that once a clear page bit has been correctly detected by 78(8), it can only be reset by the frame sync. pulses one field later, thus producing the required clear page action.

A few simple modifications which avid teletext followers may find useful are:-

i) Reduce value of C₁₆ in the analogue board from 4n7 to a value closer to 470 pF, particularly if "missing rows" are experienced. This increases the attack rate of the peak detector such that during the framing code the slice level changes by less than 5%.

ii) A spare Nand gate (e.g. 49 (4,5,6)) may be used to display rolling headers only from the selected magazine, in order to prevent the ITV/ITN characters twinkling during "roll headers".

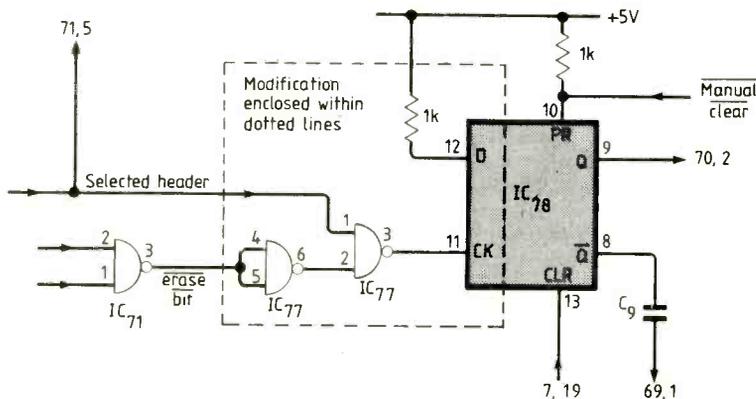iii) Of greater annoyance than (ii) are the flashing time digits on Oracle, due to a difference (at present) between magazine 200 and all other magazines. With a difference of one or two seconds, the time display gives the illusion of an incorrectly adjusted decoder, whilst greater differences are simply confusing. The cure is straight forward, 62(10) is taken from 80(4), but the time is only updated from the selected magazine, which, for example, leads to



an update every 16 seconds on Ceefax 700 magazine.

iv) If the ram disable pulse is used from IC₃₁₈(11) the page clearing function will not clear those locations where the selected page or time information is displayed. This can result in the header row changing colour during page/time selection due to the random bits stored in the rams at these locations. This can be overcome if IC₃₀₉(9) is taken from 78(9) which then ensures that Hamming bits are erased following roll or switch on.

Ken Drew
Nottingham

THE DEATH OF ELECTRIC CURRENT

Oh dear! Ivor Catt's latest letter (August) identifies him as a prime candidate for compulsory reading of Dr Scott Murray's series of articles. Then, at least, he might not confuse theories.

Classical electromagnetism, as developed by Maxwell in the 1860's, makes no appeal to the existence of the electron. For the case of a wave guided by a pair of wires, the wires determine the boundary conditions to the solution of the equations. Electrostatic theory requires that electric flux lines terminate on charges, but this is not always so for the electromagnetic wave. In any case, the classical theory of electric conduction imposes no limit on the speed of charges in the conductors - that comes from relativity theory.

So, Mr Catt is muddling models, which brings me back to the original point. Electric current and electromagnetic waves are only mechanistic models of processes which are beyond our comprehension - what Dr Scott Murray calls miracles. Hence, to say that a model does not exist is meaningless. If Mr Catt chooses not to like the electric current model that is his privilege, but it does not seriously devalue the usefulness of the model, which is judged by criteria other than credibility or personal preference.

Incidentally, M. G. Wellard may wish to note that the speed of light in water (refractive index ~ 1.33) is considerably less than that in vacuum. Cerenkov radiation is the electromagnetic equivalent of Concorde's sonic boom. Its existence (which is a fact) does not conflict with relativity. Perhaps Mr Wellard will apologize to Cerenkov.

R. T. Lamb
British Telecom
Milton Keynes

If Mr Catt's difficulties with electromagnetism are summarised by the example he gives at the end of his letter of August 82 then perhaps he can be helped.

As a pulse travels along the line the charge that terminates the electric field lines is provided by a current I . This consists of mobile electrons of charge e and if there are n such electrons per unit length of the line their velocity is $v=I/ne$. Suppose that $I=1A$ and the conductors are copper wires of 1 mm^2 cross section then, ignoring the skin effect V is about 10^{21} per cm. Thus with $e=1.6\cdot 10^{-19}C$ we have $V=6\cdot 10^{-3}\text{ cm s}^{-1}$ or $2\cdot 10^{-13}$ the velocity of light. The skin effect, for a pulse of 1 ns risetime might raise V to 2 cm s^{-1} and, if the conductor is perfect and the electronic motion is solely limited by inertia V might even be as high as 100 cm s^{-1} , so that the electrons actually have to acquire a kinetic energy of $2.5\cdot 10^{-17}\text{ eV}$ from the field.

F. N. H. Robinson
Clarendon Laboratory
Oxford

I write in response to Mr Ivor Catt's request in his letter on "The Death of Electric Current" (*W.W.* Aug. 1982).

The contradiction claimed by Mr Catt stems from his assumption that the apparent velocity with which charge moves along a conductor is the same as the velocity of individual electrons. It is well known from the free electron model of metals (see for example *Solid State Physics: Second Edition: C. Kittel, Wiley 1956*) that this is not the case. The current density, J (A/m), is given by NeV_D , where N is the number of electrons per cu. metre, e the electronic charge and V_D the drift velocity of the electrons. The drift velocity is the directed velocity component resulting from an electric field and superimposed on the thermal velocities of the electrons. The drift velocity is much less than the thermal velocity except in electric fields of very high values. The current density may be interpreted as qv , where q is the charge per unit length of conductor to sustain the electric flux of the TEM wave and v is the velocity with which the wave moves. Hence,

$$qv = NeV_D$$


and $V_D/v = q/Ne$ will be a small ratio in typical conductors. The statement that "such electrons would have to travel at the speed of light in a vacuum" is thus wrong.

Dr J. Brown, C.B.E.
Technical Director
Marconi Electronic Devices Ltd

PHASE-SHIFTING OSCILLATOR

I read with great interest the February article by Roger Rosens on a phase shifting oscillator as I developed a similar oscillator recently. A feature of this type of oscillator is that amplitude stabilization can be much simpler than usual, and the circuit exhibits no amplitude bounce as the frequency is changed. As it is necessary only to limit the amplitude of oscillation and not the loop gain - which is constant with frequency - it is not necessary to include a thermistor, and the circuit shown has been found satisfactory.

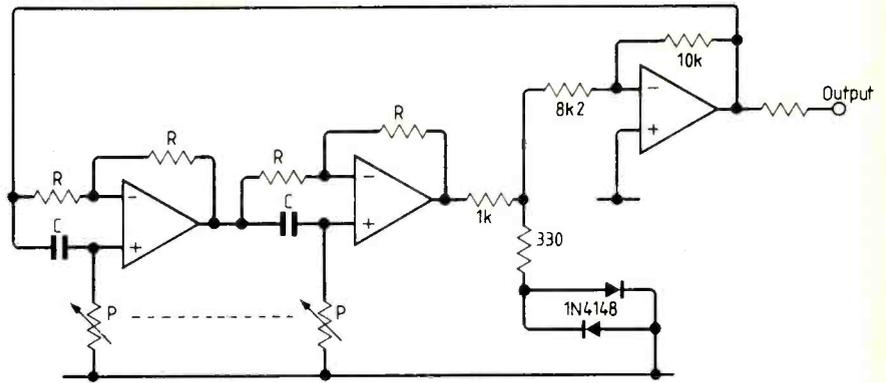This circuit is used successfully in our new high performance portable mixers, the 2000 series, giving 60Hz to 16kHz in a single sweep, at a distortion of less than 0.8%, and I have had the circuit working correctly at up to 500kHz.



Finally, another feature of this circuit, as developed by my colleague Steve Dove, is that if the loop gain is kept below unity, the circuit functions as a good bandpass filter!

Mike Law
Alice (Stancoil Ltd)

LOW-DISTORTION WIEN OSCILLATOR

With reference to Mr Linsley Hood's "New way of using Wien network . . ." in the May issue, this 'way' was described in one of my originating British patents on RC oscillators about 35 years ago. An r.f. pentode amplifier was followed by a valve phase splitter and a filament lamp was used for amplitude stabilisation. Since then, this oscillator has been continuously updated by the use of bipolars, f.e.t.s, and i.c.s for the amplifier, and thermistors, f.e.t.s, i.c.s, and opto-electronics for the amplitude stabilizer. We still think that this is the best 'way' to use a Wien bridge and are grateful for Mr Linsley Hood's enthusiastic support. As he says, quite a lot of harmonic distortion is produced at the 'input' of semiconductors and op. amps and this is made worse when using the high driving impedances that we prefer for other reasons. Our measurements of distortion on TL 072 op. amps at output voltages of about 2V are far worse than those quoted for his oscillator and we have attributed this distortion mainly to a non-true class A output stage, perhaps wrongly. It is a pity that his curve of distortion against frequency is limited by hum, as it would be interesting to see whether the worsening at the lower frequencies was mainly due to the time constant of the thermistor or the increasing drive impedance.

As a 'two for the price of one,' the voltage-controlled, variable-reactance device shown in *Circuit Ideas* in the issue November 1980 was described in my British patent, through the NRDC, about 25 years ago. The main advantages over variable-capacitance diodes are better frequency linearity and larger frequency variation due mainly to the fact that variable positive and/or negative reactance can be applied to a tuned circuit. This system allows the use of wideband swept oscillators with reasonably flat amplitude responses. It is also particularly useful for modulating the frequency of crystal-controlled oscillators. We have considered the use of this system in variable-frequency filters and would be interested to know if our New Zealand friends have also considered this.

F. G. Clifford
Wynberg
South Africa

CARTRIDGE ALIGNMENT

The letter from Mr R. J. Gilson in our August issue contained an error in the second sentence of the second paragraph, which should read "... the angular error to vary with radius . . ." - Ed.

AMATEURS AND BAND 1

G. M. Pheasant (August, 1982, page 60) expressed the hope that radio amateurs would be permitted access to the 50 MHz band when the 405-line television transmitters are withdrawn from service.

The BBC acknowledges the valuable contributions by radio amateurs to the study of propagation and wishes to encourage such activities. The Home Office and the BBC have recently discussed a proposal that exceptional permission could be given to a strictly limited number of UK radio amateurs to operate outside broadcasting hours in the 50-52 MHz band.

The BBC has no plans to continue broadcasting in Bands I and III after the existing 405-line television services have been withdrawn. The future use of these bands is being urgently considered by the Independent Review of the Radio Spectrum from 30 MHz to 960 MHz.

P. A. Laven
Assistant Head
BBC Engineering Information Department

It will be a great shame if a small portion of Band 1 isn't allocated to radio amateurs when it becomes available. This is a unique and valuable section of the spectrum for experimentation.

I propose the section 48MHz-48.6MHz, giving $48 \times 12.5\text{kHz}$ channels with the third harmonics falling in the amateur 2 metre band, and making them easily policed and identifiable. Any fourth harmonics would fall on the IBA's Ch.9 only. (As a tv technician in North Devon, I know only of one customer using this channel.)

With careful avoidance of specific local radio frequencies second harmonics shouldn't be any problem either.

These are my personal views and I welcome comment or letters of support.

John Stacey G8BXO
South Molton
Devon

MODERN PHYSICS

"Nobody ever became sunburnt as a result of exposure to a differential equation" remarks Dr Murray (The Electromagnetic Analogy, *Wireless World* August, 1982). No, but somebody may have avoided sunburn by taking note of the differential equations which describe the attenuation of ultra-violet radiation in its passage through the atmosphere and the reaction kinetics of the ozone layer. Seriously, though, there seems to be a basic misconception about the role of mathematics in physics, for its role is essentially *predictive* and in no way *explanatory*. One feeds whatever data may be available into a mathematical model and if the operation of the mathematics at least declares the input data to be mutually consistent and preferably also indicates a future state of the physical system which coincides with its actual evolution, then the mathematical model is regarded as a correct representation of the physical system.

A more fundamental and problematic question is whether every physical phenomenon can be "explained" by a mechanical analogy in which one can see a cause-and-effect relationship between the parts, of the type which occurs in the large-scale physical world and can be appreciated by our five senses. The answer appears to be negative, ever since the development of quantum mechanics, which has no parallel in ordinary large-scale mechanics. One has only to cite the application of particle/wave quality both to electrons and to photons; but worst of all, there is even doubt whether causation rules in the world of microphysics which is represented by quantum theory. At this point one has to admit that one cannot "understand" the behaviour of elementary particles in terms of mechanical models. But if one accepts the logic of mathematics, one can accept the logic of mathematical models.

D. A. Bell
Walkington
Beverley

By the end of the last century it was conceded that space contained no unique reference point.

In a book on mechanics, published in 1888, Oliver Lodge commented "No such thing as absolute rest is known, but it is convenient, in mechanics proper, to consider the earth as a body at rest". This is still the current practice and as a result we have some very funny physics and peculiar paradoxes. In his 1905 paper on moving bodies, Einstein reiterated that there is no absolute rest, adding that his theory would not require an absolutely stationary space or an ether. He then proceeded to invent his own 'stationary'. He suggested we call a set of co-ordinates the "stationary system" and then use them to define the position and movement of a point, employing rigid standards of measurement, a completely impossible task since a fictional reference point can only produce fictional position and velocity.

In fairness to Einstein it should be mentioned that every physics text extant uses the words 'the velocity of a material point' in a manner which requires whimsical decision. We are told, B has a velocity v with respect to A and so travels from B to B' a distance l , in time t , so that $l=BB'=vt$. By a simple change of mind it could be claimed with equal truth that A has a velocity v with respect to B and moves a distance $l=AA'$. This dilemma is not solved by introducing conjurers' props like co-ordinate

systems or frames of reference, inertial or otherwise.

The solution is simple. In space with no absolute rest only the separation of material bodies and the change of separation with time, can be described. Individual velocity and distance travelled must remain permanently indeterminate.

Mention would be made of Einstein's cooperative myopic observers, without whose help the theory would not have been possible. The one sitting on an imaginatively moving plank, claimed he saw a flashing lamp (A) screwed to the end of it; the other observer, riding on the declared stationary co-ordinates said he saw the lamp fastened to the x axis of his system.

Einstein's science fiction was most successful from his point of view; it earned him notoriety and a better job. How relativity theory became required reading in our universities is something I cannot understand.

Edwin Hill
Stockton
Rugby


CIRCUIT MODELLING BY HOME COMPUTER

Further to my own article appearing alongside Mr Weaver's in the August issue I compared the technique of my article using Mr Weaver's examples.

I enclose the resulting graph. It is interesting to note that whereas Mr Weaver's technique takes 75 seconds for 15 points, the enclosed graph of his Fig. 1 took 20 seconds to calculate 50 points for the same circuit, and a further minute to print the graph. This shows the undoubted power of a compiler, although the ladder technique is inherently faster than the indefinite admittance matrix technique of my article.

The ladder technique is normally superior for passive networks, but for active networks the indefinite admittance technique is essential.

R. I. Harcourt
Orpington
Kent

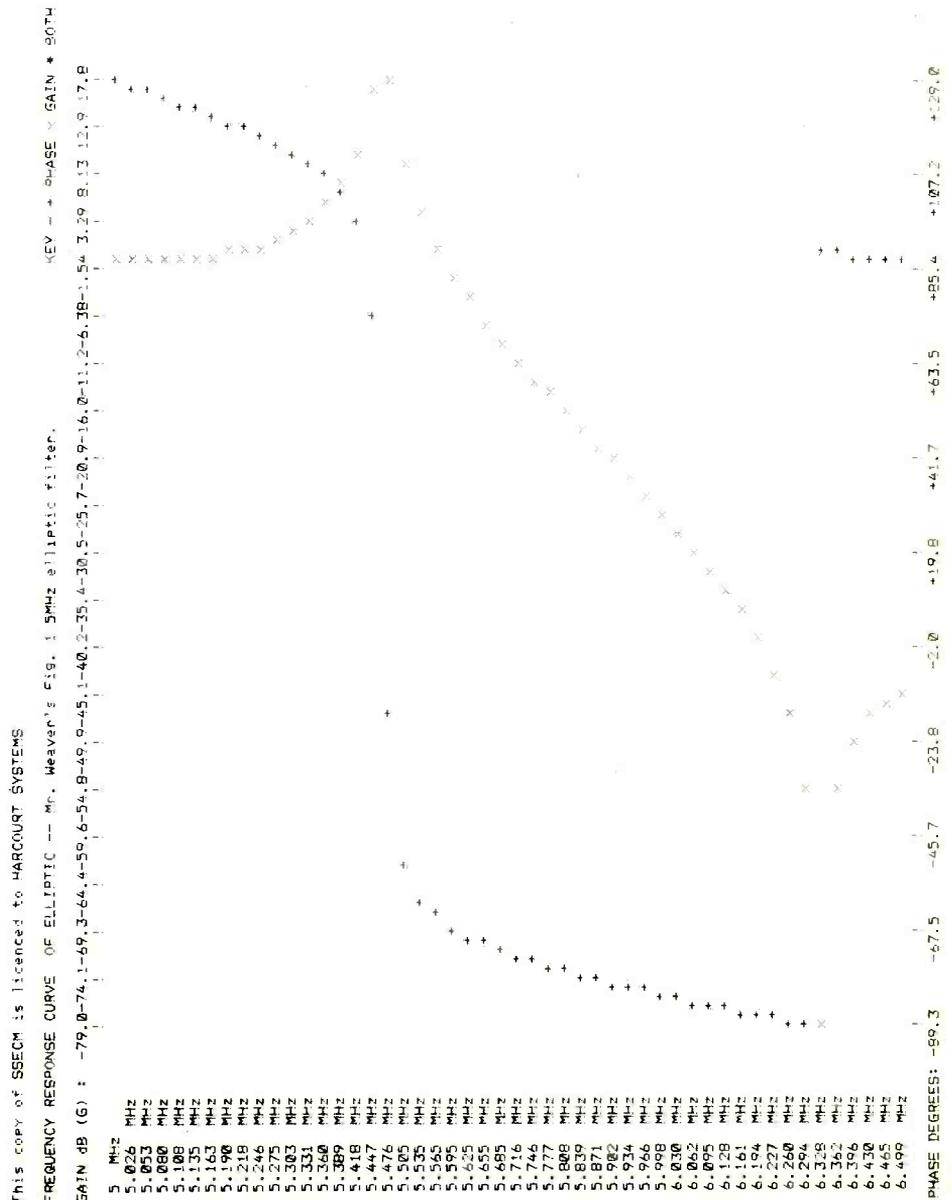

PARABOLIC ANTENNA DESIGN

Guidelines for designing and constructing parabolic antennas are presented here. Theoretical background, applications and how the prime-feed configuration is affected by reflector parameters are discussed and emphasis is given to problems that arise when constructing such an antenna using a minimum of facilities.

by M. L. Christieson*

Within the past decade or two, developments in technology caused by the demand for more frequency allocations and the need to use frequencies where background noise is less obtrusive have allowed good use of the radio spectrum above 1GHz to be made. At these frequencies reflector-type antennas come into their own. The parabolic-dish antenna — symbol of the modern communications world of satellites and microwave links — is just one variety of reflector antenna, but one with which high gains can be realized in a modest physical space, provided that it is correctly made and fed. This article discusses the theoretical background to the design and application of parabolic antennas, and how a prime-feed configuration is affected by reflector parameters.

The gain of a parabolic dish over an isotropic antenna is given by

$$G = \frac{4\pi A\eta}{\lambda^2}$$

where G is the gain in real numbers (i.e. not decibels), A is the area of the aperture, λ is the wavelength and η is the overall efficiency of the system. η is always fractional and an efficiency of greater than 0.5 is difficult to obtain.

Much information about theoretical performance can be gleaned from this equation. Gain is directly proportional to area, and therefore to the reflector-diameter's square, and is also inversely proportional to the wavelength squared, so each time the diameter is doubled, or the wavelength halved, there is a possible increase of 6dB in forward gain. A difficult figure to estimate is efficiency. Apart from a reduction in gain predicted by the equation, efficiency is reduced as the wavelength becomes a significant fraction of the dish diameter. Further reduction in efficiency is caused by the presence of the prime feed, which also obscures part of the dish aperture.

For a given frequency there is a minimum dish size below which it may well be better to examine other forms of antenna. This occurs at around 10λ although that is by no means a sharp cut off. It may be of interest to compare the dish with another type of antenna which is more common at lower frequencies. The obvious alternative to a dish is a multi-element Yagi. These are much used at u.h.f. and there is no reason why they cannot be used in the microwave bands. It

is very difficult to adjust a simple linear-element Yagi to obtain useful gain, but those with quad loops can provide excellent gain in the 1-to-3GHz region. Yagis that have more than 30 elements become inefficient and it is normal practice to stack several individual antennas. Each time the number of antennas is doubled a further 3dB is possible, but never realized, primarily because of additional loss introduced by the combiner. There is an upper limit when additional gain from further antennas is nullified by the ever more complex combiner. Parabolic dishes do not suffer from this drawback as they use a single antenna, making them the simplest type to design and adjust.

Highly directional arrays are generally used for two reasons and the type of paraboloid depends on which is more important in the particular application. The reasons are to

- reduce unwanted signals from other directions
- improve the signal from a very weak source.

The two effects are inseparable but any antenna may be optimized for one, usually at the expense of the other.

A parabolic dish may be either deep or shallow depending on the equation parameters. A deep dish obviously has its focus close to the surface while a shallow one has its focus at some distance. Rather than using the parabola equation to define

shape, it is more convenient to use the focal-length-to-diameter ratio. This ratio is very important in dish specifications. Figure 1 shows two dishes with the same diameter but with different f/d ratios. Note that because the diameter is the same, the maximum gain is the same. Dishes with a low f/d ratio, of about 0.25, are usually designed to give a high degree of side-lobe suppression while those with f/d ratios of about 0.5 are designed for optimum forward gain. The main use of the former type is in terrestrial microwave links where signal levels are quite high. For amateur work, good forward gain is usually more important and methods of optimizing this are now to be examined more fully.

For a given size of dish, it is efficiency that determines the system gain. Main factors which reduce total efficiency are

- spill-over
- aperture efficiency
- phase errors
- blocking loss.

The first three are interdependent because spill-over, the amount of energy lost when the prime feed illuminates more than the dish area, is reduced by tapering the radiation pattern towards the edge of the dish. This however reduces the aperture efficiency which is greatest when the dish is uniformly illuminated. Phase errors, which may be caused either by a poor feed or by errors in the shape of the dish, are worse if no edge taper is used.

The first consideration of the dish builder is accuracy of the paraboloid. Clearly the nearer to the ideal shape the

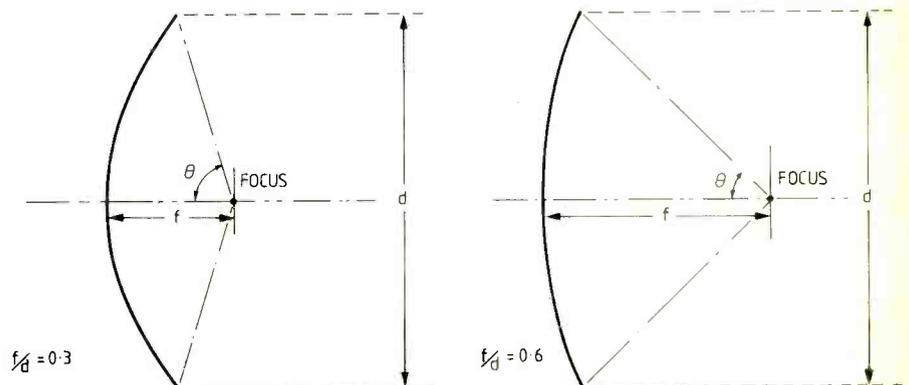


Fig. 1. Two dishes with the same diameter but with different focus-to-diameter ratios. Dishes with a low f/d ratio usually give a high degree of side-lobe suppression while those with higher f/d ratios of around 0.5 are designed for optimum forward gain.

*Feedback Instruments Ltd

better, but this is very difficult to obtain, particularly for the amateur constructor. It is generally accepted that little benefit is realized by reducing peak errors to less than $\pm 1/8$ wavelength. Sometimes this is quoted in terms of r.m.s. errors which results in a much smaller figure and may be off-putting. Peak error means that no part of the structure should be more than $\lambda/8$ in either direction away from the ideal shape, so the most serious type of error is when the dish smoothly departs from the true parabolic shape.

At 2GHz, for example, $\lambda/8$ is nearly 2cm so at the low end of the microwave spectrum there is considerable latitude for the constructor. At higher frequencies, such as those proposed for direct satellite broadcasting at 12GHz, surface errors are more of a problem.

Another factor concerning the surface is the material from which it is made. Most commercial dishes are made from spun aluminium, and clearly a solid conducting surface is ideal. For amateur purposes it is permissible to make a dish from wire mesh, providing that the holes are not too large. A good approximation is that the mesh size should not exceed $\lambda/10$. This means that various sizes of chicken wire are satisfactory at low frequencies and many good systems have been built for the 2-3GHz region using aluminium screening material. Dishes designed for operation above 10GHz should have a solid construction. The thickness need not be great; aluminium foil on a fibre-glass backing could be used. On large dishes a mesh surface reduces the wind loading and weight, although a build-up of snow or ice can demolish an installation designed on that assumption.

Feeds

Once the reflecting surface has been constructed the feed must be optimized. Referring to Fig. 1, to avoid wasting energy,

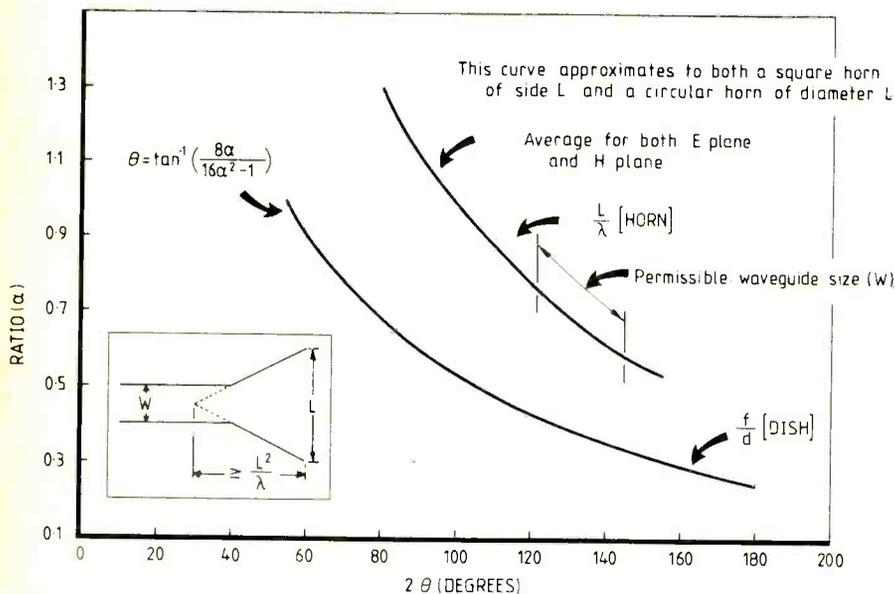


Fig. 2. Once the required f/d ratio has been judged, the dish's 2θ angle and the horn's L/λ ratio (α) can be found from this graph. There is a direct relationship between f/d ratio and 2θ angle so the f/d ratio can be chosen to ease construction of the feed. The feed is easiest to make when the 2θ angle chosen corresponds with the waveguide opening. Approximate relationships between these parameters are shown here.

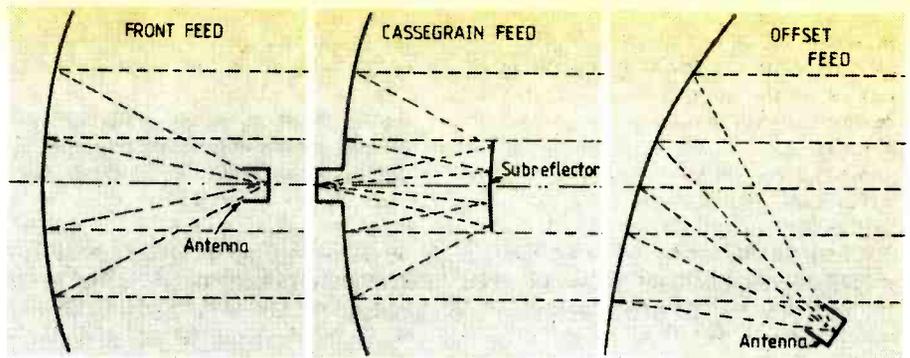


Fig. 3. Basic front-feed parabolic antenna and two variations. Cassegrain feed is used for antennas with unfavourable f/d ratios, but subreflector obscures part of the dish, causing problems with small antennas. The offset feed gives no blocking problems but is difficult to construct as the dish is neither symmetrical nor parabolic.

the radiation pattern of the prime feed should all be within a solid angle of $2\theta^\circ$. It is easier to visualize this in terms of a transmitting antenna but the same applies to a receiver. Ideally the radiation should be uniform over that area and then cut off sharply at the edge. This is impossible in practice and the compromise often used in amateur projects is a 10dB-beam width of $2\theta^\circ$.

This is difficult to achieve for 2θ angle greater than about 150° because at that point the horn aperture required becomes smaller than the waveguide capable of supporting wave transmission. A simple dipole and splash plate (reflector disc) could be used but it is difficult to adjust and its performance never equals that of a horn. It is convenient to arrange the 2θ angle to correspond with the pattern from the open end of a square or circular waveguide: this simplifies construction considerably. There is a direct relationship between f/d ratio and 2θ angle so that the f/d ratio can be chosen to ease the construction of an efficient feed. This type of work cannot be exact without specialized test

equipment, but it is surprising how efficient a system designed using these rules of thumb can be. Figure 2 shows the approximate relationships between these parameters. There have been several good designs for high-efficiency feeds developed by amateur radio operators, some of which are referred to at the end of this article.

Problems of feeding a dish with an unfavourable f/d ratio can be reduced by using a hyperboloid sub-reflector and feeding the dish from behind. This is called a Cassegrain feed and is shown in Fig. 3. The disadvantage of this is that the diameter of the sub-reflector needs to be several wavelengths, depending on its position, and so it obscures part of the dish area. This blocking loss also occurs with front fed systems and is a factor worth considering when dealing with a small dish. Larger dishes have much greater surface areas compared with their associated sub-reflectors, and Cassegrain feeds are common on communication-satellite earth stations.

One method of preventing blocking loss is to use an offset feed, also shown in Fig. 3. Although an improvement in efficiency would be obtained using this method, it is not easy to construct as the dish is no longer symmetrical or paraboloid, which makes it particularly unsuitable for amateur construction.

Another loss which may occur is polarization loss, where the polarization of the incoming signal is not matched to that of the prime feed. High loss can occur when two linear polarizations are crossed. A linear to circular mismatch will usually result in a 3dB loss, but between left- and right-hand circular polarization a high degree of isolation is possible. This effect may be exploited to re-use frequencies on the same satellite. It is worth remembering that, when reflected from the dish surface, the sense of a circularly-polarized wave is reversed.

The method by which the dish is mounted depends on its use. In some applications it is not necessary to move it, as in a ground microwave link for example. Many dishes are used with geostationary satellites which only move a small amount each day. This small movement, which is non-cumulative, is often within the beam-width of the dish so a simple fixed mounting will suffice. Where very-high gains are

required it may be necessary to use some form of automatic-tracking system. These can be simple or complex and a decision between performance and cost is not easy to make.

Many methods have been used to construct paraboloidal dishes and the exact method depends on the facilities available. Most traditional methods rely on the reflecting surface being supported by struts or pulled into shape by nylon cord. These struts can be made from metal or wood providing that it is well protected. A method that is beginning to find favour, particularly for higher frequencies, is a glass-fibre shell with a thin conductive surface which is sometimes sprayed on. Once a former has been made several dishes can be cast, so it might be worth several individuals combining their skills. A fibre dish has the overwhelming advantage of being very light but it may need to be made with a turn-over at the rim to prevent it distorting when mounted.

Any system designed for outside use must be protected against weather. Reference has already been made to the effect of

snow and ice, but excessive heat can be equally damaging. At high frequencies, dimensional changes due to temperature can be a considerable problem as can distortion caused by a gust of wind, but these effects are not often noticeable on small dishes. Front-fed systems can also focus the sun's heat on the prime feed. It would be slightly annoying to see an expensive amplifier burst into flames on the first sunny day. If the amplifier is located at the feed the rain must be kept out of it by using a sealed container, preferably with a desiccator. My view is that if rain cannot be kept out it is far better to have a semi-open cover to make sure it runs out again. Precautions such as mounting the amplifier upside down so that water cannot collect in it, and a supply of plastic dustbin liners have kept several amplifiers operational for a number of years.

It is hoped that these ideas have equipped readers with the knowledge to start designing and building dish antennas with a reasonable trade-off between performance and economics. It is likely that with the interest in satellite television

many more articles will appear describing individual practical designs; they will however all be based on the basic design parameters outlined here. **WW**

Further reading

- The ARRL Antenna Book, American Radio Relay League (latest edition)
- Performances of Fixed-Mount Earth-Station Antennas, S. E. Dinwiddy, *ESA Journal 81/3*
- Gain-Beamwidth Product and other Reflector-Antenna Relationships, A Saitto, *ESA Journal 81/3*
- Tubular Radiator for Parabolic Antennas, *VHF Communications 4/1976*, Verlag UKW-Berichte
- A Dish Anyone Can Build, Michael Brown, *73 Magazine*, February 1982
- VHF-UHF Handbook, RSGB
- Pyramidal Horn Feeds for Parabolic Dishes, D. Evans, *Radio Communications* March 1975
- Dish Antenna, D. Wardley, *Break-in*, May 1982
- Reference Data for Radio Engineers, Sections 25 and 27, Sams

PROGRAMMABLE GPIB-TO-SERIAL INTERFACE

Development of an earlier interface with talker/listener capability to remotely program functions within the instrument interface.

The original interface design (see panel) was extended to accommodate a secondary addressing feature to allow remote initialization of the uart control register, the instrument data speed generator, load an end-of-message byte into a latched comparator, and address the instrument as a GPIB/RS232C interface. These remote programmable facilities permit the designer to dispense with some of the switch packs used in the first design, adding a degree of programmable flexibility.

On any one contiguous bus up to 15 devices are permitted, but the primary address range is 31 talk and 31 listen addresses using single byte addressing. A controller may issue a primary address to identify an instrument then issue a secondary address to identify a function within that instrument. For example, before an instrument can be operated effectively it may require initialization and range information, which could be programmed into latches selected by unique secondary addresses (Table 3 shows the range of addresses). When the controller issues the primary address over the bus the instru-

by Chris Jay

The GPIB-to-serial interface featured in the July 82 issue of *WW* was conceived as a low-cost interface solution for instruments with a serial data link such as an RS232C port. When configured to a keyboard and addressed as a talker, characters typed on the keys are converted by the interface from serial to parallel data and transmitted over the bus data lines. A printer interfaced to the bus is addressed as a listener; data bytes received are serially encoded and fed to the serial input port of the printer. The interface used 13 i.c.s including a 96LS488 to perform interface functions and message decoding, an IM6402 uart for the serial/parallel encoding of data, and an MC14411 as a frequency reference for serial transmission and reception at four link-selectable rates. During the talker-active state the interface could automatically recognize an end-of-text character, and assert the EOI line concurrent with the transmission of the final data byte in the character string. A 74F521 octal comparator achieved this by comparing the binary data waiting for transmission with an 8-bit data pattern set with switches.

ment will be conditioned to receive a one-of-four secondary address. For example, my listen address followed by my secondary address 1 (MSA 1) selects the instruments control register, MSA 2 selects the instrument data rate register, and MSA 3 selects an octal latched comparator so a unique end-of-text code may be programmed¹. MSA 0 is the secondary listen address that selects the uart transmit buffer register. When addressed into the listener active state, data bytes sent to the uart are serially encoded and transmitted to the RS232C interface at a programmed speed and in the character format specified by the uart control register.

The 96LS488 may be configured for extended addressing by wire-linking the mode inputs M0-3 to the appropriate binary code as shown in Table 2 on page 72 of the July article. There are five choices of extended addressing but for a talker/listener there are two choices of TE/LE low

1. The end-of-message latched comparator is used when the interface is an active talker. A string of data bytes may be sent over the bus, terminated by the unique end-of-text character. When this character is transmitted the comparator automatically recognizes the bit pattern and asserts the bus end-or-identify (EOI) line to indicate end-of-message.

*Chris Jay was formerly with the Fairchild European Design Centre, Bristol and is now working at Marion Electronics, in Stroud.

speed, or TE/LE high speed. The choice of high speed is selected for instruments using three-state driver devices; in this design the mode inputs M0-3 are all configured to V_{cc} .

Table 4 illustrates a typical initialization procedure that should be completed by the controller-in-charge (c.i.c.) prior to the interface becoming an active talker. It does this by asserting the ATN management line; any current active talker relinquishes control of the bus lines. The first message issued is the unlisten command to ensure that unscheduled listeners do not receive data bytes intended for the interface circuit. To address the interface the c.i.c. issues the primary listen address (MLA); after receipt the interface expects to see one of its four secondary addresses. Assuming that the uart control register is to be initialized first, the controller sends MSA 1. When selected, the register is capable of receiving a data byte (DAB 1) over the bus lines. The control register is a five-bit latch in the 6402 uart; format of the control-bit pattern is shown in Table 6a. If the c.i.c. addresses itself as talker it can release the assertion on ATN and send the initializing data byte to the instrument. After sending DAB 1 it regains control of the bus by asserting ATN.

It is necessary to un-address the control register by sending the unlisten message before sending the primary listen address of the interface, followed by the secondary address MSA 2 to select the data-rate generator latch. The controller releases the true assertion of ATN and as an active talker issues DAB 2 to program the correct speed code - Table 6b gives the format. When the data byte has been sent, it re-asserts the ATN line to regain control of the bus and complete initialization. The unlisten command is sent followed by MLA and MSA 3 which selects the end-of-message latched comparator. When selected the controller releases the true assertion of ATN to send the end-of-message byte DAB 3. When latched it re-asserts the ATN line, sends the unlisten command to unaddress the latched comparator and then sends the talk address of the interface (MTA), followed by the secondary address MSA 0 of the receiver register. The controller addresses the listeners by sequentially transmitting each listen address. On completion of addressing the controller releases the assertion in ATN, enabling the interface to enter the talker active state for transmission of data bytes².

In the circuit configuration of the programmable interface, the 96LS488 handles the interface functions and message decoding. An Intersil IM4602 uart converts parallel data to serial and serial to parallel and an MC14411 bit rate generator

Table 1. Talk and listen address assignment

DIO ₈	DIO ₇	DIO ₆	DIO ₅	DIO ₄	DIO ₃	DIO ₂	DIO ₁	
X	H	L	\bar{A}_5	\bar{A}_4	\bar{A}_3	\bar{A}_2	\bar{A}_1	Primary listen address
X	H	L	\bar{L}	\bar{L}	\bar{L}	\bar{L}	\bar{L}	Unlisten
X	L	H	\bar{A}_5	\bar{A}_4	\bar{A}_3	\bar{A}_2	\bar{A}_1	Primary talk address
X	L	H	\bar{L}	\bar{L}	\bar{L}	\bar{L}	\bar{L}	Untalk
X	L	L	\bar{S}_5	\bar{S}_4	\bar{S}_3	\bar{S}_2	\bar{S}_1	Secondary address

gives a wide range of frequencies for rate generation³. Other logic circuits used are 74LS t.t.l. devices and two 74F i.cs, one of which is an inverting bus driver to buffer the cmos outputs from the uart onto the bus data lines because it satisfies the 48mA sinking requirement by the IEEE 488A specification. The μ A1488 and μ A1489 provide signal conditioning for RS232C line driving and reception.

Addressing

Secondary addressing is achieved by the quad two-to-one multiplexers of IC₁₁, 74LS157, which select the primary and secondary addresses. The 96LS488 ASEL output is low when the primary address is being received, and high for secondary address selection. Address inputs A1-4 of the 96LS488 are driven by the 74LS157 multiplexer outputs which select a one-of-four binary code set by switches 2-5. Note that A5 is configured directly to switch 1; this effectively reduces the secondary address range to 496 but saves on the multiplexing hardware. The primary address range of the interface is therefore configured on the switches 1-5. Secondary addressing is achieved when ASEL drives the select input of IC₁₁ high. The bit pattern on switches 6 & 7 routes through to the inputs A4 & 3. Address inputs A1 & 2 are derived from the bus data lines 1 & 2 respectively. So a one-of-four secondary address will select the interface, putting it into the talker or listener-addressed state. On receipt of the secondary listen or talk address the 96LS488 outputs \bar{LAD} or \bar{TAD} go low producing a rising edge at the output of gate 1, connected to the clock input of IC₇, a dual D-type latch.

So the logic state on inverted data lines 1 & 2 is strobed into the 74LS74 latch when the instrument is addressed. A one-of-four logic condition is stored, enabling the instrument to receive a data byte which can be sent to either the uart transmitter, uart control register, bit rate generator latch, or the EOI end-message comparator latch. When statized the information remains programmed until the instrument is un-addressed then re-addressed. The Q outputs of the 74LS74 latches are wired to the address inputs of IC₈, a dual one-of-four demultiplexer 74LS139. Outputs of IC_{8a} route the RXST signal to the selected latch or register; IC_{8b} outputs O0 and O3 are used as enable signals $\bar{ENBL0}$ and $\bar{ENBL3}$. Signal $\bar{ENBL0}$ drives the S input of IC₁₂, a quarter of 74LS157, which selects the correct handshake for the one-of-four instrument functions. The $\bar{ENBL3}$ IC_{8b} output, selects the load function at the S0 and S1 inputs of the 74F524 latched comparator.

Table 2. Status codes

TAD	LAD	D/S/E	State
H	H	L	Off line
H	L	L	Addressed to listen (LADS)
L	H	L	Addressed to talk (TADS)
L	H	H	Serial poll mode (SPM)
H	L	H	Receiving end-message (LACS)

DRB goes low when the interface is in talker active or serial-poll active state.

Status decoding

To perform the necessary interface status decoding the 96LS488 \bar{LAD} , \bar{TAD} and DRB outputs drive the A2, A1, A0 inputs of a 74LS138, one-of-eight decoder, IC₉. Output O2 of IC₉ will be active low when the interface is either in the talker active state, or the serial poll active state, see Table 2 for status codes. Gate 2 is enabled by the D/S/E signal to provide a low output when the instrument is talker-active. The $\bar{D/S/E}$ signal when inverted by I₃, provides an enabling low for the input of gate 3. The gate 3 output goes low when the interface enters the serial poll active state. These or-gate outputs and the output O5 of IC₉ are labelled $\bar{TACSENBF}$, $\bar{SPASENBF}$ and $\bar{LACSENBF}$ and used as low enable inputs for the three-state buffer-drivers. When talker-active the 6402 receiver buffer register outputs, buffer devices IC₄ and I₁₃ (the EOI driver circuit) are enabled. During the serial poll, one half of IC₁₀ is enabled to drive data lines 1 to 3 with status bits and a second EOI buffer driver is enabled. During the listener active state the 74LS240, IC₃ (input buffer) is enabled. Appendix 2 gives a brief description of serial and parallel poll.

Buffering

Although the 96LS488 data lines are connected to the bus, it is necessary to use buffer circuits (with hysteresis inputs essential for the listener function) to provide a data path to or from the instrument's internal logic circuitry. An internal instrument bus, eight bits wide, is isolated from the bus data lines by inverting LS240 and F240, IC 3 & 4 respectively. It is also necessary to use hysteresis buffering and inversion to the address multiplexer IC₁₁, achieved by the two inverters I₁ and I₂, of a 74LS14. The 74LS240 will be enabled by $\bar{LACSENBF}$, going low when the instrument is listener active. In this state, the octal inverter drives the internal instrument bus with valid data. The IM6402 receive buffer register is disabled so no data conflict occurs on the internal bus. During the talker-active state, the IM6402 r.r.d. input is driven low by $\bar{TACSENBF}$, which also enables 74F240 buffer circuit.

2. Data is transmitted in ASCII, a seven-bit code representation, with the eighth bit for parity checking.

3. Both the MC14411 and IM6402 devices are cmos requiring a V_{IH} of $V_{cc}-2$ volts. The 74LS outputs have a guaranteed VOH of 2.7V for a V_{cc} of 5 volts. To ensure good noise immunity provide passive pull-up resistors of 2.2k Ω on each LS output that drives a cmos input.

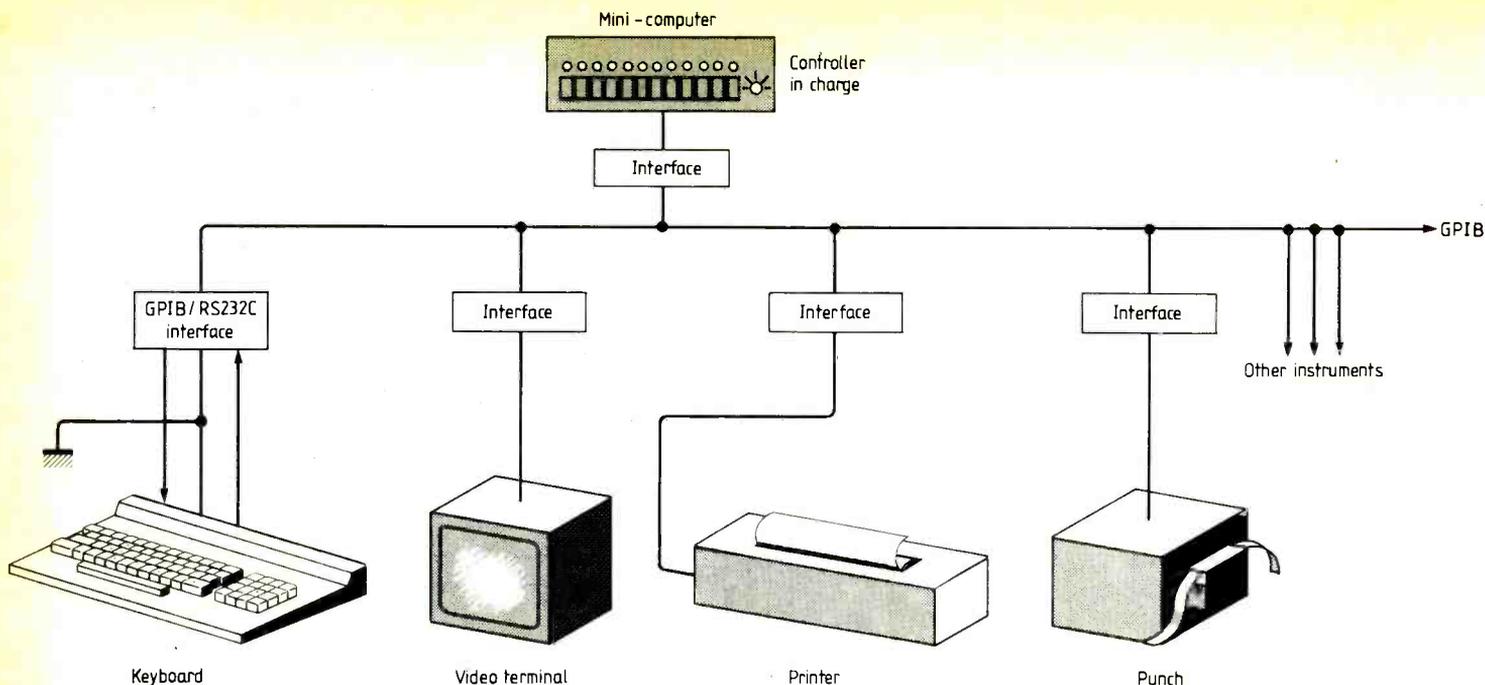


Table 3. Primary and secondary address of the interface.

MLA	My listen address, primary listen address of the instrument
MSA 0	My secondary address for g.p.i.b. uart, to provide serial/parallel conversion of data
MSA 1	My secondary address for uart control register
MSA 2	My secondary address for bit rate generator latch
MSA 3	My secondary address for end-of-message latched comparator
MTA	My talk address, primary talk address for the g.p.i.b./RS232C instrument
MSA 0	My secondary address for g.p.i.b./uart, to provide parallel/serial conversion of data
MSA 1	
MSA 2	Not used
MSA 3	

Table 4. Interface initialization procedure and talker addressing.

ATN	MSG	FUNCTION
1	UNL	Unlisten to clear the bus of listeners
1	MLA	Listen address of the instrument
1	MSA 1	Address of uart, control register
0	DAB 1	Issue the uart control register byte
1	UNL	Unlisten the control register
1	MLA	Listen address of the instrument
1	MSA 2	Address of data Speed control latch
0	DAB 2	Issue the data speed control byte
1	UNL	Unlisten the speed control latch
1	MLA	Send listen address of the instrument
1	MSA 3	Send address of the end-message latched comparator
0	DAB 3	Send end-of-message byte to the latched comparator
1	UNL	Unlisten the 'end-of-message' comparator
1	MTA	Send talk address of instrument
1	MSA 0	Send secondary address of uart
1	MLA 1	
1	MLA 1	Address listeners on to the bus.
1	MLA 1	
1	MLA n	
0	DAB	Instrument addressed as a talker, sends first data byte.
0	DAB	
0	DAB	

This establishes the data path from the RB1-8 outputs to the data bus.

Loading registers from internal bus

On receipt of MLA followed by MSA 1 the Instrument latches the binary code of 01 into IC₇ which drives the A1, A0 inputs of IC₈. Signal ENBL₀ drives the S input of IC₁₂ high, selecting the RXST to RXRDY

handshake through inverter I₅, multiplexer IC_{8a} onto the STB1 input of AG₃. The output of AG₃ drives the selected input I_{1a} of IC₁₂, and the output Za drives the RXRDY 96LS488 input. This local automatic handshake path is identical for STB2 and STB3. In the acceptor data state a data byte present on the data lines, inverted by IC₃ onto the internal instrument bus, is clocked into the uart control

register, data bits one to five, as RXST drives the control register load input high via the path through I₅, output O1 of IC_{8a} and inverter I₁₂. The bit rate generator latch is loaded in a similar manner. When the interface receives UNL, MLA followed by MSA 2, the binary code 10 is latched into IC₇. The A1 and A0 address inputs of IC₈ select output O2 of the decoders. In the acceptor-data state the rising edge of the RXST output clocks the CP input of IC₁₃, 74LS374 through the path I₅, O2 of IC_{8a} and I₄. The RXST/RXRDY handshake is achieved automatically, as described for the loading of the u.a.r.t. control register. Data present on the internal instrument bus, bits one to three of IC₁₃ are clocked through to the Q outputs on the rising edge at the CP input. The bit rate generator latch, IC₁₃, uses three of the eight internal D-type flip-flops, the other five latches are available for functional expansion. The latched code on Q0-2 outputs are used to select clock frequencies for the u.a.r.t. and inputs. See Table 5b for code input versus bit rate selection; the frequency input is 16 times the data rate. The Q0 output of IC₁₃ selects either the F3 or F7 outputs from the clock generator chip IC₆. When high, the clock output F3 is selected through the multiplexer circuit comprising OG3, OG4 and AG₂. When low the F7 clock output is selected. The Q1 and Q2 74LS374 outputs select an internal divider in IC₆, which provide the clock outputs in Table 5 (part 2). To provide a good stable frequency source for the MC14411 it is necessary to connect a 1.8432 MHz crystal to the crystal inputs.

If the instrument is to be used as a talker it will be necessary to load the EOI latched comparator. The select inputs of IC₅ are enabled high by the inversion of ENBL₃, the O3 output of 74LS139 IC_{8b}. This output goes low when MSA 3 is received. Inverted by I₁₁, it drives the select inputs S0 and S1 of the 74F524 latched comparator high.

To be continued

EPROM EMULATOR

by Peter Nicholls, M.A.

Shown here is the software for the eprom emulator featured on page 83 of last month's *Wireless World*. This emulator, based on the 8060 microprocessor, has its own hexadecimal keyboard/display and uses two memory ICs, one rom and the other ram, a parallel-interface adapter and three 'LS' c.t.l. devices.

These and a handful of other components, including batteries for memory retention and cassette-interface components, may be mounted on a single-sided board measuring 233 x 220mm. Photo-copies of an overlay used to produce such a p.c.b. can be obtained by sending an s.a.e. to *Wireless World* Emulator.

Room L303, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Fully etched but undrilled fibre-glass boards, also single-sided, and programmed eproms for the emulator are available from PKG Electronics, Oak Lodge, Tansley, Derbyshire at £8 and £5 respectively.

Prices include vat, postage and packing. Referring to last month's article, Fig. 4, C4 should be replaced by a 100nF polyester type to avoid leakage-current problems. In Fig. 5, R32-35 are 47kΩ and, of course, digits 2 and 6 are not used and will confuse the display if connected. We apologize for these inaccuracies.

08 C4 08 36 C4 00 32 C4 07 35 C4 60 31 C4 00 C9
 C4 C4 FF C9 C2 C4 07 C9 C3 C4 20 C9 28 C4 05 37
 C4 17 33 3F C4 05 37 C4 00 33 3F C1 C1 D4 98 E4
 98 9C 02 90 F5 C1 C1 C9 23 3F C1 C1 E1 23 D4 07
 9C F7 C1 C1 D4 98 E4 98 98 02 90 ED 8F 01 C1 23
 94 22 C1 21 1C 1C 1C 1C DC 08 C9 20 C1 21 1E 1E
 1E 1E D4 F0 C9 21 C1 23 D4 0F D9 21 C9 21 32 C1
 20 36 90 A9 E4 18 9C 06 C4 20 C9 28 90 A6 C1 23
 E4 1A 9C 0E C6 01 C4 05 37 C4 17 33 3F 90 17 C1
 11 C1 23 E4 19 9C 7A C4 21 C9 28 C4 05 37 C4 00 33
 12 3F C1 C1 D4 98 E4 98 9C 02 90 F5 C1 C1 C9 23 3F
 13 C1 C1 E1 23 D4 07 9C F7 C1 C1 D4 98 E4 98 02
 14 90 ED 8F 01 C1 23 94 9C D4 0F C9 23 C2 00 1E 1E
 15 1E 1E D4 F0 D9 23 C4 00 C4 05 37 C4 4E 33 3F 90
 16 B9 FF
 17 FF
 18 FF
 19 C1 23 E4 1C 9C 7A C4 07 C9 C0 C4 00 C9 C1 C4 05
 20 C9 31 C1 C1 30 98 0C C4 AA 01 69 30 9C 03 C4 69 01
 21 90 08 C6 01 01 C1 31 60 C9 31 3F 8F 00 3F 8F 00
 22 3F 8F 00 3F
 23 36 D4 0F 98 05 08 08 36 C4 01 30 9F
 24 32 C4 12 C9 2E C4 04 48 C9 2E C4 07 C9
 25 2F C4 7F C9 28 C9 2A C9 30 C1 31 01 90 BC FF FF
 26 2F C4 7F C9 28 C9 2A C9 30 C1 31 01 90 BC FF FF
 27 C1 23 E4 1D 9C 6D C4 2F C9 C0 C4 00 C9 C1 C4 05

28 37 C4 C0 33 C4 08 36 C4 00 32 C4 30 C9 30 3F C4
 29 AA 60 98 05 C4 55 60 9C F1 B9 30 9C F1 3F C4 69
 30 60 9C FA 3F
 31 36 90 F0 C4 08 36 3F
 32 36 98 03 36 90 F8 36 E4 AA 9C 1A C4 2F C9 28 C4
 33 04 C9 2C C4 27 C9 2E C4 21 C9 2F C4 7F C9 28 C9
 34 2A 93 12 90 19 C4 2F C9 2E C9 2C C9 2F C4 06 C9
 35 2A C4 23 C9 2E C4 7F C9 28 90 E6 08 08 C1 23
 36 E4 1F 9C 6D C4 02 07 C4 20 C9 30 8F 40 C1 C1 E4
 37 9F 9C 40 B9 30 9C F4 C4 04 C9 C0 C4 00 C9 C1 C4
 38 08 36 C4 00 32 C6 01 36 D4 0F 98 05 36 8F 02 90
 39 F4 C4 00 07 C4 03 C9 2A C4 63 C9 2B C4 2F C9 2C
 40 C4 2E C9 2E C4 07 C9 2F C4 7F C9 28 C4 05 37 C4
 41 D2 33 3F C4 0E C9 C0 C4 00 C9 C1 36 C9 30 36 32
 42 C9 31 32 C4 FF CE 01 36 D4 0F 98 07 36 8F 02 90
 43 F4 90 1D C4 08 36 C6 01 8F 02 32 01 C1 31 60 98
 44 04 01 32 90 F1 36 01 C1 30 60 98 A5 01 36 90 E6
 45 C4 00 37 C4 00 33 3F
 46 FF
 47
 48
 49
 1000

UK nearer to US tv encryption

Racal Electronics plc and Oak Industries Inc. of California are to form a joint company "to exploit the anticipated explosive growth of pay television services following the expansion of cable and satellite service in the UK and Europe". The new 50:50 company is formed in anticipation of Government support for the operation of cable systems for television programme distribution before the end of the year.

Although based on the UK the new company, Racal-Oak Communications, will have a mandate covering the whole of Europe, and in addition to producing equipment the joint venture will also seek to operate, license and supply pay television systems.

Commenting on the announcement, Sir Ernest Harrison, chairman and chief executive of Racal Electronics, said: "The potential in the UK alone is exciting, but total European demand is huge. Oak's imported technology will provide an opportunity to build a new and important export business. The pay television business can be measured in billions of pounds over the next 20 years and the UK must win its share". Kenneth Baker MP, Minister for information technology, said of the deal: "There have been several contacts over the years between Oak and the Government. Most recently I met Mr Carter, Oak's Chairman and Chief executive, in June when he told me of his interest expanding Oak's European interests. I am delighted that he has decided to bring Oak's technological expertise in encryption technology to the UK."

Founded in 1932, Oak Industries evolved from a manufacturer of radio switches and television tuners into a diversified supplier of products and services in electronics. In 1977, Oak's first year in the entertainment business, it started over-the-air subscription television in Los Angeles and now owns five systems in the US with around 600,000 subscribers and a turnover of \$500 million. Oak developed both the hardware and computer software to manage the systems and later adapted its software for pay cable television. It claims to be the only cable tv manufacturer which supplies all the software necessary for a pay television operation, and produces converters for American cable television, computer-addressable converter and decoders and decoders for pay cable and subscription tv.

It developed an encoding and decoding technique for satellite television signals called Orion, a more sophisticated version of the encryption technology for subscription tv. Over 8,000 Orion decoders are already in use or on order in Canada and deliveries have recently begun to Satellite TV pic (see "Cryptic satellite tv"). Through a subsidiary it is also a major supplier of programming for both pay cable and subscription television, comprising recently-released movies, sports, concerts, comedy, dramatic productions and other entertainment special events.

Last July, Oak filed an application with the FCC to construct, launch and operate communications satellites to eventually serve all four US time zones.

world first in being the first national 11GHz high-capacity digital link and yet it was largely ignored in the press. The network will cover routes from London to various points in the UK including earth stations at Goonhilly and Madley and forms part of BT's plan to convert the entire UK telecommunications to digital operation by the early 1990s. Ironically, at 140M bit/s the capacity is far greater than the new fuss-making light-fibre link of 34Mbit/s.

Electronics for peace


Two electronics engineers who are concerned at the involvement of the electronics industry in the arms trade and the nuclear arms race are intending to do something about it. They plan to set up a network to link those in the industry who feel that their skills should not be used in the cause of war, nuclear or conventional. Possible functions of this network would be to encourage conversion of military electronics research, development and production to creative and socially useful purposes; to stimulate discussion and where possible disseminate information on military electronics and constructive alternatives, both within the industry and among the general public; and to provide technical advice and information where appropriate to the peace movement.

They propose a preliminary meeting in November, in or near London, to discuss the aims and structure of the network. Interested engineers should contact either Tim Williams, Weir Cottage, The Dens, Wadhurst, East Sussex or Steve Holmes, 151 Courthouse Road, Maidenhead, Berks for further details of the meeting.

Digital radio outshines lightline

The fanfare surrounding BT's ceremonial opening of its longest fibre route last July was well justified. The BICC 8-fibre line between London and Birmingham took only nine months to install and is the longest BT fibre route at 204km. Though only two fibre pairs are currently operating, at 34Mbit/s, the other two pairs will be brought into use next year at 140Mbit/s. More significant perhaps is that it is the first to operate at the long wavelength of 1300nm, using high radiance l.e.d.s instead of the more expensive lasers. At 1.5dB/km loss they have lower attenuation than the earlier 850nm systems and allow repeaters at 10km intervals instead of 8km.

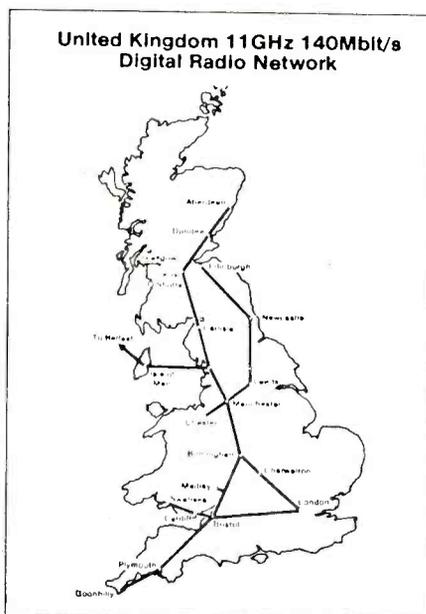It's interesting timing in view of the Project Mercury London to Birmingham announcement. But what BT didn't sing about was the fact that only the day before GEC had announced the start of a multi-million pound digital network with steam radio, albeit using q.p.s.k. This was a




Coinciding with the London to Birmingham Mercury project, BT open 34Mbit/s optical fibre and 140Mbit/s digital microwave links.

Forth they went, together

The designers of Britain's latest microcomputer have chosen the Forth programming language in a bid to gain advantage in the crowding micro market. They claim its principles are so simple that newcomers to computing need only a few minutes to learn how to calculate, and at the same time, it is easy to invent extensions to the language. The two originators of the Jupiter Ace computer, Steven Vickers and Richard Altwasser (see caption), both discovered Forth at the same time (they read the same issue of Byte) and immediately recognised it, they say, as the ideal language for microcomputers.

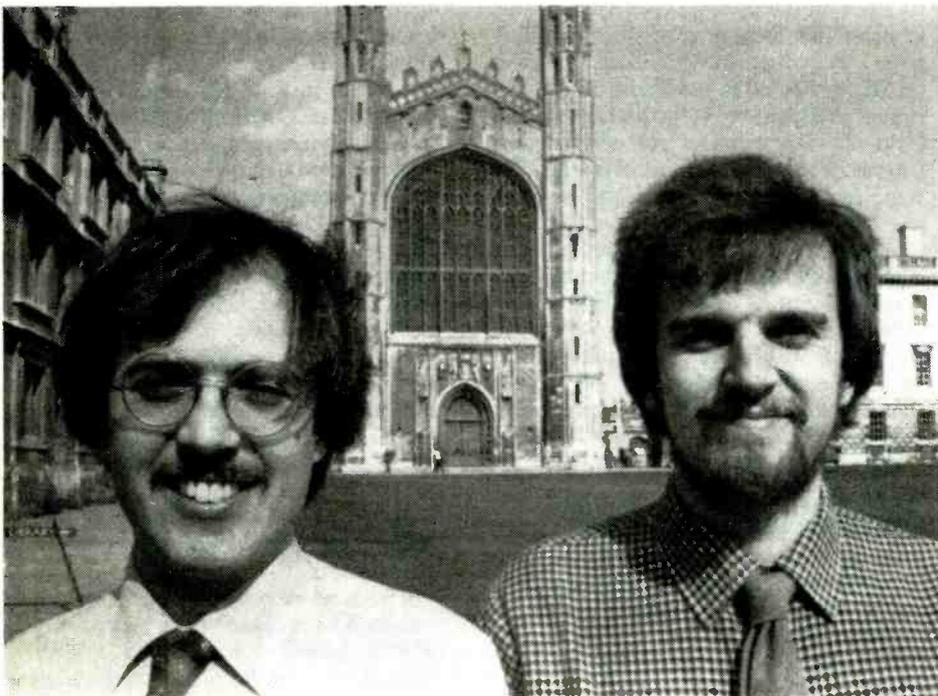Forth is fast and easier to write in as well as more compact in memory because it is



"Leading computer designers with a reputation for pushing technology forwards" is how Altwasser and Vickers describe themselves in their promotional copy for their new computer. Vickers, left, who previously had joined a software consultancy near Cambridge with a doctorate in algebra, adapted the 4K ZX80 rom into an 8K for the ZX81. He wrote the manual for the ZX81 as well as most of the Spectrum rom. Altwasser, an engineering graduate, worked on the application of microprocessors in automation before joining Sinclair. He was soon made responsible for computer research which included the hardware development of the Spectrum. "It's about time someone got away from Basic" says Vickers. Developed in 1965, it was then a lot easier to use than Fortran. "But it is hardly the language of the future; our money is on Forth".

compiled, yet its compiled code is accessible to the user in the simplest way possible, say Jupiter. One gives each compiled routine a name, a Forth word, and to run it just type in the word.

Stringing old words together can define new words, which process lies at the root of Forth's power and enables one to define an infinite variety of one's own words from the standard words provided in the

firmware. Older languages make assumptions about how they will be used that inevitably lead to a straight-jacket for the programmer; Forth is not based on any such assumptions they argue and allows the programmer "to do absolutely anything". If one doesn't have exactly the instruction needed in Forth, it is simply invented.

Forth usually relies on disc-based virtual



First shown at last month's Personal Computer Show at London's Barbican Centre, this £90 mail-order computer features full-size keyboard, user-defined high resolution graphics, programmable sound generator, upper and lower-case ascii characters, 24x32 flicker-free display, 1500baud cassette interface, and the Forth language. Jupiter Cantab are at 22 Foxhollow, Bar Hill, Cambridge, tel 0954 80437.

memory for editing the source program but the designers say unique editing facilities operating on the compiled word definitions mean that words can be defined, listed, debugged, edited and redefined without using any external storage. This they say makes Forth even easier to use on the Ace than on other implementations.

The memory saving coded form used to store programs allows it to work much faster than it would do in another language the company say – typically in less than a tenth of the time, which makes it ideal for games. Capacity is 8Kbytes of rom and 3K of ram but because of the language it is more effective than, say, the 1K memory of the ZX81. Expansion to 16K (costing £35) should be available by the year end, as well as a printer interface board (costing £25), and later next year a colour board. By then, the company hope to be selling 3000 units a month.

Cost effective satellites

The postponed launch of the second European maritime communications satellite should take place while this issue is in the press. Though European in origin, this satellite's station is over the Pacific ocean and like its Atlantic partner will be leased to Inmarsat for international telecommunication at sea.

The two Marecs satellites grew out of the earlier, lower power Marots proposal and had their frequencies reduced down to 4/6GHz for compatibility with installations for Marisat, which they replace. The delay, from April last, has given time for modifications in the light of experience with the interference from electrostatic

discharge in the Atlantic satellite (see News, May issue).

(Vienna. – According to Olof Lundberg, the director general of Inmarsat, speaking at the Unispace '82 conference, the number of ships and oil rigs fitting earth stations for Marecs increased by 30% in the first half of this year, to 1,350.)

Simultaneously with Marecs B, a second Sirio satellite is launched, using Italy's spare model built as a back-up for a 1977 communication satellite. In addition to providing meteorological data for the African continent, the satellite carries retroreflectors and time markers for laser pulses sent from ground stations. Object is

to provide a laser-based method for long-distance synchronization of atomic clocks with sub-nanosecond accuracy, as well as giving an opportunity of comparing both laser and microwave time synchronization methods, using information gained from Sirio 1.

After the first six operational satellite launchers – ordered back in 1978 – are spent next year, the responsibility for Ariane launches transfers from ESA to Arianespace, a private company formed to exploit Ariane in 1980 and ratified by ESA last year. With a capital of 120 million francs its shareholders are the 36 principal European aerospace firms, 11 banks and CNES, in 11 countries, with France having the lion's share of 60%, Germany next with about 20% and the remainder having

DATE	NAME	AUTHORITY
1982 Sept	Marecs B + Sirio 2	ESA
Nov	Exosat	ESA
1983 Jan	ECS 1 + Oscar 9B	ESA
Mar	Intelsat V F7	Amsat
May	Intelsat V F8	Intelsat
Jul/Aug	ECS 2 or Telecom 1A or Intelsat V F9	ESA
Oct	Intelsat V F9 or ECS 2 and/or Telecom 1A or B or ECS 2	France Intelsat Intelsat SEA France ESA
1984 Feb	Spacenet 1 + Arabsat or Telecom 1B	Southern Pacific Arabsat France
May	GStar 1 + Telecom 1B or Arabsat 1	GTE France Arabsat
Aug	GStr 2 + Spacenet 2	GTE Southern Pacific
Oct	Spot 1 + Viking	CNES Swedish Space Corp
Dec	Slot available	
1985 Feb	SBTS 1 + Spacenet 3 or ECS 3	Brazil Southern Pacific ESA
Mar	Intelsat VA F14	Intelsat
May	TV-Sat 1	Germany
Jun	Intelsat VA F15 or TDF-1	Intelsat France
Jul	Giotto + STC-1	ESA Satellite TV Corp
Aug	Aussat 1 + SBTS 2	Australia Brazil
Sept	TDF-1 or Intelsat VA F15	France Intelsat
Oct	Ariane 4-01	
Dec	Aussat 2 + Anik D	Australia Canada

shares varying from 0.25 to 4.4% in similar proportions to their ESA funding. Current orders with Arianspace – see table – are said to be worth 3,000 million francs at 1980 prices.

Four today, how many tomorrow?

Only 87% of the UK population will be able to receive Sianel 4 Cymru and Channel 4 television services when they start up on the first and second days of November. This is because only 31 of 51 major transmitters will come into operation by that date, and about 100 of 600 low-power relays. Twelve main stations will need to be equipped next year to bring coverage up to 94%, the remaining eight waiting till 1984. But it will take until the end of 1986 for the relay stations to be completed. Coverage for Wales is higher at 90% with all six main transmitters operational and at least 80 local relays, with 13 more for 1983. If Wales gets better than average cover, Scotland comes off worse with only three main transmitters completed in time for the launch. Three more come into use next year but it's not until 1984 that it catches up, with six of the eight main transmitters for installation being scheduled for Scotland. The IBA, who are responsible for all the UK transmitters (but not the Welsh programming, this belonging to the Welsh Fourth Channel Authority), say the rest of the relays will be equipped as soon as possible from 1984 onward to bring the new

With competition in satellite launch facilities on the increase cost per kilogram in orbit has become a significant selling point. Together with increasing mass of satellites, this led to the dual launch experiment of September 10 with Marecs B and Sirio 2. To increase cost-effectiveness further it's planned to recover the first stage rocket by parachute. And if that's not enough, the thrust of the first two stages is set for a 10% increase, together with 25% for the mass of third-stage fuel. That will put a payload of 2000kg into orbit. And that's not all; this up-rated Ariane 2 launcher will be ripe for augmentation by adding two first-stage boosters so that 2580kg can be orbited (or two lots of 1195kg).

For satellite launches from 1985 onwards, the ESA earlier this year approved development of Ariane 4, with 50% more stage-one fuel with either two or four boosters with solid or liquid propellants and a flexibility to match a range of payloads between 2000 and 4300kg. Such a rocket would reduce mean cost per kilogram to 60% of that for Ariane 1, and have the capability to launch the Intelsat VI series, scheduled for 1986 onwards.

To accommodate the launch of this vehicle a second site is being completed for 1984, but equally important, this will allow time between launches to be reduced to a month. ESA/CNES studies of requirements beyond Ariane 4 suggest that Europe could one day be in a position not only to put 15 tonnes into low orbit in 1992 but also to recover launchers, returning payloads, and perhaps humans too.

services to everybody now receiving ITV, BBC1 and BBC2 on u.h.f. They point to the sheer size of the undertaking; the number of transmitters is far greater now than it used to be with the 405-line v.h.f. broadcasts, necessitating a massive investment in new equipment amounting to some £50 million. And, they emphasize, this will be the first time a television service will have been started in all 14 regions at the same time . . .

Cryptic satellite tv for Europe

Satellite Television plc will be transferring its European subscription tv service started earlier this year from OTS-2 to the ECS satellite next year, when OTS reaches the end of its planned life. To clear a space for ECS OTS has already been moved from its old 10°E position, to a new location at 5°E.

Based in London, Satellite TV transmits programmes between 18 and 20h u.t. every night via the OTS-2 spotbeam transponder on 11.64GHz. The service, financed by advertising and consisting of a

wide variety of programmes from many countries including Britain, USA and Australia, is described as an "entertainment channel". It is received by licensed cable companies in European countries, among them Finland, Malta, Netherlands, Norway and Switzerland, although reception is not permitted by UK Home Office.

The transmissions are unfortunately encrypted at the insistence of Eutelsat, the European organisation of telecommunication authorities, to prevent "unauthorized use". There seems no prospect of an early liberalization of this rule which would make it possible for individuals to receive the programmes without having to hire or buy expensive decoders. The encryption method is the Oak Orion system developed for US cable tv (see "UK nearer to US tv encryption") and is generally accepted to be fairly difficult to break, particularly as the sound is carried on the sync pulses.

The level of power from the spotbeam transponder means that for reception with a good signal-to-noise ratio a dish of around two metres diameter is needed. Although the transponder channel is 120MHz wide only a single 18MHz channel is used, with two transponders on the same frequency, one horizontally polarized and one vertical. On the present evening schedule, one carries the programmes of STV, and the other a French programme TV Tunis for North Africa.

Smart card, smart price

Known variously as the electronic chip card, debit card, payment card, pocket data card, memory card and smart card, the electronic credit card has spawned its own (non-electronic) publication. "Electronic chip card report" is a four part work, with updates, issued in 50 page instalments over a year for intending makers and users of the cards, and containing market research reports of card developments, especially in France, Germany, Italy and the USA. The most popular format for a card, consisting of memory and microprocessor circuitry embedded inside a card that is physically indistinguishable from an ordinary plastics credit card, is already in use for payment applications in France, according to the Report's promotional blurb. It is published by Steve Sziram of HTE at \$2,500, and is available through Geoff Coole in the UK at 26 Pamber Heath Road, Pamber Heath, Basingstoke, Hants (0734 700543) – but not by electronic credit card.

● Coole Marketing Services otherwise represents Micropower Systems Inc of California, Catalyst Research Corp (maker of lithium iodide cells for cmos ram), Inmos to specific UK customers, and SIBS Report, a \$400 p.a. semiconductor industry newsletter from the same publisher.

-
- 1 Theories and Miracles
 - 2 Electromagnetic Analogy
 - ▶ 3 Impact of the Photon
 - 4 A more realistic Duality?
 - 5 Quantization and Quantization
 - 6 Waves of Improbability
 - 7 Limitation of Indeterminacy
 - 8 Haziness and its applications
 - 9 The State of Physics Today
-

IMPACT OF THE PHOTON

The experimental discovery of photons at the turn of the century showed finally that electromagnetic theory had failed. Waves or particles, or both or neither? "Double-think" became the order of the day, a required belief; but are we sure that the last word has been said about this logical conflict?

BY W. A. SCOTT MURRAY
B.Sc, Ph.D.

The impression given by writers of scientific textbooks is that everything in classical physics was tidy, or about to become tidy, until 1899 when Max Planck came along and spoiled it with his quantum hypothesis. We have seen that this popular history misrepresents the truth. Electromagnetic theory, which formed one of the three structural pillars of classical physics, had already been placed in extreme philosophical difficulty by the Michelson-Morley result – no physical ether, therefore no electromagnetic waves. The whole of fundamental thinking at this time was based on electromagnetics; even the ordinary mechanical mass of an ordinary physical particle, such as an electron, was considered to be "electromagnetic mass", attributable to the inertia of its electromagnetic field, so that this field could be thought of as replacing the electron's material mass and even, by some physicists, to be the electron itself. In these circumstances the suggestion that anything could be seriously wrong with electromagnetic theory just didn't bear thinking about. One simply had to soldier on, hoping that some solution would turn up to relieve the anxiety.

However, the inconvenient absence of a physical ether was not the only evidence of failure of the electromagnetic theory. Serious difficulty was also encountered in describing the processes of radiation and absorption of light. The trouble in the radiation process was resolved by Planck by means of the revolutionary hypothesis which finally shattered the complacency of his times: *the radiation of energy in the form of light by a material substance is not a continuous process*. Individual mechanical oscillators in the material – atoms or molecules – radiate individual quanta of light energy. In the case of the absorption of light there is additional evidence of a discontinuous process: the photoelectric effect, which had similarly defied analysis by classical theory, was readily explained by Einstein on the basis of Planck's new hypothesis. The only possible interpreta-

tion of this high-quality experimental evidence is that the whole of an individual package of light energy or quantum must always interact, at any rate in the first instance, with one individual microsystem in the photocell surface. The light energy seems to be localized in space.

There was on the face of it, and in retrospect, nothing very surprising about this deduction. The essential granularity of matter on the microphysical scale, atoms and molecules, had been recognized for a hundred years. These newly discovered quantum interactions suggested that light energy also is packaged granularly into "photons" which behave as discrete corpuscles or particles, as Newton believed. The reason for the fuss was that the concept of a light beam as a shower of photons was in direct conflict with electromagnetic theory, because the latter, being a theory of linear force fields, depended absolutely on the *continuity* and extension in space of the quantities it was dealing with. By contrast, the concept of a particle or photon epitomizes discontinuity. Electro-magnetic theory *was bound to fail* when confronted with this discontinuity – and fail it did.

To those physicists who had believed the beautiful electromagnetic theory to be universally true and who had accordingly espoused it with a quasi-religious fervour, and likewise to those who so revere it by tradition today, its overthrow in the face of the quantum evidence, undeniable though that evidence might be, was simply not to be tolerated. Human feelings at levels deeper than mere reason were involved in this conflict. If mysticism was to regain its lost foothold in science, here was fertile ground.

Naturally, various attempts were made to compromise. The most hopeful of these led to the concept of the wave-packet. In certain circumstances, chief among which

is that the physical medium in which they travel must be dispersive – a technical term – a group of water waves will propagate together across a pond and will remain concentrated together in the form of a package. The energy represented by the wave system travels at the speed of the group, which is not the same as the speed of the individual waves. (The mathematics of this situation is quite elegant). Hence it was suggested that the quantum, the particle-like concentration of light energy which was deduced from the experiments, might be merely a wave-packet of dispersive electromagnetic waves. That was the view which Planck himself took of the matter and maintained with some vehemence.

The trouble with this idea – it is distressing but noteworthy how often one is forced to say "the trouble with this idea . . ." – the main trouble with this idea is that although a suitable wave-packet could remain stable indefinitely in the longitudinal direction, no configuration of linear (Maxwell) waves can be devised which would prevent a wave packet from dissipating *across* the direction of the propagation. Now a beam of light will dissipate laterally, exactly like a wave system, but the individual quanta of which it seems to be composed *do not dissipate*. The unimpeachable experimental evidence for this is that the intensity of light decreases with distance from its source (the beam becomes more widely spread out), but the energy of its individual photoelectric impacts (its colour) does not change with distance. For this reason, Einstein, the radical, disagreed with Planck and came to regard the quanta as photons, essentially indivisible whilst in transit and therefore of the nature of particles. The wave-packet concept was a non-starter, disproved by the evidence, but it is still offered to physics students today as though it were valid and relevant.

In the end, and in my view prematurely, a thoroughly unsatisfactory compromise based on mysticism seems to have won the

day. Modern physics as now taught accepts the doctrine of duality, which says that light radiation (sunlight, radio waves and x-rays) consist of both waves and particles at the same time. Whether its wave-like or particle-like properties predominate will depend on the details of the particular experimental set-up. If I use a diffraction grating I shall see waves; if I use a photocell I shall see photons; if I follow a diffraction grating by a photocell I shall see both forms of light within the confines of the same experiment. It matters not that waves (as in electromagnetic theory) and photons (quantum theory) are mutually-exclusive concepts, each of which specifically denies the validity of the other. If I am to make a successful career in physics I must learn to ignore that logical conflict and get on with the remainder of my job as though the conflict did not exist.

The duality doctrine can be fully accepted only by a person who is able and willing to "double-think" in the George Orwell sense. For every other professional physicist the choice is either to live with the doctrine – reluctantly and with resignation, no doubt, knowing it to be unsound – or to try to do something about it: but what? The problem of the true nature of light radiation is recognized to be one of surpassing difficulty which may "for fundamental reasons" actually be insoluble. There even exists a powerful school of thought which believes that matters of this fundamental kind are intrinsically beyond the power of the human mind to understand, so that it would be wrong to expend time, effort, or public money on attempting to understand them. It is asserted by this school that modern quantum theory is "complete" (Niels Bohr), and since that ultimate theory offers no solution to the problem there *can be* no solution to it (von Neumann).

Believe me about this, please, for I am telling you the truth: that view is the accepted dogma of today's scientific establishment. It follows from the arguments of the so-called Copenhagen School during the 1930's, while the body of doctrine now known as the quantum mechanics was under development. That doctrine is no more sacrosanct than was electromagnetic theory, and it rests on very much less secure experimental foundations (see later). It categorizes the fundamental nature of light as a *non-problem* for physics, about which it would be improper to ask further questions. Its bland assertion that there "can be" no further progress toward understanding in this and similar areas constitutes the ultimate in defeatism. For myself, I do not accept it.

Now if I declare that I do not accept one of the currently established doctrines of physics, in this case the doctrine of duality, the onus is on me to provide an alternative that I and others may find more acceptable. This I cannot yet do; nor, I expect, will anyone now be found who is able to review and revise the whole of modern physics single-handed. What I can do is invite those of my colleagues who are interested and not too busy to take a fresh look with me at the duality paradox, and I

can start the ball rolling by mentioning a few neglected facts that may help us on our way.

My first hopeful factor is this. It is not waves as such, but *electromagnetic theory* – a field theory – which is inconsistent with the existence of discrete, particulate photons. When we are dealing with the most familiar waves of all, sound-waves in air, we do not normally have to remember that the true picture is one of interactions on the microphysical scale between myriads of individual air molecules. Rather than seek to follow and account in detail for the motion of each and every air molecule, which would be an impossible task anyway, it is sufficient for almost all purposes to consider their average behaviour. We speak in terms of local mean pressure and local mean velocity, and using these terms we can describe the propagation of sound as "waves" of pressure and velocity moving through the gas. Now the point to be made is that the *mathematics* of this description of sound is concerned with waves in a continuous medium, yet we know from other experiments that the true nature of a gas is not that of a continuous medium but of discontinuous, discrete molecules. The sound waves are real waves, however; their crests and troughs represent concentrations of air molecules which move progressively and systematically through the gas; and those density changes remain wavelike even though the gas is not mathematically continuous. It is not the waves but the mathematical theory of the waves which is inconsistent with the molecular nature of the gas. Clearly the theory is an *approximate description*, valid only in limited circumstances.

In electromagnetic theory the roles corresponding to local gas pressure and velocity are played roughly, but not exactly, by Maxwell's field potentials and displacement currents. It is these mathematical artefacts of the field theory, demanding as they do continuity in an ether medium, which are in conflict with the quantum evidence for the granularity of light. Light waves might very well consist of periodic

variations in the density of photons as they travel in bunches through empty space at velocity *c*. If this should be so the infamous dualistic doctrine would be shown up for the mystical nonsense that I, for one, believe it to be. And the conflict would no longer lie between the concepts of light waves and photons, no longer incompatible, but between the electromagnetic theory and the experimental evidence. That theory also would be no more than a limited analogy at best.

It would be quite wrong to pretend to any originality for this idea, which Sir Karl Popper has quoted as representing Einstein's view. The concept that light waves consist of bunches or concentrations of photons is so obvious that one has to ask why it has not been generally accepted in place of the duality doctrine. Part of the answer would seem to lie in a general belief that it has been disproved experimentally. I am now going to argue that despite popular belief the concept has not in fact been disproved, but that it deserves at least one further, careful examination.

Typical of the experiments in question is one involving the interference of light, which is so readily accounted for on a "pure-waves" theory. I cannot do better than quote from an article written by Professor Frisch, of Cambridge, in 1969:

"But what happens to the *photons* in an interferometer? At first it was thought that interference occurred when two or more photons came together; but that was disproved when G. I. Taylor (1909) showed that interference fringes were formed just the same whether the light was strong or whether it was so weak that hardly ever two photons passed through the apparatus together. It follows that single photons can exhibit interference, that 'a photon can interfere with itself'. It would seem that something does travel along both paths in the interferometer even when only one photon is admitted; but what is it? "Such questions were discussed a good deal when photons were new, and similar questions arose out of wave-particle duality of 'material' particles such as electrons. Some agreement has been reached on the way they should be answered, but the agreement is not unequivocal, and many of us are not sure what to tell our students . . ."

Summary

The crisis in electromagnetic theory threatened the whole of 19th-century physics. The threat became extreme when evidence of the radiation law (Planck, 1899) and the photoelectric effect (Einstein, 1905) showed that on these issues at least the electromagnetic theory had already definitely failed. The concept of the wave-packet, proposed by way of compromise, proved to be untenable. Eventually the mystical doctrine of the simultaneous waveparticle duality of light radiation came to be accepted, perhaps with resignation, together with the parallel doctrine that no fundamental understanding of this duality could ever be achieved. The onus was thereby placed on those

who do not accept such negative doctrines to provide more acceptable alternatives to them. One such alternative, attributable originally to Einstein, proposes that light "waves" may consist of periodic variations of photon density. It is generally believed nowadays that this concept was disproved long ago, but careful investigation suggests that this is not so. Modern technology provides the possibility of a series of more rigorous experiments which could decide this very fundamental question once and for all. The main difficulty with such experiments is the practical one of obtaining financial support, because the concept underlying them is in conflict with the established dogma of modern physics.

The G. I. Taylor referred to was a research student at Cambridge under Sir J. J. Thomson. In his experiment he set up and recorded interference fringes on photographic plates, and the essence of his result was that no change could be discerned in these fringes whether the light was of visible intensity or so weak that to record the patterns required an exposure lasting three months. In the latter, extreme, case it could be calculated that if photons existed they must on average be separated by 30cm, which was appreciably more than the dimensions of the apparatus. Hence on average only one photon was present at any one time; yet the interference fringes still appeared in the photographs.

I submit that a point may have been missed by Taylor, by Thomson, by later experimenters who may have repeated the test, and by all who have accepted this result as evidence that "a photon can interfere with itself".* Everybody seems to have assumed that natural photons are evenly distributed in space, and that their density will be diluted evenly when the light intensity is attenuated toward zero. That is the assumption on which the deduction rests in this and similar experiments, but I suggest that it may be a false assumption. I propose in its place the idea that photons generated naturally - by a black-body radiator for instance, or in a discharge tube - are generated not singly but in very large bunches. Then in the experiments of Taylor and others the photons, although infrequent in an average sense, would nevertheless have continued to manoeuvre in bunches. There never was a time when the apparatus contained only a single photon, and interference *between*

photons, rather than within individual photons, remained the order of the day.

Can I substantiate this proposal? Yes, I believe I can. In 1917 Einstein published a derivation of Planck's quantum law which later became the theoretical basis of the modern laser, and is therefore quite likely to be true. In this derivation he deduced the existence of two kinds of radiating mechanism which he denoted A and B. The A-type was spontaneous emission, self-triggering, while the B-type was stimulated emission, in which an atom or molecule previously primed with energy was triggered by the arrival of a photon already in flight. Following from Einstein's proposal, in the radiation of visible light the occurrence of B-type (stimulated) emission may be up to a thousand million times more frequent than A-type (spontaneous) emission.

We may interpret this result in non-mystical, mechanical terms. It should mean that photons are normally radiated in a cascade process: that is, in bunches. Each bunch would consist of up to a thousand million stimulated emissions, triggered ultimately from the one photon that is emitted spontaneously to initiate the cascade. This would represent the biggest snowball effect known to man - going on all the time on our doorstep, without our having noticed it. (I have coined the phrase *semi-laser action* to describe this process; the emission of *wave trains* can be explained in a natural way by interpreting Planck's $E=h\nu$ as $E=h/\tau$, where τ is the delay-time for emission of a photon of energy E).

If this argument should prove to be even moderately near to the truth (and I would gladly settle for a bunch of a million photons rather than a thousand million, not

being greedy), we would have good reasons for repeating the Taylor experiment with modern photon-counting equipment. At sufficiently low light levels the interference phenomenon should simply fade away, like sound in sufficiently rarefied air. It would not be an expensive experiment by modern standards but it would be *very* fundamental and I say, worth the trouble of performing it. (I would have done it myself at home if I could have found the necessary £50,000 for equipment!) The key to the test would be to ensure and demonstrate that the photons were constrained to pass through the apparatus truly one-at-a-time. To forestall misinterpretation in these mystical and doctrinally-loaded surroundings would call for the greatest care. Also we may note that there is nothing "impossible" about this experiment, except that according to the Copenhagen dogma the question it asks is an improper question - just a bit too fundamental for comfort.

If it were thus to be shown that, contrary to current doctrine, the interference of light is a group phenomenon not evidenced by individual photons, we would be well on the way to a resolution of the duality paradox. A series of options in physics would be re-opened, which for fifty years have been dismissed as old-fashioned, "unphysical", or merely "unrealistic" - epithets which, in context, carry a pleasing irony. In the meantime we may examine some of the consequences to which a positive experimental result might lead. WWW

*The wording of Taylor's report makes it clear that his boss, Thomson, did not hold with the new-fangled quantum ideas. Having obtained a result in accord with classical theory he was not disposed to investigate the issue further . . .

Next month

Two-metre transceiver. Complete design for a two-metre band, six-mode transceiver for mobile use by T. D. Forrester, call-sign G8GIW. Microprocessor control simplifies functions such as scanning, tuning, frequency display and use of the unit's nine memories. The transmitter power rating is 16.5 watts in the f.m. mode.

Technological choices for the UK. Robin Howes sets out to bring the

discussion about educating engineers in social responsibility down to earth in this first of two articles. Written in response to Peter Hartley's article on educating engineers, it relates the ideas to the current industrial situation: part one deals with technological choices for the UK.

Heretics guide to physics. Instead of trying to ignore Planck's quantum hypothesis because it conflicts with electromagnetic theory, suppose we were to afford it more than lip

service; what then? In A More Realistic Duality Dr Murray continues the Heretics Guide to Physics series by discussing new situations that could be tested by experiment.

Interfacing the Nano-comp. Bob Coates describes how to expand i/o interfacing for the nano-comp and gives connection details for the Cuban interface.

On sale Sept 15

FLOPPY-DISC DRIVES

Despite the floppy-disc drive's disadvantages in relation to the hard-disc drives already discussed, it is widely used and popular, particularly with microcomputer systems, because of its low cost. John Watkinson looks at the progress of floppy-disc drive technology this month.

Floppy discs are the result of a search for a convenient and fast, yet cheap non-volatile memory for storing instruction-coverting data used with a processor under development at IBM in the late 1960s. Both magnetic-tape and hard-disc storage were ruled out as means of quickly restoring the system's data after a supply interruption on grounds of cost, since only intermittent duty was required. The device designed to fulfil these requirements – the 8-inch floppy-disc drive – incorporated both magnetic-tape and disc technologies.

The floppy concept was so cost effective that it transcended its original application to become a standard in industry as an on-line data-storage device. The original floppy disc, or diskette as it is commonly called, is 8in in diameter and the more recent 'mini-floppy' is 5¼in in diameter. Still more recently, the 'micro-floppy', measuring around 3½in in diameter has been introduced.

Strictly speaking the floppy disc is a disc-storage medium since it rotates and repeatedly presents the data on any track to the heads, and it has a positioner to give the fast access characteristic of disc drives; but the device is also very similar to a tape drive in that the medium consists of an oxide coating on a flexible substrate which deforms when the read/write head is pressed against it.

Being stamped from a tape, a floppy disc is anisotropic, owing to the oxide being oriented along the tape during manufacture. On many brands this can be seen by the naked eye as parallel striations on the surface. A more serious symptom is the presence of sinusoidal amplitude modulation of the head output at the rotational frequency of the disc, illustrated in Fig. 1.

Standard and 5¼in floppy discs have straight radial apertures in their protective envelopes to allow access by the linear head positioner, but micro-floppy discs have curved slots since they use the lower cost rotary positioner, Fig. 2. A further aperture in the envelope allows a photo-electric index sensor to detect a small hole in the disc which gives an output signal once per revolution to synchronize the read/write circuits (discussed in an earlier article).

The disc is inserted into the drive edge first, and slides between an upper and lower hub assembly, Fig. 3. One of these assemblies has a fixed bearing which transmits the drive and the other is spring loaded and mates with the drive hub when the door is closed, causing the disc to be

by **J. R. Watkinson**
B.Sc., M.Sc.

gripped firmly. The moving hub is usually tapered to accurately centre the disc. To avoid frictional heating and in the interests of longevity the spindle speed is restricted to about one tenth of that used for hard discs. The spindle is commonly driven by an induction motor, but more recent units incorporate electronically-governed d.c. motors, which have the advantage of needing no modification to run on different supply frequencies, and generate less heat.

Since the rotational latency of the slowly turning disc is so great, there is little point in providing a fast positioner so the carriage is moved by a stepping motor driving a leadscrew in the case of standard and mini-floppy discs, Fig. 4. This approach also provides detenting. To appreciate why this is so, it is necessary to understand how a stepping motor works.

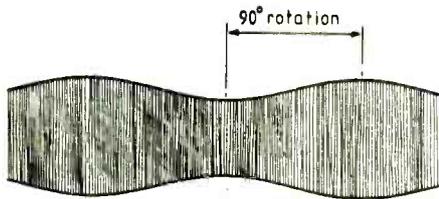


Fig. 1. Being stamped from tape, a floppy disc is anisotropic. This can cause sinusoidal-amplitude modulation of the type shown.

Figure 5 shows that this type of motor consists of a multi-lobed iron rotor and a stator with the same number of poles, each of which has a coil. If current is passed, the rotor lobes will be attracted by the poles, and will move into alignment. A smaller current, known as a holding current, will maintain this alignment against considerable external torque.

In smaller motors the holding current can be dispensed with as the rotor is a permanent magnet which naturally has a detenting action. A simple stepping motor of this type will only work if it is push-started at the frequency of the coil pulses. Motors of this type can be found in most a.c. electric clocks. To permit starting under load, extra poles and windings with separate connections are interposed between the original windings. If the windings are pulsed in turn, the rotor will jump round, following the pulses, and detent at the last coil to pass current. This is the basis of the poly-phase-stepping motor, which is the type used in floppy-disc and many 'mini-Winchester' drives. A typical standard floppy-disc drive uses a stepping motor with four windings and two steps correspond to a one cylinder seek.

Figure 6 shows a typical drive circuit, in which a 2-bit counter counts up or down according to pulse from the controller, and this count is decoded to one of four outputs which will be in the correct sequence for the chosen direction of travel. Although the pulses from the controller may

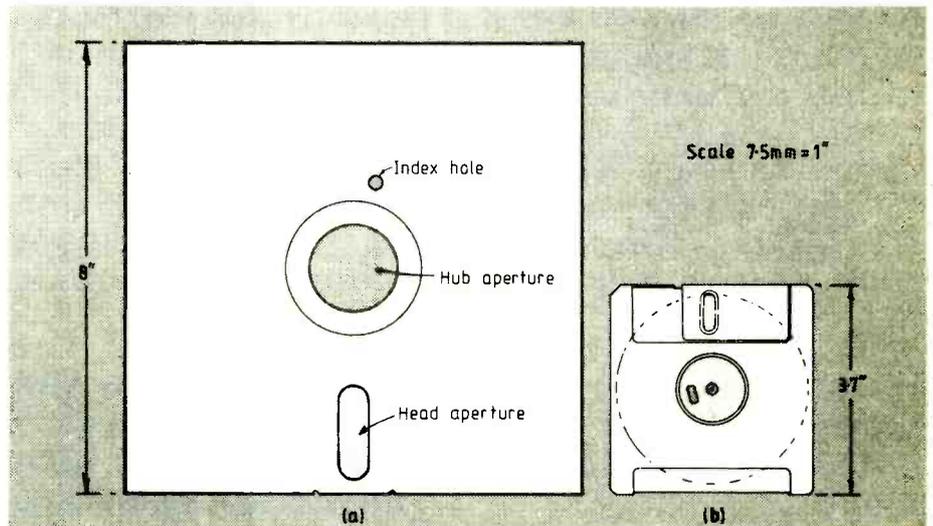


Fig. 2. A slot in the disc's protective envelope allows the read/write head to access the disc surface, and a further small aperture lets the photo-electric index sensor detect a small hole in the disc for signalling one revolution. Various types of micro-floppy disc-drives are appearing, one of which has a rotary positioner to keep costs down. Micro-disc shown is for the Sony SMC-70. Relative sizes shown are approximate.

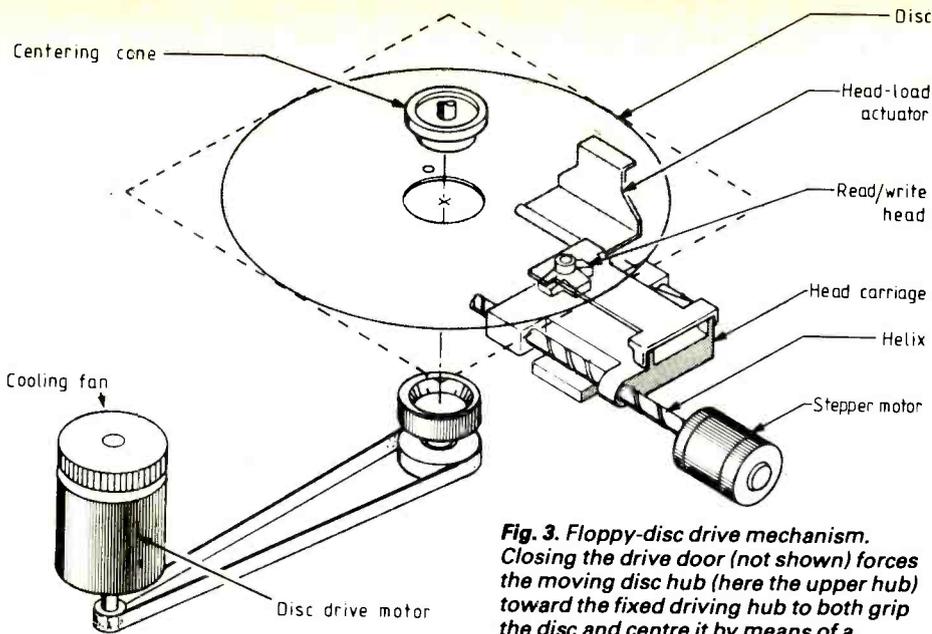


Fig. 3. Floppy-disc drive mechanism. Closing the drive door (not shown) forces the moving disc hub (here the upper hub) toward the fixed driving hub to both grip the disc and centre it by means of a location taper.

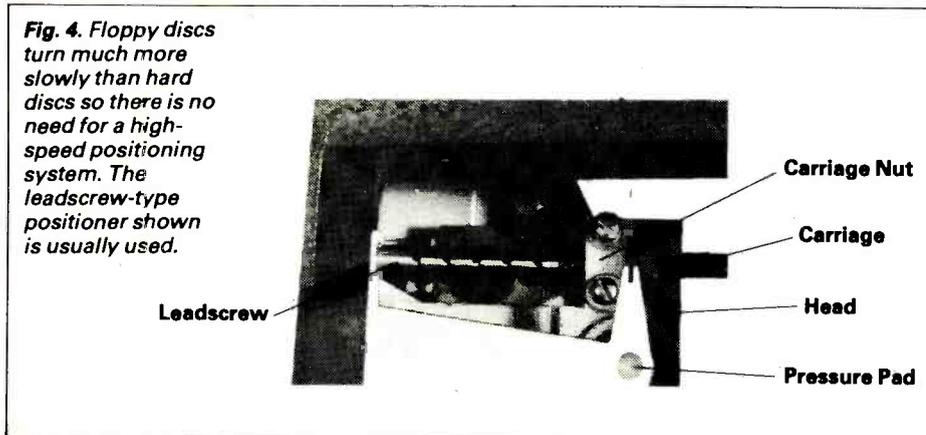


Fig. 4. Floppy discs turn much more slowly than hard discs so there is no need for a high-speed positioning system. The leadscrew-type positioner shown is usually used.

only be a few-hundred nanoseconds long, the motor drive circuit stretches these to about 10 milliseconds.

All incremental positioners need a reference from which to start counting. At the rearward limit of carriage travel, the carriage interrupts a slotted light-beam-type sensor which generates a logic signal indicating cylinder zero. From then on, the controller must remember the sum of how many pulses forward and how many back have been sent in order to know what the current cylinder is. Should this count be lost, say due to a power failure, it is necessary to execute a recalibrate function. In this case the drive is sent reverse pulses until the cylinder-zero sensor is activated.

Head alignment. One of the less endearing features of plastics materials is lack of dimensional stability. Temperature affects plastics much more than metals, and they also change their dimensions as a function of humidity. For this reason the track spacing has to be generous, being only 77 tracks on the industry-standard floppy, and 35 on the basic mini-floppy disc. Owing to this coarse track spacing, head alignment in the field is seldom necessary, but is nevertheless quite easy on a leadscrew drive. After loosening a clamp screw, the stepping motor can be turned bodily while detented, which has the effect of rotating the leadscrew, hence moving the head. It is also important that the cylinder

zero sensor be at the correct radial position, or a recalibrate could cause the positioner to detent on the wrong track.

The read/write head of a standard floppy-disc drive operates on the lower surface only, and is rigidly fixed to the carriage. Contact with the medium is achieved with the help of a spring-loaded pressure pad applied to the top surface of the disc opposite the head. To reduce head wear, the pressure pad is often retracted when data is not actually being transferred.

Fig. 6. Stepping-motor drive circuit in which a 2-bit counter counts up or down according to pulses from the controller. The count direction determines the switching sequence of four output drivers and hence the motor's direction of rotation.

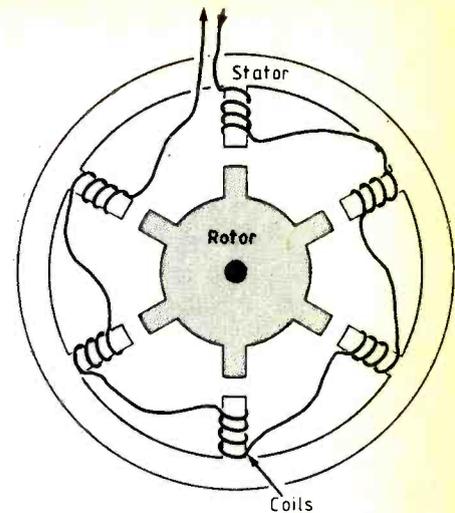
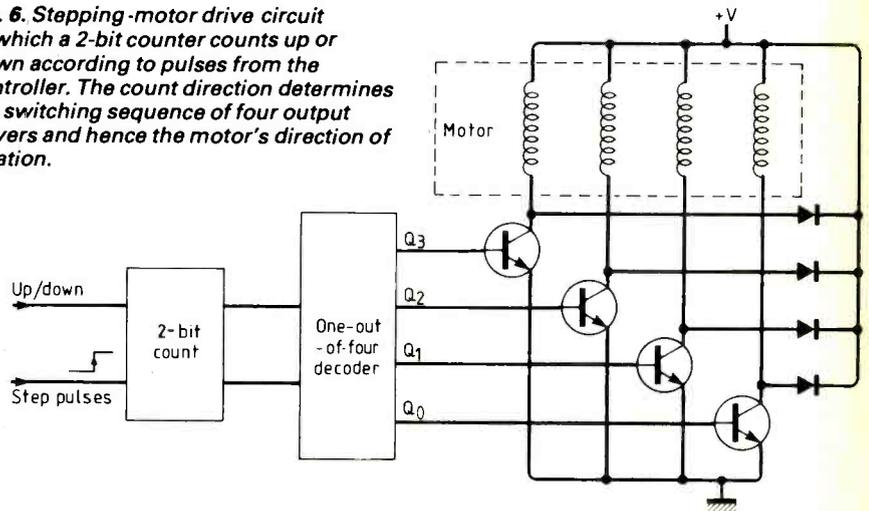


Fig. 5. Stepping motors are used to turn the floppy-disc drive positioner's leadscrew. The most basic form of stepping motor, shown here, requires external torque to start it, and if the rotor is a permanent magnet, detenting is obtained when the rotor is stationary. This type of motor may be found in mains-driven electric clocks, but a commonly used, more advanced type with extra, separately-driven windings and poles is used to turn a floppy-disc-drive positioner's leadscrew in either direction without starting torque from outside.

Some drives have provision for adjusting the pressure-pad loading. The pressure-pad solenoid can often be heard operating in an otherwise virtually silent drive. The recording technique used with standard floppy-discs is f.m. (described earlier in the series). Owing to the indifferent stability of the medium, side-trim or tunnel erase recording is used, which can withstand considerable misregistration.

Figure 7 shows the construction of a side-trimming head, and the extra erase poles can be seen. Figure 8 shows a typical write circuit from a double-sided drive which incorporates a head-select matrix. During writing, the erase poles are energized by switching power to a fourth head connection.

At the inner tracks, writing density becomes higher, and the write current needs to be reduced. This is the function of the

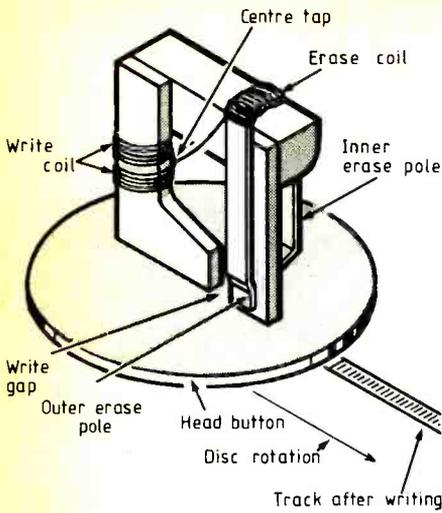


Fig. 7. If a head writes over a track that it is not accurately aligned with, chances are that some of the data that should be overwritten will be left at the edge of the new track. On a subsequent read, signal-to-noise ratio may be significantly worsened by the presence of the remaining unwanted signal. A plastic floppy disc has poor dimensional stability and would suffer from this problem were it not for two small erase heads at either side of the read/write head which clean the track edges during a write.

signal 'above-43', which refers to the higher cylinder addresses.

The major signals between the drive and its controller have now been introduced and are summarized in Fig. 9.

Formatting

Since it has become a standard, the format of the floppy-disc warrants inclusion here.

Figure 10 shows that there are 26 blocks on each track, which commence at the index point. A considerable tolerance gap is left after the last block to allow for variations in disc speed changing the length of blocks written at constant write frequency.

Figure 11 details each block, and shows that the header contains the cylinder and sector address of the block for the purpose of position confirmation before transferring data. The header finishes with a cyclic-redundancy-check character (c.r.c.) which is used to establish that the header was correctly read. Between the header and the data block proper is a space where the write current can be turned on. The block contains 128 bytes of data followed by a 2-byte check character. The IBM specification also details which tracks are to be used for particular purposes, but this is not adhered to by other manufacturers of floppy disc drives.

Developments

As with all disc drives, developments have increased the storage capacity of the floppy disc. The first step was to use modified f.m. (m.f.m.) encoding instead of f.m., which effectively doubles the capacity (described in the second article). Such drives are referred to as double-density, and are to be found in both sizes. Some drives have been built which are capable of

continued on page 84

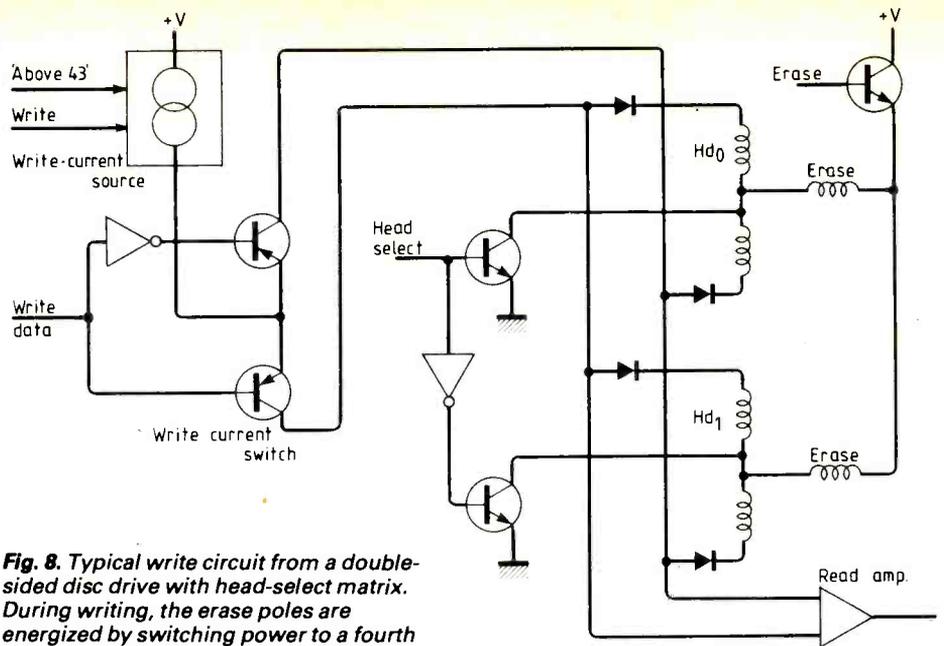


Fig. 8. Typical write circuit from a double-sided disc drive with head-select matrix. During writing, the erase poles are energized by switching power to a fourth head connection. 'Above 43' refers to higher cylinder addresses and is a signal used to reduce write current at the inner tracks where the writing density is higher.

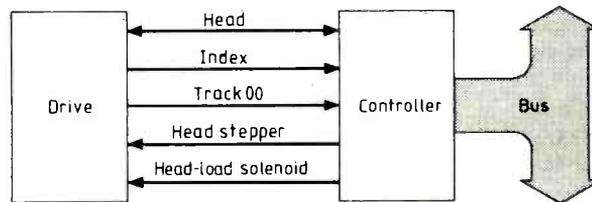


Fig. 9. Main signals between a floppy-disc drive and its associated control logic.

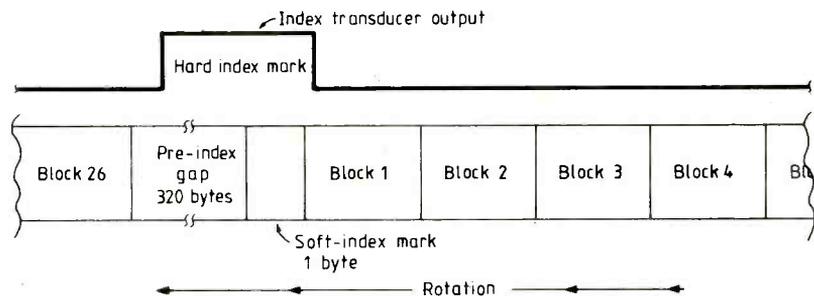


Fig. 10. There are 26 blocks on each track of a standard floppy disc commencing at the index point. A considerable gap is left at the end of the last block to allow for rotational-speed changes, which will change the length of blocks written at a constant write frequency.

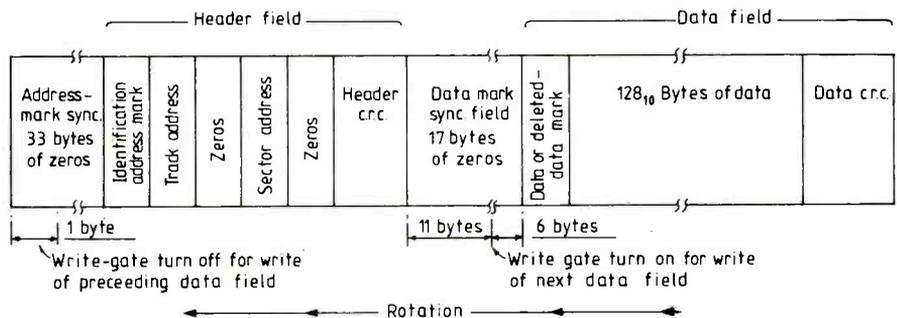


Fig. 11. Details of a data block. In the header-field section, the first byte is a unique pattern decoded by the controller to identify the beginner of the header field, called the identification-address mark. The last two bytes in the header-field section are for cyclic-redundancy checking (c.r.c.). The data field is broken into 131 bytes of information and is preceded by a field of zeros and the header field just mentioned. Here, the first byte is also a unique pattern but for identifying the beginning of the data field, called the data- or deleted-data-address mark. Bytes two to 129 comprise the data field used to store 128, 8-bytes of information. Bytes 130 and 131 are a cyclic-redundancy-check character.

METEOSAT HIGH-RESOLUTION IMAGES

Final details of circuits for receiving Meteosat high-resolution pictures on a home-built station. The original weather-satellite receiver, designed for Tiros-N high-resolution images, was described towards the end of last year.

Word and frame synchronization is achieved by passing the serial data through a 24-bit shift register and detecting the sync. sequence. This is similar to the system used for h.r.p.t. but a more straightforward method of detecting a clock-phase error is used. The effect of this type of error is that the data appears inverted, and with an increased error rate. This situation is detected by checking the serial data for sync. as well as sync. and correcting the clock if sync. is found.

Figure 5 shows the circuit of the serial-to-parallel converter together with the associated sync. detector. The error signal is fed back to the bit conditioner. This circuit should replace the sync. detector section of the serial-to-parallel converter used for h.r.p.t. The counter that provides the word clock should be changed to divide by eight because of the different word length. The sync. guarantee counter which resets at 11090 for h.r.p.t. should be decoded to reset at 364 for p.d.u.s. In the prototype

by M. L. Christieson

station, switching between the two systems is controlled by the computer.

Data handling and display

One of the advantages of using computer software to process the data is that different types of image can be handled easily. In the prototype station, the computer interface was modified to receive two 8-bit words and flags as one 18-bit word rather than the original four, 4-bit words of the experimental h.r.p.t. system. This change was made to accommodate a more advanced colour display which stores 6-bit words to give 64 colours. Reception of h.r.p.t. data is now also through this interface and colour display.

The software that controls data from the interface for the tape drive in real time has


first to locate frame zero and hence the label. Subframes containing the required image data are stripped of unwanted words, such as syncs, and the 6 most significant bits stored in the main memory. Data is then transferred to tape in a similar manner to that used for h.r.p.t., i.e., with data channel and interrupts.

The colour display, which operates as a

Meteosat now relays GEOS pictures

As pointed out in this article, Meteosat's schedule is subject to occasional revision, and since the time of writing a new schedule has been introduced. This includes formats containing data from the GEOS-E satellite situated at 75°W. These formats are relayed via CMS-Lannion in France, and comprise both p.d.u.s. and s.d.u.s. images of the Americas and the Western Atlantic. The p.d.u.s. formats, called LX, have been successfully received by the prototype station.

Fig. 5. Sync. detector with serial-to-parallel converter. The error signal if fed back to the bit conditioner, Fig. 3.

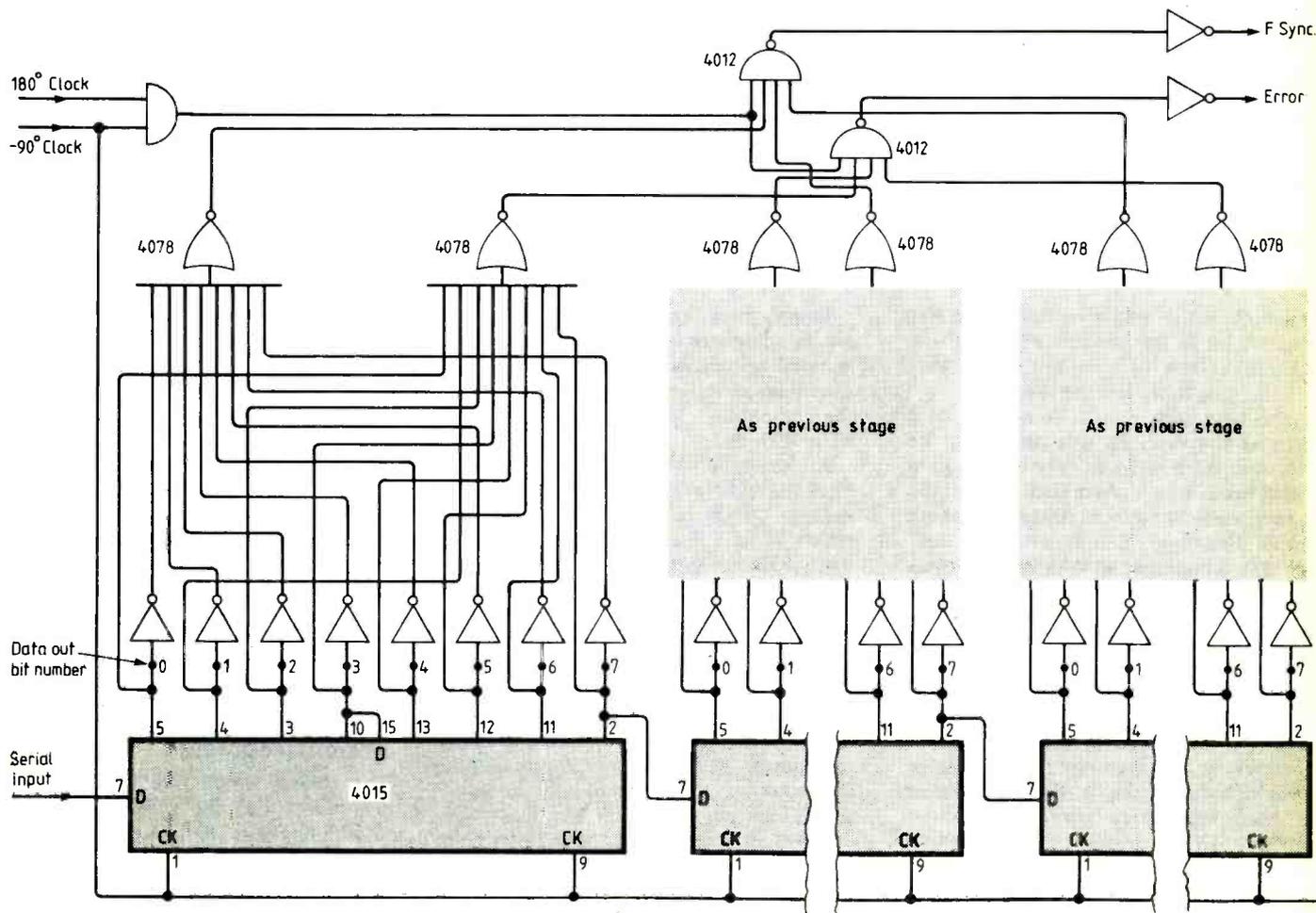

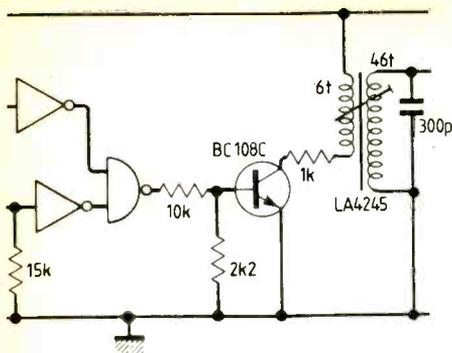


Fig. 4. This is how the top-middle section of the circuit diagram on page 64 of last month's *Wireless World* should have looked; we apologize.

computer peripheral, has a basic image of 315 lines by 384, 6-bit pixels. The raster store is made from dynamic mos memory and uses the line rate as the refresh. A one-line buffer is used to transfer data to and

from the main store. The output is fed to a d-to-a converter from a hardware adder and subtractor loaded by the computer. This means that the colours may be changed without loss of the stored image.

Adjustment and results

Final adjustment is simplified by the continuous nature of the Meteosat signal and a satellite simulator was not necessary. A final check on the system is most easily made by using the computer to check for errors in the sync. sequences. This information may be used to calculate an approximate error rate which was better than 1 in 10^7 in the prototype.

A large number of images have been received and the quality has been excellent. There are relatively few p.d.u.s. users at the moment, possibly because of the high cost of commercial equipment and the apparent reluctance of people to make it.

It is hoped that these ideas may form the basis for further exploitation of the service and facilitate further work on the interpretation and use of the data, a field where much important work remains to be done.

WW

Further reading

Use of data from Meteorological satellites, Technical conference, Lannion, Sept. 1979, ESA, SP143

Satellite meteorology of the Mediterranean, ESA, SP159

Climate and man's environment, J. E. Oliver, Wiley and Sons

Proceedings of the second Meteosat scientific user meeting, Mar. 1980, ESA

Publications relating specifically to Meteosat may be obtained from ESOC, MDMD/OPS, Robert Bosch Strasse 5, D-6100 Darmstadt, W. Germany. Other ESA publications, for which there is a charge, should be obtained from Scientific and Technical Publications Branch, ESTEC, Postbus 299, 2200 AG Noordwijk, The Netherlands.

continued from page 82

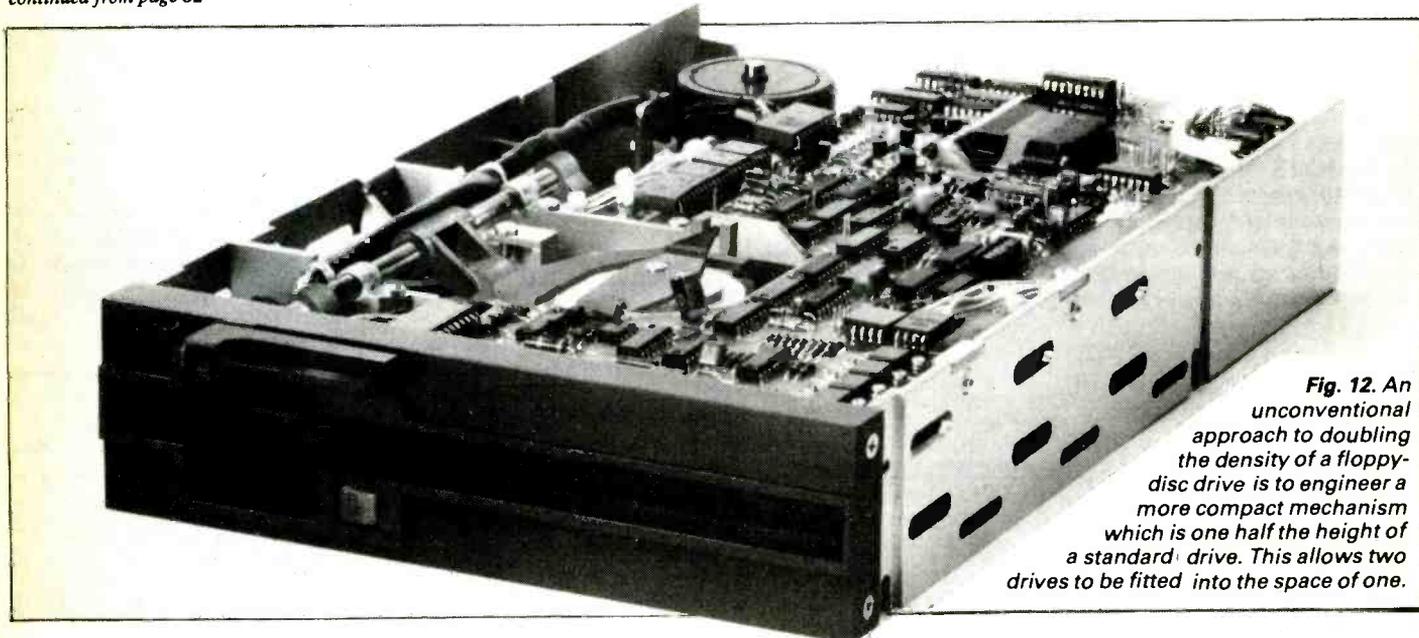


Fig. 12. An unconventional approach to doubling the density of a floppy-disc drive is to engineer a more compact mechanism which is one half the height of a standard drive. This allows two drives to be fitted into the space of one.

accepting either single or double-density discs. A bit in the headers will tell if the subsequent data is f.m. or m.f.m., the disc format being otherwise the same.

The next step was to record on both sides of the disc. In this approach, the pressure pad is replaced by a second gimbaled head, which constrains the medium to pass neatly between in contact with both heads. The floppy disc is somewhat thinner than a hard disc so to reduce crosstalk the magnetic gaps of the two heads are displaced slightly along the track from one another. The two heads are always at the same distance from the spindle. A double-sided double-density drive yield four times the storage capacity of the standard product. As the recording density increases, however, it becomes more important to have high quality media. Recent advances in head technology permit continuous contact with the medium, thus eliminating the solenoid mechanism, making it especially important to use discs recommended by the manufacturer.

Dimensional instability is compensated for in some drives by a section of disc material in the positioner baseplate. As the disc changes its dimensions, so too does the baseplate, reducing the resulting misregistration.

An unconventional approach to doubling the density of a floppy disc drive is to engineer a more compact mechanism which is half the height of a standard drive. This allows two drives to be fitted in the space of one. A unit of this type is shown in Fig. 12.

The most recent development is the use of vertical recording, where the magnetic domains in the medium are arranged on end throughout the thickness of the coating. Research has now provided a suitable medium in the form of Chromium-Cobalt crystals which are sputtered onto the substrate. It is predicted that this technique will increase the capacity of a floppy disc by initially a factor of 3 to 5. This technology can then be expected to migrate to hard discs with staggering results.

In mainframe and minicomputer applications, the floppy disc provides an excellent low-cost medium for loading diagnostic programs, particularly useful if the hard disc subsystem is faulty. In microcomputers, the floppy disc is the only product which is of the same order of cost as the other components of the system, and the disc needs less consideration in handling than the hard disc. With the current popularity of microcomputers, the floppy disc is a significant growth area. *This article concludes the information on disc drives themselves. Future articles will discuss the control logic required to support the drives, and techniques used to ensure data integrity.*

Acknowledgments

The author would like to thank HAL Computers Ltd for photographs of the mini-floppy and half-height drives, and Digital Equipment Co. Ltd for permission to use the standard floppy-disc drive photograph.

WW

SIDEBANDS: PAST, PRESENT AND FUTURE

The debate on the existence of sidebands was recently revived by letters in Wireless World. Professor Bell thinks they are here to stay – for the moment, at least.

A recent letter in *Wireless World*¹ recalled rather nostalgically some of the writer's earliest experiences of radio in the 1930s. In those days engineers did not always rely on mathematics – after all, Marconi successfully defied the predictions of diffraction theory about the propagation of short waves – and there was substantial argument as to whether sidebands really existed. The extreme point of the argument came when J. Robinson produced a type of receiver which he named "Stenode Radiostat" ("Stenode" from the Greek for "Narrow path") which he claimed utilized the modulated carrier and ignored sidebands². This receiver used a single, high-Q resonant circuit (quartz crystal) to give high selectivity. The higher modulation frequencies were admittedly attenuated by the slow response of the high-Q element to changes in carrier amplitude but this effect was compensated by a suitably large top boost in the audio-frequency circuits.

Now, in a truly linear system, the attenuation of high frequencies in one stage followed by their restoration in a later stage would restore the original condition, with no net advantage. But the Stenode Radiostat worked! It was claimed that an interfering station only one kilocycle (kilohertz) off the wanted station could be eliminated. (The weakness of the system was that the large top boost in the audio stages also magnified any harmonic distortion which might have been generated in the detector stage). The success of the Stenode Radiostat also tied in with something which had already been puzzling other experimenters. If one had, for example, a simple crystal set with a single tuned circuit of very modest Q, it was possible to separate two local medium-wave broadcasting stations much more completely than one would have calculated from the resonance curve of given Q.

A demonstration of the existence of sidebands was given at one of the Physical Society's Annual Exhibitions. One exhibit (from the N.P.L.?) showed a carrier of comparatively low frequency (perhaps 15 kHz) modulated by a single audio frequency; and a wavemeter with galvanometer indication of response (there were no spectrum analysers in those days) could be tuned across the frequency band, showing separate responses to each sideband and the carrier.

As sidebands could be shown to exist, why did the Stenode Radiostat work? Remember the qualification above that in a truly linear system no net advantage was to be expected. The fact is that a 'linear' detector, in the sense of one which has a

by D. A. Bell,
F. Inst.P., F.I.E.E.

linear relationship between input and output, is not *linear* in the circuit-theory sense of obeying the law of superposition which requires the output due to two signals applied simultaneously to be equal to the sum of the outputs obtainable from the two signals applied separately. Put very crudely, and assuming the two signals to be of very different amplitude, the opening and closing of the conducting path through the rectifier is controlled by the stronger signal and any signal of different frequency is 'mashed up' because some cycles which coincide periodically with those of the stronger carrier are allowed through but others are blocked. It turns out that only the modulation of the weaker signal is suppressed, to an extent depending on the ratio of carrier amplitudes, any heterodyne note between carriers remaining. In the *Wireless World's* then sister journal, originally entitled *Experimental Wireless* but later *Wireless Engineer*, there was a sequence of papers under the title "Apparent Demodulation of a Weak Station by a Strong One". The first was a mathematical paper by Beatty³, but the mathematics of non-linear systems is notoriously difficult and Butterworth⁴ disagreed with the results of Beatty's mathematical analysis. Then a paper by Colebrook⁵ was concerned to present a simpler mathematical treatment and finally a paper by Appleton (later Sir Edward Appleton) and Boohariwalla⁶ from King's College, London, reported an experimental verification of the theory. This last paper has a footnote suggesting that the effect in question might have some relevance to the Stenode Radiostat. So one now takes account of the effect of relative carrier amplitudes in receiver design, while using a flat-topped pre-detector filter to avoid the problem of harmonic distortion exaggeration by audio-frequency top boost.

So at the present time sidebands are universally accepted, as indeed they should be. To anyone of modest mathematical competence, the statement $\sin \omega t \cdot \sin pt = \frac{1}{2} [\cos(p-\omega)t - \cos(p+\omega)t]$ is just as true as $2 + 2 = 4$. (The modifications to the trigonometric formula to provide for a non-negative carrier and defined depth of modulation are trivial.) The important thing to remember, however, is that an equation has two sides, so that carrier-of-varying-amplitude and constant-

carrier-plus-sidebands are equally valid representations of the modulated carrier: one finds whichever one is looking for, whichever one's test apparatus is capable of detecting. Thus, if one uses an oscilloscope one will see only a carrier of varying amplitude, but if one uses a spectrum analyser one will see carrier and sidebands. The idea of time/frequency duality was not well developed in the 1930s, when one thought of applying Fourier series only to the analysis of repetitive waveforms of non-sinusoidal shape, as in the treatment of harmonic distortion.

The most graphic example of time/frequency relationships (though in a different context) was given by Gabor⁷ in 1946. A pure sine wave will appear in the spectrum (frequency) analysis as a line of zero width, but to have zero width it must extend over an infinite range in time. Conversely, a pure pulse is concentrated in an infinitesimal time but in the frequency domain is spread over all frequencies (as evidenced experimentally by its potentiality for causing interference). Any intermediate waveform – e.g. a chopped sinusoid or a lengthened pulse – will occupy a finite range in both time and frequency. The idea that the communication of information requires a finite bandwidth has somehow become associated with 'information theory' and has thereby acquired an unquestionable authority. Nowadays we expect to be able to shift between time and frequency descriptions of a phenomenon as the immediate problem may demand, by the (mathematical) Fourier Transform, where an analytic description is possible, by the (computer) Fast Fourier Transform (F.F.T.) where numerical transformation of an arbitrary signal is required or by the Wiener-Khinchine Transform to find the power spectrum of a random signal.

So sidebands are firmly with us at present, but will they always be in future? For a long time the frequency domain of sinusoids has seemed inherent in nature: there are so many natural phenomena which involve harmonic oscillation, in fact anything which involves inertia and a restoring force proportional to displacement from a central state. The most obvious electrical version of this is the combination of inductance and capacitance, and at moderate frequencies the LC resonant circuit seemed a natural part of most tuned systems. Perhaps a hint of the future lay in the low-frequency RC oscillator which avoided the use of an inconveniently large inductance. Now we have integrated circuits which are unable to produce reason-

able magnitudes of either L or C but are appropriate for digital working with an external driving clock.

This brings us to consider Walsh functions⁸ as an alternative to trigonometric functions. The use of non-sinusoidal signals has been surveyed in detail by Harmuth⁹ who has shown how to construct (with operational amplifiers) circuits analogous to the ordinary resonant circuits, but which respond selectively to particular non-sinusoidal waveforms. Direct digital transmission (without a carrier) is used for high-speed transmission over optical fibres; and Harmuth describes the use of a radar with non-sinusoidal waveform for the detection of buried pipes. As long as one is concerned with local or confined transmission there is no problem, though in optical fibres one may tend to go to a frequency description of the dispersion as a property of the medium, while still speaking of a time delay to the signal. But modulated sinusoids seem essential in free radio communication for three reasons:

1. Maxwell's equations imply sinusoidal radiation.
2. Changing the whole world's "channel" allocations from frequency-division to time-division would be a worse problem than changing the rule of the road from right to left throughout Europe and America - for in the radio case it would be necessary for everyone throughout the world to change simultaneously.
3. Time-division would require synchronism with a world-wide standard clock, in phase as well as frequency, and this could not be maintained over a long distance of propagation.

It therefore seems that modulated-carrier radio, and thus sidebands, will be with us for the foreseeable future. WW

References.

1. D. C. Sutherland, *Wireless World*, vol. 88, p.50, June 1982.
2. J. Robinson, The Stenode, *Wireless World*, vol. 28, pp. 9-11, January 7th, 1931.

3. R. T. Beatty, Apparent Demodulation of a Weak Station by a Stronger One, *Experimental Wireless*, vol. 5, pp. 300-303, 1928.
4. S. Butterworth, Apparent Demodulation of a Weak Station by a Stronger One, *Experimental Wireless*, vol. 6, pp. 619-621, 1929.
5. F. M. Colebrook, A Further Note on the Apparent Demodulation of a Weak Station by a Stronger One, *Wireless Engineer*, vol. 8, pp. 409-412, 1931.
6. E. V. Appleton and D. Boohariwalla, The Mutual Interference of Wireless Signals in Simultaneous Detection, *Wireless Engineer*, vol. 9, pp. 136-139, 1932.
7. D. Gabor, Theory of Communication, *Journ. I.E.E.*, vol. 93, part III, pp. 429-441, 1946.
8. Thomas Roddam, The Function of Functions. An Approach to Walsh Functions from Telecommunications History. *Wireless World*, vol. 87, pp. 36-39, December 1981.
9. H. F. Harmuth, Nonsinusoidal Waves for radar and radio communication. Academic Press, 1981 (Advances in Electronics and Electron Physics, Supplement 14).

continued from page 62

The author

Mr Tierman is currently manager of British Telecom's Prestel computer network. He has spent the last 12 years being largely concerned with the design and management of on-line computer systems for use within British Telecom, and the LACES air cargo control scheme. Prior to that, 12 years RAF service was spent in close company with radar and associated computers. This article is the result of a consuming interest in audio systems, to which much of his leisure time has been devoted in the past 25 years.

Construction

The only item mounted directly on the main front panel are the 4mm sockets for Sync, Common, and output; a 5 pin DIN socket with pins 2 and 3 connected to Common and output respectively; and the led D₃.

With one exception, there were no special screening or wiring constraints observed in making up the unit, but there has been a penalty in so far as there is some slight, but obvious, high-frequency breakthrough at the output (thought to be picked up at the junction of R₁₃/R₁₅) when the attenuators are set for something less than maximum output. The exception is the connexion between P₂ and TBG/B; this is a link between two high-impedance points and a screened lead should be used to prevent spurious triggering of IC_{2/1} via Tr₄. There may also be slight notching of the output sinewave at points corresponding to the switching of IC_{2/1}, and this may be minimized by using a 4069 (hex. inverter) i.c. for IC₂ in place of the 4584. If

this is done, the led driver circuit will not work properly on battery operation and C₁₆/R₂₉ should be omitted.

Readers who would like copies of Mr Tierman's suggested p.c.b. pattern sketches should send a stamped, addressed envelope to *Wireless World*, Room L302, Quadrant House, The Quadrant, Sutton, Surrey. Mark the envelope 'Oscillator'. WW

Wireless World index and binding

The index for Volume 8 (1982) of *Wireless World* is now available, price 75p including postage, from the General Sales Department, IPC Electrical-Electronic Press Ltd, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Our publishers also offer a service of binding volumes of *Wireless World*, each complete with the appropriate index. If you wish to use this service send your copies to Press Binders Ltd, 4-4a Iliffe Yard, Crampton Street, Walworth, London, SE17 with your name and address enclosed. Confirm your order to the General Sales Department (address in first paragraph) and with this letter to Quadrant House send a remittance of £6.90 for each volume (this price includes the index).

In both cases cheques should be made payable to IPC Business Press Ltd.

LITERATURE RECEIVED

Motorola now manufactures some 15,000 semiconductor devices and selection can be somewhat overwhelming. To make it easier they have published a **European Master Selection** which lists approximately 4,000 preferred devices that correspond to the majority of customers' needs in Europe. This is still quite a daunting volume but includes all the microcomputer components, integrated circuits for digital and linear operation; a wide selection of discrete components and packaged devices for hybrid circuits. Motorola Ltd, York House, Enfield Way, Wembley, Middlesex. WW401

The Technit 10-section **Electro Magnetic Interference Shielding Design Guide** is a source of reference for design engineers who are faced with EMI shielding problems. It is available from MCP Electronics Ltd. 38 Rosemount Road, Wembley, Middlesex. WW402

Perdix Components, of 98 Crofton Park Road, London SE4, have expanded with five new divisions and have produced a product guide to list the components available. There are liquid crystal, vacuum fluorescent and gas plasma display panels; switching power supplies; microprocessor application boards and video monitors. WW403

Within the Catalogue of the **Open University Press** is a technology section which includes some interesting titles on the social implications of technology. *The Future of the Printed Word* is a collection of papers edited by P. Hills. A book by David Collingridge is entitled *The Social Control of Technology*. There is also *The Future with Microelectronics* by I. Barron and R. Curnow, and *Microelectronics and Society* edited by T. W. Jones. The books are not written for specific OU courses. WW404

NEW PRODUCTS

'SIMPLE' LOGIC ANALYSER

A microprocessor-based logic analyser with a minimum of controls, the 7600, has been added to Enertec Instrumentation's range of laboratory instruments. Screen information is divided into two sections, one containing processed and labelled data from the analyser and the other containing prompts for the operator, supplemented by l.e.d. indications on the control keys. One of two 4096-bit memories is used for data storage, in either four, eight, 16 or 32-bit-word form, and the other is a truth-table memory. Four possible operating modes are automatic step, manual step, externally-triggered step and 'halt-if-different-from-truth-table'. Stored data can be displayed in seven different ways. When operated synchronously, the 7600 has a frequency range of 0 to 30MHz, or, when operated asynchronously, up to 100MHz, with thresholds adjustable in 50mV steps between $\pm 6.35V$. Propagation delay difference between channels is 5ns and glitches 10ns wide at 3V p-p can be detected. Enertec Instrumentation Ltd, Progress House, Albert Road, Aldershot, GU11 1SZ. **WW301**


DISPLAYS

Liquid-crystal displays from Sharp with 240 by 64-dot matrixes, orange and green 40-character by 12-line plasma displays from Oki, and colour and monochrome monitors for low and high-resolution applications are stocked by an offspring of the Vako group formed in June called Vako Display Systems Ltd. VDS claim to be one



of the few companies that stock the whole Sharp display range, including a 40-by-two-line character display, and they supply Oki plasma displays for graphics and character applications. They also supply 5½ to 12in monochrome chassis monitors with various phosphors and 12 to 20in colour monitors for either low or high resolution. These products will be shown at the Electronic Displays Exhibition on October 5, 6 and 7 at the Kensington Exhibition Centre. Vako Display Systems Ltd, Pass Street, Werneth, Oldham, Manchester OL9 6HZ. **WW302**

WIRELESS WORLD OCTOBER 1982

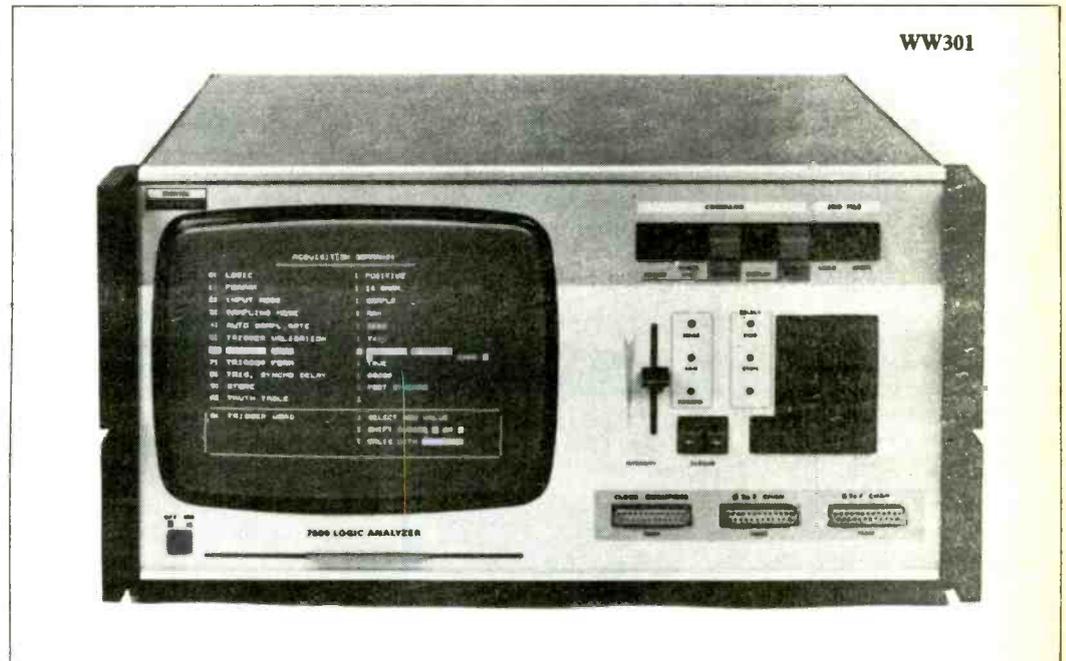

STORAGE FOR PETS

Eproms are the basis of Progstor — a unit which turns the Pet into a dedicated microcomputer with a selectable initiate-on-switch-on facility that makes the computer suitable for use by untrained operators. The program for the task concerned is written in Basic or machine-code or both and then, after debugging, is automatically stored in between 2 and 28Kbyte of eprom (2716 or 2732), so mechanically less reliable and physically more vulnerable magnetic-storage media are not required. Progstor, mounted inside the computer, can be set to operate automatically when the computer is switched on, or on receipt of a system command, and is intended for use in hostile environments, by untrained operators and in any application where the same program is used frequently. Of course, it may also be used as an eprom programmer. Microscience, P.O. Box 14, Bramhall, Stockport, Cheshire SK7 2QS. **WW303**

VIDEO PRINTER

Hard copy can be obtained from any standard composite video signal using an electro-sensitive dot-matrix printer called the TP55 from Thandar Electronics. Both positive and negative prints of information on the screen can be produced, on a 5in-wide paper roll, in 12 seconds for normal resolution, which gives 480 by 350 points, or 24 seconds for high resolution, giving 480 by 640 points. We rang to check whether a decimal point had been left out of the price, stated

as £753. There wasn't, but we were told that the actual price is £737. Thandar Electronics Ltd, London Road, St Ives, Huntingdon, Cambs PE17 4HJ. **WW304**

64K EPROM

Customers with industrial or commercial applications for a 64K eprom can obtain one free from Rapid Recall. The Intel device concerned is a 2764-4, 450ns eprom which draws 100mA from a 5V supply when enabled or 40mA in standby mode. Other versions, not free, are for $\pm 10\%$ supply-voltage variation tolerance, and with 200, 250 or 300ns access times. Rapid Recall Ltd, Rapid House, Denmark Street, High Wycombe, Bucks. **WW305**

HIGH-VOLTAGE, AND 250W POWER MOSFETS



Two high-voltage mos devices, one rated at 350V, the MTM15N35, and the other called MTM15N40 rated at 400V can dissipate 250W according to a recent product announcement by Motorola. Both 15A transistors have a 0.4 Ω on resistance and 70A peak drain-current rating. Two high-voltage p-channel mosfets, one with a 50V-higher rating than the other at 500V, are also available from Motorola. Both p-channel devices can carry 2A continuous drain currents or 8A peak. Motorola Ltd, York House, Empire Way, Wembley, Middlesex HA9 OPR. **WW306**



NEW PRODUCTS

EXPANSION FOR POPULAR MICROCOMPUTER

English is not the best language that human beings could use from a technical viewpoint, but what is perhaps more important, most English-speaking people believe that it is. Basic, the microcomputer world's equivalent of English, is contested by Forth, even in the domestic microcomputer world (note the introduction of a popular microcomputer from Jupiter Cantab Ltd with Forth as its basic language). This purportedly more practical language is also one subject of four plug-in cartridges from Adda Computers. All four cartridges, of which VicForth with 3K byte of additional memory is one, are designed for the Vic 20 computer. One cartridge of the remaining three has six 24V by 10W relay-switch outputs and two 5-to-12V-'on' d.c. inputs. The remaining two cartridges are statistics-calculation and graph-plotting aids. A forth cartridge costs £38.95 including vat and the other three cartridges cost under £30 including vat. Adda Computers Ltd, Mercury House, Hanger Green, Ealing, London W5 3BA. **WW307**

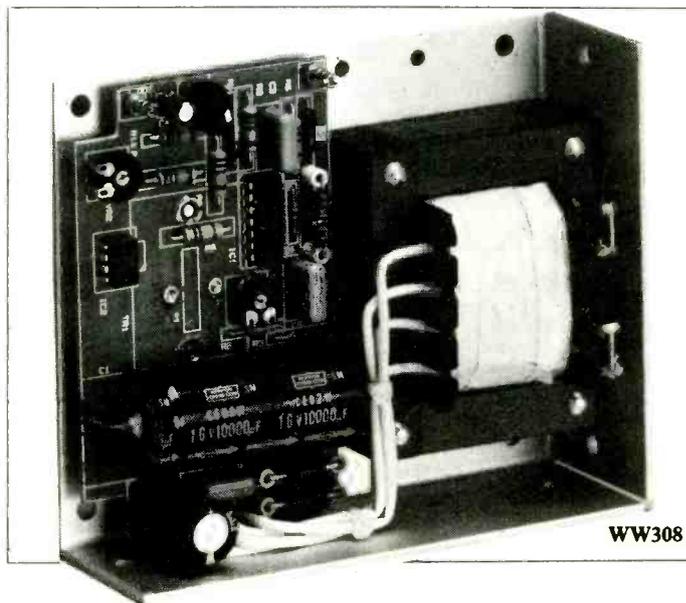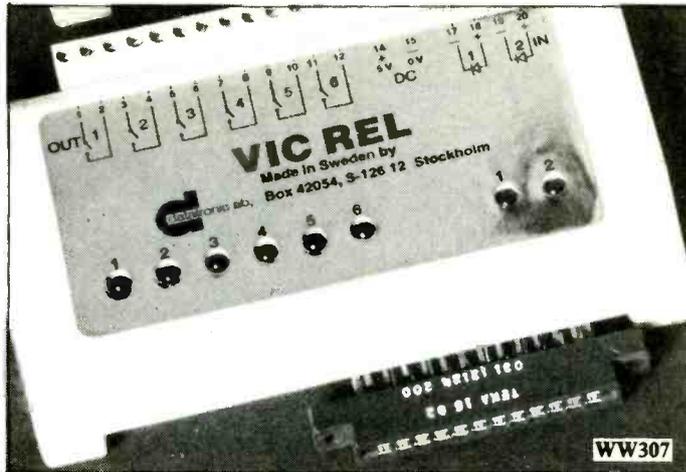


POWER SUPPLIES

Open-frame power supplies providing 5V at 3A and 3.75kV isolation form a new series from ITT Power Components. Efficiency of these units is typically 45% and output ripple 3mV pk-pk. A 10% input-voltage change produces an output change of $\pm 0.05\%$ and transient response is 30 μ s for a 50% load change. Dimensions of the series 15 power supplies are 125 by 102 by 52mm. STC Ltd, Edinburgh Way, Harlow CM20 2DE. **WW308**

1 MEGABYTE FLEXIBLE DISCS

A 5/4in flexible-disc drive similar in appearance and interface requirements to a standard 5/4 in drive but capable of storing one megabyte of data is available from Hi-Tek. 96-track double-sided discs are recorded using the modified frequency-modulation technique through ceramic read/write heads. Up to four CDC 9409T disc drives may be used with one controller. Hard or soft sectorised discs may be used, and a write-protect function is

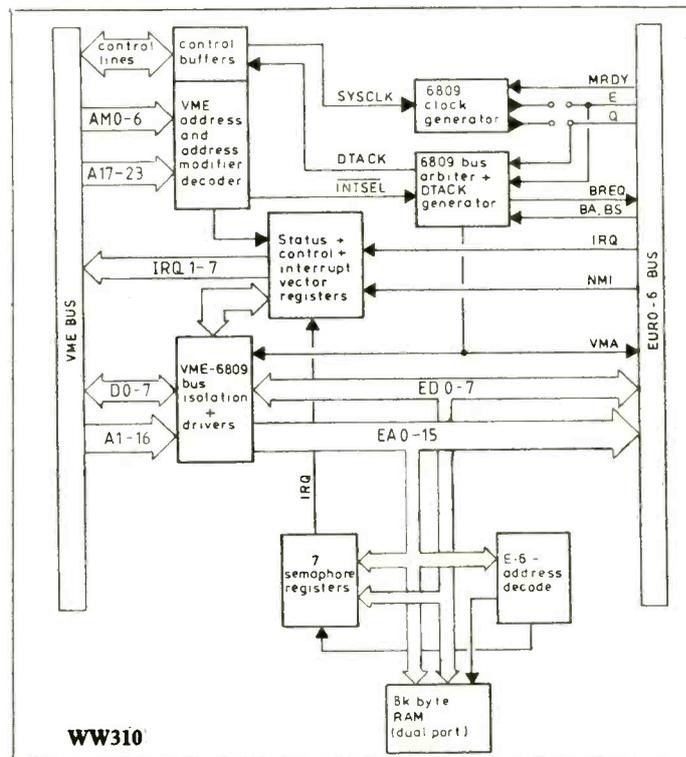

incorporated. Hi-Tek Distribution Ltd, Trafalgar Way, Bar Hill, Cambridge CB3 8SQ. **WW309**

VME-TO-EURO-6 INTERFACE

Connection between 68000-based circuit boards with VME buses (VME is a bus standard for Eurocard boards based on 16/32-bit microprocessors, agreed by a number of companies including Philips/Signetics, Motorola and Mostek) and boards with a Euro-6 bus for 6800, 6802 and 6809-based systems is possible using Euroka's VMEI interface board. With this board, various Euro-6-bus input/output modules designed for 6800 6802 and 6809 processor systems can be used with 68000 VME boards and, using a secondary processor, software written for the 6809 processor can be implemented on 68000 VME systems. Clock signals can be generated for timing i/o boards in single-processor applications, where the clock from a 6809 secondary processor is not present. Hawke Electronics Ltd, Amotex House, 45 Hanworth Road, Sunbury-on-Thames, Middlesex. **WW310**


TURNTABLE KIT

Main elements of this basic turntable kit from Input Design are a synchronous motor, glass platter with felt mat, belt, spindle components, instructions and base-plate drawings, leaving tonearm, plinth, base-plate and cover construction to the customer. The drive motor, claimed to be used in decks costing £350, is manufactured for 110V operation and an inefficient but cheap mains adapting device called a resistor is placed in series with the motor for 240V operation. (Why not have two motors driving together?) The British manufacturers, who also produce another turntable kit and an assembled deck, say they will be pleased to offer any advice, assistance or further information about the product after purchase. Each Home Constructor Turntable kit costs 49.50 including vat (an 'introductory-offer' price of £44 will run until mid-December). Input Designs Ltd, Palace Street, Biggleswade, Bedfordshire SG18 8DP. **WW311**

Professional readers are invited to request further details on items featured here by entering the appropriate WW reference number(s) on the mauve reply-paid card.

Versatower:

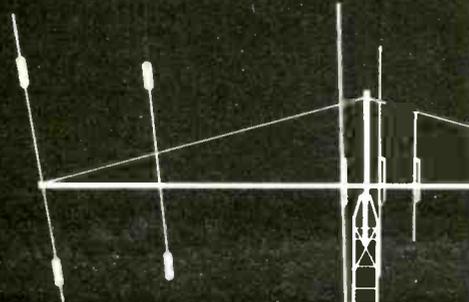
A range of telescopic towers in static and mobile models from 7.5 to 36 metres with tilt-over facility enabling all maintenance to be at ground level.



Designed in accordance with CP3 Chapter V: part 2: 1972 for a minimum wind speed of 85 mph in conditions of maximum exposure and specified by professionals world-wide where hostile environments demand the ultimate in design, quality and reliability.

Suitable for mounting equipment in the fields of:
 Communications
 Security surveillance - CCTV
 Meteorology
 Environmental monitoring
 Geographical survey
 Defence range-finding
 Marine & aero navigation
 Floodlighting
 Airport approach lighting

Further details available on request.

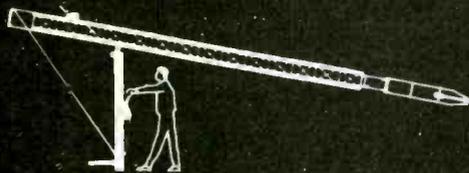

Strumech Engineering Limited,
 Portland House, Coppice Side,
 Brcwnhills, Walsall, West Midlands,
 WS8 7EX, England.
 Telephone: Brownhills (05433) 4321.
 Telex: 335243 SEL G.

WW - 080 FOR FURTHER DETAILS

TOROIDALS



The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

- ★ 294 TYPES TO CHOOSE FROM!
- ★ ORDERS DESPATCHED WITHIN 7 DAYS OF RECEIPT FOR SINGLE OR SMALL QUANTITY ORDERS
- ★ 5 YEAR NO QUIBBLE GUARANTEE

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE
30 VA 70 x 30mm 0.45Kg Regulation 18%	1x010	6+6	2.50	£5.12 +P/D E1 04 -VAT E0 92 TOTAL E7 08
	1x011	9+9	1.66	
	1x012	12+12	1.25	
	1x013	15+15	1.00	
	1x014	18+18	0.83	
	1x015	22+22	0.68	
	1x016	25+25	0.60	
1x017	30+30	0.50		
50 VA 80 x 35mm 0.9 Kg Regulation 13%	2x010	6+6	4.16	£5.70 +P/D E1 30 -VAT E1 05 TOTAL E8 05
	2x011	9+9	2.77	
	2x012	12+12	2.08	
	2x013	15+15	1.66	
	2x014	18+18	1.38	
	2x015	22+22	1.13	
	2x016	25+25	1.00	
	2x017	30+30	0.83	
80 VA 90 x 30mm 1 Kg Regulation 12%	3x010	6+6	6.64	£6.08 +P/D E1 07 -VAT E1 16 TOTAL E8 91
	3x011	9+9	4.44	
	3x012	12+12	3.33	
	3x013	15+15	2.66	
	3x014	18+18	2.22	
	3x015	22+22	1.81	
	3x016	25+25	1.60	
	3x017	30+30	1.33	
	3x028	110	0.72	
	3x029	220	0.36	
3x030	240	0.33		
120 VA 90 x 40mm 1.2 Kg Regulation 11%	4x010	6+6	10.00	£6.90 +P/D E1 67 -VAT E1 29 TOTAL E9 86
	4x011	9+9	6.66	
	4x012	12+12	5.00	
	4x013	15+15	4.00	
	4x014	18+18	3.33	
	4x015	22+22	2.72	
	4x016	25+25	2.40	
	4x017	30+30	2.00	
	4x018	35+35	1.71	
	4x029	220	0.54	
4x030	240	0.50		
160 VA 110 x 40mm 1.8 Kg Regulation 8%	5x011	9+9	8.89	£7.91 +P/D E1 57 -VAT E1 44 TOTAL E11 02
	5x012	12+12	6.66	
	5x013	15+15	5.33	
	5x014	18+18	4.44	
	5x015	22+22	3.83	
	5x016	25+25	3.20	
	5x017	30+30	2.66	
	5x018	35+35	2.28	
	5x026	40+40	2.00	
	5x028	110	1.45	
5x029	220	0.72		
5x030	240	0.66		

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE
225 VA 110 x 45mm 2.2 Kg Regulation 7%	6x012	12+12	9.38	£9.20 +P/D E2 00 -VAT E1 86 TOTAL E12 88
	6x013	15+15	7.50	
	6x014	18+18	6.25	
	6x015	22+22	5.11	
	6x016	25+25	4.50	
	6x017	30+30	3.75	
	6x018	35+35	3.21	
	6x026	40+40	2.81	
	6x025	45+45	2.50	
	6x033	50+50	2.25	
300 VA 110 x 50mm 2.6 Kg Regulation 6%	7x013	15+15	10.00	£10.17 +P/D E2 00 -VAT E1 83 TOTAL E14 00
	7x014	18+18	8.33	
	7x015	22+22	6.82	
	7x016	25+25	6.00	
	7x017	30+30	5.00	
	7x018	35+35	4.28	
	7x026	40+40	3.75	
	7x025	45+45	3.33	
	7x033	50+50	3.00	
	7x028	110	2.72	
500 VA 140 x 60mm 4 Kg Regulation 4%	8x016	25+25	10.00	£13.53 +P/D E2 35 -VAT E2 38 TOTAL E18 26
	8x017	30+30	8.33	
	8x018	35+35	7.14	
	8x026	40+40	6.25	
	8x025	45+45	5.55	
	8x033	50+50	5.00	
	8x042	55+55	4.54	
	8x028	110	4.54	
	8x029	220	2.27	
	8x030	240	2.06	
625 VA 140 x 75mm 5 Kg Regulation 4%	9x017	30+30	10.41	£16.13 +P/D E2 50 -VAT E2 79 TOTAL E21 42
	9x018	35+35	8.92	
	9x026	40+40	7.81	
	9x025	45+45	6.94	
	9x033	50+50	6.25	
	9x042	55+55	5.88	
	9x028	110	5.58	
	9x029	220	2.84	
	9x030	240	2.60	

IMPORTANT: Regulation - All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders.

Also available at Electrovalue, Maplin and Technomatic.

Please send _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

Post to: ILP Electronics Ltd., Freepost 5, Graham Bell House, Roper Close

Canterbury CT2 7EP, Kent, England

Telephone Sales (0227) 54778; Technical (0227) 64723; Telex 965780.



ILP
TRANSFORMERS
 (a division of
 I.L.P. Electronics Ltd)

WW - 068 FOR FURTHER DETAILS

BBC Micro Computer

Now available from stock



BBC Model B **£399**
(incl. VAT)
(Carr £8/unit)
Model A to Model B
upgrade kit **£60.00**
Fitting charge **£20.**

MEMORY UPGRADE
8 × 4816 AP-3 100ns
£21.60
F.D. INTERFACE KIT
IC 77-78 **£70.00**

ANALOGUE PORT KIT
IC 73, SK6 **£7.30**
RS423 & VDU Port Kit
£10.80

PRINTER & USER PORT KIT
IC 69, 70, 71 PL9, 10 **£9.50**
Bus & Tube Port Kit **£6.50**

OFFICIAL **BBC** DEALER

All mating Connectors with Cables in stock.

Full range of ACORNSOFT, PROGRAM POWER & BUGBYTE SOFTWARE AVAILABLE

Phone or send for our BBC leaflet

BBC FLOPPY DISC DRIVES
Single 5¼" Drive **£200 + £3 p&p**
Dual 5¼" Drive **£335 + £5 p&p**

CASSETTE RECORDER

Sanyo Computer Grade Recorder
£24.50 + £1.50 Carr
Cassette Leads £3.50
Computer Cassette £0.50 ea.
£4.50 for 10



NEC PC 8023 BE - C
100CPS, 80 cols
Logic Seeking, Bi-directional,
Forward and Reverse
Line Feed,
Proportional Spacing,
Auto Underline,
Hi-Res and Block
Graphics, Greek Char.
Set.
Only **£340 + Carr**
£8.00



MONITORS

BMC BM1401 14" Colour Monitor
RGB Input 18 MHz Bandwidth
400 dots at Centre 25 × 40 Char.
£240 + £8.00 Carr
BMC 12" Green Monitor
Composite Input
18MHz Bandwidth
£99 + £6.00 Carr

ACORN ATOM


8K + 2K Built 1135 12K + 12K
Expanded £175
8K + 5K + Colour Card £170
(Carr £3/unit)
Atom Disc Pack £299 + £6 Carr
3A 5v Regulated £26 + £2 Carr
Atom PSU £7.00 + 70p Carr
Full Range of Atomsoft in stock.
Phone/send for our ATOM LIST

PRINTERS

SEIKOSHA GP 100A
80 cols 30 CPS
Single and Double Width
Char.
Full Graphics, 10" wide
paper
Tractor Feed Standard
Friction Optional
Now only **£175 + £6 Carr**

Parallel Printer lead for BBC/Atom **£13.50**
Variety of interfaces, ribbons in stock.
2,000 fan fold sheets 9½" × 11" **£14 + £3 p&p**


EPSON MX 80 and 100F/T3

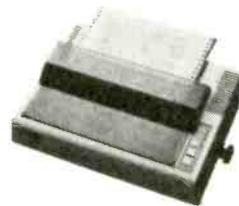

MX 80 80CPS 80 cols
MX 100 100CPS
136 cols
Logic Seeking, Bi-directional,
Bit Image Printing,
9 × 9 Matrix
Auto Underline
MX 80 F/T3 **£330**
MX 100 F/T3 **£430**
(£8 Carr/Printer)

MICRODOCTOR

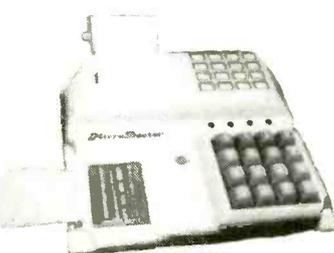This is not a logic analyser or an oscilloscope. It tests a microsystem and gives a printed re-print on RAM, ROM and I/O - it will print memory map, search for code, check dataline shorts and operates peripherals and even disassembles the ROM.
Microdoctor complete with psu, printer probe cable and two configuration board **£295.**



EP4000 EMULATING PROGRAMMER

This EPROM programmer will accept most single and three rail eproms by simple rotary switch personality selection. Output to TV and monitor. Comprehensive I/O Ports - TTL and RS232 20 mA current Loop, parallel port, cassette I/O, printer port and DMA. **£545 + £8.00 Carr.**

P4000 PRODUCTION PROGRAMMER

This unit offers simple and reliable programming of up to 8 EPROMS simultaneously. Self-check - blank check - program and verify sequence built in. **£545 + £8 Carr.**
BP4 - TI Bi-polar Prom Programming module for EP4000. This module will program most TI devices and read equivalent devices from other manufacturers enabling copies to be made. **£180 + £6 Carr.**

SOFTY II INTELLIGENT PROGRAMMER

The complete micro processor development system for Engineers and Hobbyists. You can develop programs, debug, verify and commit to EPROMS or use in host computer by using softy as a romulator. Powerful editing facilities permit bytes, blocks of bytes changed, deleted or inserted and memory contents can be observed on ordinary TV. Accepts most +5v Eproms
Softy II complete with PSU, TV Lead and Romulator lead **£169**

MENTA

A sophisticated Z80 development system and trainer. Powerful keyboard assembler and program debugging facility. Audible feedback on keyboard input. Menta and PSU and TV Lead **£115.**

UV ERASERS

UV1B up to 6 Eproms **£47.50**
UV140 up to 14 Eproms **£61.50**
UV1T with Timer **£60.00**
UV141 with Timer **£78.00**
(Carr £2/eraser)
All erasers are fitted with mains switches and safety interlocks.

TRAINER KITS

6502 Junior Computer **£85.00**
6809 Nanocomp II ... **£80.00**
1802 Micro Trainer **£64.00**
6802 Nanocomp I ... **£80.00** Full details on request

RUGBY ATOMIC CLOCK

This Z80 micro controlled clock/calendar receives coded time data from NPL Rugby. The clock never needs to be reset. The facilities include 8 independent alarms and for each alarm there is a choice of melody or alternatively these can be used for electrical switching. A separate timer allows recording of up to 240 lap times without interrupting the count. Expansion facilities provided.
See July/August ETI for details. Complete Kit **£120 + £2 p&p**

BOOKS

(No VAT p&p £1)

CMOS Cook Book **£7.75**
CRT Controller H/Book **£5.95**
Programming the Z80 **£11.50**
Z80 Microcomp handbook **£6.95**
Programming the 6502 **£10.25**
6502 Assy. Lang **£12.10**
6502 Applications **£10.20**
6502 Software Design **£9.05**
6502 Games **£10.25**
Large selection of databooks, interfacing books, books on BBC, etc in stock. Ask for our list.

★ COMMUNICATIONS TEST EQUIPMENT ★

MARCONI TF2002. AM Signal Generators. 10KHz-72MHz. Also 2002A/S available AM/FM 10KHz-72MHz.

MARCONI TF995A. 2-216MHz. AM/FM £200

MARCONI TF1066B/1. AM/FM Signal Generator. 10-470MHz 0.2uV-200mV output. FM Deviations up to ±100KHz from 30Hz-15KHz £550

MARCONI TF995A/5. AM/FM Signal Generator. Narrow deviation model 995 covering 1.5-220MHz £450

MARCONI TF1064B/5. FM Signal Generator covering in three ranges 68-108, 118-185 and 450-470MHz. Modulation FM fixed deviations of 3.5 and 10KHz. AM fixed 30% £225

MARCONI TF791D. FM Deviation meter £185

★ 'DOLBY' NOISE WEIGHTING FILTERS ★

Cat. No. 98A. Noise weighting filters for CCIR/ARM signal-to-noise ratio measurements. As new units. £40 each (+£1 p&p).

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.). Counting up to 15 turn "Helipot". Brand new with mounting instructions. Only £2.50 each.

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.). Counting up to 15 turn "Helipot". Brand new with mounting instructions. Only £2.50 each.

★ AUDIO WATTMETERS ★

Switchable 1W & 10W FSD. Internal 3.5 & 8 Ohm load impedances. Housed in grey enamelled case 6x6x3". Large easy to read 3" sq. meter. Scope output provision. £10 (+£1).


HEATHKIT Model AW-IU. Internal load switchable 3, 8, 15 & 600 Ohm. Meter scaled 0-50W (+dB scale). 5 Ranges from 5mW-50W FSD. Mains powered. £25 (+£1).

MARCONI TF893A. 1mW-10W Full scale in 5 ranges. Impedances 2.5-20K Ohm in 48 steps. Direct calibration in Watts and dBm. £85 (+£2).

GPO JACK SOCKET STRIPS. 20-WAY Type 320 (3-pole) £2.50 ea. Type 520 (3-pole with switching contacts) £4 ea. Please include 35p each for postage on these. GPO type 316 jack plugs for above 20p ea. (10+ post free). Plus VAT please.

PHILIPS Model PM6456/01 FM STEREO GENERATOR. RF Output frequency 1MHz Standardised Stereo multiplex output signal. As new with handbook. £195.

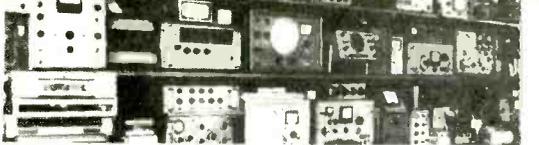P. F. RALFE ELECTRONICS
10 CHAPEL STREET, LONDON, NW1 TEL: 01-723 8753



★ OSCILLOSCOPES ★

SOLARTRON CD1740 System. DC-50MHz Sweep Delay Timebase £375

SOLARTRON CD1400. DC-15MHz £125

TEKTRONIX 585. Twin Timebase c/w two 2A63 Y-Amps (DC-300KHz. 1mV).

DYNAMCO D7200. Mains/battery portable. DC-15MHz £250

COSSOR CDU150. DC-35MHz £200

TELEQUIPMENT D53 £150

TEKTRONIX 454. DC-150MHz £750

SPECIAL PURCHASE OF TEKTRONIX 454 PORTABLE OSCILLOSCOPES

Tektronix 454 DC-150MHz dual-beam oscilloscopes in stock now. 5mV/cm Y-amplifier (1mV cascaded). 2.4ns risetime. Calibrated sweep delay. We can offer these units in first-class operational condition complete with three months' guarantee, for a once only price of £750.



MARCONI Component Bridges. Models TF1313 and TF2700 in stock.

ADVANCE VM77D Millivoltmeters. 15Hz-4.5MHz. 1mV Full scale -300V AC £55

WOELKE ME104C. Wow & Flutter Meter £95

AVO Type 1 LCR Component Bridge.

WAYNE KERR AF Signal Generator Type S121 £75

AIRMEC Wave Analysers Models 853 and 248A.

CENTRONICS P1 Printer, one only. AND Type 663 Printer.

ROHDE & SCHWARZ SDR Signal Generator. 300MHz-1GHz.

HEWLETT PACKARD 608C Signal Generator. 10-480MHz AM.

BELL & HOWELL MICROFICHE VIEWERS

Type SR5. Screen size 9x5". Recent small quantity now avail. £55

★ TEXSCAN SWEEPERS ★

Texscan Model VS40 Sweep Generators. 0-300MHz. Internal Markers. Also available Texscan PU-88 X-Y Monitor.

CABLE & WIRELESS

Telegraph Signalling Twin DC Power supply units. 240V AC Input. DC output 80.0-80V. Dimensions 8x7x19". Model No. DD30. Price ea. £12.50. Carriage £1.50.

PLEASE NOTE. All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry a three months guarantee. For our mail order customers we have a money-back scheme. Repairs and servicing to all equipment at very reasonable rates. PLEASE ADD 15% VAT TO ALL PRICES.

★ DC POWER SUPPLIES ★

1. APT.10459/8. Stabilised Regulated supplies: New stock arrival hence LOWER PRICES. Available in preset output voltages between 6 and 30V DC (state requirements) ±4V approx. Three sizes available, 5A, 7½A & 10A. Prices £20, £25 & £30 respectively (+£2 p&p & VAT).

2. Mullard Dual supplies. Pos/Neg 12V @ 1A & 0.4A. Dimensions 9x4x5". £10 ea. (+£1 p&p).

3. Farnell Current limited. 13-17V DC @ 2A. £15. 27-32V DC @ 1A. £15 (+£1 p&p).

4. Lambda LXS Series supplied 110V AC Input. 5V @ 14A. £20 (+£2.50 p&p). Various other voltages available from stock in small quantity.

5. Coutant 5/6V @ 5A. Small size (7x5x3"). £20 (+£1).

6. Variable 0-30V @ 1A. Volt-metered. £30.

7. Farnell 5V Switching. 60A. £85.

★ RF SIGNAL GENERATORS ★

ADVANCE Type E2. 100KHz-100MHz. Internal AM & Audio O/P. 1uV-100mV output. Price each £50 inc. VAT.

TAYLOR Type 68A/M. 100KHz-240MHz. Internal Modulation. £60 inc. VAT.

All of these units are in full working condition and carry our usual 90-Day Warranty. In both cases please add £2 each for carriage

★ MILLI-VOLT MEASUREMENT, ANALOGUE ★

MARCONI TF2800. Twelve ranges 1mV-300V FSD. Wide-band to 10MHz.

MARCONI TF2803. Frequency range 50KHz-1.5GHz. High Sensitivity from 300uV.

MARCONI TF2804. Electronic Multi-meter. AC/DC 300mV Full scale to 300V (1kV DC). Resistance ranged. AC Frequency range 20Hz-1500MHz.

★ BRUEL & KJOER ★

Model 2006 Heterodyne Voltmeter. AM/FM/voltage measurements to 240MHz.

★ ROTRON INSTRUMENT COOLING FANS ★

Supplied in excellent condition, fully tested.

115V. 4.5x4.5x1.5" £4.50. 230V £5.

115V. 3x3x1.5" £4 + postage ea. 35p.

Happy Memories

Part type	1 off	25-99	100 up
4116 200ns	.83	.72	.66
4116 250ns	.75	.65	.60
4816 100ns For BBC comp	2.45	2.10	1.95
4164 200ns	4.95	4.55	4.20
2114 200ns Low power	1.15	1.00	.90
2114 450ns Lower power	.95	.85	.80
4118 250ns	3.25	2.85	2.65
6116 150ns CMOS	3.70	3.20	3.00
2708 450ns	2.60	2.25	2.10
2716 450ns 5 volt	2.60	2.25	2.10
2716 450ns three rail	5.75	5.00	4.65
2732 450ns Intel type	3.95	3.45	3.25
2532 450ns Texas type	3.95	3.45	3.25

Z80A-CPU £4.35 Z80A-P10 £3.25 Z80A-CTC £3.25
6522 PIA £3.98 7805 reg. .50 7812 reg. .50

Low profile IC sockets: Pins 8 14 16 18 20 22 24 28 40
Pence 9 10 11 14 15 18 19 25 33

Soft-sectored floppy discs per 10 in plastic library case:
5 inch SSSD £17.00 5 inch SSDD £19.25 5 inch DSDD £21.00
8 inch SSSD £19.25 8 inch SSDD £23.65 8 inch DSDD £25.50

74LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or phone for list.

Please add 30p post and packing to orders under £15 and VAT to total
Access & Barclaycard welcome
24-hour service on (054 422) 618
Government and Educational orders welcome £15 minimum
Trade accounts operated, phone or write for details

HAPPY MEMORIES (WW)
Gladesty, Kingston
Herefordshire HR5 3NY
Tel: (054 422) 618 or 628

P.&R. COMPUTER SHOP

IBM GOLFBALL PRINTER 3982, £70 EACH + VAT

NEW CENTRONIC 779 PRINTERS, £325 + VAT
NEW CENTRONIC 781 PRINTERS, £350 + VAT
LA DECK WRITERS MODS. 35, 36 & 180, FROM £325 + VAT. ALL NEW
NEW CIFA VDUs. 1 ONLY £300 + VAT
POWER UNITS 5 VOLT 6 AMP, £20 EACH
FANS, PCBs, KEYBOARDS AND LOTS OF ODDS & ENDS

COME AND LOOK AROUND
SALCOTT MILL, GOLDHANGER ROAD
HEYBRIDGE, ESSEX.
PHONE MALDON (0621) 57440

WW - 069 FOR FURTHER DETAILS

DIGITAL CIRCUITS

READY REFERENCE MANUAL

by Markus COMMUNICATION CIRCUITS, READY, REF. MANUAL	Price: £10.50
by Markus ELECTRONIC PROJECTS, READY REF MANUAL	Price: £10.50
by Markus POPULAR CIRCUITS READY REF. MANUAL	Price: £10.50
by Markus ENCYCLOPAEDIA OF INTEGRATED CIRCUITS	Price: £18.00
by Buchsbaum DIGITAL INTEGRATED ELECTRONICS	Price: £10.00
by Teub INTRO. TO PASCAL 2ND EDITION	Price: £9.00
by Welsh MACHINE CODE AND BETTER BASIC	Price: £8.50
by Stewart MICROPROCESSOR DEVELOPMENT & SYSTEMS	Price: £17.00
by Teong MICROPROCESSOR SYSTEM DESIGN VOL II	Price: £23.00
by Klengitman	

★ PRICES INCLUDE POSTAGE AND PACKING ★

THE MODERN BOOK CO.
Specialist in scientific and technical books
15/21 PRAED ST., LONDON W2 1NP
PHONE: 01-402 9178 - Closed SATURDAY 1 p.m.
Please allow 14 days for reply or delivery

WW - 036 FOR FURTHER DETAILS

Well worth looking into TELEVISION

October issue ON SALE NOW 80p

GARBLEDEGOOK

A look at Teletext reception problems.

FREQUENCY SYNTHESIS TUNING

We explain theory and practice behind something which is now becoming prominent in continental and up-market British TVs.


MICROCOMPUTER CONTROL

The concept and possibilities of future and present uses in VCRs and TVs.

PLUS
TV4 VCR
servicing—
news—
developments.
GET A COPY TODAY

**International
TV Standards Chart
to pull-out and
display. Notes on most
countries' systems
and voltages.**

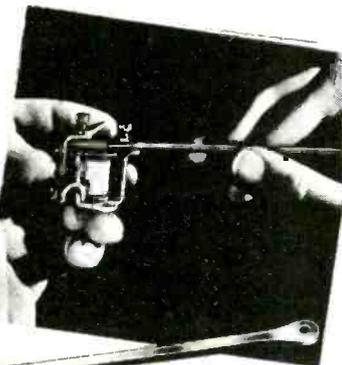Keep those Contacts CLEAN BY USING A DIACROM SPATULA



Manufactured in France
British Patents applied for

No other cleaner has all these advantages:—

1. Only 100% pure, natural diamond grains are utilised.
 2. Blades are treated with hard chrome to reinforce the setting of the diamond grains, to obviate loosening or breakaway during use. This process also prevents clogging of the diamonded surface by residues resulting from use.
 3. All diamonded blades are rectified to ensure an absolutely smooth surface by eliminating diamond grains which may rise above the surface. This eliminates all excessive scratching during use.
 4. All diamond grains are rigidly calibrated to ensure a perfectly uniform grain size of either 200, 300 or 400.
 5. The chrome gives a very weak co-efficient of friction and the rigidity of the nylon handle is calculated to permit proper utilisation and yet pliant enough to avoid undue pressures on highly delicate relays.
- Grain size 200, thickness 55/100 mm., both faces diamonded. For quick cleaning of industrial relays and switching equipment, etc.
 - Grain size 300, thickness 55/100mm., both faces diamonded. For smaller equipments, like telephone relays, computer relays, etc.
 - Grain size 400, thickness 25/100 mm., one face diamonded. For sensitive relays and tiny contacts. Two close contacts facing each other can be individually cleaned, because only one face of the spatula is abrasive.

**Sole Distributors for the United Kingdom
SPECIAL PRODUCTS (DISTRIBUTORS) LTD**

81 Piccadilly, London W1V 0HL. Phone: 01-629 9556

As supplied to the M.O.D., U.K.A.E.A., C.E.G.B. British Rail and other Public Authorities;
also major industrial and electronic users throughout the United Kingdom.

WW - 087 FOR FURTHER DETAILS


The NEW KEF Constructor Series

A new generation of drive units from KEF is now available to the home constructor.

KEF's drive units have been improved in terms of reducing audible colouration as a result of the detailed analysis of speaker vibrational characteristics, using computer aided techniques.

Now the improved units and complete technical data on them are available to you to build a system to your own design or to use in any prescribed combinations to complete a system designed by KEF.


DRIVE UNITS

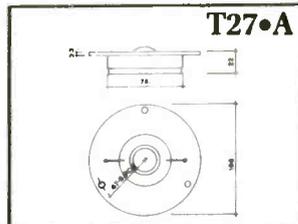


Melnex dome high frequency unit with extended frequency response and wide dispersion.



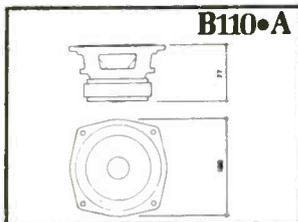Low colouration dome high frequency unit with extended frequency response.



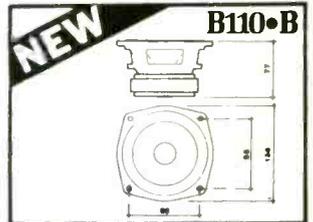
Compact, bass/mid range unit, suitable for use in either a compact full range system, or as a specialised mid range unit in a multi-way system.



Long throw bass/mid range unit, suitable for use in either a compact full range system, or as a specialised mid range unit in a multi-way system.



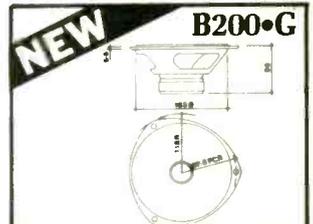Low frequency unit with foil-stressed expanded polystyrene diaphragm and highly compliant surround, suitable for totally enclosed box, reflex, transmission line, horn and other specialised low frequency applications.



Low/mid range unit with visco-elastic damped Bextreme diaphragm and high temperature voice coil assembly, suitable for use where low distortion and high power handling are required.

KEF

The Speaker Engineers

KEF Electronics Ltd., Tovil, Maidstone, Kent ME15 6QP.
Telephone: (0622) 672261. Telex: 96140.

Please send me complete technical data of
KEF Drive Units

Name: _____

Address: _____

WW/10/82

WW - 031 FOR FURTHER DETAILS



The Answer to Testing Questions




Intra Connector — Intra Switch
Test Clips — Logical Connections — Logical Clips
Ex-Stock Jumpers and Headers

IC TEST CLIPS


Type	Model	Row-to-Row-Dim	Prices
923695	TC-8	.3 inch	6.30
923698	TC-14	.3 inch	3.82
923700	TC-16	.3 inch	4.03
923702	TC-16LSI	.5/6 inch	7.59
923703	TC-18	.3 inch	8.48
923704	TC-20	.3 inch	9.80
923705	TC-22	.4 inch	11.10
923714	TC-24	.5/6 inch	11.77
923718	TC-28	.5/6 inch	12.94
923720	TC-36	.5/6 inch	16.93
923722	TC-40	.5/6 inch	17.82

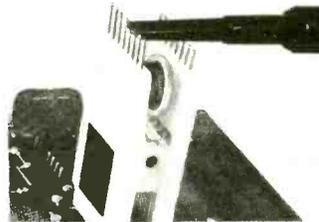Provide full access to integrated circuit DIP leads. Solve probe attachment problems. Simplify prototype and production testing, field service work, and quality control. Removes DIP's damage free. Non-shorting electrical connection. Gold-plated phosphor bronze spring contacts.



LOGICAL CONNECTIONS

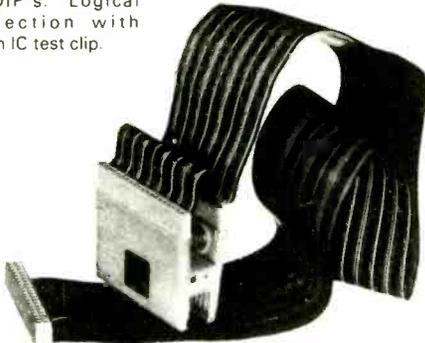Ideal for interfacing with remote logic analyzers. Simplify testing of LSI-DIP's. Logical connection with 40-pin IC test clip.



Type	Model	Remote End Termination	Prices
923880-40	LC-400	No Connector	31.68
923881-40	LC-401	Socket Connector	33.56
923882-40	LC-402	Card-Edge Connector	34.48
923883-40	LC-403	PCB Connector	35.88
923884-40	LC-404	DIP Plug	32.13



We also supply logical connections for 16 and 24 pin. Ask for free colour catalogue.

INTRA-CONNECTOR AND INTRA-SWITCH


Type	Model	Contacts	Prices
922576-20	Intra-Conn.	20	5.10
922576-26	Intra-Conn.	26	5.85
922576-34	Intra-Conn.	34	6.87
922576-40	Intra-Conn.	40	7.63
922576-50	Intra-Conn.	50	8.90

Type	Model	Contacts	Prices
922578-20	Intra-Switch	20	10.18
922578-26	Intra-Switch	26	11.70
922578-34	Intra-Switch	34	13.75
922578-40	Intra-Switch	40	15.27
922578-50	Intra-Switch	50	17.82

Both Intras mate with standard .10" x .10" dual-row connectors.

EXCLUSIVE PRODUCTS TO AP

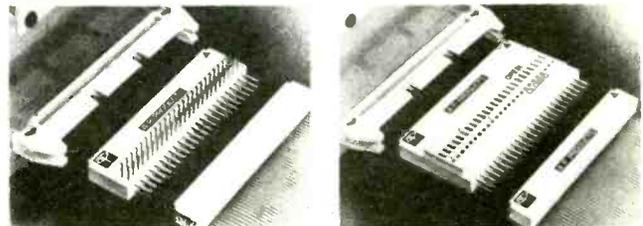Intra-Connector: Provides full access to lines. Permits quick testing of previously improbable circuits. Provides both straight-in and right-angle functions.




Intra-Switch: Allows any line to be opened or closed. Permits instant line-by-line switching for diagnostic or QA testing.

FLAT RIBBON CABLE ASSEMBLIES AND MALE AND FEMALE HEADERS

GREAT JUMPERS Choice of 3 types of end connectors moulded on and factory tested Daisy chain and single-end also available. Ask for Catalogue!

HEADERS For economical attachment of complete matrices of .025" square posts to PC-boards for interconnection systems. 78 different types are available. Ask for Catalogue!

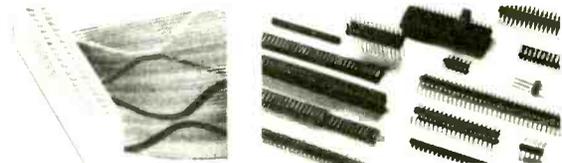Lowest cost of mating two boards together
Please add £2.00 p & p + 15% VAT to all prices.




AP PRODUCTS LTD, PO Box 19, Saffron Walden, Essex
Tel: (0799) 22036

WW - 084 FOR FURTHER DETAILS

HBED

6FT. PARABOLIC DISHES

FROM ONLY £85 PLUS V.A.T.

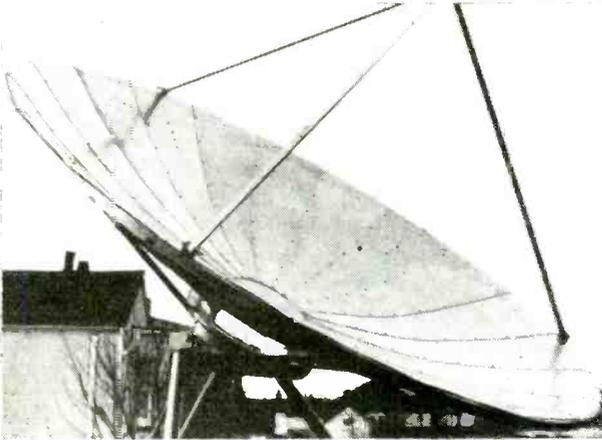

6ft dia. for use in satellite reception and microwave transmissions. 4GHz feed horns and electronics available. Please send s.a.e. for full details and data sheet.

Harrison Bros.

Electronic Distributors

22 Milton Road, Westcliff-on-Sea, Essex SS0 7JX
Tel. Southend (0702) 332338

WW - 073 FOR FURTHER DETAILS

Chiltern Electronics

High Street, Chalfont St Giles, Bucks HP8 4QH

NOTE OUR NEW ADDRESS!!

We now have a superb new computer showroom only 40 minutes from London where hundreds of bargains are on display. Over 1000 sq. ft. of space is devoted to display of processors, VDUs, printers, drives, keyboards, power supplies, monitors and 1001 other items all at incredible low prices. Thousands of bargains for callers.

Check with CHILTERN for . . .

- ★ LOWEST PRICES
- ★ LARGEST STOCK
- ★ BEST SERVICE

SURPLUS COMPUTER EQUIPMENT SALE EVERY SATURDAY

Telephone Enquiries to: Chalfont St Giles
(02407) 71234


The NEW KEF Constructor Series

The ideal design of a loudspeaker system involves the detailed and scientific study of the enclosure, drive units and crossover network. By applying computer aided techniques to the questions of enclosure volume, band width, efficiency, power handling capacity, probable system location and required directional characteristics, KEF have prepared detailed designs for the home constructor. All this experience is now available to you - to help you build your own system - successfully and at the right price.

LOUDSPEAKER DESIGNS


Model CS5

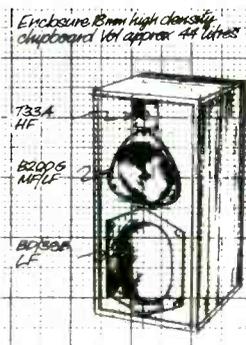This floor standing loudspeaker, based on the KEF Carlton, can provide remarkably sharp stereo imaging due to a novel method of minimising inter-unit time delay, and will produce a full frequency range with outstanding clarity and low distortion.



Model CS7

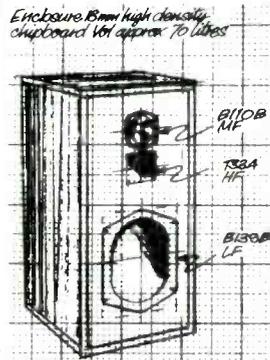A new three way design incorporating the B139, which was the world's first flat diaphragm loudspeaker. The system offers an extended bass response and excellent power handling capability, with the three drive units being combined through a computer designed crossover network to give a very smooth frequency response characteristic with finely detailed reproduction of critical mid-range information.



KEF

Making it together

KEF Electronics Ltd., Tovil, Maidstone, Kent ME15 6QP.
Telephone: (0622) 672261. Telex: 96140.


Please send me details of KEF Systems Designs

Name: _____


Address: _____

WW/10/82

WW - 032 FOR FURTHER DETAILS

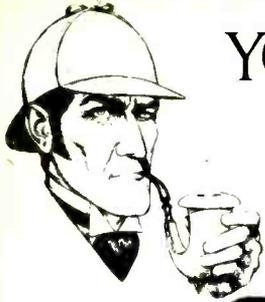

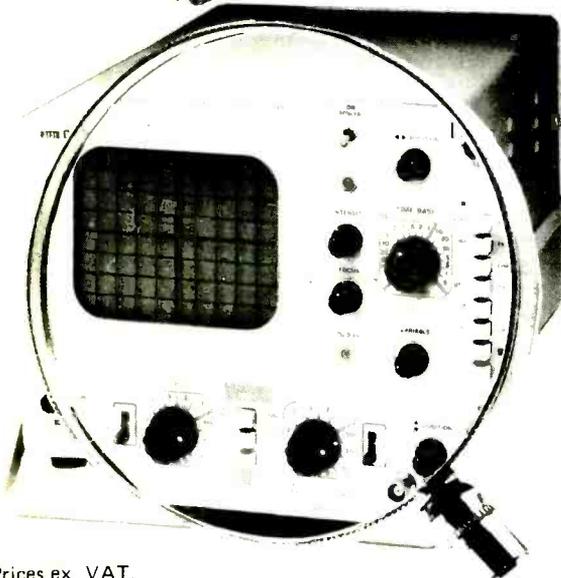YOU DON'T NEED ME TO DETECT CROTECH'S VALUE



Prices ex. VAT.

Its elementary. Just look at the **3030** at £150 and the **3131** at £240, both are 15MHz scopes with 5mV/Div maximum deflection coefficient. And the Dual Trace 3131 has matched X-Y, Algebraic Add and Subtract, and TV Trigger, all selected on easy to use clearly marked push buttons.

But that's not all, both incorporate a Component Tester, yes, even the Single Trace 3030, for the in or out of circuit testing of semiconductor and passive devices. With the resultant characteristic being displayed directly on the CRT.

Theres only one thing left to say . . .
Do you want a Violinist?

For full details just fill in the enquiry card or call us direct.

Crotech Instruments Limited

5 Nimrod Way · Elgar Road · Reading · Berkshire
RG2 0EB · United Kingdom

Telephone: (0734) 866945 Telex: 847073 POWLIN G

WW - 074 FOR FURTHER DETAILS

CHOOSING A MICRO?

Then take a look at the October issue of **YOUR COMPUTER** which reviews three new low-cost computers — the Vic 64 from Commodore, the Colour Genie and the MPF II from Multitech. Invest 60p in Your Computer and save yourself a lot of money!

Also in this issue:

Word processing on the ZX81. Yes, it can be done! And this article tells you how.

A survey of commercially available software for the BBC micro.

Also the mystery of the control key on the BBC micro — solved!

Pocket computer from Sanyo. Or, when is a calculator a computer?

All this, plus our regular advice column and pages of program listings. Get a copy from your newsagent now — or take out a subscription by completing the coupon.

To: Marketing
Department,
Room L214,
IPC Electrical-
Electronic Press Ltd,
Quadrant House,
The Quadrant,
Sutton, Surrey
SM2 5AS

Please send me 12 issues of

**YOUR
COMPUTER**

I enclose a cheque/PO for £8
UK/£14 Overseas, payable to
IPC Business Press Ltd.

Name

Address

WWO 15

LOW COST VOLTMETERS



LEVELL
PORTABLE INSTRUMENTS

LEVELL A.C. MICROVOLTMETERS AND BROADBAND VOLTMETERS are part of our comprehensive range of test and measuring instruments.

These voltmeters give accurate readings over a wide range of frequencies. They are housed in robust steel cases and are powered by long life batteries. Mains power units and leather carrying cases are available as optional extras.

A.C. MICROVOLTMETERS

VOLTAGE & dB RANGES 15 μ V, 50 μ V, 150 μ V ... 500V fsd
Acc. $\pm 1\% \pm 1\%$ fsd $\pm 1\mu$ V at 1kHz,
-100, -90 ... +50dB.
Scale -20dB/+6dB ref. 1mW/600 Ω .

type
TM3A

£140

RESPONSE ± 3 dB from 1Hz to 3MHz,
 ± 0.3 dB from 4Hz to 1MHz above
500 μ V.
TM3B filter switch; LF cut 10Hz.
HF cut 100kHz, 10kHz, or 350Hz.

type
TM3B

£156

INPUT IMPEDANCE Above 50mV: 10M Ω <20pF.
On 50 μ V to 50mV: >5M Ω <50pF.

BROADBAND VOLTMETERS

H.F. VOLTAGE & dB RANGES 1mV, 3mV, 10mV ... 3V fsd.
Acc. $\pm 4\% \pm 1\%$ fsd at 30MHz,
-50, -40 ... +20dB.
Scale -10dB/+3dB ref. 1mW/50 Ω

type
TM6A

£220

H.F. RESPONSE ± 3 dB from 300kHz to 400MHz.
 ± 0.7 dB from 1 MHz to 50MHz.

type
TM6B

£240

L.F. RANGES As TM3

LEVELL ELECTRONICS LTD.

Moxon Street, Barnet, Herts. Tel. 01-449 5028/440 8686

+P&P and VAT

See us on Stand D1 at TESTMEX 82

WW - 009 FOR FURTHER DETAILS

EUROPEAN FLOPPY DISK DRIVES AT ATTRACTIVE PRICES

+ 2/3 height 5.25 inch drives

All reconditioned, as new, with 3 month warranty
Single-sided £100 + £3 carriage + VAT = £118.45

CWO ea.

Double-sided £160 + £3 carriage + VAT = £187.45

CWO ea.

+ 8" floppy drives, reconditioned, as new with 3 months' warranty

Single-sided £210 + £6 carriage + VAT = £248.40

CWO ea.

Double-sided £270 + £6 carriage + VAT = £317.40

CWO ea.

+ Also a few US made 5 1/4" single-sided floppy drives at £60 ea. + £3 carriage and VAT = £72.45 CWO ea.

Note all prices are CWO and cheques/POs should be made payable to: "WW READERS ACCOUNT"

Manuals are £20 ea. post paid or £5 if ordered with drives

Circle enquiry number below for details

MELKUIST LTD

35A GUILDFORD STREET

LUTON, BEDS.

TELEPHONE: LUTON 416028 TELEX: 825828

MLKST-G

WW - 078 FOR FURTHER DETAILS

FIRST IN THE WORLD

The ICM-12, synthesized, marine hand-portable radio

FEATURES:

- 12 channels - 6 and 16 fitted as standard.
- No waiting for crystals, can be diode programmed between 156-164MHz.
- Automatic semi-duplex for private and link calls.
- Slide-on nicad pack recharges from mains or 12V.
- Lots of options, speaker mics, alternative battery packs, 12V leads, and desk chargers.
- Complete with nicad battery pack, mains charger, belt clip, earphone, rubber antenna.
- Home Office type approved. RTD HP 105.
- PRICE £199.13 + VAT. Free carriage.

Trade enquiries very welcome - Ask for Phil Hadler

We can also supply the ICOM IC100E and IC410A VHF & UHF. PMR Base and Mobile transceivers. Fully approved, very compact, built-in CTCSS and at very competitive prices.

Also the first synthesized hand portable - ICH2. Two channels, high band, Simplex or Duplex. Dealers, forget your crystal problems!

Dealer outlets required, ask for Dave Stockley.

Thanet Electronics  **ICOM**

143 Reuiver Road, Herne Bay, Kent
Tel: 02273 63859. Telex 965179

WW - 054 FOR FURTHER DETAILS

Item No.	1	HEWLETT PACKARD RMS VOLTMEETER type 3400A 1mV-300V, 10HZ-10MHZ	£150
	2	BOONTON SIGNAL GEN POWER AMPLIFIER type 230A 10-500MHZ	£250
	3	HEWLETT PACKARD AUDIO SIGNAL GENERATOR type 205A	£250
	4	CLAUDE LYONS AUTOMATIC VOLTAGE STABILISER 2.88KVA Compact	£260
	5	TEKTRONIX AMPLIFIER type 1121	£40
	6	SES ABSORPTON WATTMETER type TG2600 2-1000MHZ; 100 Watts 50 ohm	£100
	7	TEKTRONIX PLUG-IN type D Single Trace High Gain DC Differential	£20
	8	TEKTRONIX PLUG-IN type E Single Trace Low Level AC Differential	£20
	9	TEKTRONIX PLUG-IN type G Single Trace Wide Band DC Differential	£25
	10	TEKTRONIX PLUG-IN type L Single Trace 20MHz High Gain	£25
	11	TEKTRONIX PLUG-IN type M 4 Trace DC-20MHZ	£125
	12	TEKTRONIX PLUG-IN type O Operational Amplifier	£35
	13	TEKTRONIX PLUG-IN type Q Transducer & Strain Gauge	£75
	14	TEKTRONIX PLUG-IN type R Transistor Rise Time	£75
	15	TEKTRONIX PLUG-IN type W Differential Comparator	£75
	16	TEKTRONIX PLUG-IN type Z Differential Comparator	£75
	17	HEWLETT PACKARD LCR BRIDGE type 4281A	£795
	18	HEWLETT PACKARD AMPLIFIER type 462A	£35
	19	HEWLETT PACKARD DC CURRENT SOURCE type 6181B 0-100V; 0-250MA	£125
	20	FAST RESPONSE RECORDER type H3020-3 (3 channel) Brand new	£50
	21	HEWLETT PACKARD AUDIO OSCILLATOR type 2001	£35
	22	HEWLETT PACKARD PULSE GENERATOR Model 212A	£25
	23	HEWLETT PACKARD DC MICRO VOLT AMMETER type 425A	£40
	24	HEWLETT PACKARD OSCILLOSCOPE 182A with 1808A and 1825A 75MHz Dual Trace Delayed Sweep	£750
	25	AVO VALVE TESTER type CT160. (22 valve bases)	£29
	26	AVO TRANSISTOR ANALYSER type CT446	£29
	27	MARCONI UNIVERSAL BRIDGE type TR88A	£29
	28	GENERAL RADIO DIGITAL TIME & FREQUENCY METER type 1151-A	£45
	29	MARCONI (SANDERS) MICROWAVE POWER METER type 6598	£150
	30	MARCONI UHF SIGNAL GENERATOR type TF1060	£95
	31	MARCONI FM SIGNAL GENERATOR type TF1077/1 19.7-102.5MHZ	£30
	32	MARCONI SUPPRESSED ZERO VOLTMEETER type TF1377	£15
	33	MARCONI VARIABLE ATTENUATOR type TF1072A/25 (CT421)	£30
	34	ERNST TURNER 20KV ELECTROSTATIC VOLTMEETER 6 inch	£20
	35	MARCONI AM/FM SIGNAL GENERATOR TF995A/3 (CT402) 1.5-220MHZ	£160
	36	MARCONI AC MILLIVOLTMEETER type TF2600 10HZ-5MHZ; 1mV-300V	£95
	37	B & K ACCELEROMETER PREAMPLIFIER type 2620	£30
	38	B & K DEVIATION BRIDGE type 1503	£30
	39	B & K DEVIATION BRIDGE type 1504	£35
	40	B & K MICROPHONE AMPLIFIER type 2602	£55
	41	B & K MICROPHONE AMPLIFIER type 2605	£30
	42	B & K BEAT FREQUENCY OSCILLATOR type 1013	£35
	43	B & K BEAT AUTOMATIC VIBRATION EXCITER CONTROL type 1018	£20
	44	B & K EXCITER CONTROL PRE AMPLIFIER type 1608	£20
	45	B & K FREQUENCY RESPONSE TRACER type 4707	£20
	46	SOLAARTRON/SCHLUMBERGER SYNTH. SSB GENERATOR type SSB30 with MOD-ULATOR MA30 10HZ-32MHZ	£350
	47	TEXAS SILENT 700 PRINTER Model KSR733 - 300 baud	£225
	48	BRADLEY MULTIMETER type CT471C	£35
	49	MOSELEY WAVEFORM TRANSLATOR type 101	£30
	50	HOUSTON INSTRUMENTS LOG VOLTMEETER-CONVERTOR Model HLVC150	£80
	51	POLAROID FIELD STRENGTH METER type FIM-B2 with RF Tuning Unit FIM-X2 7300-10000MHZ	£95
	52	HEWLETT PACKARD DIGITAL VOLTMEETER type 3460B with AC CONVERTER type 3461A +/- 0.004%	£100

Item No.	53	SANDERS OSCILLATOR type CLC2-4	£75
	54	B & K ELECTRONIC VOLTMEETER type 2409 2HZ-200KHZ	£35
	55	GENERAL RADIO MICROWAVE OSCILLATOR type 1360A 7-4.1GHz	£225
	56	GENERAL RADIO FREQUENCY DISCRIMINATOR METER type 112A 0-1.5MHZ	£35
	57	HEWLETT PACKARD MEMORY DISPLAY type 5480A with CONTROL type 5486B and Two Channel Input type 5485A	£225
	58	GENERAL RADIO DECADE CAPACITOR 1413 with ANALOG LIMIT COMPARATOR 1782 and IMPEDANCE COMPARATOR 1654	£150
	59	STODART RADIO INTERFERENCE & FIELD INTENSITY METER type N-M 52A	£195
	60	KEITHLEY RELATED HIGH VOLTAGE SUPPLY type 241	£145
	61	BRANDENBURGH HIGH VOLTAGE GENERATOR type MR50	£75
	62	BRANDENBURGH HIGH VOLTAGE P.U. Model 705. Metered 0-15KV +/-	£100
	63	BELX POWER UNIT type CMT3001. +/-	£40
	64	PLESSEY TELEGRAPH SIGNAL GENERATOR TSG10 with TDMS type 70. Speed 50-750 (2 units)	£20
	65	As Above but SPEED 45.5-50.75	£30
	66	RACAL H.F. SELECTIVE ANALYSER type 9056	£200
	67	RACAL UHF FREQUENCY METER type 9639 10-560MHZ	£225
	68	RACAL 800MHZ DECADE DIVIDER type 9010	£20
	69	RACAL AUTO FREQUENCY CONVERTOR type 803R 500MHZ	£20
	70	RHODE & SCHWARZ NOISE GENERATOR SKTU BN4151/2/60 3-1000MHZ	£75
	71	R & S UHF TEST RECEIVER BN1523 280-940MHZ	£50
	72	R & S FREQUENCY METER VHF-UHF 30-300MHZ type W10 BN442	£40
	73	R & S ATTENUATOR type DPR BN1804/50	£25
	74	R & S RESONANCE FREQUENCY METER 30-500MHZ WAM BN4312/2	£50
	75	R & S WIDE BAND SIG GEN type SBF BN40861 10HZ-10MHZ	£30
	76	R & S SIGNAL GENERATOR type SMAR BN4123 30HZ-30MHZ	£30
	77	R & S CAPACITANCE METER BNS201	£50
	78	ISOLATING TRANSFORMER 240V Input 240V Output 1300 Watts	£15
	79	AUTO TRANSFORMER 1.4 KVA Pn Volts 30/240 Sec Volts 115	£15
	80	OC SERVO MOTOR 110V 2.5A Cont. Double Shaft. 4 wire 4 brush New	£15
	81	JLT TRANSISTOR A.C. VOLTAGE REGULATOR MODEL LT-11000-2S Rating 1000V	£40
	82	WAYNE KERR AUTOBALANCE CAPACITANCE BRIDGE type 8541	£75
	83	PHILIPS VIDEO COLOUR TEST GENERATOR type PM6522. No case	£225
	84	PHILIPS FM STEREO GENERATOR type PM6456. Separate L & R Signals Carrier Freq 100MHZ +/- 1% RF P/P 3mV pk-pk	£125
	85	PHILIPS COMPARATOR 278KHZ	£30
	86	PHILIPS AUTOMATIC ELECTRONIC VOLT OHM METER type PM2405	£20
	87	B & K AUTOMATIC VIBRATION EXCITER CONTROL type 1016	£50
	88	HEWLETT PACKARD DC POWER SUPPLY type 6448B 0-600 Volts 0-1.5 Amps	£225
	89	BRANDENBURGH REGULATED HIGH VOLTAGE P.U. type 928R 0-1000KV; 0-1MA	£150
	90	ADVANCE PULSE GENERATOR type PG5002D	£20
	91	GAUMONT-KALEE FLUTTER METER type 1740	£30
	92	ADVANCE SIGNAL GENERATOR LF type 81A 15HZ-200KHZ	£25
	93	ADVANCE BATCH COUNTER type 4841	£20
	94	ADVANCE AUDIO SIGNAL GENERATOR type J1	£30
	95	ADVANCE SIGNAL GENERATOR type E2 10KHZ-100MHZ	£45
	96	PYE SCALAMP 40KV RMS Max ELECTROSTATIC VOLTMEETER	£55
	97	PYE SCALAMP 20KV RMS Max ELECTROSTATIC VOLTMEETER	£35
	98	RANK ABENA E.H.T. METER 0-30KV	£35
	99	SINE & SQUARE WAVE AUDIO GENERATOR type TE-22 20HZ-200KHZ	£35
	100	BLACK & WHITE 20" MONITOR by ICKEGAMI type PM2011S. Solid State	£26

PLEASE CHECK AVAILABILITY BEFORE ORDERING
COMPONENT LIST AVAILABLE S.A.E. OR PHONE

MARCONI AM/FM SIGNAL GENERATOR type TF1066B/6S 10-470 MHZ in 5 bands **£250 each.** Carriage £6.

WAYNE KERR COMPONENT BRIDGE type B521 (CT 375) Resistance 1mOhm - 1000 MegOhm Capacitance 1pF - 5000Kuf Inductance 1µH - 500kH. With copy of manual **ONLY £40 each.** Carriage £6.

AVO VALVE TESTER type CT160 (22 valve bases) with copy of manual **£20 each.** Carriage £6.

AVO TRANSISTOR ANALYSER type CT446 with copy of manual **£20 each.** Carriage £6.

AVO SIGNAL GENERATOR No. 2 AM/FM AM 0.45-225MHZ; FM 20-100MHZ with copy of manual **£75 each.** Carriage £6.

MARCONI COUNTER/FREQUENCY METER TF1417/2 with Converter type TF 2400/TM7265 - 500MHZ **£35 each.** Carriage £6.

TELETYPE PRINTERS KSR33 - ASCII Keyboard **£50.** ASR 33 - as above with 8-bit Punch and Reader **£75.** Carriage **£6 each unit.**

DATA MODEM COLLINS TMX 202G 115/230V Operation Complete with information ONLY £25 each P&P £5	SINE & SQUARE WAVE AUDIO GENERATOR type TE-22, 20HZ-200KHZ. Portable as new ONLY £35 each. P&P £4
ISOLATING TRANSFORMER 240V input 240V Output 1300 Watts £15 each. Carr. £6	MULTIMETER Russian Type 4324 AC/DC volts; AC/DC current; ohms, etc. Brand new, boxed £12.50 each P&P £2.50


10% DISCOUNT ON ALL ORDERS RECEIVED BY SEPTEMBER 30th
For further details please contact
Dwayne Stewart

BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome All units £6 carriage. Plus V.A.T. on total
CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.

CHILTMHEAD LTD

NORWOOD ROAD, READING **TELEPHONE NO. READING 669656**
(2nd turning left past Reading Technical College in King's Road then first right - look on right for door with "Spoked Wheel")

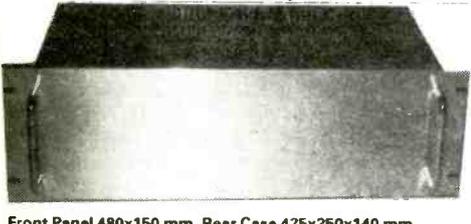19" Rack Mounting Cabinet - Or Free Standing



£23.95
£19.50

OFFER ENDS SOON

Front Panel 480x150 mm. Rear Case 425x250x140 mm
★ Top, bottom and rear cover removable for access. Plates have heavy duty grey paint finish ★ Front panel is heavy gauge - 3mm aluminium ★ Strong, screwed, construction throughout - screws included ★ Heavy gauge chassis mounting plate is pre-drilled and has four mounting positions to choose from ★ Front panel is of brushed aluminium finish enhanced with heavily chromed handles ★

Many sold to **TANGERINE** users and **INDUSTRY**

ADD VAT AT STD. RATE & ORDERS UNDER £5. P&P 50p ABOVE ITEMS £1 P&P

Ask for our **FREE Catalogue**

'metal cabinets'

a **£1.70**
b **£2.55**
c **£3.04**
d **£4.08**

SLIDE SWITCHES

1P2T	10p
2P2T pcb	12p
2P2T	12p
2P3T	20p
1P4T pcb	26p
4P2T pcb	28p
4P3T pcb	35p
6P3T pcb	42p
4P4T pcb	45p

EXPORT EXPORTEUR

Bridge WO-005 16p

a - 102(d) x 56(h) x 83(w)mm
b - 150(d) x 61(h) x 103(w)mm
c - 150(d) x 76(h) x 134(w)mm
d - 184(d) x 70(h) x 160(w)mm

RELAY-A-QUIP PRODUCTS

Moat Lodge, Stock Chase MALDON, Essex, UK
Tel. 0621 57242 10am-8pm Mon.-Sat.

TRADE P.O.A.
"SEIKO"
30w Iron
£2.95

WW - 062 FOR FURTHER DETAILS

SWITCHCRAFT XLR CONNECTORS

Line Female A3F	£1.59	Chassis Female D3F	£2.04
Line Male A3M	£1.36	Chassis Male D3M	£1.19

4, 5, 6 and 7-pin versions and large selection audio adaptors available

NEUTRIK XLR CONNECTORS

Latchless Chassis NC3-FZ	£0.67	Latchless Chassis Male NC3-MZ	£0.59
Line Female NC3-FCC	£1.34	Line Male NC3-MC	£1.15
Female Chassis NC3-FP	£1.65	Chassis Male NC3-MP	£0.87

4, 5-pin, PCB and black versions and large selection of audio adaptors available

XLR LNE MAIN SERIES

XLR LNE 11C	£3.87	XLR LNE 12C	£3.76
XLR LNE 32	£2.89	XLR LNE 31	£4.14

BELCLERE AUDIO TRANSFORMERS

EN6422 Ratio + 1.2 + 2 Freq. 40MHz-35KHz. PRI 150/600I, sec. 600/2.4KI	£4.15
EN6423 Ratio + 1 + 1.6:45 + 6.45. Freq. 40HZ - 25KHz. PRI 150/600I, sec. 6.25K/25KI	£4.15
SKT-723 Mu/Metal Screening can, 39dB reduction 50Hz ext. field	£1.30

Trade enquiries welcome: quantity discounts available. All prices subject to V.A.T. Call, write or telephone. Minimum order £10. Please add £2 postage. Access, Amex, Barclaycard.

KELSEY ACOUSTICS LTD.
28 POWIS TERRACE, LONDON W11 1JH
01-727 1046/0780

WW - 059 FOR FURTHER DETAILS

ScheTronics Limited

For repair and calibration of test equipment.
We also have the following second user LF/HF equipment for sale.

Siemens return L bridge R 273 complete 1 mghz to 100 mghz	£850
Marconi 2600 v-v	£175
Hatfield SLM 1001 30HZ to 30KHZ	£150
Siemens 17 mghz pair	£375
Siemens level difference meter D2003 300HZ to 2mghz	£350
Siemens Pegamat spares.	


**Unit 10, Dunstall Estate
Crabtree Manorway
Belvedere, Kent DA17 6AW
Telephone: 01-311 9657**

WW - 035 FOR FURTHER DETAILS

LEADER

instruments set the pace

TV & FM Test

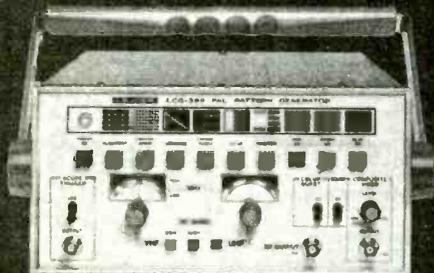

- Colour Bar Pattern Generators
- Sweep and Marker Generator
- CRT Tester
- Field Level Checker
- Signal Level Meter
- High Voltage Metered Probe
- Signal Generators

Audio Test




- Generators
- Attenuators
- System Analyser
- Audio Tester
- Distortion Meter
- Equaliser Amp
- Wow and Flutter Meter
- Frequency Response Recorders
- Millivoltmeters
- Log Amplifier
- Speaker Analyser

When you select an instrument from the Leader range, you get more than just sound engineering. That's guaranteed – by rigorous quality assurance at manufacture, and a one year warranty. A broad range that covers most areas of test, measurement and calibration, with advanced features and high specification as standard. Prices that are lower than you'd expect are the bonus. Probes, covers, hoods and pouches are all available to enhance the application potential and ensure that Leader instruments set the pace for others to follow.

 **thandar**
ELECTRONICS LIMITED

Oscilloscopes

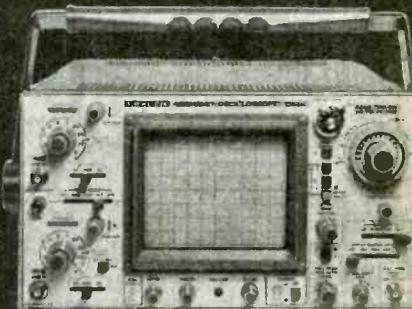

- 4 to 50MHz
- Single, Dual and Quad trace
- Delayed sweep
- Wide bandwidth
- High sensitivity
- High accuracy
- Battery operated

General Test

- LCR Bridge
- Semiconductor Curve Tracer
- Transistor Testers
- Logic Probe



Power Supplies

- Laboratory bench type
- 5 models
- 500mA to 5A
- Overload Protected

Thandar Electronics Ltd,
London Road, St. Ives,
Huntingdon,
Cambridgeshire
PE17 4HJ England.
Tel: (0480) 64646.
Telex: 32250.

WW - 092 FOR FURTHER
DETAILS

ambit[®] INTERNATIONAL

THE MOST COMPREHENSIVE RANGE OF COMPONENTS, KITS AND MODULES IN THE WORLD & THERE'S ONLY ROOM FOR A FRACTION HERE, GET THE CATALOGUE AND FIND THE REST.

CMOS-TTL :							
4001	0.11	4515	1.25	74LS10	0.12	74LS138	0.30
4007	0.13	4516	0.60	74LS11	0.12	74LS139	0.30
4009UB	0.25	4518	0.35	74LS12	0.12	74LS145	1.20
4010	0.30	4520	0.60	74LS13	0.20	74LS151	0.30
4011	0.11	4521	1.30	74LS14	0.30	74LS153	0.27
4012	0.14	4522	0.85	74LS20	0.12	74LS154	0.99
4013	0.25	4526	0.60	74LS21	0.12	74LS155	0.35
4016	0.22	4527	0.80	74LS22	0.12	74LS156	0.37
4017	0.40	4528	0.65	74LS26	0.14	74LS157	0.30
4019	0.38	4529	0.70	74LS27	0.12	74LS158	0.30
4020	0.55	4531	0.65	74LS28	0.12	74LS160	0.37
4021	0.55	4532	0.80	74LS30	0.12	74LS161	0.37
4022	0.55	4534	4.00	74LS32	0.12	74LS162	0.37
4023	0.15	4536	2.50	74LS33	0.15	74LS163	0.37
4024	0.33	4538	0.85	74LS38	0.14	74LS164	0.40
4025	0.15	4539	0.80	74LS40	0.13	74LS165	0.60
4027	0.26	4543	0.80	74LS42	0.30	74LS168	0.70
4030	0.35	4549	3.50	74LS47	0.35	74LS169	0.85
4043	0.50	4553	2.70	74LS48	0.45	74LS170	0.90
4044	0.60	4554	1.20	74LS49	0.55	74LS173	0.60
4045	0.60	4555	1.20	74LS49	0.55	74LS174	0.40
4049UB	0.24	4556	0.40	74LS54	0.14	74LS175	0.40
4050	0.24	4557	2.30	74LS55	0.14	74LS181	1.05
4051	0.55	4558	0.80	74LS73	0.21	74LS190	0.60
4060	0.75	4559	3.50	74LS74	0.16	74LS191	0.60
4066	0.30	4560	2.50	74LS75	0.25	74LS192	0.45
4068	0.16	4561	1.00	74LS76	0.20	74LS193	0.42
4069UB	0.14	4562	2.50	74LS78	0.19	74LS194	0.35
4070	0.16	4566	1.20	74LS83	0.40	74LS195	0.35
4071	0.16	4568	1.45	74LS85	0.60	74LS196	0.55
4072	0.16	4569	1.70	74LS86	0.14	74LS221	0.50
4073	0.16	4581	1.45	74LS80	0.28	74LS240	0.80
4075	0.16	4572UB	0.22	74LS92	0.31	74LS241	0.80
4076	0.55	4580	3.25	74LS93	0.31	74LS242	0.70
4077	0.18	4581	1.40	74LS95	0.40	74LS243	0.70
4078	0.18	4582	0.70	74LS96	1.20	74LS244	0.60
4081	0.12	4583	0.80	74LS107	0.25	74LS245	0.80
4093	0.30	4584	0.27	74LS109	0.20	74LS257	0.40
4175	0.80	4585	0.45	74LS112	0.20	74LS258	0.37
4502	0.60	40174	1.05	74LS113	0.20	74LS260	0.50
4503	0.50	40195	1.08	74LS114	0.19	74LS266	0.22
4506	0.70	74LS00	1.07	74LS122	0.35	74LS273	0.70
4507	0.37	74LS01	0.10	74LS124	1.80	74LS279	0.35
4508	1.50	74LS02	0.11	74LS123	0.35	74LS365	0.32
4510	0.55	74LS03	0.11	74LS125	0.24	74LS366	0.34
4511	0.45	74LS04	0.12	74LS126	0.24	74LS367	0.32
4512	0.55	74LS05	0.13	74LS132	0.42	74LS368	0.35
4514	1.25	74LS08	0.12	74LS133	0.24	74LS373	0.70

Memory Micros Linears:

LM10CN	3.88	SL1611	1.60	KB4433	1.52	U265	3.16
L149	1.86	SL1612	1.60	KB4413	1.95	U266	2.43
U237B	1.28	SL1613	2.06	KB4436	2.53	LC7137	7.50
U247B	1.28	SL1620	2.17	KB4437	1.75	ICM7216B	19.50
U257B	1.28	SL1621	2.17	KB4445	1.29	ICM7216C	19.95
U267B	1.28	SL1623	2.44	KB4446	2.75	CM7217A	9.50
LM324	0.45	SL1625	2.17	NE5044	2.25	SM7217	6.00
LM339N	0.66	SL1630	1.52	MC5229	9.60	95H90	7.80
LF347	1.66	SL1640	1.89	SL6270	2.03	HD10551	2.45
LM348	0.90	SL1641	1.89	SL6310	2.03	HA12009	6.00
LF351	0.49	TDA2002	1.25	SL6440	3.38	HD44015	4.45
LF353	0.76	ULN2242	3.05	SL6600	3.75	HD44752	8.00
LM380N	1.00	ULN2283	1.00	SA5610	1.48	MC14515P	6.00
ZN419CE	1.98	CA3089	1.84	SL6640	2.75	Z80A P10	3.75
ZN427E/B	6.28	CA3130E	0.80	SL6690	2.26	Z80A CTO	3.75
NE544	1.80	CA3130T	0.90	SL6700	2.35	Z80A DTC	4.00
NE555N	0.20	CA3140E	0.46	SA56710	1.48	Z80A DMTA	9.95
SL560C	1.98	CA3189E	2.20	LS7225	3.65	Z80A DART	7.50
NE564	4.29	CA3240E	1.27	ICM7555	0.94	Z80A S1011	11.00
NE567	1.30	MC3357	2.85	ICL8038CC	4.50	Z80A S1012	11.00
uA741CN	0.20	ULN3859	2.95	TK10170	1.87	Z80A S1019	9.95
TBA820M	0.78	LM3900	0.60	TK10321	2.75	Z80010	65.00
ZNA1034	2.10	LM3909N	0.68	HA11223	2.15	8255	2.58
LM1035	4.50	LM3914N	2.80	HA11225	1.45	6800P	2.90
TDA1062	1.95	KB4412	1.95	HA12002	1.22	6809	8.75
TDA1083	1.95	KB4417	1.80	HA12402	1.95	6802	3.50
TDA1090	3.05	KB4420B	1.09	HA12411	1.20	68A00P	4.25
HA1197	1.00	KB4423	2.30	HA12412	1.55	68B00P	4.65
MC1350	1.20	KB4424	1.65	LF13741	0.33	2114L2	1.49
HA1370	1.90	KB4430	2.30	NK50375	3.85	4116 Z	1.59
HA1388	2.75	KB4431	1.95	MM53200	3.90	2732	4.00
SL1610	1.60	KB4432	1.95	U264	2.27	2716	3.00

AND THERE'S PLENTY MORE IN THE CATALOGUE 70p inc.

Coils, Filters: Toko, Murata, NTK, Cathodeon.

SFE6.0MA	0.80	CDA10.7MA	0.70	10M15D	14.50
CFSE10.7	0.80	SFE27MA	0.94	LFB4	1.95
SFE10.7MA	0.45	SAF10.7MC-Z	3.75	LFB6/CFU455H	1.95
CFSB10.7	0.50	MF45510AZ12118.55		LFB8	1.95
SFE10.7MJ	0.50	MFL45501L	11.95	LFB10	1.95
SFA10.7MF	0.75	10M15A	1.99	LFB12/CFU455F	1.95
SFE10.7ML	0.70	21M15A	3.45	LFB6S/	
SFE10.7MX	0.95	45M15A	5.95	CFW455HT	2.45
CFSH10.7M1	0.50	10M22D	17.20	LFB8S	2.45
CFSH10.7M2	0.50	10M8D	15.50	LFB12S/	
CFSH10.7M3	0.50			CFW455FT	2.45

TOKO FIXED VALUE CHOKES (E12 Values)

7BA - 1 to 1000uH	16p	10HB - 1 to 120mH	33p
8RB - 1 to 33mH	19p	10RB - .15 to 1.5H	43p

RETAIL SHOP OPENING HOURS

Monday to Thursday 8.30-6.30
Friday 8.30-8.30 Saturday 9.00-5.30
(Access + Barclaycard orders accepted)

NOW IN STOCK

MF10 - National's new Dual Switched - Capacitor Filter.
Price £5.05

ALL PRICES SHOWN EXCLUDE VAT. P&P 50p per order.

AMBIT INTERNATIONAL DEPT. WW
200 North Service Road, Brentwood, Essex
TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

WW - 047 FOR FURTHER DETAILS

HF ANTENNAS



★ MODE; Full half wave operation.

★ BANDS; Up to 4 spot frequencies.

★ POWER; Receive to 800W (PEP).

★ SWR; Better than 1.5:1 on channel.



From £125

THE SMC TRAPPED DIPOLE ANTENNA

has been developed to satisfy the needs of commercial and military users. It is capable of operation between 2 and 30 MHz on as many as four spot frequencies - each capable of accommodating many channels. Excellent matching and efficiency with a single coaxial feed is offered by the use of SMC H1Q traps and the incorporation of a ferrite balun in a full half wave design. NB: Power absorbing terminating resistors are not employed. The antenna may be deployed using one or two support masts, installation (incorporating SMC light duty portable masts) can be easily effected by two people in half an hour.

HF SSB TRANSCEIVER



FT180 "PIONEER" HF SSB TRANSCEIVER. 1.8-18MHz, 6 channels 100 watts RF output measuring only 95(H) x 240(W) x 310(D)mm and weighing 6kg. May be operated as a base or mobile transceiver, complementing our trap dipole and HW4 mobile aerials. Prices start at £500, making this unit not only very attractive but highly competitive.

SOUTH MIDLANDS COMMUNICATIONS LTD.

OSBORNE ROAD, TOTTEN
SOUTHAMPTON SO4 4DN

Telex: 477351 SMCMM G
Tel: Totton (0703) 867333

WW - 044 FOR FURTHER DETAILS

pantechnic

THE POWERFET SPECIALISTS

POWERFET AMPLIFIER MODULES

The people at Pantechnic have been designing with powerfets since they first became commercially available. Their experience of powerfet amplifiers, coupled with their insight into the sources of non-linearity often neglected by others, has resulted in a new range of powerfet amplifiers that are fast, tough, linear and cheap.

MODEL	POWER RANGE (Continuous RMS)	TYPICAL LOADS	NOTES
PFA 100	50W-150W	4Ω, 8Ω	Physically small 30mm x 79mm x 108mm
PFA 200	100W-300W	4Ω, 8Ω	High Watts per £ ratio
PFA 500	250W-600W	2Ω, 4Ω, 8Ω	25A continuous output current
PFA HV	200W-300W	4Ω, 8Ω, 16Ω	5dB dynamic headroom Drives 70V line direct

Key features:

- RELIABLE - Powerfet freedom from thermal runaway and secondary breakdown
- LINEAR - THD zero, IM/THD < 0.01% full power, (mid band THD down to 0.0015%)
- FAST - Shew rate > 30V/μs. (45V/μs typical)
- QUIET - Signal to noise ratio 120dB
- BRIDGEABLE - (100, 200, 500 without extra circuitry)
- STABLE - Unconditionally
- LOW COST - 10watts to 20watts per £, depending on model and quantity

As they stand these modules suit most P.A. and industrial applications and satisfy all foreseeable audiophile requirements. (The HV is aimed at digital audio.) Where aspects of performance fail to meet specific requirements (e.g. in speed or power) low cost customising is often a possibility. Alternatively entirely new boards can be produced.

Pantechnic make more than just PFAs. Loudspeaker protection boards and the quietest, lowest distortion preamp boards currently available are just two of an ever-expanding range.

Pantechnic sell high quality power supply and other components at excellent prices.

CHECK US OUT

Price and Delivery
PANTECHNIC (Dept WW10)
17a WOOLTON STREET
LIVERPOOL L25 5NH
Tel: 051-428 8485

Technical Enquiries
contact
Phil Rimmer
on
01-900 6667

WW - 094 FOR FURTHER DETAILS

QUALITY OSCILLOSCOPES, THE RANGE FOR EUROPE!

HM307.4 £138

Y: Bandwidth DC-10MHz (-3dB) - Sensitivity 5mV-20V/cm ($\pm 5\%$)
X: Timebase 0.2s-0.5 μ s/cm ($\pm 5\%$) - Triggering 2Hz-30MHz (3mm) - Built in component tester - Calibrator - Screen 6 x 7 - 2kV.

HM203 £220

Y: Bandwidth DC-20MHz (-3dB) - Sensitivity 5mV-20V/cm ($\pm 3\%$) - Dual trace
X: Timebase 0.2s-40ns/cm incl. x5 Magn. - Trigger 3Hz-30MHz (4mm) - X-Y operation - Calibrator - Screen 8 x 10cm - 2kV.

HM412 £350

Bandwidth DC-20MHz (-3dB) Sensitivity 2mV/cm - 20V/cm ($\pm 3\%$) Timebase 40ns/cm Triggering DC - 40MHz (5mm) Algebraic Add., Sweep Delay, x5 Mag., Overscan Ird., Var. Holdoff, Single Sweep.

HM705 £580

Bandwidth DC-70MHz (-3dB) Sensitivity 2mV/cm - 20V/cm ($\pm 3\%$) Timebase 5ns/cm - 2.5s/cm - Triggering DC - 100MHz (5mm), Algebraic Add., Sweep Delay, x10 Mag. | Alt. Trigger, Trig. After Delay, CRT 14kV.

For free data sheets of the full range contact:

HAMEG

England
HAMEG, LTD.
74-78 Collingdon Street
Luton, LU1 1FX
Tel: (0582) 413174/Telex: 825484

France:
HAMEG S.A.R.L.
59, Avenue de la République
94800 Villejuif
Tel: 678.09.98/Telex: 270705

West German y:
HAMEG GmbH
6 Franzlart am Main 71,
Kefstebacher Str. 15-19
Tel: 061 0678017/Telex: 0413866

Spain
HAMEG IBERICA S.A.
Villaroel 112-174
Barcelona 36
Tel: 230.15.97

United States:
HAMEG, INC.
88-90 Harbor Rd.
Port Washington, N.Y. 11050
Phone: 516-883-3337/516-883-6423
TWX: 510 223 0889

Prices U.K. List Ex. VAT



WW - 006 FOR FURTHER DETAILS

MARKETING Ltd.

D&R

SERIES 600

The D&R SERIES 600 range of professional mixing consoles has found its way into hundreds of (hospital) broadcast studios, discotheques, clubs, entertainment and outdoor Public Address systems and recording studios. Available in 6, 12, 18 or 24 channel configuration with, as standard, separate balanced mic. and line inputs, insertion points, gain, three band tone controls, two auxiliary lines, pan-pot and linear fader, plus pre-fade-listening and overload LED per channel. The output section includes four master faders, echo return and phones controls and two large V.U. meters. Optional XLR-3 connectors, 48 volt phantom powering, stereo channels with R.I.A.A. correction, talkback, fader controlled start switches, balanced outputs and 24 volt D.C. mains powering are available.



SERIES 600/12
CONSOLE

D&R Electronica was founded over 10 years ago with the aim of developing and manufacturing high quality mixing consoles for the studio and entertainment industry with a special emphasis on value for money design engineering. The result is a range of five basic models with a large number of channel configurations and options. All models are highly flexible in use and give the best quality possible at today's state of technology.

SERIES 200 - A small mixer specially designed for four track recording.

SERIES 600 - A range of mixers for live amplification, broadcast studios and two track recording.

SERIES 400 - 'In-Line' mixing consoles for budget 4, 8 or 16 track recording.

SERIES 1000 - A range of comprehensive 'In-Line' consoles for professional recording studios.

SERIES 8000 - Top of the range 'In-Line' consoles with integral patch bay for top recording studios. A large number of ancillary signal processing units complement the D&R programme.

Please complete this coupon for further details:-

- D&R Series 200 D&R Series 600
 D&R Series 400 D&R Series 1000
 D&R Series 8000 D&R Ancillary Equipment
- BULLET loudspeaker components
 VITAVOX loudspeaker equipment
 HELIOS mirror balls

NAME _____

ADDRESS _____

WW/10/82

D.S.N. MARKETING LTD, Westmorland Road, London NW9 9RJ
 Telephone: 01-204 7246. Telex: 895 4243.
 Trade, Wholesale, O.E.M. & Export enquiries welcome.



VISA

WW - 085 FOR FURTHER DETAILS

DON'T MISS A GOLDEN OPPORTUNITY

Practical Wireless celebrates its 50th Anniversary with the October '82 issue.

To mark the occasion, this bumper issue will include a special supplement that not only reviews those fifty eventful years, but also takes a look at what the future might hold.

All in all, a golden opportunity to keep in touch with Britain's leading communications magazine.

Practical Wireless

October issue.

Get a copy today!

DAROM SUPPLIES Dept. AW - Tel: (0925) 64764

4 Sandy Lane, Stockton Heath
Warrington, Cheshire, WA4 2AY

sabtronics 

FREQUENCY METERS

8 digit:


- ★ Convenient single input for entire range
- ★ Big easy to read LED display
- ★ Excellent sensitivity
- ★ 10MHz crystal controlled timebase
- ★ Battery or mains operated
- ★ 3 switch selectable gate times
- ★ Leading zero suppression

8110A..... 20Hz-100MHz£67
8610A..... 20Hz-600MHz£82

9 digit:


- ★ 9 digit resolution for more precise readings
- ★ Excellent 30mV sensitivity up to 1GHz
- ★ 3 switch selectable gate times
- ★ 10 MHz crystal controlled timebase
- ★ 2 separate inputs for added versatility
- ★ Front panel sensitivity control
- ★ Battery or mains operated

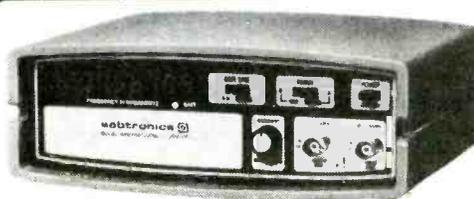8610B..... 10Hz-600MHz£99
8000B.... 10Hz-1000MHz.....£155



I.C.E. Multitester

Only
£32.00

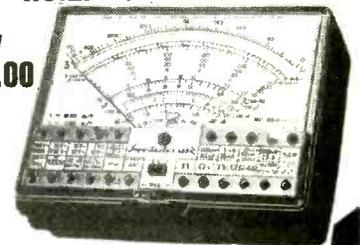

2000V. DC	2500V. AC
10 Amps DC	5 Amps AC
100 M Ω	20,000µF

Add 15% VAT on all prices correct at 1-5-82 E & OE cash with order or credit card Carriage £1 for all orders

WW - 066 FOR FURTHER DETAILS

CLEF ELECTRONIC MUSIC

PIANOS

SPECIALISTS SINCE 1972
DOMESTIC OR STAGE
SIX OR 7 1/4 OCTAVES
KITS OR MANUFACTURED



The most advanced form of touch-sensitive action simulating piano key inertia by patented technique.

Four mixable voices for serious tone variation plus electronic chorus and flanger effects.

Component Kits include Keyboard.

Full Kits further contain: Cabinets, Harness, Power Amp and Speaker.

DOMESTIC PRICES

	E	SIX	7 1/4
Comp	234	266	
Full	398	442	
MFD	620	695	



Kit **BAND-BOX**
£314
Mid £439
An Electronic Backing TRIO. Drums, Bass & Chord Instrument. User Programmable for 50-100 scores, using microprocessor.

VOCAL & INSTRUMENTAL SOLOISTS!

MASTER RHYTHM
User Programmable DRUM MACHINE. Twenty-four patterns. Eight parallel tracks. Twelve instruments sequence operation



£79 Kit £119 BUILT

Write or Phone for full details of our range of high quality Kit and manufactured Electronic Musical Instruments. Prices include V.A.T., Carr., CARD/ACCESS. Competitive EXPORT Quotations given.

CLEF PRODUCTS (ELECTRONICS) LIMITED
Dept. W, 44a Bramhall Lane South
Bramhall, Stockport, Cheshire SK7 1AH
061-439 3297

WW - 041 FOR FURTHER DETAILS

A.B. Dick Magna II WORD PROCESSORS at £850 plus V.A.T.

45 cps Qume Printer
8K Working Store
Thin Window Display
Permanent Storage on Magnetic Cards

Limited stock of ex-demonstration machines factory reconditioned by manufacturer to 'as new' standard

AUTOTYPE (The 2nd-User W.P. Specialists)
1 Church Street
Cuckfield, Sussex
Haywards Heath (0444) 414484 and 454377

WW - 097 FOR FURTHER DETAILS

U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

BSR DE LUXE AUTOCHARGER £18

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability. Stereo Ceramic Cartridge. AC 200/250V. Size 1 1/2 x 1 1/4 in. 3 speeds. Above motor board 3 3/4 in. Below motor board 2 1/2 in. Cut Board £1 extra



Post £2

HEAVY METAL PLINTHS

Cut out for most BSR or Garrard decks. Silver grey finish, black trim. Size 16x13 3/4 in.

Post £2

£4

DECCA TEAK VENEERED PLINTH. Post £1.50

Superior finish with space and panel for small amplifier. Board is cut for B.S.R. 18 3/4 in. x 14 1/4 in x 4 in. Black/chrome fascia trim. Also with boards cut out for Garrard £3. Tinted plastic cover £5

Post £1.50

£5

TINTED PLASTIC COVERS

17 7/8 x 13 1/8 x 3 1/2 in. £5
17 1/4 x 9 3/8 x 3 1/2 in. £3
13 3/4 x 12 x 2 1/2 in. £5
15 1/4 x 13 1/2 x 4 in. £5
17 x 12 7/8 x 3 1/2 in. £5

Post £2

£5

£5

£5

£5

Callers Only (not suitable for post)

21 1/2 x 14 1/4 x 2 1/2 in. £5
23 3/4 x 14 x 3 1/2 in. £5

Post £2

£5

£5

BSR SINGLE PLAYER DECKS

BSR P170 RIM DRIVE QUALITY DECK

£20

Post £2



Manual or automatic play. Precision ultra slim arm. Black with silver trim, stereo ceramic cartridge

BSR P204 SINGLE PLAYERS SPECIAL OFFERS

Two speed 33/45 r.p.m. hi-fi decks with stereo cartridges, cueing device and snake arm. Ceramic - 240V AC £15 or 9V DC £18
Magnetic - 240V AC £20 or 12V DC £24

Post £2

£15

£18

£20

£24

THE "INSTANT" BULK TAPE ERASER

Suitable for cassettes and all sizes of tape reels. AC mains 200/250V. Hand held size with switch and lead (120 volt to order). Will also demagnetise small tools. Head Demagnetiser only £5.

£9.50 Post 95p



BATTERY ELIMINATOR MAINS to 9 VOLT D.C.

Stabilised output, 9 volt 400 m.a. U.K. made in plastic case with screw terminals. Safety overload cut out. Size 5x3 1/4 x 2 1/2 in. Transformer Rectifier Unit. Suitable Radios, Cassettes, models, £4.50. Post 50p.

DE LUXE SWITCHED MODEL STABILISED. £7.50. PP £1.

3-6-7-9 volt 400ma DC max. Universal output plug and lead. Pilot light, mains switch, polarity switch.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit.

Controls up to 600 watts AC mains. £3. Post 65p.
DE LUXE MODEL READY-BUILT 800 watts. Front plate fits standard box. £5. Post 65p.

EMI 13 1/2 x 8 in. LOUSPEAKERS

Model 450, 10 watts R.M.S. with moving coil tweeter and two-way crossover: 3 ohm or 8 ohm. "Final Clearance". Sale Price **£8**
SUITABLE BOOKSHELF CABINET **£5.50**. Size 18x11x6in. Post £1.50.

Post £1.50



RELAYS. 6V DC 95p. 12V DC £1.25. 18V £1.25. 24V £1.30

BLANK ALUMINIUM CHASSIS. 6x4 - £1.45; 8x6 - £1.80; 10x7 - £2.30; 12x8 - £2.60; 14x9 - £3; 16x6 - £2.90; 18x10 - £3.20; 14x3 £1.80. All 2 1/2 in. deep. 18 swg.

ANGLE ALI. 6x3 1/2 x 3 in. 18 swg. 30p.

ALUMINIUM PANELS. 18swg. 6x4 - 45p; 8x6 - 75p; 14x3 - 75p; 10x7 - 95p; 12x8 - £1.10; 12x5 - 75p; 16x6 - £1.10; 14x9 - £1.45; 12x12 - £1.50; 16x10 - £1.75.

PLASTIC AND ALI BOXES IN STOCK. MANY SIZES

ALUMINIUM BOXES. 4x4x1 1/2 £1. 4x2 1/2 x 2 £1. 3x2x1 £1. 6x4x2 £1.60. 7x5x3 £2.40. 8x6x3 £2.50. 10x7x3 £3. 12x5x3 £2.75. 12x8x3 £3.60. All with lids.

BRIDGE RECTIFIER 200V PIV 2a £1. 4a £1.50. 6a £2.50.

TOGGLE SWITCHES SP 40p. DPST 50p. DPDT 60p.

MINIATURE TOGGLES SP 40p. DPDT 60p.

RESISTORS. 10Ω to 10M. 1/4W. 1/2W. 1W. 2p. 2W 10p.

HIGH STABILITY. 1/2w 2% 10 ohms to 1 meg. 10p.

Ditto 5%. Preferred values. 10 ohms to 10 meg. 3p.

WIRE-WOUND RESISTORS 5 watt. 10 watt. 15 watt 20p.

PICK-UP CARTRIDGES SONOTONE 9TA £2.10

BSR Stereo Ceramic SC7 Medium Output £2. SC12 £3.

PHILIPS PLUG-IN HEAD. Stereo Ceramic. AU1020 (G306 - GP310 - GP233 - AG3306. £2. A.D.C. QLM 30/3 Magnetic £5.

LOCKTITE SEALING KIT DECCA 118. Complete £1.

ANTEX SOLDERING IRON 240V 15W £5.25. 25W £6.

JACK PLUGS Mono Plastic 25p; Metal 35p.

JACK PLUGS Stereo Plastic 30p; Metal 35p.

JACK SOCKETS Mono 25p. Stereo 30p.

FREE SOCKETS - Cable end 30p. Metal 45p.

2.5mm and 3.5mm JACK SOCKETS 25p. Plugs 25p.

DIN TYPE CONNECTORS

Sockets 3-pin, 5-pin 15p. Free Sockets 3-pin, 5-pin 25p.

Plugs 3-pin 20p; 5-pin 25p; Speaker plugs 25p; Sockets 15p.

PHONO PLUGS and SOCKETS ea. 20p.

Free Socket for cable end 20p. Screened Phono Plugs 25p.

300 ohm TWIN RIBBON FEEDER 10p yd.

AERIAL MATCHING TRANSFORMER 300/75 ohm £1.

U.H.F. COAXIAL CABLE SUPER LOW LOSS. 25p yd.

COAX PLUGS 30p. COAX SOCKETS 20p.

NEON INDICATORS 250V. round 30p. Rectangular 45p.

POTENTIOMETERS Carbon Track

5kΩ to 2MΩ. LOG or LIN. L/S 50p. DP 90p. Stereo L/S £1.10. DP £1.30. Edge Pot 5k. SP 45p.

MINI-MULTI TESTER NEW

De luxe pocket size precision moving coil instrument. Impedance + Capacity - 4000 o.p.v. Battery included. 11 instant ranges measure: DC volts 5.25, 250, 500. AC volts 10, 50, 500, 1000. DC amps 0-250µA, 0-250mA. Continuity and resistance 0 to 600K ohms

£6.50

De Luxe Range Doubler Model, 50,000 o.p.v. £18.50. 7x5x2in. Post £1

NEW PANEL METERS £4.50

50µa, 100µa, 500µa, 1ma, 5ma, 50ma, 100ma, 500ma, 1 amp, 2 amp 25 volt, VU Meter. 2 1/4 x 2 x 1 1/4 Post 50p



RCS SOUND TO LIGHT CONTROL KIT

Kit of parts to build a 3 channel sound to light unit. 1,000 watts per channel. Suitable for home or disco. Easy to build. Full instructions supplied. Post 95p Cabinet £4.50 extra. Operates from 200MV to 100W. 200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights, Edison Screw. 6 for £4, or 12 for £7.50. Post 65p. Suitable panel mounting holders 85p.

£15

RCS "MINOR" 10 watt AMPLIFIER KIT £14

This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available: Mono, £14; Stereo, £20. Specification 10W per channel; size 9 1/2 x 3 x 2 in. SAE details. Full instructions supplied. 240V AC mains. Post £1.

£14

RCS STEREO PRE-AMP KIT. All parts to build this pre-amp. Inputs for high, medium or low imp per channel, with volume control and PC Board. Can be ganged to make multi-way stereo mixers

£2.95

Post 65p

MAINS TRANSFORMERS

250-250V 90mA, 6.3V 3.5A, 6.3V 1A £5.00 £2
350-250V 250mA, 6.3V 6A CT £12.00 £2
220V 25ma 6V 1amp £2.00 £1
250V 60mA, 6V 2A £3.75 £1

AUTO 115V to 240V 150W £9. 250W £10. 400W £11. 500W £12.00 £2

GENERAL PURPOSE LOW VOLTAGE

Tapped outputs available Price Post
2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V £8.00 £2
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £9.00 £2
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £10.50 £2
3 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £12.50 £2
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £18.00 £2
5-8-10-16V. 1/2 amp. £2.50 80p 15-0-15V. 2 amp £3.75 £1
6V. 1/2 amp. £2.00 £1 20V 1 amp £3.00 £1
6-0-6V. 1/2 amp. £3.00 £1 20-0-20V 1 amp £3.50 £1
9V. 250ma. £1.50 80p 20-0-60V 1 amp £4.00 £2
9V. 3 amp £3.50 £1 25-0-25V 2 amp £4.50 £1
9-0-9V. 50ma £1.50 80p 28V 1 amp twice £5.00 £2
10-0-10V. 2 amp £3.00 £1 30V 1/2 amp £3.50 £1
10-30-40V. 2 amp £3.50 £1 30V 5 amp and £4.50 £2
12V. 100ma £1.50 80p 17-0-17 2a £4.50 £2
12V. 750 ma £2.00 80p 35V 2 amp £4.00 £1
12V 3 amp £3.50 £1 TOROIDAL 20V-0-30V 4a £4.50 £1
12-0-12V. 2 amp £3.50 £1 and 20-0-20V 1/2a £10.00 £2

CHARGER TRANS

6-12 volt 3a £4.00+£2
6-12 volt 4a £5.50+£2

RECTIFIERS

6-12 volt 2a £1.10+80p
6-12 volt 4a £2.00+80p

OPUS COMPACT

SPEAKERS £22 pair Post £2

TEAK VENEERED CABINET

11x8 1/2 x 7 in. 15 watts 50 to 14,000 cps. 4 ohm or 8 ohm



OPUS TWO 15x10 1/2 x 7 3/4 in 25 watt

2-way system £39 pair. Post £3.

LOW VOLTAGE ELECTROLYTICS Wire ends

10p
1mf, 2mf, 4mf, 8mf, 10mf, 16mf, 25mf, 30mf, 50mf, 100mf, 250mf. All 15 volts. 22mf/6V/10V; 25mf/6V/10V; 47mf/10V; 50mf/6V; 68mf/6V/10V/16V/25V; 100mf/10V; 150mf/6V/10V; 200mf/10V/16V; 220mf/4V/10V/16V; 330mf/4V/10V; 500mf/6V; 680mf/6V/10V/16V; 1000mf/2.5V/4V/10V; 1500mf/6V/10V/16V; 2200mf/6V/10V; 3300mf/6V; 4700mf/4V. 500mf 12V 15p; 25V 20p; 50V 30p. 1200mf 76V 80p. 1000mf 12V 20p; 25V 35p; 50V 50p; 100V 70p. 2000mf 6V 25p; 25V 42p; 40V 60p; 1200mf 100V £1.20. 2200mf 6V 30p. 2500mf 50V 70p. 3000mf 50V 85p; 4500mf 6V 42. 4700mf 63V £1.20. 4700mf/40V 85p.

HIGH VOLTAGE ELECTROLYTICS

2/500V 45p 8+8/450V 75p 32+32+16/350V 90p
8/450V 45p 8+8/500V £1 100+100/275V 85p
16/350V 45p 8+16/450V 75p 150+200/275V 70p
32/500V 75p 32+32/350V 50p 220/450V 95p
32/350V 50p 32+32/500V £1.80 32+32+32/325V 75p
50/450V 95p 50+50/300V £1.50 50+50+50/350V 95p

CAPACITORS WIRE END High Voltage

.001 .002, .003, .005, .01, .02, .03, .05 mfd 400V 5p.
1MF 200V 5p. 400V 10p. 600V 15p. 1000V 25p.
22MF 350V 12p. 600V 20p. 1000V 30p. 1750V 50p.
47MF 1500V 10p. 400V 20p. 630V 30p. 1000V 60p.
VALVE OUTPUT Transformers (small) 90p.
TRIMMERS 30pF 50pF 10p. 100pF. 150pF 20p. 500pF 30p.
MICROSWITCH SINGLE POLE CHANGEOVER 40p.
SUB-MIN MICROSWITCH. 50p. Single pole changeover.
TWIN GANG. 120pF £1. 500+200pF £1.
GEARED TWIN GANGS 25pF 95p.
GEARED 365+365+25+25pF £1.
TRANSISTOR TWIN GANG. Japanese Replacement £1
SOLID ELECTRIC 100pF £1.50, 500pF £1.50

HEATING ELEMENTS, WAFER THIN

Size 11x9x1/8 in. Operating voltage 240V, 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, Propagation, etc. Must be clamped between two sheets of metal or ceramic, etc. ONLY 60p EACH (FOUR FOR £2) ALL POST PAID.

NEW baker Star sound

high power full range quality loudspeakers produced to give exceptional reproduction. Ideal for Hi-Fi, music P.A. or discotheques. These loudspeakers are recommended where high power handling is required with quality results. The high flux ceramic magnet ensures clear response.



MODEL	INCHES	OHMS	WATTS	TYPE	PRICE	POST
MAJOR	12	4-8-16	30	HI-FI	£14	£2
DELUXE MK II	12	8	15	HI-FI	£14	£2
SUPERS	12	8-16	30	HI-FI	£24	£2
AUDITORIUM	12	8-16	45	HI-FI	£24	£2
AUDITORIUM	15	8-16	60	HI-FI	£32	£2
GROUP 45	12	4-8-16	45	PA	£14	£2
GROUP 75	12	4-8-16	75	PA	£18	£2
GROUP 100	12	8-16	100	Guitar	£24	£2
DISCO 100	12	8-16	100	Disco	£24	£2
GROUP 100	15	8-16	100	Guitar	£32	£2
DISCO 100	15	8-16	100	Disco	£32	£2



BAKER 150 WATT MIXER/POWER AMPLIFIER £89 Post £2

For Discotheque, Vocal, Public Address. Three speaker outlets for 4, 8 or 16 ohms. Four high gain inputs, 20 mv, 50K ohm. Individual volume controls "Four channel" mixing. 150 watts 8 ohms R.M.S. Music Power. Slave output 500 M.V. 25K ohm. Response 25 Hz - 20kHz ± 3dB. Integral Hi-Fi preamp separate Bass & Treble. Size - 18" x 8" x 5 1/2". Wt - 14lb. Master volume control. British made. 12 months' guarantee. 240V AC. mains or 120V to order. All transistor and solid state. MONO SLAVE VERSION £75. 100 Volt Line Model £104. New Stereo Slave Model 150 + 150 Volt £125. Post £4. BAKER'S NEW PA150 MICROPHONE PA AMPLIFIER £129. PP £3. 4 channel 8 inputs, dual impedance. 50K-600 ohm 4 channel mixing volume, treble, bass. Presence controls, Master volume control, echo/send/return socket. Slave input/output sockets.

BAKER £69 Post £2

50 WATT AMPLIFIER

Ideal for PA systems, Discos and Groups. Two inputs, Mixer, Volume, Controls, Master Bass, Treble Gain.



RCS offers MOBILE PA AMPLIFIERS. Outputs 4-8-16 ohms

20-watt RMS 12V DC, AC 240V, 3 inputs. 50K £46 PP £2
40-watt RMS 12V DC, AC 240V, 4 inputs. 50K £75 PP £2
Mic 1; Mic 2; Phono; aux. outputs 4 or 8 or 16 or 100v line
60-watt RMS, Mobile 24 volt DC & 240-volt AC mains. inputs 50K.
3 mics + 1 music. Outputs 4-8-16 ohm + 100 volts line £95 PP £2

Battery only Portable PA Amplifier 10w max. Includes mike and speaker, OK for meetings, crowd control, stalls, fetes, traders, parties, etc. Batteries included (6 of U2) £27.50 post £1.50.

R.C.S. 100 ROBUST VALVE AMPLIFIER

4 Channel mixing. Master treble, bass and volume controls. 5 Speaker outlets, suits 4, 8, 16 ohm. Black cabinet. £125. Carr. & ins. £15.



FAMOUS LOUSPEAKERS "SPECIAL PRICES"

MAKE	MODEL	SIZE	WATTS	OHMS	PRICE	POST
SEAS	TWEETER	4in	50			

BREADBOARD '82

COMPUTERS • AUDIO • BOOKS • MUSIC • LOGIC

Breadboard '82 gives you the opportunity to have a day out in London AND attend Britain's regular exhibition for you, the enthusiast. NOT ONLY will there be stands from which you'll be able to buy the latest in kits, components, books and magazines, BUT ALSO lectures, demonstrations, competitions AND a chance to take part in a computer-assisted wargame that could make you the military tactician of tomorrow. DON'T MISS Breadboard '82 . . . Adults £2.00, children, students and senior citizens £1.00.


COMPONENTS • MAGAZINES • GAMES • KITS

BREADBOARD '82

**ROYAL
HORTICULTURAL
SOCIETY'S NEW HALL
WESTMINSTER
LONDON SW1**


**NOVEMBER
10th-14th**

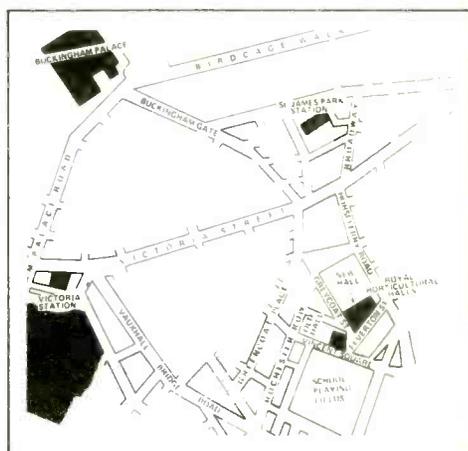Wed 10th 10am - 6pm
Thurs 11th 10am - 8pm
Friday 12th 10am - 6pm
Sat 13th 10am - 6pm
Sun 14th 10am - 4pm



DAROM SUPPLIES Dept. AW - Tel: (0925) 64764
 4 Sandy Lane, Stockton Heath,
 Warrington, Cheshire WA4 2AY

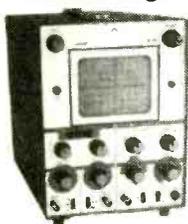SAFGAN British Made Scopes
 A range of high-performance,
 economically priced scopes
 featuring:



- ★ Dual Trace
 - ★ 5mV/div Sensitivity
 - ★ X Y Facility
 - ★ Z Modulation
 - ★ Solid Trigger with Auto., Normal and TV
 - ★ Portable/Lightweight
- DT 410 10MHz£179.00
 DT 415 15MHz£185.00
 DT 420 20MHz£198.00
 X1-REF-X10 probe.....£11.50

OSCILLOSCOPES THE FUTURE SERIES BY LEADER

All Models feature:

- ★ Dual Trace
- ★ 6-inch rectangular CRT
- ★ Max. sensitivity 500µV
- ★ TV-V, TV-H sync.
- ★ ALT trigger
- ★ Hold OFF variable
- ★ X Y Facility
- ★ Preset Sync.
- ★ Z Modulation
- ★ Includes 2 XI/XIO Probes

LBO 524 features Delayed Sweep and Dual Time Base

WW - 065 FOR FURTHER DETAILS



LBO 522 20MHz..... £298
 LBO 523 35MHz..... £425
 LBO 524 35MHz..... £540

Add 15% V.A.T. on all prices - prices correct at 1-5-82 - E&OE cash with order or credit card - Carriage £5 for Express Delivery

AIRWAVES ELECTRONICS

Call in and see us for a Comprehensive Range of Electronic Components
 Audio Leads, Adaptors
 Hobby Kits, Fuses
 Connectors
 Etc.


AIRWAVES ELECTRONICS
 151 London Road, Camberley, Surrey GU15 3JY
 Write/phone for catalogue (0276) 62949

WW - 052 FOR FURTHER DETAILS

LOW DISTORTION AUDIO SIGNAL GENERATORS

Model
149 ba

£41.60
(P&P £2.25)

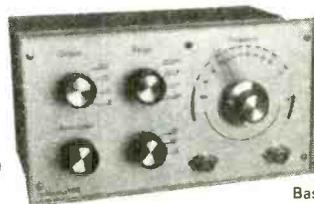


DISTORTION .002% (1Khz)
 Range 10hz - 100 khz
 Output 1v rms (600 ohms)
 Sine/Square
 Coarse/Fine Attenuation

Based on a Linsley Hood design

Also available in kit form and alternative versions, i.e.: battery or mains. With or without frequency meter.
 Literature on these units, R.F. Sig. Gen., T.H.D. meters, MVMT, Function Generators and many other instruments is available on request.

TELERADIO ELECTRONICS, 325 FORE STREET, LONDON N9 0PE
 Telephone 01-807 3719 Closed Thursdays

THE CASE FOR

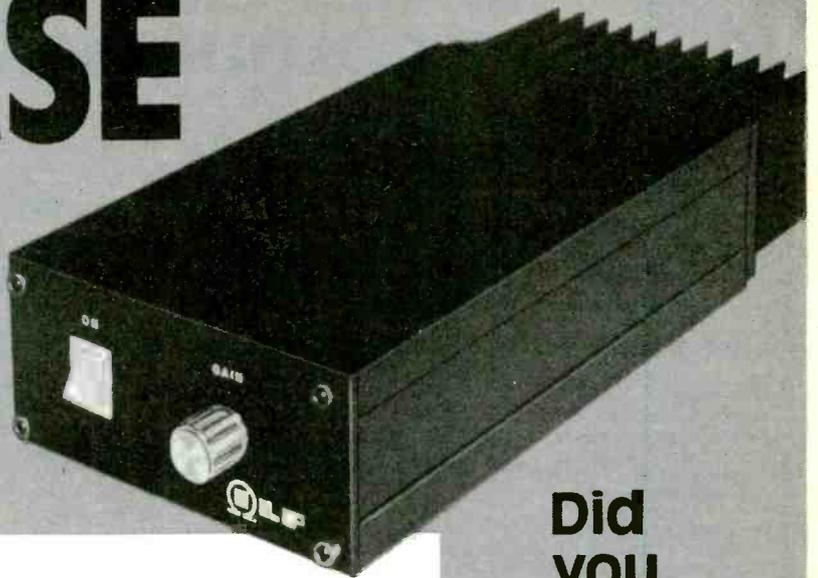

It's the chance every constructor wants

Did you know



POWER AMPS



P.S.U's



PRE-AMP MODULES

It's something you have always wanted....something to build your equipment into that's smart, modern, strong, adaptable to requirement and not expensive. The 'UniCase' is yet another triumph of I.L.P. design policy. It presents totally professional appearance and finish, ensuring easier and better assembly to make it equal to the most expensive cased equipment. The all-metal 'UniCase' is enhanced by precision aluminium extruded panels engineered for speedy and perfect aligned assembly within a mere five minutes. Designed in the first case to accommodate I.L.P. power amps with P.S.U's, the range will shortly be extended to house any other modular projects.

WHAT WE DO FOR CONSTRUCTORS

Our product range is now so vast we cannot possibly hope to show it all in our advertisements without overcrowding or abridging information to the point of uselessness. So we have devised a solution which we invite you to take advantage of without delay. ALL YOU NEED DO IS FILL IN AND FORWARD THE COUPON BELOW TO RECEIVE OUR NEWEST COMPREHENSIVE I.L.P. CATALOGUE POST FREE BY RETURN. It gives full details of all current I.L.P. products for the constructor together with prices, full technical and assembly details, wiring and circuit diagrams etc. and it's yours, FREE. You don't even have to stamp the envelope if you address it the way we tell you.



FREEPOST 5
GRAHAM BELL HOUSE, ROPER CLOSE, CANTERBURY CT2 7EP
Telephone Sales (0227) 54778 **Technical Only** (0227) 64723 Telex 965780

FREEPOST
Mark your envelope clearly **FREEPOST 5** and post it **WITHOUT** a stamp to I.L.P. at address above. We pay postage when your letter reaches us.

I.L.P. are the world's largest designers and manufacturers of hi-fi audio modules?

I.L.P. pioneered encapsulated power amps and pre-amps for enhanced thermal stability, mechanical protection and durability?

There are **TWENTY** power amplifiers from 15 to 240 watts RMS including the very latest super-quality Mosfets to choose from?

TWENTY pre-amp modules allow you to incorporate exciting professional applications to your equipment never before available to constructors and experimenters?

I.L.P. are suppliers to the B.B.C., I.B.A., N.A.S.A., British Aerospace, Marconi, Racal, Ferranti, G.E.C., Rolls Royce etc?

Goods are despatched within 7 days of your order reaching us and covered by our 5 year no-quibble guarantee?

SEND COUPON
(NO STAMP NECESSARY)
FOR YOUR FREE
I.L.P. CATALOGUE
AND OPEN UP
TO A
NEW WORLD OF
QUALITY & VALUE

To: I.L.P. ELECTRONICS LTD.
PLEASE SEND ME I.L.P. CATALOGUE,
POST PAID BY RETURN

Name: _____

Address: _____

I HAVE/HAVE NOT PREVIOUSLY
BUILT WITH I.L.P. MODULES

I.L.P. products are available also from Henry's, Marshall's, Technomatic & Watford.

WW - 087 FOR FURTHER DETAILS

LOOK
SENSATIONAL
SCOOP OFFER

OPUS SUPPLIES RGB COLOUR MONITOR

BRING YOU AN
YOU CAN AFFORD

LOOK
A COLOUR
MONITOR FOR
LESS THAN A TUBE

LIMITED QUANTITY
AVAILABLE
FOR USE WITH
B.B.C., MICRO,
VIC, APPLE,
DRAGON, etc

Specification: The VMC 22 Colour Monitor is designed to meet the high reliability and performance standards associated with the games, data and computer colour graphics industries.

Input levels: Video-TTL compatible either +ive or -ive going for RGB (IC37416 -ive going 7417 +ive going).

Composite Sync: TTL compatible either +ive or -ive going set by PCB link. Separate sync: (Frame and line) TTL compatible +ive going = video response 10 MHz.


Deflection: Scanning systems, 625 line 50 Hz and 525 line 60 Hz.

Scan linearity: Errors less than 5%.

Scan geometry: Errors less than 3%.

High voltage: 25KV.

X radiation: Less than 0.5MR/h.

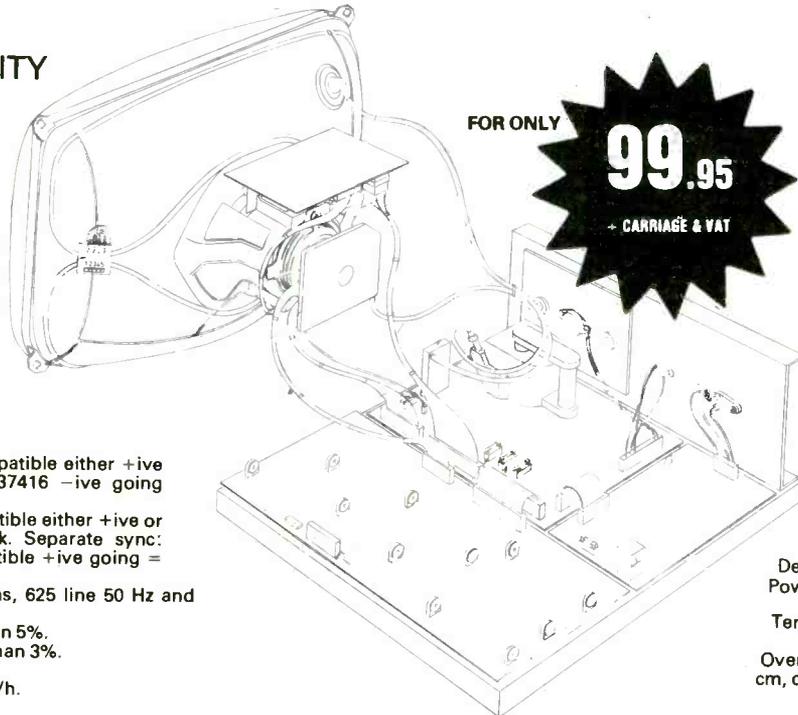

FOR ONLY

99.95

+ CARRIAGE & VAT

FREE

**ISOLATING
TRANSFORMER
ON FIRST 100
ORDERS**

A fabulous 22 inch colour monitor.
Featuring: Mullard 22 inch 110° C.C.R.T.
Controls: Brightness, RGB video amp bias, height, width, vertical hold, horizontal hold, linearity, east-west correction, phase, focus, H.T. adjust, beam cut-off switch, convergence controls.
De Gaussing: Automatic on switch on.
Power requirements: 155 VAC, 44-60Hz 120VA (isolated supply).
Temperature: Storage -10°C to +70°C. Operating 0°C to 50°C.
Overall sizes: Height 40.3 cm, width 51.0 cm, depth 39.5 cm (inc. tube neck P.C.B.).
Weight 19 kgs.

After months of negotiation we have finally secured the computer user's dream. We have bought the complete manufacturer's production of these superb British made R.G.B. Colour Monitors and can offer them to you at this unrepeatable price. This offer, available to readers of "Wireless World" also includes a **FREE** isolating transformer. So with a little of your time and our buying power - you can save pounds. For shipping purposes the C.R.T. and scan coil assembly are separate from the chassis. The lugs of the C.R.T. allow it to be mounted in a standard 22" colour TV cabinet or a unit of your own design. The unit is assembled by plugging the wires from the chassis to the tube, soldering the input connector, power connector and isolating transformer. The monitor has been fully tested and adjusted prior to packing thus simplifying assembly. A comprehensive instruction sheet will be supplied with each unit.

OPUS

A computer supplies company have established an enviable reputation for reliable service and value for money - so pick up your telephone and discuss your supplies requirement with us.

STOP PRESS
JUST ARRIVED FROM JAPAN:
NEC DOT MATRIX 100 C.P.S. PRINTER
OUTSELLS OKI & EPSON IN USA
CALL FOR PRICE & DELIVERY

LOCKABLE DISC FILING BOXES:

To hold 40 Minis £16.00

80 Minis £21.00

To hold 40 8" Discs £21.00


80 8" Discs £28.00

DISC MAILERS:

Mini 60p

8" 90p

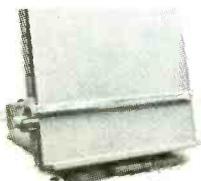DESK TOP LECTERN - ADJUSTABLE WITH MOVABLE CURSOR



ONLY £19.95

HOW TO ORDER

Carriage should be added to prices at the following rates: Monitor £10; Discs 85p; Rams 50p; Filing Boxes/Lecterns £2; Desks £10. Please add carriage as applicable and then VAT at 15% to total and send Cheque/P. Order payable to "Opus Supplies" to Dept. W.W., Opus Supplies, 10 Beckenham Grove, Shortlands, Kent BR2 0JU. Telephone order Hotline: 01-464 5040 (24-hour service) or 01-464 1598. Access and Barclaycard accepted. If you are not completely satisfied return the goods within 14 days and your money will be refunded.

ATHANA FLOPPY DISCS

MINIS WITH FREE PLASTIC LIBRARY CASE & HUB RINGS

S/S S/D £17.95 for 10

S/S D/D £19.95 for 10

D/S D/D £23.50 for 10

S/S 77 Track £26.50 for 10

S/S 96 Track £28.50 for 10

8" DISCS

S/S S/D £15.50 for 10

S/S D/D £24.50 for 10

D/S D/D £25.50 for 10

HARD SECTORED AND ALL OTHER DISCS AVAILABLE

RAM BARGAINS

PART 1 off 25-99 100

4116-200ns .80 .75 .68

4116-250ns .75 .70 .55

2114-300ns .85 .80 .75

2114-450ns .80 .75 .70

2114-L-200ns .95 .87 .83

4516-100ns

BBC RAM 3.10 2.95 2.80

4164-200ns 4.80 4.60 4.20

6116-150ns 4.20 3.95 3.50

2716-5v-450ns 2.40 2.15 2.00

2716 Triple

Rail 6.00 - -

2732-450ns 3.95 3.75 3.25

2532-450ns 3.95 3.75 3.25

8080A 1.90 1.70 -

8212 1.40 1.30 -

25-WAY D SOLDER CONNECTORS

25P £1.30 each

25S £1.50 each

OTHER DEVICES AVAILABLE PLEASE RING FOR QUOTE

OPUS DESKS

MANUFACTURED BY OPUS IN U.K. AVAILABLE FROM OUR CENTRAL WAREHOUSE

- ★ 5 MODELS AVAILABLE - CHOOSE WITHIN YOUR BUDGET ★
- ★ CREAM & BROWN CO-ORDINATING PANELS ★

- ★ DRAWER FOR DISC STORAGE ★

- ★ MOBILE ★

- ★ AMPLE SPACE FOR HARDWARE AND PERIPHERALS ★

- ★ THROUGH SHELF FOR DISC DRIVES, PAPER FEED, FILES ★

SEND S.A.E. FOR YOUR FREE COLOUR BROCHURE



For business or home use - each Desk is supplied with castors - two of which have lockable brakes

Apple 2 users **NEW** 16k printer buffer card - which saves your computer time. Serial and parallel.

Send for specification and price



TRADE ACCOUNTS OPERATED - GOVT. AND EDUCATIONAL ORDERS WELCOMED



An entire
range of
low-cost
high-
performance
instruments



sabtronics 

'Making Performance Affordable'

5020A 1Hz-200KHz Function Generator	8000B 1GHz 9-Digit Frequency Meter
2033 3½-Digit L.C.D. Hand DMM	PSC-65 600MHz Prescaler
365-S Protoboard	AT-001 x1 Passive Probe
LP-10 10MHz Logic Probe	AT-010 x10 Passive Probe
8110A 100MHz 8-Digit Frequency Meter	AT-110 x1 x10 Passive Probe (Switchable)
8610B 600MHz 9-Digit Frequency Meter	

Also Oscilloscopes 15-30MHz Single or Dual trace.

Test our low priced test equipment. It measures up to the best. Compare our specs and our prices—no-one can beat our price/performance ratio.



Illustrated brochure and price list from:

BLACK STAR LTD
9a Crown Street, St. Ives, Cambs. PE17 4EB
Tel: (0480) 62440. Telex: 32339

WW - 014 FOR FURTHER DETAILS


FREQ. CONVERTERS I/P 240v AC O/P 115v 400c/s 100 Va 1 phase sine wave, all solid state, low dist o/p, new, unused, £115. INSULATION TEST SETS, 240v I/P provides 3 O/Ps of 15/20/25kv, uses contact breaker (Vibrator) from 12v DC with test leads in fitted wood case, size 14 x 8 x 9in., thought to have been used for testing Ignition Harnesses, £27. BENCH P.U. Solartron, 200/250v I/P O/P var. from 0 to 40v DC in 100 Mill/V steps current var from 0 to 5 amps, will operate in constant voltage or current mode, O/P volts, set by dig swt, current by swt and pot, % load meter tested with book, £75. A.M. MOD UNIT, Marconi TF1102, will mod Sine, Sq, Pulse or Video on to un mod RF, req ext mod signals, for 240v with book, £25. BENCH P.U. Army 240v I/P provides 2 low HT and 2 low LT O/P all DC and Var, fitted 4x meters, volts and Ma on all circs, intended to power Army radios normally using dry batteries, two-part unit, £28. PYE PF.1 UHF FM Pocket phone Rxs nom 450Mc/s req 9v batt. with circ, £39.50. AUDIO TEST SET CT373 240v I/P AF osc 17c/s to 170Kc in 4 ranges, VTVM 30 Mill/V to 100v FSD, Dist meas set 20c to 20Kc in case, size 14 x 17 x 21 in new cond. with book and leads, £115. VIDEO RECORDERS, Philips type N1500, no cassettes, £75. Also Philips LDL.1000 reel-to-reel with 3 tapes, ½in., both with circ., £75. SPEAKER UNITS, ex-A/C, cabin spk., size 17 x 3½ x 2½in., fitted 4x 3 ohm, 3 x 3in. spks., black, crackle case, £6.50. Also small amp that fits into spk. case, need pre-amp, £3.50. HANDSETS, lightweight, with M.C. mike, 50 ohm, ext. cord and press to talk swt., £4.50. ROTARY CONVERTERS, 24v DC I/P O/P 230v AC 140-watt sine wave, in case, £45, or Rot Conv, only s/h, tested, £27. H.F. Trans Amp, part of STR.18 Equip, 2/18 Mc/s, 100-watt O/P req. ext. power and RF drive, 2x 4 x 150 in P.A. with circ., etc., £37 (new cond.) or £27 (S/H), other units available. Q BAND TEST EQUIP., RF sources and N.G. available inc. w.g. swts, etc. RADIOSONDE UNITS, old British Mk. II, new cond. with chart, £7.50; also new type M.60, £12.50. POWER UNIT, 240v I/P O/P nom 28v DC at 15 amps load range for reg. O/P, 5 to 15 amps, made by Plessey for testing A/C RT sets, tested, £38. AUTO TRANS 200/250 to nom 115v at 560 watts, fully enclosed, size 6½ x 4 x 3½, new cond., £14.50. ARMY-TYPE HEADSETS WITH THROAT MIKES, new cond. with control box, £7.50. BLOWER UNITS, single-ended, 240v, outlet size 2½ x 3½in., very powerful, new condition, £13.50. OSC AMP UNITS, 240v I/P, comprises amp 150 watt and var. freq. Osc 30c to 30Kc; the amp can be connected for various O/Ps down to 16.7 ohm, fitted O/P voltmeter, can be used as normal amp or can be used with Osc to provide var. freq. AC O/P in table case valve unit, £115.

Above prices inc. carr./post and V.A.T Allow 14 days for delivery. Goods are in secondhand condition unless stated new. S.a.e. with enquiry for List 29.

A. H. SUPPLIES

122 Handsworth Road, SHEFFIELD S9 4AE
Phone 444278 (0742)

TO YOU IT'S JUST A POWER VALVE

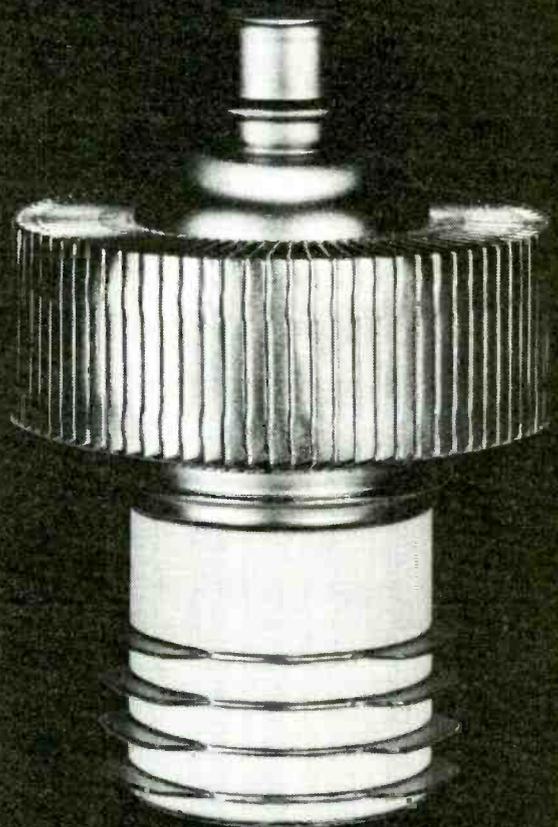

But to us it is probably the key component within a Radio Communication, Radar, Broadcast, Electronic Warfare, or Industrial Heating System.

By utilising our advanced testing and strict quality control facilities we can supply MOD and NATO approved items to DEF Standard 05-29 and 05-31.

As a major MOD Contractor holding £0.5 million of stock we can supply almost any power valve.

For the difficult to locate devices, we have an 'Out of Production' sourcing service linked to an in-house NATO, CV and Commercial Part Number microfiche system.

Contact us with your power problems.



Zaerix Electronics Limited
Electron House, Cray Avenue, St Mary Cray,
Orpington, Kent BR5 3PN England
Telephone Orpington (0689) 27099 Telex 896810 ZANDI G

WW - 075 FOR FURTHER DETAILS

LANGREX SUPPLIES LTD

Climax House Fallsbrook Rd., Streatham, London SW16 6ED

RST

Tel: 01-677 2424 Telex: 946708

RST


SEMICONDUCTORS

AA119 0.12	AS215 1.38	BC172 0.13	BD131 0.51	BF257 0.31	GEX341 5.75	OA2207 1.73	OC205 3.16	ZTX500 0.24	2N1671 5.75	2N3819 0.35
AA130 0.20	AS216 1.27	BC173 0.13	BD132 0.55	BF258 0.31	GJ3M 1.73	OC16 2.88	OC206 3.16	ZTX531 0.28	2N1893 0.37	2N3820 0.45
AA132 0.48	AS217 1.15	BC177 0.16	BD133 0.46	BF259 0.32	GM0378A 2.02	OC20 2.88	OC207 2.88	ZTX550 0.29	2N2147 4.60	2N3823 0.69
AA213 0.17	AS220 2.64	BC178 0.16	BD138 0.55	BF260 0.39	KS100A 0.52	OC22 2.88	OC228 2.88	IN914 0.06	2N2148 4.31	2N3866 1.15
AA215 0.17	AS221 2.88	BC179 0.32	BD139 0.55	BF261 0.41	MJE340 0.82	OC23 4.60	ORP12 2.30	IN916 0.10	2N2218 0.37	2N3904 0.20
AA217 0.17	AS222 2.88	BC182 0.13	BD140 0.58	BF262 0.40	MJE371 0.82	OC24 3.45	R2008B 2.30	IN4001 0.07	2N2219 0.37	2N3905 0.20
AC107 0.63	AU103 3.45	BC183 0.13	BD141 2.30	BF263 0.41	MJE520 0.84	OC25 1.15	R2009 2.59	IN4002 0.07	2N2220 0.23	2N3906 0.20
AC125 0.29	AU110 2.88	BC184 0.13	BD181 1.38	BF264 0.42	MJE521 0.84	OC26 1.73	R2010B 2.30	IN4003 0.07	2N2221 0.23	2N4058 0.23
AC126 0.29	BA145 0.15	BC212 0.13	BD182 1.36	BF265 0.42	MJE522 0.84	OC27 2.30	T1C44 0.31	IN4004 0.08	2N2222 0.23	2N4059 0.23
AC127 0.29	BA148 0.15	BC213 0.13	BD183 1.38	BF266 0.42	MJE523 0.84	OC28 2.30	T1C44 0.31	IN4005 0.10	2N2223 0.23	2N4060 0.18
AC128 0.35	BA154 0.12	BC214 0.13	BD184 1.38	BF267 0.42	MJE524 0.84	OC29 2.30	T1C44 0.31	IN4006 0.13	2N2224 0.23	2N4061 0.18
AC141 0.32	BA155 0.13	BC237 0.13	BD185 1.38	BF268 0.42	MJE525 0.84	OC30 2.30	T1C44 0.31	IN4007 0.14	2N2225 0.23	2N4062 0.18
AC141K 0.40	BA156 0.12	BC238 0.13	BD186 1.38	BF269 0.42	MJE526 0.84	OC31 2.30	T1C44 0.31	IN4008 0.08	2N2226 0.23	2N4063 0.18
AC142 0.32	BA157 0.06	BC301 0.38	BD187 1.38	BF270 0.42	MJE527 0.84	OC32 2.30	T1C44 0.31	IN4009 0.08	2N2227 0.23	2N4064 0.18
AC142K 0.40	BA158 0.07	BC302 0.38	BD188 1.38	BF271 0.42	MJE528 0.84	OC33 2.30	T1C44 0.31	IN4010 0.08	2N2228 0.23	2N4065 0.18
AC176 0.35	BA159 0.07	BC307 0.13	BD189 1.38	BF272 0.42	MJE529 0.84	OC34 2.30	T1C44 0.31	IN4011 0.08	2N2229 0.23	2N4066 0.18
AC187 0.32	BC107 0.18	BC308 0.13	BD190 1.38	BF273 0.42	MJE530 0.84	OC35 2.30	T1C44 0.31	IN4012 0.08	2N2230 0.23	2N4067 0.18
AC188 0.32	BC108 0.18	BC327 0.14	BD191 1.38	BF274 0.42	MJE531 0.84	OC36 2.30	T1C44 0.31	IN4013 0.08	2N2231 0.23	2N4068 0.18
AC187 1.50	BC109 0.18	BC328 0.14	BD192 1.38	BF275 0.42	MJE532 0.84	OC37 2.30	T1C44 0.31	IN4014 0.08	2N2232 0.23	2N4069 0.18
AC188 1.32	BC110 0.17	BC329 0.14	BD193 1.38	BF276 0.42	MJE533 0.84	OC38 2.30	T1C44 0.31	IN4015 0.08	2N2233 0.23	2N4070 0.18
AC189 1.27	BC111 0.17	BC330 0.14	BD194 1.38	BF277 0.42	MJE534 0.84	OC39 2.30	T1C44 0.31	IN4016 0.08	2N2234 0.23	2N4071 0.18
AC190 1.27	BC112 0.17	BC331 0.14	BD195 1.38	BF278 0.42	MJE535 0.84	OC40 2.30	T1C44 0.31	IN4017 0.08	2N2235 0.23	2N4072 0.18
AC191 1.32	BC113 0.22	BC332 0.14	BD196 1.38	BF279 0.42	MJE536 0.84	OC41 2.30	T1C44 0.31	IN4018 0.08	2N2236 0.23	2N4073 0.18
AC192 2.88	BC114 0.26	BC333 0.14	BD197 0.40	BF280 0.42	MJE537 0.84	OC42 2.30	T1C44 0.31	IN4019 0.08	2N2237 0.23	2N4074 0.18
AD149 0.86	BC115 0.21	BC334 1.27	BF178 0.40	BF281 0.42	MJE538 0.84	OC43 1.73	TIP30A 0.52	IN4020 0.08	2N2238 0.23	2N4075 0.18
AD161 0.40	BC125 0.21	BCY34 1.15	BF179 0.40	BF282 0.42	MJE539 0.84	OC44 0.98	TIP31A 0.38	IN4021 0.08	2N2239 0.23	2N4076 0.18
AD162 0.40	BC126 0.21	BCY39 3.91	BF180 0.32	BF283 0.42	MJE540 0.84	OC45 0.75	TIP32A 0.41	IN4022 0.08	2N2240 0.23	2N4077 0.18
AF106 0.40	BC127 0.17	BCY40 1.44	BF181 0.32	BF284 0.42	MJE541 0.84	OC46 0.75	TIP33A 0.41	IN4023 0.08	2N2241 0.23	2N4078 0.18
AF114 0.86	BC136 0.22	BCY42 0.35	BF182 0.35	BF285 0.42	MJE542 0.84	OC47 0.75	TIP34A 0.41	IN4024 0.08	2N2242 0.23	2N4079 0.18
AF115 0.86	BC137 0.22	BCY43 0.35	BF183 0.32	BF286 0.42	MJE543 0.84	OC48 0.75	TIP35A 0.41	IN4025 0.08	2N2243 0.23	2N4080 0.18
AF116 0.86	BC147 0.14	BCY58 0.22	BF184 0.32	BF287 0.42	MJE544 0.84	OC49 0.75	TIP36A 0.41	IN4026 0.08	2N2244 0.23	2N4081 0.18
AF117 0.86	BC148 0.14	BCY70 0.20	BF185 0.35	BF288 0.42	MJE545 0.84	OC50 0.75	TIP37A 0.41	IN4027 0.08	2N2245 0.23	2N4082 0.18
AF139 0.15	BC149 0.15	BCY71 0.20	BF186 0.35	BF289 0.42	MJE546 0.84	OC51 0.75	TIP38A 0.41	IN4028 0.08	2N2246 0.23	2N4083 0.18
AF186 0.15	BC157 0.15	BCY72 0.20	BF187 0.35	BF290 0.42	MJE547 0.84	OC52 0.75	TIP39A 0.41	IN4029 0.08	2N2247 0.23	2N4084 0.18
AF239 0.45	BC158 0.15	BCZ11 2.01	BF188 0.35	BF291 0.42	MJE548 0.84	OC53 0.75	TIP40A 0.41	IN4030 0.08	2N2248 0.23	2N4085 0.18
AF291 4.60	BC159 0.15	BCZ15 0.48	BF189 0.16	BF292 0.42	MJE549 0.84	OC54 0.75	TIP41A 0.41	IN4031 0.08	2N2249 0.23	2N4086 0.18
AFZ12 4.60	BC167 0.13	BD121 1.96	BF190 0.26	BF293 0.42	MJE550 0.84	OC55 0.75	TIP42A 0.41	IN4032 0.08	2N2250 0.23	2N4087 0.18
ASV26 1.61	BC170 0.13	BD123 3.22	BF191 0.26	BF294 0.42	MJE551 0.84	OC56 0.75	TIP43A 0.41	IN4033 0.08	2N2251 0.23	2N4088 0.18
ASV27 1.04	BC171 0.12	BD124 2.30	BF192 0.26	BF295 0.42	MJE552 0.84	OC57 0.75	TIP44A 0.41	IN4034 0.08	2N2252 0.23	2N4089 0.18

VALVES

E130L 19.39	E180CC 11.39	EF86 1.74	IGXU1 16.10	PC97 1.38	QV5-3000A 356.46	UL84 1.38	4B32 29.16	6CW4 8.83	12BE6 2.79	5670 5.18
A1854 18.45	E180CC 11.39	EF89 1.84	IGXU2 28.43	PC98 1.38	QZ06-20 31.25	UM80 1.15	4C35 74.75	6D2 1.01	12BH7 1.29	5675 2.17
A2087 13.58	E180CC 11.39	EF91 2.07	IGXU3 30.49	PC99 1.15	R10 5.75	UY41 1.44	4CX250B 51.75	6D6 3.00	12BZ7 3.11	5687 6.31
A2134 20.13	E186F 12.58	EF93 1.15	IGXU5 17.25	PC88 1.38	R17 1.89	YU85 1.20	4CX350A 80.50	6DQ6B 4.69	12E1 1.67	5696 4.35
A2293 8.62	E188CC 9.40	EF94 1.24	IGXU5 17.25	PC89 1.56	R18 4.89	XG1-2500 58.02	4X150A 24.41	6EA8 3.38	12E11TT 19.26	5718 7.87
A2426 17.63	E280F 25.88	EF95 6.27	GZ32 1.44	PC81 1.61	R19 1.38	XG2-6400 113.50	4X150D 28.75	6EB8 2.44	12E11A 34.50	5725 5.62
A2521 24.38	E283CC 9.02	EF98 1.44	GZ33 4.60	PC80 1.51	R20 1.66	XG5-500 28.23	5B25A 23.12	6E6 2.02	13E1 123.05	5726 3.62
A2590 14.43	E283CC 9.02	EF98 1.44	GZ34 2.88	PC82 2.17	RC2-250 35.77	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5727 3.62
A3343 51.75	EA52 28.18	EF99 4.60	GZ34 2.88	PC82 2.17	RC3-250A 37.49	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5728 3.62
AZ31 1.26	EA76 2.30	EF80A5 12.65	KT61 4.02	PC80 1.15	RG3-1250 63.94	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5729 3.62
AZ41 1.32	EACB80 1.38	EF80S5 12.65	KT66 11.50	PC82 1.15	RG4-1250 43.13	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5730 3.62
AK448 110.27	EAC91 0.92	EH90 1.61	KT88 13.80	PC86 1.84	RG4-3000 90.36	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5731 3.62
BR484 149.99	EAF42 1.44	EK90 1.24	KTW61 2.02	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5732 3.62
BS90 52.27	EAS80 1.38	EK91 1.24	KTW62 2.02	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5733 3.62
BT5 58.13	EB91 1.01	EL34 4.02	KTW63 2.02	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5734 3.62
BT17 106.89	EB91 1.01	EL34TH 2.53	M8079 12.29	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5735 3.62
BT19 36.17	EB91 1.01	EL34TH 2.53	M8080 9.49	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5736 3.62
BT59 37.49	EB91 1.01	EL34TH 2.53	M8081 11.30	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5737 3.62
BT69 333.50	EB91 1.01	EL34TH 2.53	M8082 9.87	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5738 3.62
BT75 102.46	EB91 1.01	EL34TH 2.53	M8083 11.30	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5739 3.62
BT95 127.02	EB91 1.01	EL34TH 2.53	M8084 9.87	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5740 3.62
CB131 2.30	EBF89 0.97	EL84 1.15	M8097 4.09	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5741 3.62
CL33 2.30	EBF89 0.97	EL84 1.15	M8098 5.50	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5742 3.62
CL33 2.30	EBF89 0.97	EL84 1.15	M8099 5.98	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5743 3.62
CL33 2.30	EBF89 0.97	EL84 1.15	M8100 5.98	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5744 3.62
CL33 2.30	EBF89 0.97	EL84 1.15	M8101 5.98	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5745 3.62
CL33 2.30	EBF89 0.97	EL84 1.15	M8102 5.98	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5746 3.62
CL33 2.30	EBF89 0.97	EL84 1.15	M8103 5.98	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12	6E6 2.02	13E1 123.05	5747 3.62
CL33 2.30	EBF89 0.97	EL84 1.15	M8104 5.98	PC87 1.84	RG5-250 53.54	XG5-500 28.23	5B25M 23.12			

TEST COMPONENTS ON THIS NEW OSCILLOSCOPE

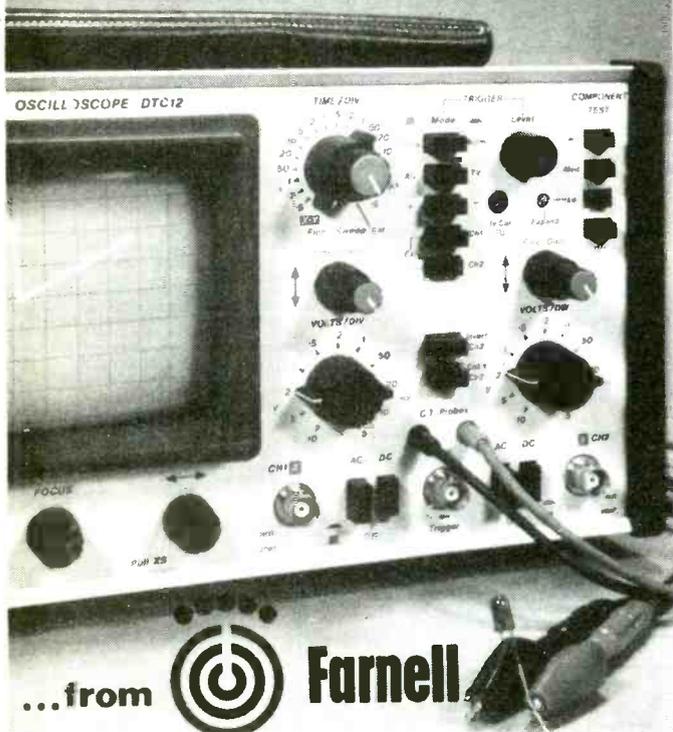

USE READER CARD FOR DETAILS
WW - 040 FOR FURTHER DETAILS

Sowter Transformers

With 40 years' experience in the design and manufacture of several hundred thousand transformers we can supply:

**AUDIO FREQUENCY
TRANSFORMERS OF EVERY TYPE
YOU NAME IT! WE MAKE IT!
OUR RANGE INCLUDES**

Microphone transformers (all types), Microphone Splitter/Combiner transformers, Input and Output transformers, Direct Injection transformers for Guitars, Multi-Secondary output transformers, Bridging transformers, Line transformers, Line transformers to G.P.O. Isolating Test Specification, Tapped impedance matching transformers, Gramophone Pickup transformers, Audio Mixing Desk transformers (all types), Miniature transformers, Microminiature transformers for PCB mounting, Experimental transformers, Ultra low frequency transformers, Ultra linear and other transformers for Transistor and Valve Amplifiers up to 500 watts, Inductive Loop Transformers, Smoothing Chokes, Filter, Inductors, Amplifier to 100 volt line transformers (from a few watts up to 1,000 watts), 100 volt line transformers to speakers, Speaker matching transformers (all powers), Column Loudspeaker transformers up to 300 watts or more.

We can design for RECORDING QUALITY, STUDIO QUALITY, HI-FI QUALITY OR P.A. QUALITY. OUR PRICES ARE HIGHLY COMPETITIVE AND WE SUPPLY LARGE OR SMALL QUANTITIES AND EVEN SINGLE TRANSFORMERS. Many standard types are in stock and normal dispatch times are short and sensible. OUR CLIENTS COVER A LARGE NUMBER OF BROADCASTING AUTHORITIES, MIXING DESK MANUFACTURERS, RECORDING STUDIOS, HI-FI ENTHUSIASTS, BAND GROUPS, AND PUBLIC ADDRESS FIRMS. Export is a speciality and we have overseas clients in the COMMONWEALTH, E.E.C., USA, MIDDLE EAST, etc. Send for our questionnaire which, when completed, enables us to post quotations by return.

E. A. Sowter Ltd.

Manufacturers and Designers

E. A. SOWTER LTD. (Established 1941) : Reg. No. England 303990
The Boat Yard, Cullingham Road, Ipswich IP1 2EG, Suffolk
P.O. Box 36, Ipswich, IP1 2EL, England
Phone: 0473 52794 and 0473 219390
Telex 987703G Sowter

WW - 033 FOR FURTHER DETAILS

TO YOU IT'S JUST A MOVING IMAGE



But to us it's the result of electrons travelling 10,000 times faster than Concorde, deflected by 100 cm² of ultra pure stainless steel plate, welded in over 1000 places, and all in a vacuum of 10⁻⁷mm Hg.

Not only are we at the forefront of modern tube technology but we can also, through our unique worldwide sourcing service, probably locate those out of production, hard to find, items.

Let us help you with your requirement.



Zaerix Electronics Limited
Electron House, Cray Avenue, St Mary Cray,
Orpington, Kent BR5 3PN England
Telephone Orpington (0689) 27099 Telex 896810 ZANDI G

WW - 076 FOR FURTHER DETAILS

SAMSONS

(ELECTRONICS) LTD.

9-10 Chapel Street, Marylebone
London NW1 5DN
21-23 Bell Street, London, NW1
01-262 5125 & 01-723 7851

MUFFIN FANS SPECIAL OFFER!!

24 0v fans
4 1/2x4 1/2x1 1/8" £5.75
inc. VAT + postage.
11 0v fans
4 1/2x4 1/2x1 1/8" £4.75
inc. VAT + postage.
Radiospares price
£14.50!!!

PLEASE ADD 15% TO ALL ORDERS INC. CARR.

12 or 24 VOLT				30 VOLT RANGE			
Ref.	12v	24v	£	Ref.	Amps	£	£
111	0.5	0.25	2.42	1.00	112	0.5	2.90
213	1.0	0.5	2.90	1.00	79	1.0	3.93
71	2	1	3.86	1.00	3	2.0	6.35
18	4	2	4.46	1.20	20	3.0	6.82
85	5	2.5	6.16	1.20	21	4.0	8.79
70	6	3	6.99	1.20	51	5.0	10.86
108	8	4	8.16	1.30	117	6.0	12.29
72	10	5	8.93	1.50	88	8.0	16.45
116	12	6	9.89	1.50	89	10.0	18.98
17	16	8	11.79	1.50	90	12.0	21.09
115	20	10	15.38	1.60	91	15.0	24.16
187	30	15	19.72	1.70	92	20.0	32.40
226	60	30	40.41	2.00			

50 VOLT RANGE			60 VOLT RANGE			
Ref.	Amps	£	Ref.	Amps	£	
102	0.5	3.75	1.10	124	0.5	4.27
103	1.0	4.57	1.10	126	1.0	6.50
104	2.0	7.88	1.30	127	2.0	8.36
105	3.0	9.42	1.50	125	3.0	12.10
106	4.0	12.82	1.60	123	4.0	13.77
107	6.0	16.57	1.70	40	5.0	17.42
118	8.0	22.29	2.00	120	6.0	19.87
119	10.0	27.48	4.00	121	8.0	27.92
109	12.0	31.79	4.00	122	10.0	32.51
				189	12.0	37.47

VOLTAGES OBTAINABLE
30v range 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30v, 12-0-12v or 15-0-15v. 50v range 5, 7, 8, 10, 13, 15, 17, 20, 25, 30, 33, 40v, 20-0-20v or 25-0-25. 60v range 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60v, 24-0-24 or 30-0-30.

AUTO STEPDOWN TRANSFORMERS FOR AMERICAN EQUIPMENT
240/110 Volts. 80-2250 watts. Regular stock line. Types 80-1500 watts are fully shrouded. Fitted with American two or three pin socket outlets and 3-core 240v mains lead. Types 1750 and 2250 watts are steel cased with two American socket outlets. Neon indicator, three-core mains lead and carrying handle. Send SAE for price list and further details. American sockets, plugs, adaptors also available.

SPECIAL OFFER: HINCHLEY MAINS ISOLATION TRANSFORMERS
Prim 240v. Sec 240v 250 watts. Open frame type. Tag connections. Fused input. £10, P&P £2, VAT £1.80. Parmeko pri tapped 115-220-240v. Sec 240v 6 amps. Fully shrouded top panel connections. Sec can be wired to give 120-0-120v, £25, carr. £5, VAT £4.50.

SPECIAL OFFER: VARIABLE TRANSFORMERS
Brand new, boxed, input 240v, output 0-265 volts 5 amps. Base or panel mounting with calibrated dial 0-265 volts and control knob. Price £28, inc. carr. and VAT.

SPECIAL OFFER: HIGH POWER AMPLIFIER TRANSFORMERS
Pri tapped 120-240v. Sec tapped 34-29-0-29-34V 6 amps and 46V 1A. Open frame type. Tag connection. Size 5x4 1/2x4ins. £9 inc. postage and VAT.

LATEST PURCHASE COMPUTER GRADE TRANSFORMERS. Conservatively rated. All Primaries 220-240V. No. 1 secs. 27V 10A, 9V 3A, 15V 1/2A x 2. Separate windings. £5.50, P&P £1.50.

No. 2 sec. tapped 26-31-36V, 11.2A £12. P&P £2.
No. 3 sec. 36V 6A £8.50, P&P £1.50.
No. 4 sec. 43V 3A £4.75, P&P £1.50.
No. 5 sec. 24V 2A £2.75, P&P £1.25.
No. 6 sec. 27.5-0-27.5V 1.2A and 7-0-7V 0.75A £3.50, P&P £1.25.
No. 7 17V 1A £2 P&P 75p.
No. 8 13V 3A and 15V 1A £3.50, P&P £1.25.
No. 9 18V 2A £2.50, P&P £1.
No. 10 sec. 29-29-27-0-27-29V 350 M/A "C" Core £3, P&P £1.
No. 11 sec. 10-7-0-7-10V 0.8A and 29-21-0-21-29V 0.37A £3, P&P £1.
No. 12 27V 1A 22V 1A 10V 1A 10V 1A, 4 separate windings "C" core type. £4.95, P&P £1.50.
No. 13. 65V 1A and 18-24V 1/2A £3.95, P&P £1.50.

No. 14. Tapped 12-15-27V 1A £2, P&P 75p.
No. 15. 6.3V 600M/A 6.3V 330M/A 6.3V 20 M/A 8V 500 M/A 50V 40 M/A £2, P&P £1.
No. 16. Tapped 14-15-16V 2A £2, P&P £1.
No. 17. Tapped 36-37-38-39-41-42-43V 1A "C" core £2.75 P&P £1.

HEAVY DUTY ISOLATION TRANSFORMERS
240-240V ex-computer equipment. Large selection available 10-15 amps. Fraction of maker price. Telephone for further details.

INDUSTRIAL 12V/24V 20-AMP BATTERY CHARGERS
AC input 240V 50Hz. DC output 20A. Built-in steel case. Size 15x12x3 1/2ins. Complete with battery leads, £85 - VAT. Callers only.

SPECIAL OFFER!!! PARV ALUX GEARED MOTORS
Cap start 240V AC RPM 44. Torque 4lb./ins., fitted with small cog on output shaft. Ideal for garage door opener or curtain puller. Our price £6.95 inc. carr. and VAT.

MONITORS
Ultronics 12" monochrome monitor 750 ohm Video in Video out circuit breaker protected, housed in stylish case with side mounted controls. A must for home computer users. Only a few left!! £45 inc. VAT. Callers only.

SPECIAL OFFER!!! Printed Circuit Board Motors manufactured by Servalco. 60v D.C. WKG 5.5 amps, 2350 r.p.m. Continuous torque 140oz. in. extremely powerful 3/4in. output shaft (keyed). List price £180 approx. Our Price only £28.50 inc. carr. V.A.T.

BLOCK PAPER CAPACITORS
8 MFD 1000v DC WKG £3, P&P £1. 8 MFD 350v DC WKG. £1. P&P 50p. 6 MFD 350v DC WKG. £75. P&P 25p. 6 MFD 300v AC WKG. £1.50. P&P 50p. 4 MFD 350v DC WKG 50p. P&P 25p. 2 MFD 350v DC WKG 40p. P&P 20p. 1 MFD 3000v DC WKG. 50p. P&P 20p.

CONSTANT VOLTAGE TRANSFORMERS
We have a wide selection of CVTs, all made by famous makers for many varied applications. Please ring for details.

IMPORTANT NEWS!!!
We would like to announce the opening of our new branch at 21-23 BELL STREET, NW1. It will, of course, stock our fantastic range of products that have made us famous over the past 25 years. PLUS!!! many new ranges, i.e. computer and electronic components, test equipment, panel meters, multimeters, semi-conductors, ICs and a large selection of plugs and sockets.

ISOLATION TRANSFORMERS
Pri tapped 220-240v sec. 240V 500 watts. Open frame type, top panel connections. Ex-equipment, but in perfect conditions. £18, carr. £3, VAT £2.70

E.H.T. TRANSFORMERS
High-grade E.H.T. Tranny, PRI 240v. sec. 10,000v. 18 M/A. Probably used for boiler ignition but with 101 other uses!!!
£5 inc. carr. - V.A.T.

DC WKG BLOCK CAPACITORS
8 MFD 1000V DC WKG £3, P&P £1, VAT 60p. 8 MFD 350V DC WKG £1.25, P&P 50p, VAT 26p. 6 MFD 350V DC WKG £1, P&P 50p, VAT 22p. 2 MFD 600V WKG. 80p, P&P 20p, VAT 12p. 1 MFD 1000V DC WKG 80p, P&P 20p, VAT 12p. 1 MFD 600V DC WKG 5 for £1.50, P&P 50p, V&P 30p. 0.25 MFD 500V DC WKG. 5 for £1.25, P&P 50p, VAT 16p. 0.1 MFD 1500V DC WKG 5 for £1.25, P&P 50p, VAT 16p. 2 MFD 100V DC WKG. 10 for £1.50, P&P 75p, VAT 33p. Tubular metalised paper caps 20 MFD 350V DC WKG with clip £3, P&P 50p, VAT 52p.

LOW CURRENT LT TRANSFORMERS
Open frame clamped type, split bobbin. All primaries 240V No. 1 sec tapped 12-15-20-24-30V 750 M/A £4. No. 2 sec. 9-0-9V 1A and 6.3V 200 M/A £2.50. No. 3 15-0-15V 600 M/A and 6.3V 200 M/A. No. 4 sec. 12-0-12V 750 M/A and 6.3V 200 M/A £4. No. 5 sec 13V 1/2A £1.50. No. 6 sec. 8V 1/2A 6.3V 600 M/A, 6.3V 300 M/A 50V 40 M/A £2.50. No. 7 sec 17V 1/2A (DC) £1.75. No. 8 sec 16.5V 1/2A x 2 £1.75. No. 9 sec 18V 2A £4. No. 10 sec 24V 2A £4.50. No. 11 sec 15V 2A £3.50. All prices include postage and VAT.

SPECIAL OFFER HEAVY DUTY TRANSFORMERS
Pri 240v sec 50V 15 Amps. Twice will give 100V CT or 50V 30A. Open frame type. Terminal block primary. Sec heavy wire leads. Frame size 8 1/2x7x5 inches. Screen winding between pri and sec. Brand new, fraction of list price. £32, carr. £5, VAT £5.55.

HEAVY DUTY LT C CORE TRANSFORMERS
Pri 110-220-240V. Secs 14V, 3V, 1 1/2V, 1V. Separate windings. All at 40 Amps. 14-15-15 1/2-17-18-18 1/2-19-19 1/2V can be obtained. £25, carr. £4, VAT £4.35.

110v. ISOLATION TRANSFORMERS
5,000w. Intermittent Rating. Housed in sturdy steel case, tapped 55v.-0-55v. Fitted with 16-amp twin outlets, ideal for any outside use of 110v. power tools, etc.
£85 inc. carr. V.A.T.

SPECIAL OFFER OF ERIE ELECTROLYTIC CAPACITORS
22,000 MFD 63V WKG £4.80 inc. postage and VAT. 6800 MFD 100V DC WKG £2.80 inc. postage and VAT. 3600 MFD 150V DC WKG £2.50 inc. postage and VAT. 10,000 MFD 16V DC WKG 5 for £2.50 inc. postage and VAT. 4.7 MFD 50V DC WKG 10 for 75p, inc. postage and VAT. 22,000 MFD 10V DC WKG 5 for £2.80 inc. postage and VAT.

SPECIAL OFFER LT TRANSFORMERS
Computer grade Pri 115-230V sec 27V 10A, 9V 3A, 15V 0.5A, 15V 0.5A, 175V 0.5A. Separate windings, open frame type, top panel connections, £3.95, postage £2.40, VAT 94p.

LATEST PURCHASE COMPUTER GRADE T TRANSFORMERS. All primaries 240V. No. 1 secs. 26V 6A £8.50, carriage £1.50. No. 2 sec. tapped 26-31-36V, 11.2A £12, P&P £2.
No. 3 sec. 36V 6A £8.50, P&P £1.50.
No. 4 sec. 43V 3A £4.75, P&P £1.50.
No. 5 sec. 24V 2A £2.75, P&P £1.25.
No. 6 sec. 27.5-0-27.5V 1.2A and 7-0-7V 0.75A £3.50, P&P £1.25.
No. 7 17V 1A £2, P&P 75p.
No. 8 13V 3A and 15V 1A £3.50, P&P £1.25.
No. 9 18V 2A £2.50, P&P £1.
PLEASE ADD VAT


WW-091 FOR FURTHER DETAILS

MONTE CARLO METHODS

Imagine using random numbers to control the firing of depth charges. Or to design a computer game. In this issue we explain Monte Carlo methods - and how they can solve numerical problems. We review a British-built product: the Dragon 32, a low-cost colour computer. We report on a programming method that uses speech synthesisers, we compare the BBC micro and the Sinclair Spectrum...

AND THAT'S JUST A SAMPLE OF PRACTICAL COMPUTING - TOGETHER WITH ADVICE FOR USERS OF PET, APPLE, TANDY AND SINCLAIR ZX 80/81 COMPUTERS. BUY BRITAIN'S LEADING PERSONAL COMPUTER MAGAZINE.

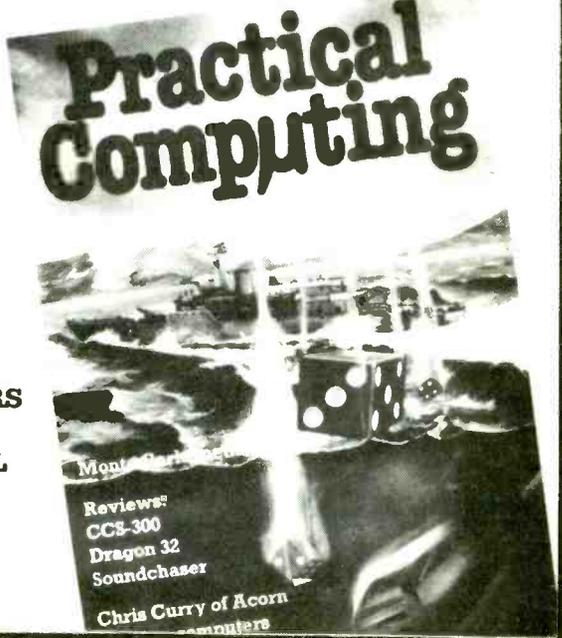**OCTOBER ISSUE OUT NOW
80p AT YOUR NEWSAGENTS - BUT HURRY**



COMPUTER WAREHOUSE

THE 'ALLADINS' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Diablo/DRE Series 30 2.5 mb. fully refurbished DEC RK05 media and software compatible. Front load **£550**. Topload **£295**.
PSL for 2 drives **£125**.
Diablo - DRE 44A-4000A or 4000B 10 mb 5+5 removable pack new and refurbished from **£995**.
CDC 80 mb removable pack DEC RM03 media and software compatible brand new from **£2,950**.
Honeywell 5+5 10 mb drives **£450** good s/h condition. For more information on controllers, expansions and ready to go sub systems contact sales office.

DISTEL ©

The UK's FIRST free of charge, 24 hr. public access data base. Get information on 1000's of stock items and order via your computer and credit card. On line now, 300 baud. CCITT tones, full duplex, fully interactive.

DON'T MISS THOSE BARGAINS CALL NOW, IT'S FREE!
7 days per week 84 hrs. per day
01-683 1133

COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU. Mains filtering and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing 1000's of pounds, and designed to run 24 hours per day. The PSU is fully screened and will deliver a massive +5v DC at 17 amps +15v DC at 1 amp and -15v DC at 5 amps. The unit is fully enclosed with removable top lid, twin fan cooling, mains filtering, trip switch, 'power on' and 'run' LED's, aluminium front panel and rear cable entries. Give your system that professional finish for only **£49.95** + £9.50 carr. — Dim. 19" wide 16" deep 10.5" high. Usable area 16" w. 10.5" h. 11.5" d. Units are in good but used condition 240 or 110 working complete with data. Large stocks of PDP8 spares — enquire.



COOLING FANS

Keep your "Hot Parts" cool and reliable with our range of professional fans.
ETRI 99XU01 Miniature equipment fan 240 v ac working DIM 92 x 25 mm BRAND NEW complete with finger guard. Makers price £16 our price **£9.95**
BUHLER 69.11.22 micro miniature 8-16 v DC reversible fan. Measures only 62 x 62 x 22 mm. Uses a brushless DC servo motor almost silent running ideal portable equipment. Life in excess of 10,000 hours. BRAND NEW manufacture price £32.00 our price **£12.95**
M JFFIN/CENTAUR cooling fans DIM 120 x 120 x 38 mm tested ex equipment 240v **£6.25** 115v **£4.95** + p&p £1.90
KOOLTRONICS Powerful small type blower gives massive air movement with centrifugal rotor or DIM as a cube 8" x 8" x 6" air aperture 2.5" x 2.5" with flange fixing. BRAND NEW 110v 50Hz ac working ONLY **£9.95** + £1.90 p&p



8" FLOPPY DISK DRIVES

Unbelievable value the DRE 7100 & 7200 8" disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today; the only difference being our PRICE and the superb manufacturing quality. The 7100 single sided & 7200 double sided drive accept hard or soft sectoring. IBM or ANSI standard giving a massive 0.8 MB (7100) & 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMENS etc compatible. Supplied BRAND NEW with user manual and 90 day warranty.
7100 single sided **£225.00** + 9.50 + vat
7200 double sided **£295.00** + 9.50 carr + vat
full technical manual **£20.00** alone **£9.00** with drive, refund of difference on purchase of drive.
SHUGART s/h 800-2 8" Drive's 110v 50Hz motor **£160** + £9.50 carr.
Removed from working equipment but untested. SA120 Alignment disk's **£9.95**

9" Monitors

DT10 Monitor a complete **MOTOROLA 9"** video monitor housed in an attractive metal case DIM approx. 10" deep 16" wide and 11" high. The monitor has a 75 ohm composite video input with a bandwidth of 18 mhz. A separate internal PSU delivers 5v dc for external use and 12v DC for video monitor. The case has sufficient room inside for mounting other units such as 5" disk drives etc. Internal pots give full control over all monitor functions. Supplied in a tested, as new or little used condition. 240v AC operation **£55.00** Carriage and Insurance **£10.50**
MOTOROLA 9" open chassis monitor. Standard 240 v AC with composite 75 ohm video input, bandwidth in excess of 18 mhz. Monitors are ex equipment and although unguaranteed they are all tested prior to despatch, and have no visible burns on the screens. Dim approx. 9" x 9" x 9". Supplied complete with mains and input lead. Ideal ZX81 etc or giving the tele back to the family!! Black and White phosphor **£35.00** + £9.00 carr.



SUPER SCOOP

CENTRONICS 739-2

The "Do everything Printer" at a price that will NEVER be repeated. Standard Centronics interface, full graphics, 4 type fonts with high definition & proportional spacing for word processor applications, 80-132 columns, single sheet, roll or sprocket paper handling plus much more. Available only from DISPLAY ELECTRONICS at a ridiculous price of only **£299.00**
Options: carriage & insurance **£10.00**
Interface Cable **£10.00**
RS232 Converter **£45.00**
SAVE £250



TELETYPE ASR33 I/O TERMINALS

FROM **£195** + CAR. + VAT
Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry. RS232 serial interface. 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order.
Options: Floor stand **£12.50** + VAT
KSR33 with 20ma loop interface **£125.00** + Sound proof enclosure **£25.00** + VAT



SOFTY 2

The amazing SOFTY 2. The complete "toolkit" for the open heart software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, JHF modulator, Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! Only **£169.00** pp £1.95 Data sheet on request

MAINS FILTERS

Professional type mains filters as used by "Main Frame" manufacturers. Ideal for curing those unerving hang ups and data glitches — fit one now and cure your problems.
Suppression Devices SA5A upto 5 amp load **£5.95**
Corcom Inc F1886 up to 20 amp load **£9.50**
Corcom Inc F1900 upto 30 amp load **£12.25**

RECHARGEABLE BATTERIES

CYCLON type D001 sealed lead acid maintenance free 2v 2.5 ah. will deliver over 300 amps on short circuit!! Brand new at only **£2.95**
SAFT VR2C size 'C' 1.2v 2 ah. nickel cadmium **£1.50** each 10 for **£11.50**

RCA FULLY CASED ASCII CODED KEYBOARDS



IDEAL TANGERINE OHIO ETC.
Straight from the USA made by the world famous RCA Co., the VP600 Series of cased freestanding keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology. Guaranteed in excess of 5 million operations. The keyboard has a host of other features including full ASCII 128 character set, user definable keys, upper/lower case, rollover protection, single 5V rail, keyboard impervious to liquids and dust. TTL or CMOS outputs, even an on-board tone generator for keypress feedback and a 1 year full RCA backed guarantee.
VP601 7 bit fully coded output with delayed stroke, etc. **£43.95**
VP611 Same as VP601 with numeric pad **£54.95**
VP606 Serial, RS232, 20MA and TTL output with 6 selectable Baud Rates **£64.26**
VP616 Same as VP606, with numeric pad **£84.34**
Plug and cable for VP601, VP611 **£2.25**
Plug for VP606, VP616 **£2.10**
Pc.st, Packing and Insurance **£1.95**
ORDER NOW OR SEND FOR DETAILS

D.C. POWER SUPPLY SPECIALS

Experimentors PSU Ex-GPO unit all silicon electronics. Outputs give +5v @ 2 amps, +12v @ 800 ma, -12v @ 800 ma, +24v @ 350 ma, 5v @ 50 ma floating. Dim 160 x 120 x 350 mm. All outputs fully regulated and short circuit proof. Removed from working equipment, but untested. Complete with circuit. Transformer guaranteed. Only **£14.50** + £2.50 pp.
POWER ONE CP143 super compact unit giving continuous output of 5v @ 5 amps. dim. 215 x 67 x 80 mm. BRAND NEW and guaranteed Only **£21.00** + £1.50 pp.
CUSTOM POWER CO55 5v @ 3 amp. Very compact unit dim. approx 60 x 90 x 190 mm. Semi open chassis full crowbar overvoltage protection. Tested Ex Equipment. **£11.95** + pp £1.25
MINI SYSTEM PSU Ex equipment unit ideal for the small micro. Outputs give 5v @ 3 amps, +12v @ 1 amp and -12v @ 300 ma. Crowbar overvoltage protection and current limit. Fully tested. Dim 70 x 165 x 320 mm. Complete with Circuit only **£12.95** + £2.00 pp.
PERIPHERAL SYSTEM SUPPLY. Fully cased unit supplied in a Brand new or little used condition. Outputs give 5v @ 11 amps, "+- 15-17v @ 8 amps, "- 15-17v @ 8 amps and "+ 24v @ 4 amps. All outputs are crowbar protected and the 5 volt output is fully regulated. Fan cooled. Supplied tested, with circuit **£55.00** + £8.50 carr.
MAIN FRAME SUPPLY. A real beefy unit designed for MINI or MAINFRAME use outputs give 5 volts @ 50 amps, +12v @ 5 amps, -12v @ 10 amps. All output are fully regulated with crowbar overvoltage protection on the 5v output. Supplied with circuit and tested. Ex-Equip. 110v AC input. Only **£49.95** + carr. £10.50.

300 BAUD DATA MODEMS

Join the communications revolution with our standard EX GPO 2a/b data MODEMS. Modem operates on standard CCITT tones with full auto answer facilities. Will switch to ANSWER or ORIGINATE. Standard RS232 i/o connections. Ideal networks. DISTEL etc Complete with data. Untested but good condition **£55.00** carr. £8.50.

1200 BAUD DATA PUMP MODEMS

Compact unit for use with private or "Dial up lines" Designed to work in pairs at any baud rate upto 1200 full duplex (4 wire circuit) or half duplex (2 wire circuit). Features include remote test facilities. RS232 i/o lines etc. Supplied with data in working order, but less case cover **£65.00** + £4.50 carr.

66% DISCOUNT

ELECTRONIC COMPONENTS & EQUIPMENT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Caps, P.C.B.'s, Sub-assemblies, Switches, etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads, for unbeatable value!! Sold by weight
2.5kls **£4.25** + pp **£1.25**
10kls **£10.25** + pp **£2.25**
5kls **£3.90** + pp **£1.80**
20kls **£17.50** + pp **£4.75**

OLIVETTI TE300 REDUCED TO CLEAR

Complete input output terminal with integral 8 hole paper tape punch and reader. Unit operates at 150 baud in standard ASCII. Ideal as a cheap printer for a MICRO etc. 120 columns. Serial data i/o. Supplied complete with 1.50. untested, unguaranteed **£65.00** + £11.50 carr.




DISPLAY ELECTRONICS

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value **£2.00**. Minimum Credit Card order **£10.00**. Minimum BONA FIDE account orders from Government depts, Schools, Universities and established companies **£20.00** Where post and packing not indicated please ADD 80p + VAT Warehouse open Mon-Fri 9.30 - 5.30. Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.
64-66 Melfort Road, Thornton Heath, Near Croydon, Surrey
01-689 7702 - 01-689 6800 Telex 27924



BRITAIN'S BETTER BARGAIN STILL IN WORLD-WIDE DEMAND

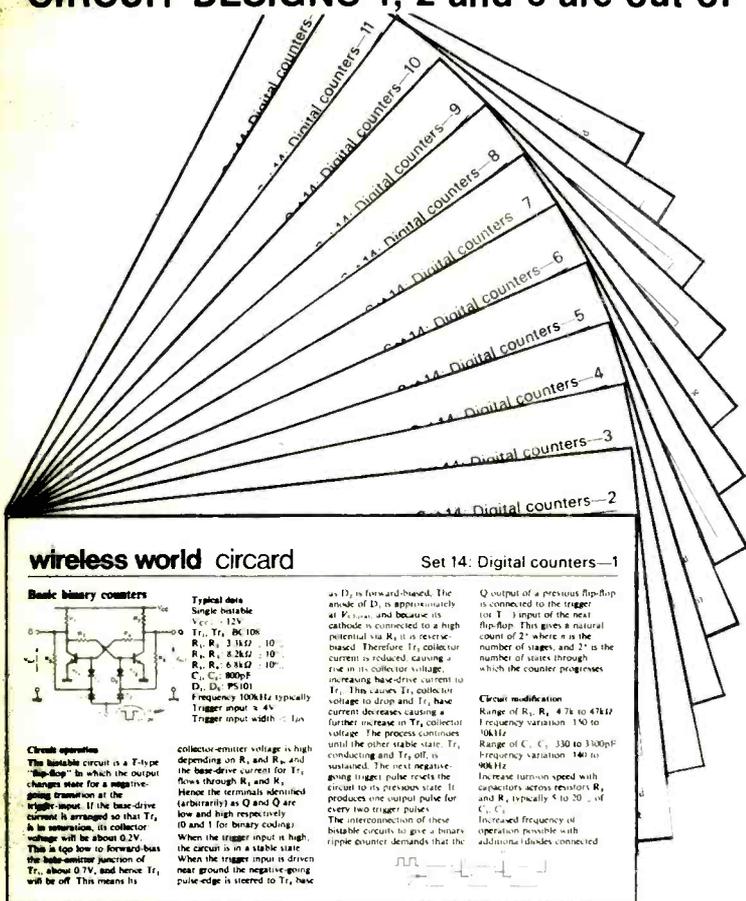WIRELESS WORLD CIRCARDS at 1976 prices 10% discount for 10 sets!
 Most sets are still available even though the companion volumes
 CIRCUIT DESIGNS 1, 2 and 3 are out of print. (CIRCARDS SETS 1 to 30).



Fill gaps in your circuit files with these sets of 127 x 204 mm cards in plastic wallets. These unique circuit cards normally contain descriptions and performance data of 10 tested circuits, together with ideas for modifying them to suit special needs.

- 1 Basic Active filters 2 Switching Circuits, comparators and Schmitts (But these gaps cannot be filled)
 6 Constant current circuits 7 Power amplifiers 8 Astable circuits 9 Optoelectronics 10 Micro power circuits 11 Basic logic gates
 12 Wideband amplifiers 13 Alarm circuits 14 Digital Counters 15 Pulse modulators 16 Current differencing amplifiers – signal processing
 17 Current differencing amplifiers – signal generation 18 Current differencing amplifiers – measurement and detection
 19 Monostable circuits 20 Transistor pairs 21 Voltage-to-frequency converters
 22 Amplitude modulation and detection 23 Reference circuits 24 Voltage regulators 25 RC oscillators – 1 26 RC oscillators – 2
 27 Linear cmos – 1 28 Linear cmos – 2 29 Analogue multipliers 30 Rms/log/power laws 31 Digital multipliers
 32 Transistor arrays 33 Differential and bridge amplifiers 34 Analogue gate applications – 1 35 Analogue gate applications – 2.

To IPC Electrical – Electronics Press Ltd.
 General Sales Department,
 Room 205,
 Quadrant House,
 Sutton,
 Surrey SM2 5AS

Company registration in England
 Quadrant House, The Quadrant,
 Sutton, Surrey SM2 5AS
 Reg. No 677128

Please send me the following sets of
 Circards: £2 each,
 £18 for 10 post free.
 Remittance enclosed payable
 to IPC BUSINESS PRESS LTD.

Name (Please print)
 Address (Please print)

TRANSFORMERS

Despatch by return

CONTINUOUS RATINGS

MAINS ISOLATORS

Pri 0-120, 0-100-120V. Sec 0-CT-115Vx2.

Ref.	VA (Watts)	£	P&P
07★	20	5.32	1.50
149	60	8.84	1.60
150	100	10.06	1.84
151	200	13.69	2.12
152	250	16.31	2.64
153	350	20.34	2.12
154	500	25.02	2.90
155	750	35.91	OA
156	1000	45.89	OA
157	1500	60.52	OA
158	2000	72.43	OA
159	3000	101.12	OA
161	6000	203.65	OA

★115 or 240v sec only. State volts required. Pri 0-220-240V.

12 or 24-VOLT RANGE

Separate 12V windings Pri 220-240V

Ref.	12V Amps	24v	£	P&P
242	300mA		2.41	.90
213	1	0.5	3.19	1.20
71	2	1.0	4.25	1.20
18	4	2.0	4.91	1.60
85	5	2.5	6.78	1.50
70	6	3.0	7.69	1.40
108	8	4.0	8.98	1.64
72	10	5.0	9.82	1.80
116	12	6.0	10.89	1.90
17	16	8.0	12.97	2.12
115	20	10.0	17.46	2.44
187	30	15.0	21.69	2.64
22F	60	30.0	44.45	OA

30 VOLT RANGE

Sec. Volts available 3, 4, 5, 7, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V

Ref.	Amps	30v	15v	£	P&P
112	0.5	1		3.19	1.20
79	1	2		4.32	1.40
3	2	4		6.99	1.60
20	3	A	6	8.10	1.85
21	4	M	8	9.67	1.90
51	5	P	10	11.95	2.00
117	6	S	12	13.52	2.02
88	8		16	18.10	2.26
89	10		20	20.88	2.24
90	12		24	23.20	OA
91	15		30	26.60	3.00
92	20		40	35.64	4.83

50 VOLT RANGE 2x25V tapped secs

Volts available 5, 7, 8, 10, 13, 15, 17, 20, 25, 30, 33, 40 or 25V-0-20V or 25V-C-25V

Ref.	Amps	50v	25v	£	P&P
102	0.5	1		4.13	1.40
103	1	2		5.03	1.40
104	2	4		8.69	1.84
105	3	6		10.36	1.90
106	4	8		14.10	1.90
107	6	12		18.01	1.84
118	8	16		24.52	2.70
119	10	20		30.23	OA
109	12	24		36.18	OA

60 VOLT RANGE

Pri 0-120Vx2

2x30V tapped secs volts available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 4C, 48, 60V, or 24V-0-24V or 30V-0-30V

Ref.	Amps	60v	30v	£	P&P
124	0.5	1		4.70	1.50
126	1	2		7.15	1.50
127	2	A	4	9.20	1.90
125	3	M	6	13.31	2.02
123	4	P	8	15.15	2.26
40	5	S	10	19.16	2.24
120	6		12	21.86	2.64
121	8		16	30.72	OA
122	10		20	35.76	OA
189	12		24	41.22	OA

SCREENED MINIATURES Pri 240V

Ref.	mA	Sec Volts	£	P&P
238	200	3-0-3	3.11	.90
212	1A, 1A	0-6, 0-6	3.45	1.20
13	100	9-0-9	2.59	.80
235	330, 330	0-9, 0-9	2.41	.90
207	500, 500	0-8-9, 0-8-9	3.36	1.20
208	1A, 1A	0-8-9, 0-8-9	4.27	1.40
236	200, 200	0-15, 0-15	2.41	.90
239	50MA	12-0-12	3.11	.90
214	300, 300	0-20, 0-20	3.39	1.20
221	700(DC)	20-12-0-12-20	4.13	1.20
206	1A, 1A	0-15-20, 0-15-20	5.60	1.60
203	500, 500	0-15-27, 0-15-27	4.83	1.50
204	1A, 1A	0-15-27, 0-15-27	7.30	1.60

AUTO TRANSFORMERS

Volts available 105, 115, 190, 200, 210, 220, 230, 240. For step up or step down.

Ref.	VA (Watts)	TAPS	£	P&P
113	15	0-10-115-210-240V	2.39	1.20
64	80	0-10-115-210-240V	4.84	1.40
4	150	0-10-115-200-220-240V	6.48	1.60
67	500	0-10-115-200-220-240V	13.30	2.24
84	1000	0-10-115-200-220-240V	22.70	2.80
93	1500	0-10-115-200-220-240V	28.17	OA
95	2000	0-10-115-200-220-240V	42.14	OA
73	3000	0-10-115-200-220-240V	71.64	OA
80	4000	0-10-115-200-220-240V	93.01	OA
57	5000	0-10-115-200-220-240V	108.30	OA

400/440V ISOLATORS

400/440 to 200/240V

VA	Ref.	£	P&P
60	243	8.11	1.50
250	246	16.07	OA
350	247	19.88	OA
500	248	24.77	OA
1000	250	50.53	OA
2000	252	74.79	OA
3000	253	104.86	OA
6000	254	207.92	OA

CASED AUTOS

240V cable input USA 115V outlets

VA	Price	P&P	Ref
20	£7.21	1.25	56W
80	£9.35	1.50	64W
150	£12.10	1.84	4W
250	£14.73	1.60	69W
500	£22.14	2.24	67W
1000	£33.74	2.80	84W
2000	£60.47	OA	95W

CONSTANT VOLTAGE TRANSFORMERS

For 'clean' mains to computers, peripherals... Tap Changing Stabilisers Type Cased. 250VA £137.36 (+ p&p) 500VA £159.43 (+ VAT) 1kVA £213.12 (+ VAT)

COTSWOLD TOROIDALS

OFF THE SHELF

30VA, 60VA, 100VA, 160VA, 230VA, 330VA, 530VA Send for list

PLEASE ADD 15% VAT AFTER P&P Overseas post extra

OTHER PRODUCTS

AVO TEST METERS

8 Mk. 5 Latest Model	£122.10
71 (Handy)	£49.30
73 (portable size)	£68.90
MM5 Minor	£43.60
DA211 LCD Digital	£58.50
DA212 LCD Digital	£81.90
DA116 LCD Digital	£131.30
Megger 70143 500v	£101.50
Megger Battery BM7	£71.60
DA117 Autorange LCD	£157.00

Avo Cases and Accessories P&P £1.60 + VAT 15%

BRIDGE RECTIFIERS

200v	2A	45p
400v	2A	55p
100v	25A+	£2.10
100v	35A	£2.60
200v	4A	65p
400v	4A	85p
400v	6A	£1.40
500v	12A	£2.85

Send 20p for catalogue. Prices correct at 27/8/81

MAINS BATTERY ELIMINATORS

No wiring, ready to plug into 13A socket. 3, 4.5V, 6, 7.5V 9, 12V DC @ 300mA £5.10 + £1.20 p&p + VAT 15%

ANTEX SOLDERING IRONS 15W CCN240 or C. £5. Safety stand £1.75 25W X25 £5.30 12V 25W car soldering kit £5.30 P&P 50p + VAT

CABLES

eg: URM 70 Multicores, singles. Phone for quote.


Precision De-Solder Pumps - Spring loaded, quick action button release for one hand working. Large £5.86 P&P 35p + VAT. Small £5.17 P&P 30p + VAT. Replacement tips: Small 65p - VAT. Large 86p + VAT.

Telephones: Trimphone £28 + £1.20 p&p + VAT. Desk phones 746 £11.50 + £1.20 p&p + VAT. Wall phones £14.50 + £1.20 p&p + VAT.

METAL OXIDE RESISTORS £1/100 + VAT Special Offer TR4 5% Electroil (100s only). Use in place of c.film. 47Ω 75Ω 180Ω 360Ω 350Ω 430Ω 470Ω 510Ω 560Ω 820Ω 1K 1K2 1K3 1K6 1K8 2K 2K4 3K 16K 20K 22K 24K 27K 47K 82K 100K 110K 120K 130K 180K 220K 270K 300K P&P 30p + VAT

hi! performance hi! competitive hi!

PATTERNS

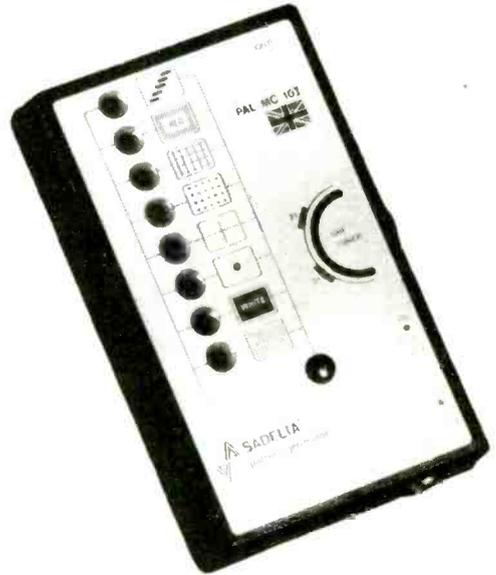

TO HAND

Hand held Colour Pattern Generators. Truly portable, an overnight charge gives a full day's use from internal batteries. Many in use, both Workshop and Field.

Pocket sized, 131 x 81 x 23mm.

MC10 SERIES

Ideal for TV servicing, both Colour and Mono, with a 10mV output level and weighing only 250g inc. battery.

AT LESS than £150 inc. P+D

RGB 11 SERIES

Just the answer for Commercial and Hobby CCTV monitors, VDU's and Video Games, with an output that is TTL Compatible and weighs only 220g inc. battery.

£120 inc. P+D

Features of both models include:

- 8 CCIR 1 PAL Colour Patterns
- Fingertip tuning: UHF channels 21 thru 41
- Subcarrier freq: 4.433619 MHz, crystal controlled
- Lines: 625 derived from subcarrier
- Sound: FM + 6 MHz, modulated at 650 Hz
- Video Modulation: Negative, double sideband
- Red, Green and Blue TTL Output signals
- Blanking Pulse and other characteristics in accordance with CCIR

BOTH COMPLETE with Carrying Case, 75 Ohms Aerial Lead or TTL Output Lead, Nicad Battery, Mains Power Unit Battery Charger and Handbook

PLUS MC32 Series of BENCH MODELS for all Applications

Fully Guaranteed for One Year, send for FREE DATA

House of Instruments
Clifton Chambers, 62 High Street
Saffron Walden, Essex CB10 1EE
Tel: (0799) 24922 Telex: 818750



hi! reliability hi! service hi! performance hi! competitive hi! hi! competitive hi! House of Instruments Ltd.

WW - 067 FOR FURTHER DETAILS

HEMMINGS ELECTRONICS AND MICROCOMPUTERS

16 BRAND ST
HITCHIN
HERTS
SG5 1JE

Tel: (0462) 33031
Shop open Mon. - Sat. 9 a.m. - 5.30 p.m.
Closed all day Wednesday



Professional quality electronic components, brand new and fully guaranteed. Mail order by return of post. Cash/Cheque/POs or Banker's Draft with order, payable to Hemmings Electronics Ltd.



Official orders from schools, colleges and universities welcome. Trade and export enquiry welcome.

P.&P. add 60p to all orders under £10. Telephone your Access orders, using our 24-hr. Answerphone service. Please send SAE for full price list.

VAT - All prices exclusive of VAT - Please add 15% to total cost including P.&P. No VAT on export orders or books.

74LS TTL	LS136	25p	LS366A	30p	4025U	18p	4515	120p	LINEAR ICs	COMPUTER ICs	TRANSISTORS	TIP35A	18p	2N3771	160p	EPSON MX80/T	£320						
LS90	11p	LS137	46p	LS367A	30p	4027	25p	4516	70p	2114	80p	BC107	12p	BD679A	60p	TIP35B	170p	2N3772	180p	Type I			
LS01	12p	LS138	30p	LS368A	30p	4028	46p	4517	741	8pin	2514	80p	BC107B	15p	BD880AX	65p	TIP35C	100p	2N3773	250p	Type II		
LS02	12p	LS139	30p	LS373	80p	4029	90p	4518	741	14pin	2532	360p	BC108	12p	BFY51	24p	TIP36	170p	2N3819	25p	As Type I but including High Resolution Bit Image Printing		
LS03	12p	LS145	80p	LS374	80p	4032	90p	4519	7415	35p	2718	210p	BC108B	15p	BFY51	24p	TIP36A	170p	2N3821	25p	960 dots/line	£330	
LS04	12p	LS151	38p	LS375	40p	4033	150p	4520	80p	747	35p	2732	370p	BC109	12p	BFY90	85p	TIP36B	185p	2N3822	120p	Type III	
LS05	26p	LS153	38p	LS377	80p	4034	130p	4521	140p	748	35p	4116	60p	BC109B	15p	BF244A	30p	TIP36C	195p	2N3823	95p	As Type II but includes Super & Subscripts Auto Underlining and Italics	£38
7406	26p	LS154	150p	LS378	80p	4035	85p	4522	110p	CA3080E	70p	6116	60p	BC109C	15p	BSX19	28p	TIP41	50p	2N3824	95p	Securicor Carriage on all Printers	£8
LS08	12p	LS155	36p	LS379	85p	4038	100p	4526	70p	CA3130E	75p	6116	60p	BC147	9p	BSX20	20p	TIP41A	50p	2N3886	90p	36W Connector IDC	£4.00
LS09	18p	LS156	36p	LS386	280p	4040	50p	4527	70p	LA4422	285p	6502	350p	BC157	9p	MJE2955	95p	TIP41B	80p	2N3903	15p		
LS10	18p	LS157	36p	LS386	45p	4042	50p	4528	70p	LF355	90p	6800	290p	BC158	9p	MJE241	80p	TIP41C	50p	2N3904	15p		
LS11	18p	LS158	36p	LS390	50p	4043	50p	4529	120p	LF356	80p	6800	290p	BC177	25p	MJE251	80p	TIP42	50p	2N3905	15p		
LS12	15p	LS160A	36p	LS393	45p	4044	50p	4530	90p	LF357	100p	6800	290p	BC178	25p	MJE340	50p	TIP42A	50p	2N3906	15p		
LS13	25p	LS161A	36p	LS395	80p	4046	55p	4531	95p	LM301A	28p	6802	340p	BC179	25p	MJE350	90p	TIP42C	50p	2N4123	25p		
LS14	25p	LS162A	36p	LS398	130p	4049U	24p	4532	80p	LM307	85p	6809	300p	BC182A	10p	MJE520	90p	TIP42C	50p	2N4125	25p		
LS15	18p	LS163A	36p	LS399	120p	4050	24p	4534	460p	LM308A	95p	6809E	1285p	BC182B	10p	MJE2955	90p	TIP48	50p	2N4391	70p		
LS20	18p	LS164	40p	LS490	120p	4051	46p	4536	230p	LM311N	85p	6810	120p	BC182B	10p	MJE3055	90p	TIP49	50p	2N4392	70p		
LS21	18p	LS165	40p	LS540	70p	4052	50p	4538	80p	LM324	35p	6821	100p	BC183A	10p	MRF450A	45p	TIP50	40p	2N4401	25p		
LS22	18p	LS166	40p	LS541	100p	4053	50p	4539	90p	LM339	50p	6821	100p	BC184	10p	MRF450A	45p	TIP50	40p	2N4402	25p		
LS26	20p	LS168	84p	LS568	345p	4060	80p	4541	110p	LM348	75p	6821	100p	BC184C	10p	MRF475	120p	TIP110	75p	2N4403	25p		
LS27	20p	LS169	120p	LS569	345p	4066	35p	4543	80p	LM358	80p	6840	390p	BC184C	10p	MRF475	120p	TIP111	75p	2N4403	25p		
LS28	20p	LS170	75p	LS569	345p	4066	35p	4544	175p	LM380	95p	6844	1285p	BC212A	10p	MPS2369	25p	TIP112	60p	2N4410	45p		
LS30	15p	LS173	80p	LS569	345p	4066	35p	4547	130p	LM393	90p	6845	790p	BC212B	10p	MPS3640	30p	TIP115	40p	2N4416	95p		
LS32	18p	LS174	40p	LS564	150p	4069U	18p	4549	290p	LM393	90p	6845	790p	BC212B	10p	MPS3640	30p	TIP116	73p	2N4856	80p		
LS33	18p	LS175	40p	LS564	150p	4070	18p	4551	100p	MC1310P	210p	6850	140p	BC213A	10p	MPSA06	20p	TIP120	39p	2N4857	80p		
LS37	45p	LS181	96p	LS564	150p	4072	18p	4553	285p	MC1455	80p	6852	250p	BC213C	10p	MPSA06	20p	TIP120	39p	2N4857	80p		
7438A	45p	LS182	120p	LS565	150p	4073	18p	4554	185p	MC1456	135p	6854	280p	BC214	10p	MPSA12	35p	TIP121	80p	2N4919	120p		
LS38	15p	LS183	120p	LS570	135p	4075	18p	4555	45p	MC1458	35p	75451	70p	BC214C	10p	MPSA13	20p	TIP122	75p	2N4920	130p		
LS40	20p	LS190	44p	LS796	120p	4076	50p	4556	45p	MC3242A	830p	75452	70p	BC237A	12p	MPSA14	20p	TIP125	45p	2N4921	100p		
LS42	30p	LS191	44p	LS797	210p	4077	18p	4557	280p	MC3302	85p	75491	70p	BC237C	12p	MPSA18	20p	TIP126	80p	2N4922	95p		
LS47	50p	LS192	44p	LS798	210p	4078	18p	4558	125p	MC3340P	120p	75492	70p	BC238	12p	MPSA27	45p	TIP141	140p	2N5180	75p		
LS48	50p	LS193	44p			4081	18p	4559	410p	MC3401	85p	8126A	120p	BC238A	12p	MPSA42	25p	TIP142	100p	2N5191	75p		
LS49	65p	LS194A	40p			4082	18p	4560	100p	MC3403	70p	8126A	120p	BC238B	12p	MPSA56	25p	TIP142	100p	2N5191	75p		
LS51	16p	LS195A	40p			4083	30p	4561	100p	MC3456	107p	8126A	120p	BC238C	12p	MPSA63	20p	TIP145	140p	2N5192	75p		
LS54	18p	LS196	50p			4099	95p	4562	380p	MC3480	580p	8126A	120p	BC307A	16p	MPSA64	45p	TIP146	180p	2N5193	90p		
LS55	18p	LS197	55p			4099	95p	4563	380p	MC3401	58p	8126A	120p	BC307B	16p	MPSA77	60p	TIP147	170p	2N5194	90p		
LS73A	28p	LS221	60p	4000	11p	4190	80p	4568	280p	NE555	50p	8126A	120p	BC307C	16p	MPSA92	30p	TIP2955	70p	2N5196	90p		
LS74A	20p	LS240	64p	4001	12p	4161	80p	4569	170p	555 CMOS	90p	8126A	120p	BC308	16p	TIP29	35p	TIP2955	70p	2N5400	40p		
LS75	30p	LS241	64p	4001U	12p	4162	80p	4572U	30p	NE556	50p	8126A	120p	BC308B	16p	TIP29C	35p	TIP2955	70p	2N5401	40p		
LS76A	30p	LS242	64p	4002	12p	4163	80p	4580	380p	SN76023	180p	8155	370p	BC308B	16p	TIP29C	35p	TIP2955	70p	2N5401	40p		
LS77	32p	LS243	64p	4002U	12p	4174	80p	4581	240p	TA7205A	125p	8212	130p	BC308B	16p	TIP29C	35p	TIP2955	70p	2N5401	40p		
LS78A	32p	LS244	64p	4003	12p	4174	80p	4582	185p	TBA480Q	175p	8212	130p	BC309	16p	TIP30	35p	TIP2955	70p	2N5401	40p		
LS83A	40p	LS245	75p	4006	60p	4175	100p	4583	90p	TBA540Q	130p	8212	130p	BC309B	16p	TIP30	35p	TIP2955	70p	2N5401	40p		
LS86	40p	LS251	36p	4008	50p	4433	80p	4584	50p	TBA800	30p	8224	160p	BC328	15p	TIP30C	40p	2N2218A	40p	2N5456	35p		
LS86	40p	LS253	36p	4011	14p	4443	390p	4585	95p	TCA650	380p	8226	280p	BC328	15p	TIP31A	40p	2N2219	25p	2N5459	35p		
LS90	28p	LS256	36p	4011U	14p	4447	390p	4597	285p	TCA910	110p	8243	210p	BC337	15p	TIP31A	40p	2N2219	25p	2N5551	40p		
LS91	75p	LS257A	36p	4012	18p	4493	320p	4598	295p	TDA1004	290p	8251A	230p	BC338	15p	TIP31B	42p	2N2221	30p	2SC495	80p		
LS92	32p	LS258A	36p	4012U	18p	4494	320p	4599	290p	TLO81	40p	8253	420p	BC337	15p	TIP32	40p	2N2221A	30p	2SC1306	80p		
LS93	28p	LS259	36p	4013	25p	4495	330p	4602	140p	TLO82	40p	8255A	270p	BC337	15p	TIP32A	40p	2N2222	25p	2SC1369	250p		
LS95B	40p	LS260	22p	4014	50p	4499	330p	4603	100p	TLO84	30p	8259A	270p	BC337	15p	TIP32B	60p	2N2222	25p	2SC2028	250p		
LS107A	38p	LS266	22p	4015	50p	4501U	25p	4606	100p	TLO71	30p	8279	440p	BD135	42p	TIP32C	45p	2N2904A	25p	2SC2078	100p		
LS108A	38p	LS273	58p	4016	25p	4502	80p</																

THE CASE FOR

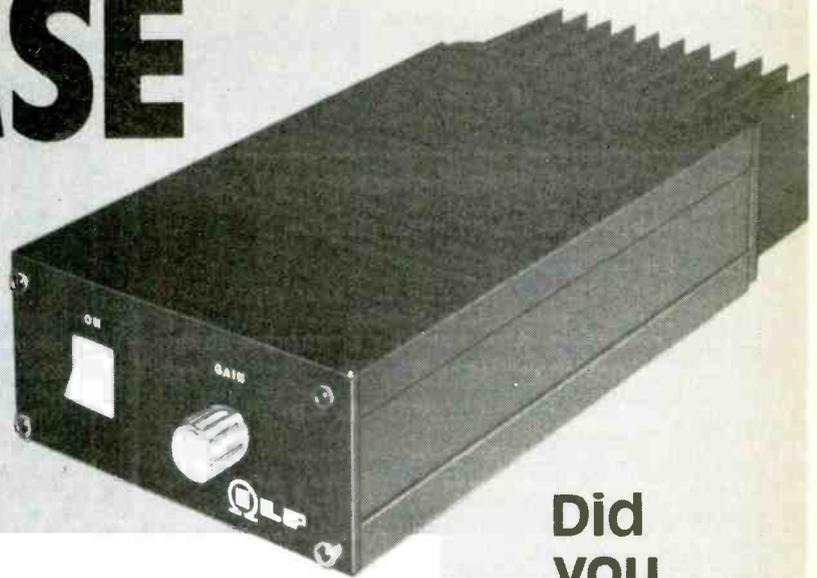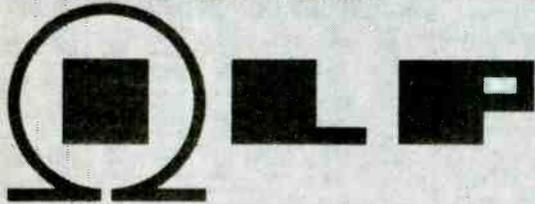

It's the chance every constructor wants



POWER AMPS



P.S.U.'s



PRE-AMP
MODULES

It's something you have always wanted... something to build your equipment into that's smart, modern, strong, adaptable to requirement and not expensive. The 'UniCase' is yet another triumph of I.L.P. design policy. It presents totally professional appearance and finish, ensuring easier and better assembly to make it equal to the most expensive cased equipment. The all-metal 'UniCase' is enhanced by precision aluminium extruded panels engineered for speedy and perfect aligned assembly within a mere five minutes. Designed in the first case to accommodate I.L.P. power amps with P.S.U.'s, the range will shortly be extended to house any other modular projects.

WHAT WE DO FOR CONSTRUCTORS

Our product range is now so vast we cannot possibly hope to show it all in our advertisements without overcrowding or abridging information to the point of uselessness. So we have devised a solution which we invite you to take advantage of without delay. ALL YOU NEED DO IS FILL IN AND FORWARD THE COUPON BELOW TO RECEIVE OUR NEWEST COMPREHENSIVE I.L.P. CATALOGUE POST FREE BY RETURN. It gives full details of all current I.L.P. products for the constructor together with prices, full technical and assembly details, wiring and circuit diagrams etc. and it's yours, FREE. You don't even have to stamp the envelope if you address it the way we tell you.



FREEPOST 5

GRAHAM BELL HOUSE, ROPER CLOSE, CANTERBURY CT2 7EP
Telephone Sales (0227) 54778 Technical Only (0227) 64723 Telex 965780

FREEPOST

Mark your envelope clearly FREEPOST 5 and post it WITHOUT a stamp to I.L.P. at address above. We pay postage when your letter reaches us.

Did you know

I.L.P. are the world's largest designers and manufacturers of hi-fi audio modules?

I.L.P. pioneered encapsulated power amps and pre-amps for enhanced thermal stability, mechanical protection and durability?

There are TWENTY power amplifiers from 15 to 240 watts RMS including the very latest super-quality Mosfets to choose from?

TWENTY pre-amp modules allow you to incorporate exciting professional applications to your equipment never before available to constructors and experimenters?

I.L.P. are suppliers to the B.B.C., I.B.A., N.A.S.A., British Aerospace, Marconi, Racal, Ferranti, G.E.C., Rolls Royce etc?

Goods are despatched within 7 days of your order reaching us and covered by our 5 year no-quibble guarantee?

**SEND COUPON
(NO STAMP NECESSARY)
FOR YOUR FREE
I.L.P. CATALOGUE
AND OPEN UP
TO A
NEW WORLD OF
QUALITY & VALUE**

To: I.L.P. ELECTRONICS LTD.
PLEASE SEND ME I.L.P. CATALOGUE,
POST PAID BY RETURN

Name: _____

Address: _____

I HAVE/HAVE NOT PREVIOUSLY
BUILT WITH I.L.P. MODULES

I.L.P. products are available also from Henry's, Marshall's, Technomatic & Watford

WW-089 FOR FURTHER DETAILS

METERS

Large range of types in stock; also probes, leads, accessories, etc.
PANEL MOUNTING in 50, 100, 500µA; 1, 5, 10, 50, 100 500mA; 1A either model.



MULTIMETERS

MINI NEW - 20KΩ/V; A.C./D.C./RES/Ω; i n 2/3 ranges; 130 x 88 x 37mm £11.20N

YN 300TR 20KΩ/V; AC/DC/R/Ω; dB/Transistor Test; LCD 3 1/2 digit (1999) Push button 28 ranges; 170 x 80 x 30mm £32.90N

DINNO (Dipswitch) LCD 3 1/2 digit (1999) Push button 28 ranges; 170 x 80 x 30mm £32.90N

SOLDERING IRONS

Also large stocks of bits, desoldering devices, accessories, etc.
ANTEX C-240V £4.80N; X-25-240V £5.30N; CSBP £5.46N; XSBP £5.56N; ST4 Stand £1.70N.
ORVX 50 watt temp. controlled £13.76N; Stand £4.00N.
SOLDER 500mA/18SWG £7.60N; Desolder braid 1.5m £4p.

SWITCHES

Wavechange Type CK - 1P/12 way; 2P/6W; 3P/4W; 4P/3W 48p.
MINI TOGGLES - S7101, SPDT 67p; S7201 DPDT 80p; S7301 3PDT £1.84; S7401 4PDT £2.75; 7211 1P3W £1.40; Centre off S7103 SPDT 71p; S7203 DPDT 80p.
 Push button min 8531 make/8533 break 62p; 8225 DPDT £1.34 - **DUAL IN LINE** ESD colour coded 0.3" x 0.11" format. On/Off single throw 2P SDS2 54p; 4P SDS4 95p; 6P SDS6 £1.36; 8P SDS8 £1.67; 10P SDS10 £2.10.
LOW COST D-L 4P DNSO4 80p; 8P DNSO8 £1.

PROFESSIONAL KEYBOARD FOR USE WITH ZX101 £31.30N
 Keyboard Case for above £13.40N

NICAD CHARGERS

For PP3 - NC75G £4.95N; for AA, C or D - NC1230 £8.20N; Power Units MW88 3/4/5/6/7/5/9/12V; 13A fitting 300mA out £3.45; HC244R DC Stabilised 3/6/7/5/9V 400mA out £8.25.

BOXES

High quality Black ABS plastic or diecast plain or stove grey.

L	W	D	ABS	PLAIN	STOVE GR
50	50	25	5001P 80p	5001P 120p	
100	80	25	5002P 80p	5002P 117p	5002 118p
113	83	31	5003P 180p	5003P 140p	5003 180p
121	86	40	5004P 115p	5004P 160p	5004 210p
152	82	50	5005P 134p	5005P 210p	5005 280p
182	113	81	5006P 210p	5006P 310p	5006 400p



VERO RANGE plastic boxes			B RANGE professional Instrument Cases		
L	W	D	L	W	D
72	47	25	21024	51p	134
120	50	35	21390	80p	224
180	110	55	21391	191p	302
					170
					84
					21095
					£7.20N
					£11.60N
					£14.80N

ELECTROVALUE

FOR SERVICE YOU CAN TRUST

VEROBOX CASES

to give a completely professional finish to a much valued project

ABS, light grey top; dark grey bottom + 2 anodised panels

L	D	H	TYPE	PRICE
205	140	40	21034	£4.82
205	140	75	21035	£5.64
205	140	110	21036	£6.46
180	120	39	21037	£4.11
180	120	65	21038	£4.40
180	120	90	21039	£4.69
155	85	39	21040	£3.31
155	85	60	21041	£3.61
155	85	80	21042	£4.30
125	65	30	21047	£2.36
125	65	39	21048	£2.99
125	65	50	21049	£3.37

ALL ITEMS BRAND NEW AND GUARANTEED TO SPEC.

CAPACITORS

POLYSTYRENE, SIEMENS 5% Tolerance. 160V
 5, 7, 10, 12, 15, 18, 22, 27, 33, 39pF 15p; 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820pF; 1n, 1n2, 1n5, 1n8, 2n, 2n7, 3n3, 3n9, 4n7 12p; 5n6, 6n8, 8n2, 10n 13p.

CERAMIC Very small. 1.8, 2.2, 2.7, etc. up to 1n 5p each. 1n5, 2n2, 3n3, 4n7, 6n8 5p; 10n, 22n 6p; 33n, 47n 7p; 100n 8p.

POLYESTER, SIEMENS LAYER-TYPE 7.5mm lead spacing 100V
 1n, 1n5, 2n2, 3n3, 4n7, 6n8, 8n2, 10n, 12n, 15n, 18n, 22n, 27n, 33n, 39n, 47n 7p; 56n, 68n 8p; 82n, 100n 8p; 120n, 150n, 11p; 180n, 220n, 12p; 270n, 330n, 390n, 470n 15p; 560n, 680n 24p; 100mm spacing 1µF 25p; 15mm spacing 2µ 36p; 22.5mm spacing 1µF 400V 50p; 3.3µF 100V 50p; In-depth stocks.

ELECTROLYTICS NON-polar (for LS X-overs) 50V peak 2µF 20p; 4µF 20p; 6, 8, 10, 15µF 32p; 25µF 37p; 40, 60µF 50p; 100µF 60p.

POLARISED, SIEMENS OR MULLARD FOR QUALITY EVERY TIME
 (µF/V) 10/40, 47/10 11p; 47/25 12p; 100/10 13p; 10/63, 22/40, 100/16 14p; 22/63, 47/40, 100/25, 100/40 15p; 220/10, 220/16 16p; 220/25 18p; 220/40 20p; 470/10, 470/16, 470/25, 100/10 19p; 470/40, 1000/16 27p; 1000/25 30p; 1000/40, 2200/16 44p; 1000/63 70p; 2200/40, 4700/16 77p.

PLUGGABLE SIEMENS single end
 1/63, 2.2/63, 4.7/63 10p; 10/63, 22/63 12p; 22/40, 47/16 10p; 47/40 12p; 47/63 15p; 100/16, 100/25 12p; 100/40 15p; 100/63 20p; 220/10 13p; 220/16, 220/25 13p; 470/6.3 15p; 470/10 16p; 470/16 18p; 470/25 22p; 470/40 25p; 1000/10 22p; 1000/16 24p.

LARGE CANS - SIEMENS
 2200/63 £1.77; 4700/40 £1.78; 4700/63 £2.96; 4700/100 £3.54; 10000/16 £1.93; 10000/25 £2.78; 22000/16 £3.20; 22000/25 £4.73.

TANTALUM
 0.1/35, 0.22/35, 0.47/35, 1/35, 2.2/16 13p; 2.2/35, 4.7/16 18p; 10/6.3 18p; 4.7/35, 10/16, 22/6.3, 10/25 18p; 22/16, 22/25, 33/10, 47/6.3, 100/3 30p.

LOW LEAKAGE All single end
 0.1/50, 0.22/50, 0.47/50, 4.7/35 10p; 1/50, 2.2/50, 4.7/50 12p; 10/16, 22/6, 10p; 10/35, 22/10, 22/16, 22/35, 47/6, 47/10 12p; 47/16, 100/6 12p.

DELIVERY BY RETURN ALL ITEMS EX STOCK

CATALOGUE £2, 70p POST FREE INC. 70p REFUND VOUCHER

RESISTORS

1/4, 1/2, 3/4 watt - all 2p each, 10 of one value 15p.
 2% Mullard metal film 5.1 ohms - 300K 5p each, 10 of one value 40p.
 5% wire wound 3W or 7W, most E12 values 1.2 ohms to 8K2 8p each, 10 for 77.

POTENTIOMETERS

CARBON ROTARY (P20) 100 ohms - 4M7 lin, 220 ohms - 2M2 log 32p or with switch - 87p; Dual gang (JP20) 4K7 - 2M2 lin, or log 95p or with switch £1.50.

SLIDERS 58mm, low cost 10K - 1M log only 22p; Std 58mm mono 4K7 - 1M lin or log 75p, stereo matched £1.20; Graduated bezels 34p.
PRESBET min. 10mm dia. Horizontal or vert. 100 ohms - 1M ea. 13p. Carmet 10mm dia. Horiz. or Vert. 100Ω - 1M ea. 22p. Carmet rectilinear type 80p; 100Ω - 1M ea. £1.08. PLESSEY MPW moulded carbon 470 - 2M2 ea. 59p.

DISCOUNTS ON ALL PRICES EXCEPT PRICES MARKED N

CMOS SUPER SAVERS!

4000	14p	4015	55p	4027	32p	4088	18p
4001	13p	4016	25p	4028	50p	4070	22p
4002	14p	4017	42p	4029	67p	4071	18p
4008	59p	4018	55p	4030	50p	4072	18p
4007	14p	4019	36p	4041	80p	4081	18p
4008	50p	4020	53p	4042	52p	4082	18p
4008	35p	4021	50p	4043	55p	4083	30p
4010	35p	4022	18p	4044	55p	4510	50p
4011	14p	4023	18p	4046	75p	4511	55p
4012	15p	4024	44p	4048	25p	4516	53p
4013	23p	4025	18p	4050	25p	4518	45p
4014	80p	4026	104p	4080	90p	4520	80p

Above prices are net



ACCEPTED BY MAIL OR TELEPHONE (to our Egham address)

GIRO A/C NO. 38/871/4002

- VAT - additional at 18% on all U.K. orders
 - FREE POSTAGE and packing on U.K. C.W.O. orders £5.75 inc. V.A.T. and upwards. Under add 40p inc. V.A.T.
 - DISCOUNTS on orders over £23.00 - 5% on orders over £57.50 - 10%
- Discounts do not apply to 'Net' items (shown by N after the price, or to orders paid for by credit card)
 Most items are available from stock and despatched promptly. Unforeseen delays are notified and customers instructions awaited


Headquarters for mail orders and shop

ELECTROVALUE LTD

28a St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB
 Telephone Egham (STD 0784); London 87 33803; Telex 254475
 Northern Branch (Personal shoppers only)
 680 Burnage, Manchester M19 1NA
 Computing at:
 700 Burnage Lane, Manchester (061-431 4866)

11000 PRINTER

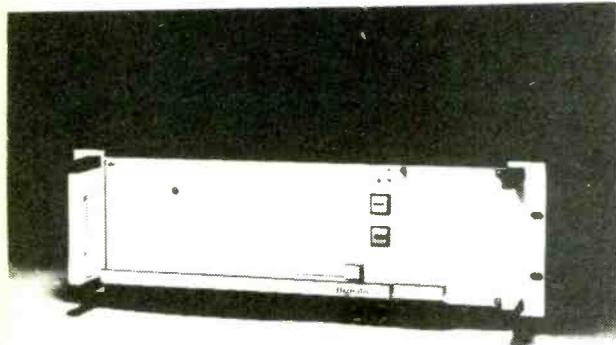A 19" rack mounted printer for industrial or laboratory data recording.



- 7 x 5 impact dot matrix.
- 32 characters on 3" plain paper.
- Red - Black printing on one line.
- Internal 4 year calendar clock option.

Available with RS232, IEEE488 & parallel BCD input options. Standard 96 character, alphanumeric character set. Foreign languages, including Arabic, Cyrillic & Greek also available.

Digitalis LTD

3 Reading rd.
 Lower Basildon
 Berks RG8 9NL
 049162 775

WW - 095 FOR FURTHER DETAILS

RADFORD

Audio Measuring Instruments, Audio Amplifiers, Loudspeakers and Loudspeaker Components for the professional and enthusiast

RADFORD AUDIO LTD.

10 BEACH ROAD
 WESTON-S-MARE, AVON BS23 2AU
 TEL. 0934 416033

WW - 058 FOR FURTHER DETAILS



ALL AT SPEED

TO BE CRYSTAL CLEAR

Tel. 029-34-5353 Telex 87116 Aero G

MOD approved

CAA approved

WW - 098 FOR FURTHER DETAILS

Appointments

Advertisements accepted up to 12 noon Wednesday, September 29th, for November issue, subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £15.50 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £3 per line, minimum £20 (prepayable).
BOX NUMBERS: £3 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS).
PHONE: IAN FAUX, 01-661 3033 (DIRECT LINE)

Cheques and Postal Orders payable to IPC Business Press Ltd.



ECM

ALWAYS AHEAD WITH THE BEST!
£5,000-£15,000

- ★ **Experienced in:** Mini/Microprocessor hardware or Software; Digital and Analogue circuitry; RF and Microwave techniques?
- ★ **Where does your interest lie:** Image processing; Automation; Datacomms; Radar; Nav-Aids; Video; Medical; Telemetry; Simulation; Satcom; Local Area Nets?
- ★ **There are opportunities in:** Design; Test; Service; Sales; Systems; Production; Quality and Research.
- ★ **First call:** Contact MIKE GERNAT on 076 384 676/7 (usually until 8 p.m.)

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED
 148-150 High St., Barkway, Royston, Herts SG8 8EG

(1750)

Electronic Engineers – What you want, where you want!

TJB Electrotechnical Personnel Services is a specialised appointments service for electrical and electronic engineers. We have clients throughout the UK who urgently need technical staff at all levels from Junior Technician to Senior Management. Vacancies exist in all branches of electronics and allied disciplines - right through from design to marketing - at salary levels from around £4000 to £12000 p.a.

If you wish to make the most of your qualifications and experience and move another rung or two up the ladder we will be pleased to help you.

All applications are treated in strict confidence and there is no danger of your present employer (or other companies you specify) being made aware of your application.

TJB ELECTROTECHNICAL PERSONNEL SERVICES,
 12 Mount Ephraim,
 Tunbridge Wells,
 Kent. TN4 8AS.

Tel: 0892 39388



Please send me a TJB Appointments Registration form:

Name

Address

(861)

BROMLEY HEALTH AUTHORITY

ELECTRONICS TECHNICIAN

(one of 3 - graded as Medical Physics III)

required for acceptance testing and routine maintenance of electriobiomedical equipment and other electronic equipment. Based in Orpington district

Salary scale £5,536-£7,155 plus £557 London Weighting p.a.

For further details telephone The Chief Electronics Technician on Orpington 27050 Ext 29

Write or telephone for job description and application form to District Personnel Officer

"Bassetts", Starts Hill Road

Farnborough, Kent

Telephone Farnborough 50254

Closing date:

29th September, 1982

(1792)

DIGITAL EXPERIENCE?

FIELD SUPPORT
 R & D AND SALES
 VACANCIES IN COMPUTERS
 NC, COMMS., MEDICAL
 VIDEO, ETC.

For free registration ring
 0453 883264
 01-290 0267

LOGEX

ELECTRONICS RECRUITMENT SERVICE
 LOGEX HOUSE, BURLEIGH, STROUD
 GLOUCESTERSHIRE GL5 2PW
 TEL 0453 883264, 01-290 0267

(321)

Test Engineers and Technicians - Wembley, Middlesex

Racal-BCC are members of the highly successful Racal Electronics Group and are world leaders in the design and manufacture of tactical radio communications equipment. We require a number of test technicians and test engineers to fill a variety of grades within the Test Department on both the day and night shift. The department is responsible for the manual and automatic testing and

fault finding of the Company's equipments at various stages of manufacture.

Applicants should be qualified to HNC/HTC level and have experience of radio communications equipment.

We offer excellent conditions of service including good basic pay and a Group Productivity scheme.



Please apply in writing to:
The Personnel Officer
Racal-BCC, South Way
Wembley, Middlesex

Racal-BCC

RACAL

World leaders in electronics

(1773)

CAREER OPPORTUNITY WITH TOP BRITISH MICRO MANUFACTURER

ELECTRONICS TECHNICIAN TO SUPPORT OUR DEVELOPMENT ENGINEERING TEAM

£5600 TO £8450, OXFORD-BASED

The Research Machines Basic Systems Group designs, develops and implements the hardware and systems software enhancements which have established the 380Z as one of the UK's top professional microcomputer systems.

We now have an opportunity for a qualified and enthusiastic electronics technician to join this important team and provide a comprehensive range of support services to it.

The job will include:

- assembly and test of prototypes
- installation and maintenance of equipment
- preparation of documentation
- control of stocks of components and consumables

- liaison with contractors

We are looking for candidates with HNC qualifications and one or two years practical experience — particularly in prototype wiring for circuit boards and digital electronics. It is likely that you will also have experience in one or more of: technical drawing; analogue systems; microprocessors; and/or prototype testing.

We offer a particularly attractive range of benefits, including good salary; 25 days paid holiday; free BUPA, life and disability insurance; pension scheme and help with relocation expenses.

If you are interested in this vacancy, please contact Pat Kember by phone or letter for an application form WW8

RESEARCH MACHINES MICROCOMPUTER SYSTEMS

RESEARCH MACHINES LTD Mill Street, Oxford OX2 0BW. Tel: (0865) 726136

APPOINTMENTS IN ELECTRONICS to £15,000

MICROPROCESSORS
COMPUTERS - MEDICAL
DATA COMMS - RADIO

Design, test, field and support engineers — for immediate action on salary and career advancement, please contact.

Technomark

Engineering and Technical Recruitment
11, Westbourne Grove
London W2. 01-229 9239 (1296)

VIDEO ENGINEER

We are looking for an engineer to service and maintain our specialist video products. Working on equipment up to broadcast level the applicant must be between 25 and 40, have a good understanding of electronics and possess a current driving licence. We offer enormous potential to the successful applicant. Salary negotiable depending upon experience.

Contact Fred Smith or Peter Rowsell, Polar Video Limited, 17-18 Brook Mews North, London W2 3BW. Telephone: 01-724 3736/3779.

(1786)

ROYAL OBSERVATORY, EDINBURGH

PROFESSIONAL AND TECHNOLOGY OFFICERS (2 POSTS)

There are two vacancies for Professional and Technology Officers at the Royal Observatory, Edinburgh which is an establishment of the Science and Engineering Research Council. Both vacancies are in the Technology Unit which provides engineering support to the three national facilities for which the Royal Observatory is responsible – the UK Infrared Telescope Unit, the UK Schmidt Telescope Unit and the Image and Data Processing Unit – and also to in-house research programmes.

PROFESSIONAL AND TECHNOLOGY OFFICER GRADE II – £6868 to £9241 pa

This vacancy is in a small team of engineers and scientists currently working on infrared techniques in the 1-5 μ m and 7-13 μ m bands on applying these techniques to the design and development of astronomical instruments such as photometers and spectrometers for use on the 3.8m UK Infrared Telescope in Hawaii.

DUTIES

The successful applicant will be responsible to the team leader, a PTO I, and will work closely with a project astronomer, who is a physicist, and will be required to:

1. Assist in the evaluation of infrared detectors, both single elements and arrays to determine their performance and optimum operating conditions using the necessary electronic and cryogenic apparatus.
2. Develop low noise preamplifiers for use with the above detectors under low infrared radiation levels.
3. Develop suitable thermal and mechanical mounting and packaging methods for detector preamplifier combinations for use in instruments.
4. Assist in the design, development, test and commissioning of such instruments both in respect of the above detector/preamplifier packages and also the associated optics, mechanics and cryostats.

The successful candidate may also be required to work abroad on short term detached duty or on postings of up to three years. It is a prerequisite of working in Hawaii that a special high altitude medical examination be taken and passed.

QUALIFICATION AND EXPERIENCE

Applicants are expected to have a degree or equivalent in an appropriate subject such as Electronic Engineering, Applied Physics or Physics leading to corporate membership of the appropriate professional body.

Recent experience of the theory and practice in any of the following would be an advantage: Low light level imaging systems, especially at infrared wavelengths, cryogenics, low noise, low-level analogue signal amplifiers, optics design.

Applicants are expected to be able to programme in a high level language such as FORTRAN, or be prepared to acquire such ability, as the instruments are controlled by means of minicomputers.

Applicants are expected to be skilled in the use of a wide variety of laboratory instruments and must possess manual skills appropriate to assembly and disassembly of small electromechanical devices and to the handling of cryofluids. Applicants must have good eyesight (with glasses if worn).

PROFESSIONAL AND TECHNOLOGY OFFICER GRADE III – £6868 to £7876 pa

This vacancy is in the Laboratory Workshop which is currently working on a variety of devices for the measuring of photographic plates and on instruments for use on telescopes at visual and infrared wavelengths.

DUTIES

1. Supervise the electronic and wiring activities of the Laboratory Workshop.
2. Organise and maintain the electronic instrument, tool, component and wire stores of the Technology Unit.
3. Be directly involved with Technology Unit Scientific and Technical staff in the instruction, development, testing and maintenance of instrumentation and equipment associated with the national facilities, in-house research and the work programmes of the Technology Unit. Preparation of drawings may form a part of these duties and training will be provided as required.
4. Deputise in the general Laboratory Workshop supervision as and when required.

QUALIFICATIONS AND EXPERIENCE

Applicants must have an ONC/SCOTEC or equivalent and should have served a recognised apprenticeship in electronic engineering. Experience in light electrical or electronic wiring and assembly is essential and knowledge of the mechanical assembly and test of complex instruments would be an advantage.

Application forms for both posts are available from the Personnel Officer, Royal Observatory, Blackford Hill, Edinburgh EH9 3HJ, and should be returned by 1 October 1982.

Appointments

Telecommunications Officers

Up to £9270

The posts available are varied, but broadly they fall into 2 groups at 5 different locations.

Hanslope Park (Milton Keynes), North Bucks and Central London

Work associated with HF communications equipment, VHF, UHF and microwave links and associated test equipment; teleprinters, telephone subscribers' apparatus, PMBXs, PAXs, PABXs and ancillary equipment including that using analogue and digital techniques and voice frequency telegraph.

Crowborough, Sussex and Orfordness, Suffolk

The maintenance and operation of high power, medium and short wave broadcasting transmitters and associated equipments.

Candidates must have had appropriate training. They should normally have 4 years' relevant experience, and hold either ONC in Engineering (with pass in Electrical Engineering 'A') or ONC in Applied Physics or TEC/SCOTEC certificate or City & Guilds Telecommunications Technicians Certificate Part II (Course No 271), or Part I plus 3 'B' subjects or a pass in the Council of Engineering Institutions Part I examination or an equivalent or higher relevant qualification. Ex-Service personnel who have had suitable training and at least 3 years' appropriate service (as Staff Sergeant or equivalent) will also be considered.

Salary: £5980-£8180; London £1087 more. Starting salary may be above minimum for those with additional relevant experience. Promotion prospects.

Relocation assistance may be available

For further information and an application form (to be returned by 7th October 1982) write to Civil Service Commission, Alencon Link, Basingstoke, Hants, RG21 1JB, or telephone Basingstoke (0256) 68551 (answering service operates outside office hours). Please quote ref: T/5782.

Foreign and Commonwealth Office

(1764)

ELECTRONICS ENGINEER

We have a world wide reputation in the design and manufacture of automatic handling equipment for the production of hybrid circuits.

We require a Technician/Electronics Engineer to join our design team. The applicant should have experience of simple Digital Control Circuits and some analogue circuitry work, and will be joining a team that is responsible for the design, development and testing of these automatic systems.

The applicant should have had several years experience in the above field and will be in possession of ONC or similar as an absolute minimum qualification.

Salary is negotiable but will reflect the seniority of the position. Applicants should write, enclosing full C.V. to:

(1772)

H. E. IRWIN
PRODUCTION DIRECTOR

DEK DEK Printing Machines Ltd.
22 Albany Road
Granby Industrial Estate
WEYMOUTH
Dorset DT4 9TH
Please mark the envelope HEI. 100

Share in the Sony Broadcast Success Story

One of the world leaders in professional broadcast television equipment and systems, we are currently undergoing a significant planned expansion programme. A number of excellent career opportunities now exist and applications are invited for the following positions:

Systems Project Engineer

To join a young and enthusiastic team involved in the design, manufacture and commissioning of complex static and mobile television systems. Candidates for this challenging and responsible position should have direct experience of sound and television principles gained in operational television or its allied manufacturing industry.

Proposals Engineer

Ideal for engineers experienced in the Broadcast TV industry who now wish to utilize their knowledge in a dynamic commercial environment. Duties will include the preparation of detailed and concise customer proposals, complete with pricing information and extensive customer and inter Company liaison will be necessary.

Field Service Engineer

To be engaged in the service and repair of a wide range of sophisticated equipment, including video cameras, VTR's and editing control systems. A high level of self motivation and initiative is required in order to successfully undertake customer visits throughout Europe, Africa and the Middle East.

Sales Engineer (UK)

An engineer with experience in operational television or its allied manufacturing industry is required to join our UK sales team. Applicants should be aged 25-35, highly motivated and able to work on their own initiative. Previous sales experience would be advantageous although this is not essential.

Commissioning/QA Support Engineer

To join a small team responsible for the evaluation of product performance. Key activities will include commissioning, assistance in product customisation and the establishment and maintenance of ATE.

Lecturer

To conduct theoretical and practical training courses on our major products. Applicants should have experience of professional broadcast television equipment and possess the ability to present ideas clearly.

If you like the thought of enjoying the success of world leadership together with a highly attractive salary and benefits package, write with details of career to date, and present salary to: Mike Jones, Senior Personnel Officer, Sony Broadcast Ltd, City Wall House, Basing View, Basingstoke, Hants RG21 2LA. Telephone (0256) 55011

SONY Broadcast 
Sony Broadcast Ltd.
City Wall House
Basing View, Basingstoke
Hampshire RG21 2LA
United Kingdom
Telephone: (0256) 55 0 11

(1787)



CAPITAL
APPOINTMENTS LTD

THE UK's No. 1 ELECTRONICS AGENCY

Design, Development and Test to £14,000
Ask for Brian Cornwell

SALES to £15,000 plus car
Ask for Maurice Wayne

FIELD SERVICE to £12,000 plus car
Ask for Paul Wallis

We have vacancies in ALL AREAS of the U.K.


Ask for a Free Jobs List

Telephone: 01-637 5551 (3 lines)

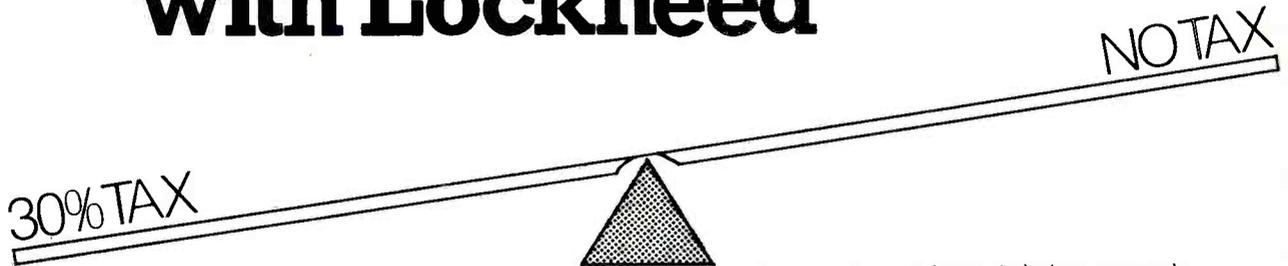(291)

Radio/Radio Relay Techs - 2-year training assignments in Saudi

On balance, you'd be better off with Lockheed



When you compare an electronics technician's job in the UK with working for Lockheed in Saudi Arabia, there's no contest.

Because with Lockheed, you win on just about every count. You won't pay any tax at all for the two years you're with us. And you'll earn over £20,000 during that time.

To help you turn earnings into savings, we give you for free all the things some of the others make you pay for — free bachelor accommodation, food and laundry; free return flights to the UK for your three leave periods a year; medical and life insurance.

But when you're tackling an important job like training Royal Saudi Air Force personnel to maintain the Kingdom's air

defence system, we figure it's the least we can do.

For a Radio Tech's job to be yours, you need a C&G or forces equivalent and at least seven years experience in HF (SSB), VHF/UHF and SHF equipment, and for Radio Relay you'll also need multiplex and tropo experience.

On balance it's not much to ask when we've so much to offer, and what's more we give you free equipment familiarisation courses before you go.

Contact The Senior Recruitment Executive (Lockheed), IAL, Personnel Consultancy, Aeradio House, Hayes Road, Southall, Middlesex UB2 5NJ. Tel: 01-574 5000. Please quote ref L130.



Television International

Television International has made some additions... a new Super Tempo 5 computer-controlled editing suite; a Rank Cintel MK IIC Telecine mastering suite, and a new lightweight Outside Broadcast vehicle to name but three! As a result, we require additional staff for the following areas:

TELECINE OPERATIONS

Two experienced engineers required — a knowledge of TOPSY and Digiscan would be an advantage.

VIDEO TAPE OPERATIONS

Engineers are required with experience of 1" C-format and 2" Quad machines, to work in Base and on Outside Broadcasts.

Staff in these areas will be required to liaise directly with clients.

MAINTENANCE

An experienced engineer is required who is capable of looking after all of this and carrying out standard Base maintenance.

Salaries and conditions will be in accordance with the ACTT grades plus local supplements but will reflect the responsibilities involved. The Company benefits from an attractive contributory Group Pension Scheme, which includes free Life Assurance. Training will be provided where necessary to keep staff abreast of current developments within the industry.

For an application form, please write to the address below quoting Ref. LJC/WW.

Lindy Campbell
Television International Operations Limited,
9-11 Windmill Street,
London W1P 1HF.
Tel: 01-637 2477.

A Subsidiary of RANK PHICOM VIDEO GROUP LTD

(1766)

HINCKLEY POWER CONSULTANTS LTD.

149 Church Street, Burbage, Hinckley
Leicestershire, LE10 2DB

A firm of international consulting engineers engaged on various exciting broadcasting and communications projects in Nigeria require keen, competent engineers to fill the following overseas appointments.

Field Contract Controller

to oversee contract implementation from equipment delivery to customer acceptance, including provision of services and technical support to field engineers. Must have comms./broadcast experience, preferably in an overseas environment.

Installation and Commissioning Engineers

Qualified and experienced in one or more of the following fields:

- VHF, UHF Television transmitters and studio equipment
- Microwave and UHF radio links
- Diesel generators and associated electrical plant
- Erection of masts, towers, antennas and feeders

Good salaries paid commensurate with experience

Apply with c.v. to Martin Rhodes, Project Manager, or telephone for more information on Hinckley 611461.

(1784)

Appointments

Engineers & Scientists

£9,126

Communications R&D...
...the leading edge

At HM Government Communications Centre, we're applying the very latest ideas on electronics and other technologies to the problems of sophisticated communications systems, designed to enable and protect the flow of essential information.

The work is of the highest technical challenge, offering full and worthwhile careers to men and women of high ability, on projects covering the following areas of interest:—

RADIO - from HF to microwave, including advanced modulation systems, propagation studies, applications of Microcircuitry.

MAGNETICS **SIGNAL ANALYSIS**
SYSTEMS ENGINEERING

Applicants, under 30 years of age, should have a good honours degree or equivalent qualification in a relevant subject, but candidates about to graduate may also apply.

Appointments are as Higher Scientific Officer (£6,840-£9,126) or Scientific Officer (£5,422-£7,399) according to qualifications and experience. Promotion prospects.

For an application form, please write to the Recruitment Officer, (Dept. W/W10), HM Government Communications Centre, Hanslope Park, Milton Keynes, MK19 7BH.

Electronic Wireman/Woman

We have a vacancy at our Glasgow studios in our installation and maintenance section for a man or woman with extensive experience in electronic wiring.

Applicants must be familiar with all types of audio and video cables and connectors and be able to work from cable schedules with minimal supervision.

A high standard of practical ability and neatness is essential and candidates invited to interview will be expected to undertake a short practical test working from drawings supplied.

Interviews will be held in Glasgow and travelling expenses will be refunded.

The company offers excellent staff conditions of employment including a contributory pension scheme with free life assurance. The starting salary is at present £6,695 per annum rising by five annual increments to £9,478 per annum but this scale is currently under annual review.

Those with the necessary experience should write giving age and brief details of experience to the Recruitment and Training Officer. (1782)



Scottish Television
Cowcaddens, Glasgow G2 3PR.

HOLIDAY OVER? REFRESHED READY FOR A NEW JOB? TRY THESE DESIGN DEVELOPMENT ENGINEERS

For lighting, heating and ventilating control systems, each one to be negotiated and designed to the requirements of a specific client. Must have experience of Z80 (and other microprocessors could be called for) and analogue switching. Salary up to £9,500 p.a. in Avon.

SENIOR ENGINEERS

Hardware or software to design TV and video products, such as digital standards converters, the hardware being PDP11 and also 16-bit microprocessors, the software Pascal, Fortran and Assembler under RSX11M operating system. Must have degree and video experience. Salary up to £10,500 p.a. in West Berks.

ALL-ROUND ENGINEER

Capable of evaluating linear LSI chip circuits. Must be graduate, preferably with hands-on experience of a test system such as the LTX MTS-77 and I-C applications. Salary rewarding, in Liverpool.

PRINCIPAL AND DESIGN ENGINEERS

For all new infra-red imaging systems under CMOS and logic control, with also analog displays. Must be graduates with both digital and analog experience. Salary up to £11,000 p.a., in West Essex.

Charles Airey Associates

Tempo House, 15 Falcon Road, Battersea, London SW11 2PJ
Tel: 01-223 7662 or 228 6294

(1357)

GO WHERE SERVICE COUNTS...

Cambs. based

To £7,400 + bonus + car

High technology company manufacturing scientific instruments seeks ONC/HNC qualified electronics engineers. Min. 2 years' experience of servicing to component level and knowledge of computer systems. U.K. and some overseas assignments.

Phone Royston (0763) 60602 till 9 p.m.

Susan Hyde - Staff Consultant

(1779)

SERVICE & INSTALLATION ENGINEERS

London & Home Counties Area

British subsidiary of French X-Ray Company requires service and installation engineers to work on modern X-ray equipment in National Health Hospitals.

The work involves an unusual blend of high-voltage plus analogue and digital technologies. Successful candidates will be qualified to BSc or HND level, be practically minded and have the initiative to cope with problem solving in the field.

Company car provided, salary negotiable, expenses paid.

Please write, enclosing CV or telephone for interview to M W Ridgeon, Asst. Service Manager, 01-890 8166.

CGR Medical Limited

Astronaut House, Hounslow Road
Feltham, Middx.



SITUATIONS VACANT

Technicians in Communications

GCHQ We are the Government Communications Headquarters, based at Cheltenham. Our interest is R & D in all types of modern radio communications - HF to satellite - and their security.

THE JOB All aspects of technician support to an unparalleled range of communications equipment, much of it at the forefront of current technology.

LOCATION Sites at Cheltenham in the very attractive Cotswolds and elsewhere in the UK; opportunities for service abroad.

PAY Competitive rates, reviewed regularly. Relevant experience may count towards increased starting pay. Promotion prospects.

TRAINING We encourage you to acquire new skills and experience.

QUALIFICATIONS You should have a TEC Certificate in Telecommunications, or acceptable equivalent, plus practical experience.

HOW TO APPLY For full details on this and information on our special scheme for those lacking practical experience, write now to

Recruitment Office
GCHQ, Oakley, Priors Road, Cheltenham
Glos. GL52 5AJ
or ring
0242 21491
ext 2269

(1530)



Radio Technician

We are an internationally successful manufacturer of mining machinery and explosion proof electrical equipment. At our Kirkintilloch site we are setting up a new Electronics Unit in which there is a vacancy for a Radio Technician to undertake special assembly operations on r.f. equipment and be responsible for performing full production tests on radio control systems.

The successful candidate will have extensive experience in the servicing and testing of VHF and UHF, P.R. equipment preferably gained in a manufacturing environment. A working knowledge of analogue and digital encoding and decoding circuits would be an advantage.

An attractive salary is offered for this position along with terms and conditions of employment to best modern standards.

Please write giving full details of age, experience and qualifications to:

Mr A. M. SMITH,
GROUP PERSONNEL
ADMINISTRATION
MANAGER

(778)

Anderson
Strathclyde PLC

47 Broad Street, Glasgow G40 2QW

SULTANATE OF OMAN, ROYAL OMAN POLICE

TELECOMMUNICATIONS TECHNICIAN

The Royal Oman Police are seeking persons for appointment as Telecommunication Technician. Applicants should be suitably qualified with at least 12 years' experience in the following subjects:

- (A) HF, VHF, UHF Fixed/Mobile Equip.
- (B) Teleprinters (Electronic)
- (C) Microwave/Multiplex Equip.
- (D) Marine Radar

Applicants should possess at least City & Guilds intermediate or equivalent. Previous Police/Military experience and a knowledge of Arabic would be an advantage, but is not essential.

GENERAL

This appointment is offered in the Uniform Rank of Superintendent Grade II on contract terms of service for an initial period of 2 years. Conditions of service include annual emoluments of the equivalent of R.O. 7980.000 (£13,017) at current rate of exchange) and normal benefits which are associated with working overseas including furnished air-conditioned accommodation, Medical Treatment, 60 days leave per annum with paid passages, plus an end-of-contract benefit equal to 25% of basic salary.

Applications with detailed curriculum vitae attached to be forwarded to:

Inspector General of Police and Customs
Attn: Assistant Commissioner of Police
(Personnel & Training)
Royal Oman Police, P.O. Box No. 2
Muscat
Sultanate of Oman

(1794)

£25,000?

1. DEVELOPMENT ENGINEERS

Des. Dev. of AM, FM and TV Broadcast transmitters. Circa 12K. Essex.

2. PROJECT LEADER

To lead team engaged on microwave project, VHF and UHF techniques, receivers and synthesizers. Circa 14K. Herts.

3. RF DESIGN ENGINEERS

RF Circuit designers to work in small design group involved in microprocessor based signal source development. Circa 10K. Herts.

4. MICROWAVE SPECIALIST

For commercial and military systems. Circa 12K. Berks.

5.

SENIOR DESIGN ENGINEER

To lead team in the design and development of RF and microwave equipment. Circa 11½K. Beds.

6. DEVELOPMENT ENGINEERS

Des. Dev. of microwave line-of-sight, tropospheric scatter and satellite communication systems. Circa 12K. Essex. 100s of other electronic and computer vacancies to £25,000.

Phone or write: Roger Howard
 C.Eng., M.I.E., R.E., M.I.E.E.

CLIVEDEN CONSULTANTS

87 St. Leonard's Road Windsor, Berks.
 Windsor (07535) 57818/58022
 24-hour service (1640)

CLIVEDEN

R & D OPPORTUNITIES. Senior level vacancies for Communications Hardware and Software Engineers, based in West Sussex. Competitive salaries offered. Please ring David Bird at Redifusion Radio Systems on 01-874 7281. (1152)

ARTICLES FOR SALE

INVERTERS

High quality DC-AC. Also "no break" (2ms) static switch, 19" rack. Auto Charger.



COMPUTER POWER SYSTEMS
Interport Mains-Store Ltd.
POB 51, London W11 3BZ
Tel: 01-727 7042 or 0225 310916

(9101)

MEGA GOLD PLATING UNIT. Type PLAU Z5. Accepts up to 12" double-sided boards. Sold complete with 250ml gold solution, accessories and instructions. Unused. £120 ono. Tel. 0592 202729. (1789)

TEST EQUIPMENT. Gould Advance 10MHz dual trace scope. Alpha 2 D.M.M. Farnell L30-1 bench power supply and LF1 audio oscillator. Almost immaculate! Old scope and some bench tools included. £280 (+ VAT). ALSO goodwill small repairs workshop in Leeds. Offers invited. Phone (0532) 793614. (1791)

LITTON 1231 BUSINESS COMPUTER-WITH PRINTER. Perfect working order. £300. 661 3039 or 515 0013. (1775)

TELETEXT (ORACLE/CEEFAX) add-on adaptors for your existing television. Only £149.95 inclusive. Also Viewdata (Prestel) adaptors and fantastic colour graphics microcomputer interface. Trade enquiries welcome. Access/Visa. Avon Office Services (WW), FREEPOST, Bristol BS10 6BR. (0272) 502008 anytime. (1767)

SITUATIONS WANTED

RADIO TELEGRAPHIST seeks position. Leaving Army shortly after 15 years service Royal Signals. Experienced in HF and VHF systems. Morse and teleprinter. City and Guilds communication operators. Certificate and RAE held. Anything considered. Box 1770.

ARTICLES FOR SALE

EXIDY SURPLUS SALE

We have thousands of these parts for 1/2 PRICE & UNDER
NO REASONABLE OFFER REFUSED
ALL ITEMS BRAND NEW

74LS04	74LS157	3130 OP AMP
74LS05	74LS373	6850 ACIA
74LS32	74LS373	6502 Processor
74LS10	74LS365	4027 RAM
7805 1 AMP 5V REG		
LSI Breakout TV Game Chip		
PCB for Breakout TV Game		
4700 MFD 10V	1K Resistors 1/2W	

Sockets: 40 PIN, 24 PIN, 20 PIN, 16 PIN, 14 PIN
Joystick Plastic Holders (Over 1,000 sets)
Transformers for Commodore Pet: 8:0-8 5AMP, 16V 1 AMP, 22V 1 AMP, 240V Primary
Telephone Answering Machines - All faulty

TEL: 01-440 7033 (1696)

POWER V MOS-FET TECHNOLOGY

We specialise in all aspects of this important subject. A comprehensive service is offered to individual or OEM users, including:

- ★ Hitachi Supertex and RCA V MOS-FET from stock.
- ★ V MOS-FET power modules from stock.
- ★ Competitive prices (120 watt modules £15.45, 1 off).
- ★ Printed circuits and kits.
- ★ Data books and application notes.
- ★ Design, evaluation and advice service.
- ★ Catalogue/sample data sent free (50p stamp appreciated towards post and packing).

Phone 02514 22303 and ask Richard Walsh about your application requirement or write:

AUDIO TECHNOLOGY
Freeport, Church Crookham
Aldershot, Hants. GU13 0BR

TS 32

CTCSS
Programmable
microminiature
encoder/decoder
1.25in. x 2in. x 0.4in.

No counter or other test equipment required to set frequency.

CAR LINK COMMUNICATIONS LTD.
29e Parham Drive
Eastleigh, Hants.
Tel: 0703 619834 (1765)

TELERADIO

For low cost instruments. Freq meters, audio & RF generators. Distortion analysers, etc. Assembled & kits. Illustrated lists sent on request.

325 Fore Street, Edmonton
London N9 0PE
Tel: 01-807 3719 (1762)

WORLD'S BIGGEST INFORMATION SERVICE

By return post - service/workshop manuals. Over 2,000 Sony - over 300 different CTV plus huge stocks VCR/TV/Audio/foreign and UK.
Any single service sheet £1 + s.p. Repair data named TV £8.50 (with circ. £8.50). SAE brings free - 50p magazine/price lists/bargain offers/quotations - unique TV publications.
TISWW, 76 Church Street, Larkhall (0638 033334), Lanarkshire ML9 1HE. (1637)

TO MANUFACTURERS, WHOLESALERS BULK BUYERS, ETC. LARGE QUANTITIES OF RADIO, TV AND ELECTRONIC COMPONENTS FOR DISPOSAL

SEMICONDUCTORS, all types, INTEGRATED CIRCUITS, TRANSISTORS, DIODES, RECTIFIERS, THYRISTORS, etc. RESISTORS, C/F, M/F, W/W, etc. CAPACITORS, SILVER MICA, POLYSTYRENE, C280, C296, DISC CERAMICS, PLATE CERAMICS, etc.
ELECTROLYTIC CONDENSERS, SPEAKERS, CONNECTING WIRE, CABLES, SCREENED WIRE, SCREWS, NUTS, CHOKES, TRANSFORMERS, etc.

ALL AT KNOCKOUT PRICES - Come and pay us a visit ALADDIN'S CAVE


TELEPHONE: 445 0749/445 2713

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, North Finchley, London, N.12

(5 minutes from Tally Ho Corner)

(1613)

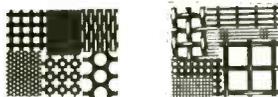

Perforated Metals - Screens, Plastics, Wire Meshes, Sifting Media, Cable Tray, Gratings, direct from Manufacturer's Stock. We can cut to size.

We specialise in one-offs or large quantities.

GRAEPEL PERFORATORS LTD.

Unit 1-B, Charles Street, Dept. WS, Walsall, Staffs WS2 9LZ. Tel. 0922 611644/611414. Telex 335291.

Printer PSL Stand PSS

★ Handsomely crafted in 8mm tinted Perspex

★ PSS model for Microline 80/82/83, Epson MX-80, Shinko GP 100, etc. £15.95 + VAT
★ PSL for Microline 84, Epson MX82, etc. £17.95 + VAT

APPLE PADDLE

★ Cable connector to Apple slot with 12" colour coded cables for proto boards, external units, etc. £5.95 inc.

CAMBRIDGE MICROELECTRONICS LTD.
One Milton Road, Cambridge CB4 1UY
Tel: 0223 314 014 (1785)

80 x 24 VDU

All the electronics for a 24 lines by 80 characters visual display unit on one assembled and tested printed circuit board measuring 8.75 inch x 6.50 inch.

You provide: power supply +5v at 1.2 amps +12v/-12v at 25mA, ASC11 encoded keyboard, video monitor.

The VDU-1 will talk to the R.S.232 serial port on your computer, at up to 19,200 Baud 56 features including cursor (X, Y) addressing.

VDU-1 Assembled and tested PCB £135
PSU-1 VDU-1 power supply £32
All prices subject to £2.50 registered delivery, plus VAT.

SIRIUS CYBERNETICS

Comyn Lodge, 66 Holly Walk
Leamington Spa, Warwickshire
Tel. (0928) 316110 (1645)

OSCILLOSCOPE. Hewlett Packard 181A storage mainframe, plug ins, 1801A dual trace 50 MHz vert. amp. 1812A delayed sweep time base. 1601A logic analyser. Offers invited. Ring Mr Chiswell 061-678 0229 (day). (1793)

PRINTED CIRCUITS. Make your own simply, cheaply and quickly. Golden Fotolak Light Sensitive Lacquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibreglass Board approx. 1mm thick £1.75 sq. ft. Post/Packing 60p. White House Electronics, Castles Drive, Praa Sands, Penzance, Cornwall. (714)

SIGNAL GENERATOR. Marconi TF144H/5 10KHz to 72MHz calibrated and resprayed by Marconi in last month. As new condition with manual. £300. Ring Allan Laner 0925 572332 for further information. (1790)

Calcomp Head Alignment Meter £45
Sweep Generators, 4-900MHz, £40-£135.
New Xuron Tools Set, £55. Avo 8 Mk. 5, £69. 24-channel UV Recorder, £75. Pneumatic Shears - fast trimming assembled PCB Boards, etc., £25. Contaflex SLR (Sinusoidal shutter), ideal video, TV stills, £49. Oxygen Analyser, £59. Decade Box (mhos), Sullivan Standard Cap, £25; another, £35. Fenlow SA4 Spectrum Analyser, £98. Phase meter, £65. 30KV EHT Meter, £29. Marconi TF 2600, £65. TF 1064, £75. Various RF, AF sig-gens. HP clip-on DC Millimeter, £65. Tektronix Transistor Curve Tracer, £95. Centrifuge, £49. EEL Universal Densimeter, £25. Headphones, stereo, mono, binocular, suit school, etc., £4.50 ea. Laser, £49. Melting Point Apparatus, £25. Cryogenic (refrigeration) Tester, £25. Watson Microscope, £89.

040-376 236

(1771)

THE SCIENTIFIC WIRE COMPANY

P.O. Box 30, London, E.4

SWG	ENAMELLED COPPER WIRE			
	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	.80	.50
30 to 34	3.20	1.80	.90	.70
35 to 40	3.40	2.00	1.10	.80
41 to 43	4.75	2.60	2.00	1.42
47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 30	6.50	3.75	2.20	1.40
----------	------	------	------	------

TINNED COPPER WIRE

14 to 30	3.38	2.36	1.34	.90
----------	------	------	------	-----

Prices include P&P. VAT and Wire Data SAE for list. Dealer enquiries welcome.

Reg Office: 22 Coningsby Gardens. (9063)

NEWBURY 7004/5 LDG. RS232/Current Loop printer, port complete with data and power cables plus terminators. Page/scroll mode, edit, line, page transmission, as new. List price £895. Our price £399 only plus VAT. Many other screens, printers and complete systems available. S.U.S. Sydney Road, Birmingham OLI. 771 3888. (1774)

STYLI ALL TYPES supplied, send SAE for price list. Watts Radio, 8 The Apple Market, Kingston, Surrey. (1709)

RK05 COMPATIBLE 2.5Mb hard disc (DRI model 33F) and Q-bus controller for DEC LSI11, including 3 disc packs. £880. Tel. Cambridge (0223) 312923. (1777)

PRINTED CIRCUIT BOARDS manufactured from artwork or films. Small or large quantities. Average turnaround two weeks. Also pre-coated positive resist boards. Sizes to order. Mayland PCB Company Ltd, 4 The Drive, Maylandsea, Chelmsford, Essex CM3 6AB. (0621) 741 560. (1763)

QUANTITY COMPONENTS! Tants .1/35V, .33/35V, 1/35V £85/1,000. Minidiscs, 1000/500V, .01/500V, .02/50V £14.50/1,000. Polystyrenes, axial 56/350V, radial 220/160V £14.50/1,000. P&P £1.50. Add VAT 15%. Also valves, speakers, etc. SAE enquiries, callers welcome. Letchworth Electronic Components, Spirella Leitchworth, Bridge Road, Letchworth, Herts. SG6 4ET. Tel. (04626) 70354. (1771)

RTTY/CW DECODER. Computerised with alphanumeric LED display or ASCII output. 5-30 w.p.m. and 45.50 baud. In world-wide use. Kits from £39.50. Construction data £2.95 (refundable). S.A.E. enquiries. MacRitchie Micros, 100 Drakes Avenue, Inverness. (1769)

RACAL COMMUNICATIONS RECEIVERS

500 Kc/s - 30Mc/s 1MHz wide. RA17L - £175. RA117E - £225. A few sets available as new at £75 extra. All receivers are air tested and calibrated in our workshop, supplied with full manual, dust cover, in fair used condition. New black metal louvered cases for above sets £25 each. RA900 - ISB - SSB - £75. RA218 - SSB - ISB and fine tune for RA117 - £50. TRANSMITTER DRIVE UNIT RA79. 1.5mc/s - 30mc/s - SSB - ISB - OSB - FSM - CW - £150. AERIAL TUNING UNIT and protection unit MA197B - £25 to £50. DECADE FREQUENCY GENERATOR MA2508. Solid state synthesiser for MA79 or RA117 - RA217 - RA1217 - £150 to £200. MA259G - 1.6mc/s to 31.6mc/s - £150 (New). MA259G - precision frequency standard - 5mc/s lmc/s 100khz - £100 to £250. RACAL MA152 - Standing wave ratio indicator. FX2mc/s - 25mc/s Power up to 1000watts - 50 ohms - Auto trip switch - Transistor mains 100 - 250AC, new and boxed - £40. RACAL COUNTER 836 (9636) 32mc/s TTL circuit design - tested with manual - £50 to £75. OSCILLOSCOPES COSSOR COU150 - 35mc/s - Twin Beam - Solid State - £175 with manual. TEXTRONIC OSCILLOSCOPE 647 and 647A Solid State - 50mc/s and 100mc/s bandwidth - £250 and £350. Tested, circuit and instructions. RACAL counter 801 M-125 Mc-S £50.

IMAGE INTENSIFIER ASSEMBLY - XX 1000 (Mullard). Very high-gain self-focusing image intensifier for night vision systems. Minimum luminance gain 35,000. £12 (used).

All items are bought direct from H.M. Government, being surplus equipment. Price is ex-works. SAE for all enquiries. Phone for appointment for demonstration of any item. John's Radio, Whitehall Works, 84 Whitehall Road East, Birkenhead, Bradford BD11 2ER. Tel. (0274) 684007. V.A.T. and Carriage extra. (848)

BRIDGES, waveform/transistor analysers. Calibrators, Standards. Millivoltmeters. Dynamometers. KW meters. Oscilloscopes. Recorders. Signal generators - sweep, low distortion, true RMS, audio, FM, deviation. Tel. 040 376236. (1627)

ENCAPSULATING EQUIPMENT FOR coils, transformers, components, degassing silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment, low cost, used and new. Also for CRT regaining metallising. Research & Development. Barratts, Mayo Road, Croydon CR0 2QP. 01-684 9917. (9678)

CAPACITY AVAILABLE

TW ELECTRONICS LTD.

THE PCB ASSEMBLERS

More and more companies are investigating the advantages of using a professional subcontractor. Such an undertaking requires certain assurances.

TW are able to satisfy all of them - quality, competitive pricing, firm delivery, and close co-operation with the customer.

Assembled boards are 100% inspected before flow soldering and reinspected after automatic cropping and cleaning. Every batch of completed boards is issued with a signed certificate of conformity and quality - our final assurance.

For further details, contact us at our new works:

Blenheim Industrial Park
Bury St. Edmunds
Suffolk IP33 3UT
Tel: 0284 3931 (1466)

ELECTRONIC DESIGN SERVICE. Immediate capacity available for circuit design and development work, PC artwork, etc. Small batch and prototype production welcome. - E.P.D.S. Ltd., 1A Eva Road, Gillingham, Kent. Tel: Medway (0634) 577854. (9667)

BATCH PRODUCTION wiring and assembly to sample or drawings. McDeane Electricals Ltd, 19b Station Parade, Ealing Common, London W5. Tel: 01-892 8976. (169)

PHONE YOUR CLASSIFIEDS TO IAN FAUX ON 01-661 3033

COMPUTER APPRECIATION

86 High Street, Bletchingley, Redhill, Surrey RH1 4PA - Tel: Godstone (0883) 843221

PDP 11/10 COMPUTER SYSTEM comprising 28KW processor with switch console, 3 x RK05/J 2.5 megabyte removable disc drives with RK11-D, 2 x Model VT50 VDU Terminals (12 lines x 80), TALLY Model 2000 200 l.p.m. line printer, bootstrap and console emulator card. The whole system is contained in two four-foot DEC cabinets and is in immaculate condition. Software includes RT11, BASIC, FORTRAN, etc. manufactured 1977 £3750

PDP 11/03 MICROCOMPUTER SYSTEM comprising LSI 11 processor in BA11 MF box with 64KB memory, DLV11J quad serial interface REV11 bootstrap and diagnostic ROM card, RK01 dual floppy disc drive, SYSTIME VDU Terminal with 24 x 80 U/L case display and Model LA120 DECwriter (120 c.p.s. bi-directional U/L case). The processor and disc drives are contained in a 24-inch high DEC cabinet. Software includes RT11 with BASIC, etc. £2950

DEC Model BA11-K UNIBUS mounting box. With power supply £150

NCR Model 8130 MICROCOMPUTER SYSTEM. INTEL 8080 based machine with 64KB memory (and battery backup), twin dual-density floppy disc drives, VDU and keyboard, 180 c.p.s. bi-directional nine wire printer and facilities for reading bar coded ledger cards. The system is under 2 years old and full support is available from NCR. £1250

RAYTHEON Model PTS100 System. Comprising 16-bit processor with 64KB MOS memory, 3 VDU terminals, cassette drive and numerous option and interface cards. A test set is included. Contained in a six-foot rack. Manufactured 1978. £550

RAYTHEON Model 704 16-bit processor with front switch panel, 12KW memory and various interfaces. £50

VENTEK Model 1200 MINICOMPUTER SYSTEM with 16K memory, 12-line x 80 VDU with U/L case, 3 x 8-inch dual density floppy disc drives. Powerful operating system includes BASIC. £375

ELBIT Model DS-1920X VDU. 24 lines x 80 U/L case VDU with 15in. green screen, detached keyboard and full functions including cursor addressing, insert/delete blink, etc. RS 232 to 9600 baud. As new. £350

HAZELTINE Model 1200 VDU. 24 x 80 VDU. Upper case only; can easily be upgraded. RS 232 to 9600 baud £175

TEXAS INSTRUMENTS Model 810, high speed (180 c.p.s.), matrix printer. RS 232 and parallel interfaces £425

IBM Selective (golfball) keyboard printer, similar to 735. £36

CENTRONICS Model 101 matrix printer (180 c.p.s.). Parallel TTL interface £150

MEMOREX Model 227B VDU. EBCDIC coded VDU 24 x 80. These modern (1979) VDUs comprise a detached keyboard, MOTOROLA or BALL Monitor, power supplies (5V at 15A, + and - 12V at 3A), and electronics. £25

A. B. DICK Model Magna II word processor. Microprocessor-controlled word processor featuring QUME printer and single-line LED display. Data is recorded on magnetic cards. £350

DIABLO Series 30. Removable disc drive. 2.5 megabyte with industry standard interface. These drives are hardware, software and media compatible with the RK05 and controllers are available for PDP 11, NOVA machines and most micros £250

Power supply for above £30

SYSTIME RK05 UNIBUS controller (similar to RK11-D), complete with a pair of DIABLO drives as above and power supply £395

PERTEC Miniature 9-track 800 b.p.i. NRZ tape drive £175

FACIT Model 4070 high-speed paper tape punch (75 c.p.s.) with parallel TTL interface £225

CALCOMP Model 563 AO size drum plotter. Step size 0.1 mm. Cost of current equivalent model is over £7,000 £350

ERA 1KVA 60Hz converter. All solid state. Contained in four-foot rack £250

PERTEC Model FD-250 dual-density, double-sided 5/4in. floppy disc drive. NEW £35

DOCUMENTATION Model M600L compact card reader £350

NDK Model 4410 CARD READER, NEW £450

LASER ASSOCIATES Nd GLASS LASER. 1.06 micron wavelength, 1-2J per pulse. Fully operational £495

NASHUA Model 1215 plain paper copier £150

Please note:
 * V.A.T. and carriage extra all items
 * We are keen to bid competitively for all good used equipment
 * Visitors welcome but by appointment please

INDEX TO ADVERTISERS OCTOBER

Appointments Vacant Advertisements appear on pages 119-127

	PAGE		PAGE		PAGE
Acoustical Mfg. Co. Ltd.	57	Galatrek International	24	Racal Recorders Ltd	cover ii
Adcola Products Ltd.	2	GAS Electronics	17	Radford Audio Ltd.	118
AEL Crystals	118	Global Specialities Corp (UK) Ltd.	25	Radio Components Specialists	103
AH Supplies	109	GP Industrial Electronics Ltd.	26, 27	Ralfe, P. F. Electronics	92
Airwaves Electronics	106	Greenweld	18	Relay-A-Quip Ltd.	98
Ambit International	9, 100	Greenwood Electronics Ltd.	cover iv	RST Valves	110
Analogue Associates	8	Hameg Ltd.	101	Sagin, M. R.	2
Anglia Components	4	Happy Memories	92	Samsons (Electronics) Ltd.	112
Antex (Electronics) Ltd.	cover iii	Harris Electronics (London)	4	Sche Tronics Ltd.	98
AP Products	94	Harrison Bros Electronic Distributors	95	Sescom Inc.	24
Armon Electronics Ltd.	14	HB Electronics	29	Shure Electronics Ltd.	30
Audio Electronics	19	Hemmings Electronics and Microcomputers	116	Sinclair Research Ltd.	20, 21
Autotype	102	Henry's Radio	6, 24	South Midlands Communications Ltd.	100
Avel Lindberg (Cotswold Electronics)	12	Hilomast Ltd.	5	Sowter, E. A. Ltd.	111
Barrie Electronics Ltd.	115	Horst F. G. Angermann, Hamburg	7	Special Products (Distributors) Ltd.	93
Beckman Instruments (Vako Display Systems)	104	House of Instruments Ltd.	115	Strumeh Engineering Ltd.	89
Black Star Ltd.	109	ILP Electronics Ltd.	89, 107, 117	Surrey Electronics Ltd.	12
Bread Board '82	106	Integrex Ltd.	6	Technomatic Ltd.	90, 91
Broadfields & Mayco Disposals	6	Interface Quartz Devices Ltd.	15	Teleradio Electronics Ltd.	106
Cambridge Kits	16	KEF Electronics Ltd.	93, 95	Television Magazine	93
Chiltern Electronics	95	Keithley Instruments Ltd.	13	Teloman Products Ltd.	16
Chiltmead Ltd.	98	Kelsey Acoustics Ltd.	98	Thandar Electronics Ltd.	99
Circuit Services	25	Langrex Supplies Ltd.	110	Thanet Electronics	97
Clark Mast Ltd.	18	Levell Electronics Ltd.	97	Time Electronics Ltd.	12
Clef Products (Electronics) Ltd.	102	LFH Associates Ltd.	18	Valradio Ltd.	2
Colomor (Electronics Ltd)	22	Marconi Communication Systems	28	Veco Electroforming/Photo-Etching Ltd.	6
Computer Appreciation	128	Melkuijst	97	Watford Electronics	10, 11
Crotech Instruments Ltd.	96	Midwich Computer Co. Ltd.	15	Which? Magazine	Loose Insert
Danavox (Gt. Britain) Ltd.	23	Modern Book Co., The	92	White House Electronics	24
Darom Supplies	102, 106	Monolith Electronics Co. Ltd.	22	Wilmslow Audio	7, 15, 25
Digitalis Ltd.	118	Olson Electronics Ltd.	4	Wireless World Circards	114
Display electronics	113	Opus Supplies	108	WK Electronics Ltd.	16
DSN Marketing Ltd.	101	Orion Scientific Products Ltd.	16	Your Computer	96
Eddystone Radio Ltd.	14	Pantechinc	100	Zaerix Electronics	109, 111
Electronic Brokers Ltd	3, 5, 7, 9	PM Components	104, 105		
Electrovalue Ltd.	118	Practical Computing	112		
Faircrest Engineering Ltd.	12	Practical Wireless	102		
Farnell Instruments Ltd.	28, Reader Card, 111	P&R Computer Shop	92		
Ferranti Electronics	58				
Fieldtech Heathrow Ltd.	22				
Flight Electronics Ltd.	8				
Foundations of Wireless and Electronics	116				

OVERSEAS ADVERTISEMENT

AGENTS:
France & Belgium: Norbert Heliin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.
Hungary: Mrs Edit Bajusz, Hungexpo Advertising Agency, Budapest XIV, Városliget.
 Telephone: 225 008 - Telex: Budapest 22-4525
 INFOIRE
Italy: Sig C. Epis, Etas Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan.
 Telephone: 347051 - Telex: 37342 Kompass.

Japan: Mr. Inatsuki, Trade Media - IBPA (Japan), 8.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106.
 Telephone: (03) 585 0581.
United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 - Telephone: (212) 867-2080. Telex: 238327.
 Mr Jack Farley Jr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone: (312) 63074.
 Mr Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 - Telex: 18-1059.

Mr Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 - Telephone: (216) 621 1919.
 Mr Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301.
 Mr Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone: (404) 237 7432.
 Mike Loughlin, IPC Business Press, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone (713) 783 8673.
Canada: Mr Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269.
 * Also subscription agents.

Printed in Great Britain by QB Ltd., Sheepen Place, Colchester, and Published by the Proprietors IPC ELECTRICAL-ELECTRONIC PRESS LTD., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS, telephone 01-661 3500. *Wireless World* can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service Ltd, Gordon & Gotch Ltd. SOUTH AFRICA: Central News Agency Ltd. William Dawson & Sons (S.A.) Ltd. UNITED STATES: Eastern News Distribution Inc., 14th floor, 111 Eighth Avenue, New York, N.Y. 10011.

Take out!

SK5-BP and SK6-BP Soldering Kits fitted with safety plugs.
SK5-BP Kit R.R.P. £7.10
SK6-BP Kit R.R.P. £7.20

ST4 Stand
R.R.P. £1.60

TCSU1 Soldering Station for safe 24 volt temperature-controlled miniature soldering iron, variable tip temperature 65 - 430°C, antistatic earth connection, with XSTC or CSTC iron.
R.R.P. £40.50

Model XS-BP
— 25 Watts fitted with safety plug 240 volts
R.R.P. £5.55

Model XS
— 25 Watts Available for 240 and 115 volts
R.R.P. £4.70
50, 24 and 12 volts
R.R.P. £4.80

Model CS-BP
— 17 Watts. Fitted with safety plug. 240 volts
R.R.P. £5.45

Model CS
— 17 Watts Available for 240 and 115 volts
R.R.P. £4.60
50, 24 and 12 volts
R.R.P. £4.80

Model C — 15 Watts
Stainless steel shaft only.
240 and 115 volts R.R.P. £4.60
50 and 24 volts R.R.P. £4.80

Model CCN — 15 Watts
Ceramic shaft only. 240 volts.
R.R.P. £5.00

SK5 Soldering kit contains model CS230 iron and the ST4 stand R.R.P. £6.25

SK6 Soldering kit contains Model XS230 iron and the ST4 stand R.R.P. £6.35

... Plug in

Everything you need in the **NEW** Antex all-in-one pack!


Iron, stand, lead, plug and solder — it's all ready to go.

The new stand is tough and compact, designed for greater efficiency in minimum bench space.

And each iron has all the Antex features — the big range of push-on bits, the low leakage factor, the superb insulation, and the strong lightweight case.

So when you need another soldering unit fast — here's a hot tip. The new Antex all-in-one pack.

WW-002 FOR FURTHER DETAILS

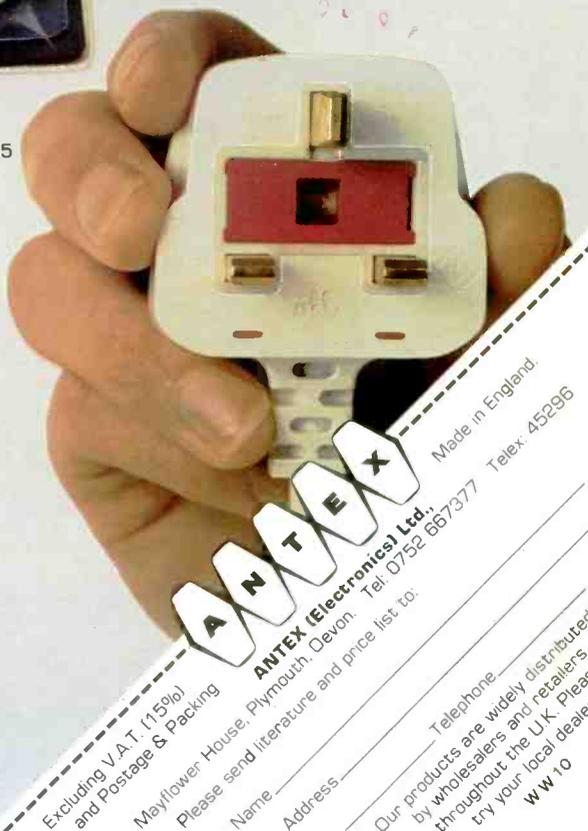

ANTEX
ANTEX (Electronics) Ltd.

Made in England
Telex: 45296

Excluding V.A.T. (15%)
and Postage & Packing
Mayflower House, Plymouth

Please send literature and price list to:
Name _____
Address _____
Telephone _____

Our products are widely distributed by wholesalers and retailers throughout the U.K. Please try your local dealer.
www.10

ORYX



the new name in quality solder

Now there is another choice in high quality solder. The new Oryx resin cored solder. Try it and you will find it spreads easier than the solder you are using. Specially formulated for fast precision solder work, it is 60% tin, 40% lead alloy with quality flux construction and melts at 183°C. Two gauges are available—18 SWG (1.2mm) and 22 SWG (0.71mm) in 2.5 Kg, 500g, 250g and 100g reels. Pocket size dispenser with 10 feet of Oryx 1-mm solder is also available at only 68p (+VAT). Oryx is competitively priced—write now for details and technical information.

Greenwood Electronics

Greenwood Electronics Limited, Portman Road, Reading, Berkshire RG3 1NE. Telephone: (0734) 595844. Telex: 848659

The TC82—a significant development in temperature controlled soldering



The new Oryx TC 82 has features unique to any temperature controlled precision soldering iron. Available in 24 V, 50 V, 115 V and 210/240 V models, the TC 82 has a facility allowing the user to accurately dial any tip temperature between 260°C and 420°C by setting a dial in the handle without changing tips.

This eliminates the need for temperature measuring equipment. You get faster and better soldering.

For 24 V models a special Oryx power unit connects directly to the iron and contains fully isolated transformer to BS3535, a safety stand, tip clean facility and illuminated mains socket switch.

The Oryx TC 82 is also **extra-safe**. Removing the handle automatically disconnects the iron from power source. Other TC 82 features include: Power-on Neon indicator in handle; burn proof cable; choice of 13 tip styles.

And more good news

The Oryx TC 82 iron costs only £13.00 (+VAT) and the power unit for 24 V operation £23.00 (+VAT).

The TC82 240 volt is also available as a 30 watt general purpose iron at only £4.95 (+VAT).

Greenwood Electronics

Greenwood Electronics Limited, Portman Road, Reading, Berkshire RG3 1NE. Telephone: (0734) 595844. Telex: 848659