


# ELECTRONICS & Wirelessworld

JANUARY 1984

85p

**XY plotter**

Australia	A\$	3.00
Denmark	DKr	34.50
Germany	Dm	7.00
Greece	Dra	220.00
Holland	DFL	8.50
Italy	L	3800
Norway	Nkr	29.20
Singapore	M\$	5.50
Spain	Pts	340.00
Switzerland	SFr	7.00
U.S.A.	\$	3.75

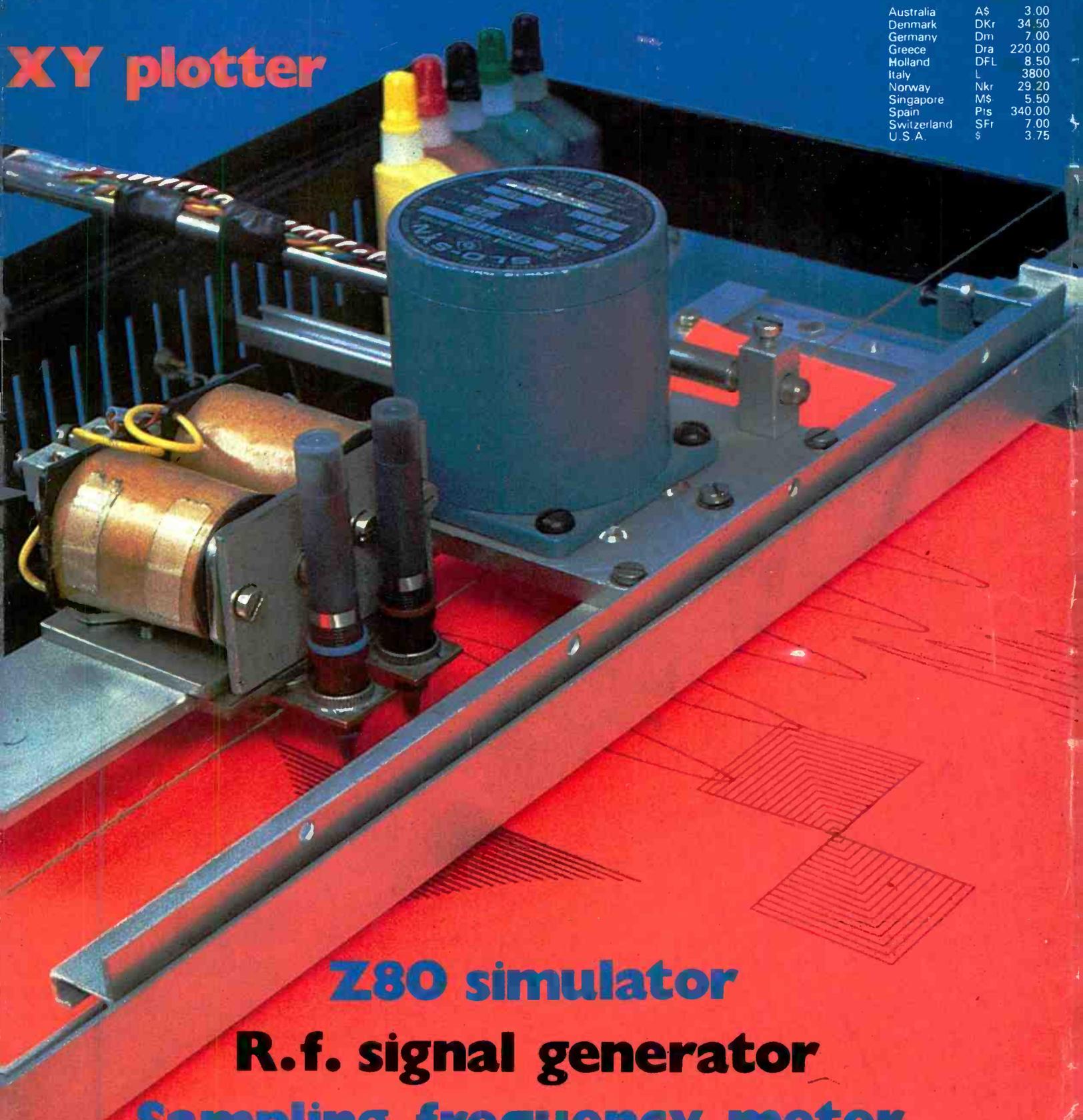

**Z80 simulator**


**R.f. signal generator**

**Sampling frequency meter**

# EP8000

## EPROM EMULATOR PROGRAMMER

**NEW  
PRODUCT**

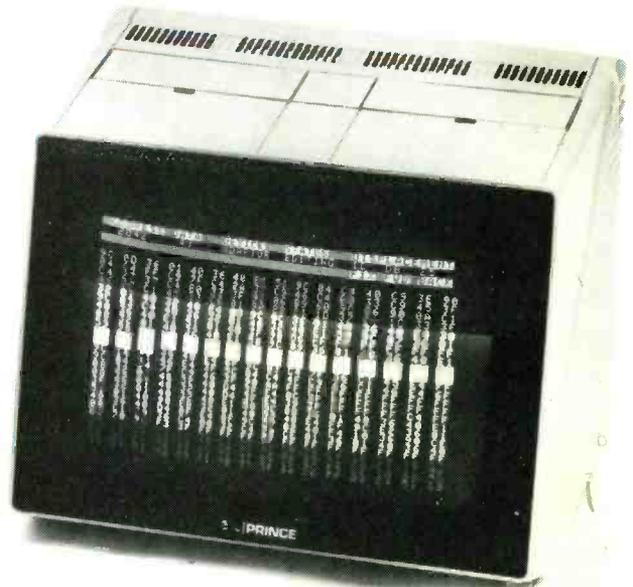

The new microprocessor controlled EP8000 Emulator Programmer will program and emulate all EPROMs up to 8k x 8 sizes, and can be extended to program other devices such as 16k x 8 EPROMs, Bipolar PROMs, single chip microprocessors with external modules.

Personality cards and hardware changes are not required as the machine configures itself for the different devices.

The EP4000 with 4k x 8 static RAM is still available with EPROM programming and emulation capacity up to 4k x 8 sizes.

● EP8000 8k x 8 Emulator Programmer – £695 + £12 delivery ● BSC8 Buffered emulation cable – £49 ● SA27128 Programming adaptor – £69 ● SA25128 Programming adaptor – £69 ● EP4000 4k x 8 Emulator Programmer – £545 + £12 de-

### FEATURES

- Software personality programming/emulation of all EPROMs up to 8k x 8 bytes including 2704, 2708, 2716(3), 2508, 2758A, 2758B, 2516, 2716, 2532, 2732, 2732A, 68732-0, 68732-1, 68766, 68764, 2564, 2764. Programs 25128, 27128 with adaptors.
- No personality cards/characterisers required.
- Use as stand alone programmer, slave programmer, or EPROM development system.
- Checks for misplaced and reversed insertion, and shorts on data lines.
- Memory mapped video output allows full use of powerful editing facilities.
- Built-in LED display for field use.
- Powerful editing facilities include: Block/Byte move, insert, delete, match, highlight, etc.
- Comprehensive input/output – RS232C serial port, parallel port, cassette, printer O/P, DMA.
- Extra 1k x 8 scratchpad RAM for block moving.

livery ● BSC4 Buffered emulation cable – £39 ● BP4 (TEXAS) Bipolar PROM Module – £190 ● Prinz video monitor – £99 ● UV141 EPROM Eraser with timer – £78 ● GP100A 80 column printer – £225 ● GR1 Centronics interface – £65

VAT should be added to all prices

**DISTRIBUTORS REQUIRED**

**EXPORT ENQUIRIES WELCOME**

**GP Industrial Electronics Ltd.**

Tel: Plymouth (0752) 332961  
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

# ELECTRONICS & Wireless World

JANUARY 1984

VOL 90 NO 1576



Cover picture shows Philip Hill's XI plotter, the construction of which is described on page 24.

## NEXT MONTH

IEEE-488 interface for the BBC Microcomputer. This full-specification interface for laboratory use allows automatic control up to 14 instruments.

Synthesised television modulator with microprocessor control for video generators, offering a frequency stability much better than free-running modulators.

F. J. Lidgley investigates the circuitry of current followers which use conventional operation amplifiers, and proposes a general-purpose amplifier system.

Current issue price 85p, back issues (if available) £1.06, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hopton Street, London SE1. Available on microfilm; please contact editor.

By post, current issue £1.30, back issues (if available) £1.40, order and payments to EEP General Sales Dept, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Tel: 01-661 8668.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Telephones: Editorial 01-661 3614. Advertising 01-661 3130. See leader page. Telex: 892084 BISPRS G.

Subscription rates: 1 year £15 UK and £19 outside UK.

Student rates: 1 year £10 UK, and £12.70 outside UK.

Distribution: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telephone: 01-661 3248.

Subscriptions: Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone: 0444 459188. Please notify a change of address.


USA: \$49.40 surface mail, \$102.60 air. Business Press International (USA). Subscriptions Office, 205 E.42nd Street, NY 10017.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd class postage paid at New York.

© Business Press International Ltd 1983  
ISSN 0043 6062.

- 
- 21** SO YOU WANT TO BE AN AUTHOR?
- 
- 22** COMMUNICATIONS COMMENTARY
- 
- 24** COMPUTER-CONTROLLED XY PLOTTER  
by P. N. C. Hill
- 
- 30** ASSEMBLY-LANGUAGE PROGRAMMING  
by R. F. Coates
- 
- 34** 16-LINE P.A.B.X. WITH OPTIONS  
by J. H. Kuiper
- 
- 37** SAMPLING FREQUENCY METER  
by N. A. Lockerbie
- 
- 41** STATIC Z80 SIMULATOR  
by Colin Walls
- 
- 44** NEWS
- 
- 49** LETTERS
- 
- 52** IMPROVING COLOUR TELEVISION DECODING  
by D. C. Read
- 
- 57** CONSTRUCTOR'S R.F. GENERATOR  
by L. Boullart
- 
- 59** ADVANCE INTO THE PAST  
by Ivor Catt
- 
- 61** RADIO-ACTIVATED IMPLANT FOR BLADDER CONTROL  
by T. E. Ivall
- 
- 65** BEHIND THE MICRO
- 
- 73** CIRCUIT IDEAS
- 
- 83** NEW PRODUCTS
-
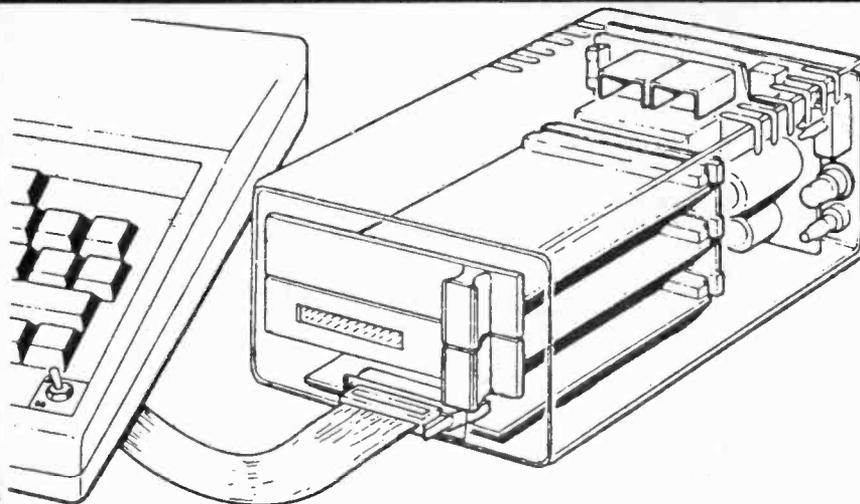
# CUBEFLEX 6809 2nd processor for the BBC micro



**CUBEFLEX for education and software development**  
CUBEFLEX is supplied with a number of useful machine code handling facilities, and FLEX itself comes complete with a text editor and machine code assembler for 6809.

However, the real strength of FLEX is the enormous range of other software to run under its operating system.

Cross assemblers and macro facilities exist which allow the CUBEFLEX to develop object code for all the 68 range from 6801 to 68000, all the 80 range, and the Z80. The CUBE ROMULATOR can be added to the spare slot in the CUBEFLEX, and so emulate the developed software in a target system.

#### COMPILERS

PL/9 is a high level compiling language whose structure resembles BBC BASIC. However, when compiled into machine code it runs four times as fast.

"C", Pascal and 6809 extended BASIC are all also available, and allow the user to employ the language of his choice.

## 6809 + FLEX - the ultimate in 8-bit systems

The BBC microcomputer is already so good, how can it be improved? FLEX is the only truly machine independent operating system for 8-bit processors. Even CP/M (for Z80) is machine specific to a significant degree. But take any standard 5 1/4" FLEX diskette and it will load on CUBEFLEX. All variations of double or single sides, 40 or 80 tracks (if 80 track drives are fitted), and even double density (if an appropriate disk interface is fitted on the BBC) are automatically catered for.

CUBEFLEX connects to the BBC via the TUBE, and uses the standard BBC disk interface and disk drives. All BBC facilities are unimpaired by the addition of CUBEFLEX, and can be called up or returned to at any time. The FLEX configuration parameters are held in EPROM, and the unconfigured FLEX diskette is read in and initialised upon entry of the start-up command.

CUBEFLEX 6809 2nd Processor unit    £299  
Unconfigured FLEX diskette + manual    £130

Send for  
our free 150  
page catalogue.

All prices exclude VAT.  
Trade enquiries welcome.

**Control Universal Ltd**  
Anderson's Court  
Newnham Road,  
Cambridge CB3 9EZ.  
Tel 0223 358757

WW - 047 FOR FURTHER DETAILS

## KONTAKT



### NEW from Kontakt

The capability and effect of compressed air in a handy can. TENSION 67 efficiently removes dust and deposits from electronic components, electronic and electrical apparatus, microscopes, medical equipment, cabinets, etc. Absolutely no spray residues. No compressed airline needed. With plug-in nozzle even blows around corners. Ready for use in the service kit.

### Kontakt 60

Dissolves oxides and sulphides, removes dirt, oil, resin and traces of metal abrasion. Protects against erosion. Ensures perfect contacts.

### Kontakt 61

Special cleaning, lubricating and anti-corrosion fluid for NEW (non oxidised) and specially sensitive contacts. An excellent lubricant for all electrical and electro-mechanical systems.

### Spray Wash WL

A rapid cleaner for reliable washing and degreasing of electrical equipment and components. For removal of dirt, grease, oil, soldering residues and other impurities.

### ALSO AVAILABLE:

#### A COMPLETE RANGE OF INDUSTRIAL AEROSOL SPRAYS

SK10 Soldering Lacquer, K75 Cold Spray, K70 Plastic Spray, K88 Oil Spray, K701 Vaseline Spray, K90 Video Spray, K33 Graphite Spray, K100 Antistatic Spray, K101 Fluid Spray and, of course, Positiv 20 positive photo resist for printed circuits.

Details from:

### Special Products Distributors Ltd.

81 Piccadilly, London W1V 0HL  
Tel: 01-629 9556. Telex: 26500 (answerback RACEN)  
Cables: Speciproduct, London W1

WW - 021 FOR FURTHER DETAILS



## MITSUBISHI

MGF-1400  
MGF-1402  
MGF-1412


## GaAs FETs

FROM STOCK
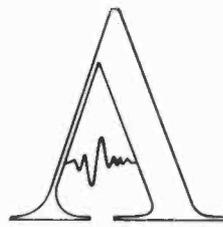
## Aspen Electronics Limited

UK representative for Mitsubishi Electric

2/3 Kildare Close, Eastcote, Ruislip  
Middlesex HA4 9UR  
Tel: 01-868 1188 Tlx: 8812727



WW - 040 FOR FURTHER DETAILS

## ELECTRONIC VALVES WANTED

All Types Receiving, Transmitting, Industrial

CV136 - CV138 - CV329 - CV345 - CV2209  
- PL508 - PL509 - PL519 - PCL805 -  
PY500A

Phone/write to:  
**PYPE HAYES RADIO LTD.**  
606 Kingsbury Road  
Birmingham B24 9PJ  
021-373 4942

WW - 015 FOR FURTHER DETAILS

# HF ANTENNAS



- ★ **MODE;** Full half wave operation.
- ★ **BANDS;** Up to 4 spot frequencies.
- ★ **POWER;** Receive to 800W (PEP).
- ★ **SWR;** Better than 1.5:1 on channel.



From £135

## THE SMC TRAPPED DIPOLE ANTENNA

has been developed to satisfy the needs of commercial and military users. It is capable of operation between 2 and 30 MHz on as many as four spot frequencies — each capable of accommodating many channels. Excellent matching and efficiency with a single coaxial feed is offered by the use of SMC H1Q traps and the incorporation of a ferrite balun in a full half wave design. NB: Power absorbing terminating resistors are not employed. The antenna may be deployed using one or two support masts, installation (incorporating SMC light duty portable masts) can be easily effected by two people in half an hour.

## HF SSB TRANSCEIVER



**TM180 "PIONEER" HF SSB TRANSCEIVER.** 1.8-18MHz, 6 channels 100 watts RF output measuring only 95(H) x 240(W) x 310(D)mm and weighing 6kg. May be operated as a base or mobile transceiver, complementing our trap dipole and HW4 mobile aerials. Prices start at £700, making this unit not only very attractive but highly competitive.

## SOUTH MIDLANDS COMMUNICATIONS LTD.

SM HOUSE  
OSBORNE ROAD, TOTTEN  
SOUTHAMPTON SO4 4DN

Telex: 477351 SMCOMM G  
Tel: Totton (0703) 867333

WW - 027 FOR FURTHER DETAILS

**pantechnic**

THE POWERFET SPECIALISTS

## OEM USERS

Pantechnic present the most adaptable high-powered amplifier ever.

### FET SYSTEM AMP

#### Features:

- **HIGH POWER.** 1.2kW (single ended)
  - **LOW VOLUME.** 1/8 Cubic foot inc. Heatsink
  - **VERSATILE.** Delivers more than 1kW into 1/2 to 8 ohms
- OR 2 x 600W into 2 to 8Ω  
OR 4 x 300W into 2 to 4Ω (200W into 8Ω)
- OR { 1 x 600W into 2 to 8Ω  
1 x 300W into 2 to 4Ω  
1 x 150W into 4 to 8Ω
- Etc., etc.

Having been closely involved in a wide variety of OEM applications of their amp boards. Pantechnic became aware of numerous implementation problems often left unattended by other amp board manufacturers. These problems specifically of size and thermal efficiency became particularly aggravated at high powers and considerably lengthened OEM product development time.

By including thermal design in the totality of board design it has been possible to reduce the size of the electronics, and increase the efficiency of the transistor to heatsink thermal circuit. The combined effect of this has been to dramatically increase the volumetric efficiency of the amplifier/heatsink assembly. The **SYSTEM** Amp offers 1.2kW of power in a space of 180mm x 102mm x 77mm, excluding PSU and Fan.

The basis of this considerable advance is the **PANTECH 74** Heat Exchanger, newly designed and manufactured by us. By eliminating the laminar air flow found in conventional, extruded heatsinks, heat transfer to the environment is greatly enhanced.

The flexibility of the 1.2kW amp stems from its division into 4 potentially separate amplifiers of 300W each (downrateable with cost savings to 150W). These can be paralleled, increasing current capability or seriesed (bridge in pairs) doubling voltage capability. In consequence a large variety of amplifier/load strategies can be implemented.

As ever Pantechnic offer a full range of customising options including DC coupling, ultra-high slew, etc. Contact Phil Rimmer on 01-800 6667 with your particular application problem.

P.S. Specs, as ever, are exemplary.

A wide range of other amplifiers and other modules available.

Price and Delivery

**PANTECHNIC (Dept. WW1)**  
17A WOOLTON STREET  
LIVERPOOL L25 5NH  
Tel: 051-428 8485

Technical Enquiries  
contact  
Phil Rimmer  
on  
01-800 6667

WW - 059 FOR FURTHER DETAILS

# THE SOURCE OF ALL GOOD USED TEST EQUIPMENT

## ANALYSERS

**Hewlett Packard**  
334A Distortion Analyser ..... £1200.00  
3581A Wave Analyser ..... £1800.00  
3582A Dual-Channel Spectrum Analyser  
0.02Hz-25.5KHz ..... £6650.00  
5004A Signature Analyser ..... £550.00

**Marconi**  
TF2330A Wave Analyser ..... £950.00

**Tektronix**  
AA501 opt.01 Distortion 10Hz — 100KHz  
to Less than 0.0025% ..... £1450.00  
DAS 9103 opt.01 02 Logic Analyser  
..... £11,000.00

DF1 Display Formatter For 7D01 ..... £850.00  
308 Portable 8 Channel 20MHz Data  
Analyser ..... £2100.00

492 [opt.01, 08] Spectrum Analyser  
50KHz-21GHz ..... £13000.00  
492P [opt.01, 2, 3] Programmable Version  
of 492 ..... £20000.00  
7L12 Spectrum Analyser 100KHz-1.8GHz  
..... £6000.00

7L13 Spectrum Analyser 1KHz-1.8GHz  
..... £7500.00

7L18 Spectrum Analyser 1.5GHz-60GHz  
..... £7500.00

TR503 Tracking Generator [for 492/496  
series] ..... £3250.00  
5L4N Spectrum Analyser 20Hz-100KHz  
..... £2350.00

7D01 16 Channel 100MHz Sample Rate  
..... £2450.00  
7002/01 Logic Analyser ..... £3950.00

## OSCILLOSCOPES

**Hewlett Packard**  
1332A High Quality CRT Display  
9.6 x 11.9cm ..... £1250.00  
1809A 100MHz 4 Channel Plug In  
..... £2000.00

1821A Timebase Plug In ..... £1000.00

**Philips**  
PM3232 Dual Beam 10MHz ..... £495.00

**Tektronix.**  
305 Portable battery scope/DMM, 0 T  
5MHz ..... £975.00  
335 Dual Trace 35MHz Small portable with  
delay T Base ..... £1300.00  
200C Trolley for 400 Series ..... £120.00  
7313 100MHz Storage Mainframe  
..... £2225.00

7603 100MHz Mainframe ..... £1850.00  
5441 50MHz Variable Persistence Storage  
Mainframe ..... £1600.00  
7704A Scope DC-200MHz Mainframe  
..... £2850.00

7613 Storage Scope Mainframe  
DC-100MHz ..... £3250.00  
7844 Dual Beam 400MHz Mainframe  
..... £7750.00

7854 Waveform Processing Scope  
DC-400MHz ..... £9000.00  
7904 opt.02, 03 500MHz ..... £5350.00

## SIGNAL SOURCES

**E H Labs**  
132A Pulse Gen ..... £1200.00  
139B Pulse Gen ..... £950.00

**Hewlett Packard**  
204C Oscillator ..... £200.00  
204D Oscillator ..... £240.00  
214A Pulse Gen ..... £950.00  
11720A Pulse Modulator ..... £1950.00

612A Sig Gen ..... £1500.00  
8004A Pulse Gen ..... £450.00

8011A-01 Pulse Gen ..... £695.00  
80138 Pulse Gen ..... £750.00  
8640A Sig Gen ..... £2750.00

**Marconi**  
TF2008 Sig Gen ..... £3000.00  
TF2015 Sig Gen ..... £1350.00  
TF2015/1 Sig Gen ..... £1350.00  
TF2169 Pulse Modulator ..... £200.00  
TF2120 Waveform Gen. .... £850.00

**Wavetek**  
148 Funct Gen ..... £650.00

## TEKTRONIX PLUG INS

We stock a complete range of Plug Ins for use with 7000 and 5000 Series Mainframes.

## TEKTRONIX TM500 SERIES

We stock a very wide range of these versatile modular equipments

## MISCELLANEOUS

**Avo**  
Model 8 Multimeters ..... £80.00  
VCM 163 Value Characteristic Meter  
..... £495.00

7 Electricians Multimeter ..... £65.00

**Bruel & Kjaer**  
2203 Sound Level Meter ..... £450.00  
2209 Sound Level Meter ..... £850.00  
1613 Filter ..... £400.00

**Datalabs**  
DL901 Transient Recorder ..... £750.00  
DL905 Transient Recorder ..... £995.00

**Fluke**  
515A Portable Calibrator ..... £1750.00  
845 AB Null Detector ..... £610.00  
931B Diff V Meter ..... £1,000.00  
1900A Counter/Timer 80MHz ..... £225.00  
2020A 3-6 Printer ..... £500.00  
5205A Precision Power  
Amplifier ..... £3500.00  
8921A DMM ..... £695.00

**Hewlett Packard.**  
467A Amplifier ..... £725.00  
415E VSWR Meter ..... £950.00  
3556A Psophometer ..... £850.00  
3552A Trans Test Set ..... £1,500.00  
4815A Vector Impedance Meter  
..... £3850.00

**Marconi**  
TF1313A LCR Bridge ..... £775.00  
TF2603 RF Millivoltmeter ..... £750.00

**Racal**  
9514 Counter/Timer IEEE ..... £850.00

**Tektronix**  
106 Square Wave Generator 1nS risetime  
10Hz-1MHz without accessories ..... £175.00  
191 Constant Amplitude Generator  
..... £250.00

832 Data Comms. Tester ..... £925.00  
833 Data Comms. Tester ..... £1350.00  
2701 Step Attenuator 50Ω 0.79dB in 1dB  
steps. DC to 2GHz ..... £295.00



**Jan Special Offer**  
TEKTRONIX. A complete  
Measurement System.  
TM506 c/w FG501, PG501,  
PS501-1, DM501, SC501,  
DC503. 1 YEAR WARRANTY.  
£2000 THE LOT

Please note: Prices shown do not include VAT or carriage.


**Electronic Brokers Ltd., 61/65 Kings Cross Road,  
London WC1X 9LN. Tel: 01-278 3461. Telex 298694**



WW - 202 FOR FURTHER DETAILS

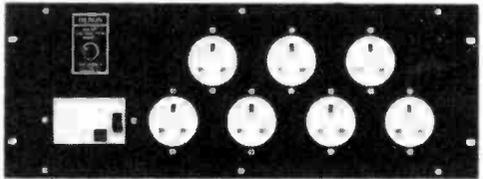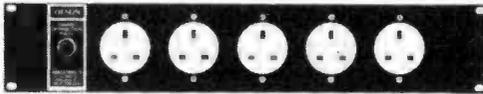

**V  
E  
R  
T  
I  
C  
A  
L**

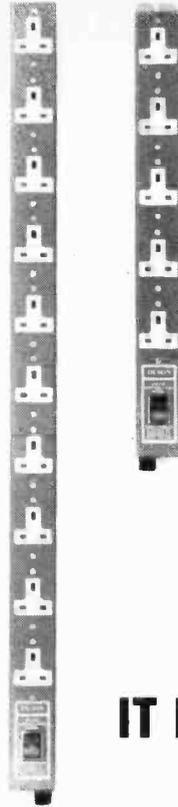

**WHEN  
IT COMES  
TO POWER  
FOR RACKS  
IT MUST BE OLSON**

**HORIZONTAL OR**

**VERTICAL RANGE FROM 3-10 SOCKETS  
ALL EX-STOCK!  
SPECIALS TO ORDER**

**OLSON ELECTRONICS LIMITED**

**5-7 LONG STREET LONDON E2 8HJ  
TEL: 01-739 2343 TELEX 296797**

WW - 037 FOR FURTHER DETAILS



**Orange aid!**

No! It's not a floating drinks dispenser, it's the Neptune hand-held radio case. Neptune is brilliant orange, it floats, it's waterproof and could save your life if your ICOM hand-held fell in the drink. Neptune cases are easily retrieved from:

**Thanet Electronics Ltd.**  
143 Reculver Road Herne Bay Kent.  
Tel: (02273) 63859/63850.  
Sole U.K. Importers of ICOM equipment.

WW - 033 FOR FURTHER DETAILS

**E.M.S. POWER  
SYSTEMS**



Solve all your Power Problems by contacting E.M.S.

E.M.S. specialise in systems to eliminate your power problems.

Products range from 35VA switched square wave Power Packs to 1KVA fully uninterruptible sine wave systems.

E.M.S. also manufacture chargers which range up to 60 amps.

For further details please contact:

**E.M.S. Manufacturing Limited**  
Chairborough Road  
High Wycombe  
Bucks  
Tel: (0494) 448484

WW - 009 FOR FURTHER DETAILS

# The lightweight mast with 101 applications

**25**  
years in this specialist field



The smoothly operated QTM Mast comes fitted with handpump or can be vehicle mounted with 'Power Pack' for extension and retraction. Available in a range of heights up to 15 metres, the QTM mast can provide the ideal answer for:

- Mobile Radio Telephone
- Police Mobile HQ (UHF)
- Field Telecommunications
- Floodlighting
- Anemometer and Wind Measurement
- Environmental - gas sampling collector
- High level photography
- Meteorology
- And a host of other uses

## CLARK MASTS

Find out more about the QTM series by writing or phoning:-

U.K.  
CLARK MASTS LTD. (W.W.)  
Evergreen House, Ringwood Road,  
Binstead, Isle of Wight.  
England PO33 3PA  
Tel: Isle of Wight (0983) 63691  
Telex: 86686

EUROPE  
GENK TECHNICAL PRODUCTS N.V. (W.W.)  
Woudstraat 21, 3600 Genk,  
Belgium.  
Telephone 011-380831  
Telex 39354 Genant B

WW-054 FOR FURTHER DETAILS

# DEC SALE

a selection from our huge stocks. All items reconditioned unless otherwise stated.

**WINTER '83/'84 CATALOGUE NOW OUT**  
Send for your Free copy now.

### DISK DRIVES

RK07ED 28MB NEW.....	£2,500
RK07PD 28MB NEW.....	£2,500
RL01A 5MB.....	£995
RM03AD 67MB NEW.....	£6,250
RM80 124MB.....	£9,500
RP06AB 176MB.....	£7,500

DLV11F Asynch. Interface.....	£150
DLV11J 4-line Interface.....	£350
DUV11A Synch. Interface.....	£395
IBV11A Gen. Purpose I/F.....	£325
KD11HA CPU Module.....	£125
KDF11AA CPU Module.....	£900
KDF11AC CPU Module.....	£695
LPV11 Printer Interface.....	£175
MRV11C Prom Module.....	£175
VTV01 A/D Controller.....	£475

### DEC LSI11

#### Systems

11/23AB Processor  
128KB MOS Memory  
DLV11J 4-line Interface  
2 x RL01 Disk Drives  
VT100 Console  
Cabinet  
**£7500**

#### Processors

11/03 64KB 5 1/4" Chassis NEW  
**£1,495**  
11/23AB 128KB 5 1/4" Chassis  
from..... **£2,950**

#### Options

AAV11A D/A Converter..... **£850**  
ADV11A A/D Converter..... **£725**  
BA11MF 3 1/2" Expander box **£595**  
DLV11 Asynch. Interface... **£125**

### PDP11 SYSTEMS

Just two from the many configurations available.

#### PDP11/34A 256KB

2 x RK07 Disk Drives  
H960 Cabinet  
VT100 Console  
**£11,500**

#### PDP11/40 32KW Core

2 x RK05 Disk Drives  
H960 Cabinet  
LA36 Console  
**£4,750**

## PRINTERS AND VDUS


### ANDERSON JACOBSON

AJ832 30cps Daisy Wheel Printer  
with Keyboard, Stand and RS232  
Interface..... **£750**  
AJ860 RO Desktop Matrix Printer  
120 cps, RS232 Interface... **£595**

1620 KSR Daisy Wheel Printer  
EIA I/F..... **£795**  
1640 KSR Daisy Wheel Printer  
EIA I/F..... **£1,350**  
1650 Daisy Wheel Printer  
EIA I/F..... **£1,275**
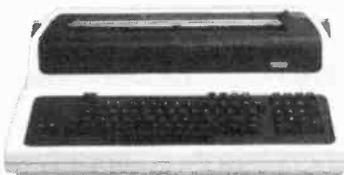
### DATA PRODUCTS

B300 Band Printer..... **£2,750**  
M200 Matrix Printer with  
Stand..... **£1,875**  
2230 300 Lpm Drum Printer, U/L  
case, NEW..... **£2,500**  
2470 1200 Lpm Drum Printer  
NEW..... **£5,500**



### DEC

LA34 30 cps DECwriter IV from  
..... **£425**  
LA35 30 cps RO DECwriter II  
with stand, 20mA I/F..... **£250**  
EIA I/F..... **£275**  
LA36 30 cps KSR DECwriter II  
with stand, 20mA I/F..... **£295**  
EIA I/F..... **£325**  
LA180PD 180 cps Matrix Printer  
with stand, parallel I/F..... **£495**

### HAZELTINE

1410 VDU Terminal..... **£295**  
1420 VDU Terminal..... **£325**  
1500 VDU Terminal..... **£325**  
1510 VDU Terminal..... **£395**  
8020E Executive 80 VDU... **£675**  
ESPRIT VDU Terminal..... **£395**

### GUME

S5/SS Daisy Wheel Terminal **£625**

### RUTISHAUSEN

Sheet feeder for Diablo Daisy  
Wheel Printer..... **£375**

### DIABLO

1345A RO Daisy Wheel Printer  
with stand, parallel I/F..... **£1,100**  
1355HS RO Daisy Wheel Printer,  
parallel I/F..... **£850**

### TEXAS

745 Portable 30 cps terminal with  
integral acoustic coupler..... **£850**

ADD 15% VAT TO ALL PRICES

Carriage and Packing extra

**Electronic Brokers Ltd., 61/65 Kings Cross Road,  
London WC1X 9LN. Tel: 01-278 3461. Telex 298694**



Electronic Brokers

WW-203 FOR FURTHER DETAILS

## NEW PRODUCT


# BX80 COLOUR MATRIX PRINTER

£495+VAT

Especially designed for use with the BBC Microcomputer

Colour printout is quickly assimilated, makes graphics more understandable and is an ideal medium for the presentation of complex data or concepts.

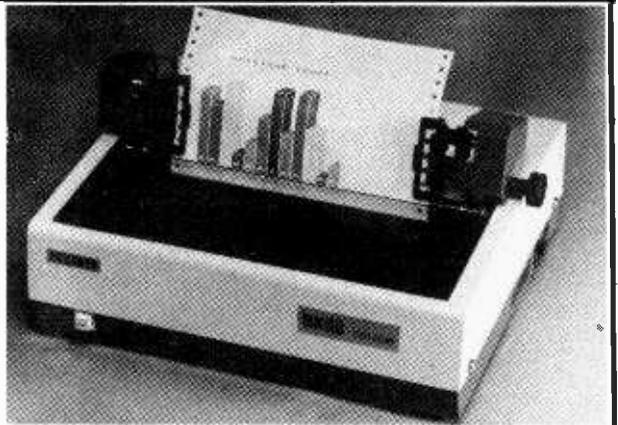Prints in 7 colours on plain paper. Colour screen printing in ALL modes (inc. mode 7 Teletext). Uses RS423 output (cable supplied). Printer RS423 input has 2.5K bytes buffer. In mode 7 Teletext, printer has a 2 page store with printout size option. 125 cps primary colour speed for listing, etc. Screen dump listing supplied.



also

Black and White printer interface for BBC micro-Epson MX\*/RX/FX80 3.5K byte buffer: all modes inc. mode 7 Teletext. Uses RS423 o/p.

Board, RS423 cable + listing **£95+VAT**

Apple II parallel interface card for MX\*/RX/FX80 gives hi res screen dumps, etc. C/w cable **£59+VAT**

Ribbons for MX/RX80 **£5.50+VAT**

Ribbons for BX80 **£5+VAT**

\* MX80 requires printer ROM change, add **£15+VAT**

NEW model VRX80 black/white viewdata printer, 3.5K byte buffer, **£425+VAT**


# INTEGREX LIMITED

Portwood Industrial Estate, Church Gresley  
Burton-on-Trent, Staffs DE11 9PT  
Burton-on-Trent (0283) 215432. Telex: 377106



**HBED**

## SATELLITE RECEIVING EQUIPMENT

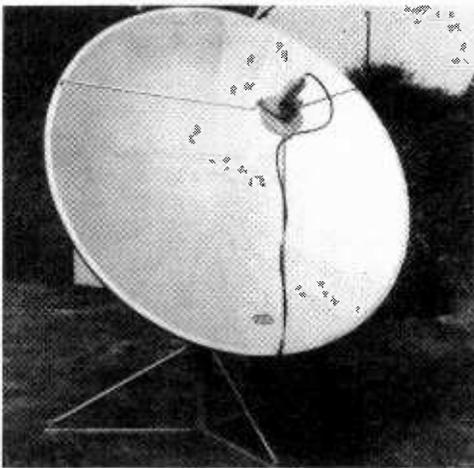

1.9M, 2.5M and 5M Harrison Dishes. Sat-Tec R5000 4GHz Receivers. Avcom COM-2B 4GHz Receivers. California Amplifier 4GHz LNAs. Chaparral Feed Horns. Harrison Feed Horns.

Demonstrations by appointment only.

**Harrison Bros.**

Electronic Distributors

22 Milton Road, Westcliff-on-Sea, Essex SS0 7JX  
Tel. Southend (0702) 332338

## ROBOTICS!!



### MOTORIZED GEARBOX

These units are as used in a computerized tank, and offer the experimenter in robotics an opportunity to buy the electromechanical parts required in building remote-controlled vehicles. The unit has 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx. 50 rpm. Data is supplied with the unit showing various options on driving the motors, etc. **£5.95**. Suitable wheels also available: 3" dia. plastic with black tyre, drilled to push-fit on spindle, 2 for **£1.30** (limited qty.), 3" dia. aluminium disc 3mm thick, drilled to push-fit on spindle, 2 for **68p**.

### MICROPROCESSOR PANELS

**Z903** Panel 240x165 with 6802uP, 6821 PIA, 6850 ACIA, 4040, 4512x2, LS00, LS367x2, 555x2 all in sockets, plus Rs, Cs, plugs, sockets, etc, also 12V sub-min relay. **£5.95**

**Z904** Panel 240x165mm with 6x4099, 723 all in sockets, 14x8A 200V triacs, 45 small signal transistors, 14 R/C networks, 30x1N4001, sub-min relay, Rs, Cs, etc. **£4.95**

**Z905** Finned black ally heatsink 125x198x23mm with 4x2N3055 and 4x0R25 5W Rs. Only **£2.50**

## ★ THE 1984 GREENWELD CATALOGUE ★

Now in the course of production, the 1984 GREENWELD catalogue will be published in December. It's Bigger, Brighter, Better, more components than ever before. With each copy there's discount vouchers, Bargain List, Wholesale Discount List, Bulk Buyers List, Order Form and Reply Paid Envelope. All for just **£1**. Order now for early delivery!

### COMPUTER GAMES

**Z901**. Can you follow the flashing light/pulsating tone sequence of this famous game? Supplied as a fully working PCB with speaker (no case) plus full instructions. Only **£4.95**

**Z902**. Probably the most popular electronic game on the market - based on the old-fashioned pencil and paper battleship game, this computerized version has brought it bang up-to-date! We supply a ready built PCB containing 76477 sound effect chip, TMS1000 microprocessor chip, Rs, Cs etc. Offered for its components value only (board may be cracked or chipped), it's only **£1.95**. Instructions and circuit, **30p**.

### BULK BUYERS - LOOK!

OUR LATEST LIST IS NOW READY - SEND FOR YOUR COPY NOW. LOW PRICES ON SEMIS AND PASSIVES

### REBON CABLE

Special purchase of multicoloured 14-way ribbon cable - **40p**/metre; 50m **£18**; 100m **£32**; 250m **£65**

### "THE SENSIBLE 64"

David Highmore's new book on the Commodore 64 now available. **£5.95**

### NUTS, SCREWS, WASHERS & BOLTS

Over 2 million in stock, metric, BA, self-tappers, etc. SAE for list.

ALL PRICES INCLUDE VAT; JUST ADD 60p P&P

# GREENWELD

443G Millbrook Road, Southampton SO1 0HX

WW - 017 FOR FURTHER DETAILS

# Happy Memories

Part type	1 off	25-99	100 up
4116 200ns.....	1.25	1.15	1.10
4164 200ns.....	4.69	4.19	3.99
2114 200ns Low power.....	1.15	1.00	.90
2114 450ns Low power.....	.95	.85	.80
6116/2016 150ns.....	3.35	3.00	2.85
6116 150ns Lower power.....	4.90	4.40	4.20
2708 450ns.....	3.25	2.95	2.80
2716 450ns 5-volt.....	2.69	2.40	2.00
2716 450ns three-rail.....	5.75	5.00	4.65
2732 450ns Intel type.....	3.45	3.05	2.95
2532 450ns Texas type.....	3.85	3.45	3.30
2764 250ns.....	4.69	4.19	3.99
27128 300ns.....	12.75	11.25	10.85

Z80A-CPU.....£2.99	Z80A-PIO.....£2.99	Z80A-CTC.....£2.99
6522 PIA.....£3.70	7805 reg. £0.50	7812 reg.....£0.50

Low-profile IC sockets:	Pins	8	14	16	18	20	22	24	28	40
Texas solder-tail:	Pence	12	13	14	16	18	22	24	27	38

Soft-sectored floppy discs per 10 in plastic library case:

5-inch SSSD £17.00	5-inch SSDD £19.25	5-inch DSDD £21.00
	5-inch DSQD £26.35	
8-inch SSSD £19.25	8-inch SSDD £23.65	8-inch DSDD £25.50

74LS Series TTL: Large stocks at low prices with D.I.Y. discounts starting at a mix of just 25 pieces. Write or phone for list.

Please add 50p post and packing to orders under £15 and V.A.T. to total  
 Access and Visa welcome : 24-hour phone service on 054-422 618  
 Government and Educational orders welcome : £15 minimum  
 Trade accounts operated - phone or write for details

**HAPPY MEMORIES (WW)**  
 Gladestry, Kington  
 Herefordshire HR5 3NY  
 Tel: (054 422) 618 or 628



**FFD have moved...  
 back to Wardour Street!**

**FFD FUTURE FILM DEVELOPMENTS**  
 114 Wardour Street, London W1V 3LP England. Telephone: 01-434 3344 & 01-437 1892.  
 Telex: 21624 ALOFFD G. Cables: Allotrope-London W1.

WW - 025 FOR FURTHER DETAILS

# Electronic Brokers Test Equipment DISTRIBUTORS

"For detailed specifications of our complete range send for our new catalogue."

**PHILIPS**



**Philips PM 2517X Handheld DMM £172**

Multi-function, 4 digit autoranging with manual override. True RMS to 10Amp. Battery operation. Optional accessories extend measurement capabilities.

**Philips PM 3207 15MHz Oscilloscope £385**

Tough light-weight portable for field service work with big screen. Dual trace, TV triggering, X-Y operation, add and invert.



**Philips PM 5107 Function Generator £295**

Designed for audio and educational applications. Low distortion LF generator 10Hz to 100kHz, sine and square waveforms. TTL output.



**Philips PM5503 Pattern Generator**

£139 Small, light-weight for TV servicing. Five different test patterns for colour and monochrome. Tone for audio checking. Video output.



**Philips PM 6667/01 Frequency Counter £290**

High resolution 7 digit computing counter from 10Hz to 120MHz. Auto ranging on all waveforms. PM 6668/01 (£425) performs to 1GHz.

**FLUKE**

**New Fluke 70 series Analog/Digital Handheld Meters** All meters have 3 year warranty, all feature measurement functions of volts, ohms, amps and diode test.


**JF 73 £65** DC accuracy 0.7% Autoranging

**JF 75 £75** DC accuracy 0.5% Auto/manual ranging

**JF 77 £95** DC accuracy 0.3% Touch hold function Multi purpose holster





**HAMEG**

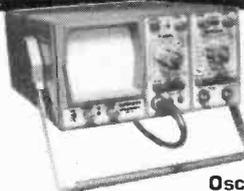

**Hameg HM 103 10MHz Oscilloscope £158** Single trace, suitable for field service or home constructor. Two year warranty applies to this and all Hameg instruments.

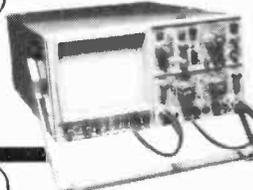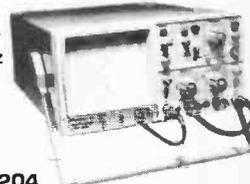**Hameg HM 203-4 20MHz Oscilloscope £264**


Dual trace for general purpose applications in industry and education. X-Y operation, TV triggering, add/invert and component tester.



**Hameg HM 204 20MHz Oscilloscope £365** High performance instrument with sweep delay. Versatile triggering to 50MHz, variable hold off control, Z modulation and internal illuminated graticule.

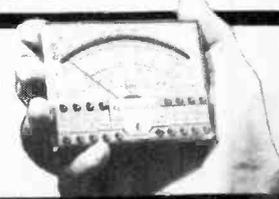**ICE**

**I.C.E. Microtest 80 Multimeter £19** Compact meter in robust case. 40 ranges of measurement with high sensitivity and accuracy. Large range of inexpensive accessories.



ADD 15% VAT TO ALL PRICES Carriage and Packing extra

**Electronic Brokers Ltd., 61/65 Kings Cross Road,  
 London WC1X 9LN. Tel: 01-8331166. Telex 298694**



Electronic Brokers

WW - 076 FOR FURTHER DETAILS


# HIGH QUALITY GREEN SCREEN VIDEO MONITORS

Designed for use with Professional and Personal Microcomputers where a high resolution display is required. Ideal for applications requiring 80 column mode or higher, high resolution graphics, etc.

CHECK THESE FEATURES:-

- ANTIGLARE SCREEN
- P31 GREEN FOR MINIMUM FATIGUE
- VIDEO RESPONSE 10Hz - 22MHz  $\pm$  3db
- SUPERB RESOLUTION - UP TO 132 CHARS/LINE
- EXCELLENT GEOMETRY/LINEARITY
- HIGH STABILITY
- 230 VOLT 50Hz MAINS OPERATION
- COMPOSITE VIDEO 0.5/2.0V INPUT
- FLICKER FREE DISPLAY

**£89**

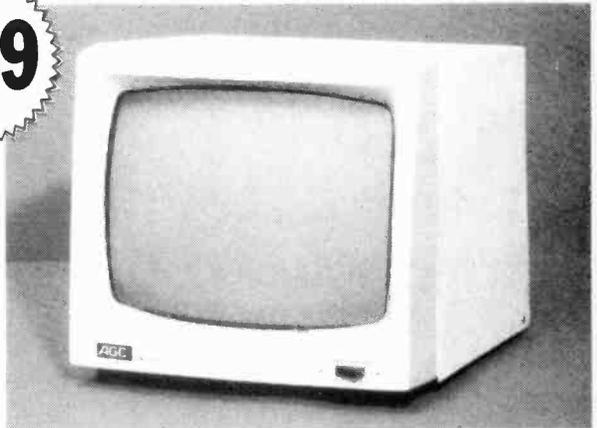

▲ 12" MODEL HM123

**£87**



▲ 9" MODEL HM910

ADD £5  
Carriage/Postage

DEALER  
ENQUIRIES  
WELCOME

**£85**



▲ 9" MODEL HM911

## THE LOWEST PRICE ANYWHERE

**£389**



FOR A PC WITH THESE FEATURES... LOOK AT THE SPEC. OF THE AMAZING UNITRON 2200...

- Dual processors - 6502 and Z80
- 64K of RAM
- 24K ROM with softswitch control
- Selectable 80 or 40 column text display
- Detachable keyboard
- Apple® II-compatible
- CP/M® compatible
- High and low resolution graphics capabilities
- Two disk I/O for your disk drives
- Game paddles/cassette/video interfaces

Prices exclusive of VAT  
Same day despatch. Access welcome.

### CHILTERN ELECTRONICS

HIGH STREET, CHALFONT ST. GILES, BUCKS. HP84QH  
TELEPHONE: 02407 71234 TELEX: 262284

ADD £9 Carriage/Insurance



TYPE 9051



TYPE 9046

**VMOS WIDEBAND LINEAR POWER AMPLIFIERS.** 4 watts RF output. Without tuning. Power gain 10 dB. 24V+ supply

TYPE 9046 100 KHz.-100 MHz .....£64.50+£3.50 p&p  
TYPE 9051 20 MHz.-200 MHz .....£64.50+£3.50 p&p




TYPE 9152



TYPE 9159

**TELEVISION LINEAR POWER AMPLIFIERS.** Tuned to your specified channels in bands IV or V

TYPE 9061 150 mV. input, 10 mW. output .....£120+£5 p&p  
TYPE 9152 10 mW. input, 500 mW. output .....£160+5 p&p  
TYPE 9159 500 mW. input, 5 watts output .....£180+£5 p&p

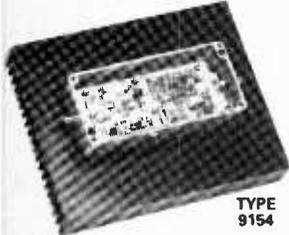

TYPE 9154



TYPE 9157

**VMOS LINEAR POWER AMPLIFIERS.** Tuned to your specified frequency in the range 10-250 MHz

TYPE 9154 200 mW. - 2 watts input, 20 watts output .....£180+£10 p&p  
TYPE 9160 As above with integral mains power supply unit .....£240+£15 p&p  
TYPE 9168 8 watts input, 80 watts output .....£240+£10 p&p  
TYPE 9157 As above with integral mains power supply unit .....£295+£15 p&p  
TYPE 9086 FM TRANSMITTER 88-108 MHz. 50 watts RF output. 24V+ supply. Complete modular system .....£380+£20 p&p  
TYPE 9087 As above with integral mains power supply unit .....£440+£25 p&p



TYPE 9010

**TWO STAGE GASFET STRIPLINE PREAMPLIFIERS**  
Tuned to your specified channels in bands IV or V

TYPE 9002 Two stage Gasfet preamplifier. N.F. 0.7 dB. Gain 25 dB. High Q filter. 15V. + DC .....£85+£2 p&p  
TYPE 9004 UHF two stage Gasfet preamplifier. N.F. 0.6 dB. Gain 25 dB. Aligned to your specified frequency in the range 250-500 MHz. High Q filter. 15V. + DC .....£85+£2 p&p  
TYPE 9012 Gasfet preamplifier mains power supply unit .....£24.50+£3 p&p  
TYPE 9010 Masthead weatherproof unit .....£6.50+£2 p&p



TYPE 9026



TYPE 9035

**GASFET/MOSFET RF PREAMPLIFIERS.** Aligned to your specified frequency in the range 30-250 MHz. Masthead/local use

TYPE 9026 N.F. 1.0 dB. Gain 10-40 dB. variable .....£39.50+£2 p&p  
TYPE 9026FM As above. Band II 88-108 MHz .....£39.50+£2 p&p  
TYPE 9006 Gasfet. N.F. 0.6 dB. Gain 10-40 dB. variable .....£85+£2 p&p  
TYPE 9035 Mains power supply unit for above types .....£24.50+£3 p&p



TYPE 8034

TYPE 8034 PHASE LOCKED SIGNAL SOURCE using low frequency reference crystal. Specify output in the range 1-600 MHz. Output 10 mW. + 10 dBm .....£79.50+£2 p&p  
TYPE 9113 TELEVISION FREQUENCY CONVERTER. Changes channels in the range 40-1000 MHz .....£242+£5 p&p  
TYPE 9056 1500 MHz. PRESCALER. Divides 100-1500 MHz. by 10 .....£69.50+£2 p&p

## RESEARCH COMMUNICATIONS LTD.

UNIT 3, DANE JOHN WORKS, GORDON ROAD, CANTERBURY, KENT CT1 3PP  
TELEPHONE: CANTERBURY (0227) 56489

PLEASE ADD 15% V.A.T. ON TOTAL

WW - 034 FOR FURTHER DETAILS

# THE CHANGING FACE OF ELECTREX ELECTREX '84

Have you noticed how each ELECTREX exhibition foreshadows the way the international electrotechnical industry is heading?

ELECTREX is the industry's exhibition attended by industry as a whole. And the reason?

## AT ELECTREX YOU'LL SEE ...

Automation, control and instrumentation and their interaction with tomorrow's communication systems, are featured predominantly. Electronic components, microprocessor-based equipment, the latest advances in cabling, trunking, power distribution systems and lighting are all there. Power generation and transmission developments are all on display.

The whole gamut of the industrial electrical and electronic industry is there pointing the way ahead, whether as a visitor or an exhibitor.

Your company's future is at Electrex!

The 1984 show is bigger than ever.

For further information please mail the coupon.

## ...SEE YOU AT ELECTREX!



**XXII INTERNATIONAL  
ELECTROTECHNICAL  
EXHIBITION**

## A 30,000 SQUARE METRES MARKET PLACE OF CONCENTRATED TECHNOLOGY



**FEBRUARY 27 - MARCH 2**  
**NATIONAL EXHIBITION CENTRE, BIRMINGHAM**

Please send further information

NAME: .....

COMPANY: .....


ADDRESS: .....

Send to: Electrex Limited, Wix Hill House, West Horsley, Surrey, KT24 6DZ, U.K.  
or: Telephone Guildford (0483) 222888, Telex 859460

WW - 016 FOR FURTHER DETAILS
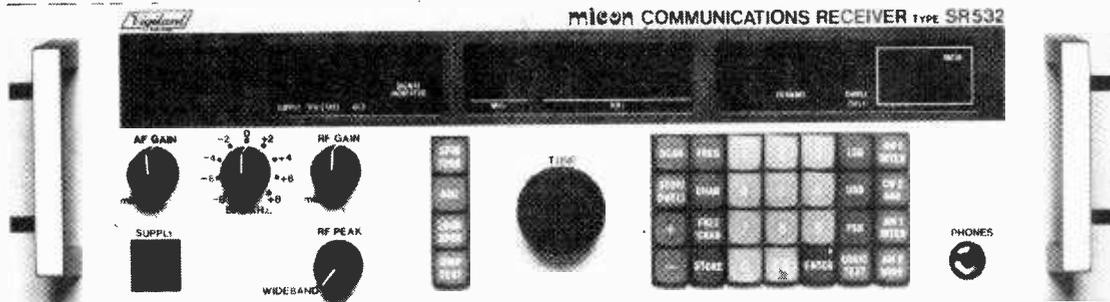
# Vigilant **micon** HF Communications Receivers MICROPROCESSOR CONTROLLED RECEIVERS

Type SR 530 USB/CW/AM/Telex – 10 Hz Steps (Marine)  
Type SR 532 USB/LSB/AM/CW – 10 Hz Steps (Static/Transportable)  
Type SR 531 USB/LSB/AM/CW – 100 Hz Steps (Static/Transportable)



DESIGNED AND MANUFACTURED TO HIGHEST INTERNATIONAL SPECS

Freq. Range : 50 KHz to 30 MHz  
Increments : 10 Hz or 100 Hz Steps  
Stability :  $\pm 1$  Part in  $10^7/^\circ\text{C}$   
Tuning : Keypad and Spin Wheel  
Power Supplies : 110/240V AC and 24V DC  
FULLY MODULAR 'PLUG IN' CONSTRUCTION

Memory : 200 Channels Freq/Mode/Filter  
Scanning : Full memory or discreet parts  
Automatic or Manual Stop  
Manual step on or Reverse  
Dwell : Variable from Keypad 1 to 9 seconds  
KEYPAD FUNCTIONS INDICATED BY DISPLAYS

NOW AVAILABLE AT HIGHLY COMPETITIVE PRICES

Send for Technical Brochure to: **Vigilant Communications Ltd.**  
Unit 5, Pontiac Works, Fernbank Road, Ascot, Berks SL5 8JH, England  
Tel: (0344) 885656  
Telex: 849769 Vigcom G

WW - 006 FOR FURTHER DETAILS

## FREQUENCY COUNTERS

HIGH PERFORMANCE  
HIGH RELIABILITY  
LOW COST


The brand new Meteor series of 8-digit Frequency Counters offer the lowest cost professional performance available anywhere.

- ★ Measuring typically 2Hz – 1.2GHz
- ★ Sensitivity <50mV at 1GHz
- ★ Setability 0.5ppm
- ★ High Accuracy
- ★ 3 Gate Times
- ★ Low Pass Filter
- ★ Battery or Mains
- ★ Factory Calibrated
- ★ 1-Year Guarantee
- ★ 0.5" easy to read L.E.D. Display

PRICES (Inc. adaptor/charger, P & P and VAT)

METEOR 100	(100MHz)	£104.36
METEOR 600	(600MHz)	£134.26
METEOR 1000	(1GHz)	£184.36

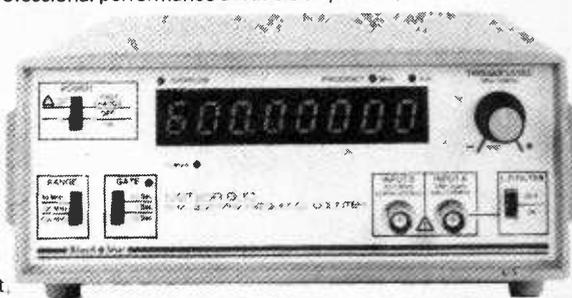Illustrated colour brochure  
with technical specification  
and prices available on request.




Designed and  
manufactured  
in Britain

**Black★Star**

BLACK STAR LTD, 9A Crown Street, St Ives,  
Huntingdon, Cambs, PE17 4EB, England,  
Tel: (0480) 62440 Telex: 32339

WW - 032 FOR FURTHER DETAILS

## METER PROBLEMS?

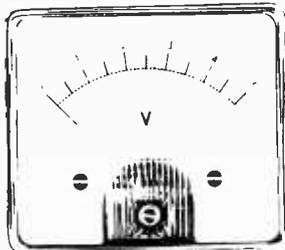

137 Standard Ranges in a variety of sizes and stylings available  
for 10-14 days' delivery. Other Ranges and special scales can be  
made to order.

Full Information from:

**HARRIS ELECTRONICS (London)**

138 GRAY'S INN ROAD, W.C.1  
Phone: 01-837 7937  
Telex: 892301

WW - 026 FOR FURTHER DETAILS

## RECHARGEABLE BATTERIES

PRIVATE & TRADE ENQUIRIES WELCOME

Full range of Ni-Cads to replace 1.5 volt dry cells and 9  
volt PP type batteries. S.A.E. for lists and prices. £1.45  
for booklet, "Nickel Cadmium Power." Sealed lead  
range stocked

★ TRADE PRICES FOR SCHOOLS AND COLLEGES ★

**Sandwell Plant Ltd, 656 Chester Road**  
Erdington, Birmingham B23 5TE


Tel. 021-373 9487

After hours Lichfield 57977

Southern Office - Hitchin 733254

# Marconi Type R1020 Hinged Antenna Column.

## Easy to raise Easy to lower

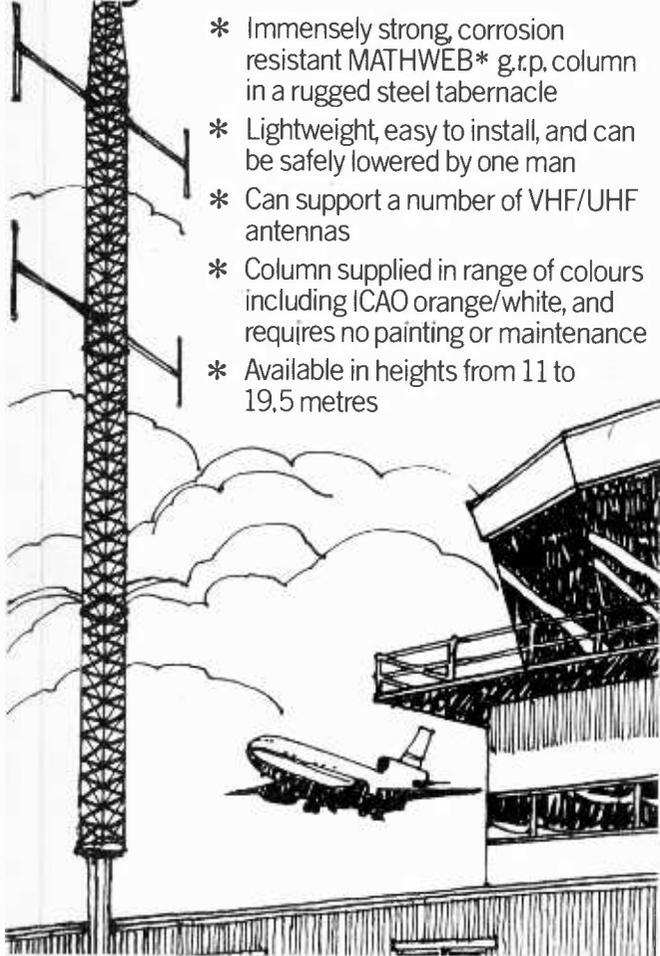

- \* Immensely strong, corrosion resistant MATHWEB\* g.r.p. column in a rugged steel tabernacle
- \* Lightweight, easy to install, and can be safely lowered by one man
- \* Can support a number of VHF/UHF antennas
- \* Column supplied in range of colours including ICAO orange/white, and requires no painting or maintenance
- \* Available in heights from 11 to 19.5 metres

### OTHER MARCONI SUPPORT STRUCTURES

Include the MATHWEB\* Lattice Antenna Mast Type R1010, and the Triangular Section Tubular Steel Self Supporting Tower Type R1060.

For more information talk to Chris Pettitt, Marketing Manager, Antenna Systems Division.

\* MATHWEB is a registered trademark of the BP Group

# Marconi

Communication Systems



Antenna Systems Division  
Marconi Communication Systems Limited,  
Lane Works, Waterhouse Lane, Chelmsford CM1 2QX, England  
Tel: 0245 67111 Telex: 99201

A GEC-Marconi Electronics Company

WW - 012 FOR FURTHER DETAILS

# MIDWICH

## COMPUTER COMPANY LIMITED

RICKINGHALL HOUSE, HINDERCLAY ROAD, RICKINGHALL, SUFFOLK IP22 1HH. TEL. DISS (0379) 898751.

### BBC Microcomputers

Model B	348.26
Model B + Disc Int	433.21
NB Credit cards are not accepted in payment for BBC Microcomputers	

### BBC Micro Econet

Full range of products available. Installation service available

### BBC Compatible Disc Drives

Cased drives, finished to match the BBC Micro are supplied complete with connecting cables, manual and utilities disc.

All single cased drives may be expanded to dual configuration by the addition of the appropriate uncased mechanism.

Disc capacity	Single	Dual	Uncased
100K 40T	175.00	315.00	140.00
200K 40T D.S.	225.00	420.00	195.00
400K 40/80T D.S.	285.00	525.00	240.00

Trade/quantity discounts are available

BBC3 Disc Interface 84.95  
Please send for our BBC Micro price list. Full range of accessories available

### Memories

2114L-20	D1	0.92
4116-15	D2	1.05
4116-20	D2	0.88
4118-15	D1	3.75
4164-15	D2	4.33
4164-20	D2	3.95
4416-20	D2	6.60
4564-15	D1	5.25
5516-25	D1	7.73
6116-3	D1	3.72
6116-LP3	D2	4.67
2532-45	D2	3.50
2708-45	D2	3.25
2716-35	D1	4.50
2716-45	D1	3.50
2716-3	D1	4.50
2732-35	D1	4.58
2732-45	D1	3.75
2764-30	D1	3.92
2764-25ONS TI	D1	3.92
2764-25ONS BBC	D1	5.95
2564-30	D2	6.00
2712B-30	D2	24.50

### Buffers

81LS95	0.95
81LS96	0.95
81LS97	0.95
81LS98	0.95
8T26A (6890AP)	0.78
8T28A (6889)	0.78
8T35 (6885)	0.78
8T97A (6887)	0.78
8T98 (6888)	0.78

### Data Converters

ZN435	D1	3.70
UPD7002	D1	4.65
ZN425E-8	D1	3.13
ZN425E-8	D1	1.67
ZN427E-8	D1	5.75
ZN428E-8	D1	4.38
ZN429E-8	D1	1.33
ZN432CJ-10	D1	25.98
ZN432E-10	D1	10.88
ZN433CJ-10	D1	20.98
ZN440	D1	47.43
ZN447	D1	6.70
ZN448	D1	5.75
ZN449	D1	2.35
ZN441	D1	40.32

### Crystals

A111B 1MHz	4.22
A112A 1.008MHz	3.42
A113A 1.8432MHz	2.88
A116A 2.4576MHz	1.00
A169A 3.6864MHz	1.55
A120B 4MHz	0.85
A132A 6MHz	0.72
A140A 8MHz	1.00
A173A 9.8304MHz	1.40
A182A 19.6608MHz	2.07

### UHF Modulators

UM1111 6MHz	2.17
UM1233 8MHz	3.25

### Floppy Disc Controllers

8271P	53.33	
FD1771P	D5	21.25
FD1791	D6	17.00
FD1793	D6	17.00
FD1795	D6	24.35
FD1797	D6	24.35
WD1691	D2	12.00
WD2143 01	D2	7.90

### 8080 Family

8085A	D4	3.07
8212	D1	1.50
8216	D1	1.37
8224	D1	1.92
8228	D1	3.25
8251A	D5	5.33
8253	D5	3.33
8255A	D5	2.50

### 8088 Family

8088A	D4	3.07
8212	D1	1.50
8216	D1	1.37
8224	D1	1.92
8228	D1	3.25
8251A	D5	5.33
8253	D5	3.33
8255A	D5	2.50

### 8080 Family

8080	D3	4.40
8502A	D3	4.67
8520	D1	2.67
8520A	D1	2.80
8522	D5	3.47
8522A	D5	4.40
8532	D2	3.33
8532A	D2	5.87

### 6500 Family

SN75454BP	0.24
SN75468N	1.08
SN75491AN	0.46
SN75492AN	0.61
TL010CP	0.38
TL061CLP	0.28
TL062CP	0.47
TL064CN	0.83
TL066CP	0.28
TL071CP	0.28
TL072CP	0.47
TL074CN	0.91
TL081CP	0.24
TL082CP	0.41
TL084CN	0.85
TL091CP	0.41
TL092CP	0.60
TL094CN	1.37
TL487CP	0.55
TL489CP	0.55
TL494CN	1.66
TL496CP	0.30
TL507CP	1.02
ZN450E	5.25
ZN451E	6.38
ZN451KIT	25.65

### Linear & Interface

#### Devices

6402	D2	6.00
AY3-1015	D2	2.92
AY3-1270	D2	6.50
AY3-8910	D6	4.48
AY5-3600	D2	7.37
DP8304	D1	1.92
LM203	0.80	
LM300	3.17	
LM301AN	0.24	
LM308AN	0.73	
LM308N	0.47	
LM311N	0.84	
LM319	2.23	
LM324N	0.32	
LM339N	0.37	
LM348N	0.53	
LM358N	0.28	
LM393N	0.34	
LM725CN	1.33	
LM741CP	0.18	
LM747CP	0.48	
LM748CP	0.22	
MC1413P	D1	0.66
MC1416	D1	0.66
MC1458CPL	0.26	
MC1495L	7.13	
MC1496P	0.65	
MC1723P	0.32	
MC3242A	5.25	
MC3302P	0.40	
MC3340P	1.93	
MC3357P	1.56	
MC3423PL	0.67	
MC3441AP	2.40	
MC3446AP	D1	2.40
MC3447P	3.58	
MC3448AP	D1	3.32
MC3470P	5.23	
MC3480P	D5	6.47
MC3487P	D1	1.50
MC14411	D1	8.52
NE555P	0.19	
NE556CP	0.45	
RO3-2513L	D1	7.82
RO3-2513U	D1	7.82
SN75107BN	0.58	
SN75110AN	0.68	
SN75150P	0.72	
SN75154N	1.87	
SN75158N	0.19	
SN75160AN	2.15	
SN75161AN	2.35	
SN75162AN	3.31	
SN75172NG	1.64	
SN75173N	1.21	
SN75174	1.64	
SN75175	1.21	
SN75182	0.62	
SN75183	0.62	
SN75188	0.44	
SN75189	C.44	
SN75451BP	0.24	
SN75452BP	0.24	
SN75453BP	0.24	

### DIL Sockets

Pin	Tin	Gold	W/W
8	0.10	0.24	0.58
14	0.12	0.28	0.77
16	0.13	0.32	0.86
18	0.16	0.32	1.08
20	0.17	0.41	1.23
22	0.17	0.48	1.31
24	0.20	0.63	1.44
28	0.23	0.57	1.59
40	0.33	0.99	1.96

### ZIF Sockets

24 Pin	5.80
28 Pin	6.35
40 Pin	8.45

### Data sheets are available on items marked D.

Prices are as follows

D1	0.75	D5	2.50
D2	1.00	D6	3.00
D3	1.25	D7	4.00
D4	2.00		

A full range of the following products is listed in stock and is carried in our FREE catalogue

- \* 741S Series TTC
- \* 4000 Series CMOS
- \* TI Bipolar Memories
- \* 9900 Series Micros
- \* Crystals
- \* IDC, Card Edge & D-Type Connectors
- \* Dip Jumpers
- \* Monochrome & Colour Monitors (NEC & KAGA)
- \* Eeprom Programmers
- \* Data Sets
- \* Custom Cable Assemblies

### SPECIAL OFFER: SPECTRUM

32K UPGRADE KIT £24.95

Carriage Orders up to £199 are sent by 1st class post and £200+ by Securicor

£0.1000 50 £100-£199 | 25 £200+ 5.00 by Securicor

Prices quoted (+ carriage charges) are exclusive of VAT and are subject to change without notice

Quantity Discounts are available on many products, please ring for details.

Official Orders are welcome from Education Establishments, Government Bodies and Public Companies

Credit Accounts are available to others subject to status. Payment is due strictly net by the 15th of the month.

Credit Cards are accepted (Access and Visa) for telephone and postal orders and NO SURCHARGE is made

Out of stock items will follow automatically, at our discretion, or a refund will be given if requested.



**SPECIAL TELEPHONE NUMBER FOR FAST, IMMEDIATE SERVICE, TELEPHONE YOUR ORDER TO: DISS (0379) 898751**

### Prices: all prices

exclude V.A.T. and

carriage. Please add

these to your order.

All prices correct at

time of going to press.

For FREE CATALOGUE post to Midwich Computer Company Limited, Rickingham House, Hinderclay Road, Rickingham, Suffolk IP22 1HH

Name

Address


Telephone

WW

WW - 022 FOR FURTHER DETAILS
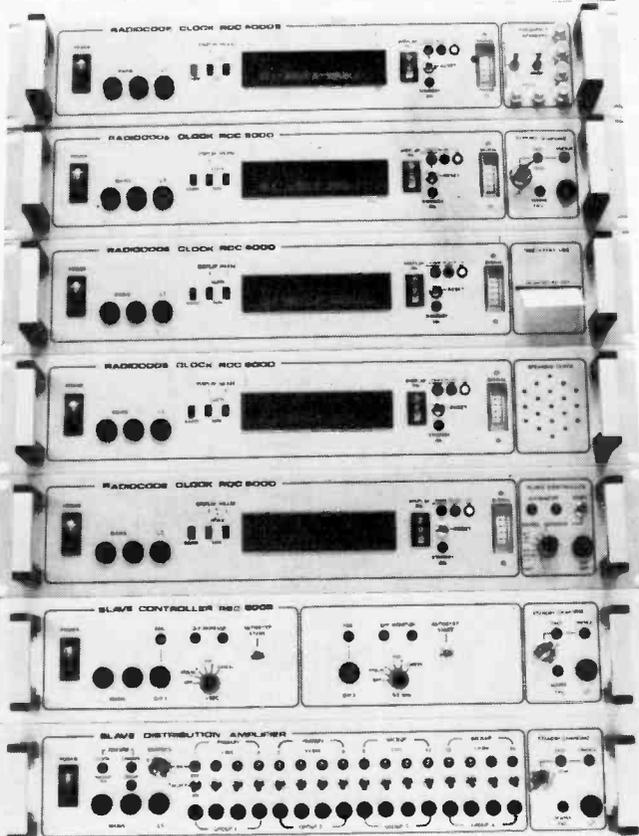
# RADIOCODE CLOCKS SOLVE PROBLEMS

ATOMIC TIME, FREQUENCY AND SYNCHRONISATION EQUIPMENT



## NEW PHASE-MODULATION SYSTEMS

Until recently, atomic time and date information was only available on v.l.f. transmissions using amplitude modulation. The RCC 8000AM series of equipment uses these transmissions to offer high noise immunity and high accuracy, particularly at very long range.

The new RCC 8000PM series of equipment uses, for the first time, phase modulated transmissions with massive radiated powers of up to 2 Mega-Watts to offer long range, excellent noise immunity and no scheduled maintenance periods.

## NEW PRODUCTS

The AM and PM series of Radiocode Clock equipment has been further expanded to include seven new models (from top) 8000S - combined clock, frequency standard and optional stopclock. **Internal standby power supply** - with dual rate constant current charger. **Time-event log** - prints hours, minutes, seconds, milliseconds and day of year, on receipt of a log pulse. **Speaking clock** - time announcement or audio recording. **Slave controller** - total control of single-standard master/slave systems ie one pulse/sec. **Dual standard slave controller** - total control of two different and independent slave systems, ie. one pulse/sec and one pulse/half min. **Slave distribution amplifier** - maximum flexibility for the largest master/slave installations requiring dual standard operation, multiple circuits and complete master/slave backup.

## NEW OPTIONS

A continuously expanding range of fully integrated software and hardware is available for both series of Radiocode Clock equipment. Standard options now include:

- IRIG B precision serial o/p
- RS232/V24 1mS resolution
- General purpose parallel o/p
- FSK record/replay system
- Keypad entry of alarm times
- Keypad entry of time/date
- Time code generators
- Intelligent slave systems
- Standard frequency outputs
- Stopclock operation
- Calibrated systems for increased accuracy

Radiocode Clocks Ltd\*

Unit 19, Parkengue, Kernick Road Industrial Estate  
Penryn, Falmouth, Cornwall. Tel: Falmouth (0326) 76007


(\*A Circuit Services Associate Co.)

WW - 013 FOR FURTHER DETAILS
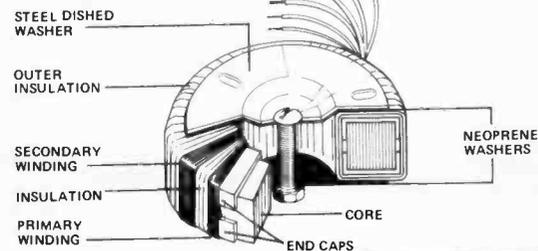
# TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our **SPECIAL DESIGN** section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



15 VA 62 x 34mm Regulation 19%	50 VA 80 x 35mm Regulation 13%	120 VA 90 x 40mm Regulation 11%	225 VA 110 x 45mm Regulation 7%	500 VA 140 x 60mm Regulation 4%																																																																																																																																																																														
<table border="1"> <tr><th>SERIES</th><th>SECONDARY No</th><th>Volts</th><th>RMS Current</th></tr> <tr><td>0x010</td><td>6+6</td><td>1.25</td><td></td></tr> <tr><td>0x011</td><td>9+9</td><td>0.83</td><td></td></tr> <tr><td>0x012</td><td>12+12</td><td>0.63</td><td></td></tr> <tr><td>0x013</td><td>15+15</td><td>0.50</td><td></td></tr> <tr><td>0x014</td><td>18+18</td><td>0.42</td><td></td></tr> <tr><td>0x015</td><td>22+22</td><td>0.34</td><td></td></tr> <tr><td>0x016</td><td>25+25</td><td>0.30</td><td></td></tr> <tr><td>0x017</td><td>30+30</td><td>0.25</td><td></td></tr> </table>	SERIES	SECONDARY No	Volts	RMS Current	0x010	6+6	1.25		0x011	9+9	0.83		0x012	12+12	0.63		0x013	15+15	0.50		0x014	18+18	0.42		0x015	22+22	0.34		0x016	25+25	0.30		0x017	30+30	0.25		<table border="1"> <tr><th>2x010</th><th>6+6</th><th>4.16</th></tr> <tr><td>2x011</td><td>9+9</td><td>2.77</td></tr> <tr><td>2x012</td><td>12+12</td><td>2.08</td></tr> <tr><td>2x013</td><td>15+15</td><td>1.66</td></tr> <tr><td>2x014</td><td>18+18</td><td>1.38</td></tr> <tr><td>2x015</td><td>22+22</td><td>1.13</td></tr> <tr><td>2x016</td><td>25+25</td><td>1.00</td></tr> <tr><td>2x017</td><td>30+30</td><td>0.83</td></tr> <tr><td>2x028</td><td>110</td><td>0.45</td></tr> <tr><td>2x029</td><td>220</td><td>0.22</td></tr> <tr><td>2x030</td><td>240</td><td>0.20</td></tr> </table>	2x010	6+6	4.16	2x011	9+9	2.77	2x012	12+12	2.08	2x013	15+15	1.66	2x014	18+18	1.38	2x015	22+22	1.13	2x016	25+25	1.00	2x017	30+30	0.83	2x028	110	0.45	2x029	220	0.22	2x030	240	0.20	<table border="1"> <tr><th>4x010</th><th>6+6</th><th>10.00</th></tr> <tr><td>4x011</td><td>9+9</td><td>6.66</td></tr> <tr><td>4x012</td><td>12+12</td><td>5.00</td></tr> <tr><td>4x013</td><td>15+15</td><td>4.00</td></tr> <tr><td>4x014</td><td>18+18</td><td>3.33</td></tr> <tr><td>4x015</td><td>22+22</td><td>2.72</td></tr> <tr><td>4x016</td><td>25+25</td><td>2.40</td></tr> <tr><td>4x017</td><td>30+30</td><td>2.00</td></tr> <tr><td>4x018</td><td>35+35</td><td>1.71</td></tr> <tr><td>4x028</td><td>110</td><td>1.09</td></tr> <tr><td>4x029</td><td>220</td><td>0.54</td></tr> <tr><td>4x030</td><td>240</td><td>0.50</td></tr> </table>	4x010	6+6	10.00	4x011	9+9	6.66	4x012	12+12	5.00	4x013	15+15	4.00	4x014	18+18	3.33	4x015	22+22	2.72	4x016	25+25	2.40	4x017	30+30	2.00	4x018	35+35	1.71	4x028	110	1.09	4x029	220	0.54	4x030	240	0.50	<table border="1"> <tr><th>6x012</th><th>12+12</th><th>9.38</th></tr> <tr><td>6x013</td><td>15+15</td><td>7.50</td></tr> <tr><td>6x014</td><td>18+18</td><td>6.25</td></tr> <tr><td>6x015</td><td>22+22</td><td>5.11</td></tr> <tr><td>6x016</td><td>25+25</td><td>4.50</td></tr> <tr><td>6x017</td><td>30+30</td><td>3.75</td></tr> <tr><td>6x018</td><td>35+35</td><td>3.21</td></tr> <tr><td>6x026</td><td>40+40</td><td>2.81</td></tr> <tr><td>6x025</td><td>45+45</td><td>2.50</td></tr> <tr><td>6x033</td><td>50+50</td><td>2.25</td></tr> <tr><td>6x028</td><td>110</td><td>2.04</td></tr> <tr><td>6x029</td><td>220</td><td>1.02</td></tr> <tr><td>6x030</td><td>240</td><td>0.93</td></tr> </table>	6x012	12+12	9.38	6x013	15+15	7.50	6x014	18+18	6.25	6x015	22+22	5.11	6x016	25+25	4.50	6x017	30+30	3.75	6x018	35+35	3.21	6x026	40+40	2.81	6x025	45+45	2.50	6x033	50+50	2.25	6x028	110	2.04	6x029	220	1.02	6x030	240	0.93	<table border="1"> <tr><th>8x016</th><th>25+25</th><th>10.00</th></tr> <tr><td>8x017</td><td>30+30</td><td>8.33</td></tr> <tr><td>8x018</td><td>35+35</td><td>7.14</td></tr> <tr><td>8x026</td><td>40+40</td><td>6.25</td></tr> <tr><td>8x025</td><td>45+45</td><td>5.55</td></tr> <tr><td>8x033</td><td>50+50</td><td>5.00</td></tr> <tr><td>8x042</td><td>55+55</td><td>4.54</td></tr> <tr><td>8x028</td><td>110</td><td>4.54</td></tr> <tr><td>8x029</td><td>220</td><td>2.27</td></tr> <tr><td>8x030</td><td>240</td><td>2.08</td></tr> </table>	8x016	25+25	10.00	8x017	30+30	8.33	8x018	35+35	7.14	8x026	40+40	6.25	8x025	45+45	5.55	8x033	50+50	5.00	8x042	55+55	4.54	8x028	110	4.54	8x029	220	2.27	8x030	240	2.08
SERIES	SECONDARY No	Volts	RMS Current																																																																																																																																																																															
0x010	6+6	1.25																																																																																																																																																																																
0x011	9+9	0.83																																																																																																																																																																																
0x012	12+12	0.63																																																																																																																																																																																
0x013	15+15	0.50																																																																																																																																																																																
0x014	18+18	0.42																																																																																																																																																																																
0x015	22+22	0.34																																																																																																																																																																																
0x016	25+25	0.30																																																																																																																																																																																
0x017	30+30	0.25																																																																																																																																																																																
2x010	6+6	4.16																																																																																																																																																																																
2x011	9+9	2.77																																																																																																																																																																																
2x012	12+12	2.08																																																																																																																																																																																
2x013	15+15	1.66																																																																																																																																																																																
2x014	18+18	1.38																																																																																																																																																																																
2x015	22+22	1.13																																																																																																																																																																																
2x016	25+25	1.00																																																																																																																																																																																
2x017	30+30	0.83																																																																																																																																																																																
2x028	110	0.45																																																																																																																																																																																
2x029	220	0.22																																																																																																																																																																																
2x030	240	0.20																																																																																																																																																																																
4x010	6+6	10.00																																																																																																																																																																																
4x011	9+9	6.66																																																																																																																																																																																
4x012	12+12	5.00																																																																																																																																																																																
4x013	15+15	4.00																																																																																																																																																																																
4x014	18+18	3.33																																																																																																																																																																																
4x015	22+22	2.72																																																																																																																																																																																
4x016	25+25	2.40																																																																																																																																																																																
4x017	30+30	2.00																																																																																																																																																																																
4x018	35+35	1.71																																																																																																																																																																																
4x028	110	1.09																																																																																																																																																																																
4x029	220	0.54																																																																																																																																																																																
4x030	240	0.50																																																																																																																																																																																
6x012	12+12	9.38																																																																																																																																																																																
6x013	15+15	7.50																																																																																																																																																																																
6x014	18+18	6.25																																																																																																																																																																																
6x015	22+22	5.11																																																																																																																																																																																
6x016	25+25	4.50																																																																																																																																																																																
6x017	30+30	3.75																																																																																																																																																																																
6x018	35+35	3.21																																																																																																																																																																																
6x026	40+40	2.81																																																																																																																																																																																
6x025	45+45	2.50																																																																																																																																																																																
6x033	50+50	2.25																																																																																																																																																																																
6x028	110	2.04																																																																																																																																																																																
6x029	220	1.02																																																																																																																																																																																
6x030	240	0.93																																																																																																																																																																																
8x016	25+25	10.00																																																																																																																																																																																
8x017	30+30	8.33																																																																																																																																																																																
8x018	35+35	7.14																																																																																																																																																																																
8x026	40+40	6.25																																																																																																																																																																																
8x025	45+45	5.55																																																																																																																																																																																
8x033	50+50	5.00																																																																																																																																																																																
8x042	55+55	4.54																																																																																																																																																																																
8x028	110	4.54																																																																																																																																																																																
8x029	220	2.27																																																																																																																																																																																
8x030	240	2.08																																																																																																																																																																																
<table border="1"> <tr><th>30 VA 70 x 30mm Regulation 18%</th><th>80 VA 90 x 30mm Regulation 12%</th><th>160 VA 110 x 40mm Regulation 8%</th><th>300 VA 110 x 50mm Regulation 6%</th><th>625 VA 140 x 75mm Regulation 4%</th></tr> <tr><td>1x010</td><td>3x010</td><td>5x011</td><td>7x013</td><td>9x017</td></tr> <tr><td>1x011</td><td>3x011</td><td>5x012</td><td>7x014</td><td>9x018</td></tr> <tr><td>1x012</td><td>3x012</td><td>5x013</td><td>7x015</td><td>9x026</td></tr> <tr><td>1x013</td><td>3x013</td><td>5x014</td><td>7x016</td><td>9x025</td></tr> <tr><td>1x014</td><td>3x014</td><td>5x015</td><td>7x017</td><td>9x033</td></tr> <tr><td>1x015</td><td>3x015</td><td>5x016</td><td>7x018</td><td>9x042</td></tr> <tr><td>1x016</td><td>3x016</td><td>5x017</td><td>7x019</td><td>9x028</td></tr> <tr><td>1x017</td><td>3x017</td><td>5x018</td><td>7x020</td><td>9x029</td></tr> <tr><td></td><td>3x028</td><td>5x026</td><td>7x025</td><td>9x030</td></tr> <tr><td></td><td>3x029</td><td>5x028</td><td>7x033</td><td></td></tr> <tr><td></td><td>3x030</td><td>5x029</td><td>7x028</td><td></td></tr> <tr><td></td><td></td><td>5x030</td><td>7x029</td><td></td></tr> <tr><td></td><td></td><td></td><td>7x030</td><td></td></tr> </table>	30 VA 70 x 30mm Regulation 18%	80 VA 90 x 30mm Regulation 12%	160 VA 110 x 40mm Regulation 8%	300 VA 110 x 50mm Regulation 6%	625 VA 140 x 75mm Regulation 4%	1x010	3x010	5x011	7x013	9x017	1x011	3x011	5x012	7x014	9x018	1x012	3x012	5x013	7x015	9x026	1x013	3x013	5x014	7x016	9x025	1x014	3x014	5x015	7x017	9x033	1x015	3x015	5x016	7x018	9x042	1x016	3x016	5x017	7x019	9x028	1x017	3x017	5x018	7x020	9x029		3x028	5x026	7x025	9x030		3x029	5x028	7x033			3x030	5x029	7x028				5x030	7x029					7x030					<table border="1"> <tr><th>Why a Toroid?</th></tr> <tr><td>* Smaller size &amp; weight to meet modern 'slimline' requirements.</td></tr> <tr><td>* Low electrically induced noise demanded by compact equipment.</td></tr> <tr><td>* High efficiency enabling conservative rating whilst maintaining size advantages.</td></tr> <tr><td>* Lower operating temperature.</td></tr> </table>	Why a Toroid?	* Smaller size & weight to meet modern 'slimline' requirements.	* Low electrically induced noise demanded by compact equipment.	* High efficiency enabling conservative rating whilst maintaining size advantages.	* Lower operating temperature.																																																																																																			
30 VA 70 x 30mm Regulation 18%	80 VA 90 x 30mm Regulation 12%	160 VA 110 x 40mm Regulation 8%	300 VA 110 x 50mm Regulation 6%	625 VA 140 x 75mm Regulation 4%																																																																																																																																																																														
1x010	3x010	5x011	7x013	9x017																																																																																																																																																																														
1x011	3x011	5x012	7x014	9x018																																																																																																																																																																														
1x012	3x012	5x013	7x015	9x026																																																																																																																																																																														
1x013	3x013	5x014	7x016	9x025																																																																																																																																																																														
1x014	3x014	5x015	7x017	9x033																																																																																																																																																																														
1x015	3x015	5x016	7x018	9x042																																																																																																																																																																														
1x016	3x016	5x017	7x019	9x028																																																																																																																																																																														
1x017	3x017	5x018	7x020	9x029																																																																																																																																																																														
	3x028	5x026	7x025	9x030																																																																																																																																																																														
	3x029	5x028	7x033																																																																																																																																																																															
	3x030	5x029	7x028																																																																																																																																																																															
		5x030	7x029																																																																																																																																																																															
			7x030																																																																																																																																																																															
Why a Toroid?																																																																																																																																																																																		
* Smaller size & weight to meet modern 'slimline' requirements.																																																																																																																																																																																		
* Low electrically induced noise demanded by compact equipment.																																																																																																																																																																																		
* High efficiency enabling conservative rating whilst maintaining size advantages.																																																																																																																																																																																		
* Lower operating temperature.																																																																																																																																																																																		
				<table border="1"> <tr><th>Why ILP?</th></tr> <tr><td>* Ex-stock delivery for small quantities.</td></tr> <tr><td>* Gold service available. 21 days manufacture for urgent deliveries.</td></tr> <tr><td>* 5 year no quibble guarantee.</td></tr> <tr><td>* Realistic delivery for volume orders.</td></tr> <tr><td>* No price penalty for call off orders.</td></tr> </table>	Why ILP?	* Ex-stock delivery for small quantities.	* Gold service available. 21 days manufacture for urgent deliveries.	* 5 year no quibble guarantee.	* Realistic delivery for volume orders.	* No price penalty for call off orders.																																																																																																																																																																								
Why ILP?																																																																																																																																																																																		
* Ex-stock delivery for small quantities.																																																																																																																																																																																		
* Gold service available. 21 days manufacture for urgent deliveries.																																																																																																																																																																																		
* 5 year no quibble guarantee.																																																																																																																																																																																		
* Realistic delivery for volume orders.																																																																																																																																																																																		
* No price penalty for call off orders.																																																																																																																																																																																		

Prices including P&P and VAT


VA Size	£	VA Size	£
15 0	7.43	160 5	12.90
30 1	8.08	225 6	16.30
50 2	10.10	300 7	18.55
80 3	10.81	500 8	25.73
120 4	11.73	625 9	31.63

For 110V primary insert "0" in place of "X" in type number.  
For 220V primary (European) insert "1" in place of "X" in type number.  
For 240V primary (UK) insert "2" in place of "X" in type number.  
**IMPORTANT:** Regulation - All voltages quoted are FULL LOAD.  
Please add regulation figure to secondary voltage to obtain off load voltage.

Mail Order - Please make your crossed cheques or postal orders payable to ILP Electronics Ltd.

Trade - We will open your credit account immediately upon receipt of your first order.

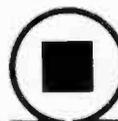Post to: ILP Electronics Ltd., Dept. 3  
Graham Bell House, Roper Close,  
Canterbury, Kent. CT2 7EP  
Tel: (0227) 54778 Telex: 965780



**ILP ELECTRONICS LTD.**

WW - 020 FOR FURTHER DETAILS

VISIT OR  
PHONE  
OPEN 6 DAYS  
A WEEK  
ALL STOCK  
ON DISPLAY

# HENRY'S AUDIO ELECTRONICS

Electronics  
Specialists  
Quantity  
Enquiries  
Invited

COMPUTERS • COMMUNICATIONS • TEST EQUIPMENT • COMPONENTS



### THERMAL • MATRIX • LINE PRINTER

150 to 180 LPM • Full 96 CH ASCII • 40 CPL • 280 Opts P/L • Auto-underline • 50 Graphic Symbols • Back Space • Self Test • VU/HRD TABS • 7 x 10 Matrix • 4 1/4" Wide Paper • Bidirectional • 220/240V AC • Size Approx. 9.8 x 2.8 x 7.2". SUITABLE FOR: TANDY • BBC • DRIC • NASCOM • GEMINI • ACORN • NEW BRAIN • DRAGON • etc. etc. (Your enquiries invited)

NEARLY 1/2 PRICE

Complete with 3 rolls paper. (Interface unit with leads £15 - state model). List price approx. £187 with paper. **£99.95** inc. VAT (UK C/P £1.05)

### SANYO DM2112 HIGH RESOLUTION MONITOR

12" green display. Composite video. 1280 characters. Over 15 MHz 8/W. 240V AC 34 w. 16" x 11 1/4" x 12 1/16". Alphanumeric and Graphic display.



Usually **£89.95** - **£99.95** Price **£69.95** incl VAT (UK C/P & ins £2.05)

SAVE £20 TO £30




ALL MODELS 3 1/2 DIGIT UNLESS STATED

### DIGITAL MULTIMETERS

Free carry case (rotary controls) + Carry case £2.95 (slide buttons)

- HAND HELD**
- KD25C 13 range D 2A DC 2 meg ohm £23.50
  - KD305 16 range 10A DC 2 meg ohm £26.95
  - KD30C 26 range 1A AC/DC 20 meg ohm £29.50
  - KD55C 28 range 10A AC/DC 20 meg ohm £33.50
  - METEX 3000 30 range 10A AC/DC 20 meg ohm £33.24
  - 601D + 28 range 10A AC/DC 20 meg ohm £34.40
  - 7030 + As 6010 but 0.1% basic £41.30
  - KD615 16 range 10A DC 2 meg plus Hie tester £39.95
  - 189M 30 range 10A AC/DC 20 meg plus Hie tester £69.95
  - DM2350 21 range 10A AC/DC 20 meg ohm miniature hand held auto range with case Beckman T100 34 range 10A AC/DC 20 meg ohm £56.35
  - Beckman T110 As T100 plus Cont. test etc. £67.85
  - Sifam 2200B 21 range 2A AC/DC 20 meg ohm SPECIAL OFFER £29.95

- SK6330 24 range P-B autorange 10A AC/DC buzzer, with case Matrix (ITT) £90.85
  - MX522 21 range 10A AC/DC £77.00
  - MX562 24 range 10A AC/DC Plus continuity buzzer £109.25
  - MX563 30 range true RMS Plus many features £178.25
  - MX575 4 1/2 Digit true RMS £201.25
- BENCH MODELS**
- TM356+ 27 range LCD 10A AC/DC 20 meg £97.75
  - TM355+ 29 range LCD 10A AC/DC 20 meg £86.25
  - TM351+ 29 range LCD 10A AC/DC 20 meg £120.75
  - Optional carry case £6.84
  - 2001 28 range LCD 10A AC/DC plus 5 range cap. Meter with case £108.00
  - TM451 4 1/2 digit LCD every facility (0.02%) £171.00
  - 1503a 4 1/2 digit LCD every facility (0.05%) £171.00
  - 1503Ha 0.03% basic version of above £189.00
  - 1504 True RMS version £201.25
  - Sifam 2500 24 range LCD 2A AC/DC 20 meg SPECIAL OFFER £79.95

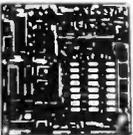

**PROFESSIONAL SERIES COMPUTERS IN STOCK**

GEMINI • GALAXY • NASCOM • 80-Bus multiboards.


Complete and part systems to suit your needs. Frames, boards, power supplies, keyboards, disc systems, etc. FOR THE PROFESSIONAL USER - SEND FOR DETAILS



### DELUXE 69 KEY ASCII KEYBOARD

General purpose, steel plate, output, redefinable, -5 and -12 volt, neg. strobe pulse, 4 user definable keys. Shift and control keys, etc. **£42.95** inc. VAT (UK C/P 85p)

ALSO Type 756A £51 Type 771 £66 inc. VAT

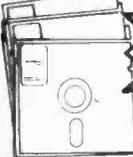

### 3 NEW SOFTWARE PRODUCTS

MDIS (IC) INTELLIGENT DIS ASSEMBLER For all CP/M based machines **£57.50** inc. VAT

IVC HI-RES (IC) For Gemini and others (please enquire) provides pseudo high resolution graphics. £17.25 inc. VAT


DISKPEN (IC) Version 3. Lost cost word processor. For Gemini and others (please enquire) **£57.50** inc. VAT

PLUS range of overlays available for Diskpen. Send for details of all above

(IC) Copyright Cubegate Ltd. 1983. All rights reserved.
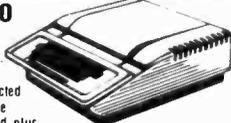
### I.T.T. 2020 CABINET

Complete PROFESIONAL Case beautifully constructed with cut out for one CHERRY keyboard, plus ample room to house a COMPLETE SYSTEM and power supply. Complete with fittings (Case top detachable). Unit is silver-grey in colour. Robust construction. Sloping front with side ventilation. Ideal for NASCOM, ACORN, TANGIERNE or your own system. Size 18" x 15" x 4" (front sloped). **£27.50** inc. VAT (UK C/P £2.50)



### FREQUENCY COUNTERS

- PFM200A 200 MHz hand held pocket 8 digit LED with batteries £77.60
- MET100 8 digit LED bench 2 ranges 100 MHz with AC Adaptors £102.35
- MET600 8 digit LED bench 3 ranges 600 MHz with AC Adaptors £132.25
- MET1000 8 digit LED 3 ranges 1 GHz with AC Adaptors £182.85
- TFD400 8 digit LCD 40 MHz with batteries £126.50
- TFD200 8 digit LCD 200 MHz with batteries £166.75
- Optional carry case £6.84 AC Adaptor £4.95
- Probe kits x1 £7.95, x10 £9.45, x1-x10 £10.50
- Prescalers - Extended range of most counters
- TP600 600 MHz £43.00
- TP1000 1 GHz with AC Adaptors £74.00



### SIGNAL GENERATORS

- (220/240V AC) (UK C/P £1.00)
- FUNCTION: All sine/square/triangle/TTL etc.
- TG101 D 0.2Hz-200KHz £113.85
- TG102 D 0.2Hz-2 MHz £166.75
- PULSE
- TG105 Various facilities 5 Hz-5 MHz £97.75
- AUDIO: Multiband Sine/Square
- LAG27 10 Hz to 1 MHz £90.85
- AG202A 20 Hz to 200 KHz (list £94.50) £83.50
- LAG 120A 10 Hz-1 MHz Low Distortion RF £159.85
- SG 402 100 KHz to 30 MHz (list £79.50) £69.50
- LSG17 100 KHz to 150 MHz (450 MHz HARM) £79.35

### COMPUTER POWER SUPPLY

Switched mode, stabilised, self protecting, S/C protected, etc. 220/240 V AC -5V 3.3A, -12V 2.4A 40%, cycle. 5V 0.5A - 12V 0.5A. Suitable Apple replacement **£57.50** inc. VAT (UK C/P £1.50)

### PRESTEL ADAPTOR

3 card set with data etc (P/S +/- 12V and +5V) **£69.95** inc. VAT

### CHERRY ADD-ON KEYPAD

16 button pad non-encoded **£5.95**

### MODEM CARD

BT approved ready assembled unit with data and accessories. **£39.95** inc. VAT

### ELECTRONIC INSULATION TESTER

YF501 500V/0-100m with carry case **£68.00**

Large range stocked. Ask for leaflet

### OSCILLOSCOPES

- Full specification any model on request. SAE by post 'HM' Series Names: 'SC' THANDAR, 'CS' TRIO, '3' CROTECH 'V' HITACHI
- SINGLE TRACE UK C/P £3.00
  - 3030 15 MHz 5mV, 95mm tube plus component tester £177.10
  - SC110A Miniature 10 MHz battery portable. Post free Nicads £12.50 AC adaptor £6.69 £171.00
  - Optional carry case £6.84
  - HM103 15MHz 2mV, 6 x 7 display plus component tester C/P £3.00 £181.70
  - DUAL TRACE (UK C/P £4.00)
  - HM203/4 Dual 20 MHz plus component tester £303.60
  - CS1562A Dual 10 MHz (List £321.00) £269.50
  - 3131 Dual 15 MHz + component tester £287.50
  - CS1566A Dual 20 MHz All facilities (List £401.35) £349.50

### MULTIMETERS (UK C/P 65p)

- HM102BZ 20kV/10A DC 22 range & cont. buzzer **£13.50**
- C7081 50 K/V Range Doubler 10A DC Total 36 Ranges **£12.50**
- SPECIAL OFFER
- TMK500 23 ranges 30K/V 12A DC plus cont. buzzer **£23.95**
- NH56R 20kV/V, 22 range pocket £10.95
- 830A 26 range 30K/V 10A AC/DC overload protection, etc. £23.95
- 360TR 23 range 100 K/V. Large scale 10A AC/DC plus Hie £39.95
- AT2100 10A AC/DC 31 range 100 K/V deluxe **£33.50**
- AT1020 18 range 20K/V, Deluxe plus Hie tester **£18.95**
- YN360TR 19 range 20K/V plus Hie tester **£15.95**
- Metrix Professional multimeters in stock 3 models from £74.75



### TOROIDAL TRANSFORMER

100 watts isolation 230/240 V AC plus 0-0 8V 4A 15 0 15V 0.845A 30V 0.16A Size approx 4" dia. x 1 1/2" **£7.95** (UK C/P 75p)

### RADIO INTERFERENCE FREE

24 hr 230/240V AC digital clock movements with alarm by Braun **£4.50** (UK C/P 50p)

### CENTAUR FANS

CU7983 115V 50/60Hz 12/13W impedance protected fuse 2 in series (for 230V) 4" x 4" x 1" Two for **£10.00** (UK C/P 70p)

### POCKET RADIATION DETECTORS

Dosimeter for Gamma and X-Rays 0-5r **£6.95** Quantities available

### CASSETTE MECHANISMS

Fitted counter, motor, record and erase heads, solenoid, etc. Brand new available 6V DC or 12V DC (state which) **£5.95** (UK C/P 65p)

### TOROIDAL POWER SUPPLY

12V and 5V 1 amp max stabilised 6" x 2" x 1" **£5.95** (UK C/P 65p)

ALSO STOCKED - LARGE RANGES All semiconductor valves, relays and other components. Plus millions of Res. Caps, presets, pots, etc. etc. for bulk and export users

### ASTEC UHF MODULATORS

UM1233 cased for computers, etc. **£3.50** (UK C/P 40p)

### TRANSISTOR TESTER

Direct reading PNP, NPN, etc. TCI **£21.95** (UK C/P 65p)

### DIGITAL THERMOMETER

TH301 LCD 50 C to -750 with thermocouple **£68.43**

### ULTRASONIC TRANSDUCERS

with cables, 40 KHz **£2.95** per pair (UK C/P 40p)

### MULLARD MODULES

(UK C/P 65p per 1-3) LP1171 FI and LP1179 AM/FM Tuner **£5.75** LP1186 Varicap Tuner **£5.00** LP1157 AM Tuner **£2.50**

## SELECTION OF SPECIAL OFFERS - QUANTITIES AVAILABLE FROM HENRY'S

Cubegate Ltd **RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL** College Dept., etc. Official Orders welcome. Also Companies, (subject to approval).

**HENRY'S** 404-406 Edgware Road, London, W2 1EO  
Computers 01-402 6822 - Equipment 01-724 0323 - Components 01-723 1008

**AUDIO ELECTRONICS** 301 Edgware Road, London, W2 1BN  
01-724 3564 (All post to 301 Edgware Road, London, W2 1BN)

ORDER BY PHONE OR BY POST OR CALL IN AND SEE FOR YOURSELF

FREE CATALOGUES  
Please state type required. Send large S.A.E. (20p UK). Test Equipment Computers Audio-Communications Components Schools, Colleges, Companies Export Free on Written Request


Order by Post with CHEQUES/ACCESS/VISA or you can telephone your orders.

## Essex Tiny Basic System

The Essex Tiny Basic Computer is an ideal choice for data acquisition and process control systems. Its crystal controlled timer and interrupts provide accurate timing and fast response to critical events, while the watchdog timer ensures reliable operation. Programs can be entered and tested from an RS232 terminal, and then be copied into EPROM. Alternatively, Instant ROM modules may be used both during development and for program storage.

£185

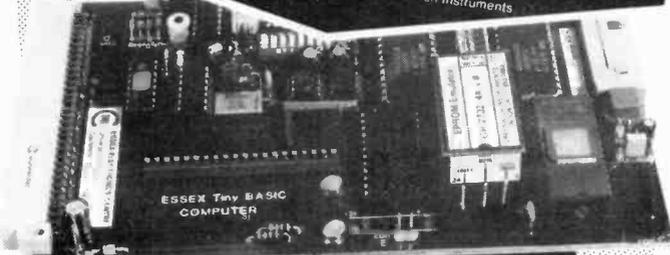
INSTANT ROM is the trademark of Greenwich Instruments



## Essex Buffer Timer

A convenient means of buffering the I/O lines of the Essex Tiny BASIC Computer provides 24 inputs, 16 outputs and four hardware timers.


£78

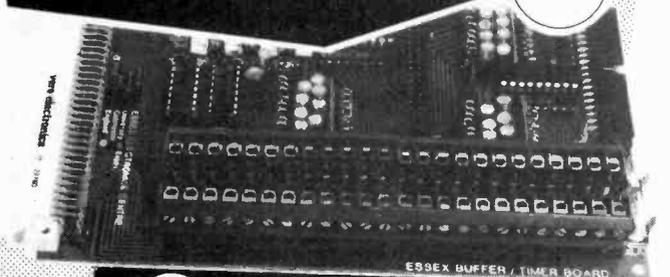

## Essex Opto-Isolator

Connects to the Essex Tiny BASIC System bus to provide an additional 12 opto-isolated inputs and 12 opto-isolated outputs per card for safe connection to external equipment, isolation voltage = 1500 volts.

£150

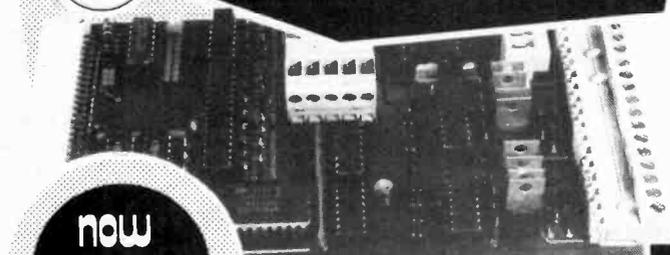

now available...

## Essex Backplane

A four slot backplane with printer and terminal connectors to accept these cards. £35

### 'Alex'

A powerful software utilities package that provides the user with an enhanced editor and all the tools needed to program efficiently in assembly language.

\* Text Editor \* Assembler

\* Disassembler \* Debug Monitor

Supplied as a 4K EPROM with comprehensive manual. £65

all prices exclude V.A.T.  
\* substantial quantity discounts available  
\* carriage within U.K. £2

## Essex Electronics Centre

Wivenhoe Park, Colchester, Essex CO4 3SQ  
Telephone: Colchester (0206) 865089

WW - 031 FOR FURTHER DETAILS

## MANUFACTURERS & DISTRIBUTORS

6 VA MINIATURE TX 240V AC input 12-0-12 V output P.C. mounting + internal thermal overload protection. £25 for 10 + VAT, £115 for 15 + VAT, £210 for 100 + VAT, £950 for 500 + VAT. Sample sent for £3 + 75p p&p (4.30 inc VAT).

MINIATURE SKELETON preset horizontal mounting 220R @ 0.1W 5.1mm x 10.2mm pitch, £35 for 1,000 + VAT.

BERG low profile 14-pin dual in-line IC socket, manufactured from glass-filled polyester to UL94V-0. £7 for 100, £31 for 500, £56 for 1,000, £256 for 5,000, £460 for 10,000, £2,100 for 50,000, £3,700 for 100,000. Sample 10 sent for £1.20 + 30p p&p (£1.37 inc VAT).

BERG low profile 16-pin dual in-line IC socket, as above. £8 per 100, £36 for 500, £65 for 1,000, £295 for 5,000, £530 for 10,000, £2,390 for 50,000, £4,300 for 100,000. Sample 10 sent for £1.40 + 30p p&p (£1.96 inc VAT).

215MA 32mm quick blow glass fuse. £5 for 100, £48 for 1,000.

TO3 HEATSINK. Efficient space saving TO3 heatsink, suitable for on-board mounting. Flat surfaces ensure high thermal conductivity. Pre-drilled to accept any standard TO3 device. Height 12mm, width 36mm, length 47mm, black anodised finish. £20 for 100 + VAT, £150 for 1,000 + VAT. Sample 10 sent for £2.50 + VAT and p&p.

HIGH POWER SILICON BRIDGE RECTIFIER, 25 amp 600V single hole fixing 250 (1/4") push on connector terminals, manufactured by I.R. £20 for 10, £90 for 50, £175 for 100, £800 for 500, £1,450 for 1,000. Special quotation for larger quantities. Sample sent for £2.50 + 25p p&p (£3.16 inc VAT).

METAL FILM RESISTOR TYPE FZ4, manufactured by C.G.S. Semi-precision with a standard tolerance of ±2% and a temperature co-efficient of better than 100 ppm/oc. We have a full range in stock from 100R to 1MO. All bandoliered. £2.50 per 1,000 any one value.

ZENER DIODES manufactured by Thompson C.F., all bandoliered, BZX79 C18 - BZX79C20-BZX-C18-BZX83-C20, £12 for 1,000 of one type, £15 per 1,000 assorted. Sample 100 sent for £3 + 25p p&p (£3.74 inc VAT).

TRANSISTORS, ICs, DIODES. Price for quantity 1,000  
 ACY 22 ..... £240 + VAT BC 157A ..... £35 + VAT BC 184 ..... £35 + VAT  
 BC 212 ..... £35 + VAT BC 384L ..... £40 + VAT BC 550 ..... £50 + VAT  
 SN 7474N ..... £150 + VAT SN 74174 ..... £260 + VAT SN 74LS96N ..... £310 + VAT  
 TIS 90T ..... £100 + VAT TIS 91T ..... £110 + VAT  
 10 samples, price on application

Terms c.w.o. Please add 5% to all orders for carriage plus 15% VAT. Export enquiries welcome. We find it impossible to advertise all we stock. Please telephone or write for further enquiries. Personal callers always welcome.

**ELECTRONIC EQUIPMENT Co.**

SPRINGFIELD HOUSE  
 TYSSEN STREET, LONDON E8  
 TEL: 01-249 5217  
 TELEX: 9853906 EECO G

WW - 051 FOR FURTHER DETAILS

IN VIEW OF THE EXTREMELY RAPID CHANGE TAKING PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTITIES OF COMPONENTS BECOME REDUNDANT. WE ARE CASH PURCHASERS OF SUCH MATERIALS AND WOULD APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE. WE PAY TOP PRICES AND COLLECT.

## BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho corner

Telephone 445 2713/0749

WW - 019 FOR FURTHER DETAILS

## WRONG TIME?



MSF CLOCK is ALWAYS CORRECT - never gains or loses. SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, 24 hour format, larger digit Hours and Minutes for easy QUICK-GLANCE time, auto GMT/BST and Leap Year, parallel BCD (including Weekday) output for computer, etc, and audio to record and show time on playback, receives Rugby 60kHz atomic time signals, only 15x5x8 cm, built-in antenna, 1,000km range, GET the RIGHT TIME, £72.70.

V.L.F.? EXPLORE 10-150kHz, Receiver £21.20.


Each fun-to-build kit (ask for full list, ready-made to order) includes all parts, printed circuit, case, instructions, by-return postage, etc, money back assurance, SEND away NOW.
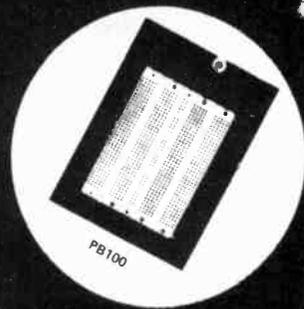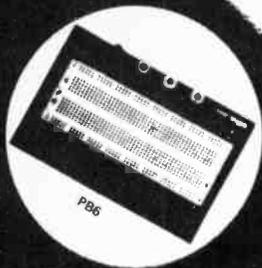
## CAMBRIDGE KITS

45 (WA) Old School Lane, Milton, Cambridge. Tel. 860150



# NEW & FREE FROM GSC

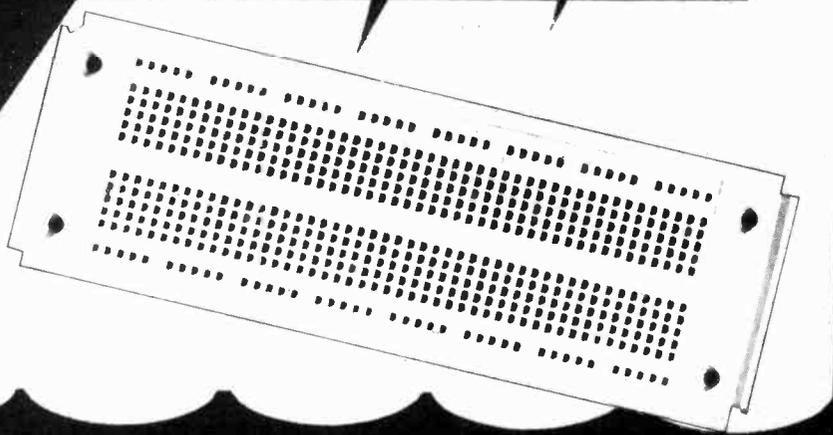

## NEW AND FREE FROM GSC.

NEW an exciting range of projects to build on the EXP300 breadboards. NOW anybody can build electronic projects using "Electronics-by-numbers", its as "Easy as A, B, C with G.S.C!"

### FREE project

#### MUSICAL DOORBELL OF THE 3RD KIND

You've seen the film, now haunt your visitors with the tune!

Each time the doorbell is pushed the eerie tune plays out, then switches off to conserve battery power.

### HOW DO YOU MAKE IT.

Our FREE project gives you clear "step-by-step" instructions. For example "take Resistor No.1 and plug it into hole numbers B45 and B47"

"Take IC No.1 and plug it into hole numbers E35 to E42 and F35 to F42, (pin 1 on the IC goes into F35)"

"Take... Well! why not "clip-the-coupon" and get your FREE step-by-step instruction sheet and your FREE 12 projects with each EXP300 bought and your FREE catalogue and...

**WW - 029 FOR FURTHER DETAILS**

## EXPERIMENTOR BREADBOARDS

The largest range of breadboards from GSC. Each hole is identified by a letter/number system. EACH NICKEL SILVER CONTACT CARRIES A LIFE-TIME GUARANTEE.

All modular construction means that any Experimentor breadboard can be "snap4ocked" together to build breadboards of any size.



**EXP325**  
The 'one-chip' breadboard. Takes 8, 14, 16 and up to 22 pin IC's. Has 730 contact points including 2 bus bars.



**EXP350**  
The 'beginners breadboard'. For limited period you can have FREE 12 'Electronics by Numbers' PROJECTS.



The most 'widely-bought' breadboard. Don't miss out on our 'NEW AND FREE' projects. They can be built on the EXP300.

**EXP600**  
The 'Hobbyist microprocessor' board.  
**EXP650**  
The 'one-chip microprocessor' board.

**EXP4B**  
'Snap-on' four extra bus bars.  
**PB6**  
The ultimate breadboard kit.  
**PB100**  
The most kit for the least money.

## NEW AND FREE FROM G.S.C. 24 HOUR SERVICE.

Tel: (0799) 21682 with your Access, American Express, Barclaycard number and your order will be put in the post immediately.

TO ORDER JUST CLIP THE COUPON.

Experimentor Breadboards	Unit Price Inc. P & P + 15% VAT	Quantity Required
Exp 325	£ 3.45	
Exp 350	£ 5.23	
Exp 300	£ 8.63	
Exp 600	£10.29	
Exp 650	£ 6.33	
Exp 4B	£ 4.03	
PB 6	£14.95	
PB 100	£20.07	

NAME .....

ADDRESS .....

I enclose cheque/PO for £ .....

Debit my credit card No. ....

Expiry date .....


Please send free catalogue Tick  Dept. 7P

GLOBAL SPECIALTIES CORPORATION  
**GSC**

GSC Unit 1, Shire Hill Ind. Estate  
Saffron Walden, Essex, CB11 3AQ.  
Telephone (0799) 21682.  
Telex 817477 Dept. 6P
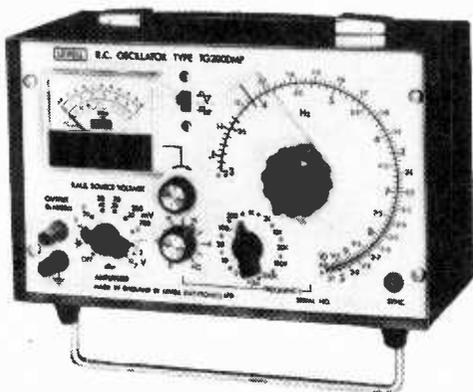
# RC OSCILLATORS

LEVELL ELECTRONICS have a range of OSCILLATORS Covering frequencies from 0.02Hz to 2MHz. There is a DECADE OSCILLATOR with digital frequency tuning and a FUNCTION GENERATOR providing sine, square, triangle, pulse, ramp and asymmetrical sine waves. Various RC OSCILLATORS are available as detailed below:



## TG152 SERIES

FREQUENCY 3Hz to 300kHz in 5 decade ranges.  
ACCURACY  $\pm 2\%$  to  $\pm 0.1\text{Hz}$  up to 100kHz, increasing to  $\pm 3\%$  at 300kHz.  
SINE OUTPUT 2.5V rms down to  $<200\mu\text{V}$ .  
DISTORTION  $<0.2\%$  from 50Hz to 50kHz,  $<1\%$  from 10Hz to 200kHz.  
SQUARE OUTPUT 2.5V peak down to  $<200\mu\text{V}$ .  
SYNC OUTPUT 2.5V rms sine.  
METER SCALES 0/2.5V & -10/+10dB on TG152DM.

## TG200 SERIES

FREQUENCY 1Hz to 1MHz in 12 ranges. 0 to 1% fine control to TG200DMP.  
ACCURACY  $\pm 1.5\%$  to  $\pm 0.01\text{Hz}$  up to 100kHz,  $\pm 2\%$  up to 1MHz.  
SINE OUTPUT 7V rms down to  $<200\mu\text{V}$  with  $R_s=600\Omega$ .  
DISTORTION  $<0.05\%$  from 50Hz to 15kHz,  $<0.1\%$  from 10Hz to 50kHz,  $<0.2\%$  from 5Hz to 150kHz,  $<1\%$  at 1Hz and 1MHz.  
SQUARE OUTPUT TG200D, DM & DMP only, 7V peak down to  $<200\mu\text{V}$ . Rise time  $<150\text{ns}$ .  
SYNC OUTPUT  $>1\text{V}$  rms sine in phase with output.  
SYNC INPUT  $\pm 1\%$  freq. lock range per volt rms.  
METER SCALES TG200DM & DMP only, 0/2V 0/7V & -14/+6dBm.

TG152 SERIES: £88 to £110

TG200 SERIES: £110 to £149

Send for data covering our range of instruments. Prices are plus carriage, packing and VAT.

## LEVELL ELECTRONICS LTD.

Moxon Street, Barnet, Herts. EN5 5SD, England.  
Telephone: 01-4 40 8686/449 5028.

WW - 018 FOR FURTHER DETAILS

## U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

### RECORD DECKS 240 volt AC. Post £2

Make	Model	Drive	Cartridge	Price
BSR	P170	Rim	Ceramic	£22
GARRARD	6200	Rim	Ceramic	£24
GARRARD	SP25	Rim	Magnetic	£36
GOLDRING	G102	Belt	Magnetic	£30

### AUTOCHANGERS 240 VOLT

BSR	Budget	Rim	Ceramic	£18
BSR	Delux	Rim <td>Ceramic</td> <td>£20</td>	Ceramic	£20
BSR	Delux	Rim <td>Magnetic</td> <td>£26</td>	Magnetic	£26

**THE "INSTANT" BULK TAPE ERASER** £10.50 Post 95p  
Suitable for cassettes and all sizes of tape reels. AC mains 200/250V. Hand held size with switch and lead (120 volt to order). Will also demagnetise small tools.  
Tape Head Demagnetiser only £5.



**ALUMINIUM CHASSIS.** 2 1/2in deep 6x4-£1.75; 8x6-£2.20; 10x7-£2.75; 12x8-£3.20; 14x9-£3.60; 16x6-£3; 16x10-£3.80; 12x3 £2.20; 14x3 £2.50; 13x3 £2.80.

**ALUMINIUM PANELS.** 6x4-55p; 8x6-90p; 14x3-90p; 10x7-£1.15; 12x8-£1.30; 12x5-90p; 16x6-£1.30; 14x9-£1.75; 12x12-£1.80; 16x10-£2.10.

**ALUMINIUM BOXES.** 4x4x1 1/2 £1.20. 4x2 1/2x2 £1.20. 3x2x1 £1.20. 6x4x2 £1.90. 7x5x3 £2.90. 8x6x3 £3. 10x7x3 £3.60. 12x5x3 £3.60. 12x8x3 £4.30.

**POTENTIOMETERS.** 5K/2meg LOG or LIN. L/S 50p. DP 90p. Stereo L/S £1.10. DP £1.30. Edge Pot 5L. SP 45p.

### MINI-MULTI TESTER

De Luxe pocket size precision moving coil instrument. Impedance + Capacity - 4000 o.p.v. Battery included. 11 instant ranges measure: DC volts 5.25, 250, 500. AC volts 10, 50, 500, 1000. DC amps 0-250µA, 0-250mA. Resistance 0 to 600K ohms. Post 50p

**De Luxe Range Doubler MULTI-METER** £19.50  
50,000 o.p.v. 7x5x2in. 50 Micro Amp Post £1  
43 Ranges, 1,000V, AC-DC, 20 MEG, 10amp DC

**PANEL METERS** 50µA, 100µA, 500µA, 1mA, 5mA, 50mA, 100mA, 500mA, 1 amp, 2 amp, 25 volt, VU 2 1/2x2x1 1/4. Stereo VU 3 1/4x1 1/8x1in. £5 p.p. 50p

### RCS SOUND TO LIGHT CONTROL BOX

Complete ready to use with cabinet size 9x3x5in. 3 channel, 1000 watt each. For home or disco OR KIT OF PARTS £19.50 £27 Post £1

MAINS UNIT 9v 400mA. Stabilised £5 post £1.

## RADIO COMPONENT SPECIALISTS

Books and Components Lists 32p stamps. (Minimum post/packing charge 65p.) Access or Barclaycard Visa. Tel: 01-684 1665 for SAME DAY DESPATCH. Cash prices include VAT.

WW - 041 FOR FURTHER DETAILS

### RCS "MINOR" 10 watt AMPLIFIER KIT £14

This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available: Mono, £14; Stereo, £20. Post £1 10W per channel; size 9 1/2x3x2in. SAE details. Full instructions supplied. 240V AC mains.

**RCS STEREO PRE-AMP KIT.** All parts to build this pre-amp. Inputs for high, medium or low imp per channel, with volume control and PC Board £3.50  
Can be ganged to make multi-way stereo mixers Post 65p

### MAINS TRANSFORMERS

	Post
250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A	£7.00 £2
350-0-350V 250mA, 6.3V 6A CT	£14.00 £2
220V 25mA 6V lamp £3.00	220V 45mA 6V 2 Amp £4.00 £1
250V 60mA, 6V 2A	£4.75 £1

**Step-Down** 115V to 240V 150W £9. 250W £12. 500W £14 £2

### GENERAL PURPOSE LOW VOLTAGE

Tapped outputs available	Price Post
2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V	£8.00 £2
1 amp. 8, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£8.00 £2
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£10.50 £2
3 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£12.50 £2
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£18.00 £2
5-8-10-16V. 1/2 amp.	£2.50 £1
6V. 1/2 amp.	£2.00 £1
6-0-6V. 1/2 amp.	£3.50 £1
9V. 400mA.	£1.50 £1
9V. 3 amp.	£5.00 £1
9-0-9V. 50mA	£1.50 £1
9-0-9V. 1 amp	£3.50 £1
10-0-10V. 2 amps	£4.00 £1
10-30-40V. 2 amps	£5.50 £1
12V. 100mA	£1.50 £1
12V. 500mA	£2.50 £1
12V 3 amps	£4.50 £1
12-0-12V. 2 amps	£5.50 £1
	and 20-0-20V 1/2a £10.00 £2

500mF 12V 15p; 25V 20p; 50V 30p; 1200mF 76V 80p.

1000mF 12V 20p; 25V 35p; 50V 50p; 100V 1.20.

2000mF 30V 42p; 40V 60p; 100V £1.40; 1500mF 100V £1.20.

2500mF 50V 70p; 3000mF 50V 65p; 4700mF 40V £1; 63V

£1.80.

**CAPACITORS WIRE END High Voltage**

.001, .002, .003, .005, .01, .02, .03, .05 mfd 400V 10p.

.1Mf 400V 14p. 600V 15p. 1000V 25p.

.22Mf 350V 12p. 600V 20p. 1000V 30p. 1750V 50p.

.47Mf 150V 10p. 400V 25p. 630V 30p.

**HIGH VOLTAGE ELECTROLYTICS**

2/500V 45p 32+32+16/350V 90p 8+16/450V 75p

8/450V 45p 100+100/275V 50p 16+16/350V 80p

16/350V 45p 150+200/275V 50p 32+32/350V 85p

32/500V 95p 32+32+32/450V 95p 32+32/500V £2

50/450V 95p 50+50+50/350V 95p 50+50/300V 50p

125/500V £2 8+8/500V £1 50+50/350V 80p

### BAKER AMPLIFIERS BRITISH MADE

#### PA150 MICROPHONE VOCAL AMPLIFIER £129

4 channel 8 inputs, dual impedance, 50K-600 ohm 4 channel mixing, volume, treble, bass. Presence controls, Master volume control, echo send return socket. Slave sockets. Post £3.

#### 150 WATT MIXER AMPLIFIER 4 Inputs £99

Discotheque, Vocal, Public Address. Speaker outlets 4, 8 or 16 ohms. Four inputs, 20 mv, 50K ohm. Individual volume controls "Four channel" mixing. Slave output 16" x 8" x 5 1/2". Wt - 14lb: Master volume control. British made. 12 months' guarantee. 240V A.C. 120V to order. All transistor and solid state. Post £2.

100 Volt Line Model 150 watt £114. MONO SLAVE 150 watt £80.

New Stereo Slave 150 + 150 watt 300 watt Mono £25. Post £4.

#### BAKER MOBILE PA AMPLIFIER. All transistor, 60 watt RMS.

12v DC & 240v AC, 4 inputs 50K. Aux + 2 mics + 1 phono.

Outputs 4-8-16 ohm + 100 volt line. £89 p.p. £2

#### BAKER PORTABLE DISCO 150 watt. Twin console + amplifier +

micro and headphones + twin speakers £300. 300 watt £390.

Carr. £30. Console + decks + pre-amp £95 Carr. £12.

#### PA CABINET SPEAKERS, Complete. 8 ohm 60 watt

17x15x9in. £25. Post £4. 4 or 8 or 16 ohm 75 watt

23x15x11in. £50. 90 watt 32x15x11in. £63. 120 watt

£77. Carr. £10. Black vinyl covered with handles.

#### WATERPROOF HORNS 8 ohms. 25 watt £20. 30 watt

£23. 40 watt £26. 40W plus 100 volt line £32. Post £2.

### FAMOUS BAKER LOUDSPEAKERS

MODEL MAJOR 12 4-8-16 30 HI-FI £16 £2

SUPERB 12 8-16 30 HI-FI £26 £2

AUDITORIUM 12 8-16 45 HI-FI £24 £2

AUDITORIUM 15 8-16 60 HI-FI £37 £2

GROUP 45 12 4-8-16 45 PA £16 £2

DG 75 12 4-8-16 75 PA £26 £2

GROUP 100 12 8-16 100 PA £26 £2

DISCO 100 12 8-16 100 Disco £26 £2

GROUP 100 15 8-16 100 PA £35 £2

DISCO 100 15 8-16 100 Disco £35 £2

#### SPEAKER COVERING MATERIALS. Samples Large S.A.E.

B.A.F. LOUDSPEAKER CABINET WADDING 18in wide 35p ft.

#### MOTOROLA PIEZO ELECTRIC HORN TWEETER, 3 1/4in. square

100 watts. No crossover required, 4-8-16 ohm, 7 1/4x3 1/4in. £10

#### CROSSOVERS. TWO-WAY 3000 cps 30 watt £3. 100W £4.

3-way 950 cps/3000 cps. 40 watt rating. £4. 60 watt £6. 100W £8.

LOUDSPEAKER BARGAINS. Please enquire, many others in stock.

4 ohm, 5in, 7x4in, £2.50; 6 1/2in, 8x5in, £3; 8in, £3.50. 6 1/2in 20W £7.50.

8 ohm, 2 1/4in, 3in, £2; 5x3in, 6x4in, 7x4in, 5in, £2.50.

8x5in, £3; 8in, £4.50; 10in, £5; 12in, £6. 8in 25W £6.50; 60W £12.50.

15 ohm, 2 1/4in, 3 1/2in, 5x3in, 6x4in £2.50. 6 1/2in 10W £5. 8in £4. 10in £7

25 ohm, 3in, £2; 5x3in, 6x4in, 7x4in, £2.50. 120 ohm, 3 1/4in dia. £1.

EMI 13x8in 4 or 8 ohm 10 watt £8 pp £1.

Dept 1, 337 WHITEHORSE ROAD, CROYDON  
Open 9-6. Closed all day Wed. Open Sat. 9-5.

£23. 40 watt £26. 40W plus 100 volt line £32. Post £2.

WW-7






# WELL WORTH A SECOND LOOK...

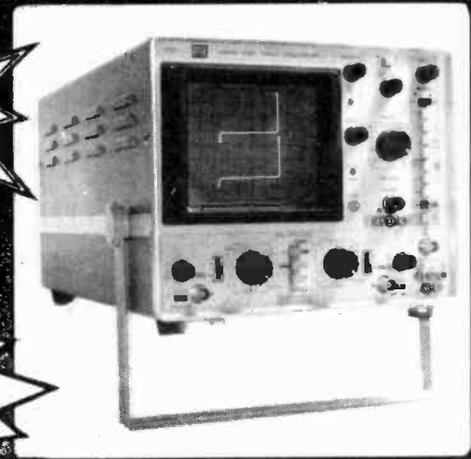**NEW!!!**

No — you're not seeing double, just the Crotech 3132's Component Comparator in action. This unique feature, using two Crotech component testers, gives you the benefit of checking an active or passive component against a known standard. Complete circuits can also be checked using signature techniques.

But that's not the only new feature. The 3132 has three DC source outlets available on the front panel, capable of powering most solid state circuits. Dare we say that the 3132 is the nearest affordable 'scope to come near to being a complete test system?



- 14 Trigger Functions  
Triggering up to 40MHz
- 2mV/div
- X-Y Mode
- DC — 20MHz
- 40ns — 0.2s/div
- Add & Subtract
- PLUS**  
COMPONENT COMPARATOR and DC SOURCE OUTLETS

**Crotech Instruments Limited**  
5 Nimrod Way, Elgar Road, Reading, Berkshire, RG2 0EB.  
Telephone: (0734) 866945

For full data sheet and a copy of our Highlight brochure — all free — just give us a call or fill in the enquiry card

WW — 028 FOR FURTHER DETAILS

## An in-depth series in understanding today's world of electronics. From Texas Instruments.

**SPECIAL OFFER**  
Order three books and get  
"Understanding" series  
**FREE.**

- The Understanding Electronics Series was specially developed and written to give you an in-depth knowledge of this world.
- Each book is comprehensive, yet easy to understand. As informative for the electronics buff as for someone who's simply interested in what's going on today.
- Together the library will give you the most complete range of titles available. Take advantage of our special offer and choose the book, or books you want from the titles below. You'll find whole new worlds of advanced technology unfolding before you.
- 1. Understanding Electronic Control of Energy Systems.** 1st edition. Ref. LCB 6642. Covers motor, generator, power distribution, heating, air conditioning, internal combustion engine, solar and nuclear systems. Softbound 272 pages. £4.50.
  - 2. Understanding Electronic Security Systems.** 1st edition. Ref. LCB 720L. A complete guide covering the basics of hard wired, photosensitive, infrared, ultrasonic and microwave systems and their use in different applications. Softbound 128 pages. £2.95.
  - 3. Understanding Solid State Electronics.** 3rd edition. Ref. LCC 336L. The principles of solid state theory. It explains electrical movement, with intermediate tuition on the applications of solid state devices. Softbound 282 pages. £4.50.
  - 4. Understanding Digital Electronics.** 1st edition. Ref. LCB 331L. Describes digital electronics in easy-to-follow stages. It covers the main families of digital integrated circuits and data processing systems. Softbound 260 pages. £4.50.
  - 5. Understanding Microprocessors.** 1st edition. Ref. LCB 4023. An in-depth look at the magic of the solid state chip. What they are, what they do, Applications of 8-bit and 16-bit microprocessors; and design from idea to hardware. Softbound 288 pages. £4.50.
  - 6. Understanding Computer Science.** 1st edition. Ref. LCB 547L. This book tells you in everyday English how today's computer has been developed, what goes on inside it, and how you tell it what to do. Softbound 278 pages. £4.50.

- 7. Understanding Communications Systems.** 1st edition. Ref. LCB 452L. An overview of all types of electronic communications systems. Softbound 282 pages. £4.50.
- 8. Understanding Calculator Maths.** 1st edition. Ref. LCB 332L. Brings together the basic information—formulae, facts, and mathematical tools—you need to "unlock" the real power of the hand-held calculator. Softbound 230 pages. £4.50.
- 9. Understanding Optronics.** 1st edition. Ref. LCB 547Z. Optronics is the application of light and electronics to perform a wide range of useful tasks. From car headlights to missile guidance systems. Softbound 270 pages. £4.50.
- 10. Understanding Automotive Electronics.** 1st edition. Ref. LCB 577L. Learn how electronics is being applied to automobiles. How the basic mechanical, electrical and electronic functions and the new microprocessors and microcomputers are being applied in innovative ways for vehicle drive train control, motion control and instrumentation. Softbound 288 pages. £4.50.
- 11. Understanding Telephone Electronics.** 1st edition. Ref. LCB 714L. The powerful, positive thrust of electronics is making the telephone an even more important communication link. Conventional telephone fundamentals, analog and digital electronics, principles, newer digital techniques and hardware implementation are covered in this book. Softbound 288 pages. £4.50.
- 12. Understanding Electronic Control of Automation Systems.** 1st edition. Ref. LCB 664L. This book is about automation—explains in simple language the subject of electronic control of automation systems, and to help the reader understand the terms, principles, techniques and effort used to automate processes. Softbound 280 pages. £4.50.

**How to order**  
Fill in the coupon below or if someone else has already used it, simply:  
1. List reference numbers and quantities required.  
2. Calculate total order value. Add £1.50 for postage and packing.  
3. Send the list, plus your cheque payable to Texas Instruments Ltd, PO Box 50, Market Harborough, Leicestershire.  
Allow 30 days for delivery.

To: Texas Instruments Limited, PO Box 50, Market Harborough, Leics.  
Please send me the following publications:

REFERENCE NO.	QTY	REFERENCE NO.	QTY
1.		7.	
2.		8.	
3.		9.	
4.		10.	
5.		11.	
6.		12.	

Free title choice: Understanding \_\_\_\_\_  
I enclose a cheque for £ \_\_\_\_\_  
Name \_\_\_\_\_  
Company (if any) \_\_\_\_\_  
Address \_\_\_\_\_  
\_\_\_\_\_

Please send me details of TI's range of Technical Books (please tick)   
Registered office: Texas Instruments Ltd, Manton Lane, Bedford MK41 7DA  
Registered number: 574102 England **WW1**

**TEXAS INSTRUMENTS**

WW — 043 FOR FURTHER DETAILS

# BBC Micro Computer System OFFICIAL DEALER

Please phone for availability



Software from ACORNSOFT/  
PROGRAM POWER/GEMINI in  
stock

BBC Model B £399  
B + DFS £470  
B + ECON £477  
B + DFS + ECON £518  
Above prices include  
VAT. Carr £7  
Model A to B Upgrade  
Kit £60  
Installation £15

LANGUAGE ROMs  
BCPL Rom + Disc + Manual £87  
PASCAL-T Rom £45

WORD PROCESSOR ROMs  
VIEW 16k Rom £52  
WORDWISE 8k Rom £34

## FLOPPY DISC INTERFACE £95 & £15 installation

### BBC COMPATIBLE DISC DRIVES

All drives are supplied with necessary cables  
Single Drive without PSU: 100k £150; 200k £215; 400k  
£225

Single Drive with PSU: 100k £185; 200k £260\*; 400k £330  
Dual Drives with PSU: 2x100k £355; 2x200k £475\*;  
2x400k £495

\* These drives are switchable 40/80 drives.

40/80 Switch Module for 1x400k and 2x400k Drive £32

### DISKETTES

40 track SS £15; 80 track SSDD £22

80 track DSDD £26

### BBC FLOPPICLENE DRIVE HEAD

Cleaning kit with 50 disposable discs £17

Phone or send for our BBC leaflet

## CASSETTE RECORDER

### SANYO Data Recorder DR101

A superior quality data recorder with dedicated  
computer output and monitoring facility on  
both record and play £39.50 + £1.50 carr.  
SLIMLINE Cassette Recorder complete with  
counter and remote control £24.50 + £1.50  
carr.

BBC Recorder £27  
Computer Grade Cassettes  
£0.50 each. £4.50 for 10 + £1 carr  
Cassette lead £3.50.

## MONITORS

MICROVITEC 14in RGB Monitors


1431 Std. Res Monitor £215  
1451 Med Res Monitor £345  
1441 Hi Res Monitor £440  
12" KAGA RGB I £235 RGB III £399  
12" Hi Res Green SANYO £99 KAGA £106

## TORCH Z-80 PACK

Your B.B.C. computer can be converted into a business machine at a cost  
slightly higher than an 800k disc drive. The Torch pack with twin disc  
drive and a Z80A processor card greatly enhances the data storing and  
processing capability of the computer. (NOTE: In BBC mode the disc  
pack functions as a normal BBC drive.). Z80A card comes with 64k of  
RAM and a CP/M compatible operating system. The system is supplied  
complete with a BBC owner's user guide, a Systems/Demo disc, a  
PERFECT software package and COMANEX, a business management  
game. The PERFECT software package comprises of a DATABASE,  
CALC, WORDPROCESSOR and SPELLER commercially valued at over  
£1,000. The complete package for only £730. Installation £20. Carr. £8.
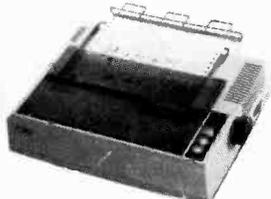
## PRINTERS

EPSON RX80 FT £305  
EPSON FX80 £370  
EPSON FX100 £565  
EPSON MX100 £400  
Carriage/Printer £7



NEC PC 8023 BE-N £320  
SEIKOSHA GP100A £170  
SEIKOSHA GP250A £210  
Parallel Printer Cable £12  
Serial Printer Cable £8

Variety of Printer Interfaces in stock  
2000 fanfold sheets £13.50 + £3 p.&p.

## SIDEWAYS ROM EXPANSION BOARD FOR BBC

SREB provides 8 additional sockets for expanding  
the computer's sideways ROM capacity by a further  
128k (8k or 16k Eproms consume 40mA on standby  
and in our opinion 8 ROMs will not overload the  
computer psu). The board is dimensioned ensuring  
clearance of components with adequate ventilation.  
Fully assembled and tested board with fitting  
instruction. With TI sockets £25. With turned pin  
sockets £30. P. & P. £2.

## BBC EPROM PROGRAMMER

A fully self-contained Eprom Programmer with its own power supply, able to  
program 2516, 2716/32/32A/64/128 single rail Eproms.

- ★ Personality selection is simplified by a single rotary switch.
- ★ Programming voltage selector switch is provided with a safe position.
- ★ Warning indicator to show programming in progress.
- ★ Programmer can read, blank check, program and verify at any address/  
addresses on the EPROM.
- ★ Simple menu driven software supplied on cassette (transferable to disc).
- ★ Full editor with ASCII disassembler.

Programmer complete with cables, software and operating instructions:  
£79.50 + £2 p. & p.

## PRODUCTION PROGRAMMER: P8000

P8000 provides reliable gang programming of up to 8 EPROMS  
simultaneously with device sizes up to 16k x 8 bytes. Devices  
supported range from 2704 to 27128 in single and three rail ver-  
sions. Simple menu driven operation ensures easy eprom  
selection and reliable programming in minimum programming  
times. £695 + £6 carriage.

## BOOKS (no VAT; p&p £1/book)

- Assembly Lang Prog. for BBC ..... £8.95
- Assembly Lang programming on BBC  
Micro by Ferguson and Shaw ..... £7.95
- Basic Prog. for BBC ..... £5.95
- BBC An Expert Guide ..... £6.95
- Easy Programming on BBC ..... £5.95
- Further Programming on BBC ..... £5.95
- Introducing BBC Micro ..... £5.95
- Programming the BBC ..... £6.50
- 30 Hour Basic ..... £5.95
- 35 Educational Programs ..... £6.95
- BBC Sound & Graphics ..... £7.95
- Creating Adventure Programs ..... £6.95
- Discovering Machine Code ..... £6.95
- Structured Programming ..... £6.50
- The Friendly Computer Book BBC ..... £4.50
- Beyond Basic BBC ..... £7.25

Large number of other titles stocked

## UV ERASERS

The following erasers are all fitted  
with safety interlocks and mains  
switches with indicators.

- UV1B up to 6 Eproms ..... £47
- UV1T as above but with timer ..... £59
- UV140 up to 14 Eproms ..... £61
- UV141 as above but with timer ..... £79

## ★ SPECIAL OFFER ★

- 2532 £3.50 27128-3 £15
- 2732 £3.50 4164-2 £4.50
- 2764-25 £5

## LIGHT PEN

(RH-1). A superior design, with a 'push  
tip', status indicator LED, and an in-  
terface box that plugs into the user  
port. Comes with manual, full soft-  
ware and four Basic demonstration  
programs £39.50.

## SMARTMOUTH

The 'infinite vocabulary' self-con-  
tained speech synthesiser unit. Uses  
only 5-10 bytes per word - no ROMs  
required - simply plugs into the user  
port. (Has Aux. Audio output skt.).  
Supplied with Demo/Development  
programs and simple software in-  
structions, £37 + £2 p. & p.

NEW COMPREHENSIVE CATALOGUE AVAIL-  
ABLE - PLEASE SEND FOR PRICE LIST

## CONNECTOR SYSTEMS

### I.D. CONNECTORS

(Speedblock Type)

No of ways	Header Plug	Receptacle	Edge Conn.
10	90p	85p	120p
20	145p	125p	195p
26	175p	150p	240p
34	200p	160p	320p
40	220p	190p	340p
50	235p	200p	390p

### D CONNECTORS

No. of ways

	9	15	25	37
MALE Solder	80p	105p	160p	250p
Angled	150p	210p	250p	365p
FEMALE Solder	105p	160p	200p	335p
Angled	165p	215p	290p	440p
Hoods	90p	85p	90p	100p
IDC 15-way plug 340p	Socket 400p			
IDC 25-way plug 385p	Socket 450p			

### TEXTTOOL ZIF

SOCKETS 24-pin £5.75

40-pin £9.75

### DIL SWITCHES

4-way 70p 8-way 90p

6-way 85p 10-way 140p

### JUMPER LEADS

24" Ribbon Cable with Headers

	14-pin	16-pin	24-pin	40-pin
1 end	145p	165p	240p	350p
2 ends	210p	230p	345p	540p

24" Ribbon Cable with Sockets

	20-pin	26-pin	34-pin	40-pin
1 end	160p	200p	280p	300p
2 ends	290p	370p	480p	525p

Ribbon Cable with D. Conn.

25-way Male 500p Female 550p

### RS 232 JUMPERS

(25-way D)

24" Single end Male	£5.00
24" Single end Female	£5.25
24" Female-Female	£10.00
24" Male-Male	£9.50
24" Male-Female	£9.50

### DIL HEADERS

Solder Type IDC Type

14pin	40p	100p
16pin	50p	110p
24pin	100p	150p
40pin	200p	225p

### AMPHENOL CONNECTORS

36-way plug Centronics Parallel

Solder £5.25 IDC £4.95

36-way socket Centronics Parallel

Solder £5.50 IDC £5.20

24-way plug IEEE Solder £5

IDC £4.75

24-way socket IEEE Solder £5

### RIBBON CABLE

(Grey/meter)

10 way	40p
16-way	60p
20-way	85p
26-way	120p
34-way	160p
40-way	180p
50-way	200p
64-way	280p

### EURO CONNECTORS

DIN 41617	Plug	Skt.
21-way	160p	165p
31-way	170p	170p

DIN 41612	2x32-way St. Pin	220p	275p
2x32-way Ang. Pin	275p	320p	
3x32-way St. Pin	260p	300p	
3x32-way Ang. Pin	375p	350p	

### EDGE CONNECTORS

0.1" 0.156"


2x12-way (Vic)	350p	
2x18-way		140p
2x22-way	190p	240p
2x23-way	175p	
2x25-way	225p	220p
2x28-way	190p	
1x43-way	260p	
2x43-way	365p	
1x77-way	600p	
S100 Conn		600p

### TEST CLIPS

14-pin 275p 40-pin £8 16-pin £3



# £180: A RECORD FOR DISC DRIVES?

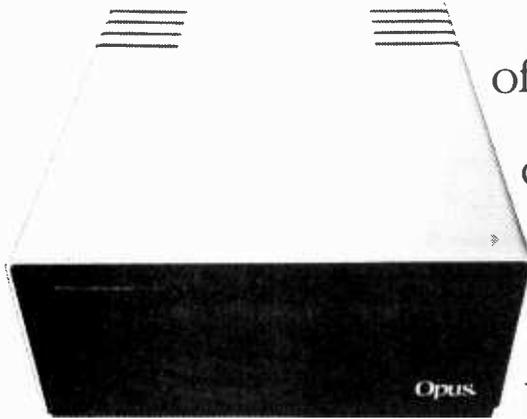

Opus are able to offer a limited quantity of 5 1/4" Slimline Double Sided 40 Track Drives. Formatted single density 200K., double density 400K.

And record value at only £179.95 and that includes everything - VAT, carriage and all necessary leads.

You can order by post (see coupon below) or direct at our showroom.

## OPUS 3" MICRODRIVE.

Double Sided 40 Track Drive 1/2 Megabyte Unformatted.

- Twice the capacity on line of other available drives
- 200K. Single Density - 400K. Double Density
- Ex-stock delivery
- 3 ms. access time
- Lowest power consumption - direct drive
- Includes case, leads and utilities disc
- Totally compatible with 5 1/4" drives

Single Drive £229.95. Dual Drive £459.95.

## 5 1/4" JAPANESE DISC DRIVES.

### SINGLE DRIVE.

Opus 5401 Single Sided 40 Track - 250K. Unformatted. Formatted: 100K. Single Density, 200K. Double Density. £179.95

Opus 5402 Double Sided 40 Track - 500K. Unformatted. Formatted: 200K. Single Density, 400K. Double Density. £229.95

Opus 5802 Double Sided 80 Track - 1 Megabyte Unformatted. Formatted: 400K. Single Density, 800K. Double Density. £299.95

- Switchable 80/40 Track.
- 1/2 Height
  - Includes case, leads and utilities disc
  - Fast access time
  - State of the Art Technology
  - Ex-stock delivery
  - Low power consumption

### DUAL DRIVES.

All Dual Drives are metal cased with separate power supply.

Opus Dual 5401D. Single Sided 40 Track, 200K./400K. on line. £379.50

Opus Dual 5402D. Doubled Sided 40 Track, 400K./800K. on line. £459.95

Opus Dual 5802D. Double Sided 80 Track, 800K./1.6 Megabyte on line. £599.95

## MONITORS.

12" Green Screen £89.95

12" Amber Screen £99.95

Lead to connect to BBC Micro £3.95


• Ex-stock delivery • 24MHz Bandwidth • Limited quantity

14" JVC Colour Monitor - Med. Res. £187.39

14" JVC Colour Monitor - High Res. £279.39
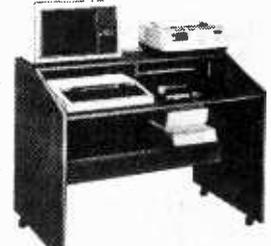
## THE ORGANISER DESK.

- Top shelf for Monitor/Printer
  - Large Desk Top Area
  - Lower Shelf for Paper/Book Storage
  - Teak Finish
  - On Casters
  - Self Assembly
  - Ample room in front of the shelf for you to sit comfortably.
- Only £59.95



## FLOPPY DISCS.

3" Cartridges £5.75 each or £25.95 for 5.

5 1/4" Discs - with full 5 year warranty + free plastic library case.

S/S S/D £19.95 for 10

S/S D/D £23.95 for 10

D/S D/D £26.95 for 10

8" Discs.

S/S S/D £21.50.

S/S D/D £28.50.

D/S D/D £29.95.

## OPUS SUPPLIES LTD.

158 Camberwell Road, London SE5 0EE.

## STOP PRESS.

Double Density filing system available.

Opening hours: 9.00-6.00 Monday-Friday, 9.00-1.30p.m. Saturday.

GOVERNMENT & EDUCATION DISCOUNTS GIVEN.

QUANTITY DISCOUNTS GIVEN. DEALER ENQUIRIES INVITED.

To: Opus Supplies Ltd., 158 Camberwell Road, London SE5 0EE. Please send me:

\_\_\_ 5 1/4" Slimline Drive(s) £179.95 (each) (inc. VAT, carriage and all leads).

Opus 3" Microdrive (s) at:  
\_\_\_ Single Drive £229.95 (each)  
\_\_\_ Double Drive £459.95 (each)

5 1/4" Japanese Disc Drive (s) at:  
\_\_\_ Opus 5401 £179.95 (each)  
\_\_\_ Opus 5402 £229.95 (each)  
\_\_\_ Opus 5802 £299.95 (each)  
\_\_\_ Opus Dual 5401D £379.50 (each)  
\_\_\_ Opus Dual 5402D £459.95 (each)  
\_\_\_ Opus Dual 5802D £599.95 (each)

Monitor (s) at:  
\_\_\_ 12" Green Screen £89.95 (each)

\_\_\_ 12" Amber Screen £99.95 (each)  
\_\_\_ Lead to connect to BBC Micro £3.95 (each)  
\_\_\_ 14" JVC Col. Mon. Med. Res. £187.39 (each)  
\_\_\_ 14" JVC Col. Mon. High Res. £279.39 (each)  
\_\_\_ Organiser Desk (s) at only £59.95 (each)

Floppy Disc (s) at:  
\_\_\_ 3" Cartridges £5.75 (each) or 5 for £25.95  
\_\_\_ 5 1/4" Discs  
\_\_\_ S/S S/D £19.95 for 10  
\_\_\_ S/S D/D £23.95 for 10  
\_\_\_ D/S D/D £26.95 for 10  
\_\_\_ S/S 80 Track £29.00 for 10  
\_\_\_ D/S 80 Track £31.95 for 10  
\_\_\_ 8" Discs  
\_\_\_ S/S S/D £21.50 for 10  
\_\_\_ S/S D/D £28.50 for 10  
\_\_\_ D/S D/D £29.95 for 10

All prices include VAT and carriage.

I enclose a cheque for £..... Or please debit my credit card account with the amount of £..... My Access/Barclaycard (please tick) No. is \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_ (W/W/4)

Telephone \_\_\_\_\_

**Opus.**  
Opus Supplies Ltd.

WW - 061 FOR FURTHER DETAILS

**Editor:**

PHILIP DARRINGTON  
01-661 3128

**Deputy Editor:**

GEOFFREY SHORTER, B.Sc.  
01-661 8639

**Technical Editor:**

MARTIN ECCLES  
01-661 8638

**Projects Editor:**

RICHARD LAMBLEY  
01-661 3039

**News Editor:**

DAVID SCOBIE  
01-661 8632

**Drawing Office Manager:**

ROGER GOODMAN  
01-661 8690

**Technical Illustrator:**

BETTY PALMER

**Advertisement Manager:**

BOB NIBBS, A.C.I.I.  
01-661 3130

BARBARA MILLER  
01-661 8640

ASHLEY WALLIS  
01-661 8641

**Northern Sales:**

HARRY AIKEN  
061-872 8861

**Midland Sales:**

BASIL MCGOWAN  
021-356 4838

**Classified Manager:**

BRIAN DURRANT  
01-661 3106

IAN FAUX  
01-661 3033

**Production:**

BRIAN BANNISTER  
(Make-up and copy)  
01-661 8648

**Publishing Director**

DAVID MONTGOMERY  
01-661 3241

## So you want to be an author?

A steady stream of letters and telephone calls to *Wireless World* continues to draw our attention to the diffidence with which some would-be contributors approach the task of writing for publication. There are evidently fears that their writing style might not compare well with some of our more august authors and that the requirements for submitted articles are so rigid that they cannot hope to do the work properly. An impression one also gains is that they are sometimes deterred from exposing their work to the public gaze by the possibility of subsequent criticism in the Letters pages.

There is no shortage of material to publish, but the enquiries do indicate that a large number of potential contributors are holding back, and that new blood to top up the bank of established authors is congealing in silence.

Perhaps these dark fears can be dispelled. A short note giving guidance to contributors appeared some time ago, but a great many people will not have seen it: a reiteration may not, therefore, be out of place.

First of all, please do not think that, because your writing style owes nothing to the great literary figures, your work will be rejected. It is a well-known fact that there are engineers and there are writers and not very often engineers who are also writers. The editorial team is perfectly happy to grind the sharp corners off awkward prose, to translate stilted English into the readable variety and to correct spelling and punctuation. The essential requirement is that the submitted piece should contain *all* necessary information, including details of any difficult to obtain components, if the

piece is a design for construction.

This is not to say that authors should not take the trouble to write good English — we cheer when a good, readable article comes in — but we can cope with writing that needs improvement. And please, do not imagine that polysyllables and a passive writing style is needed. Formality may have its place in company reports (though even then, it makes heavy reading), but in *Wireless World* we prefer the simple style, the active voice and the minimum of the 'it can be seen that' kind of remark. The function of technical writing is to explain, not to demonstrate the author's knowledge.

Drawings must be clear, but not necessarily masterpieces of draughtsmanship: if they are readable, that is all we ask. Photographs can be slides, glossy prints or negatives. To be helpful, illustrations and captions are better separated from the text, which ideally should be typed double-spaced with wide margins to allow room for our annotations and printer's instructions.

The comment on published work often seen in letters from readers need not be taken as a direct attack on one's ancestry and prospects for the after-life — the letters usually contain useful information and are quite impersonal (on the whole, at any rate) often offering very worthwhile suggestions for improvement or containing comment which clarifies obscurities in the original piece.

Articles published in *Wireless World* are, or should be, interesting, informative, instructive and entertaining. If yours is one or all of these, do not hang back — let us have a look: you have nothing to lose.

# COMMUNICATIONS

## Communicating pictures

In the UK there has been considerable soul-searching over the award of 12 interim cable tv licences to 37 applicants. Similarly, the IBA is required by Parliament to pursue what some people regard as a long and tortuous path in awarding the ITV and ILR programme contracts. But at least the UK has not yet had to face up to the mammoth number of applications flooding into the FCC in respect of "low-power television", "multi-channel multipoint distribution service", over-air "subscription tv", plus all those who see a viable future in direct broadcast satellites, high-definition television, "instructional tv fixed service", "satellite master-antenna systems", teletext, videotext, electronic mail and the like.

FCC already face a backlog of about 8000 low-power tv applications to run virtually de-regulated "secondary status" tv stations limited to 10 watts transmitter power on u.h.f. and 1kW on v.h.f. Many of the applications are to change current low-power, transposer-type, gap-filling relay stations to permit insertion of local programme material. To try and clear some of the backlog FCC have instituted a form of "lottery" to pick winners for popular areas, though based on the idea of giving those applicants who meet most closely the desired criteria more "chance" of being drawn out of the hat than others — a concept that might not go down too well in the UK. The lottery is "rigged" to favour applications that promote minority ownership and diversity. Like a roulette wheel, some numbers are more likely to turn up! There are also over 20,000 applicants for a limited number of MMDS frequency channels. This technique, fast rivaling cable, uses omnidirectional microwave (2 GHz) transmitters, often in conjunction with satellite feeds, to send video or other services direct to subscribers. It is regarded by FCC as a "common-carrier" system. FCC have been allocating only two MMDS channels to any given market, but has been pressurised to increase this to 14 channels in each of the "top 50" markets.

## More homes

Distribution of tv and radio programmes over dedicated distribution satellites, initially to provide feeds for cable systems, is rapidly extending in the USA to all multipoint services, including major tv networks who until recently have remained faithful to long-established terrestrial microwave links. Television receive-only dish aerials are located alongside many American stations, including over 500 commercial tv stations, several with more than one dish to receive from different satellites, and many more than this

are installed for the cable networks.

Despite the large increase in American subscribers to cable tv, from about 7 million to over 30 million in the past ten years, the effect on audiences for broadcast tv from the network affiliate and independent stations has been far less than predicted. One reason for this is the continued increase in the total of American "tv homes", known as "HUT" (homes using tv). In the past decade this has risen from about 65 million to well over 80 million. One result is that network tv has been achieving its largest audiences ever with, for example, the final episode of M.A.S.H. on February 28, 1983, reaching the first-ever national audience of over 50-million viewers.

The reasons for the continued increase in tv homes in the USA — a rate of increase far greater than in the UK — appears to reflect a smaller average size of households rather than growth of total population. The average size of households has dropped by about 12 per cent in the past decade and is now only two-thirds the size it was in the 1930s. Three main factors account for this: the declining birth-rate; fewer old people living with grown-up children; and an 80 per cent increase in the past decade of "single parent families" reflecting the high divorce rate. These factors have had the unanticipated effect of cushioning the commercial broadcasters against audience fragmentation by cable, as well as having a significant impact on the American consumer electronics market.

In the UK, tv licence totals at the end of September 1983 were: black-and-white 3,575,234; colour 14,925,023; old people's homes 539,000; and dealers' demonstration 20,000. This gives a UK HUT of approximately 19 million, plus the unknown number of licence evaders. At the end of 1972 the corresponding figures were: colour 2,815,703; black-and-white 14,182,880 and a HUT of roughly 17.2 million, plus the licence evaders. Both in the USA and UK there has, of course, been a large increase in the number of multi-set homes.

## Sensitive at 3 mm

A cooled 75-95 GHz receiver built at Helsinki University for use with the Finnish 13.7-m diameter radiotelescope of very high profile accuracy is believed to be one of the most sensitive millimetric receivers so far built for use at wavelengths of the order of 3mm.

The double-sideband noise temperature, when used as a continuum receiver with a bandwidth of 500MHz, is about 100K. Since no provision is made for rejection of the image band, the s.s.b. noise temperature for spectral line observations is rather over 200K.

The front-end comprises a Schottky

mixer-diode chip and 1.4 GHz i.f. amplifier cooled to 20K with a closed-cycle helium refrigerator. The i.f. amplifier, provided by the University of Massachusetts, uses two Mitsubishi MGF 1412 GaAs fet devices with a noise temperature of about 50K at room temperature and 12K when cooled to 20K. The local oscillator is a klystron.

## Secretly on satellite

Portable communications equipment displayed recently on Russian television is further evidence of the growing use of satellite systems for long-distance clandestine communications. The American-made equipment included a keyboard transmission system apparently for enciphering and sending text in high-speed bursts. The equipment was seized by the Russians from an English "journalist" shot dead while using the identity "Stuart Bodman" inside Afghanistan on what would appear to have been a freelance mission on behalf of an American intelligence agency. Similarly, a few months ago an American diplomat was expelled from the USSR after it was alleged that he was caught communicating via satellite from his car. The portable communications equipment, believed to have been manufactured by Motorola, appears to be much smaller and lighter than the man-pack satellite equipment made by Ferranti, based on work at the Royal Radar and Signals Establishment. A year or two ago an American communications engineer presented a conference paper suggesting that the two-way long-distance radio "wrist-watch" could move before long from the realms of tv spy dramas to reality.

However an indication that intelligence agencies still rely also on more traditional h.f. systems is evident from recent full-page advertisements in American amateur-radio journals seeking to recruit more technicians and operators for the CIA, proudly proclaiming itself to be "an equal opportunity employer."

The major advantage of using satellites for clandestine operation must be the restricted area from which the exact location of the ground equipment could be determined by means of direction-finding. Extremely compact and lightweight equipment would suffice to communicate via a low-orbit satellite but the equipment seized in Afghanistan must be approaching the practical limits with current technology for use with geo-stationary satellites.

The October Communications Commentary mentioned military interest in millimetric communications in frequency bands of very high attenuation. This is underlined by the Norden 54 GHz omnidirectional radio system noted in "Jane's Military Communications 1983" developed "to take advantage of the signal-

# COMMENTARY

hiding characteristics of this frequency band". With a restricted range of about 1.6km (omni-directional aerials at each end) it is claimed to reduce probability of interception or disruption by jamming. Norden also make hand-held 54 GHz equipment.

## Giant space platforms

In the 1983 Shoenberg Memorial Lecture of the Royal Television Society, Dr Delbert Smith, an American lawyer with special interest in space communications, forecast the early demise of single-purpose satellites launched by expendable rockets and the development of multi-purpose space platforms the size of a couple of football pitches, each carrying a full range of telecommunications facilities and beaming down 40 channels of DBS television from large parabolic aerial dishes. The platforms, he believes, will be assembled in low orbit, using material brought up in the cargo bays of several Space Shuttle-type launchers. The assembled platforms would then be shot into geo-stationary orbit and serviced by unmanned repair vehicles, using complex robotics technology to replace complete transponders, and sent up from manned space laboratories. Just six large platforms could cater for virtually all telecommunications and tv requirements up to the end of the century.

But he also forecast the creation of new multinational corporations and the growth of specialised space insurance business. Attempts to "regulate" tv broadcasting across frontiers would fail and the concept of "prior consent" on the part of the target country could not be enforced, he believes. Voice of America, he hinted, are actively planning radio and tv satellite broadcasting to foreign countries. The platforms, with multiple ownership and privately funded, will challenge PTT and Intelsat-type telecommunications monopolies, and bring many legal problems to lawyers.

## AMATEUR RADIO

### First DBS news

What is being claimed as the "first ever" transmission of a regular radio new service intended for direct reception from space took place on October 15. This was launched by British radio amateurs using the callsign GB2RS via the special H1 channel (145.975 MHz) using s.s.b. (upper sideband).

The 15-minute bulletin was compiled jointly by David Gough, G6EFD, Kim Mair and Ron Broadbent, G3AAJ and

recorded on tape by John Nelson, G4FRX. The tape was then transmitted by Graham Shirville, G3VZV of Milton Bryan, Bedfordshire.

Coverage area of Oscar 10 in its highly elliptical orbit varies with its position but typically these broadcasts should be receivable over much of Europe and Asia or alternatively in Europe and the eastern seaboard of North America. Reception reports of these Sunday morning and afternoon transmissions (times vary to suit orbital data) are needed and should be sent to RSGB or AMSAT UK, London E12 5EQ. Callsign is likely to change to GB2AUK.

Amateur radio provided emergency communications out of Grenada during the initial stages of the American invasion of the island. The DTI does not encourage UK amateurs to become involved in such communications and has reminded them that if they do receive emergency traffic on any occasion they should contact the Radio Regulatory Division (01-275 3000) before passing on any third party emergency messages to individuals or to the media.

The University of Surrey has estimated that during the two years in orbit of UOSAT some 5000 amateur, educational and professional ground stations have received data from the satellite. A booklet on UOSAT has recently been distributed to schools. The UOSAT team is currently building, to a tight timescale, a second satellite to develop the objectives of the first. Subject to acceptance of the proposals by NASA there is a possibility of a launch early in 1984.

G. Shirville, G3VZV, as a result of observations during a recent period of high activity by amateur television stations using 435 MHz, is convinced that serious mutual interference between the tv amateurs and those using 435 MHz as a satellite up-link frequency is unlikely to occur. There remains a potential problem with the Oscar 10 transponder which has a 436 MHz downlink.

### More on "ten"?

The RSGB, concerned with intrusion by CB operators into the "exclusive" 28.0 to 29.7 MHz amateur band, is seeking to encourage more legal use of this band during the forthcoming period of low solar activity. From about 1984-87, reliable long-distance contacts via ionospheric reflection are likely to be possible only rarely; nevertheless the band remains entirely suitable for down-links from amateur satellites; for medium-distance contacts using Sporadic E layers; auroral reflection; and by meteor scatter. It can also be used for extended-range and short-range fixed and mobile communications, on ground wave or by using ducts, etc. Efforts are being made to introduce a band plan that includes a degree of channelling for nar-

row-band frequency modulation, including provision for 29 MHz repeaters. Despite declining solar activity this winter has seen good "openings" on 28 MHz with 14 beacons, including one in Antarctica audible on October 28.

## Ageless Morse?

The minority of British Class B licensees who have been lobbying to eliminate the Morse test as an essential qualification for h.f. operation continue to seize every opportunity of putting their case and ignoring all counter-arguments. One wonders what they will make of the decision of the French authorities to issue F6 licences valid for h.f. without an obligatory Morse test – but only to persons over 65 years of age. The American ARRL, the largest of the national societies, remains adamant that "It is *wrong* to eliminate the Morse Code requirement in the Amateur Service".

## Here and there

Clive Elliot, G4MBS (ex-G8ADP) who pioneered the use of rain-scatter on 10 GHz for amateur contacts, can now operate mobile or stationary-mobile in all-weather conditions and from convenient high sites by means of a permanently-equipped ex-Army Land Rover. This has a roof-mounted 2.5ft dish aerial controlled from the driver's seat using an aeronautical compass.

The experimental 144 MHz s.s.b. (pilot carrier) repeater, GB3SF, to be located at Sheffield has now been licensed on an experimental basis for one year. The input and output frequencies are 10 kHz on the h.f. side of the R7 repeater channel (145.185 MHz and 145.785 MHz). The frequency off-set is intended to minimise interference to n.b.f.m. repeaters or other users.

RSGM membership at June 30, 1983 totalled 33,868 compared with 32,215 the year before; however, the increase of 1653 required 5498 new members . . . The British Amateur Television Club is to hold its 1984 Convention on May 20 at a larger Post House Hotel complex at Crick, near Rugby . . . Amateur tv activity on the 23cm band appears to be increasing . . . I. Waters, G8ADE has developed an extremely sensitive detector of 15,625 kHz line sync pulses, even when buried under noise, to provide an audible automatic alarm system to monitor for amateur tv activity . . . The British Amateur Radio Teleprinter Group now provides information on Prestel, British Telecom's viewdata service. Page number 8008 2001 . . . A Korean radio amateur, HL1LJ, was a member of the crew of the Boeing 747 (Flight 007) shot down in the Far East.

PAT HAWKER, G3VA

# Computer-controlled XY plotter

*An alternative to expensive, commercial plotters, which is made from easily obtained materials and exhibits a very high performance. Resolution is around 0.002in per step and total cost is less than £100*

The microcomputer is rapidly becoming an essential tool for many engineers. It can be used to perform calculations and repetitive tasks and to help in decision making by detailed analysis of data. However, to do this it must be able to communicate with the outside world. Half the battle is to represent the machine's output in a way which is understandable to humans. It is true to say that a picture paints a thousand words; it is for this reason that an XY plotter is such a useful computer peripheral.

The cost of such a piece of equipment is way beyond the budget of most amateur constructors, so an alternative was sought.

The principle is simple enough: two precision stepper motors move a pen over a sheet of paper. One controls the movement in the X direction whilst the other controls the movement in the Y direction. A facility to lift and drop the pen onto the paper is also added to enable unconnected lines to be drawn. An interface is also included so that the computer can control the movements of the pen.

## Stepper motors

The stepper motors form the central part of the project. Because of this they must be good quality precision motors with sufficient torque to move the pen without slipping or missing steps. A pair of 12V, 200 step-per-revolution, 25oz. in. motors were used in the prototype, purchased from Stewart of Reading at £12 each as second-hand but unused. The cost of new motors is not really justified, as I have been quoted £60 for motors of this type. An alternative source may be scrapped computer peripherals such as printers, disc drives, etc.

The motors used were of the four-pole variety and so have no permanent-magnet rotor. The rotor can be made to rotate by successively energizing each of the four coils in turn, stepping round to face each of the energized coils.

Although the positioning of the coils and the shape of the rotor allow 200 positions per revolution to be obtained by this method, it can be seen that, if two adjacent coils are energized in the following sequence, 1, 1+2, 2, 2+3, 3,... then 400 steps per revolution are obtained. This, combined with a pulley drive wheel of 0.8in circumference, gives a theoretical resolution of 0.002 in per step. The positioning of the pen is not repeatable to

---

by P. N. C. Hill

---

this accuracy but the resolution is greater than the thickness of the pen so perfect curves can be drawn.

## Motor-drive

The operation of stepper motors is by no means straight-forward, as the inductance of the windings combined with the mass of the rotor and associated resonances limit the maximum slip-free acceleration rate, as well as the maximum (and in some cases minimum) step rate.

To achieve the best possible performance from a given motor the driver characteristics must be tailored to suit the requirements of the motor. If the

manufacturers' data is available this task is made considerably easier. However, in the case of the second-hand motors, no data was available, so that trial and error methods had to suffice.

Each motor has four phases and so four identical drivers. The circuit for each of these is shown in Fig. 2.  $Tr_1$  and  $Tr_2$  operate in one of three modes: cutoff, saturation or conduction of a small holding current. The power dissipation in the output transistors is therefore kept to a minimum so no heat sink is required. The open collector t.t.l. buffer,  $B_1$ , will ground the base of  $Tr_1$  when its output is low. This will put both transistors into cutoff. When the buffer output is high, current flows into the base of  $Tr_1$  via  $R_1$  and  $R_2$  so saturating both transistors. If, however, the output of  $B_2$  is low then some of the current that would have flowed into the

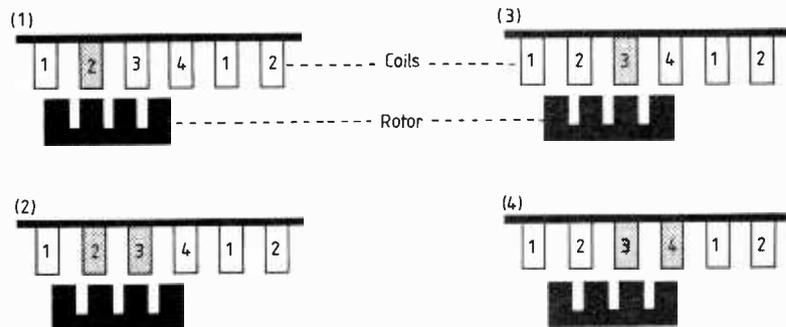


Fig. 1. Internal configuration of a typical four-pole stepper motor. The sequence shows how the half stepping is achieved.

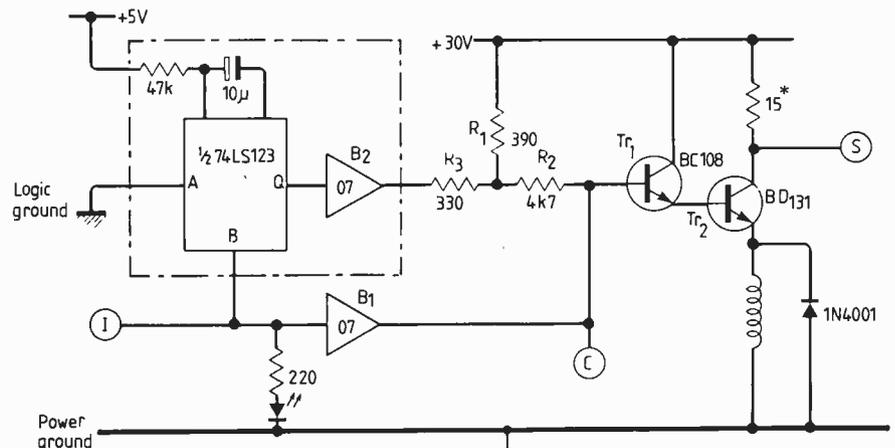


Fig. 2. Motor driver circuit. The enclosed section is required only once for each motor.

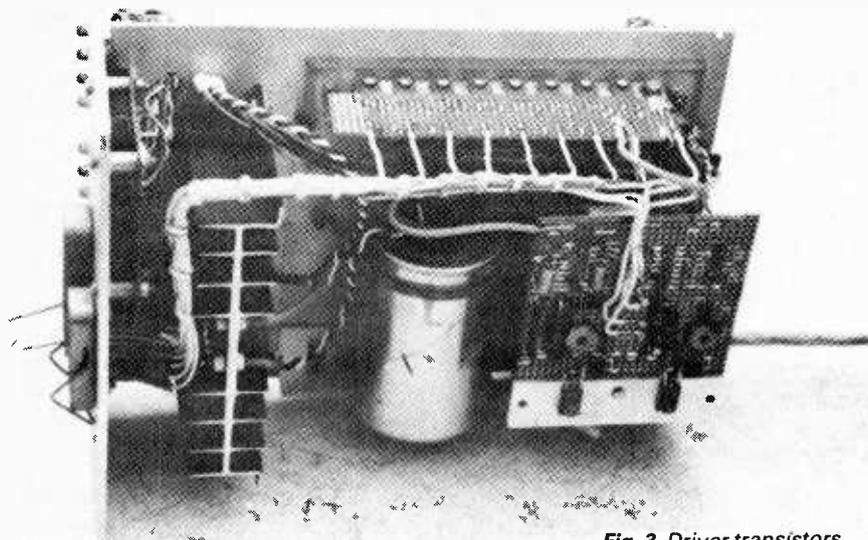


Fig. 3. Driver transistors.

base of  $Tr_2$  is taken by  $R_3$ . This causes a small quiescent current of about 100mA to flow in the stepper motor coil. The ohmic heating in the motor windings is drastically reduced, whilst the low current ensures that the motors do not continue to turn after each step because of momentum. It is the monostable associated with each motor drive circuit that controls the state of  $B_2$  output. Only when a step command is issued is the monostable triggered to deliver a short (100ms) pulse.

The relatively high supply voltage of 30V ensures that the back e.m.f. induced in the motor's coils is quickly overcome whilst the current pulsing ensures that ohmic heating is kept on a minimum. By adjusting the current pulse width and the relationship between  $R_1$ ,  $R_2$ ,  $R_3$ , the optimum performance can be obtained from the stepper motor.

### Driver current limit

The driver circuit was designed to be usable with almost any four-pole stepper motor, as it was intended to use the finished product as a piece of test equipment for future projects using stepper motors. It was partly for this reason that protective circuitry was included to prevent damage due to shorted outputs etc. Figure 4 shows how this was done. The op-amp ensures that a sharp cutoff is obtained when the current threshold is reached.

### Control circuitry

As was mentioned before, the sequence in which the current is switched in the coils controls the direction of movement of the motor. Figure 5 shows the required sequence for the four-pole stepper motors. It is simple in nature, but it must be possible to stop at any point and then reverse the process so that the motors can move both forward and backwards. The first thought, as regards the implementation, was to use an up-down counter with combinational logic converting the three-bit binary output into the correct signals to control the driver

stages. However, the realisation of this is excessively complicated and requires far too many chips to be practical, particularly as two such control circuits are needed.

The control circuit obviously has eight outputs (four for each motor) so a sequential circuit built with an eight bit r.o.m. would be suitable.

A rom can be used as a sequential controller by connecting its outputs back to some of its inputs via an edge-triggered latch. Each time the latch is triggered the present state of the outputs is fed back to the inputs. The new state of the outputs then depends on the contents of the rom at the location addressed. Figure 6 shows the block diagram of a typical rom-based controller system.

### Controller implementation

The implementation of both motor controllers in one eight-bit rom is slightly more involved. Both must operate independently despite the coding for each being in the same area of memory, the contents of the coding for each being in the same area of memory. The contents of each memory cell can be represented by a two-digit hex. number. The left hand digit thus refers to one of the controllers whilst the right hand digit refers to the other. Each byte of memory thus consists of two

unconnected nibbles of data. The coding is arranged so that each controller can operate totally independently, and the code must actually take care of all possible states of one controller for every state of the other. The result is one kilobyte of code, the listing of which is given in Appendix 1.

Figure 8 shows the controller circuit. The two address lines A8, A9 are used as direction control inputs. Outputs from the latches are connected to the driver stages as described earlier. The facility to move the plotter manually is also included. The output of the 555 astable is gated to either or both of the clock inputs on the latches when the appropriate switches are closed, its frequency being decreased when the centre button on the front panel is depressed, so both fast and slow manual adjustment is possible.

### Pen lift control

The pens can be lifted off the paper by energizing the electro-magnet concerned. Current pulsing is adopted here too to reduce ohmic heating. A short, high-current pulse ensures that the pen is lifted smartly off the paper where it is kept by a much lower holding current. The circuit is shown in Fig. 9, and the best performance is once again achieved by suitable choice of  $R_5$ ,  $R_6$  and the current pulse width.

### Plotter mechanics

Two precision stepper motors form the basis of the plotter. However, if the mechanics of the plotter are inadequate then their resolution and repeatability are wasted.

Rather than move the pen in both the X and Y directions it is obviously very much easier to limit the movement to one of the directions whilst moving the paper in the other. Various slider mechanisms were tried, but all proved to limit the perform-

Coil 1	Coil 2	Coil 3	Coil 4	
0	0	0	1	
0	0	1	1	
0	0	1	0	
0	1	1	0	
0	1	0	0	
1	1	0	0	
1	0	0	0	
1	0	0	1	

Fig. 5. Sequence for energizing stepper motor windings.

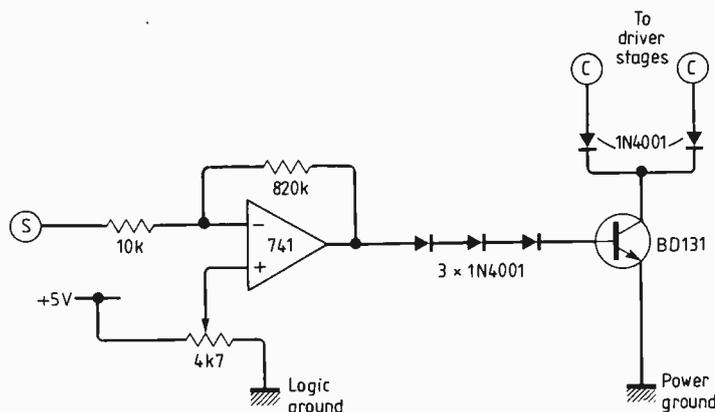


Fig. 4. Driver protection circuitry.  $RV_1$  sets maximum output current.

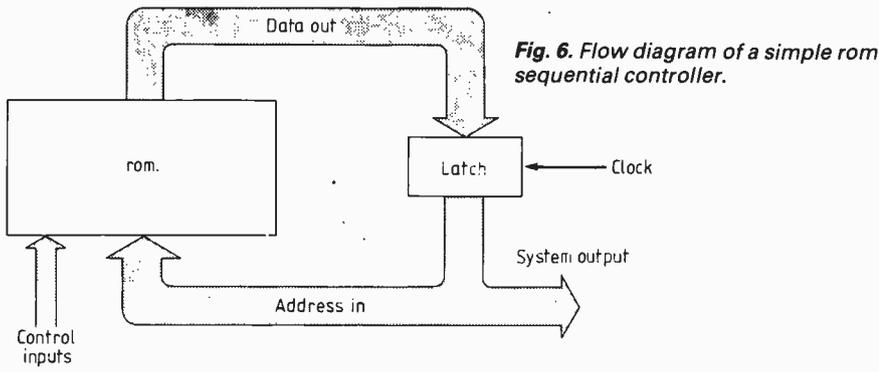


Fig. 6. Flow diagram of a simple rom sequential controller.

Address	Data (reverse) $A_4=0$	Data (forward) $A_4=1$
0000	0001 d	0001 d
0001	0011	1001
0010	0110	0011
0011	0010	0001
0100	1100	0110
0101	0001 d	0001 d
0110	0100	0010
0111	0001 d	0001 d
1000	1001	1100
1001	0001	1000
1010	0001 d	0001 d
1011	0001 d	0001 d
1100	1000	0100
1101	0001 d	0001 d
1110	0001 d	0001 d
1111	0001 d	0001 d

Fig. 7. Rom coding for a simple, four-output sequencer. The four outputs are fed back to the four least significant address inputs via edge-triggered latches. Each time the latches are triggered the system moves onto the next state. A change from the forward to the reverse sequence is accomplished by changing the state of address line  $A_4$ .

All locations marked 'd' are dummies and are never normally used. However they point back into the sequence to enable the system to be self-starting on power up.

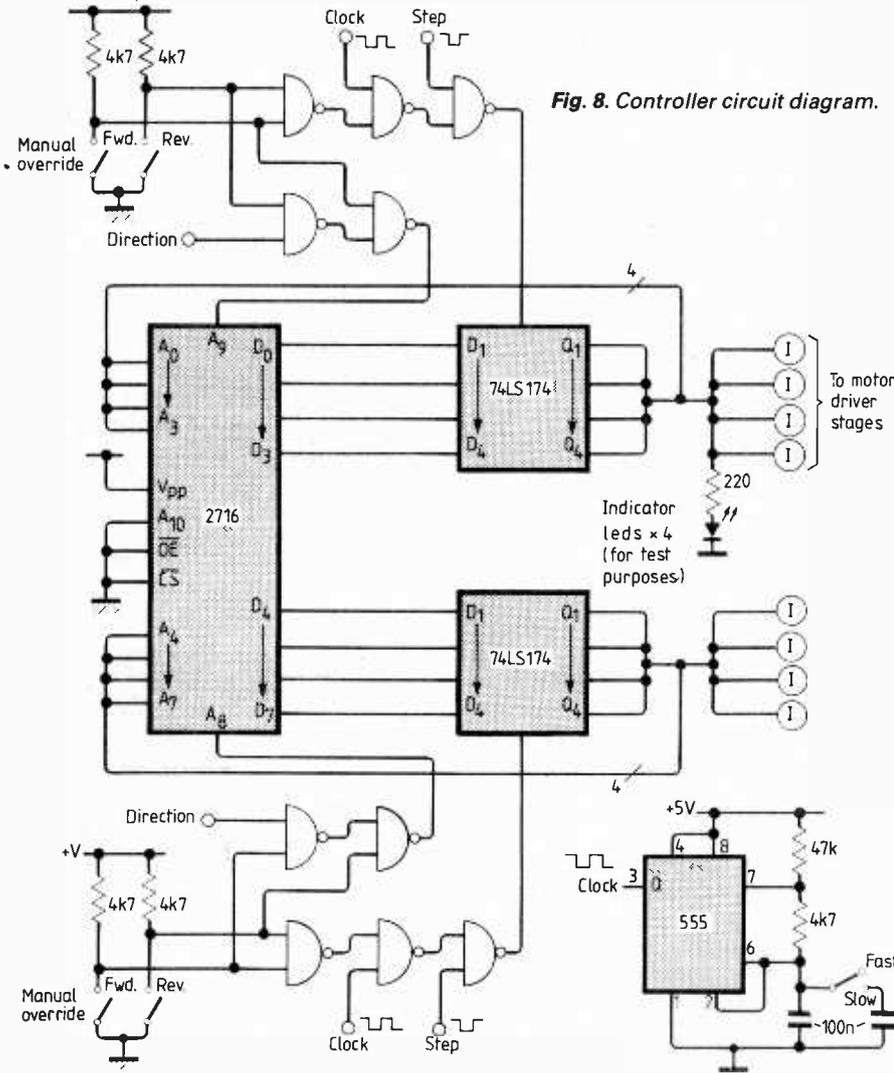


Fig. 8. Controller circuit diagram.

ance of the plotter because of excessive friction. The simplest solution turned out to be the best: the principle can be seen in Fig. 11. The moving part of the slider rides on two ball-bearings which in turn ride on a narrower channel fixed to the base of the machine. As the lower fixed part of the slider is narrower than the moving part, the ball-bearings move less relative to the upper channel than to the lower channel. This, in turn, means that the upper channel can be much shorter than the lower channel, making the entire plotter much more compact. The aluminium mouldings used were originally intended for use as curtain rails, of which several types are available, all of which conveniently differ slightly in size, so careful selection will be required. A local bicycle shop will doubtless be able to help with the ball-bearings. The resulting slider mechanism is ideal as both friction and stiction are very low, the only drawback being that the mechanism does not hold together when turned upside down!

The sliding trollies are kept upright by small wheels. A second channel and ball-bearings was not used as this would require very accurate alignment of both channels. The wheels run on a flat metal surface and are made from plastic (tap washers) so that they rotate rather than slide. Very small (1/4in) ball races form the wheel bearings.

A flat Perspex sheet was used for the plotter bed. This has a sliding rail at one end and two sets of wheels at the other and is mounted in a metal tray which forms the base of the machine. The pen-carriage slider was then fixed on stilts above the plotter bed. The carriage then fits on above this so that it slides perpendicular to the movement of the bed. See Fig. 12.

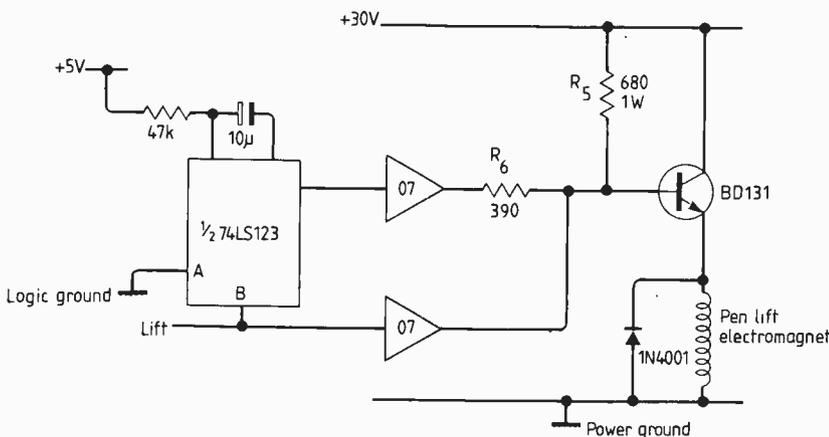


Fig. 9. Pen lift control electronics.

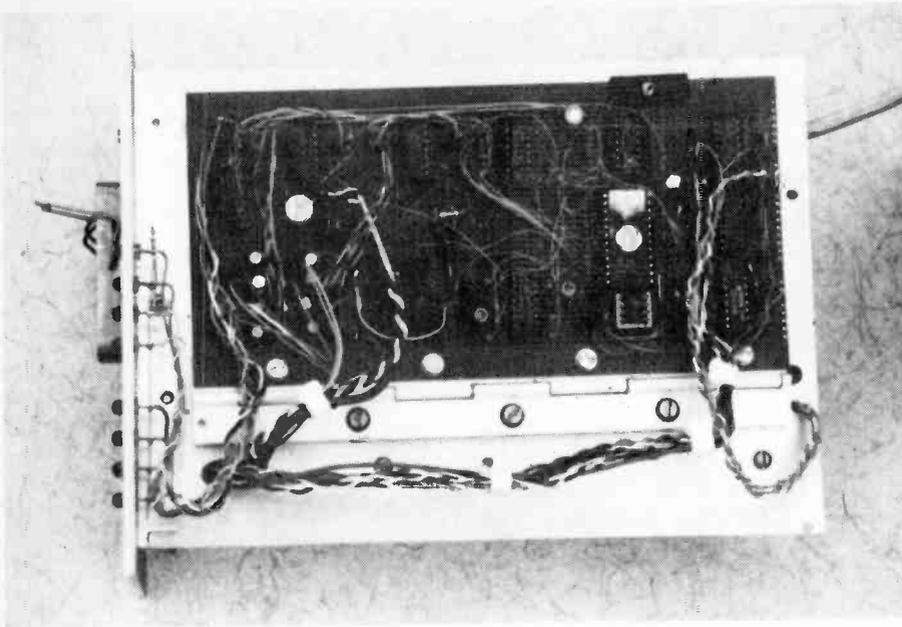


Fig. 10. Controller p.c.b. Interconnections are made with wire-wrap wire from pins on the component side.

### Stepper-motor mountings

The motors are mounted on the carriages which they move so that there is sufficient weight to keep the ball-bearing sliders in place. This extra weight limits the acceleration of the plotter and so the average plotting speed. However, it does not affect resolution or repeatability. The motors drive small flat pulleys round which is wrapped a thin piece of thread (cotton button-hole thread works best) which is kept in tension by a small stiff spring at one end. These pulleys must be of accurately known circumference if scaled plots are required. Figure 13 shows the suggested profile. To prevent slipping, the active area should be lightly knurled, and it should also be noted that in order to prevent the carriage twisting, the pulley and thread should be close to the ball-bearing slider. The wires running to the motors can be fairly thin and flexible so

that they do not hinder the movement of the carriage.

### Pen and pen mounting

Several types of marker were tried but none were ideal. Felt- and fibre-tipped pens produced lines of different thickness, depending on drawing speed. Since the speed will vary according to the nature of the shape being drawn, these pens were unsuitable. Ball-pens all require pressure to function correctly but the resulting friction affects the plotter's performance. The best choice so far has been drawing pens of the Rotring kind, which do not blotch and produce lines of known constant thickness. However, they do clog if left with their caps off for any length of time.

The pens write on the paper under their own weight and are lifted off the paper by an electromagnet, the mechanics of which can be seen in Fig. 14 and in the photo-

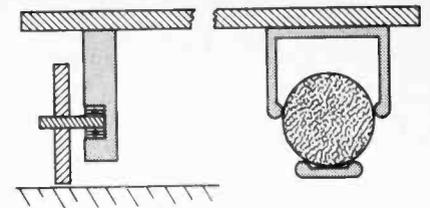


Fig. 11. Slider mechanism. Two ball-bearings are used in each slider.

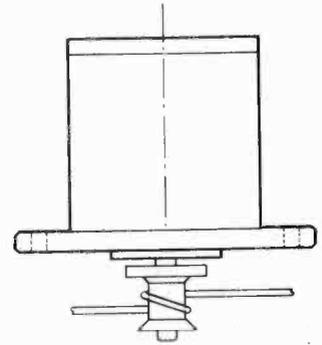


Fig. 13. Shows the pulley and thread arrangement for one of the stepper motors.

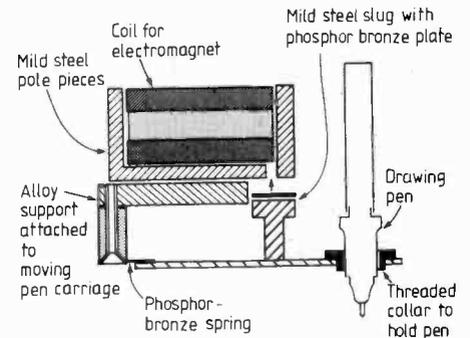


Fig. 14. Cross-section of pen lifting mechanism. More than one can be used to provide different coloured pens.

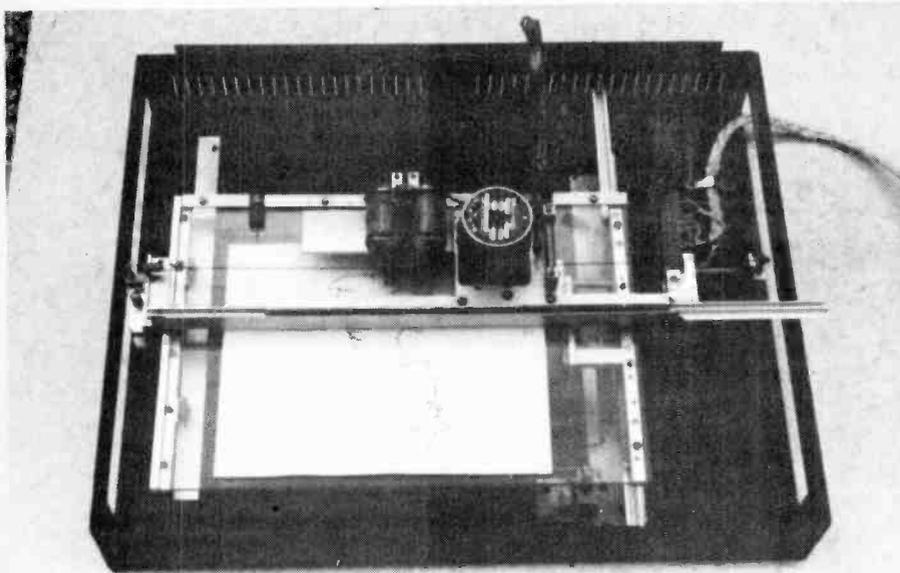


Fig. 12. Shows the completed plotter with a map of a well known country drawn on the machine earlier.

graph in Fig. 15. The pen screws into a metal ring which is soldered to the brass lever. Threaded collars can be bought from Rotring stockists as adapter rings.

The mild steel slug is attracted to the poles of the electromagnet, but is prevented from making direct contact by a thin piece of phosphor-bronze soldered to its surface, to prevent a closed magnetic path from being formed, which would cause the slug to stick even when the power is switched off. To ensure that the pen is picked up smartly, the electromagnet is pulsed hard on for a few hundred milliseconds. The current is then reduced to a lower holding value to prevent overheating of the coil.

### Computer interface

The computer is able to control every movement of the pen over the paper, but the problem comes when one has to describe to the computer what the picture required looks like. One of the most suitable languages is probably Forth, which is a control-based language, which is made for such applications. Words can be defined to perform specific rudimentary tasks such as line and arc or circle drawing.

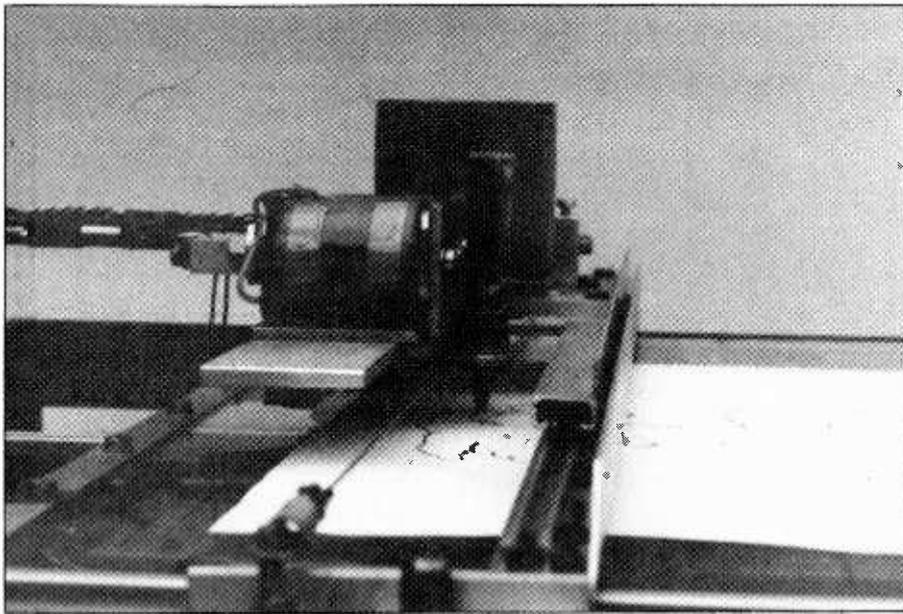


Fig. 15. The pen carriage with the lifting mechanism. The stepper motor is visible behind the pens.

Once these words are in the dictionary, they can be used as the building blocks for more complex words, which may do anything from drawing a square to plotting a map of the world.

The word used to draw straight lines might be given two parameters  $x, y$ . Execution will cause the pen to move from its current position to the point  $x, y$  relative to where it was before. The pen must draw the best possible approximation of a straight line and end up at exactly the

point  $x, y$ . Failure to ensure the latter will lead to accumulating errors when  $x$  and  $y$  have no common factors. The easiest technique used so far is to approximate successively the gradient of the line being drawn to the required gradient. If the line is too steep then an extra step in the  $x$  direction is made. Conversely, if the line is too shallow then the pen is moved a step in the  $y$  direction. This is illustrated in Fig 16: the method is not perfect, so any suggestions would be most welcome.

The circle drawing word is more of a problem. If a floating point language is available, then a plot of  $x = \text{SQR}(r^2 - y^2)$  will suffice. However, if an integer language such as Forth is being used, then all calculations must be done in fixed-point format, using a numerical method for the function evaluation. In order to avoid compounding errors all calculations should be done with sufficient accuracy (double precision arithmetic).

It is also important to ensure that every time the pen is moved a record of the number of steps moved is kept. This number is then subtracted from the required number to leave a fraction as a

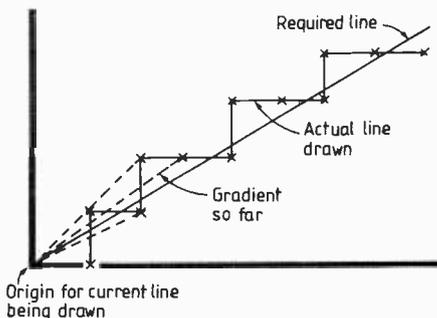


Fig. 16. Plotting a straight line by approximation of the gradient.

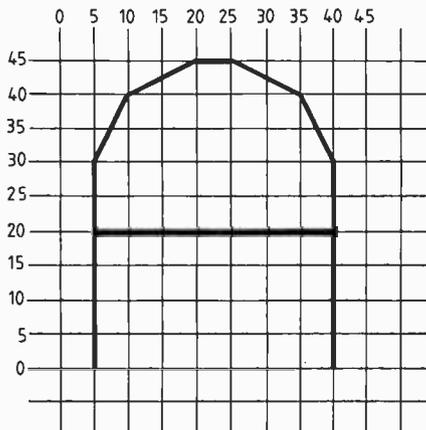


Fig. 17. Makeup of a character.

x coordinate	y coordinate	
5	0	Move to start of letter
255	255	Pen down
0	30	
5	10	
10	5	Top of the letter
5	0	
10	-5	
5	-10	
0	-10	
255	254	Pen up
-35	0	Move to start of horizontal
255	255	Pen down
35	0	Draw horizontal
0	-20	Complete the upright
255	254	Pen up
5	0	Move to start of next character

Fig. 18. Make-up of characters by approximation of shape with short straight lines. The table shows the required sequence to reproduce the letter 'A'.

ABCDEFGHIJKLMNOPQRSTUVWXYZ 1234567890

Fig. 19. An example of lettering drawn by the plotter. The alphabet was drawn with a resolution of 200 steps per revolution. The steps are just discernible.

remainder. This is then added into the calculation following to ensure that errors do not accumulate.

### Drawing alphanumeric

Although alphanumerics consist of a combination of curves and straight lines, a good character set can be made up by using straight lines only. This naturally makes the software very much easier.

The entire character set and more can be held in a few kilobytes of memory. Each pair of memory locations contain the  $x$  and  $y$  coordinates of the new position of the pen relative to its previous position. In addition various control codes are added to lift and drop the pen(s). For example, FFH and FEH can be used as control codes because it is unlikely that either will be used for coordinates.

Figures 17 and 18 show how one letter is coded. The entire ASCII character set can be coded in such a way with the least complicated characters taking up the least space in the memory table. Once the basic shape of all the characters has been recorded in the computer the software which uses the data to move the pen can be made to manipulate the shapes of the characters.

Character spacing can be altered by moving the pen between each character. The line along which the characters are drawn can be rotated by using simple matrix algebra. Characters can be slanted to produce italics by manipulating the coordinates as follows:  $x = x + c * y$ . The larger the value of 'c', the more the character slopes.

The size and aspect ratio can be altered by multiplying the  $x$  and  $y$  coordinates by constants.

The artwork shown in Fig. 21 was partly drawn on the plotter. All the bus interconnections along the lines of memory chips were plotted as was the lettering. The individual connections at the end of the board and the thickened supply lines were drawn in later by hand. As the lettering indicates, the design is laterally reversed as this is the pattern seen from the component side which is naturally the easiest side from which to design. It would not be difficult

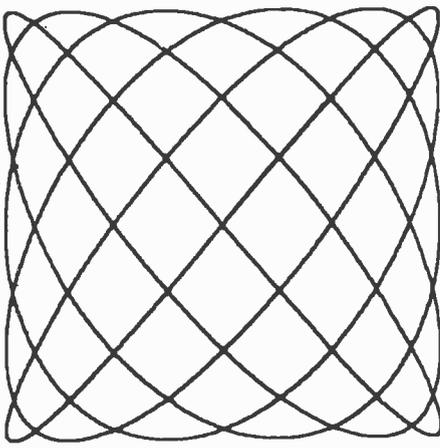


Fig. 20. Lissajous figure plotted from floating point Basic.

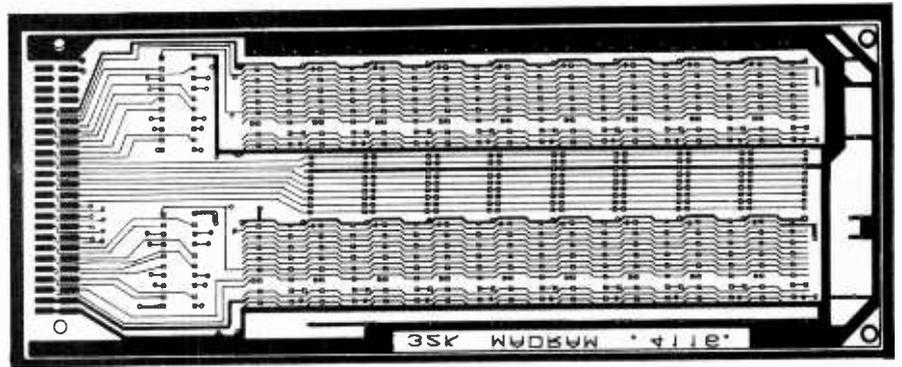


Fig. 21. Artwork for a memory board. All bus interconnections were drawn by the plotter.

to draw the design directly onto the bare copper board with etch resistant ink from one of the commonly available p.c.b. pens. However, this was not done, as photographic facilities were available at the time.

### Copying diagrams

The map shown on the picture of the plotter in Fig 12, was copied from the back of a holiday brochure. The original was placed on the plotter bed and an empty pen was used as a pointer. The pen was then moved over the outline of the map under the control of a joystick and some simple software. The further the joystick was moved away from the centre position the larger each 'jump' was in that direction. The series of small straight lines was stored in the computer's memory in much the same way as for the alphanumeric character generator. When the collection of numbers was played back, again with much the same software as for the alphanumerics, the map was reproduced. The result could, of course, be manipulated in much the same way as the characters.

### Some applications

Apart from plotting graphs and histograms it might at first appear that the plotter does not have many applications for the amateur enthusiast. However the applications are only limited by the ingenuity of the driving software.

Once a circuit has been perfected it is very often required to transfer it to a printed circuit board. This can be extremely tedious as the entire design must be drawn out and taped onto a sheet of drawing paper. The artwork is then usually photographically reduced and then transferred to the board by using photo-sensitive laquer. The operation is both time consuming and expensive.

The plotter can help by performing much of the tedious repetitive draughting work. Specific building blocks such as i.c. pads can be described to the computer in the same way as the alphanumeric characters. If a c.r.t.-based graphics display is available then this can be used to draw out and check the design of the board before it is plotted.

### Appendix 1. Rom coding

	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
7C00	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7C10	11	33	36	32	3C	11	34	11	39	31	11	11	38	11	11	11
7C20	11	63	66	62	6C	11	64	11	69	61	11	11	68	11	11	11
7C30	11	23	26	22	2C	11	24	11	29	21	11	11	28	11	11	11
7C40	11	03	06	02	0C	11	04	11	09	01	11	11	08	11	11	11
7C50	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7C60	11	43	46	42	4C	11	44	11	49	41	11	11	48	11	11	11
7C70	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7C80	11	93	96	92	9C	11	94	11	99	91	11	11	98	11	11	11
7C90	11	13	16	12	1C	11	14	11	19	11	11	11	18	11	11	11
7CA0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7CB0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7CC0	11	83	86	82	8C	11	84	11	89	81	11	11	88	11	11	11
7CD0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7CE0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7CF0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7D00	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7D10	11	39	33	31	36	11	32	11	3C	38	11	11	34	11	11	11
7D20	11	69	63	61	66	11	62	11	6C	68	11	11	64	11	11	11
7D30	11	29	23	21	26	11	22	11	2C	28	11	11	24	11	11	11
7D40	11	09	03	01	06	11	02	11	0C	08	11	11	04	11	11	11
7D50	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7D60	11	49	43	41	46	11	42	11	4C	48	11	11	44	11	11	11
7D70	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7D80	11	99	93	91	96	11	92	11	9C	98	11	11	94	11	11	11
7D90	11	19	13	11	16	11	12	11	1C	18	11	11	14	11	11	11
7DA0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7DB0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7DC0	11	89	83	81	86	11	82	11	8C	88	11	11	84	11	11	11
7DD0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7DE0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7DF0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7E00	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7E10	11	93	96	92	9C	11	94	11	99	91	11	11	98	11	11	11
7E20	11	33	36	32	3C	11	34	11	39	31	11	11	38	11	11	11
7E30	11	13	16	12	1C	11	14	11	19	11	11	11	18	11	11	11
7E40	11	63	66	62	6C	11	64	11	69	61	11	11	68	11	11	11
7E50	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7E60	11	23	26	22	2C	11	24	11	29	21	11	11	28	11	11	11
7E70	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7E80	11	03	06	02	0C	11	04	11	09	01	11	11	08	11	11	11
7E90	11	83	86	82	8C	11	84	11	89	81	11	11	88	11	11	11
7EA0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7EB0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7EC0	11	43	46	42	4C	11	44	11	49	41	11	11	48	11	11	11
7ED0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7EE0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7EF0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7F00	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7F10	11	99	93	91	96	11	92	11	9C	98	11	11	94	11	11	11
7F20	11	39	33	31	36	11	32	11	3C	38	11	11	34	11	11	11
7F30	11	19	13	11	16	11	12	11	1C	18	11	11	14	11	11	11
7F40	11	69	63	61	66	11	62	11	6C	68	11	11	64	11	11	11
7F50	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7F60	11	29	23	21	26	11	22	11	2C	28	11	11	24	11	11	11
7F70	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7F80	11	09	03	01	06	11	02	11	0C	08	11	11	04	11	11	11
7F90	11	89	83	81	86	11	82	11	8C	88	11	11	84	11	11	11
7FA0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7FB0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7FC0	11	49	43	41	46	11	42	11	4C	48	11	11	44	11	11	11
7FD0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7FE0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11
7FF0	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11	11

# Assembly language programming

Digital signals lend themselves to processing, but they can only signal two conditions and are, therefore, of limited use in the outside world. Analogue interfaces, the subject of Bob Coates' ninth tutorial, use a number of bits to sense or produce a signal with many possible voltage levels.

by R. F. Coates

Digital i.cs such as microprocessors recognize signals with two voltage levels representing either a one or a zero, but to be useful they often have to process and generate analogue signals with many different levels. Analogue interfaces are used for this purpose and they fall into two main categories; a digital-to-analogue converter, d-to-a, turns digital information from the processor into an analogue output signal with many levels, and an analogue-to-digital converter, or a-to-d, senses, analogue-input signals and turns them into digital information suitable for the micro-processor. Usually, analogue converters are separate i.cs but some microprocessors such as 'R' versions of the 6805 have built-in analogue converters.

## Digital-to-analogue converters

Such converters turn a binary number represented by digital logic levels into an output voltage which is proportional to the weighting of the binary value. Most common i.cs used for this purpose take an eight-bit binary value and produce an analogue output at any one of 256 discrete levels ( $2^8$ ). An 'R-2R' ladder network similar to the two-bit version shown in Fig. 1 is usually used. Here the two digital inputs  $b_0$  and  $b_1$  drive transistor circuits whose outputs switch between 0 and 5V supply rails on receiving a logical zero or one respectively. When both inputs are at zero, the equivalent circuit Fig. 2(a) shows that the output is about 1.25V. With respect to accuracy, the value R is

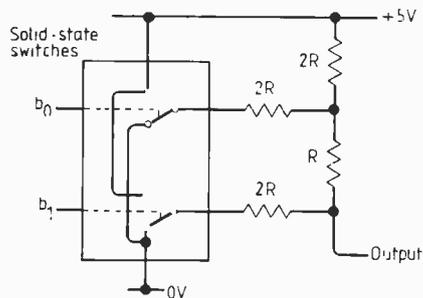


Fig. 1. Basic digital-to-analogue converter circuit. Two digital input bits,  $b_0$  and  $b_1$ , are converted to one of four output levels using an R-2R network. Bit  $b_0$  is the least-significant digit of a binary word and  $b_1$  is the most significant.

unimportant but the resistors must be matched. If input  $b_0$  is taken to logical one, the output becomes half the supply voltage as equivalent circuit Fig. 2(b) shows. With  $b_0$  at zero and  $b_1$  at one, the output is 3.75V, Fig. 2(c), and with both inputs at logical one, the output is the same as the supply voltage, Fig. 2(d).

This principle, using two digital inputs with four possible binary values to give four output-voltage levels, can be extended to produce an 8-bit d-to-a with 256 possible output levels. Circuits of Fig. 2 assume no output loading and in practice such converters are usually followed by an op-amp buffer to ensure that the resistor network is not loaded.

## Picotutor analogue board

An analogue interface board designed for Picotutor around Ferranti's ZN425E i.c. was described in the January 1983 issue of *Wireless World*, pp. 70-72. Its circuit

diagram shows the eight data lines that connect to Picotutor port A lines and an op-amp that serves to buffer the converter and multiply the output voltage by two. Instead of the R-2R ladder being fed directly from the 5V supply rail, which may not be accurately regulated, the ZN425 has its own regulated ladder feed which is typically 2.55V. Output range of the device is therefore 0 to 2.55V with steps of  $2.55/2^8$  which is 10mV. The converter circuit is shown at the end of this article.

After setting up as prescribed under the heading Voltage generation in the January 1983 issue, operation of the board can be seen without having to write a program. First, port A lines must be set as outputs by keying in MO, 004, FF which sets the A data-direction register at address 004 to all ones. Press the down-arrow key until the port A data register address, 000, is reached. A voltmeter then connected to analogue board output will show that changing the contents of this address from 00 to FF will change the analogue output from 0V to 5.1V, provided that gain potentiometer  $R_3$  is set correctly. Without

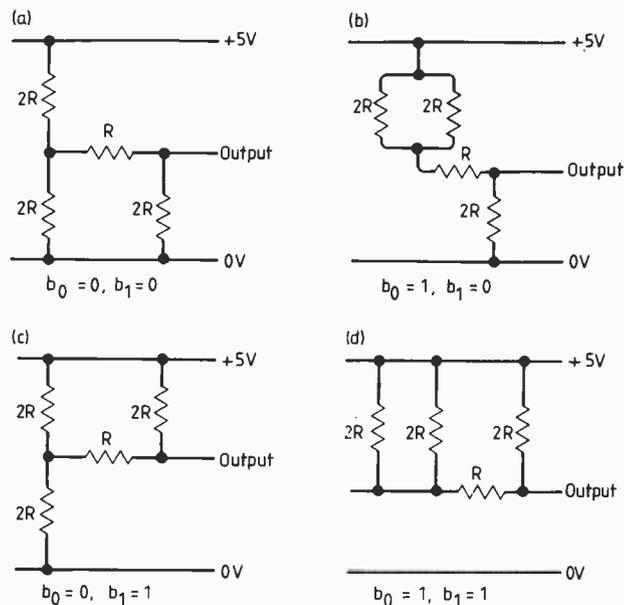


Fig. 2. Equivalent circuits of the network shown in Fig. 1 for the four input permutations.

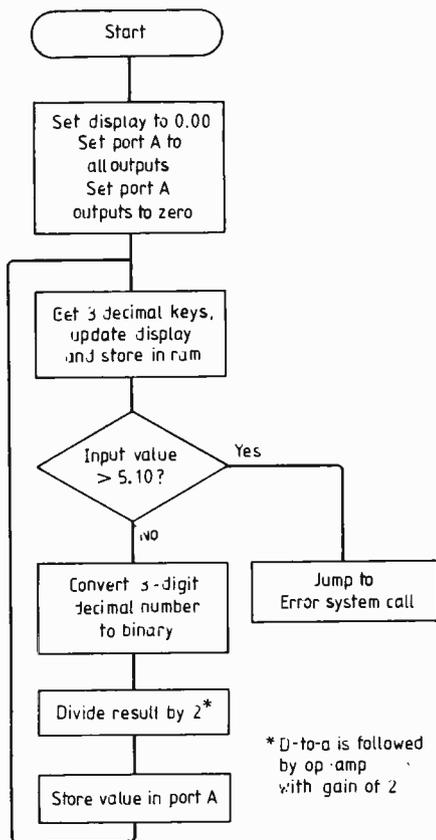


Fig. 3. Picotutor contains a program for converting three decimal digits entered on the keypad to binary form. This binary value is sent to the digital-to-analogue converter board through port A.

writing a program though, the output voltage has to be set using binary numbers as opposed to decimal ones.

### Voltage generator

There is a routine in the Picotutor monitor which allows decimal voltage values to be keyed in and appear at the analogue output. Access to this routine is through location 0CE which contains a jump to the actual routine. Three decimal digits are entered as one unit and two decimal places; these are converted to binary form and stored in the d-to-a converter by the program whose flow diagram is shown in Fig. 3. List 1 is assembled source code derived from the flow diagram. Display is initially cleared by CLRDIS and 0.00 placed on the right of the display. Port A is set for all outputs and at zero. At the start of the main loop, index register X is loaded with the address of the first display digit which is units-volts. System call THEX7 is then used. This call, not given in the list of system calls (see September 1983 issue), is similar to THEX but it only reads one key entry and if it is greater than seven, aborts to START. If the value is less than or equal to seven, the call stores the seven-segment equivalent in the effective address given by the index register, increments the index and returns with the decimal value of the key in the accumulator. If you wish to use the call in your own programs, it can be accessed at address 095. This value is then stored in ram address POINT.

We need the decimal point indication with this digit, which THEX7 will have

turned off, so this is done next. THEX is then called to get the next two key entries, updating the display and returning with the two key entries in two accumulator nibbles; these are stored in POINT+1. POINT and POINT+1 should now contain a three-digit decimal value. The maximum output from the analogue board is 5.10V, so the program checks that the entered value is not greater than this. If so, the routine is left and a jump to ERROR displays the error message. Having decided that the entered value is within limits, it is now converted to binary by calling BCDBIN. The index register is first loaded with the address of some spare ram to receive the result. If bit C in the condition-code register is set on return from BCDBIN it means that one or both of the second or third digits was not a decimal digit but one of the A to F keys, which also results in an error. The valid binary value in 0,X and 1,X, is now divided by two by LSR0,X and ROR1,X which shifts the two 8-bit bytes right by one bit. This is because the ZN425E can only produce a maximum voltage of 2.55V and we are adding a  $\times 2$  gain amplifier to achieve a maximum output of 5.10V.

The binary value divided by two is stored in port A and passed on to the inputs of the ZN425E. The program then loops back to wait for the next value to be entered.

### Analogue-to-digital conversion

These circuits allow a microprocessor to read an analogue voltage rather than generate one but the most common method of converting analogue signals to digital form uses a d-to-a converter and comparator, Fig. 4. Output from the d-to-a is taken to one of the comparator inputs and the voltage to be measured to the other input. Output of the comparator is taken to an input of the microcomputer. If the d-to-a output is less than the unknown voltage, the comparator output is low, and if greater than the unknown voltage it will be high. To determine the unknown voltage all that is needed, knowing what voltage output the d-to-a will give for a given digital input, is to perform the operation shown in Fig. 5.

Starting with zero output from the d-to-a, check to see if it exceeds the unknown, if not, increment the converter output voltage by one step and check again, and keep doing this until the d-to-a voltage exceeds the unknown one. The binary value driving the d-to-a converter is now approximately the same as the unknown voltage and can be read by the processor.

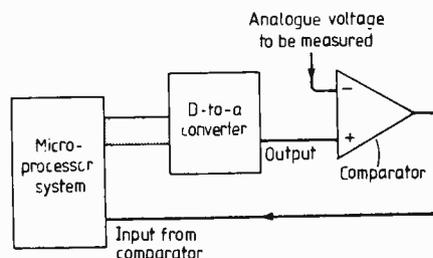


Fig. 4. Most common analogue-to-digital circuits use a digital-to-analogue converter and comparator as shown here.

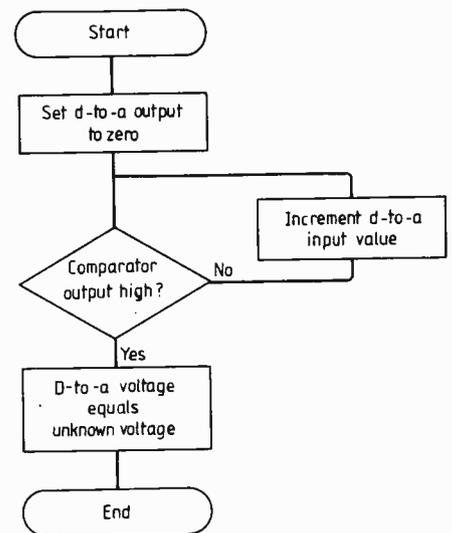


Fig. 5. Flow diagram for simple analogue-to-digital conversion. In this method, output from the converter is increased one step at a time from zero until the comparator switches.

On Picotutor, the analogue-board op-amp previously used as a buffer is now used as the comparator. With the analogue interface still connected as described for voltage generation, move  $S_1$  to the a-to-d position (toward IC<sub>2</sub>). This disconnects the op-amp feedback loop and connects its inverting input to the slider of R<sub>2</sub> and hence to the analogue-input terminal. An extra link is needed between the analogue-out pin and an input on the 68705. Any spare input would do but use the interrupt pin, int., for convenience. In this example the interrupt-request pin is used in a mode not available on most microprocessors. If the interrupt mask is set, the interrupt pin may be treated as a normal digital input, its state being tested by branch-if-interrupt-high/low instructions. If the analogue input pin is connected to +5V, the input voltage can be varied between 0 and +5V by adjusting R<sub>2</sub>.

List 2 is an assembly language example for operating the a-to-d converter. It is based on the flow diagram of Fig. 5 but after having determined the voltage, the program stores its hexadecimal equivalent in the display, refreshes the display, then loops back and starts again. Adjusting R<sub>2</sub> while the program is running will cause the display to change. If R<sub>2</sub> is over half way though the display will blank (fully anticlockwise setting is +5V) because the ZN425E reference, and hence the maximum output, is only 2.55V. If the unknown voltage exceeds this level the interrupt line remains permanently low so the program gets stuck in loop 2 and never refreshes the display.

But there is a shortcoming in this simple algorithm. If the unknown voltage is low, then it finds a match fairly quickly, but if it is at full scale it will need to execute loop 2 256 times. This will take in the region of 3ms, which may not seem long, but means it is only possible to sample at a rate of 300Hz. If the a-to-d device could convert to 12 bits, this becomes 50ms and a maximum sample rate of 20Hz. As 12-bit a-to-d converters with a sampling frequency of

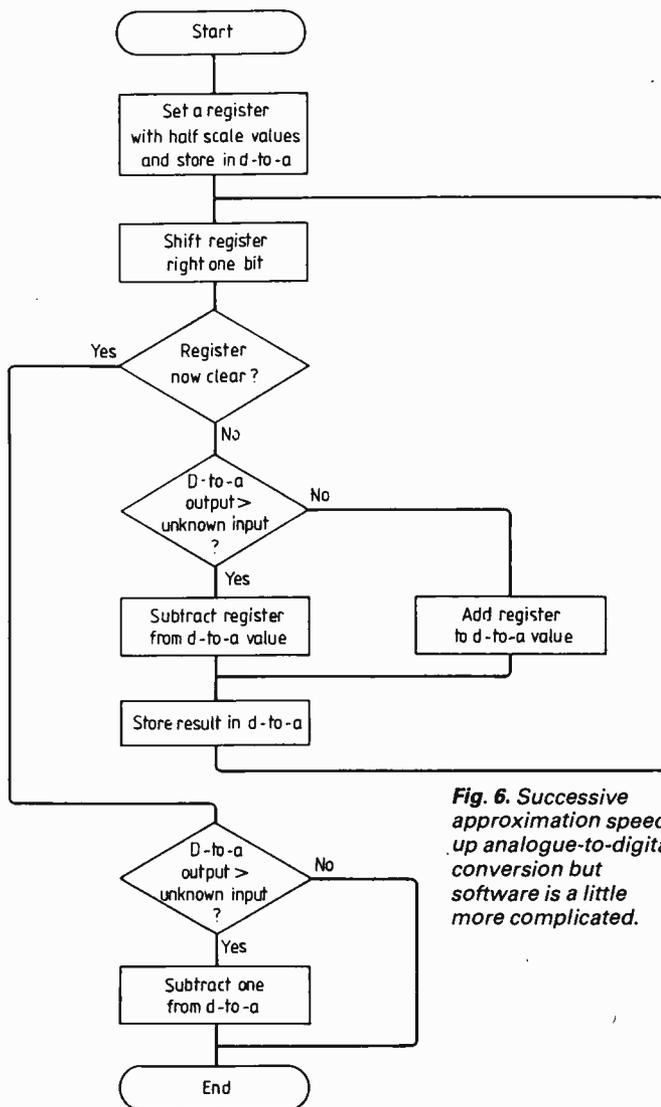


Fig. 6. Successive approximation speeds up analogue-to-digital conversion but software is a little more complicated.

25kHz are not uncommon, a better algorithm must be used.

### Successive approximation

A successive approximation algorithm may be used to speed up conversion. This involves a succession of guesses, where the next guess is based on the results of the previous one. D-to-a converter output is set to half way and the comparator output checked. The check will either say that the guess was too high or too low. If, for instance it is too low, then the unknown voltage must be between half and full scale. Next the d-to-a output is set to half way between half and full output, and checked again. This process is repeated, each time halving the error, until the converter output is within one bit of the unknown voltage. The highest number of steps required to achieve this is the same as the number of bits of the converter, in this case eight. This means that the longest time required to make a measurement on Picotutor is only 100µs, and for an equivalent 12-bit converter the time would be 150µs, a clear improvement over 50 milliseconds.

Successive approximation is a technique which lends itself to working in binary. Consider the starting point for a conversion, with the converter set at half output. With an 8-bit converter, this means storing 1000 0000 in the d-to-a. Comparator output is then checked to see if the converter output is less than or greater than the unknown input voltage. If less, the next least-significant bit must be added to the d-to-a value to get the new value

1000 0000  
+0100 0000

1100 0000

If it is greater, the next least-significant bit must be subtracted from the d-to-a value

1000 0000  
-0100 0000

0100 0000

All that is necessary for a complete conversion is for the initial value to be repeatedly shifted right, and after each shift added to or subtracted from the value that the d-to-a is set to according to the result of the comparator test. This new value is stored back into the converter.

Figure 6 shows a flowchart for a conversion based on this technique. The main loop, for an 8-bit a-to-d converter, will be executed seven times; the last time a single bit in the rightmost position will be added to or subtracted from the d-to-a value giving a final resolution of ±1bit. To correctly set the last bit to zero or one, the comparator output is finally tested and one subtracted from the d-to-a if it is still too high.



### Digital voltmeter

The digital voltmeter routine in the Picotutor monitor uses successive approximation. Added to the basic program though is the conversion from the 8-bit binary value to decimal, this being placed in the display with a decimal point in the correct place.
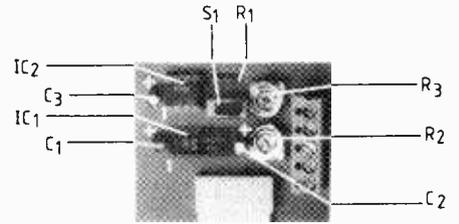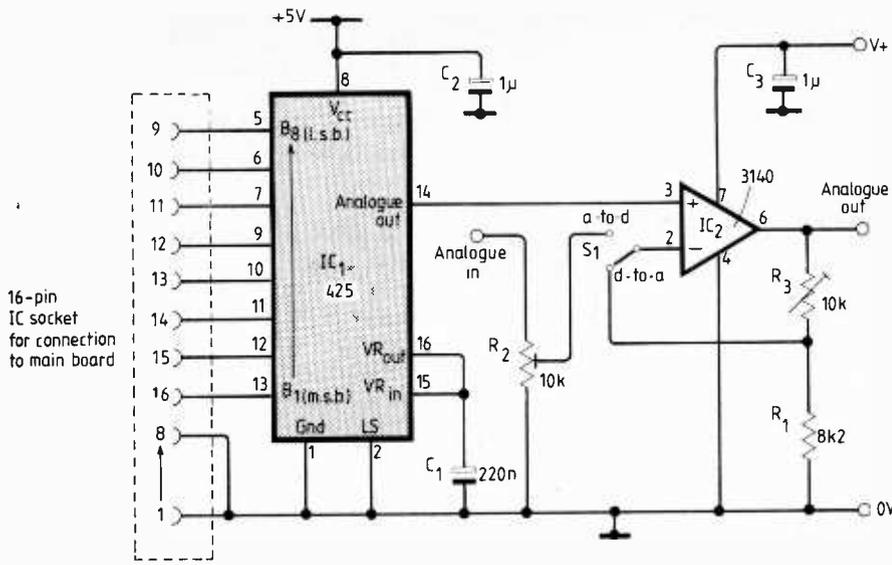
#### List 1. Picotutor voltage-generator source list.

```

*
*
* V G E N -- VOLTAGE GENERATOR. REQUIRES CONNECTION OF ANALOGUE
*           INTERFACE. D-A FORM
*
*
VGEN JSR CLRDIS CLEAR DISPLAY
      LDA #H'DF' PUT "0." IN 4TH DISPLAY
      STA DISBUF+3
      LDA #H'DD' PUT "0" IN 5TH & 6TH DISPLAYS
      STA DISBUF+4
      STA DISBUF+5
      LDA #H'FF' SET PORT A TO ALL O/P'S
      STA PORTAD
      CLR PORTA SET O/P TO ZERO
*
VGLLOOP LDX #DISBUF+3 POINT X AT 4TH DISPLAY DIGIT
        JSR THEX7 GET HEX KEY IN DISPLAY, BUMP X, VALUE IN A
        STA POINT STORE KEY VALUE
        LOA OISBUF+3
        ORA #B'00000010' ADD D.P. TO DIGIT JUST PLACED IN DISPLAY
        STA DISBUF+3
        JSR THEX GET IN NEXT TWO KEYS COMBINED
        STA POINT+1
        LDA POINT NOW CHECK THE 3 ARE NOT >5.10
        CMP #5
        BLS CHECK1 BRANCH UNLESS 1ST IS >5
ERR JMP ERROR
CHECK1 BNE CHECK2 IF NOT 5, MUST BE 0-4 SO CHECK NO MORE
        LDA POINT+1 1ST = 5, SO CHECK NEXT 2 ARE NOT >10
        CMP #H'10'
        BHI ERR
*
CHECK2 LDX #H'6E' POINT X AT SPARE RAM
        JSR BCD2BIN CONVERT ENTERED NUMBER TO BINARY
        BCS ERR IF CARRY SET, ONE OF THE DIGITS >9
        LSR ,X OIVIOE RESULT BY TWO
        ROR 1,X
        LDA 1,X GET DIVIDED RESULT (8 BITS)
        STA PORTA SET UP O-A WITH IT
        BRA VGLLOOP AND GET ANOTHER VOLTAGE ENTRY
  
```



Circuit diagram of Picotutor's analogue interface which may be switched to operate as an a-to-d or d-to-a converter

List 2. Program for simple a-to-d conversion.

```

030 98 SEI MASK INTERRUPTS
031 A6FF LDA #SFF SET PORT A LINES AS O/P'S
033 B704 STA PORTAD
035 B0B0 JSR CLRDIS CLEAR DISPLAY
037 3F00 LOOP1 CLR PORTA SET D-A TO ZERO
039 3C00 LOOP2 INC PORTA BUMPS UP D-A BY 1
03B 2EFC BIL LOOP2 BRANCH IF D-A VOLTAGE < UNKNOWN
030 B600 LDA PORTA GET 0-A VALUE
03F B09B JSR LSEG
041 B710 STA DISBUF STORE HEX DIGIT IN DISP. BUFF.
043 B600 LDA PORTA
045 B09E JSR RSEG
047 B711 STA DISBUF+1 AND RIGHT HEX DIGIT
049 B0B3 JSR DISKEY REFRESH DISPLAY
04B 20EA BRA LOOP1 AND REPEAT INDEFINITELY

```

List 3. Picotutor's d.v.m. program uses successive approximation.

```

*
*
* D V M -- DIGITAL VOLTMETER. REQUIRES CONNECTION OF
* THE ANALOGUE INTERFACE CARD, A-D FORM
*
DVM SEI SET INTERRUPT MASK
LDA #H'FF' SET PORT A LINES TO O/P'S
STA PORTAD
JSR CLRDIS CLEAR DISPLAY
LOOP LDA #H'80' SET D-A FOR HALF F.S. O/P
STA PORTA
STA H'6E' STORE ALSO IN A TEMP. REG.
LSR H'6E' SHIFT RIGHT TEMP. REG.
SUCAP1 BCS SUCAP4 IF CARRY SET, THEN 7 BITS HAVE BEEN SET SO FINISH
LDA PORTA GET THE CURRENT D-A SET VALUE
BIH SUCAP2 IF INT LINE (ALOG COMP. O/P) IS HIGH, BRANCH
ADD H'6E' INT LOW, INC D-A BY ADDING TEMP. REG.
BRA SUCAP3

SUCAP2 SUB H'6E' INT HIGH, DEC D-A BY SUBTRACTING TEMP. REG.
STA PORTA SET D-A TO NEW VALUE
SUCAP3 BRA SUCAP1 GO BACK & DO SAME WITH NLS BIT

SUCAP4 BIL DISP 7 BITS SET, NOW SET 8TH
DEC PORTA IF INT HIGH, DEC D-A. IF LOW, DON'T
DISP CLR POINT PORT A CONTAINS 8 BIT CODE = ANALOG I/P
LDA PORTA STORE IT IN POINT+1
STA POINT+1
LDX #H'6E' POINT X AT SPARE RAM
JSR BINBCD CONVERT TO BCD
LDA ,X GET MOST SIG OF THE 3 DIGIT BCD RESULT
JSR RSEG
ORA #2 ADD THE DECIMAL POINT
STA DISBUF AND PUT IN DISPLAY
LDA 1,X GET THE OTHER 2 DIGITS
JSR LSEG CONVERT MOST SIG TO 7 SEG
STA DISBUF+1 & STORE IN DISPLAY
LDA 1,X SAME WITH LEAST SIG
JSR RSEG
STA DISBUF+2

DISP1 LDX #H'1B' CALL SR WHICH REFRESHES DISPLAY, H'1B' TIMES
JSR DISKEY
DEX
BNE DISP1
BRA LOOP

```

List 3 is an extract from the Picotutor source list showing the digital-voltmeter routine. After setting the interrupt mask, port A lines are set as outputs by storing FF in the data-direction register. You will notice here, and in List 1, that the method used to indicate hexadecimal numbers is different from that used by Motorola. Instead of \$FF, H'FF is used. This is because the assembler used for this program was not produced by Motorola, but by Philips. Next the display is cleared and the main loop of the program is entered. The d-to-a converter is set for half value and a register at ram address 06E is also set with this value. This register is then shifted right, the current d-to-a value loaded into the accumulator; depending on the state of the interrupt line, the register is added to or subtracted from the accumulator and the result stored in the converter.

This loop, SUCAP1, is repeated until the bit that was originally set in bit 7 (H'80') has been shifted right through to bit 0 and into the carry bit of the condition-code register. When this carry bit is detected, the loop is terminated and execution continues at SUCAP4 where the last bit correction takes place. The binary d-to-a value is now converted to binary-coded decimal using system call BINBCD. This gives a three-digit result between 000 and 255 for the eight-bit binary input fed to it. Each digit is converted to seven-segment code, (the most significant one having the decimal point set on) and stored in the display buffer ram DISBUF. Finally DISKEY is called to light the display; it is in fact called a number of times to delay the program for about half a second before returning to LOOP to start a new conversion. If only one refresh was performed, samples would take place every 20ms which is a little too fast for a d.v.m. and could cause rapid flickering of the last digit if the voltage was half way between two digital values. Half a second is an adequate sampling rate in this sort of application.

Note that if the input voltage exceeds 2.55V, it will in fact give a full scale reading instead of blanking the display as in the previous example. An obvious refinement here would be to make the display give an over-range indication if the maximum value is exceeded.

To be continued

# 16-line p.a.b.x with options

*With the basic exchange described, this third article concentrates on options including out-door telephone connection, call transfer, auxiliary-equipment switching, paging and self test.*

by J. H. Kuiper

The section on call transfer outlined operation of the line-hold facility (ST relay switching). To provide 'music-on-hold' a tape recorder may be connected to  $s_{1,2}$  contacts (normally closed) and an st contact used to start and stop the recorder. Frequency range of the recording should be limited to between 300 and 3400Hz to avoid interference with other callers and exchange circuits.

## Ringer control

In the line interface a three-way switch and timer may be included to disconnect the ringer at certain periods, for instance each evening. Positions of the switch are normal, off and bypass; at all times visual indication is retained and dialling out is not affected.

## Out-door connection


An outdoor telephone with electronic door-opener may be connected, which involves relays L, N door opener DO, terminator relay TD (oor) and contacts  $q_1$  and  $q_2$ . All these are in the boxed section of the diagram. If this option is not required all boxed components may be omitted, but remember to strap the  $l_1$  n.o. contact between the  $\bar{g}_3$  bus and toggle. The  $g_3$  bus is not required in this case. This option involves a special type of telephone so connection is different. As no calls originate from the door, ie, no dialling takes place there, and an originator relay is not required. Terminator relay TD will be assigned an easy to remember number at the driver outputs such as 11, or 1 in a small system. As it will also be undesirable to send ringer current to this telephone, the b-line has to be connected between  $r_{11}$  and the speech coupling capacitor while the a-line goes to ground through  $td_1$  and  $n_1$ . Both positions are marked by an X. If the door telephone is a low-voltage type and ground is at 45V, a two-resistor voltage divider has to be included between  $td_1$  and  $V_{ss}$  and the a-line connected to the junction of these resistors. Remember that reply relay R still has to operate from this lower voltage.

The circuit operates by dialling the door telephone, as described in the first section, when the doorbell is rung. TD acting switches  $td_1$ , which takes over the action of the called station lifting the handset in reply to the call, thus energizing R by


completing a path from ground through  $n_1$  to  $td_1$ , the door telephone and R coil to  $V_{ss}$ . Contact  $r_2$  completes the speech path and further action of the r contacts is as for internal conversation. Contact  $td_2$  disengages coil L which is normally powered so all ground keys operate relay DO instead of the toggle; operating the ground key will switch  $do_1$  which may energize the door-lock.

Resetting is different in that this nor-

mally does not occur until both handsets are replaced or both II and R are in their off states. As the door telephone will have no handset to replace, relay N has been included. Replacing one handset disconnects II so  $ii_1$ , being off, will now provide power to N though  $td_2$  which is still on. Contact  $n_1$  disengages the door telephone and relay R to meet the standard reset requirements. Resetting now takes place as usual with N not resetting until  $td_2$  switches off. In the event of an exchange call coming in while the ground keys are controlling DO and  $l_2$  instead of the toggle, auto-switching will not take place ( $r_4$  open) and manual access to the exchange line is impossible. Therefore internal cir-

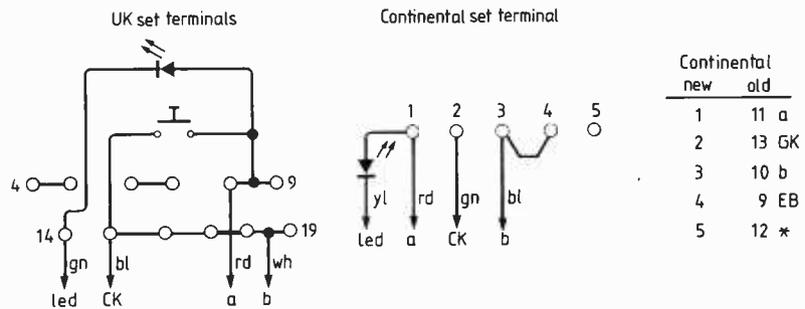

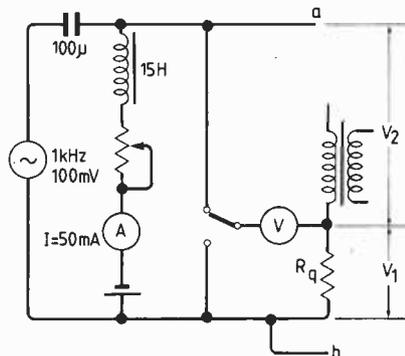*Modifications for connection of UK or Connection to public network for UK (left) and Continental sets. For UK sets, remove straps 5, 6, 17 and 18 in telephone. Change around green/white strap in terminal block and connect blue wire to tag five in telephone. In Continental telephones, change green wire from point two to point five and connect 'a' to the socket ground strap.*




*Test circuit for determination of  $rg$  value. Connect to line interface and select  $rg$  for  $V_1 = V_2$ . Impedance is 600 ohms  $\pm 20\%$ .*

uits have to be reset first. Since finding out who's at the door normally does not take long this is not too serious. On the other hand when a station is on the exchange line another station may still answer the door through the (vacant) internal circuits. This is possible by  $q_1$  offering an alternative path from the various ground keys to DO though all  $g_3$  contacts. One contact being off and  $G_2$  holding L operated retains access to the toggle through its  $g_3$  and  $l_1$  contacts in spite of  $td_2$  switching the station connected to the exchange line.
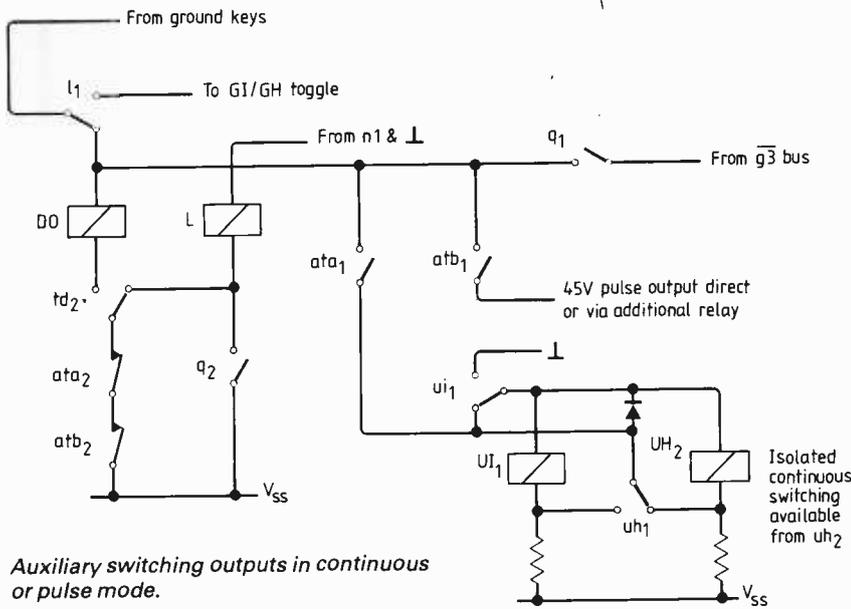
## One person transfer

As mentioned in the description of call transfer, there are two ways of returning to the exchange line when in hold mode. The second method is used here so after having put the caller on hold put the handset down which among other things resets all q contacts as well as the G relay. Then go to the station where continuation of the conversation is required, lift the handset and operate the ground key. This procedure saves walking between two stations or



Auxiliary switching outputs in continuous or pulse mode.

the aid of someone who has to take the call first. Remember, leaving the original station off-hook prevents internal reset and thus further internal calling until that handset is replaced.

### Switching auxiliary equipment

The above action once again involves use of the ground key section. If permanent switching of for instance a lamp is required, a toggle and auxiliary terminator relay, AT must be added. For momentary operation in pulse mode only an auxiliary terminator relay is required.

Circuit changes to the boxed door-opener section are shown in a separate diagram. Basically all outputs are taken from  $l_1$  normally closed contacts through auxiliary normally open t contacts of which two are shown —  $ata_1$  for permanent action and  $atb_1$  for pulse mode. Additional normally-closed auxiliary t contacts are required in series between  $td_2$  and  $V_{ss}$ . These are specified as  $ata_2$  and  $atb_2$  respectively. Various auxiliary T relay coil designated ATA, ATB, etc., are assigned a number and connected to the proper terminator-driver outputs. As each auxiliary circuit requires a connection in the terminator fewer stations can be hooked up since the total number is restricted to 16.

Upon dialling of the correct number, ringing tone will be heard as usual. Operating the ground key will now switch the auxiliary toggle to keep the output at  $l_1$  normally-closed contacts at  $V+$  as long as the key is held down. Toggled outputs may be dialled later and reset by once again operating the ground key. The isolated contact  $uh_2$  may be used to switch a lamp or whatever appliance requiring continuous power. If total isolation of equipment connected to a momentary output is necessary an intermittent relay should be connected, its contact providing the desired isolation.

After the required switching action, resetting of the internal circuitry is as if no-reply has been obtained as no contact has been made to operate reply relay R. Operating conditions with respect to a possible exchange call being in progress are as for operation of the door opener section.

Switching of the relay contacts will also be as outlined for the door opener, with auxiliary terminator contacts 1 establishing the path for the ground key while contacts two will switch L with  $l_2$  now preventing incorrect automatic switching of incoming calls.

### Paging and self test

A sensible application for a momentary-pulse output as described in the last section would be connection of a V relay with three-pole change-over contacts. These contacts would power the external ringer in the line interface and simultaneously prevent a bell-detector pulse from incorrectly operating the circuits. When a caller is on hold, by operating the ground key a series of ringer pulses may be given to page a person who is not answering at his usual extension. Alternatively correct operation of the ringer and BDT may be checked if required. A separate diagram gives the details for inclusion of the three contacts. Variations such as switching the bell only are of course possible. If it is desired to test the entire line interface a local dp change-over pushbutton in the a and b exchange line is required. This should not be used for paging as operation disconnects the exchange line and therefore a local switch rather than a relay is used.


Note that with a caller on hold after having given a paging signal, re-access to the exchange line can now only be obtained by replacing the handset, picking it up again and then operating the ground

key to reconnect the exchange line. The reason for this is that when in the hold mode all Q relays as well as the one G relay are off. After having dialled the number assigned to the paging output, L remains firmly off and re-operating the ground key immediately after now only produces another paging signal. Therefore resetting has to be initiated the alternative way before further action can be taken.

Two further points regarding equipment-status signalling are worth noting. When an outside call is in progress an internal call between two other stations may be made at the same time. When dialling the station having the outside conversation though, a busy signal will be returned to the caller. This happens because the engaged station T relay operates and since its g is already on, coil 2ENG will energize through  $g_1$  and  $t_2$ . The audible signal is sent to the caller from  $2eng_2$  now operating and the caller's  $o_2$  on and  $g_2$  contacts being off. Contact  $2eng_1$  will start the engaged oscillator. Also when dialling one's own number an engaged signal will be produced as coil 2ENG powers through  $ir_1$ , the stations  $o_1$ , the diode and  $t_2$ . Contact  $2eng_2$  blocks the ringing tone and instead connects the busy signal to  $o_2$ . Although  $T_1$  connected ringer current from  $ri_1$ ,  $o_2$  blocks it from the telephone.
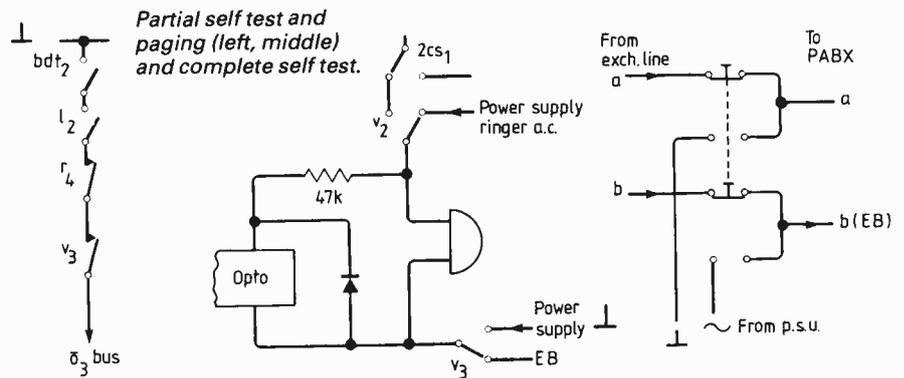
### Connection to the public network

In addition to demands made regarding loading of the network, output levels and frequency range it is also required that the network must always remain accessible as they must in the event of power cuts or faults in privately owned equipment. This is accomplished by leaving the originally installed telephone in circuit so that it operates independently of the p.a.b.x. To avoid 'bell-tinkle', which might cause incorrect operation and is therefore not allowed, some re-wiring in accordance with BTT plan 1A is required. Both Continental and UK variants are shown. In a UK connection bells are connected in series and correct wiring requires the removal of straps between terminals five and six as well as 17 and 18 in the set and in the block terminal the b-EB strap between the green and white wire (if fitted) has to be turned. As the visual indication should remain operative when using a timer to disconnect the ringers, the opto-isolator has to be connected in parallel through the blue wire to tag five in the telephone. If one ringer in the original telephone is sufficient a wire-link has to be inserted in the





# Sampling frequency meter

*Battery-powered frequency meter with memory is based on a 6805 microprocessor and monitors physical quantities such as windspeed in remote locations over periods of up to twelve months*

Physical quantities such as windspeed, temperature, humidity, often need to be monitored over extended periods in areas remote from a supply of mains electricity. When the information sought is merely the average value of a quantity, or just its distribution, commercially available battery-powered data-loggers can be an expensive solution. They are frequently too powerful for the task.

This article describes a low-cost solution to the problem in the form of a battery-powered instrument based on the c-mos Motorola MC146805 E2P microprocessor. In this instrument the input is sampled repetitively and compared with a table of values stored in memory, so that over time, a distribution of the sampled input is built up in 21 internal memory channels (20 channels + 1 'over-range' channel). The program controlling the microprocessor can be adapted to suit different needs by simply changing the values stored in this table, and/or by changing the measuring period. This again is selected in software. Besides its distribution, the maximum value attained by the input during the measuring period is also stored in memory. To extract these data from memory after an extended period of sampling, the instrument can be interrogated on site via two key-switches and an eight-digit liquid-

---

---

by N. A. Lockerbie, B.Sc., Ph.D.

---

---

crystal display. When not being interrogated the average value of the input during the previous ten-second measurement period is displayed. The total current-drain of the circuit is 1mA, implying an operational life in the field of 12 months from three alkaline D-cells.


## Operation

Only certain type types of transducers produce a variable-frequency output that is related to the physical input being measured: anemometers of the slotted-disc and light-beam variety are a good example. Nevertheless most can be adapted to do so, either by using voltage-to-frequency converters (on the output of a strain-gauge amplifier, perhaps) or in certain cases by employing the transducer as the resistive element in an RC oscillator, e.g. when measuring temperature with thermistors. As signals of this kind have inherently good noise immunity for transmission over long cables, the circuit was designed to accept this type of input.

The instrument is essentially a free-running frequency meter, with (as pro-




*Nicholas Lockerbie read physics at Nottingham University, where he gained a B.Sc., and in 1975 a Ph.D. He continued working there on the fundamental properties of solid/liquid-helium interfaces at temperatures close to absolute zero under an ICI Postdoctoral Research Fellowship. In 1977 he moved to Grenoble to work for the French Atomic Energy Authority in their Service des Basses Tempatures and went on to study the transport properties of superconductors at the Ecole Normale Supérieure, Paris, with a Royal Society Overseas Research Fellowship. In 1979 he took up a Lectureship in the Department of Applied Physics at Strathclyde University, Glasgow, and is now engaged there in the design and construction of a superconducting gravity gradiometer. He enjoys hill-walking, cycling, painting, cooking, photography, and amateur astronomy, as well as electronics.*

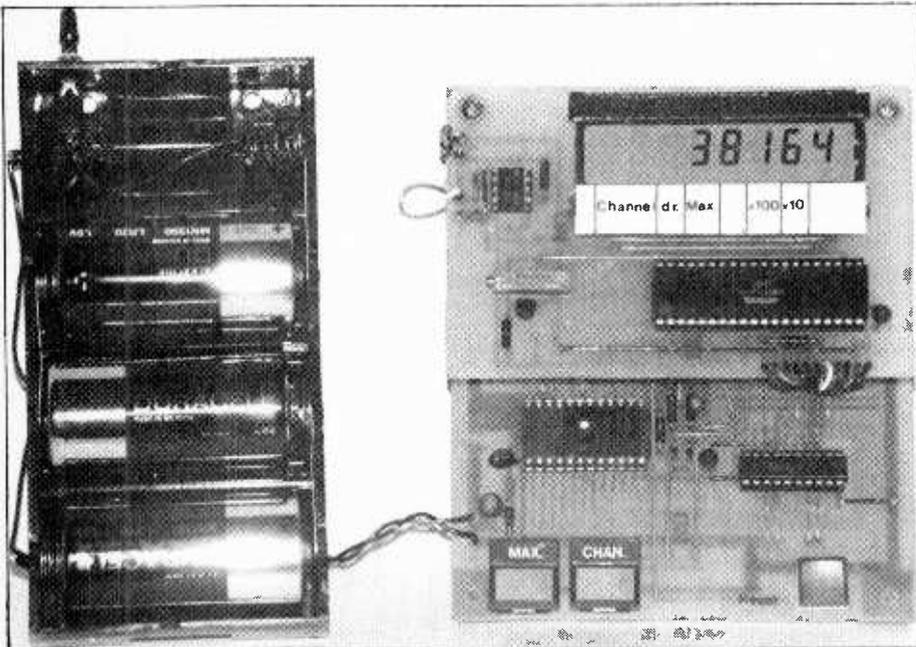

**Fig. 1.** Microprocessor-based sampling frequency meter. If the number of pulses counted in the ten-second measuring interval is greater than 65,535 "HI -----" is displayed. The i.c. to the left of the display (not included in the circuit diagram) is a small test oscillator, feeding pulses to the input of the circuit.

grammed) a fixed measuring period of ten seconds. Every ten seconds its display is updated with a new five-digit reading, the reading being the number of input pulses counted during the previous ten seconds. Because a 16-bit counter has been used in the circuit, this number must lie in the range 0-65,535 and although that clearly limits the average input frequency to a maximum of 6.55kHz with this measuring period, it has not proved to be a serious limitation. Besides being displayed, each count is also compared with a table of 20 values stored in eeprom, starting with the lowest value. These numbers, arranged in ascending order, serve as the channel delimiters and divide the range 0-65,535 into the 21 channels that are used to synthesize the distribution of the input. If these 20

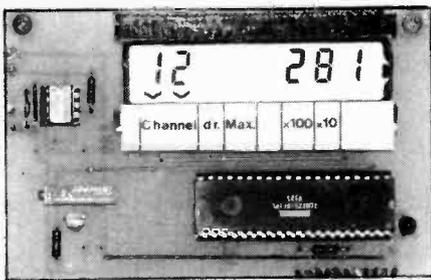

**Fig. 2.** Contents of channel 12: input has spent 281 units of ten seconds in the range of channel 12 - 36,000-38,999 in this case. Channel contents rise from 0 to 99,999, after which 10,000 is displayed, with the arrowed annunciator pointing to  $\times 10$ , etc.

numbers are labelled  $N_0, N_1, N_2, N_3, \dots, N_{19}$ , then channel 0 extends from 0 to  $N_0-1$ , channel 1 from  $N_0$  to  $N_1-1$ , channel 2 from  $N_1$  to  $N_2-1$  etc., up to channel 19, which covers the range  $N_{18}$  to  $N_{19}-1$ . The remaining interval of  $N_{19}-65,535$  becomes the over-range extension channel.

The sequential comparison of the pulse-

count with this table terminates when the count is found to be less than  $N_1$  ( $I=0$  to 19),  $N_1$  being the number with which it is currently being compared. For example, suppose the count was found to be less than  $N_2$  (and by implication,  $\geq N_1$ , then the count would lie in the range of channel 2. At this point channel 2 - in reality just a counter (in ram) - would be incremented by one unit of time, where the unit of time is ten seconds. In this fashion, the distribution of the input signal is slowly built up by the 21 channels, in the form of the amount of time the input spends in each count (and therefore frequency) range.


As the comparison table is held in eeprom, different eeproms can easily be substituted to suit different transducers. Moreover, non-linear transfer characteristics for the transducers can be ironed-out

**Fig. 3.** Complete circuit diagram of the c-mos microprocessor-based sampling frequency meter.


by judicious choice of values in the table. For example, each channel can be made to be exactly one unit of windspeed wide: or else the channels can be given deliberately different widths in the physical variable to emphasize certain regions. Channels can be made only one count wide if desired.

In addition to building up the distribution, each count as it is acquired is compared with the maximum value measured to date and the larger of the two is retained in ram as the current maximum value.

When the channel and maximum data have been accumulating for some time in ram, they can be read out by pressing one of the instrument's two key-switches. Pressing either switch generates an interrupt, and temporarily suspends the normal sampling action of the instrument. On receipt of the interrupt the two switches are polled to see which of them was pressed and the corresponding sequence follows: either the maximum value is displayed for six seconds as a five-digit

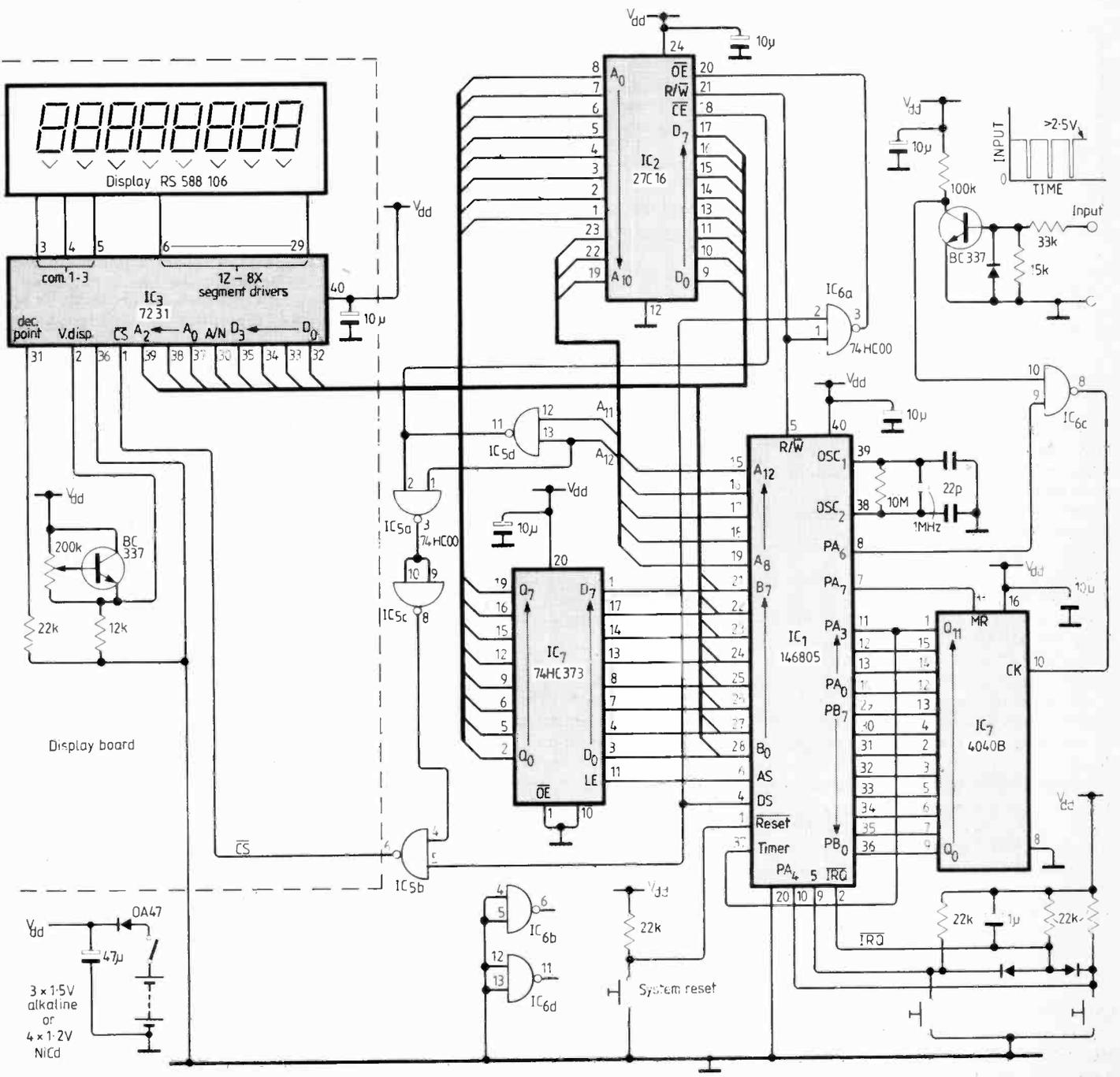

**Fig. 4.** Flow chart of the normal sampling cycle. The 10s delay was created in software, rather than using the m.p.u. internal timer (and timer interrupts), to leave the timer free for extension of the count to 16 bits by connecting pin 1 of IC<sub>7</sub> to pins 11 and 37 of IC<sub>1</sub>. In practice 16 bits proved to be adequate.

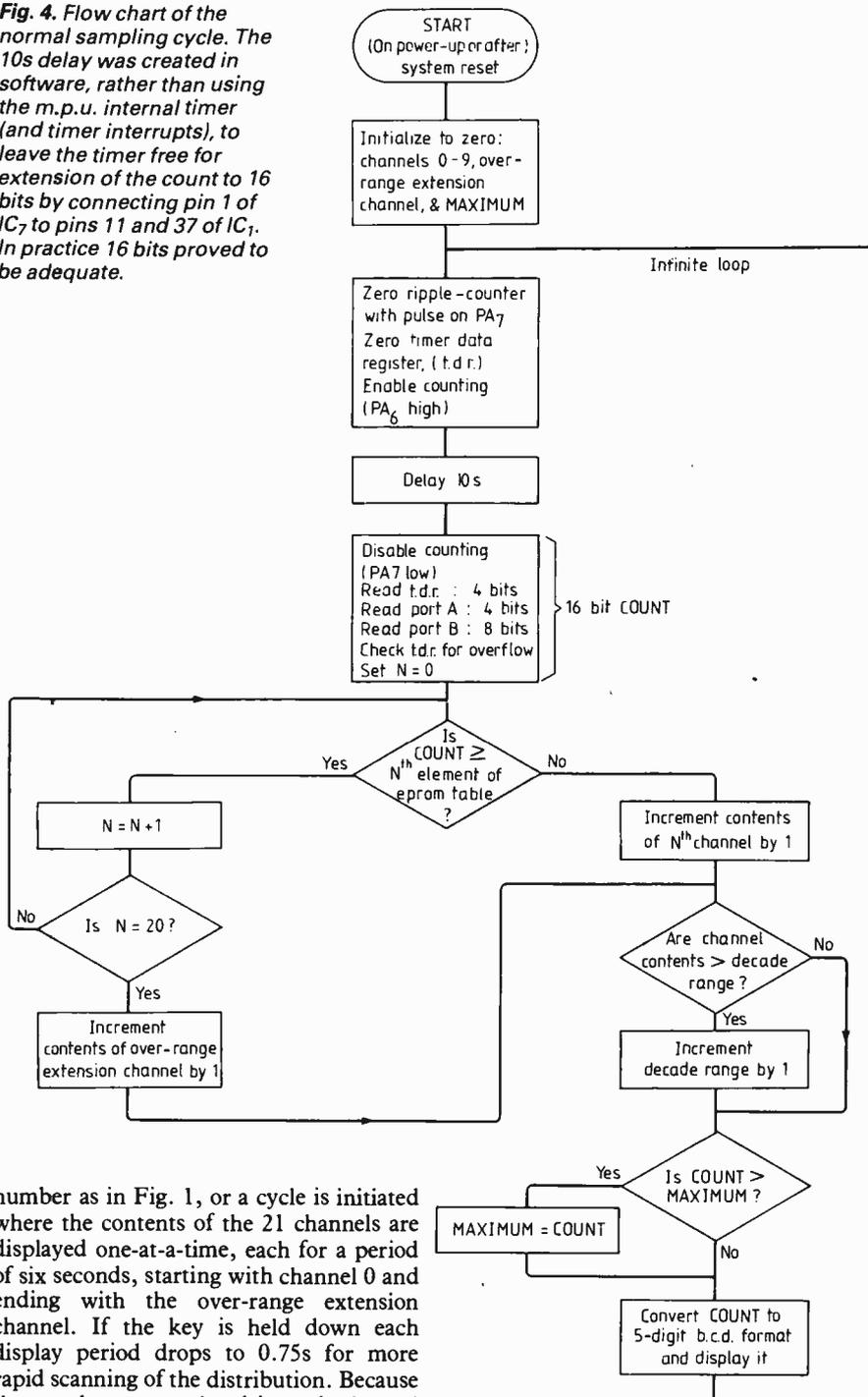

number as in Fig. 1, or a cycle is initiated where the contents of the 21 channels are displayed one-at-a-time, each for a period of six seconds, starting with channel 0 and ending with the over-range extension channel. If the key is held down each display period drops to 0.75s for more rapid scanning of the distribution. Because the number accumulated in each channel can become large over an extended sampling period, the channel contents are displayed with a resolution of five digits, together with an arrowed annunciator that is the power of ten by which the reading should be multiplied. It is kept the same for all channels, effectively normalizing the distribution to its peak value. Channel number is always displayed simultaneously with the contents of that channel, as in Fig. 2. If the 'channel' key is held down immediately after pressing the 'maximum' key, then the 20-channel delimiter values are reviewed in a manner similar to that for the channel contents. When either sequence terminates, control is passed back to the normal sampling routine, which continues as before.

### Circuit description

The heart of the circuit see Fig. 3, is an MC146805 E2P c-mos microprocessor running at a 1MHz clock frequency. It has

112 ram locations that are used for storage of the system stack, data, and program variables. Each channel for example uses three of these locations. For further information and another implementation using this m.p.u., see the article by T. D. Forrester<sup>1</sup>. Port lines PA<sub>5</sub>, PA<sub>4</sub>, PA<sub>3</sub>-PA<sub>0</sub> and PB<sub>7</sub>-PB<sub>0</sub> are configured as inputs and lines PA<sub>6</sub> and PA<sub>7</sub> as outputs. For communication with the peripheral chips, the m.p.u. is connected to the inputs of display driver IC<sub>3</sub>, and the data outputs of IC<sub>2</sub> via an eight-bit bidirectional multiplexed address/data bus. As the data and low-order memory address bits are multiplexed on the same bus the address bits have to be latched and high-speed c-mos octal latch IC<sub>4</sub> fulfils this function. Address strobe line AS (IC<sub>1</sub> pin 6) generates the necessary demultiplexing latch-


enable pulse. Lines A<sub>10</sub>-A<sub>8</sub> of IC<sub>1</sub> provide the remaining three bits of the 11-bit eeprom addresses.

The main controlling program for the microprocessor and the all-important look-up table are stored in the eeprom, IC<sub>2</sub>, a National Semiconductor NMC27C16 QE-65 (or -55, or -45), which is a c-mos version of the popular n-mos 2716 2k-by-8 eeprom. Note that using the more common n-mos 2716 increases the total current drain of the circuit by a factor of typically 30! The 20 numbers which form the look-up table can be programmed separately into 40 memory locations set aside for this purpose, in an otherwise programmed eeprom (the channel delimiters are all 16-bit numbers requiring two memory locations each).

In the circuit, the m.p.u. is connected so that it can both reset and read the binary-coded parallel output lines of IC<sub>7</sub>, and via IC<sub>6c</sub> it controls the gating of pulses through to the clock input of IC<sub>7</sub> (pin 10). This arrangement is similar in principle to that described by J. L. Gordon<sup>2</sup>. The most-significant output of IC<sub>7</sub>, a c-mos 4040B 12-stage binary ripple-counter, is fed into the 'timer' (actually a counter) input of the m.p.u., extending the ripple counter by a further eight bits. In this application, however, only the first 16 bits of the composite 20-bit ripple counter are used for counting input pulses, the remaining four being used for headroom, thereby guarding against the possibility of an overflow wrapping around and then counting up through zero again. The four highest timer bits are monitored in software to detect overflows from this 16-bit counter. Unlike the relatively low-speed 12-stage ripple-counter, nand-gates IC<sub>6</sub> and IC<sub>5</sub>, which provide gating and address decoding, are high-speed c-mos types.

The signal input to the instrument coming from the transducer must consist of a constant positive voltage level of between +2.5 and +30V w.r.t. circuit ground, interrupted by negative pulses which should fall below +1.5V for correct operation. This signal is conditioned by the level-shifting n.p.n. input transistor before being applied (now inverted) to pin 10 of the nand-gate IC<sub>6c</sub>.

Mounted for convenience on a separate board from the main circuit is the eight-digit display and driver. The liquid crystal display of the seven-segment type with a decimal-point (unused) and an arrow annunciator beneath each digit. A 7231B, IC<sub>3</sub>, drives the display in a triplexed mode via three common lines and 24 segment lines. It has a code-B font of characters. To create a digit in one of the eight positions on the display, first the digit position (0-7, 0 being the right-most digit) and its value (0-9 or -, E, H, L, P, (blank) . . . coded A-F in hexadecimal) have to be presented, in parallel binary form, to IC<sub>3</sub>'s address and data inputs: IC<sub>3</sub> inputs A<sub>2</sub>-A<sub>0</sub>, and D<sub>3</sub>-D<sub>0</sub>. If the annunciator for this position has to be on, a high level is applied to the AN input of IC<sub>3</sub>. A strobe pulse is then sent to IC<sub>3</sub> chip select input (pin 1) and that latches the digit (and annunciator) in place on the display. Address, data, and annunciator bits are assembled in software into a

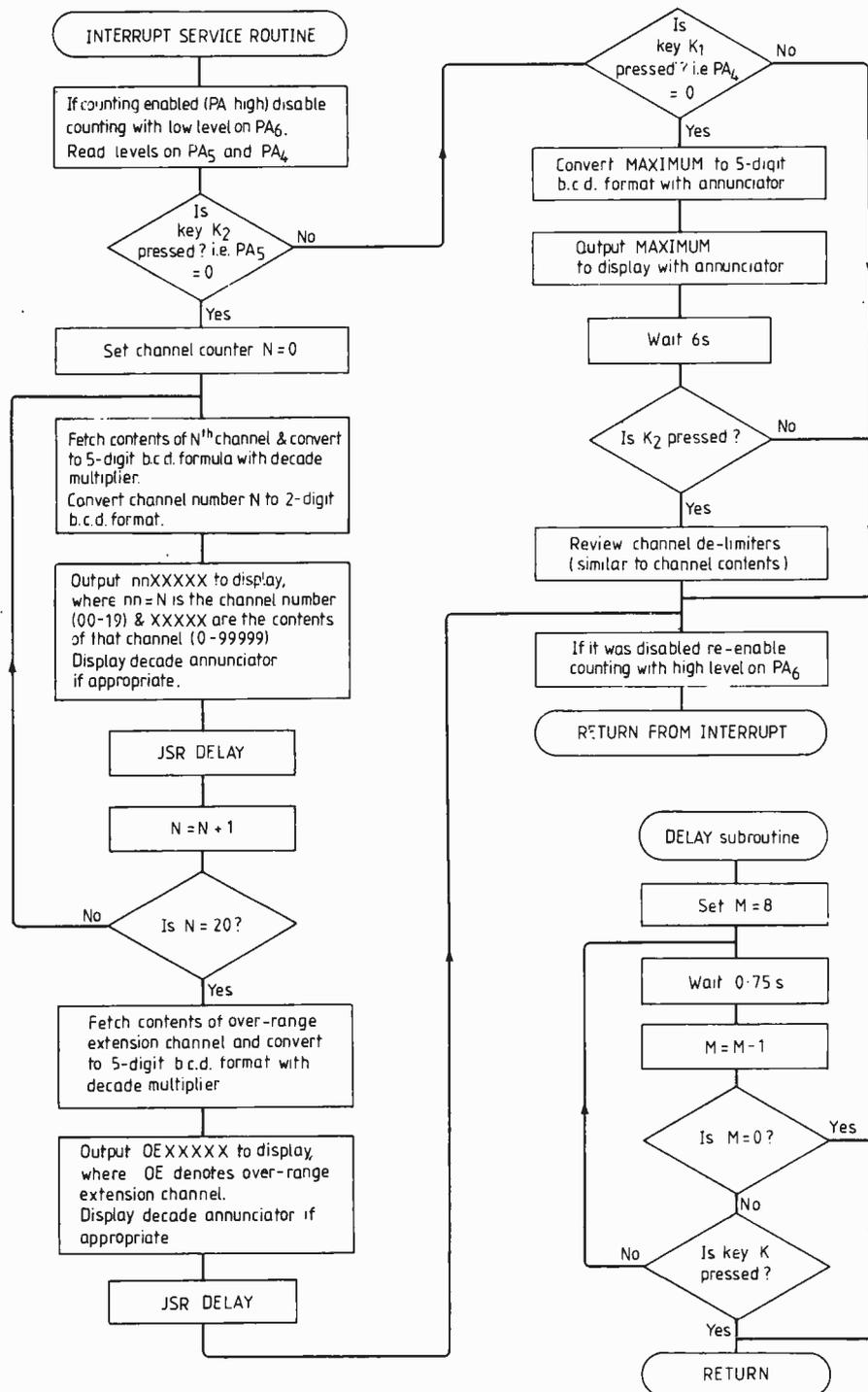

**Fig. 5.** Flow chart of interrogation mode of operation. Key switches K1 and K2 are diode or-ed to the m.p.u. interrupt request line. If K1 is closed, the maximum input value is displayed briefly. Closure of K2 initiates a cycle through all 21 channels, displaying briefly the contents of each. Holding K2 closed accelerates the scan. Note that an interrupt can be pending, even though neither switch is closed.

single byte, and it is this which is sent to IC<sub>3</sub>, by the m.p.u., on the data bus. By writing these data to the correct address, the latching CS pulse to IC<sub>3</sub> is generated automatically. The circuit around the n.p.n. transistor connected to pin 2 of IC<sub>3</sub> varies the display contrast via the 200kΩ Cermet pot.


Address decoding for i.cs 2 and 3 is carried out by nand-gates IC<sub>5d</sub> and IC<sub>6a</sub>, and IC<sub>5</sub>, respectively, which generate the CS signal for IC<sub>3</sub>, and the chip and output enable signals CE and OE for the eprom. Thus the eprom is mapped into address range IFFF-1800, whilst the display is mapped into 17FF-1000.

Power is supplied to the circuit via a

protective germanium diode by three 1.5V alkaline D-cells, resulting in a supply voltage of typically 4.3V. Although i.cs 2 and 3 are nominally 5V parts (all the rest are 3 to 6V), in practice the complete circuit functions correctly down to a supply voltage of 2.5V.

As regards the operating temperature range for the circuit, intended as it was for field use in Northern climes, the instrument functioned satisfactorily down to a temperature of -25°C, at which point the l.c.d. ceased displaying (temporarily). The rest of the circuit still functioned at -30°C, however.

Detailed operation of the circuit as a whole can best be understood with the aid

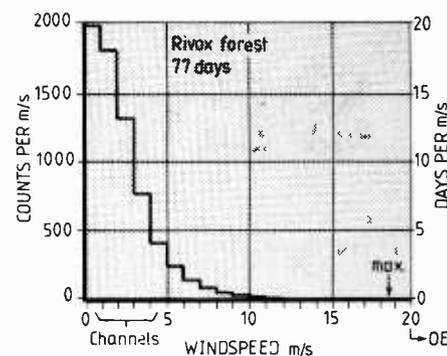

**Fig. 6.** Results from 11 weeks of windspeed measurement at Rivox Forest (see text).

of the flow diagram in Fig. 4 for normal sampling operation, and with that of Fig. 5 for the interrogation mode.

## Construction

Although wire links could be used on the component side of the printed circuit board, as in the instrument shown in Figs 1 and 2, a double-sided board greatly simplifies construction, and foil patterns for both sides of the board are avoidable (see below), and together with a component overlay assembly is straightforward. As in Figs 1 and 2, the display part of the board can be separated from the processor board to produce a more compact instrument. In this case the 11-way ribbon cable connecting it to the processor board should not exceed 30cm in length. For improved immunity to electrical interference (e.g. from lightning) the p.c.b. should be mounted close to a conducting surface, itself connected to the circuit common line.

Four versions of the instrument have now been built, and one of these has been used for monitoring windspeed 2 metres above the forest canopy in the centre of Rivox forest, near Dumfries. The results of 11 weeks of sampling during mixed weather, with mostly light winds and several thunderstorms, are shown in Fig. 6. The circuit itself was mounted in a small waterproof plastics box with a transparent lid (RS 507-977) and reed switches, operated with a small magnet from outside the enclosure, were used for K1 and K2.

I should like to thank all those at Strathclyde who have been involved in any way with this work, and in particular Dr C. R. Lloyd from the University of the South Pacific, Fiji.

Printed circuit boards, programmed eproms (except for the look-up table in the first 40 memory locations) and a program listing can be obtained from D. Smith, CII, Strathclyde University, 100 Montrose Street, Glasgow G4 0LZ.

## References

1. Forrester, T. D., *Wireless World*, March 1983, pp. 39-42.
2. Gordon, J. L., *Wireless World*, May 1981, pp. 42-44.

W

# Static Z80 simulator

*Static faults that manifest themselves as obscure bugs dynamically or that prevent the processor from running can be tedious to find. This tool simulates Z80 signals for design proving and prototype fault finding.*

When designing microprocessor-based equipment, engineers generally concern themselves with the dynamic properties and problems of the circuit. This is reflected in their armoury of instruments: logic probes, oscilloscopes, logic analysers, signature analysers, and so forth. This approach is naturally carried forward to the development of firmware, where in-circuit emulation of the processor or prom is common.

The tool described enables the engineer to quickly solve the purely static design and implementation problems before the processor or even all the active components have been installed. Problems often manifest themselves as obscure bugs in a dynamic environment (e.g. a floating interrupt line) or may prevent the processor from running at all (e.g. an address line shorted to earth). Such faults tend to be very tedious to find using conventional "bussing" of the wiring.

The circuit is designed to simulate most, but not quite all (see 'Limitations'), of the functions of a Z80 microprocessor in a static manner. The choice of the Z80 is purely arbitrary and the same principles may be applied to any device. Necessary changes are indicated, where possible. Physically, the simulation is achieved by bringing all the signals to a 40-pin header plug, which is plugged into the circuit in place of the microprocessor.

## Circuit description

The circuit is shown in Figs 1 to 4 and each group of pins is described separately below. The Z80 pin connections are summarized in the Table.

**Address lines.** There are 16 address lines,  $A_0$  to  $A_{15}$ , connected to pins 30-40 & 1-5 (Fig. 1). These lines are output only and always active. They are held at logic 1 by a mild pull-up resistor (10k $\Omega$ ) and switched to logic 0 by shorting to 0V. Red l.e.ds indicate the state of each line and any shorted to 0V can quickly be detected. For processors with multiplexed address and data lines, tri-state buffers would be needed for the address lines, enabled by the appropriate control signal ( $\overline{ALE}$ ).

**Control and status output lines.** There are eight control and status output lines (Fig. 2):

- $\overline{IORQ}$  – input/output data transfer, pin 20
- $\overline{MEMRQ}$  – memory data transfer, pin 19
- $\overline{HALT}$  – processor halted status, pin 18

---

---

## by Colin Walls

---

---

- $\overline{M1}$  – machine cycle 1, pin 27
- $\overline{RD}$  – input data transfer, pin 21
- $\overline{WR}$  output data transfer, pin 22
- RFSH – dynamic ram refresh cycle, pin 28
- BUSAK – bus ownership acknowledge, pin 23

The  $\overline{IORQ}$ ,  $\overline{MEMRQ}$ ,  $\overline{HALT}$ ,  $\overline{M1}$ ,  $\overline{RD}$  and  $\overline{WR}$  signals are de-bounced using an S-R latch implemented by means of two cross-coupled nand gates. The top normally high output provides the active-low signals. The complementary output of  $\overline{RD}$  (i.e. RD) is also used to clock data input (see 'Data lines'). Green l.e.ds indicate the inverted signals. The RFSH and BUSAK are not implemented (see 'Limitations') and are held high by a mild pull-up (10k $\Omega$ ). **Control and status input lines.** There are eight control and status input lines (Fig. 3):

- $\overline{INT}$  – maskable interrupt, pin 16
- $\overline{NMI}$  – non-maskable interrupt, pin 17
- $\overline{RESET}$  – system reset, pin 26
- $\phi$  – clock, pin 6
- $\overline{BUSRQ}$  – bus ownership request, pin 25
- $\overline{WAIT}$  – wait state request, pin 24
- $V_{cc}$  – 5V supply input, pin 11
- Gnd – 0V supply input, pin 29

The  $\overline{INT}$ ,  $\overline{NMI}$  and  $\overline{RESET}$  signals drive green l.e.d. indicators.  $\phi$  and  $\overline{BUSRQ}$  signals are not supported and are left unconnected (see 'Limitations'). Lines  $V_{cc}$  and Gnd may be used to supply power to the circuit under test (separate supply leads being provided to the simulator) or to take power from the circuit to power the simulator. An alternative would be to provide a common ground, but separate 5V supply to the simulator. The supply is confirmed by a yellow l.e.d. The  $\overline{WAIT}$  signal is stretched by the 555 monostable to catch short pulses from peripheral devices. The inverted signal is displayed on a green diode.

**Data lines.** There are eight data lines,  $D_0$ - $D_7$ , connected to pins 14, 15, 12, 8, 7, 9, 10 & 13, Fig. 4. These lines are bidirectional and may be tristated. The input (read) facility is provided by an octal latch IC<sub>10</sub> driving eight red l.e.ds, clocked by the inverted  $\overline{RD}$  signal (RD). The output (write) facility is provided by a tristate buffer IC<sub>11</sub>, enabled by the  $\overline{WR}$  signal.

The circuit enables either, neither or both read and write to be performed at any one time (see 'Operation').


## Construction

The prototype simulator was built on a piece of veroboard 81 holes long by 18 strips wide. A diagram showing the board layout can be obtained from the WW editorial office. The board was fitted into a plastics box with an aluminium front panel. The 40-pin d.i.l. header plug used as the probe was a solder lug type, to which 38 wires were connected (pins 6 & 25 not connected), bound together to form a flexible lead. An insulation-displacement type header plug could be used but ribbon cable, though neater, is less flexible.
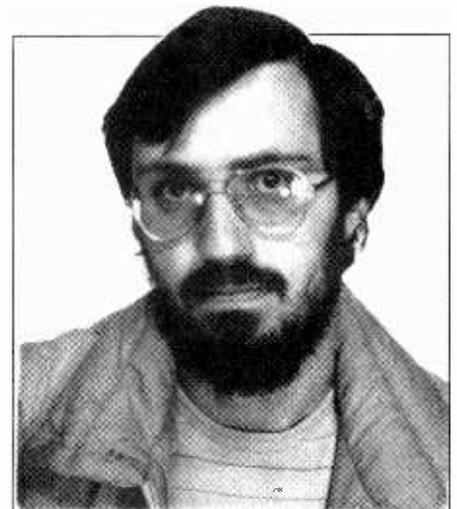
## Operation

The simulator may be used as soon as the prototype microprocessor board is available. Initially, before any i.cs are installed, the board may be checked for any shorted control or bus lines. If lines are buffered, the buffers should be shorted out for this testing phase.

The next stage is to check the address decoding and signal routing in conjunction with a logic probe. The final stage of static testing is to perform read and write operations to memory and i/o devices. A read operation is comprised of the following stages:



Colin Walls graduated from Bath University in 1979 and is now a senior systems programmer at Westcode Systems of Wokingham.

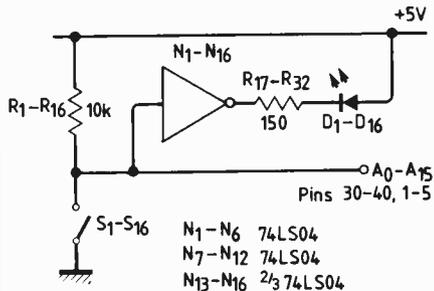


Fig. 1

**Components**

- IC<sub>1</sub> to IC<sub>3</sub> 74LS04
- IC<sub>4</sub> to IC<sub>6</sub> 74LS00
- IC<sub>7</sub>, IC<sub>8</sub> 74LS04
- IC<sub>9</sub> NE555
- IC<sub>10</sub> 74LS373
- IC<sub>11</sub> 81LS95

- D<sub>1</sub> to D<sub>16</sub> 5mm red
- D<sub>17</sub> to D<sub>26</sub> 5mm green
- D<sub>27</sub> 5mm yellow
- D<sub>28</sub> to D<sub>35</sub> 5mm red

- R<sub>1</sub> to R<sub>16</sub> 10kΩ
- R<sub>17</sub> to R<sub>32</sub> 150Ω
- R<sub>33</sub> to R<sub>38</sub> 120Ω
- R<sub>39</sub> R<sub>50</sub> 1kΩ
- R<sub>51</sub>, R<sub>52</sub> 10kΩ
- R<sub>53</sub> 1MΩ
- R<sub>54</sub> to R<sub>57</sub> 120Ω
- R<sub>58</sub> to R<sub>66</sub> 180Ω
- R<sub>67</sub> to R<sub>74</sub> 10kΩ

- S<sub>1</sub> to S<sub>16</sub>, s.p.s.t.
- S<sub>17</sub> to S<sub>22</sub>, s.p.d.t.
- S<sub>23</sub> to S<sub>30</sub> s.p.d.t.

- C<sub>1</sub> 100nF
- C<sub>2</sub> 10nF

Veroboard 81 by 18 holes, case, 40-pin d.i.l. header plug

**Z80 pinouts**

Pin	Signal	Pin	Signal
1	A11	21	RD
2	A12	22	WR
3	A13	23	BUSAK
4	A14	24	WAIT
5	A15	25	BUSRQ
6	φ - clock	26	RESET
7	D4	27	M1
8	D3	28	RFSH
9	D5	29	0V
10	D6	30	A0
11	V <sub>cc</sub> - 5V	31	A1
12	D2	32	A2
13	D7	33	A3
14	D0	34	A4
15	D1	35	A5
16	INT	36	A6
17	NMI	37	A7
18	HALT	38	A8
19	EMRQ	39	A9
20	IORQ	40	A10

Each of 16 address-line drive circuits, Fig. 1, provides a logical 0 or 1 on the address pins. Inverters (N<sub>1</sub> to N<sub>16</sub>) drive i.e.s to monitor logic levels (on=1), enabling lines shorted to ground to be easily noticed. In the control and status output-line drive circuits, Fig. 2, RFSH and BUSAK signals are not implemented, hence their pins are held high by pull-up resistors. The other control signals are generated by switches (S<sub>17</sub> to S<sub>22</sub>) debounced by an SR flip-flop. Inverters N<sub>17</sub> to N<sub>22</sub> drive i.e.s to monitor logic levels (on=0). In the indicator circuits, Fig. 3, INT, NMI and RESET lines are monitored by i.e.s driven by inverters (on=0). WAIT line is monitored by monostable circuit and hence pulses are stretched and displayed by D<sub>23</sub>. In data-line drive and indicator circuits, Fig. 4, input is performed by octal latch IC<sub>10</sub> clocked by inverted RD signal.

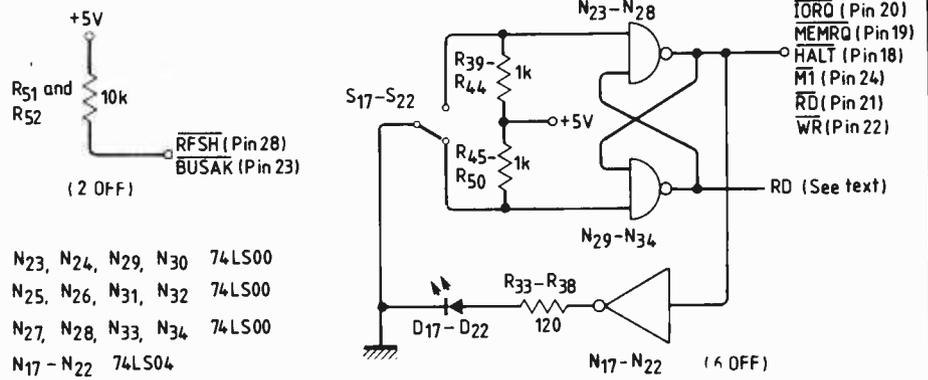


Fig. 2

- N<sub>23</sub>, N<sub>24</sub>, N<sub>29</sub>, N<sub>30</sub> 74LS00
- N<sub>25</sub>, N<sub>26</sub>, N<sub>31</sub>, N<sub>32</sub> 74LS00
- N<sub>27</sub>, N<sub>28</sub>, N<sub>33</sub>, N<sub>34</sub> 74LS00
- N<sub>17</sub> - N<sub>22</sub> 74LS04

Fig. 2

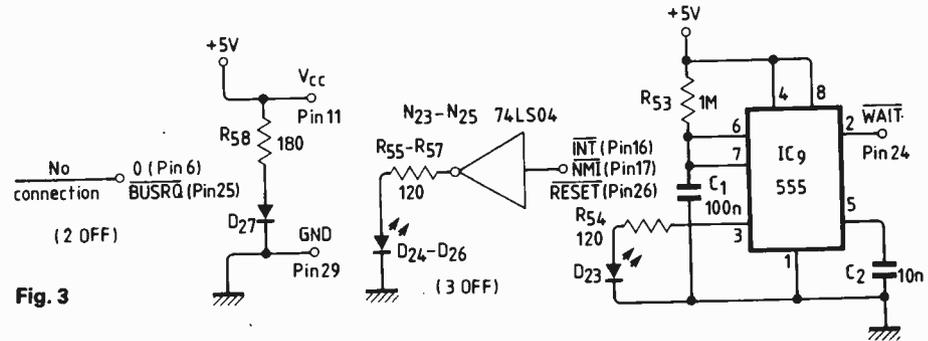


Fig. 3

- R<sub>58</sub> 180Ω
- R<sub>55</sub>-R<sub>57</sub> 120Ω
- R<sub>54</sub> 120Ω
- D<sub>24</sub>-D<sub>26</sub> (3 OFF)

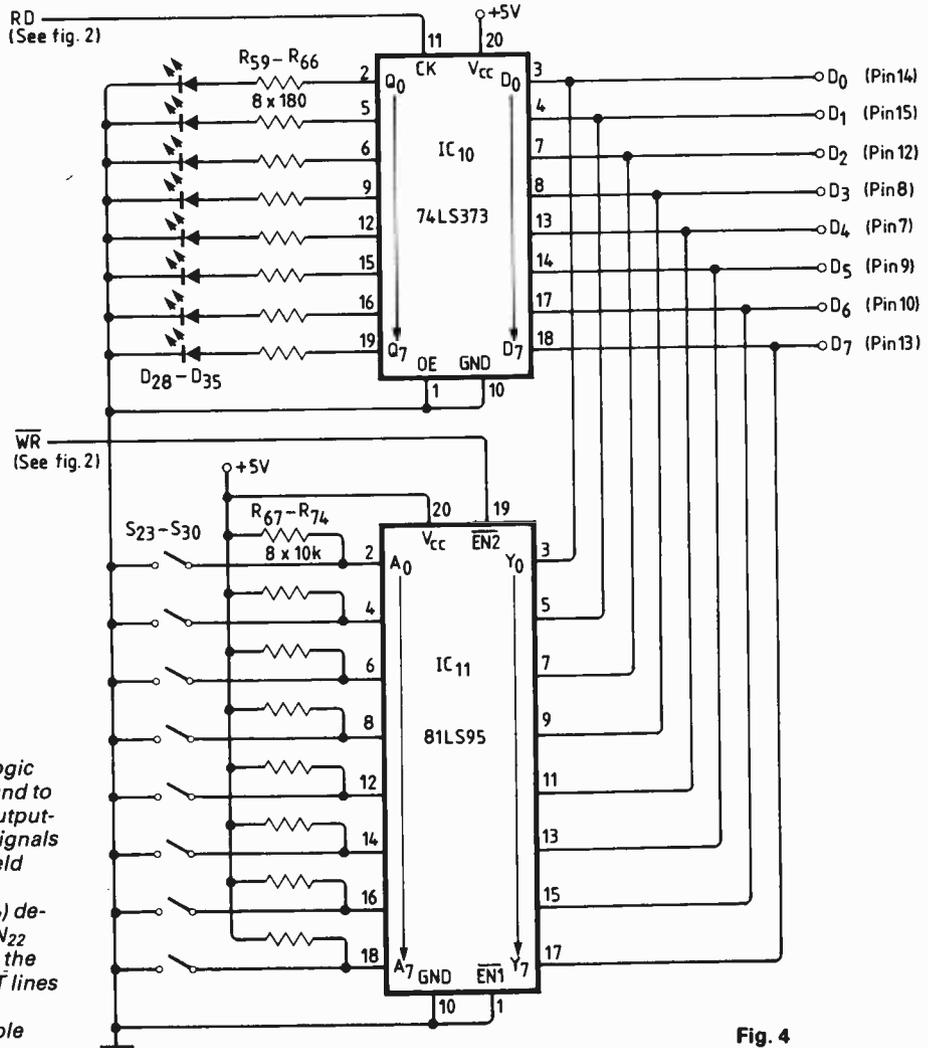
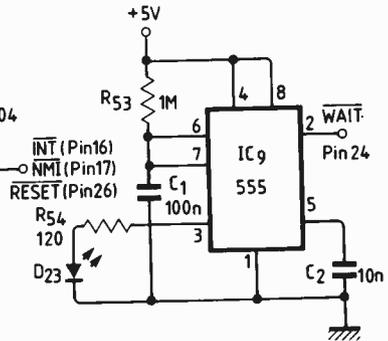


Fig. 4

Output is by octal tri-state buffer IC<sub>11</sub> enabled by WR signal. Logic levels set on the switches are thus placed on the data bus.

# BOOKS

- Set up a valid address on the address bus switches; the number of switches (up to 16 for memory and up to eight for i/o) varies according to the decoding scheme in use.
- Select memory ( $\overline{\text{MEMRQ}}$ ) or input/output ( $\overline{\text{IORQ}}$ ) access.
- Select input ( $\overline{\text{RD}}$ ).
- Data read is displayed and latched on the data bus i.e.d.s.

A write operation is comprised of the following stages:

- Set up the address.
- Set up the required data on the data bus switches.
- Select memory or i/o access.
- Select output ( $\overline{\text{WR}}$ ).

A thorough execution of these three testing phases enables the microprocessor itself to be installed with a high degree of confidence that it will run.

## Limitations

The functional simulation of the Z80 microprocessor is incomplete in three respects. The  $\overline{\text{RFSH}}$  signal is not implemented, as dynamic ram would require more sophisticated circuitry to perform refresh cycles. The clock signal is not monitored; this signal could be divided down and used to drive an l.e.d. to flash at a visible rate. And the  $\overline{\text{BUSRQ}}$  and  $\overline{\text{BUSAK}}$  signals are not implemented. These could be added in a similar manner to the other control signals. Additionally, tristate buffers, enabled by  $\overline{\text{BUSAK}}$ , would be needed on the address lines and control signals to free the buses completely.

## Enhancements

In addition to the functional enhancements listed the simulator lends itself to an improved user interface. A hexadecimal display could be connected to the data and address bus outputs in addition to, rather than instead of, the single l.e.d.s. Similarly, a hexadecimal keypad could be used to enter addresses and data values.

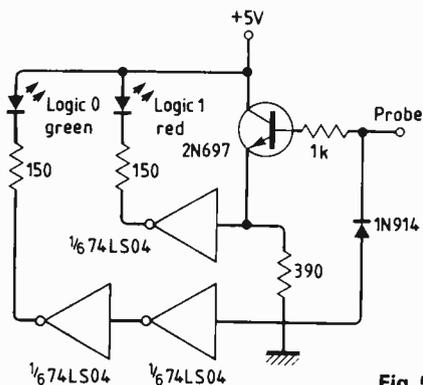


Fig. 5

A basic logic probe circuit also could be incorporated into the simulator. A suggested circuit is shown in Fig. 5, the required gates being available in IC<sub>8</sub>. 

**Einstein's Error** by A. M. Winterflood, 2nd edition, 72 pages, £3 paper cover, from H. K. Lewis & Co, 136 Gower Street, London WC1E 6BS. The author of this second edition says it could perhaps settle the long dispute over the validity or non-validity of Special Relativity. Previous critics have used logic and commonsense to attack Einstein's theory, but A. H. Winterflood argues that its physics and its mathematics are both wrong.

According to the author, the physics error which Einstein made is one which most of us habitually make, namely, the (wrong) assumption that *speed* is merely length divided by time. The mathematical error was one of omission; he failed to enter his 'p-rinciple of relativity' into the general transformation formulae for Maxwell's spherical wave equation.

The author produces these general transformation formulae and shows that they reduce to Lorentz's equations when certain assumptions are made. Lorentz's transform is therefore valid. However, when Einstein's principle of relativity is fed into the general transformation formulae, Lorentz's transform is no longer obtained. Einstein's use of Lorentz's transform is thus invalid.

**Computer-Controlled Testing and Instrumentation** by Martin Colloms, 160 pages. Pentech Press, £12.50, hard cover.

Now that most new professional measuring instruments are designed to be compatible with the IEEE 488/IEC 625 bus and there is an increasing number of small computers available as bus controllers, more and more electronics firms will be considering the advantages of testing their products automatically. This book is a good, clear introduction to the GPIB standard and test systems based on it, written by an engineer who has used this bus to set up his own automated testing system for electroacoustic products.

Its practical approach is enhanced by examples of actual test set-ups, program listings and problems that may arise. Currently available equipment is discussed and illustrated. One may question the rather large proportion of reference information (about a fifth of the text) and more guidance on the economics of using the GPIB system relative to traditional methods of testing would have been helpful. But the book is good value for money and can be recommended as achieving its stated purpose - of providing a comprehensive introduction to the bus and answering questions that may arise when it is being used to set up a test system.

**Principles of Digital Data Transmission**, 2nd edition by A. P. Clark, 310 pages. Pentech Press, £16 hard cover, £8.95 papercover.

This textbook, by an academic with industrial experience, is on the branch of

communication systems engineering resulting from the increasing use of voice-frequency channels for digital data transmission. It is the second edition of a work originally published in 1976 and has been revised, expanded and reset to take account of the changes that have occurred in data transmission systems over the intervening years - new modulation and detection processes, for example.

The first eleven chapters of the book survey the characteristics of telephone circuit and h.f. radio link v.f. channels, while the remaining five chapters are given to a theoretical analysis of the various signals that can be used for transmitting digital data. If the author has extracted even the conclusions of the 519 references presented on 23 pages at the back of the book he has saved the student an enormous workload of reading in this expanding subject. The level is suitable for final year undergraduates or first-year post-graduates.

**Advanced User Guide for the BBC Micro** by A. C. Bray, A. C. Dickens and M. A. Holmes, 510 pages. Cambridge Microcomputer Centre, £12.95, ring bound. The British Broadcasting Corporation microcomputer has acquired a wide reputation as a low-cost machine for workshop and laboratory uses; and for applications such as these, as well as for advanced programming or other kinds, this new guide is an essential reference book. Produced in the same style as Acorn's own User Guide, and with Acorn's blessing, it supplies a great deal of practical information which was not previously available.

## Index and binding

The index for Volume 88 (1982) of *Wireless World* is now available, price £1 including postage, from the General Sales Department, Electrical-Electronic Press, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Our publishers also offer a service of binding volumes of *Wireless World*, each complete with the appropriate index. If you wish to use this service send your copies to Press Binders Ltd, 4-4a Iliffe Yard, Crampton Street, London SE17 3QA with your name and address enclosed. Confirm your order to the General Sales Department (address above) and with this letter to Quadrant House send remittance of £13.80 for each volume (price includes v.a.t. and index).

In both cases cheques should be made payable to Business Press International Ltd.


## BSR clammers out of depression

After some disastrous years, culminating in a loss of £36m last year, BSR are coming back from the brink and have already reported an interim profit of £3.2M for the first half of this year. They owe their success in a great part to the appointment of a new Chairman, Bill Wyllie, who has gained a reputation in the Far East for rescuing ailing companies (BSR is registered in the UK but its headquarters are in Hong Kong, and Mr Wiley was formerly head of the BSR subsidiary Astec, itself a Hong Kong-based company). He has enthusiastically made a clean sweep. BSR, historically has been made up of a very wide diversity of companies some of which were acquired because, for example, they supplied BSR with components. The new regime has rationalized many of the company's operations and sold off many of the accretions.

The new management has put much accent on New Technology. One product was mentioned in this column last month, the Entropo Microwafer, a mass storage cartridge tape drive for computer memory.

Always known for record changer decks, they are now mass-producing an electronically-controlled linear tracking turntable for the o.e.m. market which they will also sell themselves under their ADC label.

In the home computer field they are producing many products for other manufacturers. An interesting technique is being used in the cartridge games roms, produced for the Sinclair ZX Spectrum; They have found a method of connecting the naked chip directly to the p.c.b. without any packaging except a blob of resin to encapsulate it after it is in place. They have called this CB for Chip on Board. Another

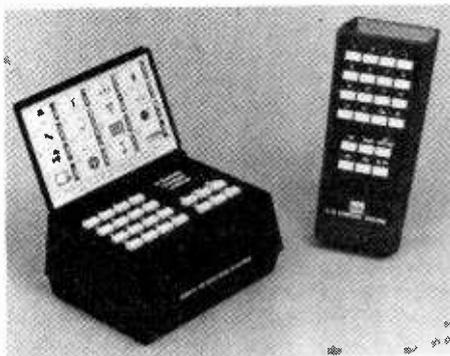

*BSR X-10 can control lighting or appliances all over a house and is itself ultrasonically remote-controlled.*

technique they are developing is surface-mounted components combined with single-sided p.c.bs, to eliminate any drilling or hole plating.

Computer control of the household is possible with the BSR X.10 Control unit which is programmed through a home computer. The system enables lighting or appliances to be switched from a central unit which sends coded f.m. pulses through the normal house wiring to decoders plugged in series with the appliance. Once programmed the computer is unplugged and is only needed if the unit is to be re-programmed.

The dbx branch of the company has produced a new model 224 noise reduction unit, which can simultaneously encode and decode. They have also produced a neat little playback decoder, battery operated, for use with headphone cassette players for both dbx and Dolby B decoding.


Another area for success has been the mass-production of switched-mode power supplies, produced for the o.e.m. market and for use in their own products. BSR is still a vast organization with products as diverse as Swan brand electric kettles and Frazer & Glass plastics pressings for cars; but they now seem to be heading back to success.

## Hunter takes a bow

A new British handheld microcomputer, claimed to be the smallest, most powerful and rugged of its type in the world, has been announced. Called Husky Hunter and designed and manufactured in Coventry by Husky Computers, it is very tough and may be used in almost any environment, even under water. It is about the size of an average book, weighs 1k and is powered by rechargeable batteries with a fail-safe system consisting of a second set of NiCid batteries which are charged from the main cells and provide an additional life of 50 hours if main set is discharged.

Where the Hunter scores over other similar portables, is in its operating system, which is rom-based CP/M compatible; and in its memory capacity, with options of 80K, 144K and 280K. Extended Basic is the resident language and other languages may be downloaded through the CP/M-compatible system or may be installed internally. These include Cobol, Fortran, Forth, Ada, Lisp, C, Pascal and MBasic. File management and a 'virtual disc' system are included. This operates on sections of memory as if they were discs.

Data communication is through an

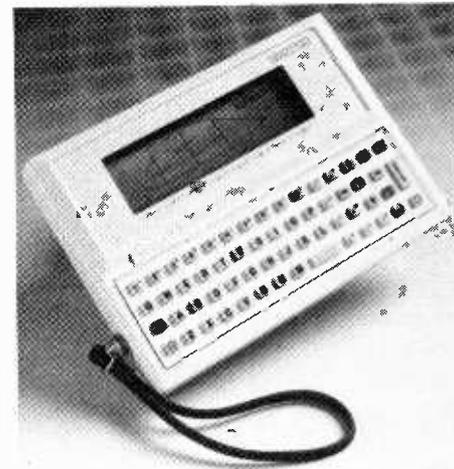

*Husky Hunter a robust portable computer with a massive memory which can run CP/M programs.*

RS232/V24, 25-pin standard connector at a data transfer rate up to 4800 baud asynchronous. A wide range of protocol formats are provided including communication with IBM mainframes.

The Husky Hunter uses an NSC800-4 microprocessor, which executes the Z80 instruction set, operating at 4MHz.

The liquid crystal display is organized as eight lines of 40 characters but is also dot-addressable for graphics and can display graphs, charts and even simple pictures. Graphics commands for lines, boxes, circles and points are included in the Basic. Five different sizes of character may be added to graphic displays. The display can also be used as a 'window' to be scrolled over a much larger display in such applica-

## Transputer unveiled

Inmos have at last revealed the details of their first microprocessor, the Transputer; a 32-bit device that is capable of processing 10mips (million instructions per second). It uses a 'reduced instruction set' (fewer instructions to process, compensated by the very high speed) but has a number of mathematical functions to make it even faster and more efficient. In addition to the processor itself there is 4Kbytes of read/write memory with 80Mbytes/s data rate, and a number of interfaces. The memory interface is a multiplexed 32-bit system which can directly address up to 4Gbytes at a data rate of 25Mbytes/s. There is also a peripheral interface, which can access all industry-standard devices at a rate of 4Mbytes/s, and finally four special Inmos links for connecting the Transputer to four

others. Such a combination would constitute a very impressive computer. One Transputer offers something like the equivalent power of 100 home computers, all networked together. Two Transputers linked could cope with 20mips.

Transputers will be able to be programmed in the standard high level languages but a lot of work has gone into the development of Occam, the Inmos language that can operate on different instruction concurrently. Occam has been used by them to design the Transputer.

So far, Inmos have built the processor, the memory and the communications interfaces on separate chips. When they are combined (it is thought that samples will be available in the third quarter of the year) there will be the equivalent of 250000 active components on a 6.3mm (0.25") square chip of silicon.

tions as spreadsheet calculations.

The Hunter is thought to have applications in many harsh environments; in the construction industry, exploration (its predecessor the Husky has been used in

the Antarctic), for transport and delivery records and for portable data recording in many fields. The makers are keen to point out that it makes a neat desk-top computer as well. Prices lie on either side of £1000

depending on the version selected. Husky claim that if you use the pounds-per-K criterion, then the Hunter is well below the price of any competitors.

## IEEE Futurebus uses Eurocard

The proposed IEEE standard for Futurebus — an advanced 32bit backplane bus for multiprocessor systems — was announced last month in London. Produced by the IEEE microprocessor standards committee working group P896, the draft specification was approved at its November meeting and presented 'hot off the press' at a colloquium organised by the IEEE's own backplane working party on November 29. But ironically there was not one American contribution to the meeting, which included discussion of P896 protocols, its arbitration scheme, system event and control, reliability and testing, and applications, as well as detailed electrical and mechanical specifications.

Discounting any suggestion of resentment over choice of venue or even of the strong European influence, one UK member of the IEEE working group put this down simply to a lack of American funding (for travelling expenses), either because employers wouldn't pay or because committee members couldn't be spared from their usual jobs for this kind of standards work. UK members of the 34-strong working group are financed by the Department of Industry for two years, which has meant that two or three delegates have been able to attend regular meetings in the USA.

The specification is expected to create a large international market for equipment and systems, according to the colloquium's chairman, Peter Fergus of AERE. "Wide

UK public awareness of the specification is essential" he said "if UK industry is to gain early access to this market". The UK was deliberately chosen as venue for the meeting, explained Paul Borrill of University College and chairman of the IEEE P896 working group, so that manufacturers could be alerted to the market — one in which we could expect to see products "within six months to a year".

A key feature of the draft is the inclusion of mechanical specifications, unusual in IEEE standards, and something which the Europeans regard as a breakthrough. It is, of course, the absence of mechanical standardization that has led to a proliferation of differing assemblies in the USA, with no compatibility between them, where buyers get locked-in to particular manufacturers as a result. In P896 the mechanical spec. is based on Eurokit, with the preferred board size being a triple-size Eurocard 280mm deep, and a 96-way DIN/IEC connector, with the possibility of interface with smaller Eurocard sub-systems such as VME. Thus existing European makers have a built-in advantage, "though this will erode" one observer puts it "as soon as the Americans realise the benefits of standardization".

Shortly after the IEEE microprocessor standards committee set about developing specifications for the 696 (S100) and 796 (Multibus) standards it became clear that they did not offer the capability of satisfying future systems, particularly of the

multiprocessor kind and, in recognition, the future bus investigations achieved independent status. That was in 1979, and since then the P896 working group has been through almost as many chairmen as drafts produced! But the result, draft 6.2, is now considered 'hard' and though now available for public comment it will be revised only if practical problems are encountered.

The objectives for the bus have made it a significant step forward in both facilities and performance available to designers. With system-architecture independence it allows distributed bus control and is software-system and processor-independent, it is optimized for 32-bit transfers at a burst rate of greater than 10 million per second, supports fault-tolerant systems, is achievable with 1983 technology and has a ten-year design lifetime, and meets IEC mechanical standards in addition to a number of other system requirements. One of the many innovations in the proposal is the specification of new interface drive devices to meet the low capacitance needed for transmission line driving; existing t.t.l. devices do not have the drive capability. Other features include technology-independent dual-edge handshake, fully handshaken broadcast and broadcast modes, provision for protocol extension, and an arbitration scheme that governs transfer of bus control amongst the 32 devices or sub-systems that may be connected to the bus.

## News at Compec

With 500 exhibitors, Compec is establishing itself as the major showcase for professional mini and microcomputer systems. Following on from our computer survey, we present some of the new products that fit into an industrial, research or educational environment, rather than purely office/business.

### Computers

A British company, Almarc, started by importing American computers but now manufactures its own range of Spirit S-100 bus computers. New to the range is the Spirit 1, based around a 68000 16-bit processor and capable of running under the Unix operating system. Based on plug-in units, a variety of configurations, including multiprocessor computing are possible, and there is a wide selection of plug-in modules for a-to-d/d-to-a converters, extra memory or

interfaces.

The Nohalt fail-safe computer is actually two computers running in tandem with an uninterruptible power supply. The system uses distributed processors and duplicates everything so that if, for example, a disc drive fails, a back-up is available. The system is expandable up to 32-bits, with networking for up to 64 terminals. It is distributed in the UK through BCU Computers (GB) Ltd.

These computers are typical of the newer generation of computers that bridge the gap between micro and minicomputers and are not one computer but systems which may be configured from many options. Similarly, Cromenco Ltd are offering a desktop micro, the C-10 which is an enhanced version of their earlier model. It is available with C-Net, a local area network and distributed networked processing.

Digital have announced the Vaxstation 100 graphics terminal for use with a Vax minicomputer running c.a.d./c.a.m. software. It supports high resolution graphics design but also acts as a text workstation and may be used as a general-purpose terminal linked to the host

computer by an optical cable up to 500 metres long.

Local data collection and processing, testing, diagnosis and controlling of systems in the field as well as normal terminal functions are possible with the 42C hand-held computer/terminal from G.R. Electronics. The unit is fully user-programmable even down to the character set and keyboard functions. Up to 64K ram is available and its contents may be retained by a lithium back-up battery. Applications may be programmed in machine code, in an interpreted high-level language or downloaded from a host computer via a serial interface. The interface can be configured as an RS232, RS422 or a 20mA loop. The 40-character display supports a full ASCII character set and user-definable symbols. A bar-code reader wand may be used.

The Merlin portable computer is an Apple IIe with a miniature 5in display screen and two disc drives which fits neatly into a carrying case. Put together by Xcalibur Computers with Apple approval, it is expected to have many applications in laboratories, industrial and other harsh environments.

## Communications

Advanced Network Communications Systems point out that the Cambridge ring is still the "only viable form of real-time local-area network in existence in the world". The company, founded a year ago with the specific purpose of promoting a British solution to network communications, had on show their 10MHz open local network. The system conforms to the CR82 Standard as specified by the SERC Joint Network Team. Ring driver software for most popular minicomputers is available.

An electronic matrix switch, the MS2000, replaces the traditional electromechanical switch system with electronic control for analogue and digital communication. It allows central test equipment to monitor any part of a network, and maintain comprehensive error reporting to supplement additional test equipment. The switch was introduced by General Audio and Data Communications Ltd, who were also displaying their new remote line monitoring system, RLM2000. This is a low-cost solution to remote site problems by controlling the analysis of all data from the central unit. A master/slave system costing about £2,000 is claimed to replace currently available systems costing ten times as much.

Camtec Electronics launch their JNT-mini pad, a 4-to-10 port version of the JNT-PAD. Packet assembler/disassemblers (pads) form the basis of a range of data communications products for both wide-area (X-25) and local-area (Cambridge ring, Ethernet) networks. The JNT (for Joint Network Team) PAD provides all the functions for connecting up to 16 asynchronous character terminals to X25 networks and is approved for connecting to the BT Packet Switch Service.

A modem giving 2400bit/s synchronous working for £350 is claimed to be half the price of its rivals. It is fully compatible with the BT 2412 V26 modem and auto-dial, auto-answer and rack mounting are all low cost options from Jaguar Communications Ltd.

## Memories are made of . . .

. . . flexible discs say Altek, who were proudly displaying the Mitsubishi 2Mbyte 5.25in drive. Using m.f.m. storage the drives are low height, provide storage at 11844bits/inch at a track density of 96 track/in. Access time is up to 94ms.

. . . cartridge discs, say APS Microsystems who have designed and developed a disc drive which, they say, combines the best features of flexible and fixed disc drives without the disadvantages of either. The Alpha 10+10 is a 20Mbyte disc system which can be used with the IBM PC and most of the more expensive personal computers. It costs £3,400.

. . . tape cartridges, according to Feedback Data Ltd, who have produced a range of quadruple density (6400b/in) drives in two models, the first of which is for data collection from non-intelligent sources, or if the data are in a continuous format where it may be used for file backup or program storage. Both models have RS232 interfaces operating at 50 to 38,400 baud with current loop option. They feature automatic formatting, read-after-write checking and may have up to 16K buffer storage.

. . . microdiscs, according to Sony and Tabor, their American rivals. Both of them were displaying double-sided 3.25in flexible disc drive, with capacities of 1Mbyte. Both seem to be compatible with each other as they both

claim to be plug-compatible with 80-track 5.25in drives. The Sony standard has been accepted by the Public Services Working Party as a suitable standard for equipment used in UK public services.

. . . drums, says Vermont Research, who have introduced a 10Mbyte memory system. This is actually a return to an old idea when each of several magnetic heads covered a single track on a drum revolving at high speed. According to computer historians, this system was a precursor of the multilayer disc pack used by most mainframe systems. The drums were often very large, weighed tons and took days to slow down if ever the system was 'powered down'. The Vermont drum is not so vast and fits neatly into a standard rack. It has an m.b.t.f. of over 25,000h with an expected lifetime of 10 years.

## On the periphery

At the cheap end there were a number of 80-column printers with a variety of typefaces and facilities selling for around £200. Closer inspection showed that many of them, including the Walters Microsystems' WM80, Mannesmann Tally MT80, Lucas LX80 and Sun SX80 were all the same machine with very slight differences in case and style. At the top end of the market is a Swiss (Wenger 4/1) printer with 136 columns and an 18-needle printhead. It can print 'letter-quality' text (i.e. you can't see the dots) at 110 characters/s and data output quality, where you can just see the dots if you look hard, at a staggering 400 char/s. It has every imaginable interface and many mainframe protocols built in. All for £4,000.


For £14,000 you can buy one of CalComps' 107X plotters which can draw on paper from a roll or on single cut sheets, has a plotting speed of up to 1320mm/s and an addressable resolution of 0.0125mm.

An all-purpose interface adaptor, called the XC50 Cross Communications Adaptor, is made by Walters Microsystems. It includes a 52K memory buffer for spooling data being output to a printer, it can convert serial-to-parallel data streams and parallel-to-serial, and convert the data speed on input and output to different data rates. An internal eeprom can be programmed to meet specific protocols, such as converting ASCII code to EBCDIC.

A low-cost graphics tablet enables the user to input drawings and diagrams to a BBC micro. It can be used as a pressure-sensitive keyboard or for cursor control. The Grafpad from British Micro has a program for c.a.d. enabling it to draw circles, squares and rectangles automatically and any design or picture can be saved or dumped to a printer. It costs £125.

Applications are many for the Data and Research Services' Optical Scanner, which can read pencil marks on a pre-printed form and convert them into data for input to a computer. Typical examples are experimental results, meter readings, time control cards. The Open University uses them to mark their assignments when multi-choice questions are answered by pencilling marks onto a form.

A sample-and-hold data acquisition system for the IBM Personal Computer has been added to several other enhancements for the PC to convert it to industrial and scientific applications. The DT2818 is made by Data Translation in Slough. It provides multichannel simultaneous analogue input and output as well as digital i/o and clock functions. Suggested applications include physiological and speed research, multiparameter materials testing and any other applications where auto- and cross-correlation is required.

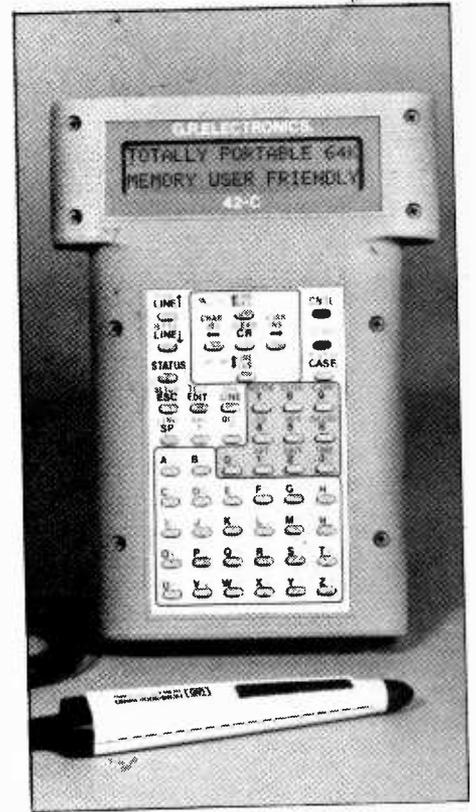

Nominally a hand-held terminal, the 42-C from G.R. Electronics has many inbuilt functions associated with a portable computer.

(See News at Compec)

## News in brief

The dangers of excessive sound level in headphones have been bothering Koss, the American headphone manufacturer. Noise-induced deafness is the most insidious as it does not become apparent until later in life and there is no cure for it; hearing aids just magnify unintelligible noises. Koss have come up with a sound pressure level indicator called the Safelite which is to be incorporated into all their personal stereo products. Research has shown that the harmful level of sound pressure is 95dBA and it is at this level that the Safelite, used in conjunction with headphones, triggers an amber warning light. The first product to incorporate this will be the Koss Music Box, a combined radio and stereo cassette player.

## Practical subwoofer design


We regret that in B.J. Sokol's article in the December issue proofs went inadvertently unchecked. The variable resistor designations were left as  $p_1$  and  $p_2$  on page 41; these correspond to the upper and lower variable resistors in Fig. 2, designated  $R_1$  and  $R_2$  in the caption. Potentiometer  $p_4$  referred to on page 43 is the 10k $\Omega$  component in the upper diagram on page 42, which diagram should have been labelled Fig. 4. Also in this diagram the input polarity of the upper right op-amp should be transposed. In the transfer functions on page 41 parameter A is  $\omega/Q$  (=sign omitted), and the sum should of course have read  $H_0 + k_1 H_1 + k_2 H_2$ . In Fig. 1 V is the a.c. voltmeter reading. Apologies to Dr Sokol, who tells us that for consistency he should have shown a 200k $\Omega$  feedback resistor around the upper op-amp in Fig. 2.



# FORMULA ONE
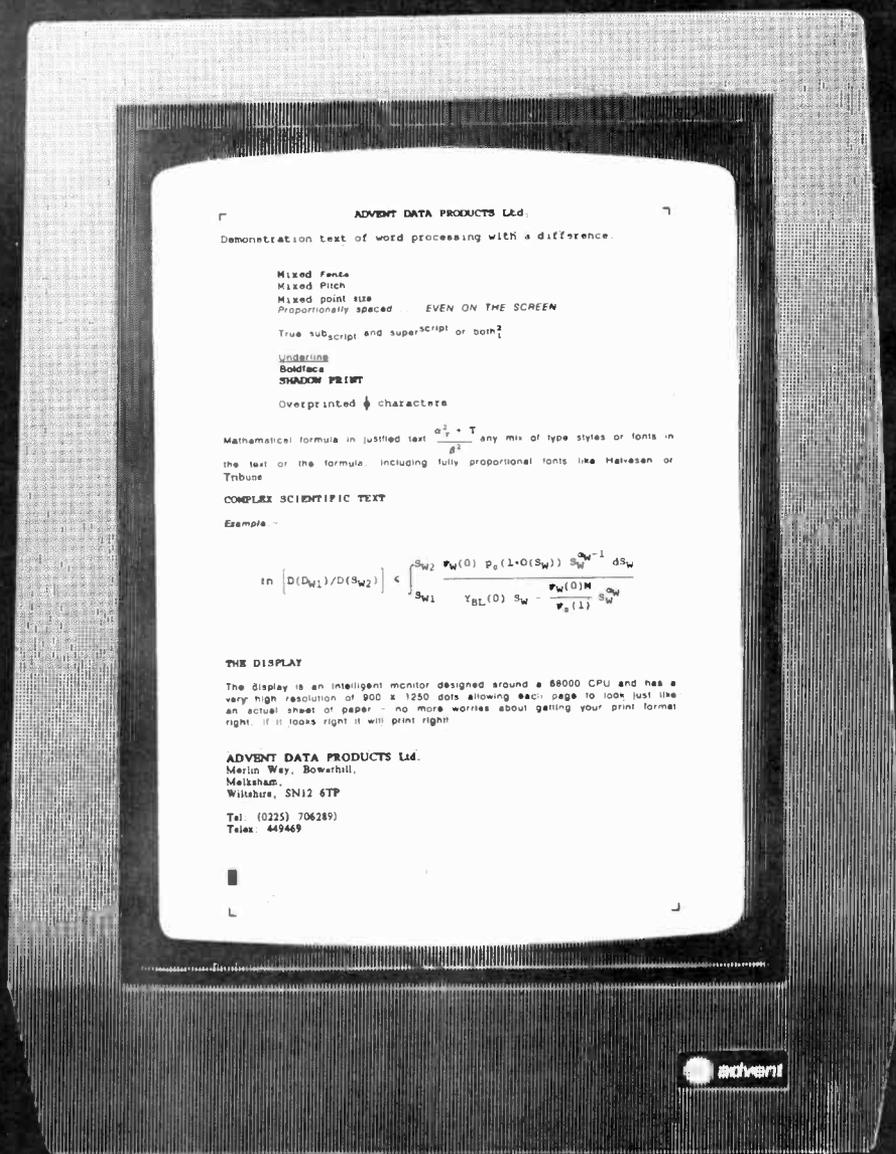
## Word and Formula Processor

FOR COMMERCIAL AND TECHNICAL TEXT  
 TYPESET WORK FROM YOUR TYPIST  
 FIRST FOR SIMPLICITY




The new Formula One system makes it easy to create complex scientific notation and quite simple to select and display different typesets or arrange text in a complex format. To obtain superscripts, subscripts, a different typeface or enhancement no commands are required to be embedded in the text.

Formula One is a new and simple approach to word and formula processing made possible by the development of a very high resolution full page display. It is possible to prepare text in a number of different typefaces which can be in various point sizes and styles coupled with a wide range of technical symbols.

The display is an exact replica of the printed output. This includes true on-screen proportional or monospaced typeface representation and spacing, part line shifts and character enhancements. At last it is possible for the word processing operator to feel confident that if the text is correct on the screen, it will be correct when printed.

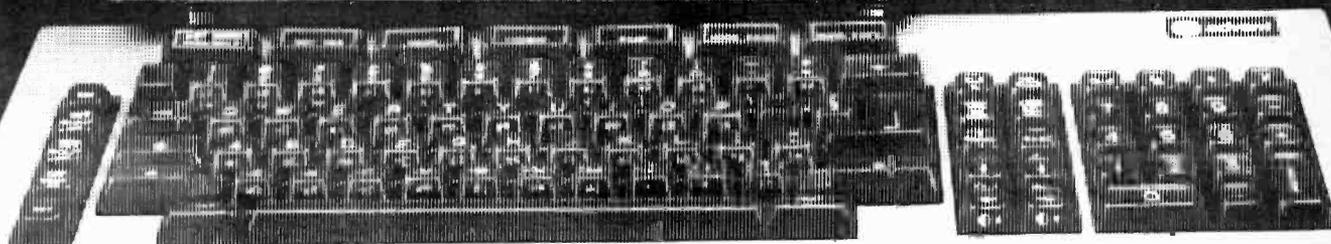Formula One the most powerful and flexible system available.



THE WHICH? COMPUTER? SHOW  
 National Exhibition Centre Birmingham  
 17-20 January 1984

WW - 065 FOR FURTHER DETAILS



**advent**  
 data products ltd

Merlin Way, Bowerhill, Melksham,  
 Wiltshire SN12 7TL Tel: (0225) 706281

# LETTERS

## WORLD TIMING

Your readers may be interested in some background to your recent article about radio time signals and their apparent errors (R. C. V. Macario and G. R. Munro, October 1983).

For very many years the time service of the Royal Greenwich Observatory has maintained accurate scales of both Earth-rotation time and atomic time, primarily for astronomical purposes, and has regularly monitored the errors of selected radio time signals. The results have been distributed to surveyors and others who need accurate time and can compensate in arrears for the effects of known timing errors. Nowadays the primary time signals that disseminate UTC (the internationally accepted version of GMT) from dedicated transmitters are all co-ordinated, and are so tightly controlled at source that, at least in the h.f. bands, propagation and reception errors are usually dominant; consequently there is now little need to monitor their reception. We still distribute the results of observation relating to Earthy rotation and to reception of the other signals that are now used for the most accurate work.

In contrast, the techniques of programme switching and distribution that are used by the broadcasting authorities may introduce unpredictable delays in time signals included in general broadcasts. This makes such signals inherently unsuitable for purposes needing high accuracy and, partly as a result of this, there may be little interest in ensuring that the controlling clock is accurately set.

The six-pips signal used by the BBC originates at the Royal Greenwich Observatory in Sussex in equipment which is adjusted to keep the signal emitted from Droitwich within about 5ms of UTC; this accuracy is poor in comparison with the 1µs or so that is available from our clocks, but it seems to be adequate for the users of this particular service and it does not seriously limit the operational flexibility of the BBC. Some other broadcasting authorities apparently have weaker links with the international time services, whose operations are co-ordinated by the Bureau International de l'Heure.

J. D. H. Pilkington  
Head of Time Department  
Royal Greenwich Observatory  
Herstmonceux Castle  
East Sussex

## CAREERS

I refer to Ron Slater's article entitled 'Careers in Electronics' November 1983. In the last section of this article the writer mentions the 'scarcity' of qualified r.f. engineers. I recall being told, by my then employer, the same thing a decade or so ago. One occasionally reads the same sentiments in r.f. related journals.

Based on our experience, over the last few years in this establishment, the numbers of students pursuing telecommunication specializations in their final undergraduate year this must indeed be the case.

The fact remains, however, that the salaries being offered for new graduates and experienced engineers in this field do not reflect their much quoted rarity value.

If one believes in the supply/demand system and that the salaries offered are geared to this relationship, then one is forced to the conclusion that in reality the demand for r.f. engineers

which is, and has been, fairly constant over the years is still being met by the supply and that their 'scarcity' is a relative term employed in this instance in relation to microprocessor and software engineers.

In the near future the undoubted surplus of the latter may significantly effect the situation?

Dr I. J. Dilworth  
University of Essex  
Colchester

The article by R. C. Slater in the November 1983 issue of *Wireless World* is most useful and informative. However I would like to raise one point.

Mr Slater suggests that the normal method of application for registration by the Engineering Council is through the institutions. The Engineering Council does, however, provide a means of registration direct to it, without the necessity for membership of an institution. The representation within the Council and the fees charged by the Council leave a lot to be desired for these registrants. Since non-institution members form a large proportion of the engineering workforce it seems strange that the Engineering Council is about to make second class citizens of them.

P. H. Milne  
Fareham  
Hants

## SPEED OR VELOCITY?

I am repeatedly bemused by references in your letters pages to the postulation of a "constant velocity for light in vacuo". We know light travels in different directions, so "constant speed" may, just, be worth discussing. If you'll excuse the pun "constant velocity" is a non-starter!

Simon Pengelly  
Tonbridge  
Kent

## WAVE MOTION

Following Mr W. M. Dalton's letter in November, by all means let us stop, but before starting again the following thoughts on wave motion may be interesting.

Waves are only visible on surfaces which may wobble about their mean stationary norm. Such surfaces include water/air surfaces and cross-sections, both of which are actually interfaces. Without a surface of this kind no wave can be apparent, though pressure changes of something approaching a sinusoidal character, sensed here and there in the medium, may allow the apperency of a wave to be deduced in exactly the same way that the existence of energy is deduced from any other change, that is from behaviour. Given such a surface, the apperency of a wave is produced.

Now, one may cut a cross-section of any medium in any plane one desires, and if that medium contains rotational motion the apperency of a wave will be provided so long as the cut is not precisely through the axis of rotation. The process is analogous to deriving a sinusoid from a circle.

Thus there are two distinct kinds of waves, firstly the apperency provided by what I have just said, and the linear pressure-wave: however, the latter can always be resolved as being caused ultimately by rotational motion, for instance by a piston operated through a connecting rod by a crank, in which case, a

"quantum" of its energy might well be a function of one rotation of the crank, and dependent upon its mass and its velocity of rotation when in free motion.

Thus in the end, all wave motion in a continuum (i.e., devoid of a surface) must perhaps of necessity be a function of circular motion, that is, spin. This is a delightful thought to me because it means that if there is an energy gradient in space, which I tried to show might be the function of gravitation in my own letter of November, the Planck Quantum would not be constant but would merely tend to constancy in any locality, being a function of spin energy. This in turn may affect one's thinking upon the speed of light and Doppler, and indeed upon the nature of the space-time continuum.

When considering a microcosm, the thing is so small that any conceivable "point" (which is essentially large by comparison) may contain randomly orientated spins of many-sub-massive building blocks, i.e. a non-polarised state of energy, and it seems that from that "point" one may derive probably everything, including the Laws of Physics, passing Abstract Law on the way as one descends the pyramid.

Conceiving a "point", i.e. a tiny static volume in space-time, is a very different matter to conceiving a dynamic function and mentally reducing the scale of it so that many such functions may be contained within the point conceived: the point must be contained within an agglomerations of quite large brain cells at a given instant of time; however, if one then zooms down the function with the lens of the mind's eye one can conceive the quark, the absolute microcosm, a sub-massive (non-apparent), sub-energetic (in wave terms) and sub-informational (non-provable) entity. It is a game of leap-frog, each leap being a leap of scale ending in unity: call it repeated differentiation, the thought process at work, the function of comparison through time, imagination, call it what you will, but it is the fount of analysis and creativity, the functions which lie behind every tiny act of man-made providence.

Having long been doubtful of the sagacity behind the planar apperency which is a surface device, shallow and superficial, I am now driven to the conclusion that wave believers are not too far removed from flat-earthers, who not only suffer from the disease of planar apperency but who seem to wobble about their stationary norm in space-time! In short, casual analysis always invokes evolution which is essentially a space-time function, and somewhat more dynamic.

J. A. MacHarg  
Wooler  
Northumbria

## FORTH COMPUTER

Brian Woodroffe is not the first to suggest that the coding of 'Next' is the most important part of a Forth interpreter (*Wireless World*, Nov. 83). However, we need only look at the number of 'U's that appear in his examples of primitives, to see that access to the data stack is far more critical. This is where the 6809 shines. It can read or write to anywhere on the data stack, directly manipulate the data stack pointer, and push or pull any number of registers with just one instruction. Its quick 'Next' and efficient return stack follow in importance.

But we mustn't let our enthusiasm colour the facts. J. O'Connor's first suggestion for '+' on

# LETTERS

Table 1 - Clock cycles taken to execute some Forth primitives by the Z80 and 6809.

Primitive	Z80	6809
+	75	32
MINUS (NEGATE)	85	28
( <i>a</i> )	78	27
!	94	33
DUP	65	26
OVER	90	27
SWAP	73	39
DROP	64	19
Total	624	231

the 8088 will certainly run correctly. This is because the result of ADD (BP), AX is written directly back to memory. (However, my 8086 data sheet implies that this method would be slower than the one suggested by Mr Woodroffe).

My own interpreter for the Z80 takes account of this processor's strengths and limitations and improves on the FIG model. In Table 1, I have compared the number of clock cycles taken by my Z80 and Brian Woodroffe's 6809, to execute several Forth primitives. From the totals we can presume that a Z80 will have to run for 624 clock cycles to approximately equal 231 on a 6809, or about 2.70 to 1. Now the ratio of clock speeds between a 4MHz Z80A and a 1.5MHz 68A09 is 2.67 to 1. So they will run Forth at nearly the same speed. Also, since it is vectored, I can quickly change 'Next' to perform error checking, single stepping, or for fast interrupt handling. The Z80A will of course need faster eproms, but the difference is not as great as Mr Woodroffe suggests. The memory access time of the 68A09 is given from 'address lines stable' and at 1.5MHz is 440ns. The equivalent figure for the Z80A at 4MHz is 340ns, whilst the time from the falling edge of MREQ is 240ns. Incidentally, these times do not vary in direct proportion to clock speed, so Brian Woodroffe's calculations of 'performance factors' hold little weight.

In his hardware design, the chip select lines of the eproms and peripherals are decoded directly from the address lines, A12 through A15, with no validation signal. Consequently the chip selects will glitch whenever two or more of these address lines change simultaneously. Also, by subtracting delays of 32ns and 38ns for the decoders, from the processors access time, we are left with 370ns. I can only leave it to Mr Woodroffe to explain why he is using 450ns eproms  
James Kidd  
Warrington  
Cheshire

## ELECTRIC CHARGE FROM A RADIO WAVE

May I come to the support of Professor Jennison, and suggest that his analogue model of a rotating waveguide differs from the real thing only in degree and not in kind?

My justification for this claim is that the model may be smoothly transformed into the waveguide via the following stages.

1. Take Professor Jennison's model and reduce the losses in the phase shift networks, simultaneously reducing the gain of the amplifiers appropriately.

2. When the losses reach zero, the amplifiers will have unity gain and may be replaced by pieces of wire.

3. Successively replace each inductor by two

inductors with half the number of turns in each, until each inductor consists of half a turn only. The ring of inductors now consists of a continuous circle of wire, with the capacitors connected at intervals.

4. Reduce the value of each capacitor, thereby increasing the speed of the wave around the ring until each capacitor consists of a single pair of rectangular plates separated by an air gap.

5. Reduce the length of the wire connecting the inductors to the capacitors until the inductors and the "live" plates of the capacitors are merged.

6. Join the "earthed" plates of the capacitors end to end, and curve them in a cylinder around the inductor.

The original phase shift oscillator has been transformed into a ring of coaxial waveguide, through six stages which do not, as far as I can see, include a discontinuity.

If Messrs Parton and Freeborn (Letters, October and November) agree with me, could they or other readers point out where I have made an unjustified assumption in the transformation?

Peter Hesketh  
Chepstow  
Gwent

## WAVES IN SPACE

I would like to make one comment on T. C. Webb's letter in the August issue. My co-author Malcolm Davidson experimented with sending data (highs and lows for 1s and 0s) in both directions down a 1 kilometre length of twisted pair. He found that the losses experienced by the signals travelling in one direction were less when pulses were being sent in the other direction.


Conventional theory would say that during the time when one positive pulse passes through another going the other way in a transmission line, the  $i^2R$  losses drop to zero. The total current is zero during this time.

Ivor Catt  
St Albans  
Herts
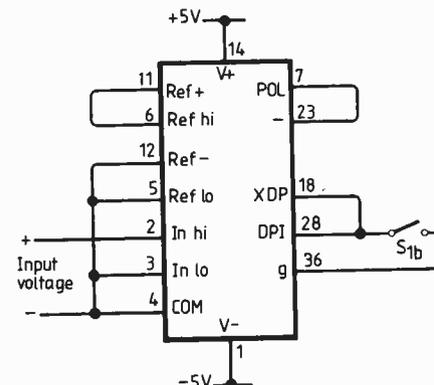
## ELECTRONIC WEIGH SCALE

I am grateful to Mr Wyre of Lascar Electronics for his comments on the use of the Lascar digital panel meter in my electronic weighing scale. (WW October, 1983).

It had not been my wish in the description of this instrument to commit any potential constructor to the use of a d.p.m. unit of any specific commercial origin, since there are a number of suitable units, and I am not in a position to arbitrate between their respective merits.



The circuit details, with reference to the d.p.m. employed, in my instrument circuit diagram were, therefore, deliberately left in outline form only, in the expectation that the would-be user would follow the particular recommendations of the manufacturer of the unit he had selected.

If the Lascar unit is to be employed, the precise connections needed are as shown below.

J. L. Linsley Hood  
West Monkton  
Taunton  
Somerset

## DESIGN COMPETITION

With reference to a letter from Mr Cohen (September 1983 issue) regarding distress alarms for the disabled, such a system was developed and marketed early in the 1970s. It consisted of a v.h.f. transmitter and receiver system. The lightweight transmitter could be easily carried or worn on the person and the receiver, situated in a near neighbour's home or in the warden room of an old people's home, could identify a number of individual transmitters. The system was in fact purchased by a number of Social Services departments. At that time cuts in the Social Services budget occurred and as a consequence widespread use of the system did not occur.

The cost of such a system is, of course, directly proportional to the market volume. Unless it is clear that the financial as well as the social commitment for such systems is both present and of reasonable longevity then however socially desirable such a product may be manufacturers will not invest the necessarily large capital to allow consumer development and marketing to proceed - at least for an attractive sale price.

The cynic may be tempted into thinking that if a volume market existed our far-eastern competitors could produce such systems much cheaper than UK based manufacturers. The net result being that the use of such devices would be at the expense of yet another net outflow of UK based money.

Perhaps if the Social Services department is convinced of the necessity of such a distress alarm it should partially fund UK development and marketing of such a product.

Dr I. J. Dilworth  
University of Essex  
Colchester

In his article and letter in November *Wireless World* Mr Woodroffe is less scrupulous than the Intel benchmark report that he obliquely criticises. This report, which compares the 68B09 with the 8088, can only really be faulted on the grounds that no allowance is made for code frequency in averaging out relative execution times and code sizes. It indicates, quite correctly, that re-entrancy is handled faster by the 6809.

By contrast, the table presented in his article by Mr Woodroffe can be faulted on several grounds. First, it omits the Texas 9995 processor, which competes in the same market sector as the 6809 (64k address, nonsegmented). I wonder why? The 9995 has a non-multiplexed bus and fast 16-bit parallel onboard ram; for 450ns access time its bus cycle is 670ns, versus 800 for the 8088 and 1000 for the 6809. It also makes use of prefetch.

Second, and more serious, some funny arithmetic occurs before the bottom line. The rela-

tive speeds for the 6809 and the 8088 are given as 4.11 and 3.19 respectively although the 8088 actually executes its code faster. This is derived from this "speed for 450 nanosecond access memory." I have news for Mr Woodroffe; in the real world it is not desirable to run a processor with a bus cycle allowing 695ns access at a speed which gives 450ns access. It tends not to work. In the real world the 8088 is faster by nearly 30%. Of course it would be perfectly practical to use a faster 6809 — the 68A or B 09 options — but then he should say so. If he is not actually using these faster devices in his own computer, he should tell us what access time his hardware actually requires, and recalculate his last line on that basis.

The third objection, however, is that in reality the 8088 programmer is unlikely to use the "JMP NEXT", as this requires that NEXT be within 127 bytes, necessitating numerous NEXTs scattered throughout the code rather like Underground stations (I nearly wrote public conveniences) in London. He or she will accept the 9-byte inline code (typical 6809 code is twice as long as typical 8088 code), losing 15 clocks and giving 8.6 microseconds. This execution time is slightly less than for the 6809 running at 1.5MHz with a comparable memory access time. The point, surely, is that the 8088 is the more expensive device, and the time and effort required to use features like segmentation mean that they are likely to be wasted in a small domestic microcomputer. There is no point in buying unused silicon.

The comments about code usage I agree with, except as regards the very arbitrary 80/20 ratio, seen quoted elsewhere as 75/25, 1/3 2/3 — it is true that in most high level languages most of the time is spent pushing garbage to keep the system happy. This is why high level languages waste silicon and time while keeping programmers employed. However, the picture can change dramatically as soon as real arithmetic starts to happen, especially when trigonometry is involved. The makers of home computers assume, generally correctly, that most users will never stretch the resources of the mathematics. I would have thought, however, that electronic engineers differed in this respect; in the days when I was limited to a programmable calculator I remember calculations that exercised the poor little thing for hours on end, leading me to wish a bleeper had been fitted to announce the result. For this reason I would have thought that, again, the TMS9995 would have been a strong contender for a CPU because of its ability to handle 16 bit signed and unsigned multiplication and division in the instruction set.

Perhaps I should add that I am in no way connected with any semiconductor manufacturer.

Martin D. Bacon  
Taunton  
Somerset

## SINE WAVES

Roy Hartkopf's letter in the November issue under the heading "Sine waves, harmonics and sidebands", will invite comment from many quarters. May I put forward mine? First of all, the type of modulation discussed by him appears to be that of amplitude. As we all know, this involves the variation of an r.f. carrier (usually) in amplitude by another waveform impressed by intelligence (hopefully!)

This operation is a multiplicative one, in general, so if the instantaneous voltage be presented by  $e_c = A \sin \omega_c t$ , and the mod. instantaneous

voltage by  $1 + m \sin \omega_m t$  where  $A$  = carrier amplitude and  $\omega_c$  and  $\omega_m$  are the carrier and modulating angular frequencies respectively, multiplying these two expressions and expanding the result gives:  $e_c e_m = A \sin \omega_c t + \frac{1}{2} mA \cos (\omega_c + \omega_m) + \frac{1}{2} mA \cos (\omega_c - \omega_m) t$ , where  $m$  is the percentage modulation.

No sign of harmonics here, Roy. In fact, the two sidebands  $\omega_c + \omega_m$  and  $\omega_c - \omega_m$  have harmonic relationship only under the particular condition mentioned when  $\omega_c = \omega_m$ . Here the lower sideband vanishes and becomes a d.c. voltage of value  $mA/2$ , since  $\cos 0 = 1$ . The upper sideband becomes  $\frac{1}{2} mA \cos 2 \omega_c t$ , which is the second harmonic of the carrier frequency. The statement therefore that sidebands and harmonics are the same would appear to be true only in this one instance.

Another thing, notice that in the process of amplitude modulation, the carrier remains at the same amplitude: this fact borne out by rectified carrier d.c. used for a.g.c. purposes etc., which, when properly filtered, remains constant with constant carrier, irrespective of modulation depth. Where then is the distortion of the varying sine wave?

Of course, harmonics appear as a result of system non-linearity, but that's another story. So until Roy explains convincingly his proposition it will remain in the "r.m.s. watt" file.

In conclusion, I would gently point out to Roy that the derivative of a sine function is not another sine function but a cosine function. Yes, the waveform is similar, but, in calculation if  $l$  were inserted instead of  $0 \dots!$

A. B. Pidgeon  
St. John's  
Worcester

## PREFERRED VALUES

D. R. Watson (November) should realise that it is not true that "the preferred values (the 20% range) are the rounded approximations of

$$1, r, r^2, r^3, r^4, r^5, r^6$$

where  $r$  is determined by the requirement that  $r^6=10$ , and equals 1.468 to 3 decimal places", as a simple test will show.

Sequence	value*	Rounded value	Preferred value
1	1	1	1
r	1.468	1.5	1.5
r <sup>2</sup>	2.155	2.2	2.2
r <sup>3</sup>	3.164	3.2	3.3*
r <sup>4</sup>	4.645	4.6	4.7*
r <sup>5</sup>	6.819	6.8	6.8
r <sup>6</sup>	10.010	10.0	10.0

\* Value is rounded to 3 decimal places. This rounded value is then multiplied by 1.468 for the next stage of the calculation.

There are two wrong answers; 3.3 should be 3.2 and 4.7 should be 4.6. But perhaps when the list of preferred values was drawn up, one preferred value was used to calculate the next one by multiplying say, 4.7 by 1.468 to get 6.900, which was then rounded to give a new preferred value of 6.9. But no, that can't be right; the new preferred value is 6.8.

I wonder how 6.900 was rounded to give 6.8. Teacher never explained that one to me.

If D. R. Watson cares to try he will find the same standard of arithmetic in the 10% and 5% ranges, and for all I know, in the other ranges as well. Surely the "Preferred Range of Values" is the radio industry's "camel" in the permanent exhibition of "horses designed by committee".

W. Scott  
London

## PRECISION PREAMPLIFIER

In your October issue, D. Self presents a design for a most elegant preamplifier. My only reservations are his comments on the reasons for the inclusion of tone controls and his lack of enthusiasm for non-electrolytic capacitors.

First of all, the inclusion of tone control these days, particularly of the Baxandall type, can only be regarded as a sop to convention and perceived desires, rather than actual needs. I never use them, finding their advantages in, for example, increasing the bass, completely outweighed by their effect on other portions of the spectrum. Therefore, as a convenience to those of us who can get along without tone controls, it would be a delight if Mr Self could present a design omitting the controls, while at the same time keeping the non-inversion of phase and the lovely balance control.

Second, the use of electrolytic capacitors as coupling elements, whilst on the surface appearing completely acceptable, ignores some of their operating parameters. It is, for example, not a good idea to reverse bias an electrolytic, and yet I cannot see any provision made to place a standing bias on the coupling electrolytics in order to ensure that the negative portions of the audio signal do not reverse bias the capacitors, however momentarily. Since op-amps are commonly used with d.c. feedback, they usually incorporate some method internally for reducing their output d.c. offset or they would quickly saturate. It is precisely this apparent lack of d.c. bias on the coupling electrolytics which worries me; further, the low-impedance design of the unit means that coupling values are relatively high in order to reduce their reactive effect. Consequently, film capacitors are not a ready alternative due to cost.

To overcome this nuisance, many preamps use non-polarized coupling electrolytics in their split-rail designs. Pure Class A designs can easily overcome the problem due to the single rail. Even using non-polar electrolytics does not overcome their distortion at zero volts, the same as a regular electrolytic. Perhaps this point has not been overlooked by Mr Self, but it would be nice to have it confirmed. From what I can see, bypassing the electrolytics with film capacitors will not help; the electrolytic characteristics will surmount those of the much smaller (presumably) capacity film unit at zero volts, if not elsewhere.

Since my profession is one of electrical engineer at an electric supply authority, I think it instructive to note that capacitors used on the power system are, these days, almost entirely film types utilizing polypropylene dielectric. We don't like 3rd harmonic generation, terrible dissipation factor and high internal losses — presumably that is why electrolytics have not penetrated the market! My opinion is that if Mr Self lashed out and bought the film capacitor, ditched the electrolytics, and listened, he would indeed hear the difference.

As for the use of decent connectors that don't tarnish, I will use gold plated units myself. Everyone else can do what they want. I only suggest reference to power system usage of continuing low resistance connections. Meanwhile I would appreciate hearing Mr Self's rebuttal to my remarks and for him to generate a design without tone controls.

W. M. B. Armstrong  
Halifax  
Nova Scotia  
Canada


# Improving colour television decoding

*This Pal modifier, which switches the V-axis signal for decoding across adjacent lines, results in full luminance bandwidth and a sharp picture, although to some it may appear busy with aliasing dot crawl. But when an adaptive notch is added, continuous high-band luminance and its associated aliasing is filtered out, large-area 'business' is removed as well as horizontal dot crawl.*

To keep costs down a decoding technique involving only one chroma line was investigated. By using adjacent lines from the field, both spatial and temporal errors are reduced to a minimum because field-length or picture-length delays are not involved. If a delay of exactly  $64\mu\text{s}$  is used the information is vertically coherent, although comb filtering by addition or subtraction across adjacent lines, as illustrated in Fig. 11 (a) left-hand side, results only in unwanted products because the two chroma components are mutually at right angles. On line N, V is vertical, On N+1 it is horizontal. The U signal behaves similarly.

Fig. 15 (a) and 15 (b) show the signals into and out of one-line delay ( $64\mu\text{s}$ ) with its PAL modifier. The PAL modifier removes the V-axis phase reversal and the phase setting of the  $2f_{sc}$  signal (driving the carrier input of the modifier/modulator) rotates the vectors. Referring to the left side of Fig. 11 (a) and taking line N at the input to the  $64\mu\text{s}$  delay line operated on by the modifier it emerges as in Fig. 15 (a) and 16 (b), which shows that the V-axis has been switched. Adjacent lines in the field can now be subtracted to cancel the chrominance to obtain luminance, but there is some luminance aliasing, shown as  $-Y$  in Fig. 15 (b).


Although the delay line used in a chrominance circuit is a quarter-cycle of the subcarrier short, to enhance U and V for feeding the chroma demodulators, in the luminance channel the delays are adjusted to be exactly  $64\mu\text{s}$  between subcarrier inputs. The modifier can rotate all the vec-

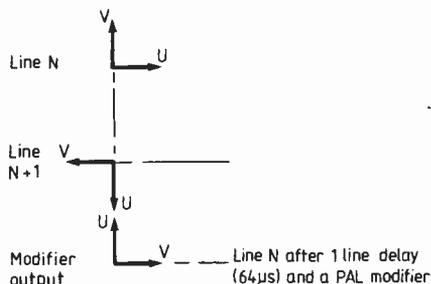


**Fig. 15.** PAL modifier chroma phase relationships (above) for line N+1 and line N emerging (at time of N+1) from line delay and modifier. Phase of  $2f_{sc}$  feed sets output phase of modifier. (b) shows improved methods of decoding PAL signals using a modifier in the comb (right).

by D. C. A. Read  
B.Sc. (Eng.), M.I.E.E.

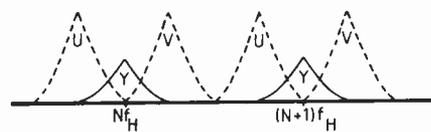tors, removing the  $\frac{1}{4}f_{sc}$  signal offset to the balanced modulator carrier input. The basic expression for PAL-coded video, Fig. 16 (a), defines the effect of the PAL modifier in mathematical terms, indicating that the  $\pm$  signs are reversed to show the




(i) PAL signal components, line N

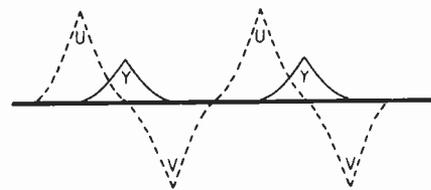


(ii) 1H delayed signal, line N-1



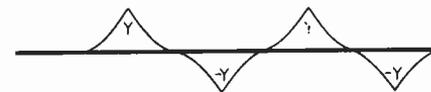
(iii) 1H delayed signal & modified signal, line N-1



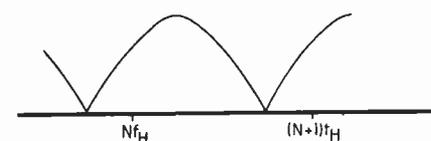(iv) Subtracted output (i)-(iii)  
 $-Y$  components are the unwanted aliasing



(v) Response of comb to U components

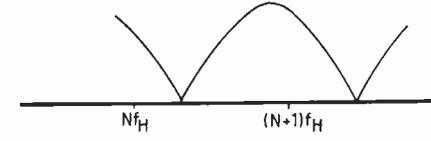

(vi) Response of comb to V components

V-axis reversal by the modifier. Fundamentally, the spectral distribution of the V signal is asymmetrically disposed with respect to the subcarrier frequency, and this asymmetry reverses on alternate lines, Fig. 4. The effect of the modifier is to counteract this reversal.

In the line sweep waveform of Fig. 17 (a) the upper trace is the notch, used when the comb filter breaks down, and the lower trace is the output of the modifier comb. The test signal frequency at the beginning of the line sweep test signal is approximately  $0.5\text{MHz}$ , while at the end of the line it is nearly  $6.5\text{MHz}$ . The effect of the modifier on the luminance channel response in the subcarrier area is thus shown.

The increase in signal amplitude shows that high-band luminance energy is passing through the modifier and is being modulated. This is an unwanted aliasing, not shown in the mathematical analysis, representing high-band luminance energy with a chroma subcarrier dot crawl, which effect is similar to viewing a saturated colour area on a monochrome set with no notch in the luminance path. In addition to this effect the lower trace shows that the modifier output extends to twice the amplitude of the original luminance signal, Figs 17 (a) and (c). Notice the increased bandwidth over which the comb is working compared to the sharp notch. This not only allows more of the chroma sidebands to be removed when comb filtering for clean luminance, but also reduces cross-luminance interference with less dot crawl on vertical chrome edges.

Subjectively the effect of luminance aliasing on pictures is not serious, so that when viewing with the chrominance circuit turned off and paying close attention to fine detail in the picture, the effect is only disturbing on high-detail, high-contrast signals. This is more than offset by the improved sharpness and freedom from notch rings.



A test signal which shows up the cross-luminance, notch and cross-colour effects particularly is a skew sweep, in which the video (sinewave) frequency is constant over the duration of each line but stepped up in frequency on each successive line, with the start-of-line phase maintained. This forms a field sweep. Fig. 17 (b) shows the test signal passing through the luminance notch, and (c) is the comb filter

decoder with PAL modifier, showing the resulting alias (luminance channel only). Fig. 17 (d) shows the typical shape of the comb teeth when using two lines only for the comb filter.

Colour print 2\* shows that the cross-colour from the diagonal luminance is far more serious than the alias introduced by the modifier. Fig. 12 (c) showed a three-line comb for obtaining clean luminance; there was no aliasing because a modifier wasn't used. But colour print 3 shows that luminance diagonal detail is lost where no cross-colour is present.

Because the comb filter method of decoding breaks down on horizontal colour transitions from line-to-line an adaptive detection technique is required to prevent horizontal colour changes producing high dot-crawl, comprising a notch filter which is automatically switched in or out of circuit. Such a scheme will also act when luminance detail produces a high level of aliasing via the modifier. The notch will switch in and reduce the aliasing visibility, unfortunately with a loss of luminance resolution because the notch reduces all the signal energy at  $4.43\text{MHz} \pm 600\text{kHz}$  (3dB points). Normally, adaptive detection recognizes the presence of non-correlation between adjacent lines of the chrominance circuits, but for simplicity the adaptive notch used detects the presence of energy at 4.43MHz in the luminance channel and therefore fulfils a dual role - horizontal colour change and high aliasing. The method of controlling an adaptive notch will depend on the type of encoder used; but as broadcasters would be unwilling to add a comb at the encoder (to reduce cross-colour and high aliasing), because of the large number installed in studios around the country, the simple solution is an adaptive notch, and this is developed later.

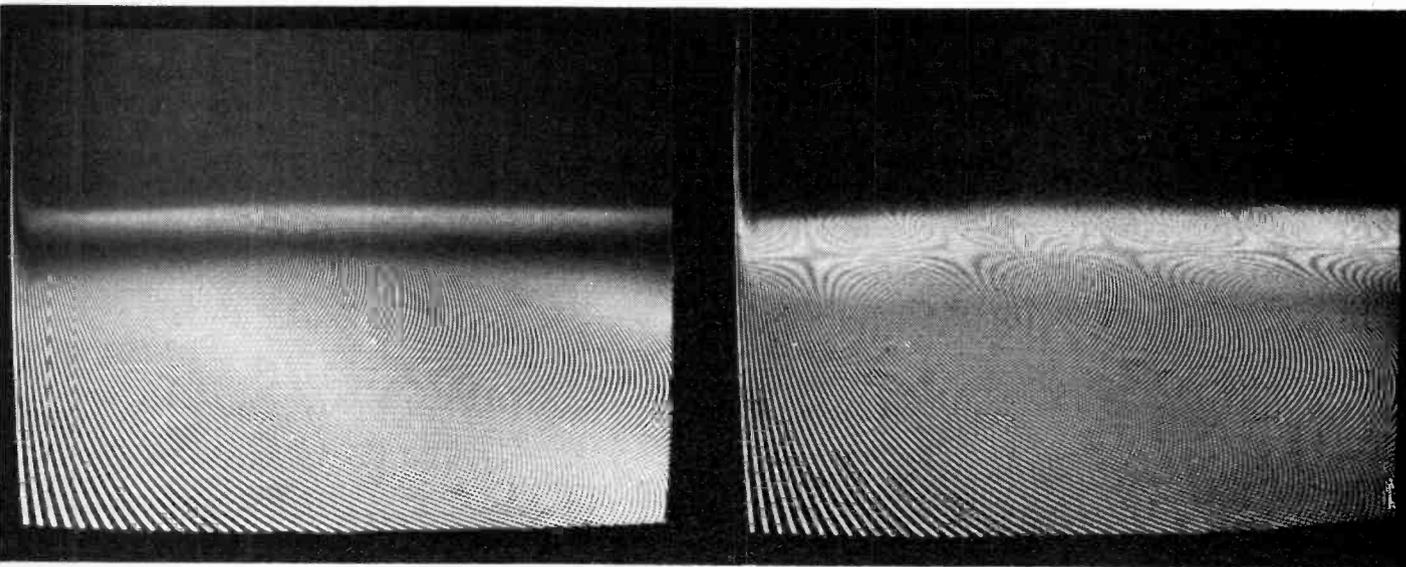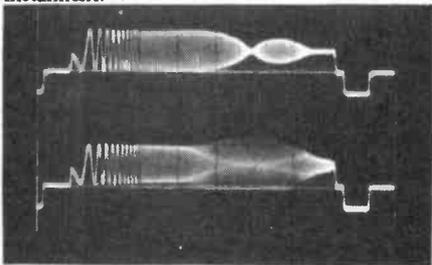\*Colour prints will be included in a subsequent instalment.



### Pal modifier for switching V axis component

The modulated coded video signal is

$$E_m = E_v + E_u \sin \omega t \pm E_v \cos \omega t$$

Using the MC1596 modulator i.c. the signal is multiplied by  $-2\cos 2\omega t$ , that is the PAL modifier operation. Considering the chroma components only, the modifier output is therefore

$$E_m = E_v + 2(-E_u \sin \omega t \cos 2\omega t \mp E_v \cos \omega t \cos 2\omega t)$$

$$= E_v - E_u (\sin(\omega t + 2\omega t) + \sin(\omega t - 2\omega t)) \mp E_v (\cos(\omega t + 2\omega t) + \cos(\omega t - 2\omega t))$$

$$= E_v + (-E_u \sin(-\omega t) \mp E_v \cos(-\omega t))$$

$$= E_v + (-E_u \sin \omega t \mp E_v \cos \omega t)$$


where  $\mp$  sign indicates V signal inversion. The  $3\omega t$  components will be removed by the output filters.

**Fig. 16.** From the PAL colour television CCIR System I specification as drawn up by the BBC and IBA the equation for the complete colour television signal is as shown above. The modulation equals  $E_v$  (luminance) plus  $E_u \sin \omega t$  (B-Y weighted colour difference signal)  $\pm E_v \cos \omega t$  (R-Y weighted colour difference signal), where  $\omega t$  represents the 4.43MHz subcarrier, and the sine and cosine terms signify quadrature modulation.

### PAL modifier using balanced modulator

In the MC1596 balanced modulator used for the modifier, Fig. 18, the  $2f_{sc}$  feed is normally obtained from the low impedance output pin on the PAL decoder i.c. assuming a  $2f_{sc}$  oscillator. Alternatively, a crystal oscillator running at  $2f_{sc}$  under the control of a phase-locked loop could be employed. Two divide-by-two circuits triggered by the negative or positive-going zero crossings of the 8.8MHz sinewave provide the U and V 4.43MHz demodulating carriers in quadrature directly, without involving delay techniques.

**Fig. 17.** Traces taken using a tv line sweep test signal (a), left. Video frequency starts at about  $\frac{1}{2}$ MHz increasing to 6-7MHz at the end. TV screen photographs show the effects of notch and comb on a field sweep signal (below). Notch causes information loss and the comb results in aliasing. With this signal the top tv line is about 10MHz and the frequency steps down to 800kHz on the bottom line. In the subcarrier region the luminance diagonal detail sweeps from near-vertical to near-horizontal. Trace on right shows the shape of comb teeth using two adjacent lines from a field (d).

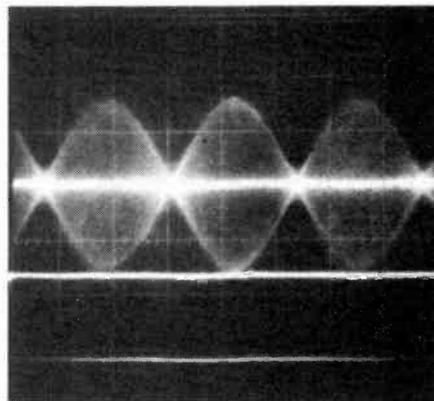

The top trace in Fig. 19 is the gaussian-filtered U and V modulated by the coder with some of the upper sideband removed by the output filter, as developed across the bases of the lower long-tailed pair of Fig. 18. The second trace is the carrier input at  $2f_{sc}$  balanced on pins 7 and 8 of the MC1596 modulator. The final trace is the output, the carrier having been suppressed by balancing at pins 7 and 8 with a potentiometer (in the circuit to be shown later). The final diagram also shows how the spectral energy has been reversed, with added energy at  $3f_{sc}$  which is later removed by the luminance filter, also to be shown in

the final circuit of the revised PAL decoder.

In the receivers which have been modified it was found easier to introduce a separate chroma delay line, as it is normal practice to use the chroma delay line present in the decoder chroma circuit for addition and subtraction enhancing of the U and V components. As a result it is difficult to extract the chroma part of the PAL signal at the output of the chroma length line; because these delay lines are fairly cheap (£2-£3) a separate chroma length delay line as shown in Fig. 20 was used. Also the chroma bandpass filter was improved to form a symmetrical gaussian filter with good group delay performance (i.e. linear phase) that is symmetrical about the subcarrier. Details of the filter are shown later.

Notice the broken line from the output of the chroma bandpassfilter in Fig. 20. This, and a signal of equal amplitude from the modifier output, are fed to the two inverting inputs of the summing circuit (both at half level) so that, when subtracted from the direct signal on the non-inverting input, the circuit will maintain a constant luminance amplitude sweep but the apparent luminance detail in the subcarrier region will be halved when viewed on the picture.

Also shown in broken line on this circuit at the output of the summer is a 'tee-ed off' subcarrier detecting circuit. This simple tuned circuit detects the high-energy 4.43MHz components and modifies one part of the output filter to introduce a notch at 4.43MHz. The output filter has phase equalization which represents several hundred nanoseconds of delay. The delay equalization is placed first in the circuit and the last filter element is the part that is modified to form a notch by the 4.43MHz detector circuit. The notch therefore is switched in before the actual luminance components that are to be removed reach the end of this circuit, having passed through the group delay equalization and the earlier section of the filter.

With horizontal colour bars fed in and the subcarrier-detecting adaptive notch circuit turned off (by lifting one end of the capacitor in the series resonant circuit), Fig. 21 shows that an on each horizontal transition the subcarrier is no longer subtracting since the colour has changed across the adjacent lines. On subtraction large components of unattenuated subcarrier appear.

A field where both luminance level and colour have changed is shown in Fig. 22 (a), top trace. The middle trace shows the luminance output with the adaptive notch working. Observe at the beginning of the line that a small pip occurs where a part cycle of subcarrier is visible because the time taken for the notch to operate is not fully compensated by the delay of the early part of the filter (plus its group delay equalizer). The bottom trace is the direct control voltage on the fet used to add a capacitor in the filter bringing a section to resonance at 4.43MHz. The long delay on the trailing edge is found to be advantageous on the picture using electronic graphics and printing. For example, the

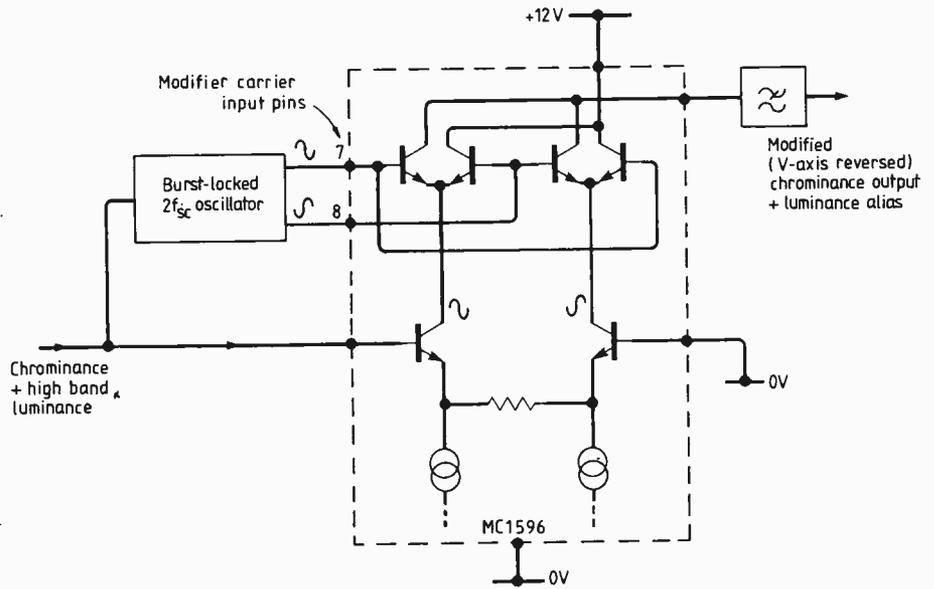


Fig. 18. Pal chrominance modifier with  $2f_{sc}$  oscillator locked to incoming burst using MC1596 i.c.



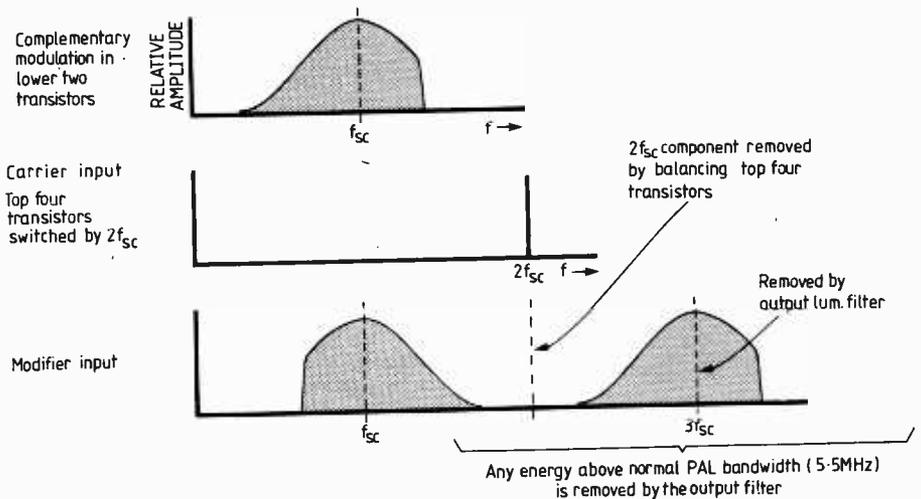


Fig. 19. Modifier chrominance signal envelopes show reversing of the sidebands as the carrier input is high w.r.t. the video signal.

top of a letter T will bring the notch on, and if the tops of Os and other rounded letters appear on the same tv line, the notch will still be on and dot crawl will not occur around these edges although the amount of energy associated with a rounded top surface would not have been

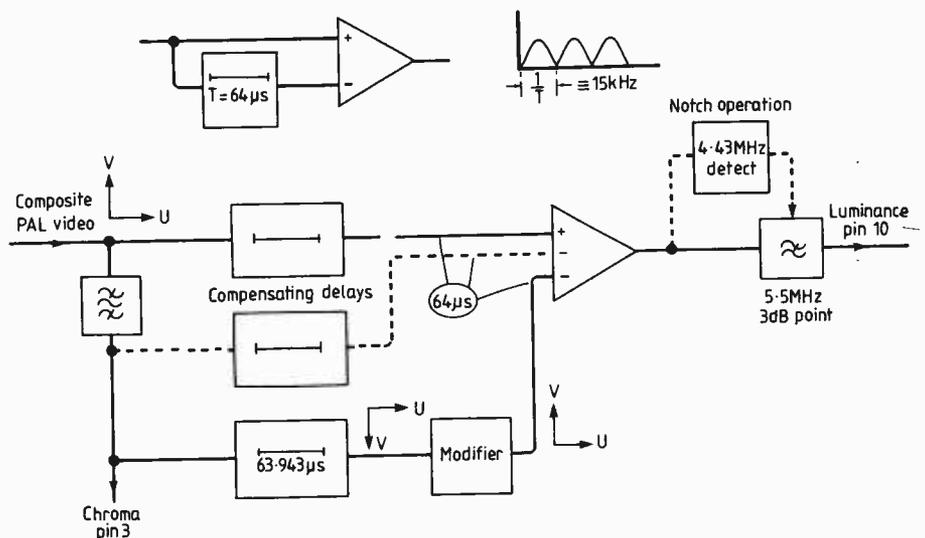

**Fig. 20.** Combing across adjacent lines with the aid of the PAL decoder (page 54, bottom). Block diagram of the PAL decoder is for Mullard one-chip decoder TDA3561A (or 3560). Components within broken-line area are replaced by diagram on p.54; pin 10 is luminance input, pin 3 chroma input.

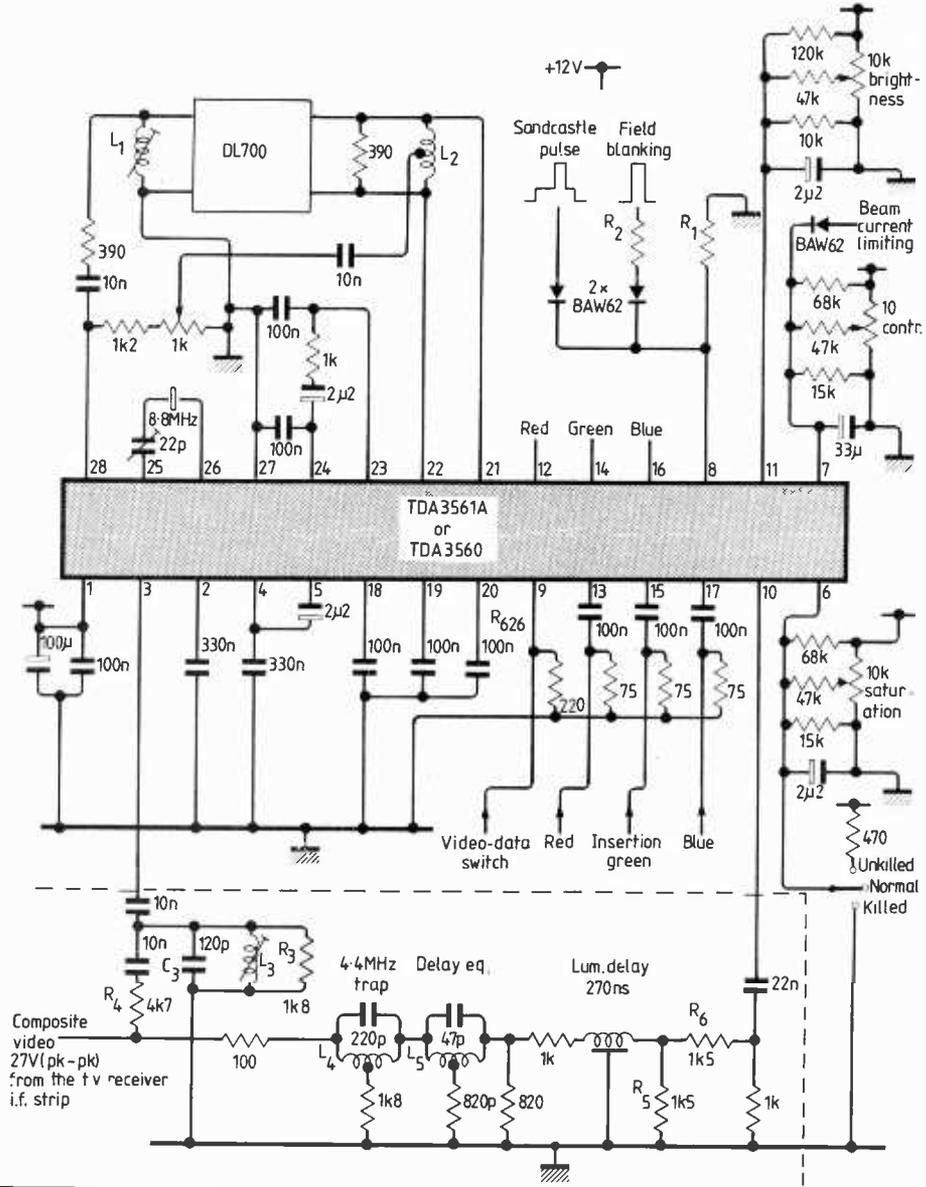


sufficient to bring the notch in. The notch effectively stays in for approximately half a line once it has been switched in by a strong component at 4.43MHz. Fig. 22 (b) and (c) show pictures of the television screen (testing signal, 100% horizontal colour bars) without and with the adaptive notch.

The middle trace of Fig. 23 (a) shows the luminance output for 100% vertical


colour bars, with the cross luminance at transitions much reduced. Also, during the burst period at the beginning of the line, there is little evidence of colour subcarrier in the black level. The bottom trace is the original notch decoder which shows the greater residual subcarrier; (b) and (c) show the resulting pictures. The zone-plate test signal of figure (d) provides a luminance sweep at all radial angles, with,

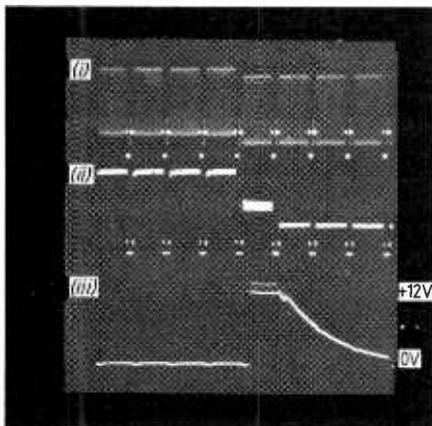(e) showing the response of a notch decoder and (f) the modifier comb with aliasing. Care must be taken not to allow any circuits to overload as the harmonics produce indecipherable patterning, as shown in colour print 4.


Traces in Fig. 24 (a) show the inverting and non-inverting inputs; the output summing point is shown in the bottom trace of (b). The envelope timing is matched, i.e.



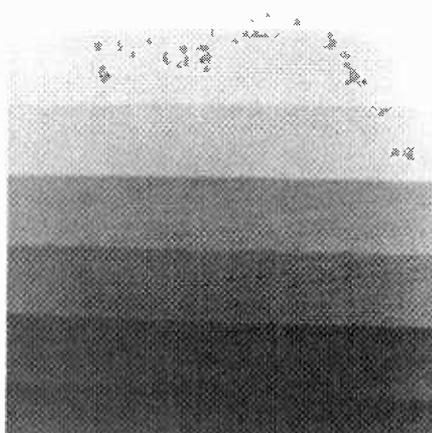(a) (i) Input composite PAL signal  
(ii) Comb Y out  
(iii) Control voltage to f.e.t. switching in adaptive mode. F.e.t. is fully on at +3V




(b)

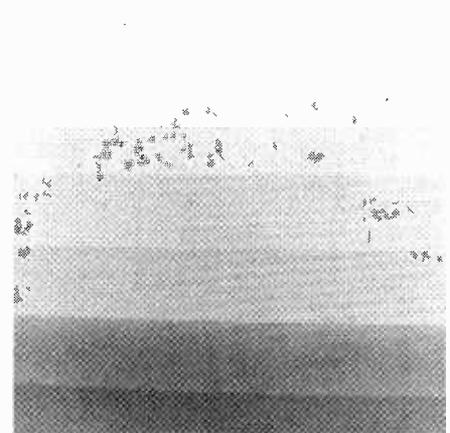


(c)


**Fig. 22.** Operation of adaptive notch (a). Screen photographs are taken without (b) and with (c) the adaptive notch in the luminance channel. Notch removes dot crawl on horizontal colour changes where the comb, subtracting across adjacent lines in the field, would otherwise cause large components of subcarrier to appear.

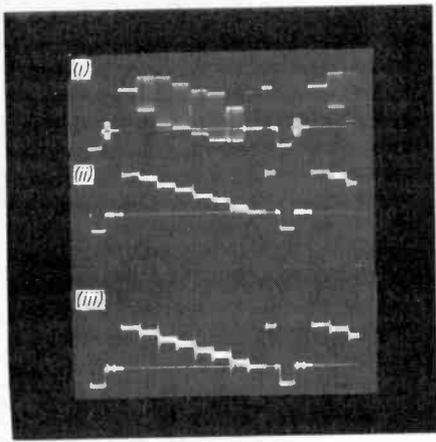

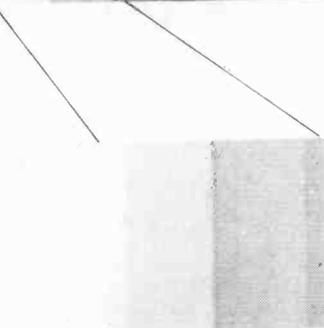(a) (i) Composite PAL video in 100% colour bars  
 (ii) Luminance output using modifier and one chroma line delay  
 (iii) Original notch decoder




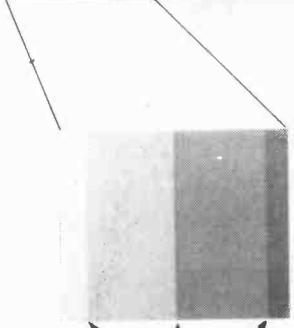(b) Dot crawl as notch cannot remove all sidebands




(c) Modifier comb removing nearly all sidebands


Enlarged areas

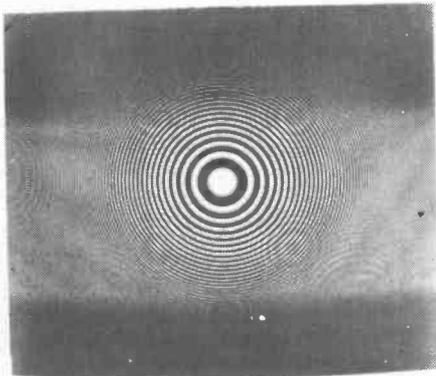

(d) Zone plate direct

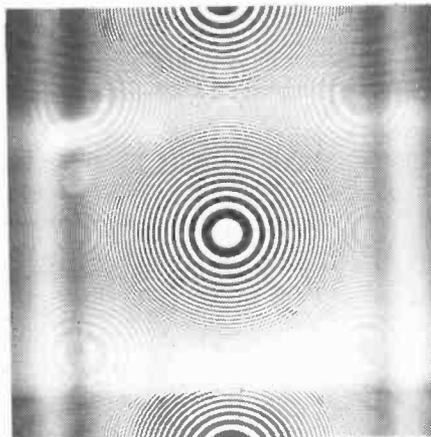

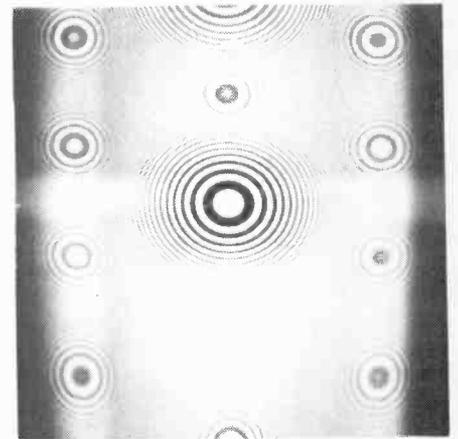(e) 5.25MHz system b.w. limit Notch at  $f_{sc}$




(f) Alias from PAL modifier affecting luminance in  $f_{sc}$  area


**Fig. 23.** Oscilloscope photographs show effect of the notch compared with the modifier comb decoder in the luminance channel (a). Horizontal dark bands on (d)-(f) are due to the camera shutter not being synchronized to the tv scanning system, please ignore and accept apologies.

the two traces of (a) are delay-adjusted to obtain the 64µs spacing, and the colour subcarrier phase and amplitude values are also balanced to achieve cancellation. In

**Fig. 21.** Oscilloscope traces show how the comb filter breaks down on horizontal colour transitions. Test signal is 100% horizontal bars. On certain transitions, the subcarrier adds to produce large amplitudes, as shown. See also Fig. 22(a) showing one transition enlarged.

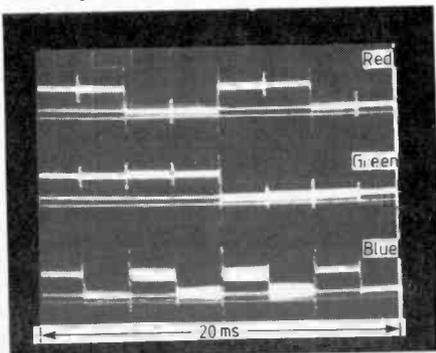


**Fig. 24.** Bottom trace is the PAL modifier and one-line delay signal which cancels the chroma of the top signal to provide clean luminance. (Top trace is a composite PAL signal of 100% colour bars at the green-magenta transition.)

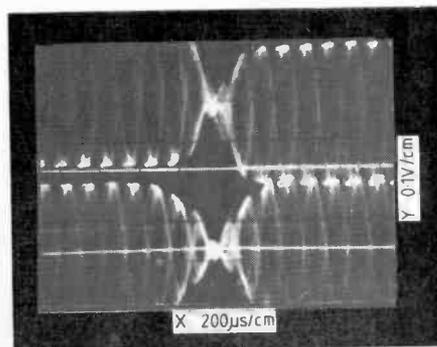

bands generated are large. Residual error is shown in the bottom trace, Y-out, (b). Some is also due to the changed rise times of the subtracting chroma transitions due to the reduced bandwidth of the chrominance signal. Comparison of the two traces at (a) shows this rise time difference. Colour print 5 shows the effect of the reduced rise time on the chroma-only display.

**To be continued**

**Fig. 25.** Group delay errors in the chroma delay line, and changed rise times, detract from the cancellation in the Y output in the bottom trace. Middle trace is the input composite signal. (Subcarrier frequency changed slightly to make it stationary w.r.t. line syncs.)

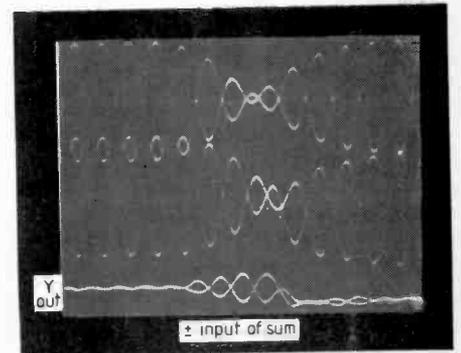

# Constructor's r.f. generator

An a.m. radio chip is the basis of this low-cost design covering 100kHz to 30MHz in five ranges.

It is a regrettable fact that there is at present little interest among amateurs for self-built a.m. or f.m. tuners. However, in the last few years an ever increasing range of integrated circuits, coils, ceramic resonators and so on has become available, and it is easier to build a home-made tuner than ever before. Perhaps one of the reasons for the general reticence is the lack of adequate measuring equipment. The present article will deal with a reliable instrument for the alignment of a.m. and f.m. tuners: an r.f. generator.

At the heart of all r.f. signal generators is a variable frequency oscillator or v.f.o. A fet oscillator makes a simple and reliable generator of high frequency sine waves, capable of working over a wide range of frequencies (Fig. 1). However, this simple

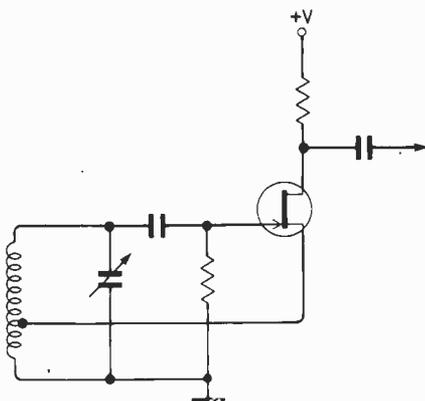


Fig. 1. Output level of this simple oscillator varies with frequency and the tapped coil makes range-switching complicated.

circuit has two major drawbacks:

- The r.f. output will not be constant, and will vary substantially between extremes of 100kHz and 30MHz.
- The need for a tap on the coils or a coupling winding greatly complicates the switching arrangement for the different wavebands.

An oscillator with a constant output and a two-pole connection for the oscillator coil is much to be preferred. One such configuration is based on a kind of r.f. multivibrator driving an LC tank circuit in the collector of the first transistor (Fig. 2). Since the circuit is driven by square waves, the output remains virtually constant over a wide frequency range.

The Mullard TDA1072 integrated circuit is ideally suited for this particular application, since it has a buffered


---

By L. Boullart

---

oscillator output (Fig. 3). Amplitude modulation could be applied to pin 1 (the i.f. output) via a resistor, but a modulation depth of 16% for 1.2V r.m.s. input is as much as can be achieved in this way. Because the output impedance at pin 10 of

the TDA1072 is rather high, separate arrangements must be made to obtain a 50 ohm r.f. output impedance. It is therefore more convenient to apply amplitude modulation elsewhere in the circuitry by means of a dual-gate mosfet in a common-source configuration. The second gate which stands normally at +4V can be used for amplitude modulation up to a depth of 50%. Incidentally, a modulation depth as great as this will result in excessive

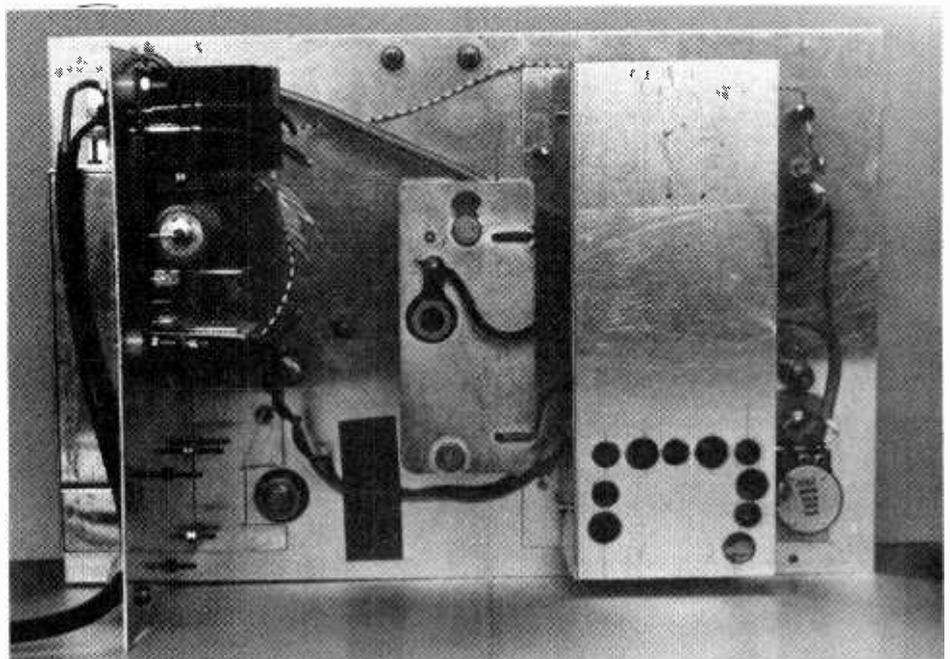

Rear view of the assembly: the r.f. generator board is enclosed in a screening box and the power supply is fixed to a bracket on the left.

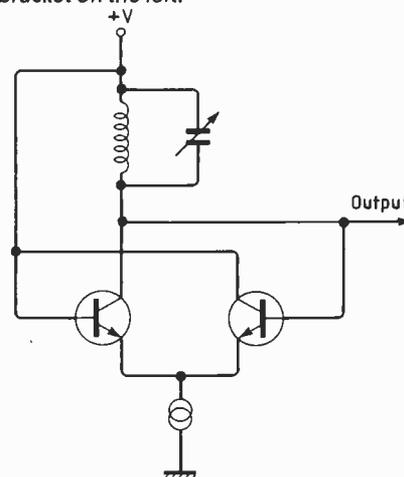


Fig. 2. This more complex design is similar to the oscillator in the TDA1072 i.c.

harmonic distortion: 30%, or even a bit lower, is a better figure to aim for in practice.

A serviceable instrument should also include a calibrated attenuator; and a ladder network consisting of a series of T-attenuators will do the job very nicely. Six independent push-button switches are used: one for 6dB, one for 14dB, four for 20dB attenuation. In practice, however, it should be noted that the last 20dB or so (below about 10 $\mu$ V) cannot be relied upon because of reactive coupling and losses. Table 1 gives full details of the attenuator networks.

Lastly we have to consider the audio oscillator for internal modulation. A Wien bridge oscillator based on an operational amplifier with a thermistor in the negative feedback loop for stabilization will deliver 1.2V r.m.s. with 0.01% distortion, but this is far better than required; besides, the thermistor is a rather expensive component.


As an alternative, silicon diodes can be used to stabilise the signal amplitude provided the polarising current is kept quite small. With three silicon signal diodes in series, the oscillator shown in Fig. 5 (IC<sub>2</sub> etc.) will yield a 1.2V r.m.s. sine wave with a distortion content of between 0.1 and 1%.

A common emitter transistor (emitter follower) ensures a low impedance output and the R-C low-pass filter in its base reduces the total harmonic distortion to 0.06 to 0.6% for a 0.6V r.m.s. signal amplitude. The lowest distortion will be attained with R<sub>18</sub> adjusted carefully to the point at which oscillation begins. The output of IC<sub>2</sub> at pin 6 must not be allowed to exceed 1.2V r.m.s.

The full circuit of the signal generator is shown in Fig. 5. The five frequency ranges are selected by the switch S<sub>2</sub>, for which only two tuning-scales are necessary: one for ranges 1,3,5 and one for ranges 2,4. Each range can be adjusted individually by means of a trimmer C<sub>21</sub> (22pF) and the ferrite core of the coil.

The r.f. output at pin 10 of the TDA1072 is approximately 65mV r.m.s., of which 50mV is available at the input to the attenuator. The audio modulation depth can be varied from 0 to 50% with R<sub>1</sub> and external modulation can be selected by S<sub>2</sub>.

**Fig. 3.** Circuit diagram of the signal generator. S<sub>1</sub> selects the range by switching in one of a bank of five coils (see Table 2). Amplitude modulation is provided by IC<sub>2</sub>; a modulation depth of up to 50% is possible.

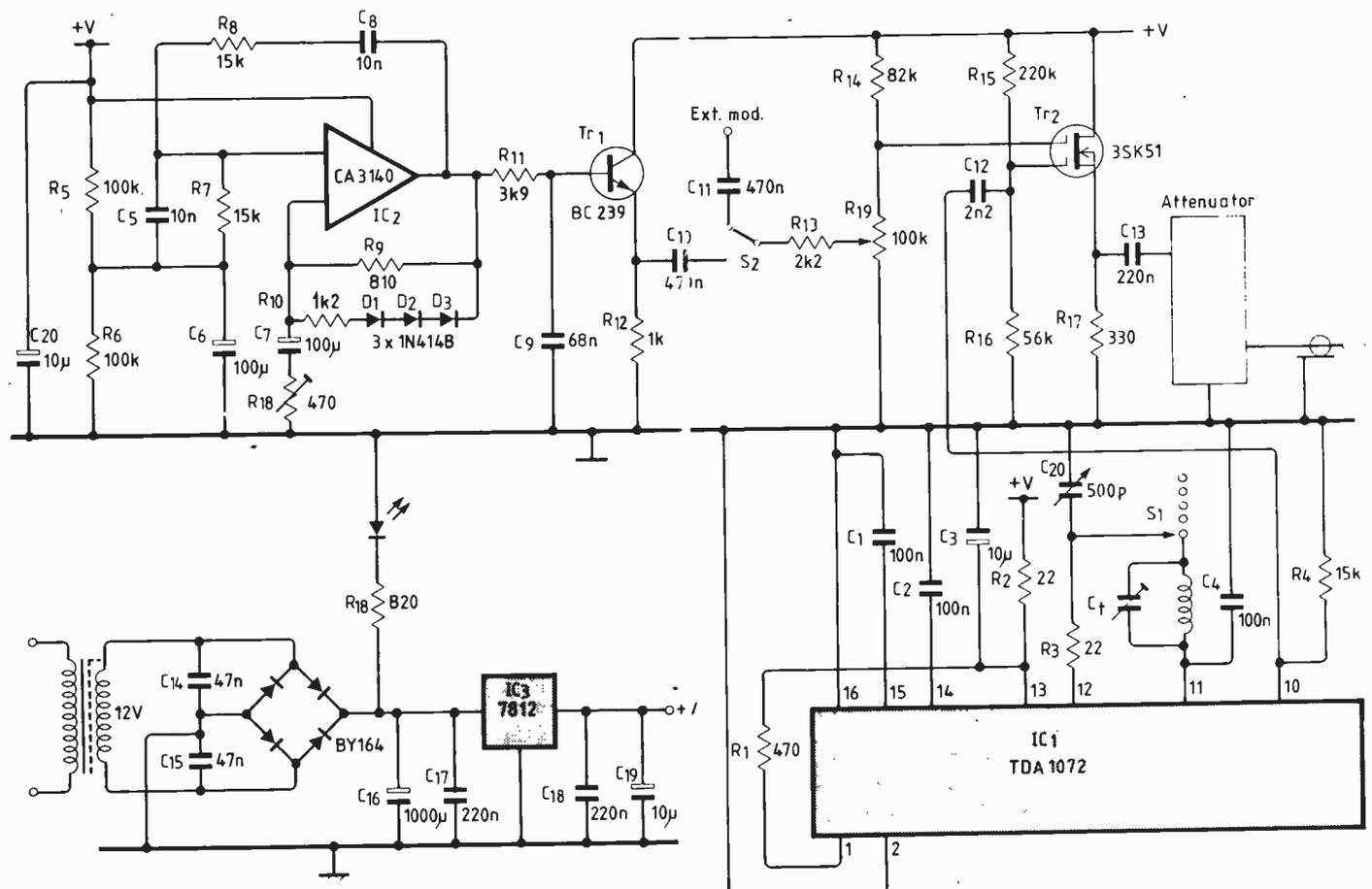

**Table 1.** Resistor values for the calibrated attenuator.

	Atten.	R <sub>1</sub> , R <sub>2</sub>	R <sub>3</sub>
	-6dB	15Ω	68Ω
	-14dB	33Ω	22//330Ω
	-20dB	39Ω	10//270Ω

### Construction notes

The complete r.f. and a.f. sections are mounted on a single printed circuit board which includes the coils and the range switch S<sub>1</sub>. Coil details are given in Table 2. The six push-button switches for the attenuators and their associated resistors are mounted on a separate printed circuit board. The attenuator assembly is divided into six compartments by tin-plate or copper screens soldered to the p.c.b. between the switches. Both boards must be encased in a metal screening can.

The tuning control used in the prototype is a much cherished 1950-vintage dial drive assembly. It is highly unlikely that such an assembly would still be available on the market, and so this aspect of the mechanical construction is

L. Boullart, who lives in Antwerp, became interested in electronics at the age of 12. Since retiring from his career in teaching in 1976, he has concentrated on measuring equipment. Mr Boullart has been a regular contributor for 30 years to periodicals in Belgium, the Netherlands, France and Britain.

left to the ingenuity of the reader. The nearest replacement I have been able to locate is a 70mm scale and reduction drive by Nimi Seiki. A Jackson Brothers SM6 slow motion drive could also be used.

It is advisable to keep more or less to the layout shown in the photograph, with R<sub>1</sub> and S<sub>2</sub> to the left of the main board, the tuning capacitor somewhere in the middle and the attenuator to the right. The attenuator is mounted on a perpendicular aluminium bracket, with the power supply on the other side as far away as possible.

W W

● A set of two ready-drilled glass fibre printed circuit boards is available for this project. The boards, which will accommodate the r.f. generator and the attenuator (though not the 12V power supply) can be obtained by mail order from Combe Martin Electronics, King Street, Combe Martin, Devon EX34 0AD. The price, £6, includes component plans and postage inland or overseas.

Range	Inductance	Toko coils	Base view	Pin connections
1	5mH	CAN 1980 BX		2-3
2	550μH	YHCS 1A589 R		1-3*
3	50μH	154FN 8A6438		1-3
4	5.5μH	154FN 8A6439		1-3
5	0.5μH	S18 8 1/2 turns	---	---

\*Remove capacitor

**Table 2.** Coil details. Pins 4 and 6 must be clipped off with a sharp cutter. Toko coils are stocked by Ambit International.

# Advance into the past

Ivor Catt looks at the inhibitions imposed on designers of computers by the conventional mythology of devices and architecture.

Rational forward progress in computer technology could only be achieved if a significant proportion of computer scientists had some mastery of most of the technologies and disciplines involved. Unfortunately this is not the case, because the necessary spread of knowledge and understanding — from semiconductor physics at one extreme to complex software and computer applications at the other — is too broad.

Computer scientists habitually assume that the conventional wisdom, or myth, imposed on other specialities than their own, is true. They find it convenient to base their views on the state of the art in other fields on information supplied by amateurs rather than those actually working in them. A specialist in any one field tends to see his professional survival as depending on the stabilization of the conventional-wisdom straight-jacket which at one time or another has been imposed on every other speciality. This is because change in these other fields would make his own speciality too fluid, and he would not survive . . . a point of view which, although usually subconscious, sometimes comes out into the open.

For example, around 1970 it was commonly said, "We are having so much difficulty mastering the software of present computers that it is important, *if we are to progress*, that computer hardware be frozen for a decade or more." Some readers will see the irony implicit in this comment, which was often made by programmers with no knowledge of engineering, which meant virtually all programmers. There followed an explosion of complex software techniques, including list processing, which could have been much more easily achieved by hardware modification; but this option had been outlawed. The result was an increase in the complexity and confusion of already over-complex software, and a deterioration in the overall position.

In general, all other disciplines ganged up on each individual discipline and forced it to remain essentially static, at least in its perceived structure when it interfaced with other disciplines. Examples are:

- The blocking of any blending of memory and processing, any move away from absolute von Neumann, and strict adherence to the 'von Neumann bottleneck', even though at one extreme the technology was demanding it and at the

---

---

by Ivor Catt

---

---

other extreme almost all applications were demanding it.

- The blocking of any deviation from the traditional drift from fully serial machines to fully word-parallel machines, even though (a) the technology demanded a reversal towards serial working, (b) the change in the relative cost of circuit and interconnection demanded it, and, strongest of all, (c) a strong mythology had developed that the computer industry was combining with an avowedly serial industry, telecommunications (citing the appointment of a Minister for Information Technology as evidence). Here we see one myth combating and overcoming another, unfortunately the wrong one, "fully parallel fetishism", being the victor.

- The imposition for all time of the t.t.l. logic signal as industry standard. This occurred even though t.t.l. logic, which came into general use in spite of its weaknesses in design (including the heavy standing current in signal lines, the high signal swing, etc), had given way as the industry standard circuit to c.m.o.s., which had much greater circuit density, in which a very different logic signal standard would have been more efficient.

- The maintenance of a key feature of the thermionic valve — the idea that hermetic seal was necessary to stop the cathode from burning up — well beyond the disappearance of the cathode through drastic changes in the technology towards silicon semiconductor l.s.i. Few computer engineers realise that the 'hermetic seal fetishism' which continues today in v.l.s.i. chips dates back to the danger of allowing oxygen to reach a hot cathode, and has nothing to do with semiconductor technology.

- The inexplicable standardization, without a murmur, on the use of Kovar as the metal for the leads coming from an integrated circuit chip, even though every parameter of Kovar except one is bad in this application. The one good parameter is that Kovar wets to glass, so allowing the formation of a hermetic seal. Kovar's bad features include the following:

- It has rather high electrical resistivity, so degrading performance by creating extra voltage drop in the signals entering a

chip.

- It is magnetic, so that signals into a chip are delayed, and energy wasted, while the magnetic field is built up.

- It is not ductile, and work hardens fast, so that there is an unnecessarily large risk of fracture due to bending or vibration.

- Worst of all, it does not wet to solder. In order to make it possible to solder to a Kovar lead, the lead has to be gold plated. However, during the soldering process, the gold dissolves into the solder, creating a brittle alloy and also, should soldering and de-soldering be repeated, the dissolving away of all the gold and the creation of a dry, non-wetted joint between solder and virgin Kovar.

- Microprocessor manufacturers have displayed ignorance of the mechanism of digital signal propagation and voltage decoupling. Placing voltage pins at opposite corners of the package, thus introducing a large single-turn inductor in series with the voltage supply, is the worst possible pin choice, limiting the speed of microprocessors and also making them pattern-sensitive. Although only marginally significant in the old 14 or 16-pin dil integrated circuit, the problem created increases rapidly as the square of the package length, making the large microprocessor chip slow (only 4 MHz), pattern sensitive, and dependent on the layout of the host printed-circuit board in a manner not understood (and so not predicted) by system designers.

- Looking at another aspect of the standard package, I suppose that I should be relieved that the industry did not standardize on the even more absurd IBM SLT package, 1965 vintage, which had a line of pins down all four sides of a square package. When deciding how the pins should exit from an integrated circuit package, the decisive aim should be to minimize the obstruction of printed circuit conductors in the host p.c.b. The two, unrelieved, lines of pins are about as obstructive, and therefore as inefficient, as it is possible to devise (*pace* the IBM SLT). Alternate pins should have been staggered, and this is a simple operation (which would not have created significant problems in the manufacture of i.c. sockets). I only mention this to show how thoughtless and casual developments have been, not to propose change at this late stage.

- The standardization by the industry of t.t.l. with its totem pole (push-pull) output was based on the mistaken idea that the

load seen by an i.c. output is capacitive. This was true for thermionic-valve logic gates, with their high impedance, low current outputs, but ceased to be true when we used transistors, at which point the load seen by a fast output became resistive; either a transmission line characteristic impedance (resistance) or a t.t.l. input load (also essentially resistive). Whereas a capacitive load could helpfully be driven push-pull, today a resistive load can perfectly well be driven by one transistor, as is demonstrated by the fact that the fastest existing circuit, 1 ns e.c.l. has a single transistor output.

### Speed of logic

Generally, the limiting factor in the speed of logic is not the time taken for a transistor to switch on or off, but rather the time taken thereafter for the switched current to charge or discharge the stray capacitance in the line connecting this transistor to the next. A good measure of the delay involved, i.e. the gate delay, is gained by multiplying the resistance of the drive transistor when switched on by the stray capacitance that it has to drive.

When a bipolar transistor, as used in a t.t.l. circuit, is switched on, its resistance is less than 10 ohms. The capacitance of the line, or wire, on the printed circuit board joining this output to the next logic element is of the order of 20 picofarads. Multiplying these two together gives us a time delay of 200 picoseconds. This shows us that, from this point of view at least, sub-nanosecond logic speeds are possible and we do not pay a speed penalty if our logic signals skip from chip to p.c.b. to chip to p.c.b. and so on.

In stark contrast, the smallest possible unipolar, or mos transistor, when switched on, still has a resistance of 10,000 ohms. If it drives 20 picofarads of capacitance on a printed circuit board, the delay, or signal rise time, resulting would be 20 pico multiplied by 10,000, that is, 200 nanoseconds. So if the physically smallest possible (i.e. square) cmos output transistor has to drive a signal off the chip onto the printed-circuit board, the achievable speed is only 200 nanoseconds, that is, one thousand times slower than bipolar t.t.l. This dire situation can be improved by making the drive transistor bigger and so reducing its resistance. Actually, we might put ten square transistors in parallel to reduce the resistance from 10,000 ohms to 1,000 ohms. However, the price we pay is that these drive transistors have to be made very big, consuming large areas on the surface of the silicon chip. This undermines the reason for using mos which is that an mos circuit takes up less area on the chip than does a bipolar. By the way, if we make the output transistor more beefy, we can make the mos output t.t.l. compatible, and this is usually done.

Let us now consider the situation when a cmos signal on an l.s.i. chip goes from one logic stage to the next without leaving the chip. In this case, the stray capacitance which must be driven is only one tenth of a picofarad, and if the drive transistor is the

smallest possible, i.e. 10,000 ohms resistance, the time constant, or delay, is only 1 nanosecond. From this we can deduce that it is not true that cmos is slow. Cmos signals across the chip have a high intrinsic speed, and so inter-chip circuitry should be serial, since this will reduce the amount of circuitry required for each function. (It is ridiculous for operations inside current microprocessor chips to be fully parallel. However, if someone made a serially operating microprocessor chip, probably nobody would buy it because, although its performance might be the same as its parallel competitors, the news would get out that the serial microprocessor contained very little hardware; there would be nothing for the salesmen to boast about.)

Note that if, by increasing the size of an output transistor by putting a number of square transistors in parallel, the output resistance of one bit of a 16-bit bus leaving the chip is brought down to 1000 ohms, so that the speed (rise time) is reduced to 20 nanoseconds, but sixteen such large transistors are needed to handle the sixteen-bit parallel word, using up valuable area on the integrated circuit surface. The same output data rate could be achieved by combining all 160 transistors in parallel to drive the sixteen bits serially down only one wire leaving the chip. In this case, assuming the same amount of chip area for the single drive transistor, a resistance of one sixteenth of 1,000 ohms could be achieved, leading to a bit rate of nearly 1,000 megabits down the single line. The point being made here is that *parallel working does not enhance speed if the circuits used are cmos*. On the other hand, a heavy price is paid when we go fully parallel – extra cost in wiring and extra pins in the i.c. package leading to extra failure (since the main cause of failure is the interconnections) and also far more failure due to pattern sensitivity with parallel data busses. Also, parallel working increases the physical size of the resulting system, because size is largely dictated by number of interconnecting wires. It also forces us to use extremely complex, expensive test and debugging equipment including logic analysers with their awkward, octopus-like probe pods. By comparison, it is trivially easy to attach a single oscilloscope probe to a point where serial data is passing.

### The Nub of computation

The heading of this section is purposely inappropriate, to illustrate the problem at the very start. The 'computer science' discipline has come to think that its objective is 'computation', 'information processing' or some such. This is not true, or alternatively, if it is true, then 'computer science' is getting in the way of a much more important discipline, which is the application of technology to society's needs.

In our society or culture, certain historical necessities arise. It is usually thought that whether or not a certain development was a historical necessity is proven after the event by whether such a thing in fact came to pass. I think this is wrong. For

instance, the wheel and axle was clearly a historical necessity in both Europe and the Americas, and the fact that the natives of the Americas never used the wheel and axle does not prove that it was not a historical necessity. More generally, we can see the extreme cases where a tribe or genus dies out because it evades a step which is a historical necessity.

Our society may well avoid historical necessity in the development of computer science, but that does not in my opinion negate the fact that what follows is a historical necessity.

The proper objective for computer science or digital electronics is to apply technology to meeting human or sociological needs. (This is a quote from my 1969 *New Scientist* article<sup>1</sup>) I would probably limit the broad range of application to physical, not intellectual, needs.

Any physical situation which our technology can usefully be applied to will be a multi-dimensional array of values which need (a) analysis and (b) manipulation. Digital electronics won over analogue twenty years ago, I believe for ever, and so our machinery needs to contain a *digital analogue of reality*, and in fact always does so. One measure of the elegance of our machinery, and probably of its efficiency and simplicity is the ease with which the analogue in our machine maps onto the reality of which it is an analogue. The design of an elegant (and also one suspects efficient) machine requires of the designer knowledge of the physical reality which is the target of our machine; of the nature of data manipulation and computation; and of the physical nature of the machine.

Since the ideal seems to be a machine which can be regarded as a *physical analogue of reality*, and the closeness with which the machine's structure and information mimics the physical reality, the 'computer scientist' must have competence in all fields above.

The problem is that today, programmers, calling themselves computer scientists but having no competence in anything except the second (with perhaps a little competence in the first), think they can usefully contribute to the design and development of our future machines.

A second measure of the elegance of our machinery is the degree to which changes in the physical reality we are mimicking (or recording) in our machine can be easily effected in our machine. This is why a machine is very bad if it does not have content-addressable memory, and in fact it needs more than that. It needs processing capability *in situ* in the memory. This is because values or parameters in physical reality change *in situ*, influenced only by parameters which are physically nearby. This leads to the next requirement of a good machine, which is that since in physical reality there is not action at a distance but all interaction is local, our machine should have superior (or even only) interaction capability between values (vectors, scalars, etc.) which relate to physically close points in the physical reality. Further, it appears that the ability to effect interaction between values which relate to

*continued on page 72*

# Radio activated implant for bladder control

Neurological prosthesis aids patients with spinal cord injuries by stimulating motor nerves

One of the distressing results of injury to the spinal cord is the patient's inability to control the passing of urine in the normal way. As is well known, paraplegics suffer paralysis in varying degrees to the lower part of the body because of the failure of motor nerves, coming from the damaged spinal cord, to innervate the muscles connected to them. Action potentials in these nerves are absent or very weak. Urination is affected by a failure of innervation in two muscles. One is a smooth muscle which surrounds the bladder and applies pressure to empty it — a detrusor muscle. The other, around the neck of the bladder, is a sphincter muscle which opens and closes the outlet for urine.

If the spinal cord has not been severely damaged the patient may regain some measure of reflex control. But many paraplegics have large residual volumes of urine which can cause urinary infections and, in extreme cases, disease of the kidneys. One treatment for this condition is to disable the sphincter muscle by surgery, but this results in permanent incontinence and the need to wear a urine collecting device.

Over the last twenty years or so attempts have been made to give the paraplegic patient a means of voluntary control over bladder emptying by applying electrical stimulation to the appropriate motor

by Tom Ivall

nerves. These techniques have used implanted electronic devices with stimulating electrodes that are attached in some cases to the bladder wall, in others to a part of the spinal cord and in yet others to motor nerves emerging from the spinal cord.

One of the latest and most successful attempts at providing such voluntary control has been made by the Medical Research Council Neurological Prostheses Unit in South London. Based on research by the neurophysiologist Professor G. S. Brindley<sup>1</sup>, it has resulted in a practical, near-field radio activated stimulator which is now being manufactured on a small scale\* and implanted in a steadily increasing number of patients (26 at the time of writing). Earlier work by the MRC Neurological Prostheses Unit on electronic implants<sup>2,3</sup> has already been reported in *Wireless World*<sup>4,5</sup>.

Electrically, the principle of the bladder control prosthesis is fairly simple, as shown in Fig. 1. Stimulating pulses are applied bilaterally to nerves at three levels

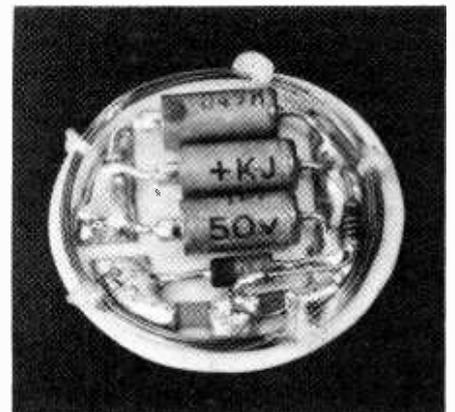
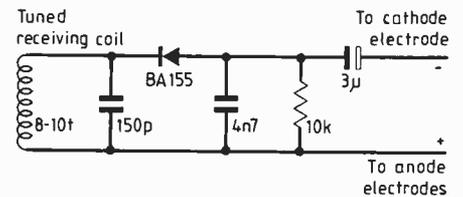


Fig. 2. Circuit (a) and construction (b) of one of the three receivers in the chest implant.

by electrodes fitted inside the outer covering (*dura mater*) of the spinal cord. These electrodes receive current pulses from three miniature radio receivers implanted as a single unit under the skin of the lower front chest wall. The receivers are simple passive circuits with a tuned coil, a semiconductor diode detector, and an RC time constant (Figs 2 and 3).

To apply stimulation the patient switches on a small hand-held unit and holds a three-coil oscillator block to the front of the chest immediately over the implanted receivers. The block generates pulse modulated r.f. power of constant amplitude, giving a combination of pulse frequency, pulse duration and pulse grouping previously determined by stimulation tests on the individual patient. The electromagnetic field passes through the patient's clothing and skin to the receivers, where the r.f. signals are demodulated to produce d.c. pulses. These pulses are carried by an implanted flexible cable to the

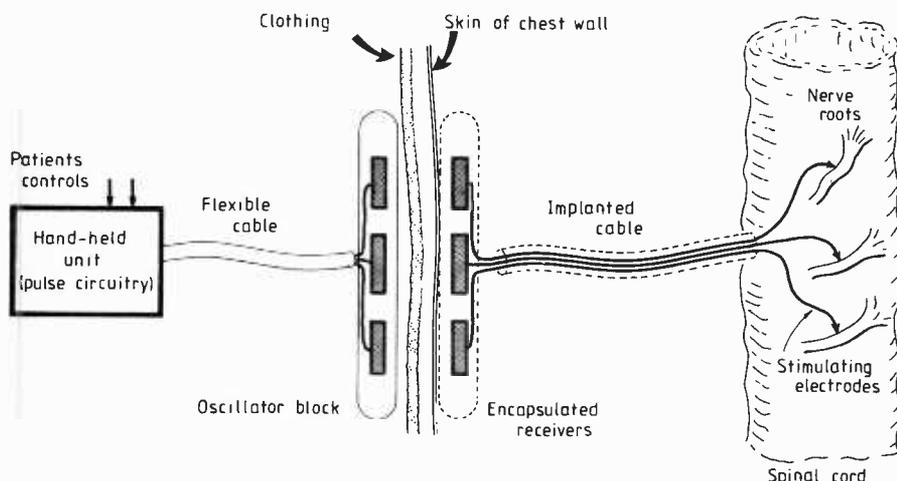


Fig. 1. Schematic showing principle of bladder control prosthesis. The implanted part of the stimulator comprises a receiver unit, a flexible cable and an assembly of stimulating electrodes.

\*By Finetech (Engineering) Ltd of Welwyn Garden City, Herts.


stimulating electrodes. All energy is supplied by the transmitter, so there is no need for implanted batteries.

The achievement in developing this electronic implant does not therefore lie in any great originality of the system as a system. On the physiological side the major problem is to find the right pattern of stimuli to innervate the detrusor and sphincter muscles successfully. This varies from patient to patient, depending on individual nerve anatomy and the nature of the spinal injury. On the electronic engineering side the real achievement lies in the techniques of constructing and packaging an implant that will work reliably over a period of years in the extremely difficult environment of the human body.


This environment is a warm, saline vapour produced by the body fluid. It's difficult to think of anything much worse for causing electrical leakage, corrosion and short circuits in the implanted receivers. And within the spinal cord the cable to the electrodes has to pass through a layer or sac of cerebrospinal (CS) fluid between the outer covering and the inner connective tissue of the cord. Fortunately, the MRC team, led by P. E. K. Donaldson, has had long experience, nearly twenty years, of coping with just these conditions.

### Nerve root stimulation

Spinal nerves emerge from openings between the vertebrae in the spinal column, roughly at the levels where the associated sensory or motor functions take place in the body — though some of the nerves, of course, then have to travel downwards from the spine. These spinal nerves are trunks containing both sensory and motor nerve fibres. For the bladder the nerves emerge through the sacral vertebrae, a group of five bones fused together in a mass immediately above the four lowest vertebrae (also joined together) forming

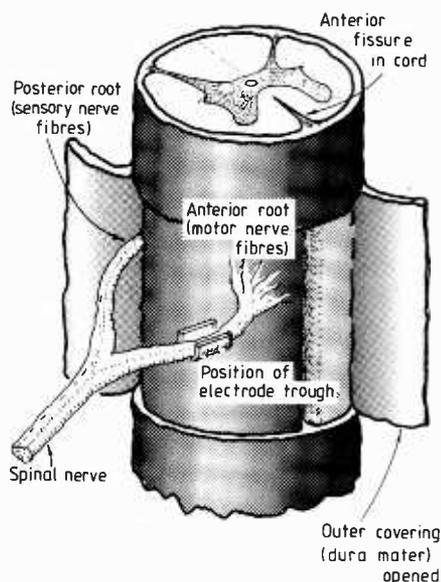

**Fig. 4.** Greatly simplified diagram of motor (anterior) and sensor (posterior) nerve roots coming from one half of the spinal cord at one level (assume a similar structure for the right-hand side of the fissure). Stimulating currents are applied by electrodes to motor nerve roots.

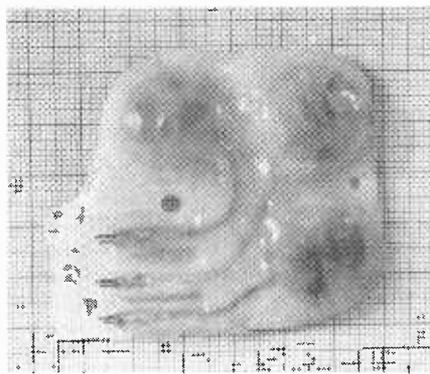

**Fig. 3.** (a) Complete three-receiver implant after encapsulation in silicone rubber. The three plugs mate with sockets on the implanted cable. (b) The corresponding oscillator block as used by the patient.



the coccyx.

Because the nerves contain both types of fibres, the motor fibres have to be distinguished from the others so that the stimulating electrodes may be attached to these alone. This can only be done at a point along the nerve where the trunk divides into separate sensory and motor nerve roots, which join the spinal cord at different places.

The highly simplified diagram in Fig. 4 shows this at one level and for one half of the cord. Motor nerve fibres arise from roots at the front of the spinal cord — the anterior or ventral roots — while the sensory nerve fibres come from roots at the back of the cord — the posterior or dorsal roots. So the stimulating electrodes must be attached to the anterior roots in the sacrum. These are in fact identified anatomically as the S2, S3 and S4 anterior roots.\*

In a surgical operation the dura mater is opened at a point just above and including the top part of the sacrum and the required anterior nerve roots are identified by their size and position. This identification is tested and confirmed by electrical stimulation during the operation. The S2 and S3 roots are large and so can be easily separated into motor and sensory groups of fibres, but the S4 roots are too small to be separated.

Stimulating electrodes for these nerve roots are mounted in small silicone rubber 'troughs', into which the nerve is laid as shown in Fig. 5. Each trough contains three U-shaped platinum foil electrodes and the nerve lies loosely inside them, immersed in the CS fluid. A silicone rubber lid is latched on to the trough to ensure that the nerve is retained. The reason for the use of three electrodes for each motor nerve is to prevent stimulation via the CS fluid of nearby sensory nerves, which might cause the patient to feel pain or other disturbing sensations. The middle electrode is a cathode, while the other two, which are connected together, form an anode. The cathode is connected via the cable to the negative terminal of the receiver's d.c. output and the anode to the positive terminal. As a result of this tripolar structure most of the electric field energy due to the cathode-anode stimulat-

\* Here 'S' stands for *sacrum*, while the numbers identify the particular nerves. Numbering runs from 1 to 5 moving down the spine.

ing potential is confined to the spaces between the electrodes, predominantly along the motor nerve. Consequently the stimulating current does not spread outside the trough and affect other nerves.

Because the nerve roots to be stimulated are close together the electrodes can be assembled into a unit, as shown in Fig. 6(a). The number of troughs used in the assembly and the disposition of the nerve roots in them depends on the stimulation requirements for a given patient. Details are given in Reference 1. In the Fig. 6(a) assembly there are in fact four sets of cathode-anode electrodes, with one trough extended beyond the others in a stack so that nerve roots at different levels can be stimulated. Fig. 6(b) shows how the S2, S3 and S4 nerve roots, from both halves of the spinal cord, are located in the four troughs.

Once the nerve roots are held in their troughs the dura mater is closed over the assembly. The cable passes through an aperture in the dura mater via flexible grommet or sealing flange which serve to prevent escape of CS fluid from the spinal cord. Of course, the covered electrode assembly makes a bump on the side of the spinal cord and a piece of bone has to be removed from inside the spinal column to make room for it.

### Receiver implant and encapsulation

As can be seen from Fig. 3, the three receivers are assembled and encapsulated to form a single implant with miniature plugs for connection to cable sockets. Each receiver is constructed on a platinum-gold thick film circuit with a circular (18mm dia.) alumina substrate. An 8-turn receiving coil runs round its periphery. The BA155 diode is encased in glass and has Kovar leads, while the tuning and reservoir capacitors are leadless chip types. The 3 $\mu$ F electrolytic in the circuit is formed by three 1 $\mu$ F capacitors in parallel — tantalum electrolytics hermetically sealed in glass.

The purpose of this 3 $\mu$ F electrolytic is to prevent a net charge from being accumulated, pulse by pulse, in the capacitance of the stimulating electrodes, as this would eventually lead to gas evolution through electrolysis. The purpose of the 10k $\Omega$  resistor is to complete a circuit, electrodes-capacitor-resistor, to provide a discharge

path, in the intervals between pulses, for the small charges resulting from these pulses.


Encapsulation follows a general principle evolved by the MRC Unit over a good many years<sup>2,3,5</sup>. Namely, to prevent water from collecting in places where unwanted conduction or electrolysis could occur it is more effective to displace the water by eliminating voids than to try to set up a barrier against it. This means that all voids between parts must be completely filled, and this in turn means the use of an encapsulant with excellent adhesion to several types of surface.

In the subcutaneous receiver implant the environment is an ionised water vapour. Experience has shown that hybrid microelectronic components will operate successfully in the presence of such vapour — as long as it remains a vapour. An encapsulant will be effective if it prevents the vapour from condensing, molecule by molecule, into a liquid. Hence the need to fill the tiniest voids where the vapour molecules would have space to coalesce.

Epoxy resin encapsulant was found inadequate to meet this condition but the MRC Unit has had considerable success with silicone rubber adhesive. This substance has the apparent disadvantages of high permeability and rapid transmission of water vapour, but against these can be set the considerable advantages, for the present task, of low water absorption, high thermodynamic stability and extremely good adhesion to surfaces.

To ensure effective filling of all spaces between parts the silicone rubber adhesive is painted on, layer by layer, using a fine syringe. This means that the thick film circuit must be constructed so that the syringe needle can be inserted into all spaces. Thin spaces between parts must be designed out. As an example, the leadless chip capacitors are raised on plinths of solder at both ends so that they do not lie practically flat against the ceramic substrate, as in conventional construction.

Another critical factor in construction is the actual shape of the cavities left between the mounted components. In the curing of the rubber adhesive a slight shrinking

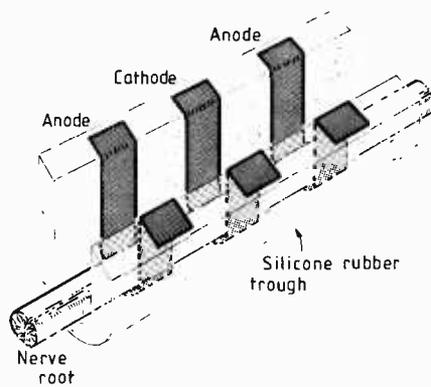

**Fig. 5.** Construction of electrodes for one nerve root. The middle platinum foil electrode is a cathode while the outer ones (connected together) form an anode.

occurs. Adhesion to two large-area opposite surfaces might continue to be perfect after curing, but the shrinking and consequent deformation might cause the cured rubber to be pulled away from other, differently shaped surfaces. The MRC Unit has made extensive studies of the adhesion behaviour of the rubber when filling various cavities and has found that a useful parameter for evaluating this behaviour is the ratio of the square root of the diameter to the length (e.g. of a 'tunnel' beneath a raised chip capacitor). From these studies it has been possible to design the receiver structure to give cavity shapes that help adhesion.

Before the receivers are encapsulated they are rigorously cleaned to remove any contaminants resulting from construction, handling or atmospheric impurities, as these could dissolve in any condensed vapour from body fluid. The units are first washed in chloroform to remove flux and human hand grease, then in an alkali rinse,

**Fig. 6(a).** Electrode assembly as implanted under the outer covering of the spinal cord. One set of electrodes is extended beyond the others because the nerve roots are at different levels. (b) Showing diagrammatically how the S2, S3 and S4 nerve roots, from both halves of the spinal cord, pass through the electrode troughs (here sketched as cylinders).

then in water which is continuously circulated through a deionizing column. The MRC Unit has built its own washing machine for this purpose. It comprises a bath, water pump and ion exchange column, with continuous electrical monitoring and recording of the water's resistivity as a measure of its purity. Whereas the theoretical ultimate resistivity of completely pure water is  $22\text{M}\Omega\text{-cm}$ , this washing machine runs until the circulating water has a resistivity of  $10\text{M}\Omega\text{-cm}$  after washing the receivers for about  $\frac{3}{4}$  hour. Finally the receivers are dried in a drying cabinet and are then ready for encapsulation.



The final silicone rubber coating applied to the whole receiver implant contains an antibiotic powder with a shelf life of 9 months.

### Connecting cable

The implanted cable connecting the receiver unit to the stimulating electrodes has been specially designed and made by the MRC Unit to meet some very stringent requirements. Chemically it must be indifferent to body fluid and non-toxic to the patient. Mechanically it must cope with potentially destructive local stresses resulting from deformations — stretching, bending, twisting and crushing — when the patient moves. For the sake of the patient it must have a long life and be sufficiently compliant to adapt to various postures. Electrically it must carry multiple conductors with a resistance low compared with the impedance of the electrode-tissue system. Medically it must withstand autoclaving before the operation.

A structure which fulfils these requirements, and has performed faultlessly in patients for periods of years, is shown in Fig. 7. Developed by J. D. Cooper, now retired from the MRC Unit, it consists of helices of platinum-iridium wires insulated with polyimide varnish and embedded in silicone rubber. The conductors are  $75\mu\text{m}$  in diameter and have a resistance of  $2.2\Omega$  per cm, while the overall diameter of the cable is 2mm.

Full details of the cable, the method of

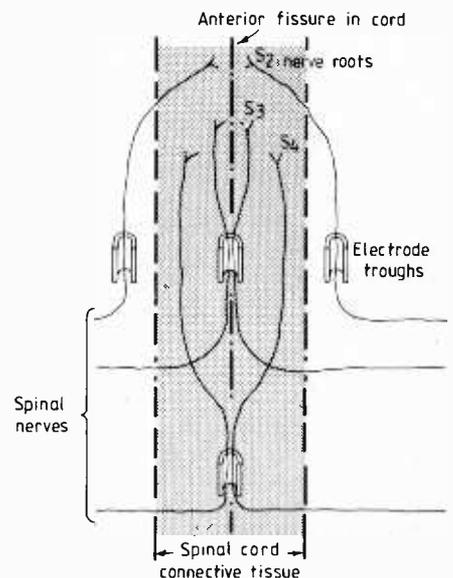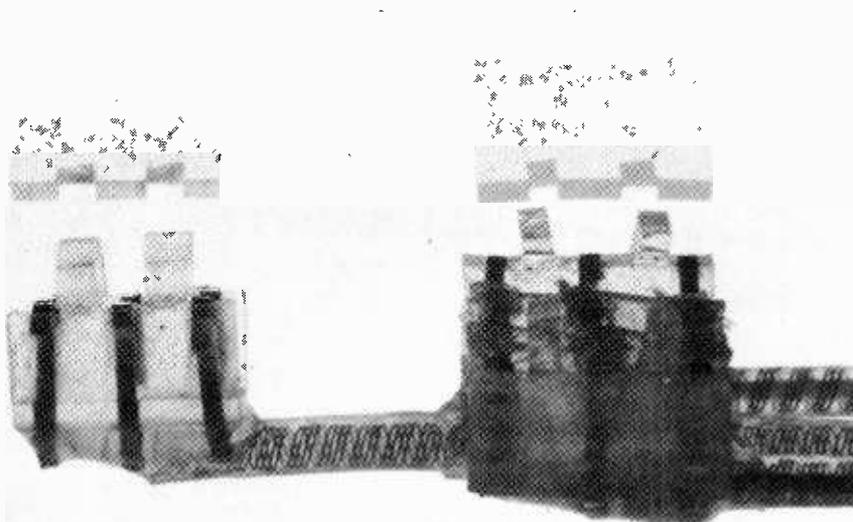

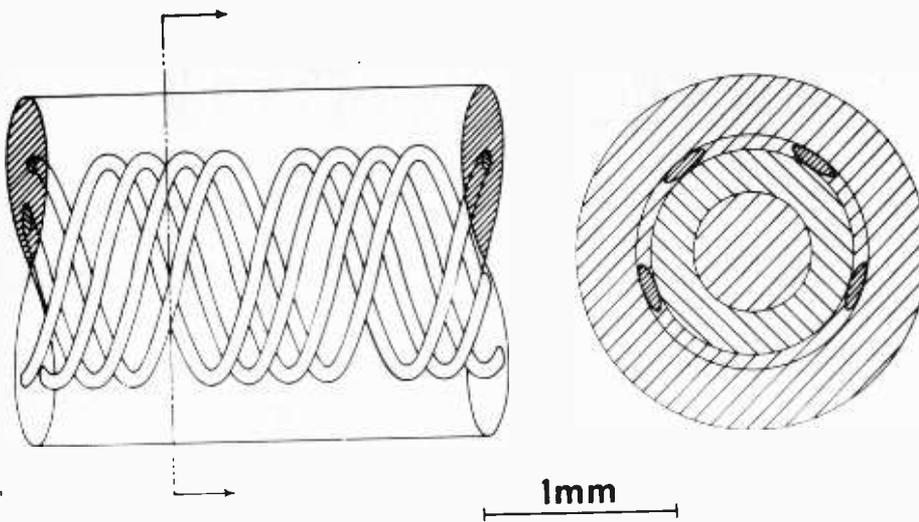


Fig. 7. Construction of connecting cable. The insulated helical conductors are wound on a silicone rubber tube and covered with an outer layer of silicone rubber adhesive.

construction and life testing results can be obtained from Reference 6. Briefly, the helical conductors are not damaged by body movements that stretch, bend or twist the cable, but implantation sites that might result in crushing (e.g. between bone and the skin) are better avoided.

A miniature plug and socket is used at the receiver end of the cable to allow the surgical operation to be done in two stages: first, implantation of the electrodes and cable; then, after about a week, implantation of the receiver.


### Transmitter pulse generation

The patient's hand-held transmitter, shown in Fig. 8, is a case containing batteries and pulse circuitry, with an output cable connected to an encapsulated oscillator block of three Hartley r.f. oscillators. The pulse circuitry modulates the oscillators to produce constant amplitude pulses of r.f. at 6 or 8 MHz which are transmitted to the three implanted receiver coils. The modulating, and hence stimulating, pulses

have durations of  $100\mu\text{s}$  to  $3\text{ms}$  and are generated in bursts (for a reason to be explained) with p.r.f.s within these bursts of 30 pulses/s to 300 pulses/s.

For each patient the optimum pulse frequency and strength of stimulation are determined by tests carried out immediately after the implantation surgery<sup>1</sup>. The basic requirement, of course, is to stimulate the motor nerve roots in such a way that the detrusor muscle will apply pressure to the bladder and allow the urine to flow out through the urethra. As in all nerve transmission, the strength of a sensory input or muscle response is shown by the frequency of the action potential pulses travelling along a fibre. (Pulse amplitude is more or less constant as the action potential obtains its electro-chemical energy locally as it travels.) With the bladder, the detrusor muscle applies maximum pressure at stimulation pulse frequencies

Fig. 8. The transmitter as used by the patient.

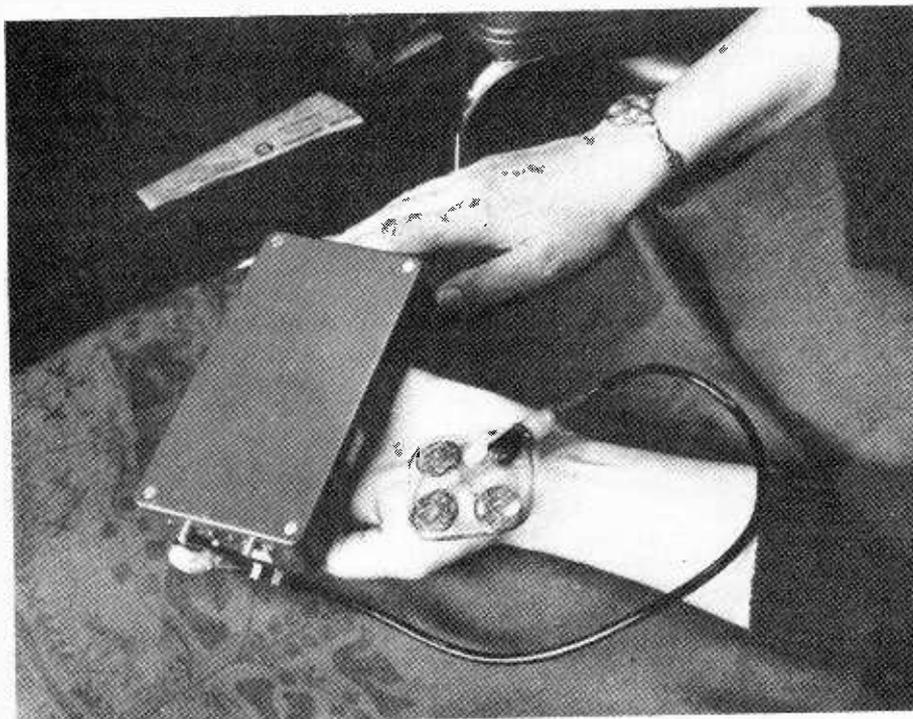

between 8 pulses/s and 30 pulses/s, depending on the patient.

A characteristic difficulty of the nerve root stimulation in this prosthesis, however, is that the detrusor and sphincter muscles are innervated through the same roots. Consequently root stimulation causes the sphincter muscle to close the neck of the bladder at the same time as the detrusor applies pressure to the bladder to empty it. There are several ways of overcoming this difficulty, but one that has proved successful with a large group of patients is to stimulate strongly with bursts of pulses.

The pulse bursts are typically 1.5s in duration and generated at a frequency of about 14 bursts/minute. They are sufficiently frequent to ensure that the detrusor remains contracted to apply a continuous pressure to the bladder, but the sphincter has a faster response and allows urine to pass in the intervals of about 3s between pulse bursts.

To provide these stimulation requirements the transmitter includes an adjustable pulse generator set at the required p.r.f. for the patient, with its output gated by a burst oscillator that can be adjusted in burst frequency and burst duration. All these functions are provided by cmos integrated circuits and the stimulation parameters are selected by a d.i.l. switch on the circuit board.

Low-level pulses from this circuitry are amplified to about 50V to modulate the r.f. oscillators. The three Hartley oscillators are turned on in sequence by the modulating pulses, through gates operated by a scale-of-three counter. The purpose of this is to smooth the current demand on the batteries. R.f. output power from each oscillator coil is sufficient, at a range of 1 cm, to provide 25V into a  $470\Omega$  load at the electrodes.

As well as allowing the patient to control urination at will, the prosthesis can also be used to ensure continence at night during sleep. For this purpose the transmitter coil unit is secured on the lower chest above the receiver implant and the transmitter is set to give a weak continuous stimulation which keeps the sphincter muscle contracted and the neck of the bladder closed.

### References

1. Brindley, G.S., Polkey, C.E., and Rushton, D.N. "Sacral anterior root stimulators for bladder control in paraplegia", *Paraplegia* vol. 20 (1982), No. 6, pp. 365-381.
2. Donaldson, P.E.K., and Davies, J.G. "Microelectronic devices for surgical implantation", *The Radio and Electronic Engineer*, vol. 43, No. 1/2, Jan/Feb 1973, pp. 125-132.
3. Donaldson, P.E.K. "Experimental visual prostheses", *Proc. IEEE*, vol. 120, Feb 1973, pp. 281-298.
4. "Artificial vision", *Wireless World*, vol. 77, May 1971, pp. 214-217.
5. Ivall, T.E. "Artificial vision progresses", *Wireless World*, vol. 81, April 1975, pp. 156-158.
6. Donaldson, P.E.K. Technical note: "The Cooper cable: an implantable multiconductor cable for neurological prostheses", *Medical & Biological Engineering & Computing*, vol. 21, May 1983, pp. 371-374.

# Behind the micro

*Inventive first-time buyers want to know about the inside of microcomputers but manufacturers usually give little away. This article – supplementing last month's microcomputer guide – will help you find and interpret the information that is available.*

There are three main sections to this article. The first includes tips for first-time microcomputer buyers with emphasis on interfacing. Frequently used standard interfaces are briefly discussed. Secondly, a handful of computer boards is described to give you some idea of what they have to offer in comparison to the 'complete' microcomputers detailed last month. Sources of information for all computers and boards mentioned in this feature form the final section.


If you intend adding hardware to your computer, information and circuit diagrams are of primary importance. It pays to check on how many books describing a computer are available before buying; the least one needs is full details of interface ports and their signal-timing and a description of how the computer is organized internally.

Choosing a computer with an industry-standard interface port is a good idea but such computers are usually expensive, as are the interface boards that connect to them. A port which brings all the processor signals to the outside world and allows address, data and control buses to be isolated from the microprocessor is the most useful feature for the experimenter, but few manufacturers provide one. With this type of port one need not rely on receiving full information from the microcomputer manufacturer, since data sheets from the processor manufacturer provide the finer details. But a sensible bidirectional parallel interface with a full specification suffices for all but the more exotic applications. In fact, most peripheral circuits may be controlled through the slower RS232 serial interface found on many computers, given the right software.

There are a few good microcomputers around for which there isn't a great deal of information. If you choose one of these, make sure that it uses one of the more popular microprocessors. As a designer of interfaces you will soon tire of writing programs in Basic and turn to machine code. There are many books describing machine-code programming for the popular processors which include the Z80, 6502, 6800 and 6809. Few of us can resist making modifications within the computer so a unit with a large physical size can be advantageous – provided it is well designed.
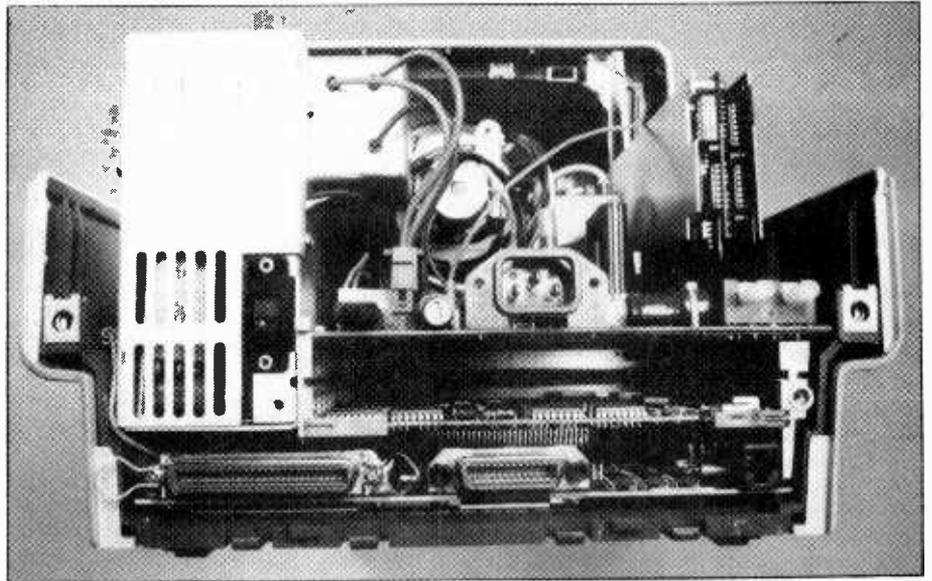
## Computers for the work-bench

In industry, time and money is often saved if an engineer or technician can use an interface-circuit board designed by some-



*A 68000-based computer with half a megabyte of ram surrounds the c.r.t. in Hewlett Packard's Series 200 Model 16. Basic for this engineering system takes up 277K of memory, but is fast as some compilation takes place when the program is entered.*

one else, and where time is money, the costs of developing software must also be given consideration. Here the choice of a microcomputer is determined not so much by its price but by how many interface and expansion boards are available for it and by which operating systems the computer is compatible with. Popular interfaces will be described later. As far as software is concerned, one of the more popular disc-operating systems\* such as CP/M and MS-DOS opens the door to a wealth of programs for design and development, but if one is considering designing microprocessor-based circuits on a regular basis a dedicated microprocessor-development system is the best choice.

Where applications software is more important than computer hardware it pays to look at operating systems rather than computers in the first instance. A list of applications software for the popular operating systems should not be difficult to get hold of. Once you have found the operating system with the most software to suit your needs, study it carefully and compare it against its competitors. Some operating systems are more efficient than others and choosing an efficient one is important, especially if you intend designing your own software. There are computers around that

can run more than one operating system, as our list indicates.

Modifying a computer to run a disc-operating system is not always easy. For instance with CP/M – an operating system designed for Z80-based computers – hardware modifications will have to be made on computers not designed to run it and part of the CP/M software has to be modified.

For designers involved with developing software for new interfaces, programs which allow machine-code to be assembled (assemblers) and programs which make machine-code programs from high-level languages such as Basic (compilers) are important. Compiled machine-code programs are often not as efficient as they would be if originally written in machine code or assembly language. Languages such as Forth, which compile the program before it is run, are more suitable for real-time applications than languages such as Basic but they can be more difficult to learn.

Few programs run first time and debugging aids are essential for all but the smallest software projects. Most assemblers will indicate more obvious errors before or while they are assembling.

## Eight or 16 bits?

Eight bit data-word processors used in today's microcomputers have 16 address lines allowing them to directly address up

\*C. Gooding. Which os to back?. *Software*. June 1983 (origins and aspects of 15 operating systems, particularly useful to the newcomer).

to 64K-bytes ( $2^{16}$  eight-bit data words) of read-only and read/write memory (read/write memory is called random-access memory, or ram, but if you try to access it in a random fashion you get good results once in a blue moon). Generally, for computers designed for use without disc drives, between  $\frac{1}{4}$  and  $\frac{1}{2}$  of the 64K-byte memory space is taken up by read-only memory (rom), holding the computer's language, which is usually Basic, and software under the vague heading of operating system. Most manufacturers don't differentiate between the operating system and the computer's language unless the operating system does something more than allow one to type in and run a program then jump out of the program again when something goes wrong. If a computer is said to have a large operating system alongside its language it is worthwhile looking into what the operating system does. If the computer language takes up an abnormally large amount of rom it also pays to ask why; it could indicate a versatile operating system, a powerful computer language or just long-winded software writing on the manufacturer's part.

Memory space can be extended above this amount in various ways. Some computers use paged memory in which two or more pages of say 32K-byte memory are switched between by software, and some use virtual memory in which pages of information are transferred between primary (usually semiconductor) and secondary memory (usually disc) by software, preferably without the user realizing it. All methods of extending memory are applied at the expense of something else such as processing speed, but many are very efficient.

Sixteen-bit processors on the other hand are not a problem as far as memory-addressing space is concerned — for the moment at least. Because 16 address lines and 16 data lines use up a lot of pins on the integrated circuit, the two buses are usually multiplexed into one, which might affect the complexity of a computer's interface port. Most 'second-generation' 16-bit devices have more than 16 address lines as shown below (note, there is no such thing as a Z8000 but there are two Z8000 family c.p.us called Z8001 and Z8002).

Processor	Address lines	Directly-addressable memory
68000	24	16M-byte
Z8001	23	8M-byte
Z8002	16	64K-byte
8086	20	1M-byte
LSI11/23	18	256K-byte
NS16000	24	16M-byte

Z8001/2 and 8086 c.p.us have a feature similar to Z80 and 8080 microprocessor which allows them to address 65,536 eight-bit i/o ports in addition to memory addressing.

For most interfacing, experimentation and hardware/software-design applications the increased processing speed offered by 16-bit processors will be far more important than the enhanced direct memory-

addressing capability. But unless you need the large memory capacity offered by a 16-bit microcomputer, make sure that you can use the extra processing power and speed. Eight-bit processors are not yet pushed to their limits and there are still many reasons why an eight-bit computer might be the best choice. The computer itself will be much cheaper and so will its interface/expansion boards and peripherals i.cs. And there are large amounts of cheap, efficient and proven software for most popular eight-bit microcomputers. Writing machine-code programs for a 16-bit processor is also more difficult than an eight-bit device.

Clock speed is not always a good yardstick for processing speed when comparing microprocessors from different families. If you intend buying the microcomputer with the best microprocessor, look at the processor's instructions and how it operates rather than at the total number of instructions available, clock speed and the number of bits in the data word.

### Peripheral i.cs

These devices, which include real-time clocks, parallel/serial converters and i/o controllers, lessen the burden on the processor leaving it free to concentrate on user programs. All functions carried out by peripheral i.cs can be carried out by the processor and software at the expense of memory space and processing time, so it pays to find out how many of these devices are, or can be fitted. Some computers have sockets for peripheral i.cs so that they may be added as desired. Data books from the microprocessor manufacturer will show which peripheral i.cs are available and what functions they carry out.

### Cheap or expensive

It is not always apparent from technical specifications why some computers are cheap and others are expensive. If you find a computer attractive but you think that it is overpriced, ask why the price is so high until you are satisfied. On the other hand, if a computer is abnormally cheap, finding out why is not so easy. There are many ways of making a computer cheap. It may be manufactured in a land where labour is inexpensive. This is sensible and need not detract from the quality of the product, but the buyer should make sure that servicing arrangements are provided. Combining the functions of very many i.cs in a single i.c. called a logic array is another way of cutting costs without cutting quality. Experimenters will normally prefer having the separate i.c.s though, since they are more accessible.

Other methods of cutting costs may detract from quality. Processing power (i.e. electronic components) involves a small proportion of the computer's cost. Keyboards, connectors and printed-circuit boards are normally expensive and it is here where manufacturers often try to save money. For instance, keyboards may have keytops with printed legends as opposed to more expensive 'stick-of-rock' moulded legends and in time the printed types may

wear off or be washed away by the wrong cleaning fluid. Many computers use the edge of the p.c.b. as a male connector for interface ports and this is fine provided that the copper on this sector of the p.c.b. is plated with a precious metal. If the computer works when you buy it, not much can go wrong with the p.c.b. but if you are thinking of making modifications inside the computer you may find that the copper tracks peel away from the board when you start soldering. Cheaper computers use few if any i.c. sockets which can also be a bind for the experimenter. There is no practical way of finding out the quality of the p.c.b. before buying but you can inspect the interface connectors and keyboard. Spend wisely, but remember that a computer that doesn't go wrong is worth much more than a guarantee in the long run.

### User groups

Finally, find out if there is an independent computer users group for the computer you intend to buy. A good user group can be invaluable and will continue to provide you with information long after the manufacturer has lost interest in you.

### Common interfaces and buses

Manufacturers, having designed a product, naturally want to keep buyers attached to them and in the computer field they often attempt to do so by introducing their own expansion bus. For companies like Hewlett-Packard, developer of the IEEE-488 bus, this has worked on a grand scale — the company not only designs computers for controlling the IEEE-488 instrument interface but also produces the measuring instruments controlled by it. But many other buses introduced by computer manufacturers, despite their quality, have not been so widely accepted.

Buying one's first computer is probably the biggest step and in the enthusiasm one will naturally choose the computer with the most impressive technical specification. If time stood still this would be the best buy, but as time goes on, one wants one's computer to do more. Manufacturers disappear and change direction but if you have a computer with a widely used interface it can be updated despite the whims of its manufacturer or the shareholders.

One of the commonest interfaces mentioned in computer specifications is the RS232 serial interface. It is neither fast nor particularly efficient in microprocessor terms but it is widely adopted and one can find many peripherals that suit it. Many microcomputers intended for serious use also have parallel buses but many of these conform to no standard other than the manufacturer's own. Below we describe some of the interfaces most commonly found.

### RS232/RS422/RS423/RS449/EIA

RS232C, defined by the Electronic Industries Association (American EIA) is the

most commonly used serial interface standard and is almost identical to the CCITT V.24 interface standard. It will eventually be replaced by a group of three standards – RS449, RS422 and RS423. RS449 defines functional and mechanical characteristics of RS422 and RS423 which are electrical standards for balanced and unbalanced serial interfaces respectively. These new standards allow longer cables and higher data rates.

Only electrical/mechanical characteristics of the interface, functional descriptions of interchange circuits and standard configurations including synchronous and asynchronous communications are defined in RS232C (RS is recommended standard and suffix C indicates revision number). Signal coding is not defined. The standard defines a 25-pin connector but not a type, although a D connector is widely used, and the number of lines used for an 'RS232 interface' varies from computer to computer. Cable lengths of up to 15 metres may be used. In an RS232C signal, logic one is anywhere between -3 to -25V and logic zero is between +3 and +25V; cable loading is also specified as is a maximum data rate of up to 20kbit/s.

For the simplest bidirectional serial interface, only three connections are required; transmit data, receive data and ground. Hand-shaking is possible using a further two signals called clear to send and ready to send (CTS and RTS). Other signals on the 25-pin connector are for modem and terminal control. Many printers may be driven using an RS232 serial interface which means that they may be positioned a long way away from the computer, but circuits required to change from parallel-to-serial and back again add to the price.

Data sent through the RS232 interface may be in any code but ASCII is widely used for communications. A flexible serial interface will have the following options:

- 5- to 8-bit data word length
- parity-bit enable/disable
- even or odd parity
- one or two stop bits

which are selected ideally by software but possibly by switches where a hardware serial interface is used. Data rates, normally expressed in baud, should be alterable either by software or by switches. Most modems operate at 300 baud or 75/1200 for Viewdata systems such as Prestel. Binary or b.c.d. words might be used in data-acquisition applications.

Adding a rudimentary serial interface to a computer is simple. If a parallel port is available, one may convert parallel words to serial and vice-versa in software and convey the serial words through one bit of the data bus to and from the outside world using suitable buffers. But this means quite a lot of work for the processor. Addition of a universal-asynchronous receiver/transmitter (uart) takes the job of timing and parallel/serial conversion away from the processor and allows selection of bits/word, parity checking, etc. Software for controlling such an interface may be simple; it becomes a little more difficult if you want programs interrupted on receipt

of data. Efficient software for fully controlling a telephone modem can be difficult to write.

### Communications interface

This term applies to an RS232 interface with a full set of modem and terminal control signals, as opposed to a communication interface which is a high-speed port allowing a computer to communicate with, say, a mainframe. Some computers have an inbuilt modem which is also a communications interface.

### IEEE-488/GPIB/HPIB

This parallel bus is mainly used for controlling electronic measuring instruments and sometimes printers and other peripherals. Hewlett-Packard developed the bus and hence call it the HPIB. Others call it the general-purpose interface bus, GPIB, or the IEEE-488 interface after the standard which defines it. To add to the confusion, Ellefsen tells us in his article describing IEEE-488 in the June/July 1980 issue of *WW* that two other names are also used – IEC bus and ASCII bus. As with RS232, data coding and interpretation are not defined in the IEEE-488 standard; however, cable and connectors are.

Twenty-four lines are used, eight for grounding and shielding and 16 carrying t.t.l.-level signals. Each line is up to 15 devices connected to the bus recognizes its own address (or addresses). Seven of eight bidirectional data lines usually carry data in the form of ASCII words and the eighth may be used as a parity bit (binary or other codes may be used). All variable information, including addresses and control signals, is carried on the asynchronous data bus. Five of these lines carry addresses. In addition to the data bus there are three hand-shaking lines and five interface-management lines.

Statuses of connected devices vary; they may be 'talkers,' 'listeners' or controllers, or any combination of these three. A computer would normally be classed as a controller, talker and listener whereas a signal generator would paradoxically be a listener and a meter a talker since it would normally only talk to controlling devices. Cable length is up to twice the number of devices connected in metres or 20m, whichever is less, and the maximum data transfer rate is 1M-byte/s, although this speed is rarely approached in practice. Adding an IEEE bus to a computer is not easy. Special-purpose i.c.s such as the TMS 9914 are available for IEEE-488 control.

### S100 bus

This is a large bus – the 100 of S100 represents the number of lines used – and having been designed for an 8080-based system it has been around for some time. It has recently been revised for use with 16-bit processors and defined as IEEE-696. Until now, no recognized standard existed for S100 with the result that slight variations have appeared, especially from manufacturers producing boards and systems based on processors other than the

8080. Widely used in industry, this bus is well established and there are many S100 boards available with functions ranging from memory expansion to speech recognition.

The original S100 bus has separate eight-bit data input and output lines, which means that eight-bit processors have to have their bidirectional data-bus divided into input and output to make them S100 compatible. In the IEEE standard, these assignments are retained for eight-bit processors but when 16-bit devices are used, these 16 lines become bidirectional. Eight address lines have been added, bringing the total to 24 which represents an addressing capability of 16M-bytes. Although certain control lines have been added and others removed, the control bus is still well suited to 8080/A80-based systems. Sixteen-bit processors such as the Z8000 have multiplexed address/data lines which have to be separated externally. After separation, these buses connect directly to the S100 system.

The IEEE standard specifies a maximum data rate of 6MHz, bus length of 635mm and a maximum of 22 boards connected to the bus. Three spare lines are left for user options and four for future use. Some processors lend themselves to S100 busing. If you are thinking of adding an S100 bus to your computer after buying, it pays to look carefully at how the control signals of the computer processor compare with those required for S100.

### Floppy-disc interface

There are interface standards for both 8 and 5¼in floppy disc-drives. As few computer manufacturers also make disc drives, their disc interfaces invariably conform to these standards to allow their product to accept any make of drive. The computer operating system usually determines whether 8 or 5in drives or both may be connected. There is no such standard in the '3in' microdrive world yet – even the sizes of the discs vary – and there is little 'off the shelf' software on microdiscs. However, most microdrives can store as much if not more information than a 5¼in drive and they are faster and rapidly becoming cheaper.

### SASI/SCSI interface

Usually associated with hard-disc drives, the SCSI i/o bus started life as the Shugart Associates System Interface (SASI) but became the Shugart Corporation System Interface (SCSI) when the company responsible for it changed its name. Now the standard has been adopted by ANSI which has given it a new title – Small Computer Systems Interface. Perhaps by coincidence, the initials SCSI still stand. Flexibility is the main claim for the SCSI interface. Housekeeping, error correction/detection, formatting, etc., are carried out by the interface. To suit changes in storage media, designers and buyers only have to modify the interface; hardware and software in the computer remain the same. Connections between the interface and processor never change either. Because of this flexibility, SCSI is already widely used on microcomputers for hard-disc and

floppy, rigid and streaming tape interfacing. It will probably survive since it is equally suitable for use with optical-disc storage media. The port uses a 50-pin connector. Even-numbered pins 2-18 carry data and odd-parity signals and pins 32-50 carry control signals.

### Centronics

Specifically a parallel-printer interface designed by a printer manufacturer but widely adopted. Connectors vary, although a 36-way Delta socket is often found on the printer, but signals used are consistent. There are seven t.t.l. level data lines representing an ASCII word and data-strobe, acknowledge, busy, select, fault and demand signals for control and hand-shaking. Centronics supply a printer cable of just over three metres, which seems quite long for t.t.l.-level signals. Converters for changing RS232 serial data to Centronics parallel are freely available but often quite expensive. Although this interface was designed to drive a printer, the port is a convenient means of transmitting data to any device since driving software is invariably included in the computer.

### Processor bus

If you intend designing your own interfaces you should look for a computer that allows you easy access to all the pins on the processor. As an experimenter you will find that this feature becomes more and more important as time goes on. Inputs for isolating address, data and control buses from the processor should be available.

### D.m.a. channel

A direct memory-access channel allows peripheral devices to gain direct access to memory without involving the processor. In this way, data can be transferred between peripherals and memory at very high speeds. Coordination of the channel requires use of a high-speed device called a d.m.a. controller, although some modern processors have the facility built in. d.m.a. may sound simple but in practice it is not.

### Other buses

Buses described below are common, but are mainly encountered by designers and experimenters since they are used for connections inside a computer rather than outside. There is a manufacturer's 'in-house' bus standard for every microprocessor family and if you intend experimenting it might be worth finding out how the computer you intend buying is assembled internally. Circuit diagrams of the inside of a computer are notoriously difficult to get hold of, but without them modifications are tricky to say the least.

**Multibus** is an 86-line bus developed by Intel for its SBC range of boards but now used by a number of manufacturers, especially in the US. It is an extensive bus and can accommodate connection of multi-function boards.

**STD** is a bus developed by Pro-Log and Mostek for smaller single-function boards, allowing a system with a specific function to be developed, as opposed to Multibus

which allows a more general system to be assembled. Again, a number of manufacturers now produce boards using the STD bus.

### Further reading

E. G. Brooner and P. Wells, Computer communication techniques, Sams. (Discussions of computer networks from the smallest to Viewdata and Ethernet).

E. C. Poe and J. C. Goodwin, The S100 and other micro buses, Sams. (Descriptions and pinouts for S100, STD, IEEE-488, STD, Versabus and other buses peculiar to microcomputer popular in America such as TRS80, Apple I & II, Pet, TI99/4, Atari and LSI 11).

P. T. H Roberts, A microcomputer bus standard at last, *Wireless World*, December 1983 (\$100).

### Table guide

The table (see over) includes details of a selection of computer boards, which the reader may like to compare with the ready-packaged computers we described last month. These computer boards are usually supplied without keyboard, display or power supply.

As with the 'complete' computers, many manufacturers offer a series of models and in these cases we have selected basic versions to represent the range. We have indicated important upgrades and features of alternative models separately. Options mentioned (open circle or brackets) are only those available from the manufacturer of the computer.

**Processor.** This column lists the main processor or processors, and optional co-processors are indicated in parentheses.

**Languages.** These are a little more difficult to tabulate. In some cases, operating system and Basic (or other language) are combined and how much rom or ram each section takes is not always clear — or even important. What is important in most 8-bit microcomputers is the total amount of rom in the system because it often limits the amount of memory-address space left for user programs. Basic is the most popular language for the smaller microcomputers, hence the number of B's under the heading language, but there is one computer which uses the more efficient language Forth (F). Many computers designed for use with disc-operating systems only use rom during the initialisation so the rom size is not significant.

**Operating system.** More expensive computers use disc operating systems and provided that the operating system is a common one, very many languages will be available. Again, the amount of rom that any operating system uses reduces the amount of directly addressable program space.

**Storage.** Ram is often called main memory. Eight-bit processors can directly address 64K-bytes of memory so the maximum amount of directly addressable ram

is 64K less however much rom is used. Memory can be arranged in pages, but paged memory takes longer to access so processing is slowed down. Sixteen-bit processors have varying numbers of address lines but nearly always more than 16.

Under the heading Disc, a computer with an open-circle entry can use a disc interface supplied by the manufacturer but disc drives are not fitted as standard on the model concerned. Where a filled circle appears, the computer is fitted with one or more disc drives. The same applies to cassette recorder entries.

**Interfaces.** The most popular interfaces are included in the table shown which of the popular interfaces each computer offers; again a filled circle indicates that the feature is included as standard and an open one that an option is available from the manufacturer.

## Computer boards


For those who want a microcomputer tailored to suit an application or to build into their own equipment, we have included this section on computer boards. These boards are outside the scope of the survey, but this list of some of those available will give you an idea of how specifications, interfacing capabilities and prices compare with those of 'complete' computers. They do not usually have a power supply, keyboard or display facilities.

**Arcom ARC:** range of Eurocard single-board microcomputers includes ARC40, a small Basic computer for developing Z8 programs (includes eprom programming facility) for use with the Arc42 Z8 prototyping board. Arc8000 is a Z8001 VMEbus c.p.u. board with CP/M Z8000 cross-assembler option. Analogue and digital i/o, IEEE-488 and eprom-programmer/cassette-interface boards are available for use with both boards. The 4 or 8MHz Arc8000 has two RS232 interfaces. **WW 501**

**Control Universal Cube series:** main c.p.u. Eurocards are identical except for the processor, which may be either 6502 or 6809. Memory boards, i/o interfaces, floppy-disc controllers, eprom programmers and software supplement the range. These c.p.u. boards include two serial i/o channels, 20 digital i/o channels four 32K-byte memory sockets for rom, ram or eprom and a battery back-up circuit for non-volatile rams. The company also manufactures a range of boards allowing a modular BBC-computer compatible system to be built. Further boards include expansion for the BBC computer. **WW 502**

**Fulcrum Computer Products S100 boards:** this company distributes a large number of S100-compatible boards for processing, interfacing and data storage, such as an 8MHz 68000-based unit for which software includes CP/M-68K and Forth. Other S100-compatible c.p.u. boards use Z80, or 8085/6/7/8/9 processors. Among the many memory, i/o and disc-controller boards is a 512-by-640 pixel colour-graphics interface providing 16 out of 4096 colours, shaded black/white, light-

*Continued after addresses*

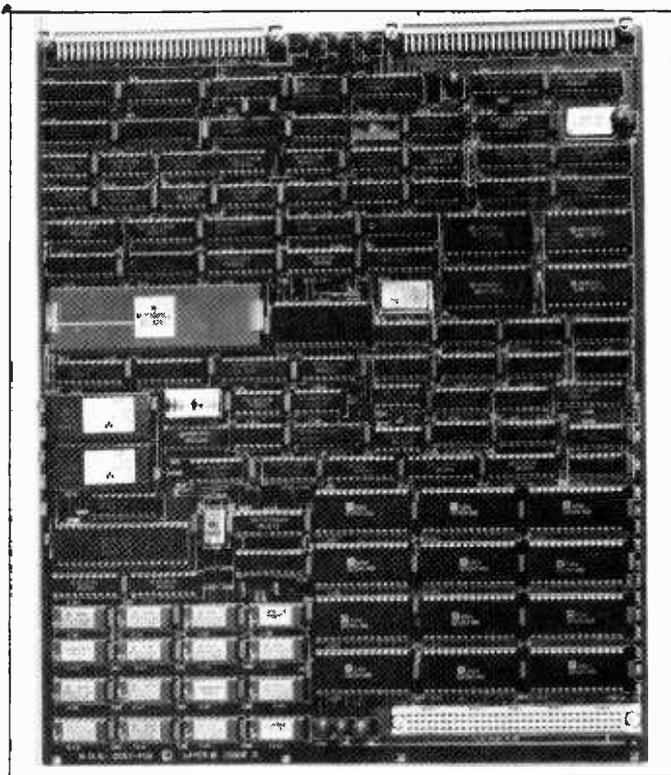

## Addresses

For more information on the computers described this month and last, contact the manufacturers and agents listed here.

**ABS Computers**  
North Street  
Portslade  
Brighton BN4 1ER  
Tel. 0273 413211

**Orb**

**Acorn Computers Ltd**  
Fulbourn Road  
Cherry Hinton  
Cambridge CB1 4JN  
Tel. 0223 245 200

**Electron, BBC computer**

**Act International Ltd**  
111 Hagley Road  
Birmingham B16 8LB  
Tel. 021 454 8585

**Apricot, Sirius**

**Action Instruments Europe Inc.**  
St James Works  
St Pancras  
Chichester  
West Sussex PO19 4NH  
Tel. 0243 774022

**PAC**

**Advance Computers**  
8a Hornsey Street  
London N7 8HR  
Tel. 01-609 0061

**Advance 86a, 86b**

**Alpha Microsystems (GB) Ltd**  
Berkshire House  
56 Herschel House  
Slough  
Berkshire  
Tel. 0753 2821922

**AM1000 series**

**Apple Computers**  
Eastman Way  
Hemel Hempstead  
Hertfordshire  
Tel. 0442 48151  
IIE, III, Lisa

**Aston Technology Ltd**  
Aston Science Park  
Love Lane  
Birmingham B7 4BJ  
Tel. 021 359 4861

**Crystal 68000 systems**

**Atari International**  
Railway Terrace  
Slough  
Berkshire  
Tel. 0753 33344

**Atari 400, 600, 800**

**Bleasdale Computer Systems**  
Francis House  
Francis Street  
London SW1P 1DE  
Tel. 01-828 6661  
BDC 680A

**BMC International**  
Encotel Systems Ltd  
7 Imperial Way  
Croydon Airport Indust Est  
Croydon  
Surrey CR0 4RR  
Tel. 01-686 9687 & 01-680 6040  
(six lines)

**BMC if800**  
Televideo TS1603H/TS1603

**British Micro**  
Penfold Works  
Imperial Way  
Watford  
Hertfordshire WD2 4YY  
Tel. 0923 43956

**Mimi**

**Bromcom**  
Bromley Computer Consultancy  
417-421 Bromley Road  
Bromley  
Kent BR1 4PJ  
Tel. 01-697 8933  
**Superstar**

**Computers**  
33A Bridge Street  
Cambridge CB2 1UW  
Tel. 0223 315063  
**Lynx 48K/96K/128K**

**Ceedata Ltd**  
Glebe House  
Armfield Close  
West Molesey Trading Estate  
East Molesey  
Surrey  
Tel. 01-941 4889  
**8200 series**

**CGL (Computer Games Ltd)**  
CGL House  
Goldings Hill  
Loughton  
Essex IG10 2RR  
Tel. 01-508 5600  
**CGL M5**

**Comart Ltd**  
Little End Road  
Eaton Socon  
St Neots  
Huntingdon  
Cambridgeshire PE19 3JG  
Tel. 0480 215005

**Comart CP100/1000 series**  
Communicator

**Commodore Bus. Machines**  
675 Ajax Avenue  
Slough SL1 4BG  
Tel. 0753 74111

**Commodore 64PC, 700 & VIC20**

**C/WP Computers**  
108 Rochester Row  
London SW1P 1JP  
Tel. 01-828 9000

**C/WP Cortex**

**Datac**  
Tudor Road  
Altrincham  
Cheshire  
Tel. 061-941 2361

**MC series**

**Digital Equipment Corp. (DEC)**  
PO Box 110  
Reading RG2 0TR  
Tel. 0734 868711

**Professional 300 series**  
DECmate II  
Rainbow 100

**Dragon Data Ltd**  
Kenfig Industrial Estate  
Margam  
Port Talbot  
West Glamorgan SA13 2PE  
Tel. 0656 744700

**Dragon 32**

**DVW Microelectronics Ltd**  
PO Box 135  
345 Foleshill Road  
Coventry CV6 5RW  
Tel. 0203 668181

**Husky**

**Eaca**  
Lowe Electronics Ltd  
Bentley Bridge  
Chesterfield Road  
Matlock  
Derbyshire DE4 5LE  
Tel. 0629 2817/2430/4057/4995  
**Colour Genie**

**Elan Computers Ltd**  
31-37 Hoxton Street  
London N1 6NJ  
Tel. 01-739 4282

**Elan Enterprise 64/128**

**Epson**  
Dorland House  
388 Wembley High Road  
Wembley  
Middlesex HA9 6UH  
Tel. 01-900 0455  
**HX20 portable, QX10**

**Flight Electronics Ltd**  
Quayside Road  
Southampton  
Hampshire SO2 4AD  
Tel. 0703-34003/27721

**Microprocessor MPF1 Plus**

**Future Computers Ltd**  
PO Box 306  
Purley  
Surrey  
Tel. 01-689 4341

**FX range**

**Haywood Electronic Associates**  
Electron House  
Leeway Close  
Hatch End  
Middlesex HA5 4SE  
Tel. 01-428 0111  
**Haywood 9000 series**

**Hewlett Packard Ltd**  
Nine Mile Ride  
Wokingham  
Berkshire RG11 3LL  
Tel. 0344 773100  
**HP-75C portable, 85B, 86B, 150, 200, 16A**

**HH Microcomputers**  
Viking Way  
Bar Hill  
Cambridge CB3 8EL  
Tel. 0954 81140

**Tiger**

**Hotel Microsystems**  
69 Loudoun Road  
London NW8 0DQ  
Tel. 01-328 3737

**Minstrel**

**Hytec Microsystems Ltd**  
Sandy Lane West  
Oxford OX4 5JX  
Tel. 0865 714545

**Prelude range**

**IBM PC Enquiry Centre**  
Rockware Avenue  
Greenford  
Middlesex UB6 0DW  
Tel. 01-578 4399

**IBM PC**

**ICL**  
ICL House  
Putney

London SW15 1SW  
Tel. 01-788 7272

ICL PC

Immediate Business Systems  
3 Clarendon Drive  
Wymbush  
Milton Keynes MK8 8DA  
Tel. 0908 568192

Fieldwork 50

Integrated Microproducts Ltd  
Number One Industrial Estate  
Medomsley Road  
Consett  
Co Durham DH8 6SY  
Tel. 0207 583481

IMP-68

ITCS  
2 Kingston Road  
Staines  
Middlesex TW18 4LP  
Tel. 0784 63211-3

Andromeda range

Iotec Ltd  
Bowling Back Lane  
Bradford BD4 8TF  
Tel. 0274 731509

Iotec 64CD

Jarogate Ltd  
197-213 Lyham Road  
London SW2 5PY  
Tel. 01-671 6321

Jarogate MP5 series (and JPU  
processor board)

Jupiter Cantab  
Cheshunt Building  
Bateman Street  
Cambridge CB2 1LZ  
Tel. 0223 313479

Jupiter Ace

Kemitron Industrial and  
Scientific Computers  
21-23 Charles Street  
Hoole  
Chester CH2 3AY  
Tel. 0224 21817

K2000E

LSI Computers Ltd  
Copse Road  
St Johns  
Woking  
Surrey GU21 1SX  
Tel. 04862 23411

Octopus

Leenshire Ltd  
Moorside Road  
Winnall  
Winchester  
Hampshire SO23 7RX  
Tel. 0962 64175

VCT 6900 series

Logica VTS Ltd  
64 Newman Street  
London W1A 4SE  
Tel. 01-637 5171

VTS Vitesse

Mattel Electronics Ltd  
Mattel House  
North End Road  
Wembley  
Middlesex HA9 0AB  
Tel. 01-900 0311

Aquarius, see Radofin

Memotech Ltd  
Station Lane  
Witney  
Oxfordshire OX8 6BX  
Tel. 0993 2977

MTX series

Micronix Computers Ltd  
Suite 2  
26 Charing Cross Road  
London WC2  
Tel. 01-240 0213/0271

MX400/800/1600/2400

Modcomp  
Sun Computing Services Ltd  
Concorde House  
St Anthony's Way  
Feltham  
Middlesex TW14 0NH  
Tel. 01-890 1440

Zorba

Modus Systems Ltd  
Park Drive  
Baldock  
Herts SG7 6EW  
Tel. 0462 894848 (4 lines)

Tensor range  
MD3A

Motorola  
Crellon Microsystems  
380 Bath Road  
Slough  
Berks SL1 6JE  
Tel. 06286 4300

Motorola Exorcet 100 & VME/10  
Syntel MC 02, MP 09 & 68K8

NEC Business Systems Europe  
Computer Division  
164/166 Drummond Street  
London NW1 1YP  
Tel. 01-388 6100

Advanced PC, PC 8000/8800  
series

Newbrain  
Brainwave Software Ltd  
Tilbury-juxta-Clare  
Great Yeldham  
Halstead, Essex  
Tel. 0787-237831

Newbrain

Oric Products International Ltd  
Coworth Park  
London Road  
Ascot  
Berks SL5 7SE  
Tel. 0990 27641

Oric

Osborne Computer Corp. (UK)  
38 Tanners Drive  
Blakelands North  
Milton Keynes MK14 5LL  
Buckinghamshire  
Tel. 0908 615274

Osborne Executive (future of  
company uncertain at time of  
writing but stock still available)

Philips Business Systems  
Electra House  
2 Bergholt Road  
Colchester CO4 5BE  
Tel. 0206 675115

P3000/3500

Phoenix Systems  
2nd Floor  
Buckingham House  
42 Princess Street  
Manchester 1  
Tel. 061 236 1172

Stratos

Plessey Microsystems Ltd  
Water Lane  
Towcester  
Northants NN12 7JN  
Tel. 0327 50312

PMM68K Multibus board  
System 68  
Miproc

Portico Technology  
South Bank House  
Black Prince Road  
London SE1  
Tel. 01-735 8171

Miracle

Positron Computers Ltd  
Unit 16  
Deacon Trading Estate  
Newton-le-Willows  
Lancashire WA12 9XQ  
Tel. 09252 28828

Sage  
Positron 900 series

Powertran  
Portway Industrial Estate  
Andover  
Hampshire SP10 3NN  
Tel. 0264 64455

Powertran Cortex kit

Radofin Electronics  
4th Floor  
Hyde House  
The Hyde  
London NW9 6LG  
Tel. 01-205 044

Aquarius

Rediffusion Computers Ltd  
Kelvin Way  
Crawley  
Sussex  
RH10 2LY  
Tel. 0293 31211

Teleputer 3

Research Machines Ltd  
PO Box 75  
Mill Street  
Oxford  
Tel. 0865 249791

RML 380Z  
Link 4802

Rockwell International  
Electronic Devices Division  
Heathrow House  
Bath Road  
Hounslow TW5 9QW  
Tel. 01-759 2366

Aim series

Seed  
Strumec Eng. Electronic  
Developments Ltd  
Portland House  
Coppice Side  
Brownhills  
Walsall  
West Midlands WS8 7EX  
Tel. 05433 78151/4321

Seed System 19 series

SBC  
Lambart Micro Computers Ltd  
52 Moorbridge Road  
Maidenhead  
Berkshire SL6 8BN  
Tel. 0628 72037

Duet 16

SemiTech Microelectronics  
145-147 Ewell Road  
Surbiton

Surrey KT6 6AW  
Tel. 01-390 6177

Pied Piper

Sharp Electronics (UK) Ltd  
Thorp Road  
Newton Heath  
Manchester M10 9BE  
Tel. 061 205 2333

MZ80

Sinclair Research Ltd  
25 Willis Road  
Cambridge CB1 2AQ  
Tel. 0223 353204

ZX81  
ZX Spectrum

Sirton Computer Systems Ltd  
Unit 14  
29 Willow Lane  
Mitcham  
Surrey CR4 4NA  
Tel. 01-640 6931

Midas MPS

Sord Computer Systems Inc  
Samuel House  
St Albans Street  
Haymarket  
London SW1Y 4SQ  
Tel. 01-930 4214

Sord M23/203/223/243/416

Southwest Tech Prods (SWTP)  
12 Tresham Road  
Orton Southgate  
Peterborough PE2 0SG  
Tel. 0773 234433

SWTP FO9/S09/S+

Stirling Microsystems  
241 Baker Street  
London NW1 6XE  
Tel. 01-486 7671

Dennis 6809 kit

Tandy Corporation  
Tameway Tower  
Bridge Street  
Walsall WS1 1LA  
Tel. 0922 648181

TRS80 models 1, 4 & 100  
PC2  
PC4  
Portable

Tashki Computer Systems  
24 Logan Road  
Wembley  
Middlesex HA9 8PX  
Tel. 01-904 4467

OM8064

Televideo  
Encotel Systems Ltd  
7 Imperial Way  
Croydon Industrial Estate  
Croydon  
Surrey CR0 4RR  
Tel. 01-686 9687 & 01-680 6040  
(6 Lines)

Televideo TS1603H/TS1603  
BMC if800

Texas Instruments  
Data Systems Division  
Manton Lane  
Bedford MK41 7PA  
Tel. 0234 67466

T199/4A



pen interface and RGB or composite-video outputs (£3400). The company also has \$100 to IEEE-488 interface and eeprom programming boards. **WW 503**

**Measurement Systems Ltd System 96:** modular approach intended for 'research, educational, industrial and commercial applications'. Memory may be up to 1M-byte and the system organized for ten users simultaneously or for one user with up to 256 independent tasks in order of priority. Virtual memory, floppy and Winchester-disc options are available and up to 12 serial ports may be added for multiple users or external communications. The c.p.u. board has four direct memory-access channels, one of which is normally allocated to the disc controller to allow data-transfer rates of up to 2M-bytes/s. Languages running under the 'Unix-like' operating system, OS9, include Basic09, i.e. Basic with Pascal features, Pascal, CIS Cobol and a C-language compiler. **WW 504**

**Micronix 80HD:** Single-board microcomputer includes Z80 counter-timer, serial and parallel i/o peripheral i.c.s with Western Digital floppy-disc controller and Texas c.r.t. controller. Has SASI-bus for hard-disc or cartridge storage, two serial and parallel ports and Z80 i/o bus. CP/M is current language but CP/M+ and MP/M2 are planned. Maximum ram size is 128K (2K video ram separate) and sockets are included to add 8K-bytes of rom, excluding 4K system monitor eeprom. Keyboard port is ASCII parallel. **WW 505**

**Plessey PSM range:** 68000-based boards using IEEE-796 bus (Multibus). Range includes c.p.u. board with Intel 8232 floating-point processor, two 512K-byte dynamic ram boards (one with parity checking, the other with error detection and correction) a 64K non-volatile memory board with battery and a 64K dynamic ram board. The processor board has three programmable 16-bit timers, two uarts, seven interrupt levels and built in fault diagnosis which is monitored through a separate port. One RS232 port is for console and the other includes modem-

control lines.

**WW 506**

**Pronto VME systems:** this company provides 68000-based VME boards from two companies - Mostek and Thomson CSF. Mostek boards include c.p.u., 256K-byte dynamic ram, serial communications and floppy-disc and SASI interface units: these are intended for products designed from the ground up. Pronto expect that a multi-user system using Unix system 3 will be available before the end of this year. One of the Thomson VME c.p.u. boards includes a port adapted for use with the G64 interface which allows over 50 existing interface memory and control boards to be used with a VME-based system. As opposed to the Mostek boards, these products allow VME boards to be used with systems already in use. Pronto also have a set of Z80 Eurocards intended for use in equipment to be manufactured on a small or medium scale. **WW 507**

**Protel Model 2000:** described as being 'particularly suited to process control, industrial, educational and certain computer functions' these 68000-based units use the VME bus and are built on extended double-Eurocard boards. The c.p.u. board has RS422/RS232 serial ports, seven interrupt levels and 32K-bytes of static ram or 64K-bytes of eeprom. Dynamic ram boards for up to 512K-bytes with parity checking and serial i/o boards with eight RS232 or RS422 ports and dynamic-memory access are included in the range. Also available are Comspeed local-area network boards based on the Cambridge ring principle for data transfer at up to 10Mbit/s. **WW 508**

**Rade Systems Rader 150:** this unit is described as a single-board computer with options and is mainly intended for manufacturers who want to put someone else's computer in their own equipment. The single board computer includes 64K-bytes of ram, floppy-disc interface, direct memory-access controller i.c., timer/counter i.c. and eight expansion connectors. An eight-bit keyboard port is standard, as are t.t.l. video outputs for a c.r.t. and a light-pen input; a serial key-

board interface is available. Optional boards that plug into this main unit provide dual parallel ports, dual serial ports, cassette interface, ram/rom expansion, hard-disc interface, hardware real-time clock and analogue conversion. **WW 509**

**Syntel 68-series boards:** some 20 Eurocard-form boards based on 6802, 6809 and 6800 processors are offered by this company. They include IEEE-488, analogue and graphics interface boards. One of the boards has two 6821 parallel-interface adapters and a 6840 counter/timer i.c. to provide 32 general-purpose i/o lines, eight interrupt/handshake lines, nine timer i/o lines and three counter/timer channels. All of the boards are compatible with the G64 bus used by Thomson CSF (see Pronto VME systems). Some development software is available from Syntel. **WW 510**

**Systime S300 series:** these boards are cased and with power supply and either floppy-discs or a combination of Winchester and floppy disc drives. An 8087 64-bit numeric-data processor may be used as co-processor for the 8080. Five RS232 serial lines provided by four uarts allow up to five users. Other peripheral i.c.s on the processor boards include an interrupt controller, 8203 dynamic-ram controller and three counter timers, one of which is spare. Initialization and diagnostic software are contained in 16K-bytes of eeprom and the c.p.u. board has room for 512K-bytes of ram. IEEE-796 bus (Multibus) allows use of up to 1M-byte of ram. **WW 511**


**Triangle Digital Services TDS900:** described as a 'Forth computer to build into products', this board is intended to act both as development tool and as an element of the finished product. Programs developed using Forth are held in eeproms in the final design. These boards are suitable for use in battery-powered equipment since they consume about 28mA. An application note describes a sound switch for the severely handicapped which allows mains appliances to be controlled using whistles. **WW 512**

continued from page 60.

points which are physically distant in reality may not be necessary at all in our machine, although this is pushing the point rather far.

A further requirement of our machine is that updating, or interaction, capability between points in physical reality and the related points in our machine where the digital analogue for that region of physical reality is stored, should be as efficient as possible.

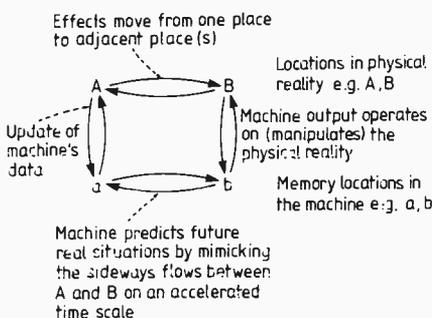The task of the machine architect is to exploit the potential of his technologies to meet these requirements. I believe I have done the best compromise in the Property 1 a invention<sup>2</sup>, but it is not ideal, considering the above criteria. The above criteria are not merely a *post hoc* rationalization



tending to show that my architectures are the best.

From the point of view of the above analysis, the reigning computer architecture theorists are doomed to failure. They (e.g. Petri nets) concentrate on the mechanism of computation in the machine, the bottom horizontal lines between a and b.

However, this has no value if the thinker does not bear in mind the dualism; that the arrows between a and b are a reflection of arrows between A and B; that computation only has value to the extent that it mimics events which occur in the real world. (This relates to my statement in the fourth paragraph above that the 'broad range of application', by which I mean the main field of application for our machine, and therefore the paradigm which should control their architecture, is directed towards practical rather than intellectual applications.

## References

1. I. Catt, Dinosaur Among The Data?, *New Scientist*, 6 March, 1969
2. For Property 1 a invention, see "Wafer Scale Integration", *Wireless World*, July, 1981, pages 57-59. **WW**

# CIRCUIT IDEAS



## Tone control

Several advantages over the Baxandall configuration are claimed for this tone control. Interaction does not occur because control potentiometers are terminated by a virtual earth. High and low-frequency turnover points are adjustable and response gives a true shelving characteristic with exact mirror images for lift and cut. Being non-

inverting, the stage may easily be bypassed.

NE5534 op-amps give best results, but an HA4605 quad op-amp i.c. saves space with little degradation. The single-pole filters may be replaced by state-variable filters to give full parametric control.

B. E. Porter  
Kings Lynn  
Norfolk

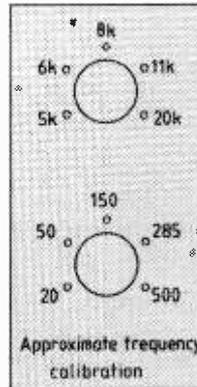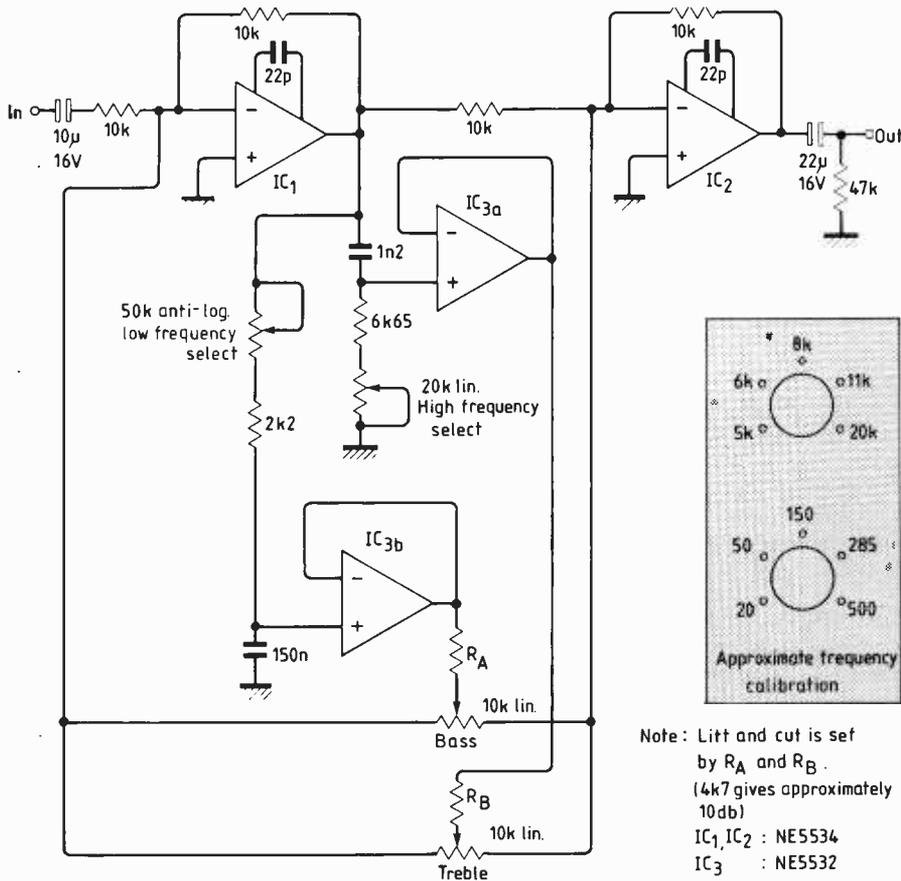


Note: Lift and cut is set by  $R_A$  and  $R_B$ . (4k7 gives approximately 10db)  
IC<sub>1</sub>, IC<sub>2</sub> : NE5534  
IC<sub>3</sub> : NE5532
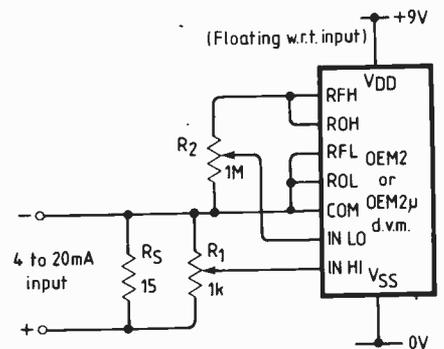
## Auto-zero with offset

Many a-to-d converters including popular 7106 and 7126 i.c.s have an auto-zero facility but this otherwise desirable feature is a limitation when a digital meter is required to display zero for a non-zero input. This circuit solves this problem and can be used for displaying for example 0 to 1600rev/min from a 4-20mA signal.

For clarity, the modified external circuit is illustrated for OEM-2/OEM-2µ digital voltmeters which incorporate 7106/7126 a-to-d converters with 3 1/2-digit i.c.s., decimal-point drivers and auxiliary components for a ±199.9mV full-scale.




d.v.m. As shown in the modified circuit  $R_S$  converts the 4-20mA signal into an input voltage of between 60 and 300mV.  $R_1$  provides full-scale calibration control and is adjusted to give a 40 to 200mV input. A 40mV offset derived through  $R_2$  from the stable 100mV reference at ROH is injected between COM and INLO. The differential voltage between INLO and INHI now gives the desired display range of 0rev/min at 4mA/40mV rising to 1600rev/min at 20mA/160mV input.

Peter Rummer  
Anders Electronics Ltd  
London

## Fuel-level indicator

When connected to a frequency counter, this circuit using a capacitive transducer made from copper central-heating pipe indicates the level of diesel fuel in a tank. Half of the 7413 is an oscillator (A) used to trigger the 74121 monostable i.c. How long the monostable i.c. is triggered for depends on the capacitance of the level transducer. While the monostable i.c. is triggered, pulses from the gated 7413 oscillator (B) pass to the output and represent the fuel level.

John Allsebrook  
Loughborough  
Leics

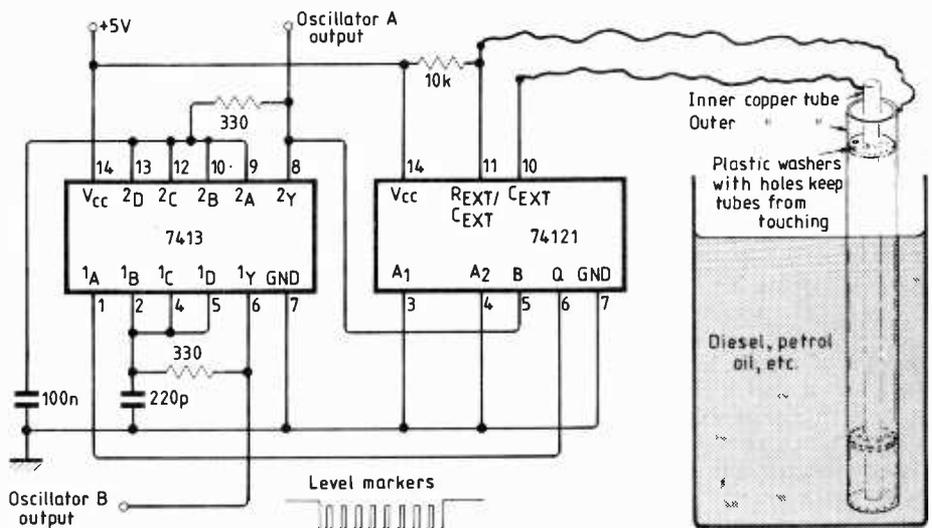



## Hard/soft sector selector

Many soft-sectored mini-floppy disc systems do not use the index-hole detector output from the disc drive so hard-sectored discs may be interchangeable with soft-sectored types. But in soft-sectored disc systems where the index hole is used, waveforms produced by extra index holes prohibit the use of hard-sectored discs, see timing diagram.

Soft-sectored discs have only one index hole which produces one pulse per revolution (200ms). Either 10 or 16 extra holes are used on hard-sectored discs to indicate the start of each sector to the controller. These extra pulses may be removed by inserting this circuit between the index line of a floppy-disc drive and a system designed for use with soft-sectored discs. The monostable i.c. is triggered by the trailing edge of each sector hole. If another hole is detected during the monostable-triggered period, it must be the true index hole and is signalled as such through the NAND gate to the controller. The two switches for selecting between hard or soft

sectored discs and 16 or 10 holes could easily be combined into one three-position switch. In multi-drive systems, it is probably desirable that the selector is only con-

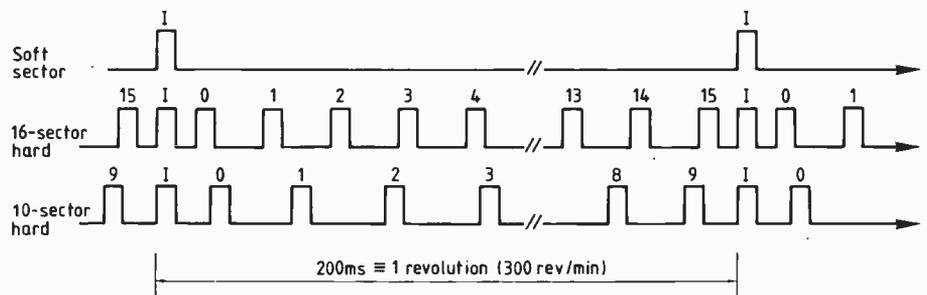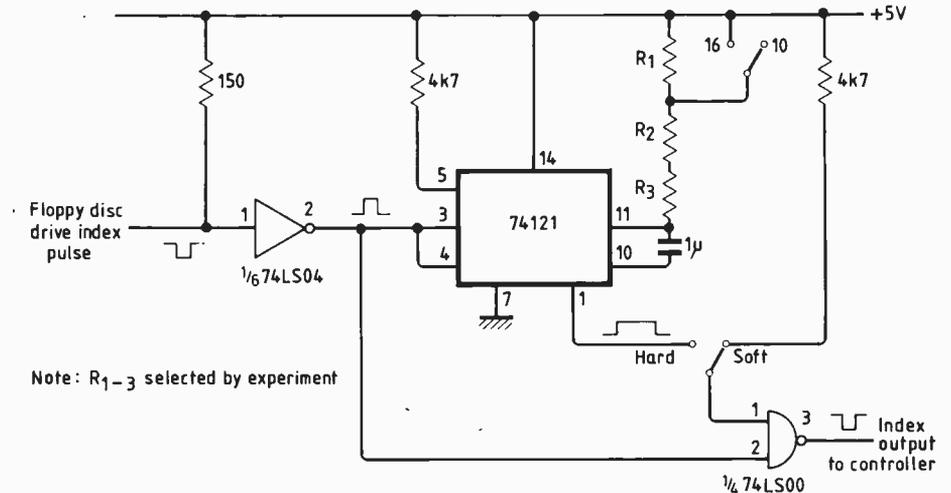nected to one drive.  
D. J. Greaves  
St Johns College  
Cambridge





## Matchbox switching regulator

Intended for a plug-mounted power supply, this small switching regulator gives 5V at 1A using an input voltage from 7 to 18V. The prototype uses a diode power mosfet (International Rectifier) as switching element and measures 27 by 36mm.

Control signals provided by the 555 totem-pole output are ideal for driving a fet. Off time of the output device is determined by values of C<sub>3</sub> and R<sub>4</sub> and is fairly constant but on time is governed by the discharge rate of C<sub>3</sub> through the bipolar current-source transistor. This current is switched through the 555 discharge pin, mainly to simplify calculations. Forward-path gain of the unit (A to B) depends heavily on the supply and at 18V is only in the region of 140 (calculated). Line regulation is therefore low but may be improved by inclusion of an op-amp or a feed-forward resistor between the supply and point A on the diagram.

In the feedback network, C<sub>1</sub> improves transient response and C<sub>2</sub> filters high-frequencies from the output. Some 30 turns

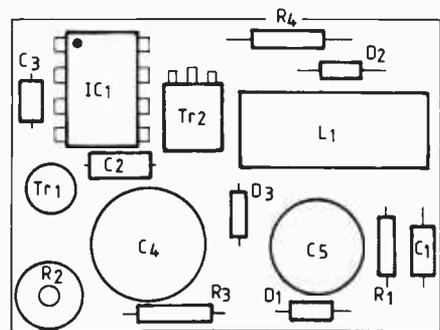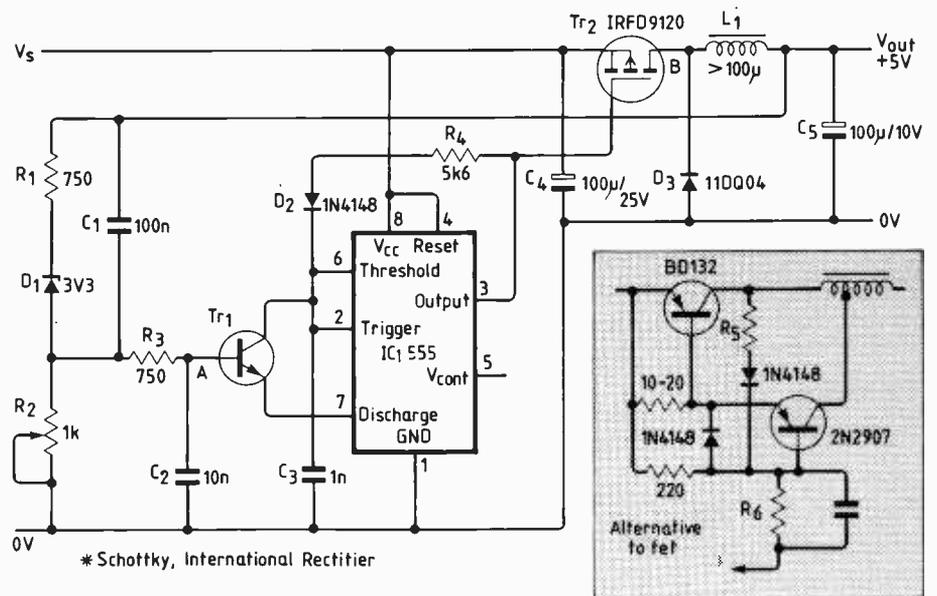

of 0.5mm wire wound on a Neosid 14mm powdered-iron toroid was used for the prototype output choke. Copper on the top surface of the p.c.b. is soldered to the fet drain terminals to act as a heat sink.

Shown separately, the bipolar alternative to the fet output device uses a tapped choke to keep the output transistor as near to saturation as R<sub>5</sub>/D<sub>4</sub> permit. Resistor R<sub>5</sub> is a trade-off between dissipation in the output device and collector current in the driver. The choke tap provides nominally between one and two volts across the

driver; R<sub>5,6</sub> are calculated using worst-case supply voltage and drive requirements of the two transistors. Other component values are determined by experiment.  
Richard Aston  
Northwich  
Cheshire

**Non-volatile ram module, September 1983. Polarity of the batteries in this module was indicated incorrectly.**

# NEW PRODUCTS

## Smaller filters cover more frequencies


The range of standard helical r.f. filters from Toko has been revised and extended to include coverage of the 800 to 1000MHz band and to provide smaller low-profile versions of the 7HW types. The 7HW filters are widely used in communications equipment including cellular radio. Over 15 types are available, offering a combination of selectivity, accurate matching and stability covering commercial, public service and amateur band frequencies in v.h.f. and u.h.f. Ambit International, 200 North Service Road, Brentwood, Essex CM14 4SG.

WW301

## Thin transformers

The latest transformers from Avel-Lindberg are claimed to be the World's thinnest. The 0.8VA version in the OB range is 10.5mm high, which enables it to be mounted in a p.c.b. frame and may be added to equipment within the existing space, if there are extra power requirements. Dual primary windings for 120 or 240V mains a.c. are complemented by centre-tapped secondaries which give 10 to 48V in series or 5 to 24V in parallel. The transformers are tested to 5kV up to a maximum operating temperature of 120°C and conform to Class 2 specifications. The connecting pins may be soldered directly to a p.c.b. and extra mechanical strength can be provided by bolting the transformer down through the holes provided in the moulded plastic casing. Others with 2, 4, 6, 8, 10 and 14VA ratings are available. Avel-Lindberg Ltd, South Ockenden, Essex RM15 5TD.

WW302

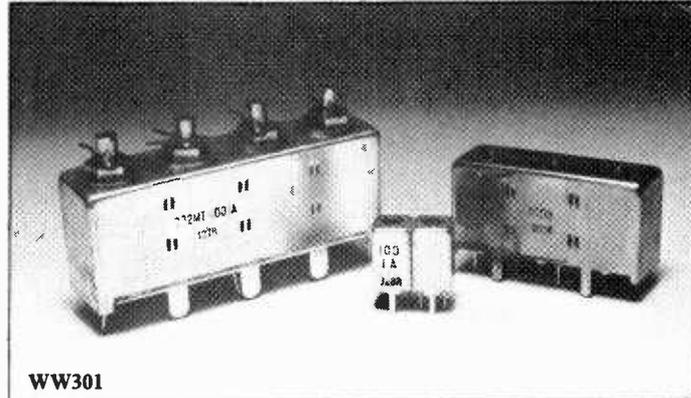

## Circuit design on home computer

A linear circuit analysis program, designed to run on the Acorn/BBC micro-computer is available from the designers, who originally wrote it for their own use as electronic design consultants. Circuits of up to 16 nodes and 60 components can be analysed. The program can simulate resistors, capacitors, inductors, transformers, bipolar and fet transistors, and operational amplifiers in any combination and analyse the circuit for input impedance, output impedance, gain and phase. The designers claim that considerable time can be saved in prototype breadboarding which in some cases may be omitted altogether. Versions of the program are being prepared for use with different computers. £35 inclusive from Number One Systems, 9A Crown Street, St Ives, Huntingdon, Cambs PE17 4EB.

WW303

## High street disc-drives

Computer peripherals are just beginning to follow computers into the high street shopping centres. An attack is being launched into this market by Cumana with their



WW304

half-eight drives for 5.25" flexible discs for use with the Acorn/BBC and or the Dragon home computer. The drives are available with 40 or 80 tracks and single or double-sided. Each drive comes with a user manual and a formatting disc, as well as the appropriate firmware operating system and interface. Cumana Ltd, Pines Trading Estate, Broad Street, Guildford, Surrey GU3 3BH.

WW304

## Linear-digital u.l.a.

Many electronics applications require analogue and digital circuitry together. This requirement can be satisfied by the Micronas MAS 7850, a c.mos integrated circuit containing both analogue and digital elements. The digital section of the circuit contains 48 D-type flip-flops which are already wired in to optimize performance and minimize silicon area. There are also 92 uncommitted logic elements, giving the digital section of the chip the equivalent total of 494 two-input gates. Circuitry at the 30 i/o pads can be configured to give various interfaces; c.mos or t.t.l. levels, tri-state, analogue switches, inputs with or without protection diodes etc. There are also 8 npn emitter follower transistors which may be connected in Darlington pairs.

The linear section of the chip contains four op.amps, two


comparators, an eight-bit resistor ladder, auto-zeroing circuitry, a +5V to -5V d.c. to d.c. converter and some i/o circuitry. Each of the op.amps can be wired into different modes to optimize performance and power consumption. Unused op.amps are 'switched off' and consume no power. The comparators have high gain with a slew-rate of 10V/ $\mu$ s. They can also be configured as additional op.amps. Applications for the circuit include switched capacitor filters, modulators and demodulators, a-to-d and d-to-a converters, and many other uses in instrumentation and process control, wherever both analogue and digital signal processing is required. Coole Marketing Services Ltd, 26 Pamber Heath Road, Pamber Heath, Basingstoke, Hants RG26 TG.

WW305

## Eprom programmer

An enhanced version of the Elan E2 eprom/eprom programmer has been made available which can directly interface with development systems. Two communications modes may be used: an RS232C link to a computer to provide a memory dump, or remote control. Any of eight serial formats are key selectable as are data transmission rates up to 9600b/s. The remote operation is defined for most development systems and is compatible with Data O 20B routines or most equivalents. This allows the device selection and programming function of the E2 to be controlled from the keyboard of the development system. Once the data has been transmitted, the programmer may be disconnected and used as a stand-alone editing programmer/copier. The E2 is supplied with 16K bytes of ram as standard and this may be expanded to 32K. A wide range of editing functions can be downloaded from the host system so that it can be released to continue other tasks. The editing instructions include: byte string search and automatic amendment, automatic block changing of data, and the splitting or merging of programs. Single bytes may be programmed instantaneously and the contents of smaller eproms may be combined to be transferred to a single larger device. All currently available single-rail devices may be programmed and an optional socket is available for use with microprocessors that have on-chip eproms. Because the E2 is software controlled it may be configured to cope with any new device, or programming algorithm that may be developed in the future. Elan Digital Systems Ltd, 16 Kelvin Way, Crawley, W Sussex RH10 2TS.


WW306

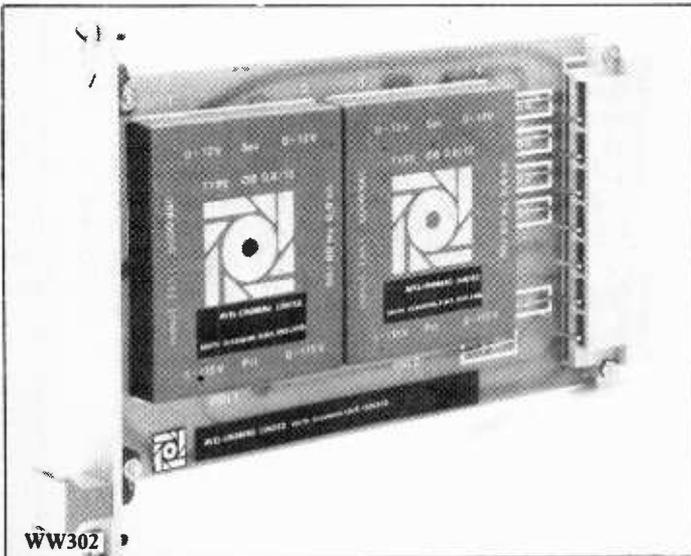

WW302

## Radio telephone tester

An integrated test system for radio telephones has applications in land mobile, marine and aeronautical services. The RTT system incorporates eleven test modules which, although linked internally, can be operated independently. As only two leads are needed to connect the system to the test transceiver, testing time is short and fault diagnosis is made simple. The instrument can measure automatically pilot tone transmission and reception and can provide selcall encoding and decoding for individual identification display. The p.l.l. signal generator has low noise, harmonic content and leakage to allow sum-microvolt sensitivity testing. Sinad measurement and a.f. monitoring are included. The r.f. power meter can measure in seven ranges up to 300W, and transmission frequency can be measured to as little as 1Hz, which is useful for quasi-synchronous testing. One feature, amongst others claimed to be unique, is the ability to test receive and transmit at the same time. This enables checks on full duplex receiver desensitivity. The unit is portable and can be operated from a 12V d.c. supply, which makes it suitable for field use. Other options include 1.5GHz testing, adjacent channel power measurement and off-air measurement. RTT, Enterprise House, Central Way, North Feltham Trading Estate, Feltham, Middx TW14 0RX. **WW307**

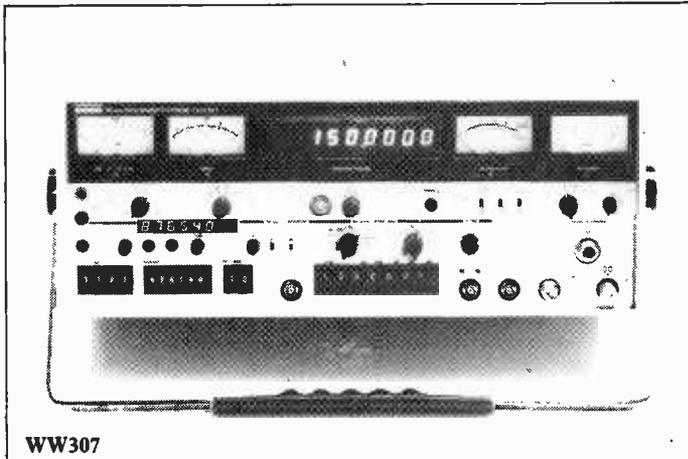

**WW307**




**WW309**

## Low cost micro-controller

Designed for use in industry, to add a controller to a product, the Xanar 680 microcontroller is also suitable for hobby and educational use. Typical applications include: printer controllers, games, digital voltmeters, digital weighing scales, a telephone timer, clock, car computer and eeprom programmer.

The controller is based on the Motorola 6802 processor with either a 6821 p.i.a. for 18 i/o lines, or a 6522 v.i.a. with the same number of lines and a shift register and two 16-bit timer/counters. The board includes a 5V regulator and a 3.5MHz crystal. The controller holds its program in a 2716 or 2732 eeprom (not supplied). The controller needs to be used with some external hardware, such as a keyboard (a 16-key hexadecimal keypad) and a display. It can also be programmed through a host computer with a rom emulator, such as the Softy II. When found to be operating correctly the program

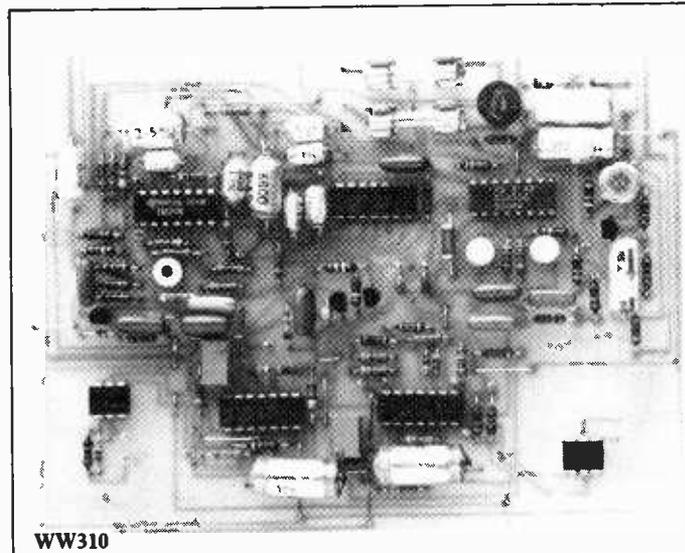

**WW310**

is transferred to eeprom. Other methods for programming the controller are by using the Greenwich Instruments' 'Instant Rom' or by trial-and-error eeprom programming (not really recommended!). In kit form, the Xanar Controller costs £19.95 for the 6821 p.i.a. version or £21.85 for the 6522 v.i.a. version. It is only £3 more to have them ready-built. Xanar, 20 Baldwin Road, King's

Lynn, Norfolk PE30 4AN. **WW308'**

## IC tester

An instrument from British designers to test most t.t.l. logic i.cs is offered at a price of £895, about half the price of the nearest competitor in the Far East. It is programmed in rom with test patterns for 14, 16, 20 and 24 pin

devices from all t.t.l. families. The z.i.f. socket used for the devices is automatically powered down when released so testing can be very rapid and safe. The tester can differentiate between the various output configurations, such as open collector or tri-state. Iterative test loops can be used to find intermittent or temperature sensitive breakdown. Physically the instrument fits into a sturdy case and is suitable for field service use. A 12-key keypad is used to enter the device number and a push of the 'test' key is all that is required of the operator. A pass or fail result is indicated on a led display. Testing rates have been found to be about 360 devices per hour with mixed components rising to 800 per hour with identical devices. Optional extras include software to test c.mos logic devices, an interface with additional software for ribbon cable testing, and another interface for in-circuit t.t.l. testing ABI Electronics, 2 Nostell Fold, Dodworth, Barnsley, S Yorks S7 3SR. **WW309**

## Build your own modem


When assembled according to easy-to-follow instructions, the MD1 modem will allow a computer to communicate over a telephone line. The completed modem is CCITT compatible, operates in full duplex over a telephone line, powered from the phone line but optically isolated from it, and may be switched between originate and answer modes. It is directly connected to the telephone line without an acoustic coupler. The kit is available for £39.95 inclusive from Racom Ltd, 81 Cholmely Road, Reading, Berks RG1 3LY. **WW310**

## Printer buffer

Suitable for Epson dot matrix computer printers, is the range of printer buffers from Electroplan. They offer considerable saving in time as they can store the text of a print-out and direct it to the printer, thus freeing the computer so that it can carry on computing without having to wait for the printer. A buffer will take seconds to load, compared with the minutes taken to print. Models are available with Centronics or RS232 interfaces and with memory capacities of 16K, 32K and 64K bytes. As a gauge, 16K represents 240 lines of solid text, about four pages of A4, or 8 to 12 pages of program listing. Electroplan Ltd, PO Box 19, Orchard Road, Royston, Herts SG8 5HH. **WW311'**

**HART  
KIT**

**LINSLEY-HOOD  
300 SERIES AMPLIFIERS**

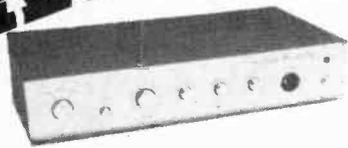

- 30 Watt Complete Kit ..... £65
- 35 Watt Complete Kit, MosFet O/P ..... £79.50
- 45 Watt Complete Kit, MosFet O/P ..... £83.50
- Reprints of 30 Watt Article from 'Hi-Fi News' ..... 50p
- Reprints of MosFet Postscript to above ..... 30p

**'P.W. WINTON' TUNER AND AMPLIFIER**



- Tuner, Complete Kit ..... £183
- Amplifier, Complete Kit ..... £98
- Amplifier Reprint ..... £1.25

**SOLENOID CONTROLLED HI FI/DIGITAL  
CASSETTE MECHANISM**



Front loading deck with full solenoid control of all functions including optional read in fast wind modes. 12 volt operation. Fitted 3-digit memory counter and Hall IC Motion Sensor. Standard erase and stereo R/P Heads. Cheapest price ever for all these features. Only £38.90 plus VAT. Full technical specification included.

**LINSLEY-HOOD 100-WATT MOSFET  
POWER AMPLIFIER**

The very latest amplifier design, published in 'Wireless World' by the renowned John Linsley-Hood. This may now be taken as the standard by which the rest are judged! Our kit, approved by the designer, has massive heat sinks and power supply and includes all components needed to build. Case size 412mm wide, 254mm deep and 145mm high. Automatic switched speaker protection is included as standard. Cost of all parts is over £120. Our complete stereo kit price £105.50.


**THIS MONTH'S SPECIAL OFFERS**

**DOLBY 'B' NOISE REDUCTION IC LM1011**  
Marvellous opportunity for home experimenters, build your own noise reduction system. Supplied complete with circuit showing typical application. Absolute knockout price only £3.50 for two inc. VAT and post.

**COMPLETE STEREO CASSETTE DECK**  
Brand new high quality top-loading Cassette Deck complete with Record/Play electronics. Supplied with connection data and circuit diagram. Automatic chrome/ferric switching. Only needs 9v DC supply. Total price only £18.34 inc. VAT and post.

**COMPLETE STEREO TUNER MODULE**  
Three band LW/MW/FM Stereo Tuner fully assembled on PCB 165 x 85mm. Supplied with Ferrite rod aerial and band switch fully wired. Facility provided to drive tuning meter and stereo LED. Only needs 12v DC supply. FM sensitivity. 2.5uV. Price only £7.99 inc. VAT and post.

**HALF HEIGHT 5 1/4" FLOPPY DISK**

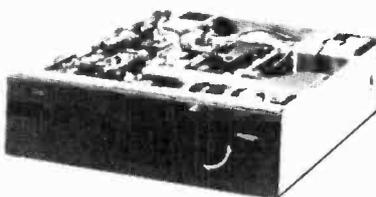

Latest MPU controlled 80 Track Drives, support single or double density. Fully compatible with Teac, Shugart and many other full and half height drives.  
80 Track Single side ..... £179  
80 Track Double side ..... £225  
Full manual for each type £14.50. No VAT.

**HIGH QUALITY REPLACEMENT  
CASSETTE HEADS**



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

- HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks ..... £5.11
  - HM90 High Beta Permalloy Head. A hard-wearing, higher performance head with metal capability ..... £8.06
  - HS16 Sandust Alloy Super Head. the best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response ..... £9.91
  - HQ551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head ..... £7.40
- Please consult our list for technical data on these and other Special Purpose Heads.

**HART TRIPLE-PURPOSE TEST  
CASSETTE TC1**

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £4.66 plus VAT and 50p postage.

**Tape Head De-magnetiser.** Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback. ..... £4.54  
Curved Pole Type for inaccessible heads ..... £4.85

**COMPONENTS**

We now list a wide range of individual components many of which are not available elsewhere. Send for your copy of our latest list which also gives further information on our Kits.

Please add part cost of post, packing and insurance as follows:

- INLAND**  
Orders up to £10 - 50p  
Orders £10 to £49 - £1  
Orders over £50 - £1.50
- OVERSEAS**  
Please send sufficient to cover  
Surface or Air Post as required.

**PLEASE ADD VAT  
TO ALL PRICES**

**HART  
KIT**  
HART ELECTRONIC KITS LTD  
PENYLAN MILL  
OSWESTRY, SHROPSHIRE  
SY10 9AF


Personal callers are always very welcome but please note that we are closed all day Saturday

**(0691) 652894**

**Hitachi Oscilloscopes**  
performance, reliability, value



**New Models!**  
immediate delivery!

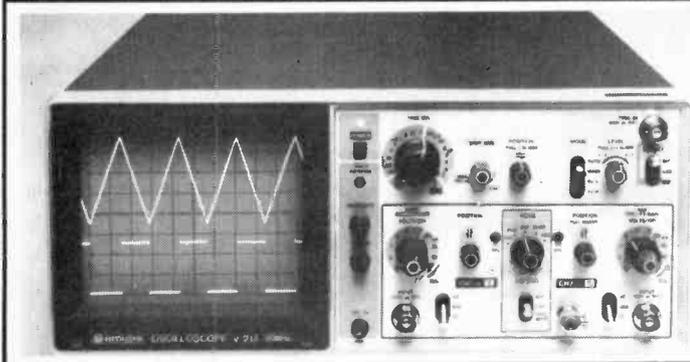

New from Hitachi are three low-cost bench 'scopes with bigger screens and extra features in a new slimline ultra-lightweight format. The range now extends to 13 models:—

- 4 dual trace single timebase models 20MHz to 40MHz
- 2 dual trace sweep delay models 20MHz and 35MHz
- 2 dual timebase multi-trace models 60MHz and 100MHz
- 2 miniature field portable models, 20MHz and 50MHz
- 3 storage models, one tube storage, two digital storage

Prices start at £295 plus vat (model illustrated) including 2 probes and a 2-year warranty. We hold the range in stock for immediate delivery.

For colour brochure giving specifications and prices ring (0480) 63570.

Reltech Instruments, 46 High Street, Solihull, W. Midlands, B91 3TB

WW - 010 FOR FURTHER DETAILS

**APOLLO 68000 SYSTEM**

Powerful 68000 runs at 10MHz without wait states. 16KB EPROM and 4KB fast static RAM, expandable 24 line programmable parallel I/O port. RS232 programmable serial port. Comprehensive monitor in 2764 Eproms. Optional plug-in Eprom programmer card. Cross Assemblers for Z80 based microcomputers. Code can be developed, downline loaded to 68000, debugged, and then written into Eprom.

- ★ 10 MHz 68000 CPU Board ..... £295+VAT
- ★ EPROM PROGRAMMER card ..... £95+VAT
- ★ CROSS ASSEMBLER for Z80 hosts from ..... £55+VAT

**APOLLO SOFTWARE. Tel: (0635) 201150**

The Alley, Cold Ash, Newbury, Berkshire RG16 9NN

WW - 063 FOR FURTHER DETAILS

**AMBISONIC  
SURROUND SOUND DECODERS**

Ambisonic surround sound gives a realism in the reproduction of music that is hard to describe without using hackneyed expressions like 'natural' and 'being there'. Positioning of the performer becomes obvious and the acoustic of the original environment comes through to the listening room. The Minim decoders also provide enhanced results from conventional stereo material. We can now supply UHJ encoded records, tapes and compact discs.

And don't forget our other products:

**PROGRAMMABLE WEEKLY TIME SWITCHES  
TELEVISION SOUND TUNERS**

Please send me information on Timeswitches/Television Tuners/Ambisonics

Name.....

Address.....

Minim Electronics Limited, Lent Rise Road  
Burnham, Slough SL1 7NY. Tel. Burnham 63724

WW - 058 FOR FURTHER DETAILS

# LANGREX SUPPLIES LTD

Climax House, Fallsbrook Rd., Streatham, London SW16 6ED

RST

Tel: 01-677 2424 Telex: 946708

RST

## SEMICONDUCTORS

AA119 0.10	AS215 1.20	BC173 0.11	BD132 0.48	BF257 0.27	GEX541 5.00	OAZ207 1.50	OC205 2.75	ZTX504 0.21	2N1671 5.00	2N3819 0.30
AA190 0.17	AS216 1.10	BC177 0.28	BD135 0.40	BF258 0.27	GJM3 1.50	OC16 2.50	OC206 2.75	ZTX531 0.24	2N1893 0.30	2N3820 0.39
AA300 0.17	AS217 1.00	BC178 0.28	BD136 0.40	BF259 0.28	GK378A 1.75	OC27 2.50	OC207 2.50	ZTX550 0.25	2N2147 4.00	2N3823 0.60
AA313 0.15	AS220 2.30	BC179 0.28	BD138 0.48	BF338 0.36	KS100A 0.45	OC22 2.50	OC22 2.50	OC207 2.50	2N2148 3.75	2N3866 1.00
AA315 0.15	AS221 2.50	BC182 0.11	BD139 0.48	BF339 0.36	MJE370 0.73	OC23 4.00	OC23 4.00	OC208 2.00	2N2218 0.32	2N3904 0.17
AA317 0.15	AU113 2.50	BC183 0.11	BD140 0.50	BF338 0.36	MJE371 0.71	OC24 3.00	OC24 3.00	OC209 2.00	2N2219 0.32	2N3905 0.17
AC107 0.55	AU110 3.00	BC184 0.11	BD144 2.00	BF339 0.36	MJE372 0.71	OC25 1.00	OC25 1.00	OC210 2.00	2N2220 0.20	2N3906 0.17
AC125 0.25	BA145 0.13	BC212 0.11	BD181 1.20	BF339 0.36	MJE373 0.71	OC26 1.50	OC26 1.50	OC211 2.00	2N2221 0.20	2N4058 0.20
AC126 0.25	BA148 0.15	BC213 0.11	BD183 0.80	BF339 0.36	MJE374 0.71	OC27 2.00	OC27 2.00	OC212 2.00	2N2222 0.20	2N4059 0.20
AC127 0.25	BA154 0.10	BC214 0.11	BD217 0.54	BF339 0.36	MJE375 0.71	OC28 2.00	OC28 2.00	OC213 2.00	2N2223 0.20	2N4060 0.16
AC128 0.30	BA155 0.11	BC237 0.11	BD238 0.54	BF339 0.36	MJE376 0.71	OC29 2.00	OC29 2.00	OC214 0.27	2N2369A 0.25	2N4061 0.16
AC141 0.28	BA156 0.10	BC238 0.11	BDX10 0.51	BF339 0.36	MJE377 0.71	OC30 2.00	OC30 2.00	OC215 1.00	2N2484 0.25	2N4124 0.16
AC141K 0.35	BAW62 0.05	BC303 0.34	BDX32 2.00	BF339 0.36	MJE378 0.71	OC31 0.90	OC31 0.90	OC216 1.00	2N2485 0.25	2N4126 0.16
AC142K 0.35	BAW62 0.05	BC303 0.34	BDY20 1.50	BF339 0.36	MJE379 0.71	OC32 0.90	OC32 0.90	OC217 1.00	2N2486 0.25	2N4128 0.18
AC176 0.30	BA148 0.15	BC307 0.11	BDY60 2.75	BF339 0.36	MJE380 0.71	OC33 1.50	OC33 1.50	OC218 1.00	2N2487 0.25	2N4289 0.18
AC176 0.30	BA148 0.15	BC308 0.11	BF115 0.35	BF339 0.36	MJE381 0.71	OC34 1.50	OC34 1.50	OC219 1.00	2N2488 0.25	2N4400 0.11
AC176 0.30	BA148 0.15	BC309 0.11	BF152 0.16	BF339 0.36	MJE382 0.71	OC35 1.50	OC35 1.50	OC220 1.00	2N2489 0.25	2N4401 0.11
AC176 0.30	BA148 0.15	BC310 0.11	BF153 0.16	BF339 0.36	MJE383 0.71	OC36 1.50	OC36 1.50	OC221 1.00	2N2490 0.25	2N4402 0.11
AC176 0.30	BA148 0.15	BC311 0.11	BF154 0.16	BF339 0.36	MJE384 0.71	OC37 1.50	OC37 1.50	OC222 1.00	2N2491 0.25	2N4403 0.11
AC176 0.30	BA148 0.15	BC312 0.11	BF155 0.16	BF339 0.36	MJE385 0.71	OC38 1.50	OC38 1.50	OC223 1.00	2N2492 0.25	2N4404 0.11
AC176 0.30	BA148 0.15	BC313 0.11	BF156 0.16	BF339 0.36	MJE386 0.71	OC39 1.50	OC39 1.50	OC224 1.00	2N2493 0.25	2N4405 0.11
AC176 0.30	BA148 0.15	BC314 0.11	BF157 0.16	BF339 0.36	MJE387 0.71	OC40 1.50	OC40 1.50	OC225 1.00	2N2494 0.25	2N4406 0.11
AC176 0.30	BA148 0.15	BC315 0.11	BF158 0.16	BF339 0.36	MJE388 0.71	OC41 1.50	OC41 1.50	OC226 1.00	2N2495 0.25	2N4407 0.11
AC176 0.30	BA148 0.15	BC316 0.11	BF159 0.17	BF339 0.36	MJE389 0.71	OC42 1.50	OC42 1.50	OC227 1.00	2N2496 0.25	2N4408 0.11
AC176 0.30	BA148 0.15	BC317 0.11	BF160 0.17	BF339 0.36	MJE390 0.71	OC43 1.50	OC43 1.50	OC228 1.00	2N2497 0.25	2N4409 0.11
AC176 0.30	BA148 0.15	BC318 0.11	BF161 0.17	BF339 0.36	MJE391 0.71	OC44 1.50	OC44 1.50	OC229 1.00	2N2498 0.25	2N4410 0.11
AC176 0.30	BA148 0.15	BC319 0.11	BF162 0.17	BF339 0.36	MJE392 0.71	OC45 1.50	OC45 1.50	OC230 1.00	2N2499 0.25	2N4411 0.11
AC176 0.30	BA148 0.15	BC320 0.11	BF163 0.17	BF339 0.36	MJE393 0.71	OC46 1.50	OC46 1.50	OC231 1.00	2N2500 0.25	2N4412 0.11
AC176 0.30	BA148 0.15	BC321 0.11	BF164 0.17	BF339 0.36	MJE394 0.71	OC47 1.50	OC47 1.50	OC232 1.00	2N2501 0.25	2N4413 0.11
AC176 0.30	BA148 0.15	BC322 0.11	BF165 0.17	BF339 0.36	MJE395 0.71	OC48 1.50	OC48 1.50	OC233 1.00	2N2502 0.25	2N4414 0.11
AC176 0.30	BA148 0.15	BC323 0.11	BF166 0.17	BF339 0.36	MJE396 0.71	OC49 1.50	OC49 1.50	OC234 1.00	2N2503 0.25	2N4415 0.11
AC176 0.30	BA148 0.15	BC324 0.11	BF167 0.17	BF339 0.36	MJE397 0.71	OC50 1.50	OC50 1.50	OC235 1.00	2N2504 0.25	2N4416 0.11
AC176 0.30	BA148 0.15	BC325 0.11	BF168 0.17	BF339 0.36	MJE398 0.71	OC51 1.50	OC51 1.50	OC236 1.00	2N2505 0.25	2N4417 0.11
AC176 0.30	BA148 0.15	BC326 0.11	BF169 0.17	BF339 0.36	MJE399 0.71	OC52 1.50	OC52 1.50	OC237 1.00	2N2506 0.25	2N4418 0.11
AC176 0.30	BA148 0.15	BC327 0.11	BF170 0.17	BF339 0.36	MJE400 0.71	OC53 1.50	OC53 1.50	OC238 1.00	2N2507 0.25	2N4419 0.11
AC176 0.30	BA148 0.15	BC328 0.11	BF171 0.17	BF339 0.36	MJE401 0.71	OC54 1.50	OC54 1.50	OC239 1.00	2N2508 0.25	2N4420 0.11
AC176 0.30	BA148 0.15	BC329 0.11	BF172 0.17	BF339 0.36	MJE402 0.71	OC55 1.50	OC55 1.50	OC240 1.00	2N2509 0.25	2N4421 0.11
AC176 0.30	BA148 0.15	BC330 0.11	BF173 0.17	BF339 0.36	MJE403 0.71	OC56 1.50	OC56 1.50	OC241 1.00	2N2510 0.25	2N4422 0.11
AC176 0.30	BA148 0.15	BC331 0.11	BF174 0.17	BF339 0.36	MJE404 0.71	OC57 1.50	OC57 1.50	OC242 1.00	2N2511 0.25	2N4423 0.11
AC176 0.30	BA148 0.15	BC332 0.11	BF175 0.17	BF339 0.36	MJE405 0.71	OC58 1.50	OC58 1.50	OC243 1.00	2N2512 0.25	2N4424 0.11
AC176 0.30	BA148 0.15	BC333 0.11	BF176 0.17	BF339 0.36	MJE406 0.71	OC59 1.50	OC59 1.50	OC244 1.00	2N2513 0.25	2N4425 0.11
AC176 0.30	BA148 0.15	BC334 0.11	BF177 0.17	BF339 0.36	MJE407 0.71	OC60 1.50	OC60 1.50	OC245 1.00	2N2514 0.25	2N4426 0.11
AC176 0.30	BA148 0.15	BC335 0.11	BF178 0.17	BF339 0.36	MJE408 0.71	OC61 1.50	OC61 1.50	OC246 1.00	2N2515 0.25	2N4427 0.11
AC176 0.30	BA148 0.15	BC336 0.11	BF179 0.17	BF339 0.36	MJE409 0.71	OC62 1.50	OC62 1.50	OC247 1.00	2N2516 0.25	2N4428 0.11
AC176 0.30	BA148 0.15	BC337 0.11	BF180 0.17	BF339 0.36	MJE410 0.71	OC63 1.50	OC63 1.50	OC248 1.00	2N2517 0.25	2N4429 0.11
AC176 0.30	BA148 0.15	BC338 0.11	BF181 0.17	BF339 0.36	MJE411 0.71	OC64 1.50	OC64 1.50	OC249 1.00	2N2518 0.25	2N4430 0.11
AC176 0.30	BA148 0.15	BC339 0.11	BF182 0.17	BF339 0.36	MJE412 0.71	OC65 1.50	OC65 1.50	OC250 1.00	2N2519 0.25	2N4431 0.11
AC176 0.30	BA148 0.15	BC340 0.11	BF183 0.17	BF339 0.36	MJE413 0.71	OC66 1.50	OC66 1.50	OC251 1.00	2N2520 0.25	2N4432 0.11
AC176 0.30	BA148 0.15	BC341 0.11	BF184 0.17	BF339 0.36	MJE414 0.71	OC67 1.50	OC67 1.50	OC252 1.00	2N2521 0.25	2N4433 0.11
AC176 0.30	BA148 0.15	BC342 0.11	BF185 0.17	BF339 0.36	MJE415 0.71	OC68 1.50	OC68 1.50	OC253 1.00	2N2522 0.25	2N4434 0.11
AC176 0.30	BA148 0.15	BC343 0.11	BF186 0.17	BF339 0.36	MJE416 0.71	OC69 1.50	OC69 1.50	OC254 1.00	2N2523 0.25	2N4435 0.11
AC176 0.30	BA148 0.15	BC344 0.11	BF187 0.17	BF339 0.36	MJE417 0.71	OC70 1.50	OC70 1.50	OC255 1.00	2N2524 0.25	2N4436 0.11
AC176 0.30	BA148 0.15	BC345 0.11	BF188 0.17	BF339 0.36	MJE418 0.71	OC71 1.50	OC71 1.50	OC256 1.00	2N2525 0.25	2N4437 0.11
AC176 0.30	BA148 0.15	BC346 0.11	BF189 0.17	BF339 0.36	MJE419 0.71	OC72 1.50	OC72 1.50	OC257 1.00	2N2526 0.25	2N4438 0.11
AC176 0.30	BA148 0.15	BC347 0.11	BF190 0.17	BF339 0.36	MJE420 0.71	OC73 1.50	OC73 1.50	OC258 1.00	2N2527 0.25	2N4439 0.11
AC176 0.30	BA148 0.15	BC348 0.11	BF191 0.17	BF339 0.36	MJE421 0.71	OC74 1.50	OC74 1.50	OC259 1.00	2N2528 0.25	2N4440 0.11
AC176 0.30	BA148 0.15	BC349 0.11	BF192 0.17	BF339 0.36	MJE422 0.71	OC75 1.50	OC75 1.50	OC260 1.00	2N2529 0.25	2N4441 0.11
AC176 0.30	BA148 0.15	BC350 0.11	BF193 0.17	BF339 0.36	MJE423 0.71	OC76 1.50	OC76 1.50	OC261 1.00	2N2530 0.25	2N4442 0.11
AC176 0.30	BA148 0.15	BC351 0.11	BF194 0.17	BF339 0.36	MJE424 0.71	OC77 1.50	OC77 1.50	OC262 1.00	2N2531 0.25	2N4443 0.11
AC176 0.30	BA148 0.15	BC352 0.11	BF195 0.17	BF339 0.36	MJE425 0.71	OC78 1.50	OC78 1.50	OC263 1.00	2N2532 0.25	2N4444 0.11
AC176 0.30	BA148 0.15	BC353 0.11	BF196 0.17	BF339 0.36	MJE426 0.71	OC79 1.50	OC79 1.50	OC264 1.00	2N2533 0.25	2N4445 0.11
AC176 0.30	BA148 0.15	BC354 0.11	BF197 0.17	BF339 0.36	MJE427 0.71	OC80 1.50	OC80 1.50	OC265 1.00	2N2534 0.25	2N4446 0.11
AC176 0.30	BA148 0.15	BC355 0.11	BF198 0.17	BF339 0.36	MJE428 0.71	OC81 1.50	OC81 1.50	OC266 1.00	2N2535 0.25	2N4447 0.11
AC176 0.30	BA148 0.15	BC356 0.11	BF199 0.17	BF339 0.36	MJE429 0.71	OC82 1.50	OC82 1.50	OC267 1.00	2N2536 0.25	2N4448 0.11
AC176 0.30	BA148 0.15	BC357 0.11	BF200 0.17	BF339 0.36	MJE430 0.71	OC83 1.50	OC83 1.50	OC268 1.00	2N2537 0.25	2N4449 0.11
AC176 0.30	BA148 0.15	BC358 0.11	BF201 0.17	BF339 0.36	MJE431 0.71	OC84 1.50	OC84 1.50	OC269 1.00	2N2538 0.25	2N4450 0.11
AC176 0.30	BA148 0.15	BC359 0.11	BF202 0.17	BF339 0.36	MJE432 0.71	OC85 1.50	OC85 1.50	OC270 1.00	2N2539 0.25	2N4451 0.11
AC176 0.30	BA148 0.15	BC360 0.11	BF203 0.17	BF339 0.36	MJE433 0.71	OC86 1.50	OC86 1.50	OC271 1.00	2N2540 0.25	2N4452 0.11
AC176 0.30	BA148 0.15	BC361 0.11	BF204 0.17	BF339 0.36	MJE434 0.71	OC87 1.50	OC87 1.50	OC272 1.00	2N2541 0.25	2N4453 0.11
AC176 0.30	BA148 0.15	BC362 0.11	BF205 0.17							

# WIN



## 14" COLOUR TV with TELETEXT and FULL REMOTE CONTROL!



## SHARP PC 1500 PORTABLE COMPUTER!



## £50 VOUCHER to spend on any product on this page!

easy to enter  
competition

HOW TO ENTER - BUY JUST ONE OF THESE PRODUCTS TO RECEIVE YOUR ENTRY FORM - BUT HURRY - CLOSING DATE IS 31.1.84 - AND YOU CAN'T BUY BETTER!

### COMPARE OUR PRICES



### COME TO US LAST!!!

**CDC DISKETTES AT CRAZY PRICES!**

STATE SOFT 10 OR 16 SECTORED

Code	Type	Price
TD1	5 1/4" 40 TRK single sided	£1.70
TD2	5 1/4" 40 TRK double sided	£2.05
TD3	5 1/4" 80 TRK single sided	£2.85
TD4	5 1/4" 80 TRK double sided	£2.99
TD5	8" 40 TRK SS-SD	£1.78
TD6	8" 40 TRK SS-DD	£2.10
TD7	8" 40 TRK DS-SD	£2.85
TD8	8" 40 TRK DS-DD	£2.95

10 per box. Prices per diskette quoted. Discounts for quantity  
ADD 15% VAT + £1.50 P&P

MINIMUM ORDER FOR PAPER = 5 BOXES

**LARGE RANGES OF PAPER AND RIBBONS AT GREAT PRICES**

e.g.: Listing Paper

Code	Type	Price
TD9	11" x 8 1/2" 60 GSM Plain	per 1000 £3.75
TD10	11" x 9 1/2" 60 GSM Perf'd Margins	per 1000 £3.95
TD11	11" x 14 1/2" 70 GSM Music Ruled	per 1000 £5.95
TD12	11" x 450mm 60 GSM Music Ruled	per 1000 £5.95
RIBBONS: 10 off EPSON FX-80		£49.95
10 off EPSON FX-100		£42.50
(Refill for metal cartridges)		

ADD 15% VAT + £1.50 CARR. PER ITEM (PAPER) OR BOX OF 10 RIBBONS. DELIVERY 10-14 DAYS

MANY MORE AVAILABLE - PHONE FOR DETAILS NOW!  
01-965 0627

### SINGLE BOARD COMPUTER

Very powerful and versatile, from Rade Systems the R150 multiprocessor SBC £385!! (ex. VAT + carr). Amazing spec. Look what you get: Z80A at 4MHz with 64K RAM 5 1/4" disk controller, Z80A CTC, Z80A DMA, Z80A P10, memory mapped VDU uses M6845 CRT, got 25x80 char display, you can use all the TD8 option cards to build your own powerful system, or build your own TD8! Suitable power supply £95. Keyboard from £85. Cased Video Monitors from £95. Supplied with full technical documentation. Demand for this excellent machine is high! Order now! Power requirements: +5V @ 1.5A, +12V @ 25A, -12V required for RS232 option - available on our standard PSU.



**DON'T WASTE MONEY!**  
ON OTHER COMPUTERS: COMPARE THE TD8 WITH OTHERS - COME TO US LAST!!

FROM £995  
(ex. VAT and monitor)  
PHILIPS 12" VDU 25x80 char. display



£149

TD8 SYSTEM

PROC. SSOR  
Dual Serial Ports £995 10MHz

Dual 250KB Drives



TD8 Keyboard

For dual 250KB disk system with 25x80 char. VDU, 93-key keyboard, user definable char. set, 128KB RAM (no upper limit to expansion, due to our unique bus structure. This also allows CPUs to be mixed). 4KB ROM with M/C monitor, bootstrap, dual RS232 ports to 19.2K baud, software controlled. Unique 'stackable' option modules allow easy and cheap expansion of your system - the first rational development from S-100 bus based machines!

CP/M80 £139. CP/M86 £225. 8086/7 with 128KB £495 extra gives you THE most powerful machine in its class. You could spend £6,000 for a machine of this specification.

Other options include: 64KB RAM expansion £135. 192KB RAM £249. IEEE488 £97.50. Sync comms £78. Dual Parallel Ports £59. Dual RS232 £59. 68000 CPU £TBA. 16032 CPU £TBA. A to D and D to A converters, high res. graphics, floppy and hard disk controllers and drives, tracker ball, real-time clock/calendar with BBU and more on the way!

CHOOSE YOUR SOFTWARE FIRST THEN COMPAARE OUR HARDWARE...



SOFTWARE: WordStar, Mailmerge, D Base II, Personal Pearl, MBasic, CBasic, Pascal 2, MT+, Fortran, CIS Cobol, C, Cardbox, FMS, Datastar, CalcStar, Supercalc, Mathemagic, Peachtree Sales Nominal, Purchase Ledgers, Inventory Management, Payroll, etc., ADA, Charger, Ratfor, Act 80, Act 65, 68, 69, 86/88, Tran8, Catchum and much more!

PHONE TO ARRANGE DEMO  
01-965 0627  
24 HOURS - SEVEN DAYS

Complete TD8 system (as illust.) with Keystar, Epson RX-80, disk filing box, CPM 2.2 and WordStar, VDU and keyboard


ONLY £1895!

ADD £19 carr. Does not include desk unit. Price is ex. VAT & carr


OR with HR15 Daisy Wheel! - £1995  
(ex. VAT, £14 carr)
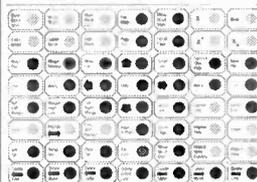
### KEYSTAR

SCALE COPY OF KEYSTAR KEYBOARD SHOWING THE FUNCTIONS PROVIDED



NO MORE FUMBLING FOR THE 'CONTROL' KEY!

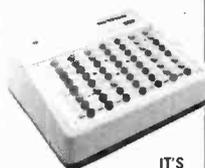

IT'S HERE!

The answer to all your WP problems!! If you use WordStar, Keystar will allow even those unfamiliar with WP to use the system straight away!

ONLY £189.95 ex. VAT & carr. Add £2 P&P)

SUITS MOST MACHINES:

Keystar's friendly keyboard allows you to work more efficiently saving time and mistakes! Demand is high for this amazing addition to the world's most popular WP package, SO ORDER NOW!  
01-965 0627 Telex: 24708

### INCREDIBLE!

A high quality daisy wheel printer with RS232 interface, 3KB character buffer, and a host of other features like full WordStar function support dual colour (red/black) printing

ONLY £475 (ex VAT + £12 carr)



SPECIAL OFFER UNTIL JANUARY 1, 1984

FREE DATA CABLE WITH EVERY BROTHER HR15! Use this printer with the low-cost TD8 micro for the ultimate in low-cost WP systems

FROM £12 DATA CABLES MADE TO YOUR SPEC/OFF SHELF

TALK ABOUT CHEAP!  
PHILIPS 12" VIDEO MONITOR - 25x80 CHARACTERS, P31 GREEN PHOSPHOR ATTRACTIVE CASE

ONLY £84.50 Excl VAT & CARRIAGE

KEEP RUNNING OUT OF SPACE? BDOS ERRORS? ADD AN EXTRA DISK DRIVE TO YOUR MACHINE

CASED AND UNCASED UNITS



New LSIs make the FD-55 Series better than ever

WITH OR WITHOUT POWER SUPPLY MODULES

TEAC

BBC COMPATIBLE

CASED - NO PSU:

250KB SS 40 TRK	£139
500KB SS 40 TRK	£195
500KB SS 80 TRK	£195
1MB DS 80 TRK	£229
1.6MB DS 80 TRK	£289
2 drive PSU Module	£69
4 drive PSU module	£99

- FD-55 features:
- Half the height of conventional drives
  - Capacity from 125 KBytes to 1.6MBytes
  - Perfect disk registration
  - Brushless DC direct drive motor
  - High-speed data access
  - Low power generation (4.9 W, operating)
  - LEO/photo sensor system

DUAL DRIVE UNITS WITH PSU

Twin 250K SS 40 TRK	£299
Twin 500K DS 40 TRK	£425
Twin 500K SS 40/80 TRK	£425
Twin 1MB DS 40/80 TRK	£495
Twin 1.6MB DS 80 TRK	£600

3.2MB  
£675!

inc. case and PSU ex VAT

2MBytes  
£495!

inc. case and PSU ex VAT. Carr. £4

Post now to: TELEDIGITAL COMPUTERS, 42 GORST ROAD, PARK ROYAL INDUSTRIAL ESTATE, LONDON NW10 6LD

Name \_\_\_\_\_ Please send me

Address \_\_\_\_\_

Phone us if you require more information on any of the above

01-965 0627

Tel. \_\_\_\_\_



Qty	Description	£	+ VAT & Carr

\*\*I enclose cheque

£.....

\*My Access/Visa

is .....

Allow up to 28 days delivery on non products. Your entry may be sent by return.

\*Delete where applicable.

WW - 044 FOR FURTHER DETAILS

# LOGIC ANALYSERS

Thandar's comprehensive range of professional specification instruments now includes 8 and 16 channel logic analysers to expand your test capabilities. Both analysers feature DC to 20MHz sampling rates, synchronous or asynchronous clocking and 15ns glitch capture in latch mode. There is also a powerful compound trigger delay by event and/or clock (two level triggering on TA2160), selectable trigger position, variable trigger filter and clock qualifier and arm facilities. All inputs are high impedance with TTL or variable threshold. Both have a composite video output to drive an external display or video printer and offer disassembler options for common microprocessors. Accessories are available for serial data capture and hard copy record printout.

**TA2080 (8 CHANNEL)** Full system information always shown in display; 8 bit data and reference memories, both 252 bytes deep; 23 bit triggering (8 data bits, 15 trigger bits); Timing display shows all 252 bytes of the 8 data channels in timing diagram format with x2, x4, x8 expansions available; State display shows 24 sequential bytes in either binary plus ASCII or hex plus octal plus ASCII; Automatic or manual compare between recording and reference memories for equality or inequality.

**TA2160 (16 CHANNEL)** 16 bit data and reference memories, 252 samples deep; Both data and reference memories configurable as 16 bit x 252 samples, 8 bit x 504 samples, or 2 x 8 bit x 252 samples; 34 bit triggering (16 data, 12 trigger and 6 qualifiers); Independent clocks and clock qualifiers in 2 x 8 bit modes; Sample or latch assignable on a per pod basis; Timing display shows 252 bytes of any 8 channels in timing diagram format with x2, x4, x8 expansions available; State display shows 16 sequential store locations of any 4 memories in 4 columns; each memory can be displayed in either binary, hex, octal, decimal, ASCII, or EBCDIC; Automatic or manual compare between any part of any two memories for equality or inequality; TTL or variable threshold assignable on a per pod basis; RS232 interface permits dumping and loading of reference memories and all system parameters.

Send for our complete catalogue and price list.  
Thandar Electronics Ltd, London Road, St. Ives,  
Huntingdon, Cambridgeshire, PE17 4HJ.  
Telephone (0480) 64646. Telex 32250.



**thandar**

ELECTRONICS LIMITED THE LOGICAL CHOICE

TH11

WW - 064 FOR FURTHER DETAILS

## Versatower:

A range of telescopic towers in static and mobile models from 7.5 to 36 metres with tilt-over facility enabling all maintenance to be at ground level.


Designed in accordance with CP3 Chapter V; part 2; 1972 for a minimum wind speed of 140 kph in conditions of maximum exposure and specified by professionals world-wide where hostile environments demand the ultimate in design, quality and reliability.

Suitable for mounting equipment in the fields of:

- Communications
- Security surveillance - CCTV
- Meteorology
- Environmental monitoring
- Geographical survey
- Defence range-finding
- Marine and aero navigation
- Floodlighting
- Airport approach lighting
- Further details available on request.



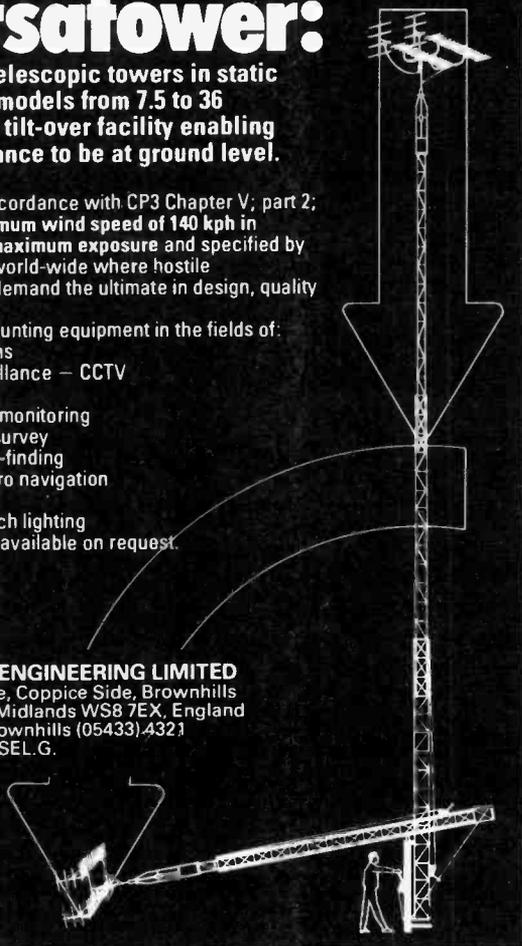**STRUMTECH ENGINEERING LIMITED**  
Portland House, Coppice Side, Brownhills  
Walsall, West Midlands WS8 7EX, England  
Telephone: Brownhills (05433) 4321  
Telex: 335243 SEL G.



WW - 014 FOR FURTHER DETAILS

## LIGHT UP YOUR CHRISTMAS

### WITH LED'S FROM LOCK

# BIG VALUES SAVINGS

**SAVE £S ON QUALITY BRANDED COMPONENTS**  
(FAIRCHILD AND NEC OPTO PRODUCTS)

<p><b>PACKAGE 1 ONLY £10.00</b></p> <p>10 off Seven Segment Displays <b>value £8.00</b></p> <p>40 off LED Lamps - <b>value £6.00</b> (mixed colours Red, Green, Amber)</p> <p>Plus one Fairchild Opto Data Book Free to first 100 customers - <b>value £2.50</b></p>	<p><b>PACKAGE 2 ONLY £5.00</b></p> <p>50 LED Lamps - <b>value £7.50</b> (mixed colours Red, Green, Amber)</p>
--	---


**Send off now limited supply only.**

Cheques or postal orders should be made payable to:  
LOCK DISTRIBUTION LTD.

**LOCK DISTRIBUTION LTD., P.O. Box OL64, Neville Street, Oldham OL9 6PY. Tel: 061-633 6236**


WW - 066 FOR FURTHER DETAILS

# AMPLIFIERS

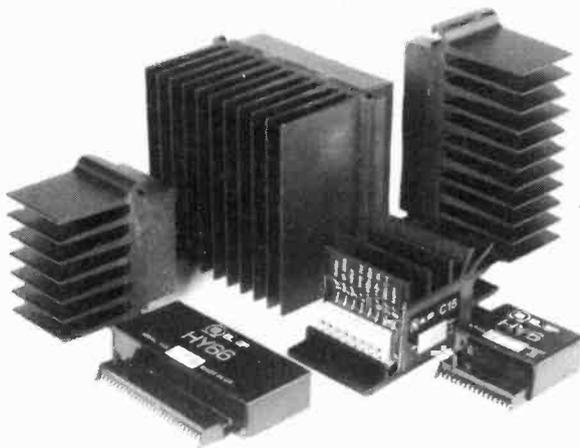

Over the last few years we have received feedback via the general public and industry that our products are from Taiwan, Singapore, Japan, etc... ILP are one of the few 'All British' electronics Companies manufacturing their own products in the United Kingdom. We have proved that we can compete in the world market during the past 12 years and currently export in excess of 60% of our production to over twenty different countries - including USA, Australia and Hong Kong. At the same time we are able to invest in research and development for the future, assuring security for the personnel, directly and indirectly, employed within the UK. We feel very proud of all this and hope you can reap some of our success.

I.L.Potts - Chairman

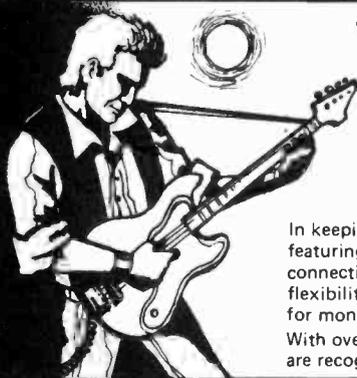

## WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



### BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance $\Omega$	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
HY30	15	4.8	0.015%	<0.006%	$\pm 18$	76 x 68 x 40	240	£8.40
HY60	30	4.8	0.015%	<0.006%	$\pm 25$	76 x 68 x 40	240	£9.55
HY6060	30 + 30	4.8	0.015%	<0.006%	$\pm 25$	120 x 78 x 40	420	£18.69
HY124	60	4	0.01%	<0.006%	$\pm 26$	120 x 78 x 40	410	£20.75
HY128	60	8	0.01%	<0.006%	$\pm 35$	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	$\pm 35$	120 x 78 x 50	520	£25.47
HY248	120	8	0.01%	<0.006%	$\pm 50$	120 x 78 x 50	520	£25.47
HY364	180	4	0.01%	<0.006%	$\pm 45$	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	$\pm 60$	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15V/ $\mu$ s. Risettime: 5 $\mu$ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K  $\Omega$ . Damping factor: 100Hz >400.

### PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

### Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

### POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83
PSU 42X	1 x HY128	£15.90
PSU 43X	1 x MOS128	£16.70
PSU 51X	2 x HY128, 1 x HY244	£17.07

Model Number	For Use With	Price inc. VAT
PSU 52X	2 x HY124	£17.07
PSU 53X	2 x MOS128	£17.86
PSU 54X	1 x HY248	£17.86
PSU 55X	1 x MOS248	£19.52
PSU 71X	2 x HY244	£21.75

Model Number	For Use With	Price inc. VAT
PSU 72X	2 x HY248	£22.54
PSU 73X	1 x HY364	£22.54
PSU 74X	1 x HY368	£24.20
PSU 75X	2 x MOS248, 1 x MOS368	£24.20

Please note: X in part no. indicates primary voltage. Please insert '0' in place of X for 110V, '1' in place of X for 220V, and '2' in place of X for 240V.

### MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance $\Omega$	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
MOS 128	60	4-8	<0.005%	<0.006%	$\pm 45$	120 x 78 x 40	420	£30.41
MOS 248	120	4-8	<0.005%	<0.006%	$\pm 55$	120 x 78 x 80	850	£39.86
MOS 364	180	4	<0.005%	<0.006%	$\pm 55$	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20V/ $\mu$ s. Rise time: 3 $\mu$ s. S/N ratio: 100db

Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms. Input impedance: 100K  $\Omega$ . Damping factor: 100Hz >400.

### 'NEW to ILP' In Car Entertainments

#### C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

Robust construction.

£9.14 (inc. VAT)

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 $\Omega$ .

Frequency response (-3dB) 15Hz to 30KHz. T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 80dB. Load Impedance 3 $\Omega$ .

Input Sensitivity and impedance (selectable) 700mV rms into 15K  $\Omega$  3V rms into 8 $\Omega$ .

Size 95 x 48 x 50mm. Weight 256 gms.

#### C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.


## ILP Electronics Ltd.

Graham Bell House, Roper Close  
Canterbury CT2 7EP, Kent, England  
Telephone: (0227) 54778. Telex: 965780

WW - 036 FOR FURTHER DETAILS

# ambit INTERNATIONAL

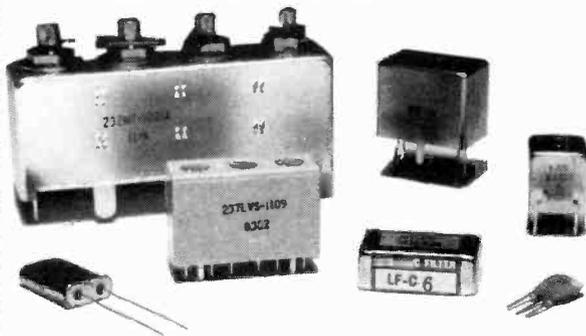**PRACTICALLY ALL THE WIRELESS PARTS YOU'LL EVER NEED, GATHERED TOGETHER IN ONE CATALOGUE...**




## Coils, crystals, filters

TOKO coils, filters chokes. UNI crystals, filters, NTK and Murata ceramic filters. Probably the broadest stock ranges of these types of component in the world, and a full service from AMBIT INDUSTRIAL MARKETING to support the OEM with custom requirements.
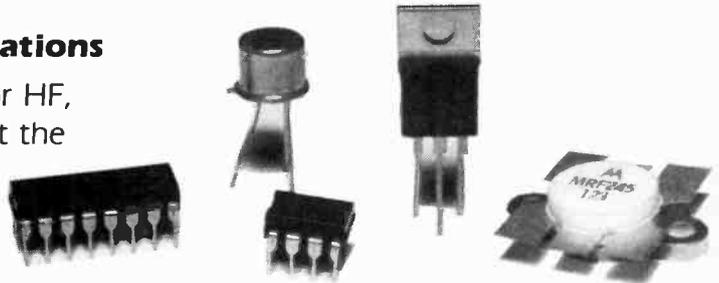
## Semiconductors for radio communications


ICs, Varicaps, FETS, MOSFETS, RF Power for HF, VHF, UHF. A broad selection that will meet the majority of requirements in receiver and transmitter designs



**High Performance Coax Relays, switches** etc. PC and connector relays engineered to the highest standards, plus a broad range of electro-mechanical support including push, toggle, and keyboard switches, rotary switches, plugs sockets etc.
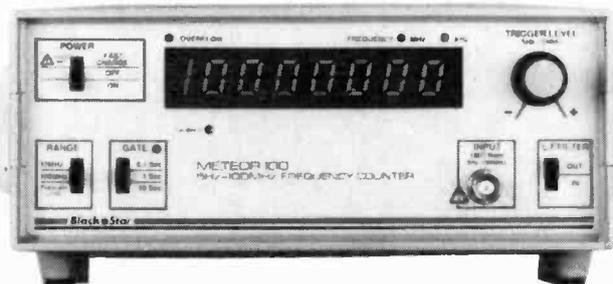
## Test Gear and Tools

New Black Star Frequency counters, Weller and Antex soldering tools, plus a wide selection of all types of equipment and tools for home and work.



# Communications Technology

for the enthusiast  
(and professional)


200 North Service Road, Brentwood, Essex CM14 4SG  
Tel: Consumer (0277) 230909. Industrial (0277) 231616  
Telex: 995194 AMBIT G.  
Data: (0277) 232628 REWTEL» (300 baud duplex)

★ **REGIONAL SALES COUNTERS**  
Solent Component Supplies, 53 Burrfields Road,  
Portsmouth  
Broxlea, Park Lane, Broxbourne, Herts

★ **SPRING CATALOGUE**  
Parts, Project Packs, Test Gear  
Info and 3 x £1 discount vouchers!  
ORDER NOW for FEB Shipment — 80p

ambit  
INTERNATIONAL  
COMPONENTS CATALOGUE 80p

# THE NEW MPF1 PLUS...

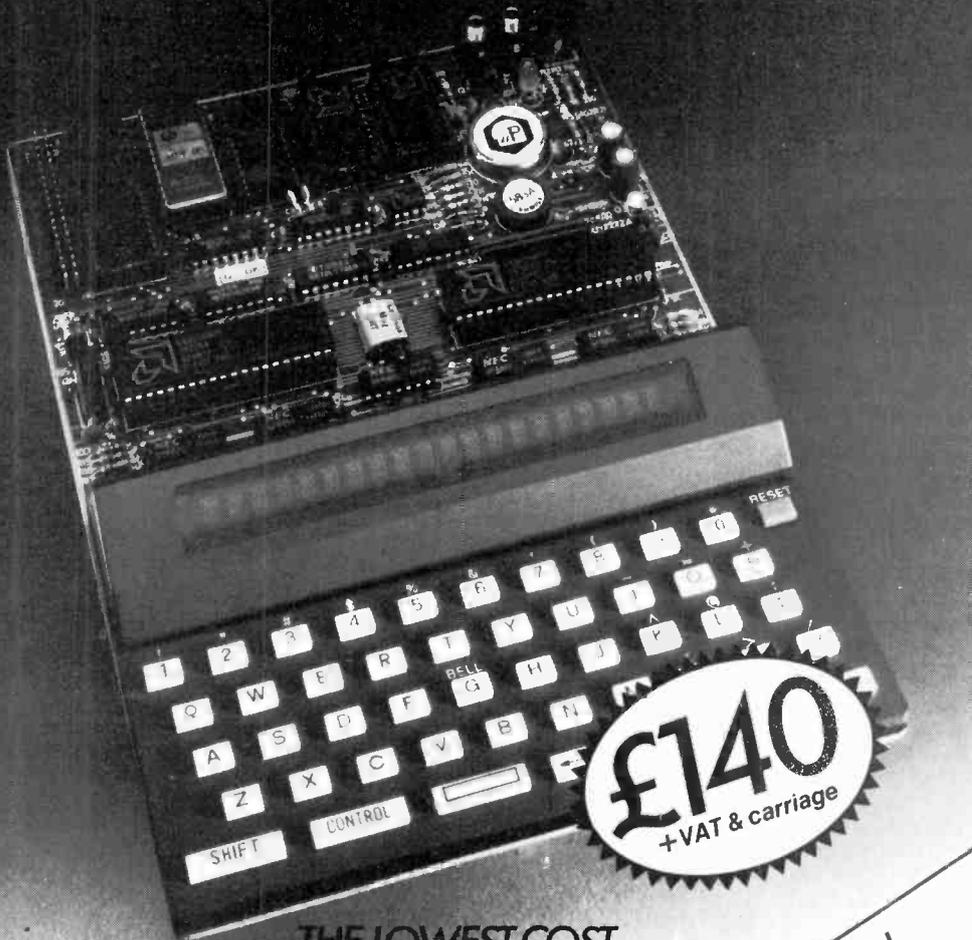

...THE LOWEST COST  
Z80 SINGLE BOARD COMPUTER  
AVAILABLE WITH ALL THESE FEATURES!

**BUILT-IN  
ASSEMBLER**

The MPF1 PLUS incorporates the Z80 – the most widely used 8-bit microprocessor in the world, to form a Single Board Computer (SBC). Packed in a plastic bookcase together with three comprehensive manuals and power supply (to BS3651 standard), the MPF1 PLUS is a microprocessor learning tool for every application.

**FLIGHT**  
Electronics Ltd.

Quayside Rd, Southampton, Hants SO2 4AD. Telex 477793. Tel. (0703) 34003/27721.

Micro-Professor is a trade mark of Multitech Industrial Corporation. Z80 is a trade mark of Zilog Inc.

Teaching you in a step-by-step method the MPF1 PLUS helps the user fully understand the Software and Hardware of a microprocessor easily and conveniently – as opposed to micro-computers that aim to teach high-level languages instead of microprocessor systems fundamentals.

Not only is the MPF1 PLUS a teaching tool but with the available accessories it can also be used as a low-cost development tool or simply for OEMs.

## THE MPF1 PLUS

Just look at the specification:-

### Technical Specification

**CPU:** Z80A – 158 instructions

**Software:**

- Z80/8080/8085 machine code
- Z80 Assembler, line and 2 pass.
- 8K BASIC interpreter (Extra)
- 8K FORTH (Extra)

**ROM:** 8K Monitor (full listing and comments)

**RAM:** 4K CMOS (2 x 6116)

**Input/Output:** 48 system I/O lines

**Speaker:** 2.25" coned linear

**Display:** 20 character 14 segment green phosphorescent

**Expansion:**

- Socket for 8K ROM
- Cassette interface
- Connectors 40 way, complete CPU bus

**Keyboard:** 49 key. Full "QWERTY" real movement good tactile feedback

**Batteries:** 4 x U11 for memory back-up (batteries not included)

**Serial Interface:** 165 baud for read/write via audio cassette

### Manuals

1. User's Manual. 8 chapters.
  1. Over view and Installation.
  2. Specification (hardware and software).
  3. Description of Operation.
  4. Operating the MPF-1 Plus.
  5. 44 Useful Sub-Routines.
  6. The Text Editor.
  7. Assembler and Disassembler.
  8. System Hardware Configuration.
2. Experiment Manual. 16 experiments.
3. Monitor Program Source Listing with full commenting.
4. Also available the MPF-1 Plus Student Work Book (self-learning text).

### Accessories

- **PRT-MPF-1P:** 20 character printer. Ready to plug in. Memory dump.
- **EPB-MPF-1P:** Copy/list/verify 1K/2K/4K/8K ROMS. Ready to plug in.
- **SSB-MPF-1P:** Speech Synthesizer. Inc. 20 words and clock program. 1200 words available.
- **SGB-MPF-1P:** Sound Synthesizer Board.
- **I/O – MPF-1P:** Input/output board

**Yes! I now realise that I need an MPF1 PLUS and that it is the lowest cost Z80 SBC available with all these features.**

**I enclose £165.00 (£140.00 + £21 VAT plus £4 carriage). Overseas P.O.A.**

**Cheques payable to  
FLIGHT ELECTRONICS LTD.**

Please debit my  Barclaycard/Access    

Account No. \_\_\_\_\_

An invoice will automatically be sent.

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

Signature \_\_\_\_\_

Date \_\_\_\_\_

 \_\_\_\_\_ WW

WW – 042 FOR FURTHER DETAILS

## TEST EQUIPMENT

	£
Feedback VPO 602 Variable Phase Oscillator	65
Marconi TF 2002B AM/FM 10kHz-88MHz	795
Flyke 8800A 4 1/2 digit DMM	150
Flyke 8020A 3 1/2 digit DMM (New)	60
Case for above (New)	12
GEC Super 50 Selectest	75
Philips PM2354 AC Millivoltmeter 0-2MHz 1mV-300V	150
Sullivan AC Test Set	350
H.P. 7100B 2 Pen Chart Recorder	195
H.P. 5000A Logic Analyser	195
Philips 2522A 4 1/2 digit DMM	145
Sanwa Multimeters	10
Pantec Electro Multimeter	10
25A/600V Clamp Meters	175
Houston DP10 Incremental XY Plotter	195
Iwatsu Dual Trace 20MHz Scope	950
Advance OS4000 10MHz Digital Storage Scope	195
Advance OS1000B Dual Trace 20MHz Scope	195
Leader LB0510B 4MHz Single Channel Scope (new)	60
Scopex 456 6MHz Single Channel Scope	325
Tequipment CT71 Curve Tracer	350
Tequipment DM64 10MHz Tube Storage Scope	375
Tequipment D75 50MHz Dual Trace Delay T/B Scope	175
Scopex 30-4D Dual Trace 30MHz Scope Dual Channel	225
Hitachi V-302 30MHz Dual Trace Scope	675
Advance OS3500 60MHz Scope with DM3010 DMM option	175
Advance OS255 15MHz Dual Trace Scope	195
Tek. 564 Storage Scope	750
Tek. 7403 75MHz Mainframe with 7B53 and 7A18 plug-ins	565
Leader LFR 560 Frequency Response Recorder	295
J. J. Lloyd PL100 X-Y Plotter with spare Amp	195
Radiometer SMG1 Stereo Generator	250
H.P. 9815A Desk Top Computer	150
H.P. 776D 940-1900MHz Directional Coupler (New)	135
Systron Donner 62 Set Timer Counter BCD output	195
Systron Donner 7344A 4 1/2 digit DMM IEEE interfaced	350
Pecker 5000 prom programmers	115
Tek. 191 Constant Amp. Signal Generator 100MHz	95
Tek. 106 Square Wave Generator	95
Tek. Amplitude Calibrator	80
3 Phase Variac 6A	50
Tek. Type M Plug-in	50
Tek. Type 1A6 Plug-in	50
Tek. 454A 150MHz Scope	95
Tek. 575 Curve Tracer	450
Yaesu Museu YC10001 Data Logger 600MHz Timer Counter, DMM, Thermometer and Printer all in box (New)	50
AD-VU Phase Angle Voltmeter	95
H.P. 612 UHF Signal Generator 450-1250 MHz	235
Tequipment D67 25MHz Dual Channel Delay T/B Scope	255
Tequipment D67A 25MHz Dual Channel Delay T/B Scope	75
Marconi TF 801/D 470MHz AM Signal Generator	40
Data Dynamics Teletypes	195
R & S SMAF AM/FM Signal Generator 300MHz	75
Philips PE4808 35V/20A Variable PSU metered	95
Philips PE4807 35V/10A Variable PSU metered	25
Pye 40kV Lamp	75
Shugart 8" floppy disc drive	95
H.P. 1803A Differential plug-in	95
H.P. 1821A T/B plug-in	50
Electrohome 19" B/W X-Y Monitors	20
Tek. 113 Delay Cable	795
Philips 3244 Scope 4 channels 50MHz	35
Wier 30V/2A, 60V/1A metered PSU	

Carriage additional. All prices exc. V.A.T.




**TIMEBASE**  
94 ALFRISTON GARDENS, SHOLING, SOUTHAMPTON SO2 8FU  
TELEPHONE: 431323 (0703)  
Callers welcome. Access/Barclaycard: Telephone your order



WW - 038 FOR FURTHER DETAILS

# FYLDE
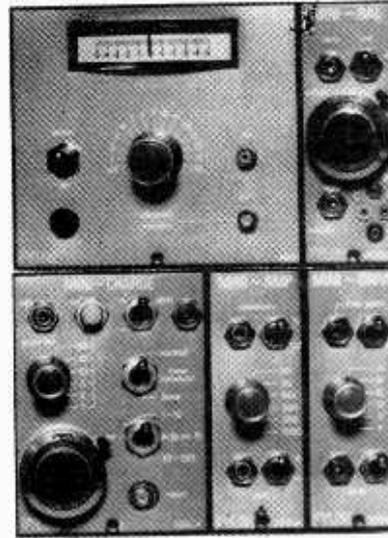
## TRANSDUCER and RECORDER AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules— mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

# FYLDE

Fylde Electronic Laboratories Limited.

49/51 Fylde Road Preston  
PR1 2XQ  
Telephone 0772 57560

WW - 030 FOR FURTHER DETAILS

## DESIGNERS AND MANUFACTURERS OF HIGH QUALITY CCTV VIDEO PROCESSORS & COLOURISERS



**INSIGHT VISION SYSTEMS LIMITED**


Unit 1, Merebrook,  
Hanley Road, Malvern,  
Worcs WR13 6NP, England  
Tel (0684) 310001  
Telex 334480 INSIGT'G'



SELF CONTAINED  
**BLACK & WHITE VIDEO PROCESSOR**

- AUTOMATIC/MANUAL GAIN
- AUTOMATIC/MANUAL BLACKLEVEL
- VARIABLE EDGE ENHANCEMENT
- 3 STAGE VARIABLE TRANSFER FUNCTIONS
- REINSERTION OF NEW SYNC & BLANKS
- 8 STYCS GREY SCALE INSERTION
- VARIABLE SHADING CORRECTION

SELF CONTAINED VIDEO COLOURISER

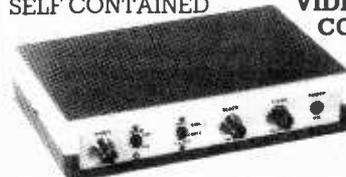

- ACCEPTS 1 VOLT COMPOSITE VIDEO
- COLOUR SEQUENCE (8 STEPS)  
BLACK BLUE CYAN GREEN  
MAGENTA RED YELLOW WHITE
- 1 VOLT PAL ENCODED RGB OUTPUT
- SWITCHABLE RESOLUTION 7.5/1.5 mHz
- CASED OR EUROCARD VERSIONS

Contact Andrew Smith on (0684) 310001

WW - 062 FOR FURTHER DETAILS

### BROADCAST MONITOR RECEIVER 150kHz-30MHz



We have taken the synthesised all mode FRG7700M communications receiver and made several well-thought-out modifications to provide a receiver for re-broadcast purposes or checking transmitter performance as well as being suited to communications and news gathering use.

**PRINCIPAL MODIFICATIONS:** Radically redesigned front end stages yielding improved noise figure and overload levels. TOIP -2dBm (originally -21dBm) ★ Flat audio frequency response on both AM and SSB ★ Lower AM distortion ★ Balanced audio line output ★ Buffered IF output for monitoring transmitted modulation envelope on an oscilloscope ★ Mains safety improvements.

The receiver is available in free standing or rack mounting form and all the original features are retained. The new am detector board achieves exceptionally low distortion: THD, 200Hz-6kHz at 90% modulation -44dB, 0.6% (originally -20dB, 10%). Reviewed Broadcast Sound, Jan/Feb 1984.

Stereo Disc Amplifier 3 and 4 ★ Peak Deviation Meter ★ Programme and Deviation Chart Recorders ★ Stabilizer ★ Frequency Shift Circuit Boards ★ 10 Outlet Distribution Amplifier ★ Peak Programme Meter Illuminated Boxes, Circuit Boards and Ernest Turner Movements ★ Stereo Microphone Amplifier.

**SURREY ELECTRONICS LIMITED**  
The Forge, Luckes Green, Cranleigh, Surrey GU8 7BG. Tel: 0483 275997

# RADFORD

Audio Measuring Instruments,  
Audio Amplifiers, Loudspeakers and  
Loudspeaker Components for the  
professional and enthusiast

**RADFORD AUDIO LTD.**

10 BEACH ROAD  
WESTON-S-MARE, AVON BS23 2AU

TEL. 0934 416033

WW - 011 FOR FURTHER DETAILS

<b>RESISTORS</b>	2.2 100 11p	Single sided	2N2905	29p	40411	3.95	BC547A	14p
<b>CARBON FILM</b>	2.2 350 30p	100 x 160	2N2905A	29p	40412	9.00	BC547B	14p
<b>5% HI-STAB</b>	3.3 25 10p	100 x 220	2N2906	25p	40673	7.00	BC548	12p
<b>LOW NOISE</b>	4.7 10 1p	100 x 114	2N2906A	30p	40822	1.80	BC548A	13p
<b>10Ω to 10MΩ</b>	4.7 16 8p	233 x 220	2N2907	25p	40823	1.80	BC548B	14p
<b>1/4W E24</b>	4.7 25 9p	Double Sided	2N2907A	25p	40824	1.90	BC549	13p
<b>1/4W E24 2 1/2p</b>	4.7 33 12p	100 x 160 2.20	2N2920	9.25	AC125	4.00	BC549B	14p
<b>1/4W E24 5p</b>	4.7 47 12p	100 x 200 2.80	2N2921	25p	AC126	3.20	BC549C	14p
<b>1/4W E24 10p</b>	4.7 62 12p	203 x 114	2N2922	15p	AC127	3.50	BC549D	14p
<b>METAL FILM</b>	4.7 100 12p	233 x 220 5.90	2N2925	15p	AC128	3.50	BC550	14p
<b>ULTRA STABLE</b>	10 25 8p	Developer for	2N2926	10p	AC132	6.80	BC550C	25p
<b>0.4W EXTRA</b>	10 30 12p	above idolo mt	2N3053	27p	AC141K	28p	BC557	15p
<b>LOW NOISE</b>	10 35 55p	Hydroxide!	2N3055	60p	AC152	4.50	BC557A	16p
<b>100 to 1MΩ</b>	22 25 11p	500 ml mix	2N3055H	1.20	AC152	4.50	BC558	14p
<b>2% E24</b>	22 25 11p		2N3250	39p	AC153	5.50	BC558A	15p
<b>1% E24</b>	22 25 11p		2N3250	39p	AC153K	6.40	BC558B	16p
<b>LOW OHM GLAZE YMC</b>	22 25 11p		2N3442	1.35	AC187K	28p	BC559	15p
<b>0.221 to 2.2</b>	47 10 25p		2N3444	8.05	AC187	27p	BC559B	16p
<b>E24 11p</b>	47 10 25p		2N3445	4.00	AC187K	28p	BC559C	17p
<b>WIREWOUND ON CERAMIC</b>	47 10 25p		2N3446	6.98	AC188K	40p	BC560	25p
<b>512 SERIES</b>	100 16 4p	Solid connecting wire	2N3447	5.72	AF239	5.50	BC560A	45p
<b>2 to 3W 270Ω</b>	100 16 4p	Twinn 1 Amp	2N3448	6.56	AF239	5.50	BC561	46p
<b>to 330Ω 270Ω</b>	100 16 4p	Twinn 2 Amp	2N3512	1.06	BC107A	12p	BC711	12p
<b>4 to 7W 470Ω</b>	100 16 4p	3 Core 2 1/2 Amp	2N3553	2.65	BC107B	12p	BC712	12p
<b>to 68Ω 33p</b>	100 16 4p	3 Core 6 Amp	2N3638	55p	BC108	10p	BD131	44p
<b>to 1W 11p</b>	220 16 17p	3 Core 13 Amp	2N3702	1.0p	BC108B	12p	BD132	44p
<b>to 33k 37p</b>	220 16 17p		2N3703	1.0p	BC108C	14p	BD133	35p
<b>POTS &amp; PRESETS</b>	220 16 17p		2N3704	10p	BC109	10p	BD136	37p
<b>ROTARY POTS</b>	220 16 17p		2N3705	10p	BC109C	12p	BD137	37p
<b>LOW NOISE</b>	470 16 22p	SCREENED	2N3706	10p	BC140	29p	BD140	38p
<b>5% TAPER</b>	470 16 22p	Single	2N3707	10p	BC141	29p	BD141	38p
<b>E3 SERIES</b>	470 16 22p	Mini Single 12p	2N3708	10p	BC142	29p	BD142	38p
<b>E3 SERIES</b>	470 16 22p	Mini Stereo 15p	2N3709	10p	BC143	30p	BD143	39p
<b>4K7 to 2M LIN</b>	1000 16 30p	4 Core Single	2N3710	10p	BC147	10p	BD239C	64p
<b>4K7 to 2M LOG</b>	1000 16 30p	Screen 54p	2N3712	2.00	BC147A	10p	BD240A	64p
<b>As above with DP Mains Switch</b>	2000 16 65p	BC Core 61p	2N3714	2.38	BC147C	10p	BD240C	73p
<b>As above with DP Mains Switch</b>	2000 16 65p	12 Core 80p	2N3715	3.31	BC148	10p	BD241	61p
<b>As above with DP Mains Switch</b>	2000 16 65p	Heavy Duty	2N3716	3.60	BC148A	12p	BD242C	65p
<b>As above with DP Mains Switch</b>	2000 16 65p	Mike Guard	2N3719	1.95	BC148C	12p	BD242C	70p
<b>As above with DP Mains Switch</b>	2000 16 65p	Lead 25p	2N3820	3.8p	BC149	10p	BD243A	82p
<b>As above with DP Mains Switch</b>	2000 16 65p	500R RG58 25p	2N3821	1.84	BC149B	10p	BD244C	82p
<b>As above with DP Mains Switch</b>	2000 16 65p	75Ω UHF 25p	2N3822	9.0p	BC152	39p	BC244C	10p
<b>As above with DP Mains Switch</b>	2000 16 65p	75Ω VHF 28p	2N3823	9.0p	BC153	23p	BD245C	13p
<b>As above with DP Mains Switch</b>	2000 16 65p	3000FD 14p	2N3824	1.70	BC154	27p	BD246C	15p
<b>As above with DP Mains Switch</b>	2000 16 65p	44 Core Single	2N3866	9.0p	BC154	27p	BD246C	15p
<b>As above with DP Mains Switch</b>	2000 16 65p	Prices per foot:	2N3903	13p	BC157A	13p	BC157B	13p
<b>As above with DP Mains Switch</b>	2000 16 65p	8 way 25p	2N3905	13p	BC158	13p	BD250C	24p
<b>As above with DP Mains Switch</b>	2000 16 65p	12 way 39p	2N3906	13p	BC158B	13p	BD250C	24p
<b>As above with DP Mains Switch</b>	2000 16 65p	20 way 48p	2N4030	75p	BC159	12p	BD437	88p
<b>As above with DP Mains Switch</b>	2000 16 65p	24 way 62p	2N4031	65p	BC159A	12p	BD438	88p
<b>As above with DP Mains Switch</b>	2000 16 65p	30 way 75p	2N4032	63p	BC159B	12p	BD439	88p
<b>As above with DP Mains Switch</b>	2000 16 65p	32 way 82p	2N4036	63p	BC192C	42p	BD440	91p
<b>As above with DP Mains Switch</b>	2000 16 65p	40 way 88p	2N4037	49p	BC160	42p	BD441	91p
<b>As above with DP Mains Switch</b>	2000 16 65p	64 way 149p	2N4240	30p	BC161	42p	BD442	93p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4400	15p	BC162	42p	BD443	93p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4401	30p	BC167A	13p	BD444	93p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4402	30p	BC167B	13p	BD445	93p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4403	30p	BC167C	13p	BD446	93p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4404	35p	BC168	10p	BD447	93p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4405	35p	BC168C	10p	BD448	93p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4416	1.00p	BC169	10p	BD449	93p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4427	1.00p	BC169B	10p	BD450	93p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4870	8.00p	BC169B	10p	BD451	93p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4871	8.00p	BC169C	10p	BD452	93p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4888	9.00p	BC177A	25p	BD675	72p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4901	1.69p	BC177A	25p	BD676	72p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4902	1.85p	BC177B	25p	BD677	72p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4903	1.85p	BC177C	25p	BD678	72p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4904	2.29p	BC178	25p	BD679	72p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4905	2.29p	BC178A	25p	BD680	72p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4906	2.75p	BC178B	25p	BD681	72p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4907	2.75p	BC178C	25p	BD682	72p
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4908	2.95p	BC179	20p	BD711	1.32
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4909	3.20p	BC179A	25p	BD712	1.32
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4910	3.20p	BC179B	25p	BD732	3.47
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4911	3.20p	BC179C	25p	BD733	3.47
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4912	3.20p	BC182	10p	BD754	1.70
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4913	3.20p	BC182A	10p	BD755	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4914	3.20p	BC182B	10p	BD756	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4915	3.20p	BC182C	10p	BD757	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4916	3.20p	BC182A	10p	BD758	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4917	3.20p	BC182B	10p	BD759	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4918	3.20p	BC182C	10p	BD760	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4919	3.20p	BC182A	10p	BD761	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4920	3.20p	BC182B	10p	BD762	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4921	3.20p	BC182C	10p	BD763	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4922	3.20p	BC182A	10p	BD764	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4923	3.20p	BC182B	10p	BD765	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4924	3.20p	BC182C	10p	BD766	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4925	3.20p	BC182A	10p	BD767	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4926	3.20p	BC182B	10p	BD768	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4927	3.20p	BC182C	10p	BD769	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4928	3.20p	BC182A	10p	BD770	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4929	3.20p	BC182B	10p	BD771	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4930	3.20p	BC182C	10p	BD772	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4931	3.20p	BC182A	10p	BD773	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4932	3.20p	BC182B	10p	BD774	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4933	3.20p	BC182C	10p	BD775	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4934	3.20p	BC182A	10p	BD776	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4935	3.20p	BC182B	10p	BD777	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4936	3.20p	BC182C	10p	BD778	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4937	3.20p	BC182A	10p	BD779	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4938	3.20p	BC182B	10p	BD780	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4939	3.20p	BC182C	10p	BD781	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4940	3.20p	BC182A	10p	BD782	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4941	3.20p	BC182B	10p	BD783	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4942	3.20p	BC182C	10p	BD784	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4943	3.20p	BC182A	10p	BD785	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4944	3.20p	BC182B	10p	BD786	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4945	3.20p	BC182C	10p	BD787	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4946	3.20p	BC182A	10p	BD788	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p		2N4947	3.20p	BC182B	10p	BD789	1.75
<b>As above with DP Mains Switch</b>	2000 16 65p							

# CHILTERN ELECTRONICS

## ★ SURPLUS EQUIPMENT SALE ★

### 9 inch VIDEO MONITORS

Once again we are able to offer these superb Motorola monitors at a fraction of the list price.

Mains and composite video input, ideal for any micro. High-resolution 80 column display, complete with circuit. Used but tested OK.

**£34** + VAT  
Carr. £6.50

### LAB. POWER SUPPLIES

Professional heavy duty power units from mainframe computers, beautifully made.

Outputs 5v 33a, ±12v 4a, ±15v 4a. Mains 240v input. Fully regulated and protected.

List price over £300. Used but fully tested.

**£34** + VAT  
Carr. £8.50

### DRI-30 DISK DRIVES (2.5Mb)

These famous disks are well known for their reliability and high engineering standards. Cartridges easily exchangeable, standard disk interface.

Untested but believed working OK.

Our price to clear **£120** + VAT  
Carr. £10

### MAINS FILTER UNITS (BRAND NEW SURPLUS)

These compact units consist of heavy duty 12amp filter and circuit breaker, and IEC socket. We also supply long mains lead with IEC plug. Ex-mainframe system, ideal for protecting TV/Micro etc.

(Cost £60 +!)

Our price **£6** + VAT  
or 2 for **£10** post free

### QUME DAISY-WHEEL PRINTERS

The Sprint-30 is the Rolls-Royce of daisy wheels, and originally cost £1.5K+. Ours are used but fully tested, with PSU for 230v. RS232 input, complete with full data. While stocks last.

**REDUCED TO CLEAR!**

**£250**  
Only **£350** + VAT  
Carr. £13  
Tractor feed option £25 extra

### ASCII KEYBOARDS

Scoop purchase allows us to offer a real professional keyboard (49-key ASCII), with Hall-effect keys and attractive case for a ridiculous price.

Circuits supplied. Used but tested. Cost £300+.

Only **£15** + VAT  
Carr. £1.85

### DEC PDP-11/03 COMPUTERS

We have a few surplus PDP 11/03's complete with box power supply, and LSI 11/1 Processor card. A real 16-bit computer that usually costs thousands of pounds. Not used but BRANDNEW.

**REDUCED TO CLEAR!**

**£270**  
at only **£320** + VAT  
Carr. £10

### ZENTEK VDU TERMINALS

Beautiful 8080 — controlled terminals that can also function as stand-alone micro. Large 14" screen, attractive case, detachable keyboard with numeric pad, 2 pages of 25 lines/80 char.

List £2K+. Ours our sold "as-is" but probably OK. With circuits.

Only **£99** + VAT  
Carr. £14.50

### MICRO-POWER SUPPLIES

Compact 5v 3amp regulated power supplies, mains input.

Used but tested OK.

Only **£11** + VAT  
Carr. £1.20

Also available 5v 6a version at **£16** + VAT Carr. £2.40

### COOLING FANS (230v)

Brand new surplus:- twin 4 inch whisper-quiet extractor fans, mounted on rack panel (19") with mains lead.

Ideal for cooling your micro; save £50 +

Our price **£11** + VAT  
Carr. £1.20

### TWIN-CASSETTE DRIVES

DEC TAIL twin digital cassette drives, intended for PDP11 but adaptable for use on micros.

Complete with circuits. As new.

Only **£99** + VAT  
Carr. £9

### RIBBON CABLES

40-way standard ribbon cable, 8 foot long, complete with two Berg connectors at either end.

In sets of three cables. As new.

Save £10 or more!

**£10** + VAT for 3  
Carr. £1

WE ALSO STOCK FULL RANGE OF DEC SYSTEMS AND SPARES, FROM PDP11/03 TO VAX 11/780. PLEASE PHONE FOR OUR DEC CATALOGUE.

HIGH STREET, CHALFONT ST. GILES, BUCKINGHAMSHIRE HP8 4QH TEL: 02407 71234  
Telephone or send your order to Gary Kent. We accept personal cheques or telephone your Access Card No.

All items despatched within 24 hours

WW - 052 FOR FURTHER DETAILS

# B. BAMBER ELECTRONICS

Rohde & Schwarz Enograph Type BN 18531, £60.  
 Rohde & Schwarz Sweep Signal Generator Type BN 4242/2, 50 kHz to 12 MHz, £85.  
 Rohde & Schwarz U.H.F. Signal Generator Type BN 41026, 1000 to 1900 MHz, £125.  
 Rohde & Schwarz Group Delay Measuring Equipment Indicator, £50.  
 Rohde & Schwarz Group Delay Measuring Equipment Modulator/Demodulator, £50.  
 Rohde & Schwarz Power Signal Generator Type BN 4105, 30 kHz to 300 MHz, £125.  
 Rohde & Schwarz U.H.F. Millivolt Meter Type BN 1091, 20mV to 10V, £50.  
 Airmec Modulation Meter Type 210, 3 to 300 MHz, £95.  
 Hewlett Packard S.H.F. Signal Generator Model 618 B, 3.8 to 7.6 GHz, £120.  
 Bryans X-Y Plotter Model 1806, £50.  
 Hewlett Packard Square Wave Generator Model 211 A, £60.  
 Solartron Pulse Generator Type GO 1005, £40.  
 Pye 12V Power Unit Type AC 15, £25.  
 Wandel Goltermann Carrier Frequency Level Meter, Type TFPM 76, £60.  
 Rohde & Schwarz Video Skop Type BN 4241, £250.  
 Schomantol Frequency Meter Type FD1, 30 to 900 MHz, £50.  
 Tektronix Delay Cable Type 113, £50.  
 Bruel & Kjoer Vibration Meter Type 2502, £50.  
 Advance Pulse Generator Type PG 54, £40.  
 Systron Donner L.F. Spectrum Analyzer Model 805, 200 Hz to 1.6 MHz, £550.  
 Ministry Oscilloscope Type CT 436 Dual Beam D.C. to 6 MHz, £85.  
 Marconi Signal Generator Type TF 995A/3/S (CT402), £95.  
 Marconi 100-Watt 7db Attenuator Type TM 5280, 150 to 185 MHz, £40.  
 Pye Aerial Tuner Unit Type ATU 4, 2 to 9 MHz, Pre-set, £15.  
 A.I.M. Electronics Pulse Generator with Clock Generator, £65.  
 Marconi V.H.F. Signal Generator Type TF 1064B/5M, £125.  
 Marconi Tx & Rx Output Test Set Type TF 1065, £85.  
 Marconi 1/4 Universal Bridge Type TF 1313, £220.  
 Tektronix L-C Meter Type 130, £65.  
 Heathkit Harmonic Distortion Meter Type 1M-12U, £20.  
 Marconi Sanders Microwave Sweep Generator Type 6600A, 10 to 15 GHz, £220.  
 Pye Vanguard Type AM 25 B, High Band Less Control Gear, £10.  
 Rohde & Schwarz Polyskop 11 Type BN 425/50, £350.  
 A.E.W. Process Cycling Oven, £600.  
 Twin Clothes Lockers, nests of 2 with keys, £20.  
 Louverd Lin Bin Panels, 4' 6" x 4' 6", £20.  
 Kodak Roll Film Drying Cabinet with Hangers, £150.  
 Potter Line Printer Type LP 3000, £150.

PDP-8/L Computer System, Dectape Units and Interface Unit, £650.  
 Digital Decwriter 11 Printer with keyboard, £100.  
 Rohde & Schwarz Z-g Diagraph Type BN 3562, 300 to 2400 MHz, £85.  
 Tektronix Rack Mount Oscilloscope Type RM 45, £50.  
 Marconi V.H.F. Alignment Oscilloscope Type TF 1104/1, £150.  
 Tektronix Sampling Oscilloscope Type 661 with 4S2 plug in, £120.  
 Avo Valve Tester Type CT160, £30.  
 Advance Oscilloscope Type OS25A, DC to 3 MHz, £120.  
 Tequipment Oscilloscope Type D43, DC to 10 MHz, £100.  
 Tequipment Oscilloscope Type S43, DC to 10 MHz, £85.  
 Tequipment Oscilloscope Type S51, £75.  
 Tequipment Oscilloscope Type S32A, DC to 3 MHz, £65.  
 Tektronix Rack Mount Oscilloscope RM17, DC to 10 MHz, £85.  
 Tektronix Oscilloscope Type 317, DC to 15 MHz, £120.  
 Marconi R.C. Oscilloscope Type TF1101, £65.  
 Airmec Millivolt Meter Type 301A, £75.  
 Advance Audio Generator Type H1, £20.  
 Tektronix Oscilloscope Type 543A with Type B plug in, £160.  
 Tektronix Oscilloscope Type 531A with Type H plug in, £160.  
 Pye Base Station Type F27, A.M. Low Band, £50.  
 Sander Oscillator Type CLC 2-4, 2 to 4.5 GHz, £95.  
 Bruel & Kjoer Microphone Amplifier Type 2604, £50.  
 Bruel & Kjoer Microphone Amplifier Type 2603, £50.  
 Labgear Compak 8 Transceiver less mike, aerial, etc., £50.  
 EMI Oscilloscope Wide Band Amplifier Type 7/1, £25.  
 Airmec Sweep Signal Generator Type 352, 20 Hz to 200 kHz, £45.  
 Belix Variable Power Unit, 0 to 50V at 2 amp, £40.  
 BTR Silvertown Anti-Static and Conductive Footwear Tester, £25.  
 Dawe True RMS Valve Voltmeter Type 612A, £20.  
 Rohde & Schwarz Power Signal Generator Type BN41001, 0.1 to 30 MHz, £75.  
 Marconi Distortion Factor Meter Type TF142F, £85.  
 Marconi A.M. Signal Generator Type TF144H/4S, £125.  
 Tektronix Time Mark Generator Type 180A, £125.  
 Marconi F.M. Signal Generator Type TF 1066B/1, £280.  
 Marconi F.M. Signal Generator Type TF 1066B/6, £300.  
 Marconi Carrier Deviation Meter Type TF 791 D, £95.  
 Airmec Modulation Meter Type 409, £120.  
 Marconi Universal Bridge Type TF 868, £50.  
 Marconi A.M./F.M. Signal Generator Type TF 995A/5, £230.  
 Marconi Vacuum Tube Voltmeter Type TF 1041 C, £25.  
 Marconi R.F. Power Meter Type TF 1020A/4, 300W, 75 ohm, £65.  
 Marconi R.F. Power Meter Type TF 1020A/1, 100W, 50 ohm, £65.

## PYE POCKETPHONE PF1 UHF RECEIVER

440-470 MHz, Single Channel, int. speaker and aerial. Supplied complete with rechargeable battery and service manual, £6 each plus £1 p.p. plus V.A.T.

## GARRARD CAR CASSETTE PLAYER MECHANISMS

12-Volt motor, stereo head, brand new, £2.50 each plus 50p p.p. plus V.A.T.

## BASF CHROMDIOXIDE VIDEO CASSETTE TAPE

for use with Philips N1500/1700 VCR. LVC30 + 5, 36min. long play, £5 each plus 50p p.p. plus V.A.T. 10 for £35 plus V.A.T. post paid.

## RADIOSONDE RS21 METEOROLOGICAL BALLOON TRANSMITTER

with Water Activated Battery, contains all-weather sensors, fully solid state, £5 each plus £1 p.p. plus V.A.T.

## CHARLES AUSTIN TWO-STAGE AIR PUMP

Type F65 DEH, complete with pressure regulator, 240 vac., chassis-mounted with hoses, etc., brand new and boxed, £45 plus £5 p.p. plus V.A.T.

P. & P. or Carriage and V.A.T. at 15% on total must be added to all orders. Callers very welcome, strictly between 9 a.m. and 1 p.m. and 2 and 5 p.m. Monday to Friday inc.

Barclaycard and Access taken


Official orders welcome ww27




5 STATION ROAD, LITTLEPORT, CAMBS CB6 1QE  
 PHONE: ELY (0353) 860185



WW - 057 FOR FURTHER DETAILS

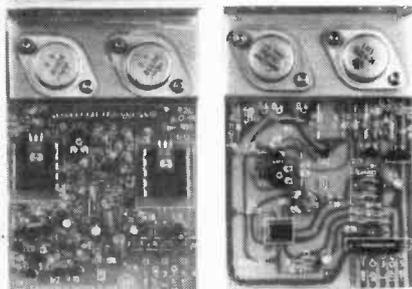

BI POLAR & FET POWER AMPLIFIERS

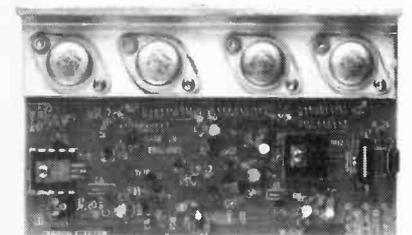

HEAVY DUTY POWER AMPLIFIERS

## CRIMSON AMPLIFICATION: First Choice of the Professionals!

Whatever your application, Crimson Modular Amplification provides a simple, efficient, and reliable solution. As many engineers in production, development and research will testify, when you need a particular amplifier you need to deal with a company who can answer your queries and supply a working unit quickly. - CRIMSON will do exactly that!

We supply a standard range of power amplifier modules (both Bipolar and Mosfet) which can be incorporated in most systems from recording studios to home hi-fi or for more difficult loads such as induction loop transmitters, vibrators, servos and line transformers. For really complex applications, our technical department can usually supply a dedicated module on request.

All modules are guaranteed for two years and offer outstanding performance and value. If you would like more details please return the coupon with a s.a.e.

### STANDARD MODULES

B I P O L A R	TYPE	MAX. O/P POWER	SUPPLY TYPE	VOLTAGE MAX.	THD TYP.	PRICE INC.
						V.A.T. & POST.
	CE 608	60W/8Ω	± 35	± 40	< .01%	£21.50
	CE 1004	100W/4Ω	± 35	± 40	< .018%	£25.00
	CE 1008	120W/8Ω	± 45	± 50	< .01%	£28.00
	CE 1704	200W/4Ω	± 45	± 63	< .015%	£35.50
	CE 1708	180W/8Ω	± 60	± 63	< .01%	£35.50
	CE 3004	320W/4Ω	± 60	± 63	< .02%	£49.50
M O S	FE 908	90W/8Ω	± 45	± 60	< .01%	£30.00
	FE 1704	170W/4Ω	± 45	± 60	< .025%	£39.00

All prices include V.A.T., Post and Packing (quantity discounts available).

To order send c.w.o. or quote Access/Mastercharge card no. All modules are available from Bradley Marshall Ltd., 325 Edgware Road, London. Export: Please write for a proforma.



**CRIMSON ELEKTRIK STROKE**  
 PHOENIX WORKS, 500 KING STREET, LONGTON  
 STROKE-ON-TRENT, STAFFS. - Tel: 0782 330520

Please send me details on -

- POWER AMPLIFIER MODULES
- HI FI KIT AMPLIFIERS
- 19IN. RACK MOUNTING P.A. AMPLIFIERS

I enclose a S.A.E.

Name .....

Address.....


.....WW/1/84

Send to: Crimson ElektriK Stoke, Phoenix Works, 500 King Street, Longton, Stoke-on-Trent.

# Until now, finding out about home computers was about as simple as

focusing your right eye here

and your left eye here.

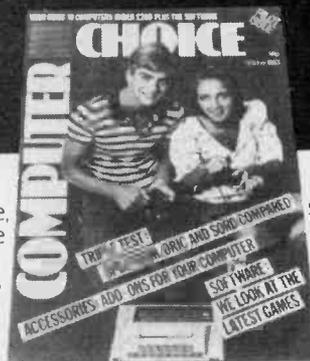

Mind boggling isn't it? But now there's Computer Choice, a new monthly magazine that gives you the facts and advice you need to choose your first home computer.

And when you've bought your computer it also helps you get the most out of it.

The first issue is out now for 60p and includes our

Special Buyer's Guide on micros under £200, a comparison of the Oric, Spectrum and Sord and a report on what Oric owners like and dislike about their computers and software.

As well as an article on how to learn Basic and reviews of all the latest games and software. Plus lots more to make choosing a computer easy. And owning one fun.



TRANSEL ODT MATRIX PRINTER Compact Serial Interface £30V. With info. £65 each  
 9 MDNITOR. Cased Non-Standard with info. £20 each  
 12" MONITOR. Cased Non-Standard with info. £15 each  
 AZTEC 20" Black & White Monitor. Video In £50 each  
 TV Style 20" MONITOR Black & White Video In £30 each  
 COSSOR VDU with KEYBOARD type CDD3000 12" Green Screen V24/20MA or TTL compatible with info. £55 each  
 CENTRONIC 704 ODT MATRIX PRINTER RS232C Upper & Lower case. Variable paper width. £250

- 1 TEKTRONIX475 Scope 200MHz. Dual Trace. Delay Sweep. £1600
- 2 TEKTRONIX 453 Scope 50MHz. Dual Trace. Delay Sweep. £1400
- 3 TEKTRONIX 647A Scope 100MHz. Dual Trace. Delay Sweep. £450
- 4 MARCONI TF2210 Scope 100MHz. Dual Trace. Dual TB Delay Sweep. £400
- 5 PHILIPS PM3234 Storage Scope with Memory 10MHz. Dual Trace. £500
- 6 TEKTRONIX 549 Storage Scope 30MHz. Dual Trace. Dual TB Delay Sweep. £400
- 7 TEKTRONIX 564B Storage Scope 10MHz. Dual Trace. Delay Sweep. £395
- 8 SOLARTRON CD1400 Scope 15MHz. Dual Beam. £90
- 9 COSSOR CDD150 Scope 35MHz. Dual Trace. Delay Sweep. £195
- 11 TELEQUIPMENT S43 Scope 25MHz. Single Beam. £65
- 12 B & K BEAT FREQUENCY OSCILLATOR type 1013 £225
- 13 B & K RANDOM NOISE GENERATOR type 1402 £125
- 14 B & K ELECTRONIC VOLTMETER type 2409 2Hz-200kHz. £50
- 15 MARCONI SIG GEN TF144H 5 10kHz-72MHz. £125
- 16 MARCONI WIDE RANGE OSC TF1370A 10Hz-10MHz. Sine/Square to 100kHz. £95
- 17 MARCONI FM AM SIG GEN TF959A/3S 15-220MHz. AM/FM Mod. £150
- 18 MARCONI R F POWER METER TF1020A 1 50 ohm. £75
- 19 MARCONI SIG GEN TF106D/2 450-1200MHz. Late style. £150
- 20 MARCONI R F POWER METER TF1152 Range 50 ohm. £50
- 21 MARCONI SIG GEN TF2002A S AM/FM 10kHz-72MHz. £475
- 22 MARCONI SIG GEN TF2002 As above. AM only. £250
- 23 MARCONI POWER METER TF834 20Hz-35kHz. £50
- 24 MARCONI UNIVERSAL BRIDGE TF688. £50
- 25 MARCONI SENSITIVE VALVE VOLTMETER TF2600 10Hz-10MHz 1mV-300V. £75
- 26 HEWLETT PACKARD DVM 3440A with Automatic Range Selector 3442A. £150
- 27 H P VHF SIG GEN 608C 10-480MHz. £150
- 28 H.P. CALCULATOR PLOTTER 9125A with Extended Memory 9101A and Cal Buffer 9102A. £250
- 30 FLANN MICROWAVE SIGNAL SOURCE type PCLS 1-4GHz. £195

- 31 FLANN SIGNAL GEN type 501 P S. 0.575-3GHz. £175
- 32 BRADLEY OSCILLOSCOPE CALIBRATOR type 156. £135
- 33 ELLIOT TRANSISTOR CURVE DISPLAY type 6106. £150
- 34 FENLOW SPECTRUM ANALYSER SA4 0.3Hz-25kHz with Plotter P4. £195
- 36 ADVANCE AM/FM SIG GEN S663F 4-230MHz. £125
- 38 ADVANCE SIG GEN S662B 150kHz-230MHz. CW Mod. £60
- 39 ADVANCE SIG GEN E2 100kHz-100MHz. CW/Mod. £40
- 40 WAYNE KERR UNIVERSAL BRIDGE CT530 (B221A) with LOW IMPEDANCE ADAPTOR DZ21A. £125
- 41 WAYNE KERR SIG GEN type S121 10Hz-120kHz. £40
- 42 BRYANS X-Y RECORDER type 24000 A3 size. With manual. £150
- 43 CALCOMP PLOTTER Model 565 Step size 1mm 12" Barrel. With manual. £175
- 44 TEKTRONIX TIME MARK GENERATOR type 184. £120
- 45 TEKTRONIX SQUARE WAVE GEN type 105. £20
- 46 AVO TRANSISTOR TESTER type TT169 with leads (P&P E2). £20
- 47 AVO VALVE TESTER type CT160 22 Valve bases. £20
- 48 FOSTER INSTRUMENTS PORTABLE POT Model 3156E. £45
- 50 BRANDENBURG POWER SUPPLY Model 374SEL 1kV. £50
- 51 MUIRHEAD K134-A WAVE ANALYSER 3Hz-300kHz. £75
- 52 AIRMEC WAVE ANALYSER type 248. 5-300MHz. £75
- 53 TEKTRONIX TIME MARK GEN type 180A. £40
- 54 ROBAND TRANSISTORISED P.U. type TSV/30/2 Metered 0H-30V. 0-2A. £40
- 55 CROPCO RESISTANCE BRIDGE SMITH No 3. £60
- 56 TINSLEY VERNIER POTENTIOMETER type 4363. £35
- 57 PYE PRECISION VERNIER POT Cat No 7568. £30
- 58 ADVANCE STAB HT-LT SUPPLY type P.P.1 Metered Scaled 0-500V-0-50mA. 0-1000V-0-250V. 0-600V. 0-200V. £50
- 59 MARCONI DOUBLE PULSE GEN TF1400S with TM6600 S 10Hz-100kHz 100 nsecs-100 uSecs. £30
- 60 MARCONI TF109F/ SWEEP GEN 20 MHz. £25
- 61 AIRMEC MILLIVOLTMETER type 264A 20Hz-10MHz. £20
- 62 VARIAC 8 amp. Case 0-270Volts. £25
- 63 AUTO TRANSFORMER 1000VA Brand New. £15
- 64 TELEQUIPMENT S54A Scope 10MHz. Single Beam. Solid State. £110
- 65 AIRMEC Sig Gen type 204 1-320MHz AM/FM Mod. £90
- 66 FARNELL STAB P.U. TSV30/5C. 30V 5A. £60
- 67 ROBAND TRANSISTORISED P.U. T139 Twin 50V 5A. £60
- 68 MARCONI CIRCUIT MAGNIFICATION METER TF1245 with TF1246. £300

**EXECUTIVE TELEPHONES - PUSH BUTTON**  
 Many functions including 10 number memory, repeat dialling, etc. Will connect to GPO System. Brand New £25 each. P&P £4.  
**EQUIPMENT IN WORKING ORDER**  
 Please check availability before ordering. Carriage all units £7. VAT to be added to total of Goods and Carriage. S.A.E. for LISTS.

**STEWART OF READING**  
**110 WYKEHAM ROAD, READING, BERKS RG6 1PL**  
**Telephone: 0734 68041**  
 Callers welcome 9 a.m. to 5.30 p.m. Monday to Saturday inclusive  
**WW - 039 FOR FURTHER DETAILS**

**SALE\* P.&R. COMPUTER SHOP SALE\***  
**IBM GOLFBALL PRINTERS from £70 EACH + V.A.T.**  
 INTERFACE FOR IBM GOLFBALL £40 + V.A.T.  
 \*BRAND-NEW LA36 DEC WRITERS - SALE £200 EACH + V.A.T.  
 CENTRONIC 779 PRINTERS - £325 + V.A.T.  
 CENTRONIC 781 PRINTER - £350 + V.A.T.  
 POWER UNITS, 5-VOLT 6-AMP - £20 EACH  
 FANS, PCBs, KEYBOARDS AND LOTS MORE  
 8-INCH IBM FLOPPY DISC DRIVES.  
**COME AND LOOK AROUND**  
**SALCOTT MILL, GOLDHANGER ROAD**  
**HEYBRIDGE, MALDON, ESSEX**  
**PHONE MALDON (0621) 57440**  
**WW - 045 FOR FURTHER DETAILS**

**EASIBINDERS Quick, neat and easy!**  
 It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold six issues and is attractively bound and blocked with the WIRELESS WORLD logo. Price U.K. £4.30 including postage, packing and V.A.T. Overseas orders add 35p per binder. Nat. Giro No. 5157552. Please allow 3/4 weeks for fulfillment of order. Payment by ACCESS/BARCLAYCARD/VISA. Send coupon below detailing credit card no. and signature. Why not place your order now? Send the completed coupon below with remittance payable to: **Easibind, 42 Hoxton Square, London N1 6NS**

**Order Form WIRELESS WORLD**  
 I enclose P.O./cheque value ..... for ..... binders  
 Years required .....  
**BLOCK LETTERS PLEASE**  
 Name .....  
 Address .....  
 Date ..... Registration No. 735718

**PM COMPONENTS LTD**  
**VALVE & COMPONENTS SPECIALISTS**

**INTEGRATED CIRCUITS**

AN124 2.50	MC1358 1.58	TA7120P 1.65	TBA641A12 2.50	TDA2523 1.95
AN214Q 2.50	MC1495 3.00	TA7130P 1.50	TBA641B1X1 3.00	TDA2524 1.95
AN240P 2.80	MC1496 1.25	TA7146 2.95	TBA651 1.75	TDA2530 1.95
AN612 2.15	MC14011BCP 0.32	TA7203 2.95	TBA651R 2.50	TDA2532 1.95
AN7140 3.50	MC145106P 7.95	TA7204P 2.15	TBA720A 2.45	TDA2540 1.25
AN7145 3.50	MC1723 0.75	TA7205AP 1.50	TBA750Q 2.65	TDA2541 2.15
AN7150 2.95	MC3357 2.50	TA7222AP 1.80	TBA800 0.89	TDA2561 2.35
BA521 3.35	MC1732 0.75	TA7227P 4.25	TBA810AS 1.65	TDA2593 2.50
CA3352E 1.75	MC2357 2.50	TA7310P 1.80	TBA810P 1.65	TDA2600 5.50
CA3086 2.46	ML231B 1.75	TA7313AP 2.95	TBA820M 0.75	TDA2610 2.50
ETT6016 0.50	ML232B 2.50	TA7321P 2.25	TBA820Q 1.45	TDA2611A 1.95
HA 1377 3.50	MSM5807 6.75	TA7609P 3.15	TBA890 2.50	TDA2620 2.60
HA1165W 1.50	PL102A 5.75	TA7611AP 2.95	TBA920 1.65	TDA2680A 2.75
HA1551 2.95	SAAS00A 5.50	TAAS50 0.25	TBA920Q 1.65	TDA2690 2.45
LA1230 1.15	SAA1025 7.25	TAAS70 1.95	TBA950/2X 2.95	TDA3560 3.95
LA4102 2.95	SAAS010 6.35	TAA621AX1 3.50	TBA970 2.35	UPC5666H 2.95
LA4250 2.95	SA5560S 1.75	TAA661B 1.20	TBA990 1.49	UPC5752C 2.75
LA4400 4.15	SA5570S 1.75	TA7A70 1.70	TBA990Q 1.49	UPC1025H 2.50
LA4422 2.50	SAS580 2.95	TBA120B 0.95	TCA270 1.10	UPC1028H 1.50
LC7120 3.25	SL901B 4.85	TBA120C 1.15	TCA270U 1.10	UPC1032H 1.50
LC7130 3.50	SL917B 6.65	TBA120T 1.05	TCAS60 2.50	UPC1156H 2.75
LC7131 5.50	SL1327 1.10	TBA120T 1.00	TCA800 2.15	UPC1167C 2.50
LC7137 5.50	SL1327 1.10	TBA231 1.25	TCA940 1.65	UPC1181H 1.15
LM324N 0.45	SN7610N 1.25	TBA395 1.50	TDA1001 1.95	UPC1181H 1.25
LM380N 0.95	SN7603N 1.95	TBA396 0.75	TDA1001 1.95	UPC1282H 2.95
LM388T 0.95	SN7603N 1.95	TBA400N 1.25	TDA1004A 2.50	UPC1185H 1.95
M51513L 2.30	SN76033N 1.95	TBA510 2.50	TDA1006A 2.50	UPC1191V 1.50
M51515L 2.95	SN76110N 0.85	TBA510Q 2.50	TDA1010 2.15	UPC1360C 2.95
M51521L 1.50	SN7615N 1.25	TBA510Q 2.50	TDA1035 2.50	UPC1353C 2.45
MB3712 2.00	SN7655N 1.15	TBA520Q 1.10	TDA1170 1.95	UPC1365C 3.95
MC1307R 3.00	SN7626N 1.55	TBA530 1.10	TDA1170S 1.95	UPC2002H 1.95
MC1307P 1.50	SN7627N 1.05	TBA530Q 1.10	TDA1190 2.15	555 0.35
MC1327 0.95	SN76533N 1.65	TBA540 1.25	TDA1270C 3.95	556 0.42
MC1327Q 0.75	SN76544N 1.95	TBA540Q 1.35	TDA1327 1.70	723 0.50
MC1349P 1.20	SN76570N 1.80	TBA550C 1.45	TDA2002 1.95	747 0.50
MC1350P 0.95	SN7660N 0.80	TBA560C 1.45	TDA2020 2.45	748 0.35
MC1351P 1.25	TA7061AP 3.95	TBA560C 1.45	TDA2532 1.95	7805 0.60
MC1352P 1.25	TA7108P 1.00	TBA570 1.00		

**SEMICONDUCTORS**

AA12 0.25	BC173B 0.10	BD166 0.55	BF362 0.38	R2008B 1.70
AC126 0.22	BC174 0.09	BD179 0.72	BF363 0.38	R2010B 1.70
AC127 0.20	BC174A 0.09	BD182 0.70	BF371 0.20	R2322 0.58
AC128 0.28	BC177 0.15	BD202 0.65	BF394 0.19	R2323 0.66
AC128K 0.32	BC180 0.10	BD203 0.78	BF422 0.32	R2450 2.48
AC141K 0.34	BC182 0.10	BD204 0.70	BF438 0.36	RC1633A 0.90
AC142K 0.30	BC182BL 0.10	BD222 0.46	BF459 0.36	SKESF 1.45
AC176 0.22	BC183 0.10	BD223 0.48	BF595 0.23	TIP29 0.40
AC176K 0.31	BC183L 0.09	BD225 0.48	BF597 0.25	TIP29C 0.42
AC178 0.28	BC184BL 0.09	BD232 0.35	BF639 0.23	TIP30C 0.42
AC181P 0.28	BC184BL 0.09	BD233 0.35	BF642 0.32	TIP31C 0.42
AC187K 0.25	BC207B 0.13	BD234 0.35	BF643 0.28	TIP32C 0.42
AC187K 0.25	BC208B 0.13	BD236 0.45	BF681 0.25	TIP33B 0.75
AC188 0.28	BC212 0.09	BD237 0.40	BF688 0.30	TIP34B 0.75
AC188K 0.37	BC212L 0.09	BD238 0.40	BF690 1.50	TIP34H 0.45
AD142 0.79	BC212LA 0.09	BD241 0.40	BF691 1.75	TIP41C 0.45
AD143 0.82	BC213 0.09	BD242 0.60	BF702 1.25	TIP42 0.35
AD149 0.70	BC213L 0.09	BD246 0.60	BF743 0.28	TIP47 0.65
AD161 0.39	BC214 0.09	BD247 0.32	BF792 0.85	TIP120 0.60
AD161/2 0.90	BC214C 0.09	BD248 0.55	BF793 0.25	TIP125 0.65
AF114 0.20	BC214L 0.09	BD249 0.55	BF794 0.26	TIP142 1.75
AF124 0.34	BC217 0.10	BD250 0.65	BF795 0.50	TIP146 2.75
AF125 0.35	BC237A 0.09	BD251 0.65	BF796 0.30	TIP161 2.95
AF125 0.32	BC237B 0.09	BD252 0.65	BF797 0.25	TIP295 0.85
AF126 0.32	BC238 0.09	BD253 0.65	BF800 0.21	TIP305 0.50
AF127 0.32	BC239 0.12	BD254 0.65	BF801 0.21	TIP305 0.50
AF139 0.40	BC251A 0.12	BD255 0.65	BF802 0.21	TIP305 0.50
AF178 0.25	BC252 0.12	BD256 0.65	BF803 0.21	TIP305 0.50
AF238 0.42	BC258 0.25	BD257 0.65	BF804 0.21	TIP305 0.50
AU106 2.00	BC258A 0.39	BD258 0.65	BF805 0.21	TIP305 0.50
AU107 1.75	BC284 0.30	BD259 0.65	BF806 0.21	TIP305 0.50
AU110 2.00	BC300 0.30	BD260 0.65	BF807 0.21	TIP305 0.50
AU113 2.95	BC301 0.30	BD261 0.65	BF808 0.21	TIP305 0.50
BC107A 0.11	BC303 0.26	BD262 0.65	BF809 0.21	TIP305 0.50
BC107B 0.11	BC307 0.09	BD263 0.65	BF810 0.21	TIP305 0.50
BC108 0.10	BC307A 0.09	BD264 0.65	BF811 0.21	TIP305 0.50
BC108A 0.11	BC307B 0.09	BD265 0.65	BF812 0.21	TIP305 0.50
BC108B 0.12	BC327 0.10	BD266 0.65	BF813 0.21	TIP305 0.50
BC108C 0.10	BC329 0.09	BD267 0.65	BF814 0.21	TIP305 0.50
BC108D 0.12	BC331 0.10	BD268 0.65	BF815 0.21	TIP305 0.50
BC109 0.12	BC338 0.09	BD269 0.65	BF816 0.21	TIP305 0.50
BC109C 0.10	BC347A 0.13	BD270 0.65	BF817 0.21	TIP305 0.50
BC114 0.11	BC461 0.35	BD271 0.65	BF818 0.21	TIP305 0.50
BC116A 0.15	BC478 0.20	BD272 0.65	BF819 0.21	TIP305 0.50
BC117 0.19	BC527 0.20	BD273 0.65	BF820 0.21	TIP305 0.50
BC119 0.24	BC547 0.10	BD274 0.65	BF821 0.21	TIP305 0.50
BC125 0.25	BC548 0.10	BD275 0.65	BF822 0.21	TIP305 0.50
BC139 0.20	BC549A 0.08	BD276 0.65	BF823 0.21	TIP305 0.50
BC140 0.31	BC550 0.08	BD277 0.65	BF824 0.21	TIP305 0.50
BC141 0.25	BC557 0.08	BD278 0.65	BF825 0.21	TIP305 0.50
BC142 0.21	BC557A 0.08	BD279 0.65	BF826 0.21	TIP305 0.50
BC143 0.24	BC557B 0.08	BD280 0.65	BF827 0.21	TIP305 0.50
BC147 0.09	BC558 0.10	BD281 0.65	BF828 0.21	TIP305 0.50
BC147B 0.09	BCY33A 1.60	BD282 0.65	BF829 0.21	TIP305 0.50
BC148A 0.09	BD115 0.30	BD283 0.65	BF830 0.21	TIP305 0.50
BC148B 0.09	BD116 0.60	BD284 0.65	BF831 0.21	TIP305 0.50
BC149 0.09	BD131 0.32	BD285 0.65	BF832 0.21	TIP305 0.50
BC157 0.12	BD132 0.35	BD286 0.65	BF833 0.21	TIP305 0.50
BC158 0.09	BD133 0.40	BD287 0.65	BF834 0.21	TIP305 0.50
BC159 0.09	BD135 0.30	BD288 0.65	BF835 0.21	TIP305 0.50
BC160 0.28	BD136 0.30	BD289 0.65	BF836 0.21	TIP305 0.50
BC161 0.28	BD137 0.32	BD290 0.65	BF837 0.21	TIP305 0.50
BC170B 0.15	BD139 0.32	BD291 0.65	BF838 0.21	TIP305 0.50
BC171 0.09	BD140 0.30	BD292 0.65	BF839 0.21	TIP305 0.50
BC172 0.10	BD141 1.10	BD293 0.65	BF840 0.21	TIP305 0.50
BC171B 0.10	BD144 1.10	BD294 0.65	BF841 0.21	TIP305 0.50
BC172 0.10	BD159 0.65			

PHONE  
0474 813225  
3 LINES

# P. M. COMPONENTS LTD

SELECTRON HOUSE, WROTHAM ROAD  
MEOPHAM GREEN, MEOPHAM, KENT DA130QY

TELEX  
966371  
PM COMP



## A SELECTION FROM OUR STOCK OF BRANDED VALVES

A1714	18.50	EAF42	1.20	EF732	1.80
A1998	11.50	EAF801	1.40	EF800	11.00
A2087	11.50	EA34	1.50	EF805	1.50
A2134	14.95	EB41	3.00	EF805S	13.50
A2293	6.50	EB91	0.52	EF806S	14.50
A2521	21.00	EBF33	2.50	EF812	0.65
A2599	37.50	EBC41	1.95	EF1200	1.50
A2900	11.50	EBC81	0.95	EH90	0.72
A3042	24.00	EBC90	0.75	EK90	0.72
A3283	24.00	EBC91	0.75	EL32	0.95
AC/HL/DO 4.00		EBF33	2.50	EL33	5.00
AC/THI	4.00	EBF80	0.50	EL34	2.25
ACT22	59.75	EBF80	0.50	EL34 Philips	
AC/VP2	4.00	EBF83	0.50	EL36	3.15
AC/S2 PEN 8.50		EBF89	0.95	EL37	9.00
AH221	39.00	EBF93	0.95	EL38	6.00
AH238	39.00	EBL1	2.50	EL41	3.50
AL80	6.00	EBL21	2.00	EL42	2.00
ARP12	0.70	EC070	0.75	EL81	6.95
ARP34	1.25	EC80	4.25	EL84	0.75
ARP35	2.00	EC81	4.50	EL85	4.50
BL63	2.00	EC86	1.00	EL86	0.85
BS450	67.00	EC90	1.10	EL90	1.20
BS810	55.00	EC92	1.25	EL91	6.00
BS814	55.00	EC93	0.80	EL93	12.15
CK	16.00	EC95	7.00	EL183E	3.50
C3JA	16.00	EC97	1.10	EL183P	3.50
C110	55.00	EC98	1.10	EL360	7.95
C1134	32.00	EC99	1.10	EL500	1.40
C1148A	115.00	EC99	1.10	EL504	1.40
C1149/1130.00		EC99	1.10	EL509	5.25
C1150/1135.00		EC99	1.10	EL519	6.95
C1534	32.00	EC99	1.10	EL802	3.85
CCA	2.80	EC99	1.10	EL821	8.50
CC3	2.00	EC99	1.10	EL822	12.95
CC33	2.00	EC99	1.10	EL822 Brimar/ Mullard	1.35
Cv Nos Prices on request		EC99	1.10	EM4	9.00
D63	1.20	EC99	1.10	EM35	1.50
DAF91	0.45	EC99	1.10	EM80	0.70
DAF96	0.85	EC99	1.10	EM81	0.70
DC70	1.75	EC99	1.10	EM84	1.65
DC90	1.20	EC99	1.10	EM85	1.50
DCX4-1000	12.00	EC99	1.10	EM87	2.50
DCX4-5000	25.00	EC99	1.10	EM89	1.00
DET22	28.00	EC99	1.10	EN32	13.50
DET24	39.00	EC99	1.10	EN32	13.50
DET25	22.00	EC99	1.10	EN32	13.50
DF91	0.70	EC99	1.10	EN32	13.50
DF92	0.60	EC99	1.10	EN32	13.50
DF96	0.65	EC99	1.10	EN32	13.50
DF97	1.00	EC99	1.10	EN32	13.50
DH63	1.20	EC99	1.10	EN32	13.50
DH77	0.90	EC99	1.10	EN32	13.50
DH79	0.56	EC99	1.10	EN32	13.50
DH149	2.00	EC99	1.10	EN32	13.50
DK91	0.90	EC99	1.10	EN32	13.50
DK92	1.20	EC99	1.10	EN32	13.50
DK96	2.50	EC99	1.10	EN32	13.50
DL35	2.50	EC99	1.10	EN32	13.50
DL63	1.00	EC99	1.10	EN32	13.50
DL70	2.50	EC99	1.10	EN32	13.50
DL73	2.50	EC99	1.10	EN32	13.50
DL91	1.50	EC99	1.10	EN32	13.50
DL92	0.60	EC99	1.10	EN32	13.50
DL93	1.10	EC99	1.10	EN32	13.50
DL94	2.50	EC99	1.10	EN32	13.50
DL96	2.50	EC99	1.10	EN32	13.50
DL97	1.50	EC99	1.10	EN32	13.50
DL98	0.60	EC99	1.10	EN32	13.50
DL99	0.60	EC99	1.10	EN32	13.50
DM160	1.10	EC99	1.10	EN32	13.50
DY51	1.00	EC99	1.10	EN32	13.50
DY86/87	0.65	EC99	1.10	EN32	13.50
DY802	0.72	EC99	1.10	EN32	13.50
E80CC	7.00	EC99	1.10	EN32	13.50
E80CC	10.00	EC99	1.10	EN32	13.50
E80F	13.50	EC99	1.10	EN32	13.50
E80L	11.50	EC99	1.10	EN32	13.50
E81CC	3.50	EC99	1.10	EN32	13.50
E81L	12.00	EC99	1.10	EN32	13.50
E82CC	3.50	EC99	1.10	EN32	13.50
E83F	5.50	EC99	1.10	EN32	13.50
E86C	9.50	EC99	1.10	EN32	13.50
E88C	7.95	EC99	1.10	EN32	13.50
E88CC	2.60	EC99	1.10	EN32	13.50
E89CC	5.00	EC99	1.10	EN32	13.50
E90F	7.95	EC99	1.10	EN32	13.50
E91H	4.50	EC99	1.10	EN32	13.50
E92CC	2.25	EC99	1.10	EN32	13.50
E99F	6.95	EC99	1.10	EN32	13.50
E130L	19.95	EC99	1.10	EN32	13.50
E180CC	6.50	EC99	1.10	EN32	13.50
E182CC	9.00	EC99	1.10	EN32	13.50
E180F	6.50	EC99	1.10	EN32	13.50
E186F	8.50	EC99	1.10	EN32	13.50
E280F	19.50	EC99	1.10	EN32	13.50
E283CC	13.50	EC99	1.10	EN32	13.50
E288CC	13.50	EC99	1.10	EN32	13.50
E810F	16.00	EC99	1.10	EN32	13.50
E1148	1.00	EC99	1.10	EN32	13.50
E1524	6.95	EC99	1.10	EN32	13.50
EA50	1.00	EC99	1.10	EN32	13.50
EA76	1.95	EC99	1.10	EN32	13.50
EA79	1.95	EC99	1.10	EN32	13.50
EA91	0.80	EC99	1.10	EN32	13.50
EAB80	0.60	EC99	1.10	EN32	13.50
EAC91	2.50	EC99	1.10	EN32	13.50

HK90	1.05	PCL200	1.50	RK2K25	62.50
HL2K	3.50	PCL200	1.50	RK4-1000	10.00
HL23DD	4.00	PCL800	0.80	RK-20A	12.00
HL41	3.50	PCL805	0.90	RL16	1.50
HL41DD	3.50	PDS50	3.50	RP16	12.00
HL42DD	3.50	PDS10	3.65	RPY13	2.50
HL90	0.70	PEN4DD	2.00	RPY43	2.50
HL133/DD	3.50	PEN4DD	2.00	RPY82	2.50
HR2	4.00	PEN45	3.00	RR3-1250	65.00
HY90	1.00	PEN45DD	3.00	RS613	45.00
HYR2	3.00	PEN46	2.00	RSE85	54.95
HL32	85.00	PFL200	1.25	RSE88	52.15
KR8/3	5.00	PL12	1.25	SF17	5.95
KT8C	7.00	PL33	1.25	SG33	28.95
KT33C	3.50	PL36	0.95	S1E12	38.00
KT36	2.00	PL38	1.50	S30/2K	12.00
KT44	4.00	PL81	0.72	S104/1K	10.00
KT45	4.00	PL81A	0.72	S109/1K	15.00
KT63	2.00	PL82	0.60	S130	5.95
KT66 USA	7.15	PL83	0.52	S130P	5.95
KT66 GEC14.95		PL84	0.65	SC1/800	5.00
KT77 Gold Line		PL88	1.00	SC1/1200	5.00
KT81	9.50	PL92	1.75	SC1/2000	9.00
KT88 USA	8.00	PL92	1.00	SP2	1.50
KT88 Gold Line		PL95	0.95	SP42	3.00
KT89	15.95	PL95A	0.95	ST11	1.50
KTW61	2.00	PL95B	1.95	STV280/40	
KTW62	2.00	PL95C	4.85	Y1060	265.00
KTW63	2.00	PL95D	4.85	Y1070	29.00
KTW63	2.00	PL95E	4.85	Y1100	115.00
L63	1.20	PL95F	4.85	Y1170	109.00
L102/2K	6.95	PL95G	4.85	Y1270	8.50
L120/2K	12.00	PL95H	4.85	Y1370	8.50
M502A	96.00	PL95I	4.85	Z77	1.20
M537A	95.00	PL95J	4.85	Z302C	12.00
M514	155.00	PL95K	4.85	Z303C	9.00
M8079	6.00	PL95L	4.85	Z5055	15.00
M8079	6.00	PL95M	4.85	Z520M	4.00
M8082	7.50	PL95N	4.85	Z521M	8.00
M8083	3.25	PL95O	4.85	Z700U	3.00
M8091	7.50	PL95P	4.85	Z749	0.60
M8096	3.00	PL95Q	4.85	Z759	19.85
M8098	5.50	PL95R	4.85	Z800U	3.00
M8099	5.00	PL95S	4.85	Z801U	3.00
M8100	5.50	PL95T	4.85	Z803U	18.95
M8136	7.00	PL95U	4.85	Z804U	12.50
M8137	5.50	PL95V	4.85	Z805U	12.50
M8161	6.50	PL95W	4.85	Z806U	12.50
M8162	6.50	PL95X	4.85	Z807U	12.50
M8163	5.50	PL95Y	4.85	Z808U	12.50
M8190	4.50	PL95Z	4.85	Z809U	12.50
M8195	6.50	PL96	4.85	Z810U	12.50
M8196	5.50	PL97	4.85	Z811U	12.50
M8204	5.50	PL98	4.85	Z812U	12.50
M8205	5.50	PL99	4.85	Z813U	12.50
M8224	2.00	PL100	4.85	Z814U	12.50
M8225	3.50	PL101	4.85	Z815U	12.50
M8226	3.50	PL102	4.85	Z816U	12.50
M8227	3.50	PL103	4.85	Z817U	12.50
M8228	3.50	PL104	4.85	Z818U	12.50
M8229	3.50	PL105	4.85	Z819U	12.50
M8230	3.50	PL106	4.85	Z820U	12.50
M8231	3.50	PL107	4.85	Z821U	12.50
M8232	3.50	PL108	4.85	Z822U	12.50
M8233	3.50	PL109	4.85	Z823U	12.50
M8234	3.50	PL110	4.85	Z824U	12.50
M8235	3.50	PL111	4.85	Z825U	12.50
M8236	3.50	PL112	4.85	Z826U	12.50
M8237	3.50	PL113	4.85	Z827U	12.50
M8238	3.50	PL114	4.85	Z828U	12.50
M8239	3.50	PL115	4.85	Z829U	12.50
M8240	3.50	PL116	4.85	Z830U	12.50
M8241	3.50	PL117	4.85	Z831U	12.50
M8242	3.50	PL118	4.85	Z832U	12.50
M8243	3.50	PL119	4.85	Z833U	12.50
M8244	3.50	PL120	4.85	Z834U	12.50
M8245	3.50	PL121	4.85	Z835U	12.50
M8246	3.50	PL122	4.85	Z836U	12.50
M8247	3.50	PL123	4.85	Z837U	12.50
M8248	3.50	PL124	4.85	Z838U	12.50
M8249	3.50	PL125	4.85	Z839U	12.50
M8250	3.50	PL126	4.85	Z840U	12.50
M8251	3.50	PL127	4.85	Z841U	12.50
M8252	3.50	PL128	4.85	Z842U	12.50
M8253	3.50	PL129	4.85	Z843U	12.50
M8254	3.50	PL130	4.85	Z844U	12.50
M8255	3.50	PL131	4.85	Z845U	12.50
M8256	3.50	PL132	4.85	Z846U	12.50
M8257	3.50	PL133	4.85	Z847U	12.50
M8258	3.50	PL134	4.85	Z848U	12.50
M8259	3.50	PL135	4.85	Z849U	12.50
M8260	3.50	PL136	4.85	Z850U	12.50
M8261	3.50	PL137	4.85	Z851U	12.50
M8262	3.50	PL138	4.85	Z852U	12.50
M8263	3.50	PL139	4.85	Z853U	12.50
M8264	3.50	PL140	4.85	Z854U	12.50
M8265	3.50	PL141	4.85	Z855U	12.50
M8266	3.50	PL142	4.85	Z856U	12.50
M8267	3.50</				

# COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

## THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

### HARD DISK DRIVES

Fully refurbished DIABLO/DRE series 30 2.5 Mb disk drives. DEC RK05, NOVA, TEXAS compatible.  
Front load. Free stand or rack mount £550.00  
Exchangeable type (via lid removal) £295.00  
me3026 PSU unit for 2 drives £125.00  
DIABLO/DRE 44-4000A/B 5+5 ex stock from 1000's of spares for S30, 4000, 3200, HAWK ex stock. £995.00  
Plus in house repair, refurbishing service. Call for details or quotation.

### CALCOMP PLOTTERS

936 3 colour digital incremental, 37" drum, parallel interface and accessories £2,500.00  
718 4 colour digital 8 x 5 FEET flat bed & controller (cost 25,000) 1 only at £1,950.00  
Viewing by appointment.

### COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.  
ETRI 99XUOI Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. £9.95.  
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. NEW £6.95  
BUHLER 09.11.22. 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. OUR PRICE ONLY £12.95 complete with data.  
MUFFIN-CENTAU standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or BRAND NEW 240 v at £10.50. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans £1.60

### HOT LINE DATA BASE

## DISTEL ©

THE ORIGINAL FREE OF CHARGE dial up data base. 1000's of stock items and one off bargains.  
ON LINE NOW - 300 baud, full duplex CCITT tones, 8 bit word, no parity.  
01-679 1888

### MAINS FILTERS

Cure those unnerfing hang ups and data glitches caused by mains interference.  
SD5A As recommended by ZX81 news letter, matchbox size up to 1000 watt load £5.95  
L2127 compact completely cased unit with 3 pin fitted socket. Up to 750 watts £9.99

### COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on Ali front panel, rear cable entries, etc. etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. Give your system that professional finish for only £49.95 + Carr. Dim. 19" wide 16" deep 10.5" high. Useable area 16" w 10.5" h 11.5" d. Also available LESS PSU, with FANS etc. Internal dim. 19" w. 16" d. 10.5" h. £19.95. Carriage & insurance £9.50.

### SCOOP!



### BRAND NEW CASED WORD PROCESSOR KEYBOARDS

Made by the famous 'KEYSWITCH' corporation, for a well known computer company's top of the range word processor at a price of over £200.00!! Constructed around an internal INTEL 8048 cpu this superbly styled 106 key keyboard was intended to interface with a main computer via a TTL serial interface. Standard HALL EFFECT long life switches are utilised on an XY matrix, buffered by 74 series TTL ic's to the eight bit CPU port enabling simple modification to your own custom decoding logic via an EPROM etc. Many other features for the most exacting user include: numeric keypad, cursor control pad, ten clear top function keys, LED indicators, single 5v supply on-off lock switch etc. Supplied BRAND NEW and boxed with circuit diagram. ONLY £49.95 + £2.00 P&P

### DRE 7100

8" Disk Drives  
New £225 + VAT

### VIDEO MONITORS

12" CASED. Made by the British KGM Co. Designed for continuous use as a data display station, unit is totally housed in an attractive brushed aluminium case with ON-OFF, BRIGHTNESS and CONTRAST controls mounted to one side. Much attention was given to construction and reliability of this unit with features such as, internal transformer isolated regulated DC supply, all components mounted on two fibre glass PCB boards - which hinge out for ease of service, many internal controls for linearity etc. The monitor accepts standard 75 ohm composite video signal via SO239 socket on rear panel. Bandwidth of the unit is estimated around 20 Mhz and will display most high def graphics and 132 x 24 lines. Units are secondhand and may have screen burns. However where burns exist they are only apparent when monitor is switched off. Although unguaranteed all monitors are tested prior to despatch. Dimensions approx. 14" high x 14" wide by 11" deep. Supplied complete with control, 240 volt AC operation. ONLY £45.00 PLUS £9.50 CARR.  
24" CASED. Again made by the KGM Co with a similar spec as the 12" monitor. Originally used for large screen data display. Very compact unit in lightweight alloy case dim. 19" H x 17" D x 22" W. All silicon electronics and composite video input make an ideal unit for schools, clubs, shops etc. Supplied in a used but working condition. ONLY £55.00 PLUS £9.50 CARR & INS.

### SAVE £250 SUPER PRINTER SCOOP



CENTRONICS 739-2  
The "Do Everything Printer" at a price that will NEVER be repeated. Standard Centronics interface, full graphics, 4 type fonts with high definition & proportional spacing for word processor applications, 80-132 columns, single sheet, roll or sprocket paper handling plus much more. Available only from DISPLAY ELECTRONICS at a ridiculous price of only £199.00  
Options: carriage & insurance £10.00  
Interface Cable £10.00

### TELETYPE ASR33 I/O TERMINALS

FROM £195 + CAR. + VAT  
Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order.  
Options: Floor stand £12.50 + VAT  
KSR33 with 20ma loop interface £125.00 + Sound proof enclosure £25.00 + VAT

### SOFTY 2

The amazing SOFTY 2. The complete "toolkit" for the open heart software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, UHF modulator, Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! Only £169.00 pp £1.95 Data sheet on request

### QUALITY INTERFACE CABLES & CONNECTORS

18/3B D25S to 10H 18 way £4.90  
22/2A D25S to 3Rt 22 way £2.90  
22/3B D25S to D25P 9H 22 way £8.50  
25/08 25 way cable 5H long 95p  
D25S ex equip 60p D25S socket new £1.25  
22/2C D25S to 16H 22 way £6.50  
22/3C D25S to D25P 15H 22 way £11.50  
1014B D15P to 12H 15 way (BBC) £2.90  
12/15 10 way cable 12H long £1.00  
D25 split shells £1.00

### SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter  
Daisy wheel printer at a fraction of its original cost.

BRAND NEW AT ONLY £499 + VAT



Made to the very highest spec the TEC Starwriter FP1500-25 features a heavy duty die cast chassis and DIABLO type print mechanism giving superb registration and print quality. Micro-processor electronics offer full DIABLO/QUME command compatibility and full control via CPM Wordstar etc. Many other features include bi directional printing, switchable 10 or 12 pitch, full width 381 mm paper handling with upto 163 characters per line, friction feed rollers for single sheet or continuous paper, internal buffer, standard RS232 serial interface with handshake. Supplied absolutely BRAND NEW with 90 day guarantee and FREE daisy wheel and dust cover. Order NOW or contact sales office for more information. Optional extras: RS232 data cable £10.00, Tech manual £7.50, Tractor feed £140.00, Spare daisy wheel £3.00, Carriage & Ins. (UK Mainland) £10.00.

### 66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME". Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay. Unbeatable value! Sold by weight.  
2.5kls £4.25 + pp £1.25  
10kls £10.25 + pp £2.25  
5kls £5.90 + £1.80  
20 kls £17.50 + £4.75

ELECTRONIC COMPONENTS EQUIPMENT

### SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s triacs, diodes, bridge recs, etc. etc. All devices guaranteed brand new full spec, with manufacturer's markings, fully guaranteed.  
50+ £2.95 100+ £3.15  
TTL 74 Series A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. 100+ £6.90 200+ £12.30 300+ £19.50

### DEC CORNER

MOSTEK CRT 80E Brand new dual eurocard, Z80 based VT100 PLUS emulator with graphics etc £499.00  
BALL-MB 3.5" Box, LTC, PSU £385.00  
RK05-J 2.5 Mb disk drives £650.00  
PDP1105 Cpu, Ram, i/o £450.00  
DIALOG DO100 RK05 LSI 4 x RK05 disk controller £450.00  
LAXX-NW LA180 RS232 serial interface and buffer option £230.00  
LAX34-AL LA34 tractor feed £85.00  
LA34 Keyboard assembly £75.00  
BC05W-15 interface cables £28.00  
H317B interface adaptor £295.00

1000's of spares EX STOCK for DEC PDP8 PDP11 PDP15 + peripherals call for details.  
ALL types of Computer equipment and spares wanted for prompt CASH PAYMENT

### DATA MODEMS

Join the communications revolution with our range of EX TELECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.  
MODEM 2B "Hackers Special" fully fledged up to 300 baud full duplex, ANSWER or CALL modes. Data i/o via standard RS232 25 way 'D' socket. Just 2 wire connection to comms line. Ideal networks etc. Complete with data, ready to run £85.00  
MODEM 20-1 Compact unit for use with MICRONET, PRESTEL or TELECOM GOLD etc. 2 wire direct connect. 75 baud transmit 1200 baud receive. Data i/o via RS232 'D' socket. Guaranteed working with data £49.95  
MODEM 20-2 same as 20-1 but 75 baud receive 1200 baud transmit £130.00  
MODEM 20-3 Made for data rates up to 1200 baud in full duplex mode over 4 wire circuit or half duplex mode over 2 wires. £130.00  
MODEM 13A compact, async, same size as telephone base. Up to 300 baud, full duplex over 2 wires, but call mode only £75.00  
DATA PUMP MODEM compact unit up to 1200 baud full duplex over 4 wires or half duplex over 2 wires. BELL specification with data i/o via RS232 25 way D socket, remote test etc. 240 v operation. Supplied complete with data £65.00 carr. £4.50.  
For more information or details of other types of ex. stock modems contact sales office.  
Carriage 13A £4.50. 2B/C & 20 £9.50.

## DISPLAY ELECTRONICS

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government depts., Schools, Universities and established companies £20.00. Where post and packing not indicated please ADD 80p + VAT. Warehouse open Mon-Fri 9.30 - 5.30. Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquires welcome.

32 Biggin Way, Upper Norwood, London SE19 3XF  
Telephone 01-679 4414 Telex 27924


WW - 060 FOR FURTHER DETAILS

# Appointments

Advertisements accepted up to 12 noon Tuesday, January 3, for February issue subject to space available.

**DISPLAYED APPOINTMENTS VACANT:** £17 per single col. centimetre (min. 3cm).  
**LINE advertisements (run on):** £3.50 per line, minimum £25 (prepayable).  
**BOX NUMBERS:** £5 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS).  
**PHONE: IAN FAUX, 01-661 3033 (DIRECT LINE)**

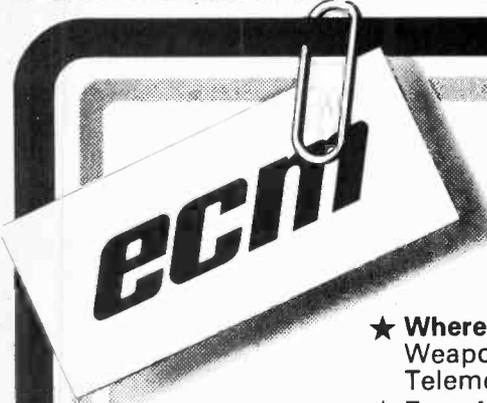*Cheques and Postal Orders payable to BUSINESS PRESS INTERNATIONAL LTD. and crossed.*



**ecm**

## ALWAYS AHEAD WITH THE BEST!

£7,000-£20,000

- ★ **Where does your interest lie:** Communications; Computers; Weapons; Radar; Sonar; Data-Comms; Signal Processing; Medical; Telemetry; Simulation; Satcom; Local Area Nets; ATE?
- ★ **Experienced in:** Microprocessor Hardware or Software; Digital and Analogue circuitry; RF and Microwave techniques?
- ★ **There are hundreds of opportunities in:** Design; Test; Sales and Service for Engineers and Managers
- ★ **Act now:** Just dial 100 and ask for **FREEPHONE JOBLINE** or send your C.V. (no stamp needed) to:

**ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED**  
Freepost, Barkway, Royston, Herts SG8 8BR

(1926)



## CAPITAL APPOINTMENTS LTD

THE UK'S No. 1 ELECTRONICS AGENCY

If you have HNC/TEC or higher qualifications and are looking for a job in design, test, customer service, technical sales or similar fields:

**Telephone now for our free Jobs list**  
**We have vacancies in all areas of the UK**  
**Salaries to £15,000 pa**

**01-637 5551 or 01-636 9659**  
(24 hours)

**CAPITAL APPOINTMENTS LTD**  
29-30 WINDMILL STREET, LONDON W1P 1HG

(291)

## CUSTOMER SERVICE TECHNICIAN

£6,000-£8,500

Due to continuing expansion, a vacancy exists for a first-class technician in our busy Service Department.

The successful applicant will be engaged primarily in the repair and calibration of our range of premium voltmeters and calibrators, and will be prepared to undertake site visits in support of our systems activities.

He or she will have practical experience in the repair to component level of precision analogue and embedded microprocessor circuitry. Some understanding of high level programming and IEEE 488 BUS is desirable.

Relocation assistance will be offered where appropriate. Please apply in writing for an application form to:

**David Marsh, Customer Service Manager**  
**DATRON INSTRUMENTS LIMITED**  
Hurricane Way, Norwich Airport  
Norwich NR6 6JB

(2365)

## WAYNE KERR

### ANALOGUE/MICROPROCESSOR DESIGN ENGINEERS

Do you have analogue design skills but feel you are missing out on the microprocessor revolution? Wayne Kerr have opportunities for analogue design engineers who want the challenge of interfacing with the microprocessor. The resulting ATE and Bridge products are in the forefront of their fields and you could be part of this exciting environment.

Our company, part of a rapidly expanding international group, offers competitive salaries with associated benefits and pleasant working conditions in the South of England.

If you are interested and would like further details, please write to:  
Miss Jo Hall, Personnel Officer, Wayne Kerr Limited, Durban Road, South Bersted, Bognor Regis, West Sussex PO22 9RL. Tel: (0243) 825811

(2393)

## ASSISTANT MAINTENANCE ENGINEER

required for our busy film/video company in the West End. Duties involve maintenance of a wide variety of film dubbing equipment (16mm and 35mm) and video equipment (1in and U-Matic standards).

Someone with lots of enthusiasm and some relevant electronics experience will have the opportunity to develop their skills and work without the boss looking over their shoulder all the time.

Write, explaining why you fit the bill, to:

**BRIAN HICKIN**  
**ROGER CHERRILL LIMITED**  
65-66 DEAN STREET, LONDON W1V 5HD

(2361)

# Appointments

Med Elect

## ELECTRONICS APPOINTMENTS £6,000 - £16,000

ANALOGUE, RADIO, MICROWAVE  
DIGITAL, MICROPROCESSOR, COMPUTER  
DATA COMMS, MEDICAL

Design, Test, Sales and Field Service Engineers —  
to use our free, confidential service and improve your salary  
and career prospects, UK and overseas, contact:



Engineering & Technical Recruitment  
11 Westbourne Grove, London W2. Tel: 01-229 9239

(1935)

## TEST ENGINEERS

The Micro Consultants Group is a world leader in the design, development and manufacture of interactive video imaging systems and data acquisition equipment.

Experienced Test Engineers are needed to perform both card and rack testing on these pieces of equipment, faultfinding to component level and conducting acceptance tests prior to despatch. As assistance may be required in the production of test procedures, the ability to develop such procedures and additional test rigs would be an advantage.

Candidates with at least three years' relevant experience together with a full TEC qualification or equivalent, should write or telephone for an application form to:

The Personnel Officer, Micro Consultants Group,  
17 West Mills, Newbury, Berkshire. Tel:  
Newbury (0635) 48222.

(2369)

**MICRO CONSULTANTS GROUP** ♦♦♦

**HUNTINGDON HEALTH AUTHORITY**  
Hinchingsbrooke Hospital

## Medical Physics Technician I

(Technician in charge of bio-medical equipment support unit)

We require an experienced technician, who will be in charge of the Bio-Medical Equipment Support Unit, which provides the technical service support for Anaesthetics, Electro-Medical and associated equipment within the Health Authority.

The post will be based at the new Hinchingsbrooke Hospital, the District General Hospital, although the duties of the post will extend to all hospitals and units within the district.

Salary scale: £8,910 to £10,398 per annum.

**Application form and job description from: District Personnel Officer, Huntingdon Health Authority, District Headquarters, Primrose Lane, Huntingdon, Cambs PE18 6SE. Tel: Huntingdon 50571 Ext. 32.**

Closing date for applications: 11th January, 1984.

*Previous applicants need not re-apply.*

(2374)

## A.B. ELECTRONIC PRODUCTS GROUP PLC

### WOLSEY ELECTRONICS LIMITED SALES ENGINEER, CABLE TELEVISION & ELECTRONIC COMMUNICATION SYSTEMS

Wolsey Electronics, market leaders in the U.K., is a company within the AB Electronic Products Group PLC.

Wolsey is the leading U.K. manufacturer of MATV and Cable Television distribution equipment and digital "Warden Call" alarm systems for the elderly and infirm. Expansion in these and allied fields, including Direct Broadcast Satellite systems and fibre optics, has created a further requirement for an experienced Sales Engineer to operate in London and South East England.

Based at home, the applicant appointed will have the full backup facilities of Wolsey's London Planning Office and Depot.

Salary and conditions of employment will be competitive and commensurate with the applicant's experience, who will probably be aged 25 to 40 years.

A company car will be provided.

Write or telephone for an application form to:

(2357)



The Personnel Manager,  
AB Electronic Products Group PLC, Abercynon,  
Mountain Ash, Mid Glamorgan. CF45 4SF.  
Telephone No.: (0443) 740331

## SENIOR DEVELOPMENT ENGINEER

**Location: West London**

An appointment exists within a long-established electronic data capture company for a Senior Development Engineer.

The following requirements associated with this appointment are:

- ★ Knowledge of microprocessor based data capture equipment.
- ★ Development of customised interfaces and software applications.
- ★ Customer liaison.

The successful applicant would probably be qualified to HNC level, and have at least three years' experience in the electronic industry, preferably in data processor type equipment, and have experience of microprocessors and data communications interfaces.

Normal large company benefits . . . + company car. Salary commensurate with experience.

**Please write or telephone in first instance for an application form to Miss Carol Cox, Kimball Systems (A Division of Litton Business Systems), 113/117 Gunnersbury Avenue, Ealing, London W5 4LR. Tel. 01-993 5934.**

(2362)

## Telecommunications for the future Maintenance Engineers

**London, Birmingham and Manchester**

**£10,000 – £13,000 plus allowances**

Mercury operates a new independent digital communications network for voice/data and T.V. transmission in the U.K. using the latest technology and techniques.

Service Centres are being established in London (Park Royal), Birmingham (Solihull) and Manchester and field maintenance engineers are required to expand our existing workforce.

Suitable applicants will have a sound knowledge of digital and analogue techniques as applied to the telecommunications field. In addition they will have had several years experience on either maintenance and repair or commissioning of customer equipments in at least one of the following areas:-

- i) Microwave point to point or point to multipoint systems.
- ii) PCM/TDM multiplex systems.
- iii) High speed data communications systems.

Salary will be dependent on age and experience and is negotiable in the range £10,000 – £13,000 p.a. The London posts carry an additional weighting of £1,200 p.a. An estate car will be provided and applicants should hold a clean driving licence. Staggered working hours and call out duties will be necessary for which additional payments will be made.

These are outstanding career opportunities offering the chance to make a significant personal contribution to the success of one of the most exciting developments of the 1980's.

Please write or telephone for an application form to: Mercury Communications Ltd., Ninety Long Acre, London WC2E 9NP; Tel. 01-836 2449 stating which location you are interested in.



(2371)

### BORED ?

**Then change your job!**

#### 1) Office Automation Systems

Repair engineer working to component level on microprocessor-based equipment. £ neg. Berks.

#### 2) Radar & Pulse Technique

Test Engineers required to work on electronics components and equipment to military standards. To £9,000. Middx.

#### 3) Field Service Engineer

With good electronics background to work on medical/X-Ray equipment. c. £7,000+. Berks.

#### 4) CAD/CAM

Field Engineers with a knowledge of graphic displays, plotters and associated peripherals, based on PDP 11. £ neg + car. Bucks.

#### 5) Service Personnel (RAF, RN, Army)

We have many clients interested in employing ex-service fitters and technicians at sites throughout the UK. Phone for details.

#### 6) £500 per week

We are paying very high rates for contract design and test engineers who have a background in RF, MICROWAVE, DIGITAL, ANALOGUE or SOFTWARE, at sites throughout the UK.

**Hundreds of other Electronic and Computer Vacancies to £12,500**

Phone or write:

Roger Howard, C.Eng., M.I.E.E., M.I.E.R.E.

#### CLIVEDEN CONSULTANTS

87 St. Leonard's Road, Windsor, Berks.  
Windsor (07535) 58022 (5 lines)

(1640)

## CLIVEDEN

### LOGEX ELECTRONICS RECRUITMENT

Specialists in Field & Customer Engineering appointments, all locations and disciplines.

Logex House, Burleigh, Stroud  
Gloucestershire GL5 2PW

0453 883264 & 01-290 0267

(24 hours)

## Electronics Technicians

Petty-Ray Geophysical Division of Geosource is one of the leading companies in the field of oil exploration and require single personnel, in the age range 21-35, who are looking for a varied and interesting career working overseas.

You should be educated to ONC/HNC in Electronics or C & G Radio and TV Technician level, and on appointment you will be assigned to one of our field crews either in AFRICA or the MIDDLE EAST for on-the-job training in the operation and maintenance of digital seismic recording equipment.

Candidates must be in possession of a current driving licence.

We offer a good starting salary which is paid NET, food and accommodation will be provided and rest leaves are generous.

If you would like to have more information about these positions please write giving brief career details to:-

The Personnel Officer, Petty-Ray Geophysical Division of Geosource, 3-5 The Grove, Slough SL1 1QG, Berks.

(2358)

**GEOSOURCE**

# Appointments

## RF ENGINEERS

### EMC/EMP assessment on high technology equipment

At Frimley, we have an international reputation for our work on the design and development of sophisticated electronic systems and equipment for both civil and defence applications. Our multi-discipline teams of engineers, both men and women, are engaged in an expanding programme of advanced projects in which extensive use is made of state-of-the-art techniques in the solving of complex problems.

Within our Technology Group, we are looking for experienced RF Engineers, with qualifications to degree/HNC level, to provide specialist support to teams engaged in equipment design. This will involve carrying out theoretical and experimental assessments of system electromagnetic compatibility (EMC) or vulnerability to nuclear electromagnetic pulse effects (EMP).

These positions call for a sound electrical/electronics engineering background and specific experience of at least one of the following: electromagnetic analysis, computer-based mathematical modelling, development of HF equipment including HF/VHF transmitters and receivers, and EMC measurements.

All appointments will provide exceptional opportunities to work in a particularly stimulating technological environment and make a significant personal contribution to our work. If you have the necessary innovative ability and professional expertise, you can look forward to a really challenging future with ample scope for career development.

We offer a competitive salary together with an attractive range of fringe benefits.

Write with details of experience and qualifications to Margaret Perceval, Personnel Department, Marconi Space and Defence Systems, Chobham Road, Frimley, Surrey GU16 5PE. Or telephone Camberley 63311 for an application form.

**Marconi**  
Space & Defence Systems



(2389)

### PETERBOROUGH HEALTH AUTHORITY

Are you looking for an interesting and challenging new position? Are you qualified to at least ONC level with practical electronics experience? Then why not come and join an expanding electronics department in Peterborough?

We are looking for a technician to maintain X-ray, radio therapy and ultrasonic scanning equipment

Salary £6,132 to £7,926 per annum by seven annual increments

Ring Allan Edwards on Peterborough (0733) 67451, ext. 250 for details and application forms or write to:

District Works Department  
Peterborough District Hospital  
"Eastlea", Thorpe Road  
Peterborough

Closing date for applications:  
28 December, 1983

(2399)

### UNIVERSITY OF LONDON INSTITUTE OF EDUCATION

#### ELECTRONICS TECHNICIAN (Grade 5/6)

Required for Child Development and Educational Psychology Department. Duties include maintenance of Audio, Video and Psychological Equipment, and the development of the use of Microcomputers in Education and Research. Good knowledge of Analogue and Digital Electronics and the ability to design, construct and service apparatus essential. Knowledge of Microcomputer programming an advantage.

Applicants should have HNC/HTEC or equivalent and seven to 10 years' experience.

Salary within range £7529-£9852 inclusive.

Please ring Mary Griffin, Personnel Section, University of London Institute of Education, 20 Bedford Way, London WC1H 0AL, 636 1500 ext 254, for further details and application form quoting ref T5-6/CDEP. Closing date 31 January.

(2391)

## COMMUNICATIONS POSITIONS TO MAKE YOU THINK A LITTLE FASTER

Below are a number of positions that will up the pulse and make the grey matter churn round a little faster.

Telephone Paul Hecquet or write to him to discuss these and many other positions we have within our Communications Division.

**Systems Engineer/Proposals – on site work** **££12,000** **South East**

The job will be to carry out complete systems appraisals/evaluations, generate a proposal for predominantly civil/civilian duty VHF/UHF users. Ref: 2/135.

**TV Design Engineers** **£8 to £14,000** **Wales**

To work in the R & D area of consumer colour TV. Ref: 12/19.

**Cable TV Design Engineers** **£9 to £16,000** **South East**

Experience in television engineering, VHF/UHF techniques and/or Data Comms would be useful to this Cable TV systems provider. Ref: 3/260.

**Studio (TV) Management & Technical Staff** **Salaries from around £9,000** **South East**

For technical and engineer level people to around £17,000 for supervisory staff. You must have experience with a TV Broadcasting organisation though not necessarily UK based. Ref: 1/241.



The Electronics  
Recruitment Company

Temple House  
25/26 High Street, Lewes  
East Sussex BN7 2LU  
Tel: Lewes (07916) 71271

(2313)

### RF ENGINEER

Degree status  
Satellite communications  
experience preferred  
Two-year Essex contract  
£12 per hour

Telephone  
Graham Williams  
(0920) 5921  
STAFFHIRE LTD.  
80-82 High Street  
Ware, Herts

(2400)

### CINE LINGUAL SOUND STUDIOS LTD.

Due to expansion we require an

#### EXPERIENCED ELECTRONICS ENGINEER

for the maintenance of our film  
dubbing theatres

Salary up to £10,000

For further information contact  
Lynne Robinson on 01-437 0136

(2368)

## ELECTRONICS ENGINEER

Auditel Systems Ltd. specialises in the manufacture of conference communication systems and designs equipment for specific applications. The company is small but expanding and an opportunity exists for an Engineer with a degree or H.N.C. in electronics to assume wide ranging technical responsibilities with the chance to become involved with the company's future. The position covers technical liaison between design and production, systems design and documentation, testing and commissioning. Candidates should have a background in audio and digital electronics with some microprocessor experience. Salary negotiable, area £9,000 p.a.

Please apply to J. M. White  
AUDITEL SYSTEMS LTD  
78 Asheridge Road  
Chesham, Bucks HP5 2PY

(2357)

## THE WAY UP!!

**Surrey £15K ++**  
Leading consultancy offers truly unique position to Electronic or Software Engineers

Call Richard Butcher NOW!!

01-549 6441 (Day)

01-337 4900

(After 7.30pm)

(2384)

ab executive (Kingston) Ltd  
Specialists In Recruitment

### TOWNLEY EMPORIUM

Bargains for callers or send for catalogue

### ELECTRICAL, ELECTRONIC & MECHANICAL COMPONENTS

Vast range of surplus test equipment; Diodes; Thyristors; Resistors; Terminals; Switches; Relays; Screws; ICs; Tools.

Harehill Street off Burnley Road, Todmorden, Lancs OL14 5JY

(2172)

GERMAN WW2 TUBES: RV2P800 £3, RV24P45 £3.50, RE084K £2, RL12P45 £4. All brand new in "Wermacht" original boxes. Alf Thunstrom, Kallvagen 2, 5-61053 Enstaberga, Sweden. (2366)

### SCOTTISH OFFICE DIRECTORATE OF TELECOMMUNICATIONS

## WIRELESS TECHNICIAN

(£6,251-£8,450)

Applications are invited for the above post based in East Kilbride near Glasgow

Candidates must have a sound theoretical and practical knowledge of Radio Communications Systems both fixed and mobile, in the frequency range HF to 2GHz. They must also be able to use test equipment and simple machine tools. A sound basic knowledge of digital techniques would be an advantage. They should have a minimum of three years' appropriate experience and should hold an Ordinary National Certificate in Electronic or Electrical Engineering or a City and Guilds of London Institute Certificate in an appropriate subject or a qualification of higher or equivalent standard. Some assistance may be given with re-location expenses.

A valid UK driving licence is essential.

Application forms and further information are obtainable from Scottish Office Personnel Division, Room 110, 16 Waterloo Place, Edinburgh EH1 3DN (quote ref. PM(PTS) 1/4/83). (031-556 8400 Ext. 4317 or 5028.)

Closing date for receipt of completed application forms is 12 December 1983. (2367)

### WEST YORKSHIRE METROPOLITAN COUNTY COUNCIL

An Equal Opportunities Employer

## RADIO TECHNICIAN

Post Ref ES 20 206/F28

£7,191-£7,896

Based at Chantry House, Wakefield, duties involve the provision of an effective service of operation, maintenance and repair of the radio telephone system. Network consists of approximately 650 vehicle-mounted radios, 5 VHF transmitter sites and numerous land lines.

A TEC/ONC level qualification in electrical, electronic or radio engineering or a similar discipline is required, and experience in the maintenance and repair of radio communication equipment is essential.

Mr R. Mackey (Wakefield 367111, Ext 3519) will answer queries.

Closing date: 30 December 1983.

Application forms are available from, and should be returned to, the Director of Manpower Services, 8 St John's North, Wakefield WF1 3QA (Tel. 367111, Ext. 2840). (2379)

RADIO

RADIO RELAY

ATC RADAR

GROUND RADAR

NAVAIDS

TECHNICALS

**Different skills,  
same rewards-  
£22,700 tax-free for  
two years in Saudi Arabia.**

It takes a lot of different skills to help maintain Saudi Arabia's integrated air defence system. It takes confidence and the ability to communicate your knowledge to train Royal Saudi Air Force personnel, which is the main task Lockheed are tackling in Saudi Arabia.

But whatever your technical background, the rewards are the same, and they're high.

They don't stop at that tax-free, two-year salary, either.

Lockheed's benefits package gives you free bachelor accommodation; free food, work clothing and laundry; free return flights to the UK

on your three paid leave periods a year; medical and life insurance; excellent sports and recreational facilities.

If you've a C&G or its forces equivalent, and at least seven years experience on the equipment areas we've specified, it's well worth your while getting in touch.

Because with us, your skills could really make a big difference.

Talk to Larry Mulhearn on 01-574 5000, or write to him at IAL, Recruitment Consultancy, Aeradio House, Hayes Road, Southall, Middx. UB2 5NJ. Please quote Ref. L229.



(2373)

# Appointments

Sandra Jeram 637 5200  
F. S. Griffin  
L/FS/617/7A7

## Are you an inventive electronics person with good, old-fashioned horse-sense?

We are looking for someone to join us in N.E. Surrey in a small but busy and creative team designing electronics for a range of laboratory and industrial measurement equipment.

We use analogue and digital circuitry and 6800/6809, and have recently started to make use of FORTH. There is plenty of opportunity for brain-stretching, and scope for the contribution of ideas from outside the electronics field.

## If this sounds as if it might suit you, or that you might adapt to it, then get in touch.

We would expect that the successful candidate will have experience in nitty gritty electronics and probably be HNC/Degree level but qualifications are of much lower importance than actual ability.

Telephone Tania Thompson (Chertsey 62671) or write for an application form to:

**KENT INDUSTRIAL MEASUREMENTS LTD.**  
Hanworth Lane, Chertsey, Surrey KT16 9LF

(2385)

National Heart and Chest Hospitals  
Brompton and London Chest Hospitals

## Medical Physics Technician ELECTRONICS

A vacancy exists for a technician with hospital experience to join the team of technicians in the Department of Medical Electronics. The department provides a comprehensive maintenance and development service to two busy Cardiothoracic hospitals. The technician will be based initially at the London Chest Hospital E2, but he/she must be willing to also work at Brompton Hospital SW3.

The post is as MPT4 but prospects for promotion to MPT3 do exist.

For further information contact Mr P. Butler, Chief Technician, 01-980 4433. Ext. 340.

For a job description and application form contact Miss J. A. Jenks, Personnel Manager, Brompton Hospital, Fulham Road, London SW3 6HP. Tel: 01-352 8121. Ext. 4357. Closing date: 13th January, 1984.

(2390)

## R.T.T. SYSTEMS RADIO TELEPHONY TESTING

### R.F. ENGINEERS - DESIGN AND SALES

We are a Division of a highly successful Electronics Group with considerable expertise in Control Systems; this new Division is involved with Radio Telephone Test Systems and has a major technical expansion programme ahead.

To assist in these exciting projects we require additional R.F. specialists to work with our small team designing, producing and selling to all markets.

### DESIGNER/PROJECT CONTROLLER

Must have sound theoretical background in circuit design applied to a practical understanding of R.F. Engineering to 1.5 GHz or above. Must have degree level in Electronics and several years' experience in design, development and project control - possibly using outside consultants. Must be highly self-motivated and results orientated. Being a Radio enthusiast would be a bonus.

### SALES ENGINEER

Must have considerable experience of customer liaison and selling test equipment preferably associated with R.F. communications.

Sales are direct to end users in private and public industries. The company therefore expects a high degree of professionalism in both planning and application. Ideally the sales engineer should be qualified with practical training in electronics/R.F. Must be prepared to stay away from home occasionally.

Applications only from people wishing to enjoy the freedom and opportunity to exercise your personal innovativeness with prospects of growing with the company. Benefits include: company car, substantial salary, bonus, plus normal benefits associated with progressive company.

Send your career details or phone for an application form to: R. J. West (01-844 1811) R.T.T. (Division of Hanworth Enterprises), Gresham House, Twickenham Road, Feltham, Middlesex TW13 6HA. (2394)

# Marine Electronics Engineer

## ECUADOR

**Duties:** To join a British team working with Ecuadorian counterparts on the assessment and efficient utilisation of Ecuador's fisheries resources. The expert will be required to run and maintain the specialist electronic equipment on a modern fisheries research vessel, particularly echosounding and sonar equipment. He/she will also advise other team members on the efficient operation of the equipment and assist in the training of Ecuadorian staff. Considerable sea-time will be involved.

**Qualifications:** Applicants, who should be British citizens, should possess relevant professional qualifications and experience and be capable of technical improvisation to meet changing needs in the development of the survey programme. A working knowledge of Spanish is preferable.

**Appointment:** Two years. The salary in the range £9,950-£12,800 will be paid commensurate with experience and qualifications, and subject to



United Kingdom Income Tax. In addition, a tax-free variable Foreign Service Allowance in the range £105-£645 per annum and a supplementary allowance in the range £325-£1,580 per annum, both dependent on salary and marital status, are payable.

The post is wholly financed by the British Government under Britain's programme of aid to the developing countries. In addition to basic salary and overseas allowances, other benefits normally include paid leave, free family passages, children's education allowances and holiday visits, free accommodation and medical attention.

For full details and application form please apply, quoting Reference AH 312/L/AJ, stating post concerned, and giving details of age, qualifications and experience to:

Appointments Officer,  
Overseas Development  
Administration,  
Room AH 351,

Abercrombie House,  
Eaglesham Road,  
EAST KILBRIDE,  
Glasgow G75 8EA

## OVERSEAS DEVELOPMENT

BRITAIN HELPING NATIONS  
TO HELP THEMSELVES (2389)

# DESIGN ENGINEER

Earn over £20,000 p.a.

We are looking for an outstanding design engineer to join the team that created the Elan Enterprise home computer.

The successful applicant will have several years' experience of digital design techniques, as well as great creative flair and boundless enthusiasm.

The situation is based in Central London and an extremely attractive salary will be negotiated.

Please write, enclosing full c.v., to:

David Levy  
INTELLIGENT SOFTWARE LTD. (DEPT. WW)  
21 Store Street, London WC1E 7DH

(2375)

It's more by design than accident that Honeywell is ahead in advanced instrumentation worldwide. The Test Instrument Division based at Bracknell, is responsible for ensuring the effective operation of Industrial Tape Systems, Video Graphic Camera Systems and Oscillographic recorders countrywide in industrial, medical and R & D establishments.

We now need experienced Electronics Engineers, who after a brief product familiarisation period,


will be able to work to maximum effectiveness in trouble-shooting hi-technology equipment. Ideally, you will have a minimum of three years experience in fault-finding and maintaining 'state-of-the-art' equipment.

The position also involves a high degree of customer contact and you will be expected to work on your own initiative to assist in expanding our customer base.

By joining us you can expect all the rewards of working for a highly

successful International company, and in addition to an excellent salary, company car and worthwhile fringe benefits, there is every opportunity for career advancement.

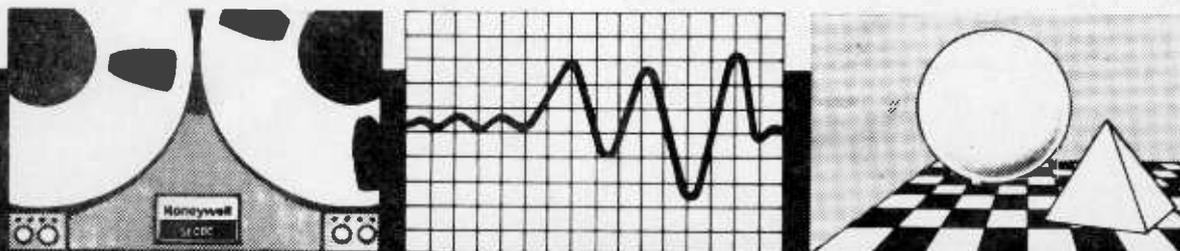Write with full career details to Richard Gould, Personnel Department, Honeywell Control Systems Limited, Honeywell House, Charles Square, Bracknell, Berkshire RG12 1EB. Telephone: Bracknell (0344) 24555. Please quote Ref WW/84/TID.



## NEW DIMENSIONS IN TEST TECHNOLOGY

# NEW CHALLENGES FOR ELECTRONICS ENGINEERS

# Honeywell

INDUSTRIAL PRODUCTS GROUP - TEST INSTRUMENTS DIVISION

(2343)

## TEST ENGINEERS (AUDIO)

We are a world leader in the design and manufacture of Computer-assisted sound mixing Consoles for the Record and Broadcast industries. To meet increasing demand we require experienced Audio test engineers to expand our existing test facilities.

Applicants should have at least two years' relevant experience and have the enthusiasm to work in a self-motivated environment. A knowledge of digital circuits would be useful.

Please write or telephone for an application form to

**Solid State Logic**  
Churchfields Stonesfield  
Oxford OX7 2PQ  
Tel. 099 389 8282

**Solid State Logic**

**Stonesfield · Oxford · England**

(2335)

## ELECTROSONIC SYSTEMS ENGINEER/MANAGER

£7K-£12K + Car

The Systems Engineering Division of ELECTROSONIC wish to recruit an experienced Project Engineer/Manager to be responsible for a wide range of projects both in the UK and Overseas.

The Company, which has extensive manufacturing facilities, produces a wide range of lighting, audio and audio visual products and is a world leader in its field.

The Systems Division is responsible for the design and production of special projects which include industrial and commercial dimming, TV and Theatrical lighting, hotel and conference low voltage systems, audio and audio visual systems, including video.

The ideal candidate will be qualified to HTC/HND/Degree level or equivalent and will have experience in one or more of the above fields; but of equal importance will be his/her practical design and manufacturing experience, together with drive and ability to take a project from the drawing board to final commissioning on site. A vacancy may also exist for a Junior Engineer who is able to demonstrate the above potential.

The salary offered will depend upon experience, but will be in the range of £7,000 to £12,000 p.a. A company car is also offered and other fringe benefits will include an overseas allowance.

Applicants should telephone or write to:

**R. D. GORTON**  
Divisional Manager - Systems Engineering  
Electrosonic Ltd, 815 Woolwich Road  
London SE7 8LT. Telephone: 01-855 1101

(2526)

## ANALOG CONSULTANT REQUIRED

Interesting short-term projects for good Analog Engineer, preferably with some telecommunications experience. Work at home or our labs. Cash if required. Please phone:

**DEREK ROWE ON 328 7145**

(2344)

## WANTED Studio Engineer/Radio Worker

for community radio project, S.E. London. 1 1/2 hours p.w.; pay approx £8,000 p.a. pro rata. Initially for six months. G.L.C. funded. To maintain studio, organise and teach courses in programme production and basic electronics. participate in admin of project.

Phone 7019010 or 703 0415 for details

(2347)

### Trainee Broadcast Engineers

We are responsible for broadcasting the programmes of Independent Television, Channel Four and Independent Local Radio. The continued growth of our broadcasting services means we have a number of vacancies for Trainee Broadcast Engineers who, on completion of their training, will work in a challenging and secure environment.

The selected candidates will embark on our 18-month residential training course which commences in June 1984. It will be conducted at our Training College, in Devon, and also at the Newcastle Polytechnic. The course is designed to give you a training in Broadcast Transmission Engineering that is second to none. It demands a high standard of understanding and personal commitment from those selected to undertake it. During the course we will pay you a salary and in addition, all your fees, accommodation and meals.

Applications are invited from men and women who are qualified or about to qualify to First Degree level in Electronic/Electrical Engineering or related disciplines.

Consideration will also be given to applicants holding an HND/HNC/HTEC in Electrical or Electronic Engineering or the City and Guilds Telecommunication Technicians Full Technological Certificate, and who have appropriate industrial experience.

Your salary while training will be £6,652 per annum. On the satisfactory completion of training, your salary will be £8,421 and will rise by annual increments to £10,461 per annum; further progression to £12,966 per annum is possible.

Employment benefits include a free life assurance and personal accident scheme, a contributory pension scheme, generous relocation expenses and subsidised mortgage facilities.



**INDEPENDENT BROADCASTING AUTHORITY**

\*An Equal Opportunities Employer\*



For a fully illustrated booklet and application form, please write to Mike Wright, Personnel Officer - Engineering Regions, IBA, Crawley Court, Winchester, Hants. SO21 2QA. Or telephone the Personnel Office between 9 am and 4 pm Monday to Friday on Winchester 822574 or 822273. Application forms must be returned by Friday 20th January 1984.

(2377)

### MAINTENANCE ENGINEER

and an experienced

### TAPE OPERATOR

required by

**MAISON ROUGE Recording Studios**

Please write with full details to:  
**Tony Taverner, 2 Wansdown Place  
Fulham Broadway, SW6 1DN**

(2387)

### ARTICLES FOR SALE

### RADIO AND TV SERVICING 1982-83 MODELS

by R. N. Wainwright Price £23.50

**THE ART OF ELECTRONICS** by Horowitz Hill Price £16.00

**INTEGRATED ELECTRONICS** by Millman-Halkias Price £11.25

**PRINCIPLES OF INTERACTIVE COMPUTER GRAPHICS** by William M. Newman Price £12.50

**BASIC PRINCIPLES AND PRACTICE OF MICROPROCESSORS** by D. E. Heffer Price £6.50

**VHF UHF MANUAL 4th Ed.** by G. R. Jessop Price £10.00

**INTERNATIONAL VIDEO YEAR-BOOK 1983/84** Price £26.00

**DOMESTIC VIDEOCASSETTE RECORDERS** by Steve Beeching Price £15.00

**1983 THE RADIO AMATEUR'S HANDBOOK** Price £10.00

**TOWERS' INTERNATIONAL MOSPOWER AND OTHER FET SELECTOR** by T. D. Towers Price £10.50

★ ALL PRICES INCLUDE POSTAGE ★

### THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

**19-21 PRAED STREET LONDON W2 1NP**

Phone 01-402 9176

Closed Saturday 1 p.m.

Please allow 14 days for reply or delivery

(2245)

### BULK COMPONENTS

Resistors - ideal for making into packs or just to increase stocks at a very low price. We're selling new, full lead length resistors in original boxes/packets/reels. Because most are packed in thousands (some are 100s) you'll need to buy a large quantity to get a reasonable mix. You'll get carbon/film/oxide mixed tolerances 1% to 20% in 1/8W, 1/4W and 1/2W. 20,000 £26; 50,000 £60; 100,000 £110; 1/4 million £250; 1 million £950. All prices inclusive. SAE for samples. We also stock capacitors, semiconductors, veroboard etc. in bulk.

SAE for latest list:  
**PC ELECTRONICS, 2 THORNHILL ROMSEY ROAD, WHITEPARISH, SALISBURY WILTS SP5 2SD**

(2380)

### THE FOWBERRY ENERGY SAVER (Patent Pending)

As described in the December Issue of *Wireless World*

Printed Circuit Board, fully silk-screen printed with component positions; component specifications and sources of supply; assembly instructions; drilling template for box-lid; window material, and self-adhesive label, fully printed. Board to fit Bimbox 2006.

£7.50 inc. postage and VAT  
**MacHARG PARTNERSHIP  
Fowberry Tower, Wooler  
Northumberland NE71 6ER**

(2382)

## WOULD YOU LIKE TO WORK IN A HIGH TECHNOLOGY AEROSPACE COMPANY AS A PRODUCTION TESTER?

Do you have the following knowledge and experience?

- ★ A minimum of ONC in electronics or equivalent experience
- ★ The ability to test or learn to test units containing Logic, Digital, Analogue and Timing Circuits
- ★ The capability to diagnose faults to component level
- ★ Can you use automatic and semi-automatic test equipment and instrumentation?
- ★ Do you have a questioning and practical mind, using your own initiative with the minimum of supervision?
- ★ Can you work in a manufacturing team?
- ★ Are you willing to learn about and constantly update your knowledge of test equipment and procedures?

If you think all this describes you, and would like to work for an established and successful company, then please contact me, enclosing personal details, at the following address: Mrs Karen Elton, Personnel Officer, Lucas Aerospace, Maylands Avenue, Hemel Hempstead, Herts HP2 4SP, or ring me on Hemel Hempstead (0442) 42233, extn 112.

(2372)

# Lucas AEROSPACE

## SITUATIONS VACANT

## ARTICLES FOR SALE

### BUCKS, BERKS W.MIDDX, OXON

**INSTALLATION MANAGER** £15K + Car  
Required to take responsibility for the installation, test and acceptance of the cellular radio system in the U.K. Applicants should be aged 30-40 years, educated to degree standard in electronics or telecommunications BERKS

**PRINCIPAL ENGINEER** £14K  
Total responsibility for the technical interface with British Telecom, including the provision and specification of link circuits, emergency services, signalling systems and transmission plans. Electronics degree and experience of public telephone systems an advantage. BERKS

**SENIOR ENGINEER (Radio)** £12K  
To be involved in the liaison with suppliers of subscriber equipment, including type approval testing, and providing a systems engineering support in relation to cell site RF equipment and antenna systems. BERKS  
For more details contact Stephen Salt, 2 Eton Court, Eton, Windsor (07535) 54256.

### SURREY, HANTS KENT, SUSSEX

**RF DESIGN ENGINEERS/MANAGERS** £8-15K  
Engineers seeking either design/dev or project/technical management roles with RF experience or voice and data communications are sought for a number of companies in Surrey and Hampshire

**DES DEVT ENGINEERS** c. £10K  
I have vacancies to interest persons with experience of the following: industrial monitoring, ATE, 8086, 8080, PDP11, Coral, Basic, Assembler, Z80, simulation, maths modelling, radar, VHF, UHF, quality Surrey, Sussex, Hampshire

**TECHNICIANS** £6-8K  
Young electronic Technicians are sought for digital, analogue and micro fault finding of systems and sub systems. Opportunity to build on good basic knowledge, interesting products, some mechanical involvement. Weybridge/Woking  
For more details contact Keith Hardy, Shaw House, 2 Tunsgate, Guildford (0483) 65566 or out of hours (0252) 870588.

### HERTS, ESSEX BEDS, N.MIDDX

**RF ELECTRONICS ENGINEERS** c. £14K  
A medium-sized consultancy requires a number of strong radio frequency circuit design/systems professionals for various industrial, commercial and military projects. You will have total project control, with client contact. Herts

**TEST EQUIPMENT DESIGNERS** c. £11K  
This 'blue chip' company, working in the forefront of communications systems requires a number of experienced Designers. Essential to have solid R/F background (HF/VHF Ranges), and ability to control a team. Essex

**TEST/SERVICE ENGINEERS** c. £9K + overtime  
Positions available for Junior and Senior Staff with either City and Guilds or H.N.C. qualifications in electronics. A good digital, analogue or micro-processor background is particularly relevant. Products range from communications equipment to medical systems. Essex  
For more details contact Alan Gall, 105 St Peter's Street, St Albans (0727) 35116 or out of hours (07073) 28623

### B&T ELECTRONICS

13 TANNERS HILL  
DEPTFORD, LONDON, S.E.8

TEL: 01-692 1441

1,000s ELECTRONIC, ELECTRICAL  
MECHANICAL ITEMS

Xenon Tubes. Type XBLU 50/00 Eclatron £2.50 each. P&P 60p. Quantity discounts. P.O.A.

Xenon Flashers. Complete panel with dual flash rate, 12-18 volts DC, inc. Tube, Base, Fuse + Holder, 10 metres connecting wire. Full instructions. 3 months' guarantee. Complete package only £10 + £1.80 P&P. Discounts. P.O.A.

Enamelled Copper Wire. .090, .080, .180 MM £5 per 1kg Reel + £1.80 P&P

AVO B Movements. Mk 3 plus spares, plus damaged Meters. P.O.A. Will sell as one lot. £400.

Measured Pressure Transducers £25 each. S.A.E. LISTS.

Meters Mcooil, dc plastic, as used in Japanese and 10 units, app. size 5.5mmx4.5mm. We have Power W. V.U. Signal, or Battery level. 100 or 200 micro amp tsd. £1.50 each. P&P 60p. (2296)

### MULTITURN CERMET TRIMMERS 3/4 INCH

Make Allan Bradley 100 1K+  
Type 94P non transparent £22p 18p  
Type 95P transparent £22p 18p  
Values 10-470R, 2K-500K. 1M, 2M, 2M2, 18 pin low profile I.C. socket 10p 7p

Please phone or telex  
DIW MARKETING  
3 Whitney Avenue, Ilford, Essex  
Tel: 01-445 6645/550 4774  
Telex 896 559 Att. DIW (2324)



**Management Personnel**  
Recruitment Selection & Search  
**WINDSOR GUILDFORD ST ALBANS**

## BRAIN TEASER

Our opinion of what motivates a design engineer to move is: 1) Location; 2) Tie between money and job satisfaction; 3) Chemistry

What is your opinion?

## DOES THIS ATTRACT YOU?

**LOCATION** - London's Green Belt. Easy access to rural Essex and tube to central London. Housing nearby to suit all tastes, local market towns, new towns, villages, suburbs and listed Georgian terraced houses ripe for conversion by anyone with basic engineering skills.

**MONEY** circa £11,500

**JOB SATISFACTION.** In this company you can design a complete system - average project 3-18 months. Participate in project management and create with the real world in mind - your systems have to withstand a rugged environment and anticipate the foibles of the human mind. Systems, broadly speaking, are passive surveillance systems incorporating electro-optics, analogue and digital signal processing, displays and the application of computer power to small instruments.

**CHEMISTRY.** Small company atmosphere with large company backing.

FOR FURTHER DETAILS PLEASE CONTACT

**Charles Airey Associates**

Tempo House, 30 Fairfield Street, London SW18 1DW  
Telephone: 01-870 4504

(2381)

## ARTICLES FOR SALE

### USED ELECTRONIC INSTRUMENTATION

MARCONI TF.2951 RADIO TEST SET ..... £4500  
MARCONI TF.995A AM/FM SIGNAL GENERATOR ..... £225  
SOLARTRON 7051 PROGRAMMABLE 5 1/2-digit Digital Multimeter with maths pack RS.232 ..... £650  
LYONS PG2 PULSE GENERATOR ..... £60  
H-P 1332A X-Y DISPLAYS ..... £250  
H-P T.141 SPECTRUM ANALYSER with 8552B I.F. Plug-in and 8553B R.F. Plug-in ..... £3250

VAT & CARRIAGE EXTRA

**MARTIN ASSOCIATES**  
PARTHIA HOUSE, BECKHAMPTON  
NR. MARLBOROUGH, WILTS  
TELEPHONE: AVEBURY (067 23) 219

(2396)

### INVERTERS

High-quality DC-AC; also "no break" (2ms) static switch, 19ln. rack. Auto Charger.



COMPUTER POWER SYSTEMS -

Interport Mains-Store Ltd.  
POB 51, London, W11 3BZ

Tel: 01-727 7042 or 0225 310916 (9101)

Autograf 2D X-Y recorder £79. Solartron Multiphase signal generator £89. Lab Variac, cased, 15A, £39. CES Television Sweep Generator, eight pre-selectable IF crystal markers, master crystal, etc., £69. Matching oscilloscope £89 (large calibrated screen). Rank Precision Wow & Flutter Meter £79. Record chart recorder 1mA £35. Variac 8A, £29. Avo Universal 20,000 ohms/volt DC £59. Solartron Stabilised PSU, 0-30v, 3A, metered, £59. Tektronix 160, 161, 162, 163 Waveform & Pulse Generator set £75. Mullard High Speed Valve Tester £75, cards 20p ea. (min. 100). pH electrodes £10. Centrifuge £49. Extraction/Ventilation fan 250 cfm, 3-phase £29. Smaller, single-phase £10 ea. Bell & Howell 16mm sound projector £89. Precision colormeter £75. Myron Conductivity Meter (water testing) £35. Instrument & watch cleaner £35. Single to three phase converter £95.

0403 76236

(2016)

## ARTICLES FOR SALE

**MARCONI POWER METER** 6460, 0.01-12.4GHz with 6422 head, new and unused, calibrated and warranted Marconi 90 days, 4 October, 1983, £600. Collins 51S1 receiver RE, virtually new, £850. Wanted KWM2A S/N 39000 plus. Shrewsbury 81425. (2356)

**CROMEMCO** high resolution colour graphics system, complete. 760x340 Pixel system with software. Ideal system for most serious graphics applications. Good support for Cromemco in the U.K. New cost over £3,500. Offers around £2,000. (0224) 572933. (2364)

**RACAL RA1792** Receiver, 30MHz, synthesized, current production £3,000, £6,000+ new. Approx. 18 months old. 0422 822075 W. Yorks. (evenings). (2253)

**VACUUM EQUIPMENT** for encapsulation. Degassing of silicones and resins. CRT regunning plant, b/w and colour. Barretts, Mayo Road, Croydon CR0 2QP. 01-684 9917. (9678)

**Quartz Crystal Units**  
ACCURATE RELIABLE  
Private enquiries, send 13p in stamps for brochure  
**THE QUARTZ CRYSTAL CO. LTD.**  
Q.C.C. WORKS, WELLINGTON CRESCENT  
NEW MALDEN, SURREY 01-942 0334 & 2988

### 6802 MICRO COMPUTER

This micro is designed for control applications both in industry and the home. Two models are available, PIA or VIA. Both are crystal controlled and have a 5V reg, 128bytes of Ram, 18in/out lines + 2 input lines. The via also has two 16-bit timers and a shift register. The programs are held in EPROM (not included). Types 2716, 2516 and 2732 are accepted, 6802 via kit £19.95. 6802 via kit £21.95. Assembled add £3. Discount available on 5+ qty.  
Orders to: Xaner, 20 Baldwin Road, King's Lynn, Norfolk PE30 4AN. (2363)

### Laboratory Technician/Demonstrator (Broadcast Engineering)

The IBA Harman Engineering Training College in Seaton, Devon, runs courses for Broadcast Engineers who operate and maintain the wide range of electronic equipment at our transmitting stations. The person we appoint will be responsible for maintaining laboratory equipment and preparing practical equipment displays to meet the needs of teaching demonstrations and equipment training tuition. Applicants should be qualified to HNC level (or equivalent) in electronics and have previous experience involving the use of electronic test equipment. Experience of maintaining television equipment would be an advantage. Salary will be on the range £8,450 - £10,490 according to qualifications and experience. Relocation expenses will be paid where appropriate.



\* An Equal Opportunities Employer \*

Please write or telephone for an application form quoting Ref: WW/828cc to Glynis Powell, Personnel Officer, IBA, Crawley Court, Winchester, Hampshire SO21 2QA. Telephone 822270.

(2376)

### THE SCIENTIFIC WIRE COMPANY

811 Forest Rd, London, E.17. Tel. 01-531 0574

ENAMELLED COPPER WIRE				
SWG	1lb	8oz	4oz	2oz
8 to 34	£3.63	£2.09	£1.10	£0.88
35 to 39	£3.82	£2.31	£1.27	£0.93
40 to 43	£6.00	£3.20	£2.25	£1.61
44 to 47	£8.67	£5.80	£3.45	£2.75
48	£15.36	£9.58	£6.38	£3.69

SILVER PLATED COPPER WIRE				
	£3.09	£5.20	£2.93	£1.97
14 to 30				

TINNED COPPER WIRE				
	£3.97	£2.41	£1.39	£0.94
14 to 30				
Fluxcore Solder	£5.90	£3.25	£1.82	£0.94

Prices include P&P and VAT. Orders under £2 add 20p. S.a.b. for list of copper and resistance wire. Dealer enquiries welcome. (9063)

**MILLENIUM MICROSYSTEM DESIGNER** with 8086 personality module, price £1,600 o.n.o. Also Powertran PS180 microcomputer and monitor, price £120. Tel. 041-644 3455 or write Clark, 54 Woodbank Crescent, Clarkston, Glasgow G76 7DR. (2398)

**CHEAP COMPONENTS.** Full spec items at unbelievable prices, also kits for magazine projects, and design, prototype manufacture of consumer and industrial systems. Piplet Marketing, Two Bridges, Blakeney, Glos. (2395)

### BRITISH ANTARCTIC SURVEY Electronic Engineer

The British Antarctic Survey requires an Electronic Engineer to join a team using a computer and microprocessor controlled high frequency radar, known as the Advanced Ionospheric Sounder (AIS), to study the high latitude ionosphere. The successful candidate will be required to maintain and operate the equipment at Halley, Antarctica (76°S, 27°W). He will also be encouraged to contribute to the research programme.

The engineer will be responsible for maintenance of the system hardware, encompassing a mini-computer, microprocessors, high power RF transmitter and a variety of instrumentation using both digital and analogue techniques. He will also need to be able to understand and modify the system software. The project team works in close co-operation with university and government groups, both in the UK and abroad, some of whom have their own equipment alongside the AIS (e.g. Fabroy Perot interferometer, all sky camera, riometer array).

As the station is isolated for most of the year, the ability to work without detailed supervision and to solve problems as they arise is paramount. The engineer will be expected to be adaptable and to take his share of the general base work.

The appointment will be for a period of approximately 39 months commencing in April 1984. After an initial period of hardware and software training in Cambridge, the successful candidate will sail for Antarctica in October 1984 to spend two Antarctic winters at Halley station. After completion of the Antarctic tour he may be required to spend a period from May 1987 in the United Kingdom undertaking development work.

Candidates should be graduates in Electronics, Electronic Engineering, Computer Science or Physics preferably with some relevant experience.

Salary: From £6,830 per annum plus annual increments.

Applicants should be physically fit, aged between 21 and 35 years and must be male as the nature and location of the work will require the successful candidate to live in premises provided by the British Antarctic Survey which are only equipped for male accommodation.

Low income tax. Clothing, messing and canteen are provided free on base and free messing on the voyage.

For an application form and further details, please write to: **The Establishment Officer, British Antarctic Survey, High Cross, Madingley Road, Cambridge CB3 0ET.**

Please quote ref: AS 3/84

Closing date for applications: 19th January, 1984.

**NATURAL ENVIRONMENT RESEARCH COUNCIL**

(2378)

### TO MANUFACTURERS, WHOLESALE BULK BUYERS, ETC. LARGE QUANTITIES OF RADIO, TV AND ELECTRONIC COMPONENTS FOR DISPOSAL

SEMICONDUCTORS, all types, INTEGRATED CIRCUITS, TRANSISTORS, DIODES, RECTIFIERS, THYRISTORS, etc. RESISTORS, C/F, M/F, W/W, etc. CAPACITORS, SILVER MICA, POLYSTYRENE, C280, C296, DISC CERAMICS, PLATE CERAMICS, etc.

ELECTROLYTIC CONDENSERS, SPEAKERS, CONNECTING WIRE, CABLES, SCREENED WIRE, SCREWS, NUTS, CHOKES, TRANSFORMERS, etc.

ALL AT KNOCKOUT PRICES - Come and pay us a visit ALADDIN'S CAVE

TELEPHONE: 445 0749/445 2713

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, North Finchley, London, N.12

(5 minutes from Tally Ho Corner)

(1613)

### LINSLEY HOOD DESIGNS

75Watt and 100W amps Audio Signal Generators

75Watt amp p.c.b. £2.30  
100Watt Mosfet p.c.b. £4.00

p&p 50p

S.A.E. for leaflets

TELERADIO ELECTRONICS  
325 Fore Street, London N9 0PE

(1762)

### TRANSPORTABLE HIGH TENSION TRANSFORMER

General Electric Model 152 Type 1

100 milliamps, 100 kV. Kenotron rectifiers. Fan motor cooling unit. Complete with covers and handle. Comprehensive instruction manual included. Realistic offers.

Mr M. Wright  
75 Cherry Road, Enfield, Middx  
01-443 1465 (2386)

### DEC FPP8-A

Complete "Fortran IV Accelerator Package" for PDP-8/E or 8/A, including very fast FP Processor, 12 slot Exp. Box and all OS8-F4 software

Price: £1,800 (o.n.o. schools only)  
Tel: Brussels 02-218 45 20 between 2-6 (2392)

### RACAL COMMUNICATION RECEIVERS

500kc/s to 30Mc/s IN 30 BANDS 1Mc/s WIDE - RA17 Mx11  
E100 - RA17L - E150 - RA17E - E225 NEW METAL LOU-  
VERED CASES FOR ABOVE £25 EACH ALL RECEIVERS ARE AIR  
TESTED AND CALIBRATED IN OUR WORKSHOP SUPPLIED  
WITH MANUAL AND DUST COVER IN FAIR USED CONDITION  
RACAL SYNTHESISERS (IDEAL FREQUENCY GENERATORS)  
MA3500 - SOLID STATE FOR USE WITH MA78 - RA17 -  
RA217 - RA1217, ETC. E100 to E150 - MA250 - 1Mc/s TO  
31.8Mc/s - E100 to E150 - MA2500 - PRECISION FRE-  
QUENCY STANDARD - 5Mc/s - 100kHz E100 to E150  
DUQUENOY RECEIVER TYPE C2647K - SOLID STATE -  
SINGLE CHANNEL - SSB - MAINS OR BATTERY POWERED -  
1.6 to 27.5Mc/s AND 400 - 535kHz - E100 WITH MANUAL  
REDIFON SSB RECEIVER TYPE R489 - SOLID STATE - 10  
FILTER CHANNELS RANGE 1.5 TO 30Mc/s AND 25KHz TO  
525KHz - POWER MAINS OR BATTERY - COMPLETE WITH  
ISB ADAPTOR AR110A - E100 WITH MANUAL REDIFON TTD  
OR T111 AUDIO TELEPRINTER CONVERTER - SOLID STATE -  
TESTED WITH CIRCUIT - £25 CREED TYPE 75 TELEPRINTER -  
50 AND 75 BAUDS FOR USE WITH ABOVE CONVERTOR - £25.

### OSCILLOSCOPES

CT438 DUAL BEAM OSCILLOSCOPES - 6Mc/s - £45  
TEKTRONIX 6A7A - 100Mc/s - DUAL TRACE - SOLID STATE  
E250 WITH MANUAL MARCONI T9995 SIGNAL GENERA-  
TORS FROM 2Mc/s OR 15Mc/s TO 220Mc/s AM - FM AZM.  
E30 - A3 E30 A5 E150 - WITH MANUALS T2606 DIF-  
FERENTIAL DC VOLT METER - 0 TO 1100 volts - E100 T2002  
AM SIGNAL GENERATOR - 10Kc/s TO 72Mc/s E200  
T2002AS - FM AND AM SIGNAL GENERATOR - 10Kc/s TO  
72Mc/s - E500 T2170B DIGITAL SYNCHRONIZER FOR ABOVE  
- E350 T21066B/5 - FM AM - SIGNAL GENERATOR -  
10Mc/s TO 470Mc/s - E500 T21245 CIRCUIT MAGNIFICATION  
METER AND T21245 OSCILLOSCOPE - £200 MARCONI AF WATT  
METER - 7 TO 11 GIGS - E150 608 - 10 - 420Mc/s  
E70 E12A - 450 - 1200Mc/s - E200 MARCONI AF WATT  
METER CT44 NOT ABSORPTION - 200 MICROWATTS TO 6  
TERESA AF WATT METER - 1 MILLIWATT TO 10 WATTS -  
2.5 Ohms TO 20K Ohms IN 48 STEPS - E65 THYRISTOR TEST  
SET - CT500 - VOLTAGES UP TO 2KV - E100 TEKTRONIX  
4002A GRAPHIC COMPUTER TERMINAL WITH JOYSTICK  
E400 TEKTRONIX 4601 - HARD COPY UNIT FOR USE WITH  
ABOVE - E150 - BOTH UNITS FOR - E500 RACAL DIGITAL  
COUNTERS: TYPE 801M - 725Mc/s - E50 RACAL 836 COUN-  
TER - 354Kc/s - E50

V.A.T. AND CARRIAGE ON ABOVE ITEMS EXTRA  
ALL ITEMS ARE BOUGHT DIRECT FROM H.M. GOVERNMENT,  
BEING SURPLUS EQUIPMENT PRICE IS EX WORKS, S.A.E. FOR  
ALL ENQUIRIES. PHONE FOR APPOINTMENT FOR DEMON-  
STRATION OF ANY ITEM

JOHN'S RADIO  
WHITEHALL WORKS, WHITEHALL ROAD EAST  
BIRKENSHAW, BRADFORD BD11 2ER  
TEL: (0274) 684007  
WANTED - REDUNDANT TEST EQUIPMENT RECEIVING AND  
TRANSMITTING EQUIPMENT - VALVES PLUGS AND  
SOCKETS - SYNCHROS, ETC. (948)

## SERVICES

### CIRCOLEC THE COMPLETE ELECTRONIC SERVICE

Artwork, Circuit Design, PCB Assembly, Test & Repair Service, Q.A. Consultancy, Prototypes, Final Assembly. Full PCB Flow Soldering Service.  
Quality workmanship by professionals at economic prices.  
Please telephone 01-646 5686 for advice or further details.

**TAMWORTH MANOR**  
302-310 COMMONSIDE EAST, MITCHAM

(1391)

### ANALOG COMPUTERS LIMITED

chartpak  
stockist

Design & Development, Complete Artwork Service, Camera Work, Prototype thru to Production PCB Manufacture/Assy.

5 Cork Street, Eccles, Maidstone, Kent, ME20 7HG  
TELEPHONE 06221 79987 TELEX 965633

(2348)

### FOR THE BEST PCB SERVICE AVAILABLE

- ★ Circuit Design & Development  
Digital and Analogue
  - ★ Artwork Layout  
Work of the highest standard by experienced draughtsmen. No minimum charge.
  - ★ Board Manufacture  
Prototype to semi-production, excellent rates, 24-hour prototype service from filerwork.
  - ★ Wiring & Assembly  
PCB assembly, wiring and cable forming by qualified staff.
  - ★ Test  
Full test facilities available.
- One or all services available, no order too small. Please telephone Chelmsford (0245) 357935, or write to HCR Electronics, The Industrial Unit, Parker Road, Chelmsford.



(1169)

### Thamescity Limited

Electronic (Analog and Digital), electro pneumatic and control systems, R. & D. facilities for long or short run assembly and test to your design or ours at our new Maidstone facility.

48 Southwark Street  
London SE1 1UN  
Tel. 01-407 7441  
Telex: 8954665

(2281)

**DESIGN AND CONSULTANCY** of microprocessor, digital and analogue equipment. Complete service from feasibility and design to prototype and commissioning. Advice on test and design of dedicated test equipment or ATE. DPM Electronics, 24 Timberrmans View, Basildon, Essex. Tel. 0268 558831. (2295)

## BOX NOS.

Box number replies should be addressed to:

Box No.....  
c/o Wireless World, Quadrant House  
The Quadrant, Sutton, Surrey SM2 5AS

## ARTICLES FOR SALE

**BRIDGES**, waveform/transistor analysers. Calibrators, Standards. Millivoltmeters. Dynamometers. KW meters. Oscilloscopes. Recorders. Signal generators - sweep, low distortion, true RMS, audio, FM, deviation. Tel. 040 376236.

**VALVES, PROJECTOR Lamps**, 6000 types, list 75p, world wide export. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. Phone (024 366) 2023. (1991)

**LAMPS AND CABLE**. Large amount of lamps and cable for sale - all types and sizes, domestic and industrial. Telephone MIRAGE LIGHTING on HITCHIN (0462) 733388 between 10am-7pm. (1809)

**ENCAPSULATING EQUIPMENT** for coils, transformers, components, degassing silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment, low cost, used and new. Also for CRT regaining metallising. Research & Development. Barratts, Mayo Road, Croydon CR0 2QP. 01-684 9917. (9678)

**EX WD Radio equipment** and test equipment. Over 500 sets in stock from £8. Send 50p for illustrated catalogue (including £1 voucher). Weirhead Ltd. 129 St. Albans Road, Watford, Herts. Tel: Watford (0923) 49456. (1974)

## CAPACITY AVAILABLE

### TW ELECTRONICS LTD THE PCB ASSEMBLERS

More and more companies are investigating the advantages of using a professional subcontractor. Such an undertaking requires certain assurances.

TW are able to satisfy all of them - quality, competitive pricing, firm delivery and close co-operation with the customer.

Assembled boards at 100% inspected before flow soldering and reinspected after automatic cropping and cleaning.

Every batch of completed boards is issued with a signed certificate of conformity and quality - our final assurance.

For further details, contact us at our new works:

**Blenheim Industrial Park**  
Bury St. Edmunds  
Suffolk IP33 3UT

Telephone: 0284 3931 (1466)

## P.C.B.'s

Printed Circuit Boards to your specification from artwork through to finished board.

QUICK DELIVERY -  
COMPETITIVE PRICES

## CROFTON ELECTRONICS LIMITED

35 Grosvenor Road,  
Twickenham, Middlesex  
TEL 01-891 1923/1513 Telex: 295093

**FREE PROTOTYPE** of the finest quality with EVERY P.C.B. artwork designed by us. Competitive hourly rates, and high standard of work. Halstead Designs Limited. Tel: Halstead (0787) 477408. (2126)

**BATCH PRODUCTION** wiring and assembly to sample or drawings. McDeane Electricals Ltd., 19b Station Parade, Ealing Common, London W5. Tel: 01-992 8976. (169)

### EPROM PROGRAMMING

From list and/or existing EPROM for most 5v N.MOS types. Charge £2.50 + 12 pence per 32 words manually entered. Erasing and EPROMS also available.

**Bendley Chipware**  
28 Boroughgate  
Appleby  
Cumbria CA16 6AG  
Tel: 0930 51027

(2202)

### MENDASCOPE LTD

Repair and recalibrate  
oscilloscopes

All makes - all models

**MENDASCOPE LTD**  
Otter House, Weston Underwood  
Olney MK46 5JS  
Tel: Bedford (0234) 712445

(2230)

**TURN YOUR SURPLUS** Capacitors, transistors, etc, into cash. Contact COLES-HARDING & Co., 103 South Brink, Wisbech, Cambs. 0945-4188. Immobile settlement. We also welcome the opportunity to quote for complete factory clearance. (9509)

**DESIGN AND DEVELOPMENT. ANALOGUE, DIGITAL, RF AND MICROWAVE CIRCUIT AND SYSTEM DESIGN.** Also PCB design, mechanical design and prototype/small batch production. - Adenmore Limited, 27 Longshot Estate, Bracknell, Berks. Tel: Bracknell (0344) 52023. (656)

**DESIGN SERVICES.** Electronic design development and production service available for digital and analogue instruments. RF Transmitters and receivers, telemetry and control systems. 20 years' experience. R.C.S. Electronics, Wolsey Road, Ashford, Middlesex. Phone Mr Falkner 53661. (834)

### PCB/ELECTRONIC ASSEMBLY

- ★ Circuit Design & Development
- ★ Prototyping
- ★ Pre-production Consultancy
- ★ Full Production Capability
- ★ Component Sourcing & Stocking
- ★ Complete Test Facilities

**STAGECRAFT (ELECTRONICS) LTD**  
3 Churchfield Road  
Acton Central, W3 6BH

Tel: 01-993 1852/3660

(2203)

## ARTICLES WANTED

### SURPLUS

We offer good prices for test equipment, components, redundant computers, PCB's connectors. Immediate settlement.

**TIMEBASE**  
94 Alfriston Gardens  
Sholing, Southampton SO2 8FU  
Telephone: (0703) 431 323

(1832)

### ANTIQUE RECEIVING VALVES

Unused and boxed  
In large quantity

Tsutom Yoshihara  
C1-105, Deguchi-cho 34  
Suita-shi, Osaka 564  
JAPAN

(2055)

### WANTED

Scrap and re-usable mainframe computer and industrial electronic equipment.

**E.M.A. Telecommunications Engineers, Orford, Woodbridge, Suffolk. Tel. 039-45 328.**

(1720)

**SMALL BATCH PCBs**, produced from your artwork. also DIALS, PANELS, LABELS. Camera work undertaken. FAST TURNAROUND. Details: Winston Promotions, 9 Hatton Place, London EC1N 8RU. Tel. 01-405 4127/0960. (9797)

**PX25, PP5/400, PX4, PP3/250 VALVES**, new or used, high prices offered. All other valves considered for purchase, small or large quantities. Vintage Wireless Co., Cossham Street, Mangotsfield, Bristol BS17 3EN. Tel. 0272 565472. (2360)

## WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap, and quantity. Prompt service and cash. Member of A.R.R.A.

### M & B RADIO

86 Bishopsgate Street  
Leeds LS1 4BB  
0532 35649

**PHONE YOUR  
CLASSIFIEDS TO  
IAN FAUX ON  
01-661 3033**



## P8000 – THE PRODUCTION PROGRAMMER THAT HANDLES ALL NMOS EPROMS



**NEW  
PRODUCT**

- Checks, Programs, Compares up to 8 devices simultaneously
- Handles all NMOS EPROMS up to projected 128K designs with no personality modules or characterisers – See list
- Easy to use, menu driven operation for blankcheck, program, verify, illegal bit check, checksum, self-test
- Constant display of device type, mode and fault codings
- Individual socket LED indicators for EPROM status
- Comprehensive EPROM integrity checks – Illegal bit check, data and address shorts, constant power line monitoring
- Full safeguard protection on all sockets
- Automatic machine self-test routine
- RS232C interface supplied as standard
- Powered down sockets
- Cost effective price – £695 + VAT
- Available from stock

Write or phone for more details

**DISTRIBUTORS REQUIRED**

**EXPORT ENQUIRIES WELCOME**


**GP Industrial Electronics Ltd.**

Tel: Plymouth (0752) 332961  
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

2704  
2708  
2716(3)  
2508  
2758A  
2758B  
2516  
2716  
48016  
2532  
2732  
2732A  
68732-0  
68732-1  
68766  
68764  
2764  
2564  
MK2764  
25128  
27128

# FERRANTI ZN451 EVALUATION KIT

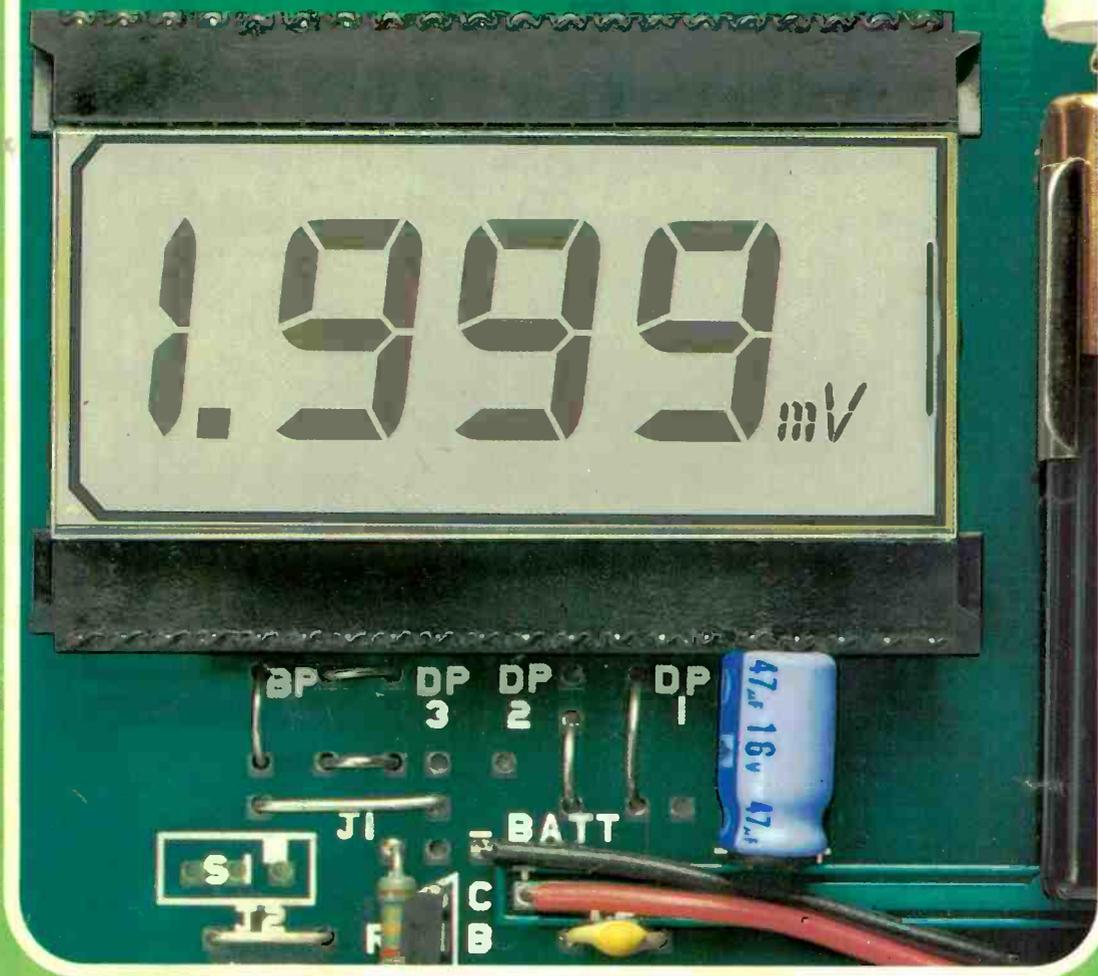

# Better by design

## If you're the sensitive type, check out the new ZN451 DVM.

Measuring microvolt signal levels is easy with the new ZN451 DVM IC. It's the first DVM that auto-zeroes external signal conditioning circuits to give full-scale readings as low as  $\pm 1.999$  mV with no zero adjustment.

Two logic outputs are provided to control external analogue switches, allowing op-amps and other circuits to be put inside the auto-zero loop and have their offsets cancelled by the ZN451's digital auto-zero system.


Use the ZN451 with pressure transducers, thermocouples, strain gauges or any low output transducer.

To make it even easier there's the ZN451 Evaluation Kit, which contains everything\* you need to make a 2mV DVM, available from your Ferranti distributor price £29.50 inc. VAT.
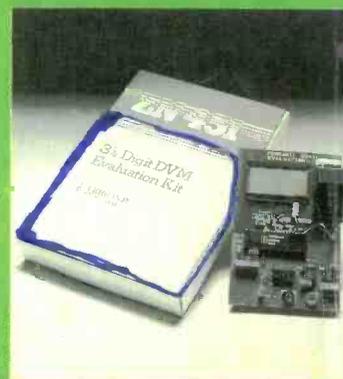
### Distributors:

Celdis, Reading, Tel: 0734 585171  
Farnell Electronic Comps., Leeds,  
Tel: 0532-636311  
Intel Electronics, Henlow,  
Tel: 0462 812505  
STC Electronic Services, Harlow,  
Tel: 0279 26777  
Midwich Computer Co., Bickingham,  
Tel: 0379 898751  
Semicomps, Keighley, Tel: 0535 65191  
Semicomps, Kelso, Tel: 0573 24366  
Swift-Sasco, Crawley, Tel: 0293 28700

Ferranti Electronics Limited,  
Fields New Road, Chadderton,  
Oldham OL9 8NP, England.  
Tel: 061-624 0515 and 061-624 6661  
Telex: 668038



\*Batteries not included

# FERRANTI Semiconductors

WW-003 FOR FURTHER DETAILS