

**150MHz RF signal generator – 15% off**

# ELECTRONICS WORLD

Austria Asch. 65.00  
Denmark DKr. 66.00  
Germany DM 15.00  
Greece Dra. 1000.00  
Holland Dfl. 11.50  
Italy L. 8500.00  
Malta Lm. 1.45  
IR £3.30  
Singapore S\$12.60  
Spain Pts. 800  
USA \$5.50

INCORPORATING WIRELESS WORLD

A REED BUSINESS PUBLICATION  
SOR DISTRIBUTION

February 1997 £2.25

**SUBWOOFER  
FLAT TO 15HZ**

**Zeros in  
pictures**

**Is coaxial best  
for speaker  
cable?**


**Beyond Marconi**

**CAD software  
on the Net**

**FPGA design**

**Wow and  
flutter meter**

**Speaking  
monitor**

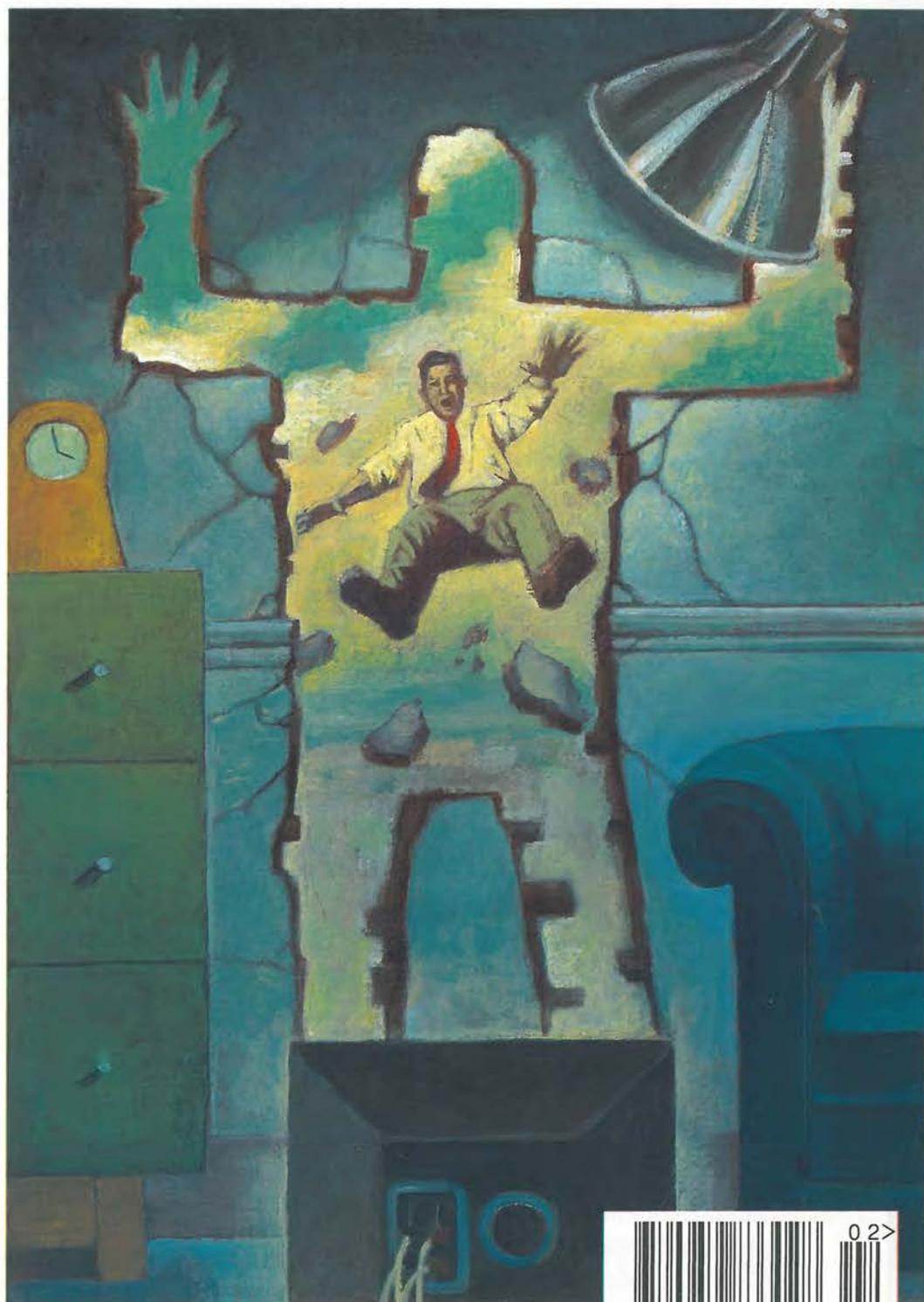

**Extended offer – DPM for less than £9**




# Small Awkward PROBLEMS? BIG No Time SOLUTION!


PIC based TOOLS to help you realise your project:  
from single applications to full scale production
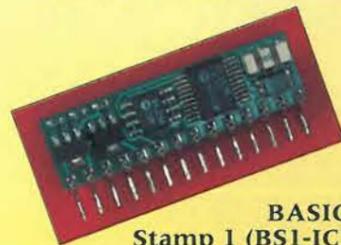
## BASIC STAMPS®

PIC based BASIC Stamps are perfect for one-off and low volume applications. Their easy to learn but powerful BASIC syntax (with familiar instructions such as GOTO, FOR ... NEXT, and IF ... THEN as well as instructions for serial I/O, pulse measurement, button debounce, DTMF, X-10 etc) will get your application up and running in hours. Once programmed, the Stamp runs independently of your PC and programs are stored in non-volatile EEPROM so they can be changed at will. Detailed manuals cover many commonly needed routines and the Stamp is well supported by a growing list of custom application kits to cut development time even further. Available in two formats:



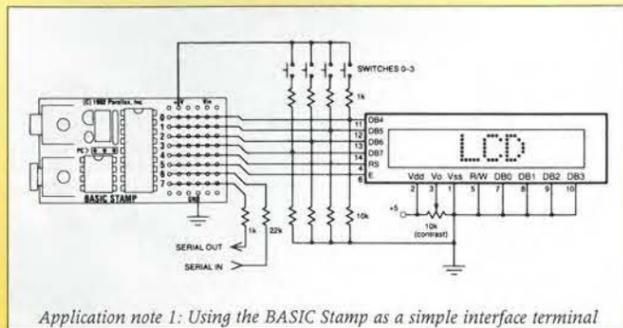**BASIC Stamp 1 (BS1-IC)**  
8 I/O Lines  
up to 80 program lines  
Comms to 2400 baud  
35x10mm size  
£29 single price



Application note 1: Using the BASIC Stamp as a simple interface terminal  
Typical Application



**BASIC Stamp 2 (BS2-IC)**  
16 I/O Lines  
up to 500 program lines  
Comms to 50 kbaud  
24pin DIP package  
£49 single price

BASIC Stamp Development Kits including PC software, manuals, 24+ application notes, downloader cables, Stamp (BS1-IC or BS2-IC) and corresponding Project Board - £99 / £119

## PIC16Cxx DEVELOPMENT TOOLS

For medium to large volumes and high speed requirements, the popular range of PICs is hard to beat. We offer an extensive range of programmers, emulators and associated hardware to support the following PICs: 52 54 55 56 57 58 620 621 622 61 62 63 64 65 71 72 73 74 84

### PIC16Cxx Programmer




Also stocked  
\* ZIF sockets  
\* SOIC/SSOP/PLCC adapters  
\* Prototyping boards  
\* Compilers/Simulator

OVER 5000 SOLD
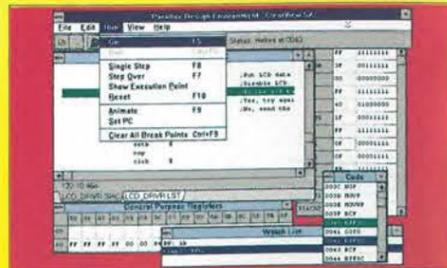
### In Circuit Emulators

- \* True hardware emulation of program memory, registers and I/O
- \* Unlimited breakpoints.
- \* Single stepping
- \* Software-programmable oscillator
- \* Windows Environment
- \* Runs from 32Khz to 10Mhz ('xx) and 20Mhz ('5x)
- \* Source level debugging for PASM(X), MPASM and MPC
- \* Optional trace facility




**Milford Instruments**  
Milford House, 120 High Street,  
SOUTH MILFORD LS25 5AQ  
01977 683665 Fax 01977 681465

Please call or fax to receive our catalogue and price list. All prices exclude VAT and £3 shipping. BASIC Stamp & the Parallax logo are registered trademarks of Parallax, Inc.

**PARALLAX**  
3805 Atherton Road, #102  
Rocklin, CA 95765 USA  
916-624-8333, Fax 916-624-8303  
<http://www.parallaxinc.com>

# Contents

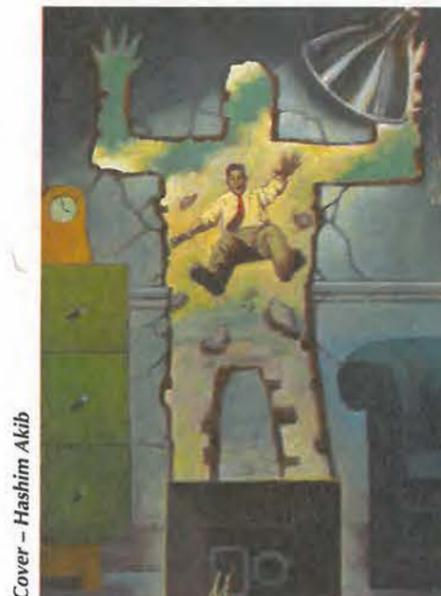

Cover - Hashim Akib

### 133 DESIGNING POWER SUPPLIES

**Ray Fautley** presents an easy-to-use procedure for designing reliable full-wave rectifiers of the centre-tapped secondary variety.

### 140 MAKING CONTINUOUS WAVES

**Tom Ivall** looks at the race to develop radio following Marconi's patent.

### 152 HANDS-ON INTERNET

**Cyril Bateman** describes his latest Spice discoveries on the net, among them fully working evaluation packages.

### 156 PHASE COMPARATOR PURITY

**Edward Forster** explains why the future of the traditional phase-comparator's charge pump looks questionable.

### 104 ROARING SUBWOOFER

Flat to 15Hz, small, fast, high sound pressure level and easily tailored to suit your existing equipment - a combination made possible through motional feedback.

### 110 MULTI-CHANNEL MONITOR

Triggered by a logic signal on one of its four channels, **Heikki Kalliola's** speaking monitor reads out a four-second message - digitally recorded and readily re-recorded.

### 113 MORE IN THE PICTURE

Ian Hickman looks at more ways in which circuit operation can be expressed graphically.

### 119 SPEAKER CABLE MEASUREMENTS

Could coaxial cables be best for wiring your loudspeakers? **Cyril Bateman's** measurements suggest they might be.

### 126 GATES OPEN UP

A quad c-mos gate forms the heart of a frequency meter, a step-down switcher or a negative supply generator, shows **Rae Perälä**.

### 128 OVERLOAD MATTERS

**Doug Self** takes a look at the complex problem of preamplifier overload.

### 130 PROGRAMMABLE LOGIC PRIMER

**Geoff Bostock** describes standard logic families in this first article based on his book 'FPGAs and Programmable Logic'.

### 163 WOW-FLUTTER METER


Analogue recording and playback systems suffer from speed fluctuations that usually worsen with age. **Christopher Kuni's** meter quantifies the problem.


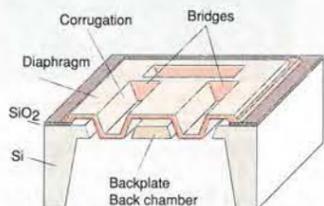
### Special offers

Exclusive 15% discount on a 100kHz to 150MHz rf generator with internal modulator, see page 112.

Panel meters for less than £9 - this exclusive special offer has been extended, see page 138.



Advances in mic-on-a-chip technology promise better fidelity and improved sensitivity - see page 98.

## Regulars

### 91 COMMENT

Europhile or Europhobe?

### 92 NEWS

Digital tv fears, DECT on one chip, Taiwan d-ram myth, Learning computer, 40Gbit/s amp, MPEG-4, new DVD players.

### 98 RESEARCH NOTES

Chip mic, **Sun-powered aircraft**, atmospheric electricity, **PCB warp**.

### 146 CIRCUIT IDEAS

**Valve amplifier**, Noise-immune antenna, FM mic, **Battery saver**, 386 write protector.

### 159 NEW PRODUCTS

Pick of the month - classified for convenience.

### 171 LETTERS

LV Directive, headphone stereo, CAD inadequacy, Phase-shifting solution.



Rotary spark transmitter - believed to be sending news of Britain's declaration of war with Germany in 1914; see page 140.

**MARCH ISSUE ON SALE 6 FEBRUARY**

# The Art Of In-Circuit Emulation

plate<...  
ptr,  
lic:  
ss rangeError()...  
rap() {  
= new T [sz];  
pwrap c  
operator() (int) throw rangeError  
if (i >= 0 && i < sz) return p[i];  
throw rangeError();  
}

Contact us now for comprehensive information on the Hitex range of state-of-the-art microprocessor tools.  
Hitex (UK) Ltd. TEL: 01203 692066 FAX: 01203 692131  
Email: sales@hitex.demon.co.uk  
CompuServe: 100646.1526

hitex CIRCLE NO. 196 ON REPLY CARD

## M&B RADIO (LEEDS)

### THE NORTH'S LEADING USED TEST EQUIPMENT DEALER

<b>OSCILLOSCOPES</b>			
HP 3111D 500 MHz digitizing scope (colour display)	£1300	MARCONI TF2018A 80 KHz-520 synthesized	£1000
HP 5412D 100 MHz 4 channel digitizing scope (colour)	£2350	MARCONI TF2018 10 MHz-520 MHz	£350
HP 54201D 300 MHz 2 channel digitizing (77 channels logic state triggering)	£1900	MARCONI TF2008 10 KHz-510 MHz RF generator	£300
TEKTRONIX 2320 100 MHz 2 channel digital storage	£1500	MARCONI 4055B 850 MHz-2150 MHz signal source	£215
TEKTRONIX 2445 150 MHz 4 channel GPIB	£1400	TEKTRONIX 5054B 2 GHz-4 GHz signal source	£225
TEKTRONIX 2248 100 MHz 4 channel oscilloscope	£1400	MARCONI TF2000 20 Hz-20 KHz audio oscillator	£135
TEKTRONIX 222 10 MHz portable digital storage	£750	FLUKE 401A 10 Hz-11 MHz synthesized signal generator	£1000
TEKTRONIX 475A 250 MHz 2 channel	£650	ROHDE & SCHWARTZ APN63 0.1 Hz-240 KHz LF gen. (new)	£2000
TEKTRONIX 475 100 MHz 2 channel	£495	FARNELL SSC2000 10 KHz-2000 MHz synthesized	£2000
TEKTRONIX 444 100 MHz 2 channel storage	£450	WILTRON 618D501 1 MHz-1300 MHz sweeper+log meter	£750
TEKTRONIX 465B 100 MHz 2 channel	£475	GIGA GR1101A 12 GHz-18 GHz pulse generator	£400
TEKTRONIX 445 100 MHz 2 channel	£450	POLARAD 1109EL 800 MHz-2.2 GHz generator	£400
TEKTRONIX SC5047M503/DH501 80 MHz-DVM	£450	POLARAD 1104E711020T 1.8 GHz-4.6 GHz with modulator	£400
TEKTRONIX 434 15 MHz 2 channel storage	£300	PHILIPS PM526 100 KHz-125 MHz RF generator	£400
TEKTRONIX 314 10 MHz 2 channel storage	£400	ADRETE 2230A 190 Hz-1 MHz synthesized source	£195
TEKTRONIX 2213 60 MHz 2 channel	£375	FARNELL LPM 3 audio oscillator	£150
TEKTRONIX 2215 60 MHz 2 channel	£400	WAYTEK 193 20 MHz sweep modulation generator	£400
TEKTRONIX 5113 storage mainframe (new)	£275	WAYTEK 171 2 MHz synthesized function generator	£300
TEKTRONIX 212 KHz 2 channel handheld battery portable	£195	THANDAR TG583 0.005 Hz-5 MHz pulse/function generator	£235
PHILIPS PM 3375 100 MHz 2 channel	£1650	SAYROSA MA 30 10 Hz-100 KHz	£175
PHILIPS PM 3055 50 MHz 2 channel	£425		
PHILIPS PM 3057 50 MHz 2 channel	£425		
PHILIPS PM 3217 50 MHz 2 channel	£400		
PHILIPS PM 3244 50 MHz 2 channel	£325		
IWATSU SS1122 100 MHz 4 channel with cursors	£800		
IWATSU SS 5710 60 MHz 4 channel	£400		
LEADER LB0514L 40 MHz 2 channel	£300		
HITACHI Y1190 100 MHz 4 channel with cursors	£750		
GOULD 420 MHz DSO 2 channel 4 colour hardcopy	£1400		
GOULD OS100 20 MHz 2 channel	£200		
GOULD OS400 10 MHz 2 channel digital storage	£195		
GOULD OS250B 15 MHz 2 channel	£145		
UNADHM G500 DT 20 MHz 2 channel (compare)	£160		
BALLANTINE 1022B 25 MHz 2 channel portable	£225		
<b>SPECTRUM ANALYSERS</b>			
TEKTRONIX 2710 10 KHz-1.8 GHz	£4000		
TEKTRONIX 2710 10 KHz-1.8 GHz OPT 001003014 new	£4950		
TEKTRONIX 7L1L3 10 KHz-1.8 GHz mainframe	£1000		
TEKTRONIX 7L1L3 OPT 25 tracking gen. mainframe	£1000		
HP8754A 4 MHz-1300 MHz network analyser	£2000		
HP84101A 1A network analyser 110 MHz-12.4 GHz	£800		
HP8548B 100 Hz-1.5 GHz High spec.	£4000		
HP 3562A 64 units-100 KHz dynamic signal analyser 1 year HP Cal.	£4000		
HP 3580A 5 Hz-50 KHz audio analyser	£850		
HP 1407B552B/8553B 1 KHz-110 MHz	£450		
HP 1417B552B/8554B 100 KHz-1250 MHz	£1000		
HP 1417B552B/8555A 10 MHz-18 GHz	£1700		
TEKTRONIX TF2370 30 Hz-110 MHz digital storage	£1100		
BRUEL & KJAER 2033 20 Hz-20 KHz audio	£100		
<b>SIGNAL GENERATORS</b>			
HP 8904A DC-500KHz multifunction synthesizer	£4000		
HP 3314A 0.001 Hz-9.99 MHz function/waveform monitor	£2950		
HP 3354C 50 Hz-32.5 MHz selective level meter	£1750		
HP 8483D 2.3 GHz-13 GHz OPT 0010003 solid state generator (as new)	£2950		
HP 8620C/8620B 1 GHz-4.2 GHz sweeper	£2000		
HP 8620C/8621B 18 GHz-4.2 GHz sweeper	£1000		
HP 8620C sweeper mainframes (as new)	£250		
HP 81 12A 50MHz programmable pulse generator	£1500		
HP 8454B 10 MHz-520 MHz RF generator	£200		
HP 3200B 10 MHz-500 MHz oscillator	£400		
HP 3314B 10 Hz-21 MHz synthesizer/level meter	£4000		
HP 3320A frequency synthesizer 0.1 Hz-13 MHz	£450		
HP 3312A 0.1 Hz-13 MHz function generator	£400		
HP 3310B 0.0005 Hz-5 MHz function generator	£200		
HP 8005B 0.3 Hz-20 MHz pulse generator	£375		
TEKTRONIX 1901 time mark generator	£250		
MARCONI TF2022C 10 KHz-100 MHz synthesized	£2350		
MARCONI TF2019A 80 KHz-1040 MHz synthesized	£2000		
ALL PRICES PLUS VAT AND CARRIAGE • ALL EQUIPMENT SUPPLIED WITH 30 DAYS WARRANTY			
86 Bishopsgate Street, Leeds LS1 4BB			
Tel: (0113) 2435649 Fax: (0113) 2426881			

**EDITOR**  
Martin Eccles  
0181 652 3128

**CONSULTANTS**  
Jonathan Campbell  
Philip Darrington  
Frank Ogden

**DESIGN**  
Alan Kerr

**EDITORIAL ADMINISTRATION**  
Jackie Lowe  
0181-652 3614

**E-MAIL ORDERS**  
jackie.lowe@rbp.co.uk

**ADVERTISEMENT MANAGER**  
Richard Napier  
0181-652 3620

**DISPLAY SALES EXECUTIVE**  
Malcolm Wells  
0181-652 3620

**ADVERTISING PRODUCTION**  
0181-652 3620

**PUBLISHER**  
Mick Elliott

**EDITORIAL FAX**  
0181-652 8956

**CLASSIFIED FAX**  
0181-652 8956

**SUBSCRIPTION HOTLINE**  
01622 778000

**SUBSCRIPTION QUERIES**  
01444 445566  
FAX 01444 445447

**ISSN 0959-8332**

**NEWSTRADE ENQUIRIES**  
0171 261 7704

**REED BUSINESS INFORMATION**

## Europhile or Europhobe?

Europhile or Europhobe? It's the political question of the day. But there's one Euro-issue on which the electronics industry should be agreed - the value of pan-European research projects.

Look at the chip business. "In the early eighties everyone was saying that the European chip industry was dead", remembers Pasquale Pistorio president of SGS-Thomson Microelectronics. Then came collaboration.

First the Siemens-Philips 'Megaproject' to get Europe up to speed on first memory technology, then JESSI added a pan-European dimension to the German-Dutch formula, now the EU is backing the JESSI successor programme MEDEA which is open to all nationalities.

"Fifteen years ago people were saying 'microelectronics is not a European kind of thing - we'll buy that in from the Americans and the Japanese'", says Horst Nasko, the chairman of JESSI and MEDEA.

Now, in the myriad disciplines which constitute a microelectronics infrastructure - from materials through to production equipment - Europe has world-class performers.

And no one could deny that our three largest microelectronics companies - Philips, Siemens and SGS - are world-class in both technology and market clout. Philips top \$4bn in chip sales while Siemens and SGS have chip revenues of over \$3bn.

In a decade and a half, these companies have been transformed into serious players with which major worldwide companies want to collaborate, as witness the IBM/Toshiba/Motorola/Siemens alliance on memory technology.

So collaboration works - as the Japanese showed in the seventies, the US Sematech programme showed in the eighties, and the Europeans showed in the nineties.

Not that we had much to do with it. Shamefully the UK's contribution to JESSI was about a tenth of the contribution of Germany or France, about a quarter that of Holland, and about the same as that of Portugal.

Now, with MEDEA coming up for funding, it looks as if the same thing is going to happen again. The provisional commitment from governments is: Germany 32 per cent; France 29 per cent; Holland 19 per cent; Italy 10 per cent; Belgium 4 per cent and the rest of Europe 6 per cent. To our shame we are in the ROE group.

Moreover the UK DTI - an organisation supposed to be helping UK industry - has decided it will only pay 25 per cent of a project's funding whereas every other country is paying 38 per cent.

As if to rub in its contempt, the DTI has also put a ceiling of £250,000 on the UK government's contribution to any one project. This effectively debars British companies from involvement in projects costing over £1m - a pitiful sum in chip research terms. Under MEDEA accounting procedures, £1m buys an eight man project lasting one year. No big deal.

So there we have it - an attitude from the UK government that is mean-spirited, petty and chauvinistic. "The attitude is more in line with people who think Europe is something the other side of the Channel", acidly comments Dr Jurgen Knorr, group president of Siemens Semiconductor and chairman of the semiconductor committee of the European Electronics Components Manufacturing Association (EECA).

**Electronics World** is published monthly. By post, current issue £2.35, back issues (if available) £2.50. Orders, payments and general correspondence to **L333, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.** Tel: 892984 REED BP G. Cheques should be made payable to Reed Business Information Ltd. **Newstrade:** Distributed by Markelforce (UK) Ltd, 247 Tottenham Court Road London W1P 0AU 0171 261-5108.

**Subscriptions:** Quadrant Subscription Services, Oakfield House Perymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address. Subscription rates 1 year £30 UK 2 years £48.00 3 years £70.00. Surface mail 1 year £35.00 2 years £56.00 3 years £80.00 Air mail Europe/Eu 1 year £43.00 2 years £68.00 ROW 1 year £52.00 2 years £83.00



...look at Eurofighter - a project costing \$40bn that has no apparent purpose...

Our government is something else. When it takes a shine to a scheme it will shovel out the money like a drunken sailor. Look at the grants being paid to Hyundai of Korea to set up a microelectronics factory in Fife - said to amount to several hundred million pounds. Lucky Goldstar and Siemens have also been given £100m+ financial inducements to set up microelectronics companies in the UK. Or look at Eurofighter - a project costing \$40bn that has no apparent purpose at all or at the really stupid 'Millennium Dome'.

Oh yes! We can dish out the lolly all right - no shortage at all when it comes to a pet government project - but when it comes to something not close to the government's heart it can be horribly mean.

Nowadays the cost of research is so great that not even regions, let alone countries, can afford to do it all alone. As Klaus Rupf from Germany's Ministry of Education, Science, Research and Technology told JESSI's last meeting, "If we really want to be world competitive we have to include partners from countries in other regions of the world."

The DTI has to wince up to the world. Otherwise the UK will be heading back to the days when we painted our backsides blue while continental Europe heads for a high-tech future.

**David Manners**

**Overseas advertising agents:** France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Roy Barnes, Reed Business Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel: (212) 679 8888 Fax: (212) 679 9455  
**USA mailing agents:** Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. 2nd class postage paid at Rahway NJ Postmaster. Send address changes to above.  
**Printed by:** BPCC Magazines (Carlisle) Ltd, Newtown Trading Estate Carlisle, Cumbria, CA2 7NR  
**Typeset by:** Marlin Imaging 2-4 Powerscrot Road, Sidcup, Kent DA1 4 SDT

© Reed Business Information Ltd 1997 ISSN 0959 8332

## Fears surround UK digital tv

Britain 18 SET to become a backwater in digital television thanks to the regulations announced by the Department of Trade and Industry late last year, writes Svetlana Josifovska.

According to the regulations, which although preliminary are close to being finalised, broadcasters wanting access to various digital technologies will need to ask the owners/controllers of the conditional access (C.A.) systems (needed for subscription) for a license. This, supposedly, will be granted "on a fair and non-discriminatory" basis, with OfTel acting as the watchdog.

Broadcasters such as the BBC, Channel 4 and others, fear that the regulations are not tough enough to guarantee open access and common set-top box standards. The broadcasters state that any digital tv operator should provide access to other service providers' technologies to ensure audiences have a choice. They also argue that CA-system owners should be made to license the technology to ensure common specifications.

The regulations threaten to delay the launch of digital satel-

## Britain cool on Euro R&D

Fears for the UK's high technology future have escalated after the British displayed a minimal commitment to collaborative European R&D at last week's JESSI Day, which kicked off a four year microelectronics research programme.

"The UK needs to get its act together - we're so late getting involved," John Brothers, technical director of GEC-Plessey Semiconductors, told EW. "If we want to get a share of the action we've got to get involved in things that much earlier."

The programme, called MEDEA (Microelectronics Development for European Applications), proposes to send 2bn ECUs (\$2.5bn) over the next four years to maintain the renaissance in Europe's high-tech fortunes following the previous Megaproject JESSI European collaborative research programmes.

Brothers said that GPS would like to get involved in projects such as a SMIF (mini-environment) project. GPS is a leader in having a fully integrated mini-environment wafer fab.

lite television, originally scheduled for late 1997. Broadcasters, such as BSKyB, were waiting for the regulations before ordering the set-top boxes.

"At first glance, these regulations would seem to be stricter than all other countries with digital television," stated BSKyB.

"It is clearly in the interest of government and BSKyB that a workable solution is found to ensure that a digital launch is achieved during 1997," said Barry Rubbery, CEO at set-top box maker Pace.

David Manners  
Electronics Weekly

## DECT on one chip

VLSI Technology has released a single-chip baseband design for DECT, the micro-cellular in-building cordless phone system.

Called Vega, the chip has a dedicated DECT (digital enhanced cordless telecommunications) processor, a general purpose cpu and interfaces including those for microphone, speaker and keyboard. The only things not present are an lcd controller and the processor's rom.

Patrick Edmond, a spokesman for VLSI, said: "Once a firmware design is stable, we can add the customer's rom into a custom Vega chip."

Vega is designed for use in handsets and base stations. VLSI claims that the DECT processor is comprehensive enough to leave the cpu, which is an ARM Thumb, with nothing to do once a call has been established. Edmond said: "In a handset, the cpu can be shut down to conserve power, or it can be used for performance enhancement like echo cancellation in base stations."

Making a chip that serves base stations and handsets could leave room for a competitor to undercut VLSI in handsets which do not require the full power of the Thumb.

Edmond said: "The Thumb core takes only the same die area as a conventional eight-bit cpu core, and it is becoming a standard in handset applications, so there isn't really any scope to make a lower-cost handset chip. There is no such thing as a half Thumb."

Sample silicon for Vega (VWS23101) is available and production volumes are planned for the second quarter of 1997.

Steve Bush  
Electronics Weekly



Raphael, a tool from Technology Modelling Associates, analyses the effects of parasitic interconnect in IC designs. When used with TMA Visual, the design can see the simulation results, in this case the electrical potential distribution in a static ram when the bit line is set to a higher voltage.

# HART

The Home of *Hi-Finesse*. Its not what you do, its HOW you do it that counts!

## VISATON® SPEAKER KITS & DRIVE UNITS

New to the UK, VISATON offer a range of speaker kits and drive units that give the home builder access to units and designs that are unrivalled for quality, performance and value. Their designs are very well known in Germany, where they are based, and over 25 years they have built up an enviable reputation for high quality sound. All their designs come from a solid background of the best in design and research and their factory contains one of the largest anechoic chambers in the World, backed up by the very latest in computerised test equipment. This quality of research facility, added to design collaboration with major universities and high end magazines, produces products of impeccable performance and value that are the best available to the home speaker builder! Their range of products covers the whole spectrum of sound reproduction and includes speaker kits for home cinema, hi-fi and car use. There is also a vast range of drive units from 15" woofers to ribbon tweeters. Speaker design software and database are available for the home user who wants to try his hand, or for commercial manufacture. A small selection follows, our lists will give you more!

### ASM100 ACTIVE SUBWOOFER MODULE



This attractive module consists of a low pass filter and power amplifier ready for you to mount in a suitable sub-woofer cabinet. The combined unit can then be combined with any new or existing hi fi or home cinema speaker system to add in the real bass punch missing from most setups.

The ASM 100 module comes as a ready-to-mount unit on a solid diecast aluminium frame/heatsink. Input signal can be at line or speaker level for easy system integration. There are three separate stereo inputs at line level and the unit will use any signal presented or mix all inputs to add bass to any signal. The speaker level inputs are used by simply wiring the unit in parallel with the existing speakers to provide them with strong bass support. Crossover frequency can be selected to 50, 100 or 200Hz and the bass level can be adjusted by a front panel control. The 'Green' power supply switches the unit to standby if no signal is present. Drawings are included free for the compact 418 x 380 x 303mm cabinet.

With its powerful 125 watt output and versatile filtering the ASM 100 is the ideal universal active driver module for all subwoofer requirements.

ASM 100 Module, complete with IEC mains lead, instructions and ASM - W20 cabinet drawings. Pt. No. V7000. £185.29

W 200 S 20cm Long Throw Drive unit for use in ASM - W20 cabinet. £36.88

### FIESTA 30 LOUDSPEAKER KIT

An Ultra High Efficiency speaker, specially suitable for Valve Amplifiers.

Specially selected as the ideal partner for the new John Linsley Hood 15W Valve Sound Amplifier, or indeed any actual valve amplifier, the FIESTA 30 features the astonishing efficiency and sensitivity needed to achieve a satisfying sound level from amplifiers of limited power output.

To complement the sound purity of such amplifiers a full three speaker system is used with a 300mm (12") woofer, 200mm (8") mid-range and high quality horn tweeter in a vented bass reflex enclosure.

All these drive units have been carefully selected for their individual virtues, and collective excellence, the tweeter for instance being a high end unit with exceptional pulse response as a result of its combination of Kapton former, aluminium diaphragm and aluminium voice coil. Nominal Power Rating is 150W, Max. Music Power 250W, Impedance 8 ohm, Mean Sound Pressure 91dB. Speaker kit comes with all parts to make a pair of speakers, but not the cabinet parts. Crossover units are factory assembled, ready to fit.

Kit No. LK5963 Per Pair. £424.93

### HOME CINEMA SPEAKERS.


The VISATON range of speaker kits includes all you will ever need for your surround sound home cinema setup. The Hi-Tower Kit is ideal as a super luxury pair of stereo main speakers. The 'Centre 80' uses special magnetically screened drivers to avoid picture disturbance and a pair of 'Effect 80's' are used as rear speakers. Any of a range of sub-woofers then adds weight to the sound of the robot feet. Centre 80 Kits include drive units, crossover, terminals and grille. (You make the box) Price each. £64.08

Effect 80, Rear Speaker Kits, per pair. £39.00
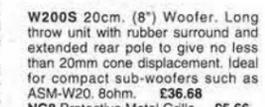
### DRIVE UNITS.



BG30NG 30cm. (12") Woofer. High efficiency, (95db) for sealed or vented cabinets. Peak power handling 250watts. 8 ohm. £69.61




W200S 20cm. (8") Woofer. Long throw unit with rubber surround and extended rear pole to give no less than 20mm cone displacement. Ideal for compact sub-woofers such as ASM-W20. 8ohm. £36.68

NG8 Protective Metal Grille. £5.66



W100S 10cm (4") Low/Midrange. Coated paper cone, rubber surround, high temperature voice coil. Suitable as woofer in mini enclosures or midrange in 3-way systems. 4ohm. £18.06


NG4 Protective Metal Grille. £3.20

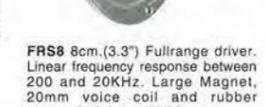

FR58 8cm. (3.3") Fullrange driver. Linear frequency response between 200 and 20KHz. Large Magnet, 20mm voice coil and rubber surround. 8ohm. £8.36



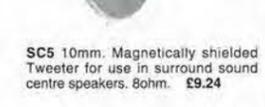DT2.5 10mm Polycarbonate Tweeter. High efficiency ferrofluid tweeter for use over 4,500Hz. Very good price/performance ratio. 8ohm. £8.77



SC5 10mm. Magnetically shielded Tweeter for use in surround sound centre speakers. 8ohm. £9.24



RHT12S High End Ribbon Tweeter. Superior double magnet construction gives an exceptionally low distortion and linear response from 4,000 to 30,000Hz. Cabinet cutout diameter 95mm. 8ohm. £87.77



DHT9AW-NG Hi-Tech, Hi-Fi, horn type tweeter. Frequency response from 3,500 to 38,000Hz and very good pulse response due to aluminium cone, Kapton voice coil and aluminium wire. Peak power handling 150W. 8ohm. £31.99

ASM100 and our 80 watt power amplifier are on demonstration at Wilmslow Audio's new premises at Broughton Astley near Leicester. Tel 01455 286603.

POSTAGE on UK orders is £2 up to £20, £4.50 over £20.

Overseas please enquire. Our LISTS are FREE on request.

Send for Your FREE copy of our LISTS

24 Hr. ORDERLINE 01691 652894 Fax. 01691 662864

All Prices include UK/EC VAT.

# HART

HART ELECTRONIC KITS LTD.  
1 Penylan Mill, OSWESTRY,  
Shropshire, SY10 9AF  
UK

# Taiwan d-ram is not to blame

The great tidal wave of Taiwanese d-ram, blamed for this year's catastrophic drop in prices, is a myth. The Taiwanese are at least a year away from significant volume in d-ram manufacturing.

The three new d-ram manufacturing entrants in Taiwan are Nan-Ya Technology, Vanguard Semiconductor and PowerChip Semiconductor. The previously existing d-ram manufacturers are TI-Acer and Mosel-Vitelic.

TI-Acer is a captive supplier to TI and Acer. Mosel-Vitelic has always been a speciality memory house though it is about to enter the commodity business via a joint venture with Siemens called proMOS Technologies.

"We'll start with the 16Mbit next year," said Mosel-Vitelic's vice-president for operations, Dr Nasa Tsai. "The first phase of the fab has been equipped for 20,000 wafer starts a month."

Most advanced of the new entrants is Vanguard. "Now we have Fab 1(a)



Mosel-Vitelic's Nasa Tsai: "16Mbit next year"

with 15,000 wafers a month and we're currently installing capacity in Fab 1(b) for another 10,000 wafers a month," said Dr F C Tseng, president of Vanguard.

Nan-Ya Technology, a subsidiary of Taiwan's largest company, Formosa Plastics, is running 16Mbit licensed from Oki Electric. "This month we will run 5000 wafers," said executive vice-president Charles Kao. "Our plan is to add another 22,000 wafers a month by the end of 1997."

The third new entrant, PowerChip Semiconductor, is a joint venture between Mitsubishi and the Umax-Elite group. "Currently, we're running 8000 wafers a month," said marketing manager K Y Tsai. "The plan is to be running 12,000 a month by March, representing three million pieces, and 15,000 a month by June."

That is the combined level of output from Taiwan this year, less than the monthly output of a Japanese or Korean fab - hardly a reason for the 1996 price collapse. "The last one in is always the scapegoat," was the wry comment from one of the island's executives.

David Manners  
Electronics Weekly

# US catching up with smartcard applications

Seven top US financial services companies have endorsed the Mondex smartcard technology in what is the USA's largest vote of confidence in the sector. So far the USA has lagged behind Europe in smartcard applications.

AT&T, Chase Manhattan, Dean Witter Discover, First Chicago NBD, MasterCard, Michigan National Bank and Wells-Fargo Bank have invested in Mondex USA Services, which will use the Mondex smartcard technology in a series of pilot programmes in the USA.

"The power of this group will propel Mondex as the pre-eminent electronic cash payment system in the USA," said Janet Hartung Crane, president and CEO of Mondex USA. In spite of its heavyweight backing, Mondex will still face stiff competition from Visa and American Express, which are pursuing their own smartcard projects.

The first commercial Mondex cards will be introduced in 1998, following the results of key trials. Mondex USA says it will license its technologies to other US companies to help further establish the technology.

In a separate move, Mondex announced its agreement with Sun Microsystems for the inclusion of its format in the Java Commerce Toolkit. This toolkit will allow the development of open, secure and integrated electronic commerce applications which will link Mondex to the Internet.

# Computer learns user habits

Australian firm Formulab Neuronetics has launched a computer in the USA which it claims learns from its user and makes decisions.

The device, called the Richter Paradigm Computer, uses a parallel-processing architecture comprising 896 simple Risc processors, and costs \$3000. The company says that the low cost of the system will help establish a large market for a "reasoning" computer.

In a demonstration, Formulab said that it can run neural network applications 180 times faster than an Intel Pentium 166MHz system.

Formulab also revealed plans for a supercomputer based on its computer architecture, which has taken more than 14 years to develop. The supercomputer would combine as many as 6000 microprocessors and could be used for scientific applications. It would run a special operating system that could manage the difficult task of splitting a computational problem into separate tasks and assembling the results.

The company also said that it is working on an add-on card for pcs which could assist users by learning from their work habits. It also plans to shrink its technology so that it can be embedded into products such as cameras and consumer electronics devices. Formulab said it will license the technology to other companies.

Other applications include stock buying, with the system noticing differences in stock prices and trading patterns.

Tom Foremski  
Electronics Weekly

# Rockwell wins 56kbit modem support

The battle to establish the dominant 56kbit/s modem technology continues apace. Rockwell Semiconductor now says that it has won the support of Compaq, Hewlett-Packard, Toshiba, and AST Computer, while rival US Robotics has added Hitachi to its list of allies.

# SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK

- HP New Colour Spectrum Analysers
- HP141T+8552B IF - 8553B RF - 1KHz-110Mc/s - £700.
- HP141T+8552B IF - 8554B RF - 100KHz-1250Mc/s - £900.
- HP141T+8552B IF - 8555A RF - 20Hz-300KHz - £700.
- Special Offer just in from MOD Qty 40 HP8555A RF Units 10Mc/s - 18GHzS.
- HP141T+8552B IF - 8555A 10Mc/s-18GHzS - £1200.
- HP ANZ Units Available separately - New Colours - Tested
- HP141T Mainframe - £350.
- HP8552B IF - £300.
- HP8553B RF 1KHz to 110Mc/s - £200.
- HP8554B RF 100KHz to 1250Mc/s - £500.
- HP8555A RF 10Mc/s to 18GHzS - £800.
- HP8556A RF 20Hz to 300KHzS - £250.
- HP8443A Tracking Generator Counter 100KHz-110Mc/s - £300.
- HP8445B Tracking Preselector DC to 18GHz - £350.
- HP3580A 5Hz - 50KHz ANZ - £750 - £1000.
- HP3582A 0.2Hz to 25.6KHz - £2k.
- HP8568A 100Hz-1500Mc/s ANZ - £6k.
- HP8569B 10Mc/s-22GHz ANZ - £6k.
- HP Mixers are available for the above ANZ's to 40GHz
- TEK 492 - 50KHz - 18GHz Opt 1+2 - £4k-£4.2k.
- TEK 492 - 50KHz - 18GHz Opt 1+2+3 - £4.5k.
- TEK 492P - 50KHz - 21 GHz Opt 1+2+3 - £5k.
- TEK 494AP 1KCS - 21GHz - £7k.
- TEK 496P 1KHz-1.8GHz - £4k.
- TEK SLAN 0-100KHz - £400.
- TEK 7L5 + L1 - 20Hz-5Mc/s - £700.
- TEK 7L5 + L3 - Opt 25 Tracking Gen - £900.
- TEK 7L12 - 100KHz-1800Mc/s - £1000.
- TEK 7L18 - 1.5-60GHzs - £1500.
- TEK 491 10Mc/s-12.4GHzs-40GHzs - £750. 12.4GHzs-40GHzs with Mixers.
- Elektronix Mixers are available for above ANZ to 60GHzs
- Syston Donner 763 Spectrum ANZ + 4745B Preselector .01-18GHz + Two Mixers 18-40GHz in Transit Case - £3k.
- HP873D Signal Generator .05-26.5GHz - £20k.
- Syston Donner 1618B Microwave AM FM Synthesizer 50Mc/s 2-18GHzs
- R8S SWP Sweep Generator Synthesizer AM FM 4-2500Mc/s - £3.5k.
- ADRET 3310A FX Synthesizer 300Hz-60Mc/s - £600.
- HP8640A Signal Generators - 1024Mc/s - AM FM - £800.
- HP3717A 70Mc/s Modulator - Demodulator - £500.
- HP8651A RF Oscillator 22KC/S - 22Mc/s.
- HP5316B Universal Counter A+B.
- HP6002A Power Unit 0-5V 0-10A 200W.
- HP6825A Bipolar Power Supply Amplifier.
- HP461A-465A-467A Amplifiers.
- HP81519A Optical Receiver DC-400Mc/s.
- HP Plotters 7470A-7475A.
- HP3770A Amplitude Delay Distortion ANZ.
- HP3770B Telephone Line Analyser.
- HP8182A Data Analyser.
- HP59401A Bus System Analyser.
- HP6260B Power Unit 0-10V 0-100 Amps.
- HP3782A Error Detector.
- HP3781A Pattern Generator.
- HP3730A - 3737A Down Converter Oscillator 3.5-6.5GHz.
- HP Microwave Amps 491 - 492 - 493 - 494 - 495 - 1GHz - 12.4GHz - £250.
- HP105B Quartz Oscillator - £400.
- HP5087A Distribution Amplifier.
- HP6034A System Power Supply 0-60V 0-10A-200W - £500.
- HP6131C Digital Voltage Source + 100V 1/2 Amp.
- HP4275A Multi Frequency L.C.R. Meter.
- HP3779A Primary Multiplex Analyser.
- HP3779C Primary Multiplex Analyser.
- HP8150A Optical Signal Source.
- HP1630G Logic Analyser.
- HP5316A Universal Counter A+B.
- HP5335A Universal Counter A+B+C.
- HP59501B Isolated Power Supply Programmer.
- HP8901A Modulation Meter AM - FM - also 8901B.
- HP5370A Universal Time Interval Counter.
- Marconi TF2370 - 30Hz-110Mc/s 750HM Output (2 BNC Sockets+Resistor for 500HM MOD with Marconi MOD Sheet supplied - £650).
- Marconi TF2370 30Hz-110Mc/s 50 ohm Output - £750.
- Marconi TF2370 as above but late type - £850.
- Marconi TF2370 as above but late type Brown Case - £1000.
- Marconi TF2374 Zero Loss Probe - £200.
- Marconi TF2440 Microwave Counter - 20GHz - £1500.
- Marconi TF2442 Microwave Counter - 26.5GHz - £2k.
- Marconi TF2305 Modulation Meter - £2.3k.
- Racal/Dana 2101 Microwave Counter - 10Hz-20GHz - £2k.
- Racal/Dana 1250-1261 Universal Switch Controller + 200Mc/s PI Cards.
- Racal/Dana 9303 True RMS Levelmeter+Head - £450. IFFE - £500.
- TEKA6902A also A6902B Isolator - £300-£400.
- TEK 1240 Logic Analyser - £400.
- TEK FG5010 Programmable Function Generator 20Mc/s - £600.
- TEK2465A 350Mc/s Oscilloscope - £2.5k + probes - £150 each.
- TEK CT-5 High Current Transformer Probe - £250.
- TEK J16 Digital Photometer + J6523-2 Luminance Probe - £300.
- TEK J16 Digital Photometer + J6503 Luminance Probe - £250.
- ROTEK 320 Calibrator + 350 High Current Adaptor AC-DC - £500.
- FLUKE 5102B AC-DC Calibrator - £4k.
- FLUKE 1120A IEEE - 488 Translator - £250.
- Tinsley Standard Cell Battery 5644B - £500.
- Tinsley Transportable Voltage Reference - £500.
- FLUKE Y5020 Current Shunt - £150.
- HP745A + 746A AC Calibrator - £600.
- HP8080A MF - 8091A 1GHz Rate Generator + 8092A Delay Generator + Two 8093A 1GHz Amps + 15400A - £800.
- HP54200A Digitizing Oscilloscope.
- HP11729B Carrier Noise Test Set .01-18GHz - LEF - £2000.
- HP3311A Function Generator - £300.
- Marconi TF2008 - AM-FM signal generator - also sweeper - 10Kc/s - 510Mc/s - from £250 - tested to £400 as new with manual - probe kit in wooden carrying box.
- HP Frequency comb generator type 8406 - £400.
- HP Vector Voltmeter type 8405A - £400 new colour.
- HP Sweep Oscillators type 8690 A & B + plug-ins from 10Mc/s to 18GHz also 18-40GHz. P.O.R.
- HP Network Analyser type 8407A + 8412A + 8501A - 100Kc/s - 110Mc/s - £500 - £1000.
- HP Amplifier type 8447A - 1-400Mc/s £200 - HP8447A Dual - £300.
- HP Frequency Counter type 5340A - 18GHz £1000 - rear output £800.
- HP 8410 - A - B - C Network Analyzer 110Mc/s to 12GHz or 18GHz - plus most other units and displays used in this set-up - 8411a - 8412 - 8413 - 8414 - 8418 - 8740 - 8741 - 8742 - 8743 - 8746 - 8650. From £1000.
- Racal/Dana 9301A - 9302 RF Millivoltmeter - 1.5-2GHz - £250-£400.
- Racal/Dana Modulation Meter type 9009 - 8Mc/s - 1.5GHz - £250.
- Marconi RCL Bridge type TF2700 - £150.
- Marconi RCL Bridge type - 6058B - 6070A - 6055A - 6059A - 6057A - 6056 - £250-£350. 400Mc/s to 18GHz.
- Marconi TF1245 Circuit Magnification meter + 1246 & 1247 Oscillators - £100-£300.
- Marconi microwave 6600A sweep osc. mainframe with 6650 PI - 18-26.5GHz or 6651 PI - 26.5-40GHz - £1000 or PI only £600. MF only £250.
- Marconi distortion meter type TF2331 - £150. TF2331A - £200.
- Tektronix Plug-ins 7A13 - 7A14 - 7A18 - 7A24 - 7A26 - 7A11 - 7M11 - 7S11 - 7D10 - 7S12 - S1 - S2 - S6 - S52 - PG506 - SC504 - SG502 - SG503 - SG504 - DC503 - DC508 - DD501 - WR501 - DM501A - FG501A - TG501 - PG502 - DC505A - FG504 - 7B80 + 85-7B92A
- Gould J38 test oscillator + manual - £150.
- Tektronix Mainframes - 7603 - 7623A - 7613 - 7704A - 7844 - 7904 - TM501 - TM503 - TM506 - 7904A - 7834 - 7823 - 7833.
- Marconi 6155A Signal Source - 1 to 2GHz - LED readout - £400.
- Barr & Stroud Variable filter EF3 0.1Hz - 100Kc/s + high pass + low pass - £150.
- Marconi TF2163S attenuator - 1GHz. £200.
- Farnell power unit H60/50 - £400 tested. H60/25 - £250.
- Racal/Dana 9300 RMS voltmeter - £250.
- HP 8750A storage normalizer - £400 with lead + S.A or N.A interface.
- Marconi TF2330 - or TF2330A wave analysers - £100-£150.
- Tektronix - 7S14 - 7T11 - 7S11 - 7S12 - S1 - S2 - S39 - S47 - S51 - S52 - S53 - 7M11.
- Marconi mod meters type TF2304 - £50.
- HP 5065A rubidium vapour FX standard - £1.5k.
- Syston Donner counter type 6054B - 20Mc/s - 24GHz - LED readout - £1k.
- Racal/Dana 9083 signal source - two tone - £250.
- Syston Donner - signal generator 1702 - synthesized to 1GHz - AM/FM - £600.
- Tektronix TM515 mainframe + TM5006 mainframe - £450 - £850.
- Farnell electronic load type RB1030-35 - £350.
- Racal/Dana counters - 9904 - 9905 - 9906 - 9915 - 9916 - 9917 - 9921 - 50Mc/s - 3GHz - £100-£450 - all fitted with FX standards.
- HP4815A RF vector impedance meter c/w probe - £500-£600.
- Marconi TF2092 noise receiver. A, B or C plus filters - £100-£350.
- Marconi TF2091 noise generator. A, B or C plus filters - £100-£350.
- Marconi 2017 S/G 10KHz - 1024MHz
- HP180TR, HP182T mainframes £300-£500.
- Philips panoramic receiver type PM7900 - 1 to 20GHz - £400.
- Marconi 6700A sweep oscillator + 18GHz PI's available.
- HP8505A network ANZ + 8503A S parameter test set + 8501A normalizer - £4k.
- HP8505 network ANZ 8505 + 8501A + 8503A.
- Racal/Dana VLF frequency standard equipment. Tracer receiver type 900A + difference meter type 527E + rubidium standard type 9475 - £2750.
- HP signal generators type TF2304 - £250.
- HP 432A - 435A or B - 436A - frequency 10GHz - £200-£1000.
- Bradley oscilloscope calibrator type 192 - £800.
- HP8614A signal generator 800Mc/s - 2.4GHz, new colour £400.
- HP8616A signal gen 1.8GHz - 4.5GHz, new colour £400.
- HP 3325A syn function gen 20Mc/s - £1500.
- HP 3336A or B syn level generator - £500-£600.
- HP 3586B or C selective level meter - £750-£1000.
- HP 3575A gain phase meter 1Hz - 13Mc/s - £400.
- HP 86630 S/G microwave 2.3 - 13GHz - opt 001 - 003 - £4.5k.
- HP 8660 A-B-C syn S/G. AM + FM + 10Kc/s to 110Mc/s PI - 1Mc/s to 1300Mc/s - 1Mc/s to 2000Mc/s - £500-£2000.
- HP 8640B S/G AM-FM 512Mc/s or 1024Mc/s. Opt 001 or 002 or 003 - £800-£1250.
- HP 8622BX Sweep PI - 01 - 2.4GHz + ATT - £1750.
- HP 8629A Sweep PI - 2 - 18GHz - £1000.
- HP 86290B Sweep PI - 2 - 18GHz - £1250.
- HP 86 Series PI's in stock - splitband from 10Mc/s - 18.6GHz - £250-£1k.
- HP 8620C Mainframe - £250. IEEE - £500.
- HP 8615A Programmable signal source - 1MHz - 50Mc/s - opt 002 - £1k.
- HP 8601A Sweep generator. 1 - 110Mc/s - £300.
- HP 3488A HP - IB switch control unit - £500 + control modules various - £175 each.
- HP 6160A 500Mc/s programmable pulse generator - £1000.
- HP 853A MF ANZ - £1.5k.
- HP 8349A Microwave Amp 2 - 20GHz Solid state - £1500
- HP 3585A Analyser 20Hz - 40Mc/s - £4k.
- HP 8569B Analyser .01 - 22GHz - £5k.
- HP 3580A Analyser 5Hz - 50KHz - £1k.
- HP 1980B Oscilloscope measurement system - £600.
- HP 3455A Digital voltmeter - £500.
- HP 3437A System voltmeter - £300.
- HP 3581C Selective voltmeter - £250.
- HP 5370A Universal time interval counter - £450.
- HP 5335A Universal counter - 200Mc/s - £500.
- HP 5328A Universal counter - 500Mc/s - £250.
- HP 6034A System power supply - 0 - 60V - 0 - 10 amps - £500.
- HP 5150A Thermal printer - £250.
- HP 1645A Data error analyser - £150.
- HP 4437A Attenuator - £150.
- HP 3717A 70Mc/s modulator - £400.
- HP 3710A - 3715A - 3716A - 3702B - 3703B - 3705A - 3711A - 3791B - 3712A - 3793B microwave link analyser - P.O.R.
- HP 3730A + B RF down converter - P.O.R.
- HP 3552A Transmission test set - £400.
- HP 3763A Error detector - £500.
- HP 3764A Digital transmission analyser - £600.
- HP 3770A Amp delay distortion analyser - £400.
- HP 3780A Pattern generator detector - £400.
- HP 3781A Pattern generator - £400.
- HP 3781B Pattern generator (bell) - £300.
- HP 3782A Error detector - £400.
- HP 3782B Error detector (bell) - £300.
- HP 3785A Jitter generator + receiver - £750-£1k.
- HP 8006A Word generator - £100-£150.
- HP 8016A Word generator - £250.
- HP 8170A Logic pattern generator - £500.
- HP 59401A Bus system analyser - £350.
- HP 59500A Multiprogrammer HP - IB - £300.
- Philips PMS390 RF syn - 0.1 - 1GHz - AM + FM - £1000.
- S.A. Spectral Dynamics SD345 spectroscope 111 - LF ANZ - £1500.
- Tektronix R7912 Transient waveform digitizer - programmable - £400.
- Tektronix TR503 + TM503 tracking generator 0.1 - 1.8GHz - £1k - or TR502.
- Tektronix 576 Curve tracer + adaptors - £900.
- Tektronix 577 Curve tracer + adaptors - £900.
- Tektronix 1502/1503 TDR cable test set - £1000.
- Tektronix AM503 Current probe + TM501 m/frame - £1000.
- Tektronix SC501 - SC502 - SC503 - SC504 oscilloscopes - £75-£350.
- Tektronix 465 - 465B - 475 - 2213A - 2215 - 2225 - 2235 - 2245 - £250-£1000.
- Kikusui 100Mc/s Oscilloscope COS6100M - £350.
- Nicolet 3091 LF oscilloscope - £400.
- Racal 1991 - 1992 - 1988 - 1300Mc/s counters - £500-£800.
- Fluke 80K-40 High voltage probe in case - BN - £100.
- Racal Recorders - Store 4 - 4D - 7 - 14 channels in stock - £250 - £500.
- Racal Store Horse Recorder & control - £400-£750 Tested.
- HP 545 microwave 18GHz counter - £1200.
- Fluke 510A AC ref standard - 400Hz - £200.
- Fluke 355A DC voltage standard - £300.
- Wiltron 610D Sweep Generator + 6124C PI - 4 - 8GHz - £400.
- Wiltron 610D Sweep Generator + 61084D PI - 1Mc/s - 1500Mc/s - £500.
- Time Electronics 9814 Voltage calibrator - £750.
- Time Electronics 9811 Programmable resistance - £600.
- Time Electronics 2004 D.C. voltage standard - £1000.
- HP 8999B Sweep PI YIG oscillator .01 - 4GHz - £300. 8690B MF - £250. Both £500.
- Schlumberger 1250 Frequency response ANZ - £1500.
- Dummy Loads & power att up to 2.5 kilowatts FX up to 18GHz - microwave parts new and ex stock - relays - attenuators - switches - waveguides - Yigs - SMA - APC7 plus - adaptors. B&K items in stock - ask for list. W&G items in stock - ask for list. Power Supplies Heavy duty + bench in stock - Farnell - HP - Weir - Thurlby - Racal etc. Ask for list.

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. SAE FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS. AVAILABILITY OR PRICE CHANGE. VAT AND CARRIAGE EXTRA

ITEMS MARKED TESTED HAVE 30 DAY WARRANTY. WANTED: TEST EQUIPMENT-VALVES-PLUGS AND SOCKETS-SYNCHROS-TRANSMITTING AND RECEIVING EQUIPMENT ETC.

Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. No: (01274) 684007. Fax: 651160



# RESEARCH NOTES

Jonathan Campbell

## Single chip mic sounds the best yet

The thin, flexible diaphragm and rigid bookplate design of the condenser microphone can already be implemented on a single chip. But there have been problems in the past with residual stress in the diaphragms affecting the sensitivity of the device.

Now three Chinese researchers have manufactured a silicon condenser microphone with a a corrugated

diaphragm that shows a dramatic reduction of stress.


This is not the first microphone to use a corrugated diaphragm to reduce stress in this way. But the Chinese microphone has also demonstrated a flat frequency response and high sensitivity ('Design and fabrication of silicon condenser microphone using corrugated diaphragm technique,' Quanbo Zou *et al*, *J of Microelectromechanical Systems*, Vol 5, No 3, pp. 197-204).

The microphone capacitor consists of the corrugated diaphragm that acts as an active electrode, and a single crystal silicon bookplate with acoustic holes that acts as the stationary electrode. It is fabricated, using seven masks, on a single wafer by use of silicon anisotropic etching and sacrificial layer etching techniques. So no bonding techniques are required.

Up to now, the microphone has demonstrated a flat frequency response between 100Hz and 8-16kHz, and open circuit sensitivities as high as 14mV/Pa while using a low bias voltage of 10V

Further work will aim to improve the overall microphone performance, boosting sensitivity and flatness of the frequency response, by optimising the structure parameters and process conditions.

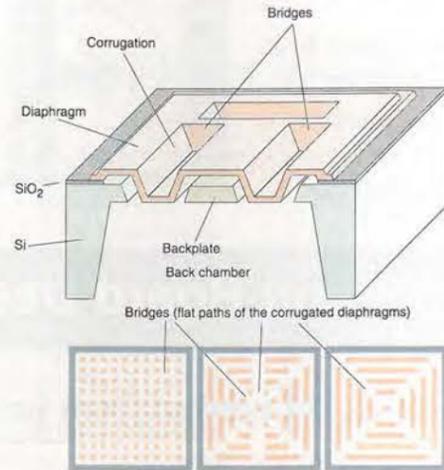Contact Quanbo Zou, Institute of Microelectronics, Tsinghua University, Beijing, China.



Corrugated diaphragm results enhances single-chip microphone. Diagram shows three alternative bridge configurations.

**Sun shines again for Pathfinder:** The record-setting Pathfinder solar-powered research aircraft has resumed flight testing at Nasa's Dryden Flight Research Center, following its disastrous damage during a ground

accident 12 months ago. In its last flight, the Pathfinder set an altitude record of more than 16,800m on a flight from Dryden which lasted nearly 12h. However, its latest flight was just a low-altitude check-out flight over

the northern portion of Rogers Dry Lake at Edwards Air Force Base, California.

Low sun angle and limited hours of sunlight during the winter limit Pathfinder's altitude capability to about 6670m. This is one of the reasons why the project will be transferred to the Navy's Pacific Missile Range Facility on the island of Kauai, which lies at a lower latitude. Kauai's latitude and more favourable prevailing northerly winds will allow more opportunity for high-altitude solar-powered flying during a five-month flight test program.

Pathfinder is one of several remotely-piloted aircraft being evaluated under Nasa's Environmental Research Aircraft and Sensor Technology (Erast) program. The joint Nasa-industry alliance is seeking to develop technologies required to operate slow-flying unpowered

aircraft at altitudes up to 34,000m on environmental-sampling missions lasting up to a week or longer. With a span of 33m, Pathfinder is basically a flying wing.

Only two small pods extend below the wing's centre section to carry a variety of scientific sensors and support the craft's landing gear. The solar arrays on the wing can provide as much as 7200 watts of power at high noon on a summer day to power the craft's six electric motors and electronic systems. A backup battery provides power for up to two hours to fly the craft after the sun is down. Built primarily of lightweight composite structure, plastic foam and a thin plastic covering, Pathfinder weighs about 230kg.

Contact: Fred Brown, Dryden Flight Research Center, Edwards, CA, USA



For all your Power Distribution Olson offer a varied choice

- Distribution Units**
- DISTRIBUTION PANELS FUSED, WITH R.F. FILTER AND R.C.D. PROTECTION**
- FUSED WITH RCD PROTECTORS**
- "The Rack Range" mains distribution panels for 19" rack mounting**
- Office Furniture Cable Management**
- Mains Distribution Panels with Non Standard Sockets**
- FUSED SUPER SUM**
- Earth Leakage Distribution Units**
- Distribution Units**
- PANELS WITH 10AMP CEE22/IEC SHUTTER SOCKETS**
- The Rack Range WITH SHUTTER SOCKETS ONLY**
- Mains Distribution Panels INTERNATIONAL RANGE**
- FUSED SUPER SUM WITH ELECTRIC AND FUSE AND POWER POLE SWITCH SOCKETS**
- DATA PROTECTOR**
- INDUSTRIAL RANGE 16 AMP 110V AND 240V TO BS 4343/IEC 309**
- Distribution Units**
- 19" FAN TRAYS**
- "The Rack Range" CEE22/IEC SOCKETS**
- SERVICE PILLAR FOR THE OPEN-PLAN OFFICE**
- Distribution Units**



## Straightening out a pcb problem

Printed circuit boards, or pcbs, remain vulnerable to a simple, heat-induced threat: warpage. Unfortunately, warped pcb may cause a device to stop working, while boards that warp during manufacturing after expensive components are added can mean costly losses.

But a technique developed at the Georgia Institute of Technology and now licensed by Electronic Packaging Services (EPS) could provide a new weapon against warpage.

Charles Ume (right) examines the fringe pattern generated when a printed circuit board is heated in the new oven.

The experimental Thermoïre process provides real-time data about pcb warpage in simple and fast manner, so that manufacturers can avoid design problems.


"Electronic packaging companies can use the warpage information to make changes in their pcb design early," says Charles Ume, an associate professor in the School of Mechanical Engineering.

The heat that can warp pcbs is generated each time computers, camcorders or other pcb-run devices are turned on. Also, temperatures up to 230°C are an integral part of pcb processing.

In addition, if the pcb is small, thin and densely populated with components, as is the current industry trend, that is an invitation for warpage-related reliability problems.

For the new process, Ume developed a special oven with a glass grating top, through which the pcb placed inside is visible. A white light shines through the glass grating onto the pcb, and an inexpensive, compact, charge-coupled device camera captures warpage digitally as it occurs.

The flat glass grating is etched with equally spaced parallel lines. It is placed above and parallel to the pcb. A beam of white light is directed onto the glass at a specific angle, causing the etched lines to create a shadow on the surface of the pcb. When the surface of the pcb curves due to warpage, a moire pattern is produced by the geometric interference between the etched lines on the glass and the

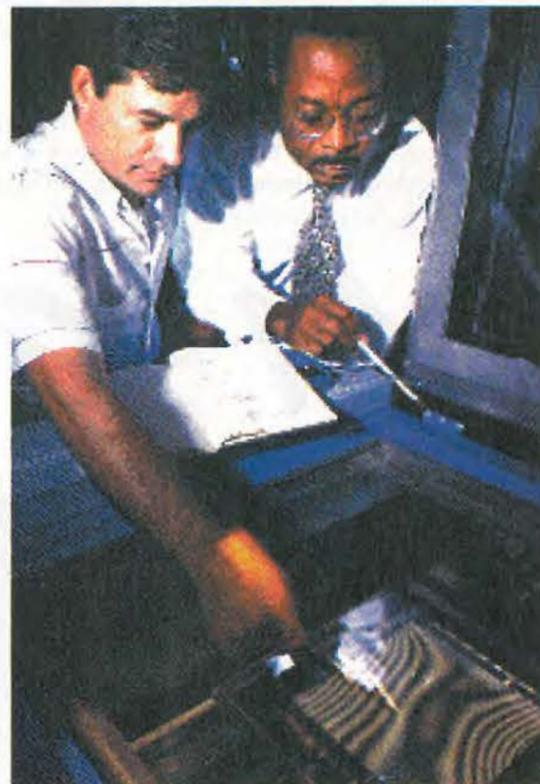

shadow of those lines on the pcb's surface. The more the pcb warps, the greater number of moire fringes that appear.

Ume counts the number of fringes, puts them into an equation, and a computer determines how much warpage has occurred. The warpage process is displayed in real time on a television screen and recorded on video and on computer.

The Thermoïre technique can be used to simulate the three major kinds of soldering processes - infrared reflow, convective reflow and wave - and the automated oven system can reproduce any given soldering temperature history used in producing a board. In this way, the system can pinpoint which processes or designs may cause the most warping.

Ume says that companies can use the results to make design or process changes before production, such as changing soldering temperature profiles, reducing or extending processing times, relocating key components, and changing the materials used in constructing the pcb.

The ability to measure thermally induced warpage could also enable manufacturers to validate their numerical warpage predictions, created using finite element modelling techniques.

If a certain amount of warpage is allowable, the new technique also lets manufacturers measure initial warpage, rather than assuming the board is flat before transistors and other items are added.

Manufacturers can then determine how much additional warpage develops during further processing or attachment of components.

Contact: Charles Ume, Georgia Institute of Technology, Atlanta, Georgia 30332-0828, USA. email: charles.ume@me.gatech.edu

## 1997 will be the year of the blue laser

Operation of blue laser diode devices should now be possible, with commercialisation coming in 1997-98, according to one of the leading researchers in the field.

Shuji Nakamura, of Nichia Chemical Industrie, Tokushima, Japan, made his prediction in an interview appearing in *OE Reports*, published by Spie (The International Society for Optical Engineering).

Nakamura has already been behind some of the major breakthroughs in blue leds and lasers. He has also stood against the prevailing wisdom underlying much work in blue device research by concentrating on GaN technology, rather than using the more usual II-VI materials and then frequency doubling.

Now, when he is reported to be close to developing a commercial product, the significant degradation

suffered by II-VI blue lasers is convincing scientists that GaN is the way forward.

So far Nakamura has produced a pulsed blue laser diode operating at room temperature, with wavelength variable between 390-440nm by changing the In content of the InGaIn well layers.

Initially, the cost of the laser devices will be many times greater than the current \$1-2 price of blue leds, though volume will naturally force this down.



The attraction of blue lasers is the impact they could have on high density storage. Current limits using a red laser diode are around 5Gbytes per side. But the shorter wavelength of blue light should allow this capability to be increased substantially, perhaps by a factor of three.

"...the ideal calculating companion for the engineer or designer"

Computer Shopper April 1995



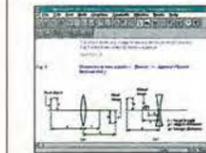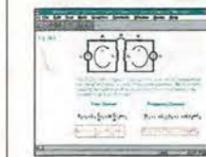designed for  
**ENGINEERS**  
**Mathcad!**



Every engineer has to solve mathematical problems. So every professional engineer needs **Mathcad**. Especially now.

Because **Mathcad PLUS 6.0** has dozens of new features to make calculations even easier - with online *QuickSheets* to guide you all the way!

**Mathcad** is a free-form, interactive environment that's perfect for formulating ideas, setting up problems, evolving solutions and sharing results. Within a Mathcad worksheet you can perform "live" numeric or symbolic calculations, add graphics and animations, annotate and format text. *Want to change a variable?* Go ahead - your formulae and graphs update themselves instantly!

Plus, with now over 50 to choose from, there's Mathcad's electronic books including - **Electric Circuits** taken from Schaums Interactive Outlines, with over 390 interactive solutions to comprehensive problems or **Electrical and Electronic Engineering** from Hicks, a practical and quick reference book for electrical and electronics engineering formulae - just cut and paste them into your own application.

So now you know how to make your working life easier - and more fun! Just fill out this card or call Adept Scientific today!



Tel: (01462) 480055


Fax: (01462) 480213

Email: mathcad@adeptsience.co.uk

http://www.adeptsience.co.uk/

CALL FOR MORE INFORMATION:  
**01462 480055**

CIRCLE NO. 155 ON REPLY CARD

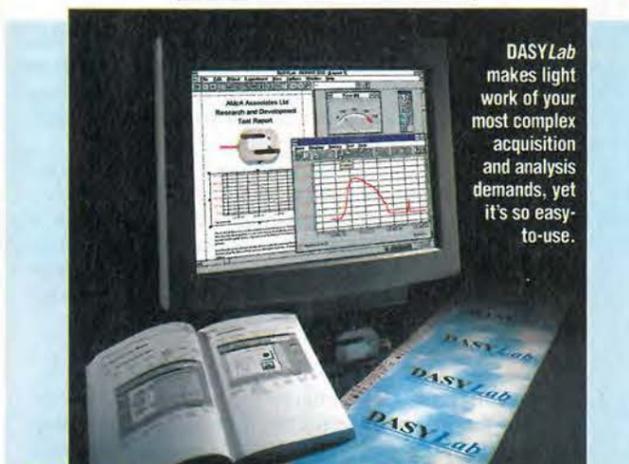

DASyLab makes light work of your most complex acquisition and analysis demands, yet it's so easy-to-use.

**DASyLab - Data Acquisition to Report**

Just a few mouse clicks is all it takes to choose from **DASyLab's** comprehensive palette of icons, drop them onto your worksheet and wire them together. There are icons for inputs and outputs, controls and displays, mathematical and statistical operations, signal analysis and triggering/messaging functions, data and file handling routines - everything you need your system to handle.

With **DASyLab** you can visualise your test rig or process and create QC and test reports without having to export data to another program. You can enter test or product batch information and store it to file along with measured and derived values. You can type equations straight into **DASyLab**, and derive real-time results as you acquire the data! There's even a **DASyLab NET** option so you can pull in data from remote PCs using standard network components.

**DASyLab** has to be the most intuitive data acquisition software money can buy.

CALL FOR MORE INFORMATION:  
**01462 480055**



Tel: (01462) 480055

Fax: (01462) 480213

Email: data.acq@adeptsience.co.uk

http://www.adeptsience.co.uk/

Adept Scientific plc 6 Business Centre West, Avenue One, Letchworth, Herts, SG6 2HB

Copyright © 1997 Adept Scientific plc. All rights reserved. All trademarks registered.

CIRCLE NO. 157 ON REPLY CARD

Don't just look at your data...

Call for your  
**FREE Interactive Demo Disk!**

"the most advanced software of its type with an excellent range of add on modules"  
Eric Adler, Laboratory Product Update

...explore it with  
**DADiSP**



Open dozens of windows onto your data, view every aspect at once. Alter a function, change a parameter - and every window updates automatically. That's why we call **DADiSP** a "graphical spreadsheet".

**DADiSP** the point-and-click software that puts signal processing and analysis under YOUR control. It's *powerful* - it can handle the very largest data sets you're likely to throw at it. It's *flexible* - it lets you construct sophisticated analysis chains in seconds. Once you try **DADiSP**, you'll never want to look at your data in any other way!

Call Adept Scientific for more information!

**01462 480055**



Adept Scientific plc 6 Business Centre West, Avenue One, Letchworth, Herts, SG6 2HB

Tel: (01462) 480055 Fax: (01462) 480213

Email: dadisp@adeptsience.co.uk http://www.adeptsience.co.uk/

CIRCLE NO. 156 ON REPLY CARD



**TEMPERATURE CURRENT PRESSURE VOLTAGE STRAIN**

WHEN YOUR PROJECT DEPENDS ON MEASURING DATA FROM DIFFERENT SENSORS AND SOURCES, YOU NEED TRULY RELIABLE, FLEXIBLE DATA ACQUISITION HARDWARE. AND YOU DON'T WANT TO SPEND AN AGE SETTING IT UP AND CHECKING IT OUT.

That's why you need **DATAshuttle**. Because **DATAshuttle** is an incredibly reliable, completely flexible way to collect your data. And it's so simple - all you do is plug it into the parallel port of your notebook or desktop PC - there's no fiddling around, no opening up your computer. And you can use **DATAshuttle** again and again, whenever and wherever you need. **DATAshuttle** is a rugged, self-contained unit that gives you 8 analogue input channels for direct connection of any mixture of voltage, thermocouples, RTDs, 4-20mA signals and other transducer inputs, and 8 digital I/O channels. The **DATAshuttle's** innovative integrating converter technology ensures extremely low noise and dynamic resolution up to 10 times better than conventional 12- or 16-bit A/D boards. It's even got a fast pass-through interface, so you can link up to 15 **DATAshuttles** (or other devices including printers) to the same parallel port. And **DATAshuttle** comes with free *QuickLog* software - or you can choose state-of-the-art *WorkBench* PC for Windows software, the easiest, most intuitive way to set up and control your **DATAshuttle** application.



CALL FOR MORE INFORMATION:  
**01462 480055**

OR FILL OUT THIS CARD AND RETURN TODAY!


Fax: (01462) 480213 Email: data.acq@adeptsience.co.uk http://www.adeptsience.co.uk/

Adept Scientific plc 6 Business Centre West, Avenue One, Letchworth, Herts, SG6 2HB

**DATA ACQUISITION... ANYWHERE!**

CIRCLE NO. 158 ON REPLY CARD

# Roaring subwoofer

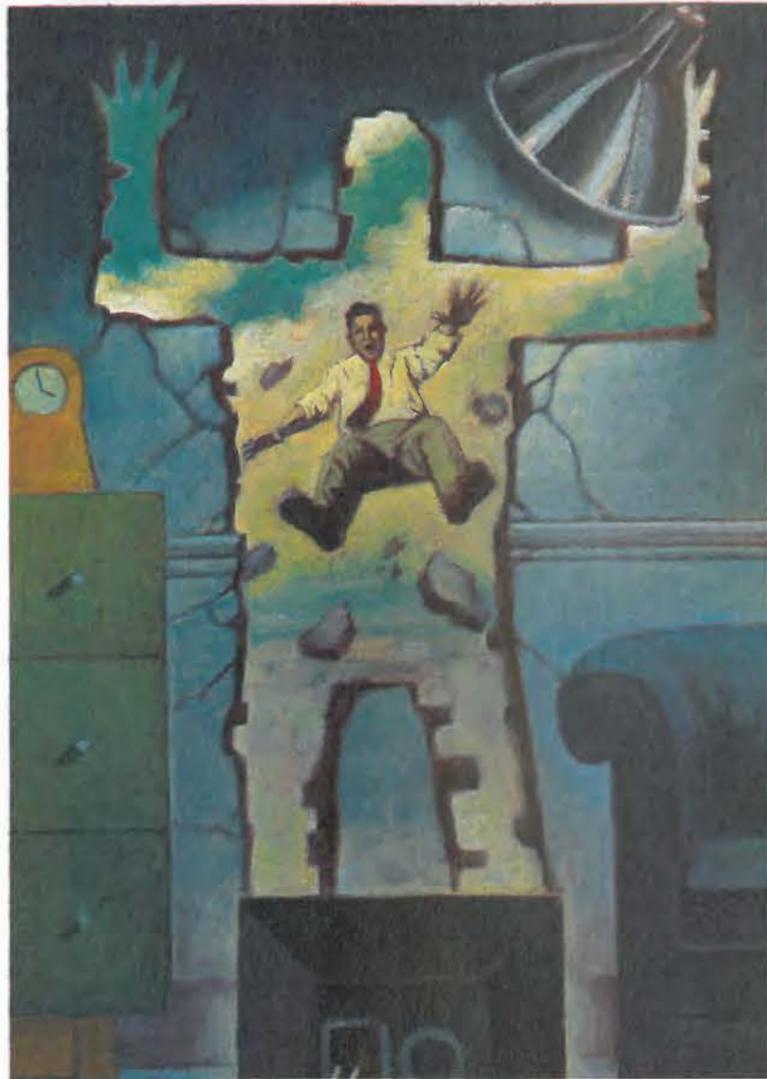

Using motional feedback, **Russel Breden's** subwoofer produces flat response down to 15Hz – despite its relatively small enclosure. Feedback also makes feasible an infinite baffle rather than a reflex design, resulting in tighter bass.

Inspired by Peter Baxandall's 'Low-cost, high-quality loud-speaker' series of articles in *Wireless World*, I built my first sub-woofer back in 1978. It was a 2.4ft<sup>3</sup> reflex using a KEF B139 driver and tuned to 30Hz.

Originally, this sub-woofer was passive, but it soon became apparent that adding a dedicated power amplifier and second-order low-pass filter produced the flexibility required to interface with my existing speakers. Built in the days when home computers were a distant dream, and Thiele/Small analysis was little known, it is surprising that it worked at all. As it was, it gave me a sense of what was missing from most of the other systems around at that time.

Nearly twenty years later, things haven't changed that much. Off-the-shelf speaker systems available today rarely produce an output below 60Hz.

### Going lower

For a system to produce bass extending to at least 30Hz normally requires large boxes and expensive drivers. But by creative use of electronic circuitry, both size and expense can be cut to reasonable proportions. These techniques however require the sacrifice of hi fi's most sacred cow – flat amplifier response.

Today, we have all the tools necessary to design economical audio systems with a flat response, even though the system's component parts may be far from linear. The work of Thiele – extended by Small – provides comprehensive details about the response of a driver in an enclosure. All that is needed is to design electronic circuitry to compensate for the non-linear response of the speaker/driver combination.

### Advantages of activity

A motional feedback system operates by sensing the speaker cone's motion and feeding this back into the power amp.

Providing negative feedback in this way forces the amplifier to produce a signal that corrects both for amplitude irregularities and the distortion generated by the speaker. The result is an acoustic output which is flat against frequency – even though both speaker and amplifier are operating in a decidedly non-linear fashion.

Motional feedback is not the only way of achieving this. You could use electrical equalisation, for example, but this would not reduce system distortion. In any event, motional feedback is an intellectually satisfying technique using well understood principles.

To produce a correcting signal, the speaker must be fitted with some form of transducer. In this design, I have used dual-coil drivers, one coil of which forms the pickup. As the cone moves, it generates a voltage signal in the coil which is proportional to cone velocity. This signal is then processed and used for correction purposes, see panel.

One major objection to motional feedback is that the feedback loop could try to force the driver beyond its limits. This

Fig. 1a). Power amplifier and motional feedback mixer for the subwoofer. Since feedback is derived directly from the voice-coil of the driver, it is possible to produce a very flat response, and reduce distortion.

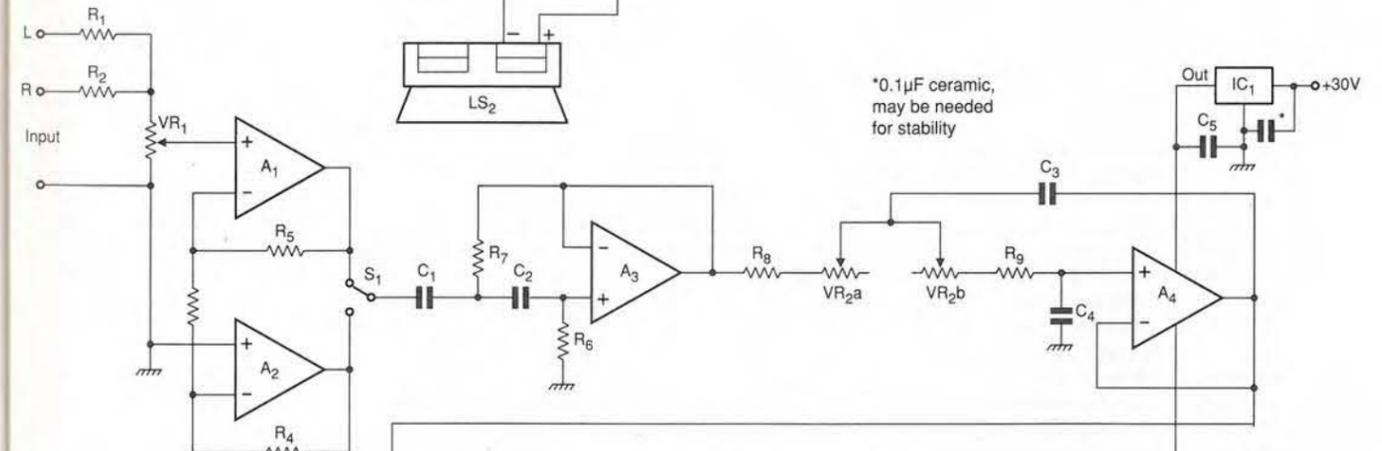
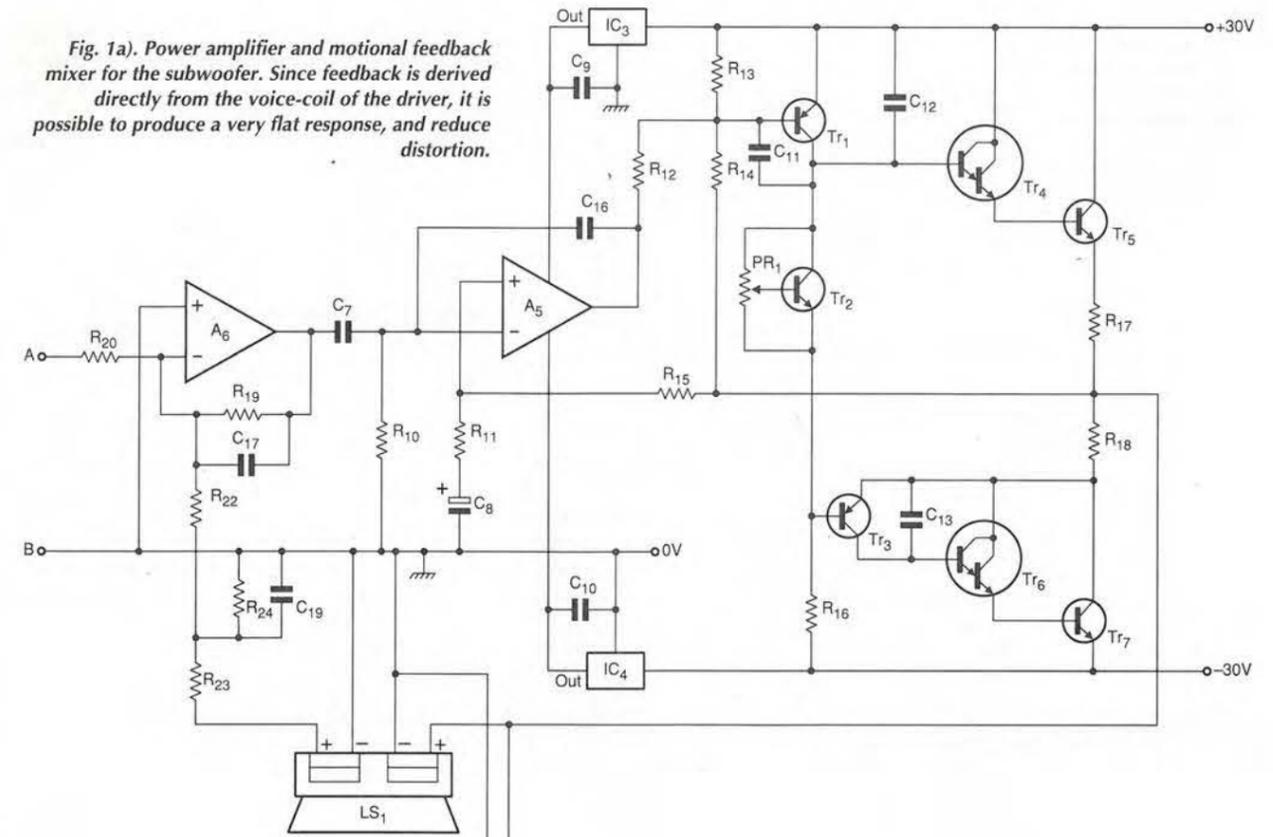


Fig. 1b). Filter chain preceding the subwoofer power amplifier. This section mixes the left and right stereo signals and allows phase to be reversed. It also contains a variable filter allowing the crossover frequency to be set anywhere between 45 and 120Hz. This allows the subwoofer to be adapted to suit most existing hi-fi systems.


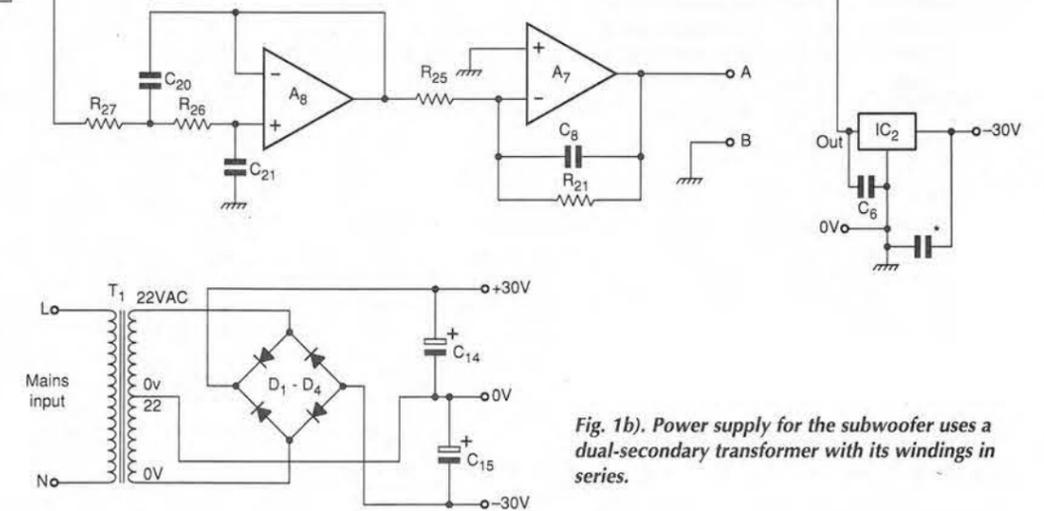


Fig. 1b). Power supply for the subwoofer uses a dual-secondary transformer with its windings in series.

Fig. 2. Curve A is initial system response while curve B is final system response but excluding low-pass filtering. Both curves are measured near filed, i.e. 1cm from cone.

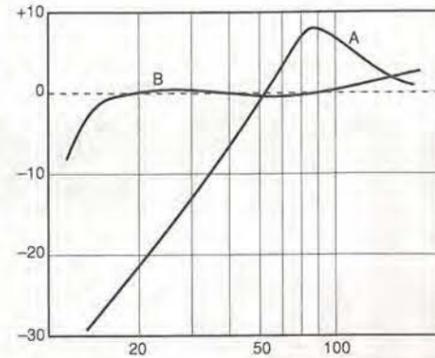

problem can be avoided by choosing a sealed box or infinite-baffle enclosure. Use can then be made of the natural roll-off of the driver to ensure that excursion limits cannot be exceeded (see panel).

Using an infinite-baffle enclosure means that the response is essentially that of a second-order filter. To produce a flat response down to dc – even if it were possible electrically – would require infinite cone excursion. To match such a driver, you would need an amplifier of infinite gain since the gain of a high-pass filter is zero at dc. For every octave of base extension, the power and cone excursion required increase fourfold. Obviously this cannot be carried too far. However the system described here has a flat resonance, with a -3dB point at 15Hz.

This frequency is at least an octave below the nominal cut-off of many subwoofer systems. Furthermore when I examined the output acoustically, sine wave distortion was below 2% at 15Hz.


The reason for going so low is mainly to minimise phase shift. There is little musical information on most recordings below 30Hz. Too rapid a roll-off at this frequency produces phase errors between fundamentals and harmonics, leading to a muddy sound. One of the joys of listening to this system is the speed at which bass notes are delivered without the overhang associated with reflex systems.

One problem that has to be considered is how much sound-pressure level, spl, can be generated. Here, we are concerned with a domestic environment. Many more-than-adequate subwoofers use a 10in driver in a reflex cabinet.

Since reflexing is out in this design, I have chosen a pair of 10in drivers, operating in parallel. This has the advantage that both drivers contribute useful output over the entire range whereas a reflex system's vent only contributes output around its resonant frequency. Additionally, the price paid for vent output is a rapid bass roll-off that must worsen the transient response of the system.

For the purposes of analysis, the circuit can be split into three parts. First the power amplifier; the requirements from this element of the circuit include high power output. Furthermore, because the load impedance is around 3Ω, fair-

Fig. 3. Curve A is response from the pick-up coil of the loudspeaker and curve B response after high-frequency equalisation.

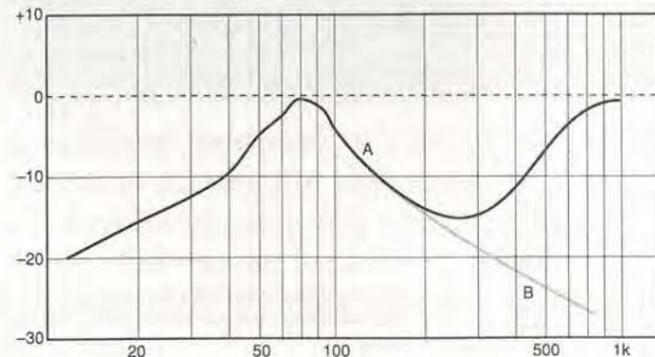

ly large current swings are required. An extended low frequency response also implies that the power supply will tend to sag under load. Precautions must be taken to make sure that this does not affect sound quality.

Taking into account these factors I make no apology for the use of rugged TO3 output devices, namely  $Tr_5$  and  $Tr_7$ , which are a pair of 2N3055s. These in turn are driven by a pair of Darlington's,  $Tr_4$  and  $Tr_6$ . A quasi-complementary output stage is used with  $Tr_3$  providing the necessary phase inversion for the lower output transistors.

**Nested feedback loops**

The entire circuit is based on TL074 quad op-amps, one of which is used in the power amplifier. However the low operating voltage and consequent low output voltage swings of this device provide insufficient power. For this reason the amplifier incorporates the idea of nested feedback loops, Fig. 1.

To explain further, the output stage operates from a split 60V power supply. The driver stage is built around  $Tr_1$ . Usually, the output stage biasing voltage is provided by the  $V_{be}$  multiplier comprising  $Tr_2$  and  $PR_1$ . Resistors  $R_{17,18}$  introduce emitter degeneration in the output stage, stabilising the operating point. Local shunt feedback around both driver and output stage is taken via  $R_{12,14}$ .

The value of  $R_{13}$  has been chosen to produce 0V output for a 0V input from  $A_5$ . This local feedback loop reduces distortion from the output stage to well below 1% before global feedback is applied around the circuit.

Closed-loop gain from  $A_5$  output to the load is approximately five. This allows the op-amp output stage to produce the required voltage swing at the output. An incidental advantage is that the op-amp output sees a relatively high impedance and therefore operates in push-pull, Class A.

Supply voltage for the op-amp is taken from the main power supply through a pair of 15V regulators,  $IC_{3,4}$ . Capacitors  $C_{9,10}$  provide hf decoupling. Op-amp  $A_5$  is the heart of the amplifier. Note that because of the inverting action of the driver/output stage, the inputs are used in the opposite sense.

Input signals are applied to the inverting input and overall feedback to the non inverting. The voltage gain of the amplifier is set by the ratio of  $R_{15}$  to  $R_{11}$ . Capacitor  $C_8$  reduces the dc gain of the circuit to unity while appearing as a short circuit to ac signals. Resistor  $R_{10}$  defines the input impedance of the amplifier.

The closed-loop gain needs to be high since most of it is used to equalise the subwoofer and reduce speaker distortion. The other components to be mentioned are mainly concerned with keeping hf stability within the amp. This is the function of  $C_{12,13}$  and  $C_{16}$ .

It could be argued that most of the parameters of the amplifier just described are well above those required for the circuit function. For example, the slew rate of the op-amps is thousands of times faster than required. Similarly, the distortion level of the amplifier is many times lower than that generated by the speakers. This is simply a reflection on the advancement of commonly available parts. This same level of performance allows supply line voltage rejection ratio of over 100dB, and this is of great importance, as mentioned earlier.

The second aspect of the design, whose overall performance is shown in Fig. 2, involves the manipulation of the pick-up coil voltage to produce motional feedback. Referring to Fig. 1, rather than feed the speaker coil voltage directly into the amplifier's feedback loop, it is fed via the mixer stage built around  $A_6$ . The voice coil output feeds the network comprising  $R_{22,24}$  and  $C_{19}$ . This is necessary because the voltage follows the impedance curve.

Below 200Hz the output is directly proportional to the velocity of the cone. Above this frequency output rises at

approximately 6dB/octave. To maintain the velocity curve – not to mention amplifier stability – the output must be suppressed at high frequency. Capacitor  $C_{19}$  flattens the curve to a straight line.

From here, the signal feeds the mixer amplifier  $A_6$ , via  $R_{22}$ . This is configured as a virtual earth mixer. Feedback resistor  $R_{19}$  is shunted by  $C_{17}$ , which provides further high-frequency roll-off to the coil signal ensuring that the required response is obtained.

The net result of adding this signal to the amplifier input is that the acoustic response from about 10Hz to 150Hz rises at 6dB/octave. In other words, amplifier output voltage is proportional to cone velocity, and acts as a power differentiator.

To obtain a flat response, the amplifier output needs to become proportional to cone acceleration. Rather than differentiate the feedback signal exactly the same result is obtained by integrating the input signal. This function is carried out by  $A_7$ , which, in conjunction with  $R_{21}$  and  $C_{18}$  forms the integrator.

At this stage we have produced a flat response speaker system – flat, at least, in the deep bass region. Plotting the response however reveals that the overall response is that of a high-Q low-pass filter. A glance at Fig. 3 reveals that further work needs to be done. The low-pass response is due to the voice coil inductance resonating with the reflected mov-

ing mass.

Rather than complicate the circuitry further, the solution used here is to tame the response by using a low-Q low-pass filter in series with the amplifier. When this has been done the final response is flat within 1.5dB from 15 to 150Hz. The mild penalty to be paid is that the response rolls off at 24dB/octave above 150Hz. Luckily, this is of little consequence in practice since this point occurs at least half an octave – and usually more than an octave – above the roll-off point required by normal speaker systems.

**Filtering the input-stage**

The main task of the input stage filtering is to extract the bass information from both incoming signals and present this to the power amplifier. In addition, the signal must be manipulated to allow 'seamless' integration of the subwoofer with the existing speakers.

For this design, I decided to drive the sub-woofer directly from the speaker outputs of the existing amplifier. This not only simplifies the design, it is the only rational place to take a signal feed. Once set up the sub-woofer will follow system volume adjustments. This is a particular advantage if, like me, you are always being told turn it down. You can also be assured plenty of drive signal.

Line outputs are rarely standard. The left and right signals

**Infinitely baffling**

In order to squeeze the maximum possible bass from an infinite-baffle enclosure, the volume has to be carefully calculated. Even motional feedback systems are not immune to the laws of physics. If the enclosure is made too large, the woofer will be driven beyond its excursion limit. If it is too small, maximum power input will not allow full excursion.

In order to calculate the required enclosure volume, Thiele-Small equations are required. When a circular piston is fed with a sine wave, it can be shown that the sound-pressure level generated at 1m into half space, A, is,

$$A(\text{dB}) = 40 \log_{10}(d) + 20 \log_{10}(app) + 40 \log_{10}(f) - 83$$

where  $d$  and  $app$  are the diameter and peak-to-peak cone excursion respectively, both expressed in mm and  $f$  is the frequency of interest.

From the term  $40 \log_{10}(f)$ , you will see that the available sound-pressure level falls with frequency at 12dB/octave. If the enclosure volume is chosen so that its response lies to the right of A, Fig. 4, then the driver will be protected from excessive excursions. If the response lies to the left of A then the speaker runs the risk of destruction from bass input. Ideal enclosure response coincides with A.

In order to calculate something useful it is essential to examine the efficiency of the driver and relate this to A. Maximum output that a driver can produce in the pass-band is independent of enclosure

size and can be calculated from the following equations, the first of which is for driver efficiency,  $\eta_o$ ,

$$\eta_o = \frac{k \cdot f_o^3 \cdot V_{as}}{Q_{es}}$$

where  $f_o$  is free-air resonant frequency,  $V_{as}$  is equivalent compliance air volume,  $Q_{es}$  is electrical Q and  $k$  is  $9.64 \times 10^{-10}$  when  $V_{as}$  is expressed in litres. Sound-pressure level in decibels at 1W and 1m distance into half space is,

$$112 + 10 \log_{10}(\eta_o)$$

Maximum sound-pressure level in

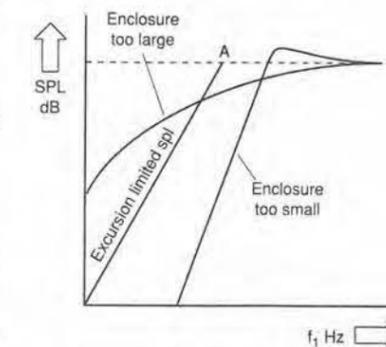


Fig. 4. Excursion sound-pressure level limit rises at 12dB/octave. Speaker responses that intersect the left of A are limited by cone excursion. Right of A are thermally limited but cannot produce maximum sound pressure level. Ideal speaker response coincides with A.

decibels at 1W and 1m distance into half space, B, is

$$112 + 10 \log_{10}(\eta_o) + 10 \log_{10}(p)$$

where  $p$  is the available amplifier output in watts continuous.

All drivers mounted in an infinite-baffle enclosure exhibit second-order high-pass filter response whose amplitude, C, is,

$$C = (\omega^4 + (d^2 - 2)\omega^2 + 1)^{-0.5}$$

where  $w$  is  $f_o/f$  and  $d$  is  $1/Q_{tc}$ ,  $f_c$  being the resonant frequency of the driver mounted in the enclosure and  $Q_{tc}$  is the Q of the driver in the enclosure.

Unfortunately this does not help much because  $Q_{tc}$  and  $f_c$  are not known until the enclosure volume has been determined. But if you choose  $f$  at a low enough frequency, say 1Hz for convenience, then  $w^4 \gg (d^2 - 2)d^2 + 1$  term. This makes it possible to simplify and rewrite the equation for an approximation of C as,  $w^{-2}$ .

To avoid the excursion limit, the 1Hz response must be  $-A+B$  (in dB) down with respect to maximum pass-band sound-pressure level, B. The corresponding amplitude is  $10^{(-A+B)/20}$ , which is  $w^{-2}$ .

As  $f$  is 1Hz,  $\omega$  must equal  $f_c$  so,  $f_c = w = 10^{(-A+B)/40}$ . Having obtained  $f_c$ , the enclosure volume can be simply calculated from,

$$V_b = V_{as} / ((f_c/f_o)^2 - 1)$$

Calculated volume is slightly conservative, but this is no bad thing considering the price of drivers.

from the speaker sockets are passively mixed by  $R_1$  and  $R_2$ . The resulting signal is made available across  $VR_1$ . From here the signal is phase split by  $A_{1,2}$ .

**Avoiding eigentones**

Phase splitting is a useful facility for the following reason. When attempting to crossover between speakers and subwoofers, a particular obstacle is avoiding eigentones. At low frequencies, the average room acts as a gigantic speaker cabinet, with resulting resonances, caused by standing waves between parallel walls.

These resonances often occur just where you want the crossover. By judicious use of the controls, you can use phase shift to tame existing boomy speakers or room characteristics. Choice of in or out-of-phase conditions is selected by  $S_1$  of Fig. 1. A small amount of voltage gain is introduced into the phase splitter circuit via  $R_{4,5}$ . This offsets the gain reduction produced by coil feedback in the power amplifier section. Resistor  $R_3$  couples the op-amps together to provide phase inversion.

Having selected your signal with  $S_1$ , it is then fed into the high-pass filter built around  $A_3$ . This stage defines the lower cut-off point of the system. This is set at 15Hz by the component values chosen. From here the signal is fed into the low pass filter built around  $A_4$ .

**Integrating the design**

In order to integrate the subwoofer easily, a low-Q second-order filter is used. This stage has a Q of 0.5, critically damped for best transient response.

The -3dB point is continuously variable between 45 and 120Hz. I have yet to find a speaker system which cannot be catered for within this range. Finally, the response of the pick-up coil is modified by the low-pass filter built around  $A_8$ , as described earlier in the text. From here the signal gets fed into the signal integrator  $A_7$ , as already discussed.

I have used separate voltage regulators to power the pream-

plifier section. This may seem like an extravagance but it is a small price to pay for total isolation on the power lines between chips.

On the subject of power supply, Fig. 1, this is completely conventional. Mains voltage is stepped down and full-wave rectified via a bridge, before being smoothed by  $C_{14,15}$ . The centre tap of the secondaries is used for the 0V line,

**Points to watch out for**

There are a few points to watch for when implementing the subwoofer. First the cabinet. Initially I intended to build the subwoofer in two enclosures with the intention of siting these below my existing speakers. Since there is no phase information at low frequencies, it is possible, in principle, to site the subwoofer wherever you choose. In practice the best position is likely to be between the speakers, against the wall. This position will give you an extra 3dB of output for as the system will be driving into quarter space.

Conventional wisdom suggests that corner positions should be avoided as this will tend to emphasise room resonances. Circumstances alter cases, and the extra 3dB of output might be useful.

An advantage of small enclosures, in addition to the improved rigidity, is that they are too small for internal standing wave generation. Since I am not a carpenter and find woodwork a chore I built my cabinets from 15mm chipboard, Fig. 6, available everywhere and in a variety of finishes.

Panel fixing is easiest using Araldite rapid fairly liberally along the seams. The drivers require 230mm diameter cut-outs. They should be mounted on gaskets made from self adhesive draught excluding strip. Before mounting the drivers, fill along the panel seams with filler or silicone sealant to ensure airtightness.

When assembling the electronics ensure that  $PR_1$  is adjusted to short  $Tr_2$ 's base to collector. For obvious reasons it is desirable to set the quiescent current in the output stage before mounting the electronics.

**Inductive motional feedback**

Inductive pickup is probably the simplest form of motional feedback control. In order to understand its operation, it is necessary to realise that the pickup voltage is proportional to cone velocity. Figure 5 shows the relevant curves. Curve A is the unequalised speaker response and corresponds with the cone acceleration.

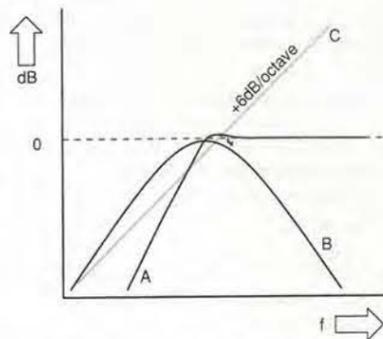


Fig. 5a. Unequalised speaker response, A, resulting velocity curve picked up by the second voice coil, B, and resulting response curve from the speaker, C.

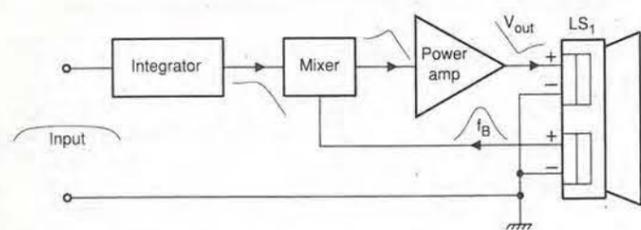


Fig. 5b. Motional feedback using a second coil within the loudspeaker to produce the feedback signal. Error correction signal is introduced via a mixer amplifier.

Curve B is the resulting velocity curve as picked up by the coil. When this voltage is used as negative feedback, the resulting response from the speaker increases with frequency at 6dB/octave, Curve C.

To obtain a flat response, the feedback voltage would need to be proportional to cone acceleration since this is identical to the system response. This would imply differentiating the coil voltage before feeding it back. The alternative, used in this design, is to integrate the incoming signal so that this falls at 6dB/octave. When fed from this signal the overall response of the speaker is flat. There is no difference in system performance either in amplitude or phase response

between differentiating the pickup signal or integrating the input.

Figure 5b shows the basic circuit in block form. Rather than complicate, and possibly destabilise, the amplifier, the feedback is introduced via a mixer amplifier. This is a virtual-earth circuit which effectively adds the input and feedback signals. This is then used to drive the amplifier.

Closed loop gain of the amplifier produces the corrected signal to the speaker. The advantage of motional feedback is that errors in both the enclosure response and in the driver are considerably reduced by negative feedback.

**Motional-feedback subwoofer parts**

**Resistors**

Unspecified types are 1% metal film

$R_{1,2}$	47k	2
$R_{3/24}$	10k	4
$R_4$	110k	1
$R_5$	100k	1
$R_6$	150k	1
$R_7$	75k	1
$R_{8,9}$	15k	2
$R_{10}$	39k	1
$R_{11}$	2k2	1
$R_{12,25}$	22k	2
$R_{13}$	330	1
$R_{14,15}$	82k	2
$R_{16}$	4k7	1
$R_{17,18}$	0.47/3W	2
$R_{19,20,26,27}$	560k	4
$R_{21}$	680k	1
$R_{22}$	180k	1
$R_{23}$	43k	1
$VR_1$	4k7 log pot	1
$VR_2$	22k lin dual pot	1
$PR_1$	10k hor. preset	1

**Capacitors**

$C_{1-4,18}$	100n Mylar	4
$C_{5,6,9,10}$	100n cer. disc	4
$C_7$	10 $\mu$ /50V	1
$C_8$	100 $\mu$ F/25V	1
$C_{11/12/13/17}$	1nF Mylar	4
$C_{14/15}$	6800 $\mu$ F/63V	2
$C_{16}$	270pF cer.	11
$C_{19}$	47nF Mylar	1
$C_{20}$	2n7 Mylar	1
$C_{21}$	4n7 Mylar	1

**Active devices**

$IC_{1,3}$	78L15	2
$IC_{2,4}$	79L15	2
$A_{1-8}$	TL074	2
$Tr_{1,3}$	BC327	2
$Tr_2$	BC337	1
$Tr_{4,6}$	BDT65C	2
$Tr_{5,7}$	2N3055	2
$D_{1-4}$	1N5408	4

**Miscellaneous**

Heat sink	see text
TO3 mounting kits	4
Volt DVC250/1, 8 $\Omega$ drivers	2
22-0-22V sec. 120VA transformer	
SPST changeover switch	1
Control knobs	2

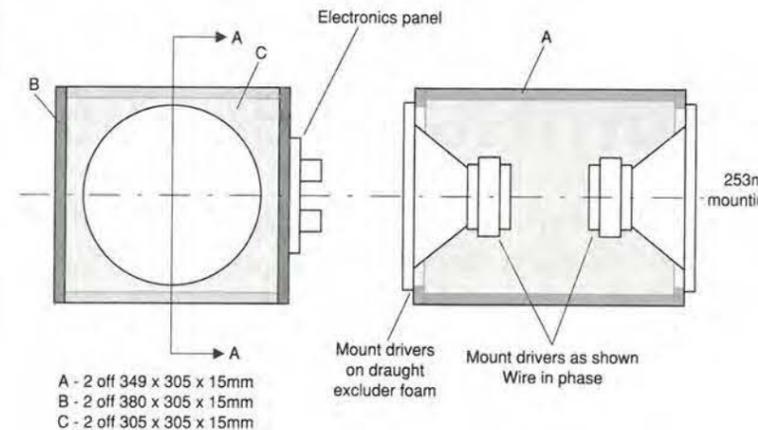


Fig. 6. Subwoofer enclosure details. Since the enclosure is small, it is rigid and inhibits standing waves.

With the speakers disconnected, test that the output is within 50mV or so of 0V. Quiescent current is set up by slowly adjusting  $PR_1$  for a 20mV drop across  $R_{17}$  and  $R_{18}$ . Although the heat sink gets rather warm under conditions of high drive, I have not found it necessary to use thermal feedback via  $Tr_2$ . But there is no reason why  $Tr_2$  cannot be adhered to the sink.

I mounted the electronics within the enclosure. The output stage requires a large heat sink, of at least 1.5 $^\circ$ /W. I used a 120 by 100mm finned sink.

Control panels are always a problem with this type of equipment. I mounted my controls and heat sink on the lid of an MB6 type ABS case which fits into a cut-out in one of the panels. This is secured by six, 30mm M3 screws. Whatever panel you use remember that an air-tight seal is needed.

The drivers are wired up as shown in the Fig. 1a, in parallel and in phase. Ensure that the pickup coil is phased as shown.

**Final adjustments**

Having set the quiescent current and fastened everything into place, all that remains is to adjust the level and cut-off frequency to suit your system. The best way to start is with the cut-off frequency set high and gain set low. Next, adjust both for the best sound.

Finally, was the effort worth it? Definitely yes. I now get to hear things I have never heard before on my cds. In addition, the clarity and speed at which bass notes are generated and disappear is something of a revelation - after years of reflexed muddiness. ■

**Special offer**

Any Electronics World reader mentioning page 109 of the February issue can obtain one pair of Volt drivers, as used in the subwoofer, at the special price of £234 - including VAT and UK delivery. Normally, the pair sells at over £257, excluding delivery. Send PO or cheque payable to Wilmslow Audio at 50 Main Street, Broughton Astley, Leicester LE9 6RD. Phone 01455 286603 or fax 286605 for further details.

# Multichannel speaking monitor

Visual displays certainly have their uses but there are times when a more immediate message is needed. Heikki Kalliola's speaking monitor provides digitally-addressable and re-recordable spoken messages.

My design for a multi-channel speaking monitor is based on an Information Storage Devices speech memory chip. With no moving parts and needing few external components, the circuit is an economical means of making many kinds of announcements, including measurements and threshold warnings.

One application of the speaking monitor is the reporting of exceptional conditions in vehicle environments. Using spoken messages, there is no need to divert your attention to the indicators on the instrument panel. This device can be mounted in an enclosure small enough

to hide behind the dashboard without any rebuilding.

The ISD1016A\* speech storage chip used can record and play back 16 seconds of voice in a number of individually-addressable segments — in this case four, of four seconds each in length. Each of the four messages can be triggered according to the situation. The chip family includes members with longer recording time, but 16 seconds is enough for the purpose described here.

Inputs 1 to 4 are constantly monitored, Fig. 1. If one or more input is grounded, a message from the corresponding memory address is fed

to the loudspeaker. The message is repeated until the grounded contacts open.

If all the inputs are used, there is time about four seconds for each message. If all inputs are not needed, the ones used can have more time allocated to them. If for example only line number 1 is used, the announcement can be a full 16 seconds.

## Recording and playing back

Recording is performed by first selecting the message to be dictated on the sensor line. Selection is done with switch  $S_1$ . As drawn,  $S_1$  points to line 1. After line selection, button  $S_3$  is

pushed while you read the message in to the microphone.

Pushing the button starts recording and releasing it stops it. Remember, that if the next line, i.e. number 2 on the diagram, is to be used, the recording time can not exceed four seconds. If it does, the tail part of the message will overlap on to next line's memory area. Accordingly the messages of other lines are recorded by first selecting the line with  $S_1$ .

Messages can be changed at any time and remain in memory when the power is removed. Messages can be checked by briefly pressing button  $S_2$ . That triggers playback from the

\*ISD1016A is obsolescent, but UK distributor Sequoia, informs us that the ISD2560 is almost identical, but has an extra address line and more memory. Sequoia's telephone and fax numbers are 01734 258000 and 258020 respectively.

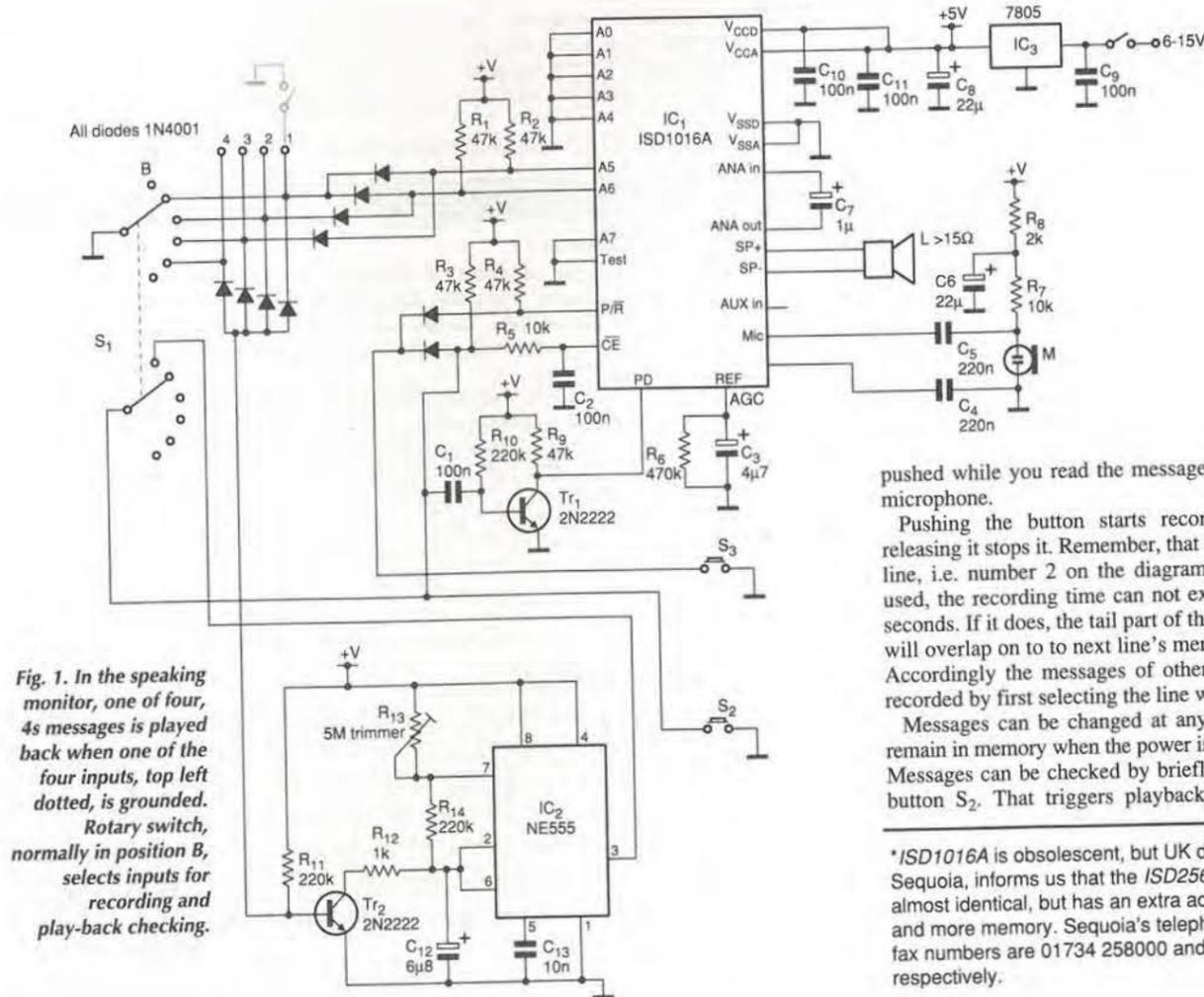


Fig. 1. In the speaking monitor, one of four, 4s messages is played back when one of the four inputs, top left dotted, is grounded. Rotary switch, normally in position B, selects inputs for recording and play-back checking.

memory location pointed to by  $S_1$ . Thus recordings are easily made.

Once the messages are loaded,  $S_1$  is turned to its base position, indicated as B on the diagram, and the device is ready for use. When one or more of the input lines is grounded, the message from that line's memory area is spoken from the loudspeaker and repeated until the line returns to its normal state.

## Circuit logic

When an input line is grounded, diodes set the right address with bits  $A_5$  and  $A_6$ . At recording and check playback this grounding is performed by  $S_1$ .

The memory chip requires that during recording pins P/R and CE are grounded. Signal PD keeps power consumption extremely low when at +5V. To record and play back, this line must be grounded. The signal also acts as reset switch, in the event of a memory overflow. Resetting is carried out by pulling the line to +5V and back to ground again.

When recording,  $S_3$  pulls pins P/R and CE down to ground via diodes. At the same time transistor  $Tr_1$  stops conducting for a moment due to grounding of the base via  $C_1$ . A positive reset-pulse is created from the collector to pin PD. Releasing of  $S_3$  generates the end-of-message mark to the memory.

To check play back,  $S_2$  starts the message by pulling down the chip enable pin, CE, and

creating a reset pulse to PD with  $Tr_1$ . Playback starts at the address pointed to by  $S_1$  and continues until the end-of-memory mark.

Grounding of input line pulls also down the base of  $Tr_2$ . The transistor stops conducting, triggering the astable multivibrator timer chip  $IC_2$ . The chip puts out negative-going pulses equivalent to pushing the playback button  $S_2$ . If  $S_1$  is at base position, B, these pulses pass through to playback triggering.

Time interval between pulses, and therefore also the rate of message repetition, is dictated by the value of  $R_{13}$ . If, for example, only one input is used and the maximum length message recorded in one location, the interval time must be over 16 seconds to avoid rolling over. If on the other hand, all the inputs are used, the minimum interval is about five seconds, and the message length cannot exceed four seconds.

## Anti down-out switch for vehicles

In vehicles, there are many possible stimuli for the monitor. Examples are oil pressure warning, over-high water temperature and low fuel indication. In many cases, easily accessible switch contacts for these are already installed in the car.

When this design is used in vehicles, the usual power supply is the 12V battery, from which the voltage is dropped to 5V via regulator  $IC_3$ .

In automotive applications, the car radio

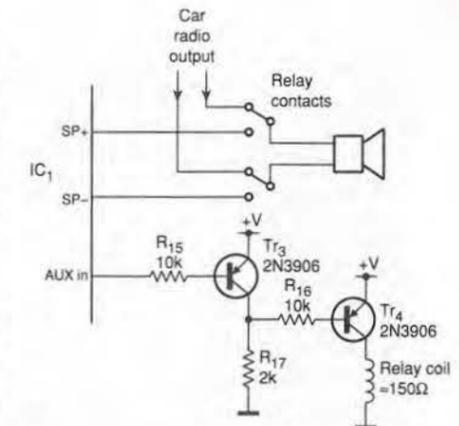


Fig. 2. In automotive applications, this switch circumvents the problem of a loud radio obscuring the announcement by automatically switching the radio's speaker over to the speaking monitor unit when a message is triggered.

might obscure messages. To avoid this, you can add the switching circuit of Fig. 2. With this modification, the radio loudspeaker replaces the monitor's loudspeaker and serves a dual purpose. Control for the output relay is taken from the speech memory's auxiliary input, which is held high during playback.

Do not forget to add a 10Ω series resistor, if the loudspeaker has very low impedance. ■

OSCILLOSCOPE LIVE CHOP Page -0.25

MEASURE MODE  
CH 1  
CH 2  
CHOP  
ADD  
COMPARE  
X-Y PLOT

1.06 0.40 -0.26 -0.93 -1.60 -2.25 -2.93 -3.60 -4.26

0.30(sec) 0.30 0.90

16.5 13.8 11.2 8.53 5.8

0.33 -0.33 -2.13 -4.80

FREQ TIME DIV TIME-MAG TIME-OUT HYSTERESIS SLOPE TRIGSOURCE PRINT COMMENT SETTINGS

SPECTRUM ANALYZER CH 1

HOLDING WINDOW  
RECTANGLE  
HANNING  
MARKING  
BLACKMAN  
BARTLETT

3.70 3.20 2.70 2.20 1.70 1.20 0.70 0.20 -0.30

0(HZ) 2441406 2441420

MEASURE HOLD-FFT MODE

FREQUENCY FREQ-MAG

PRINT COMMENT SETTINGS

**FREE** **μScope**

INPUT 20 volt max.

100 kHz sampling

to PC printerport

You get a free **μScope** when you buy a TP508 or a HS508 until september 1st 1996

resolution 8 bits  
sampling speed 100 kSamples/sec  
input range 2.5V, 5V, 10V and 20V  
connects to PC parallel printer port

**TiePieSCOPE HS508**

- interface PC parallel printer port
- sampling speed 50 Msamples/sec
- resolution 8 bits
- input range 50 mV/div - 20V/div
- record length 32KByte/channel
- price £597.00, incl. software, user manual and 2 probes (1:1/1:10 switchable)

**TP508**

- interface PC-XT/AT ISA slot
- sampling speed 50 Msamples/sec
- resolution 8 bits
- input range 5 mV/div - 20 V/div
- record length 32 KByte/channel
- price £ 630.00 incl. software, user manual and 2 probes (1:1/1:10 switchable)

contains an Oscilloscope, a Spectrum analyzer, a Voltmeter, and a Transient recorder. All instruments are controlled in the same intuitive way and provide for saving and recalling waveforms and settings, cursor measurements, hardcopy on matrix/laser printer and online help. Minimum requirements: a 80286-based PC with 2MByte and running MS-DOS 3.3 or higher.

Fax for a free demo disk and catalog of all our products

Easy installation: just plug in and measure

TiePie engineering (NL)  
P.O. Box 290  
8600 AG Sneek  
The Netherlands  
Tel: +31 515 415 416

Koperslagersstraat 37  
8601 WL Sneek  
The Netherlands  
Fax: +31 515 418 819

TiePie engineering (UK)  
28, Stephenson Road, Industrial Estate,  
St. Ives, Cambs, PE17 4WJ,  
United Kingdom  
Tel: +44 1480 460028 Fax: +44 1480 460340

Prices are excluding V.A.T.

**15% reader discount**



Covering 100kHz to 150MHz in six ranges, this RF generator with amplitude modulation is available to *Electronics World* readers for just £129 - fully inclusive of VAT and postage.

## 100kHz to 150MHz RF signal generator for just £129

Normally, the Loadstar SG4160B 150MHz signal generator sells for £129 excluding 17.5% VAT and delivery costs. But *Electronics World* readers can obtain this instrument for just £129 - fully inclusive of VAT and delivery. This represents a saving of well over 15%.

Vann Draper's SG4160B bench generator covers 100kHz to 150MHz in six ranges - and up to 450MHz via third harmonic. It has an internal 1kHz oscillator for amplitude modulation up to 30%, which is also accessible on the front panel. There are also facilities for connecting an external modulation signal of between 50Hz and 20kHz.

Featuring a crystal checker with a range of 1 to 15MHz, the 4160B provides an RF output of up to 100mV RMS, unloaded, at all frequencies up to 35MHz. Attenuation is controlled via a high/low switch and fine adjuster.

To receive your RF generator, simply fill in the coupon on the right and send it, together with a cheque or postal order for £129, to Vann Draper Electronics at Unit 5, Premier Works, Canal Street, South Wigston, Leicester LE18 2PL.

Alternatively fax credit card details with order on 0116 2773945 or telephone on 0116 2771400. Please direct all queries relating to this offer to Vann Draper Electronics

\*Overseas readers can also obtain this discount but details vary according to country. Please ring, write or fax to Vann Draper Electronics.

### Use this coupon to order your SG4160

Please send me.....SG4160(s) RF Signal Generators at the fully inclusive special offer price of £129 each.

Name

Company (if any)

Address

Phone number/fax

Total amount £.....

Make cheques payable to Vann Draper Electronics Ltd  
Or, please debit my Master, Visa or Access card.

Card No

Expiry date

Please mail this coupon to Vann Draper Electronics, together with payment. Alternatively fax credit card details with order on 0116 2773945 or telephone 0116 2771400. Address orders and all correspondence relating to this order to Vann Draper Electronics at Unit 5, Premier Works, Canal Street, South Wigston, Leicester, LE18 2PL. Overseas readers can also obtain this discount but details vary according to country. Please ring, write or fax to Vann Draper Electronics

# ELECTRONICS WORLD

+ WIRELESS WORLD

*Electronics World+ Wireless world* is applied electronic design. We'll show you how to use the latest silicon technology plus...

- ✓ CAE software
- ✓ New product reviews
- ✓ Technology reports
- ✓ Detailed circuit diagrams
- ✓ Innovations
- ✓ Explanations of complex technology
- ✓ Comment and much more in your issue.



So whether you are designing your own system or curious about your competitors *Electronics World + Wireless World* will help you keep the leading edge.

**Money back Guarantee.**  
Receive a full refund on your subscription within the first 90 days if you are not completely satisfied. Thereafter, we'll refund the unused portion of your subscription should you wish to cancel.

## SAVE UP TO 10%

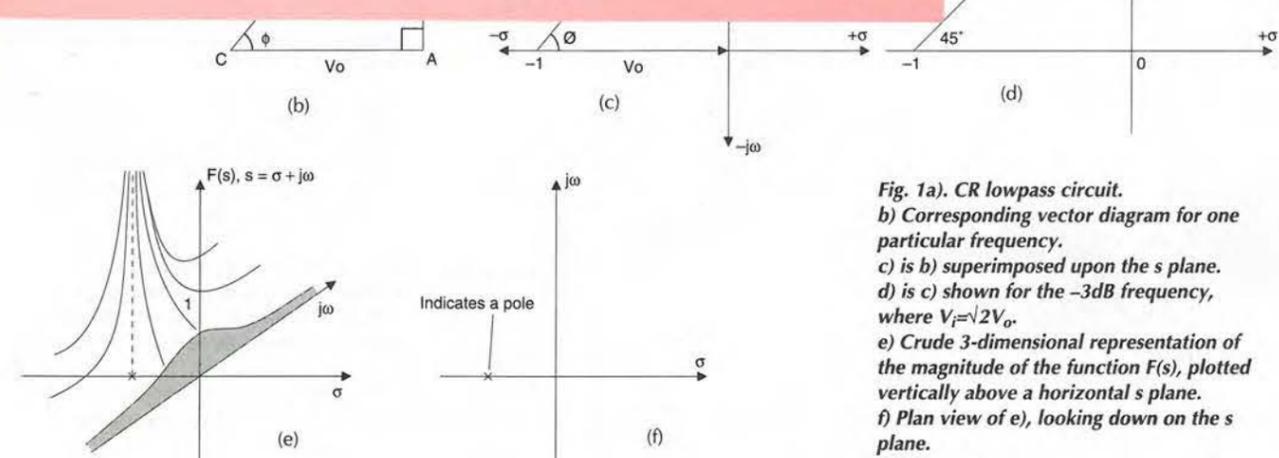


Fig. 1a). CR lowpass circuit.  
b) Corresponding vector diagram for one particular frequency.  
c) is b) superimposed upon the s plane.  
d) is c) shown for the -3dB frequency, where  $V_i = \sqrt{2}V_o$ .  
e) Crude 3-dimensional representation of the magnitude of the function  $F(s)$ , plotted vertically above a horizontal s plane.  
f) Plan view of e), looking down on the s plane.

# JRE

tor. Phase angle  $\phi$  is given by:  
 $\phi = \tan^{-1} I/R$   
 $R$  and  $I$  are the real and imaginary parts of the denominator. Clearly,  $-\omega CR/1$  is zero at  $\omega = 0$  and tends to  $-\infty$  at infinite frequency,  $0^\circ$ , at 0Hz and tends to  $-90^\circ$  at very high frequencies.

Two results give an important rule:  
The amplitude of the response at any frequency due to a pole is inversely proportional to the length of a line from the pole corresponding point on the  $j\omega$  axis. The phase is given by the angle that the line makes with the positive horizontal axis counting anticlockwise rotation from the pole as negative, indicating a lagging response.

Figure 1c) shows how the vector diagram with the pole/zero diagram. Figure 1d) shows the same again but drawn for the -3dB frequency, the frequency where the reactance of capacitor equals the resistance  $R$ .

15% read



# 100kHz generator

Normally, the Loadstar SG41 generator sells for £129 excluding delivery costs. But *Electronics World* obtain this instrument for just £101, including VAT and delivery. This represents a saving of over 15%.

Vann Draper's SG4160B 100kHz to 150MHz in six ranges oscillator for amplitude modulation is also accessible on the front panel. It is also accessible on the front panel facilities for connecting an external oscillator of between 50Hz and 20kHz.

Featuring a crystal checked to 0.1% accuracy, the 4160B provides a 100mV RMS, unloaded, at all frequencies up to 35MHz. Attenuation is controlled via a high/low switch and fine adjuster.

To receive your RF generator, simply fill in the coupon on the right and send it, together with a cheque or postal order for £129, to Vann Draper Electronics at Unit 5, Premier Works, Canal Street, South Wigston, Leicester LE18 2PL.

Alternatively fax credit card details with order on 0116 2773945 or telephone on 0116 2771400. Please direct all queries relating to this offer to Vann Draper Electronics

\*Overseas readers can also obtain this discount but details vary according to country. Please ring, write or fax to Vann Draper Electronics.

**Yes, I would like to subscribe to Electronics World + Wireless World.**

- 1 Year  UK £32  Europe £46  Rest of world £56
- 2 Years  UK £58 **SAVE 10%**  Europe £83 **SAVE 10%**  Rest of world £101 **SAVE 10%**

Name \_\_\_\_\_  
 Job Title \_\_\_\_\_  
 Company \_\_\_\_\_  
 Address \_\_\_\_\_  
 Post Code \_\_\_\_\_  
 Telephone \_\_\_\_\_  
 Fax \_\_\_\_\_  
 Country \_\_\_\_\_  
 Internet Address \_\_\_\_\_

**THREE WAYS TO PAY**

- 1  I enclose a cheque made payable to Electronics World + Wireless World for £ \_\_\_\_\_
- 2  Please charge my Mastercard/Access/Visa/Diners Club/American Express (please delete appropriate card) with the sum of £ \_\_\_\_\_

Card number \_\_\_\_\_ Expiry Date \_\_\_\_\_  
 Signed \_\_\_\_\_ Date \_\_\_\_\_

3  Please invoice me/my company. Purchase order number \_\_\_\_\_  
 Company VAT registration number \_\_\_\_\_

Please allow 28 days for delivery of your first issue.

Please tick here if you do not wish to receive direct marketing promotions from other companies.

Post in the UK to Electronics World Subscriptions, FREEPOST RCC 2619, PO Box 302, Haywards Heath, RH16 3BR. Telephone 01444 445566. Post from elsewhere to Electronics World Subscriptions, PHQ-D/1700/RH, PO Box 302, Haywards Heath, RH16 3BR, UK. Telephone +44 1444 445566

Phone number/fax \_\_\_\_\_

Total amount £ \_\_\_\_\_

Make cheques payable to Vann Draper Electronics Ltd  
 Or, please debit my Master, Visa or Access card.

Card No \_\_\_\_\_  
 Expiry date \_\_\_\_\_

Please mail this coupon to Vann Draper Electronics, together with payment. Alternatively fax credit card details with order on 0116 2773945 or telephone 0116 2771400. Address orders and all correspondence relating to this order to Vann Draper Electronics at Unit 5, Premier Works, Canal Street, South Wigston, Leicester, LE18 2PL. Overseas readers can also obtain this discount but details vary according to country. Please ring, write or fax to Vann Draper Electronics

## Ian Hickman takes a further look at how circuit operation can be represented pictorially.

# More in the PICTURE

An earlier article of mine<sup>1</sup> reviewed various ways of representing circuit action, with a view to showing how the different representations complemented each other. So the article covered vector diagrams, the circle diagram – a sort of generalised vector diagram showing what happens as the frequency varies – Bode plots – which also show what happens as the frequency varies – and pole-zero diagrams.

That was the intention, but my apologies to any readers who looked in vain for any zeros – they failed to materialise due to lack of space. This article rectifies the omission, and carries the story on another stage.

### Poles

Well, just one pole to begin with, the one to be found in the lowpass CR circuit of the last article, the response of which was shown there as Fig. 6, and here as Fig. 1b). The equation giving the frequency response, as derived in the last article, is:

$$v_o/v_i = 1/(1+j\omega CR) \quad (1)$$

Note that, as last time, the base of the triangle (of length unity) is the vector  $v_o$ , then the two terms in the denominator take you from the pole at  $\sigma=-1$  to the origin, and then a distance  $\omega$  up the  $j\omega$  axis (assuming as before that  $CR=1$ ), where this distance represents the voltage drop across the resistor  $R$ .

Adding vectorially (the  $j$  indicating that these vectors are at right angles), this brings one to the tip of the sloping line, which represents the input voltage needed to give unity output voltage. Thus  $v_i/v_o$  at any frequency is proportional to the distance from the pole at  $\sigma=-1$  to the corresponding point on the  $j\omega$  axis. So the frequency response,  $v_o/v_i$ , is proportional to the reciprocal of this distance.

Equation 1 also indicates the phase, as follows. First, make the denominator real, by multiplying top and bottom by  $(1-j\omega CR)$ , the complex conjugate of the denominator. The equation then becomes:

$$v_o/v_i = (1-j\omega CR)/(1+\omega^2 C^2 R^2)$$

and, since the denominator is now just a number, the phase angle is given just by the

numerator. Phase angle  $\phi$  is given by:

$$\phi = \tan^{-1} I/R$$

where  $R$  and  $I$  are the real and imaginary parts of the numerator. Clearly,  $-\omega CR/1$  is zero at 0Hz and minus infinity at infinite frequency, so  $\phi$  is  $0^\circ$ , at 0Hz and tends to  $-90^\circ$  at very high frequencies.

These two results give an important rule:

*The amplitude of the response at any frequency due to a pole is inversely proportional to the length of a line from the pole to the corresponding point on the  $j\omega$  axis, and the phase is given by the angle that the line makes with the positive horizontal axis, counting anticlockwise rotation round the pole as negative, indicating a lagging response.*

Figure 1c) shows how the vector diagram ties up with the pole-zero diagram. Figure 1d) is the same again but drawn for the -3dB frequency, the frequency where the reactance of the capacitor equals the resistance  $R$ .

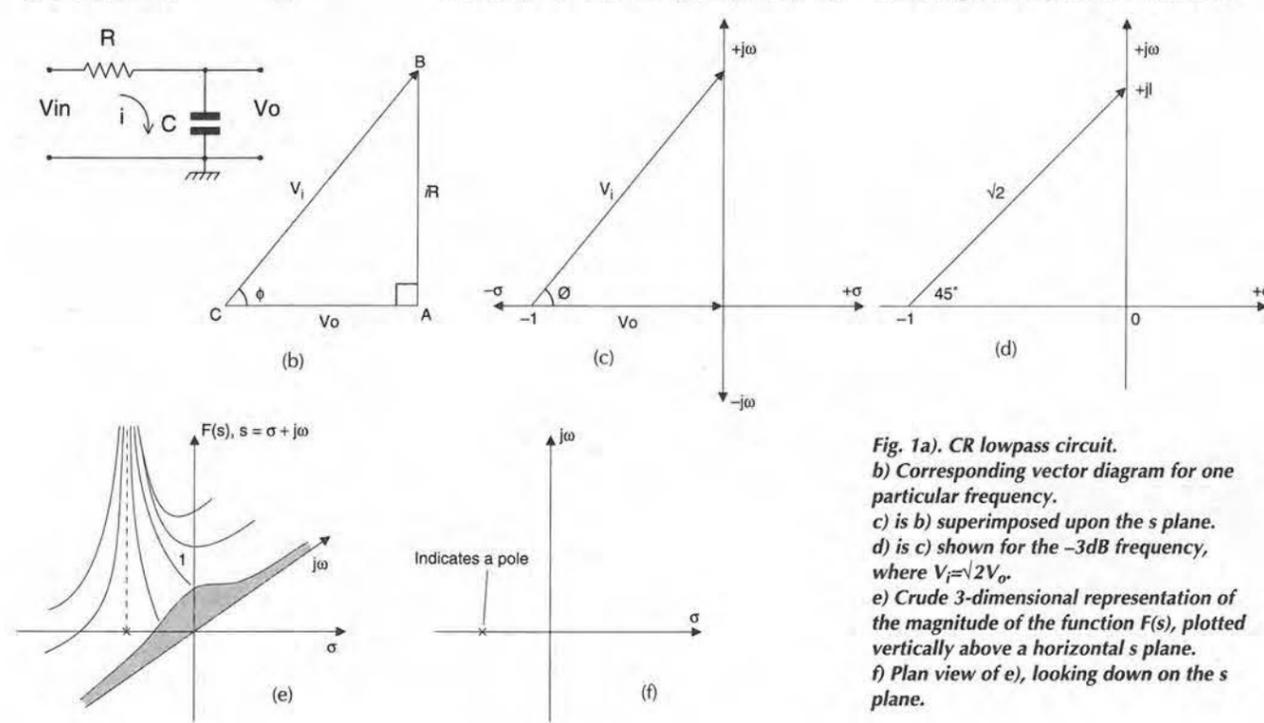


Fig. 1a). CR lowpass circuit.  
 b) Corresponding vector diagram for one particular frequency.  
 c) is b) superimposed upon the  $s$  plane.  
 d) is c) shown for the -3dB frequency, where  $V_i = \sqrt{2}V_o$ .  
 e) Crude 3-dimensional representation of the magnitude of the function  $F(s)$ , plotted vertically above a horizontal  $s$  plane.  
 f) Plan view of e), looking down on the  $s$  plane.

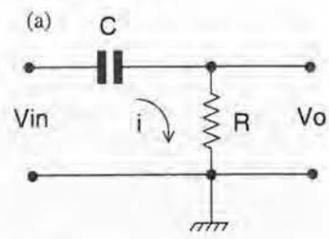


Figure 1e is a three-dimensional representation of the magnitude of  $F(s)$ , plotted vertically above a horizontal  $s$  plane. Only that part of the surface to the left of the  $j\omega$  axis (where  $\sigma$  is negative) has been shown. The 'cut edge', above the positive  $j\omega$  axis, gives the magnitude of the frequency response, as a linear plot against frequency (also linear). In plan view, the  $s$  plane looks like Figure 1f - there is a pole at the point where  $s$  has the coordinates  $(-1, 0)$ .

As noted in the earlier article, in terms of the complex frequency variable  $s$ , the transfer function  $F(s)$  which gives  $v_o/v_{in}$  becomes  $F(s)=1/(s+1)$ , where  $s=\sigma+j\omega$ .

If the pole moves further and further toward the origin, the response will rise by 6dB every time the frequency is halved, and so on indefinitely. With a pole at the origin, you have an integrator - i.e., an ideal op-amp with capacitive feedback from the output to the inverting input, and with the input applied via a resistor.

...and zeros

Now for a 'finite zero', that is to say a zero at a finite frequency, which will appear on the pole/zero diagram. You get one with a high-pass (bass cut or passive lead) circuit, shown in Figure 2a, along with its circle diagram,

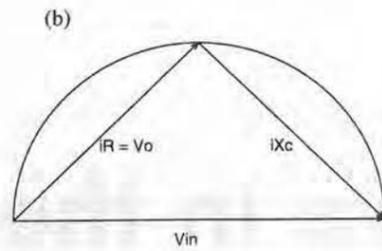


Fig. 2. a) CR highpass circuit. b) Circle diagram, with vector diagram for the -3dB frequency. Note: the input current  $i$  is in phase with  $V_o$ , i.e. leading  $V_{in}$  by 45° at this frequency. c) Vector diagram of b), superimposed on the pole/zero diagram. d) Crude 3-dimensional representation of the magnitude of the function  $F(s)$ , plotted vertically above a horizontal  $s$  plane.

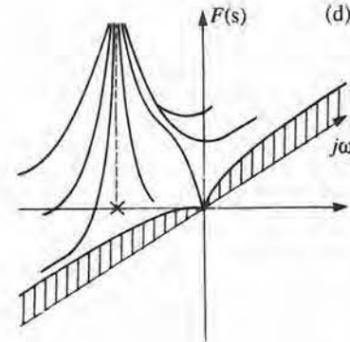
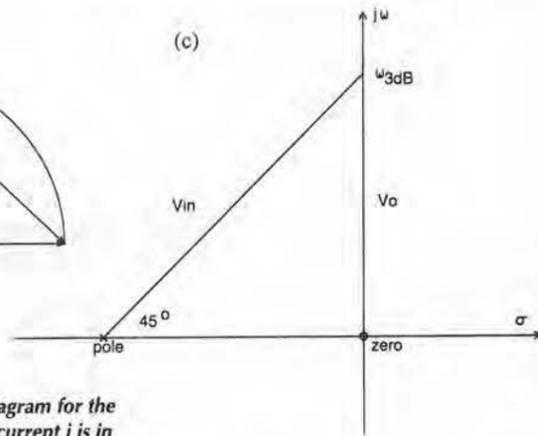


Figure 2b). Note that, by convention, a pole on the  $s$  plane (the  $j\omega$  versus  $\sigma$  plot) is denoted by a cross, and a zero by a circle or nought. From the vector/circle diagram of Figure 2b), for a simple highpass CR circuit:

$$v_o/v_i = R/(R+1/j\omega C) = j\omega CR/(1+j\omega CR) \quad (2)$$

Thus the general expression for the transfer function  $F(s)$  is  $F(s)=s/(1+s)$ , assuming that the frequency is normalised, or (effectively the same thing) that  $CR=1$ .

Clearly, as well as exploding to infinity when  $s$  is  $-1$  (when  $\omega = \text{zero}$  and  $\sigma = -1$ ),  $F(s)$  is 0 when  $s$  is 0 (when both  $\omega$  and  $\sigma = 0$ ), due to the  $s$  in the numerator. Figure 2c shows the

pole/zero diagram, with its zero at 0Hz, with the vector diagram superimposed, shown for the case where normalised  $\omega=1$ , the -3dB point.

Note that in Figure 1c),  $v_o$  is represented by the line from the pole to the origin. This is because, in the vector diagram, this is the voltage  $iX_c$  across the capacitor. In Figure 2c),  $v_o$  is represented by the line from the origin to the point on the  $j\omega$  axis representing the frequency of interest. This is because this line represents  $iR$ , across which the output voltage is developed, Fig. 2a).

You can see from Fig. 2c) and Eqn 2 that, for very low frequencies (where  $v_{in}$  is virtually horizontal and the denominator virtually equal to unity),  $v_o$  is directly proportional to the distance from the origin to the point on the  $j\omega$  axis. Also, at very low frequencies,  $v_o$  leads  $v_{in}$  by 90°. This is made clear by the vector diagram, and can be checked by making the denominator of Eqn 2 real and finding  $\tan \phi$ , as was done above for the lowpass case.

These two results give another important rule:

*the amplitude of the response at any frequency due to a zero is directly proportional to the length of a line from the zero to the corresponding point on the  $j\omega$  axis, and the phase is given by the angle that*

Fig. 3. a) Transitional lag circuit. b) The corresponding pole/zero diagram. c) Three-dimensional representation of the logarithm of the magnitude of the function  $F(s)$ . d) This circuit, has unity gain at 0Hz, falling to  $R_2/(R_1+R_2)$  at very high frequencies

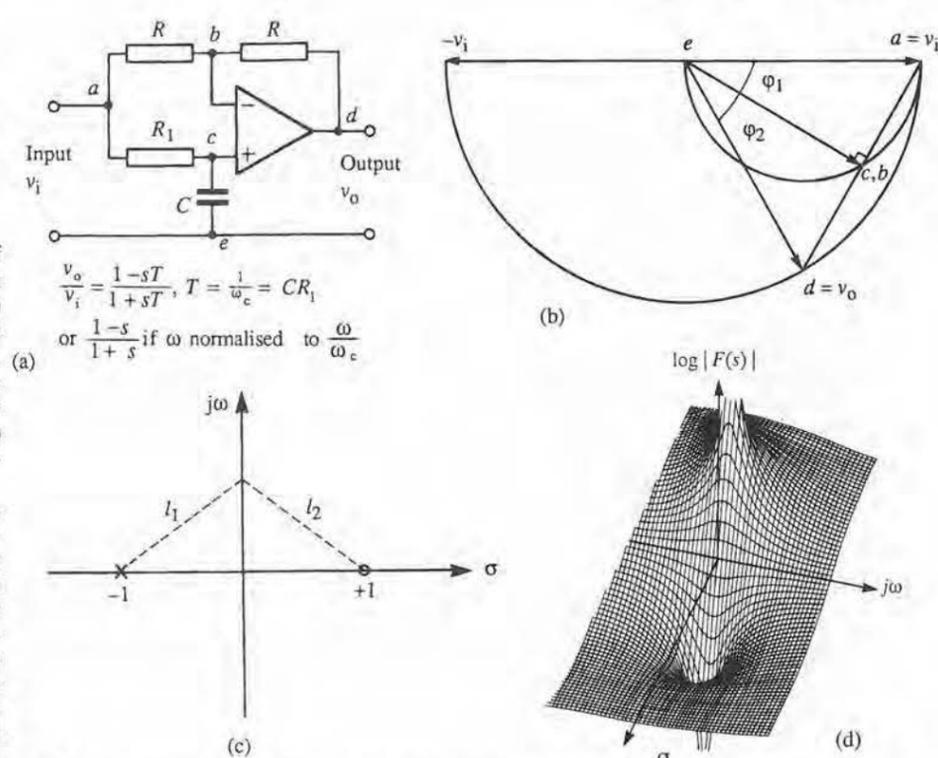
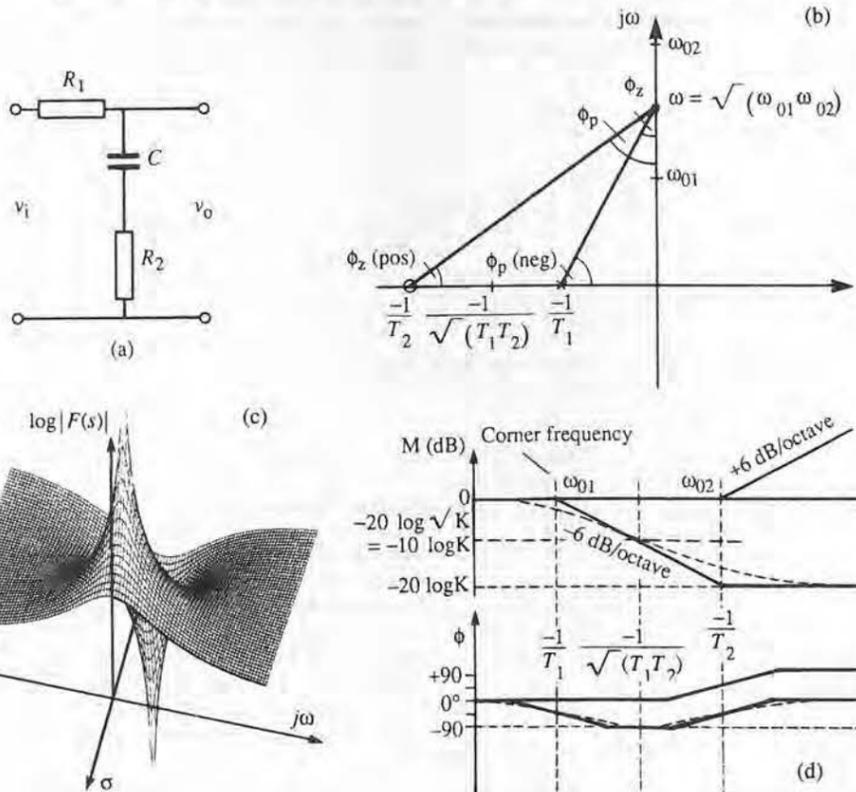


Fig. 4. a) First-order all-pass circuit with unity gain at all frequencies has a phase shift varies with frequency. b) Vector/circle diagram for the circuit a). c) Pole/zero plot for the circuit of a). d) 3-dimensional representation of the logarithm of the magnitude of the function  $F(s)$ , corresponding to c).

$K=T_2/T_1=(1/\omega_{02})/(1/\omega_{01})$ . Term  $\omega_{01}$  is the lower corner frequency, set by  $1/[C(R_1+R_2)]$  and  $\omega_{02}=1/CR_2$  is the upper, which means that  $K=R_2/(R_1+R_2)$ .

This time, the pole zero diagram Fig. 3b, instead of showing normalised frequencies, shows actual frequencies, defined in terms of the circuit time-constants. The point shown on the  $j\omega$  axis represents the frequency which is the geometric mean of  $\omega_{01}$  and  $\omega_{02}$ , the point of inflection of the response in Fig. 3d). Up to this frequency,  $\phi_p$  is increasing faster than  $\phi_z$ , so that the output lags the input, but beyond this frequency,  $\phi_z$  increases faster so the lag decreases again. Eventually, as  $\phi_p$  and  $\phi_z$  both tend to 90°, they cancel out, and the output is back in phase with the input, but reduced in amplitude to  $R_2/(R_1+R_2)$ .

because the horizontal axis, representing frequency, is logarithmic, and the vertical axis, representing the magnitude of the response  $M$ , is in dB - i.e., also logarithmic. The actual response will never quite reach a 6dB/octave cut-off rate unless the corner frequencies  $\omega_{01}$  and  $\omega_{02}$  are infinitely far apart, and of course it is curved at the corner frequencies, unlike the notional asymptote.

Up till now, it has been convenient to work with normalised frequencies since, in both the low pass and high pass circuits of Figs 1 and 2, there is just the one corner frequency, where the response changes (gradually) from flat to -6dB per octave (or vice versa). But with the transitional lag, there are two different frequencies to consider, and these can conveniently be defined in terms of the  $CR$  time constants of the circuit.

Working out the response of the transitional lag of Fig. 3a gives:

$$\begin{aligned} \frac{v_o}{v_{in}} &= \frac{(1/j\omega C) + R_2}{(1/j\omega C) + R_2 + R_1} \\ &= \frac{1 + j\omega CR_2}{1 + j\omega C(R_1 + R_2)} \\ &= \frac{1 + j\omega T_2}{1 + j\omega T_1} = \frac{T_2(1/T_2 + j\omega)}{T_1(1/T_1 + j\omega)} \end{aligned}$$

where  $T_2=CR_2$  and  $T_1=C(R_1+R_2)$ , or more generally:  $F(s)=K(s+1/T_2)/(s+1/T_1)$  where

the line makes with the horizontal axis, counting anticlockwise rotation as positive, indicating a leading response, clockwise a lagging response. The angle is measured with respect to the  $+\sigma$  axis if the zero is to the left of the  $j\omega$  axis, but with respect to the  $-\sigma$  axis if to the right of it.

In the case of Fig. 2a), however, the effect of the zero is not the whole story. To evaluate the frequency response (the magnitude of  $F(s)$  along the  $j\omega$  axis), you must take into account also the effect of the denominator of Eqn 2, representing the pole. So while initially, where  $v_{in}$  can be considered horizontal,  $v_o$  is simply directly proportional to the distance up the  $j\omega$  axis, remember that it is also inversely proportional to the distance from the pole.

At very high frequencies, these distances become more and more nearly equal. The response is thus proportional to the distance times the reciprocal of an equal distance, result unity. Likewise, the phase is everywhere equal to the sum of the angles. So for the CR highpass circuit, the phase is  $(90+\phi_{pole})^\circ$  where  $\phi_{pole}$  is zero at 0Hz, lagging by 45° at the -3dB point and reaching -90° at infinite frequency. Thus overall, the phase of  $v_o$  starts off at 90° leading at 0Hz, dropping back to being in phase at very high frequencies.

Section (d) of Fig. 2b is a three-dimensional representation of the magnitude of  $F(s)$ , plotted vertically above a horizontal  $s$  plane. Only that part of the surface to the left of the  $j\omega$  axis (where  $\sigma$  is negative) has been shown. The 'cut edge', above the positive  $j\omega$  axis, gives the magnitude of the frequency response, as a linear plot against frequency (also linear). The zero at the origin can be seen to act as a thumbtack, pinning the surface  $F(s)$  to the ground level at the origin.

If the pole is moved further and further to the left, the -3dB point, where the response is levelling out, will occur at a higher and higher frequency. If the pole moves out to infinity, the response will be rising at 6dB/octave indefinitely. With just a zero visible on the  $s$  plane, at the origin, you have a differentiator, e.g., an ideal op-amp with resistive feedback from the output to the inverting input, and with the input applied via a capacitor.

Zeros to the left of them

Zeros can occur anywhere in the  $s$  plane - not just on the  $j\omega$  axis. Figure 3a shows a circuit known as the transitional lag, which starts off behaving like the top cut circuit of Fig. 1a but, instead of the response falling indefinitely as the frequency increases, it flattens out again, the response at very high frequencies being equal to  $R_2/(R_1+R_2)$ . This is illustrated by the Bode diagram of Fig. 3d), from which you can see that the response starts to fall at a 'corner frequency', but stops falling at some higher corner frequency. The actual response is shown dotted, and a -6dB/octave asymptote is shown joining the low-frequency and high-frequency response levels - unity and  $R_2/(R_1+R_2)$  respectively.

The -6dB/octave asymptote is a straight line

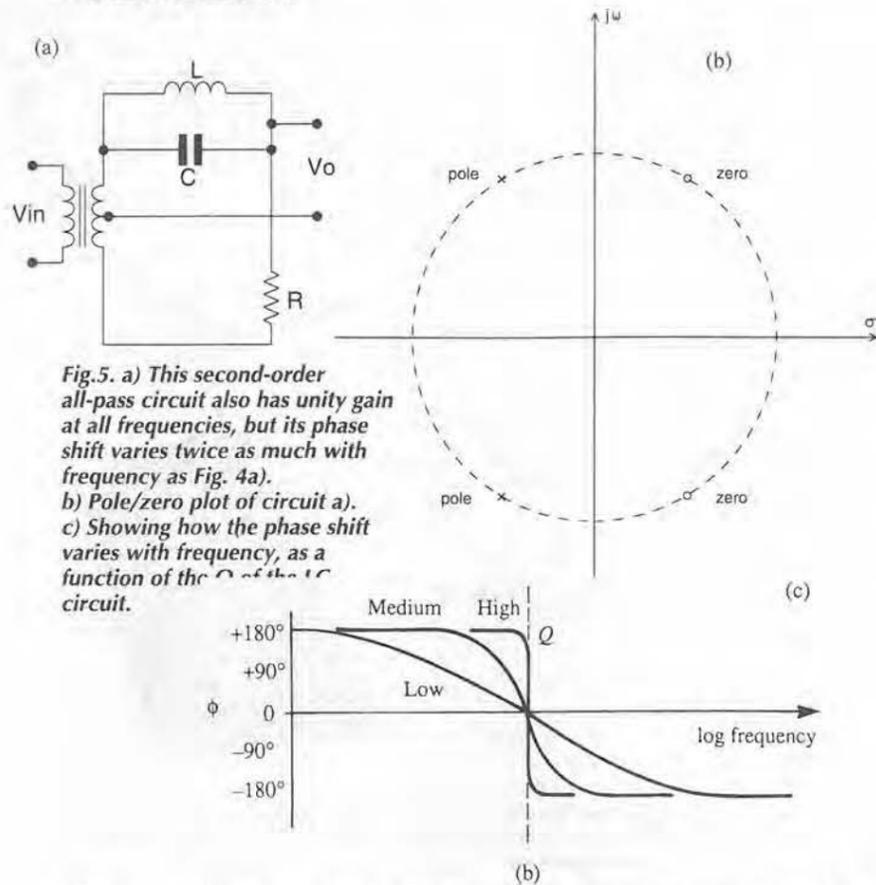


Fig. 5. a) This second-order all-pass circuit also has unity gain at all frequencies, but its phase shift varies twice as much with frequency as Fig. 4a). b) Pole/zero plot of circuit a). c) Showing how the phase shift varies with frequency, as a function of the Q of the LC circuit.

If, instead of being in series with  $R_2$ , the capacitor in Fig. 3a had been in parallel with  $R_1$ , the circuit would be a transitional lead, the response rising from  $K$  at 0Hz to unity at infinite frequency. In this case, the zero would be nearer the origin than the pole; the two have interchanged places. So as the frequency increases, starting from 0Hz, initially  $\phi_z$  increases faster than  $\phi_p$  and the phase of the output leads that of the input. Later,  $\phi_p$  increases faster, and the lead disappears, as the gain gradually reaches unity.

And zeros to the right of them

An all-pass filter is one which changes the phase of a signal by different amounts, depending on the frequency, but without affecting its amplitude. In signal transmission systems, this enables distortion due to various causes to be cancelled, and the signal restored more or less to its original condition.

The simplest all-pass circuit, also called a phase-equaliser, is the single-pole variety, Fig. 4a). The signal at the op-amp non-inverting terminal is applied through a CR low-pass circuit, exactly as considered earlier. Consequently, relative to the input  $v_i$  (vector e-a in circle diagram, Fig 4b)), the voltage at the op-amp non-inverting input is the vector e-c. This coincides with  $v_i$  at 0Hz, falling towards 0 with a 90° phase lag at very high frequencies.

Negative feedback around the op-amp forces its output to do whatever is necessary to keep the voltage at its inverting input equal to that at the non-inverting input. So point c on the circle diagram is also point b. Since the two resistors connected to the inverting input are

equal, the output  $v_o$  (vector e-d) follows the larger semicircle shown, as though drawn by a pantograph set for two times magnification.

Thus the amplitude of  $v_o$  is independent of frequency, but its phase relative to  $v_i$  swings round from 0° at 0Hz, to -180° at infinite frequency. The all-pass transfer function  $F(s)_{AP}$  is easily derived from that for the low-pass case, by observing that the output, in Fig 4b), is twice as big as the input, but shifted to the left by one unit - by the distance e-a. So  $F(s)_{AP} = 2F(s)_L - 1$ . But the  $F(s)$  for the low-pass circuit was shown earlier to be  $1/(s+1)$ .

$$F(s)_{AP} = \frac{2}{s+1} - 1 = \frac{2}{s+1} - \frac{s+1}{s+1} = \frac{1-s}{1+s}$$

There is a zero at  $\sigma=+1$ ,  $\omega=0$ , since for  $s=1+j0$ , the numerator of  $F(s)_{AP}$  is zero. This is shown on the s plane diagram of Fig. 4c). Following the rules noted earlier, the response at any frequency is directly proportional to  $l_2$  and inversely proportional to  $l_1$ . But since these are always equal, the magnitude of the response is always unity.

Also, as the frequency increases,  $\phi_p$  increases from zero to 90°, in an anticlockwise direction indicating a lagging phase angle. And  $\phi_z$  increases from 0° to 90° clockwise, this also according to the rule indicating a lagging response. Thus taking into account the phase contributions from both the pole and the zero, overall the phase drops steadily back from 0° at 0Hz to -180° at very high frequencies.

Figure 4d) shows a three dimensional wire grid model of the surface representing the magnitude of  $F(s)$ , or rather the log of the magnitude as previously. But this time the sur-

face along the + $\sigma$  axis is shown as well, since this shows up the zero. Note that the surface is exactly skew symmetrical about the  $j\omega$  axis, the magnitude of  $\log F(s)$  along the axis being everywhere zero, or 0dB.

Like all the circuits that have been considered so far, this all-pass filter is a 'first-order' circuit, that is to say that the highest power of  $s$  in the denominator is 1. If the highest power of  $s$  in the denominator is 2, then you have a second order circuit, and if the numerator is a constant, the circuit is lowpass with a 12dB per octave roll-off.

If there is just a term in  $s$  in the numerator, the circuit shows a bandpass response with a 6dB/octave roll-off either side of the peak, while a term in  $s^2$  in the numerator gives a highpass with a 12dB/octave low-frequency roll-off.

More zeros to the right of them

The first order all-pass filter described earlier causes the output phase to drop back from 0 to -180° in a fixed and fairly gentle manner, as the frequency rises from zero to infinity. If you want the phase change to take place over a smaller frequency interval, then a second order all-pass circuit can be used. This can be an entirely passive circuit, as in Fig. 5a), the corresponding pole/zero plot being as in 5b).

With this second-order all-pass circuit, the phase drops back from 0° at 0Hz, via -180° right round to -360° at infinite frequency.

If, at the resonant frequency of  $L$  and  $C$ , the reactance of each is large compared to  $R$ , then the phase change as the frequency changes will be very gradual. If on the other hand the reactance of each is small compared to  $R$ , then the phase will snap right around over a very small range of frequencies centred on the resonant frequency. This corresponds to the poles and zeros in Fig. 5b) being very close to the  $j\omega$  axis. In this case, over most of the frequency range, output voltage will be determined by the signal coming via the inductor (below the resonant frequency) or via the capacitor. Only at the resonant frequency, and in its immediate vicinity, where the dynamic impedance of the tuned circuit is high, will the output be due to the signal coming via  $R$ .

This all assumes, of course, that  $L$  and  $C$  are ideal. A more practical arrangement uses active circuitry, in particular, the state variable filter, see page 143 of Ref. 2. If you add the filter's low and high-pass outputs, plus an appropriate proportion of the bandpass output, you again get a second-order all-pass response. The transfer function is,

$F(s) = (s^2 - Ds + 1) / (s^2 + Ds + 1)$ , where  $D$  is the reciprocal of the filter Q. The  $s^2$  term in the numerator is the highpass component,  $s$  the bandpass component, while 1 represents the lowpass component. You can see that when  $s=0$  (so that  $\omega=0$ ), the transfer function is 1/1, or unity.

When  $s$  equals infinity, you can forget the other terms, so the transfer function is just  $\omega^2/\omega^2=1$  again. When  $s=(\sigma+j\omega)$ , with  $\sigma=0$  and  $\omega$ (the normalised frequency)=1, then  $s^2=-1$ , so the transfer function simply equals

$-Ds/+Ds$ . The numerator indicates a 90° phase lag, and the denominator another, giving a total of 180° lag at the filter's normalised resonant frequency.

The pole/zero diagram makes it clear that the closer the poles and zeros are to the  $j\omega$  axis (the higher the circuit's Q), the more more rapidly the phase changes as you pass between the upper pole/zero pair, travelling up the + $j\omega$  axis from 0Hz at the origin, towards infinite frequency.

The lower pole/zero pair has comparatively little effect on the phase in this region; it is there because both numerator and denominator are quadratic expressions, and their presence balances the upper pair, ensuring that the gain at 0Hz is unity and the phase shift 0°.

Lots of poles - and zeros

By now, I hope you have a feel for poles (s terms in the denominator of  $F(s)$ ) causing phase lags and gain changes, and zeros (s terms in the numerator) causing gain changes and phase lags or leads, according to where they are. So here without further ado or any detailed explanation, are some more pole zero plots, and three dimensional wire grid models of  $\log|F(s)|$ .

Figure 6a), sections i-iii shows the pole zero plots for some fourth-order lowpass filters. Those of i and ii are 'all pole' filters, i being a Butterworth maximally-flat amplitude response, and ii a Chebychev response which gives a faster initial roll-off in the stop band at the expense of ripples in the passband.

In iii is a fourth-order elliptic response, which gives an even sharper cut-off in the stop band. This is thanks to the finite zeros situated on the  $j\omega$  axis; but they do result in the stopband attenuation ultimately levelling out, rather than increasing for ever like the all pole filters. Figure 6b), sections i-iii shows the 3D wire grid representations of  $\log|F(s)|$  for these three filter types, in each case cut to show only the part over the - $\sigma$  region.

As before, the cut edge over the  $j\omega$  axis -

More on poles...

Figure 3 and 4, and parts of Figures 1,2,5, and 6 are reproduced from Analog Electronics by Ian Hickman, published by Butterworth-Heinemann, ISBN 07506 1634 2. Within the pages of this book will be found not only more on poles and zeros, but also a wealth of other information on all aspects of analog electronics, from d.c. to 1GHz. Everything analogue, in fact, except microwaves. This book is available £19.99.

Comprising 337 pages, this book is available by sending a postal order or cheque with a request for the book to Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. The fully-inclusive price is £23.50 UK, £26 Europe or £29 rest of world. Alternatively, fax your full credit card details and address on 0181 652 8956 or e-mail jackie.lowe@rbp.co.uk.

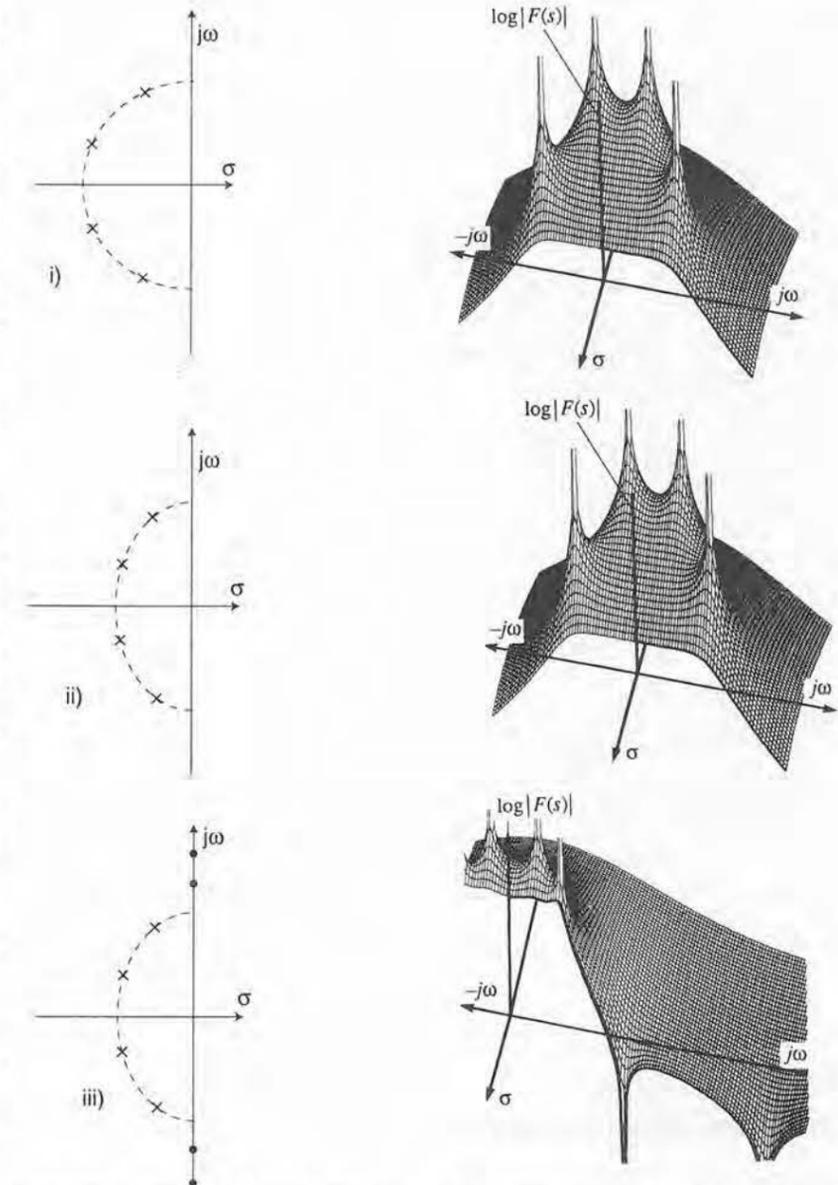


Fig. 6a) Pole/zero plots for three popular lowpass filter types; in each case, a four pole design is shown. i) The Butterworth design gives a maximally flat amplitude response. ii) The Chebychev design gives a faster cut-off in the stopband, at the expense of ripples in the passband response. iii) The elliptic or Cauer design gives an even faster stopband cut-off, but as well as passband ripples, has returns in the stopband b) Three dimensional wire grid representations of  $\log|F(s)|$  for the three filter types. The frequencies of infinite attenuation in the elliptic case correspond to the positions on the  $j$  axis of the zeros in a) iii).

Transforms ahoy

It may seem unnecessarily complicated to bother about the whole s plane, when all you need to find a circuit's frequency response if the value of  $F(s)$  for  $\sigma=0$ , i.e. how  $F(s)$  varies along the  $j\omega$  axis. But there is more to pole/zero diagrams than just a circuit's frequency response. The diagram can also represent an input signal to the circuit, and not just a steady-state sinewave either. A further mathematical trick - called the inverse Laplace transform - can then derive what the circuit's output waveform will look like, given its frequency response and the said non-sinusoidal input. But to cover that would take more space than is at my disposal. ■

References

- Hickman, I, 'In the picture', *Electronics World*, Jul/Aug 1996, pp 558-561.
- Hickman, I, *Analog Electronics*, ISBN 0 7506 1634 2, Butterworth-Heinemann 1993.

# TELFORD ELECTRONICS

<b>SIGNAL POWER/ANALYZERS</b>	<b>Marconi Type 6940 Power Meter + 8910 Power Sensor</b>	<b>Keithley Type 177 4.5 Digit 1 microV/mV milliohm/</b>	<b>Gold AF Signal Generator Type H12 15-50kHz</b>	<b>Digitizing 17.56k Rise Time, 10k System, Histogram, 408</b>	<b>7813 Delaying Time Base</b>
A & B Type AD3272 FT Analyzer + Results Printer	From £300	From £150	£65	£7000	£120
Ammon Dwyer Analyser	£150	£150	£400	£1850	£200
Anritsu Type MS420A Network/Spectrum Analyser	£4000	£150	£400	£1850	£125
8 & 4 Type 2033 High Resolution Signal Analyser	£2300	£150	£400	£1850	£140
Edget Type 2075 Noise Gate Analyser + Noise Generator	£1180 0.1-10kHz	£150	£400	£1850	£325
74186 0.1-10kHz	£2000	£150	£400	£1850	£100
Formal Type 2083 Audio Frequency Power Meter	£2000	£150	£400	£1850	£400
HP4355 Power Meter + Lead + HP4814 Power Sensor 1	£2000	£150	£400	£1850	£30
HP4355 Power Meter + Lead + HP4814 Power Sensor 2	£2000	£150	£400	£1850	£100
HP4355 Power Meter + Lead + HP4814 Power Sensor 3	£2000	£150	£400	£1850	£400
HP4355 Power Meter + Lead + HP4814 Power Sensor 4	£2000	£150	£400	£1850	£150
HP4355 Power Meter + Lead + HP4814 Power Sensor 5	£2000	£150	£400	£1850	£275
HP4355 Power Meter + Lead + HP4814 Power Sensor 6	£2000	£150	£400	£1850	£150
HP4355 Power Meter + Lead + HP4814 Power Sensor 7	£2000	£150	£400	£1850	£150
HP4355 Power Meter + Lead + HP4814 Power Sensor 8	£2000	£150	£400	£1850	£150
HP4355 Power Meter + Lead + HP4814 Power Sensor 100	£2000	£150	£400	£1850	£150

AN EXTENSIVE RANGE OF TEST EQUIPMENT IS AVAILABLE. PLEASE SEND FOR OUR NEW CATALOGUE - Postage and packing must be added. Please phone for price. VAT @ 17 1/2% to be added to all orders. Please send large SAE for details.  
**Telford Electronics, Old Officers Mess, Hoo Farm, Humbers Lane, Horton, Telford TF6 6DJ**  
**Tel: 01952 605451 Fax: 01952 677978**

CIRCLE NO. 114 ON REPLY CARD

<b>8 CAVANS WAY, BINLEY INDUSTRIAL ESTATE, COVENTRY CV3 2SF</b>	<b>TELNET</b>	<b>Hewlett Packard 1740A, 1741A, 1744A, -100MHz dual ch.</b>	<b>£350</b>
<b>Tel: 01203 650702</b>	<b>Hewlett Packard 8158B - Optical attenuator with opt 002 + 001</b>	<b>Hewlett Packard 8165A - 50MHz programmable signal source</b>	<b>£1850</b>
<b>Fax: 01203 650773</b>	<b>Hewlett Packard 8403A - Modulator</b>	<b>Hewlett Packard 8409B - Microwave broadband Amp (as new)</b>	<b>£4250</b>
<b>Mobile: 0860 400683</b>	<b>Hewlett Packard 8530B - Sweep oscillator mainframe (plug-ins avail)</b>	<b>Hewlett Packard 8530C - Sweep oscillator mainframe</b>	<b>£400</b>
<b>(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)</b>	<b>Hewlett Packard 8532A - Modulator</b>	<b>Hewlett Packard 8532B - Sweep oscillator mainframe</b>	<b>£400</b>
<b>MISCELLANEOUS</b>	<b>Hewlett Packard 8532C - Sweep oscillator mainframe</b>	<b>Hewlett Packard 8532D - Sweep oscillator mainframe</b>	<b>£400</b>
<b>Anritsu ME482B - DS-3 transmission analyser</b>	<b>Hewlett Packard 8532E - Sweep oscillator mainframe</b>	<b>Hewlett Packard 8532F - Sweep oscillator mainframe</b>	<b>£400</b>
<b>Anritsu MQ642A - Pulse pattern generator</b>	<b>Hewlett Packard 8532G - Sweep oscillator mainframe</b>	<b>Hewlett Packard 8532H - Sweep oscillator mainframe</b>	<b>£400</b>
<b>Barr &amp; Stroud - EFG variable filter (0.1Hz-100kHz)</b>	<b>Hewlett Packard 8532I - Sweep oscillator mainframe</b>	<b>Hewlett Packard 8532J - Sweep oscillator mainframe</b>	<b>£400</b>
<b>Datlab DL 1080 - Programmable Transient Recorder</b>	<b>Hewlett Packard 8532K - Sweep oscillator mainframe</b>	<b>Hewlett Packard 8532L - Sweep oscillator mainframe</b>	<b>£400</b>
<b>Datron 1081 - Precision multimeter</b>	<b>Hewlett Packard 8532M - Sweep oscillator mainframe</b>	<b>Hewlett Packard 8532N - Sweep oscillator mainframe</b>	<b>£400</b>
<b>Dynasort TP20 - Intellopace tape post tester, immac. cond.</b>	<b>Hewlett Packard 8532O - Sweep oscillator mainframe</b>	<b>Hewlett Packard 8532P - Sweep oscillator mainframe</b>	<b>£400</b>
<b>E.L.P. 331 - 18GHz frequency counter</b>	<b>Hewlett Packard 8532Q - Sweep oscillator mainframe</b>	<b>Hewlett Packard 8532R - Sweep oscillator mainframe</b>	<b>£400</b>
<b>E.L.P. 548A - frequency counter (26.5GHz)</b>	<b>Hewlett Packard 8532S - Sweep oscillator mainframe</b>	<b>Hewlett Packard 8532T - Sweep oscillator mainframe</b>	<b>£400</b>
<b>Farnell SE520 - Signal generator (10-520MHz)</b>	<b>Hewlett Packard 8532U - Sweep oscillator mainframe</b>	<b>Hewlett Packard 8532V - Sweep oscillator mainframe</b>	<b>£400</b>
<b>Farnell TSV70 Midl - Power Supply (70V-5A or 35V-10A)</b>	<b>Hewlett Packard 8532W - Sweep oscillator mainframe</b>	<b>Hewlett Packard 8532X - Sweep oscillator mainframe</b>	<b>£400</b>
<b>Fluke 5100A - Calibrator</b>	<b>Hewlett Packard 8532Y - Sweep oscillator mainframe</b>	<b>Hewlett Packard 8532Z - Sweep oscillator mainframe</b>	<b>£400</b>
<b>Fluke 5100B - Calibrator</b>	<b>Hewlett Packard 8533A - System voltmeter</b>	<b>Hewlett Packard 8533B - System voltmeter</b>	<b>£250</b>
<b>Fluke 5101B - Calibrator</b>	<b>Hewlett Packard 8533C - System voltmeter</b>	<b>Hewlett Packard 8533D - System voltmeter</b>	<b>£250</b>
<b>Fluke 5200A - A.C. calibrator</b>	<b>Hewlett Packard 8533E - System voltmeter</b>	<b>Hewlett Packard 8533F - System voltmeter</b>	<b>£250</b>
<b>Fluke 5205A - Precision power amplifier</b>	<b>Hewlett Packard 8533G - System voltmeter</b>	<b>Hewlett Packard 8533H - System voltmeter</b>	<b>£250</b>
<b>Fluke 7105A - Calibration system (As new)</b>	<b>Hewlett Packard 8533I - System voltmeter</b>	<b>Hewlett Packard 8533J - System voltmeter</b>	<b>£250</b>
<b>Heldren 1107 - 30V-10A Programmable power supply (IEEE)</b>	<b>Hewlett Packard 8533K - System voltmeter</b>	<b>Hewlett Packard 8533L - System voltmeter</b>	<b>£250</b>
<b>Hewlett Packard 338A - distortion measuring set</b>	<b>Hewlett Packard 8533M - System voltmeter</b>	<b>Hewlett Packard 8533N - System voltmeter</b>	<b>£250</b>
<b>Hewlett Packard 432A - Power Meter (with 478A Sensor)</b>	<b>Hewlett Packard 8533O - System voltmeter</b>	<b>Hewlett Packard 8533P - System voltmeter</b>	<b>£250</b>
<b>Hewlett Packard 435A or B - Power Meter (with 8481A/8484A)</b>	<b>Hewlett Packard 8533Q - System voltmeter</b>	<b>Hewlett Packard 8533R - System voltmeter</b>	<b>£250</b>
<b>Hewlett Packard 5328A - 100MHz universal frequency counter</b>	<b>Hewlett Packard 8533S - System voltmeter</b>	<b>Hewlett Packard 8533T - System voltmeter</b>	<b>£250</b>
<b>Hewlett Packard 5328B - 100MHz universal frequency counter</b>	<b>Hewlett Packard 8533U - System voltmeter</b>	<b>Hewlett Packard 8533V - System voltmeter</b>	<b>£250</b>
<b>Hewlett Packard 5328C - 21MHz synthesiser/function gen.</b>	<b>Hewlett Packard 8533W - System voltmeter</b>	<b>Hewlett Packard 8533X - System voltmeter</b>	<b>£250&lt;/</b>

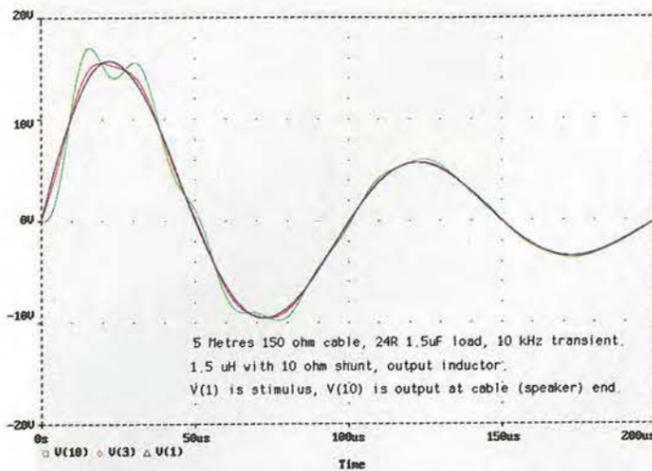


Fig. 1. Simulation of typical amplifier output stage when driving into a capacitive load with high-value shunt impedance, via a high impedance, typical figure-of-eight-style cable. This diagram was used for the first article.

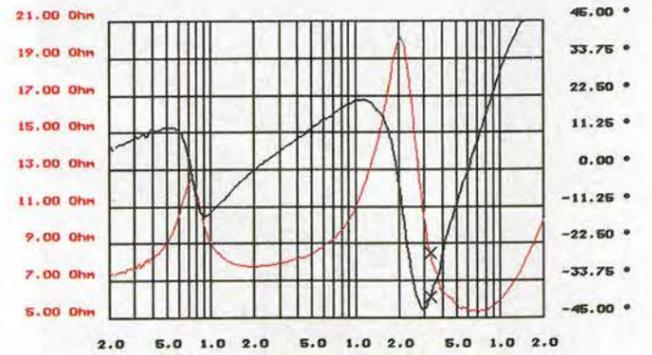


Fig. 3. Impedance and phase plot by frequency, of rebuilt two-way transmission line test speaker. Compare with published plot in reference 3.

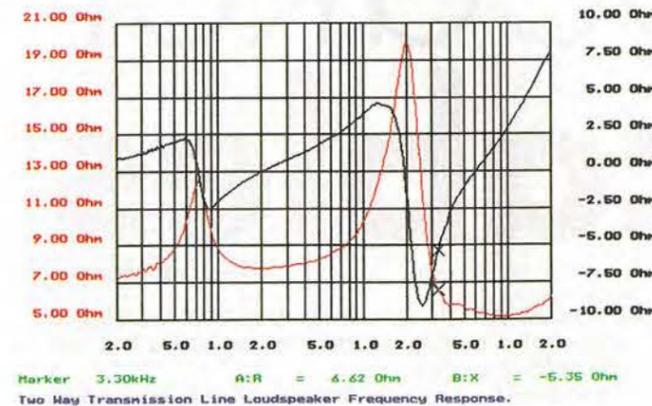


Fig. 5. The Fig. 3 plot again but this time displayed in 'R + jX' terms, clearly showing the inductive and capacitive parts of the frequency range, with negative X values being capacitive and positive X values representing inductive reactances.

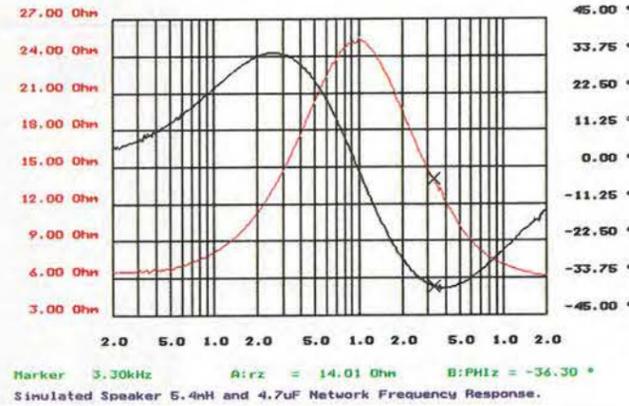


Fig. 2. Impedance and phase plot of the 'pseudo' IHF dummy reactive load, made using a 5.6Ω resistor in series with a parallel combination of 5.4mH, 4.7μF and an 18Ω damping resistor. This shows phase change with frequency for this high-impedance resonant circuit.

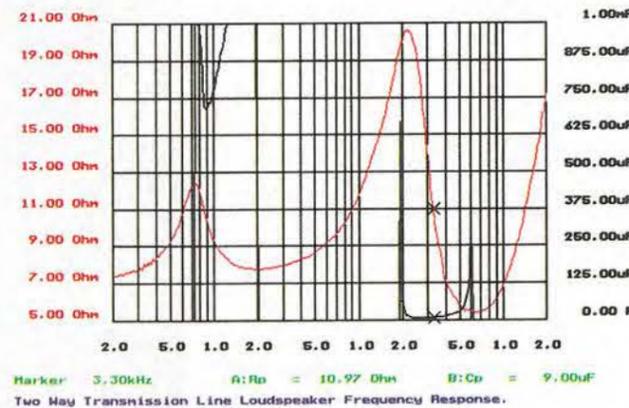


Fig. 4. Plot Fig. 3 displayed in terms of parallel resistance and equivalent parallel capacitance values. Note relatively large equivalent capacitances near bass resonance.

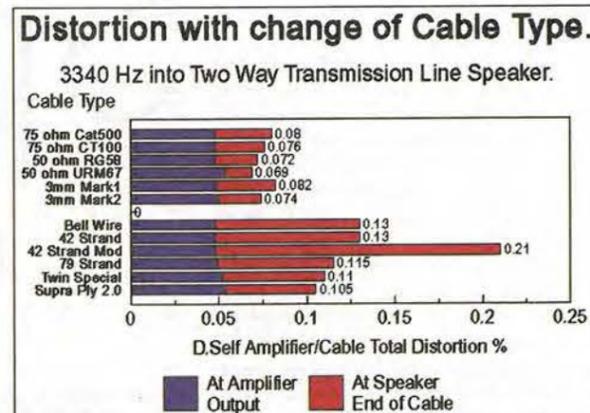


Fig. 6. This plot of harmonic distortion measured at the test speaker terminals, with the speaker acting as a capacitive load, shows clearly how distortion changes with cable. Great care was taken to maintain all other test conditions constant, as can be judged by the small changes in distortion measured at the amplifier terminals. This test was repeated on three separate days, all giving similar results, and only small levels of non-harmonic noise were noted.

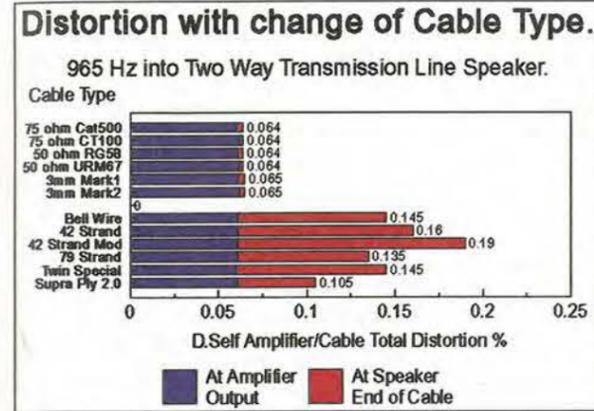


Fig. 7. Harmonic distortion measured at the test speaker terminals, with the speaker acting as an inductive load, shows smaller distortion changes with cable. During this test, non-harmonically related noise was observed for the figure-of-eight twin-line cables, clearly showing the coaxial cable's superior isolation from transmitted noise. This pick-up partly accounts for the poor performance of the Figure 8 cables with this inductive real speaker loading.

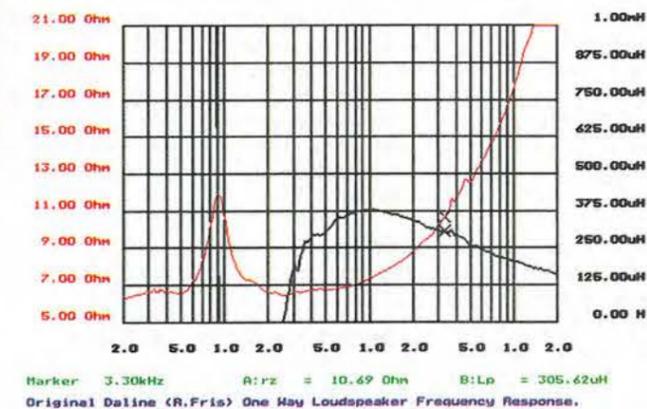


Fig. 8. Impedance and equivalent parallel inductance plot of the R. Fris original Daline cabinet, clearly showing high-frequency inductive behaviour. This cabinet was chosen since it has no crossover network.

way corner horns in my listening room.<sup>6</sup> None of these is in an infinite baffle cabinet.

How can I measure the impedances and reactances of these speakers? While impedance plots can be made using nothing more than a signal generator, a known resistor and a suitable voltmeter, phase measurement is much more difficult.

Many personal computers have a 16-bit sound card. With suitable software, such a card can provide the heart of an extremely low-cost audio frequency measurement system, capable of measuring impedance and phase angle. While not state-of-the-art, this method can produce useful measurements. Two low-cost software systems for use with these sound cards are readily available (see panel on sound cards and software).

To ensure a resonant peak at crossover, I rebuilt my two-way transmission line as an 8Ω system, with a crossover based on the old Kef DNI3 design<sup>4</sup>, built using polycarbonate and polypropylene capacitors and used with a small cone tweeter. Using the *Elektor* software with my sound card, the resulting impedance plot was similar to that published for the Tannoy D700 system<sup>3</sup>, Fig. 3.

This conventional impedance phase plot can also be viewed in terms of equivalent inductance, capacitance or as 'R+jX' - whichever is preferred. Viewed as the parallel resistance and equivalent parallel capacitance, you can see that frequencies near 3kHz could provide loading similar to the simulations used for Fig. 1, with consequent distortion, Figs 4, 5.

Having established that the conditions needed for transient distortions

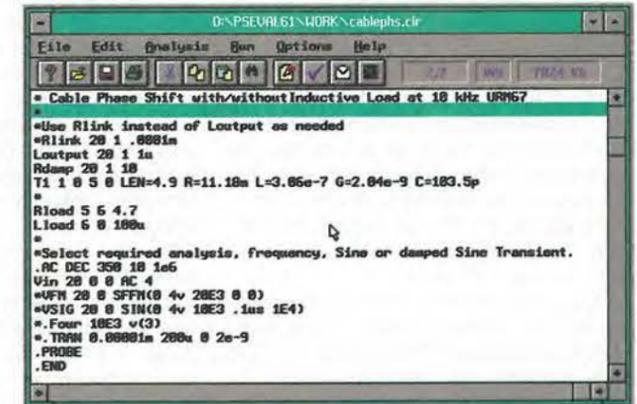


Fig. 9. PSpice net-list used to calculate the high frequency phase deviation results, with change of cable parameters, and various loading circuits, for Table 1. Note use of Spice 'SIN' waveform.

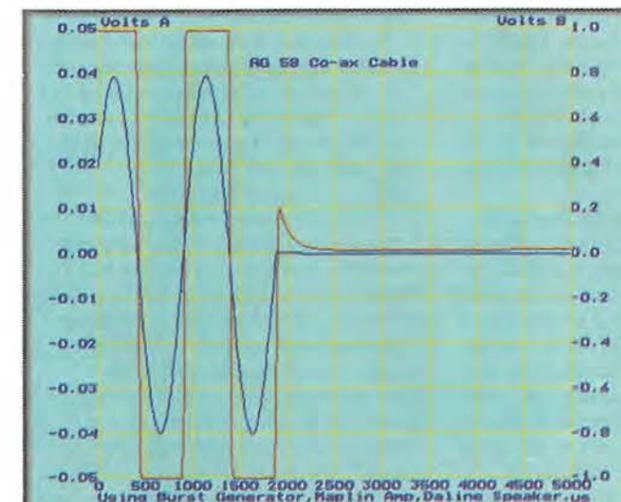


Fig. 10. Plot of loudspeaker damping, or lack of, using RG58 cable with the Daline speaker cabinet. This was made using a tone-burst generator and Maplin Amplifier set to 1.6V pk/pk output, with the Pico ADC100 virtual oscilloscope. Note the close similarity to the Duncan test plots.

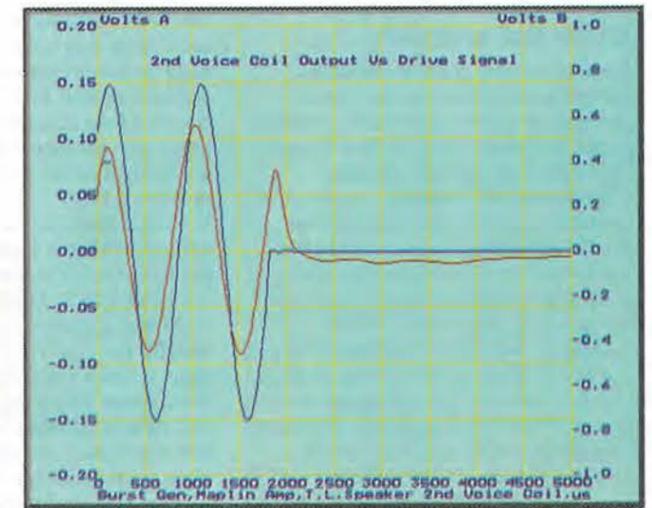


Fig. 11. Using the Fig. 10 set-up and RG58 cable to observe speaker cone overhang using the 'spare' voice coil of the transmission line speaker as a sensor. This clearly shows cone movement at reduced amplitude, continuing far longer than the initial overshoot spike.

**Table 1. Simulated phase shift in degrees at 10kHz for the various cables tested. Shows low/high frequency deviations by cable, with amplifier and various dummy speaker loads. Ranked for least overall change with above permutations.**

	No output inductor				With 1µH output inductor				Ranking
	Resistor only		Series 100µH		Resistor only		Series 100µH		
	4.7Ω	8.2Ω	+4.7Ω	+8.2Ω	4.7Ω	8.2Ω	+4.7Ω	+8.2Ω	
<b>Coaxial styles</b>									
75Ω Cat.500	-1.485	-0.859	+0.034	-0.211	-2.234	-1.293	-0.232	-0.480	5
75Ω CT100	-1.414	-0.815	-0.114	-0.284	-2.159	-1.245	-0.380	-0.553	6
50Ω RG58C/U	-1.219	-0.708	+0.386	+0.033	-1.961	-1.139	+0.118	-0.237	3
50Ω URM67	-1.149	-0.660	-0.249	-0.320	-1.903	-1.094	-0.515	-0.590	4
3mm Mark 1	-0.685	-0.394	-0.148	-0.074	-1.446	-0.831	-0.342	-0.421	1
3mm Mark 2	-0.697	-0.401	-0.083	-0.155	-1.454	-0.836	-0.351	-0.427	2
<b>Figure-of-8 styles</b>									
2192Y 'Bell' Wire	-2.684	-1.566	-0.094	-0.326	-3.399	-1.984	-0.105	-0.591	9
42-strand	-2.904	-1.685	-0.303	-0.626	-3.647	-2.117	-0.563	-0.891	11
42-strand modified	-4.629	-2.687	-0.932	-1.257	-5.369	-3.118	-1.184	-1.518	12
79-strand	-2.545	-1.466	-0.621	-0.752	-3.301	-1.902	-0.882	-1.019	10
2mm twin special	-1.939	-1.117	-0.394	-0.527	-2.695	-1.553	-0.657	-0.796	8
Supra Ply 2.0	-1.394	-0.803	-0.212	-0.338	-2.152	-1.239	-0.478	-0.608	7

can exist, might these conditions also cause distortion with continuous sine waves? This region should be explored by practical measurements.

**Conventional distortion tests**

My variable frequency generator produces 0.05% distortion, so it can only be used for comparative, rather than absolute, tests. For the purpose of comparing cables, however, it should suffice. My Hewlett Packard 331A distortion analyser cannot measure distortions much below this level.

Using this generator with a two-stage series/parallel LC clean-up filter, I measured 0.045% distortion at 3340Hz at the terminals of my Self amplifier,<sup>7</sup> loaded with 8.2Ω.

This amplifier, with the above instruments, was used with all twelve cables to test drive the rebuilt two-way transmission line speaker, making distortion measurements in sequence

**Other test methods**

Some of you may prefer to test cables using a low-cost tone burst test more in line with the Duncan test method. I include screen shots made using the Pico adapter with a low-cost, self-built generator.

Readers with a 50Ω output square wave generator and who wish to experiment using transient waveforms similar to that used in the Spice simulations can easily make a good 10kHz replica by loading the generator output with a parallel combination of 1mH with 0.22µF and 47Ω.

A variety of test signals can be found on the *Hi-Fi News and Record Review Test Disc III*. This includes a transient waveform very similar to the Spice exponentially damped sine wave, 'SIN', used for Fig. 1. However, the tone burst included on this disc equates to the IHF tone burst in having a change in level but no distinct off periods.

at both amplifier and loudspeaker terminals.

To help this rebuilt speaker survive prolonged testing, I used only half the drive voltage used by Duncan for his July/August article, i.e. 0.45V. Even at this reduced level, some ear protection is desirable.

Using a test frequency of 3340Hz, chosen to match my clean-up filter, notable changes in distortion at the loudspeaker terminals with change of cable were easily measured by my equipment, Fig. 6.

From the various simulations made investigating these cables, a similarly high but inductive impedance was expected to produce much less distortion. Change of test frequency to 965Hz, with appropriate changes to the clean-up filter, resulted in increased distortion at the amplifier terminals. However, as expected, incremental distortion was lower at the speaker end of the test cables, since the speaker was now behaving as an inductive load.

During this test, with the distortion residuals viewed by oscilloscope, non-harmonically related noise was observed for the figure-of-eight twin-line cables, providing a clear demonstration of the coaxial cable's superior isolation from transmitted noise. This pickup partly accounts for the performance of the figure-of-eight cables with this inductive speaker loading, Fig. 7.

At bass frequency, almost all loudspeaker designs exhibit a high-impedance resonant peak or peaks. It is reasonable to expect that similar distortion changes would also be measured with a change of cable. I have not tried this, for two reasons. Firstly, my test equipment is inadequate for measurements near 50Hz mains frequency. Secondly, the available speaker cabinets either have well damped low impedance resonance peaks or they peak close to the mains harmonic frequencies.

These 3340Hz distortions were much larger than expected, so I built a test circuit similar to the IHF (Institute of High Fidelity Inc, IHF publication A202) reactive load, using a 5.4mH inductor with a 4.7µF metallised poly-

carbonate capacitor to get a high impedance and similar phase to that of the speaker measured. With this test circuit, no realistic continuous sinewave incremental distortions were measured, Fig. 2.

A speaker is obviously a complex motor generator system giving results not easily represented by simple passive component models. Given time, perhaps this could be resolved – but not by me.

**Relative phase**

The final parameter influenced by cable

**Sound cards and software**

For these tests I used a Creative Labs *Soundblaster 16 Value Plug-and-Play* card with general purpose software (Elektor Electronics, part no. 966001-1). It is important to check that the dma channels and interrupts needed are not already in use in your system.

An alternative software for sound cards, targeted especially at speaker systems, is *AIRR* (Anechoic In-Room Response) by Dr J J Bunn, supplied by Old Colony Software. It is also available from Falcon Acoustics Ltd, Tabor House, Norwich Rd., Mulbarton, Norfolk NR14 8JT

Also available from Falcon and Old Colony is *Audiosuite* software, again for use with a sound card. It includes MLS functions but is much more expensive.

Those seriously interested in the design of loudspeakers rather than measurement might consider the Old Colony *IMP* (Impulse Measurement and Processing), which is a stand-alone system for a pc, available in kit form and reasonably priced. This also is available from Falcon.

Many other software and hardware systems are available, and the above list covers only some of those priced for the speaker amateur.

choice is change of high frequency phase relative to phase at lower frequencies. Every cable has a transit delay, influenced primarily by the cable's inductance and insulation material. This delay could change with frequency or test-circuit loading.

I am not well equipped to measure small phase angles but, knowing the cable's ac parameters, this could be simulated.

Most Spice-based simulators have transmission line models available but, to minimise transient simulation times, their default settings use a minimum of only two sampling points along the cable. This produces poor results with short cable lengths at audio frequencies. Also, the supplied small signal transmission line model is much simplified.

By overriding these defaults and forcing a slower simulation, acceptable results are obtainable. Many loudspeaker impedance plots show an inductively rising impedance above 10kHz. Thus, each of the twelve cables tested has been simulated using both 4.7Ω and 8.2Ω resistive loads and a series combination of these resistances with 100µH, Fig. 8.

Most – but not all – domestic amplifiers are

protected against reactive loads by a low-value inductor in series with their output. To cover all reasonable options, the above load combinations were simulated with and without a series inductance of 1µH and 10Ω damping resistor, Fig. 9.

These simulations were all made at 10kHz since, with these values, it represents a worst-case frequency. Regardless of the cable, only small changes in relative phase could be observed, Table 1.

**In summary**

The intention of these experiments was to quantify the effects of cable characteristics on amplifier speaker systems, rather than to choose a 'best buy'. This determined the cables chosen for test.

My use of coaxial cables as speaker cables is not new. Indeed, extremely low-impedance specialist *Mogami* speaker coaxial cable was reviewed by Nelson Pass<sup>8</sup> in his 1980 article.

However, these experiments would be incomplete without forming at least a ranking of cable performance. This ranking was unweighted, taken from simple addition of place

numbers for each test. Although various test weightings could be used, regardless of this, the first four placings are unlikely to change, Table 2.

These rankings were supported by listening tests. However, for the reasons outlined in my first article, listening tests were performed only as the concluding test, long after completion of all published tables or figures, and with this text at the final editing stage.


Regardless of these results, users of Naim and similar amplifiers not having an output inductor must use the maker's recommended cable and cable length, since the cable functions to replace the output inductor in protecting their amplifiers.

For all conventional inductor output amplifiers, the ideal speaker cable would have zero resistance, zero inductance and zero impedance. In other words, zero length – no cable at all<sup>8</sup>, since all cable degradations increase with cable length.

It is obvious from the results presented that a cable should have the lowest possible dc resistance, low characteristic impedance at audio frequencies, and minimal inductance.

**Table 2. Summary of cable rankings by each test performed. Final ranking derived using equal weighting for all tests. All cables 4.98m long.**

	Circuit A	Circuit B	Z <sub>0</sub>	Inductance	DCΩ	Loss	Phase change	THD	Overall
<b>Coaxial styles</b>									
75Ω Cat.500	8	8	9	7	8	7	5	5	8
75Ω CT100	7	=6	8	6	7	6	6	=2	=5
50Ω RG58C/U	10	10	6	4	11	2	3	=2	=5
50Ω URM67	3	3	4	3	1	1	4	1	3
3mm Mark 1	2	2	1	2	3	=3	1	5	2
3mm Mark 2	1	1	2	1	2	=3	2	=2	1
<b>Figure-of-8 styles</b>									
2192Y 'Bell' Wire	12	12	10	10	12	11	9	10	11
42-strand	9	9	11	11	=9	9	11	11	10
42-strand modified	11	11	12	12	=9	12	12	12	12
79-strand	6	=6	7	9	4	10	10	8	9
2mm twin special	5	5	5	8	6	8	8	9	7
Supra Ply 2.0	4	4	3	5	5	5	7	7	4

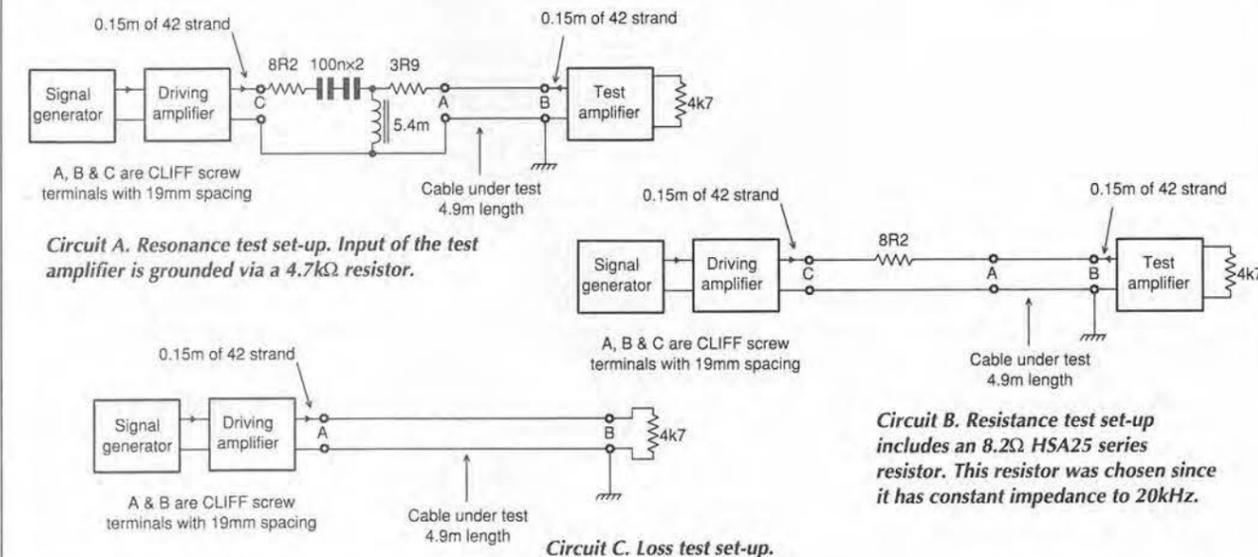

## Voice-coil driver effects

Using my tone-burst generator with a Maplin amplifier and an oscilloscope, I tested my available speaker drivers, some of which were 15Ω, and a mixture of long- and short-travel cones.

In general, smaller, lighter cones produced less cable overhang voltage. Size for size, short-travel cones produced less than long-travel cones. Similarly, 15Ω drivers produced less overhang voltage than 8Ω drivers, which produced less than 4Ω drivers, **Fig. 10**.

I was able to compare voice coil impedances quite easily. The bass driver in my two-way transmission line system is an ancient Whitley Stentorian HF1016. This has duplicated voice coils, and is designed to easily configure and be used as 4, 8 or 15Ω impedances.

Configured as 8Ω I can use the spare voice coil as a cone-travel sensor, giving most interesting results when viewed on an oscilloscope, **Fig. 11**.

Is it possible that cables are now considered so important due to the change to lower impedance, long-travel speaker drivers over the years?

These characteristics are almost impossible to achieve using twin-line or figure-of-eight constructions without incurring considerable cable self-capacitance. They are much more readily achieved using the coaxial construction and with acceptable capacitance.

Other frequently discussed parameters, such as sections of individual wire strands and cable insulation material, may well have some relevance, but these tests indicate that they are of secondary importance.

One obvious disadvantage of coaxial speaker cables having dense outer braids is cable end preparation and termination. It is important to avoid damaging any braid wire strands when stripping back, since this would substantially increase distortion levels. However, a dense braid is extremely effective in reducing cable pickup into the amplifier's feedback loop.

As to the test results table, with one exception, the cables segregated automatically into distinct performance groups – coaxial and non-coaxial. Five of the six coaxial cables were outstanding compared to all but one of the non-coaxial constructions tested – including the hand-made, 2mm twin-line special, **Table 2**. Of the non-coaxial styles, the Jenving *Supra Ply 2.0* was the exception, performing well and coming fourth overall,<sup>9</sup> **Table 2**.

By far the best cable of those tested is the custom made Mark II, followed closely by the Mark I. Neither of these is commercially available in cut lengths but they could be specially ordered in bulk, or further copies could be hand-made, as were my originals.

Both the Mark 1 and the Mark 2 are flexible, very low resistance and – being less than

## Cables sources

Initially, I decided that all test cables should be obtainable either from: Electrovalue or Maplin. I bought URM67, CT100, 42-strand, 79-strand, and 300Ω feeder from Maplin, while the RG58 was purchased from Electrovalue. *Supra Ply 2.0* came from Future Film Developments<sup>10</sup> however, and the Bell Wire and Cat 500 from local suppliers.

6mm in diameter – easily installed. Mark 2 has 19 strands of 0.45mm inner wire insulated with polythene with an outside diameter of 3mm. Its outer braid is 240 strands of 0.127mm diameter. Heat shrink sleeve provided overall insulation.

Mk I is identical, except for its 37 strands of 0.32mm inner core. Designers interested in the materials used should send an sae to me via *Electronics World's* editorial offices.

When these tests commenced, I decided to use only cables easily purchased in cut lengths so that my results could be easily replicated. However, in order to understand some early results, I needed to measure a cable having lower impedance at audio frequencies than URM67, but I was unable to buy it. I certainly didn't expect that my crude hand-made cables would perform as they did (see panel on sources of cables used for test).

Of those cables commercially available in cut lengths, the URM67 performs extremely well, coming a close third overall. It is obviously by far the best commercial cable of those tested. However, being 10.3mm in diameter with a solid polythene core and a very dense braid, it is inflexible. It could almost be used as a car tow rope.

A not-so-close fourth, the Jenving *Supra Ply 2.0*, is a specialised, relatively low-cost, high-capacitance cable, available from Jenving's UK agent<sup>10</sup> only in multiples of 10m. In direct contrast with URM67, it is much smaller and, being extremely flexible, drapes well. It is easily installed and hidden from sight.

Following closely on the *Supra Ply's* heels is a tie for fifth place between the 75Ω satellite tv cable CT100 and the 50Ω instrument cable RG58, both ranking equally well overall. However, depending on your needs, you may prefer to down-rank RG58 due to its poorer performance in the resonance and resistive circuit tests and for its high dc resistance.

CT100 and Cat 500 cables are both of larger diameter than RG58. They have a secondary inner copper-foil shield which could fatigue and crack with repetitive coiling and uncoiling, so they should only be used for permanent installations.

Once more, I ask that anyone wishing to shoot these findings down in flames should first repeat the experiments.

## Cobbler's shoes

After all these time-consuming experiments, you may wonder which brand of expensive speaker cable I use. My listening room has the 'golden' dimensions of 6.7 by 4.6 by 2.9m, and needs cables somewhat longer than those tested.

My relatively low-cost system, based on Acoustic Research electronics with corner horn speakers<sup>6</sup> crossing over at 250Hz, was cabled almost 30 years ago using the old-style 7 by 0.029in twin and earth ring mains cable buried in the plaster. I used this for no better reason than that I had plenty left over. I guess its only other merit is a cross-sectional area of more than 3mm, giving reasonably low resistance at the lengths needed. Since my corner horns are 15Ω impedance, it seemed acceptable.

## Will I change this cable?

During these experiments I too, like Saul travelling to Damascus, have revised some views and intend to further develop Mark 2 for my own use. This design is now covered by Pat. No 9624876. ■

## References

- Bateman, C., Speaker Cables, *Electronics World*, December 1996.
- Bateman, C., Measuring Speaker Cables, *Electronics World*, January 1997
- Collóms, M., A Big-Hearted Monitor, *Hi-Fi News*, July 1993
- Stamler, P., How to improve that small cheap speaker, *Speaker Builder*, 1/80 pp18-26
- Fris, R., The Daline, *Hi-Fi News*, November 1974
- Greenbank, J., Horn Loudspeaker Mk.2, *Wireless World*, January 1972, pp14/15
- Self, D., 50-Watt Class 'B' Amplifier, *Electronics World*, February 1994
- Pass, N., Speaker Cables – Science or Snake Oil?, *Speaker Builder*, 2/80
- Jenving Technology AB, Backamo 12800, S-459 91, Ljungskile, Sweden
- Future Film Developments, 64 Oxford Road, New Denham, Uxbridge UB9 4DN

## Music used for listening tests

Test Disc 3, *Hi Fi News & Record Review*, HFN020.  
*Pictures at an Exhibition*, Mussorgsky, Decca 417 299-2.  
*In The Region of The Summer Stars*, The Enid, MNTLCD7.

## 'OFF-AIR' FREQUENCY STANDARD

CIRCLE NO. 116



- Provides 10MHz, 5MHz & 1MHz
- Use it for calibrating equipment that relies on quartz crystals, TCXOs, VXCOS, oven crystals
- Phase locks to DROITWICH (rubidium controlled and traceable to NPL)
- For ADDED VALUE also phase locks to ALLOUIS (cesium controlled and traceable to OP – French eq to NPL)
- British designed and British manufactured
- Options available include enhanced receiver, sine wave outputs and 13MHz output for GSM. Prices on application.

Output frequencies – 10MHz, 5MHz, 1MHz  
 Short term stability – better than 1x10<sup>-8</sup> (1 sec)  
 Typical – 4x10<sup>-9</sup> (1 sec)  
 Long term – tends to 2x10<sup>-12</sup> (1000 sec)  
 Call for Off-Air Standard list

## TEST EQUIPMENT CIRCLE NO. 117

We are well known for our quality, new and used Test Equipment. Our list is extensive, ranging through most disciplines. Call for details and a complete list

Marconi Spectrum Analyser TF2370.....	£895	Marconi LCR Bridge TF2700.....	£149
Bradley Oscilloscope Calibrator 156.....	£395	Marconi LCR Bridge TF1313A.....	£125
Bird Termaline, 2.5kW 50Ω.....	£295	Mahogany Cased 5kV Megger (Collectors).....	£POA
Philips Function Generator PMS134.....	£995	Taylor Valve Tester 474.....	£59
Hitachi Oscilloscope V222, 20MHz.....	£249	Philips RF Generator PM5326.....	£395
Rapid Oscilloscope 7020, 20MHz.....	£249	HP Frequency Counter HP5340.....	£595
Philips Pulse Generator PM5716.....	£495	Taylor AM/FM Generator 62A.....	£69
Amprobe AC Recorder LAV3X.....	£75	Marconi Attenuator TF2163.....	£195
Amprobe Temperature Recorder LT8100.....	£75	RE Mega-Ohmmeter/pica-ammeter IM6.....	£295
Emerson UPS 1.5kW.....	£599	Ferroglyph Recorder test Set RTS2.....	£95
		HP Vector Voltmeter HP8405A.....	£249

**HALCYON ELECTRONICS**  
 423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR  
 SHOP HOURS 9-5:30 MON-SAT. TEL 0181-542 6383. FAX 0181-542 0340

## Field Electric Ltd.

Tel: 01438-353781 Fax: 01438 359397

Mobile: 0836-640328

Unit 2, Marymead Workshops, Willows Link, Stevenage, Herts. SG2 8AB.

Sony 9" Super Fine Pitch Trinitron RGB VDU	£35 c/p	12.50
AT Keyboards for IBM Compatibles		£5.99
12" Colour SVGA 800 x 600 NEC	£45.95 c/p	14
Marconi Inst = Data Comms Tester		£385
Marconi Inst = Digital Line Monitor		£350
Marconi Inst = Digital Analyser		£375
Farnell PSU 0-70V 0-5A/0-30V 0-10A		£245
Siemens Data Line Analyser K1190 with manual		£300
Black Star Multimeter 3225		£55
Tektronix DAS9100 Digital Analysis System		£175
Tektronix 7A18 D.T. Amp		£75
Tektronix 7B53A D.T. Base		£75
Tektronix 7A15A Amp		£150
Tektronix 7511 Diff = Comp =		£100
12 VAC 200 Watt Transformer		£15
27 VAC 30A Transformer New		£15
Tseng Labs 1Mb 16 bit ISA SVGA Card	£16.75 c/p	4.00
Tseng Labs Dual Port SVGA ISA 16 Bit Card to run 2 Monitors from 1PC		£39
Compaq Docking Station for Laptop & Notebooks		£24.95
Philips PM 3233 10 Mhz D/Trace Scope		£65
Leader LMV 181A AC Millivoltmeter		£145
Racal Inst. 9915 UHF Freq: Meter 500MHz		£100
Racal Inst. 9916 UHF Freq: Counter 500MHz		£145
HP Laserjet 11D Printer		£180
HP 7475 8 Pen Plotter RS232		£65
HP Colour Pro 8 Pen Plotter RS232		£75
HP 7470A Plotter RS232		£95
Roland DG XY DXY 980A 8 Pen Plotter. Needs PSU		£60
Roland DG XY DXY 880A 8 Pen Plotter. Needs PSU		£60
Roland DXY 1300 8 Pen Plotter		£135
14" VGA Colour Monitors. Various makes from		£60
PLOTTERS • COMPUTERS • COMMUNICATIONS • PSU • VDU's • VIDEO • FANS • TEST • CABLE • NETWORK • PRINTERS • DISK DRIVES ALWAYS IN STOCK. OVERSEAS ENQ. WELCOME. TELEPHONE ORDERS ACCEPTED. C/P DETAILS PLEASE RING. ALL PRICES PLUS 17.5% VAT.		

CIRCLE NO. 118 ON REPLY CARD

## LOW COST DEVELOPMENT SYSTEM

ECAL comprises a versatile relocatable assembler with integral editor which runs about ten times faster than typical assemblers. Support includes 4, 8, 16 & 32 bit processor families including 75X, 6502, 6809, 68HC05/11, 8031/51, H8-300, 78K, PICs, ST6 & Z80/180, 68000, 80C196, H8-500 & Z280.

ECAL is either available for a single processor family or all families.

Single processor version £295  
 Multiprocessor version.... £395

Overseas distributors required

**OEMA Ltd.,**  
 7 & 7A Brook Lane,  
 Warsash,  
 Southampton SO31 9FH  
 Tel: 01489 571300  
 Fax: 01489 885853



Free demo disc!

The PC based ECAL hardware emulator is fully integrated with the assembler. Connection is made to the target through the eeprom socket so a single pod can support all processors. Facilities include windows for the inspection or change of registers or memory. You can even watch your program executing at source level!

Download time is about two seconds!

Pods can be daisy-chained for 16/32 bit systems.

Applications include software development, hardware debug, test and, finally, teaching about micro-controllers in education.

ECAL emulator ..... £475

Quantity discounts of up to 50% make ECAL software ideal for education.

One c-mos gate pack can form the heart of a frequency meter, a step-down switching regulator or a negative-supply generator, explains Rae Perälä.

# Gates open up

There are many applications for the 4011 c-mos two-input-nand gate – other than just gating. This article presents three such circuits, namely a step-down regulator, a negative-voltage switching regulator, and a frequency measuring circuit.

## Step-down regulator

Operating principle of a typical step-down regulator is shown in Fig. 1. Semiconductor switch  $S_1$  is usually controlled by a pulse width modulator, or pwm.

While the switch is on, current flows through inductor  $L$  to the output. Simultaneously, magnetic energy in the inductor increases. Diode  $D$  stays in its reverse state. When the switch turns off, the inductor discharges its magnetic energy giving a current to the output. Diode  $D$  now becomes forward biased, providing path for current flow.

The on-to-off time ratio of the switch is controlled by the pwm circuit. This circuit compares output voltage,  $V_{out}$ , to reference voltage  $V_{ref}$  and changes the on-to-off ratio accordingly.

Figure 2 is a practical step-down circuit using 4011. It makes a new regulated output voltage  $V_{out}$  from a regulated +8 to +15V input voltage. Gates A and B work as an oscillator giving an asymmetrical 40kHz square

wave, Fig. 3. Gate C controls the switching transistor, which is a BS250 p-type enhancement mode mosfet. This same gate inverts the oscillator output voltage, presenting the transistor control voltage  $V_{GS}$  as in Fig. 3. The control voltage has long negative pulses interspersed with short intervals. The transistor conducts during the negative pulses.

Gate D regulates the output voltage. Its output is high when  $V_{out}$  is beneath the adjusted value. The high state activates gate C, which can now control the switching transistor. When the adjusted output voltage is reached, gate D output goes low, stopping gate C, which remains in the high state. The switching transistor has no control voltage and remains off.

The regulating circuit operates using the 'missing pulse' principle. It provides pulses when the output voltage is low and ceases pulsing when the output voltage is sufficiently high.

Output voltage is adjusted via the 470kΩ potentiometer. Usable output voltage range of the circuit is 0.5 to 0.9 of  $V_{in}$ . The circuit can be loaded to 100mA.

## Negative voltage regulator

A negative voltage switching regulator is presented in Fig. 4. Gates A and B form an oscil-

lator, giving a symmetrical square wave voltage. Gate C controls the BS250 switching transistor.

During the transistor on time, current flows through the inductor, charging the magnetic energy within it. The magnetic energy discharges while the transistor is off through the diode, producing a negative voltage at the output.

Gate C regulates the output voltage. When the output voltage is too low, the regulating input voltage of gate C is high and the oscillator voltage controls the gate C output and therefore the transistor.

When the output voltage reaches the desired negative value, the regulating input goes low and it stops the output of gate C leaving it in its high state. The transistor stays off until the output voltage goes below its adjusted value.

This circuit requires an input voltage of +8V to +15V, which can be unregulated. A regulated +5V input acts as a reference voltage.

## Frequency measurement on a dvm

A digital voltmeter can be used for frequency measurements to 1MHz using the circuit in Fig. 5. The frequency to be measured connects to the input of gate A. This input is biased with 330kΩ resistors to half the supply voltage. This allows low input voltages to change the output of gate A. Figure 6 shows the gate voltages. Output voltage of gate A changes each time the input voltage passes the half supply voltage threshold.

Gate A controls gates B and C. Gate B has a delay capacitor in its output. Figure 6 shows

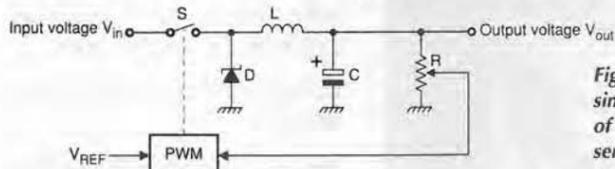


Fig. 1. Switching converter simplified. On and off times of switch  $S$ , invariably a semiconductor switch, are controlled by a pulse-width modulator.

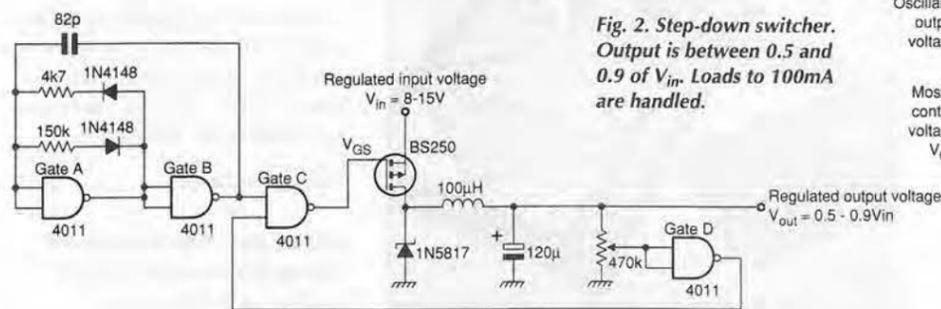


Fig. 2. Step-down switcher. Output is between 0.5 and 0.9 of  $V_{in}$ . Loads to 100mA are handled.

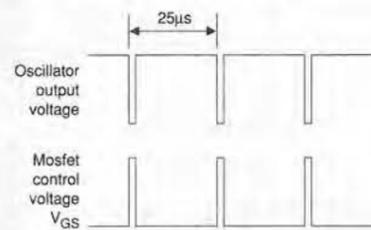


Fig. 3. Asymmetrical oscillator gates A and B of Fig. 2 runs at about 40kHz.

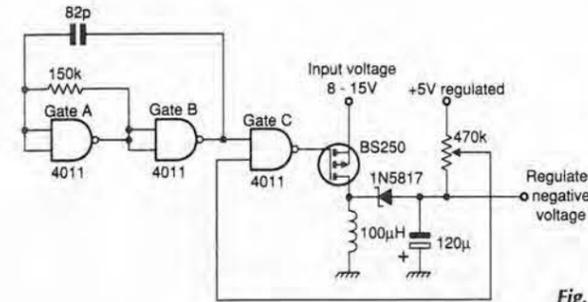


Fig. 4. Negative supply from a positive input. Again, gates A and B are an asymmetrical oscillator. Gate C determines whether drive pulses pass to the switching transistor.

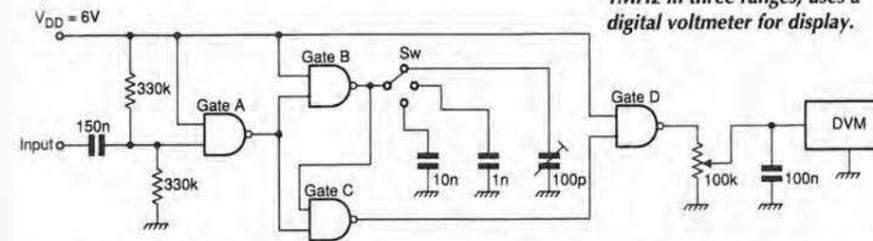


Fig. 5. Direct reading frequency meter, capable of measuring to 1MHz in three ranges, uses a digital voltmeter for display.

the gate B output voltage, which is reversed and delayed relative to gate A's output. One input of gate C is fed with the output voltage of gate A and in the other input the delayed voltage from gate B. Output of gate C comprises a negative pulse with a duration equal to the time it takes for gate B to fall from

its high state to its low state. Pulses from gate B are then inverted in gate D. These pulses are always similar in shape, independent of the amplitude and shape of the original input voltage.

The mean value of gate D's output voltage can then be measured by a digital voltmeter

with its 200mV or 2V dc voltage range selected. The meter reading can be adjusted by the 100kΩ potentiometer so that the voltage reading directly represents the unknown capacitance.

Capacitance measuring ranges are selected by the switch, which connects a suitable capacitor to gate B's output. The 100pF capacitor should be a trimmer so that gate C's input capacitance can be compensated for. ■

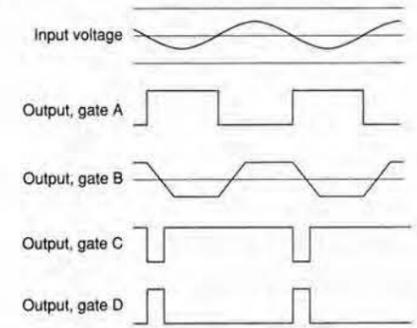


Fig. 6. Frequency meter waveforms. Top is the ac input, which is biased toward the switching point of the logic gate. In this way, the gate switches at a significantly lower input voltage than would otherwise be needed.

# Transform your PC

into a digital oscilloscope, spectrum analyser, frequency meter, voltmeter, data logger... for as little as £49.00

Pico Technology specialises only in the development of PC based data acquisition instrumentation. Call for your guide on 'Virtual Instrumentation'.

The ADC-10 supplied with PicoScope gives your computer a single channel of analog input. ADC-10 £49 with PicoLog £59

## Virtual Instrumentation

Pico's PC based oscilloscopes simply plug into the parallel port turning your PC into a fully featured oscilloscope, spectrum analyser and meter. Windows and DOS software supplied.

ADC-100 Dual Channel 12 bit resolution

The ADC-100 offers both a high sampling rate 100kHz and a high resolution. Flexible input ranges ( $\pm 50mV$  to  $\pm 20V$ ) make the unit ideal for audio, automotive and education use.

ADC-100 £199 ADC-100 with PicoLog £219

ADC-200 Digital Storage Oscilloscope

- 50 MSPS Dual Channel Digital Storage Scope
- 25 MHz Spectrum Analyser
- Windows or DOS environment
- $\pm 50mV$  to  $\pm 20V$
- Multimeter
- 20 MSPS also available

ADC 200-20 £359.00

ADC 200-50 £499.00

Both units are supplied with cables, power supply & manuals.

Pico Technology Ltd. Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ UK

Tel: +44 (0)1954 211716 Fax: +44 (0)1954 211880 E-mail: post@picotech.co.uk Web: http://www.picotech.co.uk/

Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT

## Data Logging

Pico's range of PC based data logging products enable you to easily measure, display and record temperature, pressure and voltage signals.

TC-08 Thermocouple to PC Converter

- Supplied with PicoLog software for advanced temperature processing, min/max detection and alarm.
- 8 Thermocouple inputs
- No power supply required.

TC-08 £199

TC-08 £224 with cal. Cert.

complete with serial cable & adaptor. Thermocouple probes available.

Call for free demo disk and product range catalogue


Post & Packing UK £3.50, Export customers add £9 for carriage & insurance.



Pico Technology Limited
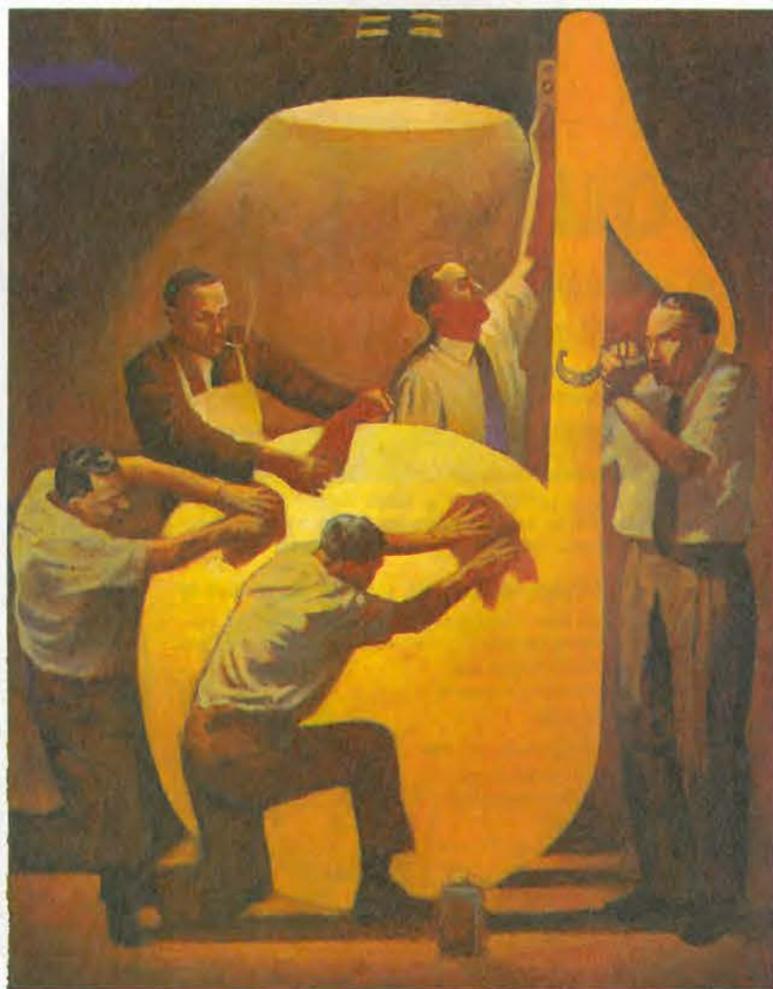
# OVERLOAD matters

**Doug Self** takes a look at the complex subject of preamplifier overload, and how to handle it.



There was no room in my Preamp '96 article for a proper discussion of the overload behaviour of RIAA preamp stages.<sup>1</sup> Like noise performance, the issue is considerably complicated by both cartridge characteristics and the RIAA equalisation.

There are some inflexible limits to the signal level possible on vinyl disc, and they impose maxima on the signal that a cartridge can reproduce. The absolute

value of these limits may not be precisely defined, but they set the way in which maximum levels vary with frequency, and this is perhaps of even greater importance.

Figure 1a shows the physical groove amplitudes that can be put onto a disc. From subsonic up to about 1kHz, groove amplitude is the constraint. If the sideways excursion is too great, the spacing will need to be increased to prevent one groove breaking into another, and playing time will be reduced. From about 1kHz to ultrasonic, the limit is groove velocity rather than amplitude. If the cutter head tries to move sideways too quickly compared with its forward motion, the back facets of the cutter destroy the groove that has just been cut by the forward edges.

At replay time, there is a third restriction – that of stylus acceleration or, to put it another way, groove curvature. This sets a limit on how well a stylus of a given size can track the groove. Allowing for this at cutting time puts an extra limit on signal level, shown by the dotted line in Fig. 1a.

The severity of this restriction depends on the stylus shape. An old-fashioned spherical type with a tip diameter of 0.0007in requires a roll-off of maximum levels from 2kHz, while a relatively modern elliptical type with 0.0002in effective diameter postpones the problem to about 8kHz.<sup>2</sup>

Thus there are at least three limits on the signal level. The distribution of amplitude with frequency for the original signal is unlikely to mimic this, because there is almost always more energy at lf than hf. Therefore the hf can be boosted to overcome surface noise without overload problems, and this is done by applying the inverse of the familiar RIAA replay equalisation.

Moving-magnet and moving-coil cartridges both operate by the relative motion of conductors and magnetic field, so the voltage produced is proportional to rate of change of flux. The cartridge is sensitive to velocity rather than to amplitude (and so sensitivity is always expressed in millivolts per cm/s) and this gives a frequency response rising steadily at 6dB/octave across the whole audio band. Therefore, a maximal signal from disc (Fig. 1a) would give a cartridge output like Fig. 1b – i.e., 1a tilted upwards.

Figure 1c shows the RIAA replay equalisation curve. The shelf in the middle corresponds with 1a, while an extra time constant at 50Hz limits the amount

of lf boost applied to warps and rumbles. The 'IEC amendment' is an extra roll-off at 20Hz, (shown dotted) to further reduce subsonics. When RIAA equalisation 1c is applied to cartridge output 1b, the result will look like Fig. 1d, with the maximum amplitudes occurring around 1-2kHz.

Clearly, the overload performance of an RIAA input can only be assessed by driving it with an inverse-RIAA equalised signal, rising at 6dB/octave except around the middle shelf. My Precision preamp '96 has an input overload margin referred to 5mV rms of 36dB across most of the audio band, i.e., 315mV

rms at 1kHz. The margin is still 36dB at 100Hz, but due to the RIAA low-frequency boost this is only 30mV rms in absolute terms.

The final complication is that preamplifier output capability almost always varies with frequency. In Preamp '96, the effects have been kept small. The output overload margin voltage – and hence input margin – falls to +33dB at 20kHz. This is due to the heavy capacitive loading of both the main RIAA feedback path and the pole-correcting RC network ( $R_{24,25}$  and  $C_{20}$ ). This could be eliminated by using an op-amp with greater load-driving capabilities, if you can find one with the low noise of a 5534.

The overload capability of Preamp 96 is also reduced to 31dB in the bottom octave 10-20Hz, because the IEC amendment is implemented in the second stage. The lf signal is fully amplified by the first stage, then attenuated by the deliberately slow initial roll-off of the subsonic filter.

Such audio impropriety always carries a penalty in headroom as the signal will clip before it is attenuated. This is the price paid for an accurate IEC amendment set by polyester caps in the second stage, as opposed to the usual method of putting a small electrolytic in the first-stage feedback path, rather than the 220µF used. Alternative input architectures that put flat amplification before an RIAA stage suffer much more severely from this kind of headroom restriction.<sup>3</sup>

These extra preamp limitations on output level are shown at Fig. 1e, and, comparing 1d, it appears they are almost irrelevant because of the falloff in possible input levels at each end of the audio band. ■

## References

- Self, D., 'Precision preamplifier '96', *Electronics World*, July/Aug and Sept 1996.
- Holman, T., 'Dynamic range requirements of phonographic preamplifiers', *Audio*, July 1977, p74.
- As [1], July/Aug 1996, p543.

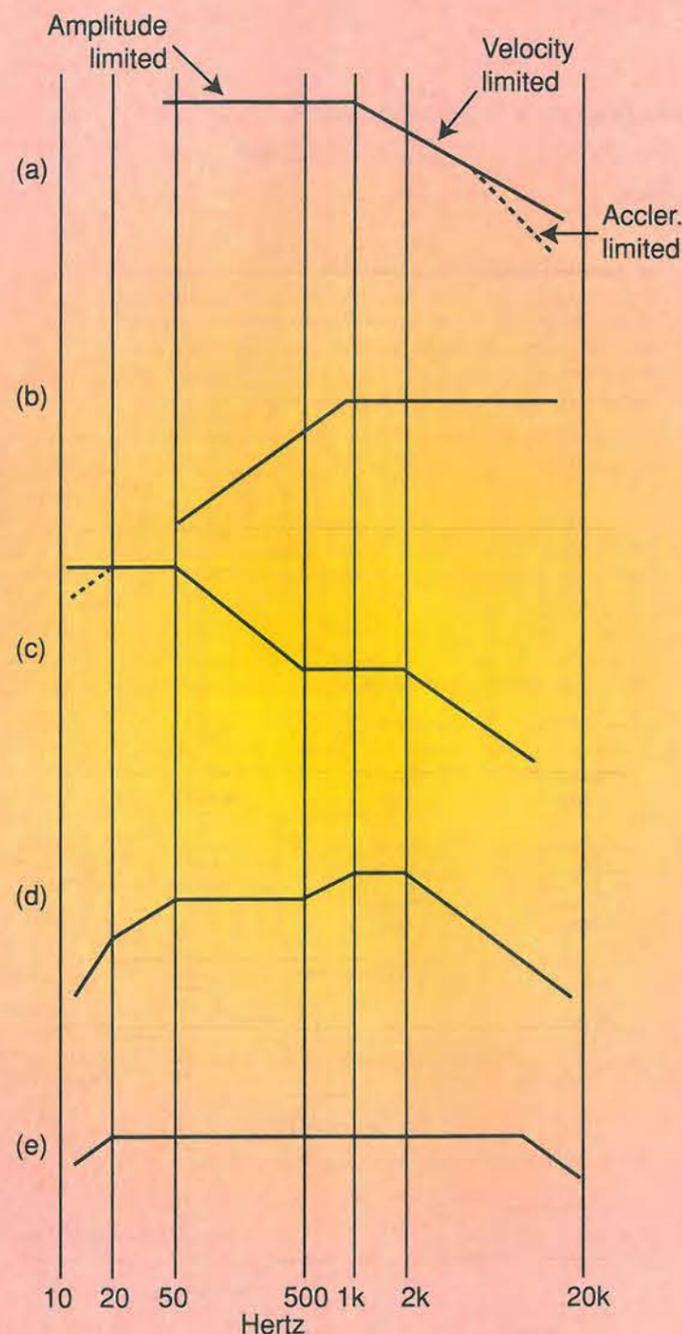


Fig. 1a). Restrictions on the level put onto a vinyl disc. The extra limit of groove curvature – stylus acceleration – is shown dotted. Fig. 1b). Response of a moving-coil or moving-magnet cartridge to a signal following the maximum contour in Fig. 1a). Fig. 1c). The RIAA replay curve. The IEC amendment is an extra roll-off at low frequency, shown dotted. Fig. 1d). The combination of b) and c). Fig. 1e). RIAA preamp output limitations. The high-frequency restriction is very common and is often much worse in discrete preamplifier stages with poor load-driving capabilities.

# Programmable logic primer

In this first article based on his new designer's handbook - 'FPGAs and programmable logic', Geoff Bostock provides an introduction to standard logic families.

The primary building block of logic circuits is the logic gate. This is a device which operates on two or more logic signals to give an output which is defined by a logic operator. The standard logic operators are And, Or and Invert, which only acts on one signal.

There are two classical logic families - ttl, which uses a non-final 5V supply, and 4000-series c-mos, which can work from a supply of between 3V and 15V. In recent years, the 4000 series has been largely superseded by the HC high-speed c-mos family. A logic low signal is usually defined as being close to 0V, or ground, while a logic high signal normally sits close to the supply voltage,  $V_{cc}$ , or at least above half  $V_{cc}$ .

An And function is defined as only giving a high output when all the inputs are high; the Or function has a high output when any one of its inputs is high. The Invert function changes a logic signal from high to low, or vice versa. These functions may be written down as logic equations as follows:

And function:  $Y=A*B*C$  or  $Y=A\&B\&C$   
 Or function:  $Y=A+B+C$  or  $Y=A\#B\#C$   
 Invert function:  $Y=!A$  or  $Y=\bar{A}$

Alternative notations exist because different logic compilers have adopted different conventions. Using '\*', '+' and '/' for logic clashes with their more familiar use as arithmetic operators in programming languages. For the remainder of this article, I will use '&', '#', and '!'.

Figure 1 shows an alternative way of showing logic relationships - the truth table. The symbol 'H' represents logic high, sometimes replaced by '1', while 'L' stands for logic low, with '0' as an alternative. The symbol 'X' represents don't care; the logic level can be high or low.

These three operators form the basis of all possible logic circuits. For example, the exclusive-Or gate has a low output if its two inputs are the same, but high if they are different. Its logic operator is written as  $Y=A\$B$  or, sometimes  $Y=A:+B$ . It is logically equivalent to  $Y=A\&!B\#!A\&B$ .

These logic functions may also be represented diagrammatically. Standard gate symbols are shown in Fig. 2; as well as And, Or, and Invert, gates with the functions Nand and Nor are also depicted. The NAND function is an And followed by an Invert, Nor is Or followed by Invert; a small bubble on an output, or an input, signifies an inversion.

The exclusive-Or symbol, and its equivalent logic circuit, are drawn in Fig. 3.

## Sequential logic

Output of a gate does not depend on the order in which the signals are applied. If both inputs of a two-input And gate are low, the output will also be low; if A goes high before B, or if B goes high before A, the result will be the same - two highs on the inputs yield a high on the output.

A	B	C	Y	A	B	C	Y	A	Y
1	1	1	H	1	X	X	H	1	H
0	X	X	L	X	1	X	H	0	L
X	0	X	L	X	X	1	H		
X	X	0	L	0	0	0	L		
AND				OR				INVERT	

Fig. 1. Logic function truth tables.

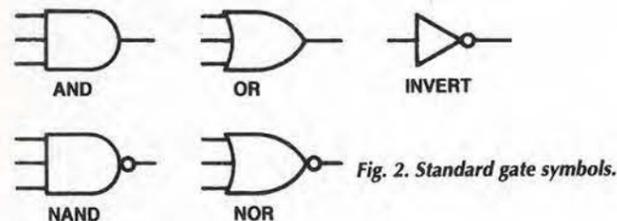


Fig. 2. Standard gate symbols.

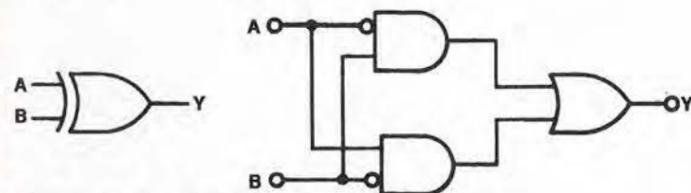


Fig. 3. Exclusive-Or symbol and its equivalent circuit.

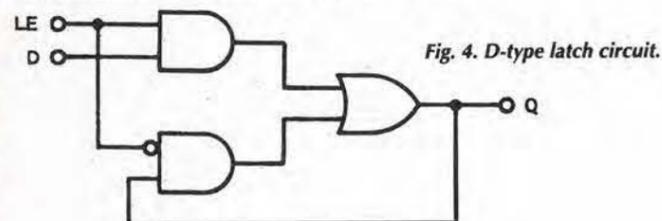


Fig. 4. D-type latch circuit.

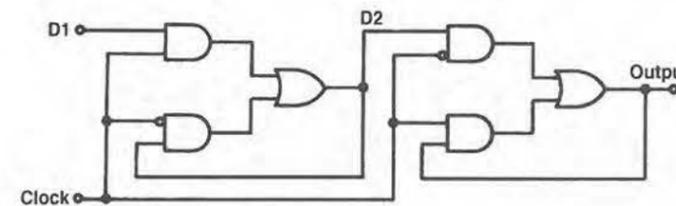


Fig. 5. Master-slave D-type flip-flop.

Fig. 6. One-to-eight line decoder and demultiplexer.

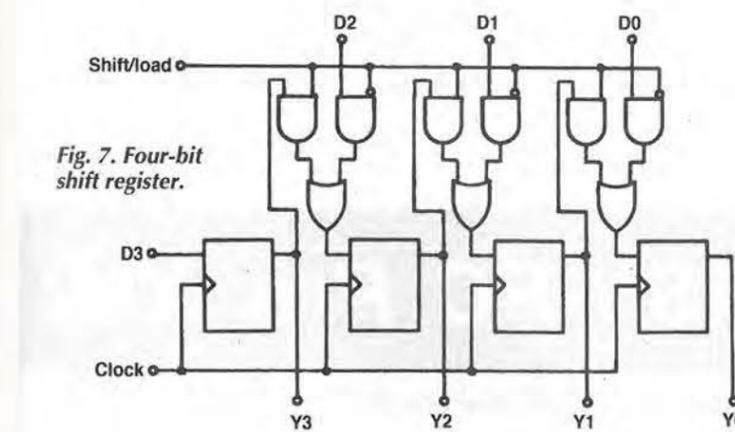
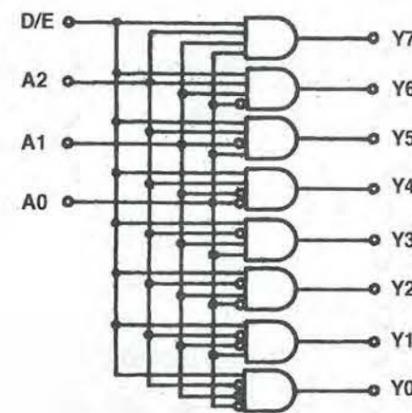


Fig. 7. Four-bit shift register.

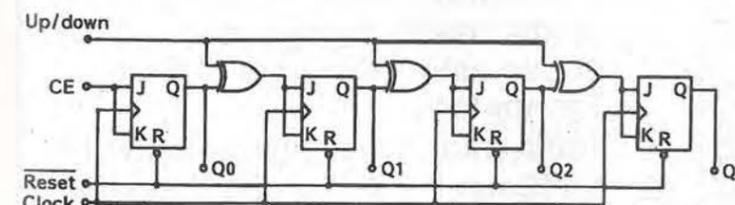


Fig. 8. Four-bit counter.

Table 1. Truth table for decoder/demultiplexer, Fig 6.

D/E	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	O <sub>7</sub>	O <sub>6</sub>	O <sub>5</sub>	O <sub>4</sub>	O <sub>3</sub>	O <sub>2</sub>	O <sub>1</sub>	O <sub>0</sub>
0	X	X	X	L	L	L	L	L	L	L	L
1	0	0	0	L	L	L	L	L	L	L	H
1	0	0	1	L	L	L	L	L	L	H	L
1	0	1	0	L	L	L	L	L	H	L	L
1	0	1	1	L	L	L	L	H	L	L	L
1	1	0	0	L	L	L	H	L	L	L	L
1	1	0	1	L	L	H	L	L	L	L	L
1	1	1	0	L	H	L	L	L	L	L	L
1	1	1	1	H	L	L	L	L	L	L	L

Consider Fig. 4. If input LE is high, the output, Q, will be the same as input D. This is because the output of the lower And gate is low - irrespective of D. Suppose that LE is now taken low; the upper gate now has a low output so Q will follow the output of the lower gate. If D was high when LE went low, Q was also high, so the lower gate was high and Q will stay high. Conversely, if D was low, Q will stay low.

This function is known as a latch. While LE is high, the latch is transparent and Q follows D; when LE is low, the level of D when LE went low is latched into Q. Output of the circuit depends on the sequence in which the signals are applied, hence the term sequential circuit.

Figure 5 shows two latches in series, with the LE signal inverted between them. When the first latch is transparent, the second is latched, and vice versa. A signal applied to D<sub>1</sub> will appear at D<sub>2</sub> while LE<sub>1</sub> is high, but will not be transmitted to Q until CLK goes low, sending LE<sub>2</sub> high. At this time, LE<sub>1</sub> goes low and locks out any changes on D<sub>1</sub>. It appears that the signal on D<sub>1</sub> is sent through to Q as CLK changes from high to low. This is the principle of the master-slave flip-flop or D-type flip-flop.

## Practical logic circuits

Devices containing one or more gates, latches or flip-flops form the basis of the standard logic families. Circuit designers can use these integrated circuits to build up more complex functions by interconnecting these ssi, or small-scale integration, devices on a printed-circuit board. However, the device manufacturers anticipated these requirements by producing medium-scale integration, or msi, parts containing many of the standard circuit functions which can be built from gates and flip-flops.

A typical combinatorial msi function is a one-to-eight line decoder/demultiplexer. The circuit diagram for this function is shown in Fig. 6. The logic levels on the three address inputs represent a binary number in the range 000<sub>2</sub> (0<sub>10</sub>) to 111<sub>2</sub> (7<sub>10</sub>). The logic level on the data/enable input is transmitted to the output selected by the input address. The truth table for this function is shown in Table 1.

Similarly, msi functions can be built from sequential elements. Figure 7 illustrates this point with the circuit of a four-bit shift register. Data on the inputs is loaded into the flip-flops when the shift/load signal is low and there is a low-to-high clock transition. When shift/load is high, the data is moved one place to the right on a clock edge. This circuit can form the basis of some arithmetic functions, or it may be used in communications to change the data format from parallel to serial or vice versa.

A different type of flip-flop, the J-K flip-flop, is used in the counter circuit in Fig. 8. A J-K flip-flop behaves like a D-type when the J and K inputs are complementary, but if both are high, the output changes from high to low, or low to high, the so-called toggle function. If both are low, no change occurs on a clock edge; the output data is unchanged, the hold condition. As long as the count enable, CE, and reset inputs are held high, the counter function will increment by one on each clock transition.

Taking the reset low makes every output low, resetting the counter to binary 0000<sub>2</sub>. Reset is an asynchronous function which is built into some flip-flops; it operates independently from the clock and allows the flip-flop to be put into a known condition. Some flip-flops also include an asynchronous set input which puts the output high.

Operation of the counter may be described by a state diagram. Each combination of output levels corresponds to a binary number from 0000<sub>2</sub> (0<sub>10</sub>) to 1111<sub>2</sub> (15<sub>10</sub>), and represents a distinct state of the counter. Figure 9 shows the counter state diagram. Each state is represented by a circle containing the output levels in that state. The arrows are labelled with the logic inputs which enable the jumps between states. A recursive arrow means that there is no jump and gives the hold

condition for that state.

The CE must be true for counting to proceed; if CE is false, the counter holds its present state.

Many sequential functions are best described by a state diagram, just as combinatorial functions are often defined in a truth table.

In the next article, Geoff takes a more in-depth look at programmable logic elements.

This article is derived from Geoff Bostock's new book 'FPGAs and Programmable LSI - a designer's handbook'. This work covers designing FPGAs, large PAL structures, RAM and antifuse-based FPGAs and FPGA

selection. Comprising 215 pages, this book is available by sending a postal order or cheque with a request for the book to Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. The fully-inclusive price is £27.50 UK, £30 Europe or £33 rest of world. Alternatively, fax your full credit card details and address on 0181 652 8956 or e-mail jackie.lowe@rbp.co.uk.

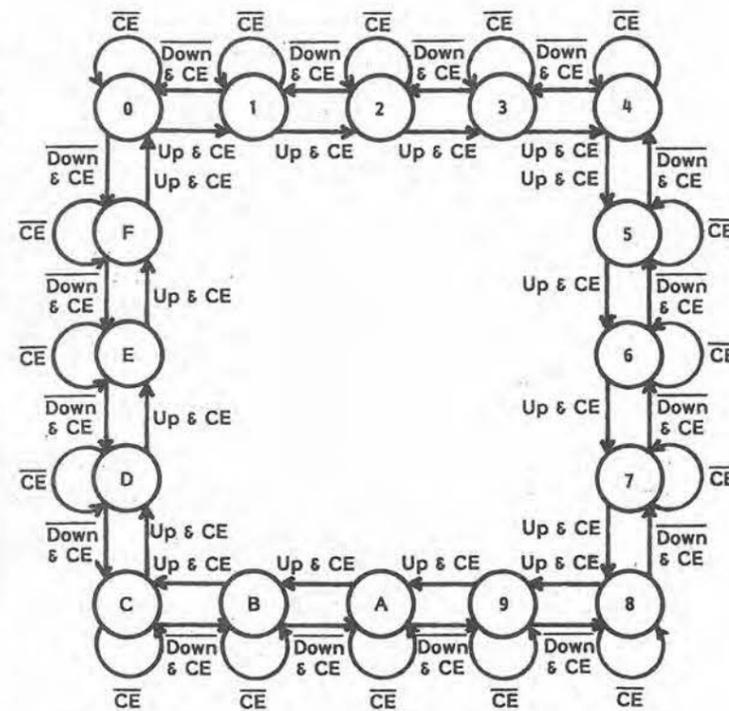


Fig. 9. Four-bit counter state diagram.

# Designing power supplies

Ray Fautley describes an easy-to-use procedure for designing reliable full-wave rectifiers of the centre-tapped secondary variety.

In this version of the full-wave rectifier, the bridge rectifier is simplified to two diodes, but the transformer needs a centre tap, which becomes the ground connection.

Alternating voltage is applied to rectifier diodes  $D_{1,2}$  where it is rectified and the output smoothed by reservoir capacitor  $C$ .

Fundamental frequency of the ripple voltage is twice that of the supply frequency. Resistance  $R_s$  represents the source of the supply and  $V_{sec}$  is the voltage across the whole of the secondary winding.

### Design procedure

- 1) Specify required dc output voltage at full load  $E_{dc(load)}$  (V).
- 2) Specify required maximum load current  $I_{dc(load)}$  (A).
- 3) Specify maximum voltage ripple acceptable  $V_{r(rms)}$  (V).
- 4) Specify the ac mains supply voltage  $V_{pri(rms)}$  (V).
- 5) Specify the frequency of the mains supply  $f$  (Hz).
- 6) Determine the value of the equivalent load resistance  $R_L$ :

$$R_L = \frac{E_{dc}}{I_{dc(load)}}$$

where  $E_{dc}$  is the design value of the dc output voltage. It is the required voltage across the load,  $E_{dc(load)}$ , added to the voltage drop across one of the diodes. As the voltage drop across the diodes occurs only while they are conducting, and they conduct alternately, the effective drop is that of just one diode.

$$E_{dc} = E_{dc(load)} + V_{rec}$$

where  $V_{rec}$  (the drop across the rectifier diode) is 0.9V, so:

$$R_L = \frac{E_{dc(load)} + 0.9}{I_{dc(load)}}$$

- 7) Determine average current through each diode. Half the average current,  $I_0$ , will flow through each diode.

$$I_0 = I_{dc(load)}/2$$



- 8) Determine a value for source resistance of the supply,  $R_s$ . If the mains transformer winding resistances are known - and it rarely is - refer to step 8 in the design procedure the the full-wave rectifier (September 1996 issue) for the method of evaluating  $R_s$ . Otherwise, assume that  $R_s$  is about 5% of  $R_L$ . Then for low resistance loads:

$$R_s = \frac{R_L \times 5}{100} + \frac{0.9}{I_0}$$

For high resistance loads, where the transformer winding resistance predominates:

$$R_s = \frac{R_L \times 5}{100}$$


- 9) Calculate the ratio of  $R_s$  to  $R_L$  as a percentage:

$$\frac{R_s}{R_L} \times 100\%$$

- 10) Determine percentage ripple voltage from the specified maximum ripple and the dc output voltage:
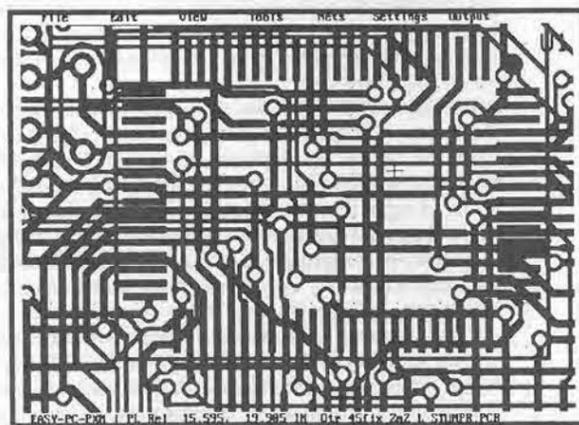
## THE Autorouter for EASY-PC Pro' XM!

MultiRouter is "the best Autorouter that I have seen costing less than £10,000!" R.H. - (Willingham, UK)



- MultiRouter uses the latest 32 bit, Shape based, Multi-pass, Shove-aside, Rip-up and Re-try Technology
- 100% routed 140 Components on a 210mm x 150mm board in less than 10 minutes! (75MHz Pentium)
- 100% Completion where other autorouters fail
- Only £295! Could Easily Pay For Itself On The First Project!

### Number One Systems

Write, fax, phone or email for full information.

UK/EEC: Ref: WW, Harding Way, St.Ives, Cambridgeshire, ENGLAND, PE17 4WR. Telephone UK: 01480 461778 (7 lines) Fax: 01480 494042  
 USA: Ref: WW, 126 Smith Creek Drive, Los Gatos, CA 95030 Telephone/Fax: (408) 395-0249  
 email: sales@numberone.com International +44 1480 461778/494042



CIRCLE NO. 121 ON REPLY CARD

Full-wave rectification using a transformer with centre tap needs two fewer diodes than the full-wave bridge rectifier.

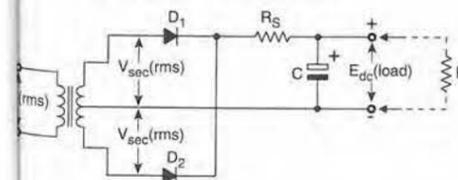


Table 1. Finding the value for X.

V <sub>r</sub> %	R <sub>s</sub> /R <sub>L</sub> %	0.1	0.3	1.0	3.0	5.0	10	30
0.1	0.1	771	740	709	646	614	583	463
0.2	0.3	381	368	354	324	309	294	233
0.3	1.0	257	247	237	218	208	199	158
0.4	3.0	195	188	177	162	154	147	120
0.5	5.0	154	148	141	129	122	116	95
0.6	10	128	123	117	108	103	98	81
0.7	20	110	106	102	94	89	85	69
0.8	30	97	93	88	81	77	74	61
0.9	40	86	82	78	72	68	65	54
1.0	50	78	75	71	65	62	59	49
2.0	60	38	37	36	33	31	30	25
3.0	70	26	25	24	22	21	20	16
4.0	80	19	19	18	17	16	15	12
5.0	90	15	15	14	13	12.5	12	10
6.0	100	13	12	12	11	10.5	10	8
7.0	110	10.6	10.3	9.9	9.2	8.8	8.5	7.0
8.0	120	9.1	8.8	8.5	8.0	7.7	7.4	6.0
9.0	130	8.0	7.7	7.5	7.0	6.7	6.5	5.3
10	140	7.1	7.0	6.8	6.4	6.1	5.9	4.9
20	150	2.9	2.8	2.7	2.6	2.5	2.4	2.2
30	160	1.6	1.6	1.5	1.5	1.4	1.4	1.2
40	170	0.9	0.9	0.9	0.9	0.8	0.8	0.7

$$V_r\% = \frac{V_{r(rms)}}{E_{dc(load)}} \times 100\%$$

- From the figures in Table 1, determine the value of X required to provide the percentage ripple voltage, V<sub>r</sub>% in step 10) above, for (R<sub>s</sub>/R<sub>L</sub>)% calculated in 9).
- Calculate reservoir capacitor C, required to provide the ripple voltage V<sub>r(rms)</sub> from:

$$C = \frac{X(10^6)\mu F}{2\pi f R_L}$$

The term used for frequency is f and not 2f (the ripple frequency in a full-wave centre-tap rectifier circuit being twice the supply frequency) because the figures in Table 1 allow for the difference.

- Find the nearest standard (or available) value for the reservoir capacitor C, close to (preferably just above) the value calculated in step 12). If the value of the capacitor is different from that in 12), call it C<sub>1</sub> and determine a new value for X (call it X<sub>1</sub>) from:

$$X_1 = 2\pi f C_1 R_L$$

with C<sub>1</sub> in μF,

$$X_1 = \frac{2\pi f C_1 R_L}{10^6}$$

- From the figures in Table 2 determine the value of Y for X in step 11), or X<sub>1</sub> in step 13), and (R<sub>s</sub>/R<sub>L</sub>)% in step 9).
- Determine the transformer secondary voltage V<sub>sec(rms)</sub> required, from the value for Y in step 14):

$$V_{sec(rms)} = \frac{E_{dc}}{\sqrt{2} \times Y}$$

where E<sub>dc</sub>=E<sub>dc(load)</sub>+V<sub>rec</sub>

Table 2. Finding the Value of Y

X	R <sub>s</sub> /R <sub>L</sub> %										
	0.05	0.1	0.5	1.0	2	4	6	8	10	12.5	
0.1	0.64	0.64	0.64	0.63	0.62	0.61	0.60	0.57	0.57	0.56	
0.2	0.64	0.64	0.64	0.63	0.62	0.62	0.60	0.58	0.57	0.57	
0.3	0.64	0.64	0.64	0.63	0.63	0.62	0.61	0.59	0.58	0.57	
0.4	0.64	0.64	0.64	0.63	0.63	0.62	0.61	0.60	0.58	0.58	
0.5	0.65	0.64	0.64	0.63	0.63	0.62	0.61	0.60	0.59	0.58	
0.6	0.65	0.65	0.64	0.64	0.64	0.63	0.62	0.60	0.59	0.58	
0.7	0.66	0.65	0.65	0.65	0.64	0.63	0.62	0.61	0.60	0.59	
0.8	0.66	0.66	0.66	0.65	0.65	0.64	0.63	0.62	0.60	0.59	
0.9	0.67	0.66	0.66	0.66	0.65	0.64	0.63	0.62	0.61	0.60	
1.0	0.68	0.68	0.67	0.67	0.66	0.65	0.64	0.63	0.62	0.61	
1.5	0.72	0.71	0.70	0.70	0.69	0.68	0.67	0.65	0.64	0.62	
2.0	0.76	0.76	0.76	0.76	0.75	0.73	0.71	0.70	0.67	0.65	
2.5	0.77	0.77	0.77	0.77	0.76	0.74	0.72	0.71	0.68	0.66	
3.0	0.79	0.78	0.78	0.78	0.77	0.75	0.73	0.72	0.69	0.68	
4.0	0.82	0.82	0.80	0.79	0.79	0.78	0.75	0.73	0.71	0.69	
5.0	0.85	0.85	0.84	0.84	0.82	0.80	0.77	0.75	0.73	0.70	
6.0	0.86	0.86	0.85	0.85	0.84	0.80	0.77	0.75	0.73	0.70	
7.0	0.88	0.87	0.86	0.86	0.85	0.82	0.78	0.75	0.74	0.71	
8.0	0.89	0.88	0.87	0.87	0.86	0.82	0.78	0.76	0.74	0.71	
9.0	0.90	0.90	0.88	0.88	0.87	0.83	0.79	0.76	0.74	0.72	
10	0.92	0.91	0.90	0.89	0.88	0.84	0.80	0.77	0.75	0.72	
15	0.95	0.93	0.91	0.90	0.89	0.85	0.80	0.77	0.75	0.72	
20	0.96	0.95	0.94	0.92	0.90	0.86	0.80	0.78	0.75	0.73	
25	0.96	0.96	0.95	0.93	0.90	0.86	0.81	0.78	0.75	0.73	
30	0.97	0.96	0.95	0.93	0.91	0.86	0.82	0.78	0.76	0.73	
40	0.98	0.97	0.96	0.93	0.91	0.86	0.82	0.78	0.76	0.73	
50	0.98	0.98	0.96	0.94	0.91	0.86	0.82	0.79	0.76	0.73	
60	0.98	0.98	0.96	0.94	0.91	0.86	0.82	0.79	0.76	0.73	
70	0.99	0.99	0.96	0.94	0.91	0.86	0.82	0.79	0.76	0.73	
80	0.99	0.99	0.96	0.94	0.91	0.86	0.82	0.79	0.76	0.73	
90	0.99	0.99	0.97	0.94	0.91	0.86	0.82	0.79	0.76	0.73	
100	0.99	0.99	0.97	0.94	0.91	0.86	0.82	0.79	0.76	0.73	
200	1.0	0.99	0.97	0.94	0.91	0.86	0.82	0.79	0.76	0.73	
300	1.0	0.99	0.97	0.95	0.91	0.86	0.82	0.79	0.76	0.73	
1000	1.0	0.99	0.97	0.95	0.91	0.86	0.82	0.79	0.76	0.73	

$$Y = \frac{0.707 \times E_{dc}}{V_{sec(rms)}}$$

Voltage V<sub>sec(rms)</sub> is only half the required secondary voltage of the transformer, which has a centre-tapped winding. So the total secondary winding will be:

$$V_{sec(rms)} - 0 - V_{sec(rms)}$$

- Determine the peak voltage (or PIV, peak inverse voltage) that each of the rectifier diodes must withstand.

$$PIV = 2 \times V_{sec(peak)} = 2 \times \sqrt{2} \times V_{sec(rms)} = 2.828 V_{sec(rms)}$$

The factor 2 occurs because each rectifier diode has both halves of the secondary winding in series applied in alternate half cycles.

- Find the value for Z from Table 3 for 2X (or 2X<sub>1</sub>), where X was found in step 11), or X<sub>1</sub> in step 13), and for (R<sub>s</sub>/2R<sub>L</sub>)%. The value for (R<sub>s</sub>/R<sub>L</sub>)% was found in step 9).

$$Z = I_{(rms)} / I_0$$

- From the value of Z found in step 17), determine current through each rectifier diode:

$$I_{(rms)} = I_0 \times Z$$

- Determine recurrent peak current I<sub>(peak)</sub> through each rectifier diode. From the figures in Table 4 for 2X (or 2X<sub>1</sub>) and (R<sub>s</sub>/2R<sub>L</sub>)% find W, which is I<sub>(peak)</sub>/I<sub>0</sub>.

Thus find I<sub>(peak)</sub>=I<sub>0</sub>×W.

- Determine initial switch-on current I<sub>on</sub>. As C (or C<sub>1</sub>) will be initially discharged, the load on the rectifier diodes will be nearly a short-circuit at the instant of switch-on, limited only by the source resistance R<sub>s</sub>. Then:

$$I_{on} = \frac{V_{sec(peak)}}{R_s}$$

This very high current flows for only a very short time, but the rectifier diodes must be capable of withstanding it. If suitable devices with such high pulse ratings are not available, source resistance R<sub>s</sub> must be increased by adding an external resistor R<sub>ext</sub> between the rectifier and the reservoir capacitor C, or C<sub>1</sub>. The value of R<sub>ext</sub> to limit the switch-on current to an acceptable lower value I<sub>on(L)</sub> is determined in step 28).

- Decide on a suitable rectifier diode type to be used. The device must have all its ratings equal to, or greater than, the following:

PIV or 2×V<sub>sec(peak)</sub> (sometimes V<sub>RRMT</sub>) see step 16)

Initial switch-on current or I<sub>on</sub> (sometimes I<sub>FSMT</sub>), see step 20)

Average current or I<sub>0</sub> (sometimes I<sub>F(AV)</sub>), see step 7)

Table 2 continued.

X	R <sub>s</sub> /R <sub>L</sub> %											
	15	20	25	30	35	40	50	60	70	80	90	100
0.1	0.56	0.54	0.51	0.49	0.47	0.46	0.44	0.40	0.38	0.35	0.33	0.32
0.2	0.56	0.54	0.51	0.49	0.47	0.46	0.44	0.40	0.38	0.35	0.33	0.32
0.3	0.56	0.54	0.51	0.49	0.47	0.46	0.44	0.40	0.38	0.35	0.33	0.32
0.4	0.56	0.54	0.51	0.49	0.48	0.46	0.44	0.40	0.38	0.36	0.33	0.32
0.5	0.57	0.54	0.51	0.50	0.48	0.46	0.44	0.41	0.38	0.36	0.34	0.32
0.6	0.57	0.54	0.51	0.50	0.48	0.46	0.44	0.41	0.38	0.36	0.34	0.32
0.7	0.57	0.55	0.52	0.50	0.48	0.46	0.44	0.41	0.38	0.37	0.34	0.32
0.8	0.58	0.55	0.52	0.50	0.48	0.47	0.44	0.41	0.39	0.38	0.34	0.33
0.9	0.58	0.55	0.53	0.51	0.49	0.47	0.45	0.41	0.39	0.38	0.34	0.33
1.0	0.59	0.56	0.53	0.51	0.49	0.47	0.45	0.42	0.40	0.38	0.35	0.33
1.5	0.60	0.57	0.55	0.52	0.50	0.48	0.45	0.42	0.40	0.38	0.35	0.33
2.0	0.63	0.59	0.56	0.53	0.51	0.49	0.46	0.43	0.41	0.38	0.35	0.33
2.5	0.64	0.60	0.57	0.54	0.52	0.50	0.47	0.43	0.41	0.38	0.36	0.34
3.0	0.65	0.61	0.58	0.55	0.52	0.50	0.47	0.43	0.41	0.38	0.36	0.34
4	0.66	0.62	0.59	0.55	0.53	0.51	0.47	0.44	0.41	0.38	0.36	0.34
5	0.67	0.63	0.60	0.56	0.54	0.52	0.48	0.44	0.42	0.39	0.37	0.35
6	0.68	0.63	0.60	0.56	0.54	0.52	0.48	0.44	0.42	0.39	0.37	0.35
7	0.68	0.64	0.60	0.57	0.54	0.52	0.48	0.44	0.42	0.39	0.37	0.35
8	0.68	0.64	0.60	0.57	0.54	0.52	0.48	0.44	0.42	0.39	0.37	0.35
9	0.69	0.64	0.60	0.57	0.54	0.52	0.48	0.44	0.42	0.39	0.37	0.35
10	0.69	0.65	0.61	0.58	0.55	0.52	0.48	0.44	0.43	0.39	0.37	0.35
15	0.69	0.65	0.61	0.58	0.55	0.52	0.48	0.44	0.43	0.39	0.37	0.35
20	0.70	0.65	0.61	0.58	0.55	0.53	0.49	0.44	0.43	0.39	0.37	0.35
25	0.70	0.65	0.61	0.58	0.55	0.53	0.49	0.45	0.43	0.39	0.37	0.35
30	0.70	0.65	0.61	0.58	0.55	0.53	0.49	0.45	0.43	0.39	0.37	0.35
40	0.70	0.65	0.61	0.58	0.55	0.53	0.49	0.45	0.43	0.39	0.37	0.35
50	0.70	0.65	0.61	0.58	0.55	0.53	0.49	0.45	0.43	0.40	0.38	0.35
60	0.70	0.65	0.61	0.58	0.55	0.53	0.49	0.45	0.43	0.40	0.38	0.35
70	0.70	0.65	0.61	0.58	0.55	0.53	0.49	0.45	0.43	0.40	0.38	0.35
80	0.70	0.65	0.61	0.58	0.55	0.53	0.49	0.45	0.43	0.40	0.38	0.35
90	0.70	0.65	0.61	0.58	0.55	0.53	0.49	0.45	0.43	0.40	0.38	0.35
100 to 1000	0.70	0.66	0.61	0.58	0.55	0.53	0.49	0.45	0.43	0.40	0.38	0.35

- Determine rms ripple current I<sub>c(rms)</sub>, flowing through reservoir capacitor C (or C<sub>1</sub>):

$$I_{c(rms)} = \sqrt{2(I_{rms}^2) - (I_{dc(load)}^2)}$$

for I<sub>(rms)</sub>

improved by the addition of a shorting-out device as recommended for the bridge rectifier circuit in the September issue.

**Putting the procedure to work**

Now for the worked example. A supply of 1200V at 0.5A is required for a valve rf power amplifier. An acceptable ripple on the supply would be 12V rms.

- 1)  $E_{dc(load)}=1200V$
- 2)  $I_{dc(load)}=0.5A$
- 3)  $V_{r(rms)}=12Vrms$
- 4)  $V_{pri(rms)}=240Vrms$
- 5)  $f=50Hz$

$$6) R_L = \frac{E_{dc}}{I_{dc(load)}} = \frac{E_{dc(load)} + V_{rec}}{I_{dc(load)}}$$

As  $V_{rec}$  is only 0.9V it can be ignored.

$$So, R_L = \frac{E_{dc}}{I_{dc(load)}} = \frac{1200}{0.5} = 2400\Omega$$

$$7) I_o = \frac{I_{dc(load)}}{2} = \frac{0.5}{2} = 0.25A$$

$$8) R_s = \frac{2400 \times 5}{100} = 120\Omega$$

$$9) \frac{R_s}{R_L} \times 100\% = \frac{120}{2400} \times 100\% = 5\%$$

$$10) V_r\% = \frac{V_{r(rms)}}{E_{dc(load)}} \times 100\% = \frac{12}{200} \times 100\% = 6\%$$

11) Find the value of X for  $V_r\%$  and  $(R_s/R_L)\%$ , i.e.

$$V_r\% = 1 \text{ and } \frac{R_s}{R_L} = 5$$

from Table 1 is found to be 62.

$$12) C = \frac{X(10^6)}{2\pi f R_L} \mu F = \frac{62 \times 10^6}{2\pi \times 50 \times 2400} \mu F = 82.2\mu F$$

13) To obtain a high enough voltage rating for the reservoir capacitor, four capacitors connected in series are necessary. Four 330μF, 385V working-voltage capacitors would be suitable. A resistor of about 100kΩ (2W rating) should be connected across each of the four capacitors to equalise the dc voltage across each capacitor.

14) From Table 2, the value of Y for X and  $(R_s/R_L)\%$ , i.e. X=62 and  $(R_s/R_L)\%=5$ , is found to be 0.84.

$$15) V_{sec(rms)} = \frac{0.707 \times E_{dc}}{Y} = \frac{0.707 \times 1200}{0.84} = 1010V_{rms}$$

Total secondary winding will be:  $V_{sec(rms)}-0-V_{sec(rms)}$  or 1010V-0-1010V.

$$16) PIV=2.828V_{sec(rms)}=2.828 \times 1010=2856V$$

17) From step 11), X = 62 and from step 9),  $(R_s/2R_L)\%=5$ . Find the value of Z for 2X and for  $(R_s/2R_L)\%$ , i.e.

$$2X = 2 \times 62 = 124 \text{ and } \frac{R_s}{2R_L} = \frac{5}{2} = 2.5,$$

which from Table 3 is found to be 2.64.

18) From step 17), Z=2.64 and from step 7),  $I_o=0.25A$ , so,

$$I_{(rms)}=I_o \times Z=2.64 \times 0.25=0.66A$$

19) From step 11), X=62 and from step 9),

$(R_s/R_L)\%=5$  so the value of W for 2X and  $(R_s/2R_L)\%$ , where 2X=124 and  $(R_s/2R_L)\%=2.5$ , from Table 4 is found to be 7.92. As a result,

$$I_{(peak)}=I_o \times W=0.25 \times 7.92=1.98$$

$$20) I_{on} = \frac{V_{sec(peak)}}{R_s} = \frac{1.414V_{sec(rms)}}{R_s} = \frac{1.414 \times 1010}{120} = 11.9A$$

21) Diode ratings required are,

$$PIV(V_{RRMT})=2856V$$

$$I_{on}(I_{FSMT})=11.9A$$

$$I_o(I_{F(ave)})=0.25A$$

To obtain a PIV of 2856V it would be necessary to wire three BYX38-1200 diodes in series for each of the two diodes required.

$$22) I_{c(rms)} = \sqrt{I_{rms}^2 - I_{dc(load)}^2} = \sqrt{2 \times 0.66^2 - 0.25^2} = \sqrt{2 \times 0.4356 - 0.25} = \sqrt{0.6212} = 0.79A$$

23) Reservoir capacitor ratings required are,

$$C=82.2\mu F$$

$$V_{sec(peak)}=V_{dc(wkg)}=\sqrt{2} \times 1010=1428V$$

$$\text{Ripple current } I_{c(rms)}=0.79A$$

Four capacitors in series of 330μF, each with a working voltage of 385V dc would be suitable. To ensure that a quarter of the output voltage appears across each capacitor, a 100kΩ, 3W resistor should be wired across each of them.

$$24) I_{t(rms)}=I_{rms}=0.66A$$

$$25) \text{Transformer VA} = 2 \times V_{sec(rms)} \times I_{t(rms)} = 2 \times 1010 \times 0.66 = 1333.2VA$$

26) Mains transformer ratings required are,

$$T_{VA}=1333VA$$

$$\text{Primary winding } V_{pri(rms)}=240Vrms$$

$$\text{Secondary winding } V_{sec(rms)} = 1010V-0-1010V$$

$$\text{Secondary current } I_{t(rms)}=0.66A$$

Previous articles in this power-supply design series covered the full-wave bridge rectifier, September 1996 issue, and the half-wave single-diode rectifier, December 1996 issue. A subsequent article will deal with the voltage doubler.

Table 4. Finding the value for W.

2X	$R_s/R_L\%$										
	0.02	0.05	0.1	0.2	0.5	1.0	2	5	10	30	100
1	3.70	3.70	3.70	3.64	3.62	3.60	3.60	3.59	3.58	3.57	3.46
2	4.60	4.57	4.55	4.53	4.52	4.50	4.28	4.20	4.08	3.72	3.51
3	5.50	5.40	5.33	5.30	5.20	5.10	5.00	4.67	4.33	4.00	3.55
4	6.20	6.17	6.13	6.10	6.00	5.98	5.45	5.20	4.95	4.05	3.57
5	7.30	6.95	6.90	6.85	6.80	6.75	6.51	5.60	5.00	4.10	3.62
6	8.00	7.90	7.70	7.60	7.50	7.30	6.90	5.84	5.09	4.19	3.63
7	8.70	8.55	8.50	8.30	8.10	7.82	7.30	6.00	5.10	4.22	3.64
8	9.60	9.50	9.35	9.00	8.50	8.20	7.69	6.15	5.14	4.23	3.64
9	10.3	9.80	9.60	9.50	9.10	8.55	7.72	6.23	5.21	4.25	3.65
10	10.9	10.7	10.5	10.1	9.50	8.64	7.74	6.30	5.28	4.26	3.66
20	16.0	15.0	14.4	13.0	11.1	9.44	7.83	6.47	5.29	4.27	3.66
30	19.7	18.0	16.3	14.3	11.7	9.60	7.92	6.50	5.31	4.27	3.66
40	21.9	20.0	17.3	14.7	12.1	9.64	8.01	6.51	5.33	4.28	3.66
50	23.7	20.8	18.2	15.2	12.2	9.70	8.10	6.51	5.34	4.28	3.66
60	24.9	21.1	18.5	15.4	12.3	9.77	8.12	6.51	5.34	4.29	3.66
70	25.9	21.4	18.9	15.6	12.4	9.84	8.14	6.51	5.34	4.29	3.66
80	26.7	21.8	19.4	15.7	12.4	9.90	8.16	6.51	5.34	4.30	3.66
90	27.5	22.2	19.5	15.8	12.5	9.93	8.18	6.51	5.34	4.30	3.66
100	28.5	22.5	19.7	15.9	12.5	9.96	8.19	6.52	5.35	4.31	3.66
200	30.5	23.0	20.0	16.3	12.6	10.0	8.19	6.52	5.36	4.31	3.67
300	31.6	23.3	20.5	16.9	12.7	10.0	8.20	6.53	5.38	4.32	3.67
400	32.8	23.5	20.9	17.0	12.7	10.0	8.20	6.54	5.40	4.32	3.67
500	33.3	23.8	21.0	17.1	12.8	10.0	8.20	6.55	5.42	4.33	3.68
600	33.8	24.0	21.1	17.2	12.8	10.1	8.20	6.56	5.44	4.33	3.68
700	34.2	24.5	21.2	17.3	12.9	10.1	8.20	6.57	5.46	4.33	3.69
800	34.4	24.9	21.4	17.4	12.9	10.1	8.20	6.58	5.48	4.33	3.69
900	34.5	25.8	21.5	17.5	13.0	10.1	8.20	6.59	5.52	4.33	3.70
1000	34.7	27.0	21.6	17.6	13.0	10.1	8.20	6.60	5.56	4.33	3.70

# AT LAST A CATALOGUE AS ADVANCED AS YOUR THINKING

The most powerful source of reference for technical products and you can get it for £5.00

Electromail has always provided an outstanding range backed by the highest levels of service. Over 70,000 products from electronic components, electrical equipment to mechanical parts and tools, each one quality selected and available over the phone for next working day delivery.

You could say that's a service hard to beat, but that's just what we've done. The new Electromail CD-ROM catalogue makes a technological breakthrough by providing full information about our complete range, with colour photographs and technical illustrations. There are powerful search functions by product type and word number - it's the fastest and easiest way ever to select and order the product you need. There's a special new products review section to keep you informed of new range additions and it contains the full RS library of Data Sheets as an added bonus.

But the best news is you can get all that for just £5 - send for your copy, and get in the fast lane to finding the components you need.



ELECTROMAIL, P.O. Box 33, Corby, Northants, NN17 9EL.  
Tel: 01536 204555 Fax: 01536 405555

Please send me  copies of the **ELECTROMAIL** CD-ROM catalogue at £5.00 each inc. V.A.T. and P & P. Total value of order £

Name:

Address:

Postcode:

Tel:  Customer Ref. No.:

Please debit my Visa/Mastercard/American Express (please delete)

Card No:

Signed:  Expiry Date:

**CREDIT CARD ORDER HOTLINE : 01536 204555**


I enclose a cheque for £  to cover all items ordered. Ref: 234-4829

# Exclusive to EW readers
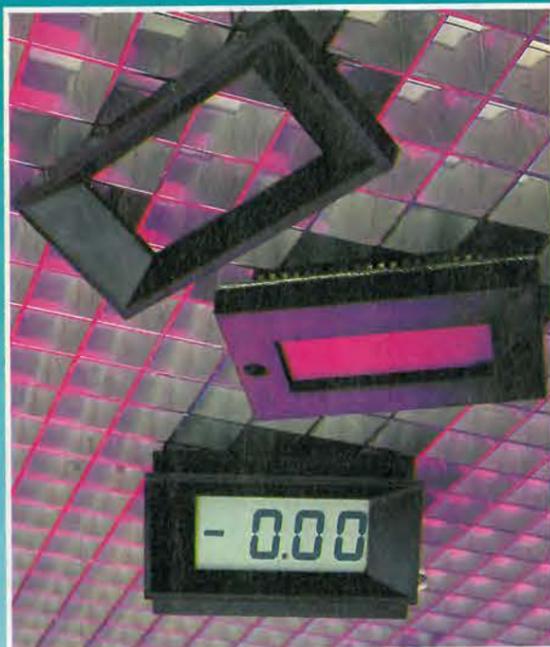
## Digital panel meter for just £8.95

The PM-128 is a 3.5-digit lcd panel meter with a full-scale reading of 199.9mV dc and is configurable for 20V, 200V or 500V full-scale reading by adding two resistors. Jumpers then set the decimal point position. Supplied complete with mounting bezel, this low-power meter is available exclusively to Electronics World readers at the special price of £8.95 – fully inclusive of postage, packing and VAT – or even less in quantities above four off. The normal selling price is £12.95 – excluding VAT and postage.

Please use the coupon to order your panel meters, and address all correspondence relating to this order to Vann Draper Electronics at Unit 5, Premier Works, Canal Street, South Wigston, Leicester LE18 2PL, fax 0116 2773945 or tel. 0116 2771400.



Incorporating the ICL7106 a-to-d converter, this digital panel meter has a full-scale input sensitivity of 200mV and a high input impedance of >100MΩ.

### PM-128 digital panel meter

#### Features

- Single 9V dc supply
- Low 1mA consumption
- Very high input impedance
- Ovrange indication
- Dual-slope integration a-to-d conversion
- Decimal point selectable
- Auto polarity indication
- Guaranteed zero reading for zero input

#### Specifications

- Maximum input 199.9mV
- 100MΩ input impedance
- Liquid crystal display
- 13.5mm high characters
- Maximum display 1999 counts, auto polarity
- Reading speed 2-3 times a second
- Accuracy ±0.5% at 23°C±5° & <80% RH
- Power requirements, 9-12V dc at 1mA
- Size 68mm by 44mm

### Use this coupon to order your PM128

Please send me

..... PM-128 digital panel meter(s)

at the fully inclusive special offer price of £8.95 each for quantities up to 4 off £8.65 each for quantities of 5 or more or £8.35 each for 10 or more quantities

for which I enclose a total of £.....

Name

Company (if any)

Address

Phone number/fax

Make cheques payable to Vann Draper Electronics Ltd  
Or, please debit my Master, Visa or Access card.

Card type (Access/Visa)

Card No

Expiry date


Please mail this coupon to Vann Draper Electronics, together with payment. Alternatively fax credit card details with order on 0116 2773945 or telephone on 0116 2771400. Address orders and all correspondence relating to this order to Vann Draper Electronics at Unit 5, Premier Works, Canal Street, South Wigston, Leicester LE18 2PL.

\*Overseas readers can also obtain this discount but details vary according to country. Please ring, write or fax to Vann Draper Electronics.
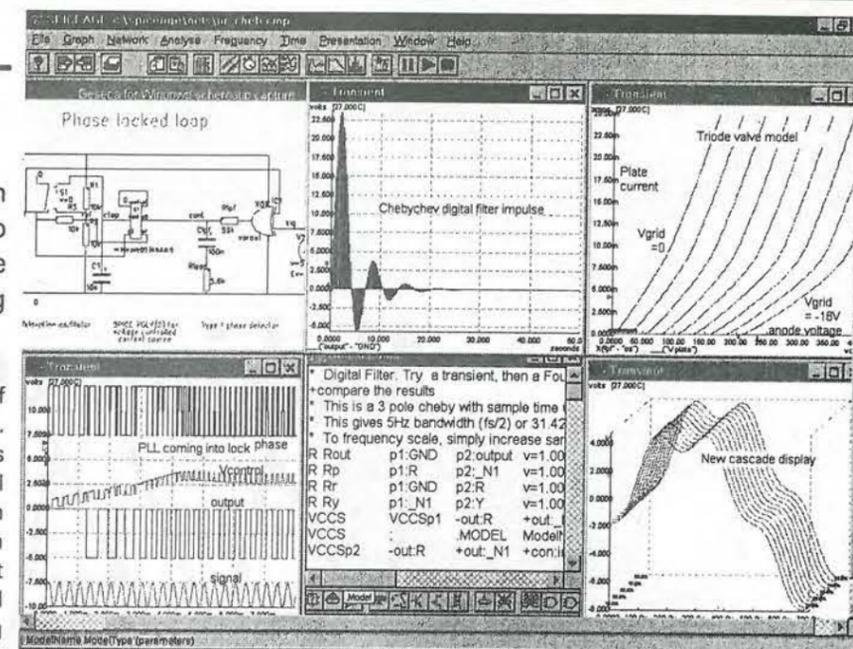
## Get out of a pickle - get into SpiceAge!

Hands up all who have been there? A great idea turns into sleepless nights: getting one thing right breaks something else...

Some circuits require the refining of many interdependent variables. SpiceAge provides a virtually limitless inventory of components, signal functions and instruments with facilities for sweeping values, with am and fm through arbitrary functions. It can guide you to a solution that could take much longer to find using hardware.



SpiceAge up your design without burning a hole in your pocket. Prices from just £85 + VAT to £695 + VAT. Friendly technical help comes free (dreadful puns optional). For a demonstration kit and details of our other and third party support programs (includes schematics, PCB layout, filter synthesis and model synthesis), please contact:

Charles Clarke at Those Engineers Ltd, 31 Birkbeck Road, LONDON NW7 4BP.  
Tel: 0181 906 0155 Fax: 0181 906 0969 Email 100550.2455@compuserve.com

Those Engineers Ltd

CIRCLE NO. 123 ON REPLY CARD

# SEETRAX CAE RANGER PCB DESIGN

## WITH COOPER & CHYAN AUTOROUTER

RANGER3 - DOS £2500  
- Windows\NT £2900

RANGER2 £150

Hierarchical or flat schematic linked to artwork.  
Unlimited design size, 1 micron resolution  
Any shaped pad, definable outline library  
Pin, gate & outline swapping - auto back annotation  
Split power planes, switchable on - line DRC

### COOPER & CHYAN SPECCTRA

autorouter (SP2)

Inputs: OrCAD, Cadstar,  
PCAD, AutoCAD DXF

Outputs: Postscript, Windows bit map

R2 & R3 Outputs: 8/9 & 24 pin printers, HP  
Desk & Laser Jet, Cannon Bubble Jet,  
HP-GL, Gerber,  
NC Drill, AutoCAD DXF

Upto 8 pages of schematic linked to artwork  
Gate & pin swapping - automatic back annotation  
Copper flood fill, Power planes, Track necking,  
Curved tracks, Clearance checking,  
Simultaneous multi-layer auto-router

RANGER2 UTILITIES £250

COOPER & CHYAN SPECCTRA auto-router (SPI)  
Gerber-in viewer, AutoCAD DXF in & out

UPGRADE YOUR PCB PACKAGE  
TO RANGER2 £60

### TRADE IN YOUR EXISTING PACKAGE TODAY

Seetrax CAE, Hinton Daubnay House, Broadway Lane, Lovedean, Hants, PO8 OSG  
Call 01705 591037 or Fax 01705 599036 + VAT & P.P

CIRCLE NO. 124 ON REPLY CARD

All Trademarks Acknowledged

# Making continuous WAVES

**With the competition for the first patent in wireless telegraphy won by Marconi, a new race began to emerge, to develop radio transmissions into a widely used medium of communication. Few guessed that it would result in the explosion of radio as we now know it. By Tom Ivall and Peter Willis**

**M**arconi may have secured the world's first patent on wireless telegraphy (*Electronics World*, June 1996) but others were already working on similar systems.

Braun in Germany, for instance, inventor of the cathode-ray oscillograph, developed a spark transmitter in 1898 and had it in service for short-range marine communication by 1900. Later, he and Marconi were to share the 1909 Nobel Prize for Physics in recognition of their radio work.

Braun and some business partners formed a wireless company called Telebraun, though this soon became a subsidiary of Siemens. At about the same time, two other German pioneers, Slaby and von Arco, supported by AEG, had set up a competing firm, Funkentelegraphie. In 1903, these two enterprises merged to form Gesellschaft für Drahtlose

Telegraphie and the result was the Telefunken system, a formidable rival to that of Marconi. By 1905, it had built more than 500 stations.

Meanwhile, in the USA, Fessenden and de Forest, separately, and the partnerships of Branly-Popp in France and Lodge-Muirhead in the UK, were also developing and operating spark transmitter systems of wireless telegraphy. All were striving for greater communication ranges through more highly powered transmissions and more sensitive receivers. They also wanted much better selectivity, to allow multi-station working without mutual interference.

One way to get more radiated power from a spark transmitter was to increase the oscillatory energy in the LCR circuit containing the spark gap. To do this, each high-voltage pulse had to get as much charge as possible into the capacitor. But the induction coil was restrict-

*Part of a rotary spark transmitter at Poldhu, Cornwall, as seen, it is claimed, while actually transmitting news of Britain's declaration of war on Germany in 1914.*



ed as a generator because it could inject only short-duration pulses of charge into a low-value capacitor.

So for higher-power transmission the induction coil was soon replaced by the engine-driven alternator, with an output of several kilovolts, plus a step-up transformer providing the necessary tens of kilovolts. This would produce as many as ten sparks, and hence damped wave-trains, per cycle of the alternator output.

As well as producing bigger charges, the alternator system could be designed to generate a relatively high spark frequency, thereby shortening the interval between wave-trains and increasing the average oscillatory energy. And this would give a musical note in receiver headphones which was more easily heard through static (atmospheric) interference than the rasping sounds produced by induction coils.

Radiated power was also increased by tighter inductive coupling between the oscillator and aerial circuits. But to achieve this, the spark had to be quenched rapidly, otherwise the interaction between the coupled circuits would cause beating and radiation on two component frequencies. This spark quenching also had the advantage of reducing arcing in fixed spark gaps. Rotary spark gaps or dischargers, driven from the alternator shafts, had the double purpose of preventing arcing and producing very regular, audible wave-train frequencies.

In the receiver, the coherer was too insensitive for long-range working and was difficult to operate. New detection techniques were invented and put into use, including anti-coherers, electrolytic and thermal principles, magnetic effects in an iron or steel medium, and rectification at contacts between crystals or between metals and crystals. Magnetic detectors proved robust in operation and were widely used.

In 1904, Fleming invented the thermionic diode, based of course on the Edison Effect,

which had been known since the late 19th century. The diode, however, did not immediately supersede the earlier devices but was used as a standby detector. Two years later, de Forest put in a third electrode, the grid, and produced the thermionic triode, or Audion as he called it. It was intended as a triggering form of detector but was not particularly successful as such. Only after years of development, on the device itself and on circuit applications, did the triode become really useful – but as an amplifier and oscillator. Subsequently, the non-linear parts of the amplifier characteristic were used for detection.

Even the earliest improvements in transmitters and receivers produced good operating results. The most dramatic was Marconi signalling across the Atlantic in 1901-02. Apart from the commercial implications, this supported early ideas of a reflecting layer and Heaviside's and Kennelly's 1902 prediction of the ionosphere, though the existence of the various layers was not fully confirmed till the 1920s. Transatlantic wireless telegraphy was also achieved by Fessenden, between Brant Rock, Massachusetts, and Macrihanish, Scotland, in 1906, and the following year Marconi started a full commercial service with stations at Clifden, Ireland, and Glace Bay, Canada.

By this time, radio was already well estab-

lished for marine communications. It had started in 1897 with fixed links such as those between the mainland and islands, lighthouses, lightships and moored vessels, and progressed to mobile communications with small ships such as ferries. The use of Morse code was universal.

During the first five years of the new century, large passenger vessels and warships were being equipped, and by 1911 wireless was compulsory on all ocean-going liners. In this first decade, several thousand lives were saved at sea through the use of radio.

Even before the wireless telegraph was fully established as a universal service, engineers were thinking about wireless telephony. They knew they needed continuous waves in place of damped wave-trains, and a means of modulating them with voice frequencies.

A short-lived proposal was to speed up the spark repetition rate to something above audible frequencies. But this idea was soon overtaken by two techniques which proved successful for nearly a decade, before the arrival of the triode valve oscillator made them obsolete. These were the multipole rf alternator, developed by Tesla and Alexanderson, and the Poulsen oscillatory arc, based on Duddell's 'singing arc' of 1900. The arc conduction process in hydrogen gas interacts with a series LC



Picture courtesy Barratts

*David Sarnoff, who, in 1916, elaborated on Lodge's early suggestion for broadcasting and outlined the main technical features of the domestic receiver, or "radio music box" as he called it. Then a manager at the American Marconi Company, he rose to become chairman of its successor, RCA. He is seen here on a visit to London in or about 1925.*



Picture courtesy Marconi

Music recital in 1922 from the 2LO broadcasting studio in London. Miss Olive Sturgess sings into a carbon-granule telephony hand microphone fixed in a laboratory-style clamp, raised to the required height on a decorative pot stand. Also singing is Mr John Huntingdon, while the accompanist in spats is Mr R Stanton Jefferies.

circuit shunted across the electrodes, so that the dc flowing through the arc varies in a periodic manner at rf.

The alternator, typically working at 30kHz, was the more stable and controllable generator, while the arc was smaller and cheaper. But both had the problem that they couldn't be voice-modulated at low level – the carbon granule microphone had to be inserted in the rf power circuits, either directly in series or by inductive coupling. This, of course, limited the rf power that could be generated and hence the transmitter range.

Nevertheless, in 1902 voice transmission was achieved, by Fessenden, and in 1906 demonstrations of radiotelephony were given almost simultaneously in the USA, Germany and Denmark. The advantages of voice communications over telegraphic signals were quickly recognised, particularly by the armed forces, and warships were the first to be equipped.

Civil applications were not far behind, and these were not limited to speech communication. After music had been transmitted on an rf alternator system in 1906 and Caruso had sung over a radio-telephone in 1910, thoughtful people began to realise that the new technology could do somewhat more than convey messages from point to point. After all, music concerts and lectures had already been distributed to subscribers over wired systems, the precursors of cable radio, in the 1890s.

Under the stimulus of the 1914-18 World War, the high-vacuum triode valve was developed into a robust and reliable device, capable of being manufactured in quantity. It now had a good amplification factor and, as a result of

tion at Arlington, USA, to the Eiffel Tower in Paris.

Triode valves were also coming into receivers. The idea of cascading several valve stages to give higher amplification appeared about 1912. Then Armstrong and others showed how the positive feedback principle could be used to reinforce the signal and improve selectivity – the technique of regenerative amplification, later called reaction. Fessenden had demonstrated the heterodyne principle in 1902 (already discovered acoustically as beats or 'resultant tones' by the 18th-century musician Tartini) and this eventually resulted in Armstrong's famous invention of the super-sonic heterodyne or superhet receiver.

The wideband fm which Armstrong eventually developed in the 1930s was the outcome of his and others' early studies of the ever-present static interference on am radiotelephony.

So thermionic valves became the basis of radio-telephony. The extension of point-to-point radio-telephony into broadcasting, already foreshadowed by the isolated experiments mentioned above, came about almost accidentally. Oliver Lodge was the first to suggest the idea of messages being 'broadcast to receivers in all directions', in 1907. Then in 1916 an employee of the American Marconi Company, David Sarnoff, not only predicted broadcasting more firmly but suggested its main elements: transmitting stations and what he called a "radio music box" for the home.

"This device must be arranged to receive on several wavelengths with the throw of a switch or the pressing of a button," said Sarnoff. "The radio music box can be supplied with amplifying tubes and a loudspeaking telephone, all of which can be neatly mounted in a box."

The plan was still under consideration when

Meissner's 1913 positive feedback circuit invention, had emerged as a new means of generating continuous oscillations, though at low frequencies.

Radio-telephone transmitters using valve oscillators began to appear. In 1913-14, speech and music were transmitted from Marconi House in London, and in 1915 the Atlantic was spanned by speech from a naval sta-



The North American end of Marconi's transatlantic radio-telegraphy link was at Glace Bay, Nova Scotia. This signed memento shows operator L R Johnstone transmitting the inaugural message in October 1907, when the commercial service started.

the USA entered the World War in 1917. After the war, American Marconi was merged with General Electric at the insistence of the US government, which required wholly US ownership. The resulting company, with a rich crop of wireless patents to exploit, was the Radio Corporation of America (RCA), and Sarnoff was eventually to become its chairman.

Regular broadcasting actually started from the US station KDKA in Pittsburg. In 1919, Westinghouse, while testing the range of a radio-telephone transmitter, decided to play some gramophone records of music as an alternative to speech. By this time, wireless enthusiasts were building crystal sets. Many of them liked what they heard and wrote to the company asking for more.

As a result, and after a well appreciated broadcast of election results, Westinghouse started regular programmes in 1920, with the idea that KDKA would create a market for radio components and receivers – which in fact it did. In the same year, regular broadcasts began in Europe from The Hague.

In the UK, the accidental birth of broadcasting came about in a similar way. At the Marconi company, the standard method of range-testing transmitters was to read out the names of railway stations from timetables. These were eagerly received by numerous amateur enthusiasts on home-built sets. To

mark the introduction of a new transmitter in 1920, something less mind-numbing was devised – a concert featuring staff and local artistes, with three instrumentalists and two singers.

Despite appreciative letters from hundreds of miles away, the company persisted in its view that the future of radio lay in speech transmission, and that the purpose of broadcasts was to demonstrate the comparative ease with which messages could be exchanged. Accordingly, it substituted news transmissions for the concerts.

In June 1920, however, the firm was persuaded to transmit from Chelmsford a recital by the operatic soprano Melba. One consequence of the success of this event – gramophone recordings were made of the reception at the Eiffel Tower – was that the Post Office withdrew Marconi's experimental licence on the grounds of "interference with legitimate services".

This happened just as commercial broadcasting and the mass production of receivers were beginning to take off in the USA. It was not until 1922 that the Post Office relented and permitted Marconi's to transmit at low power, within its existing half-hour-a-week, a 15-minute programme of speech and music.

The station set up to exploit this opportunity was housed in a wooden hut at Writtle, near Chelmsford. Its call sign was 2MT and

the cheerful informality of its amateur entertainments immediately endeared it to its listeners. Transmission, initially on 700m and later on 400m, was from a 250ft-long four-wire aerial at a height of 110ft.

A second permit quickly led to another station, the more famous 2LO, being established at Marconi House, London. Transmissions, still nominally demonstrations, were permitted first at 100W then later at 1.5kW for one hour daily on 360m.

Before 1922 was out, this had become the British Broadcasting Company, set up at the Post Office's instigation by a consortium of manufacturers including Marconi. Revenue came from a 10% levy on all receivers sold, plus half of the 10-shilling (50p) receiver licence.

Regional stations were set up quickly. The 2LO London station was reconstituted as purpose-built studios at 2 Savoy Hill and a 6kW transmitter on the roof of Selfridge's department store.

The BBC parted company from the set-makers in 1926 and in 1927 became a public-service organisation, established under Royal Charter as the British Broadcasting Corporation.

Throughout all this, spark transmissions continued to be allowed and were not internationally prohibited until 1940. ■

## High-quality circuit boards for Douglas Self's precision preamplifier '96

A high quality double-sided circuit board is available for Doug Self's precision preamplifier, exclusively via *Electronics World*. The board takes the full stereo preamplifier, including all power supply components except the transformer. Its layout is optimised to provide exceptionally low crosstalk.


Co-designed by Gareth Connor, the board is glass-fibre with plated-through holes and roller-tinned. It features solder masking and full component identification. Component lists and assembly notes – containing extra information about the preamplifier – are supplied with each order.

Each board is £59 inclusive of package, VAT and recorded postage. Please include a cheque or postal order with your request, payable to Reed Business Publishing. Alternatively, send your credit card details – i.e. card type, number and expiry date. Include delivery address in the order, which for credit card orders must be the address of the card holder. Add a daytime telephone and/or fax number if available.

Send your order to Electronics World Editorial, PCBs, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Alternatively fax us on 0181 652 8956 or e-mail: jackie.lowe@rbp.co.uk. Credit card details can be left on the answering machine on 0181 652 3614. Please allow 28 days for delivery.
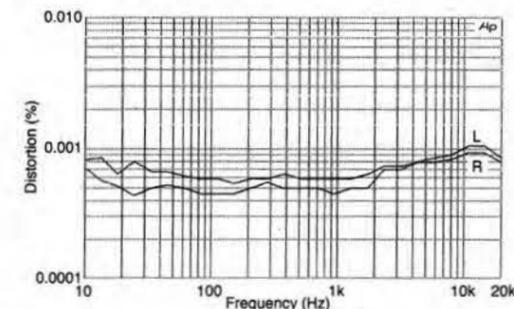
### Features of Douglas Self's precision preamplifier

- Very low noise and distortion.
- Moving-coil – sensitivity switchable 0.1 or 0.5mV,  $\pm 0.05$ dB RIAA accuracy.
- Moving-magnet input with  $\pm 0.05$ dB RIAA accuracy, 5V rms sensitivity.
- Three 150mV line inputs.
- One dedicated compact-disc input.
- Tape-monitor switch.
- Active-balance control.
- Tone control – switch defeatable – with  $\pm 10$ dB range.
- Tone control treble and bass frequencies variable over 10:1 range.
- Active volume control for optimal noise/headroom and enhanced interchannel matching.
- Intelligent relay muting on outputs.
- CD input sensitivity 1V rms.



Distortion curve of Douglas Self's high-performance preamplifier, excluding disc-input stages, shows distortion below 0.001%.

# Interfacing with C


ELECTRONICS  
WORLD  
+ WIRELESS WORLD
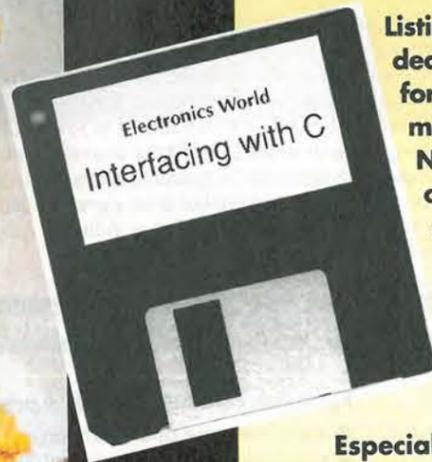
## Interfacing with




Howard Hutchings

Without an engineering degree, a pile of money, or an infinite amount of time, the revised 289-page **Interfacing With C** is worth serious consideration by anyone interested in controlling equipment via the PC. Featuring extra chapters on Z transforms, audio processing and standard programming structures, the new **Interfacing with C** will be especially useful to students and engineers interested in ports, transducer interfacing, analogue-to-digital conversion, convolution, digital filters, Fourier transforms and Kalman filtering. Full of tried and tested interfacing routines. Price £14.99.



Listings on disk - over 50k of C source code dedicated to interfacing. This 3.5in PC format disk includes all the listings mentioned in the book **Interfacing with C**. Note that this is an upgraded disk containing the original **Interfacing With C** routines rewritten for Turbo C++ Ver. 3. Price £15, or £7.50 when purchased with the above book.

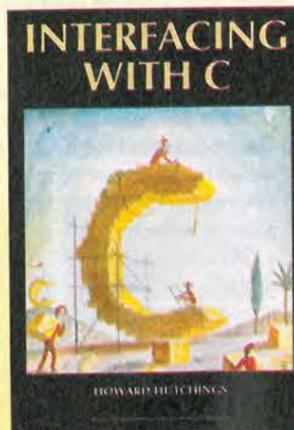Especially useful for students, the original **Interfacing with C**, written for Microsoft C Version 5.1, is still available at the special price of £7.50. Phone 0181 652 3614 for bulk purchase price.



ELECTRONICS  
WORLD  
INCORPORATING WIRELESS WORLD

READER  
INFORMATION  
SERVICE

For more information about any of the products or services in this issue of **ELECTRONICS WORLD**, simply ring the relevant enquiry number.

Enquiry numbers may be found at the bottom of each individual advertisement.

101 102 103 104 105 106 107 108 109  
110 111 112 113 114 115 116 117 118  
119 120 121 122 123 124 125 126 127  
128 129 130 131 132 133 134 135 136  
137 138 139 140 141 142 143 144 145  
146 147 148 149 150 151 152 153 154  
155 156 157 158 159 160 161 162 163  
164 165 166 167 168 169 170 171 172  
173 174 175 176 177 178 179 180 181

Name	_____
Job title	_____
Company Address	_____ _____ _____
Telephone	_____ FEB. _____
Only tick here if you do not wish to receive direct marketing promotions from other companies. <input type="checkbox"/>	

## Newsagent order form

Pass this order form to your newsagent to ensure you don't miss the next issue of *EW*.

To .....  
(name of Newsagent)

Please reserve me the March issue of *Electronics World* - on sale 6th February - and continue to order every month's issue until further notice

Name.....

Address.....

Thank you

### Use this coupon to order

Please send me:

Title	Price	Qty	Total
Enhanced Interfacing with C book @	£14.99	.....	£.....
Enh. Interfacing with C book + disk @	£22.49	.....	£.....
Interfacing with C disk @	£15	.....	£.....
Original Interfacing with C book @	£7.50	.....	£.....
Postage + packing per order UK	£3.50	.....	£.....
Postage + packing per order Eur	£7	.....	£.....
Postage + packing per order ROW	£12	.....	£.....
Total			£.....

Name

Address

Phone number/fax

Make cheques payable to Reed Business Publishing Group Ltd  
Or, please debit my Master, Visa or Access card.

Card type (Access/Visa)      Card No  
Expiry date

Mail this coupon to Electronics World Editorial, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS, together with payment. Alternatively fax full credit card details with order on 0181 652 8956 or e-mail them to jackie.lowe@rbp.co.uk. Orders will be dispatched as quickly as possible, but please allow 28 days for delivery.

# Subscribe today!

Guarantee your own personal copy each month

## Save on a 2 year subscription

ELECTRONICS  
WORLD  
INCORPORATING WIRELESS WORLD

# Subscribe today!

Guarantee your own personal copy each month

## Save on a 2 year subscription

ELECTRONICS  
WORLD  
INCORPORATING WIRELESS WORLD



# CIRCUIT IDEAS

Do you have an original circuit idea for publication? We are giving **£100** cash for the month's top design. Additional authors will receive **£35** cash for each circuit idea published. We are looking for ingenuity in the use of modern components.

## WIN A TTI PROGRAMMABLE BENCH MULTIMETER

"High accuracy, resolution and bandwidth - performance beyond the capability of hand-helds"



This high-performance bench multimeter could be yours in exchange for a good idea. Featuring a dual display, the 4.5-digit 1705 multimeter resolves down to 10µV, 10mΩ and 0.1µA and has a basic dc accuracy of 0.04%. Frequency measured is 10Hz to 120kHz with an accuracy of 0.01% and resolution to 0.01Hz. Capacitor and true rms measurements are also featured.

Recognising the importance of a good idea, Thurlby Thandar Instruments will be giving away one of these excellent instruments once every six months. This incentive is in addition to our monthly £100 'best circuit idea' award and £25 awards for each circuit published.

## £100 WINNER

### Loop aerial cuts through the noise

To allow the reception of long and medium waves in an environment polluted with computers and television receivers, this loop aerial and its


amplifier, working with a 1m square maximum loop, reduce noise to the background level of the bands. The business end of the circuit

is formed by the input transformer and fet source follower; at long- and medium-wave frequencies, fets show low noise figures at 10kΩ source impedance. Transistor  $Tr_2$  bootstraps out the gate/drain capacitance of  $Tr_1$ , the gate/source capacitance being low due to the follower configuration.

Maximising input transformer ratio while keeping shunt capacitance low results from the use of a toroid (Cirkit 55-40001 or Fair-Rite 26-43540001) with two primary turns of audio screened cable with the screen grounded at one end, and 40 on the secondary.

The op-amps form a low-noise amplifier driving a 50Ω cable and the other components form a phantom power supply, although a local supply could be used, in the 25-40V range.

J A Burnill  
Camberley, Surrey

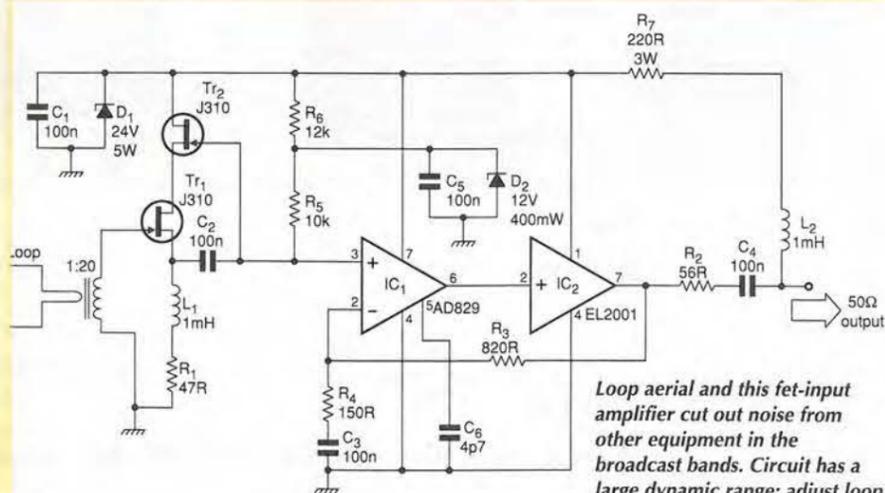

Loop aerial and this fet-input amplifier cut out noise from other equipment in the broadcast bands. Circuit has a large dynamic range; adjust loop size to give required sensitivity.

## ANCHOR SUPPLIES Ltd

The Cattle Market Depot  
Nottingham NG2 3GY. UK  
Telephone: +44 (0115) 986 4902/  
+44 (0115) 986 4041 24hr answerphone  
Fax: +44 (0115) 986 4667



## Micro Video Cameras

Following our recent Readers Offer for the 721-S Micro Camera many readers have contacted us asking about other items in our range of Micro Cameras and Security Surveillance equipment.



We are SOLE AUTHORISED IMPORTERS of the entire range of Cameras and Video Surveillance equipment produced by the world's leading manufacturer. ALL items in the range carry a full 12 Months Guarantee. If you would like to receive our comprehensive catalogue of Cameras and associated equipment please send a large SAE with 48p postage, marked "Camera Catalogue"



Here is a sample of the available stock.

- A-721-S Micro Camera 32mm x 32mm ... £85
- A-721-P Micro PIN-HOLE Camera ... 32mm x 32mm ... £85
- A-921-S Camera with AUDIO ... 30mm x 30mm ... £95
- A-1211 C/CS Mount Camera ... 110mm x 60mm x 60mm ... £110
- A-521 Micro Cased Camera 43mm x 48mm x 58mm ... metal cased ... £120
- 6001-A High Resolution COLOUR Cameras (420 lines) ... 0.45 lux ... £210
- Outdoor Camera Housings ... Aluminium ... £45
- Camera Mounting Brackets ... Universal Mounting ... £5.95
- Camera Switchers ... for up to 8 Cameras ... £85
- Auto Record Controllers ... Allow NORMAL VHS Videos to operate like professional Time Lapse or Security Recorders ... £75
- QUAD-1 Multi Vision Processors ... Digital Freeze ... Quad Pictures etc £275
- QUAD-2 Full COLOUR QUAD version of QUAD-1 ... £695
- SCI ... SCANNER ... 350° PAN ... Automatic / Manual ... £105
- IRA ... Infra Red Illuminator for "Total Darkness Surveillance" ... 20m range ... £125
- VMS-1 .. Video Motion Sensor ... replaced alarm sensors with totally electronic video monitoring system that detects changes in the video signal .. £175
- C/CS Format lenses ... Premium 3.6mm = £22.50 Superior 8mm = £27.50

PLEASE NOTE:

AS A CONTINUED SPECIAL OFFER ALL THE ABOVE CAMERA AND ACCESSORY PRICES INCLUDE VAT AND CARRIAGE TO UK ADDRESSES

### SPECIAL OFFER

New and Boxed 14" COLOUR MONITORS..Models 1412 24V DC operation @ 2.2A..Twin Composite Video Inputs (75ohm BNC) Black steel case...Supplied with a pair of trailing leads for DC connections. Very easy to convert to 240V operation by adding a 240V / 24V supply either internally or externally. 30 Day Warranty.

NEW CONDITION  
Circuit Diagram available..request at time of ordering  
**ONLY £125.00 INCL VAT**  
Courier delivery to UK addresses = £12.25)

VHS Video Players...Front Loading VHS Decks..12V operation. Rear Panel 2.6mm DC socket for power. Play..FF..RW..Stop Controls with the addition of REPEAT facility which allows the tape to be rewound and replayed time and time again. Video / Audio Outputs via Phono Sockets


AS-NEW Condition..  
**ONLY £75 INCL VAT**  
(Courier delivery to UK addresses = £8.75)

OPEN 6 DAYS A WEEK  
Mon-Fri 9am-6pm Sat 8am-4pm  
NO APPOINTMENTS NEEDED. CALLERS ALWAYS WELCOME

All Prices are Ex VAT & Carriage  
All items are Fully Tested with Verified Calibration  
and carry our Unique 30 Day Un-Conditional Warranty



## One transistor fm microphone

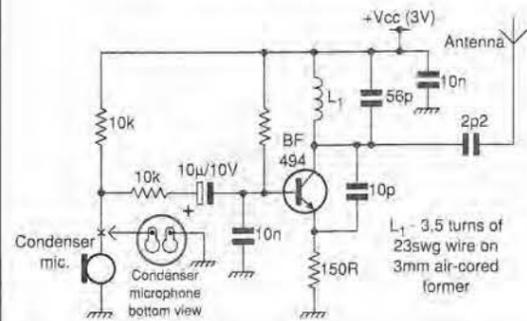


Running from two penlight cells, this sensitive fm microphone has a transmission range of around 6m. Lengthening the antenna could increase this to 30m. Due to  $L_1$ , the BF494 transistor oscillates in addition to amplifying the signal from the piezo microphone. Once the circuit is operational, tune an fm radio around 100MHz until the noise quiets.

**R J Gorkhali**  
Kathmandu  
India

In this fm microphone, one transistor doubles as an audio amplifier and transmitter oscillator.

## Write protect for 386EX architectures

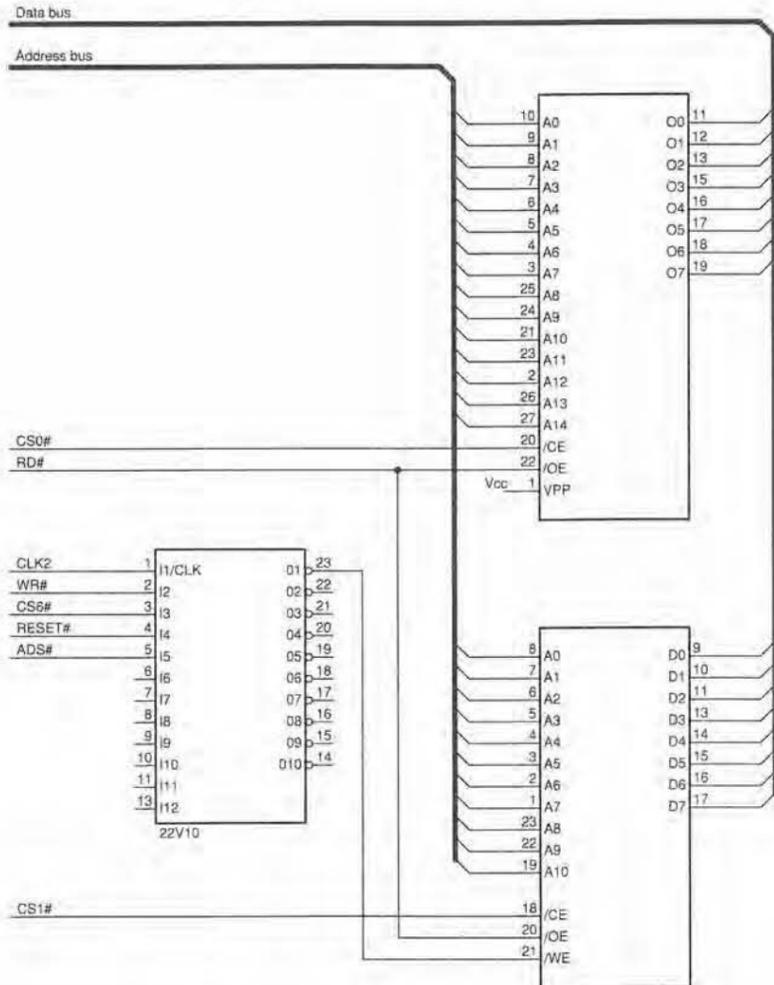

In this example, part of a circuit for write protecting memory in 386 systems, /CS1 enables the eeprom, /CS1 enables the ram and /CS6 defines the write-protect address range.

In system designs using an embedded processor, it is often useful to include a 'write-protect' circuit for part of the read/write memory. This may be to safeguard configuration parameters, or simply for debug purposes.

However, it is difficult to predict exactly which areas of ram will need to be protected, and ideally the protected area should be configurable by software, so the design can be problematic.

This circuit is a mechanism for a versatile write-protect system which may be implemented in almost any design using the Intel 386EX processor. It can often be included without adding to the component count.

Intel's 386EX processor includes a powerful chip select unit (csu) which may be programmed to provide fully decoded address blocks for memory or i/o devices; it has seven independent outputs, so most designs will not need to use them all.

In addition, the csu allows more than one output to be active during any bus cycle, although this would normally be avoided to prevent address-decode clashes. It is therefore a simple matter to gate the processor's /WR line with a spare csu output before feeding it to the memory subsystem. This csu output is then programmed to be active only when a block of ram which is to be write protected is simultaneously addressed (in the normal way) by a different csu output.

The write protected area may then be set to cover any memory address range, subject only to the limitations of the csu itself, and it may be enabled, disabled and reprogrammed entirely by software.

The current version of the 386EX (the 'B' step) has a number of deficiencies, one of which is an insufficient address hold time after /WR is removed. A common method of overcoming this problem is to use a PAL to foreshorten the /WR pulse, often in conjunction with a simple state machine to track the processor 'T' states. Feeding a spare csu output into this PAL is then a convenient way of implementing the write protect mechanism described above.

The diagram shows a simplified extract from a circuit which embodies this function. No doubt the scheme could be adapted to suit other processors which include a similar chip-select unit.

**Roy Bunce**  
Blandford Forum  
Dorset

### COMPUTER ICs

TMS 9900NL-40 PULLS	£20 ea
S9900 NEW AMD EQUIVALENT	£30 ea
MC6802 PROCESSOR	£2 ea
AM27C020-125L1 SURFACE MOUNT EPROM USED/WIPE	£1.50
P8271 BBC DISC CONTROLLER CHIP EX EQPT	£25
2817A-20 (2K X 8) EPROM ex eqpt	£2
D41256C-15 256K X 1 PULLS	9 FOR £5
P8749H MICRO	£5
DB751-8 NEW	£4
MK48202-20 ZERO POWER RAM EQUIV 6118LP	£10
USED 4184-15	£0.25
BBC VIDEO ULA	£10
8051 MICRO	£1.25
FLOPPY DISC CONTROLLER CHIPS 1771	£16
FLOPPY DISC CONTROLLER CHIPS 1772	£17.50
68000-8 PROCESSOR NEW	£5
HD8384-8	£5
27C4001 USED EPROMS	£4
27C2001 USED EPROMS	£2.50
1702 EPROM NEW	£6
2114 EX EQPT	50p
4416 EX EQPT	70p
6264-15 8K STATIC RAM	£1.50
Z80A SIO-O	£1.25
7128 3 1/2 DIGIT LCD DRIVER CHIP	£2 ea
2816A-30 HOUSE MARKED	£2
USED TMS2323JL	£2.50
2708 USED	£2
HM6167LP-8	£5p
68000-10 PROCESSOR	£6
8255-5	£1.40
2114 CMOS (RCA 5114)	£1.20
WD19C550-PC UART	£5
ZN427E-8	£4
Z27C56-26 USED	£1.50
PAL20L8-25 9000 ex stock	£2
M28F010-150K1 FLASH EPROM PLCC 500 ex stock	£15
LM091LN LCD DISPLAY	£15

### REGULATORS

LM338K	£6
LM323K 5V 3A PLASTIC	£3
LM350K (VARIABLE 3A)	£3
78H12ASC 12V 5A	£5.90 ea (£1.30)
LM317H TOS CAN	£1
LM317T PLASTIC TO220 variable	£1
LM317 METAL	£2.20
7812 METAL 12V 1A	£1
7805/12/15/24	30p
7905/12/15/24	30p
78HGASC + 79HGASC REGULATORS	£30 ea
LM123 ST93 5V 3A TO3 REGS	£3 ea
UC352AN SWITCHING REGULATOR IC	60p
78L12 SHORT LEADS	10c/£1
LM2950AC25.0	80p

### CRYSTAL OSCILLATORS

307 2KHZ 1M000000 1M8432 2M457600 3M6864 4M000000	
5M000000 5M6800 5M760000 6M000000 6M1440 7M000000	
3M372800 7M5 8M000000 9M21610000 10M 12M000000	
14M318 14M3818 16M00 17M625600 18M000000 18M432 19M050	
19M2 19M440 20M000 20M0150 21M676 22M1164 23M587	
24M0000 25M1748 25M175 25M1889 27M + 36M 27M00000	
28M322 32M000000 32M0000 *S/MOUNT 33M3330 35M4816	
38M100 40M000 41M539 42M000000 44M444 44M900 44M0	
48M00000 50M00 55M000 56M00920 64M000000 66M667 76M1	
80M0 84M0	£1.50 ea

### CRYSTALS

32K768 1MHz 1M8432 2M000 2M1432 2M304 2M4576 3M000	
3M2768 3M400 3M579545 3M5864 3M600 3M6864 3M9216	
4M000 4M190 4M194304 4M2056 4M3614 4M608 4M9152 5M000	
5M0688 6M000 6M041952 6M200 6M400 7M37280 8M000 8M06400	
8M48 8M83256 8M8670 9M3750 9M8304 10M240 10M245	
10M368 10M70000 11M000 11M052 11M98135 12M000 12M5	
13M000 13M270 13M675000 14M000 14M318 14M7450 14M7456	
15M0000 16M000 17M6250 18M432 20M000 21M300	
21M400M15A 24M000 25M000 26M996 27M045 27M095 OR	
27M145 BL 27M145 YW 27M195 GN 28M4696 30M4696 31M4696	
31M4696 34M368 36M75625 36M7875 36M78125 36M79375	
36M80625 36M81875 36M83125 36M84375 38M900 48M000	
51M05833 54M1916 55M000 57M7415 57M7583 69M545 69M550	
96M000 111M600 114M6	£1 ea

### TRANSISTORS

MPSA42	10c/£1
MPSA92	10c/£1
2N2907A	10c/£1
BC487, BC488	10c/£1
BC107 BCY70 PREFORMED LEADS	
full spec	£1 £4/100 £30/1000
BC557, BC238C, BC308B	£1.30 £3.50/100
2N2907 PLASTIC CROPPED	£1.15 £4/100
BC548B SHORT LEADS	£3/100 £20/1000

### POWER TRANSISTORS

OC29	£2 ea
2SC1520 sim BF259	2c/£1 100c/£22
TIP 141/£1 ea TIP 112/42B	2c/£1
IRF620 TO-220 6A 200V	2c/£1
SE9301 100V 10A DARL SIM TIP121	2c/£1
BD680	4c/£1
PLASTIC 3055 OR 2955 equiv 50p	100c/£35

### TEXTOL ZIF SOCKETS

28 PIN USED	£3
ZIF 64 WAY SHRINK DIP SKT TEXTOL 264-1300-00 1.78mm	
SPACING ON PCB WITH 4MHz RESONATOR	£10
SINGLE IN LINE 32 WAY CAN BE GANGED FOR USE WITH ANY DUAL IN LINE DEVICES	COUPLING SUPPLIED 2c/£1.50

**KEYTRONICS**  
TEL. 01279-505543  
FAX. 01279-75765  
E-MAIL. keytronics@btinternet.com  
PO BOX 634  
BISHOPS STORTFORD  
HERTFORDSHIRE CM23 2RX  
http://www.btinternet.com/~keytronics

### MISCELLANEOUS

AAA NICADS HI CAPACITY 360mH/HR 3 CELL PACK	£3
25A SOLID STATE RELAY 240V AC ZERO VOLTS SWITCHING	£10
XENON STROBE TUBE	£1.60
Narrow angle infra red emitter LED55C	2c/£1
UM61 116M-2L surface mount 1000 available	£1
CNY65 OPTO ISOL 3000 available	50p
OPTO ICS also available TLP550 TLP666GF	
68 way PLCC SKT 100 available	£1 each
100 wa PLCC SKT 100 available	£1.50 each
1250pF POSTAGE STAMP COMPRESSION TRIMMER	£1
LM324 (Quad 741)	4c/£1
MINIATURE FERRITE MAGNETS 4x4x3mm	10c/£1
TL071 LO NOISE OP AMP	5 for £1
TL061 OP AMP	4 for £1
47000u 25v SPRAGUE 36D	£3.50 (£2)
12 way diil sw	£3 for £1
10NF 63V X7R PHILIPS SURFACE MOUNT 100K available	
SWITCHED MODE PSU 40 WATT UNCASED QTY. AVAILABLE +5V 5A, +12V 2A, 12V 500mA FLOATING	£30/4000
220R 2.5W WIREWOUND RESISTOR 60K AVAILABLE	£9.95 (£2)
CMOS 555 TIMERS	2c/£1
2/3 AAA LITHIUM cells as used in compact cameras	2c/£1.50
PASSIVE INFRA RED SENSOR CHIP + MIRROR + CIRCUIT	£2 ea
ELUOCARD 98-WAY EXTENDER BOARD	£10 ea
290 x 100mm	
DIN 41612 26-WAY A/B/C SOCKET PCB RIGHT ANGLE	£1.30
DIN 41612 26-WAY A/B/C SOCKET WIRE WRAP PINS	£1.30
DIN 41612 64-WAY A/C SOCKET WIRE WRAP PINS	£1
DIN 41612 64-WAY A/C PLUG PCB RIGHT ANGLE	£1
DIN 41612 64-WAY A/B SOCKET WIRE WRAP (2-ROW BODY)	£1
BT PLUG + LEAD	3c/£1
MIN. TOGGLE SWITCH 1 POLE c/o PCB type	5c/£1
LCD MODULE sim. LM018 but needs 150 to 250V AC for display 40 x 2 characters 182 x 35 x 13mm	£10
6-32 UNC 5/16 POZI PAN SCREWS	£1/100
NUTS	£1.25/100
PUSH SWITCH CHANGEOVER	2c/£1
RS232 SERIAL CABLE D25 WAY MALE CONNECTORS	
25 FEET LONG, 15 PINS WIRED BRAID + FOIL SCREENS	£5.90 ea (£1.30)
AMERICAN 2/2 PIN CHASSIS SOCKET	2c/£1
WIRE ENDED FUSES D.25A	30c/£1
NEW ULTRASONIC TRANSDUCERS 32KHZ	£2/pr
POWER SMALL CYLINDRICAL MAGNETS	3c/£1
8NC 500HM SCREENED CHASSIS SOCKET	2c/£1
SMALL MICROWAVE DIODES AE1 OC1028A	2c/£1
D.I.L. SWITCHES 10-WAY £1 8-WAY 80p 4/5/6-WAY	80p
180VOLT 1 WATT ZENERS also 12V & 75V	20c/£1
MIN GLASS NEONS	10c/£1
RELAY 5V 2-pole changeover looks like RS 355-741 marked STC 47WBot	£1 ea
miniature CO-AX FREE PLUG RS 456-071	2c/£1
MINIATURE CO-AX PCB SKT RS 456-093	2c/£1
PCB WITH 2N2646 UNIJUNCTION WITH 12V 4-POLE RELAY	£1
400 MEGOHM THICK FILM RESISTORS	4c/£1
STRAIN GAUGES 40 ohm foil type polyester backed	
ballo grid alloy	£1.50 ea 10c/£1
ELECTRET MICROPHONE INSERT	2c/£1
Linear Hall effect IC Micro Switch no 613 SSA sim RS 304-267	£2.50 100c/£1.50
1 pole 12-way rotary switch	4c/£1
AUDIO ICS LM380 LM386	£1 ea
555 TIMERS £1 741 OP AMP	6c/£1
ZN414 AM RADIO CHIP	80p
COAX PLUGS nice ones	4c/£1
COAX BACK TO BACK JOINERS	3c/£1
INDUCTOR 20µH 1.5A	5c/£1
1.25 inch PANEL FUSEHOLDERS	3c/£1
STEREO CASSETTE HEAD	£2
MONO CASS. HEAD £1 ERASE HEAD	50p
THERMAL CUT OUTS 50 77 85 120°C	£1 ea
THERMAL FUSES 220°C/121°C 240V 15A	5c/£1
TRANSISTOR MOUNTING PADS TO-5/TO-18	£3/1000
TO-3 TRANSISTOR COVERS	10c/£1
PCB PINS FIT 0.1 inch VERO	20c/£1
TO-220 mica + bushes	10/50p 100c/£2
TO-3 mica + bushes	10c/£1
IEC chassis plug filter 10A	£3
POTS SHORT SPINDLES 2K5 10K 25K 1M 2M5	4c/£1
40k U/S TRANSDUCERS EX-EQPT NO DATA	£1/pr
LM234Z CONST. CURRENT I.C.	£1
BNC TO 4MM BINDING POST SIM RS 455-961	£1
MIN PCB POWER RELAYS 10.5V COIL 6A CONTACTS 1 pole c/o	
BANDOLIERY COMPONENTS ASSORTED Rs, Cs, ZENERS	£5/1000
LCD MODULE 16 CHAR X 1 LINE (SIMILAR TO HITACHI LM10)	£5
OPH126A 10K OPTO ISOLATOR	£1.35 ea 100c/£1 ea
'LOVE STORY' CLOCKWORK MUSICAL BOX MECHANISM	£1 ea
MADE BY SANKYO	£1 ea
Telephone cable clips with hardened pins	500c/£2
10,000µF 16V PCB TYPE 30mm DIA x 31mm	10 for £1
10µF 10 BEAD TANTALUM	10 for £1
EC CHASSIS FUSED PLUG B-LEE L2728	3c/£1
2A CERAMIC FUSE 1.25 inch QB	10c/£1
46 WAY IDC RIBBON CABLE 100 FOOT REEL	£5 + CARR
20mm PCB FUSEHOLDER	5c/£1
IEC CHASSIS FUSED PLUG B-LEE L2728	3c/£1
ASTEC MODULATOR VIDEO + SOUND UM1287	£2.25
BARGRAPH DISPLAY 8 RED LEDS	£1.50
NE567 PHASE LOCKED LOOP	2c/£1
NE564	£1
TL084	4c/£1
IR2432 SHARP 12 LED VU BAR GRAPH DRIVER	£1.25
10A CORCOM MAINS RFI FILTER EX. EQPT	£2 100p + £1.50
8 OHM MYLAR CONE LOUDSPEAKER 55mm DIA x 10mm	DEEP
AD592AN Temperature sensor TO-92 package with 1.5m lead	2c/£1

### DIODES AND RECTIFIERS

A115M 3A 600V FAST RECOVERY DIODE	4c/£1
1N5407 3A 1000V	8c/£1
1N4148	100c/£1.50
1N4004 SD4 1A 300V	100c/£3
1N5401 3A 100V	10c/£1
1N5819RL 20K Ex stock	1000 + 10p
BA158 1A 400V fast recovery	100c/£3
BY254 800V 3A	6c/£1
BY255 1300V 3A	6c/£1
6A 100V SIMILAR MR751	4c/£1
1A 600V BRIDGE RECTIFIER	4c/£1
4A 100V BRIDGE	3c/£1
6A 100V BRIDGE	2c/£1
10A 200V BRIDGE	1c/£1.50
25A 200V BRIDGE £2	10c/£18
25A 400V BRIDGE £2.50	10c/£22
BY287	10c/£1
KBP304 BRIDGE REC 3A 400V	4c/£1

### SCRs

PULSE TRANSFORMERS 1.1 +1	£1.25
MEU21 PROG UNIJUNCTION	3c/£1

### TRIACS

NEC TRIAC AC08F 8A 600V TO220	5c/£2 100c/£30
TXAL225 8A 500V 5mA GATE	2c/£1 100c/£35
BTA 08-400 ISO TAB 400V 5mA GATE	80p
TRAL2230D 30A 400V ISOLATED STUD	£5 ea
TRIAC 1A 800V T3C381T 16k AVAILABLE	5 FOR £1 £15/100

### PHOTO DEVICES

HI BRIGHTNESS LEDS COX24 RED	5c/£1
SLOTTED OPTO-SWITCH OPG0A OPB815	£1.30
2N5777	50p
TL181 PHOTO TRANSISTOR	£1
TL188 INFRA RED LED	5c/£1
4N25 OP12852 OPTO ISOLATOR	50p
PHOTO DIODE 50P	6c/£2
MEL12 (PHOTO DARLINGTON BASE N/O)	50p
LEDS RED 3 or 5mm 12c/£1	100c/£6
LEDS GREEN OR YELLOW 10c/£1	100c/£6
FLASHING RED LED 5mm 50p	100c/£40
HIGH SPEED MEDIUM AREA PHOTODIODE RS651-995	£10 ea
OPTEK OPB745 REFLECTIVE OPTO SENSOR	£1.50
RED LED - CHROME BEZEL	3c/£1
OPH110B HI VOLTAGE OPTO ISOLATOR	£1
MC0 3020 OPTO COUPLED TRIAC	2c/£1

### STC NTC BEAD THERMISTORS

G22 220R, G13 1K, G23 2K, G24 20K, G54 50K, G25 200K, RES 20°C	
DIRECTLY HEATED TYPE	£1 ea
FS228W NTC BEAD INSIDE END OF 1 inch GLASS PROBE RES 20°C 200R	£1 ea
A13 DIRECTLY HEATED BEAD THERMISTOR 1k res. ideal for audio Wien Bridge Oscillator	£2 ea

### CERMET MULTI TURN PRESETS 3/4 inch


10R 20R 100R 200R 250R 500R 2K 2K2 2K5 5K 10K 47K 50K 100K 200K 500K 2M	50p ea
---	--------

### IC SOCKETS

14/18/20/24/28/40-WAY DIL SKTS	£1 per TUBE
8-WAY DIL SKTS	£2 per TUBE
32-WAY TURNED PIN SKTS	3 for £1
SIMM SOCKET FOR 2 x 30-way SIMMS	£1

### POLYESTER/POLYCARB CAPS

350V 10% 250V AC X2 RATED PHILIPS TYPE 330	£20/100
100n 220n 330n 500n 1µF 10µF	20c/£1 50c/£2
10n/15n/22n/33n/47n/66n 10mm rad	100c/£3.50
100n 250V radial 10mm	100c/£3
100n 600V Sprague axial	5 for £1
2µ 2 160V rad 22mm, 2µ 2 100	

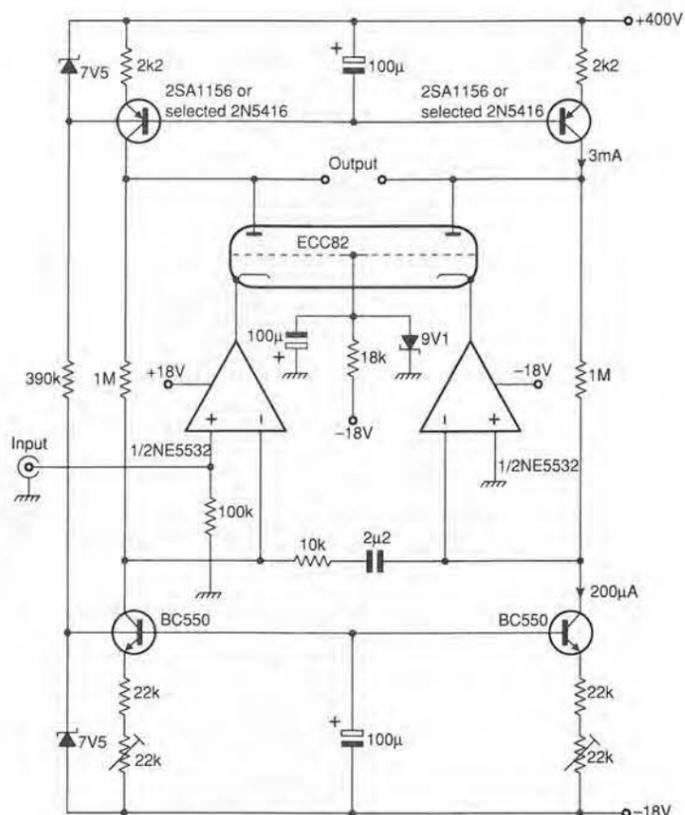

### Hybrid, high-voltage audio amplifier

A high-voltage audio output to drive an electrostatic headphone comes from a double-triode stage, itself fed by op-amps. The whole thereby combines the robustness of valves and the high gain of op-amps. Common-grid drive to the triodes is the chief peculiarity, chosen to allow the output from the op-amps to be summed for the output and to exploit the greater stability of the configuration over the more usual common-cathode drive – all without loss of bandwidth. Current sources supply triode loading and carry all the current, the output therefore being protected against short-circuits. Further current sources for bias avoid the need for a split supply; trim for half the 400V on each output. Output is 200V rms into 200kΩ – or greater from 1V rms input, although gain can be altered by varying the 10kΩ feedback resistor.

**Paolo Palazzi**  
Cervignano  
Italy

High-voltage audio for headphone drive. Variations include a differential input using the non-inverting input of the right-hand op-amp and the use of bigger triodes, with an adjustment in bias voltage.

### Simple time-out saves batteries

The circuit described here can help you avoid the problem of drained cells in a battery-powered device by breaking the current off after a certain time, determined by an RC-circuit.

The circuit is very simple, with only a few components. Transistor  $Tr_1$ , which breaks the battery current, is a BS250 p-type enhancement-mode mosfet. When power is turned on, its gate is connected to a negative potential through  $Tr_2$  – a BS170 n-type enhancement mosfet.

Transistor  $Tr_2$  turns on when voltage across its gate is positive. This voltage comes from an RC circuit formed by capacitor C and the resistor  $R_2$ . At turn on, the capacitor has no charge. During operation, it is charged through  $R_2$ . Gate voltage of  $Tr_2$  goes down as the capacitor charge

increases. When the gate voltage reaches the enhancement value of the transistor, it switches off and can no longer supply gate voltage to  $Tr_1$ . Pull-up resistor  $R_1$  connects its gate to source potential and  $Tr_1$  breaks the current.


The circuit is released by momentarily closing the switch. The capacitor is discharged and  $Tr_2$  has its gate voltage again.  $Tr_2$  switches to on-state and gives gate  $Tr_1$  a voltage, making it conductive again.

Operating voltage of the circuit ranges from 5V to 25V. The device is well suited for use with common 9V batteries. Operating time of the circuit is approximately twice the time constant  $R_2C$  of the circuit, component values shown giving an on time of around a minute. Different values of the enhancement voltage of  $Tr_2$  also influence on the operating time. Component values need to be selected if accurate timing is needed.

Transistor BS250 has an  $R_{DS(on)}$ -value of approximately 4Ω, causing a voltage drop in the circuit when loaded. Loading current should not exceed 50mA. Larger loads can be handled by using a more robust transistor instead of BS250. For instance, IRF9530 can easily reach loading currents up to 2A, if desired.

Operating time can be lengthened at any time by simply closing the switch. The capacitor loses its charge and the operating time is renewed to its starting value.

**Rae Perälä**  
Helsinki  
Finland

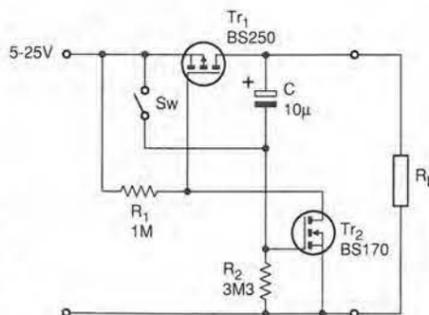

Simple, time-delayed cut-out avoids the problem of inadvertently draining batteries.

### The Headphone Amplifier Box

Balanced or unbalanced microphone or line input to headphone output

Professional portable units operating from an internal PP3 battery or external DC supply



\* Precision transformerless balanced input \* Bridged headphones output drive \* Sensitivity selectable over a wide range of input levels \* Low noise and distortion \* High common mode rejection \* Loop through facility \* Extensive RFI protection

The Balance Box (precision mic/line amplifier) – The Phantom Power Box – The OneStop DIN rail mounting radio frequency interference filter and voltage transient protector for voltage and current loop signal lines

**CONFORD ELECTRONICS**  
Conford, Liphook, Hants GU30 7QW  
Information line 01428 751469 Fax 751223  
E-mail contact@confordelec.co.uk  
Web http://www.confordelec.co.uk/catalogue/

CIRCLE NO. 125 ON REPLY CARD

### ANTRIM TRANSFORMERS LTD

TOROIDAL TRANSFORMERS

- Large standard range from 15VA to 1kVA approved to EN60742 & AS3108
- Custom designs to most international standards from 10VA to 3kVA
- Rapid quotation, design and prototype service Any size production run catered for
- All transformers manufactured at UK factory allowing fast lead times at no extra cost
- 70V / 100V Line, valve output & low noise audio designs available
- Medical designs to IEC601/BS5724 & UL544

AGENTS / DISTRIBUTORS REQUIRED WORLDWIDE

Technical Sales Department, 30 Bramley Avenue  
Canterbury, Kent, CT1 3XW, England

Tel: +44 (0)1227 450810 Fax: +44 (0)1227 764609

BRITISH MADE & BUILT TO LAST

CIRCLE NO. 126 ON REPLY CARD

### The MICRO MODULE

A NEW LOW COST controller that gives you customisation for as little as £95 one off + VAT

and that's just the half of it!!

- FEATURES**
- 16/32 bit 68037 CPU for fast operation
  - Up to 1 Mbyte of EPROM space onboard
  - Up to 512Kbyte SRAM space onboard
  - 32 Kbyte SRAM fitted as standard
  - RS232 serial with RS485 option
  - MODBUS & other protocols supported
  - Up to 22 digital I/O channels
  - 2 timer/counter/match registers
  - I<sup>2</sup>C port or Mbus & Watch dog facilities
  - Large Proto-typing area for user circuits
  - Up to 5 chip selects available
  - Program in C, C++, Modula-2 & Assembler
  - Real Time multitasking Operating System
  - OS9 or MINOS with free run time license option
  - Manufacturing available even in low volumes
  - A full range of other Controllers available

**P.C. 'C' STARTER PACK AT ONLY £295 + VAT**

The Micro Module will reduce development time for quick turnaround products/projects and with the P.C. 'C' Starter pack allow you to start coding your application immediately, all drivers and libraries are supplied as standard along with MINOS the real time operating system all ready to run from power on.

The 'C' Starter pack includes: A Micro Module with 128 Kbyte SRAM, PSU, Cables, Manuals, C compiler, Debug monitor ROM, Terminal program, Downloader, a single copy of MINOS. Extensive example software, and free unlimited technical support all for £295 + VAT.

**CMS** Cambridge Microprocessor Systems Limited  
Unit 17-18, Zone 'D', Chelmsford Road Ind. Est.,  
Great Dunmow, Essex, U.K. CM6 1XG  
Phone 01371 875644 Fax 01371 876077

CIRCLE NO. 127 ON REPLY CARD

### BROADCAST MONITOR RECEIVER 2

150kHz-30MHz



We have taken the synthesised all mode FRG8800 communications receiver and made over 30 modifications to provide a receiver for rebroadcast purposes or checking transmitter performance as well as being suited to communications use and news gathering from international short wave stations.

The modifications include four additional circuit boards providing \*Rechargeable memory and clock back-up \*Balanced Audio line output \*Reduced AM distortion \*Buffered IF output for monitoring transmitted modulation envelope on an oscilloscope \*Mains safety improvements.

The receiver is available in free standing or rack mounting form and all the original microprocessor features are retained. The new AM system achieves exceptionally low distortion: THD, 200Hz-6kHz at 90% modulation –44dB, 0.6% (originally –20dB, 10%).

\*Advanced Active Aerial 4kHz-30MHz \*PPM10 in-vision PPM and chart recorder \*Twin Twin PPM Rack and Box Units \*Stabilizer frequency shifters for howl reduction \*10 Outlet Distribution Amplifier 4 \*Stereo Variable Emphasis Limiter 3 \*Stereo Disc Amplifiers \*PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN –50/+6dB drives and movements \*Broadcast Stereo Coders.

**SURREY ELECTRONICS LTD**  
The Forge, Lucks Green, Cranleigh  
Surrey GU6 7BG  
Telephone: 01483 275997 Fax: 276477

# Hands-on Internet

Following an update on searching the net, Cyril Bateman describes his latest Spice discoveries – among them fully working free evaluation packages.

Internet search engines described in my past columns can be used to locate many different information sources. They are also frequently used for transferring computer software programs, either by an FTP client or your Web browser.

If you know the exact file name you need, FTPSearch in Norway can almost completely automate transfer of files for you. However, if you do not know the file name, the main task becomes one of file name identification.

While Archie, discussed in the April 1996 issue, can perform searches using wildcard characters, and Wais can also help, many users who now rely almost totally on Web browser access do not have these packages. Search engines such as Alta Vista, using appropriate keywords, can be successful, but correctly identifying unknown software file names can prove difficult even for experienced Web surfers.

David Agbamu's home page on Demon<sup>1</sup> is dedicated to helping to solve exactly this problem. By identifying suitable search methods and providing dedicated links, the task is simplified. His page simply and effectively combines the essential information covered in the relevant FAQ documents with direct access to Internet sources – all by simply using your Web browser. David's section on using e-mail for file transfers is particularly helpful, Fig. 1.

If you need to identify a UK or European Business and you prefer to use the conventional Yellow Pages telephone direc-

Fig. 1. A well planned route to Ftp file name identification.

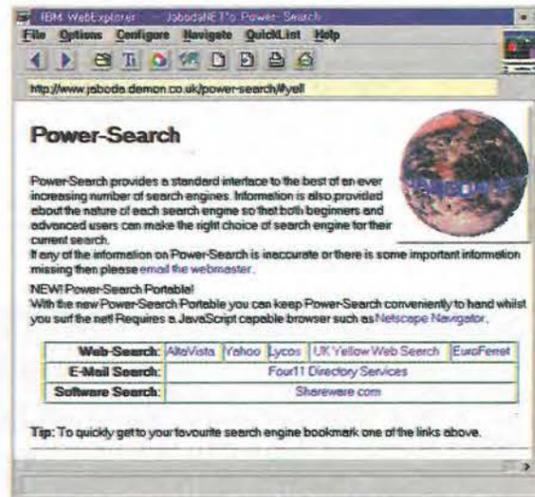
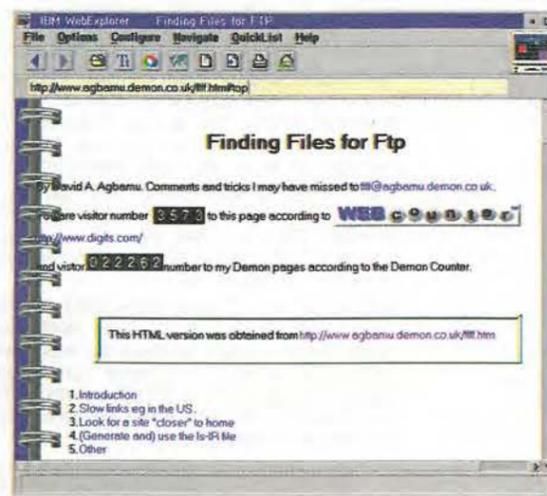


Fig. 2. Choose the most appropriate search method – use Power-Search – a uniquely English approach to Internet searches.

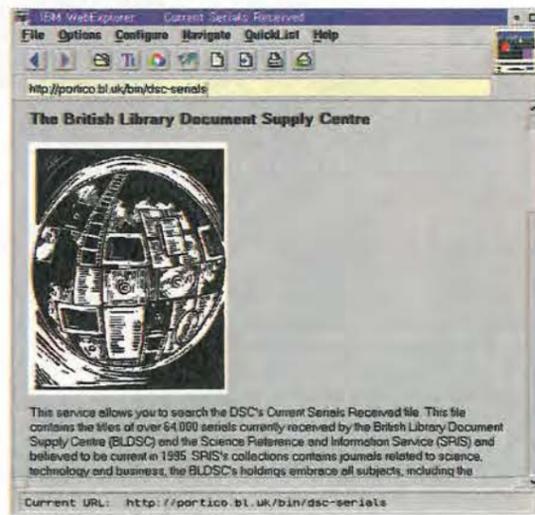


Fig. 3. The British Library Periodicals Holding on-line service. Deeper level searches are chargeable.

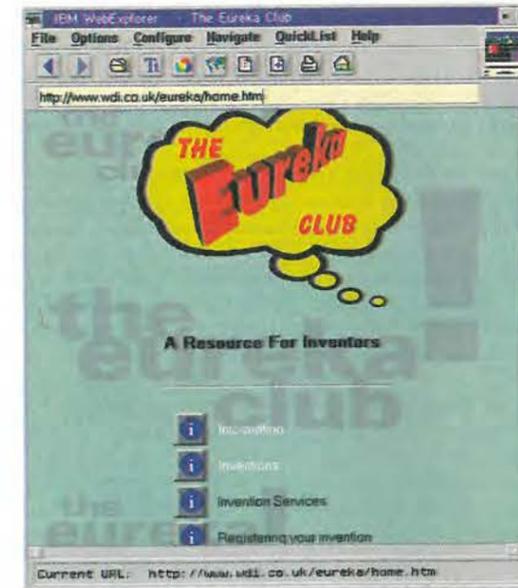


Fig. 4. On-Line Inventors Club. Mix and Match for inventors and manufacturers.

tory approach, Freepages.co.uk<sup>2</sup> or UK.Yellow Web<sup>3</sup> may provide the answer. If not, a good alternative starting point for all Web searches is Power-Search<sup>4</sup>, also on Demon. This page gives a background description for each of the search engines listed, permitting more logical selection as well as direct access, Fig. 2.

Should you need to search for previously published information, the British Library Document Supply Centre<sup>5</sup> and the Science Reference and Information Service hold more than 64,000 serial publications. These comprise journals on science, technology, business and general interest topics, with on-line searching from the British Library Page. Having established that your required document is in these holdings, it can be obtained using the Lexicon easy-order service or, within the UK, rather more economically by request to your local branch library, Fig. 3.

Perhaps you have a new design or invention, but lack the resources to market your idea. The Eureka Club<sup>6</sup>, while acting as an essential support for inventors needing assistance, also forms an on-line meeting place for designers with a new product but no production resources and manufacturers looking for their next marketable product ideas, Fig. 4.

## Simulation software

Symptomatic of the explosion in the use of computer simulations for electronic circuit design, the numbers and variety of simulation software packages constantly increases. While this market remains dominated by derivatives of the Berkeley Spice 2G6 system, newer packages have emerged based on the latest Berkeley Spice 3F5 software core.

An interesting document by Filip Gieszczykiewicz, called 'Where to get Free Spice', can be found on his page at Paranoia.Com<sup>7</sup>. This up-to-date but rather lengthy paper, sub-divided by operating system, gives a good overview of the low-cost Spice-based systems available.

The basic Berkeley Spice software kernel is in the public domain, and therefore inexpensive. Many commercial packages however, being enhanced versions of the basic Spice core, and having improved input and output systems, can become quite expensive.

Spice simulations are only as accurate as the the models used in the simulator. While most analogue integrated circuit

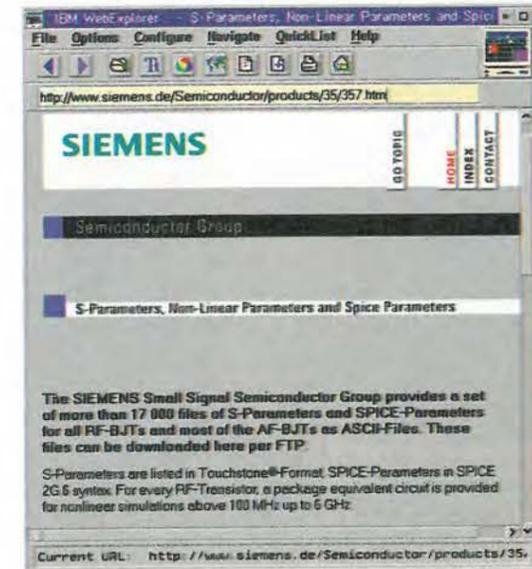


Fig. 5. Siemens Semiconductor Group's extensive model library. Modelling from dc to 6GHz and both Spice and 'S' parameters.

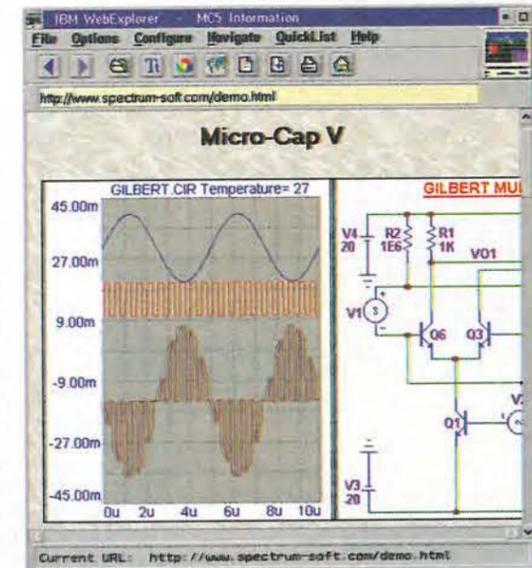


Fig. 6. Download your free evaluation demonstration version of Micro-CapV, a well established alternative pc simulator.

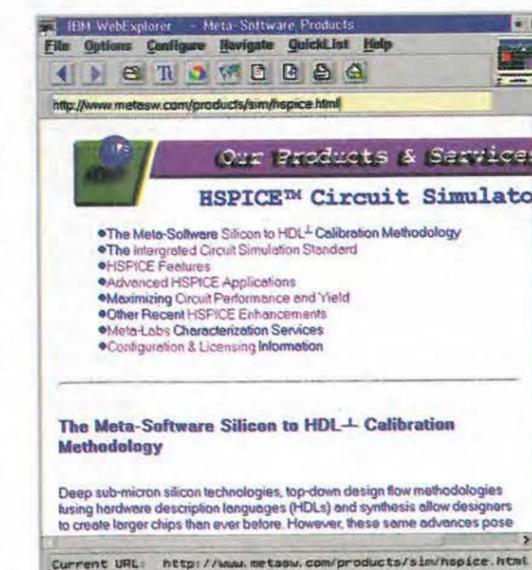


Fig. 7. Serious simulation at an appropriate price.

Fig. 8. One of the new-generation simulators. It costs nothing to try so why not download this software?



Fig. 9. If you are curious about the different variations of the basic Spice kernel, you should read the 'Free SPICE' document and the 'SPICE 3F2' document both by Filipg@paranoia.com.

makers provide free models for their products, models for discrete devices are generally only provided by the simulator software package. Contributing significantly to their cost is the extended model library now required, since older discrete devices must still be supported while new discrete devices continue to be added.

**Spice models**

One major commercial provider of Spice models is Symmetry<sup>8</sup>, part of Interface Technologies. Its *SymLib* library contains more

than 7500 analogue and mixed-signal devices of proven accuracy. Should the device you need not be otherwise available, it also offers a contract modelling service. Symmetry's models can be purchased and downloaded from its Web page.

Siemens Semiconductor Group<sup>9</sup> manufactures both radio and audio-frequency discrete semiconductors. For these, the company offers more than 17,000 files of S-Parameters for downloading in Touchstone format, plus Spice-parameters in Spice 2G.6 format. Details of this service, which comprises four libraries covering both low frequency and above 100MHz package equivalent data sets, are available on its Web page. My browser was allowed to access the page but not allowed to FTP any files, so a dedicated FTP program was used to download my required library, Fig. 5.

When I visited International Rectifier's site<sup>10</sup> in April last year, I only found fifth-generation MosFet models, but a recent return visit provided models also for the company's older generation products.

Comlinear, now part of National Semiconductor, offers Macromodels for its signal-conditioning product line, which can be downloaded from National's pages<sup>11</sup>. These Spice Macromodels are available either by individual device number or as a complete, self-extracting archive library for all types.

**Simulator engines**

Spectrum Software's<sup>12</sup> fifth-generation *Micro-Cap* simulator, *Micro-Cap V*, unlike earlier versions, runs under Windows

and is compatible with standard Spice model libraries. Note, however, that older S3 video card drivers and early Hewlett Packard printer drivers may need to be updated before running *Micro-Cap V*. A free 1.4Mbyte student/demo version can be downloaded from the company's Web page. It shows the result of simulating a Gilbert Multiplier to illustrate the use of *Micro-Cap V*, Fig. 6.

The Meta-Software<sup>13</sup> version of Spice - *HSpice* - claims to be the most accurate commercial circuit simulator available, with the MetaMOS1 (level 28) transistor model giving faster, more accurate simulations. *HSpice*, which is available integrated into major simulation frameworks from Cadence, Viewlogic, Zuken and Mentor, is targeted to the design of silicon integrated circuits including ASICs, as well as more conventional circuit design needs, Fig. 7.

*SIMetrix v1.1* is a Spice-based simulator with schematic editor for Windows 3.x available from Newbury Technical<sup>14</sup>. A free, no-time-limit version, fully working except for user definable menus, etc., called *SIMetrix intro*, can be downloaded from the company's page<sup>14</sup>. While some support for this free version is available by e-mail, those users downloading *SIMetrix intro* are advised to print out the Known Bugs page, Fig. 8.

This month's final Internet simulation offering is *AIM-Spice V2.0*<sup>15</sup>, also available for download in a free student version. This package was developed to provide a more user-friendly interface and take advantage of newer device modelling. It is based on the Berkeley Spice 3.E1 kernel and fully described in the book 'Semiconductor Device Modelling for VLSI', published by Prentice Hall (ISBN 0-13-805656-0), Fig. 9.

Readers curious about the different variations of the basic Spice kernel should read the Free Spice document and the Spice 3F2 document<sup>7</sup>, both by Filipg@paranoia.com. ■

**References**

1. Finding Files for Ftp <http://www.agbamu.demon.co.uk/ffff.htm>
2. Freepages Group Plc <http://www.freepages.co.uk>
3. UK Yellow Web Search <http://www.yell.co.uk>
4. JabodaNET's Power-Search <http://www.jaboda.demon.co.uk/power-search>
5. British Library Document Supply Centre <http://portico.bl.uk/bin/dsc-serials>
6. The Eureka Club <http://www.wdi.co.uk/eureka/home.htm>
7. Where to get Free SPICE [http://www.paranoia.com/~filipg/HTML/FAQ/BODY/F\\_Free\\_Spice1.html](http://www.paranoia.com/~filipg/HTML/FAQ/BODY/F_Free_Spice1.html)
8. Interface Technologies - Symmetry <http://www.i-t.com/engsw/symm/symlib.htm>
9. Siemens Semiconductor Group <http://www.siemens.de/Semiconductor/products/35/357.htm>
10. International Rectifier Corporation <http://www.irf.com/~ir/product-info/spice>
11. National Semiconductor Corporation <http://www.national.com/models/spice/CL/clspice.html>
12. Spectrum Software Corporation <http://www.spectrum-soft.com/demo.html>
13. Meta-Software Incorporated <http://www.metawsw.com/products/sim/hspice.html>
14. Newbury Technology Ltd, <http://www.newburytech.co.uk>
15. AIM-Spice <http://www.ecse.rpi.edu/homepages/trond/aimspice.html>

**THE ORIGINAL SURPLUS WONDERLAND!** THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

**LOW COST PC's - SPECIAL BUY 'AT 286'**  
40Mb HD + 3Mb Ram

LIMITED QUANTITY only of these 12Mhz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!  
Order as HIGRADE 286 **ONLY £129.00 (E)**

**LOW COST 486DX-33 SYSTEM**  
Limited quantity of this 2nd year, superb small size desktop unit. Fully featured with standard simm connectors 30 & 72 pin. Supplied with keyboard, 4 Mb of RAM, SVGA monitor output, 256k cache and integral 120 Mb IDE drive with single 1.44 Mb 3.5" floppy disk drive. Fully tested and guaranteed. Fully expandable  
Many other options available - call for details. **Only £399.00 (E)**

**FLOPPY DISK DRIVES 3 1/2" - 8"**  
5 1/4" or 3 1/2" from only £18.95!  
Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported on your PC).

3 1/2" Panasonic JU363/4 720K or equivalent RFE	£24.95(B)
3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only	£25.95(B)
3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop	£18.95(B)
5 1/4" Teac FD-55GFR 1.2 Meg (for IBM pc's) RFE	£18.95(B)
5 1/4" Teac FD-55F-03-U 720K 40/80 (for BBC's etc) RFE	£29.95(B)
5 1/4" BRAND NEW Mitsubishi MF501B 360K	£22.95(B)
Table top case with integral PSU for HH 5 1/4" Flopp or HD	£29.95(B)
8" Shugart 801/801 8" SS refurbished & tested	£195.00(E)
8" Shugart 810 8" SS HH Brand New	£195.00(E)
8" Shugart 851 8" double sided refurbished & tested	£250.00(E)
Mitsubishi M2894-63 8" double sided NEW	£275.00(E)
Mitsubishi M2896-63-02U 8" DS slimline NEW	£285.00(E)
Dual 8" cased drives with integral power supply 2 Mb	£499.00(E)

**HARD DISK DRIVES**  
End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte drive with industry standard SMD interface, replaces Fujitsu equivalent model. Full manual. Only £299.00 or 2 for £525.00 (E)

3 1/2" FUJII FK-309-26 20mb MFM I/F RFE	£59.95(C)
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv) RFE	£59.95(C)
3 1/2" CONNER CP3044 40mb IDE I/F (or equiv) RFE	£69.00(C)
3 1/2" RODIME R03057S 45mb SCSI I/F (Mac & Acorn)	£69.00(C)
3 1/2" WESTERN DIGITAL 850mb IDE I/F Brand New	£185.00(C)
5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE	£49.95(C)
5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb	£69.95(C)
5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested	£69.95(C)
5 1/4" HP 9754B 850 Mb SCSI RFE tested	£89.00(C)
5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested	£195.00(C)
8" FUJITSU M2322K 160Mb SMD I/F RFE tested	£195.00(E)

Hard disc controllers for MFM, IDE, SCSI, RLL etc. from £16.95

**THE AMAZING TELEBOX**  
Converts your colour monitor into a QUALITY COLOUR TV!!  
TV SOUND & VIDEO TUNER CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers\* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

**DC POWER SUPPLIES**  
Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock  
Call for info / list.

**IC's - TRANSISTORS - DIODES**  
OBSOLETE - SHORT SUPPLY - BULK  
6,000,000 items EX STOCK  
For MAJOR SAVINGS - CALL FOR SEMICONDUCTOR HOTLIST

**VIDEO MONITOR SPECIALS**  
One of the highest specification monitors you will ever see - At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PCs in CGA, EGA, VGA & SVGA modes. BBC COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features. Etched faceplate, text switching and LOW RADIATION MPP specification. Fully guaranteed, supplied in EXCEL-

LENT little used condition. Order as MITS-SVGA  
Tilt & Swivel Base £475  
VGA cable for IBM PC included.  
External cables for other types of computers CALL.  
Only £119 (E)

As New - Used on film set for 1 week only!!  
15" 0.28 SVGA 1024 x 768 res. colour monitors.  
Swivel & tilt etc. Full 90 day guarantee. £145.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors.  
Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed  
Dimensions: W14" x H12 1/2" x 15 1/2" D. 240 V AC mains powered.  
Only £95 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive tumbled black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered.  
Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 KHz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.  
Only £125 (E)

**20" 22" and 26" AV SPECIALS**  
Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

**SPECIAL INTEREST ITEMS**  
MITS. FA3445ETKL 14" Industrial spec SVGA monitors £245  
2Kw to 400 kW - 400 Hz 3 phase power sources - ex stock £90A  
IBM 8230 Type 1, Token ring base unit driver £950  
IBM 53F5001 Token Ring ICS 20 port lobe modules £750  
IBM MAU Token ring distribution panel 8228-23-5050N £95  
AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE £50  
Trend DSA 27 Data Analyser with G703(2M) 64 io £600  
Maxon 6301 Programmable 2 to 22 GHz sweep generator £6500  
HP1650B Logic Analyser £3750  
HP3781A Pattern generator & HP3782A Error Detector £950  
HP APOLLO RX700 system units £1800  
HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £175  
HP3081A Industrial workstation c/w Barcode swipe reader £675  
HP6264 Rack mount variable 0-20V @ 20A metered PSU £1850  
HP54121A DC to 22 GHz 4th channel test set £6650  
HP7580A A1 8 pen HPGL high speed drum plotter £1800  
EG+G Brookdale 95035C Precision lock in amp View Eng. Mod 1200 computerised inspection system £650  
Ling Dynamics 2Kw programmable vibration test system £90A  
Computer controlled 1056 x 560 mm X Y table & controller £1425  
Keithley 590 CV capacitor / voltage analyser £3750  
Racal ICR40 dual 40 channel video recorder system £9500  
Fiskers 45KVA 3 ph On Line UPS - New batts Dec 1995 £2200  
ICI R5030UV34 Cleanline ultrasonic cleaning system £2200  
Mann Tally MT45 High speed line printer £1200  
Intel SBC 486/133SE Multibus 486 system, 8Mb Ram £1200  
Zeta 3220-05 A0 4 pen HPGL fast drum plotters £1450  
Nikon HF-X11 (Ephiphot) exposure control unit £1450  
Motorola VME Bus Boards & Components List. SAE / CALL £550  
Trio 0-18 vdc linear, metered 30 amp bench PSU, New £1950  
Fujitsu M3041R 600 LPM band printer £1250  
Fujitsu M3041D 600 LPM printer with network interface £3750  
Perkin Elmer 2998 Infrared spectrophotometer £950  
VG Electronics 1035 TELETEK Decoding Margin Meter £950  
Andrews LARGE 3.1 m Satellite Dish + mount (For Voyager) £1995  
Sekonic SD 150H 18 channel digital Hybrid chart recorder £750  
TAYLOR HOBSON Talysurf amplifier / recorder £485  
System Video 1152 PAL waveform monitor £300  
Test Lab - 2 mir square quietest acoustic test cabinets £650  
Kenwood 9601 PAL Vectorscope NEW £650

**LOW COST RAM & CPU'S**  
INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. £59.95(A1)  
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DO NOT limit. Complete with data. Order as: XT RAM UG. 256k. £34.95 or 512k £39.95 (A1)

**SIMM SPECIALS**  
1 MB x 9 SIMM 9 chip 120ns Only £16.50 (A1)  
1 MB x 9 SIMM 9 chip 80 ns £21.50 or 70ns £22.95 (A1)  
1 MB x 9 SIMM 9 chip 80 ns £19.50 or 70ns £23.75 (A1)  
4 MB 70 ns 72 pin SIMM - with parity - Only £95.00 (A1)  
INTEL 486-DX33 CPU £55.00 INTEL 486-DX66 CPU £69.00 (A1)  
FULL RANGE OF CO-PROCESSOR'S EX STOCK - CALL FOR LIST

**RANS & BLOWERS**  
EPSON DO412 40x40x20 mm 12v DC £7.95 10 / £65  
PAPST TYPE 612 60x60x25 mm 12v DC £8.95 10 / £75  
MITSUBISHI MMF-D6D12DL 60x60x25 mm 12v DC £4.95 10 / £42  
MITSUBISHI MMF-08C12DM 80x80x25 mm 12v DC £5.25 10 / £49  
MITSUBISHI MMF-09B12DM 92x92x25 mm 12v DC £5.95 10 / £53  
PANCRAKE 12-3.5 92x92x18 mm 12v DC £7.95 10 / £69  
EX-EQUIP AC fans. ALL TESTED 120 x 120 x 38 mm spec 110 110 or 240 v. £6.95. 80 x 80 x 38 mm spec 110 or 240 v. £5.95  
IMHOF B26 1900 rack mtl 3u x 19" Blower 110/240V NEW £79.95  
Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL

**19" RACK CABINETS**  
Superb quality 6 foot 40U  
Virtually New, Ultra Smart  
Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, readily punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:  
OPT Rack 1 Complete with removable side panels. £335.00 (G)  
OPT Rack 2 Rack, Less side panels £225.00 (G)

**32U - High Quality - All steel RakCab**

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvres. The top panel may be removed for fitting of integral fans to the sub panel etc. Other features include: fitted castors and floor levelers, pre-punched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal Blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 1/2" W)  
Sold at LESS than a third of makers price !!

**A superb buy at only £195.00 (G)**

Over 1000 racks - 19" 22" & 24" wide  
3 to 44 U high. Available from stock !!  
Call with your requirements.

**TOUCH SCREEN SYSTEM**

The ultimate in 'Touch Screen Technology' made by the experts - MicroTouch - but sold at a price below cost !! System consists of a flat translucent glass laminated panel measuring 29.5 x 23.5 cm connected to an electronic controller PCB. The controller produces a standard serial RS232 or TTL output which continuously gives simple serial data containing positional X & Y co-ordinates as to where a finger is touching the panel - as the finger moves, the data instantly changes. The X & Y information is given at an incredible matrix resolution of 1024 x 1024 positions over the entire screen size !! A host of available translation software enables direct connection to a PC for a myriad of applications including: control panels, pointing devices, POS systems, controllers for the disabled or computer un-trained etc. Imagine using your finger with 'Windows', instead of a mouse !! (A driver is indeed available !!) The applications for this amazing product are only limited by your imagination!! Complete system including Controller, Power Supply and Data supplied at an incredible price of only: £145.00 (B)  
Full MICROTOUCH software support package £145.00 (B)  
and manuals for IBM compatible PC's £29.95 RFE - Tested

**LOW COST RAM & CPU'S**

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. £59.95(A1)  
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DO NOT limit. Complete with data. Order as: XT RAM UG. 256k. £34.95 or 512k £39.95 (A1)

**RANS & BLOWERS**

EPSON DO412 40x40x20 mm 12v DC £7.95 10 / £65  
PAPST TYPE 612 60x60x25 mm 12v DC £8.95 10 / £75  
MITSUBISHI MMF-D6D12DL 60x60x25 mm 12v DC £4.95 10 / £42  
MITSUBISHI MMF-08C12DM 80x80x25 mm 12v DC £5.25 10 / £49  
MITSUBISHI MMF-09B12DM 92x92x25 mm 12v DC £5.95 10 / £53  
PANCRAKE 12-3.5 92x92x18 mm 12v DC £7.95 10 / £69  
EX-EQUIP AC fans. ALL TESTED 120 x 120 x 38 mm spec 110 110 or 240 v. £6.95. 80 x 80 x 38 mm spec 110 or 240 v. £5.95  
IMHOF B26 1900 rack mtl 3u x 19" Blower 110/240V NEW £79.95  
Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL

Issue 13 of Display News now available - send large SAE - PACKED with bargains!

**DISPLAY ELECTRONICS**  
ALL MAIL & OFFICES: Open Mon-Fri 9.00-5.30 Dept WW. 32 Biggin Way Upper Norwood LONDON SE19 3XF  
LONDON SHOP: Open Mon - Sat 9:00 - 5:30 215 Whitehorse Lane South Norwood On 68A Bus Route N. Thornton Heath & Selhurst Park SR Rail Stations  
NEW DISTEL © The Original FREE On line Database Info on 20,000+ stock items! RETURNING SOON!  
ALL ENQUIRIES 0181 679 4414 FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. Scotland surcharge CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved in change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1996. E & O E 0/6

Continued use of the phase/frequency comparator's charge pump system looks questionable in view of the increasing demands for spectral purity, argues Edward Forster.

# Phase comparator purity

The phase/frequency comparator is one of the most widely used components in phase-locked loop technology. It is applied in countless applications, increasing by the day as more radio-oriented products appear.

Although the basic logic within the phase/frequency comparator is simple and well understood, the output interface to the analogue world has several variations.

### The charge pump

The most popular output circuit is the charge pump system comprising transistors  $Tr_1$  and  $Tr_2$ , Fig. 1. Disregarding the logic for the moment, it is only necessary to know that when the phases are synchronised, the output on the up/down lines consists purely of short duration pulses, normally coincident, which occur as the comparator resets in every cycle.

The duration of the reset pulses only depends on propagation delays in the logic. These can be very short compared to the reference clock period. Resulting output for these

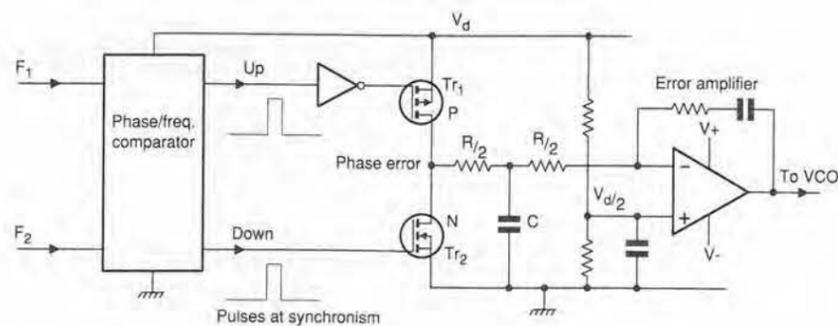


Fig. 1. Conventional phase/frequency comparator with charge-pump output.

short pulses is highly dependent on the matching of the transistors.

A perfectly complementary combination would probably avoid some of the variations in comparator gain which occur near zero error. This type of output circuitry is tri-state with the third state being a high impedance state. Presumably, this fits in with the fact that the logic also has three stable states. The fourth state, in which both up and down lines are high, is inhibited by reset.

The output logic circuitry sounds more like a digital engineer's idea of analogue design. However, the main outcome is that at phase synchronism the output is essentially in the high impedance state almost continuously except for a momentary clamping of the output ideally to  $V_d/2$ .

Figure 1 shows a typical error amplifier and active filter for this approach which has to be protected against the fast pulses, usually by splitting the input resistance and adding a capacitance to ground. But the extra delay due to the filter  $R/2, C$  must not be made so large as to affect loop stability.

The capacitor associated with the charge pump is the integrating capacitor in the active filter and not this  $C$ . The dc reference for the amplifier is  $V_d/2$  so that the loop will settle at zero phase error. Reference frequency suppression is then at a maximum and the gain of the comparator is  $V_d/4\pi$  volts/radian.

The source impedance seen by the op-amp is sometimes a critical factor in determining the intrinsic noise of the error amplifier and through the loop, noise on the voltage-controlled oscillator, or vco. That is, the vco may have higher close-in noise sidebands than expected or desired.

The differential output, Fig. 2, shows another

er arrangement in which a differential error amplifier is driven by the up/down logic outputs directly so as to subtract them. The fast coincident pulses then become a common mode problem for the amplifier which only additional  $RC$  pre-filtering will satisfactorily resolve. Note that the nominal output/common mode voltage at phase synchronism is either very close to  $V_d$  or ground, depending on the logic polarity. This is often inconvenient in single supply systems.

Overall noise performance tends to be improved by the higher gain,  $V_d/2\pi$  V/rad, and because there is no high-impedance state.

### The resistive combiner

A better approach, which does not rely on the op-amp as a subtractor, is shown in Fig. 3. It is simply to take the up line in Fig. 1 and add it to the inverted down line in a 1:1 resistive network.

At phase synchronism the pulses disappear in the output which is a dc voltage of nominally  $V_d/2$ ; the exact value depends on the high/low saturation voltages of the logic. As before, this is only true when a zero error control loop is used and adjusted correctly. The comparator gain is  $V_d/4\pi$  volts/radian. Figure 3 shows that – in principle at least – infinite reference suppression is possible without filtering and that the interface is inherently suitable for wide band applications. In practice however, additional  $RC$  filtering is still necessary in front of the error amplifier.

Noise performance of the op-amp can be adjusted by setting the resistors  $R$  and the total input resistance to optimum values for the device. At phase synchronism, the output effectively shunts the supply line with a constant resistance of  $2R$ . Since this resistance may at times be quite low, the extra current drain must be considered. It may be seen as a price worth paying.

### See it work

Typical discrete logic would use standard D-type bistable devices, namely positive edge-triggered 7474s with 'clear on low' inputs.

While it is possible to illustrate the waveforms, there is no better way to appreciate the circuit than to make one and test it. The simplest method is to take a signal generator, feed one input directly, and the other via a 100m of RG58, giving a delay of 500ns. By varying the frequency, all possible phase errors can be generated and the response seen.

While the comparator has a nearly  $-360$  to  $+360^\circ$  linear range you will find that it also has a  $360^\circ$  phase ambiguity, which depends on the initial conditions. As a result, it is not useful as an absolute phase comparator but it does excel in phase-locked loop applications.

### Differential resistive combiner

Figure 4 shows a differential comparator which allows the op-amp to reject common-mode noise arising from the supply line,  $V_d$ . This comparator also has twice the gain ( $V_d/2\pi$  volts/radian) of Fig. 3, which means that the effective op-amp noise is halved when

considering its relative effect on the noise sidebands of the voltage-controlled oscillator.

Lock detection is also shown and a complete comparator can be made with just two standard ics. Extended frequency range comparators for special applications are thus very simple indeed.

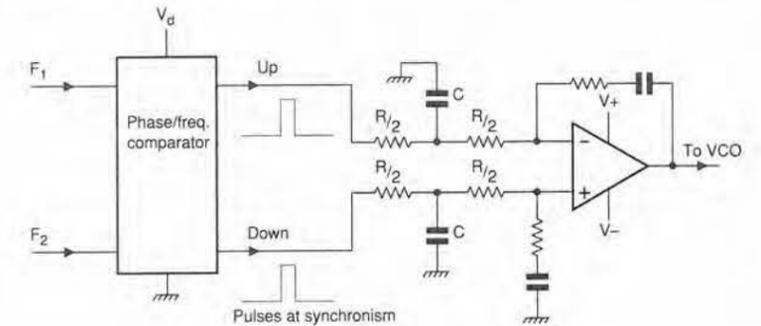


Fig. 2. Using a differential output with the conventional phase/frequency comparator improves noise performance.

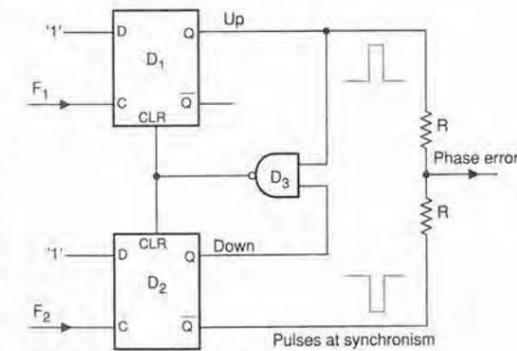


Fig. 3. Phase/frequency comparator with resistive combiner is an improvement over Fig. 2's differential output. In theory, infinite reference suppression is possible.

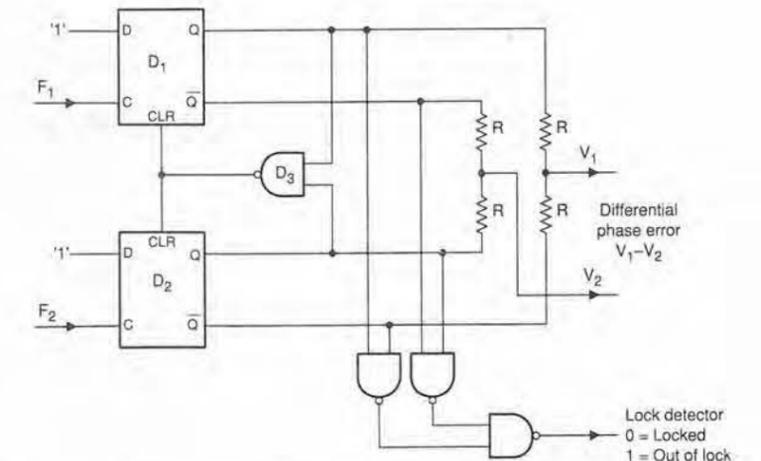


Fig. 4. Differential phase/frequency comparator allows common-mode supply noise rejection and reduces noise due to its higher gain.

**MOONSHINE BIBLE** 270 page book covering the production of alcohol from potatoes, rice, grains etc. Drawings of simple home made stills right through to commercial systems. £12 ref MS3

**NEW HIGH POWER MINI BUG** With a range of 800 metres or more and up to 100 hours use from a PP3. This will be popular! Bug measures less than 1" square! £28 Ref. LOT102.

**SINCLAIR C6 MOTORS** We have a new ones available without gearboxes at £50 ref LOT25

**BUILD YOUR OWN WINDFARM FROM SCRAP** New publication gives step by step guide to building wind generators. Armed with this publication and a good local scrap yard could make you self sufficient in electricity! £12 ref LOT81

**PC KEYBOARDS** PS2 connector, top quality suitable for all 286/386/486 etc £10 ref PCKB. 10 for £65

**TRACKING TRANSMITTER** range 1.5-5 miles, 5,000 hours on AA batteries, also transmits info on car direction and motion! Works with any FM radio. 1.5" square. £65 ref LOT101

**ELECTRIC DOOR LOCKS** Complete lock with both Yale lock and 12v operated deadlock (keys included) £10 ref LOT99

**GALLIUM ARSENIDE FISHEYE PHOTO DIODES** Complete with suggested circuits for long range communications/switching £12 complete.

**SURVEILLANCE TELESCOPE** Superb Russian zoom telescope adjustable from 15x to 60x complete with metal tripod (impossible to use without this on the higher settings) 66mm lens, leather carrying case £149 ref BAR69

**WIRELESS VIDEO BUG KIT** Transmits video and audio signals from a miniature CCTV camera (included) to any standard television! All the components including a PP3 battery will fit into a cigarette packet with the lens requiring a hole about 3mm diameter. Supplied with telescopic aerial but a piece of wire about 4" long will still give a range of up to 100 metres. A single PP3 will probably give less than 1 hours use. £99 REF EP79. (probably not licensable)

**CCTV CAMERA MODULES** 46X70X29mm, 30 grams, 12v 100mA, auto electronic shutter, 3.6mm F2 lens, CCIR, 512x492 pixels, video output is 1v p-p (75 ohm). Works directly into a scart or video input on a tv or video. IR sensitive. £79.95 ref EF137.

**IR LAMP KIT** Suitable for the above camera, enables the camera to be used in total darkness! £5.99 ref EF138

**INFRA RED POWERBEAM** Handheld battery powered lamp, 4 inch reflector, krypton bulb, gives out powerful infrared light! 4 D cells required. £39 ref PB1.

**MONO VGA MONITORS**, Perfect condition, Compaq, 14", 3 months warranty £29 ref MVGA

**SOLAR COOKER GUIDE** Comprehensive plans

**9 WATT CHIEFTAN TANK LASERS** Double beam units designed to fit in the gun barrel of a tank, each unit has two semi conductor lasers and motor drive units for alignment. 7 mile range, full circuit diagrams, new price £50,000? us? £349. Each unit has two gallium Arsenide injection lasers, 1 x 9 watt, 1 x 3 watt, 900nm wavelength, 28vdc, 600hz pulse frequency. The units also contain an electronic receiver to detect reflected signals from targets. five or more units £299 ea. £349 for one. Ref LOT4.

**TWO WAY MIRROR KIT** Includes special adhesive film to make two way mirror(s) up to 60"x20". (glass not included) includes full instructions. £12 ref TW1.

**NEW LOW PRICED COMPUTER WORKSHOP/HI-FIRCB UNITS** Complete protection from faulty equipment for everybody! Inline unit fits in standard IEC lead (extends to 750mm), fitted in less than 10 seconds, reset/test button, 10A rating. £6.99 each ref LOT5. Or a pack of 10 at £49.90 ref LOT6. If you want a box of 100 you can have one for £250!

**RADIO CONTROLLED CARS FROM £6 EACH!!!** All returns from famous manufacturer, 3 types available, single channel (left, right, forwards, backwards) £6 ref LOT1. Two channel with more features £12 ref LOT2.

**THOUSANDS AVAILABLE RING/FAX FOR DETAILS!**

**MAGNETIC CARD READERS** (Swipes) £9.95 Cased with flyleads, designed to read standard credit cards! they have 3 wires coming out of the head so they may write as well? complete with control electronics PCB. just £9.95 ref BAR31

**WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA?** We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14 ref EP74

**PANORAMIC CAMERA OFFER** Takes double width photographs using standard 35mm film. Use in horizontal or vertical mode. Complete with strap £7.99 ref BAR1

**COIN OPERATED TIMER KIT** Complete with coin slot mechanism, adjustable time delay, relay output, put a coin slot on anything you like! TV's, videos, fridges, drinks cupboards, HIFI, takes 50p's and £1 coins. DC operated, price just £7.99 ref BAR27.

**ZENITH 900 X MAGNIFICATION MICROSCOPE** Zoom, metal construction, built in light, shrimp farm, group viewing screen, lots of accessories. £29 ref ANAVLT.

**AA NICAD PACK** Pack of 4 tagged AA nicads £2.99 ref BAR34

**PLASMA SCREENS** 22x310mm, no data hence £4.99 ref BAR67

**NIGHTSIGHTS** Model TZ54 with infra red illuminator, views up to 75 metres in full darkness in infrared mode, 150m range, 45mm lens, 13 deg angle of view, focussing range 1.5m to infinity. 2 AA batteries required. 950g weight. £199 ref BAR61. 1 years warranty

**LIQUID CRYSTAL DISPLAYS** Bargain prices, 16 character 2 line, 99x24mm £2.99 ref SM1623A  
20 character 2 line, 83x19mm £3.99 ref SM2020A  
16 character 4 line, 62x25mm £5.99 ref SMC1640A

**TAL-1 110MM NEWTONIAN REFLECTOR TELESCOPE** Russian. Superb astronomical scope, everything you need for some serious star gazing! up to 169x magnification. Send or fax for further information ref TAL-1, £249

**SOLAR ENERGY/GENERATOR PLANS** For your home, loads of info on designing systems etc £7 ref PV1

**SOLAR COOKERS** Comprehensive guide to building solar powered cookers, includes plans, recipes, cooking times etc £7 ref SBC1

**WOLVERHAMPTON BRANCH  
NOW OPEN AT WORCESTER ST  
W'HAMPTON TEL. 01902 22039**

**CENTRAL POINT PC TOOLS** Award winning software, 1,300 virus checker, memory optimiser, disc optimiser, file compression, low level formatting, backup scheduler, disk defragmenter, undelete, 4 calculators, Dbase, disc editor, over 40 viewers, remote computing, password protection, encryption, comprehensive manual supplied etc £8 ref lot 97 3.5" disks.

**GOT AN EXPENSIVE BIKE?** You need one of our bottle alarms, they look like a standard water bottle, but open the top, insert a key to activate a motion sensor alarm built inside. Fits all standard bottle carriers, supplied with two keys. SALE PRICE £7.99 REF SA32.

## COLOUR CCTV VIDEO CAMERAS, BRAND NEW, CASED, £119.

**PERFECT FOR  
SURVEILLANCE  
INTERNET  
VIDEO CONFERENCING  
SECURITY  
DOMESTIC VIDEO**

**Works with most modern video's, TV's,  
Composite monitors, video grabber cards etc  
Pal, 1v P-P, composite, 75ohm, 1/3" CCD, 4mm F2.8,  
600x682, 12vdc, mounting bracket, auto shutter,  
100x60x180mm, 3 months warranty, 10 or more £99 ea.**



**Check out our  
WEB SITE**

<http://www.pavilion.co.uk/bull-electrical>

**GOT AN EXPENSIVE ANYTHING?** You need one of our cased vibration alarms, keyswitch operated, fully cased just fit it to anything from videos to caravans, provides a years protection from 1 PP3 battery, UK made. SALE PRICE £4.99 REF SA33.

**DAMAGED ANSWER PHONES** These are probably beyond repair so just £4.99 each. BT response 200 machines. REF SA30.

**IBM PS2 MODEL 150Z CASE AND POWER SUPPLY** Complete with fan etc and 200 watt power supply. £9.95 ref EP67

**DELL PC POWER SUPPLIES** 145 watt, +5, -5, +12, -12, 150x150x85mm complete with switch, flyleads and IEC socket. SALE PRICE £9.99 ref EP55

**1.44 DISC DRIVES** Standard PC 3.5" drives but returns so they will need attention SALE PRICE £4.99 ref EP68

**1.2 DISC DRIVES** Standard 5.25" drives but returns so they will need attention SALE PRICE NOW ONLY £3.50 ref EP69

**PP3 NICADS** Unused but some storage marks. £4.99 ref EP52

**DELL PC POWER SUPPLIES** (Customer returns) Standard PC psu's complete with fly leads, case and fan. +12v, -12v, +5v, -5v SALE PRICE £1.99 EACH worth it for the bits alone! ref DL1. TRADE PACK OF 20 £29.95 ref DL2.

**GAS HOBS AND OVENS** Brand new gas appliances, perfect for small flats etc. Basic 3 burner hob SALE PRICE £24.99 ref EP72. Basic small built in oven SALE PRICE £79 ref EP73

**ENERGY BANK KIT** 100 6"x6" 6v 100mA panels, 100 diodes, connection details etc. £69.95 ref EF112.

**PASTEL ACCOUNTS SOFTWARE**, does everything for all sizes of businesses, includes wordprocessor, report writer, windowing, networkable up to 10 stations, multiple cash books etc. 200 page comprehensive manual. 90 days free technical support (01342-

**\*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK**

**BULL ELECTRICAL**  
250 PORTLAND ROAD, HOVE, SUSSEX.  
BN3 5QT. (ESTABLISHED 50 YEARS).  
MAIL ORDER TERMS: CASH, PO OR CHEQUE  
WITH ORDER PLUS £3 P & P PLUS VAT.  
PLEASE ALLOW 7-10 DAYS FOR DELIVERYPHONE ORDERS  
WELCOME (ACCESS VISA, SWITCH, AMERICAN EXPRESS)  
TEL: 01273 203500  
FAX 01273 323077  
E-mail [bull@pavilion.co.uk](mailto:bull@pavilion.co.uk)

326009 try before you buy! Current retail price is £128, SALE PRICE £9.95 ref SA12. SAVE £120!!!

**RACAL MODEM BONANZA!** 1 Racal MPS1223 1200/75 modem, telephone lead, mains lead, manual and comms software, the cheapest way onto the net! all this for just £13 ref DEC13.

**BULL TENS UNIT** Fully built and tested TENS (Transcutaneous Electrical Nerve Stimulation) unit, complete with electrodes and full instructions. TENS is used for the relief of pain etc in up to 70% of sufferers. Drug free pain relief, safe and easy to use, can be used in conjunction with analgesics etc. £49 Ref TEN/1

**PC PAL VGA TO TV CONVERTER** Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and sware. Ideal for laptops or a cheap upgrade. Supplied in kit form for home assembly. SALE PRICE £25 REF SA34

**EMERGENCY LIGHTING UNIT** Complete unit with 2 double bulb floodlights, built in charger and auto switch. Fully cased, 6v 8AH lead acid req'd. (secondhand) £4 ref MAG4P11.

**YUASHA SEALED LEAD ACID BATTERIES** Two sizes currently available this month. 12v 15AH at £18 ref LOT8 and 6v 10AH (suitable for emergency lights above) at just £6 ref LOT7.

**ELECTRIC CAR WINDOW DE-ICERS** Complete with cable, plug etc SALE PRICE JUST £4.99 REF SA28

**AUTO SUNCHARGER** 155x300mm solar panel with diode and 3 metre lead fitted with a cigar plug. 12v 2watt. £8.99 REF SA25.

**MICRODRIVE STRIPPERS** Small cased tape drives ideal for stripping, lots of useful goodies including a smart case, and lots of components. SALE PRICE JUST £4.99 FOR FIVE REF SA26

**SOLAR POWER LAB SPECIAL** You get TWO 6"x6" 6v 130mA solar cells, 4 LEDs, wire, buzzer, switch plus 1 relay or motor. Superb value kit SALE PRICE JUST £4.99 REF SA27

**RGB/CGA/EGA/TTL COLOUR MONITORS** 12" in good condition. Back anodised metal case. SALE PRICE £49 REF SA16B

**PLUG IN ACORN PSU** 19v AC 14w, £2.99 REF MAG3P10

**13.8V 1.9A PSU** cased with leads. Just £9.99 REF MAG10P3

**UNIVERSAL SPEED CONTROLLER KIT** Designed by us for the C5 motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

**PHONE CABLE AND COMPUTER COMMUNICATIONS PACK** Kit contains 100m of 6 core cable, 100 cable clips, 2 line drivers with RS232 interfaces and all connectors etc. Ideal low cost method of communicating between PCs over a long distance utilizing the serial ports. Complete kit £8.99. Ref comp1.

**VIEWDATA SYSTEMS** made by Phillips, complete with internal 1200/75 modem, keyboard, psu etc RGB and composite outputs, menu driven, autodialler etc. SALE PRICE £12.99 REF SA18

**AIR RIFLES** 22 As used by the Chinese army for training purposes, so there is a lot about! £39.95 Ref EF78. 500 pellets £4.50 ref EF80

**VIDEO SENDER UNIT**. Transmits both audio and video signals from either a video camera, videorecorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £25 REF: MAG15 12v psu is £5 extra REF: MAG5P2

**\*MINIATURE RADIO TRANSCEVERS** A pair of walkie talkies with a range up to 2kmin open country. Units measure 22x52x155mm. Including cases and earpieces. 2xPP3 req'd. £30.00 pr. REF: MAG30

**\*FM TRANSMITTER KIT** housed in a standard working 13A adapter! the bug runs directly off the mains so lasts forever why pay £700? or price is £15 REF: EF62 (kit) Transmits to any FM radio

**\*FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

**GAT AIR PISTOL PACK** Complete with pistol, darts and pellets £12.95 Ref EF82B extra pellets (500) £4.50 ref EF80

**6"x12" AMORPHOUS SOLAR PANEL** 12v 155x310mm 130mA. SALE PRICE £4.99 REF SA24.

**FIBRE OPTIC CABLE BUMPER PACK** 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

**MIXED GOODIES BOX OF MIXED COMPONENTS WEIGHING 2 KILOS YOURS FOR JUST £5.99**

**4X28 TELESCOPIC SIGHTS** Suitable for all air rifles, ground lenses, good light gathering properties. £19.95 ref R7.

**GYROSCOPES** Remember these? well we have found a company that still manufactures these popular scientific toys, perfect gift for educational use etc. £6 ref EP70

**HYPOTHERMIA SPACE BLANKET** 215x150cm aluminised foil blanket, reflects more than 90% of body heat. Also suitable for the construction of two way mirror! £3.99 each ref O/L041.

**LENSTATIC RANGER COMPASS** Oil filled capsule, strong metal case, large luminous points. Sight line with magnifying viewer. 50mm dia, 86gm. £10.99 ref O/K604.

**RECHARGE ORDINARY BATTERIES UP TO 10 TIMES!** With the Battery Wizard! Uses the latest pulse wave charge system to charge all popular brands of ordinary batteries AAA, AA, C, D, four at a time! Led system shows when batteries are charged, automatically rejects unsuitable cells, complete with mains adaptor. BS approved. Price is £21.95 ref EP31.

**TALKING WATCH** Yes, it actually tells you the time at the press of a button. Also features a voice alarm that wakes you up and tells you what the time is! Lithium cell included. £7.99 ref EP26.

**PHOTOGRAPHIC RADAR TRAP CAN COST YOU YOUR LICENCE!** The new multiband 2000 radar detector can prevent even the most responsible of drivers from losing their licence! Adjustable audible alarm with 8 flashing leds gives instant warning of radar zones. Detects X, K, and Ka bands, 3 mile range, 'over the hill' 'around bends' and 'rear trap' facilities. micro size just 4.25"x2.5"x.75". Can pay for itself in just one day! £79.95 ref EP3.

**3" DISCS** As used on older Amstrad machines, Spectrum plus3's etc £3 each ref BAR400.

**STEREO MICROSCOPES BACK IN STOCK** Russian, 200x complete with lenses, lights, filters etc very comprehensive microscope that would normally be around the £700 mark, our price is just £299 (full money back guarantee) full details in catalogue.

**WE BUY SURPLUS STOCK FOR CASH**  
BUYERS DIRECT LINE 0802 660377

# NEW PRODUCTS CLASSIFIED

Please quote "Electronics World" when seeking further information

## ACTIVE

### A-to-D and D-to-A converters

**100Msample/s a-to-d converter.** From Strategic Test and Measurement comes *CompuScope 8012*, said to be the world's fastest analogue-to-digital conversion system. It is an IBM-compatible ISA bus card carrying out 12-bit a-to-d conversion in real time at sampling rates up to 100Msample/s in single-channel mode (50Msample/s in dual-channel mode), while maintaining a 60dB s:n ratio. On-board memory stores up to four million samples for later reading by the computer, since the conversion is faster than the bus, and a special 'stacking' feature enables high-prf pulses to be handled. Software supplied with the card allows it to be used as an oscilloscope, complete with storage, analysis, printing and export for spreadsheets, etc. Strategic Test and Measurement Systems Ltd. Tel., 01189 795950; fax, 01189 795951.

### Discrete active devices

**Surface-mount tunnel diodes.** Advanced Control Components' *ACTM Series* of s-m tunnel diode detector modules are meant for use in low-noise video work. Although measuring 4.6mm square and 2mm high, these devices contain full detector circuits with dc return, rf bypass capacitors and the option of input pads for range alteration or protection. In six bands, the series covers 10MHz-4GHz; sensitivity is 800-1000mV/mW with no bias supply needed, at a flatness of 0.2-0.4dB. Thermal stability is 0.015dB from -55°C to 100°C. Anglia Microwaves Ltd. Tel., 01277 630000; fax, 01277 631111.

**Voltage references.** Zetex introduces the *ZRC400/500* voltage references, which are micropower devices for 4V and 5V respectively, operating with extremely low knee currents: *ZRC400* takes a minimum 23µA and the *ZRC500* 25µA, nominal maximum being 5mA, although they will handle much more. The devices attain stable operation in microseconds, need no external stabilising capacitor and will drive capacitive loads. Power dissipation depends on package type, between 330mW and 625mW. Zetex plc. Tel., 0161-627 5105; fax, 0161-627 5467.

### Linear integrated circuits


**Cheap instrumentation amplifier.** *AD622* from Analog Devices is the first in a series of amplifiers at a price to make one think twice about rolling one's own two or three op-amp circuits - particularly as they are said to offer better cmrr (>86dB at a gain of 10), linearity and temperature stability, not to mention taking up less space; voltage noise is 12nV/√Hz at 1kHz. No external passives are needed for a unity-gain amplifier and a single resistor for gains between 2 and 1000. Analog Devices Ltd. Tel., 01932 266000; fax, 01932 247401.

**Jfet op-amps.** Linear introduces the *LT1462/3* (slew rate 0.13V/µs) and *LT1464/5* (slew rate 0.9V/µs) jfet op-amps characterised by input bias currents of 1pA and 0.5pA respectively, together with unity gain, 10nF capacitive load stability. Supply current for the 175kHz *1462/3* versions is 45µA; for the 1MHz *1464/5* types, 200µA. Linear Technology (UK) Ltd. Tel., 01276 677676; fax, 01276 64851.
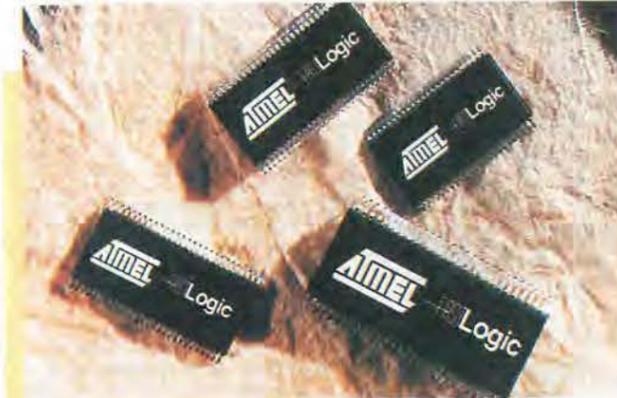
### Microprocessors and controllers

**"Most powerful" 16-bit controller.** Mitsubishi says its *M16C* family of 16-bit microcontrollers is the most powerful yet. The mcu is a compact design, optimised for high-speed, 16-bit operation, its 18mW power consumption and number of on-chip peripherals allowing its use in previously unsuitable designs. Features include efficient C programming, good noise suppression and advanced debugging. On-chip peripherals comprise 126Kbyte of rom, 10Kbyte ram, with dmac, crc, usart, fast a-to-d, d-to-a, eight 16-bit timers and multifunction input/output. Program bugs discovered after masking can be corrected by an interrupt in software. Clock speed is 10MHz, although single-cycle instructions confer a performance that belies the clock speed, being equivalent to 40-60MHz in other mcus. Mitsubishi Electric UK Ltd. Tel., 01707 276100; fax, 01707 278692.

**200MHz embedded VXI controller.** *VX1pc-850/200* is an improved version of National's 133MHz and 166MHz Pentium embedded controllers, this one using the 200MHz Pentium. Simple upgrades are available. All controllers in the series are VXI plug and play types and compatible with software tools such as the company's *LabWindows/CVI* and *LabVIEW*.



### Logic

**"World's fastest" logic family.** Already in production by Atmel Corporation are the first members of what is claimed to be the fastest industry-standard fast CMOS logic devices, the *Atmel Fast Logic (AFL)* series. Speed is down to 2ns and the first circuits in the series are 16-bit devices for 5V, a bidirectional transceiver (*AT16245*), a buffered line driver (*AT16244*), a transparent latch (*AT16373*) and a tri-state register (*AT16646*); 16-bit, 3V units are to come next. Atmel UK. Tel., 01276 686677; fax, 01276 686697.

Prices on all Pentium-based embedded VXI controllers have been reduced by 25%. National Instruments UK. Tel., 01635 523545; fax, 01635 523154.

**Control starter kit.** *EasyStart Kit* by Z-World offers a rapid and simple method of programming embedded microcontrollers in C for beginners, as well as making life easier for experienced programmers. The kit consists of the Windows-based *EasyStart C* software-development suite, including editor, compiler and debugger for a simplified version of standard C, and the *Little Star* controller, which has 16 ttl inputs and 14 high-current digital outputs. It is complete with 9MHz *Z180*, 126Kbyte of eeprom and 32Kbyte of static ram. Also in the kit are lcd and keypad, manual, demo board, power supply and cabling. Z-World. Tel., 001 916 7573737; fax, 001 916 7535141. E-mail <http://www.zworld.com>

### Mixed-signal ICs

**RS232 transceivers.** Analog's *ADM2xxE* 5V RS232 and V28 transceivers, which meet EU emc requirements, protect against ±15kV

of discharge and ±2kV of fast transients. They are meant for modems, laptop and notebook computers and generate electromagnetic emissions to EN55022 and are immune enough to satisfy IEC-1000-4-x. These devices are protected against latch-up, are immune to high rf fields and will work in unshielded enclosures in "electrically harsh environments". There is a number of driver/receiver combinations, in SOIC, SSOP and TSSOP packages. Advanced Micro Devices (UK) Ltd. Tel., 01483 740440; fax, 01483 756196.

**Optical isolators.** *PVI5013R* dual-channel opto-isolated mosfet gate drivers by IR are new members of the *Gen2* range and are the first to offer fast turn-off circuitry. The two channels will drive two devices or can be connected in parallel or series to give higher-current drive for power mosfets or higher voltage for igbts. Input/output isolation is to 3.75kV rms and input-output isolation 1.2kV dc. International Rectifier. Tel., 01883 732020; fax, 01883 733410



Please quote "Electronics World" when seeking further information

**Communications mmic.** NEC has a silicon microwave ic up-converter and quadrature modulator, the  $\mu$ PC8104GR, which has a frequency range of 900MHz-1.9GHz and is intended for digital communications work in lans and telephones. It operates from 2.7-5.5V, taking 28mA at 2V and 0.1 $\mu$ A when power-saving. There is a digital phase meter on chip, with a self-phase compensation facility, and an internal 90° phase shifter, which has a phase error of 0.86° and modulation accuracy of 2.1%. NEC Electronics (UK) Ltd. Tel., 01908 691133; fax, 01908 670290.

### Motors and drivers

**Microstepping driver.** Allegro's SLA7042 multi-chip module controls two-phase stepper motors and provides microstepping operation, containing two independent pwm current-control ics with four nmos fet's in an 18-lead Powertab sil package. It is rated for motor voltages to 46V, peak outputs to 5A and 1.2A continuous. By means of digitally

selected motor-current ratios and linear input reference control, the device may be used as a half-step, full-step and microstep driver, all modes providing smooth drive. No heat sinks are needed. Allegro MicroSystems Inc. Tel., 01932 253355; fax, 01932 246622.

### Optical devices

**Infrared receiver.** New Japan Radio has a new infrared remote-control receiver. In the one three-pin package, there are a photodiode, bandpass filters, a limiter and a preamplifier, so few external components are required. Low pulse-length distortion of 50 $\mu$ s provides a clean signal and noise becomes less of a problem, the metal case helping to increase screening and affording some physical protection. The device will operate at all the common frequencies from 32.75kHz to 56.8kHz and is effective at a range of up to 18m. Young-ECC Electronics. Tel., 01628 810727; fax, 01628 810807.

## PASSIVE

**Chip inductors.** Toko's LL Series of multi-layer chip inductors now come in the 0402 size, as well as in 0805 and 0603 sizes. This new type is suitable for frequencies up to 6GHz, inductance being 1-27nH and Q 50 at 1GHz. The 0805 1.5-470nH size copes with frequencies to 2.5GHz, with a Q of 30 at 800MHz and the 0603 operates to 3GHz, its inductance being 1.2-100nH and Q 30 at 800MHz. Cirkit Distribution Ltd. Tel., 01992 444111; fax, 01992 464457.

### Connectors and cabling

**Backplane connector.** GTK has a new range of backplane connectors to give up to 192 pins for signal or power circuits at 1A or 3A. Matrix connectors are available in 12, 24, 48 and 96mm modules with contacts on a 2 by 2mm grid, the basic 12mm module providing 24 signal contacts or eight power contacts. All can be made as press-fit or through-hole types. GTK (UK) Ltd. Tel., 01344 304123; fax, 01344 301414.

### Pga sockets with preforms.

Robinson Nugent's through-hole pga sockets eliminate the time and expense of a separate soldering operation by the provision of solder rings on the socket's pin tails, the solder preform reflowing into the pcb hole by capillary action. Matching the preform to the board ensures that there is the right amount of solder and that there is no residue and no need for screening or solder paste.



Robinson Nugent (Europe) Ltd. Tel., 01256 842626; fax, 01256 842673.

### Displays

**Loop-powered displays.** Trolex has a range of loop-powered displays with IS certified versions for hazardous areas. Displays can be in panel-mounting, DIN-rail or 19in rack-mounting form, as well as in a field-mount type. They are usable with all standard sensors, process instruments and plcs, all having a loop test facility and direct connection to two-wire process signal loops. Signal processing is to 12-bit accuracy and the four-digit display is an lcd. Trolex Ltd. Tel., 0161 483 1435; fax, 0161 483 5556.

### Hardware

**Emergency stops.** EAO-Highland now provides bright yellow shrouds for its range of emergency stop switches, which meet the requirements of the EU Machinery Directive with regard to inadvertent operation. This new shroud sticks up above the top of the E-stop actuator so that the switch cannot be accidentally operated and it has cut-outs in the side to allow it to be twisted to release it after a genuine fault. EAO-Highland Electronics Ltd. Tel., 01444 236000; fax, 01444 236641.

**Zif bga sockets.** Adding only 2.2mm to the height of a device, Methode's zero-insertion-force ball-grid array socket needs no external hold down and its 25 by 25 array of pins are inspectable. It incorporates heatsink capability and the metal-to-metal connections have a self-inductance of 5nH. A sliding carrier has actuator slots to mate with the bga device, horizontal movement locking and unlocking the device to and from the socket. Methode Electronics Europe Ltd. Tel., 01389 732123; fax, 01389 732777.

**Bobbins, bases.** Coil bobbins and mounting bases for inductors used in switched-mode power supplies and in power conversion can be had from BFI IbeXsa. They are all UL approved, are particularly suitable for development but are also offered in a low "skyline" range for EPC and EFD use. BFI IbeXsa Electronics Ltd. Tel., 01622 882467; fax, 01622 882469.

### Test and measurement

**20MHz oscilloscope.** Goldstar's OS-5020P is a 20MHz, dual-channel, general-purpose oscilloscope for use

### Multi-turn s-m pots. VTM 439

Series of multi-turn, surface-mounted trimmers will handle all soldering processes and meet the requirements of MIL-R-22097, characteristic F. Although the pots have eleven turns, dimensions are the same as those of single-turn devices. Resistance range is 10 $\Omega$  to 2M $\Omega$  at 0.25W and 300V. Surtech Interconnection Ltd. Tel., 01256 51221; fax, 01256 471180.

in education or servicing. Vertical sensitivity is 5mV/div, plus a x5 position, and sweep speed 0.2 $\mu$ s/div with a x10 switch. Combined Precision Components plc. Tel., 01772 654455; fax, 01772 654466.

**Power-off board testing.** Prober II by Huntron automatically tests boards up to 35.6cm square with power switched off, combining analogue signature analysis with a probe, which needs no additional fixture and will cope with pin or test-point spacing of 0.01in, moving in 0.001in increments. Parameters such as  $v$ ,  $i$  and  $f$  are programmable and the Star feature (safe tracker active range) prevents damage to components. There is a ccd camera vision system, which runs under Workstation for Windows, and an output for other test instruments. Martron Instruments, Tel., 01494 459200, fax 01494 535002.

**Multimeters.** MX52B/54B/55B/56B handheld multimeters by Metrix are provided with an RS232 interface with a view to data transmission to a pc or printer. All versions have a 50,000 count display, 0.025% accuracy, true-rms reading and test functions. MX56B is the top version, with its 100kHz bandwidth, timer-counter, audio power measurement (in decibels), indication of mains disturbance and pulse width measurement down to 20 $\mu$ s. Metrix Electronics plc. Tel., 01384 402731; fax, 01384 402732.

**Logic analyser.** Thurlby Thandar's TA4000-80 logic analyser provides synchronous data capture at up to 400MHz on 16 channels with a memory depth of 8Kword. At this speed, timing resolution is 2.5ns, which is usable with 50MHz logic; at 50MHz and below, the number of channels may be increased to 80. Sixteen channels can be displayed simultaneously, with a marker scale, and a group of channels can be defined as a bus and shown on one line of the screen. Triggering may be performed by up to four trigger words ORed together (NOTed, if required). GPIB and RS-232 interfaces are

provided for control and data transfer and there is a Centronics interface for screen dumps to a printer. Thurlby Thandar Instruments Ltd. Tel., 01480 412451; fax, 01480 450409.

### Literature

**Ac/dc power.** Coutant Lambda offers a new guide to the company's range of ac/dc power supplies. The guide is free of charge. Coutant Lambda Ltd. Tel., 01271 865656; fax, 01271 864894.

**Power mosfets.** Toshiba mosfets, which handle 16-1000V and 1A-60A, are described in a new short catalogue, including types for direct drive from 3.3V logic. Toshiba Electronics UK Ltd. Tel., 01276 694600; fax, 01276 694800.

**Surtech.** Surtech Distribution has a new catalogue of hardware such as Cs, Fs, Ls, suppression components, piezo and magnetic products, connectors and switches from people like Murata and Methode. Surtech Interconnection Ltd. Tel., 01256 51221; fax, 01256 471180.

### Navigation systems

**GPS starter pack.** Rockwell offers the Jupiter Starter Pack, which is an easier way to have a GPS application up and running. The unit is based on a Rockwell Jupiter-12 GPS engine to give rapid signal acquisition even in town centres and foliage. It allows the connection of power, antenna, serial cable for a pc port and differential input, with option setting. Software includes Rockwell's Labmon monitor program, the Psion NMEA GPS monitor and other utilities. Telecom Design Communications Ltd. Tel., 01256 332800; fax, 01256 332810.

### Power supplies

**Efficient dc-to-dc converter.** Philips has the TEA1204T 8W dc-to-dc converter ic which is 95% efficient. It is intended for the telephone market, to extend talk and standby time. It will convert the output of a two or three-cell NiCd/NiMH battery or a single-cell Li-ion pack to 3.3V or 5V or the output of a four-cell pack down to 3.3V or 3.6V, configurations that cover virtually all mobile telephones. A combination of pwm and pulse frequency modulation not only confers high efficiency, but allows rapid response to changing loads, so that the device is particularly suited to GSM telephones using burst-mode transmissions. Philips Semiconductors (Eindhoven). Tel., 00 31 40 2722091; fax, 00 31 40 2724825.

**Auto-ptc, ac/dc supply.** Computer Products introduces the NLP65 65W, ac/dc input, open-frame supply, said to be the smallest of its type to have

automatic power-factor correction by an active low-frequency method. The unit complies with European harmonics and flicker standards and is CE marked. Package size is 5 by 3 by 1.26in, this being achieved by means of a new 100kHz switched-mode technique, the high frequency helping to reduce emi. It also uses a patented flyback boost technique to improve efficiency under full load, giving a power sensitivity of 4W/in<sup>3</sup>. Input is universal at 85-264V ac or 120-370V dc and outputs are 5, 12, 15 or 24V dc from the single units, 5/12V or 5/24V from dual types and 5/±12V, 5/±15V from the triple versions. Computer Products, Power Conversion Ltd. Tel., 01494 883113; fax, 01494 883419.

**600W dc-to-dc supplies.** Single-output dc-to-dc power modules in Coutant Lambda's PH600S range provide 330-600W of output at fixed voltages between 3.3V and 48V. Input voltage is 200-400V dc, switching frequency 300kHz and efficiency at 280V dc and maximum output current is 86%. Facilities include remote sensing, overcurrent and overvoltage protection and there is provision for a remote on/off control. Coutant Lambda Ltd. Tel., 01271 865656; fax, 01271 864894.

**Ups.** PowerWorks A30 is a new uninterruptible power supply by Fiskars, designed to replace PowerServer 20 and 30 ranges. This one uses "double conversion on-line technology" to provide reliable protection for computers and workstations, etc. In the 600VA-6kVA range. These units are modular in form for simple installation and offer "plug-and-play" expansion, with four hours backup. An automatic switch takes power directly to the load to handle temporary overload - a feature that removes the need for excessively large ups - and the units use new Lansafe III power management software. Widened input voltage ranges help to conserve battery power. Fiskars Electronics Ltd. Tel., 01734 306600; fax, 01734 305868.

**Lead battery charger.** Mascot's 9319 lead battery charger is over 80% efficient and delivers a current up to 2.4A. Output voltage is adjustable between 11.5V and 15V, with others to special order, and there is a current limiter to prevent overcurrent at the start of the charge cycle. This CE-marked unit is provided with a UK or European mains plug built into the case and a choice of output plug leads. Relec Electronics Ltd. Tel., 01962 863141; fax, 01962 855987.

### Radio communications products

**Telemetry transceivers.** A new range of radio telemetry transceivers by Wood & Douglas enables the

company to offer equipment covering the 130MHz to 500MHz range of frequencies. The T100/200/400 range is meant for use outside Europe, being designed to meet the FCC specification; more stringent demands of European use call for the E100/200/400 alternative range, which meets ETS 300 200, MPT1328 at vhf and MPT1329 at uhf. The T series radios put out 2W at vhf and 1W at uhf, while the European ones emit 0.5W. There are 100 fixed frequencies or 16 reprogrammable ones. Wood and Douglas Ltd. Tel., 01734 811444; fax, 01734 811567.

### Switches and relays

**Audio connectors.** Deltron's range of professional audio connectors, now available from Electrospeed, covers all audio requirements, including phono connectors, loudspeaker types, and a range of circular DIN connectors of the non-latching, latching, insulated, chassis or board mounting versions. Silent Jacks are two-pole jack plugs which eliminate the buzz on insertion, a spring-loaded sleeve switch connecting tip and sleeve connected until the movement of the sleeve on connection reinstates the signal; a two-position collet allows the use of a number of cable diameters. Electrospeed. Tel., 01703 644555; fax, 01703 610282.

**Piezo switches.** Schurter's range of single-key piezo switches are rated to IP40 or IP67 and are proof against water, dust, heat and cold and the brain-dead. Piezo-ceramic discs generate small voltages when touched, the voltages being processed internally to control the normally open switching action. They come in a range of colours and materials including chrome-plated brass, steel or aluminium. Options include special finishes and normally closed versions. Actuating force is 1-3N, contact travel 0.0002mm, switching voltage and current 100V dc, 100mA and breaking capacity 10W. Radiatron Components Ltd. Tel., 01784 439393; fax, 01784 477333.

### Video

**Remote, digital camera.** Active Imaging announces the Mv-NET, a networked digital camera for remote inspection and monitoring. Images are sent to the monitoring station, which is simply a pc running the relevant software, in compressed digital form over telephone lines, lans or GSM/wireless lan. Inside the camera are colour Pal sensor, frame-grabber, processor, disk storage and a network module, all mounted in an enclosure with climate control and/or tilt and pan control; settings are controlled from the monitoring station. The presence of the processor means that the camera can notify the monitor if an

Please quote "Electronics World" when seeking further information



**Loop tester.** A digital loop tester, the Avo Megger LT7, is a hand-held instrument giving a direct reading of prospective short-circuit current and earth fault current, other tests including phase, earth and phase and neutral supply loops, performed at both 110V and 230V socket outlets and distribution boards. For circuits using rcds that would normally be tripped by high current, a low-current test is available. The instrument meets Low-Voltage and EMC directives. PIDA. Tel. and fax., 0756 799737.

alarm is activated and can then be made to record whatever nefarious deed is being perpetrated. Active Imaging plc. Tel., 01628 415444; fax, 01628 415481.

**Pc to tv.** TMC2360 by Raytheon is a single-chip VGA-to-Pal/NTSC video processor, converting analogue rgb+sync. from a pc to broadcast quality NTSC or Pal video; no external memory is needed. The device includes three a-to-d converters, an interface filter, clock processors, reference and three d-to-a converters and a three-line adaptive flicker filter with selectable operating modes. 2001-METL. Tel., 01438 742001; fax, 01438 742002.

**3-D camera.** A three-dimensional portrait camera, the C3D model 2020 by the Turing Institute, consists of a pod with a stereo camera pair and lighting, connected to a pc. In under 0.5s, high-resolution polygon models can be produced in VRML or DXF formats in monochrome or 24-bit colour. Simple operation allows non-technical users to operate the camera. The Turing Institute. Tel., 0141 337 6410; fax, 0141 339 0976.

Please quote "Electronics World" when seeking further information

**Transducers and sensors**

**Touch pad.** A semiconductive touch-pad element by Interlink Electronics Inc. is based on the company's force-sensing resistor, instead of the more often seen capacitive technique. The device requires a slight touch from a finger or stylus and will operate in wet or dry surroundings; it uses only 15% of the power needed by capacitive pads and is more flexible in its use. It is mainly intended for use in notebook computers, where its power saving, enhanced by the inclusion of a sleep mode, and its lower cost compared with that of capacitive devices, makes it an attractive choice. A complete touch-pad using the technique, the *VersaPad oem module*, is now available. Interlink Electronics Inc. Tel., 001 805 484-8855; fax, 001 805 484-8380.

**Current sensors.** Vacuumschmelze GmbH has some new compensation current sensors for current detection in motor control systems or power supplies; they are based on existing designs, but provide greater current ranges in the same shape cases, those now available being for 50A, 100A and 400A. The compensation principle allows the detection of dc as well as ac up to about 100kHz, and enables better linearity than in other

methods. Use of a metallic detector instead of a Hall device reduces offset and drift by an order of magnitude. Vacuumschmelze GmbH. Tel., 0049 61 81/38-26 29; fax, 0049 61 81/38-28 60.

**Pressure sensors.** Lucas's *NPP Series* of piezoresistive, board-mounted pressure sensors are meant for use where small size and resistance to mild corrosive fluids are important. It is the first to appear in a standard SOIC-8 package for automatic handling and insertion, the lead frame design reducing the stress found in surface-mounted ceramic types. Ranges are 0-15, 0-30 and 0-100lb/in<sup>2</sup> (absolute), producing a 60±20mV output on 3V dc. Error due to all causes is less than 0.3% of full scale. Lucas Control Systems Products. Tel., 01535 661144; fax, 01535 661174.

**Humidity sensors.** Self-cleaning, heat refresh humidity sensors in the *HS30* from Steatite are for use in industrial positions where conventional types become clogged and stop working properly. Measurement range is 10% to 95% RH, without condensation, and accuracy ±5% RH at up to 80°C. Power consumption is 1.35W, rated working voltage 1V ac and heat refresh temperature 600°C. Steatite Insulations Ltd. Tel., 0121 643 6888; fax, 0121 643 2011.

**Chip thermistor.** *NTH5G* is an ntc thermistor on an 0805-size chip made by Murata and intended for use in temperature compensation in ics, transistors and oscillators. Its construction provides resistance to humidity; resistance tolerance is ±5%; maximum power 20mW; and B tolerance ±3%. Resistance values in the range 220Ω-100kΩ are available. Murata Electronics (UK) Ltd. Tel., 01252 811666; fax, 01252 811777.

**COMPUTER****Computer board-level products**

**PCI-bus logic analyser.** From RAM Technology comes the half-card *TA200* logic analyser that is simply



plugged into the bus, no probes being needed. It allows users to debug and characterise hardware and software using Windows-based software, which, it is said, gives a good balance between simplicity and analysis capability. An enhanced parallel interface to the host enables very fast data transfer and the board is compatible with all PCI systems including short-form designs. Future developments are taken care of by on-board sram and fpga technology; updates will be available on disk and from a Web site. RAM Technology Ltd. Tel., 01825 761456; fax, 01825 761543.

**Computers**

**Fault-tolerant computer.** Blue Chip's *Icon* series of rack-mounted pcs are available with dual redundant power supplies. Both operate normally but, in the event of a fault, each is capable of handling the full 250W load, an alarm sounds and a led illuminates; this signal can also generate a pop-up alarm, using a watchdog card. Further alarms may be generated by the use of Blue Chip's Pentium cpu card, which monitors the power supply and temperatures. Blue Chip Technology. Tel., 01829 772000; fax, 01829 772001.

**Data communications**

**"World's smallest" transmitter.** An am transmitter by RF Solutions looks like a small ceramic capacitor in that it is encapsulated in epoxy and has two wires; you can have it in a key fob, if you ask properly. It is for short-range telemetry and data comms and things in cars and works over a 30m range. Licence-exempt in the UK, it is approved to MPT1340 and is available for European operation at 433MHz. Power is 5-12V at 2.5mA and the two aforementioned wires are for cmos/ttl data input and output to a whip aerial. RF Solutions Ltd. Tel., 01273 488880; fax, 01273 480661.

**Development and evaluation**

**USB controller emulator.** An emulator for Intel's *82930* universal serial bus controller, which is an Intel 251 micro with an interface to the 12Mb/s bus, is now available. iSYSTEMS *82930* power emulator probe allows real-time execution without wait states, the trace option recording every instruction cycle and

breakpoints being set at any location without slowing execution. C compilers are supported and dos or any of the Windows variants will support the emulator. Clock speed is up to 100MHz and the optional trace buffer is 96bit wide. Changing pods on the emulator adapts it to over 200 8-bit and 16-bit devices. Computer Solutions Ltd. Tel. and fax, 01932 829460.

**32-bit 68020 emulator.** Noral Micrologics's *FlexTools* family of real-time development tools now includes the *Flex-ICE020*, a handheld, non-intrusive, zero-wait-state emulator for all 68020 derivatives up to 33MHz. It is compatible with the company's Windows-based debugger, *Flex*, and has an expandable 32K by 128 real-time, time-stamped buffer for analysis without breaking execution. Dual porting provides emulator ram access for ICE and target to give real-time read and write of system memory. The unit accommodates over 500,000 breakpoints. Noral Micrologics Ltd. Tel., 01254 682092; fax, 01254 680847.

**Computer enclosure.** Completely proof against dust and water, Intek's stainless steel *Armaged Flat Panel Enclosure* takes almost any lap-top pc and any flat panel display to form an industrial pc, terminal or remote monitor, no modifications being needed to allow the pc to be housed. A lap-top pc is opened out flat, its display being viewed through a sealed transparent panel and an external membrane keyboard connected to it for data entry. Cable access is by gland plates and the rear door swings out to provide access for servicing. Intek Electronics Ltd. Tel., 01352 810603; fax, 01352 810403.

**Computer security**

**Computer enclosure.** Completely proof against dust and water, Intek's stainless steel *Armaged Flat Panel Enclosure* takes almost any lap-top pc and any flat panel display to form an industrial pc, terminal or remote monitor, no modifications being needed to allow the pc to be housed. A lap-top pc is opened out flat, its display being viewed through a sealed transparent panel and an external membrane keyboard connected to it for data entry. Cable access is by gland plates and the rear door swings out to provide access for servicing. Intek Electronics Ltd. Tel., 01352 810603; fax, 01352 810403.

# MEASURE wow and flutter

With so much digital audio equipment around, it is easy to overlook the fact that a meter for checking fluctuations in the speed of analogue replay systems is still a useful tool. Christopher Kuni explains how to design such a meter.

Measurement of wow and flutter may seem anachronistic in this age of digitised, locked-in, rock-stable audio reproduction. However, a glance at the display window of any commercial electronics shop will reveal that analogue equipment, with its susceptibility to speed variation, is still very much with us in the form of cassette and even reel-to-reel tape machines, and video recorders. And there are still millions of phonograph disks in existence.

Every turntable and analogue tape transport has measurable speed variations that worsen with age. Checking wow and flutter requires a measuring instrument with reasonable sensitivity and precision; such instruments have become rare and expensive.

The meter described here has proved more than adequate. Its most sensitive range is 0.1% full scale, peak or rms-indicating average. The -3dB points of its frequency response are 0.4Hz and 180Hz. Alternatively, the frequency response weighting curve recommended by the major standards associations can be selected<sup>1</sup>.

Output level of the typical moving-magnet cartridge provides adequate drive without preamplification. Only one simple calibration adjustment is required, or, if rudimentary accuracy can be tolerated, high precision (i.e., repeatability and internal consistency) can still be enjoyed with no calibration at all.

Figure 1 shows the overall system design. A 3 or 3.15kHz signal of a few millivolts to a few

volts rms is amplified, if necessary, to an adequate level before bandpass filtering to remove noise. A zero-crossing detector then squares the signal to further reduce noise effects and to condition the signal for a phase-locked loop, or pll, frequency discriminator.

Demodulated signal passes through a wideband bandpass filter that sets the overall wow-and-flutter frequency response. A weighting filter can be switched in if desired. Peak or average rectifiers can be chosen to drive the storage capacitor, the potential of which is measured by a dc voltmeter.

**Circuit details**

Figures 2-6 show circuit details. All op-amps in the prototype are *TL071*, *-72*, or *-74* types. Similar types will function equally well. Each nor gate is one section of a c-mos 4001.

The input carrier signal sees the high input impedance of *IC*<sub>1</sub>, Fig. 2. Together with its associated components, *IC*<sub>2</sub> provides up to 20dB gain. This gain control circuit, described by R. Williamson<sup>2</sup>, has an approximately exponential characteristic that I find convenient when the expected level of the input signal may cover several orders of magnitude; a circuit with a linear characteristic may, of course, be substituted.

Noise transmission to the pll is reduced by the filter formed by *IC*<sub>3,4,5</sub>. A biquad circuit was chosen because of the flexibility it affords in the choice of Q and gain, and because of its easy

tuning. The main trade-off in the design of this filter is between wow-and-flutter bandwidth and noise rejection. A high-Q filter will limit the upper frequency components of the wow-and-flutter signal but will also reduce the undesirable effect of noise in the input carrier signal.

This consideration is more critical than you may first think. Although the pll demodulator is inherently noise-insensitive, the modulation levels that we are dealing with are extremely low – down to less than 0.01%. Even a pll will show significant relative noise sensitivity at these levels, so line transients, clicks on the test record, rumble in the turntable and other noise signals can spoil measurements.

The bandwidth of a frequency-modulated signal is approximately equal to twice the sum of the frequency deviation and the modulating frequency<sup>3</sup>. For a 3kHz carrier modulated at 1% peak deviation at 200Hz, the bandwidth is thus about 2×(30+200)=460Hz.

For a 200Hz, 1% flutter signal, the system will suffer about a 3dB loss in sensitivity if filter Q is 3000/460=6.5. The values shown in the biquad filter give a Q of about 5.5; this filter, in conjunction with the bandpass filter following the pll, gives an overall system bandwidth of about 180Hz, a reasonable figure. Rejection of the noise in my environment is sufficient to allow measurements near the bottom of the 0.1% range.

Filter Q can be changed, if desired, by changing *R*<sub>a</sub>;  $Q=R_a/33,000$ . With the values shown, gain of the biquad filter is 50 – a value that can be maintained if Q is changed by altering *R*<sub>b</sub>;  $gain=Q(33,000/R_b)$ .

**Further noise rejection**

A zero-crossing detector with hysteresis *IC*<sub>6</sub> further rejects noise. Transistor *Tr*<sub>1</sub> still further squares the 3 or 3.15kHz signal from *IC*<sub>6</sub> and shifts the negative-most level of the square wave to near zero. The diode and associated voltage divider give a dc signal that allows for gain adjustment; gain should be adequate to give a clean square wave at *Tr*<sub>1</sub>'s collector but

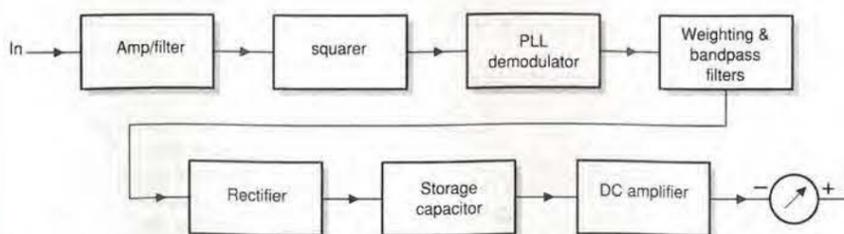


Fig. 1. In this simple sensitive wow-and-flutter, weighting is switch selectable.

**Fm wireless datacomms.** Radiometrix has a transmitter/receiver pair for 40kbit/s data communication over distances of 300m over open ground (75m inside). They are made for 433.92MHz, the transmitter providing +10dBm to ETS 300-220 in Europe and 418MHz, 0dBm to MPT1340 in the UK; the receiver is a double-conversion superhet, which powers up in under 1ms and detects carrier rapidly for power saving. The pcb-mounting modules can be used in analogue or digital communication and will work with helical, loop or whip antennas. Radiometrix Ltd. Tel., 0181 810 8647; fax, 0181 810 8648.


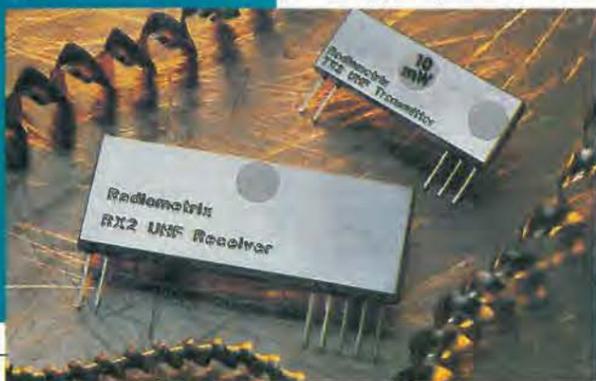


Fig. 2. In the input amplifier and filter section of the wow-and-flutter meter, the gain control has an approximately exponential characteristic.

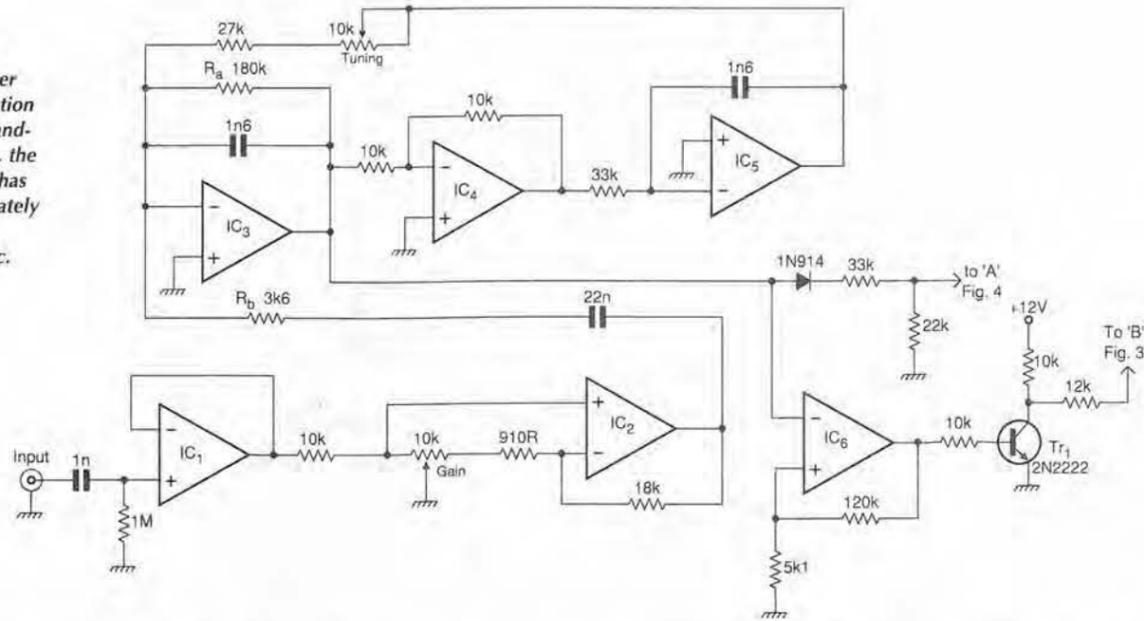

not so high that the biquad filter is overloaded. After  $S_1$  in Figs 3, 4 & 5 is switched to the 'set' position, the biquad is tuned for maximum meter reading and the gain is adjusted for a reading anywhere in the top two-thirds of the meter scale.

The squared carrier signal is sent to the 4046 pll, IC7, Fig. 3. Demodulated output from the pll goes to two filter chains, selected by  $S_2$ , to give either a flat or a weighted bandpass (IC8,9 or IC8,10,11).

Op-amp IC12 provides appropriate gain for 0.1%, 0.3%, or 1.0% full-scale meter deflection; range is selected by  $S_3$ . The 180k resistor at  $S_{1A}$  causes the gain of the IC12 circuit to yield rms-reading average measurement when  $S_1$  is set to 'average'.

The feedback resistors around IC12 are

calculated for a meter movement on which the full-scale values are 10dB apart - i.e., 1.0 on one scale and 3.16 on the other. Use of the less common movement, on which the full-scale values are 1.0 and 3.0, would require recalculation of the resistors. Output is provided for monitoring the detected, filtered signal with an oscilloscope or a spectrum analyser.

The detected signal is sent to a full-wave rectifier consisting of IC13,14, and associated parts, Fig. 4. When  $S_1$  is set for average readings, the low impedance output of IC14 charges and discharges  $C_a$  through  $R_c$  so that the voltage across  $C_a$  is the average value of the rectified signal.

Two series diodes at IC15 limit the voltage to which  $C_a$  can be charged in off-scale conditions such as switching transients. This minimises the

settling time once normal conditions have returned. When  $S_1$  is set for peak readings, IC15 and its feedback diode form a low impedance charging source for  $C_a$  through  $R_d$  but no discharge path; the sole discharge path is then through  $R_c$ .

**Time constants**  
Charge and discharge time constants for average readings and the discharge time constant for peak readings are 7.3 seconds; this somewhat long time constant gives stable readings even for the 1.8s period of 33rev/min wow. The charge time constant for peak readings is 36ms, which is short enough for a significant response to only a few cycles of a 180Hz flutter signal.

Reduce  $R_d$  to decrease the peak-reading time

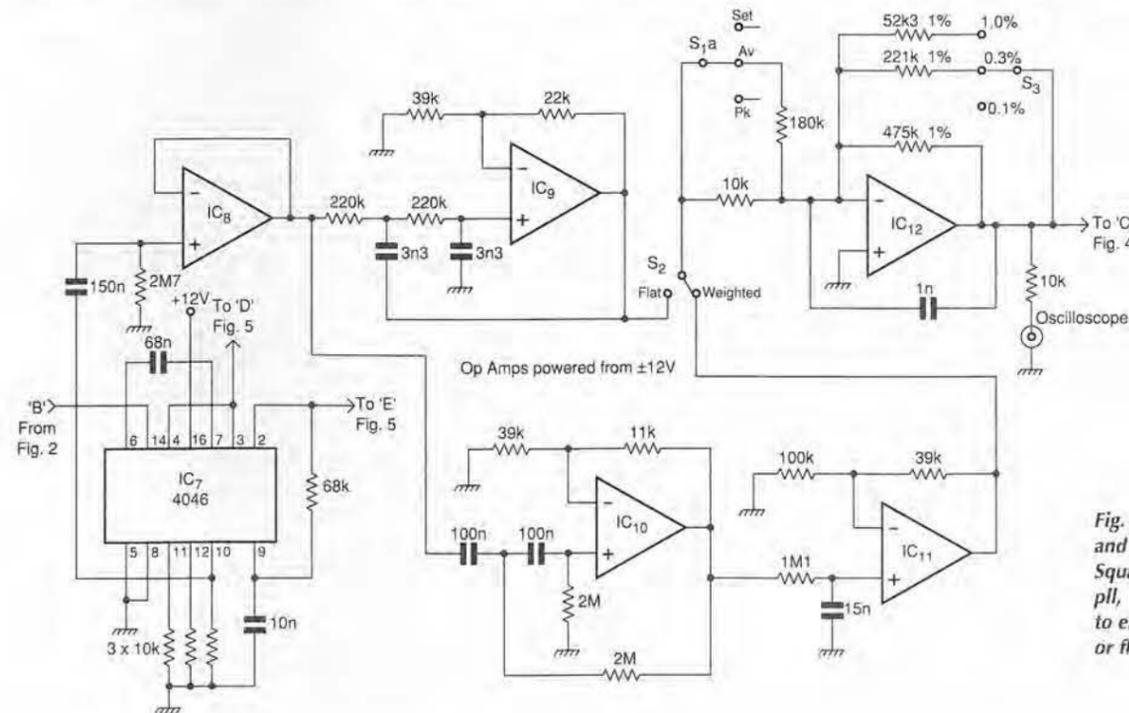


Fig. 3. Phase-locked loop and weighting filter. Squared input feeds the pll, whose output passes to either the weighted or flat filter.

constant at your own risk. Doing so will drastically increase sensitivity to impulse noise.

Charge voltage of  $C_a$  is sensed by IC16, which drives the meter movement. The movement, one that happened to be on hand, has a 200 $\mu$ A full-scale sensitivity and a resistance of 1k3 $\Omega$ . Standards associations specify meter ballistics, but I chose not to attempt to duplicate these specifications electronically. Instead, I subjectively determined a driving impedance for the movement such that the resulting ballistics appeared close to those of a borrowed professional wow-and-flutter meter.

The movement's open-circuit ballistics are on the sluggish side, so a rather high driving impedance proved satisfactory. The resistors associated with IC16 could be changed to accommodate virtually any reasonable meter movement.

Circuit Fig. 5 serves two purposes. First, the logic circuitry detects the lock condition of the pll unambiguously. I wanted the led at  $Tr_2$  to be completely extinguished when the pll is not perfectly locked and to be lighted without flicker when the pll is locked. I also wanted it to follow the state of lock virtually instantaneously. If this situation can be accomplished directly from the 4046 without external logic, I haven't discovered how.

Secondly,  $Tr_3$  discharges  $C_a$  summarily when the pll falls out of lock, preventing wild swings of the meter pointer when the carrier is switched in or out or when the instrument is switched on. This function, plus the series diodes at IC15 in Fig. 4, keeps the meter tamed.


The power supply in Fig. 6 is straightforward. A separate +12V supply for the pll is necessary to prevent 3kHz spikes originating in the pll from leaking into the rest of the circuit.

**Calibration options**  
Several options exist for calibration. When a 200 $\mu$ A, 1.3k $\Omega$  meter movement is used, the simplest is merely to set the calibration potentiometer, Fig. 4, to the centre of its range and forget it. Although absolute accuracy will suffer, the instrument will be perfectly satisfactory for almost all uses. Should you find this approach unacceptable, you have at least three alternatives for accurate calibration.

In the first method, the demodulator-filter sensitivity is measured, and a signal generator is used to inject a simulated flutter signal of amplitude corresponding to 1% into the amplifier preceding the meter rectifiers. Temporarily short the 150nF capacitor at IC8 of Fig. 3. Connect a stable audio generator set to 3kHz to the system input. With  $S_1$  switched to 'set', peak the tuning control and adjust the gain control for a reading in the top two-thirds of the meter scale.

Monitor the generator frequency with a counter and the voltage at the output of IC9 with a digital voltmeter. Vary the generator frequency around 3kHz and tabulate frequency versus the IC9 output voltage. The change in voltage divided by the corresponding percentage change in frequency is the sensitivity of the demodulator and the IC9

Fig. 4. Meter drive and full-wave rectifier. With  $S_1$  set for average readings, low-impedance output of IC4 charges and discharges  $C_a$  through  $R_c$ .

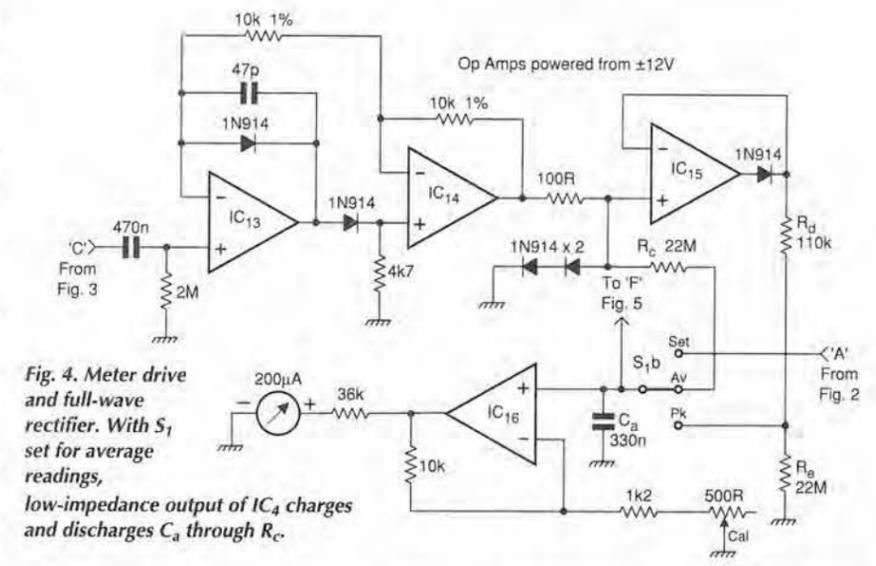

lowpass filter. In my case this was 0.18V per 1.0% frequency deviation.

Remove the short from the 150nF capacitor. Temporarily ground  $Tr_3$ 's base, Fig. 5, and disconnect the pole of  $S_2$  from the pole of  $S_{1A}$  in Fig. 3. Inject a 100Hz or so signal with an amplitude corresponding to 1.0% peak deviation, for example 0.18V peak, into the pole of  $S_{1A}$ . Set  $S_1$  to 'peak' and  $S_3$  to '1.0%'. Adjust the calibration pot for a 1.0 reading. If 3kHz and 3.15kHz are not well within the capture range of the pll, trim the 68nF capacitor at IC7.

If you have a good ear for music, a own a generator, but no counter, then zero-beat the generator to a piano or other fixed-pitch musical instrument. The frequency of each note is 1.059463 times that of its semitone-lower neighbour. On the International music scale, defined by  $A_4=435$ Hz,  $G_7$  is 3100Hz. On the American Standard scale, where  $A_4=440$ Hz,  $G_7$  is 3136Hz.

For the second method, lash up an fm generator with an 8038 function generator chip

oscillating at 3kHz and swept to 1.0% peak deviation by a low-frequency second oscillator. Initially, connect a variable dc voltage source and a dvm to the modulation terminal of the 8038, and monitor the 8038's oscillation frequency with a counter. Once the 8038's modulation sensitivity is known, its modulation terminal can be driven by a sine wave of appropriate amplitude for 1.0% peak deviation. The output of the 8038 is then used as a test signal for the wow and flutter meter.

The third method uses a desk-top computer with a sound card. A few lines of code can generate a sound file that represents a digitised 3kHz carrier modulated at any level and frequency and that can be played through the sound card. Or, to avoid the programming, use one of the several available inexpensive digital audio editors that feature flexible generators.

I have tried all three methods of calibration. The most accurate and flexible is the third, but not everyone has the necessary computer hardware and either the software or the desire

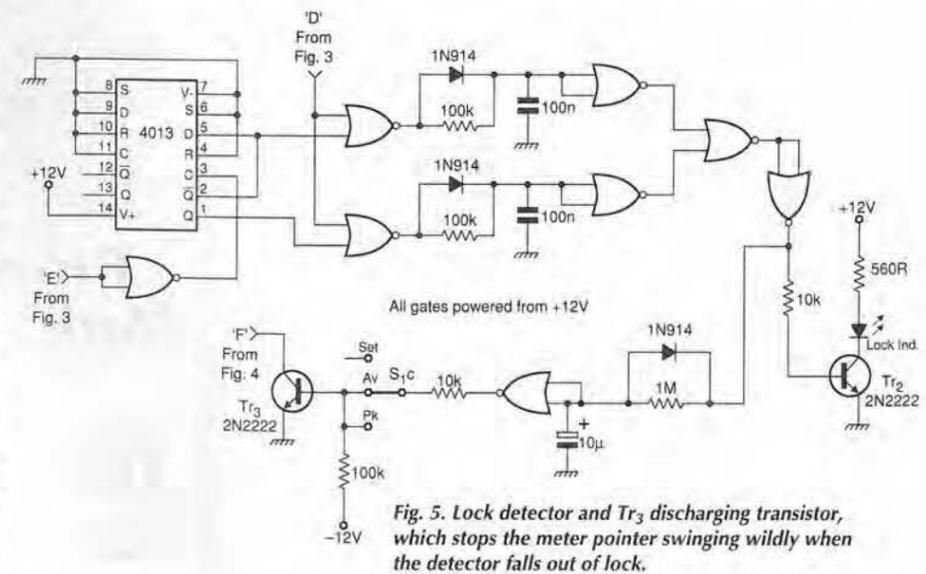


Fig. 5. Lock detector and  $Tr_3$  discharging transistor, which stops the meter pointer swinging wildly when the detector falls out of lock.

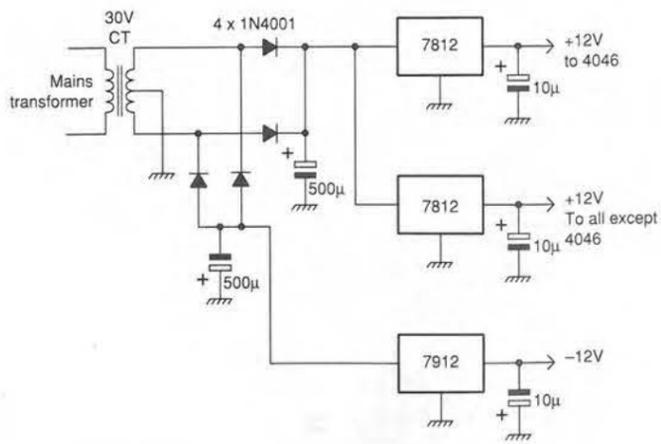


Fig. 5. Power supply. Mains-rated filtering at the transformer primary may be needed to prevent mains borne interference affecting readings.

frequency counter. This feature could be included with the addition of a dc amplifier and a second meter movement having a centre-scale zero. Provision would be required to tune the pll exactly to the carrier frequency.

One last word: if you've never measured wow and flutter, you'll be surprised at the apparent discrepancy between manufacturers' specifications and reality. The peak-reading, non-weighted settings are the most useful for trouble-shooting and for testing design changes, but new equipment is usually specified with a weighted rms-calibrated average reading. The difference between these measurements can be nearly an order of magnitude. On the other hand, a superb turntable may have less speed variation than the residual of even a good test record, especially given the difficulty of centring the record precisely on the platter. ■

References

1. Cabot, R.C., 'Audio tests and measurements' in Benson, K.B., ed., 'Audio Engineering Handbook', McGraw-Hill, New York, 1988, pp16.53-16.56.
2. Williamson, R., 'Volume control attenuates to zero', *Electronics World*, 97:29, 1991.
3. Terman, F.E., *Radio Engineering*, McGraw-Hill, New York, 1947, pp485-489.

to write software. Methods two and three have the theoretical advantage of allowing for testing or calibration of the whole system at once. The first method is fast, almost as accurate as the third, and can be done in a pinch with only an audio generator and a voltmeter.

Summary

This simple meter has been in use for years with no problems. The effects of flywheel or platter weight and balance, bearing wear, and drive-belt

quality are easy to measure objectively.

Readings are within a few percentage points of those obtained on a calibrated, professional wow and flutter meter when both meters are set up similarly and driven with a sine-modulated test carrier. Congruence is sometimes rather less for non-sinusoidal impulsive functions, and this difference may be due in part to the differences in meter movement ballistics.

Drift measurement was not included in the design, because drift is easily tracked with a

**New Special Offers**

New mini waterproof TV camera 40x40x15mm requires 10 to 20 volts at 120mA with composite video output (to feed into a video or a TV with a SCART plug) it has a high resolution of 450 TV lines Vertical and 580 TV lines horizontal, electronic auto iris for nearly dark (1 LUX) to bright sunlight operation and a pinhole lens with a 92 degree field of view, it focuses down to a few CM. It is fitted with a 3 wire lead (12v in gnd and video out)..... £93.57 + VAT = £109.95 or 10 x £92.92 + VAT = £104.95	Used 8748 Microcontroller..... £3.50
High quality stepping motor kits (all including stepping motors) 'Comstep' independent control of 2 stepping motors by PC (Via the parallel port) with 2 motors and software..... Kit £67.00 Ready built £99.00	SL952 UHF Limiting amplifier I.C. 16 surface mounting package with data sheet..... £1.95
Software support and 4 digital inputs kit..... £27.00	DC-DC converter Reliability model V12P5 12v in 5v 200ma out 300v input to output Isolation with data..... £4.95 each or pack of 10 £39.50
Power interface 4A kit..... £46.00	Hour counter used 7 digit 240v AC 30Hz..... £1.45
Stepper kit 4 (manual control) includes 200 step stepping motor and control circuit..... £23.00	QWERTY keyboard 58 key good quality switches..... £6.00
Hand held transistor analyser it tells you which lead is the base, the collector and emitter and if it is NPN or PNP or faulty..... £33.45	Airmax AS2903-C large stepping motor 14v 7.5' step 270hm 68mm dia body 6.3mm shaft..... £8.95
space 6v battery..... £1.20	or £200.00 for a box of 30
1 LEDs 3mm or 5mm red or green..... 7p each yellow 11p	Polyester capacitors box type 22.5mm lead pitch 0.9uf 250vdc..... 18p each
each cable ties 1p each £5.95 per 1000, £49.50 per 10,000	14p.....100+ 9p.....1000+..... 20p each
Rechargeable Batteries	15p.....100+ 10p.....1000+..... 20p each
AA (HP7) 500MAH.....£0.99	1uf 50v bipolar electrolytic axial leads..... 15p each
AA 700MAH.....£1.75	7.5p 1000+
C2AH with solder.....£3.60	7.5p 100+
D(HP2) 1.2AH.....£2.60	7.5p 100+
D4AH with solder.....£4.95	
tags.....£2.50	
PP3 8.4V 110MAH.....£4.95	
Sub C with solder.....£2.50	
tags.....£1.55	
1/3 AA with tags (Philips CTV).....£1.95	
180MAH.....£1.75	
Standard charger charges 4 AA cells in 5 hours or 4Cs or Ds in 12-14 hours + 1xPP3 (1, 2, 3 or 4 cells may be charged at a time).....£5.95	
High power charger as above but charges the Cs and Ds in 5 hours. AAs, Cs and Ds must be charged in 2s or 4s.....£10.95	
Nickel Metal Hydride AA cells high capacity with no memory. If charged at 100ma and discharged at 250ma or less 1100MAH capacity (lower capacity for high discharge rates).....£3.75	
Special offers, please check for availability	
Stick of 4 42x16mm Nicad batteries 17x16mm dia with red & black leads 4.8v.....£5.95	
5 button cell 6V 280MAH battery with wires (Varta 5x250DK).....£2.45	
Shaded pole motor 240Vac 5mm x 20mm shaft 80x40x5mm excluding the shaft £4.95 each	
115v AC 80v DC motor 4x22mm shaft 50mm dia x 60 long body (excluding the shaft) it has a replaceable thermal fuse and brushes..... £4.95 each (£3.95 100+)	
7 segment common anode led display 12mm.....£0.45	
LM337k TO3 case variable regulator.....£1.95	
.....£1.94 100+	
.....£12.95 each	
.....£9.95 10+	
.....£7.95 100+	
BS250 P channel mosfet.....£2.45	
BC347A transistor.....£3.95 per 100	
74LS05 hex inverter.....£1.00 per 100	
All products advertised are new and unused unless otherwise stated. Wide range of CMOS TTL 74HC 74F Linear Transistors kits. Rechargeable batteries, capacitors, tools etc always in stock. Please add £1.95 towards p&p. VAT included in all prices.	
<b>JPG Electronics, 276-278 Chatsworth Road, Chesterfield S40 2BH</b>	
Access/Visa Orders (01246) 211202 Fax: 550959	
callers welcome 9.30am to 5.30pm Monday to Saturday	

**ADVERTISERS PLEASE NOTE**

**For all your future enquiries on advertising rates**

**Please contact Malcolm Wells on**

**Tel: 0181-652 3620**


**Fax: 0181-652 8956**

# PROTEUS

For DOS and Windows 3.1, 95 & NT


The Complete Electronics Design System - Now With RIP-UP & RETRY!

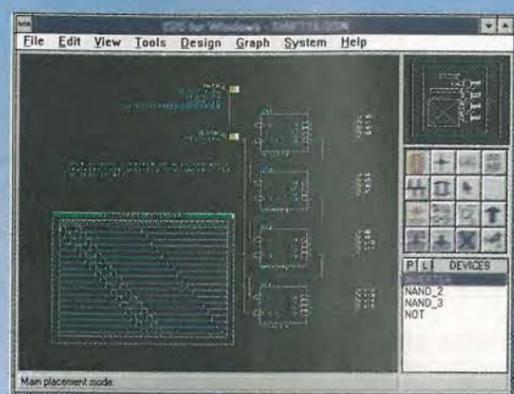NEW LOW PRICE OPTIONS AVAILABLE  
 Level 1 (500 pins) from £250  
 Level 2 (1000 pins) from £495  
 Level 3 (unlimited) from £995



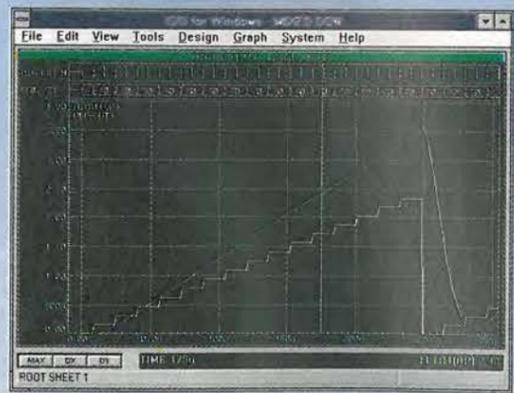
## Schematic Capture

- Easy to Use Graphical Interface under both DOS and Windows.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and


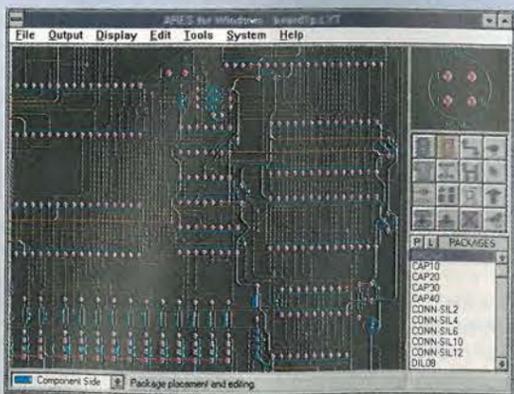
## Simulation

- Non-Linear & Linear Analogue Simulation.
- Event driven Digital Simulation with modelling language.
- Partitioned simulation of large designs with multiple analogue & digital sections.
- Graphs displayed directly on the schematic.



## PCB Design

- 32 bit high resolution database.
- Multi-Layer and SMT support.
- Full DRC and Connectivity Checking.
- RIP-UP & RETRY Autorouter.
- Shape based gridless power planes.
- Output to printers, plotters, Postscript, Gerber, DXF and clipboard.
- Gerber and DXF Import capability.

labcenter  
Electronics


Call now for your free demo disk or ask about the full evaluation kit.  
 Tel: 01756 753440. Fax: 01756 752857.  
 53-55 Main St, Grassington. BD23 5AA.

Fully interactive demo versions available for download from our WWW site. Call for educational, multi-user and dealer pricing - new dealers always wanted. Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.

EMAIL: info@labcenter.co.uk  
 WWW: http://www.labcenter.co.uk
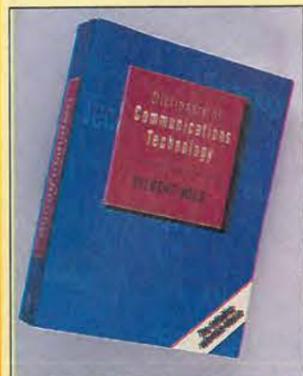
## Dictionary of Communications Technology

**Terms, definitions and abbreviations**  
 Gilbert Held, 4-Degree Consulting, Macon, Georgia, USA  
 In response to the changing face of the telecommunications industry and the rapid expansion in the use of microprocessors, fibre optics and satellites, Gil Held has updated his earlier telecommunications dictionary to bring readers in line with the very latest developments and terms in communications technology.



### Features Include:

- Over 9000 references and 250+ illustrations
- Comprehensive coverage of data and computer communications
- New entries on PC LANs, the Internet, client/server operations and communications testing
- Trade name information


### First Edition Review:

"For a consultant or telecommunications operative, this book is a must. It is comprehensive and timely ... an excellent reference for the IS professional."

**Data Processing Digest**  
 ISBN 0471 95542 6, 512pp, hardback, UK £68.50, Europe £73, ROW £85  
 ISBN 0471 95126 9, 512pp, paperback, UK £38.50, Europe £43, ROW £55
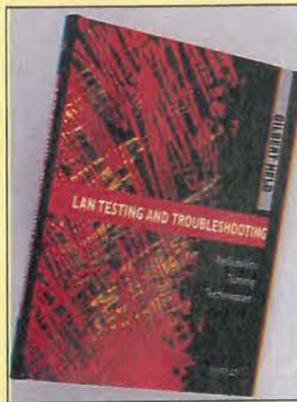
## Testing, Troubleshooting and Tuning Local Area Networks

**Techniques and tools to isolate problems and boost performance**  
 Gilbert Held, 4-Degree Consulting, Macon, Georgia, USA.  
 Recognising the problems




encountered by network users and administrators on a daily basis, this book is designed to assist readers by focusing on testing, troubleshooting and tuning of Ethernet and Token-Ring networks. It is devoted exclusively to: how things go wrong how to recognise, monitor and test for problems; network analysis and network management products that assist users in examining the flow of data in a complex network.

ISBN 0471 95880 8, 275pp, hardback, UK £37.50, Europe £40, ROW £50
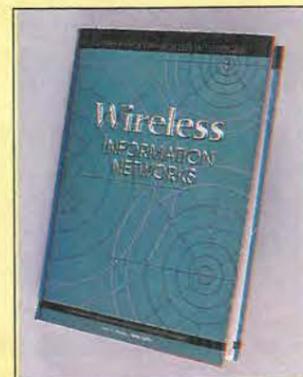
## Wireless Information Networks

Kaveh Pahlavan, Worcester Polytechnic Institute and Allen H Levesque, GTE Government Systems Corporation.

*Wireless Information Networks* organises all major elements of wireless technology - cordless and cellular telephony, Personal Communications Systems (PCS), mobile data networks and Wireless Local Area Networks (WLANs), presenting them from a logical, systems engineering perspective. Technical material is thoroughly integrated with special applications and focuses on four main areas: Wireless




standards and descriptions of systems and products; Measurement and modelling of radio and optical wave propagations; Wireless transmission techniques and Wireless multiple access techniques.

**Contents:** Overview of Wireless Networks. Frequency Administration and Standards Activities. Characterisation of Radio Propagation. Channel Measurement and Modelling for Narrow-band Signaling. Measurement of Wide-band Channel Characteristics. Computer Simulation of the Radio Channel. Modem Technology. Signal Processing for Wireless Applications. Spread Spectrum for WIN Systems. Wireless Optical Networks. Networks and Access Methods. Standards and Products.

ISBN 0471 10607 0, 304pp, hardback, UK £63.50, Europe £68, ROW £81
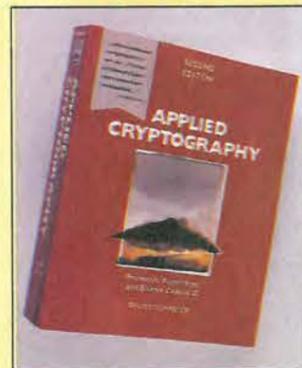
## Applied Cryptography

**2nd Edition**  
*Protocols, Algorithms and Source Code in C*  
 Bruce Schneier, Security Consultant and President of Counterpane Systems, USA  
 This revision of the programmer's and system designer's guide to the practical applications of modern cryptography



provides the most comprehensive, up-to-date survey of modern cryptographic techniques, along with practical advice on how to implement them.

### New to this edition:

- Detailed treatment of the US government's Clipper Chip encryption program
- New encryption algorithms (eg. 'GOST') recently obtained from the former Soviet Union
- More detailed information on incorporating algorithms and programming fragments

into working software

- The latest developments in the fields of message authentication ('digital signatures') and digital cash.

ISBN 0471 12845 7, 816pp, hard back, UK £59, Europe £64, ROW £78  
 ISBN 0471 11709 9, 816pp, paperback, UK £44, Europe £49, ROW £63

## Data and Image Compression

**4th edition**  
*tools and techniques*  
 Gilbert Held, 4-Degree Consulting, Macon, Georgia, USA  
 Data and image compression are key issues in computer communications with the increasing demand for data transmission capacity.




Guiding the reader through the main techniques, this book explains how practical data and image compression techniques are now vital for efficient, low-cost transmission and data storage requirements. Building on the success of the previous editions of *Data Compression*, the scope of the fourth edition has been considerably expanded. Now covering image and fax compression, the text has been restructured to take account of the many new advances in this important field. It is also accompanied by an updated disk containing compression routines.

ISBN 0471 95247 8, 450pp+disk, hardback, UK £58.50, Europe £63, ROW £75
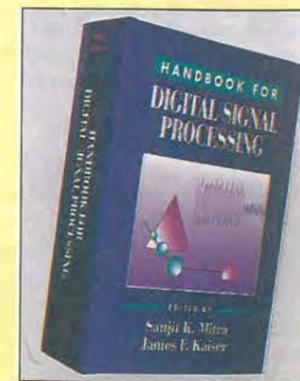
## Handbook for Digital Signal Processing

S.K. Mitra, University of California and J.F. Kaiser, Bell Communications Research, New Jersey, USA  
 This is the definitive source of detailed information on all important topics in modern



digital signal processing. The only current handbook of its kind, it meets the needs of practising engineers and designers of hardware, systems and software. Written by world authorities, the *Handbook for Digital Signal Processing* is supplemented with hundreds of informative tables and illustrations. For professional engineers, designers and researchers in electronics and telecommunications, this work will be an indispensable reference - now and for years to come.

**Contents:** Introduction; Mathematical Foundations of Signal Processing; Linear Time-Invariant Discrete-Time Systems, Finite-impulse Response Filter Design; Digital Filter Implementation Considerations; Robust Digital Filter Structures; Fast DFT and Convolution Algorithms; finite Arithmetic Concepts; Signal Conditioning and Interface Circuits; Hardware and Architecture; Software Considerations; Special Filter Designs; Multirate Signal Processing; Adaptive filtering Spectral Analysis; Index.  
 ISBN 0471 61995 7, 1302pp, hardback, UK £110.50, Europe £118, ROW £138

## Solving Interference Problems In Electronics

R. Morrison, Eureka California, USA  
 Interference in electronic equipment is a constant source of difficulty for the design and systems engineer. Until now, there has not been a coherent theory that engineers can refer to in their design work and the solution of interference problems has therefore often considered to be an 'art'. Written by an acknowledged expert in the field, this new title provides methods and techniques for testing and evaluating

designs, and covers interference questions in computer manufacturing and systems design.  
 ISBN 0471 12796 5, 206pp, hardback, UK £47.50, Europe £48.50, ROW £54



## Diode Lasers and Photonic Integrated Circuits

L. A. Coldren and S. W. Corzine, both of the University of California, Santa Barbara, USA.  
 Diode lasers are found in numerous applications in the optoelectronics industry,



telecommunications and data communications, ranging from readout sources in compact disc players to transmitters for optical fibre communications systems. This new title provides a comprehensive treatment of diode laser technology, its principles and theory, treating students as well as experienced engineers to an in-depth exploration of this fast growing field.  
 ISBN 0471 11875 3, 620pp, hardback, UK £63.50, Europe £67, ROW £78

# All prices are fully inclusive of packing and delivery

Return to Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following titles:

Qty	Title or ISBN	Price

\*\* All prices on these pages include delivery and package \*\*

Total \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_ Telephone \_\_\_\_\_

Method of payment (please circle)

Access/Mastercard/Visa/Cheque/PO

**Cheques should be made payable to Reed Business Publishing**

Credit card no \_\_\_\_\_

Card expiry date \_\_\_\_\_

Signed \_\_\_\_\_

Please allow up to 28 days for delivery

**YOUR  
Ideal Partner  
in UHF and VHF  
COMMUNICATION**



**One stop solutions  
for all your radio  
telemetry module needs.**

When the success of your products depends on radio telemetry modules, you need a business partner you can trust. A skilled and experienced manufacturer that can offer modules of the highest quality, operating over a wide range of frequencies.

In other words, a partner like Wood & Douglas. Founded on technical excellence, Wood & Douglas is a British company that specialises in the design, development and production of radio-based products. With over 30 staff dedicated to meeting your requirements, the company is able to provide true one-stop purchasing - whatever your RTM needs.

All radio modules are highly functional, capable of meeting a wide range of requirements. Designed to offer efficient, easy-to-use radio telemetry components for system designers, they can open up a whole new world of product possibilities.

From portable bar-code readers to earthquake monitors, Wood & Douglas can help you make the most of the opportunities in radio telemetry.

To find out more about the possibilities, contact...



**WOOD & DOUGLAS**

Lattice House, Baughurst, Tadley, Hampshire RG26 5LP, England  
Telephone: 0118 981 1444 Fax: 0118 981 1567  
email: info@woodanddouglas.co.uk  
web site: http://www.woodanddouglas.co.uk

CIRCLE NO. 133 ON REPLY CARD

**PCB Designer**

For Windows 3.1, '95 or NT



Looking for the price?  
It's just £49.00 all inclusive!  
...no VAT...no postage...  
...no additional charges for  
overseas orders.

Dealers and distributors wanted.  
Phone (01432) 355 414 to order

Internet  
See our Web site at [www.niche.co.uk](http://www.niche.co.uk) for  
information and a working demo. e-mail  
[pcb@niche.demon.co.uk](mailto:pcb@niche.demon.co.uk).

- ✓ Produce Single or Double sided PCBs.
- ✓ Print out to any Windows supported printer.
- ✓ Toolbar for rapid access to commonly used components.
- ✓ Helpful prompts on screen as you work.
- ✓ Pad, track & IC sizes fully customisable.
- ✓ No charges for technical support.
- ✓ Snap-to grid sizes 0.1", 0.05" 0.025" and unrestricted.
- ✓ SMT pads and other pad shapes.

Also available from,  
**South Africa:** JANCA Enterprises, PO Box 32131, 9317 Fichardpark at R299.00. Phone/FAX: (051) 223744  
**France:** Telindel, Quartier Les Pradets, Chemin des Veys, 83390 Cuers. Phone: 94 28 66 67

CIRCLE NO. 114 ON REPLY CARD

**ADVERTISERS  
PLEASE  
NOTE**

**For all your  
future enquiries  
on advertising  
rates**

**Please contact  
Malcolm Wells on**

**Tel: 0181-652 3620  
Fax: 0181-652 8956**

**LETTERS**

Letters to "Electronics World" Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

**LVD is not new**

In his editorial, EW Oct '96, Rod Cooper paints a more gloomy picture than is justified - and one statement is quite wrong. The Low Voltage Directive came into force in 1976 - yes, 20 years ago. What happened on 1 January 1997 was that you had to use CE mark. But you have had to do that, for safety as well, since 1 January 1996, for anything that falls within the EMC Directive.

It is very important for the health and welfare of the electronics industry in the UK not to encourage people to close down projects or even companies through fear of the Directives. More stringent regulations have been in force in Germany and Austria for more than a decade, and their small electronics businesses have learned how to cope: so it is possible.

The chance of any large company trying to use a Directive against a very small competitor is minimal. It is certainly impossible to forecast that there will be no chief executive who suffers a fit of paranoia and goes down that route, but most would see that the game is not worth the candle - particularly if there are actually no grounds for the complaint.

It is true that the engineering profession is disunited, but it is not to be expected that they could unite in opposition to requirements introduced under the EMC Directive. For example, the requirements of EN 61000-3 (all four Sections) are bound to be looked on with favour by the power industry, which would like to preserve their 50Hz sine-waves undistorted. But the regulations are a bane to equipment designers.

The idea of eliminating immunity tests has been raised before, and seems attractive at first sight. But lack of immunity can result in quite dangerous situations, which are almost entirely unpredictable because the manufacturer often has no idea what his equipment may be used for. Of course, these are the events that captured the imaginations of the politicians in the first place, and helped to 'sell' the Directives to them.

Furthermore, complaints of lack of immunity in the field receive virtually no publicity, but the broadcasters, BT and the electricity suppliers receive thousands of complaints every year - usually directed to quite the wrong body. The cost of following these up, and solving them where possible, is quite large.

On the subject of EMC in Australia

(page 724 of the same issue), without the 'benefit' of Brussels, the SMA seems to have produced requirements which are more severe than apply in Europe at present, although they have backed off on some points.

**John Woodgate**  
Rayleigh  
Essex

**Fooling stereo**

In his article 'Music in mind' in the Oct. '96 issue, Ian Hickman wondered why his gyroscopically-controlled headphones refuse to work in stereo.

I wasn't totally convinced by explanations from the experts in the letters pages of subsequent issues, so here's my guess. While processing time or volume differences, the brain needs the signal from both ears to be approximately equal, as in a mono-signal. It is impossible to determine phase difference from two completely different signals.

If you mixed, say, a third of the right-hand channel's signal to the left channel and a third of the left channel's signal to the right, the brain would maybe have enough information to fool it.

**Hannu Multanen**  
Joensuu  
Finland

**Preamp defence**

I would like to comment on Mr Allen Wright's letter (*Electronics World*, Nov. 1996) concerning Douglas Self's pre-amp.

My comments come from two viewpoints - as a collaborator with Douglas in the design of the pcb for the pre-amp, and as a self-employed designer in the professional audio industry.

Over the past 15 years, my work has taken me into a number of UK companies specialising in the design and manufacture of top-of-the-range mixing consoles that end up in radio, television and recording studios throughout the world. All the events that captured the imaginations of the politicians in the first place, and helped to 'sell' the Directives to them.

It is a fact that Douglas's preamplifier has been designed with the same criteria used to design professional mixing consoles.

Mr Wright states that budget mixing console manufacturers stopped using the 5532 years ago. I will not contest the budget manufacturers' lack of use of the 5532, as my experience is not at the budget end of the market. But may I be so bold as to suggest that the term

'budget' is significant? The 5532 is expensive. Is it financial constraints rather than sonic performance that preclude its use?

As for the existence of an "unpleasant sonic signature" from the 5532, I am surprised. I would like Mr Wright to tell us more about it.

The ultimate conclusion to his statement of the existence of a "signature" is that virtually all live and recorded sound will be afflicted with the "signature" by virtue of the recording and/or broadcast equipment used to get the sound to the listener.

No matter what devices are used in a preamplifier, if it is well designed, it will faithfully reproduce at its output what is offered to its input. The output will include Mr Wright's alleged, "unpleasant sonic signature", which will have been introduced earlier in the signal chain, and is therefore beyond the control of the pre-amp designer or the listener.

**Gareth Connor**  
GJC Designs  
London

**CAD inadequacies?**

The reviews on pcb cad failed to answer the one question I wanted answered. All the packages seem to work on the same basis: having designed your circuit, you use the schematic drawing package to produce a professional printable schematic and the computer does the rest - i.e. it produces for you a parts list, it captures the circuit for the layout and even simulates the circuit performance.

The problem comes in the phrase 'having designed the circuit'. A word processor package doesn't assume that you had produced hand written draft before you start typing and pcb cad shouldn't assume you have done a paper circuit first. I design the circuit on-screen. I may import bits from earlier circuits. When I draw a bias chain I don't know what the values are going to be, that is left until I'm happy that I have got the configuration right. The design process may include several changes of mind, adding components, taking the out, etc.

**Q&A**

**Shifting phases?**

I am looking for a circuit to phase shift by 90° the components of a signal with frequencies in the range 10Hz to about 350Hz. Although simple integration or differentiation can achieve this, they do so at the expense of a frequency dependent change in the signal amplitude which I cannot use.

In *Electronics World* April 1993, Terrance Finegan mentions that such 'a useful analogue function may be realised differentially with all-pass filters', but this hint has proven insufficient. Text books even mentioning all-pass filters seem to be the exception - at my level of mathematical sophistication anyhow.

Are there any readers with a solution to this problem? It would help me, and being an unusual function may inspire other interesting designs.

**Alan Scrimgeour**  
London

(This question is repeated from p 790, Oct '96 issue - ed)

In answer to Alan Scrimgeour's query, it is only possible to produce an approximation to a wide-band 90° phase-shift. The complexity of the solution depends very much on the tolerable errors. To handle 10Hz signals, only active all-pass filters are really practicable. The design procedure is too lengthy to reproduce here but is not difficult, and a good source of the information is the 'Electronic filter design handbook' by A B Williams (McGraw Hill). The ISBN of the first edition is 0 07 070430 9, and this deals with the subject fully, but there is a later edition.

**John Woodgate**  
Rayleigh  
Essex

In answer to the question from Alan Scrimgeour: The need to phase shift audio frequencies by 90° is also required in the phasing method of sbs generation. The article on this subject in *Electronics World* March 1994, pp202-206 covers this subject along with the merits of polyphase networks versus 'all-pass' filters.

**John Crabtree**  
Connecticut  
USA



# CLASSIFIED

TEL 0181 652 3620

FAX 0181 652 8956

## ARTICLES FOR SALE



**SUPPLIER OF QUALITY USED TEST INSTRUMENTS**



CONTACT

**Cooke International**

ELECTRONIC TEST & MEASURING INSTRUMENTS  
Unit Four, Fordingbridge Site, Main Road, Barnham,  
Bognor Regis, West Sussex, PO22 0EB, U.K.  
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

CIRCLE NO. 137 ON REPLY CARD



**OPERATING & SERVICE MANUALS**



CONTACT

**Cooke International**

ELECTRONIC TEST & MEASURING INSTRUMENTS  
Unit Four, Fordingbridge Site, Main Road, Barnham,  
Bognor Regis, West Sussex, PO22 0EB, U.K.  
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

CIRCLE NO. 138 ON REPLY CARD

## ADVERTISERS' INDEX

Adept .....	103	Labcenter .....	167
Anchor .....	147	M & B Radio .....	90
Antrim .....	151	Milford .....	IFC
Applied .....	166	Niche .....	170
Bull .....	158	Number One .....	132
Bull .....	173	Oema .....	125
CMS .....	151	Olson .....	99
Conford .....	151	Pico .....	127
Dataman .....	OBC	Ralfe .....	176
Display .....	155	Robinson .....	101
Electromail .....	137	Seetrax .....	139
Equinox .....	IBC	Stewart .....	172
Field .....	125	Surrey .....	151
Halcyon .....	125	Swift Designs .....	97
Hart .....	93	Telford .....	118
Hitex .....	90	Telnet .....	118
Johns .....	95	Those .....	139
JPG .....	166	Tie Pie .....	111
Keytronics .....	149	Wood & Douglas .....	170

## ARTICLES WANTED

**WE WANT TO BUY!!**  
IN VIEW OF THE EXTREMELY  
RAPID CHANGE TAKING PLACE  
IN THE ELECTRONICS  
INDUSTRY, LARGE QUANTITIES  
OF COMPONENTS BECOME  
REDUNDANT. WE ARE CASH  
PURCHASERS OF SUCH  
MATERIALS AND WOULD  
APPRECIATE A TELEPHONE  
CALL OR A LIST IF AVAILABLE.  
WE PAY TOP PRICES AND  
COLLECT.

**R. HENSON LTD.**  
21 Lodge Lane, N. Finchley,  
London N12 8JG.  
5 Mins, from Tally Ho Corner.

TELEPHONE  
0181-445-2713/0749  
FAX 0181-445-5702

## Consider .....

Your costs to continue to stock  
UNWANTED SURPLUS... EXCESS... OBSOLETE  
STOCKS OF:-  
ELECTRONIC-ELECTRICAL COMPONENTS &  
ACCESSORIES

**RELEASE**  
for  
**PAYMENT IN ADVANCE**  
OF COLLECTION  
contact

**K.B. Components,**  
21 Playle Chase, Gt. Totham, Maldon, Essex, CM9 8UT  
Tel:- 01621 893204 Fax:- 01621 893180 Mobile:- 0802 392745  
REGISTER TO RECEIVE MONTHLY PUBLISHED STOCK LISTS AT NO CHARGE OF  
ALL EXISTING NEW, UNUSED, STOCKS OF ALL COMPONENTS AND ACCESSORIES.

### TOP PRICES PAID

For all your valves, tubes, semi  
conductors and IC's.  
**Langrex Supplies Limited**  
1 Mayo Road, Croydon  
Surrey CR0 2QP  
TEL: 0181-684 1166  
FAX: 0181-684 3056

### ★★WANTED★★

Test equipment, Electronic Scrap,  
Valves, Transmitters/Receivers,  
Factory & Warehouse Clearance.  
Confidentiality Assured.  
**TELFORD ELECTRONICS**  
Phone: 01952 605451  
Fax: 01952 677978

## WANTED

**TOP PRICES PAID**  
For all your Test Equipment,  
Receivers, Transmitters etc.  
Factory Clearance, Prompt  
Service and Payment.  
**HTB ELEKTRONIK**  
Alter Apeler Weg 5  
27619 Schiffdorf, Germany  
Tel: 0049 4706 7044  
Fax: 0049 4706 7049

40 YEARS WIRELESS WORLD '52-'75  
bound, '76-'92 unbound. Offers Telephone  
01276 65529.  
TEK 576 (577) Curve Tracers. Phone 01460  
73557.

**HEWLETT PACKARD  
TEKTRONIX  
MARCONI  
TEST EQUIPMENT  
WANTED!**  
**M&B RADIO**  
86 Bishopgate Street, Leeds LS1 4BB  
Tel: (+44) 0113 2435649  
Fax: (+44) 0113 2426881

SMALL SELECTION of Aircraft Starter  
motors, DC generators and rotary converters.  
Possibly suit electric vehicles etc. £10 to £50  
depending on condition and type. Tel: Bristol  
01179 793883.  
MICROCHIP 'MICROMASTER' develop-  
ment system £1,150. Multicom 'Vaporette' sol-  
derring machine £500. Both unused. Icelab  
8051/2 Emulator £400. Tel: 01295 810859.

## RECRUITMENT

### Instrumentation Scientist/Technician

The British Antarctic Survey, a Government-funded body, organises and carries out a balanced and optimal programme of research in Antarctica of global significance in the Earth, Atmospheric and Life Sciences. As well as its headquarters building on the outskirts of Cambridge, three permanently manned stations and one summer only station are maintained in the Antarctic.

We are looking to recruit an Instrumentation Scientist/Technician to work with the atmospheric boundary layer group. Duties will include calibration and maintenance of micrometeorological equipment for eventual deployment in Antarctica. Responsible for the upkeep of hardware documentation, other duties will also include the repair and possible modification of returning field instruments and some upgrading of 'realtime' logger software.

As you will spend up to six months in the Antarctic each austral summer and assist in the deployment of new equipment, you must be physically fit.

The post is for three years.

You will have a degree in Electronic Engineering, Physics or equivalent. Post-graduate experience in instrumentation would be highly desirable. However, no experience of low temperature or extreme environment equipment design is expected and training in these areas will be provided at the BAS Headquarters in Cambridge.


Starting salary will be from £13,698 per annum depending on qualifications and experience.

For further details and an application form please contact the Personnel Section, British Antarctic Survey, High Cross, Madingley Road, Cambridge CB3 0ET. Tel: 01223 251508/507. Please quote ref: BAS 55/96. The closing date for completed application forms is 23 January 1997.


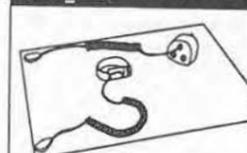
## ARTICLES FOR SALE

**SSE** Protect Your Microchips  
from STATIC DISCHARGE! **SSE**



Use an SSE grounding kit.

- Kit includes:
- static dissipative solder resistant rubber mat.
  - wrist strap
  - ground lead
  - earth plug

Mat size 70 x 30 cm - offer price £16.55 per kit + VAT - Ref: AGK1  
Mat size 25 x 20 cm - offer price £12.55 per kit + VAT - Ref: AGK2

STATIC SAFE ENVIRONMENTS Payment by CHEQUE / ACCESS  
127 Hagley Road, Birmingham B16 8XU VISA / MASTERCARD  
Tel: 0121 454 8238 Fax: 0121 625 2275 Catalogue available

**SPECTRUM ANALYSERS**



ANRITSU MS420J 10Hz-30MHz network/spectrum analyser £5000  
AVCOM - portable, battery operated, to 1000MHz £2000

TEKTRONIX 492 21GHz portable spectrum analyser, with options 1, 2 and 3 E6500 or E7500 with multiplexor and mixers to 40GHz £4000  
HP8711A 300kHz-1.3GHz network analyser £7500  
HP8753A vector network analyser, 3GHz £10000  
HP8702B lightwave component analyser (options 006/011) 6GHz £4500  
HP8559A/182T 21GHz £1500  
HP8557A/182T 350MHz £4250  
HP8590A 1.8GHz portable, RS232 option

**MARCONI INSTRUMENTS**



2018 synthesized AM/FM signal generator 80kHz-520MHz £1250  
2019 synthesized AM/FM signal gen 80kHz-1040MHz £2000  
2305 modulation meter £2500  
2828A/2829 digital simulator/analyser £500  
2955 radio communications test set £3250  
6460/6421 power meter & sensor 10MHz-12.4GHz £350  
65xx waveguide detector for use with 6501/2-scalar analysers £250  
TF2910 TV interval timer

**ralfe electronics** exclusively professional T&M ©  
• 36 Eastcote Lane • South Harrow • Middx HA2 8DB • England •  
TEL (+44) 0181-422 3593 • FAX (+44) 0181-423 4009

EST 41 YRS



DISTRIBUZIONE E ASSISTENZA, ITALY: TLC RADIO, ROMA (06) 871 90254

**TEST EQUIPMENT**

ADRET 740A synthesized signal generator 0.1-1120MHz £2500  
ANRITSU MS420J network/spectrum analyser 10Hz-30MHz £500  
BRUEL & KJAER 2307 level recorder £1000  
BRUEL & KJAER 2308 analogue X-Y pen recorder £750  
CHASE LFR1000 interference measuring receiver 9kHz-150kHz £1000  
DATRON 1061 & 1061A - various, digital multimeter & 1065 - call from £500  
DATRON 1065 digital multimeter all ranges plus IEEE £500  
FARNELL SSG2000 synthesized signal generator 10Hz-2000MHz £2500



**ISO9002 ACCREDITED STOCKIST MEASUREMENT & TEST EQUIPMENT**

PHILIPS PMS167 1mHz-10MHz function generator £275  
RACAL-DANA 9300 milli-voltmeter £400  
RACAL-DANA 9301A true RMS RF milli-voltmeter £350  
SCHLUMBERGER 7081 precision voltmeter 8.5 digits £2750  
TEKTRONIX P6201 FET PROBE £350  
WANDEL & GOLTERMANN WM30 level tracer £500  
WANDEL & GOLTERMANN PJM-4S jitter meter for SONET & SDH £5500  
WAVETEK 23 synthesized function generator 0.01Hz-12MHz £1250  
WAVETEK 1067 opt 522 1-500MHz sweep generator £500  
WAYNE KERR 3220 20A bias unit (for 3245 inductance analyser) £1250  
TEKTRONIX AM503/P6303 current probe £1500

**HEWLETT PACKARD**



1640B serial data generator £500  
3764A digital transmission analyser £1500  
3335A synthesizer/level generator £2000  
3235A switch/test unit £1000  
3324A synthesized function generator £2000  
33320G/33322G programmable attenuators 4GHz, with driver 11713A £1000  
As above but 18GHz set £1500  
3581C selective voltmeter £1250  
3779D primary multiplex analyser £5000  
37900D signalling test set with 2 x 37915A interface cards £5500  
4140B pA/meter, DC voltage source £4000  
4272A multi-frequency lcr meter £3500  
435B microwave power meter, analogue £400  
5386A 3GHz frequency counter £1500  
54100A 1GHz digitizing oscilloscope, now inc 2 x 1GHz active probes £2000  
54502A digital oscilloscope 400MHz 400MSa/s £2500  
8007B pulse generator 100MHz £950  
8018A serial data generator £1000  
8082A pulse generator 250MHz £2000  
8111A pulse generator 20MHz £1250  
8146A optical tdr, with options 2/3/plug-in 81465SH (single-mode) £8500  
816A slotted line 1.8-18GHz with 809C & 447B probe £500  
8444A tracking generator with option 059 £1000  
86222A/8620C 10MHz-2.4GHz sweep generator £2000  
87510A gain-phase analyser 100kHz-300MHz £6500  
8753A 3GHz vector network analyser £7500  
J2215A FDDI portable multimode test set £1500  
J2219A 486-based, colour option main-frame £1000  
J2219A/J2171A 486-based colour screen option network advisor £3000

SEND FOR LATEST STOCK LIST. WE FAX LISTS AND SHIP WORLDWIDE. ALL FULLY LAB-TESTED AND NO-QUIBBLE GUARANTEED

CIRCLE NO. 148 ON REPLY CARD

**ELECTRONIC UPDATE**

Contact Malcolm Wells on 0181-652 3620

A regular advertising feature enabling readers to obtain more information on companies' products or services.

**A world of colour LCD**



**Comprehensive new LCD brochure**

The widest range of colour LCDs, LCD monitors and plug and play kits available in the UK, all in one easy to use brochure, is now available FREE!

It includes products ranging from 2.9" monitors to 16.1" colour LCD screens, mono/colour STN TFTs and touch screen technology from the worlds leading manufacturers.

Phone Trident today for your free copy.

Tel.: 01737 765900 Fax: 01737 771908


CIRCLE NO. 149 ON REPLY CARD



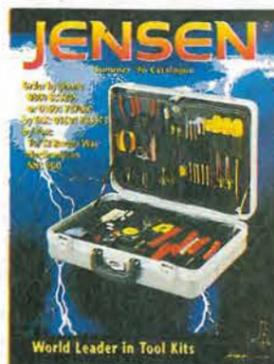**1997 Full Catalogue Data File Words.**

The National Instruments 1997 catalogue features our new BridgeVIEW and Lookout software packages for industrial automation. Other software products include LabVIEW, LabWindows/CVI, and HiQ. In addition, our new line of IMAQ products provides a complete imaging solution. Hardware products include GPIB, DAQ, VXI and new serial interfaces for industrial communications applications.

NATIONAL INSTRUMENTS, Tel: 01635 523545 CIRCLE NO. 150 ON REPLY CARD



**NEW JENSEN TOOLS CATALOGUE**

Colourful new Catalogue, hot off the press from Jensen Tools, presents unique new tool kits for service/support of communications equipment. Also latest test equipment from many major manufacturers. Includes hard-to-find tools, PC/LAN diagnostics, bench accessories, static control, technical manuals and more.

Ring 0800 833246 or Fax 01604 785573 for a free copy. Jensen Tools, 10-12 Ravens Way, Northampton NN3 9UD CIRCLE NO. 152 ON REPLY CARD

**NEW Feedback T&M Catalogue**

The latest edition of the Feedback Test & Measurement catalogue is now available. Over 60 pages packed with more than 800 products divided into over 20 sections. The catalogue is indexed for both product and manufacturer and is fully illustrated. Whether you are looking for an individual product, a complete workstation, or a solution to a particular Test & Measurement need the NEW Feedback catalogue will solve your problems, send for a copy NOW!

CIRCLE NO. 151 ON REPLY CARD

**EVERYTHING YOU NEED TO DEVELOP AN EMBEDDED 8051 PROJECT IN C**

**8051 MICROCONTROLLERS + FLASH**



**MICRO-PRO 51**

State-of-the-art programmer for the 8051 family

- Programming support for the entire Atmel 89C and 895 microcontroller families
- Also supports many Philips, Intel, Dallas & Siemens 8051 derivatives
- Field programmable hardware ensures future device support

Order code: MP51 SYS £125.00

Products are now available from Farnell Components

**Microcontroller in-circuit re-programming adaptor**

Now you can re-program the entire Atmel microcontroller family in-circuit!

No more re-moving chips - ideal for 8051 single-chip project development.

Supplied with AT89C2051 and AT89C52 + 11.0592 MHz Crystal.

(Requires Micro-Pro 51 programmer to operate - see above)

Order code: AD-MICRO-ICR £125.00


**Package Adaptors**

PLCC 44-pin adaptor

Suitable for most 8051 derivatives

Order code: AD-PLCC44-A

£65.00

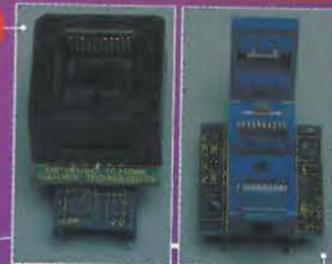

SOIC 20-pin adaptor

Suitable for Atmel AT89C1051 & AT89C2051


Order code: AD-SOIC20-A £75.00

Please enquire for our full range of adaptors

**The ATMEL 8051 FLASH microcontroller family**

Atmel Part Code	89C51	89L51	89C52	89L52	89C55	89S8252	89C2051	89C1051
Flash Code ROM (bytes)	4K	4K	8K	8K	20K	8K	2K	1K
RAM (bytes)	128	128	256	256	256	256	128	64
EEPROM	-	-	-	-	-	2K	-	-
In-system re-programmable	-	-	-	-	-	YES	-	-
I/O Pins	32	32	32	32	32	32	15	15
16-bit Timer/Counters	2	2	3	3	3	3	2	1
Watchdog timer	-	-	-	-	-	YES	-	-
Interrupt sources	6	6	8	8	8	9	6	3
Serial UART (full duplex)	YES	YES	YES	YES	YES	YES	YES	-
SPI interface	-	-	-	-	-	YES	-	-
Analogue comparator	-	-	-	-	-	-	YES	YES
Data pointers	1	1	1	1	1	2	1	1
Package Pins (DIL)	40	40	40	40	40	40	20	20

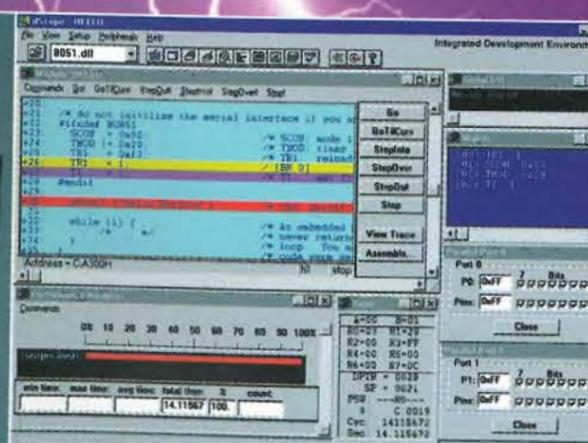- Atmel microcontrollers feature on-chip re-programmable FLASH code memory
- FLASH is electrically erasable in under 15ms (no need for UV eraser)
- 89C51/89C52 are drop-in FLASH replacements for the generic 87C51/87C52 devices
- 89C2051 is a single-chip 8051 in a 20 pin package...even retaining the serial port



**C51 STARTER SYSTEM**

- ✓ Optimising C Compiler
- ✓ Macro Assembler
- ✓ Software Simulator
- ✓ Device Programmer
- ✓ Sample Devices
- ✓ Hardware/Software Documentation

Only £199.00

Plus FREE Atmel CD ROM data book  
• System supplied with 1 x Atmel AT89C1051 and 1 x AT89C2051 Microcontrollers  
• C-compiler + Assembler output restricted to 2k total program code.

Order code: AT-89C051-ST

UPGRADE TO 8K VERSION NOW AVAILABLE

**89C-1051/2051 Microcontroller Demo Module**

A feature packed evaluation module for the 20 pin derivatives. LED SWITCH array, RS232, A/D, Lightmeter, Piezo speaker.

**89C-1051/2051 Microcontroller OEM Module**

An ideal OEM module which can be used for evaluation or can be designed into custom products. RS-232, A/D, LED, I/O Header

Order code: AT-89C051-OEM £29.00



Order code: AT-89C051-DEMO £58.00



The Embedded Solutions Company

Visit our web page at: www.equinox-tech.com

Email: sales@equinox-tech.com


229 Greenmount Lane, Bolton BL1 5JB UK

SALES: 01204 492010 TECHNICAL: 01204 491110 FAX: 01204 494883 (INTERNATIONAL DIALLING CODE +44 1204)

Equinox reserves the right to change prices & specifications of any of the above products without prior notice. £30E. All prices are exclusive of VAT and carriage

# THE WORLD'S MOST POWERFUL, PORTABLE PROGRAMMERS

£495 + VAT

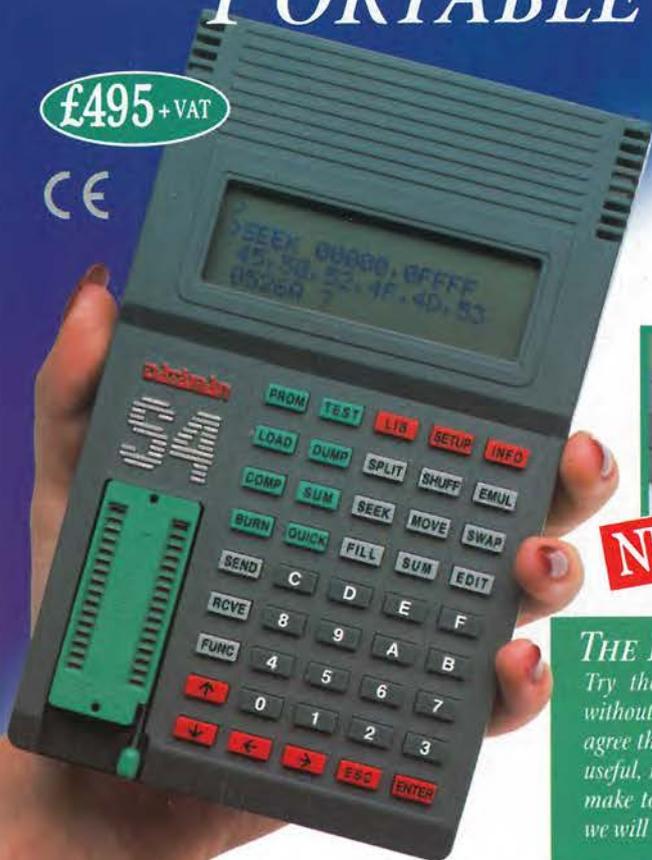

## S4 GAL module

Programs a wide range of 20 and 24 pin logic devices from the major GAL vendors. Supports JEDEC files from all popular logic compilers.

£195 + VAT



NEW

## THE DATAMAN CHALLENGE

Try the Dataman S4 or Dataman-48 without obligation for 30 days. If you do not agree that these are the most effective, most useful, most versatile additions you can make to your programming toolbox, we will refund your money in full.

## Dataman S4

Compare the Dataman S4 with any other programmer and you'll see why it's the world's undisputed number one.

S4 is capable of programming 8 and 16-bit EPROMs, EEPROMs, PEROMs, 5 and 12V FLASH, Boot-Block FLASH, PICs, 8751 Microcontrollers and more. S4 also emulates ROM and RAM as standard!

S4 is the only truly hand held programmer that ships complete with all emulation leads, organiser-style manual, AC charger, spare library ROM, both DOS and Windows terminal software, and arrives fully charged and ready to go! Who else offers you all this plus a three year guarantee?

Customer support is second to none. The very latest programming library is always available free on the Internet, and on our dedicated bulletin boards. Customers NEVER pay for upgrades or technical support.

## Dataman-48

Our new Dataman-48 programmer adds PinSmart® technology to provide true no-adaptor programming right up to 48-pin DIL devices. Dataman-48 connects straight to your PC's parallel port and works great with laptops. Coming complete with an integral world standard PSU, you can take this one-stop programming solution anywhere!

As with S4, you get free software upgrades and technical support for life, so now you don't need to keep paying just to keep programming

The current device library contains over 1800 of the most popular logic and memory devices including GALs, PALs, CEPALs, RALs, 8 and 16-bit EPROMs, EEPROMs, PEROMs, FLASH, BOOT-BLOCK, BIPOLAR, MACH, FPGAs, PICs and many other Microcontrollers. We even include a 44-pin universal PLCC adaptor.

If you need to program different packaging styles, we stock adaptors for SOP, TSOP, QFP and SDIP. The Dataman-48 is also capable of emulation when used with memory emulation pods.

Order your Dataman programming solution today via our credit card hotline and receive it tomorrow. For more detailed information on these and other market leading programming products, call now and request your free copy of our new colour brochure.



£795 + VAT

**hotline**  
01300 320719



Orders received by 4pm will normally be despatched same day.  
Order today, get it tomorrow!

**DATAMAN**

Dataman Programmers Ltd, Station Road, Maiden Newton, Dorset DT2 0AE. UK  
Telephone +44/0 1300 320719 Fax +44/0 1300 321012 BBS +44/0 1300 321095 (24hr)  
Modem V.34/V.FC/V.32bis Home page: <http://www.dataman.com>  
FTP: <ftp.dataman.com> Email: [sales@dataman.com](mailto:sales@dataman.com)

CIRCLE NO. 10 ON REPLY CARD