

**FREE** temperature indicator strips

# ELECTRONICS WORLD

INCORPORATING WIRELESS WORLD

April 1996 £2.25

Austria Asch. 65.00  
Denmark DKr. 66.00  
Germany DM 15.00  
Greece Dra. 1000.00  
Holland Dfl. 14.50  
Italy L. 8500.00  
Malta Lm. 1.45  
IR £3.30  
Singapore S\$12.60  
Spain Pts. 800  
USA \$5.50

A REED BUSINESS PUBLICATION  
SOR DISTRIBUTION

**Cancer from pylons?**  
**Radon – and more...**

**Design an SSB  
outphaser**

**BT's caller ID  
via a PC**


**A new  
electronic  
device**

**22bit a-to-d  
for PC**

**Chopping a  
bridge brings  
benefits**

**Low-mass  
accelerometer**

**PC analogue interface – 25% discount**

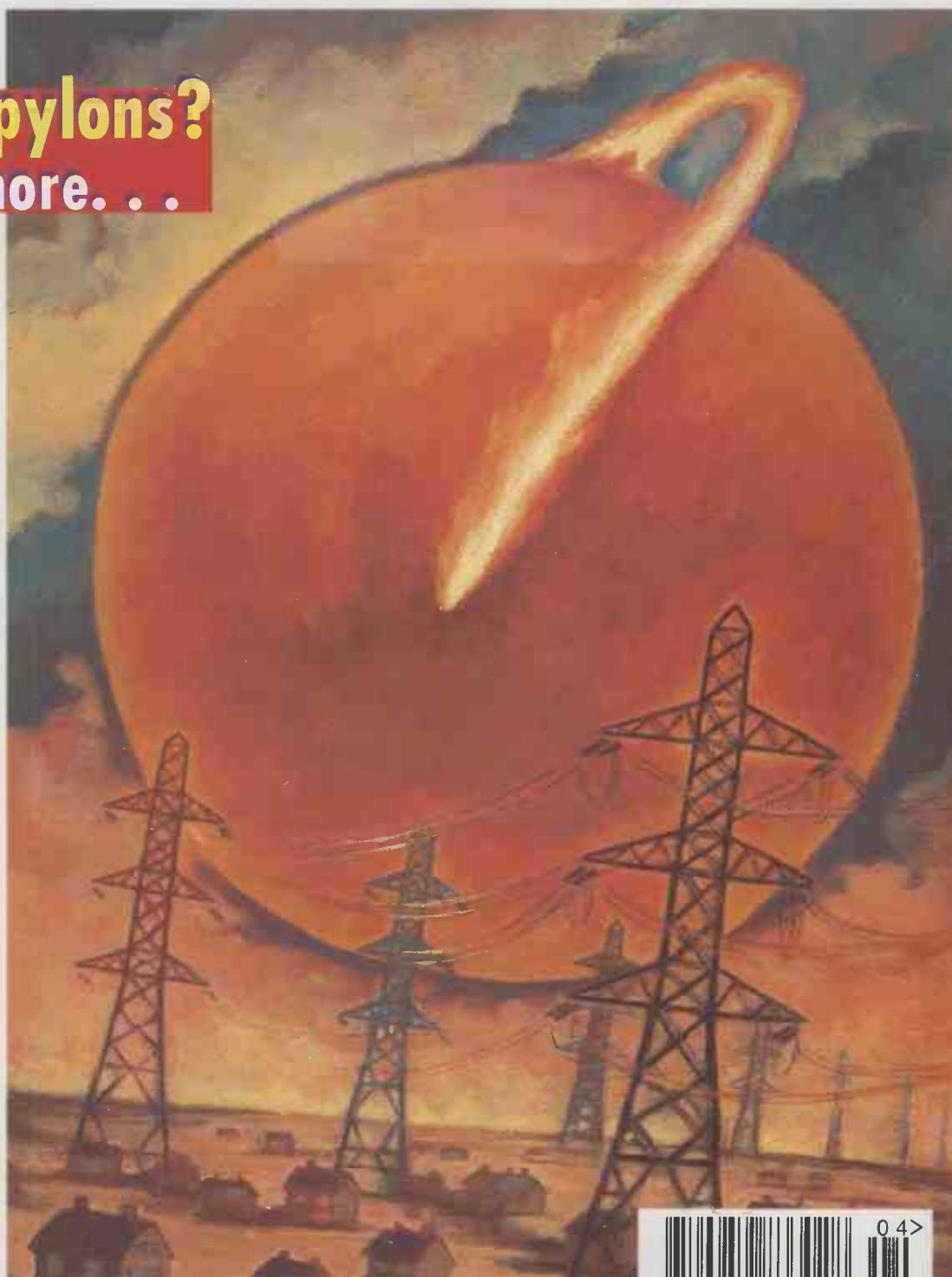

# NOW, THE BATTLE IS OVER

ULTIBOARD



## ULTIBOARD

**BUNDLED WITH**  **SPECCTRA**  
SHAPE BASED AUTOROUTER

ULTIboard's interactive strength has always been the major selection criterion of professional Printed Circuit Board designers. Now that every ULTIboard Designer system will be supplied with a SPECCTRA SP4 Autorouter, ULTIboard designers now get the best of both worlds.

All ULTIboard Designer Users with valid update subscription got a MAINTENANCE UPGRADE with the SPECCTRA SP4 (4 signal layers + power/ground layers) Shape based Autorouter. This shows that ULTIimate Technology is *the* PCB-Design Tool vendor that *really* cares for their customers!

**THE ULTIMATE  
SPECIAL OFFER**

**ULTIboard Entry Designer\* £ 1295 (excl. VAT) will now  
be supplied with SPECCTRA Shape Based Autorouter  
\*free Upgrade with EMC-EXPERT mid 1996 (list price at release £ 1875)**

CIRCLE NO. 101 ON REPLY CARD

**ULTIMATE**  
TECHNOLOGY

Corporate Headquarters:  
Energiestraat 36 • 1411 AT Naarden  
The Netherlands


tel.: (+31) 35 - 6944444  
fax: (+31) 35 - 6943345

UK/Ireland Sales-Office:  
2 Bacchus House • Calleva Park  
Aldermaston Berkshire • RG7 4QW

tel.: 01734 - 812030  
fax: 01734 - 815323

# Contents

Cover – Hashim Akib

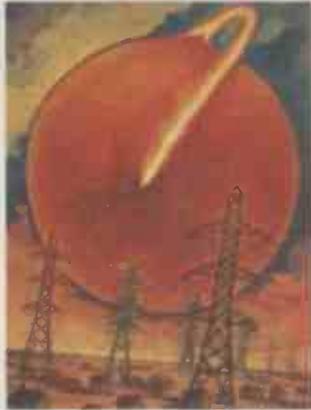

## 276 POWER LINES, PARTICLES AND CANCER

Recent reports have suggested that radon, focussed by power lines, could be linked to an increase of cancer in people living under power lines. Anthony Hopwood explains that there's more to it than that.

## 280 22BIT ANALOGUE-IN FOR PCS

Resolving analogue input to 22bits on a pc is not simply a matter of selecting the right a-to-d converter, as Simon Bateson and Andrew Woodward explain.

## 286 FAST CHARGER FOR NICD AND NIMH

Benefiting from a new high-side switching device this economical circuit allows fast charging of both NiCd and NiMH cells.

## 290 DESIGNING RIAA VALVE PREAMPS

Morgan Jones' discussion of valve preamplifiers culminates in a no-compromise balanced RIAA preamplifier combining the benefits of valves and transistors.

## 313 TWO CHIP SMART ACCELEROMETER

Silicon micro-machining has been used to produce a small, low-mass accelerometer with relatively low cost and repeatable, temperature-stable output.

## 300 TRANSMISSION LINE PRINCIPLES

Bill Russell shows how rectangular pulses and a delay line simplify the explanation of how transmission lines work.

## 304 HANDS-ON INTERNET

Cyril Bateman discusses how Archie and Gopher help you search the Net for files.

## 306 DESIGNING AN SSB OUTPHASER

Outphasers for SSB transmitters demand accurate component values, but analyses for such circuits are rare, by David Gibson.

## 296 ISSCC – THE HIGHLIGHTS

Roy Rubenstein reports on the world's top electronics innovation event.

## 317 TELEPHONE CALLER ID

Seggy Segaran looks at techniques used to relay the caller's telephone number to the destination 'phone.

## 341 CHOPPING BRIDGE

Basing a measuring bridge on a discrete chopper offers low-cost and high-stability.

# Regulars

## 267 COMMENT

In the interest of the customer.

## 268 NEWS

Panel minds language, Data protection for Internet, 1800MHz access, Pentium Pro flaw, MathWorks Wavelet Toolbox, PC security, 3D on PC

## 273 RESEARCH NOTES

Microactuator, Road rage, Quantum computing, Array design, Robot fingers, Universal remote control.

## 322 CIRCUIT IDEAS


Light measurement, **Current-conveyor crystal oscillator**, Servo driver, **Motor driver**, 24V counter from 12V, **Filters with no dc errors**, Linear phase detector.

## 330 LETTERS

V versus I feedback, Amplifier linearity, Component costs, Valve sound, Phase splitter, Windows, Question of the month, Foster Seeley detector, Sallen & Key.
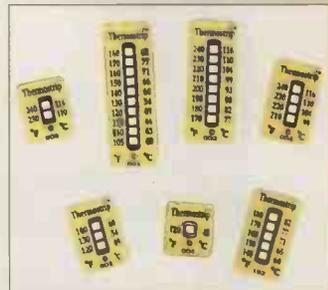
## 335 NEW PRODUCTS

Pick of the month – classified for convenience.



Obtain your free evaluation pack of one-time temperature indicator strips: page 312.



World's first 42in flat display: see page 268.

## 25% EW reader offer

Readers can obtain 25% discount on a high-precision a-to-d converter and its PC software: see page 284.



Researchers at MIT have incorporated road rage into a computer model allowing them to predict traffic flow more accurately – page 275.

## 15% DISCOUNT

Receive caller ID telephone numbers on your pc, log them and even manipulate them in Access – EW reader offer, page 319.

**MAY ISSUE**  
ON SALE APRIL 25

# The Universal Programmer that stands-alone



with everything you need. Don't buy your next programmer until you see the 'Eclipse'

- Windows and DOS user interface
- Unparalleled in speed & sophistication ideal for R&D and volume production
- 96 to 256 pin drivers
- Programs PLDs, EPLDs, FPGAs, PROMS, EPROMS, E/EPROMS, FLASH & Micros
- Universal DIP, PLCC, PGA and QFP modules - no more socket adaptors
- Stand-alone or remote operation

Europe's largest programmer manufacturer


call today on +44 (0)1707 332148 or fax +44 (0)1707 371503 for further information

All trade marks are acknowledged and respected



CIRCLE NO. 106 ON REPLY CARD

## COMPONENTS & SYSTEMS FROM IOSIS

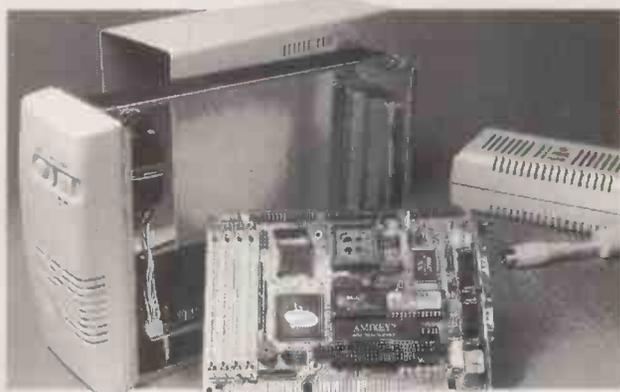

System Components from ISO9001 Source  
Half Size ISA Single Board Computers  
386SX-40 to 486DX4-100 with PC/104, 2 Serial Ports  
IDE & FDD & Printer Port  
and a variety of on-board functionality's:  
FLASH/ROM Disc. Cache. VGA CRT/Flat Panel Controller

PC/104 Modules:  
386 & 486 CPUs, Solid State Disc, Isolated RS232/485  
VGA CRT/Flat Panel Display & SVGA Controllers  
PCMCIA types I, II & III

System Enclosures with Passive Backplanes  
Colour & Mono Flat Panel LCD Displays  
System Integration and Support

2c Chandos Road, Redland  
Bristol, BS6 6PE  
Tel: 0117 973 0435  
Fax: 0117 923 7295




CIRCLE NO. 107 ON REPLY CARD



## Integrated PCB & Schematic Design System for Windows™

QUICKROUTE

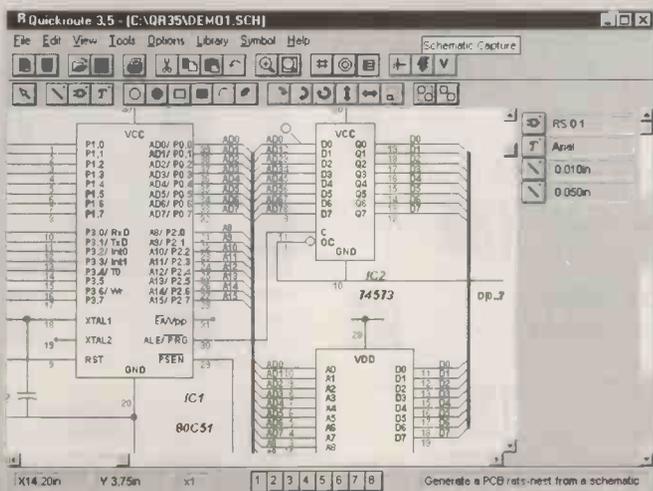

Quickroute 3.5 is a powerful, affordable and easy to use integrated schematic & PCB design system for Windows. With its multiple button bars, 'tool hints' and 'parts bin', Quickroute helps you to design quickly and efficiently

There are four different versions of Quickroute giving you a choice of features & price. Quickroute is available with multi-sheet schematic capture, auto-routing, 'engineering change' (modification of a PCB from a schematic), copper fill, and a range of file import/export options. See the table for a selection of features.

Prices are Designer (£149), PRO (£249) and PRO+ (£399). The Personal edition is available for just £68, but has the manual provided on disk as on-line help. Post & Packing is £5 (UK), £8 (EC), £12 (World). VAT must be added to the total price.

New Version 3.5

"..of all the products included here, this is my personal favourite... Really, thats all I have to say about Quickroute - it certainly gets my vote!"

Review of QR 3.0 & other products  
Computer Shopper Nov 95

Tel/Fax 0161 449 7101

Quickroute Systems Ltd., 14 Ley Lane, Marple Bridge,  
Stockport, SK6 5DD, U.K.

email info@quicksys.demon.co.uk

Prices and specifications subject to change without notice. All trade marks are acknowledged & respected.

	Personal	Designer	PRO	PRO+
PCB & Schematic Design	✓	✓	✓	✓
Schematic Capture	✓	✓	✓	✓
Auto router		✓	✓	✓
Design Rule Checking		✓	✓	✓
Export WMF & Iango		✓	✓	✓
Export Gerber/NC-Drill		✓	✓	✓
Extended Libraries		✓	✓	✓
Iango + Gerber Import		✓	✓	✓
Upgrade PCB from schematic		✓	✓	✓
DXF & SPICE Export		✓	✓	✓
Copper Fill		✓	✓	✓

CIRCLE NO. 108 ON REPLY CARD

# In the interest of the customer

## EDITOR

Martin Eccles  
0181 652 3128

## CONSULTANTS

Jonathan Campbell  
Philip Darrington  
Frank Ogden

## DESIGN

Alan Kerr

## EDITORIAL

### ADMINISTRATION

Jackie Lowe  
0181-652 3614

## E-MAIL ORDERS

jackie.lowe@rbp.co.uk

## ADVERTISEMENT MANAGER

Richard Napier  
0181-652 3620

## DISPLAY SALES EXECUTIVE

Malcolm Wells  
0181-652 3620

## ADVERTISING PRODUCTION

0181-652 3620

## PUBLISHER

Mick Elliott

## EDITORIAL FAX

0181-652 8956

## CLASSIFIED FAX

0181-652 8956

## SUBSCRIPTION HOTLINE

01622 721666  
Quote ref INJ

## SUBSCRIPTION QUERIES

01444 445566  
FAX 01444445447

## NEWSTRADE DISTRIBUTION

David G. Sanders  
0181 652 8171

## ISSN 0959-8332



It used to follow that what was good for the customer was good for profits. The customer must always come first. It is therefore surprising that the consumer software industry has a such bad record in this respect.

Of course, in any technology driven industry, such as computer software, customers have to be led somewhat. They have to be persuaded to give up their favourite DOS programme, for example, and move to something 'bigger and better', and in the long run it often really is a good move, in terms of speed and flexibility.

But that's not the real problem. What we have to contend with, quite frankly, is poor quality, over-selling and indifferent after sales service. The customer comes a poor second.

There's also little regard for the customer's equipment. Sloppy development results in applications requiring larger than necessary amounts of computer resources. Do programmes really need to be that big? Do we really have to have loads of ram? The software is delivered on a huge pile of disks, or increasingly on CD-rom. But the time is surely not far away when the setup instructions will read 'Place CD-rom #1 into drive and press enter'.

Maybe part of the problem is the impressive software development tools available today such as Visual Basic, Delphi and Visual C++. They enable surprisingly fast development of new products, but this tends to bring about a false sense of confidence. Prototypes can be up and running in hours and lots of features can be bolted on. But the more features and facilities that a programme has the more meticulous the testing has to be. Development tools can have bugs as well! Inadequate test methodology often results in uncertain interaction between applications. There is surely an analytical way of predicting how applications inter-react.

There have been cases recently when clearly product had been released before it was ready. Every industry is subject to commercial pressures, none more so than software. But shipment of immature product can cause misery. For example, a recently marketed operating system did not contain all the

device drivers it needed for Soundblaster and some CD-rom drives. The 'Plug and Play' feature became a nightmare. One punter, I heard of, tried to load the software from CD-rom. Half way though it stopped because it didn't recognise the CD-ROM drive. It left him in a total state of limbo that took days to sort out. I somehow don't think that he was alone.

Some products are hyped to a dangerously high level, raising customer expectations, only to have them dashed later. Of course, the software world is highly competitive and fast moving. Millions of dollars can be made overnight with the right break. Recent examples are Netscape and the UK company who wrote some software that would bar child access to dubious parts of the Internet.

I've heard it said that the marketing costs for any software package start at around half a million pounds. It's hard to do it for less, which makes it high risk. But looking at it from the user point of view, we need to know whether the programme really will run on a 386 with 4 Meg of ram, for example, and what applications will it not work with? We should not have to rely on the software press to tell us these things.

Now a gripe about customer support. How often have you heard from a support line "We know about the bug, there are no real workarounds, but it will be corrected in the next version". And how long do you have to wait for an answer? Furthermore, companies who used to have free call facilities on 0800 are now migrating to the more lucrative 0898 lines at the customer's expense.

Coupled with this, companies only usually give 'Limited Warranties' with their software packages. These warranties cover the cost of the floppy disks and maybe the original cost of the software but little else. There is little or no liability if it doesn't work to your satisfaction. It would be

interesting if this situation could be tested in court to see if customer's 'statutory rights' were being upheld - it would probably uncover a can of worms! Maybe the answer is some sort of code of practice whereby customers could obtain bug-fixes free of charge by mail or download for at least a year after purchase.

Any improvements in quality and customer service will inevitably cost money and companies will try pass it on to their customers in some way. But I think that it is a price worth paying. Software represents a large investment



for individuals and companies alike, and we are becoming more and more dependent on it.

Quite soon software will be available that will take decisions for us, called 'software agents'. What if they don't work properly! I think that there is still a 'start-up' and 'get rich quick' mentality in the software business. After all it's one of those few industries that even today can be started in the garage or spare bedroom. The focus is firmly on developing product as quickly as possible and getting it out of the door before anyone else does the same. Support does not really feature much.

However, the software industry has come a long way, and the lead needs to be taken by the large companies to improve customer service and set an example. Maybe survival will depend on it one day. Quality and customer service issues are not as glamorous as the technology, but they need attention - now.

Peter Marlow

Electronics World is published monthly. By post, current issue £2.35, back issues (if available) £2.50. Orders, payments and general correspondence to L333, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Tlx: 892984 REED BP G. Cheques should be made payable to Reed Business Publishing Group. Newstrade: Distributed by Marketforce (UK) Ltd, 247 Tottenham Court Road London W1P 0AU 0171 261-5108. Subscriptions: Quadrant Subscription Services, Oakfield House Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address. Subscription rates 1 year £30 UK 2 years £48.00 3 years £70.00. Surface mail 1 year £35.00 2 years £56.00 3 years £80.00 Air mail Europe/Eu 1 year

£43.00 2 years £68.00 ROW 1 year £52.00 2 years £83.00 Overseas advertising agents: France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel: (212) 679 8888 Fax: (212) 679 9455 USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. 2nd class postage paid at Rahway NJ Postmaster. Send address changes to above. Printed by BPCC Magazines (Carlisle) Ltd, Newtown Trading Estate Carlisle. Cumbria, CA2 7NR Typeset by Wace Publication Imaging 2-4 Powerscott Road, Sidcup, Kent DA1 4 SDT. Reed Business Publishing Ltd 1996 ISSN 0959 8332

## Mosfets enhance video compression

Mosfets used directly as calculators could simplify video compression systems following work at the Defence Research Agency, DRA, in Malvern.

DRA has used a twin floating gate mosfet circuit as a vector quantiser to calculate the Euclidean distance between two points. The floating gate device, fabricated using standard foundry processes, exploits a characteristic that is comparable to the Euclidean distance metric.

Gillian Marshall, a member of the research team said: "With standard analogue systems feeding a digital signal processor (DSP), there is a large bottleneck at the analogue to

digital converter. The new vector quantiser does all the calculations in analogue, only converting the final compressed data to digital for transmission."

The benefits claimed for the approach include a computation rate 20 times that of typical digital signal processors and a power consumption that is less than one-tenth.

Applications that could benefit from the approach include video conferencing where large amounts of analogue information is transmitted down telephone lines, and cost sensitive systems where a fast A/D converter is too costly.

The scheme exploits the fact that

current through the fet is proportional to the square of the difference between the gate voltage and the threshold voltage. In turn, the Euclidean distance squared equals the square of the difference between an input point and a reference point. Hence, if the input point, represented as a voltage, is applied to the gate and the reference is the threshold, the distance measure is proportional to the device's current.

Various parts of the VQ have been constructed by the research team, and have worked well. However a full scale system will have to wait for further funding.

## Chaos keeps communications secure

Chaos theory promises the ultimate in secure communications, enabling systems to emit signals indistinguishable from background noise.

Researchers at the University of Birmingham's school of electronic and electrical engineering have developed a communications system that chaotically encodes a digital data stream. At the same time, it hides the signal within a noise-like structure. This is desirable especially for military applications where the 'enemy' would not even know communications are taking place.

Dr Jim Edwards, leading the research said: "Encoded signals may

look like noise, but are in fact deterministic if both the structure of the encoder and the initial conditions are known. Being short of one or both of these makes prediction difficult."

He further pointed out that traditional 'secure' systems are not in fact because enough information is available for signal reconstruction.

The chaos system offers enhanced security since the initial conditions must be known exactly. Any slight difference and the system quickly diverges. This is comparable with the chaos theory example that says weather cannot be predicted without knowing all the starting conditions which may include a butterfly's wings

beating in Australia.

The claimed bit error rate (BER) of the current system is 1 in 10,000 at a signal-to-noise ratio of 10dB. The University is working on a system where an acceptable BER is obtained for negative signal-to-noise; in other words, the noise has more power than the signal. This would give truly undetectable communications.

Synchronising the transmitter and receiver, critical with chaotic systems, is not a problem according to Edwards: "Because the system is digital, it tends to self-synchronise."

**Richard Ball**  
*Electronics Weekly*



**Plasma displays for wall mount tvs.** The first plasma displays suitable for use in tvs will be mass-produced by Fujitsu from October at an initial \$5000 price tag.

The displays are the world's only 42in plasma panels available commercially. Although the company has had 21in displays available for two years, they are considerably more expensive than crts and are not used by tv makers.

At 42in, however, the screens are bigger than crts and, naturally much thinner. Fujitsu's panel is only 75mm thick, allowing a tv to be hung on the wall. The company is currently supplying panel samples to tv manufacturers, including Thomson, Nokia, Philips and Bang and Olufsen in Europe.

Unlike thin-film transistor alternatives, plasma displays have a wide viewing angle and are therefore useful for public information displays as well as tvs.

## 3D graphics add-on for pcs

VideoLogic will be selling this summer a £300 add-on card that brings 3D picture realism to pcs. At the heart of the boards will be a 3D graphics processor which the UK company has developed in partnership with NEC.

The two companies have adopted an approach to 3D rendering which reduces the high speed synchronous dynamic ram buffer memory requirement, and removes a fundamental memory bandwidth bottleneck.

"The consequence of no longer requiring z-buffer memory can result in a \$30 to \$60 saving in s-d-ram cost," said Trevor Wing, VideoLogic's group marketing director.

In the PowerVR 3D rendering architecture, VideoLogic has removed the need for storing picture depth information in a z-buffer. Instead, it implements in real-time the necessary hidden surface calculations. According to Wing this is possible because the design uses an array of 32 processor elements which can operate on each pixel

independently.



The NEC chips will hit the market at the same time as another UK-developed 3D graphics processor, the Permedia from 3DLabs.

NEC has integrated the complete hidden surface and polygon texturing functions into two devices which require just 2Mbyte of synchronous d-ram buffer memory. NEC will start sampling the first chips this quarter and a single chip version for the pc market will be available by the summer.

In contrast, 3DLabs' Permedia chip incorporates a 16-bit z-buffer, and also has an overall s-d-ram requirement of 2Mbyte. It is targeted at \$300 pc add-on card designs.

The first pcs to incorporate the NEC chip set will be launched next year, according to Wing, who added: "Two of the big three pc suppliers are already evaluating the 3D chips." VideoLogic has existing video partnerships with IBM and Compaq Computer.

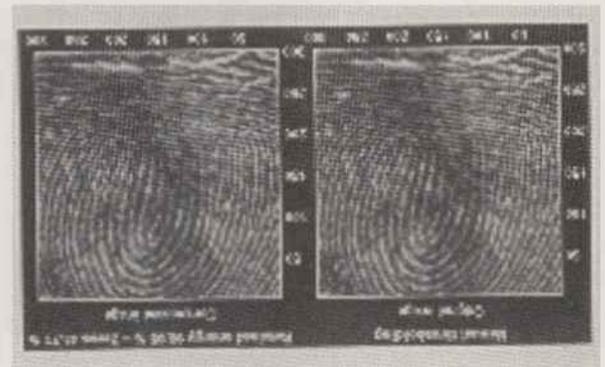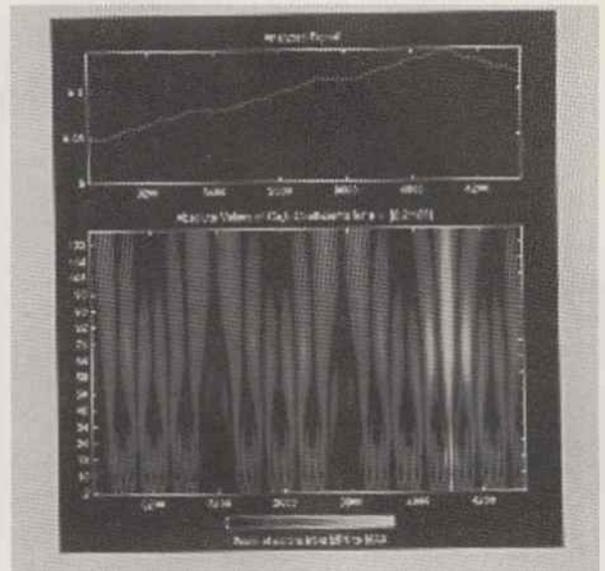**Richard Wilson**  
*Electronics Weekly*



## Slow but less volatile growth for semiconductors

The semiconductor market will grow more slowly, but with reduced volatility. So says Sergio Vicari, European application specific product manager of Texas Instruments. For Vicari the main source of growth will be computer sales: "The increasing electronic content of products, as well as emerging markets will also contribute."

He predicts that computer sales will rise from just under 100 million units in 1996 to some 200 million by 2000. The increasing semiconductor content is extrapolated from the trends over the past two decades. His figures show growth of 4.8 per cent per year in the eighties rising to 6.3 per cent per year in the nineties.

What of the total semiconductor market? Vicari said: "It depends on the industry growth. Fifteen per cent per year will mean the market is \$275bn by 2000, 20 per cent will take it to \$350bn."

Digital signal processing chips is one of TI's core businesses and these come under Vicari's wing. "The driving force for dsp sales comes from wireless communication products and hard disc drives, but high efficiency motor controllers are likely to become a large sector."

Electric motors currently consume 50 percent of the world's electricity. dsp based controllers will double their efficiency, Green pressures and lifetime costing are making them popular in new installations.

"The DSP market grew 68 percent to \$1.6bn in 1995 and I predict this will increase to \$9.4bn by 2000. During this time the unit cost of a DSP will drop from \$12.2 to \$8.8."

However, he admits the difficulty in predicting the DSP market: "The 1994 prediction for 2000 was between \$6bn and \$7bn."

*MathWorks has announced a toolbox claimed to be the first product to make wavelet analysis a practical engineering tool.*

*In these photographs, wavelets have been used to compress and decompress fingerprint data with little degradation, and fractal signals are decomposed with various scales (stretches) of wavelet.*

*Wavelet transforms are an up-and-coming technique for data compression and analysis. They transform signals into a sum of small, overlapping waves and are claimed to be more effective for analysing non-continuous waveforms than traditional Fourier methods.*

*In addition to supporting advanced applications, the Wavelet Toolbox is said to offer engineers unfamiliar with wavelets an easy way to try out the transforms on their own problems.*

## Experts to pick design language

The protracted process of defining analogue circuit modelling extensions to the VHDL digital system design language reaches a crucial point this week. A panel of experts will be presented with two competing proposals for a language specification.

The IEEE 1076.1 language design committee is to ask independent experts and users to choose between the Jade language, championed by Mentor Graphics' subsidiary Anacad, and the Opal alternative, supported by Analog, Cadence and Compass Design.

The experts will make a choice by the end of March with a full Language Reference Manual, LRM, to follow by July. An IEEE ballot on the LRM could then be completed in the following six months.

Andy Patterson, Analog's European technical director, said most arguments appeared to be supporting Opal and he was hopeful a firm choice would be made on schedule. "The committee is being spurred by the analogue Verilog efforts with Verilog-A having been published this month," he said.

## Pentium Pro flaw

In the same way that the famous Pentium flaw was first brought to public attention by an academic – Professor Nicely – another professor from San Francisco State University has pointed out a flaw associated with the Pentium's successor – Pentium Pro.

Intel conceded last week that it had not responded properly to the professor but claims that the 'few complaints' it has received result from incorrect use.

The reported problems arise when the Orion chip-set is used with the Pentium Pro microprocessor in server applications.

According to Intel they only arise when certain add-on cards – which

are not recommended for use by Intel – are used in the application.

It was claimed that Pentium Pro servers made using the Orion chip-sets were resulting in systems that operated at half the speed of previous generation Pentiums.

Intel concedes that the add-on cards can cause problems with the Pentium Pro/Orion combination resulting in sluggish performance but says there is nothing wrong with Orion and that it is not being re-engineered to speed up performance.

However, the company intends, later this year, to launch a new chip-set for use in Pentium Pro-based servers.

### Non-slewing

Giovanni's article 'Non-slewing power amplifier' in the March issue contained a couple of minor inaccuracies. In Fig. 1, there should be no 200Ω resistor in the right-hand CSA circuit. In Fig. 4, the unmarked resistor is 3.3kΩ. Apologies.

## Campaign for anti-theft chips

In response to the fastest growing area of crime in the UK, the magazine *Computer Weekly* has begun an anti-chip theft campaign bringing together the police, chip makers, insurance firms and computer manufacturers and buyers.

The idea of the scheme is threefold: to show computer owners how to secure their equipment, to lobby chip and module makers to mark their products, and promote anti-theft techniques.

The valuable parts of a computer are the simms and, to a lesser extent, the cpu. The police have already produced advice to computer owners to assist them in securing their property.

The real breakthrough will come with simms that are tagged or become unusable away from their host.

Metropolitan police commissioner

Sir Paul Condon said: "I truly believe that if consumer goods can be designed and manufactured so that they are useless to anyone other than the owner, then we could bring about a complete reversal of the figures."

Marking, tagging or putting intelligence onto the simm pcb would seem to be a waste of time as mobile phone thieves already 're-chip' their swag. This involves removing the identification prom from the phone and replacing it with one holding another identity. There is therefore no reason to believe that simm thieves could not transfer chips to new pcbs.

The need is for memory chip makers to incorporate some form of security device into the chips, but this seems unlikely until the voice of the user becomes impossible to ignore. Steve Bush, *Electronics Weekly*

## 1800MHz access for cellular carriers

Cellular operators Vodafone and Cellnet have succeeded in gaining access to radio frequencies in the 1800MHz band – a move seen as crucial in their battle with newer operators Orange and Mercury One-2-One.

"This is important to us and we intend to use any spectrum for new products and areas (of coverage)," said a spokesman for Vodafone.

As well as reserving two 10MHz blocks in the 1800MHz band for possible allocation to Orange and Mercury at the end of 1997, the government intends to make two further 11.5MHz blocks available to Vodafone and Mercury. This will be first access to the relatively under-populated 1800MHz band for Vodafone and Cellnet which depend on the increasingly congested spectrum below 900MHz for their analogue and digital GSM services.

"The government wants to set out a strategy for a fair allocation of spectrum on the basis of need between all four mobile phone operators," said science and technology minister Ian Taylor.

Vodafone and Cellnet intend to move all users from their older and cheaper analogue networks to digital services by the year 2005. This will lead to greater congestion in the digital 900MHz bands, as four out of five UK mobile phone users are connected to analogue networks.

As well as seeking proposals for new use of the 1800MHz band the government will also make additional frequencies in the 900MHz band available to the two operators.

Managing the move from analogue to digital is the biggest challenge for Vodafone and Cellnet who, like all operators, are facing falling profitability, according to market researcher CTT. RW, *Electronics Weekly*

## In Brief

### Interactive traffic information

Japan is to launch the world's first on-line interactive traffic information service that uses telephone lines in April this year. Dubbed Advanced Traffic Information Service (ATIS), the system will supply information to pcs and in-car units via land lines and cellular links.

### Power pc off the desktop at IBM

In a review of the future of PowerPC, IBM is reported to have decided to de-prioritise the microprocessor as a cpu for desktop personal computers.

Instead, IBM is said to be concentrating on Intel's x86 for desktop pcs and is focusing its PowerPC effort on workstation and server applications and as an embedded microcontroller.

### EMC testing backlog

EMC test houses are heavily oversubscribed – many up to six months in advance, now that the EMC directive is in force.

ERA Technology's civil test facility in Leatherhead is currently booked until August and SGS in Durham is full until July and both are working three shifts per day. Test slots are booked on a first come/first serve basis.

Any company committed to using test houses to CE mark their products, and expend their time slot with incomplete tests or a failed product, may find themselves out in the cold.

### Windows for hand-helds

Several major computer and telecommunications companies are planning to introduce hand-held computer devices based on a secret operating system under development at Microsoft.

The operating system, code-named Pegasus, is Microsoft's third attempt to develop a small operating system based on Windows for use in handheld computers and smart telecommunications devices.

Microsoft is expected to unveil Pegasus by the middle of this year. ■

## HART AUDIO KITS - YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

Hart Audio Kits and factory assembled units use the unique combination of circuit designs by the renowned John Linsley Hood, the very best audiophile components, and our own engineering expertise, to give you unbeatable performance and unbelievable value for money. We have always led the field for easy home construction to professional standards, even in the sixties we were using easily assembled printed circuits when Heathkit in America were still using tagboards! Many years of experience and innovation, going back to the early Dinsdale and Bailey classics gives us incomparable design background in the needs of the home constructor. This simply means that building a Hart kit is a real pleasure, resulting in a piece of equipment that not only saves you money but you will be proud to own. Why not buy the reprints and construction manual for the kit you are interested in to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase.

### K1100 AUDIO DESIGN 80 WATT POWER AMPLIFIER.



This fantastic John Linsley Hood designed amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hifi system. This kit is your way to get UK performance at bargain basement prices. Unique design features such as fully FET stabilised power supplies give this amplifier World Class performance with startling clarity and transparency of sound, allied to the famous HART quality of components and ease of construction.

Useful options are a stereo LED power meter and a versatile passive front end giving switched inputs, with ALPS precision Blue Velvet low-noise volume and balance controls. Construction is very simple and enjoyable with all the difficult work done for you, even the wiring is pre-terminated, ready for instant use! All versions are available with Standard components or specially selected Super Audiophile components at £29.60 extra per channel, plus u2.40 if you want to include Gold Plated speaker terminals.

K1100B Complete STANDARD Amplifier Kit, .....	£395.21
A1100B Factory Assembled, .....	£499.21
K1100SC Complete SLAVE Amplifier Kit, .....	£333.62
A1100SC Factory Assembled, .....	£422.62
K1100M Complete MONOBLOC Amplifier Kit, .....	£261.20
A1100M Factory Assembled, .....	£329.20
RLH11 Reprints of latest Amplifier articles, .....	£1.80
K1100CM Construction Manual with full parts lists, .....	£5.50

### "CHIARA" SINGLE ENDED CLASS "A" HEADPHONE AMPLIFIER.



This unit provides a high quality headphone output for 'stand alone' use or to supplement those many power amplifiers that do not have a headphone facility. Easily installed with special link-through feature the unit draws its power from our new Andante Ultra High Quality linear toroidal supply. Housed in the neat, black finished, Hart minibox it features the wide frequency response, low-distortion and 'musicality' that one associates with designs from the renowned John Linsley Hood. Pre-terminated interconnecting leads and PCB mounted sockets prevent supply polarity reversal and on-board diagnostics provide visual indication of supply line integrity. Volume and balance controls are Alps "Blue Velvet" components. Very easily built, even by beginners, since all components fit directly on the single printed circuit board. The kit has very detailed instructions, and even comes with a complementary roll of Hart audiograde silver solder. It can also be supplied factory assembled and tested. Selling for less than the total cost of all the components, if they were bought separately, this unit represents incredible value for money and makes an attractive and harmonious addition to any hifi system.

K2100 Complete Kit, .....	£109.50
K2100SA Series Audiophile version with selected audiophile components, .....	£112.46
A2100SA Series Audiophile version, factory Assembled, .....	£149.46
K3565 "Andante" Power Supply Kit to suit "Chiara", .....	£85.42
A3565 Power Supply, Factory Assembled, .....	£128.42
CM2100 Construction Manual, .....	£2.50
SPECIAL OFFER. Both units together, Kit Form, .....	£184.92
Factory Assembled and Tested, .....	£267.88

### "Andante" SERIES 20VA AUDIOPHILE POWER SUPPLIES


Specially designed for exacting audio use requiring absolute minimum noise, low hum field and total freedom from mechanical noise this unit is a logical development from our highly successful 1550 series.

Utilising linear technology throughout for smoothness and musicality makes it the perfect partner for any module requiring fully stabilised  $\pm 15v$  supplies.

Two versions are available. K3550 has 2  $\pm 15v$  supplies and a single 15v for relays etc, and can be used with our K1400 preamp and our K1450 RIAA pickup preamp, as well as other useful modules soon to be introduced. The K3565 is identical in appearance but only has the  $\pm 15v$  lighter current supply for use with the K1450 RIAA pickup pre amplifier or "Chiara" headphone amplifier.

K3550 Full Supply with all outputs, .....	£93.75
K3565 Power Supply for K1450 & K2100, .....	£85.42
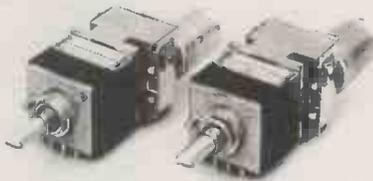
### ALPS "Blue Velvet" PRECISION AUDIO CONTROLS.



Now you can throw out those noisy ill-matched carbon pots and replace with the famous Hart exclusive ALPS "Blue Velvet" range components only used selectively in the very top flight of World class amplifiers. The improvement in track accuracy and matching really is incredible giving better tonal balance between channels and rock solid image stability. Motonsed versions have 5v DC motor.

**MANUAL POTENTIOMETERS**

2-Gang 100K Lin, .....	£15.67
2-Gang 10K, 50K or 100K Log, .....	£16.40
2-Gang 10K Special Balance, zero crosstalk and zero centre loss, .....	£17.48

**MOTORISED POTENTIOMETERS**

2-Gang 20K Log Volume Control, .....	£26.20
2-Gang 10K RD Special Balance, zero crosstalk and less than 10% loss in centre position, .....	£26.98

### TECHNICAL BOOKSHELF

NEW! Another Classic by John Linsley Hood. "AUDIO ELECTRONICS" Following the enormous ongoing success of his "Art of Linear Electronics" the latest offering is the all-new edition of "Audio Electronics", now entirely re-written by the master himself. Underlying audio techniques and equipment is a world of electronics that determines the quality of sound. For anyone involved in designing, adapting or using digital or analogue audio equipment understanding electronics leads to far greater control over the reproduced sound. The subjects covered include tape recording, tuners, power output stages, digital audio, test instruments and loudspeaker crossover systems. John's lifetime of experience and personal innovation in this field allow him to apply his gift of being so familiar with his subject that he can write clearly about it and make it both interesting and comprehensible to the reader. Containing 240 pages and over 250 line illustrations this new book represents great value for money at only .....

£18.99
--------

### "THE ART OF LINEAR ELECTRONICS."

The definitive linear electronics and audio book by John Linsley Hood. This 300+ page book will give you an unparalleled insight into the workings of all types of audio circuits. Learn how to read circuit diagrams and understand amplifiers and how they are designed to give the best sound. The virtues and vices of passive and active components are examined and there are separate sections covering power supplies and the sources of noise and hum. As one would expect from this writer the history and derivation of audio amplifier circuitry have an entire chapter, as does test and measurement equipment. Copiously illustrated this book is incredible value for the amount of information it contains on the much neglected field of linear, as opposed to digital, electronics. Indeed it must be destined to become the standard reference for all who work, or are interested in, this field. Latest reprinted edition with extended index. 1994 344 Pages. 247 x 190. 1Kg. 0-7506-0868-4. .....

£16.95
--------

"DIGITAL AUDIO AND COMPACT DISC TECHNOLOGY" 0-7506-0614-2 .....	£17.95
INTRODUCING DIGITAL AUDIO CD, DAT AND SAMPLING. ISBN 1870775 22 8 .....	£7.95
"THE ART OF SOLDERING" 0-85935-324-3 0 .....	£3.95
"TOWERS' INTERNATIONAL TRANSISTOR SELECTOR" 0-572-01062-1 .....	£19.95
"AUDIO" FA Wilson. BP111 .....	£3.95
"HOW TO USE OSCILLOSCOPES & OTHER TEST EQUIPMENT" R.A. Penfold. BP267, .....	£3.50
"THE LOUSPEAKER DESIGN COOKBOOK" Vance Dickason, .....	

(4th Edn.) 0-9624-191-7-6 .....	£22.95
ELECTROSTATIC LOUSPEAKER DESIGN AND CONSTRUCTION Ronald Wagner BKT6 .....	£18.95
"AN INTRODUCTION TO LOUSPEAKERS & ENCLOSURE DESIGN" V. Capel. BP256 .....	£2.95
"LOUSPEAKERS FOR MUSICIANS" BP297 .....	£3.95
"THE HART PRINTED CIRCUIT BOARD CONSTRUCTION GUIDE." .....	£2.50

### VALVE & EARLY CLASSIC BOOKS

THE VTL BOOK David Manley BKT1 .....	£17.95
LOUSPEAKERS; THE WHY AND HOW OF GOOD REPRODUCTION. G.Biggs. 1949 0-9624-1913-3 .....	£8.95
MULLARD TUBE CIRCUITS FOR AUDIO AMPLIFIERS BKAA27 .....	£13.95
"THE WILLIAMSON AMPLIFIER." 0-9624-1918-4. ....	£6.95
AN APPROACH TO AUDIO FREQUENCY AMPLIFIER DESIGN. GEC 1957, 1-882580-05-2 .....	£18.95
AUDIO ANTHOLOGIES, articles from Audio Engineering. Six volumes covering the days when audio was young and valves were king! BKAA3/1 to 6. All .....	£13.95 each.
"A SIMPLE CLASS A AMPLIFIER" J.L. Linsley Hood M.I.E.E. 1969. RLH12 .....	£2.50

Postage on all books, unless starred, is only u1 50 per book, maximum u4.50 for any number, any size! Starred items are heavy books costing .....


£2.50 to send.
----------------

No waiting! All listed books are normally in stock!  
SPECIAL OFFER. All book orders over £15 will receive a FREE John Linsley Hood monograph entitled "Digital versus Analogue, Black Disks or Silver?"

### SPECIAL OFFER PRECISION Triple Purpose TEST CASSETTE TC1D.

Are you sure your tape recorder is set up to give its best? Our latest triple purpose test cassette checks these three most important tape parameters without test equipment. Ideal when fitting new heads. A professional quality, digitally mastered test tape at a price anyone can afford. Test Cassette TC1D. Our price only, .....

£9.99.
--------

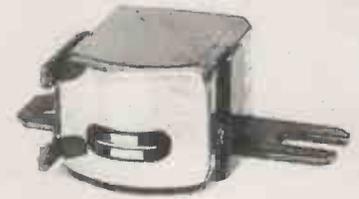

### HC80 Replacement Stereo Cassette Head.

The excellent performance of modern cassette recorders depends totally on the quality of the R/P head. Even the slightest amount of wear can impair the frequency response and distortion levels. Our HC80 is atop quality head from one of the foremost manufacturers in Japan, easily fitted to most standard stereo recorders (except Sony) and will transform the performance over a worn head. Only the fact that we buy these in vast quantities enables us to offer them at the amazing price of only £11.70 each or 2 for £17.60. We also stock a range of other heads, including "reel-to-reel stereo heads.

### SOLDERING

The size of modern components makes the right soldering equipment essential for good results. Everything we offer we actually use in our own workshops! See our Lists for the full range. 845-820 XS240 ANTEX 240v 25w Soldering Iron. This is the ideal Multi-purpose iron as the bit is designed to totally surround the element giving the best heat transfer. This excellent design also means that although it is small and handy enough for modern components its heating capacity is better than larger irons of conventional construction. Excellent Value .....

£9.93
-------

845-080 ST4 Lightweight Soldering Iron Stand. This has provision for the classic damp sponge for bit wiping .....

£3.95
-------

### HART SUPER AUDIOGRADE SILVER SOLDER.

Hart Super Audiograde Silver Solder has been specially formulated for the serious audiophile. Not only does it give beautiful easy-to-make joints but it is designed to melt at normal soldering temperatures avoiding the possibility of thermal damage to components or the need for special high temperature irons. A very low residue flux makes perfect joints easy but eliminates the need for board cleaning after assembly.

845-007 3mtrs 22SWG in Hart Mini Tube .....	£3.90
845-008 100g. Reel Special Valve Grade, 20swg .....	£12.90
845-009 100g. Precision PCB Grade, 22swg .....	£14.75
845-110 100g Reel Superline 24swg for ultra precise control and easy working .....	£21.45

QUALITY AUDIO KITS

24 hr. SALES LINE (01691) 652894

ALL PRICES INCLUDE UK/EC VAT

CIRCLE NO. 109 ON REPLY CARD

**SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK**

- HP New Colour Spectrum Analysers  
 HP141T+8552B IF + 8553B RF - 1KHz-110Mc/s-£700.  
 HP141T+8552B IF + 8554B RF - 100KHz-1250Mc/s-£900.  
 HP141T+8552B IF + 8556A RF - 20Hz-300KHz-£700.  
 Special Offer just in from MOD Qty 40 HP8555A RF Units 10Mc/s-18GHz.S.  
 HP141T+8552B IF + 8555A 10Mc/s-18GHzS-£1200.  
 HP ANZ Units Available separately - New Colours - Tested  
 HP141T Mainframe - £350.  
 HP8552B IF - £300.  
 HP8553B RF 1KHz to 110Mc/s - £200.  
 HP8554B RF 100KHz to 1250Mc/s - £500.  
 HP8555A RF 10Mc/s to 18GHzS - £800.  
 HP8556A RF 20Hz to 300KHzS - £250.  
 HP8443A Tracking Generator Counter 100KHz-110Mc/s - £300.  
 HP8445B Tracking Prescaler/DC to 18GHz - £350.  
 HP3580A 5Hz - 50KHz ANZ - £750 - £1000.  
 HP3582A .02Hz to 25.6KHz - £2k.  
 HP8568A 100Hz-1500Mc/s ANZ - £6k.  
 HP8569B 10Mc/s-22GHz ANZ - £6k.  
 HP Mixers are available for the above ANZ's to 40GHz  
 TEK 492 - 50KHz - 18GHz Opt 1+2 - £4k-£4.2k.  
 TEK 492 - 50KHz - 18GHz Opt 1+2+3 - £4.5k.  
 TEK 492P - 50KHz - 21 GHz Opt 1+2+3 - £5k.  
 TEK 494AP 1Kc/s - 21GHz - £7k.  
 TEK 496P 1KHz-1.8GHz - £4k.  
 TEK 5L4N Q-100KHz - £400.  
 TEK 7L5 + L1 - 20Hz-5Mc/s - £700.  
 TEK 7L5 + L3 - Opt 25 Tracking Gen - £900.  
 TEK 7L12 - 100KHz-1800Mc/s - £1000.  
 TEK 7L18 - 1.5-60GHz - £1500.  
 TEK 491 10Mc/s-12.4GHz-40GHz - £750. 12.4GHz-40GHz with Mixers.  
 Tektronix Mixers are available for above ANZ to 60GHz  
 Systron Donner 763 Spectrum ANZ + 4745B Preselector .01-18GHz + Two Mixers 18-40GHz in Transit Case - £3k.  
 HP8673D Signal Generator .05-26.5GHz - £20k.  
 Systron Donner 161BB Microwave AM FM Synthesizer 50Mc/s 2-18GHz  
 R&S SWP Sweep Generator Synthesizer AM FM 4-2500Mc/s - £3.5k.  
 ADRET 3310A FX Synthesizer 300Hz-60Mc/s - £600.  
 HP8640A Signal Generators - 1024Mc/s - AM FM - £800.  
 HP3717A 70Mc/s Modulator - Demodulator - £500.  
 HP8651A RF Oscillator 22Kc/s - 22Mc/s.  
 HP5316B Universal Counter A+B  
 HP6002A Power Unit 0-10V-10A 200W.  
 HP8625A Bipolar Power Supply Amplifier.  
 HP461A-465A-467A Amplifiers.  
 HP81519A Optical Receiver DC-400Mc/s.  
 HP Plotters 7470A-7475A.  
 HP3770A Amplitude Delay Distortion ANZ.  
 HP3770B Telephone Line Analyser.  
 HP8182A Data Analyser.  
 HP59401A Bus System Analyser.  
 HP6260B Power Unit 0-10V 0-100 Amps.  
 HP3782A Error Detector.  
 HP3781A Pattern Generator.  
 HP3730A+3737A Down Converter Oscillator 3.5-6.5GHz.  
 HP Microwave Amps 491-492-493-494-495-1GHz-12.4GHz - £250.  
 HP105B Quartz Oscillator - £400.  
 HP5087A Distribution Amplifier.  
 HP6034A System Power Supply 0-60V 0-10A-200W - £500.  
 HP6131C Digital Voltage Source - 100V 1/2 Amp.  
 HP4275A Multi Frequency L.C.R. Meter.  
 HP3779A Primary Multiplex Analyser.  
 HP3779C Primary Multiplex Analyser.  
 HP8150A Optical Signal Source.  
 HP1630G Logic Analyser.  
 HP5316A Universal Counter A+B.  
 HP5335A Universal Counter A+B+C.  
 HP5950 1B Isolated Power Supply Programmer.  
 HP8901A Modulation Meter AM-FM - also 8901B.  
 HP5370A Universal Time Interval Counter.  
 Marconi TF2370 - 30Hz-110Mc/s 750HM Output (2 BNC Sockets+Resistor for 500HM MOD with Marconi MOD Sheet supplied - £650.  
 Marconi TF2370 30Hz-110Mc/s 50 ohm Output - £750.  
 Marconi TF2370 as above but late type - £850.  
 Marconi TF2370 as above but late type Brown Case - £1000.  
 Marconi TF2374 Zero Loss Probe - £200.  
 Marconi TF2440 Microwave Counter - 20GHz - £1500.  
 Marconi TF2442 Microwave Counter - 26.5GHz - £2k.  
 Marconi TF2305 Modulation Meter - £2.3k.  
 Rascal/Dana 2101 Microwave Counter - 10Hz-20GHz - £2k.  
 Rascal/Dana 1250-1261 Universal Switch Controller + 200Mc/s PI Cards.  
 Rascal/Dana 9303 True RMS Levelmeter+Head - £450. IFFE - £500.  
 TEKA6902A also A6902B Isolator - £300-£400.  
 TEK 1240 Logic Analyser - £400.  
 TEK FG5010 Programmable Function Generator 20Mc/s - £600.  
 TEK2465A 350Mc/s Oscilloscope - £2.5k + probes - £150 each.  
 TEK CT-5 High Current Transformer Probe - £250.  
 TEK J16 Digital Photometer + J6523-2 Luminance Probe - £300.  
 TEK J16 Digital Photometer + J6503 Luminance Probe - £250.  
 ROTEK 320 Calibrator + 350 High Current Adaptor AC-DC - £500.  
 FLUKE 5102B AC-DC Calibrator - £4k.  
 FLUKE 1120A IEEE - 483 Translator - £250.  
 Tinsley Standard Cell Battery 5644B - £500.  
 Tinsley Transportable Voltage Reference - £500.  
 FLUKE Y5020 Current Shunt - £150.  
 HP745A+746A AC Calibrator - £600.  
 HP8080A MF + 8091A 1GHz Rate Generator + 8092A Delay Generator + Two 8093A 1GHz Amps + 15400A - £800.  
 HP54200A Digitizing Oscilloscope.  
 HP1729B Carrier Noise Test Set .01-18GHz - LEF - £2000.  
 HP3311A Function Generator - £300.  
 Marconi TF2008 - AM-FM signal generator - also sweeper - 10Kc/s - 510Mc/s - from £250 - tested to £400 as new with manual - probe kit in wooden carrying box.  
 HP Frequency comb generator type 8406 - £400.  
 HP Vector Voltmeter type 8405A - £400 new colour.  
 HP Sweep Oscillators type 8690 A & B + plug-ins from 10Mc/s to 18GHz also 18-40GHz. P.O.R..  
 HP Network Analyzer type 8407A + 8412A + 8501A - 100Kc/s - £500 - £1000.  
 HP Amplifier type 8447A - 1-400Mc/s £200 - HP8447A Dual - £300.  
 HP Frequency Counter type 5340A - 18GHz £1000 - rear output £800.  
 HP 8410 - A - B - C Network Analyzer 110Mc/s to 12GHz or 18GHz - plus most other units and displays used in this set-up - 8411a - 8412 - 8413 - 8414 - 8418 - 8740 - 8741 - 8742 - 8743 - 8746 - 8650. From £1000.  
 Rascal/Dana 9301A - 9302 RF Millivoltmeter - 1.5-2GHz - £250-£400.  
 Rascal/Dana Modulation Meter type 9009 - 8Mc/s - 1.5GHz - £250.  
 Marconi RCL Bridge type TF2700 - £150.  
 Marconi/Saunders Signal Sources type - 6058B - 6070A - 6055A - 6059A - 6057A - 6056 - £250-£350. 400Mc/s to 18GHz.  
 Marconi TF1245 Circuit Magnification meter + 1246 & 1247 Oscillators - £100-£300.  
 Marconi microwave 6600A sweep osc., mainframe with 6650 PI - 18-26.5GHz or 6651 PI - 26.5-40GHz - £1000 or PI only £600. MF only £250.  
 Marconi distortion meter type TF2331 - £150. TF2331A - £200.  
 Tektronix Plug-Ins 7A13 - 7A14 - 7A18 - 7A24 - 7A26 - 7A11 - 7M11 - 7D10 - 7S12 - 7S10 - S1 - S2 - S6 - S52 - PG506 - SC504 - SG502 - SG503 - SG504 - DC503 - DC508 - DD501 - WR501 - DM501A - FG501A - TG501 - PG502 - DC505A - FG504 - 7B80 + 85-7B92A  
 Gould J3B test oscillator + manual - £150.  
 Tektronix Mainframes - 7603 - 7623A - 7613 - 7704A - 7844 - 7904 - TM501 - TM503 - TM506 - 7904A - 7834 - 7623 - 7633.  
 Marconi 6155A Signal Source - 1 to 2GHz - LED readout - £400.  
 Barr & Stroud Variable filter EF3 0.1Hz - 100kc/s + high pass + low pass - £150.  
 Marconi TF2163S attenuator - 1GHz. £200.  
 Farnell power unit H60/50 - £400 tested. H60/25 - £250.  
 Rascal/Dana 9300 RMS voltmeter - £250.  
 HP 8750A storage normalizer - £400 with lead + S.A or N.A Interface.  
 Marconi TF2330 - or TF2330A wave analyser - £100-£150.  
 Tektronix - 7S14 - 7T11 - 7S11 - 7S12 - 7S1 - S1 - S2 - S39 - S47 - S51 - S52 - S53 - 7M11.  
 Marconi mod meters type TF2304 - £250.  
 HP 5065A rubidium vapour FX standard - £1.5k.  
 Systron Donner counter type 6054B - 20Mc/s - 24GHz - LED readout - £1k.  
 Rascal/Dana 9083 signal source - two tone - £250.  
 Systron Donner - signal generator 1702 - synthesized to 1GHz - AM/FM - £600.  
 Tektronix TM515 mainframe + TM5006 mainframe - £450 - £850.  
 Farnell electronic load type RB1030-35 - £350.  
 Rascal/Dana counters - 9904 - 9905 - 9906 - 9915 - 9916 - 9917 - 9921 - 50Mc/s - 3GHz - £100-£450 - all fitted with FX standards.  
 HP4815A RF vector impedance meter c/w probe - £500-£600.  
 Marconi TF2092 noise receiver. A, B or C plus filters - £100-£350.  
 Marconi TF2091 noise generator. A, B or C plus filters - £100-£350.  
 Marconi 2017 S/G 10KHz - 1024MHz.  
 HP180TR, HP182T mainframes £300-£500.  
 Philips panoramic receiver type PM7900 - 1 to 20GHz - £400.  
 Marconi 6700A sweep oscillator + 18GHz PI's available.  
 HP8505A network ANZ + 8503A S parameter test set + 8501A normalizer - £4k.  
 HP8505 network ANZ 8505 + 8501A + 8503A.  
 Rascal/Dana VLF frequency standard equipment. Tracer receiver type 900A + difference meter type 527E + rubidium grade type 9475 - £2750.  
 HP signal generators type 626 - 628 - frequency 10GHz - 21GHz.  
 HP 432A - 435A or B - 436A - power meters + powerheads - Mc/s - 40GHz - £200-£1000.  
 Bradley oscilloscope calibrator type 192 - £600.  
 HP8614A signal generator 800Mc/s - 2.4GHz, new colour £400.  
 HP8616A signal gen 1.8GHz - 4.5GHz, new colour £400.  
 HP 3325A syn function gen 20Mc/s - £1500.  
 HP 3336A or B syn level generator - £500-£600.  
 HP 3586B or C selective level meter - £750-£1000.  
 HP 3575A gain phase meter 1Hz - 1Mc/s - £400.  
 HP 8683D S/G microwave 2.3 - 13GHz - opt 001 - 003 - £4.5k.  
 HP 8660 A-B-C syn S/G. AM + FM + 10Kc/s to 110Mc/s PI - 1Mc/s to 1300Mc/s - 1Mc/s to 2600Mc/s - £500-£2000.  
 HP 8640B S/G AM-FM 512Mc/s or 1024Mc/s. Opt 001 or 002 or 003 - £800-£1250.  
 HP 8622BX Sweep PI - 01 - 2.4GHz + ATT - £1750.  
 HP 8629A Sweep PI - 2 - 18GHz - £1000.  
 HP 8629B Sweep PI - 2 - 18GHz - £1250.  
 HP 86 Series PI's in stock - splitband from 10Mc/s - 18.6GHz - £250-£1k.  
 HP 8620C Mainframe - £250. IEEE - £500.  
 HP 8615A Programmable signal source - 1MHz - 50Mc/s - opt 002 - £1k.  
 HP 8601A Sweep generator .1 - 110Mc/s - £300.  
 HP 3488A HP - IB switch control unit - £500 + control modules various - £175 each.  
 HP 8160A 50Mc/s programmable pulse generator - £1000.  
 HP 853A MF ANZ - £1.5k.  
 HP 8349A Microwave Amp 2 - 20GHz Solid state - £1500  
 HP 3585A Analyser 20Hz - 40Mc/s - £4k.  
 HP 8569B Analyser .01 - 22GHz - £5k.  
 HP 3580A Analyser 5Hz - 50kHz - £1k.  
 HP 1980B Oscilloscope measurement system - £600.  
 HP 3455A Digital voltmeter - £500.  
 HP 3437A System voltmeter - £300.  
 HP 3581C Selective voltmeter - £250.  
 HP 5370A Universal time interval counter - £450.  
 HP 5335A Universal counter - 200Mc/s - £500.  
 HP 5328A Universal counter - 500Mc/s - £250.  
 HP 634A System power supply - 0 - 60V - 0 - 10 amps - £500.  
 HP 5150A Thermal printer - £250.  
 HP 1645A Data error analyser - £150.  
 HP 4437A Attenuator - £150.  
 HP 3717A 70Mc/s modulator - £400.  
 HP 3710A - 3715A - 3716A - 3702B - 3703B - 3705A - 3711A - 3791B - 3712A - 3793B microwave link analyser - P.O.R.  
 HP 3730A + B RF down converter - P.O.R.  
 HP 3552A Transmission test set - £400.  
 HP 3763A Error detector - £500.  
 HP 3764A Digital transmission analyser - £600.  
 HP 3770A Amp delay distortion analyser - £400.  
 HP 3780A Pattern generator detector - £400.  
 HP 3781A Pattern generator - £400.  
 HP 3781B Pattern generator (bell) - £300.  
 HP 3782A Error detector - £400.  
 HP 3782B Error detector (bell) - £300.  
 HP 3785A Jitter generator + receiver - £750-£1k.  
 HP 8006A Word generator - £100-£150.  
 HP 8016A Word generator - £250.  
 HP 8170A Logic pattern generator - £500.  
 HP 59401A Bus system analyser - £350.  
 HP 59500A Multiprogrammer HP - IB - £300.  
 Philips PM5390 RF syn - 0.1 - 1GHz - AM + FM - £1000.  
 S.A. Spectral Dynamics SD345 spectroscope 111 - LF ANZ - £1500.  
 Tektronix R7912 transient waveform digitizer - programmable - £400.  
 Tektronix TR503 + TM503 tracking generator 0.1 - 1.8GHz - £1k - or TR502.  
 Tektronix 576 Curve tracer + adaptors - £900.  
 Tektronix 577 Curve tracer + adaptors - £900.  
 Tektronix 1502/1503 TDR cable test set - £1000.  
 Tektronix AM503 Current probe + TM501 m/frame - £1000.  
 Tektronix SC501 - SC502 - SC503 - SC504 oscilloscopes - £75-£350.  
 Tektronix 465 - 465B - 475 - 2213A - 2215 - 2225 - 2235 - 2245 - 2246 - £250-£1000.  
 Kikusui 100Mc/s Oscilloscope COS6100M - £350.  
 Nicolet 3091 LF oscilloscope - £400.  
 Rascal 1991 - 1992 - 1988 - 1300Mc/s counters - £500-£900.  
 Fluke 80K-40 High voltage probe in case - BN - £100.  
 Rascal Recorders - Store 4 - 4D - 7 - 14 channels in stock - £250 - £500.  
 Rascal Store Horse Recorder & control - £400-£750 Tested.  
 EIP 545 microwave 18GHz counter - £1200.  
 Fluke 510A AC ref standard - 400Hz - £200.  
 Fluke 355A DC voltage standard - £300.  
 Wiltron 610D Sweep Generator + 6124C PI - 4 - 8GHz - £400.  
 Wiltron 610D Sweep Generator + 61084D PI - 1Mc/s - 1500Mc/s - £500.  
 Time Electronics 9814 Voltage calibrator - £750.  
 Time Electronics 9811 Programmable resistance - £600.  
 Time Electronics 2004 D.C. voltage standard - £1000.  
 HP 8699B Sweep PI YIG oscillator .01 - 4GHz - £300. 8699B MF - £250. Both £500.  
 Schlumberger 1250 Frequency response ANZ - £1500.  
 Dummy Loads & power at up to 2.5 kilowatts FX up to 18GHz - microwave parts new and ex equip - relays - attenuators - switches - waveguides - Yigs - SMA - APC7 plugs - adaptors.  
 B&K Items in stock - ask for list.  
 W&G Items in stock - ask for list.  
 Power Supplies Heavy duty + bench in stock - Farnell - HP - Weir - Thurlby - Rascal etc. Ask for list.

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. SAE FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS. AVAILABILITY OR PRICE CHANGE. VAT AND CARRIAGE EXTRA  
 ITEMS MARKED TESTED HAVE 30 DAY WARRANTY. WANTED: TEST EQUIPMENT-VALVES-PLUGS AND SOCKETS-SYNCS-TRANSMITTING AND RECEIVING EQUIPMENT ETC.

**Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. No: (01274) 684007. Fax: 651160**

CIRCLE NO. 110 ON REPLY CARD

Jonathan Campbell

## Signalling a rethink of array receiver design

Innovative signal processing techniques developed by researchers at the University of Southern California are set to turbo-charge the performance of conventional array signal-receivers. The work carried out by Jerry Mendel and former USC doctoral student Mithat Dogan could well affect everything from how the military locates far-away submarines, to how we track objects in space, to how we design more efficient home antennas receiving signals from direct satellite broadcasts.

The invention works by combining 'higher-order statistics' with correlations of readings from adjacent detectors in an array. By returning to the fundamentals of physics and signal processing, the researchers have shown that, using the known geometry of an actual array, it is possible to compute correlations not only between pairs of physically present detectors, but also between a physically present detector and a non-existent, virtual detector. Or even between pairs of virtual detectors. This gives a small array of detectors a much larger scope.

Arrays are an attractive alternative to large dishes for picking up very faint signals. The method is to use a multitude of detectors, each one served by a much smaller radiation collector, and spread these detectors out in an array, either in a line, or in two or three dimensions.

Arrays can cover an area or volume far larger than any possible dish, and though the signal picked up by each detector is faint, engineers can construct the network so that the faint traces received by each individual site reinforce one another, creating an instrument that can perform like a single massive dish.

Mendel and Dogan's software, called a virtual cross-correlation computer, works only if the distance to the signal-producing target is large in relation to the size of the array of detectors. The detectors in the array must be tuned to a relatively narrow bandwidth too – listening to only a

limited range of sound pitches, light colours or radio frequencies.

Finally, the signal being received must be of a specific kind – namely, non-Gaussian. The Mendel-Dogan invention functions to suppress Gaussian signals and preserve non-Gaussian ones.

If these three conditions are met – and they frequently are in real-world sonar, radar and other array detectors – major improvements in performance are possible, according to Mendel. More targets can be located than before, closely spaced targets can be resolved, and interfering noise can be suppressed.

As well as improving the performance of existing array detectors, the virtual cross-correlation computer concept can be used to design new, more efficient antenna arrays. For example, a 20-by-20 planar array, which would normally require 400 elements, can be implemented with a 10-by-10 array using only 100 elements.

"But the technique also has an aesthetic appeal," says Mendel. "It uses the hidden, internal structure of a signal that is unknown, to, in effect, decode itself. It uses the characteristics of the array used to



Better reception from distant sources looks possible with the new approach to array design.



Jerry Mendel at USC has analysed exactly how a receiver array works.

detect this signal to bootstrap the array's efficiency. Even if it ultimately proves to have no uses at all, I find the technique highly satisfying to contemplate."

## Making photons interact is first step to quantum computer

Physicists at Caltech, Pasadena, have taken a step closer to quantum computing with testing of an optical gate whose output depends on the polarisation state of two photon inputs.

Photons normally do not interact. But the team led by professor of physics H Jeff Kimble at Caltech, has found that they can be made to strongly influence each other when brought together with an atom inside an optical cavity.

To be useful in computing, any legitimate logic gate must display an essential feature called conditional dynamics, where the output must

depend upon both inputs. In an optical quantum logic gate, the output state of each photon must depend on the input state of both photons.

Kimble's group has showed strong conditional dynamics for an atom in an optical cavity formed by two highly reflective mirrors, one of which allows partial transmission of light. The scientists sent pairs of photons through the cavity, and investigated the states of the photons when they re-emerged, showing that the output state of each photon depended on the polarisation of both input photons. *Cont'd over...*

In effect, the cavity functioned as a rudimentary logic gate at the single photon level. Changing the photons' polarisation is analogous to flipping the bits in conventional computers.

This is the first demonstration of

conditional dynamics at the single-quantum level, and while many complex problems remain to be solved before even primitive networks of quantum logic gates could be built, the result is being seen as a significant first step in

quantum computing. Even if it doesn't lead to a practical route to quantum computing, the researchers say optical quantum logic gate will definitely have a role in specialised applications in optical communication.

## Not a remote possibility

How we laugh as we remember those days when we used to have to pull ourselves up from our chairs and drag the 3m or across the room to press the channel changer on the tv with a finger. Now we just reach for the remote control and... hang on, I know it's here somewhere.

Unfortunately, as increasing numbers of household devices and even light switches become remote controllable, keeping track of them all is becoming more and more difficult. Universal remote controllers are a great idea – if you have small fingers and a photographic memory for densely packed keyboards. But a researcher in the Department of Electronic Engineering, The Chinese

University of Hong Kong, has proposed a solution that could be easy to implement and simple to use.

In the system proposed by C S Choy, a temporary link is established between the remote control and the target appliance. So any further key presses are only recognised by that one device.

Typically, audio-visual system offer many functions sometimes calling for tens of keys on a remote control. Choy proposes dividing these into types, according to the nature of control, such as on/off, +/- volume, and numeric.

The resulting smart universal remote control could use an optimum number of programmable keys to

keep its bulk and complexity down. Through a learning process, each key could send out different commands according to the appliance being controlled.

So far Choy has built a remote controller, based on a Motorola 68701 with 2K eeprom, 192 bytes built in ram and three i/o ports, which he has used to control light switches.

But the concept could form the basis for a universal controller that is much simpler than anything currently around.

*C S Choy is in the Department of Electronic Engineering, The Chinese University of Hong Kong, Hong Kong.*

## Soft touch brings robot breakthrough

Much work has gone into designing robot grippers that are sensitive to force so that, for example, the robot can pick up an egg and hold it firmly without breaking it. Now two US researchers have found an answer that was easily to hand all the time – robot fingertips.

The fingertips are actually an electrorheological fluid of particles of polymers suspended in a dielectric fluid. In

the presence of a strong electric field, their behaviour changes from that of a viscous, approximately Newtonian fluid to that of a plastic, with a finite shear strength as well as a viscous coefficient.


Prasad Akella and Mark Cutkosky had observed that the ability of human hands to make contact smoothly is partly due to fingertips that deform and dissipate energy. Taking this as their starting point, the two

workers have now produced their latest prototype fingertip that seems to reproduce that effect in a robot ('Contact transition control with semiactive soft fingertips', *IEEE Transactions on Robotics and Automation*, Vol 11, No 6, pp. 859-867).

The soft fingertip consists of a non-conducting rubber skin containing the fluid, with the electric potential applied across a series of plates oriented perpendicular to the skin surface. As the skin is pressed, the fluid is forced to flow between the plates with a resistance that varies with the applied voltage. A second membrane at the back side of the plates provides a restoring force that returns the system to a standard equilibrium configuration when unloaded.

Building a fingertip whose stiffness and damping properties can be directionally controlled still remains a challenge. Even so, the researchers report that the current generation of fingertips can provide compliance and damping that are very similar to human fingertips.

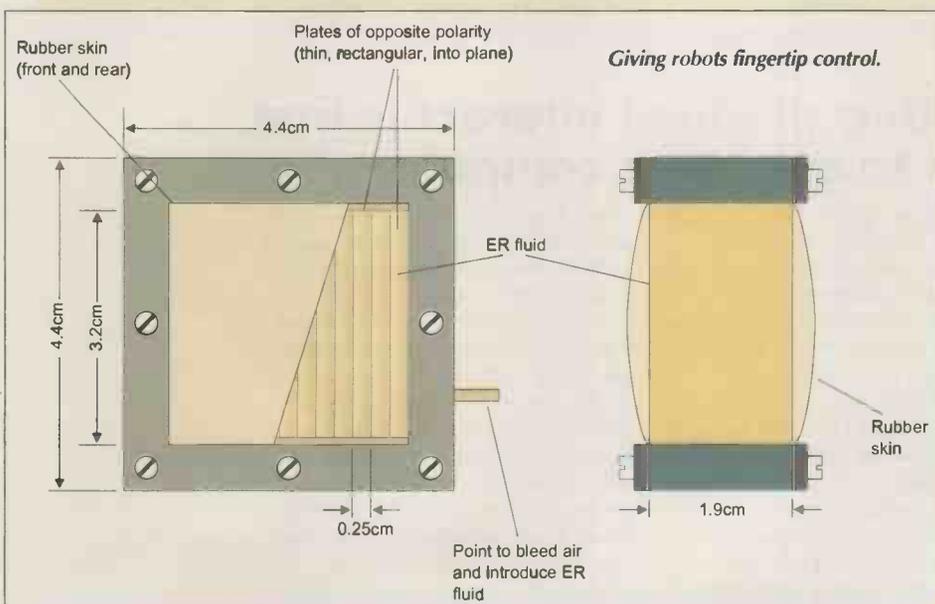*More information from P N Akella who is now at the Manufacturing Center, General Motors Corporation, 30300 Mound Road, Warren MI 48090, USA or email at akella@gmr.com. The research was carried out in the Department of Mechanical Engineering and the Center for Design Research, Stamford University, Stamford CA 94305, USA.*



## Magnetism motivates microactuator research

Researchers into microelectro-mechanical systems (Mems) at the Berkeley Sensor & Actuator Center (Bsac) have developed a powerful microactuator that uses magnetism as the actuating force and can be batch-manufactured in relatively simple processes.

Mems specialists Jack Judy, Richard Muller and Hans Zappe at Bsac report that their microactuator has so far demonstrated forces and displacements far larger than those generated by most electrostatic microactuators. In addition the microactuator can be fabricated using conventional electroplating, lithography, materials and equipment.

Novel features of the technology are that actuation can be controlled by a remote magnet – a hand-held permanent magnet was used in some of the experiments – and that structures can be actuated in three dimensions: ie movement is not restricted to the plane of the wafer.

The microactuator itself is essentially a polysilicon cantilever beam, or flexure, onto which a magnet is formed at the free end. That magnet interacts with an external magnetic field, bending the flexure.

Fabrication is straight-forward in that the magnetic layer of NiFe layer is simply electroplated onto the silicon at the end of a process which is

already in use to produce chips of polysilicon resonant structures.


Using an external magnet to provide the actuating force means surface-to-surface interactions such as those found in linear and rotary variable-capacitance, and variable reluctance structures, are not required – so fabrication is easier.

The external magnet can also be used to activate many devices simultaneously – though that also means that control of independent microactuators will require miniaturised sources of magnetic fields, perhaps even on-chip sources.


So far the tip of an 800µm-long cantilever has been deflected over a distance of 1.2mm and rotated through an angle greater than 180° under an imposed torque of 0.185nNm ('Magnetic microactuation of polysilicon structures', *Journal of Microelectromechanical Systems*, Vol 4, No 4, pp. 162-169)

The team is hopeful that similarly fabricated magnetically-actuated microstructures might be applied to micromanipulators, microgrippers, magnetometers or microphotonic systems.

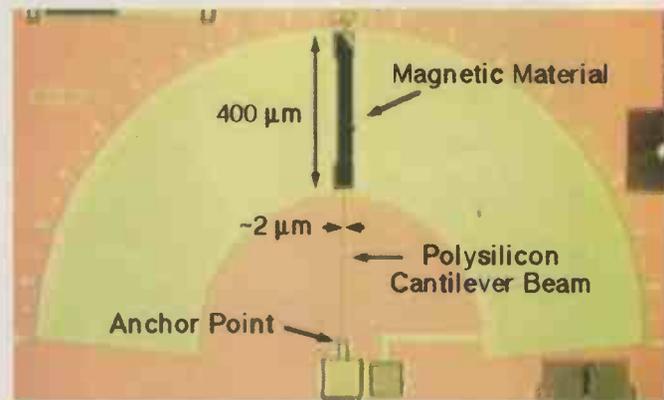Jack W. Judy can be contacted at 497 Cory Hall 2041 Francisco, Apt. #5 Berkeley, CA 94720-1770, USA or [j.judy@ieee.org](mailto:j.judy@ieee.org)



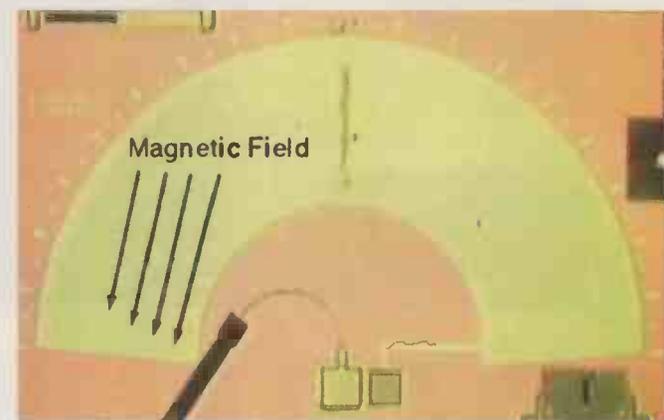Before application of the external magnetic field...



...while after the external magnet is applied the beam is deflected. Deflection is not restricted to the plane of the wafer.

## Planners get ready for road rage

Road rage seems to be the most extreme example of an ever-increasing aggression on the highways. So how are road planners reconciling their computer models of happy 'model' drivers giving way at junctions with a cheery wave, to the reality of the bumper to bumper stand-offs which increasingly are the norm.


At MIT in the US, they might have an answer. Because MIT engineers have developed a state-of-the-art traffic simulator that actually mimics the behaviour different drivers, aggressive, careless, timid or fast-and how they affect traffic flow.

The traffic simulator, which runs on a workstation, is called Mitsim for short (microscopic traffic simulator) and treats traffic as a set of individual vehicles, or particles, allowing each vehicle to move according to its own characteristics. The more common macroscopic simulator treats traffic like a fluid, assigning one set of characteristics to the entire stream of cars. Mitsim is more lifelike because it allows for differences in vehicles' movements as dictated by drivers' personalities.



As each vehicle enters the simulated road system, it grabs a packet of vehicle characteristics that determines how it will act in certain circumstances. Not only does each vehicle have a size, type, occupancy level and destination, it also has driver

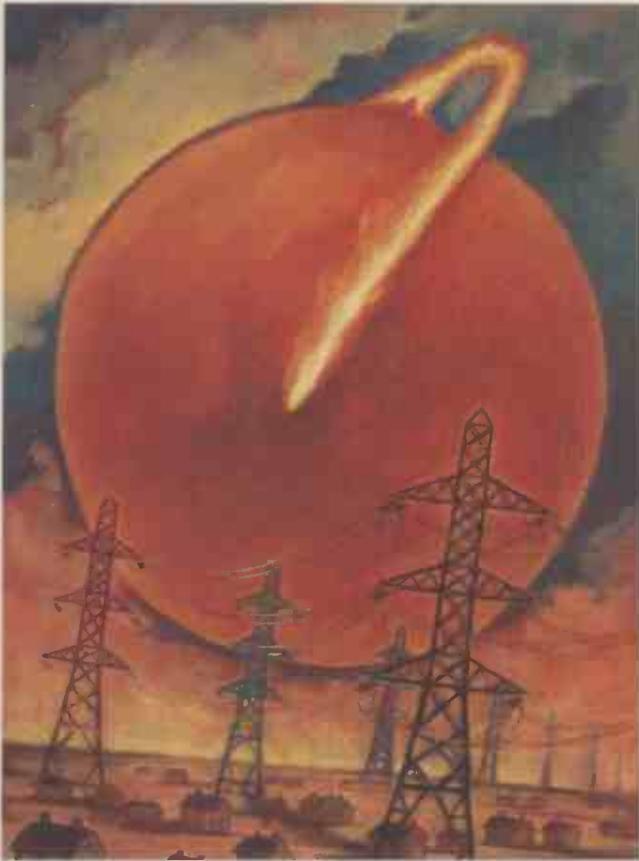characteristics. These include desired speed, propensity to yield to other vehicles, lane-changing behaviour and route decisions. There's even a driver impatience factor that makes each driver's choices more realistic. ■



Professor Denis Henshaw recently proposed that radon gas could be concentrated by high electromagnetic fields from overhead electricity supply lines. Radon causes lung cancer by ingestion of short-range alpha particles, whereas the cancer usually linked to pylons is leukemia, implying particles penetrating much deeper into the body. And if radon is highly significant, shouldn't there be a higher incidence of Leukemia in the West Country, where radon is more prevalent? There isn't. To test for radon, Prof. Henshaw tracked alpha particles. But could other factors have affected his results? **Anthony Hopwood** presents his case.

# POWER LINES

## particles and

# CANCER

**"The first suggestion that power lines might cause disease was made in 1976..."**

In my original feature in the November 1992 issue of *Electronics World*, I proposed that the electric and magnetic fields around power lines intensified natural background radiation in their vicinity.

My observations were based on many hours of measurement of the background ionising radiation close to overhead power lines over the period 1990-91 which happened to be close to the peak of solar cycle 22 sunspot maximum.

This was serendipitous because the effect is most marked at solar maximum, and the rather crude portable Geiger counter I used would not have detected any effect as the sun went off the boil in its approach to the present minimum of its 11 year cycle.

Figure 1 shows the large change in solar activity expressed by the number of sunspots. This can also be measured as the solar flux at 10.7cm wavelength. At maximum, the solar flux approaches 300, whereas it is now around 70 – a change of over 400%.

The first suggestion that power line routing might cause disease in populations close by was made in 1976 from studies in the Denver area – which happens to be a mile above sea level and therefore has less protection from the atmospheric layer. Since then, the debate has continued, but the necessary scientific proof of a credible disease mechanism has been absent.

There have been numerous theories to explain the increasing epidemiological evidence. Most have concentrated on internal cel-

lular effects observed in the presence of alternating magnetic fields, and have involved free radicals, melatonin or chemical changes in the living cell. Other theories have suggested that the electrodynamic fields have damaged cell function by precipitating pollutants from the atmosphere. Some have suggested that electric and magnetic fields per se are damaging, and that a new disease mechanism is implicated.

There is no argument that electric power lines and distribution systems create strong electromagnetic and electrostatic fields in their vicinity. Overhead power lines are a highly visible source of this radiated energy. Some 'supergrid' lines carry up to 800A per phase at 440kV and spread an electrodynamic footprint over 100 meters either side of the centre line.

There is also no argument that charged secondary atomic particles are influenced by ambient electric and magnetic fields. It was the alteration in the numbers of charged particles detected on my continuous cosmic ray monitor by the passage of electrically charged clouds that first gave me the idea of investigating whether the more intense electrodynamic fields round overhead power lines affected natural background radiation nearby.

## "Why had no one noticed this (power line) effect before?"

The results were surprising. In simple terms, a horizontal geiger tube with an L/D ratio of about 13 and a low energy cut off at about 60keV showed a background rate increase of up to three times either side of the line, compared with the rate outside the electrodynamic footprint.

Why had no-one noticed this effect before? There are two main reasons.

Firstly, only a third of the charged particle flux detected by the tube came from the sun, whose high energy particles were fissioned by collision with the atmosphere to give the 'cosmic drizzle' of lower energy charged particles reaching the ground. These low energy but still biologically damaging particles have been ignored by cosmic ray physicists because they were only interested in ultra high energy particles which could not be replicated easily on earth.

Secondly, environmental researchers were only concerned with picking up radioactive particles from pollution sources like Chernobyl, and deliberately set their Geiger tubes vertically upwards to minimise the nat-

ural background rate variation due to the sun, ground and changes in atmospheric pressure.

The key to my observations was to use a long thin Geiger tube aligned to the geomagnetic field as a coincidence detector to improve the detection statistics for down-coming solar particles against the background radiation from the ground.

## "For the first time, I could see the rate change as the sun rose..."

Textbooks suggest that typical rate variation in the UK due to solar emanations is about 3 per cent – a figure confirmed when I first set up the Geiger tube on a 7 metre pole with an east-west axis in June 1989. By October 1989, the rate variation stayed maddeningly around 3 per cent while the sun fulminated at solar maximum.

Turning the tube to a geomagnetic NS axis made a magical difference. For the first time I could see the rate change as the sun rose, and track active areas across the solar disc by the 14 day rate change they produced.

Interaction between charged particles and the geomagnetic field was also apparent during magnetic storms. During the great auroral display of 8/9 November 1991, an individual auroral ray from the geomagnetic zenith passed over my detector and increased the count by about 20 per cent for the few minutes it was focussed on my sensor.

This may have been the first time that an auroral beam of particles has been detected on the ground.

All this – plus the continuous recording of atmospheric electric field alongside particle rate – led me to try and find whether power lines could alter the solar particle rate in their vicinity.

After publication of my results and conclusions in *EW+WW*, a debate started. The Swedish Radiation Protection Institute went out into the Scandinavian winter and found there was a background radiation anomaly near power lines.

Nearer home, the NRPB was more sceptical. It did carry out joint field tests with me with inconclusive results. Some of the tests were flawed because they did not include anticoincidence counting on the multiple tube arrays. The real problem was that between my field work in 1990-91 and their tests in 1993, the solar flux had dropped by 70 percent so the effect was difficult to detect with relatively

unsophisticated sensors.

Since then, I have been working to improve my detector, as have the Swedes. Although it is early days, we now have two different types of sensor to plot any radiation anomalies near power lines.

My own instrument uses two closely matched independent Geiger tubes driving separate counters, as well as a coincident pulse monitor. Earlier work had suggested that the change in particle rate near a power line was most marked at the low energy end of the spectrum – below 100keV.

At sunspot minimum, the mix of particles entering the atmosphere still varies with solar activity. The most sensitive ground level indicator of solar particle flux is the geomagnetic field. This is easily measured. Conditions are logged from 'quiet' to 'storm' on a K index published monthly for every three-hour period. Another index of incoming solar plasma is the ionosphere. Its condition can be monitored by recording changes in high-frequency radio propagation from day to day. These two indices, plus the rates from fixed particle counters produce a clear signal when extra particles are entering the atmosphere to suggest when field measurements are best made.

The twin Geiger tube detector now used has two matched tubes with an L/D ratio of about 12:1. One tube has a plastic protective case, and the other has one of copper to give a differential screening effect of about 4:1 at the low energy end of the spectrum.

Under 'quiet' conditions, the two tubes count within 2 per cent over several hours away from a power line. The rate variation between tubes stays within 5 per cent close to the 11kV line crossing my garden under geomagnetically quiet conditions. When there is a geomagnetic disturbance, the balance changes, with a differential rate of at least 10 per cent in favour of the lightly screened tube.

The instrument has only been under test since the beginning of January, and with a quiet sun, there have been no major magnetic storms so the 10 per cent count differential is

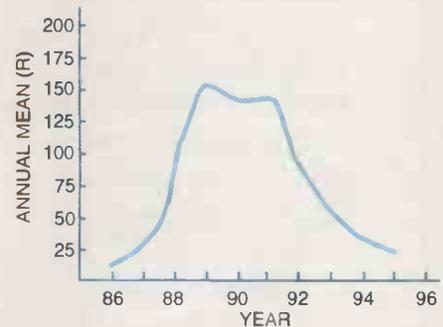


Fig. 1. Large changes in solar activity over an eleven year cycle have been linked to a delayed eleven year cycle for breast cancer.

a reasonable result which can only improve as the new solar cycle gets into gear.

I mentioned earlier some of the other research in this field. Recently a paper was published by Professor Denis Henshaw suggesting that domestic wiring was able to concentrate alpha particle emitters like radon gas in its vicinity. The particles were detected using a sensitised plastic which is pitted by alpha particles, the standard method for detecting radon emanations.

**"...it is likely that they did not all come from radon"**

Prof Henshaw proposed that the source of his particles was radon gas, which is certainly present in most homes. Given that the tracks were etched by alpha particles close to electric leads, it is equally possible that they did not come exclusively from radon. I suspect that his observations complete the penetrating particle fission chain which starts in the upper atmosphere and which I measured outdoors above 50keV – the low energy cut off for my

**"Concorde... routinely reduces height if a solar flare occurs..."**

Geiger tube charged particle detectors.

If this proves to be the case, there is a complete chain of potential ionising radiation cell damage from the sun to the wall socket.

So what other evidence is there that the sun can produce sufficient radiation to harm susceptible individuals? The atmosphere is a very effective screen which protects life on earth from the damaging emissions of the sun.

Solar background radiation exposure is already monitored for airline crews. Concorde, which flies higher than other commercial jets, has a solar particle monitor onboard and routinely reduces height if a solar flare occurs or particle rates exceed set limits.

I mentioned that charged solar particles are concentrated at high geomagnetic latitudes, and can be seen as aurorae when the magnetosphere intercepts solar plasma ejected during flares and coronal mass ejections. The geomagnetic intensification effect implies that so-

called radiation cancers should be more common in industrial nations at high geomagnetic latitudes.

Cancer statistics from the IARC seem to confirm this, Fig 2.

Further evidence implicating the sun comes from a Russian paper by T.P. Ryabyh and N.B. Bodrova in 1993 outlining a delayed solar cycle for breast cancer in women. Much earlier was the first paper linking power lines and cancer published in Denver USA in 1976. Its significance is that the 'Mile High City' is between 5-6000 feet, where solar background radiation is at least four times that at sea level.

**"What is needed now is properly funded research..."**

I am also sure it is no accident that the best statistics to date for a link between power lines and cancer come from Scandinavia which is highly electrified and at a high geomagnetic latitude.

What is now needed is properly funded research into the symbiotic reaction between electric power and background radiation using the best radiation metrology. In my opinion, the intensification of natural background radiation by the electric and magnetic fields associated with electrical installations provides the missing link between human cell damage and eventual disease in some people living and working under the aegis of the pylon.

The evidence is mounting, and won't go away. ■


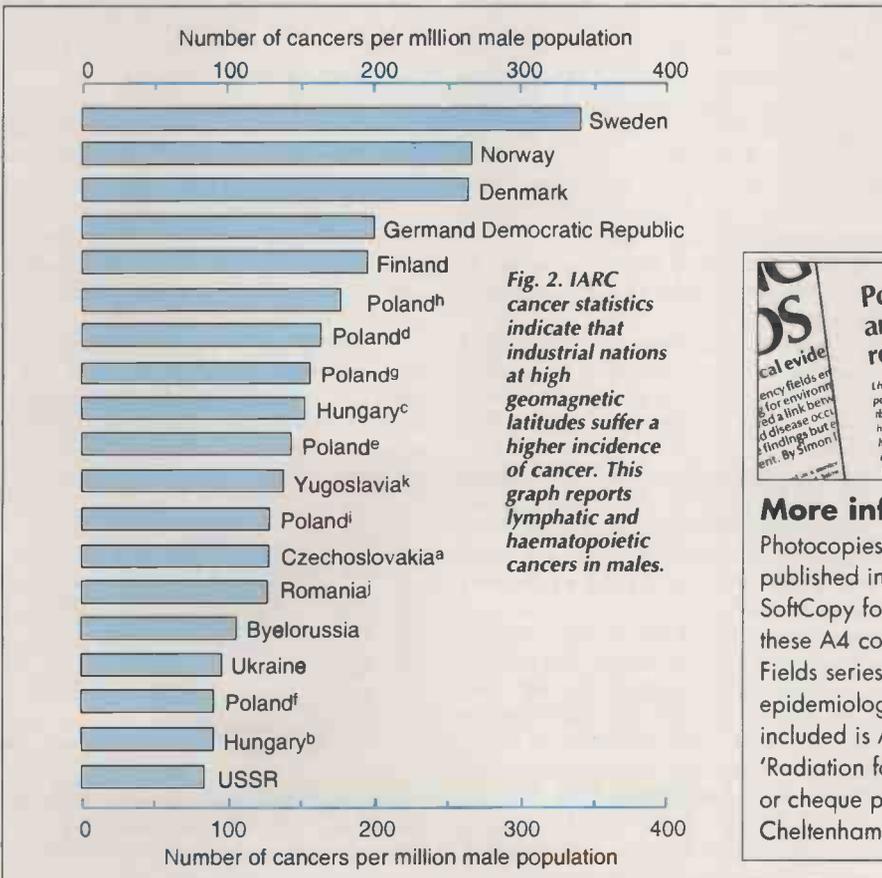


Fig. 2. IARC cancer statistics indicate that industrial nations at high geomagnetic latitudes suffer a higher incidence of cancer. This graph reports lymphatic and haematopoietic cancers in males.

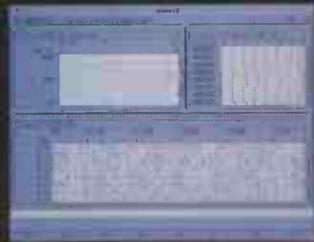

**More information**


Photocopies of earlier articles on non-ionising radiation published in *Electronics World* are available from SoftCopy for £7.50 fully inclusive. Totalling 25 pages, these A4 copies comprise five articles from the Killing Fields series covering: introduction, biophysics, epidemiology, microwaves, politics and causes. Also included is Anthony Hopwood's 1992 article – 'Radiation focused by power lines'. Send postal order or cheque payable to SoftCopy to 1 Vineries Close, Cheltenham, Gloucester GL53 0NU.



GRAPHIC DISPLAYS



SOURCE LEVEL DEBUGGER

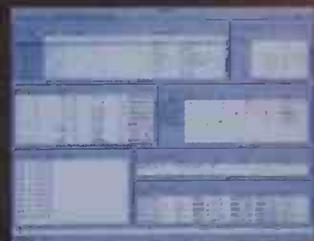

MULTI-TASKING DEBUGGER



## WHY TRACE 32 IS SIMPLY THE BEST IN-CIRCUIT EMULATOR AVAILABLE

- **Wider 8/16/32 micro-processor support** than any other in-circuit emulator
- **Integrated high level language debugger supports** most 3rd party compilers for C, C++, ADA, MODULA2, PASCAL and Assembly languages
- **High speed link to PCs or Workstations** via Ethernet LAN or fibre optic interface giving **effective code transfer rates of up to 400kbyte/sec**
- **Multitasking debugger support** for PSOS, OSE, VRTX32, OS/9 also user configurable for special kernels
- **'Free 3 year warranty'** no hidden charges'

- **A complete windowed interface development system:** in-circuit emulator, 200MHz timing analyser, pattern generator, comms analyser, port analyser, stimuli generator
- **BDM and ROM monitor debuggers** available using the same interface
- **Up to 4 MFrame real-time trace buffer;** unlimited hardware breakpoints; up to 16MB dual ported emulation memory; full real time performance analysis and statistical functions with code coverage feature.
- **On-line - 1,000 page fully integrated manual.**

### PROCESSORS SUPPORTED

68000 / 1 / 8 / 10  
 68302 / 306 / 307  
 68330...336  
 68340, 68349, 68360  
 68020 / 030  
 68040 / 060  
 Power PC  
 68HC16  
 68HC11-A...P  
 80186-EA...EC, XL  
 V20, V30, V40, V50, V53  
 80386 / 486SX / DX / EX / CX  
 80196...  
 8051...  
 H8 / 500, 300, 300H  
 90C100...301  
 80C166 / 165 / 167 / GOLD  
 Z80, Z180...  
 NS32000  
 MELPS 7700      And many more...



IN CIRCUIT EMULATOR SOLUTIONS FOR ANY BUDGET

## THE TRACE 32 — 100 YEARS IN THE MAKING — NO COMPROMISES

At Noral we are experienced at providing the right emulation solution and the Trace 32 from Lauterbach is the best there is; the result of over 100 man years development with its 4M Frame program trace, host system and network support, single intuitive user interface and upgrade flexibility — it's the ultimate solution.

If your requirements don't push the envelope to the limit however, we

can help too, with a complete range of solutions to suit any budget — we really are the emulator specialists.

Call now on 01254 682092 for a microprocessor development solution that's cost effective, upgradable, offers the widest coverage and the best technical support.



Please send me details on:  
 Trace 32 in-circuit emulation systems   
 Noral's complete range of emulator systems

Name \_\_\_\_\_

Position \_\_\_\_\_

Company \_\_\_\_\_

Tel \_\_\_\_\_



The Emulator Specialists

### NORAL MICROLOGICS LIMITED

Logic House, Gate Street, Blackburn, BB1 3AQ  
 Tel:01254 682092 Fax:01254 680847 BBS:01254 679412

CIRCLE NO. 111 ON REPLY CARD

# 22bit analogue-in for PCs

**Simon Bateson and Andrew Woodward** run through the design stages needed for achieving very high resolution analogue-to-digital conversion via a PC's LPT port – and at a relatively low cost.

A large number of analogue-to-digital converter designs have been published in electronics journals, either as free-standing units or incorporated into other test and measurement equipment. These have mostly been of 8-bit resolution, based on devices such as the ZN425, which can achieve sampling rates suitable for audio.

For even moderate measurement quality, 12-bit converters are needed, such as the AD1674 which can achieve 10µs conversion at around £35. Higher resolution and higher speeds are generally very expensive; the 'audio optimised' 16 and 18bit converters have good linearity but less good dc characteristics.

Manufacturers provide cards to fit inside pcs for analogue input and output, but it is very difficult, hence expensive, to obtain optimal performance in the electrically noisy environment of a computer.

There are many applications where high resolution is required but speed is uncritical. Here, the 'voltmeter' a-to-d converters are appropriate and ICs like the 7106 and 7135 have provided excellent performance for many years.

Recently, the development of low speed, high resolution converters has moved forward and some devices offer extremely high sensitivity, resolution and self-calibration facilities. Analog Devices' AD7710AN is a sigma-delta analogue to digital converter with an on-chip programmable gain amplifier. Given a suitable environment, this device can achieve 22bit resolution – the equivalent of 0.25ppm.

In addition, the 7710 can provide total rejection of superimposed periodic interference and better than 16 bit non-linearity at over 15 samples per second. This sampling rate is ade-

quate for many process and experimental uses, making the converter relevant for mechanical, thermal and chemical sensors, panel meter applications and research.

## Noise rejection

It is well known that integrating converters such as the voltage-to-frequency, delta-sigma and dual-slope types have the ability to reject periodic noise. They do this because the output is proportional to the average, integrated, input voltage over the measurement period.


If the measurement period is a multiple of the local supply waveform period, the converter rejects this frequency and its harmonics. For this reason, the dual-slope integrating converters used in ordinary digital panel meters all run at a similar speed, giving about three readings per second and rejecting both 50Hz and 60Hz interference.

The clock frequency must be an exact multiple of the line frequency or cancellation will be incomplete and errors will appear as before. A point that is often overlooked in the implementation of integrating converters is that they rely *totally* on the short-term stability of the clock oscillator.

Crystal and LC oscillators fulfil all practical requirements, but c-mos inverter and other RC oscillators must be carefully designed for low short-term drift and phase noise.

Noise pickup in the form of 50/60Hz interference is very common in high-impedance sensors. Among these are ion-selective electrodes, clinical electrodes and piezo transducers as well as in low-level industrial sensors such as strain gauges and katharometers.

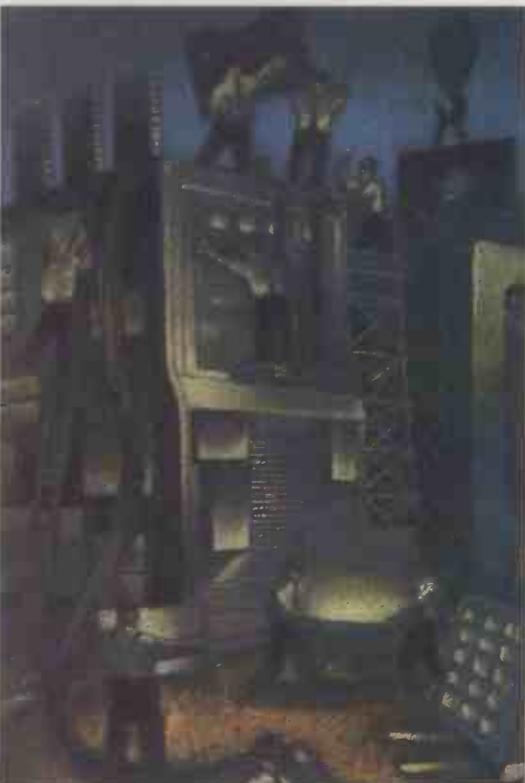
Noise is induced capacitively in high-impedance transducers and magnetically in low impedance circuits. Applying comput-



Resolutions of the a-to-d converter versus sampling rates, at gains of 1-4.

Rate (Hz)	Resolution (bits)
10	21.5
25	20
50	19.5
100	18.5
250	15.5
500	13
1000	11

PC PORT

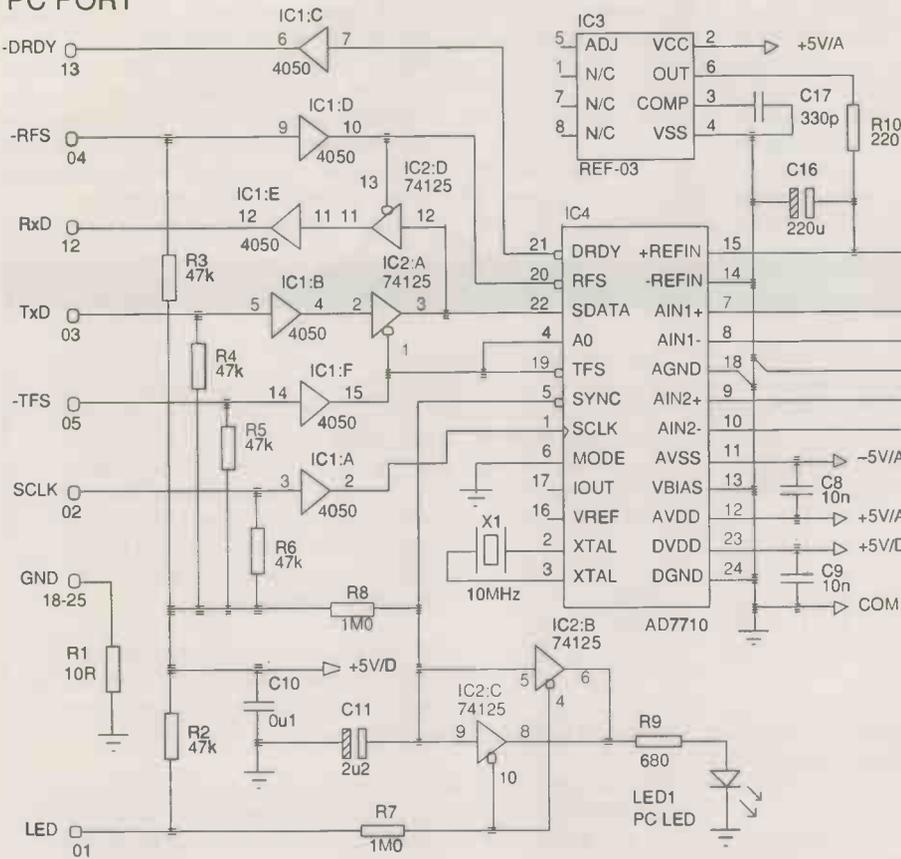

ANALOGUE PORT

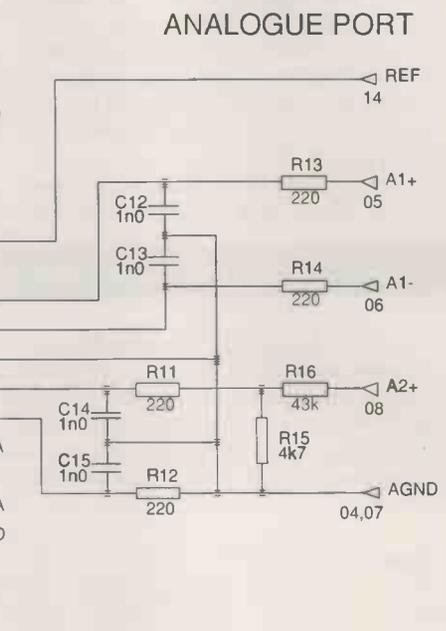


Fig. 1. Hardware-wise, the 22 bit analogue to digital converter circuit looks quite simple. The real trick to obtaining 22bit accuracy is in the layout and component choice.

erised data-collection systems in industrial plant or laboratory environment implies the interconnection of numerous mains-powered devices. Errors in input layout and grounding procedures can cause further problems and the resulting earth loop interference can be difficult to eliminate.

The successive approximation converter – the most common type found in pc cards – is not inherently differential or able to reject cyclic noise. Although pickup can be reduced by standard techniques such as balanced transmission and filtering, once the signal contains cyclic noise, the only really effective converter is one with inherent ac rejection.

This article details the design of a practical implementation of the 7710 converter which connects conveniently to a standard Centronic printer port. The necessary control software for a pc is also detailed. For readers interested in constructing the unit, pcbs are available, as is a fully featured Windows controller detailed below.

Measurement principles

This design, Fig. 1, uses an external REF-03 reference for the maximum stability and minimal noise. The converter is a 'sigma-delta' or '1-bit' converter. It comprises a differential amplifier, an integrator and a comparator, Fig. 2.

The system is a negative-feedback loop which tries to keep the net integrator charge at zero. It does this by balancing charge injected by the input voltage with charge removed by alternately applied positive and negative reference voltages.

When the analogue input voltage is zero, the only charge source is via the switched reference voltages. Assuming ideal components, the resulting duty cycle of the modulator will be 50%. Changes in input voltage cause linearly proportional variations in duty cycle. In the AD7710AN, an on-chip digital filter derives a rolling average of the modulator duty cycle.

An on-chip microcontroller allows software control of sampling frequency. The more clock periods available for the filter to calculate an average from, the closer to the true input the result will be. Consequently the converter gives its lowest noise and best resolution at low conversion speeds.

It is important to realise that, due to this averaging effect, a sudden change in input will not be reflected in an instantaneous output

change. At a sampling speed of 12 readings per second, the effective bandwidth is about 3Hz. However, the inherent noise of normal signal sources means that faster measurements would be meaningless at the voltage levels measurable with this converter – the individual readings would differ significantly due to noise and would need averaging anyway.

An additional facility of the converter is a programmable gain amplifier, pga, providing seven software programmable gains from 1 to 128. It is not really an amplifier, but uses multi-sampling to achieve the same effect. Consequently it is extremely accurate.

Converter resolution and noise

Resolution of the converter is calculated by finding the standard deviation of a number of readings. For signals with a mean value of

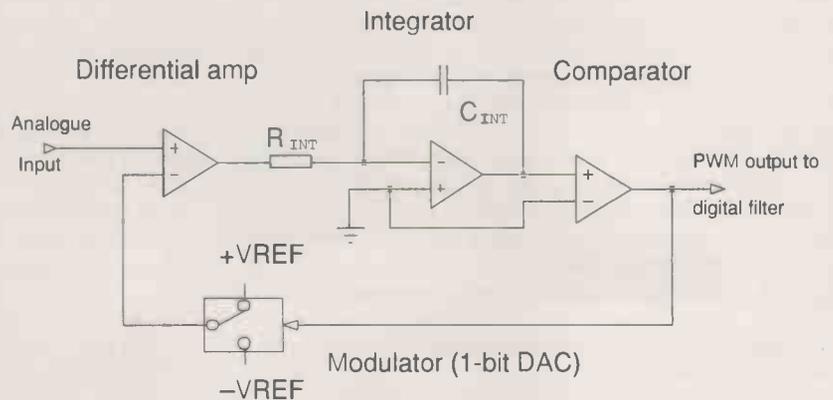


Fig. 2. Sigma-delta a-to-d converter principles. Theoretically, the '1bit' output can produce any desired resolution.

zero this value equals the rms 'noise' amplitude. The available dynamic range is then defined as the ratio of full scale deflection to rms noise. This was found in the production prototype to be around 132dB or 22 bits at a unity gain, worsening to 105dB or about 17.5 bits at a gain of 128.

A converter capable of a practical resolution of around 22 bits must be built up with con-

siderable attention to sources of digitally induced noise. At a pga gain of 128 and with a typical reference voltage of 2.5V, one bit corresponds to just over 2nV and it is possible to reliably measure to 0.2µV without external pre-amplification.

Circuit-board layout – in particular the power supply earthing sequence – is critical, which is why the pcb is being made available.

The digital filter has a  $(\sin x/x)^3$  response, Fig. 3, and rejects noise frequencies lying within the notches. For the greatest possible rejection, it is possible to retune the filter periodically, under microprocessor control, to track the mains frequency. However, for most requirements, the fixed notch frequencies suggested below are more than adequate.

When correctly tuned, the converter will

## Converter configuration and programming

For a full explanation of the facilities of the AD7710 family readers are referred to the Analog Devices data sheets. The chip incorporates a microcontroller which programs the digital filter and operates various mode switches in the converter. It is programmed with a 24 bit control word which must be sent completely, msb first, and which I have split into three bytes:

Byte	MSB	-	-	-	-	-	LSB
1	MD2	MD1	MD0	G2	G1	G0	CH
2	WL	RO	BO	B/U	FS11	FS10	FS9
3	FS7	FS6	FS5	FS4	FS3	FS2	FS1

MD2, 1 and 0 set the calibration mode. Normally, on power-up and after calibration these read 000 and the device is in normal operating mode. The other modes of interest to us are as follows:

Bit pattern 001 instigates self calibration. The input selected by CH is shorted to analogue ground internally, a conversion run and the result stored as a zero offset coefficient. The input is then connected to  $V_{ref}$  internally, converted and stored as a full scale coefficient. Calibration is then complete and the microcontroller uses these values when translating converter values for transmission. Due to thermal effects and contact potentials, there is a residual offset of a few microvolts between internal and external 'shorted inputs'. This is not important when the converter is used with a pc application program since extra coefficients can be saved by the program to remove the offset error. However, if perfect raw data is needed or if external signal conditioning is performed with drift-prone equipment, the 'system calibration' options are preferable. These are initiated by sending control words with the following mode bits:

Bit pattern 010 causes a system offset calibration. This would be sent after the external system input had been zeroed, for instance by grounding with a reed relay. The conversion result is stored as a zero offset coefficient and the converter returns to normal operation.

Bit pattern 011 causes a system full scale calibration. This would be sent after the external system input had been set to full scale, for instance by connecting to a reference voltage with a reed relay. The conversion result is stored as a full scale coefficient and the calibration is complete. Clearly any sort of signal source or conditioning can be included in this loop. In a transmission photometer, for example, zero could be a closed shutter and full scale, direct lamp illumination. By repeating system calibration every minute or so, long term drift of any component is eliminated. External system switching is facilitated in this board design by the output Darlington's which can operate relays as needed.

G2, 1 and 0 set the PGA gain in a binary sequence, from 1 to 128 – the default at power-on.

CH is the channel select, 0 = channel 1 which is the default at power-on. It should be appreciated that although the converter has two physical inputs it is not practical to use both continuously at full speed, nor is it sensible to use an analogue input multiplexer. The converter core needs to settle after a step change in input, unlike a successive approximation type, and this takes four measurement periods. If many inputs must be measured it is best to use several converters concurrently and read their outputs in turn.

PD sets the power-down mode which stops conversion to reduce power consumption but retains calibration coefficients. It defaults to normal operation (0) at power-on.

WL controls the output data word length and defaults to 16 bits (the most significant, of course) at power on. When set to 1, all 24 bits are transmitted though the last few bits are normally noise.

RO switches a 20µA current source on pin 17 and is not used in this design.

BO switches a 100nA current source to A1+ input which would typically be used to detect whether a low resistance sensor such as a thermocouple had burnt out and become open circuit.

B/U sets bipolar or unipolar mode, defaulting to 0 (bipolar). It does not alter the converter analogue section at all, just the output coding which is binary in unipolar and offset binary in bipolar. With a +2.5V reference, the unipolar differential input range is 0 to +2.5V; in bipolar it is -2.5 to +2.5V.

FS11-FS0 is a 12-bit value which must lie between 19 and 2000 and which defaults at power-on to 325. The 10MHz master clock is divided by this value and then by 512 to define the converter update frequency. Suitable decimal values for FS are 1562 (12.5 readings / second) and 1302 (15 readings per second). The filter notches occur at multiples of the update rate so 1562 will reject 12.5Hz, 25Hz, 37.5Hz, 50Hz etc., while 1302 is appropriate for 60Hz rejection. The ac response of the converter depends on the first notch frequency, such that the -3dB frequency is  $0.262 \times$  the first notch frequency. Hence with a 12.5Hz update rate, the useable bandwidth is dc to 3.3Hz. Note that noise increases with update rate and pga gain, reducing the dynamic range of the converter. The best combination of sensitivity and dynamic range occurs for a pga gain of 4 and an update rate of 12.5Hz. In combination with instructions to set bipolar mode, perform a self-calibration and select channel 1 as input, the resulting control word is 0010 1000 1000 0110 0001 1010 or, in hex, 28 86 1A.

completely reject mains frequency interference to greater than 150dB. However it cannot accept noise peaks far outside its common mode range without suffering modulator overload and consequent non-linear intermodulation. If high amplitude spikes do appear on the signal, some simple analogue filtering will also be needed.

### Interfacing to a PC

Data communication with the AD7710 is via a serial input/output pin, but several extra lines are needed to control data flow. For this reason, and since speed is not important, we found it most convenient to use a pc printer port with manually programmed serial communication. Analog Devices recommends that all digital lines to and from the converter are buffered. This was found to be essential, both to reduce noise-inducing transient currents from the converter and to prevent latchup if the data lines go high before the converter is powered.

High voltage 4050/4049 buffers are required. If ordinary c-mos gates or buffers are used, current passes through the input protection diodes to the supply rail which then powers up the digital side of the 7710 and sends it into scr latch-up. You will notice that spare gates in the 74HC125 are used to drive a front panel led – not functional, just something to flash. Latch-up-inducing input current here is simply limited by a large resistor.

Naturally, the pc is not the only possible host; the prototype was used with an 8052-based single-board microcontroller. The programming instructions shown in the Basic listing should make application to other systems quite easy. Table 1 is a list of pin functions as used by the pc and by the converter in this design.

### Converter input impedance

The converter's programmable gain amplifier is a useful inclusion. However, it is important to understand that the input current taken increases at high gains as multiple sample are taken by the integrating capacitor. Hence the input impedance decreases and this can induce loading errors.

In many applications, the loading error will be constant and can be calibrated out of existence. However, when the source impedance varies with output as is the case with some deflection bridge circuits, the variation in loading error will induce non-linearity.

Integrated circuits are incapable of being produced to high levels of absolute accuracy, so the exact input impedance cannot be quoted. It is about 720k $\Omega$  at unity gain, 360k $\Omega$  at a gain of two and reaches a minimum of 90k $\Omega$  at gains of eight and above.

Where high input impedance is important, for instance, pH electrodes, ionisation detectors and electrometers we recommend the use of an external buffer amplifier such as the AD549 'electrometer buffer amplifier'. This exhibits an extreme input impedance of 10<sup>15</sup> $\Omega$  and which can be incorporated into the self-calibration loop as discussed below in order to eliminate drift.

Table 1: Connections between the Centronics port and 7710 converter.

D25 connector	Centronics function	PC 8255 register line	Converter function	PC port Inverts!
1	/Strobe	C0	Red LED	*
2	DB0	D0	SCLK	
3	DB1	D1	TxDATA	
4	DB2	D2	/RFS	
5	DB3	D3	/TFS	
6	DB4	D4	Ext1	
7	DB5	D5	Ext2	
8	DB6	D6	Ext3	
9	DB7	D7	Ext4	
10	/ACK in	S6	ExtIn	
11	BUSY in	S7	grounded	*
12	Paper End in	S5	RxDATA	
13	On Line in	S4	/DRDY	
14	/LF/CR	C1	not used	
15	ERROR in	S3	link to 16	
16	/INITIALISE	C2	link to 15	
17	/SELECT	C3	not used	*
18-25	GROUND		GROUND	

Notes: For LPT1, the 8255 port addresses are 888 (data) 889 (status) 890 (control). For LPT2, the addresses are 632 (data) 633 (status) and 634 (control). The link between C2 and S3 can be toggled and checked to verify hardware connection of the converter.

### Analogue input connections

The IC has two inputs, either of which will operate over a wide range of voltages. For instance, the output of a strain-gauge bridge connected between 0 and 5V can be measured on input 1. The 2.5V common-mode voltage is ignored and the pga gain can be set to 128 for microvolt resolution.

The common-mode range extends from +5 to -5V. The pcb design makes the fully differential input 1 available directly and without protection on a 15-way D 'multi-function' connector. Input 2 is fed via an attenuator from the D connector and also from separate input terminals or a front panel BNC connector.

Because of its grounded attenuator, input 2 is not differential. The attenuator division ratio is not exact due to the relatively low converter input impedance. This is overcome, of course, by the self-calibration facility. The full circuit diagram of the converter is shown in Fig. 2 which also clarifies the multiple power supply regulation.

### Implementing self-calibration

Self-calibration is a facility which can be added to any microprocessor-controlled equipment, but which is generally reserved for high-accuracy systems. The commands for self-cal-

ibration are explained in the panel discussing the set-up and control word for the 7710. These commands result in a linear converter response.

Naturally, self-calibration does not imply traceable calibration or comparison with anything except the system's own reference. Thus, for instance, although the voltage reference used in this system has a very small guaranteed drift with temperature and time, it has a relatively wide initial voltage tolerance.

A typical ratiometric panel meter IC would inherently deliver a zero reading at zero input and a full scale reading when the input is equal to the reference – equal to minus one count, to be pedantic. This reference is typically 1V or 100mV, derived through a preset potentiometer from a bandgap voltage reference IC, the preset being adjusted to calibrate the meter.

A normal preset would not be sufficiently stable for this design. You can make a more stable system by connecting the REF-03 directly to the 7710 to make an 'approximately 0-2.5V' converter.

Data fed from the converter to the supervising pc are simply 24 bit numbers. The process of 'absolute calibration' is to apply zero volts and an accurate near-full-scale

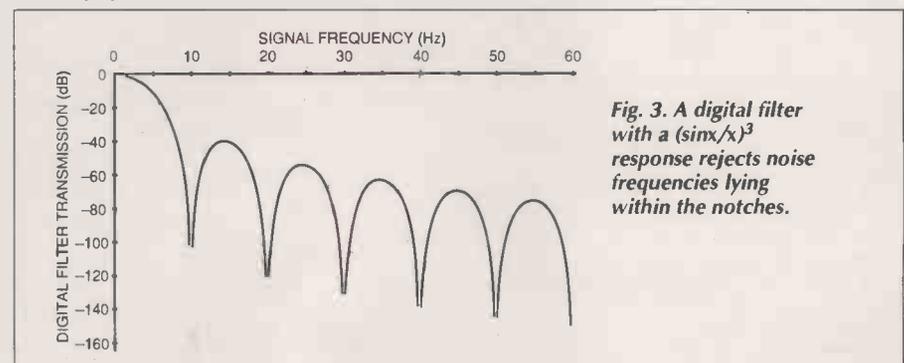


Fig. 3. A digital filter with a  $(\sin x/x)^3$  response rejects noise frequencies lying within the notches.

voltage from a high-quality calibrator. Next, note the corresponding numerical values coming into the pc and insert appropriate conversion factors in the pc program to display correct absolute values.

These conversion factors can be held in an initialisation file. If the converter is incorporated in a larger system, overall system calibration can be done the same way and an initialisation file held for any set-up. This facility is fully utilised in the Windows application program to present a virtual instrument with relevant units – a strain gauge load cell output displayed in kg, for instance.

Non-linear calibrations, incorporating corrections for the well-known non-linearities of thermocouples, for instance, can be dealt with in a couple of ways. If the polynomial coefficients are known they can be included in the user's program. Alternatively, the system can be calibrated at several fixed points and the polynomial coefficients calculated by least squares curve fitting.

### Digital input/output facilities

As there are several spare lines available on the Centronics port and some space on the pcb it was thought well worthwhile to add a few

buffered digital inputs and outputs. There is little to say about these except that the *MPSA14* can carry 300mA and hold off 30V which makes it capable of switching relays. Don't forget to add a recirculation diode across the coil.

A single protected digital input is included to allow external triggering. Its cost is negligible and it has been found very useful for automation experiments.

The 12V regulated supply is also available to power external signal conditioning. It should not be misused as a robust bench power supply since if the *AD7710* analogue

## This basic Basic routine allows communication between the 22bit a-to-d converter and a PC via the printer port.

```

DECLARE SUB screenmeter (volts!)
DECLARE SUB flash ()
DECLARE SUB digitalout (code)
DECLARE SUB digitalin (level$)
DECLARE SUB convertersetup ()
DECLARE SUB setbit (port!, bit!)
DECLARE SUB clearbit (port!, bit!)
DECLARE SUB getword (adval)
DECLARE SUB waitconverter ()
COMMON SHARED dataport, statusport, controlport, outword, s$
REM a program to test the Centronics converter functions
REM written on August 2 1995
REM printer port addresses for lpt1
dataport = 888
statusport = 889
REM only used for front panel red LED
controlport = 890:
REM initial setup - _RFS, _TFS high, rest low
outword = 12:
REM ***** Start of Program *****
OUT dataport, outword
waitconverter
convertersetup
screenmeter (0)
FOR i = 1 TO 10: flash: NEXT
DO UNTIL INKEY$ ""
  getword adval
  REM omit for unipolar
  adval = adval - 2 ^ 23:
  REM use 2^24 for unipolar
  volts = adval * 2.5 / (2 ^ 23):
  LOCATE 16, 27
  PRINT "converter INPUT IS: ";
  PRINT USING "#.#####"; volts;
  PRINT " VOLTS"
  flash
LOOP
SUB convertersetup
md$ = "001": REM mode; 001 = int zero, self-calibration
pg$ = "000": REM PGA gain, set to 1x here
ch$ = "1": REM channel selection, set to channel 2
pd$ = "0": REM power-down, turned off
wl$ = "1": REM word length, set to 24 bits
ro$ = "0": REM RTD excitation current, turned off
bo$ = "0": REM burn-out detection current, turned off
bu$ = "0": REM bipolar/unipolar, set to bipolar
f1$ = "0110": REM first 4 bits of filter '6'
f2$ = "0001": REM middle 4 bits of filter '1'
f3$ = "1010": REM last 4 bits of filter 'A'
s$ = md$ + pg$ + ch$ + pd$ + wl$ +
  ro$ + bo$ + bu$ + f1$ + f2$ + f3$
REM filter is set here to 61A = 1562 decimal,
REM ie 12.5Hz sampling rate
REM set up dataport with _RFS, _TFS high
OUT dataport, outword:
REM clears dataport bit 3, ie takes _TFS low
clearbit dataport, 3:
REM now clock out control word (24 bits)
REM by toggling SCLK line
FOR i = 1 TO 24
  IF MID$(s$, i, 1) = "1"
    THEN setbit dataport, 1 ELSE clearbit
    dataport, 1
    setbit dataport, 0: REM SCLK line
    clearbit dataport, 0
    NEXT i
  setbit dataport, 3: REM return _TFS high
END SUB
SUB clearbit (port, bit)
valbit = 2 ^ bit
outword = outword AND NOT valbit
OUT port, outword
END SUB
SUB digitalin (level$)
S6 = INP(statusport) AND 64: REM comes in on line S6
IF S6 = 64 THEN level$ = "low" ELSE level$ = "high"
END SUB
SUB digitalout (code)
REM this sends out a code from 0 to 15 on the Darlington
outword = outword AND 15: REM ensure top 4 bits are off
outword = outword OR (code * 16): REM place top 4 bits out
OUT dataport, outword
REM this is a bit simple because it's not set bit by bit
REM so there will be an 'off' glitch every time.
END SUB
SUB flash
OUT controlport, 1: FOR i = 1 TO 10000: NEXT
OUT controlport, 0: FOR i = 1 TO 10000: NEXT
END SUB
SUB getword (adval)
waitconverter
adval = 0
clearbit dataport, 2: REM take _RFS low
FOR i = 0 TO 23
  setbit dataport, 0: REM take SCLK high
  IF INP(statusport) AND 32
    THEN adval = adval + 2 ^ (23 - i)
  REM read statusport bit 5,
  REM add its value to adval, MSB first
  REM take SCLK low again
  clearbit dataport, 0:
NEXT
setbit dataport, 2: REM return _RFS high
END SUB
SUB screenmeter (volts)
SCREEN 12
LINE (0, 0)-(639, 479), , B
LINE (100, 100)-(539, 379), 5, BF
LINE (170, 220)-(470, 270), 0, BF
LOCATE 11, 27
PRINT " AD7710AN BASIC TEST PROGRAM "
END SUB
SUB setbit (port, bit)
valbit = (2 ^ bit)
outword = outword OR valbit
OUT port, outword
END SUB
SUB waitconverter
notready:
  IF INP(statusport) AND 16 THEN GOTO notready
END SUB

```

supply dips below the digital side for an instant it changes from a data converter into a thyristor and gets very hot.

Lines to the connector include current-limiting 22Ω resistors to provide some protection. Only a few tens of milliamps are available and decoupling capacitors will be needed on the external circuitry.

**Test program written in Basic**

A listing is given for a minimal test program. This routine operates the converter by somewhat agricultural data transmission methods but it serves to illustrate the important points.


Initially, the parallel port is set up for normal action and no communication. The program waits for the converter to indicate readiness by taking /DRDY low. A 24 bit set-up word is sent to the converter by taking the transmit frame synchronisation signal /TFS low, setting TxDATA high or low and toggling serial clock line SCLK for each bit. After all 24 bits have gone /TFS is returned high.

Converter values are read in a similar fashion, by taking the receive frame synchronisation signal /RFS low and clocking data into the computer by toggling the SCLK line.

A possible cause of confusion when working with the parallel printer port is that the pc hardware inverts some of the lines. Because of this, a bit set in the output register may not come out of the socket high. Port lines chosen for this design are mostly non-inverting. Table 1 provides information on the port lines.

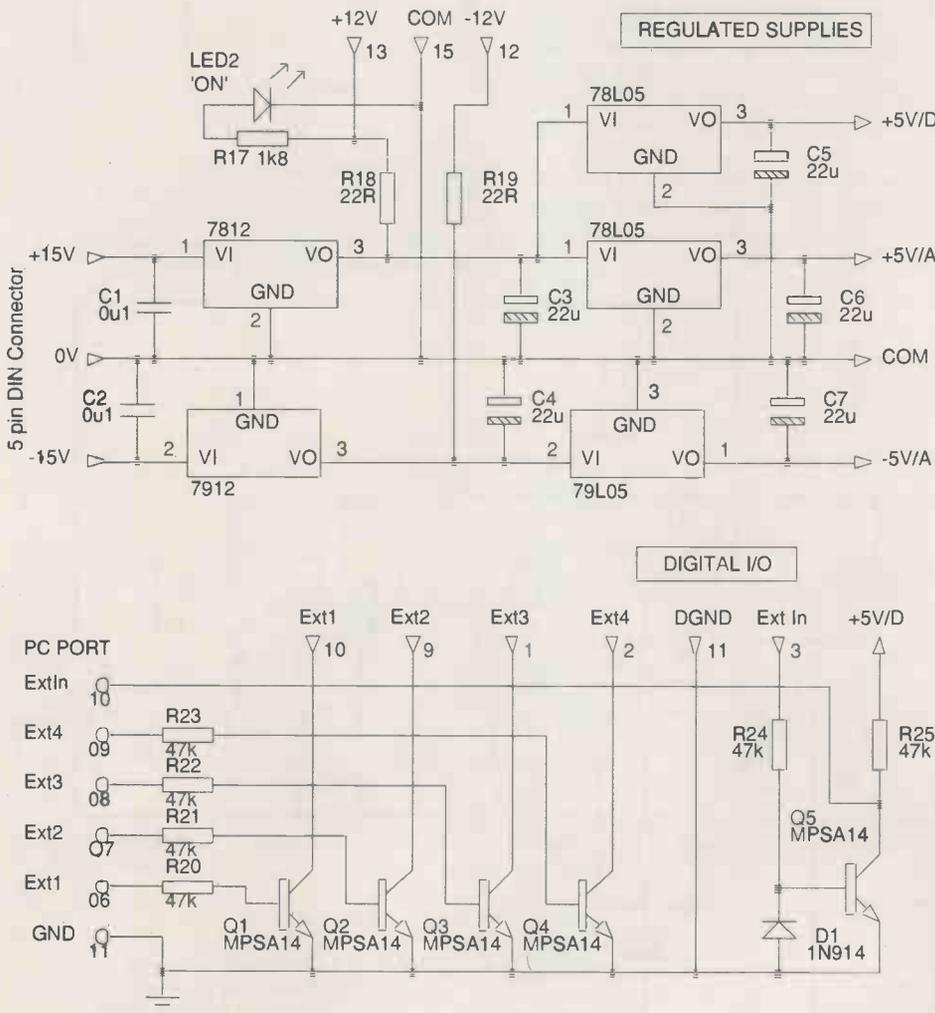**Summary**

Ultra-high resolution, high accuracy analogue measurement used to be the preserve of very expensive and exotic equipment, supplied by companies like Fluke, Hewlett Packard and Solartron. While the extremes of quality measurement must stay with such companies, this hardware/software approach should provide performance in excess of most conceivable professional and amateur requirements – at a relatively low cost. ■



Note: pins marked ○ are on rear panel PC port connector pins marked ▽ are on front 'Multifunction Connector'

'Ext In' is very high impedance and needs external pull-up or pull-down resistor

*Regulator and digital i/o for the 22bit a-to-d converter. Note that the regulators are fed from a separate dc power supply.*

**Exclusive 25% discount for EW readers**

Based on this article, the MPM ADC 22bit built and tested a-to-d converter normally sells at £340 but is available to EW readers at a special 25% discount price of £255 – fully inclusive\*.

This self contained, high performance unit has two analogue inputs and connects directly to the PC's LPT port. It is supplied with:



- Win 3.x/95 virtual-instrument software for logging, graphing, metering etc.
- independent psu
- calibration to a high accuracy of 0.01%.
- anodised aluminium enclosure

In addition, the following items are available separately:

- Circuit board, double sided, with full solder mask and component identification, disk together with Basic routine and component/supplier lists – £28.
- Anodised, machined and printed front and back panels to suit specified standard enclosure – £22.
- Windows 3.1x or Windows 95 application program with full virtual instrument facilities, data logging, experiment automation and data compatibility with all common applications, accompanied by a .dll file to incorporate ADC control into user programs – £34.

Send cheque or postal order made payable to MicroPower Measurements to 4 Elwick Terrace, Hutton Rudby, North Yorkshire TS15 0DH. Phone 01642 342266 or phone/fax 01642 701786. Please send all enquiries relating to this offer to the above address.

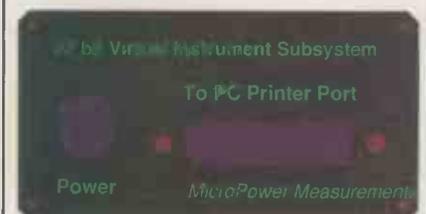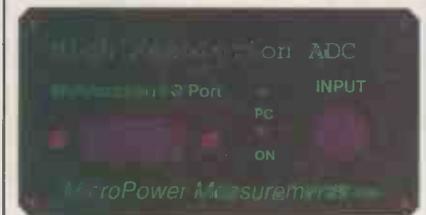\*Overseas readers should write to MicroPower Measurements for offer details.



Benefiting from a new high-side switching device - namely a Treeswitch - this economical battery charger allows fast charging of NiCd and NiMH and reduces 'memory effect' in NiCd cells.

# Fast charger for NiCd and NiMH

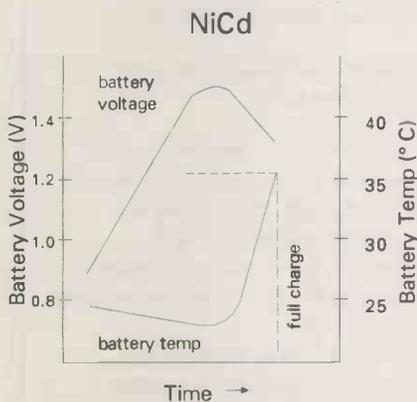


Fig. 1. Charging characteristics of NiCd cells indicate that battery voltage starts to fall significantly just before full charge.

Generally, nickel-cadmium cells, or NiCd cells, are trickle charged at 0.1C for about 14h., Fig. 1. With better understanding of battery chemistry the trend is shifting towards rapid charging at higher rates - 1C and greater for example - especially in the professional market.

The new generation of 'smart charger' employs an ASIC, often in combination with a microcontroller to optimise battery management. The methods used to detect end of charge are dv/dt inflexion, temperature and time.

We found that the monitoring of temperature to detect end of charge is as effective as the dv/dt method, which can be a problem for NiMH as the inflexion point is not well

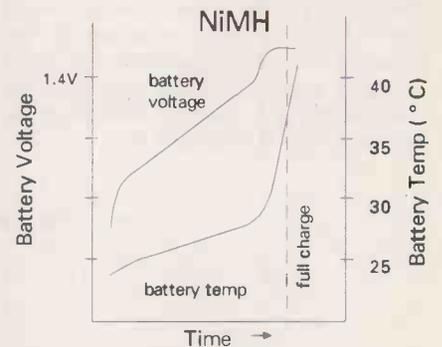


Fig. 2. With NiMH cells, charging characteristics show that the voltage fall at full charge is much less significant than with NiCd alternatives to temperature change is a more useful indicator of cell charge status.

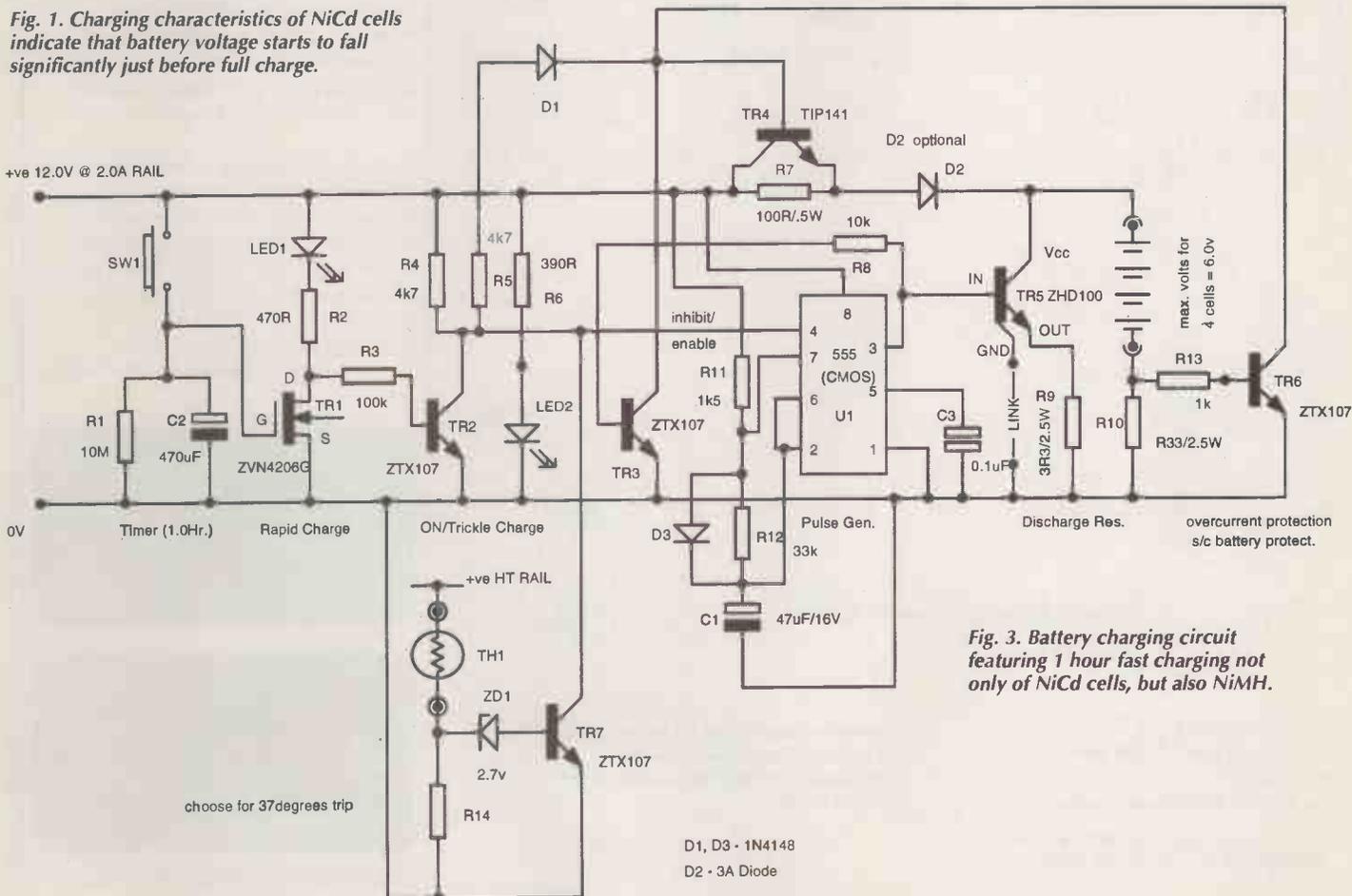


Fig. 3. Battery charging circuit featuring 1 hour fast charging not only of NiCd cells, but also NiMH.

defined, Fig. 2. However, as the 38°C end of charge temperature for nickel-metal-hydride cells, NiMH, is greater than the 35°C, of NiCd cells, using the temperature-only method results in a slight undercharge for NiMH batteries.

**Benefits of charge/discharge cycles**

Figure 3 shows a circuit capable of charging four 'AA' size cells in series within 1hr – less if the cells are not fully discharged. When rapid charging, the circuit supplies a 3s charge, then 10ms discharge current pulse. This repeated discharging during charging reduces or removes the memory effect of in NiCd cells.

At switch on, the charger defaults to trickle charging at 70mA, so it can be used as a simple conventional charger. When SW<sub>1</sub> is

momentarily closed a 1.2h timer is enabled and the charger goes into rapid charge mode, charging at a 1C rate of about 1A.

Temperature of the battery rises as it nears full charge. When it reaches 35°C, the unit reverts to trickle charge and stays indefinitely in this maintenance mode – until SW<sub>1</sub> is closed again.

The prototype unit was set so that the timer was greater than that required to charge NiMH from zero depth of discharge. This ensured the cells would be charged to maximum, whatever the initial state of the cells.

The unit has been in use for some time and has successfully recharged both NiCd and NiMH cells – some of which would not hold charge using conventional trickle chargers. In fact, we observed that only cells showing signs of physical leakage damage could not be

recharged – others, even very old ones can be charged with varying degrees of success.

A unique feature of this circuit is the incorporation of a new device called a Treeswitch. Designated the ZHD100, this discrete semiconductor comprises a bipolar power device with a mosfet input (see panel). This topology enables the discharge circuit to be implemented easily.

For safety reasons, the unit will not allow rapid charging if there are any short circuit cells in the stack; it defaults to trickle charging.

A 12V, 1A power supply is suitable for driving the circuit shown. To charge larger capacity cells – C and D sizes for example – a psu with the same current capacity of the cell to be charged is recommended for 1h fast charging. ■

**Treeswitch – a bipolar high-side driver with mosfet input characteristics**

'Treeswitch' is a term describing a new monolithic semiconductor structure combining the benefits of mosfet and bipolar transistor technology. Invented at Zetex, the device is a high-side switch featuring high input impedance and bipolar transistor power switching characteristics.

Unlike most previous bipolar/mosfet combinations, the Treeswitch is a four terminal device. Initial products in the range, namely the ZHD100 and ZDHD100, are single and dual high side switches operating from supply voltages to 80V with continuous currents to 250mA.

To achieve the integration in a rugged and cost-effective manner the designers developed a new technology platform – the structural integration of Zetex's matrix bipolar transistor technology and a mos input stage. The result is a patented bi-mos structure offering the combined advantages of a ground referenced standard logic level mos input with a V<sub>cc</sub> referenced low output voltage drop.


This seemingly simple integration task was complicated by conflicting process requirements and the presence of unwanted parasitic interactions, requiring extensive simulation and verification testing to optimise the device performance.

The advantage of separating the collector and source is that the low saturation voltage of the transistor can be fully exploited. This is in contrast to an igbt structure where the voltage drop is at least a volt.

Pulling the gate positive with respect to the source attracts electrons into the p-type material below it which forms an n-channel between the base and source. This allows base current to flow and turns the transistor on.

The transistor has Zetex's matrix architecture, which results in unusually low saturation voltage. The fet sits in the middle of it and is small in comparison, limiting the amount of current it can pass. This makes the fet approximate a constant-current device, removing the need for a drain-base current limiting resistor.

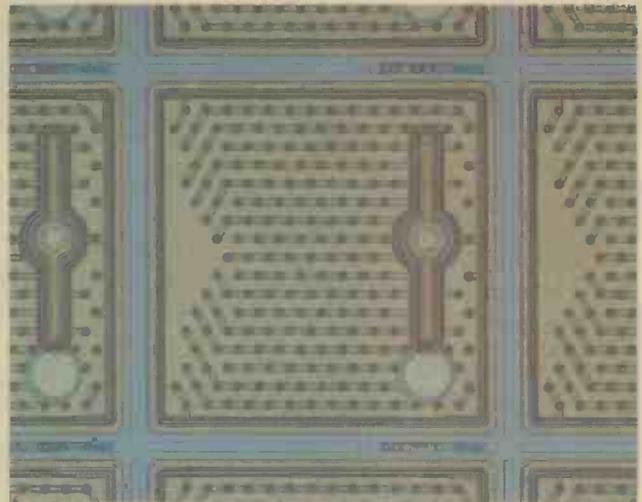Housed in SOT223 or Zetex's SMB packages, the first devices to be released are designed with ruggedness in mind, being able to switch over two amps depending on the duty cycle and drive supplied.






Photomicrograph of the Treeswitch – a four-terminal monolithic device combining the benefits of mosfet input impedance with bipolar switching characteristics.

At high voltages the device dissipation is predominantly from the 10mA base current. If the full output current of the device is not required, this can be reduced by adding a series resistor between the source and ground.

Although there are other high-side switches on the market, co-inventor of the Treeswitch David Casey said: "The matrix architecture results in a very small chip compared with its competitors. The small chip leads to a low device cost."

Structure of the Treeswitch is shown below left, followed by an example of how the device saves components in a typical relay driving application..

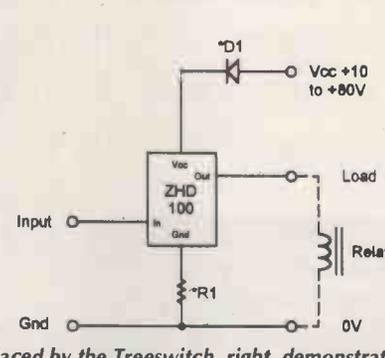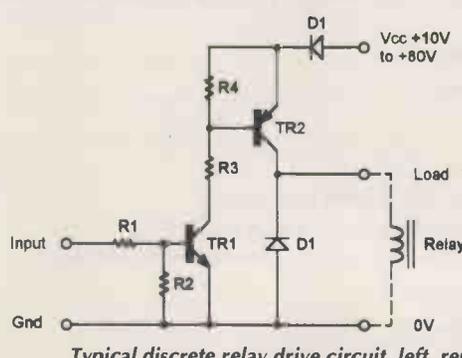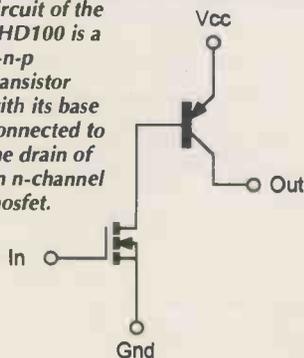Equivalent circuit of the ZHD100 is a p-n-p transistor with its base connected to the drain of an n-channel mosfet.



Typical discrete relay drive circuit, left, replaced by the Treeswitch, right, demonstrates the saving in components.






# BRIGHT SPARKS USE ELECTROMAIL

(HE DIDN'T)

**W**hatever your specific interest ; radio-controlled models, radio-communications or general electronics, the one component you can't afford to be without is Electromail.

Electromail gives you instant access to Europe's largest stock of electrical, electronic and mechanical components.

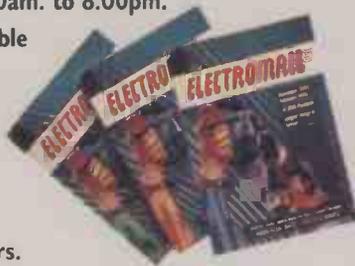- 👉 60,000 product lines available ex-stock.
- 👉 All top brands, tested and approved by our engineers.
- 👉 Order by Phone, Fax -24 hours a day, 365 days a year.
- 👉 Order lines manned 8.00am. to 8.00pm.
- 👉 Next day delivery available on request.
- 👉 Repair and Calibration service available.
- 👉 Nominal P&P charge of only £2.95+VAT on all standard delivery orders.



To find out more about Electromail, See the Internet  
<http://www.rs-components.com/rs/>

## ELECTROMAIL

Everything you need at the end of the phone!

### SPECIAL OFFER WINDOW STICKERS AND TRANSFERS



Claim one of our unique, limited edition "Bright Sparks Do It With Electromail" window stickers and transfers. We're giving away 6,000 of them. Simply place an order of any value, including orders for a catalogue, and quote reference EWW1. Please allow 28 days for delivery of your sticker and transfer.

**HURRY OFFER ENDS WHEN STOCKS RUN OUT**

### WIN A FANTASTIC PSION 3A POCKET COMPUTER

Your chance to win this powerful 256k memory PSION 3A pocket computer. To enter the prize draw simply recommend a friend you think would be interested in the Electromail service. No purchase is necessary. Send your friend's name, address and telephone number, plus your own together with your Customer Reference Number (If you have one) and tell us in not more than 20 words, why you would use Electromail. Applications can be sent by post or fax quoting reference EWW2. Full rules and conditions are available on request.

**Postal applications to:** Amanda Johnston, D.P.N.55, Electromail, P.O. Box 33, Corby, Northants, NN17 9EL

**Fax Applications:** E.A.O. Amanda Johnston on Fax No 01536 405555



All entries must be received at Electromail's office by 5.00pm on Friday 31st May to qualify. All qualifying entries will be included in the prize draw and the winner will be advised by post by 16th June. This competition is not open to employees (or their families) of Electromail or associated companies, or public servants and members of government bodies or agencies involved in this promotion. No cash alternative is available and no correspondence will be entered into. The judges decision is final.

**Electromail, P.O. Box 33, Corby, Northants NN17 9EL.**

**TELEPHONE 01536 204555 24 HOUR A DAY ORDER LINE**

Cards accepted when placing an order



# Designing valve RIAA preamps

**A**n RIAA preamplifier, to last month's philosophy, needs three individual stages. A cascode or a  $\mu$ -follower are both possibilities for the input stage, but initially, it is advisable to use a common cathode triode for simplicity. The second stage can be the same, but the third will need to be a cathode follower for reasons that will become apparent later. You can now draw a circuit diagram for the complete RIAA stage, Fig. 1.

The  $75\mu\text{s}$  hf loss is formed by the combination of  $R_4$ ,  $R_5$ , and  $C_3$ , whereas the  $3180\mu\text{s}$ ,  $318\mu\text{s}$  pairing is formed by  $R_8$ ,  $R_9$ , and  $C_5$ . The calculation of these components is simple, but you must remember to account for hidden components. Examples of these are the output impedance of the valve, and Miller input capacitance of the next stage in parallel with strays.

**Delving further into valve preamplifier design, Morgan Jones shows how to produce a no-compromise balanced design combining the benefits of valves and transistors.**

## Calculation of $75\mu\text{s}$ component values

The entire pre-amplifier is based on the E88CC dual triode, and for the dc conditions chosen for our common cathode triode input stage,  $r_a$  equals  $6\text{k}\Omega$ . This is in parallel with the  $100\text{k}\Omega$  anode load resistor, so  $Z_{\text{out}}$  is  $5.66\text{k}\Omega$ .

To calculate the capacitor needed for the  $75\mu\text{s}$  time constant, you need to find the total Thévenin resistance that the capacitor sees in parallel, as shown in Fig. 2.

For the moment, you can ignore  $C_1$ . It will be accounted for later. Capacitor  $C_3$  sees the grid-leak resistor  $R_5$  in parallel with the series combination of the output impedance of the preceding valve and  $R_4$ . As is usual, you will make the grid-leak as large as is allowed, so  $R_5$  equals  $1\text{M}\Omega$ .

You are now free to choose the value of  $R_4$ .




Impedance  $Z_{\text{out}}$  needs to be a small proportion of  $R_4$ , otherwise variations in  $r_a$  will upset the accuracy of the equalisation. Too large a value of  $R_4$  will form an unnecessarily lossy potential divider in combination with  $R_5$ . At high frequencies, capacitor  $C_3$  is a short circuit, and so the additional ac load on the input valve will be  $R_4$ . A good value for  $R_4$  is  $200\text{k}\Omega$ , and it has the bonus of being available both in 0.1% E96 series, and 1% E24 series. Very few E24 values are common to the E96 series. In combination with  $R_5$ , this gives an acceptable loss of 1.6dB, while not being an unduly onerous load for the input stage.

The capacitor now sees  $200\text{k}\Omega$  and  $5.66\text{k}\Omega$  in parallel with  $1\text{M}\Omega$ , giving a total resistance of  $170.58\text{k}\Omega$ . Dividing this value into  $75\mu\text{s}$  gives the required capacitance value of  $440\text{pF}$ , but you must subtract the stray capacitance of the next stage.

Gain of the second stage is 29, and  $C_{\text{ag}}$  is  $1.4\text{pF}$ , so the Miller capacitance will be 30 times  $1.4\text{pF}$  which is  $42\text{pF}$ . In addition to this, the cathode, the heaters, and the screen are at earth potential, and will be in parallel with this capacitance.  $C_{\text{g-k+h+s}}$  is  $3.3\text{pF}$ , and you ought to allow a few pF for external strays. A total input capacitance of  $50\text{pF}$  would be reasonable.

Total capacitance required is  $440\text{pF}$  minus  $50\text{pF}$ , or

**Fig. 1. Basic RIAA preamplifier stage incorporates two common cathode stages followed by a cathode follower.**

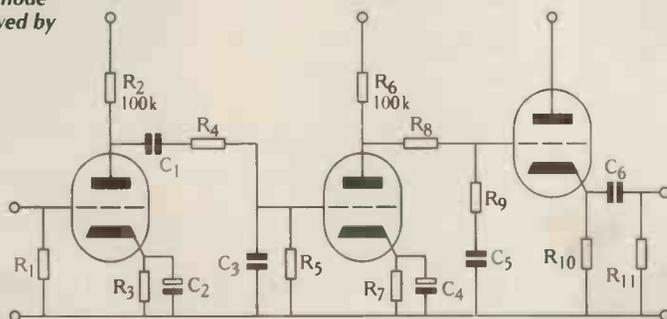

390pF, so a 390pF 1% capacitor is acceptable.

Earlier, the effect of coupling capacitor  $C_1$  was ignored, but this must have some effect on the Thévenin impedance seen by the 390pF capacitor. You could use such a large value that its reactance was negligible compared to the 200kΩ series resistor, but a more elegant method is to move its position slightly, Fig. 3.

The capacitor now only has to be negligible compared to 1MΩ. The 75μs delay corresponds to a -3dB point of approximately 2kHz, so it is at this frequency that the values of other components are critical. At 2kHz, a 100nF capacitor has a reactance of approximately 800Ω, which is less than 0.1% of 1MΩ. If you had not moved the capacitor, you would have needed a value of 470nF simply to avoid compromising RIAA accuracy.

**Interaction problems**

The second stage is direct coupled to the cathode follower, so you do not need to worry about interaction between a coupling capacitor and the 3180μs, 318μs pairing. This is fortunate, since 3180μs corresponds to 50Hz, which is close to our 1Hz cut-off. These time constants are sufficiently close that they would interact significantly.

The other reason for using a cathode follower is its low input capacitance. Any stray capacitance across the 3180μs, 318μs pairing will cause an additional high frequency roll-off. In the 75μs network, you were able to incorporate the value of stray capacitance into your calculations, but in this instance this is not possible, and it is therefore essential that stray capacitance is so small that it can be ignored. The full equation for the input capacitance of a cathode follower is,

$$C_{input} = C_{ag} + (1 - A)C_{gk}$$

For a cathode follower,  $A_v$  approximates to  $\mu/(\mu+1)$ ; for an E88CC,  $\mu$  is approximately 32, resulting in a gain, an  $A_v$  of 0.97. Capacitance  $C_{ag}$  is 1.4pF, and  $C_{gk}$  is 3.3pF. The  $C_{gk}$  term is negligible at 0.1pF, and so the input capacitance is virtually independent of gain at 8pF – including an allowance for strays.

The equations that govern the 3180μs, 318μs pairing are delightfully simple,  $CR$  is  $318 \times 10^{-6}$ , and the upper resistor is 9R. Loss at 1kHz for this network is 19.05dB, Fig. 4.

You should now check whether the 8pF stray shunt capacitance is sufficiently small not to cause a problem. To do this, you need to employ a slightly circular argument.

First assume that it will not cause any interaction. If this is true, then the frequency at which the cut-off occurs will be so high that C in the network is a short circuit. If it is a short circuit, you can replace it with a short circuit, and calculate the new Thévenin output impedance of the network.

Since the ratio of the resistors is 9:1, the potential divider must have a loss of 10:1, and the output impedance is therefore one tenth of the upper resistor. If you assume that the upper resistor will again be 200kΩ while neglecting  $Z_{out}$  of the previous stage, the Thévenin resistance that the 8pF stray capacitance sees at high frequencies is 20kΩ, this gives an hf cut-off of 1MHz.

As a rough rule of thumb, once the ratio of two interactive time constants is  $\geq 100:1$ , the response error caused by interaction is inversely proportional to that ratio. A ratio of 100:1 causes an error of approximately 0.1dB.

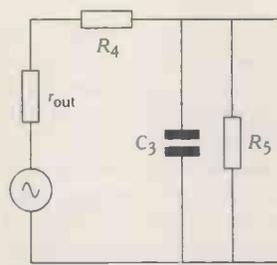


Fig. 2. Determining RIAA's 75μs time constant involves finding the total Thévenin resistance that the capacitor sees in parallel.

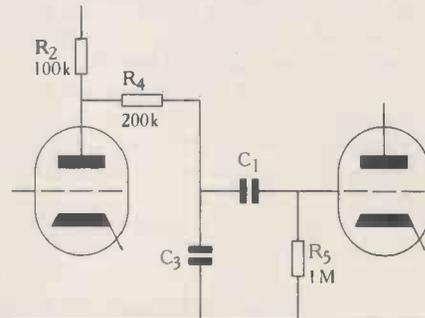


Fig. 3. Moving the coupling capacitor rightwards in the network reduces interaction.

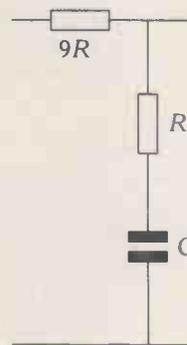


Fig. 4. These values produce the RIAA 3180 and 318μs time constants.

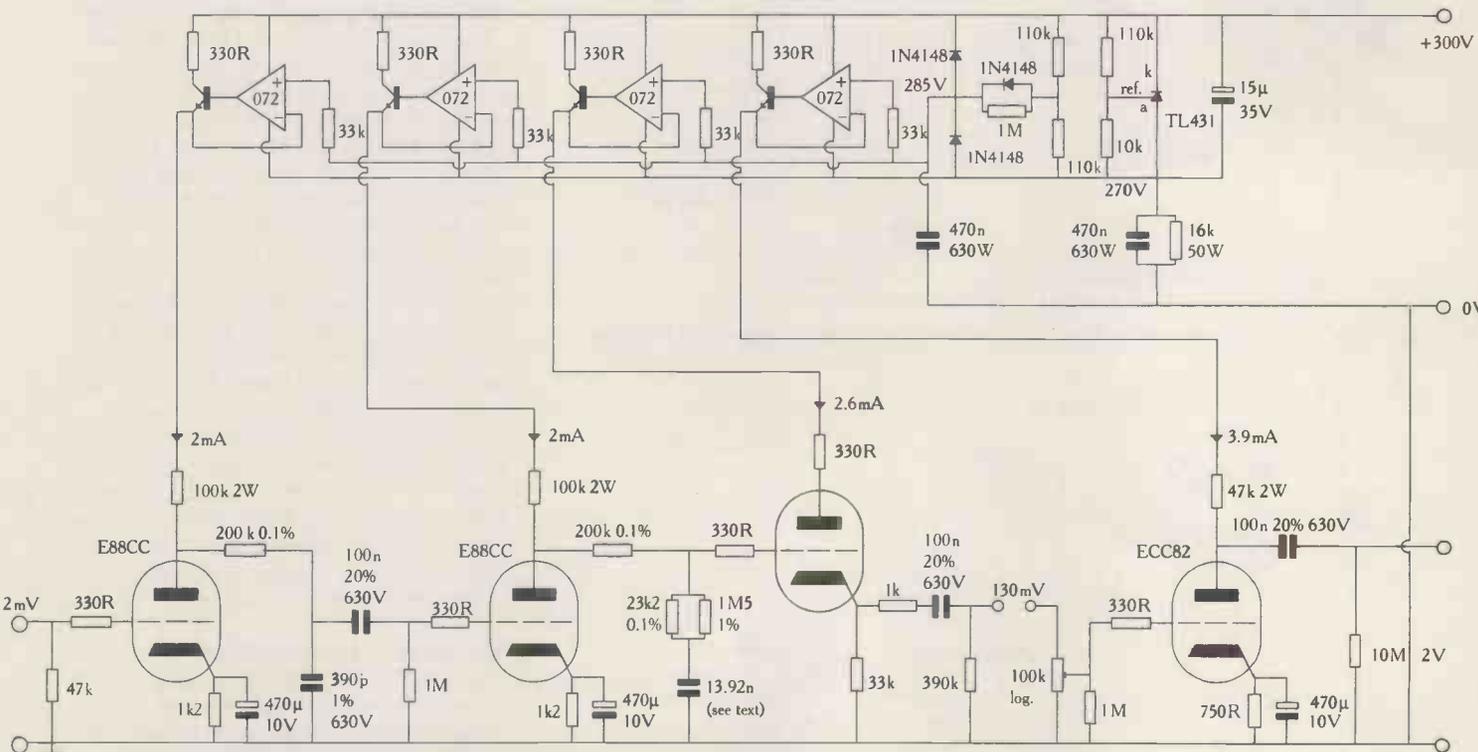


Fig. 5. Practical valve preamplifier design featuring op-amps to increase power supply rejection ratio.

In this example, the ratio of 1MHz to the nearest time constant of 318µs (500.5Hz) is 2000:1. You can now safely ignore interaction and go on to accurately calculate the values for the 3180µs, 318µs pairing.

If the network were driven from a source of negligible resistance such as an op-amp, ideal values for the resistors would be 180kΩ and 20kΩ, since these are both members of the E24 series. The capacitor could then be 16nF with only 0.6% error. Unfortunately, the source has appreciable output resistance, so you will again choose 200kΩ as the upper resistor and accept whatever values this generates for the lower two components.

Since the second stage is identical to the first, output resistance is 5.66kΩ, making a total upper resistance of 205.66kΩ. The lower resistor will therefore be 22.85kΩ, and the capacitor 13.92nF.

A resistance of 22.85kΩ can be made from a 23.2kΩ, 0.1% resistor in parallel with a 1.5MΩ, 1%. A capacitance of 13.92nF can be inconveniently made from a pair of 6.8nF in parallel with 330pF. You can now draw a full diagram of the preamplifier stage with component values, Fig. 5.

Equalisation networks for RIAA invariably generate awkward component values, requiring much manoeuvring to nudge them accurately onto the E24 series.

**Power supply rejection ratio**

Although individual stages have been designed and interconnected to form an audio system, each stage requires power. Supplies are always derived from a common source.

No practical source has zero output resistance, although ac mains is a good approxi-

mation. The issue of a common power supply with non-zero output resistance is crucial. It implies that as a given audio stage draws a varying supply current in sympathy with the audio signal, a voltage will be developed across the source resistance of the supply.

Although attenuated by individual stage rejection ratio, this voltage is now an input to all other stages. If power supply rejection ratio, psrr, is low while the signal gain between stages is high as in an RIAA stage, the loop gain via the power supply may be greater than unity. This results in oscillation.

Traditional power supplies used a shunt capacitor to define their source impedance, resulting in increased source impedance at low frequencies since,

$$Z_{source} = \frac{1}{2\pi fC}$$

Therefore instability would be more likely at low frequencies, although the non-zero effective series resistance of the normally electrolytic supply capacitors could provoke high-frequency instability if not bypassed.

Modern designs use regulators giving excellent  $Z_{source}$  down to dc. However, because the error amplifier must have a response falling with frequency in order to maintain its own stability,  $Z_{source}$  is inductive and rises with frequency, and hf instability is a possibility.

Summarising, any practical common supply will always have non-zero output resistance. System stability is only maintainable if individual stages have sufficient psrr to that common supply. It is useful to define two new terms:

- Intrinsic psrr: the psrr due to the topology of an individual stage.

- Common supply psrr: intrinsic psrr plus any added psrr – by whatever means – to the common supply point.

Any common cathode stage possesses intrinsic psrr by virtue of the potential divider formed by  $r_a$  and  $R_L$ , but an E88CC operated such that  $r_a$  is 6kΩ, and  $R_L$  is 100kΩ only results in an intrinsic psrr, referred to the output, of 24dB. Using the same valve as a µ-follower could improve this to 50dB, a differential pair might improve the 24dB figure to 64dB depending on valve matching. Used as a cascode, the valve's 24dB figure would be degraded to zero.

Any given stage may have its common supply rejection ratio increased by an arbitrary amount using individual filtering or regulation. Apart from expense, it does not matter whether the common supply rejection is made up mostly from intrinsic psrr, or added psrr via filters or regulators.

Extreme methods might even include individual mains transformers and supplies for each stage. This increases common supply rejection ratio to the ac mains, the common supply point. Use of a dedicated spur from the electricity supply company cable head would be a means of reducing  $Z_{source}$ .

A more elegant and considerably cheaper method of improving common supply rejection ratio is to add the high intrinsic psrr of an op-amp to stage intrinsic psrr by supplying each stage via a voltage follower op-amp. This was illustrated in the previous diagram. In order to obtain a low  $Z_{source}$ , a regulator is used at the common supply point, Fig. 6.

**Practicalities and performance**


For optimum performance, valve pre-amplifiers should have a 'standby' mode, whereby the heaters are supplied with approximately 63% of operating heater voltage. This ensures a minimum of gas molecules within the vacuum. These molecules become ionised when ht is applied, accelerating them to the cathode, resulting in stripping of the cathode emissive surface. As a result, they should be kept to a minimum. At switch-on, ht is applied, and the heaters are restored to full voltage, Fig. 7.

A dual colour led was fitted as a power indicator with its green led lit by the permanently applied heater supply, and the red led in series with the lower leg of the ht sink resistor for the op-amps. Switching the pre-amplifier on therefore results in an orange glow similar to the colour of a valve heater, but a pure red glow would indicate heater supply failure.

The preamplifier was designed to be as simple as possible while retaining quality. It works well. Paired with a Garrard 301 on a solid plinth, using an Ortofon *Quattro* moving coil cartridge in a unipivot arm designed and built by me, the complete LP system was comparable to a £2,000 cd-based system.

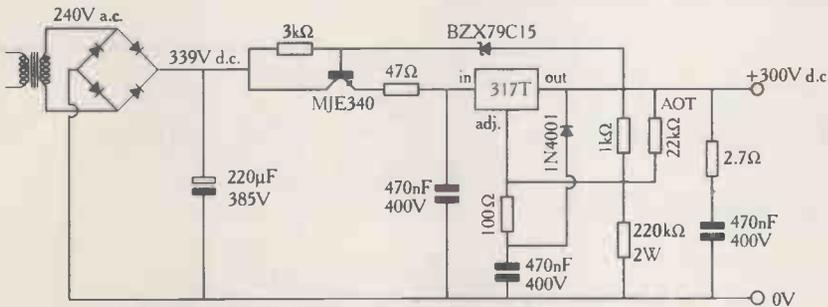**The balanced preamplifier**

Although logic dictated optimum system topology for the RIAA stage, individual stage design is flexible. Audio stage complexity can usefully be traded against power supply com-



Both the MJE340 and the 317T must be mounted on, and carefully insulated from, a substantial heatsink such as a piece of 3mm thick aluminium angle extrusion.

Fig. 6. Practical 300V regulated ht supply incorporating a floating 317 adjustable regulator.

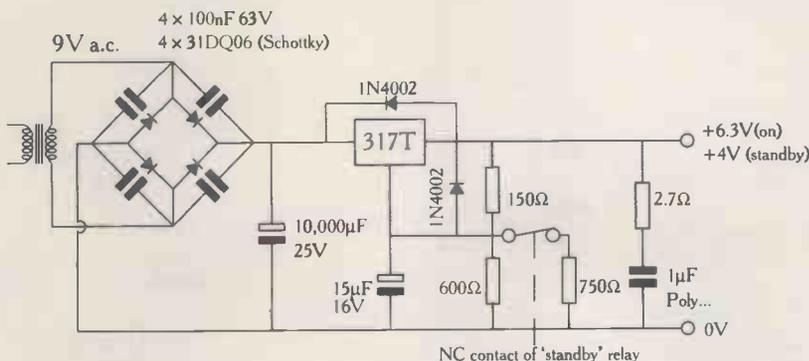


Fig. 7. Using a rectifier and dc regulator for the 6.3V heater supply eliminates hum problems associated with traditional ac heater drives.

plexity for a given common supply psrr requirement. In this respect the differential pair is most useful and has the added bonus of reducing the number of coupling and decoupling capacitors required. This naturally leads to...

**Balanced working and cables**

Balanced working is commonly used in broadcast and recording studios to protect audio signals from external electromagnetic interference. It is particularly useful for low-level signals such as microphones.

A balanced source is simply one where each terminal of the source has balanced impedances to ground. Frequently, the only path to earth from the terminals is via stray capacitances, and the source is then floating. Connecting cables for balanced systems therefore have two signal wires or legs, and an overall screen to maintain this balance. The input stage of the following amplifier also has its stray impedances carefully balanced to ground and will either be a differential pair or a transformer.

When you immerse the connecting cable in an electromagnetic field, an identical noise current is induced into both wires. The series resistance of the cable is the same on each leg, and the shunt capacitances and resistances to ground are also equal, so the noise current develops a voltage of identical amplitude and phase on both legs at the amplifier input. This common mode signal is then rejected by the differential pair or transformer, whereas the wanted audio signal is differential mode and is amplified.

Typically, a moving coil cartridge produces approximately 200µV at 1kHz and 5cm/s, but before RIAA equalisation, the level at 50Hz is approximately 15dB lower at 36µV. Achieving the goal of inaudible hum on a signal at this level is not trivial. The cartridge is a balanced device, so why unbalance it?

You should immediately rewire the output cable of the pick-up arm to maintain this balance by discarding any coaxial cable. The connecting cable from arm base to preamplifier should be replaced by a twisted pair, with overall screen, for each channel.

A cable construction I use has twisted pair covered with a braid electrostatic screen. Both cables are then threaded down one overall braid screen. Braiding also hold the cables together and further aids screening, while a nylon braid is fitted over the top to prevent handling noise.

The braid should not have voids, so most antenna cables are unsuitable. Broadcast quality video cable or multicore umbilical cable, are both ideal sources of non-voided braid. Once the plastic outer sheath has been removed, the braid will easily concertina off the inner conductors.

A professional quality metal bodied 5-pin DIN or XLR plug is ideal for connecting this cable to the preamplifier, although the cable entry will usually need to be enlarged. Ideally, the screen should be connected to mains earth at the pick-up arm end, but this is not quite so critical in a balanced system.

Incidentally, within the arm tube, most pick-up arms twist all four thin, non-screened wires from the cartridge together, because this makes the wire easier to handle. Crosstalk between channels would be improved by twisting channels individually as they pass down the arm tube, but retaining the four wire twist required for low friction as the wires pass through the bearings to the output cable.


This form of rewiring is especially beneficial for moving coil cartridges and will help hum rejection even if the preamplifier is unbalanced.

**Basic preamplifier compromises**

If you really want to achieve a significant improvement on the basic preamplifier, you will need to look closely at the fundamental design and reconsider some of the compromises that were initially made.

- Intrinsic psrr was not maximised.
- Individual anode currents were set quite low in order to minimise total current consumption, so that the preamplifier could be powered from an associated power amplifier. This meant that  $g_m$  for each stage was low, and noise was not minimised.
- Metal film resistors were used in the anode load resulting in excess noise, although most of this was shunted by  $r_a$ . To eliminate excess

**Fig. 8. A fully-balanced preamplifier maximises supply rejection and reduces noise, but it is more dearer and more complex.**

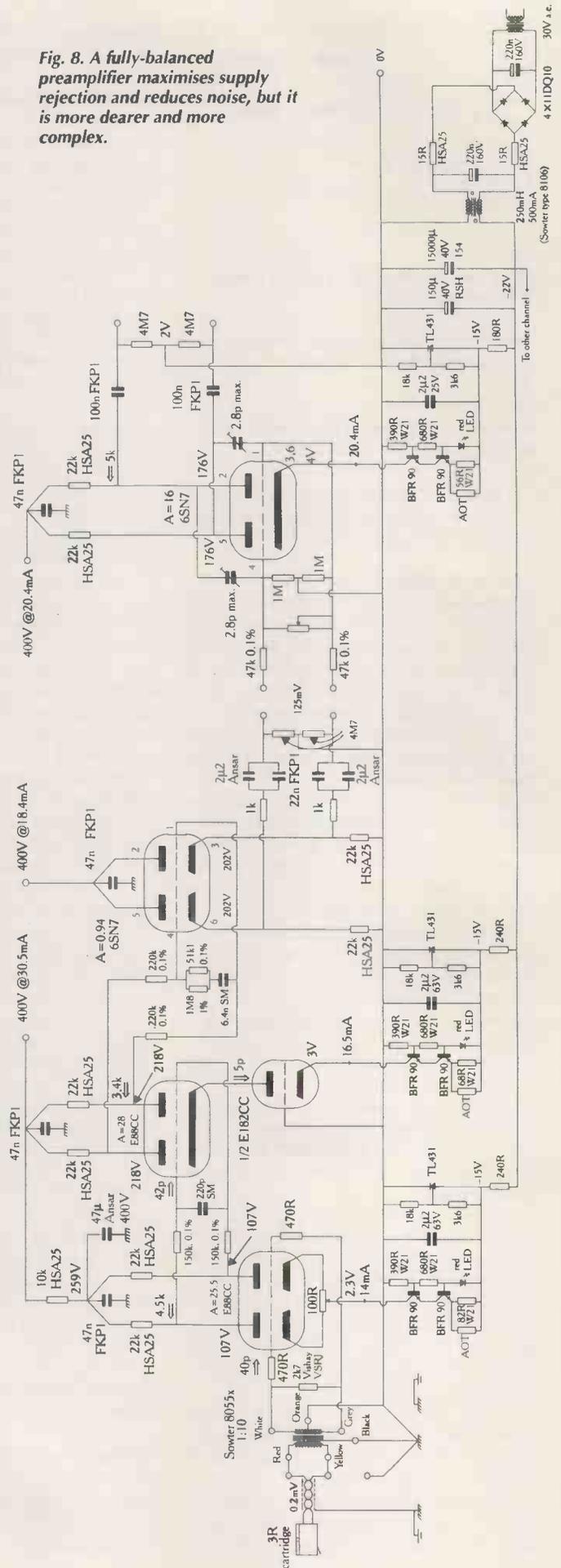

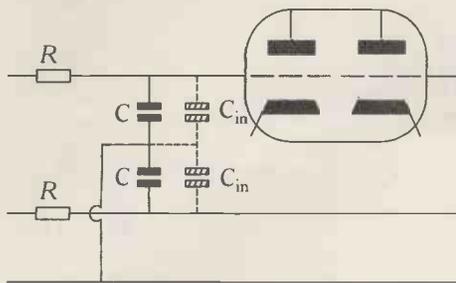


Fig. 9. Implementing the 75 $\mu$ s time constant in balanced mode.

noise, wirewound components should be used for any resistors with significant dc across them.

● Individual stages were kept simple, but linearity was therefore not optimum.

The balanced preamplifier seeks to address all of the above points but does not place such a high priority on simplicity or cost, Fig. 8.

### The input stage

In order to reap the full benefits of balanced working, a moving coil step-up transformer for 3 $\Omega$  cartridges was especially designed for this preamplifier by Sowter Transformers of Ipswich. Correctly terminated, the first batch of type 8055x had a frequency response that was flat  $\pm 0.1$ dB from 12Hz to 100kHz, while the high-frequency phase response was pure delay  $\pm 1^\circ$  to 50kHz.

The 8055x transformer also has an electrostatic screen between primary and secondary and its stray capacitances to ground have been balanced. This results in excellent rejection of common mode noise on the connecting wires from cartridge to preamplifier.

The first stage has a semiconductor constant current sink to enhance common mode rejection and the grid-leak arrangement is a little unusual. If you were to assume zero winding resistance for the input transformer, then a grid-leak connected to one valve would also serve as the grid-leak for the other, so only one resistor is required.

Since winding resistance is not zero, you move the single grid-leak to the centre tap of the transformer, which is a point of zero ac and dc potential. This assumes perfect transformer balance.

Any noise current passing through this resistor will develop a voltage that is applied equally to both inputs of the differential pair and will be rejected. If the resistor is large, then a larger noise voltage will be generated, and the input stage may no longer be able to reject it. This problem is solved by reducing the grid-leak resistor to 0 $\Omega$  and connecting the transformer centre tap directly to ground.

Because the circuit is dc coupled, it has become necessary to include a dc balance control which should be set to equalise the anode voltages of the second stage.

The resistors marked AOT, for adjust on test, in the cascode constant current sources will only need to be set once for correct anode

voltages, since they correct for individual variations in  $V_{be}$  and led voltage

### Second stage and 75 $\mu$ s time constant

In order to direct couple the first stage to the second, the cathode of the second stage must be at an elevated voltage. It seems foolish not to use a constant current sink in this position.

Initially, an E88CC triode constant current source was considered, but the calculated  $r_a$  of 200k $\Omega$  was thought to be insufficient, so an ECF80 pentode was substituted. This increased  $r_a$  to 10M $\Omega$ . However, the ECF80 was then being operated very close to its maximum rating. As mentioned before pentodes are noisy. The final design therefore uses half of an E182CC, configured as a hybrid triple cascode.

Because the second stage valve is directly coupled to the first, the second stage does not have grid-leak resistors. You therefore avoid the 1.6dB excess loss suffered in the basic preamplifier's 75 $\mu$ s network.

The 75 $\mu$ s time constant is achieved in a balanced fashion, with the shunt capacitor mounted directly onto the valve base with leads as short as possible in order to reduce stray capacitance. Similarly, the bodies of the series resistors are as close as possible to the valve pins. This means that they also perform the function of grid stopper resistors. The best way to understand the equalisation is to redraw the circuit as two unbalanced networks, Fig. 9.

The values for R and C are calculated exactly as before. However, observe that you could break the centre tap of our added capacitors away from ground, which would leave two capacitors in series. These can be replaced with a single capacitor of half the value. A noisy ground is now less able to inject noise into the audio signal.

An additional advantage is that there is now no dc across the capacitor, so a lower voltage rating may be used if desired. For this design it was convenient to use a series resistor of 150k $\Omega$ , thus needing a 220pF capacitor between the grids to set 75 $\mu$ s.

### Pairing 3180 and 318 $\mu$ s

Since this pairing is achieved in a balanced fashion, the value of the capacitor is halved, and it has virtually no dc across it, which makes it much easier to find close tolerance components.

Because it was desirable to use a balanced 3180/318 $\mu$ s pairing, twin cathode followers were required, resulting in a balanced output from the RIAA stage. Most power amplifiers are push-pull and therefore include a phase-splitter. In the light of this, why not keep the signal balanced all the way into the power amplifier, and discard the problematical phase splitter?

### Volume control and output stage

The volume control now has to be balanced, using matched fixed series resistors and a variable shunt to form a potential divider. This has the disadvantage of a high output resistance

when set for a sensible input resistance and will cause hf loss if ignored.

The output stage uses a 6SN7 configured to give  $A_v$  of 16. Capacitance  $C_{ag}$  is 4pF for the 6SN7, so the input capacitance  $C_{in}$  equals 68pF, not including any allowance for strays. The series resistors have been set to 49.9k $\Omega$ , giving a 47kHz hf cut-off, which is too low. To meet the 0.1dB loss at 20kHz criterion, you would need a  $C_{in}$  of less than 19pF. Alternatively, you would need to reduce the series resistors to 13.5k $\Omega$ , increasing the loading on the disc stage. One solution is to partially neutralise the  $C_{ag}$  capacitance by adding capacitance from each grid to the opposite anode using small trimmer capacitors.

Note that neutralisation is positive feedback and if it is not applied with care, the stage will turn into an oscillator. For the range 1 to 3.5pF, PTFE trimmer capacitors are readily available. If one of these trimmers is set with its vanes two thirds meshed, a capacitance of approximately 2.4pF results. This is sufficient to reduce input capacitance to an acceptable value.

Ideally, a square wave should be applied between ground and one input of the volume control. The other input should be grounded and the second capacitor adjusted until the output waveshapes are matched as viewed on an oscilloscope. Layout is crucial here.

An alternative to neutralisation would be to revert to using an ECC82, which has an intrinsically lower  $C_{ag}$  and a slightly lower gain, thus reducing  $C_{in}$ . Whichever course is taken, the volume control must be as close as possible to the valve in order to minimise external stray capacitances. Unscreened wires must be used.

### Constant current sinking

Although a 'ring of two' circuit could have been used as a sink for the first stage, each transistor would then have been operated at a very low voltage. But operating transistors at a low voltage is undesirable. It makes the circuit more susceptible to rf overload, due to the depletion region within the transistor being narrowed. This increases output capacitance. These factors demand the use of a subsidiary negative supply. A superior cascode constant current sink using rf transistors can then be used, making a virtue out of a necessity.

Noise on the subsidiary supply must be minimised, so a choke input supply was chosen. Potentially, the reactance of the choke and the 10,000 $\mu$ F smoothing capacitor form a resonant circuit. This resonance is critically damped by adding the 5.6 $\Omega$  series resistor to the choke and transformer resistances.

The minimum current requirement of the choke is neatly solved by the use of a TL431 shunt regulator for each stage. This ensures that a constant current is drawn – even when the ht is switched off. ■

### Further reading

Wright, Allen. 'The tube pre-amp cookbook' 1994

Morrison, J. C. 'Siren song: A phono preamplifier for hedonists.' Sound Practices, 1993, Number 3, P3 - 9; Number 4, P6.

# There are less drastic ways to cut your costs.



## Buying from this catalogue is one.

If you need to purchase quality products from a catalogue, with guaranteed next day delivery, but don't want to spend a fortune, you can always take drastic measures. However, there is a simpler way. CPC.

**You get a choice of 39,000 quality products from over 300 leading manufacturers.**

At CPC we only stock quality products from quality manufacturers. All the biggest equipment names are represented in our catalogue including TDK, 3M, Duracell, MK, Weller, Sony, CK etc.

**Over 27,000 companies get a better deal with us.**

And the list is growing by the day. From our inception in 1967, we have enjoyed year on year growth, seeing our client base of 2,000 in 1986 boosted by a further 25,000 companies who have switched to CPC - and stayed!

**The catalogue couldn't be easier to use.**

Whether you are a service engineer, OEM, school or manufacturer, whatever your component needs, you'll find them all listed in our easy to use index and cross reference section. Audio products, batteries, computer products, hardware, motor control, semiconductors, surface mount, tools and original manufacturers spares are just some of the sections included.

**CIRCLE NO. 113 ON REPLY CARD**

Open YOUR account today,  
tel 01772 654455 or fax 01772 654466

**NEW**  
Catalogue  
is now available



**10,000 NEW PRODUCTS**

**NEW SECTIONS INCLUDING**  
Datacomms & Networking  
PCB Prototyping  
Optoelectronics  
Surface Mount  
Motor Control



**Ordering couldn't be simpler.**

Our sales office is open Monday to Saturday taking orders by phone, fax and post.

**Diamond Service means same day despatch is guaranteed.**

Representing the ultimate in customer service, CPC's Diamond Service ensures all orders received before 5.30pm, are despatched the same day - guaranteed.

**How to open an account today.**

Just pick up the phone, give us the details and the job's done. And once you're on our database we'll send you bulletins on all the latest products and great offers from CPC, four times a month.

**Free catalogue, free carriage.**

Once you've opened an account, we will send you a complimentary 1,700 page catalogue and with all orders over £30 carriage is absolutely free!

So, if all you want to cut is costs, call us today.

CPC's 50,000 square foot headquarters in Preston

Our friendly staff are here to help you.



State-of-the-art storage and handling facilities

CPC. Faraday Drive,  
Fulwood, Preston, Lancashire.

# ISSCC

## the highlights

Roy Rubenstein reports on the world's top electronics innovation event – the International Solid State Circuits Conference.

If there is one event in the world's electronics calendar worth attending it is the International Solid State Circuits Conference – ISSCC – held in San Francisco. It is hard to imagine where else one could gain such a comprehensive overview of the latest analogue and digital circuit techniques and devices.

'Systems on a chip' was this year's conference theme. The opening session reviewed circuit design in the areas of multimedia, electronic imaging and TVs.

The keynote speech, given by NEC's vice president for semiconductors, Dr Hajime Sasaki, addressed multimedia. That much-touted phrase, multimedia, embraces all the emerging applications that manipulate text, graphics and



video once encapsulated as ones and zeros.

Personal computers form the present, most common embodiment of multimedia.

Sasaki's belief is that multimedia will come to predominate in home and work environments.

His presentation outlined the technology road map of the likely device that will be processing multimedia in the year 2010. His 'multimedia complex' device integrates and extends, common components found in present day PCs, namely the microprocessor, memory, three dimensional graphics accelerator and moving-image (such as video) processing circuitry.

While such a device may appear an obvious development, what is perhaps less so is the technical challenges its accomplishment presents.

### All-time top ten circuits

One of the traditions of the ISSCC is the evening session where a panel tackle such weighty issues as 'Is Electronic Imaging at a Watershed?' and 'What is the Best Memory Type for Graphics?'

This year, by far the best attended session – and certainly the most entertaining – was one that set out to name the ten most significant analogue circuits and circuit techniques. The criteria used included the need to have influenced other circuits and still be relevant today.

The panelists, which included Minoru Nagata, director of Hitachi's Central Research Laboratory and Bob Pease, the analogue guru at National Semiconductor, each selected three. The audience also contributed suggestions and the overall list were then voted on.

The resulting analogue top ten is:

1. Bandgap reference/regulator
2. Differential pair
3. Translinear circuits
4. Current mirror/source
5. Switch capacitor circuits
6. Pole splitting compensation
7. Cascode
8. Negative feedback amplifier
9. The power cord!
10. Integrator

### 0.07µm geometries by the year 2010

First, Sasaki projected present trends for device parameters such as integration densities, processing performance and power consumption, to gauge the likely system-device in the year 2010.

By then CMOS feature size will be 0.07µm, allowing hundreds of millions of transistors to be integrated on a single integrated circuit. The most advanced process technologies used today have 0.35µm feature sizes, achieving transistor densities up to ten million.

The intricacies involved in designing a 500 million transistor device is expected to be hundreds of times more complicated than that of present day microprocessors.

Looking next at processing performance, Sasaki observed that microprocessors have achieved an astonishing thousandfold improvement since 1980.

During that time, microprocessors have evolved instructions which when executed perform more than a single operation. Hence the emergence of microprocessor measures such as the millions of operations per second, or Mops, in addition to the traditional instructions per second metric, or Mips.

### MIPS – slower growth

Sasaki believes that the astonishing Mips progress achieved to date will not continue since the instruction level parallelism that can be extracted from typical software code is rapidly being approached. He expects that in the next 15

years, an improvement of only a factor of 20 can be expected.

However, he sees no reason why the number of operations executed cannot progress at the staggering pace seen to date. Such progress will be achieved as multimedia function blocks are coupled to the main processing unit.

Extrapolating the processing trends, the multimedia complex can be expected to achieve 100 billion instructions/s and 1000 billion operations/s. To better gauge such a figure, Texas Instruments' most powerful multimedia processor, the TMS320C80, can attain a peak performance of 4 billion operations/s.

In tum, to sustain such processing rates the memory will need to supply the processing unit with tens of thousands of megabytes per second. Such transfer rates will not be possible between adjacent ICs, observed Sasaki, rather the memory will have to be integrated on-chip.

Yet a further challenge to be met is having the complex consume only 1W, necessary if it is to be used in portable battery-powered equipment.

Even if progress in low power techniques is maintained until 2010, a further order of magnitude reduction has to be found if the stringent 1W target is to met.

Interestingly, the solutions Sasaki outlined to attain such a multimedia complex, including integrating ample on-chip store and evolving present low power circuit techniques, were already in evidence in present papers at this year's ISSCC. Meeting the target specification will not be easy. As Sasaki puts it: "Developing the multimedia complex is a challenging target. We have so many things to do."

### Variable voltage threshold techniques

CMOS has always been seen as a low power process technology. The success of VLSI, with the integration of millions of transistors on a device, has made CMOS hotter under its ceramic collar than it would like to be.

The most common approach to tackle device power consumption is by reducing its operating voltage. A recent example is the 433MHz Alpha processor from Digital which operates its processor core at 2V even though the device and its I/O is supplied with 3.3V. And it still consumes 23W.

With a reduced supply voltage comes a corresponding reduction in the voltage threshold,  $V_{th}$ . For CMOS,  $V_{th}$  is the voltage at which the device changes state.

Reducing  $V_{th}$  of a transistor increases its speed. However, the downside is the exponential increase in leakage current, and hence standby power consumption.

At ISSCC, a number of papers highlighted approaches that vary  $V_{th}$ . All use a reduced  $V_{th}$  when high performance is required and a high  $V_{th}$  in standby mode, when reducing leakage current is a primary concern.

One ISSCC example is a processor developed by Nippon Telegraph and Telephone (NTT) for mobile phones. The device is normally in one of two modes: strenuously active when digital encoding and decoding speech or, more commonly, in a sedate state awaiting a call.

The processor features a DSP core and an embedded processor. The DSP core is supplied with 1.1V and is implemented in a low threshold voltage CMOS ( $V_{th} = 0.25V$ ), whereas the embedded processor is implemented using a higher threshold one.

In the wait mode the DSP is inactive; a high voltage MOS-FET isolates it from the supply rail, drastically reducing its

leakage current. Here the embedded processor takes over.

Implemented using a higher threshold logic, the embedded processor has a corresponding lower standby current. Moreover, having less to do, it operates at a lower frequency, further saving power.

According to NTT, simply reducing the voltage from 3.3V to 1V reduces the device's energy consumption by one third. Energy consumed being the appropriate measure for the handset. However, employing a multi-threshold logic scheme, energy consumption is reduced to one tenth overall.

### Cellular neural network

The world may have gone digital but for applications where high accuracy is not a requirement, an analogue approach can win hands down in terms of speed and power consumption. Moreover if implemented in standard CMOS technology, any requirement to integrate digital circuitry becomes straightforward.

The Katholieke University of Leuven, Belgium has adopted such an approach for telecommunications and analogue signal processing. Taking a cue from biological systems, it has produced a simple multi-cell analogue array suited to image manipulation and sensor data processing for applications such as robot arm control.


The device consist of a 20-by-20 array of simple analogue cells that implements a cellular neural network. Each cell has an input, internal and output node, and is linked to its four nearest neighbours. A set of templates determine the weightings of the signals exchanged between cells. These, coupled with the input data, determine the state of the neural network once processing completes.

The University has developed a library of templates that can be used to program the device to perform a range of applications.

The cells operate in parallel and continuously in time. Moreover, being analogue, the cell circuits work at the full technology bandwidth ( $f_t$ ).


Processing time is measured in time constants – multiples

*Cellular neural network array. The analogue parallel architecture comprises an array of processing cells arranged in a 20 by 20 matrix. All cells execute in parallel and in continuous time. The device can perform such tasks as edge detection, hole filling and connected component detection.*

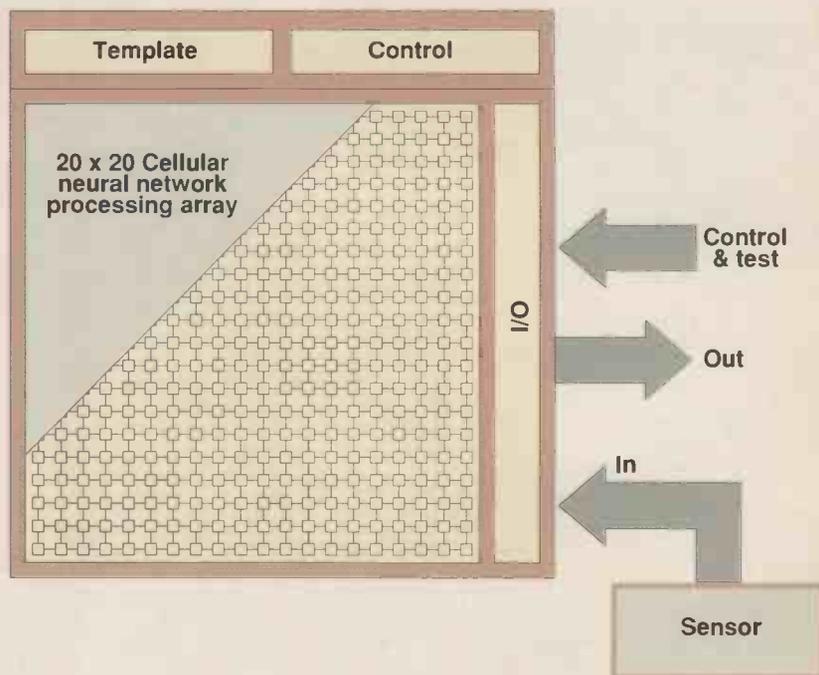

of 4.8µs. The typical execution time of a non-propagating template is 9.6µs; for the worst case information propagating template it is 145µs.

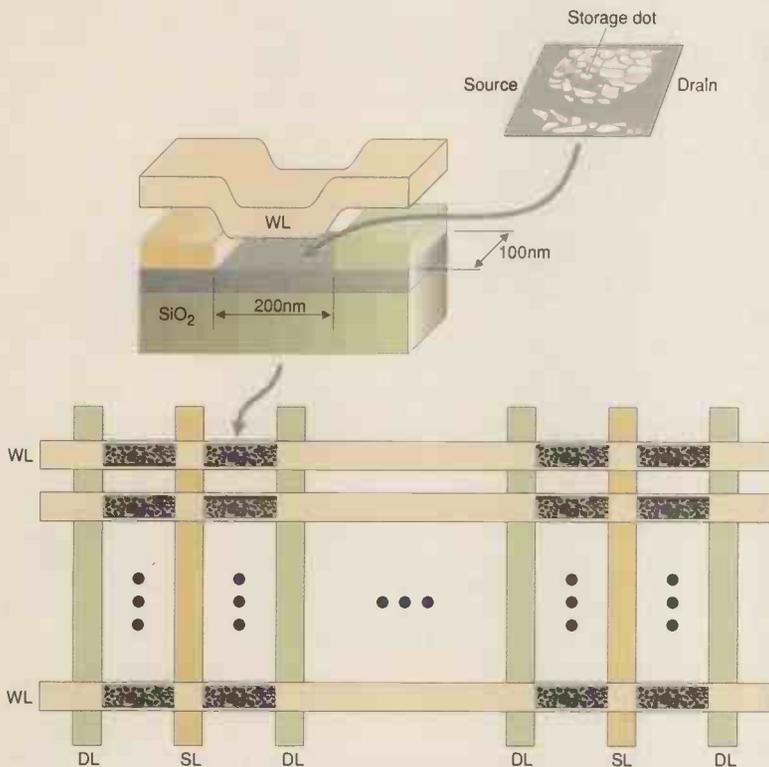The device's i/o circuitry can be clocked at 500KHz,



Single electron memory, proposed by Hitachi, promises terabit storage on one chip. It incorporates a 3nm ultra-thin-film transistor exploiting the Coulomb blockade effect.

enabling the device to process up to 25 image frames/s.

While stressing that a direct comparison with a digital signal processor is not straightforward, the University nonetheless believes the array processor requires up to twenty times less energy (power-delay product) for a given computation.

Single electron memory cells

The highlight of last year's ISSCC was the emergence of 1Gigabit dynamic rams from Hitachi and NEC. This year Hitachi gave a glimpse of a development which promises storage densities one thousand times greater using single electron memory, or SEM.

Single electron memory has received considerable attention in recent years. First demonstrated at very low temperatures, room temperature has now been attained. The benefit of SEM is its ability to control a small number of electrons, promising reduced power consumption per transistor coupled with significantly greater integration levels due to each transistor's reduced size.

The SEM device uses a 3nm ultra thin-film transistor which exploits the Coulomb blockade effect *Electronics World*, March 1996, p185. The effect works by confining a pool of electrons within a small region such that the stored charge energy is greater than the thermal energy of an external electron. Information is stored by trapping one or more electrons in the pocket and manifests itself in a constricted current.

Hitachi's accomplishment is to be the first to integrate a number of SEM cells to produce an 8-by-8bit array. Moreover, by producing a working device, Hitachi has identified the obstacles to be overcome if volume manufacturing is to occur.

Hitachi's SEM has a 10µs write/erase time. This is faster than flash memory since the number of electrons to be stored or erased is a paltry five compared to 100,000 for flash.

The device's shortfalls include a retention time of between an hour and a day, unacceptably short for nonvolatile store. ■

120MHz a-to-d converter in c-mos

Converting a complex envelope signal from rf to baseband, forming in-phase *I* and quadrature *Q* components, is a common requirement for radar and communications applications.

The traditional approach uses cosine and sine heterodynes to separate the *I* and *Q* components before being digitised

by matched a-to-d converters, Figure 1.

At ISSCC Ericsson and Linköping University detailed a 120Msamples/s a-to-d converter that digitises the baseband components to an accuracy of 10-bits.

The device uses a dual filter approach to separate the components, Figure 2. According to Linköping University,

implementing the filters using closely matched coefficient values allows its execution within the sampling circuitry of the converter. The consequence is a saving in circuit complexity and power in that the a-to-d conversion is performed at a more leisurely 2MHz rather than at 120MHz.

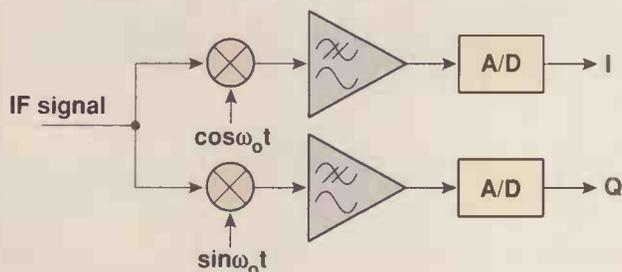


Fig. 1. Classical method for in-phase and quadrature detection. Sine and cosine heterodynes access the complex envelope signal before each arm is low-pass filtered and digitised.


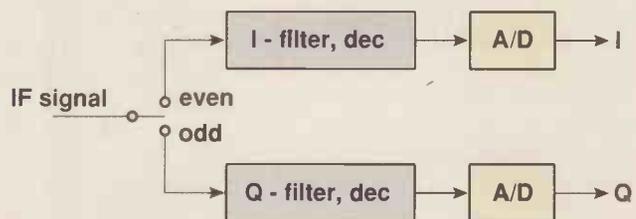


Fig. 2. New a-to-d converter samples at four times the intermediate frequency, undertakes analogue filtering and decimation before digitising the signals at baseband.
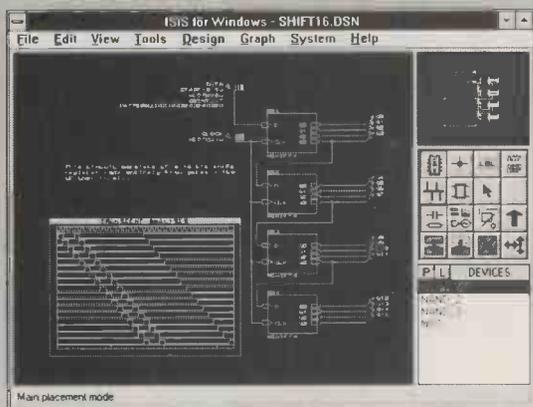
# PROTEUS


*New for Windows 3.1, 95 & NT*

*The Complete Electronics Design System - Now With RIP-UP & RETRY!*



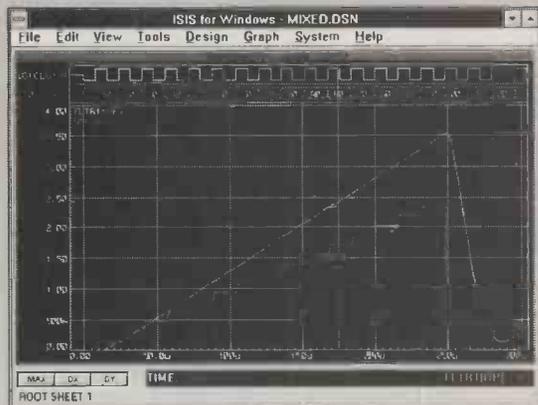
## Schematic Capture

- Easy to Use Graphical Interface under both DOS and Windows.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and PCB design.


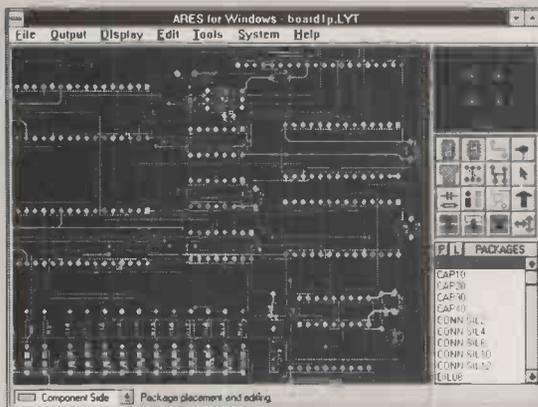
## Simulation

- Non-Linear & Linear Analogue Simulation.
- Event driven Digital Simulation with modelling language.
- Partitioned simulation of large designs with multiple analogue & digital sections.
- Graphs displayed directly on the schematic.



## PCB Design

- 32 bit high resolution database.
- Multi-Layer and SMT support.
- Full DRC and Connectivity Checking.
- RIP-UP & RETRY Autorouter.
- Shape based gridless power planes.
- Output to printers, plotters, Postscript, Gerber, DXF and clipboard.
- Gerber and DXF Import capability.

**Labcenter**  
**Electronics**

*Write, phone or fax for your free demo disk, or ask about our full evaluation kit.*  
**Tel: 01756 753440. Fax: 01756 752857.**  
**53-55 Main St, Grassington. BD23 5AA.**

Proteus runs as a 32 bit application under both DOS and Windows (3.1, 95 and NT).  
Prices start from £470 ex VAT; full system costs £1645 for DOS, £1875 for Windows. Call for upgrade pricing and/or information about our budget and educational products. All manufacturers' trademarks acknowledged.

**CIRCLE NO. 114 ON REPLY CARD**

# Relaying transmission line principles

Bill Russel demonstrates how rectangular pulses and an artificial delay line simplify the explanation of how transmission lines work.

**M**y previous article outlined a range of simple demonstrative measurements that can be made on an  $8\mu\text{s}$ ,  $8\text{k}\Omega$  artificial line fed from a sine-wave source.

This article examines the effect of applying rectangular pulses to a similar line, using basic test equipment. I constructed a simple battery-powered pulse generator based on a *74HC14* hex schmitt trigger. Since the current drain is only a few milliamps, several hours use can be obtained after each charge.

Layout shown in the upper circuit on page 214 allows for three values of source resistance. The values used give a pulse width of about  $2.5\mu\text{s}$  at a repetition frequency of around  $10\text{kHz}$ .

With the source resistance set at  $8\text{k}\Omega$ , the pulse delivered to a matched line is  $3\text{V}$ . Measurements are made with channel 1 on the input and channel 2 on the output, or one of the line taps.

Measurement possibilities of this set-up well exceed the range required for a normal laboratory session. As a result, the examples shown here are limited to recording waveforms at the output or at tap 5. Principles that can be established are as follows


**$8\text{k}\Omega$  source with  $8\text{k}\Omega$  terminal resistance.** Referring to Fig. 1, a rectangular pulse of  $3\text{V}$  amplitude travels progressively down the line at a speed of  $0.84\mu\text{s}$  per section with little attenuation but some distortion due to the lumped nature of the line. It is accompanied by a current pulse of amplitude  $3\text{V}/8\text{k}\Omega$ , which is  $0.375\text{mA}$ .

Some evidence of small reflection reaching the input after  $16.8\mu\text{s}$ , due to the reactive nature of  $Z_0$ .


**$8\text{k}\Omega$  source with line open circuit.** In Fig. 2, complete reflection of the incident  $3\text{V}$  pulse takes place at the open-circuit, producing a  $6\text{V}$  pulse. The reflected  $3\text{V}$  pulse reaches the input  $8.4\mu\text{s}$  later.

Inspection of outputs at taps 1 to 9 shows incident pulses arriving later and reflected pulses arriving earlier until they merge into the  $6\text{V}$  pulse at the termination. Note that the display shows only the voltage-time waveform at a particular point in the line, the horizontal axis being time delay in microseconds and not distance along the line. More on this later.

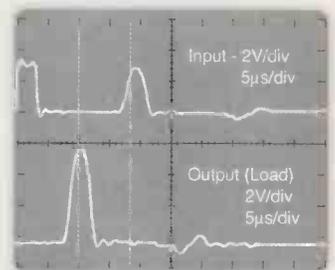**$8\text{k}\Omega$  source with line shorted.** In Fig. 3, the incident  $3\text{V}$  pulse is completely reflected at the short circuit with reversed polarity. This produces the required zero at the output, and appears at the input  $8.4\mu\text{s}$  later.




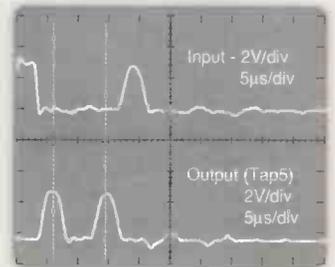Data position 0 div  
dTime 8.40µs  
1/dT 119kHz




Data position 0 div  
dTime 8.40µs  
1/dT 119kHz

*Fig. 2. Input shows incident 3V pulse, together with a pulse of the same polarity and almost the same amplitude, reflected from the open-circuit termination after  $16.8\mu\text{s}$ . Output shows a pulse of about 6V amplitude, due to the combination of more or less identical 3V incident and reflected at the termination after  $8.4\mu\text{s}$ . Output at tap 5 shows both the 3V incident pulse after  $4.2\mu\text{s}$ , and an almost identical pulse reflected from the termination after  $8.4+4.2=12.6\mu\text{s}$ . Inspection of outputs at taps 6 to 9 shows incident pulse arriving later and reflected pulse arriving earlier until they merge into the 6V resultant at the termination.*

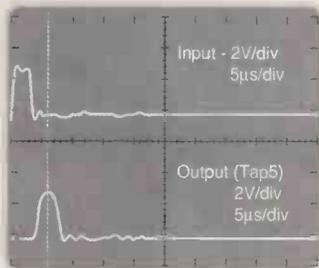


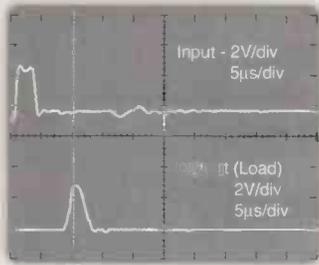Data position 0 div  
dTime 4.20µs  
1/dT 238kHz




Data position 0 div  
dTime 8.40µs  
1/dT 119kHz

*Fig. 1. The 3V input pulse appears at the output after  $8.4\mu\text{s}$ , with some distortion due the lumped nature of the line, and evidence of a minor reflection at the input after  $16.8\mu\text{s}$ . Output at tap 5 shows the 3V incident pulse arriving after  $4.2\mu\text{s}$ .*

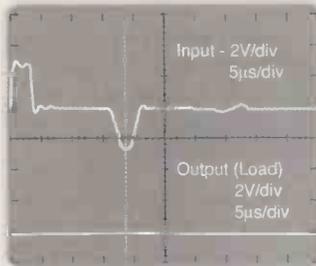


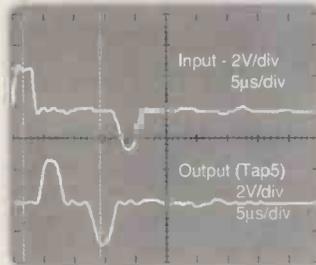Data position 0 div  
dTime 16.80µs  
1/dT 59.5kHz




Data position 0 div  
dTime 12.6µs  
1/dT 79.3kHz

**Fig. 3.** Input shows inversion of the incident 3V pulse which is reflected at the output and appears at the input after 16.8µs. Output at the short is of course zero, but this can be represented as the combination of a 3V incident pulse with its inverted reflection. This is illustrated by the output at tap 5, which has a 3V incident pulse arriving after 4.2µs together with an inverted 3V pulse reflected from the termination after 12.6µs.

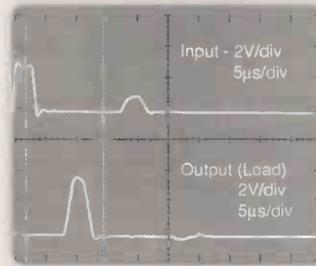

Data position 0 div

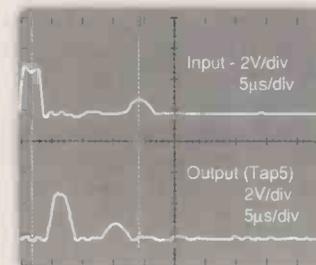

Data position 0 div

**Fig. 4.** Reflected pulse of amplitude 1V appears at the input after 16.8µs. Incident 3V and reflected 1V pulses combined results in a 4V pulse at the termination. Both incident and reflected pulses are resolved separately in output at tap 5.

Outputs at the tapping points resolve both incident and reversed reflected pulses. The results above show almost complete reflection of an incident voltage pulse at an open or short circuit. They also establish the sign or polarity of reflected pulses.

The following measurements of the magnitude of pulses reflected from loads of  $2Z_0$  and  $Z_0/2$  can be used to introduce the concept of reflection coefficient, and to deduce its value for any given mismatch ratio.

**8kΩ source, 16kΩ load.** Figure 4 shows the 2:1 mismatch at the load end causes the 3V incident pulse to be reflected as a pulse of 1V with the same polarity, producing a 4V pulse at the load.

Output at tap 5 shows incident 3V and 1V reflected pulses. These results indicate that a third of the incident voltage pulse is reflected without change of polarity at a mismatch ratio  $m$  of 2:1. This can be shown to agree with the simple formula,

$$\text{Reflection coefficient} = \frac{m - 1}{m + 1}$$

So far, no attention has been paid to the current pulses implied by the incident voltage pulse on an 8kΩ line. This is because the measurement set up does not allow for their detection. Nevertheless a fair amount of information can be inferred from the known facts.

The current pulse which must accompany the incident voltage pulse of 3V is  $3V/8k\Omega$ , which is 3/8mA. At the termination of 16kΩ, the voltage pulse rises to a combination of 3V incident plus 1V reflected without change in polarity giving a 4V resultant pulse. Hence at the termination the resultant current must be  $4V/16k\Omega$ , which is 1/4mA.

It would seem reasonable to deduce that, at the termination, a third of the incident current pulse is reflected and inverted to produce a resultant terminal current pulse of  $3/8mA - 1/8mA$ , producing the required 1/4mA.


**8kΩ source, 4kΩ load.** Figure 5 demonstrates how measurements of input and outputs of a line with a 1:2 mismatch ratio  $m$  show a voltage reflection coefficient of 1/3 with reversed polarity. By inference it can be deduced that the current reflection coefficient is also 1/3 but with no change in polarity.

The results obtained can be used to establish some basic rules for a simple treatment of reflections at any resistive termination. As for the current waveforms, the inclusion of a 100Ω current sensing resistor in the return line of both input and termination allows a lot more information to be obtained. However, it is doubtful whether many students would be capable of appreciating the implication of much of this additional data – particularly in the cases where line is mismatched at both input and output ends.


Figures 6, 7 show the voltage waveforms obtained for two of these conditions, and are included with brief comments as examples of situations which would normally be avoided.

**4kΩ source mismatch, no load.** The 4kΩ source shown in Fig. 6 now delivers a travelling incident pulse of 4V to the line. During the transient phase, this pulse is completely reflected at

**Fig. 6.** Mismatch at the source results in the incident pulse delivered to the input being about 4V rather than the 3V with a matched source. At the termination the incident pulse is completely reflected producing the pulse of almost 8V at the open-circuit after 8.4µs, and arriving at the input after 16.8µs. Simplified arithmetic of the mismatched input suggests that a third of the reflected pulse will be absorbed – increasing the input amplitude to about 5.3V and two-thirds, or 2.6V, will be inverted and reflected back to the output, arriving after a further 8.4µs. Output waveform shows the increased amplitude at the mismatched input, the large pulse at the open circuit, the 2.6V pulse reflected from the input, plus the first of a series of reflections from output and input.

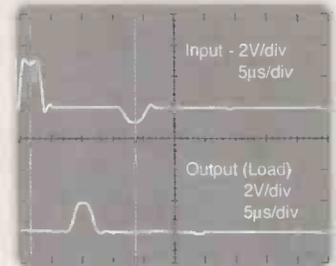


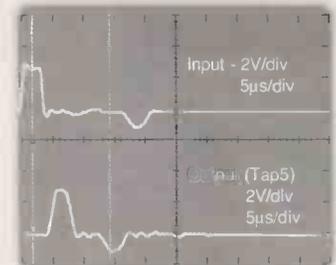Data position 0 div  
dTime 16.80µs  
1/dT 59.4kHz




Data position 0 div  
dTime 12.6µs  
1/dT 79.2kHz


**Fig. 5.** Reflected 1V pulse, inverted, appears at the input after 16.8µs. Combination of 3V incident and 1V inverted reflected pulses result in a pulse of 2V at the termination. Both incident and reflected pulses appear on the output at tap 5.

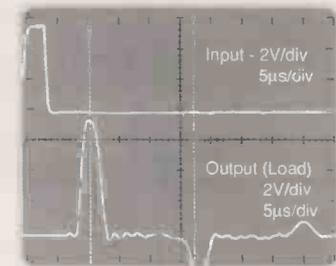

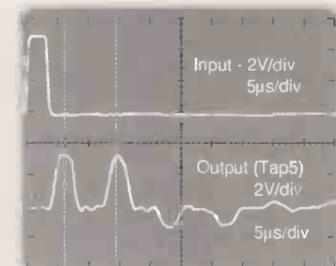Data position 0 div  
dTime 16.80µs  
1/dT 59.2kHz



Data position 0 div  
dTime 8.4µs  
1/dT 119kHz

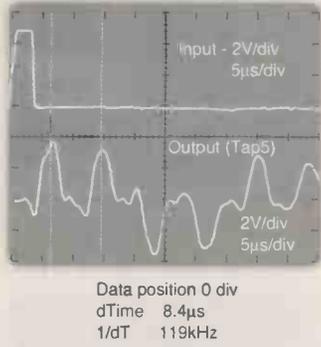

**Fig. 7. Worst case condition, where pulses reaching the open circuit are reflected as is, and those reaching the input suffer complete reflection and inversion. Output at tap 5 shows part the series of multiple reflections which then takes place.**

the open-circuit producing an 8V pulse, and the reflected 4V pulse arrives at the mismatched input after 16.8µs.

Waveforms of Fig. 6 are steady state conditions and show no sign of a reflected pulse at the input. Instead, the input shows a final value of input voltage of about 5.3V, plus an inverted pulse of about 2.6V at the output after reflection from the input.

This suggests that when the transient 4V pulse reaches the input mismatch, a third is absorbed increasing the input pulse to 5.3V, and two thirds, or 2.6V, is inverted and reflected back to the output.

**Line mismatched at source.** In this case, there is a direct connection to the pulse generator via a 50Ω resistor and the load is open circuit, Fig. 7.

Under worst-case conditions, pulses reaching the open-circuit are completely reflected as is. Reflected pulses reaching the input suffer almost complete reflection and inversion. Little, or none, of the pulse energy is absorbed by the generator, or load. The result is that a series of multiple reflections and inversions take place at the generator, accompanied by reflections without inversion at the load. Figure 7 shows part of this series.

**Extending the idea**

Explanatory comments on the above measurements assume a lossless line, and draw on the simple arithmetic of the dc equivalent circuit of the generator, line and load. However, the interest generated encourages many to tackle more rigorous analyses.

For those of you requiring merely a simple introduction to the principles involved, a selection of the more basic measurements should suffice. I have given some thought to the possibility of producing a display in which the horizontal axis represents the voltage at each successive line tap and hence distance along the line.

This problem could be solved by a computer simulation program. But the positive reaction of students who undertook these measurements on an actual line suggested that a hardware solution would be well received.

The main requirement for such a display is that the amplitude of the voltage at the successive taps should be sampled periodically. These voltages should be displayed as a vertical deflection on the oscilloscope. For rectangular dc pulses, the sampled output can be passed direct to the oscilloscope.

In order to cope with dc pulses of both polarities, the sampling device must be operated in the analogue mode.

A prototype circuit along the lines of Fig. 8, uses a 4067 analogue multiplex/demultiplexer, driven by a 4029 counter. A 2Hz clock is provided by a 40106 hex schmitt trigger. This device also provides a clock buffer and inverter for the terminal-count output to preset the counter to state 4.

The counter and hence the demultiplexer cycles continuously from states 4 to 14, giving 11 sampled lines. These lines are connected to the artificial line input and the 10 taps.

Channel 1 of the oscilloscope connects to the line input for triggering purposes only. The common output of the 4067 is simply connected to channel 2. The display is really a montage of the voltage time waveforms at a particular tap, updated at half-second intervals to the adjacent tap. It produces the illusion of incident pulses moving from left to right, and reflected pulses moving from right to left.

Where pulses meet, reinforcement or cancellation takes place depending of course on relative amplitude and polarity. The system is operated from a dual 7.2V supply as shown. As a result, it imposes a limit of less than 7.2V peak on the sampled input. This is ample to accommodate all waveforms shown in this article.


Used with a large display oscilloscope, a generator and an artificial line modified so that source and terminating resistors can be altered quickly by switches, this simplified display has proved surprisingly effective in summarising the working principles involved.

**Further reading**

Millman & Taub, *Pulse and Digital Circuits*, Chap. 10.

**Oops...**

In last month's article please note the following corrections: the caption for Fig. 4. refers to the plots of Fig. 6, the caption for Fig. 5 refers to Fig. 4 and the caption for Fig. 6 refers to Fig. 4. In Fig. 11, input current is 0.5mA, not 1mA. Sorry.

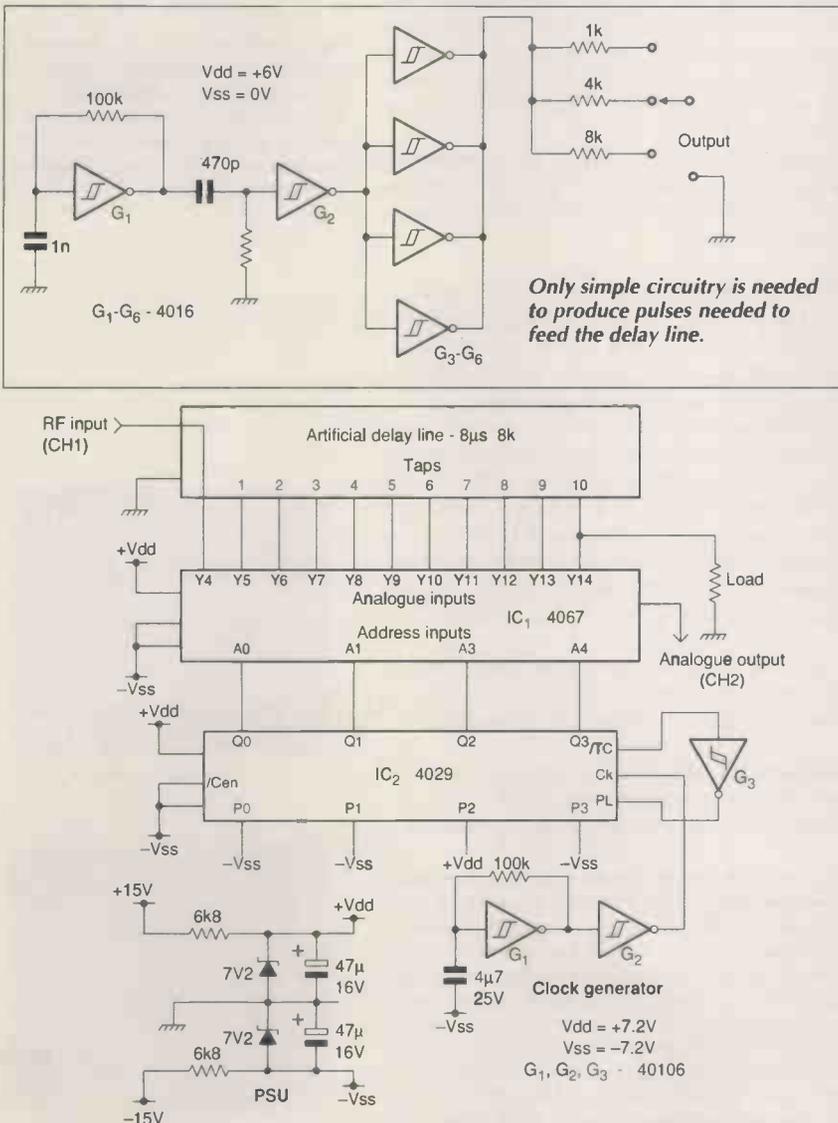

**Fig. 8. Adding such a display interface to the delay line allows successive taps to be sampled periodically and displayed as vertical deflections on an oscilloscope.**

# MIXED-MODE SIMULATION. THE POWER OF VERSION 4.

New  
Version 4

## Analog, Digital & Mixed Circuits


Electronics Workbench® Version 4 is a fully integrated schematic capture, simulator and graphical waveform generator. It is simple to mix analog and digital parts in any combination.

## Design and Verify Circuits... Fast!

Electronics Workbench's simple, direct interface helps you build circuits in a fraction of the time. Try 'what if' scenarios and fine tune your designs painlessly.

## Electronics Workbench

The electronics lab in a computer™

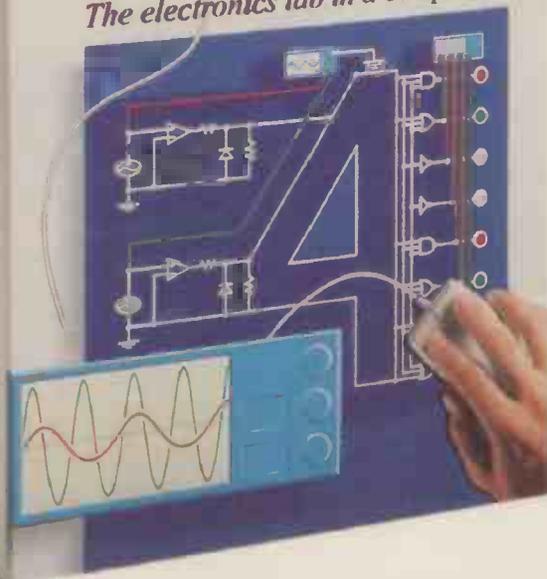

## More Power

Simulate bigger and more complex circuits. Faster. On average, Electronics Workbench Version 4 is more than 5 times faster than Version 3.

## More Parts

Multiple parts bins contain over twice the components of Version 3.


## More Models

Over 350 real world analog and digital models are included free with Electronics Workbench. And, if you need more, an additional 2,000 models are available.
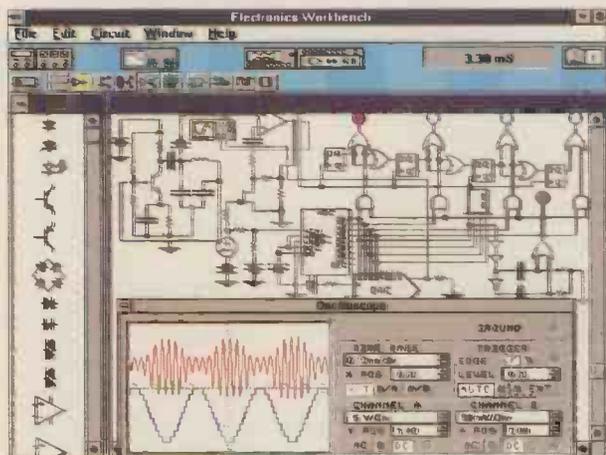
## Incredibly Powerful. Incredibly Affordable.

If you need mixed-mode power at a price you can afford, take a look at this simulator and graphical waveform generator that mixes analog and digital with ease.

With over 20,000 users world-wide, Electronics Workbench has already been tried, tested and accepted as an invaluable tool to design and verify analog and digital circuits. With Version 4 true mixed-mode simulation is now a reality with incredible simplicity.



True mixed-mode simulation: Simultaneous AM transmission, digitization and pulse-code modulation of a signal.

## Electronics Workbench™

The electronics lab in a computer™

Order Now! Just £199\*

44-(0)1203-233-216

**RM** Robinson Marshall (Europe) Plc

Nadella Building, Progress Close,  
Leofric Business Park,  
Coventry, Warwickshire CV3 2TF  
Fax: 44 (0)1203 233-210

E-mail: [rme@cityscape.co.uk](mailto:rme@cityscape.co.uk)

Shipping charges UK £5.99. All prices are plus VAT.  
All trade marks are the property of their respective owners.  
Electronics Workbench is a trademark of Interactive Image Technologies Ltd., Toronto, Canada.

\* 30 Day money-back guarantee.



Australia: 2-519-3933 • Brazil: 11-453-5588 • Cyprus: 2-62-1068 • Denmark: 33-250-109 • Finland: 0-297-5033 • France: 14-908-9000 • Germany: 711-62-7740 • Greece: 1-524-9981  
Hungary: 1-215-0082 • India: 11-544-1343 • Israel: 3-647-5613 • Italy: 11-437-5549 • Japan: 3-3382-3136 • Malaysia: 603-7778945 • Mexico: 5-396-3075 • Netherlands: 18-031-7666  
New Zealand: 9-267-1756 • Norway: 22-16-70-45 • Portugal: 1-814-6609 • Singapore: 462-0006 • Slovenia: 61-317-830 • South Africa: 331-68309 • South Korea: 2-2-222-3431  
Spain: 1-553-3234 • Sri Lanka: 1-86-5970 • Sweden: 8-740-5500 • Thailand: 66-2-398-6952 • United Kingdom: 203-23-3216

CIRCLE NO. 115 ON REPLY CARD



303

# Hands-on Internet

Cyril Bateman discusses how Archie and Gopher help you search for files on the Internet.

In order to use the File Transfer Protocol described in the last issue, two descriptions are essential – the location of the required file and the file name.

Internet is huge, and to locate specific files it is necessary to understand and use the established methods and protocols. The desired file can contain anything capable of storage in a computer. Obviously, program software is the most common. But the possibilities are almost endless, from the script of a Shakespeare play or the Dead Sea Scrolls to views from the Hubble telescope or a piece of music<sup>1</sup>.

If the file name is known, maybe only vaguely, its location is easy to find; however, the file name is usually unknown.

The one essential document 'Anonymous FTP: Frequently Asked Questions (FAQ) List' is available for down loading from a number of sites.

When you are equipped with FTP and a search tool, every facility becomes possible. As with most computer actions the most difficult part is starting out, which these articles seek to address.

For 'surfers' of the Internet, two different search engines are readily available – Archie & Gopher. These are designed for use as 'local clients' on your personal computer. They are available as starter kits or you can download them from Internet. By having access to Internet with FTP and carrying out the procedures described here, then all other packages can easily become accessible.

### Searching with Archie...

The oldest search tool – Archie – is effectively a card index for FTP files. It was developed at McGill University, Montreal for searching all available Unix based computer archive sources of directories and file names. The name Archie is derived from archive<sup>1</sup>.

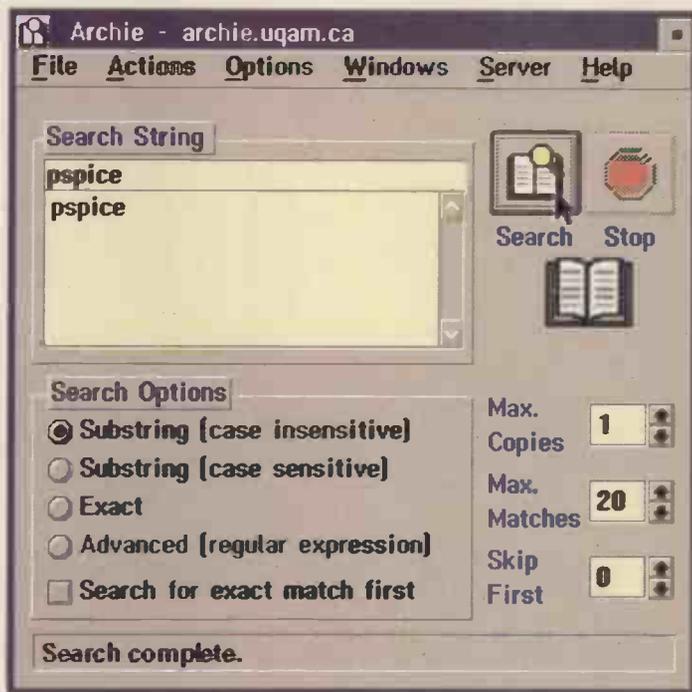


Fig. 1. Using Archie to search for the location of 'P Spice' software file. Search for 'P Spice' using the Archie server located at 'archie.uqam.ca.' in Canada. Note the 'aid memoir' display of used search strings.

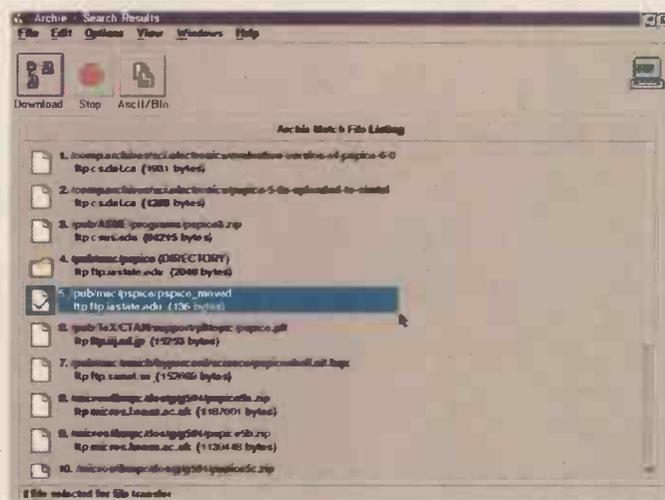


Fig. 2. Using Archie to search for the location of 'P Spice' software file. Result of Archie search for 'P Spice' using the search string 'P Spice'. Interrogation of the highlighted file revealed two locations for the required software. These locations were used for the FTP example in the previous article.

Archie servers search all the 1000 plus Unix-based computers comprising the Archie database archive of FTP files. These servers are periodically automatically updated. In theory, all the servers hold the same information, but due to the updating sequences, this is not absolutely true.

Archie searches are restricted to a directory name or file name. This name can be incomplete, since Archie looks automatically for near matches, and certain 'wildcards' are allowed. Having located the desired file, either Archie or FTP can be used for the download, Figs 1 and 2.

All anonymous FTP sites, Unix and non-Unix based, are identified in the Anonymous FTP Sitelist, however since this is an extremely large listing, be prepared for a lengthy download session<sup>2</sup>.

**... and later with the Gopher**

The newer search tool - Gopher - was developed at the University of Minnesota in 1991. While Archie is a single line, single word search at the chosen server, Gopher is menu based, allowing more flexibility and by default searches the contents of all Gopher servers, which is known as 'GopherSpace'. Two variations are included in the search engine, Veronica developed at the University of Nevada and Jughead. Both support Boolean controls and multi word search strings, Figs 3 and 4.

To avoid excessive numbers of matches, Veronica and Jughead are best used with multi word search strings. While the desired Boolean controls can be specified, the default for two or more words assumes the implicit 'and'<sup>3</sup>.

A Veronica search of the 5000 plus

Gopher servers, offers two predefined styles, Fig. 3.

- Find Gopher directories by title word(s) via xxx. This search will find only Gopher directories whose titles contain your specified search words. This is used to find major holdings of relevant information. Having selected a directory it can be 'opened' to show contents.

- Search GopherSpace by title word(s), via xxx. This search will find all types of resource whose titles contain your specified search words.

Jughead searches, like Archie, are restricted to individual locations and are distinguished from Veronica searches by the description 'Search GopherSpace AT xxx' as distinct from 'via xxx'.

Use of the multiword search with implicit 'and', together with the '\*' wildcard permitted at the end of a partial word, can provide a tightly focused query and return only the more relevant matches<sup>3</sup>.

Equipped with FTP, Archie, and Gopher, any publicly available Internet FTP resource can be located and accessed for file transfer, since it is these protocols which form the basis of the various WWW search engines. ■

**References**

1. Surfing with intent, *EW&WW*, June '95, pp. 488/492.
2. Anonymous FTP-FAQ. See panel, 'Frequently asked questions'.
3. How to compose Veronica Queries. See panel, 'Frequently asked questions'.

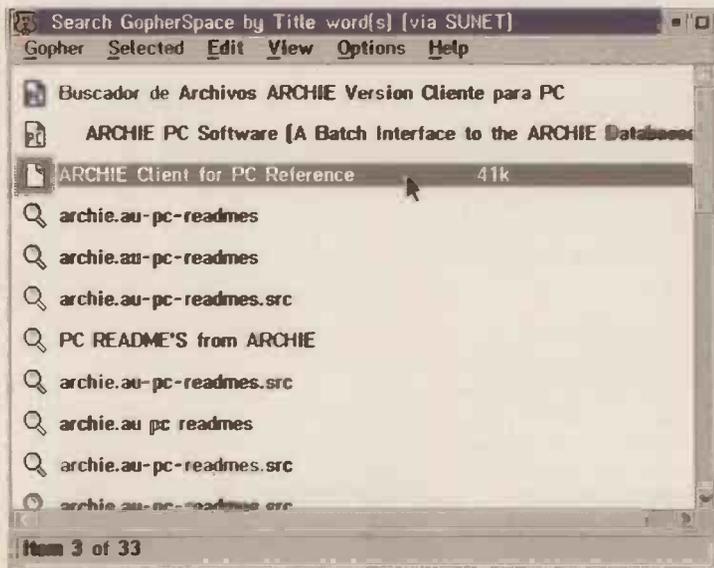


Fig. 4. Using Gopher to search for the location of 'Archie Client' software file. Result of search using the multi word search string 'Archie PC Client'. Further searches using different search strings or different servers will be needed.

**Frequently asked questions**

Frequently asked questions articles, called 'FAQs' are readily available for all Internet activities, and should be the first point of reference for any help needed.

For this reason they are widely available, and can be obtained by 'E mail' requests, as well as from the relevant NewsGroups or by anonymous FTP.

**Anonymous FTP FAQ**

- NewsGroups
  - news.newusers.questions.
  - news.announce.newusers.
  - alt.sources.wanted.
  - comp.archives.
  - comp.archives.admin.
  - comp.sources.wanted.
  - alt.answers.
  - comp.answers.
  - news.answers.

**FTP**

- garbo.uwasa.fi      pc/doc-net/ftp-list.zip
- oak.oakland.edu    /SimTel/msdos/info/ftp-list.zip

**Archie FAQ**

**FTP**

- archie.mcgill.ca      archie/pub/archie.faq

**Gopher FAQ**

- NewsGroups
  - comp.answers.
  - news.answers.

**FTP**

- rtfm.mit.edu    /pub/usenet/news.answers/gopher-faq

**Veronica. - how- to- query- veronica**

- Gopher://Veronica.scs.unr.edu    how-to-query-veronica

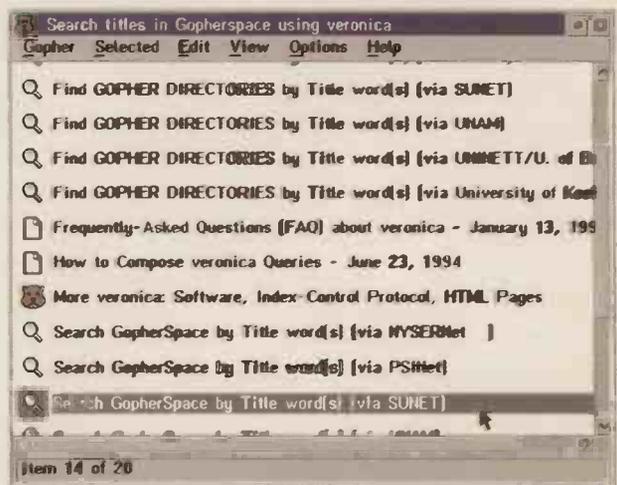


Fig. 3. Using Gopher to search for the location of 'Archie Client' software file. This illustrates just a few of the menu options available for a Gopher search. Note the two main search options discussed and the ready prepared popular Gopher servers. Many other servers throughout the world are also available from other menu selections. Note also the menus provided to supply the two required documents, 'veronica FAQ' also 'How to Compose veronica Queries'. Simply click on the highlighted selection to 'pop-up' the search box.

# Designing an SSB outphaser

**Outphasers for SSB transmitters demand accurate component values, but analyses of such circuits are rare. David Gibson not only presents such an analysis, but also explains how he has extended the outphaser's scope.**

An algebraic analysis of an outphaser, also called a phaser or Hilbert transformer\*, is difficult and is not often discussed – even in otherwise comprehensive filter textbooks. The component values are largely folk-lore, passed on from application to application.

You may say that 'if it ain't broke, don't fix it', but an analysis is useful for several reasons – not least because it allows you to check whether circuit values have been transcribed correctly. I have seen examples where this was clearly not the case.

In this article I present networks using op-amps and simple first-order networks. These are easier to adjust than conventional passive second-order networks, as well as being easier to study. This makes it possible to design more accurate networks, or ones with a wider bandwidth for applications in music, audio effects. It also allows frequency shifting, which may be required for applications such as spectrum analysis and sonar processing. In addition to presenting analogue networks, I show an example using digital signal processing techniques.

I will not give a detailed mathematical analysis due to its complexity. Most of my work was done with simple Basic programs which plotted phase and amplitude responses. Using this method I was able to tweak the component values to produce some very accurate filters. This method also made it easy to investigate the effects of component tolerances and drifts.

### SSB modulation background

The heart of a single-sideband modulator or demodulator is a circuit with the ability to shift a range of frequencies from the audio band to rf, or if. The simplest way to do this is to amplitude-modulate the signal onto a carrier using a balanced modulator.

The unwanted sideband and any residual carrier are removed in a crystal filter. This method has an advantage, namely it is conceptually simple, but also has disadvantages.

It can be difficult set up the filters to adequately attenuate the unwanted sideband, and it is inflexible.

A second method is to use an 'outphaser' which is the subject of this article. There is also a third method. Before discussing the outphaser, I will say a little bit about this because, depending on the application, there is sometimes little to choose between these two methods.

### The 'third' method

This third method for removing unwanted sideband and residuals was first described by Weaver in 1956, and modified by Turner, writing in *Wireless World* in 1973. In this method, Fig. 1, an audio signal is first modulated onto quadrature carriers at a fixed 'intermediate' frequency. The upper sidebands of the two channels are filtered out, leaving the lower sidebands which are in phase quadrature, Eqn 1.

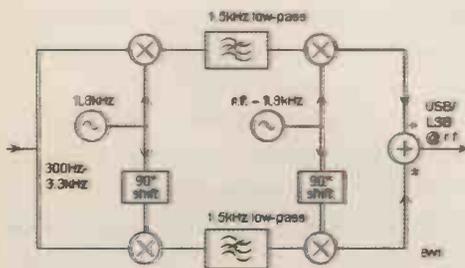


Fig. 1. 'Third method', due to Weaver and Turner. Lower sidebands in phase-quadrature at if are modulated onto an rf carrier, and summed. The unwanted sidebands cancel leaving an ssb signal. The same circuit is used for demodulation, where the salient point is the extremely low if of 1.8kHz which eases the filtering requirements as explained in the text.

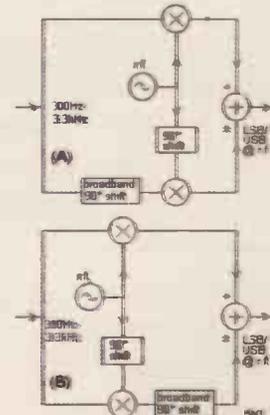


Fig. 2. Outphaser method. Audio input is shifted by 90° and modulated on to two quadrature carriers a). The signals are summed and the unwanted sidebands cancel. The outphaser can alternatively be placed after the modulators b). It is easier to construct a broadband 90° network at rf than at audio (see text) but, when it comes to changing the rf, it is less flexible.

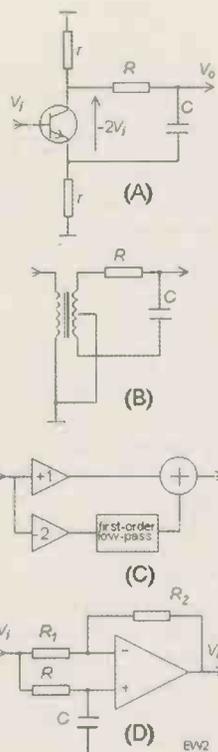


Fig. 3. First-order all-pass filters. a) Historical filter using transistor; b) Version for use at rf; c) Functional diagram; d) Implementation with op-amp.

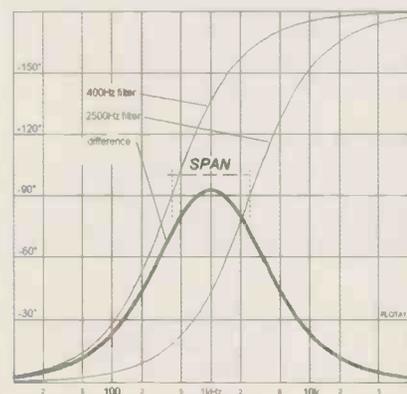
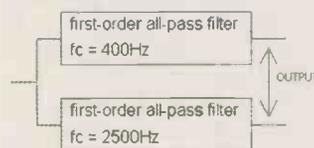


Fig. 4. Difference of one pair of first-order filters  
 a) In an attempt to increase the usable frequency range, we utilise the difference between two filters.  
 b) The phase response of the two filters in a), and the difference of the two. The range of frequencies for which the phase difference is 90° can be improved further by cascading pairs of all-pass filters.

$$\underbrace{\sin \omega_m t}_{\text{audio modulating signal}} \times \underbrace{\sin \omega_c t}_{\text{rf carrier}} = \frac{1}{2} \cos(\omega_c - \omega_m)t - \frac{1}{2} \cos(\omega_c + \omega_m)t$$

lower sideband                      upper sideband (removed by filtering)

and similarly

$$\sin \omega_m t \times \cos \omega_c t = -\frac{1}{2} \sin(\omega_c - \omega_m)t + \frac{1}{2} \sin(\omega_c + \omega_m)t \quad (1)$$

$$\underbrace{\sin(\omega_i - \omega_m)t}_{\text{lower sideband at if}} \times \underbrace{\sin(\omega_c - \omega_i)t}_{\text{rf carrier}} = \frac{1}{2} \cos(\omega_c - \omega_m)t - \frac{1}{2} \cos(\omega_c + \omega_m)t$$

lower sideband at rf                      upper sideband at rf

and similarly

$$\cos(\omega_i - \omega_m)t \times \cos(\omega_c - \omega_i)t = \frac{1}{2} \cos(\omega_c - \omega_m)t + \frac{1}{2} \cos(\omega_c + \omega_m)t \quad (2)$$

Equations 1 & 2 describe the 'third' method of ssb generation

The next step is to take the intermediate frequency signals and to modulate them onto quadrature carriers at rf – or more precisely, at the difference between the rf and the intermediate frequencies, Eqn 2.

Each of the channels provides an upper and lower sideband at the final rf. The crucial aspect of this is the phase of the signals. From eqn 2 you can see that, if the signals are added, the upper sidebands will cancel, leaving only the lower sideband. Likewise, if you subtract the signals you get only the upper sideband.

The advantage of this method is that, by using a fixed intermediate frequency, you ease the problems of filtering the unwanted sidebands. If you choose a very low intermediate frequency, then a simple audio low-pass filter will suffice.

However, the salient point of the Weaver method arises when demodulation is considered. The implementation in Fig. 1 can be used for demodulation simply by swapping the order of the two modulators. Alternatively it would be possible to demodulate directly to baseband, but this would require a highly selective filter to remove the unwanted sideband. The Weaver method uses an intermediate frequency within the audio band, at 1.8kHz.

By choosing the lowest possible intermediate frequency, so that the wanted signal 'wraps round' at zero frequency, the filtering requirement changes from a band-pass filter to a simple low-pass audio filter. Additionally, the low frequency means that the filtering is less stringent, though with an eighth-order filter (48dB/octave) would still only give 24dB attenuation at 2.1kHz, from a cut-off at 1.5kHz.

If the audio band is 300-3300Hz, the low intermediate frequency results in each channel having an upper if sideband at 2.1-5.1kHz, which is filtered out. There is also a lower sideband extending from minus 1.5kHz to plus 1.5kHz.

The concept of a negative frequency can be confusing. Physically, it appears as a 'normal' 1.5kHz, and the information that it is 'negative' comes from the relative phases of the two signal channels. The two channels contain information about the original upper and lower

rf sidebands. By adding or subtracting the signals you can cause one or other of the sidebands to cancel out, providing the required information.

One aspect of the Weaver method is that the modulators have to be ac coupled to prevent dc bias from manifesting itself as a 1.8kHz tone. The ac coupling means that there is a notch in the audio response. However, this can be made narrow enough to be un-noticeable.

The modification suggested by Turner in 1973 involved digital modulation techniques. The carriers can be square waves, and the modulators, certainly at low frequencies, can be transmission gates. At vhf it is possible to rely on the harmonic content of the square waves to generate the rf signal. Additional harmonics present throughout the circuit do not cause a problem because they either cancel out, or are filtered.

Sometimes, the audio demodulation is done with a stepped square wave. One implementation is known as a rotary mixer. The third, and some higher, harmonics are absent in a correctly stepped sine wave, which eases the filtering requirements. The size of the steps in the sine wave can be calculated using Walsh functions.

The Weaver/Turner technique was discussed by Hamilton in this magazine in 1993 and was used in a design by Dorey in 1994.

### Phasing in SSB designs

As with the Weaver method, the basic idea behind the phasing method is to generate two double-sideband channels where one of the sidebands is in antiphase and can be cancelled out, Fig. 2. An rf carrier is modulated directly to produce the sidebands described below.

$$\underbrace{\sin \omega_m t}_{\text{audio signal}} \times \underbrace{\sin \omega_c t}_{\text{rf carrier}} = \frac{1}{2} \cos(\omega_c - \omega_m)t - \frac{1}{2} \cos(\omega_c + \omega_m)t \quad (3)$$

lower sideband                      upper sideband

For the second channel the audio signal is passed through a broad-band phase-shift network which alters its phase by 90° at all frequencies, without altering its amplitude. It is

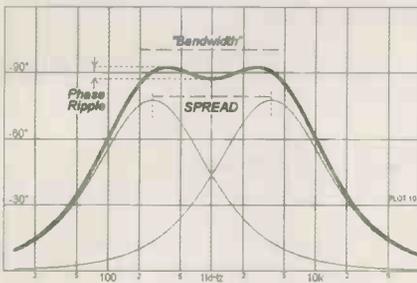


Fig. 5. Difference of two pairs of first-order sections, example 1. Phase ripple is three over a 'bandwidth' of around 200Hz to 5kHz

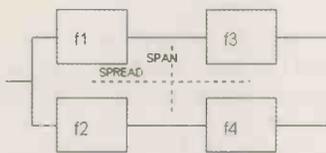


Fig. 6. Two pairs of first order filters. Difference between the two outputs approximates to a 90° phase shift. The filter is described by the span (ratio  $f_2/f_1, f_4/f_3$ ) and the spread ( $f_3/f_1, f_4/f_2$ )

then modulated onto a quadrature carrier to produce a further pair of sidebands.

$$\cos \omega_m t \times \cos \omega_c t = \frac{1}{2} \cos(\omega_c - \omega_m)t + \frac{1}{2} \cos(\omega_c + \omega_m)t \quad (4)$$

Now, by adding or subtracting the signals it is possible to cancel one or other of the rf sidebands, Fig. 2a. It is also possible to swap the order of the components and use the phase-shift network at rf, Fig. 2b.

There is not a lot to choose between the Weaver and phasing methods. The Weaver method is slightly more complex in terms of circuitry and frequency control. However, the phasing method needs some accurate components in the rather special phase-shift network.

The phasing method can be used in applications other than 3kHz audio. As I will show, a simple network can be used at rf, and the technique can be used to shift a wider band of frequencies – say 20kHz audio – for music applications. A small shift of 5-10Hz can be used to prevent 'howl-around', while a larger shift can be used for special effects.

**Designing the phase-shift network**

An integrator or differentiator achieves a 90° phase shift, but has a varying gain with frequency. For 90° phase shift and constant gain, a more complex network is required. It can be proved that a 'perfect' outphaser, which works at all frequencies, is physically impossible to construct†. Thus, any network we construct must be a compromise.

Many outphaser designs of have appeared over the years. It is interesting to look at dif-

ferent designs and to trace their origins by the obscure component values they use – a sort of electronic equivalent of genetic markers. Some designs which have appeared in this magazine are due to Hickman (1991) who reviewed some outphaser and Weaver circuits; Hosking (1994) who described the so-called 'polyphase' network; and, most recently, Green & Hosking (1996) who presented a polyphase receiver design.

The polyphase network is an old solution to the problem. It is something of a sledgehammer approach, which I will not discuss further here. Instead, I will show how an outphaser circuit can be built from simple op-amp filters to achieve varying degrees of sophistication.

**First-order network**

A simple first-order RC low-pass filter has a phase shift of 45° at its -3dB frequency,  $\omega_0$ . Two networks would result in 90°, but the gain varies with frequency. However, by driving the 'bottom' of a first-order network with an inverted signal, Fig. 3, you can get a 90° shift at  $\omega_0$  and constant gain. This response is called a first-order all-pass filter. An all-pass filter has a flat amplitude response, but the phase shift varies with frequency.

Figure 3 shows several ways of generating the response. Op-amps are cheap enough, so the method of Fig. 3d is the one I prefer. Resistors  $R_1$  and  $R_2$  set the overall gain, whilst  $R$  and  $C$  set the centre frequency to  $\omega_0=1/CR$ . I don't want to include too much maths in this article, but it is useful to note that the transfer function, in complex frequency, is,

$$\frac{V_o}{V_i} = \frac{1 - \frac{R_2}{R_1} j\omega / \omega_0}{1 + j\omega / \omega_0} \quad (5)$$

If  $R_1=R_2$  then this expression shows a unity gain, and phase shift  $\phi$  defined from,

$$\tan \frac{1}{2} \phi = -\frac{\omega}{\omega_0} \quad (6)$$

If the phaser were used at rf, Fig. 2b, in a direct-conversion radio, then its performance might well be satisfactory. The equation above

shows that, in the 50m band, at 6MHz, it is possible to maintain a 90° shift to  $\pm 3$  over a bandwidth of 600kHz. However, a simple all-pass filter is not adequate for use at baseband. With a centre frequency of 1kHz, the variation in phase shift over the audio band of 300Hz to 3kHz would be an enormous -33° to -143°. We need to resort to higher-order sections, or to chains of filters, as I will now describe.

**Multi-section filters**

Instead of building a single filter with a phase shift of 90° it is easier to build a pair of filters where the difference in phase shift is around 90°. Figure 4a shows an example. You could use two first-order filters, as in Fig. 3d, with centre frequencies of 400Hz and 2500Hz. Figure 4b shows how the phase shift of each filter varies with frequency.

There is a band, centred at around 1kHz, where the difference in phase shift is close to 90°. With this arrangement an accuracy of  $\pm 3$ ° can be achieved from 630Hz to 1600Hz, or 2.5:1. This is still not large enough for speech, where perhaps 20:1 is required, so the principle needs to be extended, as demonstrated in Fig. 4, to higher-order filters.

A common configuration is to use passive second-order filters. It is very rare to see any analysis of such a circuit, though Walters, in 1986, went some way towards explaining the design process.

Occasionally, active second-order all-pass filters are seen. A classic one was presented by Holt & Grey in 1967, and another version given by Gibson in 1992, but these are difficult to set up, and to analyse.

A historical reason for the use of passive second-order filters is that they were easier to construct than passive first-order filters. Fig. 3b gives an example. Nowadays, op-amps are cheap, and make life much easier because active first-order filters are simple and conceptually easier to analyse.

**Required accuracy**

Before discussing these enhanced filters, you need to obtain some idea of the accuracy required. Phase shift needs to be 90° and the amplitude difference between the outputs of the

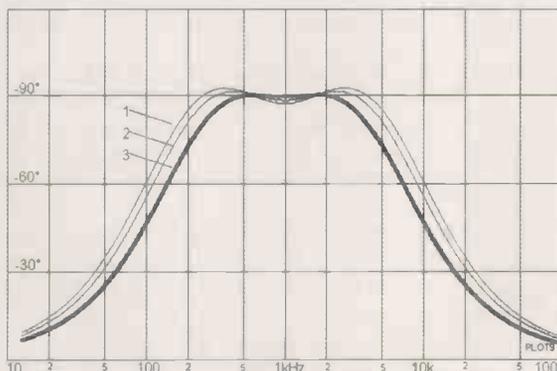


Fig. 7. Difference of two pairs of first-order sections, examples 1-3.

two filter paths should be zero at all frequencies. Unless this is the case you will not achieve perfect attenuation in the unwanted sideband.

Obtaining an expression for the 'leak-through' of the unwanted sideband is straightforward but intricate. You begin by defining the phase error between the two channels to be  $\phi$  degrees. Assuming that one channel has a gain which is a fraction  $\alpha$  too high, and the other is  $\alpha$  too low.

Clearly it is always possible to represent the gains in this symmetrical way because the absolute gain is less important. Provided that  $\alpha$  is 'small', i.e. less than 10%, you can write the ratio of the amplitudes as  $1+2\alpha$ . Voltage attenuation in the unwanted sideband,  $V_1$ , can then be written (Gibson, 1992), relative to the voltage of the wanted sideband  $V_2$  as,

$$\frac{V_1}{V_2} = \frac{\sin^2 \frac{1}{2}\phi + a^2 \cos^2 \frac{1}{2}\phi}{\cos^2 \frac{1}{2}\phi + a^2 \sin^2 \frac{1}{2}\phi} \quad (7)$$

Now if  $\phi$  is small too, say less than  $10^\circ$ , it is possible to approximate to,

$$\frac{V_1}{V_2} \approx \sqrt{\left(\frac{\pi}{360}\right)^2 \phi^2 + a^2} \quad (8)$$

For example, if you can maintain the phase error to  $8^\circ$ , and amplitude  $\alpha$  to 7%, then both errors contribute equally to the 'leak-through'. The unwanted sideband will be at a voltage level of 1/10.1 of the wanted sideband, or -20dB. An angle of  $0.8^\circ$  and an error of 0.7% would give -40dB.

Note that you will need tight tolerance components in order to achieve this level of performance. Usually, the attenuation is obtained from a combination of rf filtering and outphaser performance. This results in a good overall response with neither item being critical.

### A difference of two pairs

Figure 4 showed how you could use the difference of one pair of first-order filters. Extending this to two pairs of filters is

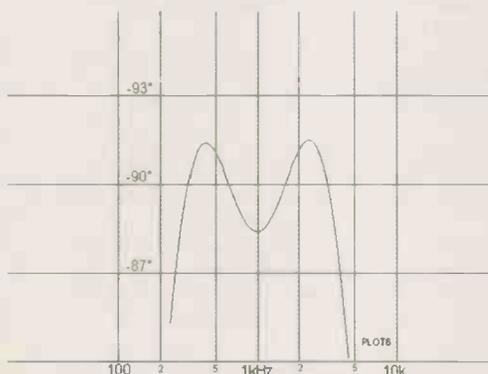


Fig. 8. Difference of two pairs of first-order sections, magnified central portion of response, component values from example 2a.

straight-forward. Each of the pairs gives rise to a 'hump' in the phase response similar to that shown in Figure 4b. If you place the two humps at the correct separation in frequency,

their effects add to give a response with an almost flat top, Fig. 5.

Figure 6 shows how the outphaser is configured. There are four first-order all-pass fil-

## Notes on the maths

Equation 6, giving the phase shift for a single first-order all-pass filter, can be used as the basis for phase plots. If you are manipulating the equations on paper then equation 9 is a useful short-cut. Its derivation is as follows.

The two filters in the pair, Fig 4, have centre frequencies  $\omega_1$  and  $\omega_2$ . The phase difference,  $\phi$ , comes from

$$\begin{aligned} \frac{1}{2}\phi &= \frac{1}{2}(\phi_1 - \phi_2) \\ &= \arctan\left(\frac{-\omega}{\omega_1}\right) - \arctan\left(\frac{-\omega}{\omega_2}\right) \quad (A1) \end{aligned}$$

Making the substitutions for span and  $\Omega$  discussed in the main text; taking the tangent of both sides of (A1); and recalling the identity:

$$\tan(a \pm b) = \frac{\tan a \pm \tan b}{1 \mp \tan a \tan b} \quad (A2)$$

produces equation 9 in the main text. This operation can be applied repeatedly as we chain the filter pairs, but the notation gets rather difficult to follow.

A full analysis should aim to give span and spread in terms of a specified phase ripple and 'bandwidth' rather than simply giving phase as a function of frequency. We can differentiate the expression to find the frequencies of the peaks of the phase response - the turning points of the curve.

By specifying the phase shift at these points to be  $\frac{1}{2}\phi$  above  $90^\circ$ , and the central trough to be at  $\frac{1}{2}\phi$  below  $90^\circ$  it is possible to simplify the procedure - although it is still rather difficult. You could differentiate (9) directly, but it is easier to start with (6) and write,

$$\tan \frac{1}{2}\phi = \Omega \Rightarrow \frac{d\phi}{d\Omega} = \frac{2}{1 + \Omega^2} \quad (A3)$$

It is now possible to combine expressions for  $d\phi/d\Omega$  for each filter and set to zero to find the turning point. This is tedious and tends to indicate that a computer analysis would save time.

### Footnotes

\*That is, a device which implements a Hilbert transform. This is one of a number of integral transforms. The Fourier and Laplace transforms belong in this category.

†Take a square wave and look at the phase and amplitude of all its harmonics. If the fundamental has unity amplitude then the amplitude of the resultant square wave is,

$$1 - \frac{1}{3} + \frac{1}{5} - \frac{1}{7} + \frac{1}{9} - \frac{1}{11} + \dots = \frac{1}{4}\pi$$

Now shift each harmonic by  $90^\circ$  and try to reconstruct the waveform. You end up with a series of the form,

$$1 + \frac{1}{3} + \frac{1}{5} + \frac{1}{7} + \frac{1}{9} + \frac{1}{11} + \dots \rightarrow \infty$$

The sum increases logarithmically and does not converge, so the resultant amplitude of the waveform is infinite. Thus it is shown that a perfect outphaser cannot cope with this specific waveform. It can be inferred that it cannot cope with a generalised waveform, and so a practical 'perfect' outphaser cannot be constructed.

††Note that finding a flat-top response in the phase domain using multiple all-pass filters is similar to the more conventional problem of finding a flat-top in the amplitude domain when using multiple tuned circuits.

ters with centre frequencies  $f_1, f_2, f_3$  and  $f_4$ . These are arranged in two paths, and the wanted signal is the difference between the two.

If only the  $f_1/f_2$  pair were used, the phase difference would be the left hand 'hump' in Fig. 5. Using only the  $f_3/f_4$  pair would give rise to the right-hand curve. Overall phase difference is found by adding the responses to give the third curve on the graph††.

**One pair of 2nd-order filters**

As I have said, traditional outphaser designs tend to use a single pair of passive second-order filters instead of two pairs of active first-order filters. A first-order network has several advantages over the more complex second-order network,

- It has unity gain, with  $r_1=r_2$  so there is no need to set an accurate non-unity gain.
- It only has a single  $C$  so this can be chosen for cost and availability. You don't need to choose two accurately matched capacitors in E24 values.
- With  $C$  fixed, the only component which affects the centre frequency is  $R$ .
- The gain can easily be trimmed to unity by altering  $r_1$  or  $r_2$ .
- If – and only if – the gain is trimmed to unity, the phase-shift only depends on  $R$  and  $C$ . This 'orthogonality' makes simulation and analysis easier, as well as the setting-up.

**Using two pairs of first-order filters**

To describe the dual first-order filter of Figs 5 and 6, I use two terms. The *span* is the ratio of the centre frequencies of the two filters which comprise a 'hump' in the phase response; i.e.  $f_2/f_1$  and  $f_4/f_3$ . The *spread* is the ratio of the centres of the humps themselves.

For a single pair of filters, Fig. 4, you can write the phase shift in a similar way to (6), as

$$\tan \frac{1}{2}(\phi_1 - \phi_2) = \frac{\sqrt{1/\gamma} - \sqrt{\gamma}}{\Omega + \frac{1}{\Omega}} \quad (9)$$

where  $\Omega$  is  $\omega/\omega_c$  is the 'normalised' frequency and  $\lambda=\omega_2/\omega_1$  is the span of the pair of filters, with  $\omega_c=\sqrt{(\omega_2\omega_1)}$ . When you try to extend the analysis to cope with two pairs of filters it becomes difficult to represent them concisely – especially when you want to use the equa-

tions to find out what values of span and spread to use.

Fortunately, iterative computer techniques are now possible, and are just as valid. I used a set of small Basic programs to investigate the filters by 'trial and error'.

**Filter examples**

**Example 1.** The filter in Figure 5 is centred around 1000Hz and the spread is 14. Thus the two humps are at  $f_{12}=267\text{Hz}$  and  $f_{34}=3742\text{Hz}$ , so that their ratio is 14:1, and the geometric mean,  $\sqrt{(f_{12}f_{34})}$ , is 1000Hz. In other words, they are at the centre frequency multiplied and divided by  $\sqrt{\text{spread}}$ . Individual spans are both 4.36 so, similarly,

$$\begin{matrix} f_1=128.0\text{Hz} & f_3=1792\text{Hz} \\ f_2=558.1\text{Hz} & f_4=7813\text{Hz} \end{matrix}$$

where  $\sqrt{(f_1f_3)}=267\text{Hz}$ ,  $f_3/f_1=4.36$ , etc.

Phase shift at the centre frequency of 1000Hz is  $87.48^\circ$ , i.e.  $2.52^\circ$  below  $90^\circ$ . The peaks are at  $92.66^\circ$ . Response dips to  $87^\circ$  at 216Hz and 4620Hz. This could be loosely called the bandwidth because of the similarity to the useful response of a bandpass filter in the amplitude domain.

**Examples 2 and 3.** The difference between the peaks of the phase response curve, and the trough at the centre frequency could be termed the 'phase ripple'. It can be reduced by reducing the spread of the filter pairs. As this is done, the phase response becomes flatter, but it is no longer centred at  $90^\circ$ . It has to be corrected by adjusting the span. Figure 7 shows the effect of reducing the spread to 12 (Example 2) and to 9 (Example 3), while reducing the span appropriately.

Notice that in Example 3, ripple is extremely low – almost within 1/4 degree. Bandwidth however is limited.

**Example 2a.** Of the above two examples, let us suppose that Example 2 looks like a suitable filter to build. The procedure is as follows. Firstly, note that all the examples used a centre frequency of 1000Hz. The individual sections of Example 2 have centre frequencies of,

$$\begin{matrix} f_1=142.9\text{Hz} & f_3=1715\text{Hz} \\ f_2=583.1\text{Hz} & f_4=6997\text{Hz} \end{matrix}$$

If you want to alter the overall centre from 1000Hz you can scale these frequencies. However, you do not need to do that for this example. Using E24 resistors you can get close to these frequencies:

$$\begin{matrix} f_1: 1.0\text{M}\Omega + 110\text{k}\Omega \ \& \ 1\text{nF} \Rightarrow 143.4\text{Hz} \\ f_2: 270\text{k}\Omega + 3.0\text{k}\Omega \ \& \ 1\text{nF} \Rightarrow 583.0\text{Hz} \\ f_3: 91\text{k}\Omega + 1.8\text{k}\Omega \ \& \ 1\text{nF} \Rightarrow 1715\text{Hz} \\ f_4: 22\text{k}\Omega + 750\Omega \ \& \ 1\text{nF} \Rightarrow 6996\text{Hz} \end{matrix}$$

Figure 8 shows the central portion of the phase response on an enlarged scale. The slight asymmetry of the curve is due to the errors caused by the resistor approximations. The response is only very slightly different from that predicted by Example 2.

Figure 9 shows a circuit diagram of the complete outphaser. The filters  $R_1/C_1$  to  $R_4/C_4$  use the values from the list above. The resistors should be 1% metal film with a low temperature coefficient. The capacitors should be polystyrene 1% parts.

Unmarked resistors are all equal in value, say  $100\text{k}\Omega$ . They should be 1% metal film or, possibly 2% thick film resistor packs, for which the temperature tracking will probably be good. The op-amps should have a low input current, for example BIFET types, or you will need to consider the effect of bias currents.

Filter inputs must be driven from a low impedance source so as not to affect the gain or phase response. ■

**Next time...**

In the concluding part of this article I will look at the effect of component tolerances, which can be significant. I will go on to look at outphasers built from three and four filter sections. These can have an extremely flat top, or a very wide bandwidth. I will conclude by looking at a digital filter implementation of an outphaser.

**Further reading**

Dorey, Frank, (1994), 'Direct conversion SSB receiver', *Electronics World + Wireless World*, 100(1702), Sept. 94, pp. 743-747.  
 Green, Rod & Hosking, Richard (1996), High performance direct conversion, *Electronics World*, 102(1718), Jan. 96, pp. 18-22.  
 Gibson, David, (1992), SSB modulation review, *Cave Radio & Electronics Group Journal*, 8, pp12-16, June 1992, British Cave Research Association.  
 Hamilton, Nic, (1993), Third method, fourth explanation, *Electronics World*, 99(1695), April 93, pp. 278-284.  
 Hickman, Ian (1991), Circuits, systems & standards: ICs simplify design of single-sideband receivers, *EW+WW*, 97(1668), Nov. 91, pp. 939-943.  
 Holt & Grey (1967), in Proc. IEE, Dec 67, p187  
 Hosking, Richard (1994), Polyphase SSB, *EW+WW*, 100(1696), March 94, pp. 202-206.  
 Lockhart, G.B. & Cheetham, B.M., (1989), BASIC Digital Signal Processing, Butterworth  
 Turner, A.J., (1973), Single-sideband suppressed carrier generation – modification of the 'third method' made possible by the use of integrated circuits, *Wireless World*, 79(1455), Sept. 73, pp. 453-455.  
 Walters, L.C., (1986), Improved Hilbert transformer for S.S.B. speech, *EW+WW* 93(1602), pp20-24, April 1986.  
 Weaver, D.K., (1956), A third method for the generation and detection of single-sideband signals, Proc. I.R.E. 44(12), pp. 1703-1705.

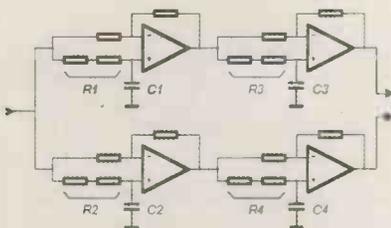


Fig. 9. Circuit of outphaser using difference of two pairs of first-order networks (see text).

# Eight year EW index Hard copy or disk

Includes over 600 circuit idea references

Whether as a PC data base or as hard copy, SoftCopy can supply a complete index of *Electronics World* articles going back over the past eight years.

The computerised index of *Electronics World* magazine covers the eight years from 1987 to 1995 – volumes 94 to 101 inclusive – and is available now. It contains almost 2000 references to articles, circuit ideas and applications – including a synopsis for each.

The *EW* index data base is easy to use and very fast. It runs on any IBM or compatible PC with 512k ram and a hard disk.

Even though the disk-based index has been expanded significantly from five years to eight, its price is still only £20 inclusive. Please specify whether you need 5 1/4in, 3.5in DD or 3.5in HD format. Existing users can obtain an upgrade for £15 by quoting their serial number with their order.

## Hard copy *Electronics World* index

Indexes on paper for volumes 100 and 101 are available at £2 each, excluding postage.


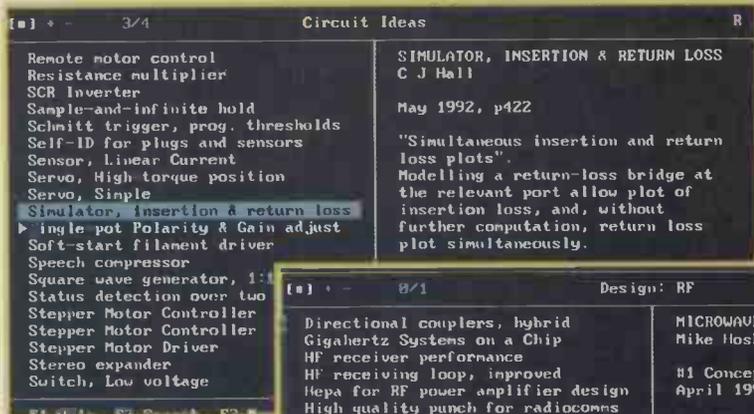


Photo copies of *Electronics World* articles  
Photo copies from back issues of *Electronics World* are available at a flat rate of £3 per article or 50p per circuit idea, both excluding postage.

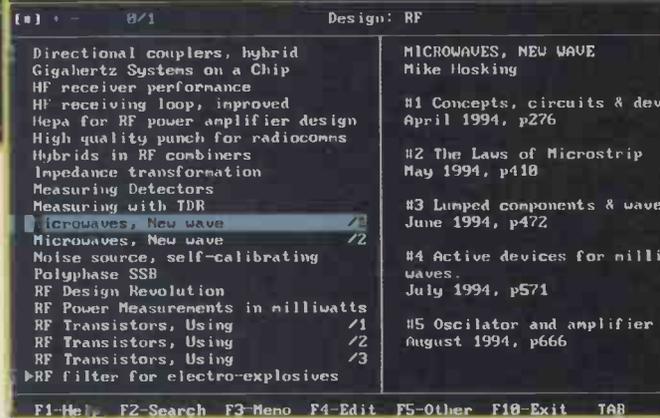

## Ordering details

The *EW* index data base price of £20 includes UK postage and VAT. Add an extra £1 for overseas EC orders or £5 for non-EC overseas orders.

Postal charges on hard copy indexes and on photocopies are 50p UK, £1 for the rest of the EC or £2 worldwide.

For enquiries about photocopies, etc,

please send an sae to SoftCopy Ltd at the address below.



Send your order to SoftCopy Ltd., 1 Vineries Close, Cheltenham GL53 0NU, tel 01242 241455, or e-mail at 100556.112@compuserver.com. Please make cheques payable to SoftCopy Ltd – not *EW* or Reed Business Publishing. Please allow up to 28 days for delivery.
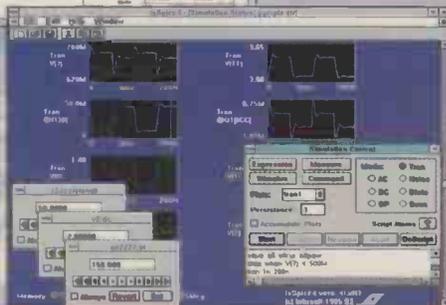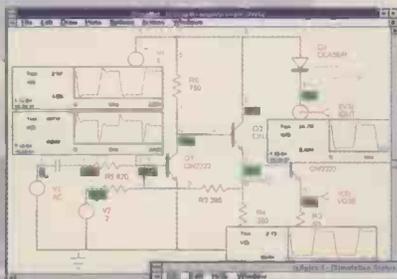
# Interactive SPICE

Stop Waiting for your simulation results!  
Experience the power and Immediate Satisfaction of IsSPICE4!



ICAP/4, The Virtual Circuit Design Lab, is a completely integrated system with schematic entry, the IsSPICE4 native analog and mixed mode simulator, extensive SPICE model libraries and powerful graphics post-processing.



## Platform Support

- Windows
- Windows 95
- Windows NT (x86, Alpha & MIPS)
- Macintosh
- Power Macintosh
- DOS, NEC

- Analyse and Simulate all types of designs with IsSPICE4, the First and Only Interactive Native Mixed Mode SPICE 3 Simulator
- System, Board, and IC level
- Analog, Digital, Sampled-Data, Mixed Mode, Behavioural elements
- Power, ASIC, RF, Mechanical, Physical, Thermal applications
- AC, DC, Transient, Distortion, Temperature, Monte Carlo, Noise, Sensitivity, Optimisation, and Fourier analyses
- Works with all popular schematic entry systems!
- Graphically Driven and Easy To Use
- Support & Service - FREE, EXPERT, UK BASED AFTER SALE SUPPORT, Web & CompuServe Forums
- Affordable, Prices from £450 to £2,300

## Technology Sources Ltd

Falmouth Avenue, NEWMARKET  
CB8 0LZ, UNITED KINGDOM  
Tel. 01638-561460  
Fax 01638-561721  
E-mail: aaj74@dial.pipex.com

Ask us for a  
**FREE Working  
SPICE  
Simulation Kit!**



**The Future Is Interactive!**

# Free to Electronics World readers: irreversible temperature indicators

**ATP Instrumentation is offering an evaluation pack comprising five irreversible temperature indication strips – completely free to Electronics World readers.**

Called Thermostrips, these light, thin indicators consist of one or more heat-sensitive squares or dots. The centre of the indicator dot turns black once the temperature rating shown next to the dot is reached. The change to black is irreversible, so the strips become a permanent record of the upper temperature threshold of a component or piece of equipment.

To aid in maintaining of a piece of equipment, for example, Thermostrips applied for the usage period can be removed during servicing and attached to the service report as evidence of correct functioning. They can also be used to help detect whether goods returned under warranty have been subjected to overheating.

Performance of the strips is not affected by contact with solvents, gases, steam, etc. Because of their size and the way they operate, Thermostrips can be the only practicable way of measuring peak temperature in situations where equipment cannot be watched round the clock, or on moving parts, etc.


Accuracy of the strips is  $\pm 1^\circ\text{C}$  for ratings to  $100^\circ\text{C}$  and  $\pm 2\%$  for ratings above.

To obtain your evaluation pack comprising:

- One single-segment strip with a  $40^\circ\text{C}$  threshold
- One triple-segment strip for 40, 43 and  $46^\circ\text{C}$
- One five-segment strip covering 60 to  $82^\circ\text{C}$
- One eight-segment strip covering 77 to  $116^\circ\text{C}$
- One four-segment mini-strip for 66, 71, 77 and  $82^\circ\text{C}$

...simply fill in the reply coupon between pages 320 and 321, apply a stamp, and send the card to ATP Instrumentation.

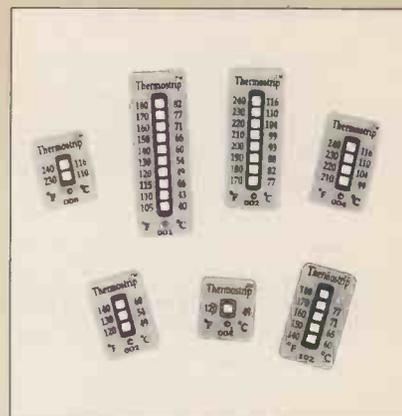To obtain details of the range of temperature strips that ATP Instrumentation supplies, write to Tournament Way, Ivanhoe Industrial Estate, Ashby-de-la-Zouch, Leicestershire LE65 2UU, or telephone 01530 416876, fax 01530 560373.



## Comprehensive instrumentation catalogue

In addition to temperature strips covering the range  $40$  to  $260^\circ\text{C}$ , ATP also supplies a vast range of instrumentation, including:

- timers
- weighers
- chart recorders
- multimeters
- pH meters
- humidity detectors
- vibration meters
- dew-point indicators
- light meters
- power supplies.
- Air flow meters

Send your request for a free catalogue on company letterhead to ATP's address shown above.

# KENWOOD

**TEST & MEASURING INSTRUMENTS  
A SUPERB RANGE OF OVER 100  
QUALITY INSTRUMENTS.**

Available from  
**B.K. ELECTRONICS**



- FM-AM Signal Generators ★ Colour Pattern Generators ★ Video Signal Analyser ★ Video Timing Analyser ★ Video Noise Meter
- ★ Distortion Meter ★ Waveform Monitors
- ★ Vectorscopes ★ Audio Generators ★ Wow and Flutter Meters ★ Electronic Voltmeters
- ★ Digital Multimeters ★ Function Generators
- ★ Frequency Counters ★ Bus Analyser
- ★ Resistance Attenuator ★ Oscilloscopes ★ Fully Programmable Digital Storage Oscilloscopes
- ★ Regulated D.C. Power Supplies

A free, 50 page colour brochure, including price list, is available on request. Please make your request on company headed notepaper, by post or by fax, to:

**B.K. ELECTRONICS**  
Unit 1 Comet Way,  
SOUTHEND-ON-SEA,  
Essex, SS2 6TR.  
Tel: 01702-627572  
Fax: 01702-420243



CIRCLE NO. 120 ON REPLY CARD

# EMBEDDED C ASSEMBLY SIMULATION

## 8051

C compiler, first released in 1991, now features:

- Easy to use Interrupt support with register bank switching
- IEEE floating point arithmetic
- IEEE 695 source level debug output
- Integrated relocatable assembler

Simulator running under Microsoft Windows provides extensive support for the 8051 code development

## 68000

Our first C compiler/assembler package

- now supports floating point arithmetic
- has been widely adopted by many OEM's to support their 68000 and 68307 hardware

## CPU32

68020 C compiler/assembler, originally developed to accompany Motorola's 68020 and 68EC020 evaluation models

- Now supports the CPU32
- 68881 co-processor support
- IEEE 695 source level debug output

Further information from:  
CROSSWARE PRODUCTS

St John's Innovation Centre, Cowley Road, Cambridge, CB4 4WS, UK  
Tel: +44 (0) 1223 421263, Fax: +44 (0) 1223 421006

BBS: +44 (0) 1223 421207 (8-N-1), Internet: sales@crossware.com



CIRCLE NO. 121 ON REPLY CARD

# Two-chip smart accelerometer

**Benefits of this accelerometer – designed using silicon micro-machining – are small size, relatively low cost and repeatable, temperature-stable output. Diedrik de Bruin and Ed Koen of EG&G IC Sensors explain.**

**T**he signal-conditioned accelerometer described here offers many advantages. Manufactured using silicon micromachining, the sensor element has proven reliability. Being wholly monolithic, the signal conditioning circuitry needs no external components and thick or thin film technology.

Both sensor and signal conditioning chips are hermetically packaged together in a ceramic leadless chip carrier. Output parameters are trimmed electrically after packaging. The chip carrier can be mounted in several orientations to allow measurement of acceleration either perpendicular to or in plane with the mounting surface.

## Accelerometer overview

Currently the majority of signal conditioned accelerometers are packaged using hybrid technology. Thick or thin-film resistors are used to set parameters such as offset and sensitivity to the desired values.

This approach results in relatively bulky designs with non-uniform mounting configurations. The user is often required to carry out additional mechanical work, such as designing a mounting bracket.

The accelerometer design discussed here is intended to not only lower the cost of the accelerometer, but also to reduce implementation costs. This is accomplished by mating a silicon micromachined sensor die to a signal-conditioning IC in a ceramic leadless chip carrier.

The two-chip approach allows the sensor and signal conditioning chips to be optimised and avoids the yield losses associated with complicated single-chip designs. The accelerometer is compatible with automated pc board assembly while offering multiple mounting options.

## Sensor element

The accelerometer structure, Fig. 1, measures 3.4 mm square. A seismic mass and four flexures are formed using bulk micromachining processes. Bulk micromachining technology was chosen over surface micromachining

because the entire thickness of the silicon wafer can be used for the seismic mass, resulting in a higher sensor output.

Each of the four beams contains two implanted resistors, interconnected to form a Wheatstone bridge. When the device undergoes an acceleration, the mass moves up or down, causing four of the resistors to increase and the other four to decrease in value. This results in an output voltage change proportional to the applied acceleration.

Eight resistors are interconnected such that the effects of any motion other than that caused by an acceleration in the primary direction are cancelled out. Piezoresistive transduction provides a relatively high output level with low impedance and good linearity. As a result, it is not necessary to include signal conditioning electronics on the same chip as the sensor to obtain good performance.


Silicon top and bottom caps attach to the section containing the seismic mass and the beams. These serve several purposes. Precision gaps are etched into the caps to provide air damping to suppress the resonance peak of the structure. Because the part is critically damped, the response is flat up to several kilohertz – independent of temperature.

Small elevated stops on the top and bottom caps limit the motion of the mass to a fraction of the deflection at which fracture occurs. The mechanical structure does not wear and mechanical latch-up cannot occur. The top and bottom cap form an enclosed cavity around the seismic mass, protecting it against contamination which may obstruct its motion.

Because the three sections are bonded together at the wafer level in the clean room the cavity is free of particles and is protected from particulate contamination during the final chip dicing and assembly operations.

Lastly, the top cap is used to enable testing of the accelerometer in the absence of acceleration<sup>1,2</sup>. The over-force stops on the top cap have been enlarged and a metal electrode has been deposited on them. This electrode has been connected to a bond pad.

When a voltage is applied between the elec-

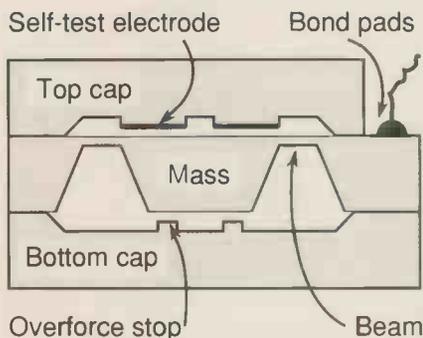

*Fig. 1. The accelerometer die's footprint is 3.4mm by 3.4mm. Piezo-resistive transduction provides a relatively high output.*

trode and the silicon of the seismic mass, an electrostatic force moves the mass toward the top cap. This results in a change in output voltage proportional to the sensitivity and to the square of the applied voltage. It is thus possible to generate an 'acceleration' using an external voltage and to check the functioning of the mechanical structure as well as the electronics.

The accelerometer has been qualified for, and used in, air bag crash detection systems and proven to be very reliable.

**Signal conditioning circuitry**

Signal conditioning circuitry is made in 1.5µm cmos technology. Signals are processed by differential amplifiers throughout most of the circuit in order to minimise common mode effects and noise.

Switched capacitor circuitry is used to save space and because high accuracy gain stages can be made easily. The -3dB bandwidth of the signal conditioning electronics is about 3kHz. The accelerometer is intended for 5V operation with an output voltage in the 0.5-4.5V range.

**Processing the signal**

The accelerometer has a differential output with source impedance of around 4kΩ and full scale output voltage of about ±50mV. The offset voltage, i.e. output at zero applied acceleration, may vary a few millivolts over the temperature range of -40 to 85°C. Also, the full scale output decreases over temperature by about -1900ppm/°C.

The signal conditioning circuitry converts the differential signal into a single-ended signal in the 0.5-4.5V range while compensating for temperature-related signal variations. As a result, the accelerometers are interchangeable with a total error of less than 5%.


The signal path is shown in block diagram, Fig. 2. Output signal of the accelerometer die is processed by the following stages:

- The first stage provides a high impedance load for the sensor and amplifies the signal to maximise the dynamic range during subsequent processing. Offset of the sensor is eliminated by adding a voltage generated by a d-to-a converter. This converter is controlled by a digital word representing the programmed offset value.

- The temperature coefficient of offset (tco) of the sensor is compensated by adding a voltage which is controlled by digital words representing the temperature and the programmed tco value. Both the offset and tco voltages are derived from the supply to ensure that the signal remains ratiometric with supply voltage.

- Signal gain can be varied by changing a capacitor ratio using a digital word. The gain can be varied in a 5:1 range to allow for different full scale specifications.

- The sensor's temperature-coefficient of sensitivity, tcs, is compensated in the next stage.

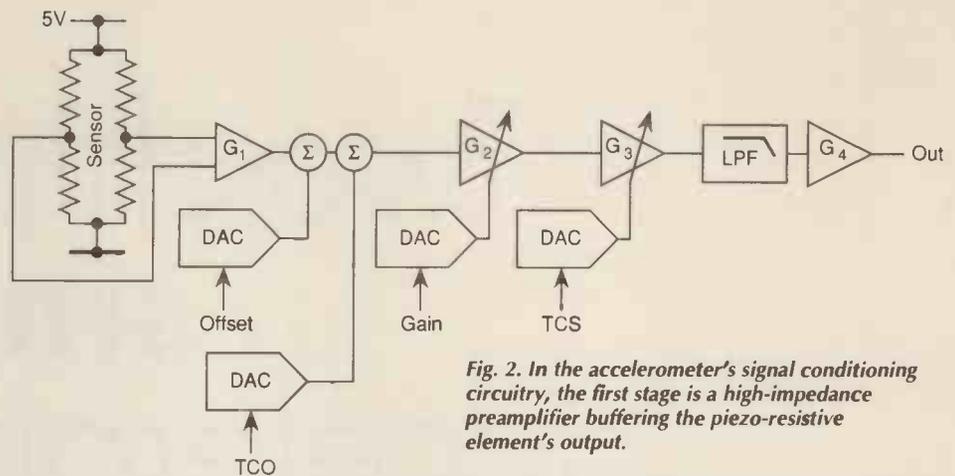

*Fig. 2. In the accelerometer's signal conditioning circuitry, the first stage is a high-impedance preamplifier buffering the piezo-resistive element's output.*

Sensitivity decrease over temperature is compensated by increasing the signal gain linearly with temperature. This method was chosen over a circuit using constant current excitation of the sensor because of the required voltage overhead of the current source. The sensor is now powered with the entire available supply voltage, maximising its signal.

- Output bias voltage can be set to either 0.5V or 2.5V by connecting an input pad on the chip to ground during assembly of the part. This allows signals to be processed with either a bipolar or unipolar range.

- A two-pole passive filter removes signals generated by the internal oscillator and switched capacitor networks. Switching noise is further minimised by having separate digital and analogue internal supply lines and by the differential signal processing.

- A low impedance output for driving resistive and capacitive loads without influencing the signal is provided by the final stage. The output enters a high impedance state if the device is not addressed.

**Error detection functions**


Because the accelerometer is intended to be used in safety-critical applications, such as airbag deployment, several features are incorporated to detect a failure of the accelerometer or circuitry.

It is important to prevent floating signals because the resulting output voltage might look like a crash signal and activate the air bag. Such signals could be caused by a discontinuity between the sensor and the circuit or by a malfunction of the sensor itself. Small current sources have been added between each of the signal inputs and the positive supply.

In case one or both of the inputs are open, output voltage is forced to the positive supply. In addition, two window comparators monitor the voltage at both inputs. If the voltage at one or both inputs exceeds the allowed range, an 'alarm' output pin is made high. This output can be monitored by a microprocessor to alert the user to a malfunction of the sensor.

In addition, the sensor has a built-in self-test function which allows the seismic mass to be

Number of sensors	Required number of lines	
	Non-multiplexed	Multiplexed
2	4	6
4	10	8
9	20	10
16	34	12
25	52	14

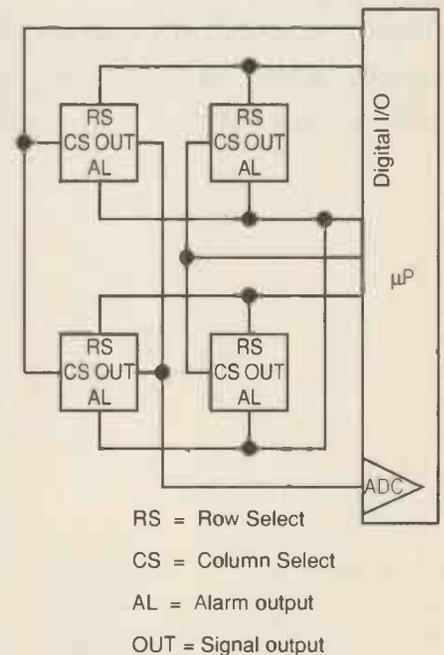

*Fig. 3. Control signals and i/o lines are structured so that multiple accelerometers can be accessed via the same bus.*

moved by means of an externally applied voltage. This allows the entire device to be tested, including the mechanical structure of the sensor and the signal conditioning electronics.

By applying a voltage to the bond pad that is connected to the self-test electrode, the output will exhibit a voltage change which is proportional to the full scale output, in contrast to

other self-test schemes where the output change is fixed. This makes it possible to verify not only complete malfunction of the device but also a parametric error, giving a better indication of a partial or a developing failure.

### Accessing the device

Addressing capabilities have been incorporated in the signal conditioning electronics in the form of row-select and column-select digital inputs.

Both input lines must be high for the accelerometer to be selected. If one or both of the select lines are in the low state, the signal and alarm outputs are in a high impedance 'tri-state' mode. This allows the outputs of multiple accelerometers to be connected together, Fig. 3, eliminating the need for analog multiplexers and reduces wiring.

The reduced number of wires is an advantage if four or more devices are needed in a system. The following table shows the number of lines – including supply and ground – required in a measurement system with sen-

sors used in non-multiplexed and multiplexed mode. The digital control lines could be driven by custom designed logic, a card that plugs into a computer, or the i/o port of a microprocessor.

The digital inputs and outputs used during testing and trimming are disabled if the device is not selected, and can therefore be bussed together. This greatly simplifies the test hardware if the accelerometers are characterised and trimmed in an array configuration.

In the case of single-sensor operation, or if multiplexing is not desired, the row and column-select inputs can be left open. Internal pull-up current sources ensure that the accelerometer is selected when these inputs are not connected.

### Electrical trimming

Optimal trim values for offset, tco, gain and tcs are different for each sensor. Often a network of thick or thin film resistors is used to set these coefficients. In that case, the desired resistor values are set by laser trimming after characterisation of the untrimmed sensor. This requires a separate trim operation using expensive equipment.

Any additional packaging steps done after trimming, sealing the substrate in a housing, for example, could change the characteristics of the sensor resulting in sensitivity or offset errors. Furthermore, trimmable resistors and the conductive traces connecting them to the electronics take up space and limit the available packaging options.

To avoid these disadvantages the trimming is done internal to the signal conditioning IC. The trim coefficients for offset, tco, gain and tcs are stored in binary registers which are connected to d-to-a converters that manipulate the signal.

In contrast to some designs that require an additional eeprom containing the coefficients, the storage registers are on the same chip as the signal conditioning electronics. The storage registers are made in fuse technology to assure data retention in safety-critical applications.

Before trimming data is permanently programmed into the fused registers, the accelerometer can be operated using data stored in volatile ram registers. This allows for the characterisation of the sensor and electronics during manufacturing in order to extract the required coefficients for offset, tco, gain and tcs.

Fuse trimming is handled by circuitry inside the signal conditioning IC and requires no external equipment. The digital i/o used for characterisation and trim consists of a serial input and a serial output line and a clock input for synchronising the data entry, which uses a 16-bit protocol.

All digital i/o lines are available after final packaging. This allows the accelerometer to be trimmed as the last manufacturing step. Because the data transfer is serial rather than parallel, the pin count is not the limiting factor for the package size.

### Packaging details

The package is a leadless chip carrier measuring 0.530in by 0.300in and is 0.150in thick. It is manufactured by screening tungsten interconnect traces onto ceramic layers which are then stacked together and fired.

The accelerometer die and signal conditioning IC are mounted into the package cavity and connections are made from the die to the package with gold-wire bonds. A gold plated Kovar lid is then soldered to the package using a Au/Sn preform. This provides a hermetic seal which will withstand the rigorous environmental requirements of the automotive and military industries.

Reliability is increased with respect to many other designs because of the reduced number of components. No external components such as capacitors are needed for operation. Stiffness and low mass of the package helps to keep its resonant frequency high. Inputs and outputs needed for operation of the accelerometer and for characterisation and trim are brought out to contact pads on the side and on the bottom of the package, Fig. 4.

Mounting surface 2 is on the opposite side from the metal lid. Because electrical contact can be made on two surfaces and because of the aspect ratio of the package, it is possible to mount the package either flush with or perpendicular to the board.

In many cases accelerometers need to be mounted at a 90° angle with respect to the circuit board. This normally requires additional brackets and is not compatible with automated manufacturing. The ceramic package allows the accelerometer to be mounted on the pcb using automatic placement equipment, reducing manufacturing cost and saving space.

Another possible application is to make a tri-axial accelerometer by mounting two accelerometers perpendicular to the board and one in parallel, Fig. 5. Dimensions of this fully signal conditioned tri-axial accelerometer is only 0.73in by 0.53in by 0.30in.

The accelerometer is available in several g ranges to cover many applications such as ride control, airbag deployment – both frontal and side impact – fusing and arming, vibration monitoring and general instrumentation.

In addition, it is possible to adapt the device to specific customer needs. ■

This article is based on a paper presented at Sensors Expo, Cleveland Ohio; contact <http://www.sensorsmag.com>

### References

1. Self-testable Accelerometer Systems. Henry V. Allen, Stephen C. Terry and Diederik W. de Bruin, Proceedings of IEEE Micro Electro Mechanical Systems, IEEE catalogue no 89TH0249-3, February 1989, pp. 113-115.
2. Accelerometer Systems with Built-in Testing. Henry V. Allen, Stephen C. Terry and Diederik W. de Bruin, Abstracts of Transducers '89; The 5th International Conference on Solid-State Sensors and Actuators, June 1989, pp.148-149.

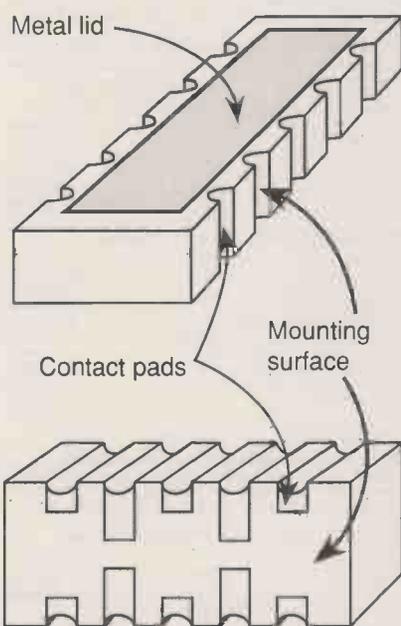


Fig. 4. Stiffness and low mass of the accelerometer's surface-mount package helps keep its resonant frequency high.

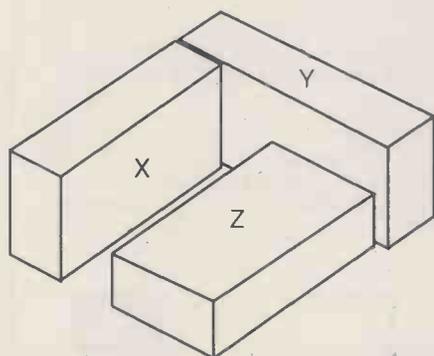


Fig. 5. Orienting three sensors in this way forms a tri-axial accelerometer.

## COMPUTER ICs

TMS990NL-40 PULLS	£20 ea
S9900 NEW AMD EQUIVALENT	£30 ea
MC6802 PROCESSOR	£2 ea
AM27C020-12S1 SURFACE MOUNT EPROM USED/WP/ED	£1.50
MX16C450 UART	£2
P8271 BBC DISC CONTROLLER CHIP EX EOPT	£25
2817A-20 (2Kx8) EEPROM ex ept.	9 FDR £5
D41256C-15 256Kx1 PULLS	£5
P8749H MICRO	£10
D8751-8 NEW	£10
MK4802-20 ZERO POWER RAM EQUIV 6118LP	£4
USED 4164-15	60p
BBC VIDEO ULA	£10
8051 MICRO	£1.25
FLOPPY DISC CONTROLLER CHIPS 1771	£16
FLOPPY DISC CONTROLLER CHIPS 1772	£17.50
68000-8 PROCESSOR NEW	£6
HD6384-8	£5
ALL USED EPROMS ERASED AND BLANK CHECKED	
2716-45 USED	£2 100/£1
2732-45 USED	£2 100/£1
2764-30 USED	£2 100/£1.60
27C256-30 USED	£2
27C512 USED	£2.50
1702 EPROM NEW	£6
2114 EX EOPT	50p 4116 EX EOPT
6284-15 8K STATIC RAM	£1.50
280A SIO-O	£1.25
7126 3 1/2 DIGIT LCD DRIVER CHIP	£2 ea
USED 16A-30 HOUSE MARKED	£2
USED TMS2532JL	£2.50 2708 USED
HM6181P-9	£2
68000-10 PROCESSOR	65p
8255-5	£5
2114 CMOS (RCA 5114)	£1.40
WD16C550-PC UART	£1.60
ZN427E-8	£5
ZN427E-8	£4
ZN427E-26 USED	£1.50

## REGULATORS

LM338K	£6
LM323K 5V 3A PLASTIC	£3
LM323K 5V 3A METAL	£3
LM350K (VARIABLE 3A)	£3
78H12ASC 12V 5A	£5
LM317H TOS CAN	£1
LM317T PLASTIC TO220 variable	£1
LM317 METAL	£2.20
7812 METAL 12V 1A	£1
7815/12/15/24	30p
7905/12/15/24	30p
CA3085 TO99 variable reg	2/£1
78H05ASC+78H05ASC REGULATORS	£30 ea
LM123 2S93 5V 3A TO3 REGS	£3 ea
UC3524AM SWITCHING REGULATOR IC	60p
78L12 SHORT LEADS	10/£1
LM2950ACZ5.0	60p

## CRYSTAL OSCILLATORS

307.2KHZ 1M000000 1M8432 2M457600 3M6864 4M000000	
5M000000 5M068000 5M760000 6M000000 6M1440 7M000000	
3M372800 7M5 8M000000 9M216 10M000 10M0 12M000000 14M318	
14M3818 16M00 17M625600 18M000000 18M432 19M050 19M32	
19M440 20M000 20M0150 21M676 22M1184 23M587 24M0000	
25M1748 25M175 25M 1889 27M + 36M 27M000000 28M322	
32M000000 32M0000 *S/MOUNT 33M3330 35M4816 38M100	
40M000 41M539 42M000000 44M444 44M900 44M0 48M000000	
50M00 55M000 56M00920 64M000000 66M667 76M1 80M0	
84M00	£1.50 ea

## CRYSTALS

32K768 1MHZ 1M8432 2M0000 2M1432 2M304 2M4576 3M000	
3M2768 3M400 3M579545 3M58564 3M600 3M6864 3M93216	
4M000 4M190 4M194304 4M2056 4M433614 4M608 4M9152 5M0000	
5M0688 6M000 6M041952 6M200 6M400 7M37280 8M000 8M06400	
8M448 8M863256 8M8670 9M3750 9M8304 10M240 10M245	
10M368 10M70000 11M000 11M052 11M98135 12M000 12M5	
13M000 13M270 13M875000 14M000 14M318 14M7450 14M7456	
15M0000 16M000 17M625018M432 18M432 20M000 21M300	
21M400015A 24M000 25M000 26M995 27M045 RD 27M095 OR	
27M145 BL 27M145 YW 27M195 GN 28M4696 30M4696 31M4696	
31M4696 34M368 36M75625 36M76875 36M78125 36M79375	
36M80625 36M81875 36M83125 36M84375 38M900 48M000	
51M05833 54M1916 55M500 57M7416 57M7583 69M545 69M550	
96M000 111M800 114M8 120M000	£1 ea

## TRANSISTORS

MPSA42	10/£1
MPSA92	10/£1
2N2907A	10/£1
BC477, BC488	10/£1
BC107 BC170 PREFORMED LEADS	
full spec	£1 £4/100 £30/1000
BC557, BC236C, BC308B	£1/30 £5.50/100
2N2907 PLASTIC CROPPED	£1/15 £4/100
BC548B SHORT LEADS	£3/100 £20/1000

## POWER TRANSISTORS

OC29	£2 ea
2SC1520 sim BF259	3/£1 100/£22
TIP 141/2 £1 ea TIP 112/42B	2/£1
IRF620 TO-220 12A 200V	2/£1
SE9301 100V 1DA DARL SIM TIP121	2/£1
BD680	4/£1
PLASTIC 305S OR 2955 equiv 50p	100/£35

## TEXTLOO ZIF SOCKETS

28 PIN USED	£3
40 PIN NEW	£10
SINGLE IN LINE 32 WAY CAN BE GANGED FOR USE WITH ANY DUAL IN LINE DEVICES	COUPLING SUPPLIED 2/£1.50

## MISCELLANEOUS

XENON STROBE TUBE	£1.60
Narrow angle infra red emitter LED55C	2/£1
UM6116M-2L surface mount 1000 available	£1
CNY85 OPTO ISOL 3000 available	50p
DP10 ICs also available TLP550 TLP666GF	
68 way PLCC SKT 1500 available	£1 each
100 wa PLCC SKT 100 available	£1.50 each
12500PF POSTAGE STAMP COMPRESSION TRIMMER	£1
LM324 (Quad 741)	4/£1
MINIATURE FERRITE MAGNETS 4x4x3mm	10/£1
TL071 LO NOISE OP AMP	5 for £1
TL081 OP AMP	4 for £1
47000u 25V SPRAGUE 36D	£3.50 (£2)
12 way dil sw	£3 for £1
10NF 63V X7R PHILIPS SURFACE MOUNT 100K available	
SWITCHED MODE PSU 40 WATT UNCASED QTY. AVAILABLE +5V 5A, +12V 2A, 12V 500mA FLOATING	£30/4000
220R 2.5W WIREWOUND RESISTOR 60K AVAILABLE	£9.95 (£2)
CMOS 555 TIMERS	£50/1000
23 AA LITHIUM cells as used in compact cameras	2/£1.50
PASSIVE INFRA RED SENSOR CHIP + MIRROR + CIRCUIT	£2 ea
EUROCARD 28-SLOT BACK PLANE 96/96-WAY	£25 ea
EUROCARD 96-WAY EXTENDER BOARD	£10 ea
290x100mm	
DIN 41612 96-WAY A/B/C SOCKET PCB RIGHT ANGLE	£1.30
DIN 41612 96-WAY A/B/C SOCKET WIRE WRAP PINS	£1.30
DIN 41612 64-WAY A/C SOCKET WIRE WRAP PINS	£1
DIN 41612 64-WAY A/C PLUG PCB RIGHT ANGLE	£1
DIN 41612 64-WAY A/B SOCKET WIRE WRAP (2-ROW BODY)	£1
BT PLUG+LEAD	3/£1
MIN. TOGGLE SWITCH 1 POLE c/o PCB type	5/£1
LCD MODULE sim. LM018 but needs 150 to 250V AC for display 40x2 characters 182x35x13mm	£10
6-32 UNC 5/16 POZI PAN SCREWS	£1/100
NUTS	£1.25/100
PUSH SWITCH CHANGEOVER	2/£1
RS232 SERIAL CABLE D25 WAY MALE CONNECTORS	
25 FEET LONG, 15 PINS WIRED BRAID + FOIL SCREENS	£5.90 ea (£1.30)
INMAC LIST PRICE £30	
AMERICAN 23 PIN CHASSIS SOCKET	2/£1
WIRE ENDED FUSES 0.25A	30/£1
NEW ULTRASONIC TRANSDUCERS 32kHz	£2/pr
POWERFUL SMALL CYLINDRICAL MAGNETS	3/£1
BNC 50OHM SCREENED CHASSIS SOCKET	2/£1
SMALL MICROWAVE DIODES AE1 OC1026A	2/£1
D.I.L. SWITCHES 10-WAY £1 8-WAY 80p 4/5/6-WAY	80p
180VOLT 1 WATT ZENERS also 12V & 75V	20/£1
MIN GLASS NEONS	10/£1
RELAY 5V 2-pole changeover looks like RS 355-741 marked STC 47WBot	£1 ea
MINIATURE CO-AX FREE PLUG RS 456-071	2/£1
MINIATURE CO-AX PCB SKT RS 456-093	2/£1
PCB WITH 2N2846 UNIJUNCTION WITH 12V 4-POLE RELAY	£1
400 MEGOHM THICK FILM RESISTORS	4/£1
STRAIN GAUGES 40 ohm Foil type polyester backed baloo grid alloy	£1.50 ea 10+ £1
ELECTRET MICROPHONE INSERT	2/£1
Linear Hall effect IC Micro Switch no 613 554 sim RS 304-267	
£2.50 100 + £1.50	
1 pole 12 way rotary switch	4/£1
AUDIO ICs LM380 LM386	£1 ea
555 TIMERS £1 741 OP AMP	6/£1
ZN414 AM RADIO CHIP	80p
COAX PLUGS nice ones	4/£1
COAX BACK TO BACK JOINERS	3/£1
INDUCTOR 20µH 1.5A	5/£1
1.25" PANEL FUSEHOLDERS	3/£1
12V 1.2W small w/e lamps fit most modern cars	10/£1
STEREO CASSETTE HEAD	£2
MONO CASS. HEAD £1 ERASE HEAD	50p
THERMAL CUT OUTS 50 77 85 120°C	£1 ea
THERMAL FUSES 220°C/121°C 240V 15A	5/£1
TRANSISTOR MOUNTING PADS TO-5/TO-18	£3/1000
TO-3 TRANSISTOR COVERS	10/£1
PCB PINS FIT 0.1" VERO	200/£1
TO-220 micas + bushes	10/50p 100/£2
TO-3 micas + bushes	10/£1
Large heat shrink sleeving pack	£2
IEC chassis plug filter 10A	£3
POTS SHORT SPINDLES 2K5 10K 25K 1M 2M5	4/£1
40K U/S TRANSDUCERS EX-EOPT NO DATA	£1/pr
LM335Z 10Mv/degree C	£1
LM234Z CONST. CURRENT I.C.	£1
BNC TO 4MM BINDING POST SIM RS 455-961	£1
MIN PCB POWER RELAYS 10.5V COIL 6A CONTACTS 1 pole c/o	£1
BANDOLIERY COMPONENTS ASSORTED Rs, Cs, ZENERS	£5/1000
LCD MODULE 16 CHAR. X 1 LINE (SIMILAR TO HITACHI LM10)	£5
OPT1264A 10KV OPTO ISOLATOR	£1.35 ea 100 + £1 ea
"LOVE STORY" CLOCKWORK MUSICAL BOX MECHANISM MADE BY SANKYO	£1 ea
Telephone cable clips with hardened pins	500/£2
10,000uF 16V PCB TYPE 30mm DIA/31mm	2/£1
EC CHASSIS FUSED PLUG B-LEE L2728	3/£1
2A CERAMIC FUSE 1.25" QB	10/£1
48 WAY IDC RIBBON CABLE 100 FOOT REEL	£5 + CARR
20mm PCB FUSEHOLDER	5/£1
IEC CHASSIS FUSED PLUG B-LEE L2728	3/£1
ASTEC MODULATOR VIDEO + SOUND UM1287	£2.25
BARGRAPH DISPLAY 8 RED LEDS	£1.50
NE567 PHASE LOCKED LOOP	2/£1
NE564	£1
TL084	4/£1
IR2432 SHARP 12 LED VU BAR GRAPH DRIVER	£1.25

## DIODES AND RECTIFIERS

A115M 3A 600V FAST RECOVERY DIODE	4/£1
1N5407 3A 1000V	8/£1
1N4148	100/£1.50
1N4004 5D4 1A 300V	100/£5
1N5401 3A 100V	10/£1
1N5819RL 20K Ex stock	1000 + 10p
BA158 1A 400V fast recovery	100/£3
BY254 300V 3A	8/£1
BY255 1300V 3A	6/£1
6A 100V SIMILAR M7751	4/£1
1A 600V BRIDGE RECTIFIER	4/£1
4A 100V BRIDGE	3/£1
6A 100V BRIDGE	2/£1
10A 200V BRIDGE	£1.50
25A 200 V BRIDGE £2	10/£18
25A 400V BRIDGE £2.50	10/£22
BY297	10/£1
KBPC304 BRIDGE REC 3A 400V	4/£1

## SCRs

PULSE TRANSFORMERS 1:1 +1	£1.25
TICV106D 800mA 400C SCR 3/£1	100/£15
MEU21 PROG. UNIJUNCTION	3/£1

## TRIACS

NEC TRIAC ACO8F 8A 600V TO220	5/£2 100/£30
TXAL225 8A 500V 5mA GATE	2/£1 100/£35
BTA 08-400 ISO TAB 400V 5mA GATE	90p
TRAL2230D 30A 400V ISOLATED STUD.	£5 ea
TRIAC 1A 800V TOLC3811 16K AVAILABLE	5 FOR £1 £15/100

## PHOTO DEVICES

HI BRIGHTNESS LEDS COX24 RED	5/£1
SLOTTED OPTO-SWITCH OPCOA OPB815	£1.30
2N5777	50p
TIL81 PHOTO TRANSISTOR	£1
TIL38 INFRA RED LED	5/£1
4N25, OP1225 OPTO ISOLATOR	50p
PHOTO DIODE 50P	6/£2
MEL12 (PHOTO DARLINGTON BASE n/c)	50p
LED's RED 3 or 5mm 12/£1	100/£6
LED's GREEN OR YELLOW 10/£1	100/£6
FLASHING RED LED 5mm 50p	100/£40
HIGH SPEED MEDIUM AREA PHOTODIODE RS651-995	£10 ea
OPTEK OPB745 REFLECTIVE OPTO SENSOR	£1.50
RED LED - CHROME BEZEL	3/£1
OP110B HI VOLTAGE OPTO ISOLATOR	£1
MOC 3020 OPTO COUPLED TRIAC	2/£1

## STC NTC BEAD THERMISTORS

G22 220R, G13 1K, G23 2K, G24 20K, G54 50K, G25 200K, RES 20°C DIRECTLY HEATED TYPE	£1 ea
F522BW NTC BEAD INSIDE END OF 1" GLASS PROBE RES 20°C 200R	£1 ea
A13 DIRECTLY HEATED BEAD THERMISTOR 1k res. ideal for audio Wien Bridge Oscillator	£2 ea

## CERMET MULTI TURN PRESETS 3/4"

10R 20R 100R 200R 250R 500R 2K 2K2 2K5 5K 10K 47K 50K 100K 200K 500K 2M	50p ea
---	--------

## IC SOCKETS

14/16/18/20/24/28/40-WAY DIL SKTS	£1 per TUBE
8-WAY DIL SKTS	£2 per TUBE
32-WAY TURNED PIN SKTS	3 for £1
SIMM SOCKET FOR 2x30-WAY SIMMS	£1

## POLYESTER/POLYCARB CAPS

330nF 10% 250V AC X2 RATED PHILIPS TYPE 330	£20/100
100n, 220n 63V 5mm	20/£1 100/£3
10n/15n/22n/33n/47n/66n 10mm rad	100/£3 50
100n 250V radial 10mm	100/£3
100n 600V Sprague axial 10/£1	100/£5 (£1)
2µ2 160V rad 22mm, 2µ2 100V rad 15mm	100/£10
10n/33n/47n 250V AC r rated 15mm	10/£1
1µ 50V MIXED DIELECTRIC	50p ea
1µ 100V rad 15mm, 1µ 22mm rad	100/£6
0.22µ 250V AC X2 RATING	4/£1
0.22µ 900V	4/£1

## RF BITS

SAW FILTERS SW662/SW661 PLESSEY SIGNAL TECHNOLOGY	
379.5 MHZ	£1.50 ea
FX3286 FERRITE RING ID 5mm OD 10mm	10 for £1
ASTEC UM1233 UHF VIDEO MODULATORS (NO SOUND) 1250 STOCK	£1.50
MARCONI MICROWAVE DIODES TYPES DC2929, DC2962, DC4229F1/F2	£1 EA
XTAL FILTERS 21M4 55M0	£2 ea
ALL TRIMMERS	3 for 50p
VIOLET	5-105pF
RED 10-110pF GREY 5-25pF SMALL MULLARD	
2 to 22pF	3 FOR 50p 100/100
TRANSISTORS 2N4427, 2N3866	80p ea
CERAMIC FILTERS 4M5/6M9M/10M7	60p ea
FREED THRU CERAMIC CAPS 1000pF	10/£1
SL610	£5
6 VOLT TELEDYNE RELAYS 2 POLE CHANGEOVER (BF51 TRANSISTOR CAN SIZE)	£2
2N2222 METAL	5/£1
P2N2222A PLASTIC	10/£1
2N2369A	5/£1
74N16 TACS CAR PHONE O/P MODULE	
EQUIV MHW806A-3 RF IN 40mW O/P 6→8w 840→910MHz	£3 ea

## MONOLITHIC CERAMIC CAPACITORS

10n 50V 2.5mm	100/£4.50
100n 50V 2.5mm or 5mm	100/£6
100n ax short leads	100/£3
100n ax long leads	100/£5
100n 50V dl package 0.3" rad	100/£8

## QUARTZ HALOGEN LAMPS

12V 50watt LAMP TYPE M312	£1 ea HOLDERS 60p ea
6V 50watt	£1

# KEYTRONICS

TEL. 01279-505543  
FAX. 01279-757656  
P O BOX 634  
BISHOPS STORTFORD  
HERTFORDSHIRE CM23 2RX

SEND £1 STAMPS FOR CURRENT IC+SEMI STOCK LIST - ALSO AVAILABLE ON 3 1/2" FLOPPY DISK

### MAIL ORDER ONLY

MIN. CASH ORDER £5.00. OFFICIAL ORDERS WELCOME  
UNIVERSITIES/COLLEGES/SCHOOLS/GOVT. DEPARTMENTS  
MIN. ACCOUNT ORDER £10.00  
P&P AS SHOWN IN BRACKETS (HEAVY ITEMS) OTHERWISE 95p

ADD 17 1/2% VAT TO TOTAL  
ELECTRONIC COMPONENTS BOUGHT FOR CASH

CIRCLE NO. 122 ON REPLY CARD

# Telephone caller

**Uses, standards, devices and receiver design for Caller ID – the system that allows you to see the number of the person phoning you – are discussed by Seggy Segaran.**

# ID

The term Caller ID is used to describe the transmission of the caller's telephone number when the telephone rings. This service was introduced by BT at the end of 1994, along with two receiver units.

The *CD50* is a stand-alone battery powered unit with display, that can store details of 50 calls. The *Relate 1000* with combined telephone, is much more sophisticated. Not only can it display the number, but it uses a local directory to look up the name of the caller. It also allows the easy redialling of any of the received numbers.

Currently, the service from BT only delivers the caller's number, the time and date. The enhancement of the service to deliver name has not yet taken place. There is no time scale from BT for this to be available. If the call is from a pay-phone or from abroad, then the text 'payphone' or 'international' is sent. Calls from a significant number of telephones are still delivered as 'number unavailable', presumably because these are connected to older exchanges.

Privacy is an important consideration. Calls from 'ex-directory' lines are delivered as 'number withheld' and so are all calls prefixed with 141. This ensures anonymity for those that require it.

The Caller ID service is only connected on request and there is a quarterly charge. However, the benefits of Caller ID as described below, will surely more than offset this modest charge.

For the domestic user, the service allows screening of incoming calls, which is espe-

cially useful during quality family time. Only expected calls or those from close family members need be answered immediately.

The Caller ID device can also be used as a complement or a replacement for an answering machine. It will record the number of those that tend to hang up as soon as the answering machine message starts to play, and also record the number – even if the call is not answered. The *Relate 1000* allows quick redialling of any of the numbers in the calls log.

For the small business user, the Caller ID service is invaluable. Taxi firms and pizza delivery services are regularly abused by pranksters. With the *CD50*, a simple check of the caller's telephone number with a verbal confirmation can sort these out.

Voluntary organisations can identify malicious callers. They can also identify calls from vulnerable people in trouble, such as emergency calls from disabled or elderly callers. For the tradesman, it allows potential enquiries to be followed up from callers reluctant to use the answering machine.

However, the real benefit to businesses come, when the Caller ID information can be presented to the com port of a pc. This allows the logging of large numbers of calls, instant look up of customer details using the telephone number as a key, and verification of customer identity when releasing sensitive information, such as bank account details.

On another front, the number information can be checked against a stored list of numbers before allowing access to a database, thus providing an effective 'anti-hacking' device.

Companies employing a mobile team, such as cleaning or security staff, can request them to call in from their various sites at the start and the end of their duties. This verifies attendance and time spent at each site. The beauty

## Useful addresses

Solwise, Princes Court, Princes Avenue, Hull HU5 3QA. Tel: 01482 473899, Fax: 01482 472245. Full catalogue on, <http://www.demon.co.uk/solwise/>

Mitel Semiconductors, Mitel Business Park Newport, Gwent NP6 4YR. Tel: 01291 430000, fax: 01291 436389.

Consumer Microcircuits, 1 Wheaton Road, Witham, Essex CM8 3TD. Tel: 01376 513833, fax: 01376 518247

## Useful standards

BT: SIN 227: BT Analogue Caller Display Service- Service description.

BT: SIN242: Calling Line Identification Service- TE requirements.

Available from: Regulatory Services Unit, Room 134, 2 City Forum, 250-258 City Road London EC1V 2TL. Tel: 0800 318601, CTA: TW/P&E/312: Terminal requirements for Caller Display Services, available from: Alan Jones, TeleWest Communications Group, Unit 1, Genesis Business Park, Albert Drive, Woking, Surrey GU21 5RW. Tel: 01483 750900

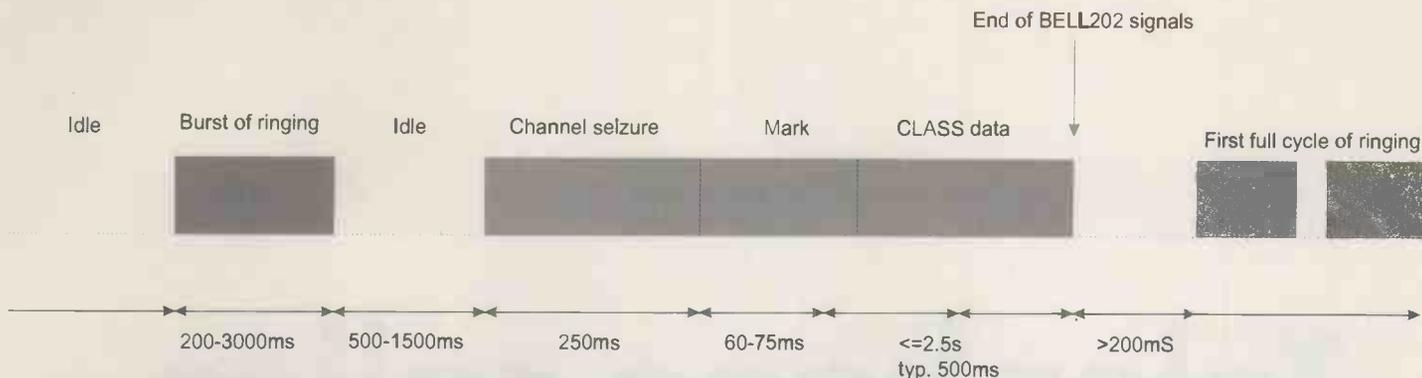


Fig. 1. Timing details for Bellcore's standard for caller ID: data-link layer, on-hook data transmission. Among the first used, this standard was first available in the US.

of this use is that, as the telephone call does not have to be answered, there are no call charges incurred.

**Caller ID – history and standards**

The Caller ID service was first introduced in the US, based on a series of standards from Bellcore. The information is coded using frequency-shift keying signals, fsk, using the Bell 202 standard. This used a 1200Hz signal for a mark, and a 2200Hz signal for a space.

On call arrival, a single ring burst is sent by the exchange, followed by a burst of fsk signal. The data is preceded by a Channel Seizure signal – comprising alternating marks and spaces – and a mark signal. This allows the fsk receiver to synchronise to the data, and to provide immunity against noise spikes. The sequence of events on call arrival is shown in Fig. 1.

The initial ring burst is used by receiving units as a 'wake up' signal. Since these units are battery powered, low power consumption is paramount. The design of the various Caller ID receiver ICs allows the receiver to be placed in a standby mode, with just the ring detector powered. In this mode, current consumption is down to tens of microamps.

On a ring signal being detected, the rest of the IC is powered, and the fsk data is decoded. Since this is done in one or two seconds, and the IC then goes back to low power mode, battery life of a year can be achieved.

**BT's Caller ID service**

This started off with the Bellcore system as its model but diverged along the way. One new requirement for the BT service was that it should be possible to pass information to the

receiving unit, without alerting the phone user. The information was for metering and message waiting status. This precluded the use of the ring signal as being the initial alert signal.

Reversal of line polarity was decided upon as the initial alerting signal. So the 'no ring' call would be presented as line reversal, data, followed by another line reversal. A normal call on the other hand, would be presented as line reversal, data and then ringing.

However, the ringing signal served the purpose of 'wetting' the cable joints, prior to fsk signalling. As there is negligible current flow during a line reversal, the 'wetting pulse' was to be supplied by the receiving unit, before the transmission of the fsk signal.

To ensure that this 'wetting pulse' was applied correctly and in synchrony with other units on multiple installations, another signal was introduced. This was the Tone Alert Signal, or TAS, and was a dual tone of 2130Hz and 2750Hz. After receipt of this, the 'wetting pulse' was to be applied. To ensure good impedance matching during fsk data transmission, the BT standard also calls for an ac impedance during this state.

In addition to the above changes, the BT specification uses V23 frequencies for the fsk signals, which involves 1300Hz for the mark and 2100Hz for the space. The sequence of events for this is shown on Fig. 2. The BT specification also allows for a number of new features to be implemented, and has built in some flexibility for future expansion.

The Caller ID service implemented by cable tv companies is closely modelled on the Bellcore service, in that a single burst of ringing is used to initiate the data. However, V23 frequencies are used for the fsk data and there

is also some allowance in the application layer for future expansion.

**Design of a pc device**

To exploit a niche in the market for Caller ID devices, a project was initiated to produce a unit that would meet two key objectives. First it would allow Caller ID data to be decoded from the telephone line, and presented to the com port of a PC. Secondly, it would supply a Windows utility that would,

- Display call details on the screen as the telephone rings
- Allow name look-up from a pre-programmed directory
- Log all calls in a database format for processing later.

The unit had to be compatible with BT and CTA Caller ID standard and would have to be priced at under £50 to reach the home pc user. With these objectives in mind, the design of the product commenced. After a period of study, the following key design decisions emerged.

First was the choice of Caller ID receiver IC: newly available were two ICs that were capable of meeting both the BT and CTA standards. One was the MT8843 from Mitel Semiconductors and the other was the FX602 from Consumer Microcircuits Ltd. They both had ringing and line reversal detection capability and also circuits for the detection of tone alert signal.

The MT8843 was chosen as samples of these were available earlier. Having decided to make the unit compatible with both standards, the actual wetting pulse and ac impedance cir-

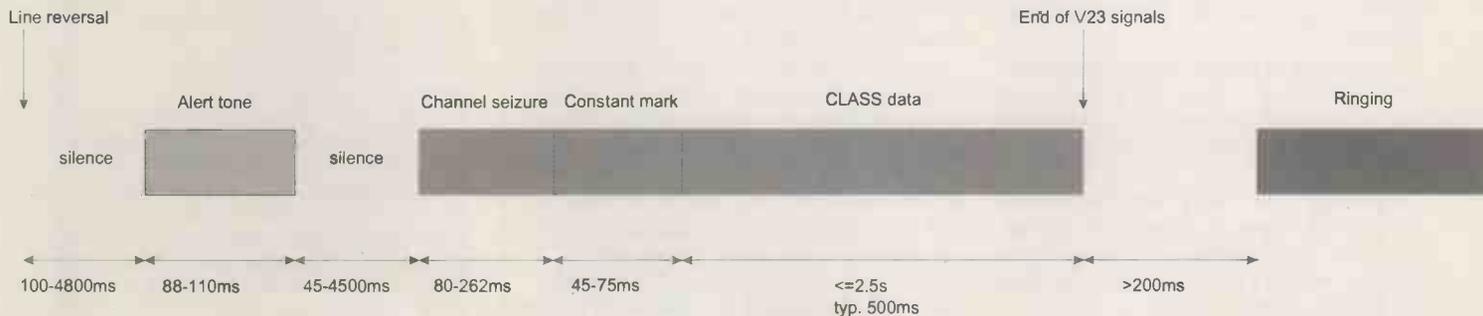


Fig. 2. BT SIN 242: data-link layer, on-hook data transmission, as used for caller telephone number identification throughout most of the UK.

circuits were made optional to save cost. The sensitivity of the receiving circuits were increased to compensate for this.

Powering of the device from a COM port was a key design target, as this would result in lower unit cost. This was made possible by careful design and power management.

To implement the critical timing of the BT standard, to carry out the power management, verification of received data and the serial communication, a Microchip PIC device was used. In addition, a single crystal of 3.579MHz was used as a clock for the PIC and MT8843 devices to keep costs down.

Visual Basic was chosen for the design of the software as this allowed software to be developed quickly and still allowed very professional screens to be displayed to the user.

A block diagram of the electronics is given in Fig 3. A sample of the Window with call details is shown in Fig 4. Following the above decisions and subsequent detailed design, the project was successfully completed and the device, CID-PC1 is now available from SOL-WISE at a cost of £45-00.

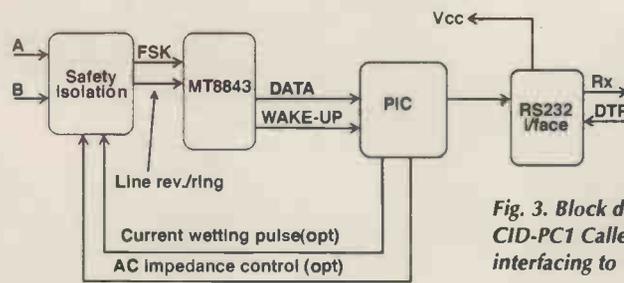


Fig. 3. Block diagram of Tele Products' CID-PC1 Caller ID unit, design for interfacing to the PC.

**Summary**

Caller ID presents many benefits to domestic and business users. The potential of Caller ID

to business users is obvious once the information can be presented to a PC. Above are details of the design of such a unit. ■

**About the author**

T. Segaran is the founder of Tele-products Ltd. The company specialises in the design and manufacture of telecommunications test equipment and the design and approvals of Telecom products. The company has a Caller ID simulator amongst its range of test instruments. This is capable of simulating most Caller ID standards from around the world.

Before founding Tele-Products T. Segaran worked for Standard Telephones and Cables and at Tunstall Telecom as a Section Leader. He has been instrumental in a number of successful product launches including the early Viscount telephone, the Piper Lifeline, the Minstrel, React, Duet and Converse range of telephones.

## Caller ID on a PC – exclusive EW reader offer

Seggy Segaran's Caller ID design, allowing callers' numbers to be read, logged and manipulated on a PC, is being made available to EW readers at a special 15% discount price until 17 May. This self-powered unit is supplied complete with Windows driver software incorporating three key features:

- On receipt of a call, the software produces a Windows pop-up menu with the caller's identification, which can then be cut and pasted.
- Calls are logged in the software's own data base for later manipulation.
- The software's own data base is Microsoft Access compatible.

Normally, the Tele-Products CID-PC1 sells for £45, excluding VAT and carriage. For the duration of the offer, EW readers can obtain the unit for £48.87 – fully inclusive of software, VAT and first-class recorded postage. Simply fill in the coupon below and post it to Dept 74, Tele-Products Ltd, Unit A8, Parkside Commercial Centre, Terry Avenue, York YO2 1JP. Tel 01904 659583, fax 01904 611465.

✂.....

Please send me ..... CID-PC1 Caller ID units for the PC, for which I enclose a postal order or cheque payable to Tele-Products Ltd for the amount £.....

Name .....


Address .....

Post Code .....

Daytime tel .....


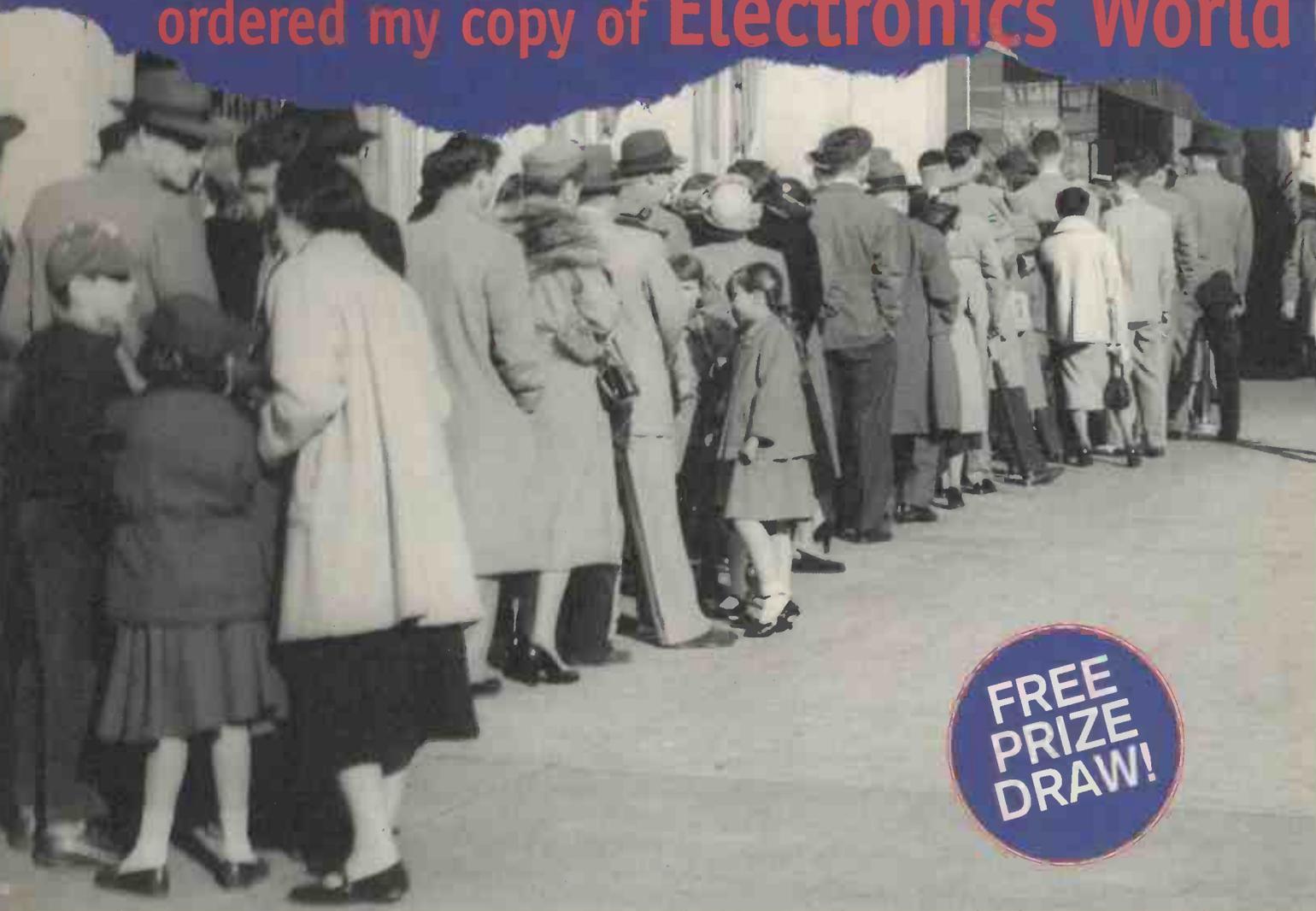
# I knew I should have ordered my copy of **Electronics World**



## Don't miss out!

Place a regular order with your newsagent for your own copy of **Electronics World**. And be entered into our **Free Prize Draw!** One reader a month will win...

**In April** A **FREE** 11-piece tool kit and a **FREE** copy of "Oscilloscopes" by Ian Hickman, worth £16.99

**In May** A **FREE** 11-piece tool kit and a **FREE** copy of "Modern CMOS Circuits Manual" by R M Marston, worth £14.99

**In June** A **FREE** 11-piece tool kit and a **FREE** copy of "Analogue Circuits Cookbook" by Ian Hickman, worth £19.95

To enter the draw simply fill in the form opposite, ask your newsagent to sign it when you place your regular order for **Electronics World** and send the forms to: **Marketing Department, Electronics World, Reed Business Publishing, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.**

 Name .....

Address .....

.....

.....

.....

Telephone number .....

Signature .....

.....

Newsagent .....

Newsagent's address .....

.....

.....

Newsagent's signature .....

# RADIO DATA MODULES MODEM TRANSCIEVERS

UK, E.E.C, Scandinavia, Eastern Europe, North & South America, Middle East, South Africa, New Zealand, Far East or Australia. Wherever you are, we have a module on the right frequency for you!

**New !: TXR-XXX-DTR100**



Only 55 x 23 x 15mm

- 400 to 500MHz Versions \*
- Range up to 5Km \*
- Compact Size ideal for Hand Helds \*
- UK, North American, Australian \*
- MPT, I-ETS & FCC Approval \*
- Up or 64 selectable channels \*

## Low Voltage Transmitters Simplify Interfacing !

- Available UK Approved MPT1340 418MHz \*
- Export I-ETS-300-220, 433.92MHz \*
- Reduce Component Count, Cost, Size & Power Drain \*
- Twice as fast as the - A version, up to 20,000 bps \*
- 3V or 5V Drives directly from a PIC output Port III \*



TXM-418-F Transmitter

## Exclusive : South African Modules on 403MHz

- TXM-403-A, SILRX-404-A, RXM-403-A \*
- High Quality FM system > 120M Range \*
- Evaluation Kits Available \*
- No Price Surcharge \*
- Eg : 1000 + TXM's Only £5.95 Each \*



RXM-403-A

## VHF Modules for UK, Australia and Beyond !

- UK, 173MHz to MPT1344 & MPT1328 Licence Exempt \*
- Miniature Low Cost 1 & 10mW Transmitters \*
- 173.500MHz Transmitters & Transceivers for Australia \*
- PCB mount or canned, Superhet Receivers \*
- Low Cost Meter Reading Transceivers on 183.8875MHz \*




RXM-173/183-4666-60

We have over 60 models / frequencies of radio module in stock. Please contact our sales office for a free catalogue.

**Radio - Tech Limited, Overbridge House, Weald Hall Lane  
Thornwood Common, Epping, Essex CM16 6NB.  
Sales +44 (0) 181 368 8277 Fax +44 (0) 181 361 3434  
Int'l +44 (0) 1992 57 6107 Fax +44 (0) 1992 56 1994**

CIRCLE NO. 123 ON REPLY CARD

# MARCONI 2370 Spectrum analyser

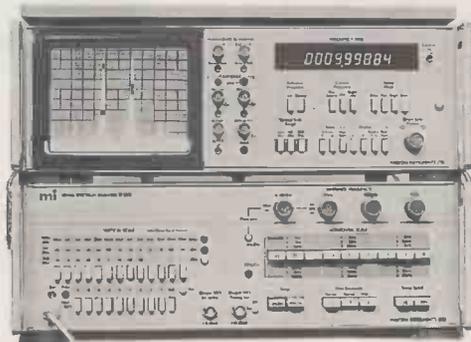

**30Hz - 110MHz Frequency range  
1Hz Resolution/phase lock tuning  
Digital storage with dual display  
Built-in tracking generator  
9 digit frequency counter**

**£850** + carriage/vat

**Includes 30 day unconditional warranty**

**M&B Radio, 86 Bishopgate Street, Leeds LS1 4BB**

**Tel: (+44) 0113 2435649**

**Fax: (+44) 0113 2426881**

CIRCLE NO. 124 ON REPLY CARD

# M & B RADIO (LEEDS)

THE NORTH'S LEADING USED TEST EQUIPMENT DEALER

## OSCILLOSCOPES

HP 5411D 500 MHz digitizing scope (colour display)	£3500
TEKTRONIX 2465 300 MHz 4 channel	£2000
TEKTRONIX 2230 100 MHz digital storage scope	£2250
TEKTRONIX 2220 60 MHz digital storage scope	£1800
TEKTRONIX 222 10 MHz portable digital storage scope (new)	£950
TEKTRONIX 7844/7A24/7A19/7B78/7B80 (600MHz/2x 400MHz)	£1250
TEKTRONIX 2213 60 MHz dual trace	£400
TEKTRONIX 2215 60 MHz dual trace/delayed TB	£450
TEKTRONIX 475 200 MHz dual trace	£495
TEKTRONIX 465B 100 KHz 2 channel	£435
TEKTRONIX 434 25 MHz 2 channel storage	£400
TEKTRONIX 5C504/TM504/DM501 80 MHz scope/DVM	£450
TEKTRONIX 212 500 KHz handheld battery portable scope	£495
BALLANTINE 1022B 25 MHz miniscope	£225
PHILIPS 3055 50 MHz dual trace	£425
PHILIPS 3057 50 MHz dual trace	£495
PHILIPS 3217 50 MHz dual trace	£375
PHILIPS 3244 50 MHz 4 channel oscilloscope	£400
IWATSU 556122 100 MHz 4 channel with cursors	£600
IWATSU 555710 60 MHz channel	£460
LEADER LB0594L 40 MHz dual trace delayed tb	£300
GOULD OS300 20 MHz dual trace	£200
GOULD OS4000 10 MHz digital storage	£195
UNA0HM G508 DT 20 MHz compact dual trace scopes + probes	£160

## SPECTRUM ANALYSERS

TEKTRONIX 2710 10 KHz-1.8 GHz	£4000
TEKTRONIX 2710 10 KHz-1.8 GHz OPT 001/003/014 new unused	£2250
TEKTRONIX 7L12 10 KHz-1.8 GHz + mainframe	£2000
HP 8410/8411A network analyser 110 MHz-12.4 GHz	£1000
HP 8569A/B 100 MHz-22 GHz spectrum analyser	£4500
HP 8903A 20 Hz-100 KHz audio analyser	£2000
HP 8754A 4 MHz-1300 MHz network analyser	£2000
HP 3580A 5 Hz-50 KHz audio analyser	£850
HP 407/8552B/8553B 1 KHz-110 MHz spectrum analyser	£450
HP 141T/8552B/8554B 100 KHz-1250 MHz	£1000
HP 141T/8552B/8555A 10 MHz-18 GHz	£1700
MARCONI TF2370 30 Hz-110 MHz spectrum analyser	£850

## SIGNAL GENERATORS

HP 8672A 2 GHz-18 GHz synthesized signal generator (new)	£6000
HP 8683D 2.3 GHz-13 GHz OPT 001/003 solid state generator (new)	£2950
HP 8620C/86290B 2 GHz-18 GHz sweeper	£2950
HP 8620C/86290B 1.8 GHz-4.2 GHz sweeper	£1000
HP 8620C sweeper mainframes (as new)	£250
HP 3325A frequency synthesizer 1 uHz-110 MHz (HB-IB)	£1500
HP 3312A function generator 0.1 Hz-13 MHz	£400
HP 3586C 50 Hz-32.5 MHz selective level meter	£1750
HP 3314A 0.001 Hz-19.99 MHz function/waveform generator	£2950
HP 9904A DC-600 KHz multifunction synthesizer	£4000
HP 3336B 10 Hz-21 MHz synthesizer level meter	£650
HP 8640A 500 KHz-1024 MHz signal generator OPT 002	£750
HP 8640A comb generator	£250
HP 214A high power pulse generator 10 Hz-10 MHz OPT 001	£750
HP 5005A 0.3 Hz-20 MHz pulse generator	£400
HP 8015B 1 Hz-50 MHz dual output pulse generator	£500
HP 1121A 50 MHz programmable pulse generator	£1200
HP 8616A 1.8 GHz-4.5 GHz signal generator	£150
TEKTRONIX 2901 time mark generator	£300

FLUKE 601A 10 Hz-11 MHz synthesized signal generator	£90A
RHODES & SCHWARTZ APN62 0.1 Hz-260 KHz LF gen (new)	£2000
FARNELL SSC2000 10 KHz-2000 MHz synthesized gen (as new)	£2000
FARNELL DSG 0.001 Hz-10 MHz synthesized (new)	£200
SYSTEM DONNER 1702 100 KHz-1000 MHz synthesized gen	£650
WILTRON 410D/501 1 MHz-1500 MHz sweeper	£750
GIGA GR101A 12 Hz-18 GHz pulse generator (as new)	£650
POLARAD 1105EL 800 MHz-2.4 GHz signal generator	£500
POLARAD 1106ET/1929T 1.8 GHz-4.8 GHz with modulator	£500
MARCONI TF2019A 80 KHz-1040 MHz synthesized	£2000
MARCONI TF2015/2171 10 MHz-520 MHz (with synchronizer)	£450
MARCONI TF2016 10 KHz-120 MHz (£250) TF2016A	£295
MARCONI 6055B 850 GHz-150 GHz signal source	£225
MARCONI 6056B 2 GHz-2 GHz signal source	£225
PHILIPS PM5190 LF Synthesizer 1uHz-2 MHz digital	£375
ADRET 2230A 200 Hz-1 MHz synthesized source	£195
LINSTEAD Q1000 10 MHz-10 MHz synthesized oscillator	£225
THANDART SG503 0.005 Hz-5 MHz pulse/function generator	£225

## TEST EQUIPMENT

ELECTRO-METRICS EMC-25 MK III Interference analyser 10 KHz-1 GHz	£90A
BALL FRATROM MRT-H rubidium frequency standard	£4000
TRACOR 527E frequency difference meter	£2000
WAVETEK 1018A log lin RF peak power meter DC-26 GHz	£1500
ANRISU MS653 2 GHz error detector	£1500
TEKTRONIX TM500K/DM501 A/TG501/PG506/SG506/SG503/SG504 cal sys	£3750
TEKTRONIX 1141/SPG11/TSG11 pal video generator	£1500
TEKTRONIX 145 gen lock test signal generator	£950
TEKTRONIX 521A vector scope	£350
SONY/TEKTRONIX 308 20 MHz data analyser	£300
TEKTRONIX A6902A isolator	£450
PHILIPS PH567 pal vector scope	£500
SCHLUMBERGER 7702 digital transmission analyser (new)	£750
ROD L M 1000V55 hip tester	£400
SCHLUMBERGER AF405 3 tone generator/modulator	£150
WANDEL & GOLTERMAN P5519 level generator	£650
MARCONI TF2305 mod meter 50 KHz-2.3 GHz (46883-527C)	£2750
MARCONI 6950/6910 10 Hz-20 GHz RF power meter	£850
MARCONI 6593A VSWR indicator	£1495
MARCONI TK237A zero loss probe	£200
MARCONI TF2432A 10 Hz-560 MHz frequency counter	£125
TEKTRONIX TF2700 LCR meter battery portable	£150
EIP 371 18 GHz source locking microwave counter	£950
HP5328A universal frequency counter 2x 100MHz + DVM	£1200
HP5342A 500 MHz-18 GHz frequency counter OPT001/003	£2000
HP5345A 1.5 MHz-26.5 GHz counter/335A/336A+B sensors	£1100
HP435B/8481A/8484A/11708A 10 MHz-18 GHz (new)	£1800
HP435B/8481A 10 MHz-18 GHz RF power meter	£550
HP435A/8482A 100 KHz-4.2 GHz power meter	£395
HP8494B step attenuators 0.1 dB DC-18 GHz	£350
HP 1716A kit (1x 8494B + 1x 8496B) 0.1 dB DC-18 GHz	£90A
HP 1158A attenuator set (4x 8491A DC-18 GHz ATT) 3/6/10/20dB	£500
HP 5087A distribution amplifier (NEW)	£225
HP8477A RF power meter calibrator	£725
HP11683A power meter calibrator	£395
HP463A digital power meters (sensors available POA)	£650
HP3581C 15 Hz-50 KHz selective voltmeter	£600
HP333A distortion analyser	£295
HP11710A down converter	£250

HP3406A true RMS voltmeter (Analogue)	£145
HP1403C true RMS voltmeter (digital)	£195
HP3406A 10 KHz-1200 MHz RF sampling voltmeter with probes	£200
HP3466A 4.5 digit autoranging multimeter	£200
HP3437A 3.5 digit high speed system voltmeter	£200
HP3455A 4 digit digital voltmeter	£495
HP3468A 5.5 digit multimeter/auto cal (LCD)	£400
HP5994A signature analyser	£150
HP5005A signature multimeter	£100
HP6332A system power supply 0-60V/0-50 amp 1000W	£1000
HP6255A dual DC power supply 0-40V/0-1.5 amp	£185
HP6253A dual DC power supply 0-20V/0-3 amp	£200
HP6825A power supply/amplifier -20V to +20V/0-2 amp	£250
HP6248B DC power supply 0-40V/0-30 amp OPT 000/10/040	£500
BIRD 43 RF wattmeters	£100
BIRD 8323 30dB coaxial attenuator 100W	£300
BIRD 8339 30dB coaxial attenuator 2000W	£500
EXACT 334 precision current calibrator	£195
FLUKE 103A frequency comparator	£250
FLUKE 330B prog constant current/voltage calibrator	£450
BALLANTINE 6125C prog time/amplitude test set	£400
BRADLEY 192 oscilloscope calibrator	£500
ALTECH 533X-11 calibrator (1 HP355C/1 HP355D ATT)	£295
REMO DP 11 Hz-100 KHz phase meter (new)	£150
WAYNE KERR CT496 LCR metre battery portable	£475
RADIOMETER TRB11 RLC component comparator	£150
AVO 215-LZ AC/DC breakdown/ionisation tester	£460
FARNELL RB103035 electronic load	£400
FARNELL TMB 10 KHz-1000 MHz true RMS sampling voltmeter	£350
SIEMENS U2303 phosphor meter (new)	£350
SIEMENS D1108 200 KHz-30 MHz level meter	£350
SIEMENS W2108 200 KHz-30 MHz level oscillator	£350
NARDA 3001 460 MHz-950 MHz directional coupler 20dB	£100
NARDA 3041-200 50 MHz-1000 MHz directional coupler 20dB	£125
NARDA 3048-20 3.7 GHz-8.3 GHz 20dB directional coupler	£150
NARDA 3004-10 4 GHz-10 GHz 10dB directional coupler	£175
NARDA 1023 solid state amplifier 8 GHz-12 GHz	£150
SAYROSA AAM 1.5 MHz-2 GHz automatic modulation meters	£195
IWATSU SC7104 10 Hz-1000 MHz frequency counter	£275
RHODES & SCHWARTZ NKS RF power meter	£600
RACAL RA1071 30 MHz receiver	£300
RACAL RA1779/MA 1107 30 MHz receiver	£1700
RACAL 9063 two tone oscillator	£200
RACAL DANA 9914 5 MHz-2000 MHz automatic modulation meter	£300
RACAL DANA 9914M 50 MHz universal counter timer	£95
RACAL DANA 9914 10 Hz-200 MHz frequency counter	£100
RACAL DANA 9915 10 Hz-520 MHz frequency counter	£100
RACAL DANA 9916 10 Hz-520 MHz frequency counter	£155
RACAL DANA 9917 10 Hz-1100 MHz frequency counter	£295
RACAL DANA 9918 10 Hz-1100 MHz universal counter timer	£400
RACAL DANA 9921 10 Hz-3000 MHz frequency counter	£400
RACAL DANA 9921 10 Hz-150 MHz universal counter timer	£495
RACAL DANA 1992 10 Hz-1300 MHz frequency counter	£600
RACAL DANA 6000 microprocessing digital voltmeter	£250
BRUEL & KJAER 2701 phase meter	£500
RACAL RA1071 30 MHz digital multimeter	£400
FLUKE 8506A thermal RMS voltmeter	£90A
FLUKE 5100B calibrator	£90A
FLUKE 5200A programmable AC calibrator	£90A
FLUKE 5205A precision power amplifier	£90A
FLUKE 5440B direct volts calibrator	£90A
RF MICROSYSTEMS INC. AN/TRC-176 VHF/UHF K & L filters	£400

ALL PRICES PLUS VAT AND CARRIAGE - ALL EQUIPMENT SUPPLIED WITH 30 DAYS WARRANTY

**86 Bishopgate Street, Leeds LS1 4BB**

**Tel: (013) 2435649 Fax: (0113) 2426881**

CIRCLE NO. 125 ON REPLY CARD

## SPECIAL OFFERS

SOLARTRON 7045 4.5 digit bench multimeter (battery/mains)	£60
FLUKE 25 High spec digital multimeters with manual/probes (as new)	£70
SMITHS 3" diameter altimeters	£65
SIEMENS PDRM82 portable LCD radiation meters (new)	£250
AVO TYPE 160 valve tester	£150

# CIRCUIT IDEAS

Do you have an original circuit idea for publication? We are giving **£100** cash for the month's top design. Additional authors will receive **£25** cash for each circuit idea published. We are looking for ingenuity in the use of modern components.

## WIN A TTI PROGRAMMABLE BENCH MULTIMETER

*"High accuracy, resolution and bandwidth - performance beyond the capability of handhelds"*



This high-performance bench multimeter could be yours in exchange for a good idea. Featuring a dual display, the 4.5-digit 1705 multimeter resolves down to 10µV, 10mΩ and 0.1µA and has a basic dc accuracy of 0.04%. Frequency measured is 10Hz to 120kHz with an accuracy of 0.01% and resolution to 0.01Hz. Capacitor and true rms measurements are also featured.

Recognising the importance of a good idea, Thurlby Thandar Instruments will be giving away one of these excellent instruments once every six months. This incentive is in addition to our monthly £100 'best circuit idea' award and £25 awards for each circuit published.

### £100 WINNER

## Night/day light measurement in one range

Since the *NORP-12* cadmium sulphide photo-conductive cell obeys a precise log-law ( $\log(R_p) = 4.630 - 0.6761 \log(L)$ , where  $R_p$  is the cell resistance at  $L$ lux), a low-bias-current op-amp with a log-diode in the feedback loop will give an accurate light reading from moonlight to sunlight in one range. Furthermore,

the technique is inherently proof against overload and is inexpensive.

Op-amp  $A_1$  drives a 100µA meter, on which zero is equivalent to 0.1lux and full scale to  $10^4$  lux. Since  $\log_2$  is 0.301 and  $\log_5$  is 0.699, the meter scale may be calibrated in a 1-2-5 sequence in these proportions. If a laboratory standard lamp is available,


calibrate the meter at 1 lux and 1000lux by the trimmers  $VR_1$  and  $VR_2$ ; if not, first replace  $R_p$  with 42.7kΩ and then 400Ω, these being the resistance values from the *NORP-12* data sheet which does not, of course, allow for tolerances.

Diode  $D_2$  provides a temperature-compensated back-off for the dark-level current at  $D_1$  anode,  $R_x$  and  $R_y$  trimming the conformance of  $D_1$  to the log-law. Other types of silicon diode such as the *OA202* would improve performance at low current and the *1N4002* at the high end, but the *1N4148*, well shielded from light, is a good compromise.

The *NORP-12* has a spectral response similar to that of the human eye, peaking at 550nm; for a response at infrared, a silicon diode, using similar circuit, would be better.

**C J D Catto**  
Cambridge

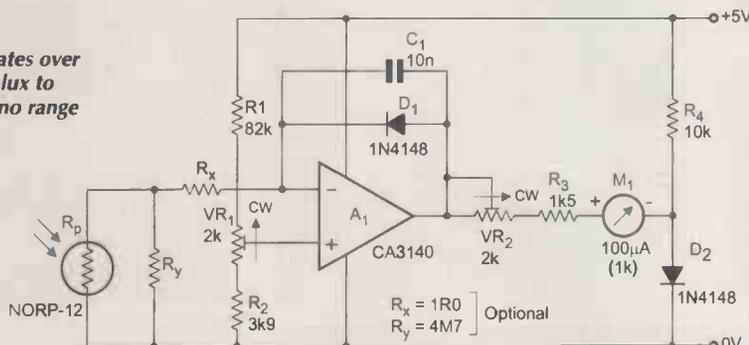Light meter indicates over five decades - 0.1lux to 10,000lux - with no range changing.



# TELFORD ELECTRONICS

## HP EQUIPMENT

HP8161A Programmable Pulse Generator (opt. 001-020)  
 HP5370B (HP1B) Universal Time Interval Counter  
 HP8445B Automatic Prescaler (opt. 002-003)  
 HP8656A Signal Generator (opt. 001)  
 HP8901A Modulation Analyzer  
 HP3586B Selective Level Meter  
 HP5335A Universal Counter (opt. 020/040)  
 HP3336B Synthesizer/Level Generator  
 HP3570A Network Analyzer  
 HP8016A Word Generator  
 HP3571A Tracking Spectrum Analyzer  
 HP3330B Automatic Synthesizer  
 HP339A Distortion Measurement Set  
 HP5328A Universal Counter  
 HP11722A Sensor Module  
 HP8015A Pulse Generator  
 HP8532A Frequency Meter  
 HP8761A S.P.D.T. RF Switch  
 HP435A (B) Power Meter c/w RF Head  
 HP432A Power Meter c/w RF Head  
 HP8170A Logic Pattern Generator  
 HP59501A Power Supply Programmer  
 HP59307A VHF Switch  
 HP59306A Relay Actuator  
 HP461A Amplifier  
 HP400FLA.C. Voltmeter  
 HP3200B VHF Oscillator  
 HP8502A Transmission/Reflection Test Set 500KHz-1.3GHz  
 HP35650 System (8 slot) c/w HP35652B x4, HP35653A, HP35651B  
 HP486A Thermistor Mount  
 HP6920 Meter Calibrator  
 VARIOUS HP PLOTTERS IN STOCK - PLEASE ASK FOR DETAILS  
 HP1740A 100MHz Dual Trace/Storage scope  
 HP180A + HP1801A + HP1821A 50MHz scope  
 HP1742A 100MHz Dual Trace/Storage scope  
 HP8654A 10-520MHz Signal Generator  
 HP8614A 0.8-2.4GHz Signal Generator  
 HP8616A 1.8-4.5GHz Signal Generator  
 HP4204A 10Hz-1MHz LF Oscillator  
 HP651B Test Oscillator  
 HP703A Variable Phase LF Generator  
 HP6261B 0-20V 0-50A Power Supply  
 HP6209B DC 0-320V 0-1A Power Supply  
 HP5342A Microwave Frequency Meter 18GHz  
 HP5308A 75MHz Counter/Timer  
 HP5305A 1100MHz Counter

## TEKTRONIX EQUIPMENT

TEK11401 Digitising Oscilloscope c/w 11A34  
 TEK2465A 35MHz Oscilloscope  
 TEXP5042 Current Probe D.C.-50MHz  
 TEK7904, 7854, 7803, 7704A, 7633, TM504, TM503 IN STOCK  
 TEK Plug-ins: 7A16A, 7851, 7887, D1, 7001, 7A26, 7B36A, DC509, DC504A, AM503, 7892A, 7853A, MANY MORE IN STOCK

## MARCONI EQUIPMENT

6460/1 Power Meter c/w Sensor Head 10MHz-18GHz  
 2830 Multiplex Tester  
 2829 Digital Analyzer  
 2828A Digital Simulator  
 2831 Channel Access Switch  
 2833 Digital Line Monitor  
 MARCONI Microwave Education Test Bench 'X' Band - Brand New  
 2015 Signal Generator 10-520MHz  
 2019 Signal Generator 80KHz-1040MHz

## OTHER TEST EQUIPMENT

ROHDE & SCHWARZ SMS Signal Generator 0.4-520MHz  
 ROHDE & SCHWARZ SMUJ Signal Generator 10KHz-130MHz  
 WATSU SAS130 Waveform Analyzer c/w SH-18 P.I.D.C.-3.5GHz  
 WATSU DM2350 Digital Memory 108n 20ns  
 WATSU DM6430 Digital Memory Scope  
 KRUSUI TOS8850 W1 Auto Tester

NARDA SMA Coaxial 90° Hybrid 2-4GHz  
 NARDA SMA Miniature Stripline Coupler 2-4GHz  
 NARDA Various SMA Attenuators DC-6GHz/DC-12GHz

SOLARTRON 7045 Digital Multi Meter 4 1/2 Digit  
 FLUKE 8860A Digital Multi Meter  
 FERROGRAPH Recorder Test Set RTS2  
 TOOL CHESTS (8 drawer) Made by H Fine & Son (BRAND NEW)  
 CLARE Fish Tester Model GCH01P  
 RACAL 9081/9082 520MHz Synthesized Signal Generator  
 GOULD J3B 10Hz-100KHz Low Distortion Oscillator  
 ADVANCE HIE 15-50MHz LF Oscillator  
 RADFORD LD04 Low Distortion Oscillator  
 RADFORD LDMS2/2 Low Distortion Measuring Set  
 PHILIPS PMS132 Function Generator 0.1Hz-50MHz  
 PHILIPS PMS715 Pulse Generator 1Hz-50MHz  
 ADRET Type 2230A  
 ROHDE & SCHWARZ SUF2  
 FARINELL TSV70 MK2 0-70V @ 5A/0-35V @ 10A  
 VARIOUS LAMBDA & KEPCO PSUs IN STOCK  
 HAVEN Temperature Calibrator 0TB-5 oil/water bath  
 HAVEN Thermo Cal IS Thermocouple Simulator/Calibrator

## TME CD Millivolt POF Source Model 404N

LEADER LOC705 Scope Calibrator  
 CASELLA WBG  
 PPM 411F Current Reference  
 CROICO Resistance Standards - Various in stock  
 H TINSLEY Resistance Bridge Type 5761  
 WALLACE & TIERNAN Precision Pneumatic Calibrator  
 MICRODINE Telemetry Receiver 2.2-2.3GHz  
 AVO DA116 Digital Multi Meter  
 FLUKE 8000A Digital Multi Meter  
 RACAL 9904 50MHz Timer/Counter  
 RACAL 9913/9914/9915/9916/9917/1992/1998 Frequency Counters  
 RACAL INSTRUMENTATION RECORDERS 40S/70S  
 RACAL WORD SAFE 8 track, 48 Hour, Secure voice recorder  
 RACAL TA1885 Auto tuned HF Transmitter 1.6-30MHz 1kW output  
 RACAL TA1800 HF Linear Amplifier 2-30MHz 10kW Output (all mode)  
 PYE T300AM 68-174MHz 300W output  
 REDIFON CA484 400M Solid State Amplifier c/w 1kW Aerial Filter, Drive Unit, PSU  
 HARRIS ATU 601A 1-30MHz, 1kW  
 DATA LAB DK1080 Programmable Transient Recorder  
 ROTEX AC/DC Precision Calibrator  
 RACAL 9084 Synthesized Generator c/w GPIB Interface  
 ROLAND Drafting Plotter A2, DPN-2200 Various Interfaces, 8 pen  
 ROLAND DG X-Y Plotter A3 DPN-980A Various Interfaces, 8 pen  
 KROHN-HITE Filter Model 3202R  
 CABLETRON Systems MR-9000C c/w lanview multicore ethernet/IEEE  
 CABLETRON Systems FR3000 c/w lanview fibre optic repeater unit  
 ANRITSU Channel Selector MS120A  
 BRUEL & KJAER Vibration Programmer ZH0100  
 MINOLTA TV Colour Analyzer c/w Probe TV2140  
 CORNIX 48/48 Audio Switch Matrix Type 921B/1  
 PHOENIX Telecommunications Analyzer 5500A  
 2nd Unit, Phoenix 5500-MSU 5500-200  
 5500-555 5500A-828  
 3rd Unit, Phoenix Control Module 5500-200 + 5500A-828  
 The above 3 items come as one unit

## WATKINS & JOHNSONS EQUIPMENT

Microwave Tuning Frame 4-8GHz  
 Frequency Extender 2-4GHz  
 Demodulator DM112.5  
 Signal Monitor  
 Receiver W8617B 2-500MHz  
**MICROWAVE COAXIAL SWITCHES**  
 'N' Type connectors R.L.C. Model S-2799  
 2kW @ 100MHz 400W @ 6GHz  
 TELEDYNE - SMA Connectors Model CS38S16 22GHz 1mw out  
 FLEXWELL COAXIAL CABLE CU2Y size 1.98th 50 Ohm

**AN EXTENSIVE RANGE OF TEST EQUIPMENT IS AVAILABLE. PLEASE SEND FOR OUR NEW CATALOGUE**  
 Postage and packing must be added. Please phone for price. VAT @ 17 1/2% to be added to all orders. Please send large SAE for details.

**Telford Electronics, Old Officers Mess, Hoo Farm, Humbers Lane, Horton, Telford TF6 6DJ**  
**Tel: 01952 605451 Fax: 01952 677978**

CIRCLE NO. 126 ON REPLY CARD


Finally an upgradeable PCB CAD system to suit any budget ...

## Board Capture

### BoardCapture - Schematic Capture

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

£395

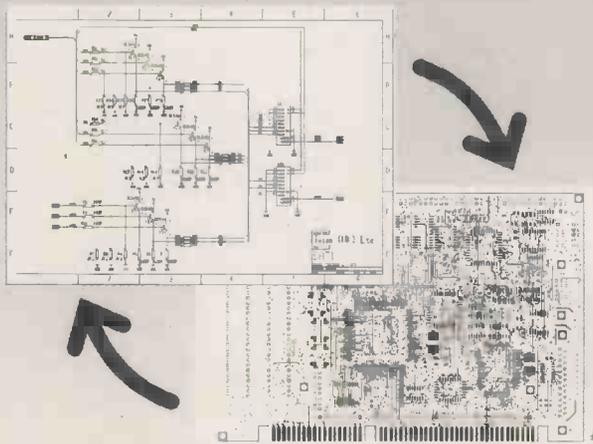

## BoardMaker

### BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

£95

### BoardMaker2 - Advanced level

- All the features of BoardMaker1 plus
- Full netlist support - OrCad, Schema, Tango, CadStar
- Full Design Rule Checking - mechanical & electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC

£395

## BoardRouter

### BoardRouter - Gridless autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

£200

### Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec, Roland & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill / Annotated drill drawings (BM2)

Contact Tsien for further information on  
 Tel 01354 695959  
 Fax 01354 695957




tsien

Tsien (UK) Ltd Aylesby House Wenny Road Chatteris Cambridge PE16 6UT

CIRCLE NO. 127 ON REPLY CARD
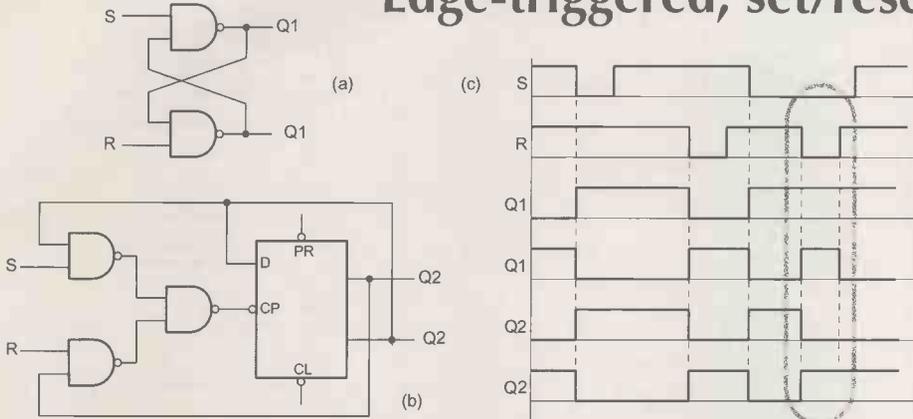
## Edge-triggered, set/reset bistable device




Edge-triggering a S/R bistable device avoids spurious resets when input pulse width is unknown.

If the widths of set or reset pulses applied to a standard S/R bistable device (a) are unknown, the state of affairs shown in (c) at  $Q_1$  and  $/Q_1$  can occur, where the reset pulse arrives during the set pulse; reset has no effect on  $Q_1$ , but produces an unlooked-for pulse on  $/Q_2$ . In addition, the next set pulse will be ignored, since  $Q_1$  is already high.

Since the circuit in (b) responds only to negative edges at the set and reset inputs, the output is as shown at (c) in  $Q_2$  and  $/Q_2$ .

**Giorgio Delfitto**  
University of Padova, Italy

## Simple servo driver

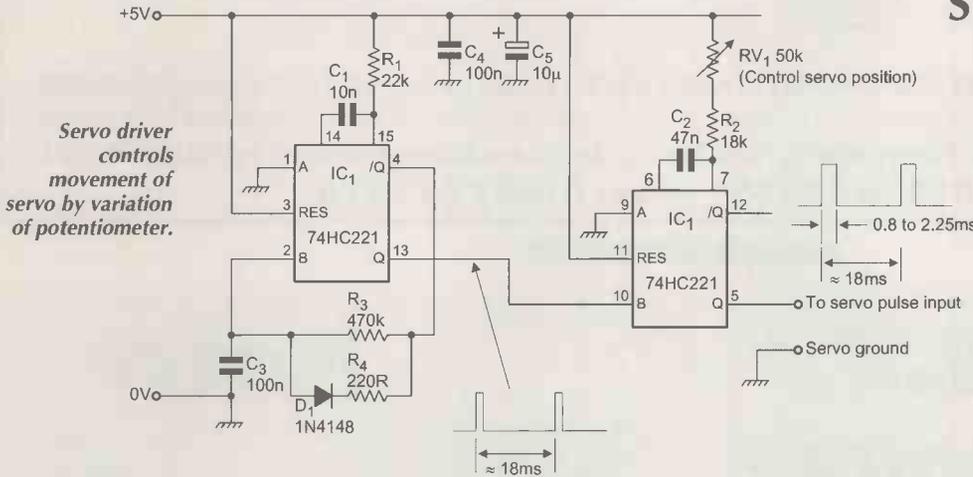


Servo driver controls movement of servo by variation of potentiometer.

This simple circuit drives model servo motors in response to the turning of a potentiometer.

Half the 74HC221 dual monostable is used as a free-running oscillator, producing narrow trigger pulses for the second half of the monostable, whose output is a train of standard servo pulses about 18ms apart, variable in length by the potentiometer from 0.8ms to 1.24ms. The potentiometer therefore controls the servo.

**R G Sutherland**  
Woking  
Surrey
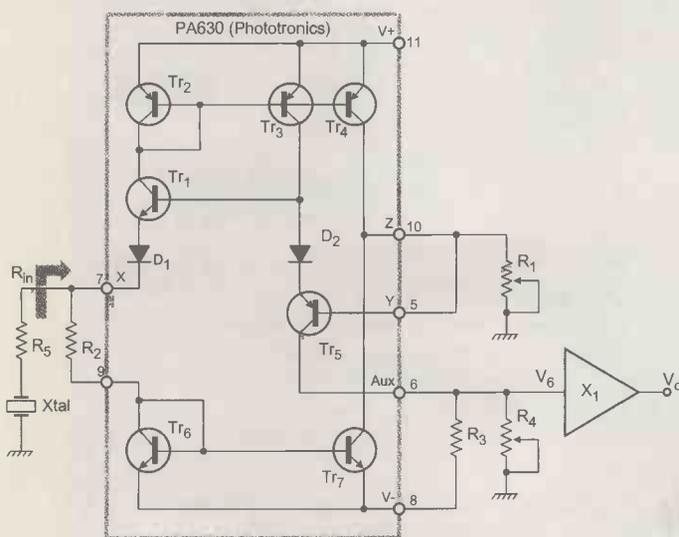
## Crystal oscillator using a current-conveyor



Audio current conveyor, in negative resistance configuration, used to drive a crystal at up to 5MHz.

A PA630 second-generation audio current conveyor, used to provide negative resistance, fulfils all the requirements of a crystal oscillator circuit: high bandwidth, optimum drive level, low damping to retain high crystal  $Q$  and good input/output isolation. Crystals in the 31.25kHz-5MHz range have been used in the circuit shown.

Transistors  $Tr_{1,7}$  form the current conveyor, bias current for all transistors ( $I_{bias}$ ) being set by  $R_2$ , according to

$$I_{bias} = (V_{EE} - 2V_{BE}) / R_2$$

Resistor  $R_2$  driving the current mirror  $Tr_{6,7}$ . Positive feedback from the high-impedance output  $Z$  and the high- $Z$  input  $Y$  causes the input resistance at the low- $Z$  input to become  $R_{in}$  is  $-R_1$ , so that, if the  $esr$  of the crystal  $R_x$  is equal to  $R_1 - R_5$ , the

circuit oscillates. Resistor  $R_5$  is not essential, but does set the best crystal current.

Output comes from the AUX pin, which gives good isolation and offers a point for level adjustment. Resistor  $R_4$  allows adjustment of  $V_6$ , the potential into the buffer stage according to,

$$V_6 = (I_{bias} R_3 - V_{EE}) R_3 / (R_3 + R_4),$$

oscillation increasing until the collector/base junction of  $Tr_5$  becomes forward-biased, reducing the magnitude of the negative resistance at point X.

For a 1MHz crystal with a  $R_x$  of  $85\Omega$ ,  $V_{cc} = V_{EE} = 15V$ ;  $R_1 = 100\Omega$ ;  $R_2 = R_3 = 9.1k\Omega$ ;  $R_4 = 75\Omega$ ; and  $R_5 = 10\Omega$ . Oscillation amplitude is 75mV.

**Dan Sturca**  
Romania


# Data Acquisition for your PC

Pico's Virtual Instrumentation enable you to use your computer as a variety of useful test and measurement Instruments or as an advanced data logger.


Hardware and software are supplied together as a package - no more worries about incompatibility or complex set-up procedures. Unlike traditional 'plug in' data acquisition cards, they simply plug into the PC's parallel or serial port, making them ideal for use with portable PC's.

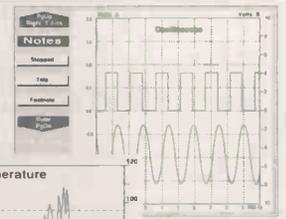**Call for your Guide on 'Virtual Instrumentation'.**

**PicoScope**  
"Virtual instrument"  
software.



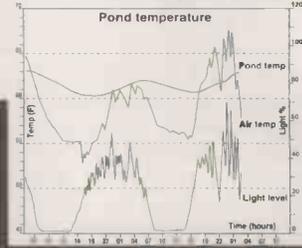**PicoLog**  
Advanced data  
logging  
software.



## SLA-16/SLA-32 Logic Analysers

Pocket sized 16 Channel Logic Analyser



- Connects to PC serial port
- Up to 50MHz Sampling
- Internal & external clock modes
- 8K Trace Buffer

**SLA-16** £219  
**SLA-32** £349  
with software, power supply and cables



## ADC-100 Virtual Instrument

Dual Channel 12 bit resolution

- Digital Storage Scope
- Frequency Meter
- Data Logger
- Spectrum Analyser
- Chart Recorder
- Voltmeter

The ADC-100 offers both a high sampling rate (100kHz) and a high resolution. It is ideal as a general purpose test instrument either in the lab or in the field.

**ADC-100** with PicoScope **£199**  
with PicoScope & PicoLog **£219**

**ADC-10**  
Gives your computer a single channel of analog input. Prices from £ 49.

**NEW**  
from Pico  
**Thermocouple**  
to PC Converter  
**TC-08** £199



**PICO TECHNOLOGY**



Pico Technology Ltd. Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ  
Tel: (0)1954 - 211716 Fax: (0)1954 - 211880 E-mail: 100073.2365 @compuserve.com



Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT. Carriage Overseas £9

CIRCLE NO. 128 ON REPLY CARD

# LOW COST DEVELOPMENT SYSTEM


ECAL comprises a versatile relocatable assembler with integral editor which runs about ten times faster than typical assemblers. Support includes 4, 8, 16 & 32 bit processor families including 75X, 6502, 6809, 68HC05/11, 8031/51, H8-300, Z8K, PICs, ST6 & Z80/180, 68000, 80C196, H8-500 & Z280.

ECAL is either available for a single processor family or all families.

Single processor version £295  
Multiprocessor version.... £395

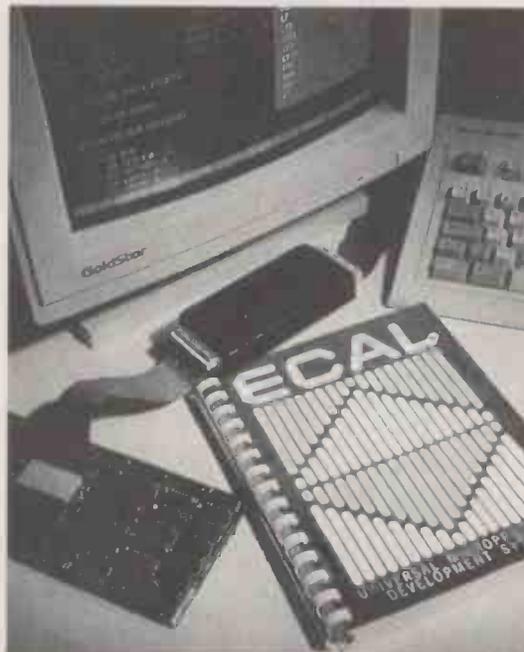**Overseas distributors required**

**OEMA Ltd.,**  
7 & 7A Brook Lane,  
Warsash,  
Southampton SO31 9FH  
Tel: 01489 571300  
Fax: 01489 885853



The PC based ECAL hardware emulator is fully integrated with the assembler. Connection is made to the target through the eprom socket so a **single** pod can support **all** processors. Facilities include windows for the inspection or change of registers or memory. You can even watch your program executing at source level!

Download time is about two seconds!

Pods can be daisy-chained for 16/32 bit systems.

Applications include software development, hardware debug, test and, finally, teaching about micro-controllers in education.

ECAL emulator ..... £475

**Quantity discounts of up to 50% make ECAL software ideal for education.**

**Free demo disc!**

CIRCLE NO. 129 ON REPLY CARD

## 24V electromechanical counter from 12V

Having a number of 24V counter mechanisms and a 12V controller, it was necessary to produce a suitable interface. This circuit performs that function with no great power dissipation and with less interference radiation than other methods.


With the driver off, the input is at 12V,  $Tr_1$  is cut off and there is no current to the counter coil. Capacitor  $C_1$  charges through  $R_3$  to around 11V via  $D_3$  and no further current flows in the circuit.

As the driver comes on,  $Tr_1$  base current flows in  $R_2$  and the top end of the counter coil goes to almost 12V. Diode  $D_1$  conducts and clamps the top end of  $C_1$  to about 1V, its bottom end and that of the coil going to about -10V, so that the coil sees enough voltage to energise it. As the charge on  $C_1$  decays, the counter still sees

about 11V, which should be enough to hold the mechanism in, with reduced steady-state dissipation.

The time constant is chosen to suit a 250ms drive every 3s, but may be varied for any use. A snubber diode is not necessary, since the driver collector never exceeds the supply voltage.

**Gerald D Pye**  
Ipswich  
Suffolk

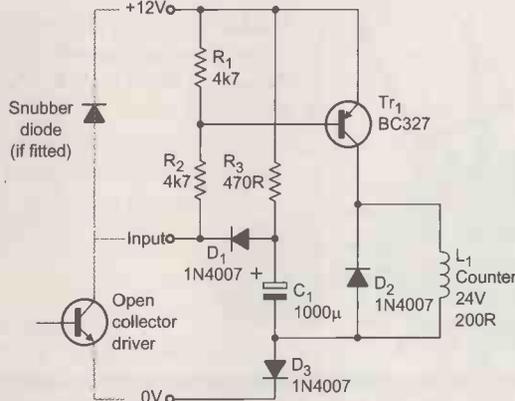

12V-to-24V converter to drive 24V counter coils from 12V, with the incidental advantages of reduced power dissipation and interference.


## One op-amp dc motor driver

Used widely in the field of robotics, this current source produces a 2.5A output from a 6.25V input, using only one power op-amp and one power resistor.

Feedback from both ends of the 3W current-sensing resistor  $R_{sc}$  got to the op-amp inputs, which is forced to maintain the current through  $R_{sc}$ , calculated to be,

$$I_{out} = (V_{in}/R_{sc})(R_2/R_1).$$

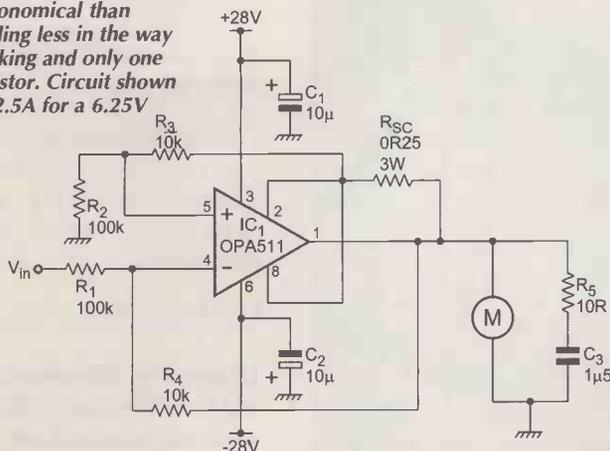**Motor driver for robots. This is more economical than most, needing less in the way of heat sinking and only one power resistor. Circuit shown produces 2.5A for a 6.25V input.**



Choosing  $R_2=R_4=10k\Omega$  and  $R_1=R_3=100k\Omega$ ,  $R_{sc}$  is  $0.25\Omega$  to give an output of 2.5A for a 6.25V input.

$$R_{sc} = 0.65/I_{out}(A) - 0.01.$$


Resistors  $R_{1-4}$  should be 1%, 0.25W types and the op-amp should be on a heat sink; the OPA511 has an insulated case and needs no isolation.

**V Vidyalal, K Rajasree and V Sivanand**  
Cochin University of Science and Technology, India
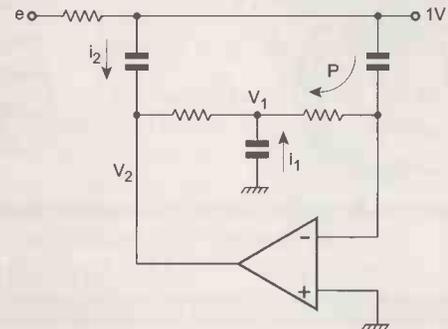
## Active, low-pass filters with no dc errors

In the arrangement illustrated, the op-amp in this low-pass, maximally flat Butterworth filter is blocked from the signal path by capacitors, this makes its offset and input current irrelevant. Two-pole, three, four and five-pole versions have been built and offer the further advantage that they use fewer components than more conventional circuits. The op-amps can be operated from a single supply, if required.

No free lunches, though: theoretically, they must work



One of a family of maximally flat low-pass active filters, in which the op-amps are dc-blocked and which are more economical in components than other designs.

into an open circuit, a requirement that can be met either by including a follower to the output or doubling the value of the input resistor and inserting an equal value to ground. This halves the dc gain and needs a purely resistive, and fairly critical, load.

To take the three-pole version shown, let  $p$  equal  $j$ , work backwards from a 1V output to find the input  $e$ .

$$v_1 = -p \quad i_1 = p^2$$

$$v_2 = v_1 - (p + i_1) = -2p - p^2$$

$$i_2 = p(1 - v_2) = p + 2p^2 + p^3$$

$$e = 1 + p + i_2 = 1 + 2p + 2p^2 + p^3.$$

So the transmission  $T$  is,

$$T = \frac{1}{1 + 2p + 2p^2 + p^3},$$

and magnitude  $|T|$  is,

$$|T| = \frac{1}{\sqrt{(1 - 2\omega^2)^2 + (2\omega - \omega^3)^2}} \\ = \frac{1}{\sqrt{1 + \omega^6}}$$

If  $R$  and  $C$  values are unknown, make one component unity and the two resistors equal. This still leaves four unknowns, so other component values are possible. It turns out that if all three capacitances are unity, so are the resistances.

**McKenny W Egerton**  
Owings Mills, Maryland, USA



## EW reader offer

### 30V, 5A power supply

For a limited period, Vann Draper is offering over 25% discount on the 305 LDD – a bench power supply featuring digital display of both voltage and current. Normally, the 305 retails at £159 excluding VAT and delivery but it is available to EW readers filling in the coupon on the right at the 25% discount price of £139 – fully inclusive of VAT and delivery. Infinitely variable between 0 and 30V – with coarse and fine controls – and adjustable between 0 and 5A, the 305 LDD has a ripple figure of typically 10mV. Its load regulation is also excellent, at typically  $\pm 0.2\%$ .

Accuracy of the supply's dual 3.5-digit liquid crystal displays is 0.1 decimal digit. The output can handle a continuous short-circuit, overloading at  $5.5A \pm 0.5A$ . When the overload circuit is activated, it causes both audible and visual alarms, resettable via a push-button on the front panel.

Dimensions of the 305 LDD are 310 by 260 by 120mm and its weight is 5.5kg. Housed in a light-grey steel enclosure, the unit is built to comply with UL, CSA and TUV safety standards.

### Features of the 305 LDD

0-30V fine and coarse adjustments

0-5A adjustable

10mV ripple

Digital displays for V and I

Continuous short circuit protection

$\pm 0.2\%$  load regulation

#### Use this coupon to order your 305 LDD

Please send me ..... 305 LDD(s) at the fully inclusive special offer of £139

Name

Company (if any)

Address

Phone number/fax

Total amount £.....

Make cheques payable to Vann Draper Electronics Ltd  
Or, please debit my Master, Visa or Access card.

Card type (Access/Visa)

Card No  
Expiry date

Please mail this coupon to Vann Draper Electronics, together with payment. Alternatively fax credit card details with order on 0116 2773945 or telephone on 0116 2771400.  
Address orders and all correspondence relating to this order to Vann Draper Electronics at Unit 5, Premier Works, Canal Street, South Wigston, Leicester LE18 2PL.

\*Overseas readers can also obtain this discount but details vary according to country. Please ring, write or fax to Vann Draper Electronics

## Virtual-capacitance timer and filter

An op-amp and five other components bootstrap a capacitor to make a 200µF component from 0.1µF.


Left is shown a low-pass filter having a time constant of 10s, determined by  $R \times C \times R_1/R_2$ . Since bootstrapping also increases the effects of op-amp bias current and input offset voltage,  $R_4$  reduces dc following error to around 10mV, its value being greater or less than that of

$R_1$ , depending on the sign of the offset; it is bypassed to ensure stability.


In the right-hand diagram, using a fet op-amp allows an increase in the amount of bootstrapping to about  $10^3$ , giving the effect here of a 2200µF

capacitor. Used with a 555 timer, and depending on how well the CA3140 offset voltage can be coped with, a time of 400-600s can be obtained to within ±1% repeatability.

**W. Gray**  
Farnborough, Hants

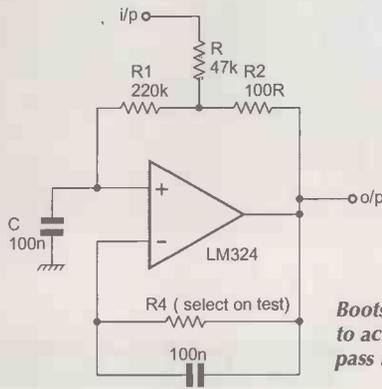

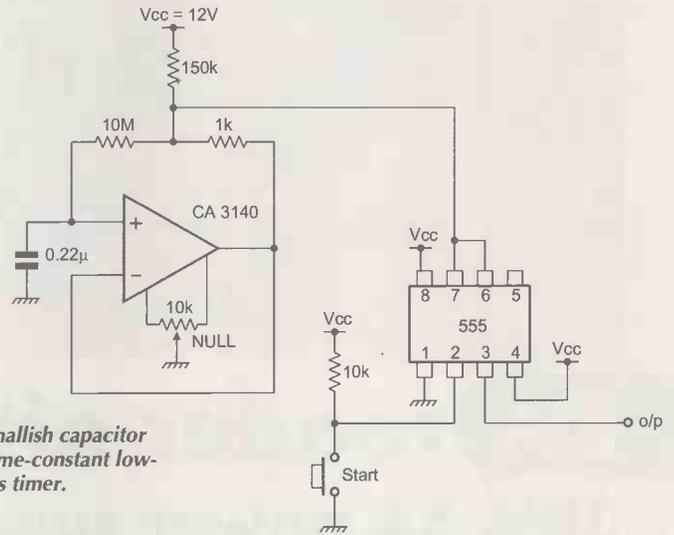*Bootstrapping a smallish capacitor to achieve a 10s time-constant low-pass filter and 500s timer.*



## Linear phase detector from two op-amps



Two op-amps and two fets form an analogue linear phase detector. An input reference square wave switches on and off the two switching

fets, which configure the first op-amp into an inverting amplifier when the fets are on and a non-inverter when they are off, both with unity gain.

If the input signal, shown as a sinusoid, is in phase with the reference, the output of the op-amp is, effectively, a full-wave-rectified version of the input to give the maximum positive circuit output when filtered by the output op-amp. When the input is 90° out of phase,

the op-amp output produces an average which is equal to zero and when in antiphase, a maximum negative version of the in-phase output.

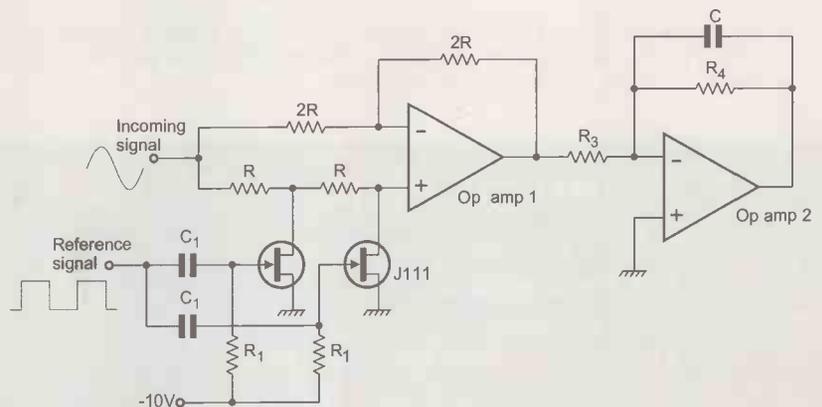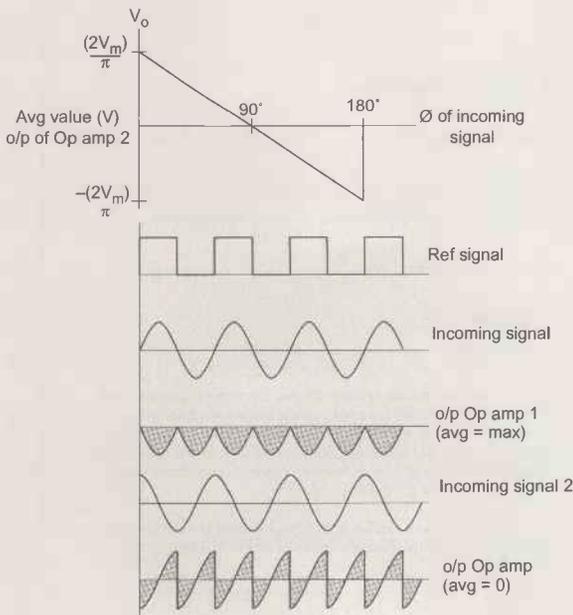Ensure accurate matching of resistors at the op-amp input and also that the on resistance of the fets is low.





# LETTERS

Letters to "Electronics World"  
 Quadrant House, The Quadrant,  
 Sutton, Surrey, SM2 5AS

## I versus V feedback

Surely current feedback, cfb, is much closer to the correct drive of a loudspeaker voice coil than voltage feedback, vfb, is?

Driving force on the coil is very simply expressed by,

$$F = \beta \cdot i \cdot l \cdot \sin \alpha$$

with wire length  $l$ ,  $\alpha$  a constant, and  $\beta$  flux density, so  $F$  is proportional to  $i$ .

A similar relationship between voltage and force cannot be written easily, due to the many ill defined terms that compose voice coil impedance.

Apart from the main resonance region, voice coil back emf is negligible, so voltage feedback is also unrelated to voice-coil velocity.

In reply to Mr Allison's query in the December issue, I can say I have tested cfb on two different designs, one low ultra-linear push-pull of EL84 in 1961 and one 18W with AD159 transistors in 1964.

Not equipped at the time with sound level measuring apparatus, I had to rely on my ungolden hearing for comparisons with identical amplifiers wired for vfb. No elaborate double-blind protocol was

necessary to note the marked differences in tonal responses.

In both modes, 20cm wideband loudspeakers from several French makers were tried.

Speaker designs with curved generatrix cones, such as Supravox T215 and GeGo 'Supersoucoupe', lacked treble response with vfb, but gave very clean and sharp treble with cfb.

On the other hand, models with dual cones - Princeps, and Audax T21PA12 for example - while displaying sufficient - if unnatural - treble response in vfb, sounded very harsh and metallic in cfb.

Clearly the cause of treble roll off in vfb is the voice coil rise in impedance above 2 or 3kHz, mainly due to the inactive coil turns in front of and behind the magnetic gap.

This impedance rise limits the drive in vfb, however in cfb it only limits the maximum available power before clipping.

While little difference in medium response between vfb and cfb was audible, the other evident feature of cfb was boomy bass, due of course to a totally undamped main resonance. This is certainly the principal drawback of this mode, as to my knowledge no simple acoustic means allows for efficient damping of the main loudspeaker resonance.

My solution at the time, to try and get the best of both worlds, was to depart from pure cfb, by insuring constant-gain gradual change from vfb at low frequencies to cfb at high medium and treble, Fig. 3.

It would be most interesting to repeat these experiments with modern amplifiers and full testing capabilities.

Jean Claude Baumeister  
 Chantraine  
 France

## Hazy linearity notions?

I would like to comment on Mr Kiyoleawa's hazy notions in the January '96 issue Letters column.

I was glad to see Mr Kiyoleawa confirm that a linear increase of power fet  $g_m$  with drain current is a poor basis for making a linear stage. What is really required is linear variation of  $I_d$  with  $V_{gs}$ . It may be possible to partly cancel fet square-law distortion by push-pull operation. But this can only work in Class-A, when both upper and lower output devices are conducting at the same time.

Economic necessity and energy conservation mean that most amplifiers are Class-B, and to date there is no practicable compromise between these two modes. If fets can only give acceptable linearity in Class-A, then this is not much of a recommendation for them.

I am unable to understand the contention that an fet output stage can have a 'lower' open-loop output impedance, presumably compared with a bipolar version. Field-effect transistor  $g_m$  is always much lower than for bipolars, and so this would appear to quite impossible.

A  $1\Omega$  output resistance is much too high. It may only have a small effect on loudspeaker damping, but will certainly cause unwanted frequency response variations because of the varying impedance curve of the speaker.

Having done a great deal of practical emc testing recently, I can assure Mr Kiyoleawa that radio-frequency entry via speaker cables is a non-problem - at 3V/m and between 30 and 1000MHz, anyway. The presence of an output inductor may be the critical factor here; at any rate it is no reason to abandon global negative feedback.

I'm afraid that Mr Kiyoleawa has

not quite appreciated the action of the voltage-amplifier stage transistor. The impedance at its collector is strongly frequency dependant, halving with each octave as local negative feedback through  $C_{dom}$  increases, and crippling its linearity with a dead load of  $5k\Omega$  will not alter this fact. I think it will be difficult to find a driver/output pair with a combined  $h_{fe}$  of 10,000 at practical current levels; but if the object is, as it appears to be, the avoidance of global negative feedback, then this line of thought is a dead-end anyway.

I have made solid-state amplifiers where the output stage worked open-loop, and the practical result is severe distortion of a unpleasantly jagged kind. I cannot believe that anyone - Subjectivist or otherwise - would find this preferable to the very low thd levels obtainable from a blameless amplifier with global negative feedback.

According to the Toshiba application notes<sup>1</sup>, igtbs consist of an fet controlling a bipolar power transistor; I have no information on the linearity of these devices, but the combination does not sound promising.

The most discouraging aspect is the presence of a parasitic bipolar-junction transistor that turns the device hard on above a critical current threshold. This inbuilt self destruct mechanism makes overload protection an extremely critical matter; it seems unlikely that igtbs will prove popular for audio amplification.

Douglas Self  
 London

## Reference

1. Langdon, S, 'Audio amplifier design-s using IGBTs, MOSFETs, and BJTs', Toshiba Application Note X3504, V.1 Mar 1991.

## Does component choice make a difference?

I enjoy EW's audio articles, but the statement by Reg Williamson in his Dec '95 audio preamp article is a little strange to me. I must say that 'audio grade' components are sometimes far too expensive and results are doubtful. I am a technician myself and also sceptical about 'audio grade' components.

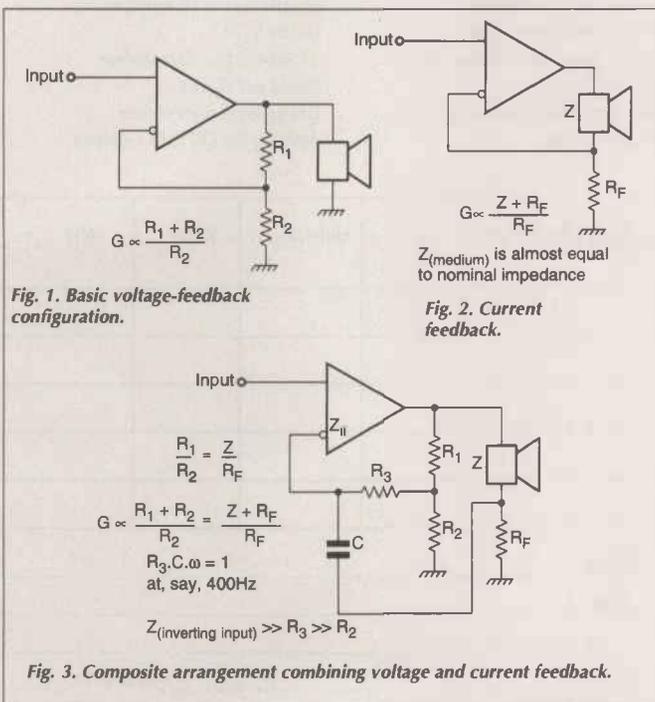


Fig. 1. Basic voltage-feedback configuration.

Fig. 2. Current feedback.

Fig. 3. Composite arrangement combining voltage and current feedback.



8 CAVANS WAY,  
BINLEY INDUSTRIAL ESTATE,  
COVENTRY CV3 2SF  
Tel: 01203 650702  
Fax: 01203 650773  
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

MISCELLANEOUS

Analogue/Digital precision - 6100Hz waveform analyser - fitted with 660B - 2 channel - 250MHz digitizing transit waveform plug-in module plus Data 2020 arbitrary waveform (25MHz) generator fitted with 682-X1 plotter + 682-60 remote option All at £12.5K

Anritsu ME462B - DS-3 transmission analyser	£3000
Anritsu MG642A - Pulse pattern generator	£1500
B-K 2307 - Level recorder	£300
B-K 2706 - Power amplifier	£250
Barr & Stroud - EF3 variable filter (0.1Hz-100kHz)	£150
Datalab DL 1080 - Programmable Transient Recorder	£350
Datron 1061 - Precision multimeter	£650
Dynapert TP20 - Intelligible tape reel tester, immac. cond.	£1950
E.I.P. 331 - 180Hz frequency counter	£850
E.I.P. 548A - frequency counter (26.5GHz)	£3000
Farnell SSE520 - Signal generator (10-520MHz)	£400
Farnell TSV70 Mill - Power Supply (70V-5A or 35V-10A)	£225
Farnell TTS520 - Transmitter Test Set	£400
Ferrogaph RTS2 - Audio test set with ATU1	£500
Fluke 5200A - A.C. calibrator	£2500
Fluke 5205A - Precision power amplifier	EP.O.A.
Fluke 7105A - Calibration system (As new)	EP.O.A.
Heiden 1107 - 30v-10A Programmable power supply (IEEE)	£650
Hewlett Packard 334A - distortion analyser	£300
Hewlett Packard 339A - distortion measuring set	£1500
Hewlett Packard 432A - Power Meter (with 478A Sensor)	£275
Hewlett Packard 435A or B - Power Meter (with 8481A/B484A)	from £750
Hewlett Packard 5328A - 100MHz universal frequency counter	£250
Hewlett Packard 3325A - 21MHz synthesiser/function gen.	£1500
Hewlett Packard 3437A - System voltmeter	£350
Hewlett Packard 3438A - Digital multimeter	£200
Hewlett Packard 3455A - 6 1/2 digit multimeter (autoscal)	£750
Hewlett Packard 3456A - Digital voltmeter	£750
Hewlett Packard 3488A - HF - IB switch/control unit (various plug-ins available)	£650
Hewlett Packard 3490A - Digital multimeter	£250
Hewlett Packard 3711A/3712A/3713B/3738B - Microwave link analyser	£3500
Hewlett Packard 3746A - selective level measuring set	£1750
Hewlett Packard 4192A - L.F. impedance analyser (5Hz-13MHz)	£6995
Hewlett Packard 4261A - LCR meter (digital)	£500
Hewlett Packard 4271B - LCR meter (digital)	£900
Hewlett Packard 4342A - Q meter	£395
Hewlett Packard 4948A - transmission impairment measuring set	£2000
Hewlett Packard 4953A - Protocol analyser	£2750
Hewlett Packard 4954A - Protocol analyser	£2995
Hewlett Packard 5314A - (new) 100MHz universal counter	£250
Hewlett Packard 5350B - (new) microwave frequency counter (20GHz)	£2500
Hewlett Packard 5359A - Time synthesiser	EP.O.A.
Hewlett Packard 5385A - Frequency counter 1GHz (HP1B) with Optis 001/003/004/005	£995
Hewlett Packard 5505A - Laser display	EP.O.A.
Hewlett Packard 6002A - autogating 50V-10A, PSU	£650
Hewlett Packard 6181C - D.C. current source	£150

TELNET

Hewlett Packard 6261B - Power supply 20V-50A	£450
DISCOUNT FOR QUANTITIES	
Hewlett Packard 7402 - Recorder with 17401A x 2 plug-ins	£300
Hewlett Packard 8005B - Pulse generator	£250
Hewlett Packard 8011A - Pulse gen. 0.1Hz-20MHz	£500
Hewlett Packard 8116A - Pulse/function generator (1MHz-50MHz)	£2500
Hewlett Packard 8152A - Optical average power meter	£1250
Hewlett Packard 8158B - Optical attenuator with opt's 002 + 001	£1100
Hewlett Packard 8165A - 50MHz programmable signal source	£1650
Hewlett Packard 8349B - Microwave broadband Amp (as new) 2-20MHz	£4250
Hewlett Packard 8350B - Sweep oscillator mainframe (plug-ins avail)	£2500
Hewlett Packard 8403A - modulator	£500
Hewlett Packard 8601A - generator/sweeper, 110MHz	£300
Hewlett Packard 8620C - Sweep oscillator mainframe	£400
Hewlett Packard 8660D - Synthesised signal gen. 10kHz-2.5GHz	£4500
Hewlett Packard 8683A - Microwave signal gen. (2.3-6.5GHz)	£3500
Hewlett Packard 8684A - 5.4GHz to 12.5GHz Sig Gen	£3500
Hewlett Packard 8750A - Storage normaliser	£375
Hewlett Packard 8903A - Audio analyser (20Hz-100kHz)	£2250
Hewlett Packard 8903B - Audio analyser (20Hz-100kHz)	£2995
Marconi 893B - A-F power meter	£295
Marconi 2019A - 80kHz-1040MHz synthesised sig gen.	£1950
Marconi 2305 - modulation meter	£2500
Marconi 2871 - data communications analyser	£2000
Marconi 6500 - automatic amplitude analyser	£1750
Philips PM 5167 - 10MHz frequency gen.	£400
Philips PM 5190 - LF synthesiser with GP1B	£800
Philips PM 5565 - Waveform monitor	£200
Philips PM 5567 - Voltscope	£600
Philips PM 8226 - 6 pen recorder	£550
Phoenix 5500A - telecomms analyser with various interface options	£2250
Racal Dana 1992 - 130MHz frequency counter opt's 4B-45	£300
Racal Dana 3100 40-130MHz synthesiser	£750
Racal Dana 9084 Synth. sig. gen. 104MHz	£450
Racal 9301A True RMS R/F millivoltmeter	£300
Racal Dana 9303 True RMS R/F level meter	£650
Racal Dana 9921 3GHz frequency counter	£450
Schaffner NSG 200E - Mainframe for NSG plug-ins	£1250
Schaffner NSG 203A - Line voltage variation simulator	£1250
Schaffner NSG 222A - Interference simulator	£850
Schaffner NSG 223 - Interference generator	£850
Schlumberger 2720 - 1250MHz Freq. Counter	£600
Schlumberger SI 4040 - Stablock, high accuracy 1GHz radio test set	£950
Schlumberger 4923 - Radio Code Test Set	£1500
Tektronix - Plug-ins - Many available such as PG508, FG504, SC504, SW503, SG 502 etc.	£1750
Tektronix TM5003 - AFG5101 Arbitrary Function Gen	£750
Tektronix 1240 Logic Analyser	£750
Tektronix 578 - Cure tracer (with test fixture)	£1250
Tektronix AM503 + TM501 + PS302 - current probe amplifier	£395
Tektronix PG506 + TG501 + SG503 + TM503 - Oscilloscope calibrator	£1995
Tektronix CG5001 - Programmable oscilloscope cal. generator	£6995
Time 9814 Programmable resistance	£600
Time 9814 Voltage calibrator	£750
Wavetek 2002B - Sweep generator (0-2.5GHz)	£1950
Wayne Kerr N905 - Precision LCR meter	£350
Wiltron 560 Scalar Network analyser	£800

Gould 5110 - 100MHz Intelligent oscilloscope	£750
Heemeg 203/203-4/203-5/203-6 - 20MHz Dual CH	From £175
Hewlett Packard 180D - 100MHz 4 channel	£300
Hewlett Packard 182C - 100MHz 4 channel	£350
Hewlett Packard 1707A, 1707B - 75MHz dual ch.	from £275
Hewlett Packard 1740A, 1741A, 1744A - 100MHz dual ch.	from £350
Hewlett Packard 1980B - 100MHz - 2 channel - HP1B programmable	£750
Hewlett Packard 54100D - 1GHz digitizing	£3995
Hewlett Packard 54201A - 300MHz digitizing	£1750
Hewlett Packard 54501A - 100MHz Digitising - 4 channel	£1950
Hitachi V650F - 60MHz Dual channel	£350
Kikusui GOS 6100 - 100MHz 5 channel 12 trace	£475
Lecroy LS 140 - 100MHz 4 channel D.S.O. (As new)	£2750
Nicolet 3091 - Low freq. D.S.O.	£1100
Philips 3217 - 50MHz Dual CH	£350
Philips 3219 - 50MHz with analogue storage, Dual CH	£400
Philips 3295 - 350MHz dual ch.	£1500
Philips 3302 - 20MHz Digital storage	£475
Philips 3315 - 60MHz D.S.O.	£750
Philips PM3295A - 400MHz dual channel	£1950
Tektronix 455 - 50MHz dual channel	£350
Tektronix 7854 - 400MHz Waveform processing oscilloscope	£1500
Tektronix 464/466 - 100MHz storage	from £350
Tektronix 465/465B - 100MHz dual ch.	from £350
Tektronix 2235 - 100Hz D.S.O.	£750
Tektronix 2213 - 60MHz dual ch.	£425
Tektronix 2215 - 60MHz dual ch.	£450
Tektronix 2225 - 50MHz dual trace	£450
Tektronix 2235 - 100MHz dual ch. (portable)	£800
Tektronix 2236 - 100MHz Dual Trace with Counter/Timer/Dmm	£995
Tektronix 2235 - 100MHz dual ch. (portable)	£750
Tektronix 7313, 7603, 7613, 7623, 7633 - 100MHz 4 ch.	from £300
Tektronix 7704 - 250MHz 4 ch.	from £650
Tektronix 7904 - 500MHz	from £850
Tequipment DB3 - 50MHz dual ch.	£200

Other scopes available too

SPECTRUM ANALYSERS

Advantest 4133A - 10kHz-20GHz	£6995
Advantest 4133B - 10kHz-20GHz (60GHz with ext. mixers)	£7995
Hewlett Packard 141T + 8552B + 8555A (10MHz-16GHz)	£1600
Hewlett Packard 182T with 8559A (10MHz-21GHz)	£3750
Hewlett Packard 853A with 8559A (0.01-21GHz)	£4250
Hewlett Packard 3562A - dynamic signal analyser, dual channel	£7500
Hewlett Packard 3580A - 5Hz-50kHz	£995
Hewlett Packard 3582A - 25kHz analyser, dual channel	£2500
Hewlett Packard 3709A - Constellation Analyser with 15709A High Impedance Interface (as new)	£6750
Hewlett Packard 8505A - Network analyser (500kHz-1.3GHz)	£4000
Hewlett Packard 8565A (0.01-22GHz)	£4000
Hewlett Packard 8590A - KHz-1.5GHz	£4250
Hewlett Packard 8754A - Network Analyser - 4-1300MHz	£3250
Hewlett Packard 35601A - Spectrum Analyser Interface	£1000
Marconi 2370 - 110MHz	£995
Marconi 2371 - 30Hz-200MHz	£1250
Polrad 641-1 - 10MHz-18GHz	£1500
Rohde & Schwarz - SWOB 5 Polyskop 0.1-1300MHz	£2500
Schlumberger 1250 - Frequency response analyser	£2500
Schlumberger 496P - 1kHz-1.8GHz programmable	£4500
Tektronix 2710 - KHz-1.8GHz	£4250


MANY MORE ITEMS AVAILABLE - SEND LARGES.A.E. FOR LIST OF EQUIPMENT ALL EQUIPMENT IS USED - WITH 30 DAYS GUARANTEE. PLEASE CHECK FOR AVAILABILITY BEFORE ORDERING - CARRIAGE & VAT TO BE ADDED TO ALL GOODS

CIRCLE NO. 130 ON REPLY CARD

We are making progress with the new version 5 of SpiceAge

- Rapid digital filter modelling with links to SuperFILTER digital and analogue filter synthesizer (optional extra)
- Non-linear magnetic modelling including ferromagnetic hysteresis
- Extended scope of Modelmaker (optional extra), the utility that synthesizes opamps, transformers, attenuators, bipolar, JFET and MOSFET transistor library models
- Other benefits from this mature product which enjoys diligent maintenance and professional support include: a new manual; new (rationalised) pin convention; faster calculating; larger circuits; touch convergence; helpful customer base (for mutual problem solving and model sharing); widening third party support with links to schematic capture and synthesis programs (native schematic capture also available as an optional extra).

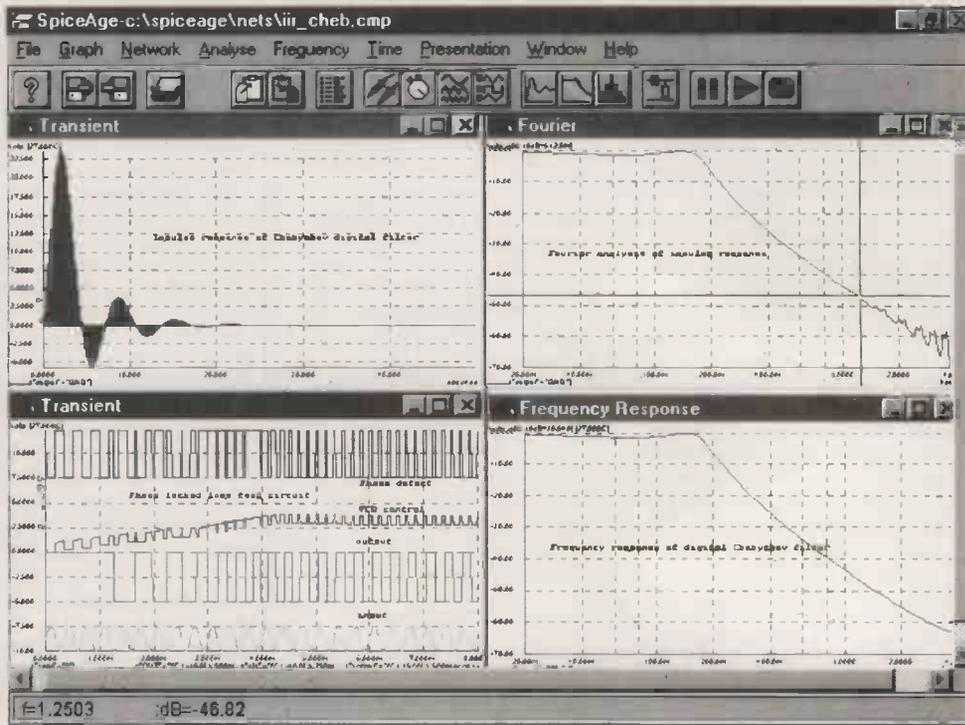Contact Those Engineers Ltd at 31 Birkbeck Road, LONDON NW7 4BP.  
Tel: 0181 906 0155 Fax: 0181 906 0969 Email 100550.2455@compuserve.com



CIRCLE NO. 131 ON REPLY CARD

But there is a big *but*. Recently I built a d-to-a convertor using Crystal Semiconductors' latest 20 bit device, the CS4329. My power supply uses LT1085CT and LT1033CT regulators. The power supply capacitors are Rubycon Black Gate FK and NX types and Sanyo Os-Con types. These are 'exotic' components and rather expensive.

The overall sound performance with these capacitors is so much better than a LT1085/LT1033 based power supply using good quality and normal priced Elna RSH capacitors. Using Keith Jarrett's 'Köln Concert' as reference music, you can easily tell which power supply is 'playing'. The soundstage is so much improved. Jarrett's piano really 'sings'. In my opinion there is no doubt that the BGs and Os-Cons improve the sonic overall performance of a system; my ears are me tell me so.

Keep up the good work,  
**W. de Haan**  
Leiden, The Netherlands

## Agreeable distortion

'Valve sound' is essentially subjectively agreeable distortion. An analogy is the measurable sensation of travelling in a vintage Bentley rather than in a modern mid-range Ford, which is noticeably better in most respects – if not at all.

However, there is one difference – cost. Preferred output valves cost upwards of £20 each.

Morgan Jones' excellently presented article – Jan '96 – exhibits at least one flaw, however, as many of the resistance values arrived at by paralleling are within a fractional percentage of standard values. For example 330kΩ in parallel with 22kΩ is 20.625kΩ. A near value in the E96 range is 20.5kΩ – less than 1% off. If cost is no object, this is the way to do it.

I worked with valves for many years and came to accept that their characteristics varied widely from part to part. Anybody who used the EF50 will remember this. There is no point in attempting exact design where key parameters can differ by as much as 20%.

In any case, the principal feature of valve amplifiers is that they include an output transformer. If one takes a good solid-state amplifier and includes a 1:1 output transformer within the feedback loop one will achieve much the same effect.

Of course, valve and solid-state amplifiers driven near to or past saturation will sound different, but if one is any sort of a purist this is not a region in which one operates. Vast power capability overkill is an essential feature of hi-fi usage.

**Nick Wheeler**  
Sutton  
Surrey

## Valve misunderstanding

As a designer of valve amplifiers since 1950 I have read with some disbelief the article by Morgan Jones in *Electronics World* January 1996 and the subsequent correspondence in the February and March issues. Both Morgan Jones and Frank Ogden seem to not understand the operation of the concertina phase splitter.

This circuit does not have the alleged difference in frequency response at the anode and cathode terminals. If the anode and cathode outputs are analysed separately then, of course the anode output resistance is high and the cathode output resistance relatively low as shown by Morgan Jones in his March 1996 letter. However when both outputs are loaded simultaneously with equal capacitances the output voltages remain equal throughout the audio frequency range.

This can be understood intuitively since the anode current is the same as the cathode current so when the two impedances are equal (i.e. equal resistances and equal capacitances) then the output voltages must be equal at all frequencies. It is obvious that the tendency for the anode voltage to decrease more rapidly as the frequency is raised is fully compensated by the by-passing effect of the cathode loading capacitance.

The circuit behaves as if the

output resistance at both ports is much the same as the source resistance of a cathode follower using the same valve and cathode load resistance. It can be shown that the effective output resistance used to determine the frequency response at both outputs is,

$$R_o = \frac{r_o R_L}{r_o + R_L (\mu + 2)}$$

Needless to say the 'build-out' resistor spoils this inherent wide-band balance of the concertina phase splitter.

There is another error in the Morgan Jones article in the January 1996 issue where he attempts to balance the signal currents of the input stage and the concertina. The concertina signal current is approximately grid voltage divided by cathode resistance thus the anode load of the input stage should be roughly equal to the concertina cathode resistance and not cathode resistance plus anode resistance as stated.

**M.H. McFadden**  
Belfast

## Reference

1. 'Radio Designer's Handbook' F. Langford-Smith p.329 Fourth Edition. Published by *Wireless World* 1953.

## Shame about the error

At present I am particularly interested in the subject of valve audio amplifiers. While not having sufficient detailed information on valve characteristics at hand to check all the calculations in the January's valve power amplifier article, I was disappointed to find a clear error in the calculation of the values for the feedback resistor and the input stage cathode resistor. While the circuit diagram indicates a 4Ω output load, the calculation is based on 8Ω.

Speakers with 3Ω or 15Ω coils were common before the advent of the 8Ω speaker. This made a dual secondary winding on the output transformer popular, giving an output impedance of 4 or 16Ω. My calculations show that with a 4Ω load, a cathode resistor of 964Ω is required, and a feedback resistor of 1728Ω; with 16Ω loads they should be 753Ω and 3456Ω respectively. The method of calculating the feedback capacitor was not explained, but this should be less critical than the resistor values, and it should be adequate to adjust this proportionately.

The required values could be obtained in the case of each resistor

by using two parallel resistors of standard values as in the article, values as follows:

**Stephen Cole**  
Winscombe  
Avon

## I can't hear you

For once I find myself in agreement with Ben Duncan, on the issue of the suitability of Windows (Review of Micro-CAP V, *EW+WW* Sep '95). It seems absurd that professional pc users should be saddled with a software package that appears to be a re-invention of an operating system designed in the early seventies for children. Windows is ok for the novice user, but without much doubt anybody with a modicum of experience with a standard keyboard would find it more efficient than a mouse. Windows is, in my opinion, poorly documented, slow, cumbersome and not very logical, and a running joke among my computer literate friends. Unfortunately it is difficult to get by without it, and maintain compatibility.

To load and run Windows at an acceptable speed requires no less than a 486 – most pcs in our department are 386s – at least 8Mb of ram and a large fast hard disk. This hardware is only now becoming acceptably cheap, but Microsoft would like us to move up to Windows 95 with even greater demands on our hardware. To quote one John McCormick, "Why would anyone in their right mind use Windows for anything? You can always buy a slower computer if yours is too fast!" (from "It's not a Bug, It's a Feature!" by David Lubar).

Unfortunately that is the end of good news for Ben. In his article 'Simulated attack on slew rates' (*EW+WW*, April '95) Ben boldly states on p. 307 that "...the headroom is demonstrably safer for drive units and ears alike – no matter how counter-intuitive this seems" in the course of his justification of very high slew rates and the reproduction of "...music transients above 165V...". Ben opened the piece by outlining the high frequency nature of the sound "during an Iron Maiden gig" engineered by a colleague.

*New Scientist* reports (p5, 27 Jan '96 No. 2014, Australian edition) that "rock concerts are more likely to damage your hearing than listening to a personal stereo or going clubbing", according to French hearing specialist Christian Meyer-Bisch. This conclusion is the result of a study of 1364 people, and

## Best rf article '95

Entries for this challenge are currently being evaluated. We hope to be able to make an announcement about the winner in next month's issue.

it is the high frequency content of rock that is identified as the major cause. "Rock is much tougher on the ear at high frequencies than classical music. When played at the same volume on a CD player, the music of heavy metal bands, such as Iron Maiden, is far louder at high frequencies than a piece of Vivaldi" (I think that should be "a piece by Vivaldi", I doubt that there would be many pieces of Vivaldi left). The situation is much worse at rock concerts because of the much higher power.

Ben is quite wrong. It is sensible to keep listening levels moderate, particularly for extended periods and especially for high frequencies. There is no good reason to believe that high slew rates are less damaging to the ears. In fact the reverse is more likely to be true. Higher sound levels are more likely to increase that risk of permanent hearing loss. Ben would be well advised to keep some of his 'counter-intuitive' ideas to himself lest he – and his colleague with Iron Maiden – become the target of litigation from deaf concert goers.

**Phil Dennis**  
University of Sydney  
Australia

## Cable rejection

If I manage to get a common-mode rejection of 3000dB does this mean the end of the universe, and we all get sucked into an audio black hole? (We all know that black noise is the equal absence of noise/Hz).

On a more realistic note, I find a cable tolerance of a couple of percent to be optimistic; have you measured a cable that has been on the road for six months or so, trodden on, run over, stretched over balconies and generally abused. Have you measured, in real life, such a cable? There is no mention of other cables such as star-quad, or multicore.

Many fixed installations use the Krone IDT method, or similar, involving overall screened cable with say 48 different signal pairs – all with various levels of signal and impedance imbalance. I've used this system a few times. Implemented with care, provides a competent way of installing audio systems.

Just simulating a single cable seems very simplistic. These days you have to consider the whole system, although a basic understanding of common-mode rejection ratio is essential.

Although I have not been involved directly with professional audio for a couple of years I found that:

- In practice you cannot beat the 5534 differential amplifier for a line receiver with a couple of 22pF trim capacitors for trimming common-mode rejection ratio. The single op-amp differential stage is fine for local use.

- The SSM2142 is a poor device with not very good output common mode rejection, and its relatively noisy. Porter produced a far superior balanced output stage, published in *EW* ca 1989. This had a cm rejection ratio of at least 60dB across the audio bandwidth – even built on veroboard.

Please can Ben Duncan stop pushing Microcap and SSM devices – and stop living in SimCity?  
**Martin Griffith**  
Compuserve

## Summing up Foster Seeley

I was interested in the article on the Foster Seeley detector in your Dec issue.

I feel the author makes heavy weather of its operation. A qualitative description of the operation of the circuit is as follows:

- The primary voltage & the voltage injected into the secondary circuit are in phase – as with all transformer circuits.
- At resonance, current in the secondary circuit is in phase with the injected voltage; this is more easily seen if the secondary circuit is drawn as a series circuit.
- Output voltage across the tuning capacitor lags this current by 90°.
- Thus, the accessible primary and secondary voltages differ by 90° at resonance, as normally drawn in analyses of the circuit.
- Off resonance, the phase of the current to the injected voltage varies, so varying the phase of the output and primary voltages.
- As a side issue, an rf transformer cannot usefully be double-tuned – primary and secondary – if it is tightly coupled. The two capacitors are just in parallel.

Regarding the ratio detector, I prefer to regard it as a sampling circuit. The voltage across the secondary switches the diodes on at its peak; and at that instant, they pass the instantaneous value of the primary voltage to the af output point (where it is stored by the capacitors, when the diodes cease to conduct). At resonance, this primary voltage is zero at the peak of the secondary, because the two are in quadrature: off resonance, it varies to give the af output.

I hope these points may help some who find the operation of the circuit difficult to picture from the bare analysis.

**J.W.E. Jones**  
South Australia

## Sallen & Key disadvantages

Following recent correspondence on the Sallen and Key filter configuration, I would like to remind readers of a further weakness in the practical implementation of the low-pass configuration. The signal passes through a resistor and then has a path, through the supposed 'feedback' capacitor, to the filter output. If the op-amp output

impedance is extremely low – which we assume – then this signal path is effectively shunted to ground.

In reality, however, the output impedance of an op-amp rises with frequency as the open-loop gain falls. It can reach many tens or even hundreds of ohms. Then, high-frequency components of an input signal can leak through to the output.

This failing can be plotted on even the student version of PSpice, where the filter attenuation plot reverses at high frequencies, passing noise and distortion components of the drive signal. It does not occur with the low-pass Rauch filter.

**Simon Bateson,**  
Hutton Rudby  
North Yorkshire

# HELP Wanted

## Any queries?

If you have any electronics-related questions that you have not been able to find an answer to, why not see if other readers can answer them? Simply write to me, the editor, at the address on page 267, fax 0181 652 8956, or e-mail [martin.eccles@rbp.co.uk](mailto:martin.eccles@rbp.co.uk).

## Can you answer this?

Could one of your readers explain to me a phenomenon connected with the distribution of lines of magnetic flux, of strength,

$$H = \frac{NI}{2\pi r}$$

around a single length of wire carrying a dc current of 1A. With this wire passing through a card at right angles to the wire; if soft iron filings are sprinkled around the wire magnetic lines may be observed which form concentric circles around the wire with spaces between them.

My question is this: has some form of standing wave been set up in the spacing between 'crests'? Being a wavelength the speed of which may be expressed as:

$$\sigma = f_0 \lambda \text{ms}^{-1}$$

where, were it not for friction would represent the speed of a

magnetic field of strength  $H$  with frequency  $f_0$  where  $f_0$  is the frequency of electrons moving around a closed circuit the direction of propagation, as with Huygens wave theory being at right angles to the tangent, of each circular path, i.e. radially. A wire being taken as the simplest and most easily analysed configuration.

Dust tube analogy. If lycopodium powder is placed uniformly within a tube and a pure note of frequency  $f$  sent down the tube, disturbances would be set up which if in antiphase with the reflected wave would cause the powder to respond by 'clumping' in heaps at the points of little disturbance, i.e. at rarefactions. This analogy is used to consider the concentric lines of force around a single turn of wire.

I would appreciate any information you may be able to supply me with.

**Terence George Heatley**  
London

# "Your low cost route to embedded 8051"



## MICRO-PRO 51

- "Hardware/software upgradeable programmer for the 8051 family"*
- Accepts up to 40 pin DIL directly via Aries ZIF socket
  - Surface mount and PLCC package adaptors available as optional extras
  - Atmel 8951/8952 & 1051/2051 ICE cables available as optional extras
  - Field programmable hardware to allow future upgradeability
  - Fast PC parallel port based design

**ONLY £125**

Programming support for the following devices:  
 Genelic 8751/8752 microcontrollers from Intel & Philips  
 Atmel 8951/8952 FLASH replacements for the 8751/8752  
 Atmel 1051/2051 20-pin FLASH 8051 microcontroller derivatives  
 Serial EEPROMS families: 24Cxx, 93Cxx, 59Cxx, 25Cxx (optional extra)



## KEIL C51 PK LITE

- "The complete Ansi-C development environment for the 8051"*
- Optimising Ansi-C compiler
  - dscope 51-8051 software simulator & source level debugger
  - uVision-Integrated Windows based C51 project management system
  - Support for most 8051 derivatives eg. Atmel, Intel, Siemens etc.
  - Numerous microcontroller language extensions for the fastest, tightest code

**ONLY £110**

(Restricted to 2K total program code, SMALL model only)



## Embedded C51 Starter Systems for the 8051 family

*"Everything you require to develop an embedded 8051-based project in C"*

- MICRO-PRO 51 device programmer
- KEIL C51 PK LITE
- Sample Atmel FLASH microcontrollers
- Full suite of C51 demonstration software



Atmel 8051 FLASH Microcontroller Range

	8951	8952	1051	2051
FLASH code ROM	4K	8K	1K	2K
RAM	128	256	64	128
I/O	32	32	15	15
Timer/Counter (16 bit)	2	3	1	2
Serial Port	YES	YES	NO	YES
Interrupt Sources	5	8	3	5
Pins (DIL/PLCC)	40/44	40/44	20	20
Special features		Timer 2	Comparator	Comparator

**895X-ST (ONLY £215)**  
 Comes complete with samples of Atmel 8951 and 8952 40 pin microcontrollers  
**X051-ST (ONLY £199)**  
 Comes complete with samples of Atmel 1051 and 2051 20 pin microcontrollers

Equinox Technologies, 229 Greenmount Lane Bolton BL1 5JB, Lancashire, ENGLAND  
 Tel: (01204) 492010 Fax: (01204) 494883 Int, dialling code (UK +44 1204)  
 E-mail: sales@equintec.demon.co.uk Web Page: www.demon.co.uk/equintec  
 All prices exclusive of VAT and carriage.



CIRCLE NO. 132 ON REPLY CARD

## New Mini Camera & Special Offers

- New mini waterproof TV camera 40x40x15mm requires 10 to 16 volts at 120mA with composite video output (to feed into a video or a TV with a SCART plug) it has a high resolution of 450 TV lines Vertical and 580 lines horizontal, electronic auto iris for nearly dark (1 Lux) to bright sunlight operation and a pinhole lens with a 92 degree field of view, it focuses down to a few CM, it is fitted with a 3 wire lead (12v in gnd and video out).....£93.57+VAT = £109.95 or 10+ £89.32+VAT = £104.95
- High quality stepping motor kits (all including stepping motors) "Comstep" independent control of 2 stepping motors by PC (Via the parallel port) with 2 motors and software.....Kit £67.00  
 Stepper kit 4 (manual control) includes 200 step stepping motor and control circuit.....£23.00
- Hand held transistor analyser it tells you which lead is the base, the collector and emitter and if it is NPN or PNP or faulty.....£38.45
- spare 6v battery.....£1.20  
 LED 3mm or 5mm red or green... 7p each yellow 11p each cable ties 1p each £5.95 per 1000, £49.50 per 10,000
- Rechargeable Batteries  
 AA (HP7) 500mAh...£0.99 AA 500mAh with solder tags.....£1.75  
 AA 700mAh.....£1.75 C(HP1) 1.2AH.....£2.20  
 D 4AH with solder.....£3.60 D(HP2) 1.2AH.....£2.60  
 D 4AH with solder.....£4.95 PPS 8.4V 1100mAh.....£4.95  
 tags.....£2.50 Sub C with solder.....£2.50  
 12AA with solder.....£1.55 1/3 AA with tags (Philips CTV).....£1.95  
 AAA (HP16) 180mAh.....£1.75  
 Standard charger charges 4 AA cells in 5 hours or 4C or Ds in 12-14 hours + 1xPP3 (1, 2, 3 or 4 cells may be charged at a time).....£5.95
- High power charger as above but charges the C's and D's in 5 hours, AA's, C's and D's must be charged in 2's or 4's.....£10.95
- Nickel Metal Hydride AA cells high capacity with no memory. If charged at 100mA and discharged at 250mA or less 1100mAh capacity (lower capacity for high discharge rates).....£3.75
- Special offers, please check for availability.  
 Slick of 4 x 2x18mm, Nicad batteries 17x16mm dia with red & black leads 4.8v.....£5.95  
 5 button cell 6V 280mAh battery with wires (Varta 5x250Dk).....£2.45  
 Shaded pole motor 240V ac 3mm x 20mm shaft 80 x 60 x 55mm excluding the shaft 14.95 each  
 115v AC 80v DC motor 4x22mm shaft 50mm dia x 60 long body (excluding the shaft) it has a replaceable thermal fuse and brushes.....£4.95 each (£3.95 100+)  
 7 segment common anode led display 12mm.....£0.45  
 LM357 T03 case variable regulator.....£1.95  
 .....£1.44 100+  
 GaAs FET low leakage current 58878.....£12.95 each  
 .....£9.95 10+, £7.95 100+  
 BS250 P channel mosfet.....£0.45  
 BC559 transistor.....£3.95 per 100  
 BC547 A transistor.....£0.30 for £1.00  
 74LS05 hex inverter.....£10.00 per 100
- Used 8748 Microcontroller.....£3.50  
 SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet.....£1.95  
 AM27502.....£1.25 each (90p 100+)  
 CD4007UB.....10p 100+ (6p 1000+)  
 Sinclair light gun terminated with a jack plug and PPS clip gives a signal when pointed at 50Hz flickering light with output wave form chart.....£3.95  
 DC-DC convertor Reliability model V12P5 12v in 5v 200mA out 300v input to output Isolation with data.....£4.95 each or pack of 10 £39.50  
 Hour counter used 7 digit 240v AC 50Hz.....£1.45  
 QWERTY keyboard 58 key good quality switches.....£6.00
- new  
 Airfax AB2905-C Large stepping motor 14v 7.5 step 27ohm 68mm dia body 6.5mm shaft.....£8.95 or £200.00 for a box of 50  
 Polyester capacitors box type 22.5mm lead pitch  
 0.9uF 250vdc.....18p each  
 14p...100+ 9p...1000+.....20p each  
 1uF 250vdc.....15p...100+ 10p...1000+.....20p each  
 1uF 50v bipolar electrolytic axial leads.....15p each  
 0.22uF 250v polyester axial leads.....7.5p 1000+ 7.5p 100+  
 Polypropylene 1uF 400vdc (Wima MKP10) 27.5mm pitch 32x29x17mm case.....7.5p each  
 .....60p 100+  
 Philips 125 series solid aluminium axial leads - 33uF 10v & 2.2uF 40v.....40p each  
 .....25p 100+  
 Philips 108 series long life 22uF 65v axial.....30p each  
 .....15p 1000+  
 Multilayer AVX ceramic capacitors all 5mm pitch 100v  
 100pF, 150pF, 220pF, 10,000pF (10n).....10p each 5p...100+ 3.5p...1000+  
 500uF compression trimmer.....60p  
 40 uF 370vdc motor start capacitor (dialectrol type containing no PCBs).....£5.95 or £49.50 for 10  
 Solid carbon resistors very low inductance ideal for RF circuits - 27ohm 2W, 68ohm 2W.....25p each  
 .....15p each 100+  
 We have a range of 0.25w, 0.5w, 1w and 2w solid carbon resistors, please send SAE for list  
 PC-400W PSU (Intel part 901035-001) with standard motherboard and 5 disk drive connectors, fan and mains inlets/output connectors on back and switch on the side (top for tower case) dims 212x149x149mm excluding switch.....£138.00 for 6  
 MX180 Digital multimeter 17 ranges 1000vdc 750vac 20ohm 200mA transistor Hfe 9v and 1.5v battery test.....£9.95  
 AMD 27256-3 Eproms.....£2.00 each £1.25 100+  
 Inmac deluxe anti-glare static control panel window size 228x161mm, overall size 264mmx200mm held to the monitor with hook & loop tape pads.....£7.95 each  
 DIP switch 3PCO 12 pin (ERC SDC-3-023).....60p each  
 .....40p 100+  
 Disk drive boxes for 3.5 disk drive with room for a power supply, light grey plastic, 67x208x24mm.....£26.00 each  
 .....£7.95 or £49.50 for 10  
 Hand held ultrasonic remote control.....£3.95  
 CV2486 gas relay, 30x10mm dia with 5 wire terminals, will also work as a neon light.....£7.50 per 100

All products advertised are new and unused unless otherwise stated. Wide range of CMOS TTL 74HC 74F Linear Transistors kits. Rechargeable batteries, capacitors, tools etc always in stock. Please add £1.95 towards p&p. VAT included in all prices.

**JPG Electronics, 276-278 Chatsworth Road, Chesterfield S40 2BH**  
 Access/Visa Orders (01246) 211202 Fax: 550959  
 callers welcome 9.30am to 5.30pm Monday to Saturday

CIRCLE NO. 133 ON REPLY CARD

# LEN COOKE ENTERPRISES

UNIT 5, SOUTHALL ENTERPRISE CENTRE, BRIDGE ROAD, SOUTHALL, MIDDLESEX UB2 4AE, ENGLAND  
 TEL: 0181 813 9946 FAX: 0181 574 2339

- HP 3400A rms Voltmeter.....£150  
 Tek 521 PAL/NTSC Vector Scope.....£375  
 Tek 7A26A/7A18 x2/7B53A.....£550  
 Tek 7A26/7V53A plug-in.....each £125  
 Hameg 203-6 Scope.....£275  
 Hitachi V-212 Scope.....£185  
 Hameg 205-2 Digital Storage.....£450  
 HP 1740A 100Mhz Scope.....£375  
 Tek 465B 100Mhz Scope.....£385  
 Tek 475 200Mhz Scope.....£450  
 Tek 2215 60Mhz Scope.....£450  
 Fluke 5200A AC Calibrator.....POA  
 Fluke 5205A Power Amplifier.....POA  
 Tek 7L18 Spectrum Analyser.....£2,850  
 HP 3580A Spectrum Analyser.....£1,200  
 HP 3581C Selective Voltmeter.....£1,250  
 Racal 5002 Wideband Level Meter.....£850  
 HP 8082A Pulse Generator.....£535  
 HP 8011A Pulse Generator.....£450  
 Top Quality Digital Multimeters.....£25 to £125  
 Frequency Counters 520Mhz.....£135  
 Gould J3B Oscillator.....£150  
 Wavetek 182A 4Mhz Function Generator.....£000

We buy all types of Electronic Instruments, in any condition. Factory visits no problem. We are geared for Mail Orders, Import/Export Transactions.  
**Phone or Fax your Inquiry Today.**

CIRCLE NO. 134 ON REPLY CARD

# NEW PRODUCTS

# CLASSIFIED

Please quote "Electronics World" when seeking further information

## ACTIVE

### A-to-D and D-to-A converters

#### Delta-sigma d-to-as.

Two 20-bit, stereo digital-to-analogue converters by Crystal Semiconductor, the CS4327/9 handle an infinitely adjustable sample rate of 1-50kHz. The 4329 uses switched-capacitor analogue, low-pass filtering to give clock-jitter tolerance and a 105dB dynamic range at 20-bit resolution and 112dB s:n ratio; thd+noise is -97dB. CS4327 gives 98dB dynamic range, 110dB s:n and -90dB thd+noise. Sequoia Technology Ltd. Tel., 01734 258000; fax, 01734 258020.

### Linear integrated circuits

#### Video amplifier. EL4093 from

Elantec is a complete, dc-restored video amplifier subsystem, providing accurate dc restoration, 300MHz bandwidth and 1500V/ $\mu$ s slewing. It contains a current-feedback amplifier and a s/h amplifier to stabilise video performance, providing signal acquisition in one line scan. If the ttl-compatible hold input is low, the s/h is used to null the dc offset of the video amplifier; when high, it stores the correction voltage on the hold capacitance to maintain dc correction during the next line scan. METL. Tel., 01844 278781; fax, 01844 278746.

**375MHz buffers. MAX4178/4278** (single) and **MAX496/497** (quad) closed-loop buffers have fixed gains of +1 or +2, give a 70mA output minimum, an output swing of more than  $\pm 2.5$ V into 50 $\Omega$  and tolerate a 70pF load without oscillating. 4178 and 496 have the +1 gain, a 375MHz bandwidth to -3dB (80MHz at -0.1dB) and slew at 1400V/ $\mu$ s, while the other two exhibit 275MHz at -3dB, 120MHz at -0.1dB and a slew rate of 1500V/ $\mu$ s. Supply current is 8mA/channel and differential phase and gain are 0.01° and 0.01%; input voltage offset is 0.5mV and input noise 5.6nV/ $\sqrt$ Hz. Maxim Integrated Products UK Ltd. Tel., 01734 303388; fax, 01734 305511.

### Memory chips

**32bit flash proms. EDI** high-speed, high-density flash SIMM and PLCC modules have a 32-bit data bus in capacities to 32Mbit. They are available in single or dual form, organised as 128K by 32 and 256K by 32 in either package; the 512K by 32 devices as SIMMs only. Micro Call

Ltd. Tel., 01844 261939; fax, 01844 261678.

**1M sram.** Toshiba's **TC55V1664/1864** 1Mbyte, 0.4 $\mu$ m cmos srams offer 15 or 12ns access times, wide bandwidth and 3.3V operating voltage, with performance equivalent to that of 5V devices. Toshiba Electronics UK Ltd. Tel., 01276 694600; fax, 01276 694800.

### Microprocessors and controllers

**Mixed-signal controller.** Microchip's **PIC14000** is compatible with the **PIC16/17** architecture, and has 4K by 14 eeprom and 192byte of ram. Its 5Mips, 8-bit risc core gives 35 single-word instructions, 20MHz operating speed, six internal and five external interrupt sources, eight levels of hardware stack and 38 special-function hardware registers. The 16ms, 16-bit a-to-d converter is accompanied by two multi-range converters, a low-voltage detector, temperature sensor, voltage control and a 4MHz clock. The device is supported by the **PICMaster** development and emulation system. Arizona Microchip Technology Ltd. Tel., 01628 851077; fax, 01628 850259.

### Optical devices

**Low-current isolator. ISP817** from Isocom is an optically coupled isolator that takes a drive current down to 0.5mA, while still producing a high output current - current transfer ratio is 70% at 0.5mA and 100% at 1mA. Forward saturation voltage is 0.4V and i/o voltage isolation is 7.5kV. Isocom Components Ltd. Tel., 01429 863609; fax, 01429 863581.

## PASSIVE

**Transformers. Clairtronic** transformers in both chassis and pcb mounted types are available from ElectroSpeed. The units are made in flame-retardant UL94V-0 material, are designed to meet EN60742/60950 safety requirements and are 100% tested for safety factors. Chassis-mounted types have a single primary and dual secondaries, the series comprising units rated at 6VA-50VA. Pcb types have two secondaries rated at 3VA-12VA. ElectroSpeed. Tel., 01703 644555; fax, 01703 610282.

**Chip resistors.** From the Taiwanese company Yageo comes sub-miniature 0402 chip resistors for both flow and reflow soldering. There is a full range,



from 1/16W to 1W types in values from 10 $\Omega$  to 10M $\Omega$ . Easby Electronics Ltd. Tel., 01748 850555; fax, 01748 850556.

**Chip capacitors.** A new range of chip capacitors on 4in diameter reels containing as few as 500 pieces, made by *miniReel*, come in 0805 and 1206 chip sizes in values from 1pF to 2.2 $\mu$ F and using COG, X7R, Z5U and Y5V dielectrics, depending on value. Flint Distribution. Tel., 01530 510333; fax, 01530 510275.

**Power electrolytics.** A useful life of 10000 hours is quoted by Philips for the **PLL-SI 058/059** series of snap-in electrolytic capacitors, which tolerate temperatures from -40°C to 105°C. Capacitance range is 33-47000 $\mu$ F at  $\pm 10\%$  and at voltages of 10-100V and 200-400V. These units are charge and discharge proof. Gothic Crellon Ltd. Tel., 01734 788878; fax, 01734 776095.

### High C, high voltage, small size.

**Wima MKS2** capacitors are particularly useful for decoupling, values available including 0.01 $\mu$ F to 2.2 $\mu$ F, 3.3 $\mu$ F and 4.7 $\mu$ F in a 5mm pitch encapsulated package and rated at 50Vdc or 30Vac. Tolerances are  $\pm 20\%$ ,  $\pm 10\%$  and  $\pm 5\%$ . Europa Components & Equipment plc. Tel., 0181-953 2379; fax, 0181-207 6646.

### Connectors and cabling

**Stackable board connector.** To connect boards in a parallel stack at varying distances, Harting Elektronik offers the *har-mik* connector system, which uses male connectors of a constant height and female connectors of different heights. Harting Elektronik Ltd. Tel., 01604 766686; fax, 01604 706777.

### Mixed-signal ICs

**Sensor/actuator.** Dallas announces the **DS2407**, addressable switch ic, a sensor/actuator to perform closed-loop control from a PC via an RS-232 link. The sensor responds to a stimulus and inputs it to the PC, which arrives at a decision and instructs the actuator to switch on or off, all over a twisted-pair wire of up to 300m in length, which includes power for the chip; driver software provides GUIs on the PC screen running something like LabView. Many such ics may be connected to the same wire to be controlled by a central PC, since each ic has its own serial number on-chip. Dallas Semiconductor Corporation. Tel., 0121-782 2959; fax, 0121-782 2156.

### Board-mating connectors.

**Samtec** make connectors to join printed boards together at right-angles or parallel to each other. They are available with surface mounting or through-hole terminations and on pin pitches of 1.27mm, 1.27 by 2.54mm and 2mm. Samtec UK Ltd. Tel., 01236 739292; fax, 01236 727113.

**Chip carriers.** Plastic-leaded chip-carrier sockets by Data I/O, provide reliable mounting for ic programming in middle to high-volume production. The sockets are available for the company's 2900, 3900 and *UniSite* programmers and fit the receptacle on the programmer, replacing programming adaptors. Data I/O Ltd. Tel., 01734 440011; fax, 01734 448700.

## NEW PRODUCTS CLASSIFIED

Please quote "Electronics World" when seeking further information

### Cable-to-cable connector.

Framatome introduces the *Trim Trio SMS Qikmate*, which connects two free cables of widely varying diameters, strain relief being incorporated. Moulded hoods are provided and there is provision for polarising the sockets with extra pins. Framatome Connectors UK Ltd. Tel., 01582 475757; fax, 01582 476203.


### Displays

**CRT shielding.** Magnetic shielding material for colour monitors is produced by Ad-Vance Magnetics to address the requirement for alternating and static field shielding in heavy industry and laboratories where higher than usual fields are experienced, of the order of 10-50 oersted. It is available in 0.64mm sheet and is usually used in two or three layers to reduce a static field of 45 oersted, for example, to 0.16 oersted near the centre of the enclosure. Ginsbury (UK) Ltd. Tel., 01634 290903; fax, 01634 290904.
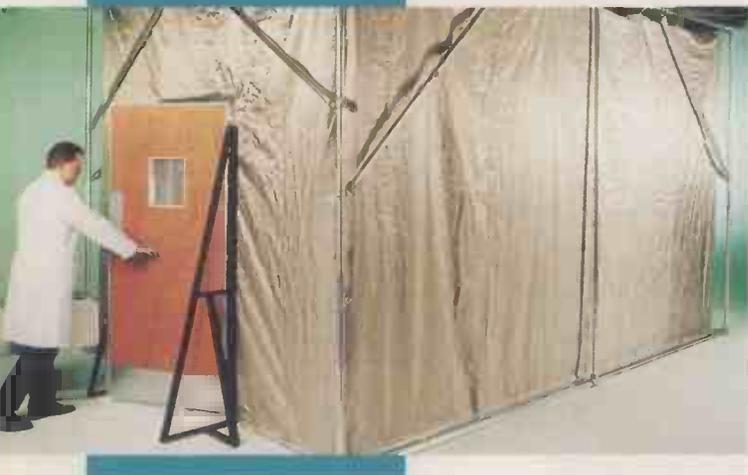
### Filters

**Emc filters.** Three new ranges of equipment filters by MPE are to protect against incoming and

Self-assembly emc test chamber. For emc testing, Seaward's *Easi-Screen* is a lightweight emc test compartment in kit form for assembly. Attenuation is better than 60dB. Construction is of polyester/copper/nickel shielding fabric with steel and veneer door and particle board and sheet steel floor. A 16A mains filter and distribution system with an isolator is provided, as is powered ventilation, coaxial inputs and a 60mm waveguide. The chamber is easily dismantled for storage. Seaward Electronic Ltd. Tel., 0191-586 3511; fax, 0191-586 0227.



outgoing interference at power inputs and cover 1-15A. General-purpose dc types are 100Vdc rated, while the ac filters and mains-input types for switched-mode supplies are rated for 250Vac at 50/60Hz. All use feedthrough capacitors and can be bulkhead mounted to help meet the EMC Directive at high frequencies. A catalogue is available. MPE Ltd. Tel., 01371 875071; fax, 01371 875037.

### Hardware

**Power backplanes.** 13-slot C and D sized, 12-layer VXIbus backplanes from Vero can handle powers of more than 3kW. The 9U size has dual 0V ground busbars and four laminated power busbars for low-impedance power distribution or seven voltage rails. The 6U size has two of each. Both conform to the latest VXIbus specification. All sizes have decoupling capacitors in the termination area and additional positions for decouplers at each slot position. Vero Electronics Ltd. Tel., 01489 780078; fax, 01489 780978.

**Command panel.** Rittal offers the *VIP 6000* housing for machine tool controls and process control stations. It takes all the common control systems and is available with a keyboard housing or tray, the housing being designed to take a machine control panel or a keyboard, the keyboard tray holding a standard keyboard. Screw channels on a 25mm matrix are provided for individual layout design and there is easy access from the rear. Rittal Ltd. Tel., 01709 704000; fax, 01709 701217.

**PCMCIA kit.** Molex has the *Snapper* kit, which contains all the bits and pieces needed to make a PCMCIA card. The resulting card is compatible with both PCMCIA and JEIDA standards; the Type II kit containing a black plastic frame, a stainless steel snap-on cover, a 68-



contact surface-mounted connector and a 15-position 1.27mm-pitch input/output connector. The *Snapper* cover only needs a small arbor press to close and seal the unit. Electrospeed. Tel., 01703 644555; fax, 01703 610282.

### Test and measurement

**Clamps.** Northern Design says it has the biggest selection of clamp-on current probes in the civilised world, from the *Micro 2000* finger-operated miniature device for 1mA-200A measurements, to the *P Series* for measurements to 3000A. The range of jaw sizes covers conductors from 15mm cables to 120 by 50mm bus bars. Output can be ac or dc voltage or current to accuracies of 0.25% in the miniature versions or Class 1 for the bigger types. Northern Design (Electronics) Ltd. Tel., 01274 729533; fax, 01274 721074.

**Microwave test.** MI's *6250 Series* millimetre wave reflectometers extend the insertion and return loss measurement performance of the 6200 microwave test set. Model 6255 multiplies the output of the 6200 to give frequencies in the 50-75GHz range (V band), while the 6256 produces frequencies from 75GHz to 110GHz (W band). Marconi Instruments Ltd. Tel., 01438 742200; fax, 01438 727601.

**Network analyser.** Rohde & Schwarz introduces the *ZVR* vector network analyser family which, among its other virtues, is modular in form for simple future upgrading. Measurement time is under 120µs per test point, which allows over 25 sweeps/s with 200 points and over 130dB dynamic range with a 10Hz if bandwidth. There are three family members, all with integral generator, test set and multi-channel receiver, and the two lower-priced units can be upgraded to perform as the most expensive one. Rohde & Schwarz UK Ltd. Tel., 01252 811377; fax, 01252 811447.

**150MHz dso.** From Metrix, the *OX2000* 150MHz, four-channel, programmable digital storage oscilloscope, which can capture data at up to 200Msamples/s in single-shot mode and to 50Gsamples/s for repetitive waveforms. Input sensitivity is 2mV-10V/div and sweep speed 2ns-50s/div. A PCMCIA slot allows long-term storage and a colour VGA output port is provided, as well as interfaces for printing or connection to a PC. Metrix Electronics plc. Tel., 01384 402731; fax, 01384 402732.

**GPB multimeter.** Model *1705GP* from Thurlby Thandar is a GPB version of the 1705 dual-display multimeter, possessing IEEE-488 and RS-232 interfaces, either of which controls the meter functions and reads back results from the display or the built-in data logger. This 4.5 digit instrument counts to 12000, has a 10µV, 10mΩ, 0.1µA resolution and direct voltage accuracy of 0.04%. Main and secondary displays show two simultaneous readings and the secondary one will show measurement units, the results of calculation, two different parameters of one signal or two different signals. Thurlby Thandar Instruments Ltd. Tel., 01480 412451; fax, 01480 450409.

**Audio monitor.** Audix's *ARM* audio monitor is now in a new version with 24 stereo inputs instead of twelve; it is meant for on-air broadcast use. There are separate buffered and control outputs for an internal mono cue speaker, an external stereo loudspeaker and stereo headphones connected to the panel's jack. There is an external communications input to inject feeds to the cue speaker. Audix Broadcast Ltd., Tel., 01799 542220; fax, 01799 541248.

**Spectrum analyser.** Advantest's *R3263* spectrum analyser is intended for use in digital mobile communications. It is small and light,

Please quote "Electronics World" when seeking further information

but provides comprehensive facilities in the 9kHz-3GHz range, with selectable bandwidth from 300Hz to 5MHz. The screen is a 6.5in colour tft type displaying a 100dB range of levels at a horizontal resolution of 1000 points. There is gated and delayed sweep and a timing function to 20µs for burst measurement and one keystroke starts fully automatic test sequences. Two PCMCIA slots allow storage, set-ups and test programs. Rohde & Schwarz UK Ltd. Tel., 01252 811377; fax, 01252 811447.

### Literature

**Display panels.** Thin-film transistor, active-matrix lcd panels by NEC are the subject of a new brochure, which shows types from a 6.5in unit for instruments to the new 1280 by 1024-pixel, 13in panel for monitors. The brochure contains a section to explain the operation of tft active-matrix displays. NEC Electronics (UK) Ltd. Tel., 01908 691133; fax, 01908 670290.

**Valves.** A note from Billington Export offers its 1996 catalogue, which contains cross-referencing data, and points out that the company has the

### Production equipment

**Pcb test.** Polar's *Toneohm* family of low-cost printed-board short-circuit fault locators is extended to include the 550A and 850A, which provide 0-40mΩ ranges for short-circuit tracing on boards with wide tracks. The 850A also has current tracing for shorts on bus-structured boards; both are usable on bare or loaded boards. In use, probes are moved along the tracks while a tone guides the user to within a few millimetres of the fault. All data is presented on a 3.5-dlgit lcd. Drive is voltage limited to avoid damage. Polar Instruments Ltd. Tel., 01481 53081; fax, 01481 52476.



SV811 power triode from Svetlana and the improved Chinese 300B with graphite anode. There is also a separate crt catalogue and both are free. Billington Export Ltd. Tel., 01403 784961; fax, 01403 783519.

**Alarms.** Roxburgh's complete range of audible alarms and indicator lights is described in the 1996 catalogue, now available. Components included are magnetic buzzers and transducers, piezoceramic transducers, pcb and panel alarms, among which is the *Sonitron* range. There is also a catalogue on the range of *Rafi* electromechanical components – switches, lamps and keyswitches. Roxburgh Electronics Ltd. Tel., 01724 281770; fax, 01724 281650.

**Floppy catalogues.** Minicat Ltd has a compression technique that will put 200 colour images and 1000 pages of text on a 3.5in floppy disk – about 450 times as much as usual. The company also offers an interactive slideshow facility with fade transitions for conferences, running under Windows. MiniCat Ltd. Tel./fax, 01923 823633.

**Hitachi on CD-ROM.** A new CD-ROM data book from Hitachi covers the H8 series of microcontrollers and the *SuperH* family of 32-bit risc devices, the disc being effectively equivalent to 19,000 pages of data. Macintosh and Windows users can read the disk. Hitachi Europe Ltd. Tel., 01628 585163; fax, 01628 585160.

### Materials

**Liquid resist.** Electra announces *Photrak*, which is a liquid photoimageable etch and plate resist for high-resolution pcbs; it can be applied to give 1mil resolution. Using standard 5kW equipment, exposure time is 15-20 seconds and with 7kW, 10 seconds. The material increases developer and stripper bath life by 100%. Application is by screen printing, curtain coating, electrostatic spray or roller and the formula is suitable for use with acid and alkaline etchants, as well as with acid gold-plating solution. Electra Polymers and Chemicals Ltd. Tel., 01732 811118; fax, 01732 811119.

### Printers and controllers

**Thermal printer.** Able Systems has the *Ap1000*, a panel thermal printer in a clear plastic case so that the amount of paper left is visible. It comes in 24 or 42 column form and gives a speed of 96 characters/s, bidirectionally. A full IBM character set is provided. Able Systems Ltd. Tel., 01606 48621; fax, 01606 44903.

**Board inspection.** *Alpha HI-Check 500Z* is an accurate, non-contact method of inspection and



measurement for printed boards, the workpiece being shown on a high-resolution monitor and/or printed copy. The instrument gives readings down to  $\pm 3\mu\text{m}$  and visual inspection of pads at a magnification of 14 to 270, a 45° attachment allowing all-round vision. Focus is automatic and the measurement readout is shown on screen. Data may be transferred to a pc running Excel. Alpha Metals. Tel., 0181-665 6666; fax, 0181-665 4734.

### Power supplies

**Switcher controller.** Linear's *LTC1430* switching regulator controller converts 5V to 3.3V, 2.5V or other processor core voltages at up to 15A and is for use in equipment based on *Pentium* and *P6* processors. Efficiency is near 95% at high currents and good transient response reduces the size of filter capacitors required. The voltage feedback technique used eliminates the current sensing resistor commonly used. A soft start feature is incorporated. Micro Call Ltd. Tel., 01844 261939; fax, 01844 261678.

**SOT-23 voltage reference.** *MAX6120* from Maxim is said to be the first micropower, 1.2V three-terminal reference in this package. It is meant for 3V equipment where battery saving is essential and is a low-power alternative to two-terminal shunt devices, since its supply current of 70µA maximum is independent of input voltage. Maxim Integrated Products UK Ltd. Tel., 01734 303388; fax, 01734 305511.

**10W, open-frame supplies.** Toko's *SW10* series of 10W ac/dc open-frame supplies stand only 18mm off the board and take up 65 by 70mm of board space. Input is universal – 85-246V ac – and the units give a single output of 5V, 12V, 15V or 24Vdc, led status indication and a fine output adjustment being standard. Closed-frame types are available. Melcher Ltd. Tel., 01425 474752; fax, 01425 474768.

**Rapid-response FORS.** If uninterrupted power supplies look likely to be interrupted, Fiskars Power Systems will instantly leap to attention and send in the cavalry. *FORS* (Fiskars On-line Remote Service) is a

### Navigation systems

**PCMCIA GPS.** Using only 650mW, Rockwell's *NavCard LP* PCMCIA Global Positioning System receiver is a five-channel unit tracking up to nine satellites to give position, direction and speed, mainly for land vehicles and marine use. It is complete with an integrated antenna, removable to allow the use of an optional remote antenna. Software includes *CityTracker* for urban navigation. If a differential receiver is available, the unit accepts input to improve position resolution to 10m from 100m. Telecom Design Communications Ltd. Tel., 01256 332800; fax, 01256 332810.

system whereby the company keeps tabs on its ups units in the field 24 hours a day by way of modems and GSM links, automatically and remotely inspecting all systems, listening for alarms and collecting the relevant data if it thinks it sees a problem. If it does, it calls out the duty engineer and gives him all the necessary data, although he can call for more if he wants to. The service is available for Fiskars PowerServer 30/40, UPS9000/10000 systems. Fiskars Electronics Ltd. Tel., 01734 306600; fax, 01734 305868.

**2.5W SOT-23 rectifiers.** Microsemi's *Powermite* family of small semiconductor devices now includes a 2.5W, fast 1A schottky rectifier, due in part to the design of the surface-mounted package. Its metal base wraps round each side of the device to increase the heat flow to the board. Its success is demonstrated by its ability to cope with an 8.3ms surge of 70A. Solid State Supplies Ltd. Tel., 01892 836836; fax, 01892 837837.

### Switches and relays

**Photovoltaic relay.** IR has increased its family of photovoltaic relays for Type II PCMCIA fax/modem cards with the *PVO402P*, which is only 2mm high and consists of a double-pole, normally open, solid-state device incorporating both relay and ring

## NEW PRODUCTS CLASSIFIED

Please quote "Electronics World" when seeking further information

detector. Input/output isolation is 3.75kVrms. Output stage is a Hexfet circuit. International Rectifier. Tel., 01883 713215; fax, 01883 714234.

**SM dip switches.** Grayhill offers the *Piano-style* and standard-profile spdt, spst and 2pst dual-in-line switches in surface-mount form, made from material to withstand infrared reflow soldering. Roxburgh Electronics Ltd. Tel., 01724 281770; fax, 01724 281650.

**Windows '95 keyboard.** Cherry's Windows '95-compatible keyboard, the *G83-6105*, is a 105-key device with three dedicated keys on the spacebar row: an applications key to pop up the content menu (equivalent to the right mouse button in some applications); and left and right keys for the user interface and its shortcuts. Its membrane switch combined with a rubber sheet, whose domes are individually moulded to provide a uniform response, give an improved action in any position. Cherry Electrical Products Ltd. Tel., 01582 763100; fax, 01582 768883.

**Reliable keypads.** Oil from the fingers is kept from Lucas rubberised keypads by means of a layer of polyester in *Duralith* barrier switches. These are polyester half switch consisting of a contact layer, screened contacts and a spacer layer. A range of options includes a choice of tactile response and pcb substrates. Lucas Control Systems Products. Tel., 01535 661144; fax, 01535 661174.

**Quiet, solid-state relays.** Solid-state relays, by Laser Energy, in the *ECO* range 'totally eliminate' additive radio frequency interference, meeting VDE 0871 well enough to class the device as noise-free. Current handling is 10-100A and forward voltage is reduced to enable a reduction in heat sink size. No additional filters are needed. Campbell Collins Ltd. Tel., 01438 369466; fax, 01438 316465.

**Keylock switches.** Grayhill's *Series 03* range of low-cost keylock switches is now available in the UK, a range that includes multi-level security switches and basic on-off types. There is an on-off model measuring 0.6in in diameter, a two-position dpdt switch, a three-position progressive-contact switch and a multi-level type giving four-operator security and limited access to switch positions. Switches have ratings of 1-2A at 240V ac. EAO-Highland Electronics Ltd. Tel., 01444 236000; fax, 01444 236641.

**Octal bus switch ics.** Bus switches in the *FST3xxx/32xxx* families serve to solve the problems associated with shared memory and multiple processors in common buses without additional propagation delay, timing skew, noise or power consumption. Quiescent current is typically 0.1µA. Integrated Device Technology. Tel., 01372 363734; fax, 01372 378851.

**Pot. switches.** Eco switches by Omeg come in rotary and push-push varieties and are meant to mount directly onto the company's 16mm ECO potentiometers. The rotary switches are produced in ratings of 1A and 4A at 250V, in single and two pole types and terminated in pcb pins or tags. Push-push models are 10A, 250V units and are also available as modules for other manufacturers. Power rating of both types is 0.25W in linear ranges of 1kΩ to 1MΩ and 0.12W for non-linear types from 4.7kΩ-470kΩ. Omeg Ltd. Tel., 01342 410420; fax, 01342 316253.

**Attenuator relays.** Teledyne's *RF300* relays are small (7mm high), are emi-shielded and handle high frequencies and are therefore suitable for use in uhf attenuators. Rf signal repeatability is 241±0.1dB from zero to 3GHz. Teledyne Electronic Technologies. Tel., 0181-571 9596; fax, 0181-571 9637.

**Keyboard switches.** Providing a snap action and a satisfying feel, NSF *Keylite* keyboard switches come in various colours and designs and possess momentary or latching action. They accept one or two leds and are fitted with lugs resistant to solder creepage and gold/silver-plated contacts. Designs in the range include half key, stepped, paddle, sloping and illuminated types. Lucas Control Systems Products. Tel., 01535 661144; fax, 01535 661174.

**Trip amplifiers.** Providing relay contact at preset ac and dc levels, *UltraSlim Pak* trip amplifiers from Weidmuller Klippon are easily configured, with setpoints from 10mV to 200V; input currents are 1mA to 100mA ac or dc. Isolation between input, output and power supply is provided and the two output relays are in spdt form and rated at 120Vac or 24Vdc. Weidmuller (Klippon Products) Ltd. Tel., 01795 580999; fax, 01732 844444.

### Transducers and sensors

**Slotted sensors.** Omron has added to its range of optoelectronic switches a number with increased slot widths of 8mm. *EE-SX1070/3070/4070* are configured as phototransistor, photo-ic (light off) and photo-ic (light on) respectively, all with resolution to 0.5mm. The photo-ic versions have an amplifier and Schmitt to give high output for direct drive of other circuits; frequency response allows 3000 operations per second. Omron Electronics Ltd. Tel., 0181-450 4646; fax, 0181-450 8087.

**Displacement transducers.** Monitran's new linear differential displacement transducers are for use in applications where they must withstand pressures up to 6000lb/in<sup>2</sup>, or 400bar. *MTNP* units can be used inside hydraulic and pneumatic cylinders to act as feedback devices for actuator control. They are in stainless steel and come in measuring ranges of ±25mm to ±500mm, giving

dc or current-loop output. Monitran Ltd. Tel., 01494 816569; fax, 01494 812256.

**Magnetic field sensor.** Designed to detect and measure a changing magnetic field, the *Zetex ZMY20M* now tolerates disturbance fields up to 30kA/m. It takes the form of thin-film magnetoresistive permalloy in a Wheatstone bridge arrangement to give an output proportional to the field. An internal magnet in the E-line or SOT223S package counteracts unwanted external disturbances to allow measurement down to 0.1kA/m. Bridge resistance is 1.7kΩ and output is 12-22mV/V at 0-1MHz. Zetex plc. Tel., 0161-627 5105; fax, 0161-627 5467.

**Rotary sensor.** Control Transducers's *WPM* absolute rotary position sensor is completely self-contained and uses the *MystR* conductive plastic for long life with excellent linearity (±0.075%) and resolution. It is contained in a 22-51mm anodised aluminium housing for servo mounting. Control Transducers. Tel., 01234 217704; fax, 01234 217083.


## COMPUTER

### Data communications

**V.34 modem.** Rockwell's *RVC288ATFW/SP* modem chip is a complete V.34 design offering 115.2kb/s data and Group 3 fax, voice and speakerphone facilities; it needs no external controller. Adpcm coding and decoding allows digital storage using 2-bit or 4-bit compression and 7200bit/s decompression, while the voice mode supports business audio and Rockwell's integrated communications system programme for digital phone answering, voice annotation and audio file play and record. Telecom Design Communications Ltd. Tel., 01256 332800; fax, 01256 332810

**Little transceiver.** *STD-300* from Circuit Design is a 50 by 28mm narrow-band radio data transceiver intended to add telemetry to portable data terminals such as data loggers and card readers. Its high selectivity programmable pll-synthesised transmitter stage and a sensitive double superhet synthesised receiver allow a reliable range of 1km at a data rate of 2400b/s. It operates in the 434MHz band and is compatible with ETS-300-220; spurious emissions are at less than -60dBm and under 200nW to adjacent channels. Low Power Radio Solutions Ltd. Tel., 01993 709418; fax, 01993 708575.

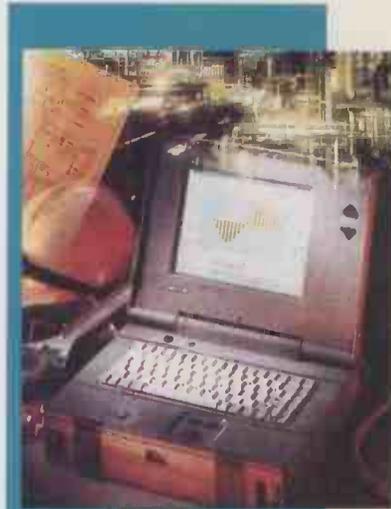**Modem modules.** *SocketModems* are a pin-compatible range of modem modules, including a low-power 2400bit/s data-only type up to a V.32bis type providing data, fax and voice. Also in the range is the *TDE-D300* parallel interface, an ISA-bus



**Industrial notebook.** A joint GE/Lockheed/Martin Marietta/Mitac project produced the *MNB* series of heavy-duty notebook computers for use in unfriendly surroundings. It has either a 486DX2 66 or a 486DX4 100 processor with 4Mb dram and a 520Mb, 2.5in removable hard disk. Lcd displays of various types can be provided, with provision to connect an external VGA monitor. There are two PCMCIA slots for Types I or II cards and a standard ISA or two PC104 cards can be used internally. The whole thing is in a cast aluminium chassis and enclosure. Kerry Technology Ltd. Tel., 01825 766776; fax, 01825 768020.


card to go in a pc's 8-bit card slot, hosting any parallel socketModem. A demonstration board has a speaker and a socket for DAAs. Telecom Design Communications Ltd. Tel., 01256 332800; fax, 01256 332810.

### Data logging

**Portable logger.** A new, portable data logger, the *SA32* from Martron, has on-board data-processing functions, takes 33 input channels and measures voltage, current, resistance and temperature. Sampling speed is 50 measurements per second on each channel to a resolution of 1µV and with an accuracy of 0.01%. The instrument will create up to 68 mathematical data channels from the original data. Software runs with Windows, dos, Modbus and J-bus. Martron Instruments Ltd. Tel., 01494 459200; fax, 01494 535002.

**Mass storage systems**  
**Solid-state file cards.** IBM's cards provide users of portable computers with an alternative to magnetic disks for PCMCIA memory modules. Two forms of card, PCMCIA Type I and II both have a standard PCMCIA-ATA interface and capacity up to 40Mbyte. They use a single 5V supply at less power than disk drives, an advantage over the drives being that there are no delays. Disadvantages of first-generation flash memory cards are avoided by the use of a controller chip and dram buffers to avoid the need to erase memory before storing data. DIP Systems. Tel., 01483 202070; fax, 01483 202023. ■
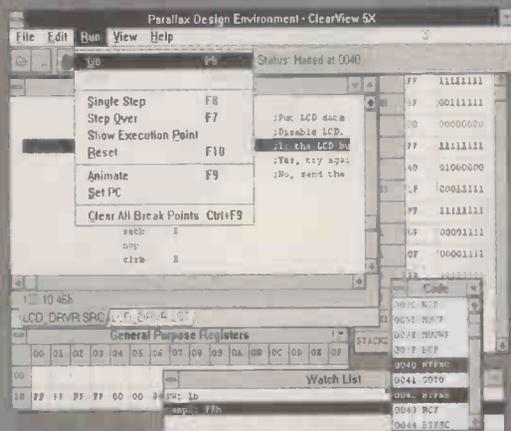
## PIC our TOOLS for Value and Performance



- Programmers from only £89.00
- Simulators
- Real-time Emulators with Bond-out Chipsets for:  
PIC 16C5X/61/620/621/622/64/65/71/73/74/84
- Large Range of Adapters and Proto-Boards
- Parallax PASM, MPASM or Byte Craft C Code

### MILFORD INSTRUMENTS

UK-Ireland Distributors for Parallax Development Tools and the BASIC Stamp

Tel: 01977 683665 Fax: 01977 681465

CIRCLE NO. 135 ON REPLY CARD

# KESTREL ELECTRONIC COMPONENTS LTD

- ☆ All items guaranteed to manufacturers' spec.
- ☆ Many other items available.

'Exclusive of V.A.T. and post and package'

	1+	100+		1+	100+
27C64-15	2.60	1.57	628128LP-85	8.30	7.10
27C128-15	2.40	2.20	62256LP10	3.60	2.60
27C256-15	2.20	1.65	6264LP-10	2.60	1.75
27C512-15	2.20	1.85	MM58274CN	4.90	3.75
27C010-15	3.95	2.75	ULN2003A	0.43	0.28
27C020-15	6.00	3.80	7805	0.32	0.25
27C040-15	8.60	6.45	MAX232	1.35	0.88
80C31-12	2.10	1.95	7406	0.35	0.23
80C552-5-16	10.50	7.50	7407	0.35	0.23
Z80A CPU	1.80	1.00	74HC244	0.35	0.21
LM317T	0.50	0.40	74HC245	0.35	0.21
75176BP	1.35	0.75	74HC373	0.35	0.21
68w PLCC skt	0.90	0.701	74HC374	0.32	0.21

Phone for full price list

All memory prices are fluctuating daily, please phone to confirm prices

178 Brighton Road, Purley,  
Surrey, England CR8 4HA

Tel: 0181-668 7522. Fax: 0181-668 4190


CIRCLE NO. 136 ON REPLY CARD


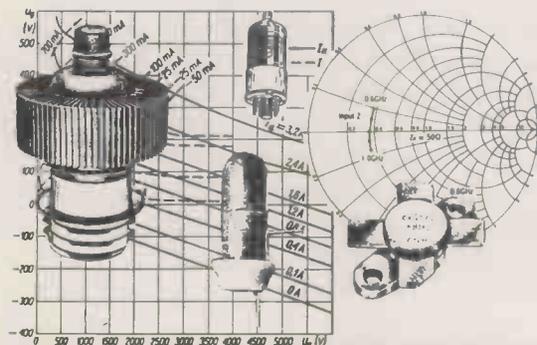
## CHELMER VALVE COMPANY

If you need Valves/Tubes or RF Power  
Transistors e.t.c. ... then try us!

We have vast stocks, widespread sources and  
33 years specialist experience in meeting our  
customers requirements.



Tuned to the needs of the Professional User

Chelmer Valve Company, 130 New London Road,  
Chelmsford, Essex CM2 0RG, England

☎ 44-01245-355296/265865

Fax: 44-01245-490064

CIRCLE NO. 137 ON REPLY CARD

## AGENTS WANTED WORLDWIDE

FOR AN EXPANDING  
COMPANY WHO  
MANUFACTURES FAN  
SPEED CONTROLS. WE  
MANUFACTURE 3A, 5A,  
10A ELECTRONIC SPEED  
CONTROLS. Also 1A, 2A,  
2.5A, 4A, 5A, 7A, 10A  
STEPPED 1 & 3 PHASE  
CONTROLS. WE ALSO  
MANUFACTURE  
THERMOSTATS,  
HUMIDISTATS &  
ENVIRONMENTAL  
CONTROLLERS.



FOR FURTHER INFORMATION CONTACT

## AIRTEX CONTROLS

8 DUNBOYNE IND PK

DUNBOYNE

CO MEATH

REP OF IRELAND

PHONE: +353 1 8251085 FAX: +353 1 8252008

CIRCLE NO. 138 ON REPLY CARD

# STOP! Just Take Two Steps to do Your Measurement



## TiePieSCOPE



**HS508 Complete set  
for £ 597.00**

You can simply plug the new TiePieSCOPE - HS508 into the parallel port of your portable or desktop PC. With the advanced software, you can use this two channel, 8 bits, 50 MHz measuring instrument as a fast digital storage oscilloscope, including a lot more features than a single oscilloscope! Moreover, the TiePieSCOPE - HS508 contains a multiple display voltmeter (up to 5 MHz true RMS), a spectrum analyzer with an harmonic distortion meter and a transient recorder for recording a variety of signals. The TiePieSCOPE - HS508 is supplied complete with user manual, software, and two probes.

Call now for a free demo diskette and our catalog!!

### TiePie engineering (UK)


✉ 28 Stephenson Rd, Industrial Est., ST. IVES, CAMBS PE17 4WJ  
Tel.: (01480) 460028 - Fax: (01480) 460340

### TiePie engineering, The Netherlands

✉ P.O. Box 115, 8900 AC LEEUWARDEN  
🏠 Batterserreed 2, 9023 AR JORWERD  
Tel.: (31) 515 415 416 - Fax: (31) 515 418 819

# Chopping on a bridge

**Darren Heywood's chopping approach to measuring bridge design results in an unusual combination of low cost and high stability.**

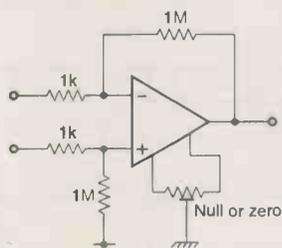

**Fig. 1. Designing a transducer amplifier with a gain of 1000 should be easy, given an op-amp with a high input impedance and a gain of a few million.**

I was challenged by a friend to design a high-sensitivity amplifier circuit for a transducer. My choice was to connect the transducer in a Wheatstone bridge configuration.

Output span from the transducer was just 0 to 5mV. This meant that the signal would have to be amplified by at least 1000 in order to bring the signal to workable levels, ie 0-5V.

I started the design by simply setting the resistor ratios  $R_f/R_i$  on a 741 op-amp to yield the required gain, Fig. 1. But the configuration was unstable and would not null. Furthermore, I noticed that by simply blowing a little air over the circuit, the output would suddenly drift towards either supply rail and saturate.

Consulting the data sheets revealed that the drift gradient for a 741 was in the region of approximately  $20\mu\text{V}/^\circ\text{C}$ . A simple calculation exposes the problem. Assume a change of say  $5^\circ\text{C}$  referred to the op-amp input. This means a  $\Delta V_{\text{offset}}$  of  $100\mu\text{V}$  ( $5 \times 20$ ) or 0.1mV. Multiply this figure by 1000 and you get 0.1V at the output due solely to temperature change.

Another contributory factor to drift in the circuit is the type of resistors used. Carbon types for instance have a drift of approximately 300ppm while metal film types exhibit approximately 50ppm. Moreover, when soldering the resistors onto a circuit board, a thermocouple is created due to Seebeck effect and noise levels inherent in the circuit change with temperature.


The obvious solution to the temperature drift problem would seem to be to obtain an op-amp with a very low drift figure. The OP27 has a drift rate of just  $1$  to  $2\mu\text{V}/^\circ\text{C}$ , depending on the part-number suffix.

Inserting the new op-amp into Fig. 1 reduced the drift problem, but the output still varied to unacceptable levels. I began to realise that a totally different circuit concept was required – namely a chopper amplifier\*.


Designing a circuit exhibiting near-zero drift is one challenge, but is it possible to incorporate chopper technology into a 4-to-20mA system? Signal transmission relying on current change is superior to an equivalent based on voltage because current operation minimises line loss. Current loops are widely used in both instrumentation and digital transmission systems, Fig. 2.

## Implementing the chopping bridge

You should first decide on an overall feedback system. I chose voltage-to-current feedback, Fig. 3. Assuming  $V_{\text{is}}$  drops slightly due to the resistance-temperature transducer increasing, the op-amp responds by increasing its output.

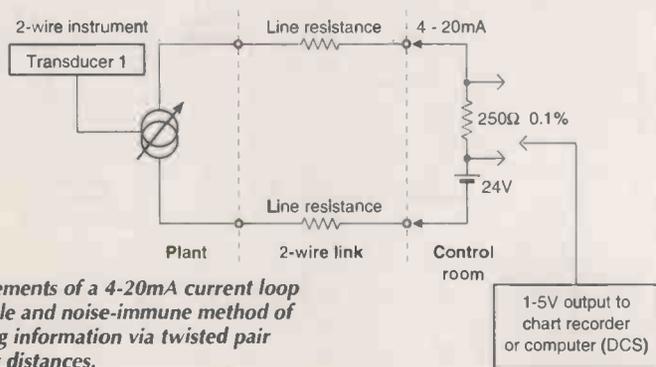

**Fig. 2. Elements of a 4-20mA current loop – a reliable and noise-immune method of conveying information via twisted pair over long distances.**

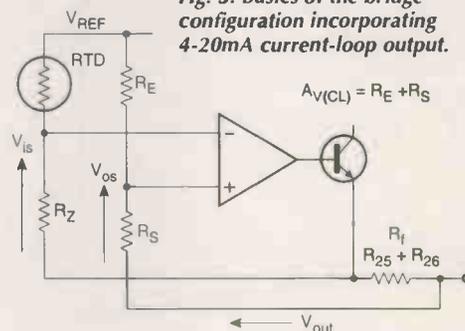

**Fig. 3. Basics of the bridge configuration incorporating 4-20mA current-loop output.**

\*At £1.33 in 100 offs, the MAX427 op-amp has a drift of  $0.8\mu\text{V}/^\circ\text{C}$ . In similar quantities, the ICL7650 chopper amplifier is £2.30 while the MAX420 chopper is £3 – Ed.

In turn, voltage across  $R_f$  starts to increase and  $V_{os}$  decreases until  $V_{is}$  equals  $V_{os}$  and equilibrium is reached.

For the op-amp, it is desirable to have high gain and lowest possible drift. This ensures temperature stability and improves resolution. Selecting a high gain 'off-the-shelf' op-amp achieves good resolution, but not temperature stability.

This dilemma forces the use of chopper amplifiers, which normally means added complexity, extra components and increased costs.

**Supplying the bridge**

To provide a reference, a temperature compensated voltage source is needed with low output impedance and low current consumption. The LM723 voltage stabiliser,  $IC_1$  of Fig.

4, is very cheap, widely available, and contains a 7.2V temperature compensated voltage reference capable of sourcing up to 20mA. In addition, it has a high gain op-amp, a pass transistor capable of sinking 150mA, a current limit transistor and a zener diode – all for approximately 40p.

A 24V supply is needed while the 723 voltage reference is about 7.2V. If the 7.2V reference is used as the op-amp pseudo ground, then  $IC_2$  can swing approximately  $\pm 7V$ . This leaves approximately 10V for external line and measurement resistance. Hence approximately 15V divided into 20mA equals 750 $\Omega$  and 1200 $\Omega$  minus 750 $\Omega$  leaves 450 $\Omega$  for external resistances.

The feedback system around  $IC_2$  is a hybrid type. You may think that the gain is set with

this feedback system,

$$A_v(CL) = \frac{R_6}{R_3} \times \left( 1 + \frac{R_7}{R_8} \right)$$


But at the gain demanded from  $IC_2$  the above equation fails. This problem occurs because,

$$A_v(CL) = \frac{A_v(OL)}{(1 + B A_v(OL))}$$

ie  $A_v(CL)$  is approximately  $A_v(OL)$ .

If you check out the gain/frequency response curves as given by the manufacturers, they reveal that in open loop mode, the LM308 outputs 110dB gain at approximately 10Hz and rolls off at the first order rate of

**Fig. 4. Full circuit of the chopping bridge amplifier with 4-20mA current-loop output.**

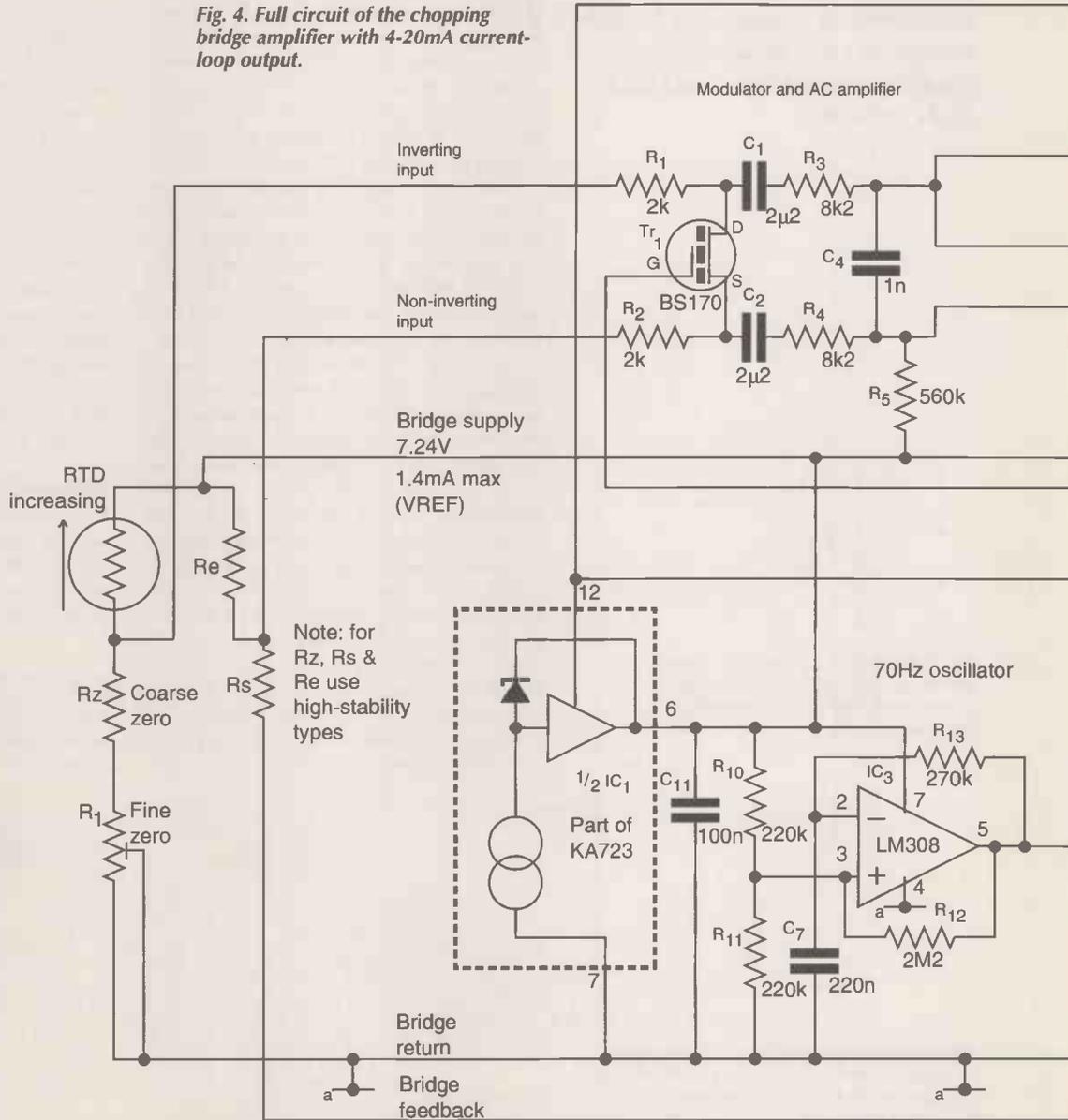

18dB/decade thereafter. Why control gain with just resistors? You can control it with frequency as well. The above then demonstrates that the chopping frequency is most important.

**Oscillator design choice**

This application needs an oscillator with a low current consumption and that remains at a stable frequency even if the 24V supply is varied from 24V down to say 15V. It must also swing from the supply to ground to ensure IC<sub>2</sub>'s common mode input range is maximised. It must also have a 180° complement output.

The simplest choice is to use another 308 since it consumes only 300µA. Notice that IC<sub>3</sub> is powered by V<sub>REF</sub>. This clamps IC<sub>3</sub> to maintain fixed stable frequency. Output of IC<sub>3</sub> is

then fed into Tr<sub>3</sub> and Tr<sub>2</sub>, the latter being driven by Tr<sub>3</sub>. Both drains are connected to the positive supply rail.

At 24V, the two zener diodes limit the common mode range to about 16V to reduce stress on the mosfet gates. Note that bipolar transistors connected in astable mode with 390kΩ load resistors as Tr<sub>3</sub> and Tr<sub>2</sub>, take too long to switch off.

One improvement that may possibly be made here is to connect Tr<sub>3</sub> and Tr<sub>2</sub> in bistable mode, using IC<sub>3</sub> as the driver. In this way, Tr<sub>3</sub> and Tr<sub>2</sub> outputs would have ideal overlapping switching times.

**Modulation and demodulation**


First, the modulation system used is synchronous. This simplifies the circuitry and

maintains excellent restoration of the amplified signal.

Assume Tr<sub>1</sub> and Tr<sub>4</sub> are both off, Tr<sub>5</sub> is on, and there is slightly less potential at the inverting input than the non-inverting input if IC<sub>2</sub>. This means that C<sub>2</sub> will have a slightly greater charge stored than C<sub>1</sub>.

Now, Tr<sub>1</sub> and Tr<sub>4</sub> are both on, Tr<sub>5</sub> is off, C<sub>1</sub> and C<sub>2</sub> are both rapidly shunted together and because C<sub>1</sub> has slightly less charge than C<sub>2</sub>. A small difference charge is forced into IC<sub>2</sub> inverting terminal. This causes IC<sub>2</sub>'s output to swing negative and equalises at some point via the feedback resistors. At the same time Tr<sub>4</sub> shunts C<sub>3</sub> from V<sub>REF</sub> point of view.

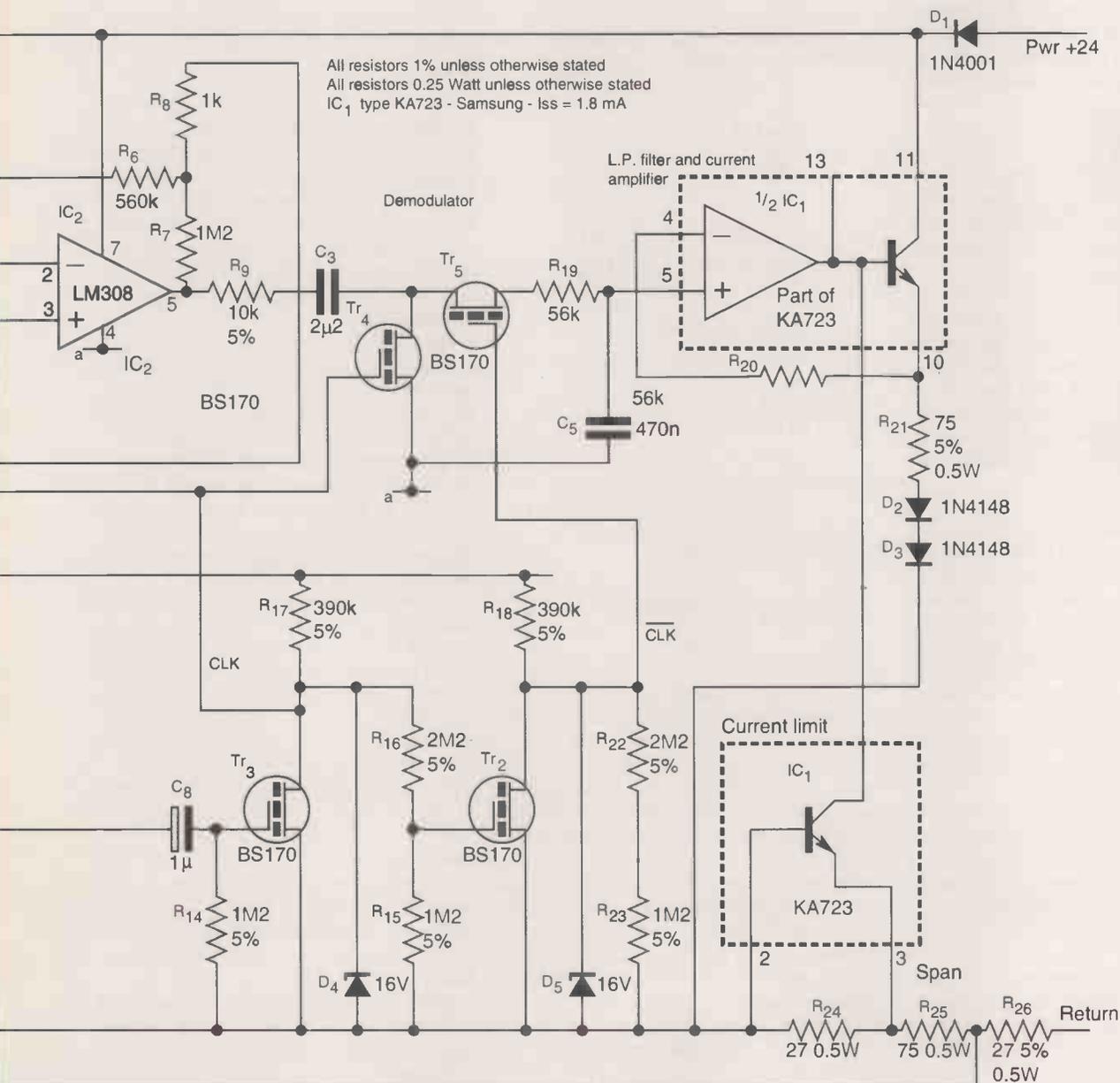At this point, Tr<sub>1</sub> and Tr<sub>4</sub> are both off, Tr<sub>5</sub> is on and C<sub>1</sub> now has a negative difference



charge and as such, current is pulled from  $IC_2$  inverting terminal. This causes  $IC_2$ 's output to swing positive until equilibrium is again reached via feedback.

Both positive and negative output pulses are equal in magnitude but opposite in polarity. During the positive pulse,  $T_{r5}$  is about  $5\Omega$  and thus the positive pulses from  $IC_2$  are sampled and stored in  $C_5$ .

Due to the previous negative cycle,  $C_3$  was charged from ground and thus positive only amplified pulses which are referenced to ground are passed onto or into  $R_{19}/C_5$ . By charging  $C_3$  from ground, level shift from  $V_{REF}$  to ground is accomplished. Remember that  $IC_2$  output swings around its pseudo ground  $V_{REF}$ .

Notice that  $C_1$ ,  $C_2$  and  $C_3$  isolate  $IC_2$ 's quiescent point so  $IC_2$  is allowed to drift. Also, increasing the dc signal on the inverting terminal of  $IC_2$  to above that of the non-inverting terminal causes a phase change at the output of  $IC_2$ . This produces dsb suppressed carrier modulation!

**Current amplifier**

To produce the current amplifier,  $IC_1$  is simply connected as a unity gain voltage buffer. Current gain, however, is determined by the current flowing through  $R_{21}$ . The smaller  $R_{21}$ , the higher the current gain.

Note the internal pass transistor within the 723 is providing the current gain and not the amp. The amp simply controls the current very accurately. Diodes  $D_2$  and  $D_3$  lift the turn on level to 1.2V. This is done because the KA723 op-amp does not saturate at exactly ground. All the above means 4mA, or zero, begins at around 1.2V and ends at around 2.4V, i.e. 20mA.

**The bridge system**

Referring to Fig. 3, assume for a range of  $0^\circ$ - $100^\circ$ C, the rtd's resistance changes from  $100\Omega$  to  $139.02\Omega$ . Also assume that  $100\Omega$  represents 4mA and  $139.02\Omega$  represents 20mA.

In my bridge configuration, an increase in rtd resistance causes  $V_{is}$  to fall. Due to feedback, the amplifier increases current output across  $R_{27}$  and  $R_{23}$  until the selected feedback resistances  $R_S/R_E$  equalise the change. Thus  $V_{is}$  is always approximately equal  $V_{os}$  and is true for any feedback system.

The higher the open-loop gain the less the error between  $V_{is}$  and  $V_{os}$ . Again assume that the rtd is  $100\Omega$ ,  $V_{is}$  equals  $V_{os}$  and the system draws 4mA. Now, the rtd begins to increase in value so voltage  $V_{is}$  starts to fall. Voltage  $V_{os}$  follows  $V_{is}$  because the system is closed loop, Fig. 5.

If the rtd carries on increasing then at some point the system will reach 20mA. In theory, any zero/span ratio can be achieved. Here are the equations governing the system calibration under static conditions are,

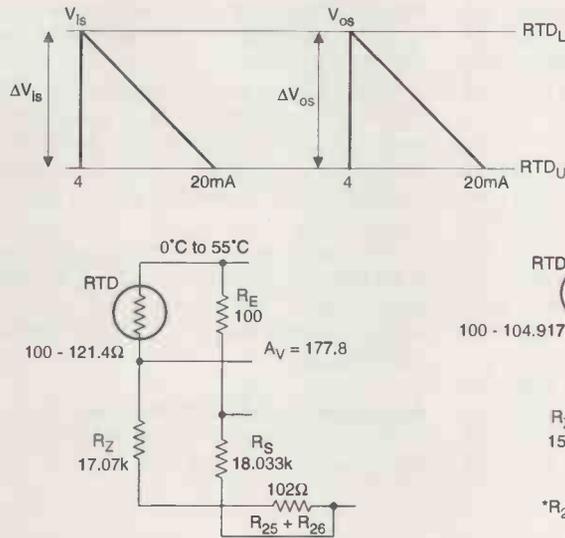


Fig. 5. Ideally, the voltage output slope of the 4-20mA converter should follow the voltage input slope in the configuration of Fig. 3.

Fig. 6. Examples of bridge connections for two resistance-temperature transducers with different characteristics.

$$\Delta V_{os} = \frac{1.632 R_E}{R_S + R_E}$$

$$\Delta V_{is} = \frac{V_{REF} R_Z (RTD_U - RTD_L)}{(RTD_L + R_Z)(RTD_U + R_Z)}$$

$$V_{os} = \frac{R_S V_{REF} - 0.408 R_E}{R_S + R_E}$$

$$V_{is} = \frac{V_{REF} R_Z}{RTD_L + R_Z}$$

and the limitation equations are,

$$\Delta V_O = \frac{1.632(V_{REF} - V_{OS})}{V_{REF} + 0.408}$$

$$\frac{R_S}{R_E} = \frac{1.632 V_{OS} + 0.408 \Delta V_O}{\Delta V_O V_{REF}}$$

Note that system span is controlled by  $R_{25}$  plus  $R_{26}$ ,  $R_S$  and  $R_E$  are span alignment resistors only and zero is controlled with  $R_Z$ . For any given calibration,  $\Delta V_{os}$  must equal  $\Delta V_{is}$  and  $V_{ostart}$  must equal  $V_{istart}$ . Also,  $\Delta V_{is}$  must not exceed approximately 9mV. This is due to the maximum current that can be drawn by the bridge.

For any given zero/span range,  $\Delta V_{is}$  should always be as large as possible - why attenuate then amplify? Reducing resistor  $R_{23}$  narrows the span, however the equations supplied have to be amended slightly. I have provided two calibration scenarios. Bridge Fig. 6a) is  $0^\circ$ C=4mA to  $55^\circ$ C=20mA, while the bridge illustrated in Fig. 6b) is  $0^\circ$ C=4mA to  $11^\circ$ C=20mA.

**Dynamic loop performance**

Unfortunately, I did not have the equipment needed to maximise speed via damping. However, you must remember that we are trying to amplify thermocouples and rtds which have an inherently slow response speed of approximately 10 to 15 seconds. So if the system is slightly overdamped, performance is not downgraded.

The system loop's dynamics and bandwidth are set via  $R_{19}$  and  $C_5$ . I chose these values to coincide with a -3dB of 7Hz. This is ten times less than the switching frequency. This is well within the criteria of the sampling theorem.

At very narrow spans  $IC_2$  has to produce higher gains and as such becomes too slow to respond to the induced error caused by KA723 pin 5. Thus no overshoot occurs at narrow span demands. Switching frequency was selected upon the above criteria.

The loop is guaranteed to be conditionally stable. The only unstable condition that can occur is if the input signal approaches 70Hz and is in phase with the switching (chopping) frequency. This is highly unlikely to happen.

Capacitor  $C_4$  was inserted between the inputs of  $IC_2$  to limit overshoot, slowing  $IC_2$  down slightly during wide span conditions.

Diode  $D_1$  protects against reverse polarity supply connection.


**Summary**

Components for the bridge amplifier are well under £5 yet open-loop gain is in excess of 48000 and temperature stability is excellent. Noise is also low since the circuit is narrow-band.

I have shown here what can be achieved with an alternative bridge topology and that high performance need not mean expensive components. ■

# Reference books to buy

## For Audio Engineers

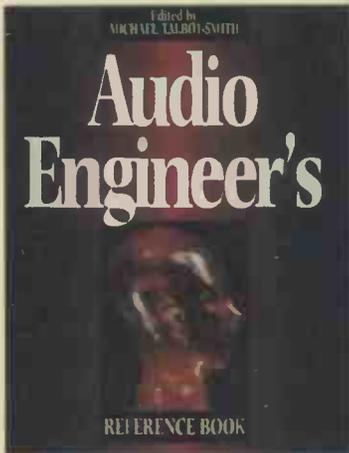

### Subjects include

Recording, microphones and loudspeakers

Digital audio techniques

Basic audio principles

Acoustics and psychoacoustics

Audio and television studios and their facilities

Radio and telephony

- Comprehensive – over 600 pages
- Written by leading authorities from the audio world
- Easy to read, compiled for maximum accessibility
- Concise and authoritative
- Covers topics from noise measurement to studio installation

Invaluable reference work for anyone involved with audio – from broadcast consultant to serious enthusiast. *Audio Engineer's Reference Book* is written by an international team of experts and edited by Michael Talbot-Smith – previously a trainer of audio engineers at BBC Wood Norton and now a freelance audio consultant and technical writer.

Please supply me \_\_\_\_\_ copies of the **Audio Engineer's Reference Book**,

(ISBN 0 7506 0386 0)

**Fully-inclusive price** – UK £77.50, Europe £83, Worldwide £93. Please add vat at local rate where applicable.

Please supply me \_\_\_\_\_ copies of the **TV & Video Engineer's Reference Book**,

(ISBN 0 7506 1953 8)

**Fully-inclusive price** – UK £42.50, Europe £48.00, Worldwide £58.00, Please add vat at local rate where applicable.

Remittance enclosed £ \_\_\_\_\_

Cheques should be made payable to Reed Business Publishing Group Ltd

**Please return to: Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS**

Please debit my credit card as follows:

Access/Master    Barclay/Visa    Amex    Diners

Credit Card No. \_\_\_\_\_

Exp date \_\_\_\_\_

NAME (Please print) \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

POST CODE \_\_\_\_\_

DATE \_\_\_\_\_ TEL \_\_\_\_\_

SIGNATURE \_\_\_\_\_

VAT RATES


6% Belgium, 25% Denmark, 5.5% France, 7% Germany, 4% Greece, 4% Italy, 3% Luxembourg, 6% Netherlands, 5% Portugal, 3% Spain. FOR COMPANIES REGISTERED FOR VAT, PLEASE SUPPLY YOUR REGISTRATION NUMBER BELOW (customers outside the EEC should leave this part blank)

VAT NO. \_\_\_\_\_

If in the UK please allow 28 days for delivery. All prices are correct at time of going to press but may be subject to change.

Please delete as appropriate. I do/do not wish to receive further details about books, journals and information services.

## For TV & Video Engineers

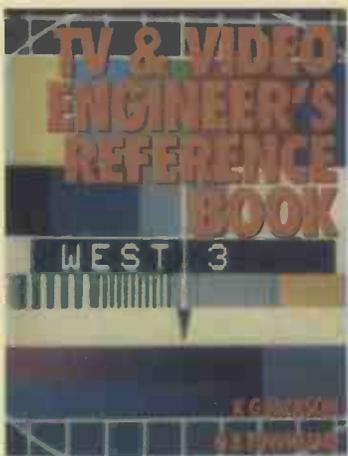

### Subjects include

Fundamentals of colour TV

TV studios

High definition TV

Satellite broadcasting

Distribution of broadband signals

TV receiver servicing

Video and audio recording and playback


Teletext

- Over sixty chapters on the latest techniques in video and television
- Up to date reference on EMC requirements, DBS and HDTV
- Easy-to-use reference, eminently suitable for students
- Topics range from materials and construction to medical and defence applications of television.

The *TV & Video Engineer's Reference Book* will be of immense value to anyone involved with modern tv & video techniques – in particular broadcast engineers. The new format makes it an excellent reference for students. Edited by KG Jackson and GB Townsend from contributions written by acknowledged international experts.

Credit card orders accepted by 'phone. Call 0181 652 3614

# INTERFACING WITH C

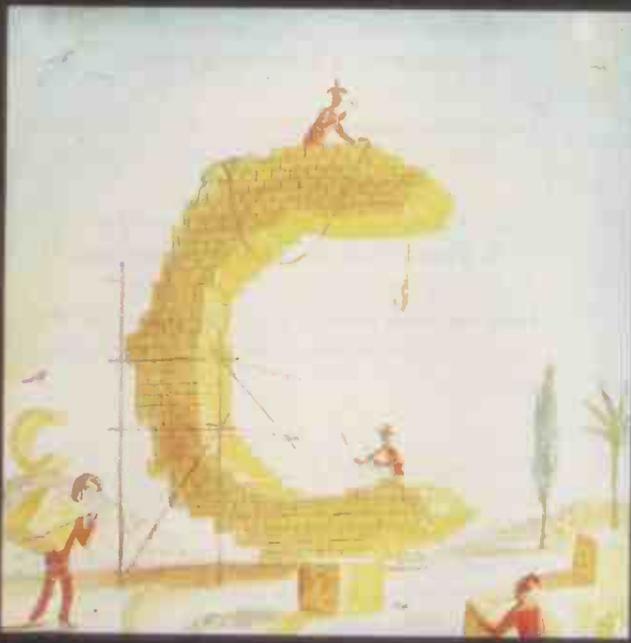

HOWARD HUTCHINGS



**A disk containing all the example listings used in this book is available, Please specify size required**

If you have followed our series on the use of the C programming language, then you will recognise its value to the practising engineer.

The book is a storehouse of information that will be of lasting value to anyone involved in the design of filters, A-to-D conversion, convolution, fourier and many other applications, with not a soldering iron in sight.

To complement the published series, Howard Hutchings has written additional chapters on D-to-A and A-to-D conversion, waveform synthesis and audio special effects, including echo and reverberation. An appendix provides a 'getting started' introduction to the running of the many programs scattered throughout the book.

This is a practical guide to real-time programming. The programs having been tested and proved. It is a distillation of the teaching of computer-assisted engineering at Humberside Polytechnic, at which Dr Hutchings is a senior lecturer.

Please supply \_\_\_\_\_ copies of  
**INTERFACING WITH C** Price **£14.95**  
Please supply \_\_\_\_\_ copies of  
**Disk containing all the example listings** £15.00

Remittance enclosed £ \_\_\_\_\_

**Interfacing with C can be obtained from Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS**

Cheques should be made payable to  
Reed Business Publishing Group Ltd

Please debit my credit card as follows:  
Access/Master    Barclay/Visa    Amex    Diners

Credit Card No. \_\_\_\_\_

Exp date \_\_\_\_\_

NAME (Please print) \_\_\_\_\_

ADDRESS \_\_\_\_\_

POST CODE \_\_\_\_\_

DATE \_\_\_\_\_ TELE \_\_\_\_\_

SIGNATURE \_\_\_\_\_

VAT NO. \_\_\_\_\_

If in the UK please allow 28 days for delivery. All prices are correct at time of going to press but may be subject to change.

**Credit card orders accepted by phone.  
Call 0181 652 3614.**

## SYNTHESISED SIGNAL SOURCE

an innovative design from an established 'Off-Air' Company

- Custom designed chip set
- Sinewave output 0dBm into 50Ω
- Can be run independently or genlocked to external source
- dc to 16MHz in 0.1Hz steps, with option 0.0001 Hz steps
- Freestanding rack mounting, or OEM options available
- Increased resolution and increased stability options available

Models available October, contact us for prices

NEW from Halcyon

CIRCLE NO. 139

## 'OFF-AIR' FREQUENCY STANDARD

CIRCLE NO. 140



- ★ Provides 10MHz, 5MHz & 1MHz
- ★ Use it for calibrating equipment that relies on quartz crystals, TCXOs, VXCOs, oven crystals
- ★ Phase locks to DROTWICH (rubidium controlled and traceable to NPL)
- ★ For ADDED VALUE also phase locks to ALLOUIS (cesium controlled and traceable to OP — French eq to NPL)
- ★ British designed and British manufactured
- ★ Options available include enhanced receiver, sine wave outputs and 13MHz output for GSM. Prices on application.

Output frequencies — 10MHz, 5MHz, 1MHz  
Short term stability — better than  $1 \times 10^{-8}$  (1 sec)  
Typical —  $4 \times 10^{-9}$  (1 sec)  
Long term — tends to  $2 \times 10^{-12}$  (1000 sec)  
Call for 'Off-Air' Standard list

## TEST EQUIPMENT

CIRCLE NO. 141

We are well known for our quality, new and used Test Equipment. Our list is extensive, ranging through most disciplines. Call for details and a complete list



HALCYON ELECTRONICS



423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR  
SHOP HOURS 9-5.30 MON-SAT. TEL 0181-542 6383. FAX 0181-542 0340

## ADVANCED ACTIVE AERIAL



The aerial consists of an outdoor head unit with a control and power unit and offers exceptional intermodulation performance: SOIP +90dBm, TOIP +55dBm. For the first time this permits full use of an active system around the 1f and mf broadcast bands where products found are only those radiated from transmitter sites.

- General purpose professional reception 4kHz-30MHz.
- -10dB gain, field strength in volts/metre to 50 Ohms.
- Preselector and attenuators allow full dynamic range to be realised on practical receivers and spectrum analysers.
- Noise — 150dBm in 1Hz. Clipping 16 volts/metre. Also 50 volts/metre version.

★ Broadcast Monitor Receiver 150kHz-30MHz. ★ Stabilizer and Frequency Shifters for Howl Reduction ★ Stereo Variable Emphasis Limiter 3 ★ 10-Outlet Distribution Amplifier 4 ★ PPM10 In-vision PPM and chart recorder ★ Twin Twin PPM Rack and Box Units. ★ PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and meter movements ★ Broadcast Stereo Coders ★ Stereo Disc Amplifiers ★ Peak Deviation Meter.

SURREY ELECTRONICS LTD

The Forge, Lucks Green, Cranleigh, GU6 7BG.  
Telephone: 01483 275997. Fax: 276477.

## JOHN MORRISON SOFTWARE and OEM HARDWARE MODULES

### PIC ICE II

#### In Circuit Emulator for PIC16C54-55-56-57-71 and 84

Replaces all 18 or 28 pin PIC's. All ports Bi-directional DSC2 output, RTCC input, on board A/D converter for PIC18C71. Supplied with PICDEV software suite, user manual, connecting leads and headers asrn, user sample files and hardware circuit projects.

£159.95



### NEW Enhanced PIC PROGRAMMER

PIC 16C54, 16C55, 16C56, 16C57, 16C58A, 16C61, 16C64, 16C65, 16C71, 16C74, 16C84, 16C620, 16C621, 16C622 and Memory Chips 24LC01, 24LC02, 24LC16, 24LC32, 24LC65

Centronics port interface, powerful editing software allows the user to Read, Write and Copy PIC devices including data memory in PIC16C84. Supplied with Editor Assembler software suite. Sample files and notes.

£99.95



### MEGAPROM EPROM PROGRAMMER

#### EPROMS, E<sup>2</sup> PROMS and FLASH memories from 2Kb to 8Mb

INC. MICROCHIP 24LC01-65 Memory

Operates via host IBM PC and centronics port, uses standard printer cable, on board production quality ZIF socket.

£99.95




### EPROM EMULATOR

#### For ROM from 1Kb to 32Kb

Operates via host IBM PC and centronics port, uses standard printer cable. Very fast download to target board EPROM socket, operates with or without our development software suite.

£69.95

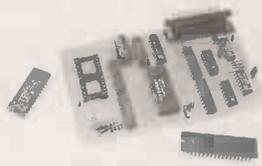

### NEW EEPROM PROGRAMMER

Programs all EEPROMS. Driver software runs on an host IBM PC MSDOS 3.1 or higher, connects to the parallel port, also detects 12C bars or the Microwave 3/4. This small neat unit has facilities for programming or copying in Intel, Hex Microchip or BIN formats, with user variable programming speeds for all devices.

£49.95

### DEVELOPMENT SOFTWARE

Develop software on your IBM PC for other Microprocessors, Controllers, PIC Chips etc. Each software suite has a fully integrated Text editor, Assembler, Disassembler and Simulator included. Code can be downloaded directly to our emulators. All software supplied with operator instructions and sample code. SMARTCARD DEVELOPMENT PACKAGES MADE TO ORDER

MCS8051/52/552 — MCS8048/49 — PIC16C54/55/56/57  
PIC16C71/84 — HD63/6809 — R6502 **£19.95 ea**

Please add £1.75 for P&P to UK mainland.

All prices subject to VAT at the prevailing rate (17.5%)



CROWNHILL ASSOCIATES LIMITED, PO BOX 845  
WATERBEACH, CAMBRIDGE, CB5 9JS

BBS: 07010 700018

TEL: 07010 700017

FAX: 01223 441645



CIRCLE NO. 142 ON REPLY CARD

**SURVEILLANCE TELESCOPE** Superb Russian zoom telescope adjustable from 15x to 60x complete with metal tripod (impossible to use without this on the higher settings) 66mm lens, leather carrying case £149 ref BAR69

**RADIATION DETECTOR SYSTEM** Designed to be wall mounted and connected into a PC, ideal for remote monitoring, whole building coverage etc. Complete with detector, cable and software. £19.95 ref BAR75.

**WIRELESS VIDEO BUG KIT** Transmits video and audio signals from a miniature CCTV camera (included) to any standard television! All the components including a PP3 battery will fit into a cigarette packet with the lens requiring a hole about 3mm diameter. Supplied with telescopic aerial but a piece of wire about 4' long will still give a range of up to 100 metres. A single PP3 will probably give less than 1 hours use. £99 REF EP79. (probably not licensable!)

**CCTV CAMERA MODULES** 46X70X29mm, 30 grams, 12v 100mA, auto electronic shutter, 3.6mm F2 lens, CCIIR, 512x492 pixels, video output is 1v p-p (75 ohm). Works directly into a scart or video input on a tv or video. IR sensitive. £79.95 ref EF137.

**IR LAMP KIT** Suitable for the above camera enables the camera to be used in total darkness! £5.99 ref EF138.

**REMOTE CONTROL/DATA TD1400 MODEM/VIEWDATA** Complete system comprising 1200/75 modem, auto dialler, infra red remote keyboard, (could be adapted for PC use) psu, UHF and RGB output, phone lead, RS232 output, composite output. Absolute bargain for parts alone! £9.95 ref BAR33.

## 9 WATT CHIEFTAN TANK LASERS

Double beam units designed to fit in the gun barrel of a tank, each unit has two semi conductor lasers and motor drive units for alignment. 7 mile range, full circuit diagrams, new price £50,000? us? £349. Each unit has two gallium Arsenide Injection lasers, 1 x 9 watt, 1 x 3 watt, 900nm wavelength, 28vdc, 600hz pulse frequency. The units also contain an electronic receiver to detect reflected signals from targets, five or more units £299 ea. £349 for one. Ref LOT4.

**TWO WAY MIRROR KIT** Includes special adhesive film to make two way mirror(s) up to 60"x20". (glass not included) Includes full instructions. £12 ref TW1.

## NEW HIGH POWER RF TRANSMITTERS

**AMPLIFIERS** Assembled PCB transmitters, 4 types available, 12.6vdc 90 watt 1.5-30mhz 75 ohm In/out FM/AM £75 ref RF1  
12.6vdc 40 watt 50-200mhz 50 ohm In/out FM/AM £65 ref RF2  
28vdc 125 watt 1.5-30mhz 75 ohm In/out FM/AM £85 ref RF3  
28vdc 100 watt 50-200mhz 50 ohm In/out FM/AM £75 ref RF4  
A heat sink will be required, ring for price and availability. If you intend using these as audio transmitters you will need a also need a preamp. Complex module available at £40 ref RF5.

**COMPUTER/WORKSHOP/HIFI RCB UNITS** Complete protection from faulty equipment for everybody! Inline unit fits in standard IEC lead (extends it by 750mm), fitted in less than 10 seconds, reset/test button, 10A rating. £9 each Ref MM5.

## RADIO CONTROLLED CARS FROM £6 EACH!!!!

All returns from famous manufacturer, 3 types available, single channel (left, right, forwards, backwards) £6 ref LOT1. Two channel with more features £12 ref LOT2. Two channel proportional (plug in crystals etc) £35 ref LOT3.

## THOUSANDS AVAILABLE RING/FAX FOR DETAILS!

**MAGNETIC CARD READERS** (Swipes) £9.95 Cased with flyleads, designed to read standard credit cards! they have 3 wires coming out of the head so they may write as well? complete with control electronics PCB. Just £9.95 ref BAR31

**WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA?** We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14 ref EP74

**PANORAMIC CAMERA OFFER** Takes double width photographs using standard 35mm film. Use in horizontal or vertical mode. Complete with strap £7.99 ref BAR1

**COIN OPERATED TIMER KIT** Complete with coin slot mechanism, adjustable time delay, relay output, put a coin on anything you like! TV's, videos, fridges, drinks cupboards, HIFI. Takes 50p's and £1 coins. DC operated, price just £7.99 ref BAR27.

**ZENITH 900 X MAGNIFICATION MICROSCOPE** Zoom, metal construction, built in light, shrimp farm, group viewing screen, lots of accessories. £29 ref ANAYLT.

**AA NICAD PACK** Pack of 4 tagged AA nicads £2.99 ref BAR34

**PLASMA SCREENS** 222x310mm, no data hence £4.99 ref BAR87

**NIGHTSIGHTS** Model TZS4 with Infra red illuminator, views up to 75 metres in full darkness Infrared mode, 150mm range, 45mm lens, 13 deg angle of view, focussing range 1.5m to infinity. 2 AA batteries required, 950g weight. £199 ref BAR61. 1 years warranty

**LIQUID CRYSTAL DISPLAYS** Bargain prices, 16 character 2 line, 99x24mm £2.99 ref SM1623A  
20 character 2 line, 83x19mm £3.99 ref SM2020A  
16 character 4 line, 62x25mm £5.99 ref SMC1640A

**TAL-1 110MM NEWTONIAN REFLECTOR TELESCOPE** Russian. Superb astronomical scope, everything you need for some serious star gazing! up to 169x magnification. Send or fax for further details £249 ref TAL-1

**GOT AN EXPENSIVE BIKE?** You need one of our bottle alarms, they look like a standard water bottle, but open the top, insert a key to activate a motion sensor alarm built inside. Fits all standard bottle carriers, supplied with two keys. SALE PRICE £7.99 REF SA32.

**GOT AN EXPENSIVE ANYTHING?** You need one of our cased vibration alarms, keyswitch operated, fully cased just fit it to

## WOLVERHAMPTON BRANCH NOW OPEN AT WORCESTER ST W'HAMPTON TEL 01902 22039

anything from videos to caravans, provides a years protection from 1 PP3 battery, UK made. SALE PRICE £4.99 REF SA33.

**DAMAGED ANSWER PHONES** These are probably beyond repair so just £4.99 each. BT response 200 machines. REF SA30.

**COMPUTER DISC CLEAROUT** We are left with a lot of software packs that need clearing so we are selling at disc value only! 50 discs for £4, that's just 8p each! (our choice of discs) £4 ref EP66

**IBM PS2 MODEL 160Z CASE AND POWER SUPPLY** Complete with fan etc and 200 watt power supply. £9.95 ref EP67

**DELL PC POWER SUPPLIES** 145 watt, +5,-5,+12,-12, 150x150x85mm complete with switch, flyleads and IEC socket. SALE PRICE £9.99 ref EP65

**1.44 DISC DRIVES** Standard PC 3.5" drives but returns so they will need attention SALE PRICE £4.99 ref EP68

**1.2 DISC DRIVES** Standard 5.25" drives but returns so they will need attention SALE PRICE NOW ONLY £3.50 ref EP69

**PP3 NICADS** Unused but some storage marks. £4.99 ref EP52

**DELL PC POWER SUPPLIES** (Customer returns) Standard PC psu's complete with flyleads, case and fan. +12v, -12v, +5v, -5v SALE PRICE £1.99 EACH worth 4 for the bits alone! ref DL1. TRADE PACK OF 20 £28.95 Ref DL2.

**GAS HOBS AND OVENS** Brand new gas appliances, perfect for small flats etc. Basic 3 burner hob SALE PRICE £24.99 ref EP72. Basic small built in oven SALE PRICE £79 ref EP73

**RED EYE SECURITY PROTECTOR** 1,000 watt outdoor PIR switch SALE PRICE £8.99 ref EP57

**ENERGY BANK KIT** 100 6"x6" 6v 100mA panels, 100 diodes, connection details etc. £69.95 ref EF112.

**PASTEL ACCOUNTS SOFTWARE**, does everything for all sizes of businesses, includes word processor, report writer, windowing, networkable up to 10 stations, multiple cash books etc. 200 page comprehensive manual, 90 days free technical support (0345-326009 try before you buy!) Current retail price is £129. SALE PRICE £9.95 ref SA12. SAVE £120!!!

**COMPLETE PC 200 WATT UPS SYSTEM** Top of the range UPS system providing protection for your computer system and valuable software against mains power fluctuations and cuts. New and boxed, UK made Provides up to 5 mins running time in the event of complete power failure to allow you to run your system down correctly. LAST FEW TO CLEAR AT £49 SAVE £30 ref LOT61

**BIG BROTHER PSU** Cased PSU, 6v 2A output, 2m o/p lead, 1.5m input lead, UK made, 220v. SALE PRICE £4.99 REF EP7



Check out our  
**WEB SITE**

<http://www.pavilion.co.uk/bull-electrical>

**RACAL MODEM BONANZA!** 1 Racal MPS1223 1200/75 modem, telephone lead, mains lead, manual and comms software, the cheapest way onto the net all this for just £13 ref DEC93.

**4.6mw LASER POINTER. BRAND NEW MODEL NOW IN STOCK!** supplied in fully built form (looks like a nice pen) complete with handy pocket clip (which also acts as the on/off switch.) About 60 metres range! Runs on 2 AAA batteries. Produces thin red beam ideal for levels, gun sights, experiments etc. just £39.95 ref DEC49 TRADE PRICE £28 MIN 10 PIECES

**BULL TENS UNIT** Fully built and tested TENS (Transcutaneous Electrical Nerve Stimulation) unit, complete with electrodes and full instructions. TENS is used for the relief of pain etc in up to 70% of sufferers. Drug free pain relief, safe and easy to use. can be used in conjunction with analgesics etc. £49 REF TEN/1

**RUSSIAN MONOCULARS** Amazing 20 times magnification, coated lenses, carrying case and shoulder strap £29.95 REF BAR73  
**PC PAL VGA TO TV CONVERTER** Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and sw/are. Ideal for laptops or a cheap upgrade. Supplied in kit form for home assembly. SALE PRICE £25 REF SA34

**EMERGENCY LIGHTING UNIT** Complete unit with 2 double bulb floodlights, built in charger and auto switch. Fully cased, 6v 8AH lead acid req'd. (secondhand) £4 ref MAG4P11.

**YUASHA SEALED LEAD ACID BATTERIES** Two sizes currently available this month. 12v 15AH at £18 ref LOT8 and 6v 10AH (suitable for emergency lights above) at just £6 ref LOT7.

**ELECTRIC CAR WINDOW DEC-ICERS** Complete with cable, plug etc SALE PRICE JUST £4.99 REF SA28

**AUTO SUNCHARGER** 155x300mm solarpanel with diode and 3 metre lead fitted with a cigar plug. 12v 2 watt. £8.99 REF SA25.

**ECLATRON FLASH TUBE** As used in police car flashing lights etc, full spec supplied, 60-100 flashes a min. £6.99 REF SA15B.

\*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

## BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.

BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE

WITH ORDER PLUS £3 P&P PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERY PHONE ORDERS

WELCOME (ACCESS VISA, SWITCH, AMERICAN EXPRESS)

TEL: 01273 203500

FAX 01273 323077

E-mail [bull@pavilion.co.uk](mailto:bull@pavilion.co.uk)

**24v AC 96WATT** Cased power supply. New. £9.99 REF SA40

**MICRODRIVE STRIPPERS** Small cased tape drives ideal for stripping, lots of useful goodies including a smart case, and lots of components. SALE PRICE JUST £4.99 FOR FIVE REF SA26

**SOLAR POWER LAB SPECIAL** You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit SALE PRICE JUST £4.99 REF SA27

**RGB/CGA/EGA/TTL COLOUR MONITORS** 12" in good condition. Back analysed metal case. SALE PRICE £49 REF SA16B

**PLUG IN A CORN PSU** 19v AC 14w, £2.99 REF MAG3P10

**13.8V 1.9A PSU** cased with leads. Just £9.99 REF MAG10P3

**UNIVERSAL SPEED CONTROLLER KIT** Designed by us for the C5 motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink will be required. £17.00 REF: MAG17

**PHONE CABLE AND COMPUTER COMMUNICATIONS PACK** Kit contains 100m of 6 core cable, 100 cable clips, 2 line drivers with RS232 interfaces and all connectors etc. Ideal low cost method of communicating between PCs over a long distance utilizing the serial ports. Complete kit £8.99. Ref comp1.

**VIEWDATA SYSTEMS** made by Phillips, complete with internal 1200/75 modem, keyboard, psu etc RGB and composite outputs, menu driver, autodialler etc. SALE PRICE £12.99 REF SA18

**AIR RIFLES .22AS** used by the Chinese army for training purposes, so there is a lot about! £39.95 Ref EF78. 500 pellets £4.50 ref EF80.

**PLUG IN POWER SUPPLY SALE FROM £1.60** Plugs in to 13A socket with output lead, three types available, 9vdc 150mA £1.50 ref SA19, 9vdc 200mA £2.00 ref SA20, 6.5vdc 500mA £2 ref SA21.

**VIDEO SENDER UNIT.** Transmits both audio and video signals from either a video camera, videorecorder, TV or Computer etc to any standard TV's set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £15 REF: MAG15 12v psu is £5 extra REF: MAG5P2

**\*MINIATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range up to 2km in open country. Units measure 22x5x2x155mm. Including cases and ear/caps. 2xPP3 req'd. £30.00 p.r. REF: MAG30

**\*FM TRANSMITTER KIT** housed in a standard working 13A adapter! the bug runs directly off the mains so lasts forever why pay £700? or price is £15 REF: EP62 (kit) Transmits to any FM radio.

**\*FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies, 9v battery req'd. £14 REF: MAG14

**TALKING COINBOX STRIPPER COMPLETE WITH COIN SLOT MECHANISMS** originally made to retail at £79 each, these units are designed to convert an ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? SALE PRICE JUST £2.50 REF SA23

**GAT AIR PISTOL PACK** Complete with pistol, darts and pellets £12.95 Ref EF82B extra pellets (500) £4.50 ref EF80.

**6"x12" AMORPHOUS SOLAR PANEL** 12v 155x310mm 130mA. SALE PRICE £4.99 REF SA24.

**FIBRE OPTIC CABLE BUMPER PACK** 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30m for £12.99 ref MAG13P1

MIXED GOODIES BOX OF  
MIXED COMPONENTS WEIGHING 2 KILOS  
YOURS FOR JUST £6.99

**4X28 TELESCOPIC SIGHTS** Suitable for all air rifles, ground lenses, good light gathering properties. £19.95 ref R77.

**RATTLE BACKS** Interesting things these, small piece of solid perspex like material that if you try to spin it on the desk it only spins one way! In fact if you spin it the 'wrong' way it stops of its own accord and goes back the other way! £1.99 ref GI/J01.

**GYROSCOPES** Remember these? well we have found a company that still manufactures these popular scientific toys, perfect gift or for educational use etc. £6 ref EP70

**HYPOTHERMIA SPACE BLANKET** 215x150cm aluminised foil blanket, reflects more than 90% of body heat. Also suitable for the construction of two way mirrors! £3.99 each ref O/L041.

**LENSTATIC RANGER COMPASS** Oil filled capsule, strong metal case, large luminous points. Sight line with magnifying view er. 50mm dia, 86gm. £10.99 ref O/K604.

**RECHARGE ORDINARY BATTERIES UP TO 10 TIMES!** With the Battery Wizard! Uses the latest pulse wave charge system to charge all popular brands of ordinary batteries AAA, AA, C, D, four at a time! Led system shows when batteries are charged, automatically rejects unsuitable cells. complete with mains adaptor. BS approved. Price is £21.95 ref EP31.

**TALKING WATCH** Yes, it actually tells you the time at the press of a button. Also features a voice alarm that wakes you up and tells you what the time is! Lithium cell included. £7.99 ref EP26.

**PHOTOGRAPHIC RADAR TRAPS CAN COST YOU YOUR LICENCE!** The new multiband 2000 radar detector can prevent even the most responsible of drivers from losing their licence! Adjustable audible alarm with 8 flashing leds gives instant warning of radar zones. Detects X, K, and Ka bands, 3 mile range, 'over the hill' 'around bends' and 'rear trap' facilities. micro size! just 4.25"x2.5"x.75". Can pay for itself in just one day! £79.95 ref EP3.

**SANYO NICAD PACKS** 120mmx14mm 4.8v 270 mAh suitable for cordless phones etc. Pack of 2 just £5 ref EP78.

**3" DISCS** As used on older Amstrad machines, Spectrum plus3's etc £3 each ref BAR400.

**STEREO MICROSCOPES BACK IN STOCK** Russian, 200x complete with lenses, lights, filters etc etc very comprehensive microscope that would normally be around the £700 mark, our price is just £299 (full money back guarantee) full details in catalogue. Ref 95300.

**WE BUY SURPLUS STOCK  
FOR CASH**  
BUYERS DIRECT LINE 0860 425692  
FREE CATALOGUE

100 PAGE CATALOGUE NOW  
AVAILABLE, 50P STAMP OR FREE  
ON REQUEST WITH ORDER.

CIRCLE NO. 143 ON REPLY CARD

**200 WATT INVERTERS** Nicely cased units 12v input 240v output 150watt continuous, 200 max. £49 ref LOT62.

**6.8MW HELIUM NEON LASERS** New units, £65 ref LOT33  
**COIN SLOT TOKENS** You may have a use for these? mixed bag of 100 tokens £10 ref LOT20.

**PORTABLE X RAY MACHINE PLANS** Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £6/SET Ref F/XP1.

**TELEKINETIC ENHANCER PLANS** Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks yet produces positive motion and effect. Excellent for science projects, magic shows, party demonstrations or serious research & development of this strange and amazing psychic phenomenon. £4/SET Ref F/TK1.

**ELECTRONIC HYPNOSIS PLANS & DATA** This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc only, by those experienced in its use. £15/SET Ref F/EH2.

**GRAVITY GENERATOR PLANS** This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of simple materials and without any visible means - cause it to levitate. £10/SET Ref F/GRA1.

**WORLDS SMALLEST TESLA COIL/LIGHTNING DISPLAY GLOBE PLANS** Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects. 'Plasma in a jar', St Elmo's fire, Corona, excellent science project of conversation piece. £5/SET Ref F/BTC1/LG5.

**COPPER VAPOUR LASER PLANS** Produces 100mw of visible green light. High coherency and spectral quality similar to Argon laser but easier and less costly to build yet far more efficient. This particular design was developed at the Atomic Energy Commission of NEGEV in Israel. £10/SET Ref F/CVL1.

**VOICE SCRAMBLER PLANS** Miniature solid state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £6/SET Ref F/VSS9.

**PULSED TV JOKER PLANS** Little hand held device utilises pulse techniques that will completely disrupt TV picture and sound works on FM too! DISCRETION ADVISED. £8/SET Ref F/TJ5.

**BODYHEAT TELESCOPE PLANS** Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hotspots, heat leaks etc. Intended for security, law enforcement, research and development, etc. Excellent security device or very interesting science project. £8/SET Ref F/BHT1.

**BURNING, CUTTING CO2 LASER PLANS** Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may very well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is easily applicable to burning and etching wood, cutting, plastics, textiles etc. £12/SET Ref F/LC7.

**MYSTERY ANTI GRAVITY DEVICE PLANS** Uses simple concept. Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or science project. £6/SET Ref F/ANT1K.

**ULTRASONIC BLASTER PLANS** Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquids. Many cleaning uses for PC boards, jewelry, coins, small parts etc. £6/SET Ref F/ULB1.

**ULTRA HIGH GAIN AMP/STETHOSCOPIC MIKE/SOUND AND VIBRATION DETECTOR PLANS** Ultrasensitive device enables one to hear a whole new world of sounds. Listen through walls, windows, floors etc. Many applications shown, from law enforcement, nature listening, medical heartbeat, to mechanical devices. £6/SET Ref F/HGA7.

**ANTI DOG FORCE FIELD PLANS** Highly effective circuit produces time variable pulses of acoustical energy that dogs cannot tolerate. £6/SET Ref F/DOG2.

**LASER BOUNCE LISTENER SYSTEM PLANS** Allows you to hear sounds from a premises without gaining access. £12/SET Ref F/LIST1.

**LASER LIGHT SHOW PLANS** Do it yourself plans show three methods. £6 Ref F/LLS1.

**PHASOR BLAST WAVE PISTOL SERIES PLANS** Handheld, has large transducer and battery capacity with external controls. £6/SET Ref F/PPS4.

**INFINITY TRANSMITTER PLANS** Telephone line grabber/room monitor. The ultimate in home/office security and safety! simple to use! Call your home or office phone, push a secret tone on your telephone to access either A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. £7 Ref F/TELEGRAB.

**BUG DETECTOR PLANS** Is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Sniffs out and finds bugs and other sources of bothersome interference. Detects low, high and UHF frequencies. £5/SET Ref F/BD1.

**ELECTROMAGNETIC GUN PLANS** Projects a metal object a considerable distance - requires adult supervision. £5 Ref F/EM2L.

**ELECTRIC MAN PLANS, SHOCK PEOPLE WITH THE TOUCH OF YOUR HAND!** £5/SET Ref F/EMM1.

**PARABOLIC DISH MICROPHONE PLANS** Listen to distant sounds and voices, open windows, sound sources in 'hard to get' or hostile premises. Uses satellite technology to gather distant sounds and focus them to our ultra sensitive electronics. Plans also show an optional wireless link system. £8/SET Ref F/PM5.

**2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND HIGH DC VOLTAGE, SOLID STATE TESLA COIL AND VARIABLE 100,000 VDC OUTPUT GENERATORS PLANS** Operates on 9-12vdc, many possible experiments. £10 Ref F/HVM7/

## WOLVERHAMPTON BRANCH NOW OPEN AT WORCESTER ST W'HAMPTON TEL. 01902 22039

**INFINITY TRANSMITTERS** The ultimate 'bug' fits to any phone or line, undetectable, listen to the conversations in the room from anywhere in the world! 24 hours a day 7 days a week! just call the number and press a button on the mini controller (supplied) and you can hear everything! Monitor conversations for as long as you choose £249 each, complete with leads and mini controller Ref LOT9. Undetectable with normal RF detectors, fitted in seconds, no batteries required, lasts forever!

**SWITCHED MODE PSU'S** 244 watt, +5 32A, +12 6A, -5 0.2A, -12 0.2A. There is also an optional 3.3v 25A rail available. 120/240v I/P. Cased, 175x90x145mm. IEC inlet Suitable for PC use (6 d/drive connectors 1 mboard), £10 Ref PSU1.

**VIDEO PROCESSOR UNITS/76V 10AH BATT/12V 8A TX** Not too sure what the function of these units is but they certainly make good stappers! Measures 390X320X120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connections on the rear. Inside 2x6V 10AH sealed lead acid batts, pcb's and a 8A? 12v toroidal transformer (mains in). Condition not known, may have one or two broken knobs due to poor storage. £17.50 Ref VP2.

**RETRO NIGHT SIGHT** Recognition of a standing man at 300m in 1/4 moonlight, hermetically sealed, runs on 2 AA batteries, 80mm F1.5 lens, 20mw infrared laser included. £325 Ref RETRON.

**MINI FM TRANSMITTER KIT** Very high gain preamp, supplied complete with FET electret microphone. Designed to cover 88-108 Mhz but easily changed to cover 63-130 Mhz. Works with a common 9v (PP3) battery. 0.2W RF. £7 Ref 1001.

**3-30V POWER SUPPLY KIT** Variable, stabilized power supply for lab use. Short circuit protected, suitable for professional or amateur use 24v 3A transformer is needed to complete the kit. £14 Ref 1007.

**1 WATT FM TRANSMITTER KIT** Supplied with piezo electric mic. 8-30vdc. At 25-30v you will get nearly 2 watts! £12 Ref 1009.

**FM/AM SCANNER KIT** Well not quite, you have to turn the knob yourself but you will hear things on this radio that you would not hear on an ordinary radio (even TV). Covers 50-160mhz on both AM and FM. Built in 5 watt amplifier, inc speaker. £15 Ref 1013.

**3 CHANNEL SOUND TO LIGHT KIT** Wireless system, mains operated, separate sensitivity adjustment for each channel, 1,200 w power handling, microphone included. £14 Ref 1014.

**4 WATT FM TRANSMITTER KIT** Small but powerful FM transmitter, 3 RF stages, microphone and audio preamp included. £20 Ref 1028.

**STROBE LIGHT KIT** Adjustable from 1-60 hz (a lot faster than conventional strobes). Mains operated. £16 Ref 1037.

**LIQUID LEVEL DETECTOR KIT** Useful for tanks, ponds, baths, rain alarm, leak detector etc. Will switch 2A mains. £5 Ref 1081.

**COMBINATION LOCK KIT** 9 key, programmable, complete with keypad, will switch 2A mains. 9v dc operation. £10 Ref 1114.

**PHONE BUG DETECTOR KIT** This device will warn you if somebody is eavesdropping on your line. £6 Ref 1130.

**ROBOT VOICE KIT** Interesting circuit that distorts your voice! adjustable, answer the phone with a different voice! 12vdc £9 Ref 1131.

**TELEPHONE BUG KIT** Small bug powered by the phone line, starts transmitting as soon as the phone is picked up! £8 Ref 1135.

**3 CHANNEL LIGHT CHASER KIT** 800 watts per channel, speed and direction controls supplied with 12 LEDs (you can fit triacs instead to make kit mains, not supplied) 9-12vdc £17 Ref 1026.

**12V FLOURESCENT LAMP DRIVER KIT** Light up 4 foot tubes from your car battery! 9v 2a transformer also required. £8 Ref 1069.

**VOX SWITCH KIT** Sound activated switch ideal for making bugging tape recorders etc. adjustable sensitivity. £8 Ref 1073.



Check out our  
WEB SITE

<http://www.pavilion.co.uk/bull-electrical>

**PREAMP MIXER KIT** 3 input mono mixer, sep bass and treble controls plus individual level controls. 18vdc, inputs sens 100mA. £15 Ref 1052.

**METAL DETECTOR KIT** Range 15-20cm, complete with case, 9vdc. £8 Ref 1022.

**SOUND EFFECTS GENERATOR KIT** Produces sounds ranging from bird chips to sirens. Complete with speaker, add sound effects to your projects for just £9 Ref 1045.

**16 WATT FM TRANSMITTER (BUILT)** 4 stage high power, preamp required 12-18vdc, can use ground plane, yagi or open dipole. £69 Ref 1021.

**HUMIDITY METER KIT** Builds into a precision LCD humidity meter, 9 Ic design, pcb, lcd display and all components included. £29

**PC TIMER KIT** Four channel output controlled by your PC, will switch high current mains with relays (supplied). Software supplied so you can program the channels to do what you want whenever you want. Minimum system configuration is 286, VGA, 4.1.640k, serial

\*SOME OF OUR PRODUCTS MAY BE UNLICENSEABLE IN THE UK

## BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.  
BN3 5QT. (ESTABLISHED 50 YEARS)

MAIL ORDER TERMS: CASH, PO OR CHEQUE  
WITH ORDER PLUS £3 P&P PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERYPHONE ORDERS  
WELCOME (ACCESS,VISA, SWITCH, AMERICAN EXPRESS)

TEL: 01273 203500

FAX 01273 323077

E-mail [bull@pavilion.co.uk](mailto:bull@pavilion.co.uk)

port. hard drive with min 100k free. £24.99

**DIVING RODS** Expensive technology cannot challenge the fool proof art of water diving, passed down from generation to generation. Seeing is believing. Use in the home, garden, countryside or desert, it's divinely simple! £4.99 a pair ref E/3.

**HUGE BUBBLE MAKING KIT** You'll be amazed at the size of the bubbles you can achieve with this bubble making kit. Once you have got the knack it is possible to make bubbles of up to 40 feet long. £11.99 ref E/9.

**FM CORDLESS MICROPHONE** This unit is an FM broadcasting station in miniature, 3 transistor transmitter with electret condenser mic - let amp design result in maximum sensitivity and broad frequency response. 90-105mhz, 50-1500hz, 500 foot range in open country! PP3 battery required. £15.00 ref 15P42A.

**MAGNETIC MARBLES** They have been around for a number of years but still give rise to curiosity and amazement. A pack of 12 is just £3.99 ref GI/R20

**STETHOSCOPES** A fully functioning stethoscope for all those intricate projects. Enables you to listen to motors, pipes, heartbeats, walls, insects etc. £5 ref MAR6P6.

**NICKEL PLATING KIT** Professional electroplating kit that will transform rusting parts into showpieces in 3 hours! Will plate onto steel, iron, bronze, gunmetal, copper, welded, silver soldered or brazed joints. Kit includes enough to plate 1,000 sq inches. You will also need a 12v supply, a container and 2 12v light bulbs. £39.99 ref NIK39.

**Miniature adjustable timers, 4 pole c/o output 3A 240v, HY1230S, 12vDC adjustable from 0-30 secs. £4.99**

**HY1260M, 12vDC adjustable from 0-60 mins. £4.99**

**HY2405S, 240v adjustable from 0-5 secs. £4.99**

**HY24060m, 240v adjustable from 0-60 mins. £6.99**

**BUGGING TAPE RECORDER** Small voice activated recorder, uses micro cassette complete with headphones. £28.99 ref MAR29P1.

**POWER SUPPLY** fully cased with mains and o/p leads 17v DC 900mA output. Bargain price £5.99 ref MAG6P9

**9v DC POWER SUPPLY** Standard plug in type 150ma 9v DC with lead and DC power plug. price for two is £2.99 ref AUG3P4.

**COMPOSITE VIDEO KIT** Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: MAG8P2.

**FUTURE PC POWER SUPPLIES** These are 295x135x60mm, 4 drive connectors 1 mother board connector. 150watt, 12v fan, iec inlet and on/off switch. £12 Ref EF6.

**VENUS FLYTRAP KIT** Grow your own carnivorous plant with this simple kit. £3 ref EF34.

**6"X12" AMORPHOUS SOLAR PANEL** 12v 155x310mm 130mA. Bargain price just £5.99 ea REF MAG6P12.

**FIBRE OPTIC CABLE BUMPER PACK** 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

**ROCK LIGHT S** Unusual things these, two pieces of rock that glow when rubbed together believed to cause rain! £3 a pair Ref EF29.

**3' by 1' AMORPHOUS SOLAR PANELS** 14.5v, 700mA 10 watts, aluminium frame, screw terminals, £44.95 ref MAG45.

**ELECTRONIC ACCUPUNCTURE KIT** Builds into an electronic version instead of needles! good to experiment with. £7 ref 7P30

**SHOCKING COIL KIT** Build this little battery operated device into all sorts of things, also gets worms out of the ground! £7 ref 7P36.

**FLYING PARROTS** Easily assembled kit that builds a parrot that actually flaps its wings and flies! 50 m range £6 ref EF2.

**HIGH POWER CATAPULTS** Hinged arm brace for stability, tempered steel yoke, super strength latex power bands. Departure speed of ammunition is in excess of 200 metres per hour! Range of over 200 metres! £7.99 ref R/9

**BALLON MANUFACTURING KIT** British made, small blob blows into a large, long lasting balloon, hours of fun! £3.99 ref GI/R99R

**9-0-9V 4A TRANSFORMERS**, chassis mount. £7 ref LOT19A.

**2.5 KILOWATT INVERTERS, Packed with batteries etc but as they weigh about 100kg CALLERS ONLY! £120.**

**MEGA LED DISPLAYS** Build your self a clock or something with these mega 7 seg displays 55mm high, 38mm wide. 5 on a pcb for just £4.99 ref LOT16 or a bumper pack of 50 displays for just £29 ref LOT17.

**CLEARANCE SECTION, MINIMUM ORDER £15, NO TECHNICAL DETAILS AVAILABLE, NO RETURNS, TRADE WELCOME.**

2000 RESISTORS ON A REEL (SAME VALUE) 99P REF BAR340  
AT LEAST 200 CAPACITORS (SAME VALUE) 99P REF BAR342  
INFRA RED REMOTE CONTROLS JUST 99P REF BAR333

CIRCUIT BREAKERS, OUR CHOICE TO CLEAR 99P REF BAR335  
MICROWAVE CONTROL PANELS TO CLEAR £2 REF BAR 328  
2 TUBES OF CHIPS (2 TYPES OUR CHOICE) 90P REF BAR305

LOTTERY PREDICTOR MACHINE! JUST £1.50 REF BAR313  
HELLA! ROVER ELECTRIC H/LAMP LEVELLER £2 REF BAR311  
SINCLAIR C5 18" TYRES TO CLEAR AT JUST 75P REF BAR318

LARGE MAINS MOTORS (NEW) TO CLEAR AT 75P REF BAR310  
MODEMS ETC FOR STRIPPING £2.50 EACH REF BAR324  
110V LARGE MOTORS (NEW) TO CLEAR AT 50P REF BAR332

MODULATOR UNITS UNKNOWN SPEC JUST 50P REF BAR323  
GX4000 GAMES COINLESS JUST £4 REF BAR320  
SMART CASED MEMORY STORAGE DEVICE, LOADS OF BITS INSIDE, PCB, MOTOR, CASE ETC. BUMPER PACK OF 5 COMPLETE UNITS TO CLEAR AT £2.50 (FOR 5) REF BAR 330.

2 CORE MAINS CABLE 2M LENGTHS PACK OF 4 £1 REF BAR337  
PC USER/BASIC MANUALS, LOADS OF INFO. £1 REF BAR304  
PCB STRIPPERS TO CLEAR AT 2 FOR 99P REF BAR341  
3 M 3CORE MAINS CABLE AND 13A PLUG. 60P REF BAR325

**WE BUY SURPLUS STOCK FOR CASH BUYERS DIRECT LINE 0860 425692**

**FREE CATALOGUE 100 PAGE CATALOGUE NOW AVAILABLE, 45P STAMP OR FREE ON REQUEST WITH ORDER.**

# CLASSIFIED

TEL 0181 652 3620

FAX 0181 652 8956

## ARTICLES WANTED

### WE WANT TO BUY!!

*IN VIEW OF THE EXTREMELY  
RAPID CHANGE TAKING PLACE  
IN THE ELECTRONICS  
INDUSTRY, LARGE QUANTITIES  
OF COMPONENTS BECOME  
REDUNDANT. WE ARE CASH  
PURCHASERS OF SUCH  
MATERIALS AND WOULD  
APPRECIATE A TELEPHONE  
CALL OR A LIST IF AVAILABLE.  
WE PAY TOP PRICES AND  
COLLECT.*

**R. HENSON LTD.**

*21 Lodge Lane, N. Finchley,  
London N12 8JG.*

*5 Mins, from Tally Ho Corner.*

**TELEPHONE**

**0181-445-2713/0749**

**FAX 0181-445-5702**

### VALVES, and CRTs AVAILABLE

ONE MILLION VALVES stocked for Audio, Receiving, Transmitting & RF Heating. Rare brands such as Mullard & GEC available. Also MAGNETRONS, KLYSTRONS, CRTs and SOCKETS.

**Large stocks of Russian & Sovtek items.**

*Please ask for our free catalogues of valves or CRTs.*

### VALVES, etc. WANTED

Most types considered but especially KT88 (£48), PX4/PX25 (£50), KT66 (£35), KT77 (£15), EL34 (£10), EL37 (£9), ECC83 (£3). Valves must be UK manufacture to achieve prices mentioned. Also various valve-era equipment e.g. Garrard 301, (up to) £80. Ask for a free copy of our wanted List.

**BILLINGTON EXPORT LTD., Billingshurst, Sussex RH14 9EZ.**  
Tel: 01403 784961 Fax: 01403 783519

VISITORS STRICTLY BY APPOINTMENT.

MINIMUM ORDER £50 plus VAT

### ! TEST EQUIPMENT WANTED !

SMALL OR LARGE QTY, WORKING OR NON WORKING  
WE PAY THE BEST PRICES FOR YOUR EXCESS INVENTORY!  
FAX YOUR INVENTORY LIST TODAY FOR AN INSTANT QUOTE  
PROMPT PAYMENT AND FAST SERVICE ARE OUR CORPORATE POLICY  
LOTHAR BAIER ELECTRONIC TEST EQUIPMENT, MICROWAVE TECHNOLOGY  
BLUMENSTRASSE 8 D-95213 MUENCHBERG/GERMANY  
PHONE: +49 925192163 FAX: +49 9251 7846

## ARTICLES FOR SALE

# SURPLUS SALE

### THIS MONTH'S SALE INCLUDES:—

Spectrum Analysers, Oscilloscopes,  
Signal Generators, Voltmeters,  
Power Units, Frequency Counters,  
Receivers, Transmitters, Ex PMR Equip,  
Photographic & Video Equipment,  
Components, & Misc Items etc.

*ALL EQUIPMENT IS SOLD AS SEEN.  
ALL PRICES EXCLUDE V.A.T.  
NO MINIMUM ORDER.*

RING TODAY FOR THIS MONTH'S CATALOGUE

### WANTED

#### SURPLUS ELECTRONIC COMPONENTS AND EQUIPMENT

We also welcome the opportunity to quote for complete factory clearance

**B. BAMBER ELECTRONICS**  
5 Station Road, Littleport, Cambs.  
Phone: Ely (01353) 860185  
Fax: Ely (01353) 863245

### ★★WANTED★★

Test equipment, Electronic Scrap,  
Valves, Transmitters/Receivers,  
Factory & Warehouse Clearance.  
Confidentiality Assured.

**TELFORD ELECTRONICS**

Phone: 01952 605451  
Fax: 01952 677978

### WANTED

Test equipment, receivers, valves,  
transmitters, components, cable  
and electronic scrap and quantity.

Prompt service and cash.

**M & B RADIO**

86 Bishopgate Street  
Leeds LS1 4BB

Tel: 0113 2435649  
Fax: 0113 2426881

### ELECTRONICS VALVES & SEMICONDUCTORS

Phone for a most  
courteous quotation

We are one of the largest  
stockists of valves etc,  
in the U.K.

### COLOMOR ELECTRONICS LTD

170 Goldhawk Road,  
London W12 8HJ  
England.

Tel: 0181 743 0899  
Fax: 0181 749 3934

### TOP PRICES PAID

For all your valves, tubes, semi  
conductors and IC's.

**Langrex Supplies Limited**

1 Mayo Road, Croydon  
Surrey CR0 2QP

TEL: 0181-684 1166  
FAX: 0181-684 3056

### WANTED

#### TOP PRICES PAID

For all your Test Equipment,  
Receivers, Transmitters etc.  
Factory Clearance, Prompt  
Service and Payment.

**HTB ELEKTRONIK**

Alter Apeler Weg 5  
27619 Schiffdorf, Germany  
Tel: 0049 4706 7044  
Fax: 0049 4706 7049

# CLASSIFIED

TEL 0181 652 3620

FAX 0181 652 8956

## ARTICLES FOR SALE



### SUPPLIER OF QUALITY USED TEST INSTRUMENTS



CONTACT


### Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS  
Unit Four, Fordingbridge Site, Main Road, Barnham,  
Bognor Regis, West Sussex, PO22 0EB  
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

**CIRCLE NO. 146 ON REPLY CARD**



### OPERATING & SERVICE MANUALS

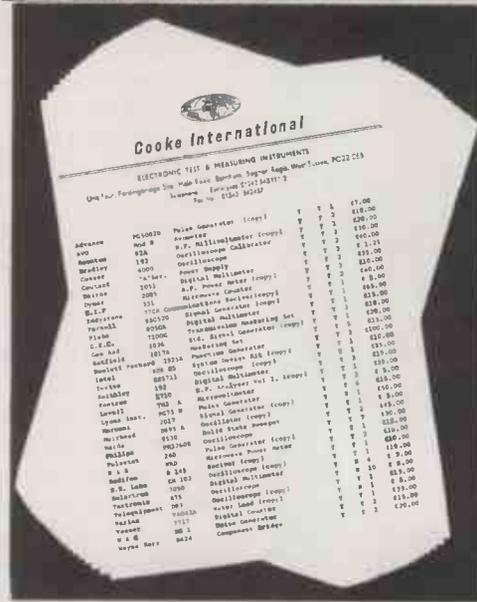

CONTACT

### Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS  
Unit Four, Fordingbridge Site, Main Road, Barnham,  
Bognor Regis, West Sussex, PO22 0EB  
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

**CIRCLE NO. 147 ON REPLY CARD**

### Field Electric Ltd

Unit 2, Willows Link, Stevenage,  
SG2 8AB

Tel: 01438 353781 Fax: 01438 359397  
0836 640328

AUDIO, COMPUTER, COMMUNICATIONS,  
TEST & PROFESSIONAL VIDEO  
HARDWARE PURCHASED, SOLD, STOCK  
LIST AVAILABLE, PLEASE RING.  
QTY-DISCOUNT & OVERSEAS  
ENQUIRIES WELCOME.

ZED was a superb editor for Gemini CP/M systems. Who wrote it? Please phone Rodney Harris 01-734 876641.

83 ELECTRONICS WORLD back issues May 87 through Jan 95. London NW. Lot for 100. Buyer collects. 0181 909 2423.

WANTED: Tektronix 7603/13/23 main-frame with plug-ins (non)working, manuals. Send your offer to M.S. Nielsen, Højker 35 6.TV 2605 Brøndby, Denmark; or call/fax +45 36 47 41 58.

WANTED: AVO model 8 Mk1 or Mk2 with broken movement. 01326 312901.

WANTED: W.S.18 W.S.62 suitcase sets (50E) crypto equipment, German WW2 gear for museum purposes only. Lashe R. Otterstad, PO Box 73, Ljan N-1113 Oslo, Norway.

MICROCHIP PICMASTER EMULATOR, 16C5X+71, PODs, £1,550. Ice-Tech Micromaster Universal programmer, £370. Philips OM4282 R.F.I.D. transponder development system, £280. 01295 810859.

PAIR OF LOWTHER PM6 units, boxed, suitable for horn design in December issue, £150. Tel. 01295 810859.

ELECTRONIC COMPONENTS. Large quantity new passive, active, cabinets, power supplies, etc, etc, £225 ono. Would suit enthusiast. Wilm-slow 01625 527282.

SMALL selection of aircraft starter motors, DC generators and rotary converters. Possibly suit electric vehicles, etc, £5 to £50 depending on condition and type. Tel. Bristol 0117 979883.

### Consider . . . . .

Your costs to continue to stock  
UNWANTED SURPLUS . . . EXCESS . . . OBSOLETE  
STOCKS OF:-  
ELECTRONIC-ELECTRICAL COMPONENTS &  
ACCESSORIES

**RELEASE**  
for  
**PAYMENT IN ADVANCE**  
OF COLLECTION  
contact

### K.B. Components,

21 Playle Chase, Gt. Totham, Maldon, Essex, CM9 8UT  
Tel:- 01621 893204 Fax:- 01621 893180 Mobile:- 0802 392745

REGISTER TO RECEIVE MONTHLY PUBLISHED STOCK LISTS AT NO CHARGE OF ALL EXISTING NEW, UNUSED, STOCKS OF ALL COMPONENTS AND ACCESSORIES.

## INDEX TO ADVERTISERS

	PAGE		PAGE		PAGE
Airtex Controls	339	Johns Radio	272	Radio Tech	321
BK Electronics	312	JGP	334	Ralfe Electronics	IBC
Bull Electrical	348, 349	Kestral	339	Robinson Marshall	303
Chelmer Value	339	Keytronics	316	Stag Programmers	266
Crownhill Associates	347	Labcentre	299	Surrey Electronics	347
CPC	295	LCE	334	Technology Sources	311
Crossware Products	312	M & B Radio (Leeds)	321	Telford	323
Dataman	OBC	Milford Instruments	339	Telnet	331
Electromail	289	Noral	279	Those Engineers	331
Equinox Technologies	334	Oema	325	Tie Pie	340
Halcyon Electronics	347	Pico Techniques	325	Tsien	323
Hart	271	Quickroute Systems	266	Ultimate Technology	IFC
Iosis	266				

# Radio Communications

RF Design

Digital Design

Digital Signal Processing

£18,000 to £37,000

Roke Manor Research is a Siemens company at the forefront of electronics R&D applied to communications, sensors and software. We offer our services to Siemens, Government and third party customers.

Roke Manor Research plays a crucial role in supplying solutions to the current personal communications revolution. As the Siemens centre of excellence for radio system design, Roke Manor Research is looking for team-players to take up the challenge of developing digital cellular terminals, digital cordless terminals, wireless local loop systems, digital audio broadcast equipment and military systems. To meet this challenge you will be a graduate with 2-5 years experience in:

- **RF design** – up to 2.5 GHz, familiarity with CAD tools and awareness of design for production.
  - **Digital Design** – VHDL, digital ASIC and EPLD design with an awareness of analogue design techniques.
  - **DSP** – Algorithm design and implementation for radio communications systems.
- The success and reputation of Roke Manor Research depends entirely on the innovation, motivation and flexibility of its employees. Your desire to succeed in this world class electronic engineering environment will be amply rewarded with a first class salary and relocation assistance. Situated in 24 secluded acres of rural Hampshire, Roke Manor Research offers a refreshingly different and dynamic working environment close to the New Forest and South Coast. To apply please send your CV to Ian Collins, Recruitment Officer, Roke Manor Research, Romsey, Hants SO51 0ZN or contact The Resourcing Team on Tel: 01794 833454, email: [ian\\_collins@roke.co.uk](mailto:ian_collins@roke.co.uk).

# Roke Manor Research

A Siemens Company  
<http://www.roke.co.uk/>

# ELECTRONIC UPDATE

Contact Malcolm Wells on  
0181-652 3620

A regular advertising feature enabling readers to obtain more information on companies' products or services.



### New Flight Electronics International Catalogue Set

You now have access to the world's latest:

- ★ Electronics Training Equipment
- ★ Microprocessor Training Equipment
- ★ Test and Measurement Equipment
- ★ PC Cards

via "Flight's" latest catalogue set. We are specialists in the provision of innovative top quality electronics trainers, breadboards, test and measurement, PC cards and microprocessor evaluation equipment.

Our extensive range covers every need, call today for your free catalogue set.

**CIRCLE NO. 116 ON REPLY CARD**



### NEW CATALOGUE

The new 1996 National Instruments Instrumentation Reference and Catalogue is available now. Discover how to develop integrated systems for test and measurement and industrial automation. Includes details of over 500 software and hardware products for PCs and workstations. Includes valuable tutorials on data acquisition and instrument control.

**NATIONAL INSTRUMENTS**  
Tel: 01635 523545

**CIRCLE NO. 117 ON REPLY CARD**



### NEW Feedback T&M Catalogue

The latest edition of the Feedback Test & Measurement catalogue is now available. Over 60 pages packed with more than 800 products divided into over 20 sections. The catalogue is indexed for both product and manufacturer and is fully illustrated. Whether you are looking for an individual product, a complete workstation, or a solution to a particular Test & Measurement catalogue will solve your problems, send for a copy NOW!

**CIRCLE NO. 118 ON REPLY CARD**



### 1995 MASTER PRODUCT CATALOGUE NOW OUT!

Test and instrument control solutions. 48 pages of full description and technical data on our own range of solutions to your PC and PS2 interlocking problems: IEEE488 (GPIB) \* DIO \* Timer/Counters \* RS232 \* RS422/485 \* A/D \* D/A \* plus Opto Isolated versions. New Parallel/Serial RS232, Opto Dual RS232, Motion Control, Converter and Repeater for 1995!

- ISO 9001 Quality guarantee ✓
- UK design and manufacture ✓
- 36 month no-quibble warranty ✓
- Telephone hotline support ✓
- Competitive pricing on the page ✓
- Intelligent solutions 8 friendly service ✓

**BRAIN BOXES**  
Unif 3f Wavertree Boulevard South  
Wavertree Technology Park  
Liverpool L7 9PF  
Tel: 0151 220 2500 Fax: 0151 252 0446

**CIRCLE NO. 119 ON REPLY CARD**

## SPECTRUM ANALYSERS



- HP8557A 350MHz (fitted in 182C mainframe) £1500
- HP3580A 5Hz-50kHz audio frequency spectrum analyser £750 to £1250
- HP3582A audio frequency fft analyser dual-channel £2000
- HP8566A high-specification 1.5GHz spectrum analyser £7500
- MARCONI 2386 100Hz-26.5GHz (in 1Hz steps!) £15000
- AVCOM-portable 2 in stock, 1GHz. No other details at this time.....
- TEKTRONIX 492 21GHz portable spectrum analyser, with options 12&3, and complete with waveguide mixer set (& diplexer) to cover 18-40GHz £7000

## MARCONI INSTRUMENTS



- 20918A synthesized AM/FM signal generator 80kHz-520MHz £1250
- 2019A synthesized AM/FM signal gen 80kHz-1040MHz £2000
- 2305 modulation analyser 50kHz-2.3GHz £2500
- 2828A/2829 digital simulator/analyser £500
- 2955B radio communications test sets - LATEST 'B' MODEL £4000
- 2926 TV generator & inserter (NTSC variant) £500
- 6460/6421 power meter & sensor 10 MHz-12.4GHz £350
- 6514 waveguide detector for use with 6500-scalar analyser 26-40GHz £350
- 6960 microwave power meter with 6910 power sensor 10MHz-20GHz £900
- OA2805A pcm regenerator test set £750
- TF2910/4 non-linear distortion (video) test set £500
- TF2910 TV interval timer £250

## ● ralf electronics ● exclusively professional T&M ©

● 36 Eastcote Lane ● South Harrow ● Middx HA2 8DB ● England ●  
TEL (+44) 0181-422 3593 ● FAX (+44) 0181-423 4009

EST  
45  
YRS



DISTRIBUZIONE E ASSISTENZA ITALY: TLC RADIO. ROMA (06) 871 90254

## TEST EQUIPMENT

- ANRITSU MF76A 18GHz microwave frequency counter £1500
- BRUEL & KJAER 1023 sine generator £1250
- BRUEL & KJAER 1027 sine random generator £1750
- BRUEL & KJAER 2033 single channel audio spectrum analyser £2500
- BRUEL & KJAER 2619 preamplifier £250
- BRUEL & KJAER 2511 vibration meter (field set with 1621 filter) £1500
- BRUEL & KJAER 2307 level recorder £1000
- BRUEL & KJAER 2317 portable level recorder £1500
- BRUEL & KJAER 2607 measuring amplifier £600
- BRUEL & KJAER 2609 measuring amplifier £750
- BRUEL & KJAER 2308 analogue X-Y pen recorder £750
- CHASE LFR 1000 interference measuring receiver 9kHz-150kHz £1000
- DATRON 1061 & 1061A - various, digital multimeter & 1065 - call from £500
- DATRON 1065 digital multimeter all ranges plus IEEE £500
- FARNELL 2081/100 100W RF power meter DC-500MHz (1GHz) £200
- JJ INSTRUMENTS CR600 2-channel pen recorder £250
- KIKUSUI 8520 frequency response analyser with sweep generator 4600 £500
- PHILIPS PM5167 1mHz-10MHz function generator £275
- PHILIPS PM8272 X-Y & Y-I dual-channel pen recorder £850
- RACAL 9008 automatic modulation meter £350
- RACAL-DANA 9300 milli-voltmeter £400
- RACAL-DANA 9301A true RMS RF milli-voltmeter £350
- SYSTRON DONNER 1300 synthesized signal generator 100Hz-1GHz GPIB £1350
- TEKTRONIX AA501 / SG505 distortion analyser (complete with TM503) £1250
- TEKTRONIX P6303 o'scope probes NEW 250MHz X1/X10 with readout pin £50ea
- TEKTRONIX 2465 option CTS oscilloscope £2000
- TEKTRONIX P6201 FET PROBE £350
- WANDEL & GOLTERMANN WM30 level tracer £500
- WANDEL & GOLTERMANN PJM-4S jitter meter for SONET & SDH £5500
- WAVETEK 23 synthesized function generator 0.01Hz-12MHz £1250
- WAVETEK 1067 opt 522 1-500MHz sweep generator £500
- WAYNE KERR 3220 20A bias unit (for 3245 inductance analyser) £1250
- WAYNE KERR 3245 inductance analyser £3000
- TEKTRONIX 1502B/03/04 short-range metal-cable tdr tester £3500
- TEKTRONIX 1503 tdr metallic-cable tester with opts 03/04 £1000

## HEWLETT PACKARD



- 1640B serial data generator £500
- 3561A dynamics signal analyser (opt 01) £5500
- 3764A digital transmission analyser £2000
- 3335A synthesizer/level generator £2000
- 3400A voltmeter, analogue 10Hz-10MHz £250
- 3235A switch/test unit £1000
- 3324A synthesized function generator £2000
- 3456A digital multimeter £750
- 3580A audio frequency spectrum analyser £750 to £1250
- 3581C selective voltmeter £1250
- 3582A dual-channel spectrum analyser 0.02Hz-25.5kHz £2000
- 3779D primary multiplex analyser £3000
- 4140B pA/meter, DC voltage source £4000
- 4339A high resistance meter c/w lead set 16117B £2000
- 4275A multi-frequency lcr meter £3500
- 435B microwave power meter, analogue £400
- 5334B frequency counter w option 010 high-stab & Channel C £1500
- 5386A 3GHz frequency counter £1500
- 54100A 1GHz digitizing oscilloscope £2250
- 6012A power supply 0-60V 0-50A 1000W £650
- 6033A system power supply 0-20V 0-30A £1000
- 6253A dual power supply 0-20V 0-1A twice £250
- 6443B power supply 0-120V 0-2.5A £400
- 6825A bipolar power supply/amplifier -20V to +20V, 0-1A £350
- 8007B pulse generator 100MHz £950
- 8018A serial date generator £1000
- 8082A pulse generator 250MHz £2000
- 8111A pulse generator 20MHz £1250
- 816A slotted line 1.8-18GHz with 809C & 447B probe £500
- 8444A tracking generator with option 059 £1250
- 8568A spectrum analyser 100Hz-1.5GHz £7500
- 8656B synthesized signal generator to 990MHz £3000
- 8673M 2-18GHz synthesized signal generator £7500
- 87510A gain-phase analyser 100kHz-300MHz £6500
- 8901A modulation analyser with option 02/010 £3500
- 8903A audio analyser £2000
- J2215A FDDI portable multimode test set £1500
- J2219A 486-based, colour option main-frame £1000
- J2219A/J2171A 486-based colour screen option network advisor £4000
- J2309A ethernet/token ring interface (for J2302A advisor) £3000

## HP37724A SDH/PDH portable test sets -

Condition as new, price £5000 (were listing at ca £20K!) - also 37772A optical interfaces available for STM-1, £1500 (list over 6K)

### \* SPECIAL OFFER THIS MONTH ONLY \*

ALL ORDERS FOR ADVERTISED EQUIPMENT RECEIVED THRU APRIL WILL BE ISSUED WITH CALIBRATION CERTIFICATION BY INDEPENDENT LABORATORY AT NO EXTRA CHARGE

Just quote reference WWApril96

## ● ralf electronics ● exclusively professional T&M ©

SEND FOR LATEST STOCK LIST. WE FAX LISTS AND SHIP WORLDWIDE. ALL FULLY LAB-TESTED AND NO-QUIBBLE GUARANTEE

ISO9002 ACCREDITED STOCKIST  
MEASUREMENT & TEST EQUIPMENT




CIRCLE NO. 101 ON REPLY CARD

ISO9002 ACCREDITED STOCKIST - MEASUREMENT & TEST EQUIPMENT

£495 + VAT
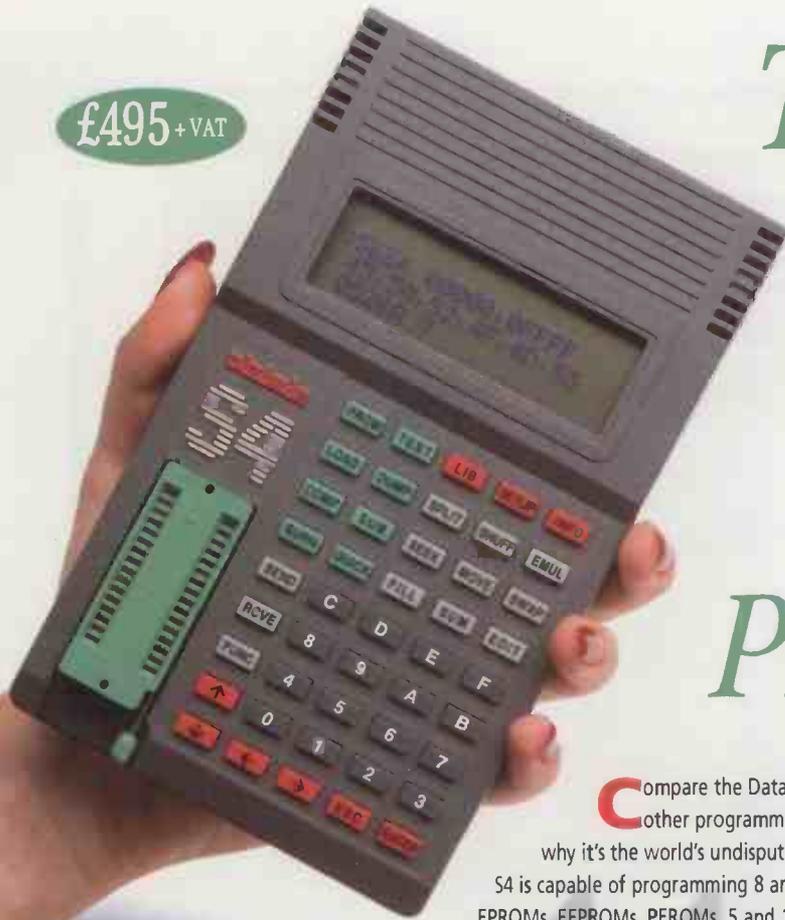
# THE WORLD'S MOST POWERFUL, PORTABLE PROGRAMMERS



Compare the Dataman S4 with any other programmer and you'll see why it's the world's undisputed number one.

S4 is capable of programming 8 and 16-bit EPROMs, EEPROMs, PEROMs, 5 and 12V FLASH, BOOT-BLOCK FLASH, PICs, 8751 Microcontrollers and more. S4 also emulates ROM and RAM as standard! S4 is the only truly hand held programmer that ships complete with all emulation leads, organiser-style manual, AC charger, spare library ROM, both DOS and Windows terminal software, and arrives fully charged and ready to go! Who else offers you all this plus a three year guarantee?

Customer support is second to none. The very latest programming library is always available free on the Internet, and on our dedicated bulletin boards. Customers NEVER pay for upgrades or technical support.

## Dataman-48

Our new Dataman-48 programmer adds Pinsmart® technology to provide true no-adaptor programming right up to 48-pin DIL devices. Dataman-48 connects

straight to your PC's parallel port and works great with laptops. Coming complete with an integral world standard PSU, you can take this one-stop programming solution anywhere!

As with S4, you get free software upgrades and technical support for life, so now you don't need to keep paying just to keep programming.

The current device library contains over 1500 of the most popular logic and memory devices including GALs, PALs, CEPALS, RALs, 8 and 16-bit EPROMs, EEPROMs, PEROMs, FLASH, BOOT-BLOCK, BIPOLAR, MACH, FPGAs, PICs and many other Micro-Controllers. We even include a 44-pin universal PLCC adaptor.

If you need to program different packaging styles, we stock adaptors for SOP, TSOP, QFP, SDIP as well as memory emulation pods.

Order your Dataman programming solution today via our credit card hotline and receive it tomorrow. For more detailed information on these and other market leading programming products, call now and request your free copy of our new colour brochure.

## The Dataman Challenge

Try the Dataman S4 or Dataman-48 without obligation for 30 days. If you do not agree that these are the most effective, most useful, most versatile additions you can make to your programming toolbox, we will refund your money in full.

£795 + VAT



Dataman Programmers Ltd,  
Station Road, Maiden Newton,  
Dorset DT2 0AE. UK

Telephone +44/0 1300 320719  
Fax +44/0 1300 321012

BBS +44/0 1300 321095 (24hr)  
Modem V.34/V.FC/V.32bis

Home page: <http://www.dataman.com>

FTP: <ftp.dataman.com>

Email: [sales@dataman.com](mailto:sales@dataman.com)

Credit  
Card Hotline  
01300 320719

Orders received by 4pm will normally be despatched same day. Order today, get it tomorrow!

