

Solid-state gyro - special reader offer

ELECTRONICS WORLD

INCORPORATING WIRELESS WORLD

October 1996 £2.25

Austria Asch. 65.00
Denmark DKr. 66.00
Germany DM 15.00
Greece Dra. 1000.00
Holland Dfl. 11.50
Italy L. 8500.00
Malta Lm. 1.45
IR £3.30
Singapore S\$12.60
Spain Pts. 800
USA \$5.50

A REED BUSINESS PUBLICATION
SOR DISTRIBUTION

Motional feedback headphones

**New voltage
multiplier**


**Selling the
radio
spectrum**

**Analogue pc
interface**

**Digits to
speech chips**

**Low-loss rf
coupler**

**Phono
preamplifier**

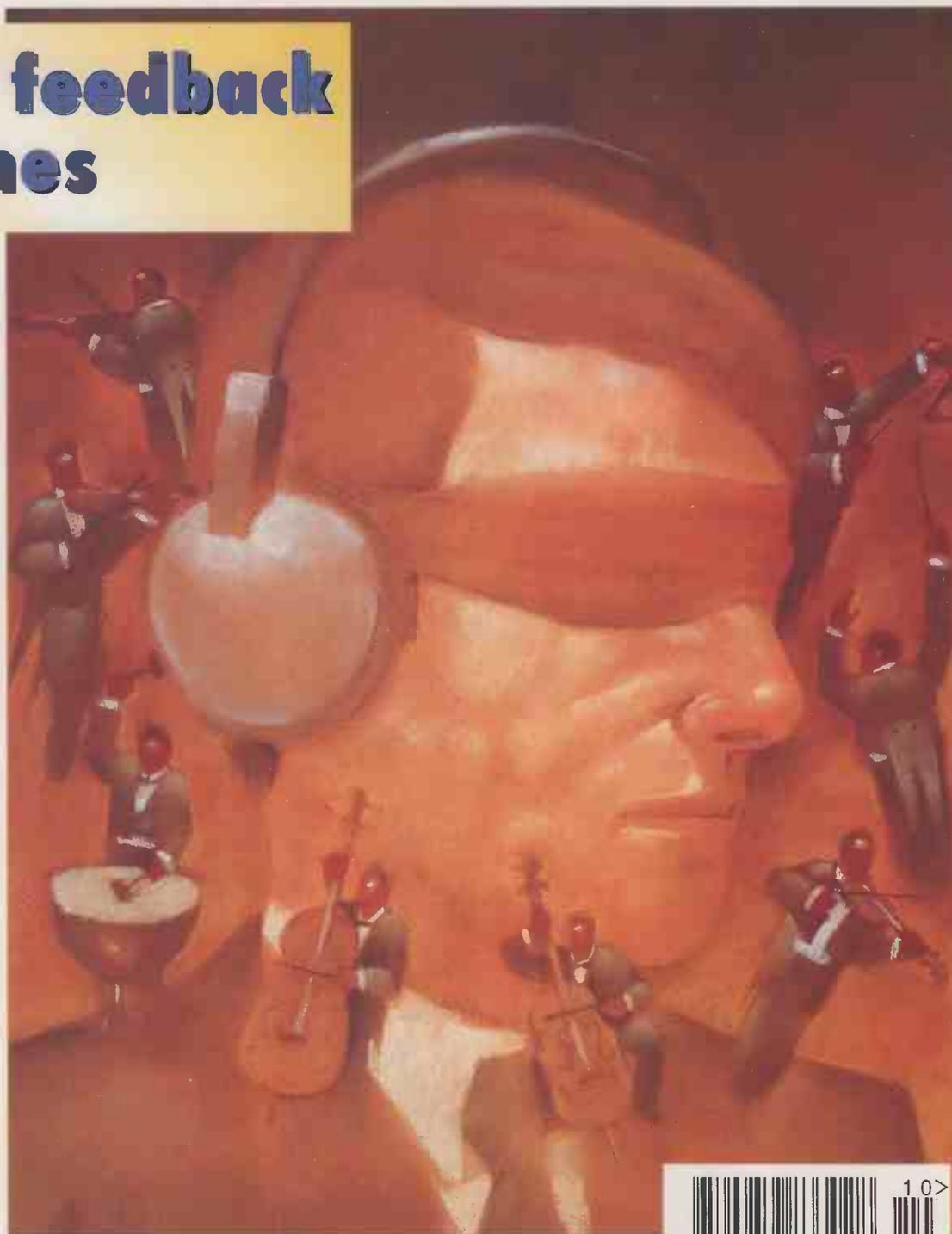

PCB CAD reviews - Ranger 2 and Workbench



MICRO-PRO 51

State-of-the-art programmer
for the 8051 family

Also programs many
SERIAL EEPROMS and
FLASH MEMORY DEVICES
(optional chargeable update)

(1) Connects to PC parallel port...

Fast parallel transfer ensures the fastest possible device programming times

(2) Field Programmable Hardware...


Optimised hardware for each target device to be programmed is downloaded from the PC into a Field Programmable Gate Array

(3) Accepts up to 40-pin DIL devices directly...

Package adaptors available for P₁CC, SOIC etc.



CERTIFIED BY

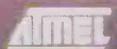

Programs the on - chip code ROM of many 8051 derivatives including:

Atmel	AT89C-1051/2051/51/52/55, 89S8252
Intel/Phillips	87C51/FA/FB, 87C52
Dallas	87C520

System now comes complete with PSU and parallel cable
PLUS FREE Atmel AT89C2051 microcontroller + Atmel CD-ROM

C2

CIRCLE NO. 102 ON REPLY CARD

ONLY £125



229 Greenmount Lane, Bolton, BL15JB UK

Tel Sales: +44(0) 1204 492010

Fax: +44(0) 1204 494883

e-mail: sales@equintec.demon.co.uk

Web page: www.demon.co.uk/equintec

Contents

Cover - Jamel Akib



730 MUSIC IN MIND

With headphones, when you turn your head, the sound source moves with you. Ian Hickman has been investigating a cure involving a low-cost gyroscope.

736 A-TO-D VIA THE COM PORT

Interfacing via the pc's COM port and accessible using simple Basic routines, David Gains' converter logs four sensors.

743 THE ROUTE TO PCB CAD

Rod Cooper complements his second set of pcb cad reviews - for Ranger2 and Electronics Workbench - with a discussion of standards and display limitations.

750 A-TO-D AND D-TO-A CONVERTER

Although simple, Yongping Xia's LPT analogue pc interface resolves to 12 bits.

754 THERMAL DYNAMICS IN AUDIO POWER

Douglas Self explains how to reduce power amplifier distortion via tighter bias accuracy.

758 A RATIONALISED PHONO PREAMPLIFIER

Simon Bateson's RIAA phono preamplifier is economical - yet offers benefits over existing designs.

760 HANDS-ON INTERNET

Cyril Bateman looks at 'mirrors', electronics design data and new ways to search old services on the Web.

763 HIGH DIRECTIVITY RF COUPLER

Paolo Antoniazzi has developed a method of producing couplers usable at gigahertz frequencies but made from standard low-cost fibreglass printed circuit.

769 FILTER VARIATIONS

Active filters are the subjects of many in-depth discussions, but Ian Hickman believes that some important design aspects are frequently overlooked.

773 VIDEO INSERTER

Ian Polczynski discusses software required for the video time, date and text inserter.

781 HESITANT PRICING OF THE RADIO SPECTRUM

DTI's proposals for spectrum pricing promise large benefits to the UK economy - provided some traditional assumptions can be relinquished, reasons David Rudd.

786 APPLYING SPEECH STORAGE CHIPS

Colin Attenborough shows how easy it is to apply speech storage and playback chips using talking weighing scales as an example.

795 STEPPING OUT

Ian Hegglun's new voltage multiplier configuration promises higher efficiency and simpler implementations.

Regulars

723 COMMENT

Testing time for EMC.

724 NEWS

Multi-level cell, Digital Ceefax, EMC down under, European CDMA, New CE guidelines, Drop in pay rises, MPEG-4, Linear radio, New FPGA tool for designers, JPEG 2000, Anti-terrorism identification chip.

727 RESEARCH NOTES

Gel for snorers, Darts in space, Gyroscope in orbit, Robot gardener, DSP helps understanding, Xenon ion rocket engine.

790 LETTERS

Questions and Answers, followed by Ball lightning, Crossover networks, Power amplifier thermal effects and more on p. 793.

799 NEW PRODUCTS

Pick of the month - classified for convenience.

807 CIRCUIT IDEAS

12-bit current loop, Message module, Diac lamp flasher, FM communicator, Fund raiser.



This directional coupler works at gigahertz frequencies but is fabricated using standard fibre-glass pcb - page 763.



Gyroscopes aboard the Gravity probe B mission could answer a lot of questions posed by Einstein's theories on gravity as a field - page 728.




Measuring 21.5 by 8.5 by 7.6mm, the ENC-05E gyroscope handles up to 50 changes in direction a second and a maximum angular velocity of $\pm 90^\circ/s$. EW readers can buy one for around £80 - see page 734.

**NOVEMBER ISSUE
ON SALE 10 OCTOBER**

"extremely good value for money for such a comprehensive package"



Practical Wireless July 96

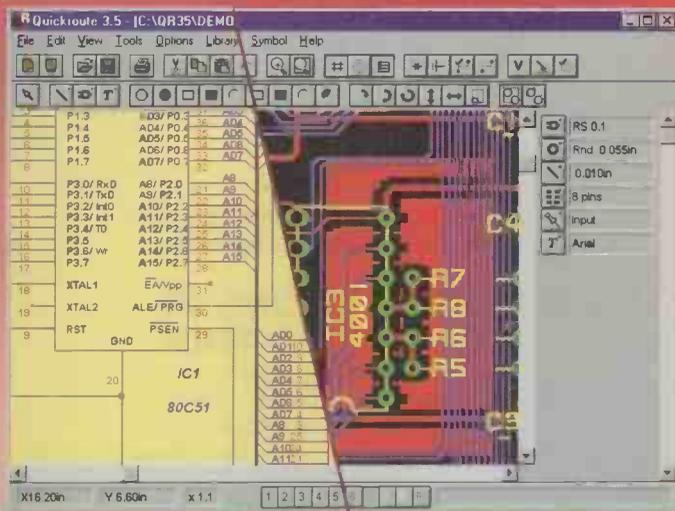

	Personal	Designer	PRO	PRO+
PCB & Schematic Design	*	*	*	*
Schematic Capture		*	*	*
Design Rule Checking		*	*	*
Connectivity Checking		1	1	2
Route ASSIST (assisted routing)		*	*	*
Auto router			*	*
Export WMF & Tango			*	*
Export Gerber/NC-Drill			*	*
Extended Libraries			*	*
Tango + Gerber Import				*
Update PC + schematic				*
DXI & IFC Import				*
Copper fill				*

1 Simple pass/fail 2 Advanced Check

NEW Library Packs Available!

Quickroute 3.5 is a powerful, affordable and easy to use integrated schematic & PCB design system for windows. With its multiple button bars, 'tool tips', and 'parts bin' Quickroute helps you to get working quickly and efficiently


Quickroute is available in 4 different versions (see Table) all of which offer great value for money. Quickroute is available with multi-sheet schematic capture, 1-8 layer auto-routing, copper fill, engineering change, and a range of popular file import/export features allowing connection to simulators and other software packages (details on request). Prices are Personal (£68), Designer (£149), PRO (£249) and PRO+ (£399). Please add P&P and V.A.T to total (see below*).



from **£68**

SMART
ROUTE

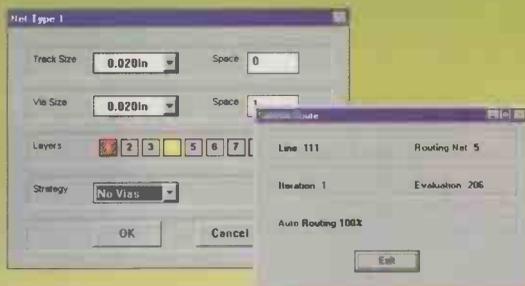NEW THE 32 BIT AUTO-ROUTER WITH FLEXIBILITY & POWER



SMARTRoute 1.0 is a new 32 bit auto-router that offers amazing flexibility & power at an affordable price! Compatible with Windows 3.1/95/NT, SMARTRoute gives you total control over routing strategies including layers used, track & via sizes, design rules, etc.

SMARTRoute is completely compatible with Quickroute 3.5 and offers improved completion rates compared with Quickroute's built in auto-router (ask for details) SMARTRoute is available for £149 plus P&P and V.A.T. Special bundle pricing for Quickroute and SMARTRoute when purchased together.



Just **£149**


M
EXPRESS

VISUALISATION, DATA ANALYSIS & APPLICATION DEVELOPMENT



MExpress is a powerful tool that can be used interactively to load, analyse and display data - or by using its powerful BASIC-like scripting language - you can create technical applications with buttons, menus, 2D & 3D graphics, and powerful numerical methods (ask for details).

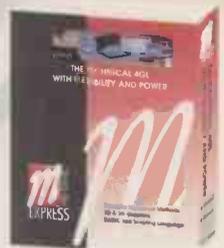MExpress is available in Standard (£99) and Developers Editions (£299). Prices exclude P&P and V.A.T (see below*). The Developers Edition includes tools for turning MExpress script files into C++ code. This can then be compiled by an MExpress compatible C++ compiler into a stand alone executable!



from **£99**

QUICKROUTE SYSTEMS

"The Engineering & Scientific Software People"

Quickroute Systems Ltd., 14 Ley Lane, Marple Bridge, Stockport, SK6 5DD, U.K.

Tel/Fax 0161 449 7101

WWW: www.quickroute.co.uk EMail: info@quicksystem.demon.co.uk

*Post & Packing £5 (UK), £8 (Europe), £12 (World). Please add V.A.T to total. Prices and specifications subject to change without notice. All trade marks are acknowledged & respected. All products sold subject to our standard terms & conditions (available on request)

Testing time for EMC

EDITOR

Martin Eccles
0181 652 3128

EDITORIAL ASSISTANT

Mark Hefley
0181 652 8638

CONSULTANTS

Jonathan Campbell
Philip Darrington
Frank Ogden

DESIGN

Alan Kerr

EDITORIAL ADMINISTRATION

Jackie Lowe
0181-652 3614

E-MAIL ORDERS

jackie.lowe@rbp.co.uk

ADVERTISEMENT MANAGER

Richard Napier
0181-652 3620

DISPLAY SALES EXECUTIVE

Malcolm Wells
0181-652 3620

ADVERTISING PRODUCTION

0181-652 3620

PUBLISHER

Mick Elliott

EDITORIAL FAX

0181-652 8956

CLASSIFIED FAX

0181-652 8956

SUBSCRIPTION HOTLINE

01622 778000

Quote ref INJ

SUBSCRIPTION QUERIES

01444 445566

FAX 01444 445447

ISSN 0959-8332

NEWSAGENT ENQUIRIES

Contact MarketForce
(UK) Ltd.

Telephone:

0171-261 5555

Fax: 0171-261 6106



While most engineers would agree with Anthony Hopwood, Letters *EW* March, that there is too much pollution of the electromagnetic spectrum, the way that the European EMC laws have been drafted by our politicians is sure to stifle innovation at grass-roots level. What small company can risk such swingeing fines or what individual engineer can risk three months in prison? To a professional engineer this is comparatively more devastating than similar sentences presently being handed out to low-life rapists and muggers, so I am sure the attitude of many engineers and small firms will be 'why bother bringing a new product to the market place in Europe?'

I have never believed that membership of the EEC has been, *per se*, a good idea for UK industry. The theory that the UK would sink without EEC membership has never been proved. It must rank as one of the more nebulous political arguments promulgated by Euro-fanatics but despite this it is always trotted out on a regular basis to silence critics of the EEC as though it were irrefutable truth.

Any benefit from the EEC – if there has in fact been any – has been overshadowed by such dismal concepts as the Common Agricultural Policy and the monetary policy. Both of these have been disasters for the UK. Industry has also had an extra bureaucratic burden in the form of Value Added Tax – that most European of taxes. And now we have the EMC harmonisation laws. But if you think these were bad, wait until the Low Voltage Directive comes into effect on 1 January next year. I can see many small electronics firms just giving up when faced with both.

I expect that many of those small businessmen who voted us into the Common Market expecting to enjoy a free trade area are now wringing their hands at the never-ending avalanche of bureaucracy aimed at them from that very source.

These two pieces of legislation have all the hallmarks of having been put together by that fatal combination of big business, bureaucrats, and lawyers; fatal that is for entrepreneurs and innovation. Under this legislation, the outlook for any aspiring small electronics company in Europe is grim. The large multinational conglomerates probably had a large say in how the legislation was drafted and will not feel the pinch at all. They are sure to use the legislation against any small competitor if they attempt self-certification, but the only alternative to self-certification is the high cost of third party certification.

I recently observed the demise of two projects due to the new EMC legislation. Due to both the cost and the uncertainty associated with complying with the new EMC regulations, the plug was pulled on these specialised short-run projects. It doesn't take much imagination to see that this will be happening to a greater or lesser extent all over Europe, with many of those useful electronic gadgets and devices produced by small firms – which oil the wheels in industry, commerce and the home – not being brought to market.

One reason why this legislation has been thrust upon the industry is that engineers have never organised themselves into a quasi-political pressure group in the way that other professionals like doctors, lawyers and those running Britain's newspapers and financial institutions have done. This could explain engineers' low status in society, relatively low pay and the almost total lack of political clout that could have prevented the present predicament with the EMC laws – a situation that shows every sign of persisting indefinitely. The professions mentioned above all have



"Common sense should have dictated that the EMC problem be resolved in a different way..."

self-regulation in their chosen field of operations. If it were suggested that the heavy hand of the law were applied to them – as it has been proposed often enough – there would be political uproar.

Even in the absence of such an engineering body to protest against such severe legislation, common sense should have dictated that the EMC problem should have been resolved in a different way from this big-stick approach. In particular, small companies and individual engineers should have been provided with an easier route to conformity. In their case, a type of test similar to the MoT test for cars, at a flat rate, and at government approved laboratories would be sufficient.

Such tests could be limited to interference emission only and the tests for EMI susceptibility could be omitted. A case could be made that EMI susceptibility tests are unnecessary, except in some obvious applications such as in aviation, where they may well be critical. In other areas, tests are unnecessary because at lower technical levels, market forces can sort out susceptibility offenders in the usual way. For example, hi-fi amps that are susceptible to EMI are soon picked out by reviewers in the hi-fi press. With an active consumer press – for example magazines such as *Which?* – few products which do not work because of susceptibility to EMI can escape the glare of publicity.

We often hear the maxim that 'tall oaks from little acorns grow'. And we have all seen examples of that in the pc sector of the electronics industry very recently. It is obvious that no acorn will grow in an unfavourable climate, so why have the people who are in control of the industrial climate in Europe created such hostile conditions for small electrical/electronics firms? At the root of this problem is, I believe, the almost total lack of understanding of the electronics industry by our politicians. They are in the curious position of looking enviously at the immense revenues generated by the electronics-based high-tech, relatively unregulated and bureaucracy-free tiger economies of the Far East, most of which sprouted comparatively recently from small beginnings, while at the same time putting another nail in the coffin of their own local small businesses.

How else can such oppressive pieces of legislation be explained?

Rod Cooper

Electronics World is published monthly. By post, current issue £2.35, back issues (if available) £2.50. Orders, payments and general correspondence to **L333, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.** Tlx:892984 REED BP G. Cheques should be made payable to Reed Business Publishing Group **Newstrade:** Distributed by Marketforce (UK) Ltd, 247 Tottenham Court Road London W1P 0AU 0171 261-5108.

Subscriptions: Quadrant Subscription Services, Oakfield House Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address. Subscription rates 1 year £30 UK 2 years £48.00 3 years £70.00. Surface mail 1 year £35.00 2 years £56.00 3 years £80.00 Air mail Europe/Eu 1 year £43.00 2 years £68.00 ROW 1 year £52.00 2 years £83.00

Overseas advertising agents: France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel; (212) 679 8888 Fax; (212) 679 9455

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. 2nd class postage paid at Rahway NJ Postmaster. Send address changes to above.

Printed by BPCC Magazines (Carlisle) Ltd, Newtown Trading Estate Carlisle. Cumbria, CA2 7NR

Typeset by Wace Publication Imaging 2-4 Powerscrott Road, Sidcup, Kent DA1 4SDT.

© Reed Business Publishing Ltd 1996 ISSN 0959 8332

New memory technology holds more than one bit per cell

The first use of multi-level cell (MLC) technology – storing more than one bit on a memory cell – is likely to come in the form of a rom from NEC in the next few months. Early next year, SGS-Thomson expects to introduce a one-time programmable eeprom based on the technology and, by mid-1997, Intel expects to have an MLC-based flash memory.

“We are developing a 64Mbit mask rom using multi-level technology for a games cartridge,” Dr Hajime Sasaki, senior executive vice-president of NEC told *EW*, “the price target for a games cartridge is very tough; by using multi-level you can reduce the chip size. We already have

a prototype and we are discussing it with customers.” NEC’s MLC technology stores two bits of memory on one cell, which in the case of a rom is made up of a single transistor.

SGS’ implementation of MLC technology also uses two bits per cell. “A test vehicle has been made at Bologna University and the first product, a multi-level one time programmable eeprom, will be laid out in Q4 this year”, said SGS’ Tony Watts. “First silicon is expected in Q1 1997.”

MLC technology has been pursued by the Big Three flash suppliers – Intel, AMD and Fujitsu – as a way of increasing density without reducing process geometries. Intel demon-

strated MLC-based flash at this year’s International Solid State Circuits Conference (ISSCC) and, according to Anne Hall of Intel, an MLC-based product will be introduced in the first half of next year. Samsung also demonstrated MLC at the ISSCC – a 128Mbit, two bit-per-cell, memory made on a 0.4 micron process.

Peter Heinrich at AMD said MLC was some years away for them. Asked if NEC was considering using multi-level technology for flash, Sasaki laughed, replying: “It’s difficult enough, for the moment, making ordinary flash.”

David Manners,
Electronics Weekly

BBC sends Ceefax via digital radio

A non-interactive Internet-style information service is being broadcast to radios in the UK. The BBC is transmitting Ceefax information in HTML format over its digital audio broadcast (DAB) network.

Glyn Jones, the BBC’s DAB project director, said: “We are calling the experimental transmissions BBC Digital Text, but will probably think up a snappier if we provide the service long term.”

The transmission illustrates two points. Jones said: “It shows that HTML, which is universally recognised and requires no expensive licensing, can be used with DAB. It also proved we can transfer data from the Ceefax data base fully automatically through to the

DAB multiplex, making broader use of our Ceefax information gathering capability.

Part of Jones’ brief is to explore the possibilities of DAB. “We have also tried transmitting live RDS-type data along with programmes. This kind of service might be used to provide the ‘story so far’ if you switched on the radio mid-way through a play,” continued Jones.

While the Ceefax information transmission is designed to be displayed on pcs linked to DAB receivers, at least one potential receiver manufacturer is thinking of incorporating a graphics display. Jones said: “DAB radios could display photographs and graphics along side station names and music titles.”

New guidelines clear CE confusion

Confusion that exists in the CE-marking of power supplies is being addressed with the issue of new guidelines for manufacturers.

The guidelines have been drawn up by a working party of the European Power Supply Manufacturers Association (EPSMA).

EPSMA Chairman Mr Jan Tipples said: “Our objective in drawing up these guidelines was to clear up the confusion surrounding the interpretation of the regulations as far as the power supply is concerned.”

The guidelines summarise the following: what a CE mark is; and how the low voltage and EMC directives apply to both stand alone and component supplies. The EPSMA represents 28 European manufacturers responsible for the sales of \$1.3bn worth of power supplies into the European market.

EMC checks down under

Our friends down under are soon to experience the joys of Euro-style EMC regulations, with a vengeance.

Based on the European EMC directive, the new Australian system will initially cover emissions only. New products must comply from 1 January 1997, older products from the start of 1999.

Even low-volume manufacturers, originally excluded from the regulations, will now have to comply.

Unlike in Europe, where the issue of enforcement is yet to be fully resolved, compliance documentation in Australia will be audited on a random basis.

The Australians’ no-nonsense approach is typified by its Spectrum Management Agency, overseer of complaints of interference, which has said it will investigate any bona fide complaints received.



A motorcycle simulator system from Virtuality is the first product to be EMC pre-compliance tested using Chloride Powerline’s free service. Dr Paul Sheppard, Virtuality’s senior engineering manager, said: “Powerline’s free service was very useful as it allowed us to ensure that the simulator hardware would pass its formal EMC compliance at an approved laboratory.” The simulator allows learner riders to experience dangerous situations without the worry of crashing a real bike.

'Independence Day' for MPEG-4 standard

The latest multimedia hardware standard, known as MPEG-4, moved a step closer to commercial products with new component standards agreed at a meeting in Finland last month.

MPEG-4 is being developed to enable the efficient communication of, and interaction with, audio and video objects.

Paul Fellows, a project manager at SGS-Thomson involved in MPEG4

development work, said: "The encoding and decoding of various shaped video objects has already been demonstrated in MPEG-4. Now it's just a case of refining the techniques used."

According to Fellows, the standard is still on course for ratification in November 1998.

The scope of the new standard means that whereas MPEG-2 was concerned with the delivery of TV to enable more channels or reduce cost, MPEG-4 reflects the advent of multiple, separate audio and video 'objects'.

Fellows cited 'virtual' TV studios and films such as 'Independence Day' as examples of what is being done at present with composited objects. The current MPEG-4 work includes the

development of verification models (VMs) for video, audio and the systems and description language. Currently over 150 contributions to the video VM are being evaluated.

The audio group is investigating an audio standard which is non-backward compatible to MPEG-2's audio standard. It uses multiple channels and offers comparable quality at a lesser bit rate. Meanwhile, the systems group is working on the definition of how the various objects are to be multiplexed into a single bit-stream. The group is also defining the various Application Program Interfaces (APIs) for the various decoding and composition tools.

JPEG 2000 proposed

JPEG 2000, a new still image compression standard, is being proposed by the Joint Photographic Expert Group (JPEG) and the Joint Bi-level Image Experts Group (JBIG).

The intention is to improve on the current JPEG standard in several areas, including low bit-rate and bi-level (text) encoding performance.

JPEG is said to introduce unacceptable subjective distortion of detailed grey-level images at low bit-rates (less than 0.25bpp). It is also optimised for natural images, and does not perform well on bi-level and computer generated images. This poor performance has precluded the widespread acceptance of JPEG for use on compound documents.

In addition, JPEG 2000 will offer both lossy and loss-less compression, and feature a single decompression architecture (JPEG has 44 decompression modes, many of which are application specific).

Moves are also afoot to provide the coding tool, or tools, for JPEG 2000 compression with an interface to those proposed for use in MPEG4 video encoding.

JPEG 2000 will remove JPEG's 64,000 by 64,000 pixel limitation without tiling.

Ambulances to test linear radio

The National Health Service (NHS) is to test a new 5kHz narrow band, linear modulation, radio system for its ambulances, to replace an existing fm system before the introduction of Tetra digital systems.

The system, based on products from Securicor Linear Modulation, will replace its traditional 2.5kHz fm system in a trial in Kent.

John Burnside, chief executive of Kent Ambulance, said: "We are faced with a pressing need to replace our current radio system. In the period prior to Tetra digital systems coming on-stream, LM is claimed to offer a number of potentially useful advantages in both spectral efficiency and data transmission."

Richard Percy, a spokesman for Securicor, said: "The linear modulation technique was developed at the Bath University. It uses dsp for modulation and demodulation, relying on an 'invisible tone' introduced by the transmitter to act as a reference for the receiver." Securicor has licensed the technology through the British Technology Group.

Data relies on a variable rate modem at up to 9.6Kbit/s. Dependent on the outcome of the trial, LM may be allowed to go forward as a technology option for ambulance trusts currently procuring radio services under the government's Private Finance Initiative.

Anti-terrorism ID chip from Micron

In an effort to combat terrorism, Micron Technology has introduced a new chip designed to be used as an identification device on shipping containers or luggage. Dubbed MicroStamp, the postage stamp sized chip, includes radio telemetry, processing and memory functions. The emitted signal can be detected within a range of three metres by an electronic scanner. Along with replacing bar codes, the company believes that the chip can be used to help combat terrorism through its ability track packages throughout their journey. Sources state that Micron has been awarded a research contract by the Federal Aviation Administration involving the use of MicroStamp in the development of a luggage security system.

Drop in pay rises

Pay rises are at an 18 month low in the engineering industry according to the Engineering Employers' Federation (EEF).

The EEF's July Pay Bulletin analysed 449 company's settlements, with a June average of 3.11%.

Pay settlements are continuing to fall, with 85% of rises at 4% or less and 44% of companies offering 3% or less.

New FPGA aimed at designers

A new field programmable gate array (fpga) synthesis tool from Exemplar Logic aims to convince designers to move from schematic capture to VHDL design entry. Dubbed VHDL Discovery, the new tool is a simplified version of the company's Galileo software. Priced at \$4,000, the software can be updated to either Galileo or Leonardo, adding simulation, timing verification other features.

Euro trial for CDMA

Cellular mobile operator T-Mobil of Germany is to run trials of a CDMA (code division multiple access) system from Motorola - one of the first in Europe.

The 800MHz system from Motorola's European Cellular Infrastructure Division has a planned start for a technical field trial of the fourth quarter this year.

Motorola believes the trials will show that CDMA can offer competitive advantages and open up new markets worldwide.

CDMA is said to offer higher capacity and better sound quality while using less power than competing systems. However, hardware is still in the development phase.

The current European cellular system, GSM, based on TDMA (time division multiple access), is two-thirds the cost of CDMA in terms of chip content. Even though prices will reduce, the imbalance is expected to remain for some time.

HART AUDIO KITS - YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

Hart Audio Kits and factory assembled units use the unique combination of circuit designs by the renowned John Linsley Hood, the very best audiophile components, and our own engineering expertise, to give you unbeatable performance and unbelievable value for money. We have always led the field for easy home construction to professional standards, even in the sixties we were using easily assembled printed circuits when Heathkit in America were still using tagboards! Many years of experience and innovation, going back to the early Dinsdale and Bailey classics gives us incomparable design background in the needs of the home constructor. This simply means that building a Hart kit is a real pleasure, resulting in a piece of equipment that not only saves you money but you will be proud to own. Why not buy the reprints and construction manual for the kit you are interested in to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase.

K1100 AUDIO DESIGN 80 WATT POWER AMPLIFIER.



This fantastic John Linsley Hood designed amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hi-fi system. This kit is your way to get UK performance at bargain basement prices. Unique design features such as fully FET stabilised power supplies give this amplifier World Class performance with startling clarity and transparency of sound, allied to the famous HART quality of components and ease of construction.

Useful options are a stereo LED power meter and a versatile passive front end giving switched inputs, with ALPS precision Blue Velvet low-noise volume and balance controls. Construction is very simple and enjoyable with all the difficult work done for you, even the wiring is pre-terminated, ready for instant use! All versions are available with Standard components or specially selected Super Audiophile components at £29.50 extra per channel, plus £2.40 if you want to include Gold Plated speaker terminals.

K1100B Complete STANDARD Amplifier Kit.....	£395.21
A1100B Factory Assembled.....	£499.21
K1100SC Complete SLAVE Amplifier Kit.....	£333.62
A1100SC Factory Assembled.....	£422.62
K1100M Complete MONOBLOC Amplifier Kit.....	£261.20
A1100M Factory Assembled.....	£329.20
RLH11 Reprints of latest Amplifier articles.....	£1.80
K1100CM Construction Manual with full parts lists.....	£5.50

"CHIARA" SINGLE ENDED CLASS "A" HEADPHONE AMPLIFIER.



This unit provides a high quality headphone output for 'stand alone' use or to supplement those many power amplifiers that do not have a headphone facility. Easily installed with special link-through feature the unit draws its power from our new Andante Ultra High Quality linear toroidal supply. Housed in the neat, black finished, Hart minibox it features the wide frequency response, low-distortion and 'musicality' that one associates with designs from the renowned John Linsley Hood. Pre-terminated interconnecting leads and PCB mounted sockets prevent supply polarity reversal and on-board diagnostics provide visual indication of supply line integrity. Volume and balance controls are Alps "Blue Velvet" components. Very easily built, even by beginners, since all components fit directly on the single printed circuit board. The kit has very detailed instructions, and even comes with a complementary roll of Hart audiograde silver solder. It can also be supplied factory assembled and tested. Selling for less than the total cost of all the components, if they were bought separately, this unit represents incredible value for money and makes an attractive and harmonious addition to any hi-fi system.

K2100 Complete Kit.....	£109.50
K2100SA Series Audiophile version with selected audiophile components.....	£112.46
A2100SA Series Audiophile version, factory Assembled.....	£149.46
K3565 "Andante" Power Supply Kit to suit "Chiara".....	£85.42
A3565 Power Supply, Factory Assembled.....	£128.42
CM2100 Construction Manual.....	£2.50
SPECIAL OFFER, Both units together, Kit Form.....	£184.92
Factory Assembled and Tested.....	£267.88

"Andante" SERIES 20VA AUDIOPHILE POWER SUPPLIES


Specially designed for exacting audio use requiring absolute minimum noise, low hum field and total freedom from mechanical noise this unit is a logical development from our highly successful 1550 series.

Utilising linear technology throughout for smoothness and musicality makes it the perfect partner for any module requiring fully stabilised ±15v supplies.

Two versions are available. K3550 has 2 ±15v supplies and a single 15v for relays etc. and can be used with our K1400 preamp and our K1450 RIAA pickup preamp, as well as other useful modules soon to be introduced. The K3565 is identical in appearance but only has the ±15v lighter current supply for use with the K1450 RIAA pickup pre amplifier or "Chiara" headphone amplifier.

K3550 Full Supply with all outputs.....	£93.75
K3565 Power Supply for K1450 & K2100.....	£85.42

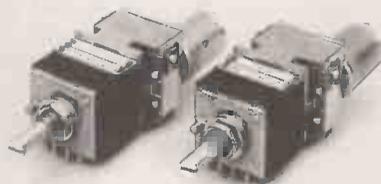ALPS "Blue Velvet" PRECISION AUDIO CONTROLS.



Now you can throw out those noisy ill-matched carbon pots and replace with the famous Hart exclusive ALPS 'Blue Velvet' range components only used selectively in the very top flight of World class amplifiers. The improvement in track accuracy and matching really is incredible giving better tonal balance between channels and rock solid image stability. Motosed versions have 5v DC motor.

MANUAL POTENTIOMETERS	
2-Gang 100K Lin.....	£15.67
2-Gang 10K, 50K or 100K Log.....	£18.40
2-Gang 10K Special Balance, zero crosstalk and zero centre loss.....	£17.48
MOTORISED POTENTIOMETERS	
2-Gang 20K Log Volume Control.....	£26.20
2-Gang 10K RD Special Balance, zero crosstalk and less than 10% loss in centre position.....	£26.98

JOHN LINSLEY HOOD SINGLE ENDED CLASS 'A' POWER AMPLIFIER

This amplifier represents an extremely novel concept in that it has been developed from a design in an earlier part of the evolutionary cycle, to meet the needs of modern users who want the warmth and purity of sound given by valve amplifiers from the vintage years, without the problems of cost, deterioration and danger associated with trying to use valves today.

It employs the newly re-discovered single-ended circuit configuration to give total freedom from crossover artifacts and to give a sound that is indistinguishable from the famous 'Williamson' design, the undisputed leader of the field, with its triode connected KT66s and all-triode drivers.

The new circuit, described in the September 1996 issue of Electronics and Wireless World, the same magazine that published the Williamson design back in 1947, is itself a development of an earlier 10watt design by the Author. The new version retains the basic simplicity and purity of the original but with modern components and an increased power rating of 15W RMS per channel.

Hart have developed a completely new and highly sophisticated kit, incorporating all the important options, within a very high quality 3U high 19" rack mountable case.

Please ask for your free copy of our list which gives full details.

Our List of these and many other Kits & Components is FREE IN UK. Ask for your copy now. Overseas customers are very welcome, but PLEASE send 2 IRCs if you want a list sent surface post, or 5 for Airmail.

Ordering is easy. Simply write, telephone or fax your order anytime. Let us know what you require, with your name address, cheque or credit card number and expiry date. Your daytime phone number is useful in case we need to get back to you. Further information on all our kits is given in our FREE lists. Overseas/trade orders are welcome and we can send anywhere in the World. Post on UK Orders up to £25 is £1.50, over £25 - £4.50. Express Courier £10. OVERSEAS postage - please enquire.

VALVE & EARLY CLASSIC BOOKS

THE VTL BOOK David Manley BKT1.....	£17.95
LOUDSPEAKERS; THE WHY AND HOW OF GOOD REPRODUCTION. G.Briggs. 1949 0-9624-1913-3.....	£8.95
MULLARD TUBE CIRCUITS FOR AUDIO AMPLIFIERS BKAA27.....	£13.95
"THE WILLIAMSON AMPLIFIER" 0-9624-1918-4.....	£6.95
AN APPROACH TO AUDIO FREQUENCY AMPLIFIER DESIGN, GEC 1957, 1-882580-05-2.....	£18.95
AUDIO ANTHOLOGIES, articles from Audio Engineering Six volumes covering the days when audio was young and valves were king! BKAA3/1 to 6. All.....	£13.95 each.
"A SIMPLE CLASS A AMPLIFIER" J.L.Linsley Hood M.I.E.E. 1969, RLH12.....	£2.50
Postage on all books, unless stated, is only 0.150 per book, maximum 0.450 for any number, any size! Starred items are heavy books costing.....	£2.50 to send.
No waiting! All listed books are normally in stock!	
SPECIAL OFFER. All book orders over £15 will receive a FREE John Linsley Hood monograph entitled "Digital versus Analogue, Black Disks or Silver?"	

SPECIAL OFFER PRECISION Triple Purpose TEST CASSETTE TC1D.

Are you sure your tape recorder is set up to give its best? Our latest triple purpose test cassette checks the three most important tape parameters without test equipment. Ideal when fitting new heads. A professional quality, digitally mastered test tape at a price anyone can afford. Test Cassette TC1D. Our price only..... £9.99.



HC80 Replacement Stereo Cassette Head.

The excellent performance of modern cassette recorders depends totally on the quality of the R/P head. Even the slightest amount of wear can impair the frequency response and distortion levels. Our HC80 is atop quality head from one of the foremost manufacturers in Japan, easily fitted to most standard stereo recorders (except Sony) and will transform the performance over a worn head. Only the fact that we buy these in vast quantities enables us to offer them at the amazing price of only £11.70 each or 2 for £17.60.

We also stock a range of other heads, including "reel-to-reel stereo heads.

SOLDERING

The size of modern components makes the right soldering equipment essential for good results. Everything we offer we actually use in our own workshops! See our Lists for the full range. 845-820 XS240 ANTEX 240v 25w Soldering Iron. This is the ideal Multi-purpose iron as the bit is designed to totally surround the element giving the best heat transfer. This excellent design also means that although it is small and handy enough for modern components its heating capacity is better than larger irons of conventional construction. Excellent Value..... £12.43

845-080 ST4 Lightweight Soldering Iron Stand. This has provision for the classic damp sponge for bit wiping..... £3.95

HART SUPER AUDIOGRADE SILVER SOLDER.

Hart Super Audiograde Silver Solder has been specially formulated for the serious audiophile. Not only does it give beautiful easy-to-make joints but it is designed to melt at normal soldering temperatures avoiding the possibility of thermal damage to components or the need for special high temperature irons. A very low residue flux makes perfect joints easy but eliminates the need for board cleaning after assembly.

845-007 3mtrs 22SWG in Hart Mini Tube.....	£3.90
845-008 100g. Reel Special Valve Grade, 20swg.....	£12.90
845-009 100g. Precision PCB Grade, 22swg.....	£14.75
845-110 100g Reel Superfine 24swg for ultra precise control and easy working.....	£21.45

QUALITY AUDIO KITS

24 hr. Orderline 01691 652894
Faxline 01691 662864

ALL PRICES INCLUDE UK/EC VAT

CIRCLE NO. 107 ON REPLY CARD

RESEARCH NOTES

Jonathan Campbell

Gel helps take the pressure off snorers

Development of a new optical fibre transducer could mean good news for serious snorers. Researchers at Leicester University who have designed the probe hope that the transducer will be used to provide valuable feedback on the pressure profile in the upper airways. The fibre transducer is able to measure pressure at various sites in the airway simultaneously. It could indicate if the snoring is a result of the potentially serious obstructive sleep apnoea syndrome, osas.


Many of us snore at one time or another, with little harmful effect – except to the sanity of our partners. But for some, the snoring is a result of the involuntary occlusion of the airway that occurs in osas, where breathing stops for ten or more seconds. Periodic hypoxaemia and sleep fragmentation are the result.

The problem for doctors is that the condition is only apparent when we are asleep, when our muscles – including those of the upper airway – relax. During respiration, the ensuing

negative gauge pressure causes the airway to collapse. Then the patient awakens momentarily, tone returns to the muscles and the obstruction is overcome. The airway may be collapsing at the palate, behind the tongue or at both sides. Unfortunately, successful treatment demands that the site of the obstruction must be identified reliably.

This has been the impetus behind the work of Paul Goodyear and colleagues who have developed a seven transducer system within a single 3mm diameter catheter, allowing measurements to be taken at selected points along the airway (“The design of an optical fibre pressure transducer for use in the upper airways,” IEE Transaction of Biomedical Engineering, Vol 43, No 6, pp. 601-606).

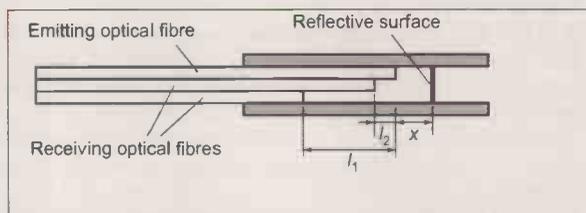Each transducer is less than 1mm in diameter, and consists of one emitting and two receiving fibres. The second receiving fibre sits in a slightly different location and at a different distance from the transduction element,



so that when the transducer is bent on its progress through the airway, the second fibre will be available as a reference to determine signal loss.

But the real breakthrough in the design of the miniature transducer has been in development of a replacement of the normal rigid diaphragm which would be too brittle at these diameters. Here the team has used a gel coated with reflective titanium dioxide. In response to pressure changes, the meniscus deforms and modulates the intensity of light reflected back into the optical fibre system.

Contact Paul Goodyear at the Department of Engineering, University of Leicester, University Road, Leicester LE1 7RH or email at pdg@leicester.ac.uk

Three-fibre pressure transducer designed to overcome amplitude modulation problems caused by optical fibre micro-bending. The reflective surface is a coated silicone gel.

Darts in space: You're floating around with your other astro-buddies twiddling your thumbs and gently bumping around inside the confines of the multi-million rouble 'tin can' (© David Bowie) that is the Mir space station. "How about a nice game of darts?"

As unlikely as it might seem, darts is very much on the approved list of activities, as part of an experiment designed by engineers at MIT to produce a better understanding of how crew members physically affect their environment. The data could save millions in the design of future space structures like the scheduled international space station.

Currently there is very little data on the forces astronauts exert on spaceships, so engineers must over-design the racks housing sensitive experiments that could be disturbed by astronauts' movements.

As part of the experiment, the researchers will videotape crew members playing darts to study how they adapt to zero gravity. With the help of four cameras, scientists back on Earth will be able to trace out the entire arm motion to obtain three-dimensional data. The plan is to have the Mir travellers perform the experiment as soon as possible after they arrive on Mir, then at the middle and end of their time there, to show how they adapt to their new environment.

As part of the same study, data will also be collected on the forces applied as the crew uses specially instrumented footholds, a handhold, and a push-off pad to get around or anchor themselves.

Back in 1994, aboard the Space Shuttle Columbia, related experiments yielded the first data on the forces associated with astronauts' everyday activities, and showed that previous estimates of those forces were off by an order of magnitude. That study showed each astronaut had an average force value of 28N, while for the space-station models, 800N was being used for crew input, based on experiments in the 1970s with astronauts aboard Spacelab. Those studies, however, represented the 'extreme', with astronauts 'pushing off one wall and soaring to another wall as fast as they could',



Has anyone seen my dart? MIT have put game into space to see how space travellers aboard the Mir space station react to weightlessness.

according to MIT.

But as anyone who has ever tottered up to the ockey in their local on a Friday night with a beer in one hand and a dart in the other will know, such behaviour is anything but extreme.

Gyroscopes that could put Einstein in a spin

Gyroscopes built to provide a reference system a million times better than the best inertial navigation gyroscopes currently available are at the heart of a space mission to be launched in year 2000 that could lead to a rethink of our understanding of time and space. Researchers at Stanford University are working with scientists at NASA on the project which some physicists believe could lead to a possible rewriting of Einstein's General Theory of Relativity.

The gyroscopes, part of the gravity probe B project, are designed to be so free from disturbance that they can provide an almost perfect space-time reference system. As such, scientists hope they will be able to measure how space and time are warped by the presence of the Earth, and how the Earth's rotation drags space-time around with it.


Calculations suggest that a gyroscope in polar orbit at 400 miles should turn with the Earth through an angle amounting after one year to 42 milliarc-seconds. Up to now this vitally important frame-dragging effect has never been seen. But gravity probe B should be able to measure it to a precision of 1% or better.

A second, much larger change in spin direction is the geodetic effect, following from the gyroscope's motion through the space-time curvature. For a gyroscope, the predicted effect is a rotation in the orbit-plane of 6600 milliarc-seconds per year – quite a large angle by relativistic standards. Gravity probe B will measure the change to 1 part in 10,000 or better, the most precise qualitative check yet of any effect predicted by general relativity.

The Stanford team explains that the experiment itself will comprise four gyroscopes and a reference telescope sighted on Rigel, a binary star in Orion. In polar orbit, with the gyro spin directions also pointing toward Rigel, the frame-dragging and geodetic effects come out at right angles, each gyroscope measuring both.

To be able to make the measurement, the gyroscopes must provide a reference system stable to 10-11°/hour. Fortunately, two factors – space and near zero temperature – help to make the problem slightly less impossible.

Electrically suspended gyroscopes have long been among the best inertial navigation instruments but ordinarily their performance is limited by support forces. Space, enhanced by 'drag-free control', allows the support to be reduced almost to nothing. Low temperature operation greatly improves the mechanical stability of the instrument; and it also brings means of shielding the gyroscopes against non-

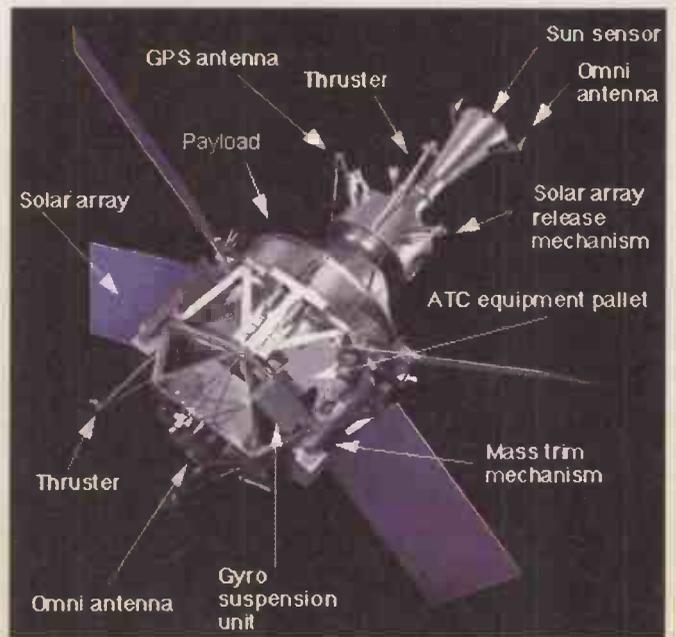

Gyroscopes aboard the Gravity probe B mission could answer a lot of questions posed by Einstein's theories on gravity as a field.

gravitational disturbances and of reading their directions of spin.

The complete Gravity Probe B instrument is made of a core of fused quartz 530mm long, bonded to a quartz telescope and containing the four gyroscopes plus the drag-free proof mass.

The gravity probe B Mission is planned for launch aboard a Delta II rocket from Vandenberg Air Force Base in October 2000.

● *Information on the gravity probe-B mission, a great deal of interesting background on relativity and Einstein, can be found on the Internet World Wide Web at <http://stugyro.stanford.edu/RELATIVITY/GPB/GPB.html>*

Weeds get the robot treatment

How do you tell a plant from a weed? It's sometimes difficult for the ordinary person (and impossible for the Research Notes office gardener). So how do you lay down the rules to enable a robot to make that distinction? R Brivot and J A Marchant at the Silsoe Research Institute think they have found the answer, and hope they have the basis of a robot that can move along lines of plants, selectively picking out the weeds to spray them with chemicals.

Motivation for the work is the huge amount of chemicals currently used in crop protection programmes, and pressure from consumers and environmentalists to make reductions. Using a robot sprayer to put the chemicals only and precisely where they are needed could help achieve that goal.

But first the robot has to be able to

see the difference between the weed and plant. Brivot and Marchant have developed an infrared-based system that, under the right conditions, is showing good results ("Segmentation of plants and weed for a precision crop protection robot using infrared images", R Brivot and J A Marchant, IEE Proc – Vis Image Signal Process, Vol 143, No 2, pp. 118-124).

The system relies on a high resolution sensor in the form of a ccd camera, permitting the use of grey-level distribution of the infrared images as well as texture information. The camera is fitted with a near-infra-red filter and is linked to a data acquisition system which stores 256 x 256 pixel image sequences.

Key to successful discrimination is the strength of the algorithms used to process the images and these are based on a number of hypotheses – for

example plants are defined by single blobs which do not touch each other. Most of the time the grey level distribution is sufficient for discriminating plants and weeds (and certainly good enough for discriminating plants and soil). But where it isn't, texture information can be used, because the grey-level surface of the plants is more constant than the weeds and the plants appear brighter than their centres.

Results so far show a 92% correct classification with "good" images and up to 72% with "bad" images. The processing can be carried out in real-time too as most of the algorithms do not need a knowledge of the whole image so multiprocessors can be used.

Unfortunately, there is some way to go yet before a robot can be built to keep the Research Notes garden free of weeds – and in that case it would need

to be fitted with a flame thrower rather than a chemical spray. For instance, the Silsoe study was carried out on the specific problem of tending cauliflowers transplanted from greenhouses into lines in a weed-free bed. The plants are nearly always bigger than the weeds, but the situation does reflect commercial practice. The work was also carried out in diffuse lighting conditions rather than direct sunlight. Even so, with 23,000 tonnes of chemicals used for treating crops last year, the incentives for continuing with the work are high.

More information from *Biotechnology and Biological Sciences Research Council, Silso Research Institute, Wrest Park, Silsoe, Bedford MK45 4HS, UK.*

Rocket engine shows promise

Tests on the prototype of NASA's xenon ion engine, which fires electrically-charged atoms from its thruster, are reportedly progressing well at the Jet Propulsion Laboratory, Pasadena, California. Once validated by the test, a similar engine will power the first New Millennium mission, called Deep Space-1, to an asteroid and a comet in 1998. The comet will be West-Kohoutek-Ikemura and the asteroid will be McAuliffe, named after the school teacher Christa McAuliffe who died in the Challenger accident.

In space, the 300mm diameter engine will use xenon gas as fuel and be powered by more than 2000 watts from large solar arrays provided by the Ballistic Missile Defence Organisation. The actual thrust comes from accelerating and expelling the positively-charged ions. The thrusting action is similar to that of chemical propellant engines which expel burning gases, except that such engines can produce up to millions of pounds of thrust.

The roaring engines in rockets that lift the Space Shuttle quickly lift the Shuttle to more than 17,000 mile/h. An ion engine, however, starts with only about 20-thousandths of a pound of thrust and there is no roar, just an eerie blue glow. While the atoms, charged by an electric arc which removes one of the 54 electrons around its nucleus, are fired in great numbers out the thruster at more than 70,000 miles an hour, their accumulative mass is so low, the spacecraft moves only millimetres per second in its early stages of flight.

However the advantage of ion propulsion is that is more propellant-efficient than chemical propulsion because it expels molecules from the engine at a much higher speed.

DSP slows speech – and speeds understanding

It makes sense to speak a little more slowly to elderly people who are hard of hearing – particularly in the light of studies that have shown that temporal processing factors other than peripheral hearing loss can be involved.

Now Japanese researchers have used recent improvements in digital-signal processing technology, dsp, to design a portable speech converter that can be used by a listener to slow down speech in real time conversation – without affecting pitch.

A user simply operates the device by pressing a button, to cause speech signals to be recorded into memory while previously-recorded signals are being slowed and generated. A 16Mb random-access memory allows two to three minutes of speech to be recorded at once, which should be enough for normal conversation.

To keep the size of the device small and reduce the complexity of dsp operation, a simplified pitch-synchronous time-scaling algorithm has been developed. Time scaling expands only the duration of those signals above a certain power level and does not change the duration of signals below that level – such as consonants. This dynamic processing feature helps minimise extra distortion in the output device.

The device's hardware, which has been squeezed into a unit that fits in the hand, consists of a 33Mflops 32bit dsp, the 16Mb memory and 14bit 13.3kHz analogue-digital interface circuits specially designed for the dsp. The dsp program itself is stored in a 256K eeprom.

Initial results (A portable digital speech-rate converter for hearing impairment," Yoshito Nejime et al, IEEE Transactions on Rehabilitation Engineering, Vol 4, No 2, pp. 73-83) showed improved understanding by seven out of ten elderly subjects who had hearing difficulties and were allowed to use the device.

The researchers say the results suggest that speech-rate conversion can be used to overcome the deterioration of peripheral ability by helping auditory memory processing. In this it may have a function complementary to that of conventional hearing aids and could be used in conjunction with them.


A smaller version of the device, with lower power consumption and using a low-voltage risc chip is currently under development.

Contact J Nejime at the Central Research Laboratory, Hitachi Ltd, Kokubunji, Tokyo 185, Japan or email at nejime@crl.hitachi.co.jp




Pressing a button on the speech rate selector allows speech to be slowed down so that it is easier to understand.

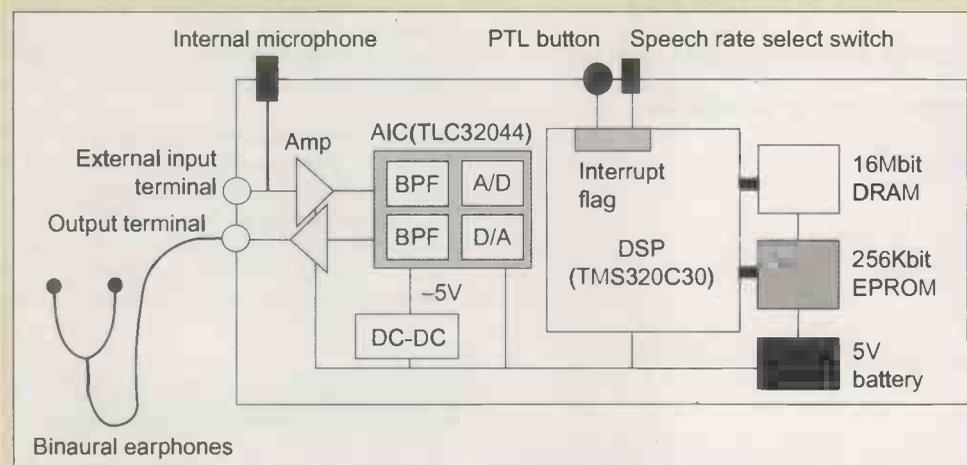16Mb dram gives enough storage to handle two-three minutes of speech which should enable listeners to get through a normal conversation.



Music in mind

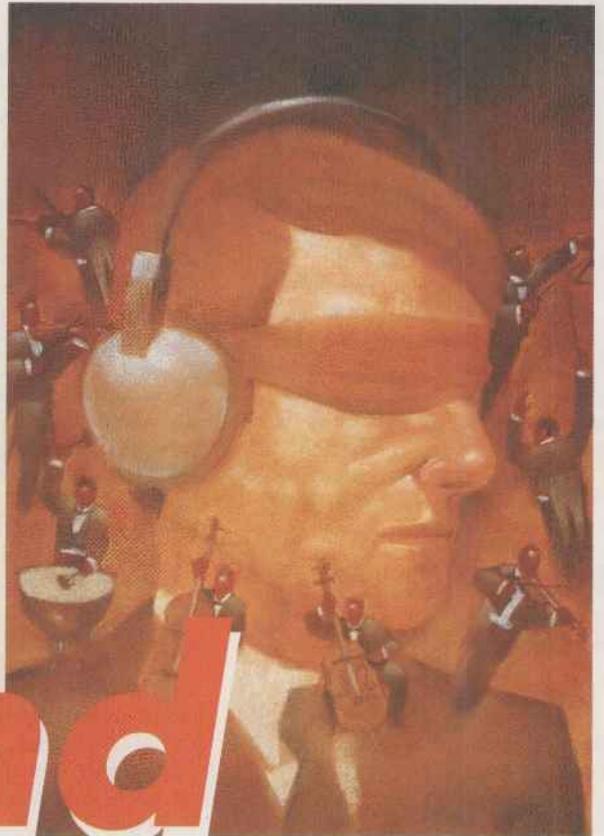

A problem with headphones is that when you move your head, the sound source moves with you. As an exercise in applying a low-cost gyroscope, Ian Hickman has designed a headphone rig that emulates a stationary sound source – but why does it only work in mono?

Listening to music through headphones has several advantages, perhaps the main being that you can have the volume as loud as you like without disturbing anyone else. But the main disadvantage is perhaps that the music sounds as though it is inside your head.

Many years ago, I was told by a colleague that this is because there is no differential change in the phase of the signals reaching the ears when the head is turned. Normally, there would be, this being the mechanism that allows you to determine which direction a sound is coming from.

I had long wanted to check out whether adding delays to the signals to the left and right earpieces – delays which varied whenever the head was turned – could 'externalise' the sound. But the opportunity to do so had not arisen. Doubtless the experiment has been performed before, but that is no reason for not trying it oneself. Besides, implementing such a concept presents some very interesting design problems.

Recently I saw an advertisement for a miniature all solid-state gyroscope. Here surely was a solution in search of a problem. One of the uses envisaged by the manufacturer is automobile navigation systems. Clearly there are many others – among them the aforementioned psychoacoustic experiment. The gyro-

scope could be used to sense rotation of the head, and this signal used to adjust the delays in the left and right channels.

Gyroscope details

The piezo-vibrating gyroscope uses a triangular prism of Elinvar metal, to which are attached piezo-electric transducers. These transducers are maintained in a flexural mode oscillation by an oscillator operating at the assembly's resonant frequency, **Fig. 1a**). Vibration is maintained by a set of three electrodes, **Fig. 1b**), two of which are also used as sensors. When the unit is rotated about the longitudinal axis of the prism, an additional component of force is applied to the piezo-electric material, **Fig. 1c**). This results in a differential component in the voltage at the two detection electrodes as in **Fig. 1d**). The differential component is picked off and synchronously detected, filtered and smoothed, providing a voltage proportional to the rate of change of direction.

Figure 2 shows an application circuit from the manufacturer's data sheet for the device. Note that the signal output is ac coupled. This is to allow for a possible standing offset between the signal output and the reference voltage to which it relates – in particular for temperature variation of this offset. There is

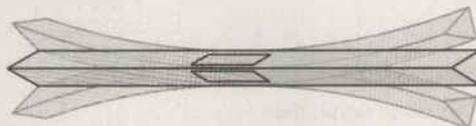


Fig. 1a) Murata's piezoelectric vibrating gyroscope uses a triangular prism, maintained in a flexure-mode vibration.

also a temperature coefficient of the nominal $1.11\text{mV}/^\circ\text{s}$ scale factor.

In an automotive navigation system, it is assumed that the vehicle will return to a straight-line course after each turn before the high-pass filter introduces too much signal loss. If you were to drive round and round a roundabout however, the system might presumably lose track of the vehicle's direction. Since the device produces a signal output relative to the reference, which indicates the rate of turn, this signal must be integrated to obtain an output giving the actual direction of travel.

It is however possible to engineer a 3dB corner frequency much lower than the 0.3Hz, Fig. 2, avoiding this problem while still blocking the much slower variations in output offset due to temperature variations.

Head-mounting gyroscope

For the purposes of the psychoacoustic experiment, I fixed the gyroscope to the headband of a pair of earphones, to detect head movements. The gyroscope was mounted on a small piece of 0.1in matrix copper strip board. A couple of metres of screened lead was used for the signal and earth connections, and two other wires, for the +5V supply to the unit and its reference output V_{ref} . Signal output was passed through an ac coupling with a time constant of 300s, giving a low-frequency cut-off of about 0.0005Hz.

Figure 3 shows the arrangement, in which the gyroscope output is applied via a low-pass filter to the input of a unity gain buffer stage A_1 . Designed to further suppress switching ripple in the signal output, the filter before the buffer comprises a 100k Ω resistor plus 10nF capacitor.

The 10M Ω resistor at the non-inverting input of A_1 is returned not to V_{ref} , but to a point at 97% of A_1 's output. This effectively

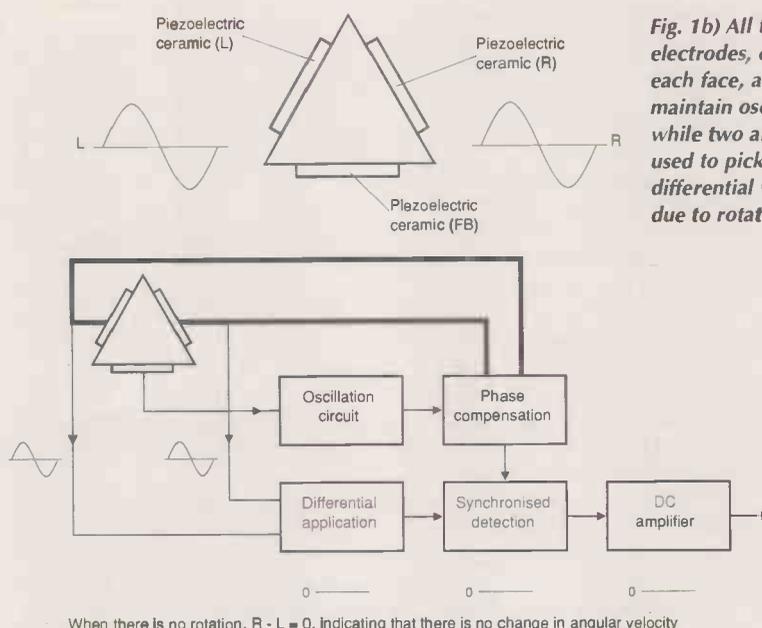


Fig. 1b) All three electrodes, one on each face, are used to maintain oscillation, while two are also used to pick off any differential voltage due to rotation.

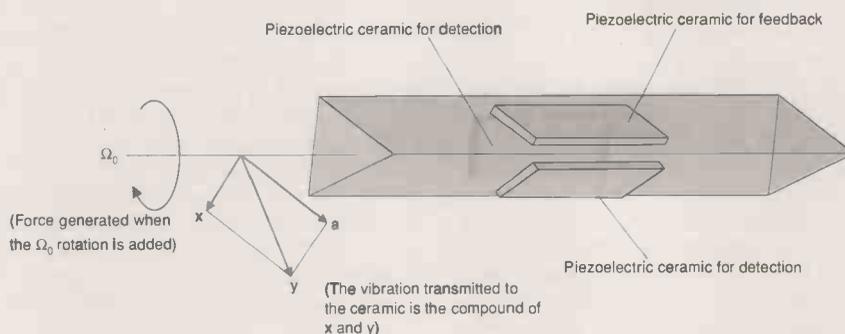


Fig. 1c) When rotation about the longitudinal axis occurs, force transmitted to the prism contains extra component 'a'.

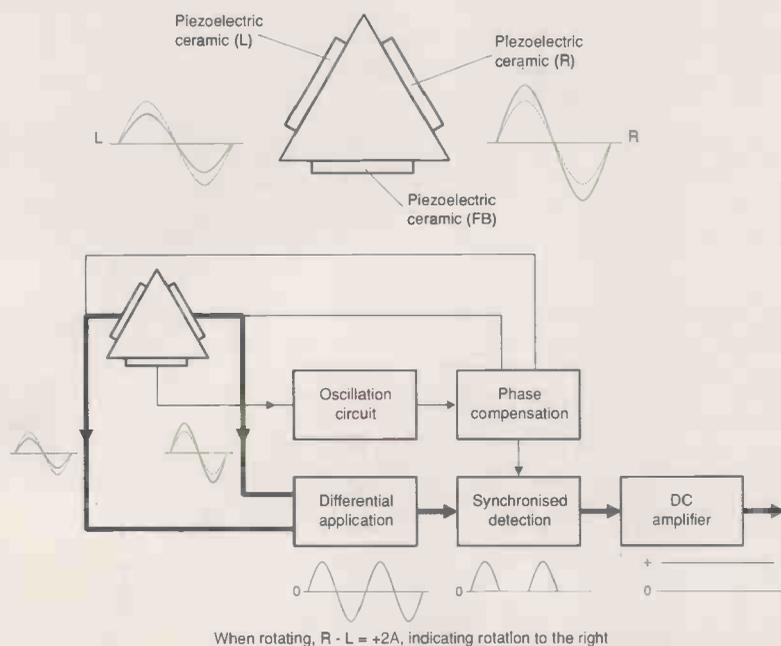


Fig. 1d) This results in a corresponding differential voltage between the detection electrodes, proportional to the rate of rotation.

multiplies its value by a factor of 30, giving in conjunction with the 1 μF capacitor, a time constant of 300s.

For A_{1-4} , I used a TLE2064 quad op-amp on account of its low bias current I_b of 3pA and offset current I_o of 1pA – both typical values, at 25°C. Buffered high and low-passed signal output, together with the reference output, are applied to A_2 . This op-amp is connected as a bridge amplifier providing rejection of the common-mode reference voltage. Its output is thus ground referenced, adequate common mode rejection being obtained due to the use of 1% metal film 100k Ω and 270k Ω resistors.

Op-amp A_2 provides a gain of $\times 2.7$. A further gain of $\times 10$ is raised in A_3 , at which stage an offset adjustment is introduced, to allow for offsets in A_1 and A_2 .

In practice, at switch-on, it was necessary to temporarily short the 10M Ω resistor at the non-inverting input of A_1 , to avoid a very long wait for the dc conditions to settle. On removing the short, there was still an offset due to I_b flowing in 10M Ω rather than a short circuit. So a 10M Ω resistor was included in the inverting input also, bypassed by a 330pF capacitor, to maintain stability.

A normally-open two-pole switch was used to short both 10MΩ resistors at switch-on, to allow for settling. Even so, drift of the output of A₁ was still experienced. I finally removed the 1μF capacitor and the resistors, and reconnected A₁ as a simple dc coupled unity gain buffer.

Offset between the signal and reference outputs of the gyroscope turned out to be only a few millivolts, and could thus be nulled with the offset adjustment at A₃'s input. As ambient temperature changes in a domestic environment are small and slow-acting, this proved acceptable for the purposes of this experiment.

To obtain the absolute rotary position of the headphones, the output of A₃ was integrated. But here there is a problem; integrators have an annoying but unavoidable habit of heading off, over the long term, to one or other of the supply rails. This is because in practice, the input voltage never remains exactly at zero.

The solution used was twofold. Firstly, when the listener's head is stationary, giving no output from the gyro and hence none from A₃, the 27kΩ resistor at the integrator's input is effectively disconnected by the two diodes.

Furthermore, to prevent the integrator from integrating its own input bias current, a 3GΩ resistor was connected across the 1μF integrating capacitor. Actually, a 10MΩ resistor was used, but since only one thirtieth of the integrator's output is applied to it, its effect is that of a 3GΩ resistor. This means that, in the absence of head movements, the 'sound stage' will over a period of many minutes, revert to straight ahead. This is where it should be of course, assuming that you will not want to spend long periods with your head cocked uncomfortably to one side or the other.


Note that considerable gain has been used ahead of the integrator. As a result, even comparatively small, slow movements of the head produce a large enough output from A₃ to turn on one or other diode. This effectively reconnects the 27kΩ resistor at the integrator's input.

Checking the delays

Output of the integrator, indicating the rotational position of a listener's head, was used to control the relative time delay of the sounds reaching the ears. To find out what this should be, some simple measurements and calculations were needed.

With the aid of a ruler and a mirror, I determined that my ears were about 14cm apart. Thus, when the head is turned through an angle of 45° to left or right, one ear moves to a position, in the fore-aft direction, 10cm ahead of the other. So each channel needs to be able to produce a delay equivalent to ±5cm, or, given the speed of sound is about 1100 feet per second, ±150μs, Fig. 4.

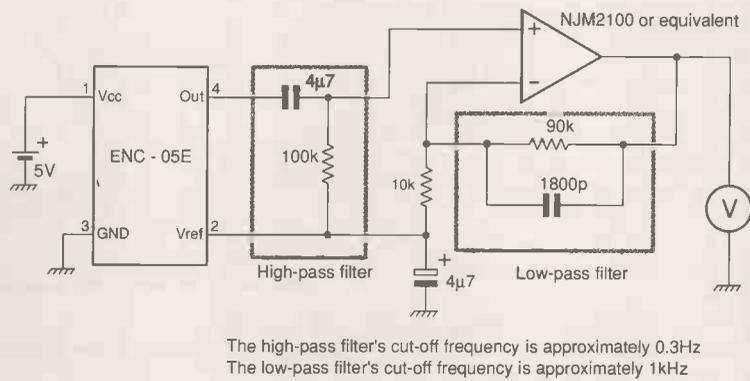Bucket-brigade devices were used to produce a delay in the signal to each earphone. The delay was varied by altering the clock frequency used to drive the bucket-brigade devices. The 1024 stage bucket-brigade chips used, namely Panasonic MN3207s, were each



The high-pass filter's cut-off frequency is approximately 0.3Hz
The low-pass filter's cut-off frequency is approximately 1kHz

Fig. 2. Sample amplifier circuit from the ENC-05EA1 solid state gyro data sheet. Note that the base diagram shown is confusing; V_{ref} is actually on the same side of the device as V_{cc}.

driven by a matching MN3102 cmos clock generator/driver. This generator contains a string of inverters which are usually used in conjunction with an external R and C, setting the clock frequency.

For this application, the R and C were omitted, and the first inverter driven by an externally generated clock. The two clock generator/drivers were driven by two voltage-controlled oscillators, or vcocs. These in turn were controlled by a long-tailed pair, driven from the output of the integrator in Fig. 3.

Initially, an elegant vco using an operational-transconductance amplifier and a TL08x op-amp was designed and tested. This had the advantage of providing a unity mark/space ratio independent of output frequency. However, I abandoned the transconductance amplifier as it would not run fast enough.

Drive to the clock generator/driver chips has to be at twice their clock output frequency. So a pair of simple vco circuits, using two sections of a CD4093 quad two-input schmitt NAND gates, were used, Fig. 5. These gates run at about 230kHz, providing a clock frequency of around 115kHz from the MN3102s for each bucket-brigade device.

The output waveform of the vcocs is distinctly asymmetrical, and varies with the long-tail pair control input. But the MN3102 device turns this into two antiphase non-overlapping clock waveforms with near unity mark/space ratios.

Differential delays

The long-tail pair provides differential control by subtracting a greater or lesser amount from the available charging current via the 27kΩ

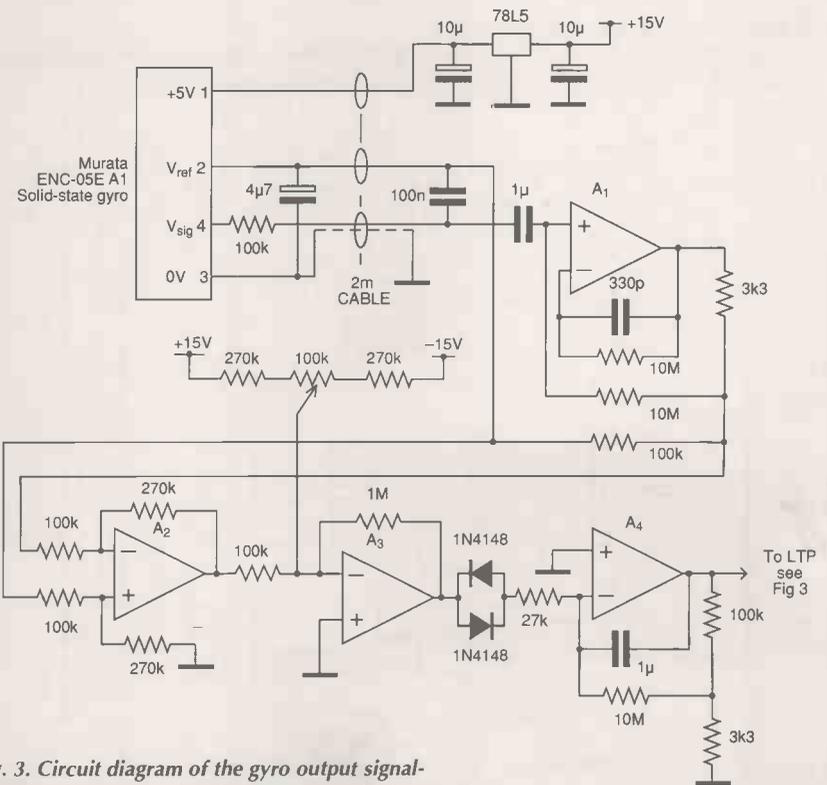


Fig. 3. Circuit diagram of the gyro output signal-conditioning stages, plus the integrator which turns the rate-of-rotation signal into an azimuth position signal.

Fig. 6a) The BBD audio delay stages, followed by three pole Chebyshev low pass filters to remove clock ripple from the output of the BBDs.

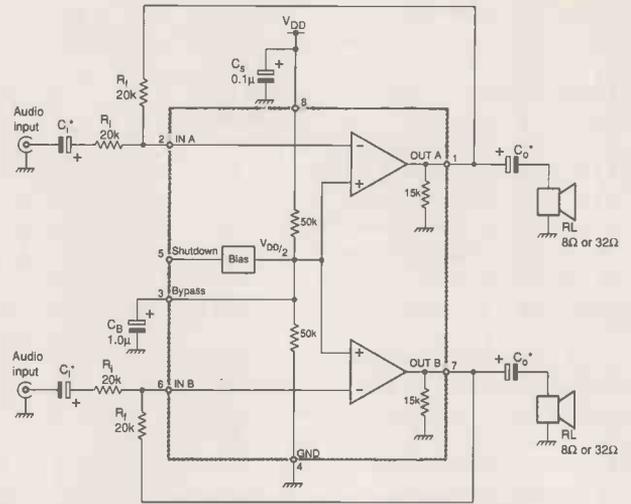
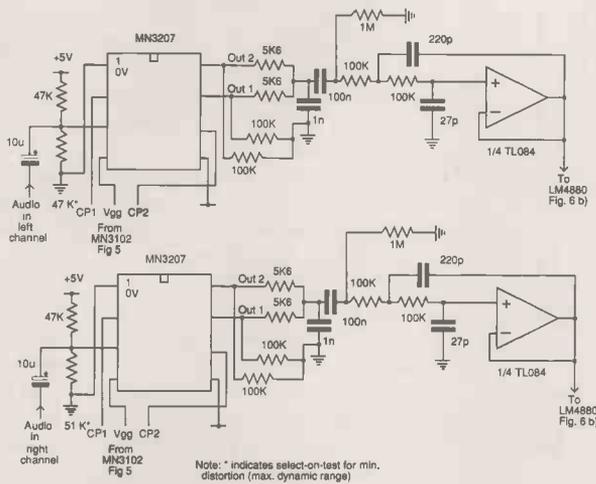


Fig. 6b) The audio output stage, using an LM4880 dual 250mW audio power amplifier with shutdown mode (not used in this application). Note, if the sound stage moves to the left instead of the right when the head is turned to the left, the audio connections between a) and b) should be interchanged.

which is near – or actually on – the speaker, stereo speech is usually virtually mono anyway.

Why no effect on stereo?

Disappointingly, results with an extended sound source, such as orchestral music in stereo, were not noticeably amenable to ‘exter-

nalisation’ by the gyroscope system. The sound stage remained doggedly stuck to the head, turning with it. The reason for this is not clear to me, so I hope that one of you is able to provide enlightenment.

Possibly the ear/brain system is so dominated by the abundance of positional information cues contained in a stereo signal, that it

cannot but hear the sound as coming from a sound stage fixed relative to the head. Whatever the explanation, the scheme is virtually ineffective on stereo material.


But that’s engineering for you; the results of an experiment are what they are, not what one might like them to be. Hypotheses have to fit the facts, not the other way round. ■

Solid-state gyroscope – 15% reader discount

Until 31 December, Willow Technologies is offering Murata’s ENC-05E solid-state gyroscope for the discount price of £70 instead of the normal price of £82, excluding VAT and delivery.

Measuring 21.5 by 8.5 by 7.6mm, the ENC-05E gyroscope handles up to 50 changes in direction a second and a maximum angular velocity of $\pm 90^\circ/s$. This velocity produces a swing of about $\pm 200mV$ dc about the zero angular velocity output reference of 2.3V dc. Requiring a maximum of 5mA, the ENC-05E is suitable for portable navigation systems.

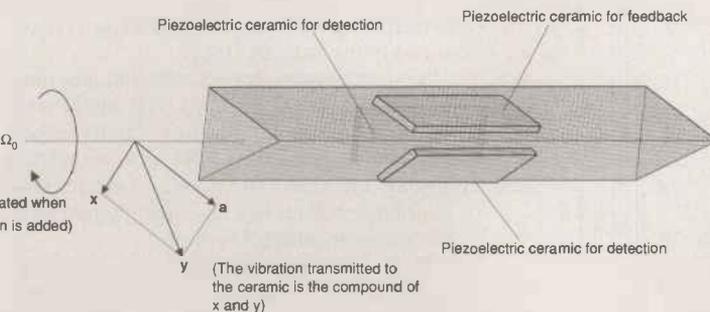Rotational sensing applications of the ENC-05E include camera stabilisation, model-aircraft control, virtual-reality headsets and robotics. Willow Technologies Ltd is at Shawlands Court, Newchapel Road, Lingfield, Surrey RH7 6BL, tel. 01342 835234, fax 01342 834306.



ENC-05E ORDER COUPON

PLEASE PRINT CLEARLY

Please send me ENC-05E gyroscope(s) at £70 each excluding VAT and £7.95 postage and packing, for which I enclose a total of £.....

Your name.....

Company (if applicable)

Address

.....

.....

.....Post code.....

Phone number.....Fax.....

Please make your cheque payable to Willow Technologies Ltd and send it to Willow at Shawlands Court, Newchapel Road, Lingfield, Surrey RH7 6BL, tel. 01342 835234, fax 01342 834306. Note that this offer is limited to five units per reader. Please allow 28 days for delivery.

Measuring 21.5 by 8.5 by 7.6mm, the ENC-05E gyroscope handles up to 50 changes in direction a second and a maximum angular velocity of $\pm 90^\circ/s$.



NEW programmers start at only £295




With prices starting as low as £295, ICE Technology's new range of parallel port programmers offers something for every budget. All programmers support dual in line devices directly in the socket - no adapters or modules are needed for any families of devices, providing extensive device coverage at very affordable prices. The full range of programmers is shown in the panel on the right. Our new easy to use device support checklist will help you to choose the programmer that is right for you, just call or use our faxback for a copy. All programmers come with FREE software updates on our BBS or our ftp site, full technical support direct from the manufacturer and one year's guarantee. All models can run from batteries or mains - ideal for use with laptops.

Low cost EPROM programmer

At only £295, the EPMaster LV is a powerful EPROM programmer which offers so much more than other EPROM programmers. With its 40 pin socket it can support all types of EPROMs including 16 bit wide with no need for additional modules. Serial PROMs, Serial EEPROMs, Flash and EEPROMs are all included in the device support at no extra cost. In addition, low voltage parts are fully supported with the programmer's separate 1.8V, 3.3V and 5V logic circuits. EPMaster LV connects to the parallel port of any PC compatible and can be operated from batteries or mains electricity. You can also add a built in ROM/RAM emulator with a capability of up to 512k by 16, turning the EPMaster LV into a powerful development tool.

CIRCLE NO. 151 ON REPLY CARD

High Speed Gang Programming

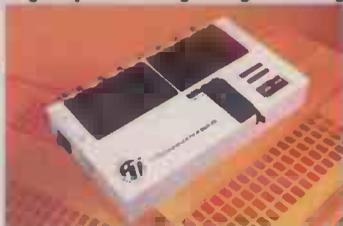

The Speedmaster GLV-32 Gang/Set programmer offers simultaneous high speed programming for up to 8 EPROMs and Flash (up to 8Mbit) at 3.3V and 5V. The 3.3V facility ensures that programmed devices will work correctly at their nominal operating voltage. Functions include gang programming, set programming and full editing. The Speedmaster GLV32 works in PC or stand alone mode.

CIRCLE NO. 152 ON REPLY CARD

Universal programmer only £525

The Speedmaster 1000+ and Micromaster 1000+ offer new levels of affordability in device programming. At only £395, the Speedmaster 1000+ supports all types of memory devices, plus 8748/51, BPROMs, GALs and erasable PALs. The Micromaster 1000+ at just £525 extends this support to include PALs, EPLDs, MACH, MAX, PSDs and over 180 microcontrollers including PIC,

ST6, MC68HC705, MC68HC711, TMS370, TMS320, 87Cxxx, 89Cxxx, COPs etc. The Micromaster 1000+ can support all device types, even Motorola micros, with NO ADAPTERS or MODULES for any dual in line devices up to and including 40 pins. As with all our programmers free software updates are included via BBS or our ftp site.


CIRCLE NO. 149 ON REPLY CARD



LV40 Portable

Reaching the parts other programmers can't reach

The NEW LV40 Portable stands head and shoulders above other portable programmers with its comprehensive device support which includes EPROMs, EEPROMs, Serial PROMs, BPROMs, Flash, NVRAMs, PSDs, PALs, GALs, PEELs, EPLDs, MACH, MAX and over 180 microcontrollers. Unlike other portables, no adapters or modules are needed for any of these devices up to 40 pins dual in line. With socket adapters the LV40 is capable of supporting devices of over 40 pins and other package types. At £995 for the complete package you'll soon see why the LV40 Portable is the best value, most powerful portable programmer in the world.

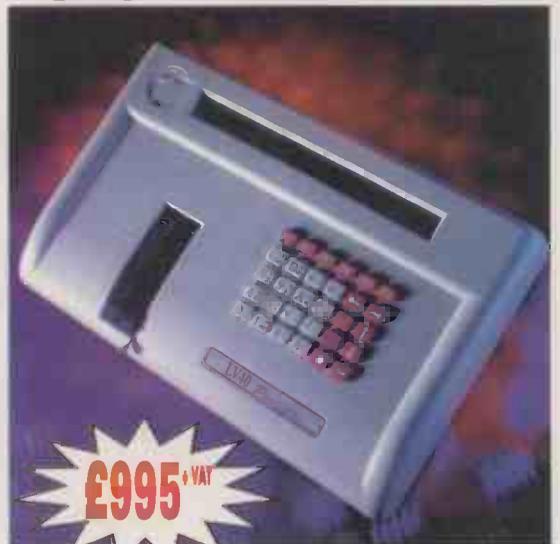

£995 + VAT

CIRCLE NO. 150 ON REPLY CARD

- Portable Universal Programmer
- High speed
- PC software included
- No modules to buy
- Supports memory, programmable logic, high density logic, and over 180 micros.
- Support for 1.8, 3.3 and 5V devices
- Battery or Mains operation
- Lifetime free updates

PROGRAMMER MODELS AND PRICES

LV MODELS (SUPPORT 1.8V, 3.3V and 5V DEVICES)		SPEEDMASTER 1000+	EPROMs, EEPROMs, Flash, NVRAMs, Serial PROMs, Serial EEPROMs, BPROMs, GALs, 8748/51	£395	
EPMASTER LV	EPROMs, EEPROMs, Flash, Serial PROMs, Serial EEPROMs 8 to 40 pins all without adapters. Built in emulator modules: 128k by 8: £395 128k by 16: £465	£295	MICROMASTER 1000+	EPROMs, EEPROMs, NVRAMs, Flash, Serial, BPROMs, PALs, GALs, PEELs, MACH, MAX, PSD, over 180 microcontrollers without adapters.	£525
SPEEDMASTER LV	EPROMs, EEPROMs, Flash, NVRAMs, Serial PROMs, Serial EEPROMs, BPROMs, GALs, PALs, EPLDs, MACH, MAX, 8748/51.	£495	SPEEDMASTER GLV32	High speed EPROM/Flash 8 way Gang/Set Programmer. Supports 3.3V and 5V	£645
MICROMASTER LV	EPROMs, EEPROMs, NVRAMs, Flash, Serial, BPROMs, PALs, GALs, PEELs, MACH, MAX, PSD, over 180 microcontrollers without adapters.	£625	COP GANG PROGRAMMER	8 way Gang programmer for National Semiconductor COP family of micros	£1500
LV40 PORTABLE	All devices supported by Micromaster LV, plus completely portable with built in keypad and LCD display.	£995	SOCKET ADAPTERS	for PLCC, TSOP, QFP, SOIC, SSOP etc.	from £65

All prices exclude VAT and delivery

For details on any of our range of programmers, call or fax us now.

You can obtain information immediately by using our faxback service or homepage.

ICE Technology Ltd, Penistone Court, Penistone, South Yorkshire S30 6HG. United Kingdom.

Tel: +44 (0)1226 767404 Fax: +44 (0)1226 370434 Faxback: +44 (0)1226 761844 email: sales@icetech.com

Homepage: <http://www.icetech.com> BBS: +44 (0)1226 761181 (14400 baud, 8N1)



CALL OUR SALES HOTLINE ON 01226 767404 - OR USE OUR FAXBACK FOR FULL DETAILS - 01226 761844

A-to-D via the COM port

Interfacing via the pc's COM port and accessible using simple Basic routines, David Gains' a-to-d converter can log up to four differential sensors with fast sampling.

My requirements were for a data acquisition system that would acquire analogue signals from transducers such as temperature sensing integrated circuits. The system had to use my PC's unused COM2 port, and it had to be capable of sampling a single channel at, say, 1-2kHz, or a few channels on demand at infrequent intervals. Further, to accommodate signals of different voltage levels, and to improve resolution, each channel had to have software programmable gain.

The resulting design, Fig. 1, provides the following features:

- four differential input channels,

- four gains of 1, 2, 4, and 8,
- single-conversion, or free-running conversion mode, and
- single-channel, or scanning channel mode.

All of the above features are software programmable. In addition, the capture module can be configured for either unipolar or bipolar input signals.

Serial interface

The MAX232 line driver-receiver, IC₁, provides the communications interface between the computer and the data acquisition system. Ostensibly, it converts signals between RS-232 compatible levels of ±12V and 5V ttl levels, but only requires a single 5V rail.

A single byte-long character command is passed to the CDP6402 universal asynchronous receiver-transmitter, IC₃. This uart takes the serial data from the receiver input RRI and converts it into a parallel word. Provided that this word has been received correctly, it then appears at the receiver buffer register output, RBR₁₋₈.

In my design, if a framing error or an overrun error occurs, it is ignored. In any case, if an error does occur, the RBR₁₋₈ outputs adopt a high impedance state. The RBR₁₋₈ outputs are then decoded to provide the functions shown in Table 1.

The uart is configured for a data format of eight data bits, and one stop bit, Table 2. In addition, there is no parity bit; the parity inhibit PI input is held high.

The serial data rate is set by programmable oscillator, IC₂, which is an EXO-19.6608. This device allows data rates of 4800baud up to 1228800baud. However, the MAX232 supports RS-232C standard, and this is only guar-

Table 1. Receiver output bits from the uart are used to configure the a-to-d conversion circuitry.

RBR ₈	RBR ₇	RBR ₆	RBR ₅	RBR _{4,3}	RBR _{2,1}
Unused	Unused	Conversion	Scan	Gain	Channel
x	x	0=single	0=off	0,0=x1	0,0=channel 1
x	x	1=running	1=on	0,1=x2	0,1=channel 2
x	x			1,0=x4	1,0=channel 3
x	x			1,1=x8	1,1=channel 4

Table 2. Three bits configure the uart serial data framing as follows.

CLS ₁	CLS ₂	SBS	Format bits	data	stop
0	0	0	5	1	
0	0	1	5	1.5	
1	0	0	6	1	
1	0	1	6	2	
0	1	0	7	1	
0	1	1	7	2	
1	1	0	8	1	
1	1	1	8	2	

Table 3. Programmable oscillator – applicable bit-rate settings.

Input	Frequency	Data rate		
S ₃	S ₂	S ₁	kHz	bps
1	1	1	76.8	4800
1	1	0	153.6	9600
1	0	1	307.2	19200

Listing 2. Object-oriented implementation of the functions used to interface to pc and a-to-d converter, in Turbo C++

```

// Standard libraries
#include <bios.h>
#include <conio.h>
#include <dos.h>
#include <process.h>
#include <stdio.h>

// Function key codes
#define F1 0x3B
#define F2 0x3C
#define F3 0x3D
#define F4 0x3E
#define F5 0x3F
#define F6 0x40
#define F7 0x41
#define F8 0x42
#define F9 0x43
#define F10 0x44

// COM port settings
#define COM2 1
#define DATA_READY 0x100
#define SETTINGS
(_COM_9600 | _COM_CHR8 | _COM_STOP1 | _COM_NOPARITY)

// Implementation of interface to unit. No error checking.
class serial {
private:
    unsigned _port; // Port identity
    unsigned _settings; // Port settings
    // Configuration
    unsigned _channel, _gain, _scan, _run;
    char str[40];
public:
    // Constructor - Configures serial port
    serial(unsigned p, unsigned s) : _port(p), _settings(s) {
        _bios_serialcom(_COM_INIT, _port, _settings);
        _channel=_gain=_scan=_run=0;
    };

    // Change run mode
    void run() {
        _run=!_run;
    }

    // Change scan mode
    void scan() {
        _scan=!_scan;
    }

    // Change gain
    void gain(unsigned g) {
        _gain=g;
    }

    // Change channel
    void channel(unsigned c) {
        _channel=c;
    }

    // Get port status
    int status() {
        unsigned s=_bios_serialcom(_COM_STATUS, _port, 0);
        return s;
    }

    // Read value from port
    unsigned read(unsigned& v) {
        return v=_bios_serialcom(_COM_RECEIVE, _port, 0);
    }

    // Write a value to port
    void write() {
        _bios_serialcom(_COM_SEND, _port,
            _channel | _gain<<2 | _run<<4 | _scan<<5);
    }

    // Get a-to-d unit's configuration
    char* config() {
        sprintf(str, "Channel:%lx Gain:%ld %s %s", _channel, 1<<_gain,
            _scan?"Scanning":"Fixed", _run?"Running":"Single");
        // If scanning, keep track of channel
        if (_scan) {
            _channel++;
            _channel%=4;
        }
        return str;
    }
}; // End of class definition

```

Listing 3. Turbo C++ routine applying the object-oriented software, Listing 2.

```

void main(void) {

    unsigned in, out;
    class serial s(COM2, SETTINGS);
    // Define and setup port

    clrscr();
    for(;;){
        if (s.status() & DATA_READY)
            // Print unit's configuration and
            // value read
            cprintf ("%s %3d\r", s.config(),
                s.read(in));

        if (kbhit()) {
            out=getch();
            if (out=='\x1B')
                // Escape key pressed. Quit.
                exit(1);
            else {
                if (out=='\x00') {
                    // Extended key pressed
                    out = getch();
                    switch (out) {
                        case F1: s.channel(0); break;
                        case F2: s.channel(1); break;
                        case F3: s.channel(2); break;
                        case F4: s.channel(3); break;
                        case F5: s.gain(0); break;
                        case F6: s.gain(1); break;
                        case F7: s.gain(2); break;
                        case F8: s.gain(3); break;
                        case F9: s.run(); break;
                        case F10: s.scan(); break;
                    }
                    s.write();
                }
            }
        }
    }
}

```

anted to work up to 19200baud. Switches, S₁₋₃, program the oscillator, Table 3.

Selecting channels

Selection of the analogue channel is carried out by the MPC509 four-channel differential multiplexer, IC₆. This device offers up to 70V_{p-p} over-voltage protection, and should it lose power, it does not cause problems for the signal sources.

Channel addressing for the multiplexer is produced by the asynchronous presettable two-bit counter-latch formed by the JK bistable devices, IC₁₀ and the steering logic, IC₁₁. Operation is as follows.

When scan mode is off, i.e. RBR₅ is low, the JK bistable device clocks are disabled, and the channel address on RBR₁₋₂ is used to preset the counter-latch outputs. The PRESET signal, created by data-received signal DR going high and triggering monostable IC_{8b}, enables the NAND gates, IC₁₁. These then derive suitable logic levels for the bistable clear and set inputs. These inputs are clock independent, or asynchronous. Since the multiplexer's ENABLE line is tied high, the analogue input channel is immediately selected.

In channel scanning mode, with RBR₅ high, the counter-latch is preset with the channel address, as before. In this case, however, after each conversion has completed, the counter is incremented by the NEXT pulse. This pulse is derived from the BUSY signal going inactive, and enabled by the inputs RBR₅₋₆ on NAND gate IC_{12c}. It results in the next analogue channel being selected.

Programmable-gain amplifiers

The PGA205 programmable amplifier, IC₅, provides fixed programmable gains of 1, 2, 4, and 8. Its gain-selection inputs are ttl-compatible and bits RBR₃₋₄ are connected directly. With the a-to-d converter configured with a reference voltage of 2.5V, the PGA205 gives the system the full scale ranges and resolutions shown in Table 4.

Conversion mode

The conversion mode allows the unit to make either a single conversion when requested, or continually provide conversions, i.e. free run, at a rate governed by the uart.

If the single conversion mode is selected, i.e. RBR₆ is low, the a-to-d converter starts converting the selected channel shortly after

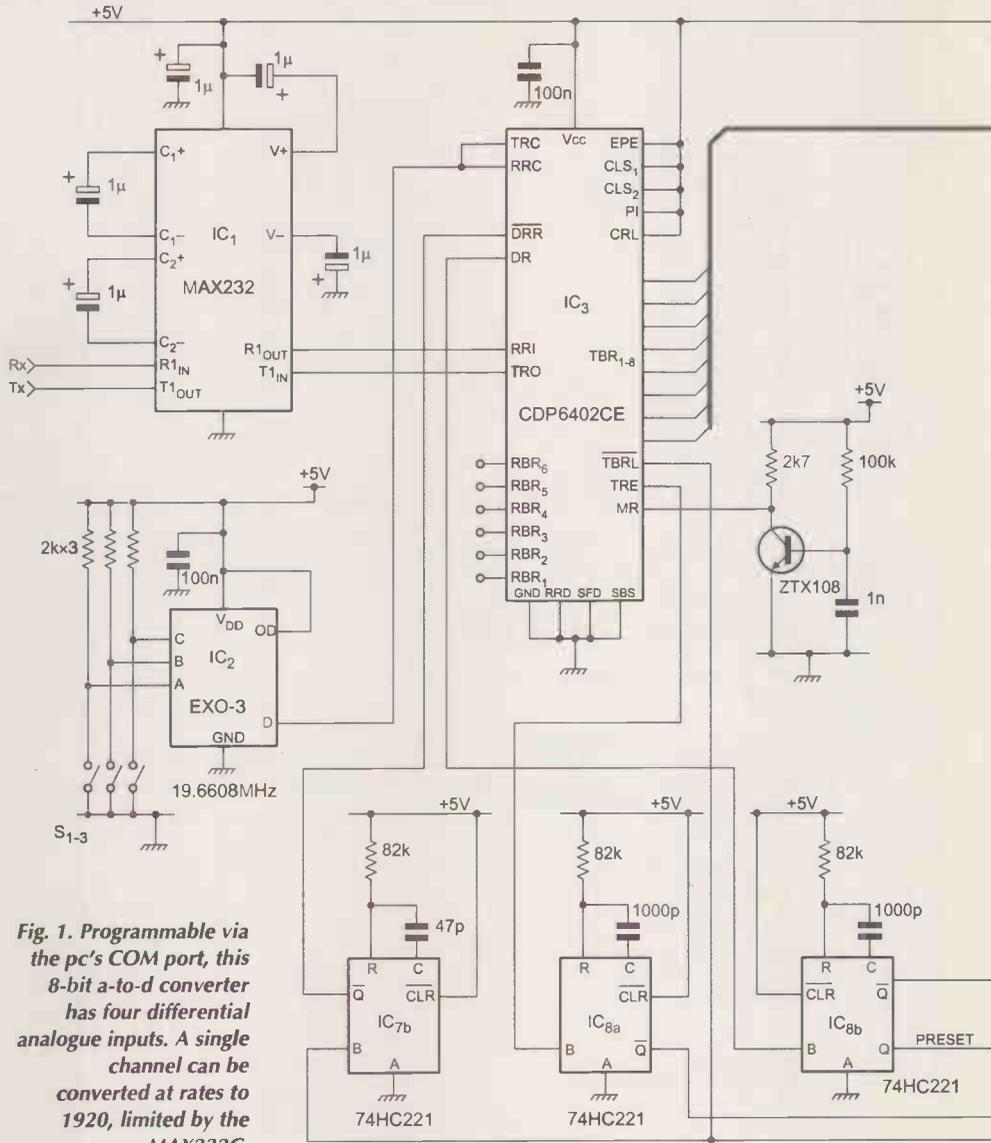


Fig. 1. Programmable via the pc's COM port, this 8-bit a-to-d converter has four differential analogue inputs. A single channel can be converted at rates to 1920, limited by the MAX232C.

the command is received from the computer. The data received status line DR goes high, and edge-triggered monostable IC_{8b} provides a low level pulse of about 82µs duration to the WRITE input of the a-to-d.

On the rising edge of the same low-level pulse, the a-to-d converter starts converting. The duration of the pulse is long enough to ensure the PGA205 gain network and multi-

plexer have settled. It is also fast enough for conversions to be performed and transmitted at up to about 19.2 kilobaud, i.e. the sampling rate is about 1.9kHz.

NAND gates within IC₉ select the source to be used for the start conversion signal. With RBR₆ low, only DR is used as the basis for the WRITE signal. When RBR₆ is high however, the start conversion signal is derived initially


Table 4. Full scale range, or fsr, and resolution at different gains.

Gain	Unipolar		Bipolar	
	FSR	Resolution	FSR	Resolution
1	2.5V	9.8 mV	±2.5V	19.5 mV
2	1.25V	4.9mV	±1.25V	9.8 mV
4	0.625V	2.4mV	±0.625V	4.9mV
8	0.3125V	1.2mV	±0.3125V	2.4mV

Listing 1. QuickBasic routine showing how simple it is to grab an analogue sample from channel 0.

```

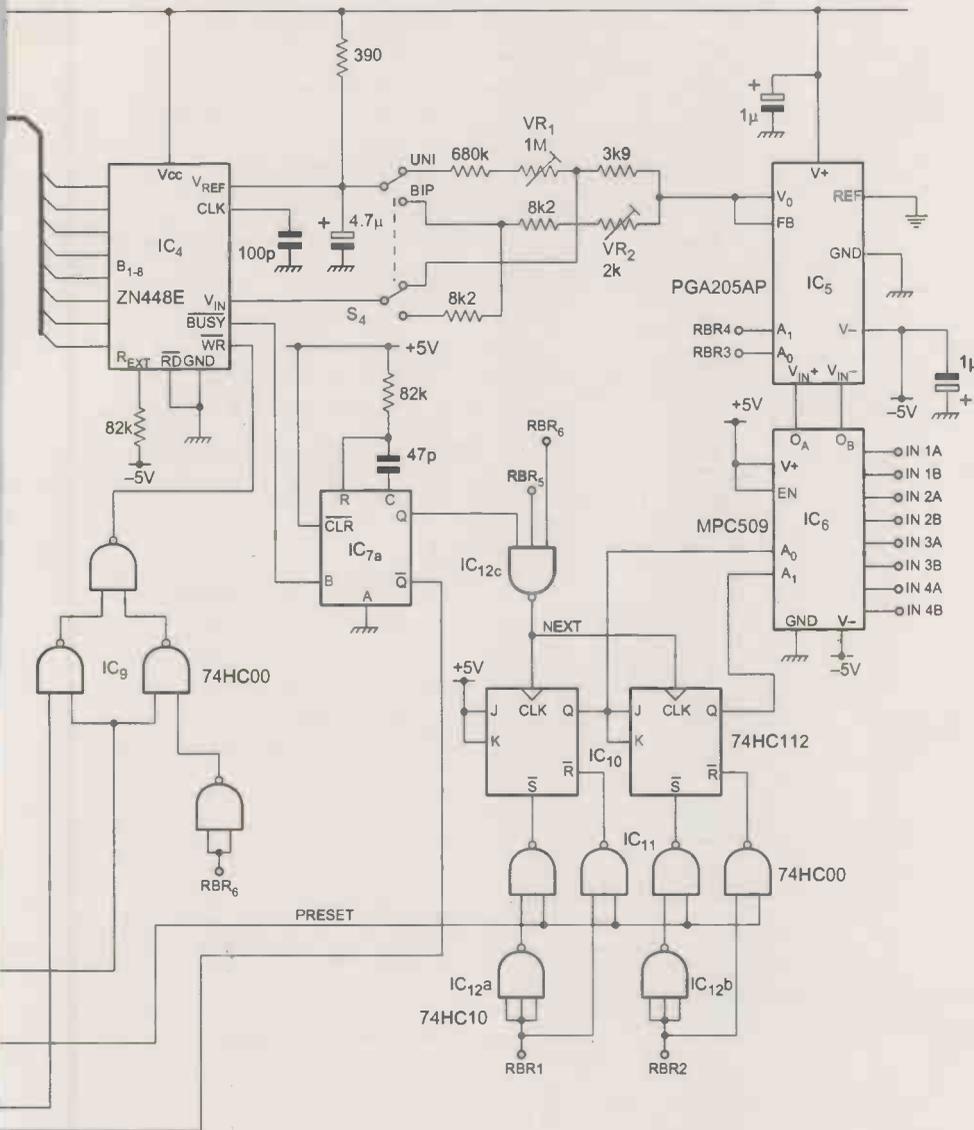REM Continually poll channel 0 (unity gain)
CLS : PRINT "Press any key to stop."
OPEN "COM2:9600,N,8,1" FOR RANDOM AS #1
A$ = ""
WHILE (A$ = "")
    PRINT #1, CHR$(0);
    LOCATE 2, 1: PRINT "Channel 0: "; ASC(INPUT$(1,
1))
    A$ = INKEY$
WEND
CLOSE #1
    
```



from DR, but then from the transmitter register empty, TRE, status flag of the uart. This signals that the last conversion has been sent to the computer, and that the UART is ready for new data. Again, the pulse is about 82µs duration.

Analogue-to-digital conversion

The a-to-d converter, IC₄, is a ZN448 8-bit successive approximation converter with internal band-gap reference and clock.

The converter is configured, by connecting the 100pF capacitor to the clock input, pin3, for conversion times of about 100ns. The input to the a-to-d converter can be either unipolar or bipolar according to the position of switch S₄. The resistor network sets the input voltage range to either 2.5V for unipolar operation or ±2.5V for bipolar.

During a conversion, the BUSY signal, active low, goes low, and when finished it goes high. On this rising edge, monostable multivibrator IC_{7a} creates a pulse that:

- automatically increments the channel

- address of the multiplexer,
- load the converted data into the uart's TBRL transmitter buffer register,
- reset the data received status flag of the uart, by taking DRR low.

Configuration and control

When the unit is powered up, the transistor, T₁ and associated passive components apply a low going pulse of 15µs to the uart's master reset MR input, and so ensures all the error/status flags, and transmitter buffers are reset.

The unit is easily configured and controlled by outputting byte commands – or appropriate ASCII characters – to the serial port.

An example *Quick-Basic* program is given in Listing 1. It shows how samples can be acquired from one channel, namely channel 0 with unity gain.

A further example is given by way of an object-oriented program using Borland *Turbo C++*, Listings 2, 3. Listing 2 gives the class implementation of the functions used to interface with the unit, while Listing 3 is an exam-

ple of the class being used. The pc's function keys are used to configure the unit's operation, and the escape key exits the program.

Neither of these examples check for framing errors nor overrun errors, which would be necessary to ensure samples are not missed, or, if scanning channels, that the channel being sampled does not become misaligned with what the program thinks is being sampled.

The serial communications functions provided by *Turbo C++* are implemented with hardware handshaking. In this case, a null modem can be used; link the request-to-send line RTS and clear to send, CTS, together, and link data set ready DSR, data carrier detect, DCD, and data terminal ready, DTR. In *Quick Basic*, setting parameters in the OPEN statement that ignore handshaking is possible.

Setting up

The only setting up required is that of the ZN448. This is easily achieved with either of the above example programs, set to sample a channel continually.

Zero adjustment is required for the unipolar range. This is done by applying 5mV to a channel, and adjusting VR₁ until the most significant bit flickers between one and zero with all the other bits at zero. No gain adjustment is provided in this design.

Only offset adjustment is required for the bipolar range, as this design offers no gain adjustment. In a similar way to the unipolar zero adjustment, apply -2.49V to a channel, and adjust VR₂ until the most significant bit flickers between one and zero with all the other bits at zero.

Further development

There are two bits of the uart's received data word spare, namely RBR_{7,8}. These could easily be used to expand the unit's capability. Obvious enhancements are to provide eight channels of differential input, or 16 channels of single-ended input, or to make the unipolar/bipolar modes software selectable.

If greater accuracy is required, gain adjustment for both unipolar and bipolar input ranges could be added to the ZN448. ■

Further reading

- MAXIM Integrated Products, MAX230-241 Data Sheet, pp 2-25 to 2-40.
- Universal asynchronous receiver transmitter, RS Data Sheet 4046, March 1985.
- Crystal Oscillators – KSS Kinseki, KSS-EXO-3 Series Data Sheet.
- MPC508A, Burr Brown Data Sheet.
- 8-bit A to D converter ZN448, RS Data Sheet 5291, March 1985.
- PGA205, Burr Brown Data Sheet, pp 4.175 to 4.187.
- MM74HC221A Dual Non-retriggerable monostable multivibrator, National Semiconductor Data Sheet, pp 3:204-3:208.

SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK

HP New Colour Spectrum Analysers
 HP141T+8552B IF + 8553B RF - 1KHz-110Mc/s - £700.
 HP141T+8552B IF + 8554B RF - 100KHz-1250Mc/s - £900.
 HP141T+8552B IF + 8556A RF - 20Hz-300KHz - £700.
 Special Offer just in from MOD Qty 40 HP8555A RF Units 10Mc/s - 18GHz.
 HP141T+8552B IF + 8555A 10Mc/s-18GHz - £1200.
 HP ANZ Units Available separately - New Colours - Tested
 HP141T Mainframe - £350.
 HP8552B IF - £300.
 HP8553B RF 1KHz to 110Mc/s - £200.
 HP8554B RF 100KHz to 1250Mc/s - £500.
 HP8555A RF 10Mc/s to 18GHz - £800.
 HP8556A RF 20Hz to 300KHz - £250.
 HP8443A Tracking Generator Counter 100KHz-110Mc/s - £300.
 HP8445B Tracking Prescaler Dc to 18GHz - £350.
 HP3580A 5Hz - 50KHz ANZ - £750 - £1000.
 HP3582A .02Hz to 25.6KHz - £2k.
 HP8568A 100Hz-1500Mc/s ANZ - £6k.
 HP8569B 10Mc/s-22GHz ANZ - £6k.
 HP Mixers are available for the above ANZ's to 40GHz
 TEK 492 - 50KHz - 18GHz Opt 1+2 - £4k-£4.2k.
 TEK 492 - 50KHz - 18GHz Opt 1+2+3 - £4.5k.
 TEK 492P - 50KHz - 21 GHz Opt 1+2+3 - £5k.
 TEK 494AP 1Kc/s - 21GHz - £7k.
 TEK 496P 1KHz-1.8GHz - £4k.
 TEK 5L4N 0-100KHz - £400.
 TEK 7L5 + L1 - 20Hz-5Mc/s - £700.
 TEK 7L5 + L3 - Opt 25 Tracking Gen - £900.
 TEK 7L12 - 100KHz-1800Mc/s - £1000.
 TEK 7L18 - 1.5-80GHz - £1500.
 TEK 491 10Mc/s-12.4GHz-40GHz - £750. 12.4Ghzs-40Ghzs with Mixers.
 Tektronix Mixers are available for above ANZ to 60GHz
 Systron Donner 763 Spectrum ANZ + 4745B Prescaler .01-18GHz + Two Mixers 18-40GHz in Transit Case - £3k.
 HP8673D Signal Generator .05-26.5GHz - £20k.
 Systron Donner 1618B Microwave AM FM Synthesizer 50Mc/s 2-18GHz
 R&S SWP Sweep Generator Synthesizer AM FM 4-2500Mc/s - £3.5k.
 ADRET 3310A FX Synthesizer 300Hz-60Mc/s - £600.
 HP8640A Signal Generators - 1024Mc/s - AM FM - £800.
 HP3717A 70Mc/s Modulator - Demodulator - £500.
 HP8651A RF Oscillator 22Kc/s - 22Mc/s.
 HP5316B Universal Counter A+B.
 HP6002A Power Unit 0-5V 0-10A 200W.
 HP6825A Bipolar Power Supply Amplifier.
 HP461A-465A-467A Amplifiers.
 HP81519A Optical Receiver DC-400Mc/s.
 HP Plotters 7470A-7475A.
 HP3770A Amplitude Delay Distortion ANZ.
 HP3770B Telephone Line Analyser.
 HP8182A Data Analyser.
 HP59401A Bus System Analyser.
 HP6260B Power Unit 0-10V 0-100 Amps.
 HP3782A Error Detector.
 HP3781A Pattern Generator.
 HP3730A+3737A Down Converter Oscillator 3.5-6.5GHz.
 HP Microwave Amps 491-492-493-494-495-1GHz-12.4GHz - £250.
 HP105B Quartz Oscillator - £400.
 HP5087A Distribution Amplifier.
 HP6034A System Power Supply 0-60V 0-10A-200W - £500.
 HP6131C Digital Voltage Source + 100V 1/2 Amp.
 HP4275A Multi Frequency L.C.R. Meter.
 HP3779A Primary Multiplex Analyser.
 HP3779C Primary Multiplex Analyser.
 HP8150A Optical Signal Source.
 HP1630G Logic Analyser.
 HP5316A Universal Counter A+B.
 HP59501B Isolated Power Supply Programmer.
 HP8901A Modulation Meter AM - FM - also 8901B.
 HP5370A Universal Time Interval Counter.
 Marconi TF2370 - 30Hz-110Mc/s 750HM Output (2 BNC Sockets+Resistor for 500HM MOD with Marconi MOD Sheet supplied - £650.
 Marconi TF2370 30Hz-110Mc/s 50 ohm Output - £750.
 Marconi TF2370 as above but late type - £850.
 Marconi TF2370 as above but late type Brown Case - £1000.
 Marconi TF2374 Zero Loss Probe - £200.
 Marconi TF2440 Microwave Counter - 20GHz - £1500.
 Marconi TF2442 Microwave Counter - 26.5GHz - £2k.
 Marconi TF2305 Modulation Meter - £2.3k.
 Rcal/Dana 2101 Microwave Counter - 10Hz-20GHz - £2k.
 Rcal/Dana 1250-1261 Universal Switch Controller + 200Mc/s PI Cards.
 Rcal/Dana 9303 True RMS Levelmeter+Head - £450. IFFE - £500.
 TEKA6902A also A6902B Isolator - £300-£400.
 TEK 1240 Logic Analyser - £400.
 TEK FG5010 Programmable Function Generator 20Mc/s - £600.
 TEK2465A 350Mc/s Oscilloscope - £2.5k + probes - £150 each.
 TEK CT-5 High Current Transformer Probe - £250.
 TEK J16 Digital Photometer + J6523-2 Luminance Probe - £300.
 TEK J16 Digital Photometer + J6503 Luminance Probe - £250.
 ROTEK 320 Calibrator + 350 High Current Adaptor AC-DC - £500.
 FLUKE 5102B AC-DC Calibrator - £4k.
 FLUKE 1120A IEEE - 488 Translator - £250.
 Tinsley Standard Cell Battery 5644B - £500.
 Tinsley Transportable Voltage Reference - £500.
 FLUKE Y5020 Current Shunt - £150.
 HP745A+746A AC Calibrator - £800.
 HP8080A MF + 8091A 1GHz Rate Generator + 8092A Delay Generator + Two 8093A 1GHz Amps + 15400A - £800.
 HP54200A Digitizing Oscilloscope.
 HP11729B Carrier Noise Test Set .01-18GHz - LEF - £2000.
 HP3311A Function Generator - £300.
 Marconi TF2008 - AM-FM signal generator - also sweeper - 10Kc/s - 510Mc/s - from £250 - tested to £400 as new with manual - probe kit in wooden carrying box.
 HP Frequency comb generator type 8406 - £400.
 HP Vector Voltmeter type 8405A - £400 new colour.
 HP Sweep Oscillators type 8690 A & B - plug-ins from 10Mc/s to 18GHz also 18-40GHz P.O.R..
 HP Network Analyzer type 8407A - 8412A + 8501A - 100Kc/s - 110Mc/s - £500 - £1000.
 HP Amplifier type 8447A - 1-400Mc/s £200 - HP8447A Dual - £300.
 HP Frequency Counter type 5340A - 18GHz £1000 - rear output £800.
 HP 8410 - A - B - C Network Analyzer 110Mc/s to 12GHz or 18GHz - plus most other units and displays used in this set-up - 8411a - 8412 - 8413 - 8414 - 8418 - 8740 - 8741 - 8742 - 8743 - 8746 - 8850. From £1000.
 Rcal/Dana 9301A - 9302 RF Millivoltmeter - 1.5-2GHz - £250-£400.
 Rcal/Dana Modulation Meter type 9009 - 8Mc/s - 1.5GHz - £250.
 Marconi RCL Bridge type TF2700 - £100.
 Marconi/Saunders Signal Sources type - 6058B - 6070A - 6055A - 6059A - 6057A - 6056 - £250-£350. 400Mc/s to 18GHz.
 Marconi TF1245 Circuit Magnification meter + 1246 & 1247 Oscillators - £100-£300.
 Marconi microwave 6600A sweep osc., mainframe with 6650 PI - 18-26.5GHz or 6651 PI - 26.5-40GHz - £1000 or PI only £600. MF only £250.
 Marconi distortion meter type TF2331 - £150; TF2331A - £200.

Tektronix Plug-Ins 7A13 - 7A14 - 7A18 - 7A24 - 7A26 - 7A11 - 7M11 - 7S11 - 7D10 - 7S12 - S1 - S2 - S8 - S52 - PG506 - SC504 - SG502 - SG503 - SG504 - DC503 - DC508 - DD501 - WR501 - DM501A - FG501A - TG501 - PG502 - DC505A - FG504 - 7880 + 85-7892A
 Gould J38 test oscillator + manual - £150.
 Tektronix Mainframes - 7603 - 7623A - 7613 - 7704A - 7844 - 7904 - TM501 - TM503 - TM506 - 7904A - 7834 - 7623 - 7633.
 Marconi 6155A Signal Source - 1 to 2GHz - LED readout - £400.
 Barr & Stroud Variable filter EF3 0.1Hz - 100Kc/s + high pass + low pass - £150.
 Marconi TF2163S attenuator - 1GHz. £200.
 Farnell power unit H60/50 - £400 tested. H60/25 - £250.
 Rcal/Dana 9300 RMS voltmeter - £250.
 HP 8750A storage normalizer - £400 with lead + S.A or N.A interface.
 Marconi TF2330 - or TF2330A wave analysers - £100-£150.
 Tektronix - 7S14 - 7T11 - 7S11 - 7S12 - S1 - S2 - S39 - S47 - S51 - S52 - S53 - 7M11.
 Marconi mod meters type TF2304 - £250.
 HP 5065A rubidium vapour FX standard - £1.5k.
 Systron Donner counter type 6054B - 20Mc/s - 24GHz - LED readout - £1k.
 Rcal/Dana 9083 signal source - two tone - £250.
 Systron Donner - signal generator 1702 - synthesized to 1GHz - AM/FM - £600.
 Tektronix TM515 mainframe + TM5006 mainframe - £450 - £850.
 Farnell electronic load type RB1030-35 - £350.
 Rcal/Dana counters - 9904 - 9905 - 9906 - 9915 - 9916 - 9917 - 9921 - 50Mc/s - 3GHz - £100-£450 - all fitted with FX standards.
 HP4815A RF vector impedance meter c/w probe - £500-£600.
 Marconi TF2092 noise receiver. A, B or C plus filters - £100-£350.
 Marconi TF2091 noise generator. A, B or C plus filters - £100-£350.
 Marconi 2017 S/G 10KHz - 1024MHz.
 HP180TR, HP182T mainframes £300-£500.
 Philips panoramic receiver type PM7900 - 1 to 20GHz - £400.
 Marconi 6700A sweep oscillator + 18GHz PI's available.
 HP8505A network ANZ + 8503A S parameter test set + 8501A normalizer - £4k.
 HP8505 network ANZ 8505 + 8501A + 8503A.
 Rcal/Dana VLF frequency standard equipment. Tracer receiver type 900A + difference meter type 527E + rubidium standard type 9475 - £2750.
 HP signal generators type 626 - 628 - frequency 10GHz - 21GHz.
 HP 432A - 435A or B - 436A - power meters + powerheads - Mc/s - 40GHz - £200-£1000.
 Bradley oscilloscope calibrator type 192 - £600.
 HP8614A signal generator 800Mc/s - 2.4GHz, new colour £400.
 HP8616A signal gen 1.8GHz - 4.5GHz, new colour £400.
 HP 3325A syn function gen 20Mc/s - £1500.
 HP 3336A or B syn level generator - £500 £600.
 HP 3586B or C selective level meter - £750-£1000.
 HP 3575A gain phase meter 1Hz - 13Mc/s - £400.
 HP 8683D S/G microwave 2.3 - 13GHz - opt 001 - 003 - £4.5k.
 HP 8660 A-B-C syn S/G. AM + FM + 10Kc/s to 110Mc/s PI - 1Mc/s to 1300Mc/s - 1Mc/s to 2600Mc/s - £500-£2000.
 HP 8640B S/G AM-FM 512Mc/s or 1024Mc/s. Opt 001 or 002 or 003 - £800-£1250.
 HP 86222BX Sweep PI - 01 - 2.4GHz + ATT - £1750.
 HP 8629A Sweep PI - 2 - 18GHz - £1000.
 HP 86290B Sweep PI - 2 - 18GHz - £1250.
 HP 86 Series PI's in stock - splitband from 10Mc/s - 18.6GHz - £250-£1k.
 HP 8620C Mainframe - £250. IEEE - £500.
 HP 8615A Programmable signal source - 1MHz - 50Mc/s - opt 002 - £1k.
 HP 8601A Sweep generator. 1 - 110Mc/s - £300.
 HP 3488A HP - IB switch control unit - £500 + control modules various - £175 each.
 HP 8160A 50Mc/s programmable pulse generator - £1000.
 HP 853A MF ANZ - £1.5k.
 HP 8349A Microwave Amp 2 - 20GHz Solid state - £1500
 HP 3585A Analyser 20Hz - 40Mc/s - £4k.
 HP 8569B Analyser .01 - 22GHz - £5k.
 HP 3580A Analyser 5Hz - 50KHz - £1k.
 HP 1980B Oscilloscope measurement system - £600.
 HP 3455A Digital voltmeter - £500.
 HP 3437A System voltmeter - £300.
 HP 3581C Selective voltmeter - £250.
 HP 5370A Universal time interval counter - £450.
 HP 5335A Universal counter - 200Mc/s - £500.
 HP 5328A Universal counter - 500Mc/s - £250.
 HP 6034A System power supply 0 - 60V - 0 - 10 amps - £500.
 HP 5150A Thermal printer - £250.
 HP 1645A Data error analyser - £150.
 HP 4437A Attenuator - £150.
 HP 3717A 70Mc/s modulator - £400.
 HP 3710A - 3715A - 3716A - 3702B - 3703B - 3705A - 3711A - 3791B - 3712A - 3793B microwave link analyser - P.O.R.
 HP 3730A+B RF down converter - P.O.R.
 HP 3552A Transmission test set - £400.
 HP 3763A Error detector - £500.
 HP 3764A Digital transmission analyser - £600.
 HP 3770A Amp delay distortion analyser - £400.
 HP 3780A Pattern generator detector - £400.
 HP 3781A Pattern generator - £400.
 HP 3781B Pattern generator (bell) - £300.
 HP 3782A Error detector - £400.
 HP 3782B Error detector (bell) - £300.
 HP 3785A Jitter generator + receiver - £750-£1k.
 HP 8006A Word generator - £100-£150.
 HP 8016A Word generator - £250.
 HP 8170A Logic pattern generator - £500.
 HP 58401A Bus system analyser - £350.
 Philips FM5990 RF syn - 0.1 - 1GHz - AM + FM - £1000.
 S.A. Spectral Dynamics SD345 spectroscope 111 - LF ANZ - £1500.
 Tektronix R7912 Transient waveform digitizer - programmable - £400.
 Tektronix TR503 + TM503 tracking generator 0.1 - 1.8GHz - £1k - or TR502.
 Tektronix 576 Curve tracer + adaptors - £900.
 Tektronix 577 Curve tracer + adaptors - £900.
 Tektronix 1502/1503 TDR cable test set - £1000.
 Tektronix AM503 Current probe + TM501 m/frame - £1000.
 Tektronix SC501 - SC502 - SC503 - SC504 oscilloscopes - £75-£350.
 Tektronix 465 - 465B - 475 - 2213A - 2215 - 2225 - 2235 - 2245 - £250-£1000.
 Kikusui 100Mc/s Oscilloscope COS6100M - £350.
 Nicolet 3091 LF oscilloscope - £400.
 Rcal 1991 - 1992 - 1988 - 1300Mc/s counters - £500-£900.
 Fluke 80K-40 High voltage probe in case - BN - £100.
 Rcal Recorders - Store 4 - 4D - 7 - 14 channels in stock - £250 - £500.
 Rcal Store Horse Recorder & control - £400-£750 Tested.
 EIP 545 microwave 18GHz counter - £1200.
 Fluke 510A AC ref standard - 400Hz - £200.
 Fluke 355A DC voltage standard - £300.
 Wiltron 610D Sweep Generator + 6124C PI - 4 - 8GHz - £400.
 Wiltron 610D Sweep Generator + 61084D PI - 1Mc/s - 1500Mc/s - £500.
 Time Electronics 9814 Voltage calibrator - £750.
 Time Electronics 9811 Programmable resistance - £600.
 Time Electronics 2004 D.C. voltage standard - £1000.
 HP 8699B Sweep PI VLF oscillator .01 - 4GHz - £300. 8699B MF - £250. Both £500.
 Schlumberger 1250 Frequency response ANZ - £1500.
 Dummer Loads & power at up to 2.5 kilowatts FX up to 18GHz - microwave parts new and ex equip - relays - attenuators - switches - waveguides - Yigs - SMA - APC7 plugs - adaptors.
 B&K items in stock - ask for list.
 W&G items in stock - ask for list.
 Power Supplies Heavy duty + bench in stock - Farnell - HP - Weir - Thurlby - Rcal etc. Ask for list.

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. SAE FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS. AVAILABILITY OR PRICE CHANGE. VAT AND CARRIAGE EXTRA

ITEMS MARKED TESTED HAVE 30 DAY WARRANTY. WANTED: TEST EQUIPMENT-VALVES-PLUGS AND SOCKETS-SYNCRS-TRANSMITTING AND RECEIVING EQUIPMENT ETC.

Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. No: (01274) 684007. Fax: 651160

SUBSCRIBE TODAY

And Electronics World will help you keep the leading edge

EVERY MONTH
- the best writing on
Electronics design applications

ELECTRONICS WORLD
INCORPORATING WIRELESS WORLD



1 Year £30 UK, £43 Europe, £52 Row

2 Years SAVE 25% £45 UK, £65 Europe, £75 Row

Phone: +44 01444 445566, Fax (+44) 01444 445447

SUBSCRIPTION FORM

YES, I WOULD LIKE TO SUBSCRIBE TO ELECTRONICS WORLD

Name _____
Job Title _____
Company Name _____
Address _____

Postcode _____ Country _____
Telephone _____ Fax _____

PAYMENT DETAILS

1 year £30 UK £43 Europe £52 Rest of World
 2 years £45 UK £65 Europe £75 Rest of World
 Please invoice me/my company. Purchase Order N° _____
 I enclose cheque made payable to Electronics World
 Please charge my Visa/Access/Amex/Mastercard
□□□□□□□□□□□□□□□□

Expiry date _____ Signature _____

Please tick box if you do not wish to receive promotions from other companies.

UK RETURN ADDRESS: Electronics World, Freeport CN 2619, Reed Business Publishing, 9th Floor, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5BR.
REST OF WORLD: ELECTRONICS WORLD, Reed Business Publishing, 9th Floor, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS, UK.

Free circuit design software TINA for Windows

This month's cover disk* is a working, interactive version of TINA for Windows. Newly launched, this comprehensive package is an electronics toolkit integrating all the functions needed for the design, development and test of electronic circuits. TINA makes it easier and faster to simulate circuits with realistic characteristics.

TINA comprises a software simulation and analysis package, together with a complete range of 'virtual' test and measurement instruments for testing design theories as well as breadboards, prototypes or any other electronic product.

The demonstration version of TINA presented free with this issue of *Electronics World* allows circuits of any size to be constructed but analysis only works on a limited number of nodes. Save and print facilities are also disabled.

PSpice compatibility

Unlike many circuit design systems, TINA can save your designs as an industry standard PSpice format netlist – which means that design concepts are based on the specifications of actual components. This makes simulation more realistic and the identification of faults easier. It also simplifies 'what if' questions, and allows different components to be tested quickly, easily and without the need to build breadboards. This obviously saves considerable time, as well as the cost of components.

Comprising all the necessary hardware and software, Tina is a complete system which allows digital, analogue or mixed-mode circuits to be simulated. Tina is also a powerful analytical tool and can perform AC, DC or transient analysis as well as noise, tolerance and Fourier analysis.

Comprehensive library

A comprehensive library of components contains power supplies, resistors, capacitors, inductors, amplifiers, switches, etc. Using familiar Windows-style commands, these are simply selected, dragged and dropped into the desired circuit diagram. Component values can then be changed to create and test the feasibility of the ideal circuit.

The library features digital components, including a large selection of TTL and CMOS standard devices.

Low price

Tina, is very cost effective. A single copy of the software costs only £299 and a 20-user site licence is only £1,800, excluding hardware. Special discounts are available for educational establishments.

For further information contact: Tandem Technology Limited, Breadbare Barns, Clay Lane, Chichester, West Sussex, PO18 8DJ, telephone: 01243 576121 fax: 01243 576119, e-mail 101626.3234@compuserv.com.

*Available to UK readers only.



Virtual instruments – supplied with the Tina circuit design tool is a complete range of test and measurement 'virtual instruments' – including a function generator, multimeter, power supply and oscilloscope. These are used to analyse test circuit designs as well as providing real time test and measurement of actual circuits, prototypes and breadboards. The benefit of these 'virtual' instruments is that they operate via the PC. This makes it easy to incorporate measurement values into calculations and analyses.

Until 4 October, this voucher is worth £100 off TINA's normal price of £299 excluding VAT and delivery. Simply send this voucher together with £237.93 – fully inclusive – to Tandem Technology Limited, Breadbare Barns, Clay Lane, Chichester, West Sussex, PO18 8DJ. Telephone: 01243 576121 fax: 01243 576119, e-mail 101626.3234@compuserv.com.

Loading your free software

Full instructions on loading the demonstration version of Tina are given in the README.TXT file on the disk. This file is accessed by inserting the disk in drive A and double-clicking on the file under Windows' File Manager. Once the software is installed, this read-me file appears as a Windows icon.

The route to pcb cad

Rod Cooper's second set of reviews covers *Ranger2* and *Electronics Workbench*.

PCB CAD review subjects

This review, which began last month and continues next, covers the following ten products.

PCB Designer: Niche Software Ltd, tel. UK 01432 355414. £49 inclusive (see September issue).

PIA: AW Software, tel. Germany +49 89 6915352. PIA std 99DM: extended 171DM 32bit 286DM inc tax (see September issue).

Easytrax: Protel International Pty, tel. Australia 408 437 7771, UK PDSL, tel. 01892 663298 (see September issue).
£6 copying charge.

Ranger2: Seetrex CAE Ltd. 01705 591037, £150 exc £10 p+p and VAT.

Electronics Workbench: Interactive Image Technologies Ltd (Canada), tel. 0014169775550. UK Robinson Marshall, tel. 01203 233 216, £199 exc p+p and VAT.

Quickroute 3.5 Pro+: Quickroute Systems Ltd.

CircuitMaker: MicroCode Engineering.

Propak: Labcenter Electronics.

Proteus: Labcenter Electronics.

EasyPC Pro XM: Number 1 Systems.

Note that although it started last month with a couple of smaller packages, this review is not in any order of complexity or competence.

A common drawback in computer-based pcb design programs is that the small crt screens often used are not an ideal drawing board. This fact is never mentioned in the glossy brochures. A standard 14in screen on a typical pc does not give you 11in by 8in to draw on. Do not be surprised if you find that you have a drawing area of 7in by 6in or less; you are not going to get much circuitry in that area.

The rest of the screen is taken up with program controls, and most irritating, the program maker's name, logo or other useless clutter. Fortunately, some programs give a much better performance in this region than others, as detailed in the individual reviews.

Most programs use a large sheet for drawing on – A3 for example – and you are supposed to pan around with your small viewing window if you want to see the rest of the circuit. This illustrates the importance of having auto-pan or a good manual panning method.

Larger circuits will have more than one page which will of course be out of sight altogether until you make a page-change request. This is not as easy as turning over a page of a circuit diagram, although some people would have you believe otherwise.

Because components appear small on a small screen, you will have to zoom in to get resolution of the parts and their pads, and zoom out again to see the circuit. This makes it essential to have an efficient method of zooming and panning.

I think relative to having the circuit drawn out before you on real paper, all methods of repre-

senting the circuit on screen are inferior if are planning a circuit from scratch – ie actually designing rather than just drafting. You could of course buy a larger monitor – say 17in or 21in, with higher resolution – but these are still very expensive and very bulky compared to the common 14in model and you still will not solve the problem completely.

Neither is the mouse a good drawing tool; a pencil and paper is much better than a mouse and mat if you are experimenting. Some people prefer a digitising tablet. Proponents of the tablet system say that it is more accurate than a mouse, easier to use in CAD, faster, and comes more naturally to someone used to drawing with a pen and paper.

I use a digitising tablet for CAD, and a mouse for everything else, and I have to agree. However, on the down side, tablets are at least twenty times more expensive than a mouse and it will come as no surprise to learn that some programs that work well with a mouse do not work well with a digitising tablet. I tried every program with both mouse and tablet.

Standards and formats – or not

Unfortunately, there is not much standardisation in this branch of computer-aided design. Each maker has its own way of presenting component outlines, drawing schematics, etc. etc. Few commands or menus are standard. This means that if you take the time and effort to learn a program produced by one company, you will have to go through the same time-consuming process all over again if you change to another.

The good news is that there is a trend towards standardisation in the output format for net lists and component lists and for computer-aided manufacturing although there is a long way to go in this respect.

Windows or dos?

The choice between dos and Windows will be of prime interest to the prospective buyer, with many opting for Windows simply because that is the trend. Much of what is presently available runs under dos. The many advantages of running a program in Windows that apply to business and accounting programs and the like, is to a large extent lost on pcb design software.

Free of the constraints of Windows, dos programmers can sometimes come up with a superior user interface. You can expect Windows programs to be more intuitive initially. But this will not enable you to operate a Windows system straight away unless it is very simple or small. You will find that you still need to read the manual, just as with a dos program. Although I am a Windows enthusiast myself, when it comes to pcb design, I regard dos as a viable alternative.

Programs written solely for dos are usually much cheaper, often have modest ram requirements, and take up less hard disk space than the equivalent Windows program. In addition, dos programs are nearly always quicker, for a given hardware setup.

Another good reason for choosing a dos program is that XT, AT, and 286 pcs that have been left behind in the Windows revolution will probably run it perfectly well. The money you save may be better spent on a 21in monitor and a digitising tablet.

Finally, most dos programs are mature products with the bugs and snags already designed out. If you buy a newly-produced Windows program it would be unreasonable to expect no bugs at all.

Printers or plotters?

Windows 3x provides a wider range of printer drivers than dos programs but on the other hand, pen plotters are not as well supported. Ironically this may provide a good reason for sticking to dos if you want to use your existing plotter.

With a few exceptions, most popular pen plotters, laser printers and matrix printers are well supported by the dos programs under review, so a list for every product is not included. Such lists are regularly updated so it is best to check that your printer is supported with the software distributor before buying.

Regarding the speed relationship between dos and Windows, if you want a bench-mark, then try screen redraws. These are fast in dos, and annoyingly slow in Windows. In fact, you need a very fast pc to make a Windows redraw to equal a dos redraw. Redraws are very important because they occur all the time in computer-aided design; for example, every time you pan, zoom or refresh.

Next month – Rod presents more reviews and explains what to watch out for with autorouters.

Review 1 –

Ranger 2 by Seetrax

Ranger2 is another dos-based product that will run on any pc from an XT upwards. The minimum requirements are modest – an IBM PC XT, 640kB of RAM, 20MB hard disk, EGA card and monitor. To test this, I ran it on a 286, and found no problem. It ran very well on the 386SX.

Ranger2 consists of a schematic drawing program with schematic capture, and an autorouter. The two are fully integrated and there is not much scope for connecting to another system. However, there is a facility to import a net list in the Futurenet format, and if you wanted to connect to a simulation program, you can export a net list in the PSpice format. For the latter, it is necessary to type in the PSPICE model types for each component before compilation.

A very good evaluation package is available which is fully-operational and will allow circuits with up to 64 components or 128 pins to be completed. The evaluation obtained via Seetrax is just £5 but, unusually, includes an excellent short-form printed manual. This is a sound marketing technique – Seetrax clearly realise that people starting out in CAD, such students and fledgling engineers, will use the full process of their evaluation package to make real boards, get to like the system and then go on to buy the full product.

This contrasts sharply with some other makers, whose evaluation packages are either of the non-usable or slide-show variety, or sometimes so cut-down and disabled that they cause more irritation than desire to buy the product. The manual for Ranger2 is comprehensive and well-written. The order in which subjects are placed is a little odd, but then most other manuals were like this.

The schematic drawing part of Ranger 2 has a large working area, about 8.5in by 6.5in on a 14in monitor. You can chose a page size from A1 to A5 to work on, and combine up to 8 pages in one design. The system is partly menu-driven by full-screen menus to start the job, leading to the drawing screen with a single vertical 17-button bar on the left with an abbreviated name

of the control on each button.

You quickly get to know the buttons from their names, and personally I think this is a much better system than using icons, even if the icons have pop-up help text added. It has been said that a well-designed GUI for dos can beat a poorly-designed Windows presentation. If so, then Ranger2 is a good example of this.

A second horizontal sub-bar can be generated from the first bar as required to give various options. I found this to be a very acceptable operating method, giving maximum drawing area without sacrificing control. The drawing method is a proper orthogonal system with automatic junction dot placement.

One excellent feature of Ranger 2 is that the drawing of any one connection is not enabled until you have located a component pin or pad, and then the drawn line is not fixed until you have connected it to another permitted point. A good snap-to system means that you do not have to hit the pin exactly as required in some

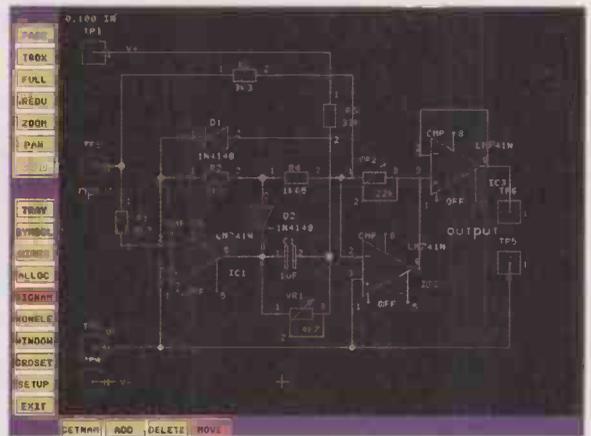


Fig. 1. Schematic of the test circuit. The lower horizontal button bar is generated from one of the vertical buttons on the left.



Fig. 2. Close-up of part of schematic showing clarity and definition of symbols.

other systems. This ensures the connectivity of your schematic.

You cannot hang lines in space by accident, your drawing cannot wander off to tie you in knots, and you cannot go wrong. This type of system, which is used in other programs as well as Ranger2, is a boon.

Power lines to ics are not shown in the schematic, just like most conventional circuit diagrams, but are automatically added later in the process.

Locating parts from the library system is easy and quick once you have read how to do it. Until you become familiar with the library, you have to refer to the manual to find out which volumes contain which parts. There is no on-screen help, but the manual provided with both the evaluation disk and full package is clear and concise.

The library size is adequate for general-purpose use. Parts are transferred to a parts bin on the screen which can be turned off to give more screen area; normally you would do this once the parts are on the screen. This is akin to the practice you would use on the real bench. Parts are described in text and only assume graphic form (ie as a symbol) when they are in the drawing area.

Moving the symbols around the drawing was smooth and precise. Text moves with the sym-

bol and stays upright if the symbol is rotated, and can be moved anywhere independent of the symbol in order to tidy up the diagram. There is no autopan, but pan is easily selected by a single click and works well. Autosave is included and the time between saves is adjustable.

Generating a net list

Generating a net list from the schematic (which incidentally Seetrax call a parts/wiring list) was a simple one-step operation. The parts/wiring list can be readily viewed to check for mistakes, but with Ranger2's connection-confirmation drawing program there are unlikely to be any errors arising from the processing system.

Defining the board profile was easy compared to other programs, but what impressed me was the way in which Ranger2 generates the rat's nest. Many programs dump a pile of components in a corner of the screen, and on big circuits it can be difficult to sort them out. Not so with Ranger – the parts are fed in one at a time and in another smooth and precise mouse manoeuvre you place them into the position you want. When all the components have been fed in, a message tells you so. This is one of the better rat's nest systems of the systems I have inspected, in my opinion.

The rat-lines move with the component, except for the power lines which are treated separately in Ranger 2. However, they can be reconnected by a single mouse-click on the appropriate button, and it is a method you soon get used to. Rat-lines self-optimize as you move components, ie they choose the shortest route, which is a considerable help.

Having arranged the rat's nest, the next step is to digitise the lines and pads prior to autorouting. This is an extra step peculiar to Ranger2 and it is hard to see why it has not been designed out. It is required less if you have the more powerful Spectra autorouter. In most circuits being routed in Ranger2 you would digitise and then autoroute the power lines first, then repeat the process for the signal lines. You could autoroute all the lines at once if you wanted but the Ranger2 approach gives the power lines priority, which in most cases is the correct way.

Pre-run configuration of the autorouter is reasonably comprehensive, but was easy to understand and perform. The operation of the autorouter can be biased for or against such things as the number of vias, 45° tracks, and tracks going in

the 'wrong' direction, ie away from the direct-line route. Interestingly, one of the parameters you can specify is how long the autorouter is allowed to take for each track it attempts. This feature is not seen on many autorouters, and on large boards it can be useful to limit overall run time. The grid size could be also varied.

One would suppose that such an autorouter would have problems with the amount of memory it would use on large boards. The notorious dos memory problem is side-stepped in Ranger2 by dividing the board into windows and doing each window in turn. This takes more time and it would be better if the autorouter utilised expanded or extended memory like other dos programs.

Routing double-sided boards

The standard autorouter does a fair job on double-sided boards. The performance on single-sided boards was not so good, despite a type of Lee's algorithm being listed as one of the autorouter's strategies. An example is shown in Fig. 4. Here, it has failed to route some of the tracks even though they are obvious to a human, and despite a generous time allowance being provided at the programming stage. This is not to single out Seetrax for criticism, because none of their competitors' autorouters at this price level were any better on single-sided boards. This autorouter falls into category C. For category system see next review.

The big advantage of the Ranger2 standard autorouter is its speed – it was comparatively quick even on large boards. Another advantage is that if a large number of un-connectable tracks is reported by the autorouter, it is particularly easy in Ranger2 to delete just the autorouter artwork, re-arrange the rat's nest and have another go.

Manually routing of the tracks that the autorouter failed to connect is performed by the rubber-banding technique. I don't think Ranger 2 is intended for making boards by manual routing – it is really meant as a fully automated program with a manual routing option for completing boards.

Summary

Ranger2 is an excellent product for double-sided and multilayer boards and is recommended. At only £150 it represents the best value for money for a full system, of the programs reviewed. It is easy to learn how to operate, and is relatively vice-free. There are two ways to upgrade, as follows.

As well as the standard autorouter, another type called the 386 Rip-up autorouter is available to purchasers of Ranger2, in an optional utilities bundle priced at £50. This bundle includes Autocad in/out and Gerber import. As the name suggests, this autorouter needs a 386 or better to make it work, as it uses the 386 protected mode to access extended memory. I used it firstly with 4MB of extended memory, but it ran better with 8MB.

It uses rip-up-and-retry strategies which improve its efficiency over the standard autorouter very considerably, but does not have push-and-shove. It can autoneck, and can route

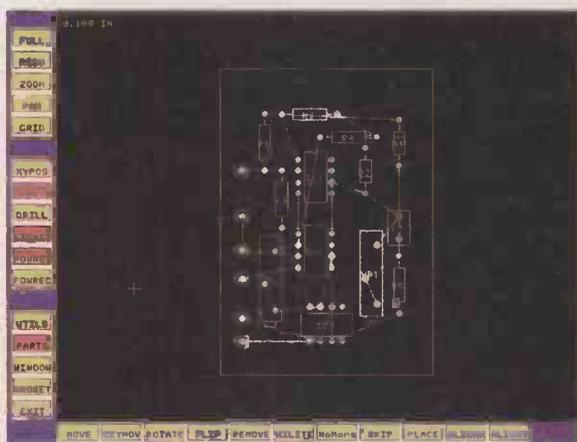


Fig. 3. Typical Ranger2 rat's nest, used for above autorouter tests. Note power rat-lines in blue.



Fig. 4. Results of standard autorouter on single-sided test circuit. Note incomplete rat-lines in green.

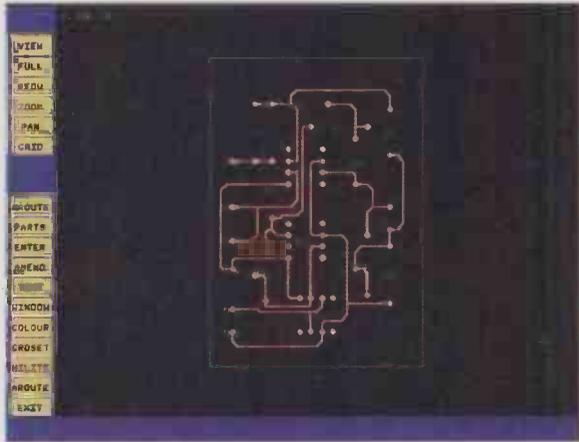


Fig. 5. Results of Specetra autorouter on the same rat's nest – 100% completion at first attempt.

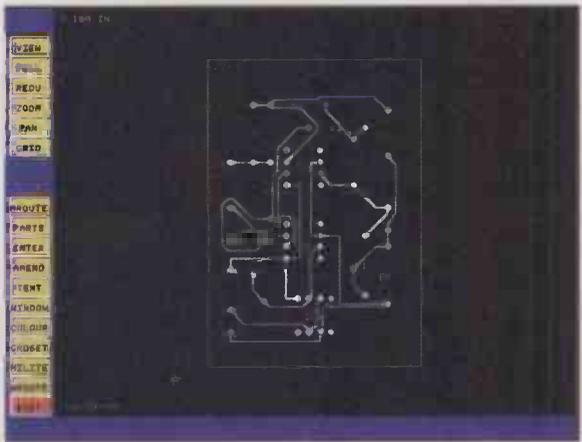


Fig. 6. Results of 386 Rip-up autorouter. Again, 100% completion.

at angles as well as in the usual orthogonal mode. It is a grid-type autorouter with an adjustable grid size. There are comprehensive means to configure it, much more so than with other autorouters in this review, and although the set-up therefore takes longer to perform than the standard Ranger2 autorouter, it is time well spent, as the results produced are much more satisfactory.

The 386 Rip-up autorouter has no difficulty in routing 100% on double-sided boards. In addition it can route small single-sided boards 100% given a good rat's nest layout, and the test circuit results put it in category A. It can be a little slow, but this can be used to advantage as you can see where it is having trouble routing – ie on a 386 the process is not so fast that it is too quick for the human eye.

This can help with re-arranging the rat's nest if you decide to re-route. I would rate the power of this 386 autorouter as lying well above the standard Ranger2 autorouter but a little below the Specetra product which is dealt with next.

The manual for the 386 Rip-up is supplied on the disk and is 34 pages of A4. Because Seetrax have fully incorporated the Specetra autorouter into Ranger2, they say they are doing no more development work on the 386 Rip-up autorouter.

few autorouters that could route small to medium single-sided boards 100%, and to achieve this it is only necessary to put in just a little extra work on the rats-nest to get optimum parts placement.

This autorouter requires a 386DX and a coprocessor and 8Mb of RAM minimum, 80MB of hard drive and at least MS-DOS 5.0. Even with this it will still page to disk on medium sized boards due to lack of RAM. If you increase RAM to 16Mb or more this becomes less noticeable. 32MB is recommended for large boards.

Protected autorouter

Unfortunately this autorouter is protected against piracy by a dongle. If you have not come across this device before, it is a small gadget which plugs into the pc's parallel port and without it you cannot run Specetra. It should (in theory) be transparent to printers, plotters and other devices that use the parallel port. Dongles got themselves a bad name in the early days for unreliability, so you don't see many of them around today. However, the Specetra dongle seems to work quite well.

The snags the dongle brings with it are three-fold. First, it is inconvenient to scabble about at the back of the pc just to get one program to work. This may be acceptable if you have only

Besides these two autorouters and perhaps in recognition that the standard autorouter, albeit capable, is a medium power router, Seetrax offer Ranger2 coupled to a much more powerful autorouter for £250 extra. This is the well-known Cooper (no relation) and Chyan gridless, re-entrant Specetra autorouter. Again, this is good marketing technique since someone starting out in CAD with Ranger2 has a well-defined path if he wants to up-grade.

With other systems, there is often no option for a more powerful autorouter, and if one is required (perhaps for a especially tough job) the only way forward is to buy a complete new system and undergo the relearning process, or buy a third-party autorouter, with the attendant problems with transfer of information between systems.

How much better is this autorouter? Amongst its many features Specetra has rip-up-and-retry, plus push-and-shove, and I quickly discovered these make it probably the most efficient autorouter in this price bracket, being able to route 100% on double-sided boards, with the fewest vias, and in very reasonable times. Specetra is one of the

one dongle, but it can become a nightmare if you have two or more to contend with from other programs.

Secondly, like any exposed piece of hardware fixed to the outside of the pc, it is vulnerable to damage, either physical or electrical. Snapping or bending a pin is a favourite. You then have to go cap-in-hand to the supplier for a new one.

Thirdly, I have found that it is very easy to misplace or lose completely such a small item as a dongle, and you are then in the same position as if you had damaged it. This isn't too bad if the supplier is still in business, at least you can buy a new one, but if the firm has been taken over or has ceased trading it means your program is then useless. There are other ways to secure software against piracy, many of them better than a dongle and cheaper too; dongles add a significant amount to the cost of software. This autorouter is the only product in this review that is routinely supplied with a dongle.

The Cooper and Chyan autorouter has extensive and flexible configuration controls. The instruction book at 120 pages long is larger than some manuals describing full systems. Most unusually, a manual on the Specetra design language – intended for use by programmers – is also provided. All this may appear daunting to those who are not fully computer-literate or who have turned their back on dos.

However, to Seetrax's credit they have provided their own Ranger2 interface and short-form configuration for Specetra, and this gets round any possible objections to the complexity of the autorouter. In addition, this approach eliminates one of the main objections to using a third-party autorouter, and that is having to learn another set of rules, another terminology, another screen format and another programmer's foibles.

In operation, Specetra is configured for routing in Ranger2, the work is done in Specetra, then a file is automatically passed back to Ranger2, so the results are viewed in Ranger2 format and processed from then on in the normal Ranger2 system – all very straightforward. Indeed, using the Seetrax interface you would not notice you are using a third-party autorouter were it not for the Specetra pages flashing past during routing.

I found Ranger2/Specetra combination easy to operate, which, considering the whole thing is in dos, and from two different sources, is remarkable. The version of Specetra provided by Seetrax gives improved manufacturability by putting an optional mitre on track corners and also by spreading tracks out to take maximum advantage of available space. This gives a very satisfactory finished product.

Summary of 386 and Specetra routers.

The 386 autorouter is a worthwhile and inexpensive addition to the standard Ranger2 package and is recommended.

The Cooper and Chyan autorouter gives even better results, and is much quicker than the 386. It is altogether a superior autorouter – perhaps the best of this review. However, there is the dongle aspect to consider.

Review 2 – Electronics Workbench

This is essentially a simulation product, ie a schematic drawing and capture program with integrated digital, analogue and mixed simulations, but there is the capability to connect it with a third-party pcb-design program. There is no specific pcb package allied to it, but an add-on program at £49.95 translates the schematic into Orcad, Tango, Eagle, Protel, Ultimate and Layo1 net lists for export. (This add-on is sometimes provided free – contact Robinson Marshal for details) Another add-on at £49.95 transfers SPICE net lists in and out. I tested the Tango and SPICE transfers – see later.

There are various versions of Electronics Workbench which can run under Windows 3.1 (4MB) as a 16-bit program, or as 32-bit program under Windows 3.1 (6MB) with Win32s, or under Windows 95 (4MB) or NT (12MB). The figures in brackets indicate the minimum amount of RAM you will need for each version. Of course, more RAM will help whichever version you choose. They are all supplied on the same set of three disks, which incidentally include Win32s if you don't already have it. The recommended minimum pc is the 486, with co-pro if you have the 486SX cpu, but I ran both 16 and 32 bit versions with Windows 3.1 on a 386SX with co-pro and 8MB of RAM and they both performed well.

Two books are supplied, one a user guide, the other a technical reference. These are well-written, but include large sections that refer to a dos version, and these can be a little distracting as they constantly get in the way. A third booklet is available as a teachers' guide with the educational version of Electronics Workbench, a version which enables faults to be set for student exercises. Of particular interest to teachers will be the many sample circuits already drawn and set up with instruments, ready to go. There is comprehensive on-line Help including a very good itemised explanation of the symbols in the generic libraries.

At first glance, Electronics Workbench may appear to be very similar to CircuitMaker. Indeed, they are both aimed at the same sector of the market, and both include facilities like fault injection for educationalists. However, both style and operating modes are different in many ways.

Using Workbench

The screen drawing area is about 9in by 5in without the parts bin, and about 7.5in by 5in with it. The actual drawing area is about four times bigger than this, with no support for multi-sheet schematics. There is a dot grid to assist drawing but I did not find it very useful because it did not appear well defined and the pale green dots did not show up well against the grey-white background. There are no colour options for the grid.

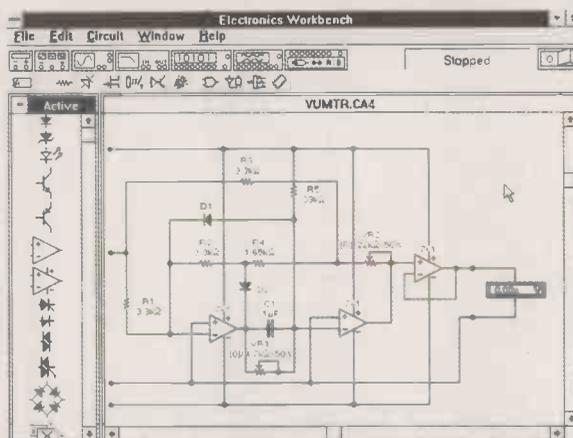


Fig. 7. Shows manually generated schematic. Note the active parts bin, how the voltmeter is connected and how readings are presented on it, and the realistic on/off switch at the top r.h.s.

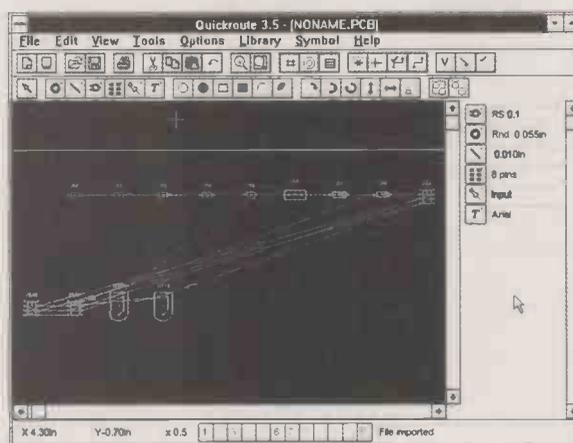


Fig. 8. This is a screen from Quickroute after a TANGO net list has been imported from Electronics Workbench for subsequent pcb artwork production. Note the rat-lines to the missing connector footprint are absent – see text for explanation.

However, use of the grid is not a high priority and is confined mainly to part placement because there is an automatic orthogonal drawing facility – you just point the mouse at the pins you want to join and the rest is done for you. This is a system similar to Propak's WAR and CircuitMaker's SmartWire. Unlike those two, there is no alternative facility for manual drawing to the automatic system.

If you do not like the results – and this can happen frequently as the schematic grows in size and density, and the auto-wiring program finds it harder to route – then you edit the connections using a technique very similar to rubber-banding, except in this case the results remain orthogonal. I prefer to have both methods at hand, using the auto-wire on small diagrams for speed, then reverting to manual if the diagram gets congested or large, because even if you are only moderately skilled at diagrams this combination saves on time otherwise spent editing. However, I should emphasise this is a personal preference.

Improved button bar?

Electronics Workbench does not use the familiar button-bar style to access functions like delete, pan, rotate etc. Where you would normally find the button-bar there is a row of simulated instruments such as signal genera-

tors and 'scopes. Underneath this there is a type of button bar, but the buttons do not implement tools; instead each of ten buttons opens a library volume. Most of the other functions you would expect to find in a button bar are in the drop-down menus. In practice, I found this a good arrangement.

The library of generic symbols is presented, one volume at a time, in a parts bin on the left-hand side of the screen, which can be scrolled to reach those symbols not on view. The method used here is to select a generic part, position it on the drawing area using drag and drop, then open the Circuit Menu and select the specific label, value and simulation model for that part.

This is repeated for each individual part – you cannot specify a group of identical parts such as resistors of the same type, for example. Although a logical system, and though I liked it, I found it to be rather slow. A few of the common symbols have default values, such as the op-amps, which are assumed to be 741 type unless re-labelled manually. The labels and values usually stay upright during rotation, although the manual advises some may rotate.

There are a little over a hundred or so generic symbols and 350 models in the basic version of Electronics Workbench. This is

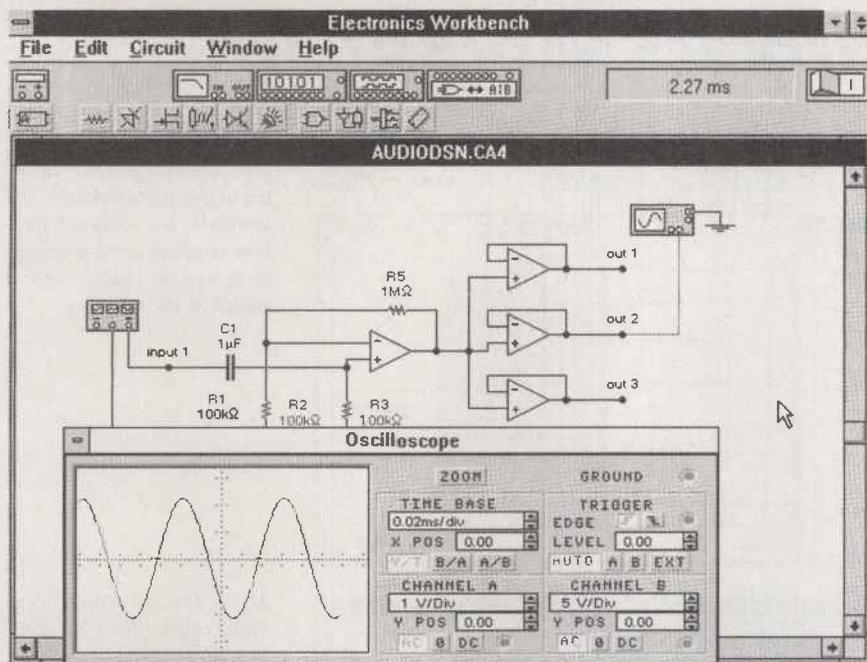


Fig. 9. Shows schematic automatically generated from imported SPICE net list from Quickroute. Note how instruments have been removed from instrument bar and connected. The 'scope window has been maximised.

probable sufficient for schematic drawing for making pcbs and for general-purpose usage as a simulation tool. An option of a further 2,100 models is available on a separate disk costing £99. A significant omission in the libraries was a volume on connectors. This does not matter in simulation, but it is of major importance when it comes to transferring a net list to a pcb program, because most circuits have connectors of one sort or another. This limits the usefulness of Electronics Workbench outside the simulator field as it stands at present.

To start drawing a connection you click on a component pin with the left mouse button. This button is also used to select symbols for editing, and at first I found it was all too easy to select symbols instead of drawing connections. It needed some practice until I was able to sort out one from the other. I would prefer to see the right-hand mouse button used for selecting symbols for edit, as in other programs. There is inhibition of bad connections and automatic junction dot placement, so it is easy to avoid making connectivity errors.

Panning the drawing area is done with the usual Windows scroll-bars. I was mildly surprised to discover there is no zoom feature for magnifying/reducing the diagram in the drawing area. The menu item called Zoom is used for something else – opening up instrument or circuit icons. With a 14in 640x480 16-colour screen, the symbols are just about sufficient in size and resolution to get away without zoom, and after a while I discovered I could carry on reasonably well, but I am sure someone with less than good eyesight would experience difficulty – they would need a larger monitor. Zoom is included with so many programs for good

reasons. Apart from this, the schematic drawing program was intuitively easy and pleasant to use.

Virtual instruments

Using the 'instruments' from the instrument bar bears an uncanny resemblance to taking a real instrument down from the shelf and making real connection to an actual circuit. The instruments in Electronics Workbench are designed to look something like the real thing, and connection to a circuit (although idealised) is also intended to re-assure the designer, and this is a success. As an added touch of realism, any plots or readouts on the 'scopes, dvms etc., appear on the actual instrument itself instead of in a window on the monitor screen.

This graphical technique is so easy and intuitive that anyone accustomed to working with proper instruments would feel at home with it. There are nine instruments provided in Electronics Workbench; voltmeter, ammeter, dual-beam oscilloscope, signal generator, d.v.m., word generator, logic analyser, logic converter and bode plotter covering the usual digital, SPICE-based analogue and mixed simulations. Like CircuitMaker, there is no plot of input/output impedance in the analogue section, and no pcb simulation such as Nol's Layan.

Creating a net list in one of the formats mentioned above for export to a pcb drawing program is also straightforward. I generated a Tango net list in Electronics Workbench and exported it to Quickroute 3.5 Pro+. I chose Quickroute for this because the net list transfer is particularly easy as both products are in Windows, and if you look at the Quickroute data, you will see that Tango is the preferred format for imports.

As Fig. 8 shows, this was successful except for the connectors; no fault of Quickroute's – I expected the connectors to be missing as there is no connector library in Electronics Workbench, as mentioned earlier, so no connector footprint can be transferred. No doubt you could overcome the connector problems by making up your own connector symbols for Electronics Workbench and then tying them in with the connector libraries in Quickroute but this is a lot of work.

You could also try adding the missing connectors by editing the rat's nest, but this is also fraught with difficulty. I think many designers would say – why go to this trouble when there are packages that are fully integrated and where these difficulties do not exist?

If you already had a schematic capture/pcb package and wanted a simulator, you might consider using Electronic Workbench as an add-on package. I tried exporting a SPICE net list from Quickroute (although I could equally well have used Propak) into Electronic Workbench, and it worked well. The schematic came out a little awry, but it was intact, and you could easily re-arrange it if you wanted to. But by adopting this system you would end up with two schematic drawing programs, one of which would be mainly redundant.

Summary

As this review is about pcb artwork production it may seem unusual to include Electronic Workbench, which is really a simulator, but as part of a pcb producing program Electronics Workbench has good potential, hence the provision of a net list exporter. The lack of a connectors volume in the symbols library is an impediment at present.

What Electronics Workbench would need in order to be considered seriously for pcb artwork production is a fully integrated Windows pcb program with autorouter, preferably with rip-up-and-retry strategies, or alternatively an alliance at the technical level with an already established pcb product. It comes so very close to meeting these criteria when allied to Quickroute3.5 (with the new AR3 autorouter) that it would be astonishing if the omission in Electronic Workbench's library was not put right. Such a combination would make a very attractive proposition indeed to a much wider group of engineers and designers.

As a simulation program, Electronics Workbench has many good points, but the absence of the zoom feature will not please many people, and this needs to be corrected. The lack of plots for input and output impedance make the analogue simulation less attractive to the serious engineer, and this feature really needs to be added. These points excepted, the presentation style of simulations is excellent for educational and demonstration purposes. ■

'OFF-AIR' FREQUENCY STANDARD



Second User Test Equipment

We are well known for our quality used Test Equipment. Our list is extensive, ranging through most disciplines. Here are a few examples – telephone for further details.

Marconi Spectrum Analyser	Marconi LCR Bridge TF2700....	£149
TF2370	Marconi LCR Bridge	
Bradley Oscilloscope Calibrator	TF1313A	£125
156.....	Mahogany Cased 5kV Megger	
Bird Termaline, 2.5kW 50Ω.....	(Collectors).....	£POA
Philips Function Generator	Taylor Valve Tester 474	£59
PM5134.....	Philips RF Generator PM5326	£395
Hitachi Oscilloscope V222,	HP Frequency Counter	
20MHz	HP5340	£595
Rapid Oscilloscope 7020,	Taylor AM/FM Generator 62A	£69
20MHz	Marconi Attenuator TF2163	£195
Philips Pulse Generator	RE Mega-Ohmmeter/pica-	
PM5716.....	Ammeter IM6.....	£295
Amprobe AC Recorder LAV3X.....	Ferrograph Recorder test Set	
Amprobe Temperature Recorder	RTS2.....	£95
LT8100.....	HP Vector Voltmeter	
Emerson UPS 1.5kW.....	HP8405A.....	£249

HALCYON ELECTRONICS

423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR
SHOP HOURS 9-5.30 MON-SAT. TEL 0181-542 6383. FAX 0181-542 0340

CIRCLE NO. 110 ON REPLY CARD

The Headphone Amplifier Box

Balanced or unbalanced microphone or line input to headphone output

Professional portable units operating from an internal PP3 battery or external DC supply



★ Precision transformerless balanced input ★ Bridged headphone output drive ★ Sensitivity selectable over a wide range of input levels ★ Low noise and distortion ★ High common mode rejection ★ Loop through facility ★ Extensive RFI protection

The Balance Box (precision mic/line amplifier)
– The Phantom Power Box – The *One Stop* DIN rail mounting radio frequency interference filter and voltage transient protector for voltage and current loop process signal lines

Conford Electronics Conford Liphook Hants GU30 7WJ
Information line 01428 751469 Fax: 751223

CIRCLE NO. 112 ON REPLY CARD

ELECTRONICS WORLD October 1996



Field Electric Ltd.

Tel: 01438-353781 Fax: 01438 359397

Mobile: 0836-640328

Unit 2, Marymead Workshops.

Willows Link, Stevenage, Herts. SG2 8AB.



Sony New 1.44Mb 3.5" D/Drives	£14.50 c/p	£2.50
Sony 9" Super Fine Pitch Trinitron RGB VDU	£35 c/p	12.50
AT Keyboards for IBM Compatibles	£7 c/p	3.50
12" Colour SVGA 800 x 600 NEC	£45.95 c/p	14
Marconi Inst = 2830 Multiplex Tester	£300	
Marconi Inst = Data Comms Tester	£385	
Marconi Inst = Digital Line Monitor	£350	
Marconi Inst = Digital Analyser	£375	
Farnell PSU 0-70V 0-5A/0-30V 0-10A	£245	
Siemens Data Line Analyser K1190	£375	
Avo AC/DC Breakdown/Ionisation Tester RM 215L1	£200	
Tektronix DAS 9100 Digital Analysis System	£175	
Tektronix 7CT 1N Curve Tracer	£295	
Tektronix 7A15A Amp	£150	
Tektronix 7511 Diff = Comp =	£100	
Tektronix 7A13	£140	
12 VAC 200 Watt Transformer	£15	
27 VAC 130A Transformer New	£18	
7 VAC 130A Transformer New	£18	
Acer Expansion Chassis (Box) for Notebook/Laptop etc. Contains 50W. PSU. Fan. 2x16 bit. 1x8 bit Slot. New & Boxed	£24.99	
Philips PM 3240. 50 Mhz. Scope D/Trace	£165	
Gould OS300 20 Mhz. Scope D/Trace	£145	
Leader LMV 181A AC Millivoltmeter	£145	
Racal Inst: 9915 UHF Freq: Meter 500Mhz	£100	
Racal Inst: 9916 UHF Freq: Counter 500Mhz	£145	
HP 8413A Phase Gain Ind:	£90	
Siemens Pattern Error Detector 140mbi/S	£175	
HP 7475 8 Pen Plotter RS 232	£55	
HP Colour Pro 8 Pen Plotter RS232	£75	
HP 7470A Plotter HPiB	£95	
Hand held microscope fibre optic	£185	

PLOTTERS · COMPUTERS · COMMUNICATIONS · PSU · VDU'S · VIDEO ·
FANS · TEST · CABLE · NETWORK · PRINTERS ·
DISK DRIVES ALWAYS IN STOCK. OVERSEA'S ENQ. WELCOME.
TELEPHONE ORDERS ACCEPTED.
C/P DETAILS PLEASE RING. ALL PRICES PLUS 17.5% VAT.

CIRCLE NO. 111 ON REPLY CARD

The MICRO MODULE
A NEW LOW COST controller
that gives you customisation
for as little as **£95** one off
+ VAT



For users of
PCs, 8051 &
68000

and that's just the half of it!..

FEATURES

- 16/32 bit 68307 CPU for fast operation
- Up to 1 Mbyte of EPROM space onboard
- Up to 512Kbyte SRAM space onboard
- 32 Kbyte SRAM fitted as standard
- RS232 serial with RS485 option
- MODBUS & other protocols supported
- Up to 22 digital I/O channels
- 2 timer/counter/match registers
- iC port or Mbus & Watch dog facilities
- Large Proto-typing area for user circuits
- Up to 5 chip selects available
- Program in C, C++, Modula-2 & Assembler
- Real Time multitasking Operating System
- OS9 or MINOS with free run time license option
- Manufacturing available even in low volumes
- A full range of other Controllers available

P.C. 'C' STARTER PACK AT ONLY £295 + VAT

The Micro Module will reduce development time for quick turnaround products/projects and with the P.C. 'C' Starter pack allow you to start coding your application immediately, all drivers and libraries are supplied as standard along with MINOS the real time operating system all ready to run from power on. The 'C' Starter pack includes: A Micro Module with 128 Kbyte SRAM, PSU, Cables, Manuals, C compiler, Debug monitor ROM, Terminal program, Downloader, a single copy of MINOS. Extensive example software, and free unlimited technical support all for £295 + VAT.

BMS

Cambridge Microprocessor
Systems Limited

Unit 17-18, Zone 'D', Chelmsford Road Ind. Est.,
Great Dunmow, Essex, U.K. CM6 1XG
Phone 01371 875644 Fax 01371 876077

CIRCLE NO. 113 ON REPLY CARD

12-bit analogue i/o via LPT

Although simple, Yongping Xia's LPT analogue interface resolves to 12 bits.

Equipped with a-to-d and d-to-a converters, a pc can perform many measurement and control functions. Figure 1 shows an easy way of providing 12-bit a-to-d and d-to-a conversion. Driven by the software below, the circuit interfaces with the pc through its printer port.

The MAX176 is a complete serial 12-bit a-to-d converter with a built-in track/hold circuit and a voltage reference. Two signals – clock and convert start – are needed to drive the chip. Once started, the a-to-d conversion result is sent out through the DATA pin in two's complement, high-to-low serial order. Analogue input is buffered by IC_{1B} with range of -5V to +5V. The MAX176 needs +5V and -15V power supplies and provides a -5V reference output.

The MAX543 is a 12-bit serial d-to-a converter. Its current output is converted to voltage by IC_{1A}. Required -5V reference is provided by a MAX176. Resistors R_{1,4} adjust the d-to-a converter offset and gain respectively. The d-to-a converter's output range is also -5V to +5V.

The a-to-d and d-to-a conversion procedures shown are in C. In this application, two printer port addresses (0x37c and 0x37d) are used. One is for output and the other input. Note that the base address may differ between computers. You should find details in your user guide.

The d-to-a conversion procedure converts 12-bit data in serial order and sends it to MAX543 through the printer port pin 5. Conversion data is stored in 'data out'. An output register named 'out' is used to map the base address printer port. The a-to-d conversion procedure generates

MAX176 required CL(oc)K and CONV(ersion start) signals through pins 2 and 3 of the printer port, reads serial data via printer port pin 15, and returns the reorganised a-to-d conversion result.

These procedures can be included in any C-based application program. If an a-to-d conversion is needed, call the a-to-d procedure and it will return the result. If a d-to-a conversion is required, simply call the d-to-a procedure and pass the data to the procedure. Conversion time depends on the type of pc is used. It takes around 75µs for a-to-d and 68µs for d-to-a on a 50MHz 486 machine.

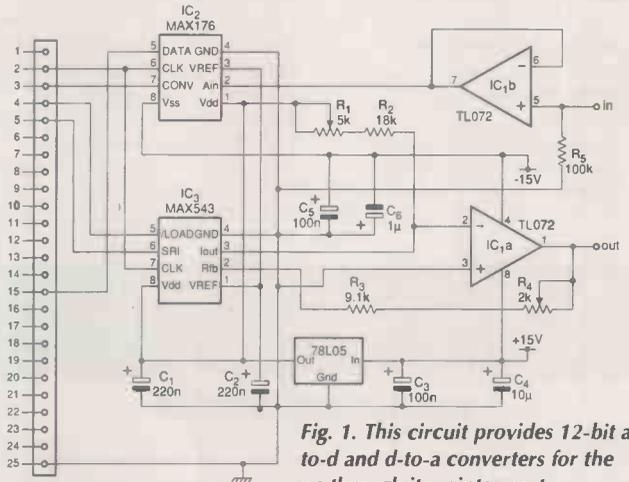


Fig. 1. This circuit provides 12-bit a-to-d and d-to-a converters for the pc through its printer port.

Assembly language for reading and writing the analogue data converters via the pc's LPT port.

```
#include <stdio.h>
#include <dos.h>
#include <conio.h>
#define OUT_PORT 0x37c /* base address */
#define IN_PORT 0x37d /* base address + 1 */
#define CLOCK_HIGH 0x01 /* set clock bit high */
#define CLOCK_LOW 0xfe /* set clock bit low */
#define CONVST_HIGH 0x02 /* set start conversion bit high */
#define CONVST_LOW 0xfd /* set start conversion bit low */
#define LOAD_HIGH 0x04 /* set load bit high */
#define LOAD_LOW 0xfb /* set load bit low */
#define DAC_HIGH 0x08 /* set data out bit high */
#define DAC_LOW 0xf7 /* set data out bit low */
void dac(int data out);
int adc(void);

/* D-to-A conversion procedure */
void dac(int data out)
{
    int i, out;
    out = 0x04; /* set DAC's LOAD to be high */
    for (i=0; i<12; i++) /* send out 12-bit DAC data */
    {
        if (data out < 0x800) /* if bit 11 is low, */
        {
            out = out & DAC_LOW; /* set output bit = 0 and */
            data out *= 2; /* double DAC data */
        }
        else /* if bit 11 is high, */
        {
            out = out | DAC_HIGH; /* set output bit = 1 and */
            data out = (data out - 0x800) * 2; /* double DAC data after set */
        }
        /* bit 11 to be 0 */
        outportb(OUT_PORT, out); /* send out */
        out = out | CLOCK_HIGH; /* turn CLOCK high */
        outportb(OUT_PORT, out); /* send out */
        out = out & CLOCK_LOW; /* turn CLOCK low */
        outportb(OUT_PORT, out); /* send out */
    }
}
```

```
out = out & LOAD_LOW; /* turn LOAD low */
outportb(OUT_PORT, out); /* send out */
out = out | LOAD_HIGH; /* turn LOAD high */
outportb(OUT_PORT, out); /* send out */
}

/* A-to-D conversion procedure */
int adc(void)
{
    int i, data, out;
    data=0; /* clean data */
    out = 0x04 | CLOCK_HIGH; /* set CLOCK and DAC's LOAD high */
    outportb(OUT_PORT, out); /* send out */
    out = out & CLOCK_LOW; /* turn CLOCK low */
    outportb(OUT_PORT, out); /* send out */
    out = out | CLOCK_HIGH; /* turn CLOCK high */
    outportb(OUT_PORT, out); /* send out */
    out = out & CONVST_HIGH; /* turn A/D CONVERT START high */
    outportb(OUT_PORT, out); /* send out */
    out = out & CLOCK_LOW; /* turn CLOCK low */
    outportb(OUT_PORT, out); /* send out */
    out = out & CONVST_LOW; /* turn A/D CONVERT START low */
    outportb(OUT_PORT, out); /* send out */
    out = out | CLOCK_HIGH; /* turn CLOCK high */
    outportb(OUT_PORT, out); /* send out */
    out = out & CLOCK_LOW; /* turn CLOCK low */
    outportb(OUT_PORT, out); /* send out */
    for (i=0; i<12; i++) /* get 12-bit conversion data */
    {
        out = out | iCLOCK_HIGH; /* CLOCK high */
        outportb(OUT_PORT, out); /* send out */
        data = data * 2 + (inportb(IN_PORT) & 0x08) / 8; /* update */
        out = out & CLOCK_LOW; /* turn CLOCK low */
        outportb(OUT_PORT, out); /* send out */
    }
    return (data); /* return A/D conversion result */
}

main()
{
    /* your application */
}
```

Take a look inside the ELECTROMAIL catalogue and you're in for a surprise. If you're looking for Electronic Components, Electrical Equipment or Mechanical Tools, with over 60,000 product lines, there's a whole galaxy of choice.

Electromail is one of Europe's largest stockists dedicated to the Home Based Professional and Electronics Enthusiast.

The fully comprehensive catalogue provides detailed descriptions, full technical information and (in most cases) colour pictures of each product to make selection easy.

Our orderline staff are light years ahead in friendly and efficient service and above all, they're committed to helping you find exactly what you need.

You'll find our despatch just as advanced, with a nominal p&p charge and range of delivery options to suit, even a Sonic Screwdriver* won't take an age to materialise.

Simply telephone or fax your order anytime between 8.00am and 8.00pm Monday to Friday Earthtime.

So - whatever your current project, anywhere in the universe, save yourself time, call Electromail.


* Not available on this planet

ELECTROMAIL

THE SERVICE FOR HOME BASED PROFESSIONALS
AND ELECTRONICS ENTHUSIASTS

Electromail P.O. Box 33, Corby, Northants, NN17 9EL. Internet <http://www.rs-components.com/rs/>

WITH OVER 60,000 PRODUCTS INSIDE

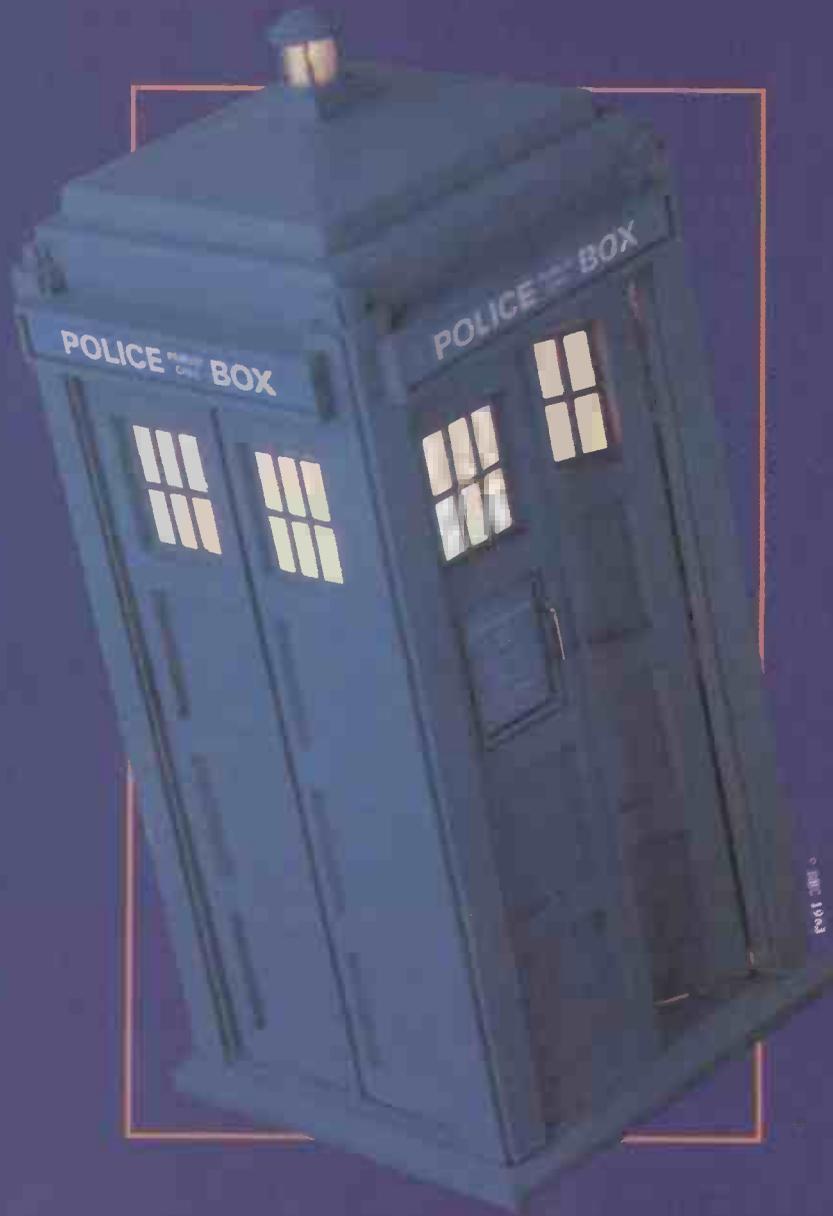

YOU'RE BOUND TO SAVE TIME

Telephone 01536 204 555
or Fax 01536 405 555.



Cards accepted when placing an order.

CIRCLE NO. 114 ON REPLY CARD

751

NOW, THE BATTLE IS OVER

ULTIBOARD



ULTIBOARD

BUNDLED WITH  **SPECCTRA**
SHAPE BASED AUTOROUTER

ULTIboard's interactive strength has always been the major selection criterion of professional Printed Circuit Board designers. Now that every ULTIboard Designer system will be supplied with a SPECCTRA SP4 Autorouter, ULTIboard designers now get the best of both worlds.

All ULTIboard Designer Users with valid update subscription got a MAINTENANCE UPGRADE with the SPECCTRA SP4 (4 signal layers + power/ground layers) Shape based Autorouter. This shows that ULTIimate Technology is *the* PCB-Design Tool vendor that *really* cares for their customers!

**THE ULTIMATE
SPECIAL OFFER**

**ULTIboard Entry Designer* £ 1295 (excl. VAT) will now
be supplied with SPECCTRA Shape Based Autorouter**

***free Upgrade with EMC-EXPERT mid 1996 (list price at release £ 1875)**

CIRCLE NO. 115 ON REPLY CARD

ULTIMATE
TECHNOLOGY

Corporate Headquarters:
Energiestraat 36 • 1411 AT Naarden
The Netherlands

tel.: (+31) 35 - 694444
fax: (+31) 35 - 6943345

UK/Ireland Sales-Office:
2 Bacchus House • Calleva Park
Aldermaston Berkshire • RG7 4QW

tel.: 01734 - 812030
fax: 01734 - 815323

SUBSCRIBE TODAY

And Electronics World will help you keep the leading edge

EVERY MONTH
- the best writing on
Electronics design applications

ELECTRONICS WORLD
INCORPORATING WIRELESS WORLD



1 Year £30 UK, £43 Europe, £52 Row

2 Years SAVE 25% £45 UK, £65 Europe, £75 Row

Phone: +44 01444 445566, Fax (+44) 01444 445447

SUBSCRIPTION FORM

YES, I WOULD LIKE TO SUBSCRIBE TO ELECTRONICS WORLD

Name _____
Job Title _____
Company Name _____
Address _____

Postcode _____ Country _____
Telephone _____ Fax _____

PAYMENT DETAILS

1 year £30 UK £43 Europe £52 Rest of World
 2 years £45 UK £65 Europe £75 Rest of World
 Please invoice me/my company. Purchase Order N° _____
 I enclose cheque made payable to Electronics World
 Please charge my Visa/Access/Amex/Mastercard
□□□□□□□□□□□□□□□□

Expiry date

Signature


Please tick box if you do not wish to receive promotions from other companies.

UK RETURN ADDRESS: Electronics World, Freepost CN 2619, Reed Business Publishing, 9th Floor, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5BR.
REST OF WORLD: ELECTRONICS WORLD, Reed Business Publishing, 9th Floor, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS, UK.

753

022

Thermal dynamics in audio power

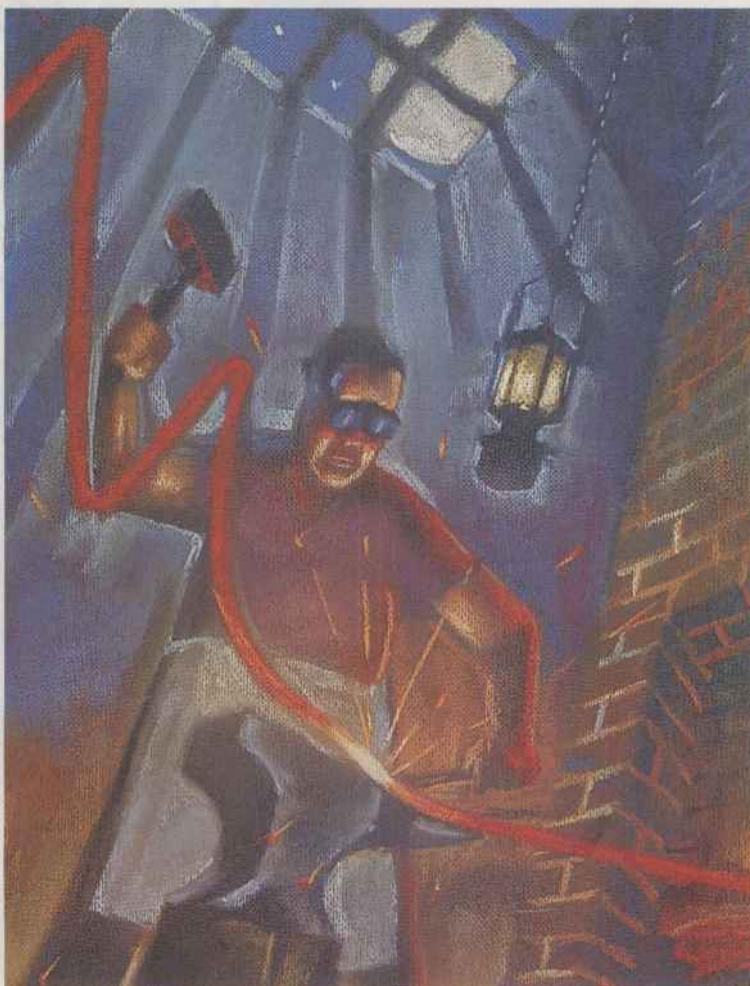

Douglas Self explains how to achieve lower power amplifier distortion by improving bias accuracy.

The first part of this series demonstrated how quite complex problems in thermal dynamics could be simply solved by using electrical analogues and a circuit simulator; the second part showed how this approach could be used to produce techniques for power amplifier thermal compensation that were much faster and more accurate than the

conventional methods. These methods explicitly assumed it would be possible to design a bias-generator with a temperature coefficient either higher or lower than the standard result¹.

Fig. 1 shows two versions of the classical V_{be} -multiplier bias-generator. Each has its lower rail grounded to simplify the results. The first (Fig. 1a) is set up for an emitter-follower output stage, where the voltage V_{bias} is $(4 \times V_{be}) + V_q$, which comes to +2.93V. Voltage V_q is the small quiescent voltage across the emitter resistors R_e ; it is this quantity that must be kept constant, rather than the quiescent current, as is usually assumed. The optimal V_q for an emitter-follower stage is about 50mV.

The second (Fig. 1b) is suitable for a complementary-feedback-pair output stage, for which the required V_{bias} is less at $(2 \times V_{be}) + V_q$, or about 1.30V. Note that the optimal V_q is smaller for the complementary-feedback pair, at about 5mV.

It is assumed that V_{bias} is trimmed by varying R_2 , which will in practice be a preset in series with an end-stop resistor that limits the maximum V_{bias} setting. This is important, because a preset normally fails by the wiper becoming disconnected, and if it is in the R_2 position the bias will default to minimum. In the R_1 position an open-circuit preset gives maximum bias, which may damage the output stage.

Since the emitter-follower version of the bias generator has a higher V_{bias} , there must be a larger V_{be} -multiplication factor to generate it, and this is reflected in the higher temperature coefficient, see Table 1.

Raising temperature coefficient

There are many approaches possible, but the problem is complicated because the bias generator may have to work within two rails only 1.3V apart. Additional circuitry outside this limit can be accommodated by bootstrapping, as in the Trimodal amplifier biasing system², but this adds complexity.

Often the thermal losses to the temperature

Table 1. The emitter follower needs a larger V_{be} multiplier.

	V_{bias}	$R_1(\Omega)$	$R_2(\Omega)$	$R_3(\Omega)$	Coeff.(mV/°C)
Emitter follower	2.93	120	470	22	-9.3
Complementary feedback pair	1.30	470	470	150	-3.6

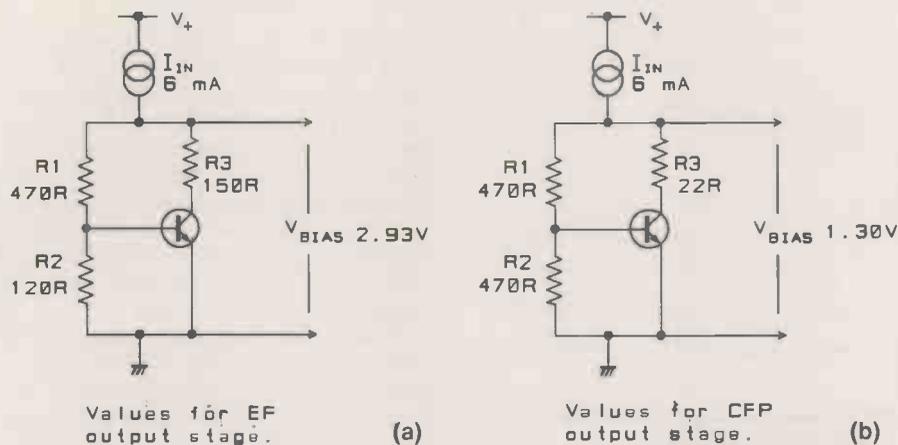


Fig. 1. Classical V_{be} -multiplier bias generator. Two versions are shown, for biasing emitter follower (at 1a) and complementary-feedback-pair output stages (at 1b). The emitter-follower requires more than twice the bias voltage for optimal crossover performance.

sensor are the major source of steady-state V_{bias} error, and to reduce this a tempco is required that is larger than the standard value given by: ' V_{be} -multiplication factor times $-2mV/^\circ C$ '.

A simple new idea is shown in Fig. 2. The aim is to increase the multiplication factor – and hence the negative temperature coefficient – required to give the same V_{bias} . The diagram shows a voltage source V_1 inserted in the R_2 arm. To keep V_{bias} the same, the value of R_2 must be reduced, and since the multiplication factor $(R_1+R_2)/R_2$ is increased, the tempco is similarly increased.

In Table 2, a complementary-feedback-pair bias circuit has its temperature coefficient varied by increasing V_1 in 100mV steps; in each case the value of R_2 is then reduced to bring V_{bias} back to the desired value.

A practical circuit is shown in Fig. 3, using a 2.56V band-gap reference to generate the extra voltage across R_4 . This has to work outside the bias generator rails, so its power-feed resistors R_7, R_8 are bootstrapped by C from the amplifier output².

Ambient temperature changes

Power amplifiers must be reasonably immune

Table 2. Complementary feedback pair bias data, showing increasing temperature coefficient.

V_1 mV	V_{bias} V	R_2 Ohms	Coeff $mV/^\circ C$
0	1.287	470	-3.6
100	1.304	390	-4.0
200	1.287	330	-4.4
300	1.286	260	-5.0
400	1.285	190	-6.9

to ambient temperature changes, as well as changes due to dissipation in power devices. The standard compensation system does this pretty well, as the V_{be} -multiplication factor is inherently almost the same as the number of junctions being biased.

This is no longer true if the tempco is significantly modified. Ideally we require a bias generator that has one increased tempco for power-device temperature changes only, and another standard temperature coefficient for ambient changes affecting all components.

One approach to this is Fig. 4, where V_1 is derived via R_6, R_4 from a silicon diode rather than a bandgap reference, giving a voltage

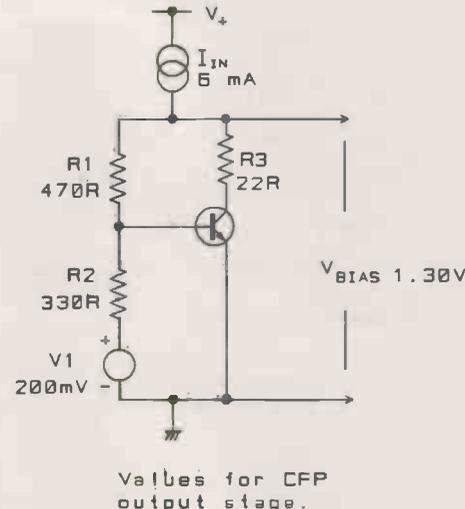


Fig. 2. Theoretical basis of V_{be} multiplier with increased tempco. Adding voltage-source V_1 means the voltage-multiplication factor must be increased to get the same V_{bias} . The temperature coefficient is therefore also increased, here to $-4.4mV/^\circ C$.

Table 3. Reducing temperature coefficient.

V_1 mV	V_{bias} V	R_1 Ω	Coeff. $mV/^\circ C$
0	1.287	470	-3.6
100	1.304	390	-3.3
200	1.287	330	-3.1
300	1.286	260	-2.8

reducing with temperature. The tempco for temperature changes to Q_1 only is $-4.0mV/^\circ C$, while the tempco for global temperature changes to both Q_1 and D_1 is lower at $-3.3mV/^\circ C$.

Lowering temperature coefficient

In Part 1¹, I showed that an emitter-follower output stage can show 'thermal gain' in that the changes in V_q make it appear that the tempco of the V_{bias} generator is higher than it really is. This is because the bias generator is set up to

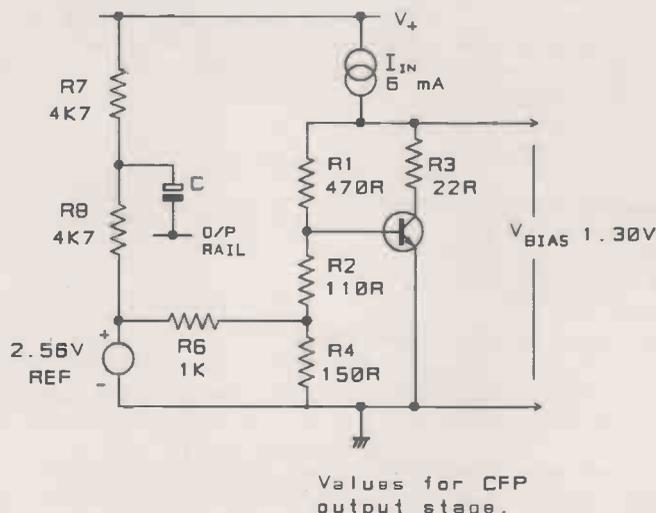


Fig. 3. Shows a practical version of a V_{be} multiplier with increased tempco. The extra voltage source is derived from the bandgap reference by R_6, R_4 , and the tempco is increased to $-5.3mV/^\circ C$

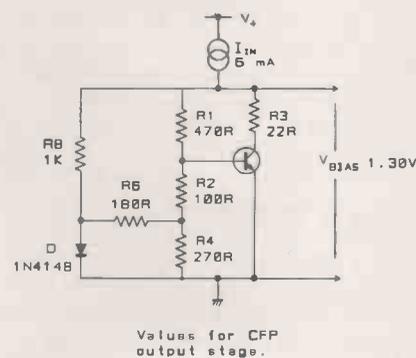


Fig. 4. Practical V_{be} multiplier with increased tempco, and also improved correction for ambient temperature changes, by using D_1 to derive the extra voltage.

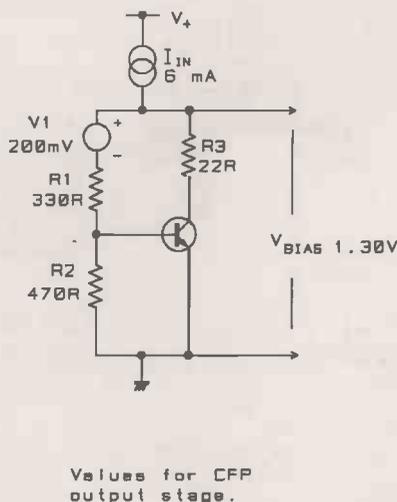


Fig. 5. The principle of a V_{be} -multiplier with reduced temperature coefficient. The values shown give $-3.1\text{mV}/^\circ\text{C}$.

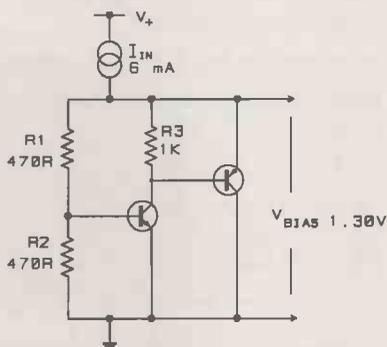


Fig. 7. Circuit of a two-transistor V_{be} -multiplier. The increased loop gain holds V_{bias} more constant against current changes.

compensate for four base-emitter junctions, but in the emitter-follower output configuration the drivers have a roughly constant power dissipation with changing output power, and do not change much in junction temperature.

The full benefit of the temperature coefficient is thus felt by the output junctions, and if the sensor is placed on the power device itself rather than the main heatsink, to reduce thermal delay, then the amplifier is likely to be seriously over-compensated for temperature. In other words, after a burst of power V_q will become too low rather than too high. We now need a V_{bias} generator with a lower temperature coefficient than the standard circuit.

The principle is exactly analogous to the method of increasing the temperature coefficient. In Fig. 5, a voltage source is inserted in the upper leg of potential divider R_1, R_2 ; the V_{be} -multiplication factor is reduced, and so therefore is the temperature coefficient.

Table 3 shows how this works as V_1 is increased in 100mV steps. Resistor R_1 has been varied to keep V_{bias} constant, in order to demonstrate the symmetry of resistor values with Table 2; in reality R_2 would be the variable element, for safety reasons described above.

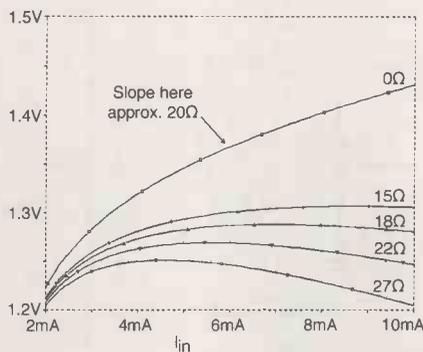


Fig. 6. Simulation results for standard V_{be} multiplier, showing how current-compensation resistor R_3 is chosen. When R_3 is fitted, V_{bias} peaks very broadly at a particular current, giving much smaller variation with current.

Fig. 8. The two-transistor configuration gives a consistently lower series resistance, and hence V_{bias} variation with current, compared with the standard version without R_3 .

Current compensation

Both bias-generators in Fig. 1 are fitted with a current-compensation resistor R_3 . The V_{be} -multiplier is a very simple shunt regulator, with a low loop gain, and hence a significant series resistance. Resistor R_3 is therefore added to give first-order cancellation of V_{bias} variations caused by current changes, by subtracting a correction voltage proportional to this current.

Rather than complete cancellation, this gives a peaking of the output voltage at a specified current, so that current changes around this peak value cause only minor voltage variations. This peaking philosophy is widely used in IC bias circuitry.

Resistor R_3 should never be omitted, as without it mains voltage fluctuations can seriously affect V_q . Table 1 shows that the optimal value for peaking at 6mA depends strongly on the V_{be} multiplication factor.

Figure 6 shows variation of V_{bias} with current for different values of R_3 . The slope of the uncompensated, $R_3=0$, curve at 6mA is $\approx 20\Omega$. This linear term is cancelled by making R_3 18 or 22 Ω .

Current through the bias generator varies because the voltage amplifier current-source is not a perfect circuit element. Biasing it with the

usual pair of silicon diodes is not sufficient to make it wholly immune to supply-rail variations. I measured a generic amplifier (essentially the original Class-B Blameless design) and varied the incoming mains from 212V to 263V, a range of 20%. This, in these uncertain times, is perfectly plausible for a power amplifier travelling around Europe. The voltage-amplifier stage current-source output varied from 9.38mA to 10.12mA, which is a 7.3% range.

Thanks to the current-compensating resistor in the bias generator, the resulting change in quiescent voltage V_q across the two R_e 's is only from 1.1mV (264V mains) to 1.5mV (212V mains). This is a very small absolute change of 0.4mV, well within the V_q tolerance bands. The ratio of change is greater, because V_{bias} has had a large fixed quantity (the devices' V_{be}) subtracted from it, so the residue varies much more. Variation in V_q could best be further suppressed by making the current source more stable against rail variations.

The finite ability of even the current-compensated bias generator to cope with changing standing current makes a bootstrap voltage-amplifier stage collector load much less attractive than the current-source version; from the above data, V_q variations will be at least three times greater.

A wholly different approach to reducing V_{bias} variations increases the loop gain in the V_{be} -multiplier. Fig. 7 shows the circuit of a two-transistor version that reduces the basic resistance slope from 20 to 1.7 Ω . The advantage is that V_{bias} variations will be smaller for all values of voltage-amplifier stage current, and no optimisation of a resistor value is required. The drawback is slightly greater complexity in an area where reliability is vital. Figure 8 compares the two-transistor configuration with the standard version, without R_3 .

Conclusion

This final part of the 'Thermal Dynamics' series shows how to build simple V_{bias} generators with temperature coefficients ranging from -2.5 to $-6.9\text{mV}/^\circ\text{C}$.

This, in combination with the techniques described in the earlier parts of this series, should allow you to design of Class-B amplifiers with greater bias accuracy, and therefore lower crossover distortion. ■

References

1. D. Self, 'Thermal Dynamics In Audio Power' *Electronics World*, May 1996, p411.
2. D. Self, 'Trimodal Audio Power' Part 2 *Electronics World*, July 1995, p585.
3. D. Self, 'Distortion In Power Amplifiers, Part 7' *Electronics World*, Feb 1994, p139 (Peaking effect of current-compensation).

Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

LOW COST PC's -

SPECIAL BUY 'AT 286'

40Mb HD + 3Mb Ram



LIMITED QUANTITY only of these 12MHz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!
Order as HIGRADE 286 **ONLY £129.00 (E)**

Optional Fitted extras: VGA graphics card	£29.00
1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb)	£19.95
Wordperfect 6.0 for Dos - when 3 1/2" FDD option ordered	£22.50
NE2000 Ethernet (thick, thin or twisted) network card	£29.00

LOW COST 486DX-33 SYSTEM

Limited quantity of this 2nd user, superb small size desktop unit. Fully featured with standard simm connectors 30 & 72 pin. Supplied with keyboard, 4 Mb of RAM, SVGA monitor output, 256k cache and integral 120 Mb IDE drive with single 1.44 Mb 3.5" floppy disk drive. Fully tested and guaranteed. Fully expandable
Many other options available - call for details. **£399.00 (E)**

FLOPPY DISK DRIVES 3 1/2" - 8"

5 1/4" or 3 1/2" from only £18.95!

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from other brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported on your PC).

3 1/2" Panasonic JU363/4 720K or equivalent RFE	£24.95(B)
3 1/2" Mitsubishi MF35C-L 1.4 Meg. Laptops only	£25.95(B)
3 1/2" Mitsubishi MF35C-D 1.4 Meg. Non laptop	£18.95(B)
5 1/4" Teac FD-55GR 1.2 Meg (for IBM pc's) RFE	£18.95(B)
5 1/4" Teac FD-55F-03-U 720K 40/80 (for PC's etc) RFE	£22.95(B)
5 1/4" BRAND NEW Mitsubishi MF501B 360K	£22.95(B)
Table top case with integral PSU for HH 5 1/4" Floppy or HD	£29.95(B)
8" Shugart 800/801 8" SS refurbished & tested	£195.00(E)
8" Shugart 810 8" SS HH Brand New	£195.00(E)
8" Shugart 851 8" double sided refurbished & tested	£250.00(E)
Mitsubishi M2894-63 8" double sided NEW	£275.00(E)
Mitsubishi M2896-63 8" DS slimline NEW	£285.00(E)
Dual 8" cased drives with integral power supply 2 Mb	£499.00(E)

HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte drive with industry standard SMD interface, replaces Fujitsu equivalent model. Full manual. Only £299.00 or 2 for £525.00 (E)

3 1/2" FUJII FK-309-26 20mb MFM I/F RFE	£59.95(C)
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv) RFE	£59.95(C)
3 1/2" CONNER CP3044 40mb IDE I/F (or equiv) RFE	£69.00(C)
3 1/2" RODIME R03057S 45mb SCSI I/F (Mac & Acorn)	£69.00(C)
3 1/2" WESTERN DIGITAL 850mb IDE I/F Brand New	£185.00(C)
5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv) RFE	£49.95(C)
5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb	£69.95(C)
5 1/4" CDC 94206-51 40mb HH MFM I/F RFE tested	£69.95(C)
5 1/4" HP 9754B 850 Mb SCSI RFE tested	£89.00(C)
5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested	£195.00(C)
8" FUJITSU M2322K 160Mb SMD I/F RFE tested	£195.00(E)

Hard disc controllers for MFM, IDE, SCSI, RLL etc. from £16.95

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

TELEBOX ST for composite video input type monitors	£36.95
TELEBOX STL as ST but fitted with integral speaker	£39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner	£69.95

For overseas PAL versions state 5.5 or 6 MHz sound specification. *For cable / hyperband reception Telebox MB should be connected to a cable type service. Shipping code on all Teleboxes is (B)

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock Call for info / list.

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK

6,000,000 items EX STOCK

For MAJOR SAVINGS - CALL FOR SEMICONDUCTOR HOTLIST

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see - At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched laeplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, supplied in EXCEL-

LENT little used condition. Order as MITS-SVGA
Tilt & Swivel Base £4.75
VGA cable for IBM PC included.
External cables for other types of computers CALL

As New - Used on film set for 1 week only!!
15" 0.28 SVGA 1024 x 768 res. colour monitors.
Swivel & tilt etc. Full 90 day guarantee. £145.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors.
Good SH condition - from £299 - CALL for Info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio direct amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed
Dimensions: W14" x H12 3/4" x 15 1/2" D.
Only £95 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered.
Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.
Only £125 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

SPECIAL INTEREST ITEMS

MITS. FA3445ETKL 14" Industrial spec SVGA monitors 2Kw to 400 kw - 400 Hz 3 phase power sources - ex stock	£245
IBM 8230 Type 1, Token ring base unit driver	£950
IBM 53F5501 Token Ring ICS 20 port lobe modules	£750
IBM MAU Token ring distribution panel 822B-23-5050N	£95
AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE	£550
Trend DSA 274 Data Analyser with G703(2M) 64 I/O	£6500
Marconi 6310 Programmable 2 to 22 GHz sweep generator	£3750
HP1650B Logic Analyser	£1800
HP3781A Pattern generator & HP3782A Error Detector	£950
HP APOLLO RX700 system units	£1800
HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts	£175
HP3081A Industria workstation c/w Barcode swipe reader	£675
HP6264 Rack mount variable 0-20V @ 20A metered PSU	£1850
HP54121A DC 2 to 22 GHz four channel test set	£650
HP7580A A1 8 pen HPGL high speed drum plotter	£650
EG+G Brookdale 95035C Precision lock in amp	£1425
View Eng. Mod 1200 computerised inspection system	£1425
Link Dynamics 2Kw programmable vibration test system	£3750
Computer controlled 1056 x 560 mm X Y table & controller	£9500
Kelley 590 CV capacitor / voltage recorder system	£1200
Racal ICR40 dual channel video recorder system	£1200
Fiskers 45KVA 3 ph On Line UPS - cleaning system	£2200
ICI R5030UV34 Cleanline ultrasonic cleaning Dec. 1995	£1200
Mann Tally MT645 High speed line printer	£1995
Intel 320-05 A0 4 pen HPGL fast drum plotters	£750
Motorola VME Bus Boards & Components List. SAE / CALL	£300
Trio 0-18 vdc linear, metered 30 amp bench PSU. New	£1950
Fujitsu M3041R 600 LPM bench printer	£1250
Fujitsu M3041D 600 LPM printer with network interface	£3750
Perkin Elmer 2998 infrared spectrophotometer	£950
VG Electronics 1035 TELETEXT Decoding Margin Meter	£1995
Andrews LARGE 3 1/2" Satellite Dish + mount (For Voyager)	£750
Sekonic SD 150H 18 channel digital Hybrid chart recorder	£485
TAYLOR HOBSON Tallysnu amplifier / recorder	£750
System Video 1152 PAL waveform monitor	£300
Test Lab - 2 mtr square quietised acoustic test cabinets	£650
Kenwood 9601 PAL Vectorscope - NEW	£650

Please call for further details on the above items



19" RACK CABINETS

Superb quality 6 foot 40U

Virtually New, Ultra Smart

Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:

OPT Rack 1 Complete with removable side panels	£335.00 (G)
OPT Rack 2 Rack, Less side panels	£225.00 (G)

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extra available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W)
Sold at LESS than a third of makers price !!

A superb buy at only £195.00 (G)

Over 1000 racks - 19" 22" & 24" wide

3 to 44 U high. Available from stock !!

Call with your requirements.

TOUCH SCREEN SYSTEM

The ultimate in 'Touch Screen Technology' made by the experts - MicroTouch - but sold at a price below cost !! System consists of a flat translucent glass laminated panel measuring 29.5 x 23.5 cm connected to an electronic controller PCB. The controller produces a standard serial RS232 or TTL output which continuously gives simple serial data containing positional X & Y co-ordinates as to where a finger is touching the panel - as the finger moves, the data instantly changes. The X & Y information is given at an incredible matrix resolution of 1024 x 1024 positions over the entire screen size !! A host of available translation software enables direct connection to a PC for a myriad of applications including: control panels, pointing devices, POS systems, controllers for the disabled or computer un-trained etc etc. Imagine using your finger with 'Windows', instead of a mouse !! (A driver is indeed available!) The applications for this amazing product are only limited by your imagination!! Complete system including Controller, Power Supply and Data supplied at an incredible price of only: **£145.00 (B)**
Full MICROTOUCH software support pack and manuals for IBM compatible PC's £29.95 RFE - Tested

LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully compatible for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. **£59.95(A1)**
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data.
Order as: XT RAM UG. 256k. £34.95 or 512k £39.95 (A1)

SIMM SPECIALS

1 MB x 9 SIMM 9 chip 120ns	Only £16.50 (A1)
1 MB x 9 SIMM 3 chip 80 ns	£19.50 or 70ns £22.95 (A1)
1 MB x 9 SIMM 9 chip 80 ns	£21.50 or 70ns £23.75 (A1)
4 MB 70 ns 72 pin SIMM - with parity	Only £59.00 (A1)
INTEL 486-DX33 CPU	£55.00 INTEL 486-DX66 CPU £69.00 (A1)

FULL RANGE OF CO-PROCESSOR'S EX STOCK - CALL FOR LIST

FANS & BLOWERS

EPSON D0412 40x40x20 mm 12v DC	£7.95 / £65
PAPST Type 612 60x60x25 mm 12v DC	£8.95 / £75
MITSUBISHI MMF-D6D12DL 60x60x25 mm 12v DC	£4.95 / £42
MITSUBISHI MMF-08C12DM 80x80x25 mm 12v DC	£5.25 / £49
MITSUBISHI MMF-09B12DH 92x92x25 mm 12v DC	£5.95 / £53
PANCAKE 12-3.5 92x92x18 mm 12v DC	£7.95 / £69
EX-EQUIP AC fans. All TESTED 120 x 120 x 38 mm specify 110 or 240 V £6.95. 80 x 80 x 38 mm specify 110 or 240 V £5.95	
IMHOF B26 1900 rack mnt 3U x 19" Blower 110/240v NEW	£79.95

Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL

Issue 13 of Display News now available - send large SAE - PACKED with bargains!

display
-ELECTRONICS-

ALL MAIL & OFFICES
Open Mon-Fri 9.00-5.30
Dept WW. 32 Biggin Way
Upper Norwood
LONDON SE19 3XF

LONDON SHOP
Open Mon - Sat 9.00 - 5.30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
N. Thornton Heath & Selhurst Park SR Rail Stations

NEW DISTEL©
The Original
FREE On line Database
Info on 20,000 + stock items!
RETURNING SOON!

ALL ENQUIRIES
0181 679 4414
FAX 0181 679 1927

SWITCH MASTER VISA EST 25 YEARS

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. Scotland surcharge CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to charge prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1996. E & O E. 066

A rationalised *phono preamplifier*

Simon Bateson's RIAA preamplifier is economical and offers benefits over existing designs.

A great number of phono preamplifier designs have been published over the years. Perhaps this is because the subject can span any realisation between the very cheap and the outrageously expensive, or because there are interesting design features hidden within an apparently simple function.

One trend was the preoccupation in the early 1980s with low noise and RIAA accuracy, another was the move from series to shunt feedback, widely promoted by John Linsley-Hood.

John has published several excellent reviews

and designs of amplifiers and preamplifiers and it will be clear that the circuitry described here is but a rearrangement of his work. However there are a couple of worthwhile advantages in this configuration. I am not about to launch into a defence of vinyl discs, but I do have a number of records and this preamp seems to make the best of them.

Circuit elements

Figures 1 & 2 are the design's block diagram and circuit. The first stage is a straightforward dc-coupled amplifier with a stage gain of 21dB. This is followed directly by a third-order Butterworth rumble filter based on a standard equal value Sallen-Key circuit with a gain of 6dB. The filter is in circuit permanently. I have large, accurate speakers, namely ATC *SCM50A* active monitors, and it is sad to see the woofer wobbling about without the filter. After some experimentation the I set the turnover frequency at 19Hz.

The third part of the filter is formed by C_4 and R_9 which feed the RIAA equalisation stage. Although this is a shunt feedback stage,

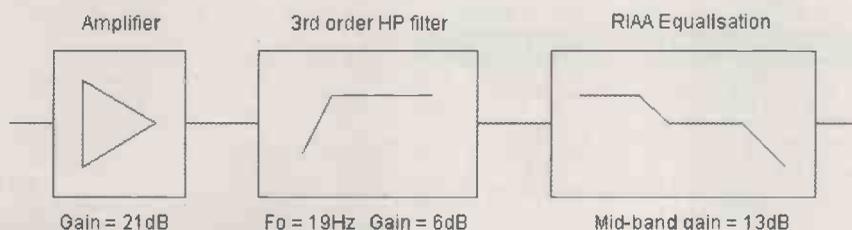


Fig. 1. There are no electrolytic capacitors in the signal path of the preamp and its noise is low.

Advantages of this RIAA preamplifier configuration

The unusual aspect of this design is the rearrangement of conventional circuit blocks so that the rumble filter appears before the RIAA equalisation. Several advantages accrue from this arrangement:

- No electrolytic capacitors appear in the signal path and the low-frequency characteristic is closely defined. Additionally, since there are no high-value capacitors to charge, the circuit settles almost immediately on switch-on.
- Large low-frequency rumble signals never reach the RIAA stage so do not compromise headroom. The mid-band gain is 40dB giving an input clip point of about 130mV with $\pm 15V$ supplies. In any case, it is a trivial matter to adjust the gain of IC_1 to suit whatever cartridge is in use, including moving coil types.
- The rumble filter is not a configuration subject to excess noise due to high impedances, since the capacitors C_2 and C_3 present a low impedance at high frequencies. $1/f$ noise from the op-amp is reduced due to the high-pass characteristic of C_4/R_9 . Meanwhile, ordinary

amplifier noise is reduced because the filter is followed by the low-pass RIAA stage.

- The input amplifier does not suffer a high dc offset due to mismatched input terminal resistances since the dc cartridge resistance is fairly close to that of R_3 and the gain is low. Therefore there is no need for a high value electrolytic in series with R_3 , or in series with the input. I do not believe that a minute bias current passing through the cartridge causes a problem although this might upset owners of £3000 handcrafted banana wood and platinum specimens.

DC feedback resistance of the RIAA stage is fairly high, at 100k Ω , so although the overall stage dc gain is zero due to C_4 it is better to use a fet op-amp such as the excellent *OPA2604*. Under these conditions there is no significant output offset voltage so the output coupling capacitor is not needed. The RIAA stage needs to achieve quite a high maximum gain, but only at low frequencies where, of course, the op-amp has the greatest open-loop gain available.

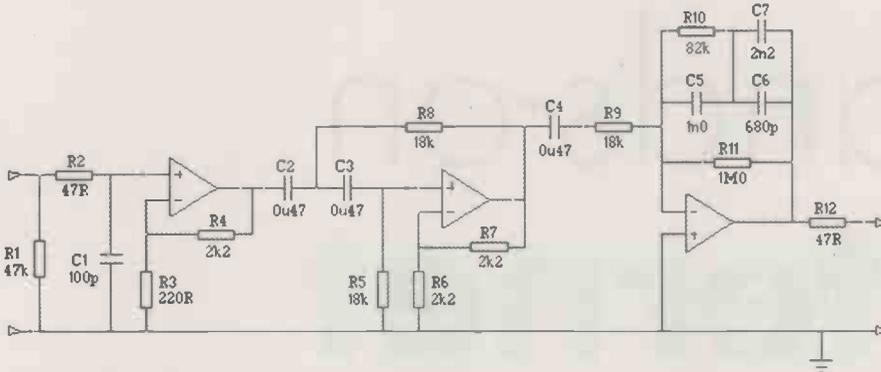


Fig. 2. The unusual aspect of this RIAA preamplifier is the rearrangement of conventional circuit blocks so that rumble filtering appears before RIAA equalisation.

it operates at a high signal level. As a result, small-value capacitors can be used in a relatively high-impedance network without any noise penalty. This is an inverting configuration. If absolute phase is considered important, it is a matter of moments to reverse the phono cartridge connections. Concerning component choice; the rumble filter capacitors should be the 5%


tolerance miniature polyester film types (available from RS), while the RIAA network uses cheap and accurate Philips 1% polyester types. Using integrated operational amplifiers such as the NE5532, the circuit is easily constructed on a small pcb, the layout of which is available from the editorial office. I recommend this pcb as carefully laid out and tested. I suspect poor pcb layout is responsible for far

more under-performing equipment than is popularly thought. Details to note are that low-value resistors are provided at the input and output to ensure stability with capacitive loads, while a single electrolytic is placed across the supply rails close to IC₁. High-performance op-amps do not take kindly to poor power supply decoupling and will oscillate at several megahertz to vent their feelings.

In summary
When the configuration first came to mind, my satisfaction at its economy and effectiveness was a little dampened by the thought that it came to mind about twenty years too late. Still, it probably won't be the final RIAA design to be published. There are a few possibilities which come to mind, such as using an SSM2015 differential amplifier for the first stage. This would offer slightly lower noise along with zero offset current through the cartridge and the usual benefits of balanced operation – which are inherently available from the cartridge if you rearrange the turntable wiring. Its surprising that balanced operation never came into fashion. You could use discrete instrumentation amplifiers and military grade capacitors. ■

Thoughts on power supply decoupling



Power rails should not be decoupled to the local earth with the usual pair of large electrolytics. Decoupling is a frequently misunderstood subject and the heavy-handed application of capacitors actually couples power rail disturbances into the ground rail. The major problem with all practical circuit layout is that the ground line is simultaneously an input signal reference point, an output signal reference point and a power ground. When the op-amp delivers transient current into a load, the current is drawn from the nearest source – the decoupling capacitor – hence output current flows in the local earth line. This line acts as a reference for the input signal and if badly laid out the earth current couples back to the op-amp inputs, inducing instability or even oscillation. One mode of coupling back is shown above, right, where the earth connections are simply in the wrong order. A good way to induce op-amp hysteresis is the pcb layout below right. Similar comments apply to non-inverting configurations. The better the op-amp, the more important it is to get the earth layout correct. I have found the best arrangement to be rail-to-rail decoupling adjacent to the IC, with rail-to-ground decoupling at the power connection to the board; this lowers the power-supply impedance at high frequencies without confusing the issue of 'what is ground?' too much.

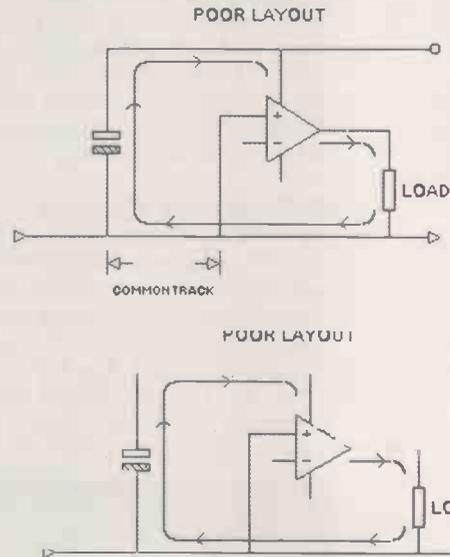

Earth currents in an amplifier physical layout are frequently misunderstood.

(a) Poor Layout

(b) Good Layout

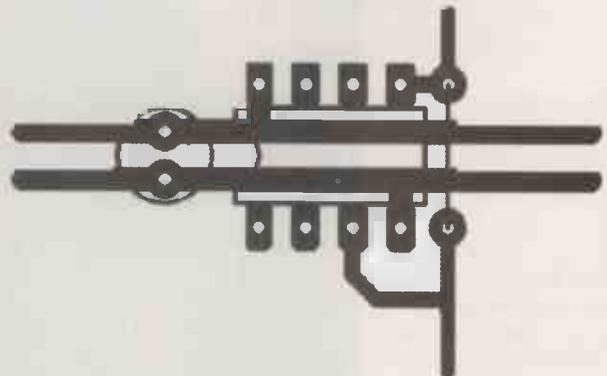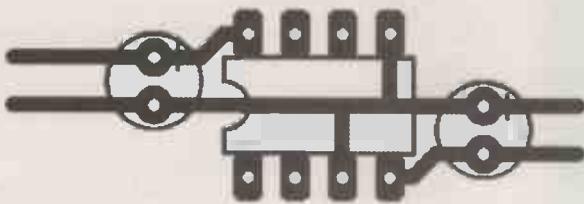

Power rail decoupling methods, good and bad.

Hands-on Internet

Cyril Bateman looks at mirrors, electronics design data, and new ways to search old services.

With the ever growing dominance of the World Wide Web, it is easy to overlook the original Internet uses; e-mail, FTP and News Groups. While for regular use, dedicated software is preferred, most Web browsers now provide working access to these functions.

While the Web browser search methods covered in my previous articles are targeted to Web page and FTP searches, Deja_News¹ searches only within the Usenet News Groups, eliminating the time consuming manual searching previously needed to locate a topic, Fig. 1.

Growing interest in emc has caused the formation of a specialist news group – sci.engr.electrical.compliance – which is dedicated to emc and safety compliance. Maintained by Bill Lyons of Claude Lyons Ltd², this group's FAQ contains much essential reading.

Closely related to emc, Texas Instruments³ recently issued an application report detailing the Bergeron Graphical Method, used to determine line reflections during transient phenomena.

Reflections on Windows

Two FTP software download sites catering for Windows systems are widely mirrored, i.e. backed up and available via different sites. Winsite⁴ has 44 mirrors while Simtel.Net⁵ has 64 mirrors. Winsite – formerly the CICA Windows FTP archive – went live on 13 October last year, Figs 2, 3.

For the UK, the Hensa⁶ archive at Lancaster University and Sunsite North Europe⁷ at Imperial College London, are particularly good FTP sources.



Fig. 2. The WinSite home page stakes its claims. This site used to be known as Cica, some archives continue to use the Cica name. Especially within their hard disc directory structure.

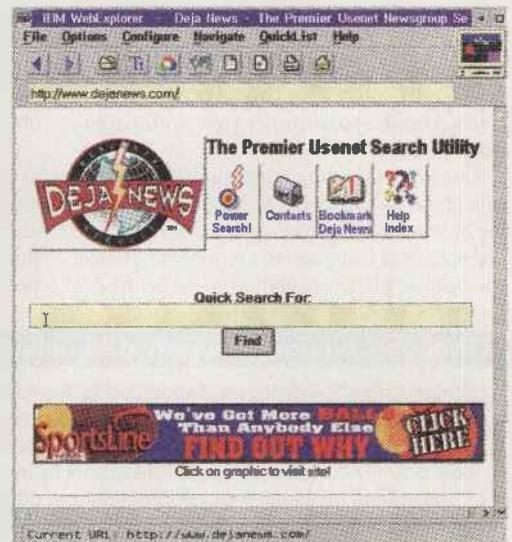


Fig. 1. Using Deja News to search for topics within Usenet. Some claim the Usenet archives hold the largest information base in Internet.

Both carry Winsite and Simtel.Net mirrors for pcs and also hold Amiga, Atari, Apple, Archimedes RiscOS and OS/2 software archives. Note external access to Hensa is not permitted during normal working hours.

Software for downloading is freely available from all mirror sites, but software for uploading is only accepted at parent sites. Uploads not conforming to the published instructions is rejected. Accepted software will be available from all mirrors after a few days delay and the Archie servers will automatically be advised.


With the enormous amounts of data and software already available, your unpublicised upload will raise little interest. By way of example, in early June I uploaded evaluation copies of my EMCFilter.zip software, used to illustrate the 'Understanding emi filters' article⁸, to three sites. These were Winsite, Simtel.Net and Funet.Fi⁹. Within two days, archie.funet.fi located this file, but four weeks later several Archie servers remained unaware. On acceptance of the software, the upload site administrator posts an Internet announcement. However, it is advisable to seek further publicity. Send mail to net-happenings¹⁰ and try Submit It¹¹ to advise the popular search engines.

While Netscape 2.01 incorporated improved security features, the latest Beta version 3.0, available by download¹², adds features and further enhances security. It also provides support for SSL3.0 and permits 'personal certificates' to prove your on-line identity.

Fig. 3. Simtel.Net is part of Walnut Creek cd-rom. For those with slow Internet access, much of this software collection is available on cd-Rom.



Fig. 4. Dedicated to searching for semiconductor sources world wide. Also can provide product briefs, application notes and datasheets.

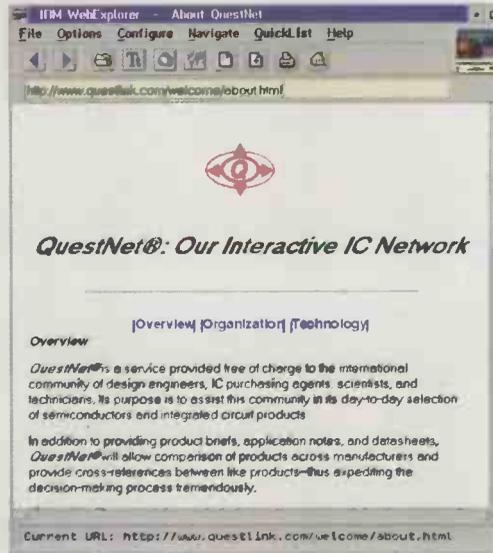

Sourcing semis

QuestNet¹³ helps designers to select and source semiconductors or integrated circuits world wide. It provides product briefs, application notes and datasheets. In addition, there are Internet facilities for semiconductor houses not yet having a Web page. Present searches are by product function, search by manufacturer and part number is being implemented, Fig. 4.

Continuing the on-line support theme, Motorola¹⁴ has an extensive Web presence. With its vast product ranges, the site is full of information and should be visited.

Elantec¹⁵ provides its full range of application notes for download and has a page devoted to interactive technical support and samples request.


Electric Library¹⁶ has now been sampled. Unlike other search methods listed, it is only available by a \$9.95 monthly subscription. And you can take advantage of the free trial offer. If sufficient of the 780 magazines and journals listed prove useful, the subscription fee can easily be recovered. This resource is similar to a conventional library of books and journals, except that it is electronically searchable using plain English. Having found the relevant document, click and it is downloaded. Unlike other search tools, you are not linked to Internet resources, it delivers the document to you, Fig. 5.

While all search engines covered to date have been US based, if all else fails, you can perhaps try a UK one¹⁷ which has an appropriate if irreverent address. While the present Web page differs, this version noticed recently, has a certain artistic appeal, Fig. 6.

The battle of OS

Expect more clashes in the operating system war, now that the latest Beta version of OS/2 Merlin has been shipped to testers for hands-on evaluation. Available to registered OS/2 users is a demo compact disk for Merlin. With built in support for Java, object-oriented technology and voice input/control allowing hands-off and eyes-off operation, Merlin claims to set the standards for ease of use.

Fig. 5. Maintains its own database of material but requires your regular subscription. Register by e-mail to gain a month's free access, without needing a credit card number. Maintains its own knowledge base and unlike some, does not pass you on to other Web links.

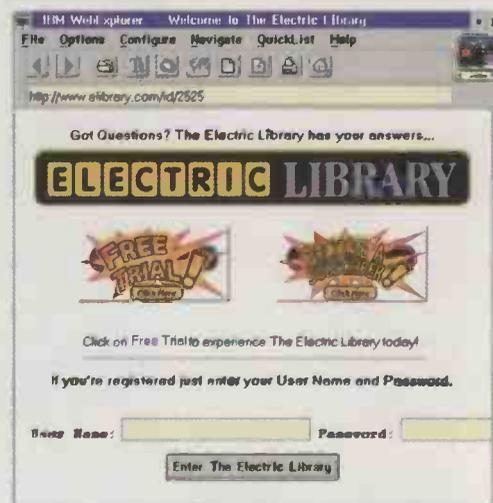

References

1. Dejanews – <http://www.dejanews.com>
2. FAQ EMC and Safety – http://world.std.com/~techbook/compliance_faq.html
3. The Bergeron Method – <http://www.TI.com>
4. Winsite – <http://www.Winsite.com>
5. Simtel.Net – <http://www.cdrom/simtel.net>
6. Hensa – <http://micros.hensa.ac.uk>
7. Imperial College – <http://src.doc.ic.ac.uk>
8. C. Bateman, Understanding emi filters, *Electronics World*, May '96 pp 384-388.
9. Funet.Fi. Finland – <ftp.funet.fi>
10. net-happenings – net-happenings@is.internic.net
11. Submit It – <http://www.submit-it.com>
12. Netscape – <http://www.netscape.com>
13. QuestNet – <http://www.questlink.com>
14. Motorola – <http://www.motorola.com>
15. Elantec Semiconductors – <http://www.elantec.com>
16. Electric Library – <http://www.elibrary.com>
17. Global Online Directory – <http://www.god.co.uk>


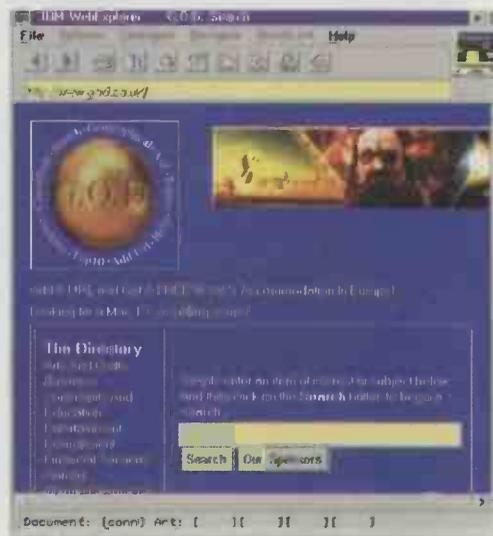


Fig. 6. Lord knows what this is. The site is organised rather differently from the established US search engines.

PROTEUS


New for Windows 3.1, 95 & NT

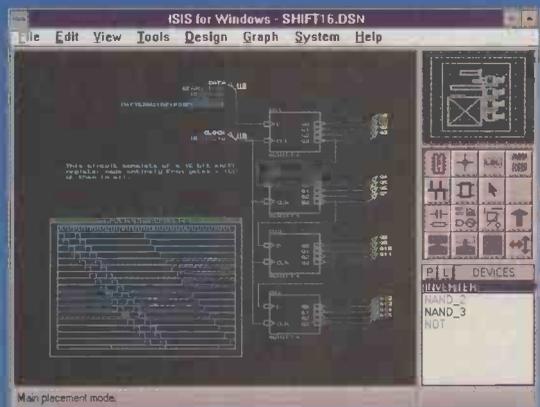The Complete Electronics Design System - Now With RIP-UP & RETRY!




Schematic Capture

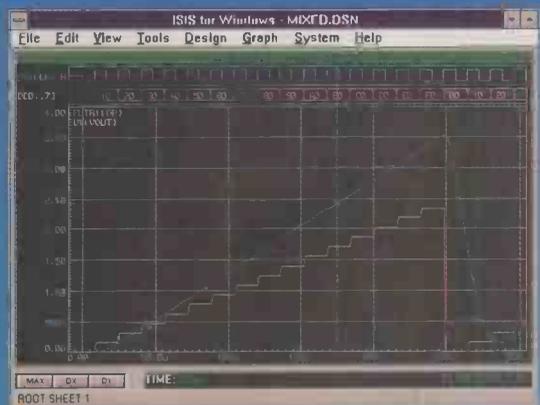- Easy to Use Graphical Interface under both DOS and Windows.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and PCB design.



Simulation

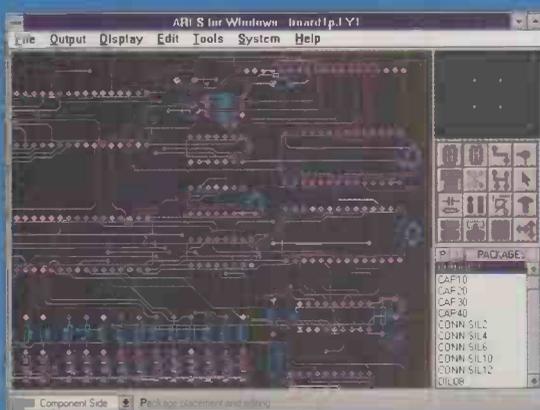- Non-Linear & Linear Analogue Simulation.
- Event driven Digital Simulation with modelling language.
- Partitioned simulation of large designs with multiple analogue & digital sections.
- Graphs displayed directly on the schematic.



PCB Design

- 32 bit high resolution database.
- Multi-Layer and SMT support.
- Full DRC and Connectivity Checking.
- RIP-UP & RETRY Autorouter.
- Shape based gridless power planes.
- Output to printers, plotters, Postscript, Gerber, DXF and clipboard.
- Gerber and DXF Import capability.

Labcenter
Electronics

*Write, phone or fax for your free demo disk, or ask about our full evaluation kit.
Tel: 01756 753440. Fax: 01756 752857.
53-55 Main St, Grassington. BD23 5AA.*

Proteus runs as a 32 bit application under both DOS and Windows (3.1, 95 and NT).

Prices start from £470 ex VAT; full system costs £1645 for DOS, £1875 for Windows. Call for upgrade pricing and/or information about our budget and educational products. All manufacturers' trademarks acknowledged.

CIRCLE NO. 117 ON REPLY CARD

HIGH DIRECTIVITY RF COUPLER

Paolo Antoniazzi has developed a method of producing couplers usable at gigahertz frequencies using standard low-cost fibreglass printed circuit.

At the beginning of the 1950's, a transmission line corresponding to a flattened coaxial with the sides removed was described¹. While yielding configurations that were somewhat simpler to fabricate, this approach still required that close tolerances be maintained as in the case of coaxial construction. The relative simplicity of the parallel-line system – or stripline – suggested further study of this type or of some equivalent open system.

This work has resulted in an interesting variation of the parallel-line system which avoids the requirements for extreme accuracy and dimensional symmetry. Because of the ease of manufacture and the apparent similarity to conventional wiring, the generic name of microstrip has been given to this transmission system². A cross section of the wire-above-ground system, as well as a cross section of the variation using a strip conductor – microstrip in place of the round wire – are shown in Fig. 1.

In the idealised case using a simple uniform dielectric and a lossless conductor, the type of transmission corresponds to the TEM mode^{3,4}. This has been confirmed approximately by theoretical work and by measurements performed on practical microstrip circuits comprising composite dielectrics and finite conductor dimensions.

As the frequency is increased, however, the

Inset 1. TEM – Transverse-ElectroMagnetic waves. These waves are characterised by the fact that both the electric vector (E vector) and the magnetic vector (H vector) are perpendicular to the direction of propagation. This is the mode commonly excited in coaxial and open-wire lines. It cannot be propagated in a waveguide.

dispersion effect becomes more obvious, and the characteristic impedance and the phase velocity defined under the quasi-TEM analysis, **Inset 1**, must be modified.

An important characteristic of the microstrip circuits is the power-flow distribution between the conductor and ground plane. **Figure 2** gives the calculations of the ratio of power-flow in a particular cross section to the total flow of power for a given b/h (b =width of the microstrip conductor, h =thickness of dielectric substrate).

While the distribution shown is approximate, it is possible to conclude that most of the power-flow is adjacent to the conductor. Essential characteristics necessary to design a microstrip system are shown in the box, **Figs. 3-5**. In particular using the information in **Fig. 4** it is possible to design the correct length of the near $\lambda/4$ coupler, for fibreglass material about 0.5 referred to air.

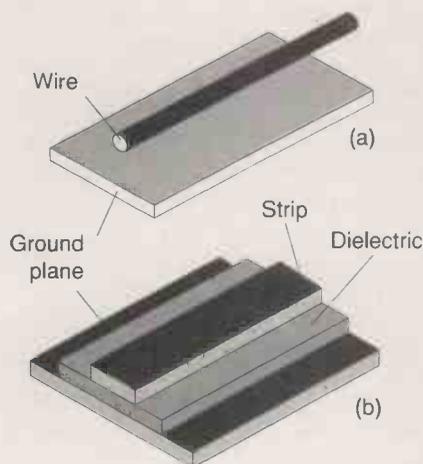


Fig. 1. Cross section of transmission systems: (a) shows the wire above ground and (b) illustrates the microstrip.

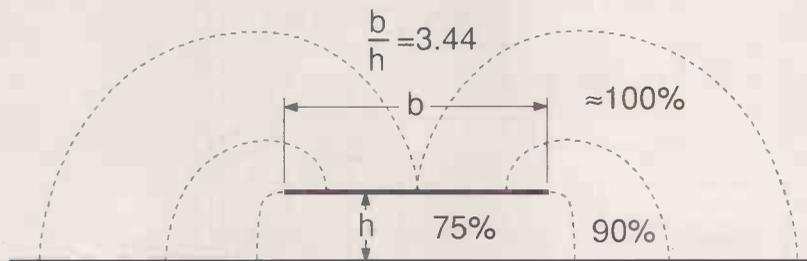


Fig. 2. Power-flow distribution in a microstrip system.

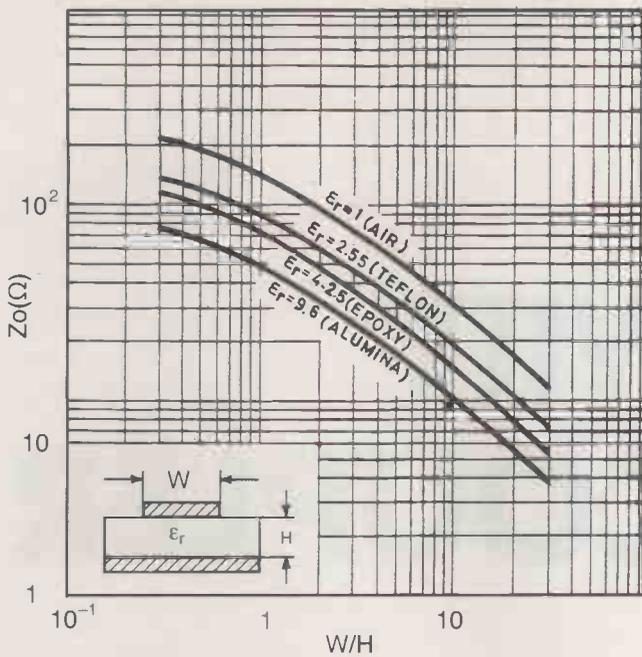


Fig. 3. Characteristic impedance versus E and W/h.

The directional coupler

A directional coupler is ideally a lossless reciprocal four-port device. It normally provides two unequal amplitude outputs when a signal is fed to one of its inputs. Depending on which port is fed, the outputs may be in-phase or out-of-phase (90° or 180°).

Directional couplers are usually described by indicating the coupling ratio of the low signal level output. Thus a 20dB directional coupler will provide a 'coupled' output which is 20dB below the input, while the through path (main line) has only a little loss, 0.04dB in this case. Naturally the main line loss increases for lower coupling ratios as indicated in Table 1.

Directional couplers can be used effectively in systems to monitor power or match, branch

Table 1.

Coupling ratio (dB)	Coupled output (dB)	Main line loss (dB)
3	-3	3.00
6	-6	1.25
10	-10	0.46
20	-20	0.04

signals, feedback power in amplifiers and for signal injection. Designer who understand the unique features of directional couplers will find many other applications where coupler properties can solve particular system problems.

A directional coupler has the ability to separate and sample signal components based on the direction of signal flow. Referring to Fig.

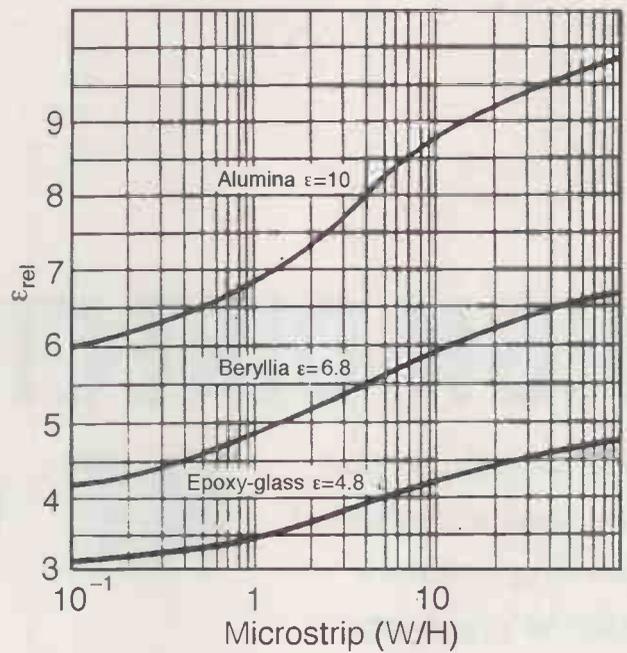


Fig. 4. Effective dielectric constant.

6, the diagram shows a 20dB directional coupler with a signal source at Port (1).

Ports (2) and (3) are terminated in Z_0 while Port (4) is loaded with an unknown impedance Z_L . We can see that if $Z_L=Z_0$ the return loss of Z_L becomes infinite and no signal reaches Port (3). This, of course, should follow from the consideration that Ports (1) and (3) and (2) and (4) are isolated when the directional coupler is terminated with Z_0 .

Practical directional couplers have finite isolation and this introduces an error in the comparative levels at Ports (3) and (2). Directional coupler directivity is a limiting parameter in the ability to accurately measure the return loss of an unknown load. As an example, if isolation (S31) is 43dB and coupling (S21) is 13dB, then directivity is 43-13, or 20dB.

The calculated error limits for a given directivity of coupler are shown in Fig. 7 and the following Table⁵. For example, if a coupler with 25dB directivity is used to measure the return loss of an antenna for wireless LAN systems and the measured value is 22dB, then the true return loss value can be anywhere between 17.3 and 32.7dB. Inserting different lengths of cable between the coupler and the antenna quickly shows that the match is not perfect, since the readings will change. The need for higher values of directivity by simple

Fig. 5. Ratio of line wavelength to free space wavelength.

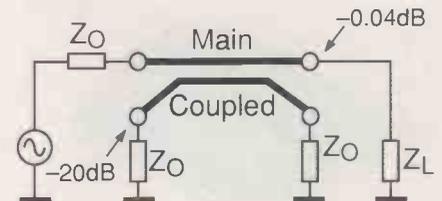
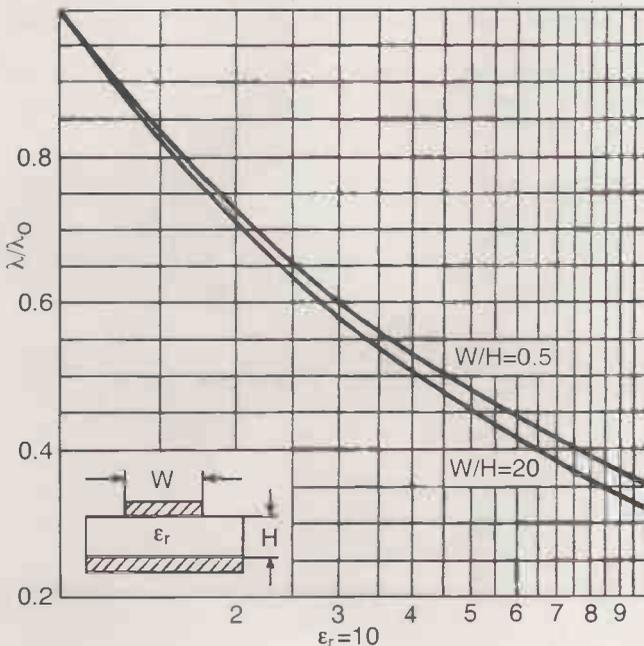


Fig. 6 Incident and reflected signal flow for a 20dB directional coupler.

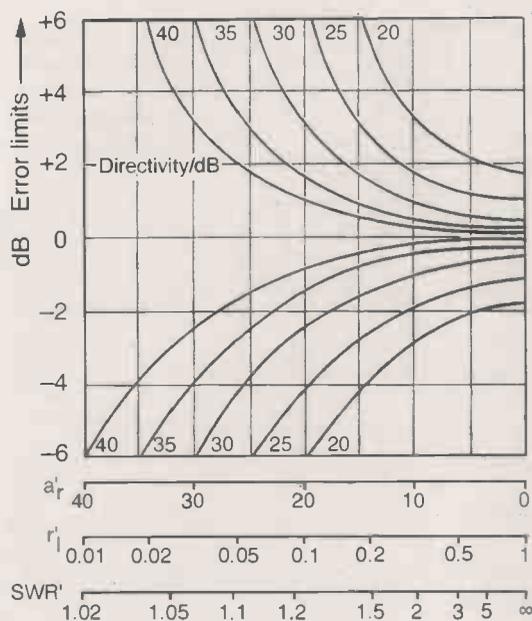


Fig. 7. Error limits due to insufficient directivity.

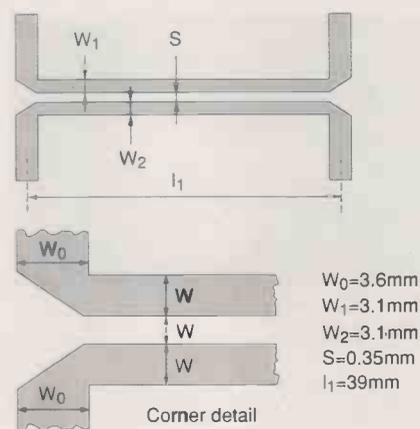


Fig. 8. Layout of the side coupled 13dB directional coupler realised with standard 1.6mm fibreglass printed circuit – dual sided.

couplers was the starting point for our experiments.

Measured return loss (dB)	Range of true return loss (dB)	
	with 20dB Directivity	with 25dB Directivity
10	7.6 to 13.3	8.6 to 11.7
14	10.5 to 20.0	11.8 to 16.9
18	12.9 to 31.7	15.0 to 23.1
22	15.0 to 33.7	17.3 to 32.7

High directivity via standard pcb

A difficulty with stripline couplers in homogeneous dielectric, where the centre board has a lower dielectric constant than the outer boards, is that the even-mode circuit will be electrically longer than the odd-mode circuit. For side coupled microstrip directional couplers of the type shown in Fig. 8, the well known even-and-odd-mode theory shows different phase velocity for the even mode (E) and odd mode (O) of propagation⁶.

Figure 9 shows the electric field of the two

modes. The system has different values of E for the different modes of propagation, since their fields are not distributed in the same way between air and dielectric. In this way, the two modes have different phase velocity.

Taking this effect into account, we can design simple high directivity couplers. A conventional microstrip 13dB directional coupler has only 26 to 28dB of isolation (directivity of 13 to 15dB) according to our tests at 900–1200MHz, Fig. 12.

The measured values are in good agreement with the theory. More expensive directional couplers realised with triplate techniques or meander-folded coupled lines⁷ have better directivity because of symmetrical distribution of the electric field. However, for microstrip circuits that also contain other passive or active components, this design is not practical.

The improved directivity of the coupler described in this article, with the layout of Fig. 8 and shown in photos of Figs 10, 11, is obtained simply by covering the central cou-

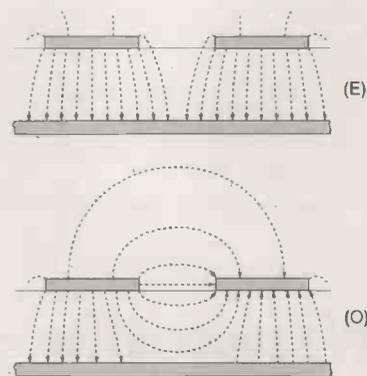


Fig. 9. Even mode (E) and odd mode (O) propagation. Electric field of the two modes.

pler structure with an unmetallized dielectric layer that consists of the same material as the microstrip substrate. This assumes standard 1.6mm fibreglass copper-clad circuit board.

Owing to this 'overlay substrate', of about 12x50mm, the electric field propagates almost entirely in an homogeneous dielectric and therefore the even and odd modes show nearly the same propagation velocity.

A comparison between conventional and 'overlay' couplers (with the same layout) is shown in Fig. 12. The reverse coupling was plotted against frequency after various adjustments of the side coupling space (s) and linewidth in the coupling zone (W₁ and W₂).

The final optimised 'overlay' coupler design shows high directivity, with reverse coupling better than 35dB in the range 950–1200MHz. The four type-N connectors – used only to permit a special high-power test – passed through the ground plane and made contact to the microstrip conductor. Compensation aluminum transitions are used in the mounting of the 'big' connectors.

References

1. R.M.Barrett and M.H.Barnes, Microwaves Printed Circuits, Radio and TV News, Vol. 46,

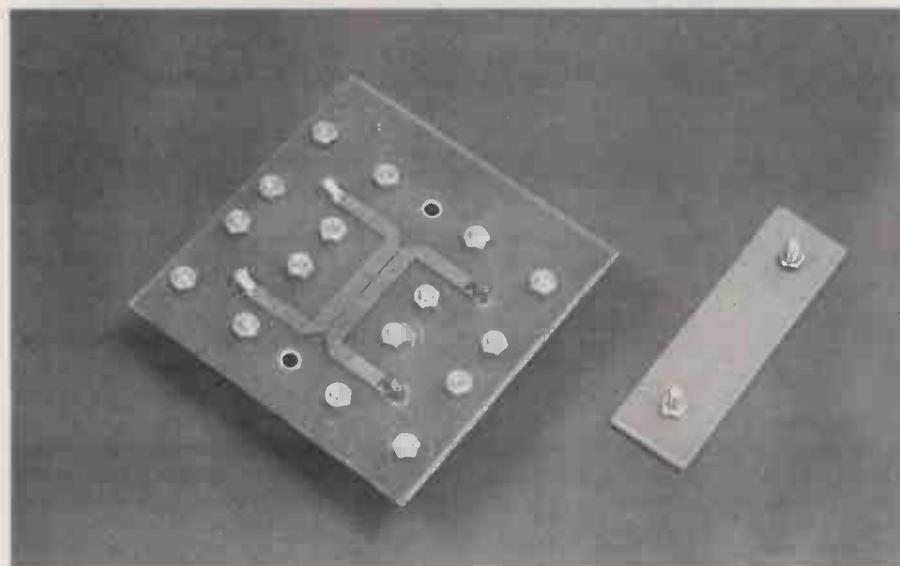


Fig. 10. Improved coupler – track side.



Fig. 11. Improved coupler, showing the connector layout.

- pp. 16, Sept. 1951.
2. D.D.Grieg and H.F.Engelmann, Microstrip—A New Transmission Technique, Proceedings of IRE, pp. 1644–1650, December 1952.
3. Reference Data for Engineers, Howard W. Sams & Co., pp. 23–29 and 30–33, 1989.
4. E.Hammerstad and O.Jensen, IEEE International Microwave Symposium, pp. 407–409, June 1980.
5. Microwave Handbook, Vol. 2, pp. 10.13, RSGB 1991.
6. T.Bryant and J.Weiss, Parameters of Microstrip Transmission Lines and Coupled Pairs of Microstrip Lines, IEEE Transactions MTT-16, pp. 1021–1027, 1968.

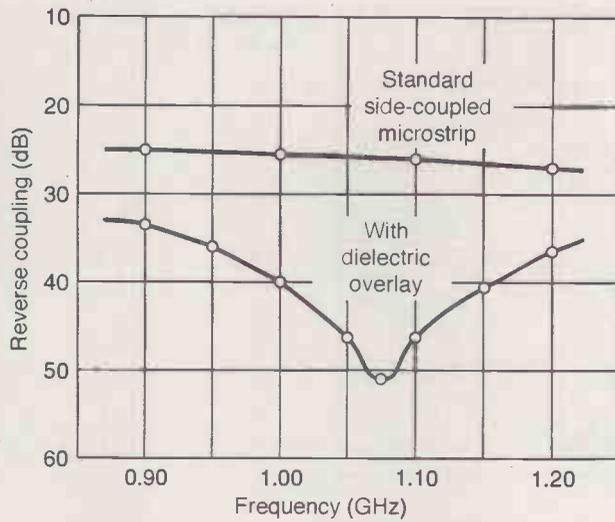


Fig. 12. Comparison between standard and 'overlay' coupler (1.6mm fibreglass, layout of Fig. 8.).

7. S.Renmark, Meander-Folded Coupled Lines, IEEE Transactions MTT-26, pp. 225–231, April 1978.
8. G.L.Matthaei, L.Young and E.Jones, Microwave Filters, Impedance Matching Networks and Coupling Structures, Mc Graw Hill.
9. News from Rohde & Schwarz, Number 148, Vol. 35, pp. 44–45, 1995/2.

EW reader offer – multi-instrument – discount and free dmm

Maxcom's MX9300 is a four-function multi-instrument featuring,

- 1Hz to 1GHz, 8-digit frequency counter
- 0.02Hz to 2MHz swept function generator
- 3¹/₂-digit DMM with 10A range
- 0 to 30V, 3A-variable psu
- 15V, 1A fixed output
- 5V, 2A fixed output

Normally, this instrument costs £399 excluding VAT and delivery but Vann Draper is making it available to EW readers at the special price of £399 – fully inclusive – and this price includes a **free hand-held digital multimeter**.

Incorporating full overload protection, the MX9300 allows a significant reduction in lab bench space needed while being more convenient than separate instruments. The free 3¹/₂-digit dmm accompanying this offer features 10A dc measuring capability and transistor 0 to 1000 h_{FE} test.



Frequency counter features – wide range, 10s to 10ms gating, 25mV sensitivity at 1GHz, autoranging, 1Hz +1dgt accuracy.
Function generator features – 0.1 to 20Vpp o/p, linear/log 20ms-2s internal or external sweep, sine, square, triangle, skewed sine, pulse, ttl.
DMM features – auto/manual ranging, DCV ACV Ω DCA ACA, 10MΩ input, ±(0.5%+2digit) basic accuracy.
PSU features – variable voltage and current, floating outputs, 2mV max. ripple on all outputs, 0.01% load regulation on 30V output.



FREE


Please send a cheque for £399 payable to Vann Draper Electronics, or your full credit-card details including expiry date and card type to Vann Draper Electronics at Unit 5, Premier Works, Canal Street, South Wigston, Leicester, LE18 2PL. Alternatively fax credit card details with your order on 0116 277 3945 or telephone on 0116 277 1400.

Address orders and all correspondence relating to this offer to Vann Draper Electronics.

Version 4.1

Electronics Workbench®

NEW
WINDOWS 95/NT
32 BIT VERSION

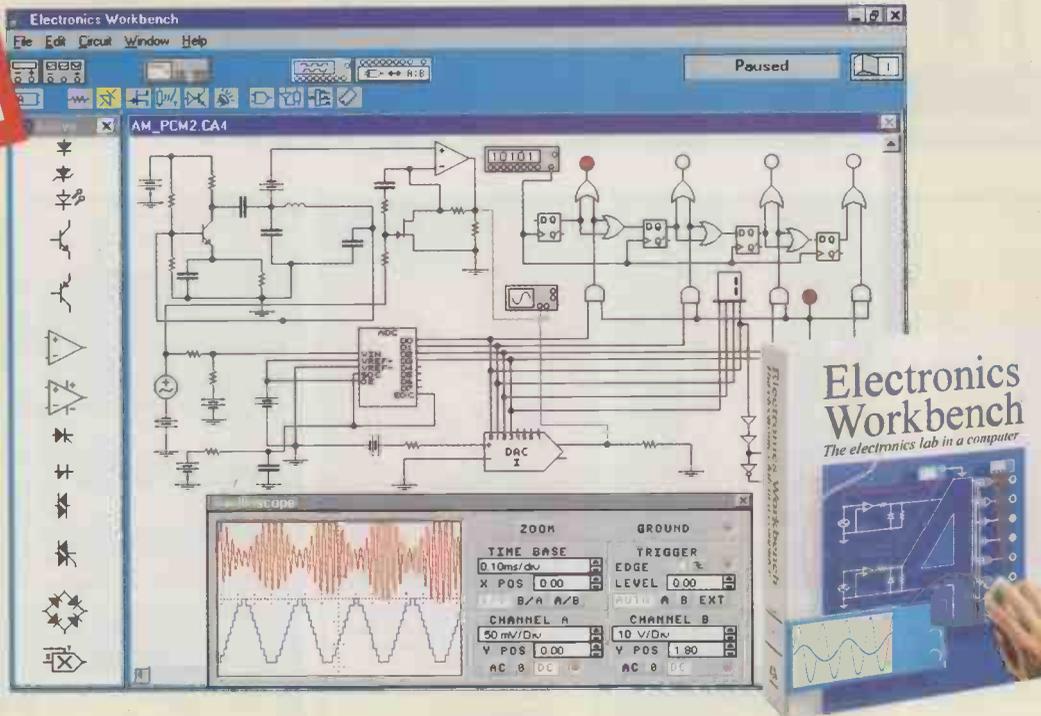

Design and Verify Circuits Faster

Join over 40,000 customers using the affordable mixed-signal simulator

Design faster with Electronics Workbench. Mix the analog and digital components and ICs in any combination. And with a click of the mouse, try 'what if' scenarios and fine tune your designs. The built-in SPICE simulator gives you real-world waveforms.

All without programming or netlist syntax errors.

And in minutes. Not hours or days.

You'll be up and running sooner. And create better designs faster with Electronics Workbench. We guarantee it!

RM Robinson Marshall (Europe) Plc

Nadella Building, Progress Close, Leofric Business Park, Coventry CV3 2TF
E-mail: sales@rme.co.uk Fax: 44 (0) 1203 233210

Shipping charges UK £6.99 All prices are plus VAT.

All trade marks are the property of their respective owners.

Electronics Workbench is a trademark of Interactive Image Technologies Ltd., Toronto, Canada.

Electronics Workbench: £199

- Click & drag schematic capture
- Mixed analog/digital SPICE simulator
- Instant Bode plots and scrollable waveforms
- 50 analog components with 350 models
- 140 digital components and ICs in TTL and CMOS
- Windows 95/NT/3.1, DOS and Macintosh versions
- Free unlimited technical support
- 30-day money-back guarantee

Engineer's Pack: £399

- Electronics Workbench
- 2,450 models
- Import/Export SPICE netlists
- Export to PCB packages

To discover more about *the* affordable mixed-signal simulator, call us today at:

44-(0)-1203-233216

Fax: 44-(0)-1203-233210



Australia: 25193993 • Belgium: 23847309 • Brazil: 11-4535988 • Chile: 2266900 • Cyprus: 2621068 • Czech Republic: 42-4823454 • Denmark: 33250109 • Finland: 02975033 • France: 149089000 • Germany: 711627740 • Greece: 15249981 • Hungary: 12150082 • India: 115441945
Indonesia: 21-4700815 • Israel: 36475613 • Italy: 11-4375549 • Japan: 3-33823136 • Malaysia: 3-7742189 • Mexico: 55935260 • Netherlands: 180317666 • New Zealand: 9-2671756 • Norway: 22-167045 • Philippines: 973-270118 • Portugal: 181-46609
Singapore: 777-2303 • Slovenia: 61-317830 • South Africa: 331-68309 • South Korea: 22-222-3431 • Spain: 1383-8335 • Sri Lanka: 1-86-5970 • Sweden: 87405500 • Taiwan: 886-2-366-0080 • Thailand: 662-398-6952 • UAE: 4453505 • UK: 203-23216



CIRCLE NO. 118 ON REPLY CARD

OLSON

®

For all your Power Distribution
Olson offer a varied choice

OLSON Distribution Units

ELECTRONICS LIMITED

OLSON DISTRIBUTION PANELS
FUSED, WITH R.F. FILTER
AND R.C.D. PROTECTION

ELECTRONICS LIMITED

OLSON The Rock Range
mains distribution panels
for 19" rack mounting

ELECTRONICS LIMITED

OLSON Office Furniture
Cable Management
Manufactured to BS 6396

ELECTRONICS LIMITED

OLSON Mains Distribution
Panels with
Non Standard Sockets

ELECTRONICS LIMITED

OLSON FUSED SUPER SLIM
WITH ELECTRA PLUG
CONV. AND OCC. POLY
SWITCHED SOCKETS

ELECTRONICS LIMITED

OLSON Earth Leakage
Distribution
Units

PORTABLE UNIT
Type PLS 1

WALL MOUNTED UNIT
Type VLS 2

BENCH UNIT Type BLS 1, 1.5 & 2

ELECTRONICS LIMITED

OLSON Distribution
Units

ELECTRONICS LIMITED

OLSON PANELS with 10AMP
CEE22/IEC
SHUTTER SOCKETS
FUSED, DOUBLE FUSED WITH HEAVY
FILTER AND RCD PROTECTION

ELECTRONICS LIMITED

OLSON From 10 Amps to 16 Amps
WITH AMERICAN
SOCKET TYPE 15A

ELECTRONICS LIMITED

OLSON Mains Distribution
Panels
INTERNATIONAL RANGE

ELECTRONICS LIMITED

OLSON FUSED SUPER SLIM
WITH ELECTRA PLUG
CONV. AND OCC. POLY
SWITCHED SOCKETS

ELECTRONICS LIMITED

OLSON DATA PROTECTOR

16 AMP MAINS RCD FUSED WITH SURTAGE
CUT OFF AND TRANSIENT SUPPRESSOR

ELECTRONICS LIMITED

OLSON INDUSTRIAL RANGE
16 AMP 110V AND 240V
TO BS 4343/IEC 309

ELECTRONICS LIMITED

TYPE	NO. OF SOCKETS	Industrial Units at challenging ambient conditions for portable or wall mounting only
16A 110V	10/15	All units housed in rugged metal boxes of robust construction
16A 240V	10/15	Available in 10 amp 10amp Single phase single
16A 240V	10/15	The various size to meet in applications with all international plug standards to BS 4343/IEC 309
16A 240V	10/15	All units available in 10amp 11amp

OLSON Distribution
Units

ELECTRONICS LIMITED

OLSON 19" FAN TRAYS

ELECTRONICS LIMITED

OLSON The Rock Range
CEE22/IEC
SOCKETS

ELECTRONICS LIMITED

OLSON SERVICE PILLAR FOR
THE OPEN-PLAN OFFICE

ELECTRONICS LIMITED

OLSON Distribution
Units
FROM 10 AMP TO 16 AMP STANDARD
TO BS 4343/IEC 309

ELECTRONICS LIMITED

768

OLSON ELECTRONICS LIMITED

CIRCLE NO. 119 ON REPLY CARD

FOUNTAYNE HOUSE, FOUNTAYNE RD., LONDON N15 4QL
TEL: 0181-885 2884 FAX: 0181-885 2496

Ian Hickman introduces aspects of passive filter design that are important yet frequently omitted from standard descriptions.

Filter

VARIATIONS

Many applications call for the filtering of signals, to pass those that are wanted, and to block those that are outside the desired passband. Sometimes digital filtering is appropriate, especially if the signals are in digital form already, but oftentimes, analog filters suffice – indeed are the only choice at rf. At lower frequencies, where inductors would be bulky, expensive and of low Q, active filters are the usual choice. Some of these are documented in every text book, but there are some useful variations upon the them which are less well known. This article explores one or two of these.

A basic active filter

Probably the best known active filter is the Sallen and Key second order circuit, the lowpass version of which is shown in Figure 1. Interchanging the Cs and Rs gives a highpass version. There has been considerable discussion recently of its demerits, both in regard to noise and distortion, from Dr D. Ryder and others in the Letters section of this magazine, see the November 1995 to April 1996 issues inclusive. But for many purposes it will prove adequate, having the minor advantage of very simple design equations. Moreover, the circuit is canonic - it uses just two resistors and two capacitors to provide its two-pole response.

Being a second order circuit, at very high frequencies the response falls away forever at 12dB per octave, at least with an ideal opamp. In practice, opamp output impedance rises at high frequencies, due to the fall in its open loop gain, resulting in the attenuation curve levelling out, or even reversing. In the maximally flat amplitude response design, at frequencies above the cutoff frequency, the response approaches 12dB/octave asymptotically, from below. At dc and well below the cutoff frequency, the response is flat, being 0dB (unity gain), again a value the response approaches asymptotically from below. The corner formed by the crossing of these two asymptotes is often called, naturally enough, the 'corner frequency'. The corner or cutoff frequency f_0 is given by $f_0 = 1/(2\pi\sqrt{C_1 C_2 R_1 R_2})$ where, usually, $R_1 = R_2$.

The dissipation factor $D = 1/Q$ where $Q = 0.5\sqrt{C_1/C_2}$ and for a maximally flat amplitude (Butterworth) design, $D = 1.414$, so $C_1 = 2C_2$. The Butterworth design exhibits no peak, and is just 3dB down (ie $V_{out}/V_{in} = 0.707$, or equal to Q) at the corner frequency. If $C_1 > 2C_2$, then there is a passband peak in the response below the corner frequency, being more pronounced and moving nearer the corner frequency as the ratio is made larger. This permits the design of filters with

four or six poles, or of even higher order, consisting of several such stages, all with the same corner frequency but each with the appropriate value of Q.

It is easy to see that the low frequency gain is unity, by simply removing the capacitors from Figure 1, for at very low frequencies their reactance becomes so high compared to R_1, R_2 , that they might as well simply not be there. At a very high frequency, way beyond cutoff, C_2 acts as a near short at the non-inverting (NI) input of the opamp, resulting in the lower plate of C_1 being held almost at ground. As C_1 is usually greater than C_2 , it acts in conjunction with R_1 as a passive lowpass circuit well into its stopband, resulting in even further attenuation of the input. At twice this frequency, both of these mechanisms will result in a halving of the signal, which thus falls to a quarter of the previous value, ie the roll-off rate is $20\log(1/4)$ or -12dB/octave . But what about that peak in the passband, assuming there is one?

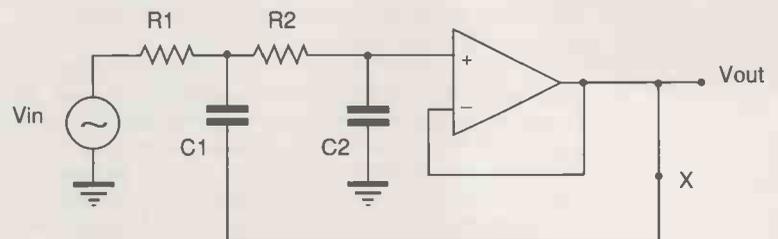


Fig. 1. The Sallen and Key second order lowpass active filter. Cut-off 'corner' frequency is given by $f_0 = 1/(2\pi\sqrt{C_1 C_2 R_1 R_2})$ and $Q = 0.5\sqrt{C_1/C_2}$ and dissipation $D = 1/Q$. For a maximally flat amplitude (Butterworth) design, $D = 1.414$, so $C_1 = 2C_2$. The Butterworth design exhibits no peak, and is just 3dB down at the corner frequency.

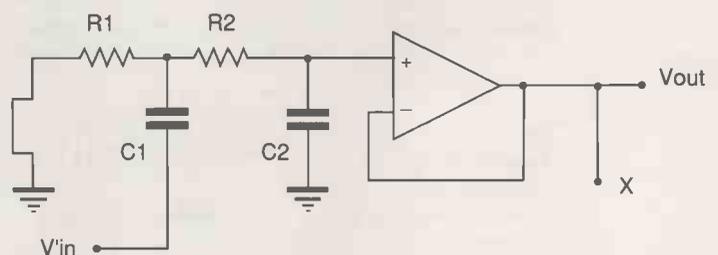


Fig. 2. Breaking the loop and opening it out helps to understand the circuit action (see text).

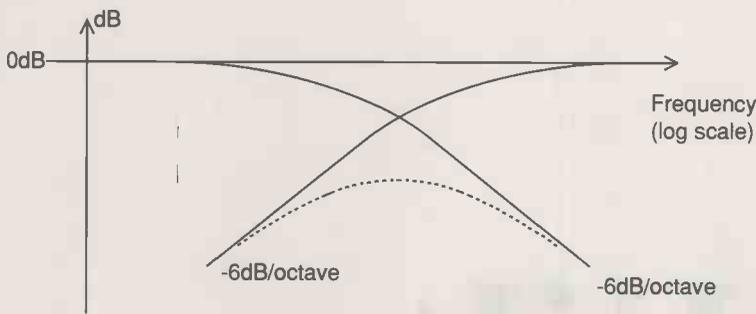


Fig. 3. Cascaded lowpass and highpass CR responses, and their resultant, (dotted).

The best way to approach this is to break the loop at point X, in Figure 1 and consider what happens to a signal V'_{in} , going round the loop, having removed the original V_{in} . Note that as the source in Figure 1 is assumed to have zero internal resistance, it has been replaced by a short circuit in Fig. 2. To V'_{in} , C_1 with R_1 now forms a passive lead circuit – highpass or bass-cut. The resultant voltage across R_1 is applied to C_2, R_2 , a passive lag circuit – lowpass or top-cut.

Each of these responses exhibits a 6dB/octave rolloff in the stopband, as shown in Fig. 3. Thus the voltage reaching the NI input of the opamp at any frequency will be roughly the sum of the attenuation of each CR section (actually rather more, as C_2R_2 loads the output of the C_1R_1 section), as indicated by the dotted line in Figure 3. At the frequency where the highpass and lowpass curves cross, the attenuation is a minimum, and the phase shift is zero since the lag of one section cancels the lead of the other.

If C_1 is now made very large, the bass cut will only appear at very low frequencies – the highpass curve in Figure 3 will shift bodily to the left. If in addition, C_1 is made very small, the top cut will appear only at very high frequencies – the lowpass curve will shift bodily to the right. Thus the curves will cross while each still contributes very little attenuation, so the peak of the dotted curve will not be much below 0dB, unity gain. Consequently, at this frequency the voltage at X is almost as large as V'_{in} , and in phase with it. The circuit can almost supply its own input, and if disturbed in any way will respond by ringing at the frequency of the dotted peak, where the loop phase shift is zero.

But however large the ratio C_1/C_2 , there must always be some attenuation, however small, between V'_{in} and the opamp's NI input, so the circuit cannot oscillate, although it can exhibit a large peak in its response, around the corner frequency. In fact, if the peak is large enough, the response above the corner frequency will approach the -12dB/octave asymptote from above, and below the corner frequency will likewise approach the flat 0dB asymptote from above.

Variations on a theme

The cutoff rate can be increased from 12dB/octave to 18dB/octave by the addition of just two components; a series R and a shunt C to ground between V_{in} and R_1 . And such a third order section can be cascaded with other second order section(s) to make filters with 5, 7, 9 poles etc. Normalised capacitor values for filters from 2 to 10 poles for various

response types (Butterworth, Chebychev with various passband ripple-depths, Bessel etc.) have been published in Refs. 1 and 2, and in many other publications as well. However, these tables assume $R_1=R_2$ (= the extra series resistor in a third order section), with the Q being set by the ratio of the capacitor values. This results in a requirement for non-standard values of capacitor, which is expensive if they are specially procured, or inconvenient if made up by parallelling smaller values.

While equal value resistors is optimum, minor variations can be accommodated without difficulty, and this can ease the capacitor requirements. Ref. 3 gives tables for the three resistors and three capacitors used in a third order section, with the capacitors selected from the standard E3 series (1.0, 2.2, 4.7) and the resistors from the E24 series, for both Butterworth and Bessel (maximally flat delay) designs.

The Kundert filter

The formula for the Q of the Sallen and Key filter is $Q=0.5\sqrt{C_1/C_2}$, so given the square root sign and the 0.5 as well, one finishes up with rather extreme ratios of C_1 to C_2 , if a high Q is needed, as it will be in a high order Chebychev filter. In this case, the Kundert circuit of Fig. 4 may provide the answer. The additional opamp buffers the second CR from the first, so that the attenuation at any frequency represented by the dotted curve in Figure 3 is now exactly equal to the sum of the other two curves. Removing the loading of C_2R_2 from C_1R_1 removes the 0.5 from the formula, which is now $Q=\sqrt{C_1/C_2}$ – assuming $R_1=R_2$. And due to the square root sign, the required ratio of C_1 to C_2 for any desired value of Q is reduced by a factor of four compared to the Sallen and Key version.


A further advantage of this circuit is the complete freedom of choice of components. Instead of making $R_1=R_2$ and setting the Q by the ratio of C_1 to C_2 , the capacitors may be made equal and the Q set by the ratio of R_1 to R_2 , or both C s and R s may differ, the Q being set by the ratio of C_1R_1 to C_2R_2 . Given that dual opamps are available in the same 8 pin DIL package as single opamps, the Kundert version of the Sallen and Key filter, with its greater freedom of choice of component values, can come in very handy for the highest Q stage in a high order filter.

The equal C filter

In addition to filtering to remove components outside the wanted passband, signals also frequently need amplification. The basic Sallen and Key circuit only provides unity gain, and with this arrangement, equal resistors are optimum. For, due to the loading of the second stage on the first, if R_2 is increased to reduce the loading, then C_2 will have to be even smaller, whilst if R_2 is decreased to permit a larger value of C_2 , the loading on C_1R_1 increases.

Where additional signal amplification is needed, there is no reason why some of this should not be provided within a filtering stage and Fig. 5 shows such a circuit. Clearly the dc and low frequency gain is given by $(R_A+R_B)/R_B$. A convenience of this circuit is that the ratio R_A to R_B can be chosen to give whatever gain is required (within reason), with C_1, C_2, R_1 and R_2 , chosen to give the required corner frequency and Q . An analysis of this most general form of the

Fig. 4. The Kundert filter, a variant of the Sallen and Key, has some advantages.

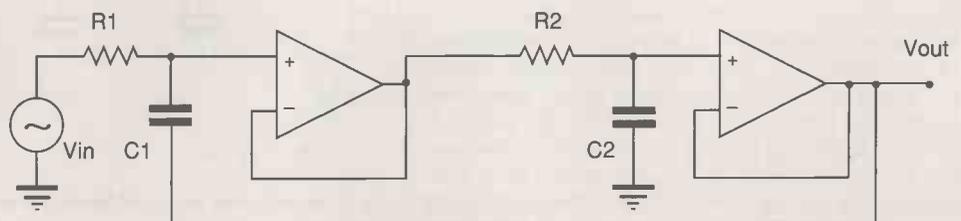

circuit can be found in Ref 4. If there were a buffer stage between R_1 and R_2 as in Figure 4, and the two CR products were equal, then at a frequency of $1/(2\pi CR)$ there would be exactly 3dB attenuation round the loop due to each CR.

So if R_A were to equal R_B , giving 6dB gain in the opamp stage, there would be no net attenuation round the loop and the Q would equal infinity – you have an oscillator. Without the buffer opamp, the sums are a little more complicated due to the second CR loading the first. But the sums have all been done, and the normalised values for R_1 and R_2 (values in ohms for a cutoff frequency of $1/2\pi Hz$, assuming $C=1F$) are given in Ref. 5 for filters of 1 to 9 poles, in Butterworth, Bessel and 0.1dB- 0.5dB- and 1dB-Chebyshev designs.

For odd numbers of poles, this reference includes an opamp buffered single pole passive CR, rather than a three pole version of the Sallen and Key filter, as one of the stages. To convert to a cutoff frequency of, say, 1kHz, regard the ohms figures in the tables as Mohms and the capacitors as $1\mu F$. Now divide the resistor values by 2000π . As the values are still not convenient, scale the capacitors in a given section down by say 100 or any other convenient value, and the resistors up by the same factor.

Reference 5 also gives the noise bandwidth of each filter type. The noise bandwidth of a given filter is the bandwidth of a fictional ideal brick wall sided filter which, fed with wideband white noise, passes as much noise power as the given filter. Ref. 5 also gives, for the Chebyshev types, the 3dB bandwidth. Note that for a Chebyshev filter, this is not the same as the specified bandwidth (unless the ripple depth is itself 3dB). For a Chebyshev filter the bandwidth quoted is the ripple bandwidth; e.g. for a 0.5dB ripple lowpass filter, the bandwidth is the highest frequency at which the attenuation is 0.5dB, beyond which it descends into the stopband, passing through -3dB at a somewhat higher frequency.

Other variants

In the Sallen and Key filter, the signal appears at both inputs of the opamp. There is thus a common mode component at the input, and this can lead to distortion, due to 'common mode failure', which, though small, may be unacceptable in critical applications. Also, as already mentioned, the ultimate attenuation in the stopband will often be limited by another non-ideal aspect of practical opamps - rising output impedance at high frequencies, due to the reduced gain within the local NFB loop back to the opamp's inverting terminal. Both of these possibilities are avoided by a different circuit configuration, shown in its lowpass form, in Figure 6a).

This is variously known as the infinite gain multiple feedback filter, or the Rausch filter, and it has the opamp's NI terminal firmly anchored to ground – good for avoiding common mode failure distortion. Another plus point is that at very high frequencies, C_1 short circuits the signal to ground, while C_2 shorts the opamp's output to its inverting input – good for maintaining high attenuation at the very highest frequencies. The design equations and tabulated component values are available in published sources; the filter is well known and is shown here just as a stepping stone to a less well known filter section, the SAB (single active biquad) with finite zero.

In some filtering applications, the main requirement is for a very fast rate of cutoff, the resultant wild variations in group delay not being important. The Chebyshev design provides a faster cut off than the Butterworth, the more so, the greater ripple depth that can be tolerated in the passband. But the attenuation curve is monotonic, it just keeps on going down at $(6n)dB/octave$, where n is the order of the filter (the number of poles), not reaching infinite attenuation until infinite frequency.

A faster cutoff still can be achieved by a filter incorporating one or more 'finite zeros', frequencies in the stop band at

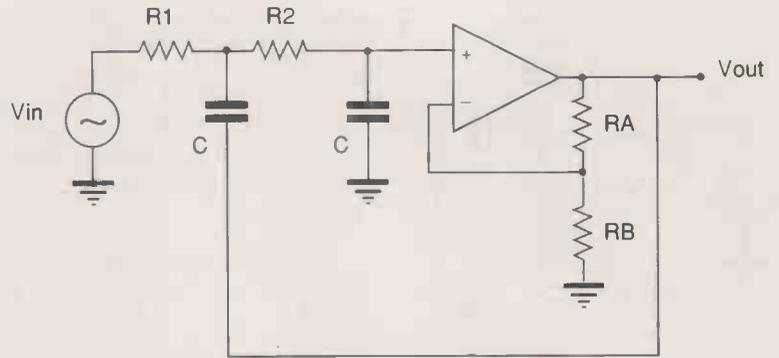


Fig. 5. The equal C version of the Sallen and Key circuit.

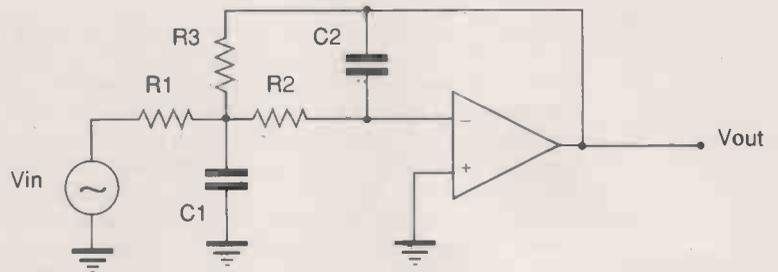


Fig. 6a). The mixed feedback or 'Rausch' filter – lowpass version.

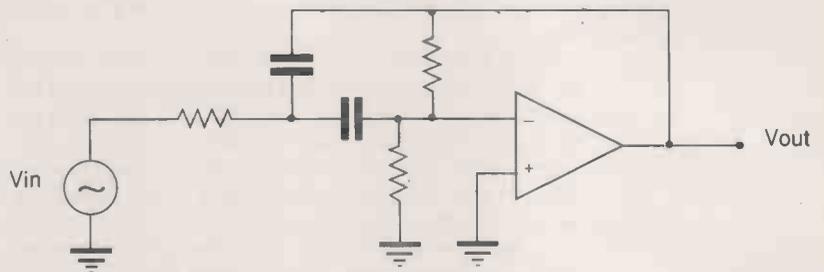


Fig. 6b). The mixed feedback or 'Rausch' filter – bandpass version.

which the response exhibits a notch. In a design with several such notches, they can be strategically placed so that the attenuation curve bulges back up in between them to the same height each time. Such a filter, with equal depth ripples in the passband (like a Chebyshev) but additionally with equal returns between notches in the stop band is known as an 'elliptic' or 'Caur' filter.

In a multipole elliptic filter, each second order section is designed to provide a notch, but beyond the notch the attenuation returns to a steady finite value, maintained up to infinite frequency. The nearer the notch to the cutoff frequency, the higher the level to which the attenuation will eventually return above the notch frequency.

So for the highest cutoff rates, while still maintaining a large attenuation beyond the first notch, a large number of poles is necessary. It is common practice to include a single pole (eg an opamp buffered passive CR lag) to ensue that, beyond the highest frequency notch, the response dies away to infinite attenuation at infinite frequency, albeit at a leisurely -6dB/octave.

The elliptic filter

The building blocks for an elliptic lowpass filter consist of second order lowpass sections of varying Q , each exhibiting a notch at an appropriate frequency above the cutoff frequency.

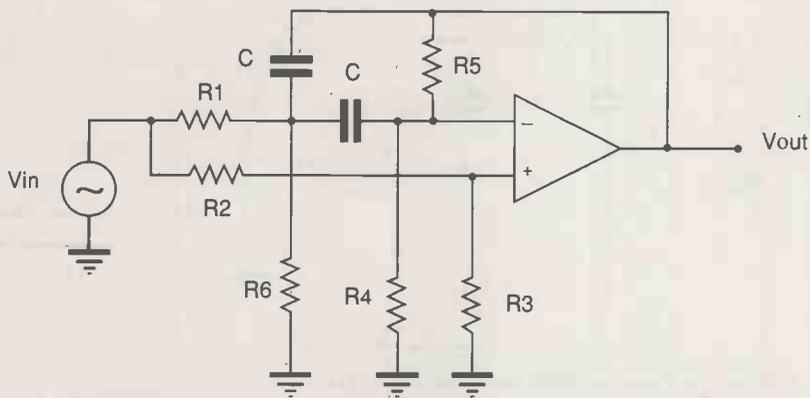


Fig. 7. The SAB circuit, with finite zero (or notch, above the passband).

A number of designs for such a section have appeared, based on the twin-tee circuit, but they are complex, using many components, and hence difficult to adjust. An alternative is provided by the SAB section mentioned earlier. This can be approached via the Rausch bandpass filter, which can be seen in Figure 6b) to be a variant on the Rausch lowpass design of Figure 6a). Clearly, due to the capacitive coupling, the circuit has infinite attenuation at 0Hz, and at infinite frequency, the capacitors effectively short the opamp's inverting input to its output, setting the gain to zero. Either side of the peak response; the gain falls off at 6dB per octave, the centre frequency Q being set by the component values. If the Q is high, the centre frequency gain will be well in excess of unity.

Figure 7 shows the same circuit with three extra resistors (R_2 , R_3 and R_6) added. Note that an attenuated version of the input signal is now fed to the NI input of the opamp via R_2 , R_3 . Consequently, the circuit will now provide finite gain down to 0Hz; it has been converted into a lowpass section, although if the Q is high there will still be a gain peak. If the ratio of R_5 to R_4 is made the same as R_2 to R_3 , then the gain of the opamp is set to the same as the attenuation suffered by the signal at its NI terminal, so the overall 0Hz gain is unity. If the other components are correctly chosen, the peak will still be there, but at some higher frequency, the signal at the opamp's inverting input will be identical in phase and amplitude to that at the NI input. The components thus form a bridge which is balanced at that frequency, resulting in zero output from the opamp, ie a notch.

Figure 8 shows a five pole elliptic filter using SAB sections, with a 0.28dB passband ripple, a -3dB point at about 3kHz and an attenuation of 54dB at 4.5kHz and above. The design equations for elliptic filters using SAB sections are given in Ref. 6. The design equations make use of the tabulated values of normalised pole and zero values given in Ref. 7.

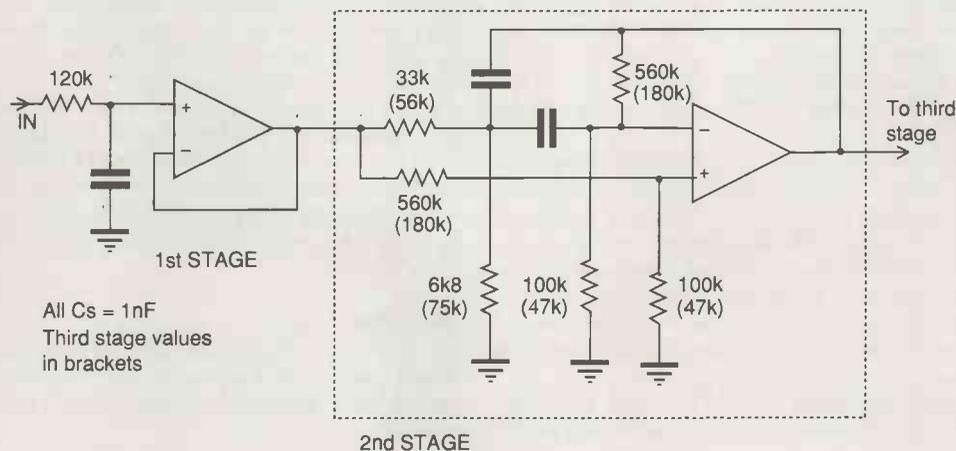


Fig. 8. A five-pole elliptic filter with 0.28dB passband ripple and an attenuation of 54dB at 1.65 times the cutoff frequency and upwards. The -3dB point is 3kHz, approx. All capacitors $C=1nF$, simply scale C for other cutoff frequencies.

All $C_s = 1nF$
Third stage values
in brackets

Some other filter types

Simple notch filters – where the gain is unity everywhere either side of the notch – can be very useful, eg for suppressing 50Hz or 60Hz hum in measurement systems. The passive TWIN TEE notch is well known, and can be sharpened up in an active circuit so that the gain is constant, say, below 45Hz and above 55Hz. However, it is inconvenient for tuning, due to the use of no less than six components. An ingenious alternative⁸ provides a design with limited notch depth, but compensating advantages. A notch depth of 20dB is easily achieved, and the filter can be fine tuned by means of a single pot. The frequency adjustment is independent of attenuation and bandwidth.

Finally, a word on linear phase (constant group delay) filters. These are easily implemented in digital form, FIR filters being inherently linear phase. But most analog filter types, including Butterworth, Chebychev and elliptic are anything but linear phase. Consequently, when passing pulse waveforms, considerable ringing is experienced on the edges, especially with high order filters, even of the Butterworth variety. The linear phase Bessel design can be used, but this gives only a very gradual transition from pass- to stop-band, even for quite high orders. However, a fact that is not widely known is that it is possible to design true linear phase filters in analog technology, both bandpass⁹ and lowpass¹⁰. These can use passive components, or – as in Reference 10 – active circuitry.

References

1. Active Filters: part 12 - Short Cuts to Network Design, R R Shepard, *Electronics* Aug. 18 1969, pp 82-91.
2. Active Filter Design, A B Williams, Artech House Inc. 1975
3. *Linear Technology Magazine*, May 1995, p 32.
4. Theory and Design of Active RC Circuits, L P Huelsman, McGraw Hill Book Company 1968. p 72.
5. Gain of two simplifies LP filter design, A Delagrange, *EDN* March 17 1983, pp 224-8. (Reproduced in 'Electronic Circuits, Systems and Standards', Ed. Hickman, Butterworth Heinemann 1991, ISBN 0 7506 0068 3).
6. Ian Hickman, Analog Electronics, Butterworth Heinemann 1993, ISBN 0 7506 1634 2.
7. A. I. Zverev, Handbook of Filter Synthesis, John Wiley and Sons Inc. 1967.
8. D. Irvine, Notch Filter, *Electronic Product Design*, May 1985, p 39.
9. R.M. Lerner, Bandpass Filters with Linear Phase, Proc. IEEE March 1964, pp 249-268.
10. A. Delagrange, 'Bring Lerner filters up to date: replace passive components with opamps', *Electronic Design* 4, Feb. 15 1979, pp 94-98.

Video inserter

The program for controlling the video insertion hardware described last month begins at address 0000_{16} . The microprocessor begins execution at this location after a hardware reset.

Address 0000_{16} contains a jump instruction to the routine which initializes the cpu and clears the software flags. Next the program sets up the real time clock by writing two state words to Reg. A and Reg. B of the 6818's ram. Table 1 shows the address map of the real-time clock while Tables 2 and 3 describe functions of registers A and B. Register details for the 6818 are shown in the Inset 1. For further information on other features of the 6818, refer to the manufactures manual. As the real-time clock IC resides in the external ram area, the MOVX instructions are used to communicate with it.

Within the real-time clock, the 24/12 control bit establishes the format of the hours bytes as either the 24-hour mode (logic one) or the 12-hour mode (logic zero). This bit is affected only by the software.

Table 1. Locations within the 6818 real-time clock. Registers A and B are used for control.

Address	Locn	Function	Range
	0	Seconds	0-59
	1	Seconds alarm	0-59
	2	Minutes	0-59
	3	Minutes alarm	0-59
	4	Hours - 12 hour mode	1-12
		Hours - 24 hour mode	0-23
	5	Hours alarm - 12 mode	1-12
		Hours alarm - 24 mode	0-23
	6	Day of week (1=Sun)	1-7
	7	Day of month	1-31
	8	Month	1-12
	9	Year	0-99
	0A	Register A	x
	0B	Register B	x

Table 2. Functions of RTC register A.

MSB	LSB
b7	b0
UIP	RS1
DV2	RS2
DV1	RS3
DV0	RS0

Table 3. Functions of RTC register B.

MSB	LSB
b7	b0
SET	DM
PIE	24/12
AIE	-
UIE	-
SQWE	-

Ian Polczynski outlines the software needed for overlaying text on standard video picture using hardware described last month.

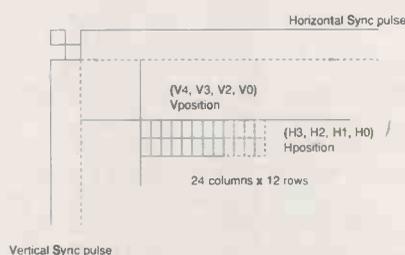


Fig. 1. The Hposition and Vposition define the top left hand corner of the displayed area.

For example, if number $A6_{16}$ ($1010\ 0110_2$) is written to register A, the time-base frequency will be 32768kHz and the SQW output frequency is 1024kHz.

If $0A_{16}$ ($0000\ 1010_2$) is written to register B, it disables all interrupts, activates SQW pin, indicates bcd format and 24-hour mode.

The following is the machine code starting from $\#081D_{16}$:

```
B8, 0A MOV R0, #0Ah
23, A6 MOV A, #0A6h
90 MOVX @R0, A ; Reg. A=A6h
B8, 0B MOV R0, #0Bh
23, 0A MOV A, #0Ah
90 MOVX @R0, A ; Reg. B=0Ah
```

The same instructions are used for a read time or calendar operation. For example,

```
B8, 00 MOV R0, #00h
; Set the R0 register to the RTC RAM
location 00.
80 MOVX A, @R0
; Read SECONDS from the RTC.
```

The second and last circuit requiring setting up is the $\mu PD6145$ on-screen display chip. As stated in the hardware article in the September issue, the $\mu PD6145$ commands consist of nine bits, but the shift register for the serial interfacing operates with eight bits. As a result,

List 1. Serial communication routine for sending a byte from the cpu to the on-screen display chip - in 8039 assembly language.

```
OSD_Ser: 9A, 7F ANL P2,
#7Fh
; OSD CS line (OSD 1) goes Low.
BF, 08 MOV R7, #08h
; Bit Counter R7 loaded with 8.
FE MOV A, R6
; Read Character/Command
OSD_Rotate:F7 RLC A
; Shift MS Bit to Carry.
F6, AC JC Was_H
; Is it 1 or 0?
9A, EF ANL P2, #0EFh
; If 0, Data (OSD 4) goes Low.
04, AE AJMP Time_Call
; Skip next instruction.
Was_H: 8A, 10 ORL P2,
#10h
; If 1, Data (OSD 4) goes High.
Time_Call: 14, F9 ACALL
OSD_Time
; Call time delay routine.
9A, DF ANL P2, #0DFh
; Now OSD Clock line goes Low.
14, F9 ACALL OSD_Time
; Wait a while again.
8A, 20 ORL P2, #20h
; Clock line goes High.
EF, A5 DJNZ R7, OSD_Rotate
; Go to OSD_Rotate if not last
bit
8A, 40 ORL P2, #40h
; Byte completed, Strobe High.
9A, AF ANL P2, #0AFh
; Now Strobe goes Low.
00 NOP
; 3 cycles of time delay.
00 NOP
00 NOP
8A, A0 ORL P2, #0A0h
; Strobe and Data are kept low.
83 RET
; Byte transferred, return.
```

The time delay routine is located at address

$08F9_{16}$. It corrupts only cpu register R5:

```
OSD_Time: BD, 10 MOV R5,
#10h
; Load the loop counter.
OSD_Time_St: 00 NOP
; Do nothing inside the loop.
00 NOP
FD, FB DJNZ R5,
OSD_Time_St
; Is the loop counter zeroed?
83 RET
; Return to the OSD subroutine.
```

To set up the $\mu PD6145$ OSD IC, first input the Format Reset Command at 0830_{16} :

```
MOV R6, #0FE
; Load R6 with "FE"
; (Format Command for Bank1)
CALL OSD_Ser
; And CALL OSD serial subroutine.
```

Table 4. Command list for the 6145 on-screen display chip.

Content	Fo	D7	D6	D5	D4	D3	D2	D1	D0
Bank-0 commands Fo=0									
Display character data	0	0	C6	C5	C4	C3	C2	C1	C0
Colour blink data for each character	0	1	0	0	0	Bk	R	G	B
Character display line address	0	1	0	0	1	R3	R2	R1	R0
Character display column address	0	1	0	1	C4	C3	C2	C1	C0
Background specification	0	1	1	0	S4	S3	Rb	Gb	Bb
Display on/off, smoothing etc.	0	1	1	1	0	0	Sy	Sm	Do
Blinking/oscillator control	0	1	1	1	0	1	B1	B2	Os
Format Selection	x	1	1	1	1	1	1	Fo	Fr
Bank-1 commands Fo=1									
CRAM write address	1	0	0	A5	A4	A3	A2	A1	A0
CRAM word address	1	0	1	0	0	W3	W2	W1	W0
CRAM line address	1	0	1	0	1	L3	L2	L1	L0
Display position vertical address	1	0	1	1	V4	V3	V2	V1	V0
Display position horizontal address	1	1	1	0	H4	H3	H2	H1	H0
Character size specification	1	1	0	S5	S4	R3	R2	R1	R0
Test mode setting	1	1	1	1	0	T3	T2	T1	T0

Control suggestions

These button functions were implemented on the prototype for programming the on-screen display via software.

+ (up arrow): To position the overlaid screen upwards

Change DATE and TIME

Select character

- (down arrow): Position overlaid screen downwards

Change DATE and TIME

Select character

(left arrow): Position the overlaid screen to the left

Step blinking text character backward

(right arrow): Position the overlaid screen to the right

DATE/TIME: Selects date and time adjustment mode (4s)

TEXT: To select text adjustment mode (4s)

TEXT OFF: To switch text line on and off

SET: To complete setting and move blinking character forward.

and,

$$V_{\text{position}} = 9H_{\text{dot}} \times [2^4 \times V_4 + 2^3 \times V_3 + 2^2 \times V_2 + 2^1 \times V_1 + 2^0 \times V_0]$$

Note that (H4... H0)=(0... 0) is not a valid combination, and Hdot represents a single tv line. The CCIR standard has 625 lines per screen. If, for example, the on-screen display chip's oscillator generates 6MHz. This frequency is determined by L₁, C₁₇ and variable capacitor C₁₈.

If (H4, H3, H2, H1, H0)=(0, 0, 1, 0, 0) then calculated Hposition is 8µs. This is about 12.5% of the duration of a single tv line ie. the position of the first displayed column will be shifted by 12.5% from the left screen edge, and so on. These sets of bits (H4... H0 and V4... V0) combined with value of capacitor C₁₈ determine the position and width of the overlaid screen.

Now back to the assembler language, located at 0834₁₆:

```
MOV R6, #60h
; Display position Vpos=0.
CALL OSD_Ser
MOV R6, #C1h
; Display position Hpos=0
CALL OSD_Ser
```

Next, the size of the displayed character has to be set. This size is defined by bits S4 and S5 from the character size command. Four size options are available: size 1 occupies 9 tv lines, size 2 18 lines, etc. The following code specifies displayed character size:

```
MOV R6, #80h ; Size-1.
CALL OSD_Ser
```

To complete the OSD set up the cpu has to send some additional properties. All belong to the Bank-0 command set. The first byte to be sent is the format reset command for Bank-0 and then the other outstanding parameters.

This code is located at 0840₁₆ of the program memory eeprom:

```
MOV R6, #0FCh
; "FC" specifies Bank-0.
CALL OSD_Ser
MOV R6, #88h
; "88" defines Blinking on and colour Blk.
CALL OSD_Ser
MOV R6, #0C0h
; "C0" means No Background.
CALL OSD_Ser
MOV R6, #0E7h
; Turns the entire display ON.
CALL OSD_Ser
MOV R6, #0E9
; Turns On oscillation and Blinking Off.
```

So, that is it. Now you can try to display something on the screen. To display '8' in row three and column five for example.

```
MOV R6, #92h
; "90" would indicate Row 1
CALL OSD_Ser
MOV R6, #A4
; "A0" would indicate Column 1
CALL OSD_Ser
MOV R6, #08h
; "08" is the number we want to display.
CALL OSD_Ser
```

and the desired number '8' will be displayed where we wanted.

After the initialization, most of the time the program will rotate around a loop, waiting for a key to be pressed or seconds from the time counter to be elapsed.

Publishing the whole firmware's source code - about 4kbyte - with assembler and explanations is not feasible, but I think that there should be enough here to give you some idea of what is involved in writing/modifying the software for the on-screen display unit. ■

Technical support

Readers interested in a designer's kit incorporating the 6145 on-screen display IC, osd and keypad pcbs and a pre-programmed e-prom can obtain one from Polvision at 77 Glanton Way, Dianella, Western Australia 6062 for AU\$99. The NEC µPD6145 is difficult to obtain in small quantities in the UK, but it is freely available in Australia. NEC's head office there can be reached on 0061 392 621111. The µPD6151 appears to be a drop-in replacement, but this device will not allow you to define your own characters. The µPD6156 could also be used, with minor circuit alterations. This device's command set is also slightly different.

instructions are divided into two banks. Table 4 shows the µPD6145 command list.

Initially, the format reset command must be input to the µPD6145 (Fr at logic one). To do this, first consider the serial communication routine. It transmits a hexadecimal byte from the cpu to the µPD6145. The byte to be transmitted must be stored in cpu register R6 before entering this routine. The CALL to OSD_Ser routine, located at the 08A0₁₆, starts transmission; List 1:


Next the horizontal and vertical display positions must be specified. As shown in Table 4, these functions belong to the Bank-1 Command Set. That is why R₆ was loaded with FE₁₆ in the previous transfer. Figure 1 shows how to calculate a position of the 24-column-by-12-row screen.

As shown in Fig. 1, Hposition and Vposition define the top left hand corner of the displayed area. Formulas are as follows:

$$H_{\text{position}}(\mu\text{s}) = [12/F_{\text{osc}}(\text{MHz})] \times [2^4 \times H_4 + 2^3 \times H_3 + 2^2 \times H_2 + 2^1 \times H_1 + 2^0 \times H_0]$$

Specialist in Parts - Broad in Outlook

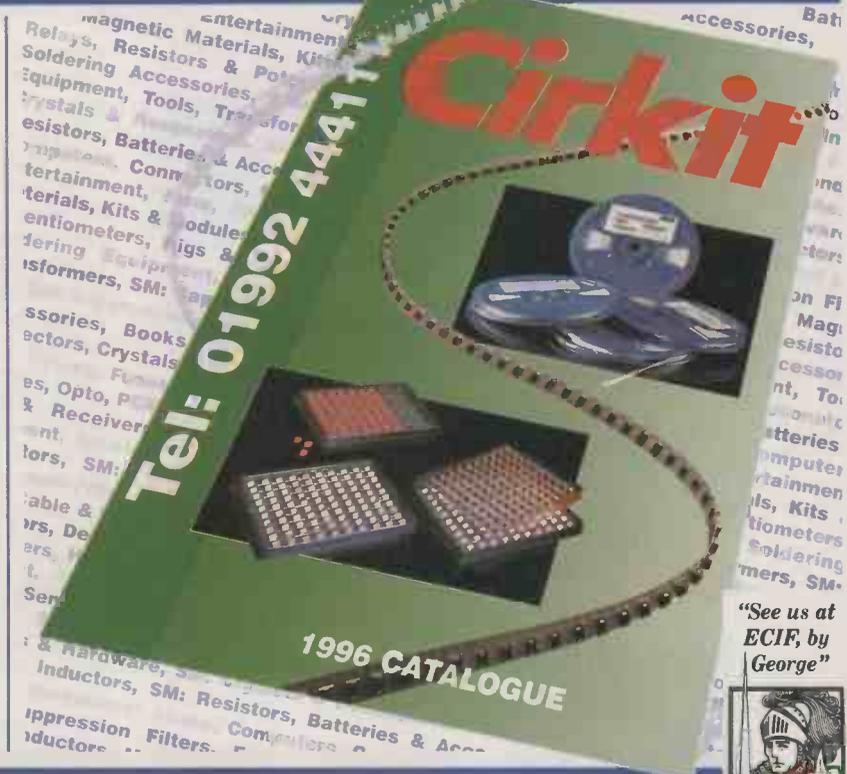The 1996 Cirkit Catalogue includes components from these and many other leading manufacturers:



"See us at ECIF, by George"




Tel: 01992 444111 Fax: 01992 464457
E-Mail: sales@cirkit.co.uk
Park Lane Broxbourne Herts EN10 7NQ

CIRCLE NO. 150 ON REPLY CARD

Get out of a pickle - get into SpiceAge!

Hands up all who have been there? A great idea turns into sleepless nights: getting one thing right breaks something else...

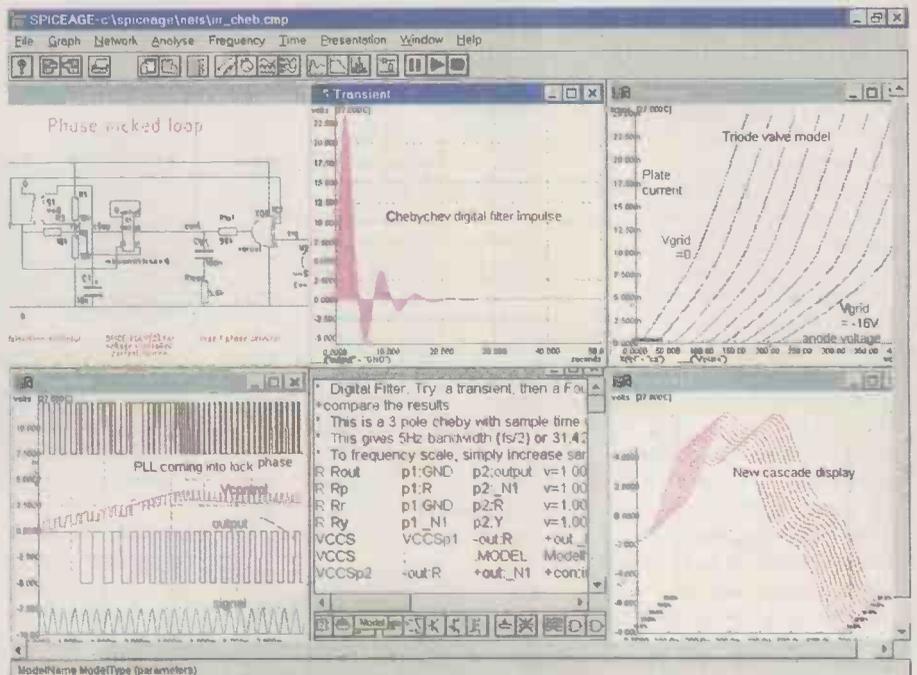Some circuits require the refining of many interdependent variables. SpiceAge provides a virtually limitless inventory of components, signal functions and instruments with facilities for sweeping values, with am and fm through arbitrary functions. It can guide you to a solution that could take much longer to find using hardware.



SpiceAge up your design without burning a hole in your pocket. Prices from just £85 + VAT to £695 + VAT. Friendly technical help comes free (dreadful puns optional). For a demonstration kit and details of our other and third party support programs (includes schematics, PCB layout, filter synthesis and model synthesis), please contact:


Charles Clarke at Those Engineers Ltd, 31 Birkbeck Road, LONDON NW7 4BP.
Tel: 0181 906 0155 Fax: 0181 906 0969 Email 100550.2455@compuserve.com



Dictionary of Communications Technology

Terms, definitions and abbreviations

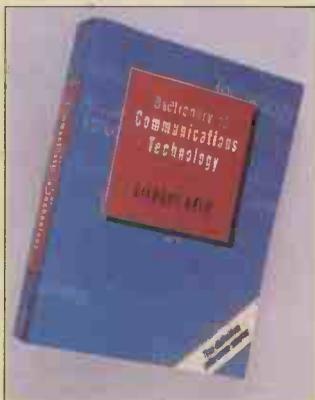Gilbert Held, 4-Degree Consulting, Macon, Georgia, USA
In response to the changing face of the telecommunications industry and the rapid expansion in the use of microprocessors, fibre optics and satellites, Gil Held has updated his earlier telecommunications dictionary to bring readers in line with the very latest developments and terms in communications technology.



Features Include:

- Over 9000 references and 250+ illustrations
- Comprehensive coverage of data and computer communications
- New entries on PC LANs, the Internet, client/server operations and communications testing
- Trade name information

First Edition Review:

"For a consultant or telecommunications operative, this book is a must. It is comprehensive and timely ... an excellent reference for the IS professional."


Data Processing Digest

ISBN 0471 95542 6, 512pp, hardback, UK £68.50, Europe £73, ROW £85
ISBN 0471 95126 9, 512pp, paperback, UK £38.50, Europe £43, ROW £55

Testing, Troubleshooting and Tuning Local Area Networks

Techniques and tools to isolate problems and boost performance

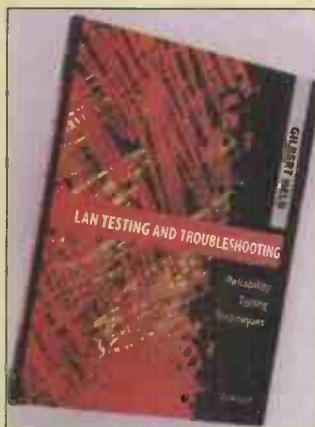Gilbert Held, 4-Degree Consulting, Macon, Georgia, USA.
Recognising the problems




encountered by network users and administrators on a daily basis, this book is designed to assist readers by focusing on testing, troubleshooting and tuning of Ethernet and Token-Ring networks. It is devoted exclusively to: how things go wrong how to recognise, monitor and test for problems; network analysis and network management products that assist users in examining the flow of data in a complex network.

ISBN 0471 95880 8, 275pp, hardback, UK £37.50, Europe £40, ROW £50

Wireless Information Networks

Kaveh Pahlavan, Worcester Polytechnic Institute and Allen H Levesque, GTE Government Systems Corporation.

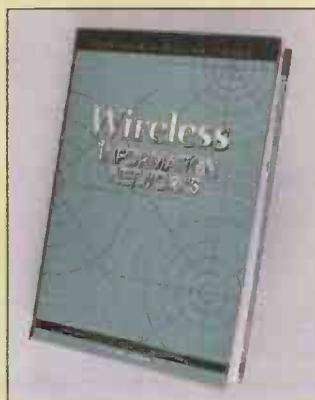Wireless Information Networks organises all major elements of wireless technology – cordless and cellular telephony, Personal Communications Systems (PCS), mobile data networks and Wireless Local Area Networks (WLANs), presenting them from a logical, systems engineering perspective. Technical material is thoroughly integrated with special applications and focuses on four main areas: Wireless



standards and descriptions of systems and products; Measurement and modelling of radio and optical wave propagations; Wireless transmission techniques and Wireless multiple access techniques.

Contents: Overview of Wireless Networks. Frequency Administration and Standards Activities. Characterisation of Radio Propagation. Channel Measurement and Modelling for Narrow-band Signaling. Measurement of Wide-band Channel Characteristics. Computer Simulation of the Radio Channel. Modem Technology. Signal Processing for Wireless Applications. Spread Spectrum for WIN Systems. Wireless Optical Networks. Networks and Access Methods. Standards and Products.


ISBN 0471 10607 0, 304pp, hardback, UK £63.50, Europe £68, ROW £81

Applied Cryptography

2nd Edition

Protocols, Algorithms and Source Code in C

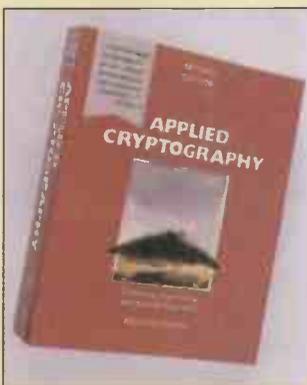Bruce Schneier, Security Consultant and President of Counterpane Systems, USA
This revision of the programmer's and system designer's guide to the practical applications of modern cryptography



provides the most comprehensive, up-to-date survey of modern cryptographic techniques, along with practical advice on how to implement them.

New to this edition:

- Detailed treatment of the US government's Clipper Chip encryption program
- New encryption algorithms (eg. 'GOST') recently obtained from the former Soviet Union
- More detailed information on incorporating algorithms and programming fragments

into working software


• The latest developments in the fields of message authentication ('digital signatures') and digital cash.
ISBN 0471 12845 7, 816pp, hard back, UK £59, Europe £64, ROW £78
ISBN 0471 11709 9, 816pp, paperback, UK £44, Europe £49, ROW £63

Data and Image Compression

4th edition

tools and techniques

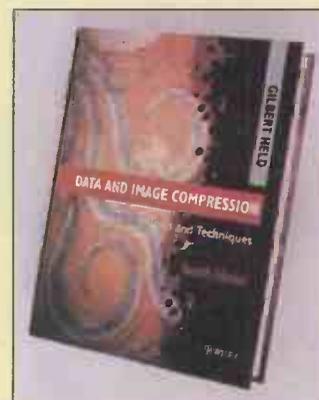Gilbert Held, 4-Degree Consulting, Macon, Georgia, USA
Data and image compression are key issues in computer communications with the increasing demand for data transmission capacity.




Guiding the reader through the main techniques, this book explains how practical data and image compression techniques are now vital for efficient, low-cost transmission and data storage requirements. Building on the success of the previous editions of *Data Compression*, the scope of the fourth edition has been considerably expanded. Now covering image and fax compression, the text has been restructured to take account of the many new advances in this important field. It is also accompanied by an updated disk containing compression routines.

ISBN 0471 95247 8, 450pp+disk, hardback, UK £58.50, Europe £63, ROW £75

Handbook for Digital Signal Processing

S.K. Mitra, University of California and J.F. Kaiser, Bell Communications Research, New Jersey, USA

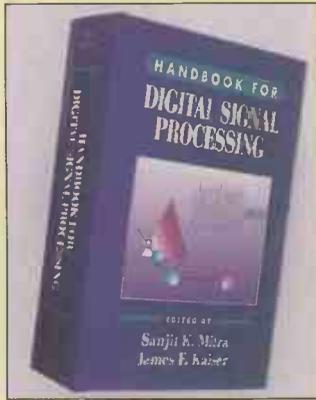This is the definitive source of detailed information on all important topics in modern




digital signal processing. The only current handbook of its kind, it meets the needs of practising engineers and designers of hardware, systems and software. Written by world authorities, the *Handbook for Digital Signal Processing* is supplemented with hundreds of informative tables and illustrations. For professional engineers, designers and researchers in electronics and telecommunications, this work will be an indispensable reference – now and for years to come.

Contents: Introduction; Mathematical Foundations of Signal Processing; Linear Time-Invariant Discrete-Time Systems, Finite-impulse Response Filter Design; Digital Filter Implementation Considerations; Robust Digital Filter Structures; Fast DFT and Convolution Algorithms; finite Arithmetic Concepts; Signal Conditioning and Interface Circuits; Hardware and Architecture; Software Considerations; Special Filter Designs; Multirate Signal Processing; Adaptive filtering Spectral Analysis; Index.
 ISBN 0471 61995 7, 1302pp, hardback, UK £110.50, Europe £118, ROW £138

Solving Interference Problems In Electronics


R. Morrison, Eureka California, USA
 Interference in electronic equipment is a constant source of difficulty for the design and systems engineer. Until now, there has not been a coherent theory that engineers can refer to in their design work and the solution of interference problems has therefore often considered to be an 'art'. Written by an acknowledged expert in the field, this new title provides methods and techniques for testing and evaluating

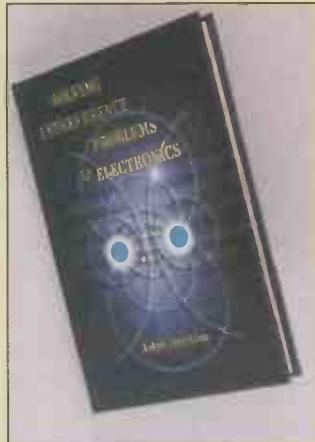designs, and covers interference questions in computer manufacturing and systems design.
 ISBN 0471 12796 5, 206pp, hardback, UK £47.50, Europe £48.50, ROW £54



Diode Lasers and Photonic Integrated Circuits

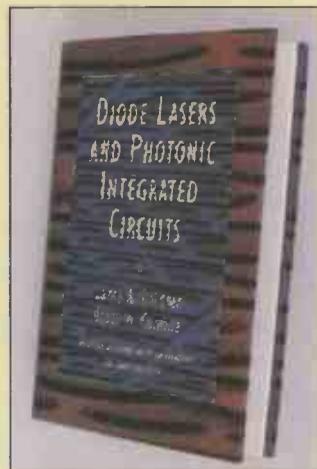L. A. Coldren and S. W. Corzine, both of the University of California, Santa Barbara, USA.
 Diode lasers are found in numerous applications in the optoelectronics industry,



telecommunications and data communications, ranging from readout sources in compact disc players to transmitters for optical fibre communications systems. This new title provides a comprehensive treatment of diode laser technology, its principles and theory, treating students as well as experienced engineers to an in-depth exploration of this fast growing field.
 ISBN 0471 11875 3, 620pp, hardback, UK £63.50, Europe £67, ROW £78

All prices are fully inclusive of packing and delivery

Return to Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following titles:

Qty	Title or ISBN	Price

** All prices on these pages include delivery and package **

Total _____

Name _____

Address _____

Postcode _____ Telephone _____

Method of payment (please circle)

Access/Mastercard/Visa/Cheque/PO

Cheques should be made payable to Reed Business Publishing

Credit card no _____

Card expiry date _____

Signed _____


Please allow up to 28 days for delivery

Exclusive *EW+WW* reader offer – versatile dmm & tester for £14.95

Featuring 10A dc measurement capability and transistor h_{FE} test facility, the DT830B is a compact, 3.5 digit multimeter with six measurement functions. This attractive meter normally sells at £23.44, excluding postage. As a special introductory offer – exclusive to *EW+WW* readers in the UK* – instrument distributor Vann Draper Electronics is offering this meter for just £14.95, fully inclusive of vat and postage.

In addition to reading dc and ac voltage, dc current and resistance, the DT830B has a diode-test function and a transistor h_{FE} range indicating gains from 0-1000. Supplied with test leads and battery, this compact multimeter weighs just 170g and measures 70 by 126 by 24 – truly a pocket sized instrument. Its liquid crystal display has high-contrast 0.5in high characters.

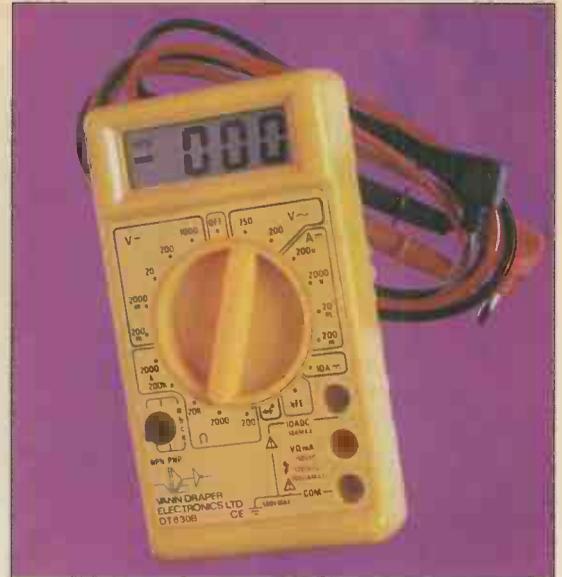*Overseas readers, please read the note on the coupon.



Use this coupon to order your meter

Name
Company (if any)

Address

Phone number
Post code
fax

Make cheques payable to Vann Draper Electronics Ltd
Or, please debit my Master, Visa or Access card.

Card No
Expiry date

Please mail this coupon to Vann Draper Electronics, together with payment. Alternatively fax credit card details with order on 0116 257 0893 or telephone on 0116 281 3091. Address orders and all correspondence relating to this offer to Vann Draper Electronics at Alexander House, Bampton Close, Wigston, Leicester LE18 2RZ.

*Overseas readers can also obtain this discount but details vary according to country. Please ring, fax or write to Vann Draper Electronics.

DT830B key specifications

DC voltage 0.2/2/20/200/1000V

Basic accuracy $\pm 0.5\%$

Input impedance 1M Ω

Max input 1000V dc

AC voltage 200/750V

Basic accuracy $\pm 1.2\%$

Input impedance 0.45M

Frequency range 45-400Hz

Max input 750V ac

DC current 200 μ /2000 μ /20m/200m/10A

Basic accuracy $\pm 1.0\%$

Overload protection 0.2A fused

10A not fused

Resistance 200/2000/20k/200k/2M

Basic accuracy $\pm 0.8\%$

Overload protection 250V dc/ac

Next issue – November – on sale 26 October

Free with *EW+WW*

Cover-mounted TO-92 three-terminal voltage regulator

Manufactured by Zetex, this high-performance 5V regulator is similar to the industry standard 78L05, except that it has a quiescent current of around 350 μ A as opposed to 2-3mA. In addition, it has double the output current, at 200mA, and improved line and load regulation.

Remember... you can reserve your copy of *Electronics World* with your local newsagent.

Simply fill in the card in the magazine to guarantee your monthly copy.



ANCHOR SURPLUS Ltd

The Cattle Market Depot
Nottingham NG2 3GY. UK

Telephone: +44 (0115) 986 4902/
+44 (0115) 986 4041 24hr answerphone
Fax: +44 (0115) 986 4667




Micro Video Cameras

Following last Month's Readers Offer for the 721-S Micro Camera many readers have contacted us asking about other items in our range of Micro Cameras and Security

Surveillance equipment.

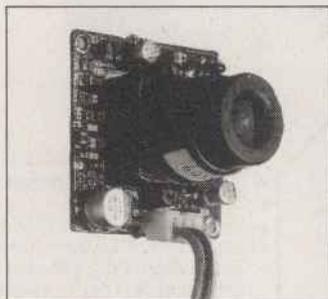We are SOLE AUTHORISED IMPORTERS of the entire range of Cameras and Video Surveillance equipment produced by the world's leading manufacturer. ALL items in the range carry a full 12 Months Guarantee. If you would like to receive our comprehensive catalogue of Cameras and associated equipment please send a large SAE with 48p postage, marked "Camera Catalogue"



Here is a sample of the available stock.

- A-721-S Micro Camera 32mm x 32mm ... £85
- A-721-P Micro PIN-HOLE Camera ... 32mm x 32mm ... £85
- A-921-S Camera with AUDIO ... 30mm x 30mm ... £95
- A-1211 C/CS Mount Camera ... 110mm x 60mm x 60mm ... £110
- A-521 Micro Cased Camera 43mm x 48mm x 58mm ... metal cased ... £120
- 6001-A High Resolution COLOUR Cameras (420 lines) ... 0.45 lux ... £210
- Outdoor Camera Housings ... Aluminium ... £45
- Camera Mounting Brackets ... Universal Mounting ... £5.95
- Camera Switchers ... for up to 8 Cameras ... £85
- Auto Record Controllers ... Allow NORMAL VHS Videos to operate like professional Time Lapse or Security Recorders ... £75
- QUAD-1 Multi Vision Processors ... Digital Freeze ... Quad Pictures etc £275

PLEASE NOTE:

AS A CONTINUED SPECIAL OFFER ALL THE ABOVE CAMERA AND ACCESSORY PRICES INCLUDE VAT AND CARRIAGE TO UK ADDRESSES

Government Surplus Electronics Equipment on Special Offer This Month

- THANDAR TC200 LCD Hand Held Digital Meters ... 0-200uF ... 0-2H ... 0-20MΩ ... ONLY £50
- THURLBY 1905a Intelligent 5 1/2 Digit MultiMeters ... 0.015% acc ... Log, Filters, Math ... ONLY £175
- TIME Electronics 404N/1021 Voltage/Current Calibrators ... 0.05% accuracy ... ONLY £275
- FRANKLIN Wavetek 3600 Power Line Disturbance Monitor + Printer ... LAST 2 NOW ONLY £350
- MARCONI TF9693 + TF2361 + TF9695 VHF Sig Gen / Sweeper sets ...
1Mhz-300Mhz ... 0.01-100Khz sweep rate ... 0-60db attenuators ...
INCL Cased Adaptor sets ... LAST FEW NOW ONLY £125
- COMARK 2007 + 3 "K" type probes ... 0.1°res ... ±0.5%acc ... Cased As New ... ONLY ... £65
- Other Digital Thermometers always in stock ... Please Phone
- SINERGY TRILINE PC5A Energy Monitor LCD Screen ... Colour Plotter 1+3ph ... ONLY £195
- MARCONI TF2300S FM/AM Mod Meter 3.5Mhz-1Ghz AM/AM ... ONLY £75
- HP8616A Signal generators 1.8Ghz-4.5Ghz AM/FM/Pulse £125
- TEK 7603 + 7A18 + 7B50A 4 Channel 100Mhz Scope ... Rack version ... FEW left ... Only £325
- CLARE A217 Earth Bond Testers .. 0-30A ... 0-250MΩ ... FEW left ... Only £75
- FARNELL TM8 Sampling RF Millivoltmeters 1mV-3V 10Khz-1.5Ghz ... FEW left ... ONLY £125
- MARCONI TF2603 RF Millivoltmeters + Accessory Kit ... LAST FEW ... ONLY £60

OPEN SEVEN DAYS A WEEK

Mon-Fri 9am-6pm Sat 8am-4pm Sun 10am-4pm

NO APPOINTMENTS NEEDED. CALLERS ALWAYS WELCOME

All Prices are Ex VAT & Carriage

All items are Fully Tested with Verified Calibration
and carry our Unique 30 Day Un-Conditional Warranty



OSCILLOSCOPE LIVE CHOP Page -0.25

MEASURE MODE
CH 1
CH 2
CHOP
ADD
COMPARE
X-Y PLOT

FREE **µScope**

INPUT 20 volt max.
100 kHz sampling
µScope
to PC printerport

SPECTRUM ANALYZER CH 1 5.937 U

WINDOW
RECTANGLE
HANNING
HAMMING
BLACKMAN
BARTLETT

You get a free **µScope** when you buy a TP508 or a HS508 until september 1st 1996

resolution 8 bits
sampling speed 100 kSamples/sec
input range 2.5V, 5V, 10V and 20V
connects to PC parallel printer port

TiePieSCOPE HS508

- ▶ interface PC parallel printer port
- ▶ sampling speed 50 Msamples/sec
- ▶ resolution 8 bits
- ▶ input range 50 mV/div - 20V/div
- ▶ record length 32KByte/channel
- ▶ price £597.00, incl. software, user manual and 2 probes (1:1/1:10 switchable)

Software for the PC-based instruments

contains an Oscilloscope, a Spectrum analyzer, a Voltmeter, and a Transient recorder. All instruments are controlled in the same intuitive way and provide for saving and recalling waveforms and settings, cursor measurements, hardcopy on matrix/laser printer and online help. Minimum requirements: a 80286-based PC with 2MByte and running MS-DOS 3.3 or higher.

Fax for a free demo disk and catalog of all our products

Easy installation: just plug in and measure

TP508

- ▶ interface PC-XT/AT ISA slot
- ▶ sampling speed 50 Msamples/sec
- ▶ resolution 8 bits
- ▶ input range 5 mV/div - 20 V/div
- ▶ record length 32 KByte/channel
- ▶ price £ 630.00 incl. software, user manual and 2 probes (1:1/1:10 switchable)

Prices are excluding V.A.T.

<p>TiePie engineering (NL) P.O. Box 290 Koperslagersstraat 37 8600 AG Sneek 8601 WL Sneek The Netherlands The Netherlands Tel: +31 515 415 416 Fax: +31 515 418 819</p>		<p>TiePie engineering (UK) 28, Stephenson Road, Industrial Estate, St. Ives, Cambs, PE17 4WJ, United Kingdom Tel: +44 1480 460028 Fax: +44 1480 460340</p>
---	--	--

CIRCLE NO. 122 ON REPLY CARD

Finally an upgradeable PCB CAD system to suit any budget ...

Board Capture

BoardCapture - Schematic Capture

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

£395

Board Maker

BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

£95

BoardMaker2 - Advanced level

- All the features of BoardMaker1 plus
- Full netlist support - OrCad, Schema, Tango, CadStar
- Full Design Rule Checking - mechanical & electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC

£395

Board Router

BoardRouter - Gridless autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

£200

Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec, Roland & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill / Annotated drill drawings (BM2)

Contact Tsien for further information on
Tel 01354 695959
Fax 01354 695957

AWV7:10.30 Tsien (UK) Ltd Aylesby House Wenny Road Chatteris Cambridge PE16 8UT

CIRCLE NO. 123 ON REPLY CARD

Hesitant pricing of the radio spectrum

DTI's proposals for spectrum pricing offer the prospect of very large benefits to the UK economy – provided some remaining traditional assumptions can be relinquished, reasons David Rudd.

David Rudd, Ph.D., F.I.E.E., C.Eng., is an engineering and economics consultant. He can be contacted at 14 Colcokes Road, Banstead, Surrey, SM7 2EW, telephone number 01737 356427.

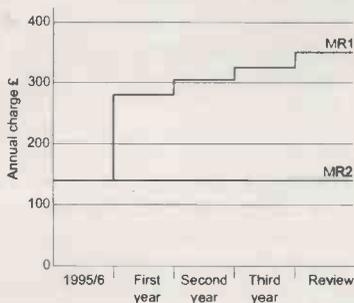


Fig. 1. Private business radio – PBR – shared local 2x12.5kHz channel, 10 mobiles, 25W in two regions. The first region covers London, Manchester and Birmingham, the other the remainder of the country.

The DTI white paper, 'Spectrum Management: into the 21st Century'¹, proposes to introduce a radically new method of charging for radio transmission licences – known as 'spectrum pricing'. It follows a two-year consultation, to which more than 400 spectrum users, industry bodies and others responded. The method of charging will come into operation when Parliament can find time for the legislation.

The purpose of spectrum pricing is to alleviate the present congestion in some parts of the spectrum. Spectrum pricing will also make future allocations and assignments (see Inset 1) depend on the scarcity value of the spectrum in those parts. In this way, users can make better informed choices and potential users who are currently denied licences may be able to obtain them. This will allow them to improve their services to their customers. The principle was discussed in last month's issue².

The proposals are largely a revival and further development of a proposal that I wrote for the Department of Transport's contribution to the Merriman Report in 1983³ and published again in 1986⁴ but which was then pigeon-holed. The main objectives are the same, as are the parameters of the charges, see Inset 2. Even the options by which the spectrum users who face increased charges will be able to avoid or reduce them, so releasing spectrum for other potential users, are the same Inset 3. But there are some serious differences.

Setting the prices


The white paper recognises that the prices should be set to reflect the value of the spectrum – not to maximise revenue. DTI's Radiocommunications Agency (RA) is considering two methods of setting the prices in the parts of the spectrum which come under its management, namely:

- Auctions – the Government's

preferred method for users in the private sector, on the supposed grounds of economic efficiency, transparency and speed. Also because auctions are thought to enable the market rather than the spectrum manager to set the prices;

- Administrative pricing – so called – under which the RA will have to set the initial prices without knowing the true value of the spectrum but which the responders to the consultation markedly prefer.

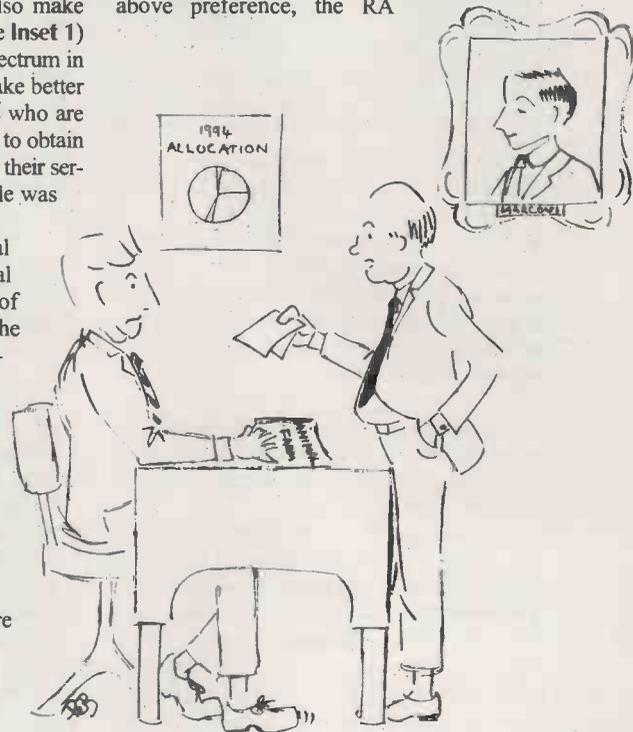Perhaps because of the above preference, the RA



"How should we develop this new policy on spectrum pricing, Sir Humphrey?"

"Well, Bernard, the principle is that all spectrum users are equal. It means they must all pay for their spectrum on a comparable basis."

"Will that include the broadcasters and the MOD, sir?"

"Certainly, but we know of course that some users are more equal than others."

"Yes Minister, Sir Humphrey!"

Inset 1 – Allocation and assignment

Allocation is the identification of frequency ranges for specific applications, e.g. broadcasting.

Assignment is the authorisation for a transmitter to use a specific frequency or channel. These two are roughly analogous to wholesaling and retailing respectively in commerce. Source – glossary of the white paper.

Inset 2 – Parameters of the charges

Administratively determined charges will depend on:

- bandwidth – pro rata,
- effective power – pro rata for private business radio,
- position in the spectrum – specific frequency or channel,
- geographical location.

All are as proposed in the IEE paper of 1986.

Inset 3 – Options for users

Users who face higher charges will have the following options or some of them:

- more spectrum-efficient technology, such as trunking,
- greater sharing with other users,
- migration to less congested bands,
- modifying operating procedures,
- using different means of communication, such as cable or optical fibre

Again, all are as previously proposed.

intends to price the spectrum for the first affected services administratively. They are:

- private business radio (PBR, previously known as private mobile radio),
- public access mobile radio (PAMR),
- personal communication networks (PCN)
- cellular telephony (CT),
- point-to-point fixed links.

The figures show the present charges and some illustrative future charges. The RA intends to phase in the new charges over three years and then review them.

For PBR, Fig. 1, there will be two regions. First is MR1, covering the major cities London, Manchester and Birmingham. Here, the charges will more than double over the three years. Second is MR2, covering the rest of the UK, in which the charges will not rise and may fall.

For PAMR, Fig. 2, the charges will rise by more than five times over the three years and for PCN and CT, Fig. 3, by more than three

Inset 4 – Implications of new charges

The implications of charges for a user will depend on their amount relative to the user's turnover. The white paper estimates that the charges are unlikely to be prohibitive, even for small firms, but of course there may be a few individual exceptions. The crucial question is whether the increases will be large enough to induce some businesses to relinquish spectrum in the congested bands (see Inset 3), thus enabling other businesses, which value that spectrum more highly, to move in. If they are not, they will have to be increased until they begin to have that effect.

and six times respectively.

For point-to-point fixed links, Fig. 4, there will also be two regions. FR1 will cover links with one or both ends in major population centres – Greater London, West Midlands, Greater Manchester, Tyneside, Liverpool, Glasgow or Leeds. Charges in FR1 will rise by up to nearly twelve times, depending on spectrum band and availability. Secondly, FR2 will cover the rest of the UK. Charges will also not rise and may fall.

Those are large increases. Some implications for the users are given in Inset 4. Unfortunately the way in which the prices have been estimated reveals some vagueness – or perhaps misunderstanding – about the objectives of spectrum management. The white paper acknowledges that the prices should reflect the scarcity value of the spectrum – as proposed in 1983 and 1986. However, the initial prices have been calculated by consultants from estimates of the marginal value of the spectrum to the user. Marginal value in that sense is not the same as scarcity value and so may lead to the spectrum being substantially over-priced or under-priced, Inset 5.

Balancing supply and demand

When the charges for spectrum begin to reflect its scarcity value, some users will begin to exercise their options for reducing their charges. This will reduce the demand for spectrum and in turn reduce its scarcity value in those bands. That is the intended effect of spectrum pricing, but that elasticity of demand cannot be measured in advance.

So the initial prices will have to be reassessed as soon as they begin to affect the demand for spectrum. This means it is probably unavailing to try and improve the estimates in advance. However the over-riding, long-term objective – which the white paper fails to emphasise – must be to try and balance the availability of spectrum in any band and the demand for it in that band.

Ideally, as the earlier proposal stated,

“any applicant should be able to obtain a licence at the going rate in any geographical location and any region of the spectrum, but there should be no unoccupied band where the rate is greater than zero. Inevitably, in practice, the rate will often be higher or lower than that, resulting in some queuing for spectrum and some bands being unoccupied, if only temporarily, where the rate is not zero.”

Such imperfections have to be accepted in the interest of making the best use of the spectrum in the long term. They are not adequate grounds

for changing or weakening the objective.

Those difficulties, coupled with fear of unformed public criticism if there are unused bands and/or queues, are probably the underlying reasons for the Government's preference for auctions in the private sector. Here, high prices, unused spectrum and queues can all be blamed on market forces, which are widely acclaimed though poorly understood. The users, on the other hand, probably associate auctions with the much publicised sales by auction of works of art, where speculation and hoarding are rife and prices fluctuate wildly from year to year.

Fluctuating prices are anathema to engineers who are trying to plan long-term projects. Some references to the RA's regulatory powers to prevent major users from hoarding spectrum to exclude competition are too vague to be reassuring. It is significant that the Government does not intend to make the public-sector users bid for spectrum in auctions. Perhaps it will reconsider its preference for auctions in the private sector when the RA has some practical experience of administrative pricing.

The principle of equality

The white paper mentions some well-known technical and international constraints on the extent to which the price mechanism can be applied to the spectrum. They are on a par with the way in which planning legislation effectively constrains the prices at which land is sold or leased. Within those constraints, the earlier proposal emphasised the importance of equality in the treatment of spectrum users. Any discrimination between commercial and non-commercial, public and private, civil and military or major and minor users will inevitably weaken the benefits of pricing on the economically efficient use of spectrum.

Inset 6 shows the percentage allocations to the major and minor user categories over four frequency ranges in 1994. The three major categories – broadcasting (BBC & ITV), defence and telecommunications (BT & Mercury) – together predominate. They occupy roughly two thirds of the total spectrum below 30GHz and one third of the spectrum so far allocated above 30GHz. Minor users – in some nineteen categories – are interspersed between them.

It follows that a small percentage improvement in the spectrum efficiency of a major user, who then relinquishes spectrum, would be worth as much in congestion relief as a large improvement in that of any minor user. So DTI's plans for the future allocations in those three major categories will be particularly important to the success of spectrum pricing.

BT and Mercury are in the private sector and the RA will presumably charge them at the new rates for their point-to-point fixed links. They can have no legitimate complaint. This is because BT's privatisation prospectus warned that the Government intended to commission a feasibility study into “some form of pricing for the radio spectrum in place of or in addition to the present licence fee basis.” In the event, the study report⁵ turned out to be mainly about deregulating and privatising the congested parts

of the spectrum. It was critically reviewed in *EW&WW* – Inset 7 – after which no action was taken on it, but the warning had been given.

Special pleading

However, as regards defence, the white paper states that: “the public sector [including the armed services and the emergency services, one of the minor categories] should have the same incentives for spectrum efficiency as the private sector. Accordingly public sector users will pay administrative charges on a comparable basis to the private sector.” That looks like a move towards equality, but ‘comparable’ is not the same as ‘equal’ and there is no mention of applying the price mechanism to determine

Inset 5 – Value definitions

The scarcity value is the amount which those who do not use the spectrum would be able and willing to pay for it and derive a net benefit from it.

The marginal value, on the other hand, is – according to the white paper – “a measure of the worth of the assignment to the user. It reflects the amount the user would have to pay [for an equivalent service] if deprived of it.” But that amount may be much greater or less than what a different user, with different problems and priorities, would be able and willing to pay.

Inset 7 – ‘Privatisation of the radio spectrum’ *EW+WW*, September 1987

The study reviewed in a my earlier article *Privatisation of the radio spectrum*⁶ had been commissioned by DTI to consider the practicality of spectrum pricing, as had been mooted in 1983 in the Merriman Report. The article criticised the study report for its change of emphasis from pricing to deregulation and in particular for two major departures from the 1983 proposals plus a remarkable privatisation proposal.

The first departure was to exclude both defence and broadcasting from the pricing system, thus leaving only a rump of mainly small users in the system. That would have undermined the operation of the price mechanism so seriously as to invalidate it.

The second departure was to allow revenue maximisation to become the guiding principle in pricing the spectrum instead of the principle of balancing supply and demand. That would have distorted the decisions of the paying users to the detriment of the whole UK economy.

The report went on to assert that there was no prospect of a general spectrum shortage for the next ten or twenty years – which was completely belied by events – and to propose that spectrum management licences should be granted to a limited number of ‘Frequency Planning Organisations’, or FPOs, in the private sector.

By defining the band(s) within which each FPO would operate exclusively, the proposal would have effectively negated their inducements to compete with one another. Moreover they would not have had to pay for the scarcity value of their spectrum but would have been allowed to charge their users as much as they could get. The article dubbed that as a remarkable example of privatisation by gift.

The white paper recognises that revenue maximisation should not be the objective in setting the prices and it does not exclude defence or the broadcasters from the pricing system, but it still instinctively tries to protect both of those categories. It does not propose any FPOs but it talks about the possibilities of ‘Spectrum Management Organisations’, which would undertake some administrative and technical management functions of parts of the spectrum.

have not been much heeded. They are therefore repeated in Inset 8.

Second-hand opinions

The white paper asserts that: “broadcasters have little scope to increase spectrum efficiency using existing technology” but that “digital broadcasting offers the prospect of considerable spectrum efficiency gains.” So the Government “wishes actively to promote the switch to digital” in the hope of generating “exciting wealth creation opportunities.”

continued on page 812...

Inset 6 – Percentage allocations

Allocation to:	BBC & ITV	Defence	BT & Mercury	Other	Unallocated
<1GHz	39.9	28.8	–	31.3	–
1–3GHz	11.7	30.4	20.0	37.9	–
3–30GHz	–	37.8	32.0	26.5	3.7
>30GHz	–	14.3	3.6	28.8	53.3

Source: ‘The Future Management of the Radio Spectrum – A Consultative Document’, Radiocommunications Agency, March 1994.

the size of those public-sector allocations.

On the contrary, the statement is followed by: “the Government’s control of spectrum allocation will ensure that the bodies concerned continue to have access to fulfil their operational needs”, without stating how such needs will be measured. Those allocations are man-

aged by the Ministry of Defence, the Home Office and so on, not by the RA.

The white paper also applies what it calls ‘particular considerations’ to the broadcasting allocations, which are managed by the Radio Authority and the Independent Television Commission – again not by the RA. It claims that the competition for Broadcasting Act licences “imputes a market-determined scarcity value for spectrum”. But again there is no mention of allowing market forces to determine the overall broadcasting allocations. This alone would ensure genuine equality of treatment between the broadcasters and other users and applicants.

The prospect which unfortunately emerges is of several government departments putting forward competing assessments of operational needs on behalf of their sponsored users to justify their retention of their privileged allocations – at much lower rates per kilohertz of bandwidth than private-sector users in immediately adjacent bands. Now an abrupt change in the price of land at, say, the edge of a marsh or a precipice may be justifiable, but the radio spectrum does not have such natural edges. It is continuous from zero to 100GHz and beyond.

Any abrupt change in its price per kilohertz will be a sure indication that it is not being used economically on the lower-price side. By pushing up the prices in the congested parts of the spectrum without inducing the privileged users to relinquish spectrum, such discrimination might bring the whole concept of spectrum pricing into disrepute.

In spite of that argument, many people will probably assume instinctively, as does the white paper, that at least the emergency services – police, fire and ambulance – ought to have special treatment. The counter-arguments have been set out more than once but so far

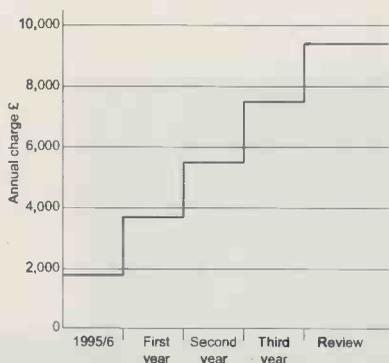


Fig. 2. Public-access mobile radio – PAMR – national 2x12.5kHz channel. Charges will rise by more than five times over three years.

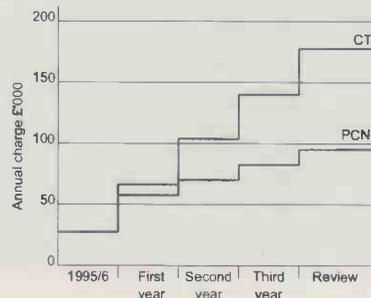


Fig. 3. Personal communications networks and cellular telephony – PCN and CT – over three years, charges will rise by more than three times for PCN and six times for CT.



MARLOW INDUSTRIES EUROPE

Marlow Industries have been leaders for over 20 years in manufacturing fine quality thermoelectric (Peltier) devices, offering a wide range of standard products alongside a custom cooler design service. As a result of listening to our customers, we have applied more resources to the provision of design services for thermal assemblies and their manufacture. If you have a thermal management problem then contact us for assistance.



ST3337
£49.50 + VAT

In addition to the custom assembly route we can provide ready built solutions to thermal management problems.

One such product is the ST3337 (pictured) which provides up to 40 Watts of pumping in a small, convenient package that needs only a 12 Volt supply and is ideal for pic-nic boxes, serum transportation, educational and experimental use, equipment cabinet cooling, dehumidifiers and component cooling.

For further details, to place an order, or to arrange for an engineer to call, contact:

Marlow Industries Europe
7 Laura House, Jengers Mead
Billingshurst, W. Sussex RH14 9NZ
Telephone: 01403 784849
Fax: 01403 782901

CIRCLE NO. 127 ON REPLY CARD

ELECTRONICS WORLD October 1996

WE ONLY USE THE BEST TEST AND MEASUREMENT INSTRUMENTS ON OUR OWN PRODUCTS...



OSCILLOSCOPES

Over 34 models including: Digital, Analogue and Portables. Bandwidths from 5MHz to 150MHz. Sophisticated triggering, single and dual timebases, Multiple channels and large memory Dso's. Prices start from £235 (20MHz 2 Channel £399)

POWER SUPPLIES

Four separate ranges comprising of 40 models from low cost analogue displays to the latest high performance digital units. Providing up to 250 volts and 120 amps with Master-slave, RS 232 and GPIB are available on many models, as are optional rack mount facilities.



AUDIO VIDEO RF

Audio Oscillators, Analysers Wow and Flutter, Millivolt Meters and Distortion Meters Pattern

Generators, Vectorscopes, Waveform Monitors Video Analysers and Noise Analysers.

Five models of AM/FM Standard RF Generators offering a highly stable frequency range of 10KHz to 2GHz with digital readouts for Level, Frequency, Modulation and Memory address.

GENERAL PURPOSE

Frequency Counters, Function Generators plus a complete range of accessories to complement the complete range of instruments.



...NOW YOU CAN DO THE SAME

If you like the idea of working with the best, contact us, we can provide brochures with a complete specification for all our measurement products.

**Kenwood UK Ltd, Kenwood House,
Dwight Road, Watford WD1 8EB, England**

TEL: +44 (0)1923 218794

FAX: +44 (0)1923 212905

KENWOOD

Applying speech storage chips

Colin Attenborough shows how easy it is to apply speech storage and playback chips, using talking weighing scale to illustrate his discussion.

I have designed several sets of speaking weighing scales during the past decade, chip counts dropping as technology advances. The availability of the *ISD1016* speech storage/playback chip, together with Microchip Technology's *PIC16C5x* microprocessors, set my fingers itching to see if I could do the job with just two integrated circuits.

Weight-to-electrical-signal conversion? I cheated by buying a set of low-cost kitchen scales with a digital readout from a well-known chemist. I was rewarded by finding a signal of 10kHz in addition to a 2kHz/lb signal accessible inside, which formed an excellent starting point.

This article summarises what I had to learn about the *ISD1016* speech storage/playback chips before I could complete the scales. Complete details about the scales are not given, but you will learn how to generate speech output for your own application.

Speech storage and playback chips

The *ISD1016* is one of a family of speech/sound storage chips manufactured by Information Storage Devices*, Fig. 1. It stores up to 16 seconds of sound.

All members of the family run from single 5V supplies, draw 20mA when quiescent, and a fraction of a microamp when powered

down. Up to 50mW of audio power can be driven into a 16Ω speaker. Sound input is supplied as a simple analogue signal and a microphone preamplifier with agc is built in.

Different members of the family, which comprises the *ISD1012*, *ISD1016* and *ISD1020*, store differing lengths of sound, of 12 seconds, 16 seconds and 20 seconds respectively. Upper frequency limits differ too, at 4.5kHz, 3.4kHz, 2.7kHz respectively.

Sound data are stored in an analogue electrically erasable and programmable rom with 128K elements, so messages are retained when the chip is unpowered or unplugged.

Analogue inputs and outputs

The main analogue input accepts signals at a maximum level of 50mV_{p-p}. A microphone preamplifier with an associated agc circuit provides a maximum gain of 24dB at low levels. As a result, microphone inputs of a little over a millivolt will drive the device fully.

During playback of a stored message, the amplifier takes its input from the analogue eeprom; however, when /CE is high, the amplifier is fed from an auxiliary input.

Digital inputs and outputs

Eight address lines, A₀₋₇, allow the definition of 160 starting points for record or playback – yes, 160 not 256. When the two most significant address lines are both taken to logic one, the device enters one of several different operational modes, depending on which of the other address lines is taken to logic one. I'll describe these modes later.

Three inputs, PD, /CE and P/R, control the state of the device. Their functions are explained in the sections on simple record and playback. One active-low output, /EOM, is provided which goes to logic zero at the end of a message.

*In the UK, the ISD parts are distributed by Sequoia, 01734 258000.

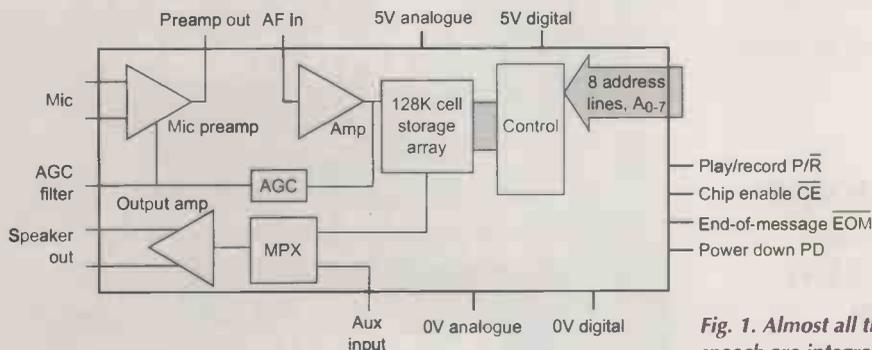


Fig. 1. Almost all the elements needed for recording and playing back speech are integrated into the *ISD1016*.

time removed by editing with the *Soundblaster* system.

I am indebted to Ifor Powell of Creative Labs UK for providing a solution. He was able to send me the source code of a program, written in Borland Turbo C++, which takes a

Soundblaster *.VOC format file and plays it without the delays associated with more direct methods. The program only works with 8-bit mono, or 16-bit mono or stereo files. I have augmented the program to read a list of *.VOC files representing sounds to be stored

on the *ISD1016*, and to provide logic signals via the printer port to control the recording process.

Figure 2 shows the hardware needed to record and play a selected message. A₀, A₄, A₆, A₇, /CE and PD are controlled by software

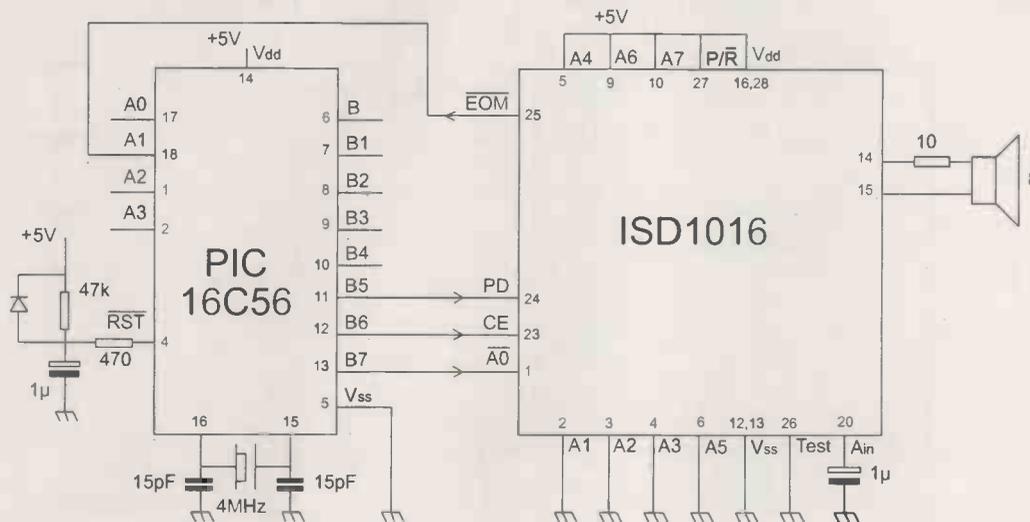


Fig. 3. Interface between PIC processor and speech chip.

List 1. Partial PIC code for speaking weighing scales

```

sub-routine for PIC processor (see fig. 3) to say a word stored in ISD1016
;***** register allocations *****
;***** and their bits *****
RTCC      equ 1
status    equ 3
C         equ 0
Z         equ 2
;ins connect to port A- define port direction in main section of program
in        equ 5
not_eom   equ 1
;outputs are port B- define port direction in main section of program
output    equ 6
A0        equ 7
not_enable equ 6
power_down equ 5
;***** to say word N, load register word_ptr with N *****
word_ptr  equ 7
;***** SUBROUTINE SAY *****
;***** START OF SEEKING & SAYING A WORD *****
;set A0, enable high
say
    movlw 192
    movwf output
;*****
;power down for >12.5ms to reset
;set max prescaler=256
;internal clock 000111
;256us output rate ASSUMING 4MHz clock
;so go round 50 times
    movlw 7
    option
;actual power down
    bsf output,power_down
    movlw (255-50)
    movwf RTCC
delay1
    movf RTCC,0
    btfss status,Z
    goto delay1
;counter is zero
;power up again
    bcf output,power_down
; apply appropriate number of /CE pulses
; is word_ptr at zero?
    cue_again
    movf word_ptr,0
    btfsc status,Z
    goto cued
send_enable
;apply not_enable pulse
    bcf output,not_enable
    bsf output,not_enable
;wait for not_eom
wait_eom
    btfsc in,not_eom
    goto wait_eom
;and wait for it to disappear
wait_end_eom
    btfss in,not_eom
    goto wait_end_eom
    decf word_ptr
;if bit 7 of word_ptr is set, must have been 0 before
; and thus have spoken, so end
    btfsc word_ptr,7
    goto endit
    goto cue_again
cued
;drop A0
    bcf output,A0
    goto send_enable
;***** end of subroutine *****
endit
    retlw 0
    
```

via the printer port; P/R is switched manually. End of message is fed back to the computer via pin 15, an input, of the printer port.

Playback hardware and software

Figure 3 is the circuit of processor/speech chip interface as used in the talking scales. The ISD1016 needs only four connections to the microcontroller. These are A0, /CE, PD outputs from controller and the /EOM input.

List 1 is a subroutine for a PIC16C56 processor; it forms part of the code for the talking kitchen scales. To speak the Nth word, load the register 'wordptr' with N, counting from zero.

It should be possible to add limited speech output to a computer with no Soundblaster card by making a unit to connect to the printer port. Such a unit would contain an ISD device and a PIC processor to wait for a printer enable pulse, produce an appropriate word, and reply with an acknowledge pulse at the end of the speech output.

Recording messages

It is convenient to record the words onto a tape recorder, rather than directly into the SoundBlaster card. When asked to make a recording of text, many people remember whatever they were told about public speaking, and speak at a low rate, ie words per minute. This is to be avoided as the time available for recording is limited, and the user of the talking scales wants to know weights, not listen to a poetry recital.

One rather morbid thought – the user of the complete equipment may want messages recorded by an anonymous person. I've

encountered the "I couldn't keep using it if you fell under a bus" phenomenon.

By the way...

Has anybody noticed how the old imperial weights, with 16 ounces to the pound, sit very nicely with a binary word where the bit zero represents half an ounce, bits one to five represent ounces, and bits six to eight represent pounds? The downside comes in the logic needed to give the correct grammar; for example 'one pound and half an ounce', 'one pound three and a half ounces'. On the other hand, the 'grammar logic' is simpler for metric. Probably the simplest route between metric and imperial is to use $1\text{oz} = (255/9)$ gram – a relationship with an error of much less than 1%.

A simpler system

For a small number of short messages, it is

possible to calculate the start address of each message so that messages don't overwrite each other during recording. A simpler playback circuit can then be used. To record, PD and P/R are taken low; recording starts (at the address defined by the address lines) when /CE is taken low, and ends when /CE is taken high. The circuit of Fig. 4 can then be used for playback. /CE is permanently low. A zero-to-one transition on the clock of the D type sends PD low to start playback; PD is reset to logic 1 when the /EOM output goes low at the end of the message. Where several messages are recorded, the address lines define the message to be played. An advantage of this method of playback is that, as the chip is powered down except during actual playback, the standby current can be very low.

I'm grateful to Cambridge Consultants for permission to publish this article. ■

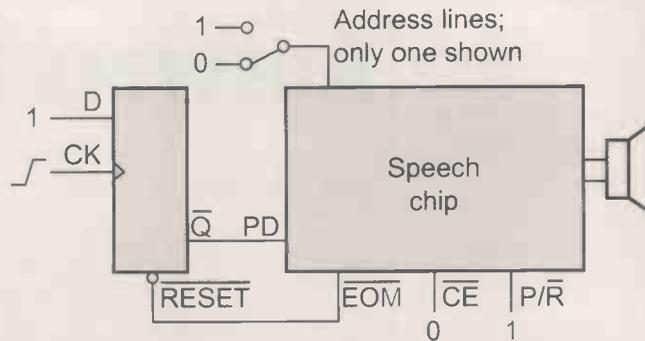


Fig. 4. Low power player; circuit outline. Playback starts when PD is sent low by a rising edge on the D type clock. The message appropriate to the state of the address lines is played. At the end of the message, the /EOM output goes low, resetting the D type and sending PD high. In this state, the ISD1016 draws a fraction of a microamp.

LOW COST DEVELOPMENT SYSTEM

ECAL comprises a versatile relocatable assembler with integral editor which runs about ten times faster than typical assemblers. Support includes 4, 8, 16 & 32 bit processor families including 75X, 6502, 6809, 68HC05/11, 8031/51, H8-300, 78K, PICs, ST6 & Z80/180, 68000, 80C196, H8-500 & Z280.

ECAL is either available for a single processor family or all families.

Single processor version £295
Multiprocessor version.... £395

Overseas
distributors
required

OEMA Ltd.,
7 & 7A Brook Lane,
Warsash,
Southampton SO31 9FH
Tel: 01489 571300
Fax: 01489 885853
CIRCLE NO. 127 ON REPLY CARD

The PC based ECAL hardware emulator is fully integrated with the assembler. Connection is made to the target through the eprom socket so a single pod

can support all processors. Facilities include windows for the inspection or change of registers or memory. You can even watch your program executing at source level!


Download time is about two seconds!

Pods can be daisy-chained for 16/32 bit systems.

Applications include software development, hardware debug, test and, finally, teaching about micro-controllers in education.

ECAL emulator £475

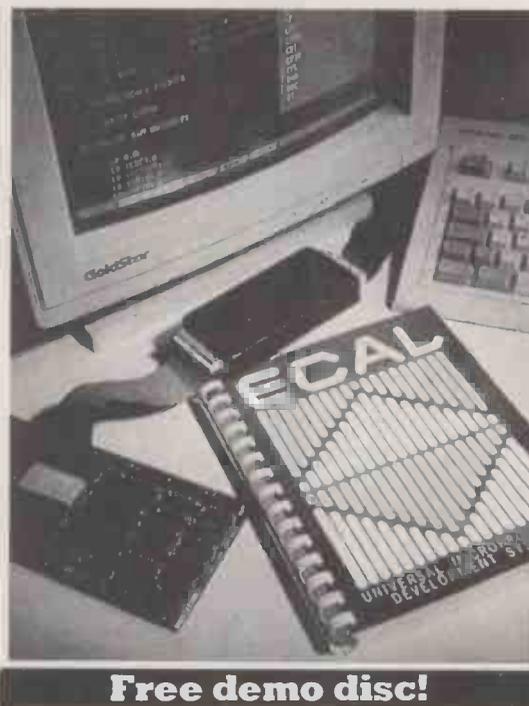Quantity discounts of up to 50% make ECAL software ideal for education.



Free demo disc!

Shifting phases?

I am looking for a circuit to phase shift by 90° the components of a signal with frequencies in the range 10Hz to about 350Hz. Although simple integration or differentiation can achieve this, they do so at the expense of a frequency dependent change in the signal amplitude which I cannot use.

In *Electronics World* of April 1993, Terrence Finegan mentions that such 'a useful analogue function' may be realised differentially with 'all-pass' filters, but this hint has proven insufficient. Text books even mentioning all-pass filters seem to be the exception, at my level of mathematical sophistication anyway.

Are there any readers with a solution to this problem? It would help me and being an unusual function may inspire other interesting designs.

Alan Scrimgeour
London

Looking for diode amplifiers

I am interested in diode amplifiers and their circuit design with regard to: a) detector or power diodes and b) variable capacity varicap diodes. Perhaps several stages would be required to obtain good amplification. I would appreciate any information about their operation and simple circuit to demonstrate the diode amplifier for low frequency rf and also af stages.

Ray Stead
Hampton, Middlesex

Looking for a small uhf tx/rx unit

To me, rf design is still a bit of a black art. Although an experienced analogue engineer, I am woefully short of rf knowledge.

I am working on a direction-finding project that requires a very small uhf transmitter, of about 1mW output and run from a 3V battery. Are there any rf engineers out there who can supply such a circuit or help with the design of such a device?

Mike Bull
Balsham, Cambs

Problem with computer read caches

Standard usage of hard disk integral caches assumes a high percentage of hits. My special requirements normally give zero hits and a greatly increased run time. Logically, with suitable hardware/software, 100% cache hits should easily be possible but so far no one has been able to suggest how. Writing to a cached disk is OK. The problem is reading delays where single runs may last hours, days - even months.

Each run uses four or more files. At any one time programs write to one file and read from two different files. Files are all the same size and may be up to 512Mbytes each. With a fast processor reads can occur tens or hundreds of times per second continuously - with each block, of any size up to a maximum of 32Kbytes, usually in 'random' sequence from anywhere in the relevant file.

The important point is that all read locations are always known before that read file is opened.

My problem is how to advise the disk cache - well in advance of each memory need - to preload the required read blocks. Surely someone has the answer to this problem? Is my type of use really unique?

R.G. Silson
Herts.

Answers to questions

In the July/August issue, P W Fry asked:

"If a short pulse is generated at one end of an open circuit transmission line then that same pulse can be observed to return at a time proportional to the line length and the line velocity factor. Conducting the same test but with the line terminated in a short circuit returns an inverted pulse. Why does this pulse inversion take place?"

If you take a snap-shot of the voltage and current when the pulse was half way down the line, eg at a quarter of total elapsed time, what would we see that would indicate if the pulse was going away from or towards the generator? That is, how does the pulse, when it is half way down the cable, know in which direction it is supposed to be travelling?"

Bryan Hart, of Leigh-on-Sea, Essex was one of a large number of readers who replied. Space permitting, we will show you more replies next month. Thank you to all who replied.

Physically, reflections occur on a line because all the energy in an incident waveform cannot be accepted at a termination. Consider the setup of Fig. 1: a) shows an ideal 50Ω line 10ns 'long'; b) shows a 2V, 2ns pulse applied at x=0, t=0, through a 50Ω source-matching resistance and its composition from step edges. The progress of the pulse down the line

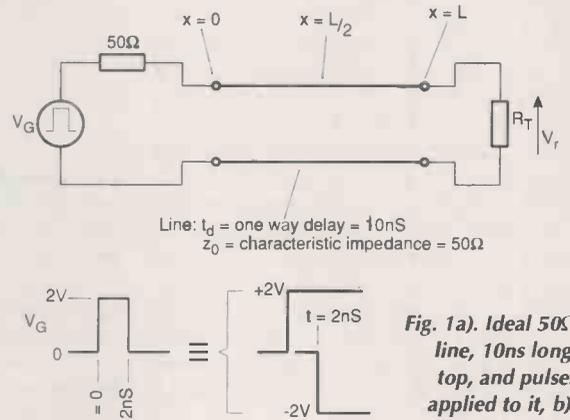


Fig. 1a). Ideal 50Ω line, 10ns long, top, and pulses applied to it, b).

and back again can be visualised using a 'reflection chart' (see, eg, 'Digital signal transmission: line circuit technology' by B. L. Hart, published by Van Nostrand Reinhold, 1987).

Fig. 2a) shows a chart for $R_T = \infty$. In this case there can be no current in the termination and this condition can only be met by having a positive going reflected pulse equal in amplitude to the incident pulse.

Fig. 2b) shows a chart for $R_T = 0$. In this case the boundary condition $V_T = 0$ can only be met by having a negative going reflected pulse.

Figs. 2c) and d) show the conditions at $x=L/2$ for $R_T = \infty$ and $R_T = 0$ respectively. In the case discussed, the negative-going pulse in Fig. 2d) is indicative of motion towards the generator.

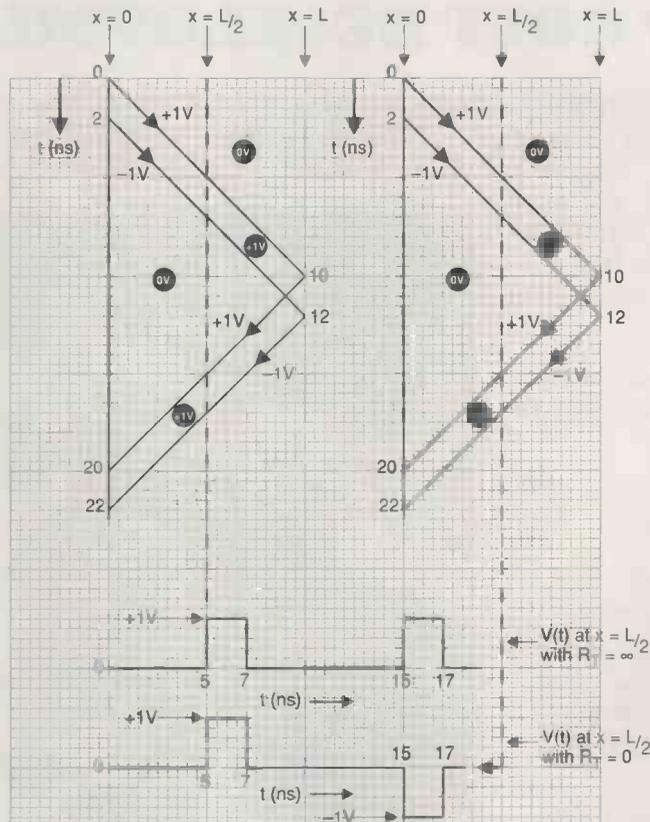


Fig. 2. a) Chart for $R_T = \infty$, b) for $R_T = 0$ and c/d) for the same, with $x=L/2$.

LANGREX SUPPLIES LTD

PHONE 0181 684 1166
 DISTRIBUTORS OF ELECTRONIC VALVES
 TUBES, SEMICONDUCTORS AND I.C.S.
 24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS

FAX 0181 684 3056

	£ p	£ p	£ p	£ p	£ p	£ p	£ p
AZ31	5.00	EL86	2.75	PY500A	4.00	6B47	5.00
CBL31	12.50	EL91	3.00	PY800	1.50	6BE6	1.50
CL33	10.00	EL95	2.00	PY801	1.50	6BH6	2.50
DY86/7	1.50	EL360	18.50	QOV02-6	12.00	6B16	2.25
EB8CC Multi	8.50	EL509	12.00	QOV03-10	5.00	6B86	2.00
E180F	3.50	EM34	15.00	QOV03-20A	15.00	6B07A	3.50
EB10F	22.00	EM81	4.00	QOV6-40A	17.50	6B87	6.00
EABC80	2.00	EM84	4.00	QOV3-12	10.00	6BR8A	4.00
EB91	1.50	EM87	4.00	U19	10.00	6B57	6.00
EBF80	1.50	EN91 Multi	7.50	UABC80	1.50	6B86	4.50
EBF89	1.50	EY51	2.50	UBC41	4.00	6B97	1.50
EBL31	15.00	EY86	1.75	UBF89	£1.50	6B26	2.50
ECC33	7.50	EY88	1.75	UCH42	4.00	6C4	2.00
ECC35	7.50	EZ80	3.50	UCH81	2.50	6C6	5.00
ECC41	3.00	EZ81	3.50	UCL82	2.00	6CB5A	3.00
ECC82	3.00	CY501	3.00	UCL83	3.00	6CB6GA	5.00
ECC83	3.50	GZ32 Multi	8.50	UF89	4.00	6CL5	3.75
ECC85	3.50	GZ33	6.00	UL41	12.00	6CG7	7.50
ECC88 Multi	6.00	GZ34 GE	7.50	UL84	3.50	6CH5	6.00
ECC91	2.00	GZ37	6.00	UY41	4.00	6CW4	8.00
ECH35	1.50	KT61	10.00	UY85	2.25	6D6	5.00
ECH42	3.50	KT66	10.00	VR105/30	2.50	6D05 GE	17.50
ECH81	3.00	KT86	15.00	VR150/30	2.50	6D06B	12.50
ECL80	1.50	W75	9.00	Z759	25.00	6E48	3.50
ECL82	3.00	QAC	2.70	Z803U	25.00	6EH5	1.85
ECL83	3.00	OR2	2.70	ZD21	3.50	6F6	3.50
ECL86 Multi	3.50	CC3	2.50	3B28	15.00	6F07	£7.50
ECL8800	25.00	OD3	2.50	4CX250B STC	55.00	6GK6	4.00
EF37A	3.50	PCF80	2.00	5R4CY	6.00	6H6	3.00
EF39	2.75	PCF82	1.50	SU4G	5.25	6H56	4.95
EF40	4.00	PCF86	2.50	SV4G	4.00	6I5	3.00
EF41	3.50	PCF801	2.50	SV3GT	2.50	6I6	3.00
EF42	4.50	PCF802	2.50	S23	4.00	6J7	4.00
EF80	1.50	PCL82	2.00	SZ4GT	2.50	6JB6A GE	19.00
EF85	1.50	PCL83	3.00	6AH6	4.00	6J6C	20.00
EF86	10.00	PCL84	2.00	6AK5	1.50	6J6C GE	20.00
EF91	2.00	PCL85	2.50	6AL5	1.00	6KG6T	3.00
EF92	2.00	PCL86	2.50	6AM6	2.00	6K7	4.00
EF183	2.00	PCL805	2.50	6AM5	5.00	6K8	4.00
EL12	2.50	POS50	6.00	6AN8A	4.50	6L6	10.00
EL13	10.00	PL36	2.50	6AQ5	3.25	6L6GSYL	12.50
EL14 Siemens	8.00	PL81	1.75	6AR5	25.00	6L6G Siemens	7.50
EL16	4.00	PL82	1.50	6AS6	3.50	6L6G GE	12.50
EL41	3.50	PL83	2.50	6ASTG	9.50	6L7	3.50
EL80	25.00	PL84	2.00	6AT6	2.00	6LQ6	20.00
EL81	5.00	PL504	2.50	6AUSGT	5.00	6O7	4.00
EL84	2.25	PL508	5.50	6AUS	2.50	6RHH/6KNB	12.00
EL84 Multi	6.00	PL509/PL519	8.00	6AW8A	4.00	6S47	3.00
				6B7	4.00	6SC7	3.00
				6BR	4.00	6SG7	2.50
				6BA6	1.50	6S17	3.00

OPEN TO CALLERS MON-FRI 9AM-4PM, CLOSED SATURDAY.
 OVER 6,000 TYPES AVAILABLE FROM STOCK. OBSOLETE ITEMS
 A SPECIALITY. QUOTATIONS FOR ANY TYPES NOT LISTED.
 TERMS: CWO/VISA/ACCESS. POST & PACKING: 1-3 VALVES £2.00,
 4-6 VALVES £3.00. ADD 17.5% VAT TO TOTAL INC. P&P.

CIRCLE NO. 128 ON REPLY CARD

YOUR Ideal Partner in UHF and VHF COMMUNICATION



One stop solutions for all your radio telemetry module needs.

When the success of your products depends on radio telemetry modules, you need a business partner you can trust. A skilled and experienced manufacturer that can offer modules of the highest quality, operating over a wide range of frequencies.

In other words, a partner like Wood & Douglas. Founded on technical excellence, Wood & Douglas is a British company that specialises in the design, development and production of radio-based products. With over 30 staff dedicated to meeting your requirements, the company is able to provide true one-stop purchasing - whatever your RTM needs.

All radio modules - highly functional, capable of meeting a wide range of requirements. Designed to offer efficient, easy-to-use radio telemetry components for system designers, they can open up a whole new world of product possibilities.



From portable bar-code readers to earthquake monitors, Wood & Douglas can help you make the most of the opportunities in radio telemetry.

To find out more about the possibilities, contact...



Lattice House, Baughurst, Tadley, Hampshire RG26 5LP, England
 Telephone: 0118 981 1444 Fax: 0118 981 1567
 email: info@woodanddouglas.co.uk
 web site: http://www.woodanddouglas.co.uk

CIRCLE NO. 129 ON REPLY CARD

10 OUTLET DISTRIBUTION AMPLIFIER 4



A compact mains powered unit with one balanced input and ten AC and DC isolated floating line outputs.

- Exemplary RF breakthrough specifications giving trouble-free operation in close proximity to radio telephones and links.
- Excellent figures for noise, THD, static and dynamic IMD.
- Any desired number of outlets may be provided at microphone level to suit certain video and audio recorders used at press conferences.
- Meets IEC65-2, BS415 safety.

*Advanced Active Aerial 4kHz-30MHz *PPM10 in-vision PPM and chart recorder *Twin Twin PPM Rack and Box Units
 *Stabilizers and Fixed Shift Circuit Boards for howl reduction
 *Broadcast Monitor Receiver 150kHz-30MHz *Stereo Variable Emphasis Limiter 3 *Stereo Disc Amplifier
 *PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and movements *Broadcast Stereo Coders.

SURREY ELECTRONICS LTD
 The Forge, Lucks Green, Cranleigh,
 Surrey GU6 7BG
 Telephone: 01483-275997 · Fax: 276477

New Special Offers

- New mini waterproof TV camera 40x10x15mm requires 10 to 20 volts at 120mA with composite video output (to feed into a video or a TV with a SCART plug) it has a high resolution of 425 TV Lines Vertical and 580 TV Lines horizontal, electronic auto iris for near dark (L.L.C.) to bright sunlight operation and a pinhole lens with a 92 degree field of view, it focuses down to a few CM. It is fitted with a 3 wire lead (12V in and video out) £99.95 + VAT £109.95 or out
- 10+ £89.92 + VAT = £104.95
- High quality stepping motor kits (including stepping motors) 'Comstep' independent control of 2 stepping motors by PC (Via the parallel port) with 2 motors and software £67.00 Ready built £99.00
- Software support and 4 digital inputs kit £27.00
- Power interface 4A kit £36.00
- Power interface 8A kit £46.00
- Stepper kit 4 (manual control) includes 200 step stepping motor and control circuit £23.00
- Hand held transistor analyser it tells you which lead is the base, the collector and emitter and its NPN or PNP or faulty £35.45
- SP5 6v battery £1.20
- Leds 5mm or 5mm red or green .7p each yellow 1p each cable ties 1p each £5.95 per 1000, £49.50 per 10,000
- Rechargeable Batteries
- AA (HP7) 500mAh £0.99 AA 500mAh with solder £1.75
- AA 700mAh £1.75
- CP(H)1 1.2Ah £2.20
- DHP2 1.2Ah £2.60
- D 4Ah with solder £4.95
- Sub-C connectors £3.95
- 1/2AA with solder £2.50
- tags £1.55
- 1/3 AA with tags (Philips) £2.95
- AAA (HP16) £1.75
- CTV £1.95
- Standard charger charges 4 AA cells in 5 hours or 4Cs or 4Ds in 12-14 hours + 1xPP3 (1, 2, 3 or 4 cells may be charged at a time) £5.95
- High power charger as above but charges the AA and Ds in 5 hours. AA's, Cs and Ds must be charged in 2s or 4s £10.95
- Nickel Metal Hydride AA cells high capacity with no memory. Charged at 100mA and discharged at 250mA or less 1100mAh capacity lower capacity for high discharge rates £3.75
- Special offers, please check for availability.
- Sick of 4x25 10mm Nicad batteries with 17x16mm dia with red & black leads 4.8v £5.95
- 5 button cell 6V 280mAh AA battery with wires (Varta 5x250Dk) £2.45
- Shaded pole motor 240Vac 5mm x 20mm shaft £1.95
- 80x65x55mm excluding the shaft £4.95 each
- 115v AC 80C Dc motor 4x22mm shaft 50mm dia x 60mm long (excluding the shaft) it has a replaceable thermal fuse and brushes £1.95 each (£3.95 100+)
- 7 segment common anode led display 12mm £1.95
- MS378 TO3 case variable regulator £1.95
- £1.44 100+ £1.95 each
- £9.95 10+
- £7.95 100+
- £0.45
- £3.95 per 100
- BC347A transistor 20 for £1.00
- BC17505 hex inverter £10.00 per 100

- Used 8748 Microcontroller £3.50
- SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet £1.95
- DC-DC converter Reliability model V1295 12v in 5v out 200mA out 300v input output Isolated (with data) £4.95 each or pack of 10 £39.50
- Hour counter used 7 digit 240v AC 50Hz £1.45
- QUERTY keyboard 58 key good quality switches £6.00
- £9.57 + VAT
- Airpac AR2903-C large stepping motor 14v 7.5' step 270mm 68mm dia body 6.3mm shaft £8.95
- or £200.00 for a box of 50
- Polyester capacitors box type 25mm lead pitch
- 0.9uf 250vdc .18p each
- 1uf .100+ 9p .1000+ .20p each
- 15p .100+ 10p .1000+
- 0.22uf 250v polyester axial leads .15p each
- 0.50uf 250v polyester axial leads .75p 1000+
- 0.22uf 250v polyester axial leads .15p each
- 15p 1000+
- Polypropylene 1uf 400vdc (Wima MKP10) 27.5mm pitch 32x29x17mm case .75p each
- 60p 100+
- Philips 123 series solid aluminium axial leads - 35uf 10v & 22uf 40v .40p each
- 25p 100+
- Philips 108 series long wire 22uf 63v axial .40p each
- 15p 100+
- Multilayer AVX ceramic capacitors all 5mm pitch 100v 100pf, 150pf, 220pf, 10,000pf (10n) 500pf resistor network 10p each 5p .100+ 3.5p .1000+
- 500pf resistor network 10p each 5p .100+ 3.5p .1000+
- 40uf 370v motor start capacitor (dielectric type containing no PCBs) £5.95 or £49.50 for 10
- Solid carbon resistors very low inductance ideal for RF circuits - 2700m 2W, 680hm 2W .15p each 100+
- We have a range of 0.25w, 0.5w, 1w and 2w solid carbon resistors, please send SAE for list
- P.C. 400V PSU (late part 20035-001) with standard motherboard and 5 disk drive connectors, fan and mains inlet/outlet connectors on back and switch on the side (top for tower case) dims 21x14x149mm excluding switch £158.00 for 6
- MX 180 Digital multimeter 17 ranges 1000vdc 750vac 200mhm 200mA transistor Hfe 9x and 1 v battery £200
- AM2 27256-3 Eproms £2.00 each £1.25 500+
- DIP switch 3PC 12 pin (ERG SDC-3025) .60p each
- Disk drive boxes for 5.25 disk drive with room for a power supply, light grey plastic, 67x268x247mm £7.95 or £49.50 for 10
- Hand held ultrasonic remote control £3.95
- CV2466 gate relay, 30x10mm dia with 3 wire terminals, with also work as a neon light £7.50 per 100
- Verbatim R300NH Streamer tape commonly used on nc machines and printing presses etc. it looks like a normal cassette with a slot cut out of the top. £1.95 ea. £3.75 100+
- Heatsink compound tube £0.95
- LV5-2405-2 24v 50mA regulator £1.95
- 8 pin DIL package £4.95
- LM 555 timer kit 16p .8 pin DIL each £1.95

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

- TEKTRONIX T4S465 Dual Trace 100MHz Delay/Cursors £1100
- TEKTRONIX 2445 4Ch, 100MHz Delay/Cursors £1500
- TEKTRONIX 2234 Dual Trace 1.4MHz Delay Sweep £800
- PHILIPS PM295 Dual Trace 350MHz Delay Cursors £2000
- N.P. 54202A Digitizing Oscilloscope 50MHz £1000
- TEKTRONIX 485 Dual Trace 350MHz Delay Sweep £1750
- TEKTRONIX 475 Dual Trace 200MHz Delay Sweep £1500
- TEKTRONIX 465 Dual Trace 100MHz Delay Sweep £1400
- N.P. 1740A Dual Trace 100MHz Delay Sweep £3250
- TEKTRONIX 2215 Dual Trace 60MHz Delay Sweep £400
- TEKTRONIX 2215 Dual Trace 200MHz Delay Sweep £400
- PHILIPS PM217 Dual Trace 50MHz Delay Sweep £2500
- MITACHI V423 Dual Trace 40MHz Delay Sweep £350
- GOLD 051100 Dual Trace 30MHz £200
- WITROW V23 Dual Trace 200MHz Delay Sweep £250
- NIKUSU 5530A Dual Trace 350MHz £200
- GOLD 05300 Dual Trace 200MHz (No handle) £180
- MITACHI V209 Dual Trace 200MHz Mains Battery £400
- TEKTRONIX 468 Dual Trace 100MHz Delay Sweep Dig Storage £750
- MITACHI V504 Dual Trace 40MHz Dig Storage £400
- N.P. 1741A Dual Trace 100MHz Analogue Storage £400
- TEKTRONIX 434 Dual Trace 250MHz Analogue Storage £250
- PHILIPS PM77 Dual Trace 50MHz Scopemeter £800
- LEADER LCD100 DMM Scope 20MHz Dig Storage LCD Display £350
- THIS IS JUST A SAMPLE. MANY OTHERS AVAILABLE
- N.P. 8620C Sweep Dc with 86209Z 2-18 GHz £2200
- N.P. 8655A Syn Sig Gen 0.1-990MHz £1000
- NARCON 2019 Synthesized AM/FM Sig Gen 80MHz-1040MHz £1750
- NARCON 2022 AM/FM Sig Gen 10kHz-1GHz £1000
- NARCON 2018A Syn AM/FM Sig Gen 80MHz-520MHz £1000
- N.P. 8640B 500MHz-512MHz Phase Lock/Syn Dig Pre-readout Sig Gen £800
- N.P. 8620C Sweep Oscillator Main Frame only £200
- RICAL 9081 Syn AM/FM Sig Gen 5-520MHz £450
- NARCON T2331A Oscillator 20MHz-20MHz 0.05% Un-used £225
- NARCON T893A Audio Power Meter Sinead £250
- MARCONI T2163 Attenuator DC-10GHz £100
- R/S Video Noise Meter UFS27 with USF22 40-Hz-10MHz £100
- WITROW 6618A Programmable Sweep Gen 1-2GHz £1000
- N.P. 4271A LC2 Meter with Test Fixture £3000
- R/S VHF Field Strength Meter Type H5-200MHz £250
- N.P. 8160A Programmable Frequency Pulse Gen 50MHz £100
- PHILIPS PM5190 Syn Fun Gen 0.001Hz-20MHz; Sine/Sq/Tri etc. £500
- N.P. 500A Signature Analyser £150
- N.P. 8459 Attenuator DC-18GHz; 0.70dB in 10dB steps £350
- SCHLUMBERGER STABLO CR 4021 Test Set £800
- N.P. 5437A Counter 240Hz HPB £1750
- N.P. 5430A Counter 180Hz HPB £1750
- MARCONI 2435 Freq Meter 10Hz-2GHz £500
- RACAL 1998 Frequency Counter 1.3GHz (Options CPB & High Stab) £800
- MARCONI 2437 Universal Counter/Timer DC-100MHz 8 digit £175
- MARCONI 2438A Frequency Counter 1Hz-30MHz 8 digit £125
- RACAL 999C Frequency Counter 10Hz-200MHz £175
- RACAL 999E Frequency Counter 10Hz-200MHz £175
- N.P. 3435A 3 1/2 digit Multimeter AC/DC/Ohms/Current LED £180
- MARCONI 2510 True RMS Voltmeter with GPE £850
- RACAL 999A Universal Counter 1Hz-30MHz 8 digit £175
- SOLARTRON 7150 6 1/2 3 1/2 digit DMM with IEEE £400
- SOLARTRON 7045 4 1/2 digit Multimeter Volt/Amps/Ohms £800
- FLUKE 801A 4 1/2 digit Multimeter with Adaptor £700
- FLUKE 877 Handheld DMM 3 1/2 digit with case £180
- FLUKE 8842A Digital Multimeter £175
- FLUKE 801BA Bench Portable DMM 4 1/2 digit True RMS £225
- FLUKE 801CA Bench Portable DMM 3 1/2 digit True RMS £175
- WAYER 187A Func Gen 0-200kHz; 4MHz; Sine/Sq/Tri/DC/TTL Pulse etc £100
- THANARD T501 Func Gen 0-200kHz; 5MHz; Sine/Sq/Tri/Ramp/Pulse/etc £175
- GOLD 388 Sine/Square Oscillator 10Hz-100kHz £150
- FREEDRAC T6000 Sine/Sq/Tri 0.1Hz-100kHz £150
- N.P. 438A Power Meter 425W +1 -20V Metered £1250
- N.P. SMTB ANTENNA TEST SET T2-602-4 £2000
- UNADON EP501 Audio Analyser £350
- PHILIPS PM5565 Waveform Monitor £300
- PHILIPS PM5565 Waveform Monitor £300
- FERRROGRAPH RT5 Recorder Test Set £250
- KEMO DMI Variable Filter VBF73 0.1Hz-10MHz £200
- LEADER LSC28 Signal Generator £100
- MARCONI T2710 Universal Bridge Battery Operated £150
- MARCONI T1131A Universal LCR Bridge 0.1% £125
- WATRE KERB G424 Digital Component Meter LCR £200
- HEATHKIT BR RC Bridge £80
- WATRE KERB G424 Digital Component Meter LCR £200
- N.P. 6268 0-40 Volts, 0-30 Amps £900
- FARNELL AP60-50 0-60 Volts, 0-50A Autoringing £500
- FARNELL H30 100-0-30 Volts, 0-100 Amps Metered £180
- FARNELL L10 0-30 Volts, 0-1 Amp Twice £130
- FARNELL L30 0-30 Volts, 0-5 Amps, 2 Meters £150
- FARNELL L30E 0-30 Volts, 0-5 Amps Metered £180
- FARNELL L30-2 0-30 Volts, 0-2 Amps Metered £180
- FARNELL L30-3 0-30 Volts, 0-1 Amp Twice £130
- FARNELL L30-1 0-30 Volts, 0-1 Amp Metered £85
- TRUBILL-THANARD TSP3222 Programmable 32mV, 22mV, 2mV GPIB £300
- TRUBILL PL32000 0-30V, 0-20A Twice Digital £225
- BRANDENBURG Model 428 +1 -20V Metered £150

NEW EQUIPMENT

- HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz Delay Timebase £847
- HAMEG OSCILLOSCOPE HM1004 Dual Trace 50MHz Delay Sweep £553
- HAMEG OSCILLOSCOPE HM1003 Dual Trace 30MHz Component Tester £420
- HAMEG OSCILLOSCOPE HM305 3 Dual Trace 20MHz Digital Display £683
- All other models available - all oscilloscopes supplied with 2 probes
- BLACK STAR EQUIPMENT (P&P all units £5)
- APOLLO 100-100MHz Counter/Timer Ratio/Period/Time Interval etc £234
- APOLLO 100-100MHz Counter/Timer Ratio/Period/Time Interval etc £232
- 1325 Frequency Meter (As above with more functions) £180
- NIPTON 800 FUNCTION GEN 0.1Hz-500kHz; Sine/Sq/Tri £243
- ORION COLOUR BAR GENERATOR P&P Video £120
- All other Black Star Equipment available £150
- HAMEG OSCILLOSCOPE Probes Switchable X1 x10 P&P £37

Used Equipment - GUARANTEED. Manuals supplied if possible. This is a VERY SMALL SAMPLE OF STOCK - SAE or Telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: (01734) 268041. Fax: (01734) 351696
Callers Welcome 9am-5.30pm Monday to Friday (other times by arrangement)

CIRCLE NO. 131 ON REPLY CARD

M & B CO. LTD

THE NORTH'S LEADING USED TEST EQUIPMENT DEALER

- OSCILLOSCOPES**
- HP 54111D 500 MHz digitizing scope (colour display) £3000
- HP 54112D 100 MHz channel digitizing scope (colour display) £2250
- TEKTRONIX 2230 100 MHz digital storage scope £2250
- TEKTRONIX 2236 60 MHz digital storage scope £1500
- TEKTRONIX 2445 150 MHz 4 channel GP-IB OPT £400
- TEKTRONIX 2246 100 MHz 4 channel £1400
- TEKTRONIX 222 100 MHz portable digital storage scope (new) £950
- TEKTRONIX 784 (A27A) 70 MHz 2 channel £1250
- TEKTRONIX 2211 60 MHz dual trace £400
- TEKTRONIX 2215 60 MHz dual trace/delayed TB £400
- TEKTRONIX 475A 250 MHz 2 channel £495
- TEKTRONIX 475 200 MHz dual trace £495
- TEKTRONIX 465B 100 MHz 2 channel £435
- TEKTRONIX 434 25 MHz 2 channel scope £400
- TEKTRONIX 434 25 MHz 2 channel scope £400
- TEKTRONIX SC594/TM594/DMS91 80 MHz scope/DVM £450
- TEKTRONIX 21 60 MHz 2 channel portable scope £225
- BALLANTINE 1022B 25 MHz milliscopes £225
- PHILIPS PM3375 100 MHz 250 MSa GP-IB £1650
- PHILIPS 3055 50 MHz dual trace £425
- PHILIPS 3067 495 MHz dual trace £495
- PHILIPS 3244 50 MHz 4 channel oscilloscope £400
- IWATSU SS6122 100 MHz 4 channel with cursors £800
- IWATSU SS5710 60 MHz 4 channel £400
- LEADER LBS024L 40 MHz dual trace delayed TB £300
- GOLD OS3000 20 MHz dual trace £200
- GOLD OS4000 10 MHz digital storage £195
- UNADON G500 D2 20 MHz compact dual trace scope + probes £160
- SPECTRUM ANALYSERS**
- TEKTRONIX 2710 10 KHz-1.8 GHz £4000
- TEKTRONIX 2710 10 KHz-1.8 GHz OPT 001/003/014 new unused £4950
- TEKTRONIX 7112 10 KHz-1.8 GHz & mainframe £1600
- HP 8410/8411A network analyser 0.1 MHz-12.4 GHz £900
- HP 8528B 100 MHz-1.5 GHz High spec (new) £1000
- HP 8525A 64 MHz-100 MHz dynamic signal analyser (1 year HP cal) £6000
- HP 8567A 100 MHz-2 GHz spectrum analyser £4500
- HP 8903A 20 Hz-100KHz audio analyser £2800
- HP 8754A 4 MHz-100 MHz network analyser £2800
- HP 3580A 5 Hz-50 KHz audio analyser £850
- HP 1407/8552B/8553B 1 KHz-1.1 GHz spectrum analyser £450
- HP 1417/8552B/8554B 100 KHz-1250 MHz £1000
- HP 1417/8552B/8555 100 KHz-1.2 GHz £1000
- HP 8904A DC-600 KHz multifunction synthesizer £4000
- HP 3334B 10 Hz-21 MHz synthesizer/level meter £450
- HP 3320A frequency synthesizer 0.1 Hz-13 MHz £450
- HP 8406A comb generator £250
- HP 2114A high power generator 10 Hz-10 MHz OPT 001 £750
- HP 8005B 0.3 Hz-20 MHz pulse generator £1500
- HP 8112A 50 MHz programmable pulse generator £1500

- HP 8616A 1.8 GHz-4.5 GHz signal generator £150
- HP 8645B 10 MHz-520 MHz RF generator £495
- HP 3200B 10 MHz-50 MHz oscillator £200
- TEKTRONIX 2901 time mark generator £2000
- FLUKE 11A 0.1 Hz-1 MHz synthesizer generator £1000
- ROHDE & SCHWARTZ APN62.0 1 Hz-20 KHz LF gen (new) £2000
- FARNELL SSG2000 10 KHz-2000 MHz synthesized gen (as new) £2000
- POLARAD 106E7 1.8 GHz-4.6 GHz with modulator £650
- GIGA GR101A 12 GHz-18 GHz pulse generator (as new) £650
- POLARAD 1105EL 800 MHz-2.4 GHz signal generator £500
- MARCONI T2019A 80 KHz-1040 MHz synthesized £2000
- MARCONI T2018A 80 KHz-520 MHz synthesized £1000
- MARCONI T2018 80 KHz-520 MHz £750
- MARCONI T2015171 10 MHz-520 MHz (with synchroniser) £300
- MARCONI T2008 10 KHz-510 MHz signal generator £1000
- MARCONI T2016 10 KHz-120 MHz (£225M) T2016A £225
- ROD-L 11008Y55 hines tester £225
- MARCONI 60548 2 GHz-4 GHz signal source £225
- ADRET 2230A 20 Hz-1 MHz synthesized source £195
- THANARD T5650 0.005 Hz-5 MHz pulsed/function generator £225
- WAYER 193 20 MHz sweep modulation generator £400
- WAYER 171 2 MHz synthesized function generator £495
- FARNELL LFM3 audio oscillator £150
- TEST EQUIPMENT**
- ELECTRO-METERICS EMC-25 MK III interference analyser £2000
- BALL FRACOR MMT-18 rubidium frequency standard £4000
- TRAFOR 327E frequency difference meter £2000
- WAVAY 108 10 MHz in RF power meter DC-26 GHz £1200
- ANRITSU MS45A 3 GHz error detector £1500
- TEKTRONIX 1141/SPG11/TSG11 pal video generator £1500
- TEKTRONIX 145 pal lock test signal generator £1500
- TEKTRONIX 1141/SPG11/TSG11 vector scope £1500
- TEKTRONIX A6902A oscilloscope £450
- YOKOGAWA LR800 8 pen recorder £1000
- SCHLUMBERGER 7702 digital transmission analyser (new) £650
- SCHLUMBERGER 4900 AF/RF measuring unit £400
- SCHLUMBERGER AF403 3 tone generator/modulator £150
- ROD-L 11008Y55 hines tester £225
- WANDEL & GOLTERMAN PSS11 level generator £650
- MARCONI T23245 mod meter 50 KHz-2.3 GHz (468B-527G) £2000
- MARCONI T23216 true RMS voltmeter £695
- HP 435A/8481A 100 KHz-4 GHz RF power meter £850
- MARCONI 6593A VSWR indicator £495
- MARCONI T23432A 10 Hz-560 MHz frequency counter £125
- EIP 535 10 Hz-18 GHz microwave frequency counter £450
- HP 11665B 0.015-18 GHz modulator £450
- HP 5335A 200 MHz universal systems counter £1200
- HP 5335B universal frequency counter 2x 100MHz + DVM £1500
- HP 5342A 500 MHz-18 GHz frequency counter OPT00A-1 sensors £1200
- HP 5345A 1.5 MHz-26.5 GHz counter/3555/5355A + B sensors £2000
- HP 436A RF power meter £650
- HP 435B/8481A/8484A/1708A 10 MHz-18 GHz (new) £1100
- HP 435B/8481A 10 MHz-18 GHz RF power meter £800
- HP 432A/8478A 10 MHz-10 GHz RF power meter £375
- HP 8087A distribution amplifier (NEW) £750
- HP 5477A RF power meter/calibrator £225
- HP 5351C 1.5 Hz-50 KHz selective voltmeter £400
- HP 333A distortion analyser £295
- HP 11710A down converter £250
- HP 3730B 173 MHz microwave oscillator £3500
- HP 3400A true RMS voltmeter (analogue) £145
- HP 3403C true RMS voltmeter (digital) £195
- HP 3406A 10 KHz-1.200 MHz RF sampling voltmeter with probes £200
- HP 3446A 4.5 digit autoringing multimeter £200
- HP 3437A 3.5 digit high speed system voltmeter £280
- HP 3455A 6.5 digit digital voltmeter £495
- HP 3455A 6.5 digit digital voltmeter/auto cal (LCD) £195
- HP 5009A 4 digit digital voltmeter/auto cal £195
- HP 5005A signature multimeter £300
- HP 6032A systems power supply 0-60V/0.5 amp 1000W £800
- HP 6032A systems power supply 0-60V/0.5 amp 1000W £800
- HP 6253A DC power supply 0-20V/0.2 amp £200
- HP 6825A power supply/amplifier -20v to +20v/0.2 amp £250
- HP 6268B DC power supply 0-40V/0.3 amp OPT 005/010/040 £580
- BIRD 43 RF wattmeter £395
- BIRD 8323 30dB coaxial attenuator 100w £600
- EKACT 234 precision current calibrator £195
- FLUKE 103A frequency counter £2250
- FLUKE 3330B prec constant current/voltage calibrator £495
- BALLANTINE 6125C prec time/amplitude test set £295
- FLUKE 103A frequency counter £2250
- ALTECH 5333X-11 calibrator (1 HP3555/1HP3550 ATT) £350
- KEMO DP1 1 Hz-1000 KHz phase meter (new) £150
- WAYNE KERR CT496 LCR meter battery portable £675
- RADOMETE R1 RLC component comparator £150
- AVO 215-L/2 AC/DC breakdown/vonstation tester £400
- FERRROGRAPH RT5 Recorder £200
- BRADY S12250 electronic load £250
- FARNELL TMS 10 Hz-1000 MHz true RMS sampling voltmeter £350
- SIEMENS D2108 20 KHz-30 MHz level meter £350
- SIEMENS D2108 20 KHz-30 MHz level meter £350
- NARDA 3001 40 MHz-950 MHz directional coupler 20db £120
- NARDA 3041 20-500 MHz 100 dB directional coupler 20db £125
- NARDA 3042 20-30 GHz-3 GHz 20db directional coupler £150
- NARDA 1064 10 4 GHz-10 GHz 10 dB directional coupler £175
- NARDA 60132 solid state amplifier 8 GHz-12 GHz £150
- SATROSA ANH 1.5 MHz-2 GHz automatic modulation meters £175
- ROHDE & SCHWARTZ NKS RF power meter £600
- WATKINS JOHNSON Receivers. Various types in stock, tel. for details £400
- REDIFUSION R500 100 Hz-30 MHz receiver £450
- RACAL RA1779/81A 1107.30 MHz receiver £1700
- RACAL RA1772 30 MHz receiver £750
- RACAL 3209/2294/2295/2296 20 MHz-1000MHz receiver £1000
- RACAL 9043 two tone oscillator £200
- RACAL 9008 1.5 MHz-2000 MHz automatic modulation meter £300
- RACAL DANA 990-40 50 Hz universal counter timer £95
- RACAL DANA 991 10 Hz-200 MHz frequency counter £165
- RACAL DANA 996 10 Hz-200 MHz timer/counter £165
- RACAL DANA 9914 10 Hz-200 MHz frequency counter £160
- EIP 535 10 Hz-18 GHz microwave frequency counter £100
- RACAL DANA 9916 10 Hz-520 MHz frequency counter £155
- RACAL DANA 9919 10 Hz-100 MHz frequency counter £295
- RACAL DANA 9908 10 Hz-100 MHz universal counter timer £400
- RACAL DANA 9921 10 Hz-300 MHz frequency counter £100
- RACAL DANA 991 10 Hz-160 MHz universal counter timer £395
- RACAL DANA 1992 10 Hz-100 MHz frequency counter £600
- HP 4325A 100 MHz RF voltmeter £1500
- RACAL DANA 9301A true RMS RF millivoltmeter £250
- RACAL DANA 6000 microprocessing digital voltmeter £250
- BRUEL & KJER 2283 precision sound level meter/WB0812 filter £400
- BRUEL & KJER 2283 precision sound level meter/WB0812 filter £400
- DATRON 1071 optical digital multimeter £1750
- FLUKE 8506A thermal RMS voltmeter £2950
- FLUKE 5200A programmable AC calibrator + 205A precision power amp £4000
- FLUKE 8400B digital callibrator £4950
- RF MICROSYS INC AN/TRC 176 VHF/UHF K & L filter £400

ALL PRICES PLUS VAT AND CARRIAGE - ALL EQUIPMENT SUPPLIED WITH 30 DAYS WARRANTY

86 Bishopgate Street, Leeds LS1 4BB
Tel: (0113) 2435649 Fax: (0113) 242688

CIRCLE NO. 132 ON REPLY CARD

LETTERS

Letters to "Electronics World"
Quadrant House, The Quadrant,
Sutton, Surrey, SM2 5AS

Great balls of fire

In July/August 1996's Research Notes, you had an item entitled 'Ball Lightning Comes Down to Earth'. I experienced ball lightning as a young farm boy in southern Minnesota back in the late forties. I also have acquaintances who have had such experiences, including a couple of physicists, of which I am now one.

Mr. Lowke's description may explain some of the movement, but, it falls short of explaining how it is formed. I have studied this quirk extensively. Unfortunately, it never lasts long enough to be properly measured, nor does it seem to occur when one is ready to study it. However, experience and observations do allow this tentative conclusion; the soap bubble model seems to at least first order describe its general characteristics.

Generally, when ball lightning does occur, there have been 'sheet lightning discharges' in the vicinity. A strong breeze, turbulent wind or other that can form a distortion in the plasma sheet that makes up sheet lightning will under certain circumstances allow a closed plasma bubble to form. It can be anywhere from a few centimeters to tens of centimeters in diameter. It is generally blue-white in color and has the distinct sound of bacon frying along with the smell of ozone and $NxOx$ products.

The one I encountered as a youngster was about 10 to 15cm in diameter. It appeared shortly after an extremely loud and bright lightning discharge near the house and drifted

through an open window of the upper floor bedroom that I was occupying.

As I remember, it moved about the foot board of my brass-pole bed and illuminated the room with blue-white light. It lasted only about 5 to 10s at the most. The ball quickly drifted up and over to a wall, dissipating itself with an enormous flash similar to a photo flash bulb going off.

The next morning my father inspected the wall for damage but found none – no sign whatsoever that it had touched the wall. There is no doubt in my mind that this was a spherical shell of ionized air molecules that was comprised of a great deal of charge. One could feel the electric effect it produced, similar to having a hand on a high-voltage generator.

Another story by a physics professor that I had at the university was about one that came down from an elaborate transformer platform at a linear accelerator facility during a lightning storm. This ball was similar in size, color, noise, etc., and followed a 440V, three phase conduit to where a large polarized receptacle was located. When the ball went in front of the receptacle, it was reported that eye witnesses saw a brilliant flash and the entire receptacle exploded outward with bits of insulator and other over the area. The breaker was opened at the event.

Now that I am ready and know what to look for in clues on the subject, I have yet to experience another.

D. D. Schendel
Arizona
USA


Forget thermal effects

Douglas Self's article on 'Thermal dynamics in audio power' was well done, but was it necessary?

As J. Linsley Hood has explained in 'The art of linear electronics, Butterworth, 1993', there is another way to approach Class B amplifier design. It is to use my 'Class S' design shown on p. 165. fig. 9.34.

My original 1982 article in this magazine (Class 'S', *Wireless World*, p.38. Sep. 1982) explained the operation of the circuit. It clearly implied that Class 'S' is immune to thermal variations and can be built without setting up. The cross over distortion performance is excellent, even if a normal tolerance variation exists on the bridge resistors. Only the large signal performance is affected by such resistor tolerances.

Dr Aubrey Sandman
London

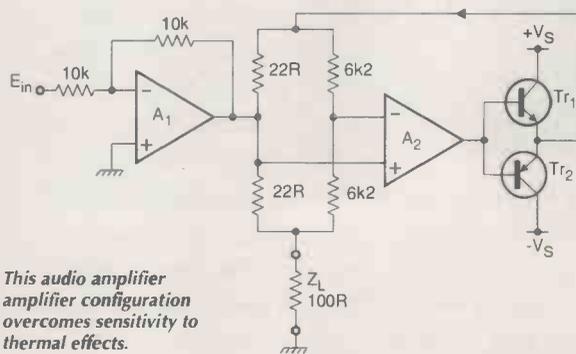

This audio amplifier amplifier configuration overcomes sensitivity to thermal effects.

Ether or not?

No physical theory can unify electricity and gravity. Or can it?

In response to Ivor Catt's call for new ideas in electromagnetic theory (Letters May 1995), a paper which seems to mechanistically and numerically unify electricity and gravity – apparently proving the ether hypothesis correct – has been written by Nigel Cook.

Interested readers may obtain eight-page copies of the complete theory for a copying, postage and administration charge of £4.50 by writing to the editorial offices.

Setting the record straight

Regarding the abusive letter from Mr M.Jones on crossover networks, I spent a substantial amount of time in the Keele University library, so the comment about homework I shall ignore.

Taking some of his points in order:

a) If correctly designed networks are specifically designed for a predetermined unit, then why do companies like Maplin sell crossovers at up to £99 each to put in your own enclosure?

c) Is Mr Jones seriously suggesting that the average hifi enthusiast who wants to build up a loudspeaker unit, get hold of an Audio Precision test set (at huge cost) and measure the performance of the unit, before they actually build their crossover network. Come on, be realistic.

d) The purpose of the article was to provide a cheaper alternative to buying the expensive crossover units.

e) The article specifically mentioned the use of emi power toroids. Toroids as anyone knows don't interact magnetically with each other, due to the closed magnetic circuit. So orientation is irrelevant. 10 years of working in the video filter industry verify this. For example using 720-2 toroids actually touching each other for the filter and group delay equaliser sections does not cause any major problems. The unit that was built up was tested at 100Wrms without problems, apart from the neighbours.

At 50p each, the toroids aren't expensive.

g) Cascading high and low pass sections to achieve a band pass response is quite a common technique actually. See the relevant sections in Williams. This also eliminates the problem of requiring more inductors at ridiculously high Q values as generated by the low pass to band pass transform. Again see Williams. If Mr Jones had bothered to look at the plots, he would have seen (in Fig 4a) that it is entirely possible to cascade sections as long as an adequate bandwidth is maintained. The reason for using C (not C++) was that it was available. Any language could have been used, or even a spreadsheet as Mr Jones suggests, however the output from the program is a bit neater as to documentation purposes. If I had only used 1 decimal digit precision, someone would have complained. You can't please everyone. If you don't want the 6 digit precision, then its a trivial matter to change the output formatting, that is unless Mr Jones cannot understand a simple language like C.

Finally, it is obvious that Mr Jones works for a crossover manufacture, by what he says at the end of point d, so he obviously doesn't want to lose business, well, thats the way the cookie crumbles, I'm afraid.

Bill Teleki
Newcastle-Under-Lyme
Staffordshire

Raked over the coals

In his letter in the July/August issue, G.E. Miller writes: "I have long ago learned that if one side in a debate or discussion resorts to personal abuse then it is clear that that person cannot make a case for his views."

The next paragraph of Mr. Miller's letter is devoted to personal abuse.


Therefore...
J.S. Linfoot
Oxford

Self Preamplifier '96

On Fig. 11 of Doug Self's preamplifier article in the September issue, R_{55} should have been 100Ω. One potentiometer is unmarked. As mentioned in the text, all potentiometers are 10kΩ.

Also, R_{207} should be reduced to 10Ω to accommodate a BC184L whose gain specification is on its minimum. Finally, C_{32} should be polyester, not ceramic as indicated. Apologies for these misprints. ■

Sell Out at Europe's Biggest Cable Show!

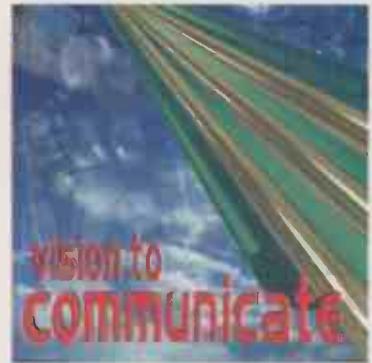

ECC'96, Europe's cable communication showcase, has completely sold out of stand space, over four months before it is due to take place.

A 30% increase in the size of the event has required a move to a larger venue, the National Hall Olympia, and now even this extra space has been taken.



ECC'96 takes place in London between 15 & 17 October 1996.

Asked to explain the event's success Sharon Chapman comments: "ECC'96 is the only

forum where there is significant representation from cable, telecoms and programming companies. I know many exhibitors are using the event to launch new products, making ECC'96 one of the few truly international exhibitions held in the UK".



200 Companies

With over 200 companies on display, the exhibition is an event in itself. By far the largest show outside the US, ECC'96 will be welcoming visitors literally from around the world.

Top Names in Cable, Telecoms & Programming

ECC'96 is the forum to launch new to market products. Among its 200 plus exhibitors, the show sees existing favourites such as Motorola, GI, Ericsson, United Artists, Sky and Nortel, joined by newcomers IBM, GEC Marconi, Nordex, Pace, Paramount and Fujikura,

Arena

Free to all exhibition visitors and one of the most dynamic parts of the convention is the ECC Arena. A show within a show, the Arena allows visitors to see launches, demonstrations, product applications as well as put top industry personnel through their paces.

Comprehensive Conference

Many visitors take advantage of the modular conference programme. Ian Lang, President of the Board of Trade and Martin Bangemann, Director DGXIII of the European Commission lead the plenary session on day one, Tuesday 15 October. This focuses upon the future and new challenges facing the industry and covers topics from digitalisation to finance and strategy.

Day two, Wednesday 16th, has top names from the BBC, Sky and BT discussing cable's competition. The European dimension has a complete session in the afternoon.



Thursday 17th deals in marketing with highlights on new programming, customer services, market penetration and customer retention.



Social Programme

"The emphasis we place on networking has contributed to the success of the event" says Sharon Chapman. ECC'96 provides a unique setting for making contact with the industry's movers in an informal and relaxed atmosphere. This year is no exception with the World Cable Dinner for 800 on the evening of Tuesday 15th, and the ECC Gala Party the following evening for 1000.

FOR YOUR FREE TICKET:

TEL: +44-171-222 2900

FAX: +44-171-791 1471

OR RETURN THE COUPON



For full details Call: +44-171 222 2900 Fax: +44-171 799 1471

- Please send me my free ticket plus travel & hotel information
- Please send me detailed conference booking information

Name.....
 Company.....
 Address.....
Zipcode.....Country.....
 Tel.....Fax.....

Organised by the Cable Communications Association, Artillery House, Artillery Row London SW1P 1RT, UK

CIRCLE NO. 133 ON REPLY CARD

STEPPING OUT

Ian Hegglun's new voltage multiplier promises higher efficiency and simpler implementations.

Cockroft-Walton voltage multipliers or charge-pumps can eliminate inductors in some power converters such as negative rail generators and voltage doublers. Higher conversion steps are possible by cascading doubler stages. But losses increase rapidly with higher ratios making high ratio multipliers less practical than inductor based converters.

A recent multiplier arrangement improves efficiency¹. To demonstrate this a 12V to $\pm 50V$ dual rail 300W converter is presented. The Mosmarx multiplier² is another technique that achieves high efficiencies, but it is limited in voltage by mosfet voltage ratings. The new arrangement is not limited and can produce hundreds of kilovolts.

Recent improvements in low-impedance electrolytics, mosfet drivers, mosfets and lower cost schottky diodes make voltage multipliers attractive for a wider range of power converter applications. Adding the improved multiplier gives higher efficiency, power density, i.e. W/kg, and specific power, W/cm³, with values similar to inductor based dc-to-dc converters at similar frequencies. Also, the problem of efficient voltage regulation with multipliers appears to be overcome in the demonstration circuit.

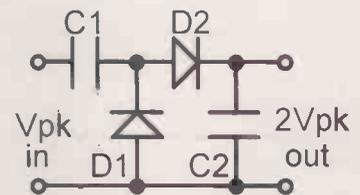


Fig. 1. The Cockroft-Walton doubler is the simplest voltage multiplier.

Conventional half-wave multipliers

The simplest multiplier, the Cockroft-Walton voltage doubler, is shown in Fig. 1. Output voltage reaches twice the peak input voltage, but when loaded the output voltage falls by two diode volt drops plus an ac ripple component. This is because of current flow in the capacitors.

Figure 2a is a simple voltage doubler based on a popular mosfet half-bridge driver. Negative rail generator Fig. 2b is similar to the doubler circuit but it sits on the 0V rail with diodes and capacitors reversed. These circuits can be very efficient with low on resistance mosfets, schottky diodes and low impedance electrolytics. Mosfet driver ics greatly simplify the circuitry.

Higher multiples are made from cascading

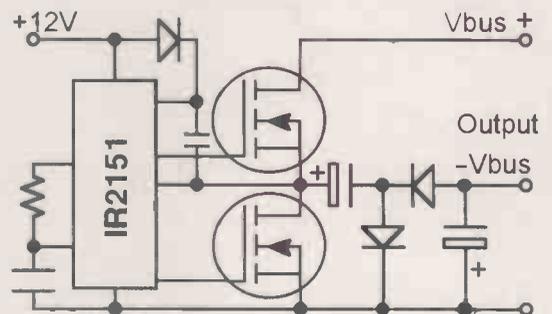
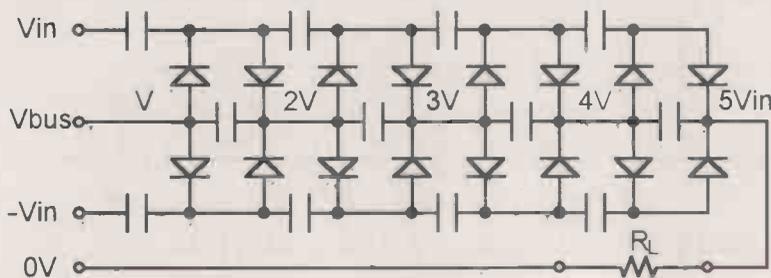


Fig. 2. a) Simple voltage doubler based on a popular mosfet half-bridge driver. Negative rail generator b) is similar to the doubler circuit but it sits on the 0V rail with diodes and capacitors reversed. b) is a negative rail generator

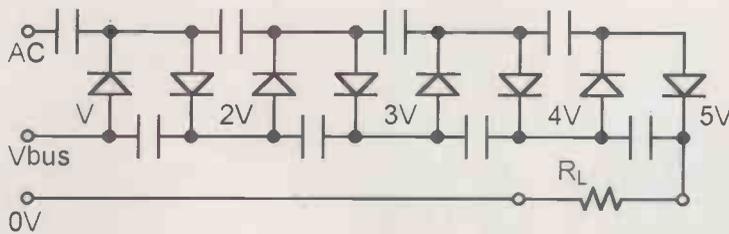


Fig. 3. Higher multiples of the input voltage are obtained by cascading several doubler sections.

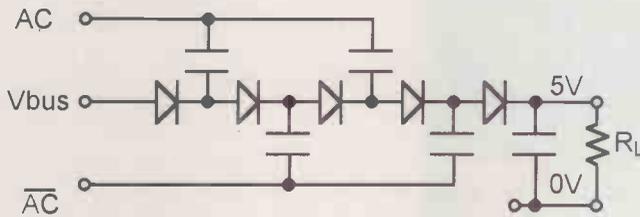


Fig. 4. Improved half-wave pentupler. Compared to Fig. 3, this multiplier needs three fewer diodes and two fewer capacitors.

several doubler sections as shown in Fig. 3. Voltages indicated are those for a multiplier that sits on the dc bus. This enables a dc-to-dc pentupler to be made with only four stages instead of five, increasing efficiency and reducing cost.

Note the difference in output when a multiplier is fed from an ac source such as from a transformer as in Fig. 1, rather than a pulsed dc waveform as in Fig. 2. With an ac source, input capacitor C_1 charges to the peak input voltage on the negative half cycle. When the input reverses, $2V_{pk}$ is presented to C_2 ultimately charging it to $2V_{pk}$. But in Fig. 2b, a pulsed dc waveform is fed to C_1 . When the low-side mosfet Tr_2 conducts the input capacitor C_1 is charged to V_{bus} via D_1 and when the high side mosfet Tr_1 conducts C_2 is charged ultimately to V_{bus} , not $2V_{bus}$ as might be expected from Fig. 1.

This can be explained by looking at the Fourier series for a pulsed dc waveform. A dc component of $0.5V_{bus}$ is present which is blocked by C_1 . The remaining ac component, a square-wave with a peak value of $0.5V_{bus}$, is doubled giving V_{bus} across C_2 and $2V_{bus}$ at the output to 0V.

As a rule, the peak-to-peak input voltage determines the output voltage of each stage and each additional stage adds another component of peak-peak input voltage.

Improved half-wave multiplier

Fig. 4 shows Ian Hickman's improved half-wave multiplier¹. Compared to Fig. 3, only five diodes are needed rather than eight for a pentupler that sits on the dc bus, and only five capacitors are required rather than seven. However, two drivers are required to generate the complementary squarewave drive but this can be done relatively simply these days with ics.

Full-wave multipliers

A full-wave pentupler is shown in Fig. 5. This circuit is effectively two half-wave multipliers in parallel. Hence the output current can be

doubled for the same output ripple and efficiency.

Apart from the complications of the extra diodes, capacitors and a differential drive either from a full-bridge converter or a transformer, these complications are partly offset by the double pulse frequency in the dc capacitors. As in conventional full wave rectifiers, the value of the filter capacitor can be half that of half-wave for a given ripple content. Also, as I discovered, the dc capacitors can be eliminated when the input is fed with a square wave.

Improved full-wave multiplier

When Fig. 5 is fed with a squarewave such as from a full H bridge, the dc capacitors can be removed without upsetting operation since the output duty cycle is close to 100%.

With the capacitors removed there is a current path through the junction of the four diodes in Fig. 6a. These current paths are independent so the junctions can be broken. Since there are now two diodes in series in

Safety hazard

The high voltage multiplier described here is potentially lethal. Do not attempt to build or use it unless you fully understand the dangers of extremely high-voltages and follow the safety warnings given in this text.

each path, the circuit can be simplified to Fig. 6b. Although I have not done an exhaustive literature search, this full-wave circuit appears to be new.

Fewer diodes means lower cost – especially in low voltage converters when using schottky diodes. Reducing diode numbers also improves efficiency; in low voltage converters diode losses tend to predominate. Eliminating the dc capacitors also reduces cost and improves efficiency because there are fewer charge transfers. In Fig. 6 for example, there are four charge transfers. This includes one from the supply reservoir capacitor, compared to eight charge transfers for a conventional full-wave pentupler. Comparing diodes, there are five diode volt drops compared to eight.

In general, there are $2n$ diodes where n is the multiplication factor and where V_{bus} is used to reduce the number of stages by one. Note that there are two diodes more than the number of capacitors; the last two diodes can be seen as termination diodes. Adding an extra two diodes at any point can tap-off different voltage steps if required.

All these improvements are achieved with the same voltage and current ratings of both diodes and capacitors and without compromising output power. Compared to the simpler half-wave multiplier the only extra components, apart from the two extra diodes, is the extra half bridge, which is relatively simple these days.

Capacitor losses

The law of charge conservation can be used to show that capacitor losses are independent of how much or little resistance is in the circuit when two capacitors are connected together. Energy loss when transferring charge from C_1 initially at V_1 to C_2 initially at V_2 is,

$$\Delta E = \frac{1}{2} \left[\frac{C_1 \times C_2}{C_1 + C_2} \right] [V_1 - V_2]^2$$

Even if diode losses could be eliminated, the efficiency of a charge pump multiplier is limited by the sum of the squares of the individual capacitor ripple voltages. Capacitors for power converters are costly so it is important to choose capacitors carefully.

Choosing capacitor values

To minimise the cost of capacitors you need to know how much output ripple is acceptable

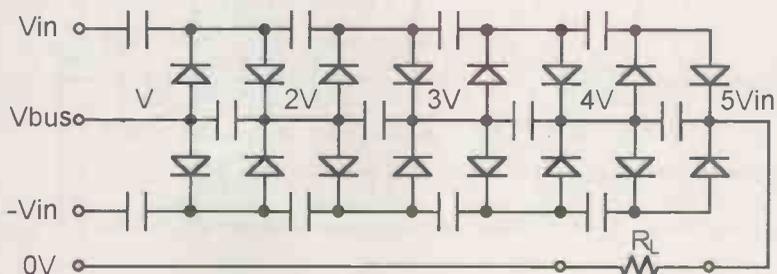


Fig. 5. Conventional full-wave pentupler. This circuit is effectively two half-wave multipliers in parallel.

and the output current. Electrolytic capacitors are useful up to several hundred volts and work best in the 3-30kHz range. Electrolytics are usually chosen for their ripple rating rather than for minimum capacitance because they have high losses. Typical D figures are 0.1 to 0.2 compared to non-electrolytics with 0.001 to 0.01, where D , and $\tan \delta$, is the dissipation factor.

I have used various types of electrolytics in multipliers. Standard electrolytics can be used but they are more bulky and require a lower frequency for minimum impedance and hence maximum efficiency. The XYB series miniature low impedance 105°C electrolytics from Rubycon are used in my recent designs. The RS catalogue provides useful ripple current data.

I have found the continuous ripple current rating of 105°C capacitors can be more than doubled for an ambient temperature not exceeding 50°C. The Philips electrolytic capacitor data book gives useful information on temperature over-rating.

In the absence of suitable data, run a test to measure the temperature rise at maximum current. From this the highest safe ambient temperature can be found. For example, a temperature rise of 45°C means 105°C capacitors can operate up to an ambient temperature of 60°C, so a 50°C ambient temperature will be safe.

Bipolar types that are non-electrolytic are chosen on the basis of output ripple voltage; for 5% peak-peak output ripple the final capacitors reactance should be a hundredth of the load resistance³. Given an operating frequency and reactance, the value of the final capacitor in the multiplier chain can be calculated.

Grading capacitor values in proportion to current helps to minimise charge transfer losses. For Figs 3 and 5, capacitors closer to the input carry more current than the final stages, increasing linearly along the chain starting from the load. For example, if I_L is the average current flowing through the load in Fig. 3 then the input capacitor carries $4I_L$.

12V-to-100V 300W converter

Fig. 7 shows a 13.8V to $\pm 50V$ 300W dc-dc converter. It demonstrates that output power of several hundred watts are relatively easy to

achieve. An efficiency of over 90% can be maintained from a few watts up 300W – even with a multiplication ratio of eight times. If load current must be returned to 0V, this reduces to 150W and ± 4 times. Peak efficiency was 95–96% for loads from 0.2A to 1A.

Comparing this multiplier to that in Fig. 6b, shows that the capacitors are arranged slightly differently; they are common to the input rather than in a string. This improves efficiency of electrolytic based multipliers, where higher voltage electrolytics generally have lower losses (D) per microfarad. Note that the capacitor voltages increase toward the output in this arrangement. Also, capacitor currents are similar so each capacitor needs to be rated for the output current. For the values shown the highest capacitor case temperature rise was 30°C with 2.2A load.

The W/kg power density and W/cm^3 specific power compare favourably to inductor based converters. For example, an *ETD34* ferrite core measures about $50cm^3$ and weighs 50gm. At 200W the power density and specific power are 400W/100gm and 4W/cm³ respectively. For this multiplier (capacitors, diodes and pcb) the values are similar at 300W/100gm and 6W/cm³. If schottky diodes are not used to maximise efficiency, the cost per watt for this converter is better than inductive converters. These comparisons are valid for non-isolated step-up converters with ratios of up to ± 5 or so – ten or so for a floating load.

Although Fig. 7 includes voltage regulation, it is easily removed if not required. By adding C_1 and R_1 , IC_1 can run in self-oscillating mode. If you only require a single output, then simply remove one of the multipliers. Also, given higher voltage mosfets, diodes (not forgetting D_1 and D_2) and capacitors, the bus voltage can be as high as 500V.

With no regulator circuitry, the operating frequency is preset with R_1 for maximum efficiency. This can be found by making R_1 variable. Best efficiency is seen as a peak in the output voltage (or input current) as the frequency is raised and for the values shown it is 12kHz.

There is little change in efficiency until 35kHz, but at 100kHz and full load the output power falls by 15% and efficiency falls from 91% to 88%. The reduction in efficiency and

power can be attributed mainly to the *IR2151*'s 1 μs dead time. Setting the operating frequency too high reduces efficiency at light loads because of the increased gate drive losses. Too low a frequency requires larger and more expensive capacitors.

The unregulated version gives 90% efficiency down to 2W. This is possible because the frequency is only 12kHz, resulting in only 4mA supply current for the ics plus 10mA from the supply bus. The regulated version is less efficient at light loads because it operates up 100kHz when lightly loaded.

This converter was intended to feed a standard 100W amplifier for operation from a nominal 12V supply. For this application it is desirable to keep the frequency above 20kHz to prevent audible interference and preferably above 40kHz to prevent intermodulation products being heard at low audio levels.

To drive a 100W amplifier, the peak current required into 8 Ω is 5A and the minimum voltage to the amplifier should be 45V. The converter in Fig. 7 is rated for 2.5A average and can deliver 5A peak without large reservoir capacitors ($C_{6,7}$).

By delivering the peak current directly rather than from say two 10,000 μF reservoir capacitors, for 30Hz low frequency roll-off, the converter is more compact. If reservoir capacitors are added it is possible to run two 100W amplifiers on music signals, but amplifier clipping needs to be avoided.

The right-hand *IR2151* is slaved from the oscillator of IC_1 via R_1 to the comparators of the 555 type internal oscillator. Propagation delay through the comparators is insignificant compared to the 1 μs dead time delay for the mosfets. Using two *IR2151* drivers was a lower cost option than full H-bridge drivers advertised at the time. This circuit does not require a separate oscillator for the unregulated option. Resistor R_2 is added as a precaution in the event of IC_2 's under-voltage shutdown being enabled before IC_1 .

Regulating the output

It is difficult to regulate the output voltage of a multiplier by the usual means, such as pulse width modulation. Attempting to reduce the frequency to increase capacitive reactance also increases losses in proportion to voltage

continued on page 805...

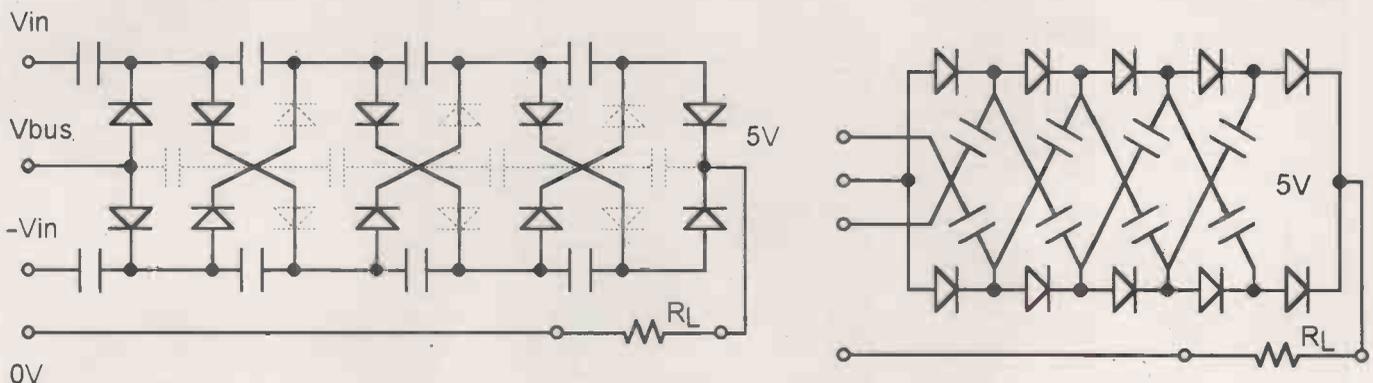


Fig. 6a. Improved full-wave pentupler. Compare with Fig. 5. Dotted components can be removed. b) is the improved pentupler redrawn.

Please quote "Electronics World" when seeking further information

ACTIVE

Arrays

'Fastest' pld. *GAL16LV8D* is the first member of the Lattice Semiconductor UltraMOS VI 3.3V low and high density plds. Its e²cmos process enables a T_{pd} of 3.5ns and typical supply current is 45mA, which provides a power consumption up to 70% lower than 5V 16V8 devices. The pld operates with 200MHz system clocks and interfaces with 100MHz buses where both clock edges are used. Compiler software is the same as that for standard 16V8 devices. Future Electronics Ltd. Tel., 01753 763000; fax, 01753 689100.

Bipolar asics at cmos prices. NEC has introduced the *QB-8* asic technique to provide the power, price and short development time of cmos with the high speed of bipolar devices, using a new architecture named *Puzzle*. A special 622MHz version of *QB-8* is intended for embedding in high-speed telecomms applications. *Puzzle* uses mos input and Bicomos output to provide low input capacitance and drivability. These devices contain up to 223,000 used gates. NEC Electronics (UK) Ltd. Tel., 01908 691133; fax, 01908 670290.

A-to-D and D-to-A converters

14-bit, 100MHz d-to-a. Harris announces the first digital-to-analogue converter to give 14-bit resolution at 100MHz. The *HIS741* simultaneously converts 20 voice channels at a 70dB thd - better than the requirement for single-channel cellular base stations; single-tone spurious-free dynamic range is 86dBc at Nyquist frequency. A significant feature is its capability of handling eight channels in one package, rather than the eight separate signal-processing chains that have until now been needed. Harris Semiconductor UK. Tel., 01276 686886; fax, 01276 682323.

Low-noise a-to-ds. Two new cmos 12-bit converters by Crystal Semiconductor are of the successive-approximation type, offer a 100kHz processing rate, 75mW power dissipation and 73dB s:r ratio. *CS7870* ($\pm 3V$) and *CS7875* (5V) are pin-compatible with existing 12-bit types and give a performance improvement without circuit modification. A self-calibrating

capacitor eliminates time and temperature drifts. Crystal Semiconductor Corporation. Tel., (USA) 001 512 442 7555; fax, 001 512 445 7581.

Multimedia data converter. Said to be meant for use in multimedia and audio, the *AKM AK4510* is a 16-bit stereo a-to-d and d-to-a converter, using fourth-order delta-sigma modulation for accuracy and low cost. The a-to-d section has an on-chip anti-aliasing filter and the d-to-a a post filter to afford tolerance of system clock jitter to 100ns. Switched-capacitor and continuous time filters give out-of-band noise down to -83dB at 44.1kHz sampling. DIP International Ltd. Tel., 01223 462244; fax, 01223 467316.

Linear integrated circuits

General-purpose op-amps. Burr-Brown's *OPA234* series of gp op-amps feature low power and good dc performance and come in single (*234*), dual (*2234*) and quad (*4234*) versions. They work on single or dual supplies; in single-supply working, input common-mode range extends below ground, output swinging to within 50mV of ground. Capacitive loads up to 10,000pF are acceptable in unity gain and the multiple versions are independent for lowest crosstalk. Specifications include a supply range of 2.7 to 36V (± 1.35 to $\pm 18V$), 250 μA /amplifier quiescent current, 25nA input bias and 100 μV input offset. Burr-Brown International. Tel., 01923 233837; fax, 01923 233979.

Microprocessors and controllers

8-pin microcontroller. Microchip has 8-pin, one-time programmable microcontroller, the *PIC12CXXX* family, which uses the risc-based *PIC16/17* architecture in a SOIC package to make, it is claimed, the world's smallest 8-bit controller. It provides maths and Boolean operation which, with its small size, makes it competitive with asics and types with greater pin numbers. Two are available: *PIC12C508* with 512word of program memory and 25byte of user ram; and the *PIC12C509* with 1024word and 41byte. Both have six i/o and an on-chip oscillator, 33 single-word instructions, 1 μs instruction cycle at 4MHz, seven special-function hardware registers and direct led drive. Operating power is 2.5-5.5V at 2mA. Arizona Microchip Technology Ltd. Tel., 01628 851077; fax, 01628 850259.



Dsp, risc microcontroller. Hitachi's *SuperH* family of 32-bit microcontrollers is joined by the *SH-DSP*, which is claimed to be the first single, integrated core to include full dsp and risc functions. It gives 60Dhrystone mips as a controller or 120mops as a dsp, or any point in between. The device is based on the *SH-2* with dsp extension and operates at 60MHz, 3V, accepting SuperH code with no need for modification. There is a good base of software tools available. Hitachi Europe Ltd. Tel., 01628 585163; fax, 01628 585160.

Supervisors. *MAX6301/2/3/4* from Maxim are microprocessor supervisor chips, issuing resets on power-up/down, brownout or failure in software execution, model difference being concerned with the nature of the reset outputs. Two external resistors set trip thresholds, resets being emitted when the supply drops below the threshold and maintained until an adjustable time after it rises again. Resets are guaranteed for supplies down to 1V. There is an internal watchdog timer to issue a reset when the adjustable timeout ends after an absence of transitions. Indicates a software failure. Maxim Integrated Products UK Ltd. Tel., 01734 303388; fax, 01734 305511.

Optical devices

'Smallest' ir transceiver. A new optical transceiver pair by Sharp is compatible with the IrDA 1.0 standard for infrared communication. Normally external components are integrated to reduce the board area needed to about 20% of that required by earlier designs. Wait time is reduced by using the half-duplex mode and the delay between transmit and receive

Power semiconductors

Rf power. New from Motorola, the *MRF927T1* rf power n-p-n silicon transistor for low-voltage, low-current use, particularly in pagers and hand-held telephones. It operates in the 2GHz region and exhibits an 8GHz gain/bandwidth product at 3V, 5mA. Unilateral gain is 15dB and noise figure 1.7dB. The company also offers the *MRF6401* rf power device, specified with a gain of 10dB minimum at 1.66GHz, output power 0.5W. Motorola Semiconductors SA. Tel., 001 33 61 199981; fax, 001 33 61 199565.

modes is down to 30 μs . Since the two devices are separate, the receiver cannot 'see' the light from the transmitter and a sunlight saturation prevention circuit is automatically matched to the receiver. Data transmission rate is in the 2.4 to 115kb/s range. Microelectronics Technology Ltd. Tel., 01844 278781; fax, 01844 278746.

PASSIVE

Passive components

Transformers for valves. Variable Voltage Technology offers the *VTM* range of transformers intended for use with valves. They are designed for valve-age but using modern methods and materials such as annealed copper wire and grain-oriented laminations. All meet emc and low-voltage directives and are CE marked where appropriate. The transformers are either frame or vertically mounted and are for use as mains transformers for ht, with or

Please quote "Electronics World" when seeking further information

without heater windings; as heater transformers; as mains smoothing chokes; or as output transformers for triodes, pentodes or in ultralinear mode using EL34 and EL84. Variable Voltage Technology Ltd. Tel., 01983 280592; fax, 01983 280593.

Thin inductors. TDK's *NLU* series of thin-film, surface-mounted inductors are for 1-3GHz application and are only 0.58mm thick. The copper spiral inductors are available in values from 1.2nH to 100nH and come in the 0805 and 0603 sizes for flow and reflow soldering. Flint Distribution. Tel., 01530 510333; fax, 01530 510275.

Resistor networks. *BCN 16 4A* resistor networks in the 1206 size are eight-terminal units containing four isolated resistors, with either internal or external termination. Resistance range is 10Ω to 1MΩ at a tolerance of ±5%, with ±2% also available. BI Technologies Ltd. Tel., 01384 442393; fax, 01384 440252.

Emc chokes. Wearnes Hollingsworth offers a range of common-mode chokes, which are designed to prevent noise entering or leaving

Audio connectors. Cliff Electronics has a range of audio connectors and terminations, including the *Plastic XLR* range of light, three-pole plugs and sockets for audio connection, in cable, panel and pcb mounting forms. All are mateable with the metal-bodied XLR connectors and all have cable strain-relief and silver-over-nickel-plate brass contacts rated at 16A, 250Vac. There is also the *Cliffcon* series of four-pole locking connectors for use in professional audio systems and instrumentation. In addition, the *Quick Connect* terminals are for loudspeakers, having spring-loaded levers to trap the wire in the terminal. Electrospead. Tel., 01703 644555; fax, 01703 610282.

equipment by way of power or signal lines, all to do with the current preoccupation with electromagnetic compatibility. Both standard and custom-made chokes are available, mainly using toroidal cores of iron powder, ferrite or amorphous alloy, in sizes from 3mm to 30mm diameter. Inductance values are in the 1-100μH range and they operate at frequencies to 30MHz. Wearnes Hollingsworth Ltd. Tel., 01433 621555; fax, 01433 621290.

Vari-C diodes. Variable-capacitance diodes from Zetex in the SOT-23 *ZC930* range give octave tuning from a 1-4V voltage change. At 1V, the seven devices in the range have a minimum capacitance range of 8.7pF to 95pF; as an example, the *ZC932* gives 17pF at 1V and 5.5pF at 4V, with a 'hyperabrupt' C/V characteristic. Stray capacitance is 0.08pF and lead inductance 2.8nH. Zetex plc. Tel., 0161 627 5105; fax, 0161 627 5467.

Small trimmer capacitors. *TZVX2* series capacitors by Murata measure 2.3 by 3.2 by 1.2mm, which makes them, says Murata, the world's smallest trimmers. The capacitance range is 2.5-20pF in five values, with temperature stability 0±300ppm/°C for 2.5-10pF and -750±500ppm/°C for 20pF. Settling drift is said to be extremely low. Murata Electronics (UK) Ltd. Tel., 01252 811666; fax, 01252 811777.

Connectors and cabling

Two-in-one optical fibre connector. Molex *SC* optical-fibre connectors use two NTT-SC standard connectors in one housing. Insertion loss is typically under 0.15dB for single-mode and below 0.34dB for multi-mode. The connectors are available in flange or snap-mounting versions. Molex Electronics Ltd. Tel., 01420 477070; fax, 01420 478185.

Solderless coax. connectors.

Transradio offers the *Coaxipress* range of coaxial connectors fitted with solderless, press-fit terminations, for use in existing plated-through holes in diameters from 0.94mm to 1.09mm on 1.6-7mm board material. Designs are available for MCX, SMB and DIN series of miniature connectors with right angles or straight receptacles. Detailed procedures for insertion and removal, and information on tooling are available. Transradio Ltd. Tel., 0181-997 8880; fax, 0181-997 0116.

Displays

Better tft lcds. Major features of Sharp's *Super-V* lcd 13.8in XGA module are a 140° horizontal viewing angle, 250cd/m² brightness, 300:1 contrast and 10W power consumption. The module is only a quarter the weight, a third the thickness and uses a fifth the power of a crt of the same size. Sharp Electronics (Europe) GmbH. Tel., 0049 040 2376 2215; fax, 0049 040 2376 2991.

Test and measurement

Dso with 'analogue' display. Aside from its other claims to fame, Gould's *Classic 6000* 4-channel, 200MHz digital storage oscilloscope has TruTrace, which is a technique to make the dso traces look like those on an analogue instrument, with variable intensity. This allows fine details, normally invisible on the usual dso display, to be seen; particularly useful for complicated signals in noise. The instrument has a range of options, from a low-end monochrome model up to a colour type with mass storage, auto sequencing and maths functions. Up to eight traces can be viewed simultaneously, to allow live traces on four channels to be compared with four reference traces or zoomed versions. Sampling rate is 100Msamples/s and basic, segmentable memory 10k/channel with options of 50k or 200k. Gould Instrument Systems Ltd. Tel., 0181 500 1000; fax, 0181 501 0116.

Line-impedance stabiliser. Thurlby Thandar offers the *LISN1600*, a line-impedance stabilisation network, to measure the level of conducted emissions at the supply of electrical equipment operating from a single-phase ac supply. It works with a spectrum analyser or measuring receiver to allow these measurements to be done without the need for test-house facilities. Its current rating is 16A continuous and various output connectors are available. The instrument meets CISPR16 for Band A measurement of 10-150kHz and Band B in the range 150kHz-30MHz. A switchable 150kHz filter limits lf signals in Band B to reduce the dynamic range requirements.

Connection is to either supply line, or the unit can be disconnected to check noise floor. Thurlby Thandar Instruments Ltd. Tel., 01480 412451; fax, 01480 450409.

Differential oscilloscopes. *OX802* and *OX8022* differential oscilloscopes by Metrix are believed to be the only differential types available. Both are 20MHz instruments; *OX802* is an analogue model, while the *8022* will also work in digital mode at a 40Msamples/s rate. Both operate in normal or differential mode, the diff. inputs giving true floating measurement and channel-to-channel isolation. A maximum input voltage of 500Vrms and the diff. inputs enable direct examination of single and three-phase mains voltage. Conversely, a sensitivity of 10mV/div is available for small signal work. The *8022*'s digital facilities include roll, refresh and single shot, a pre-trigger in steps of 1Kword from 0 to 4Kword, a 2 by 4Kword memory and an RS232 port. Metrix Electronics plc. Tel., 01384 402731; fax, 01384 402732.

20MHz and 50MHz rsos. Two low-cost real-time and storage oscilloscopes from Hitachi Denshi, the *VC-6523* and *VC-6524* have hard copy by way of a plotter interface and waveform transfer via an RS232 interface. Bandwidths are 10MHz (6523) and 50MHz with sampling rates of 20Msamples/s and 2kword/channel memory. Two waveforms may be captured and saved for 72 hours or longer if mains power has been used. Both offer roll mode, averaging, smoothing, interpolation and pre-trigger. Hitachi Denshi (UK) Ltd. Tel., 0181 202 4311; fax, 0181 202 2451.

Paperless chart recorder.

Yokogawa's *VR100* chart recorder is a paperless type using 3.5in floppy disks and samples at 125ms with 14-bit resolution. Display is a 320-by-240 pixel, 5.5in colour tft lcd, showing the data in a variety of forms with split-screen, magnification and reduction. Data is saved continuously in the built-in memory and is saved to disk at any time, each disk holding up to a month's recording of four channels with samples at 60s intervals. Software enables interaction with Windows and Lotus 1-2-3, Excel or Ascii files are supported. Martron Instruments Ltd. Tel., 01494 459200; fax, 01494 535002.

Low-cost, 20MHz oscilloscope.

Leader offers the *LS1020* 20MHz, dual-trace oscilloscope, which has a maximum Y sensitivity of 0.5mV/div and sweeps at 50ns/div. Trigger modes include alt. trigger, which allows a stable display of non-synchronous signals on both channels at the same time; hold-off time is variable from the start to the end of a



Please quote "Electronics World" when seeking further information

sweep. One channel can be used as an amplifier to provide 50mV/div output and the two channels can be used to give an XY display. Thurlby Thandar Instruments Ltd. Tel., 01480 412451; fax, 01480 450409.

Emc tester. Newly announced by Schaffner is *BEST 96*, which is a complete electromagnetic compatibility test set in one box, providing all the functions needed to for full EU compliance of electronic products; CE mark pre-compliance and compliance testing can be carried out in-house. The set comprises a generator to give burst, electrostatic discharge, surge and power quality pulses for single-phase powerline and dataline compliance test to EN-50082-1, plus ground plane, cables, ground strap and resistor and coupling clamp for dataline test. All functions are controllable from the front panel or remotely using Windows software. Schaffner EMC Ltd. Tel., 0118 9770070; fax, 0118 9792969

Literature

Suppression filters. Murata's 108-page catalogue on suppression filters and ferrites has much data on other emi products, including applications a list of emi kits and a guide to noise suppression. Murata Electronics (UK) Ltd. Tel., 01252 811666; fax, 01252 811777.

Emc filters. Arcotronics, specialising in emc filters, has a new catalogue, which contains an Informative Introduction to the filters and their characteristics and complete electrical and mechanical data on the range on offer. The catalogue is available free. Arcotronics Ltd. Tel., 01327 351515; fax, 01327 353761.

Relays, switches, etc. A new edition of the Hhv short catalogue of thermal overload and circuit protection devices is available. New this time are extensions to the thermal circuit breaker range and new ranges of power relays and rocker switches. One of the relays is the miniature (1in cube) normally open type 691, which switches 30A at 240V, equivalent to a 2hp motor. Hhv Components Ltd. Tel., 01543 416667; fax, 01543 416140.

Fpga data book. Actel offers, free, the *FPGA Data Book and Design Guide* for anyone considering using Actel programmable logic arrays. Apart from technical details of fpgas and development tools, there is information on the Designer Series development system, which allows the specification of delay through logic blocks. Application notes on design and software tools are also included. It can be obtained

through the company's web site on <http://www.actel.com>. Actel Europe Ltd. Tel., 01256 29209; fax, 01256 55420.

Production equipment

Soldering system. From Production Equipment Sales, the *AS 2000* industrial five-axis automated soldering system for post-process work. It is an in-line conveyorised station, using a high-speed positioning system and multi-tasking computer control to cope with all automated soldering applications including thermally sensitive components, flexible circuitry, connectors and others that cannot be mass reflowed or wave soldered. Temperature control is $\pm 3^{\circ}\text{C}$ with a programmable dwell time in milliseconds. An RS232 port allows communication to a computer, soldering routines being taught or derived from cad data. Production Equipment Sales Ltd. Tel., 01825 766644; fax, 01825 766464


Power supplies

Switching regulators. Semtech's *LM2575/2576* 1A and 3A miniconverter switchers are pin-compatible with National's devices. They are buck or buck/boost converters needing only four external components to provide fixed or adjustable outputs in the 3.3-35V range. Input is 40V and efficiency 82% at 5V. Semtech Ltd. Tel., 01592 773520; fax, 01592 774781.

Wide-range dc converters. The *Mascot* dc-to-dc converter range accepts all common input voltages from 6V up to 140V. Sixteen models, both linear and switched-mode types, provide all the usual voltage outputs, some being adjustable, at powers from 27W to 158W. For demanding application, there are four models with inputs and outputs isolated from each other and ground. Inputs and outputs are all fully protected against acts of God and absentmindedness. Relec Electronics Ltd. Tel., 01962 863141; fax, 01962 855987.

Low-noise dc converters. Interpoint claims that its *MHV* series of single and dual output dc-to-dc converters have the lowest output noise in the military/aerospace industry, at 10mV. Input range is 16-50V and the choice of outputs is 3.3, 5, 12, 15, ± 5 , ± 12 and $\pm 15\text{V}$ and the units will cope with transients of up to 80V for 120ms. Interpoint UK Ltd. Tel., 01252 815511; fax, 01252 815577.

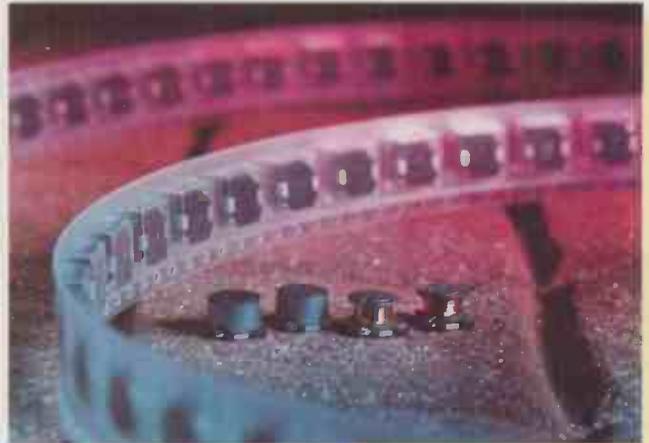Cv/ci battery charger. The Linear Technology *LT1511* current-mode pwm battery charger ic will charge a battery pack while the equipment it is powering continues to work, a control loop in the charger regulating current drawn to allow rapid charging without overwhelming to power-management



chip. The ic is 90% efficient and gives 3A out for all popular battery types, operating from an input of 8-28Vdc. Micro Call Ltd. Tel., 01844 261939; fax, 01844 261678.

Temperature-stable zener regulator. Zetex has augmented its wide range of adjustable shunt regulators with an extended temperature version of the *ZR431*, claiming the widest temperature range available for this type of device. The *ZHT431* copes with temperatures from -55°C to 125°C , a 44% increase on the typical range. It is temp. compensated over its whole working range and has a temperature coefficient of 50ppm/ $^{\circ}\text{C}$. Tolerance is 1% or 2% and quiescent current 35 μA . The device is simply programmed between 2.5V and 20V by two resistors. Package is the ultra small SOT23, but the SOT223 and SO8 surface mounts are also available. There is also a through-hole TO92 type. Zetex plc. Tel., 0161-627 5105; fax, 0161-627 5467.

Radio communications

Synthesised video Tx/Rx. Mainly for use in security applications, Wood & Douglas's *VFMT-2/VFMR-2* uhf transmitter and receiver modules offer comparable performance to that found in crystal-controlled equipment, with the advantage that frequencies are programmable. The units are in separate aluminium cases and provide a mid-range video link over a line-of-sight 20km range. Working in the 280-500MHz band, the units provide two sound channels for line or microphone level; frequencies, which are stored in eeprom for front-panel programming, are selected by internal switches, up to four video channels being available over a 50MHz operating range. Two versions of the transmitter have rf output of 2.5W or 8W. Wood and Douglas Ltd. Tel., 01734 811444; fax, 01734 811567.

Protection devices

SCSI circuit breaker. Designed particularly for 5V SCSI application or

Surface-mounted inductors.

Toko's new *D10F* range of s-m inductors is now obtainable from Cirkit. The inductors measure 9.7mm in diameter and 5mm in height and come in values from 10 μH to 1.5mH in current ratings of 0.25-2.6A. A magnetically shielded version is also available. Mounting pads are separate from the coil terminations to eliminate strain on the windings. Cirkit Distribution Ltd. Tel., 01992 444111; fax, 01992 464457.

any system needing 1.5A hot plug protection, Unitrode's *UCC3916* fixed trip-current circuit breaker provide unidirectional current flow, to emulate a series diode, and limiting in an 8-pin SOIC package. It replaces fuse/diode protection, providing a more accurate threshold and more rapid response. Trip current is 1.65A and has a programmed maximum current of 2.1A. Unitrode (UK) Ltd. Tel., 0181 318 1431; fax, 0181 318 2549.

Switches and relays

10mm reed switch. *Mini-DYAD* reed switches by C P Clare resist damage when leads are formed for mounting and exhibit a switching speed of 0.5ms. They carry 2A and switch 0.5A at 200V. C P Clare International NV. Tel., 0032 12/39 04 00; fax, 0032 12/23 57 54.

Transducers and sensors

Inclinometer. *Model 1D* is a £74 digital tilt sensor by Control Transducers, used to show the angle of an object with respect to gravity. Output is til in two or three channels, suited to equipment designed to ensure, for example, the machinery is level or that off-road vehicles or cranes are not going to topple over. An optical encoder disc, resolving to 0.25°, 0.1° or 0.05° is supported by two micro ball bearings, a

Please quote "Electronics World" when seeking further information

weight on the disc causing it to take up a constant position with respect to gravity. Internal magnetic damping provides fast response and minimises oscillations of the disc after a disturbance. Power needed is 5Vdc at 40mA maximum. Control Transducers. Tel., 01234 217704; fax, 01234 217083.

Crash accelerometer. The 7264B-2000 piezoresistive accelerometer from Endevco weighs 1gram and has integral mechanical stops to enable the unit to survive 10,000g shocks in all axes. It is designed for rough road testing, flight tests and tests where a perfectly good vehicle is driven full tilt into a concrete wall, in which the small size of the accelerometer allows it to be put into a dummy person without altering its mass too much. The unit is undamped and produces minimum phase shift over its useful frequency range of 0-5kHz. Endevco UK Ltd. Tel., 01763 261311; fax, 01763 261120.

S-m pressure sensors. MPXS4100A is the first in a new family of surface-mounted pressure sensors from Motorola, this one handling 20-105kPa absolute (manifold or barometric) pressure and incorporating bipolar amplifier circuitry and thin-film resistor networks for high output and temperature compensation. Motorola

Position sensor. Monitran's sensing probes in the MTN/EP range measure distances up to 8.5mm without contact with the moving target. An eddy current technique is used in which hf is radiated into the target and currents set. After signal conditioning, the gap is represented as a dc level, or an ac signal if the gap varies, as in a gear wheel. All models have stainless steel threaded bodies with securing nuts and armoured cable and the range covers gap measurement from 0-2mm to 0-8.5mm. Monitran also offers an eddy current driver. Monitran Ltd. Tel., 01494 816569; fax, 01494 812256.



Semiconductors. Tel., 01355 565000; fax, 01355 234582.


Hall-effect latch. Allegro has the A3197LU, a protected open-collector Hall-effect latch ic for operation in the temperature range -40°C to 150°C. It senses magnetic fields in applications such as vehicle transmission speed sensing and wheel bearing speed sensors, the latching assisting in pulse counting when used with a multi-pole ring magnet. Position and speed information are provided by a digital output when the field exceeds predefined switch points, which are stable against temperature and voltage variation. The transducer is followed by a temperature-compensated comparator, a regulator and 35mA output buffer. Allegro MicroSystems Inc. Tel., 01932 253355; fax, 01932 246622.

COMPUTER

Computer board-level products

486 cpu card. By IMS, the PCA-6144V is a full-function, half-sized 486DX/DX2/DX4 cpu card with VGA display and other enhanced i/o interfaces. There is a local-bus VGA controller with Windows accelerator and 1Mbyte of display memory and the card takes up to 64Mbyte of on-board dram and a secondary-level cache of 128Kbyte. Other interfaces are an enhanced IDE hd controller, floppy controller, PC/104 interface bus connector for expansion, RS232 and RS232C/485 ports, a parallel port and a PS/2 mouse connector. This is an industrial grade card. Integrated Measurement Systems Ltd. Tel., 01703 771143; fax, 01703 704301.

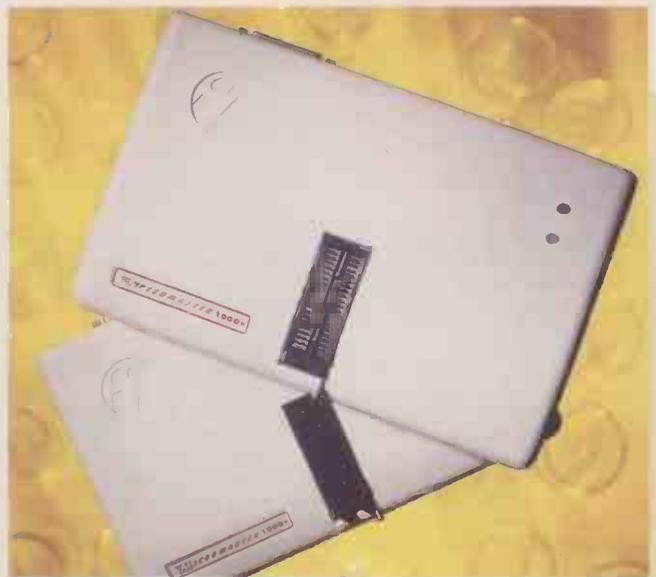Computer Industrial workstation. Fairchild's AWS-822 is a fully specified, rack-mounted pc for use on the factory floor, fully sealed against dust and water, shock mounted and pretty well



human-proof. There is a 14in monitor and a membrane keypad on the front panel containing 37 keys, which may be combined with a conventional AT-type keyboard plugged into the panel. Fairchild Ltd. Tel., 01703 211789; fax, 01703 211678.

Software Autorouter for EASY-PC. Designed for use with Number One Systems' EASY-PC Professional XM, MultiRouter offers a number of features that make it, in spite of its £295 price, equivalent to much more expensive packages. For example, it is not based on a grid, but on shapes, so that components whose pins do not lie on a grid can still be used. Tracks can be pushed aside to let more through, providing this can be physically done. Routing is usually 100%, and if not, further passes are very rapid. Track widths and corners are made suitable for production and vias and track lengths are minimised, vias being eliminated for one-off boards, if required. Number One Systems Ltd. Tel., 01480 461778; fax, 01480 494042.

Bootstrap for C16x microcontrollers. Hitex offers this utility to allow embedded communication, test and programming of a microcontroller with a pc via its serial port and is meant for the Siemens C16x Flash devices. It runs with Windows and uses the pc link to communicate with the device and allows reading of registers to confirm selected bus modes; reads and writes to external memory to test address and data bits; programs the application into the Flash; and programs external Flash. Extensive testing can then be carried out. Hitex (UK) Ltd. Tel., 01203 692066; fax, 01203 692131.

MicroSim Schematics v. 6.3. Enhancements in this new version of MicroSim's Windows-based analogue and mixed-signal design and development software include a graphical parts browser, error traceback and 'wizards' to make symbols and goal functions, expanded libraries and improved

Programming hardware

Low-cost programmers. Two new programmers from ICE, the Speedmaster 1000+, which handles eproms and pals, and the Micromaster 1000+, taking eproms, pals, plds and micros, sell at £395 and £525 respectively, both being easily upgraded to cope with more devices and to support LV devices with a voltage down to 1.8V. No adaptors are needed for diil devices with up to 40 pins and adaptors are available for other packages. All are compatible with the company's built-in rom/ram emulator upgrade and also include chip test for ttl, cmos, dram and sram. Ice's home page is on <http://www.icetech.com>. ICE Technology Ltd. Tel., 01226 767404; fax, 01226 370434.

Windows 95 and NT network licensing. The browser has a 40,000-part symbol library, accessible by name, number or description in seconds with a window to show its graphic before it is selected. Error traceback features a pop-up window to give warning of errors during netlisting, packaging, etc.; double-clicking on the message moves the cursor to the problem on the circuit diagram. If the penny has still not dropped, a more detailed message will appear. MicroSim Corporation. Tel., 001 714 770-3022; fax, 001 714 455-0554.

DASYLab v.3. DASYLab, the Windows-based data-acquisition package, is now in version 3, with many improvements. There are better trigger functions, to ease the definition of pre-trigger and post-trigger data to specify the area of interest; VITool allows a test rig or process to be visualised and documented, with icons combined with bitmap images, control buttons, switches and text to mimic the process; global strings allow sample or product batch data to be entered directly or via dde and stored in a single file with raw data and derived values. The package is in two versions: a basic edition and the extended form with VITool. Adept Scientific Micro Systems Ltd. Tel., 01462 480055; fax, 01462 480213. ■

8 CAVANS WAY,
BINLEY INDUSTRIAL ESTATE,
COVENTRY CV3 2SF
Tel: 01203 650722
Fax: 01203 650773
Mobile: 0860 400683

TELNET

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

MISCELLANEOUS	
Anritsu ME462B - DS-3 transmission analyser	£3000
Anritsu MG642A - Pulse pattern generator	£1500
Barr & Stroud - EFS variable filter (0.1Hz-100kHz)	£150
Datatab DL 1080 - Programmable Transient Recorder	£360
Deixon 1081 - Intekplace tape peel tester, immac. cond.	£1950
Dynapert TP20 - Precision multimeter	£2500
E.I.P. 331 - 18GHz frequency counter	£850
E.I.P. 548A - frequency counter (26.5GHz)	£2750
Farnell SSE520 - Signal generator (10-520MHz)	£400
Farnell TSV70 Midl - Power Supply (70V-5A or 35V-10A)	£225
Fluke 5100A - Calibrator	£3500
Fluke 5100B - Calibrator	£4500
Fluke 5101B - Calibrator	£3000
Fluke 5200A - A.C. calibrator	£2500
Fluke 5205A - Precision power amplifier	£P.O.A.
Fluke 7105A - Calibration system (As new)	£P.O.A.
Heiden 1107 - 30v-10A Programmable power supply (IEEE)	£850
Hewlett Packard 339A - distortion measuring set	£1500
Hewlett Packard 432A - Power Meter (with 478A Sensor)	£275
Hewlett Packard 435A or B - Power Meter (with 8481A/8484A)	from £750
Hewlett Packard 3328A - 100MHz universal frequency counter	£250
Hewlett Packard 3325A - 21MHz synthesiser/function gen.	£1500
Hewlett Packard 3437A - Signal voltmeter	£350
Hewlett Packard 3438A - Digital multimeter	£200
Hewlett Packard 3455A - 6 1/2 digit multimeter (autoscal)	£750
Hewlett Packard 3456A - Digital voltmeter	£750
Hewlett Packard 3488A - HP-IB switch/control unit (various plug-ins available)	£850
Hewlett Packard 3711A/3712A/3719B/3730B - Microwave link analyser	£2995
Hewlett Packard 3778A - PCM Terminal test set	£P.O.A.
Hewlett Packard 3779 A/C - Primary Mux analyser	£800/£1500
Hewlett Packard 4271B - LCR meter (digital)	£900
Hewlett Packard 4275A - Multi-frequency LCR meter	£4250
Hewlett Packard 4342A - Q meter	£995
Hewlett Packard 4948A - transmission impairment measuring set	£2000
Hewlett Packard 4953A - Protocol analyser	£2500
Hewlett Packard 4964A - Protocol analyser	£2750
Hewlett Packard 5314A - (new) 100MHz universal counter	£250
Hewlett Packard 5342A - Microwave freq. counter (18GHz)	£1500
Hewlett Packard 5359A - Time synthesiser	£P.O.A.
Hewlett Packard 5385A - Frequency counter 1GHz (HP/IB) with Opts 001/003/004/005	£995
Hewlett Packard 6022A - autoringing 50V-10A PSU	£850
Hewlett Packard 6034A - System P.S.U. 0-60W-10a	£1500
Hewlett Packard 6181C - D.C. current source	£150
Hewlett Packard 6261B - Power supply 20V-50A	£450
DISCOUNT FOR QUANTITIES	
Hewlett Packard 6652A - System Power Supply 20V-20A	£1950
Hewlett Packard 8005B - Pulse generator	£250
Hewlett Packard 8011A - Pulse gen. 0.1Hz-20MHz	£500
Hewlett Packard 8152A - Optical average power meter	£1250

Hewlett Packard 8158B - Optical attenuator with opt's 002 + 001	£1100
Hewlett Packard 8165A - 50MHz programmable signal source	£1650
Hewlett Packard 8349B - Microwave broadband Amp (as new)	
2-20MHz	£4250
Hewlett Packard 8403A - modulator	£500
Hewlett Packard 8403A - modulator (plug-ins avail)	£500
Hewlett Packard 8420C - Sweep oscillator mainframe	£400
Hewlett Packard 8660D - Synthesised signal gen. 10kHz-2.6GHz	£4500
Hewlett Packard 8683A - Microwave signal gen. (2.3-6.5GHz)	£2500
Hewlett Packard 8684A - 5.4GHz to 12.5GHz Sig Gen	£2500
Hewlett Packard 8750A - Storage normaliser	£375
Hewlett Packard 8901A - Modulation Analyser	£3400
Hewlett Packard 8903A - Audio analyser (20Hz-100kHz)	£1995
Hewlett Packard 8958A - Cellular radio interface	£4000
Hewlett Packard 11729B - Carrier noise test set	£2000
Marconi 893B - A/F power meter	£295
Marconi 2019A - 80kHz-1040MHz synthesised sig. gen.	£1950
Marconi 2871 - data communications analyser	£2000
Marconi 6500 - automatic amplitude analyser	£1750
Marconi 6960 - Microwave power meter (+ sensor)	£P.O.A.
Philips PM 5167 - 10MHz function gen.	£400
Philips PM 5190 - LF synthesiser with GPIB	£300
Philips 5518-Tx - TV pattern generator	£1500
Racal Dana 1992 - 1300MHz frequency counter opts 4B + 55	£900
Racal Dana 3100 40-130MHz synthesiser	£750
Racal Dana 9084 Synth. sig. gen. 104MHz	£450
Racal 9301A True RMS R/V millivoltmeter	£300
Racal Dana 9303 True RMS/RV level meter	£850
Racal Dana 9921 3GHz frequency counter	£450
Schaffner NSG 200E - Mainframe for NSG plug-ins	£1250
Schaffner NSG 203A - Line voltage variation simulator	£1250
Schaffner NSG 222A - Interference simulator	£850
Schaffner NSG 223 - Interference generator	£850
Schlumberger 2720 - 1250MHz Freq. Counter	£600
Schlumberger 4031 - Radio Comms Test Set	£6995
Schlumberger SI 4040 - Statlock, high accuracy 1GHz radio test set	£4995
Schlumberger 4923 - Radio Code Test Set	£1000
Syntro Donner 1980B - Microwave Sweeper (12-18GHz)	£1250
Tektronix 577 - Curve Tracer	£1150
Tektronix - Plug-ins - Many available such as PG508, FG504, SC504, SW503, SG 502 etc.	
Tektronix TM5003 + AFG5101 - Arbitrary Function Gen	£1750
Tektronix 1240 - Logic Analyser	£750
Tektronix AM503 + TM501 + P6302 - current probe amplifier	£995
Tektronix AJ5001+TM5006 - Mainframe programmable distortion analyser	£2500
Tektronix PG506 + TG501 + SG503 + TM503 - Oscilloscope calibrator	£1995
Tektronix CG5001 - Programmable oscilloscope cal generator	£4995
Time 9811 Programmable resistance	£600
Time 9814 Voltage calibrator	£750
Wavetek 172B - Programmable sig. source (0.0001Hz-13MHz)	£P.O.A.
Wayne Kerr B905 - Precision LCR meter	£850
Wiltron 560 - Scalar Network analyser	£900
Wiltron 6520S - Programmable sweep gen. (3.6-6.5GHz)	£650

OSCILLOSCOPES

Cossor 3102 - 60MHz dual channel	£250
Gould OS255 - 15 MHz dual channel	£150
Gould OS3000 - 40MHz dual channel	£150
Gould OS3351 - 40MHz dual channel	£225
Gould OS4000 - 10MHz Digital storage	£200
Gould 5110 - 100MHz intelligent oscilloscope	£750
Hewlett Packard 1800 - 100MHz 4 channel	£300
Hewlett Packard 182C - 100MHz 4 channel	£350

Hewlett Packard 1740A, 1741A, 1744A, - 100MHz dual ch	from £350
Hewlett Packard 54100D - 1GHz digitizing	£3995
Hewlett Packard 54200A - 50MHz 2 channel digitizing	£1000
Hewlett Packard 54201A - 300MHz digitizing	£1750
Hewlett Packard 54501A - 100MHz Digitising - 4 channel	£1950
Hitachi V212 - 20MHz dual channel	£180
Hitachi V222 - 20MHz dual channel	£200
Hitachi V650F - 60MHz dual channel	£350
Kikusui DSS 6522 - 20MHz digital storage	£475
Kikusui COS 6100 - 100MHz 5 channel 12 trace	£475
Kikusui COS 5100 - 100MHz dual channel	£425
Nicolet 3091 - Low freq D.S.O.	£1100
Phillips 3217 - 50MHz dual channel	£350
Phillips 3219 - 50MHz with analogue storage, Dual CH	£400
Phillips 3263 - 100MHz dual channel with microprocessor cont. timing	£400
Phillips 3540 - logic scope (25MHz dual ch. + logic an.)	£350
Phillips 3295 - 350MHz dual ch.	£1500
Phillips 3315 - 60MHz D.S.O.	£750
Phillips PM3295A - 400MHz dual channel	£1750
Tektronix 2445 - 150MHz - 4 channel	£1250
Tektronix 2445A - 150MHz - 4 channel	£1600
Tektronix 455 - 50MHz dual channel	£350
Tektronix 2221 - 60MHz digital storage	£1500
Tektronix 785A - 400MHz Waveform processing oscilloscope	£1500
Tektronix 464/466 - 100MHz storage	from £350
Tektronix 465/465B - 130MHz dual ch.	from £350
Tektronix 468 - 100MHz D.S.O.	£750
Tektronix 475/475A - 200/250 MHz dual channel	from £475
Tektronix 434 - 25MHz 2 channel + analogue storage	£250
Tektronix 454 - 150MHz 2 channel	£400
Tektronix 2213 - 60MHz dual ch.	£425
Tektronix 2215 - 60MHz dual ch.	£450
Tektronix 2225 - 50MHz dual trace	£450
Tektronix 2236 - 100MHz Dual Trace with Counter/Timer/Dmm	£395
Tektronix 2335 - 100MHz dual ch. (portable)	£750
Tektronix 7313, 7603, 7613, 7623, 7633, - 100MHz 4 ch.	from £300
Tektronix 7704 - 250MHz 4 ch.	from £650
Tektronix 7904 - 500MHz	from £850
Tektronix 7934 - 500MHz with storage	from £1000
Tequipment D83 - 50MHz dual channel	£200
Tequipment DM65 - 20MHz 4 channel	£150
Watsu SSS121 - 100MHz dual channel	£425
Watsu SSS702 - 20MHz dual channel	£175
Watsu SSS710 - 60MHz dual channel	£375

SPECTRUM ANALYSERS

Advantest 4133A - 10kHz-20GHz	£6995
Altech 757 - 10kHz-22GHz	£2750
Hewlett Packard 141T + 8552B + 8555A (10MHz-18GHz)	£1600
Hewlett Packard 182T with 8559A (10MHz-21GHz)	£3750
Hewlett Packard 853A with 8559A (0.01-21GHz)	£4250
Hewlett Packard 3582A - dynamic signal analyser, dual channel	£7500
Hewlett Packard 3580A - 5Hz-50kHz	£995
Hewlett Packard 3582A - 25kHz analyser, dual channel	£2500
Hewlett Packard 3709B - Constellation Analyser with 15709A High Impedance Interface (as new)	£6750
Hewlett Packard 8505A - Network analyser (500kHz-1.3GHz)	£4000


Other scopes available too

MANY MORE ITEMS AVAILABLE - SEND LARGE S.A.E. FOR LIST OF EQUIPMENT ALL EQUIPMENT IS USED - WITH 30 DAYS GUARANTEE. PLEASE CHECK FOR AVAILABILITY BEFORE ORDERING - CARRIAGE & VAT TO BE ADDED TO ALL GOODS

CIRCLE NO. 136 ON REPLY CARD

EASY-PC Professional XM Schematic and PCB CAD

From Super Schematics

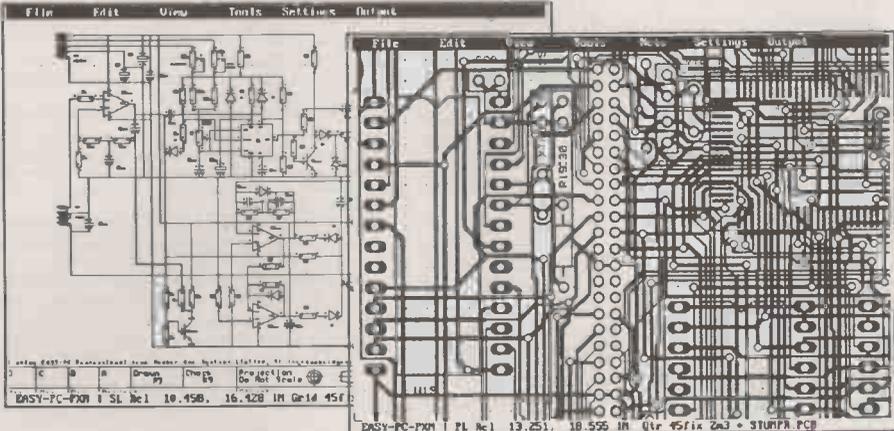

To Perfect PCB's

- Runs on:- PC/ 386/ 486 with VGA display
- Links to PULSAR (logic), ANALYSER III (analogue) & LAYAN (electromagnetic) simulators.
- Design:- Single sided, Double sided and Multi-layer boards.
- Provides full Surface Mount support.
- Standard output includes Dot Matrix / Laser / Ink-jet Printer, Pen Plotter, Photoplotter and N.C. Drill.
- Optional, powerful, 32 bit, Multi-pass, Shape based, Shove Aside, Rip-up and Re-try Autorouter.

Number One Systems

UK/EEC: Ref: WW, Harding Way, St.Ives, Cambridgeshire, ENGLAND, PE17 4WR. Email: sales@numberone.com
Telephone UK: 01480 461778 (7 lines) Fax: 01480 494042 International +44 1480 461778
USA: Ref: WW, 126 Smith Creek Drive, Los Gatos, CA 95030
Telephone/Fax: (408) 395-0249



CIRCLE NO. 137 ON REPLY CARD

MOONSHINE BIBLE 270 page book covering the production of alcohol from potatoes, rice, grains etc. Drawings of simple home made stills right through to commercial systems. £15 ref MS1

NEW HIGH POWER MINI BUG With a range of 800 metres or more and up to 100 hours use from a PP3 this will be popular! Bug measures less than 1" square £28 Ref LOT102.

SINCLAIR C6 MOTORS We have a new ones available without gearboxes at £50 ref LOT25

BUILD YOUR OWN WINDFARM FROM SCRAP New publication gives step by step guide to building wind generators. Armed with this publication and a good local scrap yard could make you self sufficient in electricity! £12 ref LOT81

PC KEYBOARDS PS2 connector, top quality suitable for all 286/386/486 etc £10 ref PCKB. 10 for £65.

TRACKING TRANSMITTER range 1.5-5 miles, 5,000 hours on AA batteries, also transmits info on car direction and motion/Works with any FM radio. 1.5" square. £65 ref LOT101

ELECTRIC DOOR LOCKS Complete lock with both Yale lock and 12v operated deadlock (keys included) £10 ref LOT99

GALLIUM ARSENIDE FISHEYE PHOTO DIODES Complete with suggested circuits for long range communications/switching £12 complete.

SURVEILLANCE TELESCOPE Superb Russian zoom telescope adjustable from 15x to 60x complete with metal tripod (impossible to use without this on the higher settings) 66mm lens, leather carrying case £149 ref BAR69

WIRELESS VIDEO BUG KIT Transmits video and audio signals from a miniature CCTV camera (included) to any standard television! All the components including a PP3 battery will fit into a cigarette packet with the lens requiring a hole about 3mm diameter. Supplied with telescopic aerial but a piece of wire about 4' long will still give a range of up to 100 metres. A single PP3 will probably give less than 1 hours use. £99 REF EP79. (probably not licensable!)

CCTV CAMERA MODULES 46X70X29mm, 30 grams, 12v 100mA, auto electronic shutter, 3.6mm F2 lens, CCIR, 512x492 pixels, video outputs 1v p-p (75 ohm). Works directly into a scart or video input on a tv or video. IR sensitive. £79.95 ref EF137.

IR LAMP KIT Suitable for the above camera enables the camera to be used in total darkness! £5.99 ref EF138.

REMOTE CONTROL TANDATA TD1400 MODEM/VIEWDATA Complete system comprising 1200/75 modem, auto dialler, infra red remote keyboard, (could be adapted for PC use?) psu, UHF and RGB output, phone lead, RS232 output, composite output. Absolute bargain for parts alone! £9.95 ref BAR33.

9 WATT CHEFTAN TANK LASERS

Double beam units designed to fit in the gun barrel of a tank, each unit has two semi conductor lasers and motor drive units for alignment. 7 mile range, full circuit diagrams, new price £50,000? us? £349. Each unit has two gallium Arsenide injection lasers, 1 x 9 watt, 1 x 3 watt, 900nm wavelength, 28vdc, 600hz pulse frequency. The units also contain an electronic receiver to detect reflected signals from targets. five or more units £299 ea. £349 for one. Ref LOT4.

TWO WAY MIRROR KIT Includes special adhesive film to make two way mirror(s) up to 60"x20". (glass not included) includes full instructions. £12 ref TW1.

NEW LOW PRICED COMPUTER/WORKSHOP/HI-FIRCB UNITS Complete protection from faulty equipment for everybody! In line unit fits in standard IEC lead (extends it by 750mm), fitted less than 10 seconds, reset/test button, 10A rating. £6.99 each ref LOT5. Or a pack of 10 at £49.90 ref LOT6. If you want a box of 100 you can have one for £250!

RADIO CONTROLLED CARS FROM £6 EACH!!!!

All returns from famous manufacturer, 3 types available, single channel (left, right, forwards, backwards) £6 ref LOT1. Two channel with more features £12 ref LOT2.

THOUSANDS AVAILABLE RING/FAX FOR DETAILS!
MAGNETIC CARD READERS (Swipes) £9.95 Cased with flyleads, designed to read standard credit cards! they have 3 wires coming out of the head so they may write as well? complete with control electronics PCB, just £9.95 ref BAR31

WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA? We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14 ref EP74

PANORAMIC CAMERA OFFER Takes double width photographs using standard 35mm film. Use in horizontal or vertical mode. Complete with strap £7.99 ref BAR1

COIN OPERATED TIMER KIT Complete with coin slot mechanism, adjustable time delay, relay output, put a coin on anything you like! TV's, videos, fridges, drinks cupboards, HiFi, takes 50p's and 1c coins. DC operated, price just £7.99 ref BAR27.

ZENTH 900 X MAGNIFICATION MICROSCOPE Zoom, metal construction, built in light, shiftparm, group viewing screen, lots of accessories £29 ref ANAYLT.

AA NICAD PACK Pack of 4 tagged AA nicads £2.99 ref BAR34

PLASMA SCREENS 22x310mm, no data hence £4.99 ref BAR67

NIGHTSIGHTS Model TZ54 with infra red illuminator, views up to 75metres in full darkness in infrared mode, 150m range, 45mm lens, 13 deg angle of view, focussing range 1.5m to infinity. 2 AA batteries required. 950g weight. £199 ref BAR61. 1 years warranty

LIQUID CRYSTAL DISPLAYS Bargain prices, 16 character 2 line, 99x24mm £2.99 ref SM1623A

20 character 2 line, 83x19mm £2.99 ref SM2020A

16 character 4 line, 62x25mm £5.99 ref SMC1640A

TAL-1110MM NEWTONIAN REFLECTOR TELESCOPE Russian. Superb astronomical scope, everything you need for some

serious star gazing! up to 160x magnification. Send or fax for further

WOLVERHAMPTON BRANCH NOW OPEN AT WORCESTER ST WOLVERHAMPTON TEL 01902 77039

detail s £249 ref TAL-1

CENTRAL POINT PC TOOLS Award winning software, 1,300 virus checker, memory optimiser, disc optimiser, file compression, low level formatting, backup scheduler, disk defragmenter, undelete, 4 calculators. Dbase disc editor, over 40 viewers, remote computing, password protection, encryption, comprehensive manual supplied etc £25 ref lot 97 3.5" disks.

GOT AN EXPENSIVE BIKE? You need one of our bottle alarms, they look like a standard water bottle, but open the top, insert a key to activate a motion sensor alarm built inside. Fits all standard bottle carriers, supplied with two keys. SALE PRICE £7.99 REF SA32.

GOT AN EXPENSIVE ANYTHING? You need one of our cased vibration alarms, keyswitch operated, fully cased just fit it to anything from videos to caravans, provides a years protection from 1 PP3 battery, UK made. SALE PRICE £4.99 REF SA33.

DAMAGED ANSWER PHONES These are probably beyond repair so just £4.99 each. BT response 200 machines. REF SA30.

COMPUTER DISC CLEAROUT We are left with a lot of software packs that need clearing so we are selling at disc value only! 50 discs for £4, that's just 8p each! (our choice of discs) £4 ref EP66

IBM PS2 MODEL 160Z CASE AND POWER SUPPLY Complete with fan etc and 200 watt power supply. £9.95 ref EP67

DELL PC POWER SUPPLIES 145 watt, +5,-5,+12,-12, 150x150x85mm complete with switch, flyleads and IEC socket. SALE PRICE £9.99 ref EP55

1.44 DISC DRIVES Standard PC 3.5" drives but returns so they will need attention SALE PRICE £4.99 ref EP68

1.2 DISC DRIVES Standard 5.25" drives but returns so they will need attention SALE PRICE NOW ONLY £3.50 ref EP69

PP3 NICADS Unused but some storage marks. £4.99 ref EP52

DELL PC POWER SUPPLIES (Customer returns) Standard PC psu's complete with flyleads, case and fan, +12v, -12v, +5v, -5v SALE PRICE £1.99 EACH worth it for the bits alone! ref DL1. TRADE PACK OF 20 £29.95 ref DL2.

GAS HOBS AND OVENS Brand new gas appliances, perfect for small flats etc. Basic 3 burner hob SALE PRICE £24.99 ref EP72. Basic small built in oven SALE PRICE £79 ref EP73

RED EYE SECURITY PROTECTOR 1,000 watt outdoor PIR switch SALE PRICE £8.99 ref EP57

ENERGY BANK KIT 100 6"x6" 6v 100mA panels, 100 diodes, connection details etc. £69.95 ref EF112.

PASTEL ACCOUNTS SOFTWARE, does everything for all sizes of businesses, includes word processor, report writer, windowing, networkable up to 10 stations, multiple cash books etc. 200 page comprehensive manual. 90 days free technical support (01342-326009 try before you buy!) Current retail price is £129, SALE PRICE £9.95 ref SA12. SAVE £120!!

COMPLETE PC 200 WATT UPS SYSTEM Top of the range UPS system providing protection for your computer system and valuable software against mains power fluctuations and cuts. New and boxed, UK made Provides up to 5 mins running time in the event of complete power failure to allow you to run your system down correctly. LAST FEW TO CLEAR AT £49.5AVE £30 ref LOT61

BIG BROTHER PSU Cased PSU, 6v 2A output, 2m o/p lead, 1.5m input lead, UK made, 220v. SALE PRICE £4.99 REF EP7



Check out our
WEB SITE

<http://www.pavillon.co.uk/bull-electrical>

RACAL MODEM BONANZA! 1 Racal MPS 1223 1200/75 modem, telephone lead, mains lead, manual and comms software, the cheapest way onto the net! all this for just £13 ref DEC13.

4.6mw LASER POINTER. BRAND NEW MODEL NOW IN STOCK!, supplied in fully built form (looks like a nice pen) complete with handy pocket clip (which also acts as the on/off switch.) About 60 metres range! Runs on 2 AAA batteries. Produces thin red beam ideal for levels, gun sights, experiments etc. just £39.95 ref DEC49 TRADE PRICE £28 MIN 10 PIECES

BULL TENS UNIT Fully built and tested TENS (Transcutaneous Electrical Nerve Stimulation) unit, complete with electrodes and full instructions. TENS is used for the relief of pain etc in up to 70% of sufferers. Drug free pain relief, safe and easy to use, can be used in conjunction with analgesics etc. £49 Ref TEN/1

PC PAL VGA TO TV CONVERTER Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and s/ware. Ideal for laptops or a cheap upgrade. Supplied in kit form for home assembly. SALE PRICE £25 REF SA34

EMERGENCY LIGHTING UNIT Complete unit with 2 double

*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX

BN3 5QT. (ESTABLISHED 50 YEARS)

MAIL-ORDER TERMS: CASH, PO OR CHEQUE

WITH ORDER PLUS £3 P&P PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERY PHONE ORDERS WELCOME (ACCESS VISA, SWITCH, AMERICAN EXPRESS)

TEL: 01273 203500

FAX 01273 323077

E-mail bull@pavillon.co.uk

bulb floodlights, built in charger and auto switch. Fully cased. 6v 8AH lead acid req'd. (secondhand) £4 ref MAG4P11.

YUASHA SEALED LEAD ACID BATTERIES Two sizes currently available this month. 12v 15AH at £18 ref LOT8 and 6v 10AH (suitable for emergency lights above) at just £6 ref LOT7.

ELECTRIC CAR WINDOW DE-ICERS Complete with cable, plug etc SALE PRICE JUST £4.99 REF SA28

AUTO SUNCHARGER 155x300mm solar panel with diode and 3 metre lead fitted with a cigar plug. 12v 2watt. £8.99 REF SA25.

MICRODRIVE STRIPPERS Small cased tape drives ideal for stripping, lots of useful goodies including a smart case, and lots of components. SALE PRICE JUST £4.99 FIVE REF SA26

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit SALE PRICE JUST £4.99 REF SA27

RGB/CGA/EGA/VTL COLOUR MONITORS 12" in good condition. Back analysed metal case. SALE PRICE £49 REF SA16B

PLUG IN ACORN PSU 19v AC 14w, £2.99 REF MAG3P10

13.8V 1.9A PSU cased with leads. Just £9.99 REF MAG10P3

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the C5 motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

PHONE CABLE AND COMPUTER COMMUNICATIONS PACK Kit contains 100m of 6 core cable, 100 cable clips, 2 line drivers with RS232 interfaces and all connectors etc. Ideal low cost method of communicating between PCs over a long distance utilizing the serial ports. Complete kit £8.99. Ref comp 1.

VIEWDATA SYSTEMS made by Phillips, complete with Internal 1200/75 modem, keyboard, psu etc RGB and composite outputs, menu driven, autodialler etc. SALE PRICE £12.99 REF SA18

AIR RIFLES .22As used by the Chinese army for training purposes, so there is a lot about! £39.95 REF EF78. 500 pellets £4.50 ref EF80.

PLUG IN POWER SUPPLY SALE FROM £1.66 Plugs in to 13A socket with output lead, three types available, 9vdc 150mA £1.50 ref SA19, 9vdc 200mA £2.00 ref SA20, 6.5vdc 500mA £2 ref SA21.

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £25 REF: MAG15 12v psu is £5 extra REF: MAG5P2

***MINIATURE RADIO TRANSCIVERS** A pair of walkie talkies with a range up to 2km in open country. Units measure 22x52x155mm. Including cases and earpieces. 2xPP3 req'd. £30.00 pr REF: MAG30

***FM TRANSMITTER KIT** housed in a standard working 13A adaptor! the bug runs directly off the mains so lasts forever why pay £700? or price is £15 REF: EF62 (kit) Transmits to any FM radio.

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

TALKING COINBOX STRIPPER COMPLETE WITH COINSLIP MECHANISMS Originally made to retail at £79 each, these units are designed to convert an ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? SALE PRICE JUST £2.50 REF SA23

GAT AIR PISTOL PACK Complete with pistol, darts and pellets £12.95 Ref EF82B extra pellets (500) £4.50 ref EF80.

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA, SALE PRICE £4.99 REF SA24.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

MIXED GOODIES BOX OF
MIXED COMPONENTS WEIGHING 2 KILOS
YOURS FOR JUST £6.99

4X28 TELESCOPIC SIGHTS Suitable for all air rifles, ground lenses, good light gathering properties. £19.95 ref R7.

GYROSCOPES Remember these? well we have found a company that still manufactures these popular scientific toys, perfect gift for educational use etc. £6 ref EP70

HYPOTHERMIA SPACE BLANKET 215x150cm aluminiumised foil blanket, reflects more than 90% of body heat. Also suitable for the construction of two way mirrors! £3.99 each ref O/L04.1.

LENSTATIC RANGER COMPASS Oil filled capsule, strong metal case, large luminous points. Sight line with magnifying view. 50mm dia, 86gm. £10.99 ref O/K604.

RECHARGE ORDINARY BATTERIES UP TO 10 TIMES! With the Battery Wizard! Uses the latest pulse wave charge system to charge all popular brands of ordinary batteries AAA, AA, C, D, four at a time! Led systems shows when batteries are charged, automatically rejects unsuitable cells, complete with mains adaptor, BS approved. Price is £21.95 ref EP31.

TALKING WATCH Yes, it actually tells you the time at the press of a button. Also features a voice alarm that wakes you up and tells you what the time is! Lithium cell included. £7.99 ref EP26.

PHOTOGRAPHIC RADAR TRAPS CAN COST YOU YOUR LICENCE! The new multiband 2000 radar detector can prevent even the most responsible of drivers from losing their licence!

Adjustable audible alarm with 8 flashing leds gives instant warning of radar zones. Detects X, K, and Ka bands, 3 mile range, 'over the hill' around bends and 'rear trap' facilities. micro size just 4.25"x2.5"x.75". Can pay for itself in just one day! £79.95 ref EP3.

3" DISCS As used on older Amstrad machines, Spectrum plus 3's etc £3 each ref BAR400.

STEREO MICROSCOPES BACK IN STOCK Russian, 200x complete with lenses, lights, filters etc etc very comprehensive microscope that would normally be around the £700 mark, our price is just £299 (full money back guarantee) full details in catalogue

WE BUY SURPLUS STOCK

FOR CASH

BUYERS DIRECT LINE 0802 660377

FREE CATALOGUE

100 PAGE CATALOGUE NOW

AVAILABLE, 50P STAMP OR FREE

ON REQUEST WITH ORDER.

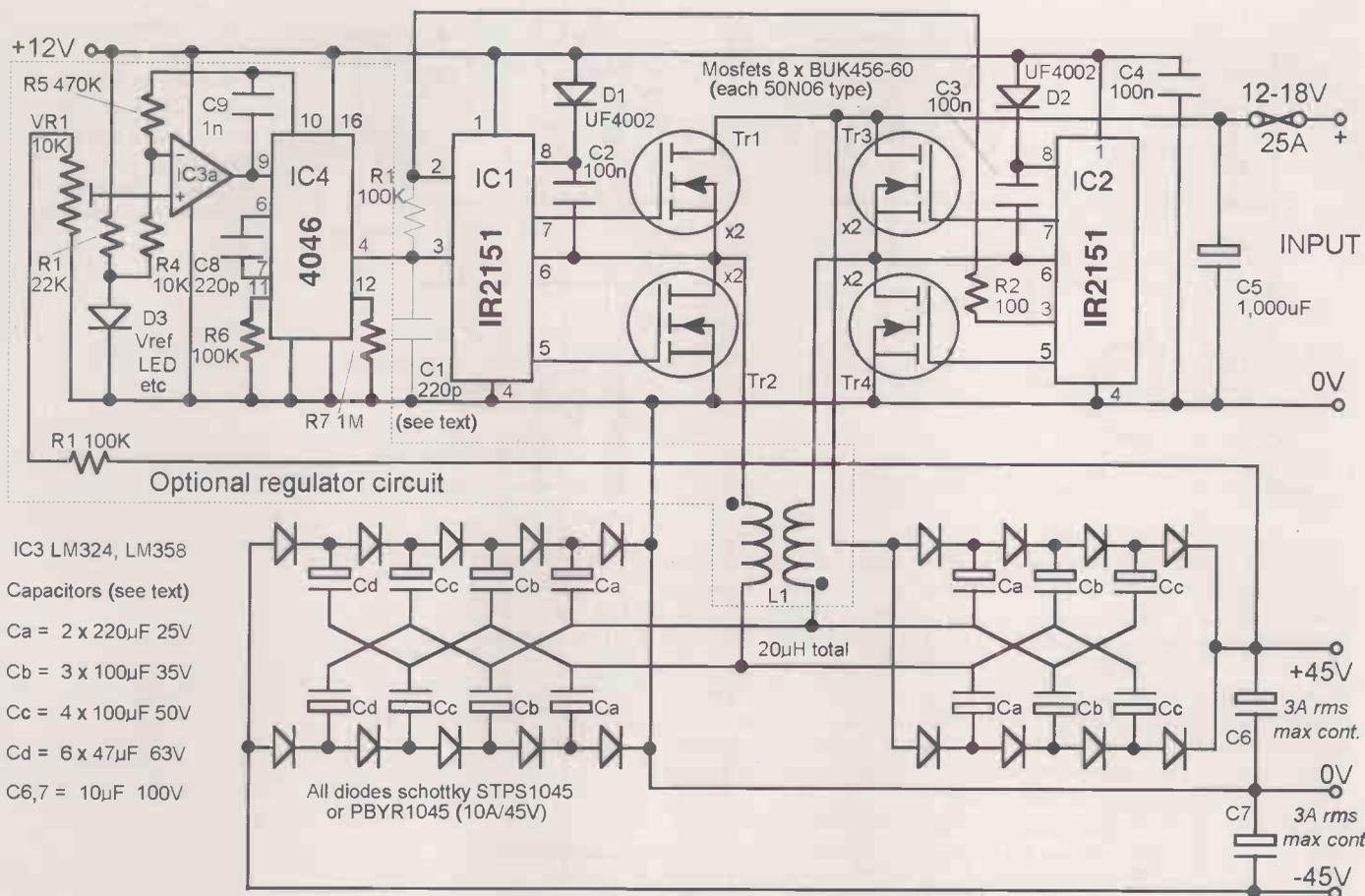


Fig. 7. 300W voltage multiplier featuring over 90% efficiency. It can be used to supply a standard 100W split rail amplifier using a 12V source.

...continued from page 797

dropped. Both methods give the same losses; the same as adding series resistance or a series regulator, which is inefficient with large voltage drops.

I concluded that the only way to efficiently vary the output voltage over a wide range is to use an inductor, either a separate switching regulator, or as part of the multiplier. The latter method was chosen, where a series inductor is inserted between the dc-to-dc converter and the multiplier.

This method of efficient regulation is possible, but only over a limited current range down to about 10 or 20% of full load. This is because frequency is increased to reduce the output current. In turn, this increases gate drive losses at light loads which pulls efficiency down. This places a practical limit on the upper frequency of around 200kHz.

The inductor value is chosen so only a small fraction of the output voltage, around 1V or 2%, is lost at full load where frequency is at its lowest. A relatively small air-cored coil is sufficient, similar to two Zobel inductors but bifilar wound. It should consist of dual seven-turn coils of 1.3mm wire on a 20mm former. Note the connection polarities.

Efficiency at half full voltage, i.e. a quarter of full power, is around 90%. The other methods mentioned above are 50% efficient. If independent regulation of the plus and minus

rails is required then two single mosfet H bridges are needed. A separate regulator circuit including a level shifted feedback signal is needed, via an opto-coupler for example.

If regulation down to no load is required, a low drop-out linear pre-regulator can regulate from the point where the main regulator loses regulation. In this way dissipation in the series regulator will be at most 1/25th of full output power. In Fig. 8a, both low-side mosfets $T_{1,2,4}$ can be used as regulators by controlling their on resistance at low loads. However, output capacitances C_6 and C_7 need to be 22µF or more to ensure linear regulation rather than burst or on-off regulation. Burst regulation can generate annoying interference in the audio range for some applications.

Figure 8b can be used where the fm regulator and inductor are omitted. A 2.2kΩ resistor is placed in the emitter of the feedback transistor to ensure linear operation. Output capacitors C_6 and C_7 should be at least 10µF.

These additions prevent the multipliers capacitors and/or diodes from being destroyed if the input voltage rises too high. The ratings of the diodes and capacitors can be rated closer to levels for normal output which reduces size and cost.

A 4046 voltage-controlled oscillator is used with an op-amp for closed loop voltage regulation. The full load (minimum) frequency is set with R_7 and the light load (maximum) frequency is set with R_6 to 100kHz in my circuit.

With the improved full-wave multiplier, voltage regulation and response time is very good since only a minimal value of output capacitance is required to remove ripple due to dead-time in the H bridge – about 10% of the multipliers capacitance. Again, 10µF is sufficient. However, if the output capacitance is too large, the feedback loop may become unstable and require lag-lead compensation around IC3a. Capacitor C_9 speeds up the oscillator's voltage follower and provides some overall loop phase advance.

Transient response time for a multiplier is related to the number of stages. Output increases from 0V at start up in an exponential way. The time constant was noted to be equal to n times the oscillators period. Here, n here is the number of multiplier stages. For example, four stages with an input frequency of 20kHz has a time constant of 200µs, which can be represented by a pole at 796Hz.

A multiplier for high voltage

The combination of a multiplier and transformer allows extremely high voltage dc to be generated – far higher than a transformer with a simple rectifier can achieve due to the limitation of secondary winding capacitance. The multiplier in Fig. 9 has been used to generate 160kV from 12V using two pentuplers parallel fed similar to Fig. 7. Feeding two multipliers in this way reduces the number of charge transfers and the size of capacitors.

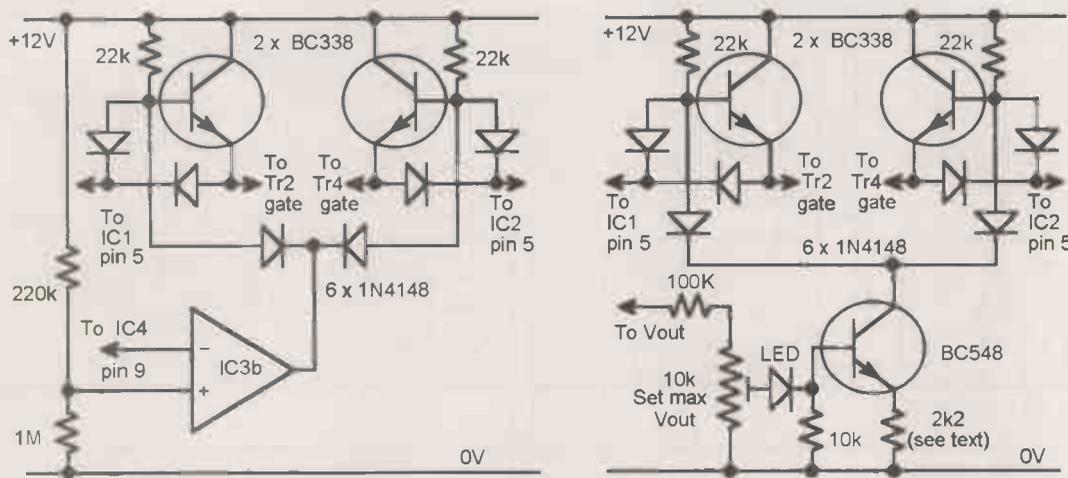


Fig. 8a) Add on circuit for Fig. 7 controls on resistance of the low side mosfets for over-voltage protection of capacitors and diodes. In b), also an add on for Fig. 7, the inductor regulator is not used.

Since the secondary is isolated, any one of the three output terminals can be earthed. This gives the option of either a positive supply, a minus supply, or a split supply. The secondary of a television line transformer provides 16kV peak with five turns on the primary using a an ht lead that can withstand 80kV. Alternatively 2mm thick SCL tubing from Raychem Corporation can be applied to normal wire.

Secondary resonance at around 30kHz is used to advantage to lift the secondary voltage from $3kV_{pk-pk}$ to 16kV. Varying the frequency from above, or below, resonance can be used for voltage control. A string of *BYV96E* 1.5A/1kV avalanche rated diodes – all 384 of them – were used to prevent over-voltage destroying diodes and capacitors by acting like zener diodes. Although the circuit in Fig. 4 can reduce the diode count to 192, the full-wave version provides a low ripple dc output without the very high voltage output capacitor in Fig. 4.

Note that the resistors in the output prevent high peak currents from damaging the diodes if the terminals flash over or are shorted. For those of you wanting to design a high voltage converter and experiment with the effects of high voltage dc, Reference 4 is a good starter. Take care with this converter – high peak currents can be delivered from the capacitors and discharge capacitors after use. When the centre rail is not earthed, the transformer core


must be isolated to withstand 80kV to ground.

A provisional patent on the improved full-wave multiplier, regulator and high voltage generator has been filed⁵. Intellectual property enquiries should be directed through Intellpro, GPO Box 1339, Brisbane 4001, Australia, Fax +61 7 3221 4762. Experimenters are free to use these circuits for non-commercial purposes. ■

References

1. Ian Hickman, Multiplier Lowers Impedance, *EDN*, 6 June 1991, p 173.
2. P. E. K. Donaldson, The Mosmarx Voltage Multiplier, *Electronics & Wireless World*, Aug 1988, p 748-750.
3. Ralph E. Tarter, Solid State Power Conversion Handbook, Wiley 1993, pp 244-251.
4. Robert E. Iannini, Build your own working Fibre-optic, Infrared & Laser space-age projects, 1987 TAB Books, pp 229-255, ISBN 0 8306 2724 3 (pbk).
5. Australian Patent Application No. PN9832 filed 15/5/96.

Fig. 9. This 160kV multiplier, made up from two pentuplers in parallel, outputs up to 100W. Compared with conventional designs, it is more efficient and uses fewer components

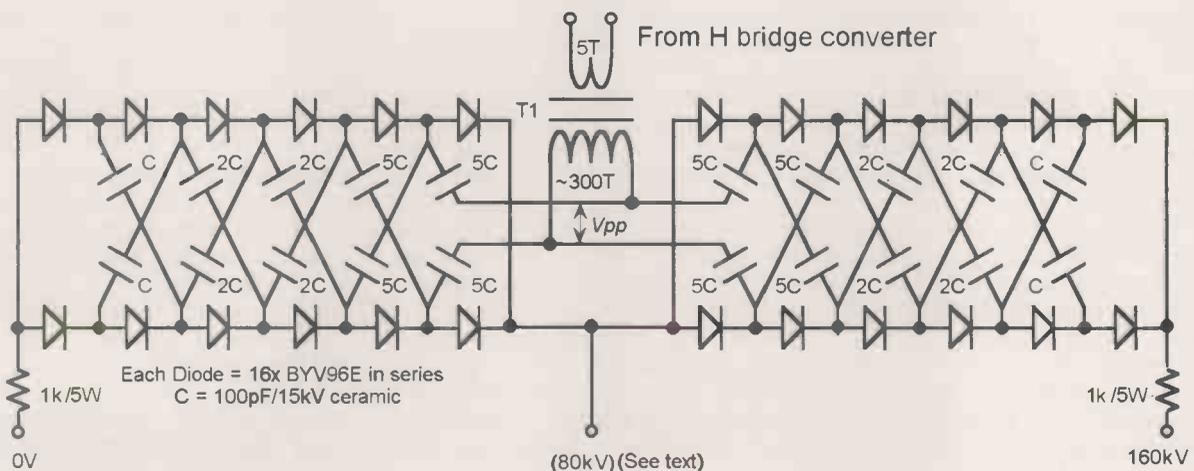

Do you have an original circuit idea for publication? We are giving **£100** cash for the month's top design. Additional authors will receive **£25** cash for each circuit idea published. We are looking for ingenuity in the use of modern components.

WIN A TTI PROGRAMMABLE BENCH MULTIMETER

"High accuracy, resolution and bandwidth - performance beyond the capability of handhelds"



This high-performance bench multimeter could be yours in exchange for a good idea. Featuring a dual display, the 4.5-digit 1705 multimeter resolves down to 10 μ V, 10m Ω and 0.1 μ A and has a basic dc accuracy of 0.04%. Frequency measured is 10Hz to 120kHz with an accuracy of 0.01% and resolution to 0.01Hz. Capacitor and true rms measurements are also featured.

Recognising the importance of a good idea, Thurlby Thandar Instruments will be giving away one of these excellent instruments once every six months. This incentive is in addition to our monthly £100 'best circuit idea' award and £25 awards for each circuit published.

Simple, isolated, 12-bit current loop


A 4-20mA analogue current loop is the recognised method of transmitting signal between instruments in the presence of noise. This circuit provides a simple, isolated interface.


Digital data, by way of the CNY17 low-cost optoisolator, go to the LTC1257 digital-to-analogue converter, which is controlled by an external processor through the other isolators and contains a 2.048V reference. Pull-up resistors of 10k Ω are needed to give

less than 4mA total current consumption, which limits bit rate to around 1kHz. The d-to-a converter gives 500 μ V/count into the LT1006, which supplies 10 μ A/count to the loop. If a different op-amp is to be used, it must operate with both inputs near the negative rail and source nearly 20mA.

Mark McLean
Skelmersdale
Lancashire

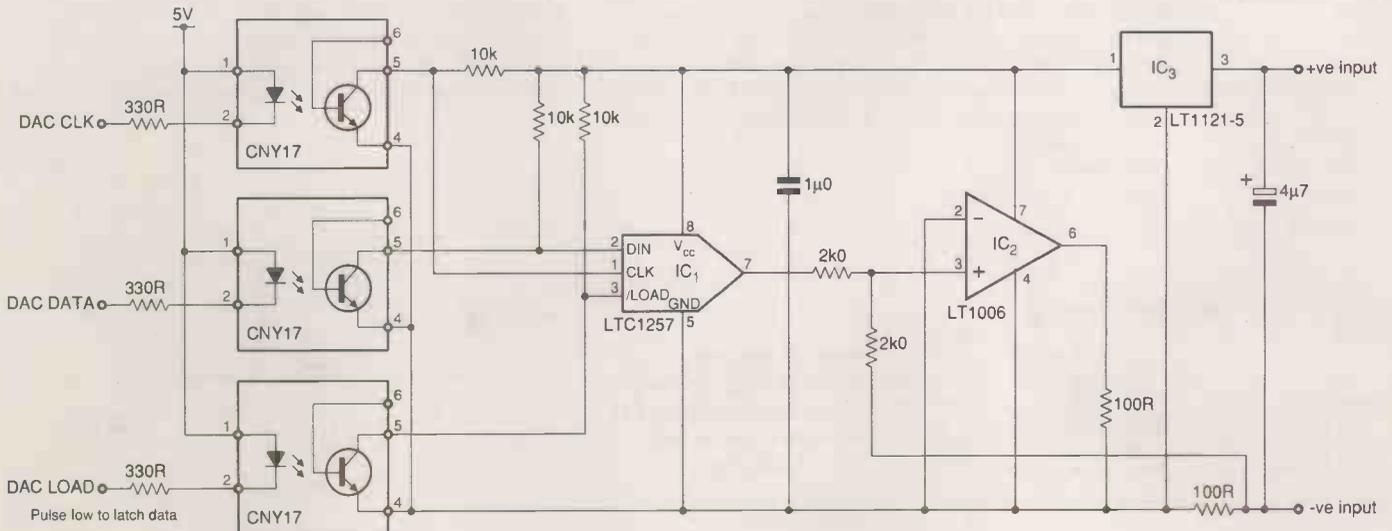This 4-20mA current loop for low-speed operation features optical isolation.



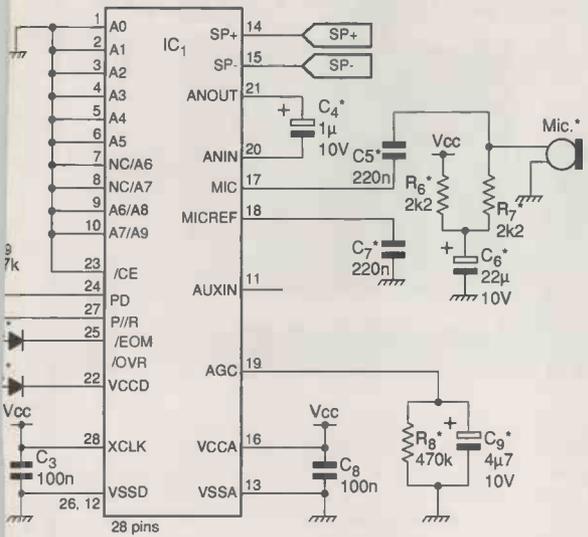

* Components not used in 'Play only' version

Place ISD1020AP in IC₁ for 20 seconds message duration
Place ISD2560P in IC₁ for 60 seconds message duration

Message record/playback for such applications as shop displays, emergency instructions and exhibitions. If you only need to play back pre-recorded messages, omit the components marked with an asterisk.


Fund raiser with odds switches

This electronic version of the "combination lock" seen at church fêtes, in which you have to guess the combination to open a door to win a prize, can be adjusted to vary the odds – high for when children try, since they always seem to do better than adults.

If the three ten-position rotary switches select an invalid combination, pressing the on/off switch activates the sounder; if it does not sound, you get a prize. It could clearly be made to operate a lock to prevent people grabbing a prize anyway, but the idea was cheapness and simplicity. Use the dil switches to vary the odds.

Keith Read
Fleet
Hampshire

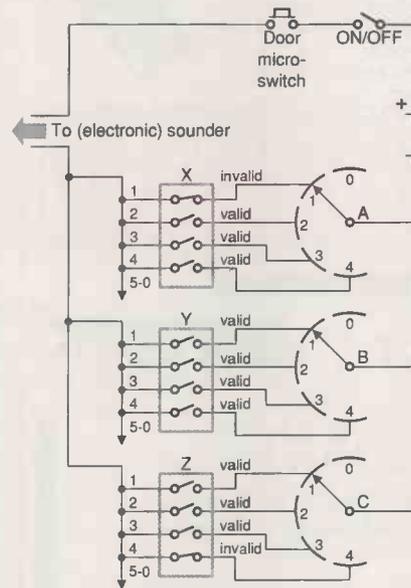Entertainment at the fête. Select the correct combination to win a prize.




amp on pin 11, to remove the supply to the output amplifier.

Since the rssi is a current output of the order of microamps, it may be advisable to use a fet-input op-amp, but the bipolar type used here works reasonably well.

S Mason
Stoke-on-Trent
Staffordshire

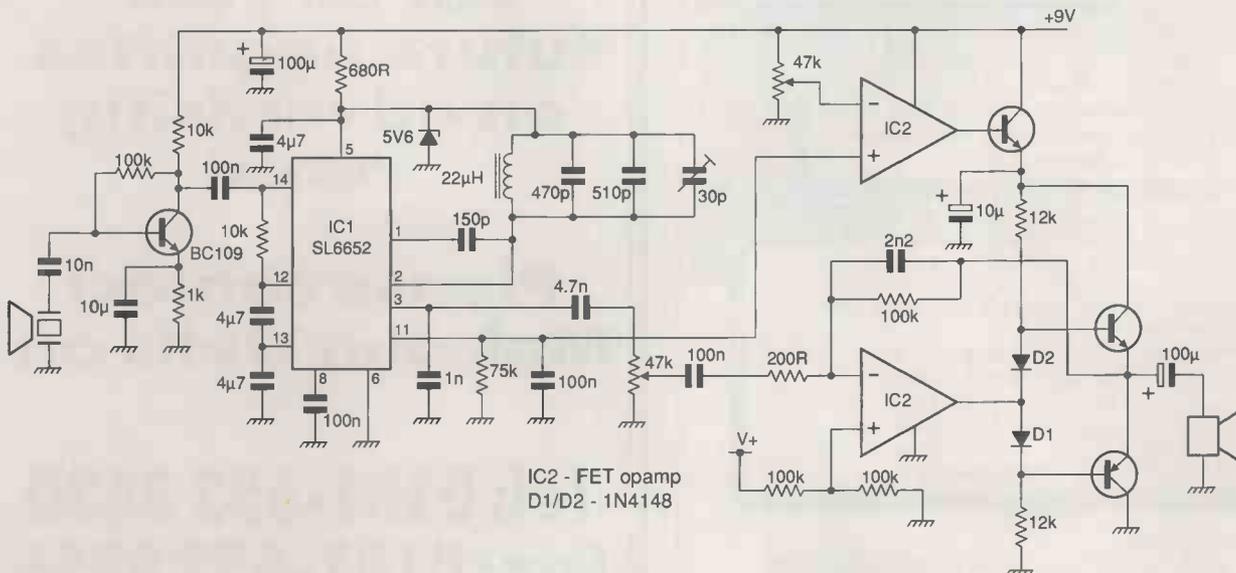Meant for future use underwater, this communicator needs little power and operates at 32kHz. Transmitter is on the left.



£100 WINNER

RADIO DATA MODULES MODEM TRANSCEIVERS

UK, E.E.C, Scandinavia, Eastern Europe, North & South America, Middle East, South Africa, New Zealand, Far East or Australia. Wherever you are, we have a module on the right frequency for you!

UHF Transceiver for the World! * 400 to 500MHz Versions *



Only 55 x 73 x 15mm

- * Range up to 5Km *
- * Compact Size Ideal for Hand Helds *
- * UK, North American, Australian *
- * MPT, I-ETS & FCC Approval *
- * Up to 64 selectable channels *
- * Starter Kit only £299.95 *

Low Cost High Speed Data Transmitters: UK, EEC and Beyond!

* Available UK Approved MPT1340 418MHz *

* Export I-ETS-300-220, 433.92MHz *

- * Reduce Component Count, Cost, Size & Power Drain *
- * Operate to 20,000 bps *

* Transceiver also available with up to 40K data rate *

TXM-418-F Transmitter



Licence Exempt Spread Spectrum on 2.45GHz



With up to 1Mbit data rate, RS485 interface and 100mW of output power these units are ideal for many high speed industrial or office data transfer applications. Even compressed colour video may be transferred. Price £480.00 each or starter kit for only £799.95.

VHF Modules for UK, Australia and Beyond!

- * UK, 173MHz to MPT1344 & MPT1328 Licence Exempt *
- * Miniature Low Cost or canned 1 & 10mW Transmitters *
- * 173.500MHz Transmitters & Transceivers for Australia & RSA *
- * PCB mount or canned, Superhet Receivers *
- * Low Cost Meter Reading Transceivers on 183.8875MHz *
- * Prices from £19.00 to £200.00 per unit *



**Radio - Tech Limited, Overbridge House, Weald Hall Lane
Thornwood Common, Epping, Essex CM16 6NB.**

Sales +44 (0) 1992 57 6107 Fax +44 (0) 1992 56 1994

Technical Support +44 (0) 1992 57 6114

Internet: <http://www.radio-tech.co.uk>

CIRCLE NO. 139 ON REPLY CARD

80C188EB Embedded CPU Card

From
£99



- 80C188EB Processor Clocked at 24MHz
- 128k Battery Backed RAM (512k option)
- 128k Eprom (32k - 512k options)
- 128k 5 volt Flash Eprom (512k option)
- Real Time Clock (On board Battery)
- Watchdog Timer/Reset with Brownout detection
- 2 Serial Ports - 1 RS232, 1 RS232/422/485
- 8 Channel 12 bit ADC (optional)
- Direct Connection to Alphanumeric LCD Display
- 48 Digital I/O lines
- Set-up and Driver routines with Full C Source Code

FAST START - Use our Full ANSI compatible Embedded C Compiler for super fast application development. Supplied complete with Editor, Compiler, Assembler, Linker, Embedded Debug and comprehensive Manual, you can compile and download and be in the Debugger with a single keypress - or back in the editor at just the right place. Generate ROMable Code direct, no struggling with .EXE conversions or messing around with reset code. Just £595.

For further information

Call now - 01379 644285 - Fax 650482

Please ask for our catalogue

Devantech Ltd - 2B/2C Gilray Road - Diss - Norfolk - IP22 3EU

CIRCLE NO. 140 ON REPLY CARD

PCB Designer

For Windows 3.1, '95 or NT



Amex/Access/Delta/Visa

Looking for the price?
It's just £49.00 all inclusive!
...no VAT...no postage...
...no additional charges for
overseas orders.

Dealers and distributors wanted.
Phone (01432) 355 414 to order

Internet
See our Web site at www.niche.co.uk for
information and a working demo. e-mail
pcb@niche.demon.co.uk.

- ✓ Produce Single or Double sided PCBs.
- ✓ Print out to any Windows supported printer.
- ✓ Toolbar for rapid access to commonly used components.
- ✓ Helpful prompts on screen as you work.
- ✓ Pad, track & IC sizes fully customisable.
- ✓ No charges for technical support.
- ✓ Snap-to grid sizes 0.1", 0.05" 0.025" and unrestricted.
- ✓ SMT pads and other pad shapes.

Also available from,

South Africa: JANCA Enterprises, PO Box 32131, 9317 Fichardtpark at R299,00. Phone/FAX: (051) 223744

France: Telindel, Quartier Les Pradets, Chemin des Veys, 83390 Cuers. Phone: 94 28 66 67

CIRCLE NO. 141 ON REPLY CARD

ADVERTISERS PLEASE NOTE


For all your
future enquiries
on advertising
rates

Please contact
Malcolm Wells on

Tel: 0181-652 3620
Fax: 0181-652 8956

Niche Software (UK)

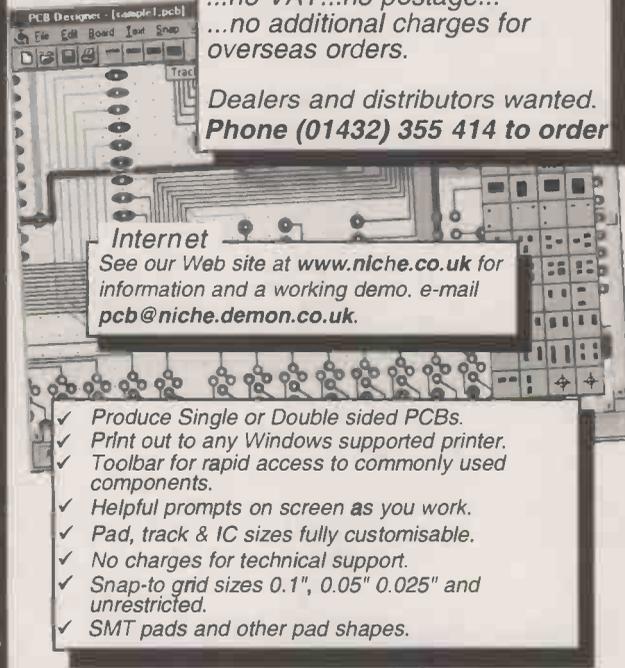12 Short Hedges Close, Northleach, Cheltenham GL54 3PD



DC TO DC CONVERTERS

DRM58 input 10-40vdc output 5v 8A £15
DRM128 input 17-40vdc output 12v 8A £50
DRM158 input 20-40vdc output 15v 8A £50
DRM248 input 29-40vdc output 24v 8A £40
DRS123 input 17-40vdc output 12v 3A £20
DRS153 input 20-40vdc output 15v 3A £20
DRS243 input 29-40vdc output 24v 3A £15

SOLID STATE RELAYS

CMP-DC-200P 3-32vdc operation, 0-200vdc 1A £2.50
SMT20000/3 3-24vdc operation, 28-280vac 3A £4.50
SMT20000/4 3-24vdc operation, 28-280vac 4A £5.00
ZRA6025F 28-280vdc operation, 28-280vac 25A £7.00

200 WATT INVERTERS Nicely cased units 12v input 240v output 150watt continuous, 200 max. £49 ref LOT62.

6.8MW HELIUM NEON LASERS New units, £65 ref LOT33

COIN SLOT TOKENS You may have a use for these? mixed bag of 100 tokens £10 ref LOT20.

PORTABLE X RAY MACHINE PLANS Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £65 set. Ref FXP1.

TELEKINETIC ENHANCER PLANS Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks, yet produces positive motion and effect. Excellent for science projects, magic shows, party demonstrations or serious research & development of this strange and amazing psychic phenomenon. £45 set Ref F/TKE1.

ELECTRONIC HYPNOSIS PLANS & DATA This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc only, by those experienced in its use. £15/set. Ref F/EH2.

GRAVITY GENERATOR PLANS This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of simple materials and without any visible means - cause it to levitate. £10/set Ref F/GRA1.

WORLDS SMALLEST TESLA COIL/LIGHTENING DISPLAY GLOBE PLANS Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects, "Plasma in a jar", St Elmo's fire, Corona, excellent science project or conversation piece. £55/set Ref F/BTC1/LG5.

COPPER VAPOUR LASER PLANS Produces 100mw of visible green light. High coherency and spectral quality similar to Argon laser but easier and less costly to build yet far more efficient. This particular design was developed at the Atomic Energy Commission of NEGEV in Israel. £10/set Ref F/CVL1.

VOICE SCRAMBLER PLANS Miniature solid state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £65/set Ref F/VSS.

PULSED TV JOKER PLANS Little hand held device utilises pulse techniques that will completely disrupt TV picture and sound works on FM tool DISCRETION ADVISED. £85/set Ref F/TJ5.

BODYHEAT TELESCOPE PLANS Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development, etc. Excellent security device or very interesting science project. £85/set Ref F/BHT1.

BURNING, CUTTING CO2 LASER PLANS Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may very well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is easily applicable to burning and etching wood, cutting, plastics, textiles etc £125/set Ref F/LC7.

MYSTERY ANTI GRAVITY DEVICE PLANS Uses simple concept. Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or science project. £65 set Ref F/ANTIK.

ULTRASONIC BLASTER PLANS Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquids. Many cleaning uses for PC boards, jewellery, coins, small parts etc. £65/set Ref F/ULB1.

ULTRAHIGH GAIN AMP/STETHOSCOPIC MIKE/SOUND AND VIBRATION DETECTOR PLANS Ultrasensitive device enables one to hear a whole new world of sounds. Listen through walls, windows, floors etc. Many applications shown, from law enforcement, nature listening, medical heartbeat, to mechanical devices. £65/set Ref F/HGA7.

ANTI DOG FORCE FIELD PLANS Highly effective circuit produces time variable pulses of acoustical energy that dogs cannot tolerate £65/set Ref F/DOG2.

LASER BOUNCE LISTENER SYSTEM PLANS Allows you to hear sounds from a premises without gaining access. £125/set Ref F/LLS1.

LASER LIGHT SHOW PLANS Do it yourself plans show three methods. £6 Ref F/LLS1.

PHASOR BLAST WAVE PISTOL SERIES PLANS Handheld, has large transducer and battery capacity with external controls. £65/set Ref F/PPSP4.

INFINITY TRANSMITTER PLANS Telephone line grabber/room monitor. The ultimate in home/office security and safety! simple to use! Call your home or office phone, push a secret tone on your telephone to access either: A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. £7 Ref F/TELEGRAB.

BUG DETECTOR PLANS Is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Sniffs out and finds bugs and other sources of bothersome

WOLVERHAMPTON BRANCH NOW OPEN AT WORCESTER ST W'HAMPTON TEL 01902 22039

Interference. Detects low, high and UHF frequencies. £55/set Ref F/BD1.

ELECTROMAGNETIC GUN PLANS Projects a metal object a considerable distance - requires adult supervision £5 ref F/EML2.

ELECTRIC MAN PLANS, SHOCK PEOPLE WITH THE TOUCH OF YOUR HAND! £55/set Ref F/EMA1.

PARABOLIC DISH MICROPHONE PLANS Listen to distant sounds and voices, open windows, sound sources in 'hard to get' or hostile premises. Uses satellite technology to gather distant sounds and focus them to our ultra sensitive electronics. Plans also show an optional wireless link system. £85/set Ref F/PM5.

2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND HIGH DC VOLTAGE, SOLID STATE TESLA COIL AND VARIABLE 100,000 VDC OUTPUT GENERATOR PLANS Operates on 9-12vdc, many possible experiments. £10 Ref F/HVM7/TCLA.

INFINITY TRANSMITTERS The ultimate 'bug' fits to any phone or line, undetectable, listen to the conversations in the room from anywhere in the world! 24 hours a day 7 days a week! Just call the number and press a button on the mini controller (supplied) and you can hear everything! Monitor conversations for as long as you choose £249 each, complete with leads and mini controller! Ref LOT9. Undetectable with normal RF detectors, fitted in seconds, no batteries required, lasts forever!

SWITCHED MODE PSU'S 244 watt, +5 32A, +12 6A, -5 0.2A, -12 0.2A. There is also an optional 3.3v 25A rail available. 120/240v I/P. Cased, 175x90x145mm. IEC inlet Suitable for PC use (6 d/drive connectors 1 m/board). £10 ref PSU1.

VIDEO PROCESSOR UNITS?/6v 10AH BATT/12V 8A TX Not too sure what the function of these units is but they certainly make good strippers! Measures 390X320X120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connectors on the rear. Inside 2x 6v 10AH sealed lead acid batts, pcb's and a 8A? 12v toroidal transformer (mains in). Condition not known, may have one or two broken knobs due to poor storage. £17.50 ref VP2.

RETRON NIGHT SIGHT Recognition of a standing man at 300m in 1/4 moonlight, hermetically sealed, runs on 2 AA batteries, 80mm F1.5 lens, 20mw infrared laser included. £325 ref RETRON.

MINI FM TRANSMITTER KIT Very high gain preamp, supplied complete with FET electret microphone. Designed to cover 88-108 Mhz but easily changed to cover 63-130 Mhz. Works with a common 9v (PP3) battery. 0.2W RF. £7 Ref 1001.

3-30V POWER SUPPLY KIT Variable, stabilized power supply for lab use. Short circuit protected, suitable for professional or amateur use 24v 3A transformer is needed to complete the kit. £14 Ref 1007.

1 WATT FM TRANSMITTER KIT Supplied with piezo electric mic. 8-30vdc. At 25-30v you will get nearly 2 watts! £12 ref 1009.

FM/AM SCANNER KIT Well not quite, you have to turn the knob yourself but you will hear things on this radio that you would not hear on an ordinary radio (even TV). Covers 50-160mhz on both AM and FM. Built in 5 watt amplifier, inc speaker. £15 ref 1013.

3 CHANNEL SOUND TO LIGHT KIT Wireless system, mains operated, separate sensitivity adjustment for each channel, 1,200 w power handling, microphone included. £14 Ref 1014.

4 WATT FM TRANSMITTER KIT Small but powerful FM transmitter, 3 RF stages, microphone and audio preamp included. £20 Ref 1028.

STROBE LIGHT KIT Adjustable from 1-80 Hz (a lot faster than conventional strobes). Mains operated. £16 Ref 1037.

COMBINATION LOCK KIT 9key, programmable, complete with keypad, will switch 2A mains. 9v dc operation. £10 ref 1114.

PHONE BUG DETECTOR KIT This device will warn you if somebody is eavesdropping on your line. £6 ref 1130.

ROBOT VOICE KIT Interesting circuit that distorts your voice adjustable, answer the phone with a different voice! 12vdc £9 ref 1131.

TELEPHONE BUG KIT Small bug powered by the phone line, starts transmitting as soon as the phone is picked up! £8 Ref 1135.

3 CHANNEL LIGHT CHASER KIT 800 watts per channel, speed and direction control supplied with 12 LEDs (you can fit triacs instead to make kit mains, not supplied) 9-12vdc £17 ref 1026.

12V FLOURESCENT LAMP DRIVER KIT Light up 4 foot tubes from your car battery! 9v 2a transformer also required £8 ref 1069.

VOX SWITCH KIT Sound activated switch ideal for making bugging tape recorders etc, adjustable sensitivity. £8 ref 1073.



Check out our
WEB SITE

<http://www.pavillon.co.uk/bull-electrol>

PREAMP MIXER KIT 3 Input mono mixer, sep bass and treble controls plus individual level controls. 18vdc, Input sens 100mA. £15 ref 1052.

*SOME OF OUR PRODUCTS MAY BE UNLICENSEABLE IN THE UK

BULL ELECTRICAL
250 PORTLAND ROAD, HOVE, SUSSEX.
BN3 5QT. (ESTABLISHED 50 YEARS)

MAIL ORDER TERMS: CASH, PO OR CHEQUE
WITH ORDER PLUS £3 P&P PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERY PHONE ORDERS WELCOME (ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

TEL: 01273 203500
FAX 01273 323077
E-mail bull@pavillon.co.uk

SOUND EFFECTS GENERATOR KIT Produces sounds ranging from bird chirps to sirens. Complete with speaker, add sound effects to your projects for just £9 ref 1045.

16 WATT FM TRANSMITTER (BUILT) 4 stage high power, preamp required 12-18vdc, can use ground plane, yagi or open dipole. £69 ref 1021.

HUMIDITY METER KIT Builds into a precision LCD humidity meter, 9ic design, pcb, lcd display and all components included. £29

PC TIMER KIT Four channel output controlled by your PC, will switch high current mains with relays (supplied). Software supplied so you can program the channels to do what you want whenever you want. Minimum system configuration is 286, VGA, 4.1, 640k, serial port, hard drive with min 100k free. £24.99

FM CORDLESS MICROPHONE This unit is an FM broadcasting station in miniature, 3 transistor transmitter with electret condenser mic + fet amp design result in maximum sensitivity and broad frequency response. 90-105mhz, 50-1500hz, 500 foot range in open country! PP3 battery required. £15.00 ref 15P42A.

MAGNETIC MARBLES They have been around for a number of years but still give you to curiosity and amazement. A pack of 12 is just £3.99 ref GI/R20.

NICKEL PLATING KIT Professional electroplating kit that will transform rusting parts into showpieces in 3 hours! Will plate onto steel, iron, bronze, gunmetal, copper, welded, silver soldered or brazed joints. Kit includes enough to plate 1,000 sq inches. You will also need a 12v supply, a container and 2 12v light bulbs. £39.99 ref NIK39.

Miniature adjustable timers, 4 pole c/o output 3A 240v, HY1230S, 12vDC adjustable from 0-30 secs. £4.99
HY1260M, 12vDC adjustable from 0-60 mins. £4.99
HY2405S, 240v adjustable from 0-5 secs. £4.99
HY24060m, 240v adjustable from 0-60 mins. £6.99

BUGGING TAPE RECORDER Small voice activated recorder, uses micro cassette complete with headphones. £28.99 ref MAR29P1.

POWER SUPPLY fully cased with mains and op leads 17v DC 900mA output. Bargain price £5.99 ref MAG6P9.

9v DC POWER SUPPLY Standard plug in type 150ma 9v DC with lead and DC power plug. price for two is £2.99 ref AUG3P4.

COMPOSITE VIDEO KIT. Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: MAG8P2.

FUTURE PC POWER SUPPLIES These are 295x135x60mm, 4 drive connectors 1 mother board connector. 150watt, 12v fan, iec inlet and on/off switch. £12 Ref EF6.

VENUS FLYTRAP KIT Grow your own carnivorous plant with this simple kit £3 ref EF34.

6"x12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just £5.99 ea REF MAG6P12.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

ROCK LIGHTS Unusual things these, two pieces of rock that glow when rubbed together believed to cause rain! £3 a pair ref EF29.

3' by 1' AMORPHOUS SOLAR PANELS 14.5v, 700mA 10 electric mats, aluminium frame, screw terminals. £44.95 ref MAG45.

ELECTRONIC ACCUPUNCTURE KIT Builds into an electronic version instead of needles! good to experiment with. £7 ref 7P30.

SHOCKING COIL KIT Build this little battery operated device into all sorts of things, also gets worms out of the ground! £7 ref 7P36.

FLYING PARROTS Easily assembled kit that builds a parrot that actually flaps its wings and flies! 50 m range £6 ref EF2.

HIGH POWER CATAPULTS Hinged arm brace for stability, tempered steel yoke, super strength latex power bands. Departure speed of ammunition is in excess of 200 miles per hour! Range of over 200 metres! £7.99 ref R9.

BALLON MANUFACTURING KIT British made, small blob blow into a large, long lasting balloon, hours of fun! £3.99 ref GI/E99R

9-0-9V 4A TRANSFORMERS, chassis mount. £7 ref LOT19A.

2.5 KILOWATT INVERTERS, Packed with batteries etc but as they weigh about 100kg CALLERS ONLY! £120.

MEGA LED DISPLAYS Build your self a clock or something with these mega 7 seg displays 55mm high, 38mm wide. 5 on a pcb for just £4.99 ref LOT16 or a bumper pack of 50 displays for just £29 ref LOT17.

CLEARANCE SECTION, MINIMUM ORDER £15, NO TECHNICAL DETAILS AVAILABLE, NO RETURNS, TRADE WELCOME.

2000 RESISTORS ON A REEL (SAME VALUE) 99P REF BAR340

AT LEAST 200 CAPACITORS (SAME VALUE) 99P REF BAR342

INFRA RED REMOTE CONTROLS JUST 99P REF BAR333

CIRCUIT BREAKERS, OUR CHOICE TO CLEAR 99P REF BAR335

MICROWAVE CONTROL PANELS TO CLEAR £2 REF BAR 329

2 TUBES OF CHIPS (2 TYPES OUR CHOICE) 90P REF BAR305

LOTTERY PREDICTOR MACHINE!! JUST £1.50 REF BAR313

HELLA L/OVER ELECTRIC LAMP LEVELLER £2 REF BAR311

SINCLAIR C5 18" TYRES TO CLEAR AT JUST 75P REF BAR318

LARGE MAINS MOTORS (NEW) TO CLEAR AT 75P REF BAR310

MODEMS ETC FOR STRIPPING £2.50 EACH REF BAR324

110V LARGE MOTORS (NEW) TO CLEAR AT 50P REF BAR332

MODULATOR UNITS UNKNOWN SPEC JUST 50P REF BAR323

GX4000 GAMES COGSOLES JUST £4 REF BAR320

SMART CASH MEMORY STORAGE DEVICE, LOADS OF BITS INSIDE, PCB, MOTOR, CASE ETC. BUMPER PACK OF 5 COMPLETE UNITS TO CLEAR AT £2.50 (FOR 5) REF BAR 330.

2 CORE MAINS CABLE 2M LENGTHS PACK OF 4 £1 REF BAR337

PC USER/BASIC MANUALS, LOADS OF INFO. £1 REF BAR304

PCB STRIPPERS TO CLEAR AT 2 FOR 99P REF BAR341

3 M 3 CORE MAINS CABLE AND 13A PLUG. 60P REF BAR325

**WE BUY SURPLUS STOCK
FOR CASH
BUYERS DIRECT LINE 0802 660377**

**FREE CATALOGUE
100 PAGE CATALOGUE NOW
AVAILABLE, 45P STAMPS.**

...continued from page 783

That opinion may be sound, but the DTI has obtained it at second hand. Only the broadcasters and their equipment suppliers can know at first hand how much scope they have for greater spectrum efficiency and the costs of their options. And even they can have only a vague idea until they study them in earnest, which they will not do until they are faced with a real prospect of having to pay for the true value of their spectrum. Meanwhile they have a vested interest in playing down the scope for better

Inset 8 – Allocations to emergency services
Police, fire and ambulance services require, and pay for, a large range of equipment and materials. They also pay salaries which are at least large enough to retain their work forces and they trade off the costs of equipment and materials against each other and against the cost of personnel like any other employer. The commercial environment is generally beneficial to those services and raises their standards, compared with countries where the price mechanism is suppressed.

Having to pay for spectrum would not undermine their ability to catch criminals, put out fires and treat injured people any more than having to pay for police cars, fire engines and ambulances, which nobody suggests should be provided free of charge.

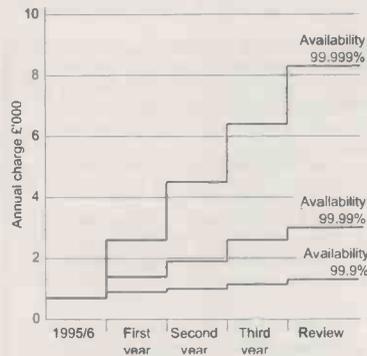


Fig. 4. Point-to-point fixed links between 4 and 15GHz. In the first of two regions involved, FR1, which includes Greater London and West Midlands, charges will rise by nearly 12 times.

spectrum efficiency and exaggerating its cost. Elsewhere the white paper speaks of using licensing powers to promote strategic objectives and develop innovative technical approaches. The white paper also speaks of giving financial assistance to accelerate desirable changes and using spectrum pricing to achieve specific management objectives. In other words the intention is for the spectrum managers to continue using their judgment of how radio communications should develop instead of relying on the price mechanism.

How much any government is wise to rely

on second-hand information from financially interested parties to decide which industrial developments to promote is always controversial. Before spectrum pricing that was the only way in which the RA or its predecessors could prevent waste in the use of spectrum. In the future however, when spectrum pricing has bedded down, it will not have to be so proactive. It could allow the users and manufacturers to take those decisions, in the knowledge that spectrum pricing will curb any tendency to extravagance. Perhaps in due course the penny will drop in ministerial circles. ■

References

1. HMSO Cm 3252, £9.10. (DTI invites comments on or before 25 October.)
2. D. Rudd, 'Pricing versus rationing', *Electronics World*, September 1996.
3. Report of the Independent Review of the Radio Spectrum (30-960MHz), chairman Dr. J.H.H. Merriman C.B. O.B.E. F.Eng., July 1983, HMSO Cmnd 9000.
4. D. Rudd, 'A renting system for radio spectrum?', IEE Proceedings, Part A, January 1986.
5. CSP International, 'Deregulation of the radio spectrum in the UK', March 1987, HMSO.
6. D. Rudd, 'Privatisation of the radio spectrum' *EW+WW*, September 1987.

High-quality circuit boards for Douglas Self's precision preamplifier '96

A high quality double-sided circuit board is available for Doug Self's precision preamplifier, exclusively via *Electronics World*. The board takes the full stereo preamplifier, including all power supply components except the transformer. Its layout is optimised to provide exceptionally low crosstalk.

Co-designed by Gareth Connor, the board is glass-fibre with plated-through holes and roller-finned. It features solder masking and full component identification. Component lists and assembly notes – containing extra information about the preamplifier – are supplied with each order.


Each board is £59 inclusive of package, VAT and recorded

postage. Please include a cheque or postal order with your request, payable to Reed Business Publishing. Alternatively, send your credit card details – i.e. card type, number and expiry date. Include the delivery address in the order, which in the case of credit card holders must be the address of the card holder. Add a daytime telephone and/or fax number if you have one.

Send your order to Electronics World Editorial, PCBs, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Alternatively fax us on 0181 652 8956 or e-mail jackie.lowe@rbp.co.uk. Credit card details can be left on the answering machine on 0181 652 3614. Please allow 28 days for delivery.

Features of Douglas Self's precision preamplifier

- Very low noise and distortion.
- Moving-coil – sensitivity switchable 0.1 or 0.5mV, ±0.05dB RIAA accuracy.
- Moving-magnet input with ±0.05dB RIAA accuracy, 5V rms sensitivity.
- Three 150mV line inputs.
- One dedicated compact-disc input.
- Tape-monitor switch.
- Active-balance control.
- Tone control – switch defeatable – with ±10dB range.
- Tone control treble and bass frequencies variable over 10:1 range.
- Active volume control for optimal noise/headroom and enhanced interchannel matching.
- Intelligent relay muting on outputs.
- CD input sensitivity 1V rms.

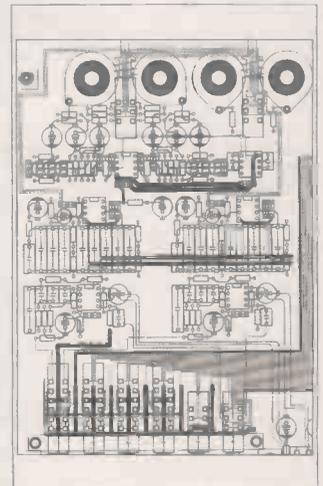

CLASSIFIED

TEL 0181 652 3620

FAX 0181 652 8956

ARTICLES WANTED

WE WANT TO BUY!!

**IN VIEW OF THE EXTREMELY
RAPID CHANGE TAKING PLACE
IN THE ELECTRONICS
INDUSTRY, LARGE QUANTITIES
OF COMPONENTS BECOME
REDUNDANT. WE ARE CASH
PURCHASERS OF SUCH
MATERIALS AND WOULD
APPRECIATE A TELEPHONE
CALL OR A LIST IF AVAILABLE.
WE PAY TOP PRICES AND
COLLECT.**

R. HENSON LTD.

**21 Lodge Lane, N. Finchley,
London N12 8JG.**

5 Mins, from Tally Ho Corner.

TELEPHONE

0181-445-2713/0749

FAX 0181-445-5702

TOP PRICES PAID

For all your valves, tubes, semi
conductors and IC's.

Langrex Supplies Limited

1 Mayo Road, Croydon
Surrey CR0 2QP

TEL: 0181-684 1166
FAX: 0181-684 3056

WANTED

TOP PRICES PAID

For all your Test Equipment,
Receivers, Transmitters etc.
Factory Clearance, Prompt
Service and Payment.

HTB ELEKTRONIK

Alter Apeler Weg 5
27619 Schiffdorf, Germany
Tel: 0049 4706 7044
Fax: 0049 4706 7049

HP TEST EQUIPMENT WANTED!

WE ARE ALWAYS LOOKING FOR:
• HP8510A, B OR C SYSTEMS +
PARTS
• NON WORKING HP8510 PARTS
• IF SECTIONS FOR HP8510 SYSTEM
• HP8350B + PLUGINS
• HP84XX POWER SENSORS
• HP436, HP437 POWERMETERS
• HP MANUALS + SOFTWARE
• HP 70000 SERIES PARTS
L. BAIER TEST EQUIPMENT
PH: +49 925192163 FAX: +49 92517846

HP478A or similar thermistor mount
needed (can be burned out!). Mueller,
Zum Goldesacker 10, D52459 Inden-
Pier, Germany (49) 24 61 61 4259.
WANTED: Schematic or manual air-
mec 732 5kV ionisation tester. R J
Ritter, Buttlershof 18 CH-9424,
Rheinneck, Switzerland.

ELECTRONICS VALVES & SEMICONDUCTORS

Phone for a most
courteous quotation

We are one of the largest
stockists of valves etc,
in the U.K.

COLOMOR ELECTRONICS LTD

170 Goldhawk Road,
London W12 8HJ
England.

Tel: 0181 743 0899
Fax: 0181 749 3934

VALVES, and CRTs AVAILABLE

ONE MILLION VALVES stocked for Audio, Receiving, Transmit-
ting & RF Heating. Rare brands such as Mullard & GEC available.
Also MAGNETRONS, KLYSTRONS, CRTs and SOCKETS.

Large stocks of Russian & Sovtek items.

Please ask for our free catalogues of valves or CRTs.

VALVES, etc. WANTED

Most types considered but especially KT88 (£48), PX4/PX25
(£50), KT66 (£35), KT77 (£15), EL34 (£10), EL37 (£9), ECC83 (£3).
Valves must be UK manufacture to achieve prices mentioned.
Also various valve-era equipment e.g. Garrard 301, (up to) £80.
Ask for a free copy of our wanted List.

BILLINGTON EXPORT LTD., Billingshurst, Sussex RH14 9EZ.
Tel: 01403 784961 Fax: 01403 783519

VISITORS STRICTLY BY APPOINTMENT.

MINIMUM ORDER £50 plus VAT

WANTED: TEST EQUIPMENT + SURPLUS

WE ARE ALWAYS BUYING:

- TEST EQUIPMENT RF + MICROWAVE PARTS
 - TEST EQUIPMENT MANUALS
 - NON-WORKING OR SCRAP TEST EQUIPMENT
- FAX YOUR LIST TODAY FOR AN INSTANT QUOTE!

LOTHAR BAIER TEST EQUIPMENT
BLUMENSTRASSE 8 D-95213 MUENCHBERG
PHONE: +49 925192183 FAX: +49 92517846

WE ALWAYS PAY THE BEST PRICE!!!

WANTED

Test equipment, receivers, valves,
transmitters, components, cable
and electronic scrap and quantity.

Prompt service and cash.

M & B RADIO

86 Bishopgate Street
Leeds LS1 4BB

Tel: 0113 2435649

Fax: 0113 2426881

★★WANTED★★

Test equipment, Electronic Scrap,
Valves, Transmitters/Receivers,
Factory & Warehouse Clearance.
Confidentiality Assured.

TELFORD ELECTRONICS

Phone: 01952 605451

Fax: 01952 677978

VALVES, and CRTs AVAILABLE

ONE MILLION VALVES stocked for Audio, Receiving, Transmit-
ting & RF Heating. Rare brands such as Mullard & GEC available.
Also MAGNETRONS, KLYSTRONS, CRTs and SOCKETS.

Large stocks of Russian & Sovtek items.

Please ask for our free catalogues of valves or CRTs.

VALVES, etc. WANTED

Most types considered but especially KT88 (£48), PX4/PX25
(£50), KT66 (£35), KT77 (£15), EL34 (£10), EL37 (£9), ECC83 (£3).
Valves must be UK manufacture to achieve prices mentioned.
Also various valve-era equipment e.g. Garrard 301, (up to) £80.
Ask for a free copy of our wanted List.

BILLINGTON EXPORT LTD., Billingshurst, Sussex RH14 9EZ.
Tel: 01403 784961 Fax: 01403 783519

VISITORS STRICTLY BY APPOINTMENT.

MINIMUM ORDER £50 plus VAT

ARTICLES FOR SALE

OVERSTOCKED TEST EQUIPMENT FOR SALE

- HP435A, HP438B, TEK 7L14, HP8569A, EATON 767, HP36241, HP3683B, HP64110D,
HP8756A, MAR 6500, WIL 560, WIL 6648B, EIP 598, HP70301, HP70900A, HP70205,
HP70206, FLUKE 6070, HP85101B-010

ALL ITEMS IN WORKING ORDER !!!

FAX YOUR OFFERS TO: +49 92517846

CLASSIFIED

TEL 0181 652 3620

FAX 0181 652 8956

ARTICLES FOR SALE

Consider

Your costs to continue to stock
UNWANTED SURPLUS . . . EXCESS . . . OBSOLETE
STOCKS OF:-
ELECTRONIC-ELECTRICAL COMPONENTS &
ACCESSORIES

RELEASE
for
PAYMENT IN ADVANCE
OF COLLECTION
contact

K.B. Components,

21 Playle Chase, Gt. Totham, Maldon, Essex, CM9 8UT
Tel:- 01621 893204 Fax:- 01621 893180 Mobile:- 0802 392745

REGISTER TO RECEIVE MONTHLY PUBLISHED STOCK LISTS AT NO CHARGE OF
ALL EXISTING NEW, UNUSED, STOCKS OF ALL COMPONENTS AND ACCESSORIES.

MAINS HARMONIC CURRENT CORRECTOR

will assist in compliance with
EN61000-3 and overcome supply
voltage distortion.

Demonstration Model, Design
Notes and Circuits for Sale

D. Thomas
01279-428935

SPECTRUM ANALYSERS Marconi
TF2370 £550, H.P. 141T 110MHz £550,
1300MHz £650. Manuals, Scopes, Sig.
Gens. Many others 01344 27869.

WW2 ROTARY TRANSFORMER
Type 29. Input 24V, 16A. Output
1230V, 200MA. New boxed p/p.
£100.00. 01472 813144.

ADVERTISERS PLEASE NOTE

For all your
future enquiries
on advertising
rates

Please contact
Malcolm Wells on

Tel: 0181-652 3620
Fax: 0181-652 8956

Memory Simms

256K £2.50 each Min Qty 4 - £10
512K £5.00 each Min Qty 2 - £10
1MB £14.00 each

DRAM

256K	
HY53C256LS - 10	£1.50
TMS4256 - 10L	£1.30
MB81256 - 10	£1.30
MCM6256 - 10	£1.30
MN41256A - 08	£1.40
1MB	
V53C104P - 12	£2.00
GM71C4256A - 80	£2.40
M514256 - 10	£2.30
KM44C256AP - 10	£2.30
MN41C4256 - 08	£2.40

EPROMS

1MB - £2.00
512K - £1.25
256K - £1.00
128K - £0.75
64K - £0.50
32K - £0.40
16K - £0.35

SRAM

TMM2063P -	£1.50
1S61C64A - 20N	£1.20
UT4264 - 20	£1.20

1000's MORE COMPONENTS IN STOCK - PLEASE CALL

ALL ITEMS PRE-USED AND TESTED MINIMUM ORDER CHARGE £10

ALL ITEMS EXCLUDE VAT @ 17.5% CREDIT CARDS WELCOME

WOODVILLE LTD TEL: 01923 213350 FAX: 01923 211650

HOW TO PROTECT YOUR POWERBASE

with the NEW Galatrek
Elite UPS range

50% smaller,
40% lighter

- Superior, Intelligent, on-line 'plug and play' operation
- High surge and spike protection
- PowerBoost advanced battery management
- Runtime battery extension packs
- FREE PowerSave UPS management software
- Part of a range from 280VA to 700KVA

For your FREE edition of our
Autumn 96 Power Information Pack



FREEPHONE
0800 269394
Ext 312

Part of the M.I. Group of Companies or fax 01492 641 828

EW+WW PC TELETEXT, Aug 1994

PCB, EPROM & DISC with
Terminal Software and Partslist,
£12 to clear! LM1414 £2.50
SN74121 50p P&P Inc.

Citifax Ltd
9 Goose Cote Hill
Bolton BL7 9UQ

Tel/Fax +44 1204 417 210

25A LISN, 85KHz, 30MHz, 50R, 1µV
receiver, pre-tuner with 2 loop and 1
rod aerials, all by Schwarzbeck £450.
01234 219756.

MARCONI 2022A signal generator for
sale £2,000. Phone: 0956 57 56 72. Fax:
0181 316 5627.

RECRUITMENT

Electronics, Computing and Motion Control Engineer

The Applicant must have a thorough knowledge of electronics, preferably as applied to film, video and motion control equipment. He or she should have design and small scale manufacturing experience and, ideally, will have experience processing microprocessors.

An ability to problem solve, work on your own initiative to deadlines and under pressure is essential.

The job will be based in Bristol, but occasional travel may be necessary.

SALARY will be commensurate with experience.

Please send CV with covering letter, before October 1, to:

Box Number 111

ELECTRONICS WORLD, Room L329
Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

CLASSIFIED

TEL 0181 652 3620

FAX 0181 652 8956

ARTICLES FOR SALE



SUPPLIER OF QUALITY USED TEST INSTRUMENTS



CONTACT


Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham,
Bognor Regis, West Sussex, PO22 0EB, U.K.
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

CIRCLE NO. 142 ON REPLY CARD



OPERATING & SERVICE MANUALS

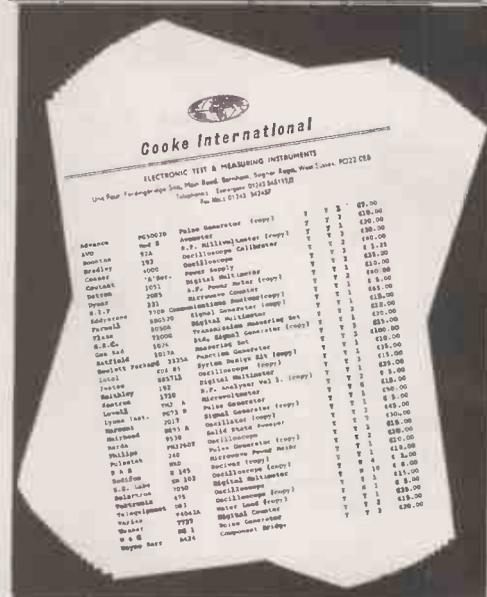

CONTACT

Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham,
Bognor Regis, West Sussex, PO22 0EB, U.K.
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

CIRCLE NO. 143 ON REPLY CARD

INDEX TO ADVERTISERS

	PAGE		PAGE		PAGE
Anchor	779	John's Radio	740	Quickroute Systems	722
Bull Electrical	804	JPG Electronics	792	Radio-Tech	810
Bull Electrical	811	Kenwood UK	785	Ralfe Electronics	816
CMS	749	Labcenter Electronics	762	Robinson Marshall	767
Conford	749	Langrex Supplies	791	Seetrex	798
Dataman Programmers	OBC	M & B Radio	792	Stewart of Reading	792
Devantech	810	Marlow Ind. Europe	785	Surrey Electronics	791
Display Electronics	757	Milford Instruments	IBC	Telford Electronics	798
Electromail	751	Niche Software	810	Telnet	803
Equinox Technologies	IFC	Number One Systems	803	Those Engineers	775
Field Electrics	749	Oema	789	Tie Pie	780
Halcyon	749	Olson Electronics	768	Tsien	780
Hart Electronics	726	Pico Technology	784	Ultimate Technology	752
				Wood & Douglas	791

SPECTRUM ANALYSERS



HP3580A 5Hz-50kHz audio frequency spectrum analyser £750 to £1250
 HP8568B high-specification 1.5GHz spectrum analyser £10000
 MARCONI 2386 100Hz-26.5GHz (in 1Hz steps) £15000
 AVCOM - portable, battery operated, to 1000 MHz £2000
 TEKTRONIX 492 21GHz portable spectrum analyser, with options 2 (digital storage and Rack-mount option) £6000 or £7000 with mixers to 60GHz
 TEK7623A/7L18 (1.8GHz) with tracking generator in TMS03 £1750

MARCONI INSTRUMENTS



2018A synthesized AM/FM signal generator 80kHz-520MHz £1250
 2019A synthesized AM/FM signal gen 80kHz-1040MHz £2000
 2828A/2829 digital simulator/analyser £500
 2955B radio communication test sets - LATEST 'B' MODEL £4000
 6460/6421 power meter & sensor 10MHz-12.4GHz £350
 6514 waveguide detector for use with 6500-scalar analyser 26-40GHz £350
 6960 microwave power meter with 6910 power sensor 10MHz-20GHz £900
 TF2910 TV interval timer £250

ralfe electronics exclusively professional T&M ©
 • 36 Eastcote Lane • South Harrow • Middx HA2 8DB • England •
 TEL (+44) 0181-422 3593 • FAX (+44) 0181-423 4009

EST
41
YRS



DISTRIBUZIONE E ASSISTENZA, ITALY: TLC RADIO, ROMA (06) 871 90254

TEST EQUIPMENT

BRUEL & KJAER 2023 single channel audio spectrum analyser £2500
 BRUEL & KJAER 2511 vibration meter (field set with 1621 filter) £1500
 BRUEL & KJAER 2307 level recorder £1000
 BRUEL & KJAER 2317 portable level recorder £1500
 BRUEL & KJAER 2308 analogue X-Y pen recorder £750
 CHASE LFR1000 interference measuring receiver 9kHz-150kHz £1000
 DATRON 1061 & 1061A - various, digital multimeter & 1065 - call from £500
 DATRON 1065 digital multimeter all ranges plus IEEE £500
 FARNELL PSG2400A signal generator 100kHz-2.4GHz £3500



CERT.: 95/013
**ISO9002 ACCREDITED STOCKIST
 MEASUREMENT & TEST EQUIPMENT**

PHILIPS PM5167 1mHz-10MHz function generator £275
 RACAL 9008 automatic modulation meter £350
 RACAL-DANA 9300 milli-voltmeter £400
 RACAL-DANA 9301A true RMS RF milli-voltmeter £350
 TEKTRONIX P6201 FET PROBE £350
 WANDEL & GOLTERMANN WM30 level tracer £500
 WANDEL & GOLTERMANN PJM-4S Jitter meter for SONET & SDH £5500
 WAVETEK 23 synthesized function generator 0.01Hz-12MHz £1250
 WAVETEK 1067 opt 522 1-500MHz sweep generator £500
 WAYNE KERR 3220 20A bias unit (for 3245 inductance analyser) £1250
 TEKTRONIX 1502B/03/04 short-range metal-cable tdr tester £3500

HEWLETT PACKARD



1640B serial data generator £500
 3561A dynamics signal analyser (opt 01) £5500
 3764A digital transmission analyser £1500
 3335A synthesizer/level generator £2000
 3400A voltmeter, analogue 10Hz-10MHz £250
 3235A switch/test unit £1000
 3324A synthesized function generator £2000
 3325A synthesizer/function generator, 21MHz £1750
 3580A audio frequency spectrum analyser £750 to £1250
 3581C selective voltmeter £1250
 3779D primary multiplex analyser £5000
 4140B pA/meter, DC voltage source £4000
 4339A high resistance meter c/w lead set 16117B £2000
 4275A multi-frequency lcr meter £3500
 435B microwave power meter, analogue £400
 5386A 3GHz frequency counter £1500
 54100A 1GHz digitizing oscilloscope £2250
 8007B pulse generator 100MHz £950
 8018A serial data generator £1000
 8082A pulse generator 250MHz £2000
 8111A pulse generator 20MHz £1250
 816A slotted line 1.8-18GHz with 809C & 447B probe £500
 8444A tracking generator with option 059 £1000
 8656B synthesized signal generator to 990MHz £3000
 87510A gain-phase analyser 100kHz-300MHz £6500
 8901A modulation analyser with option 02/010 £3500
 J2215A FDDI portable multimode test set £1500
 J2219A 486-based, colour option main-frame £1000
 J2219A/J2171A 486-based colour screen option network advisor £3000

**SEND FOR LATEST STOCK LIST. WE FAX LISTS
 AND SHIP WORLDWIDE. ALL FULLY
 LAB-TESTED AND NO-QUIBBLE GUARANTEED**

CIRCLE NO. 144 ON REPLY CARD

ELECTRONIC UPDATE

Contact Malcolm Wells on
 0181-652 3620

A regular advertising feature enabling
 readers to obtain more information
 on companies' products or services.

New Flight Electronics International Catalogue Set

You now have access to the world's latest:

- ★ Electronics Training Equipment
- ★ Microprocessor Training Equipment
- ★ Test and Measurement Equipment
- ★ PC Cards

via "Flight's" latest catalogue set.

We are specialists in the provision of innovative top quality electronics trainers, breadboards, test and measurement, PC cards and microprocessor evaluation equipment.

Our extensive range covers every need, call today for your free catalogue set.

CIRCLE NO. 145 ON REPLY CARD

FREE DEMO DISK

The LabWindows/CVI Demo Disk is a free evaluation copy of LabWindows/CVI. You can follow instructions to build Windows applications using GPIB, VXI, Serial, and plug-in DAQ instrumentation. The guide illustrates code-generation techniques, GUI development tools, event-driven programming techniques, instrument drivers, debugging and editing tools.

NATIONAL INSTRUMENTS
 For your Free Demo Disk call,
 01635 523545

CIRCLE NO. 146 ON REPLY CARD

NEW Feedback T&M Catalogue

The latest edition of the Feedback Test & Measurement catalogue is now available. Over 60 pages packed with more than 800 products divided into over 20 sections. The catalogue is indexed for both product and manufacturer and is fully illustrated. Whether you are looking for an individual product, a complete workstation, or a solution to a particular Test & Measurement need the NEW Feedback catalogue will solve your problems, send for a copy NOW!

CIRCLE NO. 147 ON REPLY CARD

NEW JENSEN TOOLS CATALOGUE

Colourful new Catalogue, hot off the press from Jensen Tools, presents unique new tool kits for service/support of communications equipment. Also latest test equipment from many major manufacturers. Includes hard-to-find tools, PC/LAN diagnostics, bench accessories, static control, technical manuals and more.

Ring 0800 833246 or
 Fax 01604 785573 for a free copy.

Jensen Tools, 10-12 Ravens Way,
 Northampton NN3 9UD

CIRCLE NO. 148 ON REPLY CARD

Small

PROBLEMS?

BIG

Awkward

No Time


SOLUTION!

PIC based TOOLS to help you realise your project:
from single applications to full scale production


BASIC STAMPS®

PIC based BASIC Stamps are perfect for one-off and low volume applications.

Their easy to learn but powerful BASIC syntax (with familiar instructions such as GOTO, FOR ... NEXT, and IF ... THEN as well as instructions for serial I/O, pulse measurement, button debounce, DTMF, X-10 etc) will get your application up and running in hours. Once programmed, the Stamp runs independently of your PC and programs are stored in non-volatile EEPROM so they can be changed at will. Detailed manuals cover many commonly needed routines and the Stamp is well supported by a growing list of custom application kits to cut development time even further. Available in two formats:

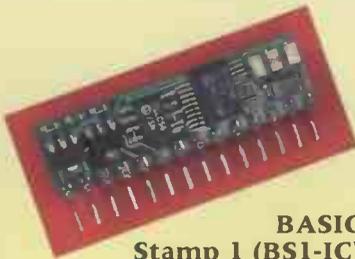

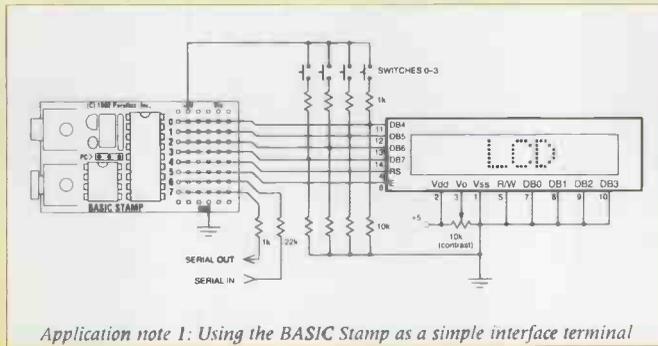BASIC Stamp 1 (BS1-IC)
8 I/O Lines
up to 80 program lines
Comms to 2400 baud
35x10mm size
£29 single price



Application note 1: Using the BASIC Stamp as a simple interface terminal

Typical Application



BASIC Stamp 2 (BS2-IC)
16 I/O Lines
up to 500 program lines
Comms to 50 kbaud
24pin DIP package
£49 single price

BASIC Stamp Development Kits including PC software, manuals, 24+ application notes, downloader cables, Stamp (BS1-IC or BS2-IC) and corresponding Project Board - £99 / £119

PIC16Cxx DEVELOPMENT TOOLS

For medium to large volumes and high speed requirements, the popular range of PICs is hard to beat. We offer an extensive range of programmers, emulators and associated hardware to support the following PICs: 52 54 55 56 57 58 620 621 622 61 62 63 64 65 71 72 73 74 84

PIC16Cxx Programmer



Also stocked
* ZIF sockets
* SOIC/SSOP/PLCC adapters
* Prototyping boards
* Compilers/Simulator

OVER 5000 SOLD

In Circuit Emulators

- * True hardware emulation of program memory, registers and I/O
- * Unlimited breakpoints.
- * Single stepping
- * Software-programmable oscillator
- * Windows Environment
- * Runs from 32Khz to 10Mhz ('xx) and 20Mhz ('5x)
- * Source level debugging for PASM(X), MPASM and MPC
- * Optional trace facility



Milford Instruments
Milford House, 120 High Street,
SOUTH MILFORD LS25 5AQ
01977 683665 Fax 01977 681465

Please call or fax to receive our catalogue and price list. All prices exclude VAT and £3 shipping.

BASIC Stamp & the Parallax logo are registered trademarks of Parallax, Inc.

PARALLAX


3805 Atherton Road, #102
Rocklin, CA 95765 USA
916-624-8333, Fax 916-624-8303
<http://www.parallaxinc.com>

C3

CIRCLE NO. 102 ON REPLY CARD

THE WORLD'S MOST POWERFUL, PORTABLE PROGRAMMERS

£495 + VAT

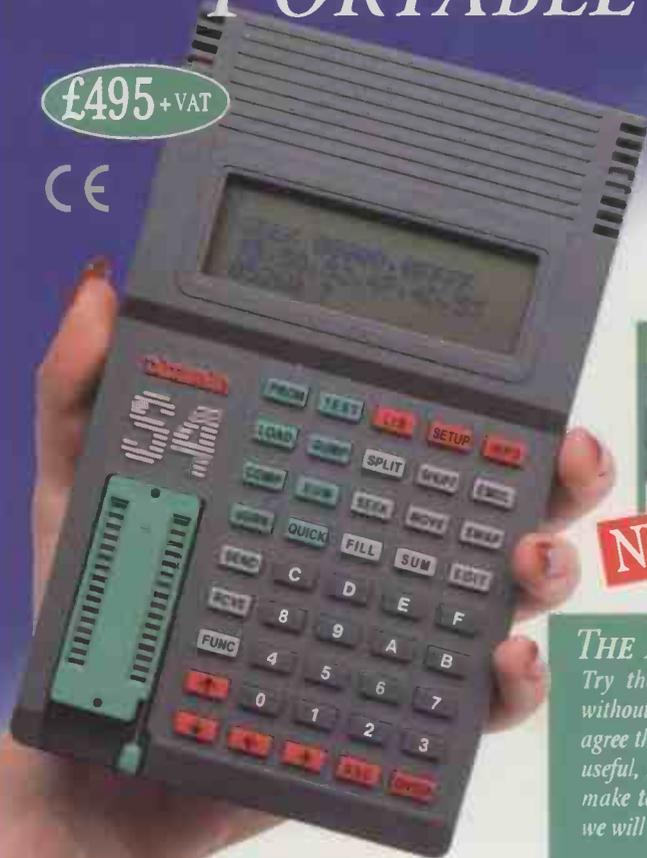

S4 GAL module

Programs a wide range of 20 and 24 pin logic devices from the major GAL vendors. Supports JEDEC files from all popular logic compilers.

£195 + VAT



NEW

THE DATAMAN CHALLENGE

Try the Dataman S4 or Dataman-48 without obligation for 30 days. If you do not agree that these are the most effective, most useful, most versatile additions you can make to your programming toolbox, we will refund your money in full.

The current device library contains over 1800 of the most popular logic and memory devices including GALs, PALs, CEPALs, RALs, 8 and 16-bit EPROMs, EEPROMs, PEROMs, FLASH, BOOT-BLOCK, BIPOlar, MACH, FPGAs, PICs and many other Microcontrollers. We even include a 44-pin universal PLCC adaptor.

If you need to program different packaging styles, we stock adaptors for SOP, TSOP, QFP and SDIP. The Dataman-48 is also capable of emulation when used with memory emulation pods.

Order your Dataman programming solution today via our credit card hotline and receive it tomorrow. For more detailed information on these and other market leading programming products, call now and request your free copy of our new colour brochure.

Dataman S4

Compare the Dataman S4 with any other programmer and you'll see why it's the world's undisputed number one.

S4 is capable of programming 8 and 16-bit EPROMs, EEPROMs, PEROMs, 5 and 12V FLASH, Boot-Block FLASH, PICs, 8751 Microcontrollers and more. S4 also emulates ROM and RAM as standard!


S4 is the only truly hand held programmer that ships complete with all emulation leads, organiser-style manual, AC charger, spare library ROM, both DOS and Windows terminal software, and arrives fully charged and ready to go! Who else offers you all this plus a three year guarantee?

Customer support is second to none. The very latest programming library is always available free on the Internet, and on our dedicated bulletin boards. Customers NEVER pay for upgrades or technical support.

Dataman-48

Our new Dataman-48 programmer adds PinSmart® technology to provide true no-adaptor programming right up to 48-pin DIL devices. Dataman-48 connects straight to your PC's parallel port and works great with laptops. Coming complete with an integral world standard PSU, you can take this one-stop programming solution anywhere!

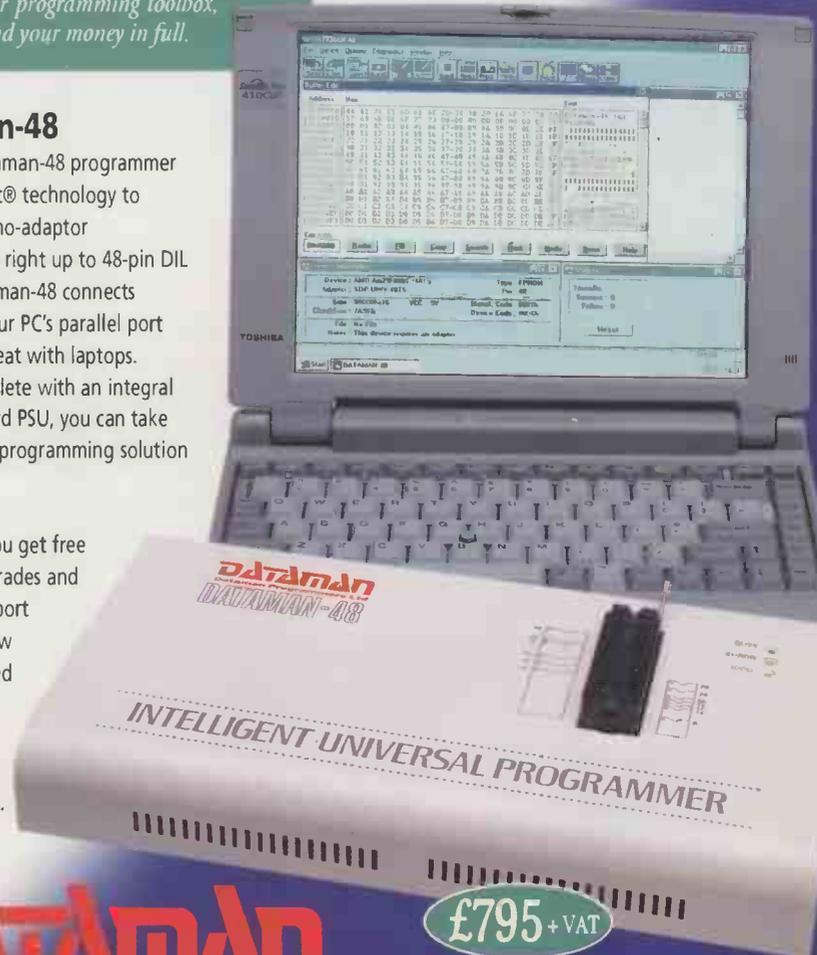As with S4, you get free software upgrades and technical support for life, so now you don't need to keep paying just to keep programming.



£795 + VAT

hotline
01300 320719



Orders received by 4pm will normally be despatched same day.

Order today, get it tomorrow!

DATAMAN

Dataman Programmers Ltd, Station Road, Maiden Newton, Dorset DT2 0AE. UK
Telephone +44/0 1300 320719 Fax +44/0 1300 321012 BBS +44/0 1300 321095 (24hr)

Modem V.34/V.FC/V.32bis Home page: <http://www.dataman.com>

FTP: <ftp://ftp.dataman.com> Email: sales@dataman.com

CIRCLE NO. 104 ON REPLY CARD