

Exclusive - 70,000+ products on CD ROM for £2.50



ELECTRONICS WORLD

Austria Asch. 65.00
Denmark DKr. 66.00
Germany DM 15.00
Greece Dra. 1000.00
Holland Dfl. 11.50
Italy L. 8500.00
Malta Lm. 1.45
IR £3.30
Singapore S\$12.60
Spain Pts. 800
USA \$5.50

INCORPORATING WIRELESS WORLD

December 1996 £2.25

A REED BUSINESS PUBLICATION
SOR DISTRIBUTION

GET WIRED

Two new tests for
speaker cables

Ultrasound
defect detector


Magnetic
sensor circuits

Using the
PC's timer

Easy rectifier
design steps

RF oscillators
from AC gates

Thoughts on
demodulation

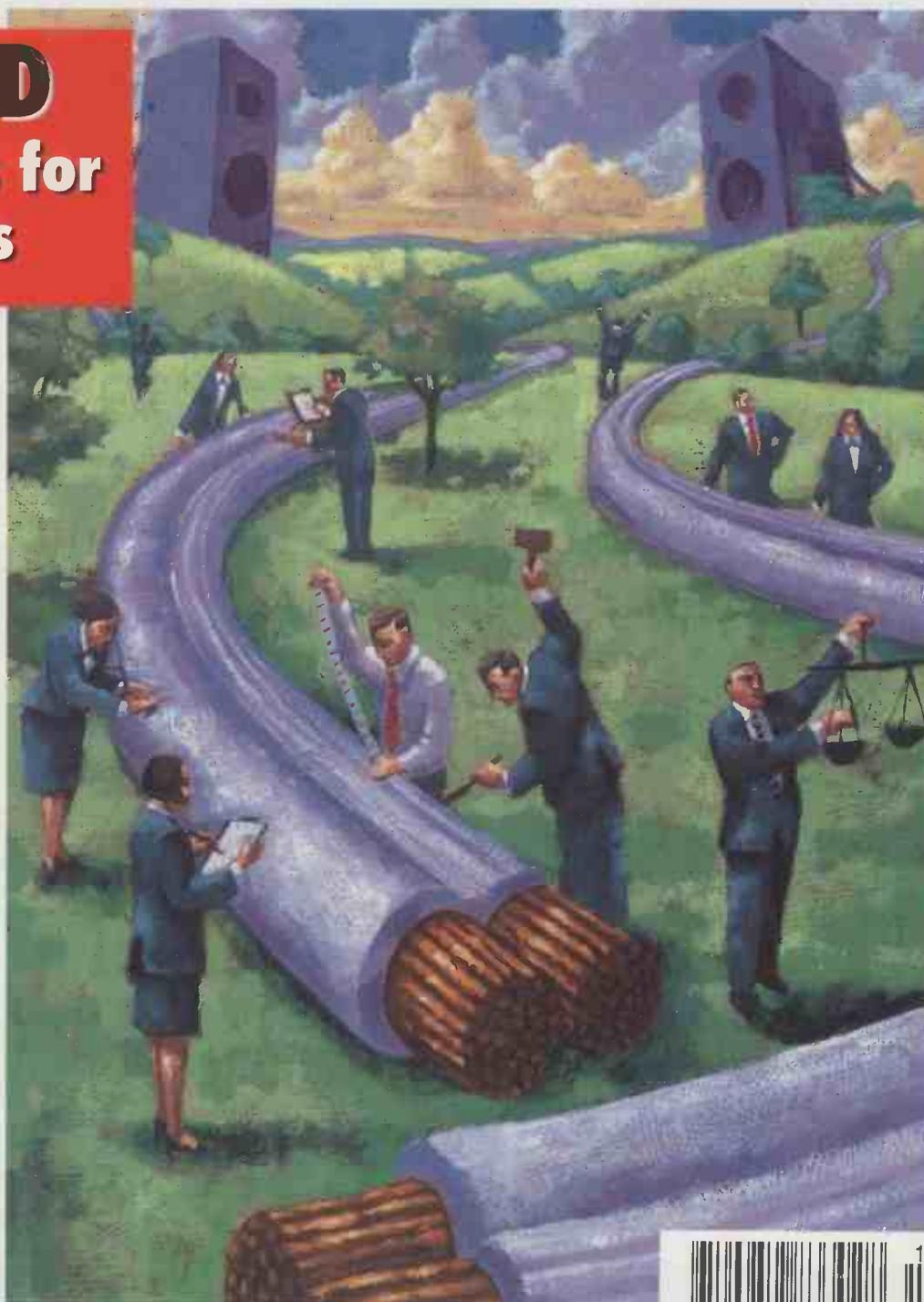

Dual PCB CAD reviews: Quickroute and Propak



Small

Awkward

PROBLEMS?

BIG


No Time

SOLUTION!


PIC based TOOLS to help you realise your project:
from single applications to full scale production

BASIC STAMPS®

PIC based BASIC Stamps are perfect for one-off and low volume applications. Their easy to learn but powerful BASIC syntax (with familiar instructions such as GOTO, FOR ... NEXT, and IF ...THEN as well as instructions for serial I/O, pulse measurement, button debounce, DTMF, X-10 etc) will get your application up and running in hours. Once programmed, the Stamp runs independently of your PC and programs are stored in non-volatile EEPROM so they can be changed at will. Detailed manuals cover many commonly needed routines and the Stamp is well supported by a growing list of custom application kits to cut development time even further. Available in two formats:

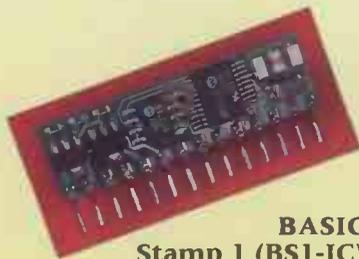


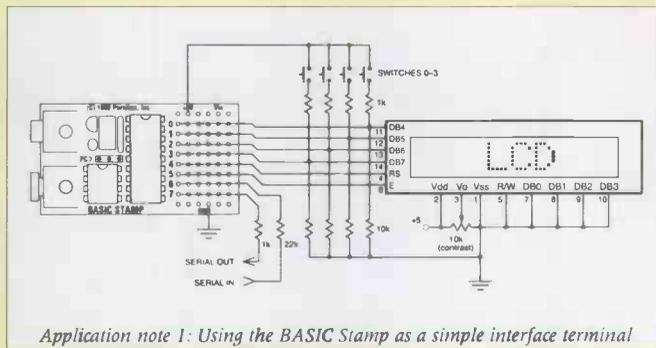BASIC Stamp 1 (BS1-IC)
8 I/O Lines
up to 80 program lines
Comms to 2400 baud
35x10mm size
£29 single price



Application note 1: Using the BASIC Stamp as a simple interface terminal

Typical Application

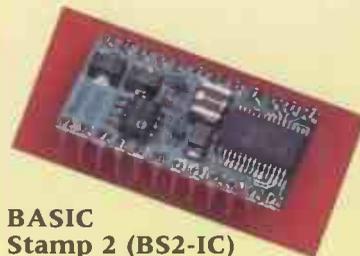

BASIC Stamp 2 (BS2-IC)
16 I/O Lines
up to 500 program lines
Comms to 50 kbaud
24pin DIP package
£49 single price

BASIC Stamp Development Kits including PC software, manuals, 24+application notes, downloader cables, Stamp (BS1-IC or BS2-IC) and corresponding Project Board - £99 / £119

PIC16Cxx DEVELOPMENT TOOLS

For medium to large volumes and high speed requirements, the popular range of PICs is hard to beat. We offer an extensive range of programmers, emulators and associated hardware to support the following PICs: 52 54 55 56 57 58 620 621 622 61 62 63 64 65 71 72 73 74 84

PIC16Cxx Programmer



Also stocked
* ZIF sockets
* SOIC/SSOP/PLCC adapters
* Prototyping boards
* Compilers/Simulator

OVER 5000 SOLD

In Circuit Emulators

- * True hardware emulation of program memory, registers and I/O
- * Unlimited breakpoints.
- * Single stepping
- * Software-programmable oscillator
- * Windows Environment
- * Runs from 32Khz to 10Mhz ('xx) and 20Mhz ('5x)
- * Source level debugging for PASM(X), MPASM and MPC
- * Optional trace facility



Milford Instruments

Milford House, 120 High Street,
SOUTH MILFORD LS25 5AQ
01977 683665 Fax 01977 681465

Please call or fax to receive our catalogue and price list. All prices exclude VAT and £3 shipping.

BASIC Stamp & the Parallax logo are registered trademarks of Parallax, Inc.


PARALLAX®

3805 Atherton Road, #102
Rocklin, CA 95765 USA
916-624-8333, Fax 916-624-8303
<http://www.parallaxinc.com>

Contents

918 THE ROUTE TO PCB CAD

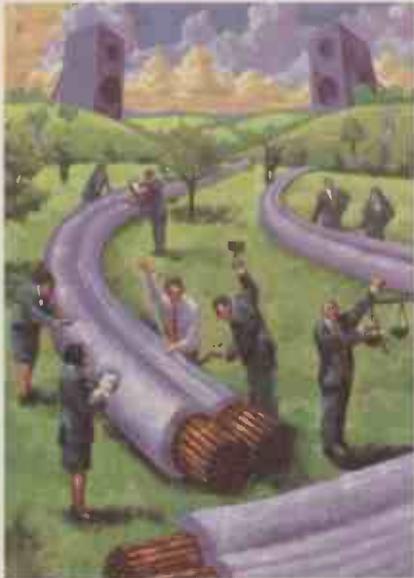Rod Cooper investigates Quickroute and Propak in this fourth article examining low-cost pcb cad packages.



Cover - Jameel Akib

925 SPEAKER CABLES

Cyril Bateman has found a new loudspeaker cable measurement technique that could be just what the subjectivists are looking for.

930 SPEAKER CABLES PULSE TESTED

Eric Foster's measurement technique shows clear cable performance differences, but at frequencies too high to hear.

937 CABLE SCIENCE?

Signals passing through a conductor are affected by a complex combination of field and semiconductor effects, says Geoff Williams.

941 HANDS -ON INTERNET

This month, net explorer Cyril Bateman has found an electronics manufacturers directory and yet more useful design software.

947 EVENT TIMING VIA THE PC

Alan Bradley explains how to program the timer chip in the pc for precise event timing.

952 FINDING FAULTS WITH SOUND

Component damage caused by the thermal stresses occurring during pcb assembly are notoriously difficult to detect. Steve Martell describes a new detection method.

956 WHEN IS A GATE NOT A GATE?

74AC gates make handy and low cost rf oscillators - Ian Forster shows a variety.

959 NEW THOUGHTS ON DEMODULATION

Edward Forster examines the amplitude-locked loop and its use as a demodulator.

969 APPLYING MAGNETO RESISTANCE

Applications for magneto-resistive sensors range from detecting Earth's magnetic field to protecting igbts.

980 DESIGNING RELIABLE RECTIFIERS

Half-wave rectifiers are simple, but they still need to be designed properly.

Regulars

907 COMMENT

Market forces rule?

908 NEWS

Video camera chip under \$20, Mixed-signal fpga, More efficient igbts.

912 RESEARCH NOTES

Computers detect facial expressions, Higher chip performance from flat silicon, Glass curtains, Water hammer.

962 CIRCUIT IDEAS

200MHz spectrum analyser, Video switch for 1km links, Linear scr trigger, PC-based battery meter.

975 NEW PRODUCTS

Pick of the month - classified for convenience.

986 LETTERS

Motional feedback headphones, anti-gravity, Marconi, Power amp design.




Special offer extended

This 10Hz to 1MHz audio signal generator is available for a second month to *Electronics World* readers at 20% discount - page 935.

Win a CD-ROM writing and development package - see page 946.



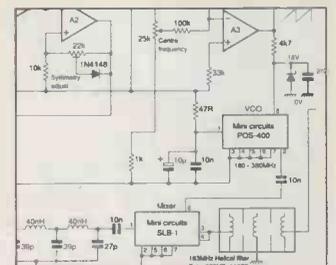Exclusive offer
Information on over 70,000 products - available exclusively to *Electronics World* readers for just £2.50 - page 946.



Want an easy to implement, low-cost 200MHz spectrum analyser that performs to -75dB? Turn to page 962.


**JANUARY ISSUE
ON SALE 5 DECEMBER**

Integrated Schematic & PCB Design System

"extremely good value for money for such a comprehensive package"



Practical Wireless July 96

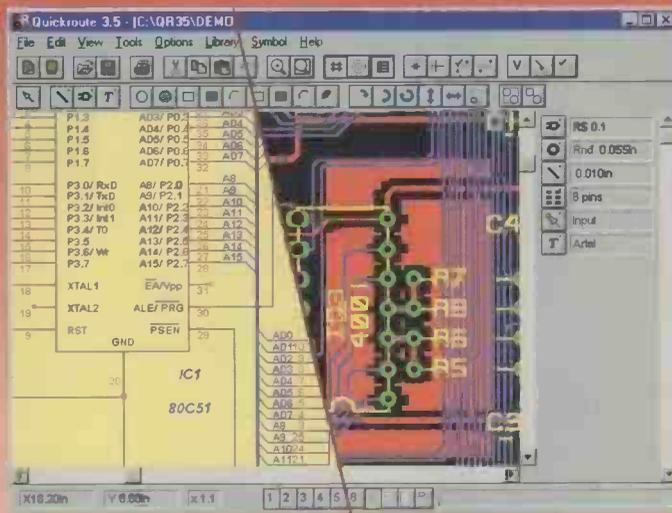

| | Personal | Designer | PRO | PRO+ |
|--------------------------------|----------|----------|-----|------|
| PCB & Schematic Design | * | * | * | * |
| Schematic Capture | * | * | * | * |
| Design Rule Checking | * | * | * | * |
| Connectivity Checking | | 1 | 1 | 2 |
| RouteASSIST (assisted routing) | * | * | * | * |
| Auto router | | * | * | * |
| Export WMF & Tongo | | * | * | * |
| Export Gerber/NC-Drill | | * | * | * |
| Extended Libraries | | T | * | * |
| Tango + Gerber Import | | | * | * |
| Update PCB from schematic | | * | * | * |
| DXF & SPICE Export | | | * | * |
| Copper Fill | | | * | * |

1 Simple pass/fail 2 Advanced Check

NEW Library Packs Available!

Quickroute 3.5 is a powerful, affordable and easy to use integrated schematic & PCB design system for windows. With its multiple button bars, 'tool tips', and 'parts bin' Quickroute helps you to get working quickly and efficiently

Quickroute is available in 4 different versions (see Table) all of which offer great value for money. Quickroute is available with multi-sheet schematic capture, 1-8 layer auto-routing, copper fill, engineering change, and a range of popular file import/export features allowing connection to simulators and other software packages (details on request). Prices are Personal (£68), Designer (£149), PRO (£249) and PRO+ (£399). Please add P&P and V.A.T to total (see below*).




£68

SMART
ROUTE

NEW

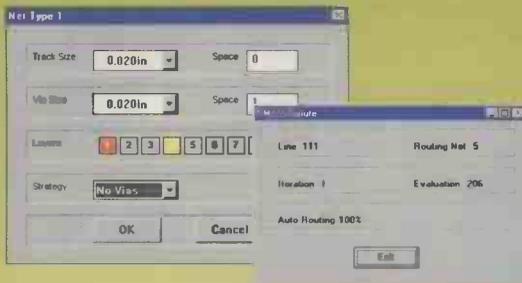THE 32 BIT AUTO-ROUTER WITH FLEXIBILITY & POWER



SMARTRoute 1.0 is a new 32 bit auto-router that offers amazing flexibility & power at an affordable price! Compatible with Windows 3.1/95/NT, SMARTRoute gives you total control over routing strategies including layers used, track & via sizes, design rules, etc.

SMARTRoute is completely compatible with Quickroute 3.5 and offers improved completion rates compared with Quickroute's built in auto-router (ask for details) SMARTRoute is available for £149 plus P&P and V.A.T. Special bundle pricing for Quickroute and SMARTRoute when purchased together.




Just £149

906


M EXPRESS

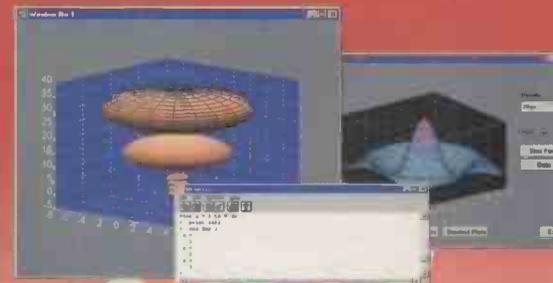VISUALISATION, DATA ANALYSIS & APPLICATION DEVELOPMENT



MExpress is a powerful tool that can be used interactively to load, analyse and display data - or by using its powerful BASIC-like scripting language - you can create technical applications with buttons, menu 2D & 3D graphics, and powerful numerical methods (ask for details).

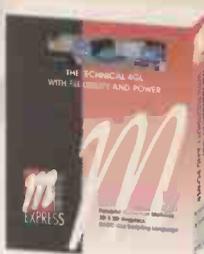MExpress is available in Standard (£99) and Developers Editions (£299). Prices exclude P&P and V.A.T (see below*). The Developers Edition includes tools for turning MExpress script files into C++ code. This can then be compiled by an MExpress compatible C++ compiler into a stand alone executable!



£99

EDITOR

Martin Eccles
0181 652 3128

CONSULTANTS

Jonathan Campbell
Philip Darrington
Frank Ogden

DESIGN

Alan Kerr

EDITORIAL

ADMINISTRATION

Jackie Lowe
0181-652 3614

E-MAIL ORDERS

jackie.lowe@rbp.co.uk

ADVERTISEMENT MANAGER

Richard Napier
0181-652 3620

DISPLAY SALES EXECUTIVE

Malcolm Wells
0181-652 3620

ADVERTISING PRODUCTION

0181-652 3620

PUBLISHER

Mick Elliott

EDITORIAL FAX

0181-652 8956

CLASSIFIED FAX

0181-652 8956

SUBSCRIPTION HOTLINE

01622 778000

SUBSCRIPTION QUERIES

01444 445566
FAX 01444 445447

ISSN 0959-8332

NEWSAGENT ENQUIRIES

Contact MarketForce
(UK) Ltd.
Telephone:
0171-261 5555
Fax: 0171-261 6106



Market forces rule?

Market forces are supreme. They always ensure the best price and the widest choice of goods and services. Or do they?

Look at the state of the consumer electronics industry. Desperately low margins and retail bankruptcies. High customer expectations of the products themselves, but an equal expectancy of low prices. Unfortunately, you get what you pay for, so generally the quality is questionable and customer satisfaction is low. Given this climate, what encourages manufacturers to invest in new ideas? Isn't it all too risky?

No, there are still great prizes to be won. Many homes do not have computers, mobile phones or satellite television. There is no need for any 'quantum-leap' products, like the change from mono to stereo radio or the move from black and white to colour television. Just bigger, faster and more features will do. The direction the market is taking seems to be quite predictable.

For example, the market driver in personal computers is speed and size of storage, but it is almost self sustaining in that software developers guzzle up extra features without much return in performance. Why does Windows 95 need over 50 megabytes of hard disk space? So pcs have to get bigger.

There are some interesting developments and huge investment in mobile communication with the advent of GSM and, shortly, hand portable satellite telephones linked to Iridium, Inmarsat or a Bill Gates variant. Maybe wrist-watch telephones are just around the corner; the pagers are already here. But no videophone yet. With its slow changing images, the worthy Amstrad attempt a couple of years ago wasn't quite what the market wanted.

The world of radio and television is less fast moving. Digital broadcasting is almost here together with wide screen tv and surround sound. The technology may be brilliant but will there be anything worth watching with the mushrooming number of mediocre tv channels?

Occasionally life is not always so predictable. Look at the Internet. No one designed it, and yet it is here. What use is it I hear you say? A massive library, a low cost communication medium, a



place for pastimes? Its applications will develop in time – did not the mobile phone develop from amateur radio?

Generally speaking market forces have delivered progress, using an incremental approach with minimal risk. However, the stage is set for another quantum leap, but one which market forces cannot deliver. It's not new but it needs saying again.

It is the provision of a terrestrial high bandwidth communications infrastructure – a proper fibre connection to businesses and homes – provided that they want it. It has been talked about for a long time but the time is right to do it.

BT has offered to install the infrastructure but is prevented by its license. Cost-conscious cable-tv companies are installing coaxial cable with separate lines for telephones, but no fibre optics. Surely, if you are going to dig up the road and disrupt the traffic why not do the job properly? The trouble is that the provision of this infrastructure benefits lots of different applications, but one application on its own cannot afford to do it. Hence there is a vacuum.

What can this connection give us? A real videophone service – hopefully compatible with the rest of the world – and fully developed on-line services including banking and reference services. Or interactive learning which could boost further education perhaps, and video-on-demand, which could turn broadcasting upside down. It could also offer telecommuting, giving a flexibility to working that companies will not countenance at the moment. And interactive television.

I think the latter is the most revolutionary application of all. It goes

***"Let us harness these ideas
....look forward and don't
be afraid of the future."***

further than tv talent shows or phone-ins. Imagine watching a parliamentary debate on tv – presented with proper visual aids – and then having a chance to vote. To have your say on devolution, European integration, a single currency – or even the proposed local bypass scheme.

Of course there would be the same arguments against it as referendums; these are that the questions can be loaded, computer security, people voting against an unpopular government rather than addressing the question, people unqualified to vote, or just plain old apathy. But isn't it worth trying?

We have to cable up. The benefits are enormous and the opportunities for industry are massive. But then the investment will be massive and it won't happen unless the Government takes the lead and defines the playing field to enable and encourage things to happen, and perhaps throw in a little vision. We must think of it in terms of supplying water, electricity and gas to people's houses – is there any argument about this?

The moral of the tale is that we cannot rely on market forces to completely shape the future that we want. We could easily get stuck in a rut. The Government must take an active role.

It should facilitate change, cajole and encourage, and above all think long term. But first, let's all get connected. ■

Peter Marlow

Electronics World is published monthly. By post, current issue £2.35, back issues (if available) £2.50. Orders, payments and general correspondence to **L333, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.** Tlx: 892984 REED BP G. Cheques should be made payable to Reed Business Publishing Group **Newsstrade:** Distributed by Marketforce (UK) Ltd, 247 Tottenham Court Road London W1P 0AU 0171 261-5108.

Subscriptions: Quadrant Subscription Services, Oakfield House Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address. Subscription rates 1 year £30 UK 2 years £48.00 3 years £70.00. Surface mail 1 year £35.00 2 years £56.00 3 years £80.00 Air mail Europe/Eu 1 year £43.00 2 years £68.00 ROW 1 year £52.00 2 years £83.00

Overseas advertising agents: France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel; (212) 679 8888 Fax; (212) 679 9455

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. 2nd class postage paid at Rahway NJ Postmaster. Send address changes to above.

Printed by BPCC Magazines (Carlisle) Ltd, Newtown Trading Estate Carlisle. Cumbria, CA2 7NR

Typeset by Wace Publication Imaging 2-4 Powerscroft Road, Sidcup, Kent DA1 4SD

© Reed Business Publishing Ltd 1996 ISSN 0959 8332

New mixed signal FPGA technology developed in UK

Mixed signal Asic design house, WML, is developing a field programmable system-on-a-chip (Fipsoc) that mixes analogue and digital blocks on the same device.

The analogue sections can be configured to implement filters, amplifiers, drivers and d-to-a/a-to-d converters. The logic section comprises some 10,000 gates configured with look-up tables and registers.


Device programming is controlled by an on-chip 8051 microprocessor. Two different configurations can be stored and swapped with a command to the processor.

The actual programs themselves are held within a separate e²prom – much like a ram-based fpga.

A CAD system has been developed by WML to design circuits and program the devices. The design flow includes mixed signal design specification, simulation, place and route, programming and emulation.

The company claims the Fipsoc can be used for analogue systems in the same way that gpgas can be used in the digital world. Designs could be prototyped on a Fipsoc and migrated to a mixed-signal Asic for volume production.

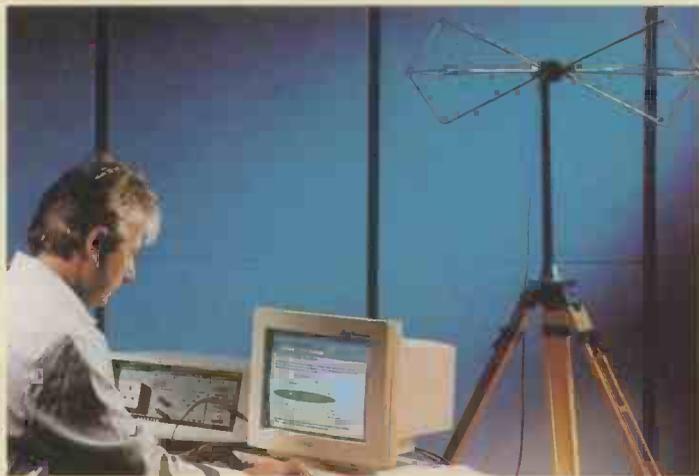First silicon of the Fipsoc is expected next month.



Rooms for rent... A full range of EMC test equipment including screened rooms is available on lease purchase terms from Seaward Electronic. Both emissions and immunity testing kits can be hired for around £100 and £150 respectively. Equipment includes spectrum analysers, a harmonics meter, a mains interference simulator and a surge generator.

Imaging sensor for under \$20


A CMOS imaging sensor, priced at under \$20 in large quantities, has been introduced by US company Marshall Electronics.

Specifications of the monochrome camera-on-a-chip are near-identical to that of Vision's CMOS sensor. However, Roy Warrender, commercial director of the Edinburgh-based company, said: "This equates to an early generation of our product."

Leonard Rogers, vice-president of Marshall, responded: "Unlike Vision, we have something working, in production and being sold into products."

Marshall's camera, developed by Omnivision Technologies, features a 300 x 240 pixel array and EIA composite video output. The chip runs from a 9V battery, consuming less than 100mW.

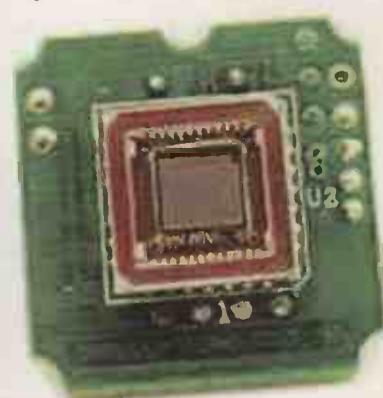A special feature allows for an unlimited number of cameras to be connected in series or parallel on a single coax cable. The multiple cameras can be mounted on buildings, for example, removing the need for expensive motors and lenses.



Design awareness initiative is extended

DTI gives Microelectronics in Business design centres 18 months to become self-financing operations. The government has extended its fpga and Asic awareness campaign in the hope that its university design centres can become self-financing within the next year and a half.

The original three-year MIB programme – which remains the government's most direct support for the microelectronics design sector – was due to end this month when funding would have run out for the project's nine design and support centres.

The DTI will now spend £800,000 to keep the design centres running for a further 18 months, after which the DTI expects many of them to be self-financing design and technology transfer centres.

Last year, existing commercial Asic design houses criticised the MIB programme for using DTI money to set up university design houses rather than supporting the existing industry. At the time the DTI denied this.

Now it seems the intention is to enable the university-based support centres to become self-financing businesses. Professor Sa'ad Medhat, head of the school of electronics at Bournemouth University, where he runs an MIB support centre, believes it is likely that some MIB centres will be self-financing technology transfer and design businesses. "Eighteen months was the period we chose and I think it is possible, if we ramp up our technology transfer node activities," he said.

Richard Wilson, Electronics weekly

LOW COST DEVELOPMENT SYSTEM

ECAL comprises a versatile relocatable assembler with integral editor which runs about ten times faster than typical assemblers. Support includes 4, 8, 16 & 32 bit processor families including 75X, 6502, 6809, 68HC05/11, 8031/51, H8-300, 78K, PICs, ST6 & Z80/180, 68000, 80C196, H8-500 & Z280.

ECAL is either available for a single processor family or all families.

Single processor version £295
Multiprocessor version.... £395

**Overseas
distributors
required**

OEMA Ltd.,
7 & 7A Brook Lane,
Warsash,
Southampton SO31 9FH
Tel: 01489 571300
Fax: 01489 885853



Free demo disc!

The PC based ECAL hardware emulator is fully integrated with the assembler. Connection is made to the target through the eprom socket so a **single** pod can support **all** processors. Facilities include windows for the inspection or change of registers or memory. You can even watch your program executing at source level!

Download time is about two seconds!

Pods can be daisy-chained for 16/32 bit systems.

Applications include software development, hardware debug, test and, finally, teaching about micro-controllers in education.

ECAL emulator £475

Quantity discounts of up to 50% make ECAL software ideal for education.

CIRCLE NO. 107 ON REPLY CARD

OSCILLOSCOPE LIVE CHOP Page -0.25

MEASURE MODE
CH 1
CH 2
CHOP
ADD
COMPARE
X-Y PLOT

1.06
0.40
-0.26
-0.93
-1.60
-2.26
-2.93
-3.60
-4.26

0.30 0.30 0.30

16.5
13.8
11.2
8.53
5.8

0.33
-2.13
-4.80

FREZE ONE SHOT MODE CH1 SET CH2 SET ZOOM
TIME DIV TIME-MAG. TIME-OUT HYSTERESIS SLOPE + TRIGSOURCE
PRINT COMMENT SETTINGS

FREE

INPUT 20 volt max.
100 kHz sampling
μScope
to PC printerport

You get a free **μScope** when you buy a TP508 or a HS508 until september 1st 1996

resolution 8 bits
sampling speed 100 kSamples/sec
input range 2.5V, 5V, 10V and 20V
connects to PC parallel printer port

SPECTRUM ANALYZER CH 1 5.967 U

WINDOW
RECTANGLE
HANNING
HANNING
BLACKMAN
BARTLETT

3.70
3.20
2.70
2.20
1.70
1.20
0.70
0.20
-0.30

0 (Hz)

MEASURE HOLD-FFT MODE
FREQUENCY FREQ-MAG. HYP
PRINT COMMENT SETTINGS

Software for the PC-based instruments

contains an Oscilloscope, a Spectrum analyzer, a Voltmeter, and a Transient recorder. All instruments are controlled in the same intuitive way and provide for saving and recalling waveforms and settings, cursor measurements, hardcopy on matrix/laser printer and online help. Minimum requirements: a 80286-based PC with 2MByte and running MS-DOS 3.3 or higher.

Fax for a free demo disk and catalog of all our products

Easy installation: just plug in and measure

TiePieSCOPE HS508

- ▶ interface PC parallel printer port
- ▶ sampling speed 50 Msamples/sec
- ▶ resolution 8 bits
- ▶ input range 50 mV/div - 20V/div
- ▶ record length 32KByte/channel
- ▶ price £597.00, incl. software, user manual and 2 probes (1:1/1:10 switchable)

TP508

- ▶ Interface PC-XT/AT ISA slot
- ▶ sampling speed 50 Msamples/sec
- ▶ resolution 8 bits
- ▶ input range 5 mV/div - 20 V/div
- ▶ record length 32 KByte/channel
- ▶ price £ 630.00 incl. software, user manual and 2 probes (1:1/1:10 switchable)

Prices are excluding V.A.T.

TiePie engineering (NL)
P.O. Box 290 Koperslagersstraat 37
8600 AG Sneek 8601 WL Sneek
The Netherlands The Netherlands
Tel: +31 515 415 416 Fax: +31 515 418 819



TiePie engineering (UK)
28, Stephenson Road, Industrial Estate,
St. Ives, Cambs, PE17 4WJ,
United Kingdom
Tel : +44 1480 460028 Fax: +44 1480 460340

Video codec based on fractals


Iterated Systems, the Atlanta-based image compression company, has released a video codec based on fractal technology.

Called ClearVideo, the video decoder is available as shareware whereas the encoder is licensable and has already been taken up by Electric Switch, which offers a video compression service, and Pro-Sieben, for use on its Web site.

ClearVideo is claimed to be capable of compressing all classes of content, from talking heads to full action video. Resulting data rates are dependent on the image resolution and the amount of image movement, but rates as low as 28.8kbit/s are reported and QCIF 15frame/s full action video can be squeezed into 120kbit/s.

"Compression is non-real time, whereas decompression can be performed in real time on a 486 PC running Windows 95. WindowsNT and Macintosh versions are also available," said an Iterated spokeswoman.

New Asics carry 12 million gates

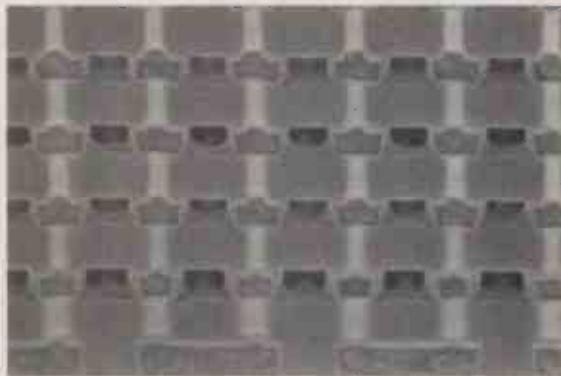

Heavy metal... Cross sectional view of TI's 0.18µm process showing the six layers of metal.

First samples of the new 0.18µm geometry Asic technology from Texas Instruments (TI) will be out in the middle of next year.

"We have test chips now, and we have designs being put through which are of about five million gates complexity," Mohan Maheswaran, TI's Asic manager in Dallas, told EW.

Currently the largest gate count gate arrays on offer in the market are the 3.5 million gate Asics offered by IBM Microelectronics.

"Our technology (called Timeline)

gives us 12 million gate count gate arrays with 70 per cent utilisation and 30m gate count standard cells also with 70 per cent utilisation", said Maheswaran. Metal layers are currently up to five, with the capability to go to six.

"It allows people to start thinking in totally new ways", said Maheswaran, "you can actually implement a number of PC boards on one chip." Current applications are in high end telecommunications uses and in high end computing, says TI.

Gate delays on the Timeline technology are 19ps ('the time it takes light to travel 6mm') and power dissipation is 0.008mW/MHz/gate.

In smaller densities some very high speed/low power circuits can be fabricated. "At 100,000 gates and 200MHz frequency, circuits can be implemented which use 0.01mW/MHz/gate," said Maheswaran.

Cores include DSPs, ARM, ATM and MPEG. Memory cells are SRAM, ROM, flash and DRAM (up to 10Mbit).

Pace looks at cable tv

Pace Micro Technology, the Yorkshire-based volume set-top box manufacturer, is currently in discussions with four UK cable operators for a deal over digital set-top boxes. In its plans to capture the digital cable market, Pace has been in discussion with a number of cable operators worldwide.

"The opportunity for us in cable in the next few years is probably larger than when we started in Direct-to-Home," said Steve Barnes, sales and

marketing director at Pace.

"Today Pace is talking to over 160 different broadcasters and operators. But not all of these will come out in a service and not every one will grant Pace their contract."

Meanwhile, BSkyB is still evaluating the bids for the next generation of digital set-top boxes for a digital satellite service expected to be launched in the autumn of 1997. One of the interested parties is Pace.

Faster fast Fourier

Fast Fourier transforms, FFTs, can now be implemented on programmable logic from Altera as part of the company's *Megafunctions* library of cores.

It is claimed that the execution speed can be increased by a factor of ten to 15 over conventional dsp-based solutions.

The company quotes a 1024 point FFT running in 0.2ms when programmed into an *EPF10K100* - the company's flagship device.

The length and data width of the transform can be set by the designer. Suggested applications include rf communications systems in cable and wireless and spread spectrum modems.

Book-to-bill looks up

Chip demand jumped in September with a book-to-bill ratio of 0.99, its largest jump this year, according to the Semiconductor Industry Association.

"From any perspective, these are the most positive numbers we've seen all year," said Douglas Andrey, analyst at the SIA. "The modest increases in orders for August and September suggest that the 1996 slowdown in growth has bottomed out."

The book-to-bill ratio is still far below its most recent peak of 1.16 in September of 1995 but it is a welcome sign of better times ahead for numerous chip companies suffering from a downturn in the market largely because of over production.

IR advances igt efficiency

International Rectifier has introduced a new range of igtbs, called *Gen 4*, that are 20 to 40 per cent more efficient than their predecessors.

Tim Munday, a field application engineer for IR, said: "The gains in efficiency come from a combination of lower saturation voltage and reduced switching losses. Much of the advance has come because we are using our new fab which has reduced the manufacturing tolerances."

Insulated-gate bipolar transistors are power devices that are used predominantly in motor drives. Current *Gen 4* devices are rated at 600V with 1200V devices to follow soon. ■

Transform your PC

into a digital oscilloscope, spectrum analyser, frequency meter, voltmeter, data logger .. for as little as £49.00

Pico Technology specialises only in the development of PC based data acquisition instrumentation. **Call for your guide on 'Virtual Instrumentation'.**

The ADC-10 supplied with PicoScope gives your computer a single channel of analog input.

ADC-10 £49 with PicoLog £59

Virtual Instrumentation

Pico's PC based oscilloscopes simply plug into the parallel port turning your PC into a fully featured oscilloscope, spectrum analyser and meter. Windows and DOS software supplied.

ADC-100 Dual Channel 12 bit resolution

The ADC-100 offers both a high sampling rate 100kHz and a high resolution. Flexible Input ranges ($\pm 50\text{mV}$ to $\pm 20\text{V}$) make the unit ideal for audio, automotive and education use.

ADC-100 £199 ADC-100 with PicoLog £219

ADC-200 Digital Storage Oscilloscope

- 50 MSPS Dual Channel Digital Storage Scope
- 25 MHz Spectrum Analyser
- Windows or DOS environment
- $\pm 50\text{mV}$ to $\pm 20\text{V}$
- Multimeter
- 20 MSPS also available

ADC 200-20 £359.00

ADC 200-50 £499.00

Both units are supplied with cables, power supply & manuals.



Data Logging

Pico's range of PC based data logging products enable you to easily measure, display and record temperature, pressure and voltage signals.

TC-08 Thermocouple to PC Converter

- Supplied with PicoLog software for advanced temperature processing, min/max detection and alarm.
- 8 Thermocouple inputs
- No power supply required.

TC-08 £199

TC-08 £224 with cal. Cert.

complete with serial cable & adaptor. Thermocouple probes available.



Call for free demo disk and product range catalogue

Post & Packing UK £3.50, Export customers add £9 for carriage & insurance.

Pico Technology Ltd. Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ UK

Tel: + 44 (0)1954 211716 Fax: + 44 (0)1954 211880 E-mail: post@picotech.co.uk Web: http://www.picotech.co.uk/

Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT

CIRCLE NO. 109 ON REPLY CARD

SEETRAX CAE RANGER PCB DESIGN

WITH COOPER & CHYAN AUTOROUTER

| | |
|---------------|-------|
| RANGER3 - DOS | £2500 |
| - Windows\NT | £2900 |

Hierarchical or flat schematic linked to artwork.

Unlimited design size, 1 micron resolution

Any shaped pad, definable outline library

Pin, gate & outline swapping - auto back annotation

Split power planes, switchable on - line DRC

COOPER & CHYAN SPECCTRA

autorouter (SP2)

Inputs: OrCAD, Cadstar,

PCAD, AutoCAD DXF

Outputs: Postscript, Windows bit map

R2 & R3 Outputs: 8/9 & 24 pin printers, HP

Desk & Laser Jet, Cannon Bubble Jet,

HP-GL, Gerber,

NC Drill, AutoCAD DXF

| | |
|---------|------|
| RANGER2 | £150 |
|---------|------|

Upto 8 pages of schematic linked to artwork
Gate & pin swapping - automatic back annotation

Copper flood fill, Power planes, Track necking,

Curved tracks, Clearance checking,

Simultaneous multi-layer auto-router

| | |
|-------------------|------|
| RANGER2 UTILITIES | £250 |
|-------------------|------|

COOPER & CHYAN SPECCTRA auto-router (SP1)

Gerber-in viewer, AutoCAD DXF in & out

| | |
|--|-----|
| UPGRADE YOUR PCB PACKAGE TO RANGER2 | £60 |
|--|-----|

TRADE IN YOUR EXISTING PACKAGE TODAY

Seetrax CAE, Hinton Daubnay House, Broadway Lane, Lovedean, Hants, PO8 0SG

Call 01705 591037 or Fax 01705 599036 + VAT & P.P

CIRCLE NO. 110 ON REPLY CARD

All Trademarks Acknowledged

releasing PC potential

PICO

Technology Limited

Jonathan Campbell

ECT used to nail hammer

Most of us know what water hammer sounds like and are aware that it can cause stress in a system: but what does it look like? Researchers at Mist in Manchester think they have the answer, by developing an electrical capacitance tomography (ect) technique that promises the first accurate method of characterising this common yet complex phenomenon.

Typically, water hammer can occur when a valve is suddenly closed at the end of a long pipe. The water flow is abruptly stopped resulting in a pressure wave that travels back up the pipe. In turn this causes an expansion at the supply end which reverses the wave making it travel back to the valve, where the process is repeated until it runs out of energy.

The problem has been that, up to now, recording techniques have not been fast enough to capture the very rapid transients that characterise hammer, while complexity of the effect has made modelling difficult and inaccurate.

But the Mist researchers have

based their technique ("Monitoring water hammer by capacitance tomography", WQ Yang *et al*, *Electronics Letters*, Vol 32, No 19, pp. 1778-1779) on the fact that the expansion cause cavitation – pockets of air – within the pipe.


To make the measurements, a set of capacitance electrodes are mounted around the pipe, so that the inter-electrode capacitance-changes caused by variations of permittivity within the pipe can be used recorded. Cross sectional images can then be constructed from the data. The Mist system uses 12 measurement electrodes, 10cm long, mounted onto the outside of 41mm uPVC pipe, just upstream of the valve. When the valve is closed, a vapour bubble is formed then collapses, its life captured by the electrodes.

Though the transient process in the Mist experiment lasts only 0.27s, the system can collect measurements at 100frame/s allowing detailed behaviour of the water hammer to be observed.

Next step for the team is correlate data between an upstream and downstream sensor to find the transport speed of the water hammer waves and to find the velocity profile of the flow.

More information contact: WQ Yang, Process Tomography Group, Department of Electrical Engineering and Electronics, Mist, PO Box 88, Manchester M60 1QD.

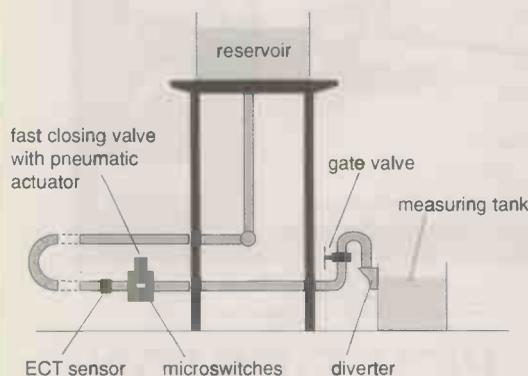ECT is being used at Mist to unravel the mysteries of water hammer.



Silicon fab goes flat out

A new technique that enables fabrication of atomically-flat silicon surfaces as opposed to the 'terraced' surfaces that exists in current devices could bring big improvements to performance and yield of silicon microelectronic and optical devices.

The technique, developed by materials scientists at Cornell University, uses high pressure and temperature to force atomic steps on the silicon surface to migrate to specially created boundaries. Though the slight irregularities, on the nanometre scale in current silicon layers, do not have much effect on the operation of the present generation of devices, future miniaturisation is going to make smoothness a critical factor.

Normal surfaces of silicon, though looking flat, consist of short, smooth terraces each ending in a step of atomic dimensions at about 1.5nm.

But using their new manufacturing procedure, the Cornell team has been able



Scanning tunnelling microscope image of a typical silicon wafer surface, taken at Cornell, shows steps each of a height corresponding to one atom spacing. Here, four atomic steps are separated by flat atomic planes, or terraces. Rows of silicon atoms are clearly visible on the terraces. Cornell materials scientists have developed a process to increase the areas of perfect atomic terraces by a factor of greater than 1000, producing a step-free surface.

to create extensive regions on a silicon wafer that have no atomic steps at all. They have achieved this by creating a grid of ridges, 0.5µm high and 1µm wide on the surface of the wafer and clearing the intervening squares of their atomic steps by forcing them into the ridges.

The grid is created using electron beam lithography, and each square, about 10µm

wide, has about a billion atoms on it, with several thousand atomic steps all across the square. The sample is then subjected to ultra-high vacuum and then high temperatures of 1020-1150°C.

At these temperatures, silicon atoms are detached from the atomic steps so that in effect the steps migrate to the ridges at the boundary of the square, leaving the surface of the square atomically flat.

"The benefit is that it should now be feasible to make smaller devices with better control of the dimensions, at the atomic level, and it should eliminate the harmful features of the surface that could get through the manufacturing process," says Jack Blakely, Cornell professor of materials science and engineering who has led the work.

"Circuits built on step-free surfaces can be designed with smaller dimensions and utilise thinner semiconductor channels and insulating layers to increase performance and decrease power consumption. By having it flat, this could be an ideal surface on which to build an integrated circuit."

More information from Jack Blakely, Materials Science and Engineering, Cornell University Ithaca, NY, USA.

PCB Designer

For Windows 3.1, '95 or NT



Niche Software (UK)
12 Short Hedges Close, Northleach, Cheltenham GL54 3PD

Looking for the price?
It's just £49.00 all inclusive!
...no VAT...no postage...
...no additional charges for
overseas orders.

Dealers and distributors wanted.
Phone (01432) 355 414 to order

Internet

See our Web site at www.niche.co.uk for
information and a working demo. e-mail
pcb@nlche.demon.co.uk.

- ✓ Produce Single or Double sided PCBs.
- ✓ Print out to any Windows supported printer.
- ✓ Toolbar for rapid access to commonly used components.
- ✓ Helpful prompts on screen as you work.
- ✓ Pad, track & IC sizes fully customisable.
- ✓ No charges for technical support.
- ✓ Snap-to grid sizes 0.1", 0.05" 0.025" and unrestricted.
- ✓ SMT pads and other pad shapes.

Also available from,

South Africa: JANCA Enterprises, PO Box 32131, 9317 Fichardtpark at R299,00. Phone/FAX: (051) 223744

France: Telindel, Quartier Les Pradets, Chemin des Veys, 83390 Cuers. Phone: 94 28 66 67

CIRCLE NO. 111 ON REPLY CARD

RADIO DATA MODULES MODEM TRANSCEIVERS

UK, E.E.C, Scandinavia, Eastern Europe, North & South America, Middle East, South Africa, New Zealand, Far East or Australia. Wherever you are, we have a module on the right frequency for you!

UHF Transceiver for the World!

- * 400 to 500MHz Versions *
- * Range up to 5Km *



Only 55 x 73 x 15mm

- * Compact Size ideal for Hand Helds *
- * UK, North American, Australian *
- * MPT, I-ETS & FCC Approval *
- * Up or 64 selectable channels *
- * Starter Kit only £299.95 *

Low Cost High Speed Data Transmitters: UK, EEC and Beyond!

- * Available UK Approved MPT1340 418MHz *
- * Export I-ETS-300-220, 433.92MHz *
- * Reduce Component Count, Cost, Size & Power Drain *
- * Operate to 20,000 bps *
- * Transceiver also available with up to 40K data rate *



TXM-418-F Transmitter


Licence Exempt Spread Spectrum on 2.45GHz

With up to 1Mbit data rate, RS485 interface and 100mW of output power these units are ideal for many high speed industrial or office data transfer applications. Even compressed colour video may be transferred. Price £480.00 each or starter kit for only £799.95.



VHF Modules for UK, Australia and Beyond!

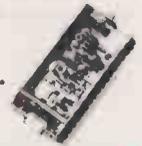- * UK, 173MHz to MPT1344 & MPT1328 Licence Exempt *
- * Miniature Low Cost or canned 1 & 10mW Transmitters *
- * 173.500MHz Transmitters & Transceivers for Australia & RSA *
- * PCB mount or canned, Superhet Receivers *
- * Low Cost Meter Reading Transceivers on 183.8875MHz *
- * Prices from £19.00 to £200.00 per unit *




Radio - Tech Limited, Overbridge House, Weald Hall Lane

Thornwood Common, Epping, Essex CM16 6NB.
Sales +44 (0) 1992 57 6107 Fax +44 (0) 1992 56 1994
Technical Support +44 (0) 1992 57 6114
Internet: <http://www.radio-tech.co.uk>

CIRCLE NO. 112 ON REPLY CARD

Design & Verify Circuits

FAST

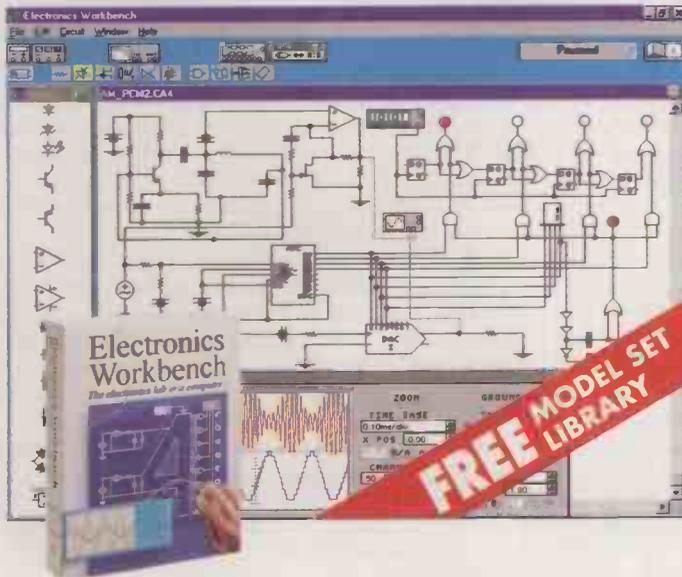

Electronics Workbench
The electronics lab on a computer

FREE MODEL SET
LIBRARY

Electronics Workbench

New 4.1 32 Bit Version

Electronics Workbench saves you time. It's highly productive simulated workbench let's you design and verify circuits faster than it would take on a real bench. Mix analogue and digital components and ICs in any combination

OVER
70,000
USERS

Electronics Workbench:

- Click & drag schematic capture
- Mixed analogue/digital SPICE simulator
- Instant Bode plots and scrollable waveforms
- 50 analogue components with 350 models
- 140 digital components and ICs in TTL and CMOS
- Windows 95/NT/3.1, DOS and Macintosh versions
- FREE unlimited technical support
- 30-day money-back guarantee

ONLY
£199



Robinson Marshall (Europe) Plc

44-(0)-1203-233216

Fax: 44-(0)-1203-233210
Nadella Building, Progress Close,
Leofric Business Park, Coventry CV3 2TF
E-mail: sales@rme.co.uk



Shipping charges UK £6.99 All prices are plus VAT.
Electronics Workbench is a trademark of
Interactive Image Technologies Ltd., Toronto, Canada
All other trademarks are the property of their respective owners.



INTERACTIVE

Put a smile on your interface

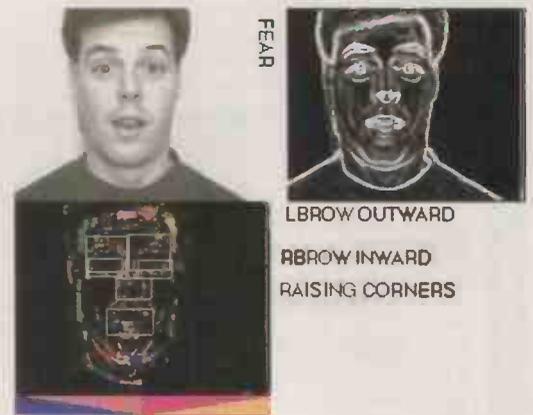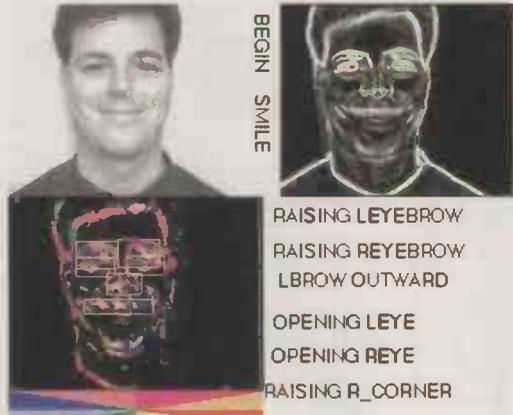Analysing our expressions. The upper left quadrant shows the intensity image, the upper right shows the gradient image, the lower left shows the optical flow field with the rectangles enclosing the face regions of interest and the mapping of colours onto directions, and the lower right shows the mid-level descriptions that were computed.



Sometimes your computer does something so stupid – like trashing a vital file it really should have known you wanted – that words just stick in the throat. But work being carried out at the University of Maryland could mean that your computer will one day be able to recognise those looks of open-mouthed disbelief and face-twisting fury, and react accordingly. (In the *Research Notes* office that would involve quietly sliding its keyboard out of the reach of a fast moving fist).

Aim of the research being undertaken by Yaser Yacoob and Larry S Davis at the Computer Vision Laboratory is to recognise facial expressions from image sequences. The work has been prompted by the fact that visual communication plays such a central role in human communication and interaction. If successful, the research will allow computers to sense our moods, concentration and understanding, while also opening up possibilities for better video transmission of facial expressions across low-bandwidth systems.

According to the authors (“Recognising human facial expressions from long image sequences using optical flow”, *IEEE Transactions on pattern analysis and machine intelligence*, Vol 18, No 6, pp. 636-642), low bandwidth transmission of facial data can be made more efficient by using mid- and high-level visual representation of the facial actions. Or as the researchers put it: “Send a smile and a few parameters that determine the mouth actions involved”.

Previous researchers have analysed the six principal expressions of happiness, sadness, surprise, fear, anger and disgust, but have tended to concentrate on static “mug-shots.”

However Yacoob and Davis have developed algorithms that use optical flow computation to identify the direction of rigid and non-rigid motions caused by human facial expressions, and have so far demonstrated recognition of the six expressions on a large set of image sequences.

Analysis involves tracking rectangles that enclose the facial features. Every rectangle encloses one feature of interest. Each of the 32 subjects so far tested was asked to display the expressions of emotion in front of a video camera, while minimising head movement – though subjects inevitably did move their heads during the experiment.

The experiments showed, through analysis of the optical flow field in the rectangles, that cues to detect the beginning of “fear” include the inward raising of the eyebrows and opening of the mouth.

Some confusion still exists between fear and surprise,

anger and disgust and sadness and surprise. There is also some difficulty where one expression begins then transforms into another.

Despite that, in the more than 30 subjects that were studied in the laboratory environment, the researchers were able to report a “good” classification of facial expressions in a very large database.

For more information contact Yaser Yacoob at the Computer Vision Laboratory, Center for Automation Research, University of Maryland, College Park, MD 20742-3275, USA. email yaser@cs.umd.edu

Millimetre antenna has no moving parts

A prototype antenna that operates at millimetre wave frequencies and has no moving parts, no phase shifters and can be implemented in plastic has been built by researchers at Georgia Institute of Technology. The electronically-scanned device, which is believed to be the first Rotman lens to operate at a frequency as high as 37GHz, could offer an inexpensive, rugged, reliable and compact alternative to current millimetre wave antenna technologies.

Most antennas operating at millimetre wave frequencies use mechanical scanning or phase shifters, both of which have disadvantages. Mechanically steered antennas are slow in response and suffer reliability problems due to shock and vibration. Phase shifters are costly to fabricate and introduce considerable rf losses.


But in a Rotman lens, such as the Georgia Tech device, millimetre wave energy coming from a particular direction is focused by passing the electromagnetic energy through a pair of parallel plates shaped like a lens. Beam-forming or focal ports are located on one side of the plates, fed by a switch array. The array ports are on the opposite side, each connected to an antenna element. Energy fed into a specific focal port will emerge from the antenna elements and produce a beam along a particular direction.

Switching the input from focal port to focal port steers the

continued on page 916...

THE Autorouter for **EASY-PC Pro' XM!**

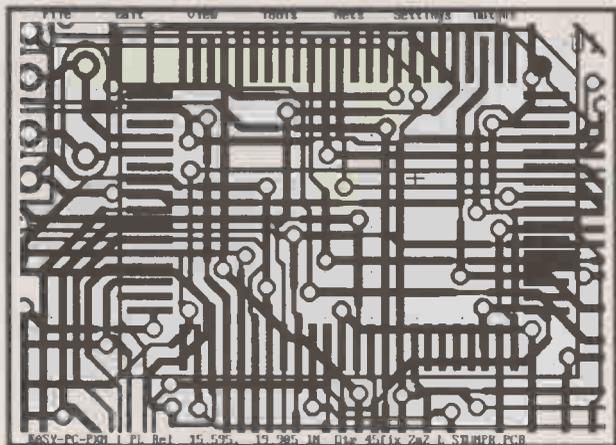MultiRouter is "the best Autorouter that I have seen costing less than £10,000!" R.H. - (Willingham, UK)



- MultiRouter uses the latest 32 bit, Shape based, Multi-pass, Shove-aside, Rip-up and Re-try Technology
- 100% routed 140 Components on a 210mm x 150mm board in less than 10 minutes! (75MHz Pentium)
- 100% Completion where other autorouters fail
- **Only £295! Could Easily Pay For Itself On The First Project!**

Number One Systems

Write, fax, phone or email for full information.

UK/EEC: Ref: WW, Harding Way, St.Ives, Cambridgeshire, ENGLAND, PE17 4WR. email: sales@numberone.com
 Telephone UK: 01480 461778 (7 lines) Fax: 01480 494042
 International +44 1480 461778/494042


USA: Ref: WW, 126 Smith Creek Drive, Los Gatos, CA 95030
 Telephone/Fax: (408) 395-0249



CIRCLE NO. 114 ON REPLY CARD

True Real-World

RESULTS

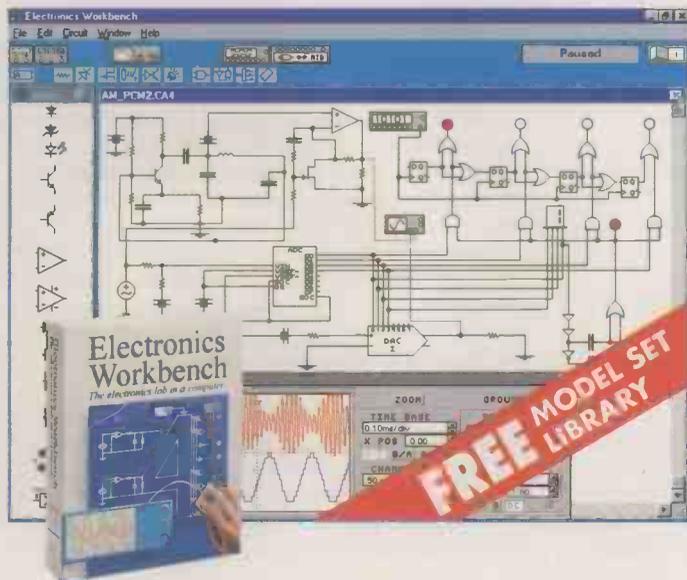

Electronics Workbench

New 4.1 32 Bit Version

Electronics Workbench uses a powerful SPICE simulator to ensure that circuits work like the real thing. And since you have complete control over the value and behaviour of all components, you control the design process.

**OVER
70,000
USERS**

Electronics Workbench:

- Click & drag schematic capture
- Mixed analogue/digital SPICE simulator
- Instant Bode plots and scrollable waveforms
- 50 analogue components with 350 models
- 140 digital components and ICs in TTL and CMOS
- Windows 95/NT/3.1, DOS and Macintosh versions
- FREE unlimited technical support
- 30-day money-back guarantee

**ONLY
£199**

Robinson Marshall (Europe) Plc

44-(0)-1203-233216


Fax: 44-(0)-1203-233210
 Nadella Building, Progress Close,
 Leofric Business Park, Coventry CV3 2TF
 E-mail: sales@rme.co.uk

Shipping charges UK £6.99 All prices are plus VAT.
 Electronics Workbench is a trademark of
 Interactive Image Technologies Ltd., Toronto, Canada
 All other trademarks are the property of their respective owners.



CIRCLE NO. 115 ON REPLY CARD

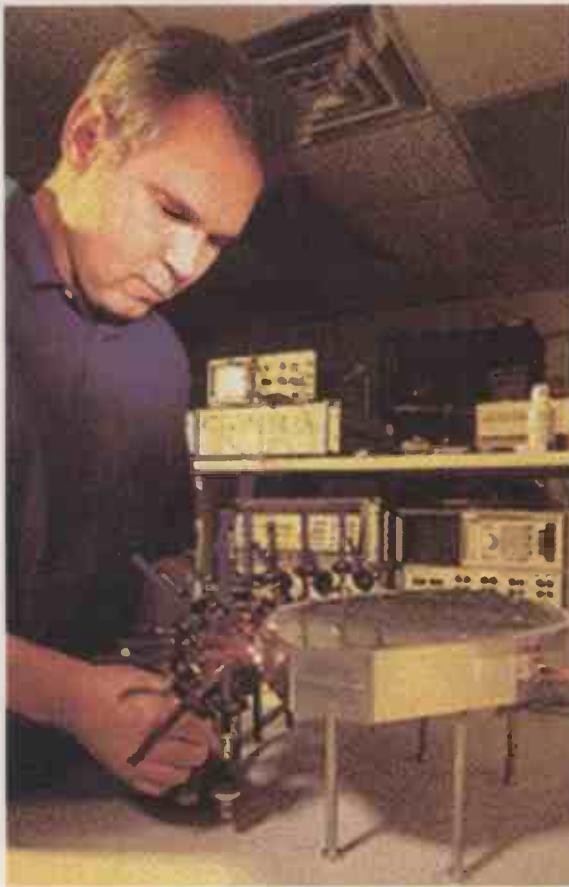Otto Rausch attaches wave guides to his prototype Rotman lens that offers a low cost and rugged method of electronically scanning millimetre waves.



beam electronically in one direction across a 45° arc, and can be accomplished with pin diode switches, which are also simple, reliable and inexpensive.

Previous Rotman lens antennas have been developed at frequencies of 18GHz or below, most in microstrip. Unfortunately microstrip is very lossy at high frequencies, and so is not suitable in the millimetre wave region.

Now, with help from colleagues, Georgia Tech senior research scientist Otto Rausch has designed and fabricated an antenna milled out of a solid block of aluminium.

Rausch's prototype required extreme machining and finishing tolerances, but the researcher says that production antennas could be hot-pressed in plastic, and then coated with a conductor such as gold. The antenna feed-horns and switch-array could be made the same way, keeping the costs down.

Besides the low cost, compact size and ruggedness, the lens antenna is also reported to offer very low throughput loss and sidelobe emissions. In the prototype, sidelobe power can be suppressed by a factor of one-thousand below the energy of the main beam, and power loss through the lens itself is less than 2 dB.

To fulfil its potential, Rausch says the antenna's operating frequency must be expanded, and the capability to scan in two dimensions added. However potential applications include autonomous aircraft landing systems, synthetic vision for ground vehicles and automobile collision avoidance systems. More information is available from Otto Rausch at the Georgia Institute of Technology, Atlanta, Georgia 30332-0828 email ekkehart.Bausch@gtri.gatech.edu

Architects get wise to electrochromic windows

One of the 'simplest' concepts for reducing air conditioning bills while keeping office buildings cool in summer is to install window glass that can be darkened or lightened automatically, or at the touch of a button. Unfortunately, how to produce practical systems with acceptable life and cost has proved anything but simple. However, work being carried out at the National Renewable Energy Laboratories in Colorado could help overcome many of the present technical barriers to electrochromic (ec) windows.

The breakthrough made at NREL ('Low-voltage electrochromic device for photovoltaic-powered smart windows', C Bechinger et al, *J. Appl. Phys.*, Vol 80, No 2, pp.1226-1232) is in developing an all-solid state electrochromic device that can be switched over a range of optical transmissions by voltages of less than 1V. This voltage is smaller than any other device tested so far, and at these levels, the researchers say, it should be possible to power the devices by an integrated semi-transparent photo-voltaic (pv) cell, so removing the associated wiring costs that substantially push up investment in ec windows.

In the NREL system, indium-tin-oxide (ito)-coated glass forms the electrically conductive transparent substrate for the device, onto which thin films of WO_3 , MgF_2 and V_2O_5 are deposited, topped by a semi-transparent gold electrode.

Colouration occurs by a complex reaction between the clear WO_3 and a light-absorbing compound of lithium and WO_3 . The reaction involves injection and extraction of electrons and metal ions. But, according to the team, the key to the low voltage switching is inclusion of the

MgF_2 layer which acts as the lithium ion conducting layer.

When electrical connection is made, the device transmission drops to about 40% of its bleached-state level in around 60s. To return to the original transparent state, the device simply needs to be short circuited to cause spontaneous bleaching within minutes.

In the tests, voltage was supplied by a semi-transparent photo-voltaic powered cell connected to the ec device. But the researchers say they expect a monolithic pv-ec device to function in a similar manner.

Degradation seems much improved over other types and the NREL devices are reported to have been cycled in air at $\pm 1V$ with almost no change in optical behaviour after 5000cycles. Eventual degradation was thought to be due to corrosion caused by reaction of lithium with water that has penetrated the device. The researchers say that in practical devices the gold electrode would be replaced with a much thicker transparent electrode that would also control the water content of the device.

Current cost of ec windows is estimated to be somewhere between \$100 and \$1000/m². However the integration of the power source into a self contained window could make the NREL devices much more attractive than other designs and also allow smart windows to be retrofitted to existing buildings.

With the cost of energy becoming much more of an issue in building-economics, electrochromic smart windows could one day become a familiar part of architectural design.

More information contact: Clemens Bechinger now at the Universitaet Konstanz, D-78434 Konstanz, Germany. email clemens.bechinger@uni-konstanz.de ■

8 CAVANS WAY,
BINLEY INDUSTRIAL ESTATE,
COVENTRY CV3 2SF
Tel: 01203 650702
Fax: 01203 650773
Mobile: 0860 400683

TELNET

(Premises situated close to Eastern-bypass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

MISCELLANEOUS

| | |
|--|------------|
| Anritsu ME462B - DS-3 transmission analyser | £3000 |
| Anritsu MG642A - Pulse pattern generator | £1500 |
| Barr & Stroud - EF3 variable filter (0.1Hz-100KHz) | £150 |
| Datatab DL 1080 - Programmable Transient Recorder | £350 |
| Deatron 1061 - Precision multimeter | £850 |
| Dynapart TP20 - Intellipace tape peel tester, immac. cond. | £1950 |
| E.L.P. 331 - 18GHz frequency counter | £350 |
| E.L.P. 848A - frequency counter (26-5GHz) | £2750 |
| Farnell 98E520 - Signal generator (10-520MHz) | £400 |
| Farnell TS70 Mill - Power Supply (70V-5A or 35V-10A) | £225 |
| Fluke 5100A - Calibrator | £3800 |
| Fluke 5100B - Calibrator | £4500 |
| Fluke 5101B - Calibrator | £5000 |
| Fluke 5200A - A.C. calibrator | £2500 |
| Fluke 5205A - Precision power amplifier | £P.O.A. |
| Fluke 7105A - Calibration system (As new) | £P.O.A. |
| Halden 1107 - 30V-10A Programmable power supply (IEEE) | £550 |
| Hewlett Packard 338A - distortion measuring set | £1500 |
| Hewlett Packard 432A - Power Meter (with 478A Sensor) | £275 |
| Hewlett Packard 436A or B - Power Meter (with 8481A/8484A) | from £750 |
| Hewlett Packard 5328A - 100MHz universal frequency counter | £250 |
| Hewlett Packard 3325A - 21MHz synthesiser/function gen | £1500 |
| Hewlett Packard 3437A - System voltmeter | £350 |
| Hewlett Packard 3438A - Digital multimeter | £200 |
| Hewlett Packard 3465A - 6 1/2 digit multimeter (autocal) | £750 |
| Hewlett Packard 3468A - Digital voltmeter | £750 |
| Hewlett Packard 3488A - HP-IB switch/control unit (various plug-ins available) | £650 |
| Hewlett Packard 3711A/3712A/3719B/3733B - Microwave link analyser | £2985 |
| Hewlett Packard 3778A - PCM Terminal test set | £P.O.A. |
| Hewlett Packard 3779 A/C - Primary flux analyser | £800/£1500 |
| Hewlett Packard 4271B - LCR meter (digital) | £300 |
| Hewlett Packard 4275A - Multi-frequency LCR meter | £4250 |
| Hewlett Packard 4342A - Q meter | £395 |
| Hewlett Packard 4948A - transmission impairment measuring set | £2000 |
| Hewlett Packard 4953A - Protocol analyser | £2500 |
| Hewlett Packard 4954A - Protocol analyser | £2750 |
| Hewlett Packard 5314A - (new) 100MHz universal counter | £250 |
| Hewlett Packard 5342A - Microwave freq. counter (18GHz) | £1500 |
| Hewlett Packard 5359A - Time synthesiser | £P.O.A. |
| Hewlett Packard 5385A - Frequency counter 1GHz (HP-IB) with Opts 001/003/004/005 | £395 |
| Hewlett Packard 6002A - autoranging 50V-10A, PSU | £850 |
| Hewlett Packard 6034A - System P.S.U. 0-60V-10a | £1500 |
| Hewlett Packard 6181C - D.C. current source | £150 |

Hewlett Packard 6281B - Power supply 20V-50A £450
DISCOUNT FOR QUANTITIES

| | |
|---|-------|
| Hewlett Packard 6652A - System Power Supply 20V-20A | £1950 |
| Hewlett Packard 8005B - Pulse generator | £250 |
| Hewlett Packard 8011A - Pulse gen. 0.1Hz-20MHz | £300 |
| Hewlett Packard 8152A - Optical average power meter | £1250 |

| | |
|---|---------|
| Hewlett Packard 8158B - Optical attenuator with opt's 002 + 001 | £1100 |
| Hewlett Packard 8165A - 50MHz programmable signal source | £1650 |
| Hewlett Packard 8349B - Microwave broadband Amp (as new) | £4250 |
| 2-20MHz | £4250 |
| Hewlett Packard 8350B - Sweep oscillator mainframe (plug-ins avail) | £2500 |
| Hewlett Packard 8403A - modulator | £500 |
| Hewlett Packard 8620C - Sweep oscillator mainframe | £400 |
| Hewlett Packard 8660 - Synthesised signal gen. 10KHz-2.6GHz | £4500 |
| Hewlett Packard 8683A - Microwave signal gen. (2.3-6.5GHz) | £2500 |
| Hewlett Packard 8684A - 5-4GHz to 12.5GHz Sig Gen. | £2500 |
| Hewlett Packard 8750A - Storage normaliser | £375 |
| Hewlett Packard 8901A - Modulation Analyser | £3400 |
| Hewlett Packard 8903A - Audio analyser (20Hz-100KHz) | £1995 |
| Hewlett Packard 8958A - Cellular radio interface | £4000 |
| Hewlett Packard 11729B - Carrier noise test set | £2000 |
| Marconi 8938 - A/F power meter | £295 |
| Marconi 2019A - 80KHz-1040MHz synthesised sig. gen | £1950 |
| Marconi 2871 - data communications analyser | £2000 |
| Marconi 6500 - automatic amplitude analyser | £1750 |
| Marconi 6960 - Microwave power meter (+ sensor) | £P.O.A. |
| Philips PM 5187 - 10MHz function gen | £400 |
| Philips PM 5190 - LF synthesiser with GPIB | £800 |
| Philips 5518 - TX - TV pattern generator | £300 |
| Racal Dana 1989 - 130MHz frequency counter ops 4B+5S | £1500 |
| Racal Dana 3100 40-130MHz synthesiser | £750 |
| Racal Dana 9084 Synth. sig. gen. 104MHz | £450 |
| Racal 9301A True RMS R/F millivoltmeter | £300 |
| Racal Dana 9303 True RMS/R/F level meter | £850 |
| Racal Dana 9921 3GHz frequency counter | £450 |
| Schaffner NSG 200E - Mainframe for NSG plug-ins | £1250 |
| Schaffner NSG 203A - Line voltage variation simulator | £1250 |
| Schaffner NSG 222A - Interference simulator | £850 |
| Schaffner NSG 223 - Interference generator | £850 |
| Schlumberger 2720 - 1250MHz Freq. Counter | £800 |
| Schlumberger 41 - Radio Comm. Test Set | £6995 |
| Schlumberger SI 4040 - Stablock, high accuracy 1GHz radio test set | £4895 |
| Schlumberger 4923 - Radio Code Test Set | £1000 |
| Syston Donner 1980B - Microwave Sweeper (12-18GHz) | £2500 |
| Tektronix 577 - Curve Tracer | £1150 |
| Tektronix - Plug-ins - Many available such as PG506, FG504, SC504, SW503, SG 502 etc. | |
| Tektronix TM5003 + AFG5101 - Arbitrary Function Gen | £1750 |
| Tektronix 1240 - Logic Analyser | £750 |
| Tektronix AM503 + TM501 + P6302 - current probe amplifier | £995 |
| Tektronix AA5001+TM5006 - Mainframe programmable distortion analyser | £2500 |
| Tektronix PG506 + TG601 + SG503 + TM503 - Oscilloscope calibrator | £1995 |
| Tektronix CG5001 - Programmable oscilloscope cal. generator | £4995 |
| Time 9814 Programmable resistance | £800 |
| Time 9814 Voltage calibrator | £750 |
| Waytek 1728 - Programmable sig. source (0.0001Hz-13MHz) | £P.O.A. |
| Wayne Kerr 8905 - Precision LCR meter | £850 |
| Wiltron 560 - Scalar Network analyser | £800 |
| Wiltron 66205 - Programmable sweep gen. (3.6-6.5GHz) | £500 |

OSCILLOSCOPES

| | |
|--|------|
| Cosor 3102 - 60MHz dual channel | £250 |
| Gould OS255 - 15 MHz dual channel | £150 |
| Gould OS3000 - 40MHz dual channel | £250 |
| Gould OS3351 - 40MHz dual channel | £225 |
| Gould OS4000 - 10MHz Digital storage | £200 |
| Gould 5110 - 100MHz intelligent oscilloscope | £750 |
| Hewlett Packard 180D - 100MHz 4 channel | £300 |
| Hewlett Packard 182C - 100MHz 4 channel | £350 |

| | |
|---|------------|
| Hewlett Packard 1740A, 1741A, 1744A, - 100MHz dual ch. | from £350 |
| Hewlett Packard 54100D - 1GHz digitizing | £3995 |
| Hewlett Packard 54200A - 50MHz 2 channel digitizing | £1000 |
| Hewlett Packard 54201A - 300MHz digitizing | £1750 |
| Hewlett Packard 54501A - 100MHz Digitising - 4 channel | £1950 |
| Hitachi V212 - 20MHz dual channel | £180 |
| Hitachi V222 - 20MHz dual channel | £200 |
| Hitachi V650F - 60MHz dual channel | £350 |
| Kikusui DSS 6522 - 20MHz digital storage | £475 |
| Kikusui COS 6100 - 100MHz 5 channel 12 trace | £475 |
| Kikusui COS 6100 - 100MHz dual channel | £425 |
| Nicolet 3091 - Low freq D.S.O. | £1100 |
| Philips 3217 - 50MHz dual channel | £350 |
| Philips 3219 - 50MHz with analogue storage, Dual Ch | £400 |
| Philips 3263 - 100MHz dual channel with microprocessor cont. timing | £400 |
| Philips 3540 - logic scope (25MHz dual ch. + logic an) | £350 |
| Philips 3295 - 350MHz dual ch. | £1500 |
| Philips 3315 - 60MHz D.S.O. | £750 |
| Philips PA3295A - 400MHz dual channel | £1750 |
| Tektronix 2445 - 150MHz - 4 channel | £1250 |
| Tektronix 2445A - 150MHz - 4 channel | £1600 |
| Tektronix 455 - 50MHz dual channel | £350 |
| Tektronix 2221 - 60MHz digital storage | £1500 |
| Tektronix 7854 - 400MHz Waveform processing oscilloscope | £1500 |
| Tektronix 484/486 - 100MHz, storage | from £350 |
| Tektronix 485/485B - 100MHz dual ch. | from £350 |
| Tektronix 488 - 100MHz D.S.O. | £750 |
| Tektronix 475/475A - 200/250 MHz dual channel | from £475 |
| Tektronix 434 - 25MHz 2 channel + analogue storage | £250 |
| Tektronix 454 - 150MHz 2 channel | £400 |
| Tektronix 2213 - 60MHz dual ch. | £425 |
| Tektronix 2215 - 60MHz dual ch. | £450 |
| Tektronix 2225 - 50MHz dual trace | £450 |
| Tektronix 2236 - 100MHz Dual Trace with Counter/Timer/Dmm | £995 |
| Tektronix 2338 - 100MHz dual ch. (portable) | £750 |
| Tektronix 7313, 7893, 7813, 7833, 7833 - 100MHz 4 ch. | from £300 |
| Tektronix 7704 - 250MHz 2 ch. | from £550 |
| Tektronix 7904 - 500MHz ch. | from £850 |
| Tektronix 7904 - 500MHz with storage | from £1000 |
| Tequipment D83 - 50MHz dual channel | £200 |
| Tequipment DM63 - 20MHz 4 channel | £150 |
| Wirtau SS5121 - 100MHz dual channel | £425 |
| Wirtau SS5702 - 20MHz dual channel | £175 |
| Wirtau SS5710 - 60MHz dual channel | £375 |

Other scopes available too

SPECTRUM ANALYSERS


| | |
|--|-------|
| Advantest 4133A - 10KHz-20GH | £8995 |
| Altech 757 - 10KHz-22GH | £2750 |
| Hewlett Packard 141T + 8552B + 8555A (10MHz-18GHz) | £1600 |
| Hewlett Packard 142T with 8559A (10MHz-21GHz) | £3750 |
| Hewlett Packard 853A with 8558A (0.01-21GHz) | £4250 |
| Hewlett Packard 3582A - dynamic signal analyser, dual channel | £7500 |
| Hewlett Packard 3580A - 5Hz-50KHz | £995 |
| Hewlett Packard 3582A - 25KHz analyser, dual channel | £2500 |
| Hewlett Packard 3709B - Constellation Analyser with 15709A High Impedance Interface (as new) | £6750 |
| Hewlett Packard 8505A - Network analyser (500KHz-1.3GHz) | £4000 |

MANY MORE ITEMS AVAILABLE - SEND
LARGE S.A.E. FOR LIST OF EQUIPMENT ALL
EQUIPMENT IS USED - WITH 30 DAYS
GUARANTEE. PLEASE CHECK FOR AVAILABILITY
BEFORE ORDERING - CARRIAGE
& VAT TO BE ADDED TO ALL GOODS

CIRCLE NO. 116 ON REPLY CARD

Analogue, Digital & Mixed Mode

CIRCUITS

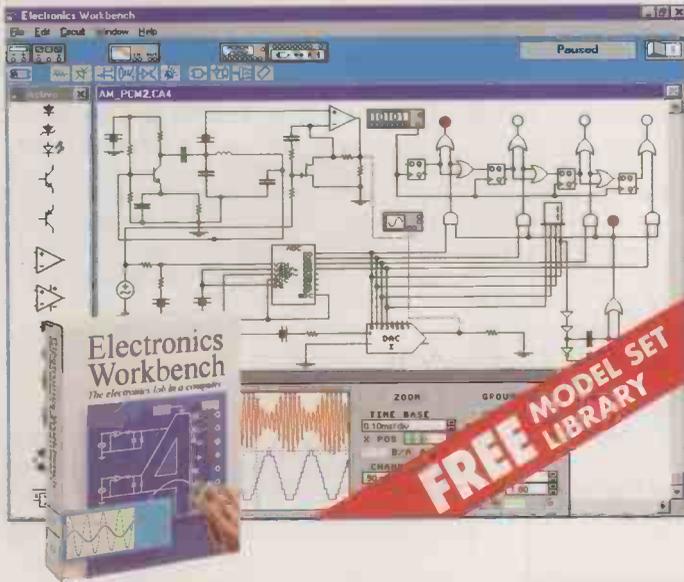

Electronics Workbench

New 4.1 32 Bit Version

Electronics Workbench is the first affordable integrated tool to offer true mixed-mode simulation. It delivers the power you need to design and verify analogue, digital and true mixed-mode circuits-fast.

OVER
70,000
USERS

Electronics Workbench:

- Click & drag schematic capture
- Mixed analogue/digital SPICE simulator
- Instant Bode plots and scrollable waveforms
- 50 analogue components with 350 models
- 140 digital components and ICs in TTL and CMOS
- Windows 95/NT/3.1, DOS and Macintosh versions
- FREE unlimited technical support
- 30-day money-back guarantee

ONLY
£199

Robinson Marshall (Europe) Plc
44-(0)-1203-233216

Fax: 44-(0)-1203-233210
Nadella Building, Progress Close,
Leofric Business Park, Coventry CV3 2TF
E-mail: sales@rme.co.uk.

Shipping charges UK £6.99 All prices are plus VAT.
Electronics Workbench is a trademark of
Interactive Image Technologies Ltd., Toronto, Canada
All other trademarks are the property of their respective owners.



CIRCLE NO. 117 ON REPLY CARD

PCB CAD review subjects

This review, which began in the September issue and continues next month, covers the following ten products.

PCB Designer: Niche Software Ltd, tel. UK 01432 355414. £49 inclusive (see September issue).

PIA: AW Software, tel. Germany +49 89 6915352. PIA std 99DM: extended 171DM 32bit 286DM inc tax (see September issue).

Easytrax: Protel International Pty, tel. Australia 408 437 7771, UK PDSL, tel. 01892 663298 (see September issue).
£6 copying charge.

Ranger2: Seetrex CAE Ltd. 01705 591037, (see October issue) £150 exc
£10 p+p and VAT.

Electronics Workbench: Interactive Image Technologies Ltd (Canada), tel. 001 4169 775550. UK Robinson Marshall, tel. 01203 233 216, (see October issue) £199 exc p+p and VAT.

CircuitMaker: MicroCode Engineering (USA) UK agent Labvolt, tel 01480 300695. Circuitmaker and Traxmaker cost £199 each excluding vat and p&p, see November issue.

Quickroute 3.5 Pro+: Quickroute Systems Ltd, fax or phone 0161 449 7101. *Pro* is priced at £249 while *Pro+* is £399. *Smartroute* is £149 or £99 supplied with Quickroute.

Propak: Labcenter Electronics, tel 01756 753440, fax 01756 752857, £495 exc VAT.

Proteus: Labcenter Electronics.

EasyPC Pro XM: Number One Systems.

Note that although this set of reviews started in the September issue with a couple of smaller packages, this review is not in any order of complexity or competence.

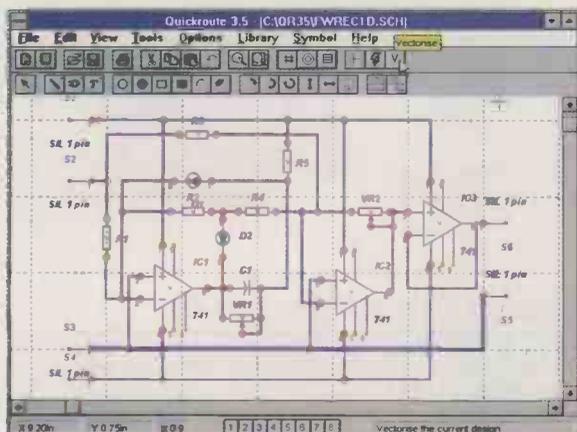


Fig. 1. Typical schematic screen when the parts bin is off, before processing so showing circles at junctions. Note the bubble-type help text on the Vectorise button.

The route

In the penultimate article in this comprehensive series of PCB CAD reviews and discussions, **Rod Cooper** investigates **Quickroute** and the **Propak** suite.

Review 1 – Quickroute 3.5

Quickroute3.5 – *QR35* for short – is a development of the popular *Quickroute3* that was reviewed in *Electronics World*, January 1995.

Most of what that review said still applies, but there have been some major changes. For example, the manual that was criticised for being written in the wrong order now starts with schematic design, and works through pcb design to the autorouter – making it one of the most logically compiled manuals available!

I remember seeing *Quickroute* some time ago as a dos-based shareware program. The version was 1.5 and I believe it was written for the American market as the pricing was in dollars. It was then a tiny 256Kbyte in size and would run on virtually any pc. For historical interest a screen from this program is shown in Fig. 7 and the similarities with the latest version will be apparent.

I used the top two versions, *Quickroute 3.5 Pro* and *Pro+*,

for this review, priced at £249 and £399 respectively. Both *Pro* and *Pro+* are integrated schematic capture/autorouter packages, combined with manual pcb design, but *Pro+* has some extra features such as of *Spice* and *Spiceage* netlist export, DFX export to mechanical cad programs, Tango and Gerber net-list import, and copper fill.

Quickroute programs are intuitive and easy to use, and perhaps because of that are easy to review, and are thus firm favourites with reviewers. The ease of use comes not just from being in Windows but also from their relative simplicity. There is for example, no autosave or autopan, no autonecking of tracks, no snap-to function for drawing, and there is not much configuration to do on the autorouters. Simplifying the structure while retaining the essentials gives a program which will have considerable appeal to those starting out in cad.

To run *QR35* you need Windows 3.1, or better and a fairly powerful pc. Although the package will run on a 386SX with 4MB of ram, it will be noticeably tardy. It would not run at all on a 286. The recommended machine is a 486 running at 60MHz or higher with at least 8MByte ram. Like most of the Windows-based programs, if you use less than

to pcb cad

the recommended hardware, you may find parts of the program such as screen redraws and autorouting irritatingly slow.

The drawing area on a 14in monitor is about 7.5in by 5in with the parts bin on screen, and 9in by 5in without it. The parts bin takes up a lot of room, and it is difficult to understand why it is quite so big. It can of course be turned off, but if I were running *QR35* with the parts bin, I would be inclined to use a larger monitor with higher definition in order to see more of the circuit. The button bar has been increased to a double bar and this also diminishes the size of the drawing area. Some of these buttons you use only once per design – such as the 'New Schematic' and 'New PCB' buttons and could be easily dispensed with. I think a return to the original single button bar and a smaller parts bin would help those people with 14in and 15in screens.

Interesting features

QR35 has some interesting features. Starting with the schematic drawing section, it made a refreshing change to see a lattice grid used for layout instead of the usual dot matrix. The default colour for line drawing is a yellow initial line on a white background – very difficult to see, as any graphics technician will tell you. But mercifully the colours can be changed. I chose a grey background with blue lines.

The schematic drawing program is not orthogonal, permitting lines in any direction. I found it required sustained attention to maintain a neat orthogonal layout during long drawing sessions. After a while, it is tempting to take few short cuts and put in a diagonal line or two, but this instantly gives any schematic an untidy look.

There is no positive confirmation that a drawn line is connected – at least not at the time of drawing. To check connectivity, you press the redraw button after drawing and visually check each connection. Properly connected lines are given a circle symbol. Although this was acceptable on small designs, on large boards this became a very tedious process. It was easy to miss some connections. I fell into the trap of just scanning the schematic, which led to error messages at later stages, which in turn meant retracing my steps back to the schematic to correct them.

The schematic sections of *Ranger2*, *Propak*, *CircuitMaker* and *Electronic WorkBench* have means of confirming a connection at the time it is made combined with a strong snap-to

function. I think this is the way it should be done.

Zoom in and out is controlled either from the button bar or by the function keys F1-7. Key F8 is a custom zoom option. These keys can also be used for panning by pointing the mouse to where you wish to pan and pressing the function key at whatever zoom level you are in.

Function keys are more helpful if you want to zoom or pan while you are already using the mouse to draw a line. You can also pan using the scroll bars. To centre the drawing and show it fully there is another function, 'Page View', which adjusts the zoom to fill the screen.

Many cad programs use the left mouse button to select or start something and the right button to stop it, but *QR35* uses the right button for various other actions. It can activate the library volumes from the button bar or pan the drawing area for example. This takes some getting used to if you have experience in other areas of cad.

The nominal drawing area is 32in by 32in. Multi-sheet schematics are supported, as are global nets. There is no map diagram showing where you are, but Page View can be used to find lost drawings.

Graphical library presentation

One of the best features of *Quickroute* is the graphical presentation of the library volumes. Clicking on the icon on the button bar gives a large screen of one page of a library volume, and you can see exactly what you are selecting from the high-quality symbols. This is a big improvement on text-only libraries.

If the library volume consists of more than one page, it is easy to flip through the pages.

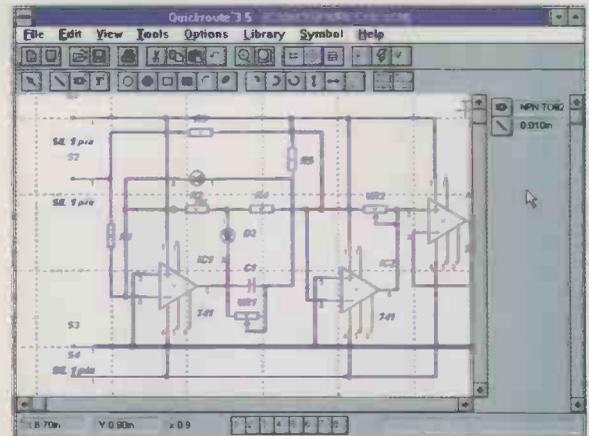


Fig. 2. Same screen with parts bin on, after processing, so many of the circles are now junction dots, indicating net formation. Note area taken up by parts bin.

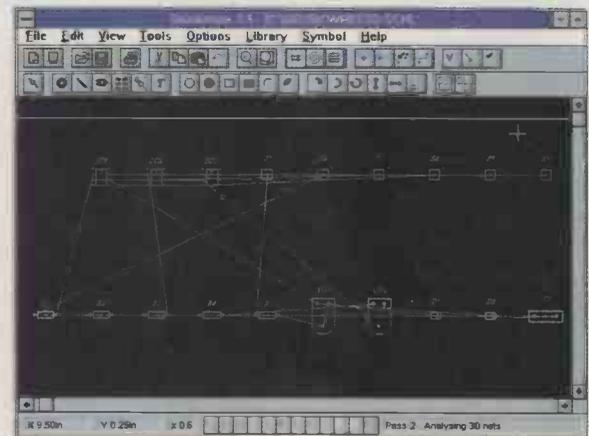


Fig. 3. The initial rat's nest formed from the above screen with components on a linear grid.

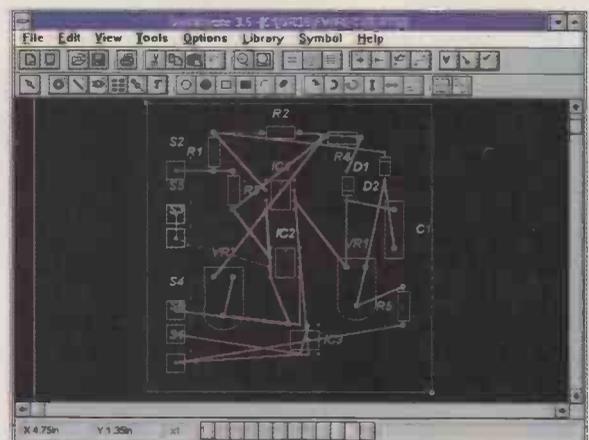


Fig. 4. Rat's nest after interactive editing. Note outline of board now inserted.

Fig. 5. Results of autorouting with standard autorouter. Note that several ratlines cannot be turned into tracks by this autorouter. The grid has been left on in this shot.

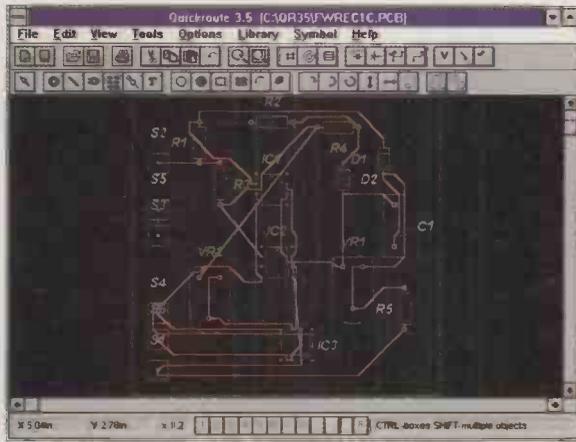


Fig. 6. Results of routing exactly the same rat's nest with the more powerful new AR3 autorouter, completing the board. The beta version of the AR3 used here can only do thin tracks, the commercial version will not have this limitation. (Grid off).



You might think this leads to some odd-looking schematics, and perhaps it does, but it has great practicality. However, there is a limitation on this method at present because the standard autorouter puts a ceiling on the maximum size of the track. If the track width exceeds 60% of the grid, a smaller track is substituted. In effect, this limits track size to less than 0.03in with the standard autorouter, but with *Quickroute's* new AR3 autorouter, I am told this limit should disappear. It should be possible to route tracks of any size.

Transferring to another volume was similarly quick and easy. For discrete devices like transistors, you do not get a long list of specific types, but a generic symbol with the package type. Information about the device is entered manually, so for this you would need a good memory or a data book. Component text is non-maneuvrable so you may need to expand the diagram a little to avoid crossing lines, other components etc.

An interesting feature of the track libraries is that track thicknesses can be entered at the schematic stage and processed through schematic capture to re-appear in the finished pcb at the correct size. This is a good system, as you can check from the schematic stage the current ratings you have designed into various parts of the circuit.

Code named AR3, the new autorouter may well appear with a different name. It is in the pre-launch stage at the time of writing, but I was able to test a beta version of it with good results.

Getting from the schematic to a rat's nest was very easy, the rat's nest being generated in linear fashion, as shown in Fig. 3 This is step in the right direction, away from rat's-nest 'heaps' that have to be separated manually, but not as quick or easy to re-arrange as the systems used in *Ranger2*, *Propak* or *Traxmaker*.

I discovered that it was possible to 'lose' small components behind large-width rat lines. Sorting out the rat's nest required some care as it is possible to disturb the ratlines when pick-

ing components

The standard autorouter is very easy to operate, has only a few pre-run configuration controls, and was unable to route the test circuit completely, see Fig. 5. This puts it in category C. The new AR3 autorouter was able to route the test circuit, putting it in category A, as shown in Fig. 6.

Note that the version of AR3 that I tested could not route all sizes of track, so those shown in Fig. 6 are thin. It is a gridded autorouter with rip-up-and-retry added to its strategy bank. It also has increased configurability; each net can, if required, be configured individually. This autorouter has considerable potential.

Summary

Quickroute 35 is probably the most intuitive of the integrated schematic-drawing and autorouter products. However, do not think you can get away with not reading the manual from cover to cover – you can't.

Being comparatively easy to learn, *QR35* will be attractive to those seeking a less fraught introduction to pcb cad, to educationalists, or to those who design pcbs only occasionally.



The relative simplicity of *QR35* has its drawbacks. Professional designers – those designing pcbs for a living – may quickly reach the limits of *Quickroute 3.5* and may be frustrated by its lack of certain features. For example it would benefit from the addition of orthogonal drawing and inhibition of incorrect lines in the schematic program, and autosave. The standard autorouter is limited in power and ability.

However, *Quickroute* is being developed further, with a policy of responding to users' comments, so this observation may not apply for very long. For example, from what I have seen of the new AR3 autorouter, this will be both powerful and versatile.

The most attractive feature of *QR35* is the excellent library presentation – quite the best of this set of reviews – while the extended library pack included with both *PRO+* and *PRO* versions gives better than average coverage of most of the commonly used components.

Fig. 8. For comparison, one page from the latest version of *Quickroute*.

Fig. 7. One page from the early dos version of *Quickroute* showing even then the library presentation was exceptionally good. Note the single button bar and large available screen area for drawing.

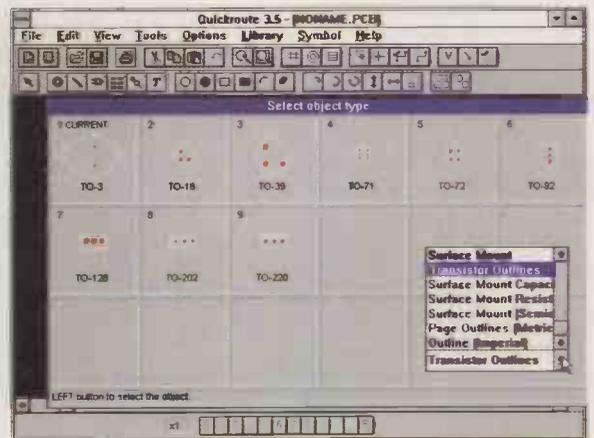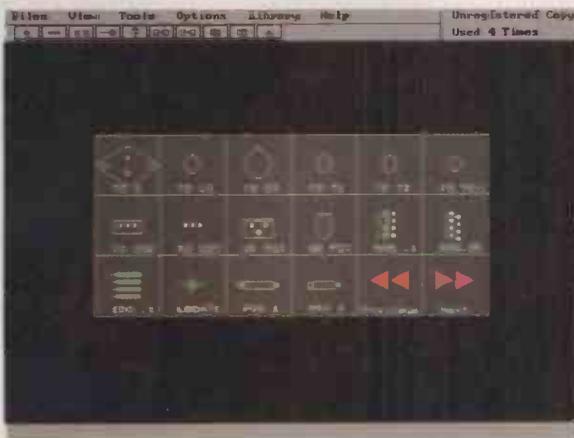

Review 2 – Propak

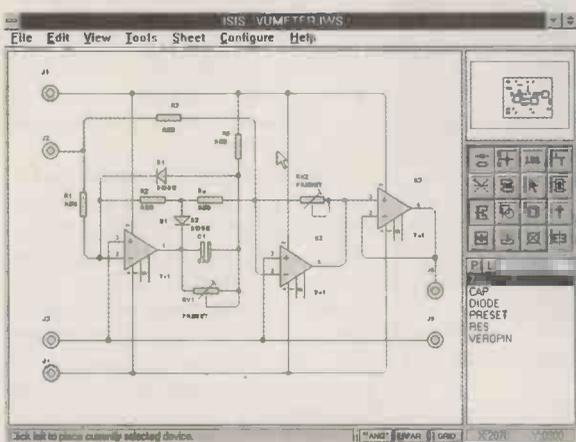


Fig. 9. Typical Propak schematic screen. Note 'map' at top right corner, icon box and parts bin. Any prompts appear on the bottom left of the screen.

There are two parts to Propak, which are integrated and both run under Windows. *Isis Illustrator+* is the schematic drawing and capture part of this program. It runs on a 386 pc running Windows 3.1 with 2Mbyte of ram, but more memory than this is recommended in the manual. It was not satisfactory on a 286 with 2Mbyte of ram.

Ares – the pcb routing part – is a full 32-bit application, so will work best on Windows 95 or Windows NT. However, it will also work with Windows 3.1 and the WIN32S extension that most readers will be familiar with.

Propak is supplied with WIN32S. I installed the whole package on a 386SX running at 20MHz, at first with 4Mbyte of ram. I thought this would be a reasonable minimum set-up for this type of Windows program as the handbook is not clear about the hardware requirements for *Ares*. Although it ran, I soon increased the ram to 8Mbyte to get it to run to my satisfaction. Needless to say, on the 486, it ran very quickly.

The manual for *Propak* is contained in a single volume with individual sections for *Isis* and *Ares*, emphasising the two-part nature of the product. For such a multi-featured program the manual is relatively short and to the point. It assumes a slightly higher level of knowledge of cad and computer literacy than the other programs and does not go into basics much, but this should not trouble most of the designers that *Propak* is aimed at.

Isis has a non-standard Windows format which gives a drawing area of 7.5in by 6in on a 14in moni, which is not very large. There is a menu bar at the top, but an icon area in a box to the right of the screen, see Fig. 9, replaces the customary Windows button bar.

Some of the icons are mode select buttons, which lead to groups of other buttons controlling graphics, symbols, pins etc. All these buttons are in a similar style and I found it very difficult to remember which were which. I only solved this by pinning an icon explanation chart next to the monitor, reminiscent of a practice common in dos.

Although there is a small icon text reference,

it is at the bottom left of the screen – i.e. nowhere near the icons; *Labcenter* could improve this system by adopting pop-up help, like the other Windows packages, or re-organising the system into a standard Windows button bar, or better still, doing both.

Isis is a sophisticated program with automatic junction dots, adjustable autosave, auto name generation and a component finder – handy for very large schematics. It also has a type of autopan, and many other worthwhile features, some of which distance it considerably from other drawing programs.

Most noteworthy of these is the 'wire autorouter', or WAR, which enables drawing to be speeded up by putting in the drawn connections between symbols automatically. You just click on the pins you want to connect and the autorouter inserts an orthogonally drawn line, putting in corners as required.

I timed myself on transferring a drawing from a rough sketch on paper and found it cut down the transfer time by about 30%. As the drawing fills up, and lines get more difficult to place, WAR gets slower just like a human operator, but it's still quicker than hand drawing. The results with WAR depend very much on the component layout, so if you need to present a good-looking schematic you may need to do some editing. Its chief advantage lies in speed.

Also of note is support for radiused corners, and this can give the drawing a smooth professional appearance if this is what you require. The ability to move component text – i.e. text such as R2, 100k, C5 etc – independently of the component also assists in making the schematic look neat and compact. Text stays upright during component editing.

The schematic drawing section is not orthogonal, but maintaining a neat diagram seemed easy due to the good snap-to system. Drawn lines can only be placed between pins; incorrectly drawn lines are inhibited just like *Ranger2* so you cannot accidentally hang lines in space etc. In this way, positive connectivity of pins is assured.

The small 's' that appears

when you are in within drawing range of a pin is of great assistance, and is comparable to *Circuitmaker's* SmartWire method. Snap-to distance can be set to suit yourself and I suggest it is one of first parameters to set before starting drawing in *Isis*. It is tempting with the 's' system to set the snap distance too small, as I did, to get more circuitry into a small screen, but then you will need to maintain a constant high level of concentration to draw. It then too easy to miss a connection and engage some other function with the mouse button. Increasing the snap distance solves this.

Another good feature is the electrical rules check – an automatic check for simple errors in design. I suppose everyone has made an embarrassing error like leaving an output pin disconnected at some time or other, only to discover it after making the pcb. If you are prone to such errors, this feature will definitely be of interest.

The sheet size can be varied from A4 to A1, and *Isis* supports multi-sheet designs in an interesting hierarchy of root sheets, which should contain the core of the design, and sub-sheets, containing peripheral designs. This could be useful for large schematics such as an active filter stereo audio amplifier: The left and right preamplifiers could be drawn on two root sheets, and three or more identical power amps per channel handling the high, medium and low frequencies, drawn on sub-sheets. Any circuit changes to one sub-sheet could then be automatically replicated in the others, a big saving in effort.

Visiting the library

Access to libraries was easy, and parts are transferred in the logical way, to the parts bin first, not to screen.. Note that in *Isis*, the parts bin is called the object selector.

Isis gives you a good graphical representation of the component before it goes to the parts bin. In most other programs, the libraries contain long lists of components. All the electrical and package information is included with each one and when you select a specific

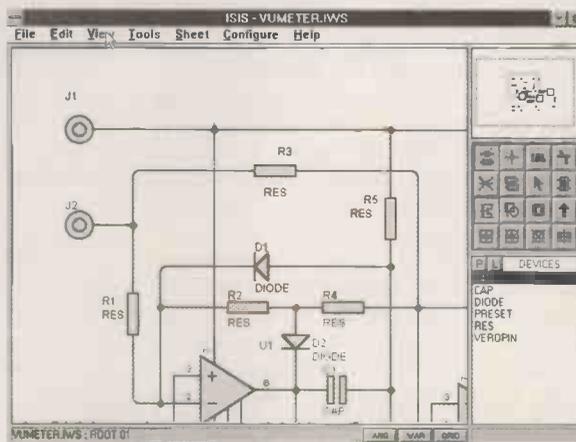


Fig. 10. Enlarged schematic showing graphics quality.

component, say a *BC108* transistor all this information is transferred with it to the netlist when the schematic is captured.

In *Isis*, the libraries are much shorter. There are indeed library volumes for analogue and digital ICs with transferable package information, but only generic library volumes for discrete components such as transistors, thyristors etc. When you select such a generic component, the package outline has to be selected manually from a drop-down menu at the ratsnest stage. So a transistor like the *BC108* is represented by the generic n-p-n transistor symbol in *Isis*. It could in theory exist in any package from TO3 to TO92 at this point. The package information is entered later manually from the package selector as TO18.

The benefit of this arrangement appears to be much shorter and more accessible libraries. They will not be full of devices you never use, but it does mean an extra step to be done later. However, if you are moderately computer literate there is a system in *Isis* which can be set up to do this automatically. This is called 'Ascii Data Import', or ADI, and it means getting out the data books and entering in your most-used devices in a simple table in text in a file called Package.ADI. You can use Window's Notebook accessory to do this.

If you set up such a library, my strong advice is to copy it immediately so that your painstaking work will not be lost if your hard disk takes a holiday. When this file is activated on any specific schematic you have drawn, the outline for each device in *Isis* is then automatically provided for *Ares* to use.

I suggest that you try the two systems from the evaluation programs and compare both methods. It would be a good idea for *Labcenter* to provide as an optional extra some ready-made extended library packs like other makers, for busy engineers who do not have the time to sort out their own libraries.

The zoom control in *Isis* is easy to use, with seven levels, so is the autopan. Like other programs the zoom is a coarse control, but there is a custom zoom feature, and I found it very useful for making a schematic fill the screen. A map at the top right of the screen – called the 'overview window' by *Labcenter* – shows you where you are on the drawing area and assists in panning and finding lost drawings.

Generating a net list is also straightforward and can be in several formats besides *Labcenter's* own SDF format – including *Tango*, *Spice* and *Futurenet*. I tried connecting to a third party simulator with the *Spice* net list and it was both easy and successful.

Although *Isis* and *Ares* are separate entities, the transfer of the schematic net list to *Ares* is painless; one click generates the netlist and triggers *Ares*, so the connection between the two for all practical purposes is seamless.

The *Ares* pcb layout format is very similar to the *Isis* schematic format and if you master one then the other will come easily. There are of course a few alterations as you would expect,

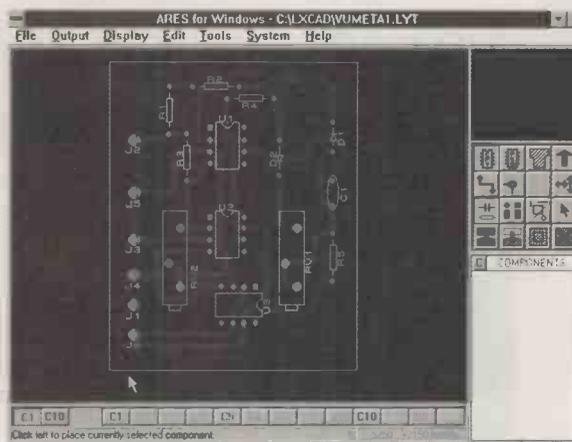


Fig. 11. Results of the *Ares* autorouter. Note the necked track at U1 putting this autorouter in category B.

but these are minor.

Ares consists of two parts – a manual drawing program and an autorouter. The manual drawing part can be used on a ratsnest generated from *Isis*, or you can, if you wish, start from scratch in *Ares* and put the package outlines on the board manually, and then connect the traces. However, the latter would be a waste of *Ares's* resources.

If you start with a net list from *Isis*, the first thing to do is to position the parts on the board. This is done in a way similar to *Ranger2*, and is a good system. The parts are selected and placed one at a time from a parts bin, or 'Object Selector', in the desired position. The rat's nest can then be automatically generated with a couple of clicks in the 'Tools' menu.

Manual routing from the rat's nest is accomplished by selecting a track size, and clicking on a component pad to start the track and tracing the track as you would in any manual system. When the far component is reached, clicking on a pad will complete the track.

There is no rubber-banding. You draw the track as you would normally in any manual pcb program. For some, this will be a most welcome feature. The rat line stays in place until the track is fully drawn, showing you the

Propak but cheaper

A similar package to *Propak* is produced by the same company in dos for about £100 less. The screen layout is in the same style and the control methods much the same.

Unless you are a hardened, blinkered Windows addict, this alternative is well worth considering, especially if your pc will not handle *Propak* for Windows.

A notable feature of this Dos version is that it overcomes the Dos memory barrier by using Expanded memory. Even if you have no expanded memory, it can be simulated from extended memory using software. MSDOS 6 for example has a facility for doing this.

target pad for your track. Only when you complete the track does the rat line disappear.

If you make an error, on erasing the track the rat line re-appears, and you can re-draw the track. This is an excellent system, and for manual drawing from schematic capture it is the program I would recommend from those reviewed.

There is support for curved tracks, autonecking, and auto via placement. Also of interest is the plotter driver, which avoids complete reliance on the Windows plotter driver. The Windows driver is only used to draw straight lines, and *Ares's* own plotter driver does the rest. This speaks volumes about the plotter driver provided in Windows 3.1.

The autorouter is moderately configurable, easy to set up and was comparatively quick. It is not a rip-up-and-retry or push-and-shove autorouter, so it would be unreasonable to expect too much of it. It worked best, as you would expect, on double-sided boards, but as the autorouter test shows, it could do a reasonable job on single-sided boards as well, falling into category B.

Summary

I spent more than the allotted time on assessing *Propak* and even then was still discovering interesting features tucked away in the program.

Isis would suit the professional designer who regularly uses it, particularly if large multi-sheet or multi-layer boards are involved. The user is unlikely to become frustrated by quickly reaching the limits of the system as it is a fully featured, sophisticated program. By the same token, anyone not using the package regularly will find the steep re-learning curve an obstacle after an absence from use.

On small boards, *Propak* would be a sledgehammer to crack a nut. For presentation of a schematic drawing, where appearance was important, *Isis* would be my choice from the programs reviewed.

The *Ares* part of the product is of particular interest to those who wish to avoid rubber-banding when manual routing from a rat's nest. It is the only schematic-capture type of manual drawing program I recommend.

The benefit of using schematic capture and then manual drawing is that you can use the built-in connectivity check to verify that your handiwork corresponds to the netlist and as a result, the schematic you have drawn. With this system it is difficult to make an unusable pcb.

For double-sided boards that are not too dense or complex, the autorouter will usually be satisfactory provided you are prepared to put some time and effort into sorting the ratsnest. For single-sided boards some manual editing or reducing of the design rules may be needed. ■

80C188EB Embedded CPU Card

From
£99



- 80C188EB Processor Clocked at 24Mhz
- 128k Battery Backed RAM (512k option)
- 128k Eprom (32k - 512k options)
 - 128k 5 volt Flash Eprom (512k option)
- Real Time Clock (On board Battery)
- Watchdog Timer/Reset with Brownout detection
- 2 Serial Ports - 1 RS232, 1 RS232/422/485
- 8 Channel 12 bit ADC (optional)
- Direct Connection to Alphanumeric LCD Display
- 48 Digital I/O lines
- Set-up and Driver routines with Full C Source Code

FAST START - Use our Full ANSI compatible Embedded C Compiler for super fast application development. Supplied complete with Editor, Compiler, Assembler, Linker, Embedded Debug and comprehensive Manual, you can compile and download and be in the Debugger with a single keypress - or back in the editor at just the right place. Generate ROMable Code direct, no struggling with .EXE conversions or messing around with reset code. Just £595.

For further information

Call now - 01379 644285 - Fax 650482

Please ask for our catalogue

Devantech Ltd - 2B/2C Gilray Road - Diss - Norfolk - IP22 3EU

CIRCLE NO. 118 ON REPLY CARD

The MICRO MODULE A NEW LOW COST controller that gives you customisation for as little as **£95** one off + VAT

**For users of
PCs, 8051 &
68000**

and that's just the half of it!..

FEATURES

- 16/32 bit 68307 CPU for fast operation
- Up to 1 Mbyte of EPROM space onboard
- Up to 512Kbyte SRAM space onboard
- 32 Kbyte SRAM fitted as standard
- RS232 serial with RS485 option
- MODBUS & other protocols supported
- Up to 22 digital I/O channels
- 2 timer/counter/match registers
- I²C port or Mbus & Watch dog facilities
- Large Proto-typing area for user circuits
- Up to 5 chip selects available
- Program in C, C++, Modula-2 & Assembler
- Real Time multitasking Operating System
- OS9 or MINOS with free run time license option
- Manufacturing available even in low volumes
- A full range of other Controllers available

P.C. 'C' STARTER PACK AT ONLY £295 + VAT

The Micro Module will reduce development time for quick turnaround products/projects and with the P.C. 'C' Starter pack allow you to start coding your application immediately, all drivers and libraries are supplied as standard along with MINOS the real time operating system all ready to run from power on.

The 'C' Starter pack includes: A Micro Module with 128 Kbyte SRAM, PSU, Cables, Manuals, C compiler, Debug monitor ROM, Terminal program, Downloader, a single copy of MINOS. Extensive example software, and free unlimited technical support all for £295 + VAT.



**Cambridge Microprocessor
Systems Limited**

Unit 17-18, Zone 'D', Chalmers Road Ind. Est.,
Great Dunmow, Essex, U.K. CM6 1XG
Phone 01371 875644 Fax 01371 876077

CIRCLE NO. 119 ON REPLY CARD


Finally an upgradeable PCB CAD system to suit any budget ...

Board Capture

BoardCapture - Schematic Capture

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

£395

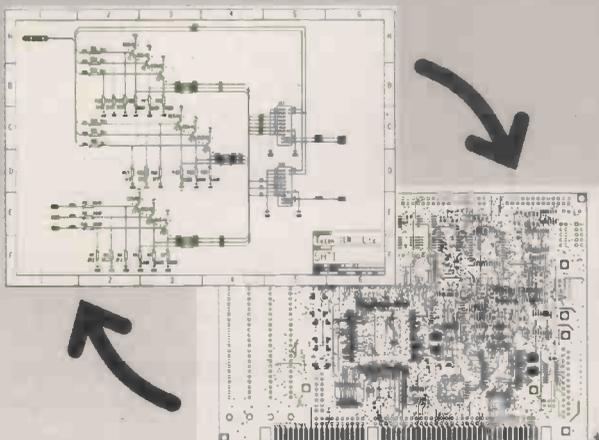

BoardMaker

BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

£95

BoardMaker2 - Advanced level

- All the features of BoardMaker1 plus
- Full netlist support - OrCad, Schema, Tango, CadStar
- Full Design Rule Checking - mechanical & electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC

£395

BoardRouter

BoardRouter - Gridless autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

£200

Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec, Roland & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill / Annotated drill drawings (BM2)

Contact Tsien for further
information on
Tel 01354 695959
Fax 01354 695957



tsien

Tsien (UK) Ltd Aylesby House Wenny Road Chatteris Cambridge PE16 6UT

CIRCLE NO. 120 ON REPLY CARD

New from Crossware

ANSI C for Embedded Development

Our new range of Professional Standard C compilers protect your investment by conforming to the ANSI specification. In addition our target specific extensions will help you get the best from your embedded system.

68000

68020/CPU32

8051

To find out more about this new range of products, call us today or visit our Website.

Distributors Wanted Worldwide!

<http://www.crossware.com>

Crossware Products
St John's Innovation Centre, Cowley Road, Cambridge, CB4 4WS, UK
Tel: + 44 (0) 1223 421263, Fax: + 44 (0) 1223 421006
E-mail: sales@crossware.com



CIRCLE NO. 121 ON REPLY CARD

New Special Offers

| | |
|---|--|
| New mini waterproof TV camera 40x40x15mm requires 10 to 20 volts at 120mA with composite video output (to feed into a video or a TV with a SCART plug) it has a high resolution of 450 TV lines Vertical and 300 TV lines horizontal, electronic auto iris for nearly dark (1 LUX) to bright sunlight operation and a pinhole lens with a 92 degree field of view, it focuses down to a few CM. It is fitted with a 3 wire lead (12v in gnd and video out)..... | £95.57 + VAT = £109.95 or 10+ £89.92 + VAT = £104.95 |
| High quality stepping motor kits (all including stepping motors) 'Comstep' independent control of 2 stepping motors by PC (Via the parallel port) with 2 motors and software..... | Kit £67.00 Ready built £99.00 |
| Software support and digital inputs kit..... | £27.00 |
| Power interface 4A kit..... | £36.00 |
| Power interface 8A kit..... | £46.00 |
| Stepper kit 4 (manual control) includes 200 step stepping motor and control circuit..... | £23.00 |
| Hand held transistor analyser it tells you which lead is the base, the collector and emitter and if it is NPN or PNP of faulty..... | £35.45 |
| spare 6v battery..... | £11.20 |
| LEDs 3mm or 5mm red or green..... | 7p each yellow 11p |
| each cable ties 1p each £5.95 per 1000, £49.50 per 10,000 | |
| Rechargeable Batteries | |
| AA (HPT) 500mAh..... | £0.99 |
| AA 700mAh..... | £1.75 |
| C2AH with solder tags..... | £3.60 |
| D4AH with solder tags..... | £4.95 |
| I2AA with solder tags..... | £2.50 |
| 1/3 AA with tags (Philips CTV)..... | £1.95 |
| 180mAh..... | £1.75 |
| Standard charger charges 4 AA cells in 5 hours or 4 Cs or Ds in 12-14 hours + 1xPP3 (1, 2, 3 or 4 cells may be charged at a time)..... | £5.95 |
| High power charger as above but charges the Cs and Ds in 5 hours, AAs, Cs and Ds must be charged in 2s or 4s..... | £10.95 |
| Nickel Metal Hydride AA cells high capacity with no memory. If charged at 100mA and discharged at 250mA or less 1100mAh capacity (lower capacity for high discharge rates)..... | £3.75 |
| Special offers, please check for availability..... | |
| Stick of 4 4x2x15mm Nicad batteries 171x16mm dia with red & black leads 4.8v..... | £5.95 |
| 5 button cell 6V 280mAh battery with wires (Varia 5x250K)..... | £2.45 |
| Shaded pole motor 240V AC 5mm x 20mm shaft 80x60x55mm excluding the shaft £4.95 each | |
| 115v AC 80v DC motor 1/2 2mm shaft 50mm dia x 60 long body (excluding the shaft) it has a replaceable the fuse and brushes..... | £4.95 each (£5.95 100+) |
| 7 segment common anode led display 12mm..... | £0.45 |
| LM557k TO3 case variable regulator..... | £1.95 |
| | £1.41 100+ |
| GAs FET low leakage current 58873..... | £12.95 each |
| | £9.95 10+ |
| | £7.95 100+ |
| RS250 P channel mosfet..... | £3.95 per 100 |
| BC547A transistor..... | 20 for £1.00 |
| 74LS05 hex inverter..... | £10.00 per 100 |
| Used 8748 Microcontroller..... | £3.50 |
| SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet V12P5 12v in 5v | £1.95 |
| DC-DC converter Reliability model V12P5 12v in 5v 200ma out 300v input to output Isolation with data..... | £4.95 each or pack of 10 £39.50 |
| Hour counter used 7 digit 240v AC 50Hz..... | £1.45 |
| QWERTY keyboard 58 key good quality switches new..... | £6.00 |
| Airpac AB2903-C large stepping motor 14v 7.5' step 270mm 68mm dia body 6.5mm shaft..... | £8.95 or £200.00 for a box of 30 |
| Polyester capacitors box type 22.5mm lead pitch 0.9uf 250vdc..... | 18p each |
| 14p...100+ 9p...1000+..... | 14p...100+ 9p...1000+ |
| 1uf 250vdc..... | 20p each |
| 15p...100+ 10p...1000+..... | 15p...100+ 10p...1000+ |
| 1uf 50v bipolar electrolytic axial leads..... | 15p each |
| 0.22uf 250v polyester axial leads..... | 7.5p 100+ |
| 7.5p 100+ | |
| Polypropylene 1uf 400vdc (Wima MKP10) 27.5mm pitch 32x29x17mm case..... | 75p each |
| 60p 100+ | |
| Philips 123 series solid aluminium axial leads - 55uf 10v & 2.2uf 40v..... | 40p each |
| 25p 100+ | |
| Philips 108 series long life 22uf 65v axial..... | 30p each |
| 15p 1000+ | |
| Multilayer AVX ceramic capacitors all 5mm pitch 100v 100pf, 150pf, 220pf, 10,000pf (10n)..... | 25p 100+ |
| 10p...100+ 5p...100+ 3.5p...1000+..... | 10p...100+ 5p...100+ 3.5p...1000+ |
| 500pf compression trimmer..... | 60p |
| 40 of 370vac motor start capacitor (dielectric type containing no pcb)..... | £138.00 for 6 |
| Solid carbon resistors very low inductance ideal for RF circuits - 270m 2W, 680m 2W..... | 25p each |
| 15p each 100+ | |
| We have a range of 0.25w, 0.5w, 1w and 2w solid carbon resistors, please send SAE for list | |
| P.C. 400W PSU (Imel part 201035-001) with standard motherboard and 5 disk drive connectors, fan and mains inlet/outlet connectors on back and switch on the side (top for tower case) dims 212x149x149mm excluding switch..... | £26.00 each |
| £138.00 for 6 | |
| MX180 Digital multimeter 17 ranges 1000vdc 750vac 2Mohm 200mA transistor Hfe 9v and 1.5v battery test..... | £9.95 |
| AMD 27256-3 Eproms..... | £2.00 each £1.25 100+ |
| DIP switch 3PCO 12 pin (ERG SDC-3-023)..... | 60p each |
| 40p 100+ | |
| Disk drive boxes for 5.25 disk drive with room for a power supply, light grey plastic, 67x268x247mm | |
| Hand held ultrasonic remote control..... | £7.95 or £49.50 for 10 |
| CV2486 ga relay, 30x10mm dia with 3 wire terminals, will also work as a neon light..... | £7.50 per 100 |
| Verbatim R3000NH Streamer tape commonly used on machines and printing presses etc. It looks like a normal cassette with a slot out of the top..... | £4.95 ea. |
| £3.75 100+ | |
| Heatsink compound tube..... | £0.95 |
| HV3-2405-E5-24v 50mA regulator ic 18-264vac input 8 pin DIL package..... | £3.49 each 100+ £2.25 |
| LM 555 timer ic 16p..... | 8 pin DIL socket 6p |

All products advertised are new and unused unless otherwise stated. Wide range of CMOS TTL 74HC 74F Linear Transistors kits. Rechargeable batteries, capacitors, tools etc always in stock. Please add £1.95 towards p&p. VAT included in all prices.

JPG Electronics, 276-278 Chatsworth Road, Chesterfield S40 2BH
Access/Visa Orders (01246) 211202 Fax: 550959
callers welcome 9.30am to 5.30pm Monday to Saturday

CIRCLE NO. 122 ON REPLY CARD


Get out of a pickle - get into SpiceAge!

Hands up all who have been there? A great idea turns into sleepless nights: getting one thing right breaks something else...

Some circuits require the refining of many interdependent variables. SpiceAge provides a virtually limitless inventory of components, signal functions and instruments with facilities for sweeping values, with am and fm through arbitrary functions. It can guide you to a solution that could take much longer to find using hardware.


SpiceAge up your design without burning a hole in your pocket. Prices from just £85 + VAT to £695 + VAT. Friendly technical help comes free (dreadful puns optional). For a demonstration kit and details of our other and third party support programs (includes schematics, PCB layout, filter synthesis and model synthesis), please contact:

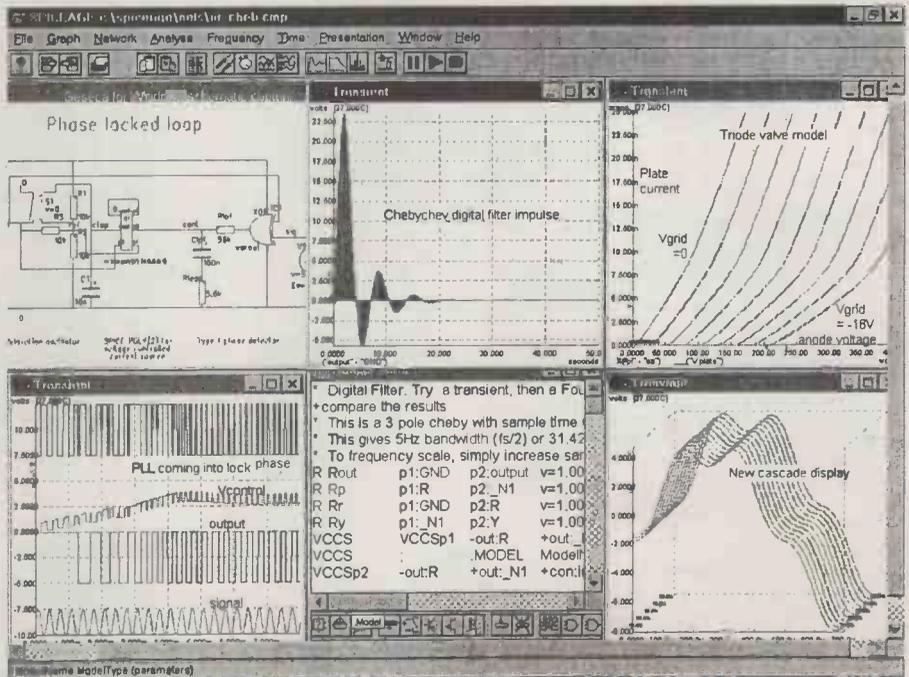Charles Clarke at Those Engineers Ltd, 31 Birkbeck Road, LONDON NW7 4BP.
Tel: 0181 906 0155 Fax: 0181 906 0969 Email 100550.2455@compuserve.com



CIRCLE NO. 123 ON REPLY CARD

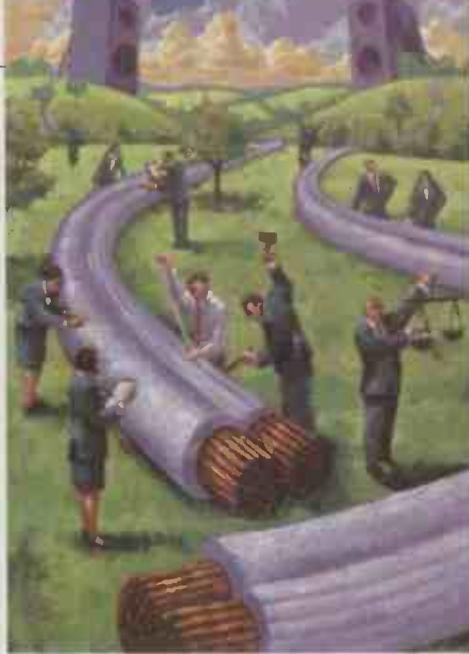Subjectivists claim to hear considerable differences in loudspeaker cable performance, but traditional distortion measurement methods do not bear this out. Cyril Bateman argues that traditional measurement methods are inappropriate.



The claim that loudspeaker cables can and do cause distortions in hi-fi sound reproduction systems has resulted in two schools of thought. One school maintains that this is impossible since these distortions cannot be measured, the other disregards the measurement problem but maintains their ability to hear a different sound with change of cables.

Consequently discussions on these cable distortions have aroused more controversy than almost any other electronics design debate. Mystical diodes, over emphasised skin effect and magical properties of differing materials have all been proffered as reasons to explain these audible distortion effects.

Much of my working life has been spent measuring the s-parameters of anomalous components at all frequencies from dc to 3GHz. As a result, I fully appreciate how important load matching and characteristic impedance of cable or test jigging are – even for extremely short electrical lengths.

I had long assumed that cable characteristic impedance remained important, even at the lengths used for audio. This was confirmed on examining the measured results in Duncan's recent articles^{1,2} and my own 42-strand cable test result.

This article, and a follow up, presents evidence that loudspeaker cables *do* behave as transmission lines and that the cable's characteristic impedance, propagation delay and mismatch behaviour is maintained down to audio frequencies.

I will also show that audible distortion results not from the cable itself, but principally from the amplifier, cable, loudspeaker combination's mismatched impedance. Simple, easily replicated methods involving both measurement and simulation confirm my results.

Hi-fi components interact

Since the combination of amplifier, cable, crossover networks and speakers all interact, speaker cables cannot be properly measured or evaluated in isolation.

Speaker cables

Amplifiers have forward propagation delay around 1 μ s and considerable closed-loop feedback. Cables have characteristic impedance and one way transit delays around 6ns/m, while loudspeakers have extremely wide impedance/phase changes with frequency. Additionally – and perhaps most importantly – a moving-coil loudspeaker generates substantial voltage and current long after its drive signal has ceased, easily observed by physically disturbing a speaker cone.


Conventional distortion measurements are based on a continuous sine wave. Many musical sounds however, those from pianos and cymbals for example, start as a fast transient and decay slowly. This envelope is similar to that of the exponentially-damped waveform included in the *PSpice* simulator. No doubt with electronic synthesisers the converse waveshape having instantaneous turn off, as used by Duncan¹, is also possible. Both transient signals should be evaluated.

Turn-off transient effects

Since badly matched or undamped loudspeakers generate a back emf into the amplifier,³ my first test, which approximates to Duncan's, involved two amplifiers. These were configured back-to-back, but separated by the test cable and a load-sensitive voltage drive circuit.

One amplifier was driven at 10kHz by a signal generator. The test amplifier input was earthed via a 4.7k Ω resistor and both amplifiers were powered. The drive circuit was resonant at 10kHz, and current energised by the driven amplifier. The cable and test amplifier impedance damped the resonating voltage, which undamped attained more than 100V.

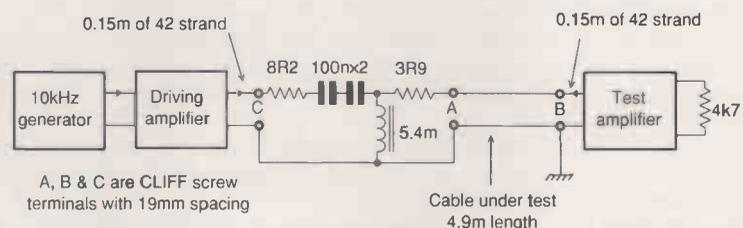I made measurements of various test cables and observed the voltages at both cable ends. Care was taken to space both amplifiers as far apart as permitted by the leads of the two 250MHz scope probes used. The *ADC100* virtual oscilloscope was placed well away from



Test set-up for comparing loudspeaker cables. Channel A of the oscilloscope was connected to terminal A at one end of the cable under test and channel B was connected at the other end, on terminal B.

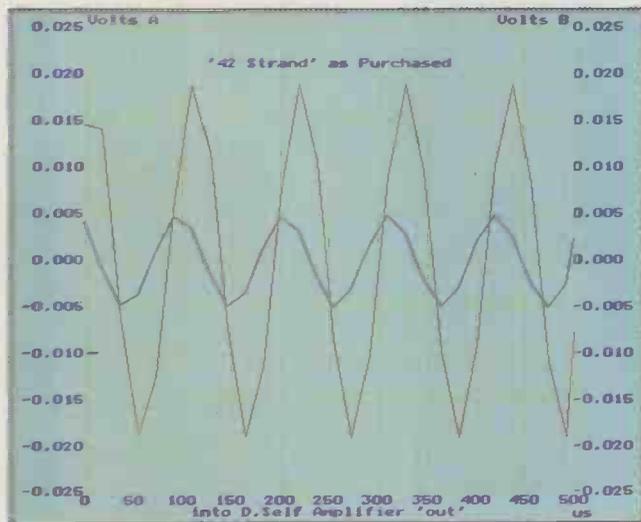


Fig. 1. Measured result of 42-strand as-purchased cable tested via a Douglas Self 50W amplifier.

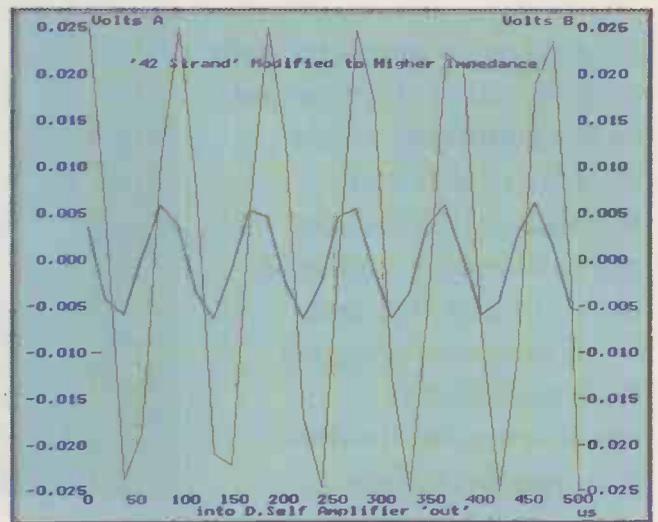


Fig. 2. Measured result of 42-strand cable modified to higher impedance using Douglas Self's test amplifier. Comparison with Fig. 1 clearly shows importance of the cable's characteristic impedance.

the computer to minimise stray pickup and the test cables were dressed in air in a wide U shape, similar to that used by Duncan. To avoid earth loops when using the ADC100, the scope probes were earthed to a single point at the test amplifier end of the test cable.

In each case, the driving amplifier was a low-cost mosfet design from Maplin (part No LP56L). I also carried out tests using Douglas Self's 'Blameless' class B⁴ as the driven amplifier. It was built with better than 1% metal film resistors and matched semiconductor pairs. This was unhappy with less than 4.7kΩ input shorting impedance. Also, at 10kHz it had a somewhat higher output impedance than the mosfet design.

Since much debate has centred on the effects of the cable's resistance, inductance and capacitance, I bought a variety of readily available cables, all cut to 4.9m long. These represented a mix of known and unknown impedance and resistance, in both coaxial and figure-of-eight constructions. They ranged in style and cost from Duncan's bell wire to Jenving *Supra Ply 2.0* constructions.

This mix of cable structures was deliberate; simple examination of their impedance equations confirms that low impedance cabling with both minimal inductance and minimal

Transmission lines

Transmission lines cables are made in two main formats each comprising two separated conductors. These formats are coaxial and line pairs.

In both cases, reduced conductor separation reduces series inductance, increases shunt capacitance and reduces the cable's characteristic impedance, Z₀.

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

which, from ref. 7, at high frequencies approximates to,

$$Z_0 = \sqrt{\frac{L}{C}}$$

This characteristic impedance assumes an infinitely long length or a shorter length terminated by this impedance and produces no reflected wave. All other termination impedances (mismatch) produce a reflection which is returned to the source. If both ends are mismatched and the cable has no loss, these reflections continue indefinitely dependant on the degree of mismatch.

At low frequencies, since the inductive reactance is small and capacitive reactance is large, the characteristic impedance can increase. If

R/L=G/C, the special case of a 'distortionless' line, then Z₀ is frequency independent.

Certain constructs can be designed for characteristic impedance by their physical dimensions. For coaxial cable,

$$Z_0 = \frac{138}{\sqrt{\epsilon}} \log \frac{D}{d}$$

where ε is the dielectric constant of the insulator. Capacitance C, also from ref. 7, is,

$$C = \frac{24.16\epsilon}{\log \frac{D}{d}} \text{ pF/m}$$

For the line pair,

$$Z_0 = \frac{276}{\sqrt{\epsilon}} \log \sqrt{\frac{2D}{d} \left(1 + \left(\frac{D}{2H} \right)^2 \right)}$$

where H is height above ground. Capacitance, see ref. 8, is,

$$C = \frac{12.07\epsilon}{\log \frac{2D}{d}} \text{ pF/m}$$

Transmission lines have a propagation delay that depends on length and dielectric materials used. In practice this approximates to 6ns/m for commonly used plastics.

Resonant drive circuit

The resonant circuit comprised a 5.4mH inductor and 50nF capacitor. The inductor was in shunt to ground thus replacing the speaker voice coil, the capacitor was used to feed current from the driven amplifier via an 8.2Ω short circuit protection resistor. A second resistor of 3.9Ω used to simulate the voice coil resistance, was used to feed the inductor's voltage into the test cable and thus into the test amplifier.

Due to the very high unloaded 10kHz voltage and current which the capacitor must sustain, I used two in series 100nF, 400V Siemens polypropylene B32650 (Electrovalue part 50.1400).

The inductor used was a 5.4mH super power low-loss 1mm wire having a Q of 15 at 10kHz, from Falcon Acoustics, Tabor House, Mulbarton, Norwich, contact Malcolm Jones. The two resistors were HSA25 wire wounds.

capacitance, is most easily manufactured using coaxial methods. On the other hand, twin-line or figure-of-eight cable, with its much increased inductance and reduced capacitance, is better suited to higher impedances.

While lowered impedance is possible using twin line, the penalty is a considerable increase of shunt capacitance, as with the *Supra Ply 2.0*.

While series resistance is important, I found the damping of the resonant voltage at the loudspeaker end to depend principally on the cable impedance. To confirm this, I took two equal lengths from a reel of 42-strand and arti-

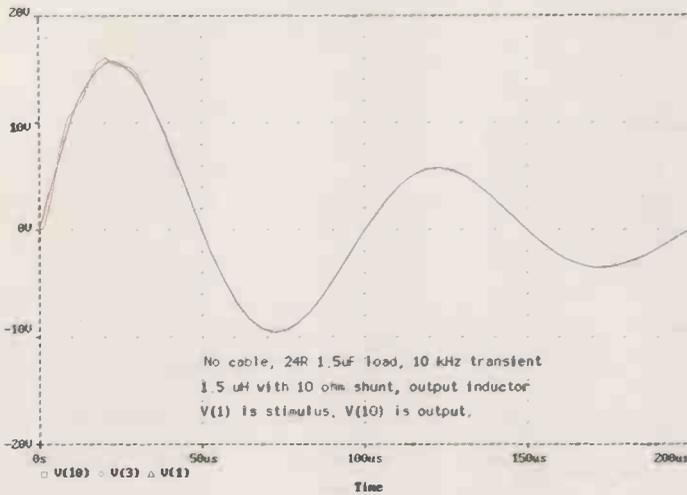


Fig. 3. Simulated behaviour of typical amplifier output configuration when driving into a capacitive and shunt resistor load. Voltage V(1) is taken as the location of the feedback connection.

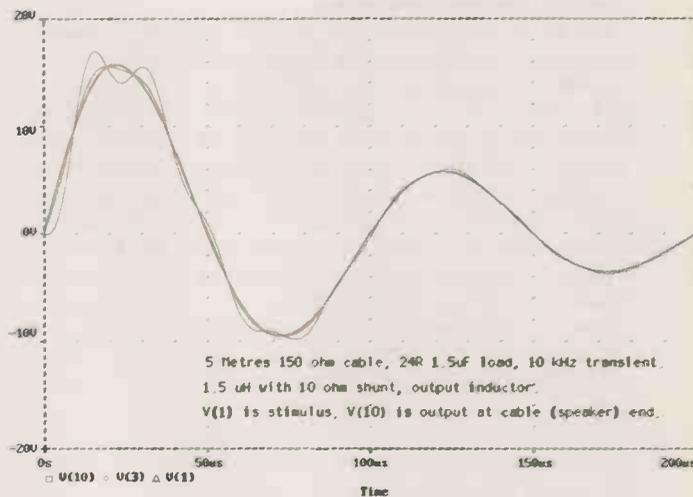


Fig. 4. Simulation of configuration identical to Fig. 3, except for the addition of 5m of high impedance Figure 8 style cable. This distortion should be clearly audible on transients. Voltage V(3) is waveform at amplifier output terminals for all simulations.

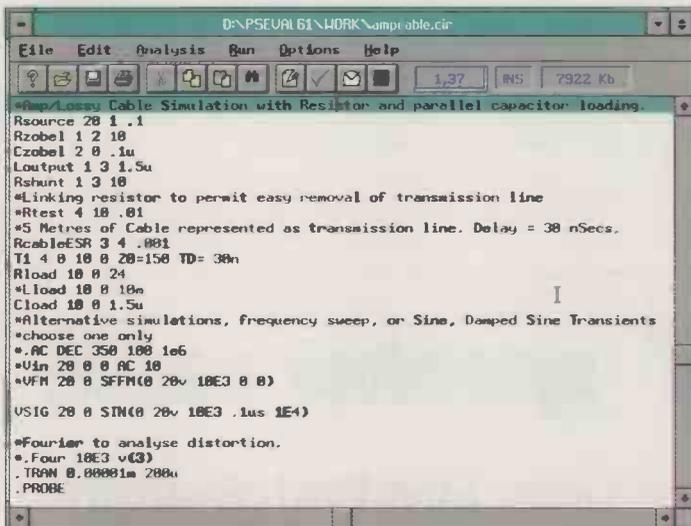


Fig. 5. Basic PSPICE Net-List as used for Figs 3 to 7. This can be simulated using the evaluation version of PSPICE.

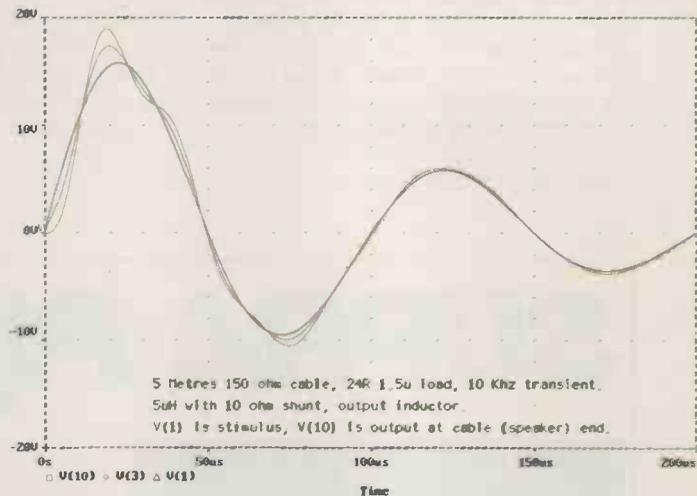


Fig. 6 Simulation of identical configuration as Fig. 3, except for increased value of amplifier output inductor to 5uH. This distortion should be clearly audible on transients.

ficially increased the characteristic impedance of one by unzipping it. This increased its separation to around 8 mm, which was retained by laminating in adhesive tape. In this way, the two cables have identical resistance, but differ in impedance.

While initial measurements used a 100MHz twin-beam scope, the published plots were obtained using the Pico ADC100 computer attachment, recently on special offer in *Electronics World*. With two channels operating, its analogue-to-digital conversion rate is 55 kHz – well above the Nyquist minimum for a 10kHz measurement. Care was also taken to ensure that at least two peaks were measured for both channels in each plot, Figs 1,2.

These results of two different cable impedances but with constant resistance, using only low cost and simply applied techniques,

are similar to those reported by Duncan for his more complex AP test method. These results prove the significance of cable impedance in controlling overhang from the speaker for the bipolar and mosfet amplifiers used.

Slowly decaying transients

Audio power amplifiers are often tested with a load of 8Ω with 1.5 or 2μF in parallel. Continuous sine-wave simulations with and without 5m of a typical figure-of-eight cable show negligible distortion when 'Fourier' transformed. Since distortion of the first cycle was clearly visible however I changed the stimulus to simulate a transient using the exponentially damped sine wave in *PSPICE*. This clearly shows the transient distortion noted, which would be audible within a music program, Fig. 3.

Further simulations to explore this show that

distortion increases with increase of load resistance or output inductor value. Regardless of load resistance however, an inductive load caused smaller distortions, Figs 4, 5, 6.

Predictably these distortions reduced as cable impedance was lowered, even though the shunt resistor remained high. This is because the input impedance of the cable/amplifier combination, now provided the necessary damping, Fig. 7.

Applying the proof

These results prove that cable characteristic impedance is important in audio systems. With this in mind I will now examine Duncan's plots.

In two articles^{1,2} Duncan concentrated on two cables. These were an undefined mains cable and Jenving *Supra Ply 2.0*. Both were tested at 1kHz using an unspecified Tannoy

15in dual-concentric loudspeaker.


In a *Studio Sound* article⁵, he also used an unspecified 15in dual-concentric Tannoy loudspeaker with tests performed at 125Hz, 1kHz, and 15kHz on eight additional cables. Examination of the published test report of Tannoy's *D700* speaker system⁶ indicates that if similar to Duncan's speaker, you could expect impedance of 3.1Ω resistive, 6.5Ω inductive and 5Ω resistive respectively. You could also expect resonant impedance peaks at around 45Hz/7Ω and 2700Hz/20Ω.

From his measurements, these cables have an estimated high frequency impedance of 79.6 and 37.5Ω respectively. At 1kHz, the inductive reactance is reduced and capacitive reactance is increased. Because of this, both impedances will be higher, but making some allowance for this also the missed peak in Fig. 3 for reference 2, cable C, you can see that Duncan's voltage ratios closely follow the mismatch ratios at the speaker end of the line.

These results clearly demonstrate how transients can be distorted in speaker/cable systems while continuous sine waves are not. They could bridge the chasm presently existing between the two opposing schools of thought.

In my next article on this topic, I explore other published test methods. I also look at how all these results pertain to a complete amplifier, cable and speaker system and pro-

Fig. 7. Much reduced distortion resulting from change in cable impedance, otherwise circuit is identical to Fig. 4.

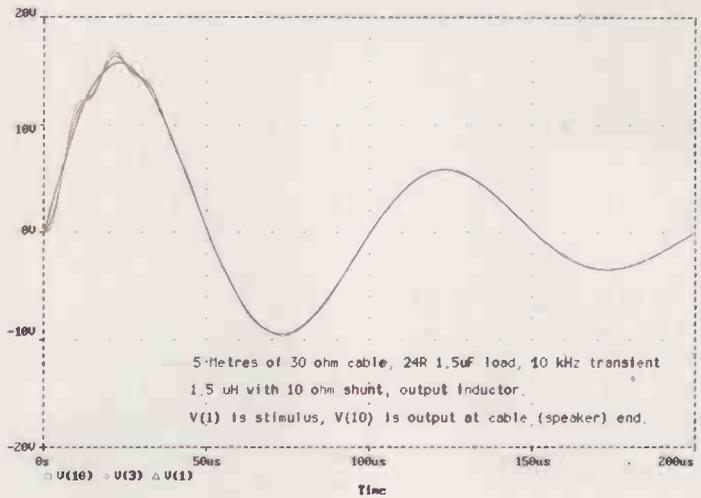

vide all measured results by plots and tables.

I would however ask that anyone wishing to shoot these findings down in flames – first repeat the experiments.


References

1. Duncan, B., Modelling Cable, *Electronics World*, p. 119, Feb. 1996.
2. Duncan, B., Measuring Speaker Cable Differences *Electronics World* July/Aug. 1996.
3. Pass, N., Speaker Cables, Science or Snake Oil,


Speaker Builder, 2/1980

4. Self, D., Distortion in power amplifiers, *EW&WW*, p. 129, Feb. 1994.
5. Duncan, B., The Cable Connection, *Studio Sound*, Dec. 1995
6. Colloms, M., A Big-Hearted Monitor, *HI-FI News*, July 1993.
7. *Reference Data for Radio Engineers*, Howard Sams & Co. Inc.
8. *Royal Signals Handbook of Line Communication*, HMSO.


SUPRA Ply[®] speaker cable

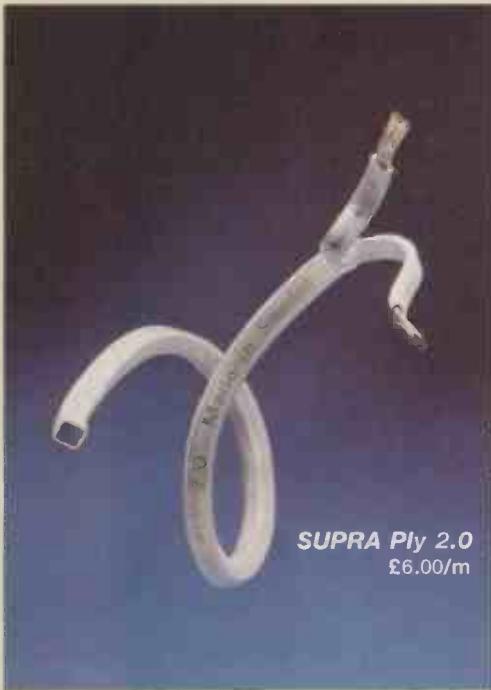

SUPRA Ply 2.0
£6.00/m

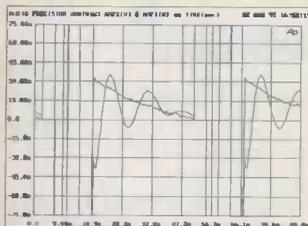

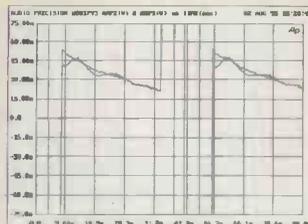Other brand 125Hz
Wavy trace shows poor damping after a transient



SUPRA Ply 125Hz
Superior damping - similar results at all audio frequencies

The test winner!

- Stereophile USA December 1995
- Studio Sound UK December 1995
- Reproduced Sound Conference Nov 1995
- "Speaker cable differences: CASE PROVEN" by Ben Duncan Research.

Low inductance concept, low, benign oxidation
Much faster, tighter damping gives you higher definition and more control. Result: less blur, less listening fatigue. Transient error in a spaced wire or a zip-wire is as much as 1/28th of the immediately preceding signal; our cable design reduces this at least ten times.

The low, benign oxidation is discussed in Ben Duncan's article in *Electronics World*, February 1996: Modelling cable

Please send for our catalog to see our complete range of cables and connectors, for pro and HiFi!

Jenving UK

28 Stonecot Hill, Sutton Surrey SM3 9HE
Tel: 0181 287 4455 Fax: 0181 287 4466

Supra Ply has got a big brother, Ply 3.4 £8.00/m for superior bass sonics

We are cable specialists since 1976 with distribution established in 24 countries

NEW programmers start at only £295



With prices starting as low as £295, ICE Technology's new range of parallel port programmers offers something for every budget. All programmers support dual in line devices directly in the socket - no adapters or modules are needed for any families of devices, providing extensive device coverage at very affordable prices. The full range of programmers is shown in the panel on the right. Our new easy to use device support checklist will help you to choose the programmer that is right for you, just call or use our faxback for a copy. All programmers come with FREE software updates on our BBS or our ftp site, full technical support direct from the manufacturer and one year's guarantee. All models can run from batteries or mains - ideal for use with laptops.

Low cost EPROM programmer

At only £295, the EPMaster LV is a powerful EPROM programmer which offers so much more than other EPROM programmers. With its 40 pin socket it can support all types of EPROMs including 16 bit wide with no need for additional modules. Serial PROMs, Serial EEPROMs, Flash and EEPROMs are all included in the device support at no extra cost. In addition, low voltage parts are fully supported with the programmer's separate 1.8V, 3.3V and 5V logic circuits. EPMaster LV connects to the parallel port of any PC compatible and can be operated from batteries or mains electricity. You can also add a built in ROM/RAM emulator with a capability of up to 512k by 16, turning the EPMaster LV into a powerful development tool.

CIRCLE NO. 162 ON REPLY CARD

High Speed Gang Programming



The Speedmaster GLV-32 Gang/Set programmer offers simultaneous high speed programming for up to 8 EPROMs and Flash (up to 8Mbit) at 3.3V and 5V. The 3.3V facility ensures that programmed devices will work correctly at their nominal operating voltage. Functions include gang programming, set programming and full editing. The Speedmaster GLV32 works in PC or stand alone mode.

CIRCLE NO. 163 ON REPLY CARD

Universal programmer only £525

The Speedmaster 1000+ and Micromaster 1000+ offer new levels of affordability in device programming. At only £395, the Speedmaster 1000+ supports all types of memory devices, plus 8748/51, BPROMs, GALs and erasable PALs. The Micromaster 1000+ at just £525 extends this support to include PALs, EPLDs, MACH, MAX, PSDs and over 180 microcontrollers including PIC,

ST6, MC68HC705, MC68HC711, TMS370, TMS320, 87Cxxx, 89Cxxx, COPs etc. The Micromaster 1000+ can support all device types, even Motorola micros, with NO ADAPTERS or MODULES for any dual in line devices up to and including 40 pins. As with all our programmers free software updates are included via BBS or our ftp site.


CIRCLE NO. 160 ON REPLY CARD



LV40 Portable

Reaching the parts other programmers can't reach

The NEW LV40 Portable stands head and shoulders above other portable programmers with its comprehensive device support which includes EPROMs, EEPROMs, Serial PROMs, BPROMs, Flash, NVRAMs, PSDs, PALs, GALs, PEELs, EPLDs, MACH, MAX and over 180 microcontrollers. Unlike other portables, no adapters or modules are needed for any of these devices up to 40 pins dual in line. With socket adapters the LV40 is capable of supporting devices of over 40 pins and other package types. At £995 for the complete package you'll soon see why the LV40 Portable is the best value, most powerful portable programmer in the world.

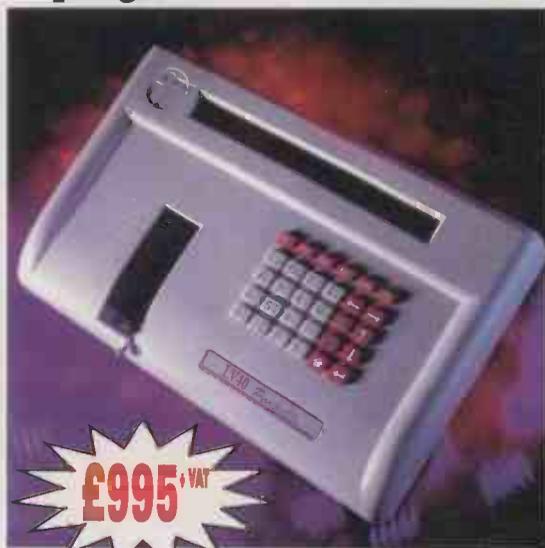

£995^{+VAT}

CIRCLE NO. 161 ON REPLY CARD

- Portable Universal Programmer
- High speed
- PC software included
- No modules to buy
- Supports memory, programmable logic, high density logic, and over 180 micros.
- Support for 1.8, 3.3 and 5V devices
- Battery or Mains operation
- Lifetime free updates

PROGRAMMER MODELS AND PRICES

| LV MODELS (SUPPORT 1.8V, 3.3V and 5V DEVICES) | | SPEEDMASTER 1000+ | EPROMs, EEPROMs, Flash, NVRAMs, Serial PROMs, Serial EEPROMs, BPROMs, GALs, 8748/51 | £395 | |
|--|---|-------------------|---|---|----------|
| EPMASTER LV | EPROMs, EEPROMs, Flash, Serial PROMs, Serial EEPROMs 8 to 40 pins all without adapters. Built in emulator modules: 128k by 8: £395 128k by 16: £465 | £295 | MICROMASTER 1000+ | EPROMs, EEPROMs, NVRAMs, Flash, Serial BPROMs, PALs, GALs, PEELs, MACH, MAX, PSD, over 180 microcontrollers without adapters. | £525 |
| SPEEDMASTER LV | EPROMs, EEPROMs, Flash, NVRAMs, Serial PROMs, Serial EEPROMs, BPROMs, GALs, PALs, EPLDs, MACH, MAX, 8748/51. | £495 | SPEEDMASTER GLV32 | High speed EPROM/Flash 8 way Gang/Set Programmer. Supports 3.3V and 5V | £645 |
| MICROMASTER LV | EPROMs, EEPROMs, NVRAMs, Flash, Serial BPROMs, PALs, GALs, PEELs, MACH, MAX, PSD, over 180 microcontrollers without adapters. | £625 | COP GANG PROGRAMMER | 8 way Gang programmer for National Semiconductor COP family of micros | £1500 |
| LV40 PORTABLE | All devices supported by Micromaster LV, plus completely portable with built in keypad and LCD display. | £995 | SOCKET ADAPTERS | for PLCC, TSOP, QFP, SOIC, SSOP etc. | from £65 |

All prices exclude VAT and delivery

For details on any of our range of programmers, call or fax us now.

You can obtain information immediately by using our faxback service or homepage.

ICE Technology Ltd, Penistone Court, Penistone, South Yorkshire S30 6HG. United Kingdom.


Tel: +44 (0)1226 767404 Fax: +44 (0)1226 370434 Faxback: +44 (0)1226 761844 email: sales@icetech.com

Homepage: <http://www.icetech.com> BBS: +44 (0)1226 761181 (14400 baud, 8N1)



CALL OUR SALES HOTLINE ON 01226 767404 - OR USE OUR FAXBACK FOR FULL DETAILS - 01226 761844

Speaker cables pulse tested

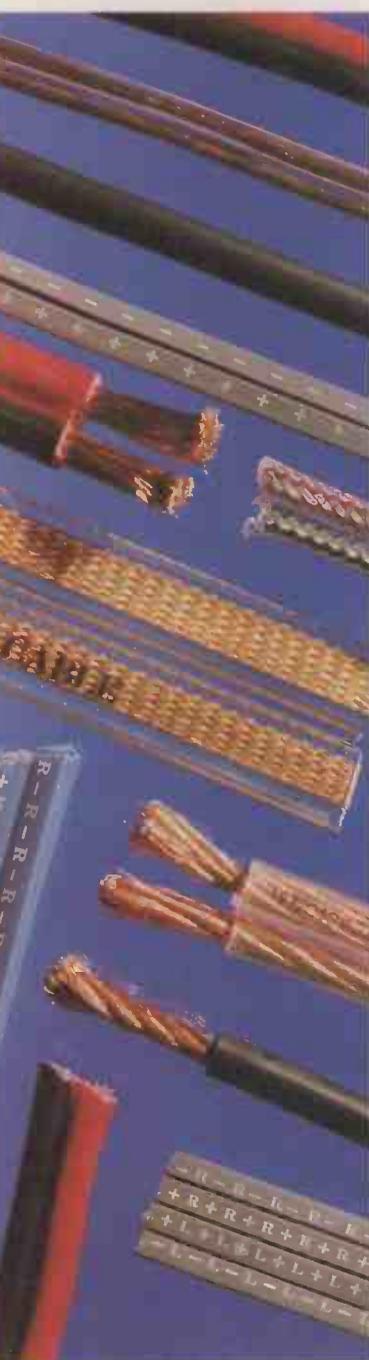


By feeding cables with fast pulses and looking at the resulting waveforms, **Eric Foster** has been able to illustrate clear capacitive, inductive and eddy differences between cables suitable for speaker driving. Sadly for the cable marketers though, these differences are too high in frequency to be audible.

Pulse induction is normally associated with metal detectors. However it can also be used as a unique method of testing loudspeaker cables to determine differences that may relate to audible effects. The measurement waveform takes place after the primary pulse has ceased and is dependent on the cable inductance, capacitance and cross sectional eddy currents. In the system outlined, cable resistance is not of

major significance as the pulse generator impedance is deliberately made high. This is done to limit the power supply current and to keep the test pulse amplitude constant over widely varying cable types and lengths.

Injecting a pulse

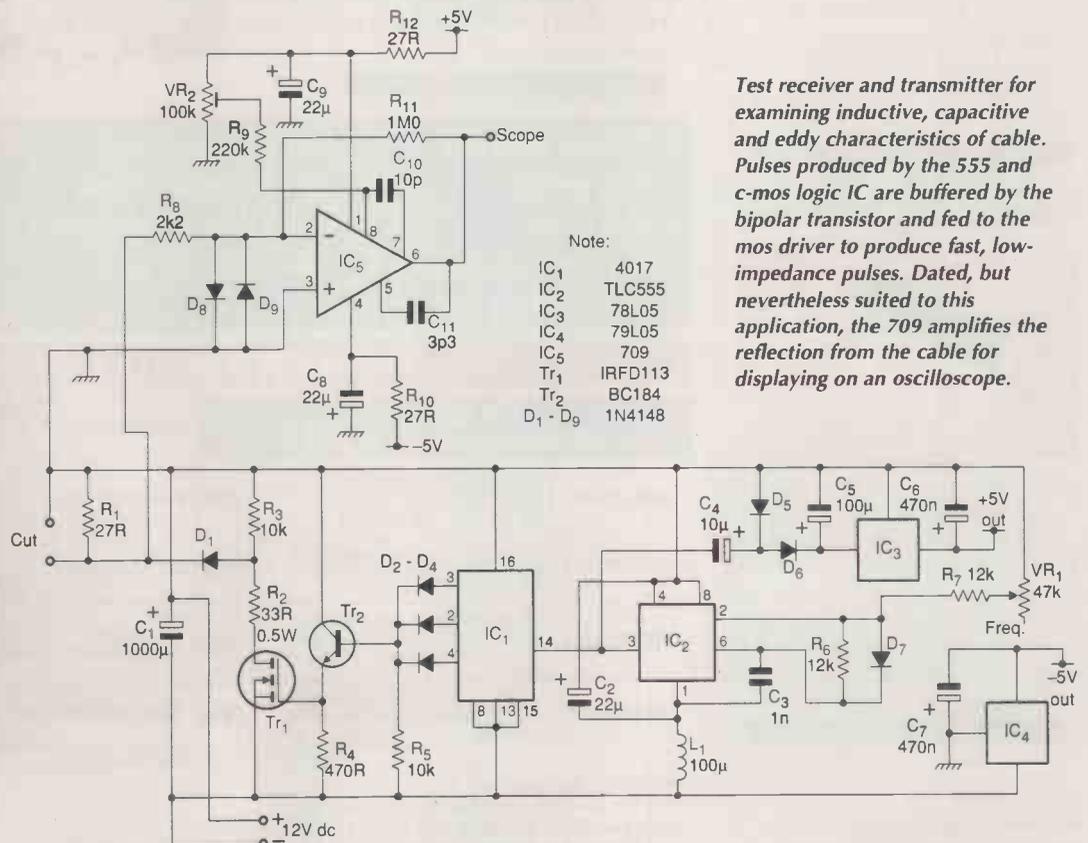The essence of the method is to inject a current pulse into a known length of cable with the far end shorted.



At the termination of the current pulse a wide band op.amp. amplifies any low level decay effects due to induced eddy currents in the wire cross section or to polarisation signals in the insulating material – if they occur.

One metre lengths were chosen as these were easier to obtain, and the measured effect can easily be extrapolated to longer lengths. For the more readily available, and inexpensive, cables such as mains lead and coaxial, 5m lengths were measured in addition to the shorter ones.

This method is unique because the resultant waveform is solely due to the cable under test

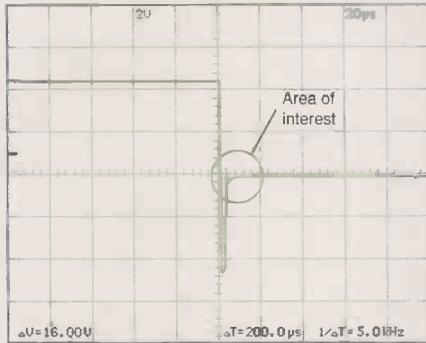


Fig. 1. Output from the 709 op-amp resulting from a test on a 1m length of mains cable. There is an initial positive excursion, followed by a short negative saturation period caused by the cable's reverse emf. This negative transition is the area of interest.

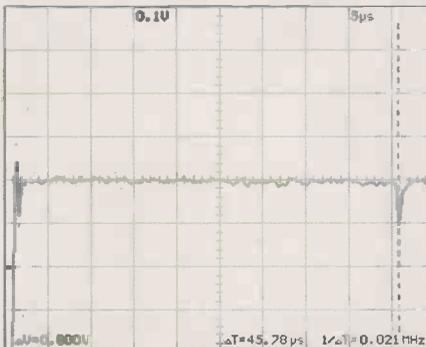


Fig. 2. Reference waveform. The nearer the cable test comes to this shape, the lower the inductance, capacitance and cross-sectional eddy currents.

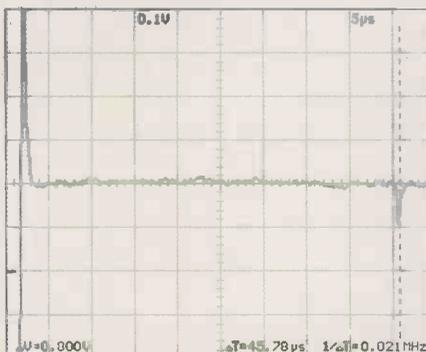


Fig. 3. Shark Wire is inexpensive speaker cable comprising 129 strands of 0.1mm oxygen-free copper.

and is not complicated by speaker impedances, reflections or power amplifier characteristics.

Implementing the test system

Transistor Tr_1 provides the current pulse to the cable via R_2 and D_1 . Resistor R_2 limits the amplitude of the pulse to about 0.36A. This corresponds to the current that would flow for 1W peak in an 8Ω load.

Duration of the pulse can be varied between 50 and 150μs by means of VR_1 and the pulse frequency varies correspondingly between 5kHz and 1.5kHz. In practice, for the cables tested, the pulse duration and frequency had no effect on the recovery waveform as the cable time constants measured were very much faster. Diode D_1 isolates the cable under test from the drain capacitance of Tr_1 after switch off which would otherwise lower the cable's resonant frequency.

Resistor R_1 , across the driven end of the cable, damps out any ringing which is due to the cable-under-test's inductance and self capacitance. Without the damping resistor the ringing frequencies measured in the range 10-20MHz for the 1m lengths. This is well outside the audible band.

Wide band amplifier IC_5 exhibits a gain of 400. Although the 709 is an early IC, dating back to the late 1960s, it has excellent gain, bandwidth and recovery characteristics. These characteristics are difficult to find in more modern ICs. This is no doubt due to its straightforward bipolar architecture.

The cable-under-test's recovery waveform is viewed on an oscilloscope connected to IC_5 output. As IC_5 is wired as an inverting amplifier the cable-under-test waveforms are inverted, but this is of no consequence in demonstrating cable recovery. If you want to pursue this further, you could re-connect IC_5 as a non-inverting amplifier or follow the existing circuit with a fast inverting buffer.

Figure 1 shows the output waveform of the test circuit with a 1m length of two-core mains cable connected as the cable-under-test. Initially, there is a positive excursion of 100μs where the amplifier is driven into saturation by the drive pulse. This is followed by a short negative saturation period caused by the reverse emf generated by the cable's series inductance.

The subsequent plots are triggered by this negative excursion and the circled area of interest magnified.

Reference waveform criteria

To generate a reference waveform, the terminals of the test unit are shorted by soldering them together. The initial negative excursion in this case is the amplified result of the back emf generated in the stray inductance of the pcb tracks associated with Tr_1 and its immediate components.

It is vital to keep this inductance to a minimum, so that the amplifier has returned to a flat baseline in 3-4μs. This constitutes the reference waveform, Fig. 2, with which to compare cable-under-test waveforms.

Cables with low inductance, low capacitance and low cross-sectional eddy currents will depart little from the reference waveform. The negative spike adjacent to the right cursor is a clock generator spike while the ripples and bumps are largely op-amp noise.

The cursor is set at $1/\Delta T$ of 21kHz, which corresponds to the highest frequency that can be obtained from a standard cd. Any transient or absorbed energy decay should have vanished well before this so as not to affect the audio band.

Measurement terminals of the test unit consisted of two 25mm lengths of 7/0.2, twisted as far as possible to minimise their inductance.

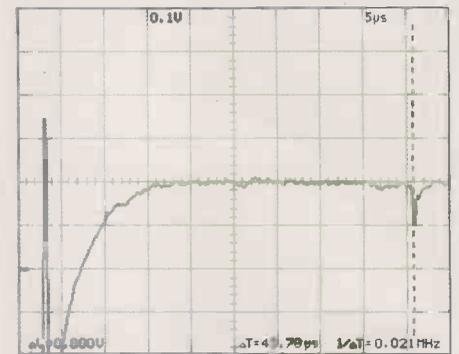


Fig. 4. Van den Hul CS122 speaker cable has seven bunches comprising 21 strands of 0.15mm silver-plated copper.

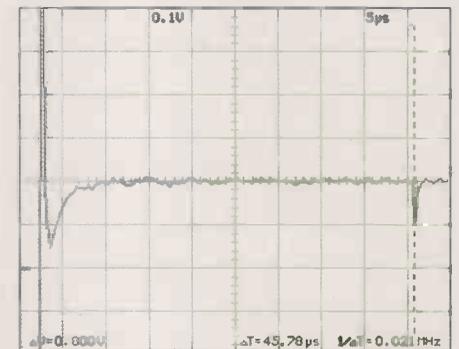


Fig. 5. Jenving Supra Ply 2.0 normally shows a small eddy current decaying within 10μs, but when twisted, the eddy current and time constant increase.

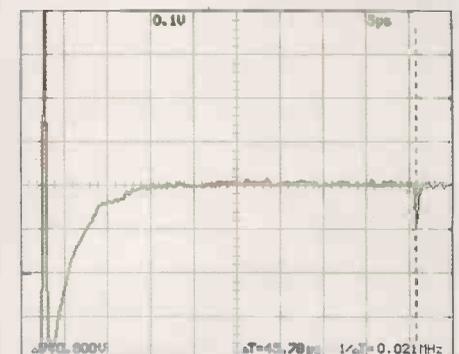


Fig. 6. When twisted, Jenving Supra Ply 2.0 performs less well under this test.

The cable-under-test was then soldered in turn to these to ensure good electrical contact. Proprietary speaker terminals or connectors were not used because they could contribute their own eddy current effects.

Figure 3 shows response from a 1m length of inexpensive speaker cable from Shark Wire Co. This is a parallel wire consisting of 129/0.1mm strands of oxygen-free copper and a conductor separation of 5mm. The negative excursion and overshoot due to the series inductance settles down in under 5µs and

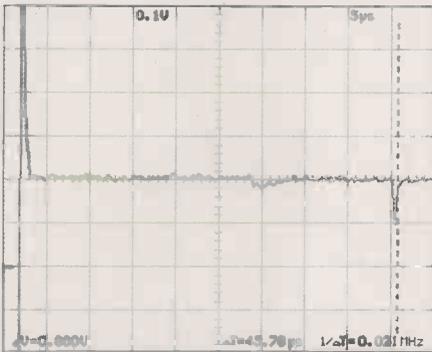


Fig. 7. Eddy currents are not a problem here, but Heywire gave the highest series inductance. Overshoot decay was short though, at 4µs.

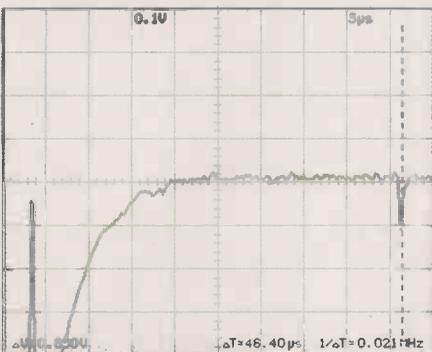


Fig. 8. Cable Talk 4 had the largest eddy-current loss, the signal taking 25µs to decay into the noise floor.

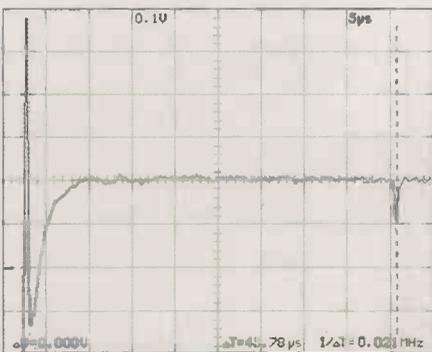


Fig. 9. Lawnmower flex performed surprisingly well, eddy currents dying away in 10µs.

there is no evidence of cross sectional eddy currents. Having experience in pulse-induction metal detection, this came as no surprise to me. It is usual to use fine stranded wire in the search coil winding to minimise cross section effects.

By comparison, Fig. 4 shows the response from 1m of Van den Hul CS/22. The conductors in this cable consist of seven bunches of 21 strands of 0.15mm silver-plated copper encased in an inner conductive plastic material with a conductor separation of 11mm.

The exponentially decaying waveform is due to eddy currents in the overall wire cross section aided by the higher conductivity of the silver coating. Even so they have decayed away within 20µs, or 1/ΔT of 50kHz.

Jenving's Supra Ply 2.0 was an interesting cable to try, endorsed as it was by Ben Duncan in his tests¹. Figure 5 shows a small eddy current signal decaying within 10µs. If the cable is twisted or bent however, the braided 0.14mm strands make better contact with one another and the eddy current amplitude and time constant increases, as in Fig. 6.

Heywire from Heybrook Audio uses single solid copper cores of 0.6mm diameter. This is small enough not to exhibit eddy currents, but combined with the 8mm conductor spacing gave the highest series inductance. However, the resulting overshoot decayed in 4µs, Fig. 7, and is similar to Shark Wire cable.

Of the cables measured, Cable Talk 4 had the largest eddy current loss – the signal taking a full 25µs to decay into the noise level, Fig. 8. The conductor bunches consist of 42 strands of 0.3mm copper separated by a 6mm spacing.

Non audio cables

Mains lead is often derided for audio use and I have never seen rf cable advocated for this application. So I tested 10A lawnmower flex and RG58C/U coaxial cable to see how they would fare.

The lawnmower cable, Fig. 9, with 32/0.2mm conductors spaced at 2mm, came out surprisingly well; the eddy currents dying away in 10µs. Type RG58 coaxial cable, Fig. 10, was the cleanest of all, showing no overshoot and the eddy currents in the braid decaying in 7µs.

Slightly less pick-up noise is also evident due to the screening effect of the coaxial braid. It is important to stress that the rf characteristics of coaxial cable have no bearing on these tests. It is simply the series inductance, capacitance and eddy current losses which affect the pulse induction tests recorded here.

Noise performance and inductance

Other waveforms can be observed with the test circuit. If the probe is connected across the damping resistor the back emf spike can be measured which relates to the series inductance.

Comparison of the parallel conductor cables with the coaxial cable shows the coaxial type to have the lowest series inductance. Compare Figs 11 and 12.

If the damping resistor is removed, the ringing frequency of the cable can be measured. Both the inductive spike and ringing are displayed on a time base ten times faster than the previous cable responses so you can see that the signal is well into the r.f. region, even for 5m lengths.

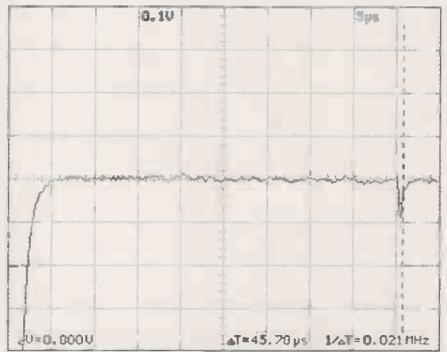


Fig. 10. Cleanest of all – plain and simple RG58 coaxial cable. There is no overshoot and eddy currents in the braid decayed within 7µs.

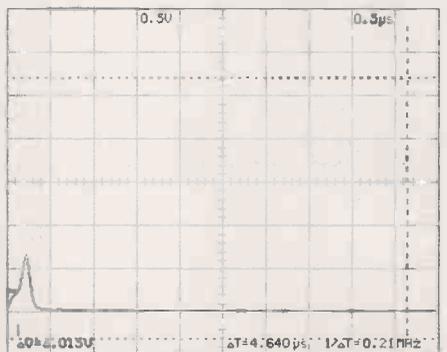


Fig. 11. RG58A/U coaxial cable again, but tested for series inductance. Compare this with Fig. 12.

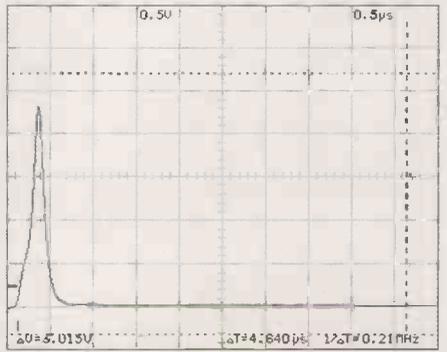


Fig. 12. Inductive spike resulting from Heywire shows that it performs less well relative to coaxial cable in this test.

While the 5m lengths were connected to the test unit, it was interesting to observe the relative noise pickup. All the tests were conducted in an electronics workshop on an industrial estate, where there is a fairly high electrical noise level.

As you can see from Figs. 15 and 16 the coaxial cable braid affords considerable screening of rf noise. The larger overshoot spike is because we now have more series inductance resulting from the greater length.

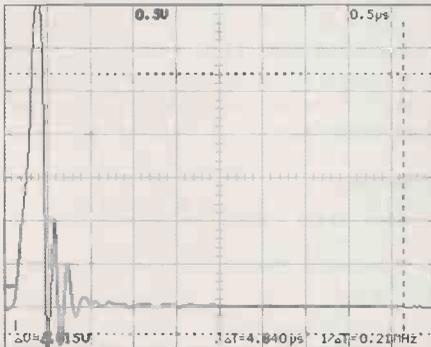


Fig. 13. Performance of a longer length of lawnmower cable – 5m – with no damping and a ten times faster time base indicates that the frequencies involved are well outside the audio range..

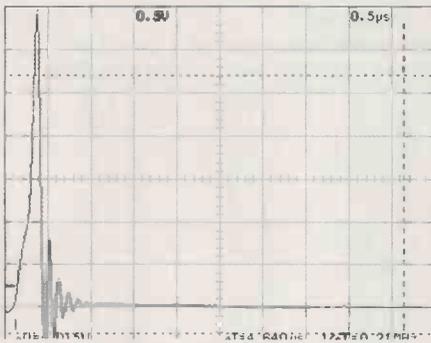


Fig. 14. RG58 coaxial cable performance for a 5m length with damping removed.

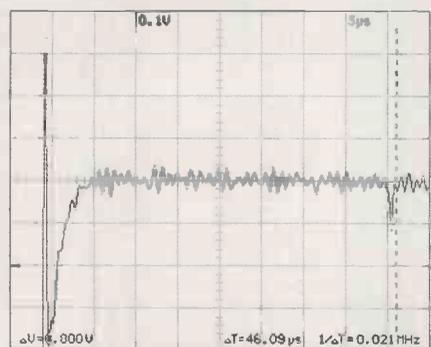


Fig. 15. Noise pickup of lawnmower cable in a noisy environment, length 5m.

Copper oxide and diode effect

Two forms of distortion mentioned in other articles on speaker cables are current jumping between strands and a diode effect² due to copper oxide on the strand surface.

No evidence of these phenomena were seen on the foregoing waveforms. However some tests were conducted on deliberately oxidised cable to see if there was any measurable effect.

Experiences with underwater pulse-induction metal detectors have shown that leakage of salt water into a cable very quickly causes oxidation of the strand surface, which takes on a dark red mat appearance. Under such conditions the conductor acquires a surface layer of copper hydroxide and copper chloride.

I injected salt water under pressure into a 1m length of lawnmower cable until it emerged from the strands at the far end. The cable was left for a couple of days and then tested. There was no change in the oscilloscope waveform.

On the third day the cable was immersed in salt water which was heated to 50°C and left overnight. The dull red coating was now in evidence to show oxidation was taking place. Again there was no measurable difference in the waveform which was again checked after one week, Fig. 17.

Some of you may object that the salt water test is not realistic, and that the oxide layer is not the same as would occur naturally in a speaker cable. However it is interesting that such a drastic contamination with a corroding electrolyte had no measurable effect on the waveform.

Another rather different oxidising test was done. This was to strip all the insulation off of a metre of one conductor of lawnmower cable and measure its eddy-current response, Fig. 18. The smaller amplitude is due to the shorter length but, as stated previously, the decay time is independent of this.

Using a butane blow torch, the cable was heated along its length until the strands took on a black appearance and the wire was in a softer annealed state. The response was then as in Fig. 19. In this case the oxide layer has broken up the eddy current paths between strands and all but removed that part of the response.

It appears, therefore, that the formation of a normal oxide layer on the strands of a speaker cable will do very little to alter the cable's characteristics. Over the long term, however, it could even serve to improve the high frequency response of a cable, if only at ultrasonic frequencies.

In summary

This relatively simple method, derived from the front end circuit of a pulse induction metal detector, can give valuable information about the characteristics of loudspeaker cables.

The signals being examined result purely from the cable itself, and occur after the drive

pulse has ended. In particular, this method clearly shows the effect of eddy currents in the cable cross section.

All of the waveforms, except where otherwise indicated, are for 1m lengths which are obviously shorter than would normally be used in a hi-fi system.

Tests on 5m lengths of lawnmower flex and coaxial cable show that all the effects increase in proportion to length. As the length increases so do the series inductance and capacitance,

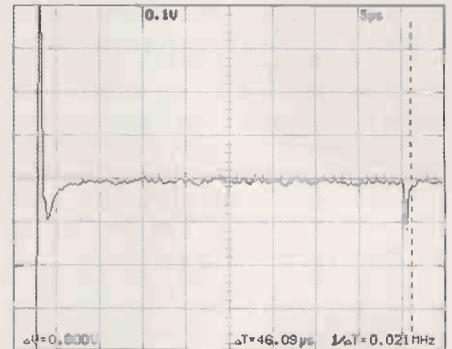


Fig. 16. In the same environment used for Fig. 15, the same length of coaxial cable picks up far less noise.

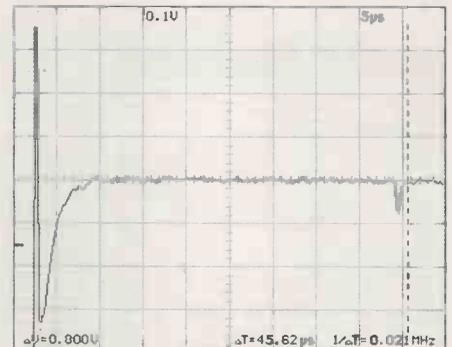


Fig. 17. Some hi-fi enthusiasts advocate the use of oxygen-free copper in audio cables. Here, lawnmower cable was injected with salt water, left for three days and tested again. No change is apparent in these tests.

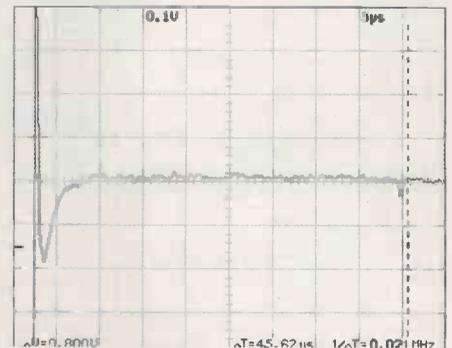


Fig. 18. A 1m length of lawnmower cable with its insulation removed.

20% EW reader discount

Audio signal generator



AG2601 is a portable mains-powered instrument covering 10Hz to 1MHz in five overlapping decades. Sinewave distortion between 500Hz and 50kHz is just 0.05%.

The AG2601 audio signal generator spans 10Hz to 1MHz in five overlapping ranges and features floating output and low distortion. This stable sine and square-wave oscillator is being made available to *Electronics World* readers at the fully-inclusive special price of £129. Its normal selling price is £129 excluding VAT and delivery.

Please use the coupon to order your signal generator, and address all correspondence relating to this order to Vann Draper Electronics at Unit 5, Premier Works, Canal Street, South Wigston, Leicester LE18 2PL, fax 0116 2773945 or tel. 0116 2771400.

AG2601 audio generator – specifications

General

Frequency range 10Hz to 1MHz
Frequency stability within $\pm 2\text{Hz}$
Output waveforms sine, square
Output impedance 600 Ω
Accuracy $\pm 5\% + 2\text{Hz}$, 10Hz-1MHz
 $\pm 3\% + 2\text{Hz}$, 100Hz-100kHz
O/P floating voltage within $\pm 1.5\text{dB}$

Sinewave characteristics

Distortion $< 0.05\%$, 500Hz to 50kHz
 $< 0.5\%$, 50Hz to 500kHz
Output voltage 8V rms, max
Output flatness $\pm 1.5\text{dB}$ (1kHz)
Output impedance 600 Ω

Squarewave characteristics

Output voltage 15V pk-pk, min
Rise time 0.5 μs

Synchronization input

Input impedance 10k Ω
Maximum input 10V rms

Supply

115/230V, 50/60Hz

Physical data

Dimensions 150 by 250 by 130mm
Weight 2.5kg

*Test leads supplied as standard

Use this coupon to order your AG2601

Please send me AG2601 Audio Generator(s) at the fully inclusive special offer price of £129.

Name

Company (if any)

Address

Phone number/fax

Total amount

£.....

Make cheques payable to Vann Draper Electronics Ltd
Or, please debit my Master, Visa or Access card.

Card type (Access/Visa)

Card No

Expiry date

Please mail this coupon to Vann Draper Electronics, together with payment. Alternatively fax credit card details with order on 0116 2773945 or telephone on 0116 2771400. Address orders and all correspondence relating to this order to Vann Draper Electronics at Unit 5, Premier Works, Canal Street, South Wigston, Leicester LE18 2PL.

*Overseas readers can also obtain this discount but details vary according to country.

OLSON

®

For all your Power Distribution Olson offer a varied choice

OLSON Distribution Units

ELECTRONICS LIMITED

OLSON DISTRIBUTION PANELS FUSED, WITH R.F. FILTER AND R.C.D. PROTECTION

ELECTRONICS LIMITED

OLSON

ELECTRONICS LIMITED

OLSON The Rack Range mains distribution panels for 19" rack mounting

ELECTRONICS LIMITED

OLSON Office Furniture Cable Management Manufactured to BS 6399

ELECTRONICS LIMITED

OLSON Mains Distribution Panels with Non Standard Sockets

ELECTRONICS LIMITED

OLSON SUPER SLIM (IN PANELS)

ELECTRONICS LIMITED

OLSON Earth Leakage Distribution Units

ELECTRONICS LIMITED

OLSON Distribution Units

ELECTRONICS LIMITED

OLSON PANELS with 10AMP CEE22/IEC SHUTTER SOCKETS FUSED, DOUBLE FUSED WITH R.F. FILTER AND R.C.D. PROTECTION

ELECTRONICS LIMITED

OLSON The Rack Range WITH ANTI-FLAME

ELECTRONICS LIMITED

OLSON Mains Distribution Panels INTERNATIONAL RANGE

ELECTRONICS LIMITED

OLSON FUSED SUPER SLIM WITH ELECTRAK PLUG, CONDUIT AND DOUBLE POLE SWITCHED SOCKETS

ELECTRONICS LIMITED

OLSON DATA PROTECTOR TO STOP STAGES OF FLUX WITH SURTUPS CIRCUIT AND FREQUENCY SUPPLY STOP

ELECTRONICS LIMITED

OLSON INDUSTRIAL RANGE 16 AMP 110V AND 240V TO BS 4343/IEC 309

ELECTRONICS LIMITED

OLSON Distribution Units

ELECTRONICS LIMITED

OLSON 19" FAN TRAYS

ELECTRONICS LIMITED

OLSON

ELECTRONICS LIMITED

OLSON SERVICE PILLAR FOR THE OPEN-PLAN OFFICE

ELECTRONICS LIMITED

OLSON Distribution Units FRENCH AND GERMAN STANDARDS IEC/EN 60361

ELECTRONICS LIMITED

936

Cable science?

Geoff Williams believes that audio signals passing through a cable are affected not just by copper cross-section, but also by a complex combination of field and semiconductor effects.

Transmission of alternating current through a cable produces a magnetic field, an electrostatic field and these are affected by the physical structure of the wire.

Magnetic field considerations

Electrons exhibit a rotating magnetic field and all magnetism derives from this. The field round a wire radiates outward in concentric circles from the centre. At the centre, the field is zero, reaching a maximum at the wire surface. It then falls off inversely proportionally to distance, Fig. 1.

Relevant expressions are inductance L which is change-of-flux divided by change-of-current, and impedance R in ohms which is $2\pi fL$ where f is frequency. In an ac circuit, the flux (field) and the current both change together with frequency. Since flux is greatest at the surface, it follows that the change of flux is also greatest at the surface for the same change of current. Consequently, the inductance will be greatest at the surface and so will be the impedance.

This increasing impedance results in a loss of efficiency as frequency rises. Considering also the eddy currents set up in the wire, the situation worsens. Eddy currents force electrons toward the surface, and the higher the frequency, the more they are forced outward into this region of high impedance, decreasing high frequency efficiency. This is the skin effect, whereby high frequencies travel down the skin of the conductor.

In Fig. 2, the circle represents the conductor and its associated magnetic field. The direction of rotation is as if the current is going into the paper as depicted by the cross in the middle. Though the field is made up of concentric circles from the centre, at an arbitrary point A, the electrons see the relative flux and direction as shown. Electrons are moving into the paper, so to speak, through a magnetic field at right angles relative to the current. From Fleming's right-hand rule, the electrons move in the direction shown. Arbitrary point A can be considered anywhere in the conductor and the direction of motion is always toward the outside of the conductor.

Flux changes with frequency so, the higher

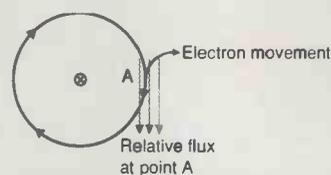


Fig. 2. High frequencies travel along the surface of a conductor – a phenomenon known as skin effect. This diagram illustrates how electrons are forced toward the skin.

the frequency, the greater the change of flux in a given period of time and the greater the tendency for electrons to be forced to the surface. Because the flux density is stronger and electrons are effectively cutting a faster moving flux at the surface, this effect is intensified at the surface.

Transients and high frequencies

Because of the skin effect, if you increase the surface area of the conductor, for example, by having a rectangular cross-section, you will improve the high-frequency performance and transient response. But this is not an elegant solution. What is best is to prevent the eddy currents using Litz wire. Being made up of separately insulated strands, Litz wire effectively prevent eddy currents moving from the centre to the outside of the conductor. Each strand however can still be considered as a solid core with its own internal eddy currents, these are tiny compared to what they would be in one large solid-cored wire.

To achieve maximum efficiency, the strands

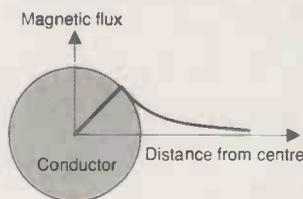


Fig. 1. Magnetic field around a wire radiates outward. It is zero at the core, maximum at the surface of the wire, and falls off exponentially as it radiates outward.

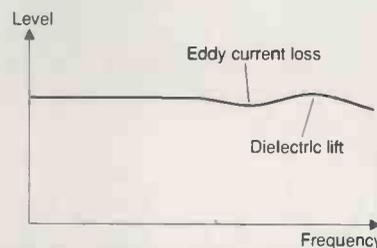



Fig. 3. Frequency response of a solid-core cable with plastic sheath. In listening tests the response dip is audible.

PROTEUS

For DOS and Windows 3.1, 95 & NT


The Complete Electronics Design System - Now With RIP-UP & RETRY!

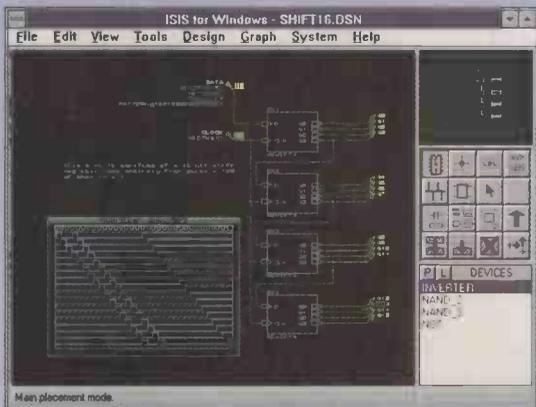NEW LOW PRICE OPTIONS AVAILABLE
Level 1 (500 pins) from £250
Level 2 (1000 pins) from £495
Level 3 (unlimited) from £995




Schematic Capture

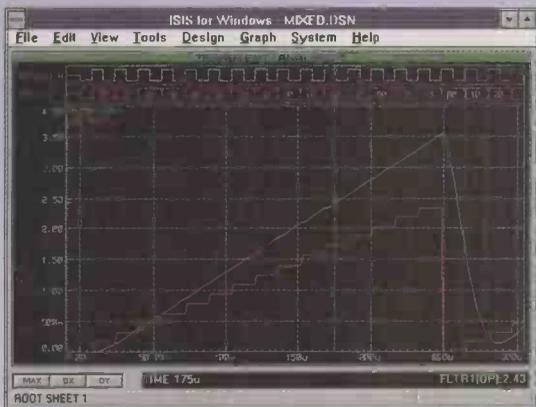- Easy to Use Graphical Interface under both DOS and Windows.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and



Simulation

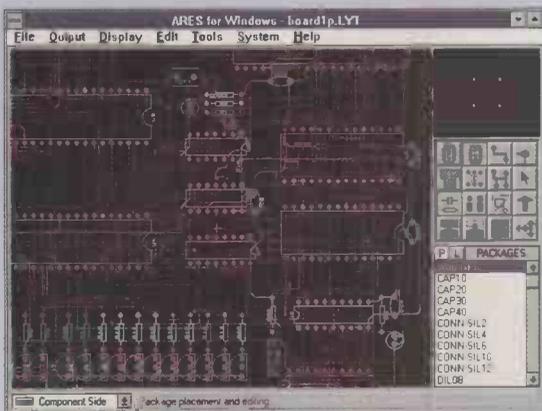- Non-Linear & Linear Analogue Simulation.
- Event driven Digital Simulation with modelling language.
- Partitioned simulation of large designs with multiple analogue & digital sections.
- Graphs displayed directly on the schematic.



PCB Design

- 32 bit high resolution database.
- Multi-Layer and SMT support.
- Full DRC and Connectivity Checking.
- RIP-UP & RETRY Autorouter.
- Shape based gridless power planes.
- Output to printers, plotters, Postscript, Gerber, DXF and clipboard.
- Gerber and DXF Import capability.

Labcenter
Electronics

Call now for your free demo disk
or ask about the full evaluation kit.
Tel: 01756 753440. Fax: 01756 752857.
53-55 Main St, Grassington. BD23 5AA.

Fully interactive demo versions available for download from our WWW site.
Call for educational, multi-user and dealer pricing - new dealers always wanted.
Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.

EMAIL: info@labcenter.co.uk
WWW: <http://www.labcenter.co.uk>

need to be bunched into the minimum cross-sectional area, meaning a circle.

Fields and insulation

Looking at the electrostatic field around wire carrying a current, the flux is considered to emanate from the positive (protons) and go to the negative (electrons). The strength of the field (voltage) falls away inversely proportionally to the distance from the surface, as in the magnetic situation.

Things change, however, when you consider the effect of encasing the wire in a plastic insulating sheath. The plastic acts as a dielectric and effectively suppresses the external electrostatic field, reducing the voltage detected at various distances from the wire.

The amount of suppression by a material is related to its dielectric constant – relative permittivity. Basically, the higher the dielectric constant, the greater the field suppression.

All insulators exhibit dielectric loss. This means that the insulator retains a small amount of electrostatic charge when excited by the signal. It does so in much the way steel retains its magnetism when it is subjected to an external magnetic field. Consequently, the insulator must be forcibly discharged by the signal when it changes polarity. This leads to signal loss and cancellation. The smaller the dielectric loss, the better.

From the above, you would expect that a material with low dielectric loss and high dielectric constant would be the best material to use as an insulating sheath for an audio cable. The best materials are polypropylene, polyethylene, teflon and, slightly down the scale, polyester. PVC is lower still and inferior. The worst insulators are probably rubber-based compounds, including polyolefins. So although the relevant electrostatic field lies outside the wire boundaries, whether you place something next to it or not can have a serious effect on the sound quality where loudspeaker cables are concerned.

The dielectric is charged and discharged by the electrostatic field of the audio signal. The more the dielectric suppresses the field, the less it is charged and discharged. The lower the dielectric loss, the less tendency there is

Proximity effects

How audio cables are arranged in space is important. As a rule, cables that are adjacent to each other carrying current in opposite directions must be at least ten times the wire diameter apart to avoid signal cancellations due to magnetic coupling. This does preclude the use of non-inductive (bifilar) winding for audio purposes. Such an arrangement causes signal loss due to phase cancellation and is clearly audible.

Consequently, it is better to have signal and return wires separate rather than combined into one cable. Avoid twisting cables together because this will create inductive turns.

Conductivity of metals

| | |
|-----------------------|--------------------------------|
| Silver | 1.620 $\mu\Omega/\text{cm}^3$ |
| Copper | 1.682 $\mu\Omega/\text{cm}^3$ |
| Gold | 2.420 $\mu\Omega/\text{cm}^3$ |
| Aluminium | 2.825 $\mu\Omega/\text{cm}^3$ |
| Rhodium | 5.100 $\mu\Omega/\text{cm}^3$ |
| Zinc ¹ | 6.000 $\mu\Omega/\text{cm}^3$ |
| Iron | 9.800 $\mu\Omega/\text{cm}^3$ |
| Platinum | 9.970 $\mu\Omega/\text{cm}^3$ |
| Nickel ² | 10.900 $\mu\Omega/\text{cm}^3$ |
| Tin ³ | 11.500 $\mu\Omega/\text{cm}^3$ |
| Chromium ⁴ | 13.100 $\mu\Omega/\text{cm}^3$ |
| Lead ⁵ | 20.650 $\mu\Omega/\text{cm}^3$ |

¹ used in brass

² used in resistance wire and screening

³ used in solder and in plating copper

⁴ used in nichrome resistance heating wire

⁵ used in solder

for the material to remain charged when the accompanying field in the wire has long been and gone.

The difference in sound I perceive between bare wire and insulated wire indicates that a bare solid core wire has a curtailed top end compared to a sheathed piece of the same. **Figure 3** represents the frequency response of a solid-cored cable with a plastic covering. My listening tests bear this out, with a noticeable dip in the response. The thicker the wire, the more apparent the effect. However, the eddy current losses are greater than the dielectric lift and the response starts to fall off again at higher frequencies.

Unfortunately, it is not possible to use the dielectric properties of the insulating sheath to correct the drop in response caused by eddy current losses. The electrostatic repulsion does not penetrate far enough into the wire, and we end up with the characteristic dip in the response. The magnetic effect is stronger than the electrostatic effect.

For audio cables, copper needs to be of a higher purity than the standard 99.99%. Impurities affect electrical transmission of complex waveforms. Non-copper atoms can cause undesirable semiconductor activity. Each crystal junction has a strong electrostatic plane (it is these electrostatic forces that create the crystal structure in the first place) and it is reasonable to assume that these planes will deflect somewhat the electron flow.

Wire with larger crystals has fewer junctions. Such wire is often advertised as monofilament or linear crystal.

Directional cables

A cable with directional qualities is undesirable. If a cable has a lower impedance in one direction than the other, it is acting to some degree as a diode.

Copper oxide is a semiconductor. Early rectifiers used copper oxide. Attempts have been made to limit the amount of oxygen in the copper in the production process, but it is impossible to eliminate all of it. Much so-called oxygen-free cable is in fact anything but

oxygen free. Many of these cables have managed to eliminate surface oxidation only.

The wire surface needs to be gas-tight to avoid oxidation after the wire has been sitting for a few months. Enamelled copper wire is gas-tight, but even this acquires a small amount of surface oxidation in the enamelling process. Plating the copper with a metal that resists oxidation might appear to solve the problem. Metals commonly used are tin, silver, gold and, more recently, rhodium. This is all very well, but there is a body of opinion that asserts that plated wire is not as good as unplated.

As far as I know, there are three aspects to consider: thermoelectricity, conductivity and crystallinity.

Thermoelectricity and conductivity

A junction of dissimilar metals makes a thermocouple. Copper is one of the commonest thermocouple metals.

If there is a temperature difference between the metal's junction and another part of the circuit, a small voltage is developed across the junction. Loudspeaker cables are heated slightly by the current flowing in them, but I think that this thermoelectric problem is very small and not one to worry unduly about.

Table 1 is a list of conductivity, as specific resistivity, of metals used in electronics. You can see that silver has only a very slightly better conductivity than copper but is far more resistant to oxidation than is copper, and this is where it scores.

Plating interferes with the skin effect. Tin-plating is a disaster, increasing even further the high-frequency resistance at the surface. Plating introduces another set of crystal boundaries which will deflect and reflect the signal, and adds credence to the arguments for non-plated wire.

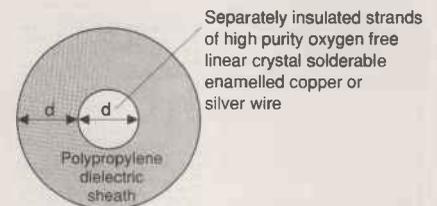


Fig. 4. Preferably, dielectric thickness should be greater than the total wire diameter.

Solid versus stranded

Early audio cable, particularly speaker wire, was made of separate strands, bunched and sheathed. These strands had a certain amount of surface oxidation contributing to the semiconductor effect. When people switched to solid core, the reduction of oxidation increased the clarity of the signal.

I have found that stranded cable outperforms solid-cored at higher frequencies. This is due to the reduction of eddy currents and the greater surface area, but this top end is certainly confused. Hence we have definite but different advantages for both types of cable and, as one would expect, both types of wire

Hands-on Internet

Cyril Bateman discusses a standardised document format and presents this month's findings – among them an electronics manufacturers directory and design software.

As the Internet Web pages continue to grow in number and sophistication, many electronics manufacturers use them to provide their traditional data packs. With the final on-screen appearance being under the control of the users Browser, not the creator of the script and the limited page formatting capability of HTML, the Adobe PDF format was plugged into Netscape to provide full page control.

Adobe's Acrobat 2.1 reader¹ for PDF, gives access to documents in their original form independent of the users computer platform, can be downloaded from most Web pages using PDF format.

An offshoot of Postscript, Portable Document Format uses the ATM font technology to render the document in your browser, ensuring WYSIWOG – an acronym for what you see is what others get. It is compatible with Netscape 1.1, Spyglass Mosaic 2.0 and newer equivalents, Fig. 1.

To date PDF usage has been restricted due to the software needed. While the reader is now freeware, the production suite was costly. All this is about to change. The beta version of Acrobat 3.0 (Amber Beta) has been available since end May. Acrobat 3.0, with a full suite of tools, is due to release in USA this

October at the incredibly low cost of \$295. It provides PDF generation from your word processor and even from scanned documents.

The version 3.0 reader, available for most browsers and operating systems, provides searching and linking as with HTML. Being fully WYSIWOG does have a down side though. HTML, unless specifically formatted, wraps a text line round if your browser width is less than the designed page width. PDF on the other hand simply chops it off. By design it cannot wrap text lines for you.

The Argus Clearinghouse²

claims to be the premier Internet Research Library, and can be a most useful data source and Internet search tool. It is managed by librarians, and founded on their belief that to encompass ambiguities of language and ideas, human effort and qualitative assessments must be combined with searching and browsing techniques, Fig. 2.

This month's bookmark site just has to be found at eenet.com, home of the Electronics Industry Inforum and Interactive Workplace³. A sample search on 'capacitors' resulted in details of some 60 capacitor makers, mostly not having their own Web presence. This site includes a facility called Info Fax. With this facility, any company wanting an Internet listing needs only a fax machine to receive and send data requests. The facilities offered by eenet provide services both for designers and marketers. They should be sampled, words alone are inadequate, Fig. 3.

Webscope.com⁴ is among the top 5% sites and offers two directories of Internet resources, in addition to its main role as a provider. While the guide to hotels and travel is interesting, Webscope's unique directory of electronic manufacturers is an essential directory service. It is indexed by manufacturing categories, and is most relevant, Fig. 4

Simulation software

The AVX *SpiCap* software⁵ calculates the effective capacitance, esr and self inductance parameters of AVX ceramic multilayer range by frequency, temperature and applied voltage.

Described last month, this software is now available on two 3.5in disks, facilitating its use by all spice designers. Copies can be ordered on-line or from the company's sales offices. Obviously while targeted to spice users, these same parameters can be applied to any simulator, whether frequency or time domain.

Readers wanting further clarification of the need to derive capacitor models with parasitics, are directed to two useful papers, the Microsim FAQ⁶ and a piece called '12 Simulation program tips/tricks/bugs.

Should you want to try out a frequency domain rf simulator, or need S parameters for Hewlett Packard rf semiconductors, a three-disk freeware package called

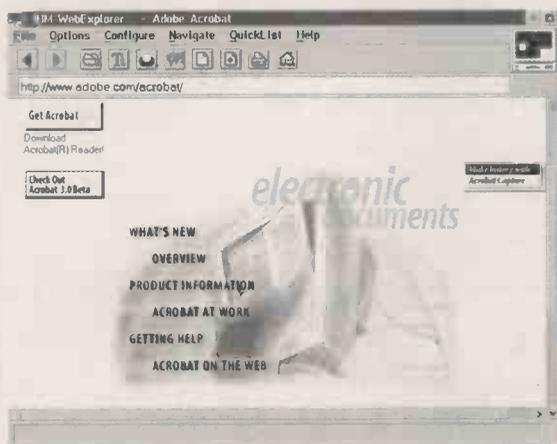


Fig. 1. Adobe Systems provides new uses for paper documents. Software for PDF document reading and creation.

ANCHOR SURPLUS Ltd

The Cattle Market Depot
Nottingham NG2 3GY. UK


Telephone: +44 (0115) 986 4902/
+44 (0115) 986 4041 24hr answerphone

Fax: +44 (0115) 986 4667



Micro Video Cameras

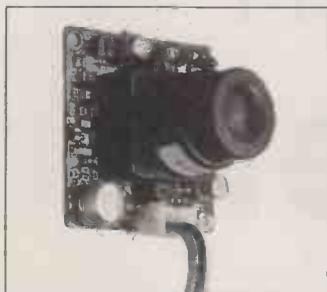Following our recent Readers Offer for the 721-S Micro Camera many readers have contacted us asking about other items in our range of Micro Cameras and Security Surveillance equipment.



We are **SOLE AUTHORISED IMPORTERS** of the entire range of Cameras and Video Surveillance equipment produced by the world's leading manufacturer. ALL items in the range carry a full 12 Months Guarantee. If you would like to receive our comprehensive catalogue of Cameras and associated equipment please send a large SAE with 48p postage, marked "Camera Catalogue"



Here is a sample of the available stock.

A-721-S Micro Camera 32mm x 32mm ... £85 A-721-P Micro PIN-HOLE Camera ... 32mm x 32mm ... £85

A-921-S Camera with AUDIO ... 30mm x 30mm ... £95

A-1211 C/CS Mount Camera ... 110mm x 60mm x 60mm ... £110

A-521 Micro Cased Camera 43mm x 48mm x 58mm ... metal cased ... £120

6001-A High Resolution COLOUR Cameras (420 lines) ... 0.45 lux ... £210

Outdoor Camera Housings ... Aluminium ... £45 Camera Mounting Brackets ... Universal Mounting ... £5.95

Camera Switchers ... for up to 8 Cameras ... £85

Auto Record Controllers ... Allow NORMAL VHS Videos to operate like professional Time Lapse or Security Recorders ... £75

QUAD-1 Multi Vision Processors ... Digital Freeze ... Quad Pictures etc £275

QUAD-2 Full COLOUR QUAD version of QUAD-1 ... £695

SCI ... SCANNER ... 350° PAN ... Automatic / Manual ... £105

IRA ... Infra Red Illuminator for "Total Darkness Surveillance" ... 20m range ... £125

VMS-1 .. Video Motion Sensor ... replaced alarm sensors with totally electronic video monitoring system that detects changes in the video signal .. £175

C/CS Format lenses ... Premium 3.6mm = £22.50 Superior 8mm = £27.50

PLEASE NOTE:

AS A CONTINUED SPECIAL OFFER ALL THE ABOVE CAMERA AND ACCESSORY PRICES INCLUDE VAT AND CARRIAGE TO UK ADDRESSES

Government Surplus Electronics Equipment on Special Offer This Month

TIME Electronics 404N/1021 Voltage/Current Calibrators ... 0.05% accuracy ... ONLY £275

FRANKLIN Wavetek 3600 Power Line Disturbance Monitor + Printer ... LAST 2 NOW ONLY £350

MARCONI TF9693 + TF2361 + TF9695 VHF Sig Gen / Sweeper sets ...

1Mhz-300Mhz ... 0.01-100Khz sweep rate ... 0-60db attenuators ...

INCL Cased Adaptor sets ... LAST FEW NOW ONLY £125

COMARK 2007 + 3 "K" type probes ... 0.1°res ... ±0.5%acc ... Cased As New ... ONLY ... £65

Other Digital Thermometers always in stock ... Please Phone

SINERGY TRILINE PCSA Energy Monitor LCD Screen ... Colour Plotter 1+3ph ... ONLY £195

MARCONI TF2300S FM/AM Mod Meter 3.5Mhz-1Ghz AM/AM ... ONLY £75

TEK 491 Spectrum Analysers ... 10Mhz to 2Ghz ... Few Left at ONLY £995

TEK 7603 + 7A18 + 7B50A 4 Channel 100Mhz Scope ... Rack version ... FEW left ... Only £325

FARNELL TM8 Sampling RF Millivoltmeters 1mV-3V 10Khz-1.5Ghz ... FEW left ... ONLY £125

MARCONI TF2603 RF Millivoltmeters + Accessory Kit ... LAST FEW ... ONLY £60

TEK 466 Storage Scopes ... Twin Trace and Timebase ... Dc-100MHz ... ONLY £475

TELEQUIPMENT D61A Scopes ... Twin Trace DC-20MHz ... ONLY £120

MARCONI TF2018 Signal Generators ... 80KHz-520MHz AM/FM ... Fully Digitally Synthesised Internal/External Modulation ... ONLY £995

OPEN 6 DAYS A WEEK

Mon-Fri 9am-6pm Sat 8am-4pm

NO APPOINTMENTS NEEDED. CALLERS ALWAYS WELCOME

All Prices are Ex VAT & Carriage

**All items are Fully Tested with Verified Calibration
and carry our Unique 30 Day Un-Conditional Warranty**



CIRCLE NO. 131 ON REPLY CARD

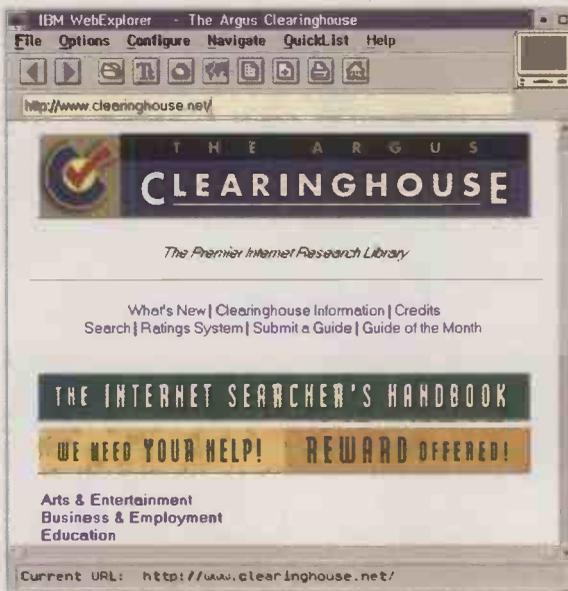


Fig. 2. Argus Clearinghouse – a value added central access point. Provides topical guides to Internet only based resources.

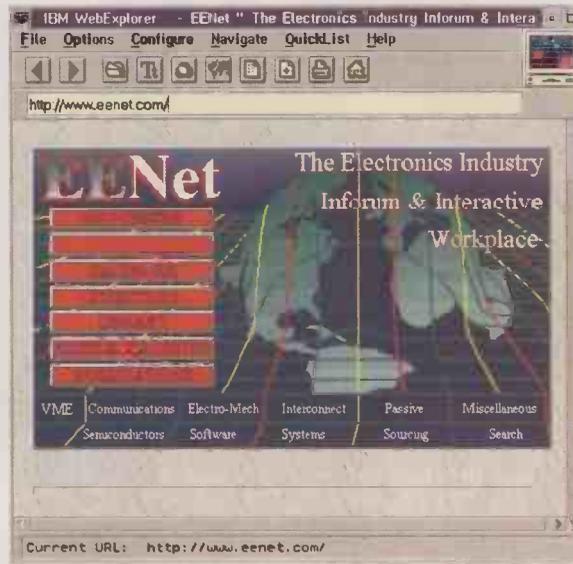


Fig. 3. EENET Corporation service for electronics. Provides listings of Internet and non-Internet based resources.

AppCad is available. Its HP part number is HAPP-0001, and it has proved invaluable to me.

This small-scale package is described as a “unique combination of application notes and rf design tools combined with an interactive product selection guide”. Its capability ranges from simple two port S parameter analysis to design of printed circuit spiral inductors. It can be downloaded from Internet. Archie located the files only at ftp.funet.fi but FTP Search⁷ at Norway found two more sites both having newer files.

A rather different but equally useful catalogue on disc is available for K&L Microwave Inc’s rf signal resonator filters. Choose the desired characteristics, view the passband response to be given their catalogue number.

Having designed and simulated your circuit you need a printed circuit board layout package. PADS Software Inc. supplies professional circuit design software at suitable prices⁹. The company also offers a more restricted but perfectly usable shareware version with schematic editor and autorouting, which I have used. The Electronic Design Software page mentioned in the last issue, describes its download from the SimTel archives, Fig. 5.

Now that prices have settled, I have finally replaced my 14.4kbit/s modem used for the past two years with a 28.8k alternative. However, I still use 57,600bit/s serial port rate, not having upgraded to a 16550-type uart. Since most data downloaded is already fully compressed, when Internet permits, the modem runs at full speed. Mostly, however, Internet is much slower, so it seems unnecessary to upgrade the serial card – at least until Internet access improves for the UK. ■

References

1. Adobe Systems Incorporated, <http://www.adobe.com/acrobat>
2. Argus Associates Incorporated, <http://www.clearinghouse.net>
3. EENET Corporation, <http://www.eenet.com>
4. Stetcom Incorporated, <http://www.webscope.com/elx>
5. AVX Corporation, <http://www.avxcorp/software>
6. Microsim Corporation, <http://www.microsim.com/>
7. FTPSearch Trondheim Norway, <http://ftpsearch.unit.no/ftpsearch>
8. K&L Microwave Incorporated, <http://www.klmicrowave.com/klmicrowave/k&l.html>
9. PADS Software Incorporated, <http://www.pads.com>.



Fig. 4. Webscope division of Stetcom provides an exclusive directory. This is a good directory of electronic sources by product category.

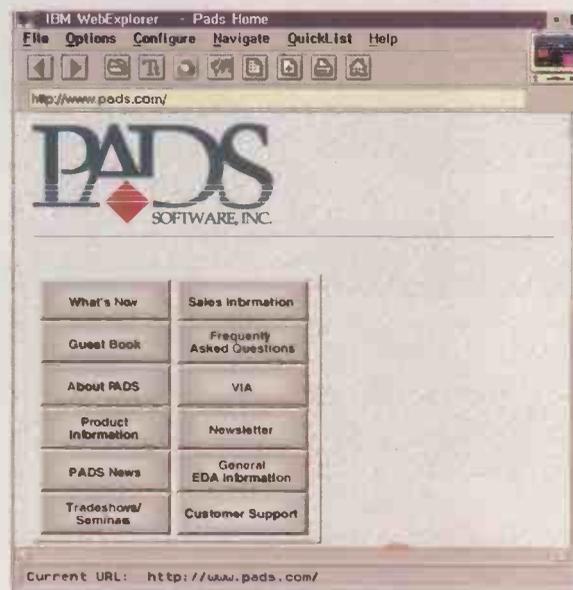


Fig. 5. PADS Software home page for pcb layout software. The company’s shareware software can be downloaded or bought from shareware libraries.

NOW, THE BATTLE IS OVER

ULTIBOARD



ULTIBOARD

BUNDLED WITH  **SPECCTRA**
SHAPE BASED AUTOROUTER

ULTIboard's interactive strength has always been the major selection criterion of professional Printed Circuit Board designers. Now that every ULTIboard Designer system will be supplied with a SPECCTRA SP4 Autorouter, ULTIboard designers now get the best of both worlds.

All ULTIboard Designer Users with valid update subscription got a MAINTENANCE UPGRADE with the SPECCTRA SP4 (4 signal layers + power/ground layers) Shape based Autorouter. This shows that ULTIimate Technology is *the* PCB-Design Tool vendor that *really* cares for their customers!

**THE ULTIMATE
SPECIAL OFFER**

**ULTIboard Entry Designer* £ 1295 (excl. VAT) will now
be supplied with SPECCTRA Shape Based Autorouter
*free Upgrade with EMC-EXPERT mid 1996 (list price at release £ 1875)**

CIRCLE NO. 132 ON REPLY CARD

ULTIMATE
TECHNOLOGY

Corporate Headquarters:
Energistraat 36 • 1411 AT Naarden
The Netherlands

tel.: (+31) 35 - 6944444
fax: (+31) 35 - 6943345

UK/Ireland Sales-Office:
2 Bacchus House • Calleva Park
Aldermaston Berkshire • RG7 4QW

tel.: 01734 - 812030
fax: 01734 - 815323

STABILIZER 5



In any public address system where microphones and loudspeakers are in the same vicinity, acoustic feedback (howlround) occurs if the amplification exceeds a critical value. By shifting the audio spectrum fed to the speakers by a few Hertz, the tendency to howl at room resonance frequencies is destroyed and increased gain is available before the onset of feedback.

★ Broadcast Monitor Receiver 150kHz-30MHz ★ Advanced Active Aerial 4kHz-30MHz ★ Stereo Variable Emphasis Limiter 3 ★ 10-Outlet Audio Distribution Amplifier 4 ★ PPM10 In-vision PPM and chart recorder ★ Twin PPM Rack and Box Units ★ PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and movements ★

SURREY ELECTRONICS LTD

The Forge, Lucks Green, Cranleigh GU6 7BG
Telephone: 01483 275997 Fax: 276477

The Phantom Power Box

48 volt microphone powering unit

Professional portable units operating from an internal PP3 battery or external DC supply



* Suitable for converting any microphone amplifier to P48 standard phantom power * High efficiency DC to DC converter for extended battery life * Accurate line balance for high common mode rejection * low noise and distortion * Extensive RFI protection

The Balance Box (mic/line amplifier) - The Headphone Amplifier Box - The OneStop DIN rail mounting radio frequency interference filter and voltage transient protector for voltage and current loop process signal lines

Conford Electronics Conford Liphook Hants GU30 7QW
Information line 01428 751469 Fax 751223

CIRCLE NO. 133 ON REPLY CARD

WE ONLY USE THE BEST TEST AND MEASUREMENT INSTRUMENTS ON OUR OWN PRODUCTS...



OSCILLOSCOPES

Over 34 models including: Digital, Analogue and Portables. Bandwidths from 5MHz to 150MHz. Sophisticated triggering, single and dual timebases, Multiple channels and large memory Dso's. Prices start from £235 (20MHz 2 Channel £399)

POWER SUPPLIES

Four separate ranges comprising of 40 models from low cost analogue displays to the latest high performance digital units. Providing up to 250 volts and 120 amps with Master-slave, RS 232 and GPIB are available on many models, as are optional rack mount facilities.



AUDIO VIDEO RF

Audio Oscillators, Analysers Wow and Flutter, Millivolt Meters and Distortion Meters Pattern

Generators, Vectorscopes, Waveform Monitors Video Analysers and Noise Analysers. Five models of AM/FM Standard RF Generators offering a highly stable frequency range of 10KHz to 2GHz with digital readouts for Level, Frequency, Modulation and Memory address.

GENERAL PURPOSE

Frequency Counters, Function Generators plus a complete range of accessories to complement the complete range of instruments.



...NOW YOU CAN DO THE SAME

If you like the idea of working with the best, contact us, we can provide brochures with a complete specification for all our measurement products.

**Kenwood UK Ltd, Kenwood House,
Dwight Road, Watford WD1 8EB, England**

TEL: +44 (0)1923 218794
FAX: +44 (0)1923 212905

KENWOOD

Exclusive to *Electronics World* readers Electromail's catalogue on CD for just £2.50



Plus the chance to win a
CD-ROM development
kit worth £649

The Electromail CD-ROM Catalogue is an invaluable tool for anyone involved with electronics. Normally, this CD sells for £5, but Electromail is making it available – exclusively to *Electronics World* readers – at the special price of £2.50 while stocks last.

The Electromail CD-ROM Catalogue makes selecting the products you need – and ordering them – unbelievably quick and easy. It also puts an incredibly powerful source of technical reference at your fingertips.

All you need is a 386 or higher PC compatible with 4Mbyte RAM, CD-ROM drive, VGA monitor, Windows 3.1™ software and a mouse. Just click on the product screen and you get the choice of searching by product type, word or part word, stock number, manufacturer's part number – or any number you care to give a part you use regularly.

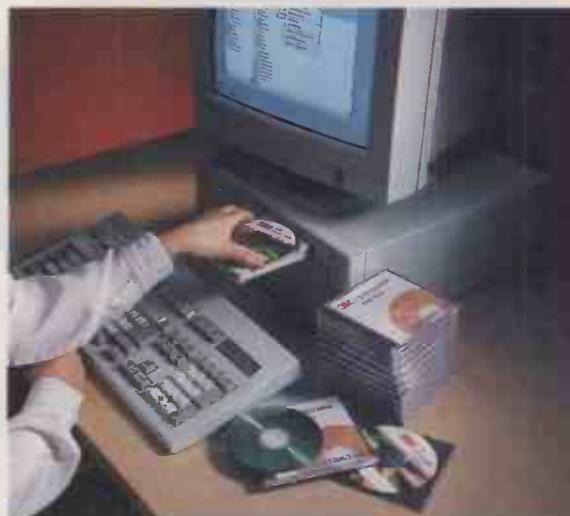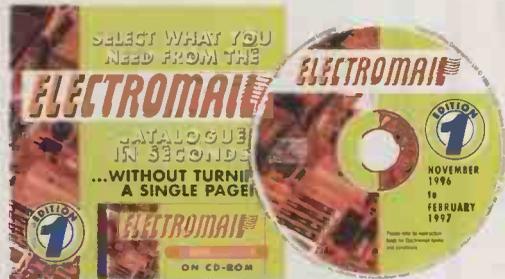If you want to search for several items, Electromail has developed an idea called Virtual Page™ that allows you to search and view all your selections together.




Simply answer the questions on the coupon below and you could win this new development kit, which lets you create your own CD-ROMS – as well as audio CDs.

Called the HP SureStore CD-Writer 4020i, this development kit is designed for an IBM-compatible 486 or higher PC. It provides all the hardware, plus four software applications, to let you build and search databases, copy disk files into standard ISO 9660 format CD-ROM, create audio CDs for playing back in your stereo CD-player and create a prompted slide show of Photo CD images.

The hardware includes an intelligent SCSI-2 interface. All major CD standards are provided and there's a customisable, automated software installation process.

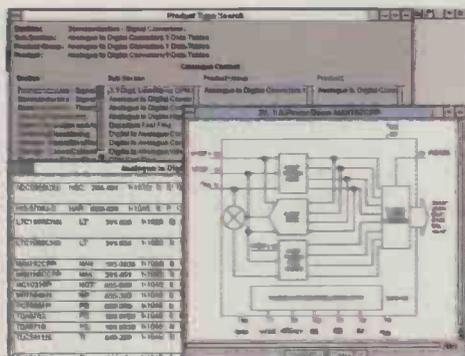CD-Writer records at dual speed and can be used as a CD-ROM player at quad speed. The kit includes two blank CDs.



A wealth of technical data

In addition to product information, certain product groups are backed by extra technical information. To find out more, all you do is click on another icon and a window appears containing the relevant RS data sheet.

The Catalogue also helps you write your order form and prints it out for you – as well as maintaining a history of your recent orders.

The Electromail CD-ROM Catalogue is one of the most advanced technical product Catalogues available, and no one

involved in electronics should be without it – at work or at home.

Please address all correspondence relating to this offer to Electromail, P.O. Box 33, Corby, Northants, NN17 9EL, quoting reference number 234-4857. Tel: 01536 204555, fax: 01536 405555.

Competition rules

- No purchase necessary. ● Entry is limited to one per reader ● Only entries on the official entry form printed in this magazine are valid. Photo copies of the entry form will not be considered ● The winning entry will have answered questions 1-3 accurately, and completed question 4 in the most apt or appropriate way possible. ● The judges' decision is final. No correspondence will be entered into. ● No cash alternative to the prize offered is available ● Only UK residents are eligible for entry ● Employees or agents of RS Components Ltd, or their relatives, are not eligible for entry ● The closing date for receipt of entries is 17:29 ● The winner will be notified in writing by 21:29 and the winners name will be published in this magazine ● Sending an entry confirms acceptance of these rules.

Use this coupon to order your CD-ROM and/or enter the competition

Please send me copies of the Electromail CD-ROM Catalogue at the special reader offer price of £2.50 each, including VAT and P&P. Total value £.....

Name.....

Address.....

.....

Postcode.....

Tel.....

.....

Please debit my VISA Mastercard Amex

Delta (please tick one box)

Card No.....

Expiry date.....

.....

Signed.....

Or, I enclose a cheque for the total order value of £.....

Post your order to Electromail, P.O. Box 33, Corby, Northants, NN17 9EL. Tel: 015636 204 5555. Fax: 01536 405555.

Competition

No CD-ROM purchase necessary. Tick here if you wish to enter the competition only

Questions

1. How many search functions does the Electromail CD-ROM offer?

2. What is the unique feature that enables you to see several selected items on screen at the same time? (tick one box)

Product preview

Slide show

Virtual page

3. In addition to full Electromail Catalogue information, what other powerful source of data does the Catalogue contain? (tick one box)

- OEM catalogues
- Full RS data sheet library
- Press cuttings from this magazine

4. Write in the most apt or appropriate way, in fewer than 12 words how you feel the Electromail Catalogue will add advantages to your technical endeavours.

.....

.....

.....

.....

Reference number 234-4857

Your pc is a programmable event timer capable of precision gating up to 55ms. Alan Bradley describes how to configure it.

Event timing via the pc

Timer channel 2 is present in all pcs. It is normally used as a variable frequency square wave generator for the pc's speaker. But this timer can also be used as an interval timer that is independent of the processor type and speed. This article describes how.

Overview

Timer 2 is within the pc's programmable universal counter/timer. This IC contains three counter/timers each with an associated control register. The original IBM pc used an Intel 8253, the IBM AT an Intel 8254. Modern clones may use custom ICs, but all have the same programming model. This universal counter/timer operates at 1.193MHz irrespective of the processor's type or clock speed. All three counters are 16 bits wide.

The three counter/timer channels, namely 0,

1 and 2, are accessed through ports 40₁₆, 41₁₆ and 42₁₆ respectively within the pc's i/o port address space. The command register is located at port 43₁₆. It selects the mode for reading and writing values to the chosen channel, selects the type of use for that channel, and selects the channel to which the previous selections apply. Examples of uses for the channel are square wave generation, one shot pulse production and terminal down count.

Applying the counter/timer

Timer channel 0 is used to calculate the time of day. This channel is set up by the bios to give 18.2 pulses per second. Each pulse causes the timer interrupt, IRQ 0, after which the counter is reset. A four-byte counter for these timer pulses is stored in the bios data area at 0040:006C₁₆. This counter also synchronises

disk operations. Reprogramming it might therefore damage disk reads and writes.

Timer channel 1 is used by ram refresh and also by disk operations. Reprogramming this channel may also cause loss of disk data.

Timer channel 2 is connected to the pc's internal speaker, generating the variable frequency square waves necessary to make simple sounds. The speaker can be turned on and off via the pc's parallel-peripheral interface chip. As this channel controls no vital hardware, and the speaker can be turned off, it can be set up as a timer. A possible use is determining the waiting period for an analogue to digital conversion.

The 8255 programmable peripheral

Timer 2 is also controlled by the pc's 8255 peripheral interface chip, or PPI. This device

Applying the timer

This pseudo-code program illustrates how the pc can form a monostable multivibrator by using timer-channel 2 in conjunction with the parallel printer port. The printer port provides the digital i/o lines for the trigger and o/p.

This pc monostable is not retriggerable, although it could easily be made so. It has a timed period of 40ms. The parallel-port input line that normally signals printer error, abbreviated PE, is used as the monostable trigger input. If it goes low, the monostable is triggered. Parallel port output line D₀ is used as the monostable output. It goes high when triggered, remains high until chosen time period has passed.

Pseudo code for a 40ms monostable multivibrator

Find location of printer port registers.

Reset monostable: set its output low: ie set printer port output data line D₀ low (pin 2 on D connector).

Set up PPI B register to allow timer-channel 2 to be used as a down counter.

Set up Timer channel 2 to select down count mode, a binary count, and READ/WRITE msb and lsb consecutively mode.

For a downcount from FFFF₁₆,

Calculate FinalTimerDownCount for a 40ms delay.

Print title message.

WHILE (forever).

IF printer port input pin PE (pin 12 on D connector) is low then:

Trigger monostable output: ie set printer port data output line D₀ high.

Load counter with maximum count value (FFFF₁₆) and start down count.

Print "triggered: output (D₀) goes high"

Wait for 40ms.

```
Reset monostable: ie set printer port D0 (pin 2
on D connector) low.
Print "Reset: output (D0) goes low"
END_IF
```

```
END_WHILE
END
```

The pc parallel port

A pc can have up to three parallel printer ports LPT1, LPT2, and LPT3. Each port interface has three 8bit registers, the data latch, the status register and the control register.

Data latch: writing to this register causes the byte sent to be latched and appear on the parallel port's 25-way D connector on pins 2 to 9. Normally reading this register returns the contents of the latch.

Status register: this register represents input lines from the printer with functions as follows: b₇ BUSY, b₆ ACK, b₅ PE b₄ SLCT and b₃ ERR. Bits b_{2,0} are unused. This is a read only register. The BUSY input is inverted between the D connector and the register.

Control register. Bit functions of this register are, b₄ IRQ DISABLE, b₃ SLCTINP, b₂ INIT, b₁ AUTOFEED, b₀ STROBE. Bits b_{7,5} are not used.

This is a latch holding printer control signals. Interrupt is disabled on a falling ACK input when b₄ is low. I always disable this interrupt as it is rarely used by printer software so the associated IRQ channels 5 and 7 are considered free, and available for other expansion cards.

STROBE, AUTOFEED and SLCT INPUT are inverted between the register and D connector output pins although this inversion is corrected again when the control register is read.

controls the keyboard and is used to obtain information about the pc's configuration. It also controls the pc speaker and the speaker's associated timer on channel 2.

Port A of the PPI is a read/write port associated with the keyboard. Port B controls the reading mode for ports A and C. It also controls the speaker and timer channel 2. Port B is located at port 61₁₆ in the pc's i/o address space.

Using timer 2 as an interval timer

I wrote the interval timing code in a mixture of C and assembly language. This is because the C compiler generated a much slower shift-by-8 loop. It did not make use of the 80x86 processor's ability to treat 16-bit data registers as 8-bit pairs, ie AX=AH+AL, BX=BH+BL, CX=CH+CL and DX=DH+DL.

The 80x86 has four more registers, SP, BP, SI and DI. These are normally used as pointer and index registers. In my program I used the DI register simply to store 16-bit data. Turbo


C uses SP, BP and SI itself. The DX data register is also used in some IN/OUT instructions results and so cannot be used by my program.

The 8086 has four segment registers, namely CS, DS, SS, ES. These allow addressing over 64K. The C compiler sets these to appropriate values automatically. The 8086 has an instruction pointer, similar to a program counter. It also has a FLAGS register, recording the result of instructions such as NON-ZERO and OVERFLOW.


Counting is interrupted if the GATE2 input is switched to a low level and restarted when the GATE2 input is switched back to a high level. Hence GATE2 should be high for a down counting interval timer.

Therefore my program sets bit 0 of the PPI B register to logic 1. I also disable the pc speaker by setting bit 1 of the PPI B register to 0. Inset 1 shows the Timer control register bit pattern required to select down count mode for Timer channel 2 and the timer control register bit pattern required to perform a latch operation on Timer channel 2.

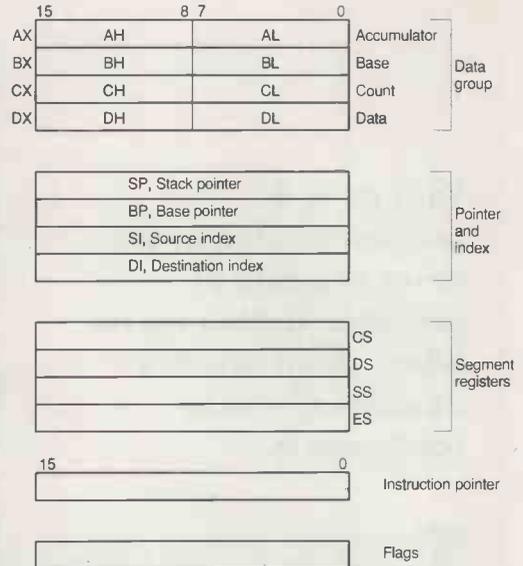After the latching command has been writ-



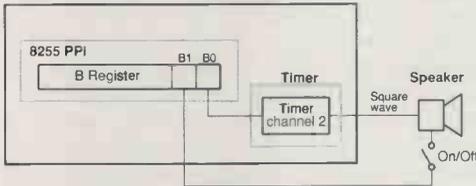80x86 registers, common to all IBM pcs. My C compiler could not treat 16-bit registers as 8-bit pairs, and a shift-by-eight loop is much slower than it needs to be. I used assembly language instead.




Standard on all pc compatibles, Timer channel 2 of the 8253 universal counter/timer ic forms the speaker driver which is controlled via Port B of the 8255 programmable peripheral interface ic but, as can be seen, the speaker can be switched off and the timer put to better use.

Control register bit usage for the pc's 8253 timer ic

PC I/O address of timer control register is 043 hex.

| Location | Bits 7,6 | Bits 5,4 | Bits 3,2,1 | Bit 0 |
|----------|--|--|--|----------------------------|
| Function | Select counter channel | Select latch operation or type of read/write | Mode | Select binary or BCD count |
| Code | Number of the channel to be programmed (0, 1 or 2) | 00 Latch current value of counter (done before a read operation) 01=Read/Load lsb 10=Read/Write msb 11=Read/Write lsb followed by msb | Select counter/timer mode 000=Terminal down count 001=Programmable one shot x10=Rate Generator x11=Square Wave Generator 100=Software triggered strobe 101=Hardware triggered strobe | 1=BCD 0=Binary |

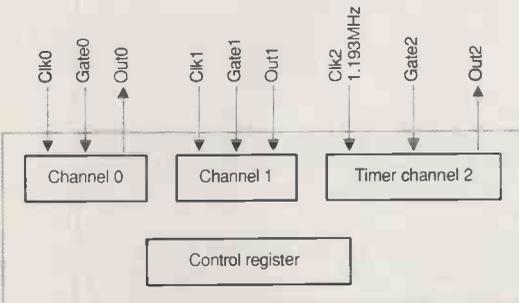

Block diagram of the pc's 8253 programmable universal counter/timer. Timer channel 2 counting is enabled when GATE2 is taken high.

Programmable peripheral interface

B register bit usage
PPI B register PC i/o address is 061₁₆.

| Bit | Purpose |
|-----|---|
| 0 | Set Timer channel 2 gate i/p high or low |
| 1 | Link/unlink timer 2 o/p from speaker: 0=off if unlinked |
| 2 | Must be 0 |
| 3 | Read high or low dip switches |
| 4 | 0=enable ram parity check, 1=disable |
| 5 | 0=enable i/o channel check |
| 6 | 0=hold keyboard clock low |
| 7 | 0=enable keyboard, 1=disable |

C pseudo code for pc timing

Calculate final count value for a 10µs delay. Calculate number of clock ticks in a 40,000µs delay.

```
PRINT "Preparing Count Down"
FINAL COUNT VALUE FOR 40,000µs DELAY:=FFFF-(number of clock ticks in a 40,000µs delay)
```

Now set up Port B of the PPI so that Timer2 can be used as a terminal down counter and disable speaker: ie set Timer gate 2 high (via PPI Port B, bit 0) (allow counting in Timer channel 2) and disable speaker (via PPI Port B, bit 1)

Set Timer Gate 2 HIGH (allow counting)

Now set up channel 2 of the timer to count in binary, perform a terminal down count and choose option: read/write lsb, msb one after the other, by writing appropriate value to the timer control register.

```
PRINT "Starting Count Down"
write FF16 (lsb) to timer channel 2
write FF16 (msb) to timer channel 2
REM: down count from FFFF16 has now begun.
Loop until 10µs has passed
Print "Ten microseconds have now passed"
Loop until whole 40,000µs delay has elapsed.
PRINT "Entire chosen timed interval of 40,000µs=40ms has now passed"
END
```

ten to the timer control register, the latched value can be read from timer channel 2 (042_{16}), least-significant bit first. According to the 8253 data sheet, a counter value of 0000 can not be read.

Programming the chosen delay

First calculate the number of counter clock ticks that equal the chosen delay interval. This is the number which the counter must count down past before the chosen interval has passed. The number of timer clock ticks before interval has passed is equal to the chosen delay interval in microseconds, multiplied by 1.193MHz.

I always start the down count from $FFFF_{16}$. In this way, when the current counter value is less than or equal to $FFFF_{16}$ minus the number of clock ticks before interval has passed, then the chosen delay interval will have expired. For example, for a 40,000µs delay:

No. of clock ticks=
 $40,000 \times 1.193 = 47720 = BA68_{16}$

Final timer downcount=
 $FFFF_{16} - BA68_{16} = 4597_{16}$.

The maximum delay is 55ms.

Example timing program in C

This timing program example is derived from my printer port sound sampler program, where I needed to wait 10µs for the a-to-d converter to complete a conversion, process this value, then wait until the end of the sample period before repeating the loop.

Outlined in the timer software panel **Inset 2**, this routine waits until the first 10µs of a 40,000µs delay has elapsed, then waits until the whole 40,000µs delay has passed.

C and Assembler details of Timer.C

The program compiles under Borland Turbo C++ and Borland C++. This allows the 80x86 registers to be used by name within a C program's asm{ } assembly blocks. Registers can also be accessed from C by preceding the register name with an underscore, eg `_AX`, `_AH`, `_AL`...

The program uses # defines to give PPI Port B, and timer control register and timer channel 2 port addresses meaningful names.

Timer channel 2 is read by sending a latch command via the Control register, then simply reading the lsb, then the msb from Timer channel 2, port 042_{16} . ■

Software on disk

The Timer.c routine and the full monostable example in c can be obtained by sending a cheque of postal order for £7.50 to *Electronics World's* editorial offices. Please mark the envelope Timer software and make your cheque payable to Reed Business Publishing Group.

Timer control register usage for interval timing.

PC i/o address 043_{16} .

Using terminal down count mode, this is timer control register bit usage to set up a down count.

| Bit | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
|----------|------------------------|---|---|---|------------------------------------|---|---|------------------------|
| Setting | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| Function | Select timer channel 2 | | Select type II read/write operation: LSB is first written to timer 2 (042_{16}) then MSB is written to timer 2 (042_{16}) counting begins as soon as MSB is written | | Select mode 0: terminal down count | | | Select binary counting |

Timer control register bit usage to perform a latch operation, current counter value prior to a read operation.

| Bit | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
|----------|------------------------|---|---|---|------------------------------------|---|---|------------------------|
| Setting | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| Function | Select timer channel 2 | | Select latch current value of counter operation | | Select mode 0: terminal down count | | | Select binary counting |

Accuracy of the pc as a timer

Instructions for reading and checking the current value of timer channel 2 take a finite amount of time, adding inaccuracy to the timing. I have calculated the worst-case delay between timer-channel 2 reaching its chosen final count value. With the program Timer.c, described later, the worst case inaccuracy for an 8MHz ISA i/o bus pc should be 7.144µs:

Calculation of Timer.c program timing limits:

| | 80x86 instr | 8MHz i/o cycle | 80386 cycle |
|--|---------------------|----------------|-------------|
| START TIMER channel 2 count: | mov reg, immed | | 2 |
| | OUT immed,al | 10 | |
| | OUT immed,al | 10 | |
| Send Counter latch command: | mov reg,reg | | 2 |
| | OUT immed,al | 10 | |
| Read and store timer lsb: | in al, immed | 12 | |
| | mov reg, reg | | 2 |
| Read and store timer msb: | in al, immed | 12 | |
| | mov reg, reg | | 2 |
| Compare msb:lsb of current timer value with FinalTimerDownCount: | cmp reg, reg | | 2 |
| 'WHILE': | ja 8bitdisplacement | | 3 |

(no jump occurs)

Total clock cycles=54 i/o clock+13 processor clock cycles

For a 33MHz 386 pc this would give a worst-case error of:

inaccuracy = i/o clock delay+processor clock delay
 $= 6.75\mu s + 0.4\mu s = 7.144\mu s$

According to my assembly language book, IN/OUT 386/486 instructions vary in the number of clock cycles they need. I have used the slowest timing, which is similar to that of the 8086/8. The 286 IN/OUT instructions are about twice as fast as those of an 8086/8.

Greater accuracy in small delays would need interrupt programming, which is more difficult to write. This would involve reprogramming timer-channel 0, which needs care to avoid affecting disk operations; timer-channel 2 has no associated interrupt.

Small delays are often needed. When reading an a-to-d converter value for example, the 7µs inaccuracy can be important. In longer delays the 7µs may be insignificant. The inaccuracy should reduce on local-bus machines and on fast ISA buses that unofficially run at 11MHz.

C code for controlling the pc's timer

This program, Timer.c, demonstrates using timer 2 as a down counter to measure time intervals. Written in Turbo c with in-line 8086 assembler. Small memory model: 64K code 64K data and stack. Register keyword enabled.

```

#include <stdio.h>
#include <dos.h>
#include <conio.h>
#include <stdlib.h>
#include <io.h>

/* Prog PPI port B, TimerControl, & Timer2 regs */
#define PPIportB 0x061
#define TimerCtlReg 0x043
#define Timer2 0x042

/* 'register' vars: #defs for direct access to */
/* DI,CX,CH,CL via meaningful names */
#define FINALTIMERDWNCOUNT DI
#define MSB CH
#define LSB CL
#define COUNT CX

/* if counter starts at FFFF16 then : */
/* (val of cntr after 10µs) ≥ FFFF - (10µs * 1.193MHz) */
/* thus tenMicroSecDwnCount = (FFFF - C) hex = FFF3 hex */
#define tenMicroSecDwnCount 0xffff3

/* clock frequency is 1.193MHz */
/* #def to set No of 1.193MHz clock tick decrements */
/* to pass before chosen timed interval has passed: */
/* noofclockticks = chosen interval in µs * 1.193MHz */
/* = 40,000 * 1.193 = 47720 dec = BA68 hex */
#define NoOfClockTicks_inFortyMilliSecDelay 0xba68

/* temporary store for B register of PPI IC */
unsigned char breg;
int main() {
    puts("\nPreparing count down\n");

    /* set FINALTIMERDWNCOUNT: */
    /* = 0xffff - NoOfClockTicks_in... delay */
    asm {
        mov ax, 0xffff;
        sub ax, NoOfClockTicks_inFortyMilliSecDelay;
        mov FINALTIMERDWNCOUNT, ax;
    }

    /* Set portB of PPI for timer2 as down counter instead
    of driving speaker */
    /* 1st get a copy of PPI port's B register */
    breg = inp( PPIportB );

    /* logic OR with 0000 0001 to set bit 0 (timer gate)
    high */
    breg = breg | 0x01;

    /* AND with 1111 1101 to set bit 1 (spkr data) off */
    breg = breg & 0xfd;

    /* set up 8255 PPI port B for speaker off & timer gate
    high */
    outp( PPIportB , breg );

    /* Now set up channel 2 (Timer2) of Timer chip:— */
    /* send 1011 0000 to Timer control reg to select: */
    /* Channel2, oper 11 (r/w both h&l
    bytes), terminalcount, binary data */
    outp( TimerCtlReg, 0xb0 );
    puts("\nStarting count down\n");

    /* set value (FFFF) from which timer counts down */
    asm{
        /* first o/p count low byte (FF) */
        mov al, 0xff;
        out Timer2, al
        /* o/p high byte (FF); timer starts on writing high
        byte */
        out Timer2, al
    }
    /* down count from ffff has now started */

    /* now wait until ten microseconds has passed */
    /* 10 00 000 0 is 8 hex */
    /* 10:ch 2, 00:ctr latch, 000:term cnt, 0:bin data */
    /* store above in ah for speed */
    asm{ mov ah , 0x80 }

    /* loop until 10µs or more has passed */
    label1DO: asm
    {
        /* read ctr latch command from ah into al for I/O
        instr */
        mov al, ah
        /* now send latch command to timer */
        out TimerCtlReg, al
        /* now read lsb from timer2 */
        in al, Timer2
        /* now store lsb */
        mov LSB, al
        /* now read msb from timer2 */
        in al, Timer2
        /* now move msb into highbyte of COUNT */
        mov MSB, al
        /* while COUNT holds value > tenMicroSecDwnCount */
        /* ie while timer2 value > tenMicroSecDwnCount */
        cmp COUNT, tenMicroSecDwnCount
        ja label1DO
    } /* WHILE COUNT > tenMicroSecDwnCount */
    puts("\nTen microseconds has now passed\n");

    /* now wait until end of chosen interval */
    /* (wait for count down past FINALTIMERDWNCOUNT) */
    /* 10:chann 2, 00:counter latch command, */
    /* 000:terminal down cnt, 0:bin data */
    /* store above 10000000b byte in ah for speed */
    asm{ mov ah , 0x80 }
    label2DO: asm
    {
        /* read ctr latch command from ah into al for i/o
        instr */
        mov al, ah
        /* send latch (0x80) command to Timer */
        out TimerCtlReg, al
        /* read lsb from timer2 */
        in al, Timer2
        /* store lsb in low byte of count */
        mov LSB, al
        /* read msb from timer2 */
        in al, Timer2
        /* move msb into highbyte of count */
        mov MSB, al
        /* while timer2 value > FINALTIMERDWNCOUNT */
        cmp COUNT, FINALTIMERDWNCOUNT
        ja label2DO
    }
    /* NOTE ! timer count value of 0000 cannot be read */

    printf(
        "\nEntire chosen timed interval of 40,000µs =
        40 msec has now passed\n\n");

    return 0;
}

```



Field Electric Ltd.

Tel: 01438-353781 Fax: 01438 359397

Mobile: 0836-640328

Unit 2, Marymead Workshops,
Willows Link, Stevenage, Herts. SG2 8AB.



| | |
|--|-----------------|
| TEAC New & Boxed N/Book: | |
| L/Top Floppy Disc Drive FD 05HF 4630V | £24 |
| Sony 9" Super Fine Pitch Trinitron RGB VDU | £35 c/p 12.50 |
| AT Keyboards for IBM Compatibles | £5.99 |
| 12" Colour SVGA 800 x 600 NEC | £45.95 c/p 14 |
| Marconi Inst = Data Comms Tester | £385 |
| Marconi Inst = Digital Line Monitor | £350 |
| Marconi Inst = Digital Analyser | £375 |
| Farnell PSU 0-70V 0-5A/0-30V 0-10A | £245 |
| Siemens Data Line Analyser K1190 with manual | £300 |
| Black Star Multimeter 3225 | £55 |
| Tektronix DAS9100 Digital Analysis System | £175 |
| Tektronix 7A18 D.T. Amp | £75 |
| Tektronix 7B53A D.T. Base | £75 |
| Tektronix 7A15A Amp | £150 |
| Tektronix 7511 Diff = Comp = | £100 |
| 12 VAC 200 Watt Transformer | £15 |
| 27 VAC 30A Transformer New | £15 |
| Tseng Labs 1Mb 16 bit ISA SVGA Card | £16.75 c/p 4.00 |
| Contains 50W PSU. Fan 2 x 16 bit. 1 x 8 bit Slot. New & Boxed | £24.99 |
| Philips PM 3240. 50 Mhz. Scope D/Trace | £165 |
| Philips PM 3233 10 Mhz D/Trace Scope | £65 |
| Leader LMV 181A AC Millivoltmeter | £145 |
| Racal Inst. 9915 UHF Freq: Meter 500Mhz | £100 |
| Racal Inst. 9916 UHF Freq: Counter 500Mhz | £145 |
| HP 8413A Phase Gain Ind: | £90 |
| HP 7475 8 Pen Plotter RS232 | £55 |
| HP Colour Pro 8 Pen Plotter RS232 | £75 |
| HP 7470A Plotter HPIB | £95 |
| Compaq 14" Mono VGA (Paper White) Refurb: 720 x 400. Text | |
| 640 x 480 Graphics | £29.50 |
| Roland DG XY DXY 980A 8 Pen Plotter. Needs PSU | £60 |
| Roland DG XY DXY 880A 8 Pen Plotter. Needs PSU | £60 |
| 14" VGA Colour Monitors. Various makes from | £75 |
| PLOTTERS • COMPUTERS • COMMUNICATIONS • PSU • VDU's • VIDEO • | |
| FANS • TEST • CABLE • NETWORK • PRINTERS • | |
| DISK DRIVES ALWAYS IN STOCK. OVERSEAS ENQ. WELCOME. | |
| TELEPHONE ORDERS ACCEPTED. | |
| C/P DETAILS PLEASE RING. ALL PRICES PLUS 17.5% VAT. | |

CIRCLE NO. 135 ON REPLY CARD

'OFF-AIR' FREQUENCY STANDARD



CIRCLE NO. 136

- ★ Provides 10MHz, 5MHz & 1MHz
- ★ Use it for calibrating equipment that relies on quartz crystals, TCXOs, VXCOs, oven crystals
- ★ Phase locks to DROITWICH (rubidium controlled and traceable to NPL)
- ★ For ADDED VALUE also phase locks to ALLOUIS (cesium controlled and traceable to OP — French eq to NPL)
- ★ British designed and British manufactured
- ★ Options available include enhanced receiver, sine wave outputs and 13MHz output for GSM. Prices on application.

Output frequencies —
10MHz, 5MHz, 1MHz
Short term stability — better
than 1×10^{-8} (1 sec)
Typical — 4×10^{-9} (1 sec)
Long term — tends to
 2×10^{-12} (1000 sec)
Call for "Off-Air" Standard list

TEST EQUIPMENT **CIRCLE NO. 137**

We are well known for our quality, new and used Test Equipment. Our list is extensive, ranging through most disciplines. Call for details and a complete list

| | | |
|---------------------------------|----------------------------------|------|
| Marconi Spectrum Analyser | Marconi LCR Bridge TF2700..... | £149 |
| TF2370 | Marconi LCR Bridge | £125 |
| Bradley Oscilloscope Calibrator | TF1313A | £125 |
| 156 | Mahogany Cased 5kV Megger | |
| Bird Termaline, 2.5kW 50Ω..... | (Collectors)..... | £POA |
| Philips Function Generator | Taylor Valve Tester 474 | £59 |
| PM5134..... | Philips RF Generator PM5326 | £395 |
| Hitachi Oscilloscope V222, | HP Frequency Counter | |
| 20MHz | HP5340 | £595 |
| 20MHz | Taylor AM/FM Generator 62A | £69 |
| Philips Pulse Generator | Marconi Attenuator TF2163 | £195 |
| PM5716..... | RE Mega-Ohmmeter/pica- | |
| Amprobe AC Recorder LAV3X | Ammeter IM6..... | £295 |
| Amprobe Temperature Recorder | Ferroglyph Recorder test Set | |
| LT8100..... | RTS2..... | £95 |
| Emerson UPS 1.5kW | HP Vector Voltmeter | |
| | HP8405A..... | £249 |



HALCYON ELECTRONICS



423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR
SHOP HOURS 9-5.30 MON-SAT. TEL 0181-542 6383. FAX 0181-542 0340

YOUR Ideal Partner in UHF and VHF COMMUNICATION



One stop solutions for all your radio telemetry module needs.

When the success of your products depends on radio telemetry modules, you need a business partner you can trust. A skilled and experienced manufacturer that can offer modules of the highest quality, operating over a wide range of frequencies.

In other words, a partner like Wood & Douglas. Founded on technical excellence, Wood & Douglas is a British company that specialises in the design, development and production of radio-based products. With over 30 staff dedicated to meeting your requirements, the company is able to provide true one-stop purchasing - whatever your RTM needs.

All radio modules are highly functional, capable of meeting a wide range of requirements. Designed to offer efficient, easy-to-use radio telemetry components for system designers, they can open up a whole new world of product possibilities.

From portable bar-code readers to earthquake monitors, Wood & Douglas can help you make the most of the opportunities in radio telemetry.

To find out more about the possibilities, contact...




Lattice House, Baughurst, Tadley, Hampshire RG26 5LP, England
Telephone: 0118 981 1444 Fax: 0118 981 1567
email: info@woodanddouglas.co.uk
web site: http://www.woodanddouglas.co.uk

Finding faults with sound

Once a component is packaged, it is notoriously difficult to check the integrity of the package's content. Steve Martell describes a new ultrasonic defect detection method that allows surprisingly detailed board inspection.

Fig. 1. Scan head visits each on-board component to perform non-destructive acoustic imaging for hidden internal defects.

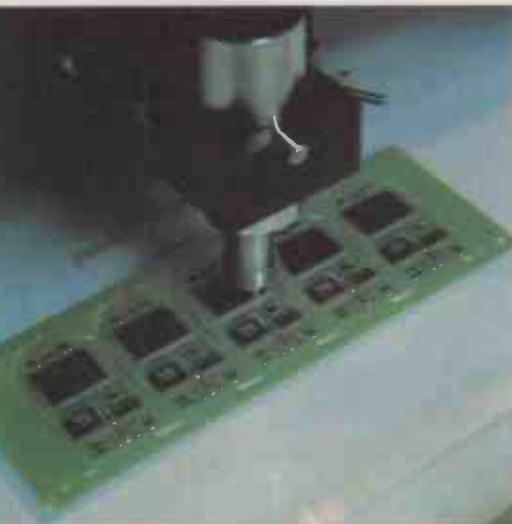

The term 'hidden internal defect' has particular meaning to companies who manufacture or mount plastic integrated circuit packages. Hidden defects are defects in, or related to, the physical structure of the package; they include delaminations, disbonds, voids, cracks, and the like. They cannot be seen optically, and few can be detected by x-ray. Still, it is vital to find these defects. They frequently worsen due to thermal cycling, causing the system they are installed in to fail unexpectedly. In short, hidden internal defects are flaws just waiting to turn into field failures.

Understandably, much research has gone into the characterising of the numerous types of hidden defects which may be lurking in an IC package. Delaminations in the die attach material are one type. Military and commercial specifications generally state, for example, that small delaminations in the die attach are not sufficient cause to reject the IC package – unless the delaminations happen to be at the corners of the die.

Even small corner delaminations, experience has shown, will grow because of the stresses located there. Eventually they detach so much of the die from the die paddle that heat sink capability is lost. The die then overheats and fails. Other hidden defects – die face delaminations of the molding compound, for example, or voids in the underfill near a flip-chip bump – are considered lethal in virtually all applications.

The sound option

Acoustic microscopes are by far the most useful tools for finding and characterising hidden internal defects. Almost all such defects consist of gaps in material, and very-high-frequency ultrasound is extremely sensitive to gap-type defects.

Failure analysis laboratories use acoustic microscopes to image the interior of IC packages for 'popcorn' cracks, lead frame delaminations, voids (bubbles) in the molding compound, cracked die, and many other defects. Some defects are imaged even though they do not consist of gaps: tilted die and irregular dis-

tribution of filler particles in the molding compound epoxy are two examples.

Finding hidden defects as early as possible in the production process is important to makers and users of IC packages. Failure analysts therefore often look at packages fresh from the mold machine which has encapsulated the die-lead frame assembly in epoxy. But failures can occur at many points in production, and it is not unusual for a manufacturer to be faced with a large quantity of populated boards some of whose IC packages are known to harbour hidden defects. This is a very significant inspection problem; no one wants to remove all of the packages from all the boards and submit each package to acoustic inspection.

A scanner for board-level inspection

A new system performs acoustic microscopy inspection on IC packages while they are still mounted on the board. It handles different types, sizes and elevations of IC packages on the same board, and can also image ceramic chip capacitors and some types of resistors.

The system operates automatically, can handle any number of components per board, and can handle two-sided boards. Its output shows both good and bad components and the locations of internal defects. Sonoscan, Inc. of Bensenville Illinois, the firm which developed and manufactures the system, call it *UltraBoard*.

Observing the system in operation, you see the board being inspected resting in a shallow water bath; a fluid is necessary to acoustically 'couple' the components to the transducer above the board, since very-high-frequency ultrasound does not travel through air.

The transducer is guided by software which has learned the coordinates of each IC package or other component it will inspect. Following this route, the transducer arrives at each component and then, because components are sometimes not placed precisely, uses ultrasound to find the actual location of the component. It then spends about 15s scanning the component.

As the head scans, very high frequency

ultrasound – generally between 10MHz and 100MHz – is beamed into the component. The return echoes from the interior of the component are collected by the same transducer for analysis.

When ultrasound is emitted by the transducer, it travels through the water couplant and enters the top surface of the IC package beneath the transducer. The speed of ultrasound through the various materials inside the IC package varies from about 3000m/s to about 9000m/s.

In a typical IC package, ultrasound travels first through the epoxy at the top of the device, and then encounters the face of the die. At this point some of the ultrasound is reflected back to the transducer, which has already switched over to its receiving mode. Data in this return echo is used to image the die face. At the same time, some ultrasound passes downward into the die itself, where it successively encounters the die-to-die attach interface, the die attach material itself, and the die attach-to-die paddle interface. Each interface in turn sends its return echo back to the transducer.

Returned signal

Each echo arrives back at the transducer bearing a given amplitude, or intensity, as well as polarity information. Polarity describes the change in acoustic velocity between two successive materials. If the ultrasound passes from a material of lower acoustic velocity to a material of higher acoustic velocity, the polarity change is positive; if the reverse, the polarity change is negative.

If no defects are present in the IC package, the pseudocolor image which appears on the monitor will show the die, the die paddle, the lead frame, and any other normal internal features. If a hidden internal defect is present, though, something quite different occurs.

Suppose there is a delamination at the top of the die, between the die surface and the molding compound. When ultrasound strikes this



Fig. 2. Digital image analysis of a single UltraBoard image. Original image with 256 grey levels – here in pseudocolor – is reduced to two levels at left for analysis. 'Window' refers to whole area of the chip. 34.6% of whole die attach area is delaminated, as is 75.0% of the upper left quadrant of the chip. 'Large' gives percentage covered by largest delamination in each area; i.e., the large delamination in the top-left quadrant covers 19.5% of chip area.

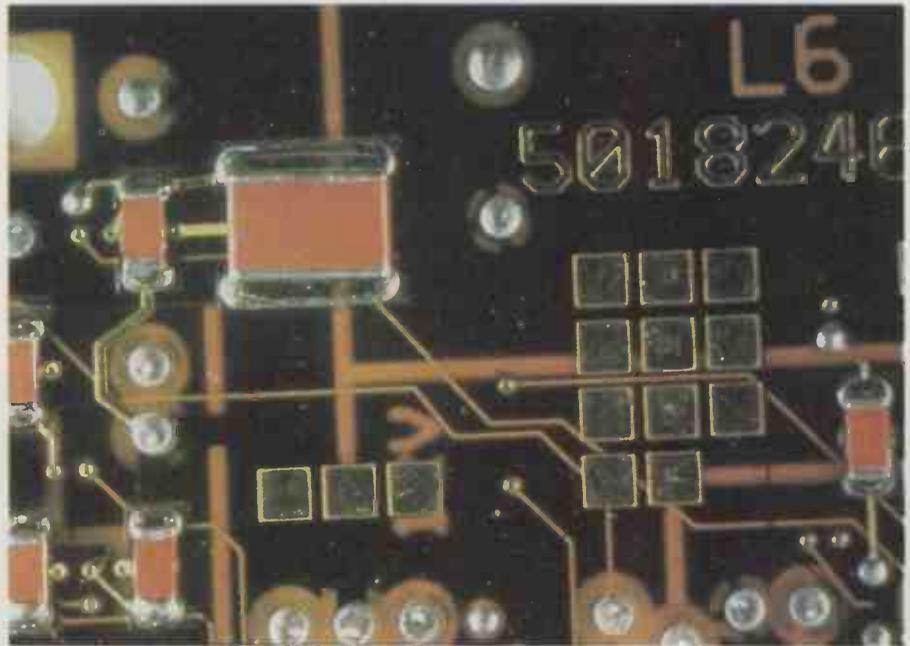


Fig. 3. Optical photograph of ceramic chip capacitor mounted on board.

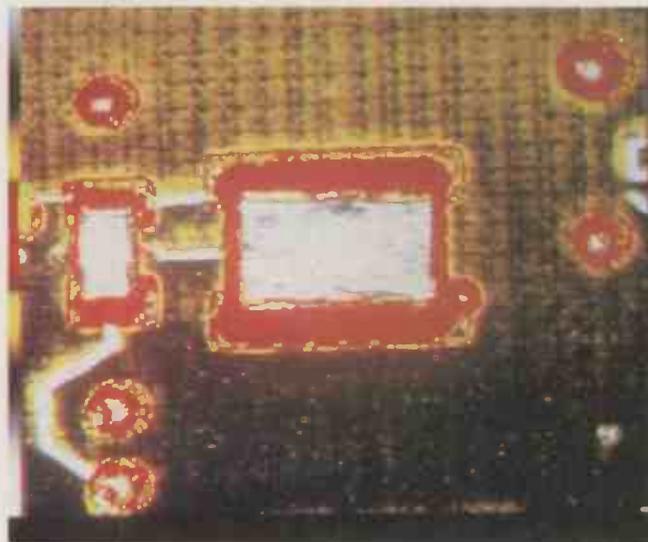


Fig. 4. Effect of electronic gating to limit internal level being imaged: when gating is near top surface, multilayer ceramic chip capacitor shown in Fig. 2 displays only merest suggestion of an internal crack at its lower edge.

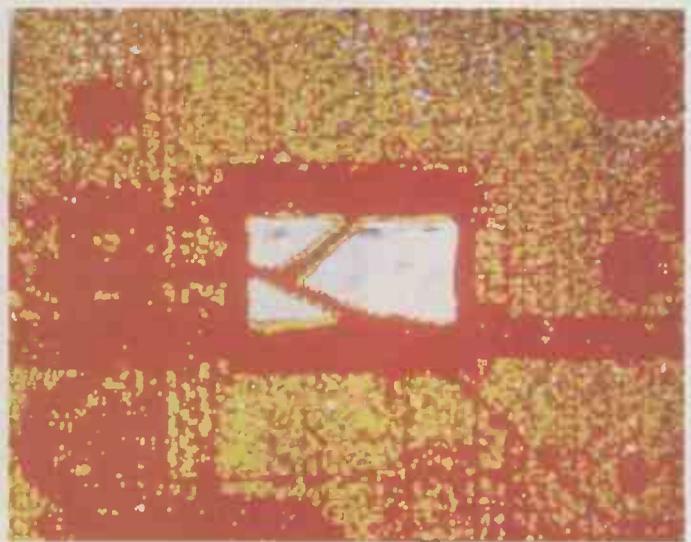


Fig. 5. When gating is lowered to mid-point of capacitor, substantial internal cracking becomes evident.

delamination – which is a gap – all of the ultrasound is reflected back to the transducer. Just as very-high-frequency ultrasound will not travel through air, it will not travel across an internal gap. The thickness of the gap is unimportant; if two internal layers are in contact but not bonded, all of the ultrasound is still reflected.

The amplitude of the echo returned from a gap is of course high; this is a very energetic echo. The echo also contains its own polarity information. As the transducer scans back and forth over the area of the IC package, it is collecting data points from hundreds or thousands of return echoes, including those echoes returned by gap-type defects at interfaces or in the bulk of a material. The data points are assembled electronically to produce the visible crt image of the interior of the IC package, and to analyse the package in various ways.

The echoes returning from the interior of the package are also separated in time as they arrive back at the transducer. In most applications, the echoes are electronically gated to accept echoes only from a defined level within the package and to ignore all other echoes. The die attach, for example, may be a suspected location for defects such as voids or delaminations.

Return echoes are then gated to accept echoes from the bulk of the die attach materi-

al and from the two interfaces at top and bottom of the die attach material. In other situations, gating may be wide or narrow, depending on the thickness of the zone to be inspected. Multiple gates – die face plus die attach, for example – can also be used.

And for smaller defects...

In addition to large defects, such as a delamination covering the entire face of a die, very-high-frequency ultrasound is capable of imaging very tiny defects and of detecting even smaller ones. Ultrasound of 100MHz, for example, is used analytically to map the distribution of individual filler particles in molding compounds.

Sonoscan has recently developed and introduced a long-reach transducer which puts out ultrasound at the very high frequency of 180MHz. This transducer was specifically designed to image the solder bumps and underfill which lie beneath the die in flip-chip devices. Its resolution is so good that it has imaged voids and cracks in the interior of individual solder bumps.

Output methods

Information from a board whose components have been scanned by the system takes several forms. The acoustic representation of each image is stored; this image is not normally

viewed, but is available for analytical purposes if it is needed.

If a defect is present, the data is also used to perform an area analysis of the defect. The analysis is based on definitions set up by the user of the system. A die attach delamination, for example, may be acceptable if it covers less than a given percentage of the die attach area, or if it is in a given location, for example, anywhere other than a corner. Similar definitions can be set up for die face delaminations, cracks in the molding compound, delaminations along the lead frame, and numerous other defect types.

Software can sort the components on the board into any defined number of accept/reject categories. Often three categories – accept, marginal, and reject – are used, because this gives the user the opportunity to examine the images of marginal components before making a decision about rework.

The system also prints out a table for each board, showing the location of each inspected component and its accept/reject status. The table then travels with the board as a guide to the rework which will transform it into a defect-free board. ■

Sonoscan, Inc. is at 530 East Green St, Bensenville IL USA 60106, phone: 630 766-7088, Fax: 630 766-4603, E-mail: sonoscan@worldnet.att.com.

**The Art
Of In-Circuit
Emulation**

8051 SABC16X 80x86

Contact us now for comprehensive information on the Hitex range of state-of-the-art microprocessor tools.
Hitex (UK) Ltd. TEL:01203 692066 FAX:01203 692181
Email:sales@hitex.demon.co.uk
CompuServe: 100646.1526

hitex



Cooke International Services
wishes you a



SANTA'S STOREHOUSE
for all your
TEST EQUIPMENT
also
OPERATING AND SERVICE
MANUALS
plus accessories

Merry Xmas



- Gould. OS4000. DC-10MHz. Portable Digital Storage Scope with:
OS4002. Analogue O/P to X-Y or Y-T Recorder(1) £150
Gould. OS4020. DC-10MHz. Portable Digital Storage Scope(1) £200
Hitachi. V203F DC-20MHz. Portable Dual Trace Scope & Delay etc.(4) £250
Hitachi. V212. DC-20MHz. Portable Dual Trace Scope(6) £250
Hitachi. V222. DC-20MHz. Portable Dual Trace Scope & Ch 1 Mag(8) £255
Kikusui. COS5020-PC. DC-20MHz. Portable Dual Trace Scope(1) £225
Kikusui. COS5021. DC-20MHz. Portable Dual Trace Scope & Delay etc.(1) £225
Tek. 5440. DC-50MHz. Three Slot Rack-mount Mainframe with Read Out.(1) £95
Tek. 7504. DC-90MHz. Four Slot Mainframe(1) £135
Tek. 7603. DC-100MHz. Three Slot Mainframe with Read Out.(2) £150
Tek. 7603. DC-100MHz. Three Slot Rack-mount Mainframe & Read Out.(2) £125
Tek. 5A19N. DC-2MHz. Differential Amp Plug In(2) £35
Tek. 5A48. DC-50MHz. Dual Trace Amp Plug In(1) £65
Tek. 5B10N. Single Sweep Time Base Plug In. 100ns-5s/div.(1) £35
Tek. 5B12N. Dual Time Base Plug In. 100ns-5s/div.(1) £35
Tek. 7A12. DC-105MHz. Dual Trace Amplifier Plug In with Offset(3) £130
Tek. 7A18. DC-75MHz. Dual Trace Amp Plug In(5) £128
Tek. 7A26. DC-200MHz. Dual Trace Amp Plug In(8) £187
Tek. 7B53A. Dual Time Base. 5ns-5s/div. Triggering to 100MHz(10) £149
Tek. 7B53AN. Dual Time Base Plug In without Read Out Opt(1) £145
Tek. 7D10. Digital Events Delay Plug In. 1 to 10.7 Events.(1) £81
Tek. 7S11. Sampling Unit. 2mV-200mV/div.(1) £450
Tek. S-3A. Sampling Head. DC-1GHz(2) £180
Tequipment. D1010. Portable DC-10MHz Dual Trace Scope(1) £95
Tequipment. D63. DC-15MHz. Scope with 2 x V5 Single Amplifiers(1) £135
Tek. 5440. DC-50MHz. Three Slot Rack-mount Mainframe with:
Read Out and 1x50A19N, 1x5A48, 1x5B12N Plug Ins(1) £172
Tek. 7504. DC-90MHz. Four Slot Mainframe with:
1x7A12, 1x7A18, 1x7B53A, 1x7B53A Plug Ins(1) £518
Tek. DC 503A. Universal DC-125MHz. Counter/Timer. 8 Digit Display(1) £225
Tek. DC 504A. DC-100MHz. Counter/Timer. 5 Digit Display(1) £200
Tek. DC 501. Digital Events Delay Unit. (10-99, 999)(1) £75
Tek. DM 501. D.M.M. AC/DC Volts. AC/DC mA. Ohms 4.5 Digit Display(1) £100
Tek. DM 502A. Auto-ranging D.M.M. AC RMS, DC, etc. 3.5 Digit Display(1) £165
Tek. FG 501A. 0.002Hz-2MHz. Function Generator. Sine, Square etc(1) £235
Tek. PS 501-1. Power Supply. 0-20V 0-400mA. and +5 Volt at 1Amp(1) £95
Tek. PS503A. Dual Power Supply. 0-20V, 0-400mA. and +5 Volt at 1Amp(2) £150
Tek. TM 503. three Slot Mainframe Power Supply(1) £175


- H.P. 8505A. Network Analyzer. 500kHz-1.3GHz. 50 Ohm Complete with:
8503A. S-Parameter Test Set. 500kHz-1.3GHz. 50 Ohm(1) £4950
H.P. 8552A. IF Section. (Plug In for 141T)(2) £200
H.P. 8553B. RF Section. 1kHz-110MHz. (Plug In for 141T)(2) £200
H.P. 11600B. Transistor Fixture with Case & Accessories(1) £485
H.P. 11608A. Transistor Fixture with Case & Accessories(2) £350
Bird. 8322. Coaxial Attenuator. 30dB, 500hm, 200 Watt, "N" Type(1) £350
Narda. 757-3. "N" Type attenuator. 3dB at 1GHz(1) £25
Narda. 757-6. "N" Type attenuator. 6dB at 1GHz(1) £25
Narda. 757-10. "N" Type attenuator. 10dB at 1GHz(1) £25
Crocico. Type SC2. Std 1.01861 Volt Cell. Twin Outputs(2) £70
E.D.C. MV-116G. DC Voltage Standard:
Range + or - 100 mVolt, 1 Volt & 10 Volt
Meter Sensitivity 10uV to 10 Volt. Galvo Input. (AS NEW)(1) £675
Elmeasco. 700A-04. Std 1.0181 Volt Cell Enclosure
Mains/Internal Stand by Battery, Oven Controlled. 4 Terminal O/P(1) £275
B & K. 2425. Electronic AC. Voltmeter. 0.5Hz-500kHz 1m-300V(1) £185
Leader. LMV-181A. AC. Millivoltmeter. 5Hz-1MHz. 1mV-300Volt(1) £45
Levell. TM-10. Microvoltmeter. 30uV-300V, 30pA-300pA. (Analog)(1) £35
Marconi. TF-2600A. Video Voltmeter. 1mV-100V, 10Hz-10MHz(1) £65
Marconi. TF-2600. Sensitive Valve Voltmeter. 1mV-300V, 10Hz-10MHz(2) £45
B & K. 1405. Noise Generator. 20Hz-100kHz. 0.3Volt O/P(1) £475
Levell. TG.66A. Transistor Decade Oscillator. 0.2Hz-1.22MHz(1) £45
Levell. TG200D. R.C. Oscillator. 2Hz-1MHz. Sine/Square. 600 Ohm(2) £60
Levell. TG200DM. R.C. Oscillator. 1Hz-1MHz. Sine/Square. 600 Ohm(2) £75
Levell. TG200DMP. R.C. Oscillator. 1Hz-1MHz. Sine/Square. 600 Ohm(2) £75
Marconi. 2017. AM/FM Signal Generator. 10kHz-1024MHz:
Microprocessor Direct Keyboard Entry with Memory Facilities.
Internal AM/FM Variable Modulation
Built In Frequency Sweep, High Output up to 4Volt e.m.f.,
External Mode Frequency Counter 10Hz-520MHz
GPIB/IEEE-488 Programmable, Internal Reference Standard
Calibration 2-7-96 Expire 1-7-97. With Certificate & Results(3) £2275
Philips. PM5571. Pulse Generator. 1Hz-100MHz. 80mV-10Volt. 50 Ohm(3) £750
Farnell. L30-1. 0-30V 0-1A Metered. Variable PS.U.(1) £45
Racal-Dana. 9232Q. Quad Mode Dual Bench Digital Power Supply,
0-30V 0-2A. Isolated, Parallel, Series, Tracking. (0-60V 0-4A)(1) £160
B & K. 2511. Vibration Meter. 0.3Hz-15kHz(1) £650
B & K. 2970. Sensitivity Comparator(1) £350
Bird. 8135. Coaxial Resistor. 50 Ohm, 150 Watt, "BNC" Type(1) £125

SEND FOR LISTS OF EQUIPMENT AND MANUALS



Our Elves await your calls on
(+44) 01243 545111 or 545112
or Fax: (+44) 01243 542457

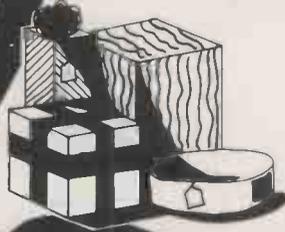ALL PRICES EXCLUDE VAT AND CARRIAGE
DISCOUNT FOR BULK ORDERS. SHIPPING ARRANGED
OPEN MONDAY TO FRIDAY, 9.00 am to 5.00 pm



Cooke International
ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham
Bognor Regis, West Sussex, PO22 0EB
U.K.

CIRCLE NO. 140 ON REPLY CARD

When is a gate not a gate?



Ian Forster has found that AC logic gates can be used to form simple, cheap yet repeatable rf oscillators.

In a recent article in *Electronics World*¹ I showed how 74AC series logic gates could be used in power conversion and switching applications. This article makes use of another useful feature of this logic gate series – namely their fast response speed and low propagation delay – to implement a series of vhf oscillators ideal for the experimenter.

All the following circuits have been tried with dual-in-line parts from different manufacturers and have proved very reliable. Good vhf construction techniques need to be used, as, linearly biased, the gates act as high-gain high-frequency amplifiers.


Most of the following circuits would not be well suited to battery powered applications. They tend to be current hungry. In addition, care must be taken when using multiple gates in one package not to exceed the maximum dissipation limits – 74AC gates are tough, but not indestructible.

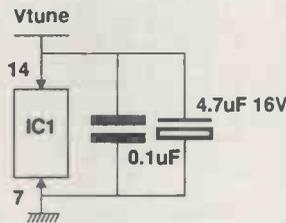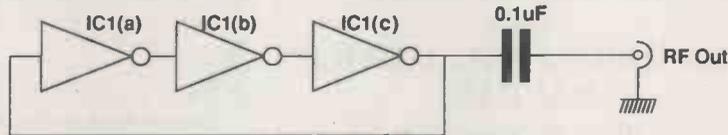Ring-of-three oscillator for high frequencies



AC gates can be used to produce a high-frequency equivalent of the standard 'ring-of-three' type oscillator. Again, operating frequency is controlled by varying the supply and hence the propagation delay of the gates. Power output is approximately 8.3dBm at 2V and +17dBm at 5V, with the third harmonic at -10dBc and the fifth at -16dBc, corresponding to +1.5dBm at 417.5MHz.

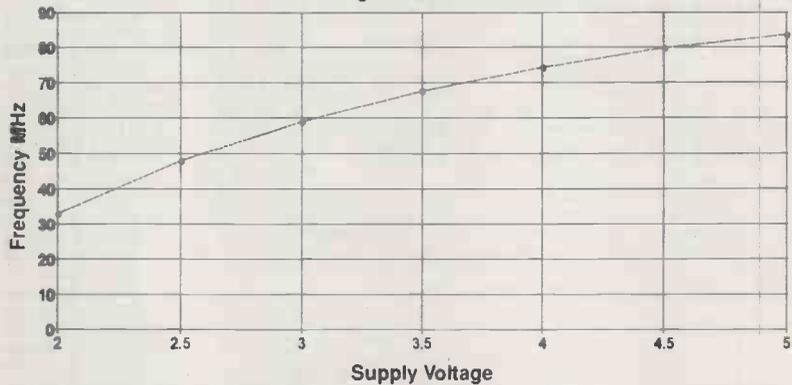Voltage / Frequency Characteristic for Ring Of Three Oscillator






Oscillator for vhf


This is the simplest implementation of a vhf oscillator using a single inverter from a 74AC04. Oscillation occurs at the frequency at which the delay of the gate is equal to 180° phase shift. Output frequency is controlled by varying the supply, and hence varying

the propagation delay of the gate. Power output is approximately +6.5dBm at 2V and +16dBm at 5V, with the third harmonic at -16dBc (corresponding to -4dBm 840MHz at 5V).

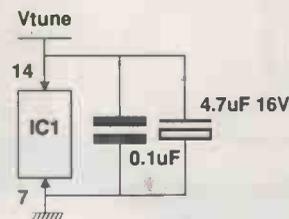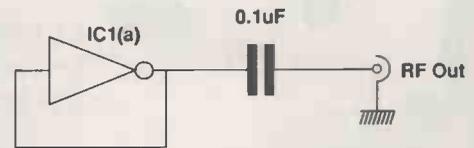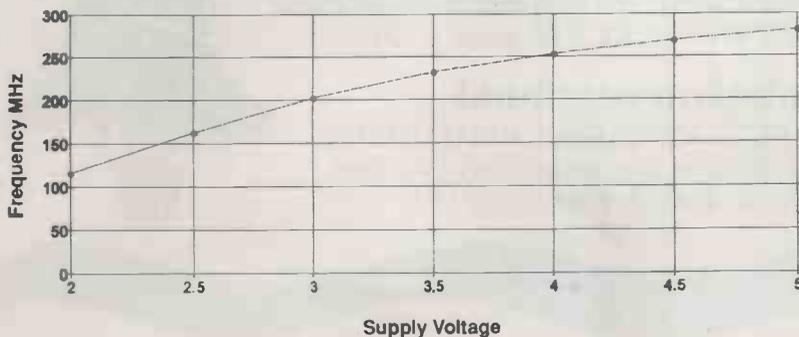Voltage / Frequency Characteristic for Single Gate Oscillator




Oscillator uses coaxial cable

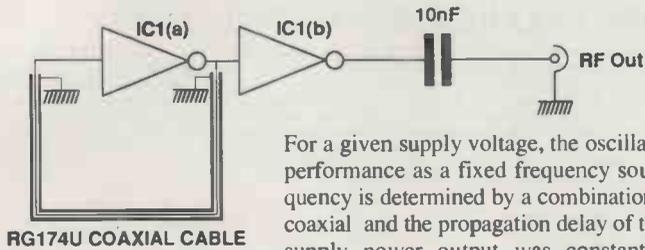


For a given supply voltage, the oscillator here gives good performance as a fixed frequency source. Operating frequency is determined by a combination of the delay in the coaxial and the propagation delay of the gate. Using a 5V supply power output was constant at approximately +16dBm.

RG174U LINE LENGTH AGAINST FREQUENCY

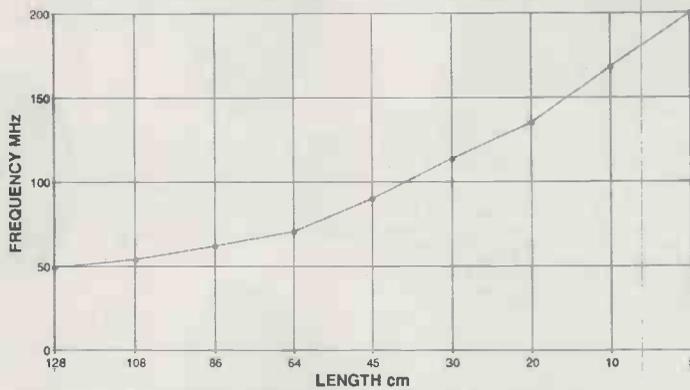

Crystal oscillator

This is a fifth-overtone crystal oscillator based on the 74AC04. It runs near series resonance and provides a stable output at high level, rich in harmonics. Typically, this would be used to form the basis of a low power vhf/uhf transmitter or, with filtering, as a vhf/uhf local oscillator for a receiver. Addition of a varactor diode, coupled via an appropriate capacitor, across C_3 , using a resistor to bias it, allows a degree of tuning.

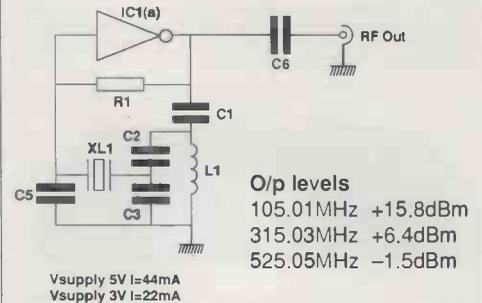


- IC₁ 74AC04
- XL₁ 105MHz 5th overtone HC18U
- L₁ 135nH MC105 variable
- C₁ 5.6pF ceramic
- C_{2,3} 39pF ceramic
- C_{1,5} 22pF ceramic

LC oscillator



For a more compact oscillator the circuit is more suitable. This is a fairly standard LC type oscillator, with the output frequency being a function of the inductance, stray and wanted capacitance and gate delay. With L at 39nH and C at 1.5pF, measured noise was -90dBc/Hz at 10kHz offset with an associated +17dBm output.

| L ₁ (nH) | VC ₁ (pF) | o/p (MHz) |
|---------------------|----------------------|-----------|
| 68 | 6 | 143.1 |
| 68 | 1.5 | 159.4 |
| 68 | - | 166.4 |
| 39 | 6 | 180.9 |
| 39 | 1.5 | 190.7 |
| 39 | - | 197.9 |

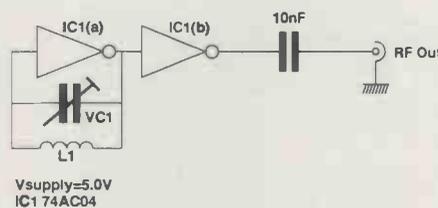



And at uhf

To complete this collection, (a) and (b) here show two oscillators designed to operate in the uhf band. In (a), C_1 provides feedback from output to input and, due to its low value, suppresses vhf oscillation, with R_1 biasing the gate into its linear mode. Inductor L_1 and the variable capacitor provide a variable phase shift to control the oscillator frequency. In (b), R_1 again places the gate in its linear mode but the feedback is a combination of C_1 and a 418MHz band surface-acoustic-wave resonator device, as used in key fob transmitters for car alarms ■

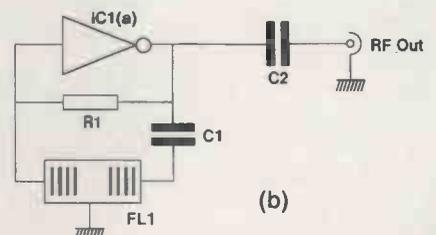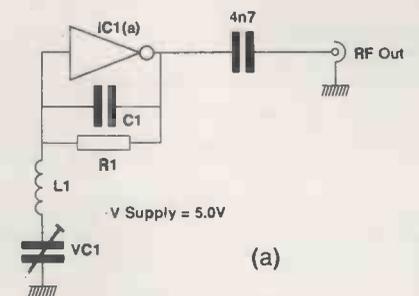

Oscillator for 2m band

An LC voltage-controlled oscillator designed to cover the 2m amateur band, can be formed from AC gates, when used with a synthesiser IC such as the National Semiconductor LMX1501A. High output level of the oscillator makes it well suited to driving a level 17 double balanced diode mixer. This, with a high intermodulation performance front-end amplifier, such as the MAVII from Mini Circuits, could form a high immunity receiver front end for cluttered signal environments.

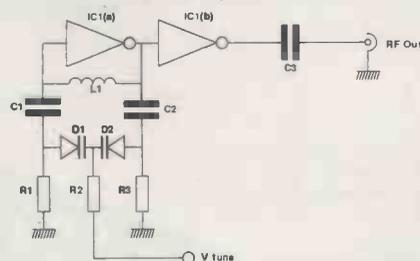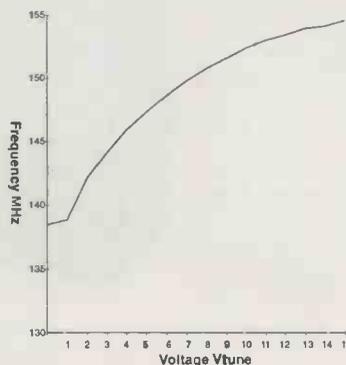

- L₁ 68nH 32CS smt
- IC₁ 74AC04
- R₁₋₃ 18kΩ
- C_{1,2} 100pF ceramic
- C₃ 10nF ceramic
- D_{1,2} BB405B varactor

HART

The Home of *Hi-Finesse*. Its not what you do,
its **HOW** you do it that counts!.

VISATON® SPEAKER KITS & DRIVE UNITS

Hart Audio Kits and factory assembled units use the unique combination of circuit designs by the renowned John Linsley Hood, the very best audiophile components, and our own engineering expertise, to give you unbeatable performance and unbelievable value for money.

We have always led the field for easy home construction to professional standards, even in the sixties we were using easily assembled printed circuits when Heathkit in America were still using tagboards! Many years of experience and innovation, going back to the early Dinsdale and Bailey classics gives us incomparable design background in the needs of the home constructor. This simply means that building a Hart kit is a real pleasure, resulting in a piece of equipment that not only saves you money but you will be proud to own.

Why not buy the reprints and construction manual for the kit you are interested in to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase.

'AUDIO DESIGN' 80 WATT POWER AMPLIFIER.



This fantastic John Linsley Hood designed amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hi-fi system. This kit is your way to get UK performance at bargain basement prices. Unique design features such as fully FET stabilised power supplies give this amplifier World Class performance with startling clarity and transparency of sound, allied to the famous HART quality components and ease of construction. Standard model comes with a versatile passive front-end giving switched inputs, with ALPS precision "Blue Velvet" low-noise volume and balance controls, no need for an external preamp. Construction is very simple and enjoyable with all the difficult work done for you, even the wiring is pre-terminated, ready for instant use! All versions are available with Standard components or specially selected Super Audiophile components and Gold Plated speaker terminals and all are also available factory assembled.

| | |
|---|---------|
| K1100 Complete STANDARD Stereo Amplifier Kit, | £415.21 |
| K1100S Complete SLAVE Amplifier Kit, | £353.62 |
| K1100M Complete MONOBLOC Amplifier Kit, | £271.20 |
| RLH11 Reprints of latest Amplifier articles, | £1.80 |
| K1100CM Construction Manual with full parts lists | £5.50 |

ALPS "Blue Velvet" PRECISION AUDIO CONTROLS.



Now you can throw out those noisy ill-matched carbon pots and replace with the famous Hart exclusive ALPS "Blue Velvet" range components only used selectively in the very top flight of World class amplifiers. The improvement in track accuracy and matching really is incredible giving better tonal balance between channels and rock solid image stability. Motorised versions have 5v DC motor.

MANUAL POTENTIOMETERS

| | |
|---|--------|
| 2-Gang 100K Lin. | £15.67 |
| 2-Gang 10K, 50K or 100K Log. | £16.40 |
| 2-Gang 10K Special Balance, zero crosstalk & centre loss. | £17.48 |

MOTORISED POTENTIOMETERS

| | |
|--|--------|
| 2-Gang 20K Log Volume Control | £26.20 |
| 2-Gang 10K RD Special Balance, zero crosstalk and less than 10% loss in centre position. | £26.98 |

32W VALVE AMP TRANSFORMERS


Special set of toroidal transformers, 2 output & 1 mains for the "Hot Audio Power" valve amplifier design described in the Oct. 1995 issue of "Wireless World". Total Wt 4.8Kg. Special price for the set. £99, Post £8. Photocopies of Article by Jeff Macaulay. £2.00

JOHN LINSLEY HOOD SINGLE ENDED CLASS 'A' POWER AMPLIFIER

A new concept in amplifier design to meet the needs of modern users who want the warmth and purity of sound given by valve amplifiers from the vintage years, without the problems of cost, deterioration and danger associated with trying to use valves today. It employs the newly re-discovered single-ended circuit configuration to give total freedom from crossover artifacts and to give a sound that is indistinguishable from the famous "Williamson" design, the undisputed leader of the field, with its triode connected KT66s and all-triode drivers. Described in the September 1996 issue of EWW the new version retains the basic simplicity and purity of the original but with modern components and an increased power rating of 15W RMS per channel.

| | |
|---|---------|
| Full Kit In 3u high Rackmount Case. | £388.25 |
| Set of 3 PCBs only. | £60.50 |

ASM100 ACTIVE SUBWOOFER MODULE

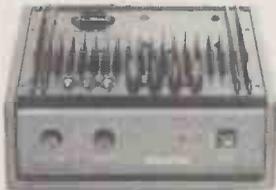

This attractive module consists of a low pass filter and power amplifier ready for you to mount in a suitable sub-woofer cabinet. The combined unit can then be combined with any new or existing hi fi or home cinema speaker system to add in the real bass punch missing from most setups.

The ASM 100 module comes as a ready-to-mount unit on a solid diecast aluminium frame/heatsink. Input signal can be at line or speaker level for easy system integration. There are three separate stereo inputs at line level and the unit will use any signal presented or mix all inputs to add bass to any signal. The speaker level inputs are used by simply wiring the unit in parallel with the existing speakers to provide them with strong bass support. Crossover frequency can be selected to 50, 100 or 200Hz and the bass level can be adjusted by a front panel control. The "Green" power supply switches the unit to standby if no signal is present. Drawings are included free for the compact 418 x 380 x 303mm cabinet. With its powerful 125 watt output and versatile filtering the ASM 100 is the ideal universal active driver module for all subwoofer requirements.

| | |
|---|---------|
| ASM 100 Module, complete with IEC mains lead, instructions and ASM - W20 cabinet drawings. Pt. No. V7000. | £185.29 |
| W 20 S 20cm Long Throw Drive unit for use in ASM - W20 cabinet. | £36.68 |

FIESTA 30 LOUDSPEAKER KIT

An Ultra High Efficiency speaker, specially suitable for Valve Amplifiers.

Specially selected as the ideal partner for the new John Linsley Hood 15W Valve Sound Amplifier, or indeed any actual valve amplifier, the FIESTA 30 features the astonishing efficiency and sensitivity needed to achieve a satisfying sound level from amplifiers of limited power output.

To complement the sound purity of such amplifiers a full three speaker system is used with a 300mm (12") woofer, 200mm (8") mid-range and high quality horn tweeter in a vented bass reflex enclosure.

All these drive units have been carefully selected for their individual virtues, and collective excellence, the tweeter for instance being a high end unit with exceptional pulse response as a result of its combination of Kapton former, aluminium diaphragm and aluminium voice coil.

Nominal Power Rating is 150W, Max. Music Power 250W, Impedance 8 ohm, Mean Sound Pressure 91dB. Speaker kit comes with all parts to make a pair of speakers, but not the cabinet parts. Crossover units are factory assembled, ready to fit.

| | |
|---------------------------------|---------|
| Kit No.LK5963 Per Pair. | £424.93 |
|---------------------------------|---------|

HOME CINEMA SPEAKERS.

The VISATON range of speaker kits includes all you will ever need for your surround sound home cinema setup. The Hi-Tower Kit is ideal as a super luxury pair of stereo main speakers. The "Centre 80" uses special magnetically screened drivers to avoid picture disturbance and a pair of "Effect 80's" are used as rear speakers. Any of a range of sub-woofers then adds weight to the sound of the robot feet! Centre 80 Kits include drive units, crossover, terminals and grille..(You make the box) Price each. £64.08
Effect 80, Rear Speaker Kits, per pair, £39.00

DRIVE UNITS.



BC30NG 30cm. (12") Woofer. High efficiency, (95db) for sealed or vented cabinets. Peak power handling 250watts. 8 ohm. £69.61

W20S 20cm. (8") Woofer. Long throw unit with rubber surround and extended rear pole to give no less than 20mm cone displacement. Ideal for compact sub-woofers such as ASM-W20. 8ohm. £36.68
NG8 Protective Metal Grille. £5.66




W100S 10cm (4") Low/Midrange. Coated paper cone, rubber surround, high temperature voice coil. Suitable as woofer in mini enclosures or midrange in 3-way systems. 4ohm. £18.06
NG4 Protective Metal Grille. £3.20

FRS8 8cm.(3.3") Fullrange driver. Linear frequency response between 200 and 20KHz. Large Magnet, 20mm voice coil and rubber surround. 8ohm. £8.36



DT2.5 10mm Polycarbonate Tweeter. High efficiency ferrofluid tweeter for use over 4,500Hz. Very good price/performance ratio. 8ohm. £8.77

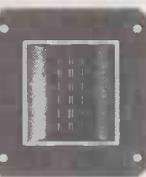SC5 10mm. Magnetically shielded Tweeter for use in surround sound centre speakers. 8ohm. £9.24



RHT12S High End Ribbon Tweeter. Superior double magnet construction gives an exceptionally low distortion and linear response from 4,000 to 30,000Hz. Cabinet cutout diameter 95mm. 8ohm. £87.77

DHT9AW-NG Hi-Tech, HI-FI, horn type tweeter. Frequency response from 3,500 to 38,000Hz and very good pulse response due to aluminium cone, Kapton voice coil and aluminium wire. Peak power handling 150W. 8ohm. £31.99



ASM100 and our 80 watt power amplifier are on demonstration at Wilmslow Audio's new premises at Broughton Astley near Leicester. Tel 01455 286603.

POSTAGE ON UK orders is £2 up to £20, £4.50 over £20.

Overseas please enquire.

Our LISTS are FREE on request.

Send for Your **FREE** copy of our **LISTS**

24 Hr. ORDERLINE 01691 652894
Fax. 01691 662864

All Prices include **UK/EC VAT.**

HART
HART ELECTRONIC KITS LTD.
1 Penylan Mill, OSWESTRY,
Shrops. SY10 9AF.
UK

New thoughts on demodulation

Edward Forster investigates the performance of Archie Pettigrew's award-winning amplitude-locked loop demodulation technique in both AM and FM receivers.

The amplitude-locked loop, or ALL, was not described as an automatic-gain system*, but it clearly is a distinct form of one. Generally, agc systems use gain-controlled amplifiers, i.e. multipliers, with a logarithmic or semi-log law to obtain large dynamic range. The dynamic range of an ALL with linear multiplier is described as 26dB.

Automatic gain control is rarely used to entirely suppress the amplitude modulation, but this is only a matter of bandwidth. It is true that the ALL outputs the reciprocal of envelope amplitude together with a fully compressed envelope signal within its operating range. But how useful this is remains to be seen.

Demodulating AM

The ALL is used here to provide a constant envelope signal to the demodulator which is of the square law carrier recovery type¹ using a phase locked loop, or pll. This might be unexceptional were it not for the claims made for this circuit. This is certainly not an advance in the art nor is it an optimum system. The ALL is said to provide special features which cannot be met by a limiter.

At threshold levels, I suggest that a soft limiter having a gain of 26dB put in place of the ALL would yield identical results. This is

*June 1996 issue, page 466, Demodulation – a new approach by Archie Pettigrew.

because at the end of its range, the ALL also has a constant gain of 26dB and it would be impossible to distinguish between the two. At high carrier levels it also makes no difference which is used.

The subsequent pll shown in the circuit as the carrier recovery device is not an optimum type. This is a common mistake. It raises the question of what the point of the system is in the first place. The problem of AM full carrier reception in conditions of multipath interference and doppler shifts – such as found on the hf broadcasting bands – was successfully solved in the *Linplex F1/2* receiver made by Phase Track Limited throughout the eighties. This used a synchronous pll AM demodulator² at intermediate frequency in a superheterodyne receiver.

Figure 1 shows the pll carrier recovery system of that receiver which is a type II system, ie, it contains two perfect integrators these being an active integrator and the voltage controlled oscillator (vco). In servo parlance this is known as a proportional plus integral feedback loop. Although this is well known some of its characteristics as applied to this problem are apparently not well known.

Figure 1b shows that the active filter can be redrawn as the equivalent sum of the proportional 'P' component and the integral 'I' component. This allows you to see more clearly what happens. Figure 2 is the idealised

response to a step offset of the vco. The 'P' component has a fast response but it eventually returns to zero. The 'I' component response is to gradually ramp towards the final control voltage needed.


When the response subsides, there is zero static error in the system. The loop may be opened without any effect. The same thing results if the input carrier also disappears for some time during a fade. The loop remains essentially locked and can provide the necessary carrier for effective synchronous demodulation of sidebands to continue undisturbed. When the carrier returns there is no re-locking as the loop never lost lock.

Another feature of the type II pll is that it offers the freedom to optimise the loop bandwidth without any restriction other than that the loop should follow any doppler shifts and vco drift. In the type I loop, setting the bandwidth correctly can result in the hold-in range of the pll being too small for practical use.

It is also necessary to have as small a loop bandwidth as possible. This is to prevent the control signal from frequency modulating the vco within the modulation band as this produces distortion.

Many such pll AM demodulators have appeared in up-market broadcast receivers. But because of this distortion, their audio quality was indistinguishable from the conventional envelope demodulator.

Fig. 1. Carrier recovery by type II PLL; b) equivalent to a).

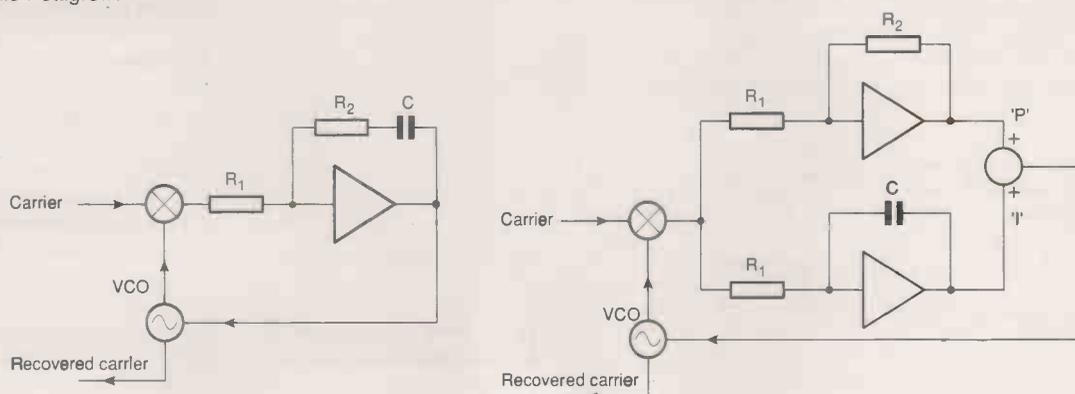

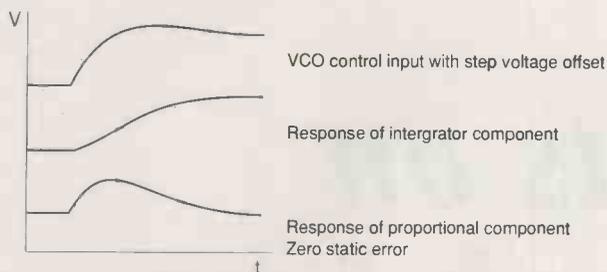


Fig. 2. Dynamics of type II PLL.

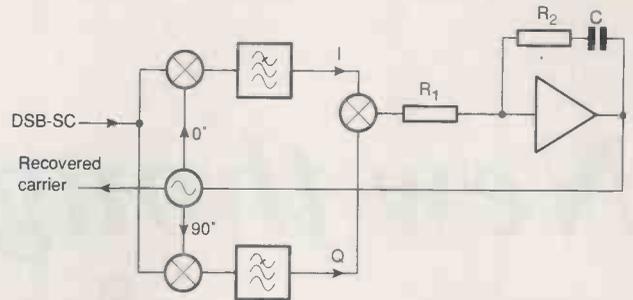


Fig. 3. Costas Loop with type II PLL.

The Costas loop

However, for the future, another old system brought up to date is preferred; this is the Costas loop³⁻⁵, Fig. 3. It is suitable for AM full carrier or double sideband, or dsb, suppressed carrier reception. It relies directly on sideband information in the I, in-phase, and Q, quadrature channels which when multiplied together give an error signal.

The feedback error signal is intermittent in sound transmission and a special pll is required. Again the type II loop serves the purpose as its, in principle, infinite memory capability allows the loop to stay in lock during modulation pauses. This time instead of acting from direct carrier phase information, it is the sidebands alone from which the virtual carrier phase is derived.

The great opportunity of the I/Q Costas loop is in I/Q direct conversion receivers where much of the former intermediate frequency processing can be equivalently replaced by on-chip audio processing whether analogue or digital. Multi-conversion superhets can be replaced by direct conversion receivers with equivalent performance but at a far cheaper cost and lower power consumption.

Although the synchronous receiver produces optimum results and also allows for electricity saving dsb broadcast transmission, a simpler non-synchronous technique⁶ has been devised for the AM I/Q receiver. The superheterodyne is fast becoming obsolete.

Demodulation for FM

The hyperbole accompanying Pettigrew's FM demodulation circuit has in many ways obscured any real understanding of how it works. But, by separating the functions and using a simple test signal, its effectiveness can be clarified.

Figure 4 shows an unmodulated carrier of unit magnitude in the presence of an offset carrier of amplitude *k*. It is clear that both amplitude and phase modulation are produced. When *k* is small, say below 0.1, the difference fre-

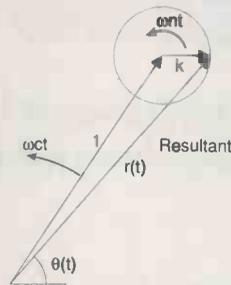


Fig. 4. Unmodulated carrier ω_c rad/sec plus interfering carrier ω_n rad/sec.

quency modulations are nearly pure sinusoids in phase quadrature. With this information you can examine how the circuit performs with relative ease.

Figure 5 shows the simplified system. The ALL is assumed perfect as is the pll fm demodulator, which differentiates perfectly the phase modulation at its input. In being differentiated, the phase modulation is shifted by 90° to appear at the output of the fm demodulator, let us say for simplicity, as $\cos a$.

Output from the ALL for small percentage amplitude modulation is also a cosine in-phase, say $\cos a$ again. The final processing is the puzzle. As shown, there can never be cancellation however the amplitudes are manipulated. Therefore, at small values of carrier interference the system cannot work.

For large levels of interfering carrier it is necessary to use computer simulation. This is, in fact, not too difficult. Using numerical differentiation it was possible to simulate the large signal case with less than 2k of Basic.

Results are as follows:

| <i>k</i> | Improvement over pll o/p in dB |
|----------|--------------------------------|
| 0.1 | 0 |
| 0.5 | 1 |
| 0.7 | 3 |
| 0.8 | 6 |
| 0.9 | 18 |
| 0.95 | 0 |

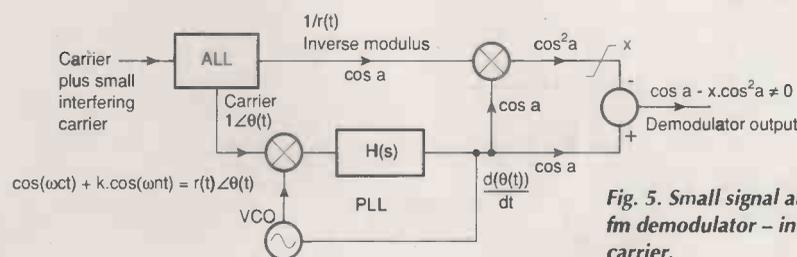


Fig. 5. Small signal analysis of fm demodulator - interfering carrier.

The improvement obtained is the result of some highly non-linear interactions but the significant improvement occurs within 3dB of the threshold, $k=1$, within a 2.2dB overall range from $k=0.7$ to $k=0.9$. Where the peak improvement occurs is a matter of adjustment but the above results are probably typical.

Outputs of both the amplitude and phase-locked loops under these circumstances are pulses, which are not necessarily well matched. This indicates that the ALL pulse is being used more as a gating or sampling pulse. You might therefore suppose that the AM related pulse could be generated elsewhere. Synchronous demodulation of the envelope, without ALL or limiter, could be devised to enable a pulse generator in this small range of *k*.

That aside, the pll frequency demodulator described by Pettigrew is fed from a constant carrier even at threshold. Presumably, it is considered that the best results will be obtained by simulating a limiter. But it is known that a limiter is detrimental to threshold extension in phase locked loops.

Schilling⁷ has noted that type II loops produce better threshold performance by virtue of the extra integrator. It is also shown⁸ that above threshold, a limiter is of no value and that near threshold it is positively damaging.

This is because, as the resultant carrier instantaneously falls to a low amplitude at the maximum rate of change of phase, the loop gain also falls to a low value. Consequently the loop does not track the rapid phase change and does not reproduce a sharp spike at its output. Maintaining full carrier level in all circumstances prevents this beneficial effect. Again we come back to the pll design. Is it a type I or type II?

If a type II pll were used for comparison in a receiver with slow agc but no limiter then any benefits may not look so great. ■

References

1. Rieke, J.W. and Graham, R.S., 'The L3 Coaxial System: Television Terminals', *BSTJ*, July, 1953.
2. Patent GB 2 077 533, Phase Track Ltd., 1980.
3. Costas, J.P., 'Synchronous Communications', *Proc. IRE*, December, 1956.
4. Patent application, Phase Track Ltd, 1991.
5. *Electronics World*, p84, January, 1992.
6. Forster, E.C., patent application, 1994.
7. Schilling, D.J., and Taub, H, *Principles of Communications Systems*, 1971.
8. Gardner, F.M., *Phaselock Techniques*, 2nd ed., 1979.

Eight year EW index Hard copy or disk

Includes over 600 circuit idea references

Whether as a PC data base or as hard copy, SoftCopy can supply a complete index of *Electronics World* articles going back over the past eight years.

The computerised index of *Electronics World* magazine covers the eight years from 1987 to 1995 – volumes 94 to 101 inclusive – and is available now. It contains almost 2000 references to articles, circuit ideas and applications – including a synopsis for each.

The EW index data base is easy to use and very fast. It runs on any IBM or compatible PC with 512k ram and a hard disk.

Even though the disk-based index has been expanded significantly from five years to eight, its price is still only £20 inclusive. Please specify whether you need 5 1/4in, 3.5in DD or 3.5in HD format. Existing users can obtain an upgrade for £15 by quoting their serial number with their order.

Hard copy *Electronics World* index

Indexes on paper for volumes 100 and 101 are available at £2 each, excluding postage.

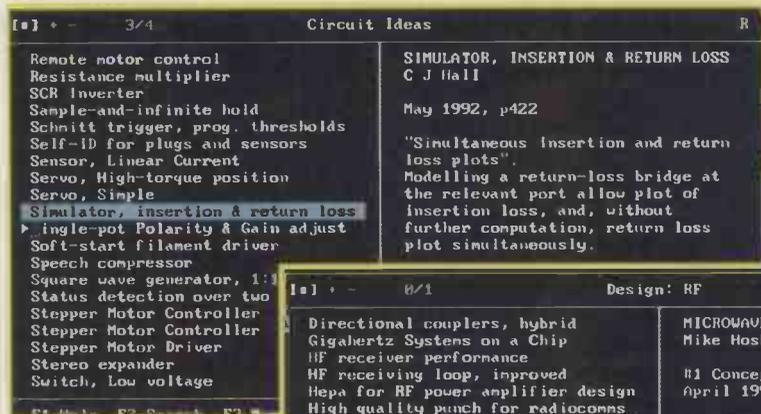


Photo copies of

Electronics World articles

Photo copies from back issues of *Electronics World* are available at a flat rate of £3 per article or 50p per circuit idea, both excluding postage.

Ordering details

The EW index data base price of £20 includes UK postage and VAT. Add an extra £1 for overseas EC orders or £5 for non-EC overseas orders.

Postal charges on hard copy indexes and on photocopies are 50p UK, £1 for the rest of the EC or £2 worldwide.

For enquiries about photocopies, etc,

please send an sae to SoftCopy Ltd at the address below.


Send your order to SoftCopy Ltd., 1 Vineries Close, Cheltenham GL53 0NU, tel 01242 241455, or e-mail at 100556.112@compuserv.com. Please make cheques payable to SoftCopy Ltd – not EW or Reed Business Publishing. Please allow up to 28 days for delivery.

HM604-3

Multifunction Oscilloscope

£ 764.00

60MHz

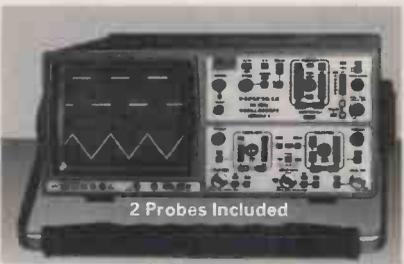

- ❑ **Autoset, Save and Recall**
6 Saved setups & built-in RS-232
- ❑ **2 Channels, DC to 60MHz**
1 mV/div.-20 V/div., Vert. Sens.
- ❑ **Time Base: 0.5 s to 5 ns/div.**
Triggering: DC to 100 MHz
- ❑ **Trigger-after-delay**
Automatic Peak to Peak Trig.
Alternate Trigger
TV-Sync-Separator
Component - Tester,
1MHz Calibrator.

HM1004

Multifunction Oscilloscope

£ 990.00

100MHz




- ❑ **Autoset, Save and Recall**
10 Saved setups & built-in RS-232
- ❑ **Readout and Cursor. Display:**
Instrument & Cursor functions.
- ❑ **2 Channels, DC to 100MHz**
1 mV/div.-20 V/div., Vert. Sens.
- ❑ **Dual Time Base with 2nd Trigger**
Time Base A: 0.5 s to 5 ns/div.
Time Base B: 20 ms to 5 ns/div.
Triggering: DC to 200 MHz
TV-Sync-Separator, Delay Line
1MHz Calibrator, 14kV CRT.

HM1007

Analog / Digital Oscilloscope

£ 1241.00

100MHz

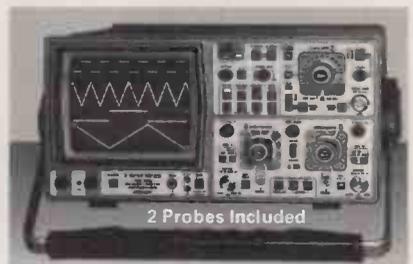

- ❑ **Analog: 2 x DC to 100MHz**
1 mV/div.-20 V/div., Vert. Sens.
- ❑ **Digital: 2 x 40MS/s**
Storage 4 x 2048 x 8 bit
- ❑ **Time Base: 50 s to 5 ns/div.**
Triggering: DC to 150 MHz
Pre-Trig., Reference memory
- ❑ **Digital operating modes:**
Roll, Refresh, Single and XY.
- ❑ **Interface for Graphic-Printer.**
Delay line, 14kV CRT.
- ❑ **Optional Interface: IEEE-488,**
RS-232 and Centronics.

Call now for more Information

HAMEG Instruments 70-78 Collingdon Street LUTON Beds. LU1 1RX ☎ 01582 413174 ☎ FAX 01582 456416

Do you have an original circuit idea for publication? We are giving **£100** cash for the month's top design. Additional authors will receive **£25** cash for each circuit idea published. We are looking for ingenuity in the use of modern components.

WIN A TTI PROGRAMMABLE BENCH MULTIMETER

"High accuracy, resolution and bandwidth - performance beyond the capability of handhelds"



This high-performance bench multimeter could be yours in exchange for a good idea. Featuring a dual display, the 4.5-digit 1705 multimeter resolves down to 10 μ V, 10m Ω and 0.1 μ A and has a basic dc accuracy of 0.04%. Frequency measured is 10Hz to 120kHz with an accuracy of 0.01% and resolution to 0.01Hz. Capacitor and true rms measurements are also featured.

Recognising the importance of a good idea, Thurlby Thandar Instruments will be giving away one of these excellent instruments once every six months. This incentive is in addition to our monthly £100 'best circuit idea' award and £25 awards for each circuit published.

200MHz spectrum analyser displays to -75dB

Used with an ordinary oscilloscope, this circuit forms a spectrum analyser for the 0-200MHz range of frequencies. To simplify examination of the wanted frequency, span and centre frequency controls are arranged to make signals in the


middle of the trace stay there as span decreases.

Amplifiers A_1 and A_2 produce a sawtooth waveform, symmetrical about the 12V rail, which is amplified in A_3 with control of amplitude for span and offset for

centre frequency. The discharge goes to the oscilloscope as a timebase trigger.

Driven by the sawtooth, the Mini Circuits POS-400 voltage-controlled oscillator provides a linear voltage/frequency output over the

Fig. 1
Complete circuit diagram of the 200MHz analyser, which will display inputs at -75dB.

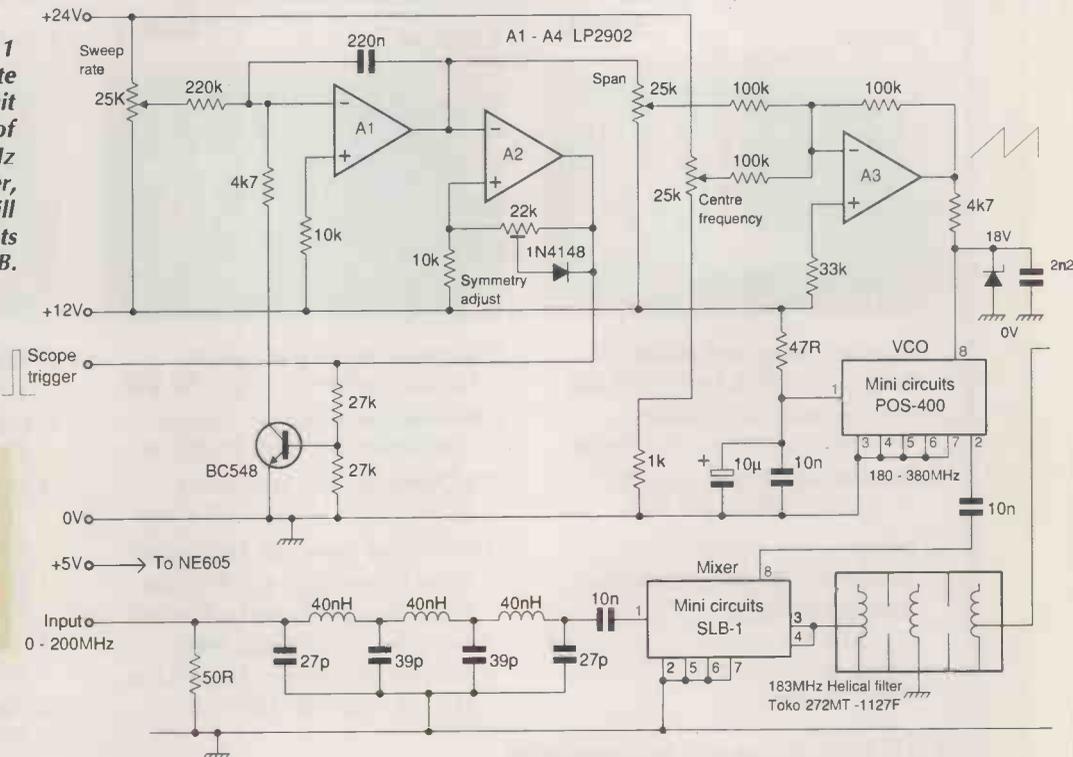

**TTI PROGRAMMABLE
BENCH MULTIMETER
WINNER**

Window detector has high input-impedance

Hysteresis at both upper and lower trip points and a high input impedance are the advantages of this detector, which uses only a dual comparator and a transistor.

There is little to say about the circuit shown but to give some formulae for trip points and hysteresis.

Lower trip point:

$$\frac{T_1}{E_p} = \frac{R_3}{R_1 + R_2 + R_3}$$

Lower trip point hysteresis

$$\frac{H_1}{E_p} = \frac{R_3(R_1 + R_2)}{R_5(R_1 + R_2 + R_3)}$$

Upper trip point:

$$\frac{T_2}{E_p} = \frac{R_2 + R_3}{R_1 + R_2 + R_3}$$

Upper trip point hysteresis:

$$\frac{H_2}{E_p} = \frac{R_1}{R_4} \cdot \frac{R_2 + R_3}{R_1 + R_2 + R_3}$$

It is usually required that the hysteresis of both points should be equal, so:


$$R_4 = R_5 \frac{R_1}{R_3} \cdot \frac{R_2 + R_3}{R_1 + R_2}$$

If the hysteresis of the lower trip point is zero or negative, it may be that the circuit will oscillate.

$$R_5 \leq R_4 \frac{R_1 + R_2}{R_1} + R_2$$

W Dijkstra
Waalre
The Netherlands

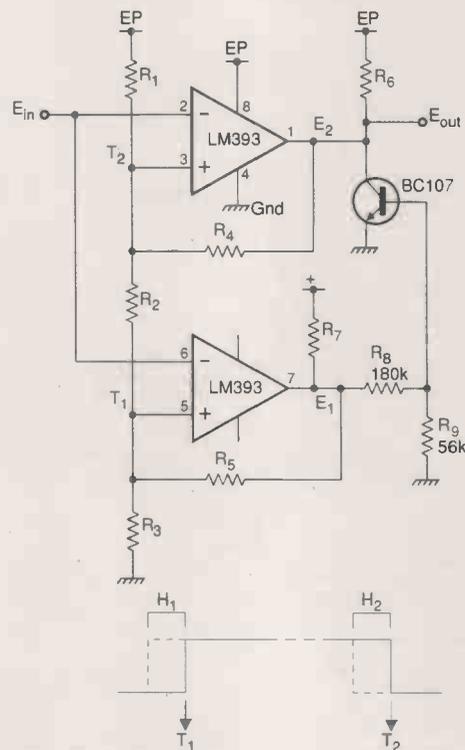Window detector has designable hysteresis at upper and lower trip points and, unusually, high input impedance.



180-380MHz range and drives the SLB-1 double-balanced mixer directly, signal input to the mixer coming via the low-pass filter.

After filtering by the Toko 272MT-1127F, mixer output is impedance matched to the NE605. This device converts down to a standard if of 10.7MHz, the local oscillator being a SAW type. A voltage proportional to the log. of the internally amplified 10.7MHz if appears at pin 7 of the

NE605 and is buffered in A4 to be used as the oscilloscope input.



Symmetry of response is maintained by the CFSK ceramic filters, which also determine the bandwidth.

A limitation is the fairly slow response of the output of the NE605. It is usable, but reduces the amplitude of the display at faster sweep rates. It may be that the ME625, which is pin-compatible and faster, would


improve matters.

Glyn Roberts
Walsall

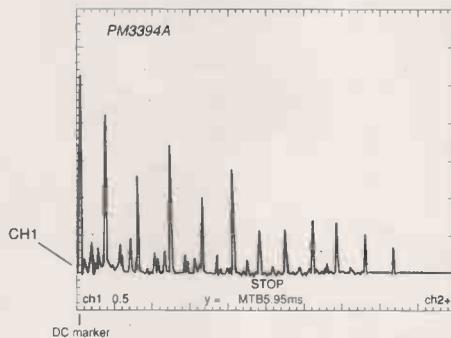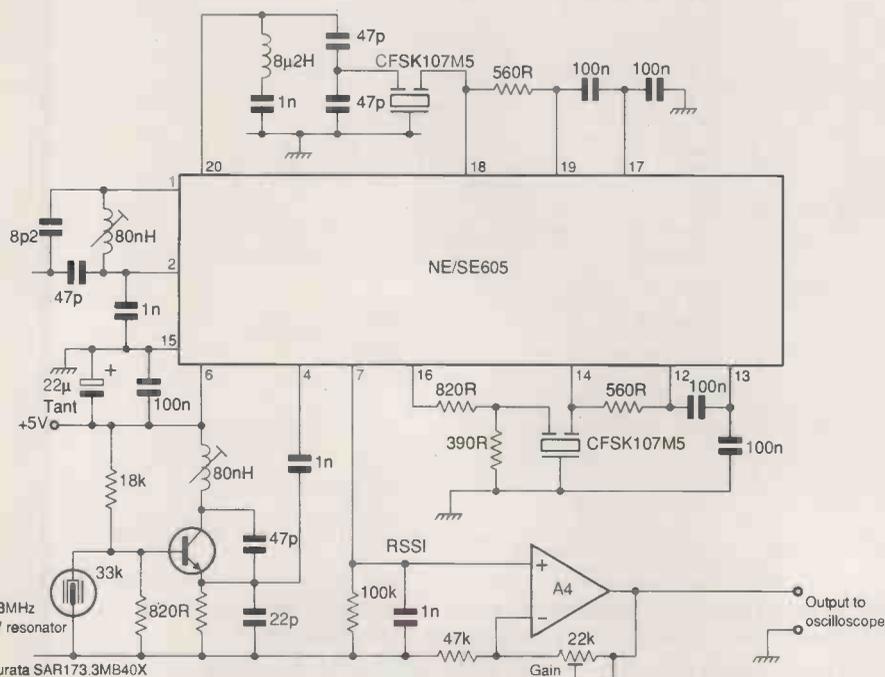Spectrum of the local fm broadcast band, 88 to 108MHz, top, and 20MHz square wave, demonstrating sweep linearity, bottom.



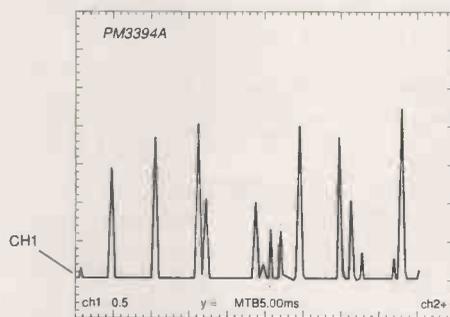Y/Div: 500mV Timebase: 5.95ms Trace: ch1
Trigger: 10:30 Time: 07:47 Date: 16-03-1992



Y/Div: 500mV Timebase: 5.00ms Trace: ch1
Trigger: 10:35 Time: 07:56 Date: 16-03-1992

SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK

HP New Colour Spectrum Analysers
 HP141T+8552B IF + 8553B RF - 1KHz-110Mc/s - £700.
 HP141T+8552B IF + 8554B RF - 100KHz-1250Mc/s - £900.
 HP141T+8552B IF + 8556A RF - 20Hz-300KHz - £700.
 Special Offer just in from MOD Qty 40 HP8555A RF Units 10Mc/s - 18GHzS.
 HP141T+8552B IF + 8555A 10Mc/s-18GHzS - £1200.
 HP ANZ Units Available separately - New Colours - Tested
 HP141T Mainframe - £350.
 HP8552B IF - £300.
 HP8553B RF 1KHz to 110Mc/s - £200.
 HP8554B RF 100KHz to 1250Mc/s - £500.
 HP8555A RF 10Mc/s to 30GHzS - £250.
 HP8555A RF 20Hz to 300KHzS - £250.
 HP8443A Tracking Generator Counter 100KHz-110Mc/s - £300.
 HP8445B Tracking Preselector DC to 18GHz - £350.
 HP3580A 5Hz - 50KHz ANZ - £750 - £1000.
 HP3582A .02Hz to 25.6KHz - £2k.
 HP8568A 100Hz-1500Mc/s ANZ - £6k.
 HP8569B 10Mc/s-22GHz ANZ - £6k.
 HP Mixers are available for the above ANZ's to 40GHz
 TEK 492 - 50KHz - 18GHz Opt 1+2 - £4k-£4.2k.
 TEK 492 - 50KHz - 18GHz Opt 1+2+3 - £4.5k.
 TEK 492P - 50KHz - 21 GHz Opt 1+2+3 - £5k.
 TEK 494AP 1KC/S - 21GHz - £7k.
 TEK 496P 1KHz-1.8GHz - £4k.
 TEK 5L4N 0-100KHz - £400.
 TEK 7L5 + L1 - 20Hz-5Mc/s - £700.
 TEK 7L5 + L3 - Opt 25 Tracking Gen - £900.
 TEK 7L12 - 100KHz-1800Mc/s - £1000.
 TEK 7L18 - 1.5-60GHz - £1500.
 TEK 491 10Mc/s-12.4GHz-40GHzS - £750. 12.4GHz-40GHz with Mixers.
 Tektronix Mixers are available for above ANZ to 60GHz
 Systron Donner 763 Spectrum ANZ + 4745B Preselector .01-18GHz + Two Mixers 18-40GHz in Transit Case - £3k.
 HP8673D Signal Generator .05-26.5GHz - £20k.
 Systron Donner 1618B Microwave AM FM Synthesizer 50Mc/s 2-18GHz
 R&S SWP Sweep Generator Synthesizer AM FM 4-2500Mc/s - £3.5k.
 ADRET 3310A FX Synthesizer 300Hz-60Mc/s - £600.
 HP8640A Signal Generators - 1024Mc/s - AM FM - £800.
 HP3717A 70Mc/s Modulator - Demodulator - £500.
 HP8651A RF Oscillator 22KC/s - 22Mc/s.
 HP5316B Universal Counter A+B.
 HP6002A Power Unit 0-5V 0-10A 200W.
 HP6825A Bipolar Power Supply Amplifier.
 HP461A-465A-467A Amplifiers.
 HP81519A Optical Receiver DC-400Mc/s.
 HP Plotters 7470A-7475A.
 HP3770A Amplitude Delay Distortion ANZ.
 HP3770B Telephone Line Analyser.
 HP8182A Data Analyser.
 HP59401A Bus System Analyser.
 HP6260B Power Unit 0-10V 0-100 Amps.
 HP3782A Error Detector.
 HP3781A Pattern Generator.
 HP3730A+3737A Down Converter Oscillator 3.5-6.5GHz.
 HP Microwave Amps 491-492-493-494-495-1GHz-12.4GHz - £250.
 HP105B Quartz Oscillator - £400.
 HP5087A Distribution Amplifier.
 HP6034A System Power Supply 0-60V 0-10A-200W - £500.
 HP131C Digital Voltage Source - 100V 1/2 Amp.
 HP4275A Multi Frequency L.C.R. Meter.
 HP3779A Primary Multiplex Analyser.
 HP3779C Primary Multiplex Analyser.
 HP8150A Optical Signal Source.
 HP1630G Logic Analyser.
 HP5316A Universal Counter A+B.
 HP5335A Universal Counter A+B+C.
 HP59501B Isolated Power Supply Programmer.
 HP8901A Modulation Meter AM - FM - also 8901B.
 HP5370A Universal Time Interval Counter.
 Marconi TF2370 - 30Hz-110Mc/s 750HM Output (2 BNC Sockets+Resistor for 500HM MOD with Marconi MOD Sheet supplied - £650.
 Marconi TF2370 30Hz-110Mc/s 50 ohm Output - £750.
 Marconi TF2370 as above but late type - £850.
 Marconi TF2370 as above but late type Brown Case - £1000.
 Marconi TF2374 Zero Loss Probe - £200.
 Marconi TF2440 Microwave Counter - 20GHz - £1500.
 Marconi TF2442 Microwave Counter - 26.5GHz - £2k.
 Marconi TF2305 Modulation Meter - £2.3k.
 Rcal/Dana 2101 Microwave Counter - 10Hz-20GHz - £2k.
 Rcal/Dana 1250-1261 Universal Switch Controller + 200Mc/s PI Cards.
 Rcal/Dana 9303 True RMS Levelmeter + Head - £450. IFFE - £500.
 TEKA6902A also A6902B Isolator - £300-£400.
 TEK 1240 Logic Analyser - £400.
 TEK FG510 Programmable Function Generator 20Mc/s - £600.
 TEK2465A 350Mc/s Oscilloscope - £2.5k + probes - £150 each.
 TEK CT-5 High Current Transformer Probe - £250.
 TEK J16 Digital Photometer + J6523-2 Luminance Probe - £300.
 TEK J16 Digital Photometer + J6503 Luminance Probe - £250.
 ROTEX 320 Calibrator + 350 High Current Adaptor AC-DC - £500.
 FLUKE 5102B AC-DC Calibrator - £4k.
 FLUKE 1120A IEE - 488 Translator - £250.
 Tinsley Standard Cell Battery 5644B - £500.
 Tinsley Transportable Voltage Reference - £500.
 FLUKE Y5020 Current Shunt - £150.
 HP745A+746A AC Calibrator - £600.
 HP8080A MF + 8091A 1GHz Rate Generator + 8092A Delay Generator + Two 8093A 1GHz Amps + 15400A - £800.
 HP54200A Digitizing Oscilloscope.
 HP11729B Carrier Noise Test Set .01-18GHz - LEF - £2000.
 HP3311A Function Generator - £300.
 Marconi TF2008 - AM-FM signal generator - also sweeper - 10Kc/s - 510Mc/s - from £250 - tested to £400 as new with manual - probe kit in wooden carrying box.
 HP Frequency comb generator type 8406 - £400.
 HP Vector Voltmeter type 8405A - £400 new colour.
 HP Sweep Oscillators type 8690 A & B + plug-ins from 10Mc/s to 18GHz also 18-40GHz P.O.R..
 HP Network Analyzer type 8407A + 8412A + 8501A - 100Kc/s - £500 - £1000.
 HP Amplifier type 8447A - 1-400Mc/s £200 - HP8447A Dual - £300.
 HP Frequency Counter type 5340A - 18GHz £1000 - rear output £800.
 HP 8410 - A - B - C Network Analyzer 110Mc/s to 12GHz or 18GHz - plus most other units and displays used in this set-up - 8411A - 8412 - 8413 - 8414 - 841B - 8740 - 8741 - 8742 - 8743 - 8746 - 8650. From £1000.
 Rcal/Dana 9301A - 9302 RF Millivoltmeter - 1.5-2GHz - £250-£400.
 Rcal/Dana Modulation Meter type 9009 - 8Mc/s - 1.5GHz - £250.
 Marconi RCL Bridge type TF2700 - £150.
 Marconi/Saunders Signal Sources type - 6058B - 6070A - 6055A - 6059A - 6057A - 6056 - £250-£350. 400Mc/s to 18GHz.
 Marconi TF1245 Circuit Magnification meter + 1246 & 1247 Oscillators - £100-£300.
 Marconi microwave 6600A sweep osc. mainframe with 6650 PI - 18-26.5GHz or 6651 PI - 26.5-40GHz - £1000 or PI only £600. MF only £250.
 Marconi distortion meter type TF2331 - £150. TF2331A - £200.

Tektronix Plug-Ins 7A13 - 7A14 - 7A18 - 7A24 - 7A26 - 7A11 - 7M11 - 7S11 - 7D10 - 7S12 - S1 - S2 - S6 - S52 - PG506 - SC504 - SG503 - SG504 - DC503 - DC508 - DD501 - WR501 - DM501A - FG501A - TG501 - PG502 - DC505A - FG504 - 7B80 + 85-7B92A
 Gould JDB test oscillator + manual - £150.
 Tektronix Mainframes - 7603 - 7623A - 7613 - 7704A - 7844 - 7904 - TM501 - TM503 - TM506 - 7904A - 7834 - 7623 - 7633.
 Marconi 6155A Signal Source - 1 to 2GHz - LED readout - £400.
 Barr & Stroud Variable filter EF3 0.1Hz - 100Kc/s + high pass + low pass - £150.
 Marconi TF2163S attenuator - 1GHz. £200.
 Farnell power unit H60/50 - £400 tested. H60/25 - £250.
 Rcal/Dana 9300 RMS voltmeter - £250.
 HP 8750A storage normalizer - £400 with lead + S.A or N.A Interface.
 Marconi TF2330 - or TF2330A wave analysers - £100-£150.
 Tektronix - 7514 - 7511 - 7511 - 7512 - S1 - S2 - S39 - S47 - S51 - S52 - S53 - 7M11.
 Marconi mod meters type TF2304 - £250.
 HP 5065A rubidium vapour FX standard - £1.5k.
 Systron Donner counter type 6054B - 20Mc/s - 24GHz - LED readout - £1k.
 Rcal/Dana 9083 signal source - two tone - £250.
 Systron Donner - signal generator 1702 - synthesized to 1GHz - AM/FM - £600.
 Tektronix TM515 mainframe + TM5006 mainframe - £450 - £850.
 Farnell electronic load type RB1030-35 - £350.
 Rcal/Dana counters - 9904 - 9905 - 9906 - 9915 - 9916 - 9917 - 9921 - 50Mc/s - 3GHz - £100-£450 - all fitted with FX standards.
 HP4815A RF vector impedance meter c/w probe - £500-£600.
 Marconi TF2092 noise receiver. A, B or C plus filters - £100-£350.
 Marconi TF2091 noise generator. A, B or C plus filters - £100-£350.
 Marconi 2017 S/G 10KHz - 1024MHz.
 HP180TR, HP182T mainframes £300-£500.
 Philips panoramic receiver type PM7900 - 1 to 20GHz - £400.
 Marconi 6700A sweep oscillator + 18GHz PI's available.
 HP8505A network ANZ + 8503A S parameter test set + 8501A normalizer - £4k.
 HP8505 network ANZ 8505 + 8501A + 8503A.
 Rcal/Dana VLF frequency standard equipment. Tracer receiver type 900A + difference meter type 527E + rubidium standard type 9475 - £2750.
 HP signal generators type 626 - 628 - frequency 10GHz - 21GHz.
 HP 432A - 435A or B - 436A - power meters + powerheads - Mc/s - 40GHz - £200-£1000.
 Bradley oscilloscope calibrator type 192 - £600.
 HP8614A signal generator 800Mc/s - 2.4GHz. new colour £400.
 HP8616A signal gen 1.8GHz - 4.5GHz. new colour £400.
 HP 3325A syn function gen 20Mc/s - £1500.
 HP 3336A or B syn level generator - £500 £600.
 HP 3586B or C selective level meter - £750-£1000.
 HP 3575A gain phase meter 1Hz - 13Mc/s - £400.
 HP 8683D S/G microwave 2.3 - 13GHz - opt 001 - 003 - £4.5k.
 HP 8660 A-B-C syn S/G. AM + FM + 10Kc/s to 110Mc/s PI - 1Mc/s to 1300Mc/s - 1Mc/s to 2600Mc/s - £500-£2000.
 HP 8640B S/G AM-FM 512Mc/s or 1024Mc/s. Opt 001 or 002 or 003 - £800-£1250.
 HP 86222BX Sweep PI - 01 - 2.4GHz + ATT - £1750.
 HP 8629A Sweep PI - 2 - 18GHz - £1000.
 HP 86290B Sweep PI - 2 - 18GHz - £1250.
 HP 86 Series PI's in stock - splitband from 10Mc/s - 18.6GHz - £250-£1k.
 HP 8620C Mainframe - £250. IEEE - £500.
 HP 8615A Programmable signal source - 1MHz - 50Mc/s - opt 002 - £1k.
 HP 8601A Sweep generator .1 - 110Mc/s - £300.
 HP 3488A HP - IB switch control unit - £500 + control modules various - £175 each.
 HP 8160A 50Mc/s programmable pulse generator - £1000.
 HP 853A MF ANZ - £1.5k.
 HP 8349A Microwave Amp 2 - 20GHz Solid state - £1500
 HP 3585A Analyser 20Hz - 40Mc/s - £4k.
 HP 8568B Analyser .01 - 2GHz - £5k.
 HP 3580A Analyser 5Hz - 50KHz - £1k.
 HP 1980B Oscilloscope measurement system - £600.
 HP 3455A Digital voltmeter - £500.
 HP 3437A System voltmeter - £300.
 HP 3581C Selective voltmeter - £250.
 HP 5370A Universal time interval counter - £450.
 HP 5335A Universal counter - 200Mc/s - £500.
 HP 5328A Universal counter - 500Mc/s - £250.
 HP 6034A System power supply - 0 - 60V - 0 - 10 amps - £500.
 HP 5150A Thermal printer - £250.
 HP 1645A Data error analyser - £150.
 HP 4437A Attenuator - £150.
 HP 3717A 70Mc/s modulator - £400.
 HP 3710A - 3715A - 3716A - 3702B - 3703B - 3705A - 3711A - 3791B - 3712A - 3793B microwave link analyser - P.O.R.
 HP 3730A+B RF down converter - P.O.R.
 HP 3552A Transmission test set - £400.
 HP 3763A Error detector - £500.
 HP 3764A Digital transmission analyser - £600.
 HP 3770A Amp delay distortion analyser - £400.
 HP 3780A Pattern generator detector - £400.
 HP 3781A Pattern generator - £400.
 HP 3781B Pattern generator (bell) - £300.
 HP 3782A Error detector - £400.
 HP 3782B Error detector (bell) - £300.
 HP 3785A Jitter generator + receiver - £750-£1k.
 HP 8006A Word generator - £100-£150.
 HP 8016A Word generator - £250.
 HP 8170A Logic pattern generator - £500.
 HP 59401A Bus system analyser - £350.
 HP 59500A Multiprogrammer HP - IB - £300.
 Philips PM5390 RF syn - 0.1 - 1GHz - AM + FM - £1000.
 S.A. Spectral Dynamics SD345 spectroscope 111 - LF ANZ - £1500.
 Tektronix R7912 Transient waveform digitizer - programmable - £400.
 Tektronix TR503 + TM503 tracking generator 0.1 - 1.8GHz - £1k - or TR502.
 Tektronix 576 Curve tracer + adaptors - £900.
 Tektronix 577 Curve tracer + adaptors - £900.
 Tektronix 1502/1503 TDR cable test set - £1000.
 Tektronix AM503 Current probe + TM501 m/frame - £1000.
 Tektronix SC501 - SC502 - SC503 - SC504 oscilloscopes - £75-£350.
 Tektronix 465 - 465B - 475 - 2213A - 2215 - 2225 - 2235 - 2245 - £250-£1000.
 Kikusui 100Mc/s Oscilloscope COS6100M - £350.
 Nicolet 3091 LF oscilloscope - £400.
 Rcal 1991 - 1992 - 1988 - 1300Mc/s counters - £500-£900.
 Fluke 80K-40 High voltage probe in case - BN - £100.
 Rcal Recorders - Store 4 - 4D - 7 - 14 channels in stock - £250 - £500.
 Rcal Store Horse Recorder & control - £400-£750 Tested.
 EIP 545 microwave 18GHz counter - £1200.
 Fluke 510A AC ref standard - 400Hz - £200.
 Fluke 355A DC voltage standard - £300.
 Witron 610D Sweep Generator + 6124C PI - 4 - 8GHz - £400.
 Witron 610D Sweep Generator + 61084D PI - 1Mc/s - 1500Mc/s - £500.
 Time Electronics 9814 Voltage calibrator - £750.
 Time Electronics 9811 Programmable resistance - £600.
 Time Electronics 2004 D.C. voltage standard - £1000.
 HP 8699B Sweep PI YIG oscillator .01 - 4GHz - £300. 8690B MF - £250. Both £500.
 Schlumberger 1250 Frequency response ANZ - £1500.
 Dummy Loads & power att up to 2.5 kilowatts FX up to 18GHz - microwave parts new and ex equip - relays - attenuators - switches - waveguides - Yigs - SMA-APC7 plugs - adaptors. B&K items in stock - ask for list.
 W&G Items in stock - ask for list.
 Power Supplies Heavy duty + bench in stock - Farnell - HP - Weir - Thurlby - Rcal etc. Ask for list.

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. SAE FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS, AVAILABILITY OR PRICE CHANGE. VAT AND CARRIAGE EXTRA

ITEMS MARKED TESTED HAVE 30 DAY WARRANTY. WANTED: TEST EQUIPMENT-VALVES-PLUGS AND SOCKETS-SYNCRS-TRANSMITTING AND RECEIVING EQUIPMENT ETC.

Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. No: (01274) 684007. Fax: 651160

Simple, latching audio/visual alarm


A pulse of greater than 1V amplitude applied to this alarm circuit illuminates a led and activates a piezoelectric sounder.

On the arrival of a pulse, the scr Tr_3 triggers, lighting the led which, with the $2.2k\Omega$ resistor passes the scr's holding current once it has triggered.

Programmable unijunction Tr_1 and its associated components form a relaxation oscillator, enabled when Tr_3 triggers, driving the mosfet and the sounder at a frequency and duty cycle dependent on the RC time constant and the gate voltage of Tr_1 .


Pressing the normally closed switch resets the alarm.

R. McGillivray
Ontario, Canada

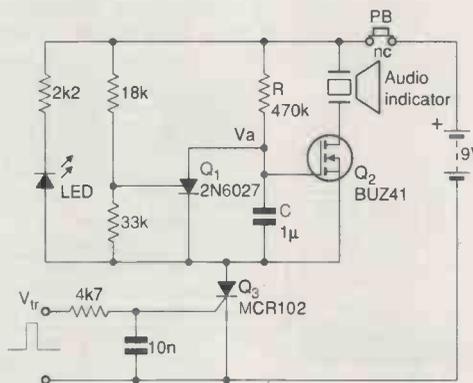

Simple alarm circuit for both visual and audible output.

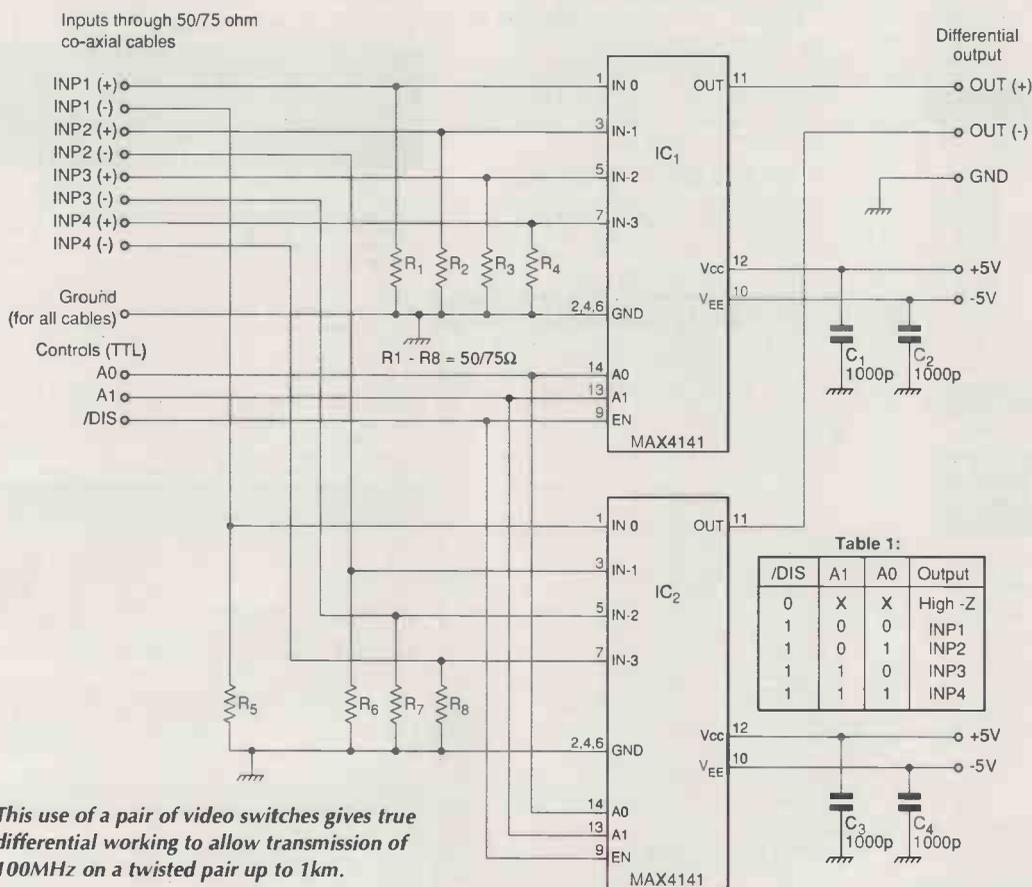Video switch transmits up to 1km on a twisted pair



This use of a pair of video switches gives true differential working to allow transmission of 100MHz on a twisted pair up to 1km.

This four-channel, differential input/output video switch was built for a computer-controlled security system, in which one of the 100MHz video signals had to be selected and transmitted 1km to control room.

Using two MAX4141 cross-point video switches confers the benefits of differential working; $\pm 5V$ input and twisted-cable transmission. Terminating resistors of 50Ω

or 75Ω , depending on the type of cable in use, should be used at the inputs to avoid reflections, and the cable receiving end must be properly terminated.

Gain response is flat at 0.98 from zero to 100MHz.

Shyam Sunder
Kalpakkam
India

£100 WINNER

Supplies always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!
THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Supplies always wanted for cash!

LOW COST PC's -

SPECIAL BUY 'AT 286'

40Mb HD + 3Mb Ram



LIMITED QUANTITY only of these 12Mhz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & Integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!
Order as HIGRADE 286 **ONLY £129.00 (E)**

| | |
|--|--------|
| Optional Fitted extras: VGA graphics card | £29.00 |
| 1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb) | £19.95 |
| Wordperfect 6.0 for Dos - when 3 1/2" FDD option ordered | £22.50 |
| NE2000 Ethernet (thick, thin or twisted) network card | £29.00 |

LOW COST 486DX-33 SYSTEM

Limited quantity of this 2nd user, superb small size desktop unit. Fully featured with standard simm connectors 30 & 72 pin. Supplied with keyboard, 4 Mb of RAM, SVGA monitor/output, 256k cache and integral 120 Mb IDE drive with single 1.44 Mb 3.5" floppy disk drive. Fully tested and guaranteed. Fully expandable
Only **£399.00 (E)**
Many other options available - call for details.

FLOPPY DISK DRIVES 3 1/2" - 8"

5 1/4" or 3 1/2" from only **£18.95 !**

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported on your PC).

| | |
|---|------------|
| 3 1/2" Panasonic JU363/4 720K or equivalent RFE | £24.95(B) |
| 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only | £25.95(B) |
| 3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop | £18.95(B) |
| 5 1/4" Teac FD-55GFR 1.2 Meg (for IBM pc's) RFE | £18.95(B) |
| 5 1/4" Teac FD-55F-03-U 720K 40/80 (for BBC's etc) RFE | £29.95(B) |
| 5 1/4" BRAND NEW Mitsubishi MF501B 360K | £22.95(B) |
| Table top case with integral PSU for HH 5 1/4" Floppy or HD | £29.95(B) |
| 8" Shugart 800/801 8" SS refurbished & tested | £195.00(E) |
| 8" Shugart 810 8" SS HH Brand New | £195.00(E) |
| 8" Shugart 851 8" double sided refurbished & tested | £250.00(E) |
| Mitsubishi M2894-63 8" double sided NEW | £275.00(E) |
| Mitsubishi M2896-63-02U 8" DS slimline NEW | £285.00(E) |
| Dual 8" cased drives with Integral power supply 2 Mb | £499.00(E) |

HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte drive with industry standard SMD interface, replaces Fujitsu equivalent model. Full manual. Only £299.00 or 2 for £525.00 (E)

| | |
|---|------------|
| 3 1/2" FUJII FK-309-26 20mb MFM I/F RFE | £59.95(C) |
| 3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv) RFE | £59.95(C) |
| 3 1/2" CONNER CP3044 40mb IDE I/F (or equiv.) RFE | £69.00(C) |
| 3 1/2" RODIME R030575 45mb SCSI I/F (Mac & Acorn) | £69.00(C) |
| 3 1/2" WESTERN DIGITAL 850mb IDE I/F Brand New | £185.00(C) |
| 5 1/4" MINGSCRIIBE 3425 20mb MFM I/F (or equiv.) RFE | £49.95(C) |
| 5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb | £69.95(C) |
| 5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested | £69.95(C) |
| 5 1/4" HP 9754B 850 Mb SCSI RFE tested | £89.00(C) |
| 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested | £195.00(C) |
| 8" FUJITSU M2322K 160Mb SMD I/F RFE tested | £195.00(E) |
| Hard disc controllers for MFM, IDE, SCSI, RLL etc. from | £16.95 |

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tunable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi-Fi audio output are provided as standard.

| | |
|--|--------|
| TELEBOX ST for composite video input type monitors | £36.95 |
| TELEBOX STL as ST but fitted with integral speaker | £39.50 |
| TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner | £69.95 |

For overseas PAL versions state 5.5 or 6 mHz sound specification.
*For cable / hyperband reception Telebox MB should be connected to a cable type service. Shipping code on all Teleboxes is (B)

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock
Call for info / list.

IC's - TRANSISTORS - DIODES

OBSELETE - SHORT SUPPLY - BULK

6,000,000 items EX STOCK

For MAJOR SAVINGS - CALL FOR SEMICONDUCTOR HOTLIST

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see -
At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, supplied in EXCEL-

LENT little used condition.
Tilt & Swivel Base £4.75
VGA cable for IBM PC included.
External cables for other types of computers CALL

Only **£119 (E)** Order as MITS-SVGA

As New - Used on film set for 1 week only!!
15" 0.28 SVGA 1024 x 768 res. colour monitors.
Swivel & tilt etc. Full 90 day guarantee. £145.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors.
Good SH condition - from £299 - CALL for Info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed
Dimensions: W14" x H12 3/4" x 15 1/2" D.
Only **£95 (E)**

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen bums). In attractive square black plastic case measuring W10" x H10" x 1 1/2" D. 240 V AC mains powered.
Only **£79.00 (D)**

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 1 1/2". Good used condition.
Only **£125 (E)**

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

SPECIAL INTEREST ITEMS

| | |
|--|-------|
| MITS. FA3445ETKL 14" Industrial spec SVGA monitors 2Kw to 400 KW - 400 Hz 3 phase power sources - ex stock | £245 |
| IBM 8230 Type 1, Token ring base unit driver | £950 |
| IBM 53F5501 Token Ring ICS 20 port lobe modules | £750 |
| IBM MAU Token ring distribution panel 8228-23-5050N | £95 |
| AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE | £550 |
| Trend DSA 274 Data Analyser with G703(2M) 64 i/o | £POA |
| Marconi 6310 Programmable 2 to 22 GHz sweep generator | £6500 |
| HP1650B Logic Analyser | £3750 |
| HP3781A Pattern generator & HP3782A Error Detector | £POA |
| HP APOLLO RX700 system units | £950 |
| HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts | £1800 |
| HP3081A Industrial workstation c/w Barcode swipe reader | £175 |
| HP6264 Rack mount variable 0-20V @ 20A metered PSU | £675 |
| HP541121A DC to 22 GHz four channel test set | £POA |
| HP7580A A1 8 pen HPGL high speed drum plotter | £1850 |
| EG+G Brookdele 95035C Precision lock in amp | £650 |
| View Eng. Mod 1200 computerised inspection system | £POA |
| Ling Dynamics 2kW programmable vibration test system | £POA |
| Computer controlled 1056 x 560 mm X Y table & controller | £1425 |
| Keithley 590 CV capacitor / voltage analyser | £POA |
| Racal ICR40 dual 40 channel voice recorder system | £3750 |
| Fiskers 45KV4 3 ph On Line UPS - New Batts Dec.1995 | £9500 |
| ICI R5030UV34 Cleanline ultrasonic cleaning system | £POA |
| Mann Tally MT645 High speed line printer | £2200 |
| Intel SBC 486/133SE Multibus 486 system. 8Mb Ram | £1200 |
| Zeta 3220-05 A0 4 pen HPGL fast drum plotters | £1150 |
| Nikon HFX-11 (Ephiphot) exposure control unit | £1450 |
| Motorola VME Bus Boards & Components List. SAE / CALL | £POA |
| Trlo 0-18 vdc linear, metered 30 amp bench PSU. New | £550 |
| Fujitsu M3041R 600 LPM band printer | £1950 |
| Fujitsu M3041D 600 LPM printer with network interface | £1250 |
| Perkin Elmer 2998 infrared spectrophotometer | £POA |
| VG Electronics 1035 TELETEXT Decoding Margin Meter | £3750 |
| Andrews LARGE 3.1 m Satellite Dish + mount (For Voyager) | £950 |
| Seikonic SD 150H 18 channel digital Hybrid chart recorder | £1995 |
| TAYLOR HOBSON Tallysurp amplifier / recorder | £750 |
| System Video 1152 PAL waveform monitor | £485 |
| Test Lab - 2 mtr square quietised acoustic test cabinets | £300 |
| Kenwood 9601 PAL Vectorscope - NEW | £650 |

Please call for further details on the above items



19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 7 1/2" H x 32 1/2" D x 22" W. Order as:

| | |
|---|-------------|
| OPT Rack 1 Complete with removable side panels. | £335.00 (G) |
| OPT Rack 2 Rack, Less side panels | £225.00 (G) |

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W)
Sold at LESS than a third of makers price !!

A superb buy at only **£195.00 (G)**

Over 1000 racks - 19" 22" & 24" wide
3 to 44 U high. Available from stock !!
Call with your requirements.

TOUCH SCREEN SYSTEM

The ultimate in 'Touch Screen Technology' made by the experts - MicroTouch - but sold at a price below cost !! System consists of a flat translucent glass laminated panel measuring 29.5 x 23.5 cm connected to an electronic controller PCB. The controller produces a standard serial RS232 or TTL output which continuously gives simple serial data containing positional X & Y co-ordinates as to where a finger is touching the panel - as the finger moves, the data instantly changes. The X & Y information is given at an incredible matrix resolution of 1024 x 1024 positions over the entire screen size !! A host of available translation software enables direct connection to a PC for a myriad of applications including: control panels, pointing devices, POS systems, controllers for the disabled or computer un-trained etc. (Imagine using your finger with 'Windows', instead of a mouse !! (a driver is indeed available !!) The applications for this amazing product are only limited by your imagination!! Complete system including Controller, Power Supply and Data supplied at an incredible price of only: **£145.00 (B)**
Full MICROTOUCH software support pack and manuals for IBM compatible PC's £29.95 RFE - Tested

LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. £59.95(A1)
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data.
Order as: XT RAM UG. 256k. £34.95 or 512k £39.95 (A1)

SIMM SPECIALS

| | |
|---|---------------------------------------|
| 1 MB x 9 SIMM 9 chip 120ns | Only £16.50 (A1) |
| 1 MB x 9 SIMM 3 chip 80 ns | £19.50 or 70ns £22.95 (A1) |
| 1 MB x 9 SIMM 9 chip 80 ns | £21.50 or 70ns £23.75 (A1) |
| 4 MB 70 ns 72 pin SIMM - with parity. | Only £95.00 (A1) |
| INTEL 486-DX33 CPU | £55.00 INTEL 486-DX66 CPU £69.00 (A1) |
| FULL RANGE OF CO-PROCESSOR'S EX STOCK - CALL FOR LIST | |

FANS & BLOWERS

| | |
|--|----------------|
| EPSON DO412 40x40x20 mm 12v DC | £7.95 10 / £65 |
| PAPST TYPE 612 60x60x25 mm 12v DC | £8.95 10 / £75 |
| MITSUBISHI MMF-D6D12DL 60x60x25 mm 12v DC | £4.95 10 / £42 |
| MITSUBISHI MMF-08C12DM 80x80x25 mm 12v DC | £5.25 10 / £43 |
| MITSUBISHI MMF-09B12DH 92x92x25 mm 12v DC | £5.95 10 / £53 |
| PANCAKE 12-3.5 92x92x18 mm 12v DC | £7.95 10 / £69 |
| EX-EQUIP AC fans. ALL TESTED 120 x 120 x 38 mm specify 110 or 240 v. £6.95. 80 x 80 x 38 mm - specify 110/240v NEW | £5.95 |
| IMHOF B26 1900 rack mnt 3U x 19" Blower 110/240v NEW | £79.95 |
| Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL | |

Issue 13 of Display News now available - send large SAE - PACKED with bargains!

DISPLAY

ALL MAIL & OFFICES
Open Mon-Fri 9.00-5.30
Dept WW. 32 Blggin Way
Upper Norwood
LONDON SE19 3XF

LONDON SHOP
Open Mon - Sat 9.00 - 5.30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
N. Thornton Health & Seahurst Park SR Rail Stations

DISTEL
The Original
FREE On line Database
Info on 20,000+ stock items!
RETURNING SOON!

ALL ENQUIRIES
0181 679 4414
FAX 0181 679 1927

-ELECTRONICS-



All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster Call. Scotland surcharge CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged © Display Electronics 1996. E & O E 06/6

Linear, 90°-180° scr trigger



When 90°-180° scr firing control is needed in an scr-controlled power supply and a simple capacitor filter is in use, this arrangement reduces non-linearity of control characteristic near 180°, where the slope of the sine wave is steep.

A comparator 741 compares the rectified output of the bridge with the control voltage, its output falling edge triggering a 555-based monostable to trigger

the scr. Firing angle now varies between 90° and 180° for a control voltage varying from the peak of the full-wave rectified ac to zero.

Output voltage on the capacitor is now stable to within about 0.05%, even at a firing angle near 180°.

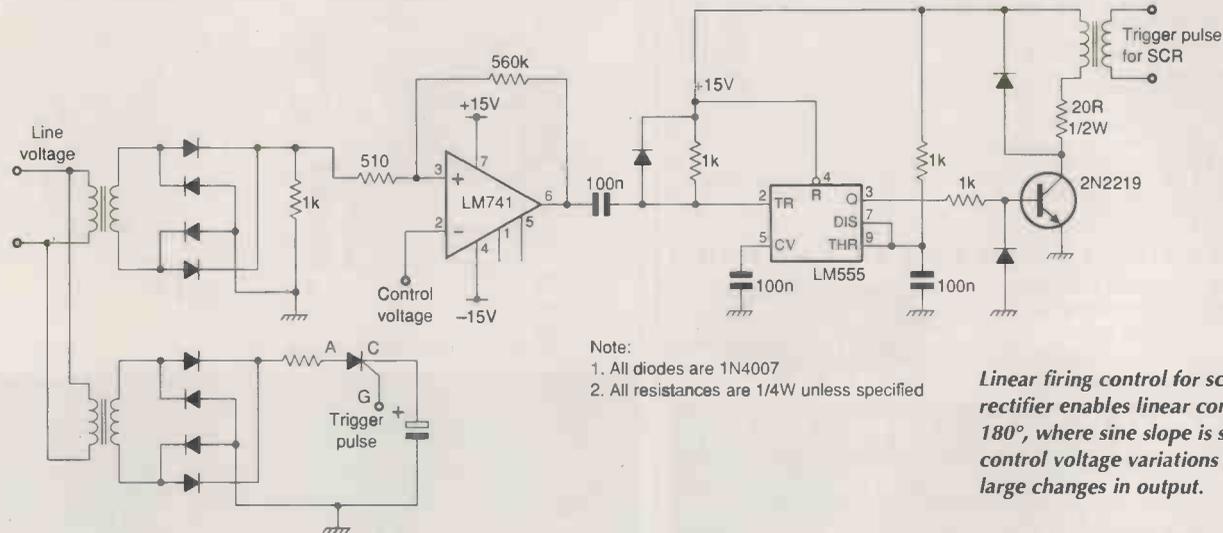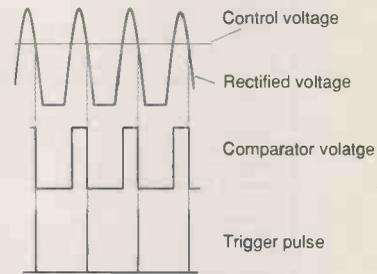*M Revathi, Ved Prakash and R Yogesh
Cat-Indore
India*



- Note:
1. All diodes are 1N4007
2. All resistances are 1/4W unless specified

Linear firing control for scr. Full-wave rectifier enables linear control even near 180°, where sine slope is steep and small control voltage variations normally give large changes in output.

Pc tests rechargeable battery capacity

This little circuit and some software, plus the pc, constitute a tester for rechargeable batteries.

The circuit shown takes its power from the pc's serial port, the voltages being set up in software. Diode D1 holds the inverting input of the op-amp to 0.6V so that a voltage over 1V from the battery, divided by $R_{2,3}$, takes the op-amp output high.


Resistor R_4 discharges the battery at 100mA, the op-amp output going low when the battery voltage falls below 1V. The C program measures the time during which the voltage is greater than 1V and, as soon as it falls below this figure, calculates the battery capacity and displays it on screen.

*Yongping Xia
Torrance
California
USA*

Listing for checking cells on the pc

```
#include <stdio.h>
#include <dos.h>
#include <time.h>
#include <conio.h>
#define DISCHARGE_CURRENT 0.12
#define MCR 4
#define MSR 6
struct time t;
time_t start_time, read_time;
int i, base_add1=0x3f8, base_add2=0x2f8;
double bat_time;
void set_port(void)
{
  outportb(base_add1+MCR, 0x01:

```

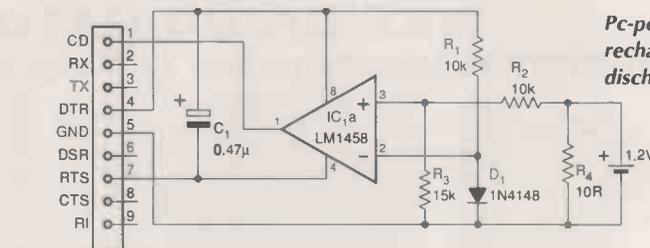


PC-powered battery tester for rechargeables. Program measures discharge time and calculates capacity.

```
delay(1000);
}
int read_port(void)
{
  int data;
  data=(inportb(base_add1+MSR)&0x80)/128;
  return (data);
}
void dis_data(void)
{
  long run_time, run_hour, run_min, run_sec,j;
  read_time=time(NULL);
  run_time=(long)difftime(read_time,
  start_time);
  run_hour=run_time/3600;
  run_min=(run_time-run_hour*3600)/60;
  run_sec=run_time-run_hour*3600-
  run_min*60;
  bat_time=DISCHARGE_CURRENT*(float)
  run_time/3.6;
  gotoxy(2, 1);
  printf("Battery has %.2fMAH", bat_time);
  gettime(&t);
  gotoxy(1,24);
  if (run_hour<10)
    printf("0");
  printf("%d:", run_hour);
  if (run_min<10)

```

```
printf("0");
printf("%d:", run_min);
if (run_sec<10)
  printf("0");
printf("%d", run_sec);
}
void main(void)
{
  int read_data;
  clrscr();
  set_port();
  start_time=time(NULL);
  gotoxy(60,24);
  printf("Hit any key to quit");
  bat_time=0;
  do{
    read_data= (read_port ());
    dis_data();
    delay(1000);
  } while(!kbhit() && read_data!=0);
  if (read_data==0)
  {
    gotoxy(1,24);
    printf("Test is done");
    getch();
  }
}
```


Applying magnetoresistance

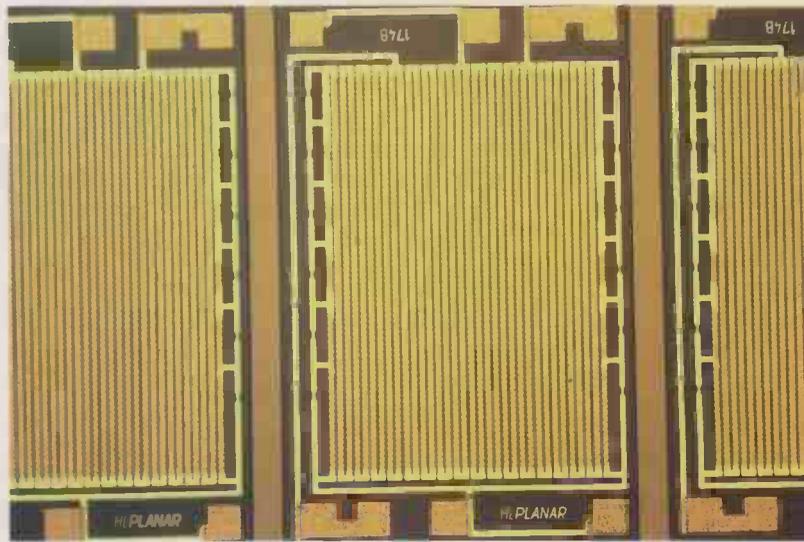

With circuits examples including a sensor for the Earth's magnetic field and an overcurrent switch for protecting igbts, Neil Chadderton demonstrates the

Layout of a typical magnetoresistive chip is shown in Fig. 1, and is for example the chip used in the ZMY20 sensor. Thin film stripes are a characteristic feature of a magnetoresistive chip. These stripes are made by photolithography and consist of permalloy, $\text{Ni}_{18}\text{Fe}_{19}$ – a magnetic material evaporated on an oxidised silicon wafer. The electrical resistivity of the stripes is changed by a magnetic field H_y due to the magnetoresistive effect. The field H_y causes a rotation of the magnetisation in the stripe, Fig. 2. Resistivity R of a permalloy stripe depends on the angle between the directions of electric current, I , and magnetisation M :

$$R = R_0 + \Delta R_0 \cos 2\alpha.$$

where ΔR_0 describes the strength of the magnetoresistive effect.

The maximum relative change of resistivity $\Delta R_0/R$ is approximately 2 to 3% for permalloy. The relationship between an external field H_y and angle α is determined by the geometrical dimensions of the stripe and the magnetic anisotropy of permalloy. This is taken into account by introducing a field H_0 that represents the demagnetising and anisotropic field. One obtains,

$$\sin^2 \alpha = \frac{H_y^2}{H_0^2} \quad \text{for } H \leq H_0$$

$$\sin^2 \alpha = 1 \quad \text{for } H \geq H_0$$

The characteristic of a magnetoresistive stripe as a field sensor is:

$$R = R_0 + \Delta R_0 \left(1 - \frac{H_y^2}{H_0^2} \right) \quad \text{for } H \leq H_0.$$

A linear characteristic of the magnetoresistive sensor is required to measure a small magnetic field. The linear behaviour of the magnetoresistive sensor is achieved by

using a 'Barber-pole' geometry. The stripes in Fig. 1 are covered with aluminium bars having an inclination of 45° to the stripe axis. Aluminum has a low resistivity compared to permalloy. Therefore the Barber poles cause a change of the current direction. The angle between current and magnetisation is shifted by 45° , Fig. 3. The relationship between resistance and magnetic field is now,

$$R = R_0 + \frac{\Delta R_0}{2} \pm \Delta R_0 \left(\frac{H_y}{H_0} \right) \sqrt{1 - \frac{H_y^2}{H_0^2}}$$

A linear characteristic of the sensor is given around $H_y^2/H_0^2=0$. The sign in this equation is determined by the inclination of the Barber poles, $\pm 45^\circ$, to the stripe axis. The characteristic of a sensor with and without Barber poles is presented in Fig. 4.

The stripes of the magnetoresistive chip are arranged as a meandering pattern. They form a Wheatstone bridge which is

Fig. 1. Above, magnetoresistive magnetic field sensor chip photograph.

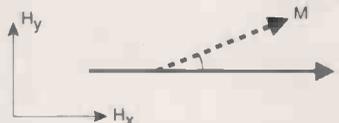


Fig. 2. Magnetoresistive effect depends on the angle between the direction of electric current I and magnetisation M . A rotation of the magnetisation in a permalloy stripe takes place when a magnetic field in the y direction is applied. Without an external field the magnetisation is along the x direction due to the shape of the stripe.

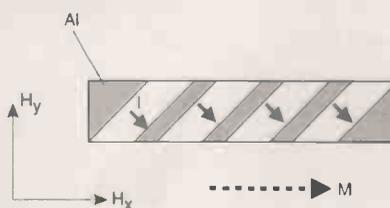


Fig. 3. Covering the stripe with 'barber poles' consisting of aluminium changes the direction of the current. This does not influence the direction of magnetisation.

shown schematically in Fig. 5. The applied voltage is V_b . Each half bridge consists of two resistors with different Barber-pole orientations. Voltage between the resistors of a half bridge changes upon application of a magnetic field. The resistance of one resistor increases, while the other

resistor has a lower resistance due to the differing field characteristic. Adding a second half bridge with an opposite arrangement of Barber poles provides a Wheatstone bridge. Voltage difference V_0 is the output signal of the sensor. Each half bridge is trimmed to $V_b/2$ with an additional resistor in order to get an output voltage close to zero when no external field is applied. The trimming structures of the resistors in Fig. 1 mark off the meander stripes on the left and right side of the chips.

Fig. 4. Characteristics of magnetoresistive sensors. The barber-pole structure enables a linear behaviour of the sensor for a small magnetic field.


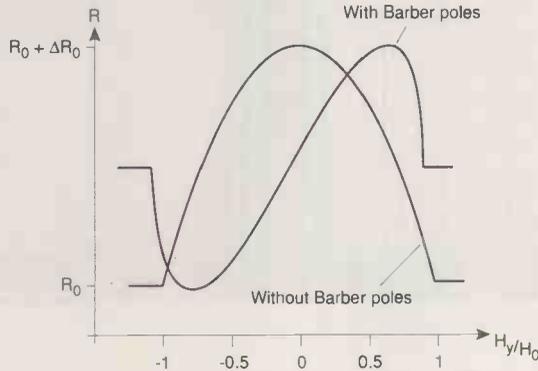


Fig. 5. Wheatstone bridge of a magnetoresistive sensor with barber-pole structure. The bridge is balanced by laser trimming.

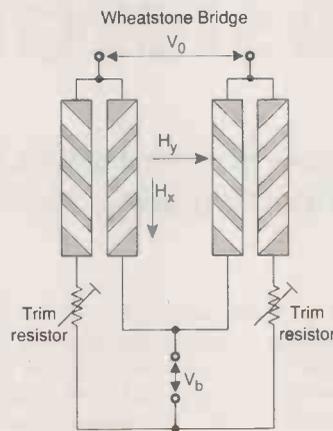

Operating conditions and parameters

The shape of the stripe and the anisotropy of permalloy only define an axis along the x-direction for the magnetisation without external field H_y . This means that in this state the stripe can have areas with a different direction of magnetisation (magnetic domains) and the sensor does not work in a stable way. A safe operation of the sensor is achieved by applying an auxiliary field H_x . This field defines the direction

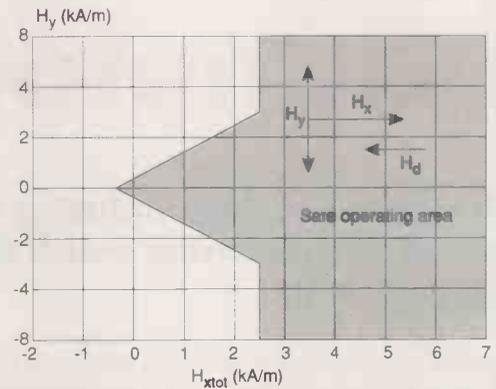


Fig. 6. Safe operating area of ZMY20/ZMZ20 magnetoresistive sensors. $H_{x(tot)}$ is $H_x + H_d$, ambient temperature is -25°C and H_d is the disturbing field.

Appendix B. Extract from the ZMY20/30, ZMZ20/30 magnetoresistive sensor data sheet. Most of these characteristics assume an ambient temperature of 25° and H_y of 3kA/m .

| Parameter | Symbol | Min. | Typ. | Max. | Unit | Test conditions |
|---|--------------------|------|------|------|-------------------------------|--|
| Bridge resistance | R_{br} | | | | | |
| ZMY20/ZMZ20 | | 1.2 | 1.7 | 2.2 | $\text{k}\Omega$ | |
| ZMY30/ZMZ30 | | 2.0 | 3.0 | 4.0 | | |
| Output voltage range | V_o/V_B | | | | | |
| ZMY20/ZMZ20 | | 16 | 18 | 22 | mV/V | |
| ZMY30/ZMZ30 | | 12 | 16 | 20 | | |
| Open-circuit sensitivity | S | 3.2 | 4.0 | 4.8 | $(\text{mV/V})/(\text{kA/m})$ | No disturbing field, H_d , allowed |
| ZMY20/ZMZ20 | | 2.0 | 3.0 | 4.0 | | |
| ZMY30/ZMZ30 | | | | | | |
| Hysteresis of output | V_{OH}/V_B | | | 50 | $\mu\text{V/V}$ | $H_y \leq 2\text{kA/m}$ |
| Offset | V_{off}/V_B | -1.0 | | +1.0 | mV/V | |
| Operating frequency | f_{max} | 0 | | 1 | MHz | |
| Temp. coeff. of offset | TCV_{off} | -3 | | +3 | $(\mu\text{V/V})/\text{K}$ | $T_{amb} = -25 \dots +125^\circ\text{C}$ |
| Temp. coeff. of bridge resistance | TCR_{br} | | 0.3 | | $\%/K$ | $T_{amb} = -25 \dots +125^\circ\text{C}$ |
| Temp. coeff. of open circuit sensitivity $V_B=5\text{V}$ | TCS_V | | -0.4 | | $\%/K$ | $T_{amb} = -25 \dots +125^\circ\text{C}$ |
| Temp. coeff. of open circuit sensitivity $I_B=3\text{mA}$ | TCS_I | | -0.1 | | $\%/K$ | $T_{amb} = -25 \dots +125^\circ\text{C}$ |

of the magnetisation. The range of H_y for safe sensor operation is determined by the strength of the auxiliary field. The safe operating area of the sensor is demonstrated in Fig. 6.

Field $H_{x(tot)}=H_y+H_d$ determines the allowed field values for H_y , where H_d is an external disturbing field in the x-direction.

There is no limitation for H_y in the case of $H_{x(tot)} \geq 2.6 \text{ kA/m}$. A small permanent magnet is sufficient to create the auxiliary field. Where ZMZ 20/30 or ZMY 20/30 devices are used, the magnet can be glued on the sensor package. Another option is the ZMY20M which provides a very compact sensor including an integrated magnet, and is available in surface mount packaging.

The operating data sheet parameters of the Wheatstone bridge are referred to an input voltage $V_b=1\text{V}$, due to the linear relationship between input and output voltage in this region.

The sensitivity S [mV/V/kA/m] of the magnetoresistive sensor is defined as the slope of the output voltage versus external field for $-1\text{kA/m} \leq H_x \leq 1\text{kA/m}$. This parameter depends on the geometry of the permalloy meander and the auxiliary field. The latter is demonstrated in Fig. 7 for $H_x=3\text{kA/m}$ and $H_x=6\text{kA/m}$. Note the small operating area in the case of $H_x=0\text{kA/m}$. A high sensitivity of the sensor leads to a small operating area for H_y .

The Wheatstone bridge is balanced without the application of an external field of $H_y \leq 0.1\text{kA/m}$.

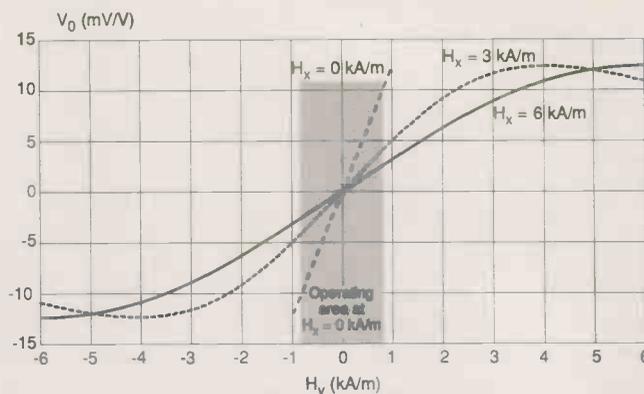


Fig. 7. Sensor output characteristic of ZMY20/ZMZ20. Sensitivity of the sensor can be controlled by applying auxiliary field H_x . This auxiliary field is necessary for sensor operation in a large field range, $V_o=f(H_y)$; H_x -parameter; $V_b=\text{const}$; $T_{\text{amb}}=-25^\circ\text{C}$.

Fig. 8. Overcurrent switch using ZMC20 for protection of power lights,

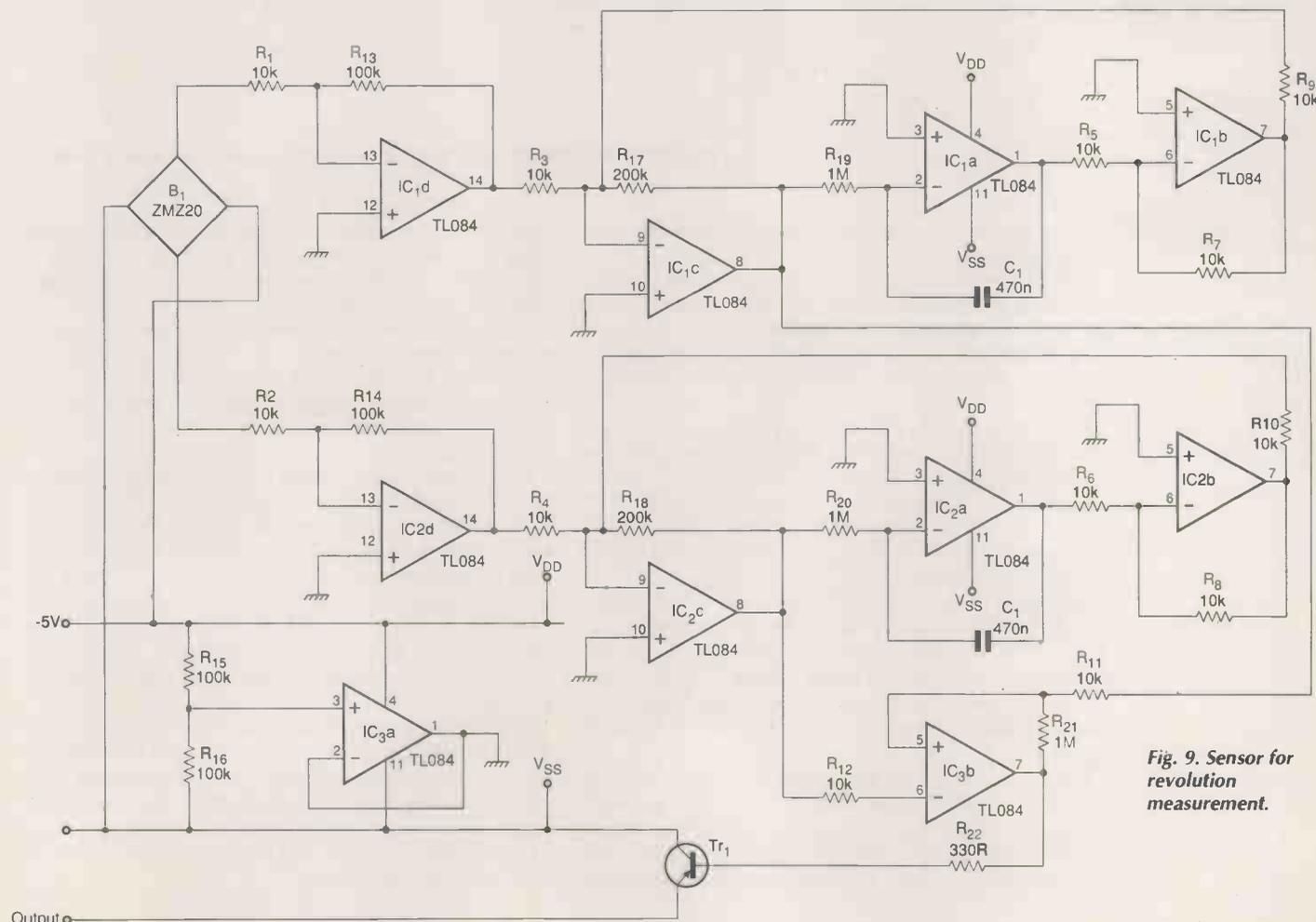
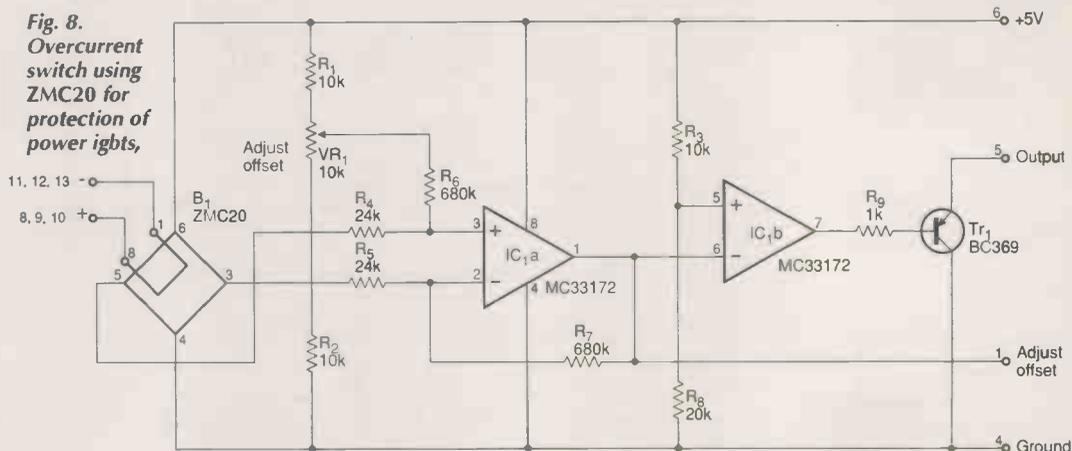


Fig. 9. Sensor for revolution measurement.

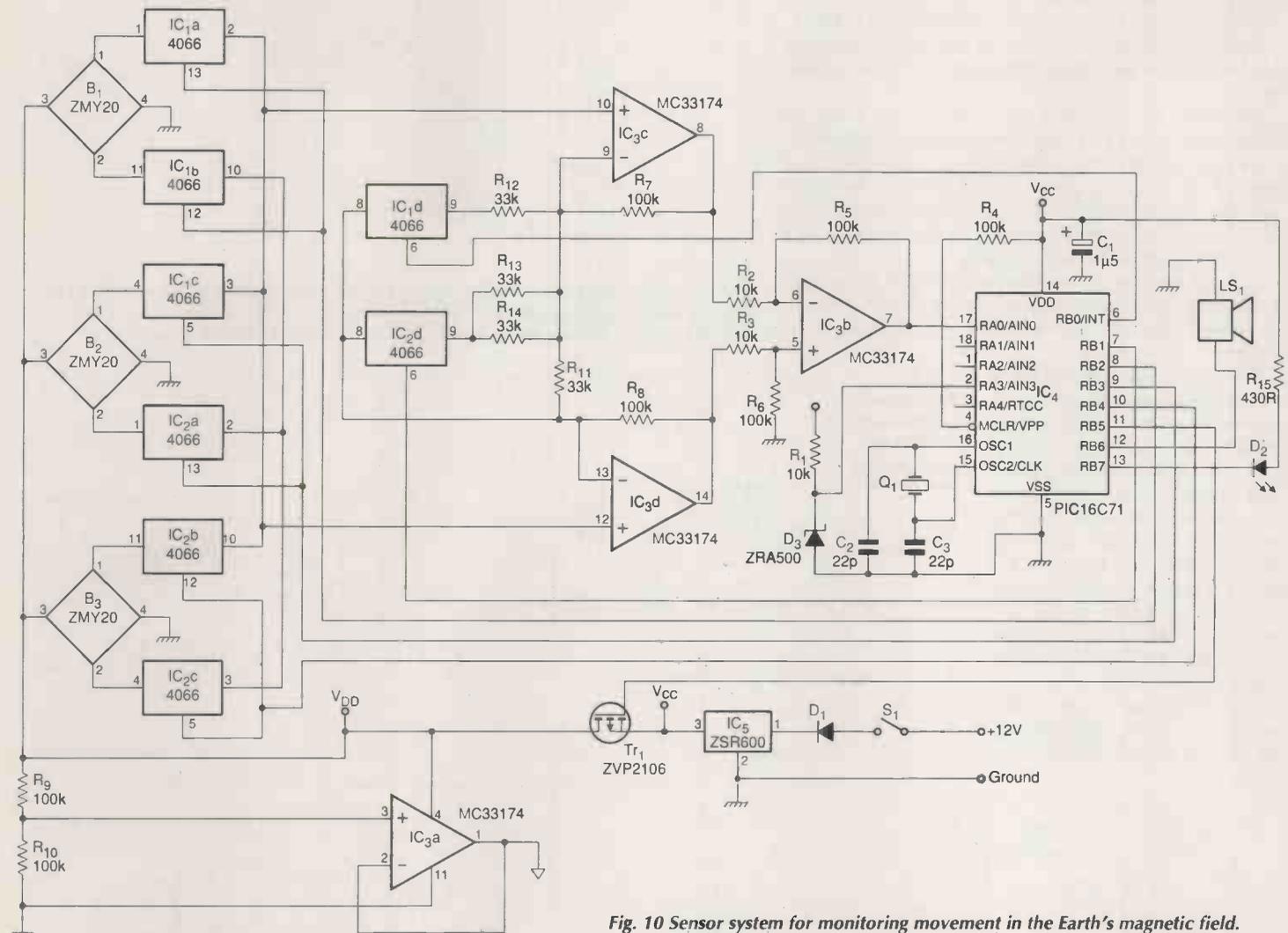


Fig. 10 Sensor system for monitoring movement in the Earth's magnetic field.

In this case, output voltage of the sensor is close to zero at room temperature.

Deviation of the output voltage from zero is called the offset voltage V_{off}/V_b [mV/V]. The offset is caused by small geometric variations of the bridge which occur during the photolithographic process. The offset of the bridge is adjusted by laser trimming. The voltage output of each half bridge is $V_b/2$.

Bridge resistance R_{br} [%/K] of the magnetoresistive sensor depends linearly on temperature. The temperature coefficient of bridge resistance TCR_{br} [%/K] is positive. This is typical for metals. The temperature coefficient of sensitivity, TCS [%/K] of the sensor is negative for $V_b = \text{const}$ (TCS_V), because the strength of the magnetoresistive effect becomes smaller with increasing temperature.

In the case of $I_B = \text{const}$ (TCS_I), when the sensor is powered by a constant current supply, the temperature dependence of the sensitivity is reduced due to the linear relationship between input and output voltage. A higher bridge resistance caused by a rise in temperature leads to an increased applied voltage, partly compensating the change of sensitivity.

The Wheatstone bridge cannot fully compensate the temperature dependence of the resistors. The temperature coefficient of offset voltage TCV_{off} [$\mu\text{V}/\text{V}/\text{K}$] is due to local changes of resistivity in the permalloy thin film and photolithographic variations. This characteristic of the magne-

toresistive sensor limits the measurement of small magnetic fields in a wide temperature range, especially in the case of static fields. Two sensors can be selected having a comparable temperature coefficient.

Offset drift is partly eliminated by using the difference of the output voltages of both sensors. Another elegant way to avoid offset drift is to invert the direction of the auxiliary field, thus inverting the output voltage of the sensor. This can be done by small coils providing an auxiliary field that can change its direction.

Hysteresis of output voltage $V_{off(H)}/V_b$ [mV/V] describes the accuracy of the magnetoresistive sensor. The magnetisation of the permalloy stripe is not completely homogeneous. There are small areas of the meander, especially at the corners of the stripes, where the magnetisation is pinned and does not correctly follow the external field. The hysteresis is measured in a magnetic field loop, where H_y goes from $-3\text{kA}/\text{m}$ to $3\text{kA}/\text{m}$ and back to $0\text{kA}/\text{m}$ ($H_x = 3\text{kA}/\text{m}$). $V_{off(H)}/V_b$ denotes the shift of the offset voltage caused by this loop.

The maximum range of output voltage $\Delta V_0/V_b$ [mV/V] is defined as the difference of output voltage for $\alpha = 0^\circ$ and $\alpha = 90^\circ$, where α denotes the angle between current and magnetisation of the magnetoresistive stripe. This means that $\Delta V_0/V_b$ represents the strength of the magnetoresistive effect. This parameter decreases with temperature and determines the sensitivity of the sensor.

Applications

Some examples of applications for magnetoresistive sensors are presented in the panel.

Figure 8 shows a ZMC20 current sensor being used as a basis for an overcurrent trip switch used to protect power igbts within a motor driver system. The circuit reacts within 3µs to prevent latch-up related failure under transient/pulse conditions, and was built within a module measuring 35×20×25mm. An external 10kΩ preset potentiometer is required for offset adjustment. Supply voltage is +5V ±10% at 10mA; output is via an open-collector transistor rated at 1A, 20V; operating temperature range is 0 to 80°C.


Figure 9 provides a method for revolution measurement by reacting to a modulated magnetic field due to a rotating cog. The circuit gives a signal whose frequency is proportional to

the rotational velocity of the cog, and a high level output for no rotation.


Figure 10 shows an application circuit for three-dimensional magnetic field observation. When the unit is enabled, it calibrates itself to the existing magnetic field of the earth, and then generates a warning signal if it is moved. The system employs three ZMY20 sensors – one for each dimension – and a c-mos e-prom microcontroller with an a-to-d converter. Similar circuits have been designed for automotive immobiliser/alarm systems that monitor the position of the vehicle by sensing the magnetic field of a movable permanent magnet. This magnet is necessary to shield the sensor from disturbing fields (generated by supply lines, car alternators, etc.) Supporting software for these systems is available on request. ■

Magnetic sensors discussed in this article are available from 2001 Electronics Components Ltd, Stevenage Business Park, Pin Green, Stevenage ST1 4SU, tel. 01438 742001, fax 742002.

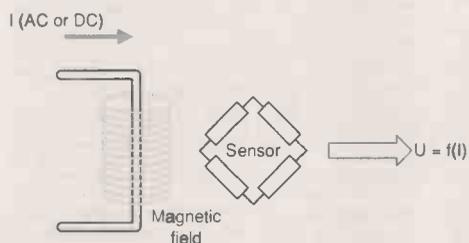
Application outlines for the magnetoresistive sensor.





Measurement of Current - ac or dc

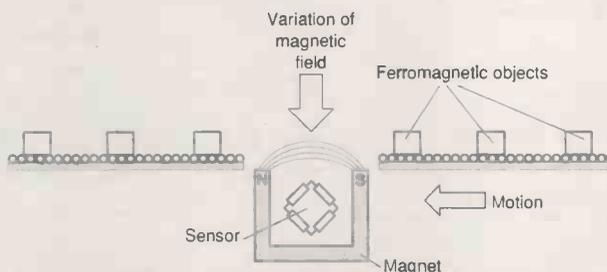



Detection of ferromagnetic objects

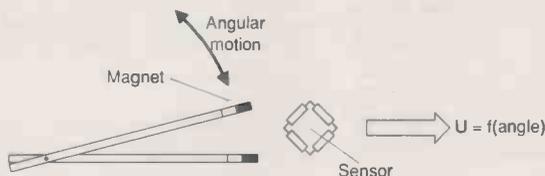


Measurement of angular position

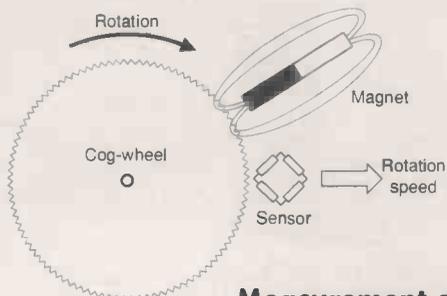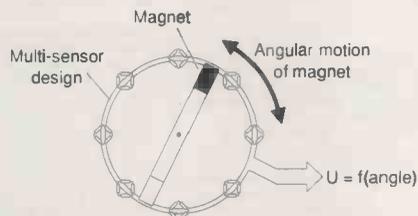

Measurement of rotation velocity

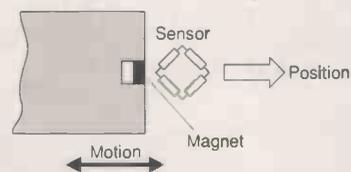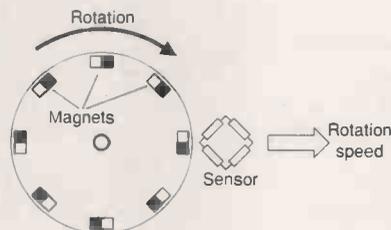

Position sensing

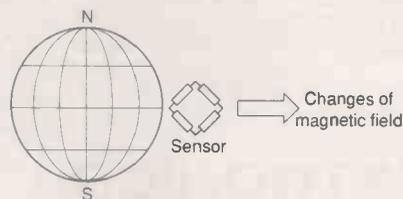

Measurement of the Earth's Magnetic Field

COMPUTER ICS

| | |
|---|----------|
| TMS 9900L-40 PULLS | £20 ea |
| S9900 NEW AMD EQUIVALENT | £30 ea |
| MC6802 PROCESSOR | £2 ea |
| AM27C020-125L1 SURFACE MOUNT EPROM USED/WIPED | £1.50 |
| P8271 BBC DISC CONTROLLER CHIP EX EQPT | £25 |
| 2817A-20 (2K X 8) EPROM ex eqpt | £2 |
| D41256C-15 256K X 1 PULLS | 9 FOR £5 |
| P8749H MICRO | £5 |
| D8751-B NEW | £10 |
| MK48202-20 ZERO POWER RAM EQUIV 6116LP | £4 |
| USED 4164-15 | £6p |
| BBC VIDEO ULA | £10 |
| 8051 MICRO | £1.25 |
| FLOPPY DISC CONTROLLER CHIPS 1771 | £16 |
| FLOPPY DISC CONTROLLER CHIPS 1772 | £17.50 |
| 68000-8 PROCESSOR NEW | £6 |
| HD6384-8 | £5 |
| 27C4001 USED EPROMS | £4 |
| 27C2001 USED EPROMS | £2.50 |
| 1702 EPROM NEW | £6 |
| 2114 EX EQPT | 50p |
| 4416 EX EQPT | 70p |
| 6264-15 8K STATIC RAM | £1.50 |
| 280A SIO-O | £1.25 |
| 7126 3/4 DIGIT LCD DRIVER CHIP | £2 ea |
| 2816A-30 HOUSE MARKED | £2 |
| USED TMS2532JL | £2.50 |
| 2708 USED | £2 |
| HM6167LP-8 | £5p |
| 68000-10 PROCESSOR | £8 |
| 8255-5 | £1.40 |
| 2114 CMOS (RCA 5114) | £1.80 |
| WD16C550-PC UART | £3 |
| ZNA27E-8 | £5 |
| 27C256-26 USED | £1.50 |

REGULATORS

| | |
|---------------------------------|--------|
| LM338K | £6 |
| LM323K 5V 3A PLASTIC | £3 |
| LM323K 5V 3A METAL | £3 |
| LM350K (VARIABLE 3A) | £3 |
| 78H12AC 12V 5A | £5 |
| LM317H T05 CAN | £1 |
| LM317T PLASTIC TO220 variable | £1 |
| LM317 METAL | £2.20 |
| 7812 METAL 12V 1A | £1 |
| 7805/12/15/24 | 30p |
| 7905/12/15/24 | 30p |
| CA3085 TO99 variable reg | 2/£1 |
| 78HGASC + 79HGASC REGULATORS | £30 ea |
| LM123 ST93 5V 3A TO3 REGS | £3 ea |
| UC3524AN SWITCHING REGULATOR IC | 60p |
| 78L12 SHORT LEADS | 10/£1 |
| LM2950ACZ5.0 | 60p |

CRYSTAL OSCILLATORS

| | |
|--|----------|
| 307 2KHZ 1M000000 1M8432 2M457000 3M6864 4M000000 | |
| 5M000000 5M06800 5M760000 6M000000 6M1440 7M000000 | |
| 3M372800 7M5 8M000000 9M2160000 10M0 12M000000 | |
| 14M318 14M3818 16M00 17M625600 18M000000 18M432 19M050 | |
| 19M2 19M440 20M000 20M0150 21M676 22M1184 23M587 | |
| 24M0000 25M1748 25M175 25M1889 27M + 36M 27M00000 | |
| 28M322 32M000000 32M0000 35M/MOUNT 33M3330 35M4816 | |
| 38M100 40M000 41M539 42M000000 44M444 44M900 44M0 | |
| 48M00000 50M000 55M000 56M00920 64M000000 66M667 76M1 | |
| 80M0 84M0 | £1.50 ea |

CRYSTALS

| | |
|---|-------|
| 32K768 1MHZ 1M8432 2M000 2M1432 2M304 2M4576 3M000 | |
| 3M2768 3M400 3M579545 3M58564 3M600 3M6864 3M93218 | |
| 4M000 4M190 4M194304 4M2056 4M33614 4M608 4M9152 5M000 | |
| 5M0688 6M000 6M041952 6M200 6M400 7M37280 8M000 8M06400 | |
| 8M448 8M63256 8M8670 9M3750 9M8304 10M240 10M245 | |
| 10M368 10M70000 11M000 11M062 11M98135 12M000 12M5 | |
| 13M000 13M270 13M875000 14M000 14M318 14M7450 14M7456 | |
| 15M0000 16M000 17M6250 18M432 20M000 21M300 | |
| 21M400M15A 24M000 25M000 26M995 27M045 RD 27M095 OR | |
| 27M145 BL 27M145 YW 27M195 GN 28M4696 30M4696 31M4696 | |
| 31M4696 34M368 36M75625 36M76875 36M78125 36M79375 | |
| 36M80625 36M81875 36M83125 36M84375 38M900 48M000 | |
| 51M05833 54M1916 55M500 57M7416 57M7583 69M545 69M550 | |
| 96M000 111M800 114M8 | £1 ea |

TRANSISTORS

| | |
|-----------------------------|--------------------|
| MPSA42 | 10/£1 |
| MPSA92 | 10/£1 |
| 2N2907A | 10/£1 |
| BC477, BC488 | 10/£1 |
| BC107 BCY70 PREFORMED LEADS | |
| full spec | £1 £4/100 £30/1000 |
| BC557, BC238C, BC308B | £1.30 £3.50/100 |
| 2N2907 PLASTIC CROPPED | £1/15 £4/100 |
| BC548B SHORT LEADS | £3/100 £20/1000 |

POWER TRANSISTORS

| | |
|---------------------------------|--------------|
| OC29 | £2 ea |
| 2SC1520 sim BF259 | 3/£1 100/£22 |
| TIP 141/2 £1 ea TIP 112/42B | 2/£1 |
| IRF620 TO-220 12A 200v | 2/£1 |
| SE9301 100V 10A DARL SIM TIP121 | 2/£1 |
| BD680 | 4/£1 |
| PLASTIC 3055 OR 2955 equiv 50p | 100/£35 |

TEXTOL ZIF SOCKETS

| | |
|---|----------|
| 28 PIN USED | £3 |
| ZIF 64 WAY SHRINK DIP SKT TEXTOL 264-1300-00 1.78mm | |
| SPACING ON PCB WITH 4MHz RESONATOR | £10 |
| SINGLE IN LINE 32 WAY CAN BE GANGED FOR USE WITH ANY DUAL IN LINE DEVICES | £2/£1.50 |
| COUPLING SUPPLIED | |

MISCELLANEOUS

| | |
|--|------------|
| AAA NICADS HI CAPACITY 360mH/HR 3 CELL PACK | £3 |
| 25A SOLID STATE RELAY 240v AC ZERO VOLTS SWITCHING | £10 |
| XENON STROBE TUBE | £1.60 |
| Narrow angle infra red emitter LED55C | 2/£1 |
| UM61 116M-2L surface mount 1000 available | £1 |
| CNY65 OPTO ISOL 3000 available | 50p |
| OPTO ICS also available TLP550 TLP666GF | |
| 68 way PLCC SKT 100 available | £1 each |
| 100 wa PLCC SKT 100 available | £1.50 each |
| 1250pF POSTAGE STAMP COMPRESSION TRIMMER | £1 |
| LM324 (Quad 741) | 4/£1 |
| MINIATURE FERRITE MAGNETS 4x4x3mm | 10/£1 |
| TL071 LO NOISE OP AMP | 5 for £1 |
| TL081 OP AMP | 4 for £1 |
| 47000u 25v SPRAGUE 36D | £3.50 (£2) |
| 12 way dll sw | £3 for £1 |
| 10NF 63V X7R PHSU SURFACE MOUNT 100K available | |

SWITCHED MODE PSU 40 WATT UNCASED QTY. AVAILABLE +5v
5A, +12V 2A, 12V 500mA FLDATING

220R 2.5W WIREWOUND RESISTOR 60K AVAILABLE £0.95 (£2)

| | |
|--|-----------|
| CMOS 555 TIMERS | £50/1000 |
| 2/3 AAA LITHIUM cells as used in compact cameras | 2/£1 50 |
| PASSIVE INFRA RED SENSOR CHIP + MIRROR + CIRCUIT | £2 ea |
| EUROCARD 96-WAY EXTENDER BOARD | £10 ea |
| 290 x 100mm | |
| DIN 41612 96-WAY A/B/C SOCKET PCB RIGHT ANGLE | £1.30 |
| DIN 41612 96-WAY A/B/C SOCKET WIRE WRAP PINS | £1.30 |
| DIN 41612 64-WAY A/C SOCKET WIRE WRAP PINS | £1 |
| DIN 41612 64-WAY A/C PLUG PCB RIGHT ANGLE | £1 |
| DIN 41612 64-WAY A/B SOCKET WIRE WRAP (2-ROW BODY) | £1 |
| BT PLUG + LEAD | 3/£1 |
| MIN. TOGGLE SWITCH 1 POLE c/o PCB type | 5/£1 |
| LCD MODULE sim. LM018 but needs 150 to 250V AC for display | |
| 40 x 2 characters 182 x 35 x 13mm | £10 |
| 6-32 UNC 5/16 POZI PAN SCREWS | £1/100 |
| NUTS | £1.25/100 |
| PUSH SWITCH CHANGEOVER | 2/£1 |
| RS232 SERIAL CABLE D25 WAY MALE CONNECTORS | |
| £5.90 ea (£1.30) | |

25 FEET LONG, 15 PINS WIRED BRAID + FOIL SCREENS
INMAC LIST PRICE £30

| | |
|---|-------|
| AMERICAN 2/3 PIN CHASSIS SOCKET | 2/£1 |
| WIRE ENDED FUSES 0.25A | 30/£1 |
| NEW ULTRASONIC TRANSDUCERS 32kHz | £2/pr |
| POWER SMALL CYLINDRICAL MAGNETS | 3/£1 |
| 8NC 500HM SCREENED CHASSIS SOCKET | 2/£1 |
| SMALL MICROWAVE DIODES AE1 OC1026A | 2/£1 |
| D.I.L. SWITCHES 10-WAY 1/8-WAY 80p 4/5/6-WAY | 80p |
| 180VOLT 1 WATT ZENERS also 12V & 75V | 20/£1 |
| MIN GLASS NEONS | 10/£1 |
| RELAY 5V 2-pole changeover looks like RS 355-741 marked STC | |
| 47W Bost | £1 ea |
| MINIATURE CO-AX FREE PLUG RS 456-071 | 2/£1 |
| MINIATURE CO-AX PCB SKT RS 456-093 | 2/£1 |
| PCB WITH 2N2646 UNIJUNCTION WITH 12V 4-POLE RELAY | 1/£1 |
| 400 MEGOHM THICK FILM RESISTORS | 4/£1 |

STRAIN GAUGES 40 ohm Foil type polyester backed
balco grid alloy £1.50 ea 10+ £1

| | |
|--|---------------|
| ELECTRET MICROPHONE INSERT | 2/£1 |
| Linear Hall effect IC Micro Switch no 613 SS4 sim RS 304-267 | |
| £2.50 100+ £1.50 | |
| 1 pole 12-way rotary switch | 4/£1 |
| AUDIO ICS LM380 LM386 | £1 ea |
| 555 TIMERS £1 741 OP AMP | 6/£1 |
| ZN414 AM RADIO CHIP | 80p |
| COAX PLUGS nice ones | 4/£1 |
| COAX BACK TO BACK JOINERS | 3/£1 |
| INDUCTOR 20µH 1.5A | 5/£1 |
| 1.25 inch PANEL FUSEHOLDERS | 3/£1 |
| 12V 1.2W small w/e lamps fit most modern cars | 10/£1 |
| STEREO CASSETTE HEAD | £2 |
| MONO CASS. HEAD £1 ERASE HEAD | 50p |
| THERMAL CUT OUTS 50 77 85 120°C | £1 ea |
| THERMAL FUSES 220°C/121°C 240V 15A | 5/£1 |
| TRANSISTOR MOUNTING PADS TO 5/TO-18 | £3/1000 |
| TO-3 TRANSISTOR COVERS | 10/£1 |
| PCB PINS FIT 0.1 inch VERO | 200/£1 |
| TO-220 mica's + bushes | 10/50p 100/£2 |
| TO-3 mica's + bushes | 15/£1 |
| Large heat shrink sleeving pack | £2 |
| IEC chassis plug filter 10A | £3 |
| POTS SHORT SPINDLES 2K5 10K 25K 1M 2M5 | 4/£1 |
| 40k U/S TRANSDUCERS EX-EQPT NO DATA | £1/pr |
| LM3352 10Mv/degree C | £1 |
| LM2342 CONST. CURRENT I.C. | £1 |
| BNC TO 4MM BINDING POST SIM RS 455-961 | £1 |
| MIN PCB POWER RELAYS 10.5v COIL 6A CONTACTS 1 pole c/o | |

BANDOLIERR COMPONENTS ASSORTED Rs, Cs, ZENERS £5/1000

| | |
|--|---------------------|
| LCD MODULE 16 CHAR. X 1 LINE (SIMILAR TO HITACHI LM10) | £5 |
| OP11264A 10Kv OPTO ISOLATOR | £1.35 ea 100+ £1 ea |
| 'LOVE STORY' CLOCKWORK MUSICAL BOX MECHANISM | £1 ea |
| MADE BY SANKYO | £1 ea |
| Telephone cable clips with hardened pins | 500/£2 |
| 10,000uF 16v PCB TYPE 30mm DIA x 31mm | 2/£1 |
| EC CHASSIS FUSED PLUG B-LEE L2728 | 3/£1 |
| 2A CERAMIC FUSE 1.25 inch OB | 10/£1 |
| 46 WAY IDC RIBBON CABLE 100 FOOT REEL | £5 + CARR |
| 20mm PCB FUSEHOLDER | 5/£1 |
| IEC CHASSIS FUSED PLUG B-LEE L2728 | 3/£1 |
| ASTEC MODULATOR VIDEO + SOUND UM1287 | £2.25 |
| BARGRAPH DISPLAY 8 RED LEDS | £1.50 |
| NE567 PHASE LOCKED LOOP | 2/£1 |
| NE564 | £1 |
| TL084 | 4/£1 |
| IR2432 SHARP 12 LED VU BAR GRAPH DRIVER | £1.25 |
| 10A CORCOM MAINS RFI FILTER EX. EQPT | £2 100 + £1.50 |
| 8 OHM MYLAR CONE LOUDSPEAKER 55mm DIA x 10mm | |
| DEEP | 2/£1 |

DIODES AND RECTIFIERS

| | |
|-----------------------------------|------------|
| A115M 3A 600V FAST RECOVERY DIODE | 4/£1 |
| 1N5407 3A 1000V | 8/£1 |
| 1N4148 | 100/£1.50 |
| 1N4004 SD4 1A 300V | 100/£3 |
| 1N5401 3A 100V | 10/£1 |
| 1N5819RL 20K Ex stock | 1000 + 10p |
| BA158 1A 400V fast recovery | 100/£3 |
| BY254 800V 3A | 8/£1 |
| BY255 1300V 3A | 6/£1 |
| 6A 100V SIMILAR MR751 | 4/£1 |
| 1A 600V BRIDGE RECTIFIER | 4/£1 |
| 4A 100V BRIDGE | 3/£1 |
| 6A 100V BRIDGE | 2/£1 |
| 10A 200V BRIDGE | £1.50 |
| 25A 200V BRIDGE £2 | 10/£18 |
| 25A 400V BRIDGE £2.50 | 10/£22 |
| BY297 | 10/£1 |
| KBPC304 BRIDGE REC 3A 400V | 4/£1 |

SCRs

| | |
|--------------------------|-------|
| PULSE TRANSFORMERS 1.1+1 | £1.25 |
| MEU21 PROG UNIJUNCTION | 3/£1 |

TRIACS

| | |
|-------------------------------------|------------------|
| NEC TRIAC ACO8F 8A 600V TO220 | 5/£2 100/£30 |
| TXAL225 8A 500V 5mA GATE | 2/£1 100/£35 |
| BTA 08-400 ISO TAB 400V 5mA GATE | 90p |
| TRAL22300 30A 400V ISOLATED STUD | £5 ea |
| TRIAK 1A 800V TLC381T 16K AVAILABLE | 5 FOR £1 £15/100 |

DIACS 4/£1

PHOTO DEVICES

| | |
|---|---------|
| HI BRIGHTNESS LEDS CQX24 RED | 5/£1 |
| SLOTTED OPTO-SWITCH OPCOA OPB815 | £1.30 |
| 2N5777 | 50p |
| TIL81 PHOTO TRANSISTOR | £1 |
| TIL38 INFRA RED LED | 5/£1 |
| 4N25, OP12252 OPTO ISOLATOR | 6/£2 |
| PHOTO DIODE 50P | 50p |
| MEL12 (PHOTO DARLINGTON BASE n/c) | 50p |
| LEDs RED 3 or 5mm 12/£1 | 100/£5 |
| LEDs GREEN OR YELLOW 10/£1 | 100/£5 |
| FLASHING RED LED 5mm 50p | 100/£40 |
| HIGH SPEED MEDIUM AREA PHOTODIODE RS651-995 | £10 ea |
| OPTK OP8745 REFLECTIVE OPTO SENSOR | £1.50 |
| RED LED - CHROME BEZEL | 3/£1 |
| OP11108 HI VOLTAGE OPTO ISOLATOR | £1 |
| MOC 3020 OPTO COUPLED TRIAC | 2/£1 |

STC NTC BEAD THERMISTORS

| | |
|--|-------|
| G22 220R, G13 1K, G23 2K, G24 20K, G54 50K, G25 200K, RES 20°C | |
| DIRECTLY HEATED TYPE | £1 ea |
| FS22BW NTC BEAD INSIDE END OF 1 inch GLASS PROBE RES | |
| 20°C 200R | £1 ea |
| A13 DIRECTLY HEATED BEAD THERMISTOR 1k res. ideal for audio Wien Bridge Oscillator | £2 ea |

CERMET MULTI TURN PRESETS 3/4 inch

| | |
|--|--------|
| 10R 20R 100R 200R 250R 500R 2K 2K2 2K5 5K 10K 47K 50K 100K | |
| 200K 500K 2M | 50p ea |

IC SOCKETS

| | |
|-----------------------------------|-------------|
| 14/16/18/20/24/28/40 PIN DIL SKTS | £1 per TUBE |
| 8-WAY DIP SKTS | £2 per TUBE |
| 32-WAY TURNED PIN SKTS | 3 for £1 |
| SIMM SOCKET FOR 2 x 30-WAY SIMMS | £1 |

POLYESTER/POLYCARB CAPS

| | |
|---|-----------------|
| 330nF 10% 250V AC X2 RATED PHILIPS TYPE 330 | £20/100 |
| 100n, 220n 63V 5mm | 20/£1 100/£3.50 |
| 100n/15v/22n/33n/47n/66n 10mm rad. | 100/£3 |
| 100n 250V radial 10mm | 100/£3 |
| 100n 600V Sprague axial | 5 for £1 |
| 2µ 2 160V rad 220m, 2µ 2 100V rad 15mm | 100/£10 |
| 10n/33n/47n 250V AC x rated 15mm | 10/£1 |
| 1µ 600V MIXED DIELECTRIC | 50p ea |
| 1µ 100V rad 15mm, 1µ 0.22mm rad | 100/£6 |
| 0.22µ 250V AC X2 RATING | 4/£1 |
| 0.22µ 900V | 4/£1 |

RF BITS

| | |
|---|-------------------|
| SAW FILTERS SW662/SW661 PLESSEY SIGNAL TECHNOLOGY | |
| 379.5 MHZ | £1.50 ea |
| FX3286 FERRITE RING ID 5mm OD 10mm | 10 for £1 |
| ASTEC UM1233 UHF VIDEO MODULATORS (NO SOUND) 1250 | |
| STOCK | £1.50 |
| MARCONI MICROWAVE DIODES TYPES DC2929, DC2962 | |
| DC4229F1/F2 | £1 ea |
| XTAL FILTERS 21M4 55M0 | £2 ea |
| ALL TRIMMERS | 3 for 50p |
| VIOLET | 5-105pF |
| RED 10-110pF GREY 5-25pF SMALL MULLARD | |
| 2 to 22pF | 3 for 50p £10/100 |
| TRANSISTORS 2N4427, 2N3866 | 80p ea |
| CERAMIC FILTERS 4M5/6M/9M/10M7 | 60p ea |
| FEED THRU CERAMIC CAPS 1000pF | 10/£1 |
| SL610 | £5 |
| 6 VOLT TELEDYNE RELAYS 2 POLE CHANGEOVER | £2 |
| (BFY51 TRANSISTOR CAN STYLE) | |
| 2N2222 METAL | 5/£1 |
| P2N2222A PLASTIC | 10/£1 |
| 2N2369 | 5/£1 |
| 74N16 TACS CAR PHONE O/P MODULE | |
| EQUIV MHW806A-3 RF IN 40mW O/P6 -8w 840-910MHz | £3 ea |

MONOLITHIC CERAMIC CAPACITORS

| | |
|----------------------------------|------------------|
| 10n 50V 2.5mm | 100/£4.50 |
| 100n 50V 2.5mm or 5mm | 100/£6 |
| 100n ax short leads | 100/£3 |
| 100n ax long leads | 100/£5 |
| 100n 50V di package 0.3 inch rad | 100/£8 |
| 1µF 50V 5mm | 8 for £1 £10/100 |

QUARTZ HALOGEN LAMPS

| | |
|---------------------------|----------------------|
| 12V 50watt LAMP TYPE M312 | £1 ea HOLDERS 60p ea |
| 6V 50watt | £1 |

KEYTRONICS
TEL. 01279-505543
FAX. 01279-757656
 P O BOX 634
BISHOPS STORTFORD

Please quote "Electronics World" when seeking further information

ACTIVE

A-to-D and D-to-A converters

Low-power a-to-ds. Fully operational on a 2.7V supply, Philips' *TDA8766* high-speed a-to-d converter offers 10-bit resolution at 20Msample/s, the *TDA8790* giving 8-bit operation at 40Msample/s. These devices dissipate 53mW and 33mW respectively and both have a standby mode at 4mW. Differential non-linearity (step-to-step variation) is $\pm 0.25\text{lsb}$ and s:n ratio 47dB. Gothic Crellon Ltd. Tel., 01734 788878; fax, 01734 776095.

Dual dac. Maxlm's *MAX549* dual, serial 8-bit, voltage-output digital-to-analogue converter uses one 2.5-5.5V supply, taking about 150 μA or under 1 μA when shut down. Its interface operates at up to 10MHz and is compatible with 3-wire SPI, QSPI and Microwire standards. An input shift register is of 16 bits: eight for data and the rest for selection and control. There is an internal power-on reset to zero all registers. Maxim Integrated Products UK Ltd. Tel., 01734 303388; fax, 01734 305511.

Close-tolerance lasers. NEL's *DFB* lasers are for use in the safe detection of toxic and flammable gases. For this purpose, the emitted wavelengths must be accurate to within $\pm 1\text{nm}$, and these are. BFI IBEXSA Electronics Ltd. Tel., 01622 882467; fax, 01622 882469.



Linear integrated circuits

Isolation amplifier. An Isolation amplifier from Analog Devices, the *AD215* features 1.5kV rms isolation voltage, 120kHz bandwidth and -80dB thd. There is an uncommitted op-amp for input buffering or amplification, which drives low-impedances and has offset trim. The 115V dc power supply is on-chip and can provide 110mA for various front ends or transducers. Analog Devices Ltd. Tel., 01932 266000; fax, 01932 247401.

Memory chips

Folding rams. Framms are foldable, rigid-assembly memory modules, which means that you can fold them in two to maximise memory density or, to put it another way, to cram more in. *ED14G3232F* and *ED14G3632F* are 32Mb-by-32 and 32Mb-by-36 types respectively, both drams meeting the 72-pin simm standard. They are direct replacements for existing modules. EDI (UK). Tel., 01276 472637; fax, 01276 473748.

Microprocessors and controllers

New Z8 microcontroller. The *Z8* family is not yet for the chop, for Zilog has introduced new members, the *Z86C02/E02/L02*, which are 8-bit devices having 512byte of rom and 61byte of ram. Operating frequency is 8MHz and the supply is 3-5.5V for the *C02*, 4.5-5.5V for the *E02* and 1-3.9V for the *L* version. There are 14 i/o lines and five vectored prioritised interrupts from five different sources, 14 digital inputs at cmos level and a fast Instruction pointer. Options include a software-enabled permanent watchdog timer and an



Television components

Catv amplifiers. For cable television, Motorola has two hybrid amplifiers for 750MHz, the *MHW7272/7292*, working from 24V and giving power gains of 27dB and 29dB, broadband noise figure of 6.5dB and good stability. Motorola. Fax, 01354 688248.

oscillator taking *RC* timing, a crystal or ceramic resonator, *LC* tuning or external drive. Gothic Crellon Ltd. Tel., 01734 788878; fax, 01734 776095.

PC/104 expansion. Industrial expansion modules from Arcom for machinery and automation applications provide combinations of digital and serial i/o and have either built-in signal conditioning or an interface to the standard Signal-Conditioning System. The *AIM104* range is used with Arcom's *PC/104* processor boards or any compatible host. There are four digital functions with combinations of 16 opto-isolated inputs and outputs or relay outputs, a 32-channel bit-programmable i/o and a model having four programmable comms channels. All come with a free driver library with its C source code. Arcom Control Systems Ltd. Tel., 01223 411200; fax, 01223 410457.

Communications controllers. Mitsubishi's *M37733/4/5* are 16-bit microcontrollers meant for DECT and portable communications and featuring direct output external bus signalling and a 32kHz dual clock. These devices are based on the *7700* series core and have a cpu and bus interface. The *37734* runs at 25MHz to give 160ns cycle time, incorporates 103 basic instructions and has

60Kbyte of rom and 1048byte of ram. Power supply is 2.7-5.5V. *M37733/5* are compatible and also have three serial i/o and a 10-bit a-to-d converter. Gothic Crellon Ltd. Tel., 01734 788878; fax, 01734 776095.

Micro with CAN module. An 8-bit microcontroller in Siemens' *C500* family, the new *C515C* is 80C515A-compatible and also has an SPI interface and an on-chip version 2.0B controller area network module, which will run the extended CAN protocol with 29-bit identifiers. Maximum clock rate of the *C515C* is 10MHz and instruction cycle time 600ns; it has 64Kbyte of rom, 2.5Kbyte of ram, three 16-bit counters, a 4-channel capture-and-compare unit for pwm generation and full duplex serial interface. Emi/rfi performance is better than in earlier *C500* family members. Siemens plc. Tel., 01344 396313; fax, 01344 396721.

8-bit flash PICs. Microchip has a new family of 8-bit *PIC* microcontrollers which have flash program memory and eeprom data memory. *PIC16F84/83* are the first and provide 1024 by 14 and 512 by 14 program memory respectively, with 64byte of eeprom. Both use 35 single-word, 400ns instructions, work from a 2-6V rail and take a 10MHz clock. There are also 13 i/o pins with individual direction control, an 8-bit timer/counter with a pre-scaler, 15 hardware registers, an 8-level-deep stack and led drive. All *PICs* have the support of a development system and other development tools. Arizona Microchip Technology Ltd. Tel., 01628 851077; fax, 01628 850259.

Mixed-signal ICs

Deserialiser. Maxim has the *MAX3680*, a bipolar chip which contains input and output buffers, a shift register and a parallel output

Please quote "Electronics World" when seeking further information

register. Its function in life is to convert a 622Mb/s, serial, 8-bit-wide input to 77Mb/s parallel output. Power needed is 265mW from 3.3V, and there is a tll-sync. input for data realignment and framing as part of the interface to the real world. Maxim Integrated Products UK Ltd. Tel., 01734 303388; fax, 01734 305511.

Optical devices

Quad optoisolators. ISQ204 optoisolators by Isocom consist of four low-power devices in the one package, each offering isolation resistance of $5 \times 10^6 \Omega$ and peak differential voltage between input and output of 7.5kV. Drive current needed is 0.5mA for full output, at which level current transfer ratio is 50%, rising to 100% at 1mA. Output saturation voltage is 0.4V. Isocom Components Ltd. Tel., 01429 863609; fax, 01429 863581

PASSIVE

Passive components

High-value resistors. Philips' VR37 and VR68 series of high-value, high-voltage metal-glaze resistors now have UL 1676 approval; they now meet all relevant standards, including VDE 0860 and BS 415. Temperature

Power meter. Covering from 10MHz to 26GHz, the Krytar 9000A low-cost power meter digitally displays power between -30dBm and 20dBm, three detectors are designed for broad coverage laboratory and limited coverage field work and there is a type N detector for portable, battery-powered applications. Tony Chapman Electronics Ltd. Tel., 01992 578231; fax, 01992 576139.



coefficients are under 200ppm. Values subject to the approval are 510k Ω -11M Ω , the full range being 100k Ω -220M Ω over the two ranges. Philips Components. Tel., 00 31 40 722790; fax, 00 31 40 724547.

Data line chokes. Surface-mounted, four-element chokes for the protection of data on lines in noisy environments are introduced by Siemens, giving up to 90% saving in space over leaded types. These chokes are primarily for the So basic access and S²m multiplex interface of an ISDN system, but will find application in other areas as well, such as CAN buses in vehicles. Inductances in the range vary from 4 by 470 μ H to 4 by 4.7mH. A variety of characteristics is available for the different applications. Siemens plc. Tel., 01344 396313; fax, 01344 396721.

Audio products

Single-chip surround-sound codec. The first single-chip surround-sound codec to support Dolby Digital Surround (AC-3) and Dolby Pro Logic is available from Crystal Semiconductor. CS4226 contains 95dB stereo a-to-d converters, six d-to-a converters, each with its volume control (which only varies volume at zero-crossings to minimise clicks) a mono a-to-d converter and a Sony/Philips digital interface format receiver, the chip replacing up to nine earlier ics. The S/PDIF receiver supports stereo pcm data and compressed 5.1 channel AC-3 and MPEG audio. Crystal Semiconductor Corporation. Tel., (USA) 001 512 442 7555; fax, 001 512 445 7581.

Connectors and cabling

Microwave connectors. Transradio has a range of coaxial terminations for commercial microwave equipment in SMA and N forms. Both types cover 0-3GHz, have resistance and impedance of 50 Ω \pm 5%, are rated at 1W and exhibit a voltage standing wave ratio of between 1.08 and 1.2



over the frequency range. The type N has a peak power rating of 500W for 1 μ s and the smaller SMA 100W for 1 μ s. Transradio Ltd. Tel., 0181-997 8880; fax, 0181-997 0116.

Cabling wall sockets. HideOut multimedia wall outlets by AMP are a convenient method of hiding and protecting connections to mixed-media cabling in networks and telephone systems. The face plate is flat and almost flush with the wall and the cables enter the bottom edge, so being protected from furniture. The sockets use exiting AMO inserts for ST and SC fibre connections and Cat. 3 and 5 unshielded and shielded twisted-pair cables. They take four copper and two fibre cables or four fibre connections. AMP. Tel., 0181-9542356; fax, 0181-954 7467.

Displays

High-contrast lcd. Using a black mask, Densitron has increased the contrast of transmissive lcds to 100:1 in displays with bright led or fluorescent backlighting. The first available provides a total of 20 digits and 12 graphics symbols for use in consumer equipment, displays with red and green backlighting, allowing viewing in all lighting conditions from a distance of 5m. Results are similar to those from a vacuum fluorescent display, but with a lifetime of 50,000 hours. Densitron Perdix. Tel., 01959 700100; fax, 01959 700300.

13-in colour lcd. NEC's NL128102AC20-07 13in colour lcd is meant principally for cad and desktop workstations, providing a high-brightness display to a resolution of 1280 by 1024. It is an active-matrix type working from rgb input, with built-in backlight and inverter and giving a good viewing angle. Vertical screen expansion (multiscan) allows images of different resolutions to fill the display area. Sunrise Electronics Ltd. Tel., 01908 263999; fax, 01908 263003.

Filters

If filter for DECT telephones. An if surface-wave filter from Siemens takes up 30% less surface area than the QCC10 case; the B4539 measures 9.1 by 4.8 by 1.8mm.

Inter-board connectors.

Siemens' surface-mounted board-to-board connectors use no pins or sockets but, instead, spring-loaded contacts on one board that mate with contact pads etched and plated on the other. The result is no need for through-board holes and a space between boards of between 2.5 and 3.2mm. Connectors come in 6-way and 30-way form and provide a 20m Ω contact resistance and 0.5A current-carrying capacity. Siemens plc. Tel., 01344 396313; fax, 01344 396721.

Insertion loss is about 8dB and group delay 250ns; adjacent-channel rejection 32dB, 52dB and 54dB for first, second and third. Although designed for use in the Siemens PMB 2420 DECT chip set, the output is 150 Ω , making the device suitable - without an impedance network - for the National Semiconductor set. Siemens plc. Tel., 01344 396313; fax, 01344 396721.

Hardware

Tailored boxes. Bafbox can now deliver small numbers of custom-designed plastic enclosures by mail order at volume prices. The company has developed cad/cam software to allow customers to specify the size and shape of box and where holes should be, so eliminating expensive machining of standard cases. If the holes are then found to need moving, it can be done at no "significant" cost difference. Rfi/emi shielding can be supplied, as can screen printing and various paint finishes. Prototypes in a few days, production in five weeks. Bafbox Ltd. Tel., 01280 705777; fax, 01280 706320.

Test and measurement

Handheld multimeters. Tektronix has a series of multimeters that are small and tough and have a 40,000-count display. The DMM800 meters possess a dual display for taking two simultaneous readings, with an analogue type of indication, and measure true rms values in addition to the full range of voltage, current, resistance, diode test, frequency and capacitance. Type DMM870 also

Please quote "Electronics World" when seeking further information

offers a 1ms peak hold, dB and dBm readings and has a backlit display. Thurlby Thandar Instruments Ltd. Tel., 01480 412451; fax, 01480 450409.

High-voltage oscilloscope amp.

Gould's *DP9010* is a differential amplifier for floating, high-voltage measurement on a grounded oscilloscope. Its bandwidth is 0-80MHz and the differential inputs are balanced to 1M Ω ; standard probes are suitable. Input voltage range with direct input is $\pm 30V$ and, with suitable probes, extends to 20kV; cmr with direct input is 70dB at 1MHz. Gould Instrument Systems Ltd. Tel., 0181-500 1000; fax, 0181-501 0116.

Interfaces

Keypad, driver/micro interface.

Rohm's *BU9768K* interface controller ic contains all keypad and lcd driver functions in the one device, operating on a three-wire bus back to the microprocessor, which is relieved of much of the routine and can therefore be of lower performance. It handles keypad scanning without attention from the processor, which downloads data to the *BU9768K* through a serial link, the interface controller doing the

rest. The *BU9768K* draws 200 μA active, 30 μA on standby. Flint Distribution. Tel., 01530 510333; fax, 01530 510275.

Literature

Programmable analogue. Imp, of San Jose, offers the *Electrically programmable Analog Circuit Design Handbook*, which describes these epac devices that are the analogue equivalent of field-programmable gate array. It also provides application notes and development tool details, with a collection of seminar reprints. Imp also offers Animal Magic, which is Windows-based design software for analogue and mixed-signal epacs. Tel., 001 408 434 1467; fax, 001 408 434 0335. E-mail <http://www.impweb.com>

Drums on cd. A cd-rom from NEC provides all details on all NEC drums and srms, including 64Mb devices. There is also information on applications, reliability and quality. The cd runs under Windows, is menu-driven and has copy-and-paste facilities, with text search and printing to speed things up. NEC Electronics (UK) Ltd. Tel., 01908 691133; fax, 01908 670290.

Harris. Harris Semiconductor offers a new brochure, *Semiconductor Solutions for Multimedia, Video and Imaging*, the solutions being op-amps and buffers, data converters, standards converters and various other video ics for these areas. There is also a section on dsp's. Harris Semiconductor UK. Tel., 01276 686886; fax, 01276 682323.

Thermal analysis on the Web.

Flomerics has a World Wide Web site on <http://www.flomerics.com>, on which the company describes its Flotherm thermal analysis software, together with case studies from some of the bigger companies who have used it. Also described is *DELPHI* which is a collection of thermal models for electronic components and hardware to assist engineers in system design. The site contains *Electronic Cooling*, a magazine published by Flomerics. Flomerics Ltd. Tel., 0181-941 8810; fax, 0181-941 8730.

Materials

Anti-static plastic compound. TBA ECP is shortly to announce some new static-dissipating plastic compound that can be moulded and made in many colours, as opposed to earlier types which have also been in any colour as long as it was black. Some of them were coloured, but only because they were laced with additives which did not last. This new material is injection moulded ABS alloy with a resistivity of around $10^9\Omega$ /square, with the appropriate



static decay characteristic. The company offers a moulding service. TBA Industrial Products Ltd. Tel., 01706 47718; fax, 01706 46170.

Cleaning fluids. Since the more ferocious solvents formerly used to clean electronic assemblies are now banned under the Montreal Protocol, new ones are now appearing. Loctite, for example, has *Loctite 7070* and *Loctite 7063*, both alternatives to 1,1,1-Trichloroethane. *7070* is for open tanks and brush use, drying in around two minutes and pervading the air with a scent of lemons, while *7063* dries in 15 seconds and is very good at cutting through oil; it has to be used in closed tanks and doesn't smell of lemons, so far as we know. Both types come in air-rechargeable aerosols, pump sprays, cans and drums. Loctite UK Ltd. Tel., 01707 821000; fax, 01707 821200.

Heat-shrink tubing. Methode offers *ShrinkMate* (why do so many people insert a capital half-way through a name?), which is heat-shrink tubing based on polymer thick-film silver ink technology to give efficient connections and eliminate emc problems on signal and power lines. The material is easily applied using a heat gun or oven and is meant for use on spliced cables or connectors,

Keylock switches. EAO offers a new range of multiposition keylock switches to the *04 Series* of push-buttons. Bezels are round or square and the switches come in a variety of forms from three-position, 60° throw, to 12-position, 30° throw, with up to 16 contacts. EAO-Highland Electronics Ltd. Tel., 01444 236000; fax, 01444 236641.

Digital wattmeter. Yokogawa's *WT130* is a three-phase wattmeter with three input modules for independent measurement on each phase. Bandwidth is 0-50kHz to allow measurement on pwm variable-speed drives. High-speed measurement is followed by calculation of effective power, apparent power, reactive power, power factor and phase individually and for the three phase system. The instrument carries out 32-bit FFTs using a rectangular window and analyses harmonic content of voltage, current and power waveforms by amplitude and by phase to the fundamental. The *WT130* has an RS 232 interface. Martron Instruments Ltd. Tel., 01494 459200; fax, 01494 535002.

Vibration sensors. Used with a zener barrier, the *MTN/1101* vibration sensors by Monitran are certified by BASEEFA as intrinsically safe for use in all hazardous areas and gas groups, being rated to EEx ia IIC T6. These piezoelectric devices with internal electronics give an ac output of 100mV/g and can be processed in a DIN-rail-mounted unit to give a 4-20mA current-loop signal. They are made in stainless steel and sealed, a choice of attachments for mounting being available. Monitran Ltd. Tel., 01494 816569; fax, 01494 812256.



Please quote "Electronics World" when seeking further information

where it gives a circumferential seal round the cable shielding and the base of nearly every connector type, also obviating the need to solder braided cable shielding. Shielding rating of a connector so treated is 40-82dB over the 30-1000MHz range. Methode Electronics Europe Ltd. Tel., 01389 732123; fax, 01389 732777.

Printers and controllers

Fast thermal printer. Star Micronics *TMP-200* is a high-speed device for oems; it provides easy access to the head with a view to simple maintenance. It prints at eight dots/mm, at up to 1.5in/s and there are options of auto cutter and interface boards. Paper feed is from the rear or bottom. Roxburgh Electronics Ltd. Tel., 01724 281770; fax, 01724 281650.

Production equipment

Ultrasonic cleaning. Since some of the cleaning agents previously in use

are now prohibited, new types of ultrasonic cleaners are needed to give the same results with new, flammable solvents. Caresonic has new equipment for this purpose which enable these vicious-sounding solvents to be used harmlessly by providing interlocking lids, purging and venting, and automatic timing. Solvent is contained under the tank, is pumped in for use and then pumped out again before the lid can be opened. Heat is not needed. Care Ultrasonics Ltd. Tel., 0151-356 4013; fax, 0151-356 4037.

Vacuum cleaner. Among life's minor irritations are items of equipment that have been computer-designed to be virtually impossible to clean, such as keyboards and cameras. Jessop, in an effort to ease the stress, have introduced the *Mini Vacuum* battery-powered cleaner kit, which also blows, possibly through various nozzles and brushes. It has a dust bag and an array of cloths, sprays, tissues and cotton buds to further the process. It cost £9.99 from Jessop photographic shops. Jessop Group Ltd. Tel., 0116-232 0033; fax, 0116-232 0066.

Power supplies

60W dc-to-dc. Emi/rfi-shielded on all sides of an aluminium case, Amplicon's *RW Series* of 50-60W dc-to-dc converters are current-mode types giving an efficiency of 83% from 10-72V input. There are 48V models for telecomms use with case to positive, 24V ones for process control and 12V versions for use in vehicles. Single, dual and triple versions combine 5V, ±12V and ±15V in various ways and the units have a remote on/off control. They switch at 300kHz, are isolated to 500V dc and are short-circuit protected, with autostart. Temperature coefficient is ±0.02%/°C, stability ±0.05%, ripple

and noise 1% pk-pk and transient response 500µs. Amplicon Liveline Ltd. Tel., 0800 525 335 (free); fax, 01273 570215.

Integrated power supply. Working without external components, National's *LM2825* is said to be six times more reliable than a psu module, provides a power density of 35W/in³ and meets Class B of CISPR 22 for radiated emissions. It handles inputs up to 40V and gives output of 1A from 3.3V and 5V at 80% efficiency and is protected against overcurrent, shorts and high temperatures. Avnet Access. Tel., 01462 480888; fax, 10262 488567.

Low-voltage Schottkys. New Schottky diodes from Philips are for use in 3V and 3.3V switch-mode power supplies and have a 0.33V forward drop at rated forward current. Low capacitance and no stored charge in nickel silicide junctions make them suitable for high-frequency use. *PBYR1025CT* is a single diode rated at 20A and *PBYR1525CT/2025CT* dual types rated at 15A and 20A respectively, all withstanding 25V reverse. Philips Semiconductor (Eindhoven). Tel., 00 31 40 2722091; fax, 00 31 40 2724825.

New Klippon range. Weidmuller Klippon has a new range of psus, including switched-mode types and dc-to-dc converters meeting a large number of standards and CE marked. All the s-m types have short-circuit, thermal, overvoltage and inrush protection, universal ac and dc inputs and variety of housings, including a 1A unit in an EG case, claimed to be the smallest available. Weidmuller (Klippon Products) Ltd. Tel., 01795 580999; fax, 01732 844444.

Minute 40W supply. XP's *NLP40* is claimed to be the smallest emc-compliant 40W supply available, measuring 4.25 by 2.5 by 1.25in and meeting low-voltage Directives and EN55022 for conducted noise. The company ascribes its power density of 3W/in³ to a new type of switch-mode operation and a fixed switching frequency, together with a patented integrated boost flyback topology. Input is universal and nine models cover outputs of 5V single to 5V with ±15V triple. XP plc. Tel., 01734 845515; fax, 01734 843423.

Radio communications products

Broadband amplifiers. Advanced Control Components Inc. announces a range of ultra-broad-band and octave band amplifiers for mobile communications between 10MHz and 4000MHz. *ACAM 8928* and *7932* both give 1W and are meant for use in level test or integration into test systems. Frequency ranges are

10-2500MHz and 100-4000MHz, both including the cellular, SMR and PCN/PCS bands. Gain of the *7928* is 36dB±0.75dB, while the compact *7932* has a 24dB±1dB gain. There are also three 10-octave amplifiers in rack-mount form covering 100-500MHz, 500-1000MHz and 1000-2000MHz. Anglia Microwaves Ltd. Tel., 01277 630000; fax, 01277 631111.

Protection devices

Shielded windows. Emc shielding for display panels and other transparent areas is available from TBA ECP. Conductive coatings based on indium tin oxide are applied to glass or plastic such as polycarbonate and acrylic and give conductivity down to 10Ω/square and up to 90.5% transparency. Tooling exists to coat complex shapes and coatings can extend up to 350 by 320mm. The company also makes windows using fine wire meshes or metal oxide interlayers in laminated glass or plastic. TBA Industrial Products Ltd. Tel., 01706 47718; fax, 01706 46170.


Switches and relays

Miniature relay. A miniature, hermetically sealed relay from Finder, the Series 30, meets BT47 and BT51 specifications and is suitable for most telecomms applications. It is rated at 250V ac for resistive loads and comes with 20mW (BT47) or 40mW coil voltages of between 5V and 48V dc. Two changeover contacts are silver/gold-plated and power handling is 125VA; maximum switching frequency is 600cycles/h. AX Electronic Component Distribution. Tel., 01403 240055; fax, 01403 255657.

Reed relay. CP Clare's *MVS Series* of reed relays use the company's *MH4* bounce-free, mercury-wetted reed switch and have a life of up to 10¹⁰ operations at low to intermediate levels. Contact resistance is stable at ±5mΩ from the 100mΩ rated figure, maximum switching voltage 1kV and switching current 2A (carry current 3A). Several of the devices in the range are fitted with diodes as an option and one has an electrostatic shield. Clare UK Sales. Tel., 01823 352541; fax, 01823 352797.

Semiconductor relays. Matsushita would like to point out that its *PhotoMos* relays do not suffer from most of the disadvantages found in electromechanical ones or even thyristor or transistor types, while providing true relay switching. You can get versions to switch very low currents or up to more than 4A, with multiple contact arrangements of the n.o. or n.c. type. Matsushita Automation Controls Ltd. Tel., 01908 231555; fax, 01908 231599.

Man-machine interface design. National Instruments announces *BridgeVIEW*, which is a graphics package for process and manufacturing application. Using techniques taken from the company's *LabVIEW*, it provides real-time process monitoring, trending, on-line configuration and programmable logic controller connectivity. It has a gui and the G development language for data acquisition and analysis, man-machine interfacing and supervisory application. National Instruments UK. Tel., 01635 572400; fax, 01635 523154.

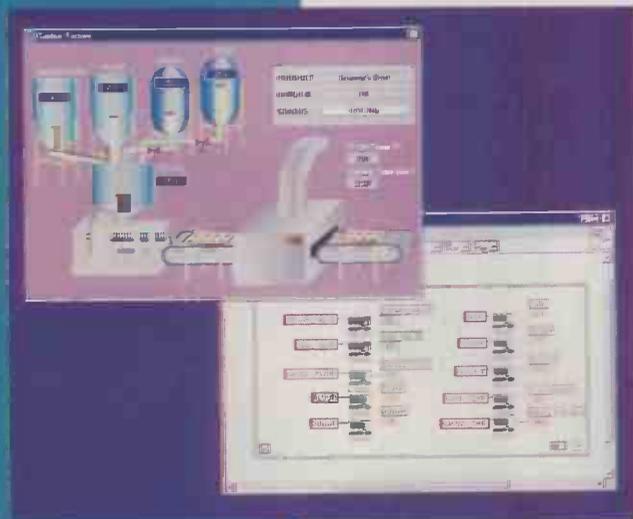

W95 keyboard. A new version of Cherry's keyboard, the *Model 3000*, works with Windows 95 and gives a better choice of "feel". It has 104 or 105 keys, two or three of them for Windows use, and the F and J keys are dished for touch typists, the 5 key on the numeric pad having a dimple for the same reason. A dial switch copes with PC, AT, XT or PS/2 modes of operation. The keyboard meets all relevant standards. Cherry Electrical Products Ltd. Tel., 01582 763100; fax, 01582 768883.

Bipolar Hall switch. Allegro offers the *3134* low-hysteresis, bipolar Hall-effect switch for automotive and industrial use. It has a novel Schmitt trigger built in which compensates for temperature changes to maintain trigger and release points. Further compensation is provided by magnetic switch points that become more sensitive with temperature. Also on-chip are a voltage regulator, a quadratic Hall generator, temperature compensation, an amplifier and a buffered open-collector output stage. Allegro Microsystems Inc. Tel., 01932 253355; fax, 01932 246622.

High-current relay. Matsushita's *LK* relay is designed to handle inrush currents up to 100A, with a barrier between coil and contacts to improve creepage, to give a 6mm clearance and to provide noise immunity. It measures 24 by 25 by 11mm, is rated at 5A, 277V ac and will withstand 10kV surges. Matsushita Automation Controls Ltd. Tel., 01908 231555; fax, 01908 231599.

Snap switches. Cherry has two new switches in its *Snap Switch* range. The *D48* high-power microswitch operates at up to 150°C, has a current rating of 21A at 240V, long life and silver contacts, while the *D3* type has a contact gap of over 3mm to take high inrush currents; this one switches continuous loads of 16A at 380V, with short-period overloads. Cherry Electrical Products Ltd. Tel., 01582 763100; fax, 01582 768883.

Sealed switches. C&K offers a range of sealed toggle, rocker and push-button switches, which are available with both through-hole and surface-mountings to withstand flow-solder, vapour phase and infrared reflow operations. All have ultrasonically sealed bodies, O-ring bushes and epoxy sealed terminals. Roxburgh Electronics Ltd. Tel., 01724 281770; fax, 01724 281650.

Transducers and sensors

Optical encoder. *HS Series* optical shaft encoders by Control Transducers are of low cost and are meant for use on machinery for feedback and positioning. The range

covers resolutions from 96 to 2048 lines per revolution in 16 models. The encoders measure from 1in to 2in diameter with mounting plates and two ball bearings handle speeds up to 10,000rev/min. Components such as cable, line drivers, power supplies are available. Control Transducers. Tel., 01234 217704; fax, 01234 217083.

Audible alarms. *Kingstate* piezoceramic alarms operate from dc and provide the requisite racket while measuring only 13.8mm diameter, and even more racket from 42mm types. They come with flying leads or pins to standard formats, most of them being sealed for soldering and cleaning. Roxburgh Electronics Ltd. Tel., 01724 281770; fax, 01724 281650.

More audible alarms. Piezoceramic alarms from Fujl also make a very loud noise – 108dB at 1kHz – from 5V rms and are only 2mm thick and use less power while doing it than many others. Connection is by flying lead, through-hole or surface mounting. Distributed Micro Technology Ltd. Tel., 01276 33391; fax, 01276 36703.

Current measurement. JJ Systems announces a range of flexible transducers for contactless current measurement, which take the form of air-cored, toroidal winding, the Rogowski coil, which is placed around a conductor carrying from 1A to 1MA to give an accurate waveform reproduction for oscilloscope or dvm; the coil is completed by plug and socket. Frequency range is 0.1Hz-1MHz with an accuracy within 1%. Sensitivity is insensitive to the position of the coil. JJ Systems Ltd. Tel., 01256 895111; fax, 01256 896100.

COMPUTER

Development and evaluation

68HC11 development. MD Electronics introduces the *MC11*, which is a development or training aid based on Motorola's *69HC11* microcontroller. The kit can also be used as a low-cost controller. It is linked to a pc by way of a standard serial port, a monitor in read-only memory allowing programs to be developed and debugged or, for longer programs, developed on the host pc and downloaded. The 40-way input/output port is compatible with much equipment used in education. Further connectors allow access to the eight analogue-to-digital channels and permit system expansion. MD Electronics. Tel., 01926 850315.



Software

Maths library. Mathtools announces *Matcom v.2* maths library, a C++ matrix library having more than 300 maths functions, including basic unary and binary operations, indexing, signal processing, linear algebra and 2D and 3D graphics. Matrices are supported. E-mail info@mathtools.com; fax, 001 215 957 1719.

Image analysis. *Image-Pro Plus* from Media Cybernetics, which runs on all Windows variants and Mac 7, provides accurate image processing and analysis of monochrome, grey scale and 24-bit colour images. It has a range of counting, sizing, statistical and image-enhancement tools and is meant to be used in any area where an image can help one to understand a process, to make comparisons or to identify objects. Examples are: measuring areas, perimeters, roundness, population density; display measurements as histograms; calculate line areas; perform FFTs; read files from a camera, disk or cd. And a great deal more. DataCell. Tel., 01628 415415; fax, 01628 415400.

8xC186 C compiler. IAR Systems and Intel introduce a C compiler for the 8xC196 embedded microcontroller. ICC196 v.5.10 is dos-based and includes compiler, assembler, linker and library. The ANSI-compliant compiler supports all current 8xC196 controllers and is future-proof. Malloc and realloc are supported to confer flexibility in controlling processor heap size. Four memory models support code and data from 64Kb to 16Mb and bank switching to 8Mb is available. Efficiency gains from the use of mixed C and assembly language listings, in which each C line is followed by the equivalent assembly code, compiler

errors being reported with line number, syntax and pointer to the error. IAR Systems Ltd. Tel., 0171-924 3334.

Graphing for Mathcad 6.0. The acquisition of the *Axum* graphics and analysis software by Mathcad publishers MathSoft now allows the integration of the two packages to provide drag-and-drop graphs, including 3-D surface mesh, linear and non-linear curve-fitting, automatic error bars and colour-filled contours, in *Mathcad* and any OLE 2-compliant application, to publication quality. Both *Mathcad Plus 6.0* and *Mathcad 6.0* standard edition now come with an *Axum* link and there is a patch disk for existing users. Adept Scientific Micro Systems Ltd. Tel., 01462 480055; fax, 01462 480213.

Designing reliable

In this second article*, Ray Fautley runs through the steps necessary to design a reliable half-wave rectifier psu.

**Ray's first article, in the September issue, ran through design steps for a full-wave bridge rectifier.*

In the conventional half-wave rectifier, alternating voltage is applied to diode *D*, where it is rectified and the output smoothed by the reservoir capacitor *C*. The fundamental frequency of the ripple voltage is the same as the supply frequency, Fig. 1.

The half-wave rectifier is mainly used for low-current supplies. This is because the dc load current flows through the mains transformer secondary winding. If this current is too high, it can produce saturation of the transformer core. This current thus lowers transformer efficiency.

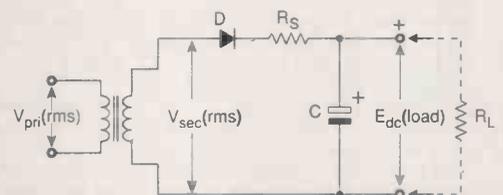


Fig. 1. The conventional half-wave rectifier is simple and useful in that it has a low component count. It is however inefficient, only suitable for low current loads and ripple is 50Hz, not 100Hz as is the case for full-wave rectifiers.

Table 1. Using the percentage ripple voltage to find value X.

| V _r % | R _s /R _L % | | | | | | |
|------------------|----------------------------------|------|------|------|------|------|------|
| | 0.1 | 0.3 | 1.0 | 3.0 | 5.0 | 10 | 30 |
| 0.1 | 1783 | 1748 | 1632 | 1602 | 1573 | 1502 | 1342 |
| 0.2 | 855 | 844 | 807 | 791 | 776 | 739 | 654 |
| 0.3 | 565 | 556 | 525 | 515 | 505 | 481 | 432 |
| 0.4 | 422 | 404 | 392 | 386 | 379 | 364 | 322 |
| 0.5 | 334 | 330 | 315 | 305 | 303 | 288 | 258 |
| 0.6 | 278 | 274 | 261 | 257 | 253 | 243 | 216 |
| 0.7 | 241 | 236 | 221 | 219 | 216 | 211 | 186 |
| 0.8 | 206 | 203 | 193 | 190 | 187 | 180 | 163 |
| 0.9 | 186 | 183 | 171 | 168 | 166 | 160 | 145 |
| 1.0 | 164 | 159 | 155 | 152 | 150 | 144 | 131 |
| 2.0 | 81 | 80 | 76 | 75 | 74 | 72 | 66 |
| 3.0 | 53 | 52 | 50 | 49 | 49 | 47 | 43 |
| 4.0 | 40 | 39 | 37 | 37 | 37 | 36 | 33 |
| 5.0 | 32 | 31 | 30 | 29 | 29 | 28 | 26 |
| 6.0 | 26 | 25 | 25 | 24 | 23 | 23 | 22 |
| 7.0 | 22 | 21 | 21 | 20 | 20 | 20 | 19 |
| 8.0 | 19 | 18 | 18 | 17 | 17 | 17 | 16 |
| 9.0 | 17 | 16 | 16 | 15 | 15 | 15 | 14 |
| 10 | 15 | 15 | 15 | 14 | 14 | 14 | 13 |
| 20 | 7.6 | 7.4 | 7.2 | 7.0 | 6.9 | 6.8 | 6.3 |
| 30 | 5.0 | 4.9 | 4.7 | 4.6 | 4.5 | 4.5 | 4.1 |
| 40 | 3.6 | 3.5 | 3.5 | 3.4 | 3.3 | 3.3 | 3.0 |
| 50 | 2.8 | 2.7 | 2.7 | 2.6 | 2.5 | 2.5 | 2.3 |
| 60 | 2.2 | 2.1 | 2.1 | 2.0 | 2.0 | 2.0 | 1.8 |
| 70 | 1.8 | 1.7 | 1.7 | 1.6 | 1.6 | 1.6 | 1.4 |
| 80 | 1.4 | 1.4 | 1.4 | 1.3 | 1.3 | 1.3 | 1.1 |
| 90 | 1.2 | 1.1 | 1.1 | 1.1 | 1.1 | 1.1 | 0.9 |
| 100 | 1.0 | 1.0 | 0.9 | 0.9 | 0.9 | 0.9 | 0.8 |

Design steps for a half-wave rectifier

- 1) Specify required dc output voltage at full load $E_{dc(load)}$ (V).
- 2) Specify required maximum load current $I_{dc(load)}$ (A)
- 3) Specify maximum ripple acceptable $V_{r(rms)}$ (V)
- 4) Specify the ac mains supply voltage $V_{pri(rms)}$ (V)
- 5) Specify the frequency of the ac mains supply f (Hz)
- 6) Determine the value of the equivalent load resistance R_L :

$R_L = E_{dc} / I_{dc}$
 where E_{dc} is the design value of the dc output voltage. This is the voltage across the load $E_{dc(load)}$ added to the voltage drop across the rectifier diode:

$E_{dc} = E_{dc(load)} + V_{rec}$
 and V_{rec} is the 0.9V drop across the rectifier diode.

So:

$$R_L = \frac{E_{dc(load)} + 0.9}{I_{dc(load)}}$$

- 7) Determine the average current through the diode, I_O . As all the current must flow through the diode:
 $I_O = I_{dc(load)}$
- 8) Determine a value for the source resistance of the supply, R_s . As only low current supplies are being considered the

rectifiers

resistance of the transformer windings will predominate. Thus: $R_s = R_{sec} + R_{pri}/N^2$. If the transformer winding resistances are not known, assume that R_s is about 5% of R_L . Then: $R_s = R_L \times 5/100$.

- 9) Calculate the ratio of R_s to R_L as a percentage:
 $R_s/R_L \times 100\% = 5\%$, as assumed in (8).
- 10) Determine percentage ripple voltage from the specified maximum ripple voltage and the dc output voltage:
 $V_r\% = V_{r(rms)}/E_{dc(load)} \times 100\%$
- 11) From Table 1, determine the value of X required to provide the percentage ripple voltage, $V_r\%$ in (10) above, for $R_s/R_L\%$ calculated in (9). If the figures for $V_r\%$ and $R_s/R_L\%$ are not exactly the same as those found in the table headings, then the required value for X must be interpolated as described in (11) for the bridge-rectifier design procedure (September issue).
- 12) Calculate the value of the reservoir capacitor C , required to provide the ripple voltage $V_{r(rms)}$ from:

$$C = \frac{X}{2\pi f \times R_L} \times 10^6 \mu\text{F}$$

- 13) Find the nearest standard value for the reservoir capacitor C , close to or preferably just above, the value calculated in (12). If the value is different from that in (12), call it C_1 and determine a new value for X (call it X_1) from: $X_1 = 2\pi f R_L C_1$, with C_1 in μF :

$$X_1 = \frac{2\pi f R_L C_1}{10^6}$$

- 14) From Table 2, determine the value of Y for X in (11), or X_1 in (13), and $R_s/R_L\%$ in (9).
- 15) Determine the transformer secondary voltage $V_{sec(rms)}$ required, from the value for Y in (14):

$$V_{sec(rms)} = \frac{E_{dc}}{\sqrt{2} \times Y}$$

Table 2. Using X and R_s/R_L , find the value of Y .

| X | $R_s/R_L\%$ | | | | | | | | | | |
|------|-------------|------|------|------|------|------|------|------|------|------|------|
| | 0.05 | 0.1 | 0.5 | 1.0 | 2 | 4 | 6 | 8 | 10 | 12.5 | 15 |
| 0.1 | 0.31 | 0.31 | 0.31 | 0.31 | 0.31 | 0.31 | 0.30 | 0.30 | 0.29 | 0.28 | 0.27 |
| 0.2 | 0.32 | 0.32 | 0.32 | 0.31 | 0.31 | 0.31 | 0.30 | 0.30 | 0.29 | 0.28 | 0.27 |
| 0.3 | 0.32 | 0.32 | 0.32 | 0.31 | 0.31 | 0.31 | 0.30 | 0.30 | 0.30 | 0.29 | 0.28 |
| 0.4 | 0.32 | 0.32 | 0.32 | 0.32 | 0.32 | 0.32 | 0.31 | 0.31 | 0.30 | 0.30 | 0.29 |
| 0.5 | 0.33 | 0.33 | 0.33 | 0.33 | 0.33 | 0.32 | 0.31 | 0.31 | 0.30 | 0.30 | 0.29 |
| 0.6 | 0.34 | 0.34 | 0.34 | 0.34 | 0.33 | 0.33 | 0.32 | 0.32 | 0.31 | 0.30 | 0.30 |
| 0.7 | 0.35 | 0.35 | 0.35 | 0.34 | 0.34 | 0.34 | 0.33 | 0.33 | 0.32 | 0.31 | 0.31 |
| 0.8 | 0.36 | 0.36 | 0.36 | 0.35 | 0.35 | 0.35 | 0.34 | 0.33 | 0.32 | 0.31 | 0.31 |
| 0.9 | 0.37 | 0.37 | 0.37 | 0.36 | 0.36 | 0.36 | 0.35 | 0.34 | 0.34 | 0.33 | 0.32 |
| 1.0 | 0.38 | 0.38 | 0.38 | 0.37 | 0.37 | 0.37 | 0.37 | 0.36 | 0.35 | 0.34 | 0.33 |
| 1.5 | 0.44 | 0.44 | 0.44 | 0.43 | 0.43 | 0.42 | 0.41 | 0.40 | 0.39 | 0.38 | 0.37 |
| 2.0 | 0.49 | 0.49 | 0.48 | 0.48 | 0.47 | 0.46 | 0.45 | 0.44 | 0.43 | 0.42 | 0.41 |
| 2.5 | 0.54 | 0.54 | 0.53 | 0.53 | 0.52 | 0.50 | 0.49 | 0.48 | 0.47 | 0.46 | 0.44 |
| 3.0 | 0.57 | 0.57 | 0.57 | 0.56 | 0.56 | 0.55 | 0.54 | 0.53 | 0.51 | 0.49 | 0.47 |
| 4.0 | 0.63 | 0.63 | 0.62 | 0.61 | 0.60 | 0.59 | 0.58 | 0.57 | 0.55 | 0.53 | 0.50 |
| 5.0 | 0.68 | 0.68 | 0.67 | 0.66 | 0.65 | 0.63 | 0.62 | 0.59 | 0.57 | 0.55 | 0.52 |
| 6.0 | 0.71 | 0.71 | 0.70 | 0.70 | 0.69 | 0.67 | 0.64 | 0.61 | 0.59 | 0.56 | 0.53 |
| 7.0 | 0.74 | 0.74 | 0.73 | 0.73 | 0.71 | 0.69 | 0.66 | 0.62 | 0.60 | 0.57 | 0.54 |
| 8.0 | 0.77 | 0.77 | 0.76 | 0.75 | 0.75 | 0.70 | 0.67 | 0.63 | 0.60 | 0.57 | 0.54 |
| 9.0 | 0.79 | 0.79 | 0.78 | 0.77 | 0.76 | 0.71 | 0.68 | 0.64 | 0.61 | 0.58 | 0.55 |
| 10 | 0.80 | 0.80 | 0.79 | 0.78 | 0.77 | 0.72 | 0.69 | 0.65 | 0.61 | 0.59 | 0.55 |
| 15 | 0.86 | 0.85 | 0.84 | 0.82 | 0.80 | 0.74 | 0.70 | 0.67 | 0.63 | 0.59 | 0.56 |
| 20 | 0.89 | 0.88 | 0.87 | 0.85 | 0.82 | 0.76 | 0.71 | 0.68 | 0.64 | 0.60 | 0.57 |
| 25 | 0.91 | 0.90 | 0.89 | 0.86 | 0.83 | 0.77 | 0.71 | 0.68 | 0.64 | 0.60 | 0.57 |
| 30 | 0.92 | 0.91 | 0.90 | 0.88 | 0.84 | 0.78 | 0.72 | 0.68 | 0.65 | 0.60 | 0.57 |
| 40 | 0.94 | 0.92 | 0.91 | 0.89 | 0.84 | 0.78 | 0.72 | 0.69 | 0.65 | 0.61 | 0.57 |
| 50 | 0.95 | 0.93 | 0.92 | 0.89 | 0.84 | 0.78 | 0.72 | 0.69 | 0.65 | 0.61 | 0.57 |
| 60 | 0.96 | 0.94 | 0.93 | 0.90 | 0.85 | 0.78 | 0.73 | 0.69 | 0.65 | 0.61 | 0.57 |
| 70 | 0.97 | 0.95 | 0.93 | 0.90 | 0.85 | 0.78 | 0.73 | 0.69 | 0.65 | 0.61 | 0.57 |
| 80 | 0.97 | 0.95 | 0.93 | 0.90 | 0.85 | 0.78 | 0.73 | 0.69 | 0.65 | 0.61 | 0.57 |
| 90 | 0.98 | 0.96 | 0.94 | 0.90 | 0.85 | 0.78 | 0.73 | 0.69 | 0.65 | 0.61 | 0.57 |
| 100 | 0.98 | 0.96 | 0.94 | 0.90 | 0.85 | 0.78 | 0.73 | 0.69 | 0.65 | 0.61 | 0.58 |
| 200 | 0.99 | 0.97 | 0.94 | 0.91 | 0.85 | 0.79 | 0.73 | 0.69 | 0.65 | 0.61 | 0.58 |
| 300 | 0.99 | 0.97 | 0.95 | 0.91 | 0.86 | 0.79 | 0.73 | 0.69 | 0.65 | 0.61 | 0.58 |
| 1000 | 1.00 | 0.98 | 0.95 | 0.91 | 0.86 | 0.79 | 0.73 | 0.69 | 0.65 | 0.61 | 0.58 |

continued over...

where $E_{dc} = E_{dc(load)} + V_{rec}$,

$$= \frac{0.707 \times E_{dc}}{Y}$$

- 16) Determine the peak voltage, or peak

inverse voltage, that the rectifier diode must withstand. For the half-wave rectifier, the peak inverse voltage varies with the degree of load. The worst case occurs when the load is zero or very

Table 2 continued - finding the value of Y.

| X | R _s /R _L % | | | | | | | | | | |
|------|----------------------------------|------|------|------|------|------|------|------|------|------|------|
| | 20 | 25 | 30 | 35 | 40 | 50 | 60 | 70 | 80 | 90 | 100 |
| 0.1 | 0.26 | 0.25 | 0.24 | 0.21 | 0.23 | 0.21 | 0.20 | 0.19 | 0.18 | 0.17 | 0.16 |
| 0.2 | 0.26 | 0.25 | 0.24 | 0.24 | 0.23 | 0.21 | 0.20 | 0.19 | 0.18 | 0.17 | 0.16 |
| 0.3 | 0.27 | 0.26 | 0.25 | 0.24 | 0.23 | 0.21 | 0.20 | 0.19 | 0.18 | 0.17 | 0.16 |
| 0.4 | 0.27 | 0.26 | 0.25 | 0.25 | 0.24 | 0.22 | 0.21 | 0.20 | 0.18 | 0.17 | 0.16 |
| 0.5 | 0.28 | 0.27 | 0.25 | 0.25 | 0.24 | 0.22 | 0.21 | 0.20 | 0.18 | 0.17 | 0.16 |
| 0.6 | 0.29 | 0.27 | 0.26 | 0.26 | 0.25 | 0.23 | 0.22 | 0.21 | 0.19 | 0.18 | 0.17 |
| 0.7 | 0.29 | 0.28 | 0.26 | 0.26 | 0.25 | 0.23 | 0.22 | 0.21 | 0.19 | 0.18 | 0.17 |
| 0.8 | 0.30 | 0.28 | 0.27 | 0.26 | 0.25 | 0.23 | 0.22 | 0.21 | 0.19 | 0.18 | 0.17 |
| 0.9 | 0.31 | 0.29 | 0.28 | 0.27 | 0.26 | 0.24 | 0.22 | 0.21 | 0.19 | 0.18 | 0.17 |
| 1.0 | 0.32 | 0.30 | 0.28 | 0.27 | 0.26 | 0.24 | 0.23 | 0.21 | 0.19 | 0.18 | 0.17 |
| 1.5 | 0.35 | 0.33 | 0.31 | 0.30 | 0.29 | 0.26 | 0.24 | 0.22 | 0.20 | 0.19 | 0.18 |
| 2.0 | 0.38 | 0.36 | 0.34 | 0.32 | 0.31 | 0.28 | 0.25 | 0.24 | 0.22 | 0.20 | 0.19 |
| 2.5 | 0.41 | 0.38 | 0.36 | 0.34 | 0.32 | 0.30 | 0.26 | 0.25 | 0.23 | 0.21 | 0.20 |
| 3.0 | 0.43 | 0.40 | 0.38 | 0.36 | 0.34 | 0.32 | 0.28 | 0.26 | 0.24 | 0.22 | 0.21 |
| 4.0 | 0.46 | 0.42 | 0.40 | 0.38 | 0.36 | 0.33 | 0.29 | 0.27 | 0.25 | 0.23 | 0.21 |
| 5.0 | 0.48 | 0.44 | 0.41 | 0.39 | 0.37 | 0.33 | 0.30 | 0.27 | 0.25 | 0.24 | 0.22 |
| 6.0 | 0.49 | 0.45 | 0.42 | 0.40 | 0.37 | 0.34 | 0.30 | 0.28 | 0.26 | 0.24 | 0.22 |
| 7.0 | 0.49 | 0.45 | 0.42 | 0.40 | 0.38 | 0.34 | 0.30 | 0.28 | 0.26 | 0.24 | 0.22 |
| 8.0 | 0.50 | 0.46 | 0.43 | 0.40 | 0.38 | 0.34 | 0.30 | 0.28 | 0.26 | 0.24 | 0.22 |
| 9.0 | 0.50 | 0.46 | 0.43 | 0.40 | 0.38 | 0.34 | 0.30 | 0.28 | 0.26 | 0.24 | 0.22 |
| 10 | 0.50 | 0.46 | 0.43 | 0.41 | 0.38 | 0.34 | 0.30 | 0.28 | 0.26 | 0.24 | 0.22 |
| 15 | 0.50 | 0.47 | 0.43 | 0.41 | 0.38 | 0.34 | 0.30 | 0.28 | 0.26 | 0.24 | 0.22 |
| 20 | 0.51 | 0.47 | 0.44 | 0.41 | 0.38 | 0.34 | 0.31 | 0.28 | 0.26 | 0.24 | 0.22 |
| 25 | 0.51 | 0.47 | 0.44 | 0.41 | 0.38 | 0.34 | 0.31 | 0.28 | 0.26 | 0.24 | 0.22 |
| 30 | 0.51 | 0.47 | 0.44 | 0.41 | 0.38 | 0.34 | 0.31 | 0.28 | 0.26 | 0.24 | 0.22 |
| 40 | 0.51 | 0.47 | 0.44 | 0.41 | 0.38 | 0.34 | 0.31 | 0.28 | 0.26 | 0.24 | 0.22 |
| 50 | 0.51 | 0.47 | 0.44 | 0.41 | 0.38 | 0.34 | 0.31 | 0.28 | 0.26 | 0.24 | 0.22 |
| 60 | 0.51 | 0.47 | 0.44 | 0.41 | 0.38 | 0.34 | 0.31 | 0.28 | 0.26 | 0.24 | 0.22 |
| 70 | 0.51 | 0.47 | 0.44 | 0.41 | 0.38 | 0.34 | 0.31 | 0.28 | 0.26 | 0.24 | 0.22 |
| 80 | 0.51 | 0.48 | 0.44 | 0.41 | 0.38 | 0.34 | 0.31 | 0.28 | 0.26 | 0.24 | 0.22 |
| 90 | 0.51 | 0.48 | 0.44 | 0.41 | 0.38 | 0.34 | 0.31 | 0.28 | 0.26 | 0.24 | 0.22 |
| 100 | 0.51 | 0.48 | 0.44 | 0.41 | 0.39 | 0.34 | 0.31 | 0.28 | 0.26 | 0.24 | 0.22 |
| 200 | 0.52 | 0.48 | 0.44 | 0.42 | 0.39 | 0.34 | 0.31 | 0.28 | 0.26 | 0.24 | 0.22 |
| 300 | 0.52 | 0.48 | 0.45 | 0.42 | 0.39 | 0.35 | 0.31 | 0.28 | 0.26 | 0.24 | 0.22 |
| 1000 | 0.52 | 0.48 | 0.45 | 0.42 | 0.39 | 0.35 | 0.31 | 0.29 | 0.26 | 0.24 | 0.22 |

low, when:

$$PIV = 2 \times V_{sec(peak)} = 2\sqrt{2} \times V_{sec(rms)} = 2.828 V_{sec(rms)}$$

17) Find Z from Table 3 for X in (11), or for X₁ in (13), and for R_s/R_L % in (9), where Z = I_(rms)/I_o

18) From the value of Z found in (17), determine current through the rectifier diode: I_(rms) = I_o × Z

19) Determine recurrent peak current I_(peak) through the diode, from Table 4 for X (or X₁) and for R_s/R_L % find W, which is I_(peak)/I_o. Thus find I_(peak) = I_o × W.

20) Determine the initial switch-on current I_{on}. As C (or C₁) will be initially discharged, load on the rectifier diode will be nearly a short-circuit at the instant of switch-on, limited only by the source resistance R_s. Then:

$$I_{on} = V_{sec(peak)} / R_s \text{ and}$$

$$V_{sec(peak)} = \sqrt{2} \times V_{sec(rms)}$$

where V_{sec(rms)} was found in (15). This very high current flows for only a very short time, but the rectifier diode must be capable of withstanding it. If a suitable device with such a high pulse current rating is not available, the source resistance R_s must be increased by

adding an external resistor R_{ext} between the rectifier and reservoir capacitor C or C₁. The value of R_{ext} to limit the switch-on current to an acceptable lower value I_{on(L)} is determined in (28).

21) Decide on a suitable rectifier diode type.

The device must have ratings equal to, or greater than, the following: PIV or 2V_{sec(peak)}, sometimes called V_{RRM}, see (16); initial switch-on current or I_{on}, sometimes I_{FSM}, see (20); average current or I_o, sometimes I_{F(AV)}, see (7).

22) Determine the rms ripple current I_{c(rms)} flowing through the reservoir capacitor C (or C₁):

$$I_{c(rms)} = \sqrt{I_{rms}^2 - I_{dc(load)}^2}$$

23) Decide on the specification for the reservoir capacitor to be used. The capacitor must have ratings equal to, or greater than, the following: Capacitance C or C₁, see (12) or (13); dc working voltage V_{sec(peak)}, see (16); ripple current I_{c(rms)}, see (22).

24) Total transformer secondary current I_{t(rms)} is the same as the current through the diode: I_{t(rms)} = I_(rms)

25) Transformer volt-amp, or VA, rating

T_{VA} decides size of the transformer:

$$T_{VA} = V_{sec(rms)} \times I_{t(rms)}$$

26) Transformer requirements:

volt-amp rating T_{VA} (25)

primary winding V_{pri(rms)} (4)

secondary winding V_{sec(rms)} (15)

secondary current I_{t(rms)} (24)

27) When a suitable transformer has been chosen, measure resistance of both windings. If measured source resistance:

$$R_{s(m)} = R_{sec} + \frac{R_{pri}}{N^2} + R_{rec}$$

is less than R_s calculated in (8), then an external resistor of R_{ext} = R_s - R_{s(m)} must be added, see (28), to limit I_{on} to the value found in (20).

28) If external resistor R_{ext} was found necessary in (20) or (27) to be fitted between the rectifier and the reservoir capacitor C or C₁ to limit the switch-on current to I_{on(L)}, its value will be:

$$R_{ext} = \frac{V_{sec(pk)}}{I_{on(L)}} - R_s$$

29) Power P_r dissipated in R_{ext} (if used) is given by: P_r = (I_{t(rms)})² × R_{ext}. A suitable resistor should have a power rating of about twice the value of P_r for reliable operation.

30) If external resistor R_{ext} is used, regulation of the supply can be improved by adding a shorting-out device as recommended for the bridge rectifier circuit in Figs. 2 and 3 of my first article.

A worked example

Here is a worked example for a half-wave rectifier design to be used as a bias supply of 100V at 10mA.

- 1) E_{dc(load)} = 100V
- 2) I_{dc(load)} = 10mA
- 3) V_{r(rms)} = 1.0V_{rms}
- 4) V_{pri(rms)} = 240V_{rms}
- 5) f = 50Hz
- 6) R_L = E_{dc} / I_{dc(load)}
where E_{dc} = E_{dc(load)} + V_{rec}
= 100 + 0.9 = 100.9V
so R_L = 100.9 / 10 × 10⁻³ = 100.9 × 10³ / 10 = 10,090Ω or 10.09kΩ
- 7) I_o = I_{dc(load)} = 10mA
- 8) R_s = R_L × 5 / 100 = 10.09 × 10³ × 5 / 100 = 504.5Ω
- 9) R_s × 100 / R_L % = 504.5 × 100 / 10.09 × 10³ % = 5%
- 10) V_r % = V_{r(rms)} × 100 / E_{dc(load)} %

Table 3. Find value Z here to determine current through the rectifier.

| X | R _s /R _L % | | | | | | | | | | |
|------|----------------------------------|------|------|------|------|------|------|------|------|------|------|
| | 0.02 | 0.05 | 0.1 | 0.2 | 0.5 | 1.0 | 2 | 5 | 10 | 30 | 100 |
| 1 | 1.80 | 1.80 | 1.79 | 1.79 | 1.79 | 1.78 | 1.77 | 1.77 | 1.73 | 1.70 | 1.66 |
| 2 | 2.03 | 2.02 | 2.01 | 2.00 | 1.99 | 1.98 | 1.97 | 1.96 | 1.89 | 1.77 | 1.67 |
| 3 | 2.19 | 2.17 | 2.16 | 2.14 | 2.13 | 2.11 | 2.10 | 2.03 | 1.95 | 1.79 | 1.67 |
| 4 | 2.32 | 2.30 | 2.28 | 2.26 | 2.24 | 2.22 | 2.17 | 2.08 | 1.98 | 1.80 | 1.68 |
| 5 | 2.43 | 2.40 | 2.36 | 2.32 | 2.27 | 2.23 | 2.19 | 2.10 | 2.01 | 1.82 | 1.68 |
| 6 | 2.50 | 2.48 | 2.46 | 2.44 | 2.42 | 2.40 | 2.28 | 2.13 | 2.04 | 1.83 | 1.68 |
| 7 | 2.58 | 2.53 | 2.51 | 2.49 | 2.47 | 2.45 | 2.31 | 2.16 | 2.05 | 1.84 | 1.68 |
| 8 | 2.66 | 2.63 | 2.61 | 2.60 | 2.58 | 2.50 | 2.35 | 2.17 | 2.06 | 1.84 | 1.68 |
| 9 | 2.73 | 2.70 | 2.68 | 2.66 | 2.64 | 2.57 | 2.38 | 2.18 | 2.07 | 1.85 | 1.68 |
| 10 | 2.80 | 2.78 | 2.75 | 2.73 | 2.70 | 2.62 | 2.40 | 2.19 | 2.08 | 1.86 | 1.68 |
| 20 | 3.30 | 3.20 | 3.17 | 3.15 | 2.83 | 2.82 | 2.53 | 2.26 | 2.12 | 1.88 | 1.68 |
| 30 | 3.64 | 3.50 | 3.40 | 3.29 | 3.05 | 2.89 | 2.59 | 2.30 | 2.15 | 1.90 | 1.68 |
| 40 | 3.91 | 3.72 | 3.55 | 3.40 | 3.13 | 2.92 | 2.62 | 2.32 | 2.16 | 1.90 | 1.68 |
| 50 | 4.08 | 3.87 | 3.68 | 3.48 | 3.22 | 2.93 | 2.64 | 2.33 | 2.17 | 1.91 | 1.68 |
| 60 | 4.23 | 3.97 | 3.78 | 3.55 | 3.25 | 2.94 | 2.66 | 2.35 | 2.18 | 1.91 | 1.68 |
| 70 | 4.35 | 4.03 | 3.87 | 3.60 | 3.27 | 2.95 | 2.67 | 2.36 | 2.18 | 1.91 | 1.68 |
| 80 | 4.45 | 4.10 | 3.94 | 3.65 | 3.30 | 2.96 | 2.68 | 2.36 | 2.18 | 1.91 | 1.68 |
| 90 | 4.52 | 4.18 | 3.98 | 3.67 | 3.31 | 2.97 | 2.68 | 2.37 | 2.19 | 1.91 | 1.68 |
| 100 | 4.62 | 4.23 | 4.02 | 3.69 | 3.32 | 2.98 | 2.69 | 2.37 | 2.19 | 1.91 | 1.68 |
| 200 | 5.03 | 4.60 | 4.27 | 3.86 | 3.37 | 2.99 | 2.69 | 2.38 | 2.19 | 1.91 | 1.68 |
| 300 | 5.20 | 4.79 | 4.33 | 3.88 | 3.38 | 3.00 | 2.69 | 2.38 | 2.19 | 1.91 | 1.68 |
| 400 | 5.35 | 4.86 | 4.37 | 3.88 | 3.38 | 3.00 | 2.70 | 2.38 | 2.19 | 1.91 | 1.68 |
| 500 | 5.45 | 4.90 | 4.38 | 3.89 | 3.38 | 3.00 | 2.70 | 2.39 | 2.19 | 1.91 | 1.68 |
| 600 | 5.51 | 4.93 | 4.38 | 3.89 | 3.39 | 3.00 | 2.70 | 2.39 | 2.19 | 1.91 | 1.68 |
| 700 | 5.60 | 4.96 | 4.39 | 3.90 | 3.39 | 3.01 | 2.70 | 2.39 | 2.19 | 1.91 | 1.68 |
| 800 | 5.67 | 4.98 | 4.39 | 3.90 | 3.39 | 3.01 | 2.70 | 2.39 | 2.19 | 1.91 | 1.68 |
| 900 | 5.70 | 4.99 | 4.39 | 3.90 | 3.39 | 3.01 | 2.70 | 2.39 | 2.19 | 1.91 | 1.68 |
| 1000 | 5.75 | 5.00 | 4.39 | 3.90 | 3.39 | 3.01 | 2.70 | 2.39 | 2.19 | 1.91 | 1.68 |

Table 4. Value W is needed to find peak current.

| X | R _s /R _L % | | | | | | | | | | |
|------|----------------------------------|------|------|------|------|------|------|------|------|------|------|
| | 0.02 | 0.05 | 0.1 | 0.2 | 0.5 | 1.0 | 2 | 5 | 10 | 30 | 100 |
| 1 | 3.70 | 3.70 | 3.70 | 3.64 | 3.62 | 3.60 | 3.60 | 3.59 | 3.58 | 3.57 | 3.46 |
| 2 | 4.60 | 4.57 | 4.55 | 4.53 | 4.52 | 4.50 | 4.28 | 4.20 | 4.08 | 3.72 | 3.51 |
| 3 | 5.50 | 5.40 | 5.33 | 5.30 | 5.20 | 5.10 | 5.00 | 4.67 | 4.33 | 4.00 | 3.55 |
| 4 | 6.20 | 6.17 | 6.13 | 6.10 | 6.00 | 5.98 | 5.45 | 5.20 | 4.95 | 4.05 | 3.57 |
| 5 | 7.30 | 6.95 | 6.90 | 6.85 | 6.80 | 6.75 | 6.51 | 5.60 | 5.00 | 4.10 | 3.62 |
| 6 | 8.00 | 7.90 | 7.70 | 7.60 | 7.50 | 7.30 | 6.90 | 5.84 | 5.09 | 4.19 | 3.63 |
| 7 | 8.70 | 8.55 | 8.50 | 8.30 | 8.10 | 7.82 | 7.30 | 6.00 | 5.10 | 4.22 | 3.64 |
| 8 | 9.60 | 9.50 | 9.35 | 9.00 | 8.50 | 8.20 | 7.69 | 6.15 | 5.14 | 4.23 | 3.64 |
| 9 | 10.3 | 9.80 | 9.60 | 9.50 | 9.10 | 8.55 | 7.72 | 6.23 | 5.21 | 4.25 | 3.65 |
| 10 | 10.9 | 10.7 | 10.5 | 10.1 | 9.50 | 8.64 | 7.74 | 6.30 | 5.28 | 4.26 | 3.66 |
| 20 | 16.0 | 15.0 | 14.4 | 13.0 | 11.1 | 9.44 | 7.83 | 6.47 | 5.29 | 4.27 | 3.66 |
| 30 | 19.7 | 18.0 | 16.3 | 14.3 | 11.7 | 9.60 | 7.92 | 6.50 | 5.31 | 4.27 | 3.66 |
| 40 | 21.9 | 20.0 | 17.3 | 14.7 | 12.1 | 9.64 | 8.01 | 6.51 | 5.33 | 4.28 | 3.66 |
| 50 | 23.7 | 20.8 | 18.2 | 15.2 | 12.2 | 9.70 | 8.10 | 6.51 | 5.34 | 4.28 | 3.66 |
| 60 | 24.9 | 21.1 | 18.5 | 15.4 | 12.3 | 9.77 | 8.12 | 6.51 | 5.34 | 4.29 | 3.66 |
| 70 | 25.9 | 21.4 | 18.9 | 15.6 | 12.4 | 9.84 | 8.14 | 6.51 | 5.34 | 4.29 | 3.66 |
| 80 | 26.7 | 21.8 | 19.4 | 15.7 | 12.4 | 9.90 | 8.16 | 6.51 | 5.34 | 4.30 | 3.66 |
| 90 | 27.5 | 22.2 | 19.5 | 15.8 | 12.5 | 9.93 | 8.18 | 6.51 | 5.34 | 4.30 | 3.66 |
| 100 | 28.5 | 22.5 | 19.7 | 15.9 | 12.5 | 9.96 | 8.19 | 6.52 | 5.35 | 4.31 | 3.66 |
| 200 | 30.5 | 23.0 | 20.0 | 16.3 | 12.6 | 10.0 | 8.19 | 6.52 | 5.36 | 4.31 | 3.67 |
| 300 | 31.6 | 23.3 | 20.5 | 16.9 | 12.7 | 10.0 | 8.20 | 6.53 | 5.38 | 4.32 | 3.67 |
| 400 | 32.8 | 23.5 | 20.9 | 17.0 | 12.7 | 10.0 | 8.20 | 6.54 | 5.40 | 4.32 | 3.67 |
| 500 | 33.3 | 23.8 | 21.0 | 17.1 | 12.8 | 10.0 | 8.20 | 6.55 | 5.42 | 4.33 | 3.68 |
| 600 | 33.8 | 24.0 | 21.1 | 17.2 | 12.8 | 10.1 | 8.20 | 6.56 | 5.44 | 4.33 | 3.68 |
| 700 | 34.2 | 24.5 | 21.2 | 17.3 | 12.9 | 10.1 | 8.20 | 6.57 | 5.46 | 4.33 | 3.69 |
| 800 | 34.4 | 24.9 | 21.4 | 17.4 | 12.9 | 10.1 | 8.20 | 6.58 | 5.48 | 4.33 | 3.69 |
| 900 | 34.5 | 25.8 | 21.5 | 17.5 | 13.0 | 10.1 | 8.20 | 6.59 | 5.52 | 4.33 | 3.70 |
| 1000 | 34.7 | 27.0 | 21.6 | 17.6 | 13.0 | 10.1 | 8.20 | 6.60 | 5.56 | 4.33 | 3.70 |

- =1×100/100%=1.0%
 - 11) Value of X for V_r% and for R_s/R_L% i.e. V_r%=1.0 and R_s/R_L%=5.0 from Table 1 is found to be 150.
 - 12) C=X/2πf×R_L×10⁶μF =150×10⁶/2π×50×10.09×10³μF =47.3μF
 - 13) 47μF is a standard value for an electrolytic capacitor and would be a suitable choice.
 - 14) The value of Y for X and for R_s/R_L% i.e. X=150 and R_s/R_L%=5.0 from Table 2 is found to be 0.76
 - 15) V_{sec(rms)}=E_{dc}/√2×Y=100.9/√2×0.76 =93.9V
 - 16) PIV=2.828V_{sec(rms)}=2.828×93.9=266V
 - 17) The value of Z for X and for R_s/R_L% i.e. X=150 and R_s/R_L%=5.0 from Table 3 is found to be 2.375
 - 18) I_(rms)=I_o×Z i.e. Z=2.375 and I_o=10mA (see (7)) =10×10⁻³×2.375=0.02375A or 23.75mA
 - 19) The value of W for X and R_s/R_L% i.e. X=150 and R_s/R_L%=5.0 from Table 4 is found to be 6.52 and so: I_(peak)=I_o×W=10×10⁻³×6.52 =0.0652A or 65.2mA.
 - 20) I_{on}=V_{sec(peak)}/R_s=√2×V_{sec(rms)}/R_s =√2×93.9/504.5=0.263A or 263mA
 - 21) Diode ratings required: PIV (or V_{RRM})=266V I_{on} (or I_{FSM})=263mA I_o (or I_{F(AV)})=10mA
 - 22) I_{c(rms)} = √(I_(rms)² - I_{dc(load)}²) = √(23.75² - 10²) = √564 - 100 = √464 = 21.54
- Both I_(rms) and I_{dc(load)} are in mA.
- 23) Reservoir capacitor ratings required: C=47μF V_{sec(peak)}=V_{DC(wkg)}=√2×V_{sec(rms)} =√2×93.9=132.7V I_{c(rms)}=21.54mA
 - 24) I_{t(rms)}=I_(rms)=23.75mA
 - 25) T_{VA}=V_{sec(rms)}×I_{t(rms)} =93.5(23.75×10⁻³)=2.22VA
 - 26) Mains transformer ratings required: T_{VA} VA = 2.22VA V_{pri(rms)} primary winding = 240V_{rms} V_{sec(rms)} secondary winding = 93.9V rms I_{t(rms)} secondary current = 23.75mA rms


In a subsequent article, Ray will describe the steps needed for designing full-wave centre-tapped rectifier circuits. The September issue contained the procedure for full-wave bridge rectifiers. ■

Dictionary of Communications Technology

Terms, definitions and abbreviations

Gilbert Held, 4-Degree Consulting, Macon, Georgia, USA

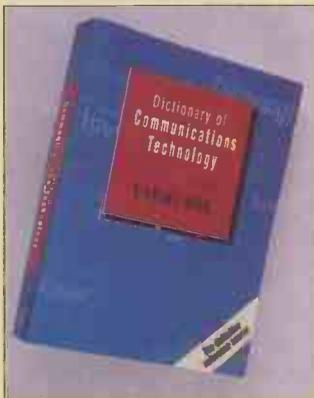In response to the changing face of the telecommunications industry and the rapid expansion in the use of microprocessors, fibre optics and satellites, Gil Held has updated his earlier telecommunications dictionary to bring readers in line with the very latest developments and terms in communications technology.



Features Include:

- Over 9000 references and 250+ illustrations
- Comprehensive coverage of data and computer communications
- New entries on PC LANs, the Internet, client/server operations and communications testing
- Trade name information

First Edition Review:

"For a consultant or telecommunications operative, this book is a must. It is comprehensive and timely ... an excellent reference for the IS professional."

Data Processing Digest

ISBN 0471 95542 6, 512pp, hardback, UK £68.50, Europe £73, ROW £85


ISBN 0471 95126 9, 512pp, paperback, UK £38.50, Europe £43, ROW £55

Testing, Troubleshooting and Tuning Local Area Networks

Techniques and tools to isolate problems and boost performance

Gilbert Held, 4-Degree Consulting, Macon, Georgia, USA.

Recognising the problems

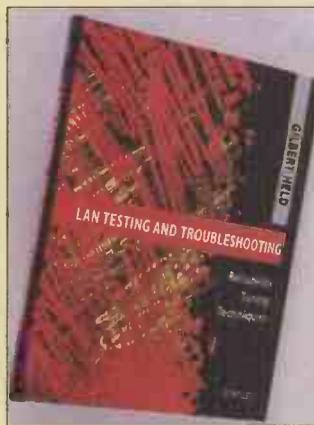

encountered by network users and administrators on a daily basis, this book is designed to assist readers by focusing on testing, troubleshooting and tuning of Ethernet and Token-Ring networks. It is devoted exclusively to: how things go wrong how to recognise, monitor and test for problems; network analysis and network management products that assist users in examining the flow of data in a complex network.

ISBN 0471 95880 8, 275pp, hardback, UK £37.50, Europe £40, ROW £50

Wireless Information Networks

Kaveh Pahlavan, Worcester Polytechnic Institute and Allen H Levesque, GTE Government Systems Corporation.

Wireless Information Networks organises all major elements of wireless technology – cordless and cellular telephony, Personal Communications Systems (PCS), mobile data networks and Wireless Local Area Networks (WLANs), presenting them from a logical, systems engineering perspective. Technical material is thoroughly integrated with special applications and focuses on four main areas: Wireless



standards and descriptions of systems and products; Measurement and modelling of radio and optical wave propagations; Wireless transmission techniques and Wireless multiple access techniques.

Contents: Overview of Wireless Networks. Frequency Administration and Standards Activities. Characterisation of Radio Propagation. Channel Measurement and Modelling for Narrow-band Signaling. Measurement of Wide-band Channel Characteristics. Computer Simulation of the Radio Channel. Modem Technology. Signal Processing for Wireless Applications. Spread Spectrum for WIN Systems. Wireless Optical Networks. Networks and Access Methods. Standards and Products.

ISBN 0471 10607 0, 304pp, hardback, UK £63.50, Europe £68, ROW £81


Applied Cryptography

2nd Edition

Protocols, Algorithms and Source Code in C

Bruce Schneier, Security Consultant and President of Counterpane Systems, USA

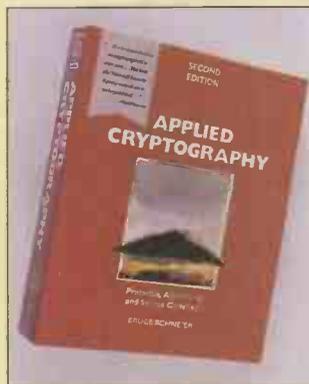This revision of the programmer's and system designer's guide to the practical applications of modern cryptography



provides the most comprehensive, up-to-date survey of modern cryptographic techniques, along with practical advice on how to implement them.

New to this edition:

- Detailed treatment of the US government's Clipper Chip encryption program
- New encryption algorithms (eg. 'GOST') recently obtained from the former Soviet Union
- More detailed information on incorporating algorithms and programming fragments

into working software


- The latest developments in the fields of message authentication ('digital signatures') and digital cash.
- ISBN 0471 12845 7, 816pp, hard back, UK £59, Europe £64, ROW £78
ISBN 0471 11709 9, 816pp, paperback, UK £44, Europe £49, ROW £63

Data and Image Compression

4th edition
tools and techniques

Gilbert Held, 4-Degree Consulting, Macon, Georgia, USA

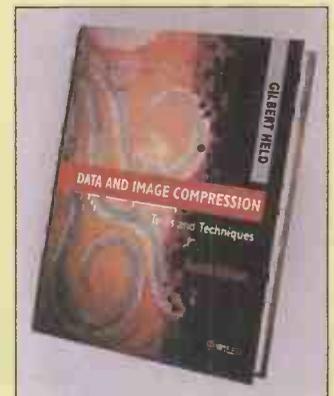Data and image compression are key issues in computer communications with the increasing demand for data transmission capacity.



Guiding the reader through the main techniques, this book explains how practical data and image compression techniques are now vital for efficient, low-cost transmission and data storage requirements. Building on the success of the previous editions of *Data Compression*, the scope of the fourth edition has been considerably expanded. Now covering image and fax compression, the text has been restructured to take account of the many new advances in this important field. It is also accompanied by an updated disk containing compression routines.

ISBN 0471 95247 8, 450pp+disk, hardback, UK £58.50, Europe £63, ROW £75

Handbook for Digital Signal Processing

S.K. Mitra, University of California and J.F. Kaiser, Bell Communications Research, New Jersey, USA

This is the definitive source of detailed information on all important topics in modern

LETTERS

Letters to "Electronics World"
Quadrant House, The Quadrant,
Sutton, Surrey, SM2 5AS

Music in Mind

In response to Ian Hickman's challenge in the October 1996 issue, as to why his gyroscope headphone system did not work on stereo, I offer the following thoughts.

Firstly, there is more to head movement than just delay shift. The acoustic signal reaching the ear is turned toward the sound source as it is increased in level at high frequencies, while the other ear receives less high frequency. This is due to the head attenuating the directional signal.

Secondly, and perhaps more importantly, is that classical recordings are made for reproduction on loudspeaker systems. In stereo, two techniques for obtaining the stereophonic effect exist: intensity differencing and time differencing. If the signal from the left speaker arrives at the ear earlier than the signal from the right speaker, the apparent source location is shifted to the left. For a source to be perceived to be entirely at the left or right, quite large time differences are needed.

In practice, it appears that stereo through time differences gives a more widespread – and often more pleasing – stereo sound on loudspeakers than does intensity stereo. Also, the omnidirectional microphones suitable for this technique are superior. As a result, most classical music recordings use time-difference stereo.

The microphones are spaced about a meter or so apart, giving spatial cues containing time differences of up to 3ms between the left and right speaker. As you can imagine, adding some 150µs extra delay to this difference to obtain an in-front localisation on head

phones, as Ian did in his experiment, would not have a noticeable effect.

If this theory is right, there should be a solution. Try listening to a stereo recording with intensity differences solely. I think that recordings from Nimbus would demonstrate this. The clue is to look for recordings that are made using coincidental, or nearly coincidental, microphone techniques. Maybe a special artificial head-recording would do.

It would be interesting to see

whether this theory gives any result.
Elco Grimm
Editor
Pro-Audio Magazine

Congratulations to Ian Hickman for his attempts at correcting for head rotation with headphone listening. The use of the piezo-vibrating gyroscope is a worthwhile contribution.

However, the parameters under control are inadequate and I suggest are the reason why sound sources remain stubbornly localised within the head.

The secret of auralisation with headphones is the accuracy to which the required signals can be reconstructed at the entrance to the ear canal, to match those produced by a real-life source. It is well known that an external sound source will have two associated transfer functions between the source and each ear. These are called the head related transfer functions, or hrtfs.

Each point in space has a unique pair of hrtfs (one for each ear) with respect to head orientation. The transfer functions are influenced by the head shape, pinna geometry and, to a lesser extent, the effect of the torso. Even more frustrating is that each listener will have a unique set of transfer functions, although fortunately there is some degree of commonality between listeners, though head size can play a role too.

When the head rotates with respect to an external point source, the transfer functions change dynamically. Any system that is intended to recreate the correct ear signals must therefore include a knowledge of these filters and an ability to process them dynamically. Computing purely on a basis of amplitude and time differentials is insufficient to recreate accurate out-of-head spatialisation. This also implies that information that is encoded using normal stereo will not readily be amenable to such processing. Binaural sources obviously have an advantage, but when the head moves the signals are so interwoven that they cannot accurately be processed into their correct perspective, although better results should in theory be possible.

Mr Hickman, however, should not feel too disheartened. I have heard several systems claiming to do this

with low-cost electronics, some using multiple drive unit headphones, and all have failed to impress. The only system (for me) so far to work using an orientation measurement was demonstrated to me by Dr Mike Hollier at British Telecom Research Laboratory.

The system used the 'Huron' manufactured by Lake, which is a digital filter costing £60,000 or so and capable of very long impulse responses that can be controlled dynamically. The system incorporates a set of hrtfs and a positional sensor is located on the headphones. Listening in real time to a person talking into a microphone, and rotating my head, an external image was perceived that was localised accurately within the room's frame of reference.

Note, however, that the Huron is a bit of overkill in this application. Its power is intended to incorporate the long impulse responses that are encountered when simulating a large acoustic environment where the aim is to be able to move around within an artificially created space. That is the acoustic wing of virtual reality.

So, any working system must use real-time dsp and include accurate hrtf data. It must also use appropriate headphones, preferably feeding directly into the ear canal as there can be significant errors introduced into the hrtfs due to the vague coupling between headphone and ear canal. Multiple drive units within headphones do not solve this particular problem. Sometimes a slight adjustment of the headphone can compromise the whole system by differentially changing the left-ear and right-ear hrtfs.

Prof Malcolm Omar Hawksford
Director
Centre for Audio Research &
Engineering
University of Essex

Anti-gravity and the aether

In EW May 1996, p. 429, Dr. David Fisher advised you to "double-check the work of anyone who is known to believe in dowsing, ball lightning, 'free energy' and/or anti-gravity." He fears incitement of panic.

In EW August 1996, p. 590, when challenged by his prey, Anthony Hopwood, Dr. Fisher stated that in

fact he was thinking of me, for my belief in this nonsense! See my article (*E&WW*, pp. 29-31, 1989).

I have not written anything on the subject of dowsing and am now wondering if Dr. Fisher has conveyed similar advice to the editor of the *Sunday Telegraph* who reported in the 1 September 1996 issue, a breakthrough in antigravity. The report concerns research at Tampere University of Technology in Finland and declares that objects on every floor of the laboratory that were positioned directly above the anti-gravity machine lost some weight when the machine on the lower floor was set spinning.

I believe that this is because the flywheel was developing spin-off owing to precessional motion in globules of aether, a weak version of thunderballs, which rose through the intervening floors. Why this causes a loss of weight is explained in my paper 'The Theory of Anti-Gravity' in *Physics Essays*, (Vol. 4, pp. 13-19; 1991).

Readers of *Electronics World* do not panic when there is noise in their radio reception; they just seek to understand the cause. However, maybe NASA might panic when faced with the dilemma of having anti-gravity space travel technology at the price of making radio communication incoherent.

Whether one induces that aether precession by magnets acting on superconductive flywheels or mechanically as in Laitwaite's faster-than-natural precession of an offset flywheel, those aetherial eddies have the power to reduce the weight of matter they occupy. They also affect the speed of light.

There is some evidence that they are produced by earthquakes because they seem to affect fm signals but not am signals. See 'Earthquake-Related EM Disturbances', *Quarterly Journal of the Royal Astronomical Society*, Vol. 28, 535-536 (1987).

Harold Aspenden
Chilworth, Hampshire

Victoria listened in too

Tom Ival's article on Marconi's patent of 1896 characterises the era by commenting: "Queen Victoria was still on the throne". But she was

MOONSHINE BIBLE 270 page book covering the production of alcohol from potatoes, rice, grains etc. Drawings of simple home made stills right through to commercial systems. £12 ref MS3
NEW HIGH POWER MINI BUG With a range of 800 metres or more and up to 100 hours use from a PP3 this will be popular! Bug measures less than 1" square £28 Ref LOT102

SINCLAIR C6 MOTORS We have a new ones available without gearboxes at £50 ref LOT25

BUILD YOUR OWN WINDFARM FROM SCRAP New publication gives step by step guide to building wind generators. Armed with this publication and a good local scrap yard could make you self sufficient in electricity! £12 ref LOT81

PC KEYBOARDS PS2 connector, top quality suitable for all 286/386/486 etc £10 ref PCKB. 10 for £65.

TRACKING TRANSMITTER range 1.5-5 miles, 5,000 hours on AA batteries, also transmits info on car direction and motion! Works with any FM radio. 1.5" square. £65 ref LOT101

ELECTRIC DOOR LOCKS Complete lock with both Yale lock and 12v operated deadlock (keys included) £10 ref LOT99

GALLIUM ARSENIDE FISHEYE PHOTO DIODES Complete with suggested circuits for long range communications/switching £12 complete.

SURVEILLANCE TELESCOPE Superb Russian zoom telescope adjustable from 15x to 60x! complete with metal tripod (impossible to use without this on the higher settings) 66mm lens, leather carrying case £149 ref BAR69

WIRELESS VIDEO BUG KIT Transmits video and audio signals from a miniature CCTV camera (included) to any standard television! All the components including a PP3 battery will fit into a cigarette packet with the lens requiring a hole about 3mm diameter. Supplied with telescopic aerial but a piece of wire about 4" long will still give a range of up to 100 metres. A single PP3 will probably give less than 1 hours use. £99 REF EP79. (probably not licensable!)

CCTV CAMERA MODULES 46X70X29mm, 30 grams, 12v 100mA, auto electronic shutter, 3.6mm F2 lens, CCIR, 512x492 pixels, video output is 1v p-p (75 ohm). Works directly into a scart or video input on a tv or video. IR sensitive. £79.95 ref EF137.

IR LAMP KIT Suitable for the above camera, enables the camera to be used in total darkness! £5.99 ref EF138

INFRA RED POWERBEAM Handheld battery powered lamp, 4 inch reflector, krypton bulb, gives out powerful infrared light! 4 D cells required. £39 ref PB1.

MONO VGA MONITORS, Perfect condition, Compaq, 14", 3 months warranty £29 ref MVGA

SOLAR COOKER GUIDE Comprehensive plans

9 WATT CHIEFTAN TANK LASERS

Double beam units designed to fit in the gun barrel of a tank, each unit has two semi conductor lasers and motor drive units for alignment. 7 mile range, full circuit diagrams, new price £50,000? us? £349. Each unit has two gallium Arsenide injection lasers, 1 x 9 watt, 1 x 3 watt, 900nm wavelength, 28vdc, 600hz pulse frequency. The units also contain an electronic receiver to detect reflected signals from targets, five or more units £299 ea. £349 for one. Ref LOT4.

TWO WAY MIRROR KIT Includes special adhesive film to make two way mirror(s) up to 60"x20". (glass not included) includes full instructions. £12 ref TW1.

NEW LOW PRICED COMPUTER WORKSHOP/HI-FI/R/CB UNITS Complete protection from faulty equipment for everybody! In line units fits in standard IEC lead (extends it by 750mm), fitted in less than 10 seconds, reset/test button, 10A rating. £6.99 each ref LOT5. Or a pack of 10 at £49.90 ref LOT6. If you want a box of 100 you can have one for £250!

RADIO CONTROLLED CARS FROM £6 EACH!!! All returns from famous manufacturer, 3 types available, single channel (left, right, forwards backwards) £6 ref LOT2. Two channel with more features £12 ref LOT2.

THOUSANDS AVAILABLE RING/FAX FOR DETAILS!
MAGNETIC CARD READERS (Swipes) £9.95 Cased with filelays, designed to read standard credit cards! they have 3 wires coming out of the head so they may write as well! complete with control electronics PCB. Just £9.95 ref BAR31

WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA? We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14 ref EP74

PANORAMIC CAMERA OFFER Takes double width photographs using standard 35mm film. Use in horizontal or vertical mode. Complete with strap £7.99 ref BAR1

COIN OPERATED TIMER KIT Complete with coin slot mechanism, adjustable time delay, relay output, put a coin slot on anything you like! TV's, videos, fridges, drinks cupboards, HiFi, takes 50p's and £1 coins. DC operated, price just £7.99 ref BAR27.

ZENITH 900 X MAGNIFICATION MICROSCOPE Zoom, metal construction, built in light, shrimp farm, group viewing screen, lots of accessories. £29 ref ANAYLT.

AA NICAD PACK Pack of 4 tagged AA nicads £2.99 ref BAR34
PLASMA SCREENS 222x310mm, no data hence £4.99 ref BAR67

NIGHTSIGHTS Model TZ54 with infra red illuminator, views up to 75 metres in full darkness in infrared mode, 150m range, 45mm lens, 13 deg angle of view, focussing range 1.5m to infinity. 2 AA batteries required. 950g weight. £199 ref BAR61. 1 years warranty

LIQUID CRYSTAL DISPLAYS Bargain prices,
 16 character 2 line, 99x24mm £2.99 ref SM1623A
 20 character 2 line, 83x19mm £3.99 ref SM2020A
 16 character 4 line, 62x25mm £5.99 ref SMC1640A

TAL-110MM NEWTONIAN REFLECTOR TELESCOPE Russian, Superb astronomical 'scope, everything you need for some serious star gazing! up to 169x magnification. Send or fax for further information ref TAL-1. £249

SOLAR ENERGY/GENERATOR PLANS For your home, loads of info on designing systems etc £7 ref PV1

SOLAR COOKERS Comprehensive guide to building solar powered cookers, includes plans, recipes, cooking times etc £7 ref SBC1

**WOLVERHAMPTON BRANCH
 NOW OPEN AT WORCESTER ST
 W'HAMPTON TEL 01902 22039**

CENTRAL POINT PC TOOLS Award winning software, 1,300 virus checker, memory optimiser, disc optimiser, file compression, low level formatting, backup scheduler, disk defragmenter, undelete, 4 calculators, Dbase, disc editor, over 40 viewers, remote computing, password protection, encryption, comprehensive manual supplied etc £8 ref lot 97 3.5" disks.

GOT AN EXPENSIVE BIKE? You need one of our bottle alarms, they look like a standard water bottle, but open the top, insert a key to activate a motion sensor alarm built inside. Fits all standard bottle carriers, supplied with two keys. SALE PRICE £7.99 REF SA32.

**C O L O U R
 C C T V V I D E O
 C A M E R A S,
 B R A N D N E W,
 C A S E D, £ 1 1 9.**

**PERFECT FOR
 SURVEILLANCE
 INTERNET
 VIDEO CONFERENCING
 SECURITY
 DOMESTIC VIDEO**

Works with most modern video's, TV's, Composite monitors, video grabber cards etc Pal, 1v P-P, composite, 76ohm, 1/3" CCD, 4mm F2.8, 600x682, 12vdc, mounting bracket, auto shutter, 100x50x180mm, 3 months warranty, 10 or more £99 ea.



**Check out our
 WEB SITE**

<http://www.pavilion.co.uk/bull-electrical>

GOT AN EXPENSIVE ANYTHING? You need one of our cased vibration alarms, keyswitch operated, fully cased just fit it to anything from videos to caravans, provides a years protection from 1 PP3 battery, UK made. SALE PRICE £4.99 REF SA33.

DAMAGED ANSWER PHONES These are probably beyond repair so just £4.99 each. BT response 200 machines. REF SA30.

IBM PS2 MODEL 160Z CASE AND POWER SUPPLY Complete with fan etc and 200 watt power supply. £9.95 ref EP67
DELL PC POWER SUPPLIES 145 watt, +5,-5,+12,-12, 150x150x85mm complete with switch, filelays and IEC socket. SALE PRICE £9.99 ref EP55

1.44 DISC DRIVES Standard PC 3.5" drives but returns so they will need attention SALE PRICE £4.99 ref EP68

1.2 DISC DRIVES Standard 5.25" drives but returns so they will need attention SALE PRICE NOW ONLY £3.50 ref EP69

PP3 NICADS Unused but some storage marks. £4.99 ref EP52

DELL PC POWER SUPPLIES (Customer returns) Standard PC psu's complete with fly leads, case and fan. +12v,-12v,+5v,-5v SALE PRICE £1.99 EACH worth if for the bits alone! ref DL1. TRADE PACK OF 20 £29.95 REF DL2.

GAS HOBS AND OVENS Brand new gas appliances, perfect for small flats etc. Basic 3 burner hob SALE PRICE £24.99 ref EP72. Basic small built in oven SALE PRICE £79 ref EP73

ENERGY BANK KIT 100 6"x6" 6v 100mA panels, 100 diodes, connection details etc. £69.95 ref EF112.

PASTEL ACCOUNTS SOFTWARE, does everything for all sizes of businesses, includes wordprocessor, report writer, windowing, networkable up to 10 stations, multiple cash books etc, 200 page comprehensive manual. 90 days free technical support (01342-

*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

BULL ELECTRICAL
 250 PORTLAND ROAD, HOVE, SUSSEX.
 BN3 5QT. (ESTABLISHED 50 YEARS).
 MAIL ORDER TERMS - CASH, PO OR CHEQUE
 WITH ORDER PLUS £3 P&P PLUS VAT.
 PLEASE ALLOW 7-10 DAYS FOR DELIVERY PHONE ORDERS
 WELCOME (ACCESS VISA, SWITCH, AMERICAN EXPRESS)
 TEL: 01273 203500
 FAX: 01273 323077
 E-mail bull@pavilion.co.uk

326009 try before you buy! Current retail price is £129, SALE PRICE £9.95 ref SA12. SAVE £120!!!

RACAL MODEM BONANZA! 1 Racal MPS1223 1200/75 modem, telephone lead, mains lead, manual and comms software, the cheapest way onto the net! all this for just £13 ref DEC13.

BULL TENS UNIT Fully built and tested TENS (Transcutaneous Electrical Nerve Stimulation) unit, complete with electrodes and full instructions. TENS is used for the relief of pain etc in up to 70% of sufferers. Drug free pain relief, safe and easy to use, can be used in conjunction with analgesics etc. £49 Ref TEN1

PC PAL VGA TO TV CONVERTER Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and s/ware. Ideal for laptops or a cheap upgrade. Supplied in kit form for home assembly. SALE PRICE £25 REF SA34

EMERGENCY LIGHTING UNIT Complete unit with 2 double bulb floodlights, built in charger and auto switch. Fully cased. 6v 8AH lead acid req'd. (secondhand) £4 ref MAG4P11.

YUASHA SEALED LEAD ACID BATTERIES Two sizes currently available this month. 12v 15AH at £18 ref LOT8 and 6v 10AH (suitable for emergency lights above) at just £6 ref LOT7.

ELECTRIC CAR WINDOW DE-ICERS Complete with cable, plug etc SALE PRICE JUST £4.99 REF SA28

AUTO SUNCHARGER 155x300mm solar panel with diode and 3 metre lead fitted with a cigar plug. 12v 2watt. £8.99 REF SA25.

MICRODRIVE STRIPPERS Small cased tape drives ideal for stripping. Lots of useful goodies including a smart case, and lots of components. SALE PRICE JUST £4.99 FOR FIVE REF SA26

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LEDs, wire, buzzer, switch plus 1 relay or motor. Superb value kit SALE PRICE JUST £4.99 REF SA27

RGB/CGA/EGA/TTL COLOUR MONITORS 12" in good condition. Back analysed metal case. SALE PRICE £49 REF SA16B

PLUG IN ACORN PSU 19v AC 14w, £2.99 REF MAG3P10

13.8V 1.9A PSU cased with leads. Just £9.99 REF MAG10P3

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the C5 motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

PHONE CABLE AND COMPUTER COMMUNICATIONS PACK Kit contains 100m of 6 core cable, 100 cable clips, 2 line drivers with RS232C interfaces and all connectors etc. Ideal low cost method of communicating between PCs over a long distance utilizing the serial ports. Complete kit £8.99. Ref comp1.

VIEWDATA SYSTEMS made by Phillips, complete with Internal 1200/75 modem, keyboard, psu etc RGB and composite outputs, menu driven, autodialler etc. SALE PRICE £12.99 REF SA18

AIR RIFLES .22As used by the Chinese army for training purposes, so there is a lot about! £39.95 Ref EF78. 500 pellets £4.50 ref EF80.

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to its spare channel) 12V DC op. Price is £25 REF: MAG15 12v psu is £5 extra REF: MAG5P2

***MINIATURE RADIO TRANSCEVERS** A pair of walkie talkies with a range up to 2km in open country. Units measure 22x52x155mm. Including cases and ear pieces. 2xPP3 req'd. £30.00 pr. REF: MAG30

***FM TRANSMITTER KIT** housed in a standard working 13A adapter! the bug runs directly off the mains so lasts forever why pay £700? or price is £15 REF: EF62 (kit) Transmits to any FM radio.

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

GAT AIR PISTOL PACK Complete with pistol, darts and pellets £12.95 Ref EF82B extra pellets (500) £4.50 ref EF80.

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. SALE PRICE £4.99 REF SA24.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

**MIXED GOODIES BOX OF
 MIXED COMPONENTS WEIGHING 2 KILOS
 YOURS FOR JUST £6.99**

4X28 TELESCOPIC SIGHTS Suitable for all air rifles, ground lenses, good light gathering properties. £19.95 ref R/7.

GYROSCOPES Remember these? well we have found a company that still manufactures these popular scientific toys, perfect gift for educational use etc. £6 ref EP70

HYPOTHERMIA SPACE BLANKET 215x150cm aluminised foil blanket, reflects more than 90% of body heat. Also suitable for the construction of two way mirrors! £3.99 each ref O/L041.

LENSTATIC RANGER COMPASS Oil filled capsule, strong metal case, large luminous points. Sight line with magnifying viewer. 50mm dia, 86gms. £10.99 ref O/K604.

RECHARGE ORDINARY BATTERIES UP TO 10 TIMES! With the Battery Wizard! Uses the latest pulse wave charge system to charge all popular brands of ordinary batteries AAA, AA, C, D, four at a time! Led system shows when batteries are charged, automatically rejects unsuitable cells, complete with mains adapter. BS approved. Price is £21.95 ref EP31.

TALKING WATCH Yes, it actually tells you the time at the press of a button. Also features a voice alarm that wakes you up and tells you what the time is! Lithium cell included. £7.99 ref EP26.

PHOTOGRAPHIC RADAR TRAPS CAN COST YOU YOUR LICENCE! The new multiband 2000 radar detector can prevent even the most responsible of drivers from losing their licence! Adjustable audible alarm with 8 flashing leds gives instant warning of radar zones. Detects X, K, and Ka bands. 3 mile range, 'over the hill' 'around bends' and 'rear trap' facilities. micro size just 4.25"x2.5"x.75". Can pay for itself in just one day! £79.95 ref EP3.

3" DISCS As used on older Amstrad machines, Spectrum plus3's etc £3 each ref BAR400.

STEREO MICROSCOPES BACK IN STOCK Russian, 200x complete with lenses, lights, filters etc etc very comprehensive microscope that would normally be around the £700 mark. our price is just £299 (full money back guarantee) full details in catalogue..

**WE BUY SURPLUS STOCK
 FOR CASH
 BUYERS DIRECT LINE 0802 660377**

far from being a passive observer of events. Two years later, in the summer of 1898, she was buying "wireless sets".

Edward Prince of Wales, convalescing after a knee injury, elected to spend some weeks aboard the Royal Yacht, which was moored two miles away in Cowes bay, discreetly out of sight of Osborne.

The 80-year old Queen-Emress determined to have some easy means of communication with him. Never one to overlook the latest technology, she commissioned Marconi to install wireless telegraphy apparatus. This was done, and a 100-foot aerial was erected in the grounds of Osborne; a similar affair with a somewhat smaller aerial was provided aboard the Royal Yacht.

The resulting traffic was irredeemably trivial, being mainly

on the "when are you coming to dinner?" level, though some sea trials were also carried out.

But: "The Prince of Wales and other Royalties gave expression to Mr. Marconi of their high appreciation of his system..." (*Electrical Review*). The publicity was immensely useful to the infant Marconi Company.

This incident, and much more fascinating material too, may be found in W.P. Jolly's biography of Marconi (Constable, London, 1972).
Ashby Tabb
Taunton, Somerset

Thermal compensation: why bother?

Of course if the only circuits available for Class B

complementary pair use were the standard ones such as those shown in Fig. 6 of Douglas Self's 'Night thoughts on crossover distortion', *EW* Nov. 1996, it would fully justify not just the article itself, but all his preceding articles.

As I have shown in 1982, (*Class S*, *Wireless World*, Sep. 1982) there another way.

Quite simply, using this legally protected circuit, crossover distortion is hard to measure and the circuit needs no setting up. It is tolerant of ageing and temperature effects. As a bonus it also has lower large signal distortion.

Why is this? Referring to page 793 of this magazine for October 1996, the output impedance of the voltage amplifier A_1 is very low, ideally zero. This forms a heavy attenuator when combined with the upper 22Ω resistor for any distortion generated

by the push-pull power stage A_2 and its transistors.

This attenuation holds just as well for low value cross over voltages as for large value amplitudes. All A_2 and its components do is provide, ideally, the load current, leaving A_1 to provide very little current while seeing a high impedance load.

Because A_1 sees for most of the time this high impedance load and only for a few millivolts of excursion (in the crossover region) has to drive the real low impedance load, which it can easily do, the net result is an amplifier with excellent performance and a clear method of operation.

Finally, apologies for the trumpet blowing but it is partly the result of exasperation and partly the result of needing the publicity in order to obtain work.

Aubrey Sandman
London

Feedback feedback please

Having built two new power amps and then found out that in use their gain was about 12dB too much, I shuddered at the thought of all the work involved to redesign for the lower gain. I thought for the umpteenth time that there must be a simpler way, like using low gain linear stages with little or no overall negative feedback.

I was happy with the output stage, Fig. 1, which is a fet version of the Texas Instruments Texan amplifier and has been described in *EW+WW*, April and September 1990. It needed a bit of experimentation with R_1 to get equal positive and negative half cycles, open loop, but that is all it needs.

Applying negative feedback to give a gain of four, the stage has quite a reasonable performance, except that the output impedance is about 1Ω. Also, when loaded, the stage distorts because there is nothing to increase the drive. I tried all sorts of comparators to apply feedback only when there was a difference between output and input, but none worked effectively.

I was about to give in when I came across a reference to an error cancelling technique by Hawksford in the *Siliconix Mospower Applications Handbook* (Application 6.6.3). Figure 2 gives the theory and Fig. 3 the way I applied it. Having got the gains right, the results were astounding.

If the gain from P-R-Q to P is less than unity, Z_o will have some small value. If the gain is unity, Z_o will be close to zero. If the gain is slightly greater than unity, Z_o will have a negative resistance characteristic. The gain from P-S-Q-P must be the reciprocal of the closed-loop gain of the corrected amplifier.

During testing, it was found that a capacitive load of more than 22nF caused a high output at high frequency. This was a surprise as the output stage itself would happily drive a 10μF at 1kHz. More experimenting gave the feeling that this was not parasitic oscillation, but rather amplified and filtered noise. While loading the output with increasing values of capacitor, the output of A_1 became increasingly noisy until it burst into oscillation at about 2MHz. Putting a small capacitor across R_8 (A_1) stopped the oscillation but was not the best place as only the error signal

was being filtered. The best solution was a 22pF across R_{12} (A_2) to filter signal and error. The amplifier now drives 10μF with no problem.

The only explanation I can give at the moment is that a capacitor across the output filters out high frequency noise at that point (22nF=3R6 at 2MHz). This would mean that the noise at S would not be cancelled in A_1 by noise from P and would be fed back as a signal. I am not entirely happy with that idea since there is not much noise at those points anyway. Resistor R_{15} is chosen to give required gain.

I would welcome your comments on this technique.

K H Ellis
Wolverhampton
England

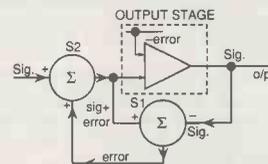


Fig. 2. Hawksford's error-cancelling technique. Output stage has -error signal added to it. Input signal has +error added to it and so cancels the error out. S_1 creates the error signal.

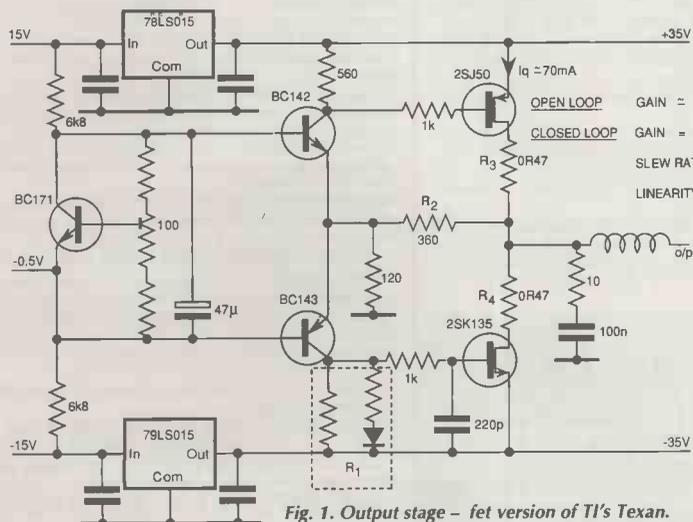


Fig. 1. Output stage - fet version of TI's Texan.

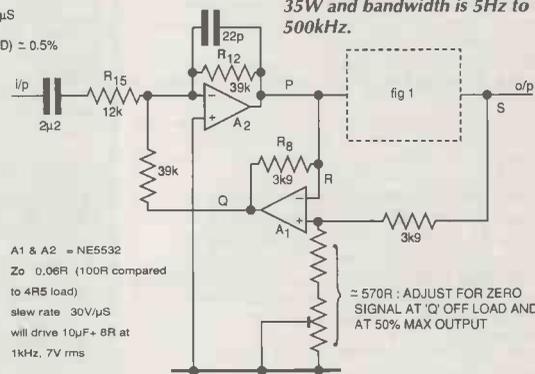


Fig. 3. Application of Hawksford's error-cancelling technique. Gain is 12, maximum power into 4.5Ω is 35W and bandwidth is 5Hz to 500kHz.

A_1 & A_2 = NE5532
 Z_o 0.06R (100R compared to 4R5 load)
slew rate 30V/μS
will drive 10μF + 8R at 1kHz, 7V rms

≈ 570R: ADJUST FOR ZERO SIGNAL AT 'Q' OFF LOAD AND AT 50% MAX OUTPUT

DC TO DC CONVERTERS

DRM58 input 10-40vdc output 5v 8A £15
DRM128 input 17-40vdc output 12v 8A £50
DRM158 input 20-40vdc output 15v 8A £50
DRM248 input 29-40vdc output 24v 8A £40
DRS123 input 17-40vdc output 12v 3A £20
DRS153 input 20-40vdc output 15v 3A £20
DRS243 input 29-40vdc output 24v 3A £15

SOLID STATE RELAYS

CMP-DC-200P 3-32vdc operation, 0-200vdc 1A £2.50
SMT20000/3 3-24vdc operation, 28-280vac 3A £4.50
SMT20000/4 3-24vdc operation, 28-280vac 4A £5.00
ZRA6025F 28-280vdc/ac operation, 28-280vac 25A £7.00

200 WATT INVERTERS Nicely cased units 12v input 240v output 150watt continuous, 200 max. £49 ref LOT62.

6.8MW HELIUM NEON LASERS New units, £65 ref LOT33

COIN SLOT TOKENS You may have a use for these? mixed bag of 100 tokens £10 ref LOT20.

PORTABLE X RAY MACHINE PLANS Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £6/set. Ref F/XP1.

TELEKINETIC ENHANCER PLANS Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks yet produces positive motion and effect. Excellent for science projects, magic shows, party demonstrations or serious research & development of this strange and amazing psychic phenomenon. £4/set Ref F/TK1.

ELECTRONIC HYPNOSIS PLANS & DATA This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc only, by those experienced in its use. £15/set. Ref F/EH2.

GRAVITY GENERATOR PLANS This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of simple materials and without any visible means - cause it to levitate. £10/set Ref F/GRA1.

WORLDS SMALLEST TESLA COIL/LIGHTENING DISPLAY GLOBE PLANS Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects, 'Plasma in a jar', St Elmo's fire, Corona, excellent science project or conversation piece. £5/set Ref F/BTC1/LG5.

COPPER VAPOUR LASER PLANS Produces 100mw of visible green light. High coherency and spectral quality similar to Argon laser but easier and less costly to build yet far more efficient. This particular design was developed at the Atomic Energy Commission of NEGEV in Israel. £10/set Ref F/CVL1.

VOICE SCRAMBLER PLANS Miniature solid state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £6/set Ref F/VS9.

PULSED TV JOKER PLANS Little hand held device utilises pulse techniques that will completely disrupt TV picture and sound! Works on FM too! DISCRETION ADVISED. £8/set Ref F/TJ5.

BODYHEAT TELESCOPE PLANS Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hotspots, heat leaks etc. Intended for security, law enforcement, research and development, etc. Excellent security device or very interesting science project £8/set Ref F/BHT1.

BURNING, CUTTING CO2 LASER PLANS Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may very well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is easily applicable to burning and etching wood, cutting, plastics, textiles etc £12/set Ref F/LC7.

MYSTERY ANTI GRAVITY DEVICE PLANS Uses simple concept. Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or science project. £6/set Ref F/ANT1K.

ULTRASONIC BLASTER PLANS Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquids. Many cleaning uses for PC boards, jewellery, coins, small parts etc. £6/set Ref F/ULB1.

ULTRA HIGH GAIN AMP/STETHOSCOPIC/MIKE/SOUND AND VIBRATION DETECTOR PLANS Ultrasensitive device enables one to hear a whole new world of sounds. Listen through walls, windows, floors etc. Many applications shown, from law enforcement, nature listening, medical heartbeat, to mechanical devices. £6/set Ref F/HGA7.

ANTI DOG FORCE FIELD PLANS Highly effective circuit produces time variable pulses of acoustical energy that dogs cannot tolerate £6/set Ref F/DOG2.

LASER BOUNCE LISTENER SYSTEM PLANS Allows you to hear sounds from a premises without gaining access. £12/set Ref F/LLIST1.

LASER LIGHT SHOW PLANS Do it yourself plans show three methods. £6 Ref F/LLS1.

PHASOR BLAST WAVE PISTOL SERIES PLANS Handheld, has large transducer and battery capacity with external controls. £6/set Ref F/PSP4.

INFINITY TRANSMITTER PLANS Telephone line grabber/room monitor. The ultimate in home/office security and safety! simple to use! Call your home or office phone, push a secret tone on your telephone to access either: A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. £7 Ref F/TELEGRAB.

BUG DETECTOR PLANS Is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Sniffs out and finds bugs and other sources of bothersome

WOLVERHAMPTON BRANCH NOW OPEN AT WORCESTER ST W'HAMPTON TEL 01902 22039

Interference. Detects low, high and UHF frequencies. £5/set Ref F/BD1.

ELECTROMAGNETIC GUN PLANS Projects a metal object a considerable distance requires adult supervision £5 ref F/EML2.

ELECTRIC MAN PLANS, SHOCK PEOPLE WITH THE TOUCH OF YOUR HAND! £5/set Ref F/EMA1.

PARABOLIC DISH MICROPHONE PLANS Listen to distant sounds and voices, open windows, sound sources in 'hard to get or hostile premises. Uses satellite technology to gather distant sounds and focus them to our ultra sensitive electronics. Plans also show an optional wireless link system. £8/set ref F/PM5.

2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND HIGH DC VOLTAGE, SOLID STATE TESLA COIL AND VARIABLE 100,000 VDC OUTPUT GENERATOR PLANS Operates on 9-12vdc, many possible experiments. £10 Ref F/HM7/TCL4.

INFINITY TRANSMITTERS The ultimate 'bug' fits to any phone or line, undetectable, listen to the conversations in the room from anywhere in the world! 24 hours a day 7 days a week! just call the number and press a button on the mini controller (supplied) and you can hear everything! Monitor conversations for as long as you choose £249 each, complete with leads and mini controller! Ref LOT9. Undetectable with normal RF detectors, fitted in seconds, no batteries required, lasts forever!

SWITCHED MODE PSU'S 244 watt, +5 32A, +12 6A, -5 0.2A, -12 0.2A. There is also an optional 3.3v 25A rail available. 120/240v I/P. Cased, 175x90x145mm. IEC inlet Suitable for PC use (6 d/drive connectors 1 m/board). £10 ref PSU1.

VIDEO PROCESSOR UNITS 7/6V 10AH BATT/12V 8A TX Not too sure what the function of these units is but they certainly make good snippers! Measures 390x320x120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connections on the rear. Inside 2x6v 10AH sealed lead acid batts, pcb's and a 8A? 12v toroidal transformer (mains in). Condition not known, may have one or two broken knobs due to poor storage. £17.50 ref VP2.

RETRON NIGHT SIGHT Recognition of a standing man at 300m in 1/4 moonlight, hematocally sealed, runs on 2 AA batteries, 80mm F1.5 lens, 20mw infrared laser included. £325 ref RETRON.

MINI FM TRANSMITTER KIT Very high gain preamp, supplied complete with FET electret microphone. Designed to cover 88-108 Mhz but easily changed to cover 63-130 Mhz. Works with a common 9v (PP3) battery. 0.2W RF. £7 Ref 1001.

3-30V POWER SUPPLY KIT Variable, stabilized power supply for lab use. Short circuit protected, suitable for professional or amateur use 24v 3A transformer is needed to complete the kit. £14 Ref 1007.

1 WATT FM TRANSMITTER KIT Supplied with piezo electric mic. 8-30vdc. At 25-30v you will get nearly 2 watts! £12 ref 1009.

FM/AM SCANNER KIT Well not quite, you have to turn the knob your self but you will hear things on this radio that you would not hear on an ordinary radio (even TV). Covers 50-160mhz on both AM and FM. Built in 5 watt amplifier, inc speaker. £15 ref 1013.

3 CHANNEL SOUND TO LIGHT KIT Wireless system, mains operated, separate sensitivity adjustment for each channel, 1,200 w power handling, microphone included. £14 Ref 1014.

4 WATT FM TRANSMITTER KIT Small but powerful FM transmitter, 3 RF stages, microphone and audio preamp included. £20 Ref 1028.

STROBE LIGHT KIT Adjustable from 1-60 hz (a lot faster than conventional strobes). Mains operated. £16 Ref 1037.

COMBINATION LOCK KIT 9key, programmable, complete with keypad, will switch 2A mains. 9v dc operation. £10 ref 1114.

PHONE BUG DETECTOR KIT This device will warn you if somebody is eavesdropping on your line. £6 ref 1130.

ROBOT VOICE KIT Interesting circuit that distorts your voice! adjustable, answer the phone with a different voice! £2vdc £9 ref 1131

TELEPHONE BUG KIT Small bug powered by the 'phone line, starts transmitting as soon as the phone is picked up! £8 Ref 1135.

3 CHANNEL LIGHT CHASER KIT 800 watts per channel, speed and direction control supplied with 12 LEDs (you can fit tracs instead to make kit mains, not supplied) 9-12vdc £17 ref 1026.

12V FLOURESCENT LAMP DRIVER KIT Light up 4 foot tubes from your car battery! 9v 2A transformer also required. £8 ref 1069.

VOX SWITCH KIT Sound activated switch ideal for making bugging tape recorders etc. adjustable sensitivity. £8 ref 1073.

*SOME OF OUR PRODUCTS MAY BE UNLICENSEABLE IN THE UK

BULL ELECTRICAL
250 PORTLAND ROAD, HOVE, SUSSEX.
BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE
WITH ORDER PLUS £3 P&P PLUS VAT.
PLEASE ALLOW 7-10 DAYS FOR DELIVERY PHONE ORDERS
WELCOME (ACCESS VISA, SWITCH, AMERICAN EXPRESS)
TEL: 01273 203500
FAX: 01273 323077
E-mail bull@pavillon.co.uk

WE BUY SURPLUS STOCK

FOR CASH
BUYERS DIRECT LINE 0802 660377

FREE CATALOGUE

100 PAGE CATALOGUE NOW

AVAILABLE, 45P STAMPS.

SOUND EFFECTS GENERATOR KIT Produces sounds ranging from bird chirps to sirens. Complete with speaker, add sound effects to your projects for just £9 ref 1045.

16 WATT FM TRANSMITTER (BUILT) 4 stage high power, preamp required 12-18vdc, can use ground plane, yaqi or open dipole. £69 ref 1021.

HUMIDITY METER KIT Builds into a precision LCD humidity meter, 9ic design, pcb, lcd display and all components included. £29

PC TIMER KIT Four channel output controlled by your PC, will switch high current mains with relays (supplied). Software supplied so you can program the channels to do what you want whenever you want. Minimum system configuration is 286, VGA, 4.1, 640k, serial port, hard drive with min 100k free. £24.99

FM CORDLESS MICROPHONE This unit is an FM broadcasting station in miniature, 3 transistor transmitter with electret condenser mic + fet amp design result in maximum sensitivity and broad frequency response. 90-105mhz, 50-15000hz, 500 foot range in open country! PP3 battery required. £15.00 ref 15P42A.

MAGNETIC MARBLES They have been around for a number of years but still give rise to curiosity and amazement. A pack of 12 is just £3.99 ref G/IR20

NICKEL PLATING KIT Professional electroplating kit that will transform rusting parts into showpieces in 3 hours! Will plate onto steel, iron, bronze, gunmetal, copper, welded, silver soldered or brazed joints. Kit includes enough to plate 1,000 sq inches. You will also need a 12v supply, a container and 2 12v light bulbs. £39.99 ref NIK39.

Miniature adjustable timers, 4 pole c/o output 3A 240v, HY1230S, 12vdc adjustable from 0-30 secs. £4.99
HY1260M, 12vdc adjustable from 0-60 mins. £4.99
HY2405S, 240v adjustable from 0-5 secs. £4.99
HY24060M, 240v adjustable from 0-60 mins. £6.99

BUGGING TAPE RECORDER Small voice activated recorder, uses micro cassette complete with headphones. £28.99 ref MAR29P1.

POWER SUPPLY fully cased with mains and o/p leads 17v DC 900mA output. Bargain price £5.99 ref MAG6P9

9v DC POWER SUPPLY Standard plug in type 150ma 9v DC with lead and DC power plug, price for two is £2.99 ref AUG3P4.

COMPOSITE VIDEO KIT. Converts composite video into separate H sync, V sync, and video, 12v DC. £8.00 REF: MAG8P2.

FUTURE PC POWER SUPPLIES These are 295x135x60mm, 4 drive connectors 1 mother board connector, 150watt, 12v fan, iec inlet and on/off switch. £12 Ref EF6.

VENUS FLYTRAP KIT Grow your own carnivorous plant with this simple kit £3 ref EF34.

6"x12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA Bargain price just £5.99 ea REF: MAG6P12.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG6P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

ROCK LIGHTS Unusual things these, two pieces of rock that glow when rubbed together believed to cause rain! £3 a pair Ref EF29.

3' by 1' AMORPHOUS SOLAR PANELS 14.5v, 700mA 10 watts, aluminium frame, screw terminals. £44.95 ref MAG45.

ELECTRONIC ACCUPUNCTURE KIT Builds into an electronic version instead of needles good to experiment with. £7 ref 7P30

SHOCKING COIL KIT Build this little battery operated device into all sorts of things, also gets worms out of the ground! £7 ref 7P36.

FLYING PARROTS Easily assembled kit that builds a parrot that actually flaps its wings and flies! 50 m range £6 ref EF2.

HIGH POWER CATAPULTS Hinged arm brace for stability, tempered steel yoke, spring strength latex power bands. Departure speed of ammunition is in excess of 200 miles per hour! Range of over 200 metres! £7.99 ref R9.

BALLON MANUFACTURING KIT British made, small blob blows into a large, longlasting balloon, hours of fun! £3.99 ref G/IE99R

9-0-9V 4A TRANSFORMERS, chassis mount. £7 ref LOT19A

2.5 KILOWATT INVERTERS, Packed with batteries etc but as they weigh about 100kg CALLERS ONLY! £120.

MEGA LED DISPLAYS Build your self a clock or something with these mega 7 seg displays 55mm high, 38mm wide. 5 on a pcb for just £4.99 ref LOT16 or a bumper pack of 50 displays for just £29 ref LOT17.

CLEARANCE SECTION, MINIMUM ORDER £15, NO TECHNICAL DETAILS AVAILABLE, NO RETURNS, TRADE WELCOME.

2000 RESISTORS ON A REEL (SAME VALUE) 99P REF BAR340
AT LEAST 200 CAPACITORS (SAME VALUE) 99P REF BAR342

INFRA RED REMOTE CONTROLS JUST 99P REF BAR333

CIRCUIT BREAKERS, OUR CHOICE TO CLEAR 99P REF BAR335

MICROWAVE CONTROL PANELS TO CLEAR £2 REF BAR 329

2 TUBES OF CHIPS (2 TYPES OUR CHOICE) 90P REF BAR305

LOTTERY PREDICTOR MACHINE!! JUST £1.50 REF BAR313

HELLA/ROVER ELECTRIC HILAMP LEVELLER £2 REF BAR311

SINCLAIR C5 18" TYRES TO CLEAR AT JUST 75P REF BAR318

LARGE MAINS MOTORS (NEW) TO CLEAR AT 75P REF BAR310

MODEMS ETC FOR STRIPPING £2.50 EACH REF BAR324

110V LARGE MOTORS (NEW) TO CLEAR AT 50P REF BAR332

MODULATOR UNITS UNKNOWN SPEC JUST 50P REF BAR323

GX4000 GAMES COLOSLES JUST £4 REF BAR320

SMART CASED MEMORY STORAGE DEVICE, LOADS OF BITS INSIDE, PCB, MOTOR, CASE ETC. BUMPER PACK OF 5 COMPLETE UNITS TO CLEAR AT £2.50(FOR 5) REF BAR 330.

2 CORE MAINS CABLE 2M LENGTHS PACK OF 4 £1 REF BAR337

PC USER/BASIC MANUALS, LOADS OF INFO. £1 REF BAR304

PCB STRIPPERS TO CLEAR AT 2 FOR 99P REF BAR341

3 M 3 CORE MAINS CABLE AND 13A PLUG. 60P REF BAR325

CLASSIFIED

TEL 0181 652 3620

FAX 0181 652 8956

ARTICLES FOR SALE



SUPPLIER OF QUALITY USED TEST INSTRUMENTS



CONTACT


Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham,
Bognor Regis, West Sussex, PO22 0EB, U.K.
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

CIRCLE NO. 150 ON REPLY CARD



OPERATING & SERVICE MANUALS

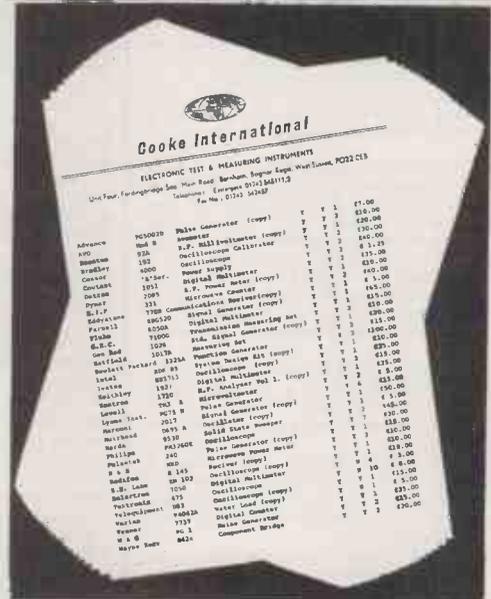

CONTACT

Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham,
Bognor Regis, West Sussex, PO22 0EB, U.K.
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

CIRCLE NO. 151 ON REPLY CARD

Consider

Your costs to continue to stock
UNWANTED SURPLUS . . . EXCESS . . . OBSOLETE
STOCKS OF:-
ELECTRONIC-ELECTRICAL COMPONENTS &
ACCESSORIES

RELEASE
for
PAYMENT IN ADVANCE
OF COLLECTION
contact

K.B. Components,
21 Playle Chase, Gt. Totham, Maldon, Essex, CM9 8UT
Tel:- 01621 893204 Fax:- 01621 893180 Mobile:- 0802 392745

REGISTER TO RECEIVE MONTHLY PUBLISHED STOCK LISTS AT NO CHARGE OF ALL EXISTING NEW, UNUSED, STOCKS OF ALL COMPONENTS AND ACCESSORIES.

TEKTRONIX 465B, 100Mhz Dual delay scope/Probes/Manuals, £375. MARCONI TF2331, Distortion Analyzer/Manuals, £195. Phone lan at work on 01256 841300, ext. 248.

HP59306A RELAY ACTUATOR, HP59313A A/D, HP59303A D/A, HP8750A, HP8709A, HP8418A, IEEE leads, £50 each. Time Electronics current calibrator, £150. Tel: 01273 707346.

WANTED, SOFTWARE AND INFO for PC-Labcard type PCL-712E analogue interface card. Tel: Peter Gascoyne 01235 868695.

SMALL SELECTION of Aircraft Starter motors, DC generators and rotary converters. Possibly suit electric vehicles etc. £10 to £50 depending on condition and type. Tel: Bristol 01179 793883.

FIRST THOUGHTS

INNOVATION AND SPECULATION IN ELECTRONICS AND PHYSICS

First Issue Only 60p inc. P&P (UK)

Includes: A 'zero distortion' amplifier, linear-phase crossover filters, relativity and acceleration, passive alarm controller, problems in e.m. theory, and more. Send 60p cheque or PO, payable to M. J. Renardson, 13, Spring Grove, Hull, HU3 1JZ, England. (80p or 2 IRCs to Europe, £1.50 or 4 IRCs to rest of world.)

- Farnel 60MHz DTV60 Oscilloscope . . . £345
- B/Star M1000 1GHz Freze/Counter . . . £85
- B/Star J2000 0.1 Hz-2MHz Sig/Gen . . . £85
- RS 610-461 30V/2A Digital FS £95
- RS208-541 0-275V/2A Variac £95
- Haplin Gold 100KHz-450MHz Sig/Gen . . £65
- Haplin Gold 10Hz-100KHz Sig/Gen . . . £48
- Weller PS20 + TCP24 PS + Iron + Stand £38
- Farnel 501-529 Fume Extractor £35
- RS 424-658 IC Leg Former £18
- RS 607-134 Axia² Lead Ben/Cutter . . . £195
- Groatmoor Radial Lead Cutter £445
- Eclipse Automatic Wire Cutter £345
- Eclipse Rotary Wire Stripper + Dies . . . £235
- Sartorius 0-2kg Component Counter . . £245

ALL GOOD CONDITION
Tel: 01722 326649

ARTICLES WANTED

TOP PRICES PAID

For all your valves, tubes, semi conductors and IC's.

Langrex Supplies Limited
1 Mayo Road, Croydon
Surrey CR0 2QP

TEL: 0181-684 1166
FAX: 0181-684 3056

RECRUITMENT



MINISTRY OF DEFENCE ASSISTANT TELECOMMUNICATIONS TECHNICAL OFFICER (ATTO)

Royal Air Force Sealand is Europe's premier electronic repair facility. We have vacancies for Assistant Telecommunications Technical Officers for permanent positions.

In addition to RAF Sealand based posts some successful candidates will need to spend time at RAF North Luffenham, Leics, on detached duty effective from their start date until Autumn '97 to receive training before the work is transferred to Sealand.

An ability to work at heights of 12 metres or more is a requirement, however, a short training course is available. Many of the North Luffenham jobs also involve regular duty travel both within Great Britain and abroad attracting the usual departmental allowances.

The ATTO grade is part of the Defence Engineering and Science Group within the Ministry of Defence and is primarily concerned with aspects of repair and maintenance of aircraft avionics and electronics, and Ground Radio Support Services.

QUALIFICATIONS

An EC approved Eng Tech qualification at Stage 1 in an appropriate electronics or telecommunications specialism or equivalent, plus 3 years recent relevant experience which may include a period of study/training.

or

BTEC/SCOTVET NC in Electronics or Telecommunications plus 3 years recent relevant experience which may include a period of study/training.

Selected applicants will be required to take an aptitude test.

The aptitude test has been upgraded and previous applicants are welcome to re-apply.

SALARY

The salary ranges from £12,865 pa to £16,168 pa with starting salary being determined by experience. The grade maximum is £19,477. The range between £16,168 and £19,477 must be attained through performance in the grade.

GENERAL

The Civil Service is an Equal Opportunities Employer.

A 'No Smoking In Work Areas' policy is in force at RAF Sealand.

HOW TO APPLY

For an application form and further details please send a large stamped addressed envelope to:

Manning and Recruitment/ATTO

No. 30 MU

RAF Sealand

Deeside

Flintshire CH5 2LS.

The last date for sending out application forms is 22 November, 1996.



ARTICLES WANTED

WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap and quantity.

Prompt service and cash.

M & B RADIO

86 Bishopgate Street

Leeds LS1 4BB

Tel: 0113 2435649

Fax: 0113 2426881

WANTED

TOP PRICES PAID

For all your Test Equipment, Receivers, Transmitters etc. Factory Clearance, Prompt Service and Payment.

HTB ELEKTRONIK

Alter Apeler Weg 5

27619 Schiffdorf, Germany

Tel: 0049 4706 7044

Fax: 0049 4706 7049

★★WANTED★★

Test equipment, Electronic Scrap, Valves, Transmitters/Receivers, Factory & Warehouse Clearance. Confidentiality Assured.

TELFORD ELECTRONICS

Phone: 01952 605451

Fax: 01952 677978

ELECTRONICS ENGINEER

Qualified Engineer required, with proven design experience in HF & VHF communications equipment, especially receivers. Ability to combine software and hardware expertise advantageously.

An exceptional opportunity for the selected candidate, who will be in at the start of a new venture, future prospects being limited only by the individual's success.

The candidate will push a product design from the 'A' model through to production with minimal support, therefore a high level of commitment and expertise is required.

A generous salary commensurate with experience is available.

Location: Sussex

Please reply in writing to:

Box No. 300, Electronics World, Room L329, Quadrant House,
The Quadrant, Sutton, Surrey SM2 5AS

VALVES, and CRTs AVAILABLE

ONE MILLION VALVES stocked for Audio, Receiving, Transmitting & RF Heating. Rare brands such as Mullard & GEC available. Also MAGNETRONS, KLYSTRONS, CRTs and SOCKETS.

Large stocks of Russian & Sovtek items.

Please ask for our free catalogues of valves or CRTs.

VALVES, etc. WANTED

Most types considered but especially KT88 (£48), PX4/PX25 (£50), KT66 (£35), KT77 (£15), EL34 (£10), EL37 (£9), ECC83 (£3).

Valves must be UK manufacture to achieve prices mentioned.

Also various valve-era equipment e.g. Garrard 301, (up to) £80.

Ask for a free copy of our wanted List.

BILLINGTON EXPORT LTD., Billingshurst, Sussex RH14 9EZ.

Tel: 01403 784961 Fax: 01403 783519

VISITORS STRICTLY BY APPOINTMENT.

MINIMUM ORDER £50 plus VAT

WE WANT TO BUY!!
IN VIEW OF THE EXTREMELY
RAPID CHANGE TAKING PLACE
IN THE ELECTRONICS
INDUSTRY, LARGE QUANTITIES
OF COMPONENTS BECOME
REDUNDANT. WE ARE CASH
PURCHASERS OF SUCH
MATERIALS AND WOULD
APPRECIATE A TELEPHONE
CALL OR A LIST IF AVAILABLE.
WE PAY TOP PRICES AND
COLLECT.

R. HENSON LTD.

21 Lodge Lane, N.Finchley,
London N12 8JG.

5 Mins, from Tally Ho Corner.

TELEPHONE

0181-445-2713/0749

FAX 0181-445-5702

SPECTRUM ANALYSERS



ANRITSU MS420J 10Hz-30MHz network/spectrum analyser £5000
AVCOM - portable, battery operated, to 1000MHz £2000

TEKTRONIX 492 21GHz portable spectrum analyser, with options 1, 2 and 3 £6500 or £7500 with multiplexor and mixers to 40GHz
HP8711A 300kHz-1.3GHz network analyser £4000
HP8753A vector network analyser, 3GHz £7500
HP8702B lightwave component analyser (options 006/011) 6GHz £10000
HP8559A/182T 21GHz £4500
HP8557A/182T 350MHz £1500
HP8590A 1.8GHz portable, RS232 option £4250

MARCONI INSTRUMENTS



2018 synthesized AM/FM signal generator 80kHz-520MHz £1250
2019 synthesized AM/FM signal gen 80kHz-1040MHz £2000
2305 modulation meter £2500
2828A/2829 digital simulator/analyser £500
2955 radio communications test set £3250
6460/6421 power meter & sensor 10MHz-12.4GHz £350
65xx waveguide detector for use with 6501/2-scalar analysers £350
TF2910 TV Interval timer £250

ralfe electronics exclusively professional T&M

• 36 Eastcote Lane • South Harrow • Middx HA2 8DB • England •
TEL (+44) 0181-422 3593 • FAX (+44) 0181-423 4009

EST
41
YRS



DISTRIBUZIONE E ASSISTENZA, ITALY: TLC RADIO, ROMA (06) 871 90254

TEST EQUIPMENT

ADRET 740A synthesized signal generator 0.1-1120MHz £2500
ANRITSU MS420J network/spectrum analyser 10Hz-30MHz £500
BRUEL & KJAER 2307 level recorder £1000
BRUEL & KJAER 2308 analogue X-Y pen recorder £750
CHASE LFR1000 interference measuring receiver 9kHz-150kHz £1000
DATRON 1061 & 1061A - various, digital multimeter & 1065 - call from £500
DATRON 1065 digital multimeter all ranges plus IEEE £500
FARNELL SSG2000 synthesized signal generator 10Hz-2000MHz £2500



ISO9002 ACCREDITED STOCKIST MEASUREMENT & TEST EQUIPMENT

PHILIPS PM5167 1mHz-10MHz function generator £275
RACAL-DANA 9300 milli-voltmeter £400
RACAL-DANA 9301A true RMS RF milli-voltmeter £350
SCHLUMBERGER 7081 precision voltmeter 8.5 digits £2750
TEKTRONIX P6201 FET PROBE £350
WANDEL & GOLTERMANN WM30 level tracer £500
WANDEL & GOLTERMANN PJM-4S jitter meter for SONET & SDH £5500
WAVETEK 23 synthesized function generator 0.01Hz-12MHz £1250
WAVETEK 1067 opt 522 1-500MHz sweep generator £500
WAYNE KERR 3220 20A bias unit (for 3245 inductance analyser) £1250
TEKTRONIX AM503/P6303 current probe £1500

HEWLETT PACKARD



1640B serial data generator £500
3764A digital transmission analyser £1500
3335A synthesizer/level generator £2000
3235A switch/test unit £1000
3324A synthesized function generator £2000
33320G/33322G programmable attenuators 4GHz, with driver 11713A £1000
As above but 18GHz set £1500
3581C selective voltmeter £1250
3779D primary multiplex analyser £5000
3790D signalling test set with 2 x 37915A interface cards £5500
4140B pA/meter, DC voltage source £4000
4272A multi-frequency Icr meter £3500
435B microwave power meter, analogue £400
5386A 3GHz frequency counter £1500
54100A 1GHz digitizing oscilloscope, now inc 2 x 1GHz active probes £2000
54502A digital oscilloscope 400MHz 400MSa/s £2500
8007B pulse generator 100MHz £950
8018A serial data generator £1000
8082A pulse generator 250MHz £2000
8111A pulse generator 20MHz £1250
8146A optical tdr, with options 2/3/plug-in 81465SH (single-mode) £8500
816A slotted line 1.8-18GHz with 809C & 447B probe £500
8444A tracking generator with option 059 £1000
86222A/8620C 10MHz-2.4GHz sweep generator £2000
87510A gain-phase analyser 100kHz-300MHz £6500
8753A 3GHz vector network analyser £7500
J2215A FDDI portable multimode test set £1500
J2219A 486-based, colour option main-frame £1000
J2219A/J2171A 486-based colour screen option network advisor £3000

SEND FOR LATEST STOCK LIST. WE FAX LISTS AND SHIP WORLDWIDE. ALL FULLY LAB-TESTED AND NO-QUIBBLE GUARANTEED

CIRCLE NO. 154 ON REPLY CARD

ELECTRONIC UPDATE

Contact Malcolm Wells on
0181-652 3620

A regular advertising feature enabling
readers to obtain more information
on companies' products or services.

New Flight Electronics International Catalogue Set

You now have access to the world's latest:

- ★ Electronics Training Equipment
- ★ Microprocessor Training Equipment
- ★ Test and Measurement Equipment
- ★ PC Cards

via "Flight's" latest catalogue set.

We are specialists in the provision of innovative top quality electronics trainers, breadboards, test and measurement, PC cards and microprocessor evaluation equipment.

Our extensive range covers every need, call today for your free catalogue set.

CIRCLE NO. 155 ON REPLY CARD

LabVIEW 4.0 Brochure.

LabVIEW Graphical Programming for Instrumentation, illustrates how users can increase productivity and save money by using LabVIEW to build virtual Instrumentation systems. The brochure includes examples of real-world test and measurement, process monitoring and control applications developed with LabVIEW.

NATIONAL INSTRUMENTS, For your FREE brochure call 01635 523545

CIRCLE NO. 156 ON REPLY CARD

NEW Feedback T&M Catalogue

The latest edition of the Feedback Test & Measurement catalogue is now available. Over 60 pages packed with more than 800 products divided into over 20 sections. The catalogue is indexed for both product and manufacturer and is fully illustrated. Whether you are looking for an individual product, a complete workstation, or a solution to a particular Test & Measurement need the NEW Feedback catalogue will solve your problems, send for a copy NOW!

CIRCLE NO. 157 ON REPLY CARD

NEW JENSEN TOOLS CATALOGUE

Colourful new Catalogue, hot off the press from Jensen Tools, presents unique new tool kits for service/support of communications equipment. Also latest test equipment from many major manufacturers. Includes hard-to-find tools, PC/LAN diagnostics, bench accessories, static control, technical manuals and more.

Ring 0800 833246 or Fax 01604 785573 for a free copy.

Jensen Tools, 10-12 Ravens Way, Northampton NN3 9UD

CIRCLE NO. 158 ON REPLY CARD

8051 MICROCONTROLLERS + FLASH

MICRO-PRO 51

State-of-the-art programmer for the 8051 family

- Programming support for the entire Atmel 89C and 89S microcontroller families
- Also supports many Philips, Intel, Dallas & Siemens 8051 derivatives
- Field programmable hardware ensure future device support

Order code: MP51-SYS £125.00

Products are now available from Farnell Components

Microcontroller in-circuit re-programming adaptor

Now you can re-program the entire Atmel microcontroller family in-circuit!

No more re-moving chips - ideal for 8051 single-chip project development.

Supplied with AT89C2051 and AT89C52 + 11.0592 MHz Crystal.

(Requires Micro-Pro 51 programmer to operate - see above)


Order code: AD-MICRO-ICR £125.00

Package Adaptors

PLCC 44-pin adaptor

Suitable for most 8051 derivatives

Order code: AD-PLCC44-A
£65.00

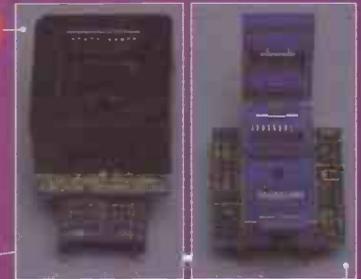

SOIC 20-pin adaptor

Suitable for Atmel AT89C1051 & AT89C2051


Order code: AD-SOIC20-A £75.00

Please enquire for our full range of adaptors

The ATMEL 8051 FLASH microcontroller family

| Atmel Part Code | 89C51 | 89LV51 | 89C52 | 89LV52 | 89C55 | 89S8252 | 89C2051 | 89C1051 |
|---------------------------|-------|--------|-------|--------|-------|---------|---------|---------|
| Flash Code ROM (bytes) | 4K | 4K | 8K | 8K | 20K | 8K | 2K | 1K |
| RAM (bytes) | 128 | 128 | 256 | 256 | 256 | 256 | 128 | 64 |
| EEPROM | - | - | - | - | - | 2K | - | - |
| In-system re-programmable | - | - | - | - | - | YES | - | - |
| I/O Pins | 32 | 32 | 32 | 32 | 32 | 32 | 15 | 15 |
| 16-bit Timer/Counters | 2 | 2 | 3 | 3 | 3 | 3 | 2 | 1 |
| Watchdog timer | - | - | - | - | - | YES | - | - |
| Interrupt sources | 6 | 6 | 8 | 8 | 8 | 9 | 6 | 3 |
| Serial UART (full duplex) | YES | YES | YES | YES | YES | YES | YES | - |
| SPI Interface | - | - | - | - | - | YES | - | - |
| Analogue comparator | - | - | - | - | - | - | YES | YES |
| Data pointers | 1 | 1 | 1 | 1 | 1 | 2 | 1 | 1 |
| Package Pins (DIL) | 40 | 40 | 40 | 40 | 40 | 40 | 20 | 20 |

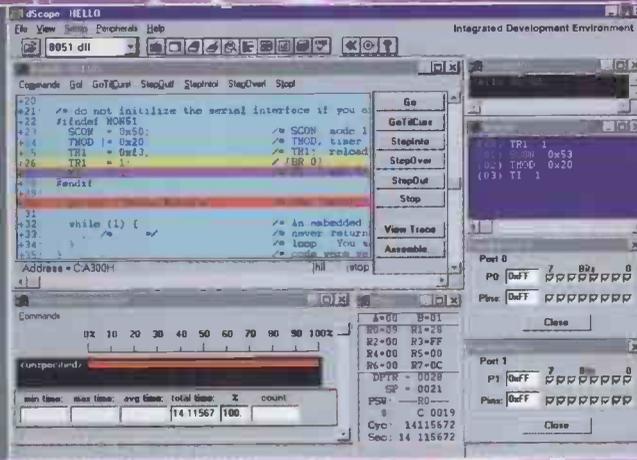- Atmel microcontrollers feature on-chip re-programmable FLASH code memory
- FLASH is electrically erasable in under 15ms (no need for UV eraser)
- 89C51/89C52 are drop-in FLASH replacements for the generic 87C51/87C52 devices
- 89C2051 is a single-chip 8051 in a 20 pin package - even retaining the serial port



C51 STARTER SYSTEM


- ✓ Optimising C Compiler
- ✓ Macro Assembler
- ✓ Software Simulator
- ✓ Device Programmer
- ✓ Sample Devices
- ✓ Hardware/Software Documentation

Plus
FREE Atmel CD ROM data book
* System supplied with 1 x Atmel AT89C1051 and 1 x AT89C2051 Microcontrollers
* C-compiler + Assembler output restricted to 2k total program code.

Order code: AT-89CX051-ST

Only £199.00

UPGRADE TO 8K VERSION NOW AVAILABLE

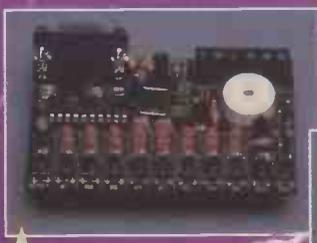

89C-1051/2051 Microcontroller Demo Module

A feature-packed evaluation module for the Atmel 20 pin derivatives. LED, WATCHDOG, RS-232, A/D, 4 digit 7 segment, Piezo speaker.

Order code: AT-89CX051-DEMO
£58.00



89C-1051/2051 Microcontroller OEM Module

An ideal OEM module which can be used for evaluation or can be designed into custom products. RS-232/485, 7k EPROM, A/D, I/O Header

Order code: AT-89CX051-OEM £29.00



The Embedded Solutions Company

Visit our web page at: www.equinox-tech.com

Email: sales@equinox-tech.com

229 Greenmount Lane, Bolton BL1 5JB UK




SALES: 01204 492010 TECHNICAL: 01204 491110 FAX: 01204 494883 (INTERNATIONAL DIALLING CODE +44 1204)

Equinox reserves the right to change prices & specifications of any of the above products without prior notice. P.O.E. All prices are exclusive of VAT and carriage

THE WORLD'S MOST POWERFUL, PORTABLE PROGRAMMERS

£495 + VAT

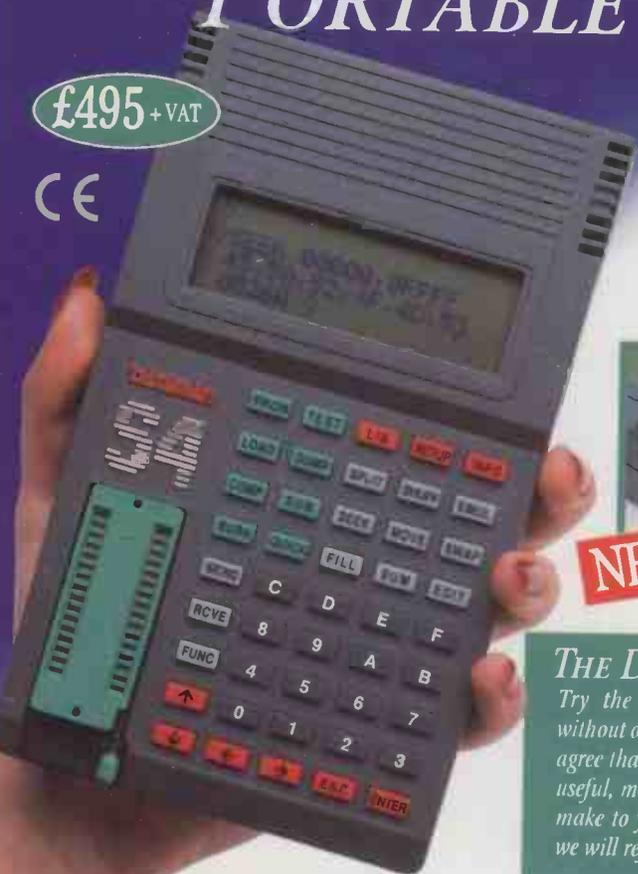

S4 GAL module

Programs a wide range of 20 and 24 pin logic devices from the major GAL vendors. Supports JEDEC files from all popular logic compilers.



NEW

THE DATAMAN CHALLENGE

Try the Dataman S4 or Dataman-48 without obligation for 30 days. If you do not agree that these are the most effective, most useful, most versatile additions you can make to your programming toolbox, we will refund your money in full.

The current device library contains over 1800 of the most popular logic and memory devices including GALs, PALs, CEPALs, RALs, 8 and 16-bit EPROMs, EEPROMs, PEROMs, FLASH, BOOT-BLOCK, BIPOLAR, MACH, FPGAs, PICs and many other Microcontrollers. We even include a 44-pin universal PLCC adaptor.

If you need to program different packaging styles, we stock adaptors for SOP, TSOP, QFP and SDIP. The Dataman-48 is also capable of emulation when used with memory emulation pods.

Order your Dataman programming solution today via our credit card hotline and receive it tomorrow. For more detailed information on these and other market leading programming products, call now and request your free copy of our new colour brochure.

Dataman S4

Compare the Dataman S4 with any other programmer and you'll see why it's the world's undisputed number one.

S4 is capable of programming 8 and 16-bit EPROMs, EEPROMs, PEROMs, 5 and 12V FLASH, Boot-Block FLASH, PICs, 8751 Microcontrollers and more. S4 also emulates ROM and RAM as standard!


S4 is the only truly hand held programmer that ships complete with all emulation leads, organiser-style manual, AC charger, spare library ROM, both DOS and Windows terminal software, and arrives fully charged and ready to go! Who else offers you all this plus a three year guarantee?

Customer support is second to none. The very latest programming library is always available free on the Internet, and on our dedicated bulletin boards. Customers NEVER pay for upgrades or technical support.

Dataman-48

Our new Dataman-48 programmer adds PinSmart® technology to provide true no-adaptor programming right up to 48-pin DIL devices. Dataman-48 connects straight to your PC's parallel port and works great with laptops. Coming complete with an integral world standard PSU, you can take this one-stop programming solution anywhere!

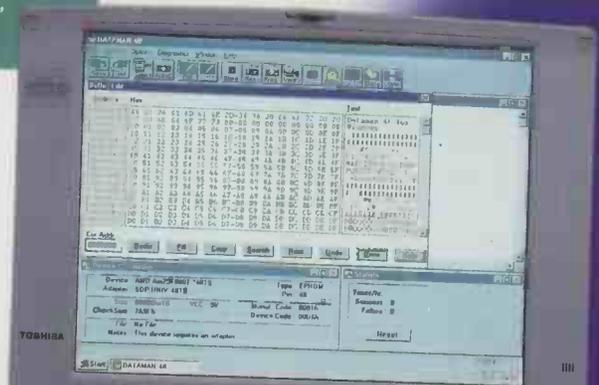As with S4, you get free software upgrades and technical support for life, so now you don't need to keep paying just to keep programming.



hotline
01300 320719

DATAMAN

£795 + VAT

Dataman Programmers Ltd, Station Road, Maiden Newton, Dorset DT2 0AE. UK
Telephone +44/0 1300 320719 Fax +44/0 1300 321012 BBS +44/0 1300 321095 (24hr)
Modem V.34/V.FC/V.32bis Home page: <http://www.dataman.com>
FTP: <ftp.dataman.com> Email: sales@dataman.com



Orders received by 4pm will normally be despatched same day.
Order today, get it tomorrow!

CIRCLE NO. 103 ON REPLY CARD