

Recruitment special: starts page 478

ELECTRONICS WORLD

INCORPORATING WIRELESS WORLD

Austria Asch. 70.00
Denmark DKr. 70.00
Germany DM 18.00
Greece Dra. 1400.00
Holland Dfl. 12.95
Italy L. 9400.00
Malta Lm. 1.80
IR £3.30
Singapore S\$7.50
Spain Pts. 925.00
USA \$6.75

A REED BUSINESS PUBLICATION
SOR DISTRIBUTION

JUNE 1999 £2.55

LW reference alarm clock

**Capacitor
quality meter**

**Efficient LED
torch**

**Novel sensor
enhancement
technique**

**Early effect
defined**

**New anti-jitter
idea**

**Unique offer: x1, x10 scope probes:
only £16 a pair**

ISSN 0959-8332



9 770959 833059

7362 DIFFERENT POWER SOLUTIONS DELIVERED IN THE LAST THREE MONTHS.

In the last three months we delivered more part numbers than any other power semi manufacturer did. Or could. Which means IR has more ways to meet your power needs from hundreds of distributor locations.

www.irf.com

SCHOTTKYS WITH THE LOWEST V_F .

It's a fact. IR has the lowest V_F Schottkys – from 1-400 amps, 15-150 volts, in surface mount, through-hole or powerful modules. More ways to optimize your design.

diodes.irf.com

MORE BENCHMARK MOSFETS THAN ANYONE.

There's a HEXFET® power MOSFET with benchmark performance from IR for nearly every application. Like the first power MOSFET chipset that meets Intel Mobile Guidelines '99. And there are thousands of others.

hexfet.irf.com

WORLD'S ONLY 1200V POWER ICs.

There's only one way to design 400VAC inverters with just one IC for the complete 3-phase gate drive. Only one way to cut component count and board space by more than 60% (the IR 2233). IR's got the only 1200V power IC family. And it's only one way we do more to meet your power IC needs.

pic.irf.com

THE WORLD'S FASTEST IGBTs.

With the world's lowest switching losses. So they're the world's first way to replace MOSFETs. And they're just part of the world's broadest line of IGBTs from International Rectifier.

igbt.irf.com

1499 PARTS TO SET MOTION CONTROL STANDARDS.

The highest density and current handling capability. With the widest selection of power packages for motion control. Driving motors from 1-100 HP. Get it right, right now with IR.

motor.irf.com

262 POWER PACKAGES.

Only IR gives you a choice of 262 different power package types. So you can find one that delivers exactly the footprint, current handling and the thermal performance you need.

packages.irf.com

BUT WAIT, THERE'S MORE POWER SEMICONDUCTOR EXPERTISE WHERE THAT CAME FROM.

Because you asked us for specific answers to your power design questions, we've answered with more power solutions. Solutions that offer more performance and reliability. Because we have more power semiconductor design and manufacturing experience and invest in more R&D. Over two times more.

Now it's time to do your part – visit our Web site today.

For a free copy of our CD-ROM iractive® call

+44 (0)1883 732 020.

For technical assistance call +44 (0)1883 733 309 or the Fax-on-Demand system on +44 (0)1883 733 420.

Available in UK from:
Abacus Polar
Arrow
Farnell
Future Electronics
RS Components
Solid State Supplies

International
IR Rectifier

www.irf.com

CIRCLE NO. 101 ON REPLY CARD


CONTENTS

443 COMMENT

What comes around...

445 NEWS

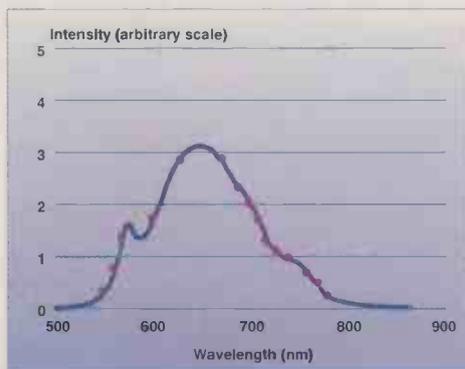- Strong pound is stifling industry
- Silicon LEDs show a promising light
- UK engineering skills shortage
- Young engineers are getting better off
- UK business costs are lowest
- Will FEDs replace plasma panels?



Researchers at Toshiba have for the first time managed to produce silicon LEDs operating below 5V, but quite how the light is being produced is a bit of a mystery. See page 445.

450 LW OFF-AIR REFERENCE CLOCK

Relying on Radio 4's often overlooked time reference on long wave, **Peter Topping's** precise alarm clock and calendar works anywhere in the UK without retuning.

458 IS THE BLOCKING OSCILLATOR DEAD?

Using an efficient LED-based torch as a design example, **Ian Hickman** demonstrates that the blocking oscillator still has its uses.

466 CIRCUIT IDEAS

- Hysteresis in a digital circuit
- Enhanced zener voltage regulator
- One-shot for microseconds to hours
- Accurate stopwatch measures to 0.01s
- Photographic flash meter

474 EARLY DEFINITION

Bryan Hart explains the Early effect – an important phenomenon not always well understood by analogue circuit designers.

480 WHO NEEDS A DEGREE?

Introducing our recruitment special, **Richard Wilson** shows that it is possible to succeed as an engineer without having a degree.

484 CHECKING C IN SITU

Cyril Bateman presents possibly the best ever general-purpose meter for checking electrolytic capacitors without removing them from the board.

493 SPEAKERS' CORNER

Why does the average 100W moving coil loudspeaker only delivers two or three watts of sound? **John Watkinson** explains.

499 ENHANCING SENSING

Joe Carr looks at an easy to apply and general-purpose technique for improving sensor resolution.

505 YAGIS

With the aid of a 300 Ω , 12-element design example, **Richard Formato** explains how high-impedance Yagis improve VHF antenna system performance.

511 NEW PRODUCTS


New product outlines, edited by **Richard Wilson**

516 JITTER BUSTER


Claimed to be at least as big a breakthrough as the PLL, this new anti-jitter technique does not suffer from recovery problems when its input frequency changes.

524 LETTERS

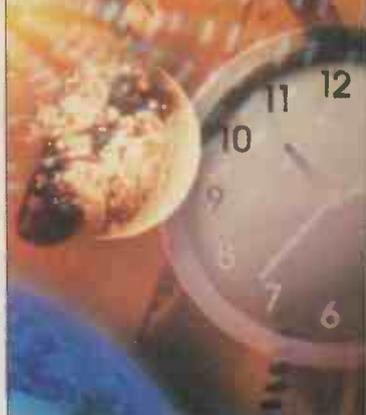
Crossover filters, Heater debate, New logic



Cover photography:
Mark Swallow

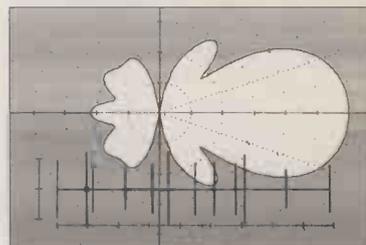

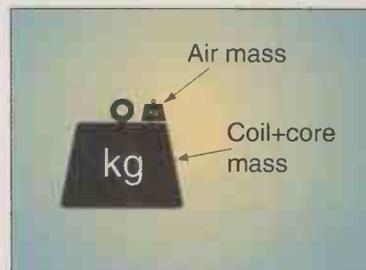Can a 300 Ω VHF antenna with open wire pair cable perform better than its low-impedance counterpart? **Richard Formato** shows that it can on page 505.



Why does the average 100W moving coil loudspeaker only deliver two or three watts of sound? **John Watkinson** explains why on page 493.

July issue on sale 27 May

SPECIAL OFFER


Unique reader offer – two switchable x1, x10 oscilloscope probes currently selling at £20 each are yours for only £21.74 a pair. See page 464.



PROTEUS

including **NEW SIMULATOR**

PRO SPICE 3F5

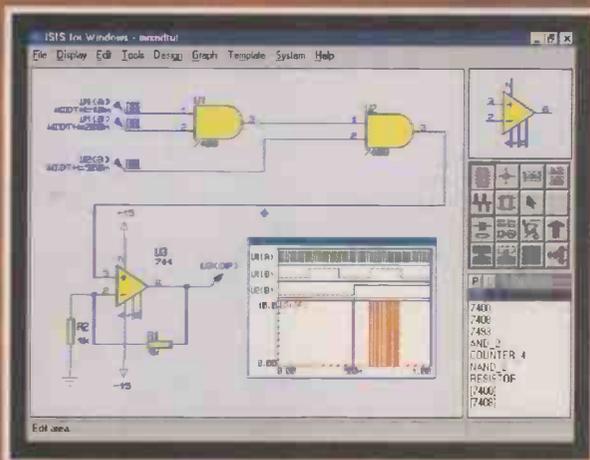

Simulation

- Berkeley SPICE3F5 analogue simulation kernel.
- True mixed mode simulation.
- New analysis types include multi-plot sweeps, transfer curves, distortion and impedance plots.
- Active Components: Switches, Pots etc.
- Over 1000 new library parts with SPICE models.
- Greater ease of use.

“a constant high level of capability throughout”

EWV CAD Review Round Up September 1998

Schematic Capture

- Produces attractive schematics like in the magazines.
- Netlist, Parts List & ERC reports
- Hierarchical Design.
- Full support for buses including bus pins.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and PCB design.

PCB Design

- Automatic Component Placement.
- Rip-Up & Retry Autorouter with tidy pass.
- Pinswap/Gateswap Optimizer & Back-Annotation.
- 32 bit high resolution database.
- Full DRC and Connectivity Checking.
- Shape based gridless power planes.
- Gerber and DXF Import capability.

Available in 5 levels - prices from £295 to £1625 + VAT.
Call now for further information & upgrade prices.

“the BEST all-round PROGRAM”

EWV CAD Review Round Up September 1998

labcenter
Electronics

Write, phone or fax for your free demo disk, or ask about our full evaluation kit.
Tel: 01756 753440. Fax: 01756 752857. EMAIL: info@labcenter.co.uk
53-55 Main St, Grassington. BD23 5AA. WWW: <http://www.labcenter.co.uk>

Fully interactive demo versions available for download from our WWW site.
Call for educational, multi-user and dealer pricing - new dealers always wanted.
Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.

EDITOR

Martin Eccles
0181 652 3614

CONSULTANTS

Ian Hickman
Philip Darrington
Frank Ogden

EDITORIAL ADMINISTRATION

Jackie Lowe
0181-652 3614

EDITORIAL E-MAIL ADDRESS

jackie.lowe@rbi.co.uk

ADVERTISEMENT MANAGER

Richard Napier
0181-652 3620

DISPLAY SALES EXECUTIVE

Joannah Cox
0181-652 3620

ADVERTISEMENT E-MAIL ADDRESS

joannah.cox@rbi.co.uk

ADVERTISING PRODUCTION

0181-652 3620

PUBLISHER

Mick Elliott

EDITORIAL FAX

0181-652 8111

CLASSIFIED FAX

0181-652 8938

NEWSTRADE ENQUIRIES

0171 261 7704

ISSN 0959-8332**SUBSCRIPTION HOTLINE**

01622 778000

SUBSCRIPTION QUERIES

rbp.subscriptions@rbi.co.uk
Tel 01444 445566
Fax 01444 445447

For a full listing of
RBI magazines:

<http://www.reedbusiness.com>

 REED
BUSINESS
INFORMATION

What goes around...

Who would ever think that the Japanese electronics majors would ever seek to model themselves on US and European companies? But they are.

It seems only yesterday that US and European companies were being urged to adopt the Japanese business model. In the mid-eighties, as kings of consumer electronics and semiconductors and bidding to overtake the Americans in computing, the Japanese electronics industry seemed unstoppable.

Japanese quality was a byword. Western businessmen were urged to adopt Japanese practices such as 'quality circles' and pre-competitive consortia. Western politicians abased themselves in pursuit of Japanese inward investment.

It was a period in which the Japanese expanded overseas and when Japanese restaurants, gardens and art galleries sprouted in the world's cities. That was a time of great self-confidence; now is a time of great self-doubt. The Japanese don't seem inclined to moderation.

The reason for the change is the huge corporate losses being recorded by the big companies, a depressed home market and a stock exchange which collapsed a decade ago and has stayed collapsed.

The most outward and visible symptom of change is the abandonment of the lifetime employment tradition. The week before last, Sony announced job losses of 17 500; the week before that NEC announced plans to lay off 15 000.

In a country with only four per cent unemployment, reducing blatantly overstuffed work-forces may seem acceptable. But in a country where social service provision for the unemployed is rudimentary, it could trigger social revolution. Behind-the-scenes, the companies are adopting Western accounting standards.

Broadly speaking these practices will promote transparency to allow the outside world to see how profitable, or not, companies are, how indebted or not they are, how much their assets are worth in current market value rather than book value, and how great are their liabilities for future retirement benefits and pensions.

In the boardroom, the accent is now on profits rather than on increasing turnover and market share. "To comply with global standards of management we have to focus on cash-flow," says Yoshihide Fujii, general manager of Toshiba's semiconductor business planning division, "Japanese companies now appreciate P&L more. To run the business more healthily we have learnt that P&L management is more important."



The new thinking of Japanese businessmen is towards seeking out new global opportunities, encouraging an entrepreneurial mind-set in their managements, and even thinking the previously unthinkable – takeovers and mergers.

The new chairman of NEC who took over on 26 March, Dr Hajime Sasaki, says: "We should be more transparent both internally and externally".

As well as adopting Western financial conventions Japan feels it has to accelerate its adoption of the new digital technologies – PCs, the Internet, LANs.

It seems surprising that, in the country that the world perceives as a high-tech stronghold, there is a feeling among the industrial elite that they have missed the digital bus.

"Japan is now lagging behind the direction in which the rest of the world is heading, especially in the digital revolution which has changed lifestyles," says Dr Tsugio Makimoto, Hitachi's Chief Corporate Technology Officer.

Language is another problem.

"In the US there are many start-up companies with good ideas using the digital revolution very effectively, particularly the Internet," says Makimoto, "such companies can do worldwide marketing via the Internet. That is a big change in favour of small companies."

"The way of management is changing because of e-mail and information flows which makes for flat organisations," he says. "But most of the Japanese industries have hierarchical, bureaucratic styles of management and it's very difficult to move them very quickly. So the digital revolution is making it very difficult for big companies in Japan."

What goes around comes around.

David Manners

Electronics World is published monthly. By post, current issue £2.45, back issues (if available) £3.00. Orders, payments and general correspondence to **L333, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS**. Tlx: 892984 REED BP G. Cheques should be made payable to Reed Business Information Ltd **Newstrade**: Distributed by Marketforce (UK) Ltd, 247 Tottenham Court Road London W1P 0AU 0171 261-5108.

Subscriptions: Quadrant Subscription Services, Oakfield House Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address. Subscription rates 1 year UK £36.00 2 years £58.00 3 years £72.00. Europe/Eu 1 year £51.00 2 years £82.00 3 years £103.00 ROW 1 year £61.00 2 years £98.00 3 years £123

Overseas advertising agents: France and Belgium: Pierre

Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel; (212) 679 8888 Fax; (212) 679 9455

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rahway NJ Postmaster. Send address changes to above.

Printed by Polestar (Carlisle) Ltd, Newtown Trading Estate Carlisle. Cumbria, CA2 7NR

Filmsetting by JJ Typographics Ltd, Unit 4 Baron Court, Chandlers Way, Southend-on-Sea, Essex SS2 5SE.

© Reed Business Information Ltd 1997 ISSN 0959 8332

UPDATE

Strong pound is stifling industry

The unusually high strength of the pound is making life difficult for the UK's electronics manufacturing industry, according to managers and industry bodies.

The Sterling Index, which gauges the relative strength of the UK's currency, reached 103.9 points – a six-month high – at the end of March.

"It has probably had a significant influence on us," said Jeffrey Davis, Viasystems' European president. "From our point of view it is a long term problem; we are not so much influenced by peaks and troughs."

The six month high, however, is part of a larger trend, said Elaine Barnett, an economic advisor at the Foundation for Manufacturing and Industry. "The Index was at 80 in January 1996, a 20 per cent rise is

quite a startling increase. [For electronics] I think there must be immense competition from Asia. The depreciation of their currencies could have an enormous detrimental impact on the electronics sector," she said.

What concerns the Federation of the Electronics Industry (FEI) is that when the pound is too strong, it curtails UK manufacturers' ability to take advantage of inherent strengths. "It can severely curtail manufacturing. The electronics industry operates on a global basis. International organisations are ready to move manufacturing from one place to another when this happens," said John Park, the FEI's deputy director general.

"We felt the Budget didn't address the strength of sterling. About 52 per cent of UK engineering [including

electronics] manufacturing is exported. If UK growth slowed down and European growth sped up, it would help the situation," said Barnett.

"When there is a problem with a currency, there is a trend to find continental based manufacturing," said Davis. "The PCB industry is complicated by the fact that a customer will approve only one or two plants. Generally it makes the PCB industry less flexible and it tends to hit harder."

Davis added: "Viasystems' main production assets are in the UK, about 65 to 70 per cent of our production. Therefore most of our production is influenced by the pound."

Alex Mayhew-Smith
Electronics Weekly

Silicon LEDs show a promising light – but why?

Exotic compound semiconductors have been needed to produce LEDs ever since General Electric used gallium arsenide (GaAs) to make the first practical one in 1962.

Since then, the materials and structures have become ever more complex. Today's LEDs often also include aluminium, nitrogen, indium and phosphorus and owe more to laser manufacture than to older LED processes.

All this complexity adds to cost. For some time, researchers have been hunting for a way to make LEDs using silicon on standard silicon processes.

There have been some successes, although none comes close to matching compound semiconductor devices for brightness or efficiency. This situation is unlikely to change for a while yet.

Porous silicon, for instance, has been shown to emit light, but making it requires processes not compatible with chip manufacture.

Silicon nanocrystals can also be persuaded to emit light. However, according to LED maker Toshiba, they have, up to now, required

between 10 and 25V to operate; excessive for today's chips.

The latest announcement comes from the Advanced Research Laboratory of Toshiba in Japan. Scientists there have pushed nanocrystal device operating voltage below 5V while using formation methods broadly compatible with current integrated circuit production.


Making Toshiba's devices involves depositing a layer of amorphous silicon around 2nm thick onto a silicon wafer. This wafer is then heated to between 700 and 850°C in an oxygen or nitrogen atmosphere for a few minutes.

During this heating, silicon nanocrystals grow on the wafer surface inside the amorphous silicon.

Once cool, the nanocrystals emit visible light at room temperature when reverse biased through a Schottky contact.

The crystals are hemispherical and, by altering the amorphous silicon layer thickness, processing temperature, atmosphere and heating duration, the researchers have made different sizes.

Orange emission came from

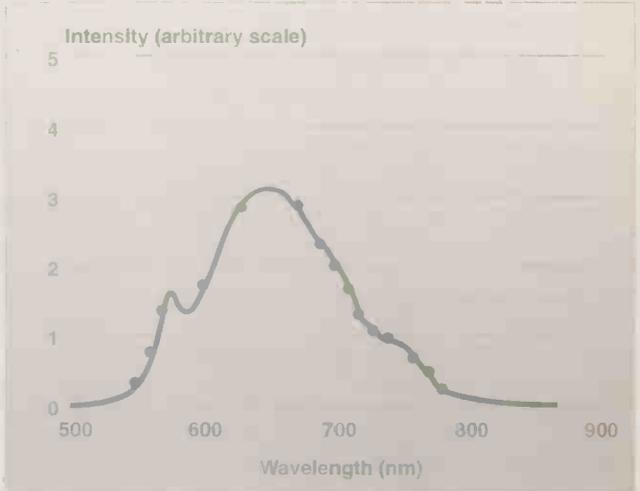


samples processed at 700°C in nitrogen or oxygen.

Red came from 800°C processing in nitrogen (at 3.5-4V), but an oxygen atmosphere at these high temperatures caused the nanocrystals to oxidise away. Similar destruction of the nanocrystals happened with nitrogen above 850°C where they were converted to polysilicon.

The experiments have narrowed down the source of the

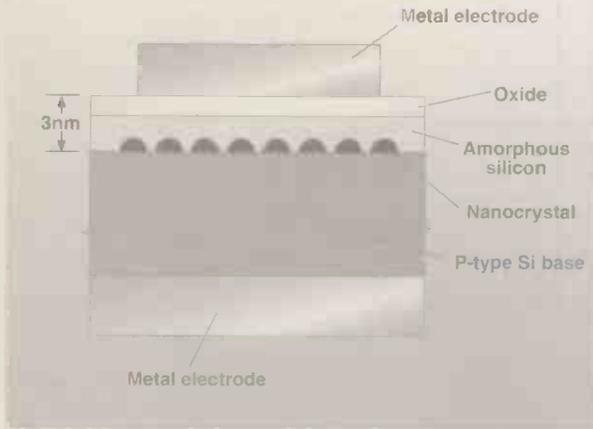Over the hump... Weak but definitely red. Toshiba is producing visible light from silicon.



electroluminescence, but not identified it.

It is not due to defects in the amorphous silicon, or defects at either of its surfaces, or the amorphous silicon-nanocrystal boundary. However, it only happens in nanocrystals less than 2nm across and 1.5nm high, and wavelength is related to crystal size.

The team's best guess at the moment is that the light is coming

Hot technology... Baking thin amorphous silicon layers produces the essential nanocrystals.

from within the nanocrystals themselves and that emission is due to "the quantum confinement effect" within them. More specifically, "the recombination of confined electrons and trapped holes".

The team's report says that efficiency, at the moment very poor, can be improved by increasing the number of nanocrystals and strengthening the carrier confinement. It concludes that: "The LEDs that have been demonstrated are promising devices for realising monolithic optoelectronic ICs".

Steve Bush *Electronics Weekly*

UK engineering skills shortage highlighted

Two-thirds of the UK's electronics companies consider a shortage in engineering skills to be one of the most serious problems affecting their business, a survey has found.

The survey by the Federation of the Electronics Industry (FEI) has found that the shortages are not confined to specific jobs, disciplines or industry sectors but includes all skilled activities in the electronics industry.

Telecommunications operator BT confirmed that there is an industry problem. "We do notice problems in recruiting in technical areas," said a

BT spokesman. "But we obviously have a bit of an advantage in that BT is a well known company." The company recruited 540 graduates last year.

Pace Micro Electronics is seeking to recruit 100 R&D engineers this year to work on its digital TV products. "We're fortunate that we're in a rapidly growing business so we can attract engineers," said Tim Fern, director of engineering, broadcast, at Pace.

However, the shortage of suitable graduates is putting pressure on pay

and conditions as companies like Pace compete to recruit the best engineers. "We're offering increasing benefits and salaries," said Fern.

The UK education system is currently producing fewer than 3000 software engineers a year and an increasing number of them are going into IT. It is a situation that the government is well aware of, according to Fern, who has already lobbied DTI ministers, John Battle and Barbara Roche in his quest for action on the problem.

Melanie Reynolds

In brief

Interactive TV turned on

The UK's first interactive TV service is now available via NTL's TV-Internet set-top box.

The communication company's service, delivered via a BT phone line, offers customers access to shopping, news, sport, travel and local information through their TV. A keyboard is available for sending e-mail. The service will be offered via digital terrestrial TV and NTL's own cable network later this year.

The service has been designed for ease of use. "The whole essence of what we're doing is making the content feel like television," said Jason Rogers, technology director. "It doesn't look like small text and a million different frames like an Internet page."

The company intends to add games over its network from the autumn. "We've been developing relationships with a number of providers to develop games onto our set-top platform," said Rogers. The network connection offers the prospect of multi-player games.

NTL is already looking for enhanced set-top box performance next year to better display graphics and content. It is also

seeking to improve the box's connectivity using greater bandwidth ISDN, ADSL and cable modem lines. "We're trying to drive the whole level of functionality up by exploiting the power of these boxes along with increased Mips and richer graphics," said Rogers.

CRTs have a bright future, researchers conclude

CRTs remain the dominant display technology, despite the rapid growth of flat panels such as LCDs and plasma displays, claims Reed Electronics Research in its latest analysis of the European display market. Over 60 per cent of sales are down to CRTs. The European market was worth \$3.8bn last year, and is expected to exceed \$5bn by 2003. LCDs dominate the flat panel sector, accounting for over 82 per cent of sales. www.rer.co.uk

UK business costs are lowest

According to a survey by KPMG Consulting, the UK has the lowest business costs in Europe for the manufacture of electronics and telecommunications equipment.

The survey, which compared the cost of doing business among 64 cities in eight countries, saw the UK leading the way in

Europe, with France second and Italy third. Charles Thomas, a consultant with KPMG, said: "The results of this study are extremely good news for the UK's prospects of attracting inward investment, particularly for non-EU companies looking for a European base."

The survey, which included the G7 countries and Austria, showed the UK to have the lowest labour costs in electronics and telecoms manufacturing and the smallest corporate income tax rates along with Austria.

The three UK cities included in the survey – Cardiff, Manchester and Telford – were found to be lower cost locations than all but one US city: San Juan.

Comms antenna health probe call

A Commons call for new research into the health effects of telecommunications masts has been backed by 28 MPs.

A special Parliamentary motion expressed concern about the possibility of short-term memory loss and other illnesses caused by "low energy electromagnetic fields". It urged the DTI, and the Department of the Environment, Transport and the Regions to commission the research and, if necessary, introduce planning guidelines to stop the siting of the masts in populated areas such as on school roofs.



PLUG IN AND MEASURE

8-12 bit
200kHz-50MHz
100mVolt-1200Volt

STORAGE OSCILLOSCOPE
SPECTRUM ANALYZER
VOLTMETER
TRANSIENT RECORDER



TiePie introduces the HANDYSCOPE 2

A powerful 12 bit virtual measuring instrument for the PC

The HANDYSCOPE 2, connected to the parallel printer port of the PC and controlled by very user friendly software under Windows or DOS, gives everybody the possibility to measure within a few minutes. The philosophy of the HANDYSCOPE 2 is: "PLUG IN AND MEASURE".

Because of the good hardware specs (two channels, 12 bit, 200 kHz sampling on both channels simultaneously, 32 KWord memory, 0.1 to 80 volt full scale, 0.2% absolute accuracy, software controlled AC/DC switch) and the very complete software (oscilloscope, voltmeter, transient recorder and spectrum analyzer) the HANDYSCOPE 2 is the best PC controlled measuring instrument in its category.

The four integrated virtual instruments give lots of possibilities for performing good measurements and making clear documentation. The software for the HANDYSCOPE 2 is suitable for Windows 3.1 and Windows 95. There is also software available for DOS 3.1 and higher.

A key point of the Windows software is the quick and easy control of the instruments. This is done by using:
- the speed button bar. Gives direct access to most settings.
- the mouse. Place the cursor on an object and press the right mouse button for the corresponding settings menu.

- menus. All settings can be changed using the menus.

Some quick examples:
The voltage axis can be set using a drag and drop principle. Both the gain and the position can be changed in an easy way. The time axis is controlled using a scalable scroll bar. With this scroll bar the measured signal (10 to 32K samples) can be zoomed live in and out.

The pre and post trigger moment is displayed graphically and can be adjusted by means of the mouse. For triggering a graphical WYSIWYG trigger symbol is available. This symbol indicates the trigger mode, slope and level. These can be adjusted with the mouse.

The oscilloscope has an AUTO DISK function with which unexpected disturbances can be captured. When the instrument is set up for the disturbance, the AUTO DISK function can be started. Each time the disturbance occurs, it is measured and the measured data is stored on disk. When pre samples are selected, both samples before and after the moment of disturbance are stored.

The spectrum analyzer is capable to calculate an 8K spectrum and disposes of 6 window functions. Because of this higher harmonics can be measured well (e.g. for power line analysis and audio analysis).

The voltmeter has 6 fully configurable displays. 11 different values can be measured and these values can be displayed in 16 different ways. This results in an easy way of reading the requested values. Besides this, for each display a bar graph is available.

When slowly changing events (like temperature or pressure) have to be measured, the transient recorder is the solution. The time between two samples can be set from 0.01 sec to 500 sec, so it is easy to measure events that last up to almost 200 days.

The extensive possibilities of the cursors in the oscilloscope, the transient recorder and the spectrum analyzer can be used to analyze the measured signal. Besides the standard measurements, also True RMS, Peak-Peak, Mean, Max and Min values of the measured signal are available.

To document the measured signal three features is provided for. For common documentation three lines of text are available. These lines are printed on every print out. They can be used e.g. for the company name and address. For measurement specific documentation 240 characters text can be added to the measurement. Also "text balloons" are available, which can be placed within the measurement. These balloons can be configured to your own demands.

For printing both black and white printers and color printers are supported. Exporting data can be done in ASCII (SCV) so the data can be read in a

spreadsheet program. All instrument settings are stored in a SET file. By reading a SET file, the instrument is configured completely and measuring can start at once. Each data file is accompanied by a settings file. The data file contains the measured values (ASCII or binary) and the settings file contains the settings of the instrument. The settings file is in ASCII and can be read easily by other programs.

Other TiePie measuring instruments are: HS508 (50MHz-8bit), TP112 (1MHz-12bit), TP208 (20MHz-8bit) and TP508 (50MHz-8bit).

Convince yourself and download the demo software from our web page: <http://www.tiepie.nl>. When you have questions and / or remarks, contact us via e-mail: support@tiepie.nl

Total Package:
The HANDYSCOPE 2 is delivered with two 1:1/1:10 switchable oscilloscope probe's, a user manual, Windows and DOS software. The price of the HANDYSCOPE 2 is £ 299,00 excl. VAT.

TiePie engineering (UK), 28 Stephenson Road, Industrial Estate, St. Ives, Cambridgeshire, PE17 4WJ, UK
Tel: 01480-460028; Fax: 01480-460340

TiePie engineering (NL)
Koperslagersstraat 37
8601 VL SNEEK
The Netherlands
Tel: +31 515 415 416
Fax +31 515 418 819

Will printed FEDs replace plasma panels?

There's a number of up-and-coming emissive display technologies emerging at the moment.

The first is from Oxfordshire's Printed Field Emitters (PFE). It has been working on an electron-emissive material to go at the back of field emission displays (FEDs) as an alternative to micromachined Spindt cathodes, diamond films and diamond-like carbon films.

The advantage of its material, claims the company's Dr Richard Tuck, is that it can be applied using a printer rather than chemical vapour deposition or other 'high-tech' process.

So keen is the company on printing that it is also looking at printing the spacers essential for preventing FEDs from imploding.

Other FED companies are investigating at more elaborate schemes. Candescent, for instance, is

using short glass fibres stood on end. Printed spacers are not necessarily as fine as fibres, but large area displays – where PFE is aiming its technology – have big pixels which can accommodate fatter spacers.

According to Tuck, the only non-printing process is a single self-aligning whole-panel lithographic stage used to open-up emission sites.

Tuck reckons that the 1m diagonal hang-on-the-wall TV market is the one to go for and claims printed FEDs will undercut the price of similarly-sized plasma panels. He says panel costs will not differ between types, but drive electronics will be considerably cheaper for printed FED panels as lower voltage, lower frequency signals are required.

At the other end of the size scale, the confusingly named FED Corporation has just licensed organic

light emitting diode (OLED) technology from Kodak.

FED Corp began life five years ago as a field-emission display company. Three years ago it changed horses to LCD and OLED technology when it realised FEDs were less suitable as micro-displays – its target market.

Micro-displays are predicted to be a fast growing market as games head sets and wearable computers become more popular.

Now FED Corp aims to sample silicon-backplane miniature LCDs this year and silicon-backplane miniature OLED displays soon afterwards.

Many companies are in production or close to production with silicon LCDs, but FED Corp sees an advantage in moving to silicon-backed OLED displays. "We think an LCD headset display will use around 2W of power. An OLED version will probably get down to 0.5W," said company executive v-p Susan James.


OLEDs are sometimes called molecular emitters, or small molecule emitters, to differentiate them from light-emitting polymer (LEP) displays of the type that Cambridge Display Technology (CDT) is working on and licensing.

OLEDs and LEPs have broadly similar characteristics and both CDT and Kodak have licensees who are making equipment with their technology. In the OLED case it is Pioneer which is using organic LEDs in car radio displays.

OLEDs, from Kodak, have been around the longest. The company is banking on this to promote its technology in the market. OLEDs can also provide a long-life blue emitter – something that the LEP brigade is only just testing. On the other hand OLEDs need to be vacuum deposited, whereas LEPs can be printed.

Steve Bush

Printed light... Oxfordshire company Printed Field Emitters (PFE) is developing electron-emissive materials for use in field emission displays that can be printed. As with all FEDs, electrons hit a phosphor to create light. The pictures show a three-colour sample under test and, inset, an early 2.5cm across large-area emitter in action. PFE claims to have materials now with around 100 000 emissive sites per square centimetre.

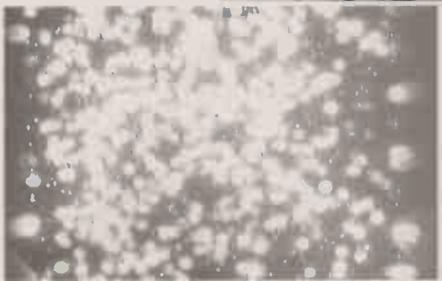

Young engineers are getting better off

The starting salary for engineering graduates is rising as a result of growing competition, according to the latest pay survey from the Institution of Electrical Engineers (IEE).

"We noticed that of the younger people who did respond, their salaries seem to have gone up quite a lot in certain areas," said Beryl Gurney, IEE professional development section. "Computer linked industry starting salaries seem quite high."

The survey based on 8510 responses from IEE members found that its

Associate Members i.e. engineers with degrees, enjoyed the sharpest rise in salary at nine per cent, bringing their median wage to £28 800. But the IEE believes that this result was skewed due to younger associate members, traditionally having lower wages, failing to respond while the older ones with higher wages did.

Chartered Engineers' salaries increased by 4.7 per cent to a median of £38 000 while Associates – engineers without degrees – achieved a rise of 2.8 per cent taking them up to £29 600.

HSE plans PC health study

A year-long study to investigate the

potential health risks of using portable and handheld computers is being funded by the Health and Safety Executive.

The study will be carried out by ergonomics consultancy, System Concepts, and will look at the issues arising from the extended use of portables.

"A lot of these things are issues which we can do something about if we know about them," said Tom Stewart, managing director of System Concepts.

According to Stewart, several manufacturers have contacted him since the study was announced and are keen to include any improvements needed in their designs.

Now the **WR3100e** external **WiNRADiO** arrives!



"WiNRADiO™ now brings you a complete choice in **personnel computer** controlled radio scanning and reception solutions.."

With either the internal or external versions, you can couple all the power of the latest Windows PCs (not just the fraction that you can squeeze down an RS232 connection) to the latest synthesised receiver design techniques, and you'll get the ultimate in wide range, all mode programmable radio reception.



VisiTune™ spectrum tuning display



Your choice of virtual front panel

New external WiNRADiO™

(WR1000e, WR1500e and new WR3100e) provide complete comms systems connecting either via the basic RS232 - or with an optional PCMCIA adaptor, for high speed control. Power from existing 12v supplies, or our optional NiMH rechargeable 12v battery pack.

Use WiNRADiO scanning PC comms receivers for...

Broadcast . Media monitoring . Professional & amateur radio communications . Scanning . Spot frequency & whole spectrum monitoring . Instrumentation Surveillance (and recording)


If you want the ultimate receiver-in-a-PC with full DSP, then you need the WR3000-DSP with its hardware for real-time recording, signal conditioning and decoding applications. (DSP is available with the ISA card version only).

Take a look at WiNRADiO's Digital Suite Software..

For WR1000/1500/3100 internal or external

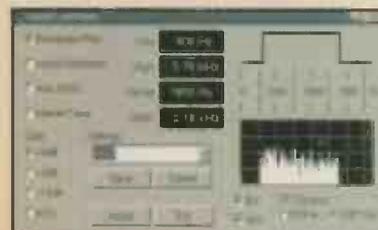1. WEFAX / HF Fax
2. Packet Radio for HF and VHF
3. Aircraft Addressing and Reporting System (ACARS)
4. Audio Oscilloscope, real time Spectrum Analyzer
5. Squelch-controlled AF Recorder
6. DTMF, CTSS decode

The DSP applet provided with the WR3100 spectrum monitor ISA card (£995+VAT) allows continuous control of audio bandwidth and other signal conditioning functions



ONLY £81.05 inc VAT

(requires SoundBlaster 16 compatible sound card)

Model Name/Number	WR-1000	WR-1500	WR-3100
Construction of internals	WR-1000i/WR-1500i-3100DSP- Internal full length ISA cards		
Construction of externals	WR-1000e/WR-1500e - 3100e - external RS232/PCMCIA (optional)		
Frequency range	0.5-1300 MHz	0.15-1500 MHz	0.15-1500 MHz
Modes	AM,SSB/CW,FM-N,FM-W	AM,LSB,USB,CW,FM-N,FM-W	AM,LSB,USB,CW,FM-N,FM-W
Tuning step size	100 Hz (5 Hz BFO)	100 Hz (1 Hz for SSB and CW)	100 Hz (1 Hz for SSB and CW)
IF bandwidths	6 kHz (AM/SSB), 17 kHz (FM-N), 230 kHz (W)	2.5 kHz(SSB/CW), 9 kHz (AM) 17 kHz (FM-N), 230 kHz (W)	2.5 kHz(SSB/CW), 9 kHz (AM) 17 kHz (FM-N), 230 kHz (W)
Receiver type	PLL-based triple-conv. superhet		
Scanning speed	10 ch/sec (AM), 50 ch/sec (FM)		
Audio output on card	200mW	200mW	200mW
Max on one motherboard	8 cards	8 cards	3-8 cards (pse ask)
Dynamic range	65 dB	65 dB	85dB
IF shift (passband tuning)	no	±2 kHz	±2 kHz
DSP in hardware	no - use optional DS software		YES (ISA card ONLY)
IRQ required	no	no	yes (for ISA card)
Spectrum Scope	yes	yes	yes
Visitune	yes	yes	yes
Published software API	yes	yes	yes (also DSP)
Internal ISA cards	£299 inc vat	£369 inc vat	£1169.13 inc vat
External units	£359 inc vat	£429 inc vat	£1169.13 inc (Hardware DSP only Internal)

PCMCIA adaptor (external): £30 when bought at same time as the 'e' series unit, otherwise: £69 inc.

PPS NiMH 12v battery pack & charger: £99 when purchased with 'e' series unit, otherwise: £139

For your free info pack and software emulation demo disk contact Broadcasting Communication Systems - and please note all available information is also available 24 hours a day on the web.

<http://www.broadercasting.com> - FREEPHONE: 0800 0746 263 - PHONE: 01245 348000

EMAIL: info@broadercasting.co.uk - FAX: 01245 287057

Unit B, Chelford Court, Robjohns Road, Chelmsford, Essex CM1 3AG

E&OE WiNRADiO and Visitune are trademarks of WiNRADiO Communications





As an alternative to MSF, VHF broadcast data can be used for precise clocks – if you don't mind retuning as you move around the country. But relying on Radio 4's often overlooked RDS-type signal on long-wave, Peter Topping's reference alarm clock works anywhere in the UK without retuning.

LW off-air reference clock

Radio 4's long-wave transmitter on 198kHz carries data as well as the audio signal. This data has some similarities with the RDS data included in VHF radio signals in many European countries, but it has a much lower data rate and is used for a different purpose.

There are 16 data-block types. Type 0 is used for time, date and 'filler' data. The other blocks are used commercially. Each one is available to the company leasing it for use in a specific application. Typical uses are elec-

tricity tariff switching, foreign exchange rate board updating and lighting control.

The whole of the UK is covered by a 500kW transmitter at Droitwich in England, with a little help from two 50kW transmitters at Westerglen and Burghead in Scotland. All three transmitters use the same frequency. The specification of LF radio data is described in a BBC document¹.

Time data is transmitted every minute on the minute and provides a very accurate clock traceable to

national standards. Local time variation, for example BST, is also transmitted.

In this application, time and date can be permanently displayed, while all incoming data can be displayed in hexadecimal form. The microprocessor converts the transmitted date information – day-of-week, week number and year type – into day-of-month and month.

The year is not transmitted and cannot be uniquely determined from the available data. The position in the 28-year leap year/year-start-day cycle can, however, be worked out and this can be used to calculate a year in the range 1995 to 2022. It is not possible to distinguish between 1995 and 2023.

Hardware involved

Figure 1 shows a block diagram of the design: the microprocessor used for decoding is the MC68HC(7)11 while an MC3371 is used for the radio receiver. Unlike RDS, where demodulation chips are available, the capability of retrieving the data bits has to be included in the hardware design.

The 3371 is a superheterodyne receiver including a mixer and limiting IF amplifier. It also has an FM demod-

Peter is an MCU applications engineer at Motorola's East Kilbride plant.

Table 1. Structure of clock-time blocks used in Radio 4 long-wave's RDS-like service.

Bit	Function	
1	Prefix (1)	Used only for synchronisation and error detection
2-5	Block type no	0000
6	Time/filler flag	0
7-8	Leap year cycle	00; this year leap 01; last year leap 10; leap year 2 or more years away 11; next year leap
9-11	Year start day	Day-of-week on 1 January (1: Monday, 0 not used)
12-17	Week number	Week number (1-53, 0 & 54-63 not used)
18-20	Day of week	Current day of week (1: Monday, 0 not used)
21-25	Hours	0-23 UTC (24-31 not used)
26-31	Minutes	0-59 UTC (60-63 not used)
32-37	Local offset	Local deviation from UTC in 2's complement form in increments of 30 minutes (BST=CET=000010)
38-50	CRC	Used only for synchronisation and error detection

ulator intended mainly for dual-conversion VHF communication equipment. The radio-data is modulated so the MC3371 is suitable, even though it works at an unusually low radio frequency.

The RF of 198kHz is converted to a standard 455kHz IF. Operational amplifiers are used to amplify, filter, integrate and limit the signal into a form that can be used by the microprocessor. Four keys control the decoder and a 16-character dot-matrix LCD module displays the data, time, etc.

This design incorporates an alarm clock similar to that described in application note AN460². If the clock is permanently powered, the alarm can be used to switch on the radio supplying the data at the required alarm time. This control could be to the power supply of the radio, or to the audio stage only.

If an audio mute is used, radio-data time information can be updated even when the radio is 'off'. Alternatively the decoder can be used simply to display time and date with its power being supplied from the radio and manually switched on and off.

Radio data on long wave

Transmitted data is conveyed using linear phase-modulation of the carrier by a shaped and bi-phase-encoded waveform. This is applied to the main carrier as there is insufficient space in the ± 4.5 kHz low-bandwidth AM signal for a subcarrier.

In order not to interfere with normal modulation, the data rate is a very low, at 25Hz. Bi-phase coding and a small deviation of $\pm 22.5^\circ$ are used so that the transmission's use as a frequency standard is retained.

The data stream is partitioned into 50-bit blocks but, like RDS data, there are no gaps between blocks. Additional cyclic-redundancy check word, or CRC, bits are added to allow synchronisation.

The bit rate of 25Hz and the block length of 50 bits mean that a block takes 2 seconds, hence 30 blocks are transmitted every minute.

Each 50-bit block contains a single-bit prefix – which is always logic 1 – a 4-bit application code or 'block number', 32 bits of data and 13 extra CRC bits used for synchronisation and error detection and correction, Table 1.

The particular code used is the 49, 13 shortened cyclic code ($G(x)=36365_8$) described by Kasami³. It is modified though by the addition of the fixed prefix to address the cyclic code's poor block-synchronisation capability.

The CRC is the remainder calculated

in the transmitter by dividing the 36 data bits – including the application code – by the generator polynomial.

As this remainder is then used as the 13-bit check word, the 49 received bits should give a remainder of zero when divided by the generator polynomial. Looking for a zero 13-bit remainder thus carries out synchronisation.

Multiplication of the 49-bit received data by the matrix shown in Table 2 is equivalent to this polynomial division and is the method used here. During synchronisation this calculation has to take place after each bit is received, using the last 50 bits – actually 49 as the first fixed bit is not used – until a valid zero remainder is found.

Once the valid remainder is found, the check need only be done after another 50 bits have been received, as this is when the next valid block would be expected. If, at that point, a zero remainder is not found the bit-by-bit check is re-started.

The CRC bits make error correction possible, but this application does not include that facility. They are only used for synchronisation and error detection.

Burst error correction

Use of burst error-correction can allow good data to be received in the presence of errors, but it also increases the undetected error rate. This is because blocks with more errors than the code is capable of correcting – a single burst of up to 6 bits – may be deemed correctable and thus pass through undetected.

Blocks of type zero are used for transmitting the time and date information and for 'filler' codes. All other types, i.e. 1 to 15, are user blocks. Their data is meaningless in this context, but it can be displayed in hexadecimal form as it comes in.

The first of the 32 data bits in a type 0 block determines whether it is a time-code block, in which case the first bit a zero, or simply a filler, when the first bit is a one. Time-code blocks are transmitted immediately prior to the

Table 2. 13 by 49 decoding matrix used to process the 49 bits of incoming data.

Hex.	Binary	Octal
17 3B	1 0111 0011 1011	13473
15 E7	1 0101 1110 0111	12747
14 89	1 0100 1000 1001	12211
14 3E	1 0100 0011 1110	12076
0A 1F	0 1010 0001 1111	05037
1B 75	1 1011 0111 0101	15565
13 C0	1 0011 1100 0000	11700
09 E0	0 1001 1110 0000	04740
04 F0	0 0100 1111 0000	02360
02 78	0 0010 0111 1000	01170
01 3C	0 0001 0011 1100	00474
00 9E	0 0000 1001 1110	00236
00 4F	0 0000 0100 1111	00117
1E 5D	1 1110 0101 1101	17135
11 54	1 0001 0101 0100	10524
08 AA	0 1000 1010 1010	04252
04 55	0 0100 0101 0101	02125
1C 50	1 1100 0101 0000	16120
0E 28	0 1110 0010 1000	07050
07 14	0 0111 0001 0100	03424
03 8A	0 0011 1000 1010	01612
01 C5	0 0001 1100 0101	00705
1E 98	1 1110 1001 1000	17230
0F 4C	0 1111 0100 1100	07514
07 A6	0 0111 1010 0110	03646
03 D3	0 0011 1101 0011	01723
1F 93	1 1111 1001 0011	17623
11 B3	1 0001 1011 0011	10663
16 A3	1 0110 1010 0011	13243
15 2B	1 0101 0010 1011	12453
14 EF	1 0100 1110 1111	12357
14 0D	1 0100 0000 1101	12015
14 7C	1 0100 0111 1100	12174
0A 3E	0 1010 0011 1110	05076
05 1F	0 0101 0001 1111	02437
1C F5	1 1100 1111 0101	16365
10 00	1 0000 0000 0000	10000
08 00	0 1000 0000 0000	04000
04 00	0 0100 0000 0000	02000
02 00	0 0010 0000 0000	01000
01 00	0 0001 0000 0000	00400
00 80	0 0000 1000 0000	00200
00 40	0 0000 0100 0000	00100
00 20	0 0000 0010 0000	00040
00 10	0 0000 0001 0000	00020
00 08	0 0000 0000 1000	00010
00 04	0 0000 0000 0100	00004
00 02	0 0000 0000 0010	00002
00 01	0 0000 0000 0001	00001

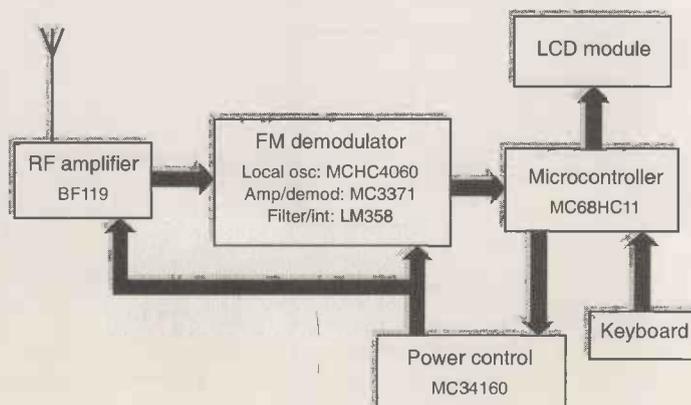


Fig. 1. Outline of the long-wave Radio 4 data decoder. Although the radio data on long-wave is similar to that on VHF broadcasts, there are no specific hardware solutions for the long-wave version so the decoding needs to be done by a microcontroller.

minute epoch so that the exact time is indicated, although only hours and minutes are included in the data.

Structure of the time-code block is shown in Table 1.

Hardware details

The microprocessor used is the *MC68HC811E2*. A *711E9* or *E20* could also be used. An *MC3371* is used for the radio receiver. The *3371* is a superheterodyne receiver including mixer, limiting IF amplifier and FM demodulator.

The radio frequency of 198kHz is converted to the standard 455kHz IF. This would normally require a crystal of 653kHz, which is not a standard frequency and would be difficult and expensive to obtain. To avoid an expensive crystal, higher standard frequency types were investigated to find one suitable for dividing down to approximately the correct frequency.

Two suitable crystals were found. One was a 10.5MHz type intended for 14MHz to 3.5MHz amateur-band conversion. Divided by 16, 10.5MHz gives 656.25kHz. The other was a 20.945MHz type intended for 21.4MHz to 455kHz conversion. Divided by 32, this one gives 654.53kHz. An *MC74HC4060* forms an oscillator and divider providing the signal for the *3371*'s mixer.

The complete circuit diagram of the analogue board is shown in Fig. 2. Radio-frequency signal is derived from a ferrite rod whose coil can be either a standard LW winding, or can be flat-wound with thin insulated wire. On a standard 0.25in ferrite rod using 36SWG wire, this winding is about 3.75in long, i.e. 190 turns.

The easiest way to get the winding to the correct inductance is to wind it on a paper former so that it can be slid along the rod. If a 4.25in winding of around 210 turns is made and the 330pF capacitor and trimmer connected, resonance will be found by sliding the winding partially off the end of the rod.

Finding antenna resonance

Resonance of the antenna can be observed on an oscilloscope, but is most easily found by holding the rod close to a radio – preferably one with a signal strength meter – tuned to 198kHz. The radio's signal will be noticeably affected as resonance is achieved.

The winding is then adjusted by slowly sliding it fully onto the rod, maintaining resonance by removing turns. If this is done with the trimmer in the mid position, the antenna can be completed and finally adjusted using the trimmer without any specialised equipment.

The output winding consists of a further 20 turns at the earthed end of the main coil. An antenna made this way worked satisfactorily but the prototype performed better and was less sensitive to orientation when using a Litz-wound rod taken from an old radio.

RF amplification

The signal is amplified by a *BF199* with a tuned load employing a Toko *CAN1A350EK* long-wave RF coil and 220pF. The coil should be tuned for maximum output.

Additional selectivity is provided by the 198kHz crystal, available from AEL.⁷ The application works without this crystal, but with a much reduced sensitivity and tolerance to interference.


This signal goes into the mixer of the *MC3371*. As this design operates at a single frequency, it is not strictly necessary to use a superheterodyne arrangement. However, it allows the use of an off-the-shelf high-Q 455kHz demodulator coil (Toko *RHCS45328AC2*) rather than using a separate coil and capacitor at 198kHz. With a separate coil and capacitor, it would be very difficult to achieve a Q value as high as 180.

Local oscillator

The local oscillator is fed by a *4060* as described above. A Murata *CFU455D2* filters the intermediate frequency. At 20kHz, this ceramic filter's bandwidth is far wider than necessary in this design, but its selectivity is not required and this width allows the use of the less precise local oscillator frequency.

Adjustment of the demodulator coil needs care due to the coil's high Q.

Fig. 2. In the analogue section, the 198kHz crystal adds selectivity and sensitivity. Use of the Toko demodulator coil next to the 3371 mixer allows a high Q of around 180.

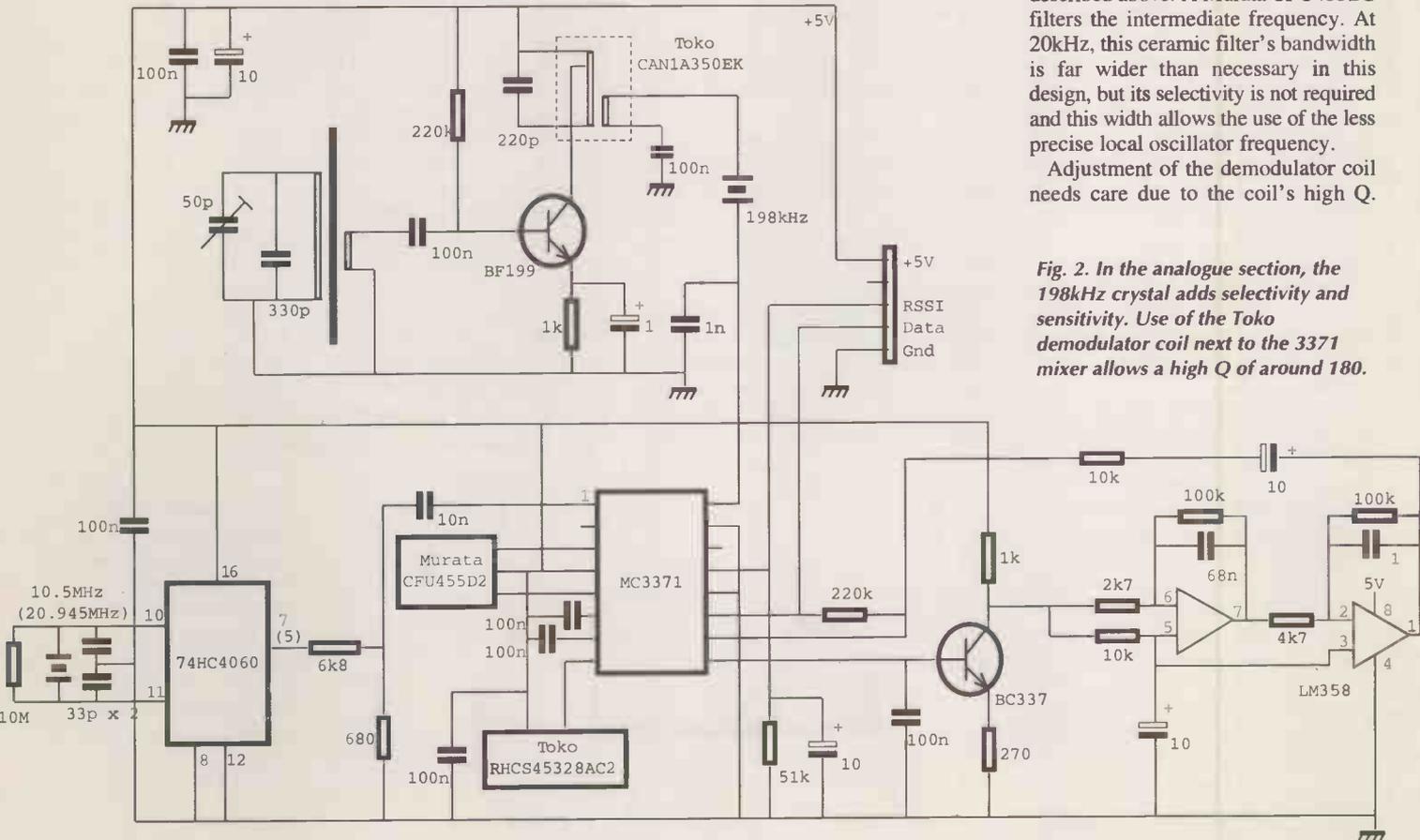

boards is the four-wire connector shown in both diagrams. With the arrangement shown, this interface provides the 5V supply to the analogue board.

Two signals are returned; the demodulated radio data signal and the signal level, or RSSI. The data signal goes directly into the IRQ interrupt-request input on the HC11.

As edge timing is used to decode the data, a timer-input capture scheme would be more appropriate. But the IRQ alternative works as well in this application, where the required accuracy is measured in milliseconds.

The IRQ was used simply because debug hardware – an HC11K4 running Pcbug11 – was available and it used the K4's port A for the LCD.

Conditional assembly, using the Introl assembler, enabled differentiation between the K4 and the intended target microcontroller, an 811E2. The link shown on the MODB pin is to allow the use of the bootstrap mode to program the 811E2 or 711E9/20.

If you are using bootstrap mode, remember to use a baud rate appropriate to the crystal being used. If the crystal is in a socket, it may be easier to change to an 8MHz crystal and use the standard Pcbug11 rate of 9600 baud.

The MC34160 is used as a 5V regulator to supply the analogue board. The regulator is switched off when the software is in standby mode. This arrangement requires a second regulator for the microcontroller and display.

If standby mode is not required then a single, simple regulator will suffice. The 10kΩ and 3.3kΩ resistors divide the battery voltage by four before the HC11's a-to-d converter reads it.

As the RSSI level is always in the range 0-5V it goes directly into an a-to-d input.

How it works

Table 3 shows the various functions available in each mode via the four-key keypad. Operation of the keys and modes is derived from the RDS application described in Motorola's note AN460.²

The 'on/off' key uses a subroutine in my software called ONOFF to toggle between 'on' and standby. Details of how you can obtain this software are given on page 453.

Port pin PD5 controls power to the analogue section and can also switch a radio or other external hardware. In standby mode, time is displayed with the date if the alarm is disabled. If the alarm is enabled, the display shows the alarm time. In 'on' mode, the time is

displayed with the current hexadecimal data. Table 4 shows these display formats.

The 'alarm' key calls the subroutine ALARM, which displays the current alarm status. A second press changes the alarm armed status.

When the alarm is armed, the alarm time is displayed. In this mode the on/off key can be used to select either hours or minutes – indicated by flashing – and the 'sleep' and 'display' keys used to increment and decrement the settings.

The alarm display has one of the two alarm formats shown in Table 4, according to whether or not the alarm is armed. All the keys have a special function in the alarm mode. If the alarm is armed, the only way to exit this mode is to wait for a timeout. If no keys are pressed, the mode returns to normal in ten seconds.

The alarm time can be entered as described above. When the alarm is enabled, the alarm time is displayed on first press of the 'alarm' key and permanently displayed in standby mode.

If the alarm is enabled, then at the alarm time the auxiliary control line PD5 goes low, activating the sleep timer for an hour. This takes place whether the decoder was previously on, off or running the sleep timer. It has the effect of switching the auxiliary line high again an hour after the alarm time, regardless of its condition prior to the alarm.

Sleep and display

The 'sleep' key controls the sleep timer. If the decoder is in standby mode, the first press of 'sleep' switches it on and initialises the sleep time to 60 minutes. When the sleep timer is running, this is indicated by a decimal point in the second character of the display module while the display mode is 'normal'.

Subsequent presses of 'sleep' decrement the time remaining by five minutes. When the sleep time has elapsed, the decoder returns to standby mode. In the alarm set-up mode this key decrements the alarm time.

The 'display' key selects the alternative displays of transmitted data, year and week information and battery and tuning voltages. In the alarm set-up mode, this key increments the alarm time.

The 'normal' display comprises the block identifier, the data in hexadecimal form split into two groups of four digits if there is room, and the time. If the block identifier indicates a time-code block, 't' is displayed.

The 'standby' display replaces the block data with the date, as the intention is that in this mode the analogue

Table 3. Four multi-purpose keys control all functions of the alarm and clock.

Mode	Key	Sleep	Alarm	Display
Standby (off)	Normal mode (on)	Sleep mode (on)	Alarm mode	Data display
	Standby mode (off)	Sleep mode (on)	Alarm mode	Data display
Alarm (off)	Standby mode (off)	Sleep mode (on)	Alarm on mode	Data display
	Alarm set-up mode	Sleep mode (on)	Alarm off mode	Data display
alarm (set-up)	Toggle hr/min	Decrement hr/min	Alarm off mode	Increment hr/min

Table 4. Display formats. In 'standby' mode, time and date are displayed, but in 'on' mode, the date is replaced by a display of the data currently being received, in hexadecimal form.

Display mode	Format
Normal (on):	t 74D32942 19:37
	- 0000 0000 0:00
Standby (off):	No radio data
	Alarm Off
	No time-code block
	--- 0 --- 0:00
	0659 Alarm 19:37
Alarm:	Alarm off
	Armed/set up
	Alarm - off
	Alarm - 6:59
Sleep:	Sleep 60 min
Alternative displays	1
	2
	3
	t 74D3 2942 F 59
	Y:3/5(1995) W:22
	B: 9.0 T: 3.45

circuitry is switched off.

The three alternative displays are available whether or not the unit is in standby mode. The first is similar to the normal display except that the time is replaced by the 'confidence' value and time seconds. When a good block is received, the confidence value is incremented up to F. If a block fails the CRC check, the value is decremented.

The second display alternative shows the year type as leap-year cycle and year starting day, the actual year and the week number. The year is assumed to be in the range 1995-2022 and is the 'week-number' year. This means that the year does not usually change at the transition between 31 December and 1 January, although it did, however, do this at the 95/96 transition. Instead, it advances to the next year when the week number goes from 52 or 53 back to 1.

While the local time offset adjusts the time and, if necessary, the date, it does not adjust the year. The method of adjusting the date can also use non-standard week numbers during the time when the local offset causes a change from 31 Dec to 1 Jan or vice versa.

During this time, a week number of 54 or 0 is possible. These non-standard week numbers will not happen though as long as the current practice of using GMT in the winter in the UK continues.

The third display indicates battery voltage up to a maximum of 19.9V, and the SSSI level up to 4.98V.

Software

The complete source code for the software is available by post. There is only room here to show the object code.

The reset routine, START, sets up the registers and i/o ports. External interrupts are enabled on negative edges so that the signal from the demodulator can interrupt the micro-processor on each falling edge.

The real-time interrupt timer, RTI, is enabled to cause an interrupt every 133ms to run the real-time clock. Correct operation of this clock in the absence of continuous data requires that a 2.0MHz crystal be used. A trimmer on pin 7 could be added to adjust for accurate timekeeping.

The main free-running timer's prescaler is set up to divide by 1. The

reset routine also enables interrupts, clears the RAM, initialises the LCD module and sets the mode to 'on' with alternative display 1. When a valid time-code block is received the mode switches to standby.

The idle loop, IDLE, uses the main free-running timer to loop at 64Hz. It regularly reads the keyboard for a key press, updates the display module, compares the current time with the alarm time and performs other time-dependent functions related to the display module and the sleep and alarm functions.

To ensure that the radio is switched on prior to a time signal, the alarm operates two seconds before the set time. This is why the displayed time is incremented by a minute before the comparison is made.

The capabilities of stopping keyboard scanning using PE7 is included in case it causes interference on a connected, or nearby, radio.

Keyboard subroutine KBD scans the four-key matrix for a key press every 16ms. If the same key is pressed on three successive scans, it executes the appropriate key function by calling the

Fig. 3. The clock's digital-processing section. Although the hardware is relatively simple, the clock provides precise electronic alarm switching and displays battery status and signal level.

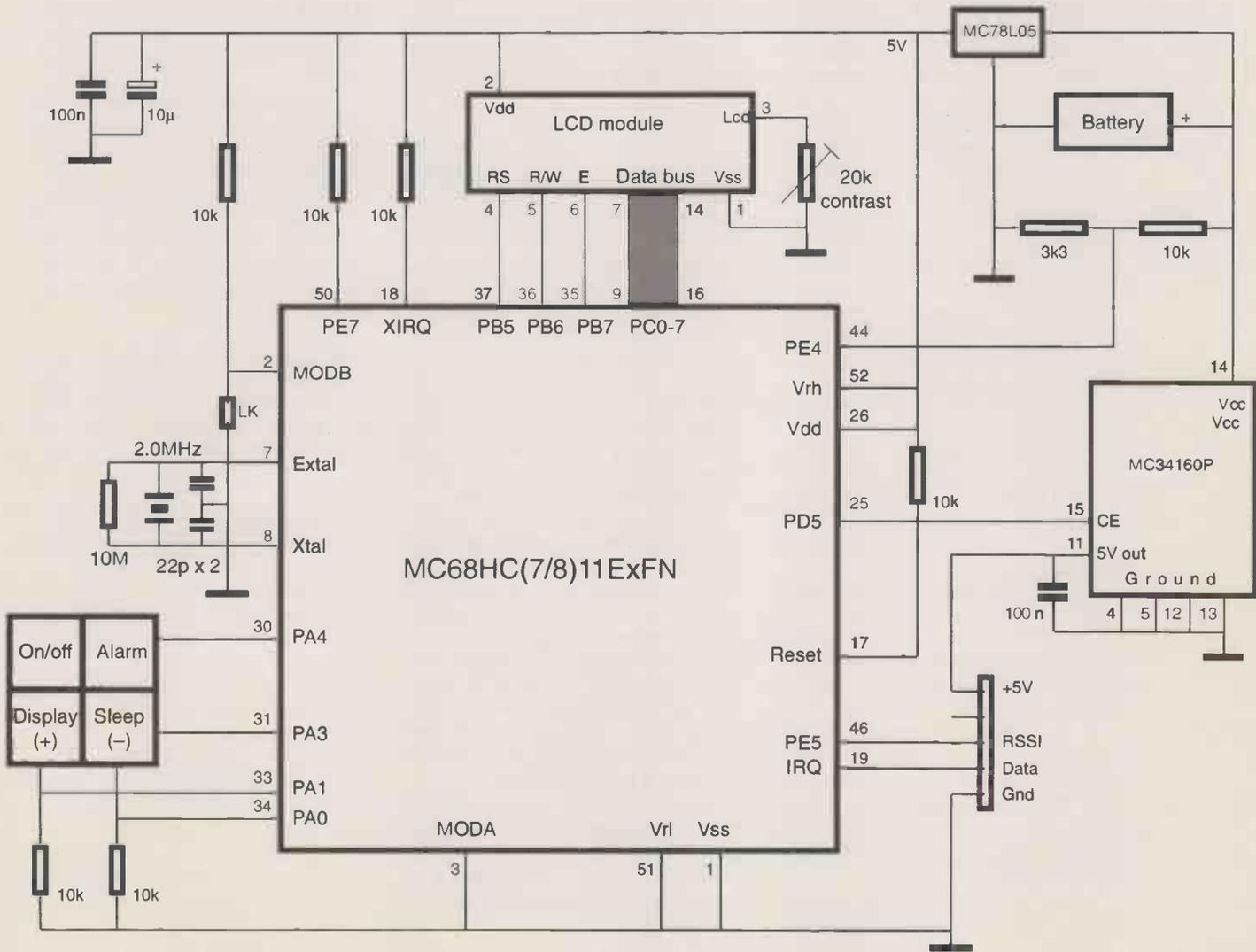


Table 5. Bi-phase decoding.

Previous bit	1 bit time	1.5 bit time	2 bit time
0	0	1	Illegal
1	1	00	01

relevant subroutine – ALARM, ONOFF, SLEEP or DCK. Table 3 shows the various functions available in each mode.

The timer interrupt routine TINTB decrements the sleep timer. It also updates the RAM locations used to store hours, minutes, seconds and eighths of seconds so that the time and date remain valid in the absence of regular time information.

Keeping time with no signal

As the 2.0MHz crystal used does not give exact eighth of a second ticks, the software compensates by counting 458 'eighths' of seconds in all but every ninth minute and 456 in the ninth minute.

The day of the week – and if necessary week number and year-type numbers – are also updated. This is done in case the clock is required to keep track of the date as well as the time in the absence of radio data. It is not the easiest way to organise a calendar, but it is necessary, as this is the form in which the time-code block provides the information.

There are 53 weeks if the year starting day was a Thursday or, in the case of a leap year, a Wednesday. The year starting day is incremented twice at the end of a leap year to allow for the extra day and wraps back from 7 to 1. The year type simply increments and wraps from 3 back to 0. The sequence repeats every 28 years until the year 2100 – which is not a leap year.

Hardware interrupts are vectored to jump to SDATA when a negative edge is received from the demodulator. This edge causes an interrupt and the data is calculated from the time interval from the previous edge.

The bi-phase coded data bit, or bits, also depends on the value of the previous bit, Table 5. The bits are shifted into a seven-byte RAM register – DAT to DAT+6 – and the matrix multiplication performed.

The state of flag STAT2,\$01 determines if the multiplication is to take place after every bit or only after all 50 bits have arrived. The multiplication is performed using exclusive-or instructions for every bit.

As the bottom of the matrix, Table 2, is a unity matrix, the first 13 bits are transferred directly into the accumulators. The matrix multiplication is done in the loop MULT. This reduces the code required but increases the execution time of the algorithm.

In the source-code listing, the table B5-B1 represents the decoding matrix,

Table 2. In this case the execution time penalty is not a problem as the bit rate is very low. I carried out the same procedure using in-line code in the RDS application mentioned earlier² as the bit rate was too high for a loop to be workable.

Because the interpretation of an edge depends on the previous bit, an error or a wrong guess at the start can cause all subsequent edges to be misunderstood. The illegal entry in the table is thus used to invert the current – perhaps the first guessed – previous bit, preventing decoding from getting stuck in this mode.

When a valid remainder is found, CONF is incremented and the 36 data bits saved in the four bytes of BLOCK. The confidence level CONF is used to decide when to switch to checking the CRC only every 50 bits. This is done once CONF has reached F₁₆, i.e. 15.

Processing valid data

If a valid block has been received, the data can be processed. A time block is used to initialise or update time, local time difference and date information. Any other block is meaningless in this application and so is displayed in its raw hexadecimal form.

The broadcast time is Universal Co-ordinated Time. Commonly referred to as UT0, this is effectively the same as GMT.

Time differences relative to UTC, including summer (daylight saving) time, are sent as a two's complement offset of up to ±12 hours in half-hour increments. The time block is checked before it is used although most errors should have been detected by the CRC check.

If the minutes are over 59, the hours over 23, the day-of-week a zero, etc., then the block is not used.

The first successful receipt of a time-code block after power-up or a reset switches the mode to standby, switching off the analogue section. The time data is transferred to other RAM locations for local offset adjustment and display.

After this adjustment is made the date, i.e. month and day of month, are calculated by first working out a day-of-year number and then converting to the usual month format using tables. A separate table is used for leap years.

The software drives a parallel LCD module based on an HD44780 driver with an HD44100 expander. Display routine MOD is executed in the idle loop if the STAT2 flag is set. It is set every 266ms by RTI timer interrupts.

The LCD module is updated with new data only if there has been a change since the last time the routine was executed. This reduces the likelihood of unnecessary i/o activity interfering with a radio.

Before anything is written to the module, the subroutine WAIT is used. This ensures that the controller in the module is not busy, as indicated by a low on bit 7 of the LCD's bus.

The listing is for use with a divide-by-8 multiplexing LCD module. To use a divide-by-16 module using only the HD44780, the subroutine LCD16 should be enabled.

Selecting display formats

The different display formats are selected by checking the various flags and the relevant routine executed. As the locations in RAM used for hours and minutes contain binary numbers, they are converted to ASCII BCD using the subroutine CBCD before being written to the display buffer.

If this subroutine is entered at the label SPLIT, then the data is simply split into nibbles and converted to ASCII. This is used for the display of the raw hexadecimal data. If the alarm is not armed, the standby display converts the day of the week and day of the month numbers into three character strings using the tables at the end of the listing.

Subroutine MNAME has an additional month at each end to facilitate a correct display when the local time offset causes a transition to the next or previous year.

Year and week display routine ALTD2 calculates a year in the range 1995 to 2022 from the year type (leap year) and year start day information. This is done using the table YRTAR, which consists of the offsets from the start of the 28 year cycle – arbitrarily taken to be 1995 – according to the values of year type listed down the table and year start day listed across the table. ■

Peter is currently trying to find time to write a short piece on programming the controller, which I will to publish as soon as it arrives. The process is said to be fairly straightforward – Ed.

References


1. LF Radio Data: Specification of BBC phase-modulated transmissions on long-wave, BBC, RD1984/19.
2. Application note AN460, 'An RDS Decoder using the MC68HC05E0.
3. Tadao Kasami, 'Optimum Shortened Cyclic Codes for Burst-Error Correction,' IEEE Transactions on Information Theory. April 1963, pp. 105-109.
4. M68HC11 Reference Manual (M68HC11RM/AD rev. 3).
5. M68HC11 E Series Technical Data.
6. Data sheets for the MC3371 and MC34160.
7. AEL Crystals, Module D, Genner Rd., Crawley RH10 2GA, 01293 524245 (Part No X198K000L001).

R

QUICKROUTE

www.quickroute.co.uk

THE QUICKROUTE

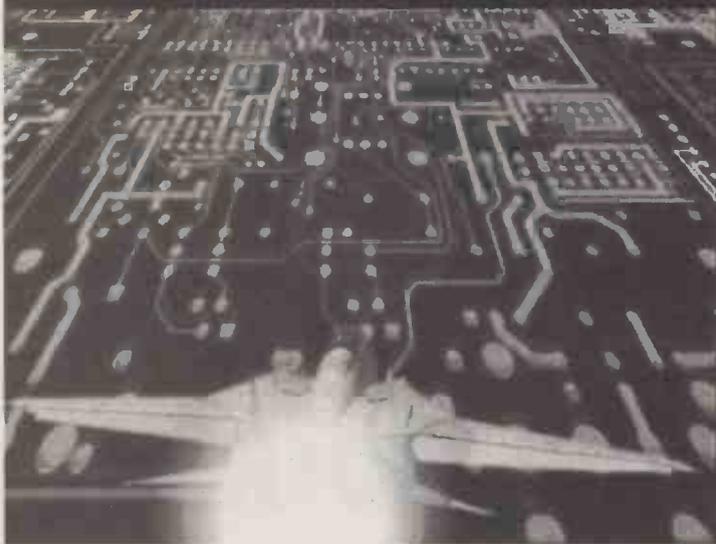

Simulation Circuit Capture PCB Autorouting CAD/CAM

Imagine an electronics design system that lets you draw schematics onto the screen and then simulate them at the touch of a button. Now imagine pressing another button and seeing the schematic replaced with a PCB rats-nest. Pressing another button starts the autorouter, and finally you can click on File then Save As to create a complete set of CAD/CAM files.

Too easy? We hope so. Quickroute has always been designed first and foremost to be easy to use. That's why simulation, circuit capture, PCB autorouting and CAD/CAM support are all integrated into **one** package, so that you only have to learn **one** package.

If you would like to find out more about Quickroute, why not call us on FREEphone 0800 731 28 24, or visit our web site on www.quickroute.co.uk. Prices start at under £100 including UK P&P and VAT for a complete system.



**"modern, powerful
and easy to use"**

Elektronics 97



FREEphone
0800 731 28 24

Int +44 161 476 0202 Fax 0161 476 0505

Copyright © 1998 Quickroute Systems Ltd Regent House Heaton Lane Stockport SK4 1BS UK

CIRCLE NO.108 ON REPLY CARD

NOW AVAILABLE

RANGER 2

for Windows 95™

Demo Software - available from our Web Address

The Complete, Integrated Schematic & PCB Layout Package

Windows Ranger 2

For Windows 95 & NT

- New Hierarchical Circuit
- Split Devices • Gate & Pin Swap
- New Edit Devices in Circuit
- Copper Fill • Power Planes
- Autorouter • Back Annotation

£250

Ranger 2 Outputs:

- Full Windows Outputs
- Plus - HP-GL
- Gerber
- NC Drill
- AutoCad DXF

Windows Ranger 2 with Spectra SP2

Ranger & Spectra Autorouter provide the most cost effective PCB Design system available. A powerful, intuitive system at an outstanding price!

£600

Windows Ranger 2 Upgrade

Upgrade your existing PCB Package to Windows Ranger 2.

£150

SPECIAL OFFER Ranger 2 Lite £35 (Prices exc VAT/P&P)

Demo Software - download from <http://biz.ukonline.co.uk/seetrax>

Call 01730 260062

Fax 01730 267273


Old Buriton Limeworks, Kiln Lane,
Buriton, Petersfield, Hants. GU31 5SJ



SEETRAX

Advanced Systems & Technology for PCB Manufacture

CIRCLE NO.109 ON REPLY CARD

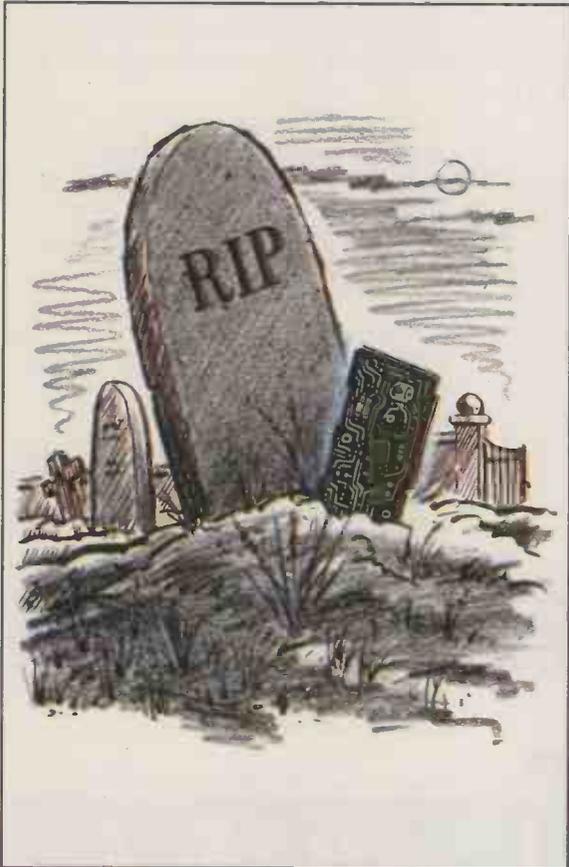

Once widely used in applications ranging from radar sets to televisions, the blocking oscillator is little remembered today. But here, Ian Hickman demonstrates that it still has its uses. His discussion includes a blocking-oscillator-based long-life emergency light using bright LEDs.

Is the blocking oscillator dead?

Back in the fifties and sixties I, like many designers, had occasion to use that very useful circuit arrangement known as the blocking oscillator. At its simplest, a blocking oscillator was just a wildly overcoupled oscillator of the Hartley variety, usually with separate feedback-coupling winding.

As normally designed, the Hartley oscillator was clean source of a continuous sinewave output. But if overcoupled, the heavy class-C operation would bias the device back to cut-off and the rf output would cease.

There then followed a recovery period during which the grid bias returned to the point at which anode current could flow once more, and another burst of rf followed. This was known as a squегging oscillator, and apart from making an excellent source of general interference, it was not of a great deal of use.

If the feedback coupling were made even tighter, then the device would bias itself back, by virtue of the heavy flow of grid, gate or base current, during the very first cycle of the rf. This, then was the blocking-oscillator circuit.

The blocking-oscillator was a popular pulse generator in the days of valves, and well into the transistor era. It was described in nearly all books on electronics, and a quick trawl through my limited library turning up several articles on the topic.

If you have, or come across, any of the references 1 to 5, you can read all about it.

What is a blocking oscillator?

Figure 1 shows a valve continuous-wave oscillator, where C and R would typically be 100pF and 10kΩ. The tri-

ode might be the oscillator portion of a triode-hexode frequency changer in short, medium and long-wave table radio.

If R were raised to 330kΩ, then the radio would still operate normally on medium and long wave, but the oscillator would squегg at around 100kHz on short wave, due to the excessive grid-bias time constant.

This dodge was sometimes used by unscrupulous radio dealers to 'rejuvenate' a set that no longer worked well on short wave, due to tired valves. The delighted customer would find that dozens of stations could be received again on short wave – just like when the set was new.

As the time constant CR is made longer, relative to the period of the oscillation, and the coupling of the feedback made tighter, the number of cycles in each burst of oscillation becomes smaller and smaller. Finally with very tight coupling, the circuit biases itself back to cut-off during the first cycle of oscillation following each recovery period: it becomes a relaxation oscillator.

Figure 2a) shows how the grid may

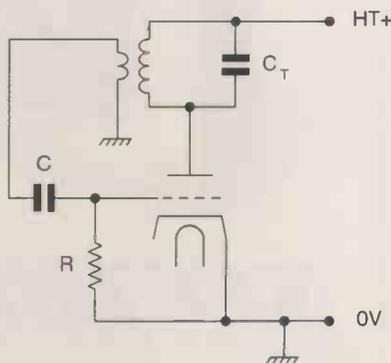


Fig. 1. Continuous-wave oscillator, squегger or blocker? It all depends.

be returned to a negative voltage just below cut-off, so that the circuit is monostable. It then only responds when it receives a trigger pulse.

Another common use for the blocking oscillator was as a frequency divider, Fig. 2b). Here, small positive-going trigger pulses of defined amplitude were applied to the grid of a blocking oscillator. The oscillator was designed to free run at just below the desired frequency, and thus fired slightly earlier when the appropriate Nth trigger pulse appeared.

With valves running on stabilised supplies, values of N up to about 5 were practical. Thus with one blocking oscillator dividing by two and another by five, a double triode implemented a decade divider.

Transistor blocking oscillators

Figure 3 shows the circuit of a particularly brutal transistorised version of the blocking oscillator. When the transistor cuts off, the collector voltage flies up positive, and the base voltage is driven negative.

Note that as is the common – but not invariable – practice with blocking oscillators, a closed magnetic path core was used to ensure tight coupling between the collector and base windings. In this case, the core was an FX2754 two-hole balun core with an A₁ of 3500nH/turn².

At switch-off, the current in the inductor cannot be instantly interrupted, and the collector voltage rises, in an attempt to maintain it. The collector voltage in fact reached +65V, higher than the minimum C_{cb0} rating of the BC107.

Due to the tight coupling, the voltage across the collector winding is reflected into the base winding as per the turns ratio. The base voltage reached -10V. This is well in excess of the rated V_{eb0} minimum of -6V, where it was clamped by the base emitter breakdown. Consequently, the voltage across the capacitor reached +25V before the stored energy was dissipated, the circuit recovered and the cycle repeated.

The on pulse width was 1.5µs and the off period, due to the very rapid dumping of the energy in internal breakdown of the device, was 300ns. Thus the pulse repetition frequency, or PRF, was 550kHz.

This is not a nice way to use a transistor, which is quite unlike a valve; that robust device can support enormous voltage excursions on anode and grid when cut off. The performance of the Fig. 3 circuit was therefore rendered more sanitary by connecting a diode to the collector, its cathode being returned to the +10V rail. Now, the operation of the circuit is completely

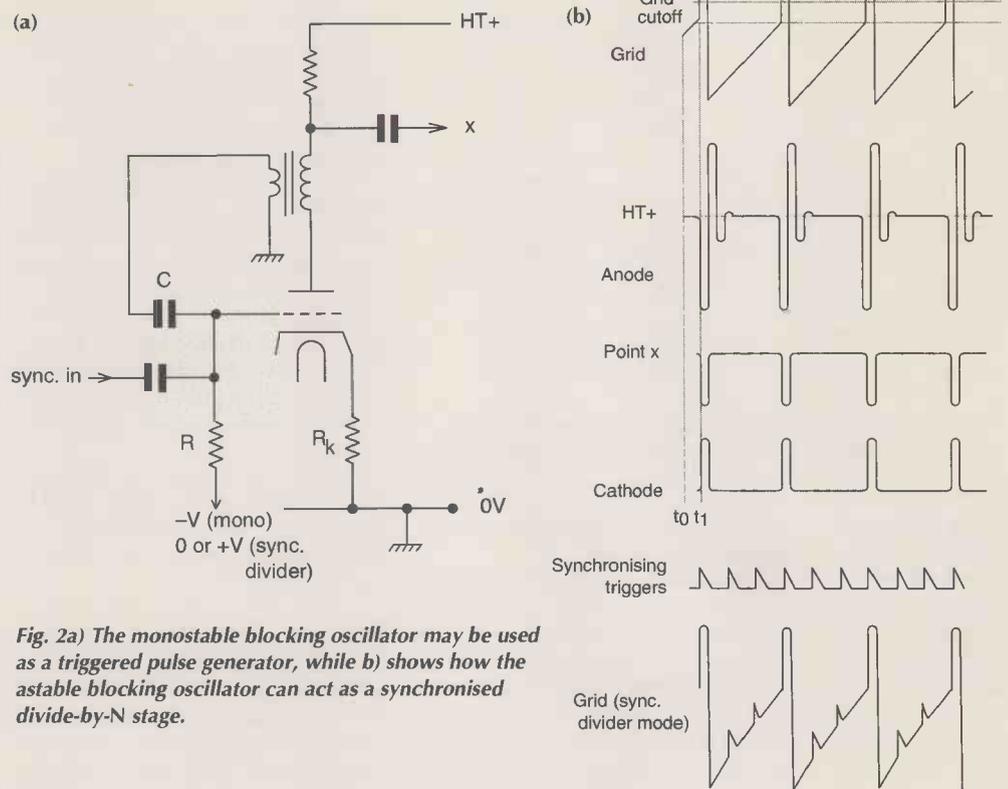


Fig. 2a) The monostable blocking oscillator may be used as a triggered pulse generator, while b) shows how the astable blocking oscillator can act as a synchronised divide-by-N stage.

changed. At no time does the voltage across the 100pF capacitor exceed +0.6V.

At 1.5µs, the on period was unchanged, but during the off period, the voltage across the collector winding was now just the small forward voltage drop of the diode. Consequently, the negative di/dt in the collector winding was also small, and the off period now extended to 15µs.

At the start of the on period, the voltage across the capacitor is driven negative, charge being drawn from it to supply the base current, charging it negative. However this source of base current soon becomes exhausted, and the available base current via the 330kΩ resistor is inadequate to keep the collector bottomed as the collector current continues to rise.

So the collector voltage starts to rise. This is reflected at the base as a negative excursion, rapidly cutting the collector current off completely. The base is now left at almost the negative voltage to which C was charged during the on period, since there is little voltage across the feedback winding.

The base voltage then rises, following a very linear ramp, as C is charged via R. This continues until it reaches about +0.6V, when the transistor starts to turn on and the cycle repeats.

With the circuit as described, the current in the collector winding does not quite have time to fall to zero before the base voltage reaches +0.6V and the cycle repeats. With two 1N4148 diodes

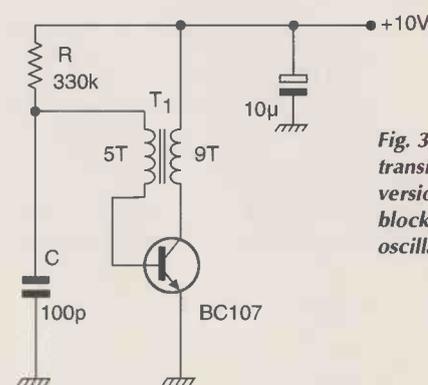



Fig. 3. A brutal transistorised version of the blocking oscillator.

in series, the higher off-period collector volts gives a larger -di/dt, and the voltage across the collector winding collapses from two diode drops to zero after 7µs.

Blocking-oscillator uses

Some of the blocking oscillator's uses have been mentioned already. But one characteristic of the circuit largely explains its popularity in the days of valves. For a given rail voltage, the period is determined by C, R and the transformer. In other words, it is determined by passive components of good long term stability.

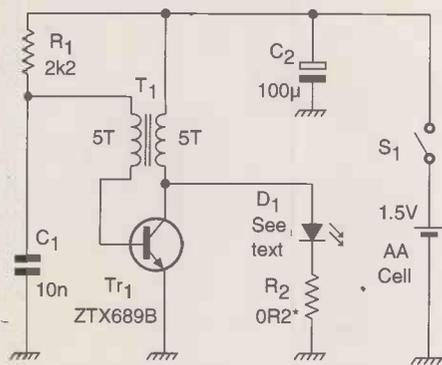The same goes for the transistorised version of Fig. 3, provided the diode is included, although the gain of the transistor has a second order effect on the period. For this reason, a popular version of the blocking oscillator for transistor applications applied the feedback



* For current waveform monitoring. Removed after tests.
T₁ windings, 26SWG Pri., 40 SWG sec., on FX2754 core

Fig. 4. Circuit of a blocking oscillator or self-excited flyback converter, arranged as a pocket emergency light.

to the emitter, using the device in the grounded base mode.

Even considering only the grounded emitter versions, however, there are various ways in which the blocking oscillator can operate. One of these, namely whether or not the current in the collector winding falls to zero in the off period, has already been mentioned. The other major factor is what causes the termination of the on period.

In the circuit of Fig. 3, it is the limited available base current. When the required collector current rises to a value beyond what this can support, the collector voltage must rise and the off transient follow. But if enough base current is available, the collector current can continue to rise until the core saturates. At this point, the voltage across the collector winding must fall.

However great $+dI/dt$ may be, the increase in flux $d\Phi/dt$ – and hence the back EMF – becomes negligible. In this entirely different mode of operation, the on period is determined by the core saturation characteristics.

This latter mode of operation gives a blocking oscillator which is in many ways similar to a currently much used circuit, the fly-back inverter. In the circuit of Fig. 3, with diode, instead of dumping the current back into the supply rail, the diode could be used to deliver it somewhere else. It could deliver it into a load, the other end of which is connected to ground for example.

Further, the voltage at which the energy is delivered to the load could be greater than the supply voltage: the blocking oscillator becomes a boost or flyback-inverter.

Efficient LED torch

I used a Zetex ZTX689B switching transistor in just such a blocking-oscillator/self-oscillating flyback inverter circuit as a handy compact emergency light. Two of these transistors were given away with the January issue of *Electronics World*.

In the interests of compactness, a single AA cell was used as the power source, and in the interests of efficiency, an LED was used as the light source.

The voltage of the cell is too low to power the LED directly. But even if two cells were used, there would be the problem of defining the current, given

the variation of supply voltage over the life of the battery. The blocking oscillator action solves the problem, maintaining a constant efficiency over the supply voltage range 1.5V down to 1V.

Figure 4 shows the circuit diagram. Compared to Figure 3, the base drive resistor is very low, despite the high gain of the transistor. The reason is twofold: firstly the low supply voltage, not greatly in excess of the transistor's V_{be} , and secondly the mode of operation. This is an example of a blocking oscillator, where the on period terminates due to saturation of the transformer core.

Figure 5, lower trace shows current through the LED, monitored across a 0.2Ω resistor. Given the 20mV/division Y sensitivity, the peak current is seen to be 280mA, while its average value measured 27mA – well within the 50mA dc maximum rating of the device used.

Just before the end of the off period, LED current falls to zero. This is indicated by the small ringing on the collector voltage trace, Fig. 5, upper trace 2V/division vertical, 5µs/division horizontal.

Note that when the transistor switches off, the current continues to flow unchanged through the transistor as the collector volts rise, until the point at which the LED conducts. Thus there is a turn-off switching loss in the transistor. This is unavoidable, but small, due to the fast switching speed of the transistor, the characteristics of which were published in the January issue.

However, with the LED current having fallen to zero just before switch-on, there is no corresponding turn-on loss. Note also the transistor's very low saturation voltage – only some 200mV at 300mA collector current shown in the upper trace of Fig. 5.

The upper trace of Fig. 6 illustrates the base voltage at 2V/division being clamped at the transistor's $V_{be(on)}$ during the active part of the cycle, and being driven to -3.8V peak at switch-off. The lower trace of Fig. 6 shows the voltage across the 10nF capacitor.

Given the transformer's 1:1 ratio, during the active part of the cycle, this voltage sits negative with respect to the base by the same voltage as appears across the collector winding. Following switch-off, the capacitor charges up via the $2.2k\Omega$ resistor.

During the latter part of this process, the LED current having terminated, the voltage across the feedback winding is zero. So when the voltage across the 10nF capacitor reaches +0.6V, the transistor turns on and the cycle repeats.

20000mcd with one cell

The prototype torch used a Toshiba

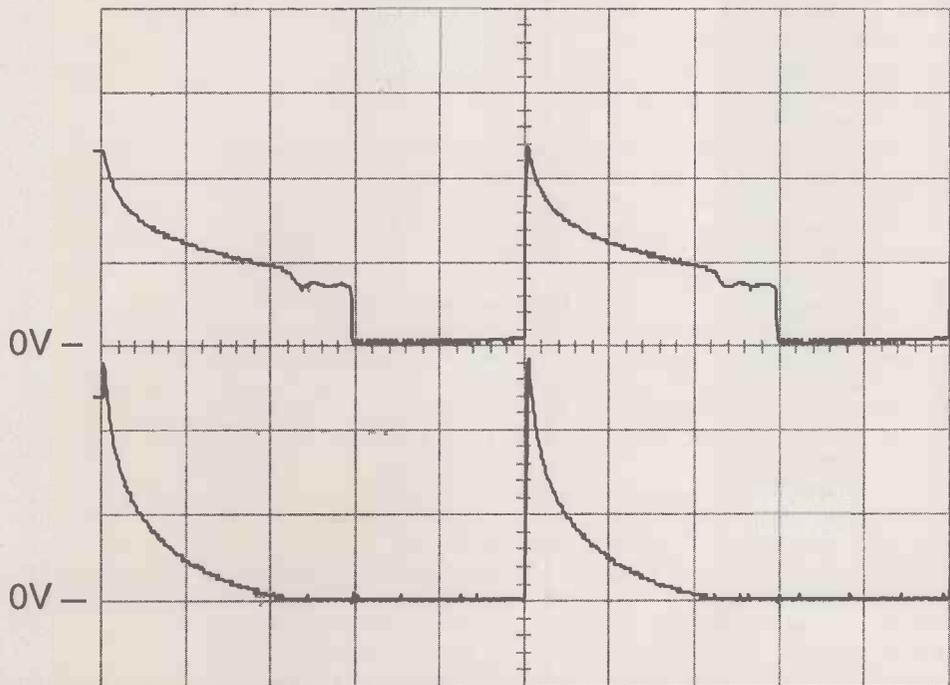


Fig. 5. Collector voltage, upper trace, 2V/div vertical, 5µs/div horizontal. Lower trace shows current through the LED, monitored across a 0.2Ω resistor, 20mV/div, 5µs/div.

Telnet

Tel: 01203 650702

Hewlett Packard

8642A - high performance R/F synthesiser
(0.1-1050MHz) £6500
3335A - synthesiser (200Hz-81MHz) £2750

Hewlett Packard

436A power meter and sensor (various) from £900
437B power meter and sensor (various) from £1250

Hewlett Packard

8753A network analyser (3GHz) from £3000
8753B network analyser (3GHz) from £4000
'S' parameter test sets 85046A and 85047A
available at £2500 & £3000

Wandel & Goltermann

PFJ-8 - error and fitter test set
(all options fitted) £POA
PCM 4 - PCM channel measurement set £9500

Marconi

2305 - modulation meter £1750
6310 - programmable sweep generator
(2 to 20GHz) - new £3500

Hewlett Packard

5342A - microwave frequency counter
(500MHz-18GHz) ops 1 & 3 £800
5370B - universal time interval counter £2000

OSCILLOSCOPES

Beckman 9020 - 20MHz - Dual channel £150
Hewlett Packard 54100D - 1GHz Digitizing £1250
Hewlett Packard 54201A - 300MHz Digitizing £1250
Hewlett Packard 54512B (300MHz-1G s/s) - 4 channel £POA
Hitachi V152/V212/V222/V302B/V302F/V353F/V550B/V650F
Htachi V1 100A - 100MHz - 4 channel from £125
Intron 2020 - 20MHz - Dual channel D.S.O. (new) £900
iwatsu SS 5710/SS 5702 - £450
Kikusui COS 5100 - 100MHz - Dual channel from £125
Lecroy 9450A - 300MHz/400 MS/s D.S.O. 2 channel £350
Lecroy 9304 AM - 200MHz - 4 channel DSO £2250
Meguro MSO 1270A - 20MHz - D.S.O. (new) £3000
Philips 3055 - 50MHz - Dual channel £450
Philips PM 3335 - 50MHz - D.S.O. Dual channel £950
Philips 3295A - 400MHz - Dual channel £1600
Tektronix 465 - 100MHz - Dual channel £350
Tektronix 464/466 - 100MHz - (with AN. storage) £350
Tektronix 475/475A - 200MHz/250MHz - from £450
Tektronix 468 - 100MHz - D.S.O. £650
Tektronix 2213/2215 - 60MHz - Dual channel £350
Tektronix 2220 - 60MHz - Dual channel D.S.O. £1250
Tektronix 2225 - 50MHz - Dual channel £395
Tektronix 2235 - 100MHz - Dual channel £600
Tektronix 2221 - 60MHz - Dual channel D.S.O. £1250
Tektronix 2245A - 100MHz - 4 channel £900
Tektronix 2440 - 300MHz/500 MS/s D.S.O. £2950
Tektronix 2445A - 150MHz - 4 channel £1200
Tektronix 2445 - 150MHz - 4 channel + DMM £1200
Tektronix TAS 475 - 100MHz - 4 channel £995
Tektronix 7000 Series (100MHz to 500MHz) from £200
Tektronix 2211 - 50MHz - 2 channel DSO £950


SPECTRUM ANALYSERS

Ando AC 821 1 - 1.7GHz £1995
Avcom PSA-65A - 2 to 1000MHz £850
Anritsu MS 62B - 50Hz to 1700MHz £1995
Anritsu MS 610B - 10KHz - 2GHz - as new £4500
Advantest/TAKEDA RIKEN - 4132 - 100KHz - 1000MHz £2100
Hewlett Packard 3562A Dual channel dynamic signal analyser
64µHz - 100KHz £5750
Hewlett Packard 3585A - 20Hz to 40MHz £4000
Hewlett Packard 8505A - 1.3GHz - Network Analyser £1995
Hewlett Packard 8756A/8757A Scaler Network Analyser from £1000
Hewlett Packard 853A Mainframe + 8559A Spec. An. (0.01 to 21GHz) £3000
Hewlett Packard 182T Mainframe + 8559A Spec. An. (0.01 to 21GHz) £2500
Hewlett Packard 8569B (0.01 to 22GHz) £4000
IFR A7550 - 10KHz-1GHz - Portable £2500
Meguro - MSA 4901 - 30MHz - Spec.Analyser £850
Meguro - MSA 4912 - 1 MHz - 1GHz Spec.Analyser £1250
Stanford Research SR760 (100KHz-FFT analyser) £2300
Tektronix 495P Spec analyser prog. - 1.8GHz £4500

Quality second-user test & measurement equipment

Radio Communications Test Sets

Marconi 2955 - calibrated £2000
Marconi 2955A - calibrated £2250
Marconi 2955R - calibrated £3750
Marconi 2958/2960 £2250
Anritsu MS555A2 £1200
Hewlett Packard 8920A £2000
Hewlett Packard 8922B (GSM) £7500
Hewlett Packard 8922G/H/M (GSM) £POA
Schlumberger Stabilock 4031 £4995
Schlumberger Stabilock 4040 £1995
Racal 611 (GSM) £2500
Racal 6115 (GSM) £5000
Rhode & Schwarz CMS 54 (new) £6250
Rhode & Schwarz CMTA 94 (GSM) £6950
IFR 1200S (calibrated) £2995

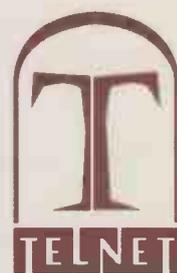

Fax 01203 650 773

Tektronix 469P - 1KHz to 1.8GHz £4250
Wiltron 6409 - 10-2000MHz R/F Analyser £2000

MISCELLANEOUS

Eaton 2075 - Noise Gain Analyser £POA
Farnell AP30250 - Power Supply 30V-250amp £1750
Fluke 5100A/5100B/5220A/5200A - Calibration Units (various available) £POA
Fluke 2625/2635 Data Buckets (various) £POA
GN ELM1 EPR31 - PCM Signalling Recorder £3000
Hewlett Packard 6033A - Autoranging System PSU (20v-30a) £750
Hewlett Packard 6632A - System Power Supply (20v-5A) £2800
Hewlett Packard 3784A - Digital Transmission Analyser £5000
Hewlett Packard 3785A - Jitter Generator & Receiver £1250
Hewlett Packard 5370B - Universal Time Interval Counter £2000
Hewlett Packard 8660D - Synth'd Sig. Gen (10 KHz-2600MHz) £3,250
Hewlett Packard 4192A - LF Impedance Analyser £6750
Hewlett Packard 16500C - Logic Analyser Mainframe £4750
Hewlett Packard 16501A/B & C - Logic Analyser System Expander Frame from £2000
Hewlett Packard 6624A - Quad Output Power Supply £2000
Hewlett Packard 6652A - 20V-25A System PSU £750
Hewlett Packard 8350B - Sweep Generator Mainframe £2000
Hewlett Packard 75000 VXI Bus Controllers £POA
HP 339A Distortion measuring set £1500
HP 3488A - Switch/Control unit £650
HP 435A + 435B Power meters from £200
HP 8656A Synthesised signal generator £850
HP 8656B Synthesised signal generator £1450
HP 8657A - Signal generator 100KHz - 1040MHz £1900
HP 37300D - Signalling test set £4250
HP 5385A - 1 GHz Frequency counter £750
HP 8901B - Modulation Analyser £3750
HP 8903B and E - Distortion Analyser from £2000
HP 5359A - High Resolution Time Synthesiser £2950
Keytek MZ-15/EC Minizap ESD Simulator (15kv - hand held) £1750
Marconi 2610 True RMS Voltmeter £700
Marconi 6950/6960 Power Meters & Sensors from £500
Phillips 5515 - TN - Colour TV pattern generator £1500
Leader 3216 Signal generator 100KHz - 140MHz - AM/FM/CW with built in FM stereo modulator (as new) a snip at £995
Racal 9087 - 1.3GHz Synthesised Signal Generator, low noise £2250
Racal 1992 - 1.3GHz Frequency Counter £600
Rohde & Schwarz 5MY-01 Signal Generator (9KHz-1040MHz) £2250
Rohde & Schwarz NRV Power Meter & NRV-Z2 Sensor £1250
Systrom Donner 6030 - 26.5GHz Microwave Freq Counter £2250
Wandel & Goltermann PRA-1 - Frame Analyser £5250
Wayne Kerr 3245 - Precision Inductance Analyser £2250
Wiltron 6474A-20 - 10MHz-20GHz - Swept Frequency Synthesiser £4950

All equipment is used - with 30 days guarantee.

Add carriage and VAT to all goods.

Telnet, 8 Cavans Way, Binley Industrial Estate,
Coventry CV3 2SF.

CIRCLE NO. 110 ON REPLY CARD

Tel: 01203 650702

Fax: 01203 650 773

Table 1. Comparison of three torch 'technologies' – two using LEDs, the other an incandescent lamp.

	Current	Brightness*	Power (mW)	Efficiency††
Red LED torch	91mA	100	126	0.79
Amber LED torch†	70mA	500	96	5.2
2.5V bulb torch	250mA	8500	643	13.2

† at 1.37V – the AA cell being used was not new.

* EAU, equivalent arbitrary units. 100 = full scale on range 1 – the most sensitive – range 2 has a tenth of the sensitivity, range 3 one hundredth, etc.

†† Relative values, calculated as EAU/mW.

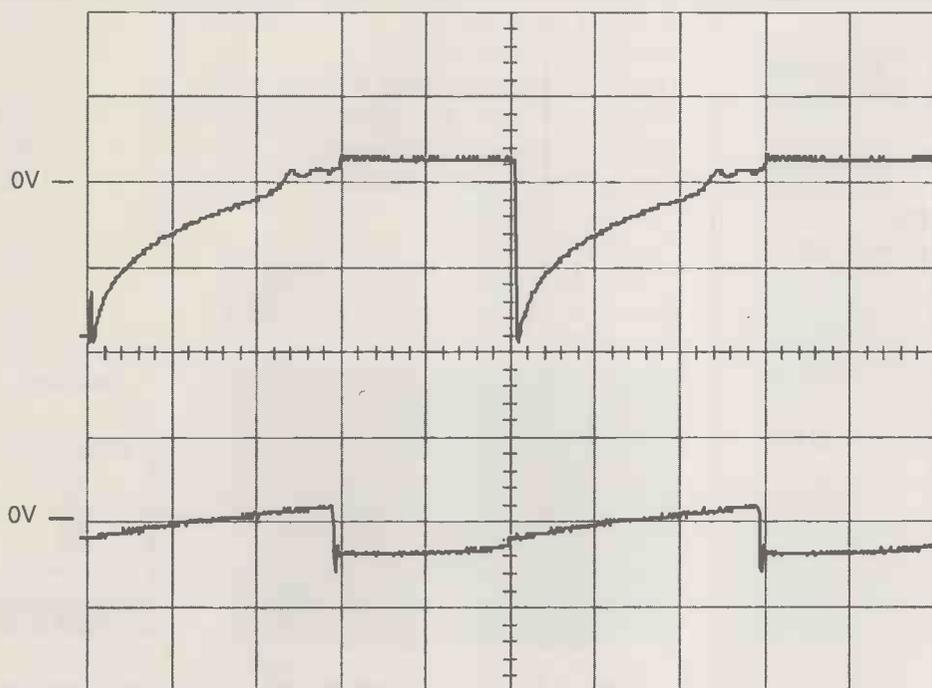


Fig. 6. Base voltage, 2V/div vertical, 5µs/div horizontal, lower trace and voltage across the 10nF capacitor, upper trace, 2V/div, 5µs/div.

TLOH 190P amber coloured LED, a InGaAlP device with a very narrow beamwidth of less than 10° at half intensity. The on-axis luminous intensity of this is rated as 20000mcd typical – 8500mcd minimum – at 20mA.

I constructed an earlier version of the torch in one of the small transparent plastic boxes used by semiconductor manufacturers for supplying samples. However, 'transparent' is a relative term, and tests with my light meter⁶ showed that although water clear to look at, such a box passed only about 90% of the available light. So the new version was built in a similar box – black, as it happens – but with the lens body of the device projecting through a hole in the end of the box.

I carried out some simple tests with the light meter, to compare the new version as per Fig. 4 with two earlier torches. One of the earlier designs used

a red LED rated at 3000mcd at 20mA, the other had two NiCd C-type cells and a 2.5V 250mA prefocus bulb.

The tests were carried out with the three torches, each at 1m from the lightmeter, and the results are in Table 1. Performance of the amber LED torch with supply voltage is shown in Table 2. You can see that at 1.0V, the unit provided 57% of the light for 51% of the power, compared with a supply voltage of 1.5V

Finding a matching hat

The results quoted above should be interpreted with caution, for the light meter was fitted with an unfiltered silicon photodiode detector. For true photometric measurements, indicating apparent brightness to the human eye, a photometric filter would be needed. This has a greenish tinge when viewed against daylight, and so the red LED

Table 2. Benefits of using a LED relative to using an incandescent lamp become clear when battery voltage starts to fall. These figures are for the amber LED torch.

Supply	Current drawn	Power	Light out*	Light/power
1.5V	72mA	108mW	35	0.32
1.0V	55mA	55mW	20	0.36

torch would have fared somewhat worse.

But some conclusions can be drawn. For efficiency, the incandescent bulb wins hands down – at least with fresh batteries. But to get that efficiency, you have to supply over half a watt. Scaling down lamp performance is simply not possible.

It is very difficult to obtain any reasonable bulb efficiency at much less than 250mA. Thus while the amber torch gives only one seventeenth of the brightness at one seventh of the power, you would get even less light than the amber LED gives if you tried to run a filament bulb at 96mW.

Furthermore, as shown above, the light output of the LED torch is proportional to the power drawn. But with the conventional torch, as the battery voltage falls, the lamp dims very rapidly. The cooler filament not only emits less light, but its resistance falls, so the current does not fall in proportion to the reduction in voltage. The result is a drastic reduction in both light output and efficiency as the battery ages.

There is a wide choice of LEDs for a small torch of the type described. If brightness is the chief criterion, a LED such as the Toshiba TLOH 190P or a high brightness type from another manufacturer is ideal. However, these devices concentrate the available light into a very narrow beam. If total light output, measured in lumens, is more important than brightness, measured in candelas, then a high-efficiency LED is more appropriate. Hewlett-Packard's HPWT-DL00 is a good example.

On this basis, the red-LED torch described was not so poor as might seem from the results. Its beam was a good deal broader than that of the amber LED, so its total light output, relative to the amber LED with its narrow beam, was probably not inferior.

But comparing total light output between devices is a much more complex task than merely comparing brightness, and quite beyond the capability of my equipment. ■



References

1. Ridenour, L N, 'Radar System Engineering,' McGraw-Hill 1947.
2. Williams, E, 'Thermionic Valve Circuits,' Pitman 1955.
3. F E Terman, F E, 'Electronic and Radio Engineering,' McGraw-Hill 1955.
4. 'The Encyclopaedia of Radio and Television,' Odhams 1957.
5. Martin Jr., T L, 'Electronic Circuits,' Prentice Hall 1959.
6. Hickman, I, A look at light, *Electronics World*, June 1997, pp. 466-471.


We make our programmers work harder

FEATURES

- ◆ Supports EPROMs, EEPROMs, Flash, Serial PROMs, BPROMs, PSDs, PALs, GALs, PEELs, MACH, MAX, EPLDs, and over 200 Microcontrollers including 87C48/51, 89C51/52, PIC, MC705/711, ST6, Z86, COP etc.
- ◆ Hands free programming so you can produce batches of the same chip without pressing a key
- ◆ Correct programming and verification at 1.8, 2.7, 3.3 and 5V
- ◆ Serial number mode supports date/time stamping, unique IDs
- ◆ Progress indicator shows number of devices programmed
- ◆ No adapters required for DIL parts upto 48-pins. Universal adapters for 44-pin PLCC, 44-pin PSOP and 48-pin TSOP parts
- ◆ Programmes and verifies Intel 28F400 in under 15 seconds
- ◆ Connects to parallel port - no PC cards needed
- ◆ Tests 7400, 4000, DRAM and SRAM
- ◆ Mains or battery operation
- ◆ FREE software device support upgrades via bulletin board and www

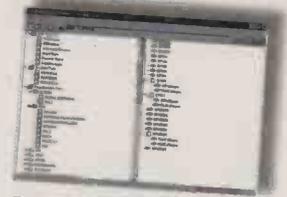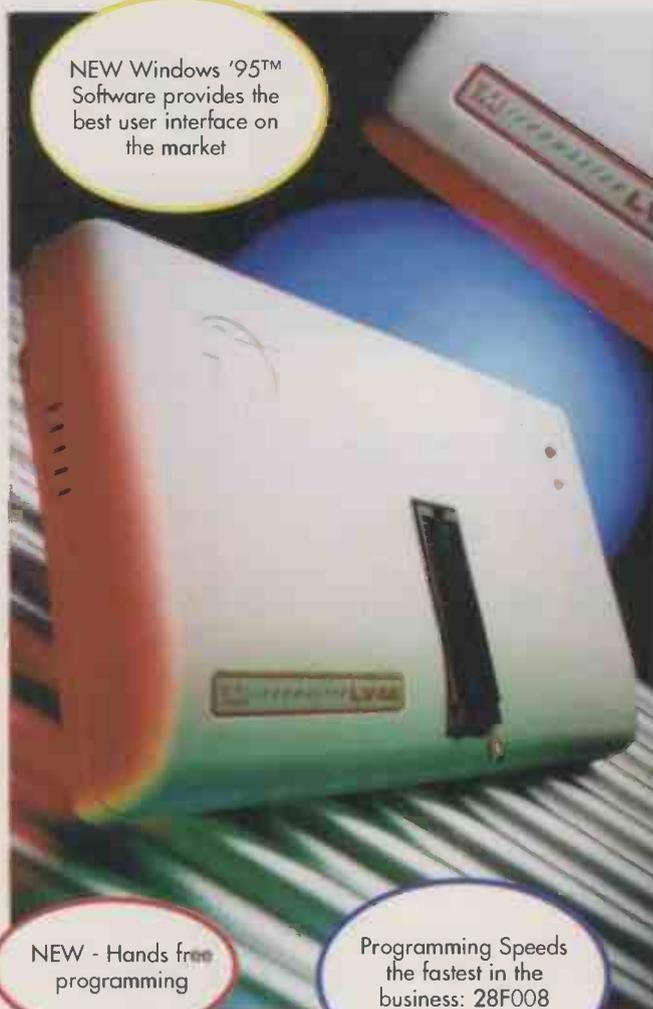

Easy device selection.

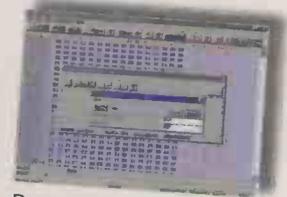

Programming, Emulation, Testing all in one easy to use application.



Full support for device-specific features



Store your favourite projects...

48-pin Universal Programmer
STILL ONLY

£695



SPEEDMASTER GLV32 £695



LV40 PORTABLE £995

PROGRAMMER MODELS AND PRICES

SINGLE SOCKET PROGRAMMER			EMULATOR OPTIONS			GANG PROGRAMMERS		
			FOR ALL PC BASED PROGRAMMERS					
MICROMASTER LV48	48-pin universal programmer	£695	LVECEMUL8	128kx8 ROM/RAM emulator with modify on the fly feature Upgradable to 512x8	£125	SPEEDMASTER GLV32	8-way 32-pin EPROM/Flash Gang/Set programmer	£695
SPEEDMASTER/MICROMASTER	40-pin programmer range (see website or call for model details)	FROM £395				SPEEDMASTER GLVCOP	8-way 40-pin gang programmer for National Semiconductor COP micros	£1500
EPMASTER LV	40-pin EPROM/Flash programmer	£295	LVECEMUL16	128x16 ROM/RAM emulator with modify on the fly feature Upgradable to 512x16	£195	SOCKET ADAPTERS	Full range of adapters for PLCC, SOIC, TSOP, PSOP etc...	FROM £65
LV40 PORTABLE	As Micromaster LV, plus completely portable with built in keypad and LCD display.	£995						

All prices exclude VAT and delivery

See for yourself - download a demo from our Website at www.icetech.com

ORDER NOW - ALL PRODUCTS IN STOCK. CREDIT CARD ORDERS: 01226 767404

For a copy of our catalogue giving full details of programmers, emulators, erasers and adapters, call, fax or e-mail us. You can also access our BBS or Home page. All our products are in stock now for next day delivery - call our credit card hotline now.



ICE Technology Ltd. Penistone Court, Sheffield Road, Penistone, Sheffield, UK S36 6HP

Tel: +44 (0)1226 767404 Fax: +44 (0)1226 370434 BBS: +44 (0)1226 761181 (14400,8N1)

Web: www.icetech.com. Email: sales@icetech.com

CIRCLE NO. 111 ON REPLY CARD





**Unique reader offer:
x1, x10 switchable
oscilloscope probes,
only £21.74 a pair,
fully inclusive***

*Additional pairs as part of the same order, only £19.24 each pair.

Seen on sale for £20 each, these high-quality oscilloscope probe sets comprise:

- two x1, x10 switchable probe bodies
- two insulating tips
- two IC tips and two sprung hooks
- trimming tools

There's also two BNC adaptors for using the cables as 1.5m-long BNC-to-BNC links. Each probe has its own storage wallet.

To order your pair of probes, send the coupon together with £21.74 UK/Europe to Probe Offer, Electronics World Editorial, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Readers outside Europe, please add £2.50 to your order.

Please supply the following:

Probes

Total _____

Name _____

Address _____

Postcode _____ Telephone _____

Method of payment (please circle)

Cheques should be made payable to Reed Business

Information

Access/Mastercard/Visa/Cheque/PO

Credit card no _____

Card expiry date _____ Signed _____

Please allow up to 28 days for delivery

Specifications

Switch position 1

Bandwidth	DC to 10MHz
Input resistance	1MΩ – i.e. oscilloscope i/p
Input capacitance	40pF+oscilloscope capacitance
Working voltage	600V DC or pk-pk AC

Switch position 2

Bandwidth	DC to 150MHz
Rise time	2.4ns
Input resistance	10MΩ ±1% if oscilloscope i/p is 1MΩ
Input capacitance	12pF if oscilloscope i/p is 20pF
Compensation range	10-60pF
Working voltage	600V DC or pk-pk AC


Switch position 'Ref'

Probe tip grounded via 9MΩ, scope i/p grounded

Pay this:



for this:

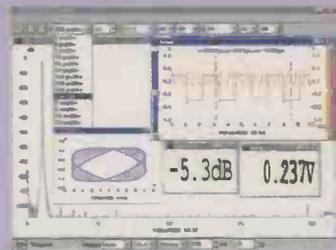

or

Pay this:



for this:




Easy choice? Then send for the Pico Technology full colour PC based test & measurement catalog and software demonstration diskette. Alternatively, visit our web site:

www.picotech.com

Use a Pico ADC together with the supplied software and transform your PC into an oscilloscope, spectrum analyser, multimeter, data logger and chart recorder. Virtual instruments replace bulky and expensive test equipment, saving money and workbench space. They make switching between instruments quick and easy. Pico Technology virtual instruments are easier to use than traditional instruments: simple to use software and on-screen help makes you an expert within minutes.

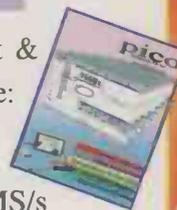- ▼ Up to 100MS/s
- ▼ Up to 16 bit resolution
- ▼ Prices from £59



pico
Technology Limited



Tel: +44 (0)1954 211716, Fax: +44 (0)1954 211880, E:mail: post@picotech.co.uk, Web: www.picotech.com

CIRCLE NO.112 ON REPLY CARD

"We never expected PCB Layout power at this price..."

EASY-PC FOR WINDOWS the top selling advanced printed circuit board and schematic design system brings you a simple and intuitive user interface with a set of powerful features normally only found in the most expensive packages.

- True Windows graphical user interface
- Easy to learn and use
- Full connectivity between SCM and PCB
- Full multi-level Undo and Redo
- Multi-Sheet project based design
- 0.1 Micron system resolution
- Unlimited layers, electrical and non-electrical
- Uses technology files for 'fast start' designs
- OrCAD and IMT EDA Workbench schematics netlist import
- Intelligent circuit copy and paste within and across designs
- Cut, copy and paste to external Windows applications
- Extensive design rules and connectivity checking / reporting
- Features a comprehensive set of libraries including SMT devices
- Automatic links to our Analogue, Digital & Electromagnetic simulators
- Runs under Windows 95/98™ and Windows NT™
- Available as Unlimited, 2000 pins, 1000 pins and 500 pins variants

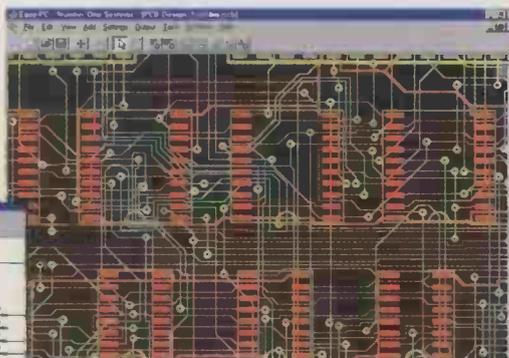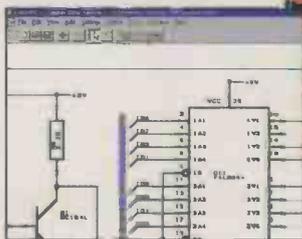

Easy-PC For Windows
from
Number One Systems
The Electronics CAD Software Specialists

Visit our web site at www.numberone.com
or Email us on sales@numberone.com
or call sales on 01684 773662 or fax 01684 773664

Sightmagic Ltd, Oak Lane, Bredon,
Tewkesbury, Glos, GL20 7LR, UK

Number One Systems and Easy-PC are trademarks of Sightmagic Ltd.
All other trademarks are acknowledged to their rightful owners.

CIRCLE NO.113 ON REPLY CARD

CIRCUIT IDEAS

Readers' circuit ideas published here earn their authors £35 or more. The month's top idea, or ideas, see anything up to £100 – sometimes more. All we ask is that the ideas you send in should be original to the best of your knowledge. Useful enhancements to previously published circuits are considered, but please be sure to acknowledge the original circuit.

Hysteresis in a digital circuit

It may be useful to arrange digital hysteresis, whereby an event occurs at a certain digital input number in an 'upward' direction and at a lower digital input in the reverse direction; digital hysteresis, in fact.

This circuit performs that function.

Imagine that input nibble A_{1-4} , i.e. DA, to the 4019 quad switch is fixed at eight, say

and the input on B_{1-4} , i.e. DB, is six.

When the input nibble DI at the top of the diagram is 0, o/p OUT12 of the 4585 comparator is high. On the switch, select inputs G_1 and G_2 are 1 and 0 respectively, so nibble DA, i.e. 8, is fed to the comparator's B input nibble.

When the input counts reaches 8, OUT12

goes low. Now DB is feeding the comparator so OUT12 only goes high again when input DI decreases to less than DB – i.e. 6.

Figure 2 shows the timing involved.

W Dijkstra

Waalre

The Netherlands

C67

(C67a)

$A_1-A_4 = 8-DA$

$B_1-B_4 = 6-DB$

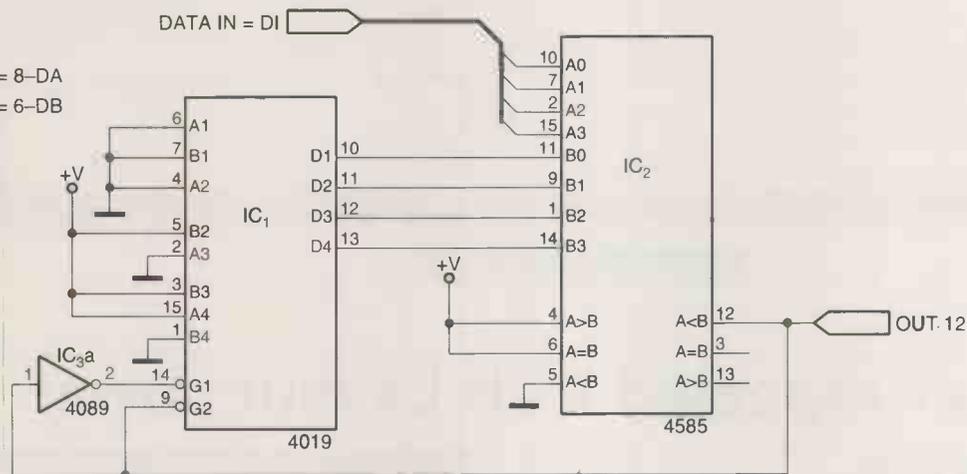


Fig.1. Digital circuit changes state at one count going up and at a lower count coming down – 8 and 6 as shown here. It is a form of digital hysteresis.

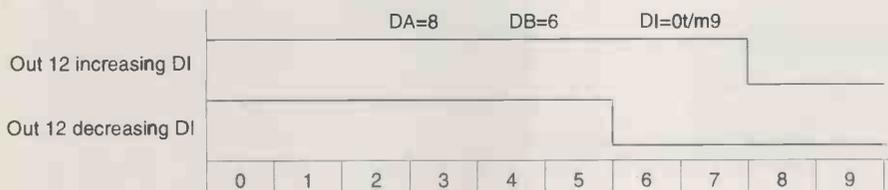


Fig.2. Timing diagram of the hysteresis switch, with switching points at 6 and 8.

(C67b)



Fact: most circuit ideas sent to *Electronics World* get published

Like life, *Electronics World* may seem surreal at times, but it is certainly not exclusive. Clearly, the best circuit ideas are ones that save time or money, or stimulate the thought process. This includes the odd solution looking for a problem – provided it has a degree of ingenuity.

Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too – provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though.

Don't forget to say why you think your idea is worthy.

Clear hand-written notes on paper are a minimum requirement: disks with separate drawing and text files in a popular form are best – but please label the disk clearly.

15 years of quality...

...makes all the difference

Faraday Technology is celebrating 15 successful years and would like to thank all our customers for their support



Faraday Technology Limited Croft Road Industrial Estate
Newcastle Staffordshire ST5 0QZ England
Tel: +44 (0)1782 661501 Fax: +44 (0)1782 630101
email: sales@faradaytech.co.uk <http://www.faradaytech.co.uk>

CIRCLE NO.114 ON REPLY CARD

CONTROL & ROBOTICS from Milford Instruments

BASIC Stamps-

- Re-Programmable
- BASIC language
- RS232 Serial ports
- 8 or 16 I/O lines
- SPI/DTMF
- Fast development



Scenix

- Fastest 8-bit micro
- 50MIPS
- Flash Eprom
- 18/28 pins
- PIC16C5x pin replacement




Serial LCDs

- RS232 Serial interface
- 2x16 to 4x40
- Simple 3-pin connection
- Integral Keypad option
- Large Numerics option
- Driver chips available for OEM use



Robotics

- Humanoid
- 5-Axis Arm
- Walking Insect

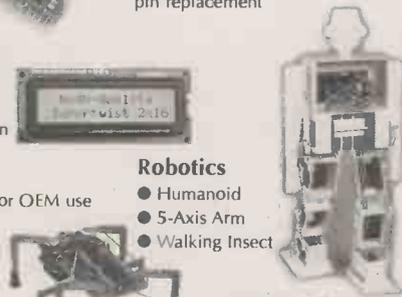

3-Axis Machine

- Stamp 2 based
- Drills PCBs
- 3-Axis movement
- Stepper drive
- 4 thou resolution
- Win 3.1 software



Servo Controller

- Control up to 8 servos
- RS232 Commands



IR Decoder

- Uses any remote
- 7 digital outputs
- Toggle/momentary
- Re-Programmable

Milford Instruments 01977 683665 www.milinst.demon.co.uk

CIRCLE NO.115 ON REPLY CARD

CROWNHILL ASSOCIATES LIMITED

The Old Bakery, New Barns Road,
Ely, Cambs. CB4 7PW
Tel: +44 (0)1353 666709 Fax: +44 (0)1353 666710

Low cost professional quality Smart Card Systems

CHIPDRIVE

The intelligent programmer for Smart Cards using the International Standard T=0 or T=1 protocols also Memory and Secure Memory using I²C, 2-wire & 3-wire interfaces. From April 1999 all ChipDrives are supplied with software to read and write to most popular secure smart cards, inc GSM, PAY PHONE and ACCESS CONTROL cards. Drivers are available for Apple Macintosh, Linux, Unix, Solaris. Microsoft PC/SC and of course WINDOWS 95/98 and NT.

Supplied with CARDSERVER API for easy development of SmartCard Applications using Visual Basic, Delphi or C++.



CHIPDRIVE INTERN
£49.95 + P&P £7.50
Exclusive of VAT

CHIPDRIVE ExTERN
£49.95 + P&P £7.50
Exclusive of VAT



CHIPDRIVE Micro
£39.95 + P&P £7.50
Exclusive of VAT



All Chipdrives are supplied with a Windows API and full documentation. ChipDrives are CE Compliant ChipDrives conform to ISO7816, T=0 or T=1 @ 3.579MHz, RS232 @ 9600-11500 bps, Internal Supply/Ni-MH. Under normal conditions power is derived from the host Serial Port. Operation is simple, full telephone and email support is provided for Windows developers.

APP-LOCK

Protect any Windows applications from Unauthorised access under Win 95/98/NT
Inclusive of Chipdrive Intern, Smart Card and Software.

FREE GSM CARD READING application supplied with CHIPDRIVE-micro

CHIPDRIVE Developer Kit

CDK consists of: CD ROM containing cardserver.dll. Applications and Source code examples. CHIPDRIVE-micro a selection of Smart Cards offering protected memory, processor and memory cards. Typical uses are Control access, Pay Phone cards and Data transport. PIN codes for the cards are supplied along with data sheets and programming data for use with cardserver.dll. A useful application with source codes shows how the CHIPDRIVE can be used to identify any Smart card inserted, giving manufacturer info, and memory map if available. Applications produced with the developer kit will operate under Windows 3.11/95/NT and are compatible with the whole CHIPDRIVE family. The CDK uses easy to use 16 bit or 32 bit DLLs with just one function call to the 'CardServer' to identify the card or carry out any instruction. Cardserver is a powerful Background task which relieves the application programmer from device and card administration. Featuring automatic protocol and card type detection. Allowing several applications to access one terminal dependent only on the type of card inserted.



£69.95 + P&P £5 Exclusive of VAT

Supplied with CHIPDRIVE micro, Smart Cards and Source Code. Full Tech Support via Email.

<http://www.towitoko.co.uk>

<http://www.crownhill.co.uk>

<http://edsim.cambs.net>

CONTACTLESS SMART CARD DEVELOPMENT SYSTEM HITAG™ Cards

The Contactless Reader/Writer is designed to communicate via an RF field with the HITAG™ range of contactless cards. A simple ASCII based command set allows direct access to the powerful features that enable data to be read and written to the card at distances up to 150mm. A RS485 multi drop facility is built onto the reader/writer unit allowing daisy chaining of up to 32 devices. Communication is via an onboard configurable RS232 Port A sounder, two opto isolated outputs, 4 LED's and 2 high current open drain Mosfets are available for interfacing.



£149.95 + P&P £5 Exclusive of VAT

CIRCLE NO.1 ON REPLY CARD

£100
WINNER

Programmable precise one-shot covers microseconds to hours

Listing for a PIC-based one shot that provides precise programmable pulse widths anywhere between 9µs and three hours long.

Traditional one-shot circuitry uses a resistor and a capacitor to determine the pulse width.

If the capacitor is fixed, a potentiometer can adjust the width within a certain range. For a longer pulse width, the capacitor becomes bulky and its leakage current could be an issue.

Figure 1 circuit uses a PIC16C84 to form a one-shot. Not only can the

pulse width be programmed from 9µs to more than 3 hours, but it also maintains high accuracy – an error of less than 0.3% within a –20°C to 85°C temperature range.

Since the PIC16C84 has built-in EEPROMs, The pulse width information is stored in the PROM and is retrieved at power on.

An input trigger signal generates an

interrupt for the microcontroller. In the interrupt service routine, PB5 is set to high before going into a delay loop. In the delay loop, a 32-bit counter that is formed by four 8-bit registers must decrease to zero before PB5 is set to low and then returns. Thus, the larger the number in the 32-bit counter, the wider the output pulse will be. The pulse width in

```

LIST p=16C84
#include "P16C84.INC"
cnt_1 equ 0x10
cnt_2 equ 0x11
data_1 equ 0x12
data_2 equ 0x13
data_3 equ 0x14
data_4 equ 0x15
bit_num equ 0x16
temp_1 equ 0x17
temp_2 equ 0x18
temp_3 equ 0x19
temp_4 equ 0x1a
temp_5 equ 0x1b

org 0x0
goto main
org 0x4
bsf PORTB, 5
loop decfsz temp_1, F
goto loop
decfsz temp_2, F
goto loop
decfsz temp_3, F
goto loop
decfsz temp_4, F
goto loop
bcf PORTB, 5
movf data_1, W ; re-load data
movwf temp_1
incf temp_1, F
movf data_2, W
movwf temp_2
incf temp_2, F
movf data_3, W
movwf temp_3
incf temp_3, F
movf data_4, W
movwf temp_4
incf temp_4, F
bcf INTCON, INTF
refie

main clrf PORTA
clrf PORTB
bsf STATUS, RP0 ; bank 1
movlw 0x40
option
movlw 0x00
movwf TRISA
movlw 0x0f
movwf TRISB
movlw 0x10
movwf INTCON
bcf STATUS, RP0 ; bank 0
clrf EEADR
bsf STATUS, RP0 ; bank 1
bsf EECON1, RD
bcf STATUS, RP0 ; bank 0
movf EEDATA, W ; read data_1 from eeprom
movwf data_1
movwf temp_1
incf temp_1, F
incf EEADR, F
bsf STATUS, RP0 ; bank 1
bsf EECON1, RD
bcf STATUS, RP0 ; bank 0
movf EEDATA, W ; read data_2 from eeprom
movwf data_2
movwf temp_2
incf temp_2, F
incf EEADR, F
bsf STATUS, RP0 ; bank 1
bsf EECON1, RD
bcf STATUS, RP0 ; bank 0
movf EEDATA, W ; read data_3 from eeprom
movwf data_3
movwf temp_3
incf temp_3, F
incf EEADR, F
bsf STATUS, RP0 ; bank 1
bsf EECON1, RD
bcf STATUS, RP0 ; bank 0
movf EEDATA, W ; read data_4 from eeprom
movwf data_4
movwf temp_4
incf temp_4, F

loop_1 ; endless loop
bsf INTCON, GIE
btfs PORTB, 1
goto loop_1
call dly_1
btfs PORTB, 1
goto loop_1
prog ; programming routine
bcf INTCON, GIE
clrf bit_num
bsf PORTB, 4 ; flash once
call dly_1
bcf PORTB, 4
call dly_1
clrf data_1
clrf data_2
clrf data_3
clrf data_4
loop_2
btfs PORTB, 1
goto finish_prg
btfs PORTB, 3
goto loop_2
call dly_1
btfs PORTB, 3
goto loop_2
shift
movlw 0x08
subwf bit_num, W
btfs STATUS, C
goto shift_1
movlw 0x10
subwf bit_num, W
btfs STATUS, C
goto shift_2
movlw 0x18
subwf bit_num, W
btfs STATUS, C
goto shift_3
movlw 0x18
subwf bit_num, W
btfs STATUS, C
goto shift_4
shift_1 ; load into data_1
bcf STATUS, C
btfs PORTB, 2
bcf STATUS, C
btfs PORTB, 2
rjf data_1, F
goto finish_sft
shift_2 ; load into data_2
bcf STATUS, C
btfs PORTB, 2
bcf STATUS, C
rjf data_2, F
goto finish_sft
shift_3 ; load into data_3
bcf STATUS, C
btfs PORTB, 2
bcf STATUS, C
rjf data_3, F
goto finish_sft
shift_4 ; load into data_4
bcf STATUS, C
btfs PORTB, 2
btfs PORTB, 2

finish_prg
movf data_1, W
movwf temp_1
incf temp_1, F
movwf EEADR
clrf write_eprom
call write_eprom
movf data_2, W
movwf temp_2
incf temp_2, F
movwf EEADR
call write_eprom
movf data_3, W
movwf temp_3
incf temp_3, F
movwf EEADR
call write_eprom
incf temp_3, F
movwf EEADR
incf EEADR, F
call write_eprom
movf data_4, W
movwf temp_4
incf temp_4, F
movwf EEADR
incf EEADR, F
call write_eprom
movlw 0x03
movwf temp_5
flashes ; flash 3 times
bsf PORTB, 4
call dly_1
bcf PORTB, 4
call dly_1
decfsz temp_5, F
goto flashes
dly_1 ; delay 0.2 seconds
clrf cnt_1
clrf cnt_2
lp_1 decfsz cnt_1, F
goto lp_1
decfsz cnt_2, F
goto lp_1
return
write_eprom
bsf STATUS, RP0 ; bank 1
bsf EECON1, WREN ; enable to write eeprom
movlw 0x55
movwf EECON2
movlw 0xaa
movwf EECON2
bsf EECON1, WR ; start write
write_dly
btfs EECON1, WR
goto write_dly
bcf STATUS, RP0 ; bank 0
return
end
    
```

microseconds can be calculated using,


$$3 * \text{data}_1 + 770 * \text{data}_2 + 197,122 * \text{data}_3 + 50,463,234 * \text{data}_4 + 9$$

The minimum pulse width of 9µs happens when all four registers are set to zero. The maximum pulse width occurs when four registers are all set logic high, which is about 3 hours 35 minutes and 19 seconds.

Three pins of the microcontroller are used to program the pulse width. PB1 selects either programming or normal one-shot function. Port PB2 is the data input and PB3 is the programming clock input.

Once PB1 is connected to the ground, a LED flashes once to indicate that all registers are cleaned up and programming starts. The 32-bit counter number is programmed into the microcontroller in a serial format with the lowest bit first.

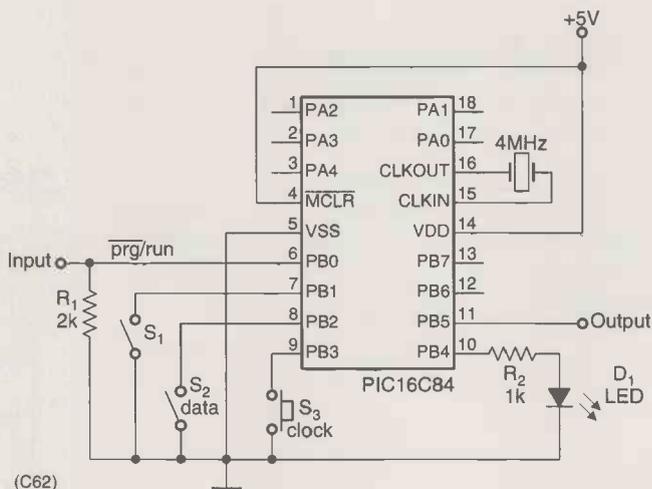For instance, assume the number is 00000000 00000000 10000000 00000000. First of all, connect PB2 to the ground. Then push the button on PB3 15 times.



Note that each time the button is pushed, the LED flashes once to show that one bit of the data is accepted.

The next step is to release PB2 from ground. Since the microcontroller has built-in pull-up resistors, PB2 will become logic high.

Push the button one more time and the 16th bit – logic high – will be sent. It is not necessary to program

the rest of the bits since they are all zeros.

The last step is to release PB1 from ground. The LED will then flash three times to indicate the programming is finished and data have been stored into the EEPROM.

Yongping Xia
Torrance, CA
USA
C62

Accurate stopwatch measures to within 0.01s

To crystal accuracy, this circuit measures time to a resolution of 0.01s or 0.1s on 100s or 1000s ranges.


A 1MHz crystal oscillator drives a chain of two 74390 dual decade

counters and a single 7490 decade, a switch selecting the latter to give a total division of 10⁴ or 10⁵, i.e. 100Hz or 10Hz.

The selected output of the divider chain is counted in the 4-digit

counter, which provides a multiplexed seven-segment display driver for low power consumption.

Raj K Gorkhali
Katmandu
Nepal, C51

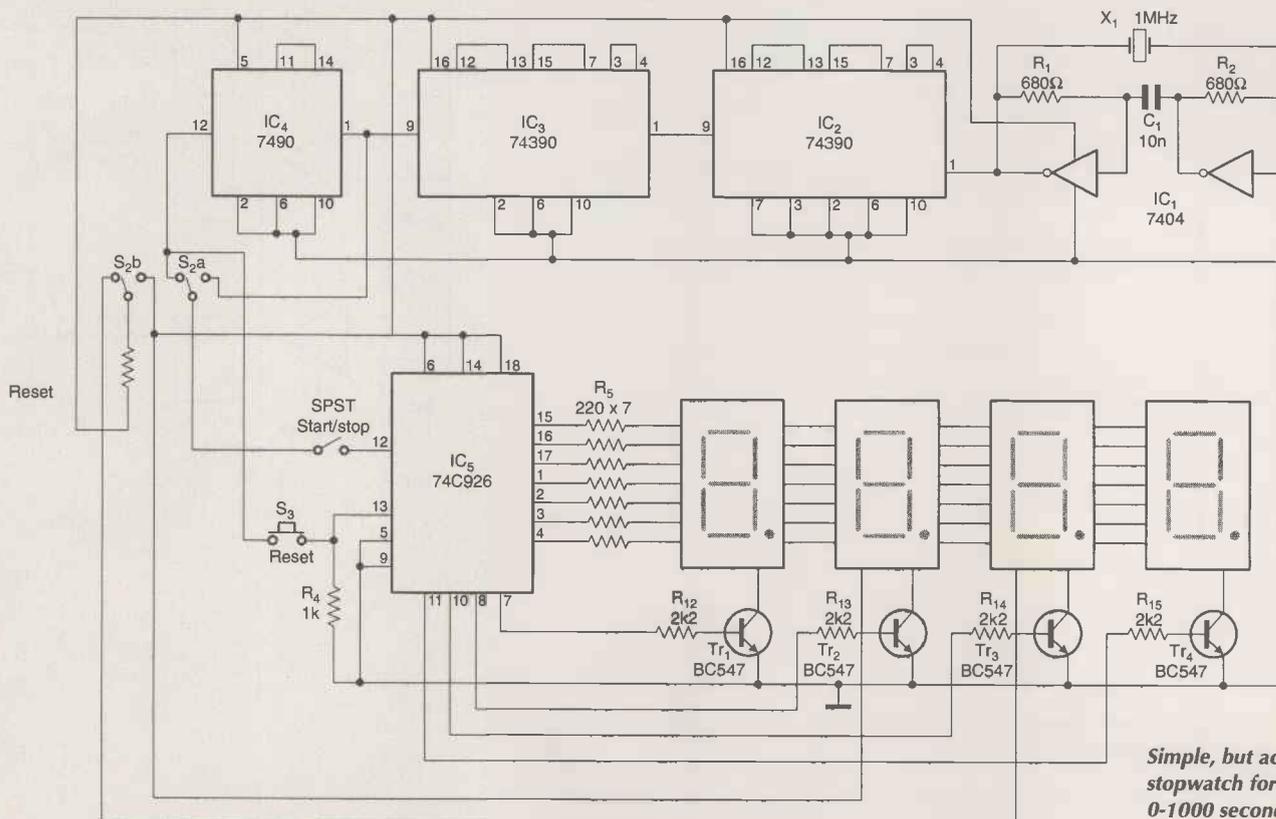



Photographic flash meter

Providing an eight-step indication, this flash meter is of the analogue variety, although it could be said to be an a-to-d converter, using latches as led drivers.

The MEL12 phototransistor, in conjunction with the CA3140E mosfet op-amp gives good linearity, the op-amp output and total ladder resistance being made adjustable to take into account the range of indication for high or low light conditions.

Calibration was carried out using a photographic grey card, a halogen lamp and by comparison with a professional light meter.

D A Williams
Sheldon
Birmingham
C68

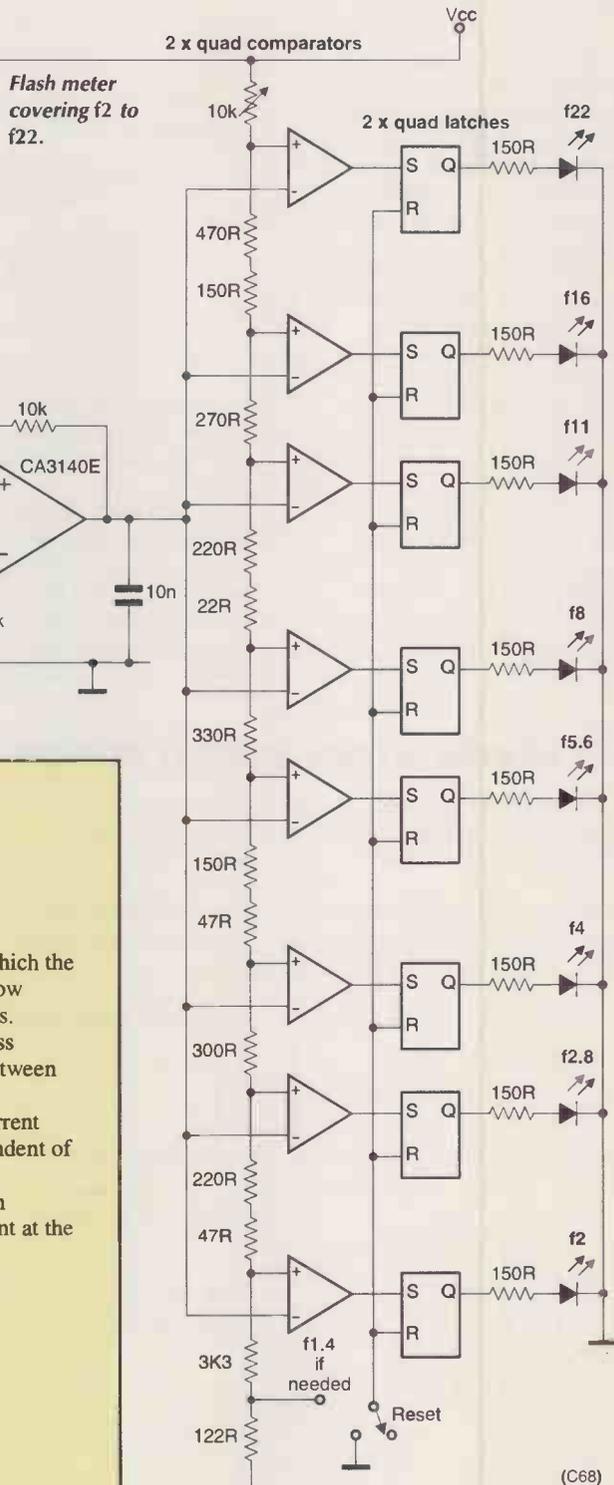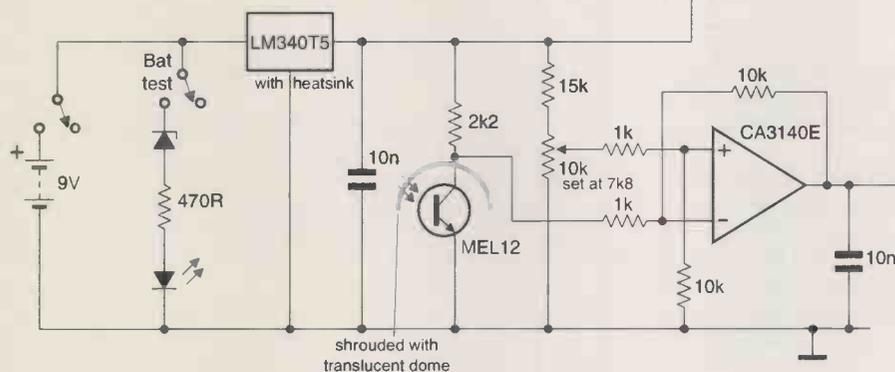

Better zener voltage regulator drops out at 0.25V


Figure 1 shows the usual type of zener regulator, in which the zener diode becomes starved of working current on low supply inputs and can become overheated on high inputs.

In the circuit of Fig. 2, the diode current is more or less proportional to the supply voltage, not the difference between the supply and zener voltages. Base current to the p-n-p transistor is amplified by the transistor, the collector current supplying the zener. Collector current is largely independent of the collector voltage.


Resistor R_1 should be selected, in view of current-gain variations between devices, to give a 10mA zener current at the lowest input voltage.

On a 13.6V car battery supply, the output of 12V was stabilised in the prototype for inputs down to 12.3V.

P Goodson
Bracknell
Berkshire
C63

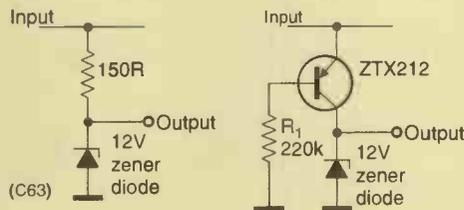

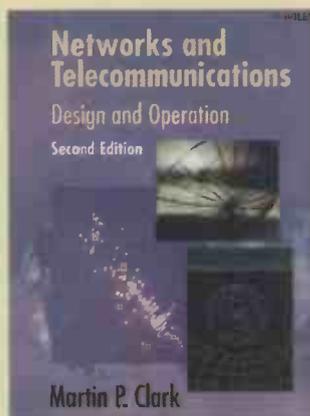Three-component voltage regulator has a drop-out voltage of only 0.25V.



Networks and Telecommunications Design and Operation

Second Edition
Martin P. Clark,
Telecommunications
Consultant, Frankfurt,
Germany

Telecommunications network design and operation is now widely regarded as an issue of business management as well as electrical engineering. In this updated edition, Martin Clark, a pioneer of this perspective, applies it to the increasing complex and diverse realm of voice, and data and multimedia networks.

Written in an accessible style and clearly illustrated throughout, this is a basic, practical and intuitive insight into modern network engineering and sections including:

- Technical accounts of modern voice, data and multimedia networks
- Coverage of ATM, B-ISDN, SDH, mobile radio and satellite networks, Internet and TCP/IP
- Practical aspects of running and setting-up networks
- Running a business based on telecommunications

A text specifically for readers new to the whole subject of telecommunications, and professional telecommunications managers who need an introduction and reference work on all aspects of technology, operational techniques and regulation.

ISBN 0 471 973 46 7

UK £80.50 Europe £86 ROW £105

Introduction to Digital Mobile Communication

Yoshihiko Akaiwa

A comprehensive treatment of the digital technologies that make personal mobile communication a reality

Although today's mobile communication engineers and designers can build upon the advances in digital telecommunications, specific technical requirements - robustness against fast fading,



spectrum and power efficiency, and the demand for low-priced equipment- post new technological challenges that demand creative solutions.

Introduction to Digital Mobile Communications is a comprehensive treatment of the digital technologies that are rapidly spawning new advances and applications. Written by a pioneer in the field, this book covers all the important concepts, from the fundamentals of signal analyses and digital communication to descriptions of the latest transmission systems. Rich in detail and broad in its coverage, this remarkable book:

- Describes equipment and circuit implementation methods and their performance characteristics
- Discusses elements of and methods for digital modulation and demodulation schemes
- Provides practical designs and circuits for spectrum-efficient modulations
- Covers mobile radio channels and digital mobile radio systems
- Includes extensive

- mathematical treatments and mathematical models
- Presents the latest research results with detailed references

This valuable resource provides a solid introduction to mobile radio communication for the students or professional in related fields. Most important, for design engineers and equipment manufacturers, its up-to-date findings will stimulate new research and creative design and system development efforts.


Yoshihiko Akaiwa is a leading researcher in the digital mobile communication field. Currently a professor at Kyushu University, he worked as a researcher for over twenty years at the NEC Corporation
ISBN 0 471 17545 5
UK £57.50 Europe £60.50 ROW £73

Cellular Mobile Radio Systems

Designing Systems for Capacity Optimization
Husni Hammuda, Ericsson
(UK) Ltd

Rapidly increasing demand for mobile radio frequency subscription is already pushing cellular networks to the point of overload. Of the various methods which are being explored to tackle this problem one of the most notable is the integration of advance modulation and multiple access techniques. In this book, Husni Hammuda, a pioneer of this hybrid, shows how it can be applied in practice to optimise the efficiency of mobile radio cells.

- Provides detailed criteria for

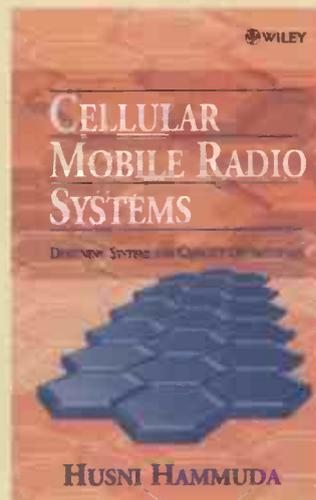

- the evaluation of combinations of modulation and multiple access techniques
- Includes primary performance data as well as predictive models
- Theoretical material is explained using examples from first and second generation transmission systems
- Covers recent innovations in personal communications

For the practising cellular communications engineer this is a systematic set of solutions for improving traffic flow in cellular networks. It also includes complete theoretical and case material ideal for post-graduate network engineering researchers.

ISBN 0 471 95641 4

UK £37.50 Europe £39.95 ROW £46.95

Network-Based Images

A Practical Guide to Acquisition, Storage, Conversion, Compression and Transmission
Gilbert Held, 4-Degree
Consulting, Macon, Georgia,
USA

Network-Based Images offers a fresh approach to the acquisition and manipulation of visual images on computer by focusing on the network application side.

This practical Guide explains the methods used to store images electronically and discusses the popular image-based applications, such as storage, conversion and compression. Gilbert Held reviews the procedures used to minimize the effects of other image-based applications to increase efficiency.

This network oriented book provides detailed information on the transmission of images to other systems and includes an overview of the associated problems.

Features include:

- Use of images on LANs includes LAN-based World Wide Web Servers
- Use of HTML image related statements
- Techniques to avoid costly network upgrades
- How to segment LANs
- Network modifications to

counter the bandwidth effect of images upon LAN transmission


Essential reading for network managers and administrators as well as Web server administrators and personal computer users. This book will provide unique coverage of images oriented to efficient use on networks: storage, acquisition, and use in applications

ISBN 0 471 97357 2
UK £37.50 Europe £39.95 ROW £46.95

Stereophonic Sound Recording

Theory and Practice
Christian Hugonnet and Pierre Walder

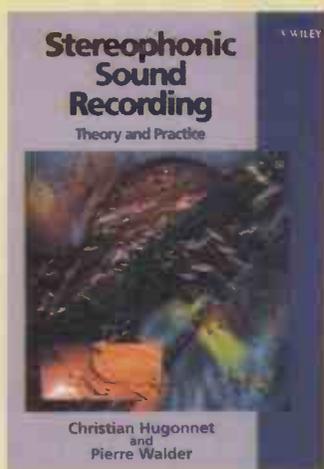Recent advances in digital audio have heralded substantial innovations in sound recording techniques and increased the importance of applying the latest microphone techniques. The authors of this book focus on these innovations, giving numerous examples of their use within the framework of an analysis-based recording



engineering theory. The book provides a complete overview of well-known sound recording procedures practised worldwide, whilst also presenting a methodology that will provide the reader with an efficient approach to sound recording of classical music, rock and pop music, drama and speech. The widely illustrated theoretical knowledge is presented in clear and simple language.

Building on their considerable experience of creating innovative recording techniques, the authors

provide an authoritative analysis of the subject that offers valuable, practical guidance that will aid the development of new recording methods. Their inside knowledge of the requirements of the phonographic, broadcasting, film and other media industries ensures expert coverage of new products and approaches including:

- recording techniques for all types of microphones
- in-depth analysis of the principles and use of stereophonics
- influence and role of the venue acoustics on the sound recording
- guidelines for mastering and mixing different levels of sound from different sources

For professional audio engineers, this manual provides systematic advice for getting optimal performance from studio equipment. For students of audio engineering it will form a comprehensive introduction to the area of stereophonic recording, backed up by real-world case studies and a wealth of practical experience.
ISBN 0 471 97487 0
UK £32.45 Europe £34.95 ROW £41.95


Protect Your Privacy on the Internet

Privacy defense tools and techniques you can use right now
Bryan Pfaffenberger

CD-ROM includes a complete collection of Windows privacy software.

Is your complete life story available to anyone with Internet access? It's really not all that hard to snoop in

Continued over page

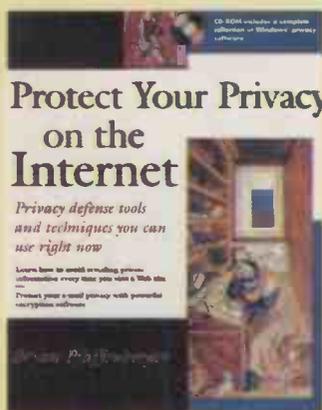

All prices are fully inclusive of packaging and delivery

Return to Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following titles:

Qty	Title or ISBN	Price

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (please circle)

Access/Mastercard/Visa/Cheque/PO

Cheques should be made payable to
Reed Business Information

Credit card no _____

Card expiry _____

Signed _____

Please allow up to 28 days for delivery

cyberspace. As more and more business is conducted over the Internet, it has become increasingly difficult for both businesses and individual users to protect private information. Your reputation, Your finances, and your basic right to privacy are on the line every day. What can you do about it?

You can fight back. Protect Your Privacy on the Internet tells you everything you need to know to ensure your privacy and use the same technology that's being used against you to protect yourself. You'll get industrial-strength encryption tools to keep your affairs secret, the way they ought to be.

Bryan Pfaffenberger arms you with privacy defense strategies such as:

- Creating a bullet-proof password
- Getting your name out of the databases
- Cleaning up your browser's trails

Protect Your Privacy on the Internet gives you proven privacy defense strategies and techniques to help you make the Net a safer place to work and play. You'll get the names of Internet privacy organizations that are working to protect your privacy rights and find out what you can do to help. On the accompanying CD-ROM you'll find a collection of Windows Privacy freeware and shareware, including:

Pronto96 - an e-mail program that works in conjunction with encryption software to protect your e-mail

Mutilate - software that thoroughly erases files beyond recovery, even by expert snoopers

Win-Secure-It® - a utility preventing unauthorised access to files on your computer

AMSD Ariadna™ - a full-featured browser that reads tables and Java but ignores "cookies", text files that transparently save where you've been


Random Password Generator - a program enabling you to generate up to 1,000,000 passwords to protect you against unauthorized access to your Internet account
Cyber Patrol™ - parental

control software that prevents kids from uploading personal and demographic information to commercial sites

ISBN 0 471 18143 9

UK £27.45 Europe £29.95 ROW £36.95

Internet Audio Sourcebook

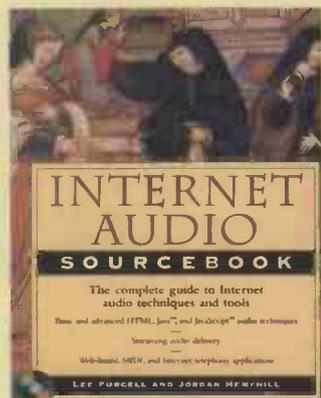

The complete guide to Internet audio techniques and tools
Lee Purcell and Jordan Hemphill

"The World Wide Web has spouted vocal cords, gained a voice, and begun to sing." – Lee Purcell and Jordan Hemphill

Internet Audio Sourcebook offers you a quick, easy way to acquire the knowledge, skills, and some of the tools you need to build cutting-edge audio capabilities into your Web pages, including:

- Music, narration, and sound effects
- Streaming audio for real-time broadcasts
- Automated, spoken-voice instruction
- Audio conferencing and Internet telephony
- MIDI techniques for musical training and analysis

Taking a step-by-step approach, the authors get you up to speed on the latest audio tools and techniques. First they school you in the basics of creating, processing, and storing audio data.

You learn the various methods of working with digital sound and how to use available tools to shape audio content for the Internet. Then they show you how to deliver your digital sound over the Web. They explain the HTML coding used to access audio files and teach you techniques for integrating Java applets,

JavaScript code, and VBScript code into your HTML documents.

Finally, the authors show you how to get the most out of new audio technologies, including streaming audio, MIDI applications, voice synthesis and recognition, and Internet telephony, as well as covering hot new products like the Headspace Beatnik audio engine and Liquid Audio.

The CD-ROM

You get fully functional demos of top-of-the-line sound processing applications, including Sonic Foundry's Sound Forge and Hohner Midia's Samplitude Studio. Authoring tools such as Symantec's Visual Café, Aimtech's Jamba, and Acadia Software's Infuse JavaScript editor are also included.

ISBN 0 471 19150 7

UK £28.45 Europe £31.95 ROW £39.95

Web Security Sourcebook

A Complete Guide to Web Security Threats and Solutions
Aviel D. Rubin, Daniel Geer, and Marcus J. Ranum

The front door is unlocked and wide open. The alarm's not working and no one's home. All of your valuable, money, and intimate details of your life are just sitting inside, waiting to be taken. No, it's not your house, it's your computer.

The Web now penetrates every aspect of our lives, from the home PC to the Business office. But with each advance in convenience comes a geometric increase in vulnerability to the integrity of data and software as well as to the confidentiality of information. Although the flaws inherent in the Web are real, solutions are available. Let Aviel Rubin, Daniel Geer, and Marcus Ranum give you the answers.

Here's a book that's valuable today and indispensable for the future. It includes basic and advanced techniques for client-side and server-side security, browser security, writing secure CGI scripts, firewalls, and secure e-commerce. There's a special appendix that demystifies the complex world of cryptography. And the book comes with access to a dedicated Web site containing

up-to-the minute information on the latest security threats and solutions.

So whether you're a Webmaster trying to close the door on sites and applications, or an everyday user hoping to keep your desktop safe, this is your essential source of:

- Protecting and securing Web pages, search engines, servers, and browsers
 - Writing impregnable applets and scripts, and avoiding the dangers inherent in every language
 - Using (and abusing) firewalls and cryptographic controls
 - Securing commerce and payment transactions
- ISBN 0 471 18148 X
UK £27.45 Europe £29.95 ROW £36.95

Encyclopaedia of Acoustics

Edited by Dr Malcolm J Crocker, Auburn University

Sound Information in 167 detailed Chapters. Now there's a new four-volume reference that covers every imaginable area of acoustics, sound and vibration - from the design of a concert hall to the intricacies of the human ear. It's the Encyclopaedia of Acoustics.

In this on-of-a-kind set, edited by well-known acoustical expert Dr Malcolm J. Crocker, you'll get:

- Extensive cross-referencing and indexing
- 2000- plus pages of insights from more than 200 international expert contributors
- An exhaustive examination of the fundamentals of acoustics and vibration in the first two volumes
- A revealing exploration of acoustic applications in Volumes Three and Four
- General Introductions at the start of every section

This up-to-date work is the definitive acoustics resource for students, engineers, scientists, and researchers in the field.

Casebound © 1997, four-volume set
approx. 2,000pp.
(750pps./volume)
ISBN 0471 80465 7

UK £372.45 Europe £384.97 ROW £390

Bryan Hart explains the Early effect - an important phenomenon not always well understood by analogue circuit designers.

Early definition

What is a reasonable estimate for the maximum theoretical small-signal, low-frequency voltage gain that can be obtained with a single low-power silicon bipolar junction transistor (bjt) operating at room temperature in the common-emitter configuration?

To be able to answer that question with confidence you will need to know about a parameter that, in my opinion, has not been covered sufficiently well in the general literature of circuit engineering. This parameter, which usually appears as if by magic, is the 'Early voltage'.¹

This pair of articles sets out to remedy this situation. The first article introduces a coherent explanation of the origin of this parameter and its role in device characterisation and modelling.

The second article, to be published later, considers its importance in the design of a range of widely used analogue circuits. These include the common-emitter and common-base configurations, the current mirror and the long-tailed pair.

Early origins

Figure 1a) shows a low power n-p-n silicon bjt biased for analogue operation and Fig. 1b) shows a schematic cross-section of it. For clarity, this greatly exaggerates the width of

the base compared with the widths of the emitter and collector regions.

Layers depleted of mobile charge carriers exist near the metallurgical junctions, i.e., where the doping polarity changes from p to n and *vice-versa*. In the absence of externally applied junction voltages these layers establish themselves to ensure that the net current flowing across each junction is zero.

The application of external bias voltages V_{BE} and V_{CB} changes the widths of these layers and the densities of minority carriers at their boundaries. The way that the resulting terminal currents are related to these changes can be deduced from an extension of the work of Moll and Ross.² They were the first to consider the transport of minority carriers across the base of a bipolar transistor with arbitrary base doping.

Assuming zero recombination of minority carriers crossing the base and operation with V_{BE} greater than 100mV, it can be shown that,

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \quad (1a)$$

where,

$$I_S = \frac{K_B}{Q_B} \quad (1b)$$


In these equations, K_B is the product of the diffusion constant in the base and the squares of the electronic charge, the emitter area and the intrinsic carrier concentration. It is independent of current but dependent on temperature.

The parameter Q_B is the magnitude of the charge associated with the net number of acceptor impurities contained within the effective base width, W , and is thus a function of the doping process.

Parameter V_T is the thermal voltage, i.e. kT/q , k being Boltzmann's constant, q the magnitude of the charge on an electron, T the absolute temperature in kelvin ($^{\circ}\text{C}+273$); at room temperature, V_T is around 25mV and this is the value assumed throughout this article.

Equation (1) is valid provided the total minority carrier charge in transit across the base is much less than Q_B - the 'low-level injection' condition. The neglect of base region recombination is normally valid for a modern low power bjt. This is because the base width and doping levels are such that the transit time of minority carriers across the base is negligible compared with the time taken

Fig. 1a) An n-p-n bipolar transistor biased for analogue operation and b), idealised cross-section of the device - base width grossly exaggerated.

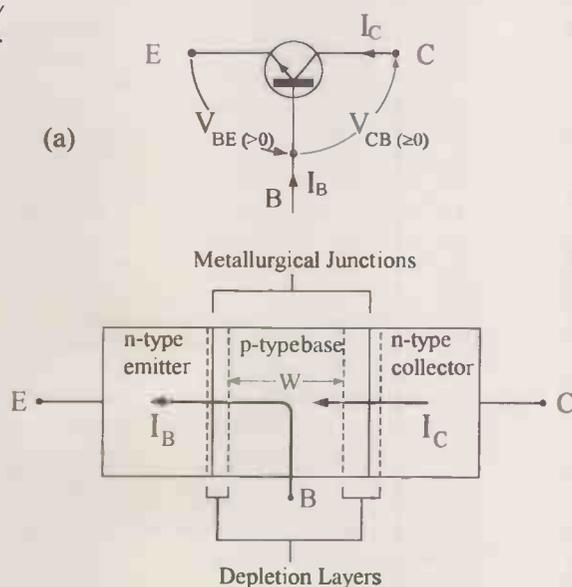

for a carrier to recombine in it.

The same is not necessarily true for high power transistors having relatively wide bases and it certainly was not true for alloy junction transistors.

If base region recombination is neglected how does a finite base current arise? The answer is, solely from holes injected from the base into the emitter. The equation for I_B is similar to that for I_C , the differences being that K_B and Q_B are replaced by their emitter counterparts K_E , Q_E .

Thus,

$$I_B = \frac{K_E}{Q_E} \exp\left(\frac{V_{BE}}{V_T}\right) \quad (2)$$

The common-emitter direct current gain is β and from eqns (1) and (2),

$$\beta = \frac{I_C}{I_B} = \frac{K_B Q_E}{K_E Q_B} \quad (3)$$

How we proceed from this point depends on the assumptions made for Q_B . A first-order model of the bipolar transistor assumes Q_B to be constant, independent of V_{CB} , for a fixed V_{BE} . A second-order model, considered from now on, takes into account the dependence of Q_B on V_{CB} .

The physical mechanism is this. The collector and base doping profiles fix the electrostatic field in the collector depletion layer. An increase in V_{CB} - dimensionally, the product field multiplied by distance - can only be accommodated by an increase in junction layer width. This is at the expense of base width ('base-width modulation') and a reduction in Q_B .

Referring to eqn (1), this leads to an increase in I_C . Since I_B does not change - K_E , Q_E are not dependent on V_{CB} - this means β increases with V_{CB} .

The effect is quantified by taking logarithms of each side of eqn (1) and then differentiating with respect to V_{CB} .

$$\frac{1}{I_C} \times \frac{dI_C}{dV_{CB}} = -\frac{1}{Q_B} \times \frac{dQ_B}{dV_{CB}} \quad (4)$$

When V_{CB} increases by an increment δV_{CB} , Q_B decreases by the same amount that the depletion layer charge Q_D increases: thus,

$$\delta Q_B = -\delta Q_D \quad (5a)$$

But, the collector depletion layer capacitance C_{JC} is defined by,

$$C_{JC} = \frac{dQ_D}{dV_{CB}} \quad (5b)$$

Hence, from eqns (4), (5),

$$\frac{1}{I_C} \times \frac{dI_C}{dV_{CB}} = \frac{C_{JC}}{Q_B} \quad (6)$$

Considering conditions at $V_{CB}=0$, for which $Q_B=Q_{B0}$, $I_S=I_{S0}$, $I_C=I_C(0)$, $\beta=\beta_0$, $C_{JC}=C_{JC0}$, we attach a meaning to the right hand side of eqn (6) by making the following definition,

$$V_A = \frac{Q_{B0}}{C_{JC0}} \quad (7)$$

Furthermore, dV_{CB}/dI_C is identified as the incremental resistance r_o .

Now, eqn (6) can be re-written,

$$I_C(0)r_o = V_A \quad (8)$$

I will now show this result graphically.

Characteristics and models

Figure 2 is a sketch of the observed characteristics of a bjt. The bold lines, for V_{CB} zero or greater than 0, correspond to the region under discussion; the feint lines, for V_{CB} less

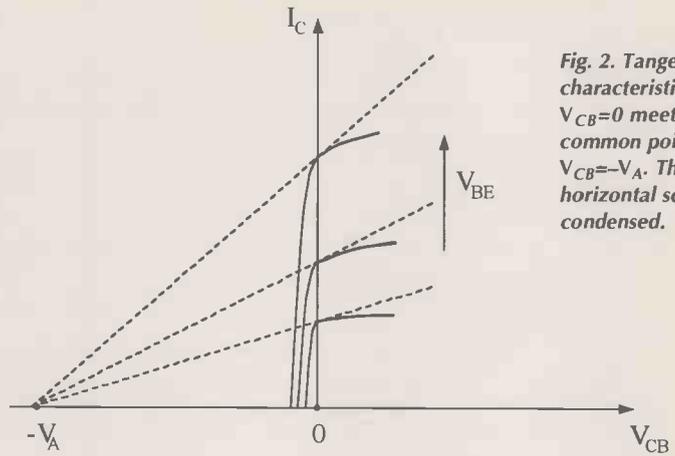


Fig. 2. Tangents to the characteristics at $V_{CB}=0$ meet at a common point, $V_{CB}=-V_A$. The horizontal scale is condensed.

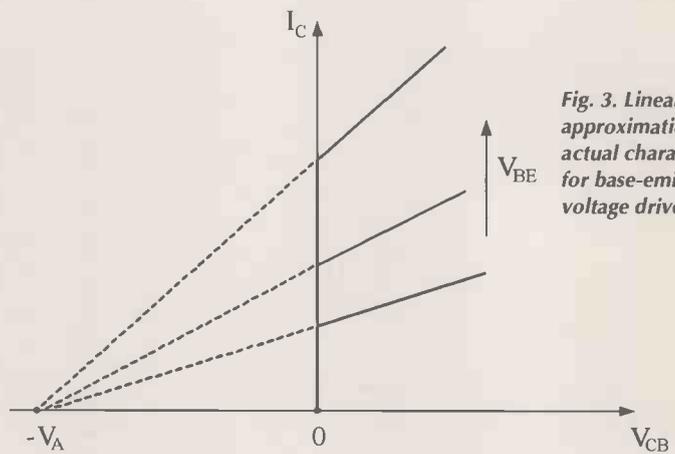


Fig. 3. Linearised approximation to actual characteristics for base-emitter voltage drive.

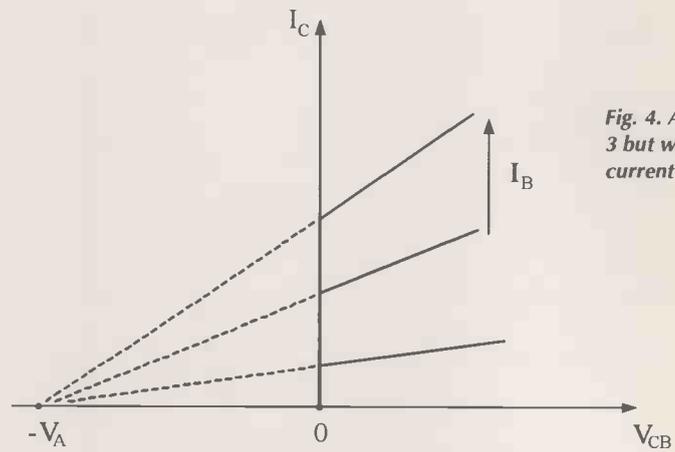


Fig. 4. As for Fig. 3 but with base current drive.

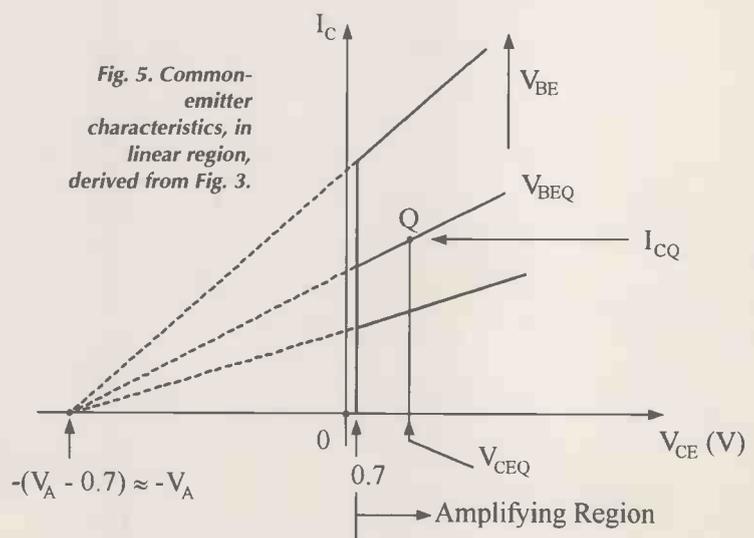


Fig. 5. Common-emitter characteristics, in linear region, derived from Fig. 3.

than zero describe the saturation region.

The saturation characteristics do not follow from eqn (1). Different equations apply. They are only indicated for completeness: they are ignored from now on.

Equation (8) states that the tangents to the output characteristics at $V_{CB}=0$, when extrapolated back, have a common point of intersection on the horizontal axis at $V_{CB}=-V_A$.

In honour of J. M. Early, who carried out pioneer work on bjt output conductance³ that led to the description 'Early Effect' for base-width modulation, V_A is known as the 'Early' voltage.

The choice of the relatively uncommitted subscript letter *A* rather than *E* saves possible confusion with an emitter voltage. Typically, V_A is around 100V for an n-p-n bipolar transistor. This a useful default figure when none

is deducible from manufacturers' data. For an n-p-n device V_A is around 50V.

What happens when V_{CB} is greater than zero? As a result of current device design and fabrication technology the ratio Q_B/C_{JC} , in eqn (6), is not a strong function of V_{CB} over a practically useful range of V_{CB} ($\ll V_A$). So, for simplicity in characterisation and modelling, it is assumed that Q_B/C_{JC} remains constant at the value, V_A , that it has for $V_{CB}=0$.

Now, equation (6) becomes,

$$\frac{1}{I_C} \times \frac{dI_C}{dV_{CB}} = \frac{1}{V_A} \tag{9}$$

Integrating with respect to V_{CB} ,

$$I_C = I_C(0) \exp \frac{V_{BE}}{V_A} \tag{10}$$

or,

$$I_C = I_{S0} \exp \frac{V_{BE}}{V_T} \times \exp \frac{V_{CB}}{V_A} \tag{11}$$

Equation (10) is only valid while V_{CB} is much less than V_A so using the following approximation is justifiable,

$$\exp \frac{V_{CB}}{V_A} \approx 1 + \frac{V_{CB}}{V_A} \tag{12}$$

Then,

$$I_C = I_{S0} \left(1 + \frac{V_{CB}}{V_A} \right) \exp \frac{V_{BE}}{V_T} \tag{13}$$

This equation describes a family of straight lines, each of which passes through $V_{CB}=0$ with a slope $I_C(0)/V_A$. These linearised approximations to the actual characteristics for $V_{CB}>0$, Fig. 3, are the tangents to the characteristics at $V_{CB}=0$ that were mentioned earlier.

For a given V_{CB} , equal increments in V_{BE} do not produce corresponding equal increments in I_C because of the exponential relationship between I_C and V_{BE} .

With V_{BE} constant – and, hence constant base current – collector current increases by a factor $[1+(V_{CB}/V_A)]$ as V_{CB} increases from zero, so β must increase by the same factor.

Thus,

$$I_C = \beta I_B = \beta_0 I_B \left(1 + \frac{V_{CB}}{V_A} \right) \tag{14}$$

For a given V_{CB} , the relevant output characteristics with I_B the controlling parameter, are now equally spaced, Fig. 4. Rather than I_C as a function of V_{CB} , we are often more interested in I_C as a function of V_{CE} . To determine this we substitute $V_{CB}=(V_{CE}-V_{BE})$ in eqn (13).

$$I_C = I_{S0} \left(1 + \frac{V_{CE}-V_{BE}}{V_A} \right) \exp \frac{V_{BE}}{V_T} \tag{15}$$

A popular assumption in biasing a bjt for linear operation is $V_{BE}=\text{constant}=0.7\text{V}$, so a safe lower bound to the linear region is also $V_{CE}=0.7\text{V}$.

In that case the output characteristics are shown in Fig. 5. They are those of Fig. 4 shifted horizontally to the right by 0.7 V. Figure 6 is derived, similarly, from Fig. 4.

The I_{BQ} of Fig. 6 is chosen to correspond to V_{BEQ} in Fig. 5. Incremental resistance at operating point Q is given by,

$$r_o = \frac{V_{CEQ} + V_A - 0.7}{I_{CQ}} \tag{16}$$

or,

$$r_o \approx \frac{V_A}{I_{CQ}} \tag{17}$$

Figure 7a) is a general view of two of the transfer characteristics and Fig. 7b) is an expanded view of them in the

Fig. 6. Common-emitter characteristics derived from Fig. 4.


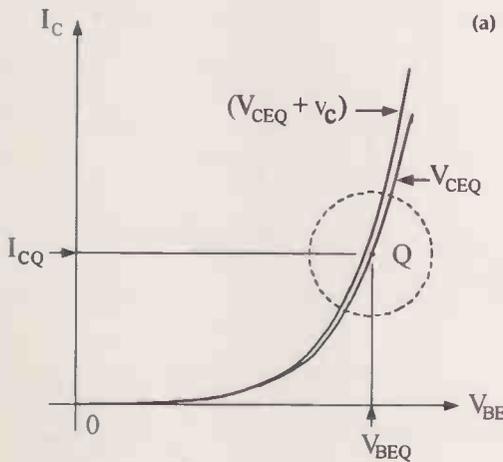
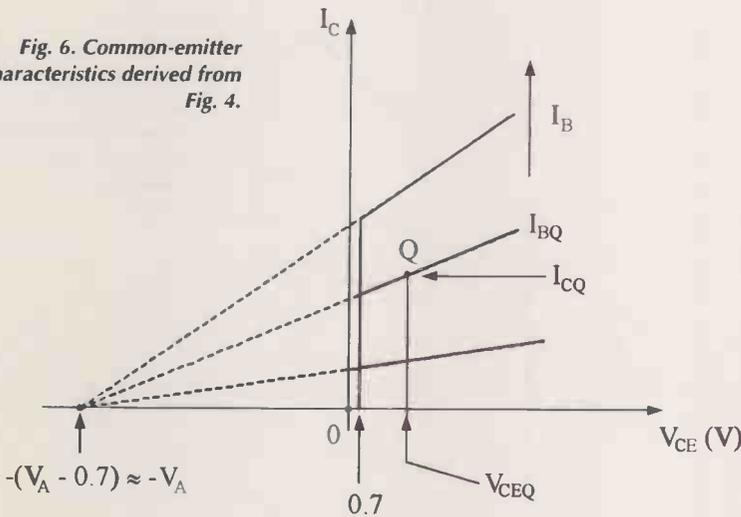


Fig. 7a). Two of the family of mutual characteristics: $V_{CEQ} \gg v_c$. Fig. 7b) is its detail in vicinity of Q point, showing parameter relationships.

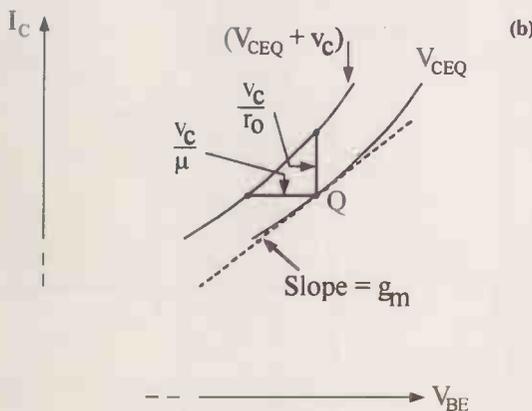

vicinity of Q. For small changes $-\delta V_{CEQ} = v_c$ etc. – the curves can be considered straight and parallel.

The parameter $r_o = (v_c/i_c)$ characterises the vertical spacing. The horizontal spacing is calculated by combining the exponential terms in equation (11).

If I_C is constant,

$$\frac{V_{BE}}{V_T} + \frac{V_{CB}}{V_A} = \text{constant} \tag{18}$$

$$\therefore \frac{v_b}{V_T} + \frac{v_c - v_b}{V_A} = 0 \tag{19}$$

It is now convenient to make the definition,

$$\mu = \frac{V_A}{V_T} \tag{20}$$

Then,

$$v_b \approx \frac{-v_c}{\mu} \tag{21}$$

The approximation $\mu \gg 1$, made in obtaining eqn (21) from eqn (19), is also used in determining the slope of the characteristics.

Differentiating eqn (15) with respect to V_{BE} , with V_{CE} constant, gives the mutual conductance g_m .

$$g_m = \frac{I_{CQ}}{V_T} \tag{22}$$

From eqns (17) and (22),

$$\mu = r_o g_m \tag{23}$$

Older readers might remember this relationship first appearing with valves and μ being dubbed the ‘amplification factor’.

The input characteristic is shown in Fig. 8. It is a single curve for $V_{CB} \geq 0$.

The incremental input resistance termed r_π is given by,

$$r_\pi = \frac{dV_{BE}}{dI_C} \times \frac{dI_C}{dI_B} \tag{24}$$

or,

$$r_\pi = \frac{\beta}{g_m} = \frac{\beta V_T}{I_{CR}} \tag{25}$$

Three choices for the small-signal low-frequency equivalent circuit of the bipolar transistor are shown in Fig. 9. These are constructed from the parameters, already defined, by standard model building procedures as, for example, in ref. 4. Thus, the output circuit of Fig. 9a) is developed from Fig. 5 by considering small changes about the point Q and the output circuit of Fig. 9b) is similarly related to Fig. 6.

Fig. 9c) is derived from Fig. 9b) by the use of Thévenin’s theorem. The input circuit of each model derives from Fig. 8. Resistance r_x has not been mentioned previously because we have considered only the idealised structure of Fig. 1.

A more practical structure is shown in Fig. 10. Here, r_x is typically 50Ω and represents the equivalent lumped resistance of the semiconductor material between the base terminal and the active base region. This region is that part in the vertical shadow of the emitter, i.e. inside the cylindrical region bounded by the vertical dotted lines.

As the junction areas are unequal, the Early voltage is V_A , as defined by equation (7), multiplied by the factor collector-junction area/emitter-junction area.

In my next article, I will show how to apply the characteristics and models to the solution of some circuit design problems, starting of with that mentioned at the beginning of this article. ■

References

1. Gummel, H K, and Poon, H C, ‘An integral charge model for the bipolar transistor’ *Bell Syst. Tech. J.*, 49, 827-852 (1970).
2. Moll, J L, and Ross, I M, ‘The Dependence of Transistor Parameters on the Distribution of Base Layer Resistivity’. *Proc. IRE*, 44, 72, (1956).
3. Early, J M, ‘The Effects of Space-Charge Layer Widening in Junction Transistors’, *Proc. IRE*, 40, 1401-1406 (1952).
4. Hart, B L, ‘Introduction to Analogue Electronics’, Chapter 4, Arnold (1997).
5. Hart, B L and Barker, R W J, ‘DC matching errors in the Wilson current source,’ *Electronics Letters* Vol. 12, No 15, pp. 389-390, July 1976.

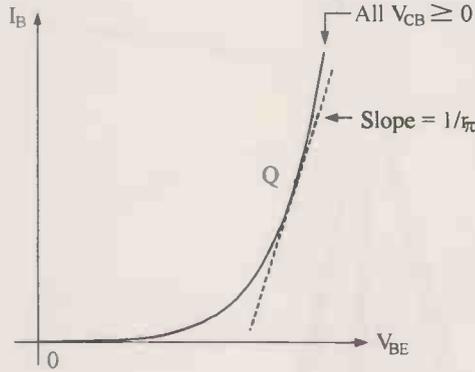


Fig. 8. Input characteristic curve, when V_{CB} is zero or greater.

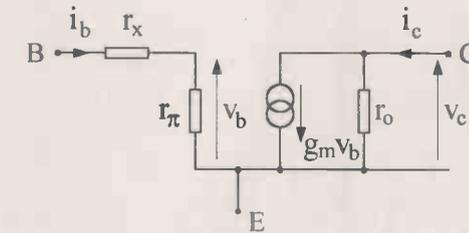


Fig. 9. Showing three choices for a small-signal low-frequency equivalent circuit of the bjt.


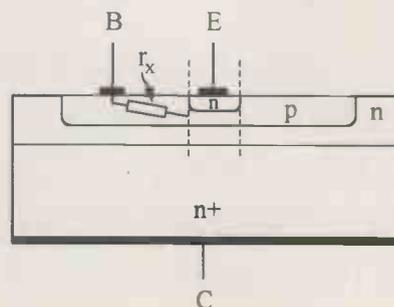
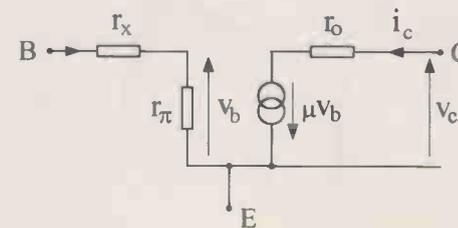


Fig. 10. Practical cross-section of a discrete bjt showing the existence of base bulk resistance (r_x) and unequal junction areas.

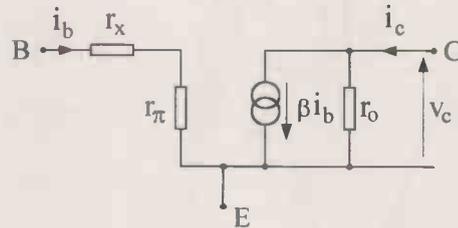

Calling all Radio Engineers

We have excellent opportunities within Research, Design and Test for Radio Engineers to work at all levels in the fields of:

GSM

Fixed Radio Access / WLL

Military CIS

PMR DECT TETRA

Satellite Communications

Mobile Switching




**John Prodger
Recruitment**
Connecting people with opportunities

We would be glad to focus our efforts on securing your next move.

Please call John Darby, ref 2984H.

Tel: 01727 818704 Fax: 01727 838272

Email: johnd@jprecruit.com

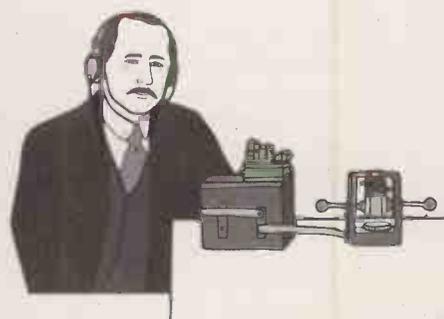

JPR, The Courtyard, Alban Park, Hatfield Rd, St Albans, Herts AL4 0LA.

HARDWARE OPPORTUNITIES

SENIOR ELECTRONICS ENGINEERS

Cambs

to £45,000

Possibly unparalleled opportunity for an excellent all round design engineer to make full use of the skills you possess. You will work as part of a small team, but with minimal supervision covering a range of electronic engineering tasks including design, project management and consultancy. With an excellent academic background and at least 5 years experience of product development in a high volume environment, covering microprocessor/digital design, analogue design and real-time software. In return a superb future awaits you in one of the UK's premier organisations. **Contact Steve Davis**

RF DESIGN ENGINEERS

Middx/Berks/Surrey/Wilts/Avon/Cambs/Beds/Yorks/Hants

to £45,000

There is, as always, a huge demand for Engineers with experience of RF circuit design, a majority of these positions exist within the mobile communications and digital broadcast marketplace with both manufacturers and consultancies. There are opportunities from Junior to Consultant level, all requiring a similar background in RF, i.e. baseband to 10GHz, modulators, synthesisers, VCOs, mixers, PAs, LNAs, diplexers and antennas, with low cost, high volume production always being issues. If you would like to find out more about the specific opportunities in your area please call for a no pressure chat. **Contact Steve Davis**

RF TEST ENGINEERS

Various

up to £25,000

Several of our clients are looking to recruit RF Test Engineers who have at least 3 years experience to work in test and development of RF products for telecoms and other coms related products such as cellular phones, base station equipment and network products. You will need previous experience of test to component level up to 20GHz using spectrum analysers, oscilloscopes, meters etc. Other useful skills would include, circuit design skills, test skills in the VHF, UHF, LF and MHz ranges and project management. **Contact Simon Alder**

TEST TECHNICIANS

Bucks

up to £22,000

This company designs and manufactures microwave components, switches, oscillators and a number of very complex intergrations, and they are looking to recruit a number of Test Technicians to work in a clean room environment. The ideal candidate will be at least HNC qualified have experience in the alignment and testing of microwave products and be expected to use a range of test equipment. In return this company offers five weeks holiday a year, private medical cover and a very good contributory pension scheme. **Contact Simon Alder**

TEST DEVELOPMENT ENGINEER

Berks

up to £25,000

This control systems company are looking to recruit a Test Development Engineer. The overall purpose of this position is to provide test engineering expertise to the test department and support to internal customers, developing cost effective test solutions to automate product testing. The ideal candidate will be BSc/HND qualified, have experience of analogue and digital circuit design, ATE test techniques, software development (Visual Basic, HP VEE), fault finding to component level and experience of volume electronic test. **Contact Simon Alder**

MATERIAL MANAGERS

Various

up to £35,000

We have a number of clients seeking Material Managers. The successful candidates preferably educated to degree standard will have a 'Hands-On' approach, proven man-management skills, experience in a materials function and excellent interface skills with customers on material issues/problems. If you are capable of developing systems and procedures to contribute towards the advancement of these companies and are looking for a challenge, please give us a call!! **Contact Simon Alder**

For further details of these and other current vacancies

Contact Simon Alder, Solution

The Tower House, High Street, Aylesbury, Bucks. HP20 1SQ

Tel: 01296 336036 Fax: 01296 336037

Email: simon@soltech.co.uk Visit our Website: www.soltech.co.uk



Who needs a degree?

It seems nothing short of BEng will do if you want to succeed as an engineer. Someone should have told last year's award winning electronics engineers Kim Dennis and Amanda Box. Richard Wilson reports

A point of view expressed during last year's *Recognising the Engineer* campaign was that you need to have spent at least three years at a university obtaining a degree before you could rightly call yourself an 'engineer.' It seems that for some engineers desperate to maintain their status, nothing short of a BEng – and probably one from a red brick university – will do if you want to succeed as an engineer.

This view of the world is surely misguided. If you still need convincing then look no further than the career paths of two award-winning electronics engineers, Kim Dennis and Amanda Box.

Kim Dennis, IT specialist skills group manager at Marconi Communications beat off stiff competition to take the title of 1998 Young Woman Engineer of the Year.

Dennis, who is responsible for career development resource management and work load scheduling, received her award and a cheque for £1000 in January from Her Royal Highness The Princess Royal.

Twenty-six year old Dennis

started her association with the telecoms manufacturer, formerly known as GPT, straight from leaving school in 1988. Under a technical apprenticeship with GPT she studied for her Ordinary National Diploma (OND) in electrical and telecommunications engineering at Coventry Technical College.

On completion of that course, Dennis studied for a further two years at college as a sponsored student with GPT. In 1992 she qualified with a Higher National Diploma (HND) in electrical and telecoms engineering.

The real benefit of being a sponsored student was that Dennis walked straight into the job she wanted at GPT. For Dennis the career ladder started as a systems support specialist with GPT's IT department. Within three years she became a team leader and by 1998 she was managing a team of 20 IT specialists within the company.

As a project manager Dennis is involved in planning and monitoring IT programmes. But she also accepts the importance of her role in managing and monitoring the career development of her team

Amanda Box, a senior software engineer with Thomson Marconi Sonar, was another electronics engineer commended in the awards.

She took an HND in software engineering and was sponsored by GEC Marconi Avionics in Rochester. Box spent three years with GEC before transferring to Thomson Marconi Sonar where she worked as a software engineer in the airborne anti-submarine warfare group.

With experience working on systems for the Royal Navy's Sea King and EH101 Merlin helicopters (pictured) under her belt she was promoted to a senior software engineer leading a team of ten staff.

As a team leader Box is involved in data processing software design and implementation, but she also has management tasks such as budget control for her area and the selection of training courses for all the project engineers. ■



Dennis... Started as a technical apprentice at GPT.

The logo for MDM (Mark Wheeler Design Management) features the lowercase letters 'mdm' in a white, sans-serif font. The letters are set against a dark blue rectangular background. To the right of the text, a white sphere is partially visible, appearing to be part of a larger graphic element.

Radio Communications

DESIGN SUPPORT ENGINEER ~ Cambs to £28K

The future in digital radio technology looks very rosy and you can be part of a design team writing product specifications and reviewing drafts for conformity in this area. 2 years radio experience (ideally PMR) is sought together with a relevant degree. Familiarity with MSOffice is also essential to write technical reports and outline specifications. Quote WW9903-51.

▼ Contact Mark Wheeler for more information.

RF IC DESIGN ENGINEER ~ Bristol to £45k

Make a mark for yourself and be the first IC designer in this established and fast growing Radio Systems Design House. You'll be working alongside a very fine multidisciplinary team of Engineers involved in some of the most stimulating projects around. Competent hands on skills are required including experience up to 3GHz together with some good ideas. Quote WW9712-17.

▼ Contact Mark Wheeler for more information.

PRODUCTION ENGINEER ~ Bristol to £30k

A sound knowledge of small to medium volume production and manufacturing techniques is required here. Experience of liaising with small multi-disciplined R+D teams and being able to pro-actively work with outside contractors is essential. A general electronics background is required, ideally with radio communications experience. Quote WW9811-54.

▼ Contact Mark Wheeler for more information.

RF PA DESIGN EXPERTS ~ Bristol to £40k

Involved in projects that seem to go on forever? Stuck in a corner working on the bit your boss says you have to do? Yes? Then your salvation is at hand with this fast growing Wireless Communications company where your talents can be truly realised. Accomplished design skills up to 3.5GHz in high power PA's ideal, receiver and synthesisers development experience very useful. Quote WW9707-56.

▼ Contact Mark Wheeler for more information.

BENCH TECHNICIANS ~ Notts £10k - £22k

Component level expertise? Board level diagnosis? Shiny new technical qualification? This leading cellular maintenance organisation wants you!! You don't have to have communications product experience (although it would help), but you'll be keen to keep abreast of the latest technology. All this in a positive, friendly environment too! Quote WW9703-37.

▼ Contact Mark Wheeler for more information.

DSP SOFTWARE ENGINEER ~ Bristol to £34k

For this one, you'll need to bring to the table at least a year's expertise in DSP Algorithm development, real time embedded software and an understanding of hardware design. You would be working on radio modems, linear amplifiers and many other interesting and challenging projects. A radio background is desirable but not essential. Call us today if it sounds like you. Quote WW9804-30.

▼ Contact Mark Wheeler for more information.

SYSTEMS ARCHITECT ~ Wilts to £44K

This prestigious company has risen to become a world leader in mobile communications. This has been achieved by attention to detail and quality systems second to none. To maintain this position, they are seeking UMTS systems specialists to define the core network architecture for mobile UMTS systems. A good team player with a flexible attitude, you should have experience in GSM protocols/simulation and data networking. Quote WW9811-30.

▼ Contact Malcolm Masters for more information.

DIGITAL DESIGN ENGINEER ~ N. Wilts to £35k

This role has been created to work within a small team on the latest digital communications systems. You will be involved in developing VHDL code for FPGA and ASICs for radio base stations. Significant experience in digital design, VHDL and FPGA is required along with strong academic achievements. Quote WW9811-34.

▼ Contact Malcolm Masters for more information.

CELLULAR REPAIR SUPERVISOR ~ N.W. Lon. to £19k

Our client is a significant player in the sales and service of cellular products. They are actively looking for a supervisor from the cellular/comms/PMR industry to repair and test a wide variety of cellular phones and run a start-up service dept. C&G/HNC or relevant industrial experience required. Quote WW9811-46.

▼ Contact Rich Wootten for more information.

SERVICE REPAIR TECHNICIANS ~ Surrey c.£18k

This is a great opportunity for a keen RF technician to work in a lively atmosphere for a major manufacturer of PMR equipment. You'll need to be able to service and repair to component level and have relevant mobile comms involvement. Some Band 3 and installation experience would be desirable but is not essential. Quote WW9811-52.

▼ Contact Rich Wootten for more information.

TEST DEVELOPMENT ENGINEER - Bristol to £30K

Our client is a fast growing British company that specialises in PC based video telephony. They require an individual to design and implement test procedures and non-ATE hardware and software used in design and production. Experience in SMT, C/C++ embedded software for PC's and HP-Vee/Labview is desirable. Quote WW9902-32.

▼ Contact Rich Wootten for more information.

PRODUCT SUPPORT ENGINEER ~ Berks to £25k

Our client is at the forefront of mobile telecoms, having released several of the most popular products on the market. Now it's your turn to get a slice of the action. You'll need to be able to support the introduction of complex mechanical parts into manufacture and maintain build standards in a demanding industry. HNC and electro-mech background required. Quote WW9811-09.

▼ Contact Rich Wootten for more information.

mdm recruitment
Brinkworth House, Brinkworth, Nr. Swindon SN15 5DF
Telephone: 01666 511311 Fax: 01666 511308
Email: markw@mdm.co.uk
Email: richw@mdm.co.uk
Email: malcolm@mdm.co.uk

ARBOUR
APPOINTMENTS LTD



PLACING ENGINEERS FIRST

SOFTWARE ENGINEER

Bath Salary £18,000 to £25,000

Software development for embedded microprocessor and microcontroller based systems. Assembler and C are both required skills. Any hardware knowledge would be a distinct advantage, as would serial communications exposure.

Quote ref. WWA389

HARDWARE ENGINEERS

North Midlands Salary £23,000 to £29,000

Engineers required with experience of FPGA and/or ASIC. There will be system architecture design and some small signal digital & analogue. Knowledge of current CE and EMC standards and PCB layout constraints would be ideal.

Quote ref. WWA401

ELECTRONICS ENGINEER

North East Salary £18,000 to £22,000

Engineer required to join fast growing company producing Audio & Video Recording Equipment for the professional sector. Analogue & digital skills required. PIC, 8051 & 16bit microcontroller exposure, EMC & product approval desirable.

Quote ref. WWA438

SOFTWARE ENGINEERS

Birmingham Salary £20,000 to £30,000

Engineers with a good degree required to join a dynamic team working in an innovative environment. To work with leading edge technologies and high-end microprocessors/DSPs. Requires C/C++ for real-time embedded systems.

Quote ref. WWA205

ELECTRONICS ENGINEER

Cotswolds Salary £18,000 to £25,000

Design consultants based in a pleasant Cotswolds setting require creative engineers with experience in digital/analogue design for microprocessor based systems. Software skills in C and assembler ideal. Variety of exciting design tasks.

Quote ref. WWA124

SOFTWARE ENGINEER

Midlands Salary £21,000 to £25,000

Graduate ideally with design experience to work on projects employing Win 95/NT/98, Visual Basic, C, and M68000/TMS320/Z80 series microprocessors. Software & firmware to control advanced materials testing equipment.

Quote ref: WWA295

SOFTWARE ENGINEERS

Derbyshire Salary £20,000 to £28,000

Probably degree educated with two or more years' experience writing real-time software for embedded control systems. You must have knowledge in C and assembly language. Hardware design exposure is also essential.

Quote ref. WWA437

SOFTWARE ENGINEERS

South Midlands Salary £16,000 to £28,000

A good degree, relevant industrial experience and a flair for embedded control applications, to join this leading edge technology driven company. Must have experience in either PIC assembler or TI TMS320 DSP development.

Quote ref. WWA132

SOFTWARE ENGINEERS

North Salary £13,000 to £24,000

Many vacancies exist from graduate entry level to Senior Engineers to work on real time process control projects. You will be using C/C++ to write software for embedded systems. Knowledge of Windows 95/NT would be an advantage.

Quote ref. WWA338

HARDWARE ENGINEER

West Midlands Salary £22,000 to £27,000

An exciting opportunity exists for an Engineer with a bias towards analogue circuit design. There will be a little digital design and some RF exposure. This is a hands-on role working for a market leader on a range of control technologies.

Quote ref. WWA393

Contact Jon Hopkins in total confidence:

Telephone on: (01902) 326460

E-mail your CV: jon@arbour.co.uk

Fax your CV 24 hrs: (01902) 326465

Post your CV, quoting reference, to:

Arbour Appointments Ltd.

The Granary, High Street, Wombourne

West Midlands WV5 9DN

Find your future with Kelly Technical

Southern Area Vacancies

→ Service Manager - Berkshire

With extensive experience of digital/analogue audio and visual avionics equipment repair to component level. Management experience including recruitment, training and performance analysis is essential for this busy and challenging environment. To £28K plus an attractive package.

→ RF Test Engineer - Middlesex

As part of a small, friendly team your experience of RF equipment fault finding to component level will make an extremely important contribution to this well established specialist mobile radio company. Salary to £18K plus benefits.

→ RF System Design Engineers - Hampshire

Working to customer or published specifications, e.g. ETSI, CCITT, HMGITT and with a minimum of 5 years experience in GSM, PCN, PCS, SATCOM or related fields. Key experience areas are frequency and level planning, spurious identification/management and the understanding of time domain considerations. Salary to £35K plus a comprehensive benefits package.

→ RF Test Engineer - Berkshire

With a Degree or HND in Electronics or a similar discipline and extensive RF test experience, you will perform functional testing of equipment to customer requirements. An appreciation of Military Standards and PC applications for report writing and procedures will also be required. An attractive salary and benefits package is on offer.

→ ASIC Designer - Hampshire

A minimum of 2 years experience of Signal Processing Design using HDL such as VHDL, Verilog or similar, Synthesis and Gate Development Simulation and a thorough understanding of ASIC Architecture design and Technology. Salary to £35K with an excellent benefits package and working environment.

For details of the above and other electronics vacancies in the South of England telephone Roy Parrick on 01703 237200 or fax on 01703 634207. Alternatively E-Mail to southtech@kellyservices.co.uk

Midlands Vacancies

Our Lincolnshire based client is an international market leader in the manufacture and sale of RF Communications Equipment and Systems. Due to continuing growth the following positions are available:

→ Procurement Manager

Degree In Economics, Business Studies or related discipline; knowledge of international purchasing and procurement strategies; 3-5 years experience in a procurement environment. Experience in an electronics or communications company would be an advantage. Applicants who do not currently have manager status who feel they are ready to move into a management role will be considered. Salary c£24-29k

→ Customer Support Engineer

To install and commission radio systems world wide, and to train customers personnel on the systems installed. Must have HNC in communications plus a minimum of 3 years experience in telecomm networks and VHF/UHF radios. Salary c£20-25k.

→ DSP/Digital Engineer

With real-time design experience in signal processing and simulation including DSPs (Analogue devices ADSP 2171, Assembler/c) and FPGAs. Must be experienced in the use of CAD tools, e.g. Matlab and MathCad with ISO9001 familiarisation. Salary c£30-35k.

→ Systems Engineer / Manager

To carry out system design and supporting calculations for proposals and produce technical proposal documentation. Degree in Electronics, Communications Engineering or related discipline required. In depth knowledge of communications system design. At least 8 years in a communication systems engineering role with a minimum of 3 years in a senior position. Salary c£25-35k.

→ Commissioning Engineer - Cambridge

To install and commission complex analogue and digital communication systems including Base Station Radio, Wide Area VHF/UHF coverage systems etc. Degree in electronics or equivalent experience and the ability to fault find at component level. World wide travel required. Salary c£20-25k

**Contact: Emma Eagle, Tel:(01733) 554315; Fax: 564132;
Email: peterboroughtech@kellyservices.co.uk**

KELLY
TECHNICAL

'Working to Develop Careers'



Checking C *in situ*

Cyril Bateman presents possibly the best ever general-purpose meter for checking electrolytic capacitors without removing them from the board.

Diagnosing a failed aluminium electrolytic capacitor mounted on a printed circuit board is more difficult than for other capacitor types, which fail as short circuits.¹

Normally, when an aluminium electrolytic capacitor fails, it exhibits a higher than normal impedance. But its capacitance value may be little changed, and usually stays well within tolerance so measuring capacitance does not help.

Aluminium electrolytic capacitors are self repairing. Defective areas in the oxide dielectric are replenished by new oxide growth, consuming some of the oxygen available from the electrolyte. This self-repairing action ultimately becomes the wear out mechanism.²

An aluminium electrolytic capacitor's service life ends when oxygen needed to maintain or repair the oxide dielectric cannot be provided by the electrolyte. Electrolyte conductivity is reduced, increasing the capacitor's equivalent series resistance, or ESR, and hence its impedance at all frequencies. There's more on this in the panel entitled 'Electrolytic capacitor ESR.'

This increase in impedance is analogous to inserting a resistor in series with the capacitor, affecting the phase angle of applied signals and lengthening the device's time constant.

Increased ESR, or impedance, of an aluminium electrolytic capacitor at room temperature indicates a failure or pending failure. The ESR and impedance of unused capacitors varies widely with capacitance value and voltage. So a change in impedance or ESR is almost impossible to diagnose reliably, except by comparing the capacitor being tested with an identical unused one, Table 1. This is discussed further in the panel entitled 'Impedance or ESR?'

By comparison, the measured tangent δ of unused capacitors at 100Hz is a relatively constant number, regardless of value or voltage rating of the capacitor. $\tan\delta$ is a direct indicator of capacitor quality, Table 2.

At any chosen frequency, a capacitor's $\tan\delta$ relates the capacitor's ESR and capacitance value. Any increase of ESR results in a corresponding, easily identified, increase of $\tan\delta$.

What is tanδ?

The tanδ of a capacitor at any frequency, is directly related to its capacitance value and ESR at that frequency.³

$$\tan \delta = \frac{ESR}{X_C} \tag{1}$$

where,

$$X_C = \frac{1}{2\pi FC}$$

Alternatively $ESR = X_C \times \tan \delta$ and $\tan \delta = ESR \times 2\pi FC$.

You might find it easier to visualise these relationships by looking at a capacitor's current, voltage and impedance vector drawing, as in Fig. 1. As you can see, with the X_C vector unchanged, increasing the ESR vector reduces the loss angle θ , increasing the complementary angle δ . On the other hand, increasing the ESR vector only slightly increases $|Z|$, the impedance vector.

As δ increases, so does its tangent. Known as tanδ, this figure indicates the quality of a capacitor. The smaller tanδ, the better the capacitor. Any increase in tanδ directly indicates a degraded component. The panel entitled 'Capacitor quality and tanδ' expands on this aspect.

Why measure tanδ at 100Hz?

All aluminium electrolytic capacitors are tested in production for tanδ at 100Hz or 120Hz, according to the frequency of the maker's mains supply. While many capacitor makers also table high-frequency impedance values, these are not production tested. To maximise yields, the measured tanδ of typical new capacitors will be around 50% of the stated limit value.

The range of 100Hz tanδ measured for new, good capacitors, is extremely small, changing little with capacitance values and voltage ratings.⁴ Tanδ of typical commercial aluminium electrolytic capacitors ranges from a low of 0.02 to a high of 0.3 for large low voltage parts, Table 2.

Aluminium electrolytic capacitor tanδ increases rapidly as the capacitor wears out. It provides a sensitive, easily interpreted measurement. As a general guide, tanδ for typical good board-mounted capacitors should be less than 0.1. Capacitors with a tanδ of greater than 0.2 should be replaced in the interests of reliability.

Good quality commercial electrolytic capacitance bridges measure tanδ, but they can be expensive and not easily portable. In addition, test voltages used may turn-on adjacent semiconductor junctions, invalidating the measurement.

Measuring the tanδ of a board-mounted capacitor requires a low cost, easily portable meter with four terminal contact probes. It also requires a suitably low test voltage and a quick unambiguous measured result. Unable to identify such an instrument I resolved to build one.

Measuring tanδ on a pcb

How then could the tanδ of a board-mounted capacitor be measured?

From equation 1, it is clear that the ratio of the capacitor's ESR to its capacitive reactance is needed. You do not need to know the true value of either, only the relative values. This simplifies the task.

Accurate measurement of individual values requires accurate control of the measurement current used and its exact frequency. Since ratios are being evaluated, circuit current is common to both

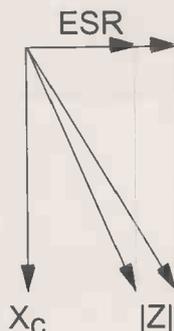


Fig. 1. Illustrating the effect an increase of ESR has on measured impedance and tanδ. The 37.5% increase of ESR shown, must, according to Pythagoras, result in a 37.5% increase in tanδ. The impedance magnitude, $|Z|$ however, only increases by 6.9%.

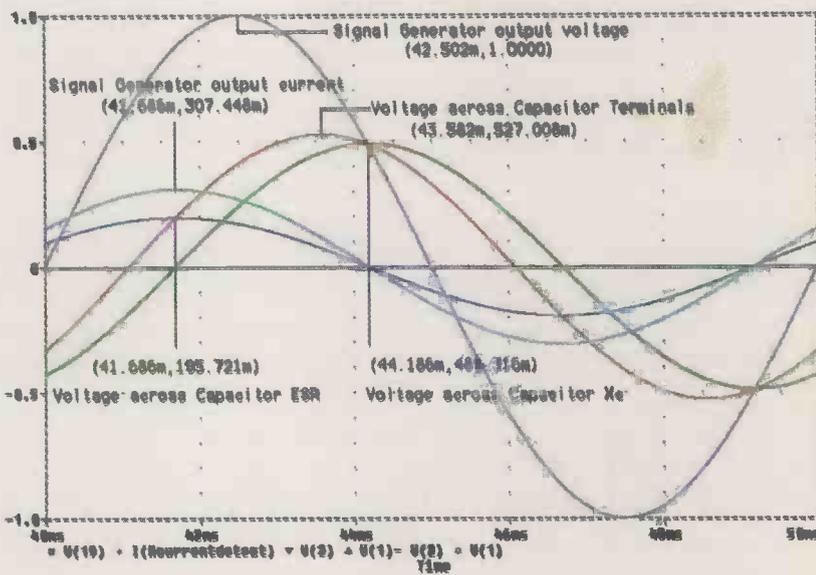


Fig. 2. PSpice plot of a simple series CR circuit representing a 'bad' 1000µF capacitor having a tanδ of 0.4 at 100Hz. Generator source impedance is 2.2Ω. This 0.4 tanδ is represented by a 0.6366Ω series resistance. The phase angle between the generator current (cyan) and the voltage across the capacitor terminals (red), is not 90°. However the phase angle between the voltage developed across the capacitor's ESR (blue) and across the capacitor's reactance (green), is exactly 90°.

Table 1a). Typical impedances measured at 100kHz – low capacitance values.

Capacitor	1µ	2.2µ	4.7µ	10µ	22µ	47µ	100µ
50V bipolar Al.	4.0Ω	3.2Ω	1.4Ω	0.9Ω	0.35Ω	0.3Ω	0.22Ω
63V polar Al.	4.3Ω	3.5Ω	1.8Ω	1.4Ω	0.5Ω	0.4Ω	0.28Ω
450V polar Al.	24Ω	11Ω	5Ω	3.8Ω	1.5Ω	1.0Ω	

Table 1b). Typical impedances measured at 100kHz – high capacitance values.

Capacitor	1000µ	2200µ	4700µ	10 000µ
25V polar Al.	0.090Ω	0.07Ω	0.045Ω	0.022Ω
63V polar Al.	0.050Ω	0.025Ω	0.015Ω	0.010Ω

Table 2a). Typical tanδ values of new capacitors measured at 100 Hz – low capacitance values.

Capacitor	1µ	2.2µ	4.7µ	10µ	22µ	47µ	100µ
50V bipolar Al.	0.05	0.05	0.05	0.05	0.05	0.05	0.06
63V polar Al.	0.04	0.04	0.035	0.035	0.035	0.045	0.04
450V polar Al.	0.1	0.1	0.08	0.05	0.05	0.05	

Table 2b). Typical tanδ values of new capacitors measured at 100Hz – high capacitance values.

Capacitor	1000µ	2200µ	4700µ	10 000µ
25V polar Al.	0.06	0.075	0.09	0.1
63V polar Al.	0.03	0.05	0.06	0.07

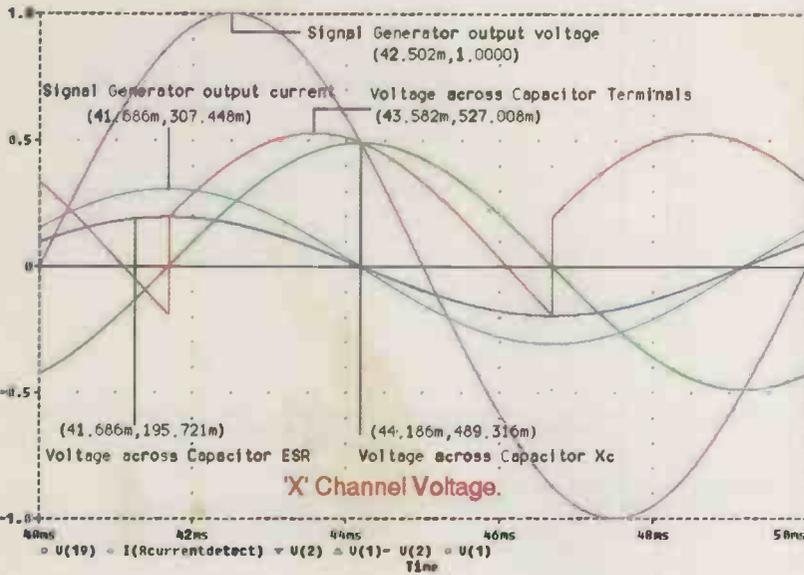


Fig. 3. Figure 2 repeated except the red trace now shows the synchronous detector voltage for the 'X' channel, which represents the capacitor's reactance. This trace must be integrated to a steady average voltage before it can be used

parameters so its value need not be known.

Capacitance and ESR are treated as separate components in the simulations that follow. With a practical capacitor, neither parameter is available at the capacitor terminals. Circuit simulation ignores such constraints. By means of a series CR circuit, a capacitor's internal voltage, current and its relative phases can all be explored.

Using PSpice and a series CR equivalent circuit, I plotted the current and voltage waveforms for a variety of capacitor tanδ values. To illustrate a failed capacitor, I assumed a 1000µF component with a tanδ of 0.4. A low generator source impedance was used to plot generator current, Fig. 2.

The phase angle between the voltage developed across the capacitor terminals and the source generator current, is clearly not 90°. It varies with capacitor tanδ or ESR and with generator source impedance, so it cannot be defined.

Current from the generator source is exactly in phase with the capacitor's through current and the voltage developed across its ESR. The voltage developed across the capacitor's reactance remains displaced in time by exactly 2.5ms, representing a quarter cycle, or 90° of phase.

Full measurement schematic, less decoupling capacitors, used in my prototype meter. Additional circuitry is included, but not shown here, for the test signal source generator and the dry battery powered, stabilised switched-mode ±5V supplies. The small modification needed to my PM128/7106 display module is described in the text.

Readers interested in PCB and parts details please send an SAE marked 'Capacitors' to Electronics World's editorial offices, from where it will be forwarded to Cyril.

The problem now is how to measure these two voltages. The only accessible voltage that can be measured is that across the capacitor terminals – i.e. its impedance.

Initially I planned to use two synchronous rectifiers. One would be timed to coincide with the generator current, representing the voltage developed by the ESR. The second would be delayed by a quarter cycle to measure the voltage developed by the capacitor's reactance. Averaging both then dividing the results would derive the capacitor's tanδ.

Further PSpice simulations show this simple approach was not practicable. Both sampled voltages contain large negative-going elements, requiring long integration times. Illustrated is the waveform of the capacitor's reactance voltage, labelled as 'X' channel, Fig. 3.


Towards faster results

Looking at Fig. 4, the curve for the capacitor's ESR in particular has nearly equal positive and negative elements and needs a long time constant to average. For the instrument to be useful as a diagnostic tool though, it is desirable for it produce results in less than a second. Assuming the standard electrolytic test frequency of 100Hz and using PSpice simulations, I was unable to achieve satisfactory averaging in an acceptable time.

A better plan

While this basic timed sampling concept was obviously correct, a means to expedite averaging was required.

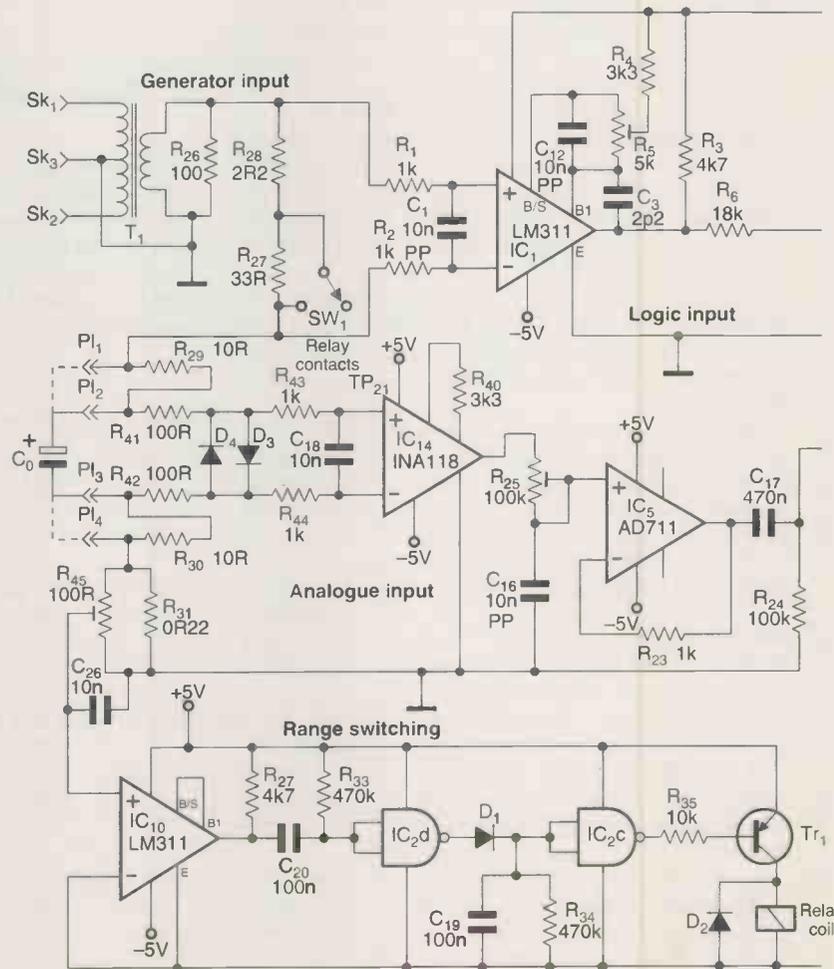From further simulations, I found a reduction of the sampling periods to 90° or less was beneficial. It was even more



as sampling time was reduced. Short sampling periods require a sample-and-hold circuit together with timing and control logic. My original concept of a simple tester had suddenly become more complicated.


My first task was to generate two sampling waveforms, exactly 90° apart, one coinciding exactly with the peak of the generator's output current. I decided to use a 4046 CMOS phase-locked-loop. While locked to an input signal, the 'phase-comparator 1' phase detector of a 4046 is claimed to have a 90° phase difference between the input signal and its VCO output.⁵

Initial trials confirmed that this figure of 90° only applied while the input signal and the PLL centre frequency coincided. Small component changes – even ambient temperature drifts – affected this phase difference. Time for a rethink.

I evaluated several options, and eventually decided to double the signal's frequency, then halve it to ensure equal mark:space ratios. Application of some decoding logic to both frequencies could produce exactly 90° phases, as needed.

As before, the 4046 phase locked loop was used, but this time, its 'phase-comparator 2' detector output was fed into a 4018 configured to divide by two. I obtained two square-wave signals, both having equal mark:space ratios. The first was at 100Hz and phase locked to the generator's current waveform. The second was at 200Hz and had rising edges coincident with the 100Hz waveform transitions.

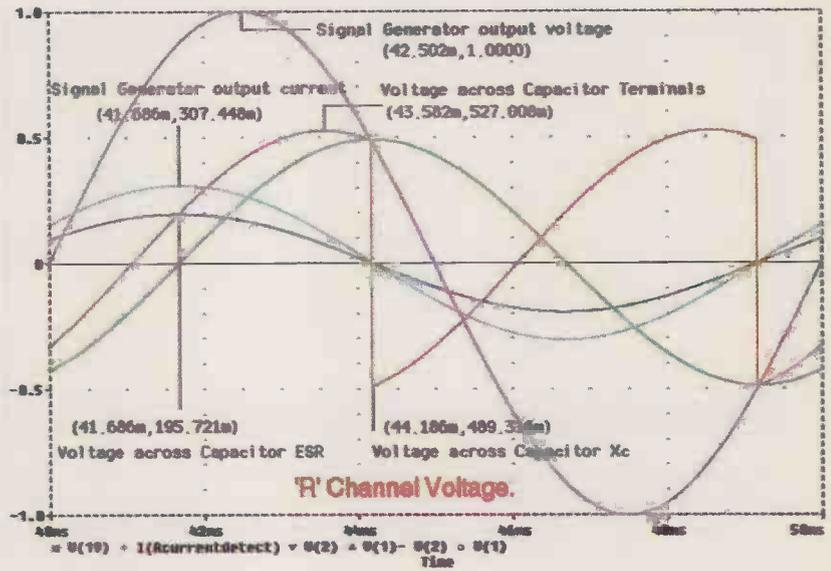
These signals were easily decoded to identify the 90° and 180° points of the generator's current waveform using a pair of dual input Nand gates, IC_{6a} and IC_{9a} in the schemat-



ic. The rising edges of these decoded outputs were used to trigger two monostable multivibrators, Fig. 5.

Sample and hold circuits need a short time to track then hold the input waveform. Any change in voltage during the sample period causes errors. From my PSpice plots, I decided to sample this changing waveform for a minimal time of, say, 5° of the waveform maximum, Fig. 6.

Fig. 4. Figure 2 again, but this time the red trace shows the synchronous detector voltage for the 'R' channel, representing the capacitor's ESR. This waveform requires excessive integration time for use in my meter. Testing unused, small tanδ capacitors, this trace after integration results in a very small output of just a few millivolts.

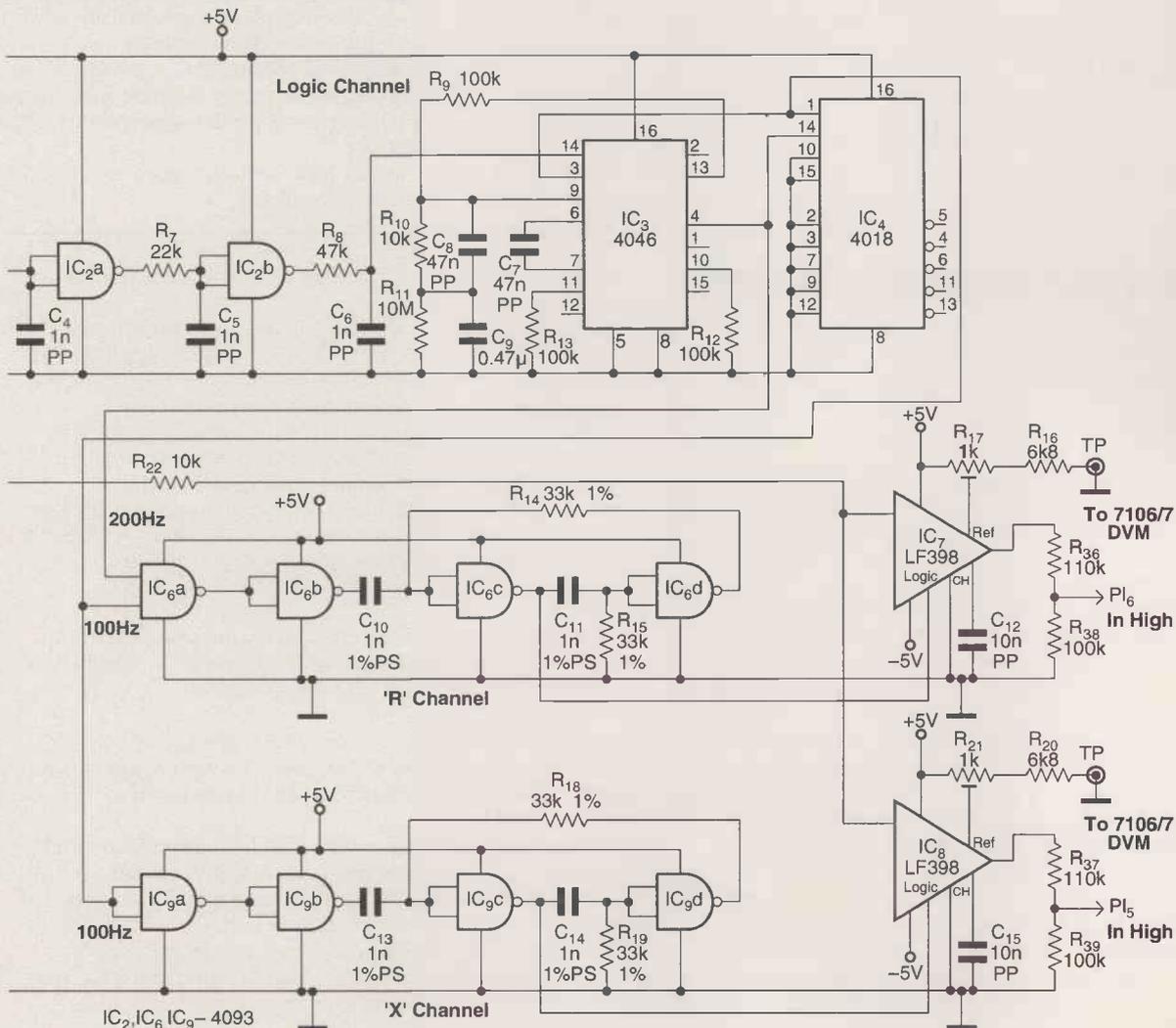

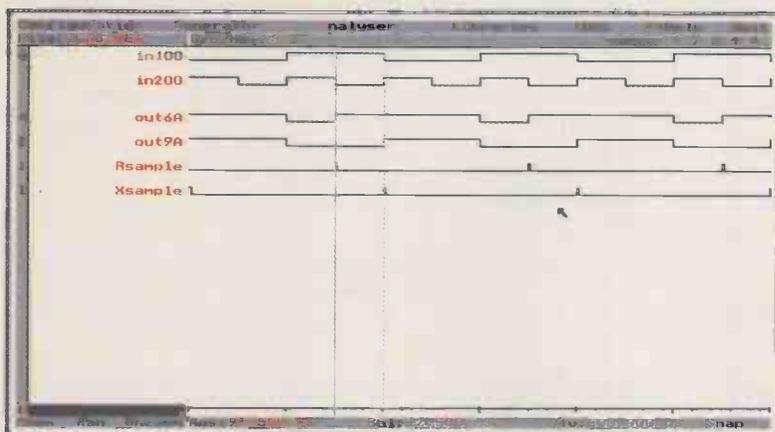


Fig. 5. This Pulsar simulation illustrates the method used to generate the logic control signals from the original 100Hz and its doubled frequency. These brief sampling pulses are used to control the 'R' and 'X' sample and hold integrated circuits.

The LF398 sample-and-hold chip requires at least 20µs to acquire the sampled signal. Practical experiments using an LF398 and test capacitors of varying tanδ indicated that 3°, or around 80µs sampling time, gave good results.

Having a method to sample the ESR and X_c components in the capacitor voltage waveform, I could now design the generator and current sensing circuits.

Generator problems

One particular difficulty was the wide range of capacitance values. I wanted to include everything from 1µF to 10000µF.

At 100Hz, a 1µF capacitor's impedance is around 1600Ω, but a 10000µF component only exhibits around 160mΩ at the same frequency. A constant test current was not possible.

To avoid turning on any semiconductor junctions connected to the capacitor, a low test voltage is essential. Some HP5082-2080 low voltage Schottky barrier diodes were found to conduct at 200mV AC. From experiments measuring tanδ of capacitors with and without a parallel

HP5082-2080 diode, I determined the maximum test voltage to be 150mV. At this voltage, any effects on capacitor tanδ value from semiconductor junctions in the same circuit as the capacitor being measured are negligible.

Allowing a low generator source impedance and a 2.2Ω current-sensing resistor, this 150mV signal requires some 50mA of generator current. With the unfavourable voltage/current phase angles needed, this proved difficult using battery powered op-amps.

Having tried various options – including high current or booster op-amps and low power audio output amplifier chips – I decided to trade voltage for current. A low-cost miniature LT700 audio transformer needing only ±1.5V push-pull drive at negligible current improves battery life.

Current sensing

Using the above generator and an LM311 comparator for the logic channel input stage, I could finalise the values of the current sensing resistors. Ideally one would ensure the test capacitor's impedance was within a factor of ten of the sensing resistance used. Experimentation confirmed that a 2.2Ω sense resistor was usable for test capacitances of 100µF or more.

Lower capacitance values proved more difficult. Ideally, three sense resistor ranges were needed but having only two would be more economical. Sense resistors larger than 100Ω were prone to trigger the comparator by noise picked up on the test leads.

Testing 1µF capacitors with a 10Ω sense resistor the comparator did not provide reliable triggering. A compromise of 35Ω was chosen, allowing good measurements down to 2.2µF – and even 1µF with reduced accuracy.

As a final refinement, two Schmidt trigger Nand gates were used to clean up and slightly delay the comparator output. This was done to prevent comparator noise from triggering the phase locked loop.

My current-sensing logic circuits, needed for the sample and hold stages, were completed.

Impedance or ESR?

The impedance of any capacitor is easily measured. Simply subject the capacitor to a known current and measure the voltage developed across the capacitor terminals. Impedance

$$|Z| = \frac{\text{voltage}}{\text{current}}$$

using Ohm's law, much like measuring a resistance value.⁶

Searching Internet and trade publications revealed a few high frequency 100kHz capacitor impedance testers, but not one single low cost meter to measure tanδ.

While many of these were labelled as ESR testers, this is a misnomer since all the meters I found measured impedance. Based on the mistaken belief that at 100kHz capacitive reactance is zero, they thus claimed to measure ESR.

This presents a problem with smaller capacitance values of, say, 100µF and below. Brand new, many makes exhibit 100kHz impedances greater than 0.5Ω, simply because their capacitive reactance approaches this value. Regrettably these are the values most used on circuit boards.

When measured, the capacitance value of all aluminium electrolytic capacitors reduces substantially as frequency increases. Typical values at 100kHz are perhaps 50% – and frequently much less – of the 100Hz value.

One brand-new 100µF capacitor I measured at 100kHz using a precision bridge had an impedance of 570mΩ. Its capacitance at 100kHz was only 37.5µF. By comparison, a better make had an impedance of 170mΩ, and 64µF

capacitance. Both these capacitors were new and well within their makers' specifications.

Capacitors of 1000µF or more will be above self-resonance by 100kHz and thus behave as DC blocking inductors. Good and bad capacitors then have an impedance of less than 0.5Ω.

These are just two of the problems met measuring impedance at 100kHz. Measured results need interpretation. Impedance values cannot simply be read as good or bad, they must be compared with a similar and unused capacitor.

Some meters incorrectly claim to be able to distinguish between good and bad capacitors in circuit. I have seen them with scales marked 'good' for values below 0.5 to 1Ω, 'compare' for values up to 10Ω and 'bad' for all higher impedances.

I have measured 100kHz impedance values ranging from 0.01Ω to 24Ω for known good, unused aluminium electrolytic capacitors. Clearly it is not possible to pre-define specific good/bad impedance values.

If their readings require interpretation, why then do these meters measure impedance? The answer is simply that it is an extremely easy measurement to perform, compared to measuring tanδ or ESR.

The results of these 'ESR' meters require interpretation and comparison against known good capacitors. Measuring a suspect capacitor's high-frequency impedance however is better than simply guessing at good or bad.

As a long time capacitor engineer also experienced in designing and repairing circuits, I have learned that what is really needed is in-circuit measurement of tanδ at 100Hz.

Capacitor analogue voltage waveform

For my prototype, I wanted to provide two capacitor test methods, flexible four-terminal test leads and a four-terminal component jig.

Typical commercial test leads have a resistance of 0.1Ω . Since it is necessary to measure ESR down to 0.010Ω , a four terminal measurement system is essential. For those of you who are not familiar with this technique, four-terminal measurement involves supplying the test current along one pair of leads and measuring capacitor voltage via a second pair.

True four-terminal measurement requires complete separation of the current and voltage leads. Contact is made to the capacitor lead wires, using 'Kelvin' clips. This is not practicable when probing printed board mounted capacitors though.

As a compromise I found some test prods that could be wired four terminal except for the final 30mm long brass probe points, which each measured $0.45m\Omega$. As a result I was forced to accept $1m\Omega$ of common contact resistance, resulting in a small but acceptable error when measuring the largest value capacitors.

The resistance of the earthy probe lead, together with the range sense 0.22Ω resistor, means the test capacitor's voltage is effectively floating. This necessitates the use of an instrumentation amplifier as the first input stage of the analogue measurement channel.


The $150mV$ generator voltage, fed via the 2.2Ω sense resistor, means large test capacitance values develop very small voltages. To minimise sample and hold errors, these low level test signals were amplified in the *INA118* in-amp, taking care to stay within the working range of the *AD711* amplifier and *LF398* sample-and-hold circuits.

The small delay deliberately built into the comparator and logic channel circuits is offset using an adjustable *RC* delay at the *INA118* output. This delay is adjusted as part of the meter calibration.

Range switching

An adjustable, voltage-sensing comparator and reed relay was used to short out the 33Ω current sensing resistor when measuring capacitors bigger than $47\mu F$.

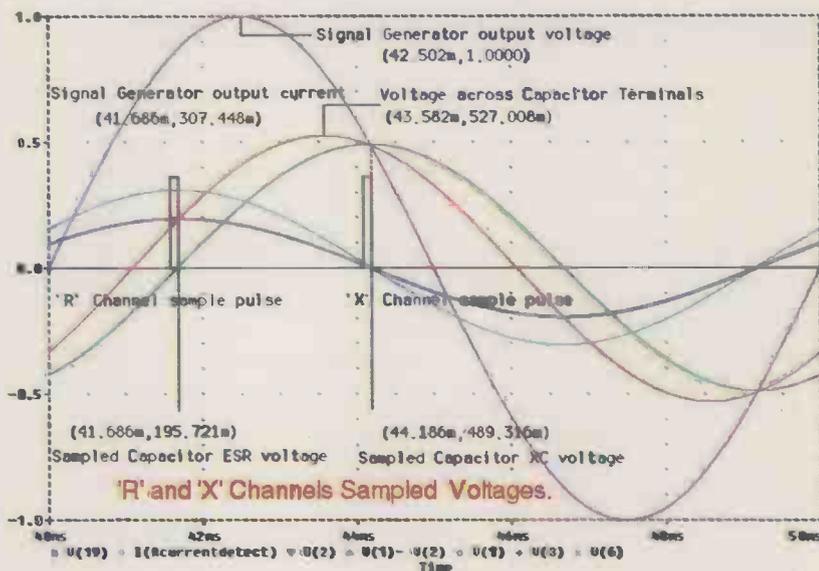Having completed the circuits needed to measure the volt-



ages relating the test capacitor's ESR and reactance, all that remains is to divide the 'R' channel voltage by the 'X' channel voltage and display the result.

Various options including multiplier/divider chips and log/antilog circuits were considered. Following some practical experimentation, I found that they could be dispensed with.

The *7106* DVM integrated circuit compares the measurement voltage against its pre-set reference voltage. This reference voltage is set to 50% of the desired full scale. Removing two resistors, R_2 and R_3 , I managed to disconnect this reference voltage from a *PM128* pre-packaged display module.

An adjustable voltage was fed to the REF-HI input terminals, a second to the normal IN-HI terminals. Both commons went to the input ground. I found this package could divide and display the result extremely accurately, provided both voltages were within the meter's maximum 2V input range.

Fig. 6. Sample-and-hold logic control voltages, superimposed onto the Fig. 2 plot. The logic decoding circuitry, which permitted the successful design of my meter, occupies over 70% of the measurement section of the 140mm by 74mm printed board.

Electrolytic capacitor ESR

Aluminium electrolytic capacitor electrolytes are conducting solutions, usually a neutralised weak acid in a solvent. This electrolyte must not freeze or boil at the extremes of the capacitor's working temperature range, or attack pure aluminium at any temperature. Most modern electrolytes are made without adding water, but a small water content, as water of crystallisation in some of the ingredients, is inevitable.

In a capacitor, some of this electrolyte is contained within the minute voids and channels in the anode and cathode foils oxide coating. These channels can be tenuous and very long relative to their cross section.² The effective electrolyte resistance in them increases with frequency.

Most of the electrolyte however will be absorbed in the separator, usually a paper tissue, interwound with the anode and cathode foils during assembly. The resistivity of the electrolyte/paper separating tissue is increased, compared to the bulk electrolyte, depending on paper type and thickness used.

The aluminium oxide films on the anode and cathode foils both contribute frequency dependent dielectric losses. A parallel loss resistor could represent these losses, but for aluminium electrolytic capacitors, equivalent series loss resistance is used.

The aluminium metal foils together with connecting leads,

etc., contribute a small metallic resistance element.

At any frequency the capacitor's ESR is the combined effect of the foils series loss resistance and these metallic resistances, added to the electrolyte paper resistance.

Consequently a capacitor's ESR varies with measurement frequency, tending initially to reduce as frequency increases. At intermediate frequencies it becomes nearly constant. Then at frequencies where the capacitor has become inductive, it increases more rapidly.

An aluminium electrolytic capacitor's ESR is strongly influenced by its internal temperature. An increase in temperature reduces ESR. Below $0^\circ C$ the capacitor's ESR increases rapidly. The viscosity of the solvent in the electrolyte increases as it approaches its freezing point.

Most of all, ESR depends on the capacitance value and to a lesser extent its voltage rating. At a particular voltage rating, all other things being equal, doubling a capacitor's value will halve its ESR.

A particularly common mistake is to consider a capacitor's ESR as having a fixed value. Clearly from the above, that is not possible.

ESR for any particular aluminium electrolytic capacitance value and voltage rating, is a combination of many effects, especially measurement frequency, temperature, physical size of the capacitor element, and details of its construction.

Setting up

I tried to make this meter as free from calibration as possible. Calculating the ratio of the 'R' and 'X' channel voltages, the sense resistor value, and test current or voltage being common to both need not be accurately known. Only one adjustment using a known or relatively loss free capacitor is needed to calibrate the meter.

First, connect a stabilised power supply delivering +5V and -5V. With a capacitor connected to the test terminals of the meter to ensure the sample and hold circuits are triggered, temporarily remove the analogue input signal to both sample and holds. This is easily done by grounding the junction of their common inputs with R_{22} .

Measuring the DC output voltages of both sample and holds in turn, trim both to 0V then unground R_{22} . Remove the test capacitor and adjust the offset of the current sensing comparator, IC_1 , for maximum output noise, then back off to just remove all noise while ensuring that the comparator output remains 'low'.

Apply a 47 μ F capacitor to the test leads or jig and adjust the range switching comparator input voltage pre-set to just turn off the relay, extinguishing the range LED. Replace the capacitor with a 100 μ F type and ensure the relay and LED just turn on when connecting the capacitor.

None of the above adjustments are particularly critical but they do help ensure consistent operation of the meter. This final adjustment sets the meter's accuracy.

Apply a 10 μ F polycarbonate, polypropylene or P.E.T. metallised-film capacitor of known $\tan\delta$ to the test leads or jig. Monitor the output voltage of the 'R' sample and hold. Turn the delay-adjusting pre-set resistor on the *INA118* output until the display reads the correct $\tan\delta$ while ensuring the output from the 'R' sample and hold remains a small but positive voltage. If you don't know the $\tan\delta$ of the 10 μ F capacitor, then adjusting the display to read 0.006 should ensure acceptable accuracy.

Supplying power. Standing idle or measuring low-value test capacitors, the meter consumes around 21mA from the negative supply and 26mA from the positive supply. Consumption increases with large capacitors to a maximum of 23mA from -5V and 45mA from +5V, but only for the few seconds while connected to a test capacitor.

Some 12mA of this additional +5V current is needed for the range switching reed relay and its indicator LED.

In practice, 6AA cells provide some 40 hours use. The prototype's power supply used a low drop-out linear +5V stabiliser and a switched capacitor inverter for the -5V side. A transistor switching stage provides the ± 9 V floating supply for the display. To conserve batteries, a 20 minute 'auto-switch-off' timer circuit disables the +5V stabiliser, removing all power.

The *LF398* sample-and-hold chips, fed with the test capacitor's amplified voltage, provide a maximum output of about 4V. A simple attenuator, halving these voltages, completed my design.

Compared with the very simple circuits using two quad op-amps to measure capacitor impedance at say 100kHz, this circuit is obviously larger and much more complex. Its setting up and calibration however is extremely simple, as described in the panel entitled 'Setting up.'

How does it perform?

In practice, this meter performs extremely well, returning a steady measured value within three display meter counts, or less than a second. As to its accuracy, this more than suffices to distinguish between good and bad board mounted capacitors.

With the exception of measurements on capacitors near 1 μ F and 10000 μ F, where accuracy reduces, it is hard to tell whether my laboratory capacitor bridge or this meter is the more accurate.

If pressed to give a number, I would guess that this meter reads $\tan\delta$ to within about ± 0.005 of the true value, except at the extremes of its capacitance range.

While I now only trouble-shoot new prototype designs, repair my own workshop equipment and the usual family TV, videos and satellite systems, I wish I had built this meter years ago. Being well equipped with laboratory capacitance bridges though, I had not seen the need.

I only built it now because when examining a 100kHz impedance 'ESR' meter, I suddenly thought 'there must be a better way'. This meter is the result of that simple desire.

As a bonus, the meter could also be used as a circuit tracer. Presented with a resistance of less than 20 Ω , the high range LED lights and the $\tan\delta$ display shows over range. ■

References

1. Bateman, C., 'Understanding capacitors,' *Electronics World* August 1998
2. Bateman, C., 'Understanding capacitors,' *Electronics World* June 1998
3. Reference Data for Radio Engineers, pub. Newnes, Oxford.
4. Data Handbook — Electrolytic Capacitors, pub. Philips Components.
5. Phase-Locked Loop Design Fundamentals, AN35 pub. Motorola Inc 1994
6. Bateman C. 'Looking into impedance,' *Electronics World* August 1997
7. Bateman, C., 'Understanding capacitors,' *Electronics World* December 1997

Capacitor quality and $\tan\delta$.

The quality of many high-frequency components, such as RF inductors and very low loss capacitors, is often defined by their 'Q' factor. Q is the result of dividing a component's measured AC reactance by its AC resistive losses.

The reciprocal of 'Q' is $\tan\delta$, which is defined as the capacitors ESR/reactance. $\tan\delta$ is used to describe the quality of almost all general-purpose capacitors.

All practical capacitors exhibit losses. There is a small DC leakage current and there are resistive dielectric losses, which combined dissipate some of the applied energy as heat. These losses reduce the theoretical 90° phase difference between the applied current and the capacitor's voltage.

At 1kHz for example, the measured phase angle of a typical 1000 μ F 25V radial electrolytic capacitor was 67°, substantially less than the theoretical 90° of phase.

This phase angle could be reproduced in a circuit by using a


high value resistor in parallel with the capacitor. Electrolytic capacitors however, use the phase equivalent circuit of a low value resistor in series with the capacitor. The series resistance for the above 1000 μ F 25V capacitor was measured at 1kHz and found to be 71m Ω , X_C was 169m Ω and $\tan\delta$ was 0.42.

At 100Hz, the ESR of this capacitor measured 104 m Ω , X_C was 1.62 Ω and $\tan\delta$ was 0.064. This series resistance is the equivalent series resistance, or ESR, of the capacitor.⁷

The capacitor's reactance reduces in proportion to its capacitance value and frequency. Being a combination of fixed and variable losses, ESR also reduces with frequency but to a lesser extent. Having reached its minimum value, ESR then usually increases at some higher frequency.

The measured $\tan\delta$ of an aluminium electrolytic capacitor is frequency dependent. It always increases as frequency increases. From equation 1, $\tan\delta$ has no upper limit and can exceed unity — especially for a failed aluminium electrolytic capacitor.

Not just a pretty interface

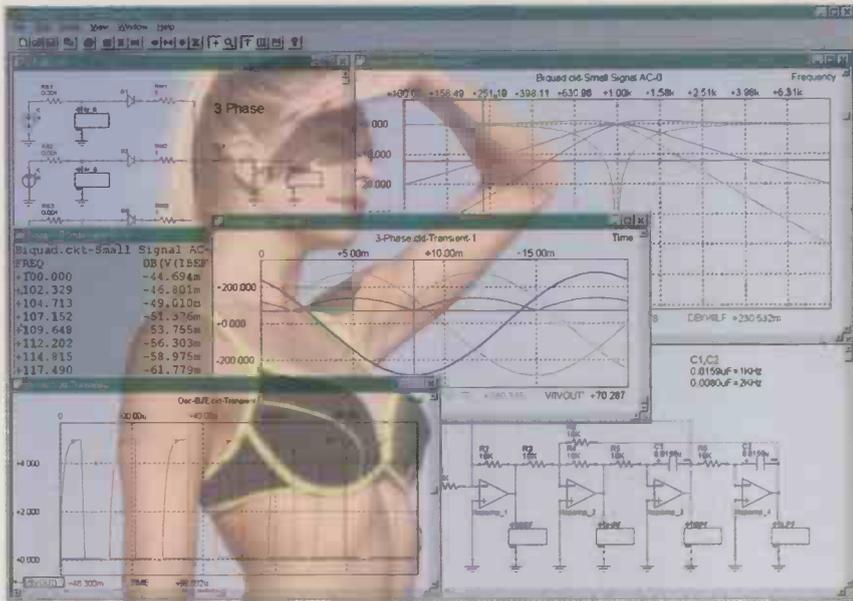

Available on 30 day evaluation
Free technical support
Mac version also available



B² Spice for analogue simulation £199
B² Logic for digital simulation £199
Special bundle price £295

All prices shown exclude VAT
Postage & Packing £5.00

B² Spice & B² Logic

Professionals, universities and designers need software that produces results they can rely on. B² Spice and B² Logic will give you the accurate results you need - fast.

The best way to find out if a package is really what you need is to try it, which is what we're giving you the chance to do, risk free for 30 days.

We guarantee you will be 100% satisfied with the results or your money back.



Tel: 01603 872331

Research House, Norwich Road, Eastgate, Norwich NR10 4HA Email rd.research@paston.co.uk www.looking.co.uk/spice

CIRCLE NO.117 ON REPLY CARD

LOW COST

Embedded Control

with extra **BYTE!**

Low cost
Embedded Control
Control Systems
Custom Design
Micro-Controllers
Logic Controllers
Data Loggers
Analogue & Digital I/O



CAMBRIDGE
MICRO
PROCESSOR
SYSTEMS LIMITED

Units 17-18, Zone 'D',
Chelmsford Road Industrial Estate,
Great Dunmow, Essex
UK CM6 1XG
Tel: +44 (0) 1371 875644
Fax: +44 (0) 1371 876077

<http://www.cms.uk.com>

CIRCLE NO.118 ON REPLY CARD

PIC BASIC

Write your PICmicro programs in BASIC!

- Quicker and easier than "C" or assembler
- Expanded BASIC Stamp I compatible instruction set
- True compiler provides faster program execution and longer programs than BASIC interpreters
- 12CIN and 12COUT instructions to access external serial EEPROMs
- More user variables
- Peek and Poke instructions to access any PICmicro register from BASIC
- Serial speeds to 9600 baud
- In-line assembler and Call support (call your assembly routines)
- Supports PIC12C67x, PIC14Cxxx, PIC16C55x, 6xx, 7xx, 84, 92x and PIC16F8x microcontrollers
- Use in DOS or Windows
- Compatible with most PICmicro programmers

The low-cost PicBased Compiler (PBC) makes it easy to write programs for the fast Microchip PICmicros. PBC converts these programs into hex or binary files that can be programmed directly into a PICmicro microcontroller. The easy-to-use BASIC language makes PICmicro programming available to everyone with its English-like Instruction set. No more scary assembly language!

The **PicBasic Pro** Compiler runs on PC compatibles. It can create programs for the PIC12C67x, PIC12CE67x, PIC14Cxxx, PIC16C55x, 6xx, 7xx, 84, 9xx, PIC16CE62x AND PIC16F8x microcontrollers. The PicBasic Pro Compiler instruction set is upward compatible with the BASIC Stamp II and Pro uses BS2 syntax. Programs can be compiled and programmed directly into a PICmicro, eliminating the need for a BASIC Stamp module. These programs execute much faster than their Stamp equivalents. They may also be protected so no one can copy your code!

Pic Basic - £49.95 Pic Basic Pro - £149.95
Supplied with manuals and sample basic programs
Pic programmers from £15.00 (kit) to £49.95
All plus £5 P&P & 17.5% VAT

Join the world wide PIC Basic mail list, email:-
majordomo@quonos.net with "subscribe picbasic-L" in the message

Call Now for a brochure and full list of Basic Instructions
or <http://www.crownhill.co.uk/picbasic/home.html>

CROWNHILL ASSOCIATES LIMITED

The Old Bakery, New Barns Road,
Ely Cambs. CB4 7PW
Tel: +44 (0) 1353 666709 Fax: +44 (0) 1353 666710

CIRCLE NO.119 ON REPLY CARD

Antenna Toolkit

by Joe Carr

Combined with antenna design software on CD-rom, Newnes' new book *Antenna Toolkit* provides a complete design solution. Prepared by antenna expert Joe Carr, this package is written for beginners and advanced users alike.

On the CD-rom is a suite of powerful software running on the pc. The software calculates the critical lengths and other parameters of the antennas in the book by having the user select the antenna type and set the frequency.

The main menu screen is in the form of tabs, one for each chapter of the book plus other topics.


This 220 page work includes 185 illustrations and 23 photographs.

** HF propagation predictor included **

Also included is a Windows freeware package, from the Voice of America organization, called VOACAP. This is an hf propagation predictor which some commercial sources have offered unmodified for hundreds of dollars.

UK Price: £27.50 Europe £30.00 ROW £32.50

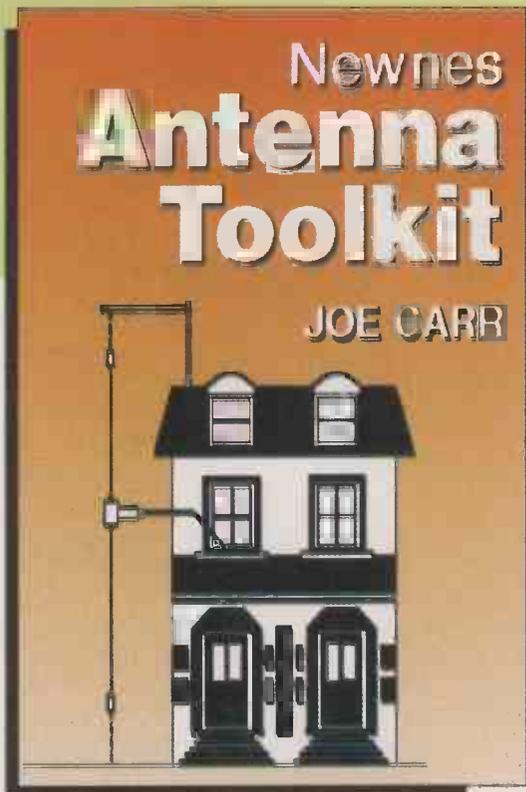
** Price includes delivery and package **



What's in the book?

Radio Signals On The Move; Antenna Basics; Wire, Connections, Grounds And All That; Marconi and Other Unbalanced Antennas; Doublets, Dipoles And Other Hertzian Antennas; Limited Space Antennas; Large Loop Antennas; Wire Array Antennas; Impedance Matching; Simple Antenna Instrumentation & Measurements

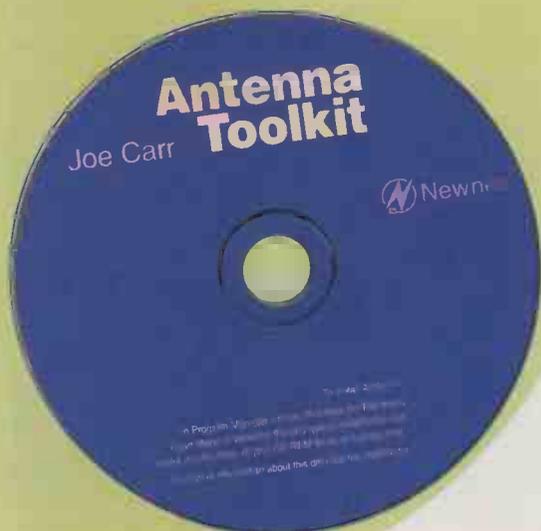Includes free CD with antenna design software



Return to Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following title:

Newnes Antenna Toolkit

Total _____

Name _____

Address _____

Postcode _____ Telephone _____

Method of payment (*please circle*)

Access/Mastercard/Visa/Cheque/PO

Cheques should be made payable to Reed Business Information


Credit card no. _____

Card expiry date _____

Signed _____

Please allow up to 28 days for delivery

SPEAKERS' CORNER

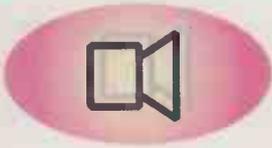

Why does the average 100W moving-coil loudspeaker only deliver two or three watts of sound? John Watkinson looks at why the moving coil loudspeaker is so inefficient, and explains the trade-offs.

The efficiency of a moving coil loudspeaker is doomed from the outset to be very low. The reason is that the density of air is low and so the acoustic impedance is correspondingly low.

To deliver power into a low impedance requires a high diaphragm or cone velocity. This in itself isn't a problem. The difficulty is that any practical cone and coil which isn't going to fall apart must have some structural mass and the impedance presented by this mass dwarfs the acoustic impedance in a real speaker.

Figure 1 shows that effectively we are transporting a massive cone in order to carry with it a tiny air mass. Its the equivalent of delivering pillows in an eight-wheeler; not very efficient.

The efficiency of a speaker is defined as the ratio of the acoustic power coming out to the electrical power going in. The electrical power is used in three ways. One is the ohmic heating of the coil. The second is the mechanical damping of the drive unit structure and the absorbent in the enclosure, which is very small above resonance and can be neglected. The third is the acoustic power transferred.

In practice, because the efficiency is so low, the acoustic power can also be neglected, leaving the input power as simply the ohmic loss in the coil. This is a great simplification. Coil dissipation is easy to calculate as it is the square of the current times the coil resistance.

Next we need to calculate the acoustic output power. In electricity, the power would be the square of the current times the resistance. In acoustics, it's the square of the cone velocity times the acoustic impedance.

Acoustic impedance

Figure 2a) shows the expression for the acoustic impedance. I'm asking for this to be accepted for the moment, but I intend to explore it further in a future article.

The expression for acoustic

impedance can be simplified by taking out the fixed values and replacing them with a constant, K, which we can't change whatever we do to the drive unit. These fixed values are things like the density of air, the speed of sound and the correction factor for the kind of baffle. Note that the acoustic impedance is a function of frequency squared.

Figure 2b) shows how the cone velocity is obtained. Clearly it is proportional to the motor force, Bli . Because the system is mass controlled, the velocity is inversely proportional to frequency and mass.

In Figure 2c), the acoustic power is derived by multiplying the acoustic impedance by the square of the velocity. Note that when this is done, the frequency term cancels out. This is the principle of the mass controlled speaker: the power is independent of frequency. In other words, there is a flat frequency response.

The efficiency is derived in 2d). Note that the current disappears from the expression. Thus an efficient speaker is simply a matter of using a strong magnet with plenty of wire in the gap and a large cone area, while keeping the weight and the coil resistance down. Unfortunately those requirements are contradictory because the more powerful we make the motor, the heavier it gets. Not so simple after all.

Expressing efficiency efficiently

A better approach is to express the efficiency in a different way so that the effect of the mass of the motor is easier to interpret. This is the approach taken in Fig. 3. If you assume a speaker whose coil is the same length as, or shorter than, the gap, then all of the coil is contributing to the motor force.

The mass of the voice coil, M_c , is given by its volume multiplied by the density of the coil material. The resistance of the voice coil also follows from its dimensions and resistivity.

With the efficiency re-expressed, it is

easier to see what to do. Firstly a powerful magnet helps, but as was shown last month, this can't be taken too far in a passive speaker because the result is an overdamped system. It is also clear that when choosing a coil material, the product of the density and the resistivity is what matters, hence the superiority of aluminium.

It should be appreciated that M_m , the

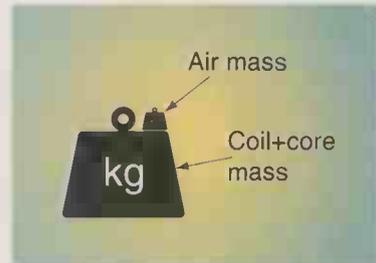


Fig. 1. Moving-coil speakers are doomed to be inefficient.

Fig. 2. Loudspeaker efficiency calculations.

$$R_m = 1.57 \frac{\rho}{c} \omega^2 r^4 = K \omega^2 r^4 \quad (a)$$

where R_m is acoustic impedance, 1.57 is the baffle factor, ω^2 is frequency in rad/s, r_4 is cone radius.

$$v = \frac{Bli}{\omega M_m} \quad (b)$$

Here, v is cone velocity, ω is frequency, B is magnetic flux density, l is the length of motor coil inside the gap, i is current and M_m is the moving mass. Below, W_a is acoustic power,

$$W_a = v^2 \times R_m = \left(\frac{Bli}{\omega M_m} \right)^2 \times K \omega^2 r^4 = Kr^4 \left(\frac{Bli}{M_m} \right)^2 \quad (c)$$

so,

$$Eff = \frac{Kr^4 B^2 l^2 i^2}{M_m^2 i^2 R_E} = Kr^4 \times \frac{B^2}{M_m^2} \times \frac{l^2}{R_E} \quad (d)$$

moving mass, incorporates M_c , the coil mass. The most striking result of the efficiency expression – which is counter intuitive – is that making the coil heavier without changing the total moving mass increases the efficiency. As a result, for efficiency we want the cone to be as light as possible so that the largest proportion of the moving mass is concentrated in the coil. The

epitome of this is the ribbon speaker where the diaphragm is the coil.

Working together

The above expressions fail when the speaker coil and cone no longer move as a rigid body. In woofers, the cone and coil are certainly rigidly coupled over the useful frequency range. So the approach is useful except for the

assumption that all of the coil was in the gap which is generally not true for woofers.

In order to have sufficient travel, woofers generally use overhung coils so that the Bl product remains constant as the coil moves.

If the coil length is described as L times the gap length, then L can be called the overhang factor. If the coil is simply extended by putting more turns above and below the gap, the coil is obviously L times as heavy and has L times as much resistance.

Figure 4 shows that the efficiency expression now contains L squared in the denominator, suggesting that a large overhang factor is bad news.

This is one of the reasons why really long throw woofers are rare. They are simply very inefficient because so little of the coil is producing thrust and the rest is adding to the mass and resistance. In practice, to obtain a given SPL it may be more efficient to put two normal woofers side by side rather than trying to engineer a long throw device. ■

Fig. 3. Efficiency considering motor construction.

$$M_c = lad \quad R_e = \frac{\sigma l}{a}$$

$$a = \frac{\sigma l}{R_e}$$


and

$$M_c = \frac{l\sigma l d}{R_e} = \frac{l^2 \sigma d}{R_e}$$

$$\therefore \frac{l^2}{R_e} = \frac{M_c}{\sigma d}$$

$$\therefore \text{Eff} = \frac{Kr^4 B^2}{\sigma d} \times \frac{M_c}{M_m^2}$$

Fig. 4. Overhung coils in woofers cause inefficiency

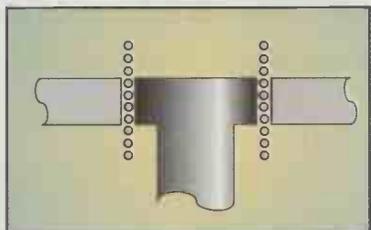

$$\text{Thus } M_c = Llad \text{ and } R_e = \frac{L\sigma l}{a}$$

$$\text{Efficiency becomes } \frac{Kr^4 B^2}{L^2 \sigma d} \times \frac{M_c}{M_m^2}$$

FM Embedded Controllers at a ground breaking price!

WEB SITE
http://www.cms.uk.com

£95 each
PER 100 UNITS



OPTIONAL EXTRAS

Additional extra features to the FM 200

- ◆ LCD Port Graphics or Alphanumeric
- ◆ Key Pad Port 64 Keys 8x8
- ◆ 8 Channels 8 bit analogue in
- ◆ 2 Channels 8 bit analogue out
- ◆ 8 Channels 13 bit analogue in
- ◆ Up to 32 Digital I/O Channels
- ◆ Up to 8 Mbytes of SRAM Battery Backed
- ◆ Up to 512 Kbytes of Flash EEPROM
- ◆ 1 Mbyte EPROM Space

The range of 'FM-Controllers' provide most of the features required for embedded control at a very low cost

FEATURES FM-200 Controller

- ◆ 68K Micro-Controller 14 MHz clock
- ◆ 512 Kbytes Flash EEPROM
- ◆ 512 Kbytes SRAM Battery Backed
- ◆ 2 RS232 Serial Ports
- ◆ 1 RS232/RS485 Serial Port
- ◆ Real Time Calendar Clock (Y2K Compliant)
- ◆ Watchdog & Power fail detect
- ◆ 10 Digital I/O Lines
- ◆ 2-16 bit Counter/Timers
- ◆ I²C Bus or M-Bus
- ◆ Expansion Bus
- ◆ Size 100x80 mm

OTHER FEATURES

- ◆ Up/Download removable card for data logging and or re-programming
- ◆ STE I/O Bus, 68000 and PC Interface
- ◆ Designed, Manufactured and supported in the UK

DEVELOPMENT

The PC Starter Pack provides the quickest method to get your application up and running

Operating System

- ◆ Real Time Multi Tasking
- ◆ Unlimited copy licence

Languages

- ◆ 'C', Modula-2 and Assembler
- ◆ Full libraries & device drivers provided

Expansion

- ◆ Easy to expand to a wide range of peripheral and I/O cards

Support

- ◆ Free unlimited telephone, FAX, email and Internet support

Custom Design

- ◆ CMS will design and manufacture to customers requirements



CAMBRIDGE MICROPROCESSOR SYSTEMS LIMITED

Units 17-18, Zone D Chelmsford Road Industrial Estate, Great Dunmow, Essex UK CM6 1XG Tel. +44 (0) 1371 875644 Fax: +44 (0) 1371 876077

CIRCLE NO.120 ON REPLY CARD

electronics **WEEKLY**

HyperACTIVE

The UK's best read for
electronics professionals
on the internet

Electronics Weekly **HyperACTIVE** is more than just a magazine on the Web. Check out the site and you will see why thousands of electronics professionals around the world regularly log on to...

www.electronicswweekly.co.uk

If you are serious about Internet marketing, then sponsorship of the Electronics Weekly **HyperACTIVE** site is something you must consider.

Whether you have your own web site or not, **HyperACTIVE** offers you a great way of delivering your company's products or message to a worldwide buying audience.

By sponsoring a section of **HyperACTIVE**, users will have the opportunity to link directly to your web site - therefore generating new traffic.

For more information on how to develop your internet marketing activity please call Shaun Barton on 0181 652 3638.

Point your browser at
<http://www.electronicswweekly.co.uk>
register now, it's free

sponsored by



TOSHIBA

XILINX
The Programmable Logic Company™



Science World Discovery Book

ADVERTISEMENT: Some details are hereby given from the above book which will be published as soon as possible. Nigel Bryan Cook, publisher.

The BBC2 Horizon programme on 28 Jan 98 showed how astronomers have recently used constant-energy supernovae at different distances to discover that there is no long-range gravitational retardation in the big bang expansion. Gravity seems to be localised, not a universal law.

This was predicted by the mechanism of gravity based on I. Catt's measurements of capacitor discharge speeds and the Catt Anomaly, and their implications for Maxwell's light "theory" and the true c-speed spinning electron, eg see *Catt's March 1983 WIRELESS WORLD* article "Waves in Space", his 2-vol "Electromagnetic Theory", his paper in *IEEE Transactions on Electronic Computers, EC-16 (Dec 67)*, and especially *SCIENCE WORLD* magazine (ISSN 1367-6172) February 1997-current.

The old (incorrect) quantum theory of gravitons has the 377Ω dielectric of free space/vacuum/ether filled with a sea of colliding virtual particles which exert a pressure by hitting objects from all sides, except sides which face large objects which shield us from them. For example, the earth in graviton theory absorbs gravitons coming from below us, so we would be pushed down from gravitons from above, but not pushed up so much because we are walking on a massive shield (the earth). This theory, considered geometrically, gives the Newtonian inverse square equation. The two errors are that (a) gravitons would cause drag on moving objects, thereby slowing down the planets and causing them to spiral into the sun, and (b) gravitons, causing the measured deflection of starlight during eclipses, would scatter photons about instead of smoothly deflecting them as actually occurs.

To correct this theory, we must take space to be a continuous medium. Einstein in his 5 May 1920 lecture at Leyden University, *Ether and Relativity* (reprinted in Einstein's *Sidelights on Relativity*, Dover, New York 1952, 1983) said (pages 15, 16, 23): "The special theory of relativity forbids us to assume the ether to consist of particles... To deny the ether is ultimately to assume that empty space has no physical qualities whatever... Recapitulating, we may say that according to the general theory of relativity, space is endowed with physical qualities... therefore, there exists an ether. According to the general theory of relativity space without ether is unthinkable."

The continuous nature of the ether is demonstrated to readers of EW by the fact that electron (particle)-filled cables have an impedance in Ω/metre (thus depending on the number of discrete electrons), but ether has an impedance of 377Ω (not Ω/metre).

Aristotle in *Physics* (350 BC), and Louis de Broglie in *Non-Linear Wave Mechanics: A Causal Interpretation* (Elsevier, Amsterdam, 1960) argued respectively that the momentum of objects and that particle-wave duality can be explained by a model which basically has particles moving through space like a fish or submarine in a frictionless, non-particulate water (the ether). The inertia to start motion is that of setting up a flow of ether around moving particles, hence an arrow continues to move after being released from the bow, and an electron sets up a motion-sustaining wave of ether around it in the ether so that it diffracts through slits. I create a sideways wave of air from front to back as I move, or a vacuum would form behind me. Since all matter is made of sub-atomic particles, the ether waves are similarly small. Ether is a continuous, frictionless, medium which flows around moving sub-atomic particles.

Hubble showed that the Doppler shift of light spectra from stars at increasing distances gives $v/d = \text{constant}$, where v is the recession speed of the star from us, and d is

the distance of the star from us *at the time the light was emitted*, which is a time into the past with increasing distance because starlight travels at $c = 300$ mega-m/s. In reality, the distance D that the stars are really at now (15 gigayears after big bang) is equal to: $D = d +$ (the distance the star has travelled in the time $t = d/c$ since the light was emitted). Hence: $D = d + vd/c$. Hence, the true Hubble ratio is not v/d , but v/D or $v/(d + vd/c)$. This is not constant. We can get a constant form of the original Hubble ratio only by dividing the speeds v into the travel times of the light, t , so v/t is a true constant, and is equal to vc/d or "Hc". This, Hc, has units of acceleration. Acceleration is significant because multiplied with mass it gives force, such as force of gravity.



The big bang universe has known mass and size, with an energy of 10^{56} megatons of TNT equivalent. A nuclear explosion in an air medium produces a supersonic shock wave in air which pushes outwards in a dense, wall-like compressed air shock front. Behind the shock front (Dr Harold Brode of the Rand Corporation calculates, *Ann. Rev. Nuc. Sci.*, v 18, pp 153-202, 1968) the air density drops to as little as just 1% of normal air density. In other words, a *near vacuum* is created *near the middle*. The phenomenon you see is the afterwind. This is a wind of air pushing back towards ground zero, filling in the partial vacuum.

The afterwinds of ether from the big bang may be calculated simply from a consideration of Einstein's proof that all that exists in volume V is matter M and ether A , or: $V = M + A$. When the big bang occurred, the matter M moving outward reduced the matter density in the inner volume V . This has to be compensated (according to the equation $V = M + A$) by an *increase* in the ether. Hence, *ether flows in as matter moves outwards*. (Using calculus, $dV/dt = dM/dt + dA/dt$, which simplified to $-dM/dt = dA/dt$, because $dV/dt = 0$, since V is a constant.)

There is a + and - 3 millikelvin cosine variation in the 2.734 K microwave background radiation (diagram on left). This, from Doppler energy shift theory, shows our absolute motion in space relative to the microwave background radiation. It turns out that the Milky Way as a whole has an absolute speed of 600 km/s, so given the 15 Gyr since the big bang it will have travelled 30 million light years from the point of origin of the big bang, which is only 0.3% of the radius of the universe, so we are probably very near the middle of the universe, which would explain why it looks fairly similar in all directions around us.

Physically combining the findings above (see diagram below), we begin by setting Newton's second law and universal law equal: $F = ma = mMG/r^2$. Dividing out by mM we obtain: $a/M = G/r^2$. The ratio a/M represents the true Hubble constant, "Hc", divided by the mass of the universe concerned (the cylinder inscribing the universe in the diagram). Hence, $a/M = Hc / (\frac{1}{2}\pi r^2 R \sigma)$, where σ is the density of the universe. As Newton states, $a/M = G/r^2$, so we find: $G/r^2 = Hc / (\frac{1}{2}\pi r^2 R \sigma)$. Since the simple estimate of the radius of the universe is given by $R = c/H$, we see that $G = 2H^2 / (\pi \sigma)$, which implies: $\sigma = 2H^2 / (\pi G)$. If we take H to be 73

km/s/Mparsec, $H = 2.4 \times 10^{-18} \text{ s}^{-1}$, and our predicted density of the universe (all matter, visible stars + invisible dust and neutrinos) is $5.3 \times 10^{-26} \text{ kg/m}^3$. Since the nearby density of illuminated matter in space is about $4 \times 10^{-28} \text{ kg/m}^3$, it is predicted that most of the matter in the universe is non-illuminated (agreeing with results from the rate of rotation of galaxies and the physics of neutrinos).

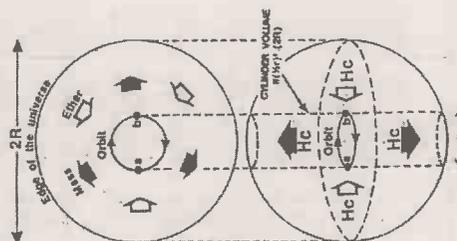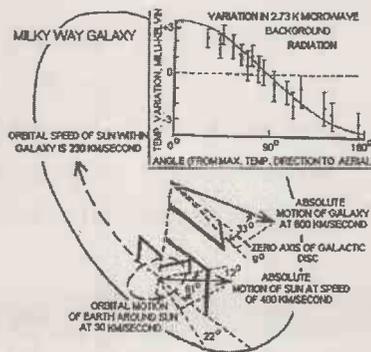

OLSON

THE IEC 320 CONNECTION

OLSON OFFICE FURNITURE CABLE MANAGEMENT WITH IEC 320 SHUTTERED SOCKETS MANUFACTURED TO BS 6396

OLSON ELECTRONICS LIMITED

OLSON PANELS with 10AMP CEE22/IEC SHUTTERED SOCKETS FUSED, DOUBLE FUSED WITH BEARS FILTER AND RCD PROTECTION

OLSON ELECTRONICS LIMITED

OLSON DISTRIBUTION PANELS WITH IEC 320 SOCKETS INDIVIDUALLY FUSED

OLSON ELECTRONICS LIMITED

OLSON DISTRIBUTION PANELS WITH IEC 320 SOCKETS INDIVIDUALLY FUSED AND NEON INDICATORS

OLSON ELECTRONICS LIMITED

OLSON 'THE RACK RANGE' MAINS DISTRIBUTION PANELS FOR 19" RACK MOUNTING HORIZONTAL

OLSON ELECTRONICS LIMITED

OLSON STRIPBLOC CEE 22 EUROPEAN STANDARD AND BS 5733

OLSON ELECTRONICS LIMITED

OLSON 'The Rack Range' CEE22/IE.C. SOCKETS

OLSON ELECTRONICS LIMITED

BUY DIRECT!



24 HOUR DELIVERY SERVICE
 MASTERCARD AND VISA
 CREDIT CARDS ACCEPTED



OLSON ELECTRONICS LIMITED

CIRCLE NO. 121 ON REPLY CARD

OLSON HOUSE, 490 HONEYPOT LANE, STANMORE, MIDDLESEX HA7 1JX
 TEL: 0181-905 7273 FAX: 0181-952 1232

497

Save over £80



Reader offer

1GHz spectrum analyser

Easy to connect and use
The adaptor connects to the oscilloscope via two BNC connectors using true 50Ω impedance for minimal vswr. A calibration button allows a standard -30dBm 50MHz marker signal to be superimposed for precise amplitude and frequency checks.

TSA1000 1GHz spectrum analyser

Designated the TSA1000, this spectrum analyser is in the form of an adaptor that converts any standard oscilloscope into a 1GHz spectrum analyser.

The instrument has a dynamic range of 70dB with a typical accuracy of 1.5dB. Its frequency range is from 400kHz to over 1GHz, and its bandwidth – i.e. selectivity – is 250kHz.

A built-in crystal-controlled marker provides a precision means of frequency and amplitude calibration. The centre frequency can be adjusted over the full 0-1GHz range using a ten-turn control, and is displayed on a large 3.5-digit liquid-crystal display.

Scan width is fully variable between 10MHz and 1GHz, and the scan rate can be set anywhere between 10Hz and 200Hz.

The TSA1000 is supplied with an operating manual describing the basics of spectrum analysis and EMC measurements. Its normal price is £581 including VAT in the UK. Electronics World readers can obtain it for just £499 – including VAT and carriage.

TSA1000 key specifications

Frequency range	400kHz to 1000MHz
Centre adjust	0MHz to 1000MHz
Bandwidth	250kHz (-6dB typical)
Meter accuracy	1% of reading +1MHz
Calibration marker	50MHz fundamental, harmonics to 1GHz
Scan width	1MHz to 100MHz/div
Scan speed	0.5ms to 35ms/div
Amplitude	
Input impedance	50Ω
Amplitude range	-70dBm to 0dBm nominal
Amplitude scale	Logarithmic, 10dB/div
Amplitude linearity	Typically ±2dB
Amplitude flatness	Typically ±1.5dB
Max. input level	+10dBm
Calibration marker	-30dBm ±1dB at 50MHz

Oscilloscope requirements

Oscilloscope mode	X-Y mode, DC coupling; bandwidth not critical
X-Input sensitivity	0.5V/div
Y-Input sensitivity	0.5V/div

Designed and manufactured to IEC1010-1 ● +5 to +40°C, 20% to 80% RH operating range ● 260(W) x 88(H) x 235(D)mm, 1.4kg
Runs from 220/240 or 110/120V at 50/60Hz ● Full operating ranges 198–264V or 99–132V ● Power consumption 8VA max

Use this coupon for your order
Please send me:

..... TSA1000 Spectrum analyser(s) at the fully-inclusive price of £499.

Name:

Address:

Tel no

Total £

Cheques payable to REED BUSINESS INFORMATION

Or debit my visa, master, access or switch card

Card type:

Card No:

Expiry date:

Switch iss no

Please post this order to TSA1000, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Overseas readers can still obtain this discount but details vary according to country. For more information, write or e-mail jackie.lowe@rbi.co.uk. We endeavour to dispatch as soon as possible, but please allow 28 days for delivery.

Enhancing sensing

Joe Carr looks at an easy to apply and general-purpose technique for improving sensor resolution.

There's a number of different forms of spatial sensor that are used to either detect the presence of some other object, or perform imaging of objects. All of these sensors have some sort of response curve that reflects their sensitivity to a target at varying distances or angles off centre.

In Fig. 1, the sensor is defined as some sort of generic electro-optical sensor, for example a photo-transistor or photo-op-amp. It could just as well be an ultrasonic imaging sensor, a radio antenna, or a radar set. When researching this article, the electro-optical sensor was easily at hand, so was used.

The response of the sensor in Fig. 1 is highest immediately opposite the lens, at point X_0 , as indicated by the peak voltage V_p . If the sensor and target translate relative to each other along the X axis, then the signal voltage V will rise from near zero, to V_p , and then decrease to near zero again as the target passes through the field of view.

Although the curve in Fig. 1 looks suspiciously like a bell-shaped curve, actual curves might be shaped a bit differently, but the general form is correct.

Figure 2 shows a somewhat more practical situation found in many circuits. The response curve is the same, but there is a *sensitivity threshold* below which there is little or no output. This threshold might be generated by the brightness or size of the target, by

ambient lighting, or be an intentionally set circuit value. In the latter case, it is common to use such thresholds to combat the effects of noise.

In essence, the threshold level is a signal-to-noise ratio issue. The effect of the threshold is to improve the field of view, increasing the resolution, by narrowing the range of values of V that will be accepted. Even as improved by threshold detection, however, the field of view may be too great to provide adequate spatial resolution.

The *resolution* of the sensor is a measure of its ability to separate two equal targets. If the resolution is not matched to the objects being measured, then an ambiguity occurs. This is seen in popular films such as *Top Gun* where what the F-14 aircrew thought was two enemy fighters suddenly broke out to four dirty smelly bad guys – much to the dismay of the good guys. The radar resolution apparently wasn't able to distinguish two fighters flying close together.

Why improve resolution?

There's a number of practical situations where sensor resolution can cause problems. For example, if a photo sensor is used to count manufactured products coming down an assembly line, poor resolution means the items being counted would have to be further apart in order to avoid a miscount. In imaging systems the resolution can deter-

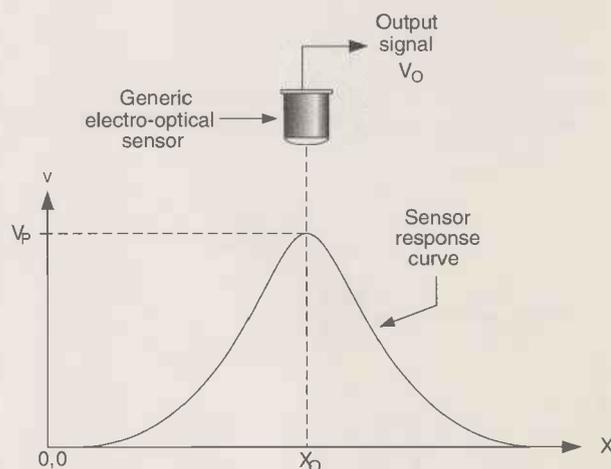


Fig. 1. A generic electro-optical sensor and its response curve.

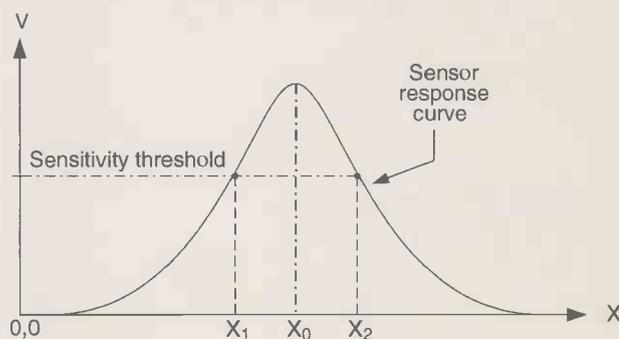


Fig. 2. Sensor response curve. A practical threshold limit narrows the field of view, but not sufficiently for high resolution operation.

mine the smallest object that can be properly displayed.

Poor resolution might cause a distortion of the object being imaged, or completely miss some important feature. It simply wouldn't do for a medical imaging system to miss your kidney stone!

In robotics, if an electro-optical sensor is used as the eyes of the robot

device, then poor resolution can hamper its ability to perceive and negotiate its environment. I recall one smart lad who built a robot that tooted around the room, and when its internal battery dropped below a certain point, then it would search the walls of the room for an electrical outlet.

The robot searched by comparing a pattern of an outlet stored in memory with what it saw in the room. Poor resolution might have caused it to mistake Aunt Annie's belt buckle for the outlet, and wouldn't that have caused a family row?

Figures 3 and 4 show these effects in graphical form. In Fig. 3 a single target is in the field of view of the optical sensor. Assume that the sensor moved left to right across the target, producing the output voltage shown.

It doesn't matter whether the sensor or target moves, so long as there is relative motion between the two along the X axis. Unfortunately, the sensor field of view, which determines the resolution, is too broad, so the target appears to be smeared in the X axis. The size and exact location data are thus distorted.

The situation in Fig. 4 shows two targets in a similar situation. Again we suppose that the sensor translated left to right across the two targets. Because both targets fall inside the field of view simultaneously, they will appear smeared, but maybe with a small dip to indicate the space.

If the dip is too small to detect, then it will not be seen.



This method is derived from a radar technique called monopulse resolution improvement, also known as MRI. There are two versions of the circuit. One uses analogue methods, but requires two sensors – a case of two being much better than one. This first approach can also be implemented in a computer version. A related method can be implemented using a digital computer, but it proves difficult in analogue circuitry.

In radar the target is illuminated with two adjacent co-planar antennas, and the returned signal processed in a special way. Assume that the two signals are V_1 and V_2 . If we create sum, V_1+V_2 , and difference, V_1-V_2 , signals from this raw signal, then we can accomplish a tremendous resolution improvement. The equation is:

$$V_0 = \frac{V_1 + V_2}{k + \text{abs}(V_1 - V_2)} \quad (1)$$

Where V_0 is the resolution-improved signal, V_1 and V_2 are the input signals, abs indicates the absolute value of V_1-V_2 and k is a small full-scale constant

By dividing the sum by the absolute

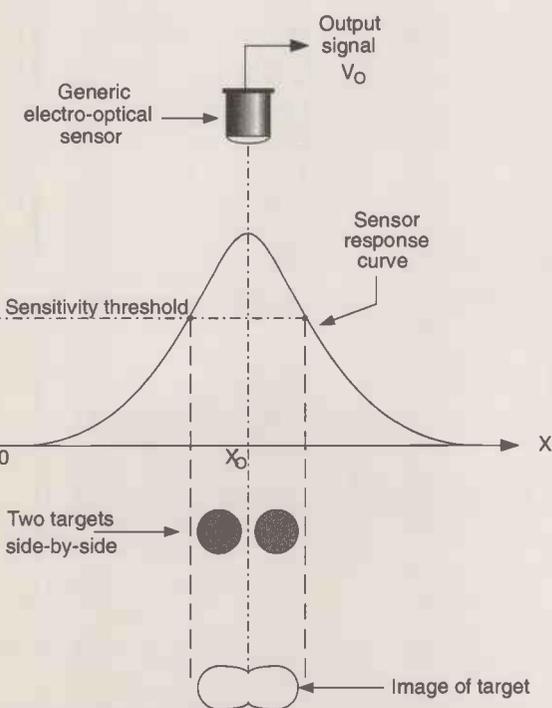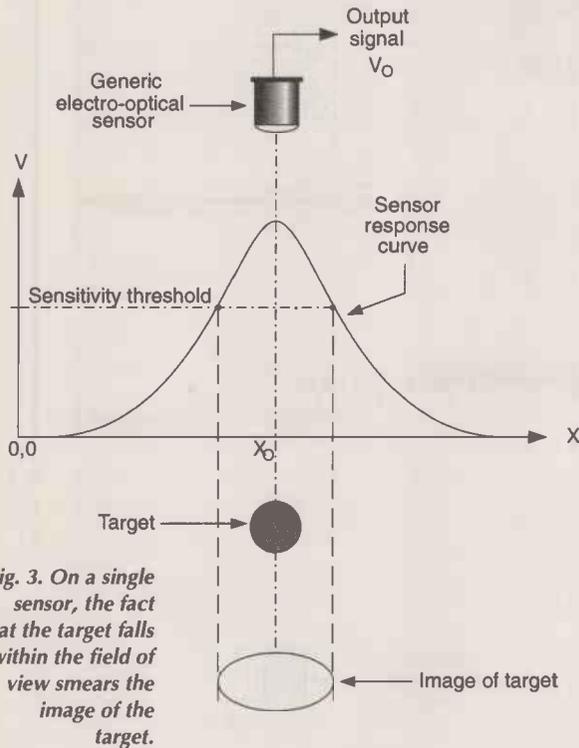

Towards better sensor resolution

Sensor resolution cannot be improved without re-designing the device. In some cases, the laws of physics might prohibit further improvement. But there is something that can be done to correct the problem.

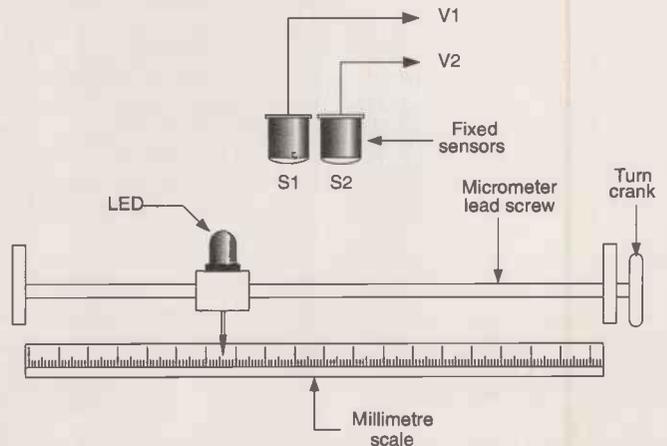
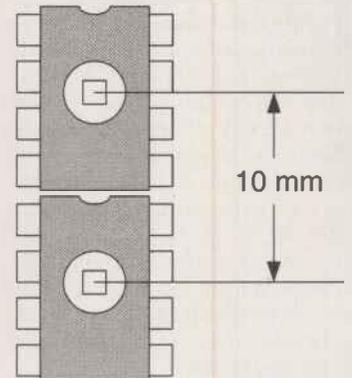


Fig. 5a) Two-sensor test device made by mating a pair of Burr-Brown OPT-101 devices; b) test fixture that allowed the LED target to be translated along the X-axis in front the sensors.

value of the difference at each point along the X-axis you create the resolution-improved signal V_0 . The factor k is a small value constant, that is set to prevent a divide by zero error when $V_1=V_2$, or an extremely high value when V_1 and V_2 are very close in value. The value of k is set to produce a full-scale output when $V_1-V_2=0$.

Initial trials

The two-sensor approach was modelled first in an Excel spreadsheet. For the first attempt a curve similar to those in Figs 1 through 4 was converted to numbers and entered in successive cells of a single column.

Each cell represented another increment along the X-axis, while the value in the cell represented the signal voltage V at that point. When the method was applied, and graphed, there was a tremendous improvement in the resolution of the hypothetical sensor. The time came to 'cut metal' and build a real circuit model.

Figure 5 shows the actual test set-up used to acquire data. Two electro-optical sensors were obtained. The optical sensors were Burr-Brown OPT-101 devices. These sensors are operational amplifiers with a photodiode device built-in to the transparent 8-pin DIP IC package.

The two OPT-101 devices were spaced 10mm apart so that their cones of acceptance overlapped – which is also the minimum possible X-axis separation due to the size of the IC packages. This mounting was convenient because the two devices would fit nicely end-to-end in a single 16-pin DIP socket.

The mid-point between the two OPT-101 devices corresponds to X_0 , while the distance between them corresponds to ΔX ; any particular point along the path between S_1 and S_2 is designated X_i .

The target was a red light emitting diode mounted on a movable stage on a micrometer gear rack device that measured distance of travel in millimetres. The initial position of the LED target was set so that it was outside the field of view of both S_1 and S_2 .

The LED was then advanced 1mm at a time until it had traversed the entire distance from the left-most extent of the field of view of S_1 to the right-most extent of the field of view of S_2 . Output voltages V_1 and V_2 from S_1 and S_2 were measured with a 3¹/₂-digit digital voltmeter at each 1mm interval.

Those data were then entered into an Excel spreadsheet and plotted on a chart. Curves shown in Fig. 6 represent actual results from this experiment, rather than simulated results.

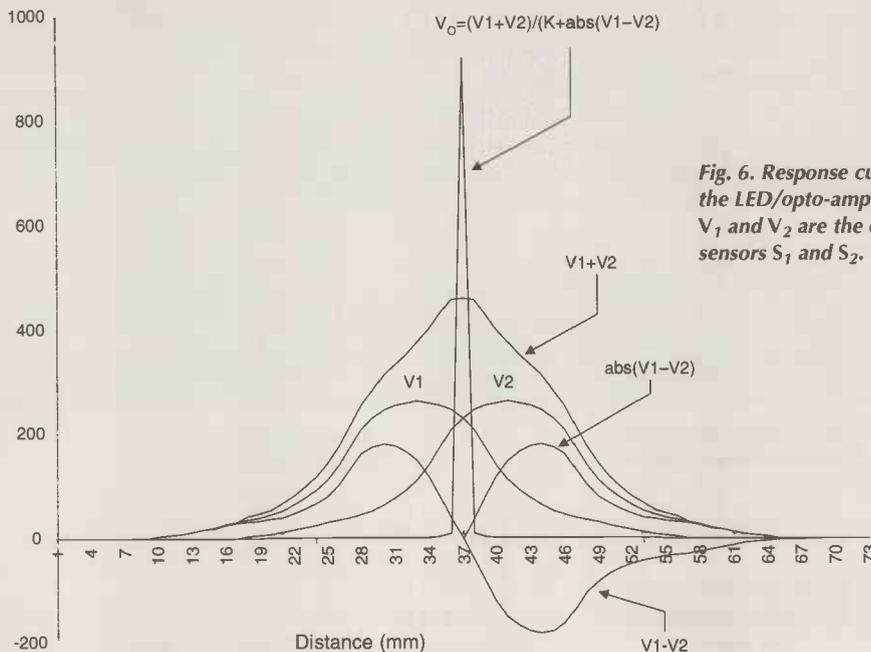


Fig. 6. Response curves of the LED/opto-amplifier trial. V_1 and V_2 are the outputs of sensors S_1 and S_2 .

The experimental and modelled results were the same.

All of the curves are shown in Fig. 6: V_1 , V_2 , V_1+V_2 , V_1-V_2 , $abs(V_1-V_2)$ and the resolution improved V_0 . The V_1 and V_2 curves represent the normal field of view of the OPT-101 devices, and therefore the effective resolution of the devices.

Note how much narrower V_0 is compared with either V_1 or V_2 . This response curve would resolve much finer separations and produce superior images than either S_1 or S_2 alone.

A single-sensor solution

The two-sensor method of sensor resolution improvement produces startling results – but at the cost of two sensors. It is easy to implement in analogue circuitry, and can also be implemented in digital circuitry.

Another approach uses a single sensor and a look-ahead technique to synthesise V_2 . It is easily implemented digitally, but is quite difficult to implement in analogue circuitry.

Assume that the values of V_1 from the sensor are a series V_i in which each value represents the signal amplitude at sequential locations along the X-axis: $V_1 V_2 V_3... V_{ith}$

Each value of V_i represents a value of V_1 in eqn 1 above. The corresponding value of V_2 in eqn 1 is found by taking a subsequent value of V_1 that is displaced a distance N , which is an integer, from V_1 . Thus, in terms of eqn 1, $V_1=V_i$ and $V_2=V_{i+N}$.

Equation 1 can be rewritten to the form:

$$V_0 = \frac{V_i + V_{i+N}}{k + (V_i + V_{i+N})}$$

When the V_1 data from the experiment are plotted, the resultant curves are very similar to those of Fig. 6 and

demonstrate very nearly the same degree of resolution improvement.

I also found that a limited amount of 'tuning' of resolution can be done by selecting values of N . However, with the 1mm spacing used in the experiment, values of N that were greater than 5 showed essentially the same curves.

In both the single-sensor and two-sensor methods there exists the possibility of creating a selectable beam width sensor system. Signal V_0 could be the narrow beam-width signal, V_1+V_2 can be the wide beam-width signal, and V_1 or V_2 can be the medium beam-width signal.

In summary

This sensor resolution improvement method is a variant on the monopulse-resolution improvement, or MRI, method used for many years in radar technology. It appears to have applications in ultrasonic imaging – which resembles radar in basic approach – and in any instrumentation problem where sensor resolution is an issue.


Perhaps one day I will try it on a metal detector and go searching for artifacts on an American Civil War battlefield near my home in Virginia. ■

Further reading

Brown, John M. Brown and Joseph J. Carr, 1997, 'Introduction to Biomedical Equipment Technology – 3rd Edition,' New York: Prentice-Hall.
 Carr, Joseph J., 1992, 'The Art of Science,' San Diego: Hightext Publications, Inc.
 Skolnik, Merrill, 1980, 'Introduction to Radar Systems,' New York: McGraw-Hill.
 Stimson, George W., 1983, 'Introduction to Airborne Radar Systems,' El Segundo, CA: Hughes Aircraft Co.

MARCONI TF 2019A

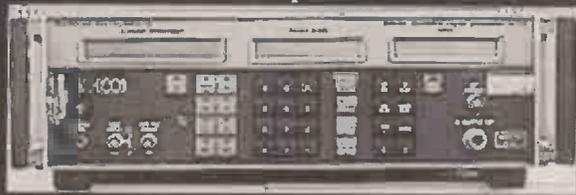Synthesised Signal Generators
80Hz to 1040Mhz AM/FM, Memories, LCD
Complete with lid, plugs and leads
FULLY TESTED and WARRANTED
A REAL Anchor Special ONLY £750



TEK 2445 Scopes

DC-150Mhz 4 Trace/2 Timebase and Cursors
A REAL Anchor Special ONLY
£495



Frequency Counters

Racal Dana 9903/4
7 segment 30Mhz £24
Racal Dana 9918
9 segment 560Mhz £75

Signal Generators

HP 8683A
2.3-6.5 GHz AM/FM
NOW ONLY £499
Hewlett Packard 8640A
500Khz to 520Mhz AM/FM/CW
ONLY £245
Hewlett Packard 8640B
As above but with
Digital Readout
ONLY £595
Rohde and Schwarz APN62
1hz to 260kHz with LCD display £995
Farnell DSG2
Synthesised 0.1mhz to 110Khz £195
Wavetek 155
Programmable VCG 0.01hz to 1Mhz sine,
square, triangle £195
Schlumberger FSD120M
Remote Synthesiser to 120Mhz in 0.01hz
steps £175

Marconi TF2015
10-520Mhz NOW ONLY £95
Marconi TF2171 Synchronizer
for 2015 NOW ONLY £95
BOTH TF2015 and TF2171
ONLY £180

Video Equipment

Panasonic AG6200
VHS ONLY £99
Panasonic AG6810
HiFi Duplication machines
VHS NOW ONLY £99
SONY VO5630
Low Band Umatic ONLY £225
PANASONIC AG6100
VHS Players ONLY £100

TEK 2445

150Mhz Four Trace/2 Time base
with Cursors, etc. Now Only £495

TEK 2445A 150Mhz Four Trace/2 Time bases
with Cursors, etc.
Now Only £995

TEK 2465 300Mhz Four Trace/2 Timebases
Now Only £1250

IWATSU SS-6711 100Mhz
Four Trace Dual Time base
Now Only £345

NICOLET 2090-111
1Mhz Digital Scope, Cursor ctrl
Now Only £150

GOULD OS3600 with
DM3010 DMM fitted, 60Mhz
Dual trace, Dual Timebase
Now Only £350

Oscilloscopes

HP 1741A 100Mhz Storage Dual
Time base only £350
TEK 465B 100Mhz Dual Trace/
Timebase Now Only £295
TEK 465M scope as 465B but built only
for Military. Only £350
TEK 475 200Mhz Dual Trace/Timebase
Now Only £395

THIS MONTH'S SPECIALS

Philips PM3217 Scopes
DC-50Mhz 2 Trace/2 Timebase
A REAL Anchor Special ONLY £275



Gould OS300 Scopes
DC-20Mhz 2 Trace
SPECIAL NOW ONLY £150



Hewlett Packard
8640A Signal Generators
500Khz to 520Mhz AM/M/CW
SPECIAL ONLY £245



Philips PM5519
Colour Pattern Generator
SPECIAL ONLY £125



Racal Dana 1991 60Mhz
NanoSecond Counters with Maths f'ctns, etc
SPECIAL ONLY £295



ANCHOR SUPPLIES LTD

All prices are EX VAT and Carriage

MAIL ORDER A PLEASURE

The Cattle Market Depot, Nottingham NG2 3GY, UK

Tel: (0115) 986 4902 Fax: (0115) 986 4667

Also at Peasehill Road, Ripley, Derby

Miscellaneous

NEOTRONICS DigiFlam850
Portable Flammable Gas Det
C/W Inst/charger
NOW ONLY £145
GIGA Pulse internal counter
2-8Ghz ONLY £150
Flike 80-40K
High Voltage probe for DMM's 40kv. Cased.
NEW £45
Farnell TTS520
Transmitter Test set to 520Mhz
NEW £750
HP8900C
Peak power meter with 84811A sensor and
attenuator £250
Farnell B30/10
Regulated + Stabilised Power supply. 0-30V
@10A £60
Wangel & Golterman DF64
Error Rate Measuring set £195

AVO Model 8 Mk 5/Mk 6
Multimeters . . . THE Standard
ONLY £85

NEW EQUIPMENT

DTA20 Oscilloscope 20Mhz
Twin trace incl probes ONLY £225
DTA40 Oscilloscope 40Mhz
Twin Trace incl probes ONLY £299
DTS40 Oscilloscope 40Mhz
Digital Storage twin channel
Cursors + readouts
Incl. Probes. ONLY £399
AMM255 Automatic Mod Meter
1.5Mhz to 2Ghz, LCD
IEEE488 ONLY £495
SCG50 Synth Clock Gen.
To 50Mhz, LED display
ONLY £125

NEW SCOPE PROBES

X1/X10 switchable to 100Mhz
Complete with adaptors
Limit 2 sets per customer
ONLY £9.95

COMPARE OUR PRICES
WITH THE COMPETITION . . .
SEE HOW MUCH YOU CAN SAVE
AT ANCHOR

Visit our Web Site: www.anchor-supplies.ltd.uk email: sales@anchor-supplies.ltd.uk

CIRCLE NO. 122 ON REPLY CARD

Power amplifier


circuit boards

Professionally designed and manufactured printed circuit boards for Giovanni Stochino's no compromise 100W power amp are available to buy.


These high-quality fibre-glass reinforced circuit boards are designed for Giovanni Stochino's fast, low-distortion 100W power amplifier described in the August 1998 issue. Layout of the double-sided, silk screened and solder masked boards has been verified and approved by Giovanni.

This offer is for the pcbs only. The layout does not accommodate the power supply scheme shown in the article. Note that a copy of the article and a few designers' notes are included with each purchase, but you will need some knowledge of electronics and thermal management in order to successfully implement this design.

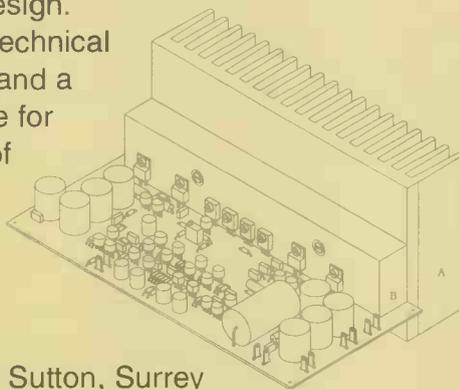You can receive a copy of the technical notes that accompany the pcbs and a copy of Giovanni's original article for £3.50, refundable on purchase of one or more pcbs. Send a postal order or cheque payable to Reed Business Information to 'Board notes,' Electronics World Editorial, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Don't forget to include your address.



£42 per pair
fully inclusive
or £25 each

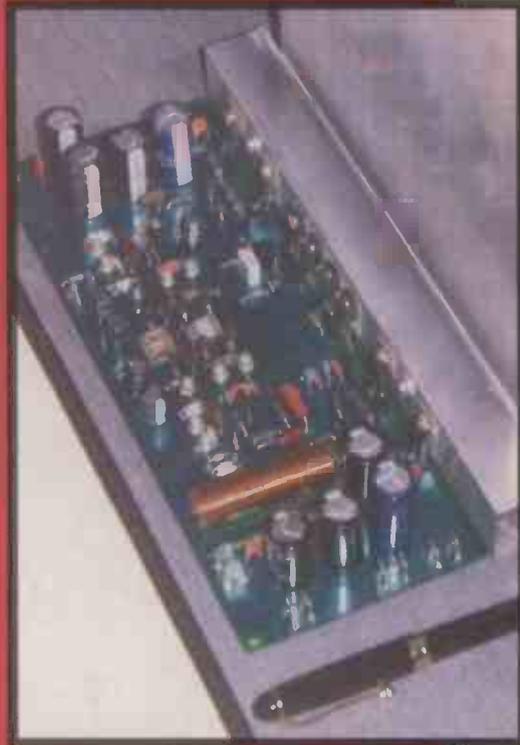

Giovanni's high-performance power amplifier mounted on its heat sink.

Please send me ___ pcbs @ £25 each or £42 a pair.

I enclose my cheque for £ _____

Please debit my credit card for £ _____

Card type MasterCard/Visa.

Card number _____

Expiry date _____ / _____

Signature _____

Name _____

Address _____

Tel _____

Cheques made payable to Reed Business Information.

Post to: PCB Offer, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS. Please allow 28 days for delivery.

Specifications

Power into 8Ω load	100W
Small-signal bandwidth before the output filter	20Hz (-0.1dB), 1.3MHz (-3dB)
Unity gain frequency before the output filter	22MHz
Output noise (BW=80kHz, input terminated with 50Ω)	42μV rms
Measured output offset voltage	+32mV

Distortion performance

V_{out} , pk-pk	1kHz	20kHz
5	0.0030%	0.0043%
10	0.0028%	0.0047%
20	0.0023%	0.0061%
40	0.0028%	0.0110%
80	0.0026%	0.0170%

Slew rate

Positive slew-rate	+320V/μs
Negative slew-rate	-300V/μs

Special Offer

to **ELECTRONICS** readers
WORLD

The **Surface Mount Technology Handbook**

New First Edition, only £50 (normal price £75)

The essential in-depth reference manual for design, process and production engineers seeking practical, cost-effective surface mount solutions.

Whether used as a practical "how-to-do" manual, or in specifying denser and more complex surface mount projects, the Surface Mount Technology Handbook in over 300 pages provides a wealth of high quality reference data covering "state-of-the-art" surface mount processes:

- assembly and technical design issues
- cost-effective design
- processes and process control
- components including fine pitch
- applications and solutions
- the pitfalls and how to avoid them
- trouble-shooting and QA
- where to go to get further advice
- comprehensive sourcing guide for equipment and materials

Order your copy now

Benefit from the most comprehensive surface mount reference available and save £25.

Contents *in Brief;*

- | | | |
|---|---|---|
| Chapter 1 Introduction to Surface Mount Technology | Chapter 4 Paste/Adhesive Application | Chapter 8 Equipment Selection criteria |
| Chapter 2 Interconnecting Media | Chapter 5 Component Placement | Chapter 9 Glossary of Terms |
| Chapter 3 Surface Mount Components | Chapter 6 Solder Reflow | Chapter 10 Buyers Guide |
| | Chapter 7 Cleaning | |

307 Pages with 10 Chapters providing in-depth coverage of all aspects of the process.

No risk 28 day Refund Guarantee - if the Surface Mount Technology Handbook does not meet your expectations, simply return the book to us within 28 days for a full refund.



in association with



Discount Order *Form*

Special reader price of £50.00 (normal price £75) plus postage and packing of £5 per copy (UK/Europe)

Yes, please send me copy/copies of the Surface Mount Technology Handbook -- ISBN 1 90158 842 4

Special Price £50 each copy total **Add postage & packing of** **Total**

European Customers please state your VAT number

Method of payment - Payment enclosed (cheques payable to Reed Electronics Research). Please charge my credit card: Mastercard/VISA/AMEX

Cardholder Name Card Number Expiry Date

Delivery


Name Job Title Organisation

Address

Town/County Postcode Country

Tel Fax Email

Signature Date

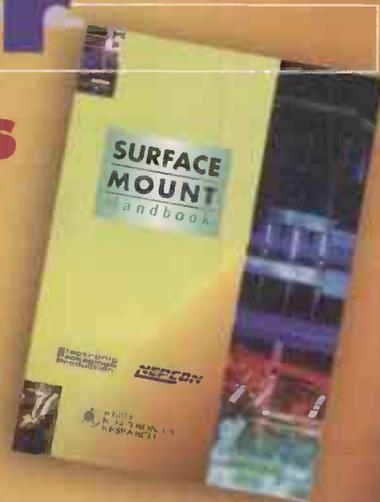

Improving VHF Yagis

One of the reasons why building good antennas is a challenge is that key parameters are often incompatible. This note examines the incompatibility between very efficient transmission lines, which have a high characteristic impedance, and typical Yagis, which have low input impedance.

Antenna optimisation often ignores the transmission line. The line is selected only after the Yagi design is complete, and it is almost always coaxial. The antenna/transmission line system is then made to work by adding a matching network.

But this approach is not necessarily the best. Designing the antenna and transmission line together may provide better overall performance, a point which is illustrated by the 12-element Yagi discussed below.

Feed-system-loss at VHF

The problem at VHF is that coaxial cable loss increases dramatically with frequency, often robbing the antenna system of its full potential.

On 2 metres, for example, the matched-line attenuation of widely used RG-8 foam-dielectric coaxial cable is about 2.1dB/100 feet¹, which is quite substantial. And this is the minimum value, because attenuation increases as SWR goes up – which also reduces system bandwidth.

Another source of attenuation is the required matching network and balun. Even the simplest network introduces some loss in its electronic components and coax connectors, and these losses are usually much higher at VHF than at lower frequencies.

At VHF, where fractions of a decibel can make a difference, using a transmission line with the lowest possible loss is obviously very important. The best transmission line is air-insulated open wire (not 'window' line).

An open wire line made with #12 AWG conductors has an attenuation of only 0.25 dB/100 feet on 2 metres⁽¹⁾. For comparison, 200 feet of open wire line delivers 89% of the input power to the antenna, while the same length of RG-8 delivers only 38%.

But there are problems with open wire line. Practical conductor spacings result in high characteristic impedance, which is difficult to match to a low impedance Yagi. Table 1 shows the centre-to-centre conductor spacing to achieve different line impedance with common wire sizes. The impedance is computed from the formula $Z_0=276\log(2S/d)$, where S is the centre-to-centre spacing and d is the conductor diameter, both in the same units.²

High-impedance Yagis

The easiest way to take advantage of the extremely low attenuation of open



With the aid of a 300Ω 12-element design example, Richard Formato explains how high-impedance Yagis improve VHF antenna system performance, and why a 300Ω pair performs better than coaxial cable.

wire line is to design a good Yagi with a *high* input impedance. One approach is to use a half-wave folded dipole as the driven element⁽³⁾. Another is to increase the input impedance of the usual centre-fed linear dipole driven element (DE) by proper placement of the array's parasitic elements. The feasibility of this design approach will be demonstrated by a 12-element Yagi that provides a nearly perfect match to 300-ohm open wire line and excellent overall performance. An added advantage is that the antenna and transmission line are both balanced, so that the balun connecting the unbalanced transmitter output to the line can be placed at the transmitter instead of at the antenna.

Free modelling software – YGO2

The high impedance array was

designed using *Yagi Genetic Optimizer* version 2, which is a freeware program available on the web.⁴ YGO2 models Yagis using NEC-2D (Numerical Electromagnetics Code, Ver. 2, Double Precision). This is also available on the web⁴ or directly from ACES.⁵ Essential data from the YGO2 config-

uration file, and the NEC-2D input file for the final optimised array, are in the panel entitled 'Yagi modelling data'.

The optimisation was done iteratively. The initial runs optimised only the input impedance by setting the coefficients *d*, *e* and *f* to zero, and by assigning a low value to coefficient *a*.

one frequency, i.e. 146MHz. The element diameter of 0.0122 waves is equal to *l*_{in} (25.4mm) divided by the wavelength at 144MHz (299.8/frequency in megahertz).

Somewhat fat elements were chosen to broaden the Yagi's response. Smaller diameter elements – but not too small – should provide more gain at the expense of bandwidth, but this was not investigated in detail.

A 12-element, 300Ω Yagi

The geometry of the YGO2-optimised Yagi appears in **Table 2**. I refer to this antenna as the 'high-Z' Yagi because it matches 300Ω line. All dimensions are in wavelengths at the design frequency *F*₀.

Length is the end-to-end element length. *Spacing* is the separation along the boom from the previous element. *Position* is the distance along the boom from element No 1 – the reflector. Element No 2 (DE) is driven at its centre – i.e. it's a centre-fed linear dipole. All elements have the same diameter of 0.0122 wave at *F*₀.

Figure 1 shows the YGO2 output screen, which plots the E-plane azimuthal radiation pattern and provides a scale representation of the array. The display is annotated with key performance data. The radiation pattern is very clean, and its structure is typical of well-designed Yagis.

One interesting aspect of this Yagi is its unusual geometry. Unlike 'standard' designs having progressively shorter directors with increasing spacing away from the DE, the element lengths do not follow any pattern. Some of them are quite out of the ordinary.

The DE, for example, is the second-longest element at 0.5992 wave. The reflector, REF, is much shorter, at 0.4839 wave, and the longest element is element No 6, D4, which is 0.6 wave. Usually, the reflector is the longest element, DE is less than half-wave and the directors become progressively shorter.

Not quite a director

Another unusual feature is the position of director No 1, or D1, which is very close to DE, separated only by 0.05 of a wave. This director appears primarily to function as an impedance matching parasitic, rather than as a true director. Even though it contains 12 elements, this Yagi looks more like an 11-element array.

The similarity to an 11-element array is even more apparent when the 12-element high-Z Yagi is com-

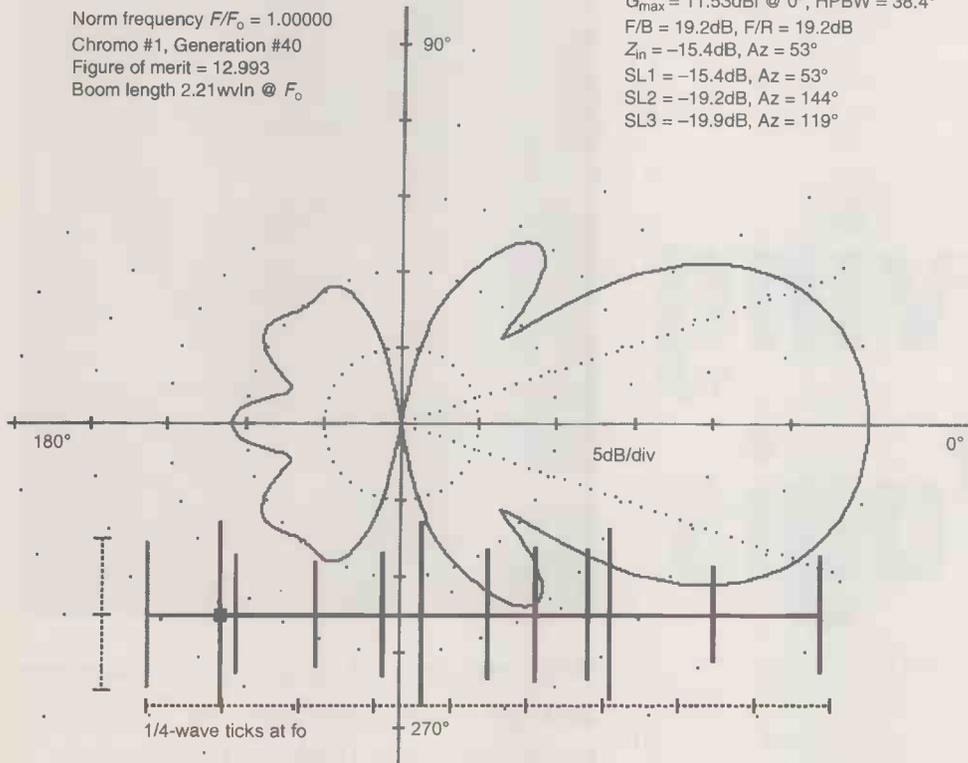


Fig. 1. Azimuthal pattern for the genetically-optimised 12-element Yagi using the NEC file YGO_1.40 listed later.

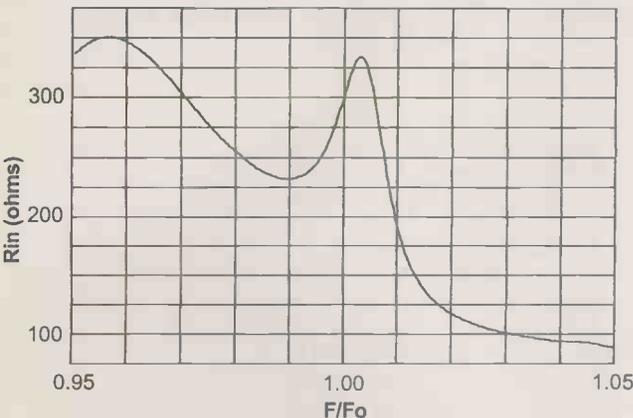


Fig. 2. Input resistance of the 12-element high-impedance Yagi around the centre normalised frequency.

Once a geometry was evolved that was a good match to 300Ω, the corresponding chromosome was used to seed subsequent optimisation runs in which coefficients *a*, *d*, and *e* were gradually increased (*f* was always zero).

This process was repeated until the desired balance between *Z*_{in}, gain, FB and FR was achieved. All runs were at

Table 2. High-Z Yagi geometry. Dimensions in wavelengths at *F*₀. Note that all elements are 0.0122 wave diameter.

El #	Length	Spacing	Position
1 (REF)	0.4839	0.0000	0.0000
2 (DE)	0.5992	0.2397	0.2397
3 (D1)	0.3865	0.0500	0.2897
4 (D2)	0.3453	0.2635	0.5532
5 (D3)	0.4094	0.2229	0.7761
6 (D4)	0.6000	0.1224	0.8985
7 (D5)	0.4306	0.2212	1.1197
8 (D6)	0.4412	0.1559	1.2756
9 (D7)	0.4271	0.1700	1.4456
10 (D8)	0.5647	0.0729	1.5185
11 (D9)	0.3141	0.3482	1.8667
12 (D10)	0.3824	0.3447	2.2114

Table 1. Conductor spacing in inches for various wires sizes and characteristic impedances.

AWG	<i>Z</i> ₀ (Ω)			
	300	350	400	450
10	0.622	0.945	1.434	2.176
12	0.494	0.749	1.137	1.725
14	0.392	0.594	0.902	1.369

pared to the 144MHz family of designs in The ARRL Antenna Book.⁶

The ARRL 11-element array has a boom length of 2.2 waves and a gain of 14.15dBi, i.e. 12dBd. It has a front-to-back ratio, shortened to FB, of 19dB, an input resistance of 38Ω, and an unspecified input reactance. This is presumably tuned out by a matching network. Because this array is intended to operate with a low-impedance transmission line, I will refer to it as the 'low-Z Yagi'.

The high-Z array in Fig. 1 is the same length as the low-Z antenna (2.21 waves), and has a gain of 11.53 dBi, and FB and front-to-rear (FR) ratios of 19.2dB. The high-Z array is essentially resonant at F_o ($Z_{in}=299.3+j2.9\Omega$), which provides a nearly perfect SWR of 1.01 on 300Ω open-wire line with no matching of any kind. In contrast, the low-Z Yagi's SWR relative to 50Ω is 1.32 without matching, assuming the antenna is resonant – almost certainly not the case.

Relative performance

The performance of the high and low-Z arrays is similar in many respects, but there are differences. It appears that the extra element in the high-Z Yagi increases the DE input impedance while contributing little to the gain. In fact, taken together, DE and D1 look much like a folded dipole.

It is interesting that YGO2's solution places D1 as close as possible to DE – at 0.05 waves. Had the minimum spacing in YGO2.CFG been lower, say 0.025 wave, YGO2 might have placed D1 even closer, which would make DE/D1 look even more like a folded dipole. There's more on YGO.CFG in the panel entitled 'Yagi modelling data'.

Another (and more important) difference is that the high-Z Yagi's gain is lower than the low-Z's by 2.62dB. But, while this gain reduction would be significant if realised, it will not occur in practice because of the different levels of transmission line loss.

If the high and low-Z systems are

compared, taking into account line loss, then the high-Z Yagi may well be the better antenna. It provides more overall gain than the low-Z array for any transmission line longer than 142 feet – comparing #12 AWG open wire and foam-dielectric RG-8. This result excludes matching network and connector losses. These are likely to be much higher for the coaxial cable than for the open-wire line, which again gives the high-Z Yagi an edge.

Another advantage of the high-Z design is that open-wire line is easily coupled to an unbalanced-transmitter output. Simple, very low loss air-core inductive circuits that act as balun and impedance matching transformer are readily available.⁷ This circuit can be located at the transmitter, which is not possible with coaxial cable because the balun must then be at the antenna input.

Placing the network in the shack reduces the weather-related losses and maintenance that are inevitable with devices mounted outdoors.

Open-wire line is also favoured because of its effect on signal-to-noise ratio. In a receiver-noise limited system, SNR is reduced by the amount of transmission line attenuation.

At VHF, the extremely low attenuation of open wire line is advantageous both for receiving and transmitting. Open-wire line provides better SNR than coax, and it delivers more power to the antenna.

Input impedance and SWR


Figures 2-7 provide detailed performance data for the high-Z Yagi computed by NEC-2D. On each plot, the abscissa is the normalised frequency, F/F_o , where F_o is the design frequency at which the array dimensions are computed.

For convenience, the ratio F/F_o is denoted by a lower case, italic f . Each parameter is plotted over a 10% bandwidth ($0.95 \leq f \leq 1.05$).


Figure 2 shows the input resistance. The design value of 300Ω is achieved at three frequencies, $f=0.97, 1.00,$ and

1.006. Maximum resistance is 350Ω at $f=0.957$, with a secondary peak of about 330Ω at $f=1.003$. The resistance is between 200 and 350Ω for frequencies from 0.95 to just below 1.01.


Input reactance is plotted in Fig. 3.

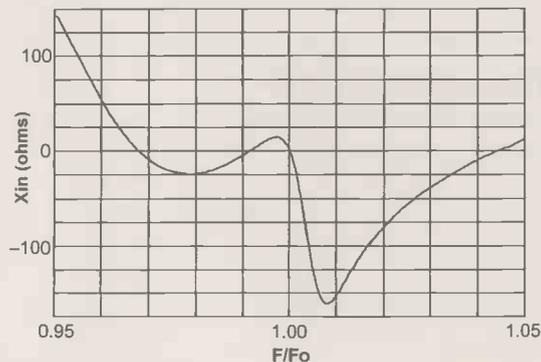


Input reactance.

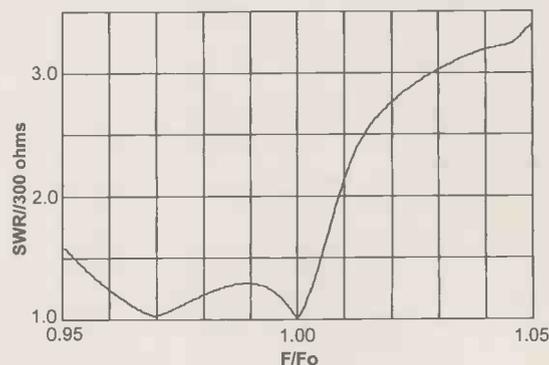

Standing-wave ratio.

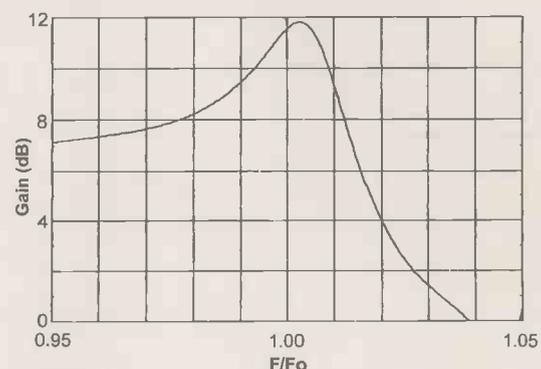


Forward gain

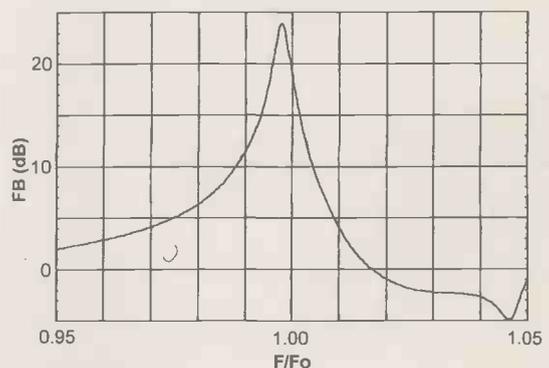

Front-to-back ratio.

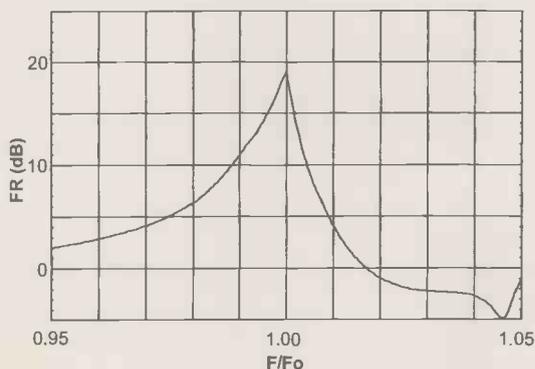Figs 3-7. Performance curves for the 12-element Yagi.



Four resonances, i.e. where $X_{in}=0$, occur at $f=0.968, 0.992, 1.00, \text{ and } 1.044$. The maximum reactance of about $+140\Omega$ (inductive) occurs at $f=0.95$, while the minimum of -161Ω (capacitive) is at $f=1.008$.

Reactance is less than 10% of the desired 300Ω input resistance from

$f=0.963$ to 1.002 (3.9%). For practical purposes, the high-Z Yagi may be considered resonant over this entire range of frequencies.

The most important antenna impedance parameter is SWR, which is plotted in Fig. 4. At the lower band edge, the SWR is just over 1.5. It is

below 1.5 from $f=0.953$ to 1.005 , yielding a 1.5:1 SWR bandwidth of 5.2%. The 2:1 SWR bandwidth is more than 5.9%, which is quite good.

Gain and FB/FR Ratios

Forward gain in dBi – i.e. decibels relative to an isotropic radiator – appears

Yagi modelling data

Essential Data from File YGO2.CFG

Name of NEC executable file NEC2D100.EXE
 # NEC input files/gen in output 5
 starting with generation number 20

Number of Elements in Array 12
 Number of Segments per Element 7
 Feed System Zo 300 ohms resistive
 Assume Feed Reactance Tuned Out? NO

Population Size 10 (# chromosomes)
 Max # Generations 1
 Save Percentage 2.0 (% best chromos/gen saved)
 Crossover Probability 0.8000
 Mutation Probability 0.0200
 Max Mutation Rate 2 bits/chromosome

Selection method # 1
 (1-binary tournament, 2-proportionate)
 Minimum Fitness [0-1] 0.5 (proportionate only)

FoM Terminology

Gfwd Forward Gain (dBi)
 FB Front-to-Back Ratio (dB)
 FR Front-to-Rear Ratio (dB)
 Rin Feed Point Input Resistance, ohms
 Xin Feed Point Input Reactance, ohms
 MaxSLL Maximum Sidelobe Level (dB/Gfwd)
 ^ Exponentiation
 * Multiplication
 / Division
 ABS Absolute Value

Figure-of-Merit (averaged over all frequencies):

$$FoM = \frac{a * Gfwd - b * ABS(Zo - Rin) - c * ABS(Xin) + d * FB + e * FR - f * MaxSLL}{a + b + c + d + e + f}$$

FREQUENCY TABLE

FREQUENCIES USED - 1

Freq #	Freq(MHz)	DE	a	b	c	d	e	f
1	146.00	2	260.0	4.0	6.0	1.0	85.0	0.0
2	144.20	2	40.0	2.0	3.0	0.0	0.0	0.0
3	144.30	2	40.0	2.0	3.0	0.0	0.0	0.0
4	144.40	2	40.0	2.0	3.0	0.0	0.0	0.0
5	144.50	2	40.0	2.0	3.0	0.0	0.0	0.0
6	144.60	2	40.0	2.0	3.0	0.0	0.0	0.0
7	144.70	2	40.0	2.0	3.0	0.0	0.0	0.0
8	144.80	2	40.0	2.0	3.0	0.0	0.0	0.0
9	144.90	2	40.0	2.0	3.0	0.0	0.0	0.0
10	145.00	2	40.0	2.0	3.0	0.0	0.0	0.0
11	145.10	2	40.0	2.0	3.0	0.0	0.0	0.0
12	145.20	2	40.0	2.0	3.0	0.0	0.0	0.0
13	145.30	2	40.0	2.0	3.0	0.0	0.0	0.0
14	145.40	2	40.0	2.0	3.0	0.0	0.0	0.0
15	145.50	2	40.0	2.0	3.0	0.0	0.0	0.0

Target FoM - 9999 (not normalised)

Crossover allowed only at gene boundary? YES
 Print Percent - 20 (% chromos/gen printed in output file)

Use Seed Chromosome? YES

Seed Chromo:
 011000010000000000000000010110110000000000000011111100000000
 000000000010000100000000000001001101110100000000010001101111
 1111000000001001010011101100000000010000110000111100000000000
 111100001101100000000001000101000011100000000101000000110000
 000000001001010101000100000000011100101

Print Chromo Sequences in YGO.DAT? NO

GENE TABLE

Gene #	Name	Length (bits)	Min (wvl/n)	Max (wvl/n)
1,	"Refl_Length "	8,	0.3000,	0.6500
2,	"Refl_Radius "	8,	0.00610,	0.00610
3,	"Refl_Spacing "	8,	0.0000,	0.0000
4,	"DE_Length "	8,	0.3000,	0.6500
5,	"DE_Radius "	8,	0.00610,	0.00610
6,	"DE_Spacing "	8,	0.0500,	0.428
7,	"D1_Length "	8,	0.3000,	0.6500
8,	"D1_Radius "	8,	0.00610,	0.00610
9,	"D1_Spacing "	8,	0.0500,	0.428
10,	"D2_Length "	8,	0.3000,	0.6500
11,	"D2_Radius "	8,	0.00610,	0.00610
12,	"D2_Spacing "	8,	0.0500,	0.428
13,	"D3_Length "	8,	0.3000,	0.6000
14,	"D3_Radius "	8,	0.00610,	0.00610
15,	"D3_Spacing "	8,	0.0500,	0.500
16,	"D4_Length "	8,	0.3000,	0.6000
17,	"D4_Radius "	8,	0.00610,	0.00610
18,	"D4_Spacing "	8,	0.0500,	0.500
19,	"D5_Length "	8,	0.3000,	0.6000
20,	"D5_Radius "	8,	0.00610,	0.00610
21,	"D5_Spacing "	8,	0.0500,	0.500
22,	"D6_Length "	8,	0.3000,	0.6000
23,	"D6_Radius "	8,	0.00610,	0.00610
24,	"D6_Spacing "	8,	0.0500,	0.500
25,	"D7_Length "	8,	0.3000,	0.6000
26,	"D7_Radius "	8,	0.00610,	0.00610
27,	"D7_Spacing "	8,	0.0500,	0.500
28,	"D8_Length "	8,	0.3000,	0.6000
29,	"D8_Radius "	8,	0.00610,	0.00610
30,	"D8_Spacing "	8,	0.0500,	0.500
31,	"D9_Length "	8,	0.3000,	0.6000
32,	"D9_Radius "	8,	0.00610,	0.00610
33,	"D9_Spacing "	8,	0.0500,	0.500
34,	"D10_Length "	8,	0.3000,	0.6000
35,	"D10_Radius "	8,	0.00610,	0.00610
36,	"D10_Spacing "	8,	0.0500,	0.500

End of Gene Table

***** End of File YGO2.CFG *****

NEC-2D Input file for YGO2-optimised array

CM NEC File: YGO_1.40 (Run ID: 11-16-1998, 23:40:45)
 CM Chromosome #1, Generation #40
 CM Figure-of-Merit = 12.993
 CM Feed System Zo = 300 ohms resistive
 CE
 GW 1,7,0,,241961,0,,0,-,241961,0,,0061
 GW 2,7,,239741,,299608,0,,239741,-,299608,0,,0061
 GW 3,7,,289741,,1932355,0,,289741,-,1932355,0,,0061
 GW 4,7,,5532,,172647,0,,5532,-,172647,0,,0061
 GW 5,7,,776141,,204706,0,,776141,-,204706,0,,0061
 GW 6,7,,898494,,3,0,,898494,-,3,0,,0061
 GW 7,7,1.11967,,215294,0,1.11967,-,215294,0,,0061
 GW 8,7,1.275552,,220588,0,1.275552,-,220588,0,,0061
 GW 9,7,1.445552,,2135295,0,1.445552,-,2135295,0,,0061
 GW 10,7,1.518493,,282353,0,1.518493,-,282353,0,,0061
 GW 11,7,1.866728,,157059,0,1.866728,-,157059,0,,0061
 GW 12,7,2.211434,,1911765,0,2.211434,-,1911765,0,,0061
 GE
 GN-1
 FR 0,1,0,0,299.8,0.
 EX 0,2,4,0,1,0.
 RP 0,1,181,1001,90,,0,,0,,1,,10000.
 XQ
 EN

in Fig. 5. Maximum gain is 11.8dBi at $f=1.003$. The gain is above 10dBi from $f=0.993$ to 1.009 – a 10dBi gain bandwidth of 1.6%. The half-power –3dB frequencies are 0.986 and 1.011, yielding a –3 dB bandwidth of 2.5%.

The FB ratio in Fig. 6 peaks at 23.9dB at $f=0.998$. FB is above 20dB from $f=0.996$ to 1.00 (0.4%), above 15dB from 0.993 to 1.002 (0.9%), and greater than 10dB from 0.988 to 1.004 (1.6%).

The FR in Fig. 7 shows similar behaviour, but its peak value is lower. Maximum FR is 19.2dB at $f=1.00$. It is above 15dB from $f=0.996$ to 1.002 (0.6%), and greater than 10dB from 0.988 to 1.004 (1.6%).

In summary

The high-Z Yagi is a high-performance antenna. It directly matches extremely low loss, balanced 300Ω open wire line. As a system, this array fed by open wire line outperforms an optimised 11-element array

of the same boom length fed by RG-8 coaxial cable, as long as the transmission line is longer than 142 feet – ignoring matching network and balun losses.

The 12-element high-Z system provides more overall gain and better SNR. If the coaxial matching network/balun has higher losses than the open wire network – which is very likely – the high-Z Yagi provides better performance even for lines shorter than 142 feet.

This design example shows that there are compelling reasons for designing high-Z Yagis to operate directly with high impedance open wire lines. The resulting antenna system can provide excellent performance which may well exceed that of more conventional designs.

High-Z Yagis merit serious consideration by any amateur who is concerned about optimising antenna system performance – especially at VHF where small differences are significant. ■

References

1. 'The ARRL Antenna Book,' 17th ed., R. Dean Straw, editor, American Radio Relay League, Inc., Newington, CT 06111, USA, 1994, Fig. 22, p. 24-16.
2. *ibid.*, Eq. (20), p. 24-14.
3. 'Antennas,' 2nd ed., John D. Kraus, McGraw-Hill Inc., New York, 1988, p. 483.
4. Ray Anderson, WB6TPU's, 'NEC Archive' website, URL: <http://www.qsl.net/wb6tpu>.
5. Applied Computational Electromagnetics Society (ACES) Attn: Dr Richard W. Adler, ACES Executive Officer, ECE Dept., Code ECAB, Naval Postgraduate School, 833 Dyer Road, Room 437, Monterey, CA 93943-5121 USA.
6. 'The ARRL Antenna Book,' 17th ed., R. Dean Straw, editor, American Radio Relay League, Inc., Newington, CT 06111, USA, 1994, Table 11, p. 18-25.
7. *ibid.*, Figs. 2(A), 2(C), p. 25-3.

TELFORD ELECTRONICS

Old Officers Mess, Hoo Farm, Humbers Lane
Horton, Telford, Shropshire TF6 6DJ, UK
Phone: (00 44) 01952 605451 Fax: (00 44) 01952 677978
e-mail: telfordelectronics@telford2.demon.co.uk
Web: <http://www.telford-electronics.com>
Carriage: £10+VAT @ 17.5% to be added to all UK orders
Overseas orders welcome – Please call

ALL OUR EQUIPMENT HAS A 30 DAY GUARANTEE (EXCEPT CLEARANCE ITEMS WHICH ARE SOLD AS-IS)

DATA/TELECOMS

Anritsu MS334A PCM Error Detector	£120.00
BT (Fulcrum) T1020 Network Transmission Performance Analyzer	£500.00
Cushman CE24 FX Selection Level Meter	£400.00
Datalog DL1000 Programmable Transient Recorder	£250.00
GM Elm EPR31 PCM Signalling Recorder	£5,000.00
HP3497A Data/Acquisition Control Unit	£400.00
HP3708 Telephone Line Analyzer	£200.00
HP3764A Digital Transmission Analyzer	£3,200.00
HP3765A Error Detector	£800.00
HP3762A Data Generator	£350.00
HP3720A HP-IB Extender	£300.00
HP37201A HP-IB Extender	£300.00
HP3586B Selective Meter	EPOA
HP3782A Error Detector	£500.00
HP3336A Synthesised Level Generator	£1,300.00
HP1331D Logic Analyzer	£550.00
HP1350A Graphics Translator	£200.00
HP3717A 70MHz Modulator/Demodulator	EPOA
HP8954A Transceiver Interface	£600.00
H3780A Pattern Generator/Error Detector	£1,100.00
HP4355A Transmission Tester	£1,100.00
HP4984A In-Service Transmission Impairment Measuring Set	EPOA
HP5005B Signature Tester	£950.00
HP5006A Signature Analyzer	£50.00
HP6942A Multi-programmer	£200.00
HP8170A Logic Pattern Generator	£500.00
HP3781A Pattern Generator	£500.00
Iwatsu DM2350 Digital Memory 10 bit 20ns	£400.00
Marconi 2830 Multiplex Tester	£200.00
Marconi 2829 Digital Analyzer	£200.00
Marconi 2831 Channel Access Switch	£200.00
Marconi OA2805 PCM Regenerator Test Set	£250.00
Marconi 2019C Noise Generator – Many filters available	£250.00
Marconi 2092C Noise Receiver	£250.00
Marconi 2808Z Pattern Generator and SLMs	£200.00
Marconi 2807A PCM Multiplex Tester	£200.00
Marconi 2828A Digital Simulator	£200.00

MICROWAVE

Digital Microwave Transmitter/Receiver 12GHz	£1,200.00
HP3424A 18GHz Frequency Counter	£800.00
HP8405 Vector Voltmeter	£250.00
HP8502A Transmission/Reflection Test Set 500KHz-1.3GHz	£200.00
HP8502B Transmission/Reflection Test Set 500KHz-1.3GHz	£750.00
HP8743B Reflection Transmission Test Unit 2-12.4GHz	£600.00
HP11720A Pulse Modulator 2-18GHz	£720.00

HP11722A Sensor Module	£600.00
HP11691D Directional Coupler	£600.00
HP11692D Directional Coupler	£700.00
HP3350 120dB Attenuator DC-1GHz	£300.00
HP4111 20GHz S/S Test Set	£1,750.00
HP H752A Directional Coupler 3dB	£150.00
HP X382A Variable Attenuator 0-50dB 8.2-12.4GHz	£120.00
HP33304A Programmable Attenuator 18GHz 0-11dB	£175.00
HP33305A Programmable Attenuator 18GHz 0-110dB	£175.00
HP33320A Attenuator 11dB	£250.00
HP33320B Attenuator 21dB	£250.00
HP33322A Attenuator 120dB	£250.00
HP352B Frequency Meter	£200.00
HP3536A Frequency Meter 3.7-12.4GHz	£200.00
HP5411A 2GHz S/S Test Set	£560.00
JFW Stepped Attenuator 0.9dB in 2dB steps DC-2GHz	£65.00
JFW Stepped Attenuator 0.10dB in 1dB steps DC-2GHz	£65.00
Mauzy Microwave Sliding Termination up to 20GHz	£300.00
Semi Rigid UT114A Co-Axial Cable 0-20GHz 3 metre length	£10.00

MISCELLANEOUS

Anritsu MS55A2 Radio Communications Analyzer 25MHz-1GHz	£1,200.00
Anritsu MS62D Spectrum Analyzer and Tracking Generator	£1,900.00
Avo Pat Tester	£300.00
Five 164 Multi-Function Counter 160MHz	£600.00
Fluke 6305 Programmable Automatic RCL Meter	£1,600.00
Fluke 96 ScopeMeter 50MHz (AS NEW)	£500.00
Fluke 98 Series 2 Automotive Scope Meter/Lab Scope	£700.00
Gltronics 8542 Power Meter & Sensor	EPOA
HP 1175A AM/FM Test Source	£650.00
HP 1650B Logic Analyzer	£1,600.00
HP 3326A Two Channel Synthesiser	£5,000.00
HP 3577A & 35677A Network Analyzer	£5,000.00
HP 3585B Spectrum Analyzer 20Hz-40MHz	£8,000.00
HP 4193A Vector Impedance Meter	£5,000.00
HP 436A Power Meter & Sensor	£300.00
HP 8511D 2GS/s Digitizing Oscilloscope	£4,500.00
HP 8111A 20MHz Programmable Pulse Generator	£1,200.00
HP 8447 Power Amplifier	£600.00
HP 8560A Tracking Generator	EPOA
HP 8568B High Performance Spectrum Analyzer	£6,000.00
HP 8591E Spectrum Analyzer opts. 004, 021, 101, 105, 110	£4,000.00
HP 8591F Spectrum Analyzer	£4,000.00
HP 8571B Synthesised Signal Generator 2-18GHz	£4,850.00
HP 8756A Scaler/Network Analyzer	£950.00
IFR A7550 1GHz Portable Spectrum Analyzer from	£1,500.00
Marconi 2022D 1GHz Signal Generator	£1,650.00

Philips PM5766B Pulse Generator 1Hz-125MHz	£1,250.00
Quartzlock 2A Off Air Frequency Standard 1, 5 & 10MHz	£275.00
R&S AFG Function Generator 20MHz	£2,000.00
R&S SMPD Signal Generator 5KHz-2750MHz	£3,750.00
R&S ZN096 Network Analyzer, Opt. B2, B5, B7	£4,000.00
Smith Weyers ART775 Portable Cellular Tester	£150.00
Tektronix 495P Programmable Spectrum Analyzer	£3,000.00
Tektronix 71047A29/7910 Mainframe/Amplifier	£2,500.00
Timebase	£2,500.00
Tektronix PG506 Time Mark Generator	£500.00
Wayne Kerr 3245 Precision Inductance Analyzer	£3,000.00
Wayne Kerr 4225 RCL Bridge	£400.00
Wayne Kerr AMM2000Z Automatic Modulation Meter	£1,100.00

SIGNAL GENERATORS

Adret 7100B 300KHz-650MHz	£700.00
Cushman CE12 Two Tone Generator	£150.00
Farnell DSG2 0.1MHz-110KHz Synthesized	£185.00
Flann 4311A 12-18GHz	£750.00
Fluke 6010A 10Hz-11MHz Synthesized	£150.00
HP11710B Down Converter (HP8640B)	£275.00
HP214B Pulse Generator 100V 2A	£1,200.00
HP3255A 1Hz-21MHz Synthesized	£1,250.00
HP4204A 10Hz-21MHz Oscillator	£125.00
HP654A 10MHz Test Oscillator	£225.00
HP8005B 0.3Hz-10MHz	£300.00
HP8008A 10Hz-200MHz	£450.00
HP8018A 1Hz-50MHz Pulse	£450.00
HP8165A Programmable Signal Source	£1,200.00
HP8620C/86222B 0.01-2.4GHz Sweeper	£1,200.00
HP8642M 0.1-2100MHz	£12,500.00
HP8657A 0.1-1040MHz	£2,800.00
HP8684B 5.4-12.5GHz	£1,950.00
Marconi 2019A 80KHz-1040MHz	£1,000.00
Marconi 6057 5.5-8.5GHz Signal Source	£200.00
Marconi 6059A 12-18GHz Signal Source	£200.00
Racal 9053 Two Tone	£120.00
Systron Donne 1702 Audio-1GHz	£600.00
Tektronix 504 0.001-240MHz	£350.00
Tektronix P3501A 2MHz Function	£250.00
Wavetek 1080 1-1000MHz Sweeper	£800.00
Wavetek 157 Programmable generator	£150.00
Wavetek 159 Waveform generator 1Hz-3MHz	£300.00
Wavetek 171 Synthesizer/Function	£400.00
Wavetek 185 Sweeper/Function 0-5MHz	£350.00
Wavetek 2001 1-1400MHz	£600.00
Wavetek 907A 7-12.4GHz	£900.00
Systron Donne 1720 50MHz-18GHz Signal Source	£2,000.00
Marconi 20152017 10-520MHz	£200.00
HP 8091A/8092A/8093A (2) 1 GHz Pulse Generator	£650.00

SIGNAL ANALYZERS

Adventest TR4132 16GHz Spectrum Analyzer	£1,200.00
B&K 2636 Measuring Amplifier	£2,500.00
B&K 5935 Dual Microphone Supply	£650.00
B&K 2033 Signal Analyzer	£2,000.00
HP8930B Audio Analyzer	£2,500.00
HP8708A Noise & Interference Test Set	EPOA
HP3561A Dynamics Signal Analyzer	£4,000.00
HP3580A 25KHz Spectrum Analyzer	£600.00
HP3334A Distortion Measuring Set	£1,000.00
HP3334A Distortion Analyzer	£250.00
HP890A Vector Analyzer	£5,000.00
HP8901A Modulation Analyzer	£1,500.00
HP830A Universal Counter/Timer	£850.00

Marconi 2955 Radio Comms Test Set	£1,600.00
Marconi 2370 110MHz Spectrum Analyzer	£600.00
Marconi 2305 Modulation Meter	£2,000.00
Marconi 2601 True RMS Voltmeter	£500.00
Philips PM6680 High Resolution Programmable Counter/Timer opt. C Fitted	£1,350.00
Philips PM6666 Timer/Counter Opt C Fitted	£650.00
R&S ZPV/E3 3-2GHz	£1,800.00
R&S URE RMS Voltmeter	£800.00
Takeda Riken TR4172 Spectrum/Network Analyzer 1.8GHz	£6,500.00
Tektronix DA8084 Programmable Distortion Analyzer	£700.00

POWER SUPPLIES

Farnell 30100 30V 100A	£700.00
Farnell TSV70 MK2 Stabilised Power Supply	£180.00
Farnell 60/25 0-60V 0-25A Metered	£400.00
General Radio 1265A DC Power Supply 0-400V 0-5A	£475.00
HP6181C DC Current Source 0-100V 0-25mA	£300.00
HP6264B 0-20V 0-20A	£250.00
HP653A Systems DC Power Supply 0-35V 0-15A	£200.00
HP6534A Systems DC Power Supply 0-100V 0-1A 100W	£650.00
Power Ten 0-30V 0-60A	£300.00
Powerline LAB532 5V-5A, 15V-0.5A, -15V-0.5A, 0-30V-2A	£200.00
Powerline LAB510 0-30V 0-10A	£300.00
Powerline Electronics 0-70V 0-10A	£175.00

OSCILLOSCOPES

Gould OS1602 20MHz Digital Storage	£1,250.00
Gould OS300 20MHz	£120.00
Gould 5110 100MHz Intelligent Oscilloscope system	£400.00
Gould (RTD)350 50MHz Oscilloscope	£200.00
Gould 4072 40MHz/sec 100MHz Digital Storage	£750.00
Hameg HM604 60MHz Oscilloscope	£200.00
Hitachi VC222 20MHz	£225.00
Hitachi VC6015 Digital Storage	£300.00
Hitachi V-260F 60MHz Oscilloscope	£200.00
Hitachi V-352F 35MHz Oscilloscope	£175.00
HP 1727A 275MHz Storage Oscilloscope	£350.00
HP 1222A 10MHz Oscilloscope	£100.00
Iso-Tech ISR640 40MHz	£200.00
Kikusui COS810 100MHz Oscilloscope	£275.00
Kikusui COS5100 100MHz Oscilloscope	£275.00
Kikusui COS5040 40MHz Oscilloscope	£160.00
Kikusui COS5041 40MHz Oscilloscope	£160.00
Philips PM3264 100MHz Oscilloscope	£300.00
Philips PM3352A 50MHz Storage	£300.00
Philips PM4923A 0-10MHz Oscilloscope	£80.00
Philips PM3325A 60MHz Digital Storage	£1,000.00
Philips PM3305 35MHz	£250.00
Philips PM3214 0-25MHz Oscilloscope	£100.00
Philips PM3262	£250.00
Philips PM3267 100MHz Oscilloscope	£300.00
Philips PM3311 0-60MHz	£200.00
Tektronix 465 100MHz	£200.00
Tektronix 2225 50MHz	£350.00
Tektronix 2235 100MHz	£500.00
Tektronix 2245 100MHz	£500.00
Tektronix 2215 60MHz	£300.00
Tektronix 475 200MHz	£350.00
Tektronix 468 100MHz Digital Storage	£500.00
Tektronix 465B DC-100MHz	£225.00
Tektronix 434 Storage	£150.00
Tektronix 2245A 60MHz 4 channel on screen cursors	£600.00
Tektronix 2465A/B/C/T 300MHz (+)	from £1,500.00
Tektronix 2336 100MHz	£500.00
Tektronix TAS455 60MHz Dual Channel	£600.00

CIRCLE NO. 134 ON REPLY CARD

HOW DOES YOUR EQUIPMENT MEASURE UP? AT STEWART OF READING THERE'S ALWAYS SCOPE FOR IMPROVEMENT!

PHILIPS PM3217 - Dual Trace 50MHz Delay



This is really a very good oscilloscope including 2 probes, Pouch & Front cover
Only **£300**

GOULD OS300 Dual trace 20MHz. Lightweight. Very good value



ONLY **£160**

THIS IS THE BEST CHEAP SCOPE YOU WILL EVER BUY!!!



GOULD OS1100 Dual trace, 30MHz delay, very bright. Supplied with manual and 2 probes.



£200

TEKTRONIX 2215 - Dual Trace 60 MHz Sweep Delay, Includes 2 probes, Only



£350

TEKTRONIX 400 SERIES



468 Digital Storage Dual Trace 100MHz Delay...£550

466 Analogue Storage Dual Trace 100MHz Delay...£250

485 Dual Trace 350MHz Delay Sweep...£750

475 Dual Trace 200MHz Delay Sweep...£450

465 Dual Trace 100MHz Delay Sweep...£350

HC 3502 Dual Trace 20MHz



5mV-20Div; 0.2u secs-0.5 SecDiv; X-Y; X5 Magnifier; TVSync etc.
Un-Used **£180**

THESE TWO HAVE NEVER BEEN SO CHEAP



TEKTRONIX 2445 4ch 150MHz delay sweep cursors readout

ONLY **£700**



MARCONI 2019 Synthesised AM/FM Sig Gen 80KHz-1040MHz LCD Display Keyboard entry. ONLY **£750**

ALL FULLY TESTED - IN GOOD CONDITION

MARCONI 2022A/C Synthesised AM/FM Sig Gen 10KHz-1GHz from...£1500

MARCONI 6311 Prog Sweep Gen 100KHz-20GHz...£4,000

H.P. 8672A Synthesised Sig Gen 2-18GHz...£6000

H.P. 8657A Synthesised Sig Gen 100KHz-1040MHz...£2500

H.P. 8656B Synthesised Sig Gen 100KHz-990MHz...£1500

H.P. 8656A Synthesised Sig Gen 100KHz-990MHz...£1250

H.P. 3325A Synthesised Function Gen 21MHz...£600

H.P. 4275A LCR Meter 10KHz-10MHz...£2750

H.P. 4192A LF Impedance Analyser 5Hz-13MHz...£6000

H.P. 8903E Distortion Analyser...£1500

MARCONI 2305 Mod Meter 500KHz-2GHz from...£1200

FARNELL AMM2000 Automatic Mod Meter 10Hz-2.4GHz Unused...£1250

MARCONI 2955A Radio Comm Test Set...£2500

STABLOCK 4031 Radio Comm Test Set...£3000

STABLOCK 4015 Radio Comm Test Set...£2250

H.P. 8640A AM/FM Sig Gen 500KHz-1024MHz **£450**

500KHz-512MHz Version - £250

PHILIPS PM3296A Dual Trace 400Hz Dual TB Delay Cursors IEEE...£2250

SPECTRUM ANALYSERS

H.P. 8595E 9KHz-6.5GHz with Opts 004/041/101/105/110. 857171A card & 85024A high freq probe...£2500

H.P. 8590A 10KHz-1.8GHz (75chms)...£3500

H.P. 8558B with Main frame 100KHz-1500MHz...£1200

ADVANTEST TR4131 100KHz-3.5GHz...£1200

MARCONI 2370 30Hz-110MHz...from £500

HP141 Systems 8553 1KHz-110MHz from...£500

8554 500KHz-1250MHz from £750; 8555 10MHz-18GHz...from £1000

MARCONI TF2015 AM/FM sig gen 10-520MHz **£175**

RACAL 9008 Automatic Mod meter 1.5MHz-2GHz **£200**

FARNELL LF1 Sine/Sq Oscillator 10Hz-1MHz **£75**

LEVELL TG200DMP RC Oscillator 1Hz-1MHz Sine/Square, Meter, Battery Operated (Batteries not supplied)...£50

CLASSIC AVO METER A Digital AVO DA 116 3.5 digit Complete with Batteries & Leads Only **£30**

SOLATRON 7045 - 4.5 Dig Bench Multimeter with leads **£45**

SOLATRON 7150 - DMM 6.5 digit True RMS IEEE **£300**

WAYNE KERR AMM255 Automatic Modulation Meter AM/FM 1.5MHz-2GHz 3.5 digit **£500**

GOODWILL GFC 8010G Frequency Counter Range 1Hz-120MHz 8 digit display 15MV RMS sensitivity **£75**

BRAND NEW OSCILLOSCOPES - NEVER USED



DMS 3850A Digital Storage/DMM

Handheld LCD display, 2 Channels 50ms/s. Auto range 4 Digit DMM/Capacity/frequency counter. Battery operation or external 7.5-9.5V DC ie. AC adaptor pouch complete with 2 scope probes, DMM leads; Manual. **For only £400**

DTS 40 Digital Storage



Dual Trace 40MHz 20 MS/s Storage. Cursors + On screen readout. Sweep Delay; interface etc etc. Supplied unused in original box complete with 2 probes and manual. **Amazing Value £400**

DTA 20 Dual Trace 20MHz



All Mag TV Trig etc unused and boxed with 2 probes and manual. **£225**

PANASONIC VP8177A 100KHz-100MHz; FM 0-100KHz; Output - 19dB - 99dB AM 0-60%; 32 preset memory; Digital display frequency and output **Used £450 Unused £750**



KENWOOD FL180A WOW/FLUTTER METER 0.003%-10%; Freq 3KHz/3.15KHz RMS/AVERAGE/PEAK. Weighted filters; Digital display of rpm; 4 digit Freq counter 0.01KHz-9.999KHz/0.01KHz-55KHz **Used £400 Unused £500**



POWER SUPPLY Model HSP3010 0-30 volts; 0-10 amps current limiting; 2 meters **Used £160**



GOODWILL GVT427 DUAL CHANNEL AC MILLIVOLTMETER 10µV 300V in 12 ranges Frequency 10Hz-1MHz **Used £100 Unused £125**

STEWART of READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Telephone: (0118) 9268041 Fax: (0118) 9351696

Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)



USED EQUIPMENT - GUARANTEED. Manuals supplied
This is VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to total of goods and carriage.

CIRCLE NO.125 ON REPLY CARD

TRANSFORMERS FOR BALANCED LINES IN HIGH PERFORMANCE AUDIO SYSTEMS



E A SOWTER LTD

PO Box 36 IPSWICH IP1 2EL ENGLAND

Tel: +44(0)1473 252794

Fax: +44(0)1473 236188


E.Mail: sales@sowter.co.uk

Web: http://www.sowter.co.uk

Design and Manufacture of all types of Audio Transformer using Nickel and Grain Oriented cores

Free catalogue
Free technical support service
Popular types from stock

CIRCLE NO.126 ON REPLY CARD

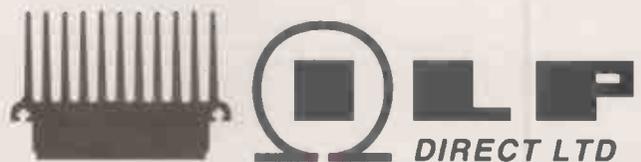

Hi-Fi POWER AMPLIFIERS

ILP 2000 SERIES POWER AMPLIFIERS ARE FULLY ENCAPSULATED HIGH QUALITY MODULES WITH INTEGRAL HEATSINKS AND CARRY A FIVE YEAR GUARANTEE.

BY SELECTING THE APPROPRIATE MAINS TRANSFORMER AND THE PROGRAMMING LINK ON THE MODULE THEY CAN BE USED WITH 4 OR 8Ω LOADS WITH THE AUTOMATIC ADJUSTMENT OF INPUT SENSITIVITY.

HY2000	30W HYBRID AMPLIFIER	£11.75
HY2001	30W HYBRID AMPLIFIER WITH P.S.U. BOARD	£17.63
HY2002	60W HYBRID AMPLIFIER	£17.63
HY2003	60W HYBRID AMPLIFIER WITH P.S.U. BOARD	£24.68
HY2004	120W MOSFET AMPLIFIER	£38.78
HY2005	120W MOSFET AMPLIFIER WITH P.S.U. BOARD	£48.18
HY2006	240W MOSFET AMPLIFIER	£79.90
HY2007	240W MOSFET AMPLIFIER WITH P.S.U. BOARD	£96.35

HI-FI QUALITY AUDIO POWER TRANSFORMER FINISHED IN BLACK WITH RESIN FILLED CENTRES FOR MAXIMUM NOISE ABSORPTION AND EASE OF MOUNTING.

AT0304	FOR ONE HY2000/1 IN 4Ω MODE	£17.63
AT0308	FOR ONE HY2000/1 IN 8Ω MODE	£17.63
AT0604	FOR ONE HY2002/3 IN 4Ω MODE	£21.15
AT0608	FOR ONE HY2002/3 IN 8Ω MODE	£21.15
AT1204	FOR ONE HY2004/5 IN 4Ω MODE	£28.20
AT1208	FOR ONE HY2004/5 IN 8Ω MODE	£28.20
AT2404	FOR ONE HY2006/7 IN 4Ω MODE	£39.95

PRICES INCLUDE VAT & POST AND PACKING

ILP DIRECT LTD

SPONG LANE, ELMSTED, ASHFORD, KENT TN25 5JU

PHONE +44 (0) 1233 750481 FAX +44 (0) 1233 750578

CIRCLE NO.127 ON REPLY CARD

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

Chip inductors

Pulse has announced 0603-sized wirewound chip inductors in 20 values from 1.8 to 120nH. The



PE-0603CD is compatible with Coucraft's 0603 series. RF applications include phase lock loop circuits and RF amplifiers in GSM mobile phones. They have a flat surface for pick-and-place compatibility, and tin-lead side metallisation.

Pulse
<http://www.pulseeng.com>
Tel: 01483 401700
Enquiry No 501

Fast boot block flash

Supporting both Asynchronous Page Mode (21ns) and Synchronous Burst Mode (54MHz) operation, Intel's fast

boot block memory is claimed to provide up to five times the system performance of standard low-voltage 80ns asynchronous flash memory. The interface provides glueless connection to the leading high performance processors.

The asymmetrically blocked architecture is supported by Intel's flash data integrator (FDI) software, to enable both code and data to be contained in the same fast boot block device. Suitable for pager, set-top box, handheld GPS, and automotive applications, the flash memory is available from Thame Components in 8- and 16-Mbit densities in industry standard 56-lead SSOP, 56-ball BGA packages.

Thame Components
Tel: 01844 261188
Enquiry No 502

Transceiver chipset

Analog Devices has announced the Softcell multicarrier transceiver chipset for use in cellular, PCS, wireless local loop, micro and pico cell, and smart antenna base stations. It is a functionally complete end-to-end, IF-to-digital transceiver that lets software radios be deployed for wireless infrastructure applications. Base stations containing the chipset can be

modified by adding services and channels, and changing wireless standards incrementally. Operators can use and move between air interface standards, for example GSM, PHS and D-Amps. The architecture eliminates redundant channel radios for transmitters and receivers. The chipset is optimised for four RF carrier channels but is expandable.

Analog Devices
<http://www.analog.com>
Tel: 01932 266014
Enquiry No 504

Sensor subsystem

Wolfson has launched the WM8181 CIS and CCD sensor image processing subsystem for low power scanners. Available in a 14-pin SOIC, it operates from single 5 or 3.3V or split 5V analogue and 3.3V digital supplies. It has a 12-bit, 2Msamples/s a-to-d converter with internal reference generation and a differential input. An optional clamp is available for linking to CCD linear image sensors. The serial output has a maximum data rate of 24Mbit/s. Requiring two clocks and supply decoupling, the product typically consumes 23mW at 3.3V operation and less than 1µW in power down mode.

Wolfson Microelectronics
<http://www.wolfson.co.uk>
Tel: 0131 667 9386
Enquiry No 505

Video multiplexer

Linear Technology has introduced the LT1675-1 single 2:1 video multiplexer by combining a two-channel multiplexer with a fixed gain amplifier. It eliminates the need for an external buffer amplifier and two gain setting resistors. Channel switching time is 2.5ns and it can toggle between sources over 100MHz with a slew rate more than 1100V/µs and a -3dB bandwidth of 250MHz. A disable function lets the output be put into a high impedance state for cascading stages, so multiple inputs can be multiplexed to one output. This function reduces power dissipation to nearly zero in the off parts.

<http://www.linear.com>
Tel: 01276 677676
Enquiry No 510

Audio accelerator

Atmel subsidiary Dream has added a PCI audio accelerator to its sound synthesis IC family. The Sam9777 delivers up to 64 streaming audio voices at up to 48kHz sampling frequency. It provides Interactive full



Pots and joysticks

Quiller Electronics has introduced potentiometers and joysticks from Tsubame Radio. The slider and rotary potentiometers are for use as faders and volume controls. Both types are available in SMT versions.

Quiller Electronics
<http://www.quiller.com>
Tel: 01202 436770
Enquiry No 503

bandwidth sound positioning on two to six speakers. Reverb, chorus, echo, pitch shifting, four band equaliser and surround sound 3DMidi have been combined with a GS compliant sound set under Roland licence.

Atmel
Tel: 01276 686677
Enquiry No 508

CAN bus microcontroller

Fujitsu has launched a CAN bus microcontroller for automotive and industrial control systems. The MB91360 is based on a modular building block idea and uses as its nucleus the firm's FR 32-bit Risc microprocessor core and CAN bus macro. Triple full-CAN bus interfaces are combined with onboard single voltage flash or ROM. The first device, the MB91F361, is fabricated in 0.35µm technology and has a CPU that clocks at 64MHz internally, with 512kbyte flash memory, 1kbyte instruction cache and 16kbyte RAM. The device integrates

TFT flat panel controllers

Philips Semiconductors has introduced video and graphics controllers for TFT flat panel displays. For use in multisync flat-panel colour monitors and LCD projectors, the SAA6712, SAA6712A (XGA resolution) and SAA6721 (SXGA resolution) RGB to TFT graphics engines perform horizontal and vertical scaling, colour adjustment, and on-screen display generation and insertion. Pixel and timing signals are generated to display the resulting images on various TFT displays. The SAA6712A and SAA6721 also accept 48-bit YUV video inputs, making them suitable for multimedia display applications. All three accept RGB data in 24-bit single-pixel format or 48-bit double-pixel interlaced format. They are packaged in 292-pin PBGAs.

Philips Semiconductors
Tel: 00 31 40 272 2091
Enquiry No 509



Please quote Electronics World when seeking further information

on-chip stepper motor controllers, real-time watch timer, sound generator, LED drivers and PPGs for light dimmers.

Fujitsu
<http://www.fujitsu.com>
 Tel: 01628 504600
 Enquiry No 507

SM package

International Rectifier has introduced the SMD-0.5 package, which weighs 1g and measures 7.5 by 10.1 by 2.9mm. For power supply, motor drive and linear regulator applications, it can be used with any Rad-Hard MOSFET, Hexfred diodes, Schottky or standard Hexfet power MOSFET device.

International Rectifier
 Tel: 01883 732020
 Enquiry No 506

LCD controller

Epson has introduced the SED1374 colour and monochrome LCD graphics controller with an embedded 40kbyte SRAM display buffer. Hardware portrait mode supports virtual display, allowing panning of larger images than panel size. Split screen display mode provides

multiple images on screen simultaneously. Display formats supported including 4 and 8-bit mono and colour LCD, 16-bit colour LCD, single panel and dual panel passives, and active matrix TFT and TFD. Display modes allow for up to 16 levels of grey scale and 256 level colour. Power saving capabilities include hardware and software suspend modes and LCD power down sequencing. Operating voltage is 2.7 to 5.5V.

Epson Electronics
<http://www.epson-electronics.de>
 Tel: 0 49 89 140 05-349
 Enquiry No 511

BGA sockets

Actel has announced ball-grid array sockets for use with its field programmable gate arrays. The sockets suit the prototyping environment and are compatible with the firm's MX and SX devices as well as upcoming reprogrammable FPGA families. The sockets have zero insertion force so the device is not stressed before, during or after testing. They use the same pad layout on the PCB that the device will eventually occupy. This avoids changes to the PCB during the crossover between prototyping and production.

Actel
 Tel: 01256 305600
 Enquiry No 512

Multi-banked DIMM module

Ambar Cascom has introduced a multi-bank synchronous and synchronous burst, flow-through SRAM module from White Electronic Designs. Made on the dual-key 168 DIMM format, the 3.3V device supports densities from 1 to 8Mbyte and has a maximum height of 3.8cm. Clock to data access times of 10, 12 and 15ns are available.

Electrical characteristics include byte write, global write and global reads, and linear and sequential burst is supported via the mode pin. The multi-banked synchronous burst flow-through architecture alleviates additional propagation delays at address boundaries that can occur with address mapping schemes.

Ambar Cascom
 Tel: 01296 332264
 Enquiry No 515

LCD controller

Harting has introduced sensors and actuators using the company's Harax



Connector cover

A nine-way D-subminiature connector cover from Stadium Cables has an inner area large enough to hold a small PCB. The PCB can be double sided if required. The two-part cover snap locks together using internal latches to give a finish similar in appearance to a moulded single-piece hood. The hood can be supplied in black plastic or be metallised for resistance to EMI and RFI. It is supplied in kit form, with two thumbscrews, grommet and strain relief. The grommet can be customised if required.

Stadium Cables
 Tel: 01622 690470
 Enquiry No 514

termination system. The axial insulation displacement termination system is claimed to combine the advantages of connectors and screwed cable glands.

Harting
 Tel: 01604 766686
 Enquiry No 516

LED lamps

QT Optoelectronics has announced surface mount chip type LED lamps. The QTLP600C and QTLP601C come in 0603 packages. They have a 100° viewing angle and moisture-proof packaging. Applications include panel illumination, push-button back lighting, LCD back lighting, and membrane switches. The QTLP600C is 0.8mm and the QTLP601C 0.6mm high. Both have water clear optics and come in four colours.

QT Optoelectronics
<http://www.qtopto.com>
 Tel: 01296 394499
 Enquiry No 517

LCDs

Trident Displays is distributing Hexa-Chain video LCD products including component form modules from 6.4 to 16.3cm at resolutions up to 0.25 VGA (960 x 234) and housed displays from 10.2 to 16.3cm using the same modules. Features include input from typically 10 to 30V, brightness up to 300cd/m², temperature range typically -30 to +80°C, Pal and NTSC input auto-switching, and antiglare screens.

Trident Displays
<http://www.tridentdisplays.co.uk/>
 Tel: 01737 780790
 Enquiry No 518

Embedded SBC

The EM-520 embedded single board computer from Steatite Systems combines sound and display features with a 10Mbps Ethernet LAN. The integrated graphics and audio sound package has VGA and LCD functionality with an NTSC and Pal TV output interface and sound blaster compatibility. It is for multimedia applications and is year 2000 tested. The graphics and audio features are supported by an onboard Cyrix Media GXi processor and Cx5520 companion chip. The processor is custom designed for multimedia applications supporting 1280 x 1024 x 8 and 1024 x 768 x 16 BPP, and including unified L1 cache memory.

Steatite Systems
<http://www.steatite.co.uk>
 Tel: 0121 678 6888
 Enquiry No 519

DCP boards

Transtech DSP has announced a family of boards ready for the introduction of Analog Devices' Sharx II DSP for applications such as radar, sonar and imaging. The Analog Devices ADSP-21160 is a floating-point DSP with six link ports for scalability. It has up to 600Mflops performance and 100Mbyte/s datacomms per link port. Power consumption is 2 to 3W. The boards include formats for PCI, VME, CompactPCI and PMC mezzanine, and are capable of up to 4.8Gflops performance per board slot.

Transtech
<http://www.transtech-dsp.com>
 Tel: 01494 464432
 Enquiry No 520



Capacitors

Pedoka is supplying Tokin capacitors with values from 0.022 to 5.0F. For use as non-battery reserve power sources, they provide currents from 1 to 100mA and protect microcomputers from power shutdowns of several seconds. They can maintain the contents of low-dissipation CMOS volatile memories for several months. Each capacitor consists of an electric double layer at the interface between activated carbon particles, and sulphuric acid solution as an electrolyte. The two electrodes are separated by an ionically conducting but electrically insulating porous membrane. Conductive rubber membranes contain the electrode and electrolyte material and make contact to the cell.

Pedoka
 Tel: 01462 422433
 Enquiry No 513

Please quote *Electronics World* when seeking further information

Development kit

Toshiba has launched a development kit for embedded applications using the company's TX 32-bit Risc microcontrollers based on the MIPS R3000A architecture. The Topas TX Risc starter kit includes an evaluation board and an evaluation version of the MULTI development environment from Green Hills Software with C and C++ compiler and a PC utility for flash programming.

Toshiba Electronics
Tel: 01276 694730
Enquiry No 522

EMC analysers

Hewlett-Packard has introduced automated in-house precompliance measurement systems to help manufacturers meet EMC regulations. The E7400 A series analysers are for EMC testing throughout the design and evaluation processes. Users require no special knowledge or training to perform precompliance measurements.

<http://www.hp.com/>
Tel: 00 49 6441 92460
Enquiry No 523

3V SiGe power amplifier

Temic Semiconductors has announced a 3V silicon germanium (SiGe) power amplifier, the TST0912, for GSM mobile phones. It is for single-band operation in the 900MHz range (GSM900), and allows the use of single-cell Li-ion or three-cell NiMH batteries. SiGe does not require

negative supply voltage. The amplifier has 35dBm maximum output power. Its power-added efficiency value is 50 per cent.

Temic
<http://www.temic-semi.com>
Tel: 01270 252209
Enquiry No 524


LEDs

Surface-mount chip-type LEDs with integrated lenses have been introduced by Hewlett-Packard. These lenses concentrate the emitted light into a typical 70° viewing angle. Applications include illuminating buttons and switches on panels, transferring light to optical light pipes used to illuminate panel legends, backlighting legends on car radios and dashboard devices, and as status indicators on computers, datacomms equipment and other office systems.

Hewlett-Packard
<http://www.hp.com/>
Tel: 00 49 6441 92460
Enquiry No 525

PSUs

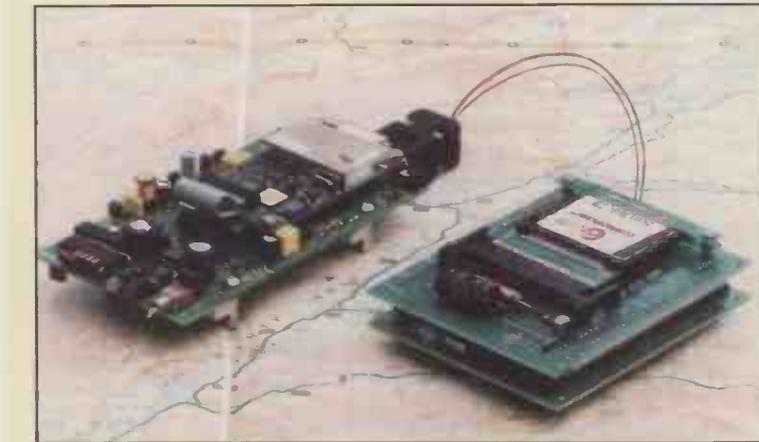Astec has introduced four 250W switched mode PSUs. Housed in a 51mm high case, the LPS250-CEF models let the single rail output be configured by the user from 3 to 6, 6 to 12, 12 to 24 and 24 to 48V DC. There are two supervisory outputs of 5 and 12V DC at 100 and 500mA respectively. The single wire current sharing feature supports the use of multiple units in parallel. This parallel



Data logger

The TDS2020 data logger from Triangle can collect information such as pressure, temperature, rotation rate and doors open or closed in Excel spreadsheet compatible format. Applications include agriculture, security, transport and shipping. Using GPS satellites, information on latitude, longitude, date and time can be incorporated. The storage medium is a PCMCIA or CompactFlash card for transfer to a PC. The module measures 100 by 80 by 30mm. The recording format on the CompactFlash card is Windows compatible.

Triangle
<http://www.triangledigital.com/>
Tel: 01845 527437
Enquiry No 536

capability also allows n+1 redundant configurations.

Astec
Tel: 01384 842211
Enquiry No 535

LED bulbs

Switchtec has introduced Sirena LED bulbs to replace low voltage filament bulbs in panels where it is difficult to change dead bulbs. Life time is claimed to be 100 000 hours. They



are resistant to vibration. There are six colours to choose from, including blue and bright green, and two sizes, 3 and 5mm diameter.
Switchtec Electronics
Tel: 01785 818600
Enquiry No 526

24-bit ADC

The LTC2400 24-bit analogue-to-digital converter. Its accuracy with total unadjusted error is less than 10ppm and it operates without


external crystals, software and additional circuitry. Integral non-linearity is 2ppm at 2.5V reference, with offset of 1ppm and drift of 0.01ppm/°C. Full-scale error is within 4ppm with drift 0.02ppm/°C. RMS noise is 0.3ppm at 1.5µV.
Linear Technology
Tel: 01276 67676
Enquiry No 527

64-bit PCI compliant PLD

Thame Components is shipping fully 66MHz, 64-bit PCI compliant programmable logic devices. Recent enhancements to Altera's FLEX10KE family of PLDs means that this 2.2V device family is specified to meet the required timing specifications contained within PCI Rev 2.1. In addition Thame has announced the availability of two intellectual property (IP) cores to support the 66MHz, 64-bit master/target function. One was developed by Altera's in-house team and the other by a member of the Altera Megafuncion Partners Program (AMPP). These cores provide designers with a 100 per cent soft implementation of the PCI Rev 2.1 specification. The range comprises five devices. The EPF10K50E contains 2880 logic elements, with 40kbits of memory structure in the patented EAB structure.
Thame Components
Tel: 01844 261188
Enquiry No 529

Chip capacitors

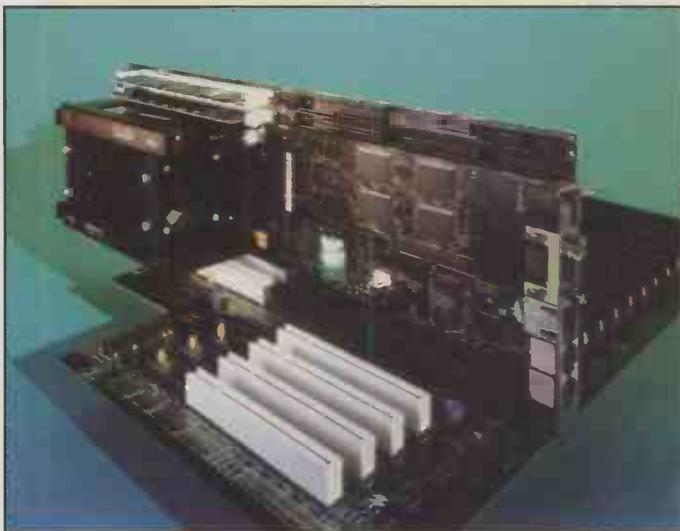Syfer has introduced 0805 feed-through chip capacitors for EMI



Processor board

The Microbus MAT 900 combines two 450MHz Pentium II processors, SCSI, 10 and 100Mbit autoswitching Ethernet, and AGP video on a board that fits into a slot in a PICMG backplane. The processors share a common sink-tunnel, creating a rigid box structure for secure retention of the processor assembly. This also allows fitting of the DIMMs above the processors, so OEMs can fit half-length cards in the slot next to the processor card in the PICMG backplane. The AGP video is based on the 3DLabs Permedia Two chipset and supports 4 or 8Mbyte SGRAM video memory. The PCI SCSI-3 supports transfers up to 40Mbyte/s.

Microbus
Tel: 01628 537333
Enquiry No 521

Please quote *Electronics World* when seeking further information

suppression, broadband i/o filtering, and DC power line applications. They are rated at 100 or 50V. Capacitances are from 22 to 820pF in COG and 470pF to 47nF in X7R dielectrics. Current rating is 300mA



Broadcast Interface

Faraday's extended range of Interface cards provides a small, convenient pre-designed solution to common conversions required between broadcast equipment.

Each card is a modular solution for a particular function, allowing easy addition of differing output and input options. This can ease design and production costs and logistics with guaranteed performance simplifying test procedures.

All relevant SMPTE and ITU specifications are adhered to. Each card contains all the filtering and buffering required to interface to external equipment and therefore require only the minimum of external components. They provide a complete drop in solution to conversion.

Common applications include the production of analogue outputs for video monitoring in digital equipment by the addition of a single card as specified by the end customer, or a permanent SDI input for different grade broadcast monitors or LCD displays.

Faraday Technology Ltd.
Tel., 01782 661501; fax 01782 630101
Enquiry No 534

and DC resistance less than 0.6Ω. Applications include power supplies, automotive, and multimedia add-on cards. Syfer Technology
Tel: 01603 629721
Enquiry No 530

Schottky diode

Zetex has introduced a Schottky diode in the SOD323 surface mount package. The ZHCS400 supports a continuous forward current of 400mA for a typical forward voltage of 425mV. This Superbat device has continuous, average and pulsed current performance providing 400mA, 1A and 6.75A respectively. Power dissipation at an ambient temperature of 25°C is 250mW. Forward voltage is 270mV at 50mA and 440mV at 500mA.

Zetex
Tel: 0161 622 4422
Enquiry No 531

Microchip

Microchip Technology has expanded its PIC16F87x family of 8-bit flash microcontrollers with the 28-pin PIC16F873 and 40-pin PIC16F874. To support these devices, the company has also introduced the MPLab in-circuit debugger evaluation kit that uses the MCU family and the firm's in-circuit serial programming to debug source code in the application, debug hardware in real-time and program a target PIC16F87x device. Operating under the MPLab integrated development environment, the kit provides real-time code execution, in-circuit debugging, built-in programmer and 3.0 to 5.5V operating range.

Microchip Technology
Tel: 0118 921 5858
Enquiry No 533

Debugger

The Huntsville BMD background mode debugger from Great Western Microsystems is for use with PowerPC, 683xx, 68HC12 and Coldfire devices and works with 3 or 5V systems, with power supplied by the target or the included external power supply. It interfaces with Motorola debug or IBM

JTAG port connections and has flexible breakpoints, flash programming support, control over target resources and the CPU, multiple compiler support, and HMI's Sourcegate II source level debugger.
<http://www.gwg.co.uk/>
Tel: 01179 830333
Enquiry No 532

Valve data

For restorers of vintage radios, G C Arnold Partners has re-introduced the Wireless World Valve Data Booklet at £2.95.
Tel: 01202 658474
Enquiry No 533

Early Valves

Characteristic Data for English and European Radio Valves from the early 1930s


BACK ISSUES

Back issues of *Electronics World* are available, priced at £3.00 UK and £3.50 elsewhere, including postage. Please send your order to *Electronics World*, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Free copy of *Electronics Engineer's* pocket book with every order while stocks last

Available issues

1994	1996	March
January	January	April
April	February	May
May	March	June
July	May	July
August	June	August
November	July/August	September
December	September	November
	October	December
	November	
1995		1999
February		January
April	1997	February
May	June	March
June	August	April
September	September	May
October		
December	1998	
	January	
	February	

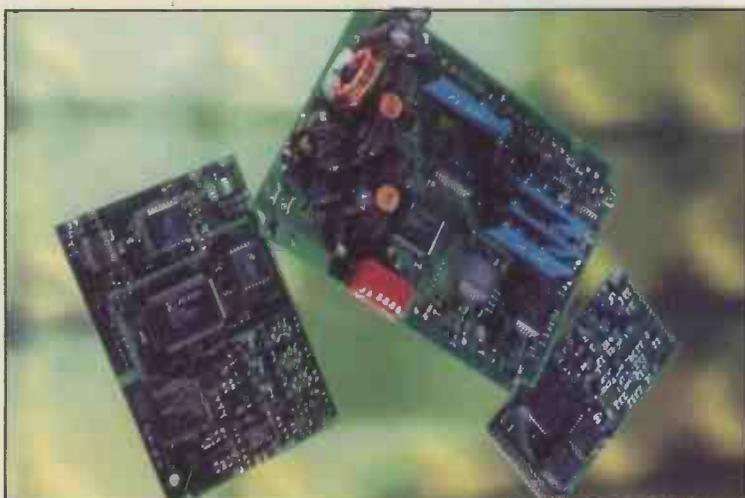

SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK

HP New Colour Spectrum Analysers LAST FEW ONLY
 HP141T + 8552B IF + 8553B RF -1KHZ -110Mc/s - £500.
 HP141T + 8552B IF + 8554B RF -100KHz -1250M - £600.
 HP141T + 8552B IF + 8556A RF -20Hz-300KHz - £400.
 HP141T + 8552B IF + 8556A 10 MC/S-18GHzS - £1000.
 HP8443A Tracking Gen Counter 100KHz-110Mc/s - £200
 HP8445B Tracking Preselector DC to 18GHz - £250.
 HP8444A Tracking Generator + 5-1300Mc/s - £450.
 HP8444A OPT 059 Tracking Gen + 5-1500Mc/s - £650.
 HP35601A Spectrum Anz Interface - £300.
 HP4953A Protocol Anz - £400.
 HP8970A Noise Figure Meter + 346B Noise Head - £3k
 HP8755A+B+C Scalar Network Anz PI - £250 + MF 180C - Heads
 11664 Extra - £150 each.
 HP3709B Constellation ANZ £1,000.
 HP11715A AM-FM Test Source - £350.
 FARNELL TVS70MII PU 0-70V 10 amps - £150.
 MARCONI 6500 Network Scaler Anz - £500. Heads available to
 40GHz many types in stock.
 Mixers are available for ANZs to 60GHz.
 HP6131C Digital Voltage Source + -100V/Amp.
 HP316A Universal Counter A+B.
 Marconi TF2374 Zero Loss Probe - £200.
 Rascal/Dana 2101 Microwave Counter - 10Hz-20GHz - with book as
 new £2k.
 Rascal/Dana 1250-1261 Universal Switch Controller + 200Mc/s PI
 Cards and other types.
 Rascal/Dana 9303 True RMS Levelmeter + Head - £450.
 TEKA6902A also A6902B Isolator - £300-£400.
 TEK CT-5 High Current Transformer Probe - £250.
 HP Frequency comb generator type B406 - £400.
 HP Sweep Oscillators type 8690 A+B + plug-ins from 20Mc/s to
 18GHz also 18-40GHz.
 HP Network Analyser type 8407A + 8412A + 8601A - 100Kc/s -
 110Mc/s - £500 - £1000.
 HP 8410-A-B-C Network Analyser 110Mc/s to 12 GHz or 18 GHz
 plus most other units and displays used in this set-up - 8411A-
 8412-8413-8414-8418-8740-8741-8742-8743-8746-8650. From £1k.
 Rascal/Dana 9301A-9302 RF millivoltmeter - 1.5-2GHz - qty in
 stock £250-£400.
 Rascal/Dana Modulation Meter Type 9009-9008 - 8Mc/s - 1.5GHz
 - £150/£250 - 9009A £350.
 Marconi RCL Bridge type TF2700 - £150.
 Marconi Microwave 6600A 1 sweep osc., mainframe with
 6650PI - 18-26.5 GHz or 6651 PI - 26.5-40GHz-£750 or PI only
 £600. MF only £250.
 Gould J3B test oscillator + manual - £150.
 Marconi 6155A Signal Source F1 to 2GHz - LED - £400.
 Barr & Stroud Variable Filter 0.1Hz-100Kc/s + high pass +
 low pass - £150, other makes in stock.
 Rascal/Dana 9300 RMS voltmeter - £250.
 HP 8750A storage normalizer - £400 with lead + S.A. or N. A
 Marconi mod meters type TF2304 - £250 - TF2305 - £1,000.
 Rascal/Dana counters-99904-9905-9906-9915-9916-9917-9921-
 50Mc/s-3GHz - £100 - £400 - all fitted with FX standards.
 HP180TR, HP181T, HP182T mainframes £300 - £500.
 HP432A-435A or B-436A-power meters + powerheads to 60GHz
 - £150 - £1750 - spare heads available.
 HP3586A or C selective level meter - £500.
 HP86222A+B Sweep PI - 0.1-2.4GHz + ATT £1000-£1250.
 HP86290A+B Sweep PI-2 - 18GHz - £1000 - £1250.
 HP8620C Mainframe - £250. IECE E350.
 HP8615A Programmable signal source - 1MHz - 50Mc/s - £1k.
 HP3455/3456A Digital voltmeter - £400.
 HP5370A Universal time interval counter - £1k.
 HP5335A Universal counter - 200Mc/s-£1000.
 HP3552A Transmission test set - £350.
 TEKTRONIX 577 Curve Tracer + adaptors - £900.
 TEKTRONIX 1502/1503 TDR cable test set - £400.
 HP8699B Sweep PI YIG oscillator .01 - 4GHz - £300. 8690B MF-
 £250. Both £500.
 Dummy Loads & Power att up to 2.5 kilowatts FX up to 18GHz -
 microwave parts new and ex equip - relays - attenuators -
 switches - waveguides - Ylgs - SMA - APC7 plugs - adaptors
 etc. qty. in stock.
 B&K Items in stock - ask for list.
 Power Supplies Heavy duty + bench in stock - Farnell - HP -
 Wei-ir - Thurlby - Rascal etc. Ask for list. Large quantity in stock,
 all types to 400 amp - 100Kv.
 HP8405A Vector voltmeter - late colour - £400.
 HP8508A Vector voltmeter - £2500.
 HP8505A Network Anz 500KHz-1.3GHz - £1000.
 HP8505A + 8502A or 8503A Test sets - £1200 - £1500.
 HP8505A + 8502A or 8503A + 8501A normalizer - £1750-£2000.
 Phillips 3217 50Mc/s oscilloscopes - £150-£250.
 Phillips 3296 350Mc/s IR remote oscilloscope - £500.
 R&S APN 62 LF S/G .1Hz - 260KHz with book - £500.
 Wavetek-Schlumberger 4031 Radio communication test set

LIGHT AND OPTICAL EQUIPMENT

Anritsu ML93A & Optical Lead Power Meter - £250.
 Anritsu ML93B & Optical Lead Power Meter - £350.
 Power Sensors for above MA96A - MA98A - MA913A - Battery
 Pack MZ95A.
 Anritsu MW97A Pulse Echo Tester.
 PI available - MH914C 1.3 - MH915B 1.3 - MH913B 0.85 -
 MH925A 1.3 - MH929A 1.55 - MH925A 1.3GI - MH914C 1.3SM -
 £500 + one PI.
 Anritsu MW98A Time Domain Reflector.
 PI available - MH914C 1.3 - MH915B 1.3 - MH913B 0.85 -
 MH925A 1.3 - MH929A 1.55 - MH925A 1.3GI - MH914C 1.3SM -
 £500 + one PI.
 Anritsu MZ100A E/O Converter.
 + MG912B (LD 1.35) Light Source + MG92B (LD 0.85)
 Light Source £350.
 Anritsu MZ118A O/E Converter.
 +MH922A 0.8 O/E unit + MH923 A1.3 O/E unit £350.
 Anritsu ML96B Power Meter & Charger £450.
 Anritsu MN95B Variable Att. 1300 £100.
 Photo Dyne 1950 XR Continuous Att. 1300 - 1500 £100.
 Photo Dyne 1800 FA. Att £100.
 Cossor-Raytheon 108L Optical Cable Fault Locator
 0-1000M 0-10KMc/s £200.
 TEK P6701 Optical Converter 700 MC/S-850 £250.
 TEK OF150 Fibre Optic TDR - £750.
 HP81512A Head 150Mc/s-1500-1700 £250.
 HP84801A Fibre Power Sensor 600-1200 £250.

HP8158B ATT OPT 002+011 1300-1550 £300.
 HP81519A RX DC-4000Mc/S 550-950 £250.
 STC OFR20 Reflectorometer - £250.
 STC OFS15 Machine jointing + eye magnifier - £250.
COMMUNICATION EQUIPMENT
 Anritsu ME453L RX Microwave ANZ - £350.
 Anritsu ME453L TX Microwave ANZ - £350.
 Anritsu MH370A Jitter Mod Oscillator - £350.
 Anritsu MG642A Pulse Patt Gen. £350.
 System MS02A Timer & Digital Printer - £500.
 Complete MS65A Error Detector.
 Anritsu ML612A Sel Level Meter - £400.
 Anritsu ML244A Sel Level Meter - £300.
 W&G PCM3 Auto Measuring Set - £300.
 W&G SPM14 Sel Level Meter - £300.
 W&G SPM15 Sel Level Meter - £350.
 W&G SPM16 Sel Level Meter - £400.
 W&G PS19 Level Gen - £500.
 W&G DA20+DA1 Data ANZ £400.
 W&G PMG3 Transmission Measuring Set - £300.
 W&G PSS16 Generator - £300.
 W&G PS14 Level Generator - £350.
 W&G EPM-1 Plus Head Milliwatt Power Meter - £450.
 W&G DLM3 Phase Jitter & Noise - £350
 W&G DLM4 Data Line Test Set - £400.
 W&G PS10 & PM10 Level Gen. - £250.
MISCELLANEOUS ITEMS
 HP 3852A Data Acquisition Control Unit + 44721A 16ch input
 £1,000.
 HP 4261 LCR meter - £650.
 HP 4274 FX LCR meter - £1,500.
 HP 4951A Protocol ANZ - £500.
 HP 3488 Switch Control Unit + PI Boards - £500.
 HP 75000 VXI Bus Controllers + £1326B-DVM-quantity.
 HP 83220A Gsm DCS/PCS 1805-1990MC/S converter for use
 with 8922A - £2,000.
 HP 1630-1631-1650 Logic ANZ's in stock.
 HP 8754A Network ANZ 4-13000Mc/S + 8502A + cables - £1,500.
 HP 8754A Network ANZ H26 4-26000Mc/S + 8502A + Cables -
 £2,000.
 HP 8350A Sweeper MF + 8350A PI 2-8.4GHz + 83545A PI 5.9-
 12.4GHz all 3 - £3,500.
 HP MICROWAVE TWT AMPLIFIER 489A 1-2GHz-30DB - £400.
 HP PREAMPLIFIER 8447A 0.1-4000Mc/S - £200. Dual - £300.
 HP PREAMPLIFIER 8447D 0.01-1.3GHz - £400.
 HP POWER AMPLIFIER 8447E 0.01-1.3GHz - £400.
 HP PRE + POWER AMPLIFIER 8447F 0.01-1.3GHz - £500.
 HP 3574 Gain-Phase Meter 1Hz-13Mc/S OPT 001 Dual - £400.
 MARCONI 2305 Modulation Meter-50KHz-2.3 GHz - £1,000.
 MARCONI 2610 True RMS Meter - £450.
 MARCONI 893B AF Power Meter (opt Sinad filter) - £250-£350.
 MARCONI 6950-6960B Power Meters + Heads - £400-£900.
 MARCONI SIGNAL SOURCE-6055-6056-6057-6058-6059 - FX
 Range 4-18GHz - £250-£400.
 RACAL 1792 COMMUNICATION RX - £500 early - £1,000 - late
 model with back lighting and byte test.
 RACAL 1772 COMMUNICATION RX - £400-£500.
 PLESSEY PR2250 A-G-H COMMUNICATION RX - £500-£900.
 TEK MODULE MAINFRAMES - TM5001-502-503-504-506-
 TM5003-5006.
 TEK PI 5010-M1 - Prog Multi Interface - £250. FG Prog 20MC/S
 Function Gen - £400 - S1 Prog Scanner - £250 - DM Prog DMM -
 £400.
 TEK 7000 OSCILLOSCOPE MAINFRAMES - 7603-7623-7633-
 7834-7854-7904-7904A-7104 - £150-£1,000.
 TEK 7000 PI's - 7A11-7A12-7A13-7A18-7A19-7A22-7A24-7A26-
 7A29-7A42-7B10-7B15-7B53A-7B80-7B85-7B92A-7D15-7D20.
 TEK 7000 - 7S11-7S12-7S14-7M11-S1-52-S3A-S4-S5-S6-S51-
 S53-S54.
RADIO COMMUNICATION TEST SETS
BULK PURCHASE ONLY FROM JOHNS RADIO
 HP 8920A RF Communication Test Set - Opts 003-004-007-011
 unit contains Syn Signal Gen-Distortion Meter-Mod Meter-Digital
 Oscilloscope etc. 1000MC/S - £1,500 each.
 MOTOROLA R2600A plus RLN4260A RF Test Set - £3,000.
 MARCONI 2955 RF Test Sets-1000MC/S - £1,200 each.
 MARCONI 2958 RF Test Sets-1000MC/S - £1,300 each.
 MARCONI 2960 RF Test Sets-1000MC/S - £1,400 each.
 MARCONI 2955A RF Test Sets-1000MC/S - £2,000 each.
 MARCONI 2960A RF Test Sets-1000MC/S - £2,500 each.
 ANRITSU MS55A2 Radio Comm Anz-1000MC/S - £1,200 each.
 MARCONI 2019A SYNTHESIZED SIGNAL GENERATORS -
 80Kc/S-1040Mc/S - AM-FM all functions tested off the pile as
 received from Gov - in average used condition - £650 each or
 in original Gov cartons 1st class condition each fitted with IEEE
 plus added protection front cover lid containing RF-IEEE-malns
 cables + N to BNC adaptor - Attenuator etc + Instruction Book
 - fully checked to high standards in our own workshop - £1k.
 MARCONI 2022E SYNTHESIZED SIGNAL GENERATOR -
 10Kc/S-1.01GHz Z AM-FM - made small and light for portability
 being the naval version - all functions tested off the pile as
 received from Gov - in average used condition - £1,000 each or
 in original Gov cartons as new condition - each fitted with IEEE
 + added protection front cover lid containing RF-IEEE - mains
 cables-N to BNC Adaptor - Attenuator-50-75OHM adaptor etc. +
 Instruction Book - fully checked to high standards in our own
 workshop - £1,250 each.
 WE KEEP IN STOCK HP and other makes of RF Frequency
 doublers which when fitted to the RF output: socket of a
 S/Generator doubles the output frequency EG.50-13000Mc/S to
 50-26000Mc/S price from £250 - £450 each.

SPECTRUM ANALYZERS

HP 3580A 5Hz-50KHz - £750.
 HP 3582A Dual 0.2Hz-25.5KHz - £1,500.
 HP 3585A 20Hz-400Mc/S - £3,500.
 HP 3588A 10Hz-1500Mc/S - £7,500.
 HP 8568A 100Hz-1.5GHz - £3,500.
 HP 8568B 100Hz-1.5GHz - £4,500.
 HP 8590B 9Kc/S-1.8GHz - £4,500.
 HP 8569B 10Mc/S (0.01-22GHz Z) - £3,500.
 HP 3581A Signal Analyzer 15Hz-50KHz - £400.
 TEK491 10Mc/S-12.4GHz + 12.4-40GHz - £500.

TEK492 50KHz-21GHz OPT 2 - £2,500.
 TEK492P 50KHz-21GHz OPT 1-2-3 - £3,500.
 TEK492AP 50KHz-21GHz OPT 1-2-3 - £4,000.
 TEK495 100KHz-1.8GHz - £2,000.
 HP 8557A 0.01Mc/S-350Mc/S - £500 + MF180T or 180C - £150 -
 182T - £500.
 HP 8558B 0.01-1500Mc/S - £750 - MF180T or 180C - £150 -
 182T - £500.
 HP 8559A 0.01-21GHz - £1,000 - MF180T or 180C - £150 - 182T
 - £500.
 HP 8901A AM FM Modulation ANZ Meter - £800.
 HP 8901B AM FM Modulation ANZ Meter - £1,750.
 HP 8903A Audio Analyzer - £1,000.
 HP 8903B Audio Analyzer - £1,500.
 MARCONI 2370 SPECTRUM ANALYZERS - HIGH QUALITY -
 DIGITAL STORAGE - 30Hz-1100Mc/S Large qty to clear as
 received from Gov - all sold as is from pile complete or add
 £100 for basic testing and adjustment - callers preferred - pick
 your own from over sixty units - discount on qty's of five or
 more.
 A EARLY MODEL GREY - horizontal alloy cooling fins - £200.
 B LATE MODEL GREY - vertical alloy cooling fins - £300.
 C LATE MODEL BROWN - as above (few only) - £500.

OSCILLOSCOPES

TEK 465-465B 100Mc/S + 2 probes - £250-£300.
 TEK 466 100Mc/S storage + 2 probes - £200.
 TEK 475-475A 200Mc/S-250Mc/S + 2 probes - £300-£350.
 TEK 2213-2213A-2215-2215A-2224-2225-2235-2236-2245-60-
 100Mc/S - £250-£400.
 TEK 2245 4ch 150Mc/S + 2 probes - £450.
 TEK 2245A 4ch 150Mc/S + 2 probes - £600.
 TEK 2245B 4ch 150Mc/S + 2 probes - £750.
 TEK 468 D.S.O. 100Mc/S + 2 probes - £500.
 TEK 485.350Mc/S + 2 probes - £550.
 TEK 2465A 4ch-300Mc/S - £1,150.
 TEK 2465A 4ch-350Mc/S - £1,550.
 TEK 2465B 4ch-400Mc/S - £2,000.
 TEK D.S.O. 2230-100Mc/S + 2 probes - £1,000.
 TEK D.S.O. 2430-150Mc/S + 2 probes - £1,250.
 TEK D.S.O. 2430A-150Mc/S + 2 probes - £1,750.
 TEK D.S.O. 2440-300Mc/S + 2 probes - £2,000.
 TEK TAS 475-485-100Mc/S-20Mc/S-4 ch + 2 probes - £900-£1.1K.
 HP1740A - 100Mc/S + 2 probes - £250.
 HP1741A - 100Mc/S storage + 2 probes - £200.
 HP1720A - 172A - 1725A - 275Mc/S + 2 probes - £300-£400.
 HP1744A - 100Mc/S storage - large screen - £250.
 HP1745A - 1746A - 100Mc/S - large screen - £350.
 HP54100A - 1GHz digitizing - £500.
 HP54200A - 50Mc/S digitizing - £500.
 HP54501A - 100Mc/S digitizing - £500.
 HP54100D - 1GHz digitizing - £1,000.

MICROWAVE COUNTERS - ALL LED READOUT

EIP 351D Autohet 20Hz-18GHz - £750.
 EIP 371 Micro Source Locking - 20Hz-18GHz - £850.
 EIP 451 Micro Pulse Counter - 300Mc/S-18GHz - £700.
 EIP 545 Microwave Frequency Counter - 10Hz-18GHz - £1k.
 EIP 548A Microwave Frequency Counter - 10Hz-26.5GHz - £1.5k.
 EIP 575 Microwave Source Locking - 10Hz-18GHz - £1.2k.
 EIP 588 Microwave Pulse Counter - 300Mc/S-26.5GHz - £1.4k.
 SD 6054B Micro Counter 20Hz-24GHz - SMA Socket - £800.
 SD 6054B Micro Counter 20Hz-18GHz - N Socket - £700.
 SD 6054D Micro Counter 800Mc/S-18GHz - £600.
 SD 6246A Micro Counter 20Hz-26GHz - £1.2k.
 SD 6244A Micro Counter 20Hz-4.5GHz - £400.
 HP5352B Micro Counter OPT 010-005-46GHz - new in box - £5k.
 HP5340A Micro Counter 10Hz-18GHz - Nixey - £500.
 HP5342A Micro Counter 10Hz-18-24GHz - £800-£1K - OPTS
 001-002-003-005-011 available.
 HP5342A + 5345S Source Synchronizer - £1.5k.
 HP5345A 500Mc/S 11 Digit LED Readout - £400.
 HP5345A + 5355A Plugin - 4GHz - £700.
 HP5345A + 5355A Plugin with 5356E 18GHz Head - £1k.
 HP5358A 1GHz 5386A-5386A 2GHz Counter - £1k-£2k.
 Rascal/Dana Counter 1991-160Mc/S - £200.
 Rascal/Dana Counter 1992-1.3GHz - £600.
 Rascal/Dana Counter 9921-3GHz - £350.

SIGNAL GENERATORS

HP8640A - AM-FM 0.5-512-1024Mc/S - £200-£400.
 HP8640B - Phase locked - AM-FM 0.5-512-1024Mc/S - £500-
 £1.2k. Opts 1-2-3 available.
 HP8654A - B AM-FM 10Mc/S-520Mc/S - £300.
 HP8656A SYN AM-FM 0.1-9900Mc/S - £900.
 HP8656B SYN AM-FM 0.1-9900Mc/S - £1.5k.
 HP8657A SYN AM-FM 0.1-1040Mc/S - £2k.
 HP8657B SYN AM-FM 0.1-2060Mc/S - £3k.
 HP8660C SYN AM-FM-PM-0.01-1300Mc/S-2600Mc/S - £2k.
 HP8660D SYN AM-FM-PM-0.01-1300Mc/S-2600Mc/S - £3k.
 HP8673D SYN AM-FM-PM-0.01-26.5 GHz - £1.2k.
 HP3312A Function Generator AM-FM 13Mc/S-Dual - £300.
 HP3314A Function Generator AM-FM-FC-20Mc/S - £600.
 HP3325A SYN Function Generator 21Mc/S - £800.
 HP3325B SYN Function Generator 21Mc/S - £2k.
 HP8673-B SYN AM-FM-PH-2-26.5 GHz - £6.5k.
 HP3326A SYN 2CH Function Generator 13Mc/S-IEEE - £1.4k.
 HP3336A-B-C SYN Func/Level Gen 21Mc/S - £400-£300-£500.
 Rascal/Dana 9081 SYN S/G AM-FM-PH-1.5-520Mc/S - £300.
 Rascal/Dana 9082 SYN S/G AM-FM-PH-1.5-520Mc/S - £400.
 Rascal/Dana 9084 SYN S/G AM-FM-PH-001-1040Mc/S - £300.
 Rascal/Dana 9087 SYN S/G AM-FM-PH-001-1300Mc/S - £1k.
 Marconi TF2008 AM-FM-Sweep 10Kc/S-510Mc/S - £200 Fully
 Tested to 300s, as new + book + probe kit in wooden box.
 Marconi TF2015 AM-FM-10-520Mc/S - £100.
 Marconi TF2016A AM-FM 10Kc/S-120Mc/S - £100.
 Marconi TF2171/3 Digital Synchronizer for 2015/2016A - £50.
 Marconi TF2018A AM-FM SYN 80Kc/S-520Mc/S - £500.
 Marconi TF2019A AM-FM SYN 80Kc/S-1040Mc/S - £650-£1k.
 Marconi TF2022E AM-FM SYN 10Kc/S-1.01GHz - £1k-£1.2k.
 Farnell EGS1000 AM-FM SYN 10Hz-1GHz - £500.
 R & S SMPD AM-FM-PH 5KHz-2720Mc/S - £3k.
 Anritsu MG3601A SYN AM-FM 0.1-1040Mc/S - £1.2k.

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. SAE FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS. AVAILABILITY OR PRICE CHANGE. VAT AND CARRIAGE EXTRA. ITEMS MARKED TESTED HAVE 30 DAY WARRANTY. WANTED: TEST EQUIPMENT-VALVES-PLUGS AND SOCKETS-SYNCRS-TRANSMITTING AND RECEIVING EQUIPMENT ETC.

Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel: (01274) 684007. Fax: 651160

CIRCLE NO. 128 ON REPLY CARD

SLS

Jitter buster

Claimed to be at least as big a breakthrough as the PLL, this new anti-jitter technique does not suffer from recovery problems when its input frequency changes.

A new class of circuits, designated 'anti-jitter circuits,' or AJCs for short, has been identified by Professor Mike Underhill at Surrey University.

The most important function of an AJC is to reduce phase noise, or equivalently time jitter, in pulse streams used to carry data in communications systems. But since the concept in its current form has been shown to be capable of working from low frequencies to 5GHz, potential applications are numerous.

The AJC involves feeding a series of pulses into an integrator then passing the result through a comparator after DC level adjustment. The pulses emerge with leading edges equally spaced and phase noise is reduced by as much as 30dB.

A key benefit of the AJC is that it recovers from a frequency change

much more rapidly than a PLL, Fig. 1.

In drawing attention to the simplicity of the basic idea, Prof Underhill comments: "The AJC is as fundamental, and is likely to be as useful, as the phase locked loop. Many of the applications for which PLL circuits are currently used might, with advantage, use a variation of the AJC instead."

Advantages of the AJC include lower phase noise and/or faster frequency switch time – the latter being key in mobile communications where the cellular principle and frequency hopping demand frequent frequency switching.

In its basic form, the AJC only de-jitters the leading edges of pulses, so the output has to be half the input frequency. But with simple enhancements, AJCs allow two pulse edges to be de-jittered, enabling output at the input frequency.

In many circuits, the AJC could simply be a 'drop-in' enhancement.

How does it work?


The concept behind the anti-jitter circuit is to feed a series of pulses into an integrator, then pass the result through a comparator, Fig. 2.

The pulses emerge equally spaced. This approach is applied to incoming signals that have 'jitter' or phase noise errors to achieve a large reduction in that noise – as much as is achieved by present techniques.

The approach adopted in AJC technology is very different from that of PLL technology. In PLLs a voltage-controlled local oscillator is made to track the average frequency of the incoming signal.

When the incoming clock hops to a new frequency there is inherently a time delay before a PLL circuit can stabilise to the correct tuning. AJCs adopt the new frequency

Fig. 1. Anti-jitter circuits inherently recover from an input frequency change much more rapidly than a pll.

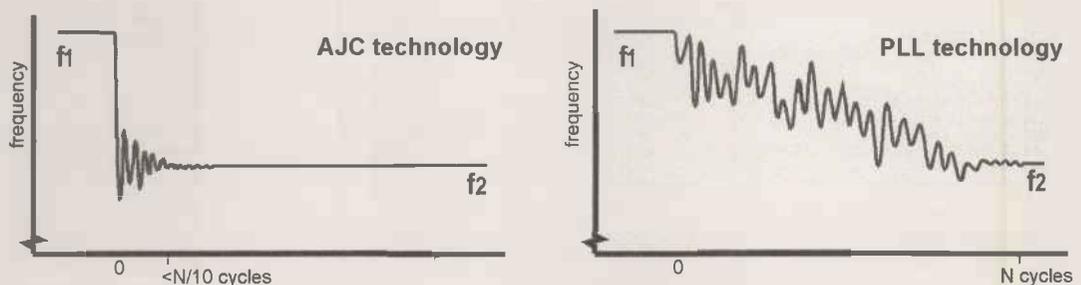

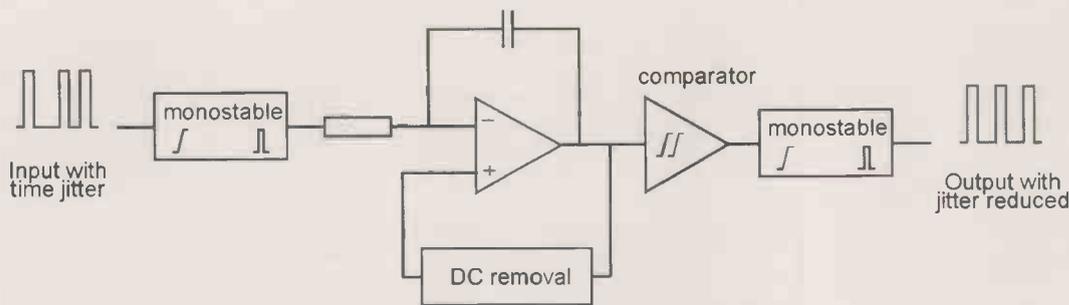


Fig. 2. Anti-jitter circuit outline. Note that there is no oscillator in this circuit. Output is derived directly from the input, having been governed to the average input frequency by the action of the integrator and comparator.

immediately. This is a significant advantage in channel-hopping systems, such as mobile telephones, where the output signals delivered by AJCs promise better reception at each frequency and much more stable reception when moving from cell to cell.

Wherever the capacity of communication systems is limited by the minimum frequency spacing at which PLL technology will reliably operate, the use of AJCs in combination with PLL circuits will multiply the utilisation of available frequencies.

The core of circuits adopting the AJC approach is shown in Fig. 2. Note that there is no oscillator in this circuit. The output signal derives directly from the input, having been governed to the average input frequency by the action of the integrator and comparator. This yields many advantages.

The core circuit just reduces phase noise. Circuits based on this core have been developed to achieve additional functions such as insertion of missing pulses, deletion of spurious pulses, fractional-N synthesis and high frequency operation.

Applications

Anti-jitter circuit technology is expected to be of value to manufacturers of all modern communications systems and their system designers.

In mobile telephone systems, the new circuit technology will deliver high noise reduction with faster lock-on and fewer dropped connections. Its use will enhance overall system utilisation and performance. It can be applied to digital cellular systems operating to any protocol, including GSM and next-generation UMTS systems.

Anti-jitter circuit technology applies widely to many other

communications systems, including high speed modems and ISDN connectors, wireless LANs, GPS, wireless local-loop telephony, satellite telephony, analogue cellular telephony, short wave radio, FMCW and hopping radar, and general electronics applications such as high performance analogue-to-digital converters and frequency synthesisers.

Circuits based on the technology are straightforward to use and can be deployed in discrete components, or in standardised ASIC cells, without any adjustment to the wider circuit environment. They will operate from less than 1kHz to above 5GHz and are fully cascable to achieve noise suppression in excess of 20dB per stage.

Anti-jitter circuit modules can be used wherever phase noise is a problem. They can be used in place of phase-lock loop circuits, or as an enhancement to allow them to operate at much narrower frequency spacing, for example. They will also replace or enhance direct digital synthesis designs.

AJC is the subject of a family of six separate patent applications that are now available for licensing for first manufacture.

Key features

Frequency limit. AJC technology has been laboratory tested in discrete component circuits operating at low frequencies – up to 10MHz – and modelled in high frequency circuits – up to 5GHz – using component specifications that match current silicon chip fabrication standards. Maximum operational frequency has been shown to be limited only by component performance.

Frequency range. Simple AJCs operate down to approximately 30% of their maximum operational

frequency. Modifications that provide either 'adaptive' or 'self-programming' modes allows this range to be extended to just 1% of the maximum where required.

Noise removal. AJCs have already achieved better than 20dB reduction in phase noise, and greater reductions can be achieved by cascading. Remaining time jitter can be reduced to subpicosecond levels. Unlike some other techniques, AJC technology achieves the reduction of total

Who needs anti-jitter?

Maintenance of accurate clock pulses is a widespread requirement in electronics. Errors in the arrival time of pulses constitute 'phase noise' or 'time jitter'.

Phase noise is a particular problem in communication systems, where large phase deviations can arise from such effects as mutual interference between transmitters, fluctuations in propagation, changes in polarisation due to Faraday rotation, weather conditions, movement of antennas or reflectors, and movement of objects in the signal path. This noise degrades the signal considerably and can cause its complete loss when the receiver can no longer track the pulse train on which the signal is encoded.

Even in compact systems, phase noise can place a limit on speed or performance. Thermal noise and 'flicker' generated by semiconductor components can produce phase noise in both analog and digital circuits. Digital circuits suffer phase noise where circuit loading and fan-out vary, and asynchronous digital circuits are prone to phase noise from unwanted cross-coupling.

To alleviate these problems a number of approaches are presently available. Careful tailoring of key circuits can minimise the generation of phase noise at source. Complex phase-lock loop and direct digital synthesis circuits allow sophisticated RF receiver strategies, but suffer from phase noise problems.

Some circuits spread or dither the noise to other frequencies. Each has disadvantages in performance, spurious effects on – or loss of – the signal, design time and manufacturing cost.

AJC technology provides a fresh approach which promises to match or outperform other methods in most respects, and is considerably easier to deploy.

Need more information?

For more information, contact Dr Neil Downie, Maran & Co Ltd via fax on +44 (0)1483 302112 or via e-mail using n.downie@maran.co.uk. Below are four references giving more information on this topic.

- 'The anti-jitter circuit for low spurious DDS square waves and low cost fractional-N synthesis,' MJ Underhill, S Stavrou, M Blewett, N Downie. European Frequency Time Forum, Warsaw, 1998
- 'Performance assessment of a delay compensation phase noise and time jitter reduction method,' MJ Underhill, M Blewett. European Frequency Time Forum, Neuchatel, 1997.
- 'Spectral improvement of direct digital frequency synthesisers and other frequency sources,' MJ Underhill, M Blewett. European Frequency Time Forum, Brighton, 1996.
- 'The Anti-Jitter Circuit for suppression of wide band phase noise,' MJ Underhill, Microwaves and Millimetre-wave Oscillators and Mixers, IEE, London December 1998 (to be published).

noise, rather than spreading the noise to other frequencies. It offers good wideband noise reduction – a unique feature – without increase in close-to-carrier noise. Good suppression of highest sideband frequencies is also achieved.

Tuning and locking. AJC technology is inherently self-tuning to lock on the average frequency of the pulse train. It tracks abrupt changes in frequency instantly, if they are small, or within typically 5 cycles if the changes are large. Very importantly, the output signal remains useful throughout – a

major advance over other technologies and a valuable contribution to better performance in cellular communication systems. Noise is reduced by typically 10-15dB while the change is tracked, full noise reduction is then progressively reasserted. Under typical conditions full noise reduction is restored within a few microseconds of the change in frequency.

Frequency spacing. AJCs should allow better use of the radio spectrum. By use of AJC technology, for example for fractional-*n* synthesis, operational frequencies are not limited in precision by the step size of a PLL analogue synthesiser, for example.

Circuit environment. The AJC normally needs an input to be in the form of pulses of equal length, which is the case in many applications. Simple variants can be adopted to deal with unequal pulse lengths. Its function is independent of its circuit environment, and so can be incorporated in almost any circuit as a 'drop-in' component or ASIC cell. Multiple AJCs can be cascaded for demanding applications.

Robustness. The tested designs are well-behaved, do not lock to the wrong frequency or stop completely, always provide phase continuity, and do not generate glitch pulses.

Wide performance envelope. In its high frequency form AJCs have been modelled at 5GHz and beyond with an operational frequency range of up to 1000:1. Frequency jumps of up to 50% are tracked, as are phase jumps of up to ±150°.

Manufacturability. AJC circuits are MSI type circuits: relatively low in complexity and manufactured at low cost. Due to its wide performance envelope, only a small number of AJC design variants is needed to serve almost every application.

Extra capabilities. As well as noise reduction, AJC circuits have been designed which insert missing pulses and delete spurious pulses. AJC variants have been developed for tasks such as multiphase clock distribution and fractional-*n* synthesis.

The underlying technology is also capable of development to deliver other related functionalities: for example, clean-up of DDS spurious frequency outputs.

AJCs can be used to enhance existing PLL and DDS technology and they are compatible with existing PLL and DDS technologies. This opens up the possibility for adding AJCs to conventional PLL circuits to make them effective at much narrower frequency spacings – an important benefit in communications.

Added to DDS circuits, AJC technology produces cleaner output signals with improved spurious sidebands. ■

New work
Mike Underhill is currently working on a new implementation of the AJC in which the comparator is replaced by a simple logic gate and the integrator is replaced with a passive charge accumulator. This will make the circuit much easier to use and manufacture.

Comparison between the AJC and PLL.

	Anti-Jitter Circuit	Phase Lock Loop
Maximum frequency	5GHz (high speed version)	5GHz (specialised designs)
Frequency range	down to 30% of maximum (standard) down to 1% of maximum (adaptive)	Down to 50% of maximum
Noise (far out)	-160dBc possible (improved 20db/stage)	-160dBc
Noise (close in)	-80dBc	-80dBc
Spurious noise	None so far detected	Generally minimal (some microphonic)
Switching delay	5 cycles typical	>20 x $f_c/\Delta f$ (e.g. 200 cycles for typ. 100MHz operation)
Output while switching	Usable output – half normal noise reduction	Unusable output, spurious signals
Self-locking	Yes	Yes, but only over narrow range
Circuit environment	Drops-in to 'any' circuit	May require tailoring to circuit environment
Cascadable	Yes, simple	No
Cost/complexity	single MSI chip	MSI chip + typically 10 external components

OSCILLOSCOPES

HP 54201D 300 MHz 2 channel digitising (27 channels logic state triggering)	£1,250
TEKTRONIX 79017A26 x27B80 200 MHz 4 channel	£450
TEKTRONIX 76017A18A x27B53A 4 channel	£350
TEKTRONIX 2445/2445A 300 MHz 4 channel from £1,800	
TEKTRONIX 2445A 150 MHz 4 channel OPT05	£1,100
TEKTRONIX 2445A 150 MHz 4 channel	£850
TEKTRONIX 2445 150 MHz 4 channel GP-IB	£900
TEKTRONIX 2246A 100 MHz 4 channel autocal	£900
TEKTRONIX 2245 100 MHz 4 channel (NEW)	£700
TEKTRONIX 2235 100 MHz 2 channel	£600
TEKTRONIX 2230 100 MHz 2 channel digital storage	£1,000
TEKTRONIX 2225 50 MHz 2 channel	£400
TEKTRONIX 2220 60 MHz 2 channel digital storage	£750
TEKTRONIX 2215 60 MHz 2 channel	£295
TEKTRONIX TM504 4 spot mainframe	£150
TEKTRONIX 475 200 MHz 2 channel	from £400
TEKTRONIX 448 100 MHz 2 channel digital storage (new)	£600
TEKTRONIX 465B 100 MHz 2 channel OPT05	£400
TEKTRONIX 465 100 MHz 2 channel	£350
FLUKE PM302 100 MHz 4 channel (new)	£1,200
PHILIPS PM 3263K 100 MHz delay/levels	£375
PHILIPS PM 3217 50 MHz 2 channel	£295
PHILIPS PM 3057 50 MHz 2 channel	£375
PHILIPS PM 3055 50 MHz 2 channel	£350
IWATSU SS 5711 100 MHz 4 channel (as new)	£325
IWATSU SS 5710 60 MHz 4 channel (as new)	£275
KIKUSUI CO55041 40 MHz 2 channel	£245
KENWOOD CS 4025 20 MHz 2 channel	£200
NICOLET 4094/4562/F43 digital scope	£250
HITACHI V1100 100 MHz 4 channel with cursors	£750
GOULD 4035 20 MHz digital storage + remote keypad	£500
GOULD OS1800A 30 MHz 2 channel DIL timebase	£160
GOULD OS350B 15 MHz 2 channel	£130

SIGNAL GENERATORS

HP 8904A DC-600 KHz multifunction synthesiser	£1,750
HP 8683D 2.3 GHz-13 GHz OPT 001/003 solid state generator (as new)	£1,500
HP 8656A 100 KHz-990 MHz signal generator	£1,200
HP 8640A 20 Hz-512 MHz signal generator	£250
HP 8640B 60 KHz-512 MHz signal generator	£600
HP 8620C/8622A 5.9-9 GHz sweeper	£1,000
HP 8620C/8624A 1.2-6.5 GHz sweeper	£900
HP 8620C/86230B 1.8 GHz-4.2 GHz sweeper	£900
HP 8620C/86220A 10-1300 MHz sweeper	£600
HP 8620C sweeper mainframes (as new)	£250
HP 8005B 0.3 Hz-20 MHz pulse generator	£250
HP 3336B 10 Hz-21 MHz synthesiser/level meter	£300
HP 3320A frequency synthesiser 0.1 Hz-13 MHz	£300
HP 3314A 0.001 Hz-19.99 MHz function/waveform monitor	£1,200
HP 3312A 0.1 Hz-13 MHz function generator	£400
THURLBY TG230 2 MHz sweep function generator	£150
TEKTRONIX 2901 time mark generator	£200
MARCONI TF2022 10 KHz-1000 MHz signal generator	£900
MARCONI TF2018 80 KHz-520 MHz signal generator	£700
MARCONI TF2015/1211 10 MHz-520 MHz with synthesiser	£350
RENELL SSG520 10 MHz-520 MHz synthesised	£300

FLUKE 6011A 10 Hz-11 MHz synthesised signal generator	£1,000
ROHDES & SCHWARTZ APN62 0.1 Hz-260 KHz LF gen (new)	£750
GIGA GR101A 12 GHz-18 GHz pulse generator	£500
PHILIPS PMS190 1 MHz-2 MHz LF synthesiser (new)	£400

SPECTRUM ANALYSERS

TEKTRONIX 494P 10 KHz-1800 MHz	£3,000
TEKTRONIX 494P 10 KHz-21 GHz (1 year Cal & warranty)	£7,000
TEKTRONIX 492P 10 KHz-21 GHz OPT 001/002/003	£5,500
ANRITSU MS610B 10 KHz-2 GHz spectrum analyser	£3,000
TAKEDA RIKEN TR4172 400 Hz-1800 MHz spectrum/network analyser	£5,500
HP 1650B 80 channel 100 MHz logic analyser (new)	£1,250
HP CALAN 3010R sweep/ingress analyser	£1,000
HP 8753A/85046A 100 KHz-3 GHz network analyser/S parameter test set opt 010	£6,000
HP 8903A audio analyser	£300
HP 8590A 10 MHz-1.5 GHz spectrum analyser	£4,000
HP 8559B/182T 10 MHz-21 GHz	£2,750
HP 8558B 100 KHz-1.500 MHz analyser + mainframe	£1,000
HP 8557A 100 KHz-350 MHz analyser + mainframe	from £500
HP 8407A/8412B network analyser 0.1-110 MHz	£400
HP 3582A 0.02 Hz-25.35 KHz dual channel signal analyser	£1,800
HP 141T/8552B/8555A 10 MHz-18 GHz	£1,500
HP 140T/8552B/8553B 10 KHz-110 MHz	£450
MARCONI 2380/2382 100 Hz-400 MHz	£2,300
MARCONI TF2370 30 Hz-110 MHz digital storage	£400
CUSHMAN CE15 1 MHz-1000 MHz spectrum monitor	£350

SPECIAL OFFERS

IWATSU S55711 100 MHz 4 channel oscilloscopes (as new)	£335
IWATSU S55710 60 MHz 4 channel oscilloscopes (as new)	£275
PLESSEY PRS2282A HF receivers	£1000
RACAL RA1772 HF receivers	£650
RACAL RA217D receiver + FSK adaptor	£300
RACAL RA17L 30 MHz receivers	£150
KENWOOD CS1575A 5MHz dual trace oscilloscopes	£50
LEADER LB552C stereoscope	£40
LEADER 189A 2 channel millivoltmeter	£45
LEADER MEGURO ETC automatic distortion meters	from £75

TEST EQUIPMENT

ANRITSU MS65A 2 GHz error detector	£500
ANRITSU MS99C1 vocodermeter (based new with manuals)	£400
AVO 215-L2 AC/DC breakdown ionisation tester	£400
AVO CT160 valve tester	£150
BALL EFRATROM MRT-H rubidium frequency standard	£3,500
BIRD 8329 100W 30dB attenuator	£400
BIRD 8323 100W 30dB attenuator	£200

BRADLEY 192 oscilloscope calibrator	£300
BRUEL & KJAER 2515 vibration analyser (AS NEW)	£3,000
DATRON 1065 autocal digital multimeter	£400
EIP 548A 10 Hz-2.6 GHz microwave counter	£2,000
EIP 331 12.5 GHz autohet microwave counter	£350
FARNELL PDA3502A dual power supply 0-35V 2 amp	£175
FARNELL RB100305 electronic load	£400
FARNELL SCG50 synthesised clock generator	£100
FARNELL TSV70 power supply 0-70V 0-10 amp	£250
FARNELL LT30-2 20-30V 2 amp	£150
FARNELL LT30-5 0-30V 5 amp	£145
FARNELL D100 0-100V 1 amp	£100
FLUKE 855A digital multimeter	£700
FLUKE 8506A thermal RMS multimeter	£900
FLUKE 5440B direct volts calibrator	£4,000
FLUKE 5205A precision power amp	£2,000
FLUKE 5200A AC calibrator	£1,500
FLUKE 3330B prog constant current/voltage calibrator	£300
HP 59403A HP-IB/Common carrier interface	£125
HP 59401A bus system analyser	£200
HP 11710A 50 MHz system analyser	£200
HP 11665B 150 MHz-18 GHz modulator	£150
HP 11582A attenuator test DC-18 GHz	£500
HP 8970A noise figure meter	£2,000
HP 8750A storage normaliser	£300
HP 8508A vector voltmeter	£3,250
HP 8477A RF power meter calibrator	£200
HP 4219A DC power supply 0-40V/0.5 amp	£185
HP 6263A DC power supply 0-20V/0.10 amp	£250
HP 5350B 10 Hz-20 GHz high performance microwave counter	£3,500
HP 5345A 1.5 MHz-26.5 GHz counter/5355A/5356A+B sensors	£3,000
HP 5342A 500 MHz-18 GHz microwave frequency meter	from £500
HP 5335A universal systems counter high stability OPT	£600
HP 5334A universal systems counter	£400
HP 5328A universal counter/DVM OPT011/021/041	£300
HP 5180A waveform recorder	£600
HP 5087A distribution amplifier (new)	£500
HP 5004A signature analyser £150 HP 5005A signature multimeter	£1,200
HP 4954A protocol analyser + HP 18135A pod	£1,200
HP 4951B protocol analyser + HP 18179A interface	£325
HP 3707B telephone line analyser	£500
HP 3761A error detector	£200
HP 3754A selective level meter	£300
HP 3702B/3705 IF/BB Receiver +3710A/3716A IF/BB transmitter	£400
HP 3488A switch controller	£400
HP 4473A matrix switch	£100
HP 4440A relay mux	£100
HP 3586C 50 Hz-32.5 MHz selective level meter	£750
HP 3581A 15 Hz-50 KHz selective voltmeters as new	£500
HP 3468A 3.5 digit multimeter/auto cal (LCD)	£400
HP 3466A 4.5 digit autoranging multimeter	£200
HP 3437A 3.5 digit high speed system voltmeter	£200
HP 1645 data error analyser	£195
HP 436A RF power meters	£650
HP 435B/4841A/4844A/11708A 10 MHz-18 GHz (new/HP case/manuals)	£1,300
HP 435A/4842A/H 100 KHz-4.2 GHz RF power meter	£500

HP 400E 10 Hz-10 MHz AC voltmeter	£95
HP 337A distortion measurement set	£1,200
HP 333A distortion analyser	£295
KEHO DP1 1 Hz-100 KHz phase meter (new)	£100
LINPLEX FI-2 HF receiver	£195
MARCONI 6593A VSWR indicator	£200
MARCONI 6960B/6910 RF power meter 10 MHz-20 GHz	£950
MARCONI 2945 communication service monitor + ETAC/Sbattery/GP-IB	£4,800
MARCONI 2955B RF communications test set	£3,500
MARCONI TF2871 data communications monitor	£500
MARCONI TF2810 true RMS voltmeter	£600
MARCONI TF2306 programmable interface unit	£200
MARCONI TF2305 mod meter 50 KHz-2.3 GHz	£1,000
MARCONI TF938 audio power meter	£150
NARDA 3044B-20 3.7 GHz-8.3 GHz 20dB directional coupler (new)	£150
NARDA 3004-10 4-10 GHz 10dB directional coupler	£100
RACAL DANA 9919 10 Hz-1100 MHz frequency counter	£195
RACAL DANA 9918 10 Hz-560 MHz 9 digit counter	£100
RACAL DANA 9916 10 Hz-520 MHz frequency counter	£100
RACAL DANA 9914 10 Hz-200 MHz frequency counter	£75
RACAL DANA 9904M 50 MHz universal counter timer	£75
RACAL DANA 9301A true RMS RF millivoltmeter	£400
RACAL DANA 9302A true RMS RF millivoltmeter 10 KHz to 1.5 GHz	£475
RACAL DANA 9300B RMS voltmeter (new)	£250
RACAL DANA 9300M RMS voltmeter	£200
RACAL 9343M LCR disabridge	£395
RACAL 9008 1.5 MHz-2000 MHz automatic modulation meter	£300
RACAL DANA 1992 10 Hz-1300 MHz nanosecond counter	£595
RACAL DANA 1991 10 Hz-160 MHz universal counter timer 9 digit	£195
RACAL DANA 4000 microprocessing digital voltmeter	£250
RF MICROSYSTEMS INC AN/TRC-176 VHF/UHF KAL filters	£400
ROHDES & SCHWARTZ, GA082 FSK analyser	£300
ROHDES & SCHWARTZ URE 10 Hz-20 MHz RMS voltmeter	£400
ROHDES & SCHWARTZ URV35 RF voltmeter	£750
RYCOM 4040 selective level meter	£250
SAYROSA AMH 1.5 MHz-2 GHz automatic modulation meters	£175
SCHLUMBERGER 7702 digital transmission analyser (new)	£500
TEKTRONIX A6902A isolator	£450
TEKTRONIX 1141SPG11/TSG11 pal video generator	£750
TEKTRONIX 321A vector scopes	£300
TEKTRONIX 145 pal gen lock test signal generator	£750
WAVETEK 1018A log lin RF peak power meter DC-26 GHz	£600
WAYNE KERR AMH255 auto modulation meter	£450
WALLIS T100 100 Kv insulation tester	£1000
W & G DLAS data line analyser	£90A
W & G DLH3 data line test set	£90A
W & G SPH19 50 Hz-25 MHz level measuring set	£500
W & G SPH31 200 Hz-420 KHz level meter	£750

86 Bishopgate Street, Leeds LS1 4BB Tel: (+44) 113 2435649 Fax: (+44) 113 2426881
 ALL EQUIPMENT SUPPLIED WITH 30 DAYS WARRANTY • PRICES PLUS CARRIAGE AND VAT Visit M&B Radio's Website <http://www.mb-radio.co.uk> e-mail info@mb-radio.co.uk

CIRCLE NO.129 ON REPLY CARD

The Headphone Amplifier Box

Balanced or unbalanced microphone or line input to headphone output

Professional portable units operating from an internal PP3 battery or external mains adaptor



- * Precision transformerless balanced input
- * Bridged headphones output drive
- * Sensitivity selectable over a wide range of input levels
- * Low noise and distortion
- * High common mode rejection
- * Loop through facility
- * Extensive RFI protection

The Balance Box (precision mic/line amplifier) –
 The Phantom Power Box – The OneStop DIN rail mounting radio frequency interference filter and voltage transient protector for voltage and current loop process signal lines

Conford Electronics Conford Liphook Hants GU30 7QW
 Information line 01428 751469 Fax 751223
 E-mail contact@confordelec.co.uk
 Web <http://www.confordelec.co.uk/catalogue/>

CIRCLE NO.130 ON REPLY CARD

Why Settle for AM when you can afford High Quality FM!

Transmitters & Transceivers

418, 433, 868 & 916MHz

Prices from £5.00

Made in UK

We can offer the lowest prices on high quality FM Radio Data Modules both In the UK and overseas!
 Our qualified engineers offer full technical support from simple advice to system design & integration.

For a free catalogue, wall chart or quotation just e-mail sales@radtec.demon.co.uk, alternatively fax or telephone quoting ref: WWRMI




Telephone +44(0)1992 576107
 Fax +44(0)1992 561994
<http://www.radio-tech.co.uk>

Radio-Tech Limited

Your official Radiometrix Distributor

CIRCLE NO.131 ON REPLY CARD

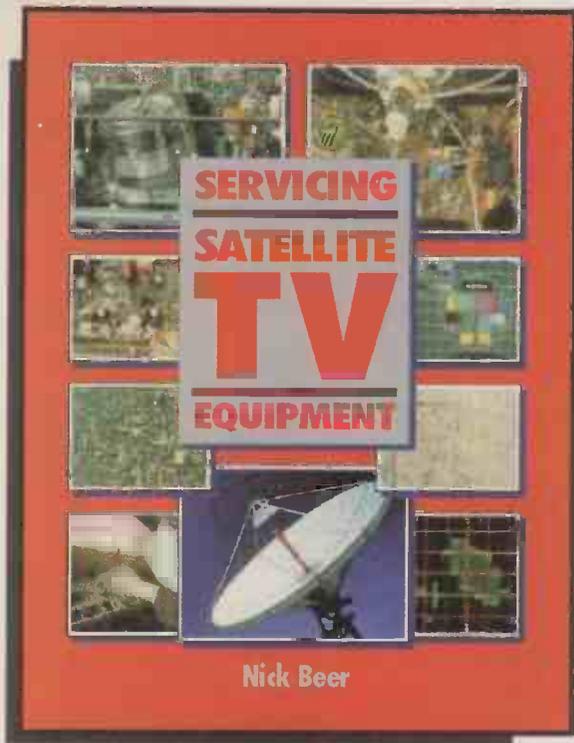

Written by Nick Beer for service engineers, enthusiasts and students

This is the definitive practical guide to fault-finding, troubleshooting and servicing satellite television equipment, both indoors and outdoors. It will take you through all areas of satellite television system servicing from the simplest fixed dish to fully motorised systems. From PAL to Mac to MPEG all contemporary systems are covered.

Satellite TV systems have been installed in a wide variety of locations, using a bewildering range of equipment. That equipment is beginning to need maintenance and repair. To cope with the volume and variety of work, Nick Beer has written the first guide to satellite TV that concentrates on what to look for and what to do when it goes wrong. This book is up to date and crammed with real-life experience - not theoretical data or manufacturer's ideal specs.

Nick Beer has already written the best-selling *Servicing Audio and Hi-fi Equipment* and is a technical correspondent for many UK and international journals such as *Television*. He also works as an engineer and teaches satellite servicing to technicians.

- A practical guide to a new and important area for service engineers
- Covers indoor and outdoor equipment
- Written by an experienced author, teacher and engineer

Servicing Satellite TV Equipment

Contents

Introduction ● Tools and test equipment ● Dishes and feeds ● De-polarisers and low noise blocks ● Distribution systems ● Actuators and positioners ● Tuners and tuning systems ● Video processing circuits ● Audio processing circuits ● Power supply circuits ● System control circuits ● RF amplifiers and modulators ● Decoders and descramblers ● MPEG Digital Television System ● Repair techniques ● Appendix ● Reference data ● Appendix 2; Safety BEAB and BS415:1990 ● Appendix 3; useful addresses.

This 224 page hard backed book contains 50 photographs and 50 line illustrations – price £34.99

** Price includes delivery and package **

Return to Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following title:

Servicing Satellite TV Equipment

Total _____

Name _____

Address _____

Postcode _____ Telephone _____

Method of payment (*please circle*)

Access/Mastercard/Visa/Cheque/PO

Cheques should be made payable to Reed Business Information

Credit card no. _____

Card expiry date _____

Signed _____

Please allow up to 28 days for delivery

WEB DIRECTIONS

To reserve your web site space contact Joannah Cox

Tel: 0181 6523620 Fax: 0181 6528938

AQUILA VISION

<http://www.aquila-vision.co.uk>

Aquila Vision specialises in supplying and supporting Embedded Microprocessor Development products from PICs to DSPs. We also stock robotics boards, Linux and general interest CD-ROM's.



ALCATEL COMPONENTS

[@alcatel.de](http://www.components)

AMBAR COMPONENTS

<http://www.ambar.memec.com>

Ambar Components, distributor for Cirrus Logic, Crystal, Cypress, Dense-Pac, Dynachip, Fairchild, IMI, Micro Linear, Mitel incorporating GEC Plessey Semiconductor, PowerDns, QLogic, Scenix, SST and Summit.

APPLE RECRUITMENT

<http://www.applerec.u-net.com/>

BF COMPONENTS

<http://www.bfcomponents.co.uk>

Visit the site for Milgray-Bell in the U.K. Full e-mail facility with instant links to Bell and Milgray web sites for stock interrogation.

CAMBRIDGE MICRO PROCESSOR SYSTEMS LTD

<http://www.cms.uk.com>

COOKE INTERNATIONAL

<http://www.cooke-int.com>
e-mail: info@cooke-int.com

Stockists of Quality Used Electronic Test Instruments and Operating & Service Manuals.



CROWN HILL ASSOCIATES LTD

<http://www.crownhill.co.uk>

Crownhill supply low cost development tools for use with Micro-Controllers and Smart Cards. Products include Smart Card development tools, Smart cards, Micro Development tools and Bespoke Design Services.

CONCEPT ELECTRONICS

<http://www.conceptkey.co.uk>

Concept Keyboards are specialists in the design and manufacture of customer specified membrane panels and keyboards, and electronic design. Concept's membrane manufacture is supported by a full electronic production facility to provide a complete turnkey keyboard and electronics service, fully accredited to ISO9001.

DISPLAY ELECTRONICS

<http://www.distel.co.uk>


FELLER UK

<http://www.feller-at.com>

Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards

ELECTRONICS WEEKLY HYPERACTIVE


<http://www.electronicweekly.co.uk/>

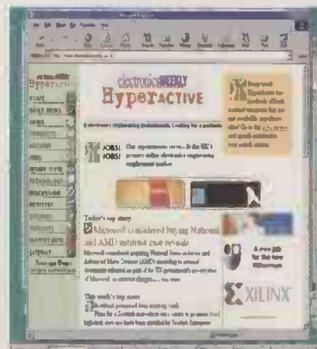

ECM SELECTION

<http://www.ecmsel.co.uk>

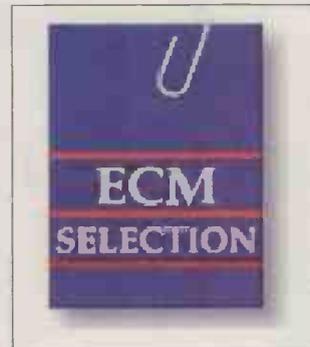
For the pick of the UK's Top High-Tech Software and Hardware career opportunities - from fresh Grad/PhD to Senior Engineer/Manager -- £22,000 - £70,000



EQUINOX TECHNOLOGIES UK LTD

<http://www.equinox-tech.com>

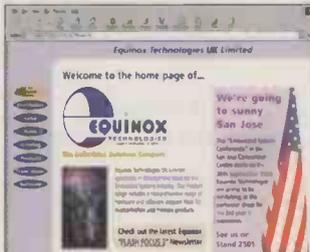Equinox Technologies UK Ltd., specialise in development tools for the embedded microcontroller market.



FLASH DESIGNS LTD

<http://www.flash.co.uk>

Portable Easy-ICE - The world's fastest, Lowest Cost, Real-time Emulator + Starter kits from £319 with unique ICE connection interface for ATMEL AT89S/C, AVR AT90S,103/603, MCS51, Dallas 80C320, Hitachi H8 + ISP programmers + 'C' Compilers

LOW POWER RADIO SOLUTIONS

<http://www.lprs.co.uk>

LPRS markets low power radio transmitters, receivers and transceiver modules manufactured by ourselves, Radiometrix, Circuit Designs, RDT and Micrel. Applications for telemetry, video and remote control.

MICRO CALL

<http://www.microcall.memec.com>

Micro Call is a distributor for the following Galleo, IDT (Integrated Device Technology), Lattice, Level 1, Linear Technology, Memec Design Service, NPC, Siliconians, Silicon laboratories, WSI, Xilinx and Xicor.

M.K. CONSULTANTS (UK) LTD

<http://www.mkconsultants.co.uk>

A global supplier of low power modules designed and manufactured by MK in the UK. Nobody beats our prices. That's the MK price challenge.

M&B RADIO

<http://www.mb-radio.co.uk>

MITRONICS

<http://www.mitronics.com>


Visit Mitronics, the leading stocking distributor of obsolete and difficult to find Motorola parts. We carry electronic components, integrated circuits, and semiconductors

NATIONAL INSTRUMENTS

<http://www.natinst.com/uk>

NEWNES - BOOKS FOR THE ELECTRONICS WORLD

<http://www.newnespress.com>

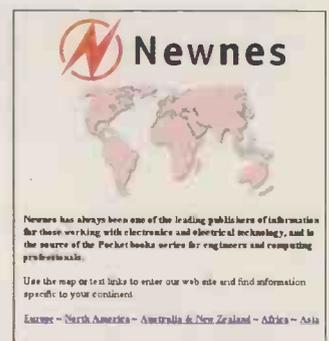

Over 300 books and information packages for those working with electronics and engineering technology. Visit our site for a free catalogue and downloads

OMEG POTENTIOMETERS

<http://www.omeg.co.uk>

Omeg 16mm and 20mm potentiometers and switched potentiometers with conductive polymer tracks. Web site has full product details, latest news, company contacts, stockists and distributors.

PCA:PHILIP COLLINS & ASSOCIATES PTY. LTD

<http://www.pca.cc>

PCA manufactures Radphone 2000DX remote control systems for shortwave broadcasters and government agencies wanting worldwide control of communications receivers and transceivers from any tone phone.

QUILLER ELECTRONICS

<http://www.quiller.com>

100+ pages of detailed technical information on Schrack Relays, MEC Switches, Hirose Connections.

RALFE ELECTRONICS


professional test & measurement
www.ralfe-electronics.co.uk



SWIFT EUROTECH

<http://www.swiftdesigns.co.uk>

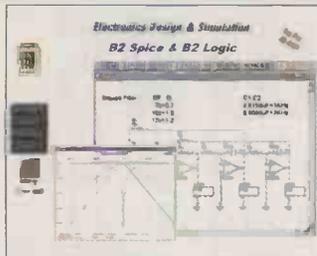EDWin NC - Professional EDA software at 90% discount! Integrated schematics, PCB layout and simulation. Plus CAMtastic! CAM software and netlist translators for most EDA systems.



RD RESEARCH

<http://www.looking.co.uk/spice>

Analogue and digital SPICE modelling software. Full details available on this site. Available on a 30 day evaluation basis.

SEETRAX LIMITED

<http://www.ukonline.co.uk/seetrax>

SUPRA AUDIO CABLES

<http://www.jenving.se>

Jenving Technology AB is the manufacturer of Supra Audio Cables. OEM productions are also accepted.



SYSONICS SYSTEMS LTD

<http://www.sysonic.com>

THOSE ENGINEERS LTD

<http://www.spiceage.com>

TRIDENT MICROSYSTEMS LTD

<http://www.trident-uk.co.uk>

Visit the Trident website for details and datasheets on their entire LCD and printer product range. Download data and subscribe for our regularly updated newsletter.

TRUMETER

<http://www.trueimeter.com>

TOTAL FERQUENCY CONTROL

<http://www.tfc.co.uk>

TRANSONICS

<http://www.transonic.com>

VANN DRAPER ELECTRONICS LTD

<http://www.vanndraper.co.uk>

Test equipment from Grundig, Kenwood, Hitachi, Fluke, Avo, Glassman, Advance in a comprehensive site including oscilloscopes, multimeters, power supplies, generators, counters, soldering, digital tv etc.

VUTRAX PCB DESIGN SOFTWARE

<http://www.vutrax.co.uk>

VUTRAX electronic schematic and pcb design system for Windows 95, 98 and NT. Limited Capacity FREE version downloads available, all upgradeable to various customised levels.

VECTOR BUSINESS COMMUNICATIONS

<http://www.vectore.co.uk/vector/>

Pressrelations, advertising web sites, direct marketing, corporate literature, exhibitions and events. Marketing communications for the electronics industry in the UK and across Europe.

WOOD & DOUGLAS

<http://www.woodanddouglas.co.uk>

Wood & Douglas Ltd is the leading independent British designer and manufacturer of quality radio products for International telemetry, data, voice & video wireless communications.

WINRADIO COMMUNICATIONS

<http://www.broadercasting.com>

XILINX

<http://www.xilinx.com/>

Xilinx is the world's largest supplier of programmable logic solutions producing industry leading device architecture and world class design software.

WEB DIRECTIONS

Put your web address in front of 21,000 Electronics fanatics. Electronics World acknowledges your companys need to promote your web site, which is why we are now dedicating page's in every issue to WEB ADDRESSES.

This gives our readers the opportunity to look up your companys name, to find your web address and to browse the magazine page to find new sites.

We also understand that cost is an important factor, as web sites are an added drain on budgets. I am sure you will agree these rates make all the difference

FOR 12 ISSUES:

Lineage only will cost £150 for a full year just £12..50 per month.

This includes your companys name, web address and a 25 word description.

Lineage with colour screen shot will cost £350 for a full year just £29.17 per month.

This will include the above plus a 3cm screen shot of your site, which we can produce if required.

To take up this offer or for more information ring Joannah Cox on 0181 652 3620 or fax on 0181 652 8938.

E-mail: joannah.cox@rbi.co.uk

Company Name	Web address



HATELY ANTENNA TECHNOLOGY

1 Kenfield Place, ABERDEEN AB15 7UW
Tel/Fax: +44 1224 316 004
e mail:- m.hately@talk21.com

CROSSED FIELD ANTENNA

Progress on the commercial application of the Crossed Field Antenna has been significant since our last announcement. Three milestones have been passed:-

1. At the NAB '99 Conference and Exhibition in Las Vegas during April a major new technical paper concerning the broadcasting use of the Ground Plane CFA has been given. The title was FOUR EGYPTIAN MW BROADCAST CROSSED-FIELD-ANTENNAS authors Kabbary, Khattab, Stewart, Hately and Fayoumi. The work of the Egyptian Radio and TV Union is presented in this presentation. At the exhibition arrangements to manufacture and supply broadcast antennas for Medium Wave throughout the USA and S. America were given, supplementing the schemes for Europe and the Middle East already in existence from our subsidiary in Egypt.

2. The Isle of Man will soon be the site of the first UK high power CFA for broadcasting. The IOM Government has announced that the Isle of Man International Broadcasting Company Ltd has been selected to be allocated the licence for the 279 kHz Long Wave broadcasting station. This company's application was attractive because of the minimal visual impact of the CFA only 30 metres high instead of the rival submissions using conventional masts of 260 metres height. Additionally the lower voltages and almost zero induction field of the CFA provides enhanced safety and minimal EMC problems.

3. Since October '98 there have been wide-ranging discussions on the Internet Magazine "Antennex". This can be seen at <http://www.antennex.com>.

Payment of a modest subscription gives the user access to archive pages which include constructional details for a small size GP CFA for the Amateur 80 Metre Band. Many constructors are reporting success and a widening understanding of the CFA is rapidly increasing throughout the professional and experimenter community.

Fax or e-mail for greater details of specific enquiries.

CIRCLE NO.132 ON REPLY CARD

PHONE 0181 684 1166
FAX 0181 684 3056
LANGREX SUPPLIES LTD
DISTRIBUTORS OF ELECTRONIC VALVES
TUBES AND SEMICONDUCTORS AND I.C.S.
1 MAYO ROAD • CROYDON • SURREY CR0 2QP
24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS
email: langrex@aol.com


	£ p						
AZ31	6.00	KT66 Special	20.00	5Z4G	6.00	6UBA	1.50
CL33	10.00	KT88 Special	20.00	5Z4GT	3.00	6V6G	8.00
E88CC	8.50	KT90	17.50	6A05	2.00	6V6GT	5.00
E180F	3.50	N78	8.00	6AR5	20.00	6X4	3.00
E810F	20.00	OA2	3.00	6AS7G	7.50	6X5GT	3.00
EABCB80	2.00	OB2	3.00	6AU5GT	4.00	12AT7	3.00
EB91	1.50	OC3	3.00	6AU6	2.00	12AU7	3.50
EBF80	1.50	OD3	3.00	6AW8A	4.00	12AX7	5.00
EBF89	1.50	PCF80	2.00	6B4G	22.00	12AX7A	7.50
EBL31	15.00	PCL82	2.00	6BA6	1.50	12AX7V	6.00
ECC33	12.00	PCL85/805	2.50	6BE6	1.50	12BA6	2.00
ECC35	12.00	PCL86	2.50	6BH6	2.00	12BE6	2.00
ECC81	3.00	PD500	6.00	6BQ7A	2.00	12BH7/1	10.00
ECC82	3.50	PL38	3.00	6BR7	4.00	12BY7A	7.00
ECC83	3.00	PL81	2.00	6BR8	4.00	12DW7	15.00
ECC85	3.50	PL504	3.00	6BW6	4.00	12E1	10.00
ECC88	6.00	PL508	3.00	6BW7	3.00	13E1	85.00
ECC88B	15.00	PL509/519	10.00	6BZ6	3.00	5725	85.00
ECCF80	1.50	PL802	4.00	6C4	2.00	805	45.00
ECH35	3.50	PY500A	3.00	6CB6A	3.00	807	7.50
ECH42	3.50	PY800/801	1.50	6DC6G	5.00	811A	25.00
ECH81	3.50	QOV02-6	12.00	6CL6	3.00	812A	55.00
ECL32	3.50	QOV03-10	5.00	6CG7	7.50	813	27.50
ECL86	3.50	QOV03-20A	10.00	6CH6	3.00	833A	85.00
ECL800	25.00	QOV06-40A	12.00	6CW4	6.00	866A	20.00
EF37A	3.50	U19	8.00	6D05	17.50	872A	30.00
EF39	2.75	UABC80	1.50	6D06B	10.00	931A	25.00
EF40	4.00	UCH42	5.50	6F6G	6.00	2050A	12.50
EF86	10.00	UCL82	2.00	6F07	7.50	5751	6.00
EF91	2.00	UCL83	2.00	6GK6	4.00	5763	6.00
EF183/4	2.00	UF89	4.00	6J5G	6.00	5814A	5.00
EL33	15.00	UL41	12.00	6J5M	4.00	5842	12.00
EL34	5.00	UL84	3.00	6J7	3.00	6072A	6.00
EL34G	5.00	UY41	4.00	6J8A	27.50	6080	6.00
EL36	5.00	UY85	2.00	6J8EC	27.50	6146B	15.00
EL41	3.50	VR105/30	3.00	6J8SC	27.50	6201	8.50
EL84	2.25	VR150/30	3.00	6KGGT	4.00	6336A	35.00
EL95	2.00	Z759	10.00	6L6G	15.00	6550A	25.00
EL360	15.00	Z803U	15.00	6L6GC	15.00	6883B	15.00
EL509/519	7.50	2D21	3.50	6L6WGB	10.00	7025	7.50
EW34	15.00	3B28	12.00	6O7	3.00	7027A	25.00
EW814/7	4.00	4CX250B	45.00	6SA7	3.00	7199	15.00
EN91	7.50	5R4GY	7.50	6SC7	3.00	7986	15.00
EZ80/81	5.00	5U4G	10.00	6S7	3.00	7581A	15.00
GZ32	8.50	5U4G	10.00	6S7J	3.00	7586	15.00
GZ33/37	6.00	5V4G	4.00	6SK7	7.50	7587	20.00
KT61	15.00	5Y3GT	2.50	6SL7GT	5.00		
		5Z3	5.00	6SN7GT	5.00		

OPEN TO CALLERS MON-FRI 9AM-4PM. CLOSED SATURDAY
This is a selection from our stock of over 6,000 types. Please enquire for types not listed. Obsolete items are our speciality. Valves are new mainly original British or American brands. Terms CWO/mln order £10 for credit cards.
P&P 1-3 valves £2.00 4-5 valves £3.00
Add 17.5% VAT to total including P&P.

CIRCLE NO.133 ON REPLY CARD

PPM5

20 PIN DUAL IN LINE

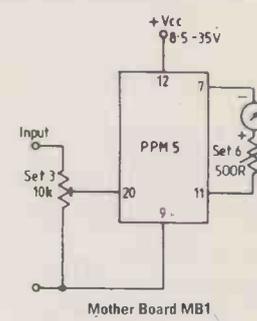

Consumption 3mA. Fully meets BS5428-9

- ★ PPM10 In-Vision PPM and Chart Recorder ★
- ★ Advanced Active Aerial 4kHz-30MHz ★ Stabilizer frequency shift units for howl reduction ★ 10 Outlet Distribution Amplifier ★ Stereo Variable Emphasis Limiter ★ PPM9, PPM5 hybrid and PPM8 IEC/DIN -50/+6dB drives and movements ★ Broadcast Stereo Coders ★ Broadcast Monitor Receiver 150kHz-30MHz ★

SURREY ELECTRONICS LTD

The Forge, Lucks Green, Cranleigh GU6 7BG
Telephone: 01483 275997 Fax: 01483 276477

WATCH SLIDES ON TV MAKE VIDEOS OF YOUR SLIDES DIGITISE YOUR SLIDES

(Using a video capture card)

"Liesegang diatv" automatic slide viewer with built-in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use £91.91 + VAT = £108.00
Board cameras all with 512 x 582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts.

They all require a power supply of between 10 and 12v DC 150mA.
47MIR size 60 x 36 x 27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye) £50.00 + VAT = £58.75
40MP size 39 x 38 x 28mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole £50.00 + VAT = £58.75
40MC size 39 x 38 x 27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses £38.79 + VAT = £45.58

economy C mount lenses all fixed focus and fixed iris.
VSL1220F 12mm F1.6 12 x 15 degrees viewing angle £15.97 + VAT = £18.76
VSL4022F 4mm F1.22 63 x 47 degrees viewing angle £17.65 + VAT = £20.74
VSL6022F 6mm F1.22 42 x 32 degrees viewing angle £19.05 + VAT = £22.38
VSL8020F 8mm F1.22 32 x 24 degrees viewing angle £19.90 + VAT = £23.38

Better quality C Mount lenses
VSL1614F 16mm F1.6 30 x 24 degrees viewing angle £26.43 + VAT £31.06
VWL813M 8mm F1.3 with Iris 56 x 42 degrees viewing angle £77.45 + VAT = £91.00
Blue and silver recordable CD ROM bulk £0.766 + VAT = £0.90
With jewel case £1.00 + VAT = £1.18
PKE103A 130v diode £0.99p + VAT = £1.15 20 for £13.00 + VAT = £15.28
RC300 Philips universal remote control.5 for £24.45 + VAT (£4.69 + VAT each) = £27.55
Konig Ultrasonic remote control clearout, limited quantities. Quantity left in brackets:
US8207 (15), US8209 (5), US8220 (4), US8224 (5), US8225 (2), US8232 (3),
US8233 (2), US8239 (8), US8260 (1), US8264 (124), US8265 (116), US8302 (2),
US8306 (1), US8309 (1), US8406 (1), US8513 (21), US8514 (40), US8516 (19),
US8519 (2), US8535 (82), US8578 (182)

..... £5.50 + VAT each, £22.00 + VAT for 5, £85.00 + VAT for 25.
1206 surface mount resistors E12 values 10 ohm to 1m ohm
..... 100 of 1 value £1.00 + VAT, 1,000 of 1 value £5.00 + VAT

Please add £1.66 + VAT = £1.95 postage & packing per order

JPG ELECTRONICS

276-278 Chatsworth Road, Chesterfield S40 2BH
Tel: 01246 211202 Fax: 01246 550905
Callers welcome 9.30am to 5.30pm Monday to Saturday

CIRCLE NO.134 ON REPLY CARD

Horse play?

The letter from Mr Cahner in the April 1999 issue of *Electronics World* – if it was not an April Fool – is easily answered because third-order Butterworth designs were indeed very common in the early seventies, in both passive and active form.

The problem, however, is not how to realise particular filter shapes with passive or active filters, but, how the sounds from the two drive units add up in a 3D acoustic environment.

In general, the output from a drive unit mounted in a box is not flat, so there will always be a requirement for some equalisation as well as the 'crossover' function of the filters.

The outputs of high and low pass third-order Butterworth filter sections are in quadrature – i.e. 90° phase difference. As the listener moves off axis, in one direction the summed output at crossover will rise and in the opposite direction there will be a dip. This led to some designs with the tweeter below the woofer in order to point the best listening axis upwards on floor standing models.

The desire to eliminate this effect fuelled a move towards 'in phase' squared Butterworth, or Linkwitz-Riley, crossover design in the late seventies. Later efforts went into getting the HF and LF voice coils co-incident rather than just in the same plane.

E. Cecconi
Principal Electroacoustics
Engineer
KEF Audio (UK) Ltd.


The transient response plot of Jim Cahner's crossover network shown here explains why the circuit is not 'perfect' – whatever that means.

To find out why the crossover circuit is not perfect, one should run the transient response simulation to see that the sum of the low and high-pass section is far from the step response at the input – apart from being 6dB down.

In fact it is more like a notch-filter response, although no notch is seen in the frequency response magnitude.

The phase diagram shows part of the story, but the envelope delay would show even more.

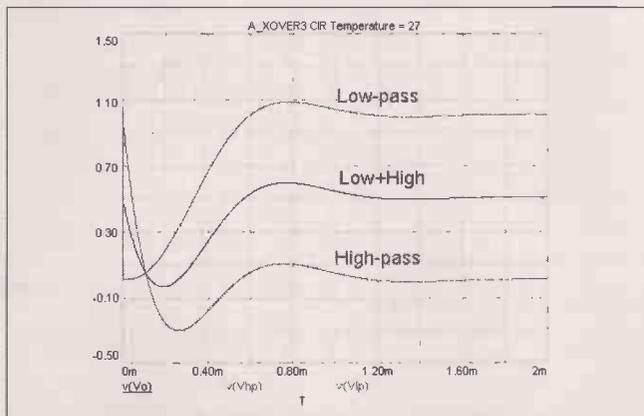An ideal transient would have a flat envelope delay, meaning that the phase is a linear function of frequency – the envelope delay is a phase-derivative *versus* frequency.



Doing the maths, you can see that the sum of the two filters,

$$H(s) = 0.5 \times \frac{s^3 + w^3}{s^3 + As^2 + Bs + w^3}$$

and for $H(s)=0.5$, the first and the second power-of-s terms are missing from the numerator.

Instead of using Butterworth tuning, you could try Bessel, or linear-phase, tuning and shift one of the filters in frequency to minimise the magnitude wiggling around the crossover point.

The result would be much better, but still not perfect

Erik Margan
Ljubljana
Slovenija

Newer logic

Some readers will have read my article 'New Logic' in the February 1999 issue of *Electronics World*. The article was on the subject of Boolean algebra.

If you have discovered the significance of this article you might like to read the second part of it. This part concludes my demonstration that Boolean algebra based on the exclusive-OR in place of the more familiar inclusive-OR is actually quite a useful and practical addition to the stock in trade of the digital circuits design engineer.

I have gone to some trouble to make the articles readable. I have now revised my web site at: <http://users.senet.com.au/~dwsmith/> to include an html version of the second part of the 'New Logic' article.

Readers might like to take a look at this site. I would appreciate any feedback via my e-mail link which will be found on some of the pages, from serious readers, particularly if

they have read the New Logic article.

You might find that html, in one of the up to date internet browsers, is a very practical way of reading an article. Html documents can have hyperlinks that make navigation easy.

The whole article can appear on one scrollable page with diagrams seamlessly incorporated.

David Warren-Smith
Elizabeth
South Australia

Phase sensitive

I was interested to read the article entitled 'The phase-sensitive detector' in the April issue of *Electronics World*. However I note that the reference information has accidentally been omitted.

The omitted reference is 'Lock-in

Amplifiers: Principles and Applications' by M L Meade, 232 pp, published by Peter Peregrinus, 1983.

The book is out of print but copies are held in many technical libraries. I'm sure there are some readers who would appreciate this information.

Fraser Robertson
Open University

Flash in the pan

Regarding the circuit idea '4-bit flash makes 16 bit flash a-to-d' in the May issue, for this approach to work you have to make the assumption that the 4-bit a-to-d converter has perfect 16-bit linearity – which it will not.

Any linearity errors will show up as errors on the d-to-a converters, which must also be linear to 16 bits.

Also, the resistors used would have to be accurate to 0.001% to retain 16-bit accuracy.

If you are lucky you may get 5 bits of performance out of this design. If it was this easy then both IC manufacturers and companies like ours would have done this long ago

I seem to remember a similar design was published a few years ago that made the same mistake – the author references Dec 91, but I think there was a more recent article than that.

Alan Tong
Pico Technology
Cambridge

Heater debate

John Norman – Letters p. 286 April issue – was a little naive in relying only upon steady-state conditions in recommending the use of a 2µF capacitor to feed 0.15A valve heaters from the 230V 50Hz main supply.


In the worst case, when switching on when at a peak instant of the supply voltage, approximately 325V will suddenly be applied to the heater chain.

If feeding only one 12V 0.15A filament, this would cause a peak current of over 3.8A – though admittedly, the pulse has a time constant of only about 170µs

Why not use an inductor, instead of a capacitor, I hear some of you ask? Another problem arises here, but now the worst case is switching on as the mains voltage goes through zero.

These were 'heated' topics of discussion when I was a lad.

Bob Pearson
Bourne Lincs

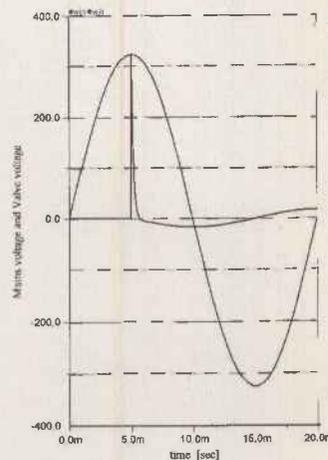

Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!



TV SOUND & VIDEO TUNER
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into a host of video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tunable 'off air' UHF colour television channels. TELEBOX MB covers virtually all UHF colour frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

TELEBOX ST for composite video input type monitors £36.95
TELEBOX STL as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
For overseas PAL versions state 5.5 or 6 MHz sound specification.
*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Teleboxes, code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite TV pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full software control via a simple 2 wire link to any IBM type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate.
BRAND NEW - Order as MY00. Only £49.95 code (B)

FLOPPY DISK DRIVES 2 1/2" - 14"

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call for over 2000 unlisted drives for spares or repair.

- 3 1/2" Panasonic JU363/4 720K or equivalent RFE £24.95(B)
- 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only £25.95(B)
- 3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop £18.95(B)
- 5 1/4" Teac FD-55GFR 1.2 Meg (for IBM pcs) RFE £18.95(B)
- 5 1/4" Teac FD-55F-03-U 720K 40/80 (for BBC's etc) RFE £22.95(B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 360K £29.95(B)
- Table top case with integral PSU for HH 5 1/4" Floppy or HD £29.95(B)
- 8" Shugart 800/801 8" SS refurbished & tested £210.00(E)
- 8" Shugart 810 8" SS HH Brand New £195.00(E)
- 8" Shugart 851 8" double sided refurbished & tested £260.00(E)
- 8" Mitsubishi M2894-63 double sided NEW £295.00(E)
- 8" Mitsubishi M2896-63-02U DS slimline NEW £295.00(E)
- Dual 8" cased drives with integral power supply 2 Mb £499.00(E)

HARD DISK DRIVES

- 2 1/2" TOSHIBA (19 mm H) MK2101MAN 2.16 Gb. New £199.00
 - 2 1/2" TOSH (12.5 mm H) MK1020MAV 1.1 Gb laptop. New £115.00
 - 2 1/2" to 3 1/2" conversion kit for PC's, complete with connectors £12.95
 - 3 1/2" FUJI FK-309-26 20mb MFM I/F RFE £59.95
 - 3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE £59.95
 - 3 1/2" CONNER CP3044 40mb IDE I/F (or equiv.) RFE £69.00
 - 3 1/2" RODIME R03057S 45mb SCSI I/F (Mac & Acom) £69.00
 - 3 1/2" QUANTUM 40S Prodrive 42mb SCSI I/F. New RFE £49.00
 - 3 1/2" WESTERN DIGITAL 850mb IDE I/F New £185.00
 - 5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE £49.95
 - 5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb £69.95
 - 5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested £69.95
 - 5 1/4" HP 97548 850 Mb SCSI RFE tested £99.00
 - 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
 - 5 1/4" NEC D2246 85 Mb SMD interface. New £199.00
 - 5 1/4" FUJITSU M2322K 160Mb SMD I/F RFE tested £195.00
 - 5 1/4" FUJITSU M2392K 2 Gb SMD I/F RFE tested £345.00
- Many other drives in stock - Shipping on all drives is code (D)

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

- MITS. FA3445ETKL 14" Industrial spec SVGA monitors £245
- 1kW to 400 kw - 400 Hz 3 phase power sources - ex stock £90A
- IBM 8230 Type 1, Token ring base unit driver £760
- Wayne Kerr RA200 Audio frequency response analyser £2500
- BM 53F5501 Token Ring ICS 20 port lobe modules £750
- BM MAU Token ring distribution panel 8228-23-5050N £95
- AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE £550
- ALLGON 8360, 11805-1880 MHz hybrid power combiners £250
- Trend DSA 274 Data Analyser with G703(2M) 64 i/o £90A
- Marconi 6310 Programmable 2 to 22 GHz sweep generator £6500
- Marconi 2022C 10KHz-1GHz RF signal generator £1550
- Marconi 2030 opt 3 10KHz-1.3 GHz signal generator, New £5150
- HP1650B Logic Analyser £3750
- IP3781A Pattern generator & HP3782A Error Detector £90A
- HP6211A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
- HP6264 Rack mount variable 0-20V @ 20A metered PSU £675
- HP54121A DC to 22 GHz four channel test set £90A
- HP8130A opt 020 300 MHz pulse generator, GPIB etc £8500
- IP A1, A0 8 pin HPGL high speed drum plotters - from £950
- 2-G Brookdeal 95035C Precision lock in amp £650
- View Eng. Mod 1200 computerised inspection system £90A
- Sony DXC-3000A High quality CCD colour TV camera £1100
- Kelthley 590 CV capacitor / voltage analyser £90A
- Racal ICR40 dual 40 channel voice recorder system £3750
- Fluors 45KVA 3 ph On Line UPS - New batteries £9500
- CI R5030UV34 Cleanline Ultrasonic cleaning system £90A
- Jann Tally MT645 High speed line printer £2200
- met SBC 486/1335E Multibus 486 system. 8Mb Ram £945
- Siemens K4400 64Kb to 140Mb demux analyser £2950

IC's - TRANSISTORS - DIODES

OBsolete - SHORT SUPPLY - BULK

6,000,000 items EX STOCK

For MAJOR SAVINGS - CALL OR SEE OUR WEBSITE

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see - At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes. BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, supplied in EXCEL-

LENT little used condition. T/R & Swivel Base £4.75

Only £119 (E) Order as MITS-SVGA

VGA cable for IBM PC included.

External cables for other types of computers CALL

As New - Ex Demo

17" 0.28 SVGA Mitsubishi Diamond Pro monitors

Full multisync etc. Full 90 day guarantee. £325.00 (E)

Just in - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for Info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed Dimensions: W14" x H12 1/4" x 15 1/2" D.

Only £99 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen bums). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered.

Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 kHz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.

Only £125 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. IN EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock Call or see our web site.

LOW COST PC'S

Always over 1000 PC's from stock. 1000's of spares and accessories. Call or see our web site for info.

19" RACK CABINETS

Superb quality 6 foot 40U Virtually New, Ultra Smart Less than Half Price!



Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 7 7/8" H x 32 1/2" D x 22" W. Order as:

- OPT Rack 1 Complete with removable side panels. £345.00 (G)
- OPT Rack 2 Rack Less side panels £245.00 (G)

Over 1000 racks, shelves, accessories

19" 22" & 24" wide 3 to 46 U high. Available from stock !!

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvres. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W) Sold at LESS than a third of makers price !!



A superb buy at only £245.00 (G)

42U version of the above only £345 - CALL

BATTERY SCOOP - 50% off !!

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12v DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type S8515 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & B56290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £70 each!

Our Price £35 each (c) or 4 for £99 (D)

RELAYS - 200,000 FROM STOCK

Save £££'s by choosing your next relay from our Massive stocks covering types such as - Military, Octal, Cradle, Hermetically Sealed, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting, CALL US WITH YOUR NEEDS. Many obsolete types from stock. Save £££'s

LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. £59.95 Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data. Order as: XT RAM UQ. 256k. £34.95 or 512k £39.95

SIMM SPECIALS

- 1 MB x 9 SIMM 9 chip 120ns Only £8.50
 - 1 MB x 9 SIMM 3 chip 80 ns £10.50 or 70ns £11.95
 - 1 MB x 9 SIMM 9 chip 80 ns £10.50 or 70ns £11.75
 - 4 MB 70 ns 72 pin SIMM -with party- Only £35.00
 - INTEL 486-DX33 CPU £19.95 INTEL 486-DX66 CPU £59.00
- FULL RANGE OF CO-PROCESSOR'S EX STOCK - CALL FOR £££
- MOTOROLA 25 Mhz 68040 (XC68040RC25M) CPU'S £59.00 shipping charges for RAM / CPU upgrades is code B

SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. Special Price ONLY £99.00 Microsoft - Windows for Workgroups 3.11 & DOS 6.22. Supplied on 3 1/2" disks with licence & concise documentation. £39.95 DOS 5.0 on 3 1/2" disks with concise books c/w QBasic. £14.95 Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95 shipping charges for software is code B

DISTEL on the web !! - Over 16,000,000 items from stock - www.distel.co.uk



ALL MAIL & OFFICES
Open Mon - Fri 9.00 - 5.30
Dept Ww, 32 Biggin Way
Upper Norwood
LONDON SE19 3XF

LONDON SHOP
Open Mon - Sat 9.00 - 5.30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
N. Thornton Heath & Selhurst Park SR Rail Stations

NEW DISTEL
Visit our web site
www.distel.co.uk
email admin@distel.co.uk


ALL ENQUIRIES
0181 679 4414
FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=£22.00. Allow approx 6 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Display Electronics 1998. E & O E. 0698

CIRCLE NO. 134 ON REPLY CARD



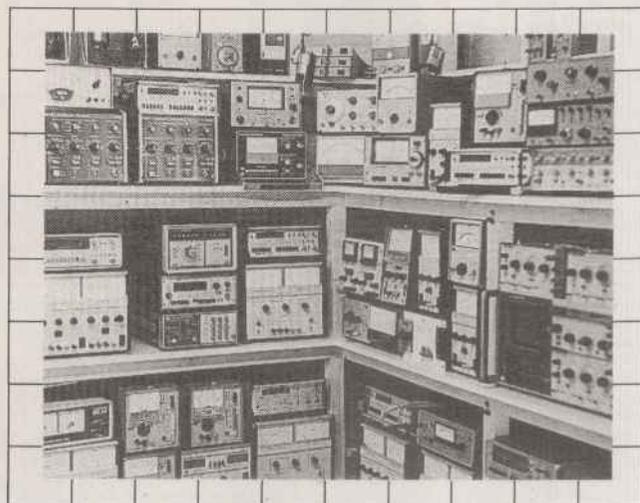SUPPLIER OF QUALITY USED TEST INSTRUMENTS



Cooke International


Unit Four, Fordingbridge Site, Barnham,
Bognor Regis, West Sussex, PO22 0HD, U.K.
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

Web: <http://www.cooke-int.com>
E-mail: info@cooke-int.com
catalogue available

CIRCLE NO.135 ON REPLY CARD



OPERATING & SERVICE MANUALS

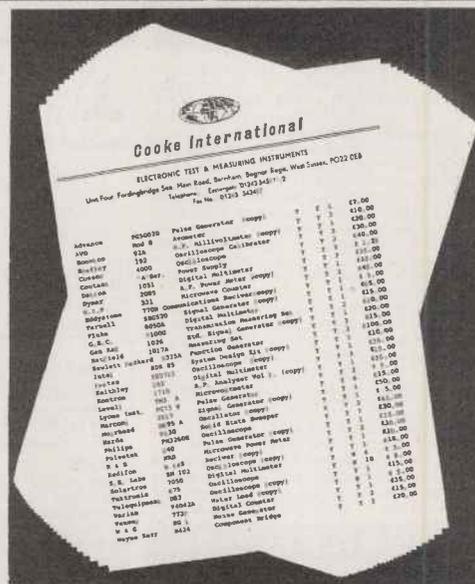

Cooke International

Unit Four, Fordingbridge Site, Barnham,
Bognor Regis, West Sussex, PO22 0HD, U.K.
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

Web: <http://www.cooke-int.com>
E-mail: info@cooke-int.com
catalogue available

CIRCLE NO.136 ON REPLY CARD

ADVERTISERS' INDEX

ANCHOR SUPPLIES.....	502	M & B RADIO.....	519
ANGLIA COMPONENTS.....	OBC	MDM RECRUITMENT.....	481
ANTRIM TRANSFORMERS.....	491	MILFORD INSTRUMENTS.....	467
ARBOUR APPOINTMENTS.....	482	OLSON ELECTRONICS.....	497
CMS.....	494	PICO.....	465
CONFORD ELECTRONICS.....	519	PS CONSULTANTS.....	449
CROWNHILL.....	467 and 491	QUICKROUTE.....	457
DISPLAY ELECTRONICS.....	525	RADIO TECH.....	519
EQUINOX TECHNOLOGY.....	IBC	RALFE ELECTRONICS.....	528
FARADAY TECHNOLOGY.....	467	RD RESEARCH.....	491
HAYELY ANTENNA.....	523	SEETRAX.....	457
ICE TECHNOLOGY.....	463	SIGHTMAGIC.....	465
ILP DIRECT.....	510	SOLUTION.....	479
INTERNATIONAL RECTIFIER.....	IFC	SOWTER TRANSFORMERS.....	510
JOHN PRODGER RECRUITMENT.....	478	STEWART OF READING.....	510
JOHNS RADIO.....	515	SURREY ELECTRONICS.....	519
JPG ELECTRONICS.....	523	SWIFT EUROTECH.....	444
KELLY TECHNICAL.....	483	TELFORD ELECTRONICS.....	509
LABCENTER ELECTRONICS.....	442	TELNET.....	461
LANGREX SUPPLIES.....	523	TIE PIE.....	447

ARTICLES WANTED

TOP PRICES PAID

For all your valves,
tubes, semi conductors
and IC's.

**Langrex
Supplies
Limited**

1 Mayo Road, Croydon
Surrey CR0 2QP
TEL: 0181 684 1166
FAX: 0181 684 3056

VALVES WANTED

Courteous, Professional Service

Ask for a free copy of our
wanted list.

BILLINGTON EXPORT LTD

Billingshurst, Sussex
Tel: 01403 784961
Fax: 01403 783519

Email:

billingtonexporttd@btinternet.com

VISITORS PLEASE PHONE FOR APPOINTMENT

WANTED. Gemstar Video+ Plus+ programmer model VIP-185 (preferably). Must be in good working order. Instructions not required. 01736 367100.

SERVICES

**From
Concept
To
Production**

Designer Systems has over a decade of experience designing innovative products for client companies and individuals. If you have a product idea, need to develop a new product or sub-assembly from scratch, want to re-develop an old product or need professionally written documentation or software, contact us for more information or see our web site.

Tel/Fax: 01872 223306

Email: designer.systems

@btinternet.com

Web: http://

designersystems.

co-td.net

**DESIGNER
SYSTEMS**
Bespoke electronic solutions

WANTED TO BUY. Used Neutrik chart recorder system. Fax USA 702/565-4828 Franklin Miller. Email fjm@anf.net

**ADVERTISERS PLEASE
NOTE FOR ALL YOUR
ENQUIRIES ON
ADVERTISING RATES
PLEASE CONTACT
JOANNAH COX ON
TEL: 0181 652 3620
FAX: 0181 652 8938**

SERVICES

**P&P
ELECTRONICS**

Design of analogue and
digital circuitry

Tel: 01924 402931

FREE CATALOGUE: Moreton Alarm Supplies/CCTV 2000. Unbeatable prices. Phone for a free catalogue 0151 630 0000.

APPOINTMENTS

Translation Partnership for
German-English documentation
is looking for a

**FREELANCE
TECHNICAL
TRANSLATOR**

— an engineer with professional and
translation experience in a German-
speaking environment, in
electrical/electronic/mechanical or
measurement technology.
E-mail is vital, DTP useful.

Detailed information please to:

ACM C & P Chadwick
15 St Olaves Road
York YO30 7AL

ARTICLES FOR SALE

CITIFAX

VBI DECODER CARDS

(Teletext Receivers)

SALE

Manufacturer has surplus to requirements Printed Circuit Boards type CF2001. These through-hole unpopulated boards when built allow reception of BBC Datacast etc. VBI transmissions as well as ordinary Teletext. For further details see www.citifax.co.uk or phone 01204 392397 office hours. Offered with programmed EPROM and Microsoft PnP Vendor ID EEPROM plus PC ISA bracket, with circuit diagram parts list and demo disk while stocks last at £25 each, £200/ten, inc. UK P&P free.

Citifax Limited, 2nd Floor, 3 Atlas House, St George's Square, BOLTON BL1 2HB, Lancashire.

**Workshop Clearout!
SPECTRUM ANALYSER**

Marconi TF2370 **£300** + VAT
Audio to 110MHz digital storage
display, also extender available.
Tektronics 466 Storage Oscilloscope
VGC **£275**.

Scanner AOR3000A (boxed) **£350**.
PC Pentium 120 new 15" monitor,
and new 3.4G HDD **£350**.

Precision Pressure Gauges

Barometric/Analogue **£100**.

Digital absolute/differential
Druck **£200**.

Camera gyrosopic stabiliser
+PSU **£100**.

Goold sweep gen. 0 to 1.6GHz **£100**.

HP 1600A Logic state analyser **£100**.

Sig gens, audio and RF — phone.

All guaranteed working

Derby **01332 670707**

**RF DESIGN
SERVICES**

All aspects of RF
hardware development
considered from
concept to production.

WATERBEACH ELECTRONICS

TEL: 01223 862550

FAX: 01223 440853

SHORTWAVE BROADCASTERS

Monitor reception from within your
target area

GOVERNMENT AGENCIES

Control radio receivers/transceivers
worldwide

Radphone 2000DX from

www.pca.cc

Intel+61-2-98889777

Fax+61-2-98050253

COMPUTER AMD K6-2, 350MHz, 6.4G
h/drive, 8MB AGP, VGA, 3D PCI sound, x36
CD-RM, 15" svga, accessories, software, brand
new. £685. Mike 01707 263953, Herts.

POWER SUPPLY DESIGN

Switched Mode PSU

Power Factor Correction

Inverter

Tel/Fax: 01243 842520

e-mail: eugen_kus@cix.co.uk

Lomond Electronic Services

19" Rack Enclosures

New and Used most sizes
16U to 50U side and rear panels
mains distribution 19" Panel mounts
optima eurocraft. Prices from £45 +vat

M&B Radio

86 Bishopsgate Street Leeds LS1 4BB
Tel. 0113 2702114 Fax. 0113 2426881

100MHz OSCILLOSCOPE with 60MHz probe
set, £580, unused (OS5100); TG230 Function
generator, £200, unused; 10MHz Oscilloscope,
£50. Evenings 01264 391165.

DATAMAN S4 as new, boxed with all
accessories. £350. Tel: 07971 165335 (Dorset).

T & M EQUIPMENT



ADVANTEST TR9407 ftt spectrum analyser to 1MHz £2000
 ADVANTEST TR4133 100kHz-20GHz spectrum analyser £6000
 ANRITSU ML93A optical power meter with MA96A power sensor (0.75-1.8uM) £1000
 ANRITSU MN95D fibre-optic attenuator 0-65db £250
 BRADLEY 192 oscilloscope calibrator £250
 CHASE LFR1000 interference measuring receiver 9kHz-150kHz £200
 DATRON 1061 Avoltmeter, 10/20/30/40/50 £1250
 DRANETZ 626-PA-6006 ac neutral monitor, c/w TR2018 clamp £250
 EIP 575 source locking frequency counter 18GHz GPIB option £1250
 FLANN MICROWAVE 27072 frequency meter 73-113GHz £275
 FLANN precision rotary waveguide attenuator 20110 0-60db 18-26GHz £750
 FLANN precision rotary waveguide attenuator 22110 0-70db 26-40GHz £750

IFR A-7550 1GHz portable spectrum analyser with receiver options AM/FM/SSB £2000
 GIGATRONICS 8542 microwave power meter to 18GHz c/w sensors £1250
 KEITHLEY 192 programmable digital multimeter £250
 MARCONI 2019A signal generator 10kHz-1GHz INCLUDING FREE CALIBRATION £1500
 MARCONI 2380/2382 400MHz high-performance spectrum analyser £2750
 PHILIPS PM5580 L.F. modulator (PAL 1)/PM5582 UHF-converter £100
 RHODE & SCHWARZ AFGU function generator 1uHz-20MHz £2000
 RHODE & SCHWARZ UPA audio analyser with B6 & B9 options £2500
 RHODE & SCHWARZ UDS 5, 5.5-digit multimeter IEE £250
 RHODE & SCHWARZ URE rms digital voltmeter IEE £250

THIS MONTHS SPECIAL

Hewlett Packard 8657B synthesized signal generators 0.1-2060MHz with 001/003 (Hi-stab & pulse mod) options. List >£10,500. Ours . . . £4,000.
 HP3561A dynamics signal analyser £4000

ralfe electronics *exclusively professional T&M*

• 36 Eastcote Lane • South Harrow • Middx HA2 8DB • England •
 TEL (+44) 0181-422 3593 • FAX (+44) 0181-423 4009

EST 45 YRS



RACAL DANA 1991 frequency counter, GPIB opt £550
 SCHLUMBERGER 4922 radio code analyser £250
 SCHLUMBERGER SRTG-GA62 selective call test set £150
 SYSTRON D0NNER 6041A 100MHz 8-digit frequency counter IEE £100
 TEKTRONIX 2432A 100MHz 250M Sa/sec digital storage oscilloscope £1000
 TEKTRONIX 2236 100MHz analogue oscilloscope £500
 TAU-TRON MN302/MB302N bert transmitter/receiver £250
 WANDEL & GOLTERMANN PCM4 pcm measuring set version 985/01, IEE opt £7500
 WANDEL & GOLTERMANN PF2 error ratio measuring set £400
 WANDEL & GOLTERMANN OLM-20 data circuit test set £250
 WANDEL & GOLTERMANN SPM31 level meter £500
 WANDEL & GOLTERMANN VM30 level tracer £500
 WANDEL & GOLTERMANN PF4 bit error rate tester (BN911/01. Opt 00.01) £2000
 WAVETEK 23 synthesized function generator 0.01Hz-12MHz £500
 WAVETEK 1080 sweep generator 1-1000MHz £750
 WAYNE KERR 3220 20A bias unit (for 3245 inductance analyser) £1000
 WAYNE KERR SR268 source and detector £250
 WILTRON 6637 sweeper generator 2-18GHz (option 03) £2000
 WILTRON 6659A sweep generator 10MHz-26.5GHz (options 01/10/13) £3000
 WILTRON 6640B sweep generator 26.5-40GHz (option 03) £3500

HEWLETT PACKARD



8714C 300kHz-3GHz vector network analyser £7500
 3585A 40MHz spectrum analyser £4000
 1640B serial data generator £500
 10715A digital interferometer £1000
 3577A network analyser 5Hz-200MHz £4000
 3314A function generator £1500
 33320G/33322G programmable attenuators 4GHz, with driver 11713A £650
 As above but 18GHz set £1000
 3561A dynamics signal analyser £5000
 3586A selective level meter £1250
 37717B communications performance analyser, call for option configs £9500
 4093B protocol tester base (PT300) £3000
 4142B DC source/monitor (with 41421B, 41420A, 41424A) £8500
 8018A serial data generator £1000
 5334B frequency counter, option 060 £1000
 83411C lightwave receiver 100/1550nm £1750
 83440C lightwave detector 20GHz 1300nm/1550nm £2000
 8350B sweep generator mainframe £2000
 83572B sweeper plug-in unit (for 8350B) 26.5-40GHz £6500
 8924C CDMA mobile station test set £25000
 85053B 3.5mm verification kit £2000
 85640A tracking generator to 2.9GHz £2000
 8672A synthesized signal generator 2-18GHz £6000
 8673D synthesized signal generator 50MHz-26.5GHz £10000
 86222A 10MHz-2.4GHz sweep generator plug-in unit £1000
 86290B 2-18GHz sweep generator plug-in unit £1500
 8684B signal generator 5.4GHz-12.5GHz £1000
 8903B audio analyser £2500 - (specify your own filter requirements - add £200 for each filter)
 8904A/001/002 multifunction synthesizer DC-600kHz £2000
 8970B noise figure meter with option 020 £5000
 J2215A FDDI portable multimode test set £1500

All equipment sold calibration-checked by independent laboratories and carries un-conditional refund and 90-day guarantees.

CALLERS WELCOME BY APPOINTMENT ONLY.


FOR COMPLETE STOCK LISTING PLEASE CHECK OUR WEBSITE

www.ralfe-electronics.co.uk



ISO9002 ACCREDITED STOCKIST MEASUREMENT & TEST EQUIPMENT

CIRCLE NO.137 ON REPLY CARD

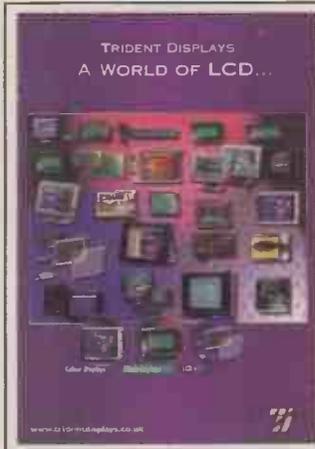

TRIDENT DISPLAYS
 A WORLD OF LCD...

The widest range of colour LCDs, LCD monitors and plug and play kits available in the UK, all in one easy to use brochure, is now available FREE!


It includes information on products ranging from 2.9" monitors to 16.1" colour LCD screens, mono/colour STN TFTs and touch screen technology from the world's leading manufacturers.

Phone TRIDENT today for your free copy.

TEL: 01737 780790
 FAX: 01737 771908

OR VISIT OUR WEBSITE:
 www.tridentdisplays.co.uk

CIRCLE NO.138 ON REPLY CARD

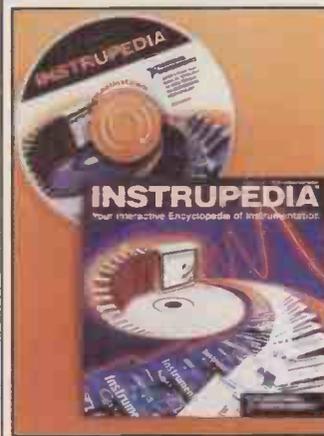

FREE Interactive Encyclopedia of Instrumentation

Instrupedia™ from National Instruments, is the latest version of the company's free CD-ROM encyclopedia for instrumentation. Featuring an enhanced user interface and a new intuitive search engine, Instrupedia is updated with the entire National Instruments product catalogue and additional information useful to scientists and engineers when building PC-Based test, measurement and automation applications. For your FREE CD-ROM call National Instruments on 01635 523545.

e-mail: info@natinst.com
 Website: www.natinst.com/uk

CIRCLE NO.140 ON REPLY CARD



INDUSTRIAL COMPUTER PRODUCTS

The latest ICP catalogue featuring a comprehensive range of CPU boards and enclosures, complete with price list, is now available from Wordsworth.

Further details from:
Wordsworth
 Tel: 01732 861000

CIRCLE NO.139 ON REPLY CARD



LCR & IMPEDANCE METERS

The 3522 LCR HiTESTER and 3531 Z HiTESTER together provide a wide range of test frequencies. The 3522 offers DC and a range from 1mHz to 100kHz and the 3531 covers the range from 42Hz to 5MHz. Test conditions can now come closer to a component's operating conditions. The high basic accuracy of ±0.08%, combined with ease of use and low price give these impedance meters characteristics.

TELONIC INSTRUMENTS LTD

Tel: 0118 9786911
 Fax: 0118 9792338

CIRCLE NO.141 ON REPLY CARD

ST Microcontrollers Roadshows

Forthcoming dates:

- ~~⊗ Highbury – 24th March '99~~
- ⊗ Villa Park – 18th May '99
- ⊗ Old Trafford – 15th June '99



**VISIT ONE OF OUR ROADSHOWS AND YOU'LL GET LUNCH,
A STADIUM TOUR AND YOU'LL RECEIVE:**

FREE ST Development Kit • **FREE** CDs and Literature • **FREE** password to exclusive Website



Or join the ST Microcontroller Design Group and win a FREE dev kit...

...simply visit our website www.st-angliamicro.com to register. Upon sign up you'll get all the information you need to design with these powerful microcontrollers including CDs, and databooks. Every month we'll also give away a dev kit to the best design idea/project. As a member of the club you receive all the technical backup you need, invitations to our forthcoming seminars, a quarterly newsletter featuring the best designs and some of the best prices anywhere!



Don't wait, get in touch NOW & you'll see why everyone's changing to ST microcontrollers and Anglia!

Anglia

Call Michelene Hircock or Claire Joyce
for your free invitation on
01945 47 47 47

- Number one choice for STMicroelectronics

