

# ELECTRONICS WORLD

+ WIRELESS WORLD

Denmark Dkr. 63.00  
Germany DM 13.00  
Greece Drs. 680  
Holland Dfl. 12.50  
Italy L 6500  
IR £2.95  
Spain Pts. 700.00  
Singapore \$5 11.25  
USA \$5.95

OCTOBER 1991 £1.95

*DESIGN*

**Working with  
quarterwave  
transformers**

*BIOELECTRICS*

**Electric fields  
and health**

*REVIEW*

**How easy is  
EasyTrax?**

*TECHNICAL  
SOFTWARE  
DISCOUNT  
SCHEME STARTS  
THIS MONTH  
SEE INSIDE FOR  
DETAILS*



# COLOURJET 132

## COLOUR INK JET PRINTER

Compatible with:-


IBM pc  
Archimedes  
Nimbus  
BBC Micro  
Amiga  
Apple Mac  
(serial version)

LOW COST

LIST PRICE  
from £636 + VAT



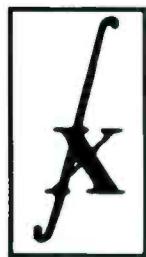EMULATES OTHER COLOUR PRINTERS EG. IBM 3852, Canon PJ1080A, Quadjet  
PRINTS OVERHEAD TRANSPARENCIES




EDUCATIONAL DISCOUNTS AVAILABLE

**INTEGREX LTD.**, CHURCH GRESLEY, SWADLINCOTE  
DERBYS. DE11 9PT  
Tel (0283) 551551  
Fax (0283) 550325  
T/x 341727 INTEGX

CIRCLE NO. 101 ON REPLY CARD

# CONTENTS

## FEATURES

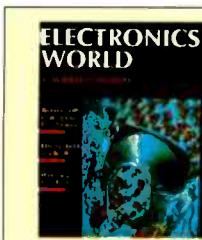

### ACTIVE FILTERS.....812

Circuit details for active filters are sometimes hard to find. John Linsley Hood brings together the most useful.

### IMPEDANCE TRANSFORMATION WITH STANDARD 50Ω CO-AX FEED .....820

Dick Manton shows how a quarter-wave transformer and a simple network of 50Ω lines can be used to avoid input/output impedance mismatches.

### SOUND MODELS FOR MICROCAP.....824

Ben Duncan illustrates the modelling of some real passive components for greater realism in simulation.

### LAYOUT PCBs WITHOUT LADLING OUT CASH.....831

Should we jump at Easylayout 2's low cost entry to computer PCB layout? Martin Cummings looks before we leap

### MATCADC ENGINEERING.....835

Allen Brown finds the new addition to MathCad is a valuable tool for electrical engineers.

### HAZARDING A GUESS AT EMR EFFECTS.....841

We are starting to understand cellular mechanisms. So will we look back on current EM limits with incredulity? Roger Coghill reports from BEMS 91.

### DESIGN BRIEF: VOLTAGE REFERENCES.....845

Ian Hickman looks at voltage reference circuit designs

### NO IFS – NO BUTS.....850

Does the classic IF routine unnecessarily complicate programming and encourage bugs? Yes, but there is a solution writes Frank Pettit.

### THE LEYDEN JAR ENIGMA.....871

Leonid N Kryzhanovsky tracks the early history which led to development of the modern capacitor.

### DSP CHIP WITH NO PARALLEL.....878

Parallel processing through six parallel 8-bit communication ports makes the TMS320C40 a landmark in chip development says Allen Brown.

### ALL SYSTEMS GO FOR DAB?.....880

Tests of digital audio broadcasting are producing excellent results. Can the practicalities of dab be overcome? Barry Fox and Pat Hawker investigate.

## REGULARS

### COMMENT.....715

Visionary stupidity

### UPDATE .....804

### RESEARCH NOTES .....808

Harnessing H-bombs to heat the home, planet that casts doubt on universal theory, imaging upset for IC fair hearing for six channel ear.

### CIRCUITS, SYSTEMS AND DESIGNS .....837

Innovative design techniques yield optimum counter oscillator.

### LETTERS.....854

Second wave of Maxwell, CD-I vs CDTV, Satellite in a spin, Back to the future I and II, CFA questions and reflections.

### CIRCUIT IDEAS.....858

Bi-directional I/O for microcontrollers, Dial a harmonic, Programmable waveform generator, UHF VCO, Class-A push-pull amplifier.

### NEW PRODUCTS.....862

EW + WW's round-up of all that's new in electronics.

### PICTURES FROM THE PAST .....868

Avionics – 1940s Luftwaffe style.

### APPLICATIONS .....874

Pressure sensing, hand-held low cost data logger, stepper motor drive

**In next months issue:** In October 1945, Wireless World published an article *Extra Terrestrial Relays* by Arthur C Clarke. It laid the basis for modern satellite communications and, in doing so, changed the world. To mark our 80th anniversary, we will publish Clarke's original paper in its entirety.

### ELECTRONICS WORLD SOFTWARE DISCOUNT SCHEME

Get 25% discount on all Labcenter electronic design software. Offer prices start at £51.75 + VAT

**Schematic:** *Isis SuperSketch*, *Isis Designer*

**PCB layout:** *PCB II*, *Ares*, *Ares Autoroute*

**Simulation:** *Spice.age* (*Those Engineers*)

*Simply collect the coupon from this issue, November and December. Ordering details will appear in the December issue.*

DISCOUNT  
SOFTWARE  
COUPON  
OCTOBER 1991  
EW+WW

# AXIOM

## SUPER SAVERS

### AMERICAN MAINBOARDS

#### 40MHz 386 TECHNOLOGY!

• Amazing 9.5 MIPS! • Norton ver 5.46! • AMD TRUE 40MHz 386 Processor • Socketed for 80387/WEITEK Sync/Async Copro • BUS Speed selectable 6/8/12 MHz • ETEQ Chipset • 7x16 bit + 1x8 bit Expansion Slots • On board Diagnostics • Up to 32Mb on board RAM Memory (SIMM) • 128K Cache Standard (up to 256K on board) • AMI BIOS with password protection • XT Sized Multilayer construction • USA Researched & Manufactured. This board is FASTER than a 486-33 with most software!  
It represents amazing value for an American board at ...  
just ... £759! (excl. RAM)

#### GOLD 386SX-20C (with Cache!)

• Intel 20MHz 386SX Processor • Built-In 32K Cache memory • 4.17 MIPS Norton 23 • Software select on CPU 8/20MHz • Intel 80387SX co-processor support • 8x16 bit expansion slots • Up to 32Mb on board RAM (SIMM) • AMI BIOS • XT Sized • USA Researched & Manufactured • TWO YEAR Warranty • Full support of DOS/OS/2/UNIT/XENIX/PICK/PC-MOS/NOVELL  
As far as we know this board is unique—being the first 386SX to use Cache Memory to improve performance. Providing real value running as fast as a 386DX clocking at 25MHz!

Priced at just ... £299! (excl. RAM)

### MAINBOARD 486 SPECIAL

486-33MHz with 256K Cache ETEQ chipset. Landmark speed 168MHz!  
£899

### GENERIC MAINBOARDS

286 16MHz inc. 1Mb RAM	110
286 20MHz	95
386-SX 20MHz	212
386 25MHz (no cache)	281
386 33MHz 64K cache	418
486 25MHz 64K cache	781
486 33MHz 128K cache	862

NEW from  HITACHI  
5.25" ULTRA-FAST ULTRA RELIABLE HIGH CAPACITY  
DK515 series 780Mb / 16ms / 256K buffer / 2.4Mb per  
sec / 100,000 hours MTBF ESDI/SCSI versions £1359  
DK516 series 1.65Gb / 13.5ms / 5.0Mb per sec / 150,000  
MTBF ESDI/SCSI versions £2395  
Available with 5 year 'Swap Out' warranty!

BUILDING YOUR OWN PC?  
Call us for the best advice  
and prices around

MODEL	HARD DISK	RAM	PRICE £
AXIOM 286/20	40Mb	2Mb	829
AXIOM 386SX/20	40Mb	2Mb	995
AXIOM 386/25	90Mb	4Mb	1337
AXIOM 386/33/64	90Mb	4Mb	1487
AXIOM 486/33/256	90Mb	4Mb	1945

Choice of desktop or Mini Tower enclosures.

All systems include:

Super VGA 1200 x 768 Colour VGA Card (1Mb) and Monitor, Hard Disk as specified - FAST IDE type AMI BIOS - dated 1991. Dual media 1.2Mb and 1.44Mb floppy drives, RAM as specified (expandable on board) 102-key enhanced keyboard.

And... ONE YEAR ON-SITE WARRANTY!

With over seven years in the business you can be assured of pre and post sales support from Digitask.  
Nobody builds a meaner machine!

### WINCHESTER DRIVES AND CONTROLLERS

#### HARD DISK DRIVES

H PACKARD 9754 340MB ES/SCSI 17ms	1,295
H PACKARD 9754 680MB ES/SCSI 17ms	1,895
NEWI MAXTOR 340Mb 3.5" SCSI-II 13ms	799
CONTROLLERS	
ADAPTEC AHA-1522 SCSI KIT WITH FLOPPY	145
ADAPTEC AHA-1540B SCSI HOST ADAPTER	236
ADAPTEC AHA-1542B SCSI HOST ADAPTER	247
ADAPTEC AHA-1542 SCSI KIT WITH FLOPPY	255
ADAPTEC AHA-1640 MCA HOST ADAPTER	289
ADAPTEC ACB-3220 ESDI WITH FLOPPY	155
SMARTCACHE AT/MCA ST506 600/FDD 512K	795
SMARTCACHE AT/MCA ESDI HDD/FDD 512K	795
SMARTCACHE 2Mb CACHE EXPANSION MODULE	375
SMARTCACHE 4Mb CACHE EXPANSION MODULE	695
NCL 5475 AT/MFM 2HD 2FDD 1:1	67
NCL 5275 AT/RLL 2HD 2FDD 1:1	82
NCL 530 AT/IDE 2HD 2FDD	44
ST-01 XT/AT SCSI 2HDD	15
ST-02 XT/AT SCSI 2HDD/2FDD	21
ST-05 XT IDE 2HDD	13
ST-07A AT IDE 2HDD	13
ST-08A AT IDE 2HDD/2FDD	22
ST-11M XT MFM 2HDD	29
ST-11R XT RLL 2HDD	30
ST-21M AT MFM 1:1 2HDD	32
ST-21R AT RLL 1:1 2HDD	32
ST-22M AT MFM 1:1 2HDD/2FDD	38
ST-22R AT RLL 1:1 2HDD/2FDD	38

1.295

1,895

799

145

236

247

255

289

155

795

795

375

695

67

82

44

15

21

13

13

13

22

29

30

32

32

38

38

ST 157A 44Mb 3.5" 28ms IDE	126
ST 1102A 84Mb 3.5" 19ms IDE	219
ST 1144A 130Mb 3.5" 17ms IDE	279
ST 1162A 143Mb 3.5" 15ms IDE	375
ST 1201A 177Mb 3.5" 15ms IDE	435
ST 1239A 211Mb 3.5" 15ms IDE	469
ST 2274A 240Mb 5.25" 16ms	779
ST 2383A 338Mb 5.25" 16ms	809
ST 1480A 426Mb 5.25" 14ms	1069
ST 251-142Mb 5.25" 28ms MFM	148
ST 4096 80Mb 5.25" E 28ms MFM	349
ST 1100 88Mb 3.5" 15ms MFM	358
ST 125N 20Mb 3.5" 28ms SCSI	137
ST 157N 49Mb 3.5" 28ms SCSI	161
ST 296N 84Mb 5.25" 28ms SCSI	215

FULL RANGE AVAILABLE—CALL FOR ESDI AND SCSI

Prices do not include Controllers and Cables.

Digitask is an authorised Seagate reseller.

### FLOPPY DRIVES AND CONTROLLERS

DUAL FLOPPY CONTROLLER XT/AT (360/720K)	49
QUAD FLOPPY CONTROLLER XT/AT 360/720/1.2/1.4	69
TEAC 5.25" 360K HALF HEIGHT	44
TEAC 5.25" 1.2Mb HALF HEIGHT	44
TEAC 3.5" 720K 1" HEIGHT	46
TEAC 3.5" 720K/1.4Mb 1" HEIGHT	46
TEAC 5.25" 3.5" ADAPTER KIT	12
BACKPACK EXT 5.25" 360K/1.2Mb*	295
BACKPACK EXT 3.5" 720K/1.4Mb*	295
BACKPACK EXT 3.5" 720K/1.2Mb/2.8Mb*	355
EXTERNAL 5.25" FLOPPY CASE	65
FLOPPY DRIVE CABLE SET	10

\*These drives are intended for portables and operate from the parallel port

### CONNER HARD DRIVES

High Performance Storage Solutions

CP 3044 3.5" 40Mb IDE 1" High	£195
CP 3104 3.5" 104Mb IDE Half Height	£273
CP 30104 3.5" 120Mb IDE 1" High	£337
CP 3204 3.5" 200Mb IDE Half Height	£499
CP 30100 3.5" 120Mb SCSI 1" High	£379
CP 3100 3.5" 104Mb SCSI Half Height	£379
CP 3040 3.5" 40Mb SCSI 1" High	£210
CP 3200 3.5" 200Mb SCSI Half Height	£599

£195

£273

£337

£499

£379

£379

£210

£599

NEW!



Danish origin, highly reliable Ethernet cards and accessories at amazing prices

PC-01 8 bit for PC/XT/AT (NE-1000 compatible)	£94
PC-02 16 bit for PC/AT (NE-2000 compatible)	£119
MC-01 Microchannel for PS/2	£169
LAP-03 for Toshiba Laptops	£198
RP-02 13 port Ethernet/IEEE 802.3 10 BASE-T Repeater	£896
RP-01 2 port Ethernet/IEEE 802.3 Repeater	£767
TRX-02 10 BASE-T Twisted pair Transceiver	£119

In addition we supply and support ● Computer Cases ● Switch Mode Power Supplies ● Eprom Programmers/PAL Programmers ● Memory: RAM/DRAM/SIMMS/SIPP/VRAM ● Chips/Processors & Co-Processors

● Data Acquisition AD/DA, DA/AD, I/O ● Scientific Solutions (PC based) ● Optical Drives ● Terminals/VDUs



**DIGITASK**

Digitask Business Systems Ltd. Unit 2, Gatwick Metro Centre  
Balcombe Road, Horley, Surrey RH6 9GA  
Telephone (0293) 776688 Fax (0293) 786902 Telex 878761 DIGIT G



Fax (0293) 786902

PRICES & MANUFACTURERS SPECIFICATIONS SUBJECT TO CHANGE PRICES DO NOT INCLUDE VAT OR CARRIAGE

DEALER & EXPORT ENQUIRIES WELCOME

CIRCLE NO. 123 ON REPLY CARD

# Visionary stupidity

## EDITOR

Frank Ogden  
081-661 3128

## DEPUTY EDITOR

Jonathan Campbell  
081-661 8638

## DESIGN & PRODUCTION

Alan Kerr

## EDITORIAL ADMINISTRATION

Lindsey Gardner  
081-661 3614

## ADVERTISEMENT MANAGER

Jan Thorpe  
081-661 3130

## DISPLAY SALES MANAGER

Shona Finnie  
081-661 8640

## ADVERTISING ADMINISTRATION

Kathy Lambert  
081-661 3139

## ADVERTISING PRODUCTION

Neil Thompson  
081-661 8675

## PUBLISHER

Robert Marcus

## FACSIMILE

081-661 8956

**A**fter the first of January, 1993, all televisions bigger than 22in will have to be D2MAC compatible if sold within EC countries. This means that every euro-consumer buying a large screen set will pay towards the cost of protecting the French company Thomson and the Dutch giant Philips from external competition. At present mac set prices, you or I would have to cough up an extra £500 although this will fall with time. The same euro-ruling insists that new satellite services use D<sup>2</sup>mac. Further, when the nation's living rooms are taken over by HDTV, the system in use will be HD-MAC.

The European Commission has chosen to conceal blatant protectionism by selling its directive as "the laying of new foundations for high quality television services in the 21st century".

We take a slightly different view. Why bother to hide the protectionist aspect at all? After all, Europe sells nothing of significance in monetary terms to far-eastern countries and the effects of a hard line pursued against Japan and Korea would do nothing but good for the long-term advantage of the European electronics industry. If Japan were to take retaliatory action, it would amount to the economic equivalent of hara kiri. Far from hiding protectionist euro-policies, we should all be dreaming up new ways to frustrate our far-eastern trading 'partners'.

It goes almost without saying that we must be prepared to behave differently with those countries which value our exports, notably the US. Here co-operation rather than confrontation seems far more fitting.

Yet there remains a disturbing aspect to the EC's imposition of mac-based television. It is not so much the fact that euro-consumers will be denied the choice of low cost Japanese and Korean equipment. It is simply that the mac systems are not flexible enough for the next generation of television broadcasting developments. If Europe

adopts mac, the industry will see it to be as limiting as we currently regard pal – and in the space of just a couple of years.

When the old IBA dreamt up the concept of multiplexed analogue components in the early eighties, it looked like a brilliant way over overcoming the shortcomings of the pal terrestrial system using the technology of the day: no cross-colour with check sports jackets, multiple languages/stereo transmission and easy interchange with other broadcasting standards. Best of all, the time domain compression on the video signals allowed broadcasting within normal TV channel bandwidths. There was even room to squeeze in digital sound and text.

Unfortunately, good as it is, the technology of the eighties has now been eclipsed and the analogue compression at the heart of all mac standards, looks stiff and inflexible. Any universally imposed broadcasting system must be based on all-digital encoding to allow for future development. After all, algorithms which can compress a standard colour TV channel into a 1MHz transmission space already exist (GI's Digicypher) and even more astonishing processing convolutions are in the pipeline.

An all digital system matches low cost manufacturing technology yet takes into account future developments in both microelectronics and future transmission technology. It is almost as if we were back in the '30s and were about to choose the Baird mechanical TV system in preference to EMI's electronic scanning method. It is not enough to say that a digital system isn't ready. After all, 99 per cent of viewers are perfectly happy with the technical quality of what appears on their screens.

That the European Commission is prepared to burden its broadcast manufacturing industries and the viewing public with a technological turkey for the short-term benefit of two companies is quite disgraceful.

**Frank Ogden**



**REED BUSINESS  
PUBLISHING  
GROUP**

*Electronics World + Wireless World* is published monthly By post, current issue £2.25, back issues (if available) £2.50. Orders, payments and general correspondence to L333, *Electronics World + Wireless World*, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telex: 892984 REED BP G Cheques should be made payable to Reed Business Publishing Group.  
**Newstrade:** IPC Marketforce, 071 261-6745.  
**Subscriptions:** Quadrant Subscription Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 441212. Please notify a change of address. Subscription rates 1 year (normal rate) £30 UK and £35 outside UK.  
**USA:** \$116.00 airmail. Reed Business Publishing (USA), Subscriptions office, 205 E. 42nd Street, NY 10117.  
**Overseas advertising agents:** France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 205 E. 42nd Street, NY 10117. Telephone (212) 867-2080. Telex 23827.  
**USA mailing agents:** Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. 2nd class postage paid at Rahway NJ Postmaster. Send address changes to above.  
© Reed Business Publishing Ltd 1991 ISSN 0266-3244

# REGULARS

UPDATE

## Single-atom logic?

IBM scientists here have reported the operation of a new type of electrical switch that relies on the motion of a single atom. They claim to have demonstrated that it is possible for switches to have individual atoms as their critical moving elements.

Writing in *Nature*, researchers Donald Eigler, Christopher Lutz and William Rudge said they had repeatedly moved a single xenon atom back and forth across the gap between two electrodes spaced just several atomic diameters apart. They found that the electrical tunnelling current that flowed between the electrodes changed according to the position of the xenon atom. Such changes could form the basis for a computer logic switch.

The scientists used a special low-temperature scanning tunnelling microscope (STM) to build and operate the atom switch. One of the atom switch's electrodes was the STM tungsten probe held stationary about 5 angstroms (20 billionths of an inch or just a little more than one xenon atom diameter) away from the other electrode – a single crystal of nickel.

To operate the atom switch, the scientists applied a short voltage pulse to one of the electrodes. The resulting electrical current caused the xenon atom to jump the gap between the electrodes and attach itself to the surface of the opposing electrode. With the xenon atom in its new position, the electrical resistance and tunnelling current measured


between the switch's electrodes changed.

By reversing the polarity of the voltage pulse, the scientists found that they could return the xenon atom to its original position and the tunnelling current in the switch to its previous level. Important to the operation of the atom switch is the asymmetric geometry of the flat nickel surface and the relatively sharp STM tip.

The active region of the atom switch is very small, just several atomic diameters. However, to realise any potential size benefits in practical devices, the atom switch's electrodes and electrical leads would have to be greatly miniaturised and arranged very closely together.

The research group is non-committal about the commercial possibilities of atom switches although it hopes to lay the scientific foundation for future generations of very small electronic devices. The initial switch model required high vacuum and low temperatures. However, another IBM research group reported that it had used an STM operating at room temperature to pick up and replace single silicon atoms and clusters of atoms from a silicon surface. This suggests that room temperature atom switches might be possible.

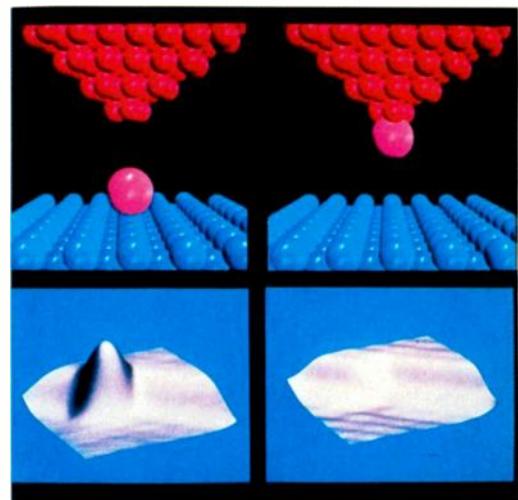The atom switch is the latest achievement of Eigler and colleagues. In April 1990, they used the STM to move and position individual atoms for the first time and had demonstrated the capability by spelling "I-B-M" in block letters with 35 xenon atoms. Since then, several other types of atoms and molecules have been moved



Computer-generated diagrams (top) and STM images demonstrating operation of the single-atom switch. An electrical pulse attracts the xenon atom to the tip, changing the current flowing between tip-surface. An opposite polarity pulse changes the switch properties.

repeatedly back and forth from the surface to the STM tip.

The STM was invented in the early 1980s by Gerd K. Binnig and Heinrich Rohrer, Nobel Prize-winning scientists at the IBM Research Division's Zurich Research Laboratory.

It can image individual atoms on a metal or semiconductor surface by scanning the tip of a needle over the surface at a height of only a few atomic diameters.

The instrument can resolve vertical changes in an atom's apparent shape as small as 0.002 Å – far smaller than any atom.

## Non ionising waves more serious – NRPB

Low-frequency non-ionising radiation could have more serious medical effects on humans than was previously believed, according to a report by the National Radiological Protection Board.

It has been assumed that the damage caused, increased with frequency and dose level. At microwave frequencies, exposure has well-established adverse biological effects. The new report, *Biological Effects of Exposure to Non-ionising Electromagnetic Fields and Radiation*, suggests that there may be other frequency windows which cause effects out of proportion to the radiation level.

The report does not come to conclusions

about medical effects at particular frequencies or dose levels. It was commissioned to find areas of study which need more work.

"In some areas there isn't a lot of information, but what information there is indicates that there might be a problem" commented a spokeswoman for the NRPB.

"But not everyone will definitely be affected by the radiation in a window", she said. "One of the major problems seems to be that people can vary from hypersensitive to completely insensitive."

The effects are fairly esoteric. The report describes some of the results of exposure to low levels of electric and magnetic fields as

"the altered mobility of calcium ions in brain tissue, changes in neuronal firing patterns and altered operant behaviour."

It suggests that densities as low as 10mA/sq m have detectable effects on the human nervous system. "It is worth noting that the endogenous current densities generated by the electrical activity of muscles are typically 1mA/sq m and may reach 10mA/sq m in the heart," according to the report.

Although the report made no recommendations, it concluded that people can perceive the effects of oscillating surface charge induced on their bodies, which can be irritating, and that such effects should be avoided.

Rob Causey

# Breakers' law breaking

Just over 300 people were successfully prosecuted for breaking various sections of the Wireless Telegraphy Act last year says the Radiocommunications Agency in its annual report.

Of the 309 cases prosecuted, there were 306 convictions resulting in fines and costs totalling £111,386. This averages to £364

per case including costs.

The bulk of prosecutions was for illegal broadcasting (143 cases) with CB related offences accounting for a further 122. Amateur radio activity attracted only five prosecutions.

The Radio Interference Service, which acts as the enforcement arm of the agency,

received more than 3000 reports of possible illegal transmitters and other suspect sources of interference from the public. Many of these, it says, were subsequently investigated leading to prosecution.

The RA issued a total of 60,885 amateur radio licences and 69,803 CB licences, a slight decline on last year's figures.

**Prosecution cases concluded in the courts & warning letters issued for financial year April 1990 - March 1991**

Category	Number of Persons Prosecuted	Number of Persons Convicted	Total of Fines Imposed (£)	Number of Costs Awarded (£)	Number of Forfeiture Orders	Number of Conditional Discharges	Number of Absolute Discharges	Number of Admonishments (Scotland)	Warning Letters Sent
CB AM	52	52	6,775	3,898	37	1	—	6	48
CB FM	71	70 <sup>A</sup>	5,085	1,444	17	5	—	4	259 <sup>B</sup>
<b>Unlicensed Broadcasters on Radio</b>	<b>145</b>	<b>143<sup>C</sup></b>	<b>37,190</b>	<b>33,123</b>	<b>122</b>	<b>32</b>	<b>2</b>	<b>—</b>	<b>2</b>
<b>Cordless Telephones</b>	<b>1</b>	<b>1</b>	<b>250</b>	<b>100</b>	<b>—</b>	<b>—</b>	<b>—</b>	<b>—</b>	<b>10</b>
<b>PMR</b>	<b>20</b>	<b>20<sup>D</sup></b>	<b>5,625</b>	<b>2,673</b>	<b>7</b>	<b>4</b>	<b>1</b>	<b>2</b>	<b>70</b>
<b>Amateur</b>	<b>5</b>	<b>5</b>	<b>1,000</b>	<b>1,730</b>	<b>2</b>	<b>1</b>	<b>—</b>	<b>—</b>	<b>2</b>
<b>Marine</b>	<b>8</b>	<b>8</b>	<b>1,180</b>	<b>1,721</b>	<b>—</b>	<b>—</b>	<b>—</b>	<b>—</b>	<b>15</b>
<b>6.6MHz</b>	<b>1</b>	<b>1</b>	<b>250</b>	<b>50</b>	<b>1</b>	<b>—</b>	<b>—</b>	<b>—</b>	<b>1</b>
<b>Others</b>	<b>6</b>	<b>6<sup>E</sup></b>	<b>5,630</b>	<b>3,662</b>	<b>2</b>	<b>—</b>	<b>—</b>	<b>—</b>	<b>9</b>
<b>TOTAL</b>	<b>309</b>	<b>306</b>	<b>62,985</b>	<b>48,401</b>	<b>188</b>	<b>43</b>	<b>3</b>	<b>12</b>	<b>416</b>

A 1 charge of playing music and 1 Section 13 offence (deliberate interference).  
 B 1 offensive language  
 C 1 sentenced to three months' imprisonment and 1 sentenced to 4 terms of 60 days imprisonment suspended for one year  
 D 1 Section 13 offence  
 E 1 charge of obstruction – CB operator; 2 of using aeronautical frequencies in hot air balloon; 1 bug placed in a taxi office by the proprietor and 2 incitement to commit WT Act offences by sale of illegal devices

## Dishing out double trouble

This winter is crunch time for Société Européennes des Satellites, the Luxembourg owners of the Astra satellites, and Eutelsat, the European telecommunications satellite organisation based in Paris. In late October, Eutelsat launches Eutelsat II F3, following the delay caused by the loss of an Atlas rocket in May. Both Eutelsat and Astra have been allocated the same frequencies.

BSkyB uses Astra to broadcast its programmes to the UK.

So far this has not mattered because Eutelsat's existing satellites are located in orbit well away from Astra's. But Eutelsat's new II F3 satellite will be at 16° East, just three degrees away from Astra at 19° East. The position is too close for some of the four million Astra aerials now installed in Europe to discriminate between satellites.

This follows a fudged report from SES which warned against using any dish smaller than 55cm to receive its satellite services. As a result both Amstrad and Sky dropped their plans for lower cost, more environmentally friendly 45cm dishes.

Simon Orme, of receiver manufacturer NEC, warns that "many viewers with popular, low cost dishes are likely to suffer interference".

NEC says that viewers will not notice any



*Small may be beautiful but the picture could get spoilt*

problems with a poorly made or too-small aerial sighted on Astra while there is no other satellite transmitting on the same frequencies from close by in orbit. But Eutelsat will be using some of the same frequencies as Astra, from just three degrees

away. With wide beam aerials, some interference is thus inevitable.

Eutelsat's satellites operate in three frequency bands, 10.95 - 11.2GHz, 11.45 - 11.7GHz, and 12.5 - 12.75GHz. Astra 1A uses 11.2 - 11.45 GHz. Astra 1B uses 11.45 - 11.7 GHz and 1C will use 10.95 - 11.2 GHz when it is launched in a couple of years. So far there is no clash between Astra 1A and anything of Eutelsat's. Eutelsat 1F5 is already at 21.5° East and thus close to the Astra slot. There are no interference problems because there is no frequency clash with Astra 1A or 1B.

But when Eutelsat II F3 launches into its allocated slot at 16° East it will use the same band as Astra 1B, 11.45 - 11.7 GHz. And when Astra 1C is launched in a couple of years it, too, will share frequencies with Eutelsat II F3.

Eutelsat II F3 is now scheduled for launch in mid October, with eight 50W transponders working in the 11.45 - 11.7GHz band. The frequency clash with Astra 1B is unlikely to affect Eutelsat users, including Spanish broadcasters and British data and news services. They will be using large dishes, which exclude Astra's signals. The people who suffer will be Astra viewers with cheap or too-small dishes. They will see double pictures or herringbone patterns

on screen. The only cure will be to fit a larger or better dish. This will not be cheap or popular with viewers.

Eutelsat in Paris feels "quietly confident" that it has legal priority. Eutelsat registered its frequency claim with the International Frequency Regulation Board in Geneva (part of the ITU) for 80 or 85cm dishes, ahead of Astra's claim for the same frequencies with 60cm dishes.

Eutelsat could thus, in the unlikely event of it becoming necessary, claim priority rights and force Astra to stop transmitting on the affected frequencies. But Astra's viewers who suffer interference will only be able to complain if they are using 80 or 85cm dishes - which no-one will be because this size exceeds the 70cm maximum now specified by the Department of the Environment.

Astra makes the valid point that its commercial success is largely due to the use of small dishes. It is out of the question to ask the four million people in Europe with small dishes to replace them with larger models.

Astra is very cagey about the channels at risk. "It depends on how Eutelsat deploys its traffic," says Koen van Driel, Astra's Commercial Director. "However British channels will almost certainly not be affected. Technical solutions exist to allow for an interference free environment with 55/60 cm dishes".

Eutelsat agrees that no-one will really know what the problems are until both satellites are in orbit and transmitting on the same frequencies. But Eutelsat says it expects a frequency clash on six of Astra 1B's transponders, with serious problems on only a couple.

But now high end Swiss hi-fi company Revox is selling the £289 ultra-compact Innova antenna. Its aperture is just 34cm and is the first domestic aerial to work on horn principles. The smaller the aperture of a satellite aerial, the wider its beam of acceptance will be. This holds good whether the aerial is a reflector dish, flat plate collector or horn aerial like the Innova.

Peter King of Innova expects interference

risks on three transponders. And the subject is closer to Innova's heart than anyone else. The 34cm aperture brings a beam width of over 5° compared to 3° for the 60cm dishes recommended by SES. The wide beam brings a reduction in the strength of the signal reaching the LNB, and a greater risk of interference from Eutelsat II F3.

"The Innova does not meet the Astra specification", says King. "We make no bones about it and have had many discussions with SES at Betzdorf. We cannot change the laws of physics. But neither do a lot of dishes. SES is in a difficult position here. Market research shows that the public wants smaller dishes. For the satellite market to explode we must have smaller dishes. And obviously SES would like to see the market explode."

"Using smaller dishes means there is a risk of interference but it can be avoided if Astra and Eutelsat negotiate and choose their frequencies carefully. And at worst there is a risk of interference on only three of Astra's 48 channels."

"With surplus capacity - and you only have to look at the unused channels on Astra 1B to know that there is surplus capacity - there is no need to use those three channels yet".

King does not know which channels are at risk, either. "Someone inside Astra must know" he says. "But of course they won't say. No-one would ever rent them if they knew, would they?"

SES can delay the crunch because it has not yet rented out all the available Astra channels and can thus steer broadcasters clear of those at risk. But when demand for channels exceeds supply, some of Astra's viewers will start seeing double pictures. This could happen if the European Commission pushes through its plan to force satellite broadcasters, such as BSkyB, to broadcast the same programmes simultaneously in both old pal and new mac systems. There will be no spare transponders on Astra and SES will be forced to allocate those at risk of interference.

Barry Fox

### 3-D chips use light, not wires

Researchers in Japan have proposed a means of using light to link multistorey memory cells. Mitsumasa Koyanagi working with a group at the Research Centre for Integrated Systems, Hiroshima University intends to stack memory chips on top of each other rather than putting the circuits alongside on large silicon die.

Each layer of the stack is a fully fabricated chip, separated top and bottom from the next device by a layer of quartz glass.


The vertical connections are made by laser diodes and photo detector cells integrated into the die. The backs of the wafers are polished to reduce the depth of

the substrate down to 5µm so that the light from the laser can pass through to the next layer.

The polishing also creates a surface underneath the wafer which can be joined to the quartz glass deposited over the active parts of the device. The bottom of the wafer is held by vacuum chuck while the next layer is lined up by microscope.

At the moment, the group has produced test silicon but has not actually built the multilevel device. The final product should allow a block of 512 bits of data to be transferred in 16ns, an equivalent speed of 128Gbit/s.

Rob Causey

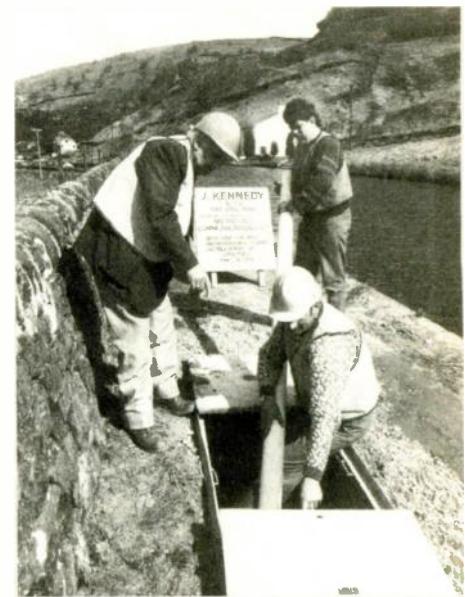

**190-year-old Rochdale canal is once again to become part of a national communication network. But this time telephone traffic rather than cargo barges will be carried. It was actually the ease of laying the cable under the towpath that attracted Mercury Communications to link Leeds and Manchester in this way. The only hazard was discarded shopping trolleys.**

### Single chip Nicam

Toshiba Semiconductor is now producing a single-chip Nicam system. The TB1204N/F is a bi-cmos device which integrates all the functions of Toshiba's earlier Nicam chip-sets to decode the UK's terrestrial Nicam 728 system.

The device demodulates a quadrant phase shift keyed signal into a 728Kbit/s pulse-code modulated data stream. The resultant signal contains sound information for left and right channels decompressed from 10 to 14-bit resolution. The chip then converts it into an analogue audio signal.

The demodulator features an automatic gain control circuit and uses phase synchronous demodulation by baseband PLL. All necessary filters are included.

The Nicam decoder stage performs frame synchronisation on the 728Kbit/s data stream, and de-interleaves it using 3.5Kbit of on-chip s-ram as temporary storage. The decoder then expands the resultant samples to full 14-bit resolution.

The resultant digital sound information is then processed by a two-times oversampling filter, before passing through a digital de-emphasis network.


This final digital signal is converted to an analogue audio signal by an on-chip sigma-delta D-to-A with a 182 times oversampling characteristic.

### Magnetometer cores

Cores for the Fluxgate magnetometer (EW+WW Sept 91) can be obtained directly from the author, Richard Noble. Please phone for details on 0873-890367.
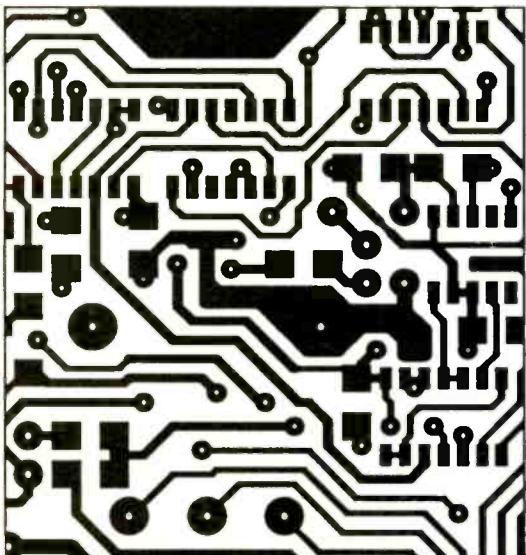
# EASY-PC, SCHEMATIC and PCB CAD

**Over 9000 Installations  
in 50 Countries Worldwide!**




- Runs on:- PC/XT/AT/286/386/486 with Herc, CGA, EGA or VGA display.
- Design:- Single sided, Double sided and Multilayer boards.
- Provides Surface Mount support.
- Standard output includes Dot Matrix / Laser / Inkjet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Superbly easy to use.
- Not copy protected.

**Still Only £98.00!**


Plus P&P+VAT

**BRITISH DESIGN AWARD 1989**

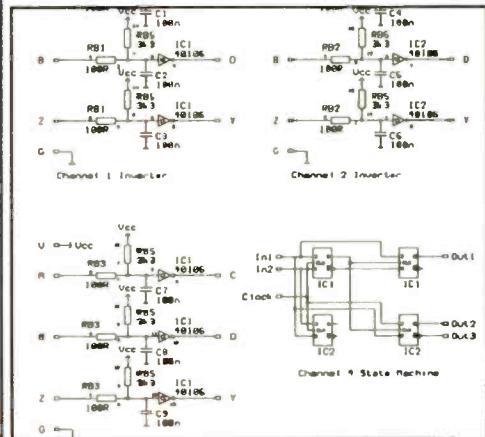


**Options:  
1000 piece Symbol Library £38, Gerber Import facility £98**

**DIGITAL SIMULATION £195**

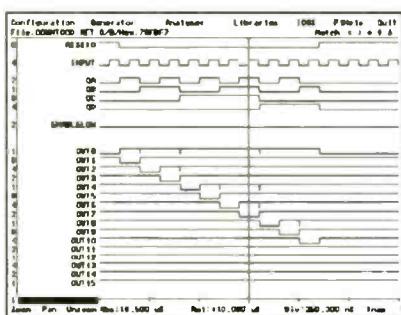


- At last! A full featured Digital Circuit Simulator for less than £1000!
- PULSAR allows you to test your designs without the need for expensive test equipment.
- Catch glitches down to a pico second per week!
- Includes 4000 Series CMOS and 74LS Libraries
- Runs on PC/XT/AT/286/386/486 with EGA or VGA.
- Not Copy protected.

**ANALOGUE SIMULATION £195**

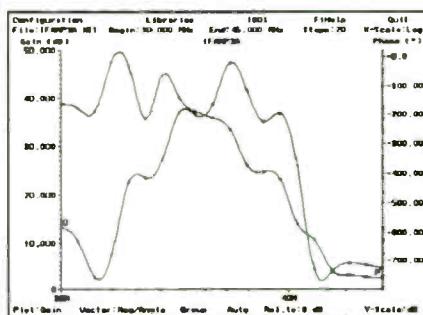

- NEW powerful ANALYSER III has full graphical output.
- Handles R's, L's, C's, BJT's, FET's, OP-amp's, Tapped and Untapped Transformers, and Microstrip and Co-axial Transmission Lines.
- Calculates Input and Output Impedance, Gain & Group Delay.
- Covers 0.001 Hz to > 10GHz
- Runs on PC/XT/AT/286/386/486 with EGA or VGA.
- Not Copy protected.

**SMITH CHART CAD £195**

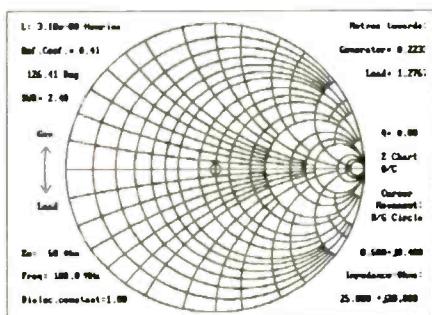

- Z-MATCH II simplifies RF matching and includes many more features than the standard Smith Chart.
- Handles transmission line transformers, stubs, discrete components, S Parameters etc.
- Supplied with many worked examples.
- Superbly easy to learn and use.
- Runs on IBM PC/XT/AT/386/486, CGA, EGA, VGA.
- Not Copy protected.

For full info Phone, Fax, or use enquiry card!

**Number One Systems Ltd.**

• See us at DES, Stand 1214, 8-11th October.

• See us at Desktop CAD, Stand 137, 5-7th November.

REF: WW, HARDING WAY, ST.IVES, HUNTINGDON, CAMBS, ENGLAND, PE17 4WR.

Telephone: 0480 61778 (7 lines) Fax: 0480 494042

International: +44-480-61778, Fax: +44-480-494042 ACCESS, AMEX, MASTERCARD, VISA Welcome.

CIRCLE NO. 149 ON REPLY CARD

# REGULARS

## RESEARCH NOTES

### Harnessing H-bombs to heat the home?

No sooner has the cold fusion saga passed into history than another fusion prospect has emerged. But this time what is being seriously suggested by two physicists at the Lawrence Livermore National Laboratory is the idea of letting off a series of small H-bombs in an advanced underground cavern and collecting the energy released.

A proposal for (very) hot fusion power is not as crazy as it sounds. Writing in MIT Technology Review (July 1991), Abraham Szoke and Ralph W Moir describe in detail their proposal for PNE (peaceful nuclear explosives), an idea put forward originally in the early 1960s by Albert Latter, then of the Rand Corporation. What is new is that this latest scheme is fully engineered and takes into account the need to reprocess the fusion and fission products.

The reactor vessel is a steel-lined chamber in which small bombs of around one kiloton yield are let off about once every 20 minutes. At the top of the chamber is a sort of elaborate shower head which injects droplets of a molten salt just before each

explosion. The liquid traps the energy which then boils water in a heat exchanger and produces steam to drive a turbine in the usual way. According to Szoke and Moir the system could easily produce 1000MW of electricity.

Calculations suggest that controlling the underground explosions would not be nearly as difficult or dangerous as it sounds: most of the explosive energy would be absorbed by the falling droplets. And if the worst did happen and the vessel were to burst, most of the radioactivity would be contained underground. What is more, because each bomblet is injected individually, there could be no thermal runaway of the sort that happened at Chernobyl or Three Mile Island. Szoke and Moir do not make extravagant claims for the safety of this arrangement but reckon that it would compare favourably with today's conventional nuclear power stations. The greatest danger derives from the fact that the reprocessing component of the plant has the inherent capability to manufacture weapons-grade plutonium. But this would be true of

any fusion power station.

Szoke and Moir acknowledge that PNE sounds a crazy method of generating electricity. Compared, though, with every other known method it comes out well in the calculations.

Fission power is no safer, fossil fuels produce carbon dioxide while photovoltaic, wind and wave energy are unsuitable for base-load generation. The real question is whether the public would ever accept canned H-bombs.

Technically the idea is simple and requires no additional engineering know-how. All the component systems are well tried and tested; so much so that the writers claim it would be possible to have a prototype up and running within ten years.


Crazy it may be, but is it any crazier than driving to the office propelled by conventional explosions in cans?

### Planet casts doubt

The first reasonably hard evidence for a planet outside our solar system was widely reported at the end of July. But behind all the hype and the speculation about life in outer space lies a fascinating research project which began back in 1985 at Jodrell Bank.

It all concerns radio pulsars – rapidly rotating neutron stars that emit beams of radiation in the direction of their magnetic poles. Each time the star rotates and the beam crosses the line of sight to Earth, we receive a radio pulse. When the first pulsar was discovered, the regular pulse repetition rate was of course seized upon as evidence of alien intelligence! Some 500 of these pulsars are now known and the main interest lies in measuring the infinitesimally small changes in their periodicity, ie the rate of spin-down. The measurement gives radio-astronomers insight into the stellar dynamics and enables them to refine theories of how pulsars form in the aftermath of supernova explosions.

Of 40 pulsars currently being observed

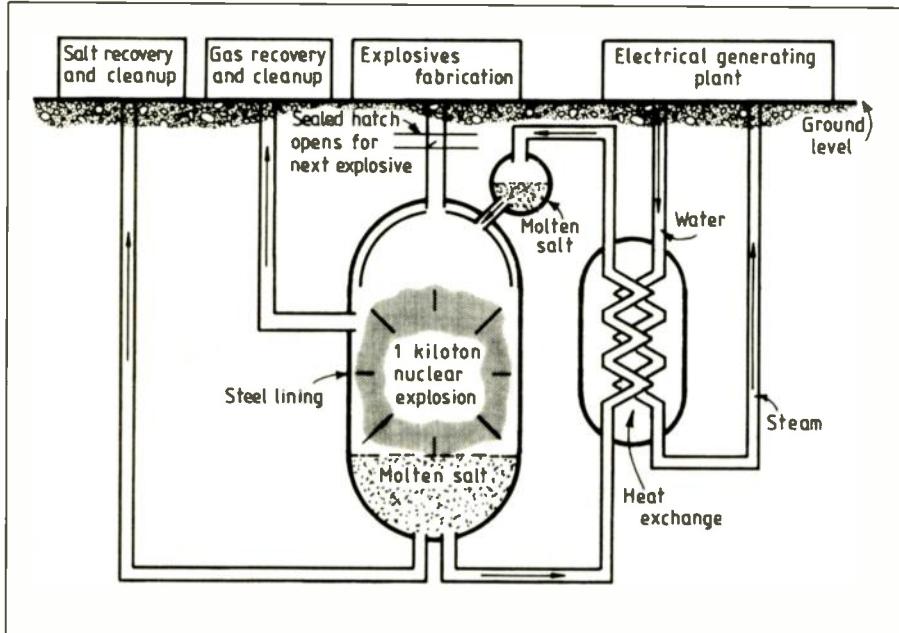

Earthshaking proposal: could nuclear explosions be used to generate power?

## Imaging upset for IC


An imaging technique which will pinpoint weaknesses in integrated circuits caused by ionising radiation has been developed by researchers at Sandia National Laboratories. The technique, called single event upset (SEU) imaging, is so precise that it can isolate malfunctions in single transistor components.

Single event upsets are temporary but critical disruptions in an integrated circuit's memory cells; they result from a collision with high-energy cosmic rays. For example, single event upsets occurring in the Hubble space telescope are causing one of the focusing circuits to lose data on a regular basis.

As advances in fabrication technology bring more densely packed ICs and a reduction in size, the problem of radiation-induced failures has become more acute.

Sandia researchers have used ion microbeam techniques to study generation of radiation-induced upsets and have produced micron-resolution "maps" of where upsets occur. The maps are compared with the circuit designer's blueprint of the chip to pinpoint the upset location.

Aim of the technique is to diagnose

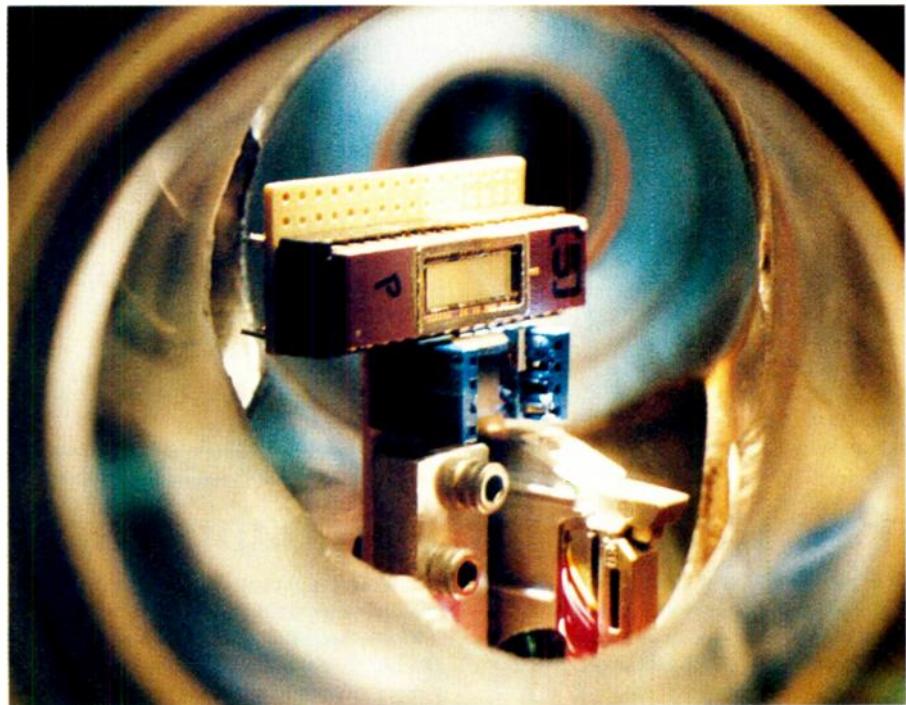

weaknesses in high-performance integrated circuits so they can be redesigned for greater radiation hardness.

Until now, traditional whole-chip radiation testing has been used to identify malfunctioning circuit elements, requiring measured values and complex calculations. But, unlike with SEU-imaging, locations of the upsets cannot be precisely determined or actually imaged.

When an energetic ion strikes and penetrates the silicon of an integrated circuit, it leaves a wake of dislodged, excited electrons as well as the holes that they previously occupied. These electrons can group together and create a collection of charge. If this persists for a sufficient length of time it can induce the memory cell to change its stored logic state.

Only certain circuit components or regions within components are susceptible to upset. But because the microbeam can individually irradiate a single memory cell, transistor or transistor component (such as drains or gates), SEU-imaging can be used to image upset-prone microscopic regions.

The ion beam is scanned across the circuit's surface and can give rise to two signals: emission of electrons from the target (when the ion strikes the surface) and generation of a malfunction, or upset in the target circuit's operation (as the ion

*SEU imaging: ion microbeam enters the target chamber (from right) and focuses on an IC mounted in the chamber to produce a "susceptibility" map.*

penetrates the chip).

One-micron resolution of the technique means it may have application in other radiation-hardness characterisations carried out at chip level.

For example, measurement of total dose effects – the cumulative effect of ionising radiation – to a single memory cell can be achieved using SEU-imaging.

It could also be used to verify software codes used to simulate radiation upset processes.

## on universal theory

at Jodrell Bank between frequencies of 1400 and 1600MHz, one code-named PSR 1829-10 aroused particular interest. Discovered in 1985 its behaviour is markedly different from the others.

Instead of spinning at a steadily changing rate, PSR 1829-10 slows down and speeds up with a period of six months. This regular disturbance, according to the Jodrell team (Nature, Vol 32 no 6333) can only be consequence of the gravitational effect of a planet with about 12 times the mass of the Earth.

This evidence for a planet in orbit around the pulsar is obviously indirect because there is no optical method of detecting it. (Ordinary telescopes can not produce anything more than a point image of even the nearest star). But what is really intriguing is how a pulsar could possibly ever acquire a planet.

Either the planet somehow survived the cataclysmic heat of the supernova which (on present theory) produced the pulsar, or else PSR 1829-10 evolved in some way as yet unknown.

## Earth free antenna gives good response


Directional HF loop antennas have been around for a long time and can be configured in omni-directional, bi-directional or cardioid radiation patterns. Adjusting the value of R (see over) gives a good broadband cardioid response, but only if the earth connection is good. Otherwise the antenna tends to have a figure-of-eight response regardless.

But P V Brennan and Y Valverde of the

Department of Electronic and Electrical Engineering at University College London describe (Electronics Letters, Vol 27 no 1) a new balanced version of the antenna which needs no earth at all.

The mirror-imaged design (Fig. 2) was arrived at by reflecting the antenna in the ground-plane and feeding the balanced output via a 180° hybrid into an MMIC amplifier.

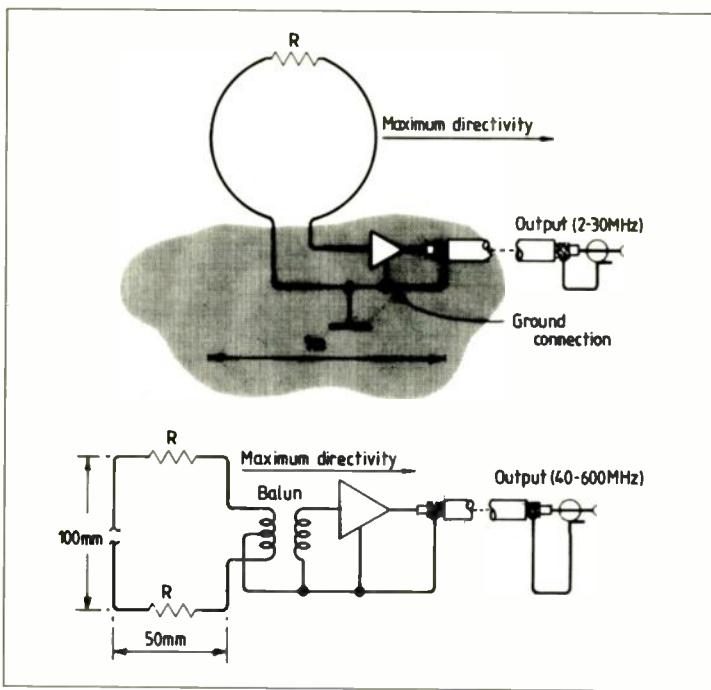As can be judged from the dimensions and components, the experimental model was a scaled down version operating at VHF and UHF frequencies – partly for ease of construction and partly to get the whole test apparatus into a



small anechoic chamber.

Over the range 150-600MHz the antenna maintains a good cardioid radiation pattern without any earth, either real or capacitive. Front-to-back ratio is 17dB at 200MHz and the response drops to a perfect theoretical -6dB at 90° to the direction of fire.

Brennan and Valverde say that even without any optimisation, a front-to-back ratio of 10dB is maintained across the whole 4:1 frequency range. They add that if the value of R is trimmed or replaced with a reactive network, it should be possible to achieve a stable pattern, regardless of frequency.

## Fair hearing for six channel ear

**T**he world's most realistic and effective artificial ear could be the result of collaborative research at a number of institutes in Massachusetts and North Carolina. The cochlear implant, to give it its proper name, has been designed to give a useful degree of hearing to people who are profoundly deaf, usually as a result of damage or disease to those natural transducers, the hair-cells of the cochlea.

In practice the ear functions as a compressor, a limiter and a multi-channel filter feeding a nerve bundle comprising 30,000 individual parallel fibres.

According to Blake S Wilson, principal author of the latest research (Nature, Vol 352 no 6332), the history of electrical stimulation of auditory nerves goes back to the 18th century when Alessandro Volta (of voltaic pile fame) connected one of his high-voltage batteries to each

ear. Volta apparently heard gurgling noises before being knocked to the floor!

More recently the approach has been the more subtle one of taking a signal from a microphone, compressing it, feeding it through four band-pass filters and applying it via surgically-inserted electrodes to the basilar membrane in the cochlea (Fig. 1).

Although six channels can only connect to a few of the 30,000 parallel nerve fibres, the results have been surprisingly good in practice. Patients vary markedly in how successfully their brains adapt to this wholly different input, but given help from lip reading, they can sometimes make good sense of what they hear.

One big problem, inherent in the system, that Blake Wilson and his team have had to overcome is crosstalk between channels.

Although present systems still use only six channels compared to the 30,000 in nature, there is nevertheless a strong tendency for the electric fields at the electrodes to interact and make the system behave as if there were fewer channels still.

What Wilson's team has done is to develop a system in which the processed multi-channel audio is chopped up into trains of fast interleaved pulses, none of which coincide (Fig. 2).

This continuous interleaved sampling (CIS) ensures that no two electrodes are simultaneously stimulated. The result is

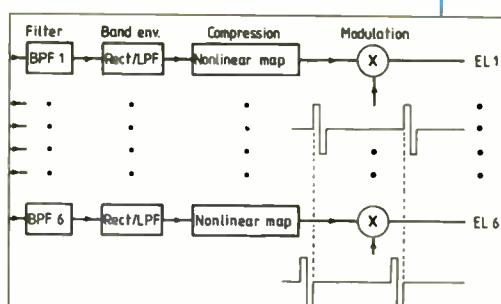


Fig. 2. Continuous interleaved sampling ensures that no two electrodes are simultaneously stimulated, eliminating crosstalk.

virtual elimination of crosstalk.

As for the patients fitted with the new system, Wilson says: "All the subjects we have studied, lost their hearing relatively late in life, so they have a good recollection of what speech sounded like with normal hearing. However, all of them have told us that the new strategy provides a highly intelligible representation of speech. It is nearly normal, but not completely normal".

Some subjects have reported that it sounds a little thin compared with what they remember with normal hearing. Nevertheless they have found speech to be intelligible without the adjunct of lip reading – a remarkable feat in view of the limited number of electrodes and the crudeness of the representation even with the new strategy.

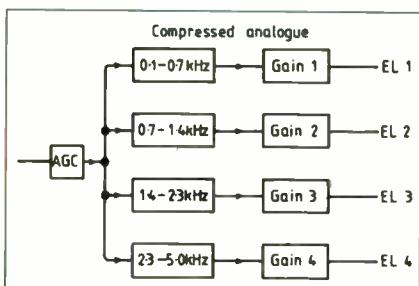



Fig. 1. Crosstalk is a problem with a compressed analogue approach.


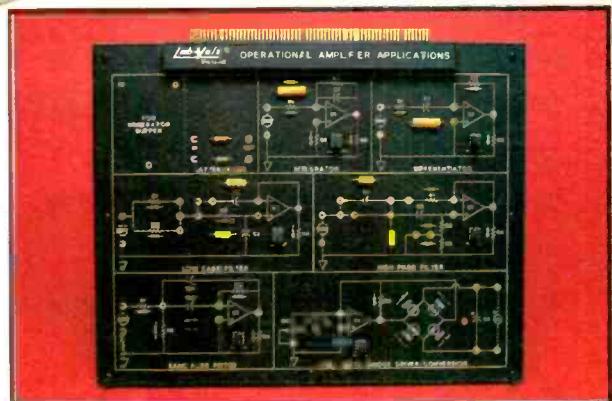
## **Lab-Volt® technology teaching technology**

The award-winning F.A.C.E.T. training system from Lab-Volt integrates software, hardware and courseware into a complete computer based training laboratory. It combines the best aspects of manual instruction with interactive, computer based learning.

F.A.C.E.T. means Fault Assisted Circuits for Electronics Training — learning through fault simulation and circuit modification. The modular hardware allows competency based teaching in all major areas of analogue and digital electronics from basics to advanced concepts. Your training department decides the curriculum.



Each F.A.C.E.T. module comprises a number of clearly identified circuit blocks with highly accessible circuit nodes. Connections are made with jumper leads.

Please complete the coupon for further information

NAME .....

ORGANISATION .....

POSITION .....

ADDRESS .....

.....

.....

PHONE .....

EWW010/91

Lab-Volt (UK) Ltd, 28 Stephenson Road, Industrial Estate, St. Ives Cambs, PE17 4WJ England. Tel:(44) 0480 300695. Fax: (44) 0480 61654

CIRCLE NO. 148 ON REPLY CARD

# ACTIVE FILTERS

**A choice of useful active filter systems is available to the linear circuit engineer but circuit details are not easily found, even in comprehensive text books. Here John Linsley Hood surveys the most useful layouts in this field.**

Often in linear electronic circuit design enhancement, or diminution, of one part of the frequency spectrum is required in relation to another. For example, in replay systems for gramophone records, it may be preferable to lessen some of the very low frequency rumble type noises which can occur due to worn turntable bearings, usually on replay but sometimes even when the disc itself was cut.

Or perhaps it becomes desirable to remove the annoying high pitched whistle, so prevalent on the reception of signals in the short-wave bands, due to the 8kHz spacing of adjacent transmitter carrier frequencies. In both cases, other parts of the frequency passband should pass through the circuit with little or no attenuation.

Such circuit systems are usually classed as filters, and may carry additional descriptive labels, such as lowpass, highpass, bandpass, notch, or frequency selective, depending on type of function.

A convenient distinction can also be drawn between passive circuits – those built up from resistors, capacitors and inductors, on their own – and active circuits, where some amplifying or impedance converting device is included, usually to improve performance.

The simplest and most primitive form of filter for this kind of application is a simple *RC* or *LR* network (Fig. 1) in which the turnover frequency,  $f_t$ , at which the gain will have fallen by -3dB, will be defined by the equation:

$$f_t = 1/(2\pi CR) \text{ or } f_t = R/(2\pi L)$$

This type of passive filter is simple and cheap, but its out-of-band attenuation rate is not very high (Fig. 2) so that if, for example, the aim was to reduce an 8kHz whistle to 1/20th of its original level, (-26dB), it would be necessary to start rolling off the HF response of the system some 4.3 octaves below 8kHz, (i.e., 406Hz).

Putting two such *RC* or *LR* filter networks in series (Figs. 1b, 1d) will increase the

attenuation slope to -12dB/octave, as shown in the dashed line in Fig. 2, but the output will then be -6dB down at  $f_t$ .

Taking the same example as before, reducing an 8kHz whistle to 1/20th of its original size will now take some 2.2 octaves, which means that it would be necessary to accept an initial -6dB point at 1.78kHz. Still not very good, but a step in the right direction.

What is needed is a way of contriving a ruler flat frequency response right up to some point at which the system transmission starts to fall. This can not be done with *Rs* and *Cs* on their own, but combining an *RC* and an *LR* type of circuit allows an improvement to be made.

On its own, the circuit of Fig. 3a, - because there are now two "reactive" components, (one *L*, one *C*) - will give a -12dB/octave slope, with an  $f_t$  of 1kHz. It also shows a small (about 1dB) peak in its response curve just before the transmission begins to fall off, as shown in Fig. 4a,



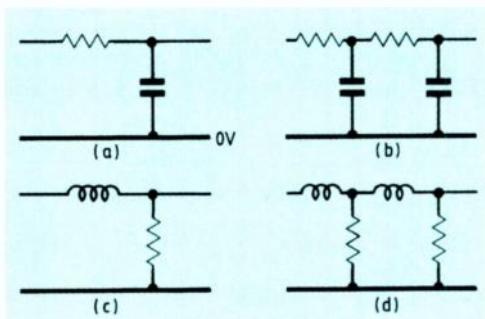


Fig. 1. Simple first and second order lowpass LR and RC passive filters.

because of the slightly under-damped series resonance of  $L_1$  and  $C_1$  acting as a tuned circuit.

If this damping is reduced a little more, say by increasing  $R_1$  to 14k, ( $/2 \times 10k$ ), the hump can be increased to +3dB (Fig. 4b). Since a straight CR network will give a -3dB point at  $f_t$ , by putting these two circuits in series (Fig. 3b), it is possible to get rid of the hump in the LRC response curve, as well as adding another -6dB/octave to the attenuation rate of the filter.

The approach does work, as shown by the frequency response curve of Fig. 4c, which indicates a -18dB/octave, (-60dB/decade), attenuation slope. But the impedance of the second half of the circuit should be made a good bit higher than the first, to make sure that it does not affect performance of the first part of the circuit, shows. This takes us nearer to the ideal type of filter characteristic (Fig. 4c), but at the expense of introducing a certain amount of "ripple" in the frequency response, just below the turn-over point.

Returning to the earlier example, such a filter could reduce the amplitude of an 8kHz whistle by a factor of 20x while still retaining a flat response to 2.7KHz, or one which was -6dB down at 3.4KHz.

Still not perhaps the best, but certainly in the right direction.

#### Filter response types

The most widely used classifications of filter characteristics are Chebyshev, Butterworth and Bessel.

Chebyshev covers filter types where design has been chosen to give maximum attenuation rate possible for that circuit, even though this leaves some unevenness in the transmission characteristics at a part of the response; ideally, it should be ruler flat. With this type of filter, it is customary to specify the amount of ripple as "±dB".

The second class of filter is the Butterworth, which broadly refers to those filter types designed to give maximum flatness in the pass-band, even if this means accepting a somewhat lower attenuation rate beyond this point.

The third broad class of filter is the Bessel, where the phase shift alters linearly as a function of frequency, leading to a nearly constant circuit time delay, and minimis-

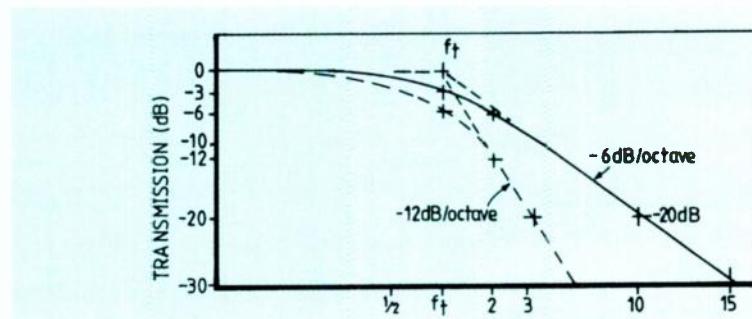


Fig. 2. Characteristic attenuation slopes of simple RC and LR filters.

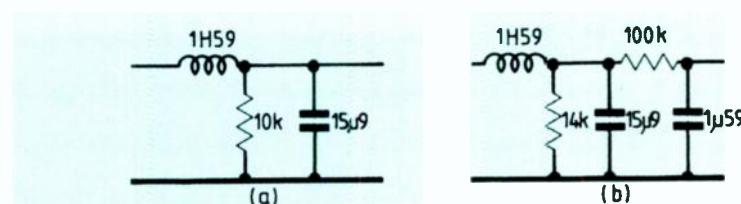


Fig. 3. Second order and third order LCR filters.

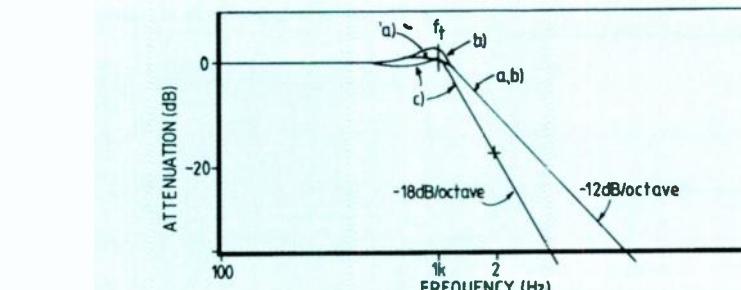


Fig. 4. Possible frequency response curves from 2nd and 3rd order LCR filters.


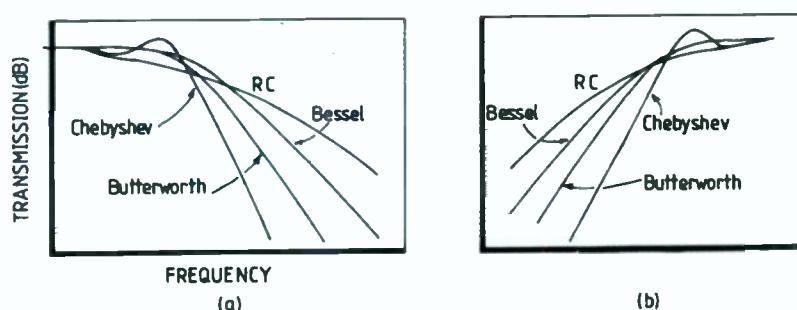


Fig. 5. General classification of filter types.

Fig. 6. Circuit rearrangements to give highpass CR and RL filters.

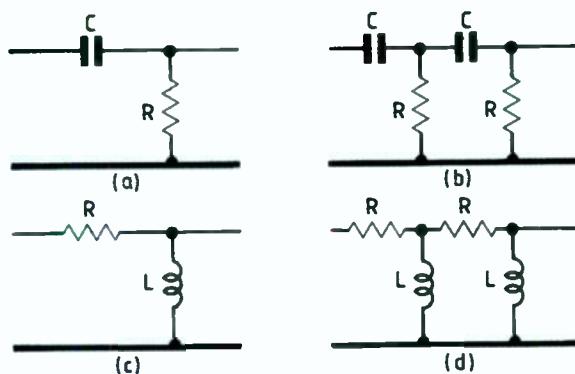

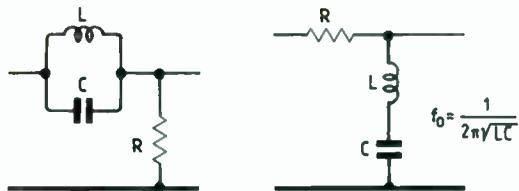


Fig. 7. LCR type notch filters.

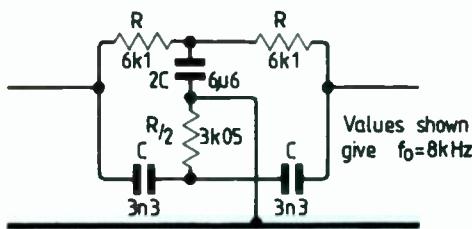


Fig. 8. The parallel-T notch filter.

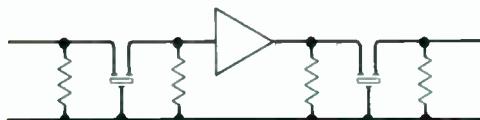


Fig. 9. Some of the possible forms of RF LC bandpass filters.

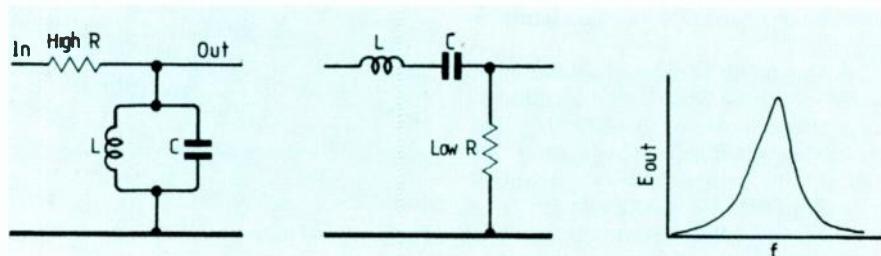


Fig. 11. Tuned response type LC filters.



Fig. 10. Typical modern bandpass RF filter design for VHF FM or TV using IC gain blocks and ceramic ladder filters.

ing distortion of step-function type waveforms.

I have shown the type of transmission responses for these three filter characteristics, along with that for a simple *RC* arrangement, in Fig. 5a. It will be apparent that all of the lowpass filter types which I have, so far, described can be changed into highpass types, giving the kinds of transmission response shown in Fig. 5b, simply by interchanging the positions of resistors and capacitors, as I have shown in Figs. 6a - 6d.

#### Notch filters

Returning again to the problem of the 8kHz whistle in short-wave broadcast reception, another useful possibility is to use a "notch" filter, tuned to cut out the offending signal, on its own.

The *LCR* arrangement shown in Fig. 7 would work, using either a parallel resonant circuit in series with the signal path, or a series resonant circuit across it. But these would need largish values of inductance, with very good Q characteristics, (low resonant energy losses) – both difficult and expensive. A much more attractive layout is the "Parallel T" (sometimes also called the "Twin T") circuit shown in Fig. 8.

Provided that the component values are

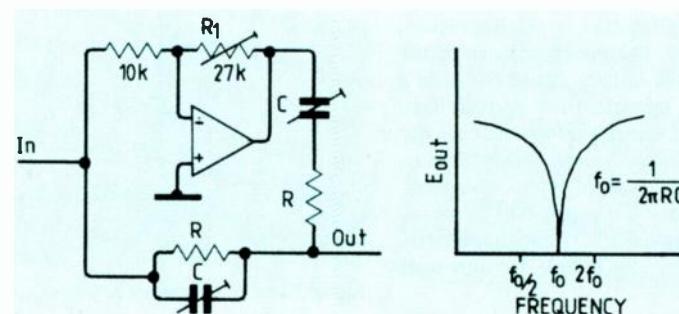


Fig. 12. Wien bridge notch filter and its frequency response.

accurate, this will give a high degree of rejection of an unwanted signal at a frequency given by:  $f_0 = 1/(2\pi RC)$ , requiring the component values shown in Fig. 8 for a notch at 8kHz. This would give a -6dB response at 4kHz; but there are ways to sharpen up the notch (see "active systems").

#### Bandpass filters and tuned response

Best known of the bandpass filters are those which used to be built up from a pair of coupled tuned circuits, (Figs. 9a-9d), and used in the IF stages of old-fashioned radio receivers - nowadays they either don't bother, or use ceramic ladder resonators instead, for example the circuit of Fig. 10.

I suppose such a bandpass system could be made with large inductors – for use in lower frequency applications – but I have never seen it done.

Just connecting a pair of *RC* highpass and lowpass filters in series would work, but not very well, so this kind of filter is mainly made up with active circuit systems.

Tuned response circuits can also be made with *Ls* and *Cs*, as in Fig. 11, but this type

of layout would mainly only be worthwhile at RF.

#### Active systems

Putting an amplifier or impedance conversion stage – and, for convenience, I have drawn all of these circuits with op amps – allows an enormous increase in scope in circuit design. For example, a quite useful notch filter can be made with an inverting 2x gain amplifier, coupled to a Wien network (Fig. 12.)

With a high impedance op amp output buffer, the variable capacitors can be air-spaced twin-gang capacitors, allowing the notch to be infinitely and delicately tunable. However, since it is unlikely that all other component values will be absolutely spot-on, it is sensible to make the gain of the amplifier somewhat adjustable, by  $R_{V1}$ , to allow the notch to be tweaked for maximum depth.

It is in L-P and H-P filters, though, that active systems really come into their own, since it is so easily possible to organise systems which will have a really flat frequency

# Beginner or advanced hobbyist EBBO® is the right system for you



Once hobbyists had to buy "professional" Solderless Breadboards paying "professional" prices, but now there is EBBO, a total Breadboarding System at a hobbyist's price. EBBO can be as simple or as ambitious as you want it to be, the only limit is your own imagination or skill.



Send for detailed colour catalogue and price list.

**AP Products Ltd**

28 Gold Street,  
Saffron Walden Essex CB10 1EJ  
Tel: 0795 26602 Fax: 0799 21408

CIRCLE NO. 124 ON REPLY CARD



## Signals Research Ltd DSP Systems Support

### AT LAST! A LOW COST HIGH QUALITY ENTRY PATH INTO THE FASTEST GROWING BRANCH OF ELECTRONIC ENGINEERING.

Beginners and experts alike can now exploit the power and flexibility of the cost-effective TMS32010 DSP in applications such as:

FFT analysis, adaptive filtering, real-time control and robotics.

- **POWERFUL MACRO ASSEMBLER AND LINKER**
- **SOPHISTICATED WINDOWS BASED SIMULATOR**

Package includes full feature macro assembler with C language expression evaluation and linker for modular system design. The simulator/debugger provides full processor simulation with the following facilities:

- ★ Mouse/Windows interface for easy operation
- ★ Full symbolic instruction disassembly
- ★ Sophisticated C language expression evaluator
- ★ Simple or expression qualified breakpoints
- ★ Full feature online assembler (labels allowed)
- ★ In-circuit emulator style memory and IO traps
- ★ INT/BIO hardware events are simulated
- ★ Map IO ports to keyboard, file or fill value
- ★ Graph main or data memories or IO port data



**Complete Package With 100 Page Manual Only £50+VAT**

**Demo Package Including Full Manual Only £5+VAT**

Please specify 3½ inch or 5¼ inch diskette

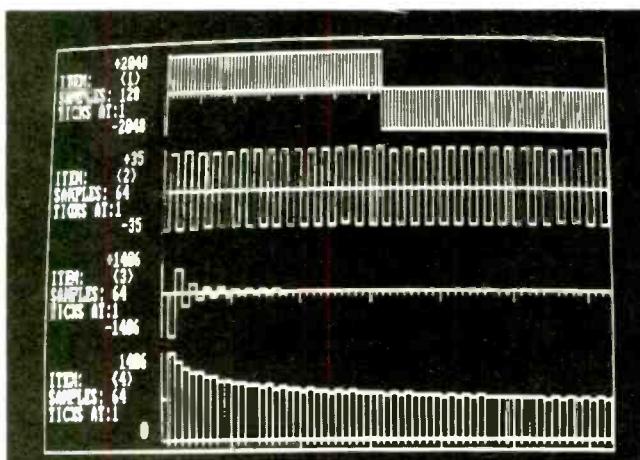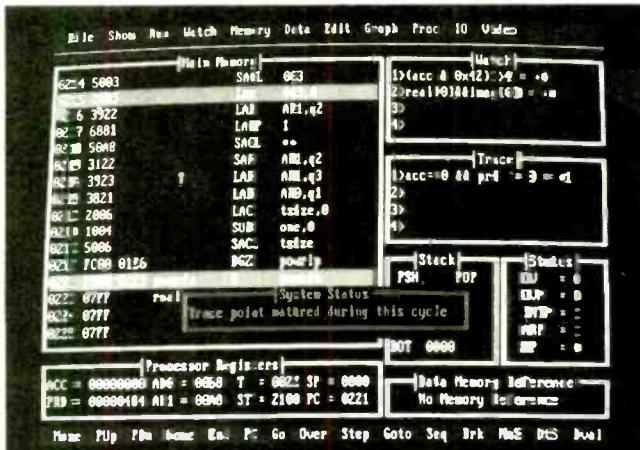**Signals Research Limited**

113/9 Bellevue Road  
Edinburgh EH7 4DG United Kingdom



CIRCLE NO. 125 ON REPLY CARD

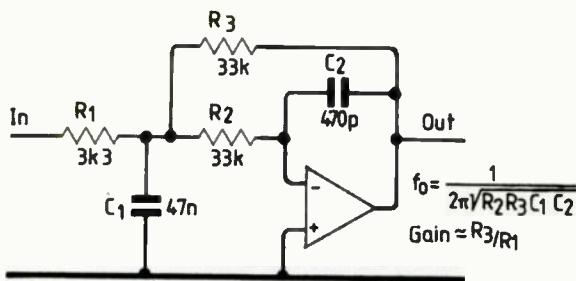


Fig. 13. Simple lowpass filter based on active integrator and overall loop negative feedback.

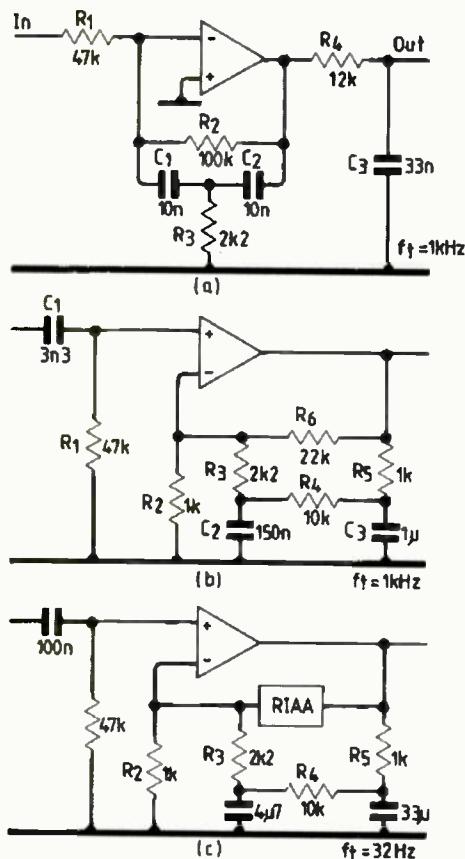


Fig. 14. Lowpass (a) and highpass (b) arrangements of "bridged T" filter.

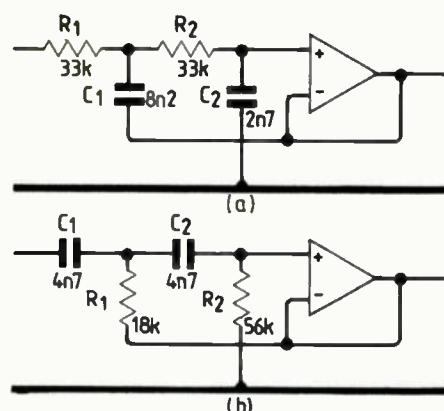


Fig. 15. Lowpass (a) and highpass (b) Sallen and key filters.

response right up to the point at which the gain starts to fall, and these can then be put in cascade to give as fast a fall-off in response as the designer needs.

The simplest of these is just an active integrator (an op amp with a capacitor between output and inverting input) with negative feedback applied overall, and an additional HF roll-off capacitor,  $C_f$ , connected to the OV rail from the junction of  $R_1$  and  $R_2$  (Fig. 13).

This gives a flat, Butterworth style fre-

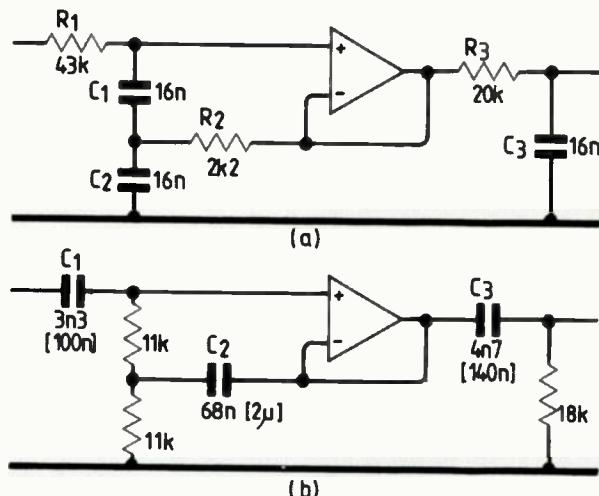


Fig. 16. Lowpass (a) and highpass (b) Bootstrap filters.

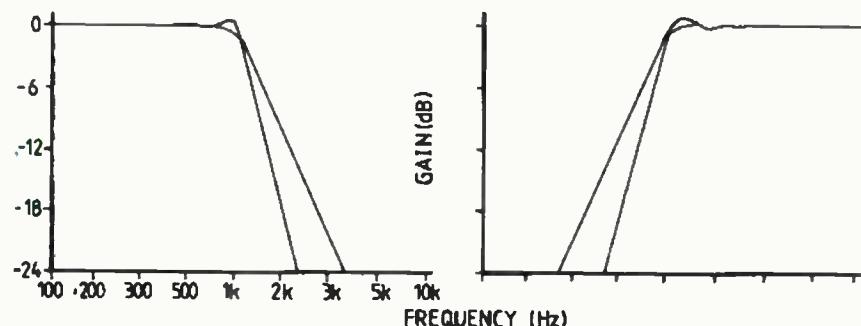


Fig. 17. Calculated frequency responses of circuits of Figs. 15 and 16.

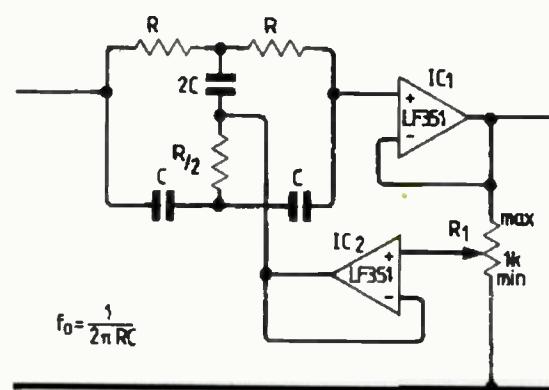


Fig. 18. Bootstrapped parallel T notch filter.

frequency response up to  $f_1$  and a -12dB slope beyond this. It can also give a gain determined by the ratio of  $R_2/R_1$ .

I have shown this circuit, and all of the others, with component values chosen to give an  $f_1$  of 1kHz, and have indicated on the diagrams the formulae by which different values of turn-over frequency, (or notch frequency, etc.) can be calculated.

The lazy option is just to alter frequencies by multiplying or dividing the values of one or other of the effective components - those shown in the formulae - by the amount necessary to shift the frequency from 1kHz to whatever other frequency is required.

Another useful family of filters, also giving some stage gain, is the type generally described as a "bridged T". I have shown circuits for low-pass and high-pass versions in Fig. 14. These are usually designed as Chebyshev type third-order filters, where the basic filter gives a hump in the frequency response, at  $f_1$ , and an RC network is then used to remove this, as well as give an additional -6dB/octave to the attenuation slope.

The high-pass version of Fig. 14b, was commonly used as a rumble filter circuit on gramophone record replay pre-amp inputs, because the RIAA frequency response correction network could be connected across it (Fig. 14c).

Nowadays designers usually prefer to make all filters capable of being switched out of circuit, so separate unity gain "Sallen and Key", or "Bootstrap" filter layouts would be chosen.

The Sallen and Key layout is widely used, since it can be organised around any convenient unity stage gain block. Even an ordinary emitter- or source-follower will do, and gives highpass and lowpass filters with a Butterworth style -12dB/octave frequency response. I have shown typical H-P and L-P versions in Figs. 15a and 15b.

The Bootstrap layout, (which I invented myself, or, more strictly, explored as a possible circuit transposition of a "bridged T" filter, and then analysed and developed), is similar in its gain-block requirements. But it is basically a third-order design, which can give a Chebyshev type -20dB/octave slope, with a ripple within  $\pm 1\text{dB}$ , for a Q value of 2. Altering the chosen Q will change the steepness of the cut-off and the amount of residual ripple. A pair of H-P and L-P designs is shown in Figs. 16a and 16b.

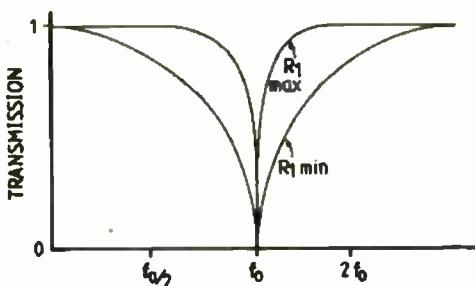


Fig. 19. Effect of setting of  $RV_1$  on frequency response.

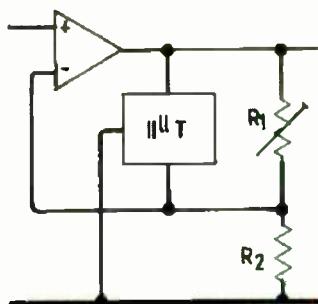


Fig. 20. Tuned response type filter based on parallel T.

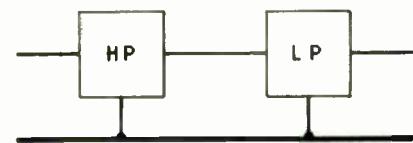


Fig. 22. Option for a frequency selective filter.

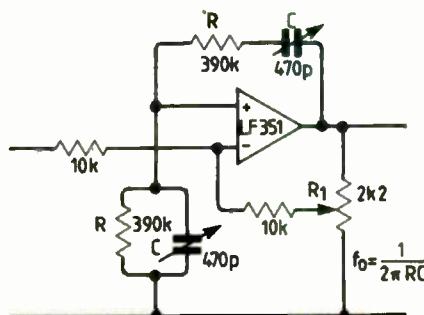


Fig. 21. Tuned response system based on Wien Bridge.



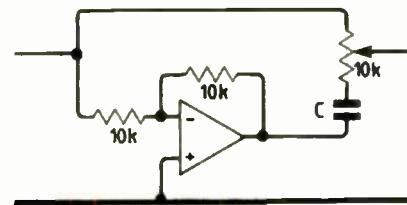


Fig. 23. The allpass filter

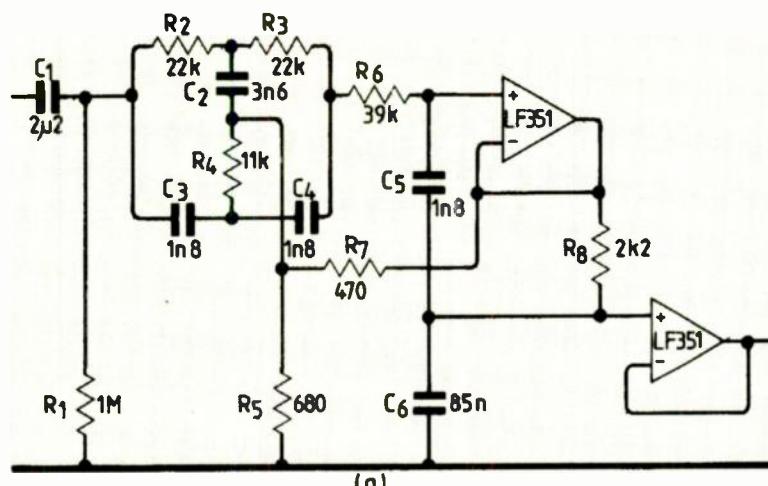


(a)

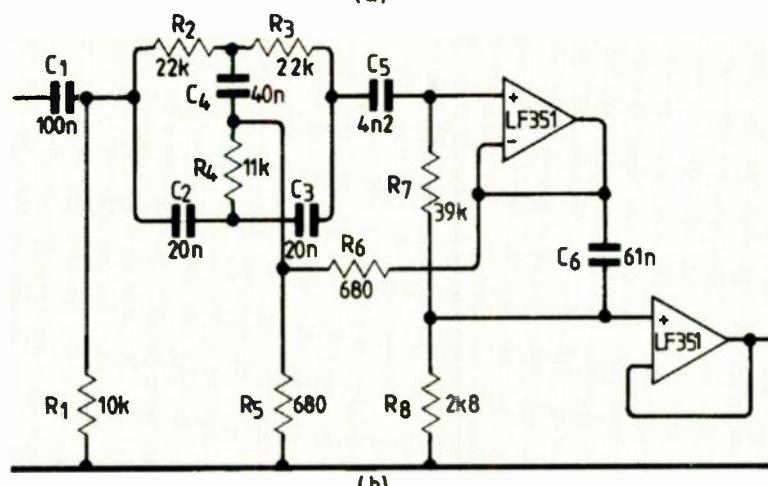

(b)

Fig. 24a. A very steep cut lowpass filter based on the combination of a Bootstrap filter and a paralleled T Fig. 24b Highpass version of Fig. 24a.

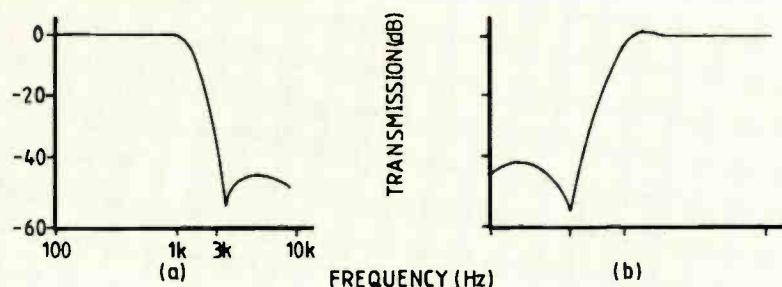

**Fig. 25. Frequency response of filter circuits of Figs. 24a-b**

Component values for a 30Hz H-P type audio amp rumble filter are quoted in the square brackets.

Some calculated frequency response curves for Sallen and Key, and Bootstrap filter designs are shown in Fig. 17.

As mentioned above, an impedance conversion block can also be used to sharpen up the notch of a Parallel T filter, by applying "bootstrap" type feedback around the loop. A circuit for this purpose is shown in Fig. 18, in which the steepness of the notch is adjustable by the setting of  $RV_1$ . Types of frequency response available are shown in Fig. 19.

Tuned response filters, giving a sharp peak in output at some chosen frequency, can also be made by putting a Parallel T fil-

ter in the feedback path of an amplifier (Fig. 20). In this case it is necessary to have a bridging resistor to prevent continuous oscillation, and the sharpness of the peak can be controlled by varying this - in this example by adjusting  $RV_1$ .

The Wien bridge circuit will also give a tuned response circuit (Fig. 21) and since its performance will only be limited by performance of the gain block, there isn't any particular reason why this type of circuit could not be used at radio frequencies, to give a "coil-less" radio tuner!

Once again, the sharpness of the peak, up to the point of continuous oscillation, is controlled by the value of  $RV_1$ .

An alternative, and slightly more docile, form of frequency selective filter is given by

putting an H-P and an L-P active filter in series (Fig. 22) as if to make an active band-pass filter, but with the values of  $f_c$  chosen to coincide.

If two high Q Bootstrap designs are cascaded like this, a very decent stable response peak, with steep out-of-band skirts can be obtained.

The "All-pass" design of Fig. 23 is not really within the class of filters, since it doesn't alter the gain but allows adjustment of the phase of the transmitted signal. Since all filters introduce phase shifts, of one frequency relative to another, this can be a useful tool for subsequent relative phase angle correction.

The final type of circuit is the combination of a standard H-P or L-P filter with a notch design. If the notch is chosen to lie at a suitable point above or below the turn-over frequency, depending on whether it is an L-P or H-P design, some quite impressive attenuation rates are possible.

A pair of Bootstrap + T filter circuits is shown in Fig. 24, with frequency responses indicated in Fig. 25. This type of frequency response is sometimes called a Cauer characteristic, a term which is used to describe a system in which the extent of attenuation in the stop band has also been exchanged for steepness of cut-off beyond the turn-over point.

## Logic Analysis breaks the £1,000 barrier

The Thurlby LA3200 and LA4800 logic analysers set new performance standards for low-cost logic analysers.

- 32 or 48 channels
- Multi-level triggering
- 100MHz asynch. capture
- Non-volatile data storage
- 5ns glitch capture
- Disassemblers for popular  $\mu$ Ps

The new LAs incorporate a vast array of features as standard and options are available to connect to a very wide range of target systems. Contact us now for full technical details:

**THURLBY THANDAR**

CIRCLE NO. 126 ON REPLY CARD

Thurlby-Thandar Ltd., Glebe Road, Huntingdon, Cambs. Tel: (0480) 412451



## 20MHz Function Generators

from £595

The Thurlby-Thandar 2001 represents the state of the art in bench function generators. Sine, square and triangle waveforms are available up to 20MHz with frequency, amplitude or offset displayed digitally. Full gating and start/stop phase control is incorporated.

The model 2002 adds a highly sophisticated sweep generator offering precise setting of sweep limits, sweep triggering and pen lift control. We offer a wide range of function generators from a very low cost 200kHz unit up to a fully programmable model with GPIB.

Contact us now for full technical details.

**THURLBY THANDAR**

CIRCLE NO. 127 ON REPLY CARD

Thurlby-Thandar Ltd., Glebe Road, Huntingdon, Cambs. Tel: (0480) 412451



## £1 BARGAIN PACKS

In fact, cheaper than £1 because if you buy 10 you can choose one other and receive it free.

- 5 13A spurs provide a fused outlet to a ring main where devices such as a clock must not be switched off. Order Ref. 2.
- 4 In flex switches with neon on/off lights, saves leaving things switched on. Order Ref. 7.
- 2 6V 1A mains transformers upright mounting with fixing clamps. Order Ref. 9.
- 1 6½in speaker cabinet ideal for extensions, takes our 6½in speaker. Order Ref. 11.
- 12 30 watt reed switches, it's surprising what you can make with these - burglar alarms, secret switches, relay, etc. Order Ref. 13.
- 2 25 watt loudspeakers two unit crossovers. Order Ref. 22.
- 2 Nicad constant current chargers adapt to charge almost any nicad battery. Order Ref. 30.
- 2 Humidity switches, as the air becomes damper the membrane stretches and operates a microswitch. Order Ref. 32.
- 5 13A rocker switch three tags so on/off, or change over with centre off. Order Ref. 42.
- 1 24hr time switch, ex-Electricity Board, automatically adjust for lengthening and shortening day. Original cost £40 each. Order Ref. 45.
- 1 Mini uniselector, one use is for an electric jigsaw puzzle, we give circuit diagram for this. One pulse into motor moves switch through one pole. Order Ref. 56.
- 2 Flat solenoids - you could make your multi-tester read AC amps with this. Order Ref. 79.
- 1 Suck or blow operated pressure switch, or it can be operated by any low pressure variation such as water level in water tanks. Order Ref. 67.
- 1 Mains operated motors with gearbox. Final speed 16 rpm, 2 watt rated. Order Ref. 91.
- 1 6V 750mA power supply, nicely cased with mains input and 6V output leads. Order Ref. 103A.
- 2 Stripper boards, each contains a 400V 2A bridge rectifier and 14 other diodes and rectifiers as well as dozens of condensers, etc. Order Ref. 120.
- 10 Twin screened flex with white pvc cover. Order Ref. 122.
- 12 Very fine drills for pcb boards etc. Normal cost about 80p each. Order Ref. 128.
- 2 Plastic boxes approx 3in cube with square hole through top so ideal for interrupted beam switch etc. Order Ref. 132.
- 5 Motors for model aeroplanes, spin to start so needs no switch. Order Ref. 134.
- 6 Microphone inserts - magnetic 400 ohm also act as speakers. Order Ref. 139.
- 4 Reed relay kits, you get 16 reed switches and 4 coil sets with notes on making c/o relays and other gadgets. Order Ref. 148.
- 6 Safety cover for 13A sockets - prevent those inquisitive little fingers from getting nasty shocks. Order Ref. 149.
- 6 Neon indicators in panel mounting holders with lens. Order Ref. 180.
- 1 In flex simmerstat - keeps your soldering iron etc. always at the ready. Order Ref. 196.
- 1 Mains solenoid, very powerful as ½in pull or could push if modified. Order Ref. 199.
- 10 Keyboard switches - made for computers but have many other applications. Order Ref. 201.
- 1 Electric clock, mains operated, put this in a box and you need never be late. Order Ref. 211.
- 4 12V alarms, make a noise about as loud as a car horn. All brand new. Order Ref. 221.
- 2 6in x 4in speakers, 4 ohm made from Radiomobile so very good quality. Order Ref. 242.
- 2 6in x 4in speakers. 16 ohm 5 watts so can be joined in parallel to make a high wattage column. Order Ref. 243.
- 1 Panostat, controls output of boiling ring from simmer up to boil. Order Ref. 252.
- 50 Leads with push-on ¼in tags - a must for hook ups - mains connections etc. Order Ref. 259.
- 2 Oblong push switches for bell or chimes, these can switch mains up to 5 amps so could be foot switch if fitted into mattress. Order Ref. 263.
- 1 Mini 1 watt amp for record player attached to unit that will also change speed of record player motor. Order Ref. 268.
- 3 Mild steel boxes approx 3in x 3in x 1in deep - standard electrical. Order Ref. 283.
- 50 Mixed silicon diodes. Order Ref. 293.
- 1 6 digit mains operated counter, standard size but counts in even numbers. Order Ref. 28.
- 1 In-flight stereo unit. Has 2 most useful mini moving coil speakers. Ex BOAC. Order Ref. 29.
- 2 6V operated reed relays, one normally on, other normally closed. Order Ref. 48.
- 2 Plug in relays with 3 changeover contacts. Coil operated by 12V DC or 24V AC. Order Ref. 50.
- 1 12V pcb mounting relay. 2 changeover. Order Ref. ??
- 1 Cabinet lock with 2 keys. Order Ref. 55.
- 4 Dials house switches or use them for any other low voltage application. Order Ref. 57.
- 1 Magnetic brake for stopping a motor or rotating tool. Order Ref. 66.
- 1 Time reminder. Set it for anything up to 60 minutes. Order Ref. 77.
- 1 Shaded pole mains motor. ½in stack so quite powerful. Order Ref. 85.
- 2 5in aluminium fan blades. Could be fitted to the above motor. Order Ref. ??

## — BARGAINS GALORE —

**BRITISH TELECOM POWER UNIT 206A** houses a 12v 6ah sealed lead/acid battery and not only charges it but ensures that it will not be over-discharged as directly voltage drops to 11.5v the output circuit is automatically disconnected. The unit if connected to the mains will charge the battery and keep it up to scratch. You can buy this in 2 ways, 1. just the unit for £16 (order ref 16P6B) or 2. unit with Jap-made 12v 6ah lead/acid battery £25 ref 25P13B.

**RESISTORS TEN A PENNY** and they are top class 5% carbon foil types either ½ or ½ watt rating. You can buy at this silly price on condition that you take a full reel, which is 3000 on a bandolier. You specify the value you want but please say if you can accept a near value as, although we have a very wide range, we do not have every value. Over a million in stock and if you will buy 50 reels or more you can have them at £2 a bandolier but please come to our store, pick them out yourself.

**LITHIUM BATTERIES** 3.5v penlight size, 2 mounted on p.c.b. with diodes, other bits. Lithium batteries as you may know are virtually everlasting (until they are put in circuit of course) so they are ideal for alarms and similar devices that do not draw current but do rely on it always being available. 4 panels that is 8 batteries altogether £2, order ref 2P258B.

**POWER SUPPLY WITH EXTRAS** output 12v lamp, mains input is fused and filtered and 12v output is voltage regulated, very well made on p.c.b., and also mounted on the board but easily removed are two 12v relays and a Piezosounder. Made for expensive equipment but never installed, price £30 ref. 3P80B.

**12 VOLT 1.9 AMP-HOUR** rechargeable battery by Jap YUASHA brand new, charged ready for use £6.50 each. Solar charger to house this and keep it ready £2.50.

**100 WATT MAINS TRANSFORMERS** all normal primaries: 20-0-20 volt 2½A 30volt 3½A, 40volt 2½A and 50volt 2A all upright mounting, all £4 each, good quantities in stock.

**COLOUR MONITORS** 12" high resolution in black metal case with mains p.s.u. built in, unused, but line rejects so will require servicing, hence offered at the very low pnce of £49.00 plus £5 delivery.

**PHILIPS 8" HIGH RESOLUTION MONITOR** black and white in metal frame for easy mounting, brand new still in makers packing, offered at less than price of tube alone, only £15 plus £5 delivery — good discount for quantities.

**16 CHARACTER 2 LINE DISPLAY** screen size 85mm × 36mm, Alphanumeric LCD dot matrix module with integral micro processor made by Epson their ref 16027AR brand £8 each, 10 for £70, 100 for £500.

**INSULATION TESTER WITH MULTIMETER** internally generates voltages which enable you to read insulation directly in megohms. The multimeter has four ranges, AC/DC volts, 3 ranges DC millamps, 3 ranges resistance and 5 amp range. These instruments are EX British Telecom, but in very good condition, tested and graded. OK, probably cost at least £50 each, yours for only £7.50 with leads, carrying case £20 extra.

**BRUSHLESS D.C. 12V FAN** tiny, only 60mm square, good air mover but causes no interference £8.00.

**2MW LASER Helium Neon** by PHILIPS, full spec, £30, power supply for this in kit form with case is £15.00, or in larger case to house tube as well £17.00. The larger unit, made up, tested and ready to use, complete with laser tube £69.00 plus £5 insured delivery.

**MAINS 230V FAN** best make "PAPST" 4½" square, metal blades £8.00.

**SOLAR CHARGER** holds 4 AA nicads and recharges these in 8 hrs., in very neat plastic case £6.00.

**SOLAR CELLS** with terminals for joining in series for higher volts or parallel for extra current. 100mA £1, 400mA £2, 700mA £2.75, 1A £3.50.

**SOLAR MOTORS** 1½-2½" precision made to operate from low current off solar cells £1.50, solar generator to drive this £7.00, has provision for battery back up when sun is not shining!

**AIR SPACED TRIMMER CAPS** 2-20 pf ideal for precision tuning u.h.f. circuits 25 each, 10 for £2, 100 for £15.

**1KHz TONE GENERATOR** this is PP3 battery operated and has a 1Khz output that can be continuous or interrupted at a rate variable by a panel mounted control. Constructed on a p.c.b and front panel size approx 105 × 50mm ex equipment but in as new condition £2 each.

**MAINS ISOLATION TRANSFORMER** stops you getting "to earth" shocks. 230V in and 230V out, 150 watt upright mounting £7.50.

**MINI MONO AMP** on p.c.b size 4" × 2" with front panel volume control and small screw hole for switch or tone control, output is 4 watt into 4 ohm speaker using 12V or 1 watt into 8 ohm using 9V. Brand new and perfect only £1 each or 12 for £10.

**5 RPM 60W MAINS DRIVEN MOTOR AND GEARBOX** this has a 3in square mounting plate and is 4in deep. It is a shaded pole motor. Price £5.

**POWER SUPPLY UNITS** mains in, dc out, based 4.5v 100mA regulated £1, 6v 200mA regulated £1, 6v 700mA £1, 9v 500mA £2, 12v 500mA £2, 12v 2A £5, 24v 200mA £2.

**TOROIDAL MAINS TRANSFORMER** with twin outputs, 6.3v 2amps and 12v 1amp, one use would be power supply, price £5.

**AMSTRAD POWER UNIT** 13.5w at 1.9A encased and with leads and output plug, normal mains input £5 each, 10 for £45.

**AMSTRAD 3.5 FLOPPY DRIVE** Reference FD9 brand new and perfect, £45.

**ATARI 64K COMPUTER** at 65K this is quite powerful so suitable for home or business, unused and in perfect order but less PSU, only £19.50. Handbook £5 extra.

**9" CATHODE RAY TUBE** Philips M24/306W, which is not only high resolution but is also X Ray and implosion protected, regular price over £30, you can have them at £12 each and you will receive the deflection coils as well tubes are guaranteed unused.

**80 Watt MAINS TRANSFORMERS** two available in good quality, both with normal primaries and upright mounting, one is 20V 4A the other 40V 2A only £3 each or 10 for £27 carriage paid.

**PROJECT BOX** size approx 8" × 4" × 4½" metal, sprayed grey, louvred ends for ventilation otherwise undrilled made for GPO so best quality, only £3 each or £10 for £27.

**12V SOLENOID** has good ½" pull or could push if modified, size approx 1½" long by 1" square, £1 each or 10 for £9.

**WATER VALVE** 230V operated with hose connections, ideal for auto plant spray or control air gas into tanks etc. £1 each or 10 for £9.

**HANG UP PHONE** won't clutter up your desk or workbench, current model, has push button dialling, last number recall, internal alarm etc., Ex-B.T. in good condition and fully working ready to plug in.

**HIGH VOLTAGE CAPS** if you use these ask for our 1-30 Kv Capacitor list, we have over ½ million in stock and might save you a lot of money.

**ELECTRONIC BUMP & GO SPACESHIP** sound and impact controlled responds to claps and shouts and reverses or diverts should it hit anything! Kit with really detailed instructions, will make ideal present for budding young electrician. Should be able to assemble but you may have to help with the soldering of the components on the PCB. Complete kit £8.95.

**500V BRIDGE MEGGER** developed for G.P.O. technicians the Ohmeter 18B is the modern equivalent of the bridge megger. 9V battery operated it incorporates a 500V generator for insulation testing and a null balance bridge for very accurate resistance measurement. Ex-B.T. in quite good condition with data & tested. Yours for a fraction of original cost £45+£5 insured delivery.

**EXPERIMENTING WITH VALVES** don't spend a fortune on a mains transformer we can supply one with standard mains input and secs. of 250-0-250V at 75 mA and 6.3V at 3 A. price £5.

**15Watt 8ohm 1" SPEAKER & 3" TWEETER** made for a discontinued high quality music centre, give real hi-fi, and for only £4 pair.

**TIMES TEN IONISER** using transformers and novel circuitry, our ioniser emits at least ten times as many ions as does any other kit on offer, nor do we know of a ready built model that is as good, you don't need a tester to see if it is working just bring your hand close to it and feel the stream of neg ions. It's a kit complete with case, nothing else to buy yours for £14.50.

**ULTRASONIC TRANSMITTER/RECEIVER** with Piezo alarm, built into preformed case, is triggered by movement disturbing reflected signal, intended for burglar alarm, car alarm etc. has many extras, time delay, auto reset, secret off device etc. A £40 instrument yours for £10.

**MOVEMENT ALARM** goes off with slightest touch, ideal to protect car, cycle, doorway, window, stairway, etc. etc. Complete with piezo shrieker ready to use. Only £2 (PP3 battery not supplied).

**STEREO HEADPHONE** extra lightweight with plug £2 each or 10 pairs for £18.

**8.5 TELEPHONE LEAD** 3m long and with B.T. flat plug ideal to make extension for phone, Fax, etc. 50p each, £40 per 100, £300 per 1000.

**WATER PUMP** very powerful and with twin outlets, mains operated, £10.00.

**STUDIO 100** by Amstrad, the ultimate disco control panel, has four separately controlled and metered channels, twin cassettes, AM/FM radio, stereo audio amplifier, phone & C.D. inputs, etc. etc. regular price over £400 we have a few still in maker's packing, brand new and guaranteed, yours for £99.

**ROTARY POSITION CONTROLLER** for aerials, ventilators, dampers, rheostats, dampers or applications requiring 180 degrees clockwise and anti-clockwise movement. We have the Sauter MVE4 154 servo motor drive ref AR30W3S regular price over £70 brand new, £15 each.

**12VOLT 8AMP MAINS TRANSFORMER** £4, waterproof metal box for same, £4.

**110WATT SWITCHMODE POWER SUPPLY** 230V mains operated, outputs 38v 2½A and 5v 3A, we have a lot of these and need the space so you can have these at a fraction of their cost if you order before Oct 31 price is £6.

**10VA MAINS TRANSFORMERS** all p.c.b. mounting, all £1 each, 10 for £9, 100 for £75, for output 12-0-12v order ref WA1, 15-0-15v order ref WA2, 20-0/20v order ref WA3, 18-0-18v not p.c.b. mounting but fully shrouded same price order ref WA4.

**0-1mA FULL VISION PANEL METER**

2½" square, scaled 0-100 but scale easily removed for re-writing £1 each, 10 for £10, 100 for £75.

**PANEL AMP-METERS** 80 × 70mm

beautiful instruments £5 each 30 amp order ref WA5, 5 amp order ref WA7.



**VU METER** illuminate this from behind becomes on/off indicator as well, 1½" square 75p each, 10 for £6, 100 for £50.

**EDGE-WISE PANEL METER** ideal when short of panel space only 40 × 14mm, also have built-in led, 500 uA f.s.d, scaled 0-5, £1 each, 10 for £9, 100 for £7.50.

**VIBRATING REED FREQUENCY PANEL METER** 4" square, 55-65 Hz only £9 each.

**P.C.B. DRILLS** 12 assorted sizes between .75 and 1.5mm £1 the lot.

**LOW PRICED FIELD TELEPHONES**. You will know from current advertising that we are selling ex-B.T. field telephones at £12.50 each. We have acquired some earlier ex-GPO models, not quite so nice-looking but quite efficient, and have the big advantage that the ringing is done by means of a hand operated internal generator. This saves a lot of batteries - the only battery required is something like a PP3 for the speech. These phones have the normal type of rotary dial built in and can still be connected into a normal B.T. system. Tested, guaranteed in good order, price only £9.50 each. Order ref 9P5.

**HAND GENERATORS** as fitted in the above field telephones, this hand generator is a permanent magnet type and has an AC output of approximately 50v depending on how quickly you wind it. If you want a higher voltage then simply connect the output to a transformer. We have lots of 6 watt bulb quite successfully. The hand generator, complete with handle, £4.00. Order ref 4P51.

**AMSTRAD 3" FLOPPY DRIVE** cased and with built-in power supply so a self contained extra drive for you if you use 3" discs, real bargain £35.00. Order ref 35P28.

**DRY BATTERIES CAN BE RECHARGED** but not with a normal dc charger, it must be a periodic current reversal type. We can supply the kit, with data, £6.50. Order ref 6P98.

**THE COMPUTER GRADE CAPACITOR** ideal for low volt, high current experiments, 75p each or 10 for £6.00. Two types available, 15000µF 10V or 10000µF 15V.

**HELP YOUR BOYS INTO ELECTRONICS** let them learn by experiments with our simple kits. See our latest newsletter which will be sent to you with any order or ask us for a copy.

Prices include V.A.T. Send cheque/postal order or ring and quote credit card number. Add £3 post and packing. Orders over £25 post free, unless postage quoted separately.

## M&B ELECTRICAL (WW)

12 Boundary Road, Hove, Sussex BN3 4EH

Telephone (0273) 430380 Fax (0273) 410142

CIRCLE NO. 128 ON REPLY CARD

# Impedance transformation with standard 50Ω coaxial feeder

**RF equipment, transmission lines or feeders usually have input/output impedances matched to 50Ω. Occasionally matching problems arise. Dick Manton suggests using a quarter-wave transformer and shows how simple networks of 50Ω lines can be used to perform this task.**

Propagation of waves along a transmission line is very similar to the propagation of water waves in a long, narrow channel. If the channel is uniformly wide and deep, and fitted with a perfect wave absorber at the far end then, assuming there is no attenuation as the waves proceed, the wave pattern will consist solely of forward travelling waves which have a constant amplitude or wave height along the channel.

If, however, the channel changes width abruptly at some point, then waves having a fraction of the amplitude of the forward waves will be reflected back from the discontinuity towards the wave generator. Stationary or standing waves will be produced between the generator and the discon-

tinuity as the forward and backward waves slide in and out of phase. These conditions are shown in Fig. 1.

With radio frequencies the characteristic impedance of the transmission line corresponds to the width of the channel and a matched load or matched antenna corresponds to a perfect wave absorber. A change in line impedance, or the presence of an unmatched load impedance, will result in reflected waves of voltage and hence voltage standing waves. The voltage standing wave is quantified by the voltage standing wave ratio (VSWR), which is the ratio of the maximum amplitude of voltage along the line to the minimum amplitude of voltage a quarter-wavelength away.

By convention, the ratio is always greater than or equal to 1. In Fig. 2 a transmission line of impedance  $Z_0$  changes to impedance  $Z_1$  which is then terminated by a resistive load impedance  $Z_L$ . The resulting VSWR between the generator and the discontinuity is  $Z_L/Z_0$  if  $Z_L > Z_0$ , or  $Z_0/Z_L$  if  $Z_0 > Z_L$ . The relationship between the VSWR and the reflection coefficient  $P_r$ , which is usually expressed as a percentage, is

$$P_r = \frac{(VSWR - 1)}{(VSWR + 1)} \times 100\%$$

or

$$VSWR = \frac{1 + \frac{P_r}{100}}{1 - \frac{P_r}{100}}$$

Provided that the minimum amplitude of voltage on the line is greater than zero, one fraction of the forward power remains, which will travel on past the discontinuity to be absorbed by the load. This is more easily visualised by considering the voltage reflection coefficient  $P_r$ . If the forward power is  $W$ , the power reflected back is equal to  $P_r W$ . The remaining forward power is therefore:

$$\left(1 - \left(\frac{P_r}{100}\right)^2\right)W$$

Disadvantages of having reflected waves in a transmission system include loss of available power in the load or antenna, increased voltages at half-wave intervals along the line and correspondingly increased currents at half-wave intervals between them, and distortion in FM, TV and pulse modulated systems if the transmission line is sufficiently long, typically when it is longer than 50m. The reflection coefficient of a TV broadcasting antenna has to be kept below 2% ( $VSWR < 1.04$ ) to avoid transmitting an appreciable level of ghost image.

## Quarter-wave transformers

If quarter-wavelength of transmission line of characteristic impedance  $Z_2 = \sqrt{Z_0 Z_1}$  is interposed at the junction of two unequal line impedances  $Z_0$  and  $Z_1$ , then the system will become matched at the design frequency. This is because  $Z_0/Z_2 = Z_2/Z_1$  resulting in equal-amplitude reflections from Junction

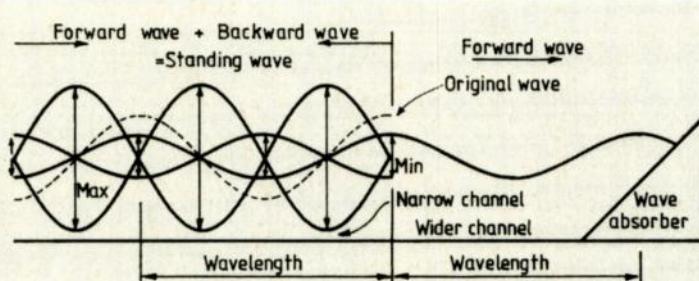


Fig. 1. Standing water waves formed in a channel as a result of an abrupt change in channel width.

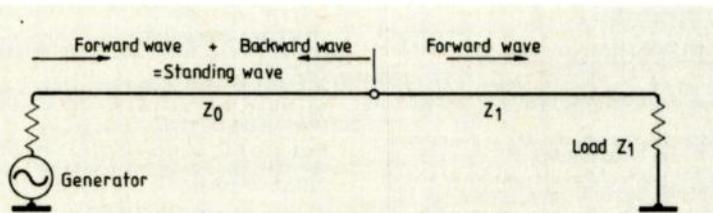


Fig. 2. Standing electric waves formed in a transmission line as a result of an abrupt change of impedance from  $Z_0$  to  $Z_1$ .

points A and B (Fig. 3). Because of the time delay for waves getting from A to B and back and the relative phases of the reflected waves at their points of generation, the reflected waves will completely cancel at A and no reflected waves will proceed back beyond that point. In Fig. 3 and elsewhere  $\lambda$  equals the wavelength in the feeder, is  $300v/f$  metre where  $v$  is the velocity factor of the feeder and  $f$  is frequency in MHz.

#### Equivalent quarter-wave transformers

In general, the characteristic impedance  $Z_2$  will turn out to be a non-standard value. In strip-lines or microstrip-lines a wide range of impedance can easily be fabricated but non-standard-impedance coaxial lines are likely to be inconvenient to construct and are unlikely to be obtainable commercially. Fortunately, however, "equivalent" quarter-wave transformers of any characteristic impedance  $Z_E$  can be formed by three sections of  $50\Omega$  feeder in the form of a T, with two equal arms of (length  $l_1$ ) for the input and output line. The third arm of length  $l_2$  forms a stub line at the junction of the other two. If the required equivalent characteristic impedance  $Z_E$  is less than  $50\Omega$ , then the stub has an open-circuited end; if  $Z_E$  is greater than  $50\Omega$ , the stub has a short circuited end. The lengths  $l_1$  and  $l_2$ , which are indicated and plotted in Fig. 4, are given by

$$l_1 = \frac{\tan^{-1} \frac{Z_E}{50}}{360}$$

and if  $Z_E < 50$

$$l_2 = \frac{\tan^{-1} \left( \frac{50 - Z_E}{Z_E - 50} \right)}{360} \text{ open-circuited end}$$

or if  $Z_E > 50$

$$l_2 = 0.25 + \frac{\tan^{-1} \left( \frac{50 - Z_E}{Z_E - 50} \right)}{360} \text{ short-circuited end}$$

At frequencies close to the design frequency, the equivalent quarter-wave lines have

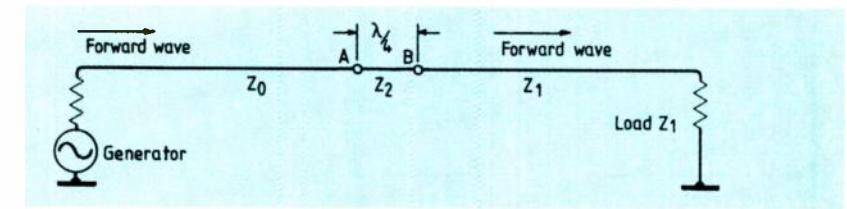


Fig. 3 Standing waves eliminated by the use of a quarter-wave transformer.  $Z_2 = \sqrt{(Z_0 Z_1)}$

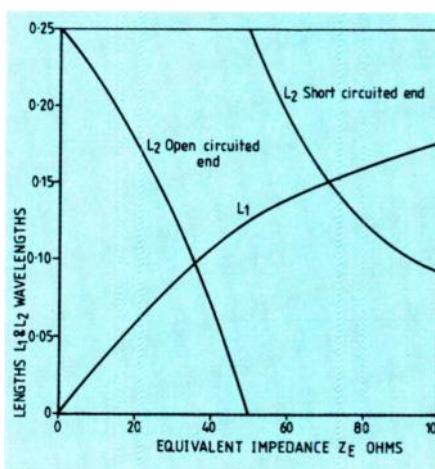


Fig. 4 Dimensions of the 'equivalent' quarter-wave transformer

all the attributes of real quarter-wave lines. That is, they delay phase by  $90^\circ$  and transform impedances in the same way, even to the extent of transforming open-circuits to short-circuits and vice versa.

#### Performance conflicts

As one might expect, the penalty for using a substitute product is a decrease in operational bandwidth when compared with a real quarter-wave transformer. This is best illustrated by comparing the variation of reflection coefficients with frequency for transformers which are designed to transfer from  $25\Omega$  to  $50\Omega$  and to transfer from  $100\Omega$  to  $50\Omega$ . Either of these transformers can be used to feed two  $50\Omega$  loads in parallel, as illustrated in Figs 5(a) and (b).

If an equivalent transformer circuit is

being used to transform a load impedance to or from  $50\Omega$ , regardless of phase delay, the arm of the T that adjoins the  $50\Omega$  can, of course, be omitted.

Resulting variations of reflection co-efficients with frequency are shown and compared with reflection coefficients of real quarter-wave transformers. It is immediately apparent that the equivalent quarter-wave line with an impedance lower than  $50\Omega$  has two advantages: its bandwidth is greater and the number of connections that are required is less.

#### Increased bandwidth transformers

The transformers that are illustrated in Fig. 4 and 5 are specifically designed to be matched at the design frequency. If, however, the transformer arms are slightly modified a matching stub is added, a good compromise in reflection coefficient can be achieved over a much wider frequency band. Figs 6(a) and (b) show  $25\Omega$  to  $50\Omega$  transformers and  $100\Omega$  to  $50\Omega$  transformers that have been optimised for frequency bands of  $\pm 10\%$  (Band II 88-108 MHz) and  $\pm 20\%$  (B and V 614-854 MHz).

Some further improvement might have been possible if multiple stubs had been used but this possibility has not been explored here. If four  $50\text{-ohm}$  loads have to be fed in parallel from a single generator, an improved bandwidth can be obtained by first transforming pairs of  $50\text{-ohm}$  loads in parallel to produce single  $50\text{-ohm}$  impedances and then transforming these to produce a final single  $50\text{-ohm}$  input.

Specific length of feeder has to be used between the two sets of transformers to ensure that the residual reflection in the first


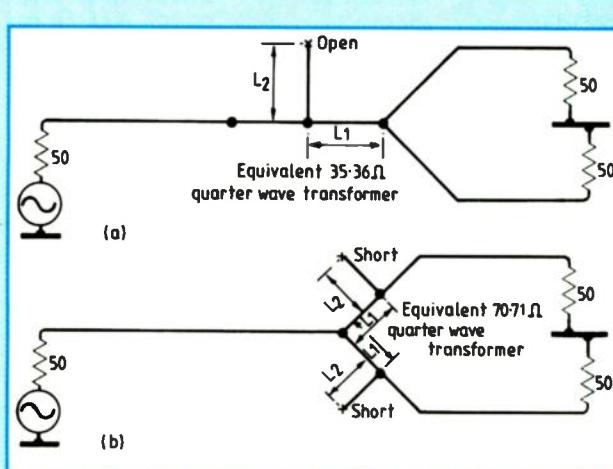


Fig. 5. Alternative transmission line circuits for feeding two  $50\Omega$  loads in parallel using equivalent quarter-wave transformers. Dimensions:  
(a)  $l_1 = 0.098\lambda$ ,  $l_2 = 0.098\lambda$  oc; (b)  $l_1 = 0.152\lambda$ ,  $l_2 = 0.152\lambda$  sc.  
Resulting reflection coefficients are compared with those of "real" quarter-wave transformers.

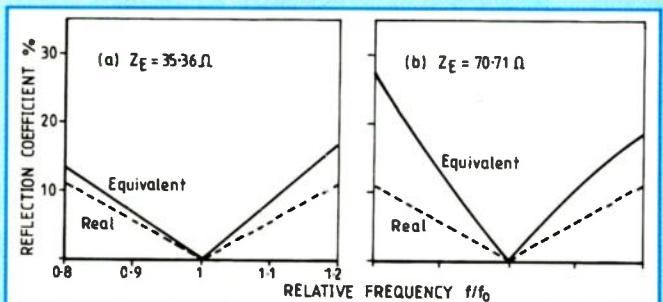



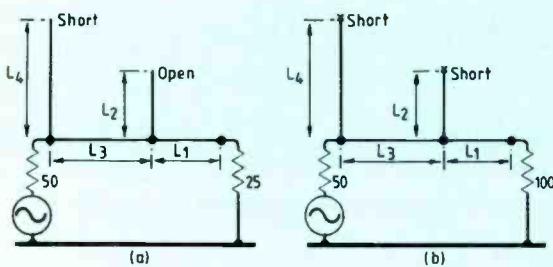
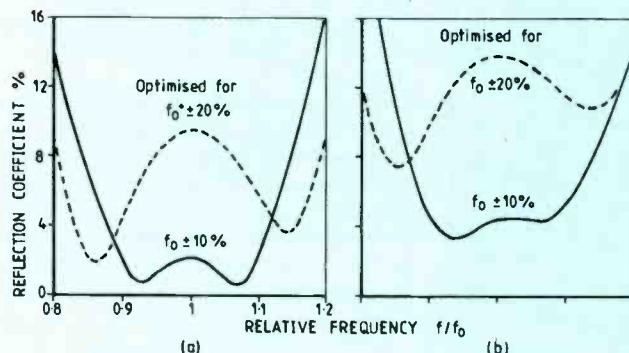


Fig. 6. Wideband circuits for transforming (a) from 25Ω to 50Ω and (b) from 100Ω to 50Ω.

Fig. 7. Wideband circuits for connecting four 50Ω loads in parallel.

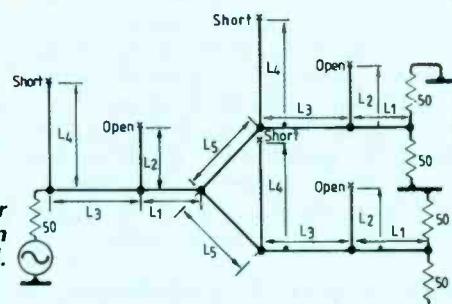

$f_0 \pm 10\%$	$f_0 \pm 20\%$
$L_1 .102\lambda$	$.117\lambda$
$L_2 .094\lambda_{oc}$	$.079\lambda_{oc}$
$L_3 .297\lambda$	$.297\lambda$
$L_4 .252\lambda_{sc}$	$.250\lambda_{sc}$
$L_5 .297\lambda$	$.292\lambda$

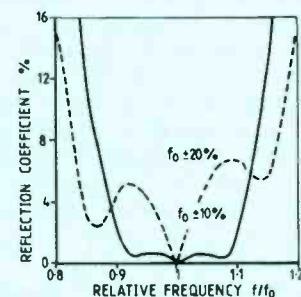

$25\Omega - 50\Omega$	$100\Omega - 50\Omega$
$f_0 \pm 10\% f_0 \pm 20\%$	$f_0 \pm 10\% f_0 \pm 20\%$
$L_1 .102\lambda$	$.117\lambda$
$L_2 .094\lambda_{oc}$	$.079\lambda_{oc}$
$L_3 .297\lambda$	$.297\lambda$
$L_4 .252\lambda_{sc}$	$.250\lambda_{sc}$
$L_5 .297\lambda$	$.250\lambda_{sc}$

pair of transformers are optimally compensated by the residual reflections in the second transformer. Fig. 7 shows the dimensions and performances of four-way splitters using transformers designed for  $\pm 10\%$  and  $\pm 20\%$  bandwidth.

Small modification can be made to improve the bandwidth. All reflection coefficients, that are illustrated above, were calculated by means of a network analysis computer program which was written by the author. ■


## HALF PRICE MEMORIES . . . GUARANTEED ... Recycled, quality i.c's for next day delivery

### WHY PAY MORE?
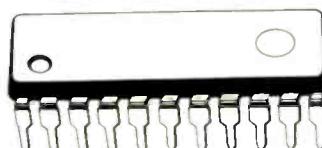
#### ALL DEVICES SUPPLIED ARE

- ★ Ultrasonically cleaned
- ★ UV erased and tested
- ★ Handled in accordance with BS5783
- ★ Packed in antistatic tubes or boxes
- ★ Original OEM brands

We are major suppliers to colleges, Universities, R&D Departments and OEMs who recognise our commitment to quality. Export orders welcome.  
UK Orders please add £2 Carriage and VAT to total.



**Abracadabra** – for an environmentally friendly service!

#### EXTENSIVE STOCKS

*DRAMS	1-25	25+	100+
41256-10	£0.95	0.80	0.70
4164-15	£0.55	0.45	0.35
*SRAMS			
62256LP-10	£1.90	1.70	1.50
6264LP-15	£0.79	0.69	0.59
6116LP-15	£0.55	0.45	0.39
*EPROMS			
27C1000-15	£3.50	3.10	2.90
27C512-15	£2.20	1.99	1.80
27C256-25	£1.20	1.10	1.00
27128-25	£1.00	0.90	0.80
2764-25	£0.90	0.80	0.70
2732-25	£0.80	0.70	0.60
2532-5v	£2.50	2.40	2.30
2716-45	£0.80	0.70	0.60

#### 3 WAYS TO ORDER


- 1 By 'phone 0480 891119  
(8am-7pm Mon-Fri)  
All major Credit Cards accepted
- 2 By Post – send cheque or Banker's Draft to:  
Abracadabra Electronics Ltd, 25 High Street, Ellington,  
HUNTINGDON, Cambs. PE18 0AB
- 3 By Fax: Official orders to 0480 890980  
(24-Hour Service)



Many other items in stock, for FREE List use reader enquiry service or 'phone now.

## USING SIGNAL ACQUISITION CARDS IN YOUR PC?

### ALIASING?

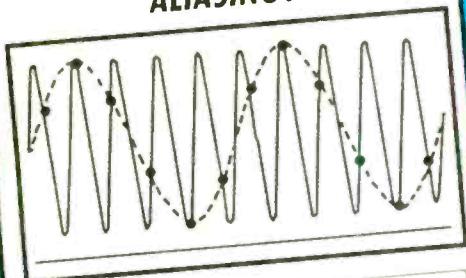


Insufficient sampling of high frequency components leads to low frequency aliasing.

- Aliasing occurs as an inevitable result of digital sampling.
- It can occur regardless of sampling rate or type of ADC.
- Its effect is to completely change certain frequency components in your signal.
- This can distort a signal and, if using frequency analysis techniques (FFT...etc) will lead to gross errors.
- The only means of completely eliminating aliases is to use a properly specified Anti-Alias filter.

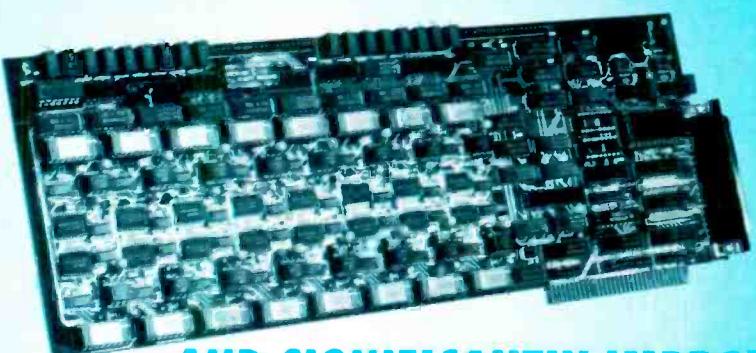**DON'T RISK IT - FILTER IT!**

THIS CARD WILL SOLVE YOUR ALIASING WORRIES...



...AND SIGNIFICANTLY IMPROVE YOUR SYSTEM PERFORMANCE

- Up to 16 channels
- 1 Hz to 25 KHz cutoff at 72 dB/oct
- 1, 10, 100, 1000 gain
- Differential to single ended mode
- Compatible with all standard A/D cards
- Fully software programmable
- Very easy to use



LAPLACE INSTRUMENTS LIMITED PHONE 0692 500777 FAX 0692 406177

CIRCLE NO. 130 ON REPLY CARD

### FIBRE-OPTICS EDUCATOR

Versatile training equipment for education and industry.




### FIBRE-OPTICS POWER METER



dBm and  $\mu$ W scale; battery life 500 hours.

### FIBRE-OPTICS MONITOR


For continuity testing and voice comms.

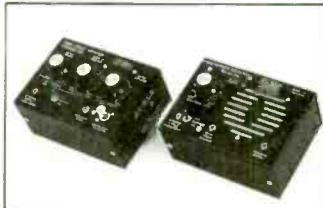

For further details contact:  
ELLMAX ELECTRONICS LTD.,  
Unit 29, Leyton Business Centre,  
Etloe Road, Leyton, London, E10 7BT.  
Telephone: (081) 539 0136  
Fax: (081) 539 7746

CIRCLE NO. 129 ON REPLY CARD

Custom metalwork — good and quick!

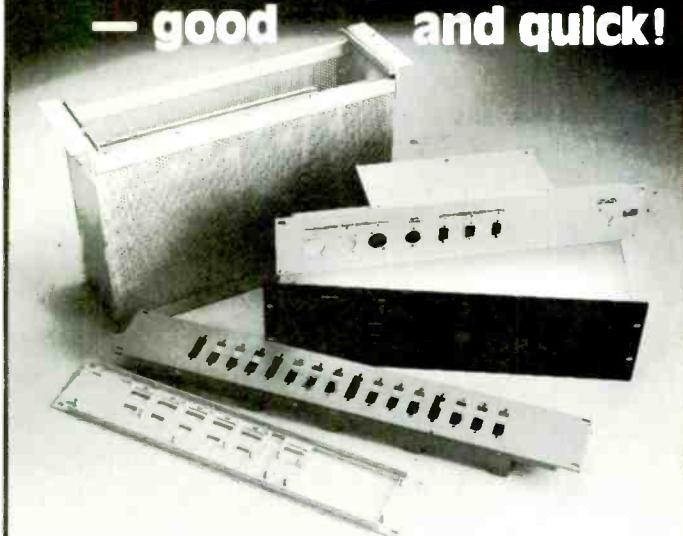

Plus a wide range of stock products including:

- Nine sizes of standard 19" rack cases
- New "clam" case in any depth
- Eight-card 1U Eurocard case
- Audio, video and data patch panels
- Rack blanking and ventilation panels

All use the unique IPK extrusion, giving strength and rigidity with no visible fixing screws. Rack mounting strips, cable trays etc. from stock.



IPK Broadcast Systems  
3 Darwin Close Reading Berks RG2 0TB  
Tel: (0734) 311030 Fax: (0734) 313836

CIRCLE NO. 131 ON REPLY CARD

# Designing audio components

## Sound models for MicroCap

**Ben Duncan illustrates the modelling of some real passive components for greater realism in simulation of audio components.**


Passive components (resistors, capacitors, inductors and their derivatives) used in both pen and paper design and computer simulation, as well as in circuit schematics, are pure or "primitive" parts. But the map is not the territory and nothing quite like them ever pertains in nature or exists as a manufactured part. Instead, real components contain, in addition to their explicit behaviour as R or L or C, the other two terms.

For example, all capacitors exhibit inductance and resistance, albeit small in good specimens. Additional, second order phenomena include dielectric absorption, transmission line effects, mechanical losses, and non-linearities in magnetic cores – where applicable. Parasitic elements are well heeded by RF designers (they have to be), but are commonly ignored or only hazily appreciated by practitioners in other areas. In analogue audio and instrumentation, passive component parasitics become important when developing and analysing circuits to high precision (eg to  $<0.5\text{dB}$ ,  $<1^\circ$ ). Even with purely nominal circuitry, component imperfections become increasingly significant when operating above 100kHz and in some cases below 10Hz, or wherever extreme part values, power, voltage, current ratings and network impedances are involved. Awareness of passive component parasitics is no less important in digital design, for the optimising of power supply decoupling and suppression networks. References<sup>1,2,3,4</sup> provide introductory reading on the attributes of real components.

This article introduces some passive component models and describes how they have been created and evaluated, using Spectrum Software's MicroCap-III premium simulator software<sup>5</sup>. Known as MC3 for short, it's friendlier and more versatile than most if not all of the Spice-based programs, but nonetheless, it has much in common, and Spice users will have no difficulty translating the model information into their local dialect.

**Resistors and pots**  
Real resistors feature a shunt capacitance of about 0.3pF, for modern, 1/4 watt metal film types. The value depends on physical size, core geometry – hence type and wattage –

Fig. 1. Using MC3 as a first order resistor model

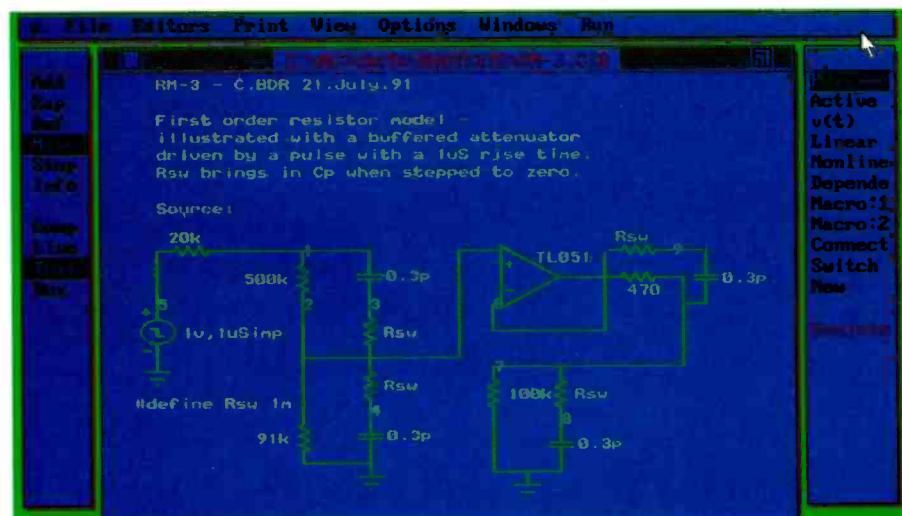

and is fairly independent of ohmic value. So whether operating frequencies and/or network impedances are high enough for it to matter in particular instances will generally be intuitively obvious to the designer. If uncertain, Fig. 1 shows how you can use MC3 as an A/B demonstrator. The parasitic capacitors ( $C_p$ ) are connected via resistors ( $R_{sw}$ ) which can be used to switch them in and out by stepping from zero to a very high resistance. The resulting time domain or transient graph Fig. 2 shows the  $\pm 1V$  stimulus (input) at the top, and the two output plots, with and without  $C_p$ . Note the peaking and timing advance when  $C_p$  is included.

Potentiometers are modelled in MC3 by causing two resistors to step in opposite directions, maintaining a constant value. The value of each resistor is equal to the pot's nominal value. In Fig. 3, which models a log pot used as an audio volume control, it is done with the aid of the sub-circuit artifice at the bottom right. The voltage of battery called "set" is stepped during analysis, and drives the adjacent polysource "Logstep". The polysource acts as the multiplier in the #DEFINE statements which comprise equations governing upper and lower arm resistances (UAR and LAR). A log term linearises step increments on the dB scale.

The stepping equations include the parasitic capacitance ( $C_p$ ) across the element, which can be quite substantial in some dual carbon models with close tracking, eg. ALPS. Their values, in the order of 5pF, are arrived at by multiplying the pot's value ( $10^4$ ) by a huge 0.005p ( $5^{-15}$ )! Real pots also have endstop resistance ( $R_e$ ), a wiper resistance ( $R_w$ ), and capacitance between their pins (5pF). These values have been written as #DEFINE statements to keep the page tidy.

Real loads have finite resistances and with shielded cable, capacitance may be tens or hundreds of pF too. The load model contains typical values. The source generator (it's not visible but appears across the  $10^8$  input tie-down resistor during an AC run) has the default  $R_s$  of  $1m\Omega$ . This is an allowable simplification as the direct source impedance of any halfway decent driving op-amp will be within the tolerance of the upper  $R_e$ .

Figure 4 shows the pot's frequency response versus attenuation setting, demonstrating the way in which the capacitive portion of the divider turns the HF response from a roll-off to a roll-up as attenuation increases, with a nearly flat response occurring at around -20dB. By altering the stepping range, the maximum attenuation will be found to be around -66dB, and by appending tolerances to all the resistive values, and performing a worst case Monte-Carlo run, you can predict the maximum and minimum of full audio band attenuation in production.

### Capacitors

The first order model of a real, capacitor comprises equivalent series resistance (ESR), equivalent series inductance (ESL) and leakage resistance (RL). Despite their

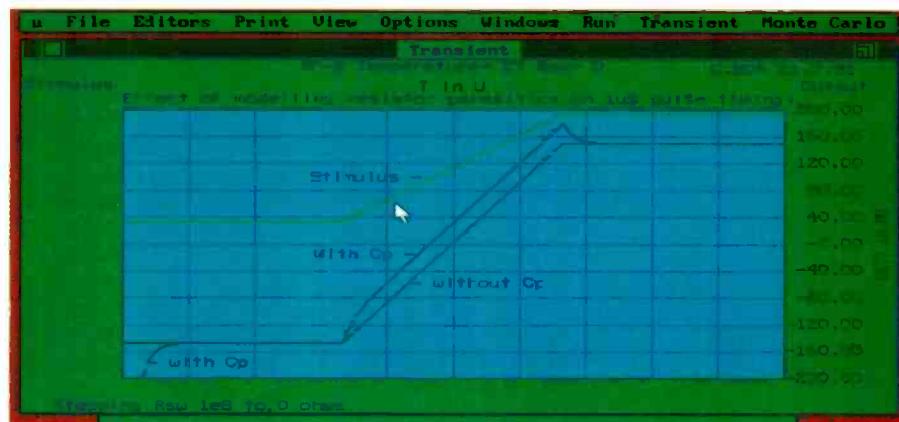


Fig. 2. Transient graph for Fig. 1. model

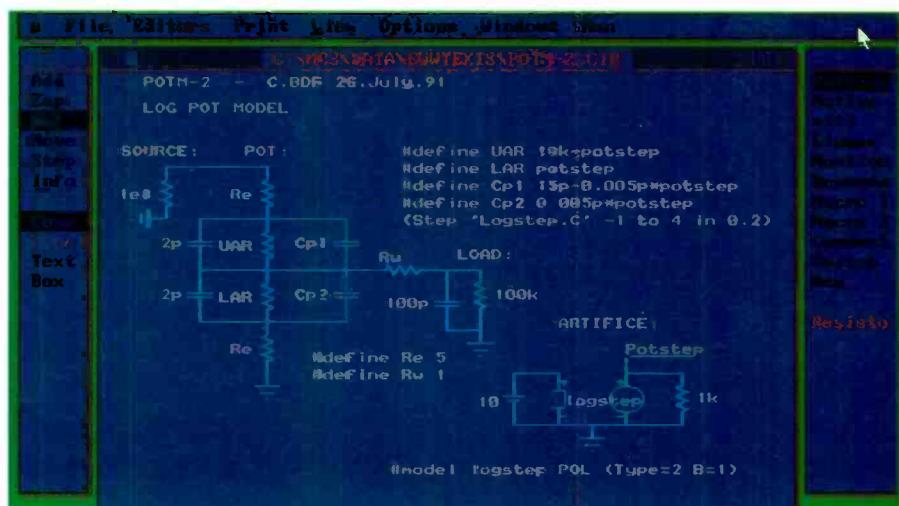


Fig. 3. Model of a log pot used as an audio volume control

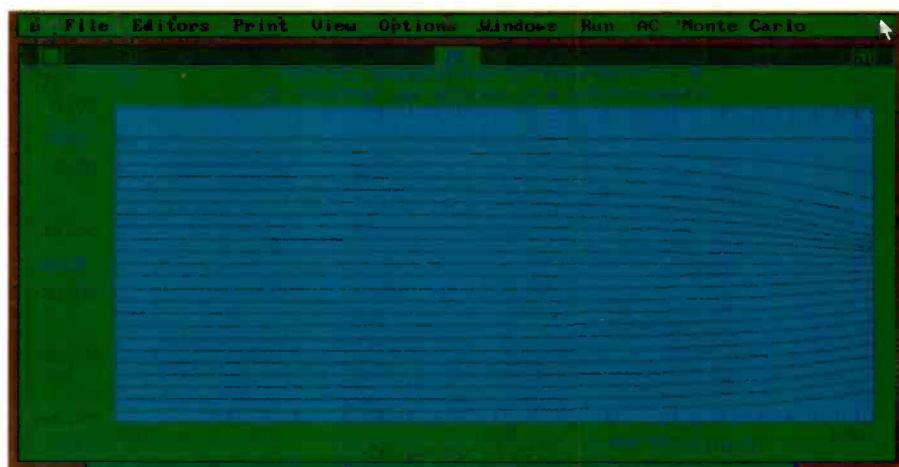
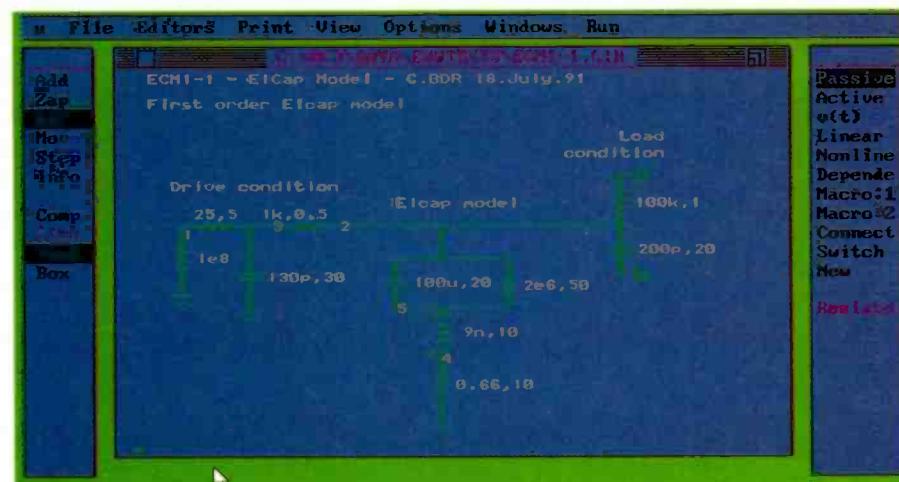
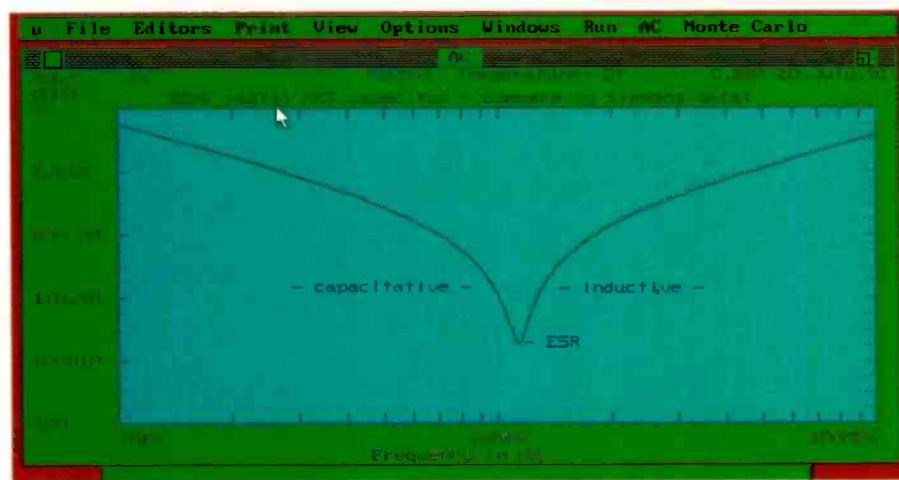
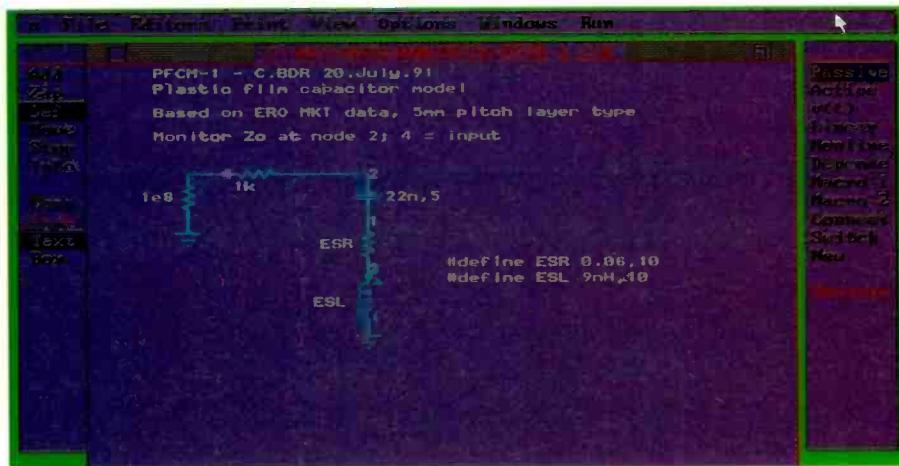


Fig. 4. Capacitive portion of divider changes the HF response as attenuation increases.

title, the "equivalent" parts are real, physical quantities. MC3 readily plots input and output impedance (or conductance if you prefer) in AC analysis mode. A suitably large series resistance is needed to separate input from output, else the  $1m\Omega$  AC analysis source would dominate.

The parasitic values for the 22nF capacitor in Fig. 5 have been arrived at by inspecting spot values on the maker's impedance against frequency graph, then entering rea-

sonable initial values. The ESR is the resistance at the impedance minima. ESL will be in the order of a few nH for most physically small components. The values can then be adjusted by stepping them until the capacitor's impedance versus frequency plot (Fig. 6) closely corroborates with the maker's data. An uncertainty, hence tolerance of 10% has been included in the ESR and ESL "#define" statements. The leakage term has been excluded, as with the plastic film

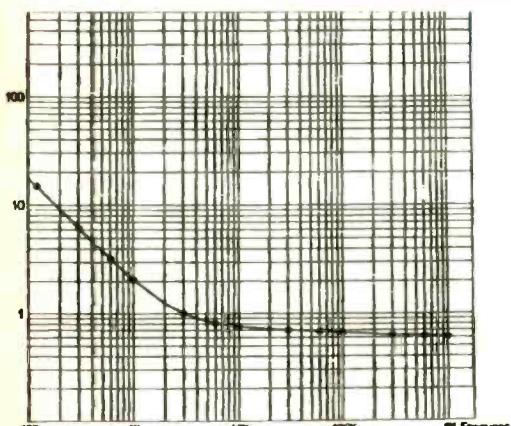


**Fig. 5. (top)** Parasitic values are arrived at by taking "reasonable" initial values then stepping until the impedance vs frequency plot, **Fig. 6 (middle)** matches the maker's data.

**Fig. 7. (above)** Model of a modern 100 $\mu$ F electrolytic and maker's data, **Fig. 8 (left)**.

capacitor modelled here, it is at least 100MΩ, so only significant in very high impedance networks and at VLF.

Figure 7 presents a model for a modern 100 $\mu$ F electrolytic, made by Elna. The model closely follows the maker's impedance data (Fig. 8) as shown in Fig. 9.



## MODEL IN CONFIDENCE

Analysis with MicroCap-III or MC3 for short involves entering the circuit as a schematic in a windows type of environment. Simple circuits are speedily tested and then developed into bigger ones by copying blocks and merging. Nodes are numbered automatically.

In the latest V3.08 used here, numbering is fairly cumulative so the addition of new parts rarely alters existing node numbers. The latest version is also thoroughly gamekeepered by factual error messages which leap out to prevent you entering a hang or making a fool of yourself. Component values can be stepped and may be optionally defined by statements (which may include formulae) on the screen. Notation is a mixture of engineering shorthand and floating point numbers, as convenient. MC3 already allows you to model two kinds of real-world passive component errors neglected in the main text, namely value tolerances, and temperature coefficients.

Confidence in the results have been gained by rigorous comparisons between simulations and measurements of the resulting physical circuits using Audio Precision System One and Technicon TDS "TEF" test sets. In the majority of cases of disparity, an error in the physical circuit was revealed – rather than a modelling oversight. Thus simulation, so easily casually vilified as "inaccurate", actually has a role to play in verifying that the expensive PTH PCB you're about to make is the circuit you think it is.

but not an Audio Precision (AP) test-set's plot of magnitude, Fig. 10. The 1kΩ series input resistor is the same value as that used in the physical measurements and the latter test set's source and load conditions have been included in the modelling circuit. Looking at the AP plot, note the change of slope towards -3dB/octave above 1kHz. This phenomenon is common in wound capacitors (not just electrolytics) and arises because of the transmission line quality of the plates, owing to their sheer length.<sup>6</sup>

The second-order circuit in Fig. 11 replaces and upgrades the basic model, and retains a similar total capacitance, but spreads it along a line of distributed ESRs (DESR) having much higher values (330mΩ), with the leadouts' resistance (10mΩ) and lumped inductance (4.5nH) expressed separately. Leakage resistance (10<sup>8</sup>) with a fair uncertainty (60 means 60% to 160%) has been included for completeness. The network is then connected across the existing source and load conditions in the previous circuit (using the tie marked ec+), and yields the curve in Fig. 12. The change of slope above 1kHz now closely follows the AP plot in Fig. 10, although the different aspect ratios make this hard to see at first.

In case there are any doubts, Fig. 13 shows 15 worst case Monte Carlo tolerance

runs, homing in on the bottom portion of the original graph. The variation is the sum of the two tolerances expressed, ie. DESR varies  $\pm 5\%$  and C varies  $\pm 20\%$ . ESL variation has been expressly excluded by not appending a tolerance to its value. Note how the difference is a linear offset below 1kHz, with a change of slope at higher frequencies – where the plots cross each other. Thus it can be seen that any lack of corroboration in the slope and the corner are within the tolerance band of the distributed elements alone. If desired, the model can be refined by further sub-division and dispersion of the R, C and even L components.

### Dielectric absorption

Dielectric absorption (DA) or soakage is the ability of high permittivity dielectrics – notably electrolytic, medium and hi-k ceramic, and the polar plastic films – to release charge more slowly than predicted by first order equations.


The ideal equivalent circuit for DA is a series of nested RC networks, across the main capacitance. For a first order approach to this third order problem, the series can be simplified to a single, nested RC network. It may not be good enough to give definite answers to audio mysteries, but it may come in handy with problems in sample and hold, and integrator circuits. The values needed to replicate DA in a  $4.7\mu F$  polyester capacitor were established by building the standard US Mil Spec DA test-set in MC3.

It comprises an electrometer looking across the capacitor under test, which is charged for five minutes, then shorted. MC3's time switches vastly simplify the accurate and automatic timing of the charge/dump/read cycle. A virtual electrometer built in MC3 (or other simulators) has perfect leakage and noise specifications and, unlike real instruments, it doesn't need cleaning and a bake in the oven after a period of disuse!

The DA term values were stepped in transient analysis until the recovery voltage 5s after discharge followed the results for the  $4.7\mu F$  MKT capacitor in Jung & Marsh's classic report<sup>7</sup>.


Looking at Fig. 14, the op-amp gain stage has three high pass poles built around it, all using the  $4.7\mu F$  polyester capacitor.  $10^8\Omega$  models leakage resistance, and  $0.1\Omega$  the ESR. ESL isn't modelled as we're only looking at low to sub-audio frequencies. The DA term is the  $158nF$ , in conjunction with  $R_{sw}$ , when the latter is  $10M\Omega$ . When stepped to a much higher value ( $10^{11}\Omega$ ) DA can be safely assumed to be out of the picture. The op-amp is a Jung-Boyle macro of LT1037, based on recent work by Walt Jung while working as staff scientist at Linear Technology.

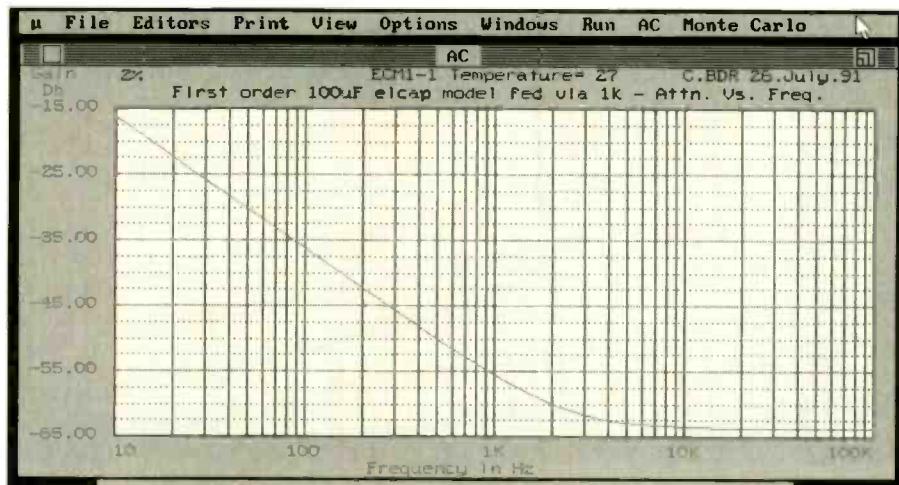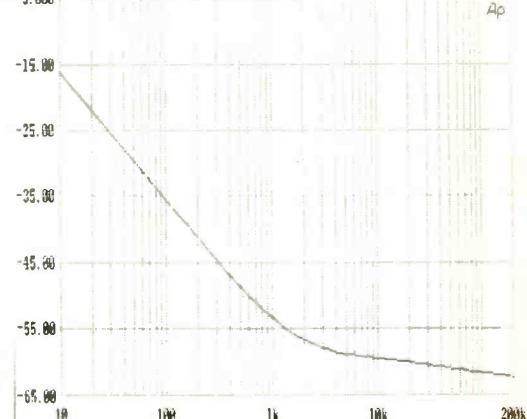It has the advantage of more closely modelling the op-amp's second order performance aspects, such as CMR and  $I_{out}$ . As a Jung macro, it's easier to enter than Spice based macros released by other op-amp


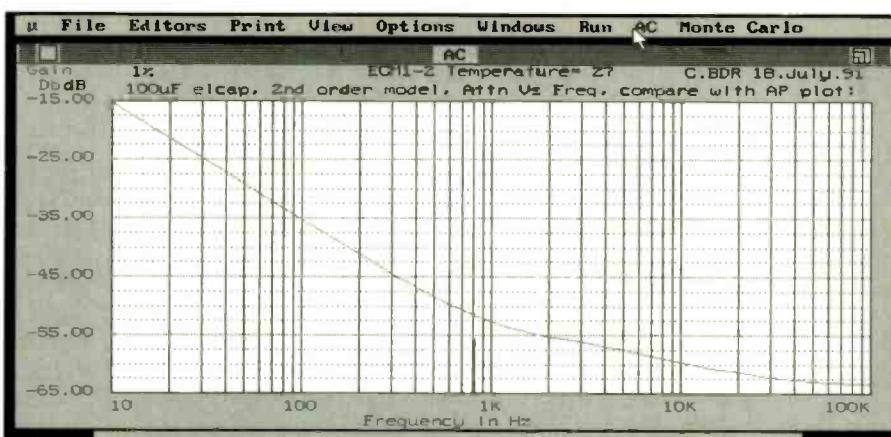


**Fig. 9.** The model closely follows maker's data (Fig. 8) but not an Audio Precision test-set plot, Fig. 10. (right).

AUDIO PRECISION BE AMPL(dBu) vs FREQ(Hz)  
28 FEB 91 13:04:01  
Ap

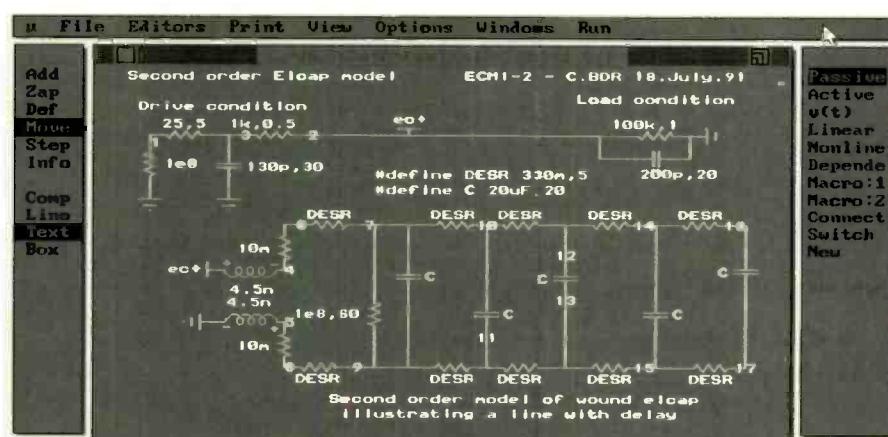

**Fig. 11.** (below) An upgrade of the basic model with total capacitance retained. Connecting the network across the existing source yields Fig. 12 (bottom).



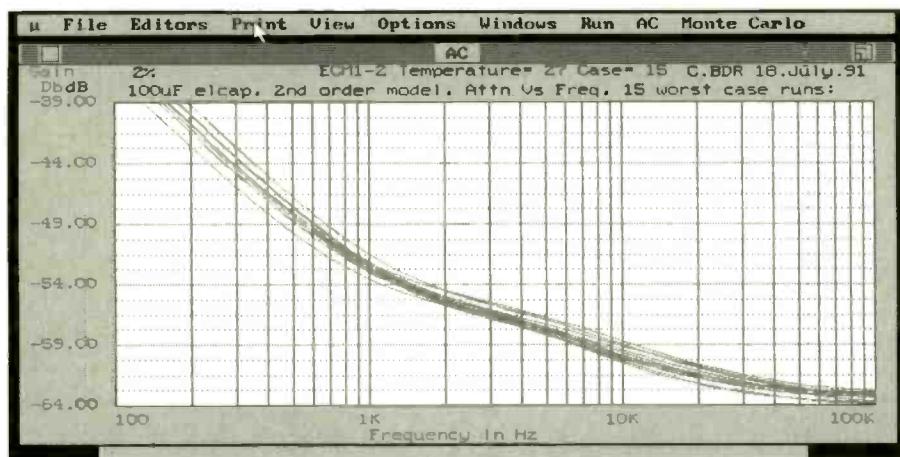


Fig. 13. Checking "worst case" matches.

Fig. 14. Evaluating a model of DA in polyester film capacitors.

Fig. 15. AC response with and without DA term.

Fig. 16. First order model for an inductor

manufacturers, by avoiding the more esoteric types of sources. A recent issue of Spectrum Software's MC3 newsletter has covered the conversion and entry of Spice macros into MC3.




Some years ago, the correspondence columns of *EW + WW* and *Hi-Fi News* echoed with exchanges about whether or not capacitor DA (amongst other things) could give rise to audible differences and/or loss of sonic quality. The debate locked-up with both sides disputing the relevance of each other's evidence and viewpoint but, as it came to a close, the mathematician Stanley Lipshitz issued a challenge: If there were any effects, they should be demonstrable in the AC domain.

**Figure 15** replies by plotting the AC response of the circuit with and without the DA term. The plot shows an abrupt change in group delay and a smaller change in phase response, albeit at subsonic frequencies. There must also be some accompanying change in amplitude response. So yes, DA has effects in the frequency domain, albeit very small (<0.1dB), and in realms where signal magnitude is extremely small, as well as occurring over seconds. Still, the way is now open to model DA with more nested terms integrated with Hawksford's transmission line model. Across a complete studio chain, and considering the much higher DA at large in electrolytic coupling capacitors, and how broadband amplitude variations of well below 0.1dB are now rated as psychoacoustically significant to experienced listeners, who knows what may transpire?

#### Inductors and transformers

**Figure 16** illustrates the first order model for an inductor. Note that as the resonant impedance for an inductor is a maximum, the driving resistance (test fixture) has been made very high, so it doesn't appreciably shunt the impedance around resonance. A value as high as 100MΩ wouldn't be very feasible in a physical setup, due to the effects of parasitic impedances and stray field pick-up, but simulation just doesn't have this problem. The inductor's nominal self-resonant frequency,  $F_{res}$  is 2.8MHz; the impedance versus frequency plot in Fig. 17,  $C_p$  has been stepped (from 1pF to 4pF in 1pF steps) to find the value which fits the spec. MC3's ruler scale has been selected so the grid lines don't obscure the near vertical resonant portions.

For problems where a ferrite or iron cored inductor is operating at very low current lev-

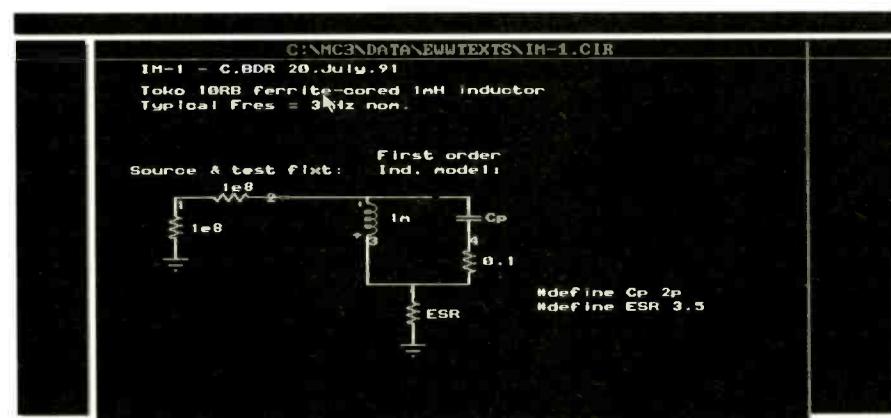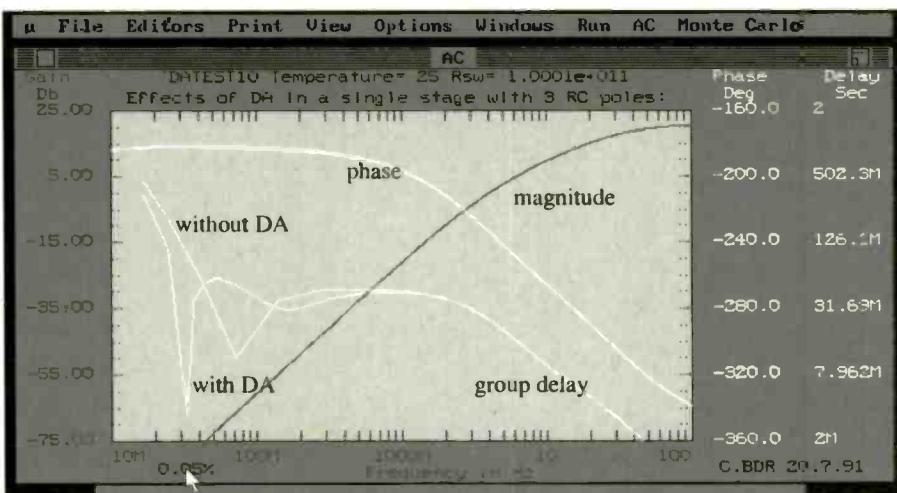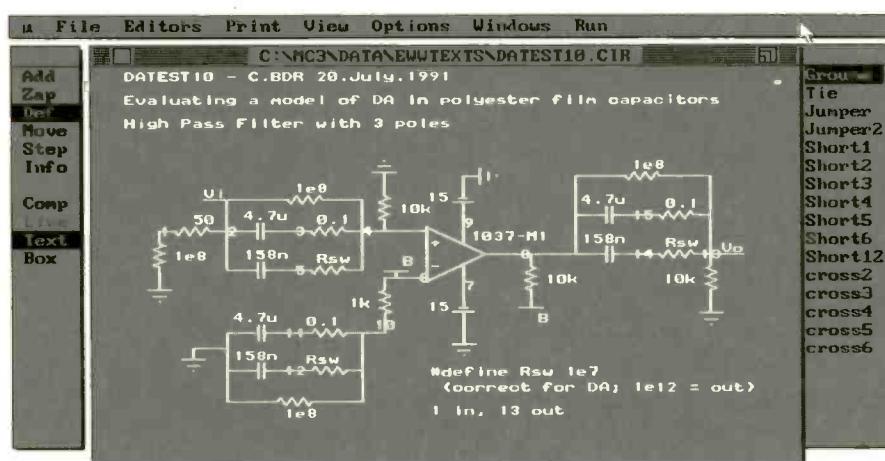

**Fig. 17.** Stepping  $C_p$  to find the value which fits the spec.

**Fig. 18** modelling an audio splitter transformer and frequency.

**Fig. 19.** Transformer and frequency responses under load.

els or close to saturation, one can use MC3's Jiles-Atherton magnetics model to simulate core saturation and hysteresis. Inductors can also be given values which are a function of the current they're passing.

Finally, the circuit in **Fig. 18** uses MC3's mutual inductance capability to model an audio splitter transformer. The model has enabled a leading UK pro-audio manufacturer to evaluate the interactions between different microphones, multicore cables and buffering techniques without the great cost and fraught logistics of borrowing, hiring and physically assembling the £20,000+ worth of equipment in one place for a measurement session.

On the left,  $150\Omega$  is the source resistance used in the maker's data.  $R_{wp}$  is the primary DC resistance. The #MUTUAL statements define coupling between the primary (p) and secondary (s) windings, whose inductance ( $L$ ) is given in the adjacent #DEFINE statements.


The transformer's frequency response is governed by the winding inductance and coupling factors.  $R_{ws}$  is the secondary DC resistance, while  $LLs$  and  $Cs$  are reasonable values for leadout and lead inductance and capacitance to the test set used by the maker. The nominal load's parasitic capacitance is cited separately.

Finally, an op-amp normalises the amplitude to 0dB at 1kHz, for ease of reading. The second secondary ( $L_{s2}$ ) is loaded when  $R_{sw}$  is stepped to zero ohms. When this happens, the op-amp's gain is also increased to place the second plot exactly one division under the first to make comparison easy. **Figure 19** then shows the frequency and phase responses under the two load conditions. This closely follows the maker's data except for a linear slope below 120Hz. Refinements to incorporate this will involve distributed L-R sections, the invert of the wound capacitor.


In closing, I'd like to acknowledge Walt Jung in the USA, for making helpful suggestions about DA modelling, Rita Drew at Calona for securing elusive Elna data, and BSS Audio, for their support of the transformer modelling project.

#### References

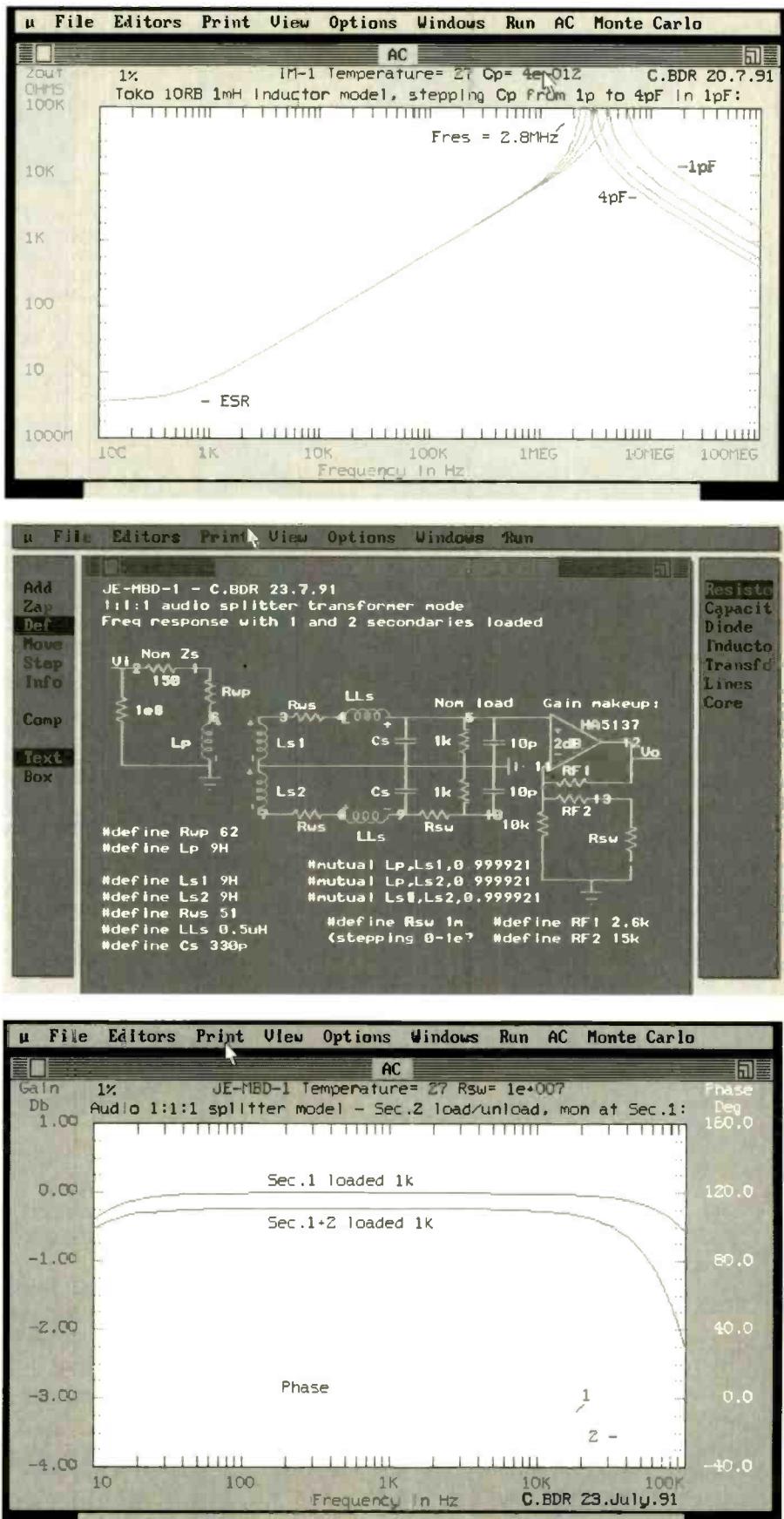1. Daniel Metzger, *Electronic Components, Instruments & Troubleshooting*, Chapters 2,3,4,5, Prentice-Hall, 1981.
2. G W Dummer, *Capacitors*, Pitman, 1960.
3. Ben Duncan, *With a strange device - an investigation into capacitor quality*, parts 1-7, *Hi-Fi News*, April to Nov '86.
4. Ben Duncan, *Piece de Resistance*, *Hi-Fi News*, Mar & April '87.
5. Ben Duncan, *MicroCAP III under test*, *EW+WW*, July '90.
6. Malcolm Hawksford, *The Essex Echo: Unification*, Track four, *Hi-Fi News*, P.43, Feb '87.
7. Walt Jung & Richard Marsh, *Picking Capacitors*, *Audio (USA)*, Feb and March 1980.



**THURLBY  
THANDAR**

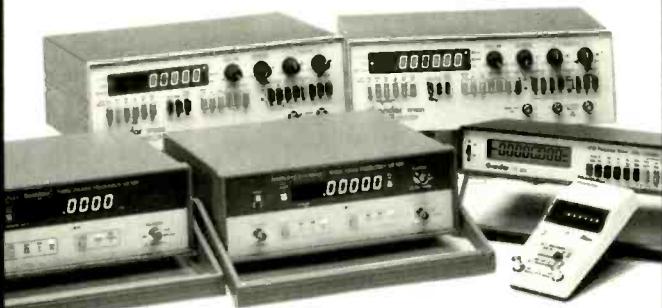

## For Frequency Counters

Whatever your need in frequency counters, Thurlby-Thandar can supply it.

The range includes basic frequency counters, models with period and totalise functions and dual channel universal counter-timers with TCXO options. Prices start from only £89 + VAT.

Bench and portable applications are catered for with models offering up to 200 hours operation from batteries. Frequencies from DC up to 1.3GHz can be measured to high accuracy.



TF820

This low-cost 1.3GHz frequency meter features high sensitivity over its full frequency range.

The 8 digit display provides a maximum resolution of 0.1Hz. A choice of battery or mains operation is available. It costs £169 + VAT.

Contact us now for full details of all our counters.

Thurlby-Thandar Ltd.

Glebe Rd., Huntingdon, Cambs. PE18 7DX  
Tel: (0480) 412451 Fax: (0480) 450409

CIRCLE NO. 106 ON REPLY CARD

## BROADCAST MONITOR RECEIVER 2 150kHz-30MHz



We have taken the synthesised all mode FRG880 communications receiver and made over 30 modifications to provide a receiver for rebroadcast purposes or checking transmitter performance as well as being suited to communications use and news gathering from international short wave stations.

The modifications include four additional circuit boards providing:  
\*Rechargeable memory and clock back-up \*Balanced Audio line output  
\*Reduced AM distortion \*Buffered IF output for monitoring transmitted modulation envelope on an oscilloscope \*Mains safety improvements.

The receiver is available in free standing or rack mounting form and all the original microprocessor features are retained. The new AM system achieves exceptionally low distortion: THD, 200Hz-6kHz at 90% modulation -44dB, 0.6% (originally -20dB, 10%).


- \* Advanced Active Aerial 4kHz-30MHz \*PPM10 In-vision PPM and chart recorder \*Twin Twin PPM Rack and Box Units
- \*Stabilisers and Fixed Shift Circuit Boards for howl reduction
- \*10 Outlet Distribution Amplifier 4 \*Stereo Variable Emphasis Limiter 3 \*Stereo Disc Amplifier \*Peak Deviation Meter \*PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and movements \*Broadcast Stereo Coders \*Philips DC777 Short Wave Car Combination: discount £205 + VAT.

### SURREY ELECTRONICS LTD

The Forge, Lucks Green, Cranleigh,  
Surrey GU6 7BG. Tel: 0483 275997. Fax: 276477

CIRCLE NO. 104 ON REPLY CARD

## Not a data logger ...

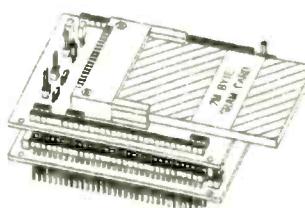

... but a module to build into your own products. It enables you to quickly build tailor-made data collection systems with removable memory which can be read by a Personal Computer.

As a **Data Logger Module** you've little to add to its low current, up to 8Mbytes of non-volatile card memory, 10-bit 8-channel A to D and real-time clock. Directly connect a matrix keypad and graphics or character LCDs.

As a **High Performance 16-bit Control Computer** its on-board Assembler & multitasking Forth high level language make programming and debugging a pleasure, yet give the 3 MIPS execution speed you need in a real-time system.

### Triangle Digital Services Ltd

223 Lea Bridge Road, LONDON E10 7NE

Tel 081-539 0285

Fax 081-558 8110



CIRCLE NO. 105 ON REPLY CARD

**Easytrax devotes most of the screen to layout.**

**A**t £95 Easytrax is part of a family of cad software which includes an elaborate autorouter costing ten times more. But though it is the baby, it certainly appears to have gained from being part of the family.

In keeping with its low cost approach, the package will run on quite modest hardware and a 640K machine with twin floppy drives will suffice though a hard disk will speed things up. Even a mouse is not essential (but money has to be very short to take that route). Most current PCB layout packages require EGA graphics or above so no doubt some will be pleased to know that it will run with CGA and Hercules cards, but at the other end of the scale it supports some 1024 x 768 modes.

Six signal layers can be routed together with a power and ground plane and a single silk screen overlay. A further layer is provided for board outline, alignment marks and text such as drawing numbers. I have yet to see a printed circuit board 32in square, but if needed, Easytrax could lay it out. Calculations are performed to one thou resolution (0.001in) so in practice, layout accuracy will be limited by what happens after Easytrax, not the programme itself.

No problems are experienced in getting the package up and running and it soon becomes enticing to experiment without reading the manual.

A fully completed layout file is provided as an example and this together with the very easy-to-use menus mean that within minutes you can be drawing and moving tracks and components.


The manual takes the form of a small paperback, well produced with plenty of diagrams and handy hints, and the fact that most important items are covered in a paragraph or two is a tribute to the package's ease of operation. My only criticism is that it will not stay open on the desk at the right page, but some people are never satisfied.

#### Screen design

Almost all the screen is devoted to the artwork, two lines at the bottom being reserved for useful things such as XY coordinates, the current layer, track size and pad type. A single drop down menu with 16 items appears at the press of a key or mouse button and selecting one of these items usually leads to further sub-menus.

Sensible names have been given to menu items and operation quickly becomes second nature. As an alternative to mouse control, pressing the first letter of the menu items can help navigate with considerable speed through the command sequences. The user/machine interface would do credit to many more expensive packages.

All the usual screen manipulation com-

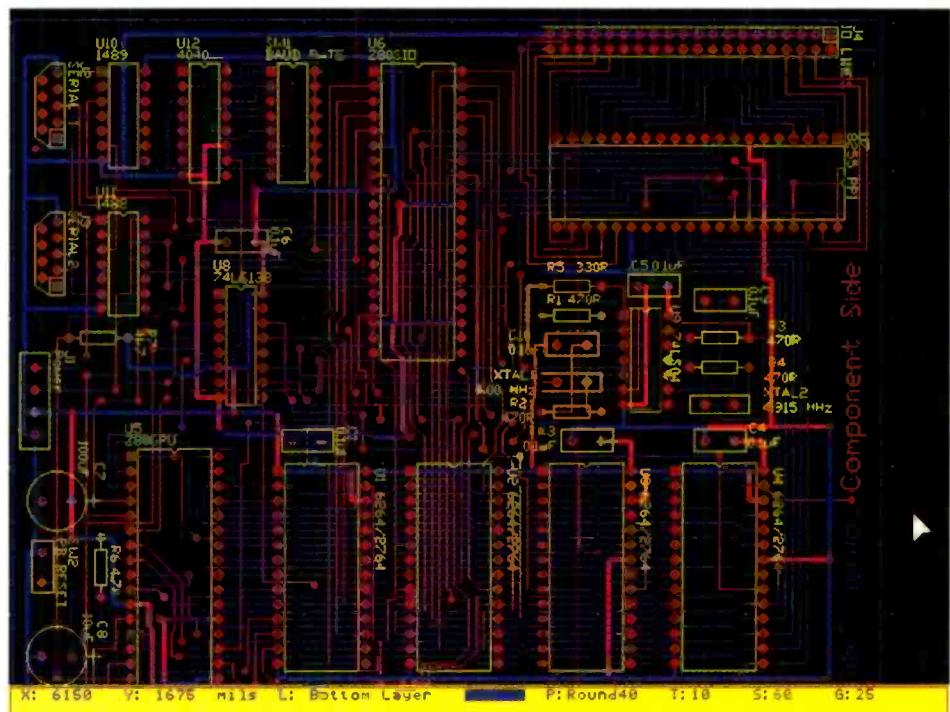

# Layout PCBs without ladling out cash

*Should you jump at Easytrax 2's low cost entry to computer PCB layout? Martin Cummings looks for the compromises.*

mands are here. Panning around the drawing can be automatic or at the press of a button and zooming can be with any of seven magnification factors or, as is more usual, by defining a window of interest. Screen colours for each item can be reconfigured.

There are two grids, one visible the other hidden, and both are fully adjustable in pitch and if required the cursor will snap onto the hidden grid. Easytrax performs all its operations in thou, but it can be set to metric units, so that everything is converted to millimetres. The calculations to perform the conversions noticeably slow down screen refresh so there is a distinct advantage in staying imperial and for the moment component manufacturers seem to concur.

#### Full library

A full library of pre-defined components is

included with the software, containing just over 100 items – not a great deal but probably providing 99% of components because it covers all the common component and IC layout arrangements including pin grid arrays.

The library does not however include surface mount components and Easytrax does not support them.

I toyed with the idea of creating some surface mount parts by using short stub tracks instead of pads for pins and this would probably work with the exception of the solder resist layer which would cover the pads. So if you are prepared to live without the solder resist and have a silk screen on just one side you can probably deal with surface mount though this could not be recommended for professional use.

It is also possible to browse sequentially

through at the click of a mouse – a convenient way to explore the library – but in practice the method is far too slow for selecting the components; names are reasonably meaningful and are a much quicker way of choosing.

Rectangular sections of the layout including tracks and devices can be saved as blocks and imported into fresh layouts at some future date. In this simple but rather elegant way fresh devices can be added to libraries.


At the start of a layout, positioning components follows the usual sequence of choose, rotate, then place in position. As each component is placed it can be automatically numbered in sequence or the program can be overwritten with an own identifier. Alongside the component identity, another piece of text can be placed to define, for example, the resistor value.

Placing tracks is just a matter of deciding position and dragging the cursor around. Tracks can be forced into 90 or 45° angles or, by switching this feature off, giving free range to adopt any angle. Track widths range in discrete steps from 10 thou up to 100 thou and spacing is defined by the grid which can go down to 1 thou if needed. At any time whilst drawing tracks, a single key press will change layers and a via hole is automatically created at that spot.

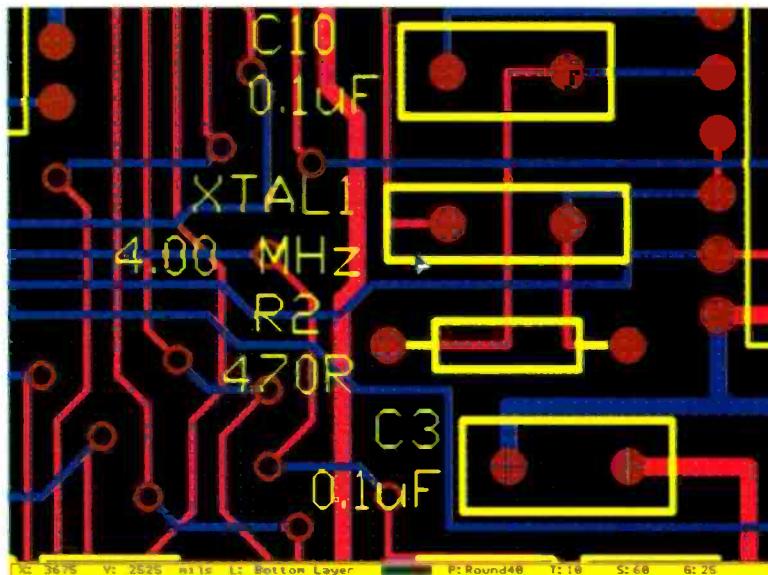
### Automation

"Repeat" is particularly useful feature allowing duplication of an operation an infinite number of times (or 5000 times anyway), but each time with a user-defined XY offset. Hence laying a bus, memory grids, edge connectors and anything repetitive can be automated in this curious way.

Easytrax includes a "pad to pad autorouter" and once the pads to be linked have been clicked on this will automatically place the tracks to make a connection. The operation is quite interesting to watch as the programme temporarily draws lines on the screen as it tries various routes. Its approach should not be compared with a full autorouter that creates the board from a netlist. But it is probably the best that can be managed in the absence of a netlist file and



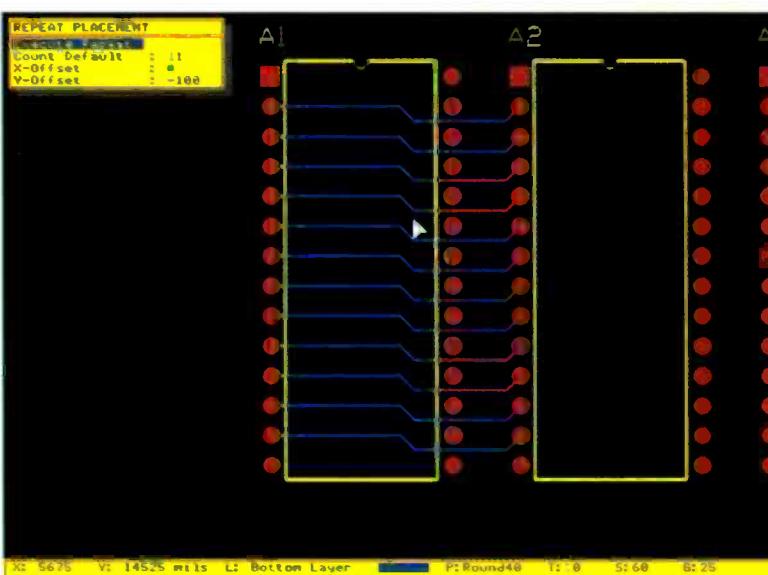*Visible and snap grids are fully adjustable.*



*The repeat feature is ideal for memory arrays.*

is quicker than placing the track step by step using the mouse, particularly on low-density boards where it could halve or more the design time compared to a similar package

### SYSTEM REQUIREMENTS

IBM-PC/XT/AT or compatible  
640K ram  
Dos version 2.0 or later  
Two floppy drives or hard disk  
Hercules, CGA, EGA, VGA etc.

### SUPPLIER DETAILS

JAV Electronics Limited  
Unit 12A Heaton Street  
Denton  
Manchester  
M34 3RG  
£95  
Tel: 061 320 7210

without such a tool.

Once all tracks have been placed, the electrical connectivity has been defined and Easytrax will generate a netlist file. It is unusual to have a netlist appear this late in the design sequence; netlists are generally prepared prior to laying out and serve little purpose afterwards. Probably the only use of such a netlist print out, as suggested in the manual, is to check the layout against the original circuit. A list of parts used on the board can also be generated. Again it is more common to see this earlier in the process but both these features are probably quite easy to include in the package and may be of use to some users.

True aficionados of design automation can further increase the power of Easytrax by creating their own macros. As in many other programmes, these are merely combinations of keystrokes that can be called up together at the press of a single key. They can be created by a special keystroke editor or learnt in action. Easytrax predefined macros are in most cases mere duplicates of single menu selections. They have been assigned to function keys to simulate the user interface of previous Protel products hence providing compatibility.

### Easy options for hard copy

There are several ways of obtaining a hard copy of artwork. Supplied with Easytrax is Easyplot, a separate programme allowing output on dot matrix printers, laser printers, plotters and photoplotters.

Range of printers and plotters is limited, but all the old favourites are there such as Epsons, HP and postscript lasers and Roland plotters. Being a separate programme Easyplot can be run simultaneously on a different machine or even on another site if required.

Printing the layout on a dot matrix printer is a cheap, easy and effective way to get a check print. It can be scaled up or down if required and can be completed with filled or skeleton tracks.

Skeleton tracks are quicker and wear the ribbon less, and are quite adequate for checking.

Results on a simple dot matrix printer are impressive to the point where it is tempting to use for artwork though in reality definition will not suffice. Any combination of layers can be combined onto a print and a mirror image selected for each layer.


The manual devotes considerable space to advice on using laser printers to generate artwork – an increasingly popular means of producing artwork. The major consideration is that of dimensional accuracy and Easyplot provides independent X and Y axis fine tune scaling factors to compensate for variations in the laser printer.

A whole chapter in the manual is devoted to Gerber plots (RS-274) and NC drill files, explaining not only how to generate them but some useful background information. It covers things like apertures, flash or stroke exposures and helps match settings to machines.
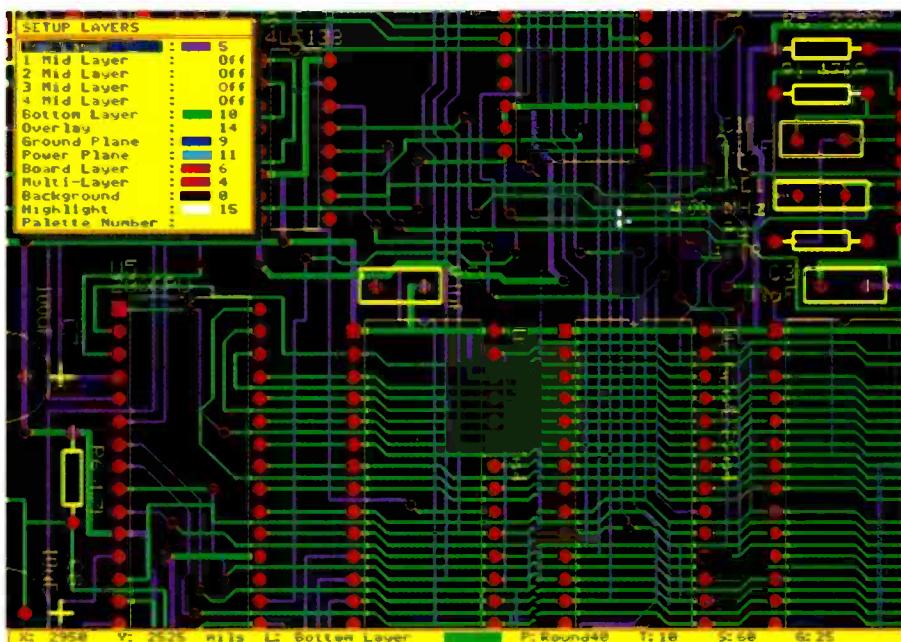
#### Professional feel

The look and feel of this package is that of a well tried and tested professional piece of software. Used on its own, it cannot be faulted. Organisations involved with surface mount components will not choose Easytrax. But they are likely to have a lot more than £100 to spend and Easytrax is aimed at a different market.

Anyone serious about computer aided design must question whether PCB layout



Layer colours are fully configurable.

enough or whether this together with a compatible schematic capture programme is needed.


Even the most accomplished layout software will require a lot of manual input if not fed data automatically from a schematic and

Easytrax suffers in this respect. But this must be seen in the context of the price which puts it into the reach of people who may be prepared to spend time to achieve a very high quality computer generated artwork. For these people Easytrax will prove to be a skilled and dedicated friend with features to satisfy any reasonable requirement and an easy to work with personality. ■
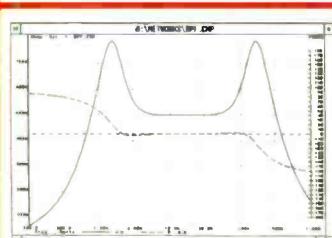
## SPICE•AGE Non-Linear Analogue Circuit Simulator £245 complete or £70 per Module

Those Engineers have a reputation for supplying the best value-for-money in microcomputer-based circuit simulation software. Just look at what the latest fully-integrated SPICE Advanced Graphics Environment (AGE) package offers in ease-of-use, performance, and facilities:

- Module 1 – Frequency response ● Module 3 – Transient analysis
- Module 2 – DC quiescent analysis ● Module 4 – Fourier analysis



Impedance sweep

#### 2 DC Quiescent analysis

SPICE•AGE analyses DC voltages in any network and is useful, for example, for setting transistor bias. Non-linear components such as transistors and diodes are catered for. (The disk library of network models contains many commonly-used components – see below). This type of analysis is ideal for confirming bias conditions and establishing clipping margin prior to performing a transient analysis. Tabular results are given for each node; the reference node is user-selectable.


**1 Frequency response**  
SPICE•AGE provides a clever hidden benefit. It first solves for circuit quiescence and only when the operating point is established does it release the correct small-signal results. This essential concept is featured in all Those Engineers' software. Numerical and graphical (log & lin) impedance, gain and phase results can be generated. A 'probe node' feature allows the output nodes to be changed. Output may be either dB or volts; the zero dB reference can be defined in six different ways.

**DC conditions within amplifier circuit**

Node	Voltage (V)	Current (A)
0	0.0000	0.0000
1	1.2000e-01	2.7000e-01
2	0.0000	0.0000
3	1.4164e-01	0.0000
4	0.0000	0.0000
5	7.4250e-01	0.0000
6	1.4164e-01	0.0000

## NEW VERSION 3.00 JUST RELEASED

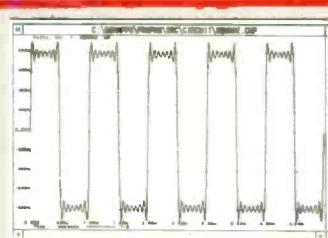
**FEATURES:** New manual with introductory text on Fourier analysis, Fourier Zoom window. **UPGRADES £65.**



Square wave synthesis (transient analysis)
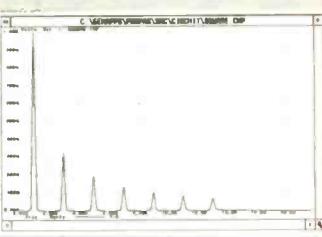
#### 4 Fourier analyses now with Hanning window option

SPICE•AGE performs Fourier transforms on transient analysis data. This allows users to examine transient analysis waveforms for the most prevalent frequency components (amplitude is plotted against frequency). Functions as a simple spectrum analyser for snapshot of transients. Automatically interpolates from transient analysis data and handles up to 512 data values. Allows examination of waveform through different windows. Powerful analytical function is extremely easy to use.



Spectrum of synthesised square wave (Fourier analysis)

If your work involves designing, developing or verifying analogue or digital circuits, you will wonder how you ever managed without Those Engineers circuit Simulation Software.

A good range of properly supported and proven programs is available and our expert staff are at your service.

Telephone: Charles Clarke on 071-435 2771 for a demonstration disk.

106a Fortune Green Road West Hampstead

London NW6 1DS

Tel: 071-435 2771 Fax: 071-435 3757


# Those Engineers LTD

# PCB CAD/CAE SOFTWARE FROM J.A.V. ELECTRONICS LIMITED

**Protel Autotrax Basic Ver. 1.61** offers the same excellent professional quality as Protel Autotrax Extended but with out full autorouting and autoplace. Includes CNC Drill, Photoplot and DXF export. Pads Import and EDF netlist support. Upgradeable to Protel Autotrax Extended.

**Protel Autotrax Extended** new Ver. 1.61 is a precision design tool that improves productivity for occasional and expert user alike. With full autorouting and autoplace.

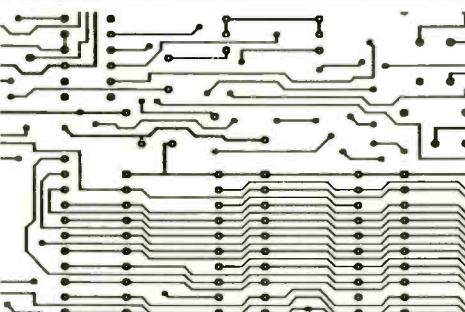**STARTING AT £75.00#  
WITH AUTOROUTING**



Please contact our Sales Office  
for Evaluation pack and full  
details of latest Versions

For MS/ Dos & MAC

**Protel Traxstar** new Ver. 1.38 is a costed rip-up and re-router option to Autotrax. Now includes redesigned rip-up algorithm, improved smoothing and new file re-start and file continue options.

**Protel Easytrax 2** at £75.00# is the low cost entry level package to the Protel Range. Upgradeable to Autotrax.

**Protel Schematic** Ver. 3.30 is a cost effective, high performance program for creating Schematic Diagrams. Netlist Generation.

The Sole UK Distributor for Protel CAD Software. Main Dealers for Roland A3 - A0 Plotters.

**J.A.V. ELECTRONICS LIMITED**


Unit 12a Heaton Street, Denton, Manchester, M34 3RG. Tel: 061 320 7210 Fax: 061 335 0119  
Price quoted is a cash with order price and excludes delivery and VAT. #Limited Period Only

CIRCLE NO. 108 ON REPLY CARD
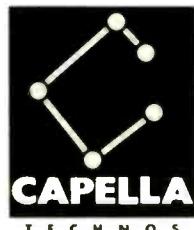
## A two year guarantee on all our second-hand Test and Measurement equipment!

To give you the confidence that you really did save money by buying second-hand, we are the only company to offer you the protection of a two year parts and labour guarantee on all the Test and Measurement equipment we supply.

Dealing in equipment from the leading manufacturers such as Hewlett Packard, Tektronix, Marconi, Philips, Gould, etc., we can offer you the best in test. Call us now for more information.



**0800 521231**


International Callers No. 44 344 869 226

Capella-Technos, Park House, The Pavilions, Downmill Road,  
Bracknell, Berkshire, RG12 1QS. Fax 0344 869230

11A

CIRCLE NO. 109 ON REPLY CARD

## brain boxes

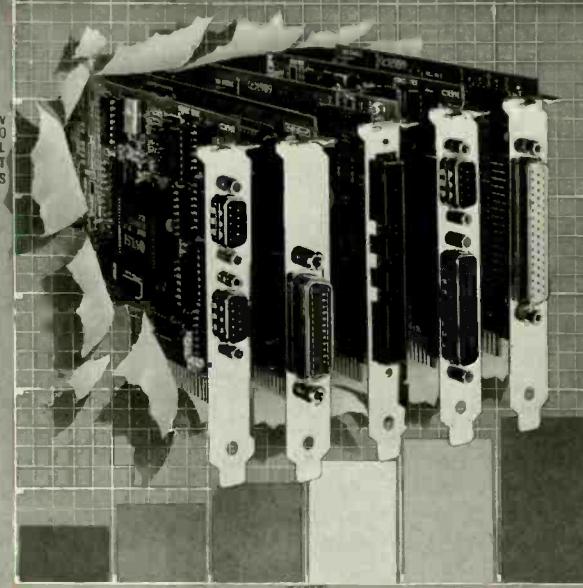

**IEEE488, Digital I/O, Timer  
Counters, RS232, RS422,  
RS485, D/A, A/D, Acquisition,  
Analysis**

**AND A WHOLE LOT MORE!**

Brain Boxes, Unit 3G,  
Wavertree Technology Park, Liverpool.

Tel: 051-220 7190  
& 051-220 2500

CIRCLE NO. 110 ON REPLY CARD

# MATHCAD ENGINEERING

**M**athsoft, the creator of MathCad, has issued an Electrical Engineering Application Pack for use with the package. Not only does it serve as a useful set of programs in its own right, but it also provides many welcome tips on applying MathCad to other problems.

As we have seen in a previous review (Modelling with MathCad, *EW + WW* March, pp. 230-233) MathCad has several features of interest to the electronics engineer. It is a page oriented-environment where mathematical expressions can be entered directly and evaluated, and has a good facility for graphing results and also displaying data in tabular form.

Many built-in functions are included such as ROOT and SOLVE which are quite powerful tools for solving iterative equations. Data can be imported from disk files and subjected to a range of text processing options. From an engineering prospective, there are several interesting features including a fix on the units which are used during the course of the calculations.

In the EEA pack some of the programs are of limited use but others are applicable to every-day engineering problems. The pack comes as a booklet with listings of each program and a generous description of application. The booklet is also accompanied by a floppy disk with the programs

## EEA PACK CONTENTS

Field patterns of a uniform linear array; waveguide, striplines, coaxial lines; two-port parameter conversions; network analysis using an admittance matrix; American wire gauge table transmission line impedance as function of frequency; Smith chart; transmission line calculations; FIR filter design by windowing design of a IIR filter; elliptical IIR filter design; Chebyshev polynomials; transfer function calculations; polar plots and Nyquist plots; Convolution and deconvolution; algebraic codes; quantising a signal; delta modulation; Z-transform applications, and unit definitions.


**Allen Brown finds the new addition to MathCad is a valuable tool for electrical engineers**

which can be imported directly into the MathCad environment.

A typical example from the selection is the Smith chart, used to map impedance as a function of reflection coefficient (Fig. 1). Data for creating the Smith chart is provided on the disc as a data file. As the changes are made to the load impedance  $Z$ , the contours change accordingly.

Engineers already using MathCad will find the EEA-pack helpful as it will most certainly suggest unrealised techniques which are available within the MathCad environment. ■

Fig. 1. Using the Smith chart from the MathCad EEA pack

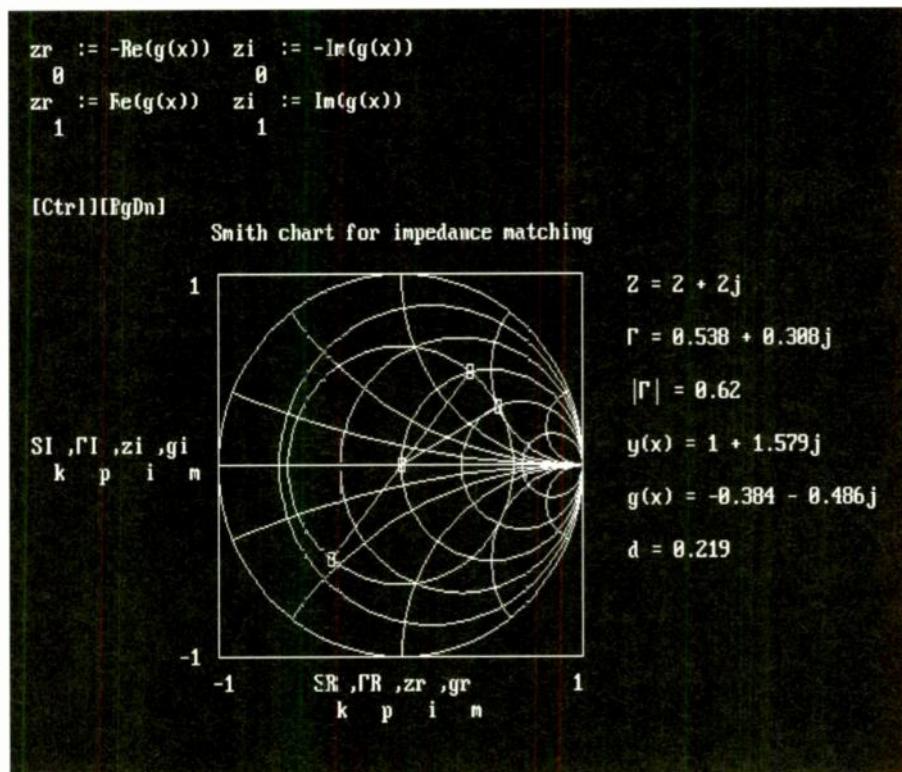

# Take the Sensible Route!

**B**oardMaker is a powerful software tool which provides a convenient and fast method of designing printed circuit boards. Engineers worldwide have discovered that it provides an unparalleled price performance advantage over other PC-based and dedicated design systems by integrating sophisticated graphical editors and CAM outputs at an affordable price.

## NEW VERSION

In the new version V2.40, full consideration has been given to allow designers to continue using their existing schematic capture package as a front end to BoardMaker. Even powerful facilities such as Top Down Modification, Component renumber and Back Annotation have been accommodated to provide overall design integrity between your schematic package and BoardMaker. Equally, powerful features are included to ensure that users who do not have schematic capture software can still take full advantage of BoardMaker's net capabilities.

**BoardMaker V2.40 is a remarkable £295.00 (ex. carriage & VAT) and includes 3 months FREE software updates and full telephone technical support.**

## A U T O R O U T E R

BoardRouter is a new integrated gridless autoroute module which overcomes the limitations normally associated with autorouting. **YOU** specify the track width, via size and design rules for individual nets. BoardRouter then routes the board based on these settings in the same way you would route it yourself manually.

This ability allows you to autoroute mixed technology designs (SMD, analogue, digital, power switching etc) in **ONE PASS** while respecting **ALL** design rules.

## GRIDLESS ROUTING

No worrying about whether tracks will fit between pins. If the track widths and clearances allow, BoardRouter will automatically place 1, 2 or even 3 tracks between pins.

## FULLY RE-ENTRANT


You can freely pre-route any tracks manually using BoardMaker prior to autorouting. Whilst autorouting you can pan and zoom to inspect the routes placed, interrupt it, manually modify the layout and resume autorouting.

**BoardRouter is priced at £295.00, which includes 3 months FREE software updates and full telephone technical support. BoardMaker and BoardRouter can be bought together for only £495.00. (ex. carriage & VAT)**




Tsien (UK) Limited  
Cambridge Research Laboratories  
181A Huntingdon Road  
Cambridge CB3 0DJ UK  
Tel 0223 277777  
Fax 0223 277747

All trademarks acknowledged

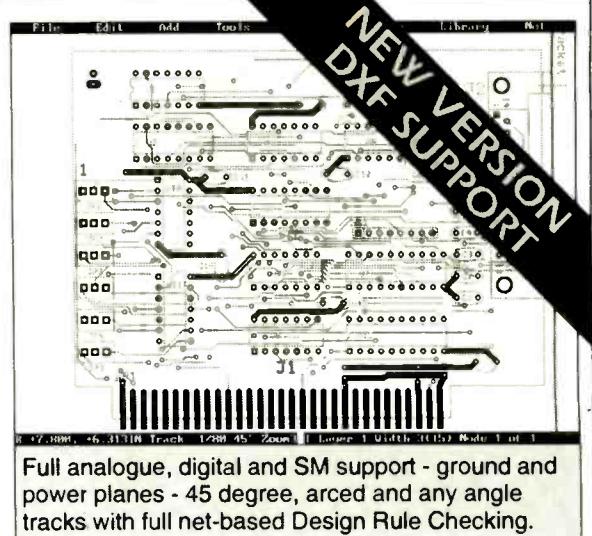

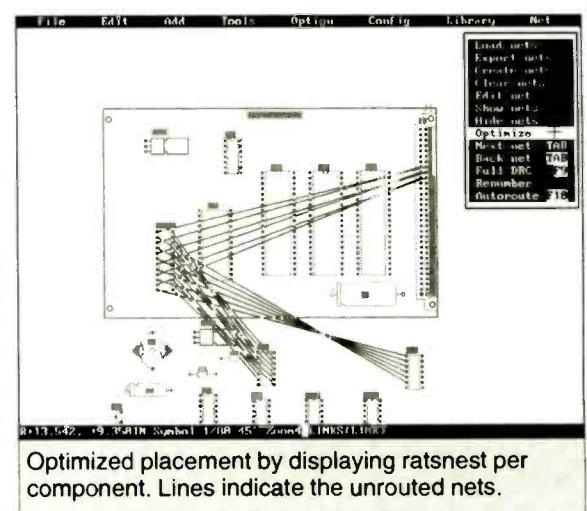Full analogue, digital and SMD support - ground and power planes - 45 degree, arced and any angle tracks with full net-based Design Rule Checking.



Optimized placement by displaying ratsnest per component. Lines indicate the unrouted nets.

## HIGHLIGHTS

- Net list import from OrCAD, Schema etc.
- Graphical and manual netlist entry
- Top down modification for ECOs
- Forward and back annotation
- Component renumber
- Effortless manual routing
- Fully re-entrant gridless autorouting
- Simultaneously routes up to eight layers
- Powerful component placement tools
- Copper fill
- Curved tracks
- Extensive Design Rule Checking
- Full complement of CAM outputs
- Support and update service
- Reports generator
- Gerber, PostScript & DXF output
- Full SMD support

**Don't just take our word for it. Call us today for a FREE Evaluation Pack and judge for yourself.**



# Circuits, Systems & Standards

*First published in the US magazine EDN and edited here by Ian Hickman.*

## Innovative design techniques yield optimum counter oscillator

### Need a noisy oscillator?


How to ruin the coherence of a frequency standard! RF engineers are used to designing or procuring frequency standards, for example a 10MHz reference for a synthesizer, where the requirement is not only for long-term frequency accuracy but also short-term stability and low sideband noise. This article describes an application where long-term frequency accuracy is just as important, but short-term stability is deliberately degraded in the interests of measurement accuracy. In addition, it also describes a novel application of that good old stand-by, the 1496 double balanced modulator. IH

**S**tarting with a 10-MHz oscillator and a handful of readily available commercial ICs, you can use the techniques described in this article to configure a 100-MHz counter oscillator that incorporates the random phase modulation needed to break coherence in time-interval-averaging systems.

#### The quest for incoherence


To eliminate any possibility of harmonic relationships between the oscillator's frequency and that of the input signal, you must randomly modulate the 10-MHz

**Fig. 1.** Using an electronic organ IC, the circuit in (a) yields random phase modulation of the 10-MHz reference-oscillator signal. The digital white noise from the IC varies  $D_1$ 's capacitance to detune the LC tank circuit. (b) shows the phase variation as a function of the varactor's capacitance.

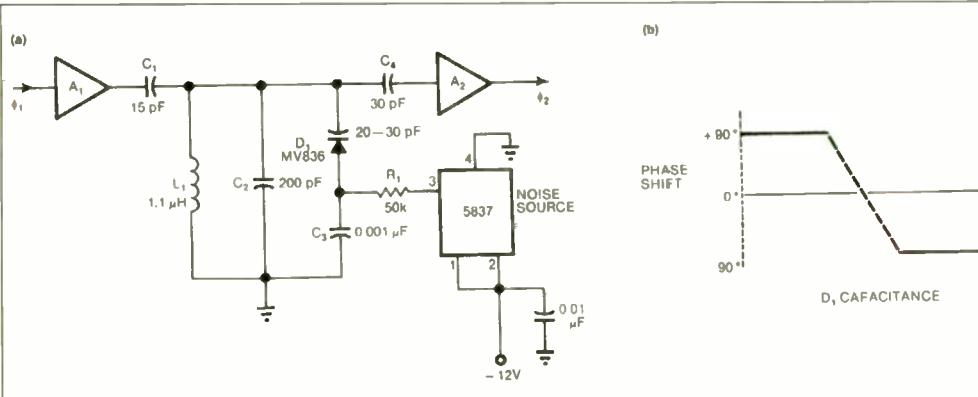


oscillator's phase before multiplying its frequency by ten. The phase-modulator section (Fig 1a.) comprises a 10-MHz tank, a varactor diode and a digital noise source applied to an RC timing circuit.

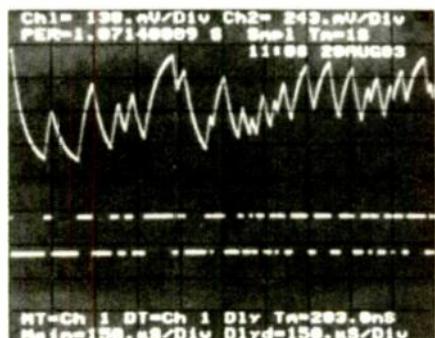The noise source used in the 1965A counter is an 8-pin IC widely used in electronic organs. The part – National Semiconductor's Model MM5837 – is a mos/MSI pseudo-random sequence



Trace A	Vertical	Horizontal
138mV/div	150μs/div	150μs/div
Trace B	243mV/div	150μs/div

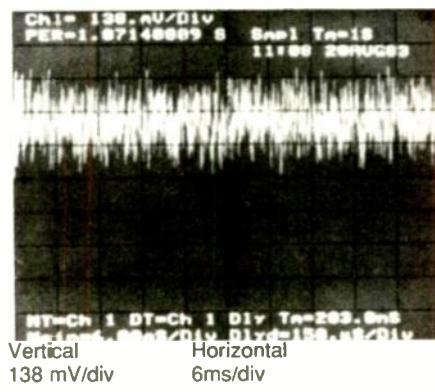

**Fig. 2.** Random ramping of the varactor's anode voltage is evident in (a)'s upper trace. The ramping is caused by the digital noise seen in the lower trace. (b) shows the anode voltage with a slower time scale.

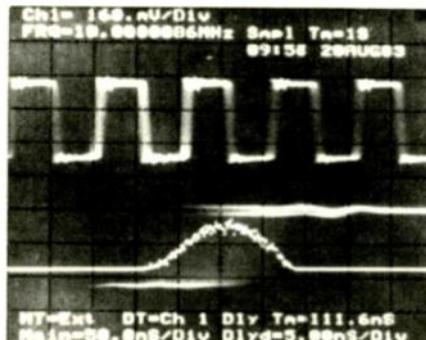


Fig. 3. The bell-shaped Gaussian distribution of the 10-MHz reference signal's phase is evident in trace C's digitised waveform.

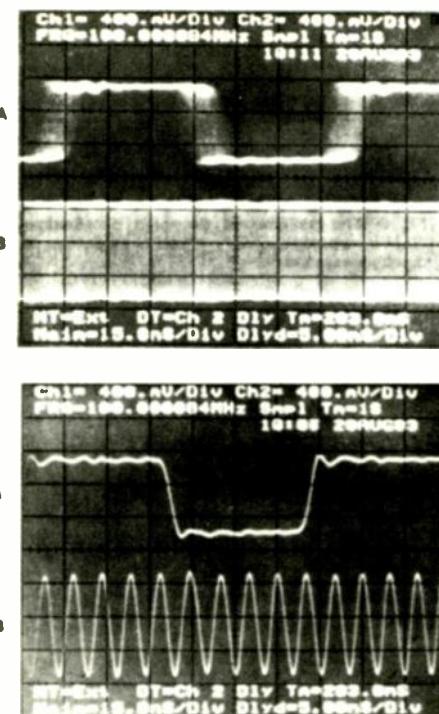



Fig. 4. Modulated and unmodulated 10- and 100MHz signals are seen in (a) and (b), respectively. The modulation shows up, naturally, as jitter in the scope traces.

generator designed to produce a broadband white-noise signal for audio applications. A built-in oscillator provides an output that switches between ground and the -12V rail.  $L_1$ ,  $C_2$ ,  $C_3$  and  $D_1$  constitute a tank circuit

**Electronic Circuits, Systems & Standards**  
edited by Ian Hickman, published by Butterworth Heinemann Newnes. ISBN 0 7506 0068 3. Price £20.

Since its appearance in 1956 the US-based EDN has established itself as a leader in controlled circulation electronics magazines. Now this "best" of EDN - with useful information on components, equipment, circuits, systems and standards is available in a 216 page hardback publication

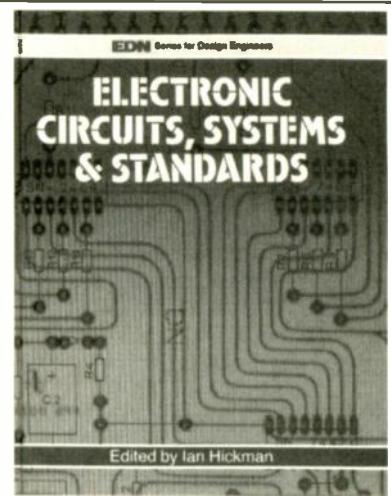Available from bookshops, or direct by postal application to EW + WW, Quadrant House, The Quadrant, Sutton Surrey SM2 5AS. Cost £20 plus £1.50 post and packing.



tuned close to 10MHz.  $D_1$  is an MV836 varactor diode whose capacitance is a function of the reverse-bias voltage; it varies from approximately 20 to 30pF.  $C_3$  and  $D_1$  form a series capacitance in parallel with the  $L_1/C_2$  parallel combination.  $C_2$ 's 200pF value in parallel with the diode's 20 to 30pF results in a 220 to 230pF tank capacitance, depending on the diode's reverse bias. With the tank tuned close to 10MHz, any change in tuning (arising from  $D_1$ 's variations) results in a phase shift of  $\phi_2$  relative to  $\phi_1$ . The change in phase is a function of the non-ideal properties of the tank's components and the amplifier circuitry's input and output impedances. Figure 1b shows the phase shift as a function of  $D_1$ 's capacitance variations.

$R_p$ , connected to the digital noise source output forms an RC time constant with  $C_3$ . Because the noise source pulse widths are always less than one time constant, the potential at  $D_1$  anode is a virtually random ramping of the reverse-bias voltage. In Fig. 2a, trace B shows the digital noise applied to the RC integrator; trace A, the virtually random ramping of  $D_1$  anode voltage. Figure 2b shows the same ramping signal on a different time scale.

The instantaneous voltage has an approximately Gaussian distribution, because the voltage applied to  $R_p$  is a broadband white-noise signal that itself has a Gaussian pulse-width distribution. The change in  $D_1$ 's capacitance has a nearly one-to-one relationship with the change in its reverse-bias voltage, resulting in an approximately Gaussian  $\phi_2/\phi_1$  phase distribution. Figure 3 trace A shows the phase-modulated, 10-MHz reference signal - trace B waveform is an expansion of a leading edge; trace C digitised waveform

shows the relative phase distribution at the leading edge's 50% point.

Although the 10 x frequency multiplier multiplies the relative phase shift, the absolute time shift remains constant. For example, if the  $\phi_2/\phi_1$  shift changes randomly by 10° p-p, the output shifts by 100° p-p - however, the 10MHz, 10° and 100MHz, 100° shifts result in a 2.78ns time shift.

How much total phase modulation is needed? This is a critical design parameter, but the answer is not intuitively obvious. The final 100MHz output needs to have an even distribution of phase shift relative to the unmodulated 10MHz ( $\phi_1$ ) reference. With an even phase distribution, a rising edge of the 100MHz clock occurs on the average only once in every 10ns window. The exact time occurrence of each edge of the oscillator waveform, however, is totally random.


This situation apparently creates a problem. With a Gaussianly modulated 10MHz reference clock, the 100MHz clock also exhibits Gaussian phase-shift distribution rather than the desired even distribution.

If the amount of modulation exceeds one full period (>10ns, or >360°), the distribution is effectively even for any 10ns window. When the output phase shift exceeds 360° p-p, the clock occurrences overlap into preceding and succeeding windows, resulting in overlapping distributions.

#### Why use Gaussian modulation?

Summing these overlapping distributions results in an almost even distribution.

Figures 4a and 4b show photos of unmodulated and Gaussian-modulated 10- and 100MHz signals. But, because this

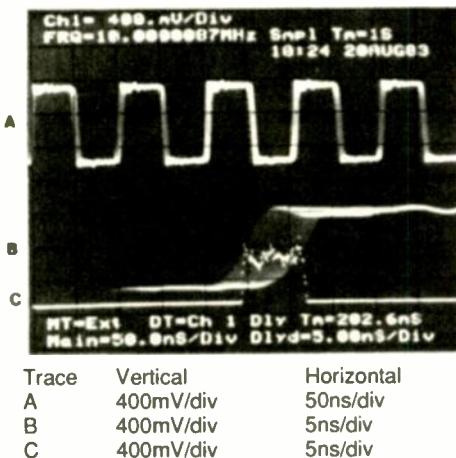

**Fig. 5.** A triangular waveform applied to the varactor's anode results in trace C's even distribution of phase shifts. This method, however, is difficult to control.

technique only allows you to approach an even distribution, why use Gaussian modulation at all? It would seem the ideal solution is to modulate evenly, and you could do this fairly easily.


First, remove the digital noise source and  $R_1$  from the phase-modulator circuit and apply a triangular waveform to  $D_1$ 's anode. Apply negative offset to the source and tune the frequency for a non-harmonic of 10MHz in the audio band. Monitor  $\phi_2$  relative to  $\phi_1$  and adjust the triangular-waveform peak-to-peak amplitude until exactly 36° phase shift results. With triangular-waveform reverse bias applied to  $D_1$ 's anode, the anode's instantaneous voltage is always evenly

distributed, resulting in a correspondingly even  $\phi_2/\phi_1$  phase-shift distribution, as shown in Fig. 5.

This technique is not without problems, however – you must obtain exactly 36° phase shift; no more, no less. If you obtain only 35° p-p shift, for example, the output will shift by 350° p-p. This scenario produces "voids" in the 100MHz signal (Fig. 6a). If, on the other hand, you overmodulate by 1°, the output displays 370° p-p shift. This situation results in the shift's overlapping into preceding and succeeding windows, destroying the evenness of the distribution (Fig. 6b).

Undermodulation and overmodulation conditions create undesirable bias, which occurs when clock edges are no longer totally random; the counter is biased to trigger in some areas of any 10ns window, in preference to other areas in the same window. The result is biased (ie, wrong) answers. For the two described undesirable conditions, each 10ns window has two distinct levels of even distribution, as shown in Figs 6a and 6b.

The exact amount of peak-to-peak phase shift depends on component values in the phase modulator's tank circuit. Because it's not practical to control tightly the components' variances, the best technique for attaining almost-even phase modulation is to overmodulate the 10MHz signal (in Gaussian fashion) in the range of 50° to 80°. This action results in 500° to 800° p-p modulation of the 100MHz output. With this Gaussian technique, the exact amount of peak-to-peak modulation is not critical.

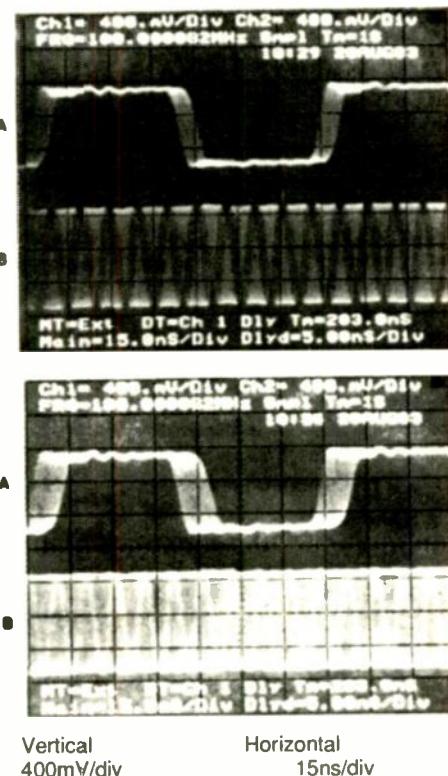

**Fig. 6.** Undermodulation and overmodulation create problems in the even-distribution method, evident in these photos. Undermodulation creates voids in the 100MHz signal (a); overmodulation, an uneven distribution (b).

#### Multiplier steps up the reference


The frequency multiplier steps up the reference oscillator's frequency from 10 to 100MHz, resulting in a 10ns reference-clock interval. As Fig. 7a shows, the multiplier circuit comprises three blocks: a current impulse generator, a 100MHz tank and a comparator amplifier. Figure 7b gives a detailed schematic of the multiplier chain.



The 20MHz current-impulse generator uses a modulator/demodulator IC to create current spikes for each transition of the 10MHz input signal.

The IC used is the industry-standard 1496, produced by Motorola, National Semiconductor, Signetics and Silicon General. Figure 8a shows the IC's internal configuration and associated input/output circuitry.

In this application, the unit is always

**Fig. 7.** Multiplying the 10MHz reference signal by ten is easy with widely available modulator/demodulator and comparator ICs. Current impulses from the first IC cause 100MHz ringing in the tank circuit; the comparator evens up the waveform.

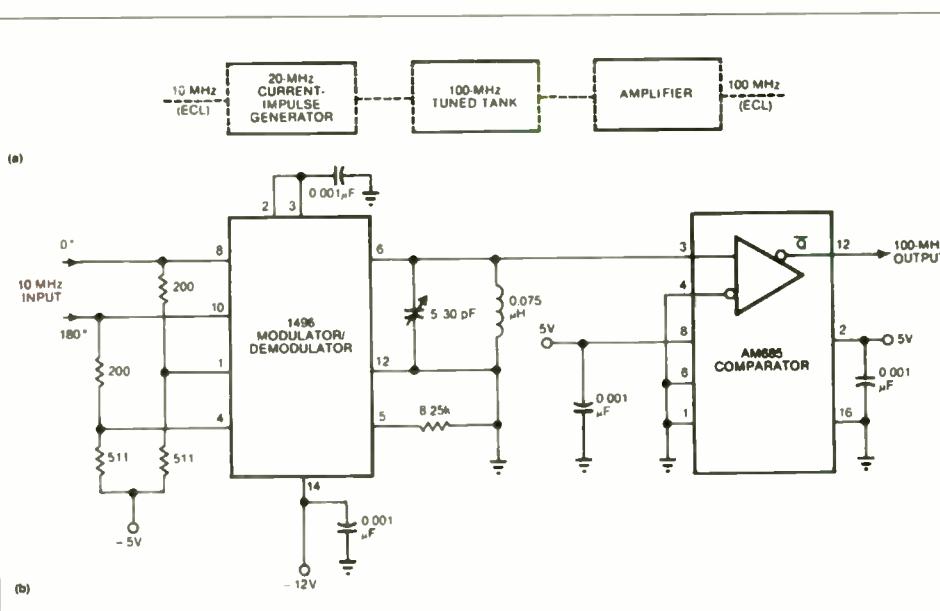

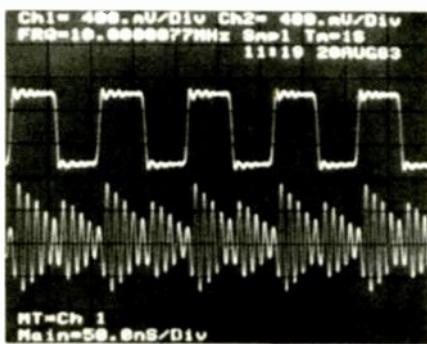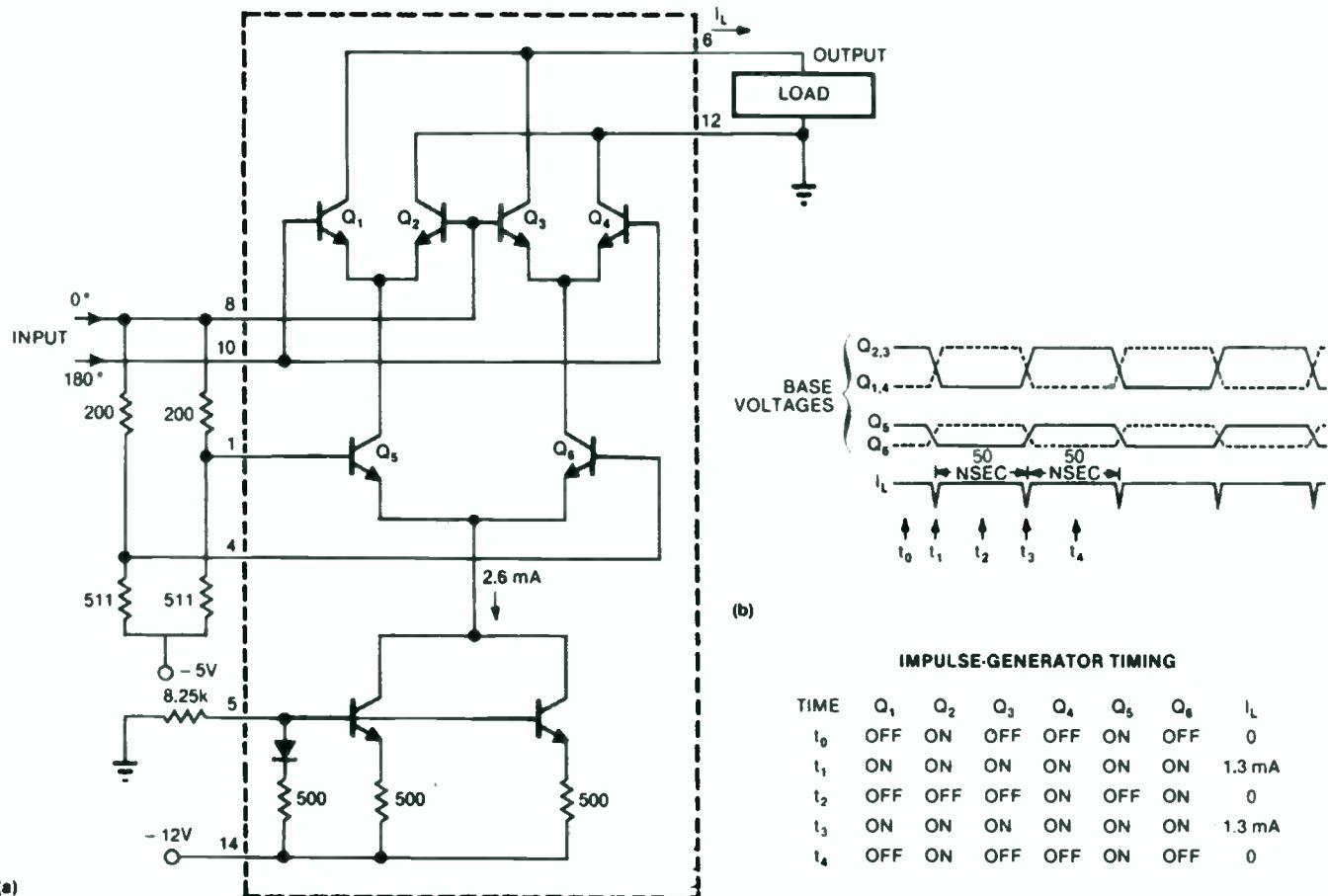

Vertical 400mV/div      Horizontal 15ns/div

**Fig. 9.** Excited once every 50ns by a jolt of current, the tank circuit creates a series of exponentially decaying 100MHz waveforms. The comparator then does its limiting and amplifying job to produce a uniform 100MHz output.

**Fig. 8.** The modulator/demodulator IC emits a current pulse for each transition of the 10MHz signal's waveform, resulting in a 20MHz chain of pulses.

operated in a saturated mode, resulting in digital current switching.

The 1496 has two differential-input pairs. The 10MHz oscillator connects to the upper inputs (pins 8 and 10), driving a quad differential pair (Q<sub>1,2,3,4</sub>). The same signal, slightly attenuated and shifted toward the negative, connects to the lower inputs (pins 1 and 4), driving a differential current switch (Q<sub>5,6</sub>). In steady state conditions, all current supplied by the constant current source (-2.6mA) is dumped from pin 12 to ground. When the input at pins 8 and 10 is high relative to that at pins 1 and 4, the current is channelled through Q<sub>5</sub> and Q<sub>2</sub>.

When the input's polarity reverses, all

current is channelled through Q<sub>6</sub> and Q<sub>4</sub>. The only time the load receives any excitation is during the input's high-to-low or low-to-high transition. At one point during each transition, all transistors are equally biased in their active range, resulting in the dumping of approximately half the current (-1.3mA) from pin 6 to the load. **Figure 8b** shows a functional timing diagram of the relative transistor base voltages and output current.

With the output of 20MHz current pulses, it's relatively easy to pick off the fifth harmonic (100MHz) with a highly tuned, high-Q tank circuit. **Figure 9** shows the tank's output – an exponentially decaying sinusoid excited once every 50ns. Finally, the AM685 high speed comparator (made by Advanced Micro Devices) yields the amplified 100-MHz output.

**Johnnie Hancock, Hewlett-Packard Corp.**

**A** record 170 papers from 13 countries drew over 400 delegates to Salt Lake City to hear the latest research results from the world's major bio-effects laboratories – and there was plenty to interest electronics engineers wondering whether their daily exposure to electromagnetic fields could be a long-term health hazard.

Most of the presented papers concerned ELF effects, but there were also insights into RF and microwave interaction with human and animal tissues.

Arguably the highlight of these was a further sneak preview of a new Electric Power Research Institute-funded study measuring EM fields in the homes of 232 leukaemic children in six counties round Los Angeles.

The EPRI study has already received much media attention, but has still not been accepted for publication. The research team, headed by Dr. John Peters of Southern California University and Joe Bowman had clearly hit difficulties with their dosimetry. Bowman admitted that instrument battery failure and related problems had necessitated substitution by another make after the study was underway. So data-sets were not comparable, and that (perhaps in consequence) no correlation was likely to be reported between electric field strength and leukaemia incidence.

A correlation was found, however, with external wiring configurations, and with certain appliance use (eg hair-dryers, monochrome TVs) – seen by cynics as a move which neatly shifts product responsibility from EPRI members to appliance manufacturers.


Further question marks hang over the

#### UK BEHIND THE TIMES?

Shamefully only one (minor) paper presented at BEMS came from the UK, demonstrating how far behind we are in this field. It was from the NRPB and looked at what happens to fetal development of mice in a 20mT field – a level somewhat removed from the real world.

The researchers found no adverse effects. The paucity of UK bio-electromagnetics research effort contrasted with the appointment of Brian Maddock from the UK National Grid to the chair of the mysterious "Research Coordinators' Group", which met during the two days prior to the main meeting behind tightly closed doors.

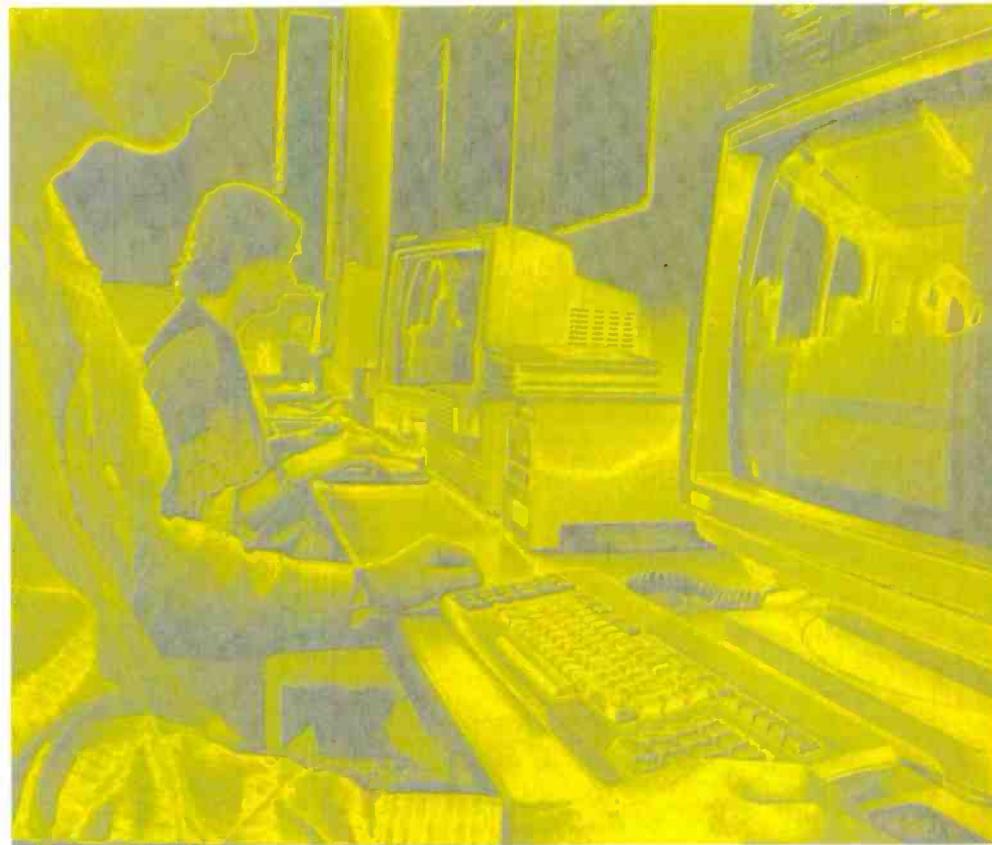Despite all the media publicity voicing concerns about power-lines, computer screens, electric blankets and microwave ovens, the Grid has not researched the measured effects of power-lines on adult members of the public (though one promised study is underway), and its current modest £600,000 research programme is largely confined to peripheral cell studies.



## Hazarding a guess at EMR effects

**We are starting to understand cellular mechanisms. So will we look back on current EM limits with incredulity? Roger Coghill reports from bio-hazard conference BEMS 1991.**

Peters' protocol. Spot measurements of ambient EM fields were taken in the middle of children's bedrooms, rather than at the bed itself, and thus were well away from domestic electric circuits, which are usually routed round the walls. Mid-room fields thus measured are likely to be minimal: other research has shown that within one room alone ambient EM fields can vary up to ten-fold.

Another somewhat disappointing paper came from Bob McLaughlin of EPA, who last year caused an international storm by proposing in his 400-page draft review of the published research that EM fields should be viewed as a "probable human carcinogen". Publication of the final version of the EPA report has been delayed ever since, and his BEMS presentation did not build on last year's conclusions. Some were

saying that the final EPA document may never actually see publication.

#### New initiatives

Several new initiatives were announced at the conference, and the Health Effects Research Laboratory (previously connected with auto exhaust emission research) announced a \$2.5 million annual research effort. The initiative will commence in June 1992 consisting mainly of US research project applications and 60Hz. studies.

In Canada a 600 case-control study of childhood cancer was just beginning, expected to report in four years time, while the National Academy of Sciences and the FDA are also beginning major projects in a research field previously dominated by EPRI funding.



The AR3000 now extends your listening horizons. Frequency coverage is from 100KHz to 2036MHz without any gaps in the range. All mode: USB, LSB, CW, AM, FM (narrow) FM (wide). 400 memory channels are arranged in 4 banks x 100 channels. 15 band pass filters before the GaAsFet RF amplifiers ensure high sensitivity throughout the entire range with outstanding dynamic range and freedom from intermodulation effects. An RS232 port is provided to enable remote operation by plugging directly into most personal computers. ACEPAC3 is an exclusively developed multi-function IBM-PC based program to further increase the versatility of the AR3000. A sweep facility provides a spectrum analysis graph. The very latest version displays frequencies in X axis and squelch opening percentage on each frequency in the programmed frequency search range. This indicates 'how active' the frequencies are in the programmed search range. In addition to the graphic display, ACEPAC3 can produce a detailed numerical list from the graphic information. One memory file has 400 channels divided into 4 banks of 100 channels. More than one memory file can be created to increase the memory storage capability. If you make just one extra memory file you can store 800 memory channels!

R.R.P. Inc VAT AR3000 £765 ACEPAC-3 £119

CIRCLE NO. 112 ON REPLY CARD

## KESTREL ELECTRONIC COMPONENTS LTD

★ All items guaranteed to manufacturers' spec.  
★ Many other items available.

'Exclusive of V.A.T. and post and package'

	1+	100+		1+	100+
Z8530 (4 MEG)	0.60	0.30	62256LP-100	3.60	2.45
Z80A CPU	0.80	0.65	6264LP-10	1.40	1.10
Z80A CTC	0.50	0.30	6116LP-10	1.40	0.70
Z80A PIO	0.60	0.40	2764A-25	1.60	1.30
Z80A DMA	0.95	0.65	27C64-25	1.65	1.35
Z80A DART	1.20	0.90	27C128-25	1.60	1.20
Z80A (CMOS) CPU	1.20	0.90	27128A-25	1.60	1.38
Z80B (CMOS) CTC	0.70	0.45	27256-25	1.80	1.40
1488	0.16	0.12	27C256-25	1.80	1.55
1489	0.16	0.12	27C512-20	2.40	2.04
LM324	0.25	0.14	74LS75	0.16	0.12
ILO-74	1.20	0.85	74LS83	0.11	0.08
ULN2803A	0.50	0.35	74LS93	0.14	0.10
6502P	2.20	1.56	74LS109	0.16	0.12
6522P	2.20	1.56	74LS125	0.12	0.09
65C02P2	3.40	3.00	74LS138	0.16	0.12
65C21P2	3.00	2.60	74LS148	0.20	0.16
74HCT02	0.10	0.07	74LS221	0.24	0.18
74HCT04	0.10	0.07	74LS273	0.21	0.16
74HCT125	0.26	0.23	74LS368	0.14	0.10
74HCT373	0.22	0.20	74LS374	0.19	0.14
74HCT541	0.34	0.27	8255-5	1.20	0.90

All memory prices are fluctuating daily, please phone to confirm prices

178 Brighton Road,  
Purley, Surrey CR2 4HA  
Tel: 081-668 7522. Fax: 081-668 4190.

CIRCLE NO. 113 ON REPLY CARD

# Complete your tools with Antex Soldering Irons and Stations



The art of accurate soldering is to maintain the bit temperature at the optimum level.

Antex fixed setting, thermally balanced, high efficiency irons maintain constant tip temperature and offer a wide range of soldering bits to suit your particular application.

For the more sophisticated applications, control at lower temperatures is essential. In these cases an adjustable temperature soldering iron is required. Also available are soldering stations with the option of digital temperature read out.

Antex products are designed for precision soldering to meet the demands of precision electronics.

Ask for Antex by name at leading Electronics distributors or return the coupon to receive full details of the complete range.



**ANTEX**

Please send me full details of the complete range of Antex Soldering Products.

Name \_\_\_\_\_

Address \_\_\_\_\_

CIRCLE NO. 114 ON REPLY CARD

Energetech Consultants and The National Cancer Institute are also investigating childhood lymphocytic leukaemia and low frequency EM fields, a happy combination of public and private enterprise. They reported in a pilot study that geometric mean magnetic field exposure in 29 test cases (between four months and 8 years) ranged between 0.8-1.4mG with a standard deviation of 2.4. This suggests maxima in excess of 3.36 mG, which is above the "carcinogen threshold" found by Savitz and others. Final results from these studies will not report for some years.

#### Limits announced on VDU exposure

High on the list at Salt Lake were VDU bio-effects papers. The Swedish Government agency Swedac has announced permitted exposure guidelines for ELF fields emitted from computer screens (effective from January 1991) at only 25V/m electric and 2.5 mG magnetic, and the US is likely to follow soon with similar if slightly higher E-field guidelines, possibly 50V/m.

The problem - ultimately likely to cause an even bigger stir than the EPA report - is that several of the BEMS papers were reporting consistently that such levels are by no means uncommon in the bedrooms of sleeping adults or children. The Peters-Bowman report for example found outlier fields averaging 27mG, with a maximum of 67mG.

Houses under power-lines and utility- or related occupations could exhibit even higher levels.

Clearly it is illogical that NRPB guidelines should permit chronic exposure to field levels in the home, or factory, which are likely to be banned for computer screen operators. By January 1993 the European Commission will have to set its own standards, probably following the Swedish model. LCD or gas plasma screens (which emit little if any EM radiation) are not likely

to become common-place before the mid 1990s, there are some 8 million aging VDUs being used right now in the UK alone, many of which are probably illegal by the new Swedish standard. These can be tested by cheap Gauss and E-field meters now becoming available at under £50 both here and in the US.

Against this controversial background all eyes were on the latest VDU research findings. Monica Sandstrom from Sweden's National Institute of Occupational Health at Umea reported a 3.0 odds ratio of likely skin symptoms from VDU use, and another Swedish paper (Hamnerius and Galt from Goteborg) revealed a means of reducing magnetic VDU fields by superimposing equal and opposite fields round the deflection coils. (Incidentally Howard Bassen from the FDA's Center for Devices and Radiological Health coyly announced a similar reduction technique for electric blankets, which the FDA has patented.

But if the FDA is already recognising EM bio-hazards it must be asked why the epidemiology results are so controversial? Could it be because of a delicate dance of avoidance by vested interests, resulting in contrived or dubiously flawed studies like that of Peters- and indeed Fulton before him?).

Other studies on eggs and rats fuelled the VDU controversy, and from Serduk and Polka in the USSR one significant, but overlooked paper, reported the bio-effects on 1386 children living in 13 cities near radar sites.

The children showed psychoneurological impairment 2-3 times more often than that of controls, including delay in puberty by up to one year, and also haemodynamic lability, increasing in proportion to exposure. These effects were confirmed by clinical examination of their CNS physiology. Exposure levels were stated as being in the order of  $50\mu\text{W/cm}^2$ , which is of course wildly below current Western exposure limits.

#### Dramatic confrontation

The most dramatic moments in the meeting happened during a set-piece confrontation between Professor Robert Park of the American Physical Society and former Nobel laureate Eberhardt Neumann. They debated the existence of any bio-effects from non-ionising EM fields.

Park's brave opening argument was that thermal noise is some 2000 times the levels supposed to cause bio-effects, and that experimental "evidence" is far from robust.

He cited the difficulties confronting exponents of the ion cyclotron resonance hypothesis of EM-cell interaction (eg the resonating radius of the ion's path is over a metre across, during which orbit it will inevitably collide with other particles). He also recalled the famous calcium efflux experiments of Ross Adey and Carl Blackman, where quite differing results

#### HOME EXPERIMENTS

New light is emerging on why some homes have high fields and others do not. Creation and elimination of unbalanced ground return or "vagabonding" currents was the subject of at least three papers, mainly from Europe. These imbalances occur when the current from a transformer returns not via the neutral cable offered for the purpose, but directly through the ground, usually because this is a quicker route. Such unbalanced currents can cause magnetic fields as high as 12mG in some homes, and since mere distance from a sub-station is not crucial to the field strength (as we have shown), they may provide a clue to childhood leukaemias and to certain kinds of adult ill health.

(both inhibition and enhancement) were found in very similar protocols, and suggested it all simply boiled down to temperature differences. He even cited the new Peters study as being atypically equivocal and confusing result.

In fact Park's information on ion cyclotron resonance is out of date - Lednev's precession hypothesis has probably now superseded it - and one paper by Bob Fitzsimmons from Loma Linda reported good experimental confirmation of his notion, (though another from Goteborg using patch clamped techniques found no effect).

Neumann replied that organic cells were clearly capable of selective signal recognition and amplification. He cited the acetylcholine receptor as an example of information storage, and alluded to the late Professor Frohlich's examples of retinal signal amplifying systems. Because of electrochemistry there is always an E-field effect in biological systems, he concluded, just as there is always  $kT$  thermal noise.

But just as radio technology allows us to select radio signals and amplify them coherently, cells can also distinguish signals against a high noise background. Moreover they are capable of co-operative action, and this alone can be viewed as an amplification system.

Ross Adey had his own view on the exchanges and accused professor Parks of "an appalling ignorance of the way biology works" and questioned whether he should have been allowed to address the meeting at all.

But controversy apart, BEMS this year gave the distinct impression that real progress has been made in understanding cellular processes and mechanisms, and that epidemiology is not far behind. Within a few years the current NRPB guidelines will surely be looked back on with almost incredulity, just as we look back today with horror at the early days of X-radiation limits.

#### PIONEER WORK

This year's D'Arsonval Award went to Andy Bassett for his pioneer work in non-union fracture repair using specially structured EM waveforms applied to the locus of the fracture.

Thousands of people would have now been amputees if it had not been for his techniques.

But Bassett's influence stretches far beyond that. Reba Goodman went first to him before commencing her decades-long programme of investigation into EM-induced RNA transcription, which has gained us so much knowledge about how weak EM fields cause important genetic changes. The emergence of electromagnetic medicine of this sort precludes a new paradigm in therapeutic practice, and once more there were a scattering of papers this year on such research.

**UNIDEN SATELLITE RECEIVER** Brand new units (model 8008) £60.00 ref 60P4R also some 7007's also £60.00 ref 60P5R

**SPECTRUM +2 COMPUTER** Built in data recorder, 128K, psu and manuals £59.00 ref 59P4R

**SPECTRUM +3 COMPUTER** Built in disc drive, 128K, psu and manuals £79.00 ref 79P4R

**AMSTRAD CPC464 COMPUTER** No manuals but only £79.00 ref 79P5R

**AMSTRAD CPC6128 COMPUTER** Again no manuals but only £149.00 ref 149P4R

**AMSTRAD GT65** Green screen monitor £49.00 ref 49P4R

**AMSTRAD PORTABLE PC'S FROM £149 (PPC1512SD), £179 (PPC1512DD), £179 (PPC1640SD), £209 (PPC1640DD).** MODEMS £30 EXTRA. NO MANUALS OR PSU.

AMSTRAD PC BARGAIN!!!!!!

PC 1512D COMPLETE WITH CGA COLOUR MONITOR, 2 DISC DRIVES, MANUALS ETC ONLY £249.00 REF 249P4R

**HIGH POWER CAR SPEAKERS.** Stereo pair output 100w each, 4ohm impedance and consisting of 6.1/2" woofer 2" mid range and 1" tweeter. Ideal to work with the amplifier described above. Price per pair £30.00 Order ref 30P7R.

**2KV 500 WATT TRANSFORMERS** Suitable for high voltage experiments or as a spare for a microwave oven etc. 250V AC input. £10.00 ref 10P39R

**MICROWAVE CONTROL PANEL** Mains operated, with touch switches. Complete with 4 digit display, digital clock, and 2 relay outputs one for power and one for pulsed power (programmable). Ideal for all sorts of precision timer applications etc. £6.00 ref 6P18R

**FIBRE OPTIC CABLE.** Stranded optical fibres sheathed in black PVC. Five metre length £7.00 ref 7P29R

**12V SOLAR CELL.** 200mA output ideal for trickle charging etc. 300 mm square. Our price £15.00 ref 15P42R

**PASSIVE INFRA-RED MOTION SENSOR.**

Complete with daylight sensor, adjustable lights on timer (8 secs -15 mins), 50' range with a 90 deg coverage. Manual override facility. Complete with wall brackets, bulb holders etc. Brand new and guaranteed. £25.00 ref 25P24R

Pack of two PAR38 bulbs for above unit £12.00 ref 12P43R

**VIDEO SENDER UNIT** Transmit both audio and video signals from either a video camera, video recorder or computer to any standard TV set within a 100' range! (tune TV to a spare channel). 12V DC op. £15.00 ref 15P39R Suitable mains adaptor £5.00 ref 5P19R

**FM TRANSMITTER** housed in a standard working 13A adapter (bus is mains driven). £26.00 ref 26P2R

**MINIATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range of up to 2 kilometres. Units measure 22x52x15mm. Complete with cases. £30.00 ref 30P12R

**FM CORDLESS MICROPHONE** Small hand held unit with a 50' range! 2 transmit power levels reqs PP3 battery. Tuneable to any FM receiver. Our price £15. ref 15P42AR

**10 BAND COMMUNICATIONS RECEIVER.** 7 short bands, FM, AM and LW/DX/local switch, tuning eye! mains or battery. Complete with shoulder strap and mains lead. **NOW ONLY £19.00!! REF 19P14R.**

**WHISPER 2000 LISTENING AID.** Enables you to hear sounds that would otherwise be inaudible. Complete with headphones. Cased. £5.00 ref 5P17R

**CAR STEREO AND FM RADIO** Low cost stereo system giving 5 watts per channel. Signal to noise ratio better than 45db, wow and flutter less than 35%. Neg earth. £25.00 ref 25P21R

**LOW COST WALKIE TALKIES.** Pair of battery operated units with a range of about 150'. Our price £8.00 a pair ref 8P50R


**7 CHANNEL GRAPHIC EQUALIZER** plus a 60 watt power amp! 20-21kHz 4-8R 12-14v DC negative earth. Cased. £25. ref 25P14R

**NICAD BATTERIES.** Brand new top quality. 4 x AA's £4.00 ref 4P44R, 2 x C's £4.00 ref 4P73R, 4 x D's £9.00 ref 9P12R, 1 x PP3 £6.00 ref 6P35R

**TOWERS INTERNATIONAL TRANSISTOR SELECTOR GUIDE.** The ultimate equivalents book. Latest edition £20.00 ref 20P32R

**CABLE TIES.** 142mm x 3.2mm white nylon pack of 100 £3.00 ref 3P104R Bumper pack of 1,000 ties £14.00 ref 14P6R

## VIDEO AND AUDIO MONITORING SYSTEM

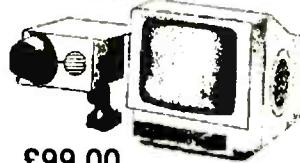

£99.00

Brand new units consisting of a camera, 14cm monitor, 70 metres of cable, AC adapter, mounting bracket and owners manual. 240v AC or 12v DC operation complete with built in 2 way intercom. £99.00 ref 99P2R

1991 CATALOGUE AVAILABLE NOW IF YOU DO NOT HAVE A COPY PLEASE REQUEST ONE WHEN ORDERING OR SEND US A 6" X 9" SAE FOR A FREE COPY.

**GEIGER COUNTER KIT.** Complete with tube, PCB and all components to build a battery operated geiger counter. £39.00 ref 39P1R

**FM BUG KIT.** New design with PCB embedded coil. Transmits to any FM radio. 9v battery reqd. £5.00 ref 5P15R

**FM BUG** Built and tested superior 9v operation. £14.00 ref 14P3R

**COMPOSITE VIDEO KITS.** These convert composite video into separate H sync, V sync and video. 12v DC. £8.00 ref 8P39R

**SINCLAIR CS MOTORS** 12v 29A (full load) 3300 rpm 6"x4" 1/4" O/P shaft. New. £20.00 ref 20P22R

As above but with fitted 4 to 1 inline reduction box (800rpm) and toothed nylon belt drive cog £40.00 ref 40P6R

**SINCLAIR CS WHEELS** 13" or 16" dia including treaded tyre and inner tube. Wheels are black, spokes one piece poly carbonate. 13" wheel £5.00 ref 6P20R, 16" wheel £6.00 ref 6P21R

**ELECTRONIC SPEED CONTROL KIT** for cs motor. PCB and all components to build a speed controller (0-95% of speed). Uses pulse width modulation. £17.00 ref 17P3R

**SOLAR POWERED NICAD CHARGER.** Charges 4 AA nicads in 8 hours. Brand new and cased £6.00 ref 6P3R

MO

## AT 286 MOTHERBOARD

640K RAM

## UPGRADABLE TO 4M

AT CASE

## AT POWER SUPPLY

AT KEYBOARD

MANUAL

## NO I/O CARDS

£139

**ANSWER MACHINES BT** approved remote message playback, intergal push button phone, power supply and tape. Exceptional value at £45.00 ref 45P2R

**CAR IONIZER KIT** Improve the air in your car! clears smoke and helps to reduce fatigue. Case required. £12.00 ref 12P8R

**6V 10AH LEAD ACID** sealed battery by yuasa ex equipment but in excellent condition now only 2 for £10.00 ref 10P95R

**12 TO 220V INVERTER KIT** As supplied it will handle up to about 15w at 220v but with a larger transformer it will handle 80 watts. Basic kit £12.00 ref 12P17R Larger transformer £12.00 ref 12P41R

**VERO EASI WIRE PROTOTYPING SYSTEM** ideal for designing projects on etc. Complete with tools, wire and reusable board. Our price £6.00 ref 6P33R

**MICROWAVE TURNTABLE MOTORS.** Ideal for window displays etc. £5.00 ref 5P165R

**STC SWITCHED MODE POWER SUPPLY** 220v or 110v input giving 5v at 2A, +24v at 0.25A, +12v at 0.15A and +9v at 0.4A £6.00 ref 6P59R

**HIGH RESOLUTION 12" AMBER MONITOR** 12v 1.5A Hercules compatible (TTL input) new and cased £22.00 ref 22P2R

**VGA PAPER WHITE MONO** monitors new and cased 240v AC. £59.00 ref 59P4R

**25 WATT STEREO AMPLIFIER** STK043. With the addition of a handful of components you can build a 25 watt amplifier. £4.00 ref 4P69R (Circuit dia included).

**LINEAR POWER SUPPLY** Brand new 220v input +5 at 3A, +12 at 1A, -12 at 1A. Short circuit protected. £12.00 ref 12P21R

**MAINS FANS** Snail type construction. Approx 4" x 5" mounted on a metal plate for easy fixing. Now £5.00 ref 5P166R

**POWERFUL IONIZER KIT.** Generates 10 times more ions than commercial units! Complete kit including case. £18.00 ref 18P2R

**MINI RADIO MODULE** Only 2" square with ferite aerial and tuner. Superhet. Req's PP3 battery. £1.00 ref BD716R

**HIGH RESOLUTION MONITOR** 9" black and white Phillips tube in chassis made for OPD computer but may be suitable for others. £20.00 ref 20P26R

**BARGAIN NICADS AAA SIZE 200MAH 1.2V PACK OF 10** £4.00 ref 4P92R, **PACK OF 100** £30.00 ref 30P16R

**CB CONVERTORS.** Converts a car radio into an AM CB receiver. Cased with circuit diagram. £4.00 ref 4P48R

**FLOPPY DISCS.** Pack of 15 £1.31/2" DSDD £10.00 ref 10P88R. Pack of 10 5 1/4" DSDD £5.00 ref 5P168R

**SONIC CONTROLLED MOTOR** One click to start, two click to reverse direction, 3 click to stop! £3.00 each ref 3P137R

**FRESNEL MAGNIFYING LENS** 83 x 52mm £1.00 ref BD827R

**LCD DISPLAY.** 4 1/2 digits supplied with connection data £3.00 ref 3P77R or 5 for £10.00 ref 10P78R

**ALARM TRANSMITTERS.** No data available but nicely made complex transmitters 9v operation. £4.00 each ref 4P81R

**TRANSMITTER RECEIVER SYSTEM** Originally made for nurse call systems they consist of a pendant style transmitter and a receiver with telescopic aerial 12v. 80 different channels. £12.00 ref 12P26R

**CLAP LIGHT.** This device turns on a lamp at a finger 'snap' etc nicely cased with built in battery operated light. Ideal bedside light etc. £4.00 each ref 4P82R

**ELECTRONIC DIPSTICK KIT.** Contains all you need to build an electronic device to give a 10 level liquid indicator. £5.00 (ex case) ref 5P194R

**UNIVERSAL BATTERY CHARGER.** Takes AA's, C's, D's and PP3 nicads. Holds up to 5 batteries at once. New and cased, mains operated. £6.00 ref 6P36R

**ONE THOUSAND CABLE TIES!** 75mm x 2.4mm white nylon cable ties only £5.00 ref 5P181R

**PC MODEM** 1200/75 baud modems designed to plug into a PC complete with manual but no software. £18.00 ref 18P12R

**ASTEC SWITCHED MODE POWER SUPPLY** 80mm x 165mm (PCB size) gives +5 at 3.75A, +12 at 1.5A, -12 at 0.4A. Brand new £12.00 ref 12P39R

**VENTILATED CASE FOR ABOVE PSU** with IEC filtered socket and power switch. £5.00 ref 5P190R

**IN CAR POWER SUPPLY.** Plugs into cigar socket and gives 3.4, 5.6, 7.5, 9, and 12v outputs at 800mA. Complete with universal spider plug. £5.00 ref 5P167R

**CUSTOMER RETURNED** switched mode power supplies. Mixed type, good for spares or repair. £2.00 each ref 2P292R

**DRILL OPERATED PUMP.** Fits any drill and is self priming. £3.00 ref 3P140R

**POWERFUL SOLAR CELL 1AMP .45 VOLTS** b/nly £5.00 ref 5P192R (other sizes available in catalogue)

**SOLAR PROJECT KIT.** Consists of a solar cell, special DC motor, plastic fan and turntables etc plus a 20 page book on solar energy! Price is £8.00 ref 8P51R

**RESISTOR PACK.** 10 x 50 values (500 resistors) all 1/4 watt 2% metal film. £5.00 ref 5P170R

**CAPACITOR PACK** 1.100 assorted non electrolytic capacitors £2.00 ref 2P286R

**CAPACITOR PACK 2.** 40 assorted electrolytic capacitors £2.00 ref 2P287R

**QUICK CUPPA?** 12v immersion heater with lead and cigar lighter plug £3.00 ref 3P92R

**LED PACK** .50 red leds, 50 green leds and 50 yellow leds all 5mm £6.00 ref 8P52R

**FERRARI TESTAROSSA.** A true 2 channel radio controlled car with forward, reverse, 2 gears plus turbo. Working headlights £22.00 ref 22P26R

**ULTRASONIC WIRELESS ALARM SYSTEM** Two units, one a sensor which plugs into a 13A socket in the area you wish to protect. The other, a central alarm unit plugs into any other socket elsewhere in the building. When the sensor is triggered (by body movement etc) the alarm sounds. Adjustable sensitivity. Price per pair £20.00 ref 20P34R. Additional sensors (max 5 per alarm unit) £11.00 ref 11P6R

**WASHING MACHINE PUMP.** Mains operated new pump. Not self priming. £5.00 ref 5P18R

**IBM PRINTER LEAD.** (D25 to centronics plug) 2 metre parallel £5.00 ref 5P186R

**COPPER CLAD STRIP BOARD** 17" x 4" of 1" pitch "vero" board £4.00 a sheet ref 4P62R or 2 sheets for £7.00 ref 7P22R

**STRIP BOARD CUTTING TOOL** £2.00 ref 2P35Z

3 1/2" disc drive. 720K capacity made by NEC £60.00 ref 60P2R

**TV LOUDSPEAKERS.** 5 watt magnetically screened 4 ohm 55 x 125mm £3.00 a pair ref 3P109R

**SPEAKER GRILLS** set of 3 matching grills of different diameters

2 packs for £2.00 (6 grills) ref 2P364R

**50 METRES OF MAINS CABLE** £3.00 2 core black pre-cut in convenient 2 m lengths. Ideal for repairs and projects. ref 3P91R

**4 CORE SCREENED AUDIO CABLE** 24 METRES £2.00 Pre-cut into convenient 1.2 m lengths. Ref 2P365R

**TWEETERS** 2 1/4" DIA 8 ohm mounted on a smart metal plate for easy fixing £2.00 ref 2P366R

**COMPUTER MICE** Originally made for Future PC's but can be adapted for other machines. Swiss made £8.00 ref 8P57R. Atan ST conversion kit £2.00 ref 2P362R

**6 1/2" 20 WATT SPEAKER** Built in tweeter 4 ohm £5.00 ref 5P205R

**5" X 3" 16 OHM SPEAKER** 3 for £1.00! ref CD213R

**ADJUSTABLE SPEAKER BRACKETS** Ideal for mounting speakers on internal or external corners, uneven surfaces etc. 2 for £5.00 ref 5P207R

**PIR LIGHT SWITCH** Replaces a standard light switch in seconds

Light operates when anybody comes within detection range (4m) and stays on for an adjustable time (15 secs to 15 mins). Complete with daylight sensor. Unit also functions as a dimmer switch! 200 watt max. Not suitable for fluorescents. £14.00 ref 14P10R

**CUSTOMER RETURNED** 2 channel full function radio controlled cars only £8.00 ref 8P200R

**WINDUP SOLAR POWERED RADIO!** FM AM radio takes rechargeable batteries complete with hand charger and solar panel 14P200R

**240 WATT RMS AMP KIT** Stereo 30-30 psu required £40.00 ref 4P200R

**300 WATT RMS MONO AMP KIT** £55.00 Psu required ref 55P200

**ALARM PIR SENSORS** Standard 12v alarm type sensor will interface to most alarm panels. £16.00 ref 16P200


**ALARM PANELS** 2 zone cased keypad entry, entry exit time delay etc. £18.00 ref 18P200

**35MM CAMERAS** Customer returned units with built in flash and 28mm lens 2 for £8.00 ref 8P200

**STEAM ENGINE** Standard Mamod 1332 engine complete with boiler piston etc £30.00 ref 3P200

**TALKING CLOCK** What more can we say??

£14.00 ref 14P200.R

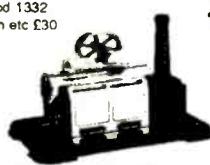

SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

CIRCLE NO. 115 ON REPLY CARD

# Design brief: voltage references

Ian Hickman looks at voltage reference circuit designs.

**V**oltage references have made great strides in the last quarter of a century, since solid state types replaced gas tubes. First on the scene was the zener diode, used with a simple series current-limiting resistor, Fig. 1a. Popular ranges were the BZY88-series (Mullard/Philips) and the American 1N821-827 series.

Slope (incremental) resistance and the temperature coefficient of a zener diode each affect both the stabilisation (change of output voltage with change of supply voltage) and the regulation (change of output voltage with output current drawn) of the circuit.

Operating mechanism is true zener breakdown for low voltage diodes and avalanche breakdown for higher voltage types. The former has a negative "tempco" and the latter a positive, accordingly at the changeover point – somewhere between 4.7 and 5.6V where both mechanisms occur – the tempco is near zero, varying with the device process used and also with operating current.

Thus it was tempting to use a nominal 5.1V diode where high stability was required, but unfortunately the lowest slope resistance is found in diodes of about 7.5V nominal; these were therefore often preferred where good regulation and particularly stabilisation were important. But, the quoted slope resistance of a zener is always measured adiabatically, by superimposing a small AC ripple component on the DC current and observing the ripple voltage.

The temperature of the diode does not vary in sympathy with the instantaneous current as the frequency of the AC is too high, so the tempco does not influence the result. Many an unwary circuit designer has chosen a zener with the lowest slope resistance only

to find the apparent stabilisation of a circuit much worse than expected: when the supply voltage is suddenly increased, the increased dissipation in the diode raises its temperature and the positive tempco then contributes a rise in output voltage above and beyond that due to the extra current flowing through the slope resistance.

In Fig. 1b and 1c the high slope resistance of a depletion mode fet greatly reduces any current variations through the diode due to change of supply voltage. But a fet is comparatively expensive, and anyway has an embarrassingly high variation, up to 5:1, in drain saturation current  $I_{dss}$ , controlled to some extent by the self-bias resistor in Fig. 1c.

The circuit of Fig. 1d seems to be comparatively little known but is very economical: any increase in current through the zener diode due to increased supply voltage would tend to increase the base emitter voltage across  $R_2$ , shunting most of any increase in current through  $R_1$  to ground via the collector circuit.

Straightforward zeners had a long run for their money, with many ingenious circuit variations to improve regulation and stabilisation.

One I developed many years ago, published in Wireless World under the title "Two for the Price of One", provided two stabilised supply rails using a single zener diode. However my favourite augmented zener circuit is shown in Fig. 2a. Here, the zener is incorporated in a bridge circuit which is driven by an op-amp whose input signal is the bridge output. The circuit is thus a little incestuous and usually needs a resistor (shown dotted) to ensure reliable start-up.

However its value can be as high as  $10\text{M}\Omega$ , so that although it feeds some current into the zener from the unregulated input voltage, its effect on stabilisation is negligible. The op-amp buffers the load current, result-

ing in excellent regulation, whilst the bridge is fed from a constant voltage, resulting in constant current through the zener and hence excellent stabilisation.

This circuit is available in IC form, for example the Burr-Brown REF10, which is shown in Fig. 2b and provides  $1\text{ppm}/^\circ\text{C}$  max tempco,  $10\text{ppm}/1000\text{h}$  stability,  $6\mu\text{V}$  p/p noise,  $0.001\%/\text{V}$  stabilisation and  $0.001\%/\text{mA}$  regulation.

These are two-terminal devices, needing an external current limiting resistor just like a zener diode. However the "knee current", that is, the current at which the slope resistance has fallen to a low value, is very low for these devices – less than  $100\mu\text{A}$ , making them ideal for battery-powered applications. They are also available in trimmable three-terminal styles and in SMD – surface mount – packages.

## Variations and applications

Voltage references are available in a wide range of output voltages such as 2.5V, 5.0V and 10.0V while others cater for binary-oriented instrumentation, with 2.56V, 10.24V outputs etc. Two-terminal types are subject to a selection tolerance but many three or more terminal devices offer the facility to adjust the output voltage exactly to the nominal. Where an output voltage is required which is not available as standard, the circuit of Fig. 2a is ideal; by choosing appropriate values for the bridge resistors, any desired output voltage can be obtained. Where several different voltages are required simultaneously, the highest can be produced with a Fig. 2a type circuit and the others obtained from it with a potential divider string of precision (or adjustable) resistors, the tappings being buffered with non-inverting op amps.

Very often however, only one voltage is required at a time, but it must be adjustable

Fig. 2. Two of the many augmented zener circuits developed.



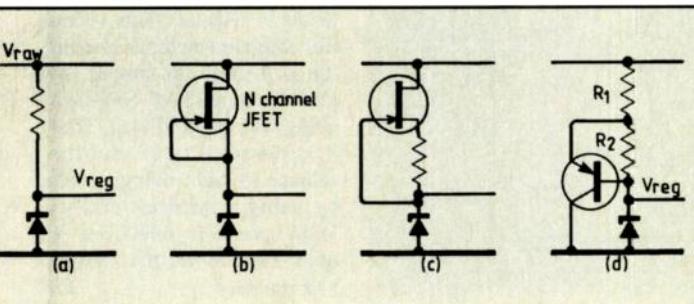
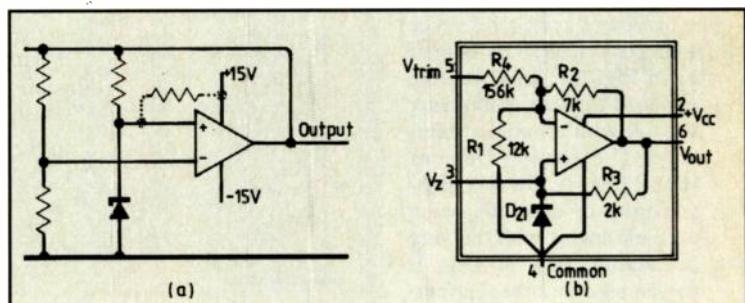
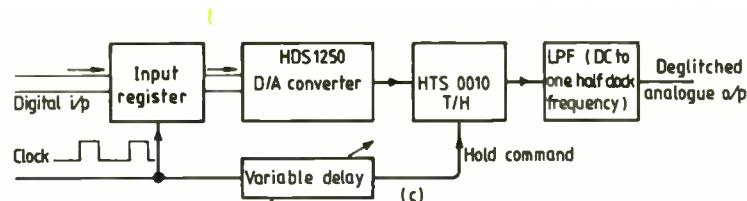


Fig. 1. Voltage references built around the zener diode (From Analog Electronics, Ian Hickman, 1990. By permission of Heinemann Newnes).

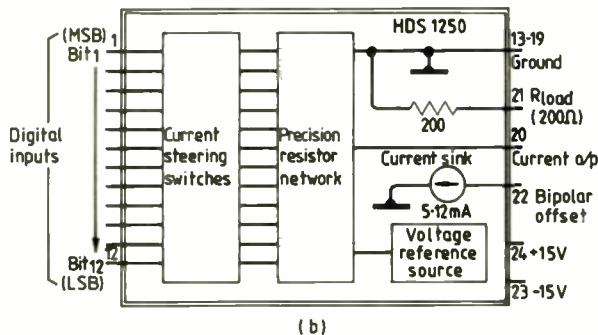

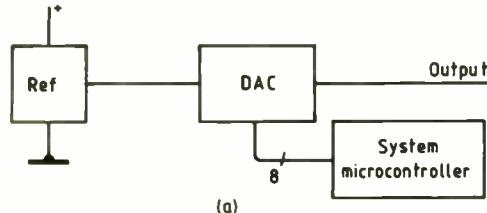

**Fig. 3.** A voltage reference and D-to-A converter can give a simple solution.

to any one of a number of possibilities. A typical application might be in ATE. In this case, the above schemes are less attractive and another arrangement must be sought.

#### Programmable sources

A simple solution, particularly attractive in ATE where a microcontroller is incorporated to organise the operation of the system, is to use a voltage reference and a multiplying D-to-A converter, as indicated in Fig. 3a. The D-to-A chosen will determine the resolution to which the voltage can be set. For instance, with an 8-bit D-to-A and a 10.24V reference such as National Semiconductor's LH0071-OH, the resolution will be 40mV, ie. 0.39% of full scale, which in many cases would be inadequate.



Using a 10-bit unit, such as Philips' MC3410F, would improve the resolution to 10mV or better than 0.1% FS, while a 12, 14 or 16-bit multiplying D-to-A would clearly provide much greater resolution. The accuracy of the output would also improve generally in line with the resolution, but the designer must decide just what is needed and can be afforded: many D-to-As are available in various selection grades offering an accuracy which may be as high as 1/4 of an LSB (least significant bit) in better devices, to as poor as one and a half LSBs in more economical sorts.

Instead of using a reference source and a separate D-to-A as in Fig. 3a, an attractive option is to use a multiplying D-to-A with a built-in reference. The Analog Devices HDS-1250 Fig. 3b is a high-performance example, being a 12-bit device with the very fast settling time of 35ns. It can be used in either current-

or voltage-output mode, in the former providing a full scale output of 10.24mA – or more strictly speaking 10.2375mA – with an all-ones input code. (10.24mA would correspond to an all naughts input code plus a one in the non-existent thirteenth bit).

Glitches commonly occur when the output of a D-to-A changes, and these can be pronounced if there is any skew between the various bits of the control word. In some circuit applications, this can be most embarrassing. One way to reduce these is to include input buffer registers in the D-to-A, as in the AD7224 CMOS monolithic 8-bit double buffered voltage output unit from Maxim. In addition to de-skewing the input data word, double buffering permits simultaneous updating in systems where several D-

**Fig. 4.** Circuit providing one of four different outputs of 1.26V or more.

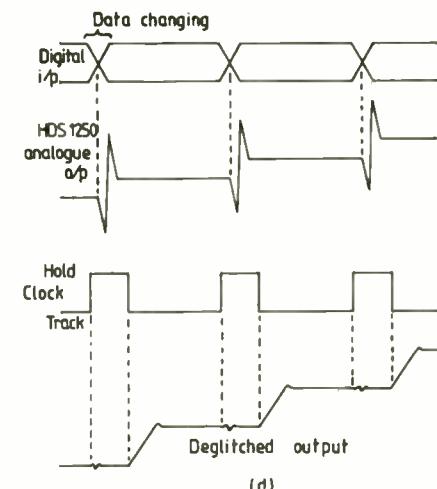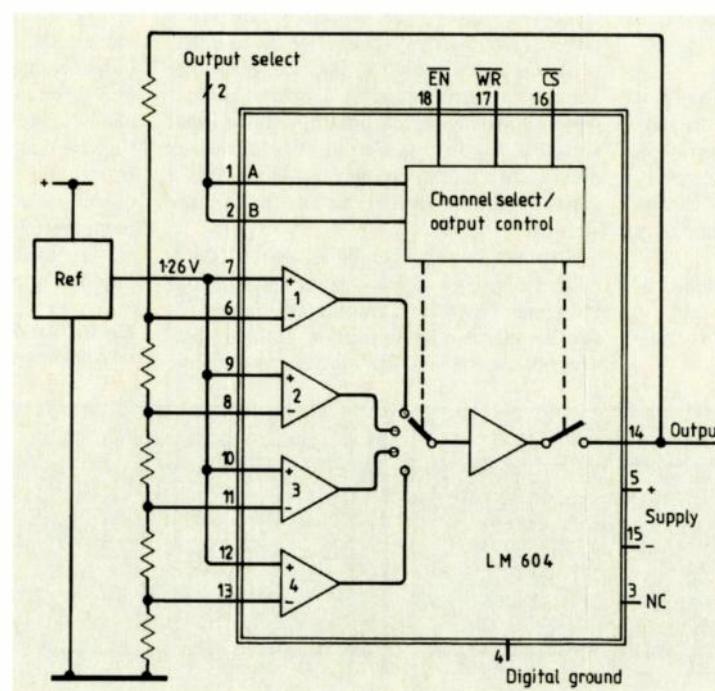


to-A channels are successively written to by a single controller. Figure 3c shows alternatively how a T/H (track-and-hold circuit) can be used in conjunction with an unbuffered device such as the HDS-1250 mentioned earlier. The minor residual switching transients introduced by the action of the T/H are very fast and contain little energy. Fig. 3d: they are easily eliminated by a little light lowpass filtering.

In electronics there are usually many ways of achieving the desired result; and that is true here, especially where only a few output levels are required.

In this case an economical solution is to use a voltage reference plus a mux-amp. The latter is an op-amp with two or more input stages, only one of which is activated at a time. The gain is thus determined by the feedback components associated with the selected stage.

A good example is the National Semiconductors LM604, with four input stages, and a typical application is shown in Fig. 4, where two data bits determine, under control of the CHIP SELECT BAR and WRITE BAR pins, which of the four output levels is selected. This versatile chip also includes a facility to disable the output, so that the outputs of two such chips may be paralleled. Thus it is possible to extend the scheme to eight output levels by using a third bit and its logic inverse to select one or other LM604 via the ENABLE BAR inputs.
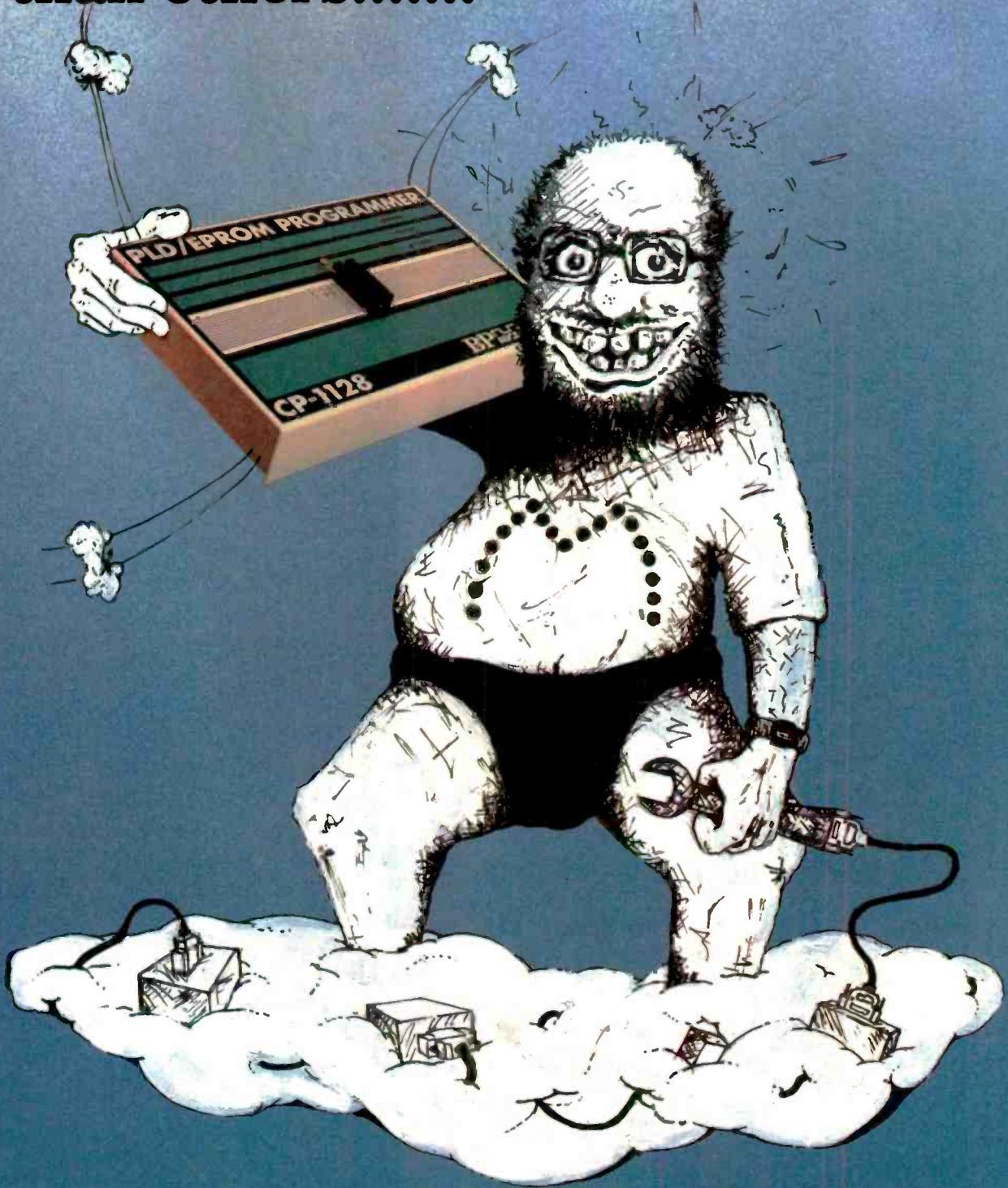
# Some programmers are more powerful than others.....



**The CP1128 is qualified by all major device manufacturers – like AMD, Lattice, Samsung and TI.**  
This means that you can feel secure that you'll be programming exactly as the manufacturer specifies and you won't get field failures from poorly programmed devices.

**It programs over 2000 different devices – – GALs, PALs, EPROMs, ERASICs, EPLDs .....**

Nothing's worse than finding that your shiny new programmer won't work with the device you need. We've added more than 600 devices during the last 4 months and we're working hard to keep up with the manufacturers.


**We offer an absolutely free, lifetime, software update service.**

When you use a BP programmer you get on demand support for new devices as we produce the software. The new software costs you nothing and we'll continue to support you as long as you own the programmer.

**Last, but not least, the CP1128 costs less than £1000.**

It costs £985 and has a years guarantee. Like we've always said - power, reliability and value for money.

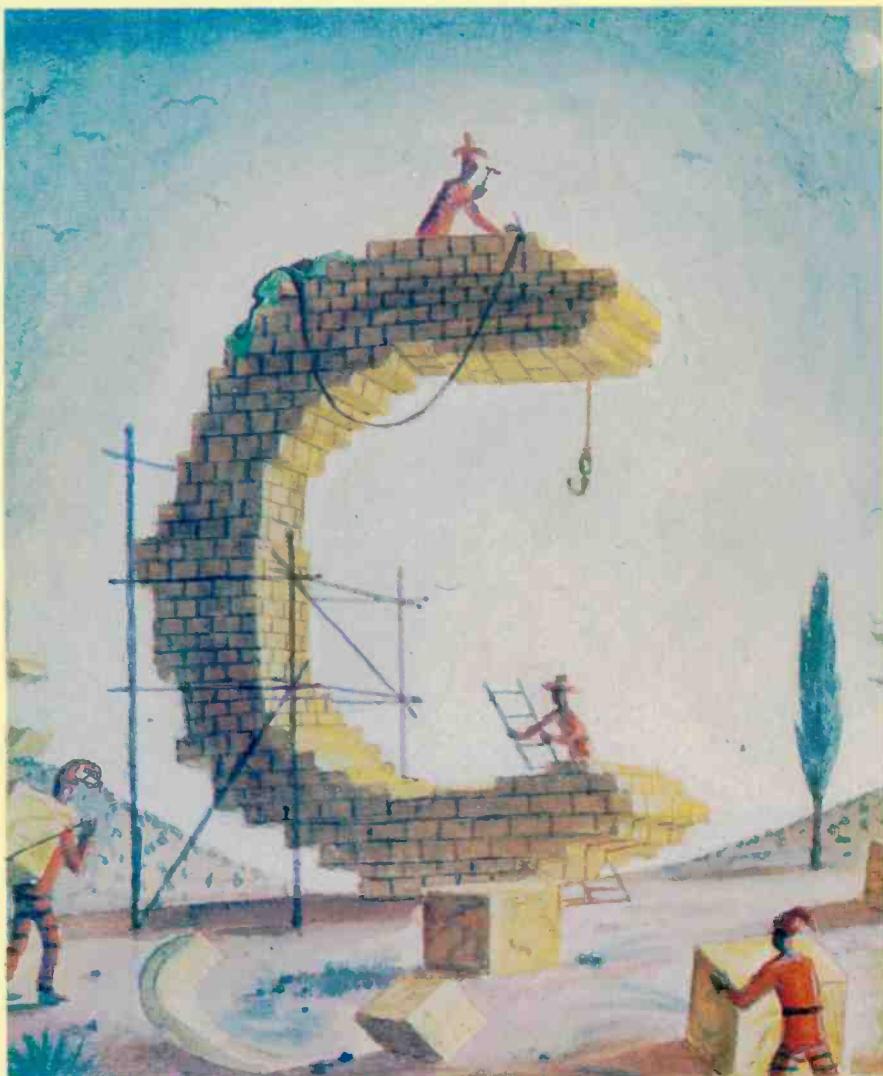**MUTEK (MSS) Ltd. Frome Road, Bradford on Avon, Wilts. BA15 1LE 02216 6501/6502 or fax -5083**



# INTERFACING WITH C

by

HOWARD HUTCHINGS

Interfacing with C can be obtained from Lindsey Gardner, Room L333, Quadrant House, The Quadrant, Sutton, Surrey SM5 2AS.

Please make cheques for £14.95 (which includes postage and packing) payable to Reed Business Publishing Group.

Alternatively, you can telephone your order, quoting a credit card number. Telephone 081-661 3614 (mornings only, please).

A disk containing all the example listings used in the book is available at £25.50 + VAT. Please specify size required.

## C HERE!

If you have followed our series on the use of the C programming language, then you will recognise its value to the practising engineer.

But, rather than turning up old issues of the journal to check your design for a digital filter, why not have all the articles collected together in one book, *Interfacing with C*?

The book is a storehouse of information that will be of lasting value to anyone involved in the design of filters, A-to-D conversion, convolution, Fourier and many other applications, with not a soldering iron in sight.

To complement the published series, Howard Hutchings has written additional chapters on D-to-A and A-to-D conversion, waveform synthesis and audio special effects, including echo and reverberation. An appendix provides a "getting started" introduction to the running of the many programs scattered throughout the book.

This is a practical guide to real-time programming, the programs provided having been tested and proved. It is a distillation of the teaching of computer-assisted engineering at Humberside Polytechnic, at which Dr Hutchings is a senior lecturer.

Source code listings for the programs described in the book are available on disk.

**Many Radio Amateurs and SWLS are puzzled. Just what are all those strange signals you can hear but not identify on the I.f. and h.f. frequencies? A few of them, such as c.w., RTTY, and Packet you'll know – but what about the many other signals?**

Hoka Electronics have the answer! There are some well known CW/RTTY decoders with limited facilities and high prices, complete with expensive PROMS for upgrading, etc., but then there is **Code 3** from Hoka Electronic!

It's up to you to make your choice – but it will be easy once you know more about **Code 3**.

**Code 3** works on any IBM-compatible computer with MS-DOS having at least 640kB of RAM.

**Code 3** hardware includes a complete digital FSK Converter with built-in 230V ac power supply and RS232 cable, ready to use. You'll also get the best software ever made to decode all kinds of data transmissions. **Code 3** is the most sophisticated decoder available, and the best news of all is that it STILL only costs £249 plus VAT!

The following modes are included in the basic-program (with the exact protocols).

**Packet Radio AX 25.** Any speed up to 480 baud

**Hell.** Synchronous/asynchronous, all speeds

**Fax.** Weather charts, photographs with 16 grey

scales at 60, 90, 120, 180, 240 rpm

**Morse.** Automatic and Manual speed with wpm

indication

**Press OPA.** F7b spec., 300 Bd ASCII

**Wirtschaftsdienst.** F7b spec., 300 Bd ASCII

**Sport Information.** F7b spec., 300 Bd ASCII

**Autospec.** MK's I and II with all known

interleaves

**DUP ARQ.** Artag ITA2

**TWINPLEX F7b1 ... F7b6 Simplex ARQ**

**ASCII ITA 5** all speeds, parity

**Baudot.** ITA 2 plus all types of Bit inversion, at any speed

**SITOR Automatic Mode A and B (ARQ and FEC)**

**ARQ:** CCIR 476, CCIR 625 mode A

**ARQ-6.** -90/98 spec. ARQ variant

**ARQ-S** ARQ 1000S

**ARQ-Swe.** CCIR 518 variant

**ARQ-E.** ARQ 1000, ITA 2-p Duplex

**ARQ-N.** ITA 2 Duplex

**ARQ-E3.** CCIR 519 ITA 3

**POL-ARQ.** spec. ARQ-variant

**TDM 242.** CCIR 242 1/2/4 channels

**TDM 342.** CCIR 342 1/2/4 channels

**FEC-A FEC 100(A).** ITA 2-P FEC Broadcast

**FEC CCIR 625 476-4 mode B** Sitor both

collective and selective FEC.

**FEC-S FEC 1000S ITA 3**

All modes in preset and variable user-defined baud rates and shifts.

**Six options** are available to use with the **Code 3** and consist of:

**1: OSCILLOSCOPE,** this facility displays the measured frequency versus time, including split-screen, storage and non-storage modes at £25.

**2: PICCOLO MK VI** (Everybody wants this facility, but it's only on offer from Hoka), the well-known multitone-mode at £60.

**3: ASCII 'SAVE TO DISC'** Store all decoded text to Disc as ASCII. £25.

**4: COQUELET** (Another multi/tone system. Only on offer from HOKA!). £60.

**5: SPECIAL ARQ/FEC.** Various other new ARQ/FEC systems. £80.

**6: AUTO-CLASSIFICATION** Stop wasting time on uncrackable systems! Let option 6 classify the system for you. Average answer in 10 seconds! £35.

Plus many other special codes. Send for details, price on application.

Along with the many facilities listed above, the analysis section of the **Code 3** offers you a wide choice of unique facilities such as: a built-in AF frequency spectrum-analyser for shift measurement and tuning, plus precision speed measurement up to 0.0001 Baud resolution. Other analysis facilities include Speed Bit analysis, Speed Measurement, Character Analysis, Auto-correlation of MOD and RAW signal, Bit Analysis. All these state-of-the-art features are included in **Code 3** to assist the experienced user.

All options are available from the main menu, saving or loading to or from hard or floppy disk in RAW Bit form (no loss of unknown signals), hard copy with printer, on-screen tuning indicator and very easy to use online Help-files.

To order, phone us for more details or send cheque, payable to:

**HOKA Electronics**  
Feiko Clockstr. 31  
NL-9665 BB Oude Pekela  
The Netherlands  
Tel: 010-31-5978-12327  
Fax: 010-31-5978-12645

**HOKA Electronics (UK)**  
84 Church Street  
Langford, Biggleswade,  
SG18 9QA, Beds  
Tel: 0462-700644  
Fax: 0462 700893

Please specify disk size 3½ or 5¼" when ordering!  
All prices ex. VAT and shipping; price includes a free 6-month software update and life-time tech. support.

CIRCLE NO. 116 ON REPLY CARD

October 1991 ELECTRONICS WORLD+WIRELESS WORLD

1991-1992

# HENRY'S

## ALL NEW COLOUR CATALOGUE

PLUS Test Instruments,  
Security, and Component  
Supplement

WITH  
**£90.00**  
WORTH OF PURCHASE VOUCHERS  
FREE and £2.00 OFF first purchase

To obtain  
Henry's new catalogue  
send envelope, minimum size C4 (12¾" x 9"),  
self addressed with £2.65 stamps affixed OR  
send £4 ch/po with request for catalogue,  
(Export £6) to the address below.

Also available for callers.

Trade/Industry/Education.  
Attach notepaper request for FREE  
catalogue with trade price lists.

**HENRY'S** OPEN 6 DAYS  
A WEEK

404 EDGWARE ROAD, LONDON, W2 1ED

Sales: 071-258 1831 Fax: 071-724 0322

**Audio and Electronics Specialists**

CIRCLE NO. 117 ON REPLY CARD

# ALL VALVES AND TRANSISTORS

We are one of the largest stockists  
of valves etc in the U.K.

**CALL OR PHONE**

for a most courteous quotation.

**081 743 0899**

**COLOMOR ELECTRONICS LTD**

170, Goldhawk Road, London, W12 8HJ

**FAX 081-749 3934**

CIRCLE NO. 118 ON REPLY CARD

# NO IFs— NO BUTS



***Does the classic IF routine unnecessarily complicate program and encourage bugs? Yes, but there is a solution, writes Frank Pettit.***

That every non-trivial programme contains at least one bug is an accepted part of computing. But from my own experience as programming skills improve, the count of IFs per programme decreases while program success increases.

The result of this observation has been analysis of domain partitioning (see box), a phenomenon that takes place whenever an IF is encountered in a programme, resulting in partitioning of a data domain and its corresponding function.

#### Logical origin of IFs

High-level programming languages were derived from formal logic, which includes the propositions p and q: "if p then q", closely associated with the implication: p implies q, and also with the Boolean: p Or Not q. But why was the fuzzy if... form ever introduced into programming?

IFs can result in non-analytic programs which cannot be "proved" and are fairly certain to contain complex domain partitioning conditions possibly leading to those unwanted behavioural characteristics known as bugs.

In the programming world an inordinate amount of time is wasted on debugging programmes – even high flying professionals cannot escape from the problem. In addition, valuable time has to be devoted to teaching principles of debugging. In any software production kit, whether assembler, C, or dos, a major component of the kit is the debug software.

Having traced a bug we normally cheer, denote the conditions which exist "when the bug appears" and set about constructing a

trap, by slipping in either an IF with a clutch of ANDs, or a few IFs with some ORs and NOTs. Unfortunately we often fail to consider how the IFs will affect domain partitioning.

An important question is when does an IF cease? At the end of a repeat? At the end of a block or procedure or function - do IFs affect behaviour throughout programme execution? The main consideration is, at a given point in programme execution time, how many IFs actually remain effective (Fig. 4.)?

In my view, the answer governs the true complexity of the programme and hence its reliability. I believe determining dynamic data complexity is more appropriate than the popular view that complexity is determined by number of variables in a program.

### Making matters worse

As a result of slipping in the standard "IF-else" for a bug, further domain-partitioning complexity is introduced into the program,

## Data and control domains partitioned by IF

Consider a simple domain with a few ordered items:  $\alpha, \beta, \gamma, \delta, \epsilon$ .

Given a data item ' $\chi$ ' which has a proper place in this domain, we can determine such conditions as:

if  $\chi$  precedes  $\delta$ .


The result of this test or query is that the original domain is partitioned into two sub-domains, one contains the precedents of ' $\delta$ ', the other contains ' $\delta$ ' and its successors. The variable ' $\chi$ ' belongs in one of the two sub-domains.

### Domain of integers

This domain is two-dimensional, by name and value. Thus we could query:

"Which is the first named item to have less than a given value?" In conventional programming languages we would be tempted to use IF again as in:
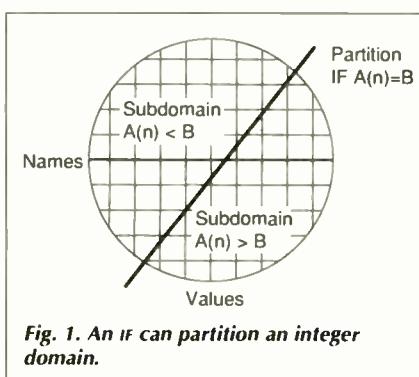
```
for n := 1 to k do if l[n] < j then....
```



which results in a line which traverses the finite domain and again, partitions it (Fig. 1).

This time, our partition can actually pass through some of the cells of our domain. Thus the partition has some cells either side, giving two sub-domains, while other cells are

possibly creating even more bugs. In other words, we can introduce non-analytic temporal IF-persistence and extreme partitioning complexity. This IF-cure normally introduces a kind of superbug which is usually untraceable and very often catastrophic.

Yet since founding of the Computer Teaching Centre at Oxford, debugging has never been taught and system programmers are not allowed near the system. Debug kits can only slow the tracing of "obvious" faults and fail when tracing "difficult" faults.

Key to successful programs is good design not skilful application of complex debugging kits. The best way is to avoid the awful traps into which IF...ENDIF, IF...GOTO, and IF-THEN-ELSE programming and there are many ways which this can be done.

### Transformations of IFs

AND: OR and IF: AND transformation


The famous DeMorgan theorems of Not (a

or b) = Not a And Not b, and Not (a and b) = Not a Or Not b allow us to transform between And and Or operators, transforming between conjunctive and disjunctive forms.

But beware the story of a research-student whose program contained almost a page of IFs to obtain a value from a multi-condition field.

The program was successful but slow. After being treated to a personal seminar on better problem analysis and programming techniques and a rethink, the student returned with a revised offering and a triumphant claim of "its much better now - only one IF".


But that IF took the form: IF...AND... AND... AND... AND - almost a page of continued ANDs. Oh the sadness when the realisation dawned that the problem had not been transformed, simply the many IFs had been transformed into ANDs.

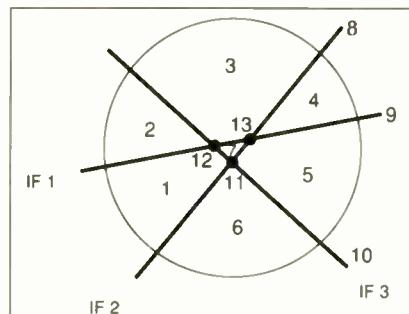


**Fig. 2. The subdomains due to three intersecting IFs.**

However, we are aware that the "proper" way to do computer arithmetic is to use mathematical libraries produced by specialists in numerical analysis. The Nag library is a fine example.

Even so, we must give valid data to the library routines and make provision for the error conditions which are bound to occur in practise and which are directly indicated by the library routines. We usually cater for this by slipping in a few more IFs, just to make sure.

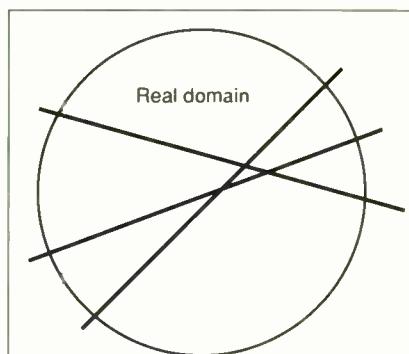

**Fig. 3. IFs produce real domain partitioning.**

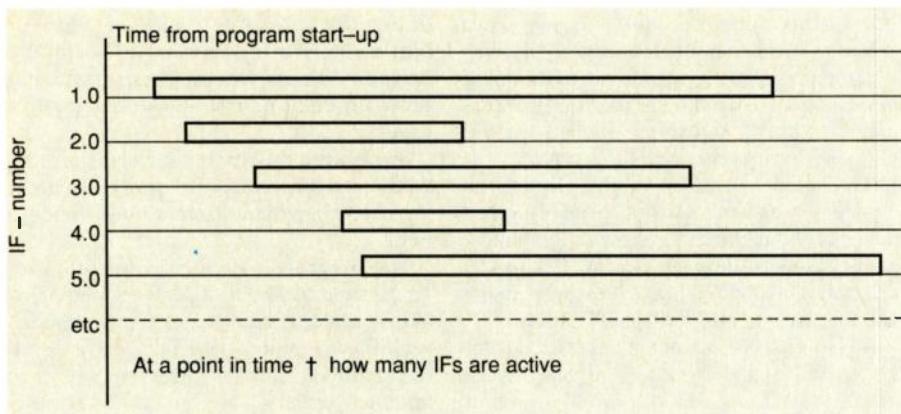

**Fig. 4. Temporal persistence of program IFs.**

The program remained successful but slow. A further briefing, a data-control transform plus a case-structured selector was substituted – program successful, fast – and no IFs.

In a recent instance, a program suffering multiple failure modes was dissected, to isolate almost all IFs. The data structures and each of the algorithms were removed and stored in disc-files. They were then re-loaded into a standard program framework and all failure modes had vanished. No debugging, no re-programming!

#### IF :function transformation

Take the simple problem of "Into C place the higher of the values from A and B".

An old-style Fortran-IV solution would be:

```
C = A
IF(B .GT. A) C = B
```

A modern alternative is:

```
IF A>B THEN C := A ELSE C := B
```

but the IF can be expunged by the use of a function. A function solution in Fortran (and others) is:

```
C = Max(A,B).
```

In this revised approach to programming, many IF-structures can, with considerable advantage, be replaced by functions. The efficacy of the IF... is in the domain of programmer - the function is a trusted routine with efficacy bounded only by the published data domain of the Function.

#### IF: boolean transformation

As a more interesting example, let us search for a peak and a trough in a varying data stream. The program segment

```
FOR n = 2 TO k-1
IF (a[n] > a[n-1]) AND (a[n+1] < a[n])
THEN peak = n
IF (a[n] < a[n-1]) AND (a[n+1] > a[n])
THEN
trough = n
NEXT n
```

might, with any luck, provide the positions of a peak and a trough. The simple algorithm can be modified to collect a sequence

of peak and trough positions in integer arrays.

But there must be further tests to handle a sequence of repeated data values, disturbed by "noise". This normal signal condition can result in a galaxy of erroneous peaks and troughs. To correct for these circumstances, we would scatter IFs allover the place and produce a slow, delicate and un-debuggable algorithm.

Detection of a peak is when (not if but when!) data values stop rising and commence to fall.

A trough is indicated when values stop falling and commence to rise. These are two-state conditions which can be set as Boolean expressions.

To cater for noise, we use a smoothed version of the data and instead of comparing adjacent items, we compare items two or three positions apart. This removes most of the IFs. Then we set Boolean variables in place of the IFs and have an algorithm which will operate reliably under highly variable data streams:

```
rising := this > previous;
falling := this < previous;
peak := rising AND next < this;
trough := falling AND next > this;
```

This can be taken further to include automatic detection and replacement of outliers (rogue values) in data sets of widely differing characteristics.

These ideas were first introduced for analysis of on-line lunar radar data during the Apollo moonflights in the late 1960s. The same logical algorithm has been applied with confidence to many bio-medical and engineering problems.

#### IF : arithmetic transformation

A common problem is to partition a range of values to provide upper and lower acceptance limits as in:

```
IF x < lower THEN out-of-range
IF x > higher THEN out-of-range
IF (x > lower) AND (x < higher) THEN in-range
IF (x = lower) OR (x = higher) THEN limit of range
```

We could set this directly into almost any programming language, and be fairly confident that such errors as do occur will probably be non-serious. But we could encounter oddities such as two differing conditions being satisfied simultaneously when using those wretched real numbers.

But normal arithmetic can be cajoled into producing unique results:

```
required test lower < x < higher
indicator k := sign(lower - x)*(x - higher)
```

This indicator will take the value of -1 when out-of-range; 0 when limit-of-range, and +1 when in-range giving a fast, unique selection with not an IF in sight.

#### Reliability and IF

The case for avoiding IF is further strengthened by hardware considerations. With many pipelined computers, to encounter an IF means unloading the pipeline and reloading it with the new work before processing can recommence. This can consume enough time to destroy the advantages of pipelining.

Some array processors need to have programs with no array bounds checks and certainly no IFs checking the array boundaries in the parallel maths unit. A few supercomputers rely for their speed on Fortran-derived code with no IFs and some signal processor computers have no provision for IF in their instruction codes.

#### Are there any jobs left for IF?

What uses are left for IFs? Maybe to escape from a loop? But this too can be a source of mystical failure. Many loops are compiled into machine-code subroutines, making use of stacks.

To exit a subroutine under strange conditions can store up stack problems which only strike after multiple re-use causes failure of run-time stack management.

Safe loop exit depends on the language, software and conditions of use. (To avoid loss of much software-theorists hair, keep this hint secret...escape from a BASIC FOR-loop by setting the control variable to its final value, an n = k, rather than by an IF...GOTO...). Using WHILE has its own horror stories.

By deduction from the preceding facts and ideas, I believe we can propose that only programs without IFs can be bug-free. Computer programs are presented in the imperative style - so why were sloppy implicative/hypothetical forms ever introduced into programming languages?

The temporal connotation of ACTIONS by a program suggests use of the decision "WHEN condition..." which would have retained the imperative style and avoided the hypothetical form.

This would have given program designers a different attitude of mind. The concept of: "I wonder what would happen if....?" and "let's see if this will fix it...!", would no longer encourage today's shoddy work. ■

Surplus always wanted for cash!

# THE ORIGINAL SURPLUS WONDERLAND!

Surplus always wanted for cash!

## BBC Model B APM Board

WIN £100 CASH!

£100 CASH FOR THE MOST NOVEL DEMONSTRATABLE APPLICATION!

BBC Model B type computer on a board. A major purchase allows us to offer you the PROFESSIONAL version of the BBC computer at a parts only price. Used as a front end graphics system on large networked systems the architecture of the BBC board has so many similarities to the regular BBC model B that we are sure that with a bit of experimentation and ingenuity many useful applications will be found for this board! It is supplied complete with a connector panel which brings all the I/O to 'D' and BNC type connectors - all you have to do is provide +5 and ±12 v DC. The APM consists of a single PCB with most major IC's socketed. The IC's are too numerous to list but include a 6502, RAM and an SAA5050 teletext chip. Three 27128 EPROMS contain the custom operating system on which we have no data. On application of DC power the system boots and provides diagnostic information on the video output. On board DIP switches and jumpers select the ECONET address and enable the four extra EPROM sockets for user software. Appx. dims: main board 13" x 10". I/O board 14" x 3". Supplied tested with circuit diagram, data and competition entry form.

Only £29.95 or 2 for £53 (B)

## MONITORS

### MONOCHROME MONITORS

#### THIS MONTH'S SPECIAL!

There has never been a deal like this one! Brand spanking new & boxed monitors from NEC, normally selling at about £140! These are over-engineered for ultra-reliability. 9" green screen composite input with etched non-glare screen plus switchable high/low impedance input and output for daisy-chaining. 3 front controls and 6 at rear. Standard BNC sockets. Beautiful high contrast screen and attractive case with carrying ledge. Perfect as a main or backup monitor and for quantity users! £39.95 each (D) or 5 for £185 (G)

CALL FOR DISCOUNTS ON HIGHER QUANTITIES!

### COLOUR MONITORS

Decca 16" 80 budget range colour monitor. Features a P11 tube, beautiful teak style case and guaranteed 80 column resolution, features usually seen only on colour monitors costing 3 times our price! Ready to connect to most computers or video outputs. 750 composite input with integral audio amp & speaker. Fully tested surplus, sold in little or hardly used condition with 90 day full RTB guarantee. Ideal for use with video recorder or our Telebox ST, and other audio visual uses. £99(E) 3/£275(G)

### 20", 22" and 26" AV SPECIALS

Superbly made UK manufacture. P11 all solid state colour monitors, complete with composite video & sound inputs. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

CALL FOR PRICING ON NTSC VERSIONS!

### HI-DEFINITION COLOUR MONITORS

Brand new 12" multi input high definition colour monitors by Microvitek. Nice tight 0.31" dot pitch for superb clarity and modern metal black box styling. Operates from any 15.625 khz sync RGB video source, with either individual H & V syncs such as CGA IBM PC's or RGB analog with composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 14" x 12" square. Free data sheet including connection information. Will also function as quality TV with our RGB Telebox.

Only £145 (E)

Brand new Centronic 14" monitor for IBM PC and compatibles at a lower than ever price! Completely CGA equivalent. Hi-res Mitsubishi 0.42 dot pitch giving 669 x 507 pixels. Big 28 Mhz bandwidth. A super monitor in attractive style moulded case. Full 90 day guarantee.

Only £129 (E)

NEC CGA IBM-PC compatible. High quality ex equipment fully tested with a 90 day guarantee. In an attractive two tone ribbed grey plastic case measuring 15" x 13" x 12". A terrific purchase enables us to pass these on at only.... £79 (E)

### V22 1200 BAUD MODEMS

Master Systems 2/12 microprocessor controlled V22 full duplex 1200 baud modem. Fully BT approved unit, provides standard V22 high speed data comm, which at 120 cps, can save your phone bill and connect time by a staggering 75%! Ultra slim 45mm high. Full featured with LED status indicators and remote error diagnostics. Sync or Async use; speech or data switching, built in 240v mains supply and 2 wire connection to BT. Units are in used but good condition. Fully tested prior despatch, data and a full 90 day guarantee. What more can you ask for - and at this price!

ONLY £69 (D)

LARGE QUANTITIES OF OSCILLOSCOPES AND TEST GEAR ALWAYS AVAILABLE - CALL NOW!

**DISPLAY**  
- ELECTRONICS -

MAIL ORDER & OFFICES  
Open Mon-Fri 9.00-5.30  
Dept WW, 32 Biggins Way,  
Upper Norwood,  
London SE19 3XF.

All prices for UK Mainland, UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. PO-orders from Government, Universities, Schools & Local Authorities welcome minimum account order £25. Carriage charges (A)=£2.00, (B)=£5.00, (C)=£8.50, (D)=£11.50, (E)=£14.00, (F)=£18.00 (G)=Call. All goods supplied subject to our standard Conditions of Sale and unless otherwise stated guaranteed for 90 days. All guarantees on a return to base basis. We reserve the right to change prices & specifications without prior notice. Orders accepted subject to stock. Quotations willingly given for higher quantities than those stated. Bulk surplus always required for cash.

## IBM KEYBOARD DEALS

A replacement or backup keyboard, switchable for IBM PC, PC-XT or PC-AT. LEDs for Caps, Scroll & Num Locks. Standard 84 keyboard layout. Made by NCR for the English & US markets. Absolutely standard. Brand new & boxed with manual and key template for user slogans on the function keys. Attractive beige, grey and cream finish, with the usual retractable legs underneath. A generous length of curly cord, terminating in the standard 5 pin DIN plug. A beautiful clean piece of manufacturers surplus. What a deal!

£39 (B) 5/£175 (D)

Brand new and boxed 84 key PC/XT type keyboards in standard IBM grey with very attractive mottled finish and "clicky" solid feel keys. 10 function keys on side. English layout and £ sign. Green LEDs for Caps, Scroll & Num locks. £29.95 (B) 5/£135 (D)

CALL FOR DISCOUNTS ON HIGHER QUANTITIES!


## FLOPPY DISK DRIVES BARGAINS GALORE!

NEW 5 1/4 Inch from £29.95!

Massive purchases of standard 5 1/4" drives enables us to present prime product at industry beating low prices! All units (unless stated) are removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from +5 & +12vdc, are of standard size and accept the standard 34 way connector.

TANDON TM100-2A IBM compatible DS £39.95 (C)  
CANON, TEC etc. DS half height. State 40 or 80T £79.00 (C)  
TEAC FD-55-F.40-80 DS half height. BRAND NEW £79.00 (C)

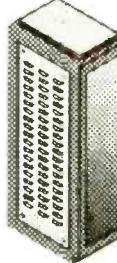punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels or stand singly. Overall dimensions are 77-1/2" H x 32-1/2" D x 22" W. Order as:



Surb Quality 6 foot 40u

## 19" Rack Cabinets

Massive Reductions

Virtually New, Ultra Smart!

Less Than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvred back door and removable side panels. Fully adjustable internal fixing struts, ready

for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels or stand singly. Overall dimensions are 77-1/2" H x 32-1/2" D x 22" W. Order as:

Rack 1 Complete with removable side panels.....£275.00 (G)

Rack 2 Less side panels.....£145.00 (G)

## POWER SUPPLIES

Power One SPL200-5200P 200 watt (250 w peak). Semi open frame giving +5v 35a, -5v 1.5a, +12v 4a (8a peak), -12v 1.5a, +24v 4a (6a peak). All outputs fully regulated with over voltage protection on the +5v output. AC Input selectable for 110/240 vac. Dims 13" x 5" x 2.5". Fully guaranteed RFE. £85.00 (B)

Power One SPL130. 130 watts. Selectable for 12v (4A) or 24v (2A). 5v @ 20A, 12v @ 1.5A. Switch mode. New. £58.95 (B)

Astec AC-8151 40 watts. Switch mode. +5v @ 2.5a, +12v @ 2a, -12v @ 0.1a, 6-1/4" x 4" x 1-3/4". New. £19.95 (B)

Greendale 19AB060 60 watts switch mode, +5v @ 6a, ±12v @ 1a, +15v @ 1a. RFE and fully tested. 11 x 20 x 5.5cm. £24.95 (C)

Conver AC130. 130 watt hi-grade VDE spec. Switch mode, +5v @ 1.5a, -5v @ 1a, ±12v @ 6a. 27 x 12.5 x 6.5cm. New. £49.95 (C)

Boshert 13090. Switch mode. Ideal for drives & system. +5v @ 6a, +12v @ 2.5a, -12v @ 0.5a, -5v @ 0.5a. £29.95 (B)

Farnell G6/40A. Switch mode. 5v @ 40a. Encased. £95.00 (C)

## COOLING FANS

Please specify 110 or 240 volts for AC fans.

3 inch AC 11/2" thick £ 8.50 (B)

3 1/2 inch AC ETI slimline. Only 1" thick. £ 9.95 (B)

3 1/2 inch AC 230 v 8 watts. Only 3/4" thick £12.95 (A)

4 inch AC 110/240v 11/2" thick. £10.95 (B)

10 inch AC round, 3 1/2 thick. Rotron 110v £10.95 (B)

10 inch As above but 230 volts £24.95 (B)

60 mm DC 1" thick. No.812 for 6/12v 814 24v. £15.95 (A)

80 mm DC 5 v. Papst 8105G 4w. 38mm. RFE. £19.95 (A)

92 mm DC 12v. 18 mm thick. £14.95 (A)

4 inch DC 12v. 12w 11/2" thick £12.50 (B)

DC 24v 8w. 1" thick. £14.50 (B)

## THE AMAZING TELEBOX!

Converts your colour monitor into a

## QUALITY COLOUR TV!!

TV SOUND & VIDEO TUNER!

Brand new high quality, fully cased, 7 channel UHF PAL TV tuner system. Unit simply connects to your TV aerial socket and colour video monitor turning same into a fabulous colour TV. Don't worry if your monitor doesn't have sound, the TELEBOX even has an integral audio amp for driving a speaker plus an auxiliary output for headphones or HI FI system etc. Many other features: LED Status Indicator, Smart moulded case, Mains powered, Built to BS safety specs. Many other uses for TV sound or video etc. Supplied BRAND NEW with full 1 year guarantee.

Telebox ST for composite video input monitors. £32.95 (B)

Telebox STL as ST but with integral speaker. £36.50 (B)

Telebox RGB for analogue RGB monitors. £68.95 (B)

RGB Telebox also suitable for IBM multisync monitors with RGB analog and composite sync. Overseas versions VHF & UHF call.

SECAM / NTSC not available.

## BRAND NEW PRINTERS

TEC Starwriter Model FP1500-25 daisywheel printer renowned for its reliability. Diablo type print mechanism gives superb registration and quality. On board microprocessor gives full Diablo/Qume command capability. Serial RS-232C with full handshake. Bidirectional 25 cps, switchable 10 or 12 pitch, 136 cpi in Pica, 163 in Elite. Friction or tractor feed. Full ASCII including £ sign. Font and ribbon Diablo compatible. £199 (E)

DED D-3/G21 miniature ball point pen printer plotter mechanism with full 40 characters per line. Complete with data sheet which includes circuit diagrams for simple driver electronics. £49 (B)

Centronics 150 series. Always known for their reliability in continuous use - real workhorses in any environment. Fast 150 cps with 4 fonts and choice of interfaces at a fantastic price!

159-4 Serial up to 9.5" paper, fan fold tractor. £99.00 (E)

150-4 Serial up to 9.5" paper, tractor, roll or s/sheet. £129.00 (E)

152-2 parallel up to 14.5" paper, tractor or s/sheet. £149.00 (E)

CALL FOR THE MANY OTHERS IN STOCK.

## VISIT OUR SHOP FOR BARGAINS

DISTEL © The Original  
Free dial-up database!  
100's of items+info On Line  
V21, V22 & V22 bis  
081-679-1888

ALL ENQUIRIES

081-679-4414

Fax- 081-679-1927

Telex- 894502



# REGULARS

## LETTERS

### Second wave

The approach to unravelling Maxwell's waves adopted by Marti Nissinen (*EW + WW* August 1991) can be further extended by using the principle of projective geometry. This is to say that all the essential features of a "pure" sinusoidal EM wave in three dimensions (ie wavelength, amplitude and phase) will remain dimensionally unaltered by orthogonal projection into the Euclidean plane under such a condition. For example, the amplitude of a pure sinusoidal EM wave of constant frequency may be regarded geometrically to be a spiral on the external surface of a cylinder of fixed radius; its projection into the plane is a straight line enclosed in a rectangle. The exchange of energy quanta between EM waves of differing amplitude, wavelength and frequency can then be massively simplified using the modulo four geometry of orthogonal knots.

The conclusion to be drawn from this approach is that the definition of electromagnetic phenomena in terms of the mathematics of continuous functions is a tautology in that the ability of human beings to carry out any kind of mathematical manipulation has its origin in the quantized electrochemistry of the brain. The tautology can be eliminated simply by re-defining mathematics in terms of electromagnetism, as outlined above.

**B E P Clement**  
Crickhowell  
Powys

### CD-I vs CDTV

I was disappointed by the article on CD-I ("Vision of the future", *EW + WW* August pp. 636-640).

Just when the author was about to make a proper technical comparison between CD-I and CDTV (which I would really like to read), he dissolved into vague generalities. "Because it is based on older technology, CDTV is inherently more limited..."

Both machines are based around 68000 chips running compact multi-tasking operating systems. OS-9 is

some years older than the Amiga Exec, but both have good reputations and are well documented. In both machines, the main processors are supported by graphics and audio chips.

The CD-I is planned to have 24-bit colour at launch time; the CDTV has 12-bit colour, but a simple plug-in up-grade to 24-bit colour has been demonstrated by Commodore. Both will show Kodak Photo-CDs.

The CDTV will accept a keyboard, mouse, joystick and disk drive and will then run general computer software - games, paint programs, etc, so the user is not limited to the rather expensive CD disks. So far as I know, the CD-I cannot be accessed as a general-purpose computer.

There must be some other differences which justify the remark about "old technology".

More facts, please!  
**Don Cox**  
Middlesbrough

### Satellite in a spin

It is with reluctance that I have to write such a critical letter with reference to the Hypothesis feature "Satellites Ride the Solar Wind" (*EW + WW* June 1991). Quite apart from his audacious claim to inventing the "Sailsat" the concept is devoid of analytical merit.

There is no way for a comsat or any other satellite to maintain a stationary position above any latitude-longitude point on the earth's surface if the orbital plane does not contain the equatorial plane.

The gravity force referred to is always radial and does not have a component to pull it back to the equatorial plane the diurnal effect of the sun and the moon have a much more pronounced effect on the inclination vector than any gravity anomalies (though important for geosynchronous orbits).

Other errors abound, but even in geostationary, or any, orbit there are periods of eclipse (by the earth, moon system) for considerable periods especially around the equinoxes.

The small inclination he ultimately "settles" for,  $2.5^\circ$ , is quite laughable considering that a number of

### Back to the future

Hugh Pincherie (Letters, *EW + WW* August 1991) suggests that a superconducting Faraday cage might be used as the basis for a "stasis device", ie a stationary volume of space wherein time is slowed or stopped relative to time in the space surrounding it. Such a device may quite simply

be demonstrated to be incompatible with the laws of conservation of energy and of momentum, and therefore impossible in the Universe as we presently understand it.

**James M Bryant**  
Newbury  
Berkshire

### Back to the future II

Hugh Pincherie's letter (*EW + WW* August 1991) regarding the possibility of time-travel, or at least the production of time dilation effects by the use of gyroscopic motion, may seem off-beat. But there are several anomalies connected with gyroscopes that still remain unexplained. This is evidenced by such machines as those of Strachan and Kidd that appear to lose weight when measured against a counterbalance.

It is doubtful whether the slowing of time would be achievable by gyroscopic spin, as the material is unlikely to hold together at relativistic speeds.

The most interesting aspect raised by Mr Pincherie is the question of variation of relativistic effects with direction, contrary to Einstein's General Theory.

However, a recent experiment to duplicate Michelson-Morley has shown a different value for the velocity of light dependent on direction. Maybe the ether needs to be revived for a complete understanding of physical science, as instanced by Dr Aspden's book "Physics Unified".

The Hayaski-Takeuchi

experiment is further evidence of a speed dependent weight reduction that cannot be accounted for by the Theory of Relativity, but is adequately explained in Dr Aspden's paper "*The Theory of Antigravity*".

Einstein struggled for many years to unify field theory by relating electromagnetic and gravitational interactions, but died before accomplishing the task. Even today there is a weak link between quantum physics and relativity. Many questions still remain unanswered and modern physicists may not be as close to the Grand Unified Theory (GUT) as they think.

Levitating gyroscopes are a phenomenon in which there has been government, academic and commercial interest, but sadly the scientific community is slow to follow. This is indicative of an authority that will not concede to accept the antigravity phenomenon, but is more willing to accept the abstract philosophies of time-travel.

**George Overton**  
The Anti-Gravity Society  
Tadley  
Hampshire

scientific satellites in geosynchronous orbit are allowed to drift up to  $3^\circ$  without sailsats of any kind. However the sub-satellite track then describes an elongated figure of eight

Numerous complexities are omitted: an associated drift in the

orbital nodes is one which by international agreement has to be closely controlled.

Perhaps Paul Birch could do no better than be referred to the numerous published papers in the *Journal of the British Interplanetary Society* where the analysis is correct,

# M & B RADIO (LEEDS)

THE NORTH'S LEADING USED TEST/EQUIPMENT DEALER

Oscilloscopes		General T/M	
Tektronix 2455 250MHz 4 trace	£1600	Tektronix 521A PAL vectorscope	£1500
Tektronix 2445 150MHz 4 trace	£1500	Tektronix 1481R waveform monitor	£600
Tektronix 2455 50MHz dual trace delayed T/B	£1500	Tektronix 1485C waveform monitor	£500
Tektronix 521A digital oscilloscope	£1250	Iwatsu SC7104 1GHz freq counter	£400
Tektronix 475A 250MHz dual trace	£1200	Iwatsu SC7104 1GHz freq counter	£295
Tektronix 468 digital storage	£1200	Racal D2000 9.6-56MHz freq counter	£85
Tektronix 5403 5448 5A18 5B42	£450	Racal D2000 9.6-56MHz freq counter	£235
Tektronix 7603 7A18 7A18 7B53	£500	HP 5381 7-digit 80MHz counter	£90
HP 1703 storage oscilloscope	£195	HP 5345A timer counter	£400
HP 1715 200MHz with DVM opt	£550	HP 5340A 10Hz to 18GHz freq counter	£1000
HP 1712A 200MHz dual trace	£400	Sayreco 252 automatic mod meter (20Hz)	£225
Kikusui COS6100 100MHz 4 trace	£495	Farnell AMM automatic mod meter	£250
Iwatsu SS571 100MHz 4 trace	£550	Racal 9009 mod meter	£325
Iwatsu SS5702 20MHz dual trace	£195	Marconi TF2300 mod meter	£150
Telequipment D67A 35MHz dual trace delayed T/B	£145	Rank Kalee 1742 wowl and flutter meter	£250
Telequipment DB8 50MHz dual trace	£250	Farnell TM4 millivoltmeter	£95
Tektronix 647A 100MHz dual trace	£100	Marconi TF2604 RF millivoltmeters 1.5GHz	£55
Gould DS300 200MHz dual trace oscilloscope	£200	Brüel & Kjaer elec voltmeter	£350
Farnell DTS12 digital storage oscilloscope	£395	HP 34506 GPIB multimeter/counter	£235
Tektronix 2215 60MHz dual trace D/L timebase	£350	HP 3465A digital multimeter	£125
HP 1707B dual trace 35MHz D/L timebase portable int.batt.	£300	HP 3478A digital LCD multimeter	£500
		HP 3455A hi stability voltmeter HP1B	£1500
		Tektronix DM501 TM501 digital voltmeter	£195
		HP 3400A true RMS voltmeter	£145
		Racal Dana 9100 1MHz to 1GHz wattmeter	£85
		Bird 8201 Termaflim 500-watt	£150
		Bird 8080 Termaflim 25 watts 3.5GHz	£45
		Genrad 1606E RI bridge	£150
		Genrad 1422B precision capacitor	£150
		Genrad 1617A capacitance bridge	£200
		Farnell 830/20 0 to 30 volts 20-amp PSU	£100
		HP 6294A 0 to 60 volts 1-amp PSU	£100
		Racal RA17L communications receivers	£195
		Racal 9908 10MHz counter	£350

## BRAND NEW AND BOXED

Gould OS300 20MHz oscilloscopes with probes and manual

£250

## Signal Generators

Marconi TF2008 10kHz to 520MHz AM/FM complete with RF kit box and manual	£350
Marconi TF2015/2171 synchronizer 10 to 520MHz AM/FM	£400
Marconi TF2016/2173 synchronizer 10kHz to 12MHz AM/FM	£375
Marconi TF2016A 10kHz to 12MHz AM/FM (as new)	£200
Marconi TF2361/9694/9695 1GHz sweep generator	£450
HP 8620B 1.3GHz sweep generator	£700
Wavetek 1080 1GHz sweep gen with 1905 X-Y display	£1500
Racal 9081 synthesized signal generator	£1500
Farnell SSG 520 synthesized 520MHz generator	£550
Farnell TTS 520 transmitter test set	£700
Marconi 2050 module RT 100	£450
Philips PM5234 100kHz to 110MHz signal generator	£100
Philips PM6456 stereo generator	£250
Wavetek 20MHz function generator	£250
Farnell FG1 function generator	£125
Tektronix 141A PAL colour test generator	£750
Philips 5500 colour bar generator	£225
Philips 5500 colour bar generators	£185
Marconi TF2000 oscilloscope	£175
HP 3336A synthesizer/level generator	£750

## Spectrum Analysers

Marconi TF2008 10kHz to 520MHz AM/FM complete with RF kit box and manual	£350
HP 8620B 1.3GHz sweep generator	£700
Wavetek 1080 1GHz sweep gen with 1905 X-Y display	£1500
Racal 9081 synthesized signal generator	£1500
Farnell SSG 520 synthesized 520MHz generator	£550
Farnell TTS 520 transmitter test set	£700
Marconi 2050 module RT 100	£450
Philips PM5234 100kHz to 110MHz signal generator	£100
Philips PM6456 stereo generator	£250
Wavetek 20MHz function generator	£250
Farnell FG1 function generator	£125
Tektronix 141A PAL colour test generator	£750
Philips 5500 colour bar generator	£225
Philips 5500 colour bar generators	£185
Marconi TF2000 oscilloscope	£175
HP 3336A synthesizer/level generator	£750

## SPECIAL OFFERS

Cossor CDDU150 35MHz dual trace scopes	£135
Telequipment D61A 15MHz dual trace scopes	£95
Scopex 4D10 10MHz dual trace	£75
Western Towers 75ft masts and tilt-over fittings	£75
19-inch racks 4ft, 5ft, 6ft, 6.6ft, less than 1 year old, from	£350
HP 8732B pin modulator 1.8 to 4.5GHz	£75
HP 8734B pin modulator 7 to 12.4GHz	£150
Tektronix 134 6019 current probes	£250
Genrad 1602B UHF admittance meter with adaptors	£185

ALL PRICES PLUS VAT AND CARRIAGE

86 Bishopsgate Street, Leeds LS1 4BB

Tel: 0532 435649 Fax: (0532) 426881

CIRCLE NO. 120 ON REPLY CARD

## Micro AMPS

### ICE 751

An emulator/programmer for the Philips 24-pin skinny DIP 8051; the 87C751. The ICE751 provides the cheapest way to emulate and program these devices.

### ICE51™

A low-cost emulator for the industry standard 8051. This product is also available in kit form.

### PEB552

The official Philips 80C552 evaluation board for this highly integrated 8051 variant. Optional debug monitor and 87C552 programming adapter are available.

### BASIC COMPILER

A PC-based cross-compiler that enables code written for the 8052AH-BASIC processor to be compiled for the standard 8051 or 8052. Interpreted Basic is also available on the ICE51.

### 8051 BOOK

8051 Architecture, Programming and Applications. A recommended book for readers who require a text on the 8051 and interfacing techniques. This book is supplied with a PC-based cross-assembler and simulator for personal or educational use only.

### OTHER

Contact us for information on these and many other related products such as 'C' compilers, I<sup>2</sup>C tools and drivers.

ICE51 is a trademark of Intel.

### Micro AMPS Ltd


66 Smithbrook Kilns, Cranleigh,  
Surrey, GU6 8JJ

Tel: +44(0)483-268999 Fax: +44(0)483-268397

CIRCLE NO. 121 ON REPLY CARD

## RADIO REMOTE

CONTROL . . .

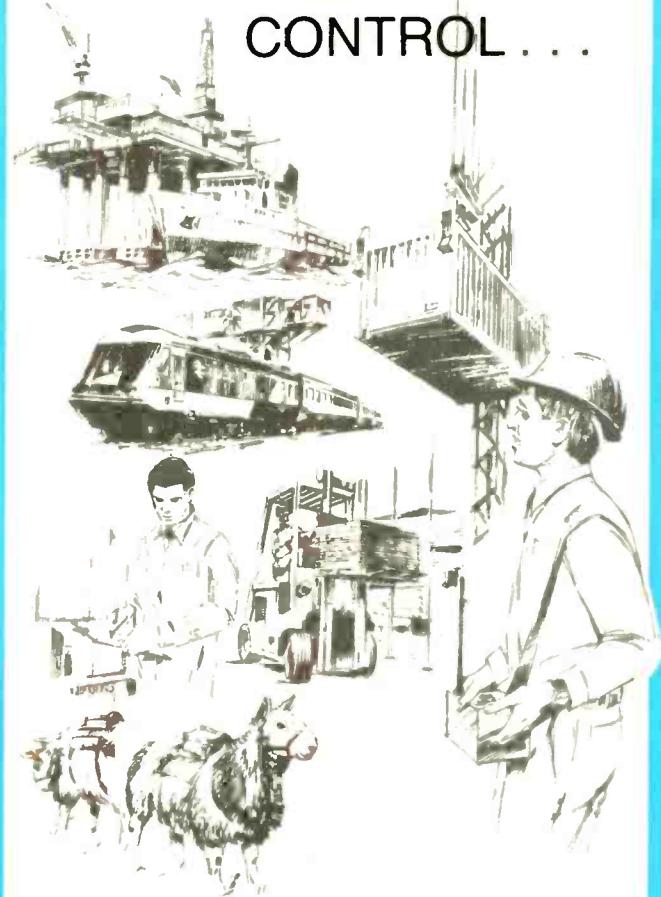

... wherever and whenever it's needed

Radio linking is the 1990's answer to the question of data transference and remote control . . . cutting out the need for fixed cables and direct connections. At Wood & Douglas we've developed this technology to a fine art with a range of compact, radio link modules capable of simple, highly efficient application across a wide spectrum of commercial and industrial uses. Where standard modules are not applicable we custom-build to precise requirements.

Over the past ten years we've successfully applied radio linking over such diverse areas as water leak detection, remote control of cranes and other industrial equipment, medical and veterinary monitoring, data logging, fuel and power control, automated warehousing . . . the list is endless.

In short, give us the problem . . . and we'll give you wireless control, wherever and whenever it's needed.



**WOOD & DOUGLAS**  
VHF/UHF COMMUNICATIONS PRODUCTS

Lattice House, Baughurst, Basingstoke, Hampshire RG26 5LL England  
Telephone: 0734 811444. Fax: 0734 811567



CIRCLE NO. 122 ON REPLY CARD

and to a publication of the European Space Agency ESA SP-1053". An Introduction to Geostationary Orbits", November 1983.

**A Pathan**  
School of Engineering  
Sheffield City Polytechnic

## CFA questions...

The correspondence on the crossed-field antenna has rumbled on for long enough. I told Mr Hately, its inventor in 1987, that it would not be credible until proper measurements had been made to establish what its typical radiating efficiency was. These measurements were needed because current physics shows that the radiation efficiency is probably small. That is to say that any given effect claimed for the CFA could probably be produced using a much less powerful transmitter and an efficient antenna.

In the intervening years a lot of hype has appeared in this magazine in praise of the CFA, and a few letters urging caution. Not once have you printed the essential quantity required to judge the antenna, which is the field-strength produced at a known distance when a known RF power is input to the antenna.

At this year's International Conference on Antennas and Propagation (Icap), a paper was presented on the CFA, giving the field strength as 2V/m at a distance of 500m from the CFA, measured in

an area of good ground conductivity in the Nile delta region of Egypt. At last a figure had been published that would give an idea of the CFA's efficiency. Simple theory shows that this level of field at this distance can be produced by transmitting from a quarter-wave monopole antenna radiating 10.1kW.

In the trade it is known that a quarter-wave monopole for medium wave broadcasting can usually achieve 90% efficiency, and we therefore arrive at the result that 12kW transmitter with a quarter wave monopole will easily produce in practice the field claimed for the CFA in the Icap paper. The paper does not give the input power to the CFA, but the nominal transmitter power was – wait for it – 60kW!

On the assumption that 60kW was delivered to the CFA, its radiation efficiency was in the region of 20%. This in itself is higher than I suspect is being achieved, and considerable allowance must be made for tolerances in the measurement technique (which is not described) and radiation from the feeder (which is probably significant).

Plenty of radio amateurs (myself included) would be able to produce better efficiency at HF with the traditional piece of wire bought for £5 from Woolworth's than these results quoted for the CFA.

In medium-wave broadcasting, for any given application one has to decide on the required transmitter power and antenna efficiency by

trading-off the antenna efficiency against the cost of a high-power transmitter. A cheap inefficient antenna will require a powerful and expensive transmitter. The optimum usually occurs with antenna efficiencies of 60-90%. The economics therefore make the CFA an unlikely candidate for any application below 30MHz.

I strongly advise anybody contemplating the purchase of a CFA to make sure before ordering that the product carries proper certification by a competent agency (such as the BSI or the NPL), that its radiation efficiency has been measured, and that the result of the test is stated. An additional test, essential for personal safety, is determination of the exact intensity of the fields in the region near the antenna. You would require adequate testing for a microwave oven or a vacuum cleaner, and it is perfectly possible to be equally scientific about antenna measurements.

On the theoretical side of the argument about the CFA, it should be said that the physical interpretation of Poynting's theorem of 1884 has always been problematical and liable to error. Poynting's theorem makes no statement about the direction in which energy flows, because the three major terms in his equation are all scalars. The theoretical basis for the CFA (Poynting vector synthesis) is therefore nonexistent. It is also ridiculous to claim, as the CFA's inventors have done, that rewriting Maxwell's equations the other way round will allow important new ideas to be deduced. The equations of applied mathematics don't work like that. They simply state that the quantity on the left equals the quantity on the right, without implying anything about cause and effect.

It is also in my view wrong to claim that the H-field plates in the CFA produce significant H-fields close to the antenna. What is true is that both pairs of plates will produce E-fields and H-fields. When the field equations are solved for the region near the CFA, it is most likely that the H-fields near the antenna will turn out to be insignificant. The experiment described in your March 1989 issue by Kabbaray, Hately and Stewart to investigate this effect is entirely spurious, because the rf driving

voltage is wrongly applied. Figure 3 in that article shows the rf voltage applied between the inner and outer regions of a conducting sheet, the regions being separated by a circular gap. To represent the CFA plates the rf obviously should have been applied between the sheet and the ground plane.

To sum up, I would say that the CFA is a typical inefficient small antenna. Nothing magic is happening, and when the hype is stripped away we are left with very little. Is it unreasonable to request that no more articles appear on this device until the radiation efficiency can be reliably measured? Without this, anything else is a waste of your readers' time.

I notice with pleasure that your August edition contains a letter on time machines. This holds the promise of plenty of material in months to come that is cranky, entertaining and undoubtedly more academically respectable than the crossed field antenna!

**Alan Boswell**  
Chelmsford  
Essex

## ...and reflections

I always thought that brief letters stood a greater chance of being printed without cuts, but you made a critical cut in my two paragraph letter (EW + WW August 1991).

The point about CFAs is that it is claimed that they produce waves with a tightly curved waveform and that they can therefore be reflected by a much smaller reflector than would otherwise be the case. Simply claiming that the waves "are smaller" is a very vague way of putting it, and not what I intended to say.

**David Gibson**  
Leeds

## Diary Note?

WH Powell of Warwickshire (EW + WW August 1991) can relax. To the rescue is one of a series of regular events updates to be sold on modest subscription. If W H Powell, or any other reader, would like a free copy write to the address below, marking your envelope EW.

**G Beaumont**  
Events Publications  
PO Box 2500  
London N4 4QE

## Jiggers


Your article "End of the beginning" (Pictures from the Past, EW + WW July 1991) refers to the name "jiggers" given to aerial coupling transformers in earlier times, and suggests that the reason for this name has been forgotten. My investigations find that the terms "jig" and "jiggers" may have been introduced by James Erskine-Murray. I quote from his Handbook of Wireless Telegraphy, 1907:

"I... propose to adopt a good old English word which signifies a periodic motion of high frequency, to stand for 'a damped train of electrical oscillations of a frequency of the same order as is employed in wireless telegraphy'; or the corresponding 'oscillatory

currents, voltages, or magnetic fields of high frequency,' associated with them in the sending or receiving circuits of a wireless installation. The word chosen is brief and descriptive, viz, jig. It may be qualified where necessary to prevent confusion – thus an electric jig, a magnetic jig, an Irish jig – all implying periodic motions of very high frequency. A transformer of the high frequency currents used in wireless telegraphy has been called a jigger, hence it also seems natural to call these currents 'jigs'..."

Indeed we might have ended up with the "kilo-jig" and the "mega-jig", but things worked out differently.

**Peter E Musk**  
Rickmansworth  
Herts

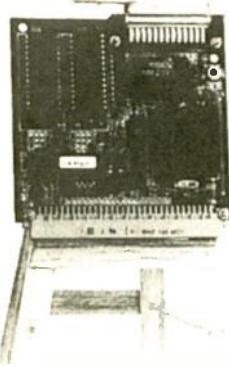

## FROM CLASSROOM ...

### THE BeTA MICROCONTROLLER TRAINER

The BeTA Microcontroller Trainer provides an in depth course in the programming and use of microcontrollers through hands on experience using ready built applications circuits. Based on the Phillips range of 8051 microcontrollers the course uses the CAMEO board which in addition to providing the interface to a VDU is suitable for incorporation in small batch production projects.

The BeTA Microcontroller Course Provides:-

- CAMEO Board incorporating:-
- Powerful 80C552 Microcontroller
- Eight A to D Inputs
- Four Capture and Three Compare Timer Inputs
- RS232 Serial Interface


#### PLUS:-

- Mains Power Supply
- Interconnect Unit
- Applications Board
- Multiway Computer Cable
- Student and User Manuals

Price £450.00
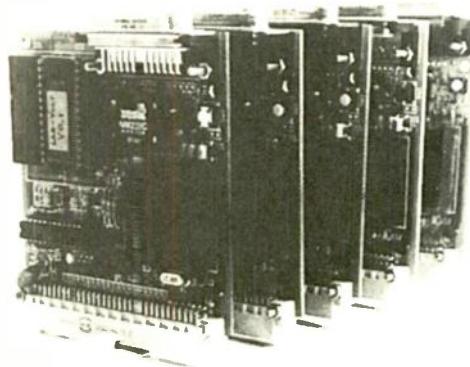
#### BeTA Marketing

Frog Mill, Tedburn St. Mary, Exeter, Devon EX6 6ES.  
Telephone (0647) 24239 Fax (0647) 24059




## ... TO PRODUCTION LINE

CIRCLE NO. 133 ON REPLY CARD
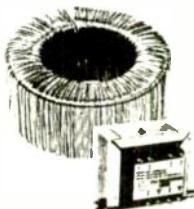
### Toroidal Transformers

As manufacturers we are able to offer a range of quality toroidal and laminated transformers at highly competitive prices.



#### Toroidal Price List

Quantity prices Exclude VAT & carriage

VA	Mail Order	Quantity Price Excluding VAT & Carriage			
		2+	10+	25+	100+
15	12.16	8.51	6.89	5.17	5.02
30	13.37	9.36	7.35	5.68	5.35
50	14.86	10.40	8.17	6.32	6.13
60	15.02	10.51	8.26	6.38	6.20
80	14.98	10.50	8.25	6.38	6.00
100	17.58	12.29	9.88	7.48	7.24
120	17.95	12.57	9.87	7.63	7.41
150	21.65	15.16	11.81	9.20	8.93
160	19.86	13.90	10.92	8.44	8.19
225	25.09	17.56	13.80	10.66	10.35
300	28.60	20.02	15.73	12.16	11.80
400	38.49	26.94	21.17	16.36	15.88
500	42.07	29.45	23.14	17.88	17.35
625	44.24	34.47	27.08	20.93	19.31
750	48.66	38.86	28.98	22.38	21.72
1000	65.67	45.97	36.12	27.91	27.09
1200	68.71	48.10	37.78	29.20	28.34
1500	87.58	61.36	48.17	37.22	36.13
2000	114.45	80.11	62.95	48.64	47.21
2500	135.87	95.11	74.73	57.71	58.04

These prices are for single primary with two equal secondaries with 5% colour coded fly leads. Each transformer is supplied with a mounting kit, consisting of one steel washer, two neoprene pads, and a nut and bolt.

Please do not hesitate to telephone or write with your particular requirements.

Available in the following voltages: 6-0-6, 9-0-9, 12-0-12, 15-0-15, 18-0-18, 22-0-22, 25-0-25, 30-0-30, 35-0-35, 40-0-40, 45-0-45, 50-0-50, 110, 220, 240, Primary 240 volt.



#### Air Link Transformers

Unit 6, The Maltings, Station Road, Sawbridgeworth, Herts.  
Tel: 0279 600139 Fax: 0279 726379

CIRCLE NO. 134 ON REPLY CARD

### COMMERCIAL QUALITY VHF/UHF RECEIVER



The IC-R7000, advanced technology, continuous coverage communications receiver has 99 programmable memories covering aircraft, marine, FM broadcast, Amateur radio, television and weather satellite bands. For simplified operation and quick tuning the IC-R7000 features direct keyboard entry. Precise frequencies can be selected by pushing the digit keys in sequence of the frequency or by tuning the main tuning knob FM wide/FM narrow/AM upper and lower SSB modes with 6 tuning speeds: 0.1, 1.0, 5, 10, 12.5 and 25kHz. A sophisticated scanning system provides instant access to the most used frequencies. By depressing the Auto-M switch the IC-R7000 automatically memorises frequencies in use whilst it is in the scan mode, this allows you to recall frequencies that were in use. Readout is clearly shown on a dual-colour fluorescent display. Options include the RC-12 infra-red remote controller, voice synthesizer and HP-2 headphones.

**ICOM** Post to: Icom (UK) Ltd. Dept WW  
Sea Street Herne Bay Kent CT6 8LD  
Tel: 0227 741741 (24hr). Fax: 0227 360155

Name/address/postcode ..... 10

Call sign: ..... Tel: ..... Dept: WW

CIRCLE NO. 135 ON REPLY CARD

# REGULARS


CIRCUIT IDEAS

## Bi-directional i/o for microcontrollers

I/O pins on microcontrollers which are configurable as either input or output are not usually capable of driving much of a load in one role or providing any schmitt action to shape inputs in the other. For useful interfacing, one must therefore provide drivers or schmitt outputs with, possibly, filters which effectively ruin any chance of software pin assignment.

This circuit does, however, allow more flexibility. The darlington output driver and the schmitt input gate go to the same pin, contentions being handled by software. Values cannot be shown, since they have to be determined by drive capability of the controller concerned and loading on the pin.

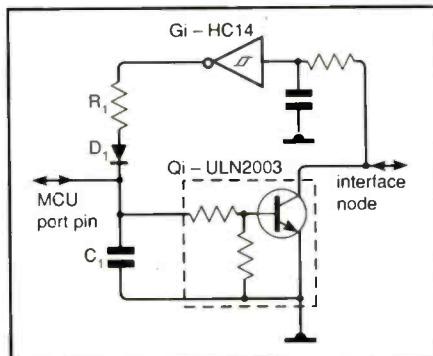**Input.** Set the port pin to "output" and program it low, switching  $T_{R1}$  off to prevent it affecting the interface node. Data on the node is inverted by  $G_1$  and it may be found



*Bi-directional buffer allows configurable i/o pins on microcontrollers to be software controlled without any need for hard wiring.*

that there is now contention with the port, so  $R_1$  is inserted. To read, the port is momentarily configured as an input. Any tendency for  $T_{R1}$  and  $G_1$  to latch disappears when it becomes an output again. If  $T_{R1}$  conducts briefly, use  $C_1$ . Do not make  $R_1$

too high, or the port pin voltage might not reach 1 because of loading by  $T_{R1}$ .

**Output.** When the port is high, the output of  $T_{R1}$  goes low, so that the output of  $G_1$  is high and is out of contention with the port. When low, it works against  $G_1$  output for a short time until  $T_{R1}$  goes off and  $G_1$  is low; this sets the lower limit of  $R_1$ . When the port goes high, it again works against  $G_1$  for a short time; some n-mos controllers have weak pull-ups and the diode assists the action.

**David Gibson**  
Leeds  
West Yorkshire

## Dial a harmonic

Setting a switch allows the selection of a harmonic of  $2nf$  of an input, for use with a modulator.


At the input, the signal meets a low-signal amplifier and is then squared in 4011 comparator, which provides a stable input and does not need a multi-turn control. The signal from the amplifier also goes to the modulator.

Squared signals are the reference in a phase-locked loop, the n-divider to produce a  $2nf$  frequency consisting of the 4017, a 4001 and half a 4013, which divides the  $2nf$  to give in-phase and antiphase harmonics (nf and -nf). Capacitor  $C_x$  determines the range over which the circuit operates and the led indicates lock.

The second TL071 takes the sum and difference frequencies of the two inputs. If the difference is zero, the output is DC, indicating the value of the harmonic n.

You should balance the 1496 modulator by the potentiometer, using an oscilloscope on the TL071 output, with no input (pin 4 shorted).

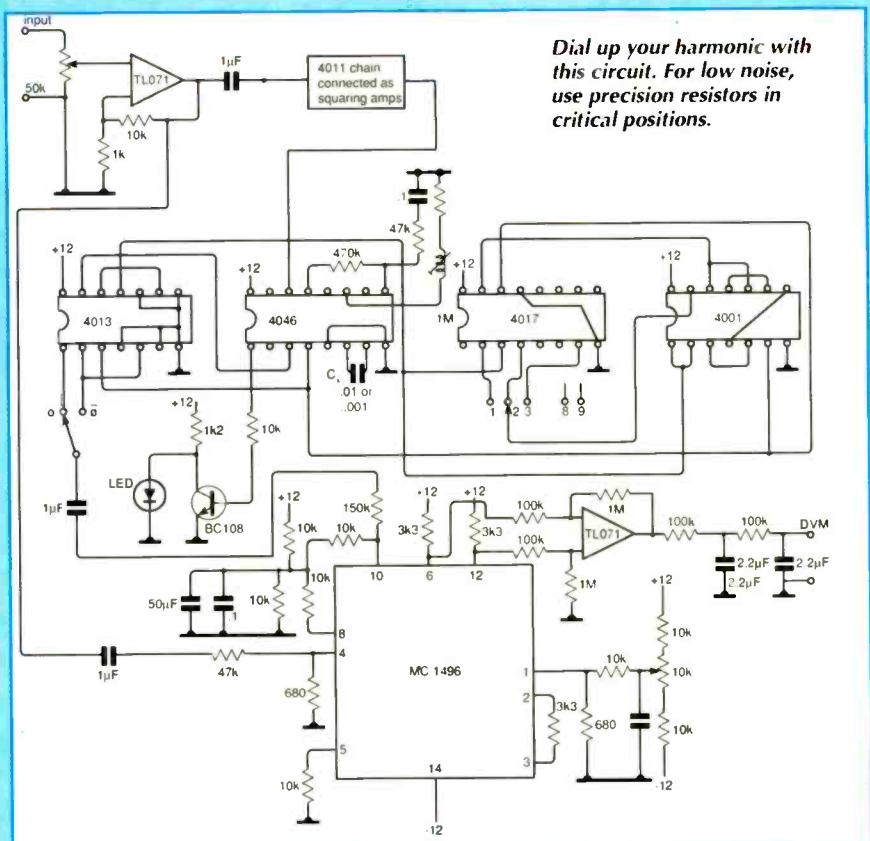**E Rangel Marins**  
Instituto Nacional de Tecnologia  
Rio  
Brazil



## Programmable waveform generator


This provides three-function waveform generation from 0.01Hz to 1MHz under the control of a microprocessor, which also indicates frequency digitally.

Control voltage for the 8038 function generator comes from the micro via an 0832 8-bit D-to-A converter, a buffer, a voltage amplifier with a gain of ten and a voltage follower. Sine (top switch position), square and triangular (bottom) waves are taken out through a further voltage follower and variable-gain amplifier, the micro indicating frequency via the 8255 programmable peripheral interface and led display. It is assumed that a linear relationship exists between control voltage and frequency.

Sensitivity to frequency control is adjusted by the values of C, R<sub>8</sub> and R<sub>9</sub> and R<sub>6,7,10</sub> adjust waveform shape. Output voltage is about 20V.

**M T Songping Liu**  
China

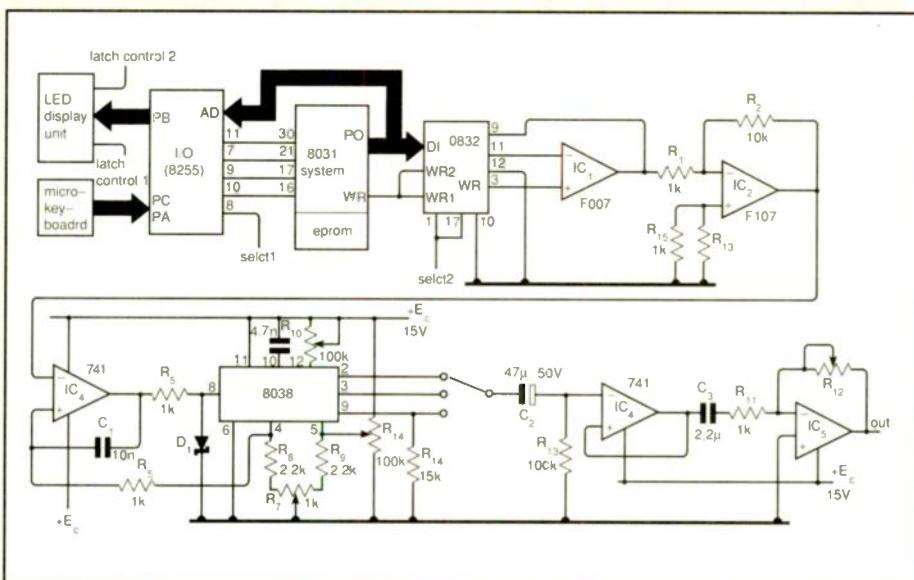(If Mr Liu would like to let me have his address, I will send his cheque. — Ed)



Waveform generator controlled by microprocessor, which also gives a direct indication of frequency.



### HAVING INTERFACING PROBLEMS?

At last the best solution you are ever likely to find!

### A COMPLETE MULTI BOARD COMPUTER

£199+VAT for the standard unit

(The screen and keyboard alone are worth more than that)

Z80 CPU  
Complete with BASIC ROM  
Keyboard, 80-character, 8-line display  
Battery backed (All functions)  
Two RS232 ports  
Two A/D ports

Programming advice for first 3 months  
Full technical manuals provided  
Software included to connect to other computers  
30-day money back guarantee  
Add-on boards and other interfacing boards available

Order direct or contact us for more details

**COVEND ELECTRONICS**  
32 Poplar Grove, London W6 7RE  
Tel: (071) 371 6497 Fax: (081) 741 1135

CIRCLE NO. 161 ON REPLY CARD

**Field Electric Ltd. Tel: 081-953 6009. 3 Shenley Road, Borehamwood, Herts. WD6 1AA. Fax: 081-207 6375, 0836 640328**

### SPECIAL OFFERS

Philips HCS115 Viewdata terminals. Pulse/tone selectable; memory; full size k/ board; modem; autodial; colour VDU; etc. £95+VAT c/p £15.50.

HT12 fully 286 compatible; half size mother board; Intel 286 CPU; running at 12/16/ 20MHz; zero wait state; 1Mb RAM supplied; up to 4Mb. AMI BIOS; set-up disk. New & boxed. £115+VAT c/p £6.00.

386sx half size mother board same as above but expandable to 8Mb. New & boxed. New XT computers in stock from £265 Inc VAT supplied with mono monitor running at 8MHz. Small footprint case.

Sola mini UPS. 500watt + line conditioner & inverter. £95 Inc VAT c/p please ring. Chloride Powersafe batteries 12V DC 24Ah sealed lead acid. £19.95 c/p £9.00. New, marked cases.

3.5" floppy disk drive Chinon BBC compatible, new £35 c/p £4.00.

3.5" floppy disk drive NEC IBM compatible. Full height unit. £39.95 new & boxed, 1.6Mb, c/p £3.00.

Various high-capacity hard disk drives in stock – please ring.

Switch mode power supplies 240V AC input 5V DC 40amp £29; 12V DC 10amp £46; 5V DC 40amp – 12V DC 4amp + 15V DC 11amp £48.

NEC 9" mono monitor composite video input, switchable high-low impedance input & output for daisy-chaining. BNC sockets. Built-in carry handle. £29.95 c/p £7.50.

5" mono monitor, composite video input, 12V DC 1.2amp chassis £25.95 c/p £5.00.

EGA 8-bit display cards £17 c/p £2.00.

H.P. 4328A milliohmometer £450 c/p £11.00.

H.P. 3400A RMS voltmeter £225 c/p £11.00.

H.P. 3330B auto synthesizer £550 c/p please ring.

Tektronix 191 constant amplitude sig.gen. £175 c/p £12.00.

Tektronix 178 linear IC test fixture £POA.

Tektronix 067-502 standard amplitude calibrator £120 c/p £12.00.

HML Model 411 cap. tester 20kV new £POA.

Leader LBO-5810A dual trace programmable 25MHz o'scope £200 c/p £18.00.



We would like the opportunity to tender for surplus equipment

Official orders credit card telephone orders accepted with

Access, Amex, Diners, Visa cards. Overseas enquiries

welcome c/p rates U.K. mainland only.

Please ring for c/p rates not shown.

All prices inc. V.A.T. unless stated. Stock list available.

CIRCLE NO. 156 ON REPLY CARD

# UHF VCO

A simple UHF voltage-controlled oscillator for satellite receivers, offering a frequency range of 1200-2100MHz, output power of +7dBm into 50Ω, Varicap range

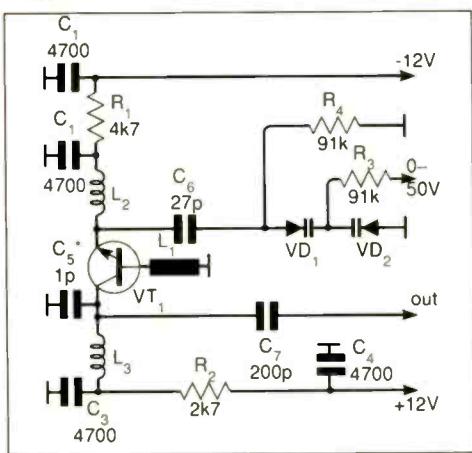


Fig.1. UHF voltage-controlled oscillator for satellite broadcast working.

0V-50V and supply requirement of  $\pm 12V$ .

**Figure 1** shows a design using inexpensive components. Parasitic inductance is a major problem at these frequencies, since it is comparable with designed inductance in the resonator circuit and makes decoupling difficult. In this design, some of the problems are avoided by connecting load to the collector and the resonator components to base and emitter.

Construction is much more important in this type of equipment than that for lower frequencies, so a description is needed; **Fig.2** shows a successful layout. A 1.5mm double-sided glass-fibre board, measuring 35 by 30mm is used. Ground pads under  $C_{2,3,5}$  are connected to the back plane by plated-through holes. Leads on  $R_{1-4}$  and  $C_{6,7}$  must be short. It would have been possible to use only one Varicap, but the transistor base would have been taken directly to ground and matching would have been difficult. Capacitors  $C_{1-4}$  are disc ceramic;  $L_{1,2,3}$  are 2 or 3 turns of 0.4mm wire on a

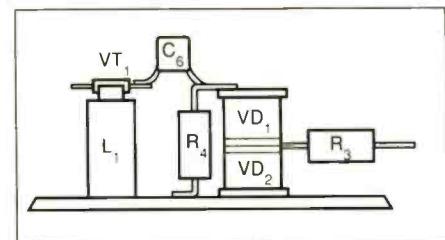


Fig.2. Suggested layout of UHF VCO reduces problems set by stray inductance assuming same proportions as intended variety

diameter of 3mm;  $L_1$  is 2.5 by 7mm copper foil, 3mm of it being soldered to ground; the transistor is BFQ69, BFR93, BFR34A or an equivalent, mounted directly onto inductors  $L_{1-3}$ .

**Raimundas Markevicius**  
Vilnius  
Lithuania


## Class-A push-pull amplifier

**M**r Richards provides a circuit for an amplifier in which the output bipolar transistors are permanently forward biased. Input signal divides into two halves by means of the diode-feedback "perfect" diodes IC3,4, while IC2, a simple inverter,

is needed to allow overall feedback to be in the correct phase. We have no further information on the circuit.

**W O Richards**  
Battersea  
London SW11

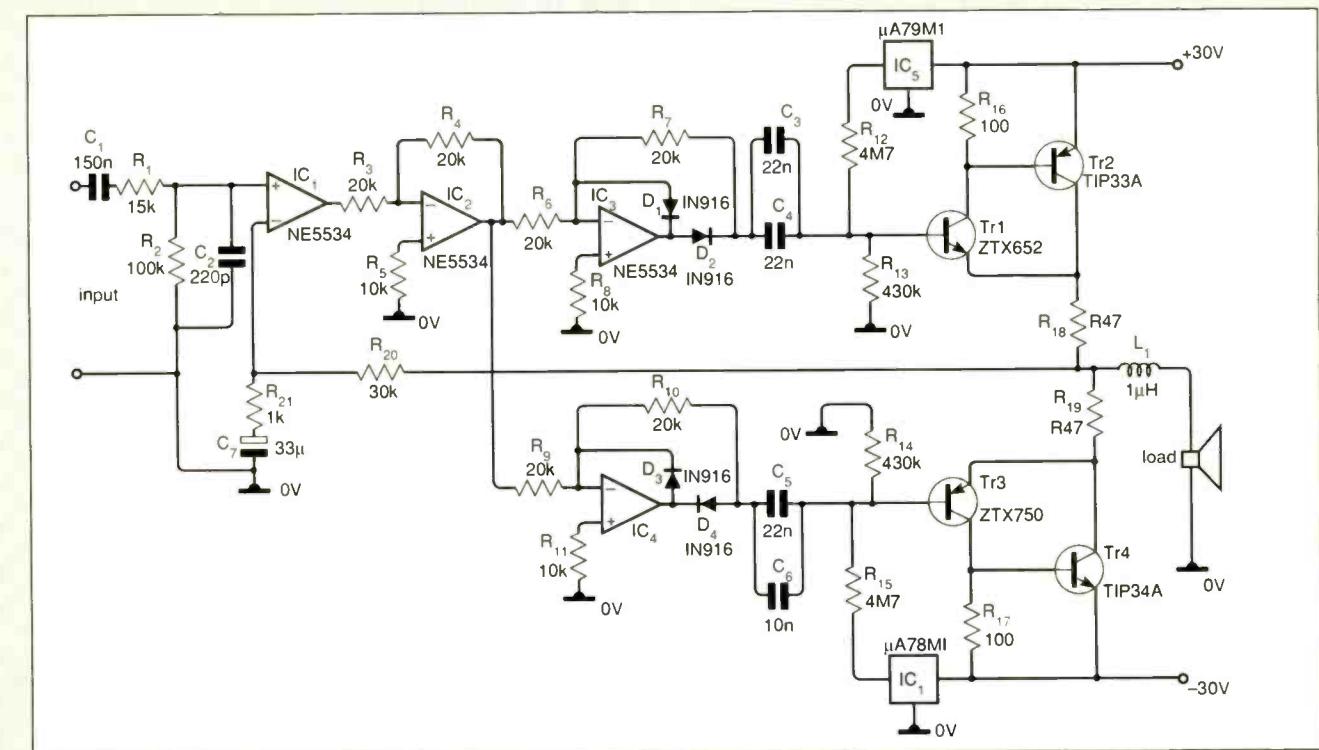**Amplifier has permanently conducting output transistors. Phase splitting is by unity-gain diode-feedback stages and IC<sub>2</sub> arranges the various inversions to present overall NFB to IC<sub>1</sub>.**



# Microprocessor Development Tools

EMULATORS - SIMULATORS - COMPILERS - ASSEMBLERS - PROGRAMMERS  
 77C82 8085 Z8 68000 8051 32010 68HC11 6301 6502 87C751 6805 Z80 6809 8096 740 Series 7720 MIPS R2000 etc . . .

## SMAC UNIVERSAL ASSEMBLER

- ✓ Relocatable
- ✓ Fast Assembly
- ✓ Caters for ALL Microprocessors and Controllers with bus widths from 1 to 255 bits wide
- ✓ Instruction sets for many microprocessors included
  - from Z80 to RISC 2000
- ✓ Instruction set compiler AND VERIFIER included
  - add your own micro!
- ✓ Iterative macros
- ✓ Intelligent jump facilities
- ✓ Linker and *MAKE* facility

## SIMULATORS

- ✓ Debug microprocessor and controller software on your pc
- ✓ Break points and trace
- ✓ Free run or single step

**NEW**

## ROM EMULATOR

- ✓ Covers ROM sizes from 16 kbit to 8 Mbit
- ✓ Full screen editor
- ✓ Emulates all 24, 28, 32 & 40 pin devices
- ✓ Fast download - loads 1 Meg in under 5 seconds
- ✓ Split and shuffle capability

## PROGRAMMERS

- ✓ PB-10  
Low cost E(E)PROM programmer to 4Mbit includes 16 bit wide microcontrollers and gang options
- ✓ SA-10  
Stand alone E(E)PROM programmer
- ✓ SA-20  
8 gang version of SA-10
- ✓ TUP-300  
Universal device programmer

2 Field End, Arkley, Barnet, Herts, EN5 3EZ Telephone : 081-441 3890

**SMART**  
COMMUNICATIONS

CIRCLE NO. 136 ON REPLY CARD

## EPROM PROGRAMMER OR UNIVERSAL PROGRAMMING SYSTEM FOR YOUR PC? From Low Cost EPROM PROGRAMMER

The Model 160 programs virtually every EPROM and costs £195 + VAT

## To UNIVERSAL PROGRAMMING SYSTEM

The Model 200AP programs EPROMs, serial and parallel EEPROMs, Flash memories, Micro-processors and controllers, PALs, GALs and Bipolar PROMs and costs £345 + VAT (adapters where required from £75).

This includes all the 8751 and 8748 families, the PIC micro-controllers, Z8s and EPROM Emulators. Nearly 900 devices in all.



New devices are constantly being added - ask if you want any programmable device added to our list.

All our programmers are designed, manufactured and supported by us in the UK.

Programming times are faster than most of our competitors, e.g. using the parallel port of your PC they program 2764s in 4 seconds and take less than one minute to blank check, program and verify 1 Megabit Flash Memories (*and this time includes download time*).

We also sell Gang Programmers, EPROM Emulators and Erasers and a universal cross-assembler for IBM PCs and compatibles.

**Write or phone today for Free Information Pack:  
Phone: (0666) 825146      Fax: (0666) 825141**

**MOP ELECTRONICS LTD., PARK ROAD CENTRE,  
MALMESBURY, WILTSHIRE, SN16 0BX UK**



Scandinavian distributor:	Digitron A/S, Alesund, Norway	Phone 071-45 890 Fax 071-45 453
German distributor:	Synatron GmbH, Grasbrunn B.	Phone 089/4602071 Fax 089/4605661

CIRCLE NO. 137 ON REPLY CARD

October 1991 ELECTRONICS WORLD+WIRELESS WORLD

## HALCYON ELECTRONICS

Test equipment, video monitors, amateur radio gear, printers, power supplies, communications, disk drives, multimeters, oscilloscopes, scientific instruments, connectors, component bridges, frequency counters, signal generators, computers.

Visit our bargain corner in shop.  
Many valuable items at knock-down prices.

MICROWAVE 1-20GHz ATTENUATORS, DIRECTIONAL DETECTORS COUPLERS, NOISE SOURCE, SIGNAL GENERATORS, SWEEP OSCILLATORS, LP FILTERS, PIN MODULATORS, CARRIAGES, TERMINATIONS, MOVING & ADJUSTABLE SHORTS, ETC	POA SYSTRON DONNER 3522 IEEE488 BUSER 2	£495
BBC-B COMPUTERS	£199 SANYO MBC555 COMPUTER MON. D DRIVES	£95
GEN RADIO 1531A XENON STROBOTAC	£49 CAMBRIDGE PORTABLE POTENTIOMETERS	£29
FARINELL E350 PSU 0-35V 6.3V's	£49 TINSLEY 4281A LAB STD. VIRATIO BOX	£275
CITOH 8510 DOT MATRIX PRINTERS RS232	£35 FERROGRAPH 4A TAPE RECORDER	£39
APPLE 2E - 128K, TWIN DISK DRIVES ETC	£95 SULLIVAN GRIFFITHS TAPPED INDUCTANCES	£39
STORMATIC 900 MOBILE R/T, COMPLETE COMMUNICATIONS RECEIVERS From MARCONI TF1245/1246 Q METER	£95 WESTON STANDARD TWIN CELL TINSLEY	£75
MARCONI LODESTAR 2464A AUTO DF RECEIVER	£49 REDPOINT 6E-1 HSINKS 1.5 C/W QTY	POA
TEKTRONIX 7403N DFT 7001 LOGIC ANAL	£275 STAG PP41 EPROM PROGRAMMER	£495
NELSON ROSS SPECTRUM ANALYSER 0-20KHz	£39 MARCONI TF2330 WAVE ANALYSER	£150
RACAL DANA 9341 DIGITAL LCR BRIDGE	POA COHU 301 0-500V DC VOLTAGE STD. INT REF	£125
AVO CZ 4575 COMPONENT COMPARATOR	£295 MICROWA ANALYTICAL BALANCE	£49
MARCONI TF2300 FM AM MODULATION METER	£295 SULLIVAN & G STD DEC AIR CAP 0-1100PF	£495
TEKTRONIX 535A, 545B, 585 SCOPES FROM WANDEL & GOLTERMAN TFPM-43 & TFP-42 EA	£75 LYONS WG716 16MHz WORD GENERATOR	£245
UV SOURCE SHUTTER OP. TIMER, 200W 240V	£195 PRESTEL ALCATEL TERMS/KB/RS232 ETC	£45
NEOTRONICS OTX91 OXYGEN ANAL PRTABLE LEAKSEEKER 4E PORTABLE GAS DETECTOR	£49 B&T LAB OVENS 12x13x14 INTERNAL 210°C	£195
TEKTRONIX 834 PROG DATACOMMS TESTER	£49 PASCALL BALL MILL VARIABLE SPEED	£95
AVO 85 MK2, 5 & 6 From VARIABLE OUTPUT PSU's From	£89 TEKTRONIX 462 PLottERS, GPIB & RS232	£179
TEKTRONIX 520 PAL OR NTSC VECTOROSCOPES	£475 HP COMPUTER 9825B, 15263A, 98032A OPT 066	£95
METROHM V8 500V ELECTRONIC MEGGERS OTHER MEGGERS/MEGGER BRIDGES From	£95 TECMAR Q1C-60H TAPE STREAMER	£95
	£395 LEADER LCG 396 NTSC PATT GENERATOR	£395
	£55 CONRAD 7211 HI-RES RGB MONITOR	£395
	£35 OSCILLOSCOPES DUAL TRACE S-STATE From	£99
	£475 12 GREEN SCREEN MONITORS From	£39
	£29 LEADER LBO-9C ALIGNMENT SCOPE	£249
	£10 SIGNAL GENERATORS AF TO 21GHz From	£15

LIST AVAILABLE, BUT 100'S OF UNLISTED BARGAINS FOR CALLERS  
QUALITY ELECTRONIC EQUIPMENT BOUGHT ALL PRICE EXC. OF P&P AND VAT

423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR  
SHOP HOURS 9-5.30 MON-SAT. TEL 081-542 6383.

CIRCLE NO. 138 ON REPLY CARD

# REGULARS

## NEW PRODUCTS CLASSIFIED

### ACTIVE

#### Asic


**Gate array library.** The VGT353 is a three-layer metal  $1\mu$  gate array library that increases the number of usable gates on the array by 80% and performance by 20% compared with the corresponding two-layer process. Up to 130,000 usable gates are available on a single array. VLSI Technology, 0908 667595. For more information on asics, see the literature section of this review.

#### A-to-D & D-to-A converters

**18bit adc.** The PCM1750 dual 18bit cmos a-to-d converter has serial data outputs and is for digital audio applications. It includes separate sample and hold circuitry for each channel so that the inputs are sampled in phase. Switched capacitor techniques are used in the conversion stage and the entire conversion process takes 4.5 $\mu$ s. Input level is 5.5V peak to peak with full power input bandwidth of 500kHz. Burr-Brown International, 0923 33837.

**Video dac.** A triple 8bit 30MHz video d-to-a converter is for use in high-resolution TV, satellite TV encoder

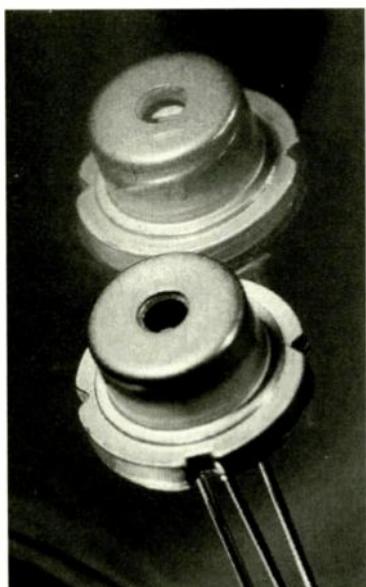**Seeing is believing: the HL7851G is a visible light laser diode for optical disc systems.**



and decoder systems, image processing, and computer colour graphics. The MV95338 is a variant on GPS' VP101 video dac but at a lower cost. It is a drop-in replacement for the Brooktree BT101 and works with GPS' D2MACchip set. It uses video control inputs to provide the video pedestal levels needed to generate RS343A compatible video signals into a doubly terminated  $75\Omega$  load or RS170 signals across a singly terminated  $75\Omega$  load. GEC Plessey Semiconductors, 0793 518000.

**12bit adcs.** The Max183 a-to-d converter has a 3 $\mu$ s conversion time. Also available are its two sisters – the 5 $\mu$ s Max184 and the 10 $\mu$ s Max185. Power consumption for all three is typically 90mW. They have +5, +10 and  $\pm 5V$  input ranges and a reference input that is internally buffered. Data access time is 100ns and there are three-state data outputs and standard control inputs for connection to most microprocessors. Maxim Integrated Products, 0734 845255.

#### Discrete active devices

**Transistor array.** A transistor array for use as an output device in fast video amplifier circuits consists of a complimentary pair of silicon bipolar transistors connected as emitter followers. Collector-base breakdown voltage is 120V for the npn transistor and -80V for the pnp. Cut-off frequency for each chip is 1GHz. The CR820 is expected to be used in black and white video monitors and other applications where discrete steps of brightness are required. Motorola, 0908 614614.

**Barrier diode.** The U1GWJ49 is a 1A schottky barrier diode with a reverse recovery time of 35ns. Repetitive peak reverse voltage ratings of 30 and 40V are available and maximum forward voltage is 0.55V. It comes in a SOT-89 housing but is also available in axial lead packages or a miniature I-flat package for surface mounting. Toshiba Electronics, 0276 694600.

#### Digital signal processor

**DSP chip.** A DSP IC has an architecture optimised for signal processing algorithms and executing code written in high level languages including ANSI C and ANSI numerical C. The ADSP21020 has independent parallel computational units with 32 and 40bit IEEE floating point precision and 32bit fixed point. Executing an

arithmetic operation takes a single 40ns machine cycle on the fastest-100 grade. The 1024-point complex FFT executes on 0.77ms. Analog Devices, 0932 232222.

**MPU training system.** A range of C3M digital signal processors is based on the T13020 processor and offers users a way to use and learn digital signal processing. Among the range's capabilities are real-time signal processing, digital and adaptive filtering, acoustic measurements, speech recognition, and digital radio. All models have a fast no-wait state memory. The range comes with software consisting of a cross assembler, monitor/debugger, and simulator. The units are linked to host computers via a parallel port. Flight Electronics, 0703 227721.

#### Linear integrated circuits

**Low-power op amp.** The Max406 op amp has a  $1\mu$ A quiescent current that is relatively constant over the entire supply range in unity gain stable and high-speed operating modes. The output can source 2mA when powered by a 9V battery and smaller loads with a supply down to 2.5V. Common-mode input voltage range extends from the negative rail to within 1.1V of the positive supply. The output stage swings from rail to rail. Input offset voltage is specified at 0.5mV maximum and input bias current is less than 0.1pA. 2001 Electronic Components, 0483 742001.

**Clock generator.** A dual video and memory clock generator, the ICS2494, has provision for external frequency input; the internal clock stays locked when the external frequency input is selected. It has a buffered Xtal out and integral loop filter components. It works up to 135MHz and comes in a 20-pin DIP. Amega Electronics, 0256 843166.

**Op amp.** The AD745 monolithic FET-input op amp has a current noise of 6.9fA/ $\sqrt{\text{Hz}}$  at 1kHz and voltage noise with 10kHz inputs of 2.9nV/ $\sqrt{\text{Hz}}$  (4nV/ $\sqrt{\text{Hz}}$  guaranteed and tested maximum). Its 0.0002% total harmonic distortion at 1kHz makes it suitable as a preamp or current-to-voltage converter in systems with high source impedance. Bandwidth is 20MHz and slew rate 12.5V/ $\mu$ s. Analog Devices, 0932 232222.

**350V op amp.** The Apex PA41 op

amp is of linear mosfet design and can work from  $\pm 175V$  rails, drawing a quiescent current of 2mA. But it can drive 60mA continuously with no secondary breakdown problems. Slew rate is 40V/ $\mu$ s and full power bandwidth is 26kHz. It maintains unity gain operation even when driving capacitive loads up to 10nF. Microelectronics Technology, 0844 278781.

**Linear amplifier.** The Elantec EL2071 is a wide bandwidth fast settling monolithic amplifier which uses current mode feedback and is for closed loop gains of  $\pm 7$  to  $\pm 50$ . It has a 150MHz -3dB bandwidth at a gain of 20 and a 2.5ns rise and fall time for a 2V step. It consumes 15mA of supply current which reduces to 1.5mA with the disable feature on. Microelectronics Technology, 0844 278781.

**Voltage monitor ICs.** The MC34161 and 33161 are universal voltage monitor ICs for implementing over, under and window detection of positive and negative voltages. The circuit consists of two comparator channels each with hysteresis, pinned-out 2.54V reference, two open collector outputs that sink more than 10mA, and a mode select input for programming the functions of the two channels. They are fully functional from 2 to 40V for positive voltage sensing and from 4 to 40V for negative sensing. Motorola, 0908 614614.

**Memory chips**

**36bit fifo.** The LH5420 36bit fifo has two fifo buffers which operate in parallel but opposite directions for bidirectional data buffering. There is a word width select option for 9, 18 or 36 bits on one port to allow word width matching between two data buses with no extra logic needed. This means two of the units can be used as a bidirectional interface between a 64/72bit databus and a 73/64/36/32, 18/16 or 8/9bit databus. The unit is organised as 256 word  $\times 36$ bit  $\times 2$  with either 15/25, 20/30 or 25/35 access/cycle times. Sharp Electronics, +40 23775-0.

**256K eprom.** A 16bit 256K eprom is available with 45, 55, 70 and 90ns speeds and a 40ns version is due out soon. The Microchip 27HC1616 was developed for 16 and 32bit applications. There is no need for cache ram as the microprocessor can address the eprom directly. Package options include 40-lead plastic dip,

44-lead PLCC, 40-lead cerdip, and 44-lead LCC. Thame Components, 0844 261188.

**Microprocessors and controllers**  
**486 microprocessor.** The 486DX microprocessor runs at 50MHz letting it perform 50% faster than the current 33MHz version. It is compatible with MS-Dos, OS/2, Windows 3, and Unix software bases. The chip has 1.2 million transistors and has line widths of 0.8µm. Intel, 0793 696000.

#### Optical devices

**Laser diode.** The HL7851G is a 785nm laser diode for use in optical disc memory systems. It has a multiple quantum well structure and an output power of 50mW. Because it uses shorter wavelength visible rather than infra-red beams, smaller pits can be used in the disc increasing the recording density. Typical threshold current is 60mA and typical operating current 160mA. Hitachi Europe, 0628 585000.


#### Oscillators

**Clock oscillator.** The CS6691 is a 32.768kHz clock oscillator with a typical current consumption of 30µA. It uses discrete components to minimise power consumption and includes an H-cmos buffered output. Accuracy is ±100ppm over the range -10 to +60°C at a supply voltage of 5V DC. Rise and fall time is 10ns maximum. Total Frequency Control, 0903 740000.
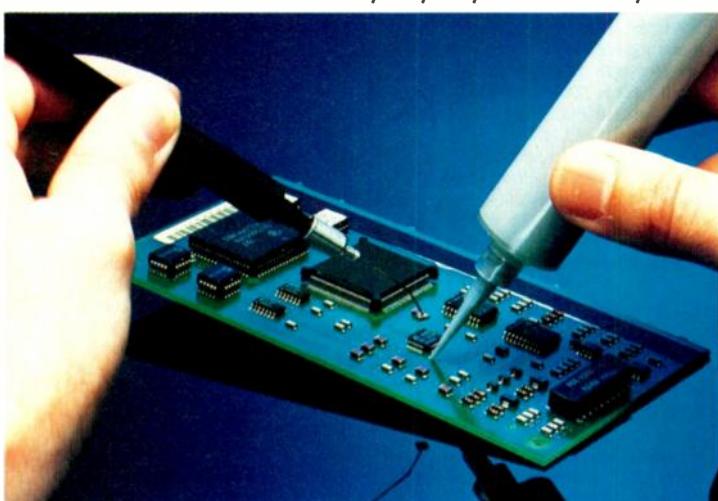
#### Power semiconductors

**Power mosfet.** A 200W 200MHz power mosfet, the 2SK1575, uses a lateral construction to give better high frequency performance. Because the substrate forms the source electrode, ground inductance is smaller than with bipolar transistors where the substrate is the collector electrode.

*Suck it and flee: the VPP803A vacuum pick up and place tool for small parts.*



The negative temperature coefficient of mosfet drain current provides protection against thermal runaway. A drain-source withstand voltage of more than 180V can be achieved, allowing circuit designs to be based on a supply of 80 to 90V. Typical drain efficiency is 55%. Hitachi Europe, 0628 585000.

**SM transistors.** A range of 50 surface mounted bipolar transistors and darlingtons dissipates up to 3W. The npn and pnp power devices in the BDS family come in SOT223 packages and work as switches and analogue drivers. Maximum collector-emitter voltages range from 32 to 120V and average collector currents are 3A (6 and 7A maximum). Maximum junction temperature is 150°C and, for ambient temperatures of 25°C, they dissipate up to 8W with an infinite heatsink. Philips Components, 071-580 6633.


## PASSIVE

#### Passive components

**Chip resistors.** CR10, CR21 and CR32 thick-film chip fixed resistors for surface mount assembly are available in bulk or tape packing with tolerances down to ±1%. The CRA3A has three resistors in an 1206 case and the CRA2A has two resistors in an 0805 case. The resistance values can be a mix from 1kΩ to 2.2MΩ in the E12 and E24 series. Noise is from 32 to 0.32µV/V. AVX, 0252 336868.

**Thin-film resistors.** The TO220 series of 20W thin-film power resistors is suitable for surface mount or through hole applications and comes in either TO220 plastic or TO257 hermetic metal packages. Resistance range is from 1Ω to 50kΩ, resistance tolerances are 0.1 to 0.5%.

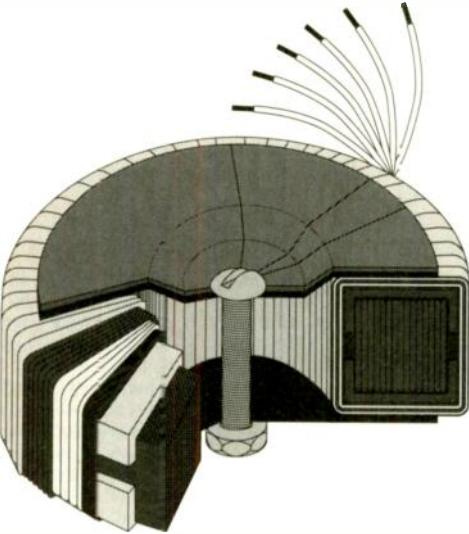**SEWEMI**  
**TRANSFORMERS**  
**COMPONENTS**  
**TRADING**



- Comprehensive standard range of high quality toroidal transformers. Competitive price and ex-stock delivery.

- In-house core manufacture allows fast and competitive custom design service for non-standard requirements —up to 3kVA.

- Low noise designs available for the most demanding audio applications.

- Triple insulation to IEC 742 on all standard transformers and where specified on custom designs.

- All types of toroid power transformers supplied —low profile, potted centres, cased, auto transformers, control gear, lighting and others.

**UK and overseas distributorships are available**

**Telephone or fax for details**

**QELP®**  
**ELECTRONICS LTD.**

**COTTON ROAD • WINCHEAP  
 CANTERBURY • KENT CT1 3RB**

**Telephone: (0227) 454778  
 Facsimile: (0227) 450507**

**CIRCLE NO. 139 ON REPLY CARD**

absolute, ratio tolerances are from 0.01 to 0.1% and low TCR to  $\pm 10\text{ppm}/^\circ\text{C}$  absolute and  $1\text{ppm}/^\circ\text{C}$  ratio. Stability is 250ppm after 1000h at  $70^\circ\text{C}$ . Electro-Films (Europe), 0784 246273.

**Wirewound resistors.** The K2 series of miniature wirewound resistors comprises 2.5W units with a 3.8mm diameter and 8.9mm length. Values are from  $50\text{m}\Omega$  to  $1\text{k}\Omega$  and standard 5% tolerance with options down to 2 or 1%. Construction is entirely welded while the coating is flame-proof and can withstand most cleaning solvents. They are available taped or in bulk. Meggett Electronic, 0793 611666.

**Ceramic capacitors.** A series of radial leaded ceramic capacitors covers the range 1 to 47,000pF in a uniform 3.5mm diameter format. The DD003 units have a maximum inserted height of 6mm and maximum thickness of 2.5mm. They come with a choice of dielectrics including temperature compensating Class 1 types and high-K Class 2 types. Most are rated at 50V DC but the high-K units also come in 12, 16 and 25V DC versions. Lead types can be straight, low profile or crimp. Murata Electronics, 0252 811666.

**Electrolytic capacitors.** MJ ultra-miniature electrolytic capacitors are 5.2mm high and work from -40 to  $+85^\circ\text{C}$ . Capacitances are from 0.1 to  $220\mu\text{F} \pm 20\%$  tolerance and working voltages are from 4 to 50V DC. The radial lead units have a leakage current of  $3\mu\text{A}$  and an allowable ripple at  $85^\circ\text{C}$  of 96mA maximum. Nichicon (Europe), 0276 685393.

**Electrolytic capacitors.** The AML138 range of axial miniature long-life electrolytic capacitors has

*Low profile: AMP SIMM connectors protect your modules while you're changing.*



specifications similar to DIN41257 but in cases 60% of the volume. This means that CV products up to  $2200\mu\text{F}$  16V are available on tape for automatic insertion. Mounting height is between 6.3 and 21mm and life is more than 20 years at  $40^\circ\text{C}$ . There are more than 100 units in the range with values between 0.22 and  $15,000\mu\text{F}$ . Rated voltage is from 6.3 to 100V. Philips Components, 071 580 6633.

### Connectors and cabling

**Fibre optic connector.** A fibre optic cable connector which can be assembled in five minutes obviates the need for the contact face to be polished. It consists of a stainless steel ferrule containing a glass capillary within which a short length of fibre is secured by epoxy resin and precisely centred using trimming techniques. Because the contact face of the ferrule and fibre is already polished, it is only necessary to splice the fibre mechanically in the ferrule with the cable to be terminated. Hakuto International, 0992 769090.

**SIMM connector.** The Amp Micro-Edge SIMM connector for leadless single in-line memory modules has a low-profile high-pressure tin-plated contact which accepts standard module board thicknesses between 1.19 and 1.37mm. The connector wipes the board pad during card installation and provides a minimum normal contact force of 200g. Jermyn Distribution, 0732 740100.

**All-weather terminals.** Terminal assemblies that are impervious to corrosion at the crimp have been designed by combining shrinkable tubing and Molex Perma-seal crimp technologies. The terminals and

pieces are pre-insulated but instead of using pieces with moulded or extruded insulations, these terminals have insulators made of nylon dual wall shrink tubing. Time 24, 0403 864947.

### Displays

**5mm leds.** A range of 5mm diameter leds are fitted with an internal resistor which eliminates the need to wire a current limiting or direct drive resistor to a PCB. At an ambient temperature of  $25^\circ\text{C}$  and operating at 5V, the red leds have a typical luminous intensity of 4.5mcd at 10mA forward current. They are also available in green and yellow. Camden Electronics, 0727 864437.

**Filters Solder-in filter.** A solder-in filter has a maximum installation temperature of  $400^\circ\text{C}$  and comes in an hermetic package with glass-to-metal seals at both ends. Operating temperature range is -55 to  $+200^\circ\text{C}$ . The high installation temperature is designed to get round problems caused when there is, say, an array of 40 to 50 filters in a bulkhead. With lower temperature ratings not all the filters will solder perfectly and the whole assembly usually has to be reflowed twice causing unreliable solder joints. AVX, 0252 336868.

**Tracking filter IC.** The IMP42C555-30 is a 30MHz programmable tracking filter with asymmetrical pulse slimming and phase equalisation. Applications include disc drives, video processing, networking and data acquisition. In disc drives using zoned density recording, the chip's automatic zone tracking feature lets zones be switched or unlimited zones added without external components or reprogramming. It also allows programming corner frequencies between 3 and 30MHz unboosted. It comes in 16-pin SOIC and DIL packages. Dialog Semiconductor, 0793 875327.

**SM filter.** The NFM52R surface mounting filter is available in four versions with cut-off frequencies of 10, 20, 50 or 100MHz. Maximum attenuation is 60dB and all types are rated at 50V and 200mA. They are housed in ceramic packages measuring 5 x 2.5 x 3mm and are suitable for flow and reflow soldering. They can be supplied in bulk or taped and reeled for automatic placement. Murata Electronics, 0252 811666.

### Instrumentation

**Bus monitor/tester.** Designed for fault finding on the IEEE 488bus and as a programming aid for GPIB devices, the Mini 488 bus monitor and tester has four modes of operation - tristate, slow, fast, and single stop. Each mode provides a different level of access to data on the GPIB bus. It

has an alphanumeric display that can be hexadecimal or binary and LEDs to indicate the state of each handshake and control line. An SRQ button simulates a service request. Amplicon Liveline, 0273 608331.

**Digital multimeter.** The Q19001 10A digital multimeter has a 0.7% basic accuracy. Measurement ranges are:  $200\mu\text{A}$  to 2A (plus 10A on a separate terminal) over six ranges; 200mV to 1kV DC over five ranges; 200 to 750V AC over two ranges; and  $200\Omega$  to  $2M\Omega$  over five ranges. The display is a 3.5 digit LCD. Resolution is 0.1mV to 1V DC, 0.1 $\mu\text{A}$  to 10mA, 100mV to 1V AC, and  $100M\Omega$  to 1k $\Omega$ . It has a 2.8V/mA diode check and it measures 75 x 130 x 25mm. Electronic & Computer Workshop, 0376 517413.

**LCR meters.** Two LCR meters can measure R+Q, L+Q, C+R and C+D at frequencies from 100Hz to 100kHz. The SR715 has four and the SR720 five selectable measurement frequencies. Drive voltages are adjustable from 0.1 to 1V. Measurement rates of 2, 10 and 20 per second are available and up to ten measurements can be averaged to produce a single result. Fieldtech Heathrow, 081-8976446.

**Multimeter.** The Escort EDM82 multimeter is a DC and AC voltmeter, 20A ammeter, ohmmeter, diode and transistor tester, capacitance tester, frequency counter, logic probe, and continuity tester in one instrument. It has a high voltage warning detector, auto ranging and peak hold functions. Its fire retardant case measures 90 x 37 x 193mm and the unit weighs 420g. HT Electrical, 0384 288504.

**Fault finder.** The Huntron Switcher 640 is an automatic scanning and comparison unit for use with the Tracker 2000 analogue signature analyser. The Tracker isolates faulty and failing components and the Switcher automates the process by comparing the analogue signatures of a suspect component with a known good component and reporting the differences. L & M Test Services, 0280813707.

**Function generator.** Pure sine waves and built-in modulation are two attributes of the DS345 30MHz synthesised function generator. It can produce frequency, amplitude, phase, and burst modulations as well as linear and logarithmic sweeps. Users can pick sine, square, ramp, triangle or arbitrary wave shapes. Modulation trigger rate can be set from 0.001Hz to 20kHz with two digits of resolution. LambdaPhotometrics, 0582 764334.

**OTDR.** The Siemens K2300 optical time domain reflectometer (OTDR) comprises a mainframe and various plug-in modules including dual 850 and 1300nm multimode. The optional

built-in printer prints the trace and all related information in less than 30s. The standard disc drive allows trace storage. The companion Batch software package can print an entire disc of traces, including length and loss measurements. Laser Lines, 0295 267755.

**Signal generator.** The SMGL is a multipurpose signal generator covering 9kHz to 1000MHz in 1Hz steps. It delivers a power output of 2W (+33dBm) which can be attenuated in 0.1dB steps down to -118dBm. Non-harmonic spurious signals are less than -70dBc, residual FM is less than 4Hz and SSB phase noise is 144dBc at an RF of 100MHz. It has RF sweep facilities, 40 nonvolatile memory stores, and an IEEE 488.2 control interface. Rohde & Schwarz, 0252 811377.

**100 MHz oscilloscope.** The Kikusui Cor5501U digital storage and real time oscilloscope has 100MHz real time bandwidth, two channels, CRT readout, cursor measurement, comment, and ALT/MAG timebase functions, as well as a 20M sample/s rate simultaneously on both channels, acquisition and save memories of 4K word/channel, pre and post trigger, and up to x1000 horizontal magnification. A GPIB interface is optional. Telonic Instruments, 0734 786911.

#### Literature

**Product catalogue.** Amplicon's product catalogue has 288 pages and more than 40 new product families. The firm's Live Lines newsletter is included to provide a quick visual reference to some of the products in the catalogue as well as giving in-depth technical features and applications stories. Products listed include a data acquisition board, fibre optic or coaxial GPIB bus extender, GPIB interface for Mac II computers, and an input scanner and keyboard. Amplicon Lineline, 0273 608331.

**Analogue components.** A 28-page selection guide for analogue components includes charts for each product area such as op amps, isolation amplifiers, d-to-a converters and 12bit multichannel data acquisition systems. A summary of video and audio products is also provided. Some products have block diagrams to explain their operation. Burr-Brown International, 0923 33837.

**Asic range.** An asic product catalogue details the full range of ES2's services. It is divided into sections on asic design, prototypes, production parts, processes, qualification, packaging, testing, and special silicon products. Current processes are 1.7µm effective (2µm drawn), 1.1µm effective (1.5 and

1.2µm drawn) and 0.8µm effective (1µm drawn). All are based on double layer metal n-well cmos technology. The firm can also offer MIL883 compliant asics. ES2, 0344 525252.

**Asic shortform.** A 93 page shortform catalogue gives details of VLSI Technology's full asic capability including gate array, cell based functional system blocks, and microprocessor cores. The range includes a 32bit rise processor. Details of asic design tools sold by subsidiary Compass are also included. VLSI Technology, 0908 667595.

#### Production equipment

**Vacuum pick-up tool.** The VPP803A is for picking up and placing small parts such as chips and miniature components especially in surface mount applications. The vacuum can be adjusted to up to 16in of mercury. The kit comprises the vacuum pencil, three sizes of tip, five sizes of pad, and a 6ft input air hose. The control box measures 9.5 x 19 x 6.7cm. I&J Fisnar, 0101 201 796 1477.


#### Power supplies

**DC/DC converters.** Two families of DC/DC converters for circuit board mounting have been introduced. The Modupower MP7000 series is available with 3.3, 5, 12 and 15V outputs and MP9000 series units are rated at 2, 6 and 20W. Both mount onto the board with a DIP socket. Ambar Components, 0844 261144.

**DC/DC converters.** The FCI range of 1.8, 2.25 and 3W DC/DC converters is available in 16 or 24-pin packages for auto-insertion or surface mount designs. The range provides 5, 12, 24 and 48V input and single and dual outputs of 5, 9, 12 and 15V with input voltage variation of 5 or 10%. They have a fully isolated design rated at 500V and 1000MΩ. Microelectronics Technology, 0844 278781.

**Eurocard supplies.** A range of Power Technics Eurocard power supplies are 100W units that meet UL, CSA and VDE standards and take up a cassette space of 3HE/5TE. There are single, dual and triple output versions with adjustment available on each output. A power failure signal is generated for external use as well as an input inhibit facility. Efficiency is 75%. Pascall Electronics, 081 9790123.

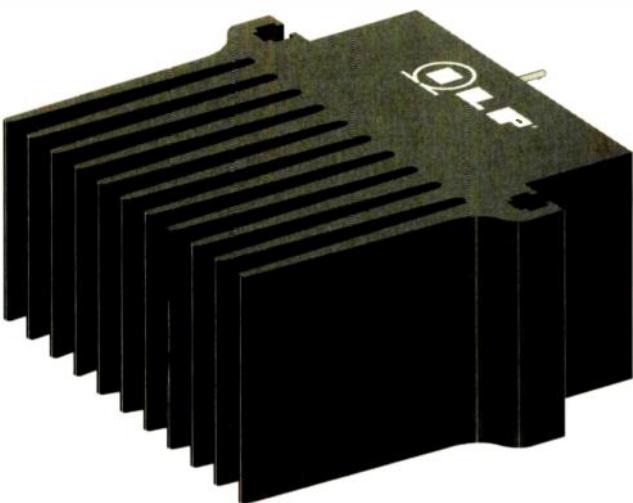**Switched mode units.** A family of configurable switched mode power supply units have outputs from 150 to 650W. Each of the 41 models in the Ferrus range can be specified to accept AC or DC inputs with various outputs to suit customer requirements. Auxiliaries providing up to six further outputs can be specified



- Fully encapsulated audio amplifier modules with integral heatsinks.



- Output powers from 15 to 180 watts.



- Cost effective for professional and hobby/enthusiast applications.



- New, latest designs available incorporating BIPOLAR, MOSFET and CLASS A technology.



- New range of pre-amplifiers now available.



**UK and overseas distributorships are available**



**Telephone or fax for details**



**ELP ELECTRONICS LTD.**

COTTON ROAD • WINCHEAP  
CANTERBURY • KENT CT1 3RB

Telephone: (0227) 454778  
Facsimile: (0227) 450507

CIRCLE NO. 140 ON REPLY CARD

as either mag amp, switching regulator, linear or semi-regulated topologies. Input scan be either 110/240V AC or 24/48V DC. Thame Power, 0844261682.

**1.5W converters.** The TPD-Hi Traco DC-DC converters are rated at 1.5W and cover three input ranges from 4.75 to 5.5V, 10.8 to 13.2V and 21.6 to 26.4V. Providing six single and six dual voltage rails, the devices are packaged in plastic cases measuring 32.8 x 20x 10.5mm and are configured for PCB mounting. I/O isolation is 4kVAC RMS. VeroSpeed, 0703 641111.

### Radio communications products

**Yagi antenna software.** The Yagi Optimizer software for antenna design has been upgraded with frequency-swept performance graphs, allowance for conductor losses and other features. Up to 50 element scan be optimised to meet user-defined criteria of gain, side-lobe suppression, VSWR and broadband performance. IFW Technical Services, 0235 535981.

**Mobile antennas.** A range of VHF and UHF mobile antennas has DuraFlex elastomer shock springs and comes with a bright finish or a black chrome. Mounts include 0.375in snap-in, 0.75in hole, magnetic, and Quick-Grip. The Antenna Specialists, 0101 216 349 8400.

### Transducers and sensors

**Ultrasonic sensors.** Selectron Lyss has introduced a range of ultrasonic sensors in M18 format which will detect targets within 600 or 1000mm depending on type. An analogue

output option is available for the 1000mm version giving a 0.1V output corresponding to the target distance. Also available is a 45 x 70 x 49mm unit with a range of 2000mm. Centiflex Systems, 0799 27602.

**Pressure transducer.** A pressure transducer has been introduced that is compatible with hydraulic fluid and can measure up to 38MPa sealed gauge. Over pressure rating of the PDPCR360 is 57MPa. The monitored pressure is denoted by the pulse repetition frequency of 0 to 10V (nominal) square-wave output at between 1.7 and 9.3kHz (0 to 38MPa). The total error band from -31 to +96°C is  $\pm 2$  to  $\pm 2.75\%$  corresponding to frequency errors of  $\pm 152$  and  $\pm 209$ Hz, respectively. Druck, 0533 314314.


### Computer-aided design

**Engineering workstation.** The MS6000 is a microform digitiser and workstation that accepts all common microfilm formats including 35mm. It can be used as a reader and printer for viewing and laser printing engineering drawings, editing and enhancing stored film images and producing copies up to A3. Images can be converted from film for storing on digital media or transferred to a computer assisted drawing system. Bell & Howell, 0784 251234.

## COMPUTER
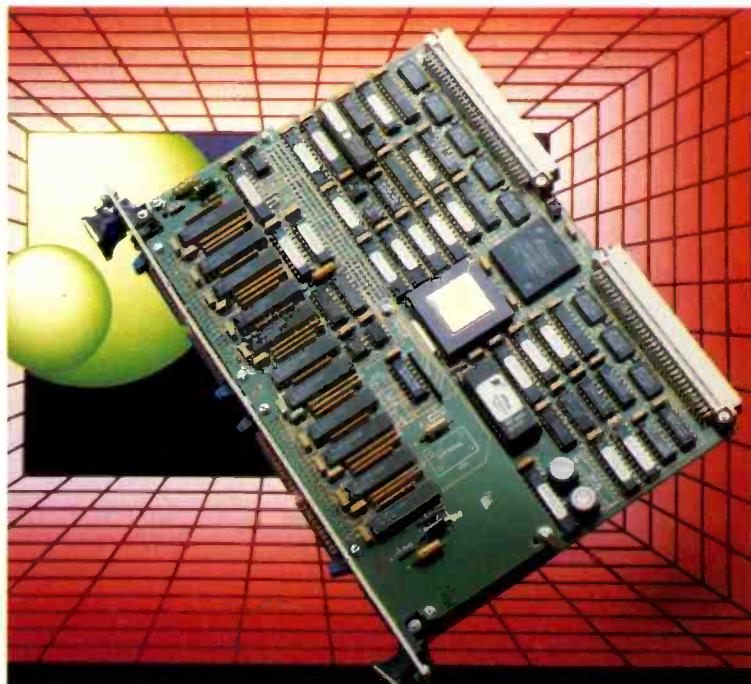
### Computer board level products

**Port boards.** Two PC/XT/AT (ISA) compatible board level products provide dual independent RS232 and



RS422/485 ports. The PC48AT has two independent serial interfaces via nine-way male D connectors. Each port is jumper selected to be RS485 full duplex, half duplex, multi-drop operation, or RS422 full duplex with RTS-CTS control lines. The PC49AT also has two independent serial interfaces, one RS232 via a 25-way D connector and one RS422/485 via a nine-way D connector. Amplicon Liveline, 0273 608331.


**Converter card.** The API36005 synchro/resolver to digital converter card plugs directly into the PC bus structure. Data can be passed to and from the instrument at rates more than an order of magnitude faster than conventional IEEE bus test systems. The card contains a broadband instrumentation-grade angle position indicator which accepts synchro/resolver signals of 11.8, 26 or 90V line-to-line and converts them to 16 or 20bit binary information. Data Device, 0635 40158.

**VMEbus interface.** A PerfTech VMEbus chassis-to-chassis interface can transfer data at up to 50Mbyte/s. The PTVM940 integrates up to 16 VMEbus systems in a parallel network. The board uses the VME64 operating mode and high speed fifos under the control of a 68020 processor to supervise the data transfer operations and execute the resident network firmware. Dean Microsystems, 0734 845155.

**Image capture card.** The MicroEye RT real time image capture card for PC based applications feeds images into a 32K buffer at frame rate and

**Boldly going:** PerfTech's VME940 can send data at 50M byte/s between systems.

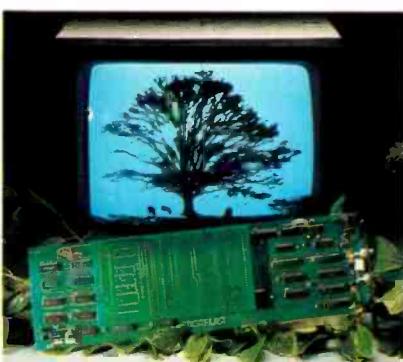**Take a peak:** MicroEye image capture system escaping from the undergrowth.



with a resolution of 512 x 512 pixels. A second 32K buffer on the card provides a graphic overlay plane. A copy plane facility lets images be transferred out of the image buffer into the graphics plane for comparison purposes. A library of C language routines is supplied. Digithurst, 0763 242955.

### Data communications

**Modems.** Two modems use the Toshiba T-slot. The MicroQuin provide asynchronous, synchronous and fax dial up speeds up to V32(9600bit/s). And the MicroQuad provides all the above except V32 but



**Heuristic:** BoardRouter emulates human characteristics to improve layout quality.

has a software upgrade facility to V32. Other standards covered include V27ter, V26bis, V22bis, V22, V23, V21, and MNP 4 and 5. They have AT autodialing and answering and a built-in SDLC synchronous adapter. Kerridge Network Systems, 0635 524155.

### Development and evaluation

**Development system.** The MPE PLD development system for GALs and PLDs integrates the logic design software and the device programmer. It also has Jedecl file support and documentation tools. The hardware consists of a PC plug-in card connected by ribbon cable to an external pod housing the zif programming socket. Three pods are available. Devices can be programmed from logic equations or from standard Jedecl files. MicroProcessor Engineering, 0703 631441.

**68040 system.** A development system for the 68040 processor consists of C compiler, C source level simulator and debugger, and assembler. They are available for PCs and compatibles, Sun 3 and 4 workstations, Apollo, HP9000, DEC station and Vax VMS computers. Code produced by the compiler and assembler can be executed and debugged by the X-ray 68K debugger, making it possible to carry out software and hardware development in parallel. Microtec Research, 0256 57551.

**Computer peripherals Keyboards.** NMB mechanical and membrane keyboards are available in two versions - the RT101 using the industry standard keyswitch layout, and the RT101+ with a large AT-style enter key. They are compatible with IBM PC, XT, AT and PS/2 systems and have a slide switch for changing between the systems. Numeric pad and cursor keys may be used simultaneously without toggling Num Lock keys. A 2m cable is provided as standard. Jermyn Distribution, 0732 740100.

**Dot matrix printers.** The IBM Personal Printer Series II is a range of dot matrix printers with flexible paper handling. It comprises the 238X and 239X printers in nine-wire narrow and 24-wire carriage formats. The control panel lets the user check the status of a print job at a glance. The standard parallel interface operates with all IBM compatible PCs and there is an optional serial interface for connection to workstations running AIX and other systems. Lexmark International, 0705 321212.

### Computer security

**Computer locks.** A range of

computer locks made to BS5750 includes units which can electronically immobilise the screen or keyboard or mechanically prevent tampering to the computer case. There are also models for security covers, storage cupboards, desk drawers and floppy disc boxes. The locks are made to individual requirements. Lowe & Fletcher, 0952 680381.

**Safe software.** The S versions of the V series processors have a security feature based around a customer-specific conversion table stored in the internal rom. Real-time conversion of every machine-code instruction on the V25S and V35S chips uses the conversion table to give protection against software piracy. The contents of the table are known only to the customer and cannot be accessed by any program, in-circuit emulator or other hardware device. NEC Electronics, 0908 691133.

### Software

**Management system.** The Atoms automated test operations management system for test and process engineers provides data management of test or process parameters. Windows 3 multi-tasking software integrates data acquisition, analysis, reporting and database functions. It is built for an IBM AT, PS/2 or compatible computer. Biodata, 061 834 6688.

**OS-9 release.** The 68040 based Version 2.4 of OS-9 is available on the CPU-30 general purpose VME single board computer, the CPU-33 68030 VMEbus entry, and the CPU-40. A range of turn-key OS-9 2.4 systems has also been introduced for industrial and desk-top use. The 2.4 release has features such as write-through disc caching to optimise disc I/O. Force Computers, 0296 625456.

**Auto-router.** The Tango-Route PRO is an auto-router for use with a 386-based PC with 387 maths coprocessor or a 486-based PC with at least 4Mbyte of ram (8Mbyte recommended). It supports most graphics adapters up to 1024 x 768. Features include non-uniform routing grids and off-grid routing to handle most board densities and combinations of design rules and pad sizes. It has true diagonal routing, net-by-net variable track widths, and copper sharing (T-routing). Pentica Systems, 0734 792101.

**PCB autorouter.** BoardRouter is an autorouter for use with the Board Maker-2 cad system for pcb design. The PC-based software combines a gridless channel routing algorithm with heuristic attributes. It can handle all parts of a pcb's circuitry including those with metric pitch such as many of the new surface mount devices. Tsien, 0223 277777.



Range of quality products for the lighting industry.

Electronic Lighting Transformers for 12 volt Tungsten Halogen lighting. 75 and 105VA types available, suitable for use with all types of dimmer.

Full custom design facility for Electronic Lighting Transformers.

Toroidal Transformers for low voltage lighting.

Electronic Ballast units

Latest Design ILP Electronic Starter—a direct replacement for outdated glowstarter switches.

UK and overseas distributorships are available


Telephone or fax for details

**QLP ELECTRONICS LTD.**

COTTON ROAD · WINCHEAP  
CANTERBURY · KENT CT1 3RB

Telephone: (0227) 454778  
Facsimile: (0227) 450507

CIRCLE NO. 141 ON REPLY CARD

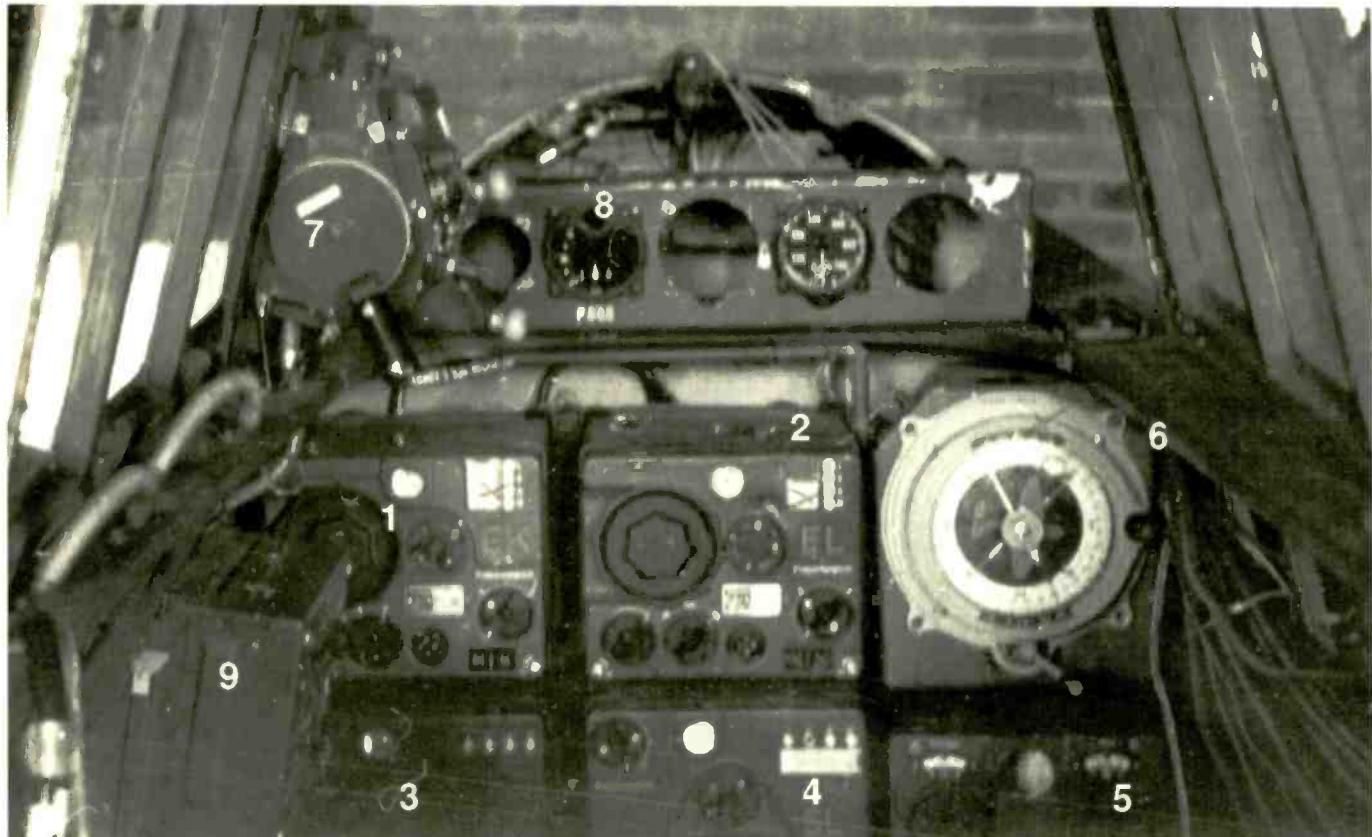

## AVIONICS — 1940s Luftwaffe style

**N**ovember 1940 issue of *Wireless World* carried an item on radio equipment which, for the time, was particularly unusual. It was an article describing equipment found in crashed German aircraft.

As the piece pointed out, the samples were not in the prime of life when received, but no time was lost in gluing them together again so that aircraft and equipment could be tested against their Allied equivalents.

In single-seat fighters such as the Messerschmitt 109, the transmitter receiver was of a fairly rudimentary type. It was continuously variable from 2.5 to 3.7MHz and was mounted behind, and out of reach of, the pilot, so that the frequency had to be preset before take-off. Range was around 35 miles.

But larger aircraft carried rather more exotic equipment. When a crew member could be spared to concentrate on radio operation in aircraft such as the ME.110, Heinkel 111 or Junkers 88, then the FuG 10 was installed — perhaps the most extensive





**Fig. 1. (top left)** Cockpit assembly of the FuG 10 in an Me110 fighter. The observer sat behind the pilot and, at least in the early days, was aircraft commander. At (1) and (2) are SW and LW receivers; (3) and (4) are the transmitters; (5) is the remote aerial matching and tuning control; (6) compass repeater and loop bearing indicator; (7) is the D/F loop control and polar diagram selector; (8) is the Lorenz blind-landing indicator and (9) the intercom amplifier panel.

**Fig. 2. (left)** Receiver unit of compact design for panel mounting. Chassis were die-cast.

**Fig. 3. (right)** Pentode receiving valve, one of only two types used throughout the equipment.

**Fig. 4. (above)** D/F loop was a frame aerial but with a massive dust-iron core. Performance was effectively that of a much larger frame, but it could fit into a small blister on the fuselage skin.

piece of equipment then in use in any air force.

FuG 10 was in four main parts and was no lightweight. It weighed well over 350lb and was compared in the WW article to a contemporary 500cc motor-bike. There were LW/SW transmitters and aerial matching unit; for navigation a D/F set with remote control for wave-change and polar diagram selection and a compass repeater (the compass was in the tail, away from magnetic components); a blind landing system of the Lorenz type first used in the mid-1930s in Germany and later adopted world-wide; and an intercom audio unit for crew intercom, to produce a side tone for CW keying, modulation for voice communication and pulses for ground-based D/F.

In pre-war and early war-time days, the Beobachter or observer was commander of the aircraft and operated D/F and communications gear. But as the war went on losses mounted and the observer/commanders, who were very experienced ex-pilots, were pressed into service as pilots again and the pilot became responsible for command and navigation. Hastily trained personnel had to map-read and use the D/F system. They sat next to the



pilot (no dual controls) and had no table to work on – as was the case in the RAF. This meant that the FuG 10 operational parts had to be mounted on the dash, although its generator, D/F loop, blind-landing receivers and aerial matching were elsewhere. An extremely compact, modular design was adopted, as the picture shows.

There were only two kinds of valve in the whole arrangement: a type RV12P pentode receiving type, usable as triode, mixer etc, with side contacts and a ring seal; and a high-power transmitting valve putting out about 65W from each transmitter. ■

# Talent Computers

## Disk

380Mb ESDI disk drive ..... £400  
52Mb 3.5" IDE disk drive ..... £170  
32Mb 3.5" RLL disk drive ..... £85  
20Mb 3.5" MFM disk drive ..... £70

## Mother Boards

386sx 20MHz 0Kb RAM ..... £160

## Video Cards

256Kb VGA card XT/AT ..... £30  
512Kb VGA card XT/AT ..... £65  
1024Kb VGA card AT ..... £100

## Disk Controllers

IDE with FD, 2S, 1P, 1G ..... £30  
ESDI WD1007A-WHA ..... £50  
8-bit RLL and MFM ..... £30

**Tel 0533-376909**  
**Fax 0533-376770**

For all your computer requirements  
call Paul on (0533) 376909

Prices exclude VAT and Postage

## Computer Systems

Quality Computers at  
affordable prices.

All computers custom built to  
your specification.

Prices start from

AT-16MHz	£430
SX-20MHz	£520
386-25MHz	£660
386-33MHz	£760

CIRCLE NO. 142 ON REPLY CARD

IN VIEW OF THE EXTREMELY  
RAPID CHANGE TAKING PLACE  
IN THE ELECTRONICS  
INDUSTRY, LARGE QUANTITIES  
OF COMPONENTS BECOME  
REDUNDANT. WE ARE CASH  
PURCHASERS OF SUCH  
MATERIALS AND WOULD  
APPRECIATE A TELEPHONE  
CALL OR A LIST IF AVAILABLE.  
WE PAY TOP PRICES AND  
COLLECT.

**R. Henson Ltd.**

21 Lodge Lane, N. Finchley,  
London, N12 8JG.  
5 mins from Tally Ho Corner

**Telephone:**  
**081-445 2713/0749**

CIRCLE NO. 143 ON REPLY CARD

October 1991 ELECTRONICS WORLD+WIRELESS WORLD

**I**n the world of electrical retailing there's a premiere brand that has been the number one product of its kind for over a hundred years. It is a brand that changes each and every week - keeping pace with all the latest developments in the market. And it is a brand that is available direct to you from the manufacturer.



The product  
is a magazine,  
the manufacturer  
is Reed and the brand is ERT.

ERT - News and  
product information  
from around the  
world every week.

• CALL OUR HOTLINE  
NUMBER 0739 200 255  
REMEMBERING TO  
QUOTE REF. NO. ERT1

CIRCLE NO. 144 ON REPLY CARD

*"The Electrical Experiment" by Van Loo showing early investigation of the Leyden jar.*

The earliest electronic component, the capacitor, will soon be 250 years old, and despite forecasts made in the late 60s, world production of discrete capacitors has kept expanding, now exceeding over two hundred thousand million units per annum.

The first capacitor, baptised the Leyden jar, and its discharge through a human body, the Leyden experiment, are inseparably associated with the name of the Dutch physicist Pieter van Musschenbroek (1692-1761).

Without engaging in the still unsettled debate on the priority of the invention, undoubtedly most Western European scientists first learnt of the Leyden jar from the January 1746 letter of Musschenbroek to the Paris Academy of Sciences<sup>1</sup>.

The Leyden experiment was an 18th century scientific sensation. Everybody admired a long bluish spark and was surprised by "electrical commotion" resulting from a discharge of the Leyden jar through the experimenter's body. It became "painfully clear" that the Leyden jar was capable of accumulating large quantities of electricity and storing them for a long time.

**Pictures of the Leyden experiment**  
In the Arkhangelskoye Museum located in the environs of Moscow, a painting titled *The Electrical Experiment* (dated 1777) by Charles-Amadee-Philippe Van Loo (1719-1795) describes an early experiment.

Before the advent of the voltaic pile (1799), the laboratory sources of electricity constituted exclusively of machines based on frictional electrification. Such a machine

*Pieter van Musschenbroek. An engraving by J. Koubraen after the painting by J. M. Quinkhard 1738.*



## The Leyden jar enigma

*On the tercentenary of the birth of Pieter van Musschenbroek, the pioneer of Leyden experiments, Leonid N Kryzhanosky tracks the early history which led to subsequent development of the modern capacitor.*

is shown in the painting. This is a glass globe which, when rotated, is rubbed against an amalgamated leather cushion to produce an electric charge (earlier it was rubbed just against the hands of an assistant).

In the centre of the painting a girl stands on an insulating support with a rod in her left hand nearly touching the rotating globe. Sparks jump between the globe and rod. The human body as a whole is a good conductor so that the rod in her right hand is also charged. The latter rod is dipped into the water-filled glass held by the principal actor of the episode, the black boy.


The glass is the proper Leyden jar in its original form, the glass serving as the capacitor dielectric, and the water and the boy's hand, as the inner and outer electrodes, respectively (using the modern terminology). The painting shows charging of the


capacitor: the boy is going to bring his free hand closer to the rod, which will result in an electric spark jumping between the rod and his finger, and the capacitor will be discharged through his body, giving him an electric shock.
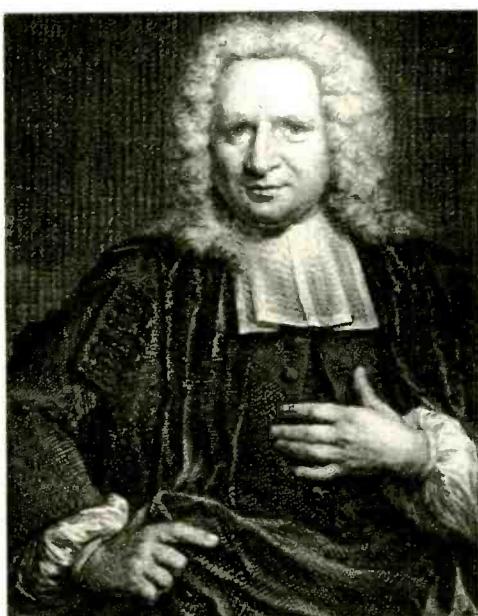
### Law of charge accumulation

Immediately after their acquaintance with the Leyden jar, researchers began to ask why it produced such amazingly strong effects (shock and spark).

It had been recognised that the larger the prime conductor, the more painful would be the sensation caused by a discharge of the prime conductor through the experimenter's body. But the Leyden jar produced much stronger effects, despite its relatively small size. Two researchers established independently in 1746 that the greater the surface



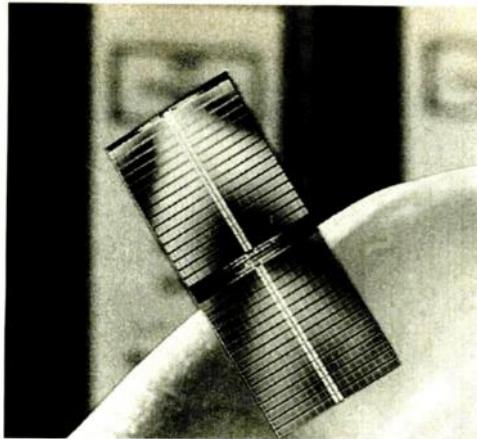

16 million capacitors on this memory chip owe their existence to van Musschenbroek

area of the electrodes and the thinner the glass, the more electricity would be accumulated by the Leyden jar.

These researchers were the British portrait painter Benjamin Wilson (1708-1788)<sup>3</sup> and Dutch professor Jean-Nicholas-Sebastien Allamand (1713-1787), of Swiss descent<sup>4</sup>. But how did they establish the above law using the then experimental techniques? The answer is a Leyden jar with both electrodes of water, the jar being filled with and immersed in water.

Such a setup is represented in a popular book by Leonhard Euler (1707-1783) published in St. Petersburg<sup>5</sup>. It allows simple variation in the geometry of the Leyden jar under investigation. The researchers used their own body as a 'sensing device'.

The same year 1746 saw the advent of metal foil coatings used as electrodes<sup>6</sup>.

#### Franklin's experiment

Benjamin Franklin (1706-1790) of Philadelphia was also captivated by "Musschenbroek's wonderful bottle". He had found, among other things, that charges equal in magnitude and of opposite sign are stored in the Leyden jar. Franklin undertook to find out where exactly the charges resid-

**Illustration from Euler's book depicting an experiment to determine the effect of stored charge in a Leyden jar of variable geometry**

ed. For this purpose, he charged the Leyden jar, then drew out the rod from it and poured the supposedly "electrified" water into an empty jar. The Leyden experiment with the new jar failed but upon filling the original jar with fresh "electrified" water, he discharged it through his body receiving a shock as if the "electrified" water had not been poured out, "which demonstrated the power to reside in glass as glass", not in the water, according to Franklin's letter of 1748<sup>7</sup>. The experiment has been described by many historians who explicitly or tacitly agree with Franklin<sup>8</sup>.

#### Addenbrooke's study

Curiously enough, a 20th century study showing that Franklin was wrong<sup>9</sup> has been ignored by many historians.

Addenbrooke built a dissectible capacitor made up of three hollow cylinders, a glass one and two metal ones, the latter fitting the former on its inside and outside, respectively. He charged the capacitor, then disassembled it carefully and brought the metal cylinders into contact with each other to discharge them should they be charged. Then he reassembled the capacitor which was found to be charged virtually to the same extent, as in Franklin's original experiment.

However, Addenbrooke did not jump to the same conclusion as Franklin. He performed a similar experiment with a paraffin-wax cylinder in lieu of the glass cylinder and obtained a result opposite to Franklin; the reassembled capacitor with known uncharged electrodes was found uncharged – the charges being found to reside on the electrodes of the capacitor.

Addenbrooke thus established that "Franklin's effect" was due to a water film which normally covers the glass. If the glass is thoroughly dried and the experiment is performed in a dry atmosphere, Franklin's

effect would not be observed.

Of course, in Franklin's experiment, ion conduction by the glass does takes place but is relatively insignificant; so is the electrical effect of glass.

Note that a possible water film on the rim of the Leyden jar does not prevent charging of the jar since the mobility of ions on the glass is low. The water film and the low mobility of ions account for a phenomenon observed by Franklin on a dissectible parallel-plate capacitor<sup>10</sup>. If we charge the capacitor, remove an electrode and touch different points at the glass surface one after another, then a spark jumps each time between the finger and glass.

In contrast, an assembled capacitor will be discharged almost completely in one touch.


The Leyden jar gained a paramount importance in wireless telegraphy in 1898 when Karl Ferdinand Braun (1850-1918) patented a transmitter in which a dipole was excited through an oscillatory circuit containing a Leyden jar – virtually the only capacitor type of the time – which substantially increased the transmitter power and hence transmission distance<sup>11</sup>.

The Leyden jar has been subsequently replaced by other capacitor types but was used in radio engineering even in the early 1940s<sup>12</sup>.

#### References

1. J.-A. Nollet. Observations sur quelques nouveaux phénomènes d'électricité. Mémoires de l'Académie Royale des Sciences (Paris), 1746, pp.2-23.
2. W. Coffeen. A Capacitor History: from Leyden Jars to Stacks. Ceramic Industry, 1974, Vol.103, No.5, pp. 32-35.
3. Joseph Priestley. "The History and Present State of Electricity, with Original Experiments". London: Dodsley, Johnson Davenport, and Cadell, 1767, p.92.
4. J.-R. Sigaud de la Fond. "Précis historique et expérimental des phénomènes électriques". Paris: Rue et Hotel Serpente, 1781, p.268.5. Leonard Euler. "Lettres à une princesse d'Allemagne sur divers sujets de physique et de philosophie", St. Petersburg, 1768, Tol.2, pp.316-320.
6. "Benjamin Franklin's Experiments: A New Edition of Franklin's Experiments and Observations on Electricity", ed. I.B.Cohen, Cambridge, Mass.: Harvard University Press, 1941, p.180.
7. Ibid., pp.191-192.8. See for example I. Bernard Cohen. "Benjamin Franklin's Science", Cambridge, Mass.: Harvard University Press, 1990, pp.25-26.
9. G. Addenbrooke. A Study of Franklin's Experiment on the Leyden Jar with Movable Coatings, Phil. Ma., 1922, Vol.43, 6th Series, pp.489-493.
10. Franklin. Op. cit., p.192.
11. F. Braun. Methoden zur Vergroßerung der Senderenergiefurdrahtlose Telegraphie (sog. Energieschaltung). Physikalische Zeitschrift, 1904, Vol.5, No.8, pp.193-199.
12. H. Nottebrock. "Kondensatoren", Berlin: Schiele & Schon, 1949, p.115.

LETTRE CXLIX pag: 32r

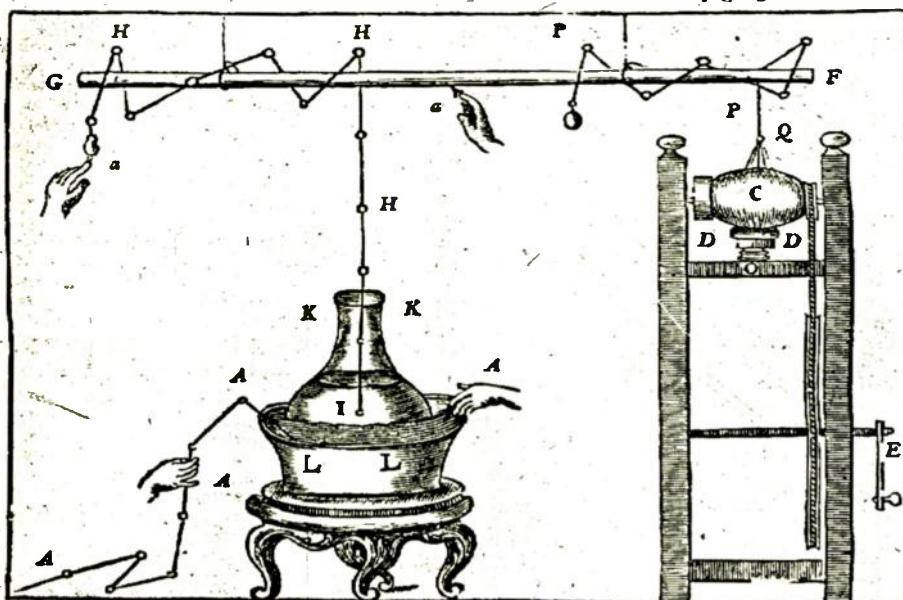

The author is with the A.S. Popov Central Museum of communications, Leningrad.



# FERN ELECTRONIC FILTERS

Fern Developments Limited, 7 Springburn Place, College Milton North,  
East Kilbride, Glasgow G74 5NU. Tel: 03552 29464. Telex: 776665. Fax: 03552 63273

## QUALITY SIGNALS FROM QUALITY PRODUCTS


### General Purpose Low Pass, High Pass & Universal Active Filter Modules

**LOW COST**

To meet the need for easily incorporated filtering elements in such as experimental rigs, test signal conditioning, servo loop modification or instrument design, Fern Developments offers a range of Active Filter Modules.

They are "ready-to-use", encapsulated, compact filter units, each containing a basic filter function and adjustable by user for cut-off or centre frequency. Adjustment is simple, generally requiring the addition of 3 or 4 external resistors, sometimes a capacitor; all in accordance with simple design equations or tables of values given in the data sheets.

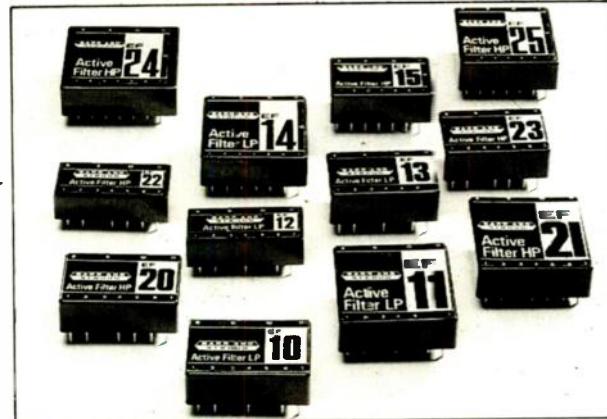All low pass and high pass filters in this range offer the choice of Bessel, Butterworth or Chebychev responses selectable by the user.



Filter reference	Mode	Attenuation rate dB/octave	Frequency setting range Hz	Price 1-OFF
EF10	Low Pass	12	1 to 300	£28.00
EF11	Low Pass	18	1 to 300	£32.00
EF12	Low Pass	12	100 to 30K	£28.00
EF13	Low Pass	18	100 to 30K	£32.00
EF14	Low Pass	24	1 to 300	£36.00
EF15	Low Pass	24	100 to 30K	£36.00
EF20	High Pass	12	1 to 300	£28.00
EF21	High Pass	18	1 to 300	£32.00
EF22	High Pass	12	100 to 30K	£28.00
EF23	High Pass	18	100 to 30K	£32.00
EF24	High Pass	24	1 to 300	£38.00
EF25	High Pass	24	100 to 30K	£38.00

Filter reference	Mode	Attenuation rate dB/octave	Frequency setting range Hz	Price
EF40	LP/HP/BP/BS (Universal)	Depending on mode selected	0.1 to 200	£34.00
EF41	LP/HP/BP/BS (Universal)	Depending on mode selected	10 to 20K	£34.00
EF42	LP/HP/BP/BS (Universal)	Depending on mode selected	100 to 200K	£38.00
EF43	LP/HP/BP/BS (Universal)	Depending on mode selected	0.001 to 100	£38.00
EF44	LP/HP/BP/BS (Universal)	Depending on mode selected	1 to 1K	£34.00
EF45	LP/HP/BP/BS (Universal)	Depending on mode selected	100 to 30K	£34.00
EF60	Low Pass/High Pass	24	0.2 to 2K (HP) 1 to 10K (LP)	£40.00
EF61	Low Pass/High Pass	24	3 to 30K	£40.00

**Volume Discounts**  
on All Models  
1-4 List Price  
5-9 Less 5%  
10-24 Less 10%  
25-99 Less 20%  
100-200 Less 30%  
200-up on Quotation

#### High Slope Active Filter Modules

##### EF 16 (ANTI-ALIAS)

This low pass module is based on a new class of monotonic passband, equal ripple stop band filter functions. Referred to as an LSM (least square monotonic) filter it provides sharp cut-off, high stop band attenuation and improved group delay response. A prime use for this module is as an anti-aliasing filter in A/D conversion applications.

- Frequency cut-off range 2Hz to 20kHz
- Minimum stop band attenuation 60dB
- Stop band attenuation roll-off 100dB/octave

##### EF 16X (POST PROCESSING)

This low pass module is intended for use as a post processing Filter, ie to follow analogue to digital conversion in a signal processing system.

Its specially shaped passband compensates for the distortion introduced during the digital to analogue conversion.

The EF 16X complements the EF 16 when the latter is used as an anti-alias Filter.

Both have the same format in terms of dimensions, pin connections, frequency range and stopband attenuation response shape.

##### EF26

This high pass filter is based on a conventional elliptic design having an equal ripple pass band, sharp cut-off and high stop band attenuation. It has many applications such as the removal of low frequency interference mains or rectifier hum from signal paths. It can be used with the EF16 to form a band pass unit. Roll-off rate is 80dB/octave, stop band attenuation 60dB and cut-off frequency range 2Hz to 20kHz.

##### Eurocard Mounted EF16, 16X and EF26

To simplify connection both filters can be supplied mounted on a standard single Eurocard fitted with a 32-way connector. The card accommodates 4 sets of frequency determining resistors which can be switched, either locally or remotely, in a binary format to provide a maximum of 15 cut-off frequency settings.

#### Voice Frequency Filters Types EF117, 118, 118A, 119

These modules are designed primarily for use as voice frequency channel filters in telecommunications. They provide separate band pass, low pass and high pass units, enabling the user to select the most cost-effective arrangement. Common specification points are an attenuation in the stop band of >40dB, with a pass band insertion loss of nominally 0dB.

Other basic specifications are:

- EF117 – Band Pass 300Hz to 3.4kHz
- EF118 – Low Pass d.c. to 3.4kHz
- EF118A – Low Pass d.c. to 1.8kHz
- EF119 – High Pass 300Hz to 50kHz

Volume Discounts  
As Above

**Price 1-4-OFF**

EF117	£58.00
EF118	£38.00
EF118A	£35.00
EF119	£30.00

# REGULARS

## APPLICATIONS



# Pressure sensing

**M**otorola produces a booklet entitled *Pressure Sensors* which, not surprisingly, is concerned with that company's range of fluid pressure sensors using piezoresistive elements to give ranges from 1.5 to 100 psi at up to 60mV full-scale output. An important part of the publication is to do with interfacing the devices, which are available as ported, assembled units or as unported elements, giving absolute, differential or gauge pressure measurements.


A number of interface circuits are shown, of both the simple type and slightly more exotic variety with more precise offset and span settings. **Figure 1** is a precision pressure-to-voltage converter using a quad op-amp, which will drive either a DVM or a microprocessor. The span is determined by the setting of  $R_g$  and offset voltage with  $R_{OFF}$ . Output is 8V at full application of pressure.

**Figure 2** is a portable manometer, using an MX2050P device to provide a scale factor of 1mV/1mm mercury. The booklet provides a method of calculating the value of  $R_g$ . Types of op-amp used are not specified, but Motorola points out that the choice must be

**Fig.1. Precision pressure-to-voltage converter using Motorola MPX2000 series of piezoresistive transducers. This is the more advanced version of two shown.**

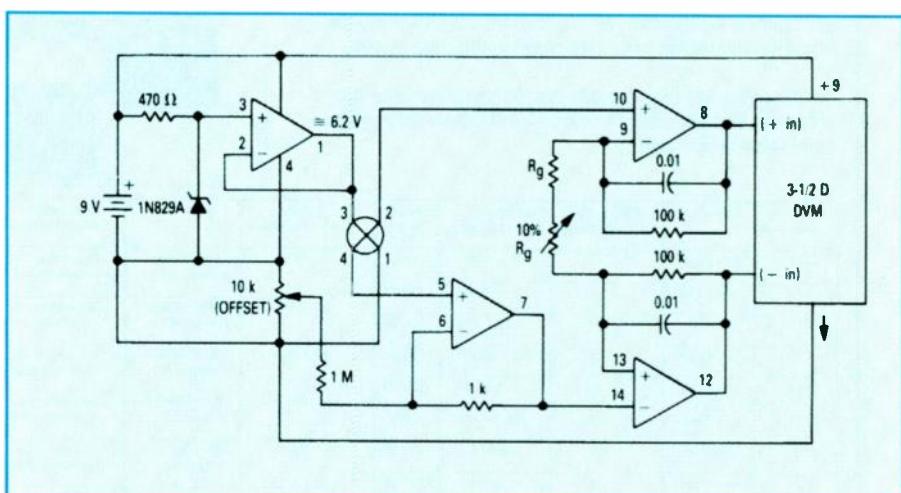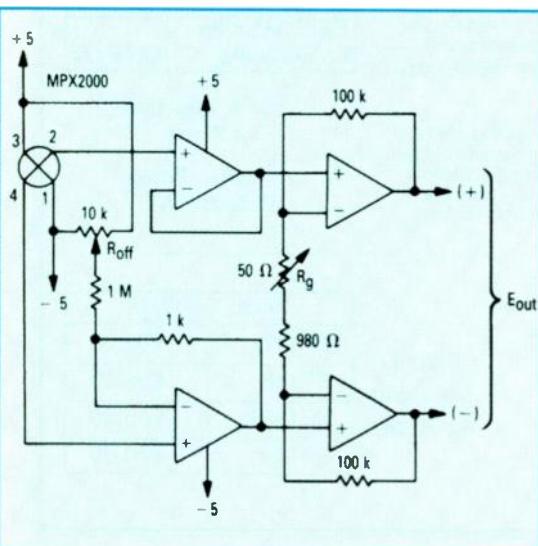

**Fig.2 Portable manometer, which presents its readings on DVM to within 0.5%.**

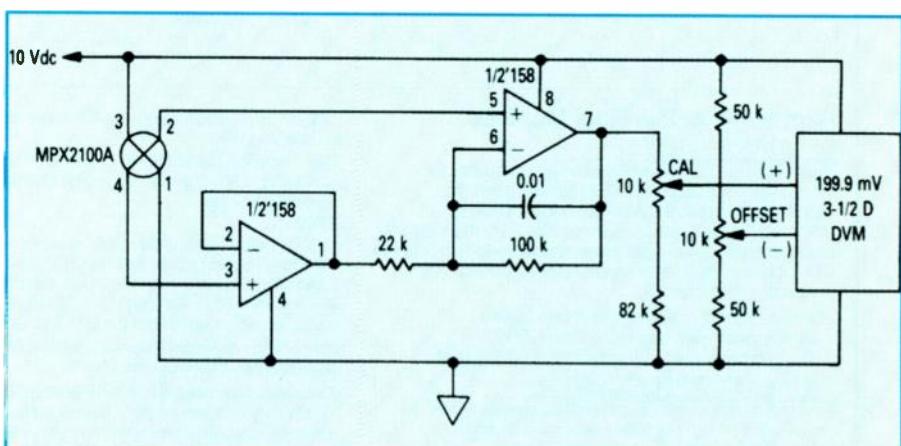

**Fig.3. Electronic barometer, displaying its readings in kilopascals on a 199.9mV DVM.**

relevant to the design aims with regard to temperature, drift and noise. For example, this manometer design offers error better than 0.5% over the normal ambient range and could easily be degraded by an unwise choice of active and passive support components.

**Figure 3** is a barometer, which displays kPa on a 199.9mV digital voltmeter. Calibration is as follows, assuming one does not have access to a vacuum pump. Record

reading and local pressure; with a change in pressure, record new pressure and reading; adjust cal so that the change in reading equals the change in pressure, repeating as necessary; adjust offset to make displayed reading equal local pressure. (100kPa = 29.529 inches mercury.)

**Motorola Ltd European Literature Centre,**  
88 Tanners Drive, Blakelands, Milton  
Keynes MK14 5BP. 0908 614614.

# Hand-held, low-cost data logger

**A**pplication Note AN175 from NEC describes a data logger that does not rely on the assistance of the usual PC, but which uses an NEC µPD75308 microcontroller to provide a very economical instrument for use in chain stores and the like.

A simple solution is shown in the diagram, in which the µPPD75308 possesses features on-chip that render it particularly suitable for the purpose. There is, for example, an LCD controller/driver; a real-time clock timer; a general-purpose 8-bit timer; interrupt controller; 32 I/O pins; and ample rom and ram.

The LCD controller drives up to 17 seven-

segment characters or eight starburst alphanumeric characters or a combination. Data storage is provided by the 8K sram, which needs 5V during data access, although since the micro works from a 2.2-6V supply, one supply will suffice.

One port is a serial comms bus, supporting half-duplex RS232C at up to 9600 baud, and four more ports form the address and control bus for memory and control operation of the Max632 voltage booster during memory access in circumstances when the micro is powered from a lower voltage.


Two ports form the memory data bus and carry key-scan lines for the keyboard. Port 1

being keyboard input on four lines with interrupt.

µPPD75308 is either masked for large-scale users or is one-time programmable for development. There are in-circuit emulators, relocatable assemblers and PC simulation.

**NEC Electronics (UK) Ltd, Cygnus House, Linford Wood Business Centre, Sunrise Parkway, Linford Wood, Milton Keynes MK14 6NP. 0908 691133.**

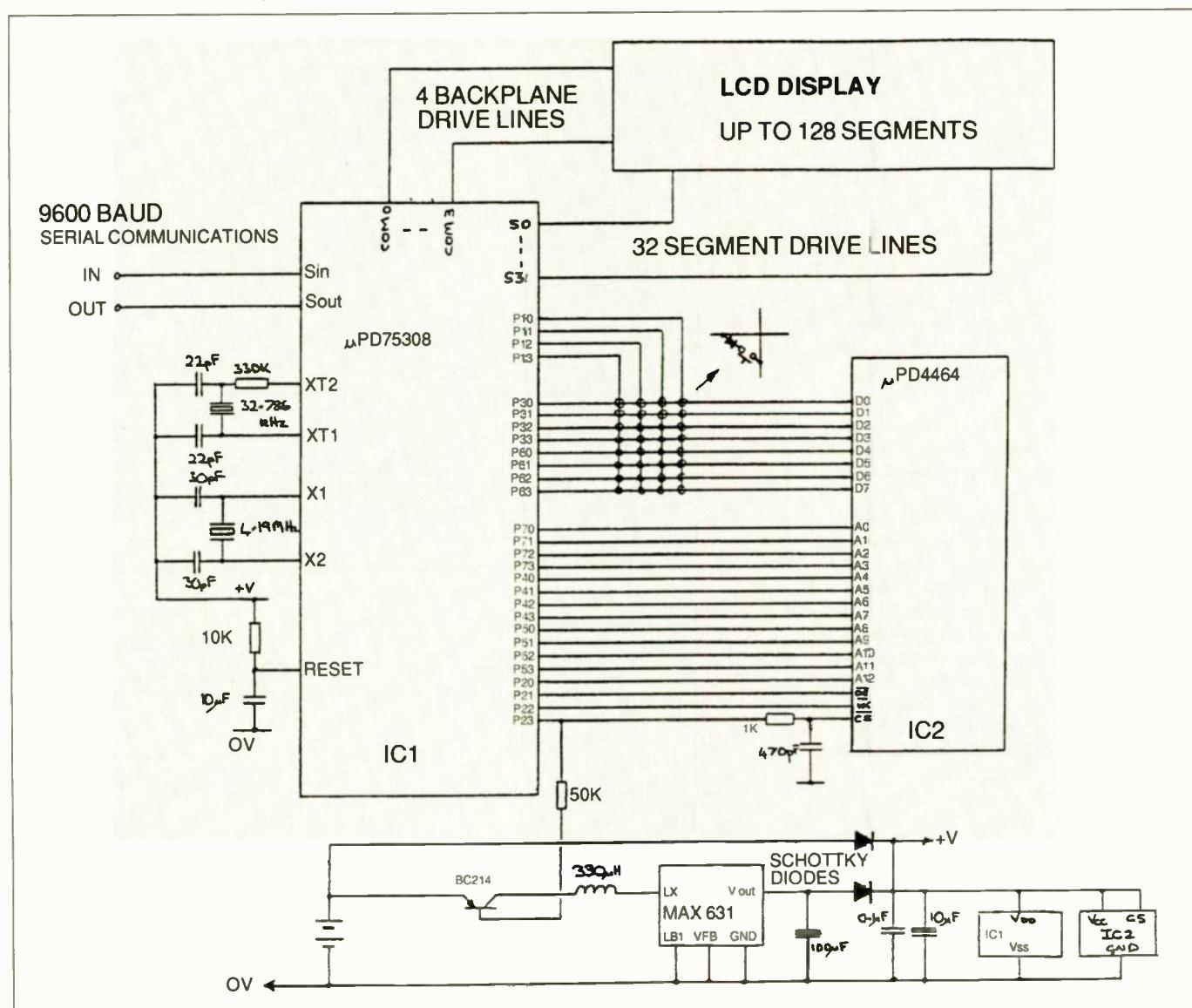
**Minimal data logger/retriever from NEC, meant for use in large stores or, perhaps, meter reading.**



# Stepper-motor driver

International Rectifier's PIH2001 hybrid power device is intended to drive stepper motors; its single in-line package contains all power and control functions to establish pulse-width modulated current control. Inputs are TTL-compatible. As a result of the use of PWM, a high motor speed is allowed, and the mosfet drivers enable high-speed chopping for better performance and a wider choice of motor.

Half a PIH2001 is shown in Fig.1. If the current in this motor phase (A) is to flow in A+, Q1 is turned on. Resistor R<sub>s</sub> senses current in the winding and feeds the control IC with the information. When the current reaches the correct level, Q<sub>1</sub> starts to chop to keep the current constant until the input

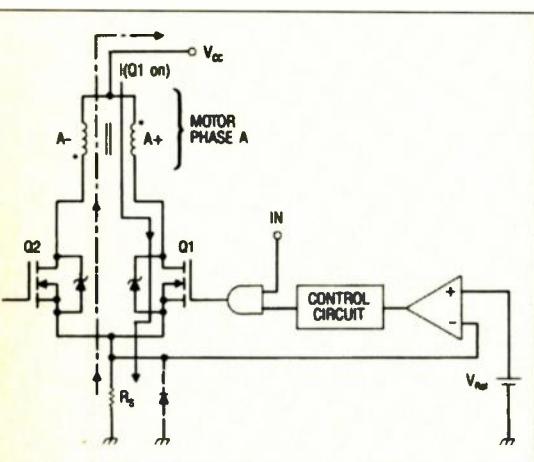

**Fig.1.** One side of the International Rectifier PIH2001 stepper motor driver/controller. Mosfets allow high-frequency chopping and an extended choice of motor.


controlling this phase (IN) changes state, Q<sub>1</sub> turns off and the other half of the device takes over in the same way. Figure 2 shows the relevant waveforms.

A practical arrangement in Fig.3. shows control circuit details; each is supplied from its own regulator. The reference voltage for the control IC inputs is obtained from the potential divider on the external regulated supply V<sub>b</sub>, which in practice is obtainable from the motor supply via a zener regulator, as can the control circuit supply if the motor supply is 30V or over. Typical values for external components are shown in Fig.4.



**International Rectifier, Hurst Green, Oxted, Surrey RH8 9BB. 0883 713215.**

**Fig.4.** Recommended component values.

**Fig.2.** Waveforms in the control circuit of half the device.

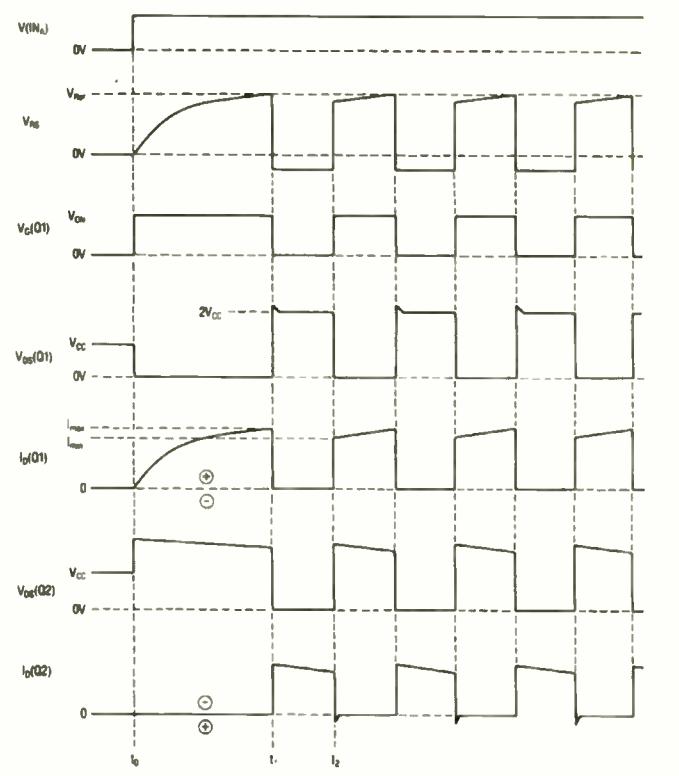

**Fig.3.** Practical details of the device in use, showing the control circuit in more detail. All active circuitry is on-chip.

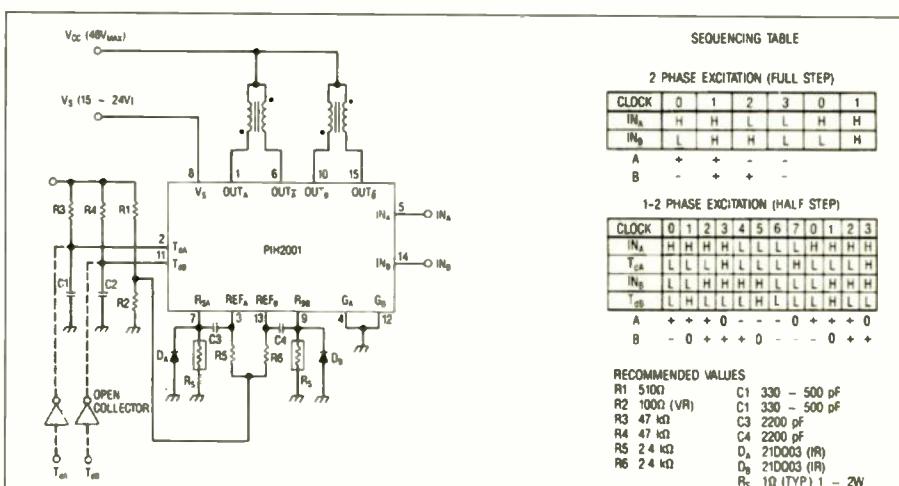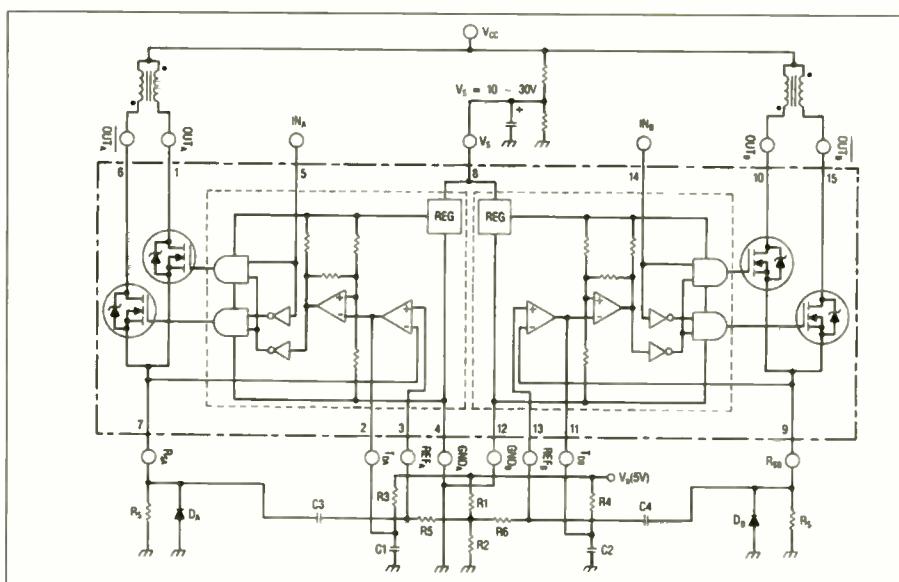

**SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK**

**Tektronix 475** - 200Mc/s oscilloscopes - tested from £400 less attachments to £500 C/W manual probes.

**Marconi TF2008** - AM-FM signal generator - Also sweeper - 10Kc/s - 510Mc/s - from £350 tested to £500 as new with manual - probe kit in wooden carrying box - £50.

**HP DC Current source type 6177C** - £200.

**HP Frequency comb generator type 8406A** - £400.

**HP Sampling Voltmeter** (Broadband) type 3406A - £200.

**HP Vector Voltmeter** type 8405A - £400 to £600.

**HP Synthesiser**/signal generator type 8672A - 2 to 18GHz S - £6000.

**HP Network Analyser** type 8754A + HP8502A test set - £4000.

**HP 8505A network analyser** - 500Kc/s-1.3GHz + HP8502A test set - £5500.

**HP 8640A signal generator** - OPT 001 - 002 - 5Mc/s - 1024Mc/s - £1000.

**HP Oscillographic recorder type 7404A** - 4 track - £350.

**HP Plotter** type 9872B - 4 pen - £300.

**HP Sweep Oscillators** type 8690 A & B + plug-ins from 10Mc/s to 18GHz also 18-40GHz. P.O.R.

**HP Signal Generators** type 612 - 614 - 618 - 620 - 628 - frequency from 450Mc/s to 21GHz.

**HP Network Analyser** type 8407A + 8412A + 8601A - 100Kc/s - 110Mc/s - £1000.

**HP 1811 Mainframe** £400 - HP1821 Mainframe £500 - HP141T Mainframe £500-£1000.

**HP 432A-435A or B Power Meters** + Powerheads - 10Mc/s - 40GHz - £200-£650.

**HP Down Converter** type 11710B - 0.1-11Mc/s - £450.

**HP Pulse Modulator** type 11720A - 2-18GHz - £1000.

**HP Modulator** type 8403A - £100-£200.

**HP Modulators** for above-many different frequencies - £150.

**HP Power Meter** type 435A (no head) - £150.

**HP Counter** type 5342A - 18GHz - LED readout - £1500.

**HP Signal Generator** type 8640B - Opt001 + 003 - 5-512Mc/s AM/FM - £1200.

**HP Spectrum Display** type 3720A £200 - HP Correlator type 3721A £150.

**HP 37555 + 3756A** - 90Mc/s Switch - £500.

**HP Amplifier** type 8447A - 1-400Mc/s £400 - HP8447F - 1-1300Mc/s £800.

**HP Frequency Counter** type 5340A - 18GHz £1000 - rear output £800.

**HP Programmable pulse generator** type 8161A - £1500.

**HP 8410 - A - B - C Network Analyser** 110Mc/s to 12GHz or 18GHz - plus most other units and displays used in this set-up - 8411A - 8412 - 8413 - 8414 - 8418 - 8740 - 8741 - 8742 - 8743 - 8746 - 8650. P.O.R.

**HP Signal Generator** type 8660C - 1-2600Mc/s. AM-FM - £3000.

**HP Signal Generator** type 8656A - 0.1-990Mc/s. AM/FM - £2250.

**HP 3730B + HP3736B** Down Converter Mainframe + 1.7GHz-4.2GHz PI - £500.

**HP Counter Mainframe** type 8345A - £400.

**HP 8699B Sweep PI** - 0.1-4GHz £750 - HP8690B Mainframe £250.

**HP Digital Voltmeter** type 3456A - £900.

**HP Multi-FX LCR Meter** type 4274A - £1750.

**HP 9000 - 216 Computer** +HP9121 Dual Disc Drive - £350.

**Racal/Dana digital multimeter** type 5001 - £250.

**Racal/Dana Interface** type 9932 - £150.

**Racal/Dana GPIB Interface** type 9934A - £100.

**Racal/Dana Timer/counter** type 9500 (9515 OPT42) - 1250Mc/s - £450.

**Racal/Dana 9301A-9303 RF Millivoltmeter** - 1.5-2GHz - £350-£750.

**Racal/Dana Counters** 9915M - 9916 - 9917 - 9921 - £150 to £450. Fitted FX standards.

**Racal/Dana Modulation Meter** type 9009 - 8Mc/s - 1.5GHz - £250.

**Racal - SG Brown Comprehensive Headset Tester** (with artificial head) Z1A200/1 - £450.

**EIN 310L RF Power Amp** - 250KHz - 110Mc/s - 50Dbs - £250.

**Adrel Signal Generator** type 7100A - 300KHz-1.3GHz - £1500.

**Marconi AF Power Meter** type 893B - £300.

**Marconi Bridge** type TF2700 - £150.

**Marconi/Saunders Signal Sources** type - 6058B - 6070A - 6055B - 6059A - 400 to 18GHz S. P.O.R.

**Marconi TF2015** Signal Generators - 10MHz - 520Mc/s - AM/FM - £250.

**Marconi TF1245** Circuit magnification meter + 1246 & 1247 Oscillators - £100-£300.

**Marconi microwave** 6600A sweep osc., mainframe with 6650 PI - 18-26.5GHz or 6651 PI - 26.5-40GHz - £1000 or PI only £600.

**Marconi distortion meter** type TF2331 - £150.

**Marconi 6700B** sweep mainframe + PI 6790A - .01-2GHz or 6738A - 1.7-4.3GHz or 6766A - .8-12.4GHz - £500.

**Thurby converter** 19 - GP - IEEE - 488 - £150.

**Philips logic multimeter** type PM2544 - £100.

**Microwave Systems MOS/3600** Microwave frequency stabilizer - 1 to 18GHzs & 18 to 40GHzs - £1000.

**Bradley Oscilloscope calibrator** type 156 - £150.

**Bradley Oscilloscope calibrator** type 192 - £500.

**Tektronix Plug-In** 7A13 - 7A14 - 7A18 - 7A24 - 7A26 - 7A11 - 7M11 - 7S11 - 7D10 - 7S12 - S1 - S2 - S6 - S52 - PG506 - SC504 - SG502 - SG503 - SG504 - DC503 - DC508 - DD501 - WR501 - DM501A - FG501A - TG501 - PG502 - DC505A - FG504 - P.O.R.

**Alltech Stoddart receiver** type 17/27A - 01-32Mc/s - £5000.

**Alltech Stoddart receiver** type 37/57 - 30-1000Mc/s - £5000.

**Alltech Stoddart receiver** type NM65T - 1 to 10GHz - £3000.

**Gould J3B Test oscillator** + manual - £200.

**Image Intensifiers** - ex MOD - tripod fitting for long range night viewing - as new - £1500-£2000.

**Don 10 Telephone Cable** - ½ mile canvas containers or wooden drum - new - MK2-3 or 4. P.O.R.

**Infra-red Binoculars** in fibre-glass carrying case - tested - £100ea. also Infra-red AFV sights - £100ea.

**B & K 2019 Analyser** - 2305 level recorder - 2425 meter - 4220 piston phones etc. P.O.R.

**ACL Field Intensity meter** receiver type SR - 209 - 6. Plugs-Ins from 5Mc/s to 4GHz - P.O.R.

**Systron Donner Counter** Model 6057 - 18GHz - £800.

**Clark Air Masts** - Heavy Duty - Type Scam - 40ft or 70ft - £200-£600.

**Tektronix 491** spectrum analyser - 1.5GHz-40GHz - as new - £1200 + manual.

**Tektronix Mainframes** - 7603 - 7623A - 7633 - 7704A - 7844 - 7904 - TM501 - TM503 - TM506 - P.O.R.

**Knott Polyskanner** WM1001 + WM5001 + WM3002 + WM4001 - £1000.

**Alltech 136 Precision test RX** + 13505 head 2 - 4GHz - £350.

**SE Lab Eight Four** - FM 4 Channel recorder - £200.

**Alltech 757 Spectrum Analyser** - 001 22GHz - Digital Storage + Readout - £5000.

**Oranet 606** Power line disturbance analyser - £500.

**Precision Aeroidot barometers** - 900-1050Mb - mechanical digit readout with electronic indicator - battery powered. Housed in polished wood carrying box - tested - £100-£200-£250. MK1, 2 or 3.

**HP8443A Tracking Generator** + Counter - 110Mc/s - £500.

**B & K Sound Level Meter** type 2206 - small - lightweight - precision - 1/2" microphone - in foam protected filled brief type carrying case with windsheild & battery + books + pistol grip handle - tested - £170. Carr: £8 - B & K 2206 Meter + Mike + Book - less carrying case etc. - £145. Carr: £8. **DISCOUNT ON QUANTITY**.

**HP 141T Spectrum Analysers**. All new colours supplied with instruction manuals.

**HP 141T-8552A** or B - 8556A - 20Hz to 300kHz £2000 A - £2200 B.

**HP 141T-8552A or B - 8555B** - 1kHz to 110Mc/s. £1800 A - £2000 B.

**HP 141T-8552A or B - 8554B** - 100kHz to 1250Mc/s. £2050 A - £2250 B.

**HP 141T-8552A or B - 8555A** - 10Mc/s to 18GHz. £3250 A - £3450 B.

**HP 141T** - old colour mainframe + 8552A; 8553B - 1kHz to 110Mc/s. Instruction manuals - £1500.

**HP 141T** - old colour mainframe + 8552A + 8553L - 1kHz-110Mc/s. Instruction manuals - £1300.

**HP 3580A LF-spectrum analyser** - 5kHz to 50kHz - LED readout - digital storage - £1600 with instruction manual or £1750 with internal rechargeable battery.

**ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. S.A.E. FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS. AVAILABILITY OR PRICE CHANGE. VAT AND CARR. EXTRA.**

**Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. No. (0274) 684007. Fax 651160.**

**CIRCLE NO. 155 ON REPLY CARD**

**HP5352B** - 40GHz counter - Liquid crystal readout with instruction manual - £5000.

**Spectrums 11 SD335 (S.A.)** realtime LF analyser - 20Hz to 50kHz - LED readout with manual - £850.

**Tektronix 7D20** plug-in 2-channel programmable digitizer - 70 Mc/s - for 7000 mainframes - £500 - manual - £50.

**Datron 1065 Auto Cal** digital multimeter with instruction manual - £750.

**Racal MA 259** FX standard. Output 100kc/s-1Mc/s-5Mc/s - Internal NiCad battery - with manual. £150.

**Tektronix 2235** 100Mc/s oscilloscope + two probes + manual £1000.

**Tektronix 2465** 300Mc/s oscilloscope + two probes + manual £1600.

**Tektronix 485** 350Mc/s oscilloscope + two probes + manual £500.

**Tektronix TR503** tracking generator - 10Mc/s to 1800Mc/s + manual - £1500.

**Tektronix 7L12** spectrum analyser 100kc/s to 1800Mc/s with manual - £1500 - for 7000 mainframe.

**Aerial array on metal plate** 9" x 9" containing 4 aerials plus Narda detector - 100-11GHz. Using N type and SMA plugs & sockets - ex eqpt - £100.

**EIP 451** microwave pulse counter 18GHz - £150.

**Marconi RF Power Amplifier** TF2175 - 1.5Mc/s to 520Mc/s with book - £100.

**HP 8614A** Signal Generator 800Mc/s to 2.4GHz - old colour - £300. New colour - £600.

**HP 8616A** Signal Generator 1.8GHz to 4.5GHz - old colour - £200. New colour - £400.

**HP 8620A** or 8620C Sweep Generators - £100 or £900.

**HP Sweeper** Plug-Ins. 86222B - 01 to 2.4GHz - £900 - 86290A - 2 to 18GHz - £1750 - 8626A - 12.4 to 18GHz - £600. 86240 - 2 to 8.4GHz - £600.

**Marconi 6155A** Signal Source - 1 to 2 GHz - LED readout - £600.

**Schlumberger 2741** Programmable Microwave Counter - 10Hz to 7.1GHz - £750.

**Schlumberger 2720** Programmable Universal Counter 0 to 1250Mc/s - £600.

**HP 8565A** Spectrum Analyser 10Mc/s to 22GHz - £5000.

**Rotek 610** AC-DC Calibrator - with 650 high current adaptor - £2000.

**Tracor 900A VLF/LF Receiver** - £1000.

**Tracor 527A Frequency Difference Meter** - £400.

**HP 37203A** MP-IB Extender - £150.

**Marconi TF2700** L.C.R. Bridge - £200.

**PPM 411F** Current Reference - £150.

**HP 5363B** Time Interval Probes - £150.

**Marconi B057B** Signal Source - 4.50 to 8.50 GHz - £300.

**HP 8900A** Peak Power Calibrator - £100.

**HP 5931A** AD Converter - £150.

**HP 59306A** Relay Actuator - £150.

**HP 2225CR** Thinkjet Printer - £150.

**TEK 178** Linear IC Test Fixture - £150.

**TEK 576** Calibration Fixture - 067-0597-99 - £250.

**HP 4437A** 600 Ohm Attenuator - £100.

**Marconi Signal Source** 6059A - 12-18 GHz - £400.

**HP 8006A** Word Generator - £150.

**HP 1645A** Data Error Analyser - £150.

**HP 3570A** Network Analyser - £150.

**Texscan Rotary Attenuators** - BNC/SMA 10-10-60-100DBS - £50-£150.

**HP 809C** Slotted Line Cartridges - various frequencies to 18GHz - £100 to £300.

**HP 532-536-537** Frequency Meters - various frequencies - £150-£250.

**HP 3200B** VHF Oscillator - 10MC/S-500MC/S - £200.

**B&K 1612** Bandpass Filter Set - £150.

**B&K 2425** Electronic Voltmeter - £250.

**B&K 2603** Micro Amplifier - £200.

**B&K 4220** Pistonphone & Barometer - £200.

**B&K 4712** Frequency Response Tracer with CRT - £150.

**B&K 2305** Level Recorder with ZR0005 Potentiometer - £180.

**B&K 1014** Beat Frequency Oscillator - £150.

**B&K 2010** Heterodyne Analyser - £600.

**B&K 2604** Microphone Amp (broken meter glass) - £80.

**B&K 1606** Vibration Pick-up Pre-Amp and Leads - £40.

**B&K T1.0001** Input Transformer - £10.

**B&K 2344** Potentiometer - £10.

**B&K ZR0005** Potentiometer - £40.

**B&K 2107** Frequency Analyser - £150.

**B&K 2019** Analyser - £250.

**B&K 2626** Conditioning Amp - £100.

**B&K 2871** Phase Meter.

**B&K 3921** Turntable.

**B&K 4712** Frequency Response Tracer + ZS0120.

**B&K 2307** Level Recorder + ZR0005 - £250.

**B&K 1902** Distortion Measurement Control - £150.

**B&K 8101** Hydophone - new - £500.

**B&K Ext Cables** for above - £100.

**SPECIAL END OF LINE OFFER**

**Marconi TF2008** Signal Generators 10Kc/s to 510Mc/s - AM-FM - off the pile - tested - working - £300. Not working or part-working - £20. Kit box of attachments - £25. All supplied with manual. quick test only given, working or non-working - fair looking condition - 300 only available. As new ones still available as normal, fully tested with box of attachments - £400-£500.

**Clark Scam Heavy Duty 40'** Telescopic Pneumatic Masts - retracted 7'8" - head load 40lbs - with or without supporting legs & erection kit - In bag + handbook - £200-£500.

**Clark Scam Heavy Duty 70'** Telescopic Pneumatic Masts - retracted 13'5" - head load 90lbs - with or without legs + erection kit + handbook - £500-£800.

**Texscan CATV Set Top Converter Tuner** - FX range 54MHz-450MHz output on channel 48 UHF - PAL synthesiser controlled - keypad or IR remote controller - brand new and boxed with circuits & information - not tested - £20 or two for £30 - IR control - £5.

**Racal MA4204** Encryption Unit (speech or data security scrambling) - for use with HF-VHF or field telephone equipment - solid state - alloy air sealed case - 12V DC supply - each unit can send or receive but two must be used, one to receive the other for sending, both switched to the same number selectable from rotary switches on the front panel - 512 operating codes available - brand new with book - not tested - £100 or two for £175 or four for £300.

**Racal MA4230 - MA4231** Automatic Morse Receiving and Sending System - MA4230 Automatic Morse Send - small solid state unit incorporates a full alphanumeric keyboard for entering messages which can be sent immediately or stored for 30 days - output is in Morse code 10 to 20 wpm or 8 to 16 times this speed - internal storage of up to 1000 characters, etc, contained in small alloy airtight case with book - brand new - not tested. MA4231 Automatic Morse Reader - self contained - receives Morse code from above unit or radio audio output at up to 160 words per minute by hand or automatically stores up to 912 characters - readout on unit - letter by letter - LED display or printer - VDU, etc - many adjustable speeds - ASCII or Baudot - power 11-30V DC or AC mains by MA4232 power unit with book. MA4230-MA4231+battery charger+line adaptor & book - not tested - internal battery (NiCad) may need replacing due to storage - brand new - £100. **As Above** but Arabic not English - supplied with kit to convert to English - new keyboard cover + prompts + book - line adaptor - brand new - not tested - £50.

**Army Type Morse Keys** - large quantity available - £5 plus p&p.

**Army Whip Aerials and Base** - 12' or 16' - new - £20-£25.

# DSP chip with no parallel?

**P**erformance of Texas Instruments TMS320C40 is impressive; with a 40ns cycle time it can perform 275 million operations per second with a data transfer rate of 320Mbyte/s. For calculations it can execute 25 million floating point operation per second (25Mflops).

But the innovation is an ability to configure any number of C40s into a multiprocessor array, allowing construction of a very impressive number cruncher.

## Architectural features

C40 is an enhancement of TI's C30, with common features allowing C30 object code to be executed.

The CPU has several sections (Fig. 1.) with a wealth of buses servicing each section. The multiplier performs either 32-bit integer or 40-bit floating point multiplications and the 40-bit result can be added to the contents of one of the extended precision registers (R0-R7) – all within one clock cycle (40ns).

Working in parallel with the multiplier is the arithmetic logic unit (ALU) which can act as a 32-bit barrel shifter. The normal arithmetic operations (add, subtract – fixed and floating point numbers) are performed by the ALU along with the standard logical operations (AND, OR and EOR). Two auxiliary register arithmetic units (araus) in the CPU can generate two simultaneous addresses with the necessary displacement, indexing, circular or bit-reversal addressing options.

Again these operate in parallel with the multiplier and ALU.

Address space of the C40 is 4Gigabits and most of this can be occupied by 32-bit external memory.

On-chip memory is partitioned into four sections; a 128 32-bit word cache, 2K of 32-bit words of ram in Blocks 0 & 1 and 4K of 32-bit rom. External memory of the C40 is mapped by either the local address bus or the global address bus. In a multiprocessor system each processor will need its own local memory and shared global memory which can be accessed by the other processors in the system.


As part of the general CPU architecture there is a primary register file containing 32 registers and an expansion register file consisting of two registers for coping with inter-

**Parallel processing through six parallel 8-bit communication ports makes the TMS320C40 a landmark in chip development says Allen Brown**

rupts. As part of the primary register file there are twelve extended precision, 40-bit registers designed to maintain extended floating point precision. In the normal sense of a microprocessor these act as accumulators.

Eight auxiliary 32-bit registers (AR0-AR7) support a variety of addressing modes and are used to generate a 32-bit address for local or global memory.

Remaining registers support other system functions such as stack management, processor status, interrupt management, block

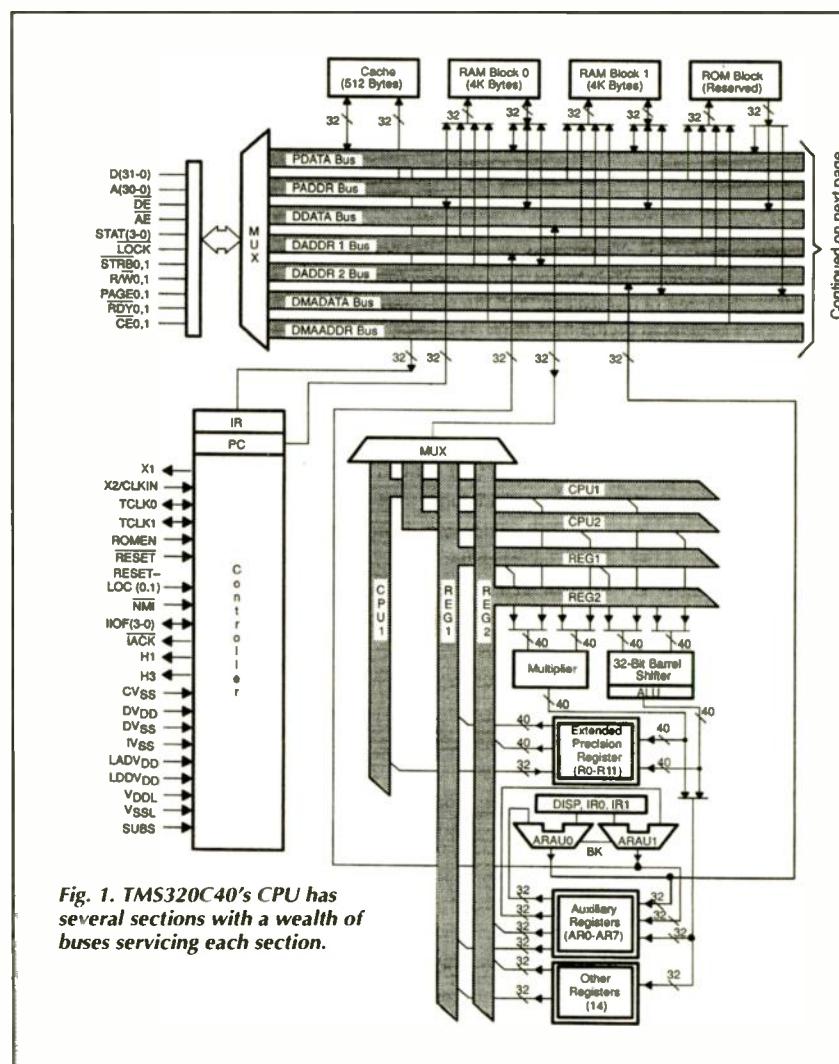

**Fig. 1. TMS320C40's CPU has several sections with a wealth of buses servicing each section.**

instruction repeats and various addressing modes. The components in the CPU are serviced by two 32-bit register buses (REG1 & 2) and two 40-bit CPU buses (CPU1 & CPU2), enabling the CPU to achieve a very high degree of parallelism – one of the principal attributes of the C40.

#### Peripheral bus memory map

All internal peripherals are controlled by a set of registers mapped into the device's memory map in a peripheral bus memory map. The left hand side of Fig. 1. shows peripherals, consisting of the six 8-bit parallel, bi-directional communication ports and two timers. The peripheral module is serviced by an extraordinary wealth of the 32-bit buses: an interesting feature is the facility for concurrent data transfer via the DMA.

Data movement and its potential bottleneck has been tackled by including a dedicated coprocessor for controlling DMA operations through eight channels. The coprocessor can access all memory locations in processor address space.

Six communication ports provide efficient processor-to-processor data transfer and enable a closely coupled system to be realised.

```

DISASSEMBLY
main: Invalid address
      PUSH AR3
      LD1 SP,AR3
      LDF 0.03,R0
      STF R0,<+2
      LDF aic_command
      STF R1,<+4
      LDF @08:6H,R2
      STF R2,<+6

main()
{
    /* Input data and perform autocorrelation */
    x[1][0] = 0.000000;
    x[2][0] = 0.587785;
}

63 Symbols loaded
Done

```

CPU

00000000	00000000	00000000
00000014	00000000	00000000
07608000	00000000	00000000
142006bb	00000000	00000000
072108c5	00000000	00000000
142106bd	00000000	00000000
072208c6	00000000	00000000
142206bf	00000000	00000000
0f2b0000	00000000	00000000
142006bb	072108c5	142106bd
072208c6	142206bf	142206c1
142106c3	142006c5	072308c7

Fig. 2. Display of the software simulator for the TMS320C40 showing source C code and assembly language.

Each port has separate input and output fifos coupled to a port arbitrator unit – arbitration is necessary to control data buffering, handshaking and to manage the inter-processor data transfer. Ports also have their own interface and can accommodate a direct transfer rate of 20Mbytes/s without the need of additional logic. Arbitration is performed automatically to ensure synchronisation between system processors.

#### Support tools

Software and hardware support includes a C compiler, a cross assembler, linker, software simulator, a XDS510 in-circuit emulator and an evaluation board hosting four C40s.

Software tools are compatible with operating systems such as VMS, Sun OS, MS-dos and for Macintosh with MPW. The C compiler conforms to the Kernighan and Ritchie standard and the software simulator has a window configuration (Fig. 2).

Usefully, the simulator can single step code while simultaneously displaying the C source code together with the assembly language code. The real-time operating system for digital signal processors, Spox, is also available.


#### New applications

C40's provision for multiprocessor design, with its six communication channels, is ideal for realising a variety of topologies including hexagonal grid (honeycomb structure), 4-D hypercube and hex star.

New areas of application for C40s span advanced image processing (techniques such as maximum entropy spectral estimation), multichannel cross-correlation analysis and array processing for signals from microwave sources.

Similarity between the C40 and the new version of the Transputer (T9000) has not gone unnoticed and some projects are currently in design which include a mix of T9000s and C40s.

Continued from previous page

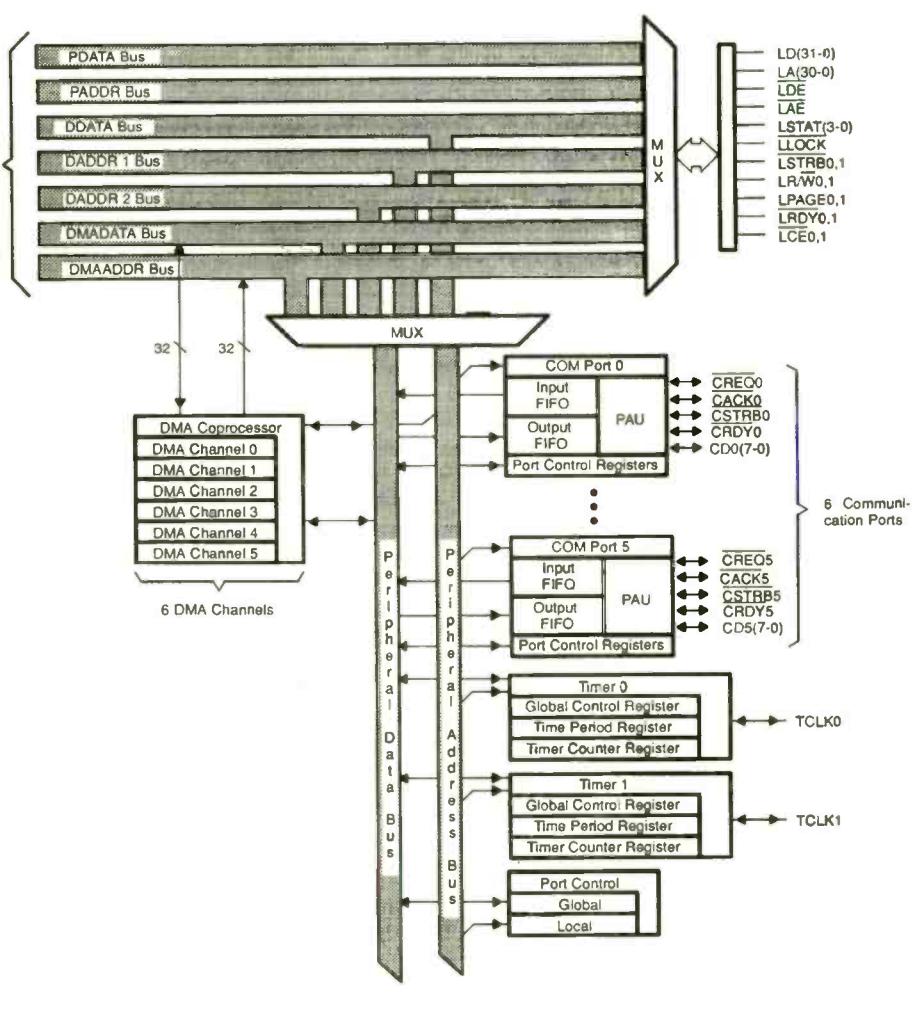

**S**uccess of the first live demonstration of digital audio broadcasting (dab) in the UK has been so dramatic that BBC engineers are now stuck with a problem. They have effectively proved the inadequacy of FM broadcasting.

As a result of the demonstration, given by the BBC in Birmingham during the Radio Academy's annual Radio Festival, the current game plan (though "not a BBC commitment") is to press ahead for a public dab service as soon as possible.

Privately the BBC has doubts about the practicality of transmitting dab signals from satellites and allocation of suitable frequencies. So the corporation will now ask the government for a slice of VHF band for terrestrial transmission.

For quite different reasons, US broadcasters also want to use the dab system for terrestrial broadcasting. They fear that the wide coverage of a satellite system would spoil business for local radio stations, which rely on local advertising.

This puts the BBC and US out of line with the original thinking behind Eureka project 147, which came up with the dab technology. Until now the Eureka team, of

# All systems go for dab?

**Tests of digital audio broadcasting are producing excellent results. Can the practicalities of dab be overcome? Barry Fox and Pat Hawker investigate.**

aim was for Warc to allocate an international band of frequencies in the 1.5GHz band (see box). But the UK government now seems keener on 2.5GHz. Hence the BBC's decision to forget about satellites for the time being and go for a slice in VHF Band I, II or III - whatever is available.

Companies participating in EU-147 include electronics manufacturers AEG, Bosch, Grundig, ITT and Philips, along with broadcast and telecommunication bodies such as the BBC in Britain, the Centre National D'Etudes des Telecommunications in France and the Bundespost in Germany. The British, French, Dutch and German governments have given financial support. Germany is particularly keen to start a terrestrial service. Receivers (from German manufacturers) could be ready by 1995.

## Moving target

Existing digital audio broadcast systems (eg Nicam and DBS) all suffer from the same problem; they only work when the receiver is getting its signal direct from a satellite or terrestrial TV transmitter, via a directional aerial. Fading and multipath will kill reception, so existing systems cannot be used with moving vehicles.

Before joining the Eureka project, the BBC tried using its transmitter at Pontop Pike in County Durham to broadcast digital radio programmes to cars using a radio-only version of the Nicam TV system. The test satisfied the BBC but there was no hope of making Nicam work for car radio.

The only way to make a digital system immune from multipath is to reduce the bit rate to very low speeds, so that there are very long gaps between bits. The receiver can then recognise and reject bits which arrive in the gaps as reflections.

First step in the dab process is digital compression, using the new systems which

rely on masking; when two sounds of similar frequency exist together, the ear only hears the louder of the two. So only the louder need be coded. The original work on digital coding with masking was done five years ago by the Institute Fur Rundfunktechnik, the German radio research centre in Munich. IRT's system was called Mascam (masking-pattern adaptive sub-band coding and multiplexing).


Filters divide the full frequency range of sound into narrow sub-bands. The sound in each band is continually analysed, masking effects predicted and only the minimum number of digital bits are needed to code each band. As all ears are different, and the sounds of music are infinitely variable, there can never be a cast iron rule book to guide the computer. Philips new digital compact cassette, DCC, and Sony's Mini Disc, rely on masking coding.

Two rival systems have been proposed for dab, both derived from Mascam. The French government's radio and communications research centre in Rennes, CNET (Centre Commun d'Etudes de Telediffusion et de Telecommunications), offers Musicam (masking-pattern adaptive universal sub-band integrated coding and multiplexing). Aspec (adaptive spectral entropy coding) is a joint proposal from AT & T Bell Laboratories, Thomson Consumer Electronics, Germany's Fraunhofer Society and CNET (France's Centre Nationale d'Etudes des Telecommunications).

For the Birmingham tests the BBC was equipped to use either, and the final dab system will probably combine the best features of both.
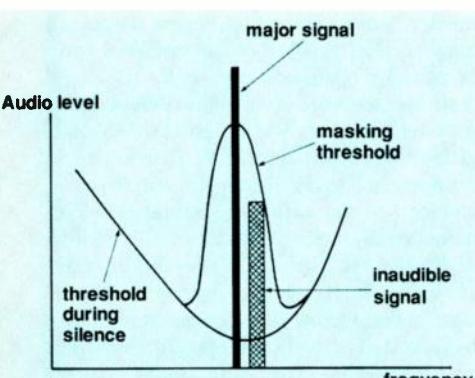
## Birmingham witnesses dab excellence

The Birmingham experiments used VHF frequencies and a terrestrial transmitter, and proved without a shadow of doubt that dab works far better than FM. BBC engineers



**Noise masking by a loud audio signal:** low amplitude sounds close in frequency to a loud signal are inaudible – and not coded in mascot dramatically reducing the number of bits required

which the BBC is the only UK member, has seen satellite transmission as an essential part of dab. This follows from the fact that dab has been under development for four years, with the investment of 360 man-years of engineer time and \$50 million, all coordinated by DLR, the Aerospace Establishment, in Cologne.

Recently there has been a rush to prove the system in time for the next World Administrative Radio Conference (Warc), to be held in Spain early next February. The

## SPECTRUM ANALYSERS



HP182C/8558B 0.1-1500MHz £2250  
HP182T/8559A 21GHz system £5000  
HPS590A 1500MHz GPIB £4000  
HPS569A 21GHz £6500

HP141T/8552B/8553B 110MHz system £2000  
HP141T/8552B/8554B 1250MHz system £2250  
ANRITSU MS62B 1700MHz analyser £9000  
MARCONI 2382/2380 400MHz system

## MARCONI INSTRUMENTS

2019A synthesized signal generator 10kHz-1040MHz £SOLD  
2091C/2092C white noise receiver/transmitter pair £1750  
2015 signal generator AM/FM 10-520MHz REDUCED £300  
2015/2171 above but with synchronizer REDUCED £450  
2177 RF amplifier 3W 40dB gain to 1GHz £950  
2356/2357 level oscillator/level meter £1000  
2380/82 400MHz spectrum analyser REDUCED £9000  
2430A 80MHz frequency counter £95  
2431A 200MHz frequency counter £110  
2501 RF power meter 0.3W DC-1GHz £150  
2503 RF power meter to 100W DC-1GHz £200  
2828A/2829 digital simulator/analyser £1500  
2833 digital in-line monitor £250  
2870 data communications tester £1000  
6460 microwave power meter with head 6421 £300  
A02805A PCM regenerator test set £750  
TF1240 Q-Meter with 1246 and 47 oscillators £500  
TF2006 FM signal generator 10-1000MHz £500  
TF2011 FM signal generator 130-180MHz REDUCED £50  
TF2013 FM signal generator 800-960MHz REDUCED £250  
TF2162 audio frequency attenuator £100  
TF2163S DC-1GHz attenuator £350  
TF2370 110MHz spectrum analyser £3250  
TF2500 audio frequency power meter REDUCED £75  
TF2600B video voltmeter 1mV-300V fstd £125  
TF2807A PCM multiplex tester £400  
TF2905/8 sine squared pulse & bar generator £275  
TF2908A blanking & sync mixer £150  
TF893A audio power meter £50  
TM4520 Inductor set £250

**URGENTLY REQUIRED —  
'HIGH-END' test Equipment  
by brand names. TOP prices paid  
for HP, TEK, MARCONI etc.  
PLEASE CALL.**

## RALFE · ELECTRONICS

36 EASTCOTE LANE, S. HARROW, MIDDLESEX HA2 8DB  
TEL: 081-422 3593. FAX: 081-423 4009

EST  
35  
YEARS



## TEST EQUIPMENT

ANRITSU MW98A/MH925A optical TDR £2500  
ANRITSU MS62B 1700MHz spectrum analyser £2250  
AVO CB154/5 electrolytic & tant' cap bridge £750  
AVO RM160/3 megohmmeter £175  
AVO RM215L-2 ac/dc breakdown tester to 12kV £695  
BRANDENBURG Alpha II 5070 R-5kV £300  
BROEL & KJAER 4416 response test unit £550  
BOONTON 102B AM/FM signal generator £1000  
FARNELL PSG520 signal generator AM/FM 10-520MHz £1000  
FARNELL AMM automatic modulation meter £325  
GIGATRONICS CU1240A signal source 0.01-4GHz £1250  
NATIONAL PV 7750A wow & flutter meter £225  
PHILIPS PM5190 synthesized function generator £950  
PHILIPS PM5534 standard pattern generator NTSC £2500  
PHILIPS PM5545 colour encoder PAL £1000  
PHILIPS PM5597 WFM modulators £250, PM5598 UHF £500  
PHILIPS PM5580/1 F. modulator £1500  
PHILIPS PM6671 120MHz counter/timer 8 digits £600  
PHILIPS PM8202 recorder with 9874/01 tempo unit £1250  
RACAL 9081 signal generator 5-520MHz synthesized £850  
RACAL 9082 signal generator 1.5-520MHz synthesized £950  
RACAL 9084 synthesized signal generator to 104MHz £650  
RACAL 9105 RF cm-wattmeter 0.02μW-200mW £250  
RACAL 9300 RMS voltmeter -80dB to +50 £275  
RACAL 9301A RF millivoltmeter £450  
RACAL Store 4-channel tape recorder £1000  
RACAL Store 7DS instrumented tape recorder £1750  
SCHAFFNER NSG200C/NSG222 mains interference gen £900  
SCHAFFNER NSG200C/NSG23A interference generator £1100  
SCHLUMBERGER 4021 mobile radio test set £1500  
SHIBASOKU 217A/33 SECAM colour bar generator £325  
TEKTRONIX 2215 60MHz oscilloscope £400  
TEKTRONIX 475A 250MHz oscilloscope £600  
TEKTRONIX 2336 ruggedized 100MHz oscilloscope £950  
TEKTRONIX SG503/PG506/TG501 calibration system £2250  
TEKTRONIX 7623A 100MHz storage scope 7853A.7A18s £1250  
TEKTRONIX 7613/TA19/B710 storage scope system £750  
TEKTRONIX 7A13, 7A26, 7853A, 7A18, 7B85, 7887 P.I. units POA  
TEKTRONIX FG504 function generator £550  
TEXSCAN VS60C 1000MHz sweep generator £1100  
TEXSCAN VS901 5MHz-2400MHz sweep generator £850  
TOA PM-30R RF volt-meter 1mV-10V fstd £250  
WAYNE KERR RA200 AF response analyser/ALM2/ADS1 £950  
YOKOGAWA 3655 analysing recorder £950  
YOKOGAWA 3061-21 6-channel chart recorder £350

## HEWLETT PACKARD



11602B transistor fixture for S-parameter test £350  
11701 frequency down-converter for 8640B £650  
1417/8552B/8554B 1250MHz spectrum analyser

£2250

£450

£450

£1750

£325

£3500

£700

£1000

£1750

£150

£250

£250

£1250

£1250

£1250

£1250

## BROADCAST

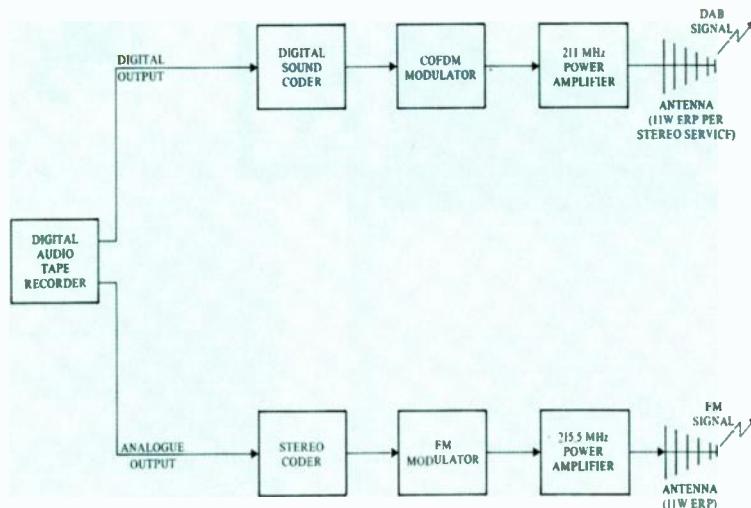**Transmitting equipment used in the Birmingham dab test: the system required just 11W of RF compared to 1kW for a comparable FM transmission.**




**Receiving equipment was installed in fifty-seater bus and allowed A/B comparison of reception quality.**

The results convinced even the most cynical engineers. All observers were particularly impressed with the resistance of dab to multipath distortion typical of standard FM transmissions.

believe that if the British government will urgently allocate a 4MHz slice in any of the three VHF bands (I, II and III), a network of low powered transmitters could, by the mid 90s, start serving the UK with twelve digital stereo radio programmes, half from the BBC and half from commercial stations.

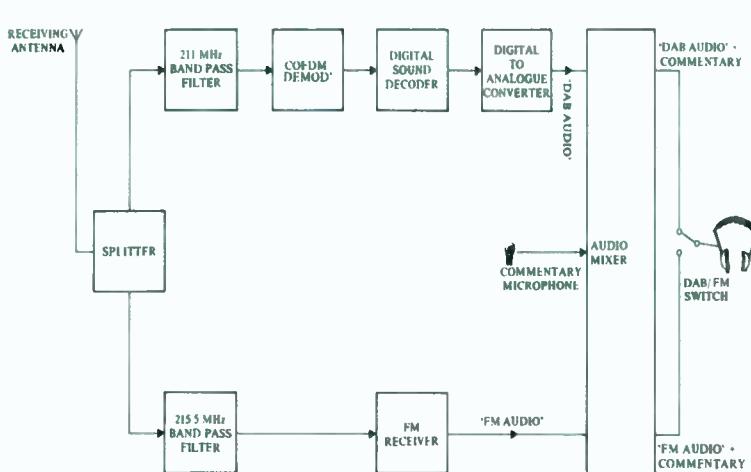The BBC put the FM and dab transmitters on the top of a building in the city centre.



Both broadcast with a power of 11W in Band III at around 215MHz. By comparison, at least 1000W is currently needed to cover a city with FM stereo.

FM stereo and dab receivers were installed in a fifty-seater bus, with audio headphones at each seat and a switch to give a direct comparison of FM and dab reception. The results surprised even hardened engineers.

As the bus toured the city centre the FM signals were frequently spoiled by hiss, flutter and pops caused by reflections of the signal from buildings and interference from cars, office computers and electronic cash registers. All the time the dab signal remained absolutely clear. It only failed briefly, when the bus went under a long underpass.

As an acid test, the BBC drove the bus radially out of town to see how far the 11W signals would carry. FM reception failed after 10km, but dab kept on working for 25km.

Tests in Band I and II will follow in London and Birmingham.

As well as being immune from interference, and carrying further, dab is also far more efficient in its use of radio spectrum. FM needs around 2.2MHz of the VHF band for each national radio stereo programme. The Birmingham tests proved that dab can reliably squeeze 12 stereo programmes in a 4MHz slice of the VHF band with a network of transmitters on the same frequency covering the whole country.

When dab broadcasting begins, the public will need to buy new receivers so FM broadcasting must continue alongside dab for decades into the future, much like the transition from 405 to 625 line TV.

The tragedy of the situation is that if dab had been ready a couple of years earlier, UK government could have allocated a 4MHz slice in Band II, to carry a mix of commercial and BBC national stations. Now the Radio Authority has been given chunks of Band II for Independent National FM Radio, which means there is no room in the band for dab. The most likely home for dab is thus Band I or III.

### Caution advised

But Michael Gerzon of the BBC has warned against standards being set too fast and early: "The Eureka researchers have had very little input from the audio industry about the practical effects of masking, and

### FREQUENCY REQUIREMENTS

Direct-satellite broadcasting still has no suitable international frequency allocation. Most engineers believe that an allocation of about 50MHz for space-broadcasting should be sought at around 1500MHz (L-Band) but there is more possibility of obtaining an allocation in the region of 2300MHz (S-Band) despite the technical and economic disadvantages of the higher frequency.

For terrestrial networks there would be advantages in reducing frequency to around 500 to 700MHz or, even better to VHF (30 to 300MHz). The private BBC tests at Croydon/Kenley-active-deflector last year (see *EW + WW*, December 1990, p.1106) used 531MHz whereas the Birmingham demonstration system (for nine stereo radio services and additional data) transmitted in a 3.5MHz bandwidth in VHF Band III

(211MHz).

The BBC's "planned operational system" would offer up to 12 stereo radio services in a 4MHz bandwidth, and, importantly, could use a single frequency for a national terrestrial VHF network.

Bands I (41 to 68MHz) and Band III (174 to 216MHz) remain international "broadcasting" frequency allocations, although closed to British broadcasters for almost a decade, except for some "ancillary" applications. Much of this 69MHz of spectrum has since been allocated in the UK for "land mobile" services, but there remain unallocated portions and it would be entirely within the competence of the Radiocommunication Agency, with DTI approval and relatively simple international co-ordination with neighbouring countries, to

re-allocate a 4MHz band to UK broadcasters.

The BBC indicated that possibly six of the 12 channels might be made available to independent Radio services although with the single frequency network (SFN) concept these would presumably need to be national rather than local services. A relatively minor objection to using such an allocation is that terrestrial dab services could not be set up identically throughout Europe where Bands I and III remain in use for television – although it would be possible even there to utilise "taboo" television channels for local dab relays. A UK SFN dab network could be fed from a "conventional" geostationary distribution satellite.

**Pat Hawker**



**ANCHOR SURPLUS LTD  
THE CATTLE MARKET  
NOTTINGHAM  
NG2 3GY**

**TEL: (0602) 864902 & 864041  
FAX: (0602) 864667**

**TEKTRONIX 7834 400MHz STORAGE SYSTEM  
c/w 2×7A19, 1×7B80, 1×7B85**

This fully tested system is complete with manuals and is fully tested with verified calibration. Mint cond: one only at

**£2350**

**TEKTRONIX 2455B 250MHz FOUR-CHAN' SCOPE**

Fully tested, calibration verified. Truly excellent "as new" condition, with manual.

**£1750**

**GOULD OS300 S1**

NEW – BOXED with manual, CCT's and two  $\times 1 \times 10$  switchable probes. Tested & calibration verified. DC–20MHz minimum.

**£230**

**Tek 475 200MHz scopes tested & cal' verified with original Tek service manual.**

Still only

**£499**

**Philips PM3217 scopes 50MHz tested & cal' verified with Philips manual.**

Still only

**£300**

**SPECIAL**

Racal Dana 9915 UHF Freq' Counters

**£195**

Racal Dana 9904M Universal Counters

**£195**

1M6 Megohmmeter ( $1M\Omega$ – $10^9$ Meg $\Omega$ )

**£99**

**SPECIAL**

**Spectra 40600 Laser Alignment System.**

**£1000**

**Beautiful lens system incl. monitor**

**Metals Research Quantimet QTM System.**

**£1000**

**With acc. & cabinets, monitor etc.**

Service/User Manuals ... 1000's in stock ...  
Send 30p SAE marked *MANUALS CATALOG*

Newsletter/Stock List ... Updated monthly ... Send 30p SAE marked *NEWSLETTER*

**WE ALSO BUY YOUR TOP QUALITY SURPLUS EQUIPMENT.**

**TRY US . . . YOU WILL NOT BE DISAPPOINTED!**

**All prices plus VAT & carriage.**

**COSTS OF CAR RADIOS**

Little has been published on the cost comparisons between car radios for FM and for terrestrial-dab requiring only a simple whip antenna. Henry Price (BBC) has written: "Computer-based technology will be used in the receiver to implement the advanced digital systems needed for dab. After suitable RF filtering, the dab signal will be digitised and all the subsequent processing will be done in the digital domain.

Carriers will be demodulated using fast Fourier transform processing. The desired audio signal will be selected by altering the demodulation process rather than by modifying or changing components. As far as the listener is concerned there will be no "tuning" and the receiver will be totally "push-button".

Virtually the whole receiver will be implemented using VLSI circuits. If worldwide frequency allocations are made available for satellite-dab and agreement can be reached on a single world standard then with large scale production, the cost of receivers would be extremely low. It is very important that this technology be inexpensive and readily available if it is to be attractive to developing countries, since in many of these countries it will be cheaper to install such a dab service than a terrestrial VHF-FM network. **PH**

how it can sometimes fail unpredictably. I am worried that this system is being rushed through without adequate knowledge of how it will cope with critical sound material".

Egon Meier-Engelen, Eureka team leader at DLR, pledges that whatever compression system the Eureka team finally adopt, it will be flexible so that future developments in

coding technology can be implemented. The same receiver can cope with incoming data rates of 192, 128, 96 and 64Kbit/s.

Similarity between Musicam, Aspec and the Philips DCC and Sony MD coding systems, means that DCC and MD decks should be able to make direct digital recordings of dab signals.

**Tackling multipath**

The compressed code still streams too fast to be immune from multipath. So the Eureka dab system spreads the bits over a large number of channels of closely spaced frequency. The technique, called CODFM (coded orthogonal frequency division multiplex), was proposed by the CCETT, and is analogous to sending a digital signal down a large number of thin parallel wires, instead of a single large cable.

The Eureka plan is to group a cluster of stereo radio programmes together in a slice of the radio spectrum which, with a frequency width of 7MHz, is equivalent to a single analogue TV channel. Each sound channel is accompanied by 4Kbit/s of data.

Because the dab system is so resistant to multipath, it can also cope with the area of overlap between different transmitters operating on the same frequency. This means that a dab network can operate across the entire country on a single frequency.

Originally the plan was to put 16 stereo programmes into the 7MHz slice. But latest Eureka thinking is that it may be possible to split each 7MHz frequency slice into four separate blocks, each 1.5MHz wide, with blocks carrying up to six different stereo radio programmes. This will let neighbouring countries draw radio boundaries by broadcasting on different blocks of frequencies.

**US STRATEGY**

In the USA, the National Association of Broadcasters (NAB) representing many existing AM and FM broadcasters, has set up a dab task-force, chaired by Alan Box, and last January NAB's Radio Board of Directors unanimously adopted an eleven-point plan to implement dab for the entire radio industry. The decision represents a formal expression of a willingness to embrace new digital technology and an attempt to manage and influence that technology for the benefit of existing broadcasters.

The task force is seeking new dab spectrum and plans to establish a single dab technical standard. It will also seek to introduce dab in such a way as to minimise economic dislocation to broadcasters and also, in effect, to oppose entry of newcomers into any new satellite or terrestrial dab services. Nine American industry representatives visited Rennes, France last March to assess Eureka-147 dab technology. Apart from the Gannett representative (one of the several organisations that have been developing

alternative dab system) all agreed that Eureka-147 "met or exceeded" expectations.

The task force considers that spectrum should be found in the region of 1500MHz (L-Band) although it recognises that the FCC and some European administrations are likely to press for an allocation around 2300MHz (S-Band) at WARC-92, despite the technical and economic disadvantages of the higher band.

In the US, space could still be found for dab in unused channels in the UHF television but at present these are reserved for possible "simulcasting" of HDTV.

At Rennes, a 16-channel demonstration system operated at 794MHz with 16-watts ERP (1-watt per programme) and there were also two very low-power gap-filling relays (0.016W and 1.0W ERP). Together these covered the city of Rennes to a distance of about 15 miles. Eureka-147 dab was demonstrated for the first time in the US at NAB-91 using American UHF channel 15. Further tests at L-band are planned by the Task Force this autumn. **PH**

**MOLYNINA ORBITS**

An additional problem with direct-to-home satellite system for dab is that a geostationary satellite would not be suitable for mobile reception since it requires a "tracking" reception dish to cover the changes in direction of a moving vehicle. But the problem could be overcome by using multiple satellites in highly-elliptical (Molynina-type) orbits.

With the Molynina orbits, as used for many years by the USSR, a satellite at its apogee hovers nearly overhead its target area for some six to eight hours, permitting the use of high-gain receiving antennas pointed directly upwards. This means that a flat-panel antenna could be mounted on the vehicle roof, unaffected by the direction in which the car is moving. To provide continuous 24-hour service, four satellites in synchronous orbits would be needed. While each satellite would be capable of transmitting, say 100 stereo programmes simultaneously, serving several countries, it would take time to establish such a system and the launch and satellite costs would be substantial. For the UK, with its mature FM networks, currently being energetically promoted on BBC Radio, the VHF terrestrial SFN would seem likely to prove a more cost-effective approach, at least initially. The next step would be to agree a final specification on an international basis, particularly for the mascam-type bit rate reduction system for which there are already competing specifications. **PH**

Eureka also proposes that the signals be broadcast by satellite, with ground relays retransmitting on the same frequencies to fill in areas of shaded reception.

**Satellite requirements**

Conventional geostationary satellites are not ideal for dab. They hang too low in the sky in Northern countries. Two years ago the European Space Agency commissioned a report from British Aerospace on the use of highly elliptical inclined orbits, as pioneered by the USSR for its Molynina satellites (see box).

ESA's project is code-named Archimedes. Four spacecraft orbit the earth with each craft six hours behind the other and all following a highly elliptical path. So, like balls tossed in the air by a juggler, each spacecraft in turn rises very steeply into space over the targeted land area then falls, equally steeply, back towards the earth.

The BBC acknowledges the theory, but is not convinced that highly elliptical orbits will be ideal in practice - eg for reception inside buildings. In any case the BBC fears that disagreement over frequency allocations (and the UK's interest in 2.5GHz, which means lower signal strength on the ground because of greater atmospheric attenuation) will delay satellite dab until the next century. ■

## COMPUTER ICS

IMS1400P-45	£2
80C31 MICRO	£2
P8749H MICRO	£5
D8751H	£10
NEW 4164-15	£1
USED 41256-15	£1
USED 4164-15	60p
BBC VIDEO ULA	£10
VIDEO ULA 201647	£10 ea, 10+ £8
6845 CRT	£5
6522 PIA	£3
DM88LS120	£4.50
AY3-1015D UART	£2.50
9 x 41256-15 SIMM	£10
8 x 4164 SIP MODULE NEW	£8
HD 146818 CLOCK IC	£2
2864 EPROM	£3
27128A 250ns EPROM USED	£2 NEW £2.30
2TC1001-20Z NEW 1M EPROM	£6
FLOPPY DISC CONTROLLER CHIPS 1771	£10 ea
68000-8 PROCESSOR NEW	£6
HD6384-8	£5
ALL USED EPROMS ERASED AND BLANK CHECKED CAN BE PROGRAMMED IF DESIRED	
2716-45 USED	£2 100/£1
2732-45 USED	£2 100/£1
2764-30 USED	£2 100/£1.60
2TC256-30 USED	£2
2TC512 USED	£3.50
1702 EPROM EX EQPT	£5
2114 EX EQPT 50p 4116 EX EQPT	70p
6264-15 8K STATIC RAM	£2
SN76489AN	£3
GR281 NON VOLATILE RAM EQUIV 6116	£5
Z80A SIO-O	£1.25

## REGULATORS

78M05 5V 0.5A	7/£1
LM317H T05 CAN	£1
LM317 PLASTIC TO220 variable	£1
LM317 METAL	£2.20
7812 METAL 12V 1A	£1
7805/12/15/24/28 plastic	25p 100+ 20p 1000+ 15p
7905/12/15/24 plastic	25p 100+ 20p 1000+ 15p
CA3085 TO99 variable reg	2/£1
LM338 5A VARIABLE	£8
L387 5v 1/2A WITH RESET OUTPUT	£1 ea £50/100

## CRYSTAL OSCILLATORS

1M000 1M8432 1M000 4M000 16M000 20M500 32M0000 56M6092	£1.50 each
---	------------

## CRYSTALS

1M0 2M77 4M000 4M9152 5M0688 6M0000 8M0000 14M31818 15M000 16M000 16M5888 17M000 20M000 21M855 22M1184 49M50	£1 each
--	---------

## TRANSISTORS

BC107 BCY70 PREFORMED LEADS full spec	£1 £4/100 £30/1000
BC557, BC546B, BC238C, BC308B	£1/30 £3.50/100
POWER TRANSISTORS	
P POWER FET IRF9531 8A 60V	3/£1
N POWER FET IRF531 8A 60V	2/£1
25C1520 sim BF259	3/£1 100/£22
TIP 141/2/£1 sim TIP 112/125/42B	2/£1
TIP35B/TIP35C	£1.50
SE8301 100V 1DA DARL SIM TIP121	2/£1
PLASTIC 3055 OR 2955 equiv 50p	100/£35
2N3773 NPN 25A 160V £1.60	10/£14
2N3055H	4 for £2

## TEXTOL ZIF SOCKETS

28 WAY ZIF EX NEW EQUIPMENT	£2.50
40 WAY NEW	£5
SINGLE IN LINE 32 WAY CAN BE GANGED FOR USE WITH ANY DUAL IN LINE DEVICES . . . COUPLING SUPPLIED	2/£1.50

## CAPACITORS COMPUTER GRADE

2200µF 160V SIC SAFCO FELSIC C038	£4 (£1.20)
24,000µF 50V	£3 (£1.30)
10,000µF 100V SPRAGUE 36D	£6
TOROID 350VA 35V+35V AND 15V+15V 24VA	£12

## QUARTZ HALOGEN LAMPS

12V 50 WATT LAMP TYPE M312 . . . £1 ea HOLDERS 60p ea	
24V 150 WATTS LAMP TYPE A1/215 . . . £2.50 each	

## MISCELLANEOUS

RS232 SERIAL CABLE D25 WAY MALE CONNECTORS £5.90 ea (£1.30)	
15 FEET LONG, 15 PINS WIRED BRAID + FOIL SCREENS . . . INMAC LIST PRICE £30	
STICK ON CABINET FEET RS NO . . . £30/£1	
LEMAK EARTH LEAKAGE TRIP 35A 35mA TRIP . . . £9	
FANS 240V 120MM . . . £6 (£1.50) (OTHER VOLTAGES/SIZES USUALLY AVAILABLE)	
AMERICAN 2/3 PIN CHASSIS SOCKET . . . 2/£1	
HUMIDITY SWITCH ADJUSTABLE	£2

## KEYTRONICS

TEL. 0279-505543

FAX. 0279-757656

P O BOX 634  
BISHOPS STORTFORD  
HERTFORDSHIRE CM23 2RX

WIRE ENDED FUSES 0.25A	30/£1
NEW ULTRASONIC TRANSDUCERS 32kHz	£2/pr
12-CORE CABLE 7/0.2mm OVERALL SCREEN	70p/metre
POWERFUL SMALL CYLINDRICAL MAGNETS	3/£1
BNC 50OHM SCREENED CHASSIS SOCKET	2/£1
SMALL MICROWAVE DIODES AE1 OC1026A	2/£1
D.I.L. SWITCHES 10-WAY £1 8-WAY 80p 4/5/6-WAY 80p	
180VOLT 1WATT ZENERS also 12V & 75V	20/£1
PLASTIC EQUIPMENT CASE 9x6x1.25 WITH FRONT AND REAR PANELS CONTAINING PCB WITH EPROM	
2764-30 AND ICS 7417 LS17 LS30 LS32 LS367 7805 REG. 9-WAY D PLUG, PUSH BUTTON SWITCH, DIN SOCKET	

TXL225 8A 500V 5mA GATE	2/£1 100/£35
BTA 08-400 ISO TAB 400V 5mA GATE	90p

## CONNECTORS

D25 IDC SOCKET FUJITSU	£2
34-way card edge IDC CONNECTOR (disk drive type)	
CENTRONICS 36 WAY IDC PLUG	£2.50
CENTRONICS 36 WAY IDC SKT	£4.00
BBC TO CENTRONICS PRINTER LEAD 1.5M	£3
CENTRONICS 36 WAY PLUG SOLDER TYPE	£4
USED CENTRONICS 36W PLUG+SKT	£3

## USED D CONNECTORS price per pair

D9 60p, D15 £1.50, D25 £2, D37 £2, D50 £3.50, covers	
50p ea	

## WIRE WOUND RESISTORS

W21 or sim 2.5W 10 of one value	
R10 0R15 OR21 2R0 4R7 5R0 5R6 8R2 10R 12R 15R 18R	
20R 22R 27R 33R 47R 56R 62R 91R 120R 180R 390R	
430R 470R 680R 820R 910R 1K15 1K2 1K5 1K8 2K4 2K7	
3K3 3K0 5K0	
R05 (50 milli ohm) 1% 3W	1 for £1
W22 or sim 6W OF ONE VALUE	£1

## PHOTO DEVICES

HI BRIGHTNESS LEDs COX24 RED	5/£1
SLOTTED OPTO-SWITCH OPCOA OPB815	£1.30
2N5777	50p
TIL81 PHOTO TRANSISTOR	£1
TIL38 INFRA RED LED	5/£1
4N25, OP1225 OPTO ISOLATOR	50p
PHOTO DIODE 50p	6/£2
MEL12 (PHOTO DARLINGTON BASE n/c)	50p
LED'S RED 3 or 5 mm 12/£1	100/£6
LED'S GREEN OR YELLOW 10/£1	100/£6
FLASHING RED OR GREEN LED 5mm 50p	100/£40
HIGH SPEED MEDIUM AREA PHOTODIODE RS65-995	995/£10

## STC NTC BEAD THERMISTORS

G22 220R, G13 1K, G23 2K, G24 20K, G54 50K, G25 200K, RES 20°C DIRECTLY HEATED TYPE	£1 ea
FS22BW NTC BEAD INSIDE END OF 1" GLASS PROBE RES 20°C 200R	£1 ea
A13 DIRECTLY HEATED BEAD THERMISTOR 1k res. ideal for audio Wien Bridge Oscillator	£2 ea

## CERMET MULTI TURN PRESETS 3/4"

10R 20R 100R 200R 250R 500R 2K 2K2 2K5 5K 10K 47K 50K 100K 200K 500K 2M	50p ea
--	--------

## IC SOCKETS

6 pin 15/18 pin 12/£1 14/16 pin 10/£1 18/20 pin 7/£1 22/24/28 pin 4/£1 40 30p	
SIMM SOCKET TAKES 2X30 WAY SIMMS . . . £1	

## SOLID STATE RELAYS

40A 250V AC SOLID STATE RELAYS	£10
--------------------------------	-----

## POLYESTER/POLYCARB CAPS

100n, 220n 63V 5mm	20/£1 100/£3
1n/3n/5n/8n/2/10n 1% 63V 10mm	100/£5
10/15/22n/33n/47n/66n 10mm rad	100/£3.50
100n 250V 'radial' 10mm	100/£3
100n 600V Sprague axial 10/£1	100/£8 (£1)
2/2 160V rad 22mm, 2/2 100V rad 15mm	100/£10
10/33/47n 250V AC rated 15mm	10/£1
1µ 600V MIXED DIELECTRIC	50p ea
1/10 100V rad 15mm, 1/12 22mm rad	100/£6

## RF BITS

TRW 50watt 50ohm DUMMY LOADS	£50
TRIMMER CAPS	ALL 4/50p
SMALL 5p 2 pin mounting 5mm centres	
SMALL MULLARD 2 to 22pF	4/50p
Larger type grey 2 to 25pF black 15 to 20pF	
TRANSISTORS 2N4427	70p
FEED THRU CERAMIC CAPS 1000pF	10/£1

## MINIATURE RELAYS Suitable for RF

5 volt coil 1 pole changeover	£1
5 volt coil 2 pole changeover	£1
12 volt coil 1 pole changeover	£1

## MONOLITHIC CERAMIC CAPACITORS

10n 50V 2.5mm	100/£4.50
100n 25.5mm or 5mm	100/£3
100n ax short leads	100/£5
100n ax	



081  
661  
8469

# CLASSIFIED

081  
661  
8640



## ARTICLES FOR SALE

### VALVES AND C.R.T.s

(also Magnetrons, Klystrons, 4CX250/350)

Minimum order charge of £50 + VAT

One million valves in stock. Obsolete types a speciality! Fax or phone for quote.

Special prices for wholesale quantities.

Orders from government departments, overseas etc. most welcome.

Many other types in stock. Please enquire re any type not listed.

**CATHODE RAY TUBES** 400 different types in stock.

Please enquire if your requirements are not listed below.

3J1	POA	D10 230GM	£45.00	E723 (EEV)	POA	M28 13LG	£45.00
12CSP4	£35.00	D13 611G	£59.00	F28-130LDS	POA	M31 182GV	£45.00
1074H	£45.00	D13 630GH	£59.00	F31 12L	POA	M31 184W	£55.00
1396P	POA	D14 200GM	£75.00	LDT708	£75.00	M31 190GR	£45.00
8931 (W.H.)	POA	D16 100GH7	£65.00	M7 120W	£75.00	M31 191W	£55.00
CME82W	£7.00	DG7-5	£45.00	M14 100GM	£35.00	M31 325GH	£35.00
CME1523W	£9.50	DG7-6	£45.00	M17 151GVR	£175.00	M40 120W	£59.00
CRE1400	£29.50	DG7-32	£55.00	M23 112GV	£45.00	MV6-5 (Mu)	£50.00
D9.11UGH	£45.00	DG7-36	£55.00	M24 121GH	£55.00	SE5FP31	£45.00
CME143W	POA	DH3-91	£50.00	M24 122WA	£55.00	VLS429AG	POA

**VALVES**

Prices on application. Please enquire re any type not listed below.

A2426	ECC804 Maz	M8136 Mul	VLS631	6Bj6
A2521	ECC81	M8162 Mul	Z759	6BM6
C1149-1	ECC81 Spec Q	M513B	Z803U	6CH6
C1166	ECC82	Magnetrone	Y644	6CJ6
CCS1	ECC82 Spec Q	PC900	1B35A	6F33
CV TYPES. Many in stock. Not all listed below.	ECC83	PCC89	2K25	6L6GC
Please inquire	ECC83 Spec Q	PD500	3B28	6SL7GT
CV488	ECC88 Spec Q	PL509	3C800E	6SN7GT
CV1881	ECC804	QQV03-10	3J160E	12BH7
CV2355	ECC804	QQV03-10 Mul	4-6SA	12E1
CV4014	ECC804	QQV03-20A	4-125A Eimac	13E1
EF86 Siemens	EF73	QQV03-20A EEV	4-400A	19AQ5
EF92	EF91	QQV06-40A	4C28	211
EF93	EF92	QQV06-40A Mul	4C250B	805
EF95	EF94	QV1-125	4C350A	807
EF96	EF95	QV4-250	4C350A	811A
EF97	EF96	QV4-250	4C1000A	813
EF98	EF97	R10	4C5000A	4635
EF99	EF98	SU2150	5B 25M	5763
DET22	EL81	TT21	5B 25M	6336A
DET23	EL81	S11E12	5B 25M	6973
DF91	EL84	TD03-10E	5B 25M	8056
E80L	EL5070	TY4-400A	5U4G	8122
E83F	GY501	U19	5V4G	Sockets:
E88QC	Klystrons	UBC41	6AK5W	B9A PCB
E180F	KT61	UCL82	6A56	B9A chassis
EC158	KT81	UL41	6B4G	Octal chassis
EC235 Mu	KT88/6550	UY85	6BH6	Many others

Testing to special quality - Military/CV, low microphony etc available on request

### BILLINGTON EXPORT

Unit F2, Oakendene Industrial Estate, Near Horsham, Sussex RH13 8AZ.

Callers by appointment only.

Telephone: 0403 865105 Fax: 0403 865106

Min. UK order £50 + VAT. Min. Export order £50 + Carriage.

### B. BAMBER ELECTRONICS

#### Ex PMR Equipment

Pye Westminsters W15AM Low Band & High Band	£20	Pye Europas MF5U, UHF	£35
Pye Motophones MF5AM Low Band	£15	Pye Europas MF5FM High Band & Mid Band	£35
Pye Reporters MF6AM High Band & Low Band	£65	Pye Olympics M201 AM Low Band	£35
Pye Pagers PG1FM High Band	£20	Pye Base Station F496 UHF 24volt	£250
Pye M294 FM High Band & Low Band	£160	Pye Power Unit Type AC200	£100
Pye M293 AM High Band & Low Band	£140	Pye Controller Type PC1	£50
Pye M296 UHF U Band	£120	Pye Controller Type M81	£190
Pye M295 Band III	£100	Pye Base Station Type F9U, UHF	£45
		Pye Base Station Receiver Type R414, UHF	£45
		Pye Base Station Transmitter Type T414 UHF	£45

All Equipment is less Mikes, Speakers, Crystals etc.

All Prices Exclude Carriage and VAT. WANTED EX PYE PMR EQUIPMENT.

Callers by appointment only

5 STATION ROAD, LITTLEPORT, CAMBS CB6 1QE  
PHONE: ELY (0353) 860185

#### Technical & Scientific Supplies

HP A700 Computer	£480
HP 2392A Digital Terminal	£95
HP 2225A Ink Jet Printer (HP1B)	£90
HP 7470A Plotter A4 (HP1B)	£95
HP 45611A CPU (HP150 Touchscreen Computer)	£95
HP 9121D Dual 3.5" drive	£85
Computer Bridge A101 401	£80
Modem/Modem Wild T16 with tripod	£2000
WaveBuoy receiver, EDI	£400
Watel current meter, acoustic, Neil Brown	
DRCM2	£P.O.A.
Water current meter, ElectroMec, Prop't type, unused	£175

Special Laboratory clearance sale:  
Desks, filing cabinets, tables, notice boards, chairs, bookcases etc. Enquiries invited.  
All prices exclude carriage and VAT  
Please write/fax/phone (any time)

Technical & Scientific Supplies, PO Box 19, Hythe, Southampton, Hampshire SO4 6XQ  
Tel: (0703) 848666. Fax: (0703) 897079.

#### NEWMARKET TRANSFORMER LTD.

Unit 15, Craven Way Industrial Estate,  
Newmarket, Suffolk CB8 0AP.  
Tel: Newmarket (0638) 662989/660799  
Fax: (0638) 660799

TOROIDAL LAMINATED AND 100-110V  
AMERICAN ELECTRICAL APPLIANCE  
TRANSFORMER MANUFACTURERS.

VERY COMPETITIVE PRICES. FAST  
DELIVERY. QUALITY GUARANTEED.

PHONE OR FAX MR. DORNAN  
FOR IMMEDIATE QUOTE.



### Cooke International

Alitech 757 Spectrum Analyser 1.0MHz-22GHz including Digital Read Out, Digital Storage Mint Condition  
Alitech 446 Power Signal Source with optional plug-ins  
195 200-500MHz 150Watt Output  
197 500-1000MHz 150Watt Output  
Rotek 610 AC/DC/Ohms Universal Calibrator All Modes  
H.P. 3490A Digital Volt Meter 5 Digit AC/DC/Ohms, self test, autorange  
H.P. 400EL AC/RMS Voltmeter, 001-300V 10Hz-10MHz  
H.P. 419A DC Null Voltmeter  
Marconi TF 1313A Universal L.C.R. Bridge  
Racial 9686 25MHz Dual Trace Oscilloscope  
Marconi TF 2167 Linear R.F. Amp. 0.5-80MHz 47db gain  
Racial 9822 HF Frequency Meter 10Hz-80MHz 8 digits  
Solartron AS1164.2 -0-20v-1 amp Twicel Twin P.S.U's  
MUCH MORE AVAILABLE INCLUDING COMPUTERS, PERIPHERALS ETC ETC IN OUR SHOWROOM AND BARGAIN WALK ROUND STORE. PRICES FROM £5.  
SEND S.A.E. FOR STOCK LISTS, PHONE ALL PRICES EXCL VAT AND CARAGE OPEN MON-FRI 9am-5pm. LARGE FREE CAR PARK.

Contact: Cooke International, Unit Four, Pordingtonbridge Site, Main Road, Barnham, Bognor Regis, West Sussex PO22 0EB. Tel: 0243 545111. Fax: 0243 542457.

### TO MANUFACTURERS, WHOLESALERS, BULK BUYERS, ETC.

### LARGE QUANTITIES OF RADIO, TV AND ELECTRONIC COMPONENTS FOR DISPOSAL

SEMICONDUCTORS, all types, INTEGRATED CIRCUITS, TRANSISTORS, DIODES, RECTIFIERS, THYRISTORS, etc. RESISTORS, C/F, M/F, W/W, etc. CAPACITORS, SILVER MICA, POLYSTYRENE, C280, C296, DISC CERAMICS, PLATE CERAMICS, etc. ELECTROLYTIC CONDENSERS, SPEAKERS, CONNECTING WIRE, CABLES SCREENED WIRE, SCREWS, NUTS, CHOKES, TRANSFORMERS, ETC ALL AT KNOCKOUT PRICES

- Come and pay us a visit ALADDIN'S CAVE

TELEPHONE 081 445 0749/445 2713

R. HENSON LTD

21 Lodge Lane, North Finchley, London N12 8JG.  
(5 minutes from Tally Ho Corner)

### NAGRA IV-SJ

Professional instrumentation  
1/4-inch tape recorder, for noise and vibration recordings.

### AS NEW £4800

New price over £8000.  
Operation spec/manual sent on request.

Tel. Rupert Murray  
061 941 2313

### FOR SALE

Linsley Hood 75 Amplifier, Nelson-Jones AM/FM Tuner.  
Spares/Repairs £30 each. RS UV Exposer Unit 555-279.  
£99 new - Accept £60.

Tel: 0533 555670

### FOR ARTICLES WANTED SEE OPPOSITE

### APPOINTMENTS

#### Calling all competent radio engineers

Would you enjoy working for a small company that designs, commissions and installs PMR Radio and Repeater Trunking Systems?

#### ACE/CDS NEEDS YOU NOW!

Excellent salary and relocation expenses.

Write or phone

ACE Ltd. Unit 4, Summerlea Court, Southrop, Herriard, Basingstoke, Hants RG25 2PN. Tel: 0256 381528

# ARTICLES WANTED

## Power Supply Manufacturers

Can you supply a custom switchmode 70W 12v power supply that meets relevant safety and EMC specifications?

**Target price £25 each**  
**Quantity 3000 pa +**

Tel: S. Harding 0256 381656

## WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap and quantity. Prompt service and cash.

M & B RADIO  
 86 Bishopton Street,  
 Leeds LS1 4BB.  
 Tel: 0532 435649  
 Fax: 0532 426881

9556

## WANTED

Receivers, Transmitters, Test Equipment, Components, Cable and Electronic Scrap. Boxes. PCB's, Plugs and Sockets, Computers, Edge Connectors.

**TOP PRICES PAID FOR ALL TYPES OF ELECTRONICS EQUIPMENT**

A.R. Sinclair, Electronics, Stockholders, 2 Normans Lane, Rabley Heath, Welwyn, Herts AL6 9TQ. Telephone: 0438 812 193. Mobile: 0860 214302. Fax: 0438 812 387

780

## STEWART OF READING

110 WYKEHAM ROAD,  
 READING, RG6 1PL.  
 TEL: 0734 68041  
 FAX: 0734 351696

**TOP PRICES PAID FOR ALL TYPES OF SURPLUS TEST EQUIPMENT, COMPUTER EQUIPMENT, COMPONENTS etc. ANY QUANTITY.**

103


## WANTED URGENTLY

Marconi 2951 RT test set or similar plus any used two-way radio equipment.

Tel: 0256 381528

Please mention **ELECTRONICS WORLD** when replying to any advertisement

# INSIDE INFORMATION

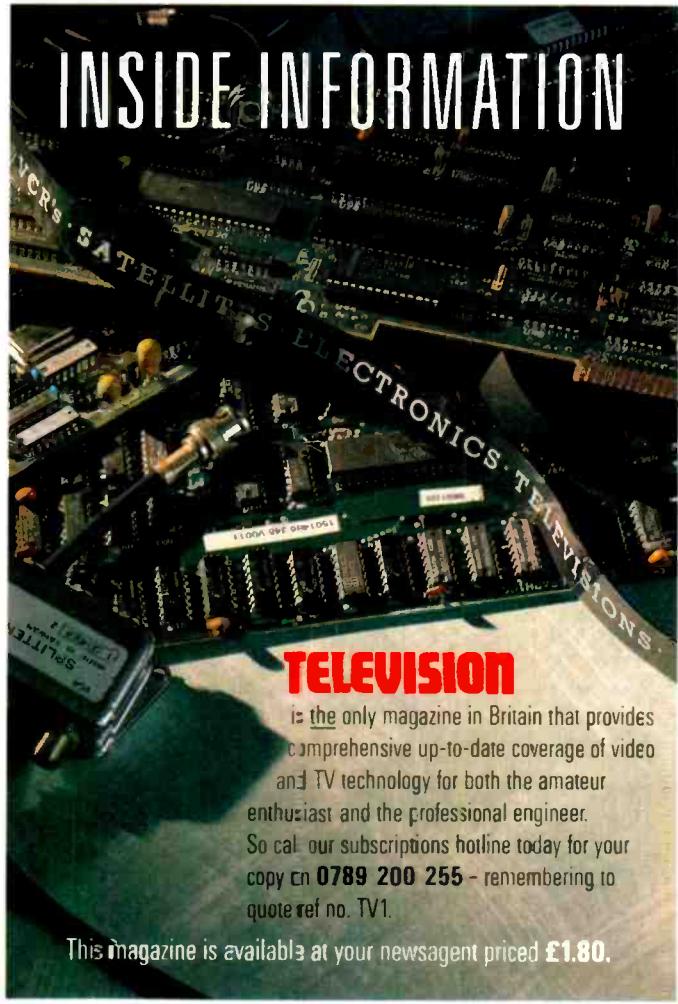

## TELEVISION

is the only magazine in Britain that provides comprehensive up-to-date coverage of video and TV technology for both the amateur enthusiast and the professional engineer. So call our subscriptions hotline today for your copy on 0789 200 255 - remembering to quote ref no. TV1.

This magazine is available at your newsagent priced £1.80.

CIRCLE NO. 153 ON REPLY CARD

# Write in Assembler?

Then you can vastly increase your productivity by moving up to our METAi range of PC-Based Development Tools. We have support for almost every micro-controller under the sun, from 4-bitters through DSPs and 80286/ 68K.

All our tools are fast, clean and powerful, from our Macro Meta Assembler to our £295 ASIC-based Universal EPROM Emulator, with its unique comms link and breakpoints. Call or fax now for full data by return fax or post.

"Editor...incredibly useful. METAi ...can assemble source code for any processor ...without compromising on speed. ...excellent backup and tech support."

Electronics & Wireless World, Feb '91

"METAi is the Rolls Royce of Development Gear"

Unsolicited fax from G.E.M.S. Ltd

Crash Barrier Ltd, 18 Oxford Street, Wellingborough, Northants, NN8 4HY, United Kingdom  
 Tel: (0933) 224366, Fax: (0933) 441877, Modem: (0933) 224377 V22(bis), HST, V32(bis)



CIRCLE NO. 154 ON REPLY CARD

WORLD+WIRELESS WORLD



### TATUNG TCS8000 386 COMPUTER SYSTEM at £399

Full 386DX (not SX) computer system complete with 102 keyboard and manual. Includes 210 watt PSU, I/O card, hard and floppy controller (please state MFM, RLL, IDE or SCSI), 1.2 Mbyte floppy drive, 1 Mbyte RAM upgradeable to 16 Mbytes on the motherboard, eight expansion slots, C and T "CHIPS" chipset, co-proc. socket, MS-DOS 3.3, GW BASIC and manuals.

16 MHz clock £399. 20 MHz as above but with 2 Mbyte RAM £529.

### MATMOS HIGH PERFORMANCE 286 SYSTEM at £299

A quality 286 system running at a Landmark speed of 16 MHz; clock speed 12 MHz. 1 Mbyte RAM, expandable to 4 Mbytes. Serial and parallel ports, 101 keyboard, mono card, 1.44 Mbyte 3.5-inch drive, IDE hard drive controller (add £20 for MFM or RLL unless purchased with Matmos hard drives), eight slots. AMI bios with setup and diagnostics, well-made stylish case, full manuals included £299. Fitted with 40 Mbyte hard drive £399; fitted with 60 Mbyte hard drive £435.

### TOP SPEC. 386 AND 486 SYSTEMS

25 MHz 386 system, 1 Mbyte RAM, 1.2 Mbyte floppy drive, etc. £599.

25 MHz 486 cache system £1299.

Phone for details: carriage on systems £15. See below for add-ons and other stock items.

### FLOPPY DISK DRIVES

#### Internal

360K 5.25-inch IBM standard half-height drive £29.95 (carr £3.50).

1.2 Mbyte 5.25-inch Panasonic IBM standard half-height drive £49.50 (carr £3.50).

720K 3.5-inch Citizen OSD third-height drive for XT (NDT Amstrad 1512/1640) £29.50 (carr £3).

720K 3.5-inch Citizen OSDA45 third-height drive for AT/286/386 cream bezel £32.50 (carr £3).

As above but XT/AT switchable £35.50 (carr £3).

1.44 Mbyte 3.5-inch Citizen OSDA39 third-height drive for ATs, grey bezel £47.50 (carr £3).

1.44 Mbyte 3.5-inch Sony drive in 5.25-inch chassis, £47.50 (carr £4).

Fitting kit for 5.25-inch space suitable for all Citizen 3.5-inch drives inc. cable adaptors £8.49 (carr free with drives).

IBM standard floppy disk drive cable £4.

#### External

720K 3.5-inch in smart case (suitable for ATs only) £39.50 (carr £3.50). Cable adaptor kit for AT £12.50.

### HARD DISK DRIVES

10 Mbyte NEC 5.25-inch MFM £44.95 (carr £4).

20 Mbyte NEC 5.25-inch 40 ms MFM £89.95 (carr £4).

20 Mbyte Miniscribe 8225 3.5-inch in 5.25-inch chassis, 24 msec IDE with controller and all cabling - AT only - £109 (carr £5).

30 Mbyte NEC 5.25-inch RLL £109 (carr £5).

44 Mbyte Microscience MH1050 5.25-inch, 28 msec MFM £135 - £125 in systems (carr £4).

40 Mbyte Quantum 40S Pro 3.5-inch, 18 msec SCSI £159 - £149 in systems (carr £4).

55 Mbyte NEC 5.25-inch RLL £149 (carr £4).

62 Mbyte Micropolis 1324A 5.25-inch, 28 msec MFM, full height £149 (carr £5).

91 Mbyte Seagate/Imprimus ST2106N 5.25-inch, 16.5 msec SCSI £239 (carr £5).

94 Mbyte Seagate/Imprimus ST2106E 5.25-inch, 16.5 msec ESDI drive with 16-bit high-speed controller card and cables £259 (carr £5).

ALL DRIVES HALF HEIGHT UNLESS STATED

HDD cable set £5.

### DISK DRIVE CONTROLLER CARDS (carr £2.50)

XT MFM £37.50, XT RLL £37.50, XT SCSI £29.50.

AT RLL £37.50, AT MFM £39.95, AT IDE £12.95, AT SCSI £37.50, AT ESDI £69.

### HITACHI CD ROM DRIVE (ex dem.)

External cased AT bus CDR15C2S, half-height, 5.25-inch with card and cable £199 (carr £5).

### IBM COMPATIBLE AT MOTHERBOARDS, CARDS etc.

25 MHz 486 Very latest 80486 baby size motherboard with extra 64K cache. Landmark speed 115 MHz. Floating point co-processor built into CPU. Eight expansion slots. £99 (carr £5).

25 MHz 386 motherboard, 80386 CPU, Landmark speed 33 MHz, accepts up to 8 Mbytes SIMMS RAM, £349 (carr £3.50).

20 MHz 386 motherboard, accepts up to 8 Mbytes SIMMS RAM, £299 (carr £3.50).

1 Mbyte RAM for 386/486 £45.

12 MHz AT motherboard, 80286 CPU, 8 expansion slots, full AMI BIOS with diagnostics etc., 80287 socket, manual, Landmark speed of 16MHz, accepts up to 4 Mbytes of SIMPS RAM on board, £89.00 (carr £3.50).

AT multi I/O board with 1 parallel, 2 serial, 1 game, 2 floppy, IDE hard drive £34.50.

AT/XT floppy disk controller £39.

Mono graphics card £9.95 (all carr. £2).

### INTEL 386 PROCESSOR AND 287 AND 387 CO-PROCESSORS

80287 maths co-processor £89.

386 and 387 processors extracted from new systems and guaranteed 1 year.

20 MHz 386-20 DX CPU £99. 25 MHz 386-25 DX CPU £119.

20 MHz 387-20 co-processor £99. 25 MHz 387-25 co-processor £119.

### MOUSE

Microsoft compatible, serial with software, £25.99 (carr £3).

### MONITOR - MONO

12-inch Philips Hercules green screen, smart case with tilt-and-swivel base, high res. display, £59.95 (carr £6.50).

### SVGA COLOUR MONITOR

14-inch super VGA Tystar multisync. 0.28 dot pitch. High quality 1024x768 display £249 (carr £10).

### HITACHI CAD COLOUR MONITORS

20-inch multisync CM2085M from VGA up to 64kHz at 1280 by 1024 (ex dem.) £899.

20-inch fixed frequency 48kHz CM2086A1-D (ex dem.) £299.

20-inch fixed frequency 64kHz CM2086A3-EX (ex dem.) £399.

16-inch fixed frequency 64kHz CM1686A (new) £299.

15-inch fixed frequency 64kHz with microfield TM8 driver card for ACAD, Windows 3 etc (1280x1024) £449 (p.o.s. for carriage for above).

### VGA CARDS

16-bit VGA card, 256K, all emulations, up to 800x600, with software to run all major packages. Dak chip set. Switchable for use in XT's E59.

16-bit 1024x768 super VGA card. Very high resolution with 512K and drivers for Windows 3, Acad, VP etc. Full manuals and disks. Trident chip set. £95. 1 Mbyte version £109.95 (carr on cards £2.00).

### FAX CARD

Plug into PC expansion slot. Giving powerful fax features: AT5 Cipher BT approved Group III intelligent receiver/transmit, with multiple output and call scheduling. With disks, cables and full user manual £119 (carr £5).

### ETHERNET CARD

Novell compatible 16 bit £89 (carr £2).

### POWER SUPPLIES

Astec BM140 IBM XT/AT compatible 150W; +5V at 15A, +12V at 5A, -5V at 0.3A, -12V at 0.5A; fan cooled, rear panel switch, good value at £19.50 (carr £4).

\* VAT + Vat & carriage must be added to all items (quotes for carriage overseas).

\* Everything new, and guaranteed one year unless stated; ex-dem products guaranteed 6 months.

\* Access and Visa telephone service.

**MATMOS LTD., UNIT 11, LINDFIELD ENTERPRISE PARK,  
LEWES ROAD, LINDFIELD, WEST SUSSEX RH16 2LX.  
0444 482091 and 0444 483830 (Fax: 0444 484258).**

Matmos Ltd. has been trading successfully since 1976.

CIRCLE NO. 147 ON REPLY CARD

## INDEX TO ADVERTISERS

PAGE	
A.P. Products .....	815
A.O.R. (UK).....	842
Abracadabra Electronics .....	822
Airlink Transformers....	857
Anchor Surplus .....	883
Antex Electronics .....	842
Audio Electronics .....	849
Beta Marketing .....	857
Billington Valves .....	886
Brain Boxes .....	834
Capella .....	834
Citadel Products .....	OBC
Colomore Electronics .....	859
Covend Electronics .....	859
Crash Barrier .....	887
Digitask .....	802
Display Electronics .....	853
Electrical and Radio Trading .....	870

PAGE	
Ellmax Electronics .....	823
Fern Developments.....	873
Field Electric .....	859
Halcyon Electronics .....	861
Hitek Calibration Services .....	881
Hoka Electronics .....	849
I.P.K.....	823
Icom UK .....	857
ILP Electronics .....	863,865,867
Integrex .....	IFC
J. & N. Bull Electrical....	844
J.A.V. Electronics .....	834
John's Radio .....	877
Kestrel .....	842
Keytronics.....	885
La Place .....	823
Lab Volt UK.....	811
M&B Electrical .....	811
M&B Radio.....	811

PAGE	
Matmos .....	888
Micro Amps .....	855
MQP Electronics .....	861
Mutek .....	847
Number One Systems ...	807
R. Henson .....	870
Ralfe Electronics .....	881
Signals Research .....	815
Smart Communications .....	861
Stewart of Reading .....	881
Surrey Electronics .....	881
Talent Computers .....	881
Taylor Brothers .....	881
Television M.....	881
Thurlby .....	881
Thurley .....	881

October 1991

ELECTRONICS

### OVERSEAS ADVERTISEMENT AGENTS


France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008.

United States of America: Jay Fenman, Reed Business Ltd., 205 East 42nd Street, New York, NY 10017 - Telep.

Printed in Great Britain by Riverside Press, Gillingham, Kent, and typeset by Marlin Graphics, Sidcup, Kent DA14 9AS. © Reed Publishing Ltd 1991. *Electronics and Wireless World* can be sold, lent or otherwise disposed of. Gordon & Gotch Ltd, INDIA: A.H. Wheeler & Co, CANADA: The Wm Dawson Subscription Service Ltd; Gordon & Sons (S.A.) Ltd, UNITED STATES: Worldwide Media Services Inc., 115 East 23rd Street, NEW YORK, NY 10016.


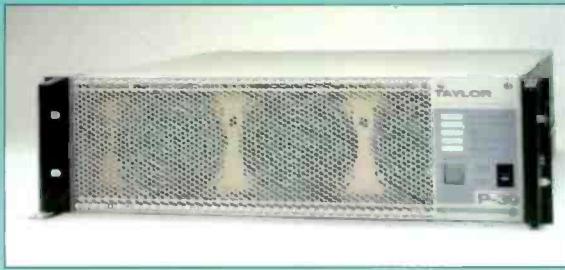
### STEREO RADIO TRANSMITTERS & TRANSPOERS



**ASK ABOUT**  
STEREO RADIO TRANSMITTERS AND TRANSPOERS  
UP TO 1 KILOWATT

TV TRANSMITTERS AND TRANSPOERS  
UP TO 100 WATTS

FM-AM-SSB RADIO TRANSMITTERS AND TRANSPOERS  
3-400MHz UP TO 1 KILOWATT

FM RADIO MICROWAVE LINKS UP TO 4.2GHz

### P30 902P BAND 2 FM STEREO MODULATOR £540.00

19" Rack Mounting 2u 350mm deep  
Any specified frequency 88-110MHz  
Crystal controlled LF. - R.E. frequency stability <5ppm  
Temp. controlled VCO, frequency stability ± 2.5KHz  
Audio Input .7V 600Ω Balanced (isolating transformer) XLR Sockets  
Audio Bandwidth 40Hz - 15KHz  
Crosstalk <40dB 1KHz  
Deviation level control with analogue deviation meter  
1KHz tone generator switchable L or R, L & R  
Voltage 220-240V AC 50Hz (110-120V AC no cost Option F)  
Output level 6.3dBmV (150mV) 75Ω (IEC Connector)  
OPTION G 50Ω no cost (N Connector)  
OPTION A Output Level 1 Watt 50Ω £190.00  
OPTION B Output frequency 420-460MHz 900-920MHz Specify Frequency £80.00

### P30-30VF 30 WATT BAND 2 POWER AMP WITH A.G.C. £901.00

19" Rack Mounting 2u 425mm deep  
Gain 3dB +20dB A.G.C.  
Input Impedance 75Ω (IEC Connector)  
Output Power 30 Watts into 50Ω (N Connector)  
Voltage 220-240V AC 50Hz (110-120V no cost Option F)

### P30-30VFT 30 WATT BAND 2 TRANSPOSER £1261.00

Power: Specification as P30-30VF  
Input: 88-110MHz/420-460MHz/900-920MHz 50Ω  
(N Connector) Specify Frequency  
Crystal Controlled Frequency Stability <5ppm  
Gain 9.3dB  
A.G.C. 40dB (± 20dB)

### P30-300VF 300 WATT BAND 2 POWER AMP WITH A.G.C. £2628.00

19" Rack Mounting 3u 500mm deep  
Gain 42dB +20dB A.G.C.  
Input Impedance 75Ω (IEC Connector)  
Output Power 300 Watts into 50Ω (N Connector)  
Voltage 220-240V AC 50Hz (110-120V no cost Option F)

### P30-300VFT 30 WATT BAND 2 TRANSPOSER £2928.00

Power: Specification as P30-300VF  
Input: 88-110MHz/420-460MHz/900-920MHz 50Ω  
(N Connector) Specify Frequency  
Crystal Controlled Frequency Stability <5ppm  
Gain 10.3dB  
A.G.C. 44dB (± 22dB)

All Prices Exc VAT & Ex Works CIRCLE NO. 102 ON REPLY CARD

# IC PROGRAMMING TESTING & ERASING SOLUTIONS

## PC82 UNIVERSAL PROGRAMMER & TESTER

£395



Universal programmer. The complete designer's kit. This will program EPROMS, EEPROMS, BPROMS, PALS, GALS, EPLD's, Z8 and 87XX microprocessors. A unique feature is the testing of logic parts such as 74LS393 etc. The PC82 can check and identify parts. Already programmed are the TTL & CMOS logic test vectors. Software is supplied to write vectors for most unique chips. One of the most popular programmers in the USA.

### TTL, CMOS, DRAM & SRAM TESTING

PC82 can test and verify any TTL/CMOS logic chip, DRAM & SRAM. The software will also identify a TTL chip. Do you have a few TTL chips aside not knowing whether they are working?



### DEVICE GUIDE

EPROM N/CMOS 2716-27010 (1 mBit) Vpp 12.5,12.9,21,25	✓	✓
EPROM 27513,27011,572000/4000,8764-87256,CYC2XX SERIES	✓	—
EEPROM 2816,2816A,2817,2817A,2864A	✓	✓
EEPROM 9306,9307,9346,9356,93CS06,26,44,56,66,28256A	✓	—
BPROM 32x8 to 4096x8, incl. 63S080,7C28X,29X	✓	—
PAL 10,12,14,16,18,20-L,R,X,P,1,2,4,8,10 (20/24-pin)	✓	—
GAL 16V8,18P8,20V8,22V10	✓	—
EPLD 20G10,22V10, EP310,320,600,610,900,910,5C031,32,60,90	✓	—
CMOS EPAL C16L8,R8,R6,R4,C18V8,C20G10,L8,R8,R6,R4, C22V10	✓	—
MPU Z8,8741,42,48,49,50,51,C51,C52,C252,TMS7742,77C82,63701	✓	—
Device testing TTL/CMOS logic, DRAM & SRAM	✓	—

### PC82      PC84

**ADAPTERS FOR PC82      FROM £95**  
A wide range of plug-in adapters to expand the capability of the PC82.  
Various PLCC convertors & 4 gang 28/32/40 pin Eprom, Gal & Pal. Popular CPU types include PIC 16C54/5/6/7, 8796/7, 68705, 87C751/2, & TMS320E25.

### FEATURES ALL MODELS

For the IBM PC, install the interface card and programming socket, load the menu-driven software and you have a complete design system at your fingertips.

#### EASY TO INSTALL

The programmer comes with an interface card that plugs into any free slot of your PC. There is no DMA channel to worry about and it occupies limited I/O space. The programmer socket box is connected via a ribbon cable to the back of the interface card so that the socket box is external. After the interface card is installed the PC never need be opened again.

#### SUITS ALL PC's

The programmers will run on any compatible IBM machines such as XT's, AT's, '386 and '486. Whether it be AMSTRAD or COMPAQ the programmers will work. The software is text only monographic so is compatible with any machine.

#### SOFTWARE DRIVEN

All software for the programmers is supplied on 5 1/4" low-density disks. The software can be copied onto hard disk using the DOS copy command. Programs are supplied for the various features and are menu-driven. All programming is done from the menu, no hardware switches are needed. Just select the type and manufacturer and the programming is done automatically. Free software updates for new types which are continually being added.

The menu-driven software is a full editing, filing and compiling package as well as a programming package. Save to disk and load from disk allows full filing of patterns on disk, to be saved and recalled instantaneously. Device blank check, checksum, program, verify, read and modify are all standard features. Hex to bin file conversions included for popular file formats including Intel Motorola etc. 2 ways/4 ways bin file splitter for 16/32 bit file data. Selection of speed algorithm for FAST, INTELLIGENT, INTEL, etc.

## PC86 HANDY POCKET TESTER £99

Tests all popular TTL 74/54, CMOS 4045 & DRAM types, can search and display type number of unknown/house marked types. Simple operation. 9 volt battery operated with LCD display.



## M1 FAST ERASER £99

NO MORE WAITING FOR EPROMS TO ERASE. New advanced UV source gives under 2 minute erasure time on most types of modern EPROM. Digital down counter & display plus added features for simple operation in use. Large capacity e.g. 13x28 pin devices. Small footprint. Designed for heavy industrial/workshop use. UK design & manufacture.



## PC84 EPROM PROGRAMMERS

**1-GANG £139, 4-GANG £199 & 8-GANG £299**

PC84 -1, -4, -8 Eprom programmers only. The variant is only gang size. The -4 and -8 gang will program multiple EPROMs simultaneously. Device sizes are from 2716 to 271000 both C and NMOS. ZIF (zero insertion force) sockets are used on all models.



## ORDER INFORMATION

Please include £7 for carriage by courier, plus VAT on all UK orders. (£20 for exports.) All pricing for programmers includes software, interface card, socket box and full instructions. (Prices do not include VAT or carriage). ACCESS, VISA or CWO. Official orders welcome from Government bodies & local authorities.



## CITADEL PRODUCTS LTD

Dept. WW, 50 High St,  
Edgware, Middx. HA8 7EP  
Tel: 081-951 1848