

# ELECTRONICS WORLD

## + WIRELESS WORLD

Denmark DKr. 70.00  
Germany DM 15.00  
Greece Dra. 760  
Holland Dfl. 14  
Italy L. 7300  
IR £3.30  
Spain Pts. 780  
Singapore S\$ 12.60  
USA \$6.70

SOR DISTRIBUTION

A REED BUSINESS PUBLICATION

AUGUST 1992 £1.95

### APPLICATIONS

Putting the  
pressure on  
measurement

### PC REVIEW

Updated  
LabWindows/  
EE Designer III

### ENGINEERING


Direct Digital Synthesis

### ANALOGUE

Going linear  
with power  
mosfets

### DIGITAL

Getting DSP  
into pictures  
and radios

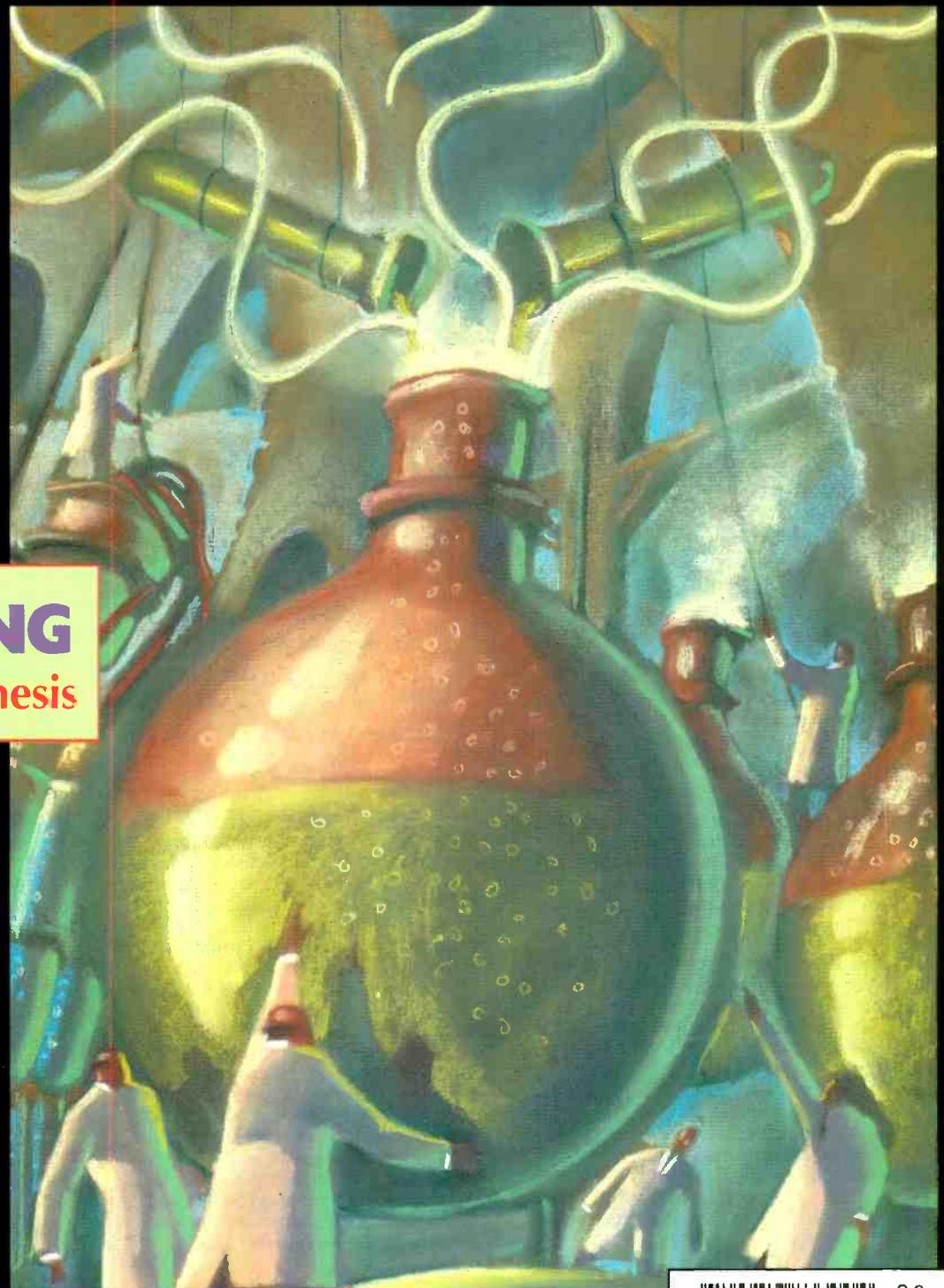

# FREE:

**Harris HA-5020 current  
mode amplifier\***

\*Limited to the first 1000 replies. This offer applies to the UK and Scandinavia only



# Dataman's new S4 programmer costs £495 You could have one tomorrow on approval\*

If you've been waiting for S4 we have some good news. It's available now. S4 is the 1992 successor to Dataman's S3 programmer, which was launched in 1987. The range goes back through S2, in 1982, to the original Softy created in 1978. Like its predecessors, Softy4 is a practical and versatile tool with emulation and product development features. S4 is portable, powerful and self-contained. Design and manufacture are State of the Art. S4 holds a huge library of EPROMS, EEPROMS, FLASH and One Time Programmables. Software upgrades to the Library are free for the life of the product, and may be installed from a PROM by pressing a key. *S4 makes other programmers seem oversized, slow and outdated.* S4 is now the preferred tool for engineers working on microsystem development.

## Battery Powered

S4 has a rechargeable NICAD battery. On average, you can do a week's work without recharging. On a single charge, up to a thousand PROMS can be programmed – and charging is fast: it only takes an hour. Normal operation can continue during the charging process.

## Continuous Memory


Continuous Memory means never losing your Data, Configuration or Device Library. You can pick up S4 and carry on where you left off, even after a year on the shelf. If the NICAD battery loses all of its charge, RAM contents are preserved by the LITHIUM backup battery.

## Remote Control

S4 can be operated via its RS232 Serial Port. The standard D25 socket connects to your computer. Using batch files or a terminal program, all functions are available from your PC keyboard and screen.
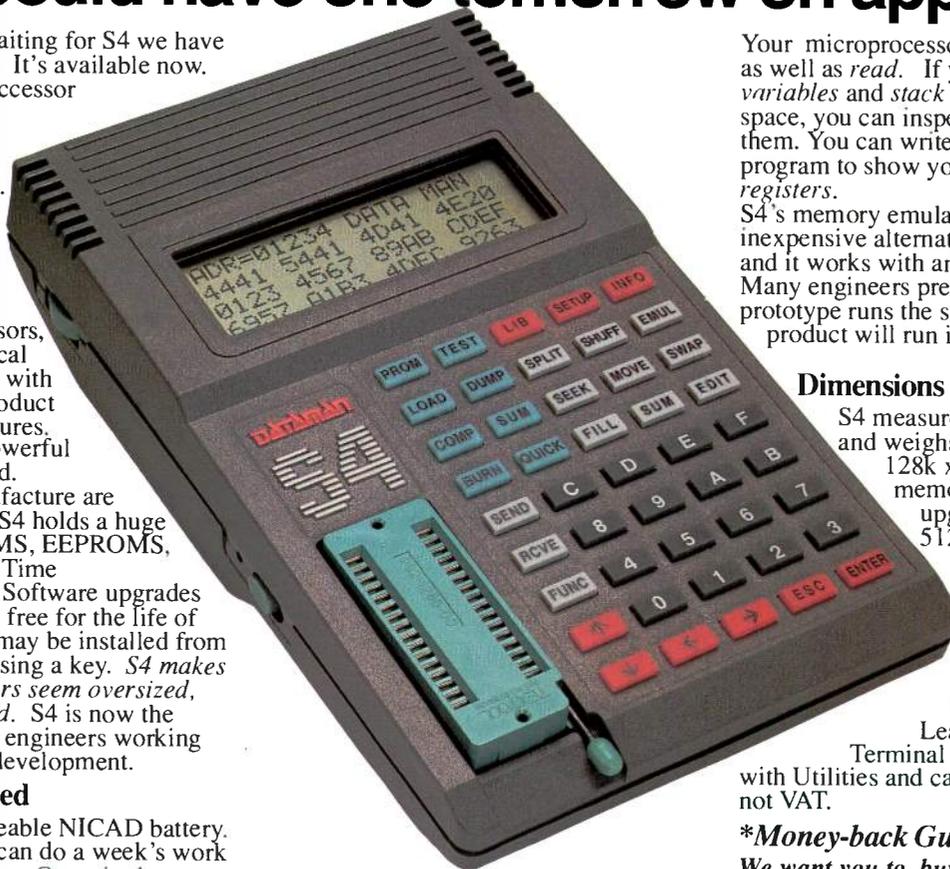
## Free Terminal Program

You could use any communications software to talk to S4. But the Terminal Driver program, which we include free, is the best choice. It has Help Screens to explain S4's functions and it sends and receives at up to 115200 baud – that's twelve times as fast as 9600 baud. At this speed a 64 kilobyte file downloads in 9 seconds. There is a memory resident (TSR) option too, which uses only 6k of your precious memory, and lets you "hot key" a file to S4. Standard upload and



Your microprocessor can write to S4 as well as read. If you put your variables and stack in S4's memory space, you can inspect and edit them. You can write a short monitor program to show your internal registers. S4's memory emulation is an inexpensive alternative to a full MDS and it works with any microprocessor. Many engineers prefer it because their prototype runs the same code that their product will run in the real world.

## Dimensions & Options

S4 measures 18 x 11 x 4 cm and weighs 520 grams.

128k x 8 (1MB) of user memory is standard, but upgrading to 512k x 8 is as easy as plugging in a 4MB low-power static CMOS RAM.

The stated price includes Charger, EMUlead, Write Lead, Library ROM,

Terminal Driver Software

with Utilities and carriage in U.K. but not VAT.

## \*Money-back Guarantee

We want you to buy an S4 and use it for up to 30 days. If it doesn't meet with your complete approval you will get your money back, immediately, no questions asked.

download formats include: ASCII, BINARY, INTELHEX, MOTOROLA and TEKHEX.

**S4 loads its Library of programmables from a PROM in its socket, like a computer loads data from disk. Software upgrades are available free. Download the latest Device Library from our Bulletin Board.**

## Microsystem Development

With S4 you can develop and debug microsystems using Memory Emulation. This is an extension of ROM emulation, used for prototype development, especially useful for single-chip "piggy back" micros. When you unpack your S4 you will find an Emulator Lead with a 24/28/32 pin DIL plug and a Write Lead with a microhook. Plug the EMULead in place of your ROM. Hook the Write-Lead to your microprocessor's write-line. Download your assembled code into S4. Press the EMULate key and your prototype runs the program. S4 can look like ROM or RAM, up to 512K bytes, to your target system. Access-time depends on S4's RAM. We are currently shipping 85ns parts.

CIRCLE NO. 101 ON REPLY CARD



Call us with your credit card details. Stock permitting, we are willing send goods on 30 days sale-or-return to established U.K. companies on sight of a legitimate order.

## Customer Support

Dataman's customer list reads like Who's Who In Electronics. Dataman provides support, information interchange, utilities and latest software for S4, S3, Omni-Pro and SDE Editor-Assembler on our Bulletin Board which can be reached at any time, day or night.



Station Road MAIDEN NEWTON  
Dorset DT2 0AE United Kingdom  
Phone 0300-20719  
Fax 0300-21012  
Telex 418442  
BBS 0300-21095  
Modem 12/24/96 V32 HST N,8,1

# CONTENTS

## FEATURES



**COVER: DIRECT DIGITAL SYNTHESIS** 630  
DDS is changing the way RF engineers design radio systems. In a new series, Ian Hickman shows how DDS systems lend themselves to chip integration, with few conventional components.

### GOING LINEAR WITH POWER MOSFETS.....635

Even when linear parameters are known, different manufacturers' devices show considerable variation. Terence Finnegan goes back to basics to determine linear characteristics.

### CURRENT ALTERNATIVE TO OPERATIONAL AMPLIFIERS.....643

Application circuits may look similar, but Frank Ogden demonstrates why the mechanisms that give current mode amps their performance are very different.

### UPDATING THE CHOICE FOR HANDLING DATA IN THE LAB.....646

How does the updated LabWindows meet data acquisition demands? Allen Brown measures the improvements.

### DON'T SAY GOODBYE TO THE DESIGN ENGINEER - YET.....649

EE Designer III is an electronic design engineering system - according to the literature. John Anderson puts those claims to the test.

### HYBRIDS AT THE HEART OF RADIO-FREQUENCY COMBINERS.....653

Several VHF or UHF broadcasting channels can be transmitted simultaneously from a single antenna. Dick Manton explains the combining role of hybrids.

### SQUEEZING INTO THE PICTURE.....663

The Fractal Transform is gaining wide endorsement in commercial image compression. Andy Wright reports on how far the technique is proving itself in motion picture compression.

### APPLYING DIGITAL SIGNAL PROCESSING.....669

Availability of high performance DSP is encouraging its use by designers. Allen Brown examines two of the most widely used applications for the technique.

### DIGITAL SIGNAL PROCESSING YIELDS NEW HARDWARE.....674

DSP is no longer just a way of obtaining analogue performance at lower costs. Pat Hawker reports on how DSP is opening up entirely new applications.

## REGULARS

### UPDATE.....620

Big names design single chip PC, Racing performance from battery micro, Electronic holograms colour our world, Wristwatch technology opens up mini hard disc market, Shining prospect for cheap lasers.

### RESEARCH NOTES.....626

How to sneak up on a submarine, Hot tip for Braille interface, Reversing the effects of electric shock, The magnetic attraction in all of us, World's smallest mosfets.

### LETTERS.....657

Distorted logic, Dinged angle on physics, Power politics and the knowledge gap,

### PRODUCTS.....679

EW + WW's round-up of all that's new in electronics and engineering software.

### CIRCUIT IDEAS.....684

Two mic-amp tips, Current-shunt amplifier for bipolar inputs, Positive-feedback op-amp booster, One-gate memory, Latched oscillator, Low-loss voltage dropper feeds S-M controller, Asymmetrical on/off 4060, Programmed Nand/Nor or And/Or gate.

### PICTURES FROM THE PAST.....687

Marconi had talked, in 1906, of linking together the Empire by wireless links. EW + WW looks at the painful process of a long birth.

### APPLICATIONS.....691

Simple precision timer, Pressure measurement.

### CIRCUITS, SYSTEMS AND STANDARDS.....695

Non-linear components lower settling time of noise reduction filters, Analogue delay line uses digital techniques, Transistor powers low-drop-out regulator.

### RF CONNECTIONS.....699

Getting a word in edgeways: Pat Hawker reports on development success in reducing the bit-rate of digital speech

**In next month's issue:** Designing a digital audio pre-amplifier. The Philips I<sup>2</sup>C microprocessor bus provides an effective control system for audio applications. EW+WW presents the complete hardware and software solution to easy listening.

### PROFESSIONAL SERVICES OFFER

Get your **free** fully working copy of Protel's Easytrax 2 PCB layout software as reviewed in EW+WW October 1991. This offer is presented in association with J A V Electronics. Only available through next month's issue.

**SEPTEMBER ISSUE ON SALE FROM AUG 27**

# SPECTRUM ANALYSIS

If you've got  
an oscilloscope  
and £350...



## ...you've also got a 250MHz Spectrum Analyser


A small investment in our new TSA250 can make a big difference to the scope of your 'scope. Using standard connections the TSA250 will adapt virtually any oscilloscope into a powerful Spectrum Analyser.

**EMC** investigations then become easy, you can check oscillators, transmitters, receivers and RF amplifiers and speed up a range of tasks in development, production and servicing.


With a frequency range of 400kHz to 250MHz plus accurate amplitude and frequency calibrations, the TSA250 is an exceptionally powerful tool. With a price tag of just £350 it's also an exceptionally inexpensive one.

For full details of the TSA250 plus a **free** copy of our booklet "Understanding Spectrum Analysis and EMC Investigations" contact us now.

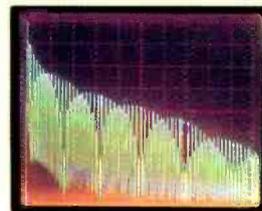- Digital Multimeters • LCR Meters • Thermometers • Frequency Meters • Timer Counters
- Bench Power Supplies • System Power Supplies • Function Generators • Pulse Generators
- Oscilloscopes • Digital Storage Adaptors • Logic Analysers • Logic Probes • Data Analysers



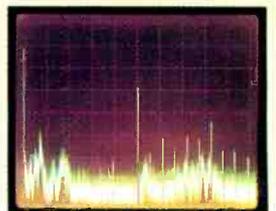*Spectrum of a near equal duty cycle pulse waveform*



*Noise emanating from a personal computer*

**THURLBY-THANDAR**

**Measurably better value**

Thurlby-Thandar Limited  
2 Glebe Road, Huntingdon, Cambs. PE18 7DX  
Tel: (0480) 412451 Fax: (0480) 450409

CIRCLE NO. 105 ON REPLY CARD

## Flights of fantasy

EDITOR  
Frank Ogden  
081-652 3128

DEPUTY EDITOR  
Jonathan Campbell  
081-652 8638

CONSULTANT  
Derek Rowe

DESIGN & PRODUCTION  
Alan Kerr

EDITORIAL ADMINISTRATION  
Lorraine Spindler  
081-652 3614

ADVERTISEMENT MANAGER  
Jan Thorpe  
081-652 3130

SALES MANAGER  
Shona Finnie  
081-652 8640

CLASSIFIED SALES EXECUTIVE  
Pat Bunce  
081-652 8339

ADVERTISING ADMINISTRATION  
Kathy Lambart  
081-652 3139

ADVERTISING PRODUCTION  
Shirley Lawrence  
081-652 8659

PUBLISHER  
Robert Marcus

FACSIMILE  
081-652 8956

CLASSIFIED FACSIMILE  
081-652 8931

### ARE WE HARD TO GET?

**Just one phone call to our Circulation Actionline brings instant assistance.**

If you have any difficulty purchasing your copy of *EW + WW*, call our Circulation Actionline.

**Call Kathy Lambart on 081-652 3139 and let us tackle your supply problems**



**H**ow on earth could the British, Italian and Spanish governments consider continuing with the European Fighter Aircraft project? This particular piece of euro-madness looked more like a turkey than an aeroplane even before the Germans decided to press the ejector button. After all, it was conceived five years before the Berlin wall came down as a singular response to a specific military threat from the old Warsaw Pact.

Examining UK domestic politics for a moment, EFA has welded together some extraordinary domestic alliances: the Foreign Office says it remains a good idea because it proves that we in the UK are good Europeans; the Department of Trade and Industry says that it is a good idea because it believes what British Aerospace told it about 40,000 job losses; the Ministry of Defence says that EFA is a good idea because the old soviet defence industry is still selling some pretty mean warplanes to the rest of the world. But most surprising of all, the Labour opposition supports the government in this £20 billion job creation scheme, presumably because it thinks that is what it is.

Few people would suggest that a government has no responsibility to promote high technology, even for defence purposes, but the sort of money which EFA will gobble up is almost unimaginable; it could pay for the equally anachronistic Trident submarine defence system in its entirety.

Just a fraction of the £20 billion spend could launch a global class electronics initiative to research, design and produce the sort of products which the rest of the world wants to buy: a fully digital broadcast television system is such an example. Associated programmes for chip research and display technology would spin off far more widely than overpriced, esoteric airframes and weapons systems.

UK electronics desperately needs inducement on a scale that only a massive government programme can provide but EFA is definitely the wrong programme. So how can our politicians be so stupid or corrupt in failing to recognise this? It is simply that the aerospace/defence industry led by British Aerospace and GEC enjoys an incredibly effective lobbying system in which retiring Forces personnel are engaged by these companies to promote corporate interests in their old Ministry departments. The result has been a run of spectacularly expensive defence contracts followed by equally spectacular failures. For example, GEC's Nimrod programme wasted £800 million. EFA will make this look like petty cash. The economist John Maynard Keynes was only half joking when he suggested that the easiest way of involving industry in public spending programmes was to dig a large hole, fill it with old banknotes, cover them with earth, and then issue companies with licences to dig them out again.

But it isn't just the money which lunatic programmes consume. They distort the entire industry infrastructure – or that which remains – because defence contracts do not encourage the commercial discipline which participating electronics companies need in servicing wider markets.

If there is a real defence requirement for a new fighter aircraft, this should be put out to tender in a free competition which includes Mikoyan and Sukoi. Who knows, the result could be a MiG-29 airframe stuffed with British electronics. This would put the wind up the boardroom gangsters who currently control the UK defence industry, give concrete help to the struggling CIS, provide defence of the realm and save the taxpayer vast sums of money.

**Frank Ogden**

*Electronics World + Wireless World* is published monthly by post, current issue £2.25, back issues (if available) £2.50. Orders, payments and general correspondence to L333, **Electronics World + Wireless World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.** Telex: 892984 REED BP G. Cheques should be made payable to Reed Business Publishing Group.

**Newstrade:** IPC Marketforce, 071 261-6745.

**Subscriptions:** Quadrant Subscription Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 441212. Please notify a change of address. Subscription rates 1 year (normal rate) £30 UK and £35 outside UK.

**USA:** \$116.00 airmail. Reed Business Publishing (USA), Subscriptions office, 205 E. 42nd Street, NY 10117.

**Overseas advertising agents:** France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 205 E. 42nd Street, NY 10117. Telephone (212) 867-2080. Telex 23827.

**USA mailing agents:** Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. 2nd class postage paid at Rahway NJ Postmaster. Send address changes to above.

©Reed Business Publishing Ltd 1992 ISSN 0959 8330

# REGULARS

UPDATE

## Big names design single chip PC

US semiconductor makers are racing to produce a single chip processor combining all the logic and processing required for a 32-bit PC.

Recent talks between Intel and VLSI Technology Incorporated (VTI) may be aimed at developing just such products, according to insiders. Intel executives have already said that the company plans to compress all the logic needed for a 32-bit PC onto a single chip by 1993. Intel recently announced it was working with IBM in this area.

Texas Instruments and chipset vendor Chips & Technologies are also working on single chip PCs which should appear next year.

Such devices will produce powerful new laptop and palm top computers and cut the cost of desktop machines, as well as fusing microprocessor and chipset sales into a single \$1.5bn-plus annual market.

VTI already makes house-keeping chipsets for 386 and 486 microprocessors which are being redesigned to operate on 3.3V power supplies. Low power single chip devices combining Intel 386 and 486 microprocessor cores with VTI chipset circuitry could result from an agreement.

Meanwhile TI plans to integrate the 486 clone microprocessor licensed from Cyrix with its own 32-bit PC chipsets using a

0.5µm cmos semiconductor process.

Single chip PCs will increase competition for stand-alone 386 and 486 microprocessors and clones. But Intel rival AMD will not undermine sales of 386 clone products with integrated chipsets unless it can add value,

according to UK chief Dave Brand.

However, Intel will be able to protect profits from stand-alone processors by ramping up production of a new device, code-named P5.

Leon Clifford, *Electronics Weekly*.

## Racing performance from battery micro

A microprocessor claiming the highest available ratio of computing performance to power consumption has been launched by US chip maker VLSI Technology Incorporated (VTI).

VTI's implementation of the *Arm610* 32-bit risc micro delivers around 18Mips or 29kDhrystones at 25MHz with a power dissipation of less than 600mW.

It is aimed squarely at portable and hand-held applications, according to VTI's new product director Jeff Hendy. The chip is fully compatible with Sun, Dos and Macintosh operating systems.

Based on advanced samples, US computer maker Apple designed the chip into its *Newton* hand-held battery powered computer, launched recently, because of its combination of performance and low power – according to Apple *Newton* chief Larry Tesler. Apple reportedly clocks the chip at 20MHz so that it can run at 3.3V on 90mA of current supplied by batteries.

Based on the architecture developed by


VTI-backed Cambridge-based Advanced Risc Machines, the *Arm610* includes a 32-bit processor core, on-board memory management, 4kbytes of cache and a write buffer. It is functionally identical to the recently announced *Arm600* but comes without support for a coprocessor.

Made on VTI's 1µm cmos process samples are available now. A 0.8µm implementation will be sampled in September delivering 25Mips at 35MHz running on a 5V supply.

● Cambridge-based Acorn Computers is planning to launch a new generation of Archimedes PCs based around the *Arm600* risc microprocessor. The machines will deliver between 20 and 25Mips.

By integrating key logic circuitry, Acorn plans to cut the chip count and keep prices down. Plans involve eventually integrating memory control, video and i/o together with the processor core on a single chip.

LC

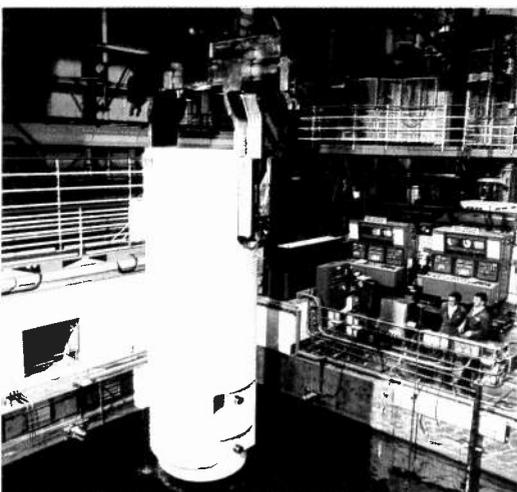


Removing an oxide fuel flask from the storage pond at BNF's new nuclear reprocessing plant. Safety at the 750 acre site relies on integrity of information, from field transmitters, ensured by signal conditioning equipment from Rochester Instrument Systems.

## Electronic holograms colour our world

A combination of computers and holograms may provide colour images in three dimensions suitable for designing cars and viewing holographic TV as a result of work carried out at Massachusetts Institute of Technology.

The MIT method relies on eliminating image details not essential in creating the image. To achieve this, a description of the information contained in a holographic image is transmitted from a supercomputer database in a type of semantic image encoding.

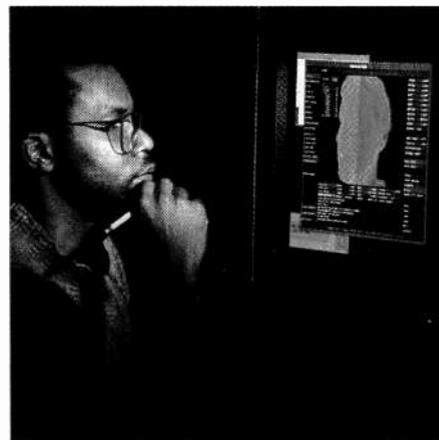
The computer takes these simplified image codes and converts them into signals representing the optical fringe patterns which will display a hologram made up of 192 horizontal lines. Each of the lines




GeorgiaTech: looking for a third dimension.
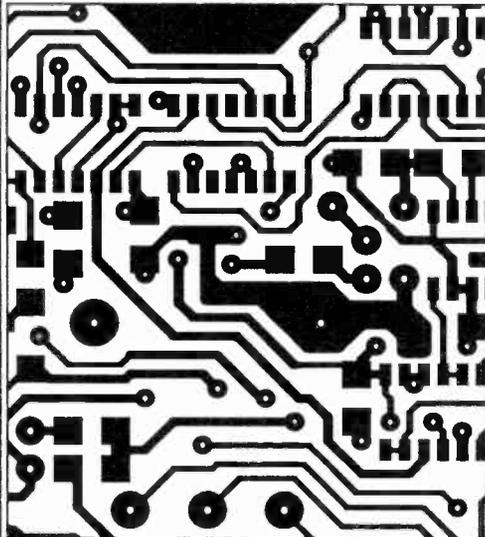
# EASY-PC PCB and Circuit Diagram CAD

Forget using tapes and lightbox! Create your Circuit Boards using CAD - like the professionals.



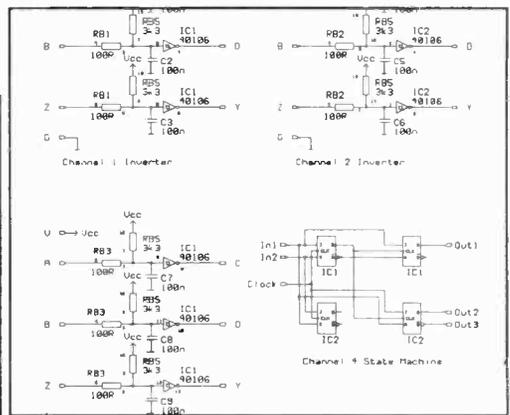- Runs on PC/XT/AT etc. with Hercules, CGA, EGA or VGA display and many DOS emulations.
- Design Schematics Single and Double sided and Multilayer boards including Surface Mount.
- Standard output includes Dot Matrix / Laser / Inkjet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Extremely powerful.
- Very easy to use.



## EASY-PC

Technical support is free, for life!


**Only  
£98.00!**

Plus P&P + VAT

Over 12,000 Installations in 70 Countries Worldwide!


Options:-500 piece Surface Mount Symbol Library £48,  
1000 piece Symbol Library £38, Gerber Import facility £98.

**DIGITAL  
SIMULATION     £195**

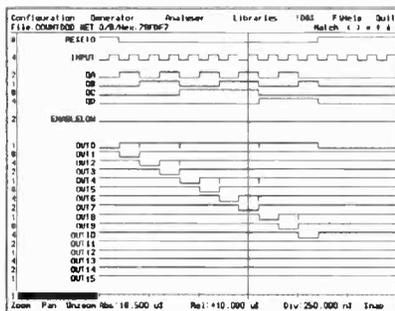


- At last! A full featured Digital Circuit Simulator for less than £1000!
- PULSAR allows you to test your designs without the need for expensive test equipment.
- Catch glitches down to a pico second per week!
- Includes 4000 Series CMOS and 74LS Libraries. 74HC/HCT libraries only £48.00 each.
- Runs on PC/XT/AT/286/386/486 with EGA or VGA.

**ANALOGUE  
SIMULATION     £195**

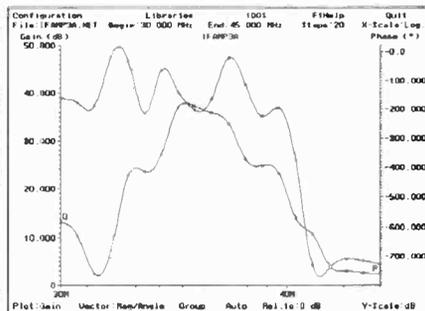

- NEW powerful ANALYSER III has full graphical output.
- Handles R's, L's, C's, Bipolar Transistors, FET's, OP-amp's, Tapped and Untapped Transformers, and Microstrip and Co-axial Transmission Lines.
- Plots Input / Output Impedance, Gain, Phase & Group Delay.
- Covers 0.001 Hz to > 10GHz
- For PC/XT/AT/286/386/486 with EGA or VGA.
- Very fast computation.

**SMITH CHART CAD  
£195**

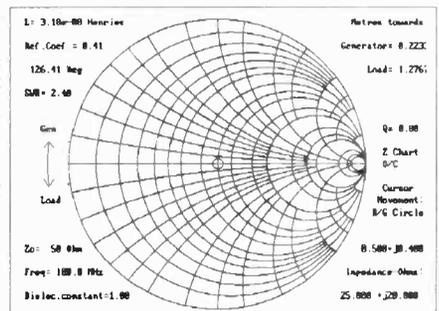

- Z-MATCH II simplifies RF matching and includes many more features than the standard Smith Chart.
- Handles transmission line transformers, stubs, discrete components, S Parameters etc.
- Supplied with many worked examples.
- Superbly easy to learn and use.
- Runs on IBM PC/XT/AT/386/486, CGA, EGA, VGA.
- Ideal for Education and Industry.

For full info Phone, Fax, or use enquiry card!

**Number One Systems Ltd. I**

REF: WW, HARDING WAY, ST. IVES, HUNTINGDON, CAMBS, ENGLAND, PE17 4WR.

Telephone: 0480 61778 (7 lines) Fax: 0480 494042

International: +44 -480-61778, Fax: +44-480-494042 ACCESS, AMEX, MASTERCARD, VISA Welcome.

- TECHNICAL SUPPORT FREE FOR LIFE!
- PROGRAMS NOT COPY PROTECTED.
- SPECIAL PRICES FOR EDUCATION.

CIRCLE NO. 106 ON REPLY CARD

contains 16 other lines to create 32,000 picture elements.

After removal of unnecessary holographic data, the light signals modulate radio frequency signals. These are then amplified and applied to three transducers connected to a tellurium dioxide, acousto-optical crystal. The resulting ultrasonic waves travel through the crystal, thus changing the refractive index as the pitch changes and the wavefront moves forward.

A laser sends light through the crystal which is diffracted. The laser beam hits a polygon mirror which freezes the information by spinning in the opposite

direction and at the same speed as the sound waves. At every 16 lines, a vertical scanner moves down a step for the scan line that follows. Finally, a lens focused on the spinning mirror magnifies the scan lines into a holographic image that appears to "float" in a background of black.

To date, the images have been simple ones such as three-dimensional cubes. More complex detail in a scene will require more complex code to achieve a holographic effect using the computer.

The Multimedia Laboratory at the Georgia Tech is also developing 3-D with an optical digitiser which automatically provides

detailed computer descriptions of three-dimensional objects. The device is intended to replace the tiring work currently done in manually digitising objects using a pen and other basic tools.

GeorgiaTech's scanner uses three video cameras to obtain data about an object's contours as it slowly rotates on a turntable. Proprietary electronic equipment converts the video input to the basic mathematical description that models complex objects. This information is stored in a standard .DXF format file which can then be manipulated in colour, form and texture. **Martin Cheek.**

## Wristwatch technology opens up mini hard disc market

**H**ewlett-Packard has launched a 1.3in 21Mbyte drive measuring 10.5mm by 36.5mm by 50.8mm. For the first time mini hard drives are appearing that rival the space and power advantages boasted by more costly memory chips – vital to the emerging generation of handheld electronic gadgets. Other drive makers led by US-firms Seagate and Conner are set to follow. Indeed, two weeks ago Seagate unveiled a 65Mbyte 1.8in drive.

Mini drive makers will be helped by the appearance of highly integrated disk drive control chipsets. Chip maker AT&T Microelectronics collaborated in developing the control chips for the HP drive – slashing



the chip count from 15 chips in a 1.8in drive down to eight – and has now launched its contribution as a stand-alone product called Reach 2.

With the annual worldwide market for mobile computer memories expected to reach \$20bn a year by the end of the decade, the race is on to develop cheap and small non-volatile mass storage.

Solid state memory gained an edge back in the early 1980s when the semiconductor arm of Japanese giant Toshiba developed flash memory chips which retain data when the power goes off. However, flash is still expensive. A 20Mbyte flash-based plug-in computer memory card costs around \$600. Compare that with the \$250 apiece volume price offered by HP for its 21Mbyte Kittyhawk 1.3in drive. That works out \$30 per Mbyte for flash as against \$12 per Mbyte for Kittyhawk. US chip maker Intel

is predicting that flash will reach \$10 per Mbyte sometime in 1995.

HP is confident mini drive costs will fall even further as production volumes increase.

HP is highlighting the built-in shock-sensing chip-based technology analogous to the air-bag crash systems being fitted to modern cars. The chip can sense a fall and brace the drive for the shock before it happens: it will survive a 1m drop on to concrete.

Manufacturing techniques borrowed directly from the watch making industry contribute to shock resistance. Indeed, HP has signed up Japanese watch maker Citizen to manufacture its new generation of mini hard drives..

The reliability of mini hard drive technology is also improving. HP is claiming a mean time between failures of 300,000 hours – over 34 years. Seagate claims 250,000 hours for its 1.8in drive.

The Kittyhawk mechanical module is designed to perform 100,000 start/stops without failing, over 100 times a working day for five years. This compares directly with the 100,000 read-write cycles available to eeprom type memory.

The use of different materials adds to the ruggedness and reliability of the mini drive. HP has opted to use sputtered, thin film glass-based media to make the double deck 1.3in diameter disks rather than conventional aluminium substrate media. Glass is stronger than steel in its unblemished form.

The material also has the advantage that it is inherently smoother than aluminium allowing the read/write heads to fly round closer to the surface.

But semiconductor mass memory scores in power consumption. Both HP's and Seagate's newly launched mini drives require 5V power supplies rather than the 3.3V standard that is emerging for battery powered handheld electronic devices.

"It's our firm intention to go to 3.3V as soon as we can," said HP market development manager Dayrell Drake. This will happen as soon as we can implement the full drive control chipset on a 3.3V

process, he said. And Seagate president Alan Shugart said that his company is also developing drives capable of running off 3.3V power supplies.

Flash also offers quicker access than hard drives. But the new HP mini drive powers up in 0.75s, has an average seek time of 18ms, a data transfer rate of 0.9Mbyte/s and a latency of 5.6ms. These should all improve as mini drives shrink further.

Capacity of mini drives also looks set to grow. The use of glass disk media has helped push the along track storage density up to 20,000 bits per linear cm and a track density of 945 tracks per cm. (Compared with 18,900 bits per inch and 780 tracks per inch on 1.8in drive technology).

That works out at a storage density of around 20Mbits per square cm. Densities of 330Mbits per square cm have been achieved in the laboratory and will eventually lead to 350Mbyte capacity double-platter mini drives. Currently, Kittyhawk only makes use of three of the four available storage surfaces, although new small head technology should allow all four surfaces to be used and may even make four-platter gigabyte drives possible.

Mini drives will be battling with flash memory for control of the potentially huge market for plug-in memory cards as well as going into the traditional hard drive market for built-in mass storage.

HP is already said to be working on a 0.9in version.

LC

### LM12458 FREE SAMPLES

Are you still waiting for your LM12458 sample pack? We know that quite a few people are and the reason is simply that National Semiconductor has been overwhelmed by the response to this offer.

Please have patience. All requests will be honoured although it might take another eight weeks to do so.

Meanwhile, if you have a commercial application which is being held back through lack of a sample pack, you are invited to contact National Semiconductor at its Swindon office: the company has held back a few packs for this contingency.

Editor

# Micro AMPS

## £99 8051 'C' COMPILER £99

- Preprocessor, compiler, optimiser
- Integer implementation
- Inline assembler
- Assembler level simulator and monitor
- Single chip to fully expanded memory
- Micro C is not a re-worked small C
- Other code generators available: 68HC11, 6809, 8085/Z80
- Low cost cross assembler available: 8031/8051, 6800/01/03/05/09/11, 8085/Z80, 8096

## £99 8051 BASIC COMPILER £99

- Integer BASIC compiler
- Supports single chip mode
- 8051 cross assembler included
- High level debugger runs on PC
- Standard Basic commands supported
- Specific functions to access 8051 SFRs and internal memory
- Line editor included, accepts text files
- Generates INTEL hex format output
- Output suitable for 87C751

## 8051 ICE (ICE51™)

- Low cost 8051 In-Circuit Emulator
- Low power, 5 volt operation
- Plugs directly into the 8051 processor socket on target hardware
- 32K Bytes of battery-backed RAM for program/data
- Single stepping and break points
- Assign memory and SFRs
- Upload/download INTEL hex files
- PC host software communicates via serial port
- Monitor file supplied in assembly form
- On-screen disassembly of code
- I<sup>2</sup>C drivers available
- Real time clock version available

™ ICE51 is a trademark of Intel Corp.

## 87C751 ICE (ICE751)

- Low cost 87C751 In-Circuit Emulator
- Emulation cable plugs into the 87C751 processor socket on target hardware
- On-board programmer for DIL devices
- PLCC adaptor available for 87C751
- Programs 87C752 DIL and PLCC devices through optional adaptors
- Monitor uses only 48 bytes of program memory
- Upload/download INTEL hex files
- Assign memory and SFRs
- Set break points
- I<sup>2</sup>C drivers available
- On-screen disassembly of code
- PC host software communicates via serial port

### 8051 BOOK

Architecture, Programming and Applications (£49.95). This book includes a free assembler and simulator for personal or educational use

### PEB552

The Philips evaluation board for the 80C552 processor variant, a monitor and programming adaptor are available for this product

### I<sup>2</sup>C

Quick Basic development tools available which includes I<sup>2</sup>C monitor program, I<sup>2</sup>C connector/cable assembly and parallel I/O demo board

### MACH 1

An RTX2000/1 PC based evaluation board featuring the RTX2001 RISC Forth processor capable of sustaining up to 12 MIPS

### ICC2000

An 8 channel intelligent communications card using the RTX2001 RISC Forth processor capable of sustaining up to 12 MIPS

### FORTH++

A low cost RTX200/1 compiler optimised for use on the IBM PC based MACH1 development board but can be interfaced to other boards

### The 8051: An Introductory Course

This is a one day course aimed at customers who need to become familiar with the MCS51 (8051) microcontroller family, and designed to give a detailed look at the generic 8051 processor facilities.



66 Smithbrook Kilns, Cranleigh, Surrey, GU6 8JJ, UK

Tel: +44(0)483 268999, Fax: +44(0)483 268397



## Shining prospect for cheap lasers

A research team at Bell Northern Research, a division of Northern Telecom, Canada, claims to have made a breakthrough in semiconductor laser design which will result in powerful, low cost devices for all branches of the public switched network.

The new device, smaller than a grain of salt, is called a circular-grating surface emitting laser. It emits a powerful, collimated circular column of light from its top surface that notably improves the coupling efficiency of laser light into optical fibres. In contrast, conventional lasers generate a divergent light beam that requires a precise positioning of the fibre to capture the light efficiently.

The new laser uses a circular grating, similar in appearance to the tracks of a compact disc, to reflect light upward. The grating, only a fraction of a millimetre in diameter, consists of hundreds of concentric

grooves, critically spaced to collimate the beam from an area 10,000 times larger than conventional lasers. The resulting low-divergence beam closely matches the numerical aperture (acceptance angle) of the fibre and facilitates the transfer of optical signals.

The active device is a multilayer laser structure of indium-gallium-arsenide-phosphide (InGaAsP), grown on an indium phosphide (InP) substrate that produces a wavelength of 1.3µm.

Because its surface emitting design can be fabricated as laser arrays, circular grating lasers could be integrated into advanced applications such as optical switching, optical computing, and optical backplanes.

BNR estimates that its new laser could reduce the price of telecomms quality lasers to tens of dollars, an order of magnitude reduction.

## Air robots fail challenge

The 1992 International Aerial Robotics Competition, organised by the Georgia Institute of Technology brought teams from eight colleges, more than twice as many as joined the first event in 1991. Four of the machines were able to fly at least briefly under their own computer control, and only one crashed.

The task of finding, retrieving and flying metal disks across a three-foot barrier was still too difficult for the student-built craft, which were designed to fly without a human operator.

But Georgia Tech is not discouraged: "We had more vehicles flying this year, and more vehicles flying autonomously for at least a portion of their flights," said Rob Michelson, vice-president of the Association for Unmanned Vehicle Systems, the event's sponsor. "They are moving toward longer and longer flights in which the vehicles are using their own sensing and intelligence to fly by themselves."

The armada of air vehicles assembled in Georgia Tech's Bobby Dodd Stadium included several helicopters, a billowing grey blimp, a "tailsitter" aircraft and the top scoring vehicle: a "flying gyroscope" based on a toy store hula-hoop and built for \$700.

After nine hours of flying and attempting to fly under the blistering sun, a panel of judges awarded prize to three home town teams: \$5000 to the Georgia Tech builders of the "flying gyroscope," \$3000 to the student builders of a helicopter from the Southern College of Technology in Marietta, and \$2000 to a second Georgia Tech team also fielding a helicopter.



**Remote sense:** Fresh air, solitude and a healthy lifestyle. What more could the villagers of Kilchiaran on the remote and beautiful Scottish island of Islay want? A digital telecommunications network it seems. That at least is the view of BT and the Highlands and Islands Enterprise. In a joint exercise they are spending £16 million to link the Islands into the digital world. Surely only the introduction of multi-story car-parks now stands between the islanders and complete integration into the 1990s.

## Virtual certainty for space

Scientists at Nasa's Ames Research Center are researching the possibilities of virtual reality as a tool for planetary exploration. A prototype multi-sensory virtual workstation contains a custom-built, head-mounted stereo video display, fibre optic gloves and magnetic motion trackers. It recognizes voice commands and can talk in its own electronic speech.

Researchers hope that virtual-reality tools will allow astronauts and scientists to get a feel for computer-generated worlds. For example, it will let scientists plan optimal routes for robots and humans to explore the surface of the Moon and Mars. Astronauts can also try out space repair tasks and perfect their skills before they launch.

With Nasa's developing technology,

researchers can also study the flow of air over an airplane or spacecraft from any angle, or take a supposedly realistic voyage into the heart of a black hole.

The virtual system contains a computerised description, known as the database, in which a user can study and manipulate objects. This database can be a physical place, such as a planet's surface created from digitised images sent back by space probes but it can also be abstract ozone levels at various heights in the Earth's atmosphere.

Nasa's system is capable of rendering 4000 flat-shaded polygons in 1/30th of a second, thus allowing smooth real-time animation of scenes of moderate complexity.

MC

### MISSING...

CUTTING ANTENNA TESTING DOWN TO SIZE - July issue: Those who read Mike Christieson's excellent article about antenna modelling in last month's issue may have been left wondering about the identity of the supplier of the equipment which formed the basis for the article. It was Feedback Instruments Ltd of Crowborough, 0892-663719 without whose assistance this article would not have been possible.

### ...LINK

ABI ELECTRONICS: Last issue subscribers missed out on an information insert prepared by ABI Electronics and circulated with newsstand copies. This issue we have included that information in the details of the Professional Services offer - see p.658.

Editor

# Omni-Pro II - The Next Generation

When you get a new product, what are your main concerns? Freedom from frustration is certainly one important consideration, for your time is valuable. You will want a product which is reliable and sophisticated, yet simple to use, with clearly written documentation. You will be looking for a high standard of technical support and regular upgrades for the product.

We at Dataman recognise how difficult it can be to choose between programmers which look and cost much the same. So, instead, why not concentrate your effort into choosing a reliable vendor. Dataman has been the leading vendor of low-cost programmers for as long as the

market has existed. Any of our customers will tell you that Dataman has always supplied excellent well-supported products. That's why we're still here! We take technical support seriously. We give you your money back, if you're not satisfied. These are important points to consider. But now let's take a look at some of the special benefits of owning Omni-Pro II.

## What Benefits?

Well, for instance, the interface is not via the computer's parallel port, which is speed-limited, and probably connected to your printer. A dedicated plug-in half card performs fast data transfers.

The software is a professional package in full colour that will run in only 400K of RAM. What's more it will run on any PC/AT or compatible - even the latest 486 machines. That's because Omni-Pro II has its own independent clock - some programmers rely on the computer for timing, and won't work with faster machines.

Ground pins are connected by relays - not by logic outputs. Some vendors won't approve programmers which don't ground pins in this way.


The 40-pin Textool socket can be changed without even having to remove the cover. A complete range of PLCC adapters is available.

## Truly Universal

Omni-Pro II has universal pin-drivers which will accommodate a very wide selection of parts. You can program BIPOLARS, PROMS, E/EEPROMS, PALS, GALS, FPLAS, PEELS, E/EEPROMS and MICRO-CONTROLLERS. The latest FLASH EPROMS are supported too. The list has 1250 devices already and substantial numbers of new devices will be added

FREE every quarter.

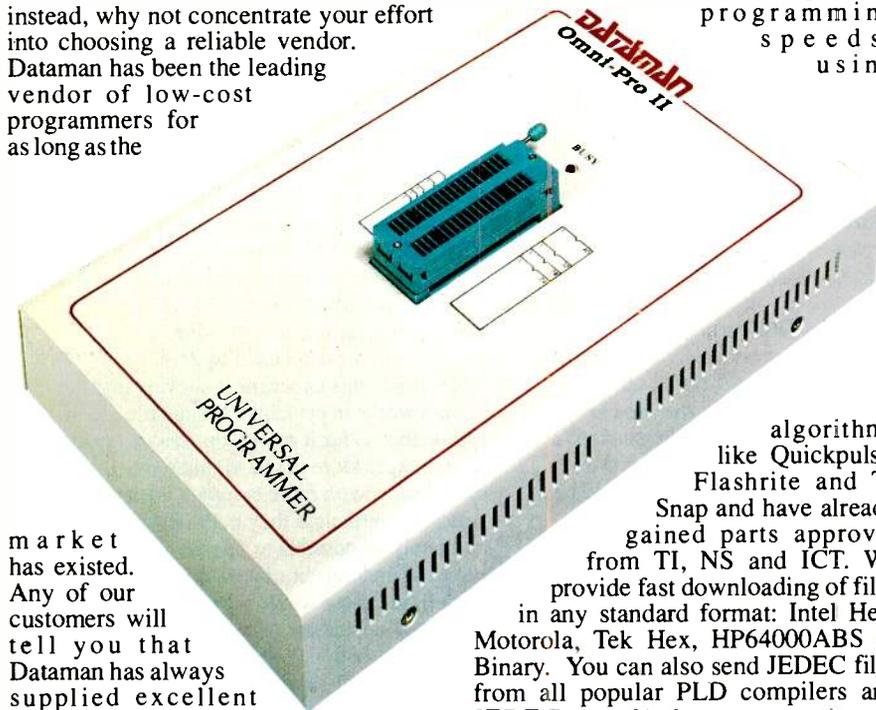We have optimised programming speeds using



algorithms like Quickpulse, Flashrite and TI Snap and have already gained parts approval from TI, NS and ICT. We provide fast downloading of files in any standard format: Intel Hex, Motorola, Tek Hex, HP64000ABS or Binary. You can also send JEDEC files from all popular PLD compilers and JEDEC standard vector testing is supported: a full array of test condition codes can be generated.

*Remember - you get a 30 day money-back guarantee, FREE quarterly software updates and FREE technical support - as much as you need. Phone now for a free Demo Disk and up-to-date Device-List.*

Omni-Pro II comes with a FREE copy of NS's superb Open Programmable Architecture Language - OPAL Junior.

**Omni-Pro II - complete ..... £495**

## Gang-of-eight Programmer..... £395

This production programmer from Dataman can handle all 25 and 27 pin EPROMs up to 512K bits. Programs eight copies from a master EPROM, or from an object file. The G8 offers fast programming methods and three, user-selectable programming voltages. G8 is clearly designed for the busy workshop being supplied, as standard, in a high quality steel case.

## Software Development from £195

Dataman's Software Development Environment, SDE, comprises a two-window Editor, Macro Assembler, Linker, Librarian, Serial Comms and intelligent Make facility. The latter reassembles selectively just those files you have edited, links them and downloads the object-code to your Emulator or Programmer. It's quick and painless. If the assembler finds a mistake it puts you back in the Editor at the right place to fix it.

The Multi-Processor version supports all common micros - please ask for list. The Disassembler makes source files out of object code - from a ROM, for example. SDE is not copy-protected.

SDE Multi-processors & Disassemblers.....£695

SDE Multi-processors (includes 82 micros) ...£395

SDE Single-processor.....£195

## OPAL from NS ..... £297

Are you looking for a PLD design tool? Then OPAL could be just what you need. It supports state machine, truth table and Boolean equation entry, also optimisation, verification and implementation, for a great many PLDs.

## Erase an EPROM in ten seconds!

Simply hold the gun right over the EPROM's window and squeeze the trigger. The strobe eraser puts out intense UV light at the right wavelength (253.7nm). Erase EPROMS on the bench, in the PCB or in the programmer.



**Strobe Eraser.....£175**

*UK customers please add VAT. Major credit cards accepted. UK delivery available next working day.*



Station Road, MAIDEN NEWTON, Dorset DT2 0AE, England

Phone .....0300-20719

Fax.....0300-21012

Telex .....418442

Bulletin Board.....0300-21095

(300/1200/2400/9600 V. 32)

# REGULARS

## RESEARCH NOTES

### How to sneak up on a submarine

A new “silent” method of detecting underwater objects offers the chance to track submarines without the submariners being aware that they are under observation. The technique is entirely passive – unlike sonar, the acoustic equivalent of radar – and no sound is emitted from the equipment itself, making it ideal for any covert form of monitoring.

Fundamental to the new technique – described by researchers from the Scripps Institution of Oceanography in La Jolla, California, and Florida Atlantic University (*Nature*, Vol 356 No 6367) – is the presence of a continuous and continual spectrum of underwater background noise. At all frequencies up to around 50kHz there is a constant wash of sound created by breaking waves and by wind on the sea surface (Fig. 1).

Because of the obvious analogy with white light the researchers describe it as acoustic “daylight”, and what they are now working on is the acoustic equivalent of daylight photography.

But compared with photography, the use of natural underwater noise is fraught with

difficulties, the most limiting of which is sound absorption in the ocean. Although acoustic energy travels better in water than in air, the team reckons that a useful detection range for their system would be about 1km at 20kHz. Lower frequencies suffer less attenuation, but would offer much less in terms of angular resolution.

Even at 50kHz – considered the maximum practical limit where thermal noise swamps ambient noise – the wavelength of sound in seawater is around 3cm. This is around 100,000 times longer than the wavelength of green light in air. The researchers admit in their paper that an acoustic system would need an aperture of around 600m to achieve a similar resolution to the human eye!

Nevertheless they say that a very useful performance could be achieved by image enhancement techniques of the sort used in synthetic aperture radar and infra red remote sensing. They add that, unlike active sonar systems, acoustic daylight techniques would actually benefit from unwanted noise sources and from multipath reflections underwater. This would make them idea for

use in harbours, estuaries and in the vicinity of oil rigs.

To test the principle, a 1.22m diameter parabolic reflector fitted with a low-noise hydrophone was lowered off the end of the Scripps pier. Three rectangular plywood targets 0.9m x 0.7m were then lowered into the sea about 7m from the reflector; they could be rotated on a vertical axis, thus making them alternately “visible” and “invisible” to the detector (Fig 2).

Results of this experiment showed that the system works in principle, though the group admits that so far it represents just one pixel of an image. More pixels would require more beams with more complex acoustic optics. Nevertheless they believe it should ultimately be possible to display a colour image of underwater objects on a screen. Such false colour would represent the frequency-dependent reflectivity of the objects in question. Even without the colour, an acoustic daylight system would offer what no current active systems offer – a pictorial output that can be interpreted by untrained operators.

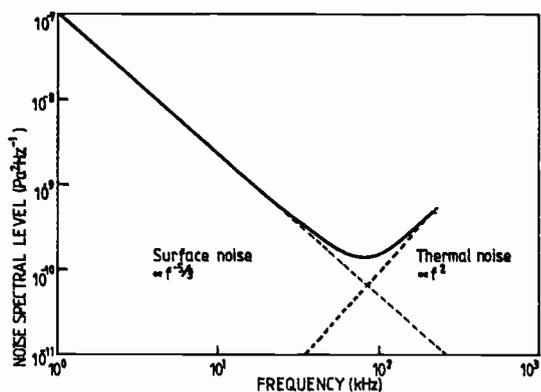


Fig. 1. At all frequencies up to around 50kHz there is a constant wash of sound.

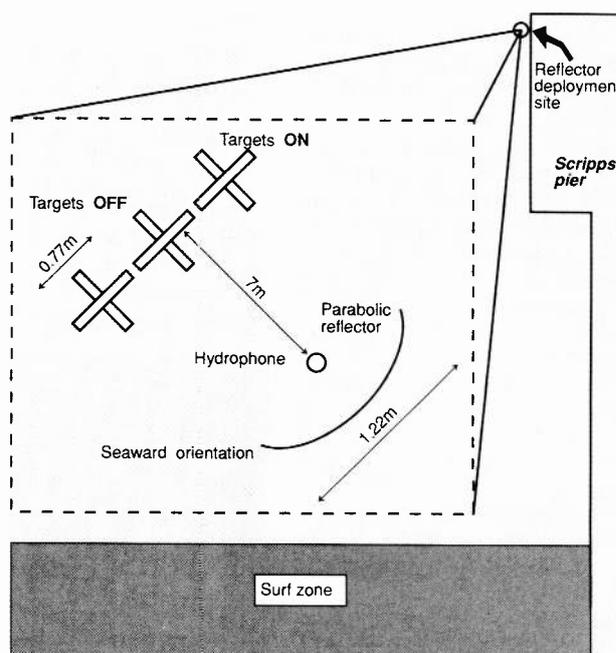



Fig. 2. Evaluating underwater testing using ambient sound.

## Hot tip for a Braille interface

Blind people may find it a little easier to make more effective use of computers thanks to a development by electronics engineer Gilbert De May and psychologist Andre Vandierendonck of the University of Ghent in Belgium. De May and Vandierendonck have built a new output device that translates electrical signals into Braille that can be read with the fingers. But unlike existing electromagnetic readers or Braillers that use paper or raised pins, the Belgian device translates the signals into heat.

De May says that the technology is really nothing more than thick film resistance elements printed onto a ceramic substrate. The individual elements are dots 0.25mm across and arranged in the standard Braille pattern, ie a vertical 3 x 2 matrix. The eventual idea is to stack the units so as to make 80 characters available at once. Each character is switched off immediately it has been read so as to prevent the substrate heating up and destroying the heat differential.

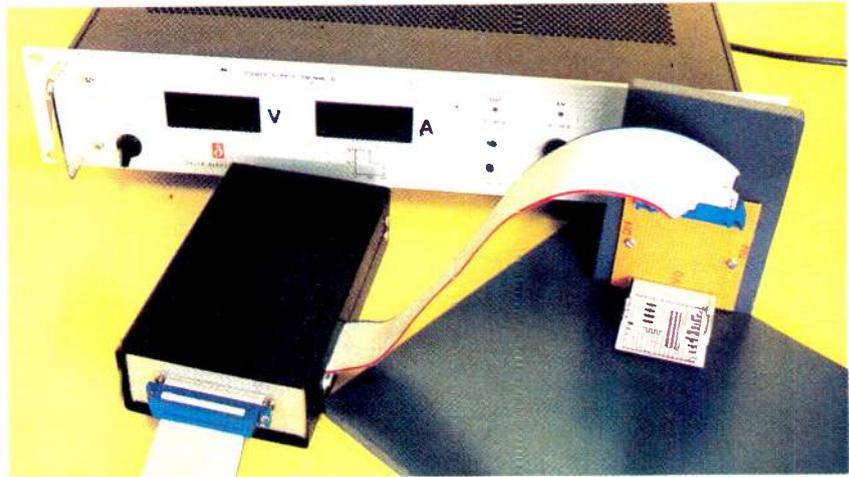At the moment the researchers are testing prototypes on both blind and sighted people and the results are encouraging. They reckon that the use of



eight instead of six resistors will enable the system to create not just Braille, but also normal english characters and mathematical symbols. Given several rows of characters, it should also be possible to make graphics that are readable by blind people.

Depending on how much support is forthcoming from industry, De May believes it ought to be possible to produce

**Sensitive technology:** blind computer users could benefit from a new device which makes use of heat to convey alphanumeric and graphics.

a whole screen thermal reader for no more than £350. This compares with several thousand for current 80-character electromagnetic device.

## Reversing the effects of electric shock

Future victims of high voltage industrial accidents may have a better chance of recovering from the associated severe tissue damage. The possibility has been opened up by researchers at the University of Chicago Medical Center who claim to have demonstrated, for the first time, the ability to repair damaged cell membranes in the body.

Their treatment, described in a paper published in May in the *Proceedings of the National Academy of Sciences*, depends on intravenous injection of an industrial emulsifier – a poloxamer – to prevent and even reverse much of the damage caused by severe electrical trauma.

Dr Raphael Lee, author of the paper, says that although the work has so far only involved animal organs there is clear evidence from tissue culture studies that the substance is just as effective at restoring the damaged membranes of human cells. Clinical trials in humans with life-threatening or limb-threatening injuries caused by high-voltage electrical energy are expected to begin next year.

In a series of studies, Lee and colleagues Philip River, Fu Shih Pan and Robert Wollman, exposed muscles, which were still attached by the artery and vein to the hind legs of rats, to high-voltage supply,

simulating a typical industrial accident. The shocks were strong enough to cause severe damage to the muscles – the tissue most vulnerable to electrical trauma – but brief enough to avoid the excess tissue heating caused by extended contact.

Each rat showed immediate evidence of tissue damage in the shocked limb. Electrical impedance, a sensitive measure of all membrane damage, fell abruptly by 50%.

Twenty minutes after the shock, the rats were injected with either poloxamer, a saline solution or a solution of saline plus neutrally charged dextran. Rats which received the poloxamer showed dramatic and lasting recovery. Within 15min, the electrical impedance in the isolated muscles returned to 77% of normal, enough of a recovery to rescue the tissue. "The recovery was not complete," says Lee. "But the critical defect, damage to the cell membrane, was apparently repaired and the cells remained viable."

Although an estimated 2500 Americans each year are victims of industrial accidents resulting in severe electrical trauma and another 1000 to 1500 are hospitalised for injuries caused by lightning, fundamental research into the precise mechanism that causes those injuries is still in its infancy.

### Mechanism revealed

Progress in treating electrical trauma has long been hampered by misunderstanding of the basic mechanism of tissue damage caused by an electrical current. Until recently, the damage was primarily attributed to thermal mechanisms, excessive heating in the region through which the current passed. In many electrical trauma victims, the thermal injury may be less important; cell-membrane damage resulting from exposure to a strong electric field is probably the central event leading to tissue death.

Cells in a current's path, Lee has demonstrated, are damaged by a process called electroporation. Electric forces bore minute pores into the cell's membrane, which allows substances outside the cell, primarily calcium and sodium ions, to flow in unregulated. If the pores become large enough, the cell ruptures, spilling out its contents like a water-filled balloon pricked with a pin.

The timing of cell death is also unusual; tissues damaged by pure electrical forces can appear perfectly healthy hours after the injury and still not survive.

While nothing can salvage the charred cells near the points of contact with a

powerful electrical current, there is a window of opportunity for cells damaged primarily by electroporation. From 30min to as long as a few hours after contact, even perforated cells can be saved. The injected poloxamer is taken up by damaged cells, where it apparently seals the tiny leaks in the membranes and allows the repair process to begin.

Details of timing, dose and methods of delivery of poloxamer – as well as new diagnostic tools to assess electrical damage

prior to treatment and measure the effects of therapy – are still being refined. Lee and his colleagues hope to begin clinical trials of poloxamer for electrical trauma victims once the precision of these diagnostic tests has been confirmed.

Since the chemical has long been approved by the Food and Drug Administration for other medical uses, this finding sets the stage for the development of effective medical therapy for victims of high-voltage electrical shock.

Southern California. The samples came from autopsies of seven patients within 12 to 24 hours after their deaths. (Four of these patients were suspected of having Alzheimer's Disease, and three were not. The researchers noted no systematic differences between the brains of the Alzheimer's patients and the others in their magnetic characteristics.)

To avoid possible metallic contamination, brain samples were dissected using ceramic or Teflon-coated instruments. The samples were transported to a magnetically shielded, dust-free clean room within Kirschvink's Caltech laboratory. In this room elaborate precautions are taken to keep microscopic dust particles, some of which are magnetic, from contaminating the samples or the chemicals used in their preparation.

Kirschvink says he is struck by the similarities between the human magnetite and the magnetite found in magnetic bacteria. Magnetic bacteria sometimes have long strings of magnetite crystals organised in cellular organelles called magnetosomes. These bacteria clearly use the magnetosomes to sense the Earth's magnetic field. Bacteria swimming in a pond could use information about the Earth's magnetic field to tell up from down, as long as the pond wasn't right on the equator, since magnetic field lines descend into the Earth's interior. A bacterium that wanted to go down, away from the surface and toward the nutrient-rich mud on the bottom, would follow the north pole of its magnet in the northern hemisphere and the south pole of its magnet in the southern hemisphere."

Kirschvink emphasises, however, that the amount of magnetite in the human brain is tiny – less than 70ng/g of tissue. It is so little that he doubts if it will ever be found *in situ*.

He is also unsure about the practical significance of his discovery. "Our studies of the magnetite crystals we isolated from human brain tissue show that they could be moved around by magnetic fields only slightly stronger than the Earth's natural magnetic field. If, for example, these crystals are coupled to ion channels within human cells, electromagnetic fields could be opening and closing these channels, with unknown biological consequences."

Kirschvink says he knows his study has the potential to be misunderstood. "I want to be absolutely clear about what I am saying and what I am not saying. Yes, there is magnetite in human brain tissue. Yes, it is possible that the presence of magnetite may mediate any health effects of electromagnetic fields. But in my opinion, the jury is definitely still out on whether electromagnetic fields actually do have health effects."

He also states, explicitly, that he as yet sees no evidence that humans have a magnetic sense. ■

## The magnetic attraction in all of us

Molluscs, bacteria, honeybees, pigeons and salmon all have it – and so do human beings according to a team at the California Institute of Technology: magnetic sense.

Researchers, led by Dr Joe Kirschvink, have reported isolation of microscopic crystals of the magnetic mineral magnetite from samples of human brain tissue. Presence of the magnetite may explain a variety of observations from the apparent existence of a primitive human magnetic sense, right through to some of the possible biological effects of electromagnetic fields that have been hotly debated in these pages.

Kirschvink's paper: "Magnetite Biomineralisation in the Human Brain," has been accepted for publicity in the

*Proceedings of the National Academy of Sciences* and was recently revealed at a news conference hosted by Caltech.

The presence of magnetite in biological materials is something that has been known for a long time, and the fact that it has now been demonstrated in human tissue is therefore no great surprise. But it does provide a plausible mechanism for the ability of humans to sense or react to electromagnetic influences. This is especially so since the magnetite crystals are not only permanently magnetised, but also exhibit metallic-type electrical conductivity.

The scientists obtained samples of human brain material from the Alzheimer's Disease Research Center Consortium of

## World's smallest mosfets

A team from IBM's Thomas J Watson Research Center in Yorktown Heights, NY, claim to have made the world's smallest transistors. These experimental devices – n-channel mosfets – are a mere 700nm by 150nm and are enclosed by an isolation trench 150nm wide. Within this structure is a gate electrode of 100nm by 150nm, while source, drain and gate contacts measure 150nm by 200nm.


The IBM team, who presented details of their achievement at the 36th

International Symposium on Electron, Ion and Photo beams, in Orlando, says that overlay and fabrication tolerances need to be within 25nm for all levels of the device. These tolerances were achieved using special electron beam nanolithography fabrication techniques which IBM says are not necessarily appropriate for mass production at the present time.

The new transistors, which operate at room temperature, are scaled down versions of conventional mosfets and work along entirely conventional lines. This is in spite of the fact that the dimensions are in the size range where quantum effects would be expected.

Work is now going on to optimise the device characteristics and to test them as part of prototype high speed logic and memory circuits. The intention is to implement them in cmos and eventually to create 4Gbit dynamic random access memory chips within the first decade of the 21st century

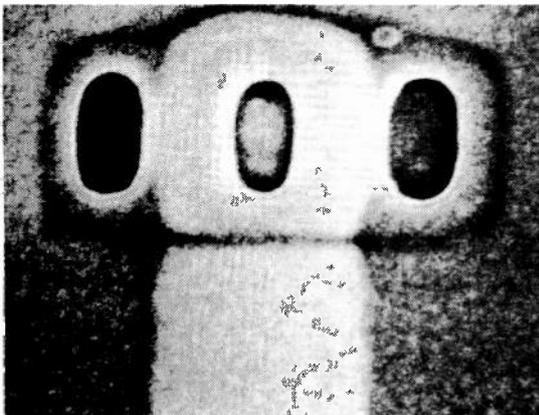*Smaller than a wavelength of visible light. IBM's mosfets may eventually find themselves in gigabit memories.*



# IEEE-488.2

for Your PC

## PC, PC AT, and PS/2 Boards


- 100% IEEE-488.2 compatible
- NAT4882™ IEEE-488.2 Controller chip
  - Optimised GPIB functionality
- Turbo488™ performance chip
  - Over 1Mbytes/sec reads and writes\*

\*Between boards, adhering to IEEE 488.1 SECTION 5.2.3

## Windows and DOS Software

- High-speed IEEE-488.2 routines
- Standard NI-488™ functions
- HP-style commands
- Standard Windows DLL entry points
- Interactive control utility
- Controller and Talker/Listener functions

## Call for Free 1992 Catalogue

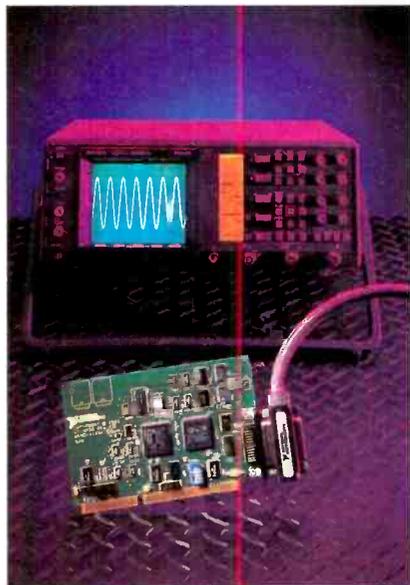

Corporate Headquarters USA (512) 794-0100  
 Branch Offices: AUSTRALIA 03 679 9422 • BELGIUM 02 757 00 02  
 CANADA 519 622 9310 • DENMARK 45 76 73 22 • FRANCE 1 48 65 33 70  
 GERMANY 089 714 5093 • ITALY 02 4830 892 • JAPAN 03 3798 1921  
 NETHERLANDS 01720 45761 • NORWAY 03 846866 • SPAIN 91 896 0675  
 SWEDEN 08 984 970 • SWITZERLAND 056 45 58 80 • U.K. 0635 523 545




21 Kingfisher Court  
 Hambridge Road  
 Newbury, Berkshire  
 RG14 5SJ  
 Tel: 0635 523 545  
 Freephone: 0800 289 877  
 Fax: 0635 523 154


Product names listed are trademarks of their respective manufacturers. Company names listed are trademark or trade names of their respective companies. © Copyright 1992 National Instruments Corporation. All rights reserved.

CIRCLE NO. 145 ON REPLY CARD
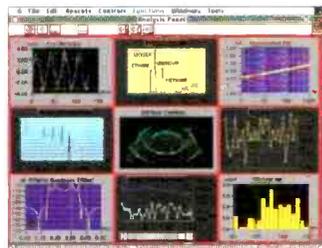
# INSTRUMENT CONTROL AND DATA ACQUISITION SOFTWARE



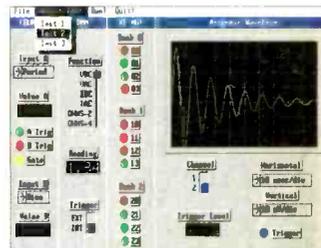LabVIEW™ 2 – For the Macintosh  
 Graphical Programming Environment



LabWindows® – For DOS computers  
 Program Development Tools For C and BASIC

**ACQUISITION** – Integrated libraries for GPIB, RS-232, and VXI instruments, and A/D-D/A-DIO plug-in boards

**ANALYSIS** – Extensive libraries for data reduction, digital signal processing, digital filtering, and statistical analysis

**PRESENTATION** – Flexible high-performance graphical user interface and report generation

CALL FOR FREE DEMO DISK



National Instruments UK  
 21 Kingfisher Court  
 Newbury, Berkshire  
 RG14 5SJ  
 Tel: 0635 523 545  
 Freephone: 0800 289 877  
 Fax: 0635 523 154

Corporate Headquarters USA  
 Tel: (512) 794-0100  
 Fax: (512) 794-8411

CIRCLE NO. 146 ON REPLY CARD

# DSP

High-Performance Digital Signal Processing for Your Computer

## PC-AT


- AT-DSP2200 plug-in board
- AT&T WEDSP32C processor
- 25 MFLOPS
- Two 16-bit analogue input channels
- Two 16-bit analogue output channels

## Macintosh NuBus

- NB-DSP230X Series plug-in boards
- TI TMS320C30 processor
- 27, 33.3, or 40 MFLOPS

All DSP boards have the RTSP™ bus to synchronise multiple boards and transmit serial data. NI-DSP™ driver software is also included with all boards.

## Call for Free 1992 Catalogue

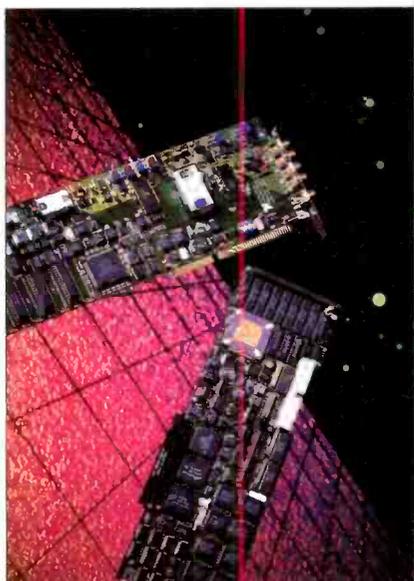

Call for Free  
 DAQ Designer™ Software




National Instruments U.K. Corporation  
 21 Kingfisher Court  
 Hambridge Road  
 Newbury, Berkshire  
 RG14 5SJ  
 Tel: (0635) 523545  
 Freephone: 0800 289 877  
 Fax: (0635) 523154

U.S. Corporate Headquarters  
 Tel: (512) 794-0100  
 Fax: (512) 794-8411



© Copyright 1992 National Instruments Corporation. All rights reserved. Product and company names listed are trademarks or trade-names of their respective companies.

CIRCLE NO. 147 ON REPLY CARD

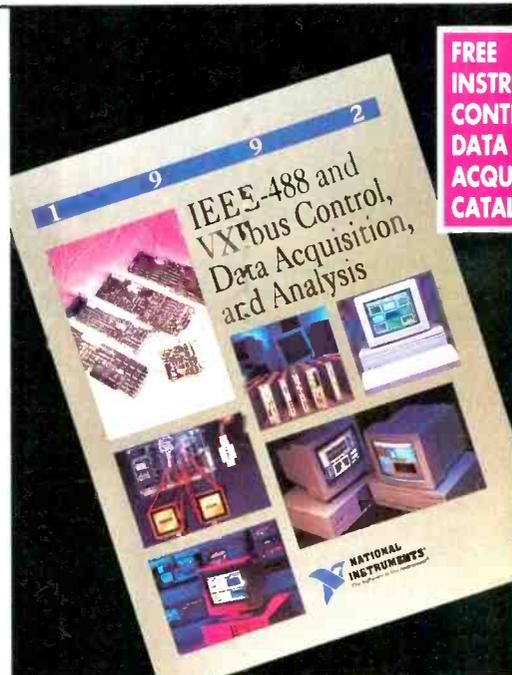

FREE  
 INSTRUMENT  
 CONTROL AND  
 DATA  
 ACQUISITION  
 CATALOGUE

Free 1992 catalogue of instrumentation products for PCs, workstation, and more. Features IEEE-488.2 interfaces and software, plug-in data acquisition boards, VXIbus controllers, DSP hardware and software, and signal conditioning accessories. Application software for complete acquisition, analysis, and presentation of data, including graphical user interfaces. Application tutorials and training classes also detailed.


CALL (0635) 523 545 or  
 (0800) 289 877 (Free phone)  
 Fax: (0635) 523 154



National Instruments UK  
 21 Kingfisher Court  
 Hambridge Road  
 Newbury, Berkshire RG14 5SJ

© Copyright 1992 National Instruments Corporation. All rights reserved.

CIRCLE NO. 148 ON REPLY CARD

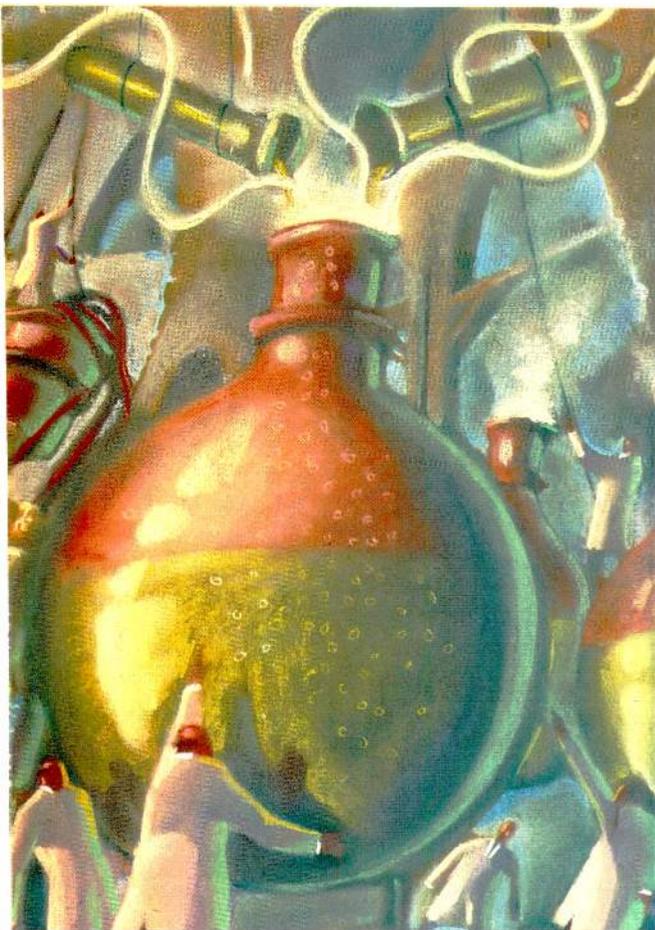

# DIRECT DIGITAL SYNTHESIS

*Direct digital synthesis is changing the way that RF engineers design radio systems. Capable of producing stable, clean carrier waves well into the UHF spectrum, these systems lend themselves to chip integration and require few, if any, conventional RF components. A new design series by Ian Hickman.*

**T**here has been a steadily increasing degree of interest, especially in recent years, in direct digital synthesis. The technique emerged in the early '80s and was probably known in principle for several years before that.

In those early days, the highest output frequency attainable was no more than a few MHz, limited by the performance of the logic ICs and dacs (digital to analog converters) then available. A prototype DDS at the Roke Manor laboratories of the then Plessey company in 1981 occupied several complete boards of logic laid out on the bench and, being clocked at 10MHz, provided an output frequency of up to about 3MHz, with all spurious responses about 40dB down on the wanted output.

Since then, with advances in semiconductor technology, the attainable performance has increased by leaps and bounds: DDS chips realised in gallium arsenide now provide output frequencies of over 400MHz. Silicon technology delivers output frequencies in excess of 300MHz. However, at least when operating

at the top end of their frequency range, the worst case levels of spurious outputs have not changed much, still being in the region of 40 to 45dB down on the wanted output. The reasons for this will be covered later on but, before looking at the advantages and limitations of DDS in detail, it will be useful to compare it with the various other methods used for the generation of an RF carrier.

The temperature and long term frequency stability of an LC oscillator is generally poor; it is difficult to construct a small inductor with a stability of much better than 0.01%, while its spectral purity (noise sidebands) can only be reduced by increasing the operating Q of the tuned circuit. This again is not easy especially in miniaturised equipment: a working Q in excess of 100 is good going at HF, although at V/UHF and microwave where cavity resonators become feasible, a Q of thousands is possible.

In fixed frequency applications, the situation is much more rosy; a crystal resonator can have a Q in the range 10000 to a million, making it possible to design oscillators with very low sideband noise and excellent temperature and long term stability, especially if the crystal is maintained at a constant temperature in an oven.

## Direct synthesis

The ideal carrier generator would be one with the tuning capability of an LC oscillator but the stability and purity of a crystal oscillator – and the next major advance in frequency generation provided just this.

Clearly, with just two crystals, at frequencies  $f_1$  and  $f_2$ , one can obtain four different frequencies by mixing them so as to provide also  $(f_1 + f_2)$  and  $(f_1 - f_2)$ , while if you use harmonics or subharmonics of  $f_1$  and  $f_2$  as well, the possibilities rapidly increase. This principle can be extended to any frequency to be

generated and with any desired degree of resolution.

This system was called a direct synthesiser, since ultimately the output frequency was obtained from one master crystal oscillator and had almost the purity of this master. A good example was the General Radio 1160 series of lab bench synthesisers, where additional decade plug-in units could be added to provide as many significant digits of resolution as required (at a price). The term "direct analogue synthesiser" is sometimes now used to describe this type of instrument, to distinguish it from the direct digital synthesiser. The basic operating principle of the direct synthesiser is ingenious, see Fig. 1.

Although different manufacturers used frequencies differing from those shown, the principle was the same. It can be seen that the output frequency is the same as the input frequency, but that the resolution has been increased by a factor of ten. So if the output is used as the input to another similar block of circuitry, a 1MHz tuning range with 10kHz resolution is available. This scheme can then be further extended with additional blocks to obtain whatever resolution is required. Note that Fig. 1 only uses seven fixed frequencies to obtain the ten output frequency steps, and that all additional modules will use only these same seven frequencies, all of which can be obtained from the synthesiser's internal 10MHz reference source, or from an external 10MHz frequency standard if required. The divide by ten stage at the output of the block reduces by 20dB any phase noise and spurious outputs which may have been introduced in obtaining the reference frequencies and in the mixing processes.

The scheme can be simplified somewhat by adding resolution a factor of two (one bit) per stage, instead of a factor of ten per stage and this scheme was adopted in the Ailtech model 360 signal generator and derivatives, now out of production. The result was exceptional output purity - sideband noise of -100dB at 10Hz off tune and 1Hz resolution over a 1GHz range. The only disadvantage was cost; also size and weight if you had the job of moving it from one lab to another! Other advantages of direct synthesis include a very fast frequency change capability (switching speed in the microsecond region) and very low non-harmonically related spurious outputs, typically -80dB.

Where high purity, low spurious outputs and fast switching are all required, direct synthesis is an attractive route, at least in the case of lab and ATE equipment, but the size and cost make it difficult to apply in portable, military or OEM equipments.

**The phase locked loop**

The next technology for carrier generation was the PLL (phase lock loop) technique. This is widely applied in space applications, e.g. for synchronising a receiver to a space craft signal with Doppler shift, or a varying shift if the craft is tumbling or spinning, an application described in Reference 1. An even earlier

**SETTING THE RELATIONSHIPS**

Designate the clock frequency as  $F_c$  with  $t = 1/F_c$  being its period, the output frequency as  $F_o$  with  $P_o = 1/F_o$  being its period, and the current value of the FSW as  $F_p$ . Let the accumulator be  $N$  bits wide and let the most significant  $M$  of these control the rom (which it is assumed holds one complete cycle of sinewave). Thus  $2M$  bits correspond to  $360^\circ$  so that (referring to the

figure) the MSB of  $M$  (and  $N$ ) corresponds to  $180^\circ$  and the LSB of  $M$  corresponds to  $(360/2^M)^\circ$ .

Likewise, the LSB of  $N$  corresponds to  $(360/2^N)^\circ$ .  $(360/2^N)^\circ$  is thus the smallest possible phase increment and the phase of  $F_o$  must advance by at least this amount in time  $t$ . The value  $F_p$  of the FSW thus corresponds to a phase increment of  $F_p(360/2^N)^\circ$  and one cycle will therefore be complete after  $\lceil 360/(F_p(360/2^N)) \rceil$  clock cycles, i.e. after  $2^N/F_p$  clock cycles. Therefore one output cycle is completed in a time  $P_o = 2^N t / F_p$  and since  $F_o = 1/P_o$ , then  $F_o = F_p / 2^N t$ . But  $t = 1/F_c$ , so  $F_o = F_c F_p / 2^N$ . This is independent of  $M$ . It is as well to emphasise that the FSW is actually a phase (increment), not a frequency. Its value sets the rate of change of phase of  $F_o$ , and the differential of phase with respect to time is of course frequency.

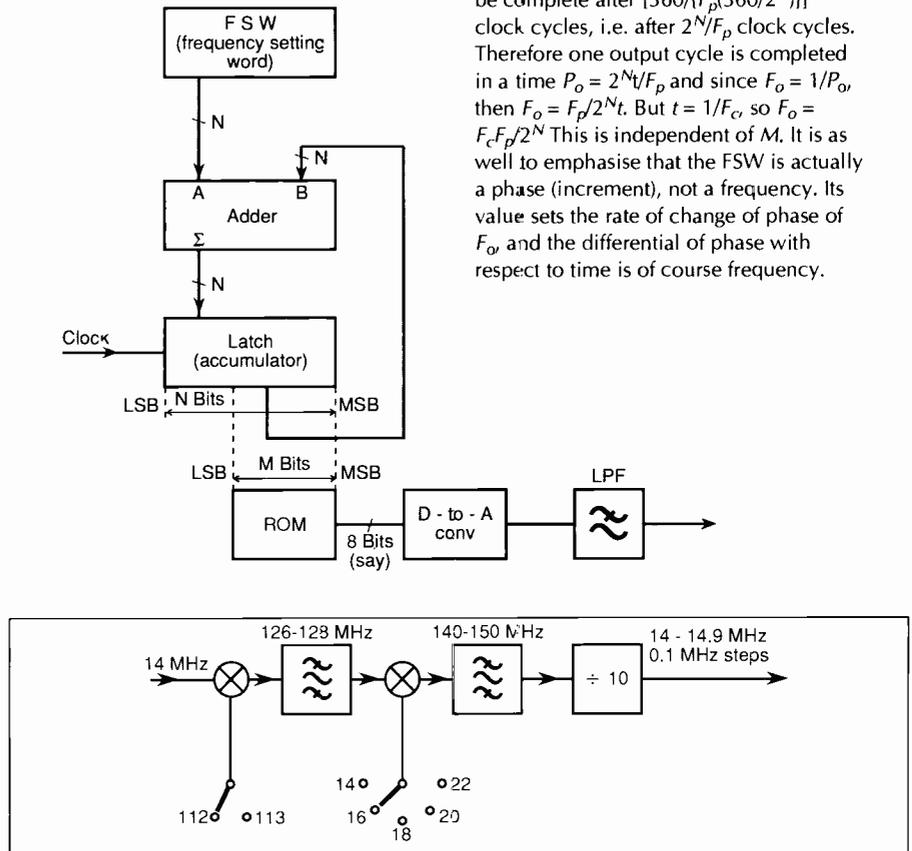


Fig. 1. Principle of the conventional direct synthesiser. The mix filter/divide block provides 100kHz steps. Using the output as the input to another similar block provides an output with 10kHz steps. Further blocks can be added to provide any required degree of resolution. High performance filters and careful screening within and between blocks enable all non-harmonically related spurious to be held at 80dB down on the wanted output, at a price.


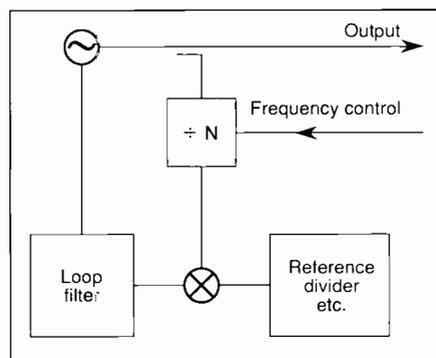


Fig. 2. Principle of the phase-lock loop synthesiser. A sample of  $F_{out}$ , the output of the VCO, is divided by  $N$  and mixed with a reference frequency  $F_{ref}$ . When these two frequencies are exactly equal the loop is said to be in lock with a DC component in the mixer's output. This is extracted by the loop lowpass filter and applied to the VCO's tuning input: the overall loop feedback is negative and maintains equality between  $F_{out}/N$  and  $F_{ref}$ . Additional measures are often employed to assist loop lock-up and further arrangements can enable  $N$  to be effectively non-integer.

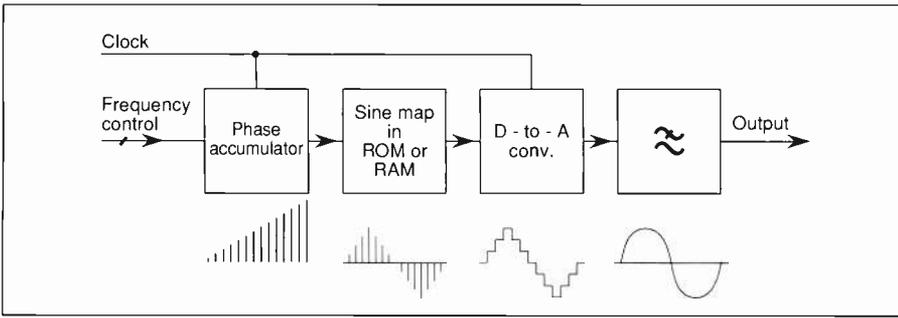

**Figure 2** shows the block diagram of a system for producing an output at  $N$  times the reference frequency, which may itself be obtained directly from a crystal oscillator, or be a sub-harmonic of it obtained by divider circuits. When the loop is in lock, the output of the divide by  $N$  stage is at exactly the same frequency as the reference, but there will be a small phase offset, leading or lagging, resulting in a DC component in the output of the mixer. This is applied (often after amplification) via a lowpass filter to the varactor in the voltage controlled oscillator and results in exactly the desired output frequency.

If  $N$  is set to a different value, the output frequency will change; thus if  $N$  is changed to, say  $N + 2$ , the output frequency will increase by twice the reference frequency. Special arrangements, not considered here, are used to ensure that the loop locks up at the desired frequency. Figure 2 shows an elementary single loop indirect or PLL synthesiser, where the step size is equal to the reference frequency. Enhancements of the technique such as dual modulus prescalers and a multiple loop architecture enable fine resolution to be obtained comparatively cheaply. A "fractional  $N$ " approach enables the performance/price ratio to be improved even further making the PLL


**Fig. 3. Principle of the direct digital synthesiser.** A frequency control number is added into the phase accumulator on every clock cycle. The most significant bits of the accumulator address a sine look-up table in rom or ram. The output of this is passed to a dac, whose output is a stepwise approximation to a sinewave. Lowpass filtering exerts a flywheel effect, smoothing the waveform and suppressing harmonics.

synthesiser currently by far the most commonly encountered scheme. PLL synthesisers can offer fine frequency resolution and very low levels of spurious outputs at comparatively low cost, but cannot achieve the same very low levels of close-in phase noise as the direct synthesiser. Furthermore it has inherently slow switching times, due to loop filter settling time.

**Direct digital synthesis**

This brings us back to the latest carrier generation technology, DDS. The basic procedure is

**Fig. 4. Part of a practical but, for the sake of explanation, exceedingly rudimentary DDS – the phase accumulator.** The lowest possible output frequency results when the frequency setting word is 000001. In this case, every eighth clock pulse advances the rom address by one.

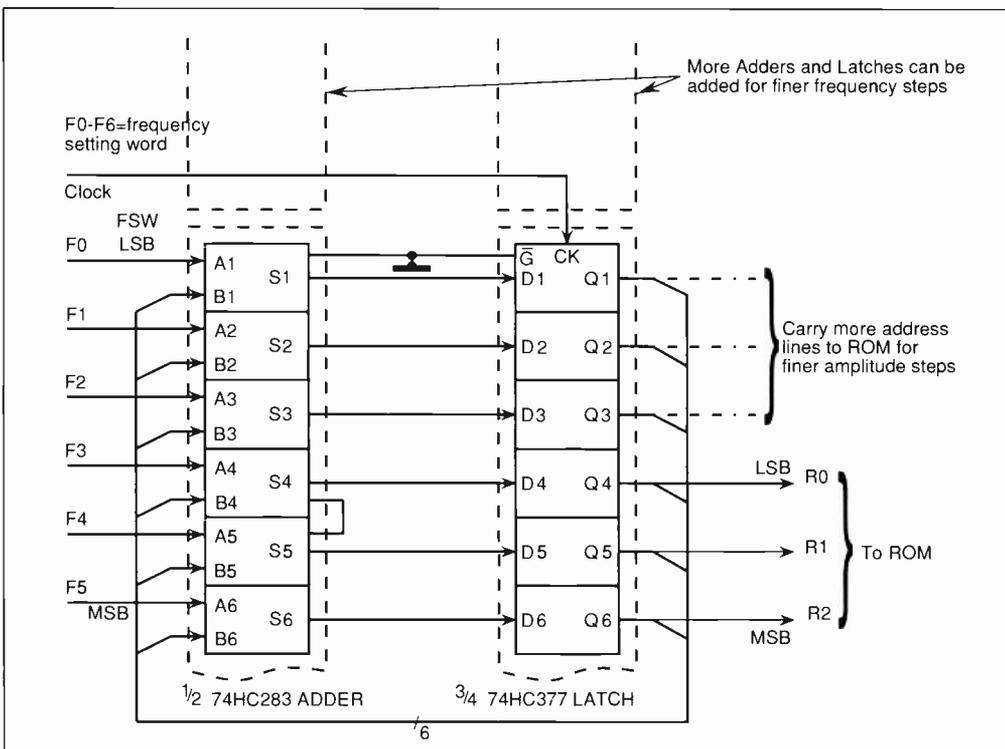

shown in outline in Fig. 3. With the exception of the output lowpass filter, the whole scheme is entirely digital and eminently suitable for large scale integration onto a single chip. The output frequency is directly proportional to the magnitude of the frequency setting word, labelled frequency control in Fig. 3.

Figure 4 shows how the phase accumulator works. For simplicity, a 6-bit accumulator with the three most significant bits (MSBs) controlling a read only memory with just eight memory locations has been assumed. The three MSBs output from the latch to the rom need to represent one complete cycle of the output waveform, so the eight values in the rom need to represent the amplitude of a sinewave at  $45^\circ$  intervals. The higher the value of the frequency setting word, the fewer clock cycles will be needed to cycle through the rom once, and hence the higher the output frequency.


Figure 5 shows the rest of the rudimentary system, the rom, dac and output filter. (Only the three least significant rom address lines have been used in this system, which is deliberately crude for purposes of explanation. In a real DDS system, there would probably be between 18 and 32 frequency setting input lines, with the top eight or more addressing the rom.) The values stored in the rom range from one, representing the negative peak of the sinewave to 255, representing its positive peak and define points on a sinewave in offset binary, where the value 128 corresponds to the 0V mean level of the waveform. One to 255 represents an odd number of levels and this is convenient since a sinewave is symmetrical about the mid level, this is one of the subtle points that many explanations of DDS tend glibly to gloss over or ignore entirely. Of course one could use the 0 level as well, but

an even number of levels can land you in difficulties, for example if you want to economise on high speed rom by storing only half or a quarter of a sinewave, as is done in some commercial DDS chips.

When using two roms and dacs to produce quadrature sinewaves, one should be at its peak when the other is exactly at mid level – but with an even number of levels this cannot be. However, this is no real problem as long as the two roms are addressed with an address offset corresponding to  $90^\circ$ . It just means that the sinewave is not centred in the rom, and that no address corresponds exactly to peak of the sinewave.)

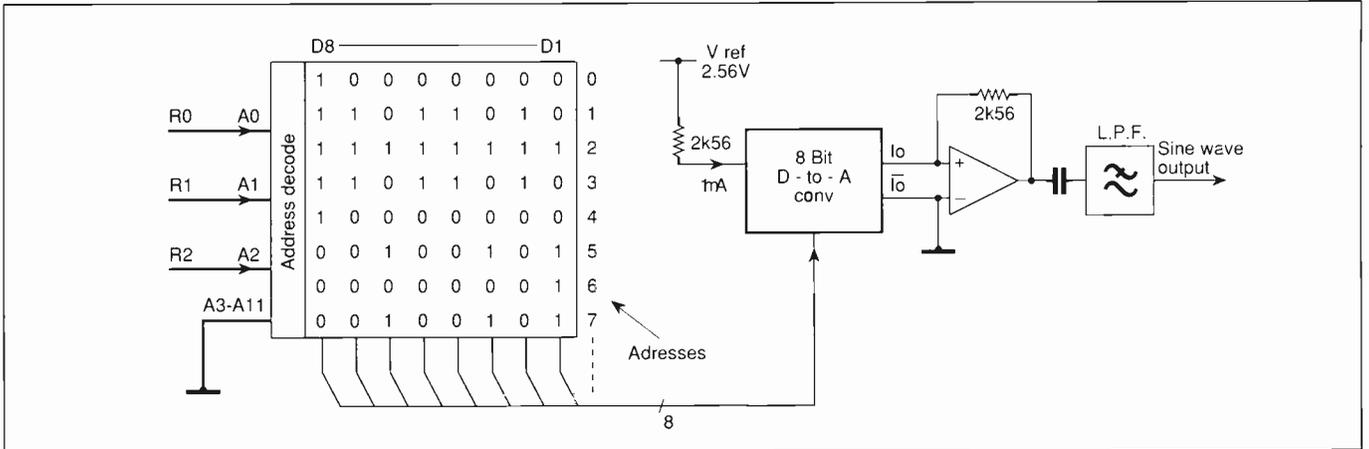**Operation**

Imagine the 6-bit latch clocked at 64Hz and the accumulator (Figure 4) loaded with 000001, i.e. just a 1 in the LSB. Whatever the current value held in the latch, the output of the adder will exceed this by one. So on the next clock pulse this new value will be loaded into the



latch, and so on repeatedly. Starting from the state where the latch content is all zeros, the three rom address lines will all be zero so the rom will output 10000000, causing the dac output to be 1.28V, corresponding to the zero value of a sinewave at 0°. The output of the LPF (lowpass filter) will indeed be 0V, due to the blocking capacitor between it and the op-amp, the purpose of the latter being to turn the dac's current output back into a voltage. Eight clock cycles later, the accumulator contents will be 001000;  $R_0$  is now a 1 so the rom will output 11011010, corresponding to the offset binary representation of the value of a sinewave at +45° and accordingly the dac output becomes 2.18V. After 64 clock cycles the accumulator is full and the dac will have delivered a complete cycle of a stepwise approximation to a sinewave. Thus the lowest non-zero output frequency is 1Hz, or generally  $f_{clock}/2^N$  where  $N$  is the number of accumulator bits. This is illustrated in Fig. 6. If the FSW (frequency setting word) is changed to 000010, the whole process will complete one output cycle in half as many clock periods, so  $f_{clock}/2^N$  is also the smallest frequency increment available.

For those wishing to experiment with a rudimentary DDS system (Figs 4 and 5) built using standard logic, this could be made using two 74HC283 4-bit binary full adders and an 74HC273 or 74HC377 8-bit D flip-flop. The CO - carry out - pin of the less significant adder must be wired to the CI - carry in - pin of the more significant adder, the CO pin of which is unused. The scheme is readily extended using more of the same ICs to a 16 bit register with, say, the eight MSBs controlling the rom. Clocked at 6.5536MHz, this

**Fig. 5. The rest of the rudimentary DDS. After 64 clock cycles, one complete cycle of (stepwise) sinewave has been delivered from the dac, dwelling for eight clock periods at each step. In practice, an 8-bit latch would probably be interspersed in the line between the rom and the dac, loaded by the other edge of the clock waveform from that which increments the accumulator. This would benefit very high speed operation, by preventing any glitches, as the rom output settles, from reaching the dac.**

would provide outputs up to about 2MHz with 100Hz resolution.

Any byte wide prom such as a 2716 would do, together with the inexpensive dac, the DAC08, though the clock frequency would need downrating somewhat on account of the rom. The values loaded in the rom cause the dac to deliver a peak negative voltage of +10mV, +1.28V representing the sinewave's zero mean level and 2.55V for the positive peak. If you check the intermediate values you will find that 11011010 (binary) or 218 (decimal) is just about what it should be:  $(218 - 128)/127 = 0.70866$  which is within 0.2% of the correct value of  $\sin(45^\circ)$ , and similarly for 00100101 ( $\sin(25^\circ)$ ).


**Fig. 6. 8Hz and 4Hz outputs from the DDS of Figs 4 and 5, with a 64Hz clock. With eight rom address lines the steps would be much finer, giving a very small maximum instantaneous phase error.**


**a) FSW (frequency setting word) = 001000, rom address increments by 1 each clock cycle, one cycle of output for each 8 clock pulses: 8Hz output.**

**b) FSW = 000100, the dac output dwells at each level for two clock periods: 4Hz output.**

This raises the important point of the accuracy of the representation in rom of the values of a sinewave. Clearly they must be rounded to the nearest value that can be represented in binary, given the width of the rom, in our example, just eight bits. However accurate the dac, there will be truncation errors in the representation of the sinewave's amplitude, and these will be worse at some steps than others. For a rough and ready sinewave this wouldn't matter, but one would like all spurious frequency components in the output to be 60 or 80dB or more down; remember the DDS has to compete with PLLs, which are very good in this respect. But let's confine attention for now to basic DDS operation.

Figure 6 also shows the instantaneous departure of the output stepwise approximation from a continuous sinewave. Clearly these phase perturbations occur at a rate equal to the clock frequency which is well above the highest output frequency and so they can be suppressed by the LPF (which in this case would have a sharp cut-off at about 30Hz), at least if we had a perfect dac with infinite resolution. Amplitude truncation errors will cause the sinewave representation to be imperfect, resulting (in this case) in harmonics in the output: whether these appear in the output depends upon whether they are higher than 30Hz, i.e. on the commanded output frequency. Apart from this possible harmonic content (and harmonics are a fact of life with any other sort of oscillator anyway), the output of the 6 bit DDS is perfect at frequency settings of 1, 2, 4 and 8Hz. In DDS terms, these are "good" frequencies; at other frequencies, the operation becomes a little more complicated and much more interesting. There are many

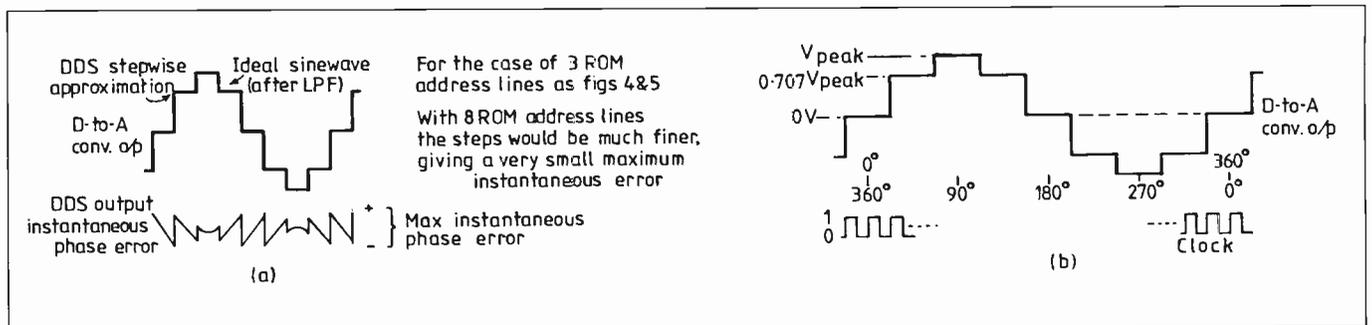

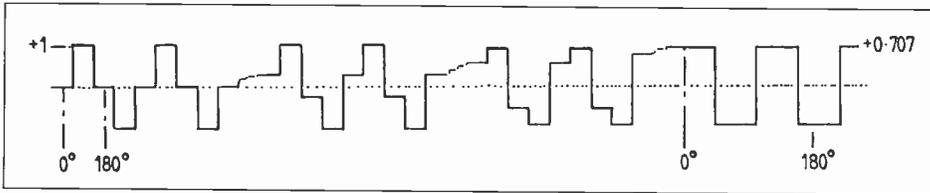


other mechanisms capable of producing unwanted, non-harmonically related spurious outputs. These will be examined in a later article, but for the moment note that when the demanded frequency is so high that the rom only outputs a subset of its contents on each cycle, the waveform into the LPF can take various quite different forms from a sinewave. This is illustrated in Fig. 7 which shows some of the shapes the waveform can take (when many more than three accumulator lines address the rom) at a good frequency where the rom address is incrementing so as to output just four equally spaced locations. Fourier analysis shows that the amplitude of the fundamental component of all the waveforms

Fig. 7. When the output frequency of a DDS equals  $f_{clock}/4$ , any of the above waveforms (or other intermediate versions) may be delivered from the dac, depending upon the accumulator contents at the instant the FSW was set to produce this output frequency. Many DDS chips include an accumulator reset input, enabling the output to be forced to a given phase after setting the FSW.

shown (which are computer generated and hence to scale) is the same.

#### References:

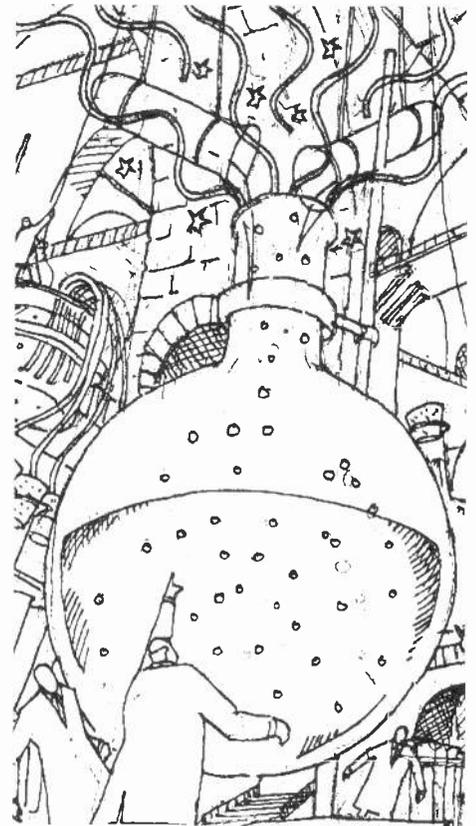1) Phaselock Techniques F M Gardner John Wiley and Sons Inc 1966



**Next month:** operation of a DDS at frequencies other than the good ones that have been considered so far. Unwanted non-harmonically related spurious components in the output; how they arise and what can be done about them.

## LOW COST RANGER1 PCB DESIGN FROM SEETRAX

- Circuit Schematic
  - Circuit Capture
  - PCB Design
  - Host Of Outputs
- All-In-One Design System**

**£100**

**Fully Integrated Auto Router**  
**£50**

**Ask Us About Trade-In Deals**

**Call Now For Demo Disk on 0705 591037**

Seetrax CAE • Hinton Daubnay House  
Broadway Lane • Lovedean • Hants • PO8 0SG  
Tel: 0705 591037 • Fax: 0705 599036

**REDUCED  
PRICE!**

### What The Press Said About RANGER1

For most small users, Seetrax Ranger1 provides a sophisticated system at an affordable price. It is better than EasyPC or Tsien's Boardmaker since it provides a lot more automation and takes the design all the way from schematic to PCB - other packages separate designs for both, that is, no schematic capture. It is more expensive but the ability to draw in the circuit diagram and quickly turn it into a board design easily makes up for this.

**Source JUNE 1991  
Practical Electronics**

Pay by Visa or Access



CIRCLE NO. 133 ON REPLY CARD

**Even when linear parameters are known, different manufacturers' devices show considerable variation. Terence Finnegan examines operation of power mosfets from first principles to show how linear characteristics can be determined.**

# Going linear with power mosfets

part 1 of 2

Almost all power mosfets available today have been developed and characterised for their use as resistive on-off switches, and specifications stress the relevant parameters of  $R_{DS(on)}$ , peak drain current, gate charge, avalanche rating etc.

These parameters may be vital when the device is used as a simple switch and components external to the mosfet usually control the drain current. But they do not apply at all in linear analogue design. Indeed, an examination of the data sheets shows that linear parameters such as threshold voltage, mutual conductance and dynamic drain resistance are hardly defined at all. Even when these parameters are known for a device, there is a considerable variation between manufacturers.

But we can determine useful linear characteristics, both in theory and practice, by examining the operation of a power mosfet from first principles, using straightforward semiconductor physics. Here we concentrate on the gate threshold voltage  $V_T$ , the mutual conductance  $G_{fs}$ , the drain-source output admittance  $G_{os}$ , and the variation of these parameters with temperature, for both n-channel and p-channel units. Linear high frequency performance is also discussed briefly.


## Present design goals

The expression: area  $\times$  on-resistance = (breakdown voltage)<sup>2.5</sup> defines the fundamental lim-

itation of power mosfet switching performance. The product of the resistance of a block of silicon and its surface area plotted against breakdown voltage determines this limit – assuming that 100% of the silicon surface is injecting carriers and 100% of the theoretical breakdown voltage of silicon is obtained. But both these assumptions can never apply in real devices and Fig. 1 shows the present state-of-the-art, including the performance of various contemporary mosfets. The practical limit, defined by the dotted line, assumes an 85% surface utilisation efficiency, to account for: bonding pads etc. We can show (see drain current box) that:

$$R_{DS(on)} = \frac{L}{\mu_n C_{ox} W (V_G - V_T)}$$

and manufacturers are concentrating all their efforts on improving the fabrication processes to come ever closer to the silicon limit and reduce  $R_{DS(on)}$  to an absolute minimum at the lowest cost for a given breakdown voltage. Different techniques are used to achieve this aim; connecting many cells in parallel to increase  $W$  and reducing the channel length  $L$  are obvious ones. Unfortunately reducing  $L$  has adverse effects on  $G_{os}$ , a parameter rarely specified for power mosfets, and there is little or no control over the threshold voltage  $V_T$ , the transconductance  $G_{fs}$  or the unspecified

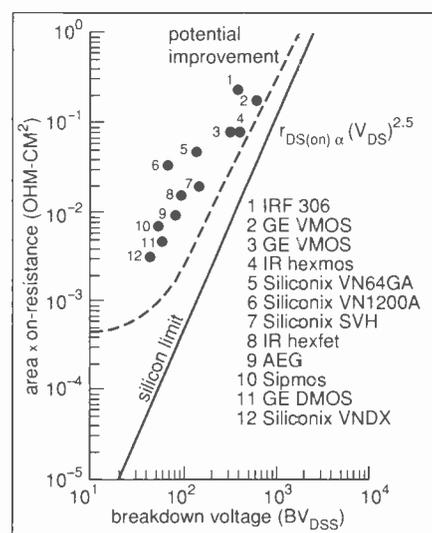

**Fig. 1. Review of characteristics showing theoretical performance limits against the characteristics obtainable from a selection of real devices**

but fundamental gain parameter  $\beta$ . For example, a comparison of the published data for the *IRF720* from IR has  $G_{fs}$  typically 2.7A/V at 1.8A drain current, while the *IRF720* from Siliconix has  $G_{fs}$  typically 1.2A/V at 1.5A drain current. The mosfet gain  $\beta$  is a fundamental performance parameter and yet this is

List of symbols

$C_{ak}$	Anode-cathode capacitance (of valve)
$C_{Dch}$	Total capacitance from the drain to the active channel
$C_{Gch}$	Capacitance from gate electrode to active channel
$C_{gk}$	Grid-cathode capacitance (valve)
$C_{in}$	Gate-source input capacitance ( $=C_{iss}-C_{rss}$ )
$C_{iss}$	Input capacitance (data sheet)
$C_{oss}$	Output capacitance (data sheet)
$C_{rss}$	Reverse transfer capacitance from data sheet
$C_{ox}$	Dielectric capacitance per unit area across the insulating gate oxide
$C_{tox}$	Total oxide capacitance
$E_{G0}$	Band-gap energy at 0°K
$Gfs$	Mutual conductance
$G_{os}$	Incremental drain conductance in saturated region
$I_D$	Drain current
$I_{Dsat}$	Drain current in saturation region
$k$	Boltzmann's constant
$L$	Channel length
$q$	Electronic charge
$N_a$	Acceptor doping concentration
$N_d$	Donor doping concentration
$n_i$	Intrinsic concentration
$Q_d$	Charge density/unit area associated with depletion region
$Q_n$	Total charge in the channel
$Q_{ss}$	Fixed positive charge density per unit area at the silicon silicon dioxide interface
$R_{DS(on)}$	Drain-to-source on-resistance
$T$	Absolute temperature °K
$T_{ox}$	Oxide thickness
$T_{tr}$	Channel transit time
$V_D$	Drain voltage
$V_{Dsat}$	Drain voltage at which current saturation occurs, also known as pinch-off voltage
$V_G$	Gate voltage
$V_{GD}$	Gate voltage at which $I_D$ has zero temp coefficient
$V_{Gch}$	Voltage between gate and channel
$V_R$	Reverse bias across drain junction
$v_{drift}$	Channel drift velocity
$v_{sat}$	Carrier saturation velocity
$V_T$	Gate threshold voltage
$W$	Channel width
$\beta$	Mosfet gain factor
$\epsilon_o$	Permittivity of free space
$\epsilon_{ox}$	Permittivity of insulating layer
$\epsilon_s$	Permittivity of silicon
$\epsilon_r$	Relative permittivity of material
$\theta$	Channel mobility modn factor
$\Phi_F$	Fermi potential
$\Phi_{MS}$	Metal-semiconductor work function difference
$\mu$	Amplification factor
$\mu_n$	Electron mobility in channel
$\mu_p$	Hole mobility in the channel

different by a factor of over four in this instance, showing that the fundamental parameters needed for analogue design are not controlled.

Theoretical power mosfet performance

In the following text all terminal voltages such as  $V_G$ ,  $V_T$  etc are "with respect to the source terminal" unless otherwise specified.

Let us start by reviewing the gate and drain characteristics of a power mosfet, before considering the semiconductor physics which give rise to them. The gate transfer curve of Fig. 2 defines the variation between the saturated drain current and the applied gate voltage, for a constant drain voltage. There are three distinct regions on this curve and each results from differing conduction phenomena.

In the region A to B, a small drain current flows, with the gate voltage  $V_G$  below the mosfet threshold voltage  $V_T$ . Since the magnitude of the current that flows in this sub-threshold region is negligible compared with the maximum current of a device, very little work has been done to characterise power mosfets here. But theory suggests that the drain current increases exponentially with gate voltage. In the region B to C on the transfer curve, the drain current is proportional to  $(V_G - V_T)^2$ . This square-law is characteristic of all mosfets, both enhancement-mode power devices and depletion-mode small signal devices. After point C, the curve gradually becomes linear because the charge carriers tend to reach a saturation velocity, when the gate voltage becomes high enough.

The drain transfer curve of Fig. 3 defines the variation between the drain current and the applied drain voltage, for a constant gate voltage above threshold. This curve has obviously two distinct regions. In the region below "pinch-off", defined as the saturated drain voltage  $V_{Dsat}$ , the drain current increases parabolically with increasing drain volts until a maximum is reached. Above  $V_{Dsat}$ , the drain current remains nearly constant at the maximum or saturated value, and is nearly independent of the applied drain voltage thereafter.

Action of the gate

In construction, a typical n-channel power mosfet (Figs. 4a and 4b) is essentially an NPN transistor with the drain junction having an extra lightly doped  $n^-$  epitaxial layer inserted between the more heavily doped  $p^+$  substrate and the  $n^+$  drain layers. (The superscripts denote doping concentration, not polarity). A metal electrode is placed over the  $p^+$  substrate and insulated from it by a layer of silicon dioxide. This electrode forms the gate and controls the current flow through the device. To be fully effective, the gate must have low resistance. It was usually aluminium in the early days but heavily doped polysilicon is now preferred.

The p-type substrate beneath the gate is doped with acceptor impurities, so there are a majority of holes and a minority of electrons uniformly dispersed through it. When the voltage on the gate is zero, no current will flow

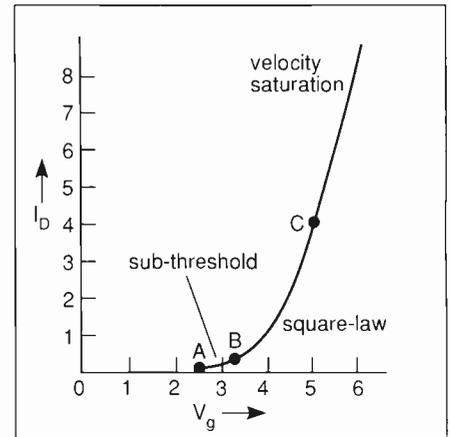


Fig. 2. Gate transfer characteristic

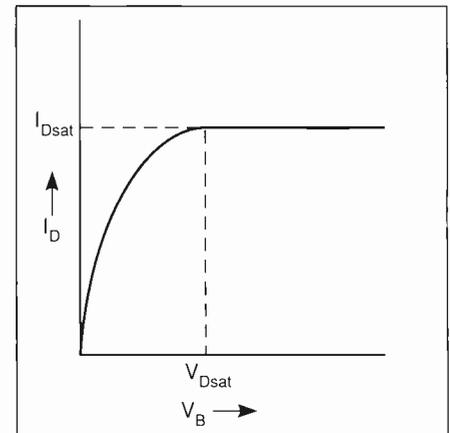


Fig. 3. Drain output characteristic

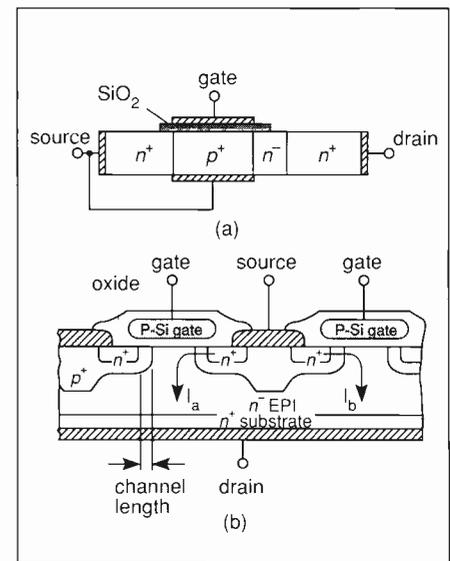


Fig. 4a. N-channel mosfet structure  
b. Modern planar vertical double-diffused mosfet

because the device looks like two back-to-back diodes. However when the gate voltage is gradually increased positively, the semiconductor surface goes through several distinct changes which characterise mosfet operation.

Stage 1. The increasing gate voltage first overcomes the "contact potential" existing

between the gate electrode and the silicon surface. The metal gate-silicon dioxide-silicon surface system forms a capacitor which has a built-in reverse potential across it, due mainly to the difference between the work functions of the gate metal and of the silicon surface. This built-in potential varies with the substrate doping as well as with the specific metal used for the gate. Small manufacturing imperfections during the oxide formation (eg. Na<sup>+</sup> ions in the washing water) which develop fixed charges in the oxide also add to this voltage.

**Stage 2.** As the gate voltage increases, the in-built reverse bias potential is gradually overcome and the metal-silicon dioxide-silicon surface system will eventually reach a charge neutral condition. Because the energy bands are all flat in this charge neutral condition, the total voltage needed to reach this state is usually known as the flat-band voltage.

**Stage 3.** After the flat-band voltage has been passed, any increase in gate voltage will now require a negative charge at the silicon surface to balance the increasingly positive gate charge. Hence electrons in the p-type substrate will drift to the surface, attracted by the positive gate charge, and the holes will be repelled. The surface will thus gradually invert to form an n-type channel in the p-type substrate, which will then allow conduction between the source and drain in either direction. Electron concentration at the surface will increase progressively as the gate-source voltage increases. This in turn will progressively increase the depth and conductivity of the n-type channel, allowing normal drain current to flow.

Before conduction can begin and drain current can flow, the applied gate voltage must reach the level needed to strongly invert the surface (Table 1). This voltage level is referred as the threshold voltage and is controlled to lie between 2 and 4V for both n-channel and p-channel power devices. The threshold is positive for n-channel and negative for p-channel devices.

**Gate transfer characteristics**

If the drain voltage is large enough for the drain current to reach its saturation value  $I_{Dsat}$ , then the simplified expression (derived in drain current box) shows the familiar square-law variation of drain current versus gate voltage, ie  $I_{Dsat} = 0.5\beta(V_G - V_T)^2$  where  $\beta = \mu_n C_{ox} W/L$ .

Differentiating this expression relative to  $V_G$  gives the value for transconductance  $G_{fs}$  as:

$$G_{fs} = \beta(V_G - V_T)$$

after substituting for  $(V_G - V_T)$ .

$$G_{fs} = \sqrt{2\beta I_{Dsat}}$$

This typical square-law relationship applies to all mosfets and holds quite accurately when  $(V_G - V_T)$  is small. But as the voltage increases, the square-law gradually changes into a linear law, so for high values of  $(V_G - V_T)$ ,  $I_{Dsat} \rightarrow k(V_G - V_T)$

The carriers move in the channel under the influence of both a normal field produced by

**Table 1. Surface changes which take place in an n-channel device as the gate voltage is gradually increased.**

Gate voltage	State of semiconductor surface
Zero	Accumulative; positive charges accumulate making the silicon surface positive with respect to the gate, due to the difference in the work functions.
"Flat-band"	Neutral; the gate and silicon surface potentials are now equal.
Positive	Depletion; small negative charge with the surface electron density less than the surface hole density and both less than the acceptor doping.
Positive (more)	Intrinsic; surface electron and hole densities now equal.
Positive (more)	Weak inversion; surface electron density greater than intrinsic but less than acceptor doping. <i>Sub-threshold state.</i>
Positive (more)	Onset of strong inversion; surface electron density equal to acceptor doping. <i>Threshold state definition.</i>
Positive (more)	Strong inversion; surface electron density much greater than acceptor doping, forming a well-defined n-channel. <i>Normal conduction state.</i>

the gate voltage and a tangential field produced by the applied drain voltage. The voltage at the source end of the channel is zero, while at the drain end it equals  $V_{Dsat}$  or  $(V_G - V_T)$ . The tangential field produced by the differential voltage increases the carrier velocity, and it also reduces the carrier mobility as well. When the field strength reaches a value of about  $3 \times 10^4$  V/cm, the carrier velocity reaches the limiting or saturation value of about  $7 \times 10^6$  cm/s for electrons in silicon. In addition, the normal field produced by the free carrier scattering at the silicon dioxide interface.

The effects of these two fields apply at all values of gate voltage above threshold and the following expression will more accurately model the saturated drain current in practical devices throughout the operating range where  $\theta V^{-1}$  is a mobility modulation factor:

$$I_{Dsat} = \frac{\beta}{2} \frac{(V_G - V_T)^2}{[1 + \theta(V_G - V_T)]} \quad (1)$$

This factor accounts for both the normal and the tangential field effects and usually lies between 0.03 and 0.5, with 0.1 being typical.  $\theta$  will also account for small parasitic resistances in series with the source terminal, which reduce  $\beta$  from its theoretical value. (See: Effect of source resistance.)

As the gate voltage increases, the carrier velocity approaches the saturation value  $v_{sat}$  and the above expression simplifies to:

$$I_{Dsat} = 0.5 C_{ox} W v_{sat} (V_G - V_T)$$

so the drain current in velocity saturation is now directly proportional to  $(V_G - V_T)$  and the transconductance approaches a constant value of  $G_{fs} = 0.5 C_{ox} W v_{sat}$ .

The transconductance thus varies linearly with  $V_G$  in the square-law region, but then levels off to a constant value when the carrier velocity saturates. The effect is a characteristic of all short channel mosfets. No other device shows such a linear relationship between input voltage and output current and the relationship can often prove beneficial in linear design. The electric field needed to achieve saturation velocity is easily generated. Effective channel length is in the 1-2µm range and gate voltages just a few volts above threshold are sufficient to achieve the necessary field strength.

For p-channel devices, the limiting velocity for holes in silicon is about  $4 \times 10^6$  cm/s and velocity saturation is much more common. Further differences are discussed in a later section.

**Determining  $V_T$ ,  $\beta$ ,  $\theta$  and  $G_{fs}$ .**

Threshold voltage is the value of  $V_G$  at which the drain current becomes meaningful in a

**Table 2. Mosfet characteristics at 25°C. (Taken from International Rectifier data)**

Part	Die size	Rating	Theoretical gain, $\beta$ (A/V <sup>2</sup> )	Actual gain, $\beta$ (A/V <sup>2</sup> )	Mobility mod <sup>n</sup> factor, $\theta$ (1/V)
IRF510	Hex 1	100V, 5A	1.8	1.3	0.11
IRF710	Hex 1	400V, 1A	1.8	1.1	0.03
IRF045	Hex 5	60V, 53A	28.0	16.5	0.11
IRF460	Hex 5	500V, 21A	28.0	18.1	0.02

Part	Mutual cond $G_{fs}$ (A/V)	Amp factor $\mu$	Intercept voltage $V_q$ (V)	Threshold voltage $V_T$ (V)	$dV_T/dT$ (mV/°C)
IRF510	$1.2\sqrt{I_D}$	$3000\sqrt{I_D}$	-2400	3.4	-6.3
IRF710	$1.3\sqrt{I_D}$	$13000\sqrt{I_D}$	-9800	3.3	-4.8
IRF045	$4.0\sqrt{I_D}$	$5000\sqrt{I_D}$	-1300	3.5	-6.0
IRF460	$6.0\sqrt{I_D}$	$50000\sqrt{I_D}$	-8400	3.6	-6.4

**Effect of a source resistance  $R_s$**

In the practical mosfet, accurately modelled by the circuit in Fig. 6, the actual voltage between the gate and the channel  $V_{Gch}$  is given by  $V_{Gch} = V_G - I_D R_s$ .

But

$$I_D = \frac{\beta}{2}(V_{Gch} - V_T)^2$$

and after substituting and neglecting  $R_s$ ;

$$I_D = \frac{\beta}{2} \left\{ \frac{(V_G - V_T)^2}{1 + \beta R_s (V_G - V_T)} \right\}$$

or

$$I_D = \frac{\beta'}{2}(V_G - V_T)^2$$

where  $\beta' < \beta$  is the practical measured value of  $\beta$ . Equating the two expressions gives :

$$\frac{\beta}{\beta'} = 1 + \beta R_s (V_G - V_T)$$

$$\frac{\beta}{\beta'} = 1 + R_s G_{fs}$$

Hence  $I_D$  is modelled as

$$I_D = \frac{\beta}{2} \frac{(V_G - V_T)^2}{\{1 + \beta R_s (V_G - V_T)\} \{1 + \theta(V_G - V_T)\}}$$

$$I_D \approx \frac{\beta}{2} \frac{(V_G - V_T)^2}{\{1 + \theta'(V_G - V_T)\}}$$

Thus the source resistance  $R_s$  reduces the value of  $\beta$  from its theoretical value to the practical measured value and  $\theta' \approx \theta + \beta R_s$ , so if this is derived from the published transconductance data, the value determined will automatically include any effects due to the source resistance.

For example,  $R_s$  is given by IR as 0.02 $\Omega$  and its effect is minimal at low current. But for a device like the IRF044,  $G_{fs} = 24A/V$  at a current of 40A and  $\beta/\beta' = 1.48$ . This is a 32% reduction from the theoretical value of  $\beta$  and the performance of the higher current devices is limited more by the connections than by the semiconductor itself.

practical sense.  $V_T$  can be accurately determined in practice by measuring corresponding values of  $I_D$  and  $V_G$  up to perhaps 250mA and then plotting a graph of  $\sqrt{I_D}$  against  $V_G$ . The extrapolated intercept of the straight line portion of the curve onto the  $V_G$  axis gives the true value of  $V_T$ . The slope of the line is  $\sqrt{0.5\beta}$ , from which the mosfet gain at low current, and the transconductance  $G_{fs}$  can be derived. Unfortunately, the value for  $\beta$  obtained in this way does not always give the best results for modelling purposes and it is often much smaller than the theoretical value. As an example, the curves in Fig. 5 show the  $\sqrt{I_{Dsat}}$  versus  $V_G$  curve of the IRF510 at both 25°C and at 175°C. The extrapolated intercept onto the  $V_G$  axis gives the true device threshold of 3.4V and the slope of the line yields a gain  $\beta$  of 0.87A/V<sup>2</sup>, with a corresponding transconductance of 1.32 $\sqrt{I_D}$  A/V, at 25°C.

However for the IRF510, the IR data sheet gives the following information:  $\mu_n = 450\text{cm}^2/\text{Vs}$ ,  $W = 14.2\text{cm}$  and  $L = 1.2 \times 10^{-4}\text{cm}$ .

Assuming a typical oxide thickness of 1000 $\text{\AA}$  and a relative permittivity of 3.9, then  $C_{ox} = 3.45 \times 10^{-8}\text{F/cm}^2$  and the theoretical value for  $\beta$  is 1.82A/V<sup>2</sup>, considerably greater than the 0.87A/V<sup>2</sup> estimated from the  $\sqrt{I_D}$  plot. The difference between the theoretical and measured values of  $\beta$  is usually due to the parasitic resistances of the source connections and the source depletion region. Proper choice of the value for  $\theta$  will usually account for this parasitic resistance in practice (see Effect of source resistance).

The transconductance curve is usually a much better starting point, if one is available, as data from this can give good values for both  $\beta$  and  $\theta$  for modelling purposes. If we assume that equation (1) accurately models the device, then after differentiation, we have equation (2). Assuming that  $\theta$  is small allows considerable simplification to this expression giving equation (3). Substituting for  $(V_G - V_T)$  gives alternate expression equation (4).

$$G_{fs} = \frac{\beta}{2} \left\{ \frac{2(V_G - V_T) + \theta(V_G - V_T)^2}{[1 + \theta(V_G - V_T)]^2} \right\} \quad (2)$$

$$G_{fs} = \frac{\beta}{2} \{ 2(V_G - V_T) - 3(V_G - V_T)^2 \} \quad (3)$$

$$G_{fs} = \sqrt{2\beta I_{Dsat}} - 3\theta I_{Dsat} \quad (4)$$

**Theoretical behaviour of the drain current with increasing drain-source voltage and gate-source voltage**

For low drain voltages, the equations representing mosfet action are derived in a straightforward manner by using a simplified charge control analysis, which assumes that the electric field lines within the gate insulator are perpendicular to the surface of the silicon and that Gauss' law leads to a charge neutral condition. The drain current  $I_D$  is related to the total charge in the channel  $Q_n$  and the channel transit time  $T_{tr}$  by  $I_D = -Q_n/T_{tr}$ . Because the current in the channel is primarily a drift flow,  $T_{tr}$  is just the channel length  $L$  divided by the drift velocity  $v_{drift}$ . But  $v_{drift}$  equals the mobility multiplied by the voltage across the channel per unit length,  $V_D/L$ ;

$$T_{tr} = \frac{L^2}{\mu_n V_D}$$

The total channel charge  $Q_n$  is given by

$$Q_n = -C_{ox} W L (V_G - V_T)$$

Hence for low drain - source volts

$$I_D = \frac{\mu_n C_{ox} W}{L} (V_G - V_T) V_D$$

$$I_D = \beta (V_G - V_T) V_D$$

where  $\beta$ , theoretical mosfet gain, is defined as

$$\beta = \frac{\mu_n C_{ox} W}{L} = \frac{\mu_n \epsilon_{ox} W}{T_{ox} L}$$

The expression for  $I_D$  represents an effective resistance between drain and source of:

$$R_{D(som)} = \frac{V_D}{I_D} = \frac{1}{\beta(V_G - V_T)}$$

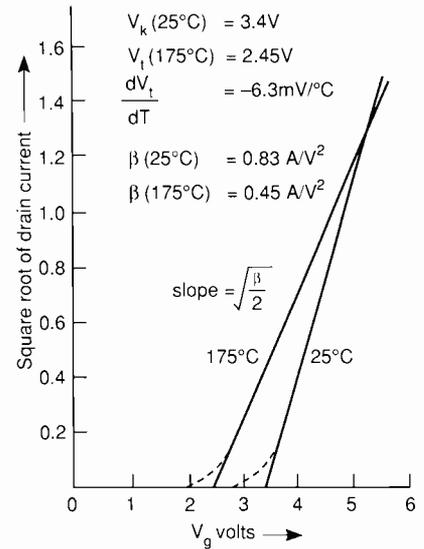


Fig. 5. Plot of  $\sqrt{I_{Dsat}}$  versus  $V_G$  for the IRF510 showing the variation in transconductance and the threshold voltage with temperature.

Note also the square law relationship between gate voltage and drain current: the x-axis is plotted as linear gate volts while the y-axis depicts the square root of drain current. When plotted in this way, the result should be a straight line for perfect devices.

This defines the mosfet "on resistance" for low drain voltages and is the chief parameter of interest when the device is used as a switch.

If  $V_D$  is now increased so that it is no longer negligible compared to  $V_G$ , the above simple analysis fails because  $V_D$  acts to reduce  $Q_n$ . A more comprehensive distributed analysis gives a more accurate though still simplified expression for  $I_D$  as:

$$I_D = \beta \left[ (V_G - V_T) V_D - \frac{V_D^2}{2} \right] \quad (1.1)$$

Therefore, as  $V_D$  is increased from zero with  $V_G > V_T$ ,  $I_D$  increases parabolically with  $V_D$  until it eventually reaches a maximum at a drain voltage defined as  $V_{Dsat}$ . For drain voltages above  $V_{Dsat}$ , the drain current maintains a constant value and is said to be in current saturation. Ideally when this occurs, the slope of the drain voltage versus drain current curve should be zero and the effective drain-source resistance should be infinite. But this does not occur in practice due to second order effects, which limit the drain resistance.  $V_{Dsat}$  is obtained from (1.1) by differentiating and equating to zero. Differentiating (1.1) gives:

$$\frac{dI_D}{dV_D} = \beta(V_G - V_T - V_D)$$

For a maximum value,  $dI_D/dV_D = 0$  and hence  $V_{Dsat} = V_G - V_T$ . If this value is now substituted back into Equation (1.1) for  $V_D$ , we finally derive the expression for the saturated drain current  $I_{Dsat}$  in the square-law region as:

$$I_{Dsat} = \frac{\beta}{2} (V_G - V_T)^2 \quad (1.2)$$

Equation (4) has a maximum when  $I_{Dsat} = \beta/18\theta^2$  and provides a quite accurate model for  $G_{fs}$ , particularly for those devices which show a maximum in the transconductance curve.

The values for both  $\beta$  and  $\theta$  can now be derived, by choosing corresponding low and high values for  $G_{fs}$  and  $I_{Dsat}$  from the transconductance curve and substituting into the above expression. For example, from the curve for the IRF510,  $G_{fs}=1A/V$  when  $I_{Dsat}=0.5A$  and  $G_{fs}=2A/V$  when  $I_{Dsat}=4A$ . From these values,  $\beta=1.34A/V^2$  and  $\theta=0.11/V$ . This value for  $\beta$  is much closer to the theoretical value of  $1.82A/V^2$  and the expression

$$I_{Dsat} = \frac{0.67(V_G - V_T)^2}{1 + 0.11(V_G - V_T)}$$

accurately models both the  $V_G$  versus  $I_{Dsat}$  curve and the  $G_{fs}$  versus  $I_{Dsat}$  curve for the IRF510, perhaps better than the International Rectifier data given for Spice modelling.

If the transconductance curve is not avail-

able, there are two options. Either the designer can derive  $\beta$  from the slope of the  $\sqrt{I_{Dsat}}$  plot and assume that  $\theta$  equals zero; or can assume that  $\theta$  equals 0.1 and then choose a value for  $\beta$  which gives a best fit to the available data. The value for  $\theta$  can also be adjusted, depending on the shape of the gate transfer curve. If this follows a square-law over the desired operating range, then  $\theta$  should be low perhaps 0.03; if there is a tendency to saturation, then a higher value for  $\theta$ , perhaps 0.3 is more appropriate.

Designers should not attempt to extract the value for  $\beta$  from the  $R_{D(Stom)}$  saturation characteristics, because it is impossible to know how much of  $R_{D(Stom)}$  is actually due to the channel. For high voltage devices, most of the on-resistance is in the epitaxial layer; for low voltage devices, an unknown percentage lies in parasitic elements – such as the internal lead resistances – as well as in the epitaxial layer.

The circuit of Fig. 6 accurately models real devices.  $R_d$  represents the resistances of the epitaxial layer and connections, varying from

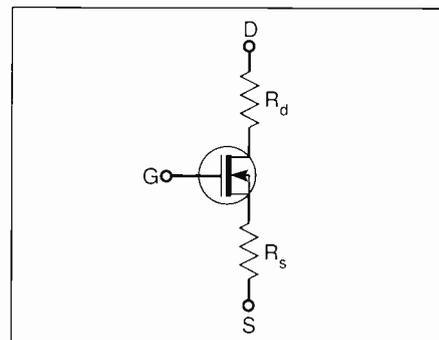


Fig. 6. Circuit showing source resistance.

0.05Ω to 3.5Ω depending on voltage rating, and is of little interest in linear design.  $R_s$  is the resistance of the source n<sup>+</sup> region plus connections and is about 0.02Ω for TO-220 packages. This resistance will reduce the value of  $\beta$  and  $G_{fs}$  from theoretical (see box: Effect of source resistance) and is automatically taken into account when deriving  $\beta$  and  $\theta$  from the  $G_{fs}$  curve.

**Variation of the transfer characteristic with temperature**

We have already derived the saturated drain current in the square-law region to a first order (see Theoretical behaviour of drain current). Now both  $V_T$  and  $\mu_n$  and hence  $\beta$  vary with temperature and so the variation of  $I_{Dsat}$  with temperature can be defined by

$$\frac{\partial I_D}{\partial T} = I_D \left( \frac{1}{\beta} \frac{\partial \beta}{\partial T} - \frac{2}{V_G - V_T} \frac{\partial V_T}{\partial T} \right) \quad (2.1)$$

partial differentiation of equation (1.2) as: Theoretical analysis indicates that the mobility of both holes and electrons should decrease with absolute temperature in proportion to  $T^{-n}$ . As the free carriers move through the silicon under the influence of an applied field, they are scattered by interaction with the crystal lattice and these collisions become more effective as the temperature increases, thereby reducing the carrier mobility. For bulk silicon,  $n$  varies between 1.66 and 2.5 and depends quite strongly on the doping level, with the higher values of  $n$  applying to the lower doping levels. However, since the carrier mobility in a mosfet channel is only about 35% of that in bulk silicon, temperature variation of the mobility is also less.

Experimental studies have concluded that in the temperature range from -55°C to +125°C, the value of  $n$  lies between 1.5 and 2. Higher voltage mosfets have a substrate doping of about  $10^{14}$  atoms/cm<sup>3</sup> and the gain  $\beta$  is proportional to about  $T^{-1.9}$ , while lower voltage mosfets have a substrate doping of about  $5 \times 10^{15}$  atoms/cm<sup>3</sup> and  $\beta$  is proportional to about  $T^{-1.8}$ . These figures apply to n-channel devices, with the temperature in °K and they correspond to a change in gain at 25°C of about -0.5%/°C.

For p-channel devices, the temperature variation of  $\beta$  is slightly different; for 200V units,  $\beta$  is proportional to  $T^{-1.3}$ , while for 50V units,  $\beta$  is proportional to  $T^{-1.2}$ , giving

an average change in gain at 25°C of about -0.6%/°C.

Variation of  $V_T$  is much more complex as a large number of factors contribute. It is well to start discussion from the theoretical expression for  $V_T$ , which for an n-channel device is:

$$V_T = -\phi_{MS} - \frac{Q_{ss}}{C_{ox}} + \frac{Q_d}{C_{ox}} + 2\phi_F$$

The voltage required to create strong inversion must first be large enough to achieve the flat-band condition ( $\phi_{MS}$  and  $Q_{ss}/C_{ox}$  terms), then accommodate the charge in the depletion region ( $Q_d/C_{ox}$ ) and finally to induce the inverted region ( $2\phi_F$ ). This equation accounts for all the dominant voltage effects in typical mos devices and all the terms except  $Q_{ss}/C_{ox}$  depend on the substrate doping. Now both  $Q_{ss}$  and  $\phi_{MS}$  can be considered to be independent of temperature and differentiation of the remaining terms in the above equation with temperature yields the following expression,

$$\frac{dV_T}{dT} = \frac{1}{T} \left\{ \left( \phi_F - \frac{E_{GO}}{2q} \right) \left( \frac{Q_d}{2C_{ox}\phi_F} + 2 \right) \right\}$$

after considerable manipulation and simplification:

An analogous expression can be determined for p-channel devices.

For a typical mosfet the following figures apply: p-region body doping with  $N_a=4 \times 10^{16}$  atoms/cm<sup>3</sup>,  $Q_{ss}/q=5 \times 10^{10}$ /cm<sup>2</sup>,  $\phi_{MS}=0.5V$  and  $Q_d/q$  is adjusted to  $8 \times 10^{11}$ /cm<sup>2</sup>. Assuming a pure oxide thickness of 1000Å, then  $C_{ox}=3.45 \times 10^{-8}F/cm^2$  and  $\phi_F=0.383V$ . This gives a value for  $V_T$  of 3.36V and a value for  $dV_T/dT$  of -5mV/°C. Experimental results for both n-channel and p-channel devices show a threshold voltage temperature variation between -3mV/°C to -8mV/°C, depending on geometry and cell size. The larger cell

sizes tend to have the larger values of  $V_T$  and larger values of  $dV_T/dT$ . The variation is probably due to the adjustment of the depletion charge term  $Q_d$  made during fabrication by ionic bombardment to set the threshold voltage.

Variation of threshold voltage with temperature for p-channel devices also falls into the 3mV to 8mV/°C range, and so the variation for the two types is about equal – but of opposite sign.

These theoretical expressions have been included to show that both  $V_T$  and  $dV_T/dT$  are dependent only on the lattice parameters and on manufacturing geometry. Thus both can be fairly accurately predicted and values for a given device are quite stable over time.

Since the derivatives of n-channel mosfet gain and threshold voltage with temperature are both negative, the change in drain current with temperature will be zero at a specific value of applied gate voltage. This is clearly seen in all published gate transfer characteristics, where the curves at different temperatures cross at a specific value of gate voltage. In the square-law region, this zero

$$V_{G0} = V_T + \frac{2\beta \frac{dV_T}{dT}}{\frac{d\beta}{dT}}$$

TC gate voltage is derived by setting the term in brackets in (2.1) to zero. This yields: An IRF510 has the following parameters at 25°C:  $V_T = 3.3V$ ;  $\beta = 1.34A/V^2$ ;  $dV_T/dT = -6mV/°C$ ;  $d\beta/dT = -0.55\%/°C$  (which equals -7.4mA/V<sup>2</sup>·°C). Substituting these figures into the above expression gives a value for the zero TC gate voltage of 5.5V, which agrees well with the published curves.

## COMPONENTS

### Subthreshold region

When the gate voltage is less than the conventional threshold voltage, the inversion charge can produce only a small drain current – primarily a diffusion current and not a drift current as is normal for  $I_D$  above threshold. In this region,  $I_D$  varies exponentially with gate voltage in a manner defined by:

$$I_{Dsat} = I_0 \exp k(V_G - V_T)$$

$I_0$  depends on the size of the mosfet die and is about 0.01A for low current devices and about 0.1A for high current devices.  $k$  is reasonably independent of size and a value of 4.6/V fits the available data. Little is known about operation in this region and it is rarely used. But it maybe of practical interest to calculate the variation of  $I_{Dsat}$  with temperature for a mosfet operating in the threshold region, with a fixed gate bias voltage near  $V_T$ , as this is the effective bias condition in class AB output stages. In the threshold region:

$$\frac{dI_{Dsat}}{dV_G} = kI_0 \exp(V_G - V_T)$$

$$= kI_0 \text{ when } V_G \approx V_T$$

and

$$\frac{dI_{Dsat}}{dT} \approx -5kI_0 \text{ mA / } ^\circ\text{C}$$

because  $dV_T/dT$  is approximately  $-5\text{mV/}^\circ\text{C}$

### Properties of silicon, mosfets and insulators at 300°K

Lattice mobility, electron	$\mu_n$	1367cm <sup>2</sup> /V-s
Lattice mobility, hole	$\mu_p$	478cm <sup>2</sup> /V-s
Channel mobility, electron		450cm <sup>2</sup> /V-s
Channel mobility, hole		150cm <sup>2</sup> /V-s
Permittivity of free space	$\epsilon_0$	8.854x10 <sup>-8</sup> F/cm
Relative dielectric constant		11.7
	silicon	11.7
	SiO <sub>2</sub>	3.9
	Si <sub>3</sub> N <sub>4</sub>	7.5
Electron charge	$\theta$	1.602x10 <sup>-19</sup> C
Boltzmann's constant	$k$	1.381x10 <sup>-23</sup> J/°K
		8.617x10 <sup>-5</sup> eV/°K
Energy gap at 0°K	$E_{G0}$	1.205eV
Temp coefficient of $E_{G0}$		-2.7x10 <sup>-4</sup> eV/°K
Intrinsic concentration	$n_i$	1.45x10 <sup>10</sup> /cm <sup>3</sup>
Thermal voltage	$kT/q$	0.02586V
Typical fixed positive charge density	$Q_{ss}/q$	5x10 <sup>10</sup> /cm <sup>2</sup>
Nominal thickness of SiO <sub>2</sub>	$T_{ox}$	1000Å

### Doping

Donor, or n-type impurities: antimony, arsenic, phosphorus  
 Acceptor, or p-type impurities: boron, gallium, indium  
 Typical doping concentrations vary from 10<sup>14</sup> to 10<sup>16</sup> atoms/cm<sup>3</sup>.

### Useful dimensions

1 micron = 10<sup>-6</sup>m  
 1Å (Angstrom) = 10<sup>-10</sup>m

(See: Variation of transfer with temperature).  
 The variation of  $I_{Dsat}$  at threshold is of the order of  $-0.23\text{mA/}^\circ\text{C}$  for small die sizes and  $-2.3\text{mA/}^\circ\text{C}$  for large die sizes. Bias conditions should therefore be defined at the operating junction temperature and temperature com-

pensation used, if necessary  
**NEXT ISSUE: Drain transfer characteristics; Determination of the drain output conductance; Amplification factor; Differences between n-channel and p-channel; High frequency performance.**

# Microprocessor Development Tools

## EMULATORS - SIMULATORS - COMPILERS - ASSEMBLERS - PROGRAMMERS

77C82 8085 Z8 68000 8051 32010 68HC11 6301 6502 87C751 6805 Z80 6809 8096 740 Series 7720 MIPS R2000 etc . . .

### ROM/RAM EMULATOR

- ✓ ROM sizes from 16 kbit to 16 Mbit ! ! !  
- supports 8/16/24/32 bit applications
- ✓ Full bi-directional communications  
- run a monitor or debugger  
- or use PC as a dumb terminal
- ✓ Connects direct to PC parallel port  
- no dongle required
- ✓ Emulates all 24, 28, 32 and 40 pin devices
- ✓ Fast download - loads 1 meg in under 3 Secs
- ✓ Comprehensive format support  
- Binary, Intel Hex, Motorola S-Records
- ✓ Split and shuffle and paged ROM capability  
- offsets and incremental loading
- ✓ Full screen edit of ROM contents
- ✓ Battery back up

### SIMULATORS

- ✓ Debug microprocessor software on your pc
- ✓ Break points and trace
- ✓ Free run or single step

### 8051 DEVELOPMENT

- ✓ New Version 4
- ✓ Pascal, C and Modula2 Compilers
- ✓ Simulator, Cross-Assembler, Linker and Editor
- ✓ Source Level Debug
- ✓ Multitasking Support
- ✓ Integrated environment  
- or command line
- ✓ Supports ALL 8051 variants  
- including 80751, 80552 etc..

### UNIVERSAL ASSEMBLER


- ✓ Relocatable - fast assembly
- ✓ Caters for ALL Microprocessors and Controllers
- ✓ Instruction sets for many microprocessors included  
- from Z80 to RISC 2000  
- or add your own
- ✓ Iterative macros,
- ✓ Intelligent jump facilities
- ✓ Linker and MAKE facility

**NEW**

2 Field End, Arkley, Barnet, Herts, EN5 3EZ Telephone : 081-441 3890

**SMART**  
COMMUNICATIONS

CIRCLE NO. 111 ON REPLY CARD

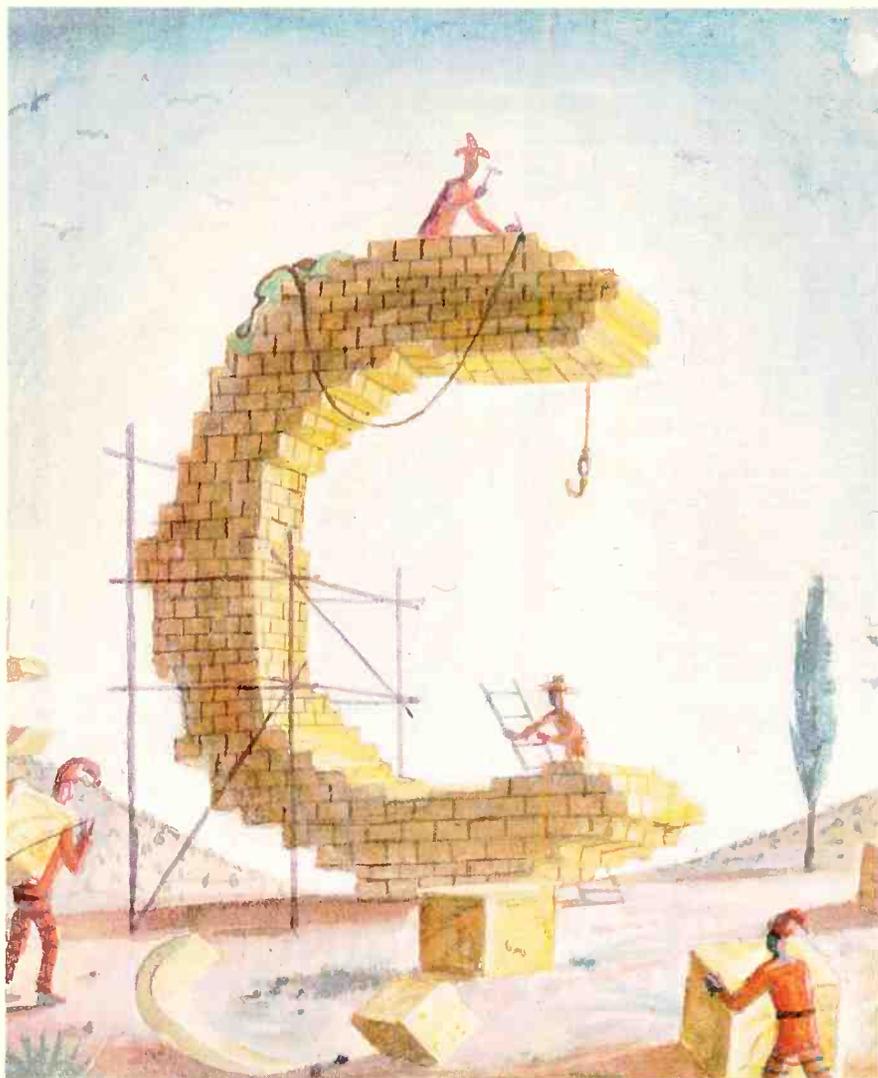

# INTERFACING WITH C

by  
HOWARD HUTCHINGS

Interfacing with C can be obtained from Lorraine Spindler, Room L333, Quadrant House, The Quadrant, Sutton, Surrey SM5 2AS.

Please make cheques for £14.95 (which includes postage and packing) payable to Reed Business Publishing Group.

Alternatively, you can telephone your order, quoting a credit card number. Telephone 081-652 3614.

A disk containing all the example listings used in this book is available at £25.50 + VAT. Please specify size required.

## C HERE!

If you have followed our series on the use of the C programming language, then you will recognise its value to the practising engineer.

But, rather than turning up old issues of the journal to check your design for a digital filter, why not have all the articles collected together in one book, *Interfacing with C*?

The book is a storehouse of information that will be of lasting value to anyone involved in the design of filters, A-to-D conversion, convolution, Fourier and many other applications, with not a soldering iron in sight.

To complement the published series, Howard Hutchings has written additional chapters on D-to-A and A-to-D conversion, waveform synthesis and audio special effects, including echo and reverberation. An appendix provides a "getting started" introduction to the running of the many programs scattered throughout the book.

This is a practical guide to real-time programming, the programs provided having been tested and proved. It is a distillation of the teaching of computer-assisted engineering at Humberside Polytechnic, at which Dr Hutchings is a senior lecturer.

Source code listings for the programs described in the book are available on disk.

## SPECTRUM ANALYSERS



HP141T/8552B/8554B 1250MHz system	£1750
HP182C/8558B 0.1-1500MHz spectrum analyser	£1750
HP182T/8559A 21GHz system	£5000
HP35660A dynamic analyser 244µHz-102kHz	£3500
HP3580A 5Hz-50kHz opt O1. Digital readout model	£2000

As above but without option, mechanical readout	£1500
HP3582A dual-channel 25kHz analyser	£4000
HP3585A 40MHz analyser	£6000
MARCONI TF2370 110MHz analyser	£2250
TEKTRONIX 7L12 0.1MHz-1.5GHz in 7403N frame	£1350
ANRITSU MS62B 10kHz-1700MHz	£2000
ANRITSU MS68B 10kHz-4.4GHz	£4000
MARCONI 2380/2382 400MHz system	£5000
ANRITSU MS610A 2GHz spectrum analyser	£1950

## MARCONI INSTRUMENTS

2019 synthesized signal generator 10kHz-1040MHz	£2000
2091C/2092C white noise receiver/transmitter, pair	£500
2356/2357 level oscillator/level meter	£500
2380/82 400MHz spectrum analyser	£5000
2388 1GHz active probe	£400
2347 100MHz timer/counter	£175
2501 RF power meter 0.3W DC-1GHz	£100
2503 RF power meter to 100W DC-1GHz	£200
2828A/2829 digital simulator/analyser	£1000
2830 multiplex tester	£1500
2833 digital in-line monitor	£250
2970 data communications tester	£500
2955 mobile radio test set (75W version)	£3750
2956 NMT cellular adaptor, latest issue software	£1250
6460 microwave power meter with head 6421	£300
6700B sweep oscillator 8-12.4 GHz	£750
0A2805A PCM regenerator test set	£400
TF1245A Q-Meter with 1246 and 47 oscillators	£350
TF2006 FM signal generator 10-1000MHz	£400
TF2015/2171 signal generator AM/FM 10-520MHz	£400
TF2162 audio frequency attenuator	£100
TF2304 automatic modulation meter	£350
TF2370 110MHz spectrum analyser	£2000
TF2908 blanking & sync mixer	£50
TF2910/4 non-linear distortion (video) analyser	£1000
TF2914A TV insertion signal analyser	£1250
TF2910 TV interval timer	£500

**URGENTLY REQUIRED —**  
**'HIGH-END' test equipment**  
 by brand names. **TOP prices paid**  
 for HP, TEK, MARCONI etc.  
**PLEASE CALL.**

## RALFE · ELECTRONICS

36 EASTCOTE LANE, S. HARROW, MIDDLESEX HA2 8DB  
 TEL: 081-422 3593. FAX: 081-423 4009



EST  
35  
YEARS

## TEST EQUIPMENT

ADRET 7100B AM/FM signal generators 10kHz-1.3GHz	£2000
AIM 501 low distortion oscillator GPIB/RS232	£500
ANRITSU MW98A/MH925A optical TDR	£1500
AVO CB154/5 electrolytic & tant' cap' bridge	£450
BRUEL & KJAER 4230 sound level calibrator	£200
BRUEL & KJAER 2307 level recorder	£1000
DATRON 1071 digital voltmeter (R & IEEE options)	£1250
GOULD J3B audio oscillator	£200
HAMEG HM605 60MHz dual-trace oscilloscope	£295
HITACHI V1050F 100MHz dual-trace oscilloscope	£500
KIKUSUI COS5040TM 40MHz dual-trace oscilloscope	£150
LING DYNAMICS LA500 (500W vibrator amplifier)	£275
MAURY MICROWAVE 8650E TNC-calibration kit	£1750
MOTOROLA R 2010D mobile radio test set	£2950
PHILIPS PM9355 current probe	£350
PHILIPS PM5134 function generator 1mHz-20MHz	£550
PHILIPS PM5534 standard pattern generator NTSC	£2500
PHILIPS PM5545 colour encoder PAL	£500
PHILIPS PM5597 VHF modulators £250. PM5598 UHF	£500
PHILIPS PM5580 I.F. modulator	£1500
PHILIPS PM6652 1.5GHz timer/counter GPIB	£850
PHILIPS PM8202 recorder with 9874/01 temp' unit	£250
RACAL DANA 9008A automatic modulation meter	£400
RACAL 9082 signal generator 1.5-520MHz synthesized	£850
RACAL 9105 RF micro wattmeter 0.02µW-200mW	£250
RACAL 9300 RMS voltmeter - 80dB to +50	£325
RACAL Store 4-channel tape recorder	£1000
RACAL 9341 LCR databridge component tester	£300
ROHDE & SCHWARZ SMFP mobile radio test set	£1500
SCHLUMBERGER 1250 frequency response analyser	£3200
SCHLUMBERGER 4010A mobile radio test set	£1250
TEKTRONIX 7L12 1.8GHz spec' an' plug-in	£1250
TEKTRONIX J16 digital photometer	£275
TEKTRONIX 1485R full spec' TV waveform monitor	£1500
TEKTRONIX 1503/03/04 TDR cable tester	£1750
TEKTRONIX 465 100MHz dual-trace o'scope	£400
TEKTRONIX 465B as above	£450
TEKTRONIX 7623A 100MHz storage main-frame	£750
TEKTRONIX 7613/7A19/7B10 storage scope system	£295
TEKTRONIX 7904/7A19/7A15A/7B70/7B71 500MHz o'scope	£1000
TEKTRONIX 7A13, 7B53A, 7A18, 7B85, 7B87, 7C1N	£call
TEKTRONIX 475 200MHz dual-trace oscilloscope	£550
TEKTRONIX AF65110 arbitrary function generator	£1750
THURLBY PL320T-GP 0-30V 2A twice psu. GPIB	£350
WAYNE KERR B905 automatic precision bridge	£1150

## HEWLETT PACKARD



11602B transistor fixture for S parameter test	£250
11710 frequency down-converter for 8640B	£500
1741A 100MHz storage (analogue) oscilloscope	£450
214B pulse generator high-power	£650
333A distortion meter	£400
3456A digital voltmeter	£850
3478A multi-meter	£550
35660A dynamic signal analyser 244µHz-102kHz	£3500
3580A audio spectrum analyser 15 Hz-50kHz LED version	£2000
3582A audio frequency spectrum analyser	£3500
3585A 40MHz spectrum analyser	£6000
400FL mV Meter 100µV-300V fs. 20Hz-4MHz	£325
4275/001 LC2 meter	£1750
436A/8481A RF power meter	£1000
5005B signature multi-meter, programmable	£750
5328A 100MHz counter with DVM and HP/IB options	£350
5334A frequency counter 100MHz HP/IB	£1000
5334B frequency counter 100MHz HP/IB	£1000
6825A bipolar power supply/amp -20 to +20vdc 0-1A	£350
70300A tracking generator plug-in unit	£3000
70907A external mixer	£2750
7470A HP/IB plotter	£295
8405A vector voltmeter, voltage and phase to 1000MHz	£1250
8406A comb generator	£1000
8505A network analyser including 8503A S-parameter test set and 8501A storage normaliser	£5000
8548B/141T/8552B spectrum analyser system to 1250MHz	£1750
8558B/182C 1500MHz spectrum analyser system	£2000
8559A/182T 21GHz spectrum analyser system	£5000
8590A 1500MHz spectrum analyser GPIB option	£3500
8600A digital marker generator for 8601A	£325
8614A signal generator 800MHz-2.4GHz	£1250
8620C/8622A 10MHz-2.4GHz sweep generator	£2000
86290B 2-18GHz sweep generator plug-in	£2000
8640A signal generator 5-520MHz AM/FM	£750
8640B signal generator option 001/003	£1250
8656A AM/FM synthesized signal generator 0.1-990MHz	£1500
8901A modulation analyser	£2500
8901B modulation analyser options 01/02/04	£4000
8903A audio test set	£2500
8903B audio analyser options 001/010/051	£2750
8954A transceiver interface	£500

PLEASE NOTE. ALL OUR EQUIPMENT IS NOW OPERATION-VERIFICATION TESTED BEFORE DESPATCH BY INDEPENDENT B5750-REGISTERED LABORATORY. We would be pleased to handle Certificates of Calibration or NAMAS Certification by same laboratory at 'cost price'. All items covered by our 90-day parts and labour guarantee and 7 day 'Right to Refuse' warranty. URGENTLY REQUIRED FOR STOCK 'HIGH-END' TEST EQUIPMENT. Top prices paid.

CIRCLE NO. 112 ON REPLY CARD

## Antrim Transformers Ltd

25 Randalstown Road, Antrim, Co. Antrim, N. Ireland. BT41 4LD


Tel: 08494 28734

Fax: 08494 68745

## Approved standard range of toroidal transformers

to EN 60 742 ! \*

From 15VA to 1000VA !

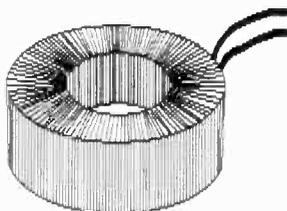

Antrim leading the way  
with better transformers  
all round.

Why not check us out ?

- ✓ Low prices and carriage charges - why pay more ?
- ✓ Reliable delivery - we won't let you down !
- ✓ QA system with 100% test - approved to ISO 9003 !
- ✓ Additional standard range to IEC 65 requirements !
- ✓ Rapid quotation service for custom designs !

\* KEMA KEUR agreement no. 919691

CIRCLE NO. 110 ON REPLY CARD

## ADVANCED ACTIVE AERIAL



The aerial consists of an outdoor head unit with a control and power unit and offers exceptional intermodulation performances: SOIP +90dBm, TOIP +55dBm. For the first time this permits full use of an active system around the lf and mf broadcast bands where products found are only those radiated from transmitter sites.

- General purpose professional reception 4kHz-30MHz.
- -10dB gain, field strength in volts/metre to 50 Ohms.
- Preselector and attenuators allow full dynamic range to be realised on practical receivers and spectrum analysers.
- Noise -150dBm in 1Hz. Clipping 16 volts/metre. Also 50 volts/metre version.

★ Broadcast Monitor Receiver 150kHz-30MHz. ★ Stabilizer and Frequency Shifters for Howl Reduction ★ Stereo Variable Emphasis Limiter 3 ★ 10-Outlet Distribution Amplifier 4 ★ PPM10 In-vision PPM and chart recorder. ★ Twin Twin PPM Rack and Box Units. ★ PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and meter movements ★ Broadcast Stereo Coders. ★ Stereo Disc Amplifiers ★ Philips DC777 short wave car combination: discount £215+VAT.

**SURREY ELECTRONICS LTD**

The Forge, Lucks Green, Cranleigh, GU6 7BG  
 Telephone: 0483 275997. Fax: 276477.


# The current alternative to operational amplifiers

**Current mode amplifiers maintain their performance over a much wider frequency span than conventional operational amplifier alternatives. Although the application circuits look similar, the mechanisms which produce the performance are very different.**

By Frank Ogden.

Compare the pinout of a typical current mode amplifier with a standard pattern op-amp and things look very similar. Pins 2 and 3 are marked as inverting/non-inverting, pin 6 delivers the output while pins 4 and 7 hook up to the power supply. A typical application circuit will use the standard virtual earth resistive feedback connection. Yet, although it seems unlikely, a current mode amplifier shows little degradation of bandwidth with set gain.

Compare this with the typical 6dB/octave degradation in open loop gain with frequency of a standard op-amp. A 741 for instance will begin to roll off in gain from about 5Hz. By contrast the HA-5020 current mode amplifier from Harris Semiconductor enjoys a typical full power bandwidth of 12MHz and performs usefully up to 50MHz. The output will slew around 800V/ $\mu$ s. It exhibits the sort of gain and phase flatness which broadcast engineers look for when designing video facilities.

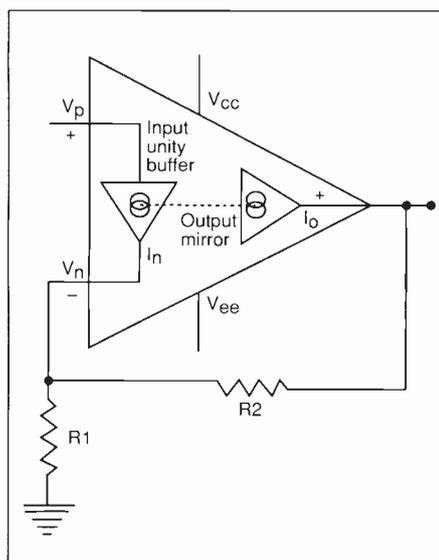



**Fig. 1. Conventional and current mode amplifiers differ in one particularly fundamental respect: where a conventional op-amp has two true input terminals, the current mode device possesses only one. The non-inverting ( $V_p$ ) terminal, the input to an internal current follower, exhibits an input impedance in the order of  $20M\Omega$  which has its output connected to the 'inverting' terminal,  $V_n$ , a very low impedance node. If  $V_n$  is connected to ground via a resistor, a current will flow dependent on the value of the resistance and the voltage present at the  $V_p$  terminal. A multiplying current mirror reflects this current flowing into or out from the  $V_n$  terminal at the output of the device. If the multiplying factor is very large, the effective system gain will be determined almost entirely by the current flowing in the network connected to the inverting terminal. Thus for an ideal current mode amplifier used in the circuit shown above, the voltage gain from  $V_p$  to the output terminal is simply  $(R_2 + R_1)/R_1$ .**

A conventional op-amp relies on possessing enough internal voltage gain such that its output voltage will reduce the voltage difference between its inverting and non-inverting inputs close to zero. Thus large signals produce large internal voltage swings within the device, usually at high impedance nodes. Collector-base capacitance in voltage amplifying devices inevitably leads to frequency dependent feedback: the equivalent shunt capacitance is equal to the collector-base capacitance multiplied by the gain of the stage. Thus what might have a very small value actually presents a capacitive drag of many times this value. If the op-amp possesses a number of gain stages, individual Miller (for that is the name of the multiplying effect) capacitances produce enough collective phase shift to make the device unstable at low values of the closed loop gain (where the level of feedback is high). "Internally compensated" is actually a euphemism for adding a comparatively large internal capacitor to lump all the phase shift into a single, dominant pole. But its effect on performance is a disaster.

Conventional op-amps are just as bad at handling step changes in voltage: all this internal Miller capacitance needs to be charged up – or down – before the device output can reg-

## HA-5020 KEY SPECIFICATIONS

Unity gain bandwidth	100MHz
Full power bandwidth	12MHz
Slew rate	800V/ $\mu$ s
Output current	$\pm 30$ mA
Output voltage swing	$\pm 12$ V
Open loop gain	70dB  400 $\Omega$ $R_L$
Drive capability	3.5V  75 $\Omega$
Differential gain	<0.02%
Differential phase	<0.03%
Rise/fall time	5ns
Input noise voltage	4.5nV/ $\sqrt$ Hz
Supply current	10mA
Supply voltage	$\pm 5$ V to $\pm 15$ V

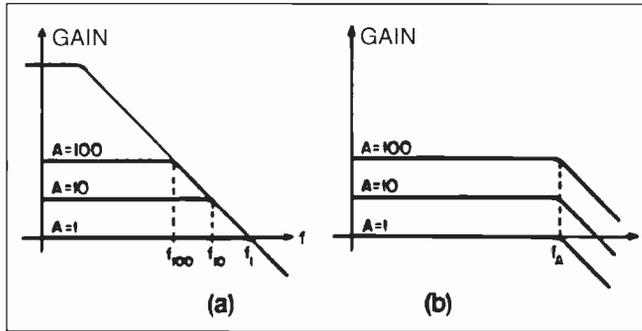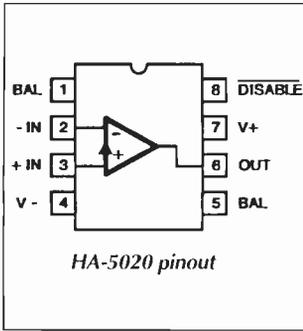

Conventional op-amps suffer a linear reduction in open loop gain vs frequency (a). CM amplifiers by contrast exhibit very low internal voltage swings which dramatically reduces the fall in open loop gain with frequency (b).

## ELECTRONICS WORLD PROFESSIONAL SERVICES

TO OBTAIN YOUR FREE HA-5020 SAMPLE AND DATA SHEET

Simply fill out the coupon between pages 672 and 673 making sure that you answer all the questions. Please note that this offer applies to the UK and Scandinavia only and is restricted to the first 1000 replies.

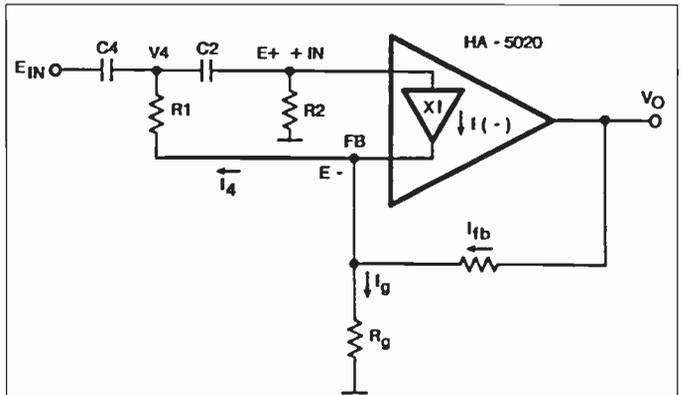


Fig. 2. The HA-5020 connected as a high pass active filter. This circuit will function effectively up to 12MHz with appropriate passive component values.

ister the change. The slew rate is set by the maximum current available from the internal voltage amplifiers in charging or discharging the internal Miller capacitance.

### The current alternative

A current mode amplifier comprises two sections: a non-inverting unity gain input buffer with its high impedance input connected as the non-inverting input while the buffer output, a complementary emitter follower, brought out as the "inverting" terminal. The second section comprises an output complementary current mirror, the output value and polarity of which depends on the current flowing into or out from the "inverting" amplifier terminal sensed by a current mirror in the unity gain input buffer.

None of this looks particularly promising at first glance for commonsense seems to suggest that the output of a low impedance buffer (marked input unity buffer in Fig. 1) could not readily serve as an inverting input connection to a precision amplifier.

Neglecting the maths for a moment, look at the amplifier function this way. Apply a positive input voltage to the high impedance ( $20M\Omega$ ) input terminal  $V_p$  relative to ground. This will cause the same output voltage – give or take a few microvolts – to be delivered to the inverting terminal  $V_n$  but at an impedance of just a few ohms. Thus the full input voltage is developed across  $R_1$  causing a current to flow in the buffer proportional to the input voltage and inversely proportional to the value of  $R_1$ , i.e. Ohm's Law.

The input unity buffer measures the current flowing into or out from the terminal  $V_n$  through a complementary current mirror integrated into the buffer circuit. The mirror current in turn drives an independent output current mirror with a current transfer ratio of several thousand. Effectively this means that a current of microamps flowing into or out of the inverting terminal  $V_n$  produces a current of milliamps ( $I_o$ ) at the output terminal of the amplifier.

By coupling this output current back to the inverting input terminal via  $R_2$ , two things happen. Firstly, an output voltage is developed proportional to the value of  $I_o \times R_2$ . Secondly, the current flowing in  $R_2$  acts in a sense to reduce the current flowing into or out from the unity gain buffer. Thus, provided that the current transfer ratio between the input and output mirrors is very large, the overall system voltage gain approximates to  $(R_2 + R_1)/R_1$ .

This type of circuit configuration derives its gain/bandwidth independence through a complete absence of internal signal voltage nodes. Even the largest signal swings are restricted to internal voltage changes in the order of 100mV or so. Thus the Miller effect cannot apply to current mode amplifiers. Compare this situation to the large voltage swing inside a conventional op-amp. The only place in a C-M amplifier where large swings occur is the output node; first order bandwidth is determined by the time constant formed between the device output capacitance and the feedback resistor,  $R_2$ .

Second order effects do result in reduced

bandwidth with increasing open loop gain but these are small when compared with conventional devices. For instance a C-M amplifier set up for unity gain might deliver a  $-3dB$  turnover at 100MHz, a figure which falls to 65MHz when the system gain is increased to 10. By contrast, a conventional 100MHz op-amp would suffer a bandwidth reduction to 10MHz as its closed loop gain was increased to 10.

### The HA-5020

This device uses current mode operation and was designed for video applications at system gains of between 1 and 10, for instance in video mixers and multiplexers. For instance, it will drive up to two  $75\Omega$  lines at video levels with very low distortion and an accompanying gain flatness of 0.1dB. Other applications include high frequency active filters and IF amplifiers. The general form follows the organisation of Fig. 1. Typical values for  $R_2$  would be around  $1k\Omega$ . Gain variation would normally be achieved by choosing an appropriate value for  $R_1$ .

The device also includes a disable function which significantly reduces supply current and forces the output to a true high impedance state. This allows multiple amplifiers to be wire OR'd as amplifying video multiplexers.

The availability of a high impedance buffer at the front end of a C-M amplifiers in general and the HA-5020 specifically allows the easy construction of Sallen & Key 12dB/octave active filters. The general form is shown in Fig. 2.



**AMSTRAD PORTABLE PC'S FROM £149 (PPC1512SD), £179 (PPC1512DD), £179 (PPC1640SD), £209 (PPC1640DD), MODEMS £30 EXTRA. NO MANUALS OR PSU.**

**HIGH POWER CAR SPEAKERS.** Stereo pair output 100w each. 4ohm impedance and consisting of 6 1/2" woofer 2" mid range and 1" tweeter. Ideal to work with the amplifier described above. Price per pair £30.00 Order ref 30P7R

**2KV 500 WATT TRANSFORMERS** Suitable for high voltage experiments or as a spare for a microwave oven etc. 250v AC input. Now only £4.00 ref 4P157

**MICROWAVE CONTROL PANEL.** Mains operated, with touch switches. Complete with 4 digit display, digital clock, and 2 relay outputs one for power and one for pulsed power (programmable). Ideal for all sorts of precision timer applications etc. Now only £4.00 ref 4P151.

**FIBRE OPTIC CABLE.** Stranded optical fibres sheathed in black PVC. Five metre length £7.00 ref 7P29R

**12V SOLAR CELL.** 200mA output ideal for trickle charging etc. 300 mm square. Our price £15.00 ref 15P42R

**PASSIVE INFRA-RED MOTION SENSOR.** Complete with daylight sensor, adjustable lights on timer (8 secs -15 mins), 50' range with a 90 deg coverage. Manual override facility. Complete with wall brackets, bulb holders etc. Brand new and guaranteed. Now only £19.00 ref 19P29

Pack of two PAR38 bulbs for above unit £12.00 ref 12P43R  
**VIDEO SENDER UNIT** Transmit both audio and video signals from either a video camera, video recorder or computer to any standard TV set within a 100' range! (tune TV to a spare channel). 12v DC op. £15.00 ref 15P39R Suitable mains adaptor £5.00 ref 5P191R

**FM TRANSMITTER** housed in a standard working 13A adapter (bug is mains driven) £26.00 ref 26P2R

**MINIATURE RADIO TRANSCIEVERS** A pair of walkie talkies with a range of up to 2 kilometres. Units measure 22x52x155mm. Complete with cases. £30.00 ref 30P12R

**FM CORDLESS MICROPHONE.** Small hand held unit with a 500' range! 2 transmit power levels reqs PP3 battery. Tuneable to any FM receiver. Our price £15. ref 15P42AR

**12 BAND COMMUNICATIONS RECEIVER.** 9 short bands. FM, AM and LW DX/local switch, tuning 'eye' mains or battery. Complete with shoulder strap and mains lead. **NOW ONLY £19.00!! REF 19P14R.**

**CAR STEREO AND FM RADIO.** Low cost stereo system giving 5 watts per channel. Signal to noise ratio better than 45db. wow and flutter less than .35%. Neg earth. £19.00 ref 19P30

**LOW COST WALKIE TALKIES.** Pair of battery operated units with a range of about 200'. Our price £8.00 a pair ref 8P50R

**7 CHANNEL GRAPHIC EQUALIZER.** plus a 60 watt power amp! 20-21KHz 4-8R 12-14v DC negative earth. Cased. £25. ref 25P14R

**NICAD BATTERIES.** Brand new top quality. 4 x AA's £4.00 ref 4P44R. 2 x C's £4.00 ref 4P73R. 4 x D's £9.00 ref 9P12R. 1 x PP3 £6.00 ref 6P35R

**TOWERS INTERNATIONAL TRANSISTOR SELECTOR GUIDE.** The ultimate equivalents book. Latest edition £20.00 ref 20P32R

**CABLE TIES.** 142mm x 3.2mm white nylon pack of 100 £3.00 ref 3P104R. Bumper pack of 1,000 ties £14.00 ref 14P6R

**GOT A CARAVAN OR BOAT?**

**NEW 80 PAGE FULL COLOUR LEISURE CATALOGUE**

**2,500 NEW LINES FREE WITH ORDER ON REQUEST**

**OR SEND £1.00**

**GEIGER COUNTER KIT.** Complete with tube, PCB and all components to build a battery operated geiger counter. £39.00 ref 39P1R

**FM BUG KIT.** New design with PCB embedded coil. Transmits to any FM radio. 9v battery req'd. £5.00 ref 5P158R

**FM BUG.** Built and tested superior 9v operation. £14.00 ref 14P3R

**COMPOSITE VIDEO KITS.** These convert composite video into separate H sync, V sync and video. 12v DC. £8.00 ref 8P39R

**SINCLAIR C5 MOTORS.** 12v 29A (full load) 3300 rpm 6" x 4" 1/4" O/P shaft. New £20.00 ref 20P22R

As above but with fitted 4 to 1 inline reduction box (800rpm) and toothed nylon belt drive cog £40.00 ref 40P8R

**SINCLAIR C5 WHEELS.** 13" or 16" dia including treaded tyre and inner tube. Wheels are black, spoked one piece poly carbonate. 13" wheel £6.00 ref 6P20R. 16" wheel £6.00 ref 6P21R

**ELECTRONIC SPEED CONTROL KIT.** For c5 motor. PCB and all components to build a speed controller (0.95% of speed). Uses pulse width modulation. £17.00 ref 17P3R

**SOLAR POWERED NICAD CHARGER.** Charges 4 AA nicads in 8 hours. Brand new and cased £6.00 ref 6P3R

**12 VOLT BRUSHLESS FAN.** 1/2" square brand new ideal for boat, car, caravan etc. £5.00 ref 5P206

**ACORN DATA RECORDER ALF503.** Made for BBC computer but suitable for others. Includes mains adaptor, leads and book. £15.00 ref 15P43R

**VIDEO TAPES.** Three hour superior quality tapes made under licence from the famous JVC company. Pack of 5 tapes. New low price £8.00 ref 8P161

**PHILIPS LASER. 2MW HELIUM NEON LASER TUBE.** BRAND NEW FULL SPEC £40.00 REF 40P10R. MAINS POWER SUPPLY KIT £20.00 REF 20P33R. READY BUILT AND TESTED LASER IN ONE CASE £75.00 REF 75P4R.

**15 TO 220V INVERTER KITs** supplied it will handle up to about 15w at 220v but with a larger transformer it will handle 80 watts. Basic kit £12.00 ref 12P17R. Larger transformer £12.00 ref 12P41R

**VERO EASI WIRE PROTOTYPING SYSTEM.** Ideal for designing projects on etc. Complete with tools, wire and reusable board. New low bargain price only £2.00 ref 2P21

**HIGH RESOLUTION 12" AMBER MONITOR.** 2v 1.5A Hercules compatible (TTL input) new and cased £22.00 ref 22P2R

**VGA PAPER WHITE MONO monitors** new and cased 240v AC. £55.00 ref 59P4R

**25 WATT STEREO AMPLIFIER.** c. STK043. With the addition of a handful of components you can build a 25 watt amplifier. £4.00 ref 4P69R (Circuit dia included)

**BARGAIN NICADS AAA SIZE 200MAH 1.2V PACK OF 10** £4.00 REF 4P92R. PAAK OF 100 £30.00 REF 30P16R

**FRESNEL MAGNIFYING LENS** 83 x 52mm £1.00 ref BD827R

**ALARM TRANSMITTERS.** No data available but nicely made complex radio transmitters 9v operation. £4.00 each ref 4P81R

**12V 19A TRANSFORMER.** Ex equipment but otherwise ok. Our price £2.00

**GX4000 COMPUTERS.** Customer returned games machines complete with plug in game, joysticks and power supply. Retail price is almost £100. Ours is £12.00 ref B12P1

**ULTRASONIC ALARM SYSTEM.** Once again in stock these units consist of a detector that plugs into a 13A socket in the area to protect. The receiver plugs into a 13A socket anywhere else on the same supply. Ideal for protecting garages, sheds etc. Complete system £25.00 ref B25P1 additional detectors £11.00 ref B11P1

**IBM XT KEYBOARDS.** Brand new 86 key keyboards £5.00 ref 5P612

**IBM AT KEYBOARDS.** Brand new 86 key keyboards £15.00 ref 15P612

**386 MOTHER BOARDS.** Customer returned units without a cpu fitted. £22.00 ref A22P1

**BSB SATELLITE SYSTEMS**

**BRAND NEW**

**REMOTE CONTROL**

**£49.00 REF F49P1**

**286 MOTHER BOARDS.** Brand new but customer returns so may need attention. Complete with technical manual £20.00 ref A20P2

**286 MOTHER BOARDS.** Brand new and tested complete with technical manual. £49.00 ref A49P1

**UNIVERSAL BATTERY CHARGER.** Takes AA's, C's, D's and PP3 nicads. Holds up to 5 batteries at once. New and cased, mains operated. £6.00 ref 6P36R

**IN CAR POWER SUPPLY.** Plugs into cigar socket and gives 3, 4, 5, 6, 7, 5.9, and 12v outputs at 800mA. Complete with universal spider plug. £5.00 ref 5P167R

**RESISTOR PACK.** 10 x 50 values (500 resistors) all 1/4 watt 2% metal film. £5.00 ref 5P170R

**CAPACITOR PACK.** £4.00

**MIRACOM WS4000 MODEMS**

**V21/23**

**AT COMAND SET**

**AUTODIAL/AUTOANSWER**

**FULL SOFTWARE CONTROL**

**STONE AND PULSE DIALLING**

**£29**

**IBM PRINTER LEAD.** (D25 to centronics plug) 2 metre parallel. £5.00 ref 5P186R

**COPPER CLAD STRIP BOARD.** 17" x 4" of 1" pitch 'vero' board. £4.00 a sheet ref 4P62R or 2 sheets for £7.00 ref 7P22R

**STRIP BOARD CUTTING TOOL.** £2.00 ref 2P352R

**50 METRES OF MAINS CABLE.** £3.00 2 core black precut in convenient 2 m lengths. Ideal for repairs and projects. ref 3P91R

**4 CORE SCREENED AUDIO CABLE.** 24 METRES £2.00. Precut into convenient 1.2 m lengths. Ref 2P365R

**TWEETERS 2 1/4" DIA.** 8 ohm mounted on a smart metal plate for easy fixing. £2.00 ref 2P366R

**COMPUTER MICE.** Originally made for Future PC's but can be adapted for other machines. Swiss made £8.00 ref 8P57R. Atari ST conversion kit £2.00 ref 2P362R

**6 1/2" 20 WATT SPEAKER.** Built in tweeter 4 ohm £5.00 ref 5P205R

**WINDUP SOLAR POWERED RADIO!** FM/AM radio takes rechargeable batteries complete with hand charger and solar panel. 14P200R

**PC STYLE POWER SUPPLY.** Made by AZTEC. 110v or 240v input. +5 @ 15A, +12 @ 5A, -12 @ 5A, -5 @ 3A. Fully cased with fan, on/off switch, IEC inlet and standard PC flyleads. £15.00 ref F15P4

**ALARM PIR SENSORS.** Standard 12v alarm type sensor will interface to most alarm panels. £16.00 ref 16P200

**ALARM PANELS.** 2 zone cased keypad entry, entry exit time delay

**BULL ELECTRICAL**

**250 PORTLAND ROAD HOVE SUSSEX**  
**BN3 5QT TELEPHONE 0273 203500**

**MAIL ORDER TERMS: CASH PO OR CHEQUE**  
**WITH ORDER PLUS £3.00 POST PLUS VAT.**

**PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY**

**NEXT DAY DELIVERY £8.00**

**FAX 0273 23077**



etc. £18.00 ref 18P200

**MODEMS FOR THREE POUNDS!!**  
Fully cased UK modems designed for dial up system (PSTN) no data cr info but only £3.00 ref 3P145R

**TELEPHONE HANDSETS**

Bargain pack of 10 brand new handsets with mic and speaker only £3.00 ref 3P146R

**BARGAIN STRIPPERS**

Computer keyboards. Loads of switches and components excellent value at £1.00 ref CD40R

**DATA RECORDERS**

Customer returned mains battery units built in mic ideal for Computer or general purpose audio use. Price is £4.00 ref 4P100R

**SPECTRUM JOYSTICK INTERFACE**

Plugs into 48K Spectrum to provide a standard Atari type joystick port. Our price £4.00 ref 4P101R

**ATARI JOYSTICKS**

Ok for use with the above interface, our price £4.00 ref 4P102R

**BENCH POWER SUPPLIES**

Superbly made fully cased (metal) giving 12v at 2A plus a 6V supply. Fused and short circuit protected. For sale at less than the cost of the case! Our price is £4.00 ref 4P103R

**SPEAKER WIRE**

Brown twin core insulated cable 100 feet for £2.00 REF 2P79R

**MAINS FANS**

Brand new 5" x 3" complete with mounting plate quite powerful and quite quiet. Our price £1.00 ref CD41R

**DISC DRIVES**

Customer returned units mixed capacities (up to 1.44M) We have not sorted these so you just get the next one on the shelf. Price is only £7.00 ref 7P1R (worth it even as a stripper)

**HEX KEYBOARDS**

Brand new units approx 5" x 3" only £1.00 each ref CD42R

**PROJECT BOX**

5 1/2" x 3 1/2" x 1 1/2" black ABS with screw on lid. £1.00 ref CD43R

**SCART TO SCART LEADS**

Bargain price leads at 2 for £3.00 ref 3P147R

**SCART TO D TYPE LEADS**

Standard Scart on one end, Hi density D type on the other. Pack of ten leads only £7.00 ref 7P2R

**OZONE FRIENDLY LATEX**

250ml bottle of liquid rubber sets in 2 hours. Ideal for mounting PCB's. Fixing wires etc. £2.00 each ref 2P379R

**QUICK SHOTS**

Standard Atari compatible hand controller (same as joysticks) our price is 2 for £2.00 ref 2P380R

**VIEWDATA SYSTEMS**

Brand new units made by TANDATA complete with 1200/75 built in modem infra red remote controlled qwerty keyboard BT approved Prestel compatible, Centronics printer port RGB colour and composite output (works with ordinary television) complete with power supply and fully cased. Our price is only £20.00 ref 20P1R

**AC STEPDOWN CONVERTOR**

Cased units that convert 240v to 110v 3" x 2" with mains input lead and 2 pin American output socket (suitable for resistive loads only) our price £2.00 ref 2P381R

**SPECTRUM +2 LIGHT GUN PACK**

complete with software and instructions £8.00 ref 8P58R/2

**CURLY CABLE**

Extends from 8" to 6 feet! D connector on one end, spade connectors on the other ideal for joysticks etc (6 core) £1.00 each ref CD44R

**COMPUTER JOYSTICK BARGAIN**

Pack of 2 joysticks only £2.00 ref 2P382R

**BUGGING TAPE RECORDER**

Small hand held cassette recorders that only operate when there is sound then turn off 6 seconds after so you could leave it in a room all day and just record any thing that was said. Price is £20.00 ref 20P3R

**IEC MAINS LEADS**

Complete with 13A plug our price is only £3.00 for TWO! ref 3P148R

**NEW SOLAR ENERGY KIT**

Contains 8 solar cells, motor, tools, fan etc plus educational booklet. Ideal for the budding enthusiast! Price is £12.00 ref 12P2R

**286 AT PC**

**286 MOTHER BOARD WITH 640K RAM FULL SIZE METAL CASE, TECHNICAL MANUAL, KEYBOARD AND POWER SUPPLY £139 REF 139P1** (no i/o cards or drives included) Some metal work req'd phone for details.

**35MM CAMERAS** Customer returned units with built in flash and 28mm lens 2 for £8.00 ref 8P200

**STEAM ENGINE** Standard Mamod 1332 engine complete with boiler piston etc £30 ref 30P200

**TALKING CLOCK**

LCD display, alarm, battery operated. Clock will announce the time at the push of a button and when the alarm is due. The alarm is switchable from voice to a cock crowing! £14.00 ref 14P200R

**HANDHELD TONE DIALLERS**

Small units that are designed to hold over the mouth piece of a telephone to send MF dialling tones. Ideal for the remote control of answer machines. £5.00 ref 5P209R

**COMMODORE 64 MICRODRIVE SYSTEM**

Complete cased brand new drives with cartndge and software 10 times faster than tape machines works with any Commodore 64 setup. The original price for these was £49.00 but we can offer them to you at only £25.00! Ref 25P1R


**ATARI 2600 GAMES COMPUTER** Brand new with joystick and 32 game cartridge (plugs into TV) £29.00 ref F29P1 also some with 1 game at £19.00 ref F19P2

**BEER PUMPS** Mains operated with fluid detector and electronic timer standard connections. Ex equipment. £18.00 ref F18P1

**90 WATT MAINS MOTORS** Ex equipment but ok (as fitted to above pump) Good general purpose unit £9.00 ref F9P1

**HI FI SPEAKER BARGAIN** Originally made for TV sets they consist of a 4" 10 watt 4R speaker and a 2" 140R tweeter. If you want two of each plus 2 of our crossovers you can have the lot for £5.00 ref F5P2

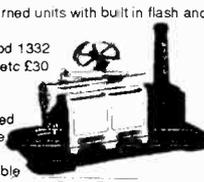**VIDEO TAPES E180 FIFTY TAPES FOR £70.00 REF F70P1**  
**360K 5 1/4" Brand new drives white front. £20.00 Ref F20P1**



SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

CIRCLE NO. 114 ON REPLY CARD

# UPDATING the choice for handling data in the lab

*How does the updated LabWindows meet current data acquisition demands? Allen Brown measures the improvements.*

National Instruments updated *LabWindows* data acquisition and processing package is not so much an improvement but an extension to the previous version, and a much broader range of options is now on offer.

The basic product is essentially a software development environment, producing code for processing data derived from instruments via the *IEEE488*, the *RS232* or PC expansion cards.

Two programming languages are available, *QuickBasic* and *C* – though the version of *C* does not entirely conform to the ansi standard and so programs ported into *LabWindows* may require some modification to be accepted by its *C* compiler. For example, it does not recognise `float x;`.

## Powerful library

It is *LabWindows*' impressive library containing a large variety of subroutines for performing data acquisition, data processing and display that makes the package so attractive. When creating code in *LabWindows* the designer in, effect, assembles a list of library subroutines to perform the required task. Appearance is very similar to the standard Microsoft language development packages with mouse driven drop-down menus and easy access to help files and compiler facilities. Code produced by the designer may have the constructs of *C* (or *QuickBasic*) but all functional i/o operations and analysis consists of subroutines drawn from the extensive library.

Prompting the subroutine to do what is needed is achieved by entering a series of dialogue boxes which present the user with the various options and are clicked with the mouse.

When complete, *LabWindows* generates the appropriate code and this is attached to the user's own code.

For example the code shown in the top half of **Fig. 1** generates a sine wave with added noise (pseudo random). Having created the data, it can be displayed graphically by entering the appropriate dialogue boxes from the drop down menu. By responding to the various options the original code is duly amended (bottom half **Fig. 1**).

Evoking the `run` option from the appropriate drop-down menu makes the source program compile and execute (provided there are no errors) with the resulting graphical display (**Fig. 2**). Users can single step through the source code in one window while watching the progress of variables in another.

Programming in the *LabWindows* environment is not too different from object oriented design where the library subroutines may be referred to as pre-designed and tested objects. Programming is therefore performed at quite a high level, allowing the user to concentrate on design aspects of the code and avoid low level problems such as interfacing, storage and display.

Part of the *LabWindows* library is an extensive set of device drivers for commonly used test instruments with the *IEEE488* interface. It is even possible to reproduce with relative ease the front panel of an instrument (**Fig. 3**).

## Exploiting the 386 PC

One of the main drawbacks of early versions of *LabWindows* was a constraint on memory, where the package was expected to work entirely within the normal dos 640K. The problem was that though the source language is *C* (or *QuickBasic*), the technique of attaching routines from the run-time libraries renders *LabWindows* coding as high level programming. Like all high level languages, large executable programs could be produced. But in the new version the 640K boundary has been removed by employing a dos/16M

**System requirements**  
386/486 PC  
4Mbyte extended ram  
Mouse coprocessor  
(for 386 PC)  
VGA graphics

**Supplier details**  
*LabWindows* 2.1  
£695; Advanced  
analysis £1495,  
National Instruments  
UK Ltd,  
21 Kingfisher Court,  
Hambridge Road,  
Newbury, Berkshire  
RG14 5SJ. Tel: 0635  
523545.

extender and the virtual memory manager (VMM) from Rational Systems. The dos/16M allows programs greater than 640K to be run on a PC with extended memory. When there is inadequate extended memory the VMM comes into play by exchanging segments of program between ram and hard disc. As a result the package now fully utilises the advanced features of the 386 and 486 PCs – it can run on 286 PCs but the operational speed makes this combination quite unattractive.

For computational intensive needs National Instruments also supplies an advanced analysis package containing routines specifically for the 80387 maths coprocessor (though this is generally expected these days with high performance PCs based on 80486 CPUs).

A few years ago no-one would complain about waiting a minute or two for a 2048-point FFT; today we expect this to take only a couple of seconds at most. But since intensive computation is now a general requirement for data processing, the advanced analysis option really should be a standard part of the *LabWindows* package.

**Added power**

*LabWindows* has been designed primarily as a package for development of data acquisition from laboratory instrumentation. But to complement this, the product is supplied with an extended library of device drivers for a wide range of well known instruments which have the IEEE488 interface. HP instruments feature strongly among the library entries. Access to the facilities offered by the library instruments can be gained with relative ease: users need not rely on low level programming to configure remote instruments as this is achieved by options in the device drivers.

Since VGA has become a universal standard in PCs the need for numerous fonts often arises. *LabWindows* has a variety of fonts which can be used to great effect to enhance the quality of the graphics displays and the full resolution offered by the VGA standard has been used to create quite pleasing display effects. Of course these effects can easily be evoked by accessing the library sub-routines.

For development of a data acquisition systems *LabWindows* must rate among one of the most attractive products on the market – not only for its ease of use but also for its extensive range of device drivers for instruments and expansion cards out in its library.

So what *LabWindows* does, it does well and there is no doubt that it is a sensibly-designed, quality product. But with the trend towards real-time processing, it might be more appropriate for the processing to be off-loaded to an auxiliary expansion card hosting a high performance DSP processor. This feature is already available with Display-XL and future versions of *LabWindows* should really move in this direction. One final point is that with the emergence of Numerical C, National Instruments will have to look very carefully at their particular version of C.

```

File Edit Program Instruments Libraries View Options
PROGRAM
int err, i ;

main()
{
  cls() ;
  for(i=1 ; i < 400 ; i++){
    my_array[i] = sin(.05*i) + 0.5 - (double)rand*1/32767.0 ;
  }
}

INTERACTIVE
double my_array[400] ;
int err, i ;

main()
{
  cls() ;
  for(i=1 ; i < 400 ; i++){
    my_array[i] = sin(.05*i) + 0.5 - (double)rand*1/32767.0 ;
  }
}
    
```


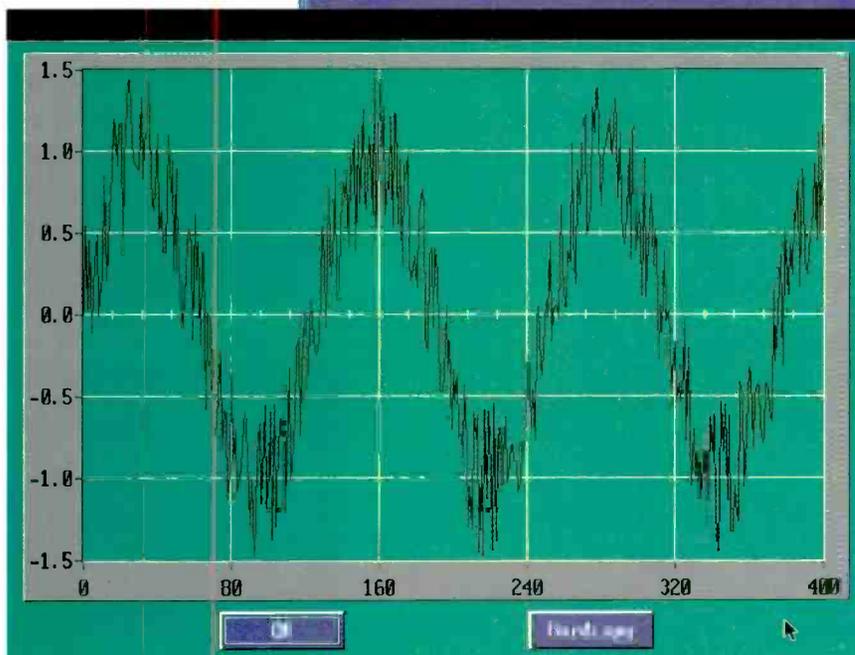


Fig. 1. *LabWindows* offers a standard PC software development environment.

Fig. 2. Graphics display exploits the full resolution of the VGA standard.

Fig. 3. A front panel instrument set-up for remote access purposes can be set up with ease.

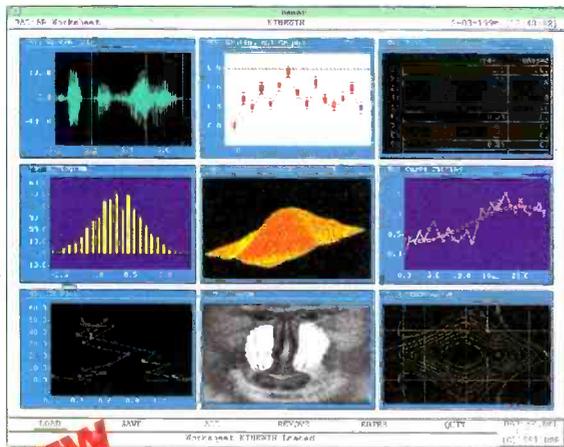**The Big Picture in Data Analysis**  
**Just Got Bigger**



**NEW**

# DADiSP 3.0®

DADiSP 3.0's new point-and-click menus put *you* in control: from Data Collection, Data Reduction and Management, through Visual Data Analysis and Hypothesis testing, on to final results. *DADiSP the best way to view, analyse and manipulate your data.*

DADiSP automatically builds a permanent and reusable worksheet as you work. So you can organise your data, methods and graphs in DADiSP worksheets for future reference and future projects. Then automate DADiSP with your own macros and menus.

DADiSP also has powerful add-in modules. You can talk to your test instruments with the DADiSP/488 driver or use DADiSP/LT for Data Acquisition or *add-in and run your own favourite programs from within DADiSP.*

NEW DADiSP 3.0 is available now for IBM PC compatibles (80286, 80386 or 80486 with 2Mb of extended RAM) and also for SUN, HP, IBM, NeXT, DEC. Concurrent & other workstations. Call Adept Scientific today for a full information pack.

**Adept Scientific Micro Systems Ltd**  
**Tel: (0462) 480055 — Fax: (0462) 480213**



### Matrix Processing

*Matrix Math, 2D FFTs  
 Eigen Values & Vectors  
 Inverse/Transpose*

### Image Processing

*Medical Imaging  
 Seismology  
 Communications*

### Lab Automation

*Data Acquisition  
 IEEE-488  
 Test & Measurement*

### Science

*Statistics,  
 Hypothesis Testing  
 Peak Analysis*

### Engineering

*Signal Processing & FFTs  
 Filter Design  
 Speech Analysis  
 Vibration Analysis*


CIRCLE NO. 115 ON REPLY CARD

# PICO ADC-10

8-bit Analog to Digital Convertor  
 for IBM PCs & compatibles  
 • 10-25 kHz typical sampling speed  
 • 0-5 v input range

# £49

+ VAT  
 (including p+p)

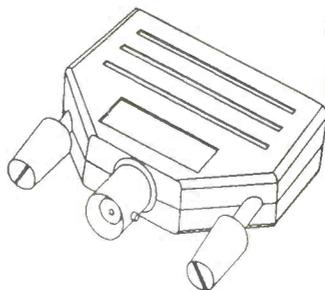


- Plugs directly into parallel printer port
- Requires no external power or expansion slots
- BNC input connector
- Supplied with software to use as a voltmeter & oscilloscope, plus Turbo C and Pascal drivers

**Pico Technology Limited**  
 Broadway House, 149-151 St. Neots Road,  
 Hardwick, Cambridge CB3 7QJ  
 Tel. 0954 211716 Fax. 0954 211880

CIRCLE NO. 124 ON REPLY CARD
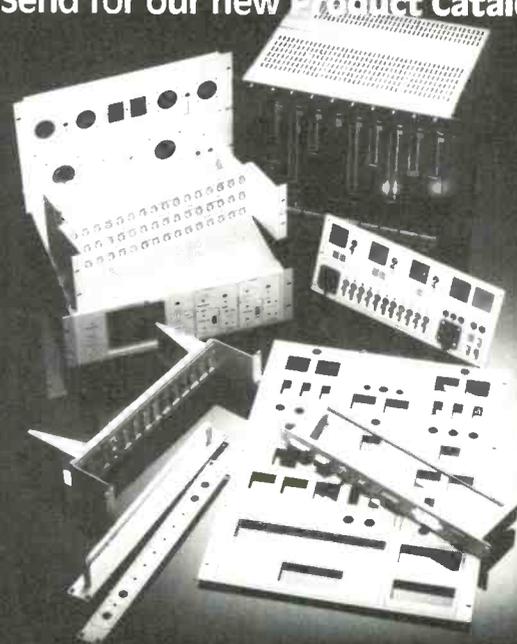
## Custom metalwork — good & quick!

Plus a wide range of rack-mounting cases etc. from stock.  
 Send for our new Product Catalogue.



**IPK Broadcast Systems**  
 3 Darwin Close Reading Berks RG2 0TB  
 Tel: (0734) 311030 Fax: (0734) 313836

CIRCLE NO. 125 ON REPLY CARD

# Don't say goodbye to the design engineer – yet

*EE Designer III is an electronic design engineering system – according to the literature. John Anderson puts those claims to the test.*

**E**E Designer claims to be an integrated electronic design engineering system. So is the electronic designer redundant? Not yet, but the package is certainly comprehensive, blending tasks as diverse as layout design and logic simulation. Functionality of the product is good too, though it does have a less than ideal user interface and the sound system is guaranteed to turn the user into the least popular person in the design office.

One undoubted plus is that the software is available on rental at 10% of the purchase price per month enabling the unsure to use it and understand its capabilities at leisure, with a minimal outlay.


Origins of *EE Designer* itself are complex. Author Visionics is based in Singapore and Sweden, and sales literature is clearly targeted at an American market. But Betronex has been its agent in the UK for many years, so support should be good.

Visionics has built its system around front annotation and back annotation. Front annotation is where definitions of the system components occur at the schematic capture stage. But back annotation is usually offered by only the better PCB design products and allows decisions such as gate allocations made on the PCB to be translated back to the schematic. An amazing claim by the authors is that *EE Designer* can be used to back annotate a complete design from PCB (though this was not checked during the review).

On execution, the package presents



the user with a textual selection menu, traversed by the mouse-controlled highlight, with the menu controlling execution of a number of editor environments and processing programs.

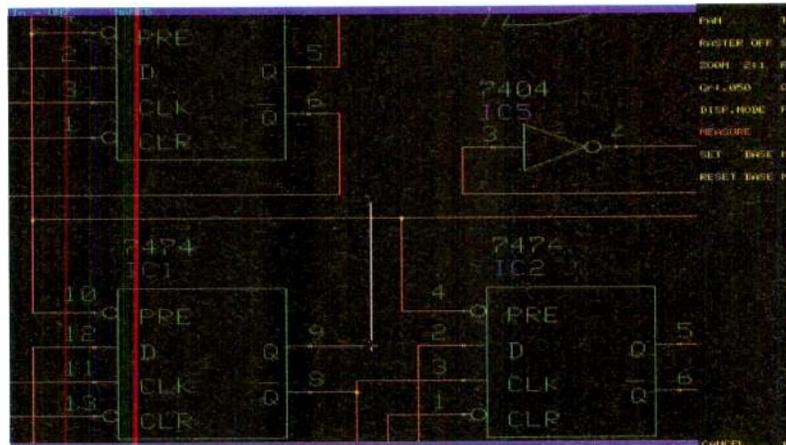Connection between the various parts of the program is through the databases, so the schematic capture database is used to produce the bill of materials, netlist and circuit simulation data, and the PCB database is used to produce the final artwork and thermal analysis with inputs from a netlist.



*Main menu contains a large number of options*

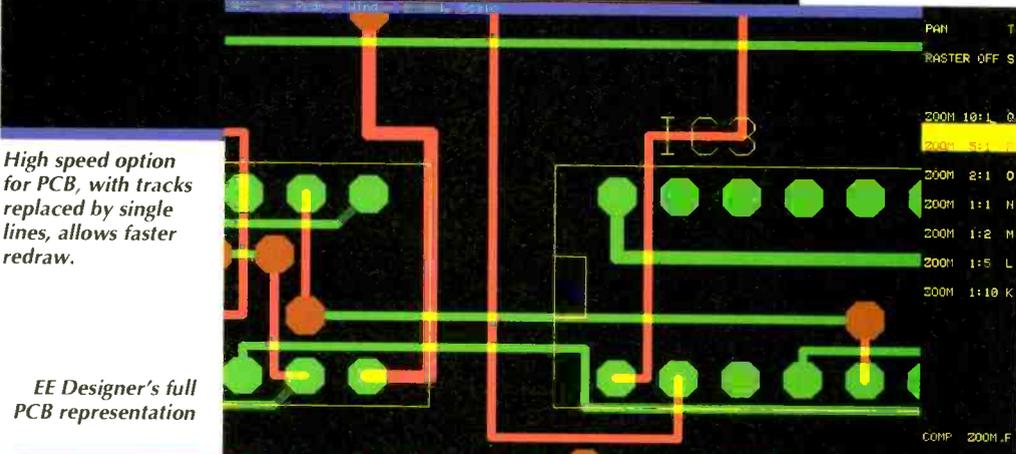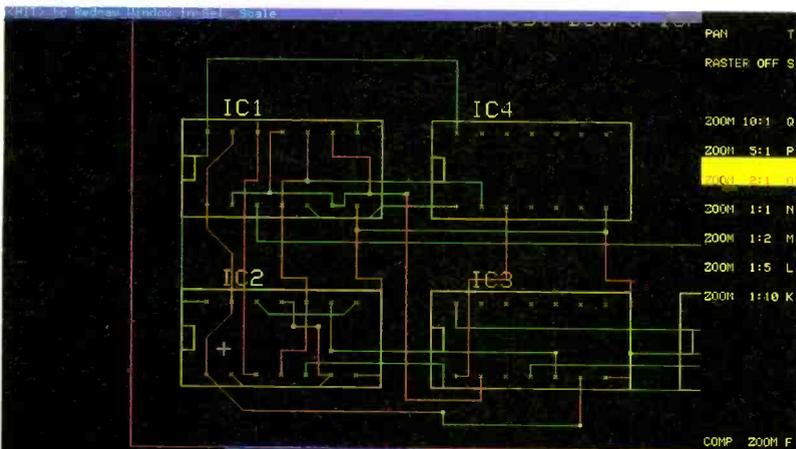*EE Designer's schematic editor: the white trace is in the process of being moved.*



High speed option for PCB, with tracks replaced by single lines, allows faster redraw.

EE Designer's full PCB representation

EE SYSTEM by Visionics - EE Designer STD. (Ver. 1.10 Rev. 920715)

DATABASE INTEGRATOR

INITIAL DEFINITIONS: Job Files path: **\\EED3JOB\**

Define Integrated Database Name	counter	Integrated	After integration
Define SCHEMATICS Database file	counter	Found	Dbase files will be:
Define LAYOUT Database file	counter	Found	Unchanged counter

STATUS DEFINITION:

Set FRONT ANNOTATION REQ. FLAG **Front Annotation: Not required**

Reset FRONT ANNOTATION REQ. flag

Set BACK ANNOTATION REQ. flag **Back Annotation: Not required**

Reset BACK ANNOTATION REQ. flag

EXECUTION MODE:

Create Scratch Database **EE SYSTEM by Visionics - EE Designer STD. (Ver. 1.10 Rev. 920715)**

Do not Create Scratch Database **DEFAULT PARAMETERS SETUP**

Execute Integ

SCHEMATIC CAPTURE:	GENERAL OPTIONS:
Initial Working Options	Graphics Display Options
Text Size Table	System Unit of Measure
LAYOUT DESIGN:	Menu Cursor Display Options
Initial Working Options	Automatic Backup Setup
Graphics Menu Trace Width Table	INPUT/OUTPUT:
Symbol Creation Pad Sizes	Disk/Subdirectories
Board/Silk Screen Outline Width	Output Channels Setup
Text Lines Width Table	Output Devices
Via Pad Diameters	FORMAT NAMES&SIZES:
LAYOUT postprocessing:	Default Formats for Schematics
Select Aperture Table file	Default Formats for Penplotting
Update Aperture Table file	Default Formats for Photoplotting

Selected Aperture Table file: **LASER**

Return to MAIN MENU

All files generated in the design process are linked through the database integrator

A bewildering list of default parameters

All the files generated in the design process are linked together through the database integrator system. Thus when moving from schematic to PCB or back there is no question about the name of the file - this is all defined by the integrated system.

A competent graphics editor, with a keyword menu on the right hand side of the display, is used for all the various schematic, PCB and component editing. Operations are carried out through a hierarchy of such menus - which can make some operations a bit slow. But this is mitigated by a series of single keystroke short-cuts; for example traversing three menus can be achieved by pressing just three keys. Unfortunately, the chosen key letters appear to have little if any relevance to the function selected (r is the short cut for zoom), so it is something of an uphill struggle to learn the short cuts, though prompts are available on each menu.

A crucial measure of graphic editors for PCBs is how fast they can redraw. I tested the software on a 33MHz 486 machine but found that even a small PCB of five ICs was taking about a second to redraw with the full representation of the tracks - though when switched to single line representation the redraw was acceptably fast.

Throughout operation, sound is brought into play - and it is terrible! A beep might be expected to indicate an error, but the package insists on beeping and burbling during normal operation and I could not find any way to turn it off.

**Design rule check**

EE Designer's comprehensive design rule check system operates either manually or automatically. In manual mode, the user selects two items, and the program displays the clearance; no remedial action is taken.

The automatic design rule checker allows checking of the whole board, or indeed just a window of the board. Errors spotted during the design rule check are written on the PCB layout directly.

Distances defining the minimum clearances are defined by a separate menu, allowing definition of track to track

**SPECIFICATIONS**

- Schematic:**
- Sheet size to 64in x 64in
  - Up to 100 sheets
  - Up to 1500 components
  - Real time dragging of parts
  - Automatic bus increment
- PCB layout:**
- 32in x 32in maximum board size on 0.001in grid.
  - 32 user definable track widths
  - 64 user definable pad sizes
  - curved track routing and fills
  - Automatic via insertion
  - 12 routing layers
  - Track repeat
  - Electrical conductivity checking

(referred to in the US as trace to trace), track to pad, pad to pad and via clearances.

### Unusual features

Two unusual features are the package's communication and simulation. Communication is to some extent over the top! The idea is that files generated by *EE Designer* can be sent via a modem to specialist photoplot houses. But re-inventing the modem communications wheel is only helpful if you do not already have a proper modem and file transfer software.

For simulation, the package can be supplied with mixed mode simulation, advanced shove and sweep autorouter and thermal analysis, with interfaces to *PSpice* and *Autocad* via DXF – though my review copy had none of these features.

### Fighting the system

Lack of a proper library data base and manager is a real weakness and using the dos filing system is a very inefficient way to store this type of data.

But overall, all the functionality is there – if you are prepared to fight the system. Unfortunately, the signposts in the manual needed to unravel operation are chaotic making learning more of a struggle than it should be, and productivity in the early stages will remain low. The short-cut single key strokes and excellent autorouter should eventually reap benefits. But despite claims in the sales literature, the package can hardly be described as friendly, and there is no help let alone a modern context sensitive scheme.

There is integration between component parts, and the package's ability to integrate mixed mode simulation as well as thermal predictions distinguishes it from its competitors. None the less I tested only the PCB schematic capture and layout facilities and found them no better than lower priced products and typically more tedious to use.

### INSTALLATION AND DOCUMENTATION

Installation is something of a drawn out affair with the install routine unpacking files and creating directories. Component libraries are stored on hard disc as thousands of little files creating a severe problem. Each file comprises only a few hundred bytes, but on hard disc this is rounded up to the nearest cluster of say 2K. Result is that *EE Designer* eats disc space in a big way, with 3.5Mbytes for the programs and a further 7Mbytes for three (of the ten or so) libraries that I loaded. Be warned, during the installation process, *EE Designer* fiddles with your CONFIG.SYS file.

The software comes with five spiral bound manuals and a parallel port dongle. The Libraries manual is a 200 page list of the components supported - very impressive. A supplemental manual describes the changes of the various releases and details the database formats and primitives.

Of all the manuals, only the Users Guide has an index, and bearing in mind the complexity of the system, this is not helpful for the new user.

One small example PCB is supplied, and this did not really test the system, though all aspects of the example were described in the tutorial manual.

Absence of a context-sensitive help system makes learning a slow task.

### SUPPLIER DETAILS

*EE Designer Standard* (as reviewed) £995. From Betronex Ltd, 1 Wells Yard, High Street, Ware SG12 9AS. Tel: 0920 469131

Top of the range is *EE Designer Elite* at £3990, offering mixed mode simulation, shove and sweep autorouter, thermal analysis interface to *PSpice*

Is it a fully integrated electronic design system? Hardly design, but reasonably competent for PCB layout, with the promise of upgrades for logic and analogue simulation using the same captured data. ■

## HALCYON ELECTRONICS

Test equipment, video monitors, amateur radio gear, printers, power supplies, communications, disk drives, multimeters, oscilloscopes, scientific instruments, connectors, component bridges, frequency counters, signal generators, computers.

BECKMAN 9020 20MHZ DUAL TRACE	£249	OERTLING V20 SINGLE PAN BALANCES 300GM	£95
CROTECH 3030 1 TRACE 15MHZ COMP TESTER	£99	MAGNIFYING BENCH LAMPS	From £25
DATA PRECISION 6000 WITH 611 PLUG-IN AND 681 DISK DRIVE UNIT	£3995	RHOIDE & SCHWARZ PZM PHASE METER	£125
GOULD OS3000A 40MHZ 2 TRACE, DEL T/B	£249	R&S SDR UHF SIG GEN 290-1020MHz	£175
HAMEG 203-5 20MHZ, 2 TRACE, COMP TESTER	£199	WIRELESS WORLD CIRCARDS SER 1-25 cased	£49
HAMEG 203 20MHZ DUAL TRACE	£199	SAGE 2-WAY CO-AX SWITCH SAN 2120 4 CONNS	£95
HITACHI VC 6015 10MHZ DIGITAL STORAGE	£395	UDI 2026 SONAR SCANNER, SURFACE UNIT	£895
HITACHI V422 40MHZ DUAL TRACE	£295	B&K 1013 BF0 & 2305 LEVEL RECORDER	£195
H.P. 1340A X-Y DISPLAYS	£99	JPA CAVIDERM CD6 P.T.H. TESTER	£750
LEADER LBO-9C ALIGNMENT SCOPE	£195	GOULD BRUSH 260 6-PEN CHART RECORDER	£95
PHILIPS PM3400 SAMPLING SCOPE	£125	CANON ZOOM LENS C-MOUNT V6x17 17-102mm	£95
TEK 5L4N 100KHZ SPECT ANAL WITH 5110 M/F 2x 5A18N 5B10N TIME BASE	£750	SONY HVC2010P COLOUR CAMERA	£95
TELEQUIPMENT D75 50MHZ 2 TRACE DEL T/B	£225	MARCONI MARINE KESTREL 3	POA
TELEQUIPMENT D83 50MHZ 2 TRACE DEL T/B	£249	LOGIC ANALYSERS,VARIOUS	From £45 to £95
TEKTRONIX 7403N, DF1,7D01 LOGIC ANAL	£495	AVO C2457/5 LCR COMPONENT COMPARATOR	£75
		ANALYTICAL BALANCES WITH WEIGHTS	£69
		LIGHT BOXES 230V 10x12" area	£49

### SUMMER CLEARANCE

MANY UNLISTED ITEMS AT GREATLY REDUCED PRICES FOR CALLERS ONLY

TEK 545B, 585, 535A, 541A etc	From £49	DECADE R/CV BOXES	From £15
TEK 545/585 SERIES PLUG-INS	From £10	KAYE DEE PNEUMO UV EXP UNIT 390x260mm	£175
CONSTANT VOLTAGE TRANSF'S 150VA-2KV	POA	VACUUM PUMPS TYP 100MBAR (28L/MIN)	£95
IBM POLAROID PALETTE, CGA	£195	CALIBRATION STANDARDS CAVILR	POA
COMMUNICATIONS RECEIVERS, VARIOUS	POA	COSSOR CRM533A VHF NAV/COM RF SIG GEN	£750
VALRADIO PCB230/200 50Hz to 60Hz 200W	£95	COSSOR CRM511 ILS/VCR AUDIO SIG GEN	£750
WANDAL/GOLTERMAN SPM-2 SEL LEVEL METER	£169	TOPAZ 91007-11 7.5KVA 120/240-120/240 ISOL	£249
GAUGE BLOCKS (SLIP GAUGES) VARIOUS	From £5	KINGSHILL NS1540 15V 40A PSU CASED	£295
MARCONI TF2331 DISTN FACTOR METER	£175	MARCONI TF2303 AM/FM MOD METER £20MHZ	£245
BBC-B & MASTER COMPUTERS	From £99	ROBIN 4112 PHASE EARTH LOOP TESTER	£75
MARCONI TF2300 FM/AM MODULATION METER	£195	ROBIN 5402 DIGITAL RCC8 (ELCB) TESTER	£75
TEKTRONIX 834 PROG DATA/COMMS TESTER	£395	MARCONI TF2330 WAVE ANALYSER	£150
VARIABLE OUTPUT PSU'S HV & LV	From £29	HP 618C, 626A, 628A SIG GENS	£35 ea
TEKTRONIX 520 521A PAL VSCOPES	From £475	SIGNAL GENERATORS AF TO 21GHz	From £15

LIST AVAILABLE, BUT 1000'S OF UNLISTED BARGAINS FOR CALLERS  
QUALITY ELECTRONIC EQUIPMENT BOUGHT. ALL PRICES EXC. OF P&P AND VAT

423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR  
SHOP HOURS 9-5.30 MON-SAT. TEL 081-542 6383.

CIRCLE NO. 116 ON REPLY CARD

## ALL-MODE WIDE-BAND IC-R7100 RECEIVER



### THE IC-R7100 FEATURES:

- 25 to 2000 MHz continuous coverage allowing you to receive VHF, UHF, amateur, marine, CB, utility bands, FM and TV broadcasts
- All-mode capability.
- 900 memory channels in 9 banks
- 20 Scan edge memory channels.
- Dual scan with over 40 combinations
- High sensitivity and reliable frequency stability
- 0.1, 1, 5, 10, 12.5, 20, 25, 100 kHz and 1 MHz tuning steps available
- Built-in 24-hour system clock with 5 ON/OFF timers.
- Effective 20dB attenuator for strong signals.
- Automatic recording so important programmes can be caught when away from receiver.
- Dial lock function.
- Noise blanker circuit for eliminating pulse noise.
- Noise squelch and S-meter squelch.
- Ct-V system for computer control through an optional CT-17
- Frequency announcement in English with an optional UT-36.
- Large function display with selectable LCD backlighting brightness.
- Easy-to-read S-meter plus FM centre indicators.
- AC and DC power operation

**ICOM** Post to: Icom (UK) Ltd. Dept WW  
Sea Street Herne Bay Kent CT6 8LD  
Tel: 0227 741741 (24hr). Fax: 0227 360155

Name/address/postcode .....

Call sign: ..... Tel: ..... Dept: WW

CIRCLE NO. 117 ON REPLY CARD

**SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK**

Tektronix 475 - 200Mc/s oscilloscopes - tested from £400 less attachments to £500 C/W manual probes  
 Marconi TF2008 - AM-FM signal generator - Also sweeper - 10Kc/s - 510Mc/s - from £350 tested to £500 as new with manual - probe kit in wooden carrying box.  
 HP DC Current source type 6177C - £200.  
 HP Frequency comb generator type 8406A - £400.  
 HP Sampling Voltmeter (Broadband) type 3406A - £200.  
 HP Vector Voltmeter type 8405A - £400 to £600.  
 HP Synthesiser/signal generator type 8672A - 2 to 18GHz S old or new colour £4000.  
 HP Oscillographic recorder type 7404A - 4 track - £350.  
 HP Plotter type 9872B - 4 pen - £300.  
 HP Sweep Oscillators type 8690 A & B + plug-ins from 10Mc/s to 18GHz also 18-40GHz. P.O.R.  
 HP Signal Generators type 612 - 614 - 618 - 620 - 628 - frequency from 450Mc/s to 21GHz.  
 HP Network Analyser type 8407A + 8412A + 8601A - 100Kc/s - 110Mc/s - £500-£1000.  
 HP 432A-435A or B Power Meters + Powerheads - 10Mc/s-40GHz - £200-£650.  
 HP Down Converter type 11710B - 0.1-11Mc/s - £450  
 HP Pulse Modulator type 11720A - 2-18GHz - £1000  
 HP Modulator type 8403A - £100-£200.  
 HP Pin Modulators for above many different frequencies - £150.  
 HP Counter type 5342A - 18GHz - LED readout - £1500.  
 HP Signal Generator type 8640B - Opt001 + 003 - 5-512Mc/s AM/FM - £1200.  
 HP Spectrum Display type 3720A £200 - HP Correalator type 3721A £150.  
 HP 37555 + 3756A - 90Mc/s Switch - £500.  
 HP Amplifier type 8447A - 1-400Mc/s £400 - HP8447F 1-1300Mc/s £800.  
 HP Frequency Counter type 5340A - 18GHz £1000 - rear output £800.  
 HP 8410 - A - B - C Network Analyser 110Mc/s to 12GHz or 18GHz - plus most other units and displays used in this set-up - 8411A - 8412 - 8413 - 8414 - 8418 - 8740 - 8741 - 8742 - 8743 - 8746 - 8650. From £1000.  
 HP Signal Generator type 8660C - 1-2600Mc/s. AM/FM - £3000. 1300Mc/s £2000  
 HP Signal Generator type 8656A - 0.1-990Mc/s. AM/FM - £2250  
 HP 3730B Mainframe £200  
 HP 8699B Sweep Pl - 0.1-4GHz £750 - HP8690B Mainframe £250.  
 HP Digital Voltmeter type 3456A - £900.  
 Racal/Dana digital multimeter type 5001 - £250.  
 Racal/Dana Interface type 9932 - £150.  
 Racal/Dana GPIB Interface type 9934A - £100.  
 Racal/Dana 9301A-9303 RF Millivoltmeter - 1.5-2GHz - £350-£750.  
 Racal/Dana Counters 9915M - 9916 - 9917 - 9921 - £150 to £450. Fitted FX standards.  
 Racal/Dana Modulation Meter type 9009 - 8Mc/s - 1.5GHz - £250  
 Racal - SG Brown Comprehensive Headset Tester (with artificial head) Z12A00/1 - £450.  
 EIN 310L. RF Power Amp - 250KHz - 110Mc/s - 50Db - £250.  
 Marconi AF Power Meter type 893B - £300.  
 Marconi Bridge type TF2700 - £150.  
 Marconi/Saunders Signal Sources type - 6058B - 6070A - 6055B - 6059A - 6057B - 6056 - P.O.R. 400Mc/s to 18GHz.  
 Marconi TF1245 Circuit magnification meter + 1246 & 1247 Oscillators - £100-£300  
 Marconi microwave 6600A sweep osc. mainframe with 6650 PI - 18-26 5GHz or 6651 PI - 26 5-40GHz - £1000 or PI only £600  
 Marconi distortion meter type TF2331 - £150. TF2331A - £200.  
 Thurlby converter 19 - GP - IEEE - 488 - £150  
 Philips logic multimeter type PM2544 - £100  
 Microwave Systems MOS/3600 Microwave frequency stabilizer - 1 to 18GHz & 18 to 40GHz - £1000  
 Bradley Oscilloscope calibrator type 156 - £150  
 Tektronix Plug-Ins 7A13 - 7A14 - 7A18 - 7A24 - 7A26 - 7A11 - 7M11 - 7S11 - 7D10 - 7S12 - S1 - S2 - S6 - S52 - SC504 - SC502 - SG502 - SG503 - SG504 - DC503 - DC508 - DD501 - WR501 - DM501A - FG501A - TG501 - PG502 - DC505A - FG504 - P.O.R.  
 Ailtech Stoddart receiver type 1727A - 0.1-32Mc/s - £2500  
 Ailtech Stoddart receiver type 3757 - 30-1000Mc/s - £2500  
 Ailtech Stoddart receiver type NM65T - 1 to 10GHz - £1500.  
 Gould J3B Test oscillator - manual - £200.  
 Image Intensifiers - ex MOD - tripod fitting for long range night viewing - as new - £1500-£2000.  
 Don 10 Telephone Cable - 1/2 mile canvas containers or wooden drum - new - Mk2-3 or 4.  
 Infra-red Binoculars in fibre-glass carrying case - tested - £100. Infra-red AFV sights £100  
 ACL Field intensity meter receiver type SR - 209 - 6. Plugs-ins from 5Mc/s to 4GHz - P.O.R.  
 Syston Donner Counter Model 6057 - 18GHz - £800.  
 Tektronix 491 spectrum analyser - 1.5GHz-40GHz - as new - £1200 or 10Mc/s 40GHz  
 Tektronix Mainframes - 7603 - 7623A - 7633 - 7704A - 7844 - 7904 - TM501 - TM503 - TM506 - 7904 - 7834 - 7104.  
 Knott Polyskanner WM1001 + WM5001 + WM3002 + WM4001 - £500  
 Ailtech 136 Precision test RX + 13505 head 2 - 4GHz - £350.  
 SE Lab Eight Four - FM 4 Channel recorder - £200.  
 Ailtech 757 Spectrum Analyser - 001 22GHz - Digital Storage + Readout - £5000  
 Dranetz 606 Power line disturbance analyser - £250.  
 Precision Aneroid barometers - 900-1050Mb - mechanical digit readout with electronic indicator - battery powered. Housed in polished wood carrying box - tested - £100-£200-£250. 1, 2 or 3  
 B & K Sound Level Meter type 2206 - small - lightweight - precision - 1/2" microphone - in foam protected filled brief type carrying case with windshield & battery + books + pistol grip handle - tested - £170. Carr. £8 - B & K 2206 Meter + Mike + Book - less carrying case etc. - £145. Carr. £8.  
**DISCOUNT ON QUANTITY**  
 HP 141T Spectrum Analysers. All new colours supplied with instruction manuals.  
 HP 141T-8552B - 8556A - 20Hz to 300KHz. £2000.  
 HP 141T-8552B - 8553B - 1kHz to 110Mc/s. £1750.  
 HP 141T-8552B - 8554B - 100kHz to 1250Mc/s. £2250.  
 HP 141T-8552B - 8555A - 10Mc/s to 18GHz. £3000.  
 HP 141T - old colour mainframe + 8552A, 8553B - 1kHz to 110Mc/s. Instruction manuals - £1250 or 8552B £1500.  
 HP 3580A LF-spectrum analyser - 5kHz to 50kHz - LED readout - digital storage - £1600 with instruction manual - internal rechargeable battery.  
 Spectrascope 11 SD335 (S.A.) realtime LF analyser - 20Hz to 50kHz - LED readout with manual - £500 tested.  
 Tektronix 7D20 plug-in 2-channel programmable digitizer - 70 Mc/s - for 7000 mainframes - £500 - manual - £50.  
 Datron 1065 Auto Cal digital multimeter with instruction manual - £500.  
 Racal MA 259 FX standard. Output 100Kc/s-1Mc/s-5Mc/s - internal NiCad battery - £150.  
 Tektronix TR503 tracking generator - 10Mc/s to 1800Mc/s + manual - £1500.  
 Aerial array on metal plate 9" x 9" containing 4 aeriels plus Narda detector - 100-11GHz. Using N type and SMA plugs & sockets - ex eqpt - £100.  
 EIP 451 microwave pulse counter 18GHz - £1500.  
 Marconi RF Power Amplifier TF2175 - 1.5Mc/s to 520Mc/s with book - £100.  
 HP 8614A Signal Generator 800Mc/s to 2.4GHz - old colour - £300. New colour - £600.  
 HP 8616A Signal Generator 1.8GHz to 4.5GHz - old colour - £200. New colour - £400.  
 HP 8620A or 8620C Sweep Generators - £400 or £900.  
 Marconi 6155A Signal Source - 1 to 2 GHz - LED readout - £600  
 Schiumberger 2741 Programmable Microwave Counter - 10Hz to 7.1GHz - £750.  
 Schiumberger 2720 Programmable Universal Counter 0 to 1250Mc/s - £600.  
 HP 37203A HP-IB Extender - £150.  
 PPM 411F Current Reference - £150.

HP 5363B Time Interval Probes - £150.  
 HP 8900B Peak Power Calibrator - £100.  
 HP 59313A A/D Converter - £150.  
 HP 59306A Relay Actuator - £150.  
 HP 2225CR Thinkjet Printer - £100.  
 TEK 178 Linear IC Test Fixture - £150.  
 TEK 576 Calibration Fixture - 067-0597-99 - £250  
 HP 4437A 600 Ohm Attenuator - £100.  
 HP 8006A Word Generator - £150  
 HP 1645A Data Error Analyser - £150.  
 Texscan Rotary Attenuators - BNC/SMA 0-10-60-100DBS - £50-£150  
 HP 809C Slotted Line Carriages - various frequencies to 18GHz - £100 to £300.  
 HP 532-536-537 Frequency Meters - various frequencies - £150-£250.  
 HP 3200B VHF Oscillator - 10Mc/s-5000Mc/s - £200.  
 Barr & Stroud variable filter EF3 0.1Hz-100Kc/s + high pass + low pass - mains - battery - £150  
 Krohn-Hite Model 3202R filter - low pass. high pass.  
 Krohn-Hite 4100 oscillator.  
 Krohn-Hite 4141R oscillator - .1Hz-10,000KHz  
 Krohn-Hite 6880 programmable distortion ANZ-IEEE-488.  
 Krohn-Hite 3750 filter. low pass, high pass - 0.2Hz-20KHz.  
 Parametron D150 variable active filter. low pass - high pass - 1.5Hz-10KHz. £100  
 S.E. Lab SM215 Mk11 transfer standard voltmeter - 1000 volts.  
 Fluke 4210A programmable voltage source.  
 Ailtech Stoddart P7 programmer - £200  
 Fluke 8500A digital multimeter  
 H.P. 3490A multimeter  
 H.P. 6941B multiprogrammer extender £100.  
 Fluke Y2000 RTD selector + Fluke 1120A IEEE-488-translator + Fluke 2180 RTD digital thermometer + 9 probes. £350 all three items.  
 H.P. 6181 DC current source. £150  
 H.P. 59501A - HP-IB isolated D/A power supply programmer.  
 H.P. 3438A digital multimeter.  
 H.P. 61775 DC current source.  
 H.P. 6207B DC power supply.  
 H.P. 741B AC/DC differential voltmeter standard (old colour) £100.  
 H.P. 6209B DC power unit.  
 Fluke 80 high voltage divider.  
 Fluke 887AB AC - DC differential voltmeter.  
 Fluke 431C high voltage DC supply.  
 H.P. 1104A trigger countdown unit  
 Tektronix M2 gated delay calibration fixture. 067-0712-00  
 Tektronix precision DC divider calibration fixture. 067-0503-00.  
 Tektronix overdrive recovery calibration fixture. 067-0608-00.  
 Avo VCM163 valve tester + book £300  
 H.P. 5011T logic trouble shooting kit. £150  
 Marconi TF2163S attenuator - 1GHz. £200.  
 PPM 8000 programmable scanner.  
 H.P. 9133 disk drive + 7907A + 9121 twin disk.  
 Fluke 730A DC transfer standard.  
 B&K level recorder 2307 - £500  
 B&K 2113 audio frequency spectrometer - £150  
 B&K 4815 calibrator head.  
 B&K 4812 calibrator head.  
 B&K 4142 microphone calibrator - £100.  
 B&K 1022 band FX oscillator - £100.  
 B&K 1612 band pass filter set - £150  
 B&K 2127 frequency analyser - £150.  
 B&K 1013 BFO - £100  
 B&K 1014 BFO - £150  
 B&K 4712 FX response tracer - £250.  
 B&K 2603 microphone amp - £150  
 B&K 2604 microphone amp - £200  
 B&K 2019 analyser - £350  
 Farnell power unit H60/50 - £400 tested.  
 H.P. FX doubler 938A, also 940A - £300.  
 Racal/Dana 9300 RMS voltmeter - £250  
 A.B. noise figure meter 117B - £400  
 Ailtech 360D11 + 3601 + 3602 FX synthesizer 1Mc/s-2000Mc/s. £500.  
 H.P. sweeper plug-ins - 86240A - 2-8.4GHz - 86260A - 12-4-18GHz - 86260AH03 - 10-15GHz - 86290B - 2-18.6GHz. 86245A 5.9-12.4GHz.  
 Tequipment CT171 curve tracer - £200  
 H.P. 461A amplifier - 1kc-150Mc/s - old colour - £100  
 H.P. 8750A storage normalizer.  
 Tektronix oscilloscopes type 2215A - 60Mc/s - c/w book & probe - £400  
 Tektronix monitor type 604 - £100  
 Wiltron 560 network scaler + 2 heads + book - £1000.  
 Marconi TF2330 or TF2330A wave analysers - £100-£150.  
 HP5006A Signature Analyser £250 + book.  
 HP10783A numeric display. £150.  
 HP239A oscillator - £250.  
 Ailtech 7009 hot-cold standard noise generator.  
 HP 3763A error detector. £250  
 Cushman CE-15 spectrum analyser - LED Readout - 1000Mc/s £650.  
 Tektronix 5L4N spectrum analyser - 0-100Kc/s £500.  
 HP1742A 100Mc/s oscilloscope. £250.  
 HP1741A 100Mc/s oscilloscope. £250.  
 Tektronix 7104-7A29-7A24-7B15-7B10 - £2K.  
 Racal/Dana signal generator 9082 - 1.5-520Mc/s - £800.  
 Racal/Dana signal generator 9082H - 1.5-520Mc/s - £900.  
 Claude Lyons Compuline - line condition monitor - in case - LMP1 + LCM1 £500.  
 HP1815B T.D.R. sampler + 1817A head - 1104A trigger + 1106B TD mount £500  
 Texscan AL-51A spectrum analyser - 4-1000Mc/s - £750.  
 Efratom Atomic FX standard FRT - FRK - 1-1-5-10Mc/s £3K.  
 Muirhead fax receivers K649 - TR4 - solid state - speed - 60-90-120-240 - auto - IC 288-576 - auto. £250 with book.  
 Racal 4D recorder - £350.  
 HP8350A sweep oscilloscope mainframe + HP11869A RF Pi adaptor - £2.5K.  
 Ailtech - precision automatic noise figure indicator type 75 - £250.  
 Adret FX synthesizer 2230A - 1Mc/s. £250.  
 Tektronix - 7S12-7S14-7T11-7S11-S1-S52-S53  
 Rotek 610 AC/DC calibrator. £2K + book.  
 Tektronix 7L12 analyser - 1Mc/s-1.8GHz. £1500.  
 Clark Scam Heavy Duty 40' Telescopic Pneumatic Masts - retracted 7'8" - head load 40lbs - with or without supporting legs & erection kit - in bag + handbook - £200-£500  
 Clark Scam Heavy Duty 70' Telescopic Pneumatic Masts - retracted 13'5" - head load 90lbs - with or without legs + erection kit + handbook - £500-£800.

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. S.A.E. FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS. AVAILABILITY OR PRICE CHANGE. VAT AND CARR., EXTRA.

Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. No. (0274) 684007. Fax 651160.

CIRCLE NO. 118 ON REPLY CARD

Early VHF television transmissions in the UK used separate antennas for vision and sound channels. But today all UK television stations combine at least two vision and sound channels into a single antenna. At most stations the transmission authorities cooperate to combine all four local channels. Similarly, at least three FM channels are combined into most of the FM broadcasting antennas in the UK.

At the heart of most of these channel combiners is a pair of hybrids.

The illustration shows part of A Band 2 combiner which has been manufactured by Alan Dick & Co Ltd to combine five 20kW FM channels. The hybrid shown in the foreground has 6.125in IEC ports and a body diameter of 15in (381mm) to deal with high peak voltage and output power.

We have already seen (Split personality of hybrid directional couplers, *EW + WW*, July, pp. 556-559) how some radio-frequency hybrids are able to split power, reasonably equally, between two output loads over a wide frequency range while maintaining a very well matched input impedance. The same hybrids are also capable of combining two phase-locked signals into a single output load – provided that the relative phases applied to their input terminals are taken into account.

Hybrids can also be used to form two-channel-combining networks if the two channels are within the working band of the hybrid (Fig. 1). Here we will consider only the "3dB" hybrid which (see July article) is formed when a quarter-wavelength of a pair of parallel transmission lines are coupled in a particular way. The physical and corresponding symbolic arrangements, showing the phase differences between ports, are illustrated in Fig. 1. Power entering at *A* is split equally between *B* (phase lag  $90^\circ$ ) and *C* (no phase lag); no power reaches *D*. Similarly, power entering *D* is split equally between *B* (no phase lag) and *C* (phase lag  $90^\circ$ ); notice that in the latter case

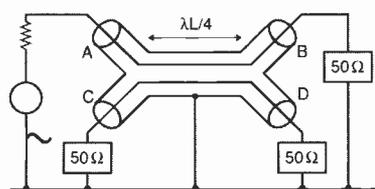


Fig. 1. 3dB coupler hybrid and its symbol showing phase relationships.

# Hybrids at the heart of radio-frequency combiners

**Several VHF or UHF broadcasting channels can be transmitted simultaneously from a single antenna. Dick Manton explains the combining role of hybrids.**

the phase relationship between *B* and *C* has been reversed.

## Channel combiners with no resonators

One type of channel combiner that is widely used at low-power television transmitting stations in the UK makes use of the *B* and *C* phase reversal, when either *A* or *D* is used as the input port.

The combiner consists (Fig. 2) of two hybrids connected back-to-back by two unequal lengths of coaxial transmission line. If  $f_1$  and  $f_2$  are the two input frequencies in MHz, the two transmission lines (velocity factor  $v$ ) have to differ by a length  $d$ , in m, equal to  $150v/(f_2 - f_1)$ . If the difference in electrical path lengths at  $f_1$  is  $n$  wavelengths, the difference at  $f_2$  is then  $n+0.5$  wavelengths. By tracing out electrical path lengths for  $f_1$  and  $f_2$  in Fig. 2, we can see that  $f_1$  and  $f_2$  both combine in phase when they reach port *D* of the second hybrid and cancel out at the load on port *A*.

Other frequencies apportion themselves between *A* and *D*, with a result that the input impedance remains constant with frequency. There are two other major advantages with this type of combiner: the combiner contains no resonators, so there is no voltage or current magnification at any point in the circuit and there is a constant group delay (linear phase change with frequency) across each input band.

Also, the frequency of any 3rd-order intermodulation product such as  $2f_2 - f_1$ , which may be generated in the  $f_2$  transmitter, is such that it is absorbed in the load *A* on the second hybrid.

Where four channels at the same transmitting site are reasonably spaced it is usually possible to combine them by means of three units similar to those shown in Fig. 2. Frequencies  $f_1$  and  $f_3$  are combined in one unit and  $f_2$  and  $f_4$  in another. Both pairs of channels are then fed to the input ports of a third unit

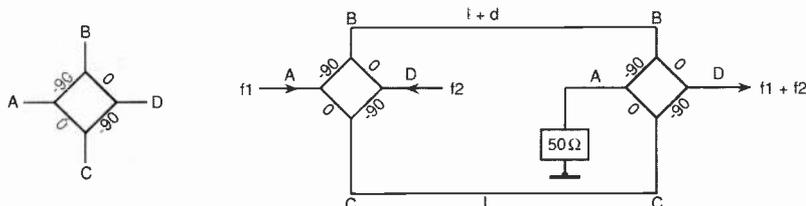


Fig. 2. Multichannel combiner using two hybrids and unequal lengths of interconnecting feeders, widely used at low-power television transmitting stations.

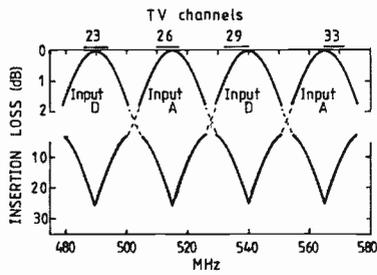


Fig. 3. Insertion loss characteristics of the combiner shown in Fig. 2, designed to combine two pairs of television channels. ( $d = 3.9\text{m}$ ; velocity factor of feeder = 0.67)

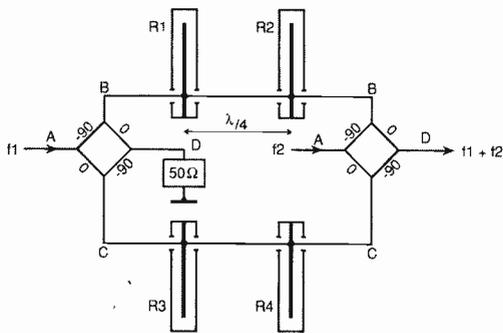


Fig. 4. A narrow-band/wide-band combiner.  $R_1, R_2, R_3$  and  $R_4$  are  $f_1$  bandpass resonators. The  $f_1$  input is narrow-band and the  $f_2$  input is wide-band.

where  $d$  is a compromise for establishing suitable phase differences between paths – path lengths at alternative frequencies must differ as closely as possible by a half-wavelength.

At a UK television station, where channels with mid-band frequencies of 490MHz, 514MHz, 538MHz and 570MHz have to be combined, suitable feeder length differences  $d$  (when  $v = 0.67$ ) for 490MHz and 538MHz would be 2.1mm; 514MHz and 570MHz require 1.8m and the four-channel combiner requires 3.9m. Through-loss characteristics of the final four-channel combiner for these frequencies demonstrate (Fig. 3) that though the bandwidths of all channels are the same, they are slightly displaced relative to the desired centre frequencies because of the irregular channel spacing. All losses between input ports are dependent on the construction of the

hybrids, but they will normally be in excess of 25dB. (Some bandpass filters in the outputs of the transmitters may be needed to keep intermodulation products down to an acceptable level.)

**Channel combiners with resonators**

Another type of channel combiner employs back-to-back hybrids, but uses resonators to provide frequency-dependent paths.

In Fig. 4,  $R_1, R_2, R_3$  and  $R_4$  are resonators attached in pairs one quarter-wavelength apart along the equal interconnecting coaxial lines between the hybrids.

The resonators are band-pass circuits, designed so that they resonate at frequency  $f_1$  and so allow free access along the interconnecting lines only at that frequency. Power at frequency  $f_1$  which enters port A of the first hybrid, splits then recombines at port D of the second hybrid. Because the loaded  $Q_L$  of each resonator is relatively high (typically 100 for an FM combiner) each resonator creates a near short-circuit (ie approx 100% 180° voltage reflection) across the line for frequencies far removed from  $f_1$ . As a consequence, any power at these frequencies entering port A of the second hybrid emerges at B and C, where it is 100% reflected and also recombines at output port D. By symmetry, any frequency other than  $f_1$ , such as an intermodulation product, entering port A of the first hybrid will be transferred to the resistive load on port D of the first hybrid. The result is that matched input impedances are again seen at all frequencies.

Cross-loss between input ports at frequency  $f_1$  is determined by the balance of the hybrids, and is typically better than 30dB. At other frequencies the cross-loss is supplemented by the very high susceptance of the resonators.

Figure 5 shows the through-loss characteristics of this type of channel combiner using four resonators, each with  $Q_U = 10,000$  and  $Q_L = 100$ . The  $Q_L$ s of the resonators in each arm determine the shape of both the narrow-band and wide-band input characteristics, while the  $Q_U$ s determine the absolute levels of losses. As stated earlier, the use of resonators leads to a sloping group-delay curve – noticeable on both the narrow-band channel and on the wide-band channel close to the frequency of the narrow-band signal. Broadcasting authorities sometimes impose tight restrictions

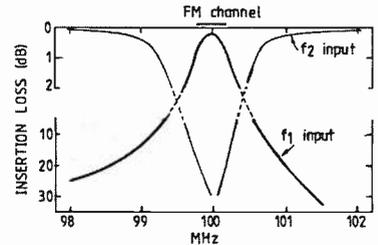


Fig. 5. Insertion loss characteristics of the combiner shown in Fig. 2 when it is designed to combine a 100MHz FM channel with several others. (Each resonator has  $Q_U = 10,000$  and  $Q_L = 100$ .)

on the change of group delay across a channel to preserve pulse shapes and colour information in TV, or integrity of subcarrier information on FM. It can be modified by increasing the number of resonators or by changing to different combinations of loaded  $Q$ s.

The usual mechanical layout of a 3dB coupler hybrid does not lend itself readily to a symmetrical combiner layout. But this disadvantage is easily overcome by arranging a 180° twist in the coupled lines or their end-connections within the casing of the hybrid (Fig. 6a). Several wide-band/narrow-band channel combiner units can be coupled in series to combine more than two channels (Fig. 6b). The maximum peak RF voltage in a combiner of this type is developed in the resonators closest to the last wide-band input port and is  $(1.1 \text{ to } 1.4)\sqrt{Q_L}$  multiplied by the peak RF voltage of the narrow-band input carrier – depending on the internal construction of the resonators – plus about twice the sum of the peak RF voltages of the remaining carriers. There are correspondingly high currents at the other end of each of the resonators. ■

In a future article Dick Manton will describe one further type of channel combiner, using ordinary directional couplers instead of hybrids. The device is probably more interesting from the point of view of power multiplication than for its practical use.

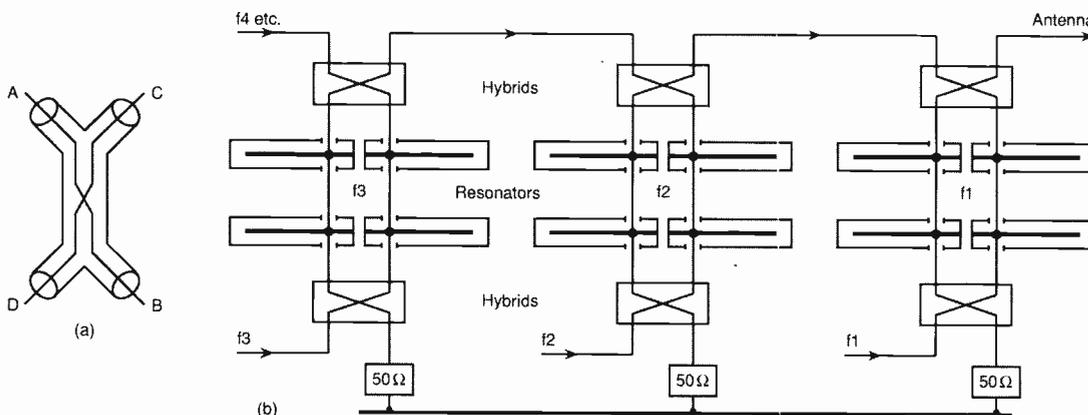


Fig. 6(a). Crossover 3dB coupler hybrid having symmetrically-disposed outputs on the same side of the coupler. (b) Multichannel FM combiner using crossover 3dB coupler hybrids and band-pass resonators.

# ALL VALVES AND TRANSISTORS

We are one of the largest stockists of valves etc in the U.K.

**CALL OR PHONE**

for a most courteous quotation.

**081 743 0899**

**COLOMOR ELECTRONICS LTD**

170, Goldhawk Road, London, W12 8HJ

**FAX 081-749 3934**

CIRCLE NO. 119 ON REPLY CARD

## MQP ELECTRONICS SYSTEM 200 UNIVERSAL DEVICE PROGRAMMING SYSTEM

- Fast and reliable programming
- Low cost
- Expandable system – buy only what you need
- Virtually all programmable devices covered
- Easy to upgrade
- Manufacturer approved algorithms
- Efficient and attractive software interface
- Special batch mode for production
- Not a plug-in card



System 200 is one of the most versatile programming systems available. At the heart of the system is the award-winning Model 200A programmer. Designed to quickly connect to the serial or parallel port of any PC compatible, the Model 200A is controlled by PROMDRIVER, widely acclaimed as the best driver software available for any programmer.

- EPROMs, EEPROMs and FLASH memories up to 8Mbit and beyond
- Microcontrollers from most manufacturers including
  - 8748 Family
  - 8751 Family (including 87C751/2 and 87C552)
  - Z8 Family
  - PIC16C5X Family
- Emulators
- 8-pin Serial EEPROMs
- PALs, GALs, EPLDs etc
- Bipolar PROMs

Write or phone today for Free Information Pack:  
Phone: (0666) 825146 Fax: (0666) 825141



MQP ELECTRONICS LTD,  
PARK ROAD CENTRE,  
MALMESBURY,  
WILTSHIRE SN16 0BX UK

European Distributors: Digitron, Norway Tel 071-17 890;  
Synatron, Germany Tel 089/4602071; Elexind, Italy Tel 02 92 10 35 54

CIRCLE NO. 120 ON REPLY CARD

## RADIO REMOTE CONTROL . . .



**. . . wherever and whenever it's needed**

Radio linking is the 1990's answer to the question of data transference and remote control . . . cutting out the need for fixed cables and direct connections. At Wood & Douglas we've developed this technology to a fine art with a range of compact, radio link modules capable of simple, highly efficient application across a wide spectrum of commercial and industrial uses. Where standard modules are not applicable we custom-build to precise requirements.

Over the past ten years we've successfully applied radio linking over such diverse areas as water leak detection, remote control of cranes and other industrial equipment, medical and veterinary monitoring, data logging, fuel and power control, automated warehousing . . . the list is endless.

In short, give us the problem . . . and we'll give you wireless control, wherever and whenever it's needed.



**WOOD & DOUGLAS**  
VHF UHF COMMUNICATIONS PRODUCTS

Lattice House, Baughurst, Basingstoke, Hampshire RG26 5LL England  
Telephone: 0734 811444. Fax: 0734 811567




CIRCLE NO. 121 ON REPLY CARD

# Are You Operating In The Dark?

**IMAGE PROCESSING** is the only European publication written specifically for image processing professionals - whatever the application.

- From medical imaging to remote sensing, industrial inspection to document imaging, **IMAGE PROCESSING** can brief you on advances in your area while giving a refreshing insight into the way imaging technology is being used in other disciplines throughout industry and science.
- Available at the special offer price of **£14.95** for five issues - a saving of over **£10** off the normal subscription price of **£25**.
- The special offer price is valid if subscriptions are returned within three weeks.

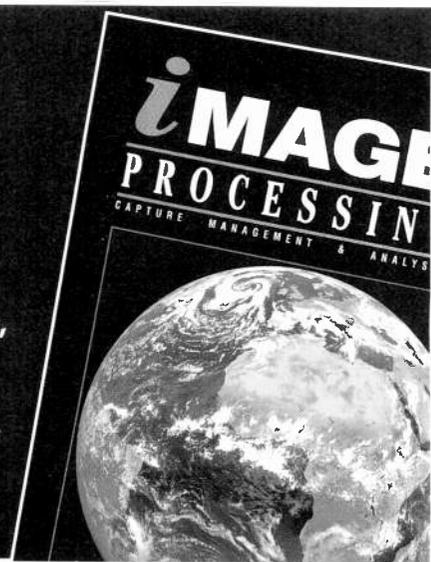**The only authoritative voice in the market**



**YES, I would like to take out a subscription to IMAGE PROCESSING at £14.95 for one year.(inc five issues)**

Please tick one box (either)

Please invoice my company for £14.95 OR  Please debit my credit card account by £14.95

Please indicate which credit card

Access  Visa  American Express  Diners Club

Please give credit card number

Expiry date

Signature

Date

Please tick here: if you do not wish to receive direct mail promotions from other companies

EW/O

NAME

JOB TITLE

COMPANY NAME

ADDRESS

POSTCODE

TEL NO

PLEASE RETURN TO: IMAGE PROCESSING SUBS DEPT, FREEPOST, ROOM H320, REED BUSINESS PUBLISHING, QUADRANT HOUSE, THE QUADRANT, SUTTON, SURREY SM2 5BR



CIRCLE NO. 123 ON REPLY CARD

## M & B RADIO (LEEDS)

THE NORTH'S LEADING USED TEST/EQUIPMENT DEALER

### GENERAL TEST EQUIPMENT

Amber 4400A Multipurpose Audio Test Set	£750
Datalab DL1080 Programmable Transient Recorder	£750
Genrad 1658 RLC Digibridge	£750
EMT422 Audio Threshold Monitor	£250
Systron Donner Dual PSU 0 to 40 volts 1 amp	£115
Schaffner NSG430 Static Discharge Simulator	£400
Woele ME104C Wow and Flutter Meter	£150
Telonic TSM2 Rho Meter	£600
Texscan CS76 460 to 960 Hz Sweep Generator	£350
Tektronix 521A PAL Vectorscopes	£1000
Tektronix 1485 Video Waveform Monitor	£500
HP 5340A 10 Hz to 18 GHz Freq Counter	£1000
HP 5345A Timer Counter	£350
HP 5381 80 MHz Freq Counter	£75
Iwatsu SC7104 1 GHz Freq Counter	£400
Tektronix DC508 1 GHz Counter	£500
Racal 9904M Counter Timer	£125
Racal 9908 1.1 GHz Freq Counter	£375
Racal 9009 Mod Meters	£300
Sayrosa 252 Automatic Mod Meter 2 GHz	£225
Bird 8201 Termaline 500 Watt	£150
Farnell Amm Auto Mod Meter	£250
Marconi 2950 RT Test Set	£400
HP 5306 GPIB Multimeter/Counter	£235
HP 3478A LCD Digital Multimeter	£450
HP 3455A Hi Stability Digital Voltmeter GPIB	£1450
HP 3400A True RMS Voltmeter	£145
HP 400E Voltmeters	£145
HP 461A Amplifiers	£100
HP 432A Power Meter with Mount	£495
Tektronix 576 Curve Tracer/172 Programmer	£1500
Rank Kalee 1742 Wow Flutter Meter	£195
RFL 5950A Crystal Impedance Meter	£150
HP 3556A Posphometer	£75
HP 8750A Storage Normalizer	£450
HP 6294A PSU 0 to 60 Volts 1 Amp	£100

HP 6453A PSU 0 to 15 Volts 200 Amps	£350
Racal Dana 211 Logic Analyser	£150
Racal/Dana Wide Band Level Meter 5002	£850
Racal/Dana True RMS RF Level Meter 9303	£850

### SIGNAL GENERATORS

Farnell SSG1000 10Hz to 1GHz synthesised	£1650
Farnell SSG2000 10Hz to 2GHz synthesised	£2500
Farnell SSG520 AM/FM signal generator	£650
Farnell TTS520 transmitter test set	£650
Farnell TTS1000 transmitter test set	£800
Marconi TF2015/2171 Synchronizer 10MHz to 520MHz AM/FM signal generator	£375
Marconi TF2015 signal generator	£200
Marconi TF2016 10Hz to 110MHz AM/FM	£150
Marconi TF2016A with rev' power trip	£200
Philips PM 5224 110MHz	£195
Philips PM4556 stereo generator	£150
Sound Technology 1000A stereo generator	£200
Radiometer SMG1 stereo generator	£100
RS SHF 4.8 to 12.6GHz signal generator	£850
Marconi TF2000 AF signal generator + mon' att'	£125

### RADIO EQUIPMENT

Racal RA1792 HF receivers	£2000
Racal MA1723 HF drive units	£1500
Plessey PR1553 receivers	£500
Philips 88MHz to 108MHz 10kW broadcast TX	£4500

### SPECTRUM ANALYSERS

HP 182T 8558B 1 to 1500 MHz (as new)	£2300
HP 141T Complete with 8554B 1250 MHz Analyser 8553B 1 kHz to 110 MHz Analyser and 8552B IF Section (as new condition)	£3000
HP 8555A 10MHz to 18GHz Analyser Plugin brand new	£3000
HP 8592A 50 KHz to 22 GHz Portable Analyser	£4500
HP 8406A Comb Generator	£500
HP 3582A Dynamic Signal Analyser	£4000

Marconi TF2371/1 110 MHz Spectrum Analyser	£1650
Wayne Kerr RA200 Audio Response Analyser	£450
Wayne Kerr 240A Audio Response Tracer	£195

### OSCILLOSCOPES

Tektronix 2455 250MHz four-trace portable	£1650
Tektronix 2445A 150MHz four-channel	£1500
Tektronix 5223 digitizing oscilloscope	£950
Nicolet 4094A digital oscilloscope	£1000
Farnell DTS12 digital storage oscilloscope	£300
Philips 3217 50MHz (as new)	£375
Philips 3244 50MHz four-trace	£300
Philips 3234 10MHz storage	£225
Philips 3232 10MHz true dual trace	£200
Gould OS300 20MHz dual trace	£185
Telequipment D83 50MHz	£200
Telequipment D755 50MHz dual trace	£250
HP 1703A storage oscilloscope	£195
HP 1727A 275MHz storage oscilloscope	£450
Tektronix 647 100MHz dual trace	£100
Tektronix T922R rack mounting	£225
Cossor CDU 150 35MHz dual trace	£125

### SPECIAL OFFERS

AVO 8 multimeters (Testset No.1) inc. case and leads	£25
Radiometer SMG1 stereo generators	£100
Clare V158 electrical safety testers	£125
Ferrograph RTS2 tape recorder testset	£125
Farnell TOPS1 PSU	£95
Lyons PG73A pulse generators	£75
Philips PM2521 automatic multimeters	£145
Farnell C2 power supplies 0 to 30 volts 2 amps dual	£95
Tektronix DM501 DVM+TM501 frame	£150
Telequipment DM63 50MHz 4-trace storage oscilloscope	£195

ALL PRICES PLUS VAT AND CARRIAGE

**86 Bishopgate Street, Leeds LS1 4BB**  
**Tel: 0532 435649 Fax: (0532) 426881**

CIRCLE NO. 139 ON REPLY CARD

## Distorted logic

Having followed recent debates on crossover distortion (*EW + WW*, October 1990 and *EW + WW*, Letters, April 1992) I have become perturbed that Mr McLoughlin has devoted so much energy in attempting to solve a non-problem in such an unpromising way. It has been taken as fact that the best way to design a good amplifier is to make it as linear as possible before applying feedback. Admittedly this is rather easier said than done. But McLoughlin has deliberately introduced discontinuity into input/output characteristics, and negative feedback is not very good at coping with such defects.

Thermal runaway in power amplifiers has been almost unheard of since silicon power transistors became established and it is quite wrong to portray average amplifiers as balancing on the edge of thermal doom. Quiescent current is a critical parameter in usual class B amplifiers, but it can be set in a second or two by using a distortion analyser and letting crossover spikes sink placidly into residuals. Even with good thermal feedback to an amplified diode, compensation for level and hence dissipation changes

is only approximate. It is made much easier, as Mr Ellis ably pointed out in his letter (*EW + WW*, January 1991), if complementary feedback-pair configuration is chosen so only driver junction temperatures (which can be kept much lower) are allowed to get into the act. Why does the Darlington version still persist? It seems to have no countervailing advantages. With thermal feedback it is theoretically possible for a little crossover distortion to get through for short periods, but it is greatly preferable to a circuit which guarantees lots of it all the time.

McLoughlin takes 6mV crossover spikes on his audio far too casually. Crossover distortion has been recognised for a long time as a distortion mechanism to be feared most. It is always present at any signal level, its percentage increases sharply in quiet musical passages, and it produces high-order harmonics more subjectively disturbing than second or third.

McLoughlin's circuit leaves easily visible crossover spikes on output waveform, even when running with 100% negative feedback, and suggests a poor starting point for amplifier design. Normal class-B biasing keeps combined

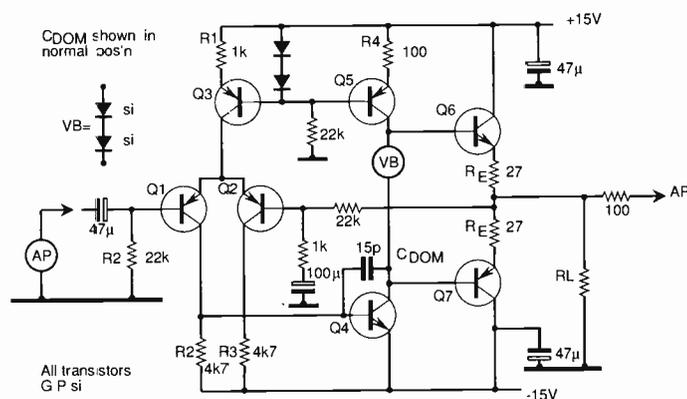


Fig. 1. Test circuit.

transconductance of an output pair roughly constant, but in this circuit each one traverses the most non-linear part of its characteristic, where it begins to turn on, in splendid isolation.

Circuits modelled using small-signal transistors often prove quite impossible to translate to realistic power levels, as power transistors are so much slower. If McLoughlin's amplifier was scaled up to produce say 30W, it would prove very difficult to stabilise with 100% NFB. How much ordinary non-linear distortion is generated by this circuit? Reported figures are absent so we are surely justified in fearing it may be truly diabolical.

Driving a dominant-pole compensation capacitor  $C_{dom}$  from output rather than voltage-amplifier-stage (VAS) collector is not a new idea – it was advocated by Cherry in 1982<sup>1</sup> and others. But current through it must be sunk as well as sourced, and in the circuit shown can only go through the VAS base or  $R_E$ . It is limiting sinking current that causes slew-limiting.

Output-driving of  $C_{dom}$  reduces high frequency distortion effects at the output stage as this is now included with the local feedback loop to provide stabilisation. Practical effects are very small unless HF distortion is deliberately introduced as crossover spikes by under-biasing, as shown. I used a small-signal circuit (Fig. 1), which

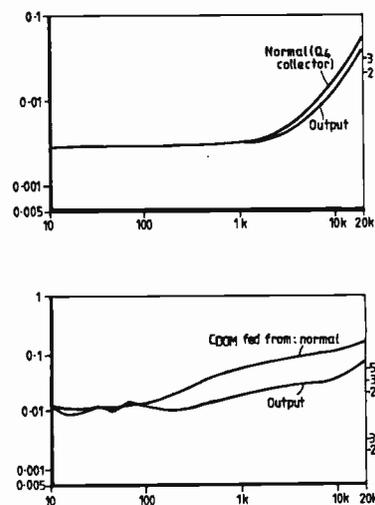


Fig. 2. O/p stage correctly biased (a), and underbiased (b) to give a peak reading of 0.05% (1kHz). Very narrow crossover spikes: Cherry is right.

is representative in many ways of real power amps, and can easily be turned into one by adding power output devices. Under-biasing is arranged to give 0.05% THD Peak at 1kHz, reading 0.003% RMS, showing just how narrow such spikes are, feeding  $C_{dom}$  output reduced it to 0.02% Peak. But spikes were clearly present on the residual

## Audio interest revitalised

My interest in audio amplifier design had waned – until I read Greg Ball's letter "Distorted truth" (*EW + WW*, May 92). Now I realise a whole new area of discovery lies ahead; power supply and PSRR, and I know why some people can hear fuses and mains cable, maybe they are not crazy after all.

Here are some ideas which might solve the problem.

Don't use supply rails as references. How many amps use common emitter output stages or quasi-complementary connections?

Use differential amps before the power stage with stiff current sources. Use separately regulated supply rails for these stages.

Finally, as a professional switched-mode power supply designer I have long been looking at an excuse to use this sort of supply in an audio power amp. Regular linear supplies produce volts of audio frequency ripple at supply rails, large magnetic fields, have poor regulation, high output impedance and are big and ugly. But look at the SMPS; tightly regulated rails, low impedance, recoverable short-circuit protection, small size and above all noise and ripple outside the audio spectrum. Excuse me, I must find my ferrite data book!

A M Wilkes  
Brentwood



and in no way could such an amplifier be considered for high-quality audio.

Circuit results (Fig. 2) appear to put driving  $C_{dim}$  from output into a "can't hurt-might help" category – but there is a real snag. Such a connection tends to induce parasitic VHF oscillation in its drivers, and can be very hard to cure without compromising other parameters.

I am sorry to appear negative towards McLoughlin's efforts, but I was prompted to write because he intends to put his circuit into a school textbook. I am afraid he will do his readers a disservice if this happens.

**Douglas Self**  
London

#### References

1. Cherry. "Nested Differentiating Loops." *Journal of the Audio Engineering Society*; Vol 30, #5, May 1982.

## Dingled angle on physics

It is now some 20 years since a British physicist (the late professor H Dingle) wrote his astonishing book, "*Science at the Crossroads*", in which he *proved* that Einstein's theory of Special Relativity is wrong!

Unfortunately Dingle made the tragic mistake of not putting his fantastic discovery into

mathematical language. Special Relativity violates common sense, but one can hardly stomach a theory that violates mathematics too! Putting Dingle's discovery into mathematical form instantly reveals Einstein had got a sign wrong in his calculations, and would have been fatal for his relativity theory.

But Dingle's neglect of the mathematics meant his book, the most important in physics this century, now lies forgotten on library shelves, classified under "History of Physics".

We owe a great debt to Dingle. It is high time his incredible discovery is recognised. Inevitably, it will take us back to his crossroads, and an evolution of entirely new physics.

Why not call that new discipline, Post Dingle Physics. That's the least we can do to honour a forgotten pioneer.

**A H Winterflood**  
North London

## Power politics and the knowledge gap

Alasdair Philips' article "Power Politics: playing with children's lives" (*EW + WW*, April 1992) demonstrates just how fluid the situation is regarding health effects of electromagnetic radiation. New evidence and theories appear regularly, yet there is still no prospect of a definitive statement about real hazards due to exposure

to low level EM fields. Between epidemiological studies on one hand, and a plethora of cellular-level research and theories on another, there is a yawning knowledge gap.

Knowledge gaps allow those with responsibility and authority, but who have interests vested in promoting growth of electricity consumption, to continue to prevaricate. It also allows an uninformed public to speculate about health hazards in a way which is stressful to individuals concerned and creates suspicion and mistrust of expert opinion.

But epidemiology can only take us so far. There are confounding factors, such as possible exposure to toxic chemicals in electrical/electronic occupations which have an apparently elevated risk, or possible exposure to exhaust fumes in a case study which showed an elevated risk associated with wiring configuration and road traffic density. There are immense difficulties in assessing actual doses received, surrogate measurements cannot give even an approximate indication of complex time- and spatially-dependent dose factors which apply to people moving in real time-varying fields. Only a prospective cohort study in which subjects were constantly monitored could do this which would be prohibitively lengthy and expensive to achieve any degree of statistical significance.

Published research papers regarding cellular interactions and animal behaviour claim and disprove observable effects of field interaction. But few are independently replicated to claim scientific consensus because detail levels are insufficient. If environmental synergies are responsible for the effect – such as geomagnetic field or chemical promoter presence – it is not surprising that the effects cannot be replicated under different conditions, if parameters of original environments were not noted. Nevertheless continuing research, although better co-ordinated, will overcome many of these objections.

An approach is needed which recognises variable susceptibility and researches factors affecting sensitive people, to gain a better picture of the real hazards.

Authorities have problems admitting any kind of hazard which will open floodgates to all kinds of litigation.

Research funded by interested

## Please explain

We are told by nearly all experts there is no ether – but surely fields must have some existence.

The speed of light is said to be constant for an observer, but no one has satisfactorily explained to me how the Doppler effect operates when an observer is moving towards a source of light or radio waves. Surely if received frequency rises, it means an observer is catching up faster with peaks and troughs.

It is also claimed that the magnetic monopoles exist. I feel magnetic fields are movements of ether, or something similar, from North to South Poles and must always have entry and exit. If so, no monopole could exist because there would be no return for "Fluid".

I must admit I still think of electrons as little bullets rather than waves.

But perhaps a *EW + WW* readers could help clear up these puzzles – in non-mathematical terms.

**A J Quinton**  
Victoria  
Australia

parties, such as the National Grid Company, will produce biased results. Credibility needs to come from a disinterested source of funds or independent administration. All those addressing the issue must be encouraged to keep open minds to all available evidence.

**Tim Williams**  
Elmac Services  
Chichester

## Impulsive comment

Professor Grundy's idea of structured analogue blocks is a good one ("Structured Analogue Design Builds perfect filters", *EW + WW*, May 1992) but I do not think it will work for filters. His claim that analogue filtering is made easier is tenuous and Grundy offers no solid arguments in justification. He dismisses a very serious problem of

## Unity mark-space ratio

Most text books on digital logic contain a statement such as: "To obtain an exact unity mark-space ratio, generate a signal at twice the frequency required and divide by two."

If only that were true! A perfect square wave contains only desirable odd harmonics, and there is no difficulty in suppressing third and higher harmonics by passive filtration.

I attempted to make a spectrally pure VHF signal source using a 74AC74 as a divider, but with disappointing results. The second harmonic was significantly present. Close inspection of data sheet small print shows why. (I am quoting from Texas data for centre-power type 74AC11074). Time given of the propagation low-high ( $t_{PLH}$ ) as ranging from 1.5 to 8.2ns and  $t_{PHL}$  as 1.5 to 7.5ns. So a greater proportion of each cycle will be spent in output low-state rather than high.

At a clock frequency of 100MHz, the output period is 20ns. A few tenths difference of a nanosecond is significant in terms of second harmonic content. The effect is readily seen in Fig. 3 of my article "Spectrum Analysis on the Cheap" (*EW + WW*, March 1992).

It is a shame to dispose of this old myth, but as clock frequencies move constantly higher now seems to be time to do so.

**Nick Wheeler**  
Surrey

Surplus always wanted for cash!


# THE ORIGINAL SURPLUS WONDERLAND!

Surplus always wanted for cash!

## COMPUTER SCOOPS
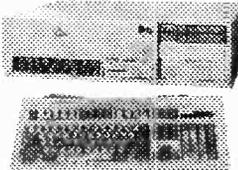
### PC-AT 386 20-DX FULLY LOADED FOR £499!

- 20 Mhz DX processor
- 2 megs RAM. Exp 10 meg
- 40 meg hard drive
- 1.2 meg 5-1/4" floppy
- 32K cache exp. 64K
- Installed VGA card
- Enhanced 102 key k/board
- Complete with MS-DOS 3.3
- 2 serial 1 parallel ports
- 8 free slots- 6 off 16 bit!




The MP386 quality made by Mitsubishi last a lifetime! Brand new with all manuals and software plus Super PC-Quick Disk Accelerator for lightning disk access.

Only **£499** (F)

## MONITORS

### MONOCHROME MONITORS

#### THIS MONTH'S SPECIAL!

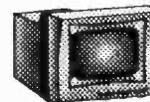

There has never been a deal like this one! Brand spanking new & boxed monitors from NEC, normally selling at about £140! These are over-engineered for ultra reliability. 9" green screen composite input with etched non-glare screen plus switchable high/low impedance input and output for daisy-chaining. 3 front controls and 6 at rear. Standard BNC sockets. Beautiful high contrast screen and attractive case with carrying ledge. Perfect as a main or backup monitor and for quantity users! **£39.95 each (D) or 5 for £185 (G)**

CALL FOR DISCOUNTS ON HIGHER QUANTITIES! COLOUR MONITORS

### HI-DEFINITION COLOUR MONITORS

#### JUST ARRIVED!


MULTISYNC - VGA -

14" Philips Model CM8873 VGA multisync all the way up to 34KHz with 640 x 480 resolution. This one has everything! Two switches enable you to select CGA, EGA or VGA and Digital/analog. Unusual for a professional monitor, sound is also provided, with a volume control. There is also a special "Text" switch for word processing, spreadsheets and the like. Compatible with virtually all computers including IBM PCs, Amiga, Atari, BBC, Archimedes etc. Good used condition (possible minor screen burn) 90 day guarantee. 15" x 14" x 12". **£159 (E)**

Brand new 12" multitilt high definition colour monitors by KME. Nice tight 0.28" dot pitch for superb clarity and modern two tone plastic styling. Operates from any 15.625 kHz sync RGB video source, with either individual H & V syncs such as CGA IBM PC's or RGB analog with composite sync such as Atari, Commodore Amiga, Acom Archimedes & BBC. Measures only 13.5" x 12" x 11". Also functions as quality TV with our RGB Telexbox. Excellent used condition with 90 day guarantee. In nice two tone beige and brown case. Only **£149 (E)**

Brand new Centronic 14" monitor for IBM PC and compatibles at a lower than ever price! Completely CGA equivalent. Hi-res Mitsubishi 0.42 dot pitch giving 669 x 507 pixels. Big 28 MHz bandwidth. A superb monitor in attractive style moulded case. Full 90 day guarantee. Only **£129 (E)**

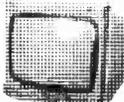
NEC CGA 12" IBM-PC compatible. High quality ex-equipment fully tested with a 90 day guarantee. In an attractive two tone ribbed grey plastic case measuring 15" x 13" x 12" H. The front cosmetic bezel has been removed for contractual reasons. Only **£79**


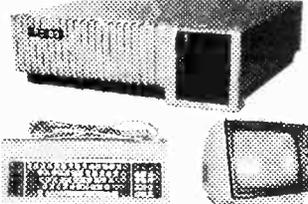
### A COMPLETE IBM PC COMPAT SYSTEM FOR ONLY £99!!

Just plug in and go - fully expandable - the Display PC-991 System supplied complete with 12" mono monitor, 84 key keyboard, 360K 5-1/4" floppy disk drive, 128K RAM, 2 serial and 1 parallel port plus DOS with manual. Many other features include 7 slot backplane, all metal case, 180 watt PSU and US made motherboard. In very good used condition with 90 day guarantee. At the unique price of:

Optional FITTED extras: 256K RAM £15; 640K RAM £39. 12" CGA colour monitor with card £89. 2nd 5-1/4" 720K floppy (or 360K if preferred) £29.95. 20 mbyte hard drive £99. **£99 (E)**



## FLOPPY DISK DRIVES

5 1/4" from £22.95 - 3 1/2" from £21.95!

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported).

- 3.5" Panasonic JU364 720K\* £21.95(B)
- 3.5" Mitsubishi MF353C-L 1.4 Meg. Laptops only £29.95(B)
- 3.5" Mitsubishi MF353C-D 1.4 Meg. Non laptop £29.95(B)
- 5.25" Teac FD-55(36) 360K half height. £22.95(B)
- 5.25" Teac FD-55(72) 720K half height. £24.95(B)

\* Data cache included in price.

Shugart 800/801 SS refurbished & tested £175.00(E)

Shugart 851 double sided refurbished & tested £275.00(E)

Mitsubishi M2894-83 double sided switchable hard or soft sectors - BRAND NEW £250.00(E)

Dual 8" drives with 2 mbyte capacity housed in a smart case with built in power supply! Ideal as exterior drives! £499.00(F)

End of line purchase scoop! Brand new NEC D2246 8" 85 megabyte of hard disk storage! Full CPU control and industry standard SMD interfaces. Ultra high speed transfer and access time leaves the good old ST506 interface standing. In mint condition and comes complete with manual. Only **£299 (E)**

## THE AMAZING TELEBOX!

Converts your colour monitor into a

QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by manufacturers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD and many more. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television or video channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Composite and RGB video outputs are located on the rear panel for direct connection to most makes of monitor. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

- Telebox ST for composite video input monitors £32.95
  - Telebox STL as ST but with integral speaker £38.50
  - Telebox MB as ST with Multiband tuner VHF-UHF-Cable. & hyperband For overseas PAL versions state 5.5 or 6mhz sound specification. £69.95
  - Telebox RGB for analogue RGB monitors (15khz) £89.95
- Shipping code on all Teleboxes is (B)

RGB Telebox also suitable for IBM multsync monitors with RGB analog and composite sync. Overseas versions VHF & UHF call. SECAM / NTSC not available.

## No Break Uninterruptable PSU's

Brand new and boxed 230 volts uninterruptable power supplies from Denzel. Model MUK 0565-AUAF is 0.5 kva and MUD 1085-AHBH is 1 kva. Both have sealed lead acid batteries. MUK are internal, MUD has them in a matching case. Times from interrupt are 5 and 15 minutes respectively. Complete with full operation manuals.....MUK.....£249 (F) MUD.....£525 (G)

## POWER SUPPLIES

Power One SPL200-£200P 200 watt (250 w peak). Semi open frame giving +5v 35a, -5v 1.5a, +12v 4a (8a peak), -12v 1.5a, +24v 4a (6a peak). All outputs fully regulated with over voltage protection on the +5v output. AC input selectable for 110/240 vac. Dims 13" x 5" x 2.5". Fully guaranteed RFE. **£85.00 (B)**

Power One SPL130. 130 watts. Selectable for 12v (4A) or 24 v (2A). 5v @ 20A. ±12v @ 1.5A. Switch mode. New. **£59.95(B)**

Aesac AC-8151 40 watts. Switch mode. +5v @ 2.5a. +12v @ 2a. -12v @ 0.1a. 6-1/4" x 4" x 1-3/4". New **£19.95(B)**

Greendale 19AB0E 60 watts switch mode. +5v @ 6a. ±12v @ 1a. +15v @ 1a. RFE and fully tested. 11 x 20 x 5.5cms. **£24.95(C)**

Conver AC130. 130 watt hi-grade VDE spec. switch mode. +5v @ 15a, -5v @ 1a. ±12v @ 6a. 27 x 12.5 x 6.5cms. New. **£49.95(B)**

Boshart 13090. Switch mode. Ideal for drives & system. +5v @ 6a, +12v @ 2.5a, -12v @ 0.5a, -5v @ 0.5a. **£29.95(B)**

Farnell G6/40A. Switch mode. 5v @ 40a. Encased. **£95.00(C)**

## BBC Model B APM Board

BBC Model B type computer on a board. A major purchase allows us to offer you the PROFESSIONAL version of the BBC computer at a parts only price. Used as a front end graphics system on large networked systems the architecture of the BBC board has so many similarities to the regular BBC model B that we are sure that with a bit of experimentation and ingenuity many useful applications will be found for this board! It is supplied complete with a connector panel which brings all the VO to 'D' and BNC type connectors - all you have to do is provide +5 and ±12 v DC. The APM consists of a single PCB with most major IC's socketed. The IC's are too numerous to list but include a 6502, RAM and an SAA5050 teletext chip. Three 27128 EPROMS contain the custom operating system on which we have no data. On application of DC power the system boots and provides diagnostic information on the video output. On board DIP switches and jumpers select the ECONET address and enable the four extra EPROM sockets for user software. Appx. dims: main board 13" x 10". VO board 14" x 3". Supplied tested with circuit diagram, data and competition entry form.

Only **£29.95 or 2 for £53 (B)**

## SPECIAL INTEREST

- Tri-o 0-18 vdc bench PSU. 30 amps. New £ 470
- Fujitsu M3041 600 LPM band printer £2950
- DEC LS/02 CPU board £ 150
- Rhodes & Schwarz SBUF TV test transmitter 25-1000mhz. Complete with SBTFT Modulator £8500
- Calcomp 1036 large drum 3 pen plotter £ 650
- Thurby LA 1608 logic analyser £ 375
- 1.5kw 115v 60hz power source £ 950
- Anton Piller 400 Hz 3 phase frequency converter 75Kw POA £ 650
- Sony KTX 1000 Videotex system - brand new £ 225
- ADDS 2020 VDU terminals - brand new £2000
- Selkonic SD 150H 18 channel Hybrid recorder £1850
- HP 7580A A1 8 pen high speed drum plotter £ 350
- Kerwood DA-3501 CD tester, laser pickup simulator

## BRAND NEW PRINTERS

- Microline 183. NLO 17x17 dot matrix. Full width. £130 (D)
- Hyundai HDP-920. NLO 24x18 dot matrix full width. £140 (D)
- Game LetterPro 20 daisy. Qume OS-3 Interface. £39.95 (D)
- Centronics 152-2 9 x 7 dot matrix. Full width. £140 (D)
- Centronics 150-4 9 x 7 dot matrix. Serial. 9-1/2" width £ 99 (D)

20", 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & sound inputs. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

CALL FOR PRICING ON NTSC VERSIONS!

## Superb Quality 6 foot 4ou 19" Rack Cabinets

Massive Reductions  
Virtually New, Ultra Smart!  
Less Than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half covered back door and removable side panels. Fully adjustable internal fixing struts, ready

punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels or stand singly. Overall dimensions are 77-1/2"H x 32-1/2"D x 22"W. Order as:

- £ 650 Rack 1 Complete with removable side panels.....£275.00 (G)
- £ 375 Rack 2 Less side panels.....£145.00 (G)

## COOLING FANS

- 3 inch AC. 112" thick £ 8.50(B)
- 92 mm AC 230 v. 18mm thick £12.95(B)
- 3 1/2 inch AC ETRI slimline. Only 1" thick. £ 9.95(B)
- 3 1/2 inch AC 230 v 8 watts. Only 3/4" thick £12.95(A)
- 4 inch AC 110/240v 11/2" thick. £10.95(B)
- 10 inch AC round. 3 1/2" thick. Rotron 110v £10.95(B)
- 10 inch As above. but 230 volts £24.95(B)
- 60 mm DC 1" thick. No.812 for 6/12v.814 24v. £15.95(A)
- 90 mm DC 5 v. Papst 8105G 4w. 38mm. RFE. £19.95(A)
- 92 mm DC 12v. 18 mm thick. £14.95(A)
- 4 inch DC 12v. 12w 1 1/2" thick £12.50(B)
- 4 inch DC 24v 8w. 1" thick £14.50(B)

LARGE QUANTITIES OF OSCILLOSCOPES AND TEST GEAR ALWAYS AVAILABLE - CALL NOW!

# DISPLAY

MAIL ORDER & OFFICES  
Open Mon-Fri 9.00-5.30  
Dept WW. 32 Biggin Way,  
Upper Norwood,  
London SE19 3XF.

LONDON SHOP  
Open Mon-Sat 9-5.30  
Thursday till 9.00pm  
215 Whitehorse Lane,  
South Norwood,  
London, SE25.

DISTEL © The Original  
Free dial-up database!  
1000's of items+info On Line  
V21, V22 & V22 bis  
**081-679-1888**

ALL ENQUIRIES  
**081-679-4414**  
Fax- 081-679-1927



# -ELECTRONICS-

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. PO orders from Government, Universities, Schools & Local Authorities welcome-minimum account order £30. Carriage charges (A)=£2.00. (A1)=£3.75. (B)=£5.50. (C)=£8.50. (D)=£11.50. (E)=£14.00. (F)=£18.00. (G)=Call. Scotland surcharge: call. All goods supplied subject to our standard Conditions of Sale and unless otherwise stated guaranteed for 90 days. All guarantees on a return to base basis. Rights reserved to change prices & specifications without prior notice. Orders subject to stock. Quotations willingly given for higher quantities than those stated. Bulk surplus always wanted for cash.

CIRCLE NO. 127 ON REPLY CARD

component tolerances in a single sentence by stating they "should not be a problem". Surely he should have analysed possible errors and given more definite conclusions.

But, my main criticism is that he has not attempted to analyse filter response in a rigorous way.

Grundy's fundamental argument – that double differentiating a signal results in an amplitude scaling with no phase shift – is fatally flawed. Whatever his filters do (and they are non-linear systems for a start) they certainly do not perform like a low pass filter with no phase shift. His problem is that the real world is not made up of sine waves, but impulses. Contrary to Grundy's introduction, digital filters *do* introduce a phase shift, or at least a constant delay. Put an impulse into a low-pass filter with no phase shift at all and it will not be stable.

**David Gibson**  
Leeds

## Caution casual reader

David Grundy's article entitled "Structured Analogue Design Builds Perfect Filters" (*EW + WW*, May 1992) proposes two non-linear filter designs. Type II design is based on the equation

$$V_{out} = \frac{V_{in}^{\lambda+1}}{V_{in}^{\lambda} + \left(-\frac{d^2}{dt^2} V_{in}\right)^{\lambda}}$$

and the type I is based on

$$V_{out} = \frac{V_{in}^{\lambda+1}}{\left(V_{in} - \frac{d^2}{dt^2} V_{in}\right)^{\lambda}}$$

While these designs will work as advertised for single frequency sinusoidal input signals, their performance will be quite different when subjected to multiple frequency inputs and are due to large amounts of intermodulation distortion caused by the non-linear exponentiation process.

If an input signal is the sum of two sinusoids whose respective frequencies place one in the passband and a second in the stopband, then an ideal filter would have only the pass band signal present at its output. Unfortunately, this does not occur for these filters. To illustrate, consider Grundy's type

II  $N=5$  design with an input of  $V_{in} = \sin 0.5t + \sin 4t$   
Output will be given by:

$$V_{out} = \frac{(\sin 0.5t + \sin 4t)^6}{(\sin 0.5t + \sin 4t)^5 + (0.25 \sin 0.5t + 16 \sin 4t)^5}$$

In plots detailing  $V_{in}$  and  $V_{out}$ , notice that the output does not represent the desired response but contains many



high order mixing products.

While there may be valid real world applications for these types of

filters, casual readers should be cautioned against their generalised application.

Plots detailing  $V_{in}$  (top) and  $V_{out}$  (above). Output does not represent desired response but contains many high order mixing products.

**Jim Mittel**  
Motorola  
Florida

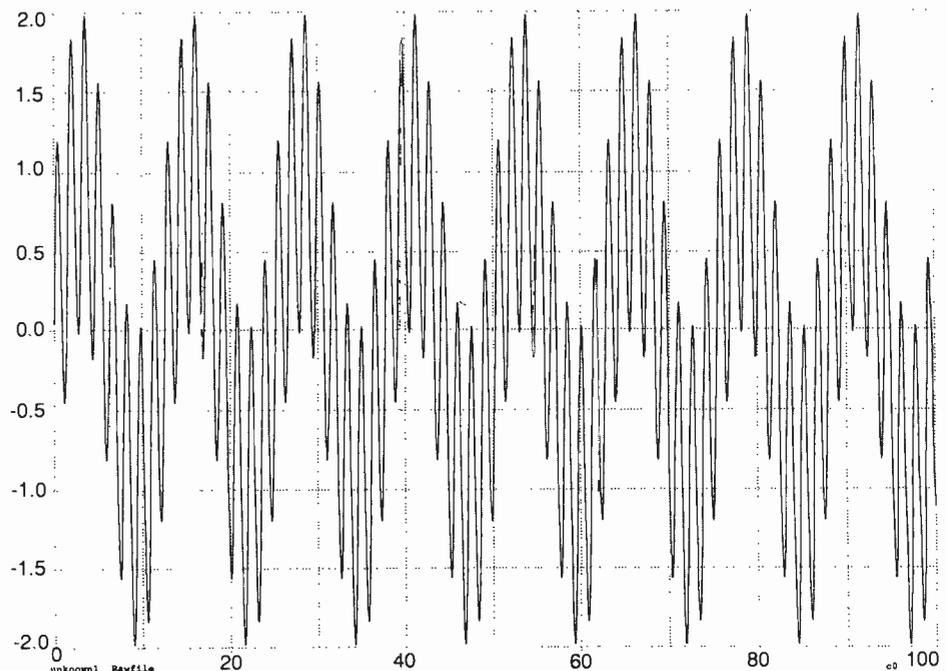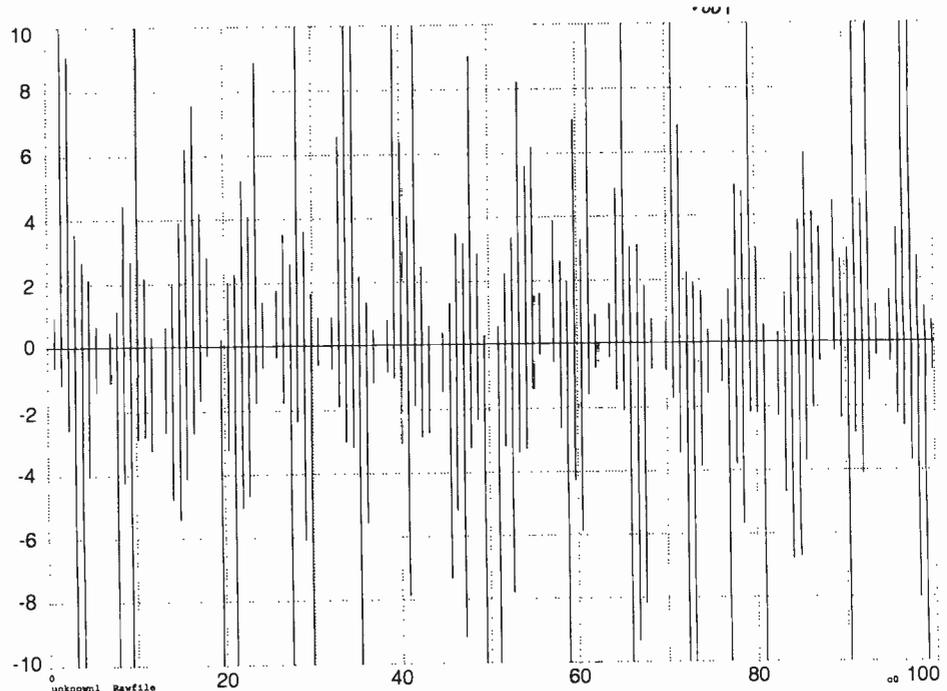

# J. & M. Computers

Reliability DC-DC Power Source, 12½m 5V out  
600MA out .....£9.00 each

DS Connector 9→50 way male-female,  
all types ..... from 20p each to 60p each

24V Fans, 18V Fans ..... from £1.75 each

Hitachi LMO87LN, LMO32LN Displays .....£6.50 each

Cable Ribbon, Multi-way Coax ..... On Request

Connectors, Coax 75a Type 43 & B37AT JO12X,  
many others ..... from £1.00 each

E. Prom 2764A-200 N/S, E. Prom 27128-200,  
E. Prom 27C256-2-OPT, E. Prom 27C1001-20FX1,  
E. Prom 27C256-15 ..... all at £2.30 each

8086-Z-P ..... £5.00

I.C. Sockets ..... Various

RF Attenuator 50a 6DB 250 Watt 1.59Hz .....£150.00 each

BLW 50F, BLY 92C, BLW 60R, MHU 5222A,  
MRF 4921 ..... all at £8.00 each

NE 27177-3B, FLC053 WG109, FSX51  
WF-141 ..... all at £40.00 each

Battery, Varta CR2032 3V, 20mm round ..... £1.00 each

Duracell TR146X 8.4V, PP3 type ..... £1.00 each

## FIBRE OPTIC TELECOMMUNICATION

CW Laser Devices

STC MS6189/AC Type TS 8079

Lasertron SS 4070/10 At 1.3mm and 1.5mm SS 4070

Laser Diode SN 50470 Type LTD-362E-80 SS 4070

STC Type PT 1609-19C6

Laser Diode SN DN 2957 Type LDT-362E-80 SS4070

HR 1103TR-B

PCD 0311-FC-A-B

Pin Diode MLS 1023/2

Microwave Tube Transmitting YA 1198/G REG

Travelling Wave Amplifier Type W4 MC 13A STC

Travelling Wave Amplifier Type KS-49 493-1 STC

NEC OD 9470B-1-2M-D

ALL NEW BOXED

## TRANSISTORS & IC's

BD3535  
PMS77C01NL  
D780C-1  
SFC2741M  
ZTX750L  
BC559  
DS00269 MIL V/S  
Photodiode detector  
HR1103TR-B  
PCD0311-FC-A-B  
Crystal 4.416  
Pin diode  
ML61023/2

---

PPR300 10-3  
CCS 272018-3  
Resistor

---

Filter E 10.7 H  
KTXD-18503D-7.200418MHz

---

ICN1KV  
Type HPX613  
HAX1035DACFDX

---

130 160V  
Z084004VSC  
Z84C4204PEC  
Z84C4004PEC  
Z7220A08VSC  
Z8028010VSC  
Z0853004PSC  
Z8440ASIO  
Z8430APS  
Z8430AC-TC  
Z80ACTC  
N8821  
SN84161N  
T74LS126B  
HCDBAXAA143  
SN74S15W  
T74LS139BI  
GD74HC175  
GD74HC175  
GD4053B  
GD4519B  
GD74HC153  
GD74HC05  
G7905CU  
BD202  
HEF404DBDI  
HEF4023BD  
HEF4021BPI  
PC74HC368P  
HEF400988P  
NE5592N  
PC74HC283F

PC74HC368P  
MC1489  
Z8028010VSC  
Z84C4004PEC  
Z84C4204PEC  
Z84C4004PEC  
Z0868112PSC  
Z641800PSC  
Z85308PE  
Z0803006VSC  
Z84C4004AEE  
Z84C4404VEC  
Z0841004PSC  
Z0853606DSE  
Z0844404VSC  
Z0858106CSE  
Z84C400CMB  
Z0853004PSC  
Z84C2004VSC  
Z0853604CMB  
Z8536ACEA  
Z860312RSE  
Z82KXFOJ  
T74LS138BI  
T1001GRHCT373  
MC74AC174N  
GD74HCT245  
GD74HC125  
HEF4028BP  
HEF4028BP  
HEF4028BP  
AD75BILCWI  
MX7547JN  
GD74HC257  
GD74LS393  
GD74HCT245  
AD7581JN  
GD74HCT245  
MX7538JN  
MX7502JN  
AD7537JCW  
MAX131CPL  
AD7538JCWG  
IC17614DCPA  
GD7475393  
ICL76140CPA  
HCT373/T1001GR  
GAL16U8-35HD  
ICL76140CPA  
MAX134CQH  
14584BX819  
MAX1232  
MAX251  
ESD938  
GD4516B  
GD74HC10

TC74HC20P  
GD400IB  
GD74HCT241  
GGD4510B  
GD4052B  
GD74HC365  
GD74LS393  
GD74LS393  
GD74HC293E  
MC14070B  
MC14070B  
SN7400N  
SN7400N  
SN7400N  
SN7400N  
SN7400N  
SP8650B  
MC10141L  
MC10174L  
MC14070B  
MC14070B  
SN7406N  
MC14070B  
SN7406N  
MC14070B  
MEDL8434  
TDA1060B  
CD40103BE  
SN74HC109N  
MC14070B  
MC14070BCL  
MC14070B  
2N2907A  
BFX80  
BXY71  
BF421  
MPAA92  
IN5829  
IRF610  
BC557BT  
BYV32  
MC14070BCLD  
MC34070BCLD  
SM74LS390N  
SN74ALS500AN  
M9112LP311N  
SN74ALS27N  
SN7406N  
TLD80CD  
MC14001BCL  
MC14001BCL  
MC14001BCL  
MC14001BCL  
MC14001BCL  
MC14001BCPP  
SB9124A  
TDA1060B  
SI91100J  
MEDL8930I

TDA1060B  
ILQ74L8946H  
AM685DL  
MC14015BCP  
MCP3022  
74LS05N  
FFPQ2907  
H11AIL8918H  
H11BIL8833H  
ZM477E  
FFXY9119  
4W28V923  
74F258APC  
MX7524KN  
SFH615-4  
PC74HC20T  
T74LS10BI  
ICL7126CPL  
M74HC20BI  
LM748CN  
M74HCOOB1  
GD4731B  
ICL7126CPL  
T74LS139B1  
LM748CN  
2N2222  
BC178C  
2N2903  
BCY71  
2N2369A  
BD165A  
IRF640  
IRF642  
IRF630  
MBR1035  
BDX34A  
2NREFO25CI  
L7905CV  
IRF230  
BR220-140  
HA178L05  
HA179L05  
HA178L12  
HA179L12  
HA179L15  
BDX62A  
UA7915  
L7905CV  
BD952  
M3E350  
HA19216  
HA19508A  
TA7676P  
HA11544  
AR5836  
PAL8L14AC

27C256-20N-H  
P8049AH  
DMP3000-001  
TA7778P  
LM339N  
DICA  
TA8611AN  
LA3624  
STA401A  
SSD1196  
SSC930  
JC556  
25C930  
25A1015-Y  
25C3000  
S740GN  
STB8912  
DS3691N  
VN2406L  
F421  
F420  
C557  
MPSA92  
2N6519  
C547  
C337  
C640  
BC639  
BXY95A  
BFR37  
BF521A  
BCY71  
ZN1308  
ZN1302  
CV9790  
BCY34A  
ACY18  
1ZLN1309  
CV7438  
1AUGET895  
1UGALY20  
1UGACY17  
BSY39  
BFY18  
ZN1986  
BCY32  
ML102M  
LU308X  
DS75452H  
BF756  
BCY40  
ZN5179  
OC139/RO18  
CV9507  
BFY30  
ADZX2  
CCBX003

PRICES PLUS VAT & POSTAGE & PACKING

**J. & M. COMPUTERS**  
**EIGHT ACRES,**  
**GT TOTHAM ROAD,**  
**WICKHAM BISHOPS,**  
**WITHAM, ESSEX.**

**Tel: (0621) 892701**

**Fax: (0621) 891414**

CIRCLE NO. 128 ON REPLY CARD



# SQUEEZING INTO THE PICTURE

*Much has happened since the Fractal Transform emerged as a contender for commercial image compression and decompression products. OEM products using the technique have appeared, and the technique now has gained wide endorsement. But the technique has yet to prove itself for motion picture compression.*

*Andy Wright reports.*

**F**ractal image compression and decompression exploits the mathematics of fractals to provide very high compression ratios together with resolution independence. Despite its youth compared with industry standards like JPEG, the Fractal Transform is rapidly winning fans throughout the industry. According to Greg Riker, director of product development at Microsoft's multimedia publishing group: "Fractal technology offers the highest usable compression on the market." Microsoft has now licensed Iterated Systems' software and fractal products are scheduled to appear on the market later this year.

Image compression has long been a vital tool in computer graphics and digital video. Until recently, techniques based on the discrete cosine transform (DCT) have set the standard. It is estimated that around 90% of applications use the DCT, incorporated as it is in international standards such as the ISO Joint Photographic Experts Group, JPEG.

Details of the DCT are explained in a previous article in *EW + WW* (Vol. 97, No. 1675, p. 431, June 1992). Briefly, it is a particular

type of discrete Fourier transform, which maps the image into frequency space. A predefined set of cosines is applied as 'basis functions' to the image, resulting in a set of amplitudes (DCT coefficients) that, together with the basis functions, reproduces the original image in frequency space. Large-scale features form low-frequency components, whilst smaller-scale features become high-frequency components.

Finding DCT coefficients does not in itself lead to any data compression. However, as the human eye is less sensitive to high-frequency components, these can be eliminated to compress the image.

One disadvantage is that, at large compression ratios, pixelation becomes apparent; the decompressed image looks 'blocky'. Furthermore, artifacts begin to appear, such as the Gibbs phenomenon; rippling that appears where there is a high degree of contrast.

*Standard compression (left) vs Fractal Transform compression. Detail from a larger picture blown up to demonstrate the resolution enhancement available with the Fractal Transform process.*

between areas of the original picture.

Such artifacts can be reduced by variations on the DCT, such as wavelet image compression. Here more complex functions than simple cosines are applied as the basis functions. But there is a further drawback. JPEG and other standards have fixed on the 8 x 8 pixel block as the basic unit for compression, resulting in 64 DCT coefficients for each block. Decompression has to be performed at the same resolution.

Nevertheless, the development of special hardware, dedicated silicon and improved calculation techniques have produced substantial progress. Most crucially, there is substantial applications, development and silicon support. Its commercial progress is virtually unstoppable. However there are fundamental limitations to how much improvement is possible with the DCT.

Not so with the Fractal Transform, say its proponents. New it may be, but many believe it has a promising future because of its scalability and resolution independence, ability to produce 'pleasing' images even at high compression ratios together with a fundamentally limitless scope for improvement. These are all features uniquely inherent in the Fractal Transform.

Central to the algorithm is the idea that many parts of an image are self-similar: regions of the image can describe each other when twisted, distorted and shifted by an affine transformation, a type of linear transform. For example:

$$W(x,y) = (x/2 + y/4 + 1, x/4 + y/2 + 2).$$

The more general form is:

$$W(x1, x2) = (ax1+bx2+e, cx1+dx2+f)$$

where *a*, *b*, *c*, *d*, *e* and *f* are real numbers. Expressed as percentages (i.e. multiplied by 100) they are referred to as Iterated Function System codes.

A collection of contractive affine transfor-

mations, known as an iterated function system (IFS), describes a unique fractal image called an attractor. Applying the affine transformation to its attractor produces the original fractal image.

Quite complex images can be generated by taking a dot, performing an affine transformation on it, overlaying the second dot, then performing the same transformation on the new shape in its new location, and so on.

The resulting image can therefore be stored very compactly by simply storing its IFS codes. Decoding the image is simply a matter of repeatedly applying the affine transformation. All very well for decompression, but how to find the IFS codes for a complex real-world image?

Solving that problem was the pioneering breakthrough of former mathematics professor, and Iterated Systems' founder, Dr. Michael Barnsley.

His company's solution first breaks the image up into areas called domain blocks. For each domain block, it then scans the rest of the image and identifies so-called 'range regions', areas that are best described by an affine transformation from the domain block. The result is a series of affine maps, each not only describing the shrinking, twisting and deformation of the image within the range regions, but also changing brightness and contrast relative to the original. The compressed data also carry a header defining the domain block geometry of the original image.

The next stage is to store the resulting IFS codes. It is here of course that the compression comes in; identifying similar data and discarding redundant pieces of information.

The technique only works because many affine redundancies are found. In fact, it is basic tenet of Fractal Transform that real world images exhibit a high level of affine redundancy, that is, they contain many self-

*Right hand picture is detail extracted from a 4kbyte Fractal Transform file compared with the same detail taken from the 301k original file.*



referencing objects. The success of the technique bears out the truth of this axiom.

Decompression is computationally much easier using a technique known as pixel chaining. For example, take two images of equal size. Call them A and B. They can be any image, even random data. Transform the contents of A into B using the IFS codes generated from the original image. B is divided into domain blocks according to the header of the compressed file, and for each domain, locate and transform the range block data from A. B becomes a completely new image.

Next, transform the data from B into A, again using the affine maps from the compressed image. This time, A is divided into domain blocks and B has the range data.

Keep on doing this repeatedly until there are no significant differences between A and B. At this point, we are back to the original image: a consequence of Fractal geometry.

The beauty of pixel chaining is that it can start with any images, at any resolution. All video and graphics standards can be accommodated.

How closely the result matches the real-life original depends on how accurately the range regions had matched the domain blocks in the original compression process.

#### Improving on 1000 years

Refinement of the Fractal Transform method has been largely the refinement of fractal theory to improve the probabilistic search routines and enhance this match. To get a perfect match would take many years of calculation. Indeed when the Fractal Transform was first proposed, it was estimated that the calculation time would be of the order of 1023 years.

To get to a more realistic time scale, it is necessary to make approximations. Iterated Systems' skill is largely attributed to knowledge of when errors of approximation are important; being an iterative process, even small discrepancies could be amplified explosively. The art is to make approximations where the computation will damp errors rather than multiplying them.

With such research, there is no theoretical limit to the amount of improvement possible. One could go on improving the probabilistic search routines, modifying the geometry of domain blocks – all in the search for greater affine redundancy.

The company has now refined the process to the extent that it is now able to offer compression as well as decompression in software. Previously, compression required special optimised hardware.

Naturally compromises have had to be made. The software compression algorithms perform less of the deep searches that dedicated hardware can make but, at the end of the day, the result is only 5% worse than is possible with dedicated hardware in terms of image quality.

The process is still highly asymmetrical: where decompression can be processed on the fly at frame rate, with a 33MHz '386 compression typically takes several minutes.

A further demonstration of its potential came about with Racal Radio's announcement of PICTOR, a system for transmitting images over HF radio links. With PICTOR, the Fractal Transform is used to compress 768Kbyte images down to just 10Kbytes. As a result, images that would normally take hours to transmit can be sent in just six or so minutes. The system has obvious applications with security services and civilian authorities.

Endorsements like this, together with improvements in the technique itself, bode well for the future of fractals. A recent research report from the Gartner Group of market analysts predicts that the Fractal Transform has a 50% probability of becoming the *de facto* image compression standard. Previously it had given the technique a 20% chance.

Silicon support for the Fractal Transform has recently received a boost in the form of a \$2million grant from the US government. Under its Advanced Technology Program, the National Institute of Standards and Technology is funding research into devices for fractal based high-fidelity image compression. The ultimate aim is silicon that could be used in high definition TV applications.

Whether based on DCT or Fractals, real image compression systems incorporate further lossless techniques to code the data more compactly. Run-length coding squeezes data by contracting strings of similar values; for example the sequence 1, 1, 1, 2, 2, 2, 2, 2, 5, 5, 5, 5, 1, 1, 1 is expressed as 3, 1, 4, 2, 4, 5, 3, 1. Huffman coding is a technique where patterns of data are assigned a compact code. The most frequently-occurring patterns have the shortest codes, whilst uncommon patterns have longer codes. Hence this is variable-length coding, more generally referred to as statistical coding. Thus the JPEG standard applies various techniques in following order: DCT; quantisation; run-length code; Huffman code.


### Moving images

For moving images, additional techniques are employed, which can be combined with various types of lossy and lossless compression.

Although fractals are pining JPEG for still pictures – coding times are measured in minutes while decoding takes seconds – they have yet to make an impact on moving pictures. Clearly, since a moving picture can be broken down into a series of still images, applying any of the standard image compression techniques to each frame will provide a degree of compression, say a factor of 10 or 20 would be acceptable. But the computational and bandwidth constraints are much greater for displaying moving pictures.

For instance a compact disc player is capable of transferring data at 1.4Mbyte/s. Even TV-standard images are equivalent to 260 lines of 350 pixels, at 50Hz frame rates, an order of magnitude greater than this.

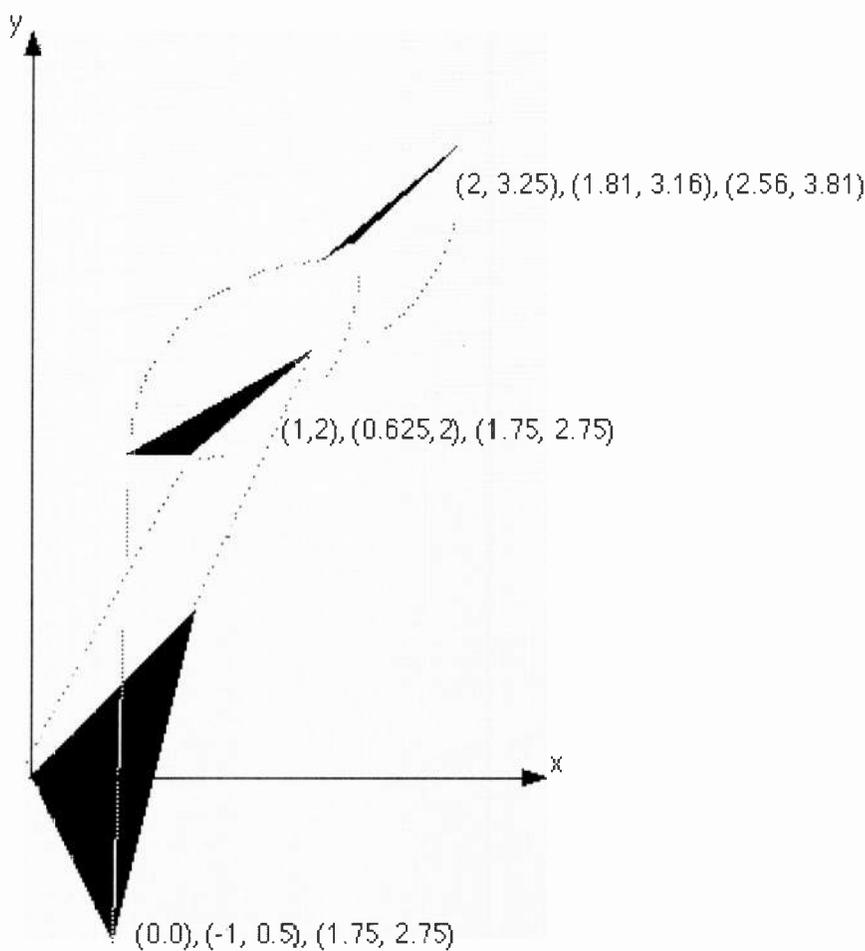Fortunately, most real-world moving images already have a degree of redundancy built-in. The image changes little between successive



*Central to the Fractal Transform is the idea that many parts of an image are self-similar: regions of the image can describe each other when twisted, distorted and shifted by an affine transformation, a type of linear transform. For example this drawing shows a triangle undergoing successive affine transformation derived from the function  $W(x,y) = (x/2 + y/4 + 1, x/4 + y/2 + 2)$*

frames, so compression can be achieved by storing differences between successive frames, rather than the whole image.

This is the approach adopted in Intel's RTV and PLV standards used for its Digital Video Interactive (DV-I) technology. Here, a reference frame is stored, then subsequent frames are subtracted from it and coded as differences known as delta frames. The reference frame is refreshed after around 60 frames.

Further compression is achieved by storing colour information only for every fourth pixel. Hardware interpolates between pixels to avoid blockiness.

The motion estimation principle undergoing standardisation by the ISO Motion Picture Experts Group likewise exploits the fact that images do not change much between frames. However, it improves on the delta frame concept by making the reasonable assumption that changes between successive frames can be described by groups of pixels moving within the image. In other words, parts of the current picture are translations of parts of another picture at another time.


Inter-frame coding with MPEG-1 works on 16 x 16 blocks of pixels. It searches adjacent

frames for a macro block of pixels that match the macro block of pixels in the current frame, and derives a motion vector defining the relative position of the matched macro block.

It works both forward and backward in time. For areas that exist in a previous frame, it uses an earlier reference, whilst for an area uncovered by a subject moving, it can use a later reference.

In practical applications, there will still be differences between the predicted image produced by motion estimation, and the actual current image. Small errors can be smoothed by filtering through a loop filter, and the errors still present can also be coded as differences. Thus the MPEG compressed video image is a complex combination of an intra-frame coded base image; inter-frame coded motion vectors and intra-coded difference data.

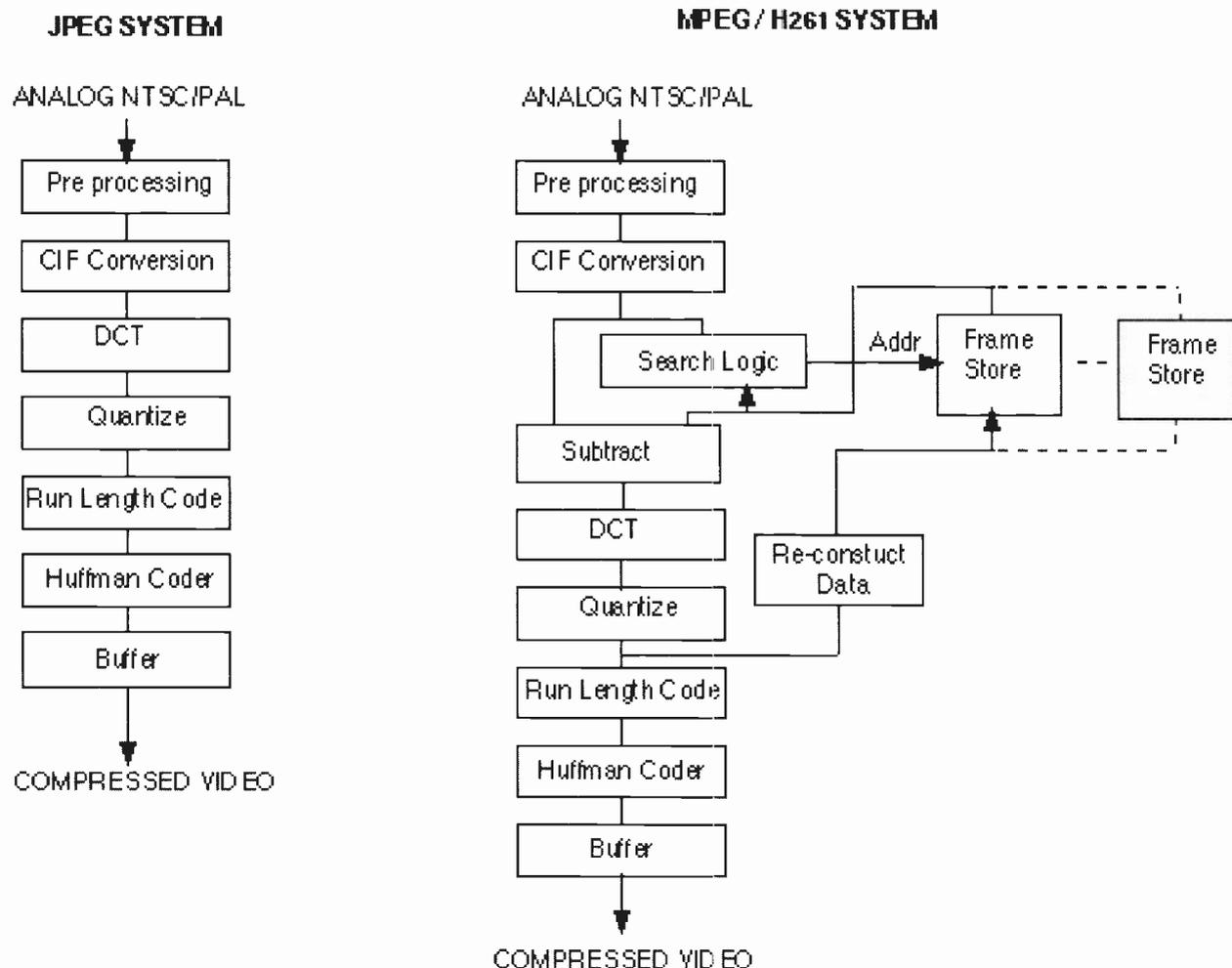Where JPEG is symmetrical, applying DCT and coding one way, the inverse DCT and decoding in the reverse path, the MPEG approach is asymmetrical with moving images. More computational power is required for compressing the data than decompressing it, the latter having only inverse DCT as its main computational requirement.



**Pictures in silicon**

With standards very much under development, it is not surprising that image compression and decompression have moved slowly to silicon.

Intel's DV-1 is perhaps the furthest advanced. The i750 video processor chips use DSP technology, with a pixel processor implementing video and graphics compression routines via an on-chip microcode instruction ram. Being programmable, the processor can implement a range of compression algorithms, and can be reprogrammed to accommodate evolving standards.

Closely coupled to an associated display processor chip, both devices use on-chip hardware to perform frequently-used operations such as filtering and statistical decoding. There is extensive support including JPEG for still images, and improved routines for motion estimation. RTV can also be ported to other processor architectures.

MPEG has less direct support in silicon. But major vendors have separate devices performing individual image manipulation tasks, and are moving towards single chip solutions.

SGS-Thomson, for example, has discrete cosine transform processors for JPEG-standard 8 x 8 pixel blocks, as well as multi-pixel block size operation from 4 x 4 to 16 x 16. Its most recent offering is a motion estimation

*The principal difference between JPEG – intended for still images – and MPEG involves the motion detection mechanism which records only the differences from frame to frame to reduce data rate. Although the MPEG compression process is computationally more intensive, decompression is essentially the same for both systems.*

processor capable of computing motion vectors and mean absolute errors for matching blocks. It conforms with CCITT and MPEG standards, but requires additional circuitry for a full MPEG solution. Needless to say, more integrated solutions are in the pipeline.

GEC Plessey Semiconductors is into the second generation of image compression and decompression devices. Its activities currently focus on low cost applications such as video telephony, and plans are well advanced to introduce a highly integrated encoder for H.261 – effectively a subset of MPEG standards specifically for video phones. First silicon should be sampling as you read this.

The H.261 encoder will incorporate motion compensation as well as lossy transmission. A cell-based silicon design approach has been adopted to combine flexibility with optimised performance. Such versatility means much of the design effort could be reused in develop-

ing future JPEG and MPEG devices.

Conversely Motorola addressed the MPEG ISO standard directly with its recent announcement of a single-chip full motion video (FMV) decoder, which has all the functionality required to implement Level 1 of the MPEG standard, plus interface circuitry to ease development of multi-media applications. This is specifically directed at Compact Disc Interactive (CD-I) players. Rather than going the programmable route, Motorola has benefited from close ties with multi-media market leaders like Philips, and gone straight to an optimised solution. ■

**USEFUL CONTACT NUMBERS**

GEC Plessey Semiconductors	0793-518000
Intel Corporation UK	0793-696000
Iterated Systems	0734-880261
Motorola	0296-395292
SGS-Thomson	0628-890800
Zoran (Amega)	0256 843166

## COMPUTER ICs

2817A-20 (2Kx8) EEPROM ex eqpt.	£2
AM7910 Modern chip ex. eqpt £5 new	£10
80C88A-2 used	£1.25
27C64-25 used/wiped	£1.50 100+ £1
27S191 PROM	£2
IMS1400P-45	£2
80C31 MICRO	£2
P8749H MICRO	£5
8D751H USED	£6
NEW 4164-15	£1
USED 41256-15	£1
USED 4164-15	60p
BBC VIDEO ULA	£10
6845 CRT	£5
6522 PIA	£3
AY3-1015D UART	£2.50
9 x 41256-15 SIMM	£10
8 x 4164 SIP MODULE NEW	£8
HD 146818 CLOCK IC	£2
2864 EPROM	£3
27128A 250ns EPROM USED	£2 NEW £2.30
27C1001-20Z NEW 1M EPROM	£6
FLOPPY DISC CONTROLLER CHIPS 1771	£10
FLOPPY DISC CONTROLLER CHIPS 1772	£17.50
68000-8 PROCESSOR NEW	£6
HD6384-8	£5
ALL USED EPROMS ERASED AND BLANK CHECKED CAN BE PROGRAMMED IF DESIRED	
2716-45 USED	£2 100/£1
2732-45 USED	£2 100/£1
2764-30 USED	£2 100/£1.60
27C256-30 US:FD	£2
27C512 USED	£3.50
1702 EPROM EX EQPT	£5
2114 EX EQPT 50p 4116 EX EQPT	70p
6264-15 8K STATIC RAM	£2
GR281 NON VOLATILE RAM EQUIV 6116	£5
Z80A SIO-O	£1.25
TMS27C256-25 ONE SHOT 27C256	£1 ea 100/£70
P80387-16 CO-PROCESSOR	£80
M27C1024-12Xf1 (40-pin 1 MEG EPROM)	£4.50
NMC9306EN EEPROM 256 bits	£1

## REGULATORS

78H12ASC 12V 5A	£5
78M05 5V 0.5A	7/£1
LM317H T05 CAN	£1
LM317T PLASTIC TO220 variable	£1
LM317 METAL	£2.20
7812 METAL 12V 1A	£1
7805/12/15/24V plastic	25p 100+ 20p 1000+ 15p
7905/12/15/24 plastic	25p 100+ 20p 1000+ 15p
CA3085 T099 variable reg	2/£1
LM338 5A VARIABLE 1.2-30V	£8
L387 5v 1/2A WITH RESET OUTPUT	£1ea £50/100

## CRYSTAL OSCILLATORS

1M000 1M8432 1M000 4M000 10M000 16M000	
18M432000 20M500 56M6092	£1.50 each

## CRYSTALS

1M0 1M8432 2M000 2M304 2M77 3M000 3M2768 3M400	
3M579545 3M58564 3M93216 4M000 4M194304	
4M194304 4M4336 4M9152 5M000 5M0688 6M000	
6M400 8M000 8M448 8M9304 10M240 10M245 11M000	
12M000 13M000 13M270 14M000 14M318 16M000	
15M000 16M000 16M5888 17M000 20M000 21M300	
21M855 22M1 184 24M000 34M368 36M36875 36M5625	
36M78125 36M79375 36M80625 36M81875 26M83125	
36M84375 38M900 49M50 54M19166 57M7416 57M7583	
69M545 69M550	£1 each

## TRANSISTORS

BC107 BCY70 PREFORMED LEADS	
full spec	£1 £4/100 £30/1000
BC557, BC546B, BC238C, BC308B	£1/30 £3.50/100
2N3819 FETS short leads	4/£1

## POWER TRANSISTORS

P POWER FET IRF9531 8A 60V	3/£1
N POWER FET IRF531 8A 60V	2/£1
2SC1520 sim BF259	3/£1 100/£22
TIP 141/2 £1 ea TIP 112/125/42B	2/£1
TIP35B/TIP35C	£1.50
SE9301 100V 1DA DARL SIM TIP121	2/£1
PLASTIC 3055 OR 2955 equiv 50p	100/£35
2N3773 NPN 25A 160V £1.60	10/£14
2N3055H	4 for £2

## TEXTLOO ZIF SOCKETS

28 WAY ZIF EX NEW EQUIPMENT	£2.50
40 WAY NEW	£5
SINGLE IN LINE 32 WAY CAN BE GANGED FOR USE WITH ANY DUAL IN LINE DEVICES... COUPLING SUPPLIED	2/£1.50

## CAPACITORS COMPUTER GRADE

2200uF 160V SIC SAFCO FELSIC C038	£4 (£1.20)
24.000uF 50V	£3 (£1.30)
10.000uF 100V SPRAGUE/PHILIPS	£6 (£2.00)

## QUARTZ HALOGEN LAMPS

12V 50watt LAMP TYPE M312	£1 ea HOLDERS 60p ea
24V 150 WATTS LAMP TYPE A1/215	£2.50 each

## NEW BITS

'SAFEBLOCKS' MADE BY RENDAR... MAINS 'RAT TRAP' USED	£4 ea
7126 3 1/2-DIGIT LCD DRIVER CHIP	£2 ea
74N16 MOTOROLA CELLULAR CAR PHONE O/P MODULE	£5 ea
CMOS 555 TIMERS 20k available	2/£1 £30/100

## MISCELLANEOUS

36 CORE 7/0.2mm OVERALL SCREENED	£50/100m
----------------------------------	----------

## LITHIUM CELL 1/2 AA SIZE 2 FOR £1

PASSIVE INFRA RED SENSOR CHIP + MIRROR + CIRCUIT £2 each	
EUROCARD 21-SLOT BACK PLANE 96/96-WAY	£25 ea
"PROTONIC 24 VARIBUS" 16.7"x5" FIBREGLASS MULTILAYER PTH PCB	
EUROCARD 96-WAY EXTENDER BOARD 290x100mm	£10 ea
"PROTONIC 24" c/w 2 SUPPORT ARMS/EJECTORS. DIN 41612 96-WAY A/B/C SOCKET PCB RIGHT ANGLE	£1.30
DIN 41612 96-WAY A/B/C SOCKET WIRE WRAP PINS	£1.30
DIN 41612 64-WAY A/C SOCKET WIRE WRAP PINS	£1
DIN 41612 64-WAY A/C SOCKET PCB RIGHT ANGLE	£1
DIN 41612 64-WAY A/B SOCKET WIRE WRAP (2-ROW BODY)	£1
BT PLUG + LEAD	3/£1
PC PARALLEL PRINTER CABLE	£5.90
13A MOULDED PLUG+2m lead	£1
MIN. TOGGLE SWITCH 1 POLE c/o PCB type	5/£1
LCD MODULE sim. LM018 but needs 150 to 250V AC for display 40x2 characters 182x35x13mm	£10
TL431 2.5 to 36V TO92 ADJ. SHUNT REG	2/£1
6-32 UNC 5/16 POZI PAN SCREWS	£1/100
NUTS	£1.25/100
PUSH SWITCH CHANGEOVER	2/£1
RS232 SERIAL CABLE D25 WAY MALE CONNECTORS	£5.90 ea (£1.30)
25 FEET LONG, 15 PINS WIRED BRAID + FOIL SCREENS INMAC LIST PRICE £30	
STICK ON CABINET FEET RS NO 543-327	30/£1
LEMAG EARTH LEAKAGE TRIP 35A 35mA TRIP	£9
FANS 240V 120MM	£6 (£1.50)
(OTHER VOLTAGES/SIZES USUALLY AVAILABLE)	
AMERICAN 2/3 PIN CHASSIS SOCKET	2/£1
HUMIDITY SWITCH ADJUSTABLE	£2
WIRE ENDED FUSES 0.25A	30/£1
NEW ULTRASONIC TRANSDUCERS 32kHz	£2/pr
12-CORE CABLE 7/0.2mm OVERALL SCREEN	70p/metre

POWERFUL SMALL CYLINDRICAL MAGNETS	3/£1
BNC 50OHM SCREENED CHASSIS SOCKET	2/£1
SMALL MICROWAVE DIODES AET1 OC1026A	2/£1
D.I.L. SWITCHES 10-WAY £1 8-WAY 80p 4/5/6-WAY	
180VOLT 1WATT ZENERS also 12V & 75V	20/£1
VN 10LM 60V 1/2A 5 Ohm TO-92 mostet	4/£1 100/£20
MIN GLASS NEONS	10/£1
RELAY 5V 2-pole changeover looks like RS 355-741 marked STC 47Wbost	£1 ea
MINIATURE CO-AX FREE PLUG RS 456-071	2/£1
MINIATURE CO-AX FREE SKT RS 456-273	2/£1.50
DIL REED RELAY 2 POLE n/o CONTACTS	£2
PCB WITH 2N2646 UNIJUNCTION WITH 12V 4-POLE RELAY	£1
400m 0.5W thick film resistors (yes four hundred megohms)	4/£1

STRAIN GAUGES 40 ohm Foil type polyester backed balco grid alloy	£1 50 ea 10+ £1
ELECTRET MICROPHONE INSERT	£0.90
Linear Hall effect IC Micro Switch no 613 S54 sim RS 304- 287	£2.50 100+ £1.50
HALL EFFECT IC UGS3040 + magnet	£1
OSCILLOSCOPE PROBE SWITCHED x1 x10	£12
1 pole 12-way rotary switch	4/£1
AUDIO ICS LM380 LM386 TDA 2003	£1 ea
555 TIMERS £1 741 OP AMP	6/£1
ZN414 AM RADIO CHIP	80p
COAX PLUGS nice ones	4/£1
COAX BACK TO BACK JOINERS	3/£1
4x4 MEMBRANE KEYBOARD	£1.50
INDUCTOR 20uH 1.5A	5/£1
1.25" PANEL FUSEHOLDERS	3/£1
CHROMED STEEL HINGES 14.5x1" OPEN	£1 each
12V 1.2W small w/lamps fit most modern cars	10/£1
STEREO CASSETTE HEAD	£2
MONO CASS. HEAD £1 ERASE HEAD	50p
THERMAL CUT OUTS 50 77 85 120°C	£1 ea
THERMAL FUSES 220°C/121°C 240V 15A	5/£1
TRANSISTOR MOUNTING PADS TO-5/TO-18	£3/1000
TO-3 TRANSISTOR COVERS	10/£1
PCB PINS FIT 0.1" VERO	200/£1
TO-220 micas + bushes	10/50p 100/£2
TO-3 micas + bushes	15/£1
PTFE min screened cable	10m/£1
Large heat shrink sleeving pack	£2
IEC chassis plug filter 10A	£3
POTS SHORT SPINDLES 2K5 10K 25K 1M 2M5	4/£1
40k U/S TRANSDUCERS EX-EQPT NO DATA	£1/pr
LM335Z 10MV/degree C	£1
LM234Z CONST. CURRENT I.C.	£1
PAPST 18-24V FAN 120MM WORKS OK ON 12V	£5
BNC TO 4MM BINDING POST SIM RS 455-961	£1
BUTTON CELLS SIM. AG10/AG12	4/£1
MIN PCB POWER RELAY 12V COIL 6V CONTACTS 2 P C/O	£1.25

AVEL-LINDBERG MOULDED TRANSFORMER TYPE OB10 15+15V 10VA QTY. AVAILABLE	£2 ea
BANDLIERED COMPONENTS ASSORTED Rs, Cs, ZENERS	£5/1000
LCD MODULE 16 CHAR. X 1 LINE (SIMILAR TO HITACHI LM10)	£5
KYNAR WIRE WRAP WIRE	£1/REEL
OPTI264A 10kV OPTO ISOLATOR	£1.35 ea 100+ £1 ea
'LOVE STORY' CLOCKWORK MUSICAL BOX MECHANISM MADE BY SANKYO	£1 ea

## DIODES AND RECTIFIERS

A115M 3A 600V FAST RECOVERY DIODE	4/£1
1N5407 3A 1000V	8/£1
1N4148	100/£1.50

1N4004 SD4 1A 300V	100/£3
1N5401 3A 100V	10/£1
BA158 1A 400V fast recovery	100/£3
BY127 1200V 1.2A	10/£1
BY254 800V 3A	8/£1
BY255 1300V 3A	6/£1
6A 100V SIMILAR MR751	4/£1
1A 600V BRIDGE RECTIFIER	4/£1
4A 100V BRIDGE	3/£1
6A 100V BRIDGE	2/£1
8A 200V BRIDGE	2 £1.35
10A 200V BRIDGE	£1.50
25A 200 V BRIDGE £2	10/£18
25A 400V BRIDGE £2.50	10/£22

## SCRs

PULSE TRANSFORMERS 1:1+1	£1.25
2P4M EQUIV C106D	3/£1
TICV106G 800mA 400C SCR 3/£1	100/£15
MEU21 PROG. UNIJUNCTION	3/£1

## TRIACS

NEC TRIAC AC08F 8A 600V TO220	5/£2 100/£30
TXAL225 8A 500V 5mA GATE	2/£1 100/£35
BTA 08-400 ISO TAB 400V 5mA GATE	90p
TRAL2230D 30A 400V ISOLATED STUD	£5 ea
TRIAC 1A 800V TLC381T 16k AVAILABLE	

5 FOR £1 £15/100

## CONNECTORS

D25 IDC SOCKET FUJITSU	£2
34-way card edge IDCONNECTOR (disk drive type)	
CENTRONICS 36 WAY IDC PLUG	£2.50
CENTRONICS 36 WAY IDC SKT	£4.00
BBC TO CENTRONICS PRINTER LEAD 1.5M	£3
CENTRONICS 36 WAY PLUG SOLDER TYPE	£4
USED CENTRONICS 36W PLUG+SKT	£3

## PHOTO DEVICES

HI BRIGHTNESS LEDS COX24 RED	5/£1
SLOTTED OPTO-SWITCH OPCOA OPB815	£1.30
2N5777	50p
TIL81 PHOTO TRANSISTOR	£1
TIL38 INFRA RED LED	5/£1
4N25, OP1252 OPTO ISOLATOR	50p
PHOTO DIODE 50P	6/£2
MEL12 (PHOTO DARLINGTON BASE n/c)	50p
LED's RED 3 or 5mm 12/£1	100/£6
LED's GREEN OR YELLOW 10/£1	100/£6
FLASHING RED OR GREEN LED 5mm 50p	100/£40
HIGH SPEED MEDIUM AREA PHOTODIODE RS651- 995	£10 ea

## STC NTC BEAD THERMISTORS

G22 220R, G13 1K, G23 2K, G24 20K, G54 50K, G25 200K, RES 20°C DIRECTLY HEATED TYPE	£1 ea
FS22BW NTC BEAD INSIDE END OF 1" GLASS PROBE RES 20°C 200R	£1 ea
A13 DIRECTLY HEATED BEAD THERMISTOR 1k res. ideal for audio Wien Bridge Oscillator	£2 ea

## CERMET MULTI TURN PRESETS 3/4"

10R 20R 100R 200R 250R 500R 2K 2K2 2K5 5K 10K 47K 50K 100K 200K 500K 2M	50p ea
--	--------

## IC SOCKETS

14/16/18/20/24/28/40-WAY DIL SKTS	£1 per TUBE
8-WAY DIL SKTS	£2 per TUBE
32-WAY TURNED PIN SKTS, 7k available	3 for £1
SIMM SOCKET FOR 2x30-way SIMMS	£1

## SOLID STATE RELAYS

40A 250V AC SOLID STATE RELAYS	£10
--------------------------------	-----

## POLYESTER/POLYCARB CAPS

100n, 220n 63V 5mm	20/£1 100/£3
1n/3n/5n/6n/8n/2/10n 1% 63V 10mm	100/£5
10n/15n/22n/33n/47n/66n 10mm rad	100/£3.50
100n 250V radial 10mm	100/£3
100n 600V Sprague axial 10/£1	100/£6 (£1.10)
2u2 160V rad 22mm, 2u2 100V rad 15mm	100/£10
10n/33n/47n 250V AC x rated 15mm	10/£1
1u 600V MIXED DIELECTRIC	50p ea
1u0 100V rad 15mm, 1u0 22mm rad	100/£6

## RF BITS

CONHE X 50ohm PCB RIGHT ANGLE PLUG	
ITT/SEALCTRO 051 053 9029 22-0 4K AVAILABLE	

ALL TRIMMERS	2/£1
TRIMMERS larger type GREY 2-25pF	3 for 50p
VIOLET	5-105pF
SMALL 5pF 2 pin mounting 5mm centres	
SMALL MULLARD 2 to 22pF	3 FOR 50p £10/100
TRANSISTORS 2N4427	70p
CERAMIC FILTERS 4M5/6M/9M/10M7	60p ea
FEED THRU CERAMIC CAPS 100pF	10/£1
SL610	£5

## MINIATURE RELAYS Suitable for RF

5 volt coil 1 pole changeover	£1
5 volt coil 2 pole changeover	£1
12 volt coil 1 pole changeover	£1

## MONOLITHIC CERAMIC CAPACITORS

10n 50V 2.5mm	100/£4.50
100n 50V 2.5mm or 5mm	100/£6
100n ax short leads	100/£3
100n ax long leads	100/£5
100n 50V di package 0.3" rad	100/£8
1uF 50v 5mm	£6/100

## STEPPER MOTORS

2 CENTRE-TAPPED 9 VOLT WINDINGS 7.5° STEPS	£4
--	----

# KEYTRONICS

TEL. 0279-505543

FAX. 0279-757656

P O BOX 634

BISHOPS STORTFORD

HERTFORDSHIRE CM23 2RX

SEND £1 STAMPS FOR CURRENT IC+SEMI STOCK LIST - ALSO AVAILABLE ON

3 1/2" FLOPPY DISK

MAIL ORDER ONLY

MIN. CASH ORDER £3.00. OFFICIAL ORDERS WELCOME

UNIVERSITIES/COLLEGES/SCHOOLS/GOVT. DEPARTMENTS

MIN. ACCOUNT ORDER £10.00

P&P AS SHOWN IN BRACKETS (HEAVY ITEMS) OTHERWISE 65p

ADD 17 1/2% VAT TO TOTAL

ELECTRONIC COMPONENTS BOUGHT FOR CASH



CIRCLE NO


# PROGRAMMING FLEXIBILITY FOR PROFESSIONALS

## HARDWARE FEATURES

- PC-BASED PROGRAMMERS
- UK DESIGN, MANUFACTURE AND SUPPORT
- NO MESSY INTERNAL CARD
- PLUGS DIRECTLY INTO PARALLEL PORT (LPT1-3)
- EASILY TRANSPORTABLE BETWEEN MACHINES
- WORKS WITH XT, AT, 386, & 486. EVEN LAPTOPS!
- INCREDIBLY FAST PROGRAMMING TIMES
- FLEXIBLE DESIGN MEANS NO ADAPTORS NEEDED FOR MOST DIP PACKAGES
- UPGRADES BY FLOPPY
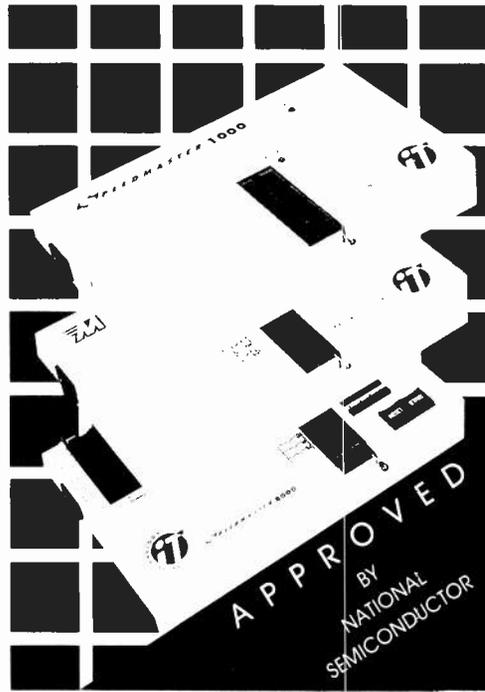
## SOFTWARE FEATURES

- MENU DRIVEN
- FLEXIBLE FILE LOADING (HEX, BINARY, JEDEC)
- READS, VERIFIES, BLANK CHECKS, BIT TESTS, OVER-PROGRAMMES AND AUTO-PROGRAMMES
- CAN MODIFY PARAMETERS OF EXISTING MEMORY DEVICES AND STORE IN USER DATABASE
- HANDLES SECURITY FEATURES OF ALL DEVICES
- AUTOMATIC PAL TO GAL CONVERSIONS
- FULL BUFFER EDITING CAPABILITIES
- TEST VECTOR SUPPORT



## SPEEDMASTER 1000

- LOW COST, UNIVERSAL PROGRAMMER
- EPROMS, EEPROMS, FLASH EPROMS, NVRAMS, SERIAL EEPROMS, PALS, GALS, PEELS, EPLDS
- SUPER FAST PROGRAMMING e.g. 27C256 (32kx8) IN 4.5 Seconds
- JEDEC TEST VECTOR SUPPORT FOR PALS
- INCLUDES PAL DEVELOPMENT SOFTWARE
- UP TO 40 PIN DIPS WITHOUT ADAPTORS

**£445**

## MICROMASTER 1000

- ALL FUNCTIONS OF SPEEDMASTER 1000
- MICROCONTROLLERS FROM T.I. (including TMS370-SERIES, TMS77C82), INTEL, ZILOG, MICROCHIP (PICS), MOTOROLA, PHILIPS AND OTHERS

**£575**

## SPEEDMASTER 8000

- 8 WAY GANG/SET PROGRAMMER
- MASTER SOCKET
- EPROMS, EEPROMS, FLASH EPROMS
- UP TO 32 PIN
- PC OR STAND ALONE MODE
- SUPER FAST PROGRAMMING e.g. 8x27c256 (32Kx8) IN 6 Seconds

**£645**

Prices exclude VAT & delivery

ICE TECHNOLOGY LTD

UNIT 4, PENISTONE COURT, STATION BUILDINGS, PENISTONE, SOUTH YORKSHIRE S30 6HG

TEL (+44) 0226 767404 FAX (+44) 0226 370434

CIRCLE NO. 130 ON REPLY CARD

## WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 2445B 4-Ch 150MHz D.S. with Cursors.....	£1750
IWATSU SS5711 4-Channel 100MHz Delay Sweep.....	£700
TEKTRONIX 2336 Dual Trace 100MHz D.S. Ruggedised.....	£1000
TEKTRONIX 2235 Dual Trace 100MHz Delay Sweep.....	£800
TEKTRONIX 7603 Dual Trace 100MHz D.S. with Cursors.....	£500
HITACHI 1050F D.Tr. 100MHz Dual TB with 4-Ch Mode.....	£550
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep.....	£550
TEKTRONIX 465 Dual Trace 100MHz Delay Sweep.....	£450
TEKTRONIX 2215A Dual Trace 60MHz Delay Sweep.....	£500
TEKTRONIX 7403 Dual Trace 60MHz Delay Sweep.....	£400
HUNG CHANG OS650 D.Tr. 50MHz D.S. Unused.....	£375
PHILIPS PM317 Dual Trace 50MHz Delay Sweep.....	£400
TEKTRONIX 2225 D.Tr. 50MHz Alternate TB Magnification.....	£500
HAMEG 605 Dual Trace 60MHz Delay Sweep.....	£400
GOULD OS1100 Dual Trace 30MHz.....	£180
BECKMAN 9020 Dual Trace 20MHz Delay Sweep.....	£250
IWATSU CS5070 Dual Trace 20MHz.....	£225
GOULD OS300 Dual Trace 20MHz.....	£200
GOULD OS250B Dual Trace 15MHz.....	£150
FARNELL DT12-5 Dual Trace 12MHz.....	£125
HITACHI V209 Dual Trace 20MHz (AC/DC Operation).....	£400

THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE

## ELECTRON MICROSCOPES

A.E.I. Corinth 500 - Transmission  
I.S.I. Super 111A - Scanning

MARCONI 2440 200Hz Microwave Counter.....	£1500
MARCONI 2610 True RMS Voltmeter.....	£800
FARNELL SSC1000 Sig Gen 10MHz-1GHz Synthesised.....	£1750
MARCONI 2019 Sig Gen 80kHz-10MHz.....	£150
MARCONI 2022A Sig Gen 10kHz-1GHz.....	£1500
FARNELL Synthesised Oscillator DSG1 - 0.0001Hz-99.99kHz.....	£275
MARCONI TF2015 AM/FM 10-520MHz Sig Gen with TF2171.....	£400
MARCONI TF2015 without Synchroniser TF2171.....	£250
MARCONI TF2016 AM/FM 10kHz-120MHz with TF2173.....	£350
MARCONI TF2016 without Synchroniser TF2173.....	£175
MARCONI TF2356/2357 Level Osc/Meter 20MHz the pair.....	£950
MARCONI SANDERS Sig Sources. Various models. Covering 400Hz-8.5GHz.....	from £300
RACAL 9009 Mod Meter 10MHz-15GHz.....	£350
RACAL Instrumentation Recorders Store 4D and Store 7D.....	from £500
KEITHLEY Y 224 Programmable Current Source.....	£1000
FERROGRAPH RT52 Recorder Test Set.....	from £150
FARNELL SSG520 Synthesised Sig Gen 10-520MHz.....	£600
FARNELL TTS520 Transmitter Test Set. Comprising of R/AF Counter, RF Mod Meter, RF Power Meter, AF Voltmeter, AF Distortion Meter, AF Synthesiser.....	£600
SOLD as a pair for ONLY.....	£1000

## SPECTRUM ANALYSERS

TEKTRONIX 494AP 10kHz-325GHz.....	P.O.A.
ANRITSU MS68B 10kHz-4GHz.....	£4000
ANRITSU MS63B 10kHz-1700MHz.....	£2000
HP 141T with 8555A & IF Plug-in 10MHz-18GHz.....	£2500
HP 141T with 8554B & 8552B 500kHz-1250MHz.....	£1500
HP 140T with 8554L & 8552A 500kHz-1250MHz.....	£1200
HP 141T with 8554A & 8552B 20kHz-300kHz.....	£1250
TEKTRONIX 491 Option 01 10MHz to 2GHz.....	£1000

PHILIPS PM2525 Multi Function DMM 4.5-5.5-digit with GPIB/IEEE 488.....	Only £300
THURLBY PL320T-GP Bench PSU 0-30V 2-Amp Twice with GPIB.....	£350
HAND-HELD MULTIMETERS - 3.5-digit DM105 - 14 Ranges DC-2Amp.....	Only £18
M2355 - 32 ranges AC/DC 10 Amps Diode/Transistor Tester; Freq counter etc.....	Only £32.50

RACAL/DANA Syn Sig Gen 9084 0.01-104MHz.....	£500
RACAL/DANA RF Power Meter 9104.....	£800
RACAL/DANA 302 Logic State Analyser with 68000 Dassembler.....	£500
WAYNE KERR LCR Meter 4210. Accuracy 0.1%.....	£600
WAYNE KERR LCR Meter 4225. Accuracy 0.25%.....	£500
AYO AC/DC Breakdown Leakage & Ionisation Tester RM215L/2.....	£600

MARCONI DIGITAL FREQUENCY METERS	
Type 2430A 10MHz-80MHz.....	£125
Type 2431A 10MHz-200MHz.....	£130
MARCONI UNIVERSAL COUNTER TIMERS	
Type 2437 DC-100MHz.....	£175
Type 2438 DC-520MHz.....	£225

THORN PSU 0-40V; 0-50Amps Metered.....	£300
FARNELL PSU H6075 0-40V; 0-25Amps Metered.....	£400
FARNELL PSU L30E 0-30V; 0-5Amps Metered.....	£80
TELEQUIPMENT CT71 Curve Tracer.....	£250
MARCONI TF2700 Universal LCR Bridge. Battery.....	from £125
MARCONI TF2337A Auto Distort Meter 400Hz/1kHz 0.01%.....	£175
RACAL 9915 Freq Counter 10Hz-520MHz (Crystal Oven).....	£150
MANNESMAN TALLY Pixy 3 X Y Plotter. RS232.....	£100

## AVO MULTIMETERS

MODEL 8 or 9 (what's available).....	£40 each
Test Set No. 1 BX, 95X.....	from £45
8 Mk 5 with Carrying Case.....	£20
8 Mk 6 with Carrying Case.....	£120

All Meters Supplied with Batteries & Leads

## NEW EQUIPMENT

HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz Delay Timebase.....	£792
HAMEG OSCILLOSCOPE HM604 Dual Trace 60MHz Delay Sweep.....	£610
HAMEG OSCILLOSCOPE HM203.7 Dual Trace 20MHz Component Tester.....	£338
HAMEG OSCILLOSCOPE HM205.3 Dual Trace 20MHz Digital Storage.....	£610
All other models available - all oscilloscopes supplied with 2 probes	
BLACK STAR EQUIPMENT (P&P all units £5)	
APOLLO 10 - 100MHz Counter Timer Rate/Period/Time interval etc.....	£222
APOLLO 100 - 100MHz (As above with more functions).....	£325
METEOR 100 FREQUENCY COUNTER 100MHz.....	£109
METEOR 600 FREQUENCY COUNTER 600MHz.....	£135
METEOR 1000 FREQUENCY COUNTER 1GHz.....	£178
JUPITOR 500 FREQUENCY GEN 0.1Hz-500kHz Sine/Sq.....	£110
ORION COLOUR BAR GENERATOR Pal/TV/Video.....	£229
All other Black Star Equipment available	
OSCILLOSCOPE PROBES Switchable x1 x10 (P&P £3).....	£11

Used Equipment - With 30 days guarantee. Manuals supplied if possible.  
This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering.  
CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.



STEWART OF READING  
110 WYKEHAM ROAD, READING, BERKS RG6 1PL



Telephone: (0734) 268041. Fax: (0734) 351696. Callers Welcome 9am-5.30pm Mon-Fri (until 8pm Thurs).

CIRCLE NO. 131 ON REPLY CARD

# KESTREL ELECTRONIC COMPONENTS LTD

- ☆ All items guaranteed to manufacturers' spec.
- ☆ Many other items available.

'Exclusive of V.A.T. and post and package'


	1+	100+	1+	100+
<b>EPROMS</b>				
2764A-250	1.48	1.20	62256LP-100	3.00 2.15
27C64-150	1.65	1.25	62256LP-70	4.20 2.45
27C128-150	1.85	1.55	6264LP-100	1.50 1.35
27C28A-200	1.45	1.25	6116LP-100	0.75 0.65
27256-250	1.45	1.30	628128LP-80	12.60 11.50
27C256-200	1.85	1.45		
27C512-150	2.50	1.90	<b>DRAM</b>	
27C010-150	3.10	2.35	4164-10	1.00 0.81
			41256-100	1.05 0.85
<b>MODULES/SIMMS</b>			511000-100	3.40 2.85
256Kx9-70ns	11.60	8.30	514256-80	3.30 2.65
1Mx9-70 (3 chip)	27.60	23.60		

74LS, 74HC, 74HCT Series available  
Phone for full price list

All memory prices are fluctuating daily, please phone to confirm prices


**178 Brighton Road,  
Purley, Surrey CR8 4HA  
Tel: 081-668 7522. Fax: 081-668 4190.**

CIRCLE NO. 132 ON REPLY CARD

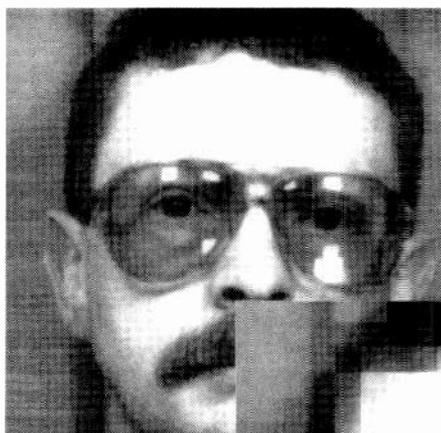

# Applying digital signal processing

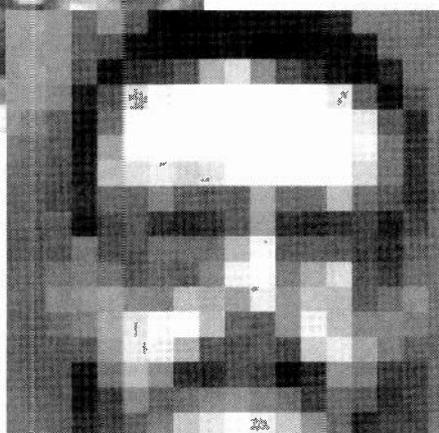**Digital signal processing (DSP) has become a growth area in the development of electronic systems. The low cost and availability of high performance digital signal processors has enabled the system designer to use many of the DSP techniques developed over a decade ago. Allen Brown examines a couple of the most widely used applications for the technique.**



**T**en years ago the execution of the Fast Fourier Transform was limited to main frames and mini computers. Today it is a standard algorithm run on all digital signal processors. The slow acceptance of digital signal processors over the past six years has been in part due to the difficulty of programming them in assembly language and the generally poor understanding of DSP algorithms.

Although many applications of digital signal processors are for real time systems where assembly language programming is usually a must, there are many applications where batch processing is the order of the day. This lifts the burden off the software because C can be used instead of assembly language.

As a programming high level language (HLL) C has increased in popularity over the past few years. There are several reasons for

this: all advanced microprocessors and digital signal processors have C compilers; C has become the defacto standard programming language; C is machine independent; it is easier to maintain and design for test a C program than an assembly language program; once a C program has been debugged and is functional then it is reusable, even if the target processors are upgraded; the application of software engineering methods is generally easier for code sourced in a HLL.

However the merit of C is only part of the equation. The target hardware characteristics also merit attention. The second generation of digital signal processors were mainly fixed point devices and many useful DSP algorithms coded in C require floating point precision and arithmetic. Although C compilers for these processors have provision for coping with floating point arithmetic (through the calling of subroutines) the resultant code is often excessively long and inefficient in using the processor's on-board resources. As a result, it is common place to avoid the use of floating point numbers when trying to implement DSP algorithms in C.

In general this is poor practice since the HLL code becomes fashioned for a restrictive class of target processors and would therefore not be ideally reusable. However with the recent appearance in the market place of several floating point digital signal processors (FP-DSPs) the appeal of coding DSP algorithms in C for non real-time applications has been enhanced greatly. The FP-DSPs which are currently available from the four main pro-

cessor manufacturers are given in Table 1. Each of the processors in the table has an optimised C compiler which naturally employs the architecture of FP-DSPs. The principal feature is the 32-bit by 32-bit floating point multiplier and accumulator (FP-MAC) which performs its calculation in a single clock cycle. The C compilers should therefore produce assembly language code which contains instructions relating to the FP-MAC thereby ensuring minimum assembly language code generation during the C compilation phase.

Many DSP algorithms have been coded in C and the availability of floating point devices opens up new opportunities for applying DSP techniques. A suitable text which contains many listings (complete with floppy disk) has been published by Embrée and Kimble [1].

**Applications**

The Discrete Cosine Transform (DCT) is a useful DSP algorithm for image storage and transmission. For image storage purposes, a compression of at 4:1 can be achieved with relative ease using the DCT.

An image is subjected to a DCT to produce a DCT image which is then compressed before storage. To recover the image, its stored DCT version is decompressed and the resultant image is subjected to an inverse DCT (i-DCT) thus producing a good rendition of the original image.

When discussing images one uses the concept of spatial frequencies. A spatial-frequency is related to the rate at which contrasts change. If one area is totally black and the adjacent area is totally white, then the spatial frequency on the boundary between the two areas is high. On the other hand if the adjacent area is dark grey, then the spatial frequency on the boundary between the black and the dark grey areas is low. Therefore when there are sharp contrasts, the spatial frequencies are high. However in most photographs and images the relative distribution of high spatial frequencies is low and this fact is used to

Manufacturer	Family and device Number
Texas Instruments	TMS320C30 TMS320C31 TMS320C40 (multiprocessing)
Analog Devices	ADSP-21020 ADSP-21010 (low cost)
AT&T	DSP32C DSP3210 (Multimedia processor)
Motorola	DSP96002

Table 1. Floating point digital signal processors from the four main manufacturers

determine the amount of data area allocated to each spatial frequency.

An image can be represented by a two dimensional set or an array of elements  $\{f[m,n]\}$ . The function  $f[m,n]$  is the intensity (or greyness) of the image at the coordinate m,n. Coloured images will consist of three elements for every coordinate m,n and these will give rise to three distinct arrays which are processed separately, one for each primary colour. In the following discussion only one array will be considered (monochrome) but the argument is applicable to colour images. On a screen the image would be made up from  $M \times N$  pixels (picture elements) and the Discrete Cosine Transform is defined (1) as:

$$F[u,v] = \frac{1}{NM} \sum_{m=0}^{M-1} \sum_{n=0}^{N-1} f[m,n] C_M[m,u] C_N[n,v]$$

where

$$C_M[m,u] = \cos \left[ \frac{(2M+1)u\pi}{2M} m \right]$$

In general the images (and their DCT) tend to be square therefore  $N = M$ .  $u,v$  are the spatial frequency variables (coordinates in the frequency domain) which have values ranging from 0, 1, ..., (N-1) and  $\{f[u,v]\}$  is the image result of performing the process in Equation 1. The i-DCT, which is the restored image is defined (2) as:

$$\hat{f}[m,n] = \frac{1}{N^2} \sum_{u=0}^{M-1} \sum_{v=0}^{N-1} F[u,v] c[u] c[v] C_M[m,u] C_N[n,v]$$

where,  $c[k] = 1$  when  $k = 0$  and 2 for all other values of  $k$ . Data compression can be achieved because of the large degree of redundancy in images. Normally each value of  $\{f[u,v]\}$  is stored as a byte. However much of  $f[u,v]$  contains very little information from the original image  $\{f[m,n]\}$  therefore a lot of  $\{f[u,v]\}$  is redundant and can be discarded.

How do we measure the information content of a set of pixels? One way is to measure the variance of  $f[u,v]$  over a set of images. If the variance is low then the information content is also low. When a DCT is performed on an image, the variance values tend to have a contour profiles as seen in Fig. 1. The variance tends to be a maximum for low index values

$(u,v)$  of  $\{f[u,v]\}$  and a minimum for large index values of  $f[u,v]$ . This is actually true for the majority of images. Therefore redundant data can be discarded by applying a discrimination quantisation scheme based on the variance profiles which is referred to as zonal coding. The quantisation value (number of bits used to store each pixel) depends on the index values of  $f[u,v]$ . Eight bits are allocated to store low index values of  $f[u,v]$  whereas the high index values are discarded completely (0-bit allocation) with graduated values between 8 and 0 for the intermedi-

ate indices. According to the zonal coding of Fig. 1 the distribution of quantisation levels is shown in Fig. 2. This is equivalent to low pass spatial filtering. Using this technique a compression ratio of the order of 4:1 can be achieved – an average 8-bit pixel can be compressed into 1.5 bits.

Having established a technique for image compression, the next hurdle is to implement efficiently the DCT. It is well known that the discrete Fourier transform (DFT) requires  $N^2$  calculations (where  $N$  is number of pixels) and when the Fast Fourier Transform is used the number of calculations is reduced to  $M \log_2(N)$ . When applied to the DCT the number of calculations is reduced from  $N^2$  to  $[N \log_2(N)]^2$ .

To implement a fast transform in 2-dimensions a block coding method is used such that an image  $\{f[m,n]\}$  can be divided into many sub-images of 16 X 16 pixels (the size of the zonal coding in Fig. 2) and the DCT and zonal coding is applied to each sub-image. When starting with an image of 256 X 256 pixels, by using block coding the improvement in speed is a factor 256. However the problem with this method is that, during the reconstruction, the sub-image boundaries become perceptibly visible thus degrading the appearance of the image. But for many applications (fax machines for example) the added degradation is acceptable.

For colour images this process is performed for each primary colour. It is quite possible to

code a fixed point digital signal processor using C to perform this image compression technique. However to ensure efficient compilation, it will be necessary to

remove all references to floating point numbers and divisions from the source code. In effect it will be necessary to tailor the code to the target hardware. By using a floating point DSP, this restriction is removed leaving the software engineer to use the full range of options offered by the ANSI C standard. Specific application areas where image compression can be used include the manufacture of fax machines which emphasise the fast transmission of images.

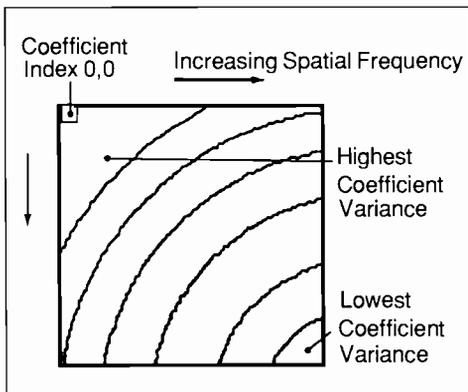


Figure 1 Zonal coding resulting from the application of the Discrete Cosine Transform on an image.


Continued over page

INTRODUCTORY  
PRICE JUST £179
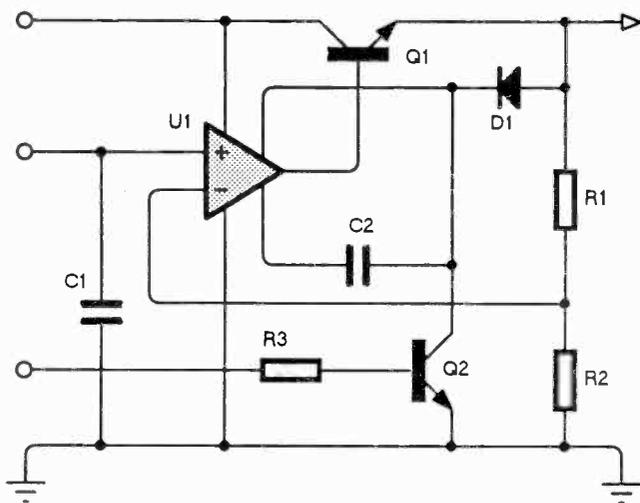
# SCHEMATIC DRAWING FOR WINDOWS

NEW

**ISIS ILLUSTRATOR** combines the high functionality of our DOS based ISIS products with the graphics capabilities of Windows 3. The result is the ability to create presentation quality schematics like you see in the magazines. ILLUSTRATOR gives you full control of line widths, fill styles, fonts, colours and much more. When the drawing is complete, transferring it your WP or DTP program is simply a matter of cutting and pasting through the Windows Clipboard.



## Features

- Runs under Windows 3.0 or 3.1.
- Full control of drawing appearance including line widths, fill styles, fonts, colours and more.
- Curved or angular wire corners.
- Automatic wire routing and dot placement.
- Fully automatic annotator
- Comes complete with component libraries; edit your own parts directly on the drawing.
- Full set of 2D drawing primitives + symbol library for logos etc.
- Output to Windows printer devices including POSTSCRIPT and colour printers.
- Loads ISIS SUPERSKETCH and DESIGNER files directly.

## ISIS - Intelligent Schematics

### ISIS SUPERSKETCH (from £69)

A superb entry level schematic drawing package offering all the editing features of ISIS DESIGNER but without the netlisting, bill of materials and electrical rules check features.

Extended device library available for an additional £30.

### ISIS DESIGNER (£275)

Provides all you need to create and edit schematics prior to further processing with ARES or other EDA software. Through the provision of user definable menu options and a special script language, ISIS acts as a 'framework' from which you can control all your CAD software.

### ISIS DESIGNER+ (£475)

This top of the range schematics package adds hierarchical design, automatic annotation/packaging, ASCII data import and Design Global Annotation to make it one of the most advanced schematics packages available for DOS.

## ARES - Advanced Routing

### PCB II (£69)

Our Graphical User Interface makes this PCB drafting package exceptionally easy to learn and use. Advanced features include Auto Track Necking, Gerber viewing, curved tracks, and DXF export.

### ARES (£275)

This package offers multi-layer, netlist based PCB design together with Power Plane Generation, EMS memory support and back-annotation to ISIS DESIGNER+.

### ARES AUTOROUTE (£475)

Adds a multi-strategy auto-router to ARES to provide the ultimate in design automation. Special strategy management features allow all design rules to be defined in ISIS so there is very little setting up to do.

Also available as **ARES 386** - a 32 bit version offering up to 400% faster operation, virtually unlimited design capacity and 1024x768 graphics support.

**Labcenter**  
E l e c t r o n i c s



Call us today on 0274 542868 or  
fax 0274 481078 for a demo pack.  
Combination, multi-copy and educational  
discounts available. Prices exc P&P and VAT.

14 Marriner's Drive, Bradford, BD9 4JT.

CIRCLE NO. 134 ON REPLY CARD

8	8	8	7	7	7	5	5	4	4	4	4	4	4	4
8	8	7	6	5	5	3	3	3	3	3	2	2	2	2
8	7	6	4	4	4	3	3	2	2	2	2	2	2	2
7	6	4	3	2	2	2	2	1	1	1	1	0	0	0
7	5	4	2	2	2	2	1	1	1	0	0	0	0	0
7	5	4	2	2	2	1	1	0	0	0	0	0	0	0
5	3	3	2	2	1	1	0	0	0	0	0	0	0	0
5	3	3	2	1	1	0	0	0	0	0	0	0	0	0
4	3	2	1	1	0	0	0	0	0	0	0	0	0	0
4	3	2	1	1	0	0	0	0	0	0	0	0	0	0
4	3	2	1	1	0	0	0	0	0	0	0	0	0	0
4	3	2	1	0	0	0	0	0	0	0	0	0	0	0
4	2	2	0	0	0	0	0	0	0	0	0	0	0	0
4	2	2	0	0	0	0	0	0	0	0	0	0	0	0
4	2	2	0	0	0	0	0	0	0	0	0	0	0	0
4	2	2	0	0	0	0	0	0	0	0	0	0	0	0

Fig. 2. In zonal coding, the variance zones are allocated different quantisation values. Most of the image information is contained in the low index (top left) values hence they have the quantisation values of 8-bits

CD-ROMs are essential components of Multimedia systems and efficient methods of image compression are vital. Although signal compression process outlined above can be performed by the 80486 CPU in a PC, the throughput would be unnecessarily slow. This type of intensive processing task is best off-loaded with relative ease to an auxiliary expansion card hosting a FP-DSP.

**Other uses**

Signal generation is another application well suited to FP-DSPs, in the realisation of a two phase quadrature oscillator based on recursive processing [2]. This can be represented by the expression (3):

$$R(n+1) = R(n)e^{j2\pi\alpha}$$

and

$$R(n) = C(n) + jS(n)$$

where the frequency is set by the phase factor  $2\pi\alpha$ . The frequency is given by  $f = \alpha/t_s$ , where  $t_s$  is the time for one iteration of the difference

equation given in Equation 2. Expanding Equation 3 gives two recursive equations (4):

$$C(n+1) = C(n)\cos(2\pi\alpha) - S(n)\sin(2\pi\alpha)$$

$$S(n+1) = C(n)\sin(2\pi\alpha) + S(n)\cos(2\pi\alpha)$$

which can implemented with relative ease in assembly language or in C as shown in Listing 1. If the program is executed on a fixed point processor (after tweaking to avoid the floating point calculations) there are problems. There is a slight growth in signal amplitude due to the round off effects. However when implemented on a FP-DSP directly, this effect does no occur on the same scale. Figure 3 shows the output of the algorithm in the form of a Lissajous Figure consisting of 512 data samples.

This algorithm can be used to great effect in several applications, some of these are: quadrature amplitude modulation (QAM) requires the generation quadrature signals of precision frequency and low harmonic distortion; generating the twiddle (phase) factor when excising an FFT; as a frequency generator with precision frequency and amplitude control.

When designing a DSP based system using a floating point processor, consideration should be given to the software engineering aspects together with savings in cost. This will necessitate careful attention to the advantages offered by C language compilers. The imminent announcement from the ANSI group of the new version of C especially devised for mathematical programming is an interesting development. Referred to as Numerical C, it is designed to deal with matrices and vectors. For example, to convolve two matrices, the following code would be used:

```
float a[100], b[100], c[100];
void vector_convolve() {
    c[:] = a[:] @@ b[:];
}
```

The new version of C will make DSP algorithm coding much easier and Analog Devices are in the process of producing a version called DSP/C for their ADSP-210xx processors and this will be reviewed in a later edition of EW + WW.

**References**

- [1] P M Embree & B Kimble, C Language Algorithms for Digital Signal Processing, Prentice Hall 1991.
- [2] R J Higgins, Digital Signal Processing in VLSI, Prentice Hall 1990.

**Listing 1**

```
/*Two phase quadrature oscillator */
#include<math.h>

#define PI 3.141592653
#define alpha 0.01 /* define the
frequency */
float C[2], S[2], cosine, sine;
main()
{
    cosine = cos ( 2 * PI * alpha )
    sine = sin(2 * PI * alpha);
    C[0] = 1.0;
    S[0] = 0;

    loop:
    C[1] = C[0]*cosine - S[0]*sine
    S[1] = C[0]*sine + C[1]*cosine;
    /* output C[1] and S[1] here */

    C[0] = C[1];
    S[0] = S[1];
    goto loop;
}
```

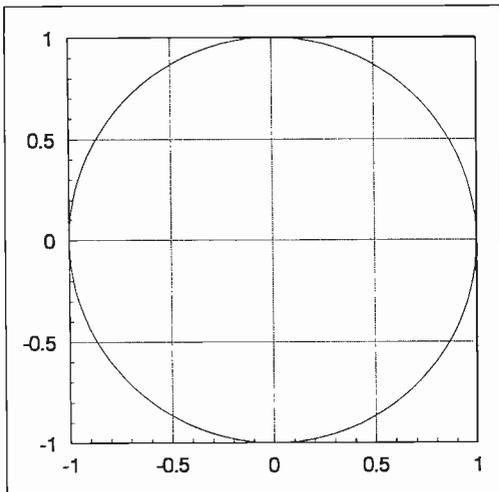


Fig. 3. Lissajous figure generated from combining the output from the quadrature algorithm Eq:4.

been recognised for specific elements of terminals, there has been neglect of the concept of a complete radio system design using these new techniques. Development of a systems architecture that would rationalise and enhance the optimal use of embedded processing is seen as offering benefits to system designers. A generic architecture was outlined that provides the benefit of linking the system performance independently so increasing computational power (both for the DSP devices and the general purpose computer host) as well as improving signal interface technology.

Professor J E Pearson (King's College London) presented a paper on behalf of Jianjun Wu and A H Aghvami on implementation of an IF adaptive equaliser for digital radio communications. The equaliser has already been shown to be capable of providing significant compensation for multipath selective fading and, by increasing the number of stages of the Bode bell network, being applicable to high-capacity digital radio communications systems. It is controlled by a micro-processor with improved Kalman algorithm to update the gain of the Bode networks. A four-stage Bode bell network equaliser has been implemented using parameters given by cad.

**DSP pros and cons**

At an IEE tutorial colloquium—"Circuit theory and DSP" earlier this year, Professor I. F Lind (University of Essex) reviewed the pros and cons of DSP. Among the advantages, he listed:

*Precision:* no drift with time; 32-bit floating point arithmetic available, an absolute repeatability from unit to unit.


*Versatility:* ability to perform both linear and non-linear functions; chips with a powerful instruction set.

*Limited time delay:* Whereas analogue coils and capacitors have a (theoretically) infinite memory of past events, a finite impulse response filter has a limited memory which may be useful in avoiding pattern dependent errors such as timing jitter.


*Linear phase:* can be achieved with FIR filters.

*One-way operation:* There is no unwanted effect on input samples from output values. Pitfalls include the need for support hardware (crystal clock, read-only-memory, A-to-D and D-to-A converters, power supply, shift registers, input and output conditioning filters). Also, to amplify an analogue signal by ten, the cost of support hardware is larger than that of a complete op-amp solution. Currently, analogue circuits work at higher speeds too, although DSP chips are improving, with higher clock frequencies and multi-action instructions.

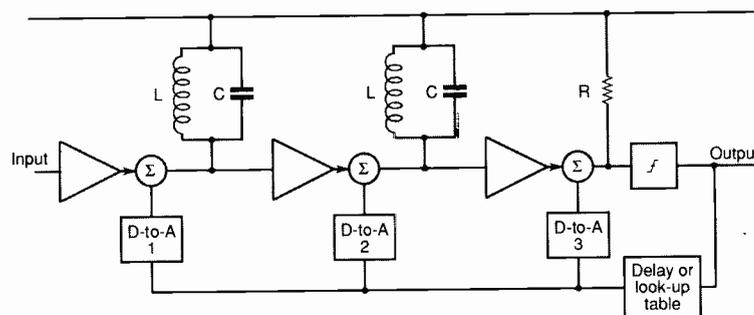Another drawback is that to achieve optimum performance from DSP, microcode must be used – which takes a long time to learn. A complicated system code can take months to write, is then difficult to change and the chip (and instruction set) may suddenly become obsolete. The delay time of an FIR filter (some 16ms with 256 taps) may present diffi-



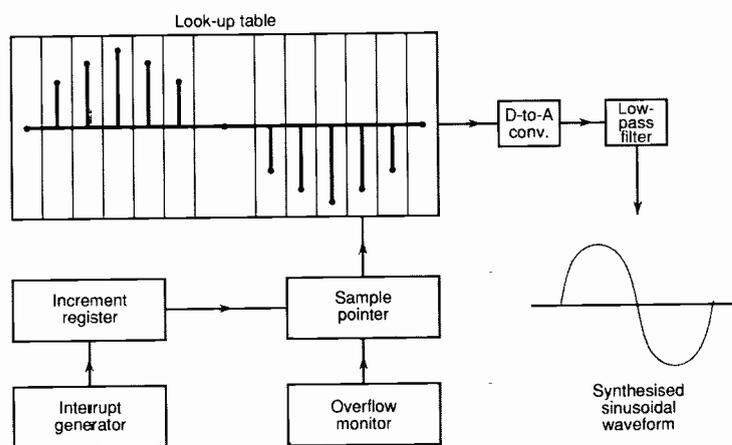*Practical implementation of a bandpass sigma-delta A-to-D converter (source A M Thurston and M O J Hawksford).*



*A flexible look-up table-based synthesiser for Piccolo-type data modem (source P D J Clark and M Darnell)*


culties for two-way speech.

But with the improved DSP chips now becoming available, the pluses can much exceed the minuses. Further benefits of DSP presented by Prof Lind included: time multiplexing enabling one DSP to be used as a multisection transmit filter, a multisection receive filter, and a peak detector circuit; noise immunity giving freedom from crosstalk, mains hum etc with perfect regeneration of noisy pulses; the increasingly-digital environment makes it natural to use DSP processing algorithms as additional system software.

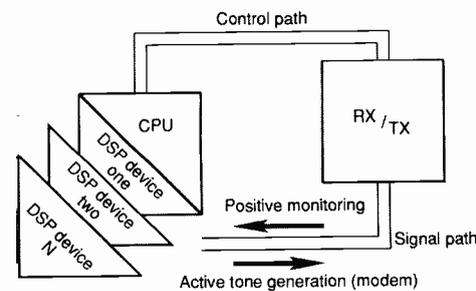**Cost/performance trade-off**

As DSP chips continue to evolve and become less costly a variety of cost/performance trade-offs are now available, making it possible to have several chips in a system working in parallel and opening new vistas for system designers. High-level software is improving – easing the design burden – and floating-point computation, increased speed, lower power consumption, lower cost, and more bits/data-word are all factors receiving attention of the chip designers.

Professor Maurice Bellanger (CNAM, Paris) stressed that virtually all forms of digital signal processing techniques can and will find application in communications and broadcasting (digital filters, filter banks, adaptive filters and vector quantisation-code represen-



*Proposed generic architecture for multi-functional terminal (source M Gallagher and M Darnell).*

tation where a set of signal samples are represented by a code). He concluded that: "The most striking point is the ever-increasing processing which is being considered for more and more diverse and demanding applications: speech coding, computer data compression, HDTV coding, hands-free telephony. While the technology is more and more ready to offer the necessary computation power, the designer has to cope with the complexity of operations. To handle these challenges successfully, the designer needs good computer-aided-engineering cae tools as well as regular contacts with current research in order to be aware of the latest results."

## Handier interfacing for data communication on the move

*In portable applications, the 25-way D-connector specified in RS232D is a distinct embarrassment. SN75C185 allows implementation of the DB9S nine-way D-connector*

### Developing the standard

RS232 was introduced by the Electronic Industries Association in 1962, originally as an attempt to standardise the interface between data terminal equipment (DTE), such as the serial communications port of a computer, and associated data communications equipment (DCE), eg a modem interfacing to a telephone line or whatever.

But, other applications were quick to adopt the standard and its use in PCs rapidly ensured that it became the industry specification for all low-cost serial interfaces between a DTE and a peripheral – mouse, plotter, printer etc. The C revision, RS2323C, appeared in 1969 and is still often referred to though it was superseded by RS232D in 1986. The revision largely brought it into line with CCITT V24 and V28, and with ISO IS2110.

In addition to defining line signal characteristics in terms of voltage levels, impedances and rates of change, RS232D also specified the mechanical interface as a 25-way D-connector.

Under the standard, a fully interlocked handshaking system controls the exchange

of information over the link. Some technologies – like communications using the HF band – never seem to die, despite repeated predictions of their imminent decease. The RS232 standard is a prime example: it just goes on and on, because it is so useful.

As a result, most semiconductor manufacturers produce ICs specifically designed to implement the interface, in place of the discrete component interface circuits originally used.

The SN75C185 is particularly aimed at size/cost/weight/power consumption sensitive applications such as hand-held test and medi-

cal equipment, and laptops. In these applications, the size of the 25-way D-connector specified in RS232D (see box) is a distinct embarrassment, and a *de-facto* standard has grown up around the DB9S nine-way D-connector. The SN75C185 provides just the driving and receiving elements needed to implement this version of the RS232D interface. Built-in circuitry provides 30V/μs limiting for the transmitters and lowpass input filters reject spikes and impulsive noise for the receivers.


Figure 1 shows the device's three transmitters and five receivers connected to a nine-pin D connector, and indicates clearly the simple

of information over the link.

V24 defines many more lines than RS232D, but those that are common are compatible, and few practical applications use, or even implement, all of the lines, the most commonly used being listed in Table 1.

Characteristics of the signals over the communication link – an unbalanced line – are summarised in Fig 1. Note that while RS232C specified a maximum line length of 15m, RS232D does not specify a maximum length. Instead, a maximum cable capacitance for any line of 2500pF is specified. Assuming a typical 150pF/m, the specification comes to much the same thing. With this length of line and given the specified maximum data rate of 20kb/s

**Fig. 1. Electrical details of the 232D. Maximum data rate 20kb/s; max cable length depends on capacitance; single ended system; receiver input impedance  $R_T=3-7k\Omega$ ; driver power-off impedance  $R_S>300\Omega$ ; load capacitance  $<2500pF$ ; output rise/time falls within the transition region: 1ms below 40b/s, 4% of pulse duration (50%) 40 to 8000b/s and  $5\mu s >8000b/s$ ; slew rate 30V/μs max.**

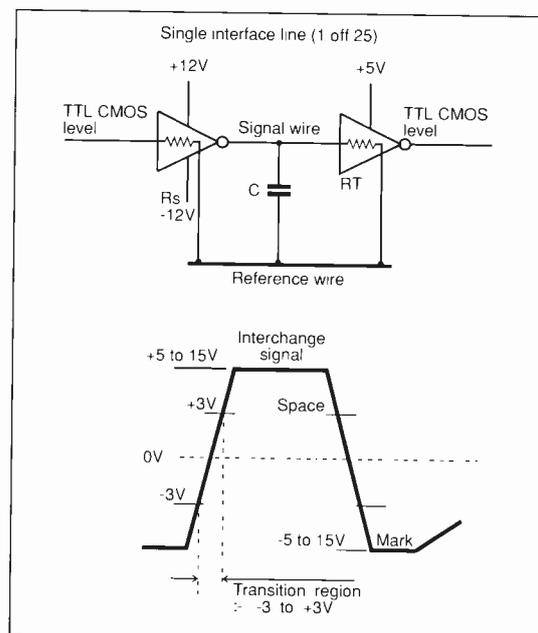

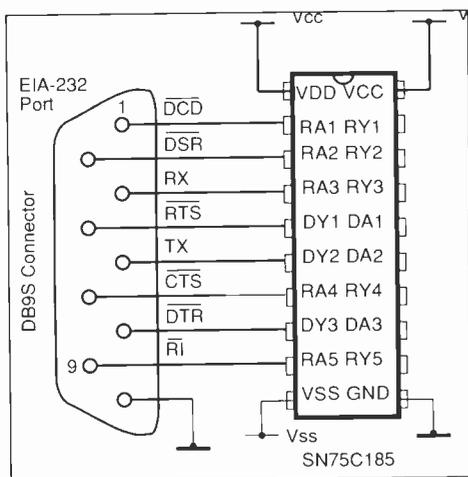


Fig. 1. SN75C185's three transmitters and five receivers connect to a nine-pin D connector. Simple interfacing is provided by the flow-through pin-out architecture.

interfacing provided by the flow-through pin-out architecture. A quick check on how the device operates is made possible by the fact that the drivers and receivers are inverting (Fig. 2). Logic 1 becomes a negative level on the line and a logic 0 a positive level (perhaps dating back to the days of holes and lack of them, in perforated paper tape). Connecting the three drivers in series with three of the receivers and then closing the loop back to the

input of the first via one of the spare receivers (Fig. 3) puts the output of a receiver at logic levels, nominal ground or +5V. One receiver will quite happily drive another because, with its single +5V supply, the receiver's threshold voltages are typically +2.1V and +1.0V (positive-going and negative-going respectively, the 1V or so of hysteresis providing additional noise rejection to supplement that provided by the input lowpass filter).

The resultant odd number of inversions round the loop represents negative feedback, acting to make the devices all sit half-on and half-off. But the propagation delay round the loop ensures that the loop phase shift is way in excess of 180° at the frequency at which the loop gain has fallen to unity. In other words, we have a ring oscillator.

Figure 4 shows the output of line driver three at pin eight; the frequency of oscillation is 31kHz. With 3000pF capacitors from each driver output to ground (in lieu of the rated 2500pF maximum capacitive load), the edges slow down and as a result, the oscillation frequency is pulled down to 21.7kHz (Fig. 5). However, for both positive and negative going edges, the transition time through the ±3V range is a shade over 1.5µs, easily meeting both the RS232D and -C specs at 20kb/s and, with the rated 2500pF rather than 3000pF, doubtless also the 1.5µs V28 spec. The SN75C185 is only one of a range of RS232D interface devices available from the same

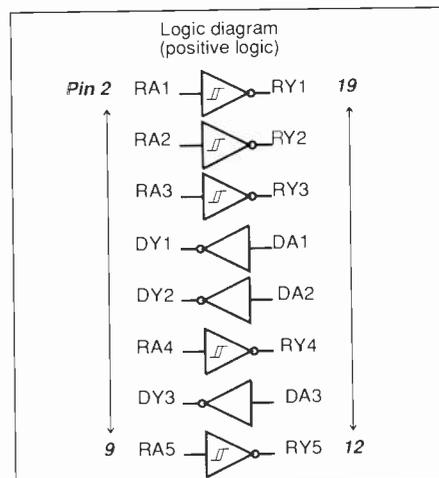


Fig. 2. A quick check on how the device operates is made possible by the fact that the drivers and receivers are inverting.

Fig. 4. TX and RX waveforms of a ring oscillator.

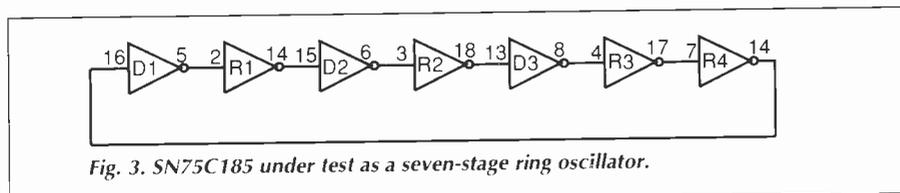
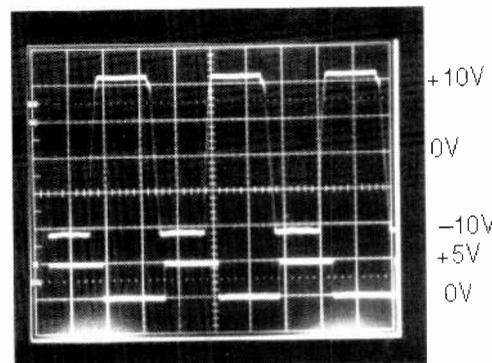


Fig. 3. SN75C185 under test as a seven-stage ring oscillator.

Table 1. RS232 signal designations.

Designation	DB25S	Common usage
Signal ground	SG Pin 7	Interface ground reference
Signal out	SOUT Pin 2	From the DTE to the DCE
Signal in	SIN Pin 3	From the DCE to the DTE
Request to send	RTS Pin 4	DTE informing the DCE it wants to transmit. Also used to control direction of communication in half-duplex system
Clear to send	CTS Pin 5	DCE informs the DTE that the DTE may transmit. This is usually in response to a RTS and its own ready condition
DCE ready	DSR Pin 6	The DCE informing the DTE that it is connected to a communications channel and all dialling, talking, testing etc is over. (Also called data set ready.)
DTE ready	DTR Pin 20	The DTE informing the DCE that it is ready to transmit or receive data
Received line signal detector	DCD (Pin 8)	The DCE informing the DTE that it is receiving valid signals over the channel. Sometimes called carrier detect
Ring indicator	RI (Pin 22)	The DCE informing the DTE that a ringing signal is being received on the communication channel. (Used in auto-answer systems)

(more likely 19.6kb/s in practice), reflections are not a significant problem. So the line's characteristic impedance is not specified and terminating resistors are not used.

Traditionally, to meet the specified minimum driver output swing of ±5V, the output stage uses +12V and -12V supplies. But a single +5V supply suffices for the receiver, even though, in principle, positive and negative supplies would permit a slightly greater noise immunity margin.

V28 specifies that for data lines, the time taken for the line voltage to pass through the ±3V transition region should not exceed 1ms or 3% of the nominal element period, whereas RS232C and -D both specify 1ms or 4% (or 5µs above 8kb/s, in the case of RS232D). Any device meeting the V28 spec will easily meet both RS232C and -D.

Transition time should not exceed 1ms for control signals, but for all signals, the minimum transition time (200ns) is set by the maximum permitted slew rate of 30V/µs, to minimise crosstalk and radiation.


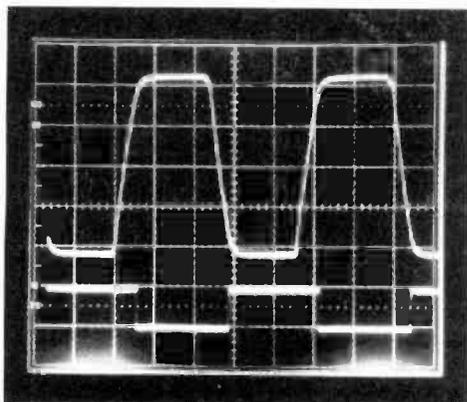


Fig. 5. TX and RX waveforms with 3000pF loading on each TX output, pins 5, 6 and 8.

manufacturer. The SN75C198/189 ICs are four line drivers and receivers offering unusually low dissipation when driving a fully loaded RS232D interface, while the SN75186 is a really bomb-proof device with some extra very useful facilities. The 186 will withstand a short from a ground referenced + or -30V supply to any of its EIA RS232 input or output pins, and furthermore has an ESD (electrostatic discharge rating) in excess of 4000V when tested per MIL-STD-883C (method 3015). Four transmitters and four receivers – all conforming to V28 and RS232D – 30V/ $\mu$ s driver slew-rate-control and preset 1 $\mu$ s receiver filtering are all included on chip.

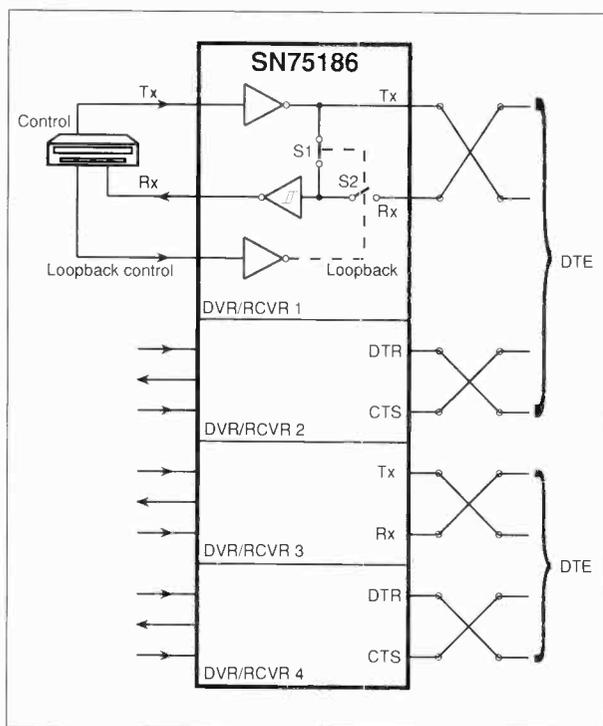

The extra plus is loop-back control, permitting any receiver to be disconnected from the incoming line and patched to the TX output of its associated transmitter by a loop-back control-input pin. So fault-finding routines can be built in, using the intelligence available in

the standard compared to some of the naughty (non-)implementations of RS232 that exist.

Some cut-price versions even dispense with the negative-going aspects entirely, relying on the fact that the receiver thresholds are both positive.

Fig. 6. SN75C185 incorporates a loop-back test facility, providing a powerful diagnostic test.

an associated DTE (Fig. 6).

These Texas Instruments ICs can be used with voltages other than the usual + and -12V  $V_{dd}$  and  $V_{ss}$  supplies. For example, + and -5V can be used, permitting  $V_{dd}$  to be common linked with the +5V  $V_{cc}$  rail used to power the receivers. Of course, the TX outputs can not then quite meet the RS232D specified +5V to +15V and -5V to -15V space and mark level voltages. But at  $\pm 4.5$ V typical ( $\pm 4$ V min) they come close. Indeed, this represents a very minor departure from

## Many Radio Amateurs and SWL's are puzzled. Just what are all those strange signals you can hear but not identify on the Short Wave Bands? A few of them such as CW, RTTY, Packet and Amtor you'll know – but what about the many other signals?

Hoka Electronics have the answer! There are some well known CW/RTTY decoders with limited facilities and high prices, complete with expensive PROMS for upgrading etc., but then there is CODE3 from Hoka Electronics! It's up to you to make the choice – but it will be easy once you know more about Code3. Code3 works on any IBM-compatible computer with MS-DOS 2.0 or later and having at least 640k of RAM. The Code3 hardware includes a digital FSK Converter unit with built-in 230V ac power supply and RS232 cable, ready to use. You'll also get the best software ever made to decode all kinds of data transmissions. Code3 is the most sophisticated decoder available and the best news of all is that it only costs £299!

- Morse – Manual/Auto speed follow. On screen WPM indicator
- RTTY/Baudot/Murray/ITA2/CCITT2 plus all bit inversions
- Sitor – CCIR 625/476-4, ARQ, 5BRS/CBRS FEC, NAVTEX etc
- AX25 Packet with selective call sign monitoring, 300 Baud
- Facsimile, all RPM/IOC (up to 16 shades at 1024x768 pixels)
- Autospec – Mk's I and II with all known interleaves
- DUP-ARQ Artrac – 125 Baud Simplex ARQ
- Twinplex – 100 Baud F7BC Simplex ARQ
- ASCII – CCITT 6, variable character lengths/parity

- ARQ6-90/98 – 200 Baud Simplex ARQ
- SI-ARQ/ARQ-S – ARQ 1000 simplex
- SWED-ARQ/ARQ-SWE – CCIR 518 variant
- ARQ-E/ARQ1000 Duplex
- ARQ-N – ARQ1000 Duplex variant
- ARQ-E3 – CCIR 519 variant
- ARQ6-70 – 200 Baud Simplex ARQ
- POL-ARQ – 100 baud Duplex ARQ
- TDM242/ARQ-M2/M4-242 – CCIR 242 with 1/2/4 channels

- TDM342/ARQ-M2/M4 – CCIR 342-2 with 1/2/4 channels
- FEC-A – FEC 100A/FEC101
- FEC-S – FEC1000 Simplex
- Sports info. – 300 Baud ASCII F7BC
- Hellsreiber – Synch./Asynch
- Sitor RAW – (Normal Sitor but without synchronisation)
- F7 BBN – 2-channel FDM RTTY

COMING SOON: Packtor

All the above modes are preset with the most commonly seen baudrate setting and number of channels which can be easily changed at will whilst decoding. Multi-channel systems display ALL channels on screen at the same time. Split screen with one window continually displaying channel control signal status e.g. Idle Alphas/Beta/RQ's etc., along with all system parameter settings e.g. Unshift on space, Shift on Space, multiple carriage returns inhibit, auto receiver drift compensation, printer on, system sub-mode. Any transmitted error correction information is used to minimise received errors. Baudot and Sitor both react correctly to third shift signals (e.g. Cyrillic) to generate ungarbled text unlike some other decoders which get 'stuck' in figures mode!

Six Options are currently available extra to the above standard specification as follows: 1) Oscilloscope. Displays frequency against time. Split screen storage/real time. Great for tuning and analysis. £29. 2) Piccolo Mk 6. British multi-tone system that only we can decode with a PCI £59. 3) Ascii Storage. Save to disc any decoded ascii text for later processing. £29. 4) Coquelet – French multi-tone system, again only on offer from Hoka! £59. 5) 4 Special ARQ and FEC systems i.e. TORG-10/11, ROU-FEC/RUM-FEC, HC-ARQ (ICRC) and HNG-FEC. £69. 6) Auto-classification. Why not let the PC tell YOU what the keying system is? £59.

### NEW VERSION 4.00 JUST RELEASED – Now with improved user interface and even more features!

Please add £5 to the above prices for Carriage by fully insured First Class postal delivery (default mode).

Call or write for our comprehensive information leaflet – there is just not enough room here to tell you everything about Code3! Professional users – please ask about our new CODE30 DSP unit available soon! (Piccolo down to -12dB S/N!!!). Prices start from £1250.

**HOKA ELECTRONICS (UK)**  
26 Bury Road, Shillington, Hitchin, Herts., SG5 3NY  
Phone (0462) 711600 or Fax (0462) 711769

CIRCLE NO. 135 ON REPLY CARD

# REGULARS

NEW PRODUCTS CLASSIFIED

## ACTIVE

### Asics

**Cmos 3 $\mu$  prototyping.** For several years, Mietec Alcatel has run a low-cost prototype service for 2 $\mu$  cmos, using the multi-project method of processing several devices on one wafer. The method is now available for 40V and 100V bicmos devices, providing low cost since masks and fabrication are shared between several projects; low lead time; flexibility of design and manufacture in the same environment as for volume production. High-voltage bicmos gives 150gates/square mm; 18V cmos, 40V bipolar and 100V dmos; mixed analogue and digital circuits; and 320pF/mm<sup>2</sup> for the thin oxide capacitors. Mietec Alcatel, +33 146 32 53 86.

**Fast 3V gate arrays.** Gate delays of 0.21ns (about the time it takes a ray of light to travel 2.5 inches), are obtained in Toshiba's new sea-of-gates arrays, which use the dram-type 0.5micron cmos process. The TC180G series uses a 3.3V supply, the new standard, and consumes 65% less power than 5V types. 800,000 raw gates are available (560,000 usable gates) and the cell library is compatible with the earlier TC163G series of arrays. Orders are being taken from September 1992.

### A-to-D & D-to-A converters

**PCM audio D-to-A.** A new member of Analog's Soundport family is the AD1866, a stereo 16-bit PCM audio D-to-A converter operating from one 5V supply and needing only a few externals. It has two independent references, output amplifiers and converters and DC bias pins position the output signal at 2.5V to eliminate the need for false-ground circuitry. Distortion plus noise at 990.5Hz is between 0.005% and 2% for inputs of 0dB to -60dB. Dynamic range is 90dB and channel separation 115dB. Analog Devices, 0932 253320.

**Low-power A-to-Ds.** Crystal Semiconductor have a new family of 1.5mW (50 $\mu$ W standby) 16-bit and 20-bit analogue-to-digital converters, CS5505/6/7/8, intended for use in low-frequency measurements or where low power consumption is needed. No integrating capacitors are needed, so the devices are suitable

for intrinsically safe working. The delta-sigma oversampling technique is used to give better performance than found in V-to-F converters or the multi-slope integrating type. Special attention has been paid to line-frequency elimination. Sequoia Technology Ltd, 0734 311822.

### Discrete active devices

**Transient suppressor.** SA series transient voltage suppressors protect equipment against spikes from 5V to 170V. These are glass passivated chip junction devices with a surge capability of 500W at 1 $\mu$ s and a response time from zero to minimum breakdown voltage of less than 1ps. Steady state power derating is 5W and operating temperature is -65 to 175°C. General Instrument (UK) Ltd, 0895 272911.

**RF power transistors.** Philips's BLV101A and B are chip transistors with input and output matching networks for operation at 800-900MHz and 900-960MHz respectively. Both are high-gain n-p-n types delivering 50W at 960MHz and at over 50% efficiency. Power gain for the A version is 8.5dB minimum at 900MHz and 7.5dB at 960MHz for the B. Collector/emitter rating is 26V. Philips Semiconductors Ltd, 071 436 4144.

**Beefy transistor.** Zetex has a new version of the Super E-line transistor, the ZTX688, which has a saturation voltage of 0.35V maximum at 3A and a minimum gain of 400; at 0.1A, saturation voltage is 0.04V - Jp to four times lower than a darlington. Peak current is 10A, at which gain is 100, while power dissipation is 1.5W free-standing. Transition frequency is 150MHz. Zetex plc, 061 627 4963.

### Linear integrated circuits

**Temperature sensor.** Seiko's S-8100B cmos temperature sensor comprises the sensor, a constant-current circuit and an op-amp, all on the same chip, to give a linear output voltage of -8mV/K. Operating voltage is 3V-5.5V, repeatability  $\pm$ 0.3% and temperature range -40 to 100°C. Linearity is claimed to be much better than in other types such as thermistors. Amega Electronics Ltd, 0256 843166.

**VCOs.** Fujitsu's D300 series of voltage-controlled oscillators are meant for use in satellite receivers, CD players and digital audio tape machines. The oscillators conform to EIAJ standards and use a single lithium tantalate crystal, which offers a frequency variability of 0.1% and 100

times better stability than LC or TTL IC VCOs. Fundamental oscillation frequency lies in the 4-30MHz range, three sampling frequencies of 32kHz, 44.1kHz and 48kHz being selectable by cmos logic levels. Fujitsu Microelectronics Ltd, 0628 76100.

**Video amplifier.** Linear's LT1227 current-feedback video amplifier has a 140MHz bandwidth, diff gain of 0.01% and diff. phase of 0.01°. Output current is 30mA. With a supply voltage range of  $\pm$ 2V to  $\pm$ 15V at 10mA, slew rate is 1100V/ $\mu$ s. A shutdown pin switches the amplifier into a high-impedance mode with a supply current of less than 200 $\mu$ A, which allows several devices to be parallel connected and selected by a logic level in 4 $\mu$ s. Linear Technology (UK) Ltd, 0276 677676.

**Tunable LP filters.** Maxim's MAX291/2/5/6 are eighth-order, switched-capacitor low-pass filters, which are tuned by the frequency of the clock. The 291 and 295 exhibit a Butterworth profile and the other two a Bessel type. Ratio between corner frequency and clock is 100:1 for the 291/2 and 50:1 for the 295/6, so that tuning ranges of 0.1Hz-25kHz and 0.1Hz-50kHz are available. Alternatively, an external clock can be used, for example for a swept characteristic. An inverting op-amp is provided for use as a low-pass post or anti-alias filter. Maxim Integrated Products Ltd, 0734 845255

**Frequency generators.** All the many clock frequencies needed on a large motherboard can be supplied by an Avasem frequency generator IC. A reference frequency drives PLL circuitry, the division ratios being stored in rom, so that different frequencies are derived from the same reference. The range includes a device with seven clock frequencies for VGA displays and LCDs and motherboard type with four clock generators and eleven output clocks, selected from mask-programmed

frequencies. Microelectronics Technology, 0844 278781.

**Small voltage reference.** New voltage references from National Semiconductor, the LM4040 family, are accurate to within 0.1% and come in the SOT-23 pack. Curvature correction provides an output voltage drift of around 20ppm/degC over the full -40°C to 85°C operating range and output noise is about 35 $\mu$ V RMS. No external stabilising capacitor is needed. Outputs in the family are 2.5V, 4.096V, 5V, 8.192V and 10V. National Semiconductor, 0793 697 428.


**Frequency synthesiser.** UMA1014T from Philips is a low-power synthesiser meant for use in cellphones, pagers and the like and forms part of the new chipset for mobiles. It includes prescalers and programmable dividers, with a view to avoiding the problems of interfacing with external circuitry: the phase/frequency comparator is on-chip. Comparator output settles rapidly and needs very little filtering before the VCO and, since charge-pump current is stable, few external components are needed. Active and powered-down current requirements are 13mA and 2.5mA. Philips Semiconductors Ltd, 071 436 4144.

### Logic building blocks

**Fast, dense fifo.** Running at 40MHz, the Am7205A cmos first-in-first-out memory is claimed to be the only 8K by 9 fifo with an access time of 15ns. It also, AMD says, has the lowest operating current in the industry and provides empty, half-full and full flags. Advanced Micro Devices UK Ltd, 0483 740440.

**35V LCD drivers.** H18010/20/40 from Holt Integrated Circuits are cmos display drivers which drive dichroic and twisted-nematic LCDs and vacuum fluorescent displays of up to 35V at 2MHz. They are cmos and

**Oscillators.** Four new clock oscillators are on offer by AVX. HC1 is a cmos device compatible with cmos or TTL circuitry and with an enable/disable pin; EH is designed to withstand mechanical shock and offers a frequency accurate to within 100ppm from 0-70°C; K680S produces a direct drive for the Motorola MC68040 microprocessor, for which it generates a stable symmetry with temperature; and 386-HC is for use with the Intel 80386 microprocessor. AVX Ltd, 0252 336868.

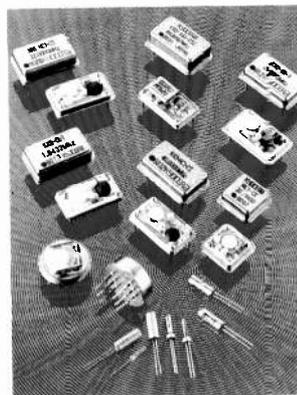

TTL compatible and need only clock, data in and load inputs. *HI8010/20* drive up to 38 segments and the *HI8040* up to 85, the latter also having test inputs for display testing, optional negative display voltage converter and a fail-safe circuit. Britcomp Sales Ltd, 0372 377779.

**Data comms controller.** Providing transfer rates of up to 12Mb/s at 16.7MHz, the *HD64570* serial communications adaptor from Impulse carries out protocol processing for lan servers, gateways, multiplexers, PBXs and modems. Its two-channel, multi-protocol, serial comms interface supports a range of comms protocol modes, including asynchronous, byte synchronous and bit synchronous modes such as HDLC and SDLC. Fifo buffers in the interface are 32byte deep. Impulse Electronics, 0883 347011.

**Rapid comparators.** Single and dual comparators from Maxim, the *MAX905* and *MAX906*, offer a 2ns data-to-clock setup, are edge-triggered and ECL-compatible. Architecture is of the master/slave type for oscillation-free, 3mV resolution and propagation delay of 2ns for 500MHz clocking. Analogue and digital power lines are separate; requirement is either  $\pm 5V$  or one negative supply. The *MAX906* is the dual version. Maxim Integrated Products Ltd, 0734 845255.

**3.3V logic.** Semiconductor announces a range of 3.3V logic devices designed for a low noise signature. The Low Voltage Quiet (LVQ) devices are in CMOS and consists of gates, multiplexers, flip-flops and octal transceivers, intended for battery-powered computing equipment. It is estimated that a typical notebook computer motherboard in LVQ will draw about 4W against the usual 8W. Devices are said to generate up to 20% less EMI than other 3V logic. National Semiconductor, 0793 697 428.

## Microprocessors and controllers

**200ns microcontroller.** Single-cycle, single-word instruction times of 200ns and an i/o speed of up to 5MHz give the Microchip *PIC16C5X* device a speed of up to ten times that of other 8-bit microcontrollers. As an example, these units will generate high-speed PWM in software for motor control and can transmit and receive data at 1MHz. They are available with up to 80 by 80 ram and 2K by 12 eeprom. Arizona Microchip Technology, 0628 850303.

**Fast Zilogs.** Speed increases for the Zilog *Z80180* and *Z80181* microprocessors are from 12.5MHz to 15MHz and from 10MHz to 12.5MHz respectively. *Z80180* is based on an enhanced *Z80* and includes memory management, two DMA controllers, two uarts, two 16-bit timer channels

and an oscillator. *Z80181* is the *Z80180* with one channel of the *Z85C30 SCC*, two 8-bit parallel ports and a pair of memory-configurable ram and rom chip-select pins. Gothic Crellion Ltd, 0734 788878.

**8-bit microcontroller.** *K4* is a new member of the Motorola *MC68HC11* family of microcontrollers and is an eeprom-based, high-speed, low-power type running at up to 4MHz. It has power-saving stop and wait modes, 24Kbyte of eeprom, 640byte of eeprom and 768byte of ram. 512Kbyte of memory is available by means of memory-mapping logic on-chip. *K4* comes in either eeprom or one-time-programmable form. Macro Group, 0628 604383.

## Mixed-signal ICs.

**Analogue multiplexer.** 12-bit settling times of 17ns to within 0.1% and an adjustable noise bandwidth make the *CLC532* 2:1 analogue multiplexer from Joseph suitable for use in IR imaging, CCD, HDTV and radar application. Channel isolation is better than 80dB at 10MHz and harmonic suppression 80dBc at 5MHz. Other features include a noise level of 32 $\mu$ V RMS from 0 to 100MHz, diff. gain and phase of 0.01° and 0.05% and a slew rate of 130V/ $\mu$ s. Joseph Electronics Ltd, 021 643 6999.

**ADPCM codec.** Motorola's *MC145540* adaptive differential pulse-code modulated codec is now available and is meant for digital cordless telephone use in which it offers a 2.7V-5.25V supply range and 65mW dissipation at 3V. The device encodes analogue signals to digital ADPCM form at bit rates of 32, 24 or 16kb/s or to PCM at 64kb/s, simultaneously decoding digital code back to analogue. An evaluation board, the *MC145537EVK*, is also available. Motorola Ltd, 0908 614614.

## Programmable logic arrays

**85MHz FPGA.** Actel's *A1225-1* is a 2500-gate field-programmable gate array with a 75MHz system speed and enables the design of 16-bit counters working at 85MHz. It is claimed to be the fastest 2500-gate FPGA available and can be designed and programmed by the Actel Action Logic system (new version available). Actel Europe Ltd, 0256 29209.

## Power semiconductors

**Frugal DC converter.** For application where 50mA at 5V is needed, Linear's *LTC1046* replaces *ICL7660* ICs pin-for-pin, using only 300 $\mu$ A of supply current. Output impedance is one third that of the *ICL7660* and output drive is 2.5 times greater. Supply voltage is 1.5V-6V and there is a boost pin to allow a higher conversion frequency. Power conversion is 95% efficient. Linear Technology (UK) Ltd, 0276 677676.

**Step-up converters.** MAX731/2/3/5 form a new series of current-mode PWM step-up converters which are meant for small and 80%-95% efficient power supplies. Inputs are between 2V and 4V, outputs either 125mA or 200mA at 5V, 12V, 15V or adjustable from 2.7V to 15.75V. All have a logic-compatible shutdown pin that reduces quiescent current to 6 $\mu$ A. PWM pulse-width current-mode operation is at 170kHz. Maxim Integrated Products Ltd, 0734 845255



## Passive components

**Video filters.** Range of RF and video filters from Active Labs in di and sil packages are phase and amplitude equalised, with high attenuation in the stop band. *Sinx/x* correction for D-to-A processing is incorporated. This range is for low-pass filtering, but other configurations are available. The company provides a specification chart for ease of ordering. Active Electronic Labs, Ltd, 0926 484050.

**SM resistor network.** 20-pin, surface-mounting resistor network from Bourns is meant to provide balanced IC terminations or improved damping when used with memories and comes in isolated-resistor, bussed-resistor or dual-termination forms. The *4820P* is in EIA SOGN-0002 pack and resistance range is from 10 $\Omega$  to 1M $\Omega$ . Bourns Electronics Ltd, 0276 692392.

**Sealed rotary switch.** Rotary switches in the Grayhill series *50/51* feature a range of throw angles in one device, the choice being 35°, 45°, 60° or 90° in the series *50* and 30° in series *51*. They are 0.5in in diameter and are completely sealed, with shaft grounding to assist shielding. Four poles are available on each deck, with up to 12 positions per switch. Highland Electronics Ltd, 0444 245021.



**Radio data modem.** *RM1200* is a single-unit UHF FM synthesise transceiver, which incorporates a 1200b/s FFSK baseband modem. It operates in bands from 430MHz to 468MHz, putting out 500mW in half-duplex mode. Its serial data interface allows data interchange at clock speeds up to 1MHz and facilitates control functions such as channel, power level and signal strength indication. Radio Data Technology Ltd, 0376 501255.

**Miniature chip Cs.** Murata's range of chip capacitors now includes 200pF Class I and 33nF Class II components in the *0402* size and 750pF Class I and 220nF Class II types in the *0603* size. All have nickel-barrier terminations to prevent solder leaching. *0402* capacitors measure 1 by 0.5mm to give a mounting density of 70 per square centimetre, that for the *0603* size being 35. Working voltages are in the 16-50V range. Murata Electronics (UK) Ltd, 0252 811666.

## Displays

**Led lamps.** China Semiconductor Corporation now offer a range of led lamps in addition to their led displays. There round types from 2mm to 10mm diameter and rectangular ones from 5mm by 1mm to 8mm by 8mm, with superbright and bi-colour types as well as the standards. CSC also provide a custom design service. Clere Electronics Ltd, 0635 298574.

## Instrumentation

**'Scope into spectrum analyser.** By means of Thurlby-Thandar's *TSA250* adaptor, an ordinary oscilloscope becomes a spectrum analyser whose centre frequency is adjustable over the range 400kHz-250MHz and is digitally displayed. Scan width and rate can be adjusted over the range; amplitude range is -70dBm to 0dBm. B K Electronics, 0702 527572.

**Real-time spectra.** PC-hosted spectrum analyser by Bores displays data in time and frequency domains, auto and cross-correlation and transfer function measurement, with sample rates to 50kHz on dual channels - 400kHz as an option. Stimuli for transfer function and frequency response measurement are generated in real time and include pure tones and flat random noise, synthesis and analysis being carried out simultaneously. System is capable of updating by development kits and associated software. Bores Signal Processing, 0483 740138.

**EMI testing.** Chase's EMI Signature Scope allows manufacturers to examine the noise output of their products. *ESS7500* is connected to a standard oscilloscope with a low-cost

line network to display the noise signature in the range 3kHz-30MHz. A broad-band field probe is also available. Up to fifteen limit lines can be set to give an alarm if they are exceeded. Chase EMC Ltd, 081 878 7747.

#### Lightweight FFT analyser.

Diagnostic Instruments's *PL202* fast Fourier analyser offers a frequency up to 40MHz, 1Mbyte static ram and up to 80 times zoom; it will dump to a printer via *RS232* and stores data for review—and yet it weighs only 3kg. For acoustics, full and third-octave analysis with A weighting is available; for transients, there is comprehensive triggering; in vibration, the integral spectrum process is used with directly connected accelerometers; and in machinery analysis, orbital plots are standard. Chase Electronics Ltd, 081-878 7747.

**Windows oscilloscope.** In conjunction with a PC running *Windows 3*, the Nicolet Multipro is a multi-channel waveform analyser, with its display on the PC screen. Triggering has received much attention, since it is often necessary to record once-only and highly expensive events and a missed or false trigger would be a catastrophe. The *Windows* data is portable to other programs such as spreadsheets, word processors and the Nicolet *Famos*, which is a set of waveform-processing utilities. Memory length is 3Mwords/channel for occasions when event timing is indeterminate. Systems range from a seven-slot tower to a 500-channel rack. Nicolet Instruments Ltd, 0926 494111.

**RCL meter.** In less than one second, the Philips *PM6303A* resistance/capacitance/inductance meter indicates the value of the component to within 0.25% and provides the component dimension and one of seven equivalent circuit diagrams. If the component is totally unknown, a "green" button gives an immediate display of dominant value (R,C or L) with no need for further setting up. *PM6303A* offers readings of series and parallel *R*, *Z*, *C*, *L*, dissipation, *Q* and *C* of electrolytics under DC bias. A trim key compensates for strays in various test adaptors, which include a surface-mount type. Philips Test & Measurement, 0923 240511.

#### Interfaces

**Digital pots.** Optical encoders are used in the DP 16 digital "potentiometer" to give an output of 16 two-phase pulses per revolution, or 64 binary code changes. Devices in the range offer from 50 to 2048 pulses/rev, or 200-8192 changes. Applications are seen in manual data input to computers or in digital feedback from servos. Control Transducers, 0234 217704.

**VGA/PAL converter.** *VGAPAL* from



**Waveform monitor/vectorscope.** Model 5783 from Thurlby-Thandar is virtually the same as the 5871, but has the phase reference facility deleted for those people who use only one signal source. Colour television vector and waveform displays are seen either alternately or simultaneously on the 16 $\frac{1}{2}$ " PDA tube. Line-selector function can be used with vertical interval test signal, v. interval reference, Text and insert test signal, up to nine line numbers and fields being stored in memory. Thurlby-Thandar Ltd, 0480 412451.

Research Development Application Ltd converts the output from a VGA graphics card into pal video in real time, for viewing or recording on video tape. It is a simple add-on and does not interfere with the PC's graphics functions. The card plugs into any spare slot and needs no setting changes to the graphics card, being connected between the graphics card output socket and the monitor plug by means of a special plug provided with *VGAPAL*. RDA Ltd, 0495 224098.

#### Literature

**Semiconductor database.** Data Business Publishing have produced a PC AT database which identifies components and gives the manufacturer, local sales offices and distributors. The details of over 400,000 active devices from more than 500 makers include maker, address and telephone number, part number and key, description, availability and how to find the operating data in the library. This "low-cost" database, *ISD*, costs £249 plus vat and comes on 3.5in or 5.25in floppies for installation on a hard disk or in a Novell network. HTI Ltd, 0277 375000.

**Bus driving.** Three new application notes from NI discuss new features in

the *IEEE-488.2* driver software (340056-01), sharing local ram with the *VXibus* (340059-01) and using *NI-VXI* software to configure and program a *VMEbus* system (340060-01). All notes are free. National Instruments UK, 0635 523345.

#### Materials

**Conductive foil tape.** *Cho-mask 1* tape for anti-EMI measures comes with a peel-off paint mask. A 0.07mm tin-plated copper foil has a conductive, pressure-sensitive adhesive on one side and a 0.076mm nylon paint mask on the other for ease of use in EMI gaskets or earthing, the mask being removed after paint or bake cycles. Used with Monel mesh, shielding performance is better than 100dB at 1GHz. It comes in rolls or in die-cut form. Chomerics (UK) Ltd, 0628 486030.

#### Production equipment

**Water-washable solder cream.** Series 400 creams from ESP for use on ceramic or epoxy glass boards leave residues that are easily removable in water, eliminating the costs of solvents and their reclamation. They are equivalent in performance to standard *RMA* fluxes. The creams can be dispensed, screened or stencilled and they do not slump, so that they are particularly suitable for fine-pitch use. Moisture resistance, eight hours of screen life, thermal stability, a 48-hour tack time and storage life of 12 months are offered. ESP, 0234 211532.

#### Power supplies

**Boxed power.** Three ranges of general-purpose power supplies from Davtrend are meant for soak testing, battery simulation and goods-inward testing. *DL* types are of the linear variety providing stabilisation and regulation of  $\pm 0.1\%$  and  $\pm 0.5\%$ ; *DS* units are secondary switchers and there are also unregulated versions. Davtrend Ltd, 0705 372004.

**Four-output, 150W SMPS.** Power

General's *FLU4-150* series of open-frame switchers are contained in a 4 by 9.5 by 2in area of board. Each model has a +5V output and there is a choice of 5V, 12V, 15V or 24V for the other three, all of them with a zero minimum load. Inputs between 90 and 265V AC are automatically accepted, as are those between 100 and 370V DC. Line filtering eliminates conducted noise and MTBF is 165,000 hours. Stabilisation is 0.3% for the 5V output and 0.5% for the others; regulation is 1%. Dowty Power Electronics, 0722 413060.

**30W DC converters.** *3000LP* series DC-to-DC converters, intended by Conversion Devices for OEM use, are contained in a 0.375in high package for 0.5in board mounting. There are single, dual and triple outputs, working over a 2:1 input voltage range, all with pi-type input filters and input/output isolation. All six sides are continuously shielded. Devices can be paralleled for more power or connected in master/slave configuration for increased input voltage. Outputs are 5, 12 and 15V DC;  $\pm 12$ ,  $\pm 15$  V DC and 5; and 5,  $\pm 12$  V DC or 5,  $\pm 15$  V DC. Eurosource Electronics Ltd, 081 977 1105.

#### Radio communications products

**Saw filters.** Kinseki is a Japanese company, new to the UK, which manufactures quartz crystal devices. Recently, saw filters have been introduced in versions for pagers and general telecomms work, types for the Global System Mobile Phone (GSM) system now being in development. Kinseki (UK) Ltd, 0454 614638.

**Radio data network.** RDI have introduced *Versanet*, which it says is the first deregulated radio data network to use a frequency-agile system to avoid interference automatically, listening to the permitted channels and selecting a clear one. *Versanet* includes an *RS232* serial data highway port to exchange data with PCs or PLC equipment. Radio Data Technology Ltd, 0376 501255.

#### Transducers and sensors


**Load-measuring washer.** Load washer Model *LW* from Control Transducers measures bolt stresses to determine overloads and to ensure clamping forces. Capacities are from 100kg to 100,000kg in sizes from 25mm diameter and 9mm thick to 76mm and 32mm. A domed load button and load base are supplied as standard and spherical washers for use on uneven surfaces or in the case of misalignment are optional. Temperature range is up to 200°C; repeatability, non-linearity and hysteresis are all 0.15% of full scale. Control Transducers, 0234 217704.

**Proximity detectors.** A range of

proximity detectors by Crouzet, the V3 series, will cope with both metallic and non-metallic substances. They work normally, in that the approach of a metallic object activates the V3, but the addition of a metal lever enables the detector to react to the touch of a non-metallic object, becoming in effect a non-mechanical limit switch without the contacts. A led indicates switch status; switching capability is 200mA continuous. Crouzet Ltd, 0252 513211.

**Accelerometer.** Weighing less than 1g, Endevo's model 7264A piezoresistive accelerometer uses a silicon microsensors in full Wheatstone bridge form with fixed  $R_s$  for calibration. Full-scale range is 2000g, at which output is 400mV with 10V DC supply. Resonant frequency is 65kHz and measurement frequency range is 0 to 13kHz. Endevo UK Ltd, 0763 261311.

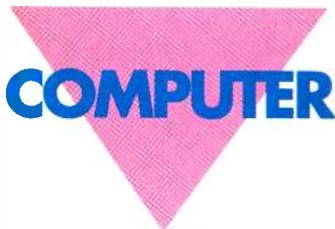
**Proximity sensor.** IP67 inductive proximity sensors from EuroSensor offer a reproducibility of 10 $\mu$ , come in p-n-p and n-p-n forms and indicate activity by a led. They measure 4mm in diameter by 26mm, accept between 6V and 35V DC supply and draw less than 5mA when idling. Kynmore Engineering Co. Ltd, 071 405 6060.



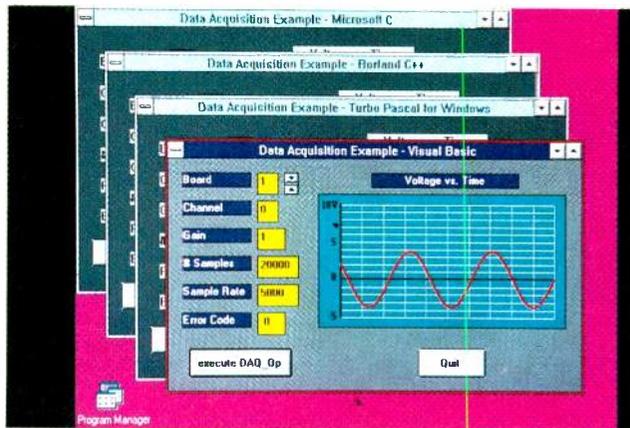**Computer board level products**

**Frame grabber.** Amplicon's VDGI frame grabber board plugs into a PC XT/AT to provide real-time video signal capture and storage. It includes a 64K frame buffer and 4-bit TTL i/o for external control and monitoring. Resolution is 256 by 256 by 7bit and there is internal/external sync., horizontal and vertical sync output and a low pass filter for noise and colour. Operation is interactive by menu, including setup and lighting conditions and output is in PCX or TIF file form. Amplicon Liveline Ltd, (Free)0800 525 335.

**Open local bus.** Scim is an open-architecture local bus by Arcom, which offers lower-cost, yet powerful expansion for industrial computing. Choice of modules includes those for VMEbus, STEbus and PCbus host carrier boards. The bus accommodates 16 data and 24 address lines, four interrupts, DMA and serial lines. Two connectors are used for data and address, with STEbus and PCbus in mind, but dual connectors can be used for 16-bit transfers. In the range of modules are analogue input and output, RS232 serial i/o, RS485 serial i/o, 40-line



**Analogue output.** Two analogue output boards for the PC AT have either six (AT-AO-6) or 10 (AT-AO-10) high-speed multiplying DAC82222 digital-to-analogue converters. Each channel on these NI boards has 4-20mA output and a bipolar or unipolar voltage output. DMA capability allows operation at conversion rates up to 200kHz and there is an 8-bit DIO port for additional control. For programming, there is NI-DAQ dos and NI-DAQ Windows driver software and LabWindows software development, the software being free with each board. Boards will be available from December 1992. National Instruments UK, 0635 523545.

programmable digital i/o, Ethernet interface, flash rom/ram, comms and VGA/EGA/CGA graphics. Arcom Control Systems Ltd, 0223 411200.

**Eight-i/o PC card.** Data acquisition and control card for PC ATs will hold up to eight different input/output modules, so enabling choice of the required channels on one card and taking up fewer expansion slots in the PC. Modules already available include multi-channel analogue, digital and comms versions. Intek Electronics Ltd, 0352 85603.

**S-B computer for logging.** Logicom's single-board computer is based on the Siemens SAB80C535 microcontroller and is meant for OEM use in data logging, monitoring and control. It offers eight extended-

resolution analogue inputs, 16 digital i/o lines and an RS232 port. There is 32K of battery-backed ram, 64K of eeprom, a watchdog and Power supply supervisor. Programming is in C, Basic or assembler. Logicom Communications Ltd, 08-756 1284.

**Data acquisition.** AT-DSP2200 from NI is a DSP accelerator board for the PC AT, delta-sigma modulating A-to-D and D-to-A converters. It performs scientific calculation faster than the PC's 80X86. AT-A2150 is a further plug-in board to provide four channels of audio-frequency analogue input with low noise and low differential non-linearity. National Instruments UK, 0635 523545.

**Development and evaluation**

**Low-cost ICE.** Nice 51 is claimed to be the cheapest 8051 hardware in-circuit emulator available. This new ICE from Comsol has the ability to substitute emulated for target memory and to stop execution on a combination of internal and external events while running at speed. The PC program allows memory, registers and SFRs to be displayed and modified and it will assemble code changes to allow mods to be tested. Execution speed is 12MHz. Computer Solutions Ltd, 0932 352744.

**Programmer.** Softy-Four is Dataman's new programmer, designed to cope with eeproms, eeproms and flash eeproms. S4 has large nicad batteries and will program up to 1000 proms on a one-hour charge, although its lithium battery backup preserves data even when the nicads run down. Built-in memory

emulation allows the development and debugging of microsystems. 1Mb of user memory, upgradeable to 4Mb. Dataman, 0300 20719.

**Eeprom programmers.** Hilo eeprom/eeprom programmers by Nohau will download a 4Mbit file in a few seconds and program eight 27256 eeproms in 20s. An interface card in the PC shares the PC's CPU, memory, i/o, keyboard, display and disk to achieve the speed. Eeproms of up to 8Mbit can be programmed. Software includes a hex-to-binary converter, 2 or 4-way binary file splitter and "dump file to console". Nohau (UK) Ltd, 0962 733140.

**Transputer kits.** Transkits from Sunnyside contain hardware and software needed to familiarise engineers with the use of transputers by turning their PCs into "virtual instruments" - an oscilloscope and a spectrum analyser. TransKit 500 is the first, consisting of a two-channel, 16-bit A-to-D transputer module (tram), a two-channel D-to-A tram and a compute tram mounted on a single-slot AT card. Accompanying software turns the PC into a combined dual-channel digital storage oscilloscope and function generator. An enhanced version has C source code of the system software, a C compiler and debugger. Sunnyside Systems Ltd, 0506 460345.

**Software**

**Abel 4.1.** Version 4.1 of Data I/O's Abel programmable-logic design tool allows the compilation and simulation of larger PLD designs by means of dos extended memory and now supports Intel's 85C22V10, the Lattice GAL6002, Atmel's ATV5000 and other devices by Cypress, Ricoh and Toshiba. Abel-FPGA is also announced in its 4.1 version. Data I/O Ltd, 0734 440011.

**Gate array programming.** Actel have made the route to field-programmable gate arrays easier by introducing an entry-level Action Logic System, which is a combined software/hardware kit including Viewlogic schematic capture, Viewlogic/Orcad interface libraries, validation, place-and-route and timing analysis. The hardware is an Activator 1 programmer with sockets for 68PLCC, 84PLCC and 84PGA. The kit is for Actel Act1 logic, but is upgradeable to Act2 and Act3. MMD Ltd, 0734 313232.

**PC graphics editor.** Integrated Circuit Editor is a PC AT/XT-based graphics editor for IC layout, featuring fast refresh, auto-open and nested view commands, input and output stream (Calma-GDS II) and CIF files, as well as definable commands and technology files. Compatible with most plotters, laser and dot-matrix printers and will handle polygons up to circles with text for annotation. Silicon Microsystems Ltd, 0666 824844.

# BoardMaker

Finally... an upgradeable PCB CAD system to suit any budget

## BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount support
- 90°, 45° and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

**£95**

## BoardMaker2 - Advanced level

- All the features of BoardMaker1 plus
- Full netlist support - OrCad, Schema, Tango, CadStar
- Full Design Rule Checking - mechanical & electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC

**£295**

NEW

## BoardRouter - Gridless autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

**£200**

## Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Roland, Houston & Graphtec
- Photoplotters - All Gerber 3X00 and 4X00
- NC Drill plus annotated drill drawings to HPGL, Gerber and DXF (BM2)



Call for info or FREE evaluation kit:  
Tsien (UK) Limited  
Phone: (0223) 277 777  
Fax: (0223) 277 747



Tsien (UK) Ltd, Cambridge Research Labs, 181A Huntingdon Road, Cambridge CB3 0DJ

CIRCLE NO. 136 ON REPLY CARD

# CVC

## Chelmer Valve Company

Worldwide supplier  
with 30 year's experience

- **Electron tubes: Transmitting, Industrial, Microwave, Audio, Receiving, Display, etc, etc.**
- **For Maintenance, Spares or Production.**
- **Semiconductors: Transistors, Thyristors, Diodes, RF, Power I/C's, etc.**
- **We have one of the largest stocks in the U.K.**

★ TRY US! ★

FAX, PHONE, POST OR TELEX YOUR REQUIREMENTS  
130 NEW LONDON ROAD, CHELMSFORD,  
ESSEX CM2 0RG, ENGLAND

Telephone: (0245) 355296/265865  
Telex: 995398 SEEVVE G Fax: (0245) 490064

CIRCLE NO. 142 ON REPLY CARD

Field Electric Ltd. Tel: 081-953 6009. 3 Shenley Road, Borehamwood, Herts. WD6 1AA. Fax: 081-207 6375, 0836 640328

- 3.5" floppy disk drive Chinon BBC compatible, new £35 c/p £4.00.
- Astrolux Mono Headset New £15.95 c/p £3.50.
- Tektronix 7403N Mainframe only £80.
- 3.5" floppy disk drive NEC IBM compatible. Full height unit. £39.95 new & boxed, 1.6Mb, c/p £3.00.
- Switch mode power supplies 240V AC input 5V DC 40amp £29; 12V DC 10amp £46; 5V DC 40amp -12V DC 4amp +15V DC 11amp £48.
- Western Digital 3.5" hard disk drive new 40Mb RLL ST506 £120 c/p £6.00.
- H.P. 4328A milliohmmeter £450 c/p £11.00.
- H.P. 3400A RMS voltmeter £225 c/p £11.00.
- NEC new & boxed 5.25" floppy disk drive model FD1055-311 BBC compat. 1/2 height £48 c/p £6.00.
- Plantronics (Auralite) type headsets very lightweight new BT approved ideal for comms. £25 c/p £3.00.
- Farnell fan-cooled PSU 240V AC input +12V DC 4amp -12V DC 1amp +5V DC 10A -5V DC 5amp £16 c/p £7.00.
- NEC 1/2 height 3.5" hard disk drive. IDE 40Mb 25ms £80 c/p £5.50.
- IBM compatible printer lead right angle £8 inc. c/p.
- All flight case for computers 510x480x175 £45 c/p £10.
- Low profile gender changer 25w male/male £5.50 inc. c/p.
- Low profile gender changer 25w socket/socket £6.75 inc. c/p.
- Auto data switch 401. Up to 4 PC to 1 modem or printer. New & boxed £46 c/p £5.50.
- Auto data switch 801. Up to 8 PC to 1 modem or printer. New & boxed £56 c/p £5.50.

Lambda power supply model LMG12 0VRV 12V DC 56A linear £200.00.

KSM power supply model SCT 200-15 0-240V 0-15A £160.00.

Hewlett Packard 618B SHF signal generator £75.00.

Hewlett Packard 606B signal generator £75.00.

Hewlett Packard 612A UHF signal generator £75.00.

Hewlett Packard 86A personal computer new £95.00.

Hewlett Packard 500CA logic state analyser £60.00.

Hewlett Packard 3450B multi-function meter £65.00.

Hewlett Packard 693D sweep oscillator £175.00.

Hewlett Packard 651B test oscillator £75.00.

Hewlett Packard 9868 I/O expander £55.00.

Iswatsu SS5705 40 MHz O'scope £295.

Kikusui COS 5040 40MHz O'Scope Calto 1-92 £350.

Hameg HM605 60MHz O'Scope £400.

Hitachi V212 20MHz O'scope £230.

Hitachi V202F 20MHz O'scope Calto 1-92 £230.

Hitachi V509 50MHz O'Scope £400.

Tektronix 455 O'scope £350.

Tektronix 7B70 time base plug-in £100.00.

Tektronix 7D01 logic analyser plug-in £100.00.

Paratronics Model 532 logic state analyser 32chn £165.00.

All above prices + 17 1/2% VAT. Please ring for c/p rates.



We would like the opportunity to tender for surplus equipment  
Official orders credit card telephone orders accepted with  
Access, Amex, Diners, Visa cards. Overseas enquiries welcome  
c/p rates U.K. mainland only.

Please ring for c/p rates not shown.

All prices inc. V.A.T. unless stated. Stock list available.

CIRCLE NO. 137 ON REPLY CARD

# REGULARS

## CIRCUIT IDEAS

### Two mic-amp tips

This electret microphone preamplifier is of fairly standard form, but contains input and output arrangements of particular interest.

As well as giving an on/off indication, the led in the input provides bias for the electret module, since led forward voltage is essentially constant; the 4.7k $\Omega$  microphone load, selected experimentally, gives best output.

At the output, the 100 $\Omega$  resistor in series, but inside the feedback loop of the stage, allows the use of long, capacitive cables.


**D M Bridgen**

Racal Mexico

Bosques de Las Lomas

Mexico

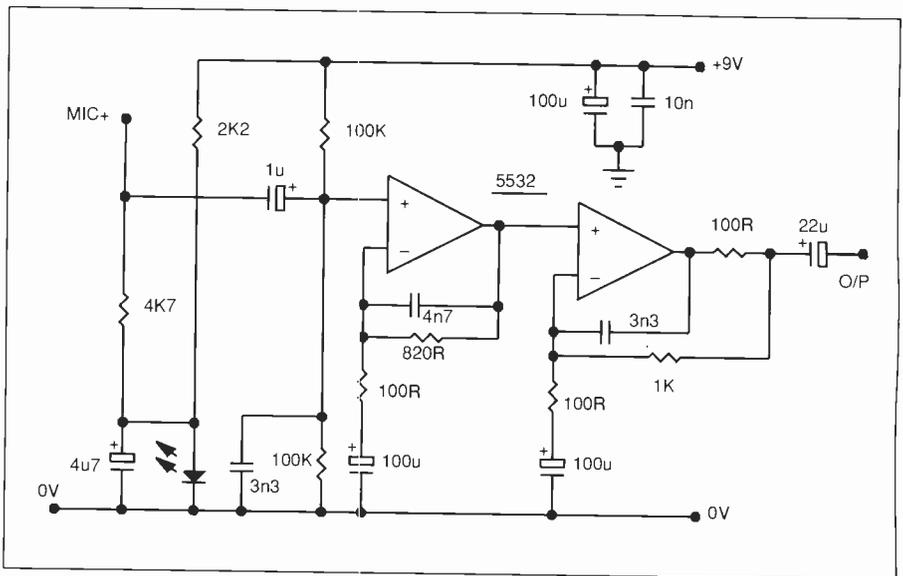*Led at the input and small resistor at the output of this electret microphone amplifier provide bias for the microphone module and drive for long cables.*



### Current-shunt amplifier for bipolar inputs

Operating from a single supply, this amplifier copes with both positive and negative low voltages derived from a high-current shunt.

Gain in the shunt feedback arrangement is set by  $R_{5,6}$  and centre bias voltage by  $R_{1,2}$ . The current-shunt resistor is taken directly to ground where the voltage developed across it produces a current in  $R_5$ , which is amplified; no decoupling capacitor is needed. To balance the offset voltage caused by the shunt ground connection, a balance current flows through  $R_4$  – which must be


equal to  $R_5$  – whatever gain is needed. With no input, the output voltage sits at half the supply voltage. An *OP07* op-amp has a low offset voltage and is particularly suitable for this design.

**Norman Jones**

Cobridge

Staffordshire

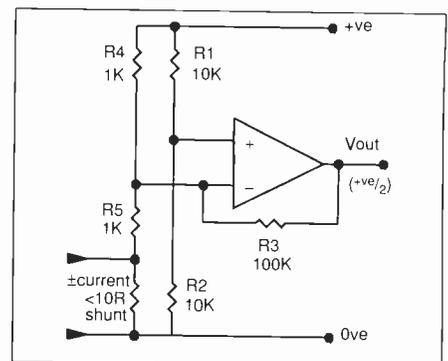*Voltages produced by both positive and negative direct and alternating currents flowing through the shunt are amplified by this single-supply circuit.*



### Positive-feedback op-amp booster

Since the gain/bandwidth product of an op-amp is a constant  $f_1$ , increasing closed-loop gain reduces its bandwidth and therefore rise time in direct proportion. This circuit reduces the effect by counteracting the increased voltage at the summing mode when the input frequency increases.

The effect is achieved by means of the simple CR circuit in a positive-feedback connection, which makes the circuit a second-order system with its complex pole pair higher than the first-order bandwidth  $G = f_1/B$ . To avoid oscillation, the -3dB point of

the CR must be greater than  $f_1$ .


The plots show the greatly improved rise time with  $R = 470\Omega$  and  $C = 150\text{pF}$ ; measured bandwidth is improved to 160kHz from 25.7kHz.

**D Baert**

Rijksuniversiteit Gent

Chent Belgium

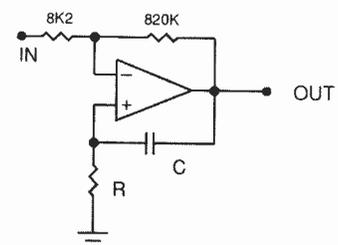*Judicious application of suitably shaped positive feedback improves bandwidth and rise time of an op-amp. Roll-off frequency of CR must exceed op-amp cut-off frequency for stability.*



## One-gate memory

Non-inverting gates – Ands, buffers, Ors – will make single-element memories, using one resistor. In effect, the gates are made to latch by applying positive feedback via the resistor and forcing the input to either state by switches or logic levels. Resistor value is not critical, but is related to the response time.

Figure 1 shows the principle using a buffer and one input; in Fig.2, an And gate gives the same effect, but the two inputs are used as set and reset. Using a capacitor instead of the resistor produces curious monostable flip-flops.

D J Long  
Brighouse  
West Yorkshire

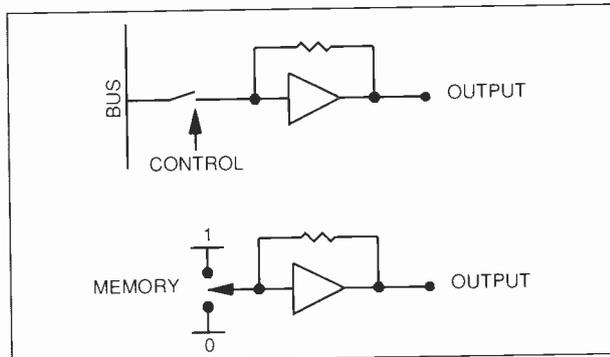


Fig.1. Making a buffer latch up produces a one-bit memory. Once its input is forced to one state, it will stay there.


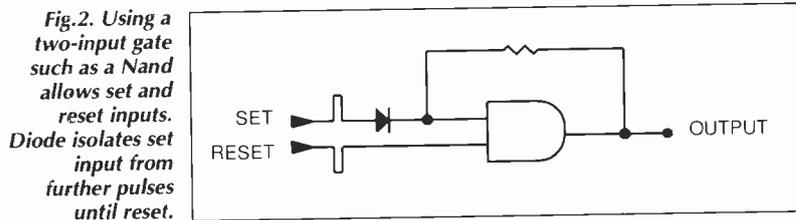


Fig.2. Using a two-input gate such as a Nand allows set and reset inputs. Diode isolates set input from further pulses until reset.
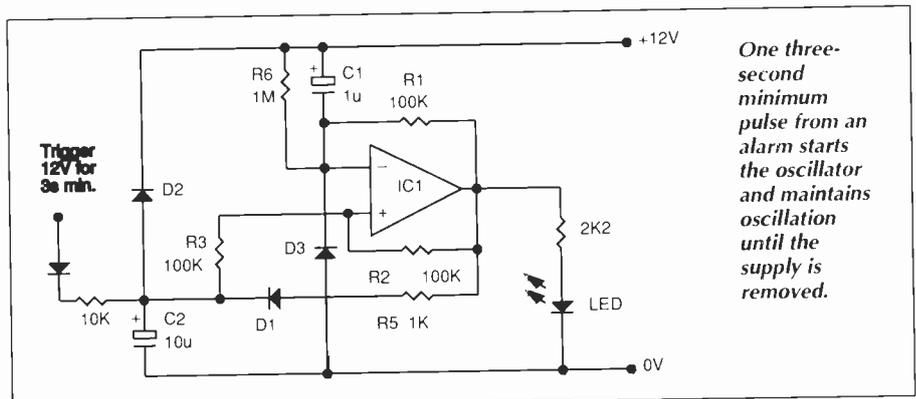
## Latched oscillator

In an alarm system, an operation from which a three-second supply-voltage trigger pulse was available was required to flash a led – reset being by means of removing the supply voltage. I had available an LM358N op-amp, a type that allows inputs down to the negative rail, and combined an oscillator and latch using the single device.

Resistors  $R_{1-4}$  and  $C_1$  with the op-amp form a relaxation oscillator starting in the off condition when power is applied:  $R_5$ ,  $D_1$  and  $C_2$  provide a latching action to maintain the alarm condition after the trigger pulse ends. In the inactive state, the voltage on the non-inverting input is lower than that on the inverting input and the oscillator is off. On receiving a trigger,  $C_2$  goes to 12V, less a diode drop, and the oscillator starts;  $D_1$  and  $R_5$  keep the voltage on  $C_2$  high after the



One three-second minimum pulse from an alarm starts the oscillator and maintains oscillation until the supply is removed.

trigger.

To avoid spurious triggers,  $R_6$  keeps the inverting input above the non-inverting input in the standby condition. Diodes  $D_{2,3}$  discharge  $C_{1,2}$  when the supply is removed.

Time constant  $C_1R_1$  must be much less than  $R_{2-4}C_2$  to eliminate the possibility of

$C_2$  discharging during the low state to the point where the non-inverting input is always higher than the inverting input, stopping oscillation.

M J Brettle  
Potton Marine Equipment  
Gamlingay Bedfordshire

## Low-loss voltage dropper feeds S-M controller


Low power consumption switched-mode controllers can be fed from the rectified input, thereby avoiding the need for a separate transformer winding, but a simple dropper resistor wastes power. This circuit uses a capacitor and has minimal loss.

Its feed is taken across the SMPSU input bridge and gives a 9V, 3mA output, sufficient for low-power mos controllers driving a power mosfet. The circuit must only be used where there is no chance of a

user gaining access to it, since it is live, and an isolation transformer should be used during test.

A M Wilkes  
Brentwood  
Essex

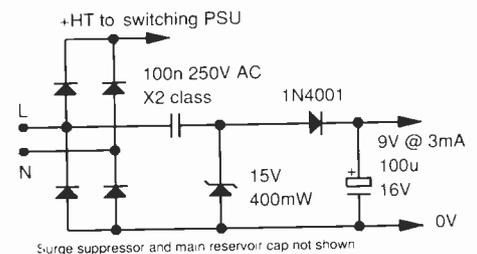Low-loss voltage dropper replaces a resistor when powering low-consumption switched-mode power supply controllers from the rectified mains input.




## Asymmetrical on/off for 4060

An internal oscillator and 14-stage ripple counter in the 4060 make a useful long-duration on/off timer, but with a possibly inconvenient symmetrical output duty cycle.

This circuit avoids any complication of additional circuitry by splitting the oscillator frequency-setting resistor and shorting on part of it by a relay driven by the output of the timer. Timing now becomes, with the relay on,  $2.2CR_12^n$ , and with it off,  $2.2C(R_1+R_2)2^n$ ,  $n$  being the divider output driving the relay. You could use an analogue switch in place of the relay.

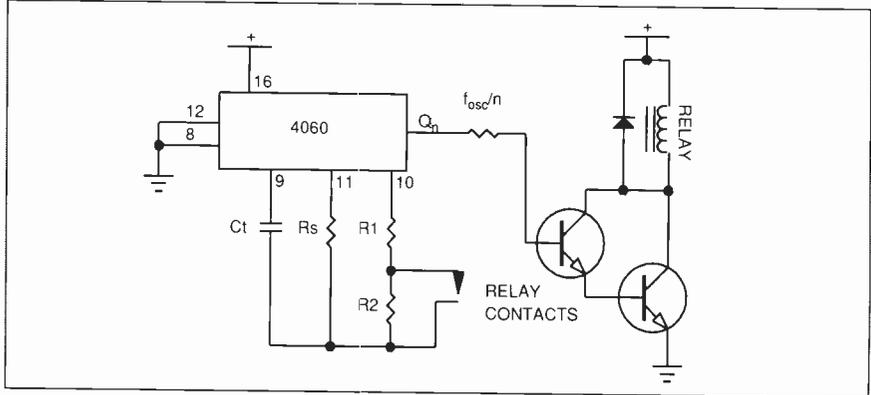**J V Sawant**  
Haffkine Institute  
Bombay  
India



Relay or analogue switch driven by a counter output allows asymmetrical on/off times in this long-duration timer.

## Programmed Nand/Nor or And/Or gate

Using a pair of triple, two-channel multiplexer/demultiplexers, you can make a logic gate which is selected as an And/Or gate or a Nand/Nor under the control of two inputs.




In Fig.1, the logic inputs are  $A$  and  $B$  and the function-select inputs  $S_1$  and  $S_2$ , the four combinations of the two giving four logic functions. An advantage of this scheme is that the output impedance is low, being the on impedance of two analogue switches in series or less than  $200\Omega$ .


Figure 2, taken from a data sheet, shows the arrangement. When, for example, input  $A$  is low,  $S_1$  is on; and when  $A$  is high,  $S_2$  is on and so on.

**Emad Hamdoon Said**  
Baghdad  
Iraq

Fig.1. Function-select inputs  $S_1$  and  $S_2$  configure the two 74HC4053s as an And, Or, Nand or Nor gate.

Fig.2. Internal block diagram of 74HC4053 multiplexer/demultiplexer.

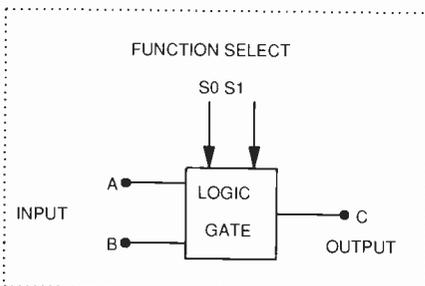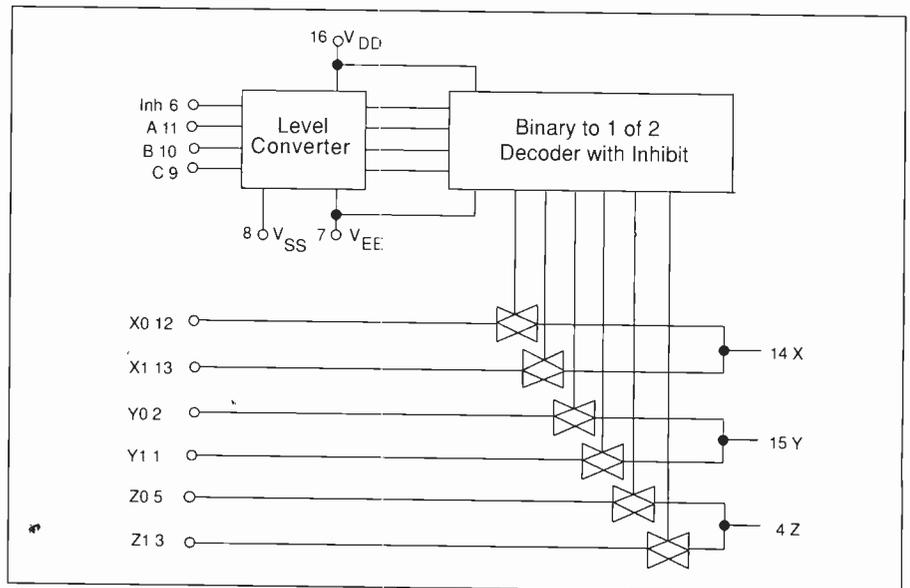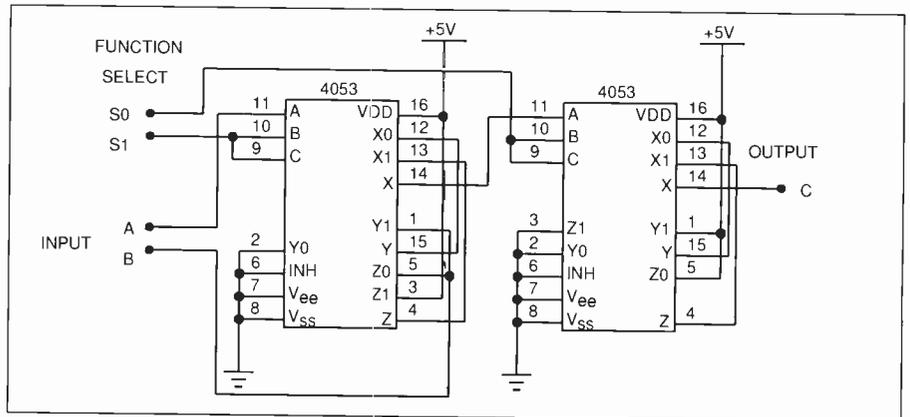

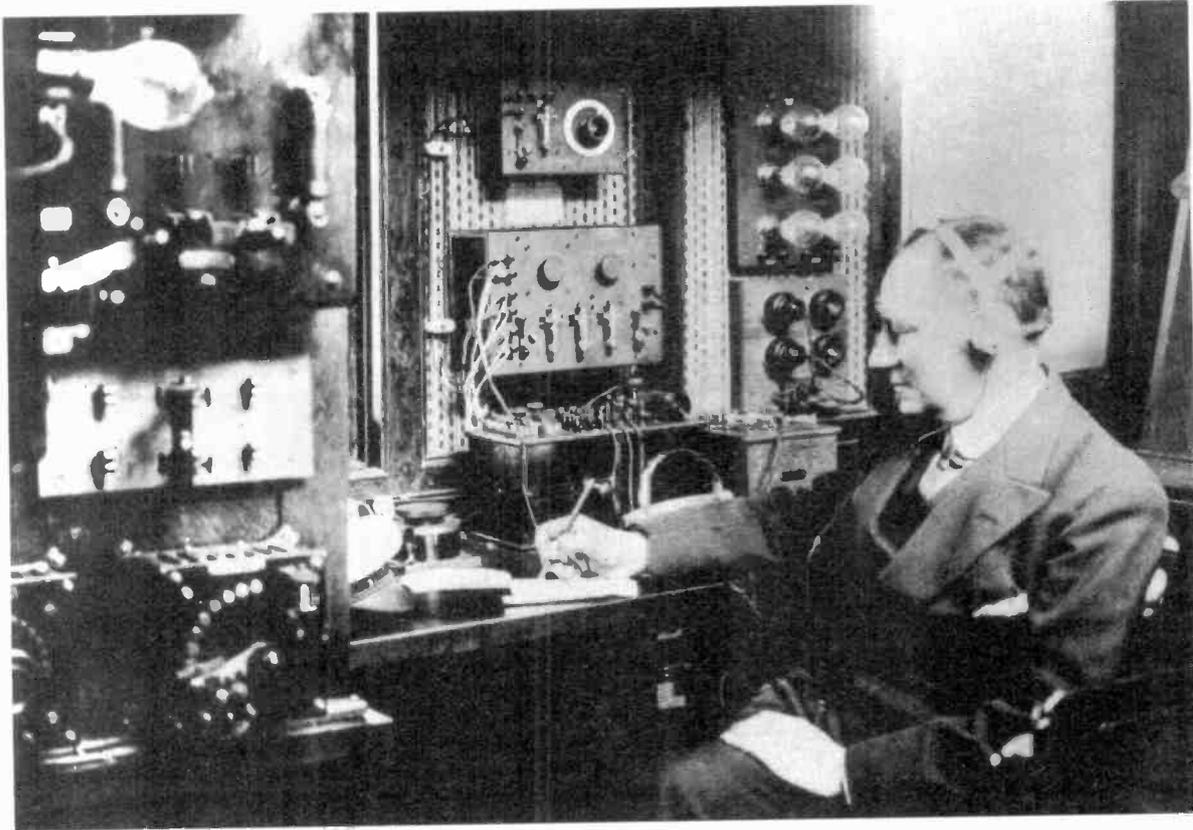

*Marconi in his steam yacht Elettra. In 1923 he sailed westward to test the range of shortwave transmissions*


# UNITING THE EMPIRE

Connecting Britain with its Empire by means of 1000 mile wireless links was an idea that had been put forward by the Marconi company as early as 1906. But the project did not take root until the Imperial Wireless Conference of 1911, following which Marconi was awarded a contract by the Post Office to supply a series of long-wave, high-power stations.

Unfortunately start of the work was severely delayed by a complicated political row (the so-called Marconi scandal, where members of the government were accused of favouritism and improper share dealing), and then cancelled due to outbreak of the first World War.

Following the war, work on a European network progressed, including the building, in 1921-2, of a transmission station at Ongar and a receiving station at Brentwood. These were linked to a central telegraph office, Radio House, in Wilson Street, London.

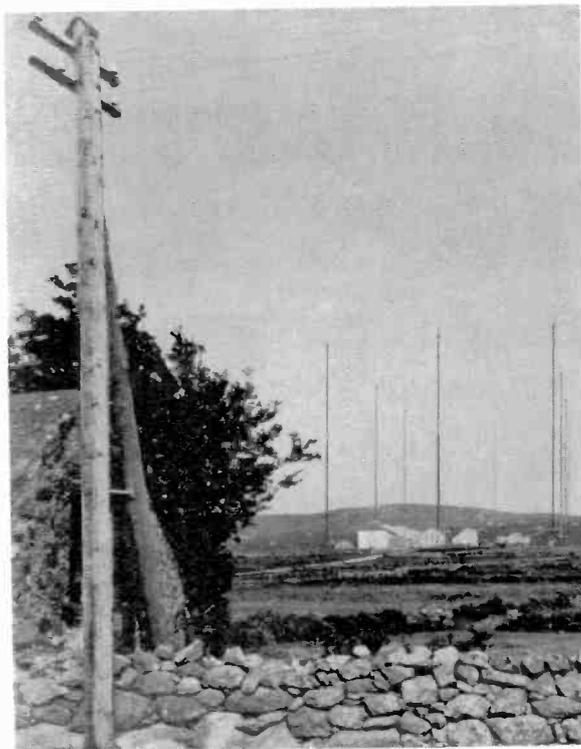
But the Imperial scheme was held up by continuing wrangles within the UK government and between it and those of the dominions. The Post Office embarked on a high-power station in Rugby, while Australia and South Africa commissioned stations from the Marconi company. But by 1924, a coherent plan of action had still not emerged.



*Caernarvon station – high power transmissions to America.*
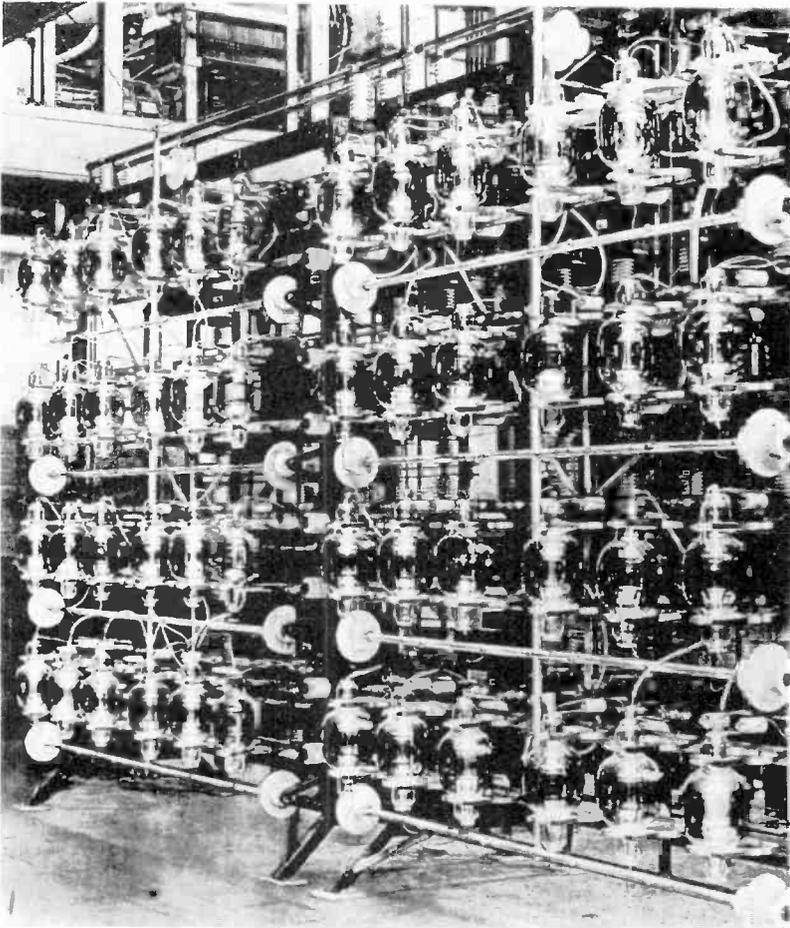
#### Short wave experimentation

The one unquestioned assumption was that the chain would use long-wave frequencies. Longer wavelengths



Caernarvon's 1921 valve panel – 56 air-cooled MT2 valves.

The high-power transatlantic transmitting station at Caernarvon, was, with its companion receiving station at Towyn, commissioned before the 1914-18 war. In 1922 they took over traffic from Clifden, destroyed in the struggle for Irish home rule. Caernarvon had three transmitting systems in its time. First was a timed-spark disc, joined in 1920 by a 200kW Alexanderson high frequency alternator. A valve transmitter was added in 1921. It employed 56 air-cooled Marconi MT2 valves, powered by two or three direct-current generators in series, supplying up to 15,000V.


A contemporary account noted: "The constancy of frequency of the valve generator is very remarkable, being of an order altogether higher than that of the alternator, and no highly complicated means is necessary to ensure it." A European transmitter at Ongar (with receiver at Brentwood) was opened in 1922, and also took over some transatlantic traffic. Together with Caernarvon they were operated by remote control over landlines from the newly-opened Radio House, the Central Telegraph Office in Wilson Street, London.

and higher powers were accepted as the recipe for covering longer distances. But since 1916, Marconi had been experimenting with shorter-wave transmissions, initially for naval signalling over line-of-sight distances. In 1917, he lost a £5 bet with one of his staff, CS Franklin, who succeeded in demonstrating, despite his employer's scepticism, a short wave (15m) link between London and Birmingham. Another Marconi man, HJ Round, noted freak long- distance reception of 100m signals.

Amateur radio enthusiasts, working post-war in sub-200m wavebands, were also finding that they could occasionally make transatlantic contact.

Marconi set up a shortwave transmitter at Poldhu in 1923 and, as in 1902, sailed westwards – this time in his steam yacht Elettra – to test reception. Ranges of 1400 miles were achieved in daylight, and signals received in New York after dark.

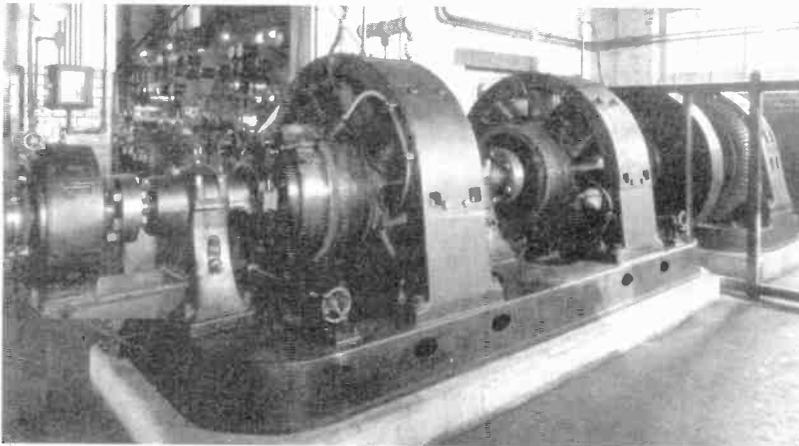
By May 30, 1924, following further experiments and improvements, the signal to



Up to three DC generators, in series, supplied 15,000V to the Caernarvon valve panel



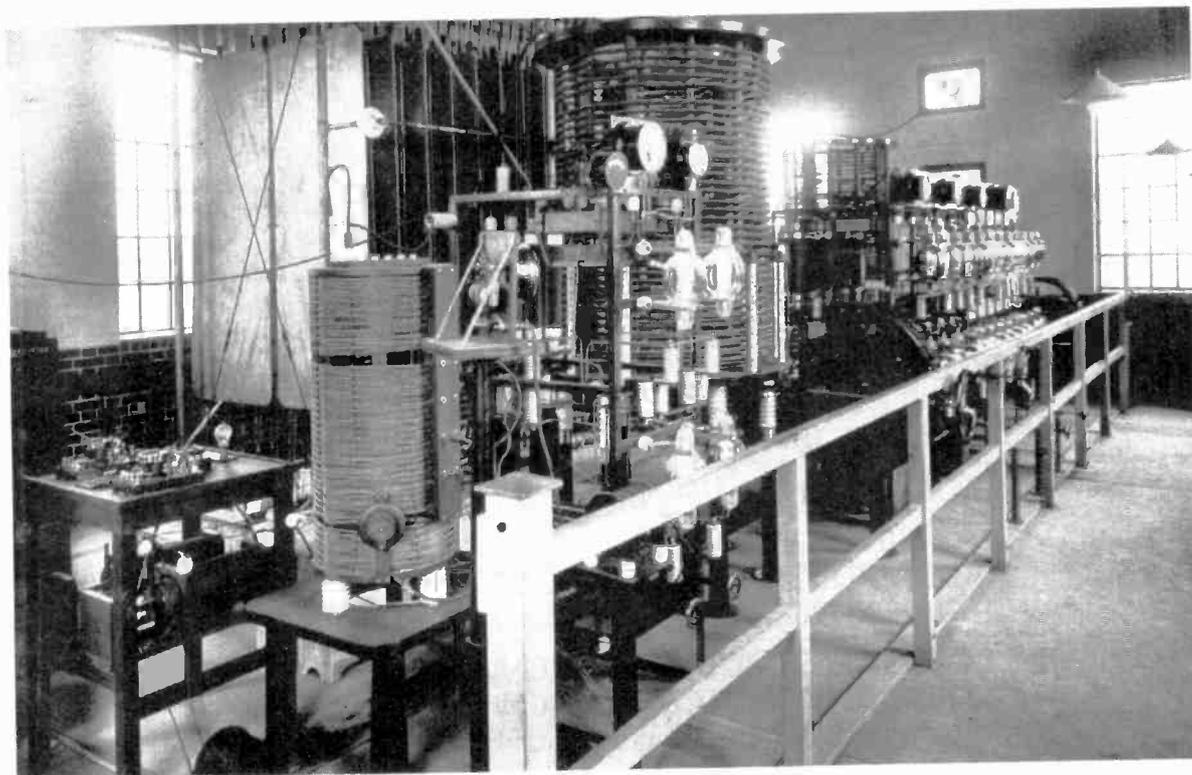The Brentwood receiving station, companion to Ongar.



One of the three European transmitting stations at Ongar, opened in 1923.

Sydney, on 92m, was so strong that Marconi was able to speak from Poldhu to Australia by wireless telephone. This presented the company with a dilemma: although successful in experiments, directional shortwave transmission was far from being a proven, marketable system. Contracts for British government was at last on the verge of reaching a decision on the Imperial scheme.

Yet the shortwave beam system's potential cost-benefits over longwave were enormous, requiring a fraction of the transmission power, so meaning smaller, cheaper stations and lower running costs. The company decided that to conceal the shortwave progress, while pressing ahead with costly longwave installations would be to break faith with its customers (and also, perhaps with its own technological integrity).

Australia and South Africa readily agreed to modification of the already-started stations, and, under pressure from the dominions, the British government reached a decision on July 2.

The Imperial Wireless Chain, with Marconi as contractor, would go ahead, and would use the short-wave beam system in a contract loaded with penalty clauses, though these proved unnecessary.

#### The expensive irony of C&W

Ironically, it was success of the system that was to cost the company most dearly. The wireless chain quickly attracted traffic from the cable links, being both three times as fast, in terms of words-per-minute (these were still the days of telegraphy) and cheaper to operate and maintain. Nevertheless cable had some advantages over shorter distances, and was regarded as a strategic defence necessity by the UK and Dominion governments.

The upshot, in 1929, was a government-induced merger – the creation of a new company which would buy-out the communications interests of the Marconi company and the cable companies. This was Cable and Wireless. In view of the weakness of the cable group's position, and the strength of Marconi's, it is odd that the voting rights in the new company were 56.25% to the cable group and only

43.75 to Marconi.

For the company, the merger marked the end of its involvement in transmitting messages as a business, and a return to its origins as a research, inventor and manufacturing operation. Marconi himself saw the beam system as the culmination of his ambitions – from experimental transmission of a few yards to a worldwide communications system in 30 years.

Central Telegraph Office at Radio House.





**ANCHOR SURPLUS LTD  
THE CATTLE MARKET  
NOTTINGHAM  
NG2 3GY**

**TEL: (0602) 864902 & 864041**

**FAX: (0602) 864667**



**TECHTEST 250 VHF/UHF SIGNAL GENERATORS**  
LOW BAND, HIGH BAND, UHF, FM/AM.  
EPROM CONTROLLED, SYNTHESISED, 200CH. 12-VOLT MAINS.  
Phone for info. £99

**PHILIPS PM3217 50MHz OSCILLOSCOPES**  
CALIBRATION VERIFIED £325

**HP 1476 100MHz OSCILLOSCOPES**  
DUAL TRACE AND TIMEBASE  
CALIBRATION VERIFIED £599

**HP 1600A LOGIC STATE ANALYSER 16bit 20MHz £199**  
**HP 1607A LOGIC STATE ANALYSER 16bit 20MHz £125**  
Buy both and get 32bit analysis (1600S System)  
for only £299

**MARCONI TF2370 SPECTRUM ANALYSER 30Hz-110MHz**  
9-digit LED Display - Excellent Condition £1250

**MATRIX 3000 COLOUR GRAPHICS RECORDER + M<sup>2</sup> Matrix Monitor**  
Takes RGB + Composite + BW Video inputs  
and has CAMERA (still). Mount to Photograph Images.  
Incl. Service Manual. 1 only - £525

**ORTEC BROOKDEAL ORTHOLOC SC 9505**  
Two-phase lock-in analysers. 3 only.  
Excellent condition. £220

**VU-DATA MULTISCOPE. 7 Micro-sized Scopes (each removable)**  
in one frame. £160

**MARCONI TF2008 SIG GENS 10kHz-520MHz AM FM**  
CALIBRATION VERIFIED £325

**SAYROSA 252 AUTOMATIC MODULATION METERS**  
1.5MHz-2GHz AM FM (SAME AS FARNELL AMM)  
CALIBRATION VERIFIED £125

**HP 4951A PROTOCOL ANALYSER WITH HP18179A**  
INTERFACE MINT CONDX £525

Service/User Manuals . . . 1000's in stock . . .  
Send 30p SAE marked *MANUALS CATALOG*



**WE ALSO BUY YOUR TOP QUALITY SURPLUS EQUIPMENT.**  
**TRY US . . . YOU WILL NOT BE DISAPPOINTED!**

All prices excluding VAT & carriage.



### Simple, precision timer

Analogue and digital circuitry come together in the GEC Plessey ZN1034 to generate time intervals from 16ms to hours, without the use of excessively large components. Repetition accuracy is within 0.01% and stability with temperature is 0.01%/°C.

Figure 1 shows its essentials; a precision oscillator with external RC timing components drives a 12-stage binary counter to give a 4096:1 division ratio. After either the trigger pin or the supply voltage changes state, 4095 cycles of the oscillator occur before the output pin sees a change — for 3MΩ and 10μF, that means a twenty-four-hour wait. And, of course, you can trim the timing resistor to obtain the exact time delay needed. GEC Plessey's Consumer IC handbook presents a great deal of information on the components in the timing circuit.

Figure 2 is the basic idea. You can get a variation of 1500:1 in time delay by choosing the timing components for that purpose, but it is pointed out that a more restrained range of 400:1 (1.5s-10m) gives better control linearity, ±2% instead of ±8%. Switched decades of resistance can be used in the R<sub>T</sub> position and the note gives a table of correction factors and errors, with values of shunt resistor needed.

Starting the process going is a matter of either keeping the supply on and taking the trigger pin low or keeping the trigger low and switching on the supply; Fig. 3 shows the process. Supply dropouts during operation cause an increase (supply initiated) or

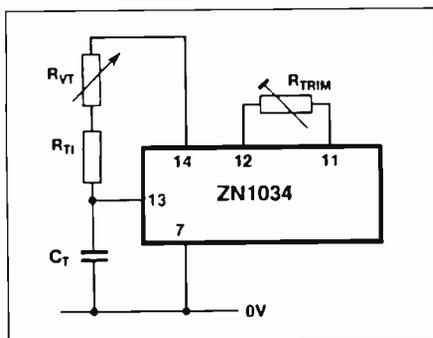


Fig. 2. Basic timing circuit using the ZN1034. Timing range is 1500:1, or 400:1 with a little better control linearity. Minimum delay is 16ms; maximum 24 hours.

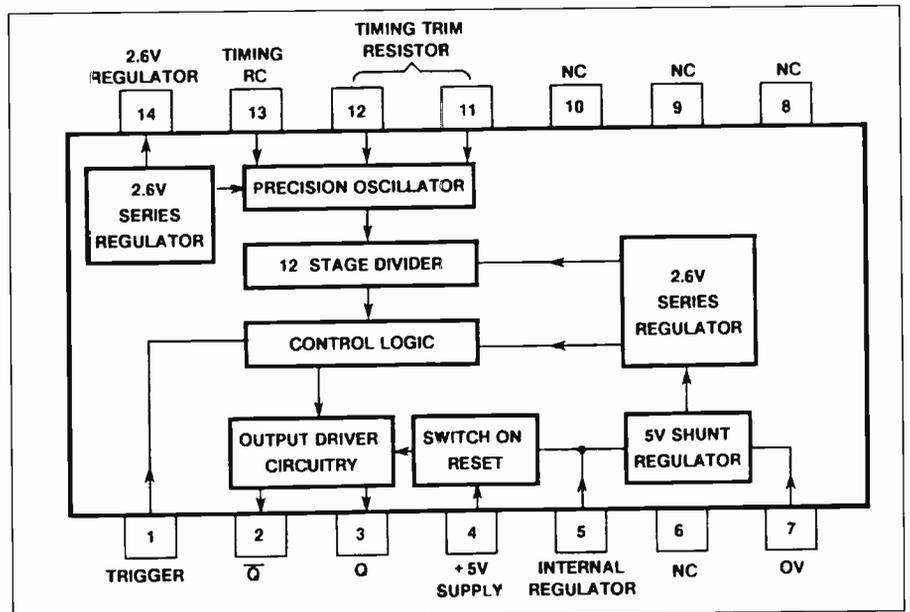


Fig. 1. GEC Plessey's ZN1034 precision counter/timer, which will generate an accurate time interval of up to many hours duration with relatively small timing components.

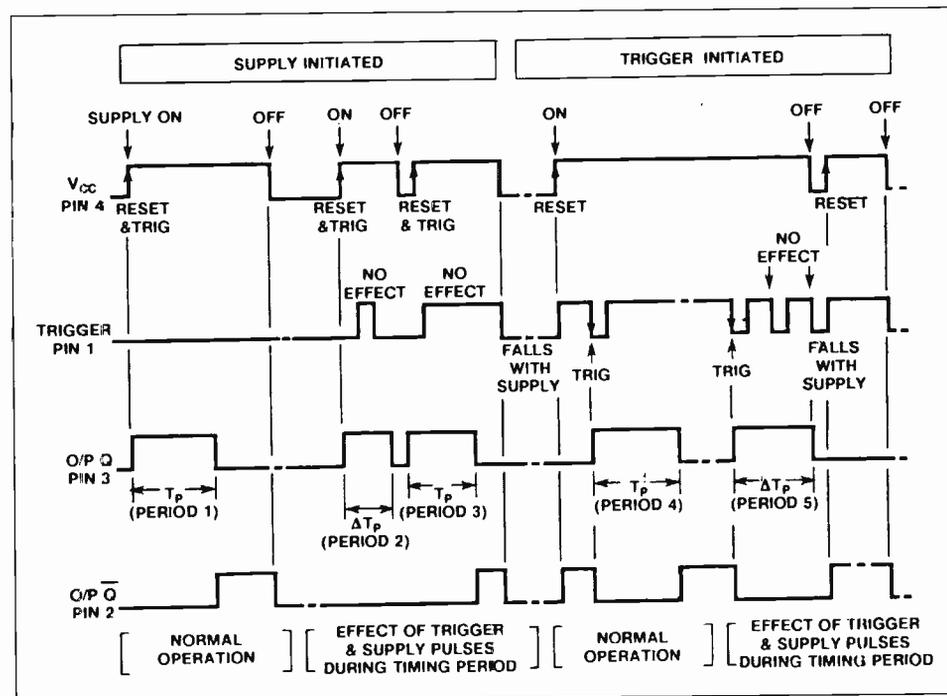


Fig. 3. Methods of setting the ball rolling. Initiation is either by trigger input or by switching the supply.

Fig. 4. Typical circuit for a delay-to-off using a thyristor and a DC relay. Pin 2 will supply up to 25mA, but R1 should be high enough to just saturate the transistor.



decrease (trigger initiated) in the time delay.

Figure 4 shows a typical application – a delay-to-off timer using a thyristor. For 240V mains, you might have to use a 100V DC relay with a dropper, 220V DC relays being thin on the ground.

A complete design for a mains delay-to-on plug-in timer is shown in Fig. 5, which also indicates methods of avoiding the effects of mains and EM noise spikes. The smoother  $R_1C_1$  combines that function with spike reduction, further efforts in this direction being made by  $R_2C_2$ . A shunt regulator is built into the chip and also reduces mains noise – in the circuit shown it reduces the noise by 15000:1. Of course, a 5V supply designed to power logic as well as the ZN1034 will not present much of a problem even without the regulator, since noise spikes should not be present. As regards EM noise, pin 13 must be screened and the note gives a recommended PCB layout for that purpose.

GEC Plessey Semiconductors, Cheney Manor, Swindon, Wiltshire SN2 2QW. Telephone 0793 518000.

Fig. 5. Delay-to-on plug-in timer module, showing methods of rendering mains and EM noise harmless.

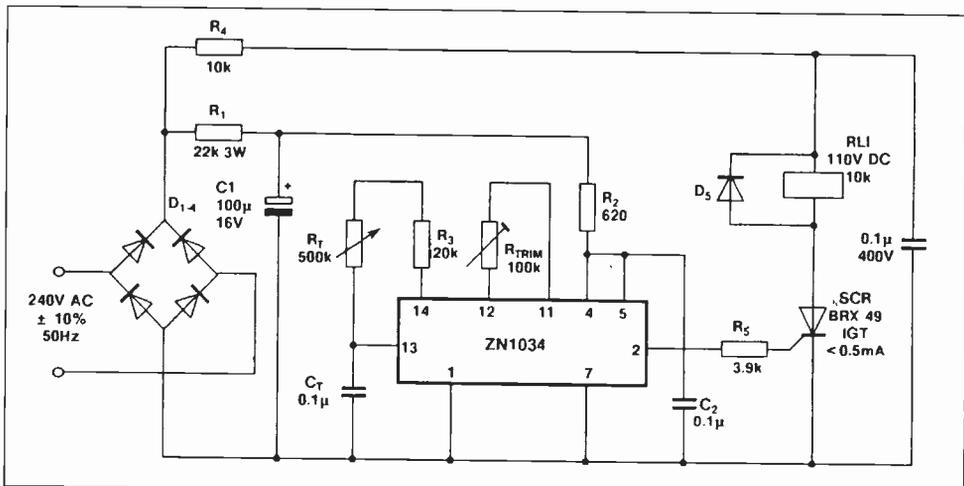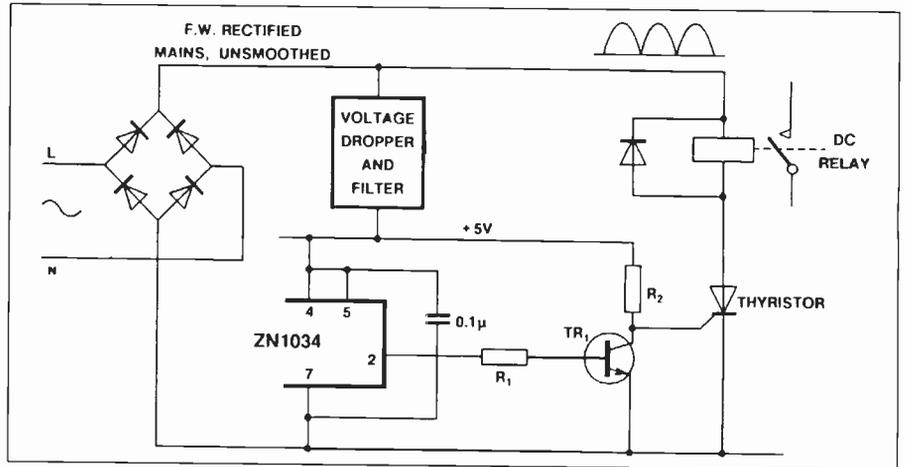

## Pressure measurement

Motorola's MPX2000 series of pressure transducers are temperature-compensated and calibrated on-chip; the MPX5100 has, in addition, its own amplifier. These units are therefore well suited to use without much extra work; indeed, the MPX5100 can be connected directly to a microprocessor to make a direct-reading pressure meter. MPX2000 units

have full scales ranging from 1.5 to 100psi and the MPX5100 measures up to 15psi, the former producing 40mV full scale and the 5100, 4V. Linearities are of the order of  $\pm 0.1$  to  $\pm 0.2\%$ .

Motorola's booklet BR121/D "Pressure Sensors" includes the circuit shown in Fig. 1, a portable manometer in which the pressure sensor provides a differential output to a digital panel meter. This will give a moderate performance, being limited to some extent by the amplifiers and power supply; for greater precision, you could use a more exotic instru-



mentation amplifier and replace the zener by a voltage regulator.

Figure 2 is the circuit of a pressure switch, meant to control compressor and pump motors and heaters in liquid level applications.

In Fig. 3, the amplifier and MC1455, which is a 555 timer replacement, form a voltage-to-frequency converter which could be driven directly by an MPX5100 but which driven in the MPX2000 case by temperature compensation and amplification circuitry. The amplified and compensated output of the pressure

Fig. 2. Pressure switch for motor control, switch point being set by  $R_{set}$ .

Fig. 1. Portable manometer using one of Motorola's MPX2000 series of pressure transducers to give a direct digital indication of pressure on the internally compensated sensor.

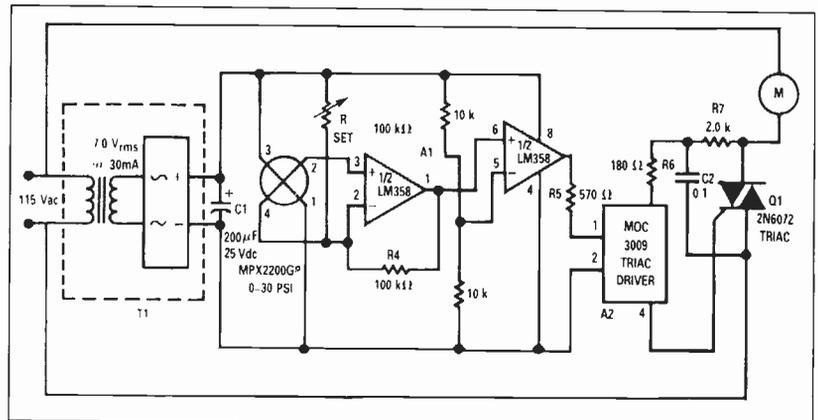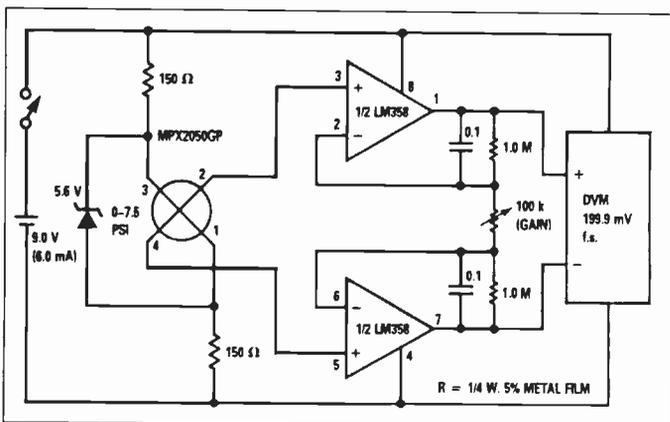

sensor drives an LM258, which acts as a constant-current source to the charging capacitor on the MC1455, so that the output frequency is a linear representation of pressure — 6V into the LM258 gives a 0.14kHz change.

Application Note AN1305 describes an evaluation board to familiarise engineers with the direct interfacing of the MPX5100 to a microprocessor. Figure 4 is the circuit of the DEVB-114 board, which shows very few externals indeed: there are simply the sensor, clock components, a few bias resistors and an LCD to provide a direct reading in pounds per square inch in 0.1psi increments. No manual calibration is needed, since the offset voltage of the sensor without applied pressure is computed at every power-up and stored in ram. MC34064P-5 is an under-voltage detector used to reset the system at switch-on and the jumpers J1 and J2 are for a slight tailoring of span by  $\pm 1.5\%$ . The application note gives full details of setting up and the microprocessor software listing in C source code.

Motorola Ltd, European Literature Centre, 88 Tanners Drive, Blakelands, Milton Keynes MK14 5BP. Telephone 0908 614614.

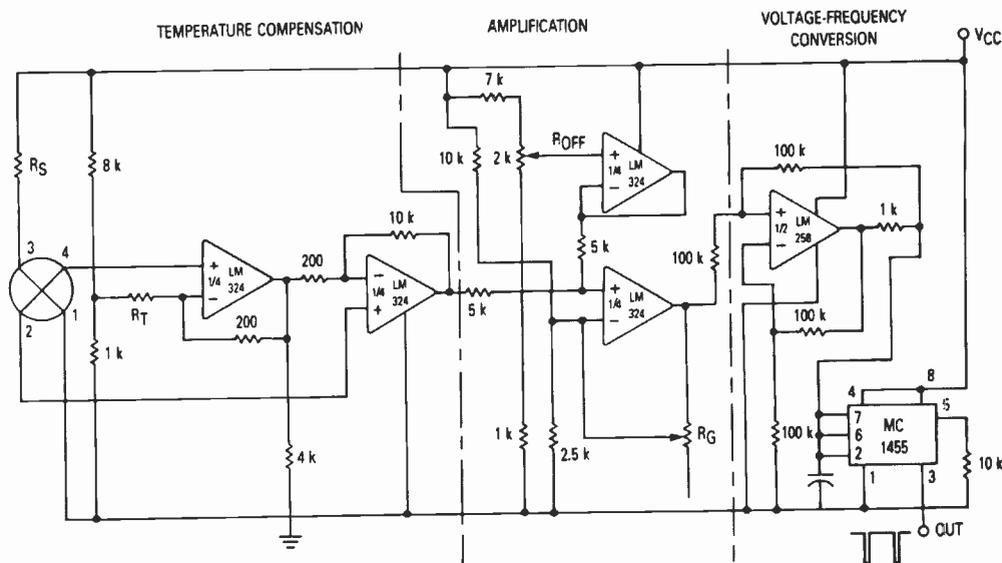


Fig. 3. Pressure-to-frequency converter using MPX2000 series. MC1455 is a direct 555 timer replacement and is used as an astable multivibrator, its frequency directly controlled by the constant-current source of the LM258.

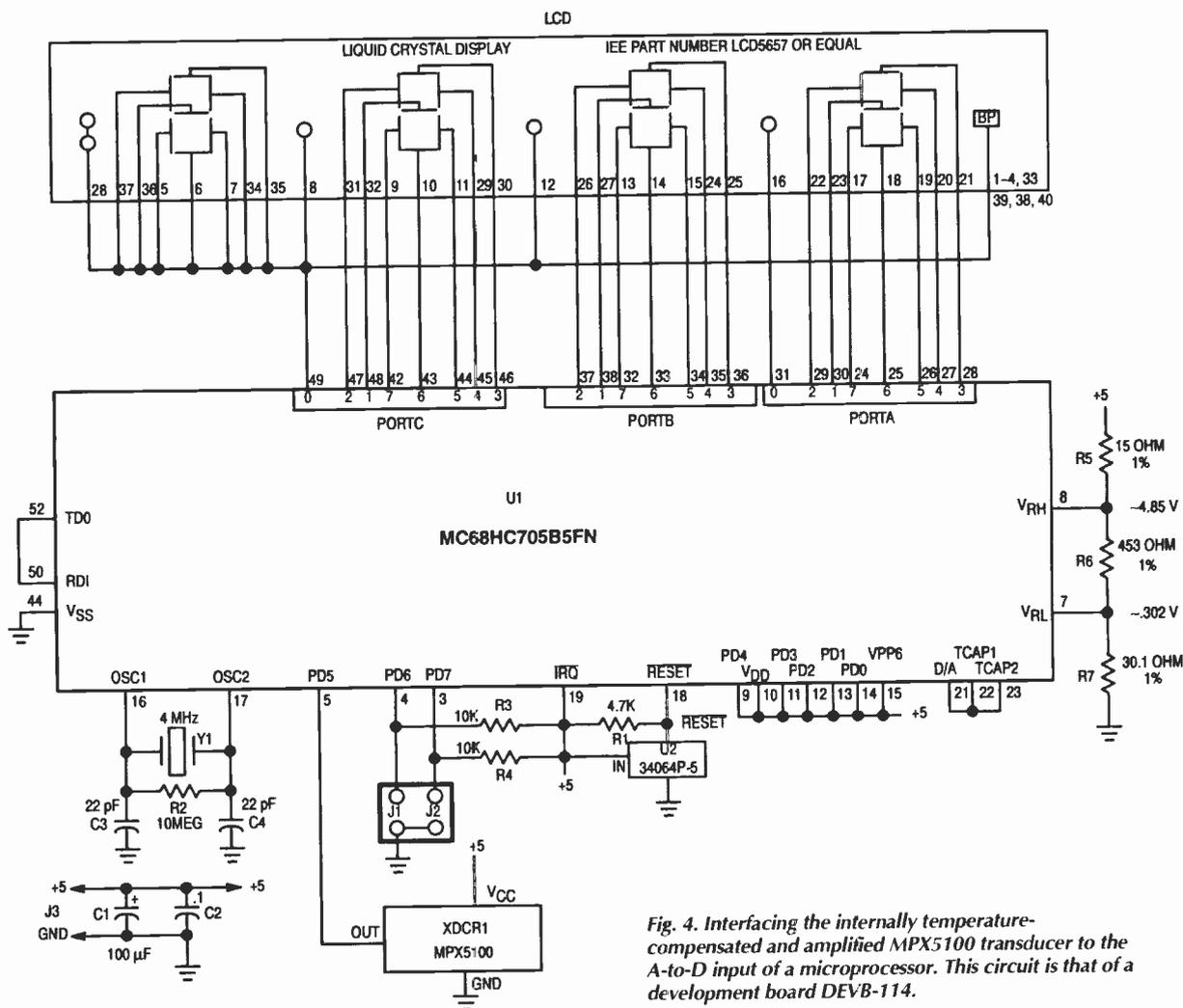


Fig. 4. Interfacing the internally temperature-compensated and amplified MPX5100 transducer to the A-to-D input of a microprocessor. This circuit is that of a development board DEVB-114.

# BARGAINS - 10 New Ones This Month

**SUPER MULTIMETER** Ex British Telecom, this is a 19-range 20k o.p.v. top grade instrument, covers AC & DC voltages, current and resistance, very good condition, fully working and complete with leads £8.50. Carrying case £2 extra (batteries not included but readily available).

**MULTI-CORE CABLES** all with 8A 230V cores so suitable for disco and other special lighting effects. With earthable woven screen and thick pvc outer. 3 core, 30p per metre, 16 core, 50p per metre, 18 core, 80p per metre, 25 core, £1 metre and 36 core, £1.50 per metre.

**VARIAC** an infinitely variable unit gives any voltage from 0-230 a.c. at ½A. Obviously an invaluable piece of equipment which should be in every workshop and probably would be except that the usual price for this is £35 plus VAT. Now is your chance to buy one, brand new, at £15 including VAT, Order Ref. 15P42B.

**ULTRA THIN DRILLS** Actually 0.3mm. To buy these regular costs a fortune. However, these are packed in half dozens and the price to you is £1 per pack, Order Ref. 797B.

**YOU CAN STAND ON IT!** Made to house GPO telephone equipment, this box is extremely tough and would be ideal for keeping your small tools. Internal size approx. 10½" x 4½" x 6" high. These are complete with snap closure lip and shoulder-length carrying strap. Taken from used equipment but in good condition, price £2, Order Ref. 2P283B.

**BUILD YOUR OWN NIGHT LIGHT**, battery charger or any other gadget that you want to enclose in a plastic case and be able to plug into a 13A socket. We have two cases, one 3½" x 2¼" x 1¼" deep, £1 each, Order Ref. 845. The other one is 2½" x 2¼" x 1¼" deep, 2 for £1, Order Ref. 565.

**SAFETY LEADS** curly coil so they contract but don't hang down. Could easily save a child from being scalded. 2 core, 5A, extends to 3m, £1, Order Ref. 846, 3 core, 13A, extends to 1m, £1 each, Order Ref. 847, 3 core, 13A, extends to 3m, £2 each, Order Ref. 2P290.

**POWER SUPPLY WITH EXTRAS** mains input is fused and filtered and the 12V dc output is voltage regulated. Intended for high class equipment, this is mounted on a PCB and, also mounted on the board but easily removed, are 2 12V relays and a Piezo sounder. £3, Order Ref. 3P80B  
**5V 2.5A POWER SUPPLY UNIT** £5. Mains Filtered, Output Regulated. Order Ref. 5P186.

**ULTRASONIC TRANSDUCERS** 2 metal cased units, one transmits, one receives. Built to operate around 40kHz. Price £1.50 the pair, Order Ref. 1.5P/4.  
**100W MAINS TRANSFORMERS** normal primaries 20-0-20 at 2.5A. or 30V at 3.5A, £4, Order Ref. 4P24. 40V at 2.5A, £4, Order Ref. 4P59. 50V at 2A, £4, Order Ref. 4P60.

**PHILIPS 9" HIGH RESOLUTION MONITOR** black & white in metal frame for easy mounting, brand new still in maker's packing, offered at less than price of tube alone, only £15, Order Ref. 15P1.

**16 CHARACTER 2-LINE DISPLAY** screen size 85mm x 36mm, Alpha-numeric LCD dot matrix module with integral micro processor made by Epson, their Ref. 16027AR, £8, Order Ref. 8P48.

**INSULATION TESTER WITH MULTIMETER** internally generates voltages which enable you to read insulation directly in megohms. The multimeter has four ranges. AC/DC volts, 3 ranges DC milliamps, 3 ranges resistance and 5 amp range. These instruments are ex British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50 each, yours for only £7.50, with leads, carrying case £2 extra, Order Ref. 7.5P/4.

**BRUSHLESS DC 12V FAN** tiny, only 60mm square, good air mover but causes no interference, £8, Order Ref. 8P26.

**MAINS 230V FAN** best make "PAPST" 4½" square, metal blades, £8, Order Ref. 8P8.

**2MW LASER** Helium neon by Philips, full spec. £30, Order Ref. 30P1. Power supply for this in kit form with case is £15, Order Ref. 15P16, or in larger case to house tube as well £18, Order Ref. 18P2. The larger unit, made up, tested and ready to use, complete with laser tube £69, Order Ref. 69P1.

**1/3 HP 12V MOTOR - THE FAMOUS SINCLAIR C5** brand new, £15, Order Ref. 15P8.

**SOLAR CHARGER** holds 4 AA nicads and recharges these in 8 hours, in very neat plastic case, £6, Order Ref. 6P3.

**FERRITE AERIAL ROD** 8" Long x ¼" diameter, made by Mullard. Complete with 2 coil formers. 2 for £1, Order Ref. 832B.

**AIR SPACED TRIMMER CAPS** 2-20 pf ideal for precision tuning UHF circuits, 4 for £1, Order Ref. 818B.

**FIELD TELEPHONES** just right for building sites, rallies, horse shows, etc., just join two by twin wire and you have two way calling and talking and you can join into regular phone lines if you want to. Ex British Telecom in very good condition, powered by batteries (not included) complete with shoulder slung carrying case, £9.50, Order Ref. 9.5P/2.

**MAINS ISOLATION TRANSFORMER** stops you getting "to earth" shocks. 230V in and 230V out. 150watt upright mounting, £7.50, Order Ref. 7.5P/5 and a 250W version is £10, Order Ref. 10P79.



## DIGITAL FREQUENCY METER.

This is a hand-held instrument with an LCD display allowing 8 digits of frequency to be read, has internal nicad batteries, and a power supply which will recharge the batteries. Ideal for field and service work as well as general and industrial applications. Has high and low BNC inputs and a plug-in antenna which enables remote tests. It covers a very wide range of frequencies: switch position 'A' covers 10Hz to 20MHz and switch position 'B' covers 20MHz to 1200MHz. Price £99, but it compares very favourably with instruments selling at over £500 by our competitors. Order Ref. 99P2.

## LIMITED SUPPLY ITEMS

are only described in our newsletter. Over 50 appear in our current issue. If you order something this month you will receive this and the next three issues posted to you free of charge.

## THIS MONTH'S SNIP

A £60 UNIT FOR LESS THAN £10 - switch mode power supply with outputs +12V at 4A, +5V at 16A and -12V at ½A. Enclosed in plated steel case, brand new, offered at a special price of £9.50 until Sept. 30th. Order Ref. 9.5P1.

## JUST ARRIVED

3 core 15A flex. Price is 10m for £2.50, Order Ref. 2.5P/3. You can have this in longer lengths, multiples of 10m up to 100m. Also available: 3 Core 20A flex, 10m for £3, Order Ref. 3P109 and 2 core 20A flex, 15m for £3, Order Ref. 3P110.

**MINI MONO AMP** on PCB. Size 4" x 2" with front panel holding volume control and with spare hole for switch or tone control. Output is 4 watt into 4 ohm speaker using 12V or 1 watt into 8 ohm using 9V. Brand new and perfect, only £1 each, Order Ref. 495.

**5RP MAINS DRIVEN** This is a shaded pole motor, £5, Order Ref. 5P54.

**POWER SUPPLY UNIT** mains in, dc out, cased 4.5V 100mA, £1, Order Ref. 104, 6V 200mA £1, Order Ref. 103, 6V 700mA, £1, Order Ref. 103A, 9V 500mA, £2, Order Ref. 2P134, 24V 200mA, £2, Order Ref. 2P4, 12V 2A, £6, Order Ref. 6P23.

**AMSTRAD POWER UNIT** 13.5V at 1.9A encased and with leads and output plug, normal mains input £6, Order Ref. 6P23.

**AMSTRAD 3.5 FLOPPY DRIVE** brand new and cased, £35, Order Ref. 35P4.

**ATARI 65XE** at 65K this is quite powerful, so suitable for home or business, unused and in perfect order but less PSU, only £19.50, Order Ref. 19.5P/5B.

**80W MAINS TRANSFORMER** two available, good quality, both with normal primaries and upright mounting, one is 20V 4A, Order Ref. 3P106 the other 40V 2A, Order Ref. 3P107, only £3 each.

**PROJECT BOX** size approx 8" x 4" x 4½" metal, sprayed grey, louvred ends for ventilation otherwise undrilled. Made for GPO so best quality, only £3 each, Order Ref. 3P74.

**12V SOLENOID** has good ½" pull or could push if modified, size approx 1½" long x 1" square, £1, Order Ref. 372.

**WATER VALVE** 230V operated with hose connections, ideal for auto plant spray or would control air or gas into tanks etc., £1 each, Order Ref. 370.

**10W ISOLATION TRANSFORMER** if you want to isolate some small piece of equipment from earth this may be what you are looking for. You can use it either with a tapped input or a tapped output. It's upright mounting and well insulated. Price £1, Order Ref. 821.

**BT POWER SUPPLY UNIT** output 9.5V AC at 600mA, in black plastic case with 13A plugs to go straight into socket and approximately 3 metres of twin output lead. Price £1.50, Order Ref. 1.5P7.

**BUILDING YOUR OWN PSU**, battery charger, night light, or any other gadget that you want to enclose in a plastic case and be able to plug into a 13A socket? We have two cases, one 3½" x 2¼" x 1¼" deep, £1 each, Order Ref. 845. The other one is 2½" x 2¼" x 1¼" deep, 2 for £1, Order Ref. 565.

**500V BRIDGE MEGGER** developed for GPO technicians the Ohmmeter 18B is the modern equivalent of the bridge megger. 9V battery operated, it incorporates a 500V generator for insulation testing and a null balance bridge for very accurate resistance measurement. Ex B.T. in quite good condition with data & tested. Yours for a fraction of original cost, £45, Order Ref. 45P2.

**EXPERIMENTING WITH VALVES** don't spend a fortune on a mains transformer, we can supply one with standard mains input and secs. of 250-0-250V at 75mA and 6.3V at 3A. £5, Order Ref. 5P167.

**15W 8 OHM 8" SPEAKER & 3" TWEETER** made for a discontinued high quality music centre, gives real hi-fi, and only £4 per pair, Order Ref. 4P57.

**FREE POWER!** Can be yours if you use our solar cells - sturdily made modules with new system bubble magnifiers to concentrate the light and so eliminate the need for actual sunshine - they work just as well in bright light. Voltage output is .45 - you join in series to get desired voltage - and in parallel for more amps.

**Module A** gives 100mA Price £1 Order Ref. BD631

**Module B** gives 400mA Price £2 Order Ref. 2P199

**Module D** gives 700mA Price £3 Order Ref. 3P42

**Module E** gives 1A Price £3.50 Order Ref. 3.5P4

**3V SOLAR PANEL** price £3, Order Ref. 3P99B.

**3 GANG .0005 MFD TUNING CONDENSER** with slow motion drive. Beautifully made by Jackson Brothers and current list price is probably around £20. Yours for £5, Order Ref. 5P189.

**STEREO HEADPHONES** extra lightweight with plug, £2 each, Order Ref. 2P261.

**BT TELEPHONE LEAD** 3m long and with B.T. flat plug ideal to make extension for phone, fax, etc. 2 for £1, Order Ref. 552.

**WATER PUMP** very powerful with twin outlets, an ideal shower controller, mains operated, £10, Order Ref. 10P74.

**STUDIO 100** by Amstrad, the ultimate disco control panel, has four separately controlled and metered channels, twin cassettes, AM/FM radio, stereo audio amplifier, phono & CD inputs, etc., regular price over £400, we have a few still in maker's packing, brand new and guaranteed, yours for £99, Order Ref. 99P1.

**0-1MA FULL VISION PANEL METER** 2½" square, scaled 0-100 but scale easily removed for re-writing, £1 each, Order Ref. 756.

**VU METER** illuminate this from behind becomes on/off indicator as well, 1½" square, 75p each, Order Ref. 366.

**EDGE-WISE PANEL METER** ideal when short of panel space only 40 x 14mm, also have built-in led, 500µA f.s.d., scaled 0-5, £1 each, Order Ref. 131.

**PCB DRILLS** 12 assorted sizes between .75 and 1.5mm, £1 the lot, Order Ref. 128.

Prices include V.A.T. Send cheque/postal order or ring and quote credit card number. Add £3 post and packing. Orders over £25 post free.

## M & B ELECTRICAL SUPPLIES LTD

12 Boundary Road, Hove, Sussex BN3 4EH

Telephone (0273) 430380

Fax or phone (0273) 410142

Telephone Order Hotline Monday to Friday until 9.00pm on 0273-430380

CIRCLE NO. 140 ON REPLY CARD

# Circuits, Systems & Standards

First published in the US magazine EDN and edited here by Ian Hickman

## Nonlinear components lower settling time of noise reduction filters

Most common method of improving S/N ratio is noise reduction by filtering. But the attendant increase in settling time can be a serious disadvantage in certain applications, such as high-speed data acquisition. A nonlinear filter is a simple way to achieve a four-to-one improvement in settling time over conventional filters.

First, consider the dynamics of a single-pole RC filter (Fig. 1a). Filtering reduces broadband or white noise by the square root of the bandwidth reduction, according to the following equations, where  $e_n$  is the total noise in  $V_{RMS}$ ,  $e_B$  is the broadband noise in  $V/\sqrt{Hz}$ , and  $f_1$  to  $f_2$  is the filter's frequency range in Hz:

$$e_n^2 = \int_{f_1}^{f_2} e_B^2 df$$

$$= e_B^2 \cdot f \Big|_{f_1}^{f_2}$$

and thus

$$e_n = e_B \sqrt{f_2 - f_1}$$

These equations show that if the frequency range is reduced,  $f_2 - f_1$ , by a factor of 100, the total noise decreases by a factor of 10.

Unfortunately, the settling time increases as the bandwidth decreases. For a single-pole filter, the time needed for the signal to settle to any given accuracy can be calculated using the following equations, where  $t_s$  is the settling time in seconds, % is the percent of accuracy at time  $t_s$  and  $R_1 C_1$  is the RC time constant in  $\Omega F$ . At time  $t_s$ ,

$$\frac{V_{out}}{V_{in}} = 1 - e^{-\left(\frac{t_s}{R_1 C_1}\right)}$$

and

$$\left( \frac{V_{out}}{V_{in}} - 1 \right) 100 = \%$$

Therefore

$$t_s = -\ln\left(\frac{\%}{100}\right) R_1 C_1$$

### Fast settling filters

Filters are often incorporated at the input of an instrument to reduce noise, for example in a DVM to clean up the DC input ahead of the measuring circuit. However, they frequently increase the settling time by an embarrassing amount: this can be substantially reduced by incorporating nonlinear techniques, as the following article shows.

IH

To determine the number of time constants required for the signal to settle within 0.01%, simply calculate  $\ln(0.01/100)$ , which equals  $-9.2$ . Thus, it takes  $9.2RC$  time constants for an input step to settle to within 0.01% of its final value.

A simple, diode-clamped nonlinear filter (Fig. 1b) can improve the settling time of a simple RC filter. When a large input step is applied to  $V_{in}$  the filter capacitor,  $C_1$ , charges faster through the forward-biased diode's low impedance than it can through  $R_1$ . When the difference between the input and output voltages becomes less than the forward-biased diode's drop (about 0.6V), the diode stops conducting, and  $C_1$  and  $R_1$  are the only active components. At this point, the circuit behaves like a normal, single-pole RC filter.


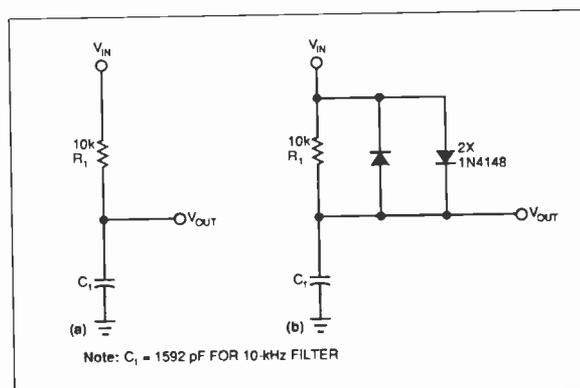


Fig. 1. Settling time of the standard RC filter (a) by adding two diodes (b).  $C_1$  charges and discharges much faster through the diode's low on-resistance than it can through  $R_1$ , thus improving settling time.

Fig. 2. To improve settling time for small inputs, as well as large inputs, this circuit allows setting of the noise threshold by choosing the values of  $R_1$  and  $R_2$ .

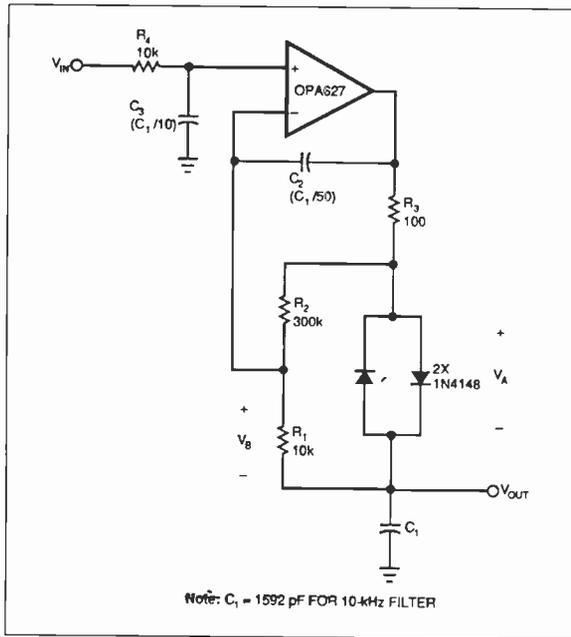

time improvement decreases for smaller input steps. When the input step equals the forward-biased diode's voltage drop, the circuit provides no improvement in settling time.

**Lower the threshold**

By reducing the threshold to below 0.6V, settling time can be improved for even smaller inputs. The improved nonlinear filter shown in Fig. 2 allows adjustment of the clamp threshold by choosing the values of  $R_1$  and  $R_2$ .

Figure 2's op amp forces the voltage at its inverting input to be the same as the signal at the non-inverting input. Small voltage differences between the input and the output voltages appear across  $R_1$ , because the diodes don't have adequate forward bias and are therefore off. Under these conditions, the filter behaves like a single-pole filter with a time constant determined by the values of  $R_1$  and  $C_1$ .

The voltage divider formed by  $R_1$  and  $R_2$  forces the voltage  $V_A$  to equal

$$V_A = V_B [1 + (R_2/R_1)]$$

When the input voltage increases (applying a step voltage, for example),  $V_A$  increases. When the voltage difference between the input and output approaches  $0.6V / (1 + R_2/R_1)$ , the diode that corresponds to the input's signal polarity will begin to conduct, and the capacitor will rapidly charge through that diode.

To determine Fig. 2's component values, noise-reduction requirements of the filter must be considered. For example, to filter the noise of a 20V step to 0.01% resolution, filter the signal's peak noise to less than 0.01% of 20V, or 2mV peak. A clamp threshold of ten times this peak, or 20mV, is an arbitrary but ample nonlinear threshold. The component values shown in Fig. 2 set the filter's threshold to 20mV. The time constant of the filter is very small, regardless of which diode is on, and the settling time is limited only by the op amp's slew rate or current limit. For a 20V step, Fig. 2's improvement in settling time is  $\ln(0.02/20) = 6.9$  time constants.

In other words, the improved nonlinear filter can improve the 0.01% settling time of a 20V step from 9.2 time constants to 9.2-6.9, or 2.3 time constants – a four-to-one improvement. Further reducing the 20mV threshold provides little additional settling-time improvement.

To use this filter successfully, noise content of the input signal must be known. If the noise of the signal is greater than the threshold – 20mV in this case – the filter will mistake the noise as a step input and fail to filter it out. Thus, Fig. 2 only behaves as the desired filter for noise signals below the threshold that is set.


If the noise exceeds 20mV, Fig. 2's circuit will not behave as an RC filter with the desired 10kHz cutoff. To prevent this situation, ensure that the noise signal at the op amp's input does not exceed 20mV by using  $C_3$  and  $R_4$  to prefilter the input.

To reduce the prefilter's effect on settling time, the values of  $R_4$  and  $C_3$  set the prefilter's bandwidth ten times higher than the bandwidth of the noise filter. At this higher bandwidth, the prefilter's effect on settling time is negligible, and the noise at the prefilter's output is  $\sqrt{10}$  times greater than 2mV, or a little over 6mV peak. (Recall that noise is proportional to the square root of the bandwidth.) A noise level of 6mV provides a comfortable margin for a 20mV threshold.

**Choose the right filter ingredients**

Op amps tend to become unstable and to oscillate when driving large capacitive loads. The network comprising  $C_2$  and  $R_3$  in Fig. 2 ensures circuit stability when the op amp is driving large values of  $C_1$  through the low impedance of

Fig. 3. Response of each filter (a) to an input step (trace A) shows the graduated settling-time improvement from the simple RC filter (trace B) to the improved non-linear filter (trace D). The double-exposure scope photo in (b) contrasts the small-signal (trace A) and large-signal (trace B) settling times of the improved non-linear filter.

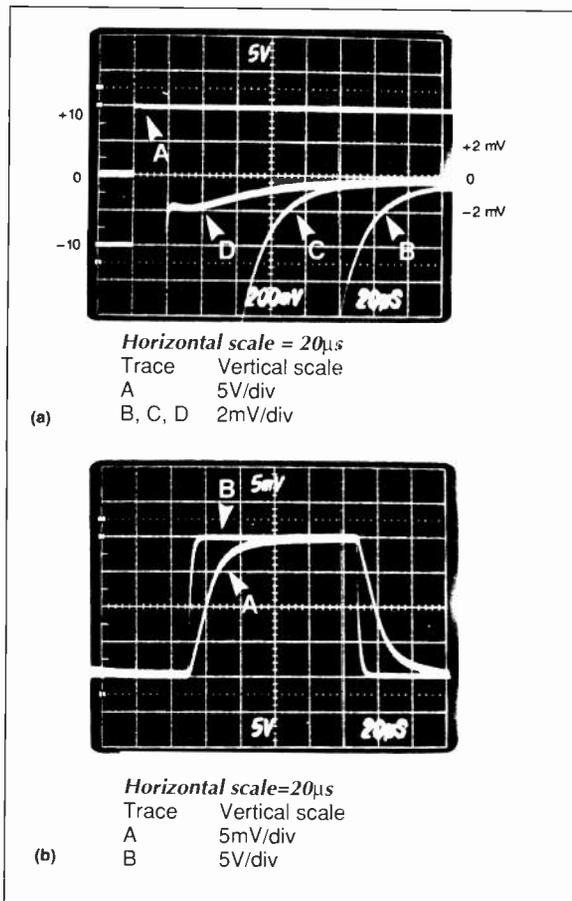

Assuming that the diode's  $R_{on}$  is very small and thus negligible, this filter's improvement in settling time depends on the ratio of the input step and the forward-biased diode's voltage. For a 20V step, -10 to +10V for example, the filter improves settling time by  $\ln(0.6/20)$ , or 3.5 time constants. In other words, for a 20V step, the simple, diode-clamped nonlinear filter shortens the normal RC filter's 0.01% settling time from 9.2 time constants to 9.2-3.5=5.7 time constants. However, as the ratio between the input voltage and the diode's forward voltage decreases, so does this circuit's advantages. The settling-

the forward-based diode network. This network may not be needed if  $C_f$  is a small value.

When choosing the op amp for the improved filter, make sure it has enough output-drive capability to charge  $C_f$ . Also, the op amp's bandwidth, slew rate, settling time, and DC precision must be adequate for the necessary filter response. Choose an op amp such as the *OPA627*, which combines DC precision, high slew rate, fast settling time and high output-drive capability. Also, notice that any unity-gain op amp's noise adds noise to the signal. If a low-noise op amp is chosen, the op amp's noise contribution is usually negligible. For example, the *OPA627* adds only 6% of the 10k $\Omega$  resistor's theoretical minimum noise to the total system noise. Remember that noise adds as the square root of the sum of the squares. Therefore, to determine how much the 4.5nV $\sqrt{\text{Hz}}$  noise of the op amp adds to the 12.8nV $\sqrt{\text{Hz}}$  noise of the resistor, calculate the square root of the sum of the squares of the combination and compare that to the noise of the resistor alone. In this case,  $\sqrt{(4.5^2+12.8^2)}/12.8=1.06$ , or a 6% increase.

Figure 3a shows the responses of the standard *RC*, diode-clamped, and improved nonlinear filters to a -10 to +10V input step. Bandwidth of each filter is 1kHz. The measurement circuit adds a gain of 100 between the scope and the circuit, so each horizontal division for traces B, C, and D represents 2mV, or 0.01% of a 20V step. Thus, the filters settle to within 0.01% when their corresponding traces lie within one division below the centre line of the scope.

For a 10kHz filter, one *RC* time constant is 15.9s. Table 1 displays the theoretical settling times of each filter.

Table 1. Theoretical time constants and settling times.

Filter type	Theoretical settling time (time constants)	Theoretical settling time ( $\mu\text{s}$ )*
Single pole RC	9.2	147
Diode clamped nonlinear	5.7	91
Improved nonlinear	2.3	37

\*Time required to settle within 0.01% of the final value for a 10kHz filter.

These tabulated settling times ignore the input slew rate and the diode forward resistance, which are good approximations for the *OPA627*-based, 10kHz filter. The actual measurements closely match the theoretical calculations.

Figure 3b is a double-exposure scope photo of the improved nonlinear filter operating with a low (trace A) and high (trace B) input signal level. The filter's response to a  $\pm 10\text{mV}$  step looks like the response of a standard, 110kHz, single-pole *RC* filter. This response is expected, because the input is equal to the threshold voltage. When the circuit operates with a high input level (a  $\pm 10\text{V}$  input step), the settling time greatly improves.

Rod Burt and R Mark Stitt, *Burr-Brown Corp*


## Analogue delay line uses digital techniques

The analogue delay line in the figure uses a digital technique to delay an analogue signal for as long as 2s, reconstructing the signal with 8-bit resolution. The product of the delay time and the bandwidth is a constant: For a 1.024kHz clock frequency (2s delay), the analogue bandwidth is 1001Hz; for the maximum 40.96kHz clock frequency (50ms delay), the analogue bandwidth is 4kHz. There is no lower limit for the clock frequency.

The clock signal drives a binary counter ( $IC_2$ ), which
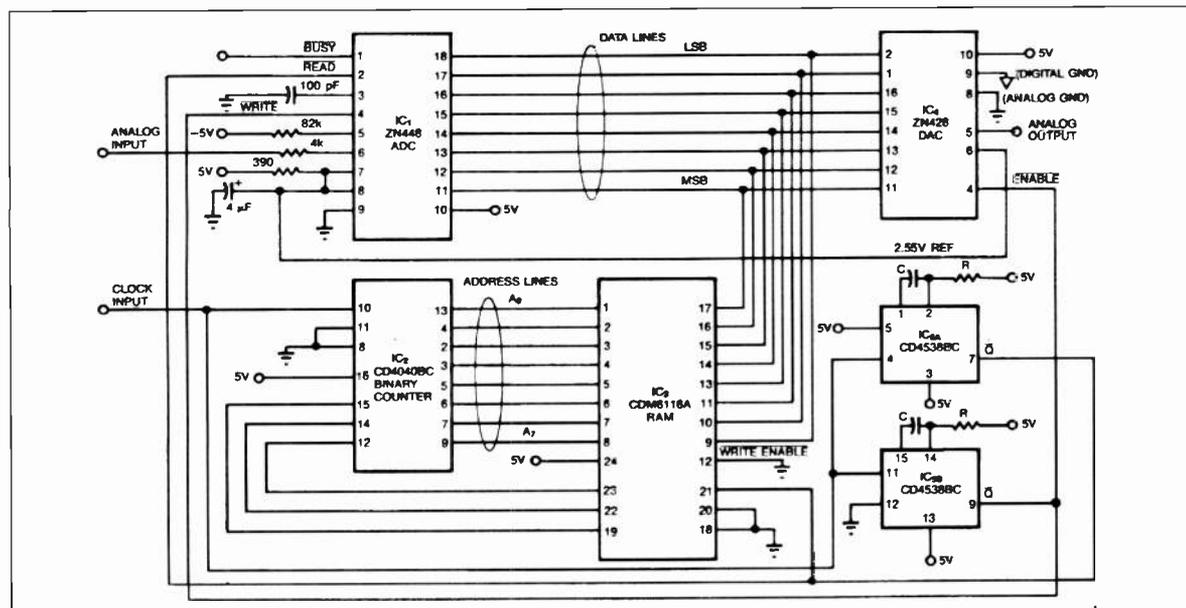
### Digital analogue delay line

This circuit will produce a delayed exact replica of a sampled input signal, without any of the approximations involved in schemes designed to handle speech – such as delta modulation and its derivatives – which cannot handle large signal energies in the upper part of the passband. By using a counter providing more address bits, in conjunction with an 8K x 8 sram or larger, the time delay product can be extended as required. IH



Analogue delay digitising a signal once per clock cycle, storing the result in a 2048 word ram, and converting one sample per clock cycle with a D-to-A converter. The resulting delay equals 2048 divided by the clock frequency.

then scans the address inputs of a 2048-byte x 8-bit ram ( $IC_3$ ). The ram writes the contents of each memo location to the D-to-A converter ( $IC_4$ ) and then reads out the results of a just-completed conversion by the 8-bit A-to-D converter  $IC_1$ . The ram reads out each data sample 2048 cycles after it is read in, so the delay is 2048 times the clock period, or 2048 divided by the clock frequency.

The clock signal also drives two monostable multivibrators in parallel ( $IC_{5A}$  and  $IC_{5B}$ ).  $IC_{5A}$  triggers on the clock's rising edge;  $IC_{5B}$  triggers on the clock's falling edge. The timing components  $R$  and  $C$  can be chosen so that each device produces a pulse of approximately 1 $\mu$ s. These pulses have the proper polarity and phase to control the A-to-D converter, D-to-A converter, and ram as shown.

The analogue input should be scaled for a range of 0 to 2.5V. The 100pF capacitor sets the A-to-D converter's internal clock to its maximum rate of 900kHz; the  $/busy$  signal (pin 1) should be monitored and capacitor value adjusted as required to achieve 900kHz. Both converters include a 2.5V voltage reference. But to improve accuracy use the A-to-D converter's reference for both. Power consumption is 120mA from the 5V supply and 50 $\mu$ A from the -5V supply. The current drain from the positive supply can be greatly reduced by adding logic to control the ram's chip-enable input (pin 18).

TG Barnett and J Millar, The London Hospital Medical College, London.

## Transistor powers low-dropout regulator

The monolithic regulator chip in the figure, combined with an external PNP transistor, forms a very-low dropout regulator, and can apply several hundred milliamps at 5V from an input as low as 5.3V. Such low-dropout performance suits battery-powered applications, because it extends the useful life of batteries having sloping discharge curves – such as sealed lead-acid and lithium batteries.

The monolithic regulator derives its supply current from the base circuit of the external PNP transistor. The feedback-resistor ratio sets the output voltage:

$$V_{out} = 1.3V \times (R_1 + R_2) / R_1$$

If the output-voltage feedback to the chip's  $V_{set}$  input is below the bandgap-reference voltage (1.3V), the supply

### Low headroom regulator

In battery-powered instruments, a regulator needing very little headroom can substantially extend the useful life of primary batteries, or allow less frequent recharging of secondary (rechargeable) batteries. This circuit can provide 100mA at 5V from an input as low as 5.1V. IH

current into  $V_{in}$  – the PNP transistor's base current – increases. The transistor multiplies this base current by  $\beta$  and delivers it to the load. The circuit's quiescent current is a function of the transistor's  $\beta$  and load current.



When there is no load, the quiescent current is typically 10 $\mu$ A. For larger load currents, the quiescent current is simply the load current divided by the transistor's  $\beta$ . The regulator chip can sink 40mA max, and when the chip's shut-down input is enabled, the circuit consumes 6 $\mu$ A typically.  $R_4$  supplies current to the chip under no-load conditions.

$R_2$  can limit the transistor's base current. The chip's  $V_{out}$  pin will try to raise its voltage level to that of the  $V_{in}$  pin when the output voltage of the chip is low. Reducing  $R_3$  has the effect of supplying larger base currents to the external transistor.

A 2N2945 can be substituted for the 2N2907 shown in the figure. With this substitution, the circuit will supply a 5V, 100mA max output from a 5.1V input.

James E Dekis, Maxim Integrated Products, Sunnyvale, Ca and Terry Blake, Motorola, Schaumburg, Il.

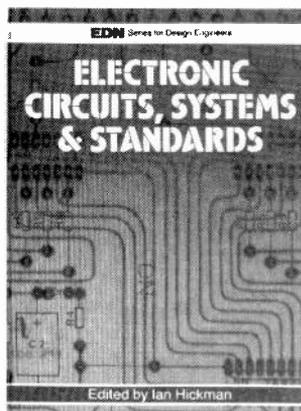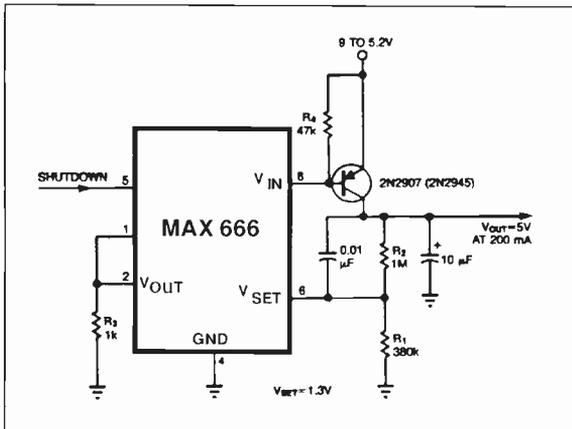A monolithic regulator chip driving a dummy load sets the base current of an external, series-pass PNP transistor; the result is a very-low-dropout regulator for batteries whose output voltage drops under load.



### Electronics Circuits, Systems & Standards

Since its appearance in 1956 the US-based EDN has established itself as a leader in controlled circulation electronics magazine. Now this "best" of EDN- with useful information on components, equipment, circuits, systems and standards - is available in a 216 page hardback publication.

Available direct by postal application to EW + WW, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS. Cost £20 plus £1.50 post and packing. Cheques payable to Reed Business Publishing Group.

Edited by Ian Hickman, published by Butterworth Heinemann Newnes. ISBN 07506 0068 3. price £20.

# Getting a word in edgeways

As telecommunications assume an increasingly digital aspect, the question of just how much material can be squeezed into a low-rate bit stream without excessive cost and quality degradation has become crucial. Decisions on standards and algorithms made now will have implications well into the 21st century.

Today, the packaging of speech and video, with their high degrees of redundancy, has moved on a long way from basic PCM. Professor C Xydeas, University of Manchester, emphasised the current level of development at a recent IEE colloquium *Speech coding - techniques and application*: "Present day techniques seek to exploit the intrinsic properties of speech signals in order to remove redundancy and thus achieve improved compression/speech quality performance."

## Mean opinion scoring

In an overview of the subject, Xydeas described use of the 1-5 scale of mean opinion score (mos) for assessing speech quality of 200Hz to 3.4kHz channels. For network (toll) channels, a mos of 4.0 or better is needed and for communication channels a score of 3.5 to 4.0. Mos values in the region 2.5-3.0 imply "synthetic" quality speech. Although still highly intelligible, this quality has a reduced naturalness and speaker recognisability, but can be transmitted at bit rates of less than 2.4kbit/s, making such vocoders suitable for HF radio circuits. For "broadcast-quality" speech a baseband of 50 to 7000Hz "offers a dramatic improvement in naturalness and intelligibility (unvoiced sounds) compared with conventional telephone speech... voice applications such as ISDN teleconferencing and loudspeaker telephones are based on broadcast quality speech and require codecs that can produce a mos score equal or better than 4.0".

Several presentations stressed that decoded speech quality is closely linked to output bit-rate and the codec complexity. As the required bit-rate decreases, codecs become ever more

complicated, with algorithms having a direct impact on implementation costs and power consumption.

To achieve good quality at the lowest bit rate requires complex processing that may introduce excessive time-delay for real-time, two-way speech.

But where the material is to be stored, good-quality speech can be recorded using repeated processing. D Y-K Wong (Enigma Ltd) demonstrated a variable rate linear prediction coder which works on four major types of segment.

Wong explained how very high coding efficiency and good quality speech reproduction on material recorded

at an average bit-rate of 3.5kbit/s (peak rate of 7kbit/s) were possible, achieving a perceptually weighted SNR of 17.5dB in the voiced region. This would, for example, enable a "voice dictionary" to be recorded on compact disc.


## Real-time communications

For real-time communications, Liverpool University and BT are jointly developing a pitch synchronous scheme for voiced frames and celp (codebook excitation linear prediction) for coding unvoiced speech frames. The scheme has been tested in simulation, obtaining good communications-quality speech at 3.1kbit/s. The simulated coder produces reconstructed speech of good and natural quality.

Nigel Sedgwick (Cambridge Algorithmica) described a formant vocoder being developed to operate at 600bit/s. Such vocoders are mainly of interest for military use where communication bandwidth is at a premium, for example over tactical HF radio using frequency hopping as an electronic counter-counter-measure where users would be prepared to accept the disadvantages of increased cost and lower speech quality compared with vocoders operating at 2.4kbit/s. The work is supported by a contract from RSRE Malvern covering specification, design and implementation of a non-real-time

*Speech quality versus bit rate for telephone bandwidth speech codecs: from An overview of speech coding techniques, C Xydeas.*

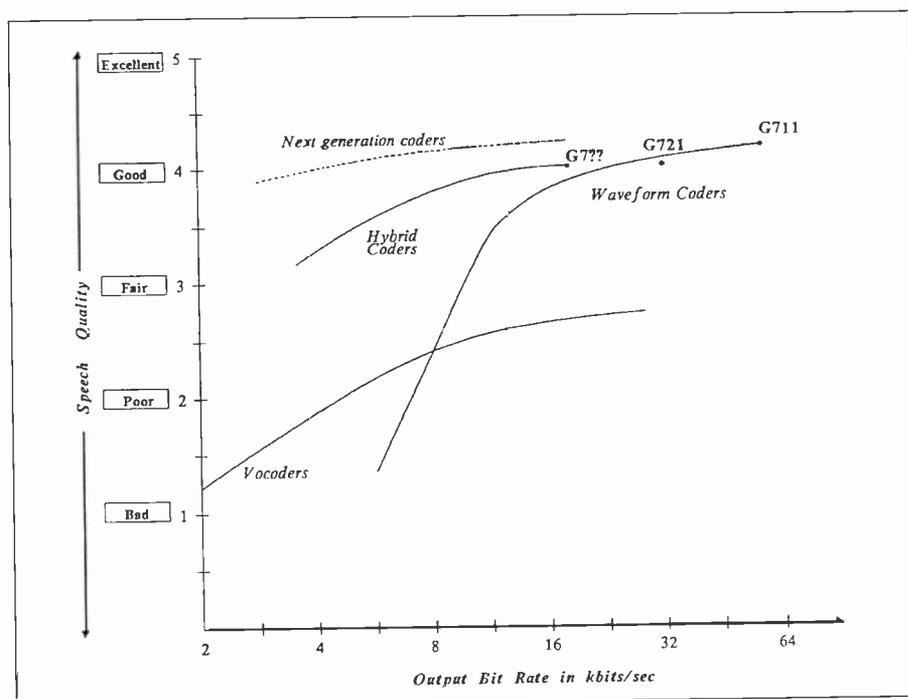Pat Hawker reports on development success in reducing the bit-rate of digital speech



software simulation of the vocoder.

The formant analysis adopted draws on investigations, later abandoned, by the Joint Speech Research Unit (GCHQ) at Eastcote and Cheltenham in the 1970s and early 1980s. It includes variable frame-rate (VFR) coding using a dynamic programming algorithm to select, simultaneously, the optimal sequence of frames to transmit, plus the use of a vector-quantised codebook of formant frequencies and amplitudes. As part of the codebook generation software, there has been an early implementation of a scalar-quantised VFR vocoder but with less complex coding of the side information and with an effective data rate of 1320bit/s. At this level, speech from good quality recording remains intelligible but leaves much to be desired. With parameter tuning etc a VQ/VFR vocoder at 600bit/s should be better.

**Broadcasting in bits**

Simon Shute (BBC) gave a rather different meaning to "low" in speaking of "low bit-rate digital audio broadcasting (dab)". He noted that the accepted standard for coding audio in studio applications uses a sampling frequency of 48kHz, with up to 20bits per audio sample – although most current equipment can handle only 16bit. This AES/EBU digital audio interface standard when implemented for a stereo pair and multiplexed with the necessary


**Cryptic beginnings**

It is now almost 45 years since Claude Shannon defined, in the *Bell System Technical Journal*, the intellectual framework for efficient packaging and transmission of electronic data. As noted recently by John Hogan in *IEEE Spectrum*, Shannon's classic paper "The Mathematical Theory of Communication" still stands as a beacon of the communications age.

Shannon, like our own Dr Alan Turing, gained an insight into digital communications during his wartime work in the field of cryptography – in his case while working on the "Green Hornet" (project X or Sisaly) long-range HF secure speech system in which "one-time" keys in the form of digital bits were distributed on disc recordings.

Green Hornet was used, for example, in the later years of the war to provide a secure telephone link that was almost certainly the first-ever crude implementation of Alec Reeves's pulse code modulation patent, between London and Washington DC. Built around thermionic valves, the London terminal behind Selfridge's required 30 racks of equipment and consumed many kilowatts of electricity to provide a few milliwatts of just-intelligible speech.

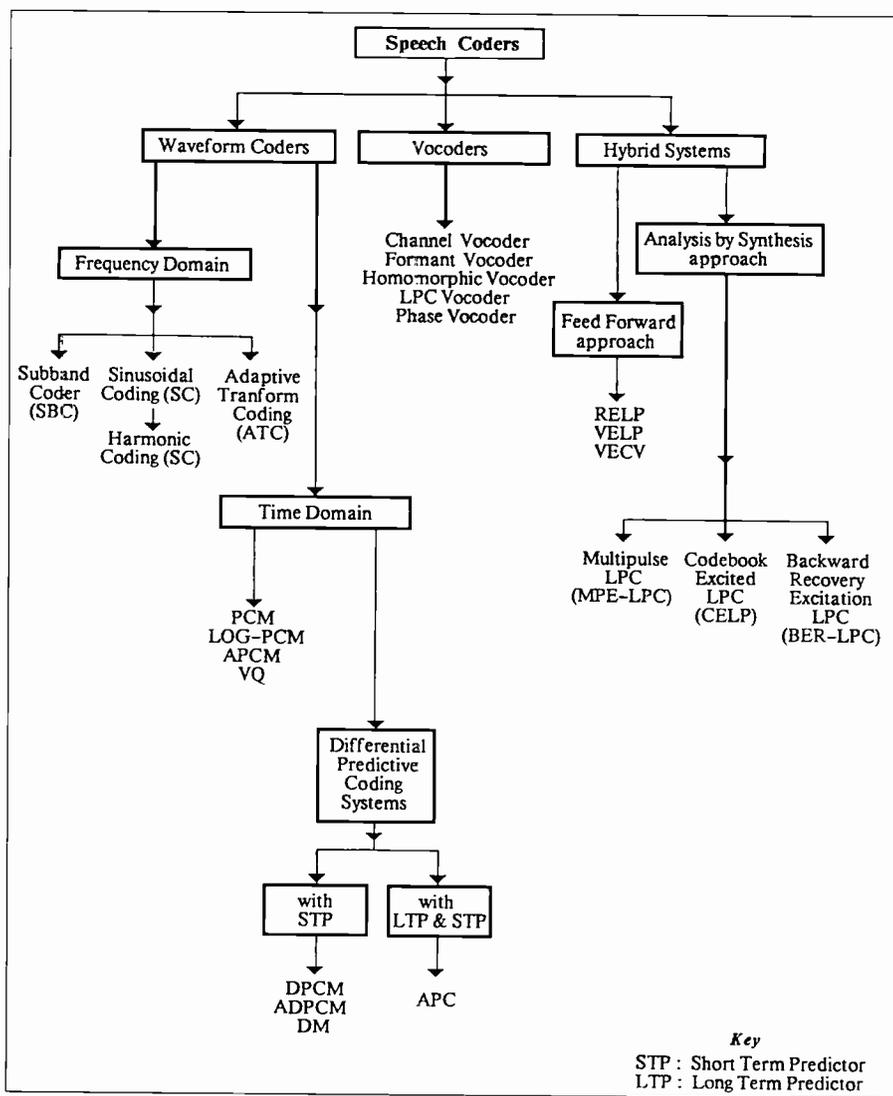But Shannon has acknowledged that it was his cryptographic work that led him to develop his theory of communication. He realised that, just as digital signals could protect information from prying eyes and ears so codes could also be used to package information more efficiently, allowing more of it to be carried over a given channel.



Speech coding methodologies. C Xydeas.

framing, signalling and control information represents a bit rate of 3.072Mbit/s. It is against this yardstick that broadcast engineers judge their "low bit-rate" coding systems.

Shute concentrated on musicam, the coding system chosen for audio coding for the European musicam/cofdm dab system developed by the Eureka 147 Group as a means of delivering to listeners CD-quality stereo at a bit-rate of around 200bit/s per stereo channel. He emphasised the advantages of using cofdm transmission with its high resistance to multipath problems that continue to place severe limits on the performance of pilot-tone FM received in moving vehicles.

Incidentally, he admits that the addition during the 1980s of a vertically polarised component to BBC VHF/FM transmission has "to some extent" proved counter-productive. (His comments fulfilled the fears I expressed

in *Multipath distortion – does polarisation matter?*, *Wireless World*, April 1981, pp. 83-85 which brought on my head the wrath of the Directors of Engineering of both the BBC and the IBA!)

The musicam/cofdm system is also much more spectrum-efficient than analogue FM, permitting six multiplexed stereo-channels to

be accommodated in a bandwidth of 1.5MHz compared with 2.2MHz per single national channel for FM. Because cofdm is intrinsically immune to delayed echoes resulting from reflections, it is equally immune to co-channel signals arriving from other transmitters in adjacent areas, and can thus be re-used for as many transmitters as are needed to provide national coverage.

Shute admits that the BBC is seeking a VHF channel for terrestrial dab (possibly in Bands I or III) with the original proposal for direct reception from a non-synchronous-orbit satellite now on the back-burner, although national distribution of the digital signals would most likely be based on a satellite. The BBC believes that dab may eventually supersede FM for national services in Band II, although FM transmissions are likely to continue for a number of years.

He says that a number of hurdles remain before dab can be introduced in the UK. But its technical and economic attractions are such that he is convinced that the necessary steps will be taken and that we can look forward to a dab service beginning in the mid-1990s, with significant area coverage and affordable receivers for home and car reception. ■

# PATENT NEWS

**Signal receiver for satellite broadcast.** In UK patent 2235340 Funal Electric Engineering Co Ltd. describes a signal receiver. It has probe antennas provided in a waveguide for receiving differently polarised waves such as vertical and horizontal polarised waves. The probe antennas are arranged to intersect at right angles in the waveguide where each antenna is connected to input terminals of an amplifier. According to the structure, it is possible to receive both vertical and horizontal polarised waves simultaneously without using a rotational probe antenna. In a modification, clockwise and anti-clockwise circular polarisation waves can be received. The amplifiers may each include a gallium arsenide field effect transistor selectively switched on to receive the required vertical or horizontal polarised waves.

**FMCW intruder alarm system.** In U.K. patent 2236926 GEC-Marconi Ltd. describes a range-sensitive intruder alarm system using FMCW radar. A sinusoidal FMCW signal is generated and mixed with

reflected signals to produce an output signal comprising a series of frequency components which correspond to sidebands of the FMCW signal. Each frequency component has a unique amplitude variation with the range of the source of the return signal. Selected frequency components are filtered and their amplitudes compared to define a range limit of the system. The alarm is triggered by the output of a threshold circuit which monitors the amplitude of one of the frequency components. Triggering of the alarm is inhibited if the comparison reveals a disturbance occurring outside the defined range limit. A second range limit may be defined by comparing the amplitude of a third frequency component with one of the first two.

**Detection circuitry.** In UK patent 2221294 Formula Systems Ltd describes detection circuitry with improved range and signal-to-noise ratio. It includes a number of light emitting diodes connected in series and powered by a current source gated by an oscillator and a number of photodiodes. Each photodiode has its own separate

detection circuit which is gated by the oscillator and AC decoupled by capacitors to filter out the DC content of sunlight and the AC content of fluorescent artificial lighting. Summing means sum the outputs of the detection circuits so the resultant output signal is increased by a factor equal to the product of the number of light emitting diodes and the number of photodiodes, over the situation where only one diode of each type is used.

**Capacitance measuring.** In UK patent 2223320 Northern Engineering Industries describes the measurement of line capacitance, eg of a telephone line, using a known capacitance in series with the line conductors. An oscillatory signal sent to the conductors through the known capacitance and an output current signal is obtained, dependent on the line capacitance. After passing the output through amplifying and phase sensing stages the output signal in phase with the input is obtained and is scaled to drive a meter. An output voltage signal from the line conductors is used to determine line capacitance.

## FREE TO SUBSCRIBERS

### Electronics World offers you the chance to advertise **ABSOLUTELY FREE OF CHARGE!**

Simply write your ad in the form below, using one word per box, up to a maximum of twenty words (remember to include your telephone number as one word). You must include your latest mailing label with your form, as this **free** offer applies to private subscribers only. Your ad will be placed in the first available issue.

This offer applies to private sales of electrical and electronic equipment only.

Trade advertisers should call **Pat Bunce on 081 652 8339**

All adverts will be placed as soon as possible. However, we are unable to guarantee insertion dates. We regret that we are unable to enter into correspondence with readers using this service, we also reserve the right to reject adverts which do not fulfil the terms of this offer.


Please send your completed forms to:  
Free Classified Offer: Electronics World, L327 Quadrant House, The Quadrant, Sutton  
Surrey SM2 5AS



# ARTICLES FOR SALE

## PRODUCTION/A.T.E. SECOND USER EQUIPMENT

### HUGE SAVINGS ON NEW PRICES

PRODUCTION EQUIPMENT		TEST EQUIPMENT	
BLAKELL LS210 c/w LS34 Assembly Station	£895	TEKTRONIX 2445 150MHz Oscilloscope	£1,350
BLUNDELL Cromatic/Vacuclamp Package.	£5,500	TEKTRONIX 2465 300MHz Oscilloscope	£1,995
DEK 245 (New in Box)	£5,000	Completely refurbished, Tested & Calibrated, Re-sprayed cabinet, Manuals; Probes and accessories as supplied new. Packed, ready to ship. Carriage £20 (UK Mainland)	£ F.O.A.
Screen Printer		Calibration certification available	
DEKXON Automated Horizontal Warehouse Storage System	£1,190	MARCONI 2019 1GHz Signal Generator	£2,000
DYNAPERT 118 Pick and Place Machine	£8,750	MARCONI 2371 200MHz Spectrum Analyser	£2,350
DYNAPERT 318HR Pick and Place Machine	£29,975	H.P. 3325A Function Generator	£2,650
DYNAPERT 500 Pick and Place Machine	£16,500	PHILIPS 3320 250Ms/s DSO	£2,995
FISCHER Betascope 870C With Z5NGB2 Platform	£2,995	<b>ENVIRONMENTAL TEST</b>	
ICI SCREENKLENE A0 Solder screen cleaner	£1,450	A.C.E. 350litre Burn-in Oven	£995
ICI 1214 Vapour Phase Reflow Tank	£2,550	A.C.E. -20 to +150 C Chamber	£2,900
ICI 2818 UV 28 Ultrasonic cleaning plant	£1,995	RINGWAY Cold Chamber/Hot and Humid Chamber	£ call
UNIVERSAL 6241A Sequencer/Axial inserter	£45,000	<b>ATE</b>	
UNIVERSAL 6241B Sequencer/Axial inserter	£45,000	GENRAD 2270, 2271, 2272, 2275, 2276	£ call
UNIVERSAL 6348A Sequencer/Radial inserter	call	MARCONI 80X 1024 Test Points	£28,000
UNIVERSAL 6772 Multimod 3" 6"	£20,000	MARCONI 540 Midata 256 Digital 768 Universal	£ call
DEK 255 Pass Thru Brand New/unused	£28,000		
UNIVERSAL 6348A 40 ssn. Radial inserter	£82,500		
ROYONIC Light guided assembly benches	£ call		
HELLER 715 Axial Lead former	£2,800		

See latest issue of Buyers News for full listing and Terms & Conditions. Prices exclude VAT. Buyer's Premium not included.

**BUYERS NEWS Tel: 071-284 4074 (UK)**  
**Fax: 071-267 7363 (UK)**  
**146 Camden Street, London NW1 9PF**



# SERVICES

## SERVICES OFFERED of an ENGINEER

for installation, commissioning and maintenance.  
 UK/overseas.  
 Daily Rates.  
**MOBILE: 0831 869788**  
**TEL/FAX: 0333 424797**

## Classified Advertisers please note

## The Sept. issue of ELECTRONICS WORLD + WIRELESS WORLD

**will close for press on Thursday 6th August 1992**

**To reserve your space telephone Pat Bunce on 081-652 8339**

# FREE PRIVATE CLASSIFIED

**RACAL RA 17** Communication Receiver, good condition, £140. Tel. 0702 529299

**OSCILLOSCOPE PORTABLE** Tektronix 453, dual channel 50MHz, good condition. £230. Tonbridge: 0732 353970.

**EPROM PROGRAMMER** Stag PP28 16K to 64K output/input RS232. £150.00 ono. Phone Ray 0903 883986 (W. Sussex).

**405-LINE TV CAMERAS, Monitors,** etc. Wanted. Andrew Emerson, 71 Falcutt Way, Northampton, NN2 8PH. Tel. 0604 844130. Fax 0604 821647.

**TRIO R2000** with VHF VC10, narrow CW filter, compare £800 New. First offer £400 must collect, Lancashire. Tel 0706 218290 evenings.

**TEKTRONIX 581A** oscilloscope, complete, but no EHT, plus other components. Transformers etc. free if collected. Telephone Witham (0376) 5115511.

**MARCONI 2437** 100 MHz Timer/Counter £125.00. HP 651B Test/Generator 10Hz-10MHz £60.00 perfect condition with manual. Chandran 28700 Houville-La-Branche, France. Tel 37.25.91.04.

**PHILLIPS ENGINEERING** Development system, Unix-based, hardware emulation pods, Pascal and assembler for 609 and 8085 processing, printer. £1,200. 051-652-4324.

**MANZA SEVEN** Segment LED displays 0.3 inch red common anode LH DP similar RS587-894 brand new 70p each. £15.00/25. Tel: 0438-812730.

**ALTECH 707** Spectram Analyzer 10MHz to 12GHz kit for 26GHz, £1,900. Tel 0444 412460.

**KENWOOD TS-5995 HF TX** VGC £120.00. R532 VHF Airband RX £90.00 pp. URR35 UHF RX 220-399MHz £220. Righy, Tel: 0224-589947.

## Please ring if what you want is not on this list!

IBM COMPATIBLE M/C's		NORTHWEST COMMUNICATIONS	
286	£395.50	<b>Specialists in Cellular Communications - Cellular Repair/Maintenance - Computer Sales/Repairs - Phone Systems - Facsimiles PX Welcome</b> Balceder House, Goulding Avenue, Leyland PR5 2HE Telephone: (0772) 623 143 (5 lines) Fax: (0772) 621 488	
386	£447.00		
486	£579.00		
All above systems come with VGA Mono, 20meg H/Drive, Keyboard etc.			
<b>OR FOR THE DIY ENTHUSIAST COMPLETE KITS SUPPLIED</b>		<b>10 off OLIVETTI 9-P N PRINTERS Special Price £115.00</b>	
286	£371.00	<b>MS DOS 6.00 THIS MONTH'S GIVEAWAY Price £31.95</b>	
386	£417.00		
486	£540.00	<b>BARGAIN BASEMENT Used Units</b>	
<b>MICE £16.95</b>		Amstrad 1512 mono 20meg hard drive £345	
<b>MOTHERBOARDS</b>		Amstrad 1640 col. 30meg hard drive £395	
286 16	£49.40	IBM PS2 Model 30 20meg hard drive, colour VGA £365	
386SX-25	£84.50	<b>FLOPPY DRIVES</b>	
386SX-33	£97.50	1.44 3 1/2" £29.90	
386DX-33	£149.50	1.2 5 1/4" £39.00	
486SX-20	£156.00	360K 5 1/4" £19.50	
486SX-25	£175.50	<b>CASE &amp; PSU</b>	
486DX-33	£403.00	Slimline desktop £53.50	
<b>IO &amp; VIDEO CARDS</b>		Standard desktop (very high quality) £54.60	
Super IO 25/1/PI/IG/IDE	£14.95	Mini tower (modern design) £71.50	
IO 25/1 part 1 game	£9.95	Full tower £84.50	
IDE/FDD 2F/2HDD	£9.95	<b>HARD DRIVES</b>	
256 video card	£29.95	MF/M 20meg £49.00	
512 video card	£32.95	IDE 40meg £130.00	
1M video card	£52.00	IDE 70meg £162.50	
MF/M card/2FD (inc. cables)	£32.00	IDE 100meg £208.00	
<b>KEYBOARDS</b>	£22.00	IDE 200meg £383.50	

Brand new boxed AMSTRAD 286DX 65meg hard drive, VGA monitor, Windows 3.1 £525

SVGA col £130.00  
 Larger hard drives £8.00  
 Memory 1meg £30.00

Brand new boxed AMSTRAD 286DX 65meg hard drive, VGA monitor, Windows 3.1 £525

MS DOS £42.00

All prices subject to VAT and + postage/packing. All systems carry a 1-year warranty. We are major suppliers of computer equipment. Please phone or fax with your enquiries. Access/Visa please add 2.5%.

### Technical & Scientific Supplies

TSI Correlator Model 1015C	£50
Hot film probes, hot wire probes	from £10
DIM 41612 Connectors. 3-row AC 64W skt + plug wired, used	£2
Ovens, testing, various conditions sizes	£20 to £260
AC Calibrator HP 745A	£1200
NIM Bins, NIM power supplies	£45 to £95
HP 8600 computer	£500
Accelerometer Sundstrand Q-Rex 979-1200-001	New £550
Pressure Transducer 10psi vented gauge B&H 4-366	New £75
Other Pressure transducers, mostly low ranges	from £10
B&K microphone 1/8 inch 4138, with UA0160	Unused £500

Hire Services Also Valves, Components, etc.  
 All prices are ex carriage and VAT.  
 Lists now available, please write/fax/phone  
 Technical & Scientific Supplies, PO Box 19, Mythe, Southampton, Hampshire SO4 6XQ. Tel: (0703) 848 666. Fax: (0703) 897 073.

# ARTICLES WANTED

**STEWART OF READING**  
 110 WYKEHAM ROAD  
 READING, RG6 1PL.  
 TEL: 0734 68041  
 FAX: 0734 351696

**TOP PRICES PAID FOR ALL TYPES OF SURPLUS TEST EQUIPMENT, COMPUTER EQUIPMENT, COMPONENTS etc. ANY QUANTITY.**

# WANTED

Receivers, Transmitters, Test Equipment, Components, Cable and Electronic, Scrap Boxes, PCB's, Plugs and Sockets, Computers, Edge Connectors.

**TOP PRICES PAID FOR ALL TYPES OF ELECTRONICS EQUIPMENT**

A.R. Sinclair, Electronics, Stockholders, 2 Normans Lane, Rabley Heath, Welwyn, Herts AL6 9TQ. Telephone: 0436 812 193. Mobile: 0860 214302. Fax: 0438 812 387

**WANTED: VALVES, TRANSISTORS, I.Cs** (especially types KT66, KT88, PX4, PX25). Also capacitors, antique radios, shop clearance considered. If possible, send written list for offer by return. Billington Valves, phone 0403 865105. Fax: 0403 865106. See adjoining advert.

**Tel: 081-652-8339**  
**Fax: 081-652-8931**

# Versatower:

A range of telescopic towers in static and mobile models from 7.5 to 36 metres with tilt-over facility enabling all maintenance to be at ground level.

Designed in accordance with CP3 Chapter V, part 2. 1972 for a minimum wind speed of 140 kph in conditions of maximum exposure and specified by professionals world-wide where hostile environments demand the ultimate in design, quality and reliability. Suitable for mounting equipment in the fields of: Communications, Security surveillance - CCTV, Meteorology, Environmental monitoring, Geographical survey, Defence range-finding, Marine and aero navigation, Floodlighting, Airport approach lighting. Further details available on request.

**STRUMECH ENGINEERING LIMITED**  
 Portland House, Coppice Side, Brownhills Walsall West Midlands WS8 7EX, England  
 Telephone: Brownhills (0543) 452321  
 Telex: 335243 SEL.G  
 Fax: 0543 361050



**TATUNG TCS8000 386 COMPUTER SYSTEM last few at £249**

386DX with 102 keyboard manuals, 210 watt PSU, I/O card, hard and floppy controller (please state MFM, ESDI, IDE or SCSI), 1 or 1.4 Mbyte floppy drive, 1 Mbyte RAM (upgradable to 16 Mbyte), eight slots, MS-DOS, 16 MHz clock £249, with 2 Mbytes RAM £269, 4 Mbytes RAM £289, 20 MHz version 2 Mbytes RAM £299. Fitted with 62 Meg hard drive add £100. Stocks limited - please hurry.

**MATMOS 25 MHz 386 SYSTEM**

Latest style high quality 386 DX computer with AMI Bios, 2 serial, 1 parallel ports, 1 Mbyte RAM, eight slots, Hard and Floppy controller (state SCSI, ESDI, MFM or IDE), 1.2 or 1.44 Mbyte floppy drive and small footprint luxury desktop case £319.

**TOP SPEC. 486 SYSTEMS**

20 MHz 486 SX system, 64K 1 Mbyte RAM, 1.44 Mbyte floppy drive, I/O card etc. £449  
33 MHz DX 486 cache system, with 1 Mbyte RAM £599, 50 MHz DX 486 cache system £849  
Phone for details and a quote for complete system to your requirements.  
Carnage on systems £15. See below for add-ons and other stock items.

**486 CAD/DTP SYSTEM WITH 1280x1024 MONITOR**

486 33 MHz cache system with 91 Mbyte Seagate hard drive, 3.5-inch 1.44 floppy, 4 megs RAM (upgradable to 32 Megs), tower case, 102 keyboard, 2 serial, 1 parallel ports, OPTI chipset, AMI bios, Microfield Graphics T8 colour graphics controller with 2 Mbytes video RAM and 8 MIPS processor, Hitachi 15-inch ultra high resolution monitor to display 1280x1024 non-interlaced. Will drive Windows 3/1, ACAD etc. Cancelled defence order limited stocks £1399. Ask for quote leaflet\* or quote for machine to your spec

**HIGH SPEED A4 FLATBED SCANNER**

AVR-302 high-resolution flatbed scanner. Linear CCD element scans 300 DPI with 32 grey shade dithering. Supplied complete with Megascan high-speed card with 1.3 Mbyte of RAM on board and powerful image manipulation software. Will output to TIFF, PCX and GEM files or provide OCR function. £299 (original cost over £1500) (carr £9.30).

**FLOPPY DISK DRIVES**

360K 5.25-inch IBM standard half-height drive £29.95 (carr £3.50)  
720K 3.5-inch Citizen OSD third-height drive for XT or AT (NOT Amstrad 1512/1640) £24.50 (carr £3)  
1.44 Mbyte 3.5-inch Citizen OSD 38C third-height drive for ATs, grey bezel £39.95 (carr £3)  
1.2 Mbyte 5.25-inch Panasonic half height £39.95 (carr £4)  
Fitting kit for 5.25-inch space suitable all Citizen 3.5-inch drives inc. cable adaptors £4.99 (carr free with drives) IBM standard floppy disk drive cable £3.

**HARD DISK DRIVES**

MFM: 10 Mbyte NEC 5124 5.25-inch £29, 62 Mbyte Micropolis 1324A 5.25 full height £129 - £100 in systems.  
RL: 30 Mbyte NEC 5127 5.25-inch £89.  
SCSI: 20 Mbyte Miniscrbe 92255 3.5-inch £69.95, 91 Mbyte Seagate/Imprimus ST2106N 5.25-inch £189, 330 Mbyte Seagate ST4376N 5.25-inch full height £399.  
ESDI: all with 16-bit high speed controllers - 94 Mbyte Seagate/Imprimus ST2106N 5.25-inch £209, 115 Mbyte NEC D3661 3.5-inch £239, 141 Mbyte Micropolis 1355 5.25-inch full height £229, 160 Mbyte Micropolis 5.25-inch half-height £279. Access time on ESDI drives 17 msec or better (carr on hard drives £5), HDD cable set £5.

**DISK DRIVE CONTROLLER CARDS (carr £2.50)**

XT MFM £37.50, XT RLL £37.50, XT SCSI £29.50, AT MFM £19.95, AT IDE £12.95, AT SCSI £37.50, AT ESDI (Cache) £49  
Multi SCSI card for hard drive, CD, WORM, tape etc. Future Domain firmware. £49.  
High transfer rate intelligent SCSI card supports all devices under MS-DOS, Unix, OS/2 and Netware. £139. As above with SCSI and IDE interfaces on one card £149. New Ultra-fast (33 msec) SCSI cache cards expected soon. Also EISA cache controllers.

**IBM COMPATIBLE AT MOTHERBOARDS, CARDS etc**

66 MHz 486 DX2 baby size motherboard with 256K cache, Co-processor built in. Fan cooled CPU. £649, Landmark 220 MHz.  
33 MHz 486 DX baby size motherboard with extra 64K cache. Floating point co-processor built into CPU. Eight expansion slots. OPTI VIB chipset. £449 (carr £5), 50 MHz DX or DX2 P.O.A.  
20 MHz 486 SX motherboard. The 486 SX is the same as the DX but without the Co-Processor £199 (carr £3.50)  
40 MHz 486 SX motherboard as above but twice the speed! Fan cooled CPU £249.  
20 MHz 386 motherboard, accepts up to 8 Mbytes SIMMS RAM, £99, 25 MHz £129 (carr £3.50).  
1 Mbyte RAM for 386/486 (70ns) £24.  
EISA 486 top spec EISA systems now in stock, please ring for quote on a system  
AT MULTI I/O card with 1 parallel, 2 serial, 1 game, 2 floppy, IDE hard drive £19.95.  
AT I/O card, parallel, 2 serial, game £14.95.  
Mono graphics card £12.95 (all carr £2).  
Mouse Microsoft compatible, serial with all software £14.95 (carr £4).  
Keyboard 102-key UK, top quality click action, £29.95 (carr £4).

**NETWORK PRODUCTS**

Ethernet card Novell NE-2000 compatible 16-bit £89 (carr £2). Novell Lite network software £65. All network cables and connectors in stock.

**AT/XT CASES WITH PSU**

Desktop with 3x5.25-inch and 1x3.5-inch bays, latest styling, £34.95. With 200W psu £59 (carr £6.50).  
Luxury desktop as above, with psu, but to accept full size motherboard, small footprint, £89. Mini tower £69 (carr £6.50).  
Full size tower with 6x5.25-inch bays, 230W psu, digital speed display, suits all motherboards inc. 486. £109 (carr £10)

**INTEL 386 PROCESSOR AND 387 CO-PROCESSOR**

(386 and 387 processors extracted from new systems and guaranteed 1 year)  
20 MHz 386-20 DX cpu £49 (carr £1)  
20 MHz 387-20 co-processor £39, 25 MHz £59 (carr £1)

**MONITORS**

MONO HERCULES' 14-inch paper white screen, high res. display, £49 (carr £6.50)  
MONO VGA 12-inch paper white high resolution £59 (carr £6.50).  
MONO SVGA PORTRAIT A4 13-inch Screen 800 by 1000, full VGA and Windows 3/3 1 compatibility. Complete with 512K card and drivers £125 (carr £6.50).  
COLOUR SUPER VGA 14-inch up to 1024 by 768 multisync., 0.28 dot pitch. Very high quality display. £219 (interlaced), £249 (non-interlaced) (carr £10).

**CAD COLOUR**

20-inch fixed frequency 48kHz Hitachi CH2086 monitors, £299.  
15-inch fixed frequency 64kHz Hitachi HM4115 with Microfield Graphics T8 driver card for Autocad and Windows 3/3 1 at 1280 by 1024 non interlaced (new) £399  
14-inch fixed frequency 48kHz Seiko 1024 by 768 non-interlaced, very high res. requires mod. to run from VGA card. New but sold without technical support or guarantee. £59 (p.o.a for carriage for above)

**VGA CARDS AND WINDOWS ACCELERATORS**

16-bit VGA card, 256K, all emulations, up to 800x600, with software to run all major packages. Oak chip set. Switchable for use in XT's £29.95.  
16-bit 1024x768 super VGA card. Very high resolution with 512K and drivers for Windows, Acad, VP etc. Full manuals and disks. Latest version of the industry standard Trident chip set. £49; 1 Mbyte version £59 (carr on cards £2.00).  
50 MHz 53 Windows Accelerator. Latest high speed accelerator card using the full 50 MHz 53 chipset (carr £2).  
NCR Windows Accelerator with 2 Mbyte video RAM £149 (carr £2).  
VGA to TV PAL card. Connects between VGA card and TV or video at up to 640 by 480 256 colours. Composite video (PAL) output. VGA monitor can still be used. £39 (carr £2).

**DIGITISERS**

Hitachi Puma Series Digitisers - end of stock! 24 by 36 inches and 36 by 48 inches only; new, no psu's £150 to clear (carr on application).

**MODEM AND FAX CARDS**

Fax/modem card 9600BPS latest internal card can transmit and receive group 3 faxes at up to 9600BPS\* and also be used as a Hayes compatible modem at 2400BPS. Complete with software for both functions. Handles TIF and PCX graph; file formats. £99 (carr £4).  
WINFAX SOFTWARE for above to enable fax to run under Windows. Highly recommended. £39.95.  
Hayes Compatible 2400BPS internal modem fully compatible with MNP error correction. Auto dial/answer and speed sensing. Works with Windows 3, Procom, Crosstalk etc. £69 (carr £4).

**POWER SUPPLY**

Astec BM140 IBM XT/AT compatible 150W, +5V at 15A, +12V at 5A, -5V at 0.3A, -12V at 0.5A, fan cooled, rear panel switch, good value at £19.50 (carr £4).

**SOFTWARE AND DISKS**

DR DOS 6 Latest operating system from Digital Research with many extra features including file compression and good memory handling £39.95, MS DOS 5 £49.95 (carr £4).  
WINDOWS 3.1 Latest version from Microsoft on 3.5-inch disks £69.95 (carr £4)  
3.5-INCH DISKS Box of ten 1.44 Mbyte preformatted £9.95 (carr £2).

**Stop Press! 386-16 motherboards not working but with guaranteed good 386DX cpu £29 (carr £4) Few only, no guarantee on motherboard.**

NB \* VAT and carriage must be added to all items (quotes for carriage overseas).  
\* Everything new and guaranteed one year unless stated; ex-dam. products guaranteed 6 months.  
\* Access and Visa telephone service.

**MATMOS LTD., UNIT 11, THE ENTERPRISE PARK, LEWES ROAD, LINDFIELD, WEST SUSSEX RH16 2LX. 0444 482091 and 0444 483830 (Fax: 0444 484258).**

Matmos Ltd. has been trading successfully since 1976.

CIRCLE NO. 143 ON REPLY CARD

**INDEX TO ADVERTISERS**

PAGE	PAGE	PAGE
Adept Scientific ..... 648	ICOM (UK) Limited ..... 651	Micro Amps Ltd ..... 623
Anchor Surplus ..... 690	Image Processing ..... 657	National Instruments ..... 629
Antrim Transformers Ltd ... 642	IPK Broadcast Systems ..... 648	Number One Systems Ltd ... 621
Bull Electrical ..... 645	J & M Computers ..... 662	Pico Technology ..... 648
Chelmer Valve Company ... 683	Johns Radio ..... 652	Ralfe Electronics ..... 642
Citadel Products Ltd ..... IBC	Kestral Electronic Components Ltd ..... 668	Seetrax Ltd ..... 634
Colomere Electronics Ltd .. 655	Keytronics ..... 667	Smart Communications ..... 640
Dataman Designs ..... IFC,625	Labcenter Electronics ..... 671	Specialist Semiconductors .. 673
Display Electronics Ltd ..... 660	M & B Electrical ..... 656	Stewart of Reading ..... 668
Field Electric Ltd ..... 683	M & B Radio (Leeds) ..... 694	Strumtech Engineering Ltd .. 703
Halcyon Electronics ..... 651	M Q P Electronics ..... 655	Surrey Electronics Ltd ..... 642
Hoka Electronics (UK) ..... 678	Maplin Electronics ..... OBC	Thurlby Thandar Ltd ..... 618
ICE Technology Ltd ..... 668	Matmos Ltd ..... 704	Tsien Ltd ..... 683
		Wood & Douglas ..... 655


**OVERSEAS ADVERTISEMENT AGENTS**

France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008.

United States of America: Jay Fenman, Reed Business Ltd., 205 East 42nd Street, New York, NY 10017 - Telephone (212) 867 2080 - Telex 23827.

Printed in Great Britain by Riverside Press, Gillingham, Kent, and typeset by Marlin Graphics, Sidcup, Kent DA14 5DT, for the proprietors, Reed Business Publishing Ltd, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. © Reed Publishing Ltd 1992. Electronics and Wireless World can be obtained from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd, INDIA: A.H. Wheeler & Co. CANADA: The Wm Dawson Subscription Service Ltd.; Gordon & Gotch Ltd., SOUTH AFRICA: Central News Agency Ltd.; William Dawson & Sons (S.A.) Ltd.; UNITED STATES: Worldwide Media Services Inc., 115 East 23rd Street, NEW YORK, N.Y. 10010. USA. Electronics & Wireless World \$5.95 (74513).

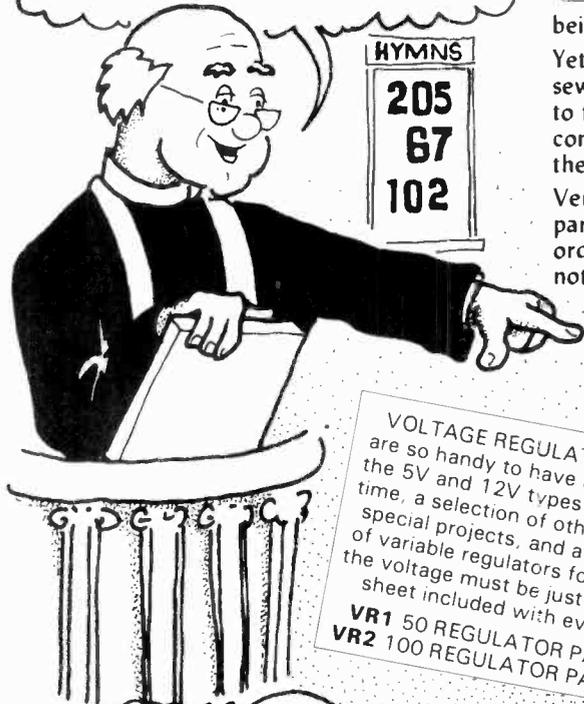HERE ENDETH THE  
LESSON AND BEGINNETH  
THE BARGAINS...



And lo, a great wailing and lamenting was heard in the land, and the people did cast themselves downward did tear their raiments, yea even unto their Marks and Spencers underpants. For it was feared that Hygrade had fallen by the wayside, there being no tidings of that company since the time of their forefathers.

Yet there did come in the seventh year a time of great rejoicing and a sewing up of raiments previously rent in twain. For it was made known to the people that Hygrade was still a power in the land. And there did come tidings of such bargains as they had not thought possible. And their joy knew no bounds.

Verily the people did say unto themselves: Your parcels shall be my parcels, and your goods my goods And there came a time of much ordering and receiving, in which many things were possessed that were not possessed before. And the people did give thanks.

MY PRAYERS ARE  
ANSWERED...



VOLTAGE REGULATOR PARCELS are so handy to have around. Lots of the 5V and 12V types you use all the time, a selection of other voltages for special projects, and a good helping of variable regulators for times when the voltage must be just so. Free data sheet included with every parcel.

VR1 50 REGULATOR PARCEL £8!  
VR2 100 REGULATOR PARCEL £15!

REMARKABLE  
VALUE!



HIGH VALUE CAPACITOR PARCELS give you a wide selection of high capacitance non-polar caps in values way up to 6µ8. Audio buffs use them in preference to electrolytics; other find them useful in situations where a DC polarising voltage is not available. But a half a dozen high value non-polar caps can easily cost as much as this parcel! If it wasn't Hygrade I wouldn't believe it.

HV1 200 HIGH VALUE CAPACITOR PARCEL £12!  
HV2 600 H.V. CAPACITORS £29!

SWITCH PARCELS are for the practical man. If any household appliance needs a new switch, if a control breaks on your car dashboard, if you repair or maintain any type of electrical or electronic equipment, chances are you'll save a fortune in expensive replacements. It makes sense.

SP1 100 EMERGENCY SWITCH PARCEL £12!  
SP2 300 MIXED SWITCHES £29!

PRESET PARCELS to make life easy. Never be stuck for the type you need. There are carbon types, open and enclosed, cermet in several different case styles, multi-turns, you name it. And we're not mean with the expensive ones. Zillions of different values from a few ohms to several Meg.

PP1 100 PRESET PARCEL £5!  
PP2 500 PRESET PARCEL £19!  
PP3 1000 PRESETS £35!

INFRA-RED PARCELS will be appreciated by anyone who makes intruder alarms, remote controls, object detection, limit switching, production line automation, and the like. These are very expensive components, and as you'd expect from Hygrade are a all new, perfect, and to the highest specifications. Free data sheet supplied with every parcel.

IR1 100 INFRA-RED PARCEL £12!  
IR2 300 INFRA-RED PARCEL £29!

RELAY PARCELS return, with a better selection than ever! Need a low voltage relay? You won't get much lower than out 3.6V TTL compatible types. Want a miniature one? Some are so small I'm surprised they don't float away. One for signal switching? No problem. One with 10A contacts? There'll be plenty. One for 12V car electrics? You'll be spoiled for choice. A magnificent selection.

RP1 50 RELAY PARCEL £15!  
RP2 100 RELAY PARCEL £26!

**SPECIAL  
CLEARANCE  
BARGAINS:**

Electronic components, computers, power supplies, test equipment. Call us on

**0600  
772541**  
today for your  
**FREE list!**

IC LABORATORY PARCELS are this month's favourite. Packed with CMOS and TTL logic ICs, linears, op-amps, regulators, memories, EPROMS, microprocessors and support ICs, data converters, MODEM ICs, encoders, and so on and on and on. Some are pre-packed, some have data sheets, many are common types you should easily recognise. £1000s worth of ICs!

LAB1 200 IC PARCEL £29!  
LAB2 500 IC PARCEL £65!

MIRACULOUS  
SAVINGS!



THANKYOU  
OH...THANK  
You!



**HYGRADE, 2 Founders House, Redbrook, Monmouth, Gwent, NP5 4LU**

Credit card orders: Tel 0600 772541, or include your credit card number and expiry date on your order. Please add £4 postage and VAT at the current rate to your order total.

CIRCLE NO. 113 ON REPLY CARD

# DIGITAL SIGNAL PROCESSING YIELDS NEW HARDWARE

*DSP is no longer seen as just a way of obtaining analogue performance at lower costs. Pat Hawker reports on how DSP is opening up entirely new applications.*

The all-digital communications receiver, with incoming signals converted into digits at the signal frequency, still seems some way off. But analogue-to-digital conversion as a prelude to digital signal processing, at either base band or increasingly at a bandpass intermediate frequency, is undoubtedly opening the way to an increasing number of novel hardware implementations.

It is already some six years since the Rockwell-Collins VLF/HF receiver *EF2050* was introduced – a pioneering effort using the concept of flexibility of final receiver bandwidth, ripple and selectivity being determined by programmed data within VLSI signal processors. Even then it was recognised that further advantages would come with development of more linear A-to-D chips working at higher speeds. The aim was (and remains) a receiver with an overall performance in no

way inferior to that of the best conventional analogue receiver, but offering advantages such as accurate, calculable multiple bandpass filter, a lower component count, and easier assembly – all pointing to lower costs.

Front-end signal processing in receivers is only one of the many applications of digital signal processing currently attracting attention. DSP is not only about achieving similar performance at lower cost than conventional analogue circuitry; now it is seen as opening the way to new systems, incapable of implementation in purely analogue electronics. For example, in video and speech coding and compression, and HF direction-finders (with relatively simple installations able to distinguish between signals separated in bearing by only about 2° using beam-forming techniques).

## Implementing novel hardware

An IEE colloquium “*Implementations of novel hardware for radio systems*” concentrated on currently-sponsored university research projects involving DSP techniques. The paper presented by A M Thurston of GEC-Marconi Research (jointly authored by M O J Hawksford of the University of Essex) set out to show the advantages of IF converters used to digitise signals in high-performance receivers, over use of baseband converters to encode *I* and *Q* signal components. IF conversion can overcome the disadvantage of achieving two accurately matched mixers fed with precise in-phase and quadrature carriers to minimise images, and the problem that DC offsets and low-frequency *1/f* noise at the mixer outputs produces components which cannot be distinguished from signals at the IF centre frequency. Both problems can be over-

come by encoding the IF signal directly.

Thurston showed the various advantages that can stem from use of bandpass delta-sigma A-to-D converters. He explained how these can be designed by first converting the baseband modulator into its bandpass equivalent and then designing a system of D-to-A converters and analogue loop filters for which the pulse response at the sampling instants is identical to the impulse response of the bandpass digital filter. The approach is commonly known as “impulse invariant design”.

Thurston stressed that practical results have demonstrated the high linearity which may be achieved with sampling and subsampling converters. Simulation results show the extended performance which should result from an interpolating carrier (Table 1).

## Long distance modem

In the first of two papers from members of the Hull/Warwick Communications Research Group, P D J Clark described a flexible MFSK data modem based on an AT&T *DSP32C* processor integrated within an IBM PC compatible host and employing a novel data-derived synchronisation scheme. The adaptive modem has been based on the original 32-tone Piccolo concept as developed in the 1960s by the Diplomatic Wireless Service (now Foreign & Commonwealth Communications Branch).

The modem exhibits a far greater degree of responsiveness to both user requirements and channel state than previous implementations. It is capable of transmitting and receiving up to 32 signal tones in simplex mode, independently agile within a 2kHz bandwidth with a resolution of 1Hz.

Symbol transmission rate may be configured from 10symbols/s to 500symbols/s. The work is supported by the Farnborough defence research establishment and a possible application is for long-distance aeronautical HF communication.


Recent work on a multi-functional radio system terminal at Hull University – including the generation of low-cost ionograms – was reported by M Gallagher.

With professor M Darnell, he believes that although the benefits of DSP technology have

**Table 1. Extended performance through an interpolating carrier**



Performance	Sampling	Subsampling	Interpolative
Noise power density/Hz	-117dB0	-114dB0	-130dB0
Third order intercept	26dB0	24dB0	32dB0
Spurious free dynamic range in Hz (single tone)	95dB	92dB	108dB
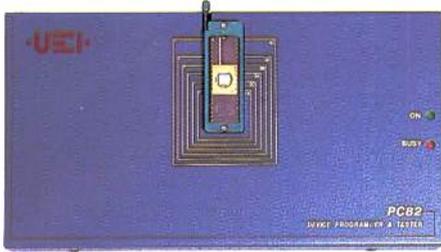
# TOTAL PROGRAMMING SOLUTIONS FROM CITADEL


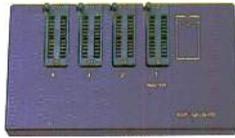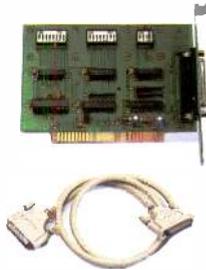
## PC82 UNIVERSAL PROGRAMMER £449.00

- Universal programmer – the complete designers kit.
- Over 1,500 devices – call for list on FREE disk.
- EPROM, EEPROM, Flash, BPROM, GAL, PAL, MPU etc.
- Serial EEPROM, EPLD, MACH, MAX, MAPL, CMOS EPAL.
- Device testing – 74XX, 40XX, 45XX, DRAM, SRAM.
- PAL vector test.
- Clear menu driven software
- Text mode only, suits any video card.
- 40 pin Zero insertion force socket.
- Device testing – 74XX, 40XX, 45XX, DRAM, SRAM.
- Small half card to install in PC may be left in place.
- Secure round cable and locking D connectors.
- Proven reliability – over 100,000 units sold.
- Programmer pod size – 260×140×38mm.



## ADAPTERS FOR THE PC82 From £85.00

- Extend programming facility for special devices.
- Allows alternative socket types eg PLCC.
- Multi-gang adapters for fast programming of EPROMS, GAL, PAL and popular CPU types.

## FEATURES ALL PROGRAMMERS

For the IBM PC, install the interface card and programming socket, load the menu-driven software and you have a complete design system at your fingertips. The programmers will run on any compatible IBM machines such as XT, AT, '286, '386 or '486. Whether it be an Amstrad or Compaq the system will work. All features are software-driven and supplied on 5 1/4" disks, these may be copied onto your hard disk using the DOS copy command. All control of the programmer, programme voltages etc are menu-driven by selecting manufacture, type number, and selection of a suitable speed algorithm. Blank check, read & modify, verify, programme, auto programme, security blow etc.

**FREE SOFTWARE UPDATES** as new devices become available.

## FILE CONVERSION FACILITIES

- HEX to BIN File conversions for Intel, Motorola and Tektronics.
- 2 way/4 way Bin file splitter for 16/32 bit data.
- Dump file to Console, modify and re-programme.



For further information and your **FREE PC82 Simulation and device disk**

**PHONE SAMANTHA NOW ON:**  
081 951 1848  
081 951 1849



## M25 BULK FAST ERASER £199.00

- Same advanced UV source as the M1 but 4 lamps.
- Very large capacity 64×32 pin chips or one double Eurocard.
- All other features as M1.
- Low profile steel case finished in powder coat.
- Size 365×240×65mm high.

## M1 FAST ERASER £99.00

- Advanced UV source.
- Typical erase time three minutes.
- LED display of set time and countdown.
- End of time indicated by beep and display.
- Large capacity 13×28 pin devices.
- Sturdy construction, plated steel & aluminium
- Small footprint only 65×225×100mm high.



## PC86 HANDY POCKET DEVICE TESTER £99.00



- Tests and identifies virtually all TTL & CMOS.
- Test many DRAM and SRAM memory chips.
- LCD display of type number and results.
- Battery operated (PP3) and completely self-contained.
- Zero insertion force test socket.
- Dimensions 90×140×30mm.



## PC84-1 to -8 ROM PROGRAMMERS From £139.00

- Low cost EPROM programmer – devices up to 1Mb CMOS and NMOS.
- One to eight gang versions.
- To program 2716 to 271000.
- 32 pin Zero insertion force sockets.



## ORDER INFORMATION

Please include £7 for carriage by overnight courier (£20 for exports) and VAT on all UK orders. ACCESS, VISA or CWO. Official orders welcome from Government bodies and local authorities.



**CITADEL PRODUCTS LTD**  
DEPT WW  
50 HIGH STREET, EDGWARE  
MIDDLESEX HA8 7EP



BUYER'S GUIDE TO ELECTRONIC COMPONENTS 1993

# Maplin



BS 5750  
Part 2 1987  
Level B:  
Quality Assurance  
RS12750

**Order your copy of the New MAPLIN Catalogue on sale 4th September!**  
Pick up a copy from any branch of WHSMITH or from our chain of shops for just £2.95 or  
post this coupon now to receive your copy for just £3.45 inc. p&p. If you live outside the  
U.K. send £5.50 or 14 IRCs for Airmail in Europe/surface mail outside Europe,  
or £10.65 or 27 IRCs for Airmail outside Europe.  
I enclose £3.45/£5.50/£10.65 (delete as applicable).

Name.....  
Address.....  
Post Code.....  
Send to Maplin Electronics,  
P.O. Box 3, Royleigh,  
Essex, England,  
SS6 8LR,  
www3

Over 700 product packed pages with  
hundreds of brand new products.  
On sale from September 4th, only £2.95

Available from all branches of WHSMITH and  
Maplin shops nationwide. Hundreds of new  
products at super low prices!

CIRCLE NO. 103 ON REPLY CARD