

ELECTRONICS WORLD

Denmark DKr. 70.00
Germany DM 15.00
Greece Dra.760
Holland Dfl. 14
Italy L. 7300
IR £3.30
Spain Pts. 780
Singapore S\$ 12.60
USA \$6.70

+ WIRELESS WORLD

A REED BUSINESS PUBLICATION

AUGUST 1994

£1.95

FREE Crystal sample pack*

*First 300 replies only

TECHNOLOGY

Heterojunctions:
bigger than cmos?

COMPUTING

Self-build teletext
card for the PC

APPLICATIONS

Low power switch
mode psu

REVIEW


Charting Smith's
computer world

RF ENGINEERING

Designing
combiners and
splitters

DIGITAL

Applying FPGA

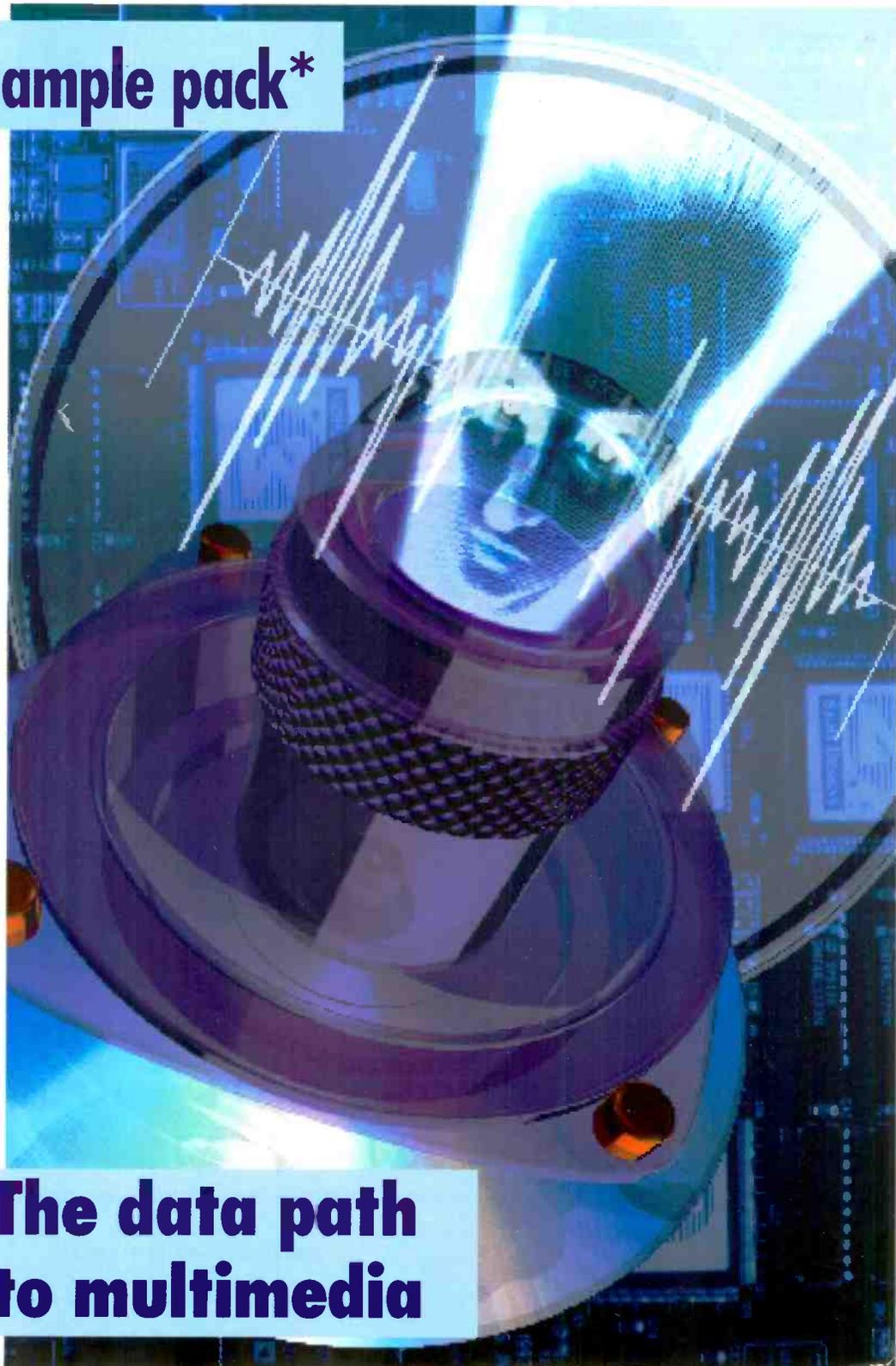


The data path to multimedia



9 770959 833004

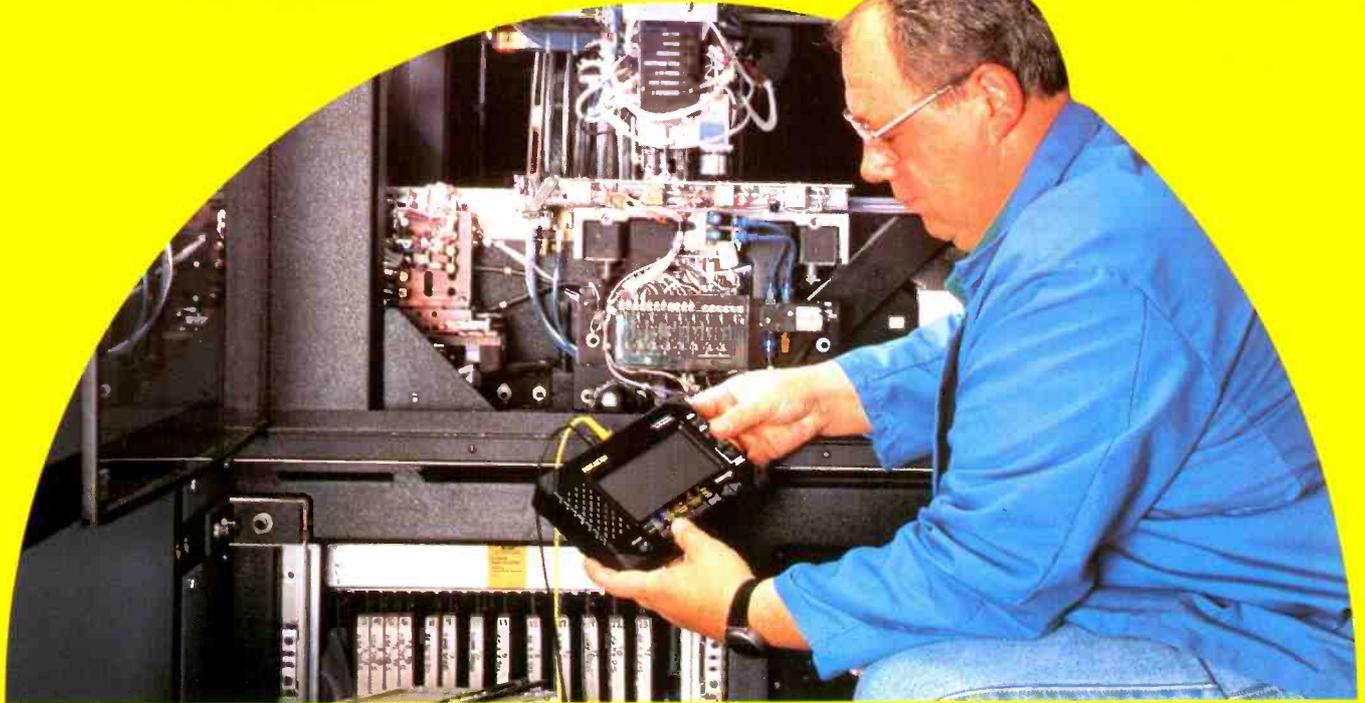
INTRODUCING THE “WHAT THE HECK IS GOING ON?” METER




TEKMETER™

For Installation and Maintenance of:

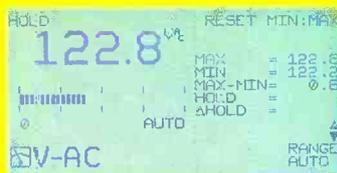
- POWER DISTRIBUTION SYSTEMS
- VARIABLE SPEED MOTOR CONTROLLERS
- PROCESS CONTROL EQUIPMENT
- SECURITY & OTHER VIDEO SYSTEMS
- COMMUNICATION EQUIPMENT



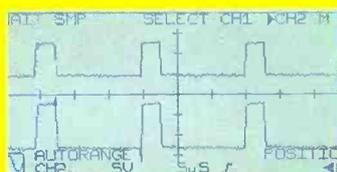Large LCD Display gives clear indication including Max, Min and Max-Min values.



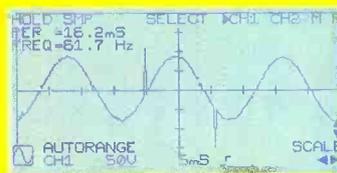Dual channel operation allows relative timing of signals to be observed.



Display of signal shape lets you find faults that DMM can not show.

Today the Digital MultiMeter (DMM) is not always enough! Modern electronics permeates our lives and the installation/maintenance professional is faced with problems where voltage and current measurements are just not enough. The shape and timing of signals is an important factor in many applications.

The New TekMeter is a rugged, fully-featured, autoranging DMM and a rugged, fully featured autoranging oscilloscope all in one battery-powered 1kg package. TekMeter is so simple to use you don't need a training course – even to look at signal shapes!

Choose between 3 new models – the THM550 single-channel version at £649.00, the THM560 dual-channel version at £775.00 and the THM565 dual-channel version, with backlight at £995.00. Whichever one you choose, it will help you to find out what's going on and solve the problem!

TekTools™ - Smart Tools Work Better

Tel: 0800 412200

Tektronix

TekDIRECT, FREEPOST, Fourth Avenue, Globe Park, Marlow, Bucks, SL7 1YZ. Fax: 0628 474799

CIRCLE NO. 100 ON REPLY CARD

CONTENTS

FEATURES

TELETEXT VIA YOUR PC630

Teletext on a tv screen is handy but being able to access the broadcast data via a PC is much more useful. Laurence Cook describes a self-build PC plug-in comprising a complete tv tuner and teletext decoder.

APPLYING CRYSTALS.....659

Circuitry needed to drive a quartz crystal is both application and frequency dependent. Martin Eccles looks at discrete component and logic-gate oscillators for frequencies from kilohertz to 200MHz.

NEW WAVE MICROWAVES.....666

Traditionally, the GaAs mesfet has been the choice for low noise, medium-power amplifiers to 30GHz but emerging technologies are looking increasingly attractive. Mike Hosking reports on new semiconductors for microwave oscillators and amplifiers.

THE GENETIC PICTURE674

Use of dna 'fingerprinting' to identify people is set to increase substantially. Tom Ivall explains how the instrumentation behind the technique is evolving.

DIGITAL FILTERS SIMPLIFIED.....684

Bob Lawlor explains how field programmable logic can simplify the design of both finite and infinite-impulse response filters.

USING RF TRANSISTORS.....694

A common way of boosting rf power is to use multiple amplifiers together with combiners and splitters – of which there are numerous types. Norm Dye and Helge Granberg discuss the options.

MEASURING RMS RF POWER700

Normally, measuring rf power at milliwatt levels needs expensive equipment. Nick Wheeler describes a true rms solution that provides both easy calibration and good overload capability.

THE DATA PATH TO MULTIMEDIA.....537

With video cd set to appear in the shops, George Cole takes a look at the technology involved and some of the events that have led to the confusion over standards.

DESIGNING FOR NOISE IMMUNITY642

Inevitably, signals from transducers pick up unwanted noise en route to their destination. There are ways of removing noise but designing the system to minimise it is a far better alternative, as Dave Robinson explains.

NEW MAPS FOR SMITH'S WORLD.....647

According to Ian White, *Z-Match for Windows* meets the challenge of retaining all the features of paper Smith charts while adding the advantages of computerised post processing and manipulation.

SILICON-GERMANIUM656

Currently under research, silicon-germanium could represent the most significant breakthrough in electronics technology since cmos. Jon Mosely has been investigating how and why.

REGULARS

COMMENT.....619

Its all in the game.

NEWS.....620

Intel and H-P in micro design pact, PowerPC outsells Pentium, World's first 64Mbit dram, Self wins EW+WW/H-P writer's award, Rough ride for video CD.

RESEARCH NOTES.....626

DSP flattens steel precisely... and sharpens hearing
Sharing the secret to scientific problem solving.
Polarity proposal that is music to the ears.

APPLICATIONS.....651

Low-power PWM, Video selection, Integrated front end chips for DECT, Micropower op-amp for 2.7V supplies.

DESIGN BRIEF.....670

Ian Hickman takes a speculative look at a new concept in instrumentation based on bridge measurement – the transformer ratio arm bridge.

NEW PRODUCTS.....679

Classified run-down of new electronic products.

CIRCUIT IDEAS.....688

Single-pot polarity and gain adjustment, Full-wave rectifier uses single amplifier, Frequency doubler, Low-level crossover – and more.

LETTERS.....692

Critical response, Beach buff, Small world, Amnesty appeal, Hidden meaning, Graphic example, IC-can you? Decoding US actions, Calling cable suppliers... to prove a difference.

In next month's issue: In next month's issue: Circuits for rms conversion. There only two types of circuit which will measure the power content of a signal directly. You can either amplify it and use the resulting output to heat a thermocouple, or you can process the signal with a root mean square algorithm. Danny Ayers tells all.

Plus a FREE pair of ZTX689B Zetex super-performance power transistors for every UK reader.


THE SEPTEMBER ISSUE IS ON SALE FROM AUGUST 25

FREE: Crystal sample pack p659



Cover: Nick Lloyd

SYSTEM 200 DEVICE PROGRAMMER

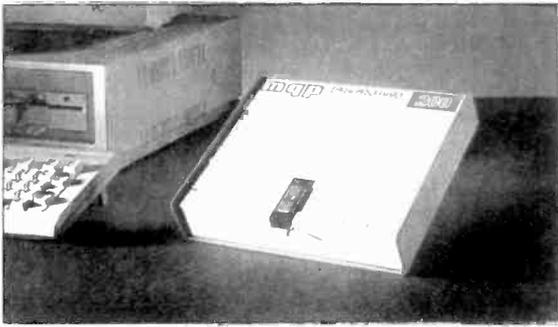

SYSTEM: Programs 24,28,32 pin EPROMS, EEPROMS, FLASH and Emulators as standard, quickly, reliably and at low cost.

Expandable to cover virtually any programmable part including serial EEPROMs, PALs, GALs, EPLDs and microcontrollers, in many different packages.

DESIGN: Not a plug in card but connecting to the PC serial or parallel port; it comes complete with powerful yet easy to control software, cable and manual.

SUPPORT: UK design, manufacture and support. Same day dispatch, 12 month warranty. 10 day money back guarantee.



MQP ELECTRONICS Ltd.

Park Road Centre

Malmesbury, Wiltshire. SN16 0BX. UK
TEL. 0666 825146 FAX. 0666 825141



ASK FOR FREE
INFORMATION
PACK

IRELAND 1-2800395
GERMANY 089/4602071
NORWAY 0702-17890
ITALY 02 92 10 35 54
FRANCE 1 69 30 13 79
SWEDEN 08 590 32185
Also from ELECTROSPEED UK

CIRCLE NO. 103 ON REPLY CARD

KESTREL ELECTRONIC COMPONENTS LTD

- ☆ All items guaranteed to manufacturers' spec.
- ☆ Many other items available.

'Exclusive of V.A.T. and post and package'

	1+	100+		1+	100+
EPROMS			STATIC RAMS		
2764A	2.50	2.20	62256LP-10	3.00	2.25
27C64-150	2.30	1.68	6264LP-10	1.85	2.28
27128A-25	2.20	2.10	6522P	2.40	1.80
27256-25	2.20	1.85	65C02P2	2.90	2.38
27C256-15	2.50	2.20	65C21P2	2.90	2.50
27C512-15	3.00	2.40	65C22P2	2.80	2.30
27C010-15	5.60	3.70	MC146818AP	2.20	1.65
MAX232	1.35	0.95	MM58274CN	4.90	3.98
D8748H	4.20	3.40	SN75176BP	1.60	0.80
D8749H	4.40	3.50	Z80A CPU	1.50	1.00
80C31-12	2.60	1.80	Z80A CTC	1.30	0.85
80C85A	2.60	1.80	Z80A DART	2.10	1.40
82C55-8MEG	1.95	1.58	1488P/1489P	0.32	0.25

74LS, 74HC, 74HCT Series available

Phone for full price list

All memory prices are fluctuating daily, please phone to confirm prices

**178 Brighton Road,
Purley, Surrey CR8 4HA**

Tel: 081-668 7522. Fax: 081-668 4190.

CIRCLE NO. 104 ON REPLY CARD

Low cost data acquisition for IBM PCs & compatibles

Easy to use data acquisition products that allow your PC to be used as a range of useful test and measurement instruments, or as an advanced data logger. Installed in seconds they simply plug into the parallel port (except the ADC-16 which connects to the serial port). They require no power supply and take up no expansion slots. Each comes with a comprehensive manual. Software drivers are included for users who wish to write their own software. Software supplied on 3.5" disk.

PicoScope



'Virtual instrument' software. Storage scope with trigger, timebase, rulers and offset. Real time spectrum analysis with min/max frequency and signal averaging. Multiple meters on screen (digital and bargraph). Printer and file handling support.



ADC-10/12

Single channel of analog input
8 bit resolution 22kHz sampling (ADC-10)
12 bit resolution 18kHz sampling (ADC-12)
(sampling speed based on 33MHz/386PC)
0-5V input range
BNC input allows use of scope probes

PicoLog



Advanced data logging software package. Collect, store, display and print data from 1 sample per ms to 1 per day. Record average, min/max or scaled values (linear, equation, table look-up). Report types: monitor (with min/max alarms), y-t graphs, x-y graphs, tabulation

NEW ADC100 Virtual Instrument



ADC-100

Dual Channel 12-bit resolution

The ADC 100 offers both a high sampling rate (100kHz) and a high resolution. It is ideal as a general purpose test instrument either in the lab or in the field. A flexible input range ($\pm 200\text{mV}$ to $\pm 20\text{V}$) allows the unit to connect directly to a wide variety of signals.

- Digital Storage Scope
- Chart Recorder
- Spectrum Analyser
- Data Logger
- Frequency Meter
- Voltmeter

ADC-100 with PicoScope £199

ADC-100 with PicoScope & PicoLog £209

Prices

ADC-10 with PicoScope £49
ADC-11 with PicoScope £85
ADC-12 with PicoScope £85
ADC-16 with PicoLog £115

The ADC-10/11/12 are available with both PicoScope and PicoLog for an additional £10. Existing ADC-10/11/12 users can add PicoLog for £25.



Pico Technology Ltd. Broadway House, 149-151 St Neots Road, Hardwick, Cambridge CB3 7QJ, UK

TEL: 0954-211716 FAX: 0954-211880



Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT.

CIRCLE NO. 105 ON REPLY CARD

PICO TECHNOLOGY

EDITOR

Frank Ogden
081-652 3128

DEPUTY EDITOR

Martin Eccles
081-652 8638

CONSULTANT

Derek Rowe

DESIGN & PRODUCTION

Alan Kerr

EDITORIAL ADMINISTRATION

Jackie Lowe
081-652 3614

ADVERTISEMENT MANAGER

Richard Napier
081-652 3620

DISPLAY SALES EXECUTIVE

Malcolm Wells
081-652 3620

ADVERTISING PRODUCTION

Paul Burgess
081-652 8355

PUBLISHER

Susan Downey

EDITORIAL FAX

081-652 8956

CLASSIFIED FAX

081-652 8956

SUBSCRIPTION HOTLINE

0622 721666
Quote ref INJ

SUBSCRIPTION QUERIES

0444 445566

NEWSTRADE DISTRIBUTION

Martin Parr
081 652 8171

BACK ISSUES

Available at £2.50
081 652 3614

ISSN 0959-8332



Its all in the game

One often gets the impression that electronics for such things as business, defence, communication and scientific research leads development of the art. This may just about be true at present, but not for much longer. The drive increasingly comes from consumer leisure.

We are about to see real changes in our everyday experience coming from consumer electronics. And they will also affect the way in which we do business. Let me give an example of consumer technology affecting our own business, magazine publishing.

British Telecom and other PTTs are currently experimenting with video-on-demand, a service to deliver your personal viewing schedule directly to your home. At present, if you don't like the terrestrial or satellite offerings of an evening, you must rent a video from your local newsagent or wherever. Very soon, the PTT will be able to deliver your viewing choice in 1.5Mb/s digital form directly to your home via the same exchange line which operates the telephone. The viewer dials in a viewing request and back comes the film down the telephone line.

Compare this with the existing business equivalent. While a great improvement on the 14.2kbaud of a top quality analogue line, data at 64kb/s from ISDN seems primitive by comparison. Video compression and modem technology for consumer use is streets ahead of the commercial equivalent. Important for its acceptance, it will be cheap because it will have been designed for a mass market. Businesses of all sorts will jump at the chance to squirt high bandwidth signals about using consumer derived equipment. For instance, all those things which we as publishers may offer our readers on cd-rom could be made available via the telephone network. The

magazine which you are now reading could soon be transmitted in its entirety by electronics. This might include the current issue plus the complete archive going back five years.

And for those people who are sceptical about the possibility of electronics ever replacing paper, I would recommend that they take a look at *Encarta*, Microsoft's encyclopaedia on cd-rom. While one may hate the Americanised content of this work, the hierarchal data access is without parallel. Everything on the cd-rom is content addressable and searchable and all subject texts include highlighted keywords for cross reference. These may be examined at will by double mouse click on the highlighted word. I assure you that if you had your magazines and other pictorial/textual matter delivered and updated regularly in electronic form, you would never look at a paper magazine again... except on a train or plane, perhaps.

But who wants to be tied to a telephone line? There are currently some 250 high power satellite transponders available for rental with operators bending over backwards to find suitable traffic. Ten seconds of transponder time could squirt this entire magazine, diagrams and all, to every corner of the country. The reader would plug his PC into a decoder connected to a standard domestic satellite receiver. We could then update your magazine once a month, once a week, once a day or once an hour...

All this goes full-circle to Arthur C Clarke's seminal article *Extra Terrestrial Relays*. Upheavals in magazine publishing will be just a single shot in the information revolution which is about to overwhelm us.

Frank Ogden.

Electronics World + Wireless World is published monthly. By post, current issue £2.25, back issues (if available) £2.50. Orders, payments and general correspondence to L333, **Electronics World + Wireless World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS**. Tlx:892984 REED BP G. Cheques should be made payable to Reed Business Publishing Group.

Newstrade: IPC Marketforce, 071 261-5108.

Subscriptions: Quadrant Subscription Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 445566. Please notify change of address. Subscription rates 1 year (normal rate) £30 UK and £43 outside UK.

USA: \$52.00 airmail. Reed Business Publishing (USA), Subscriptions office, 205 E. 42nd Street, NY 10117.

Overseas advertising agents: France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 205 E. 42nd Street, NY 10117. Telephone (212) 867-2080. Tlx 23827.

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. 2nd class postage paid at Rahway NJ Postmaster. Send address changes to above.

Printed by BPPC Magazines (Carlisle) Ltd, Newtown Trading Estate, Carlisle, Cumbria, CA2 7NR
Typeset by Marlin Graphics 2-4 Powerscroft Road, Sidcup, Kent DA14 5DT

©Reed Business Publishing Ltd 1992 ISSN 0959 8332

Intel and Hewlett-Packard in micro design pact

After two decades of sticking to the x86 architecture, Intel has announced it is devising a new microprocessor architecture in association with Hewlett-Packard.

Both companies claim that the reason for the link-up is a technological breakthrough that will dramatically increase microprocessor power. First fruits of the link are not expected until 1999 and Intel will carry on with its proposed development of Pentium successors P6 and P7.

Unlike its main micro rival, the IBM/Motorola/Apple consortium making PowerPC, Intel does not intend to set up a common microprocessor development centre. Instead, Intel and HP will design chip

sets independently but with a common architecture.

It is expected that HP will concentrate on making high-end chips for mainframes, servers and workstations while Intel concentrates on chips for the lower-end, mainly PCs. Only Intel will sell the chips to other manufacturers but H-P will have the right to use them in its products.

The companies have been collaborating on the project since January and only announced it now because the teams of people had become so large that the project was becoming leaky.

It is generally thought that the reasons propelling Intel into the deal are a feeling that the x86 architecture

is running out of steam. There is also a perception among big computer systems buyers that Intel is a provider of components for desk-top computing and not one for the heavy-duty end of the computer market.

The chips developed under the link will run all existing Intel and HP applications software. Neither company would say if applications will run under some form of hardware emulation, the emerging technique of performing the emulation function on-chip, or if they will be truly native to the architecture. Nor is it revealed whether the chips will be able to run other people's software, for instance PowerPC's. **David Manners**, *Electronics Weekly*.

PowerPC outsells Pentium

Apple Computers *PowerPC* machines have out sold their Pentium-based rivals since their launch in March.

According to market research firm Computer Intelligence Infocorp, Apple sold 66,300 *PowerPC* based systems in the first three months since its introduction in March 14. This compares with 40,900 systems sold in the same period based on Intel's *Pentium* microprocessor.

The sales figures were for the US market. Worldwide sales of the Power Macintosh were 200,900 units. The results, while encouraging for Apple, include a large initial demand for Power Macintosh models with at least 45,000 units sold within the first two weeks. Apple's goal is to sell at least one million *PowerPC* based systems

within the first year of introduction.

The market research firm had some other good news for Apple. Profit margins on *PowerPC* based systems are more than double compared with *Pentium* models. This means that Apple can reinvest more money in new product development and marketing than competitors manufacturing Intel based systems.

But despite the good sales figures, Apple's attempts to win over PC users with emulation technology running on its Power Macintosh systems has not worked. Almost all buyers of Power Macintosh models are Macintosh users. The failure to win PC customers is blamed on poor emulation technology. Apple and other companies are developing better emulation technology.

More to Harwell than nuclear reactors: AEA Technology recently opened its doors at the Culham and Didcot research centres to show of its commercial R&D capability. Its expertise in semiconductor processing and battery design are just a couple of examples where its work could be of direct relevance to the electronics industry.

The picture shows a batch of 100mm wafers about to be bombarded with protons at high energy which will deform the silicon structure to leave gaps. These gaps will later act as trapping centres or 'lifetime killers' which terminate the minority carriers in semiconductor junctions. This improves device switching time. By controlling the energy of the proton source, the gaps may be controlled in size and depth to produce an optimum substrate for bipolar switching transistors.

Other work at AEA Technology includes development of a lithium polymer battery system which allows the construction of a battery laminate just 200µm thick. This can be shaped and sized to any requirement.





**ANCHOR SURPLUS LTD
THE CATTLE MARKET
NOTTINGHAM
NG2 3GY**

TEL: (0602) 864902 & 864041

FAX: (0602) 864667



OSCILLOSCOPE SPECIAL

**50MHZ
TWIN TRACE
TWIN TIMEBASE**



**Philips PM3217
oscilloscope
Special Offer**

**tested +
Cal verified**

£295.00

HP 141 Spectrum Analyser Special Offers

**HP 8554B Plug Ins – 1250Mhz
TESTED with Verified Calibration
£395.00**

**HP 8555A Plug Ins – 18Ghz
TESTED with Verified Calibration
£595.00**

Other Modules for the 141T available . . . Complete Service Manuals . . .
140 and 141T Frames . . . Modules and Frames for Spares . . .

**TEK 492P Spectrum Analysers 50Khz to 21Ghz 1Khz res. IEEE (GP1B).
Rack/bench option 4999
H/P 5328A 8 digit DFM with DVM option IEF E Fitted £275.00**

**We are now open 7 DAYS a week
Monday-Friday 9am to 6pm
Saturday 8am to 4pm
SUNDAY 10am to 4pm**



World's first 64Mbit synchronous dram

Ahead of everyone, Fujitsu has announced a synchronous 64Mbit dram and says it will present engineering samples in August. Access time for the chip is just 6ns. The process used is 0.35µm.

The six-man Fujitsu design team, led by Yukinori Kodama, divided the column access path into three pipeline stages.

To increase operating speed they developed an address incrementing pipeline scheme which can concurrently access data at two consecutive addresses. Using this scheme, the area penalty is 1.5% more than that of conventional drams but it can operate at high clock rates: at 100MHz, the device allows data transfer rates of 100Mbyte/s.

Instead of the conventional two-bank structure, the designers have gone for four data banks allowing for greater independence of operating areas and, consequently, increased throughput.

Each bank has two cell array

blocks which are separated by the word decoder. Each block has eight global bus lines which are connected to eight DQ pins.

The global bus lines are formed with the second metal layer and are laid out on the shunting area – they do not carry an area penalty. During a burst read/write operation, the separated cell array blocks are activated concurrently.

Bit data from each of the eight DQ pins at two consecutive addresses is read or written simultaneously. This

2-bit prefetch increases the bandwidth of a sequential data transfer.

The Fujitsu team recommends a terminated low voltage t1 interface which terminates a transfer line in the middle potential of the power supply voltage and the ground potential. The output circuit matches the impedance of the transfer line and therefore the interface responds to data transfer at 100MHz.

The chip size is 21.06 × 11.02mm and contains 140 million transistors and capacitors.

Callbox in the sky: US dominated consortium Globalstar, one of around half a dozen groups planning to offer satellite based mobile telephone services in 1998, claims that it has the simplest proposal. Forty eight low earth orbit satellites will act as radio basestations for a new breed of dual mode handsets which will work on either existing terrestrial cellular networks or the CDMA based Globalstar network. There is no complex routing of calls in space, radio calls are quickly beamed back down to an earth station and onto the local PSTN. Globalstar's partners include cellular operator Vodafone and CDMA specialist Qualcomm.

PDA's fail to deliver the goods

The market for Personal Digital Assistant (PDA) devices has failed to develop as quickly as industry analysts predicted, creating problems for computer firms that expected it to be the next growth market.

According to market research firm Link Resources, fewer than 49,000 PDAs were sold in the first quarter of 1994, and the rate for the second

quarter is not expected to be much better.

In addition to the slow market, Motorola and IBM report manufacturing problems for their PDAs and Compaq Computer has delayed plans for its *Mobile Companions* PDA-like devices based on Microsoft's *WinPad* software interface.

Cordless videophone uses dect

UK researchers have demonstrated the feasibility of a cordless videophone, by transmitting compressed video pictures over the dect, the European digital cordless telephone protocol.

Paul Stein, head of radio comms research at Roke Manor Research, said that it is technically feasible to use a dect cordless phone, fitted with a solid state camera and screen, as a

video telephone. Siemens, which owns Roke, is believed to be interested in commercialising the technology in its dect handsets.

Roke's first demonstration system is a slow scan tv format which allows a cordless network of dect handsets to be used for security surveillance. The system uses a single timeslot in the dect 32kbit/s radio channel to transmit a compressed video picture


running at two frames per second. A dect transceiver fitted with a camera transmits the video data via a standard wall-mounted base station to a second handset linked to a PC, which displays the picture.

Although dect's ADPCM coding scheme limits the picture quality achievable in a single 32kbit/s channel, Stein said that picture quality can be increased by using more than one time slot to transmit the video data.

Standard H.261 videoconferencing codecs rely on a minimum 64kbit/s data channel, which can be supported by the dect protocol using two 32kbit/s slots. Because time division multiple access (TDMA) radio carrier modulation is used, the relevant time slots need not be adjacent and can be multiplexed with other traffic on the cordless network.

Video data inevitably makes heavy use of the 12 available radio channels in each dect carrier and consequently there is a trade off between picture quality and network capacity. Stein, however, is confident that video telephony, running at 30 frames per second is realistic.

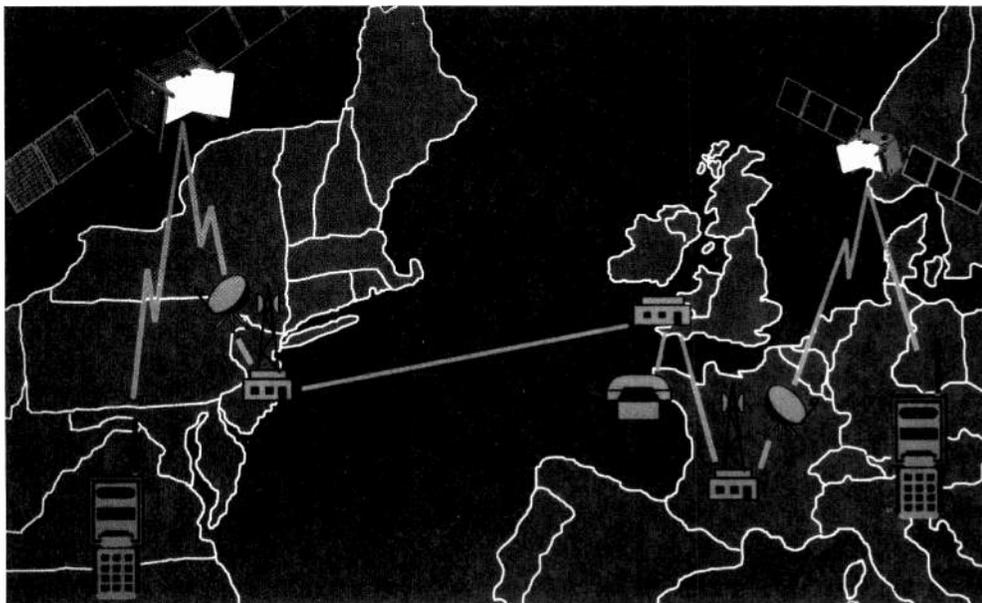Siemens is said to be very interested in the possibilities of cordless videophones.



Nynex backs video on demand

Nynex, one of the largest UK cable operators, will offer the first video-on-demand services on its broadband cable network by the end of the year, and it is investing £200m in the venture.

The cable company is buying a head-end system and set-top decoders from General Instruments in a contract worth at least £120m over the next six years. A Nynex spokesman said the value could be larger if the market for video-on-demand took off. "This gives us a

potential for video-on-demand and we will be offering a kind of video-on-demand service late 1994, early 1995," said the spokesman.

Nynex is also buying £80m worth of switching and transmission systems from Nokia Telecom which, like the General Instruments equipment, will be deployed in the company's ten franchises in the north west of England.

This represents Nokia's largest contract with a UK cable company. It will supply it DX200 digital

switches which will support a total of 100,000 telephone lines.

General Instruments' MPEG-based ICFT 2000 set top box will allow users to select, order and pay for individual tv programmes.

Last year Nynex executives said there were no plans for interactive TV services. The U-turn is possibly a response to BT, which is testing a service using ADSL technology on analogue telephone lines this year.

Richard Wilson, *Electronics Weekly*.


British police test remote control car stop

Three British police forces are testing radio technology which will enable them to remotely control and stop stolen vehicles. The police in Northumbria, Kent and London are testing an electronic device, called *DemonScan*, which once fitted in a car as an anti-theft device, allows remote control of the vehicle's speed, down to between 20 and 80 per cent of its full value, and eventually stopping it.

The system activates itself once a thief has bypassed the immobiliser system, causing it to send a signal which can be picked up by police vehicles fitted with a radio

transceiver up to 1 km away. The police car can then follow it and gradually reduce its speed by remotely controlling the car's fuelling via its engine management system.

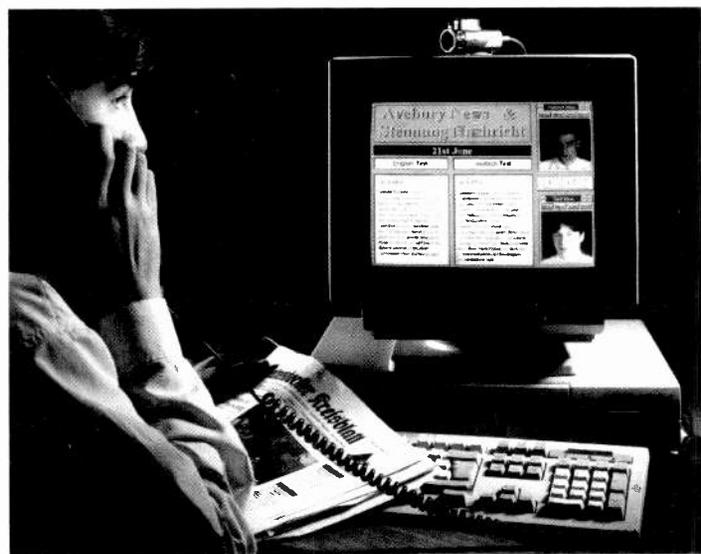DemonScan, when perfected, will add £250 to vehicle price but will be free to the police force. The company behind *DemonScan*, is the Kent based Knightwatch, which developed the device under the 'Sold Secure - Partnership Against Car Theft' organisation, that provides testing and endorsement services for vehicle security devices.



Microsoft loses software patent battle

Microsoft and Stac Electronics have settled their differences on data compression for computer disks. Although the two companies now talk of cooperation, the agreement is a climb down by Microsoft, following a decision handed down in June by a judge in Los Angeles.

In February, Judge Edward Rafeedie held that Microsoft's *DoubleSpace* infringed Stac's patents and a jury awarded Stac \$120 million damages. Microsoft took the module out of dos in the USA, and gave customers a token promising a new system when it was ready.

In granting the injunction Judge Rafeedie was at pains to reassure the 15 million people who have bought the Version 6 of dos which includes *DoubleSpace*, and the near 100 million others who use earlier versions of dos which have no compression. They can all continue to use their PCs.

Stac's two US patents, USP 4 701 745 and 5 016 009, claim the root idea of searching data for sequences of bytes which are identical to sequences already processed, and then storing only code which identifies the location of previously stored identical sequences.

Within weeks Microsoft and Stac Electronics settled a cross licensing agreement. Microsoft will now be

Full colour led display

Integrated full-colour led based displays can now be built thanks to a breakthrough from Toshiba scientists.

They have developed a high-brightness blue-green led that can be constructed with conventional red leds on a single substrate to create full-colour displays. Leds have found favour in outdoor displays because of their high brightness, but full-colour displays

able to use Stac's compression technology.

In return, Stac will be able to use the 'pre-load' technique which Microsoft developed for seamlessly strapping a compression system to the MS-DOS operating system on which 90% of all personal computers now rely.

Microsoft will pay Stac \$1 million a month in royalties, for 43 months, and pay \$39.9m for shares in Stac. **Barry Fox**

could not be built because the blue primary colour was lacking.

The Toshiba led structure employs p and n-type layers of zinc selenide (ZnSe) grown on a gallium arsenide substrate. The blue-green led produces a brightness of 2Cd at a wavelength of 500nm. Its spectra width is just 10nm. The structure is designed to ensure current flows horizontally across the p and n-type layers.

School to school: ISDN was at the centre of a technology link-up demonstration between St John's School, Marlborough, and Bookholzberg School, Ganderkesee in North Germany. Arranged by multimedia expert Digithurst, the demonstration is part of a European Union research programme. The system includes video conference, translation and co-working facilities. The latter lets two people work together remotely using the same computer screen. The system is designed for use in schools as a language learning aid, and also in the publishing industry.

Self wins EW+WW/H-P writer's award

The winner of this year's Author Award Scheme sponsored by Hewlett-Packard is Douglas Self for his series of articles *Distortion in power amplifiers* which appeared between July 93 and March 94.

The judges, who were unanimous in their decision, were impressed both by the original observations presented in the series, and the rigorous investigations undertaken by Douglas Self used to support his assertions.

Douglas was presented with his prize, a Hewlett-Packard HP54600A 100MHz digital storage scope worth £2500, by Alan Grahame, UK director of Test and Measurement at the company's Bracknell headquarters.

Calling rf designers: 94/95 Writer's Award features £4000 prize


Following the success of last year's Writers Award, *Electronics World + Wireless World* and Hewlett-Packard will be launching a new scheme to run from October 1, 1994 to September 30, 1995.

The prize for the coming year's award is truly magnificent: a £4000 Hewlett-Packard HP8647A 1GHz programmable signal generator with GPIB interface, solid state programmable attenuator and built in AM-FM modulation capability.

Unlike last year's scheme, only articles which have an element of rf design will be eligible for consideration by the judging panel. It is hoped that this year's award will focus writer interest on rf engineering in line with the growing importance of radio frequency systems to an increasingly cordless world.

The aim of the award scheme is to locate freelance authors who can bring applied electronics design alive for other people. We want to commission articles on circuit design using the wealth of modern components and techniques now available but, for this year, with a focus on rf and microwaves.

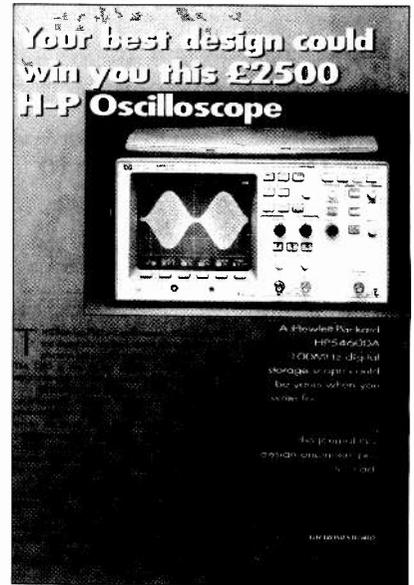Qualifying topics might include direct digital synthesis, microstrip design, application engineering for commercially available rf ICs and modules, receiver design, PLL, frequency generation and rf



measurement, wideband circuit design, spread spectrum systems, microstrip and planar aerials... The list will hopefully be endless.

All articles accepted for publication will be paid for – in the region of several hundred pounds for a typical design feature.

If you have a potential article to discuss, please call us on 081-652 3128, or write for further details to The Editor, *Electronics World*, Quadrant House, The Quadrant, Sutton SM2 5AS.



Rough ride for video CD

Video CDs are now going on sale amid total confusion and compatibility problems in the PC and video market.

Stickers on the covers of the first discs (*Pavarotti* and *Dinosaurs* from Castle Communications) explain that "video cd will play back on cd-i players with fmv cartridge, Amiga CD-32, 3DO, PCs with MPEG, Apple Mac with MPEG". Inside an insert slip promises that, "This disc can be viewed on any player which is MPEG compatible". Wisely Philips plays it safer and labels its first White Book CDs (movies such as *Indecent Proposal*) with talk of playback on cd-i players or any system that is "compatible with the video cd standard".

In theory a video cd should play back on any PC fitted with a cd-rom drive and MPEG video decoder board (eg Sigma Designs' *ReelMagic*). In practice it will often display pictures which lurch and

jerk, with sound that spurts in bursts.

This may happen on fast, high spec PCs, hooked to fast, high spec rom drives. To add to the confusion, the same PC rom systems may deliver smooth motion and sound when playing MPEG game discs marketed by Sigma.

So far the manufacturers have failed to give a clear explanation for this.

There are now three types of cd-rom disc. The MPEG CDs sold for use with the *ReelMagic* board do not follow the White Book standard. Instead they package the MPEG video as ISO 9660 rom files which any fast rom drive can read at full speed. This is why a rom drive and RM board may play RM's MPEG discs perfectly, while failing to play White Book video cds properly.


Sony has modified its 33A rom drive to work at full speed in 2/2 mode. The modification involved changing rom chips

in the player which store the firmware. Sigma now bundles the Sony drive with an RM decoder as an upgrade kit.

This will be no consolation to all those PC users who have already bought what they believe to be fast drives, and now find that they are obsolete. It will be no consolation to PC users who now buy new drives, or multimedia PCs, before the manufacturers are forced to admit that they are obsolete. Even if manufacturers provide new firmware in replacement rom chips, retrofitting will be a clumsy and expensive operation.

The situation will not resolve until the 2/2 requirement is publicised and manufacturers start labelling rom drives as 'White Book' or 'video cd compatible'. No manufacturer with a warehouse full of White Book incompatible drives will start 'compatible' labelling any sooner than absolutely necessary. **B. F.**

TELEVISION TRANSMITTERS AND TRANSPOSERS

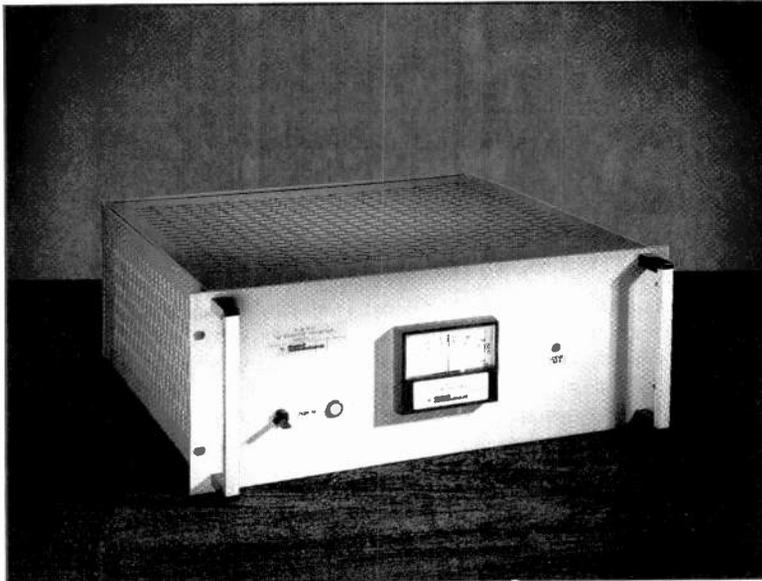

- ★ High stability crystal locked output
- ★ Phase lock loop and saw filter technology
- ★ Transposers can up or down convert in bands I, III, IV or V.
- ★ Aerials and feeder cables also supplied

- ★ Up to 100 watts RF output
- ★ Studio, satellite, VCR or RF input
- ★ Single channel – bands I, III, IV or V
- ★ NTSC or PAL system B, G, H or I
- ★ Automatic output protection
- ★ Output power meter
- ★ Integral forced air cooling
- ★ Integral power supply
- ★ Dimensions 4 units high 19" panel
- ★ Prices (ex-works and ex-VAT)

5W	£2,650
10W	£2,950
15W	£3,250
30W	£3,950
50W	£4,950
100W	£9,950

RESEARCH COMMUNICATIONS LTD

Unit 1, Aerodrome Industrial Complex, Aerodrome Road, Hawkinge, Folkestone, Kent CT18 7AG, UK
 Tel: (UK) 0303 893631 (Overseas) 44 303 893631 Fax: (UK) 0303 893838 (Overseas) 44 303 893838

CIRCLE NO. 106 ON REPLY CARD

JPG Electronics

Inverter toroidal transformers 225VA 10.5-0-10.5 primary 0-260-285 secondary £29.95
 1 FT8 5mm or 5mm, red on green 6p each
 Yellow 12.75 1p each
 High intensity red, green or yellow 5mm 30p each
 Cable ties, 1p each, £5.95 per 1000, £49.50 per 10,000
 High quality photo resist copper clad epoxy glass boards
 Dimensions single sided double sided
 48 inches £1.00 £1.25
 48 inches £2.75 £2.90
 6x12 inches £9.20
 12x12 inches £12.25
 Rechargeable batteries
 AA (HP 7) AA 500mAh with solder tags £1.55
 AA 700mAh £1.75 C(HP11) 1.8AH £2.20
 C 2 AH with solder D(HP2) 1.2 AH £2.60
 tags £3.00 P/P 3 8 1A
 D 1AH with solder 110mAh £1.95
 tags £1.95 Sub C with solder
 1/2 AA with solder tags £2.50
 tags £1.75 1 1/2 AA with tags (Philips) £1.55
 A AA (HP 1.6) C1V £1.55
 180mAh £1.75
 Standard charger charges 1 AA cells in 5 hours or 1 C or D in 12 1/4 hours + 1 x HP (1, 2, 3 or 4 cells may be charged at a time) £5.95
 High power charger as above but charges the C and D in 5 hours. AAs, Cs and Ds must be charged in 2 or 4.
 Nickel Metal Hydride AA cells high capacity with no memory 1000mAh £3.85 1200mAh £4.40
 Special offers, please check for availability
 12 x 16mm dia 1.2 £1.45
 Sock of 1.171mm x 16mm dia with red & black leads 18p £4.95
 Computer grade capacitors with screw terminals
 8800uf 20v £2.50
 87 0 0 0 u1 10v £1.95 6 8 0 0 0 u1 15v £2.95 10000uf 16v £1.50 58000uf 60v £1.95
 7 segment common anode led display 12mm £0.15
 LM2931A 1.5V low drop out 5A regulator 10220 package £0.85
 7812 and 7912 12V LA regulators £26.00 per 100
 LM337K 100k case variable regulator £1.95 (£1.41 100+)
 GaAs FET low leakage current S8873 £12.95 each (£2.95 10+ £7.95 100+)
 BS250 P channel mosfet £0.15 BC 559 transistor £3.95
 7H1505 hex inverter £10.00 per 100 Used 87.18
 Microcontroller £4.50
 SL952 UHF limiting amplifier 1G 16 surface mounting package with data sheet £1.95
 AM 27 S 0 2 £1.25 each 90 p 100 +
 (C11007)UB £1.10 per 100
 100+ (top 1000+)

Similar light gun terminated with a jack plug and PP3 clip gives a signal when pointed at 50Hz flickering light with output wave form chart
 DC-DC converter Reliability model V12P5 12v in 5v 200ma out 300v input to output isolation with data £4.95 each or pack of 10 £39.50
 Hour counter used 7 digit 240 ac 50 Hz £1.35
 QWERTY keyboard 58 keys good quality switches new £5.00
 Atlix A829004 large stepping motor 11v 7.5 step 27ohm 68mm dia body 6 3mm shaft £8.95 or £20.00 for a box of 30
 Polyester capacitors box type 22 5mm lead pitch 0.9uf 250vdc 18p each 11p 100+ 4p 1000+ 1uf 250vdc 20p each 15p 100+ 10p 1000+ 2.2uf 250vdc (27 5mm pitch) 30p each 20p 100+ 15p 1000+
 3.3uf 100vdc 30p each 20p 100+ 15p 1000+ 1uf 50v bipolar electrolytic axial leads £1.15p each 7.5p 1000+
 0.22uf 250v polyester axial leads 15p each 7.5p 100+
 Polypropylene 1uf 100vdc (Wima MKP10) 27 5mm pitch 32x29x17mm case 75p each 90p 100+
 Philips 123 series solid aluminium axial leads 33uf 10v & 2uf 10v 40p each 25p 100+
 Philips 108 series 22uf 63v axial 30p each 15p 1000+
 Multilayer AVX ceramic capacitors all 5mm pitch 100v 100pf, 150pf, 220pf, 10,000pf (10m) £1.10p each 5p 100+ 3.5p 1000+ £0.60p 10 of 370v ac motor start capacitor (dielectric type containing no PCB) £3.95 or £49.50 for 10
 Welwyn A23 9W 120ohm 85p each 20p 100+ 680ohm 2W metal film resistor 4p 100+ 2p 1000+ Solid carbon resistors very low inductance ideal for RL circuits 270hm 2W, 68ohm 2W £25p each 15p each 100+
 We have a range of 0.25w 0.5w 1w and 2w solid carbon resistors, please send SAE for list
 P.C. 100W PSU (Intel part 201035 001) with standard motherboard and 5 disk drive connectors, fans and mains inlet/output connectors on back and switch on the side (top for lower case) dims 212x149x149mm excluding swch £26.00 each £138.00 for 6
 MX180 Digital multimeter 17 ranges 1000vdc 750vac 2Mohm 200mA transistor Hfe 9x and 15v battery test £2.95 or £49.50 for 10
 AMD 27256-3 E-promis £2.00 each £1.25 100+ DIP switch 3P 0.12 pin (FRG SDC-X-023) 60p each 30p 100+
 Disk drive boxes for 5.25 disk drive with room for a power supply, light grey plastic, 67x208x247mm £4.95 £49.50 for 10
 Hand held ultrasonic remote control £3.95
 CV2486 gas relay, 30x10mm dia with 3 wire terminals, will also work as a neon sign £2.90p each £7.50 per 100
 A23 12v battery for car alarms or lighters £75p each £50.00 per 100


All products advertised are new and unused unless otherwise stated.
 Wide range of CMOS TTL 74HC 74F Linear Transistors kits, Rechargeable batteries, capacitors, tools etc always in stock. Please add £1.95 towards p&P. VAT included in all prices

JPG Electronics, 276-278 Chatsworth Road, Chesterfield S40 2BH
 Access/Visa (0246) 211202 Callers welcome

CIRCLE NO. 107 ON REPLY CARD

August 1994 ELECTRONICS WORLD+WIRELESS WORLD

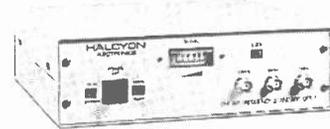THE DEFINITIVE 'OFF-AIR' FREQUENCY STANDARD



Still Only
£195+VAT
 carriage extra

- ★ Provides 10MHz, 5MHz & 1MHz
- ★ Use it for calibrating equipment that relies on quartz crystals, TCXOs, VXCOs, oven crystals
- ★ Phase locks to DROITWICH (rubidium controlled and traceable to NPL)
- ★ For ADDED VALUE also phase locks to ALLOUIS (cesium controlled and traceable to OP – French eq to NPL)
- ★ British designed and British manufactured
- ★ Options available include enhanced receiver, sine wave outputs and 13MHz output for GSM. Prices on application.

Output frequencies –
 10MHz, 5MHz, 1MHz
 Short term stability – better than 1x10⁻⁸ (1 sec)
 Typical – 4x10⁻⁹ (1 sec)
 Long term – tends to 2x10⁻¹² (1000 sec)

SUPERB DUAL TRACE SCOPES, TELEQUIPMENT D61A, 10mV SENSITIVITY, 10uS-500mS/DIV (& x5), X-Y INPUTS, Z-MOD, INT/EXT/TR/TVIGS, ETC. FROM £99

HP 608F SIG GEN 10-455MHz AM/CW £69
 PLESSEY TCT10 SIG GEN ANAL 50-300 BD 5 £95
 MUIRHEAD K231A TEMP CONT PRECISION STD CELL £10 TO £25
 MARCONI TF2212 X-Y DISPLAY £195
 LEVELL TM2 TRANSISTOR CHARACTER METER £59
 MARCONI TF2300 FM/AM MODULATION METER £95
 B&K 4420 STATISTICAL DIST ANALYSER £35
 BACHARACH MV2 MERCURY SNIFTERS £35
 DAWE 1405DR S SOUND LEVEL METER £95
 QUAD 333 STEREO POWER AMPS £95
 DRAKE VM2700 MATCHING N/WORK & PS PSU £95
 PHILIPS PM3065 100MHz DUAL TRACE & TB £750
 SCOPE 4 456 6MHz SINGLE TRACE £95
 SCOPE 4 4D10BL S 10MHz WITH EXTEND CD LF TB £149
 LEADER _BO-9C ALIGNMENT SCOPE £115
 IWATSU SS116 DUAL TRACE 0MHz £175
 TELEQUIPMENT D1011 10MHz DUAL TRACE £165
 TEKTRONIX 2215 60MHz DUAL TRACE DE, T/B £215
 TEKTRONIX 453A 50MHz DUAL TRACE DE, T/B £249
 H P 8445A VECTOR VMETER 1GHz £395
 TELEQ PMENT D67A 25MHz, 2T, DEL T/E £295
 HITACHI VC 6015 10MHz DIGITAL STORAGE £79
 HP134A X-Y DISPLAYS £149
 OERTL NG V20 SINGLE PAN BAL D 1mg/2Cdg £69
 ANALYTICAL BALANCES WITH WEIGHTS 250g £89
 MARCONI TF2330 WAVE ANALYSER 20Hz-50KHz £149
 LEVELL TM66 MICRO V-METER F 450MHz £95
 ROBIN OM200 LIGHT METER 0-50K LUX £75
 TEKTRONIX 545 PUG-IRIS VARIOUS £10 TO £25
 XT's WITH MONITORS AND KEYBOARDS FROM £95
 LEVELL TM38 MICRO V-METER 3MHz £95
 HP4951C PROTOCOL ANAL & 18179A RS232CV24 POA £35
 TIME ELECTRONICS 2003M DC V POT 0.02% POA £35
 HP6131C DIGITAL VOLTAGE SOURCE POA £95
 LING 140A DIGITAL CURRENT SOURCE POA £95
 LING DYN VIB GEN 406 & PA300 PWR OSC POA £95
 RADIOMETER BKF6 DIST METER 20Hz-20KHz £95
 CITOH CX6000 6-PEN A4 PLOTTER, CENT/RS232 £135
 GOULD 2400 4-PEN CHART RECORDER £149
 X-Y RECORDERS A3 & A4 FROM £35 TO £139
 PHILIPS PM6456 FM STEREO GENERATOR £175
 MARCONI TF2300 FM/AM MODULATION METER £95
 HEMPHILL MIDWAY RECORDER £195
 FEEDBACK SS0603 1MHz SINE/SO OSC £195
 LCR BRIDGE WAYNE KERR CT492 £79
 LCR BRIDGE AVO B151 £195
 LCR BRIDGE MARCON TF2700 £145
 LCR BRIDGE MARCON TF2701 £125
 LCR MARCONI TF1313 0.25% £95
 LCR COMPONENT COMPARATOR AVO CZ457/S £95

LIST AVAILABLE BUT 1000's OF UNLISTED BARGAINS FOR CALLERS. ALL PRICES EXC. OF P&P AND VAT
 QUALITY ELECTRONIC EQUIPMENT ALWAYS WANTED

HALCYON ELECTRONICS
 423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR
 SHOP HOURS 9-5.30 MON-SAT. TEL 081-542 6383. FAX 081-542 0340

CIRCLE NO. 108 ON REPLY CARD

RESEARCH NOTES

Jonathan Campbell

DSP flattens steel precisely...

In the arduous environment of a steel rolling mill, DSP can be used to track the distance between rollers up to 60mm apart to a resolution of 0.25µm.

DSP technology could find itself being used in the anything but quiet environment of a prototype steel rolling mill. Engineering research consultant Adrian March has developed a system that relies on dsp to process linear measurements in absolute terms rather than relative ones.

Normally coordinate measuring systems simply count the number of scale positions between one position

and another. March's optical device determines the 'actual' position under the reading head so it can not be thrown off by dirt or power cuts – or steel sheet slamming into the mechanics. In the steel mill the system will need to measure roll separation of up to 60mm with a resolution of 0.25µm.

Measurement depends on reading a transmissive scale consisting of binary pseudo-random patterns. By

reading a small length, absolute position can be determined.


Imaging optics have been replaced by a lens that focuses light from a led into a parallel beam to shadow the scale on a standard linear charge-coupled device. The image from the sensor is read out at intervals between 0.5-5ms.

DSP interpretation consists first in recognising the position to the nearest ccd pixel of the primary pseudo-random number pattern. The process involves a mathematical correlation which establishes the position in which the best match is obtained against a reference number string. That done, an interpolation can be performed to a fraction of a scale division.

Any variations in scale accuracy are overcome by reading at least 256 scale divisions at all times. For highest accuracy a scale can be calibrated and a look-up table used by the processor to correct residual errors at all points along its length.

In theory, March says, the system can measure up to 24m and down to fractions of a mm, with claimed resolution of an Angstrom.

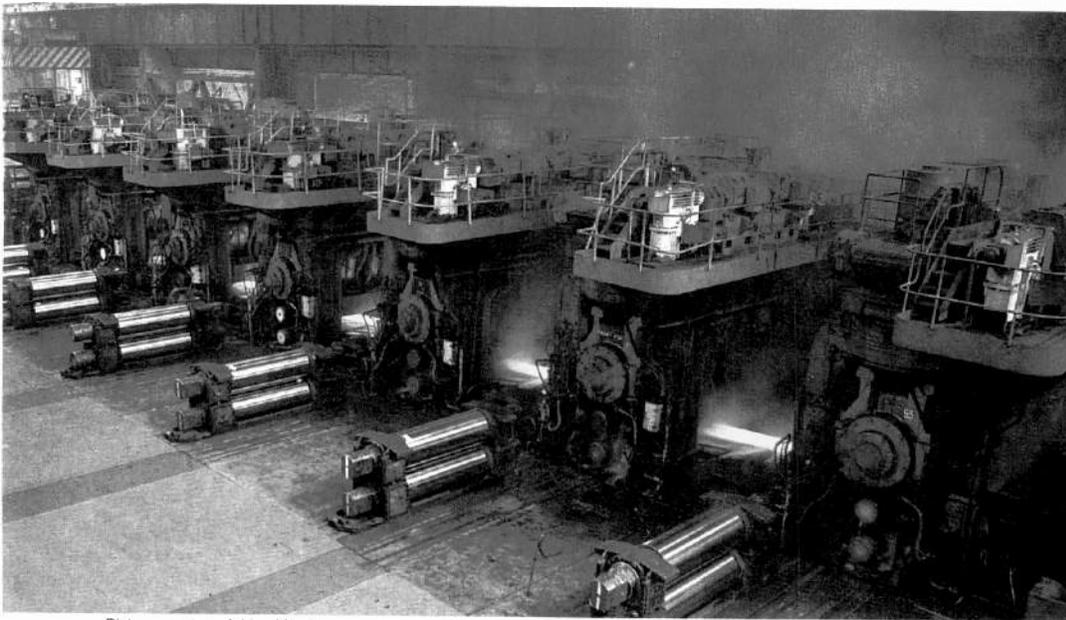A second system, aimed at a different application, is due to go into production at the end of this year. It will measure a distance of 1mm with a resolution of 1nm.



Picture courtesy Adrian March

...and sharpens hearing

Fast developing dsp technology could hold out new hope for millions of partially deaf people who are unable to benefit from current hearing aid design, if work being carried out at Washington University comes to fruition.

Devices that work and people actually want to use would be the result, according to Washington's A. Maynard Engbretson who has been testing a dsp-based device with impressive results.

Professor Engbretson, who holds posts in both the Department of Otolaryngology and the department of Computer Science at Washington University, says (*IEEE Engineering in Medicine and Biology*, April/May 1994, pp.238-248) that today's hearing aids are simply not good

enough. "It is not uncommon for a person to buy a hearing aid and then not use it because it does not help very much", he says.

But with dsp technology: "it would appear that the stage is set for a major advance in hearing aid development".

Engbretson likens the impaired ear to a flawed instrument such as a spectrum analyser with defective channels.

Part of the difficulty with hearing aid design is that the ear behaves differently for soft sounds near the hearing threshold than it does for loud sounds. There are also physiological and psychological characteristics of an impaired ear that have to be taken into account. The situation is complicated by the

fact that hearing aid development requires a knowledge of acoustics, transducers, signal processing, auditory physiology and psychophysics as well as low power semiconductor technology.

Current hearing aid design using analogue circuitry is very close to its limits in terms of size constraints and fundamental transistor scaling considerations. Dynamic range of an op amp – the building block of an electronic filter – decreases as the three-halves power of feature size. With hearing aid dynamic range only just being acceptable now, further size reduction is not practical. But the elementary amplifier (inverter) of a digital processor requires only enough dynamic range to resolve two states.

Overall dynamic range is determined by the number of digital stages used.

In a digital processing structure, complexity increases as the inverse of the square of the feature size and switching energy decreases as the cube of feature size. So as feature size is reduced, greater dynamic range and complexity is possible with less power consumed.

Modern hearing aids still reflect their 1940s origins, though growing from single-transistor amplifiers to modern multichannel designs containing thousands of transistors. Multiple channels attempt to provide different compression characteristics for different frequency ranges and tiny potentiometers are often used to adjust the compression characteristics. Newer hearing aids may be electronically programmable, with parameters down-loaded from a computer-based fitting system and stored in digital registers.

But tests on digital hearing aids carried out at the Central Institute for the Deaf at Washington University could radically alter hearing aid design. Functionality of the prototype devices includes four-channel compression, adaptive noise reduction and feedback cancellation. For example, feedback cancellation, using an adaptive fir filter, provided an additional hearing aid gain margin of between 10-15dB, meaning roughly an additional 20-30dB of patient hearing loss that can


be accommodated by the aid. Partially deaf people, using the device adjusted to a gain of their own liking for various conditions, improved their word identification scores by 7% with this facility.

Adaptive noise reduction creates an estimate of the stationary components of signal and noise then uses an inverse filter to reduce hearing-aid gain at frequencies where the estimate is large. Engebretson says noise reduction was preferred by patients for both soft and loud speech, and word intelligibility scores was much improved for soft speech in the presence of machinery noise.

FIR filters were also used to experiment with what Engebretson refers to as level-dependent-spectral shaping (LDSS). Work was based on the fact that hearing-impaired people preferred different gains and frequency responses depending on signal level. Frequency responses of two channels were set to the person's preferred frequency responses when listening to soft and loud speech and the other two channels set at in-between, interpolated, values.

Though there was little difference in loud speech in noise conditions, soft speech in noise using LDSS produced significant improvements over a wide range of signal levels.

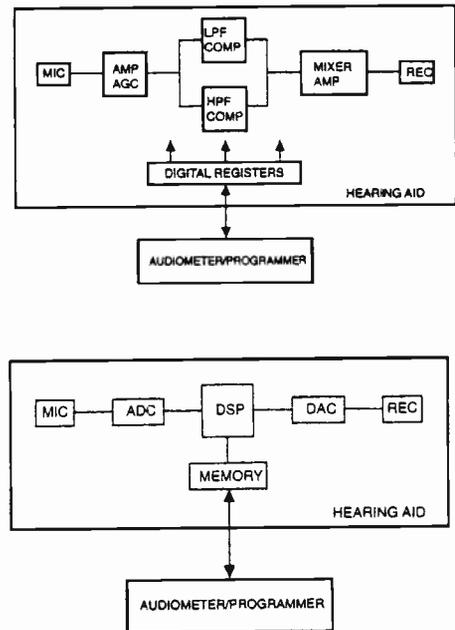Much work still has to be done before dsp hearing aids become a reality. One question yet to be answered is: what exactly is required from a hearing aid?



Top – multichannel hearing aid pushing current hearing aid design to its limits. Bottom – dsp design could open up new possibilities for people with hearing impairments.

Engebretson summed up the current position as that we are technically at a point where we can create very sophisticated hearing aids. But the question is what exactly do we want to do?

“Building circuitry is just a matter of putting up the money and getting people together. The problem is that we don't have nice neat categories of hearing impairment. Research depends so much on the individual patient that it is difficult to produce general solutions”.

Sharing the secret to scientific problem solving

How secret is secret? If you've got a PC, 599 computer-powered friends, access to the Internet communications network and eight months to spare you might just be able to find out. That's what it took Arjen Lenstra of Bellcore in Redbank, USA, Paul Leyland of Oxford University and colleagues at MIT to unzip one of the methods used by cryptographers to keep messages for their eyes only. But the record-breaking cooperative computing feat may have ramifications far outside the arcane world of cryptography.

What the code-breakers did was to find the two massive prime factor keys of a 129-digit code. In effect they had cracked the code used in the RSA method of encryption where two very large prime numbers are multiplied together to create a third gigantic number. The

shear physical size of the numbers involved makes it very difficult to find those original factors from the product alone. Decoding encoded messages depends on knowing both factors as well as the large number that has been used to code the message.

The degree of security given by using a 129 digit product can be judged from the massive amount of computing power and time that was needed to factor it. But as far as cryptographers are concerned, the code was cracked, and indicates that they must move to using much bigger numbers, perhaps 400 digits long.

There is, however, a much broader lesson for the scientific community in terms of problem solving.

Dividing a task between 600 volunteers running 1600 machines

varying in size between parallel supercomputers and humble PCs, is the biggest demonstration of distributed number-crunching so far attempted.

In the search for the factors, with such large numbers involved, the only way to progress was to use an algorithm to look at the relationships between pairs of numbers and see how close they come to a solution. All those relationships were then collected together and cross-referenced in a database.

Paul Leyland of Oxford University told *EW + WW* that finding the prime factors involved a search similar in magnitude to needing to find millions of needles in a galactic-sized haystack.

“We were using an algorithm that looked for interesting relationships between numbers. When we had

enough interesting relationships, we put them together”.

But there are an infinite number of relationships and only one relationship in 100 million is interesting. The team had decided they needed 8.2 million interesting bits of data to solve the puzzle, meaning they had to investigate 8.2 million x 100 million relationships.

Their method was to call on volunteers to link up to a central

MIT computer, using electronic mail, and download the necessary code to enable them to do their own chunk of processing. The MIT computer also gave them instructions on what to do and a place in the haystack to start searching for their needles.

When their program had been processed, volunteer data was e-mailed back to MIT where it was batched up.

After eight months toil, two prime numbers of 64 and 65 digits, were squeezed out the other end.

“Similar techniques have been used over the past 5 years though ours was by far the largest project to do this”, says Paul Leyland.

But without doubt, the real achievement was the coordination of so much, and so diverse, computing power in the pursuit of a single scientific goal.

Polarity proposal that is music to the ears

Would the kettledrum sound different if struck from the inside rather than outside? It might seem the sort of problem to worry only the most dedicated of percussionists. In fact it is part of the much wider issue of acoustic polarity – can we hear when polarity of reproduced music has

transient signal. But it does present the ear with a fundamentally different signal – compressions are replaced by rarefactions and vice versa.

The eardrum at any instant is “pushed” instead of “pulled”, an effect that audiophiles have long wondered if they should include on their hit list along with the need for reduced phaseshift, phase linearity and minimum phaseness in audio equipment.

Up to now, there seems to have been little attempt in recording practice to maintain original polarity – in the consumer market Greiner and Melton describe the situation as “total chaos”. But with processing in the digital domain making it easier to control polarity, they decided that now was the time to determine the contribution that absolute acoustic polarity makes to the accuracy of reproduced sound.

Previous experiments have proved that when the polarity of a simple waveform is switched, listeners describe a change of pitch or timbre of the signal. So Greiner and Melton set up a listening room in such a way that this effect was apparent to almost everyone. Then with the help of 39 students at Wisconsin they set out to listen to a range of instruments played in various styles to see if the effect could still be heard.


Musical examples demonstrating large asymmetry in the time domain were selected, as this property was felt to be significant when a signal was inverted, with individual instruments highlighted in the pieces. The result was that the ability to hear the polarity inversion gave only a slight positive bias, with piano and classical guitar yielding

significantly higher correct responses.

The masking factor seems to be that music is usually so complex that there is often too much going on to allow human concentration on subtle effects, and vibrato, tremolo and instrument filigree may obscure inversion.

The fact that the guitar and piano were most often picked out when inverted, instruments showing little asymmetry, suggests that is not the property most affecting inversion. More likely, they say, is that there are other psychoacoustic effects caused by the attack and decay properties of the signal that help the ear identify the correct acoustic polarity of the signal.

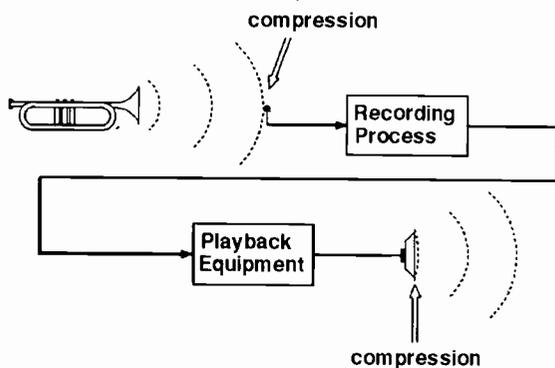The authors conclude that though polarity inversion is not easily heard, it can be picked up in certain circumstances. It makes sense to keep track of polarity during the recording process to avoid any problems later. Then, when someone actually does play their kettledrum from the inside, we'll all be able to appreciate their efforts. ■



If compressions at the microphone were reproduced as rarefactions at the loudspeaker, the polarity of trumpet sound reaching our ear would have been inverted. But would we notice the difference?

been reversed: when loudspeakers have been incorrectly wired up for example? The answer is a qualified yes, but you have to look hard to find out cases where it matters.

The researchers who posed the kettledrum question, throwing down the gauntlet for avant garde musicians the world over, are Richard Greiner, professor of electrical and computer engineering at University of Wisconsin, and Douglas Melton, a sound and vibration specialist at Digisonix Inc. They were prompted (*Journal of the Audio Engineering Society*, Vol 42, No 4, pp.245-253) by the fact that polarity inversion does not distort the phase and amplitude relationships between frequency components of a signal, nor does it change the temporal shape of a

John Wilson has relinquished his post as EW+WW Research Notes creator – a function he has executed splendidly for the past eight years. This results from his promotion to a new and more demanding position at the BBC. Although this means the loss of one of our most valued contributors, we wish John every success in his new position.

Taking over from John is former EW+WW deputy editor Johnathan Campbell, who has a lust for scientific knowledge and a keen nose for a story. Of course we wish Johnathan every success too.

Field Electric Ltd.

Tel: 0438-353781 Fax: 0438 359397

Mobile: 0836-640328/0860-213370

Unit 2, Marymead Workshops,
Willows Link, Stevenage, Herts, SG2 8AB

Apple II GS and Apple colour monitor etc £200 C/P £24
1.44Mb Laptop floppy disk drives new £16 C/P £3
72 pin Simms for PS2 Compat Dell etc
Parallel & Serial data switches up to 8 ways - Ring for details
Compaq enhanced at keyboards (no cable) £11 C/P £5
IBM 3363 optical disk drive £00 C/P £20
102 key AT enhanced keyboard with PS2 type plug £13.95 PS2 to 5 pin Din
Toshiba external 5.25" F.D. drive PA7225E new and boxed £3.25 C/P £3.50
TEAC 5.25" BBC compatible F.D. drives 360K/720K refurbis £45 C/P £7.50
16 bit hard disk/F. disk controller card £8.55 C/P £3.75
SCSI hard disk drive's new CDC 344Mb £2.00 C/P £3
Yusasa maintenance-free rechargeable battery NP7-12 12v 7.0Ah 15x6.4x9.2 £20.00 C/P £4.50
Rose die-cast box 17.5x5.6x7.8 new £2.25 C/P £1.80
Sony 7" colour monitor KTX-9000UB 240vAC input with manual: inbuilt modem, needs to be converted to RGB etc £25 C/P £16.00
386 5x16 CPU (Intel) motherboard with Phonix Bios 6x16 slots: 2x8 bit slot. Takes dram or Srr m memory £25 inc C/P
310mmx215mm £14 inc C/P
386 5x16 CPU (Intel) motherboard without Bios etc

TEST AND MEASUREMENT EQUIPMENT

H.P. 3490A Multimeter	£185	JJ Inst. PL4 recorder	£75
H&H TEI O'scope reference unit for Philips & Tektronix O'scopes	£95	Sorensen SRL 40-12 0-40 VDC 0-12A metered 115 VAC input	£125
486DX 20/25/33 CPU's from	£110	KSM SCT-200 15 power supply 0.200V 0-15A	£200
Micropolis 382mb SCSI hard drives NEW	£350	AVO RM 215F3 AC Breakdown Tester	£95
Seagate 426mb SCSI 2 hard drives NEW	£425	Schlumberger 4000 Precision Sig. Gen.	£150
Maxtor 760mb SCSI hard drives NEW	£550	Schlumberger 4900 RF-AF Measuring Jnit	£150
Wangtek 525mb SCSI tape drives NEW	£150	Wyse 60A Terminals new & boxed with keyboards	£195
Tektronix standard amplitude calibrator 067-502	£100	Tektronix 2213 O'scope 60MHz	£395
Fluke 8010A digital multimeter	£105	Fluke 335A DC voltage standard: differential voltmeter, null detector	£350
EH microwave swept oscillator model 574-1 7-12.4 GHz	£450	Farnell B30/20 0-30VDC @ 20A	£250
Systron donner pulse gen, 100c	£95	AEI Gauss meter FB22 form with p-obc	£117
Compiot series 7000 digitizer tablet with Compiot series 7000 digitizer	£600	HP 331A distortion analyzer	£150
Hydrostatic stability indicator HSM-400 P1	£800	FM Rotary attenuator 27/11	POA
Astec SA 30/1306, new and boxed PSU 240V ac input, +5V at 2a + 15v at 1.8a - 15v at 0.3a	£1250	HP Frequency meter X532B	POA
HP 7221A plotter	£150	HP 1740A 100MHZ oscilloscope. Cuat-CHN with 3rd CHN, trigger view etc	£325
HP 1332 x-Y display with options 215/300 315/570/631	£150	AS Eletek switch mode variable PSU 25VAC input, 0-60VDC 25A max metered: 7x: 2.5x5"	£325
Hughes model 639 scan conversion memory	£300	HP 9872c plotter	£175

All above equipment + 17.5% VAT - Please ring for c/p prices

We would like the opportunity to tender for surplus equipment
Official orders, credit card telephone orders accepted with Access,
Amex, Diners, Visa cards. Overseas enquiries welcome
c/p rates UK mainland only. Please ring for c/p rates not shown
All prices inc VAT unless stated. Stock list available



CIRCLE NO. 109 ON REPLY CARD

KENWOOD

TEST & MEASURING INSTRUMENTS
A SUPERB RANGE OF OVER 100
QUALITY INSTRUMENTS.

Available from
B.K. ELECTRONICS



FM-AM Signal Generators ★ Colour Pattern Generators ★ Video Signal Analyser ★ Video Timing Analyser ★ Video Noise Meter
★ Distortion Meter ★ Waveform Monitors
★ Vectorscopes ★ Audio Generators ★ Wow and Flutter Meters ★ Electronic Voltmeters
★ Digital Multimeters ★ Function Generators
★ Frequency Counters ★ Bus Analyser
★ Resistance Attenuator ★ Oscilloscopes ★ Fully Programmable Digital Storage Oscilloscopes
★ Regulated D.C. Power Supplies

A free, 50 page colour brochure, including price list, is available on request. Please make your request on company headed notepaper, by post or by fax, to:


B.K. ELECTRONICS
Unit 1 Comet Way,
SOUTHEND-ON-SEA,
Essex, SS2 6TR.
Tel: 0702-527572
Fax: 0702-420243



CIRCLE NO. 110 ON REPLY CARD


Electronic Designs Right First Time?

Schematic Design and Capture

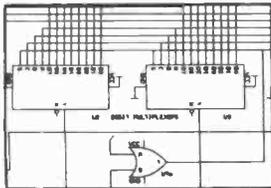


Create your schematics quickly and efficiently using EASY-PC Professional. Areas of the circuit can be highlighted on screen and simulated automatically using PULSAR, ANALYSER III and Z-MATCH our simulation and design programs.


Digital and Analogue Simulation

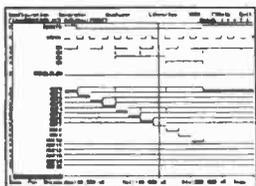

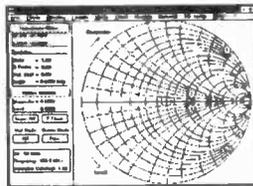Modify the configuration and change component values until the required performance is achieved.



PCB Design

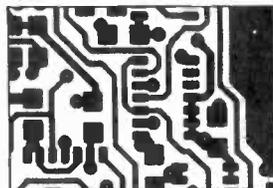

The design, complete with connectivity, can then be translated into the PCB. The connectivity and design rules can be checked automatically to ensure that the PCB matches the schematic.

Visa, MasterCard, Amex welcome

CIRCLE NO. 111 ON REPLY CARD

Affordable Electronics CAD

EASY-PC: Entry level PCB and Schematic CAD	£98.00
EASY-PC Professional: Schematic Capture and PCB CAD. Links to ANALYSER III and PULSAR.	£195.00
EASY-PC Pro' XM: Greater Capacity, XMS Version.	£245.00
PULSAR: Entry level Digital Circuit Simulator ~ 1500 gate capacity.	£98.00
PULSAR Professional: Digital Circuit Simulator ~ 50,000 gate capacity.	£195.00
ANALYSER III: Entry level Linear Analogue Circuit Simulator ~ 130 nodes.	£98.00
ANALYSER III Professional: Linear Analogue Circuit Simulator ~ 750 nodes.	£195.00
Z-MATCH for Windows: Smith Chart based problem solving program for R.F. Engineers.	£245.00
FILTECH: Active and Passive Filter design program.	£145.00

No penalty upgrade policy. Prices exclude P&P and VAT.

Number One Systems Ltd.

Ref WW, Harding Way, St. Ives,
Huntingdon, Cambs. PE17 4WR, UK.

For Full Information Please Write, Phone or Fax.

Tel: 0480-461778
Fax: 0480-494042



Teletext via your PC

Today's teletext broadcasts contain a wealth of information on diverse subjects from share prices to weather. Laurence Cook's teletext plug-in for the PC opens up the possibility of grabbing this information and printing it, processing it or turning it into a database.

Broadcast teletext services are a useful, regularly updated and essentially free source of information on a wide range of topics. Accessed via a tv screen however, teletext information cannot be printed or saved for future reference.

A solution to the transient nature of teletext is the subject of this article. Described here is a complete teletext adaptor that plugs into a single slot in your PC. It accepts a standard antenna input and appears to the PC as a standard serial communication port.

With suitable software, your PC becomes a teletext terminal with the ability to print or save pages to disk or ram. Built into the adaptor's tuner is an intermediate-frequency stage together with high-performance, factory pre-aligned video and audio demodulators. As a result, baseband video and audio signals can be made available via

sockets at the rear of the PC. These can feed multimedia cards or other devices which might rely on such signals in the future.

My complete teletext adaptor is a three-quarter length printed circuit board laid out entirely for conventional through-hole components. As such it lends itself to small quantity and one-offs. Details of the board are presented at the end of this article.

Design overview

As is clear from **Fig. 1**, the adaptor divides into distinct functional blocks.

Using a ready built module with baseband outputs for the tuner section save a lot of design and commissioning work. Made by Philips, the chosen module has a digitally synthesised front-end. Using an enclosed and decoupled module also avoids problems with emi emanating from inside the PC.

Control of the tuner is carried out via an I²C bus interface, which is common in many modern TV sets. Synchronous clock and data lines of the I²C bus are driven by simply toggling bits on a parallel port.

Since I had already developed PC terminal software for an external adaptor that connect-

ed to a serial communication port, I developed the teletext adaptor with the same interface. This has the advantage of making software easy to write. Jumpers allow setting the interface up as COM1 to COM4, with interrupts IRQ3 or IRQ4. More on this later.

Because the Philips tuner has varicap diodes it needs a stabilised 30V, but the PC only has 12 and 5V rails. A simple charge pump generates about 50V from the PC's 12V rail. This is then shunt stabilised to 30V. The 5 and 12V supplies are used by the adaptor's co-processor and analogue circuits respectively. They are first filtered by small inductors and decoupled capacitively.

Off-air video from the tuner module passes to the video interface. Here, recovery of the 6.9375MHz clock and data from up to 16 data lines per tv frame take place.

Within the video interface, data slicing is carried out by a Philips SAA5231. This device connects to a separate level shifter which converts the chip's output to ttl levels for connection to the digital block that follows. Off-air sync is extracted by the chip and conditioned as line and frame syncs before also passing to the digital block.

System requirements

IBM PC-AT or compatible with DOS 3.3 or higher
640K ram minimum
Hercules, CGA, EGA, VGA or SVGA graphics adaptor
Free 8 or 16 bit slot for 3/4-length card.

In earlier designs, level shifting was performed by two expensive high-speed comparators to minimise skew between clock and data. This design uses a much cheaper dual comparator. Initially I discounted the dual comparator because it had poorer switching times combined with a broader tolerance. This could have caused reception errors due to skew with jittery off-air signals.

A little thought and experimentation revealed however that differential delay between channels is most important. Since the chosen IC has both comparators on the same substrate, the actual skew is no worse than with two separate, expensive chips.

At the core of the logic block is a 10MHz Hitachi HD64180S microprocessor. This highly integrated device has a Z80-compatible instruction set but with additional instructions and enhanced microcode.

Integrated features of the processor include a high-speed multi-protocol serial communications interface and direct memory access controller.

These were key factors in my decision to use the device. Off-air data is clocked into the serial controller and shifted by the direct-memory-access controller into memory for processing. Even with the fast serial interface feeding the dma controller, the data capture leaves only 20ms for processing before the next packet of data arrives.

Pages requested by the host PC are processed by the 64180, which maintains an output buffer in ram. It then offloads the buffer more slowly at 9600 baud via its on-chip uart directly into the PC communication-port uart. From there, the data passes to the ISA bus and onward to the terminal software.

Design details

Tuner module. I chose the Philips FQ844 digitally-synthesised tv tuner. It has an integral IF strip and demodulates to baseband audio and video. Designed for European channels E21 to E69, the tuner covers the entire UK uhf tv band.

Tuner input is via a standard coaxial antenna socket which is an integral part of the casing housing the electronics. Since the casing is slightly too large to pass through the PC chassis slot, it needs filing. Make sure that absolutely all filings are accounted for before attempting to plug in the board.

Remaining connections are presented as pins on the edge of the case, which is intended for vertical mounting in a tv set. There is little room between slots in the PC so the tuner is laid flat on the pcb and connected via long wire-wrap type pins. Double-sided adhesive tape may be needed for anchoring the tuner to the board.

Audio from the tuner is fed via point TP₂₅ and dc block C₃₁ to phono socket P₄. This is off-air sound. When debugging the adaptor it's handy to have a monitor amplifier to hear whether the tuner has actually locked on to a given channel if the data side of things still isn't working.

Off-air video from the tuner feeds a phono

socket for external use but its main purpose is driving the data slicer in the video interface.

PC communications. Signals of interest on the 31 way card edge connector of the PC ISA bus are shown in Fig. 2. These are the lower eight data bits, SD0 to SD7, the lower ten address bits, SA0 to SA9, address enable, i/o read and write signals and system reset. Power rails and ground are also used. Interfacing

these straightforward signals to the chosen uart, a National Semiconductor NS16550AF, is simple.

In the original IBM PC specification only addresses for communication ports COM1 and COM2 were defined. However a de-facto standard has developed defining addresses for COM3 and COM4.

My design follows the four communication-port standard, jumpers J_{101,102} setting the


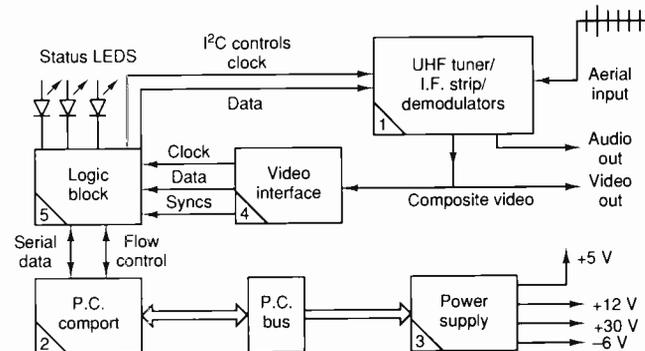


Fig. 1. Essentials of an off-air teletext decoder card for the PC. In addition to feeding teletext data to the PC, the adaptor also makes tv audio and video from the synthesised tuner available. No external power supplies are needed, but some power conditioning is required for comparators and the tuner varicap.

Fig. 2. To make hardware convenient and software writing easy, the teletext decoder is designed as a PC-slot card with an interface to any one of the four dos COM ports. The NS16550 universal asynchronous receiver/transmitter, or uart, interfaces to the PC slot using straightforward data, addressing and control signals.

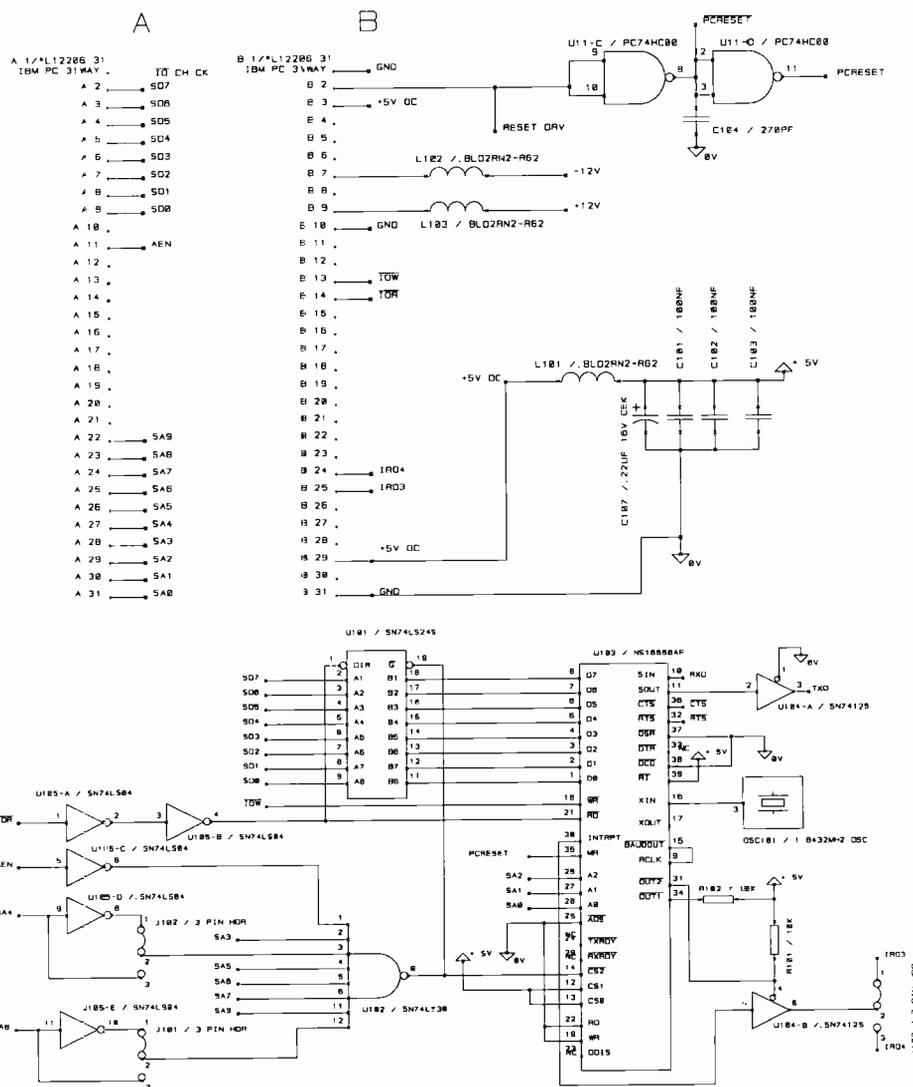

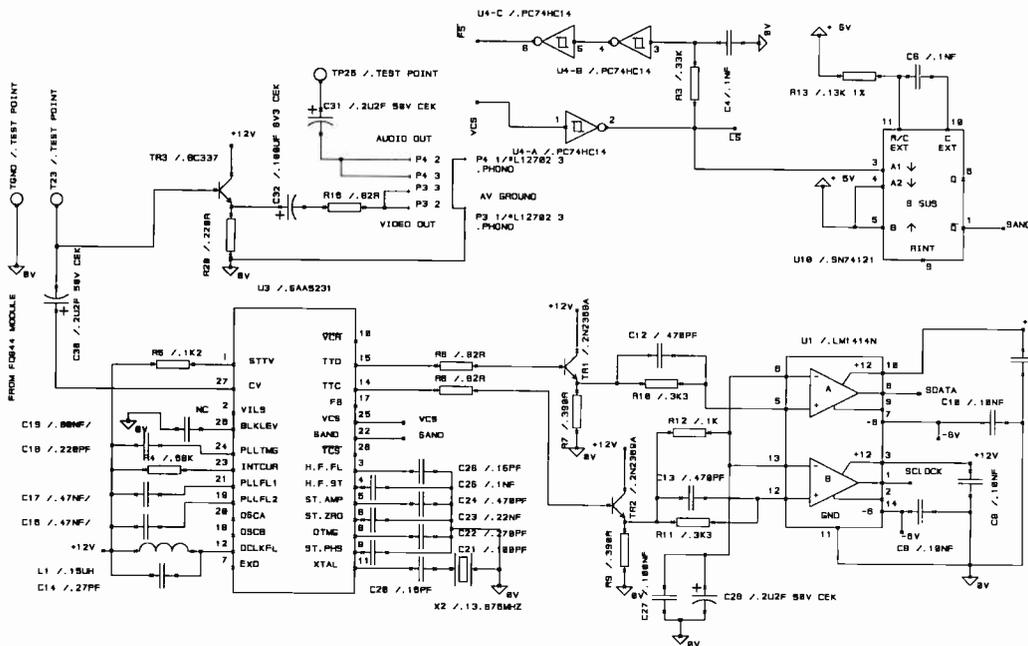


Fig. 3. Teletext information is separated from raw video by an SAA5231 data slicer. Off-air composite video appears at pin 27 while sync pulses are presented at pin 25.

required address according to Table 1. These jumpers select the true or complement address lines A4 and A8 for decoding together with remaining addresses from A3 to A9 in nand gate IC102. This generates an active-low chip-select signal directly feeding uart IC103 and bi-directional buffer IC101.

Buffering is needed to provide sufficient drive for the uart when it has to send data or status messages via the ISA bus. Should several cards be plugged into the bus, the uart would be overloaded if connected directly.

On the arrival of data, the uart alerts the PC by generating an interrupt signal. This is fed via IC104B to ISA bus common-interrupt line IRQ3 or IRQ4, depending on the setting of jumper J103. Recommended settings are shown in the table.

Serial data lines SIN and SOUT, together with handshake lines RTS and CTS, connected to the uart in the microprocessor. This provides out-of-band flow control between the microprocessor and the system, ensuring commands and data are not lost. All other uart serial port signals are ignored, being left unconnected or strapped to an appropriate level.

A separate oscillator module provides the 1.8432MHz ttl clock needed for the uart. My attempts to find a clever way of obtaining this clock from one of the other chips failed.

Video interfacing. Shown in Fig. 3, the video interface revolves around a Philips SAA5231 bipolar data slicer. Off-air composite video appears at pin 27. The chip strips out sync pulses and presents them at pin 25. They are

inverted by IC4A and presented as active low line syncs to the 64180 uart's data-carrier detect (DCD) pin. This is configured as a general-purpose input pin.

Monostable IC10 produces an 8.5µs pulse every line sync which is fed back to the sandcastle input of IC3, pin 22. This makes the chip respond as though it had other members of its family connected to it.

Timing components R13 and C6 should be accurate for correct operation. In the data slicer, crystal X2 oscillates at twice the broadcast data rate, which is exactly 444 times line rate. Inductor L1 and C14 prevent the crystal from oscillating at harmonics of its fundamental.

The oscillator locks onto the data stream, and is divided by two to provide true recovered data and clock signals at pins 15 and 14 respectively. Since these signals are not at ttl levels IC1 – a rather unusual dual comparator – is needed to convert them. It is powered from +12V and -6V, will accept inputs with a high dc offset, and produces complementary ttl outputs.

In this design, recovered clock from IC3 is buffered by Tr2 then integrated by R12/C27/C28 so as to generate a reference level at pin 13 of the comparator. This reference is the midpoint of the signal.

After hf compensation provided by C13, the signal is fed via R11 to pin 13 of the comparator. This makes dc offset on IC3 irrelevant. As a result, a ttl version of the data clock appears with unity mark-space ratio at pin 1 of IC1.

Recovered data follows a similar path through Tr1 to arrive at pin 8 of IC1. Delays through IC1 are closely matched between each half, so the phase relationship between important clock and data signals is preserved.

Now, the clock and data signals are applied directly to the microprocessor serial interface clock and data pins.

Logic block. Although the heart of the system, this section is essentially simple.

Referring to Fig. 4, IC14 is a watchdog chip made by Maxim, which serves as a longstop should the software run out of control. It also provides a clean power-on reset signal for the microprocessor; its output is or-ed with a reset signal from the ISA bus so pressing the PC reset button also resets the co-processor.

Inclusion of a watchdog reset timer, in conjunction with on-board non-volatile memory, IC9, means that the teletext receiver can operate without supervision. It can survive power failure or static-induced interruptions and recover whatever configuration it was last loaded with.

Connected to the microprocessor are 32K of eeprom and 32K of ram, decoded on-chip by /CS0 and /CS1 respectively. These occupy the full lower 64K physical address space. The third on-chip decode line, /CS2, is used to trigger the watchdog and is selected via the on-chip memory manager. No external decoding logic is involved in selecting memory devices.

Or gate IC13 generates memory and i/o read and write pulses. Access to the control port IC12 and associated circuitry by the read and write pulses is possible when A11 is true, /LATCH is low.

The lower three bits control the status leds, the next three control eeprom IC9, and the top two bits produce I2C clock and data signals. These are applied to the tuner module via points T13 and T14. Gates IC5B,C direct the I2C and eeprom data onto the microprocessor data bus from the latch when an IN instruction is executed. Thus with very little circuitry, the firmware is able to indicate its status, save and reload its configuration, and control the Philips tuner.

Connector P1 is provided for future expansion, such as the control of auxiliary I2C devices in commercial applications, or as a medium speed link to, say, text-to-speech converters. This could be a useful application of teletext for the blind.

Since the microprocessor is only available as a surface-mount plcc part, the board has been tracked to take an 84-pin through-hole socket. A bonus of the socket is that it allows the relatively expensive processor to be fitted last, minimising the chances of esd damage.

The processor needs to be a 10MHz part, specifically the IID64180SCPI0, which can be clocked at up to 20MHz. In this design the clock is 19.6608MHz which divides down to allow the uart to operate at 9600baud exactly. In addition, the maximum data rate of the communication interface under dma transfer is a function of clock speed. This clock frequency is high enough to accommodate the broadcast data rate.

Table 1. COM-port jumper settings used on the PC teletext board

	IRQ	J101	J102
COM1	4	3	3
COM2	3	1	3
COM3	4	3	1
COM4	3	1	1

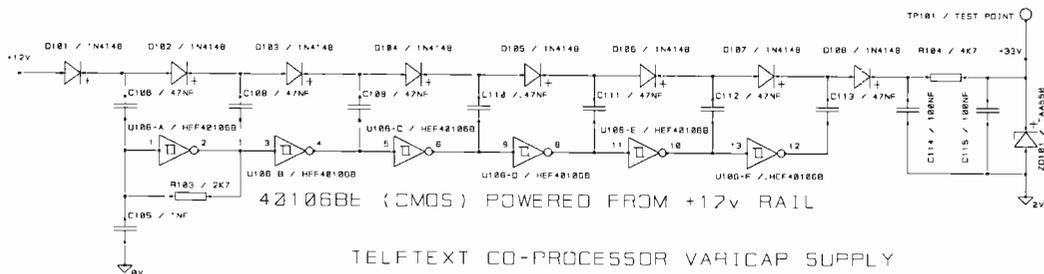


Fig. 5. Voltage multiplier used to supply the synthesized tuner's varicap. The free-running oscillator on the left feeds the multiplier chain, producing around 50V on the right. Following current limiting, a shunt zener produces a stable 30V varicap feed.

play on-screen. Headers are the top row of the display, the line with the date in it, while a magazine is the jargon for page hundreds. Empty page buffers are thus available for assembling the next transmission of the required pages, row by row.

Control of the co-processor is achieved over the serial link, using a well-established protocol. Operator page requests are converted into a format that the firmware understands by the terminal software. This protocol is available to programmers.

Addition of a tuner required the command set to be extended to select Channels E21 to E69, which was fairly easy to implement. Less easy was modifying the terminal software which in a commercial application had been produced without regard for such extensions.

In order to leave working software well alone, I chose to use a terminate-stay-resident (tsr) program to supplement the keyboard commands. The required channel, 0 to 9, is simply typed in as, say, Alt-C2 for BBC2, and so on.

Correspondence between E channel numbers and single-digit selection is achieved by extending the default configuration file to include local tv channel numbers. To invoke teletext operation, a batch file is run on the host PC which first loads the tsr then runs the

terminal software. The tsr picks up the local channel numbers from the configuration file and uses them to send to the PC communication port as required. On quitting the program, the tsr is unloaded.

Commissioning

There is no substitute for a thorough visual inspection of all the components before powering-on. Time spent here is worthwhile. Further testing depends on what test equipment you have access to.

A PC card extender for example allows easy access to a powered board for measurements. Clearly the first thing to check is the power supply and look for activity on the crystals and oscillator module. Thereafter you should set up the communication so as not to clash with existing devices. I used COM3.

Next, connect a good quality tv aerial and run the batch program supplied, having first edited the default.cnf file to include local channels and the chosen PC communication port and IRQ settings. Type Alt-C1, to select BBC1, and 100, for page 100. You should be rewarded with page 100 on screen with headers rolling past. If not, then there is a fault.

The external audio and video outputs are a good starting point although the software will need to have selected a channel for this to

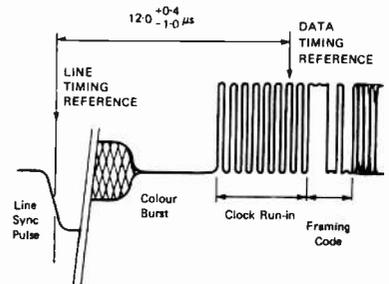


Fig. 8. Signalling the start of teletext data is a clock synchronisation run in comprising ones and zeroes. Immediately following is framing information that ensures that whatever is decoding the data starts reading it at the first bit of the first byte.

work. You can look for activity on the I²C bus when a channel is selected. A command from the PC causes LED₁ to flash. Off-air syncs cause LED₂ to flash, and data to the PC causes LED₃ to flash.

Reading

Figures 6, 7 and 8 are taken from the September 1976 *Broadcast Teletext Specification*, ISBN 0 563 17261 4.


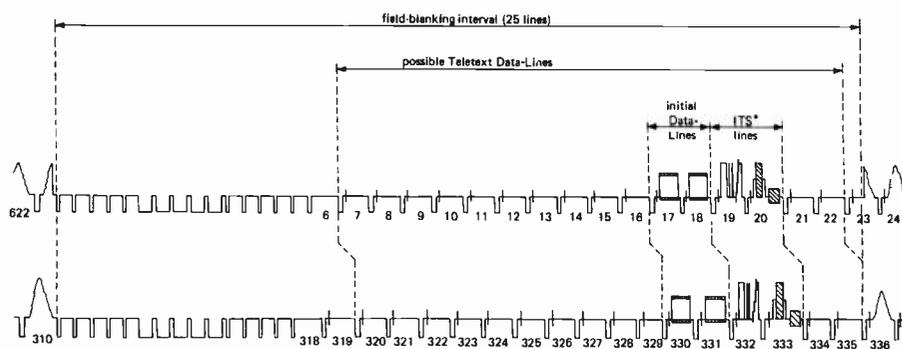


Fig. 6. Broadcast teletext data streams appear in up to 16 lines per tv frame, all within the blanking period. Data is transmitted at 6.9375Mbit/s.


Fig. 7. In the teletext lines of a broadcast tv frame, a logic 0 corresponds to black level while 66% white represents a logic one.

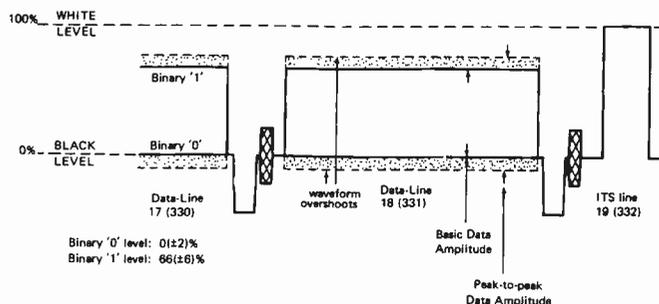

Please note that although this offer is made in good faith, EW+WW has no involvement in it and therefore cannot take responsibility for any problems that may arise relating to transactions between Citifax and readers.

Quickroute 3.0

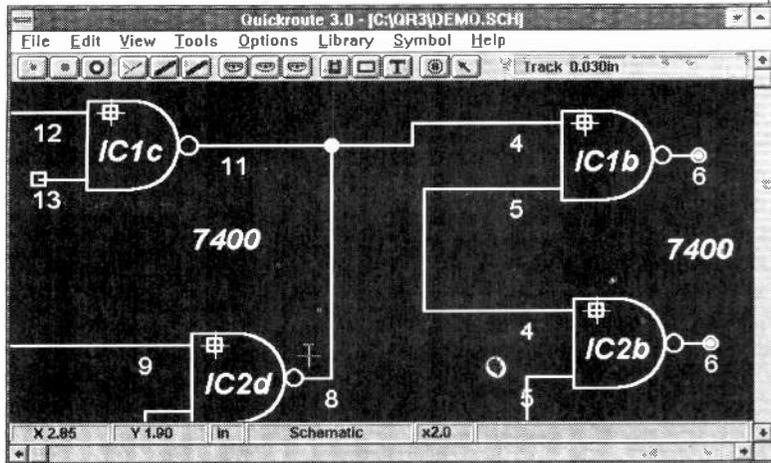PCB & Schematic Design System for Windows 3.1



Announcing a new range of affordable, powerful Windows based PCB and schematic design packages from **POWERware**.

DESIGNER £99 *

PCB and schematic design with all the new 'Easy-Edit' features and an Auto router!

DESIGNER+ £149 *

For larger PCB and schematic designs, adds Gerber and NC-Drill support.

PRO £199 *

Schematic capture, with integrated rats-nest generation and auto-router. Export net-lists for design checking.

PRO+ £299 *

Advanced schematic capture for management of larger schematics. Gerber Import facility for file exchanging.

For more details, contact **POWERware**, 14 Ley Lane, Marple Bridge, Stockport, SK6 5DD, UK.

* Prices exclude post & packing, etc.

Tel/Fax 061 449 7101

from
£99*
excluding P+P

CIRCLE NO. 112 ON REPLY CARD

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEXTRONIX 7000 SERIES OSCILLOSCOPES AVAILABLE FROM £200. PLUG-INS SOLD SEPARATELY

TEXTRONIX 2235 Dual Trace 100MHz Delay Sweep	£700
PHILIPS 3065 2+1 Channels 100MHz Dual Trace Delay Sweep	£500
TEXTRONIX 465 Dual Trace 50MHz Delay Sweep	£500
TEXTRONIX 475 Dual Trace 200MHz Delay Sweep	£500
TEXTRONIX 465B Dual Trace 100MHz Delay Sweep	£500
TEXTRONIX 465 Dual Trace 100MHz Delay Sweep	£500
TEXTRONIX SC524 Dual Trace 80MHz on TM4508 As New	£450
TEXTRONIX 2215 Dual Trace 60MHz Delay Sweep	£400
TEXTRONIX 455 Dual Trace 50MHz Delay Sweep	£400
HITACHI VS50P Dual Trace 60MHz Delay Sweep	£350
PHILIPS PM3127 Dual Trace 50MHz Delay Sweep	£400
LEADER L80-520A Dual Trace 35MHz	£225
GOLDL O51100 Dual Trace 30MHz	£160
FWTSU SS5702 Dual Trace 20MHz	£200
GOLDL O52508 Dual Trace 15MHz	£125
TELEQUIPMENT D32 Dual Trace 10MHz Mains/Battery*	£200
THANBAR T0315 Dual Trace 20MHz Mains/Battery	£300
N.P. 1714A Dual Trace 100MHz Delay Sweep Analogue Storage	£350

* THIS IS JUST A SAMPLE, MANY OTHERS AVAILABLE

NEWLETT PACKARD 1740A Oscilloscopes 100MHz Dual Trace Delay Sweep	only £350
MARCONI 201B Synthesized AM/FM Sig Gen 80kHz - 520MHz	£800
N.P. 8640B Signal Generator 20kHz - 1024MHz (opts 801/002/003)	£1500
N.P. 8620C Sweep Oscillator with 8624A 5.5 - 12.4GHz	£500
SYSTEM DOWNER 1702 Synthesized AM/FM Sig Gen 100kHz - 1GHz	£600
RACAL 9081 Synthesized AM/FM Sig Gen 1.5 - 520MHz	£500
FARNELL SS6520 Synthesized AM/FM Sig Gen 10 - 520MHz	£400
MARCONI TF2016 AM/FM Sig Gen 10kHz - 100MHz	£200
MARCONI TF2008 AM/FM Sig Gen 10kHz - 510MHz Sweep Facility	£250
MARCONI TF2015 AM/FM Sig Gen 10 - 520MHz	£200
MARCONI TF2016 with Synchronizer TF2171 (Lock box)	£375
MARCONI TF2016 with Synchronizer TF2173 (Lock box)	£375
PHILIPS PM5326 AM/FM Sig Gen 10 - 125MHz (FM limited)	£300
N.P. 8601A Sweep Generator 100kHz - 110MHz	£300
MARCONI TF2002B AM/FM Sig Gen 10kHz - 80MHz with Dig Synchronizer	£150
MAR/SARBERS 6600A Microwave Sweep Osc with 6651 Plug-in 26.5 40GHz	£250
N.P. 8650B Microwave Sweep Osc with 8657A Plug-in 26.5-40GHz	£300
LYONS PC711 Pulse Gen PRF 1Hz - 5MHz 10 nanoseconds	£75
FARNELL PG101 Pulse Gen 100ns 10MHz (1 sec 1Hz)	£125
RACAL/DANA P25 Pulse Gen 1Hz - 50MHz Dual Output	£200

OTHER B&K EQUIPMENT AVAILABLE

SPECTRUM ANALYSERS	
N.P. 3580A LED 0.5Hz - 50kHz	£1000
ANRITSU MS520B Tracking Generator 10kHz - 1700MHz	£1500
POLARON 641-1 10MHz - 10kHz	£100
N.P. 1431 with 8555A & 8552B 10MHz - 180kHz	£1700

Used Equipment - GUARANTEED. Manuals supplied if possible.
This is a VERY SMALL SAMPLE OF STOCK, SAE or Telephone for lists. Please check availability before ordering.
CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage

STEWART of READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: (0734) 268041. Fax: (0734) 351696
Callers Welcome 9am-5.30pm Monday to Friday (until 8pm Thursday)

EIP DANA 351D Microwave Frequency Counter 20Hz - 180GHz	£350
N.P. 5317A Frequency Counter 30MHz - 1.5GHz LED	£350
MARCONI 2435 Digital Frequency Counter 2GHz	£900
MARCONI 2437 Universal Counter/Timer DC - 100MHz 8 digit	£175
MARCONI 2431A Frequency Counter 10Hz - 200MHz 9 digit	£150
MARCONI 2430A Frequency Counter 10Hz - 80MHz 8 digit	£125
RACAL 9918 Frequency Counter 10Hz 520MHz 9 digit	£200
RACAL 9913 Frequency Meter 10Hz - 200MHz 1 digit	£125
RACAL 9911 Frequency Meter 10Hz - 120MHz 1 digit	£100
RACAL 9905 Universal Counter/Timer DC 200MHz 8 digit	£150
RACAL 9904 Universal Counter/Timer DC 50MHz 7 digit	£175
RACAL 9901 Universal Counter/Timer DC 50MHz 6 digit	£100
DATRON 1061A 4 1/2 digit Autocal Multimeter True RMS AC/Current	£1250
DATRON 1065 5 1/2 digit Autocal Multimeter with AC/DC/Ohms IEEE	£500
N.P. 3495A 5 digit Multimeter AC/DC/Ohms	£200
SOLARTRON 7045 4 1/2 digit Multimeter True RMS AC/Ohms	£400
MARCONI T1131A Universal LCR Bridge 0.1%	£125
WAYNE KERR B424 Digital Component Meter LCR	£80
HEATNET IB RLC Bridge	£60
MARCONI TF2308B Modulation Meter AM FM 0MHz - 1.2GHz	£100
DYMER 2055 Distortion Factor Meter 64Hz - 4.4MHz 0.1%	£100
RACAL 9301A True RMS Millivoltmeter 10kHz - 1GHz	£300
UKJUSUI AV23 AC Voltmeter Dual Channel 10Hz - 500kHz 300uV - 100V	£100
LEADER LRV181A AC Millivoltmeter 5Hz - 1MHz 100uV - 300V	£75
FARNELL TV570M2 70 Volts 5 Amps 35 Volts 10 Amps Metered	£300
FARNELL B30/20 30 Volts 20 Amps Variable	£250
FARNELL B30/10 30 Volts 10 Amps Variable	£200
FARNELL L30A 0 - 50 Volts 0 - 0.5 Amps Metered	£50
MARCONI (WEIR) TF2154 0 - 30V IA 0 - 15V 2A C - 7.5V 4A Metered	£60
BRANDENBURG Model 472R +/- 7KV Metered	£200
HAMEC 9009 Automatic Mod Meter 10MHz - 1.5GHz Wide Deviation	£200
RACAL/DANA 9104 RF Power Meter 1MHz - 1GHz 13mW - 30W	£400
AVO CT160 Valve Tester (Valve Data not included)	£75
N.P. 5006 Signature Analyser	£150
N.P. 5004A Signature Analyser	£100
FERRISBAP RT22 Audio Test Set with ATU	£50
LINDSAY LM1 M2B Audio Analyser	£500
UNADIM GP501 Audio Analyser	£350

NEW EQUIPMENT

FARNELL Isolating Transformers	
GUS500 240v 500VA unused	£50
Isolating Transformers 500VA uncased	£30
BLACK STAR EQUIPMENT (P&P all units £5)	
APOLLO 10-100MHz Counter/Timer Ratio/Pe/Int'l Me Interval etc	£222
APOLLO 100-100MHz (As above with more functions)	£325
METEOR 100 FREQUENCY COUNTER 100MHz	£119
METEOR 500 FREQUENCY COUNTER 600MHz	£145
METEOR 1000 FREQUENCY COUNTER 1GHz	£189
JUPITOR 500 FUNCTION GEN 0.1Hz-500kHz sine/sq/tri	£119
ORION COLOUR BAR GENERATOR Pal/TV/Video	£229
All other Black Star Equipment available	
OSCILLOSCOPE PROBES Switchable x1 x10 (PaP E3)	£12

MEGAPROM device programmer EPROMS, E2PROMS, and FLASH memories from 2k (2716) to 8 Meg (27C80). Runs on IBM PC via the centronics port using standard printer cable. Works on all PC compatibles, laptops, and notebooks. No special port requirements
Uses approved programming algorithms. Very fast program and verify 27C512 (64K Bytes) in 45 seconds.

Full screen editor software supports Bin, Intel Hex, Motorola S and Asc formats
Top quality components used throughout including production ZIF socket
Requires external power supply 18-24v AC or DC @ 250ma (optional extra £46.50)

PICPROG Programs Pic16C54-55-56-57-71-84 Centronics port interface same as Megaprom
Powerful editing software to Read, write & copy Pic devices including data memory in Pic16C84
Unit supplied with IBM software & 12 months parts & labour guarantee
Requires external power 15-20v AC or DC @ 250ma. (optional extra £6.50)

EPRM EMULATOR Works on ANY computer with centronics printer port. Data sent to the printer appears in the target board I.prom socket. Emulates from 1k to 32k Byte (27C 256) roms board switchable. Power supplied from target Rom socket (less than 10ma). Very fast download

Software supplied for IBM PC to convert and send Intel Hex, Motorola S, ASC and Bin files
Board supplied with software and 12 months parts and labour guarantee

PC SCOPE Convert your IBM PC into a Storage Oscilloscope with our A/D converter. Simply plug into the printer port (no power required). Sample rate 10k to 30k per second
Software supplied for Scope and Voltmeter. A/D source to write your own programs.

DEVELOPMENT SOFTWARE
Develop software on your IBM PC for other Microprocessors, Controllers, Pics etc. Software has fully integrated Text Editor, Assembler, Disassembler and Simulator
The Simulator displays all registers along with disassembled code program counter, condition code register. The user can single-step, go with breakpoints, watch memory etc. change any all registers memory locations at any time on the fly

Code can be Saved to disk and or downloaded directly to our EPROM Emulator. All software supplied with sample ASM files and user documentation
Very powerful software as supplied to universities, colleges, PLCs and Industry

Available for the following:-

MCS8051/52/552 series	Software £19.95	MCS8048/49 series	Software £19.95
PIC16C54/5/6/7	Software £29.95	PIC16C71/84	Software £29.95
HD636809	Software £49.95		

LOW COST PIC ICE (In-Circuit Emulator)
Plus into the printer port and runs in conjunction with the PIC development simulator software
Appears to the target system as a normal Pic device including OSC2 and RTC in out. Runs in real time from the IBM PC changes made to file registers reflected on target.
Supplied with Software of your choice Pic54-57 or Pic 71-84

All hardware carries a 12 months parts and labour Guarantee. No VAT payable
Please add £1.50 for Carriage SAE or TLL for further details

JOHN MORRISON DEPT WW
4 Rein Gardens, Tingley
West Yorkshire
Tel (or Fax): 0532 537507

CIRCLE NO. 114 ON REPLY CARD

SEALED LEAD ACID Battery, 6v 80/100 AH made for BT, ex equipment but ok £45 each ref APR47. Ideal electric vehicle etc.

ASTEC SWITCHED MODE PSU Gives +5 @ 3.75A, +12 @ 1.5A, -12 @ 4A 230/110, cased, BM41012. £9.99 ref APR10P3.

TORRODIAL TX 30-0-30 480VA, Perfect for Mosfet amplifiers etc. 120mm dia 55mm thick. £18.99 ref APR19.

MOD WIRE Perfect for repairing PCB's, wire wrap etc. Thin insulated wire on 500m reels. Our price just £9.99 ref APR10P8.

12v MOVING LIGHT Controller. Made by Hella, 6 channels rated at 90watts each. Speed control, cased. £34.99 ref APR35.

ELECTRON FLASH TUBE As used in police car flashing lights etc, full spec supplied. 60-100 flashes a min. £9.99 ref APR10P5.

24v 96WATT Cased power supply. New. £13.99 ref APR14.

STETHOSCOPE Fully functioning stethoscope, ideal for listening to hearts, pipes, motors etc. £6 ref MAR6P6.

OUTDOOR SOLAR PATH LIGHT Captures sunlight during the day and automatically switches on a built in lamp at dusk. Complete with sealed lead acid battery etc. £19.99 ref MAR20P1.

ALARM VERSION Of above unit comes with built in alarm and p/r to deter intruders. £24.99 ref MAR25P4.

CLOCKMAKER KIT Hours of fun making your own clock, complete instructions and everything you need. £7.99 ref MAR8P2.

CARETAKER VOLUMETRIC Alarm, will cover the whole of the ground floor against forced entry. Includes mains power supply and integral battery backup. Powerful internal siren, will take external bell if req'd. Retail £150+, ours? £49.99 ref MAR50P1.

TELEPHONE CABLE White 6 core 100m reel complete with a pack of 100 dips. Ideal 'phone extns etc. £7.99 ref MAR8P3.

VIEWDATA RETURNS £6 made by Tandata, includes 1200.75 modem, k/bd, RGB and comp o/p, printer po... No PSU. £6 MAG6P7

IBM PC CASE AND PSU Ideal base for building your own PC. Ex equipment but OK. £14.00 each REF: MAG14P2

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor Superb value kit just £5.99 REF: MAG6P8

SOLID STATE RELAYS Will switch 25A mains. Input 3.5-26V DC 57x43x21mm with terminal screws £3.99 REF: MAG4P10

300DPI A4 DTP MONITOR Brand new, TTL/ECL inputs, 15" landscape, 1200x1664 pixel complete with circuit diag to help you interface with your projects. JUST £24.99. REF: MAG25P1

ULTRAMINI BUG MIC 6mmx3.5mm made by AKG, 5-12v electret condenser. Cost £12 ea, Our? four for £9.99 REF: MAG10P2

RGB/CGA/EGA/TTL COLOUR MONITORS 12" in good condition. Back anodised metal case £99 each REF: MAG99P1

GX4000 GAMES MACHINES returns so ok for spares or repair £9 each (no games) REF: MAG99P1

64 COMPUTERS Returns, so ok for spares etc £9 ref MAG99P2

FUSELAGE LIGHTS 3 foot by 4" panel 1/8" thick with 3 panels that glow green when a voltage is applied. Good for night lights, front panels, signs, disco etc. 50-100v per step. £25 ref MAG25P2

ANSWER PHONES Returns with 2 faults, we give you the bits for 1 fault, you have to find the other yourself. BT Response 200's £18 ea REF: MAG18P1. PSU £5 ref MAG5P12

SWITCHED MODE PSU ex equip, 60w +5v @5A -5v @.5A, +12v @2A, -12v @.5A 120/220v cased 245x88x55mm IEC input socket £6.99 REF: MAG7P1

PLUG IN PSU 9V 200mA DC £2.99 each REF: MAG3P9

PLUG IN ACORN PSU 19v AC 14w. £2.99 REF: MAG3P10

POWER SUPPLY fully cased with mains and o/p leads 17v DC 900mA output. Bargain price £5.99 ref: MAG6P9

ACORN ARCHIMEDES PSU +5v @ 4.4A on/off sw uncased, selectable mains input, 145x100x45mm £7 REF: MAG7P2

GEKER COUNTER KIT Low cost professional thin tube, complete with PCB and components. £29 REF: MAG29P1

SINCLAIR C5 13" wheels complete with tube, tyre and cycle style bearing £6 ea REF: MAG6P10

AA NICAD PACK encapsulated pack of 8 AA nicad batteries (tagged) ex equip, 55x32x32mm £3 a pack REF: MAG3P11

13.8V 1.9A psu cased with leads. Just £9.99 REF: MAG10P3

360K 5.25 brand new half height floppy drives IBM compatible industry standard. Just £6.99 REF: MAG7P3

PPC MODEM CARDS. These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud dial up unit complete with leads. Clearance price is £5 REF: MAG5P1

INFRA RED REMOTE CONTROLLERS Originally made for hi spec satellite equipment but perfect for all sorts of remote control projects. Our clearance price is just £2 REF: MAG2

TOWERS INTERNATIONAL TRANSISTOR GUIDE. A very useful book for finding equivalent transistors, leadouts, specs etc. £20 REF: MAG20P1

SINCLAIR C5 MOTORS We have a few left without gearboxes. These are 12v DC 3,300 rpm 6"x4", 1/4" OP shaft. £25 REF: MAG25

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the above motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

VIDEOSENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £15 REF: MAG15 12v psu is £5 extra REF: MAG5P2

***FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

LOW COST WALKIE TALKIES Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: MAG 8P1 2 x PP3 req'd.

***MINATURE RADIO TRANSCIEVERS** A pair of walkie talkies with a range of up to 2 kilometres in open country. Units measure 22x52x155mm. Complete with cases and earpieces. 2xPP3 req'd £30.00 pair REF: MAG30.

COMPOSITE VIDEO KIT. Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: MAG8P2.

LQ3600 PRINTER ASSEMBLIES Made by Amstrad they are entire mechanical printer assemblies including printhead, stepper motors etc etc In fact everything bar the case and electronics, a good stripper! £5 REF: MAG5P3 or 2 for £8 REF: MAG8P3

NEW BULL ELECTRICAL STORE WOLVERHAMPTON BRANCH

NOW OPEN AT 55A WORCESTER
ST TEL 0902 22039

100MHZ OSCILLOSCOPES now in stock, 12x10cm screen, delayed sweep, 1Mohm/25pf inputs, modes-ch1, ch2, add, chop, alt, dual. 460 x 305 x 200mm, 17kgs, £267+Vat includes insurance and carriage.

INFRARED LASER NIGHT SCOPES
Second generation image intensifier complete with hand grip attachment with built in laser lamp for zero light conditions. Supplied with Pentax 42mm camera mount, 1.6kg, uses 1xPP3, 3xAA's (all supplied) £245+Vat

NEW HIGH POWER LASERS
15mW, Helium neon, 3 switchable wave lengths .63um, 1.15um, 3.39um (2 of them are infrared) 500:1 polarizer built in so good for holography. Supplied complete with mains power supply. 790x65mm. Use with EXTREME CAUTION AND UNDER QUALIFIED GUIDANCE. £349+Vat.

'PC PAL' VGA TO TV CONVERTER
Just plug in and it converts your colour television into a basic VGA screen, perfect for laptops, saves lugging monitors about or just as a cheap upgrade. Intro price £49.99 +Vat.

AMSTRAD 1512DD
1512 BASE UNIT AND KEYBOARD AND TWO 5.25" 360K DRIVES. ALL YOU NEED IS A MONITOR AND POWER SUPPLY WAS £59.00
NOW ONLY £39.00
REF: MAG39

3FT X 1FT 10WATT SOLAR PANELS
14.5v/700mA
NOW AVAILABLE BY MAIL ORDER
£33.95

(PLUS £2.00 SPECIAL PACKAGING CHARGE)
TOP QUALITY AMORPHOUS SILICON CELLS HAVE ALMOST A TIMELESS LIFESPAN WITH AN INFINITE NUMBER OF POSSIBLE APPLICATIONS, SOME OF WHICH MAY BE CAR BATTERY CHARGING, FOR USE ON BOATS OR CARAVANS, OR ANY WHERE A PORTABLE 12V SUPPLY IS REQUIRED. REF: MAG34

££££££££ BUY SURPLUS STOCK ££££££££
TURN YOUR SURPLUS STOCK INTO CASH.
IMMEDIATE SETTLEMENT. WE WILL ALSO QUOTE FOR COMPLETE FACTORY CLEARANCE.

1994 CATALOGUE.
PLEASE SEND 45P, A4 SIZED SAE FOR YOUR FREE COPY.
MINIMUM GOODS ORDER IS 50 TRADE ORDERS FROM GOVERNMENT, SCHOOLS, UNIVERSITIES, & LOCAL AUTHORITIES WELCOME. ALL GOODS SUPPLIED SUBJECT TO OUR CONDITIONS OF SALE AND UNLESS OTHERWISE STATED GUARANTEED FOR 30 DAYS. RIGHTS RESERVED TO CHANGE PRICES & SPECIFICATIONS WITHOUT PRIOR NOTICE. ORDERS SUBJECT TO STOCK. QUOTATIONS WILLINGLY GIVEN FOR QUANTITIES HIGHER THAN THOSE STATED.

*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

BULL ELECTRICAL
250 PORTLAND ROAD HOVE SUSSEX
BN3 5QT
MAIL ORDER TERMS: CASH PO OR CHEQUE
WITH ORDER PLUS £3.00 POST PLUS VAT.
PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY
TELEPHONE ORDERS WELCOME
TEL: 0273 203500
FAX: 0273 323077

SPEAKER WIRE Brown 2 core 100 foot hank £2 REF: MAG2P1

LED PACK of 100 standard red 5m leds £5 REF: MAG5P4

UNIVERSAL PC POWER SUPPLY complete with flylead switch, fan etc. Two types available 150w at £15 REF: MAG15P (23x23x23mm) and 200w at £20 REF: MAG20P3 (23x23x23mm)

***FM TRANSMITTER** housed in a standard working 13A adaptor! the bug runs directly off the mains so lasts forever! why pay £700? or price is £26 REF: MAG26 T transmits to any FM radio.

***FM BUG KIT** New design with PCB embedded coil for extra stability. Works to any FM radio. 9v battery req'd. £5 REF: MAG5P5

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

TALKING COINBOX STRIPPER originally made to retail at £79 each, these units are designed to convert and ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? Price is just £3 REF: MAG3P1

100 WATT MOSFET PAIR same spec as 2SK343 and 2SJ413 (8A, 140v, 100w) 1 N channel, 1 P channel, £3 a pair REF: MAG3P2

TOP QUALITY SPEAKERS Made for Hi Fi televisions these are 10 watt 4R Jap made 4" round with large shielded magnets. Good quality. £2 each REF: MAG2P4 or 4 for £6 REF: MAG6P2

TWEETERS 2" diameter good quality tweeter 140R (ok with the above speaker) 2 for £2 REF: MAG2P5 or 4 for £3 REF: MAG3P4

AT KEYBOARDS Made by Apricot these quality keyboards need just a small mod to run on any AT, they work perfectly but you will have to put up with 1 or 2 foreign keycaps! Price £6 REF: MAG6P3

PC CASES Again mixed types so you take a chance next one off the pile! £12 REF: MAG12 or two the same for £20 REF: MAG20P4

COMMODORE MICRODRIVE SYSTEM mini storage device for C64's 4 times faster than disc drives, 10 times faster than tapes. Complete unit just £12 REF: MAG12P1

SCHOOL STRIPPERS We have quite a few of the above units which are 'returns' as they are quite comprehensive units they could be used for other projects etc. Let us know how many you need at just 50p a unit (minimum 10)

HEADPHONES Ex Virgin Atlantic 8 pairs for £2 REF: MAG2P8

PROXIMITY SENSORS These are small PCB's with what look like a source and sensor LED on one end and lots of components on the rest of the PCB. Complete with flyleads. Pack of 5 £3 REF: MAG: 3P5 or 20 for £8 REF: MAG8P4

SNOOPERS EAR? Original made to clip over the earpiece of telephone to amplify the sound it also works quite well on the cable running along the wall! Price is £5 REF: MAG5P7

DOS PACKS Microsoft version 3.3 or higher complete with all manuals or price just £5 REF: MAG5P8 Worth it just for the very comprehensive manual! 5.25" only.

DOS PACK Microsoft version 5 Original software but no manuals hence only £3 REF: MAG3P8 5.25" only.

CTM644 COLOUR MONITOR Made to work with the CPC464 home computer. Standard RGB input so will work with other machines. Refurbished £59.00 REF: MAG59

PIR DETECTOR Made by famous UK alarm manufacturer these are hi spec, long range internal units. 12v operation. Slight marks on case and unboxed (although brand new) £8 REF: MAG8P5

WINDUP SOLAR POWERED RADIO AM/FM radio complete with hand charger and solar panel! £14 REF: MAG14P1

COMMODORE 64 TAPE DRIVES Customer returns at £4 REF: MAG4P9 Fully tested units are £12 REF: MAG12P5.

MAINS CABLES These are 2 core standard black 2 metre mains cables fitted with a 13A plug on one end, cable the other. Ideal for projects, low cost manufacturing etc. Pack of 10 for £3 REF: MAG3P8 Pack of 100 £20 REF: MAG20P5

MICROWAVE TIMER Electronic timer with relay output suitable to make enlarger timer etc £4 REF: MAG4P4

MOBILE CAR PHONE £6.99 Well almost! complete in car phone excluding the box of electronics normally hidden under seat. Can be made to illuminate with 12v also has built in light sensor so display only illuminates when dark. Totally convincing! REF: MAG6P6

ALARM BEACONS Zenon strobe made to mount on an external bell box but could be used for caravans etc. 12v operation. Just connect up and it flashes regularly! £5 REF: MAG5P11

FIRE ALARM CONTROL PANEL High quality metal cased alarm panel 350x165x50mm. With key. Comes with electronics but no information. sale price 7.99 REF: MAG7P9

REMOTE CONTROL PCB These are receiver boards for garage door opening systems. Another use? £4 ea REF: MAG4P5

6"x12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just £5.99 ea REF: MAG6P12

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1


LOPTX Line output transformers believed to be for hi res colour monitors but useful for getting high voltages from low ones! £2 each REF: MAG2P12 bumper pack of 10 for £12 REF: MAG12P3.

**BOTH SHOPS OPEN 9-5.30
SIX DAYS A WEEK**

PORTABLE RADIATION DETECTOR
£49.99
A Hand held personal Gamma and X Ray detector. This unit contains two Geiger Tubes, has a 4 digit LCD display with a Piezo speaker, giving an audio visual indication. The unit detects high energy electromagnetic quanta with an energy from 30K eV to over 1.2M eV and a measuring range of 5-9999 UR/h or 10-99990 Nr/h. Supplied complete with handbook.
REF: MAG50

CIRCLE NO. 115 ON REPLY CARD

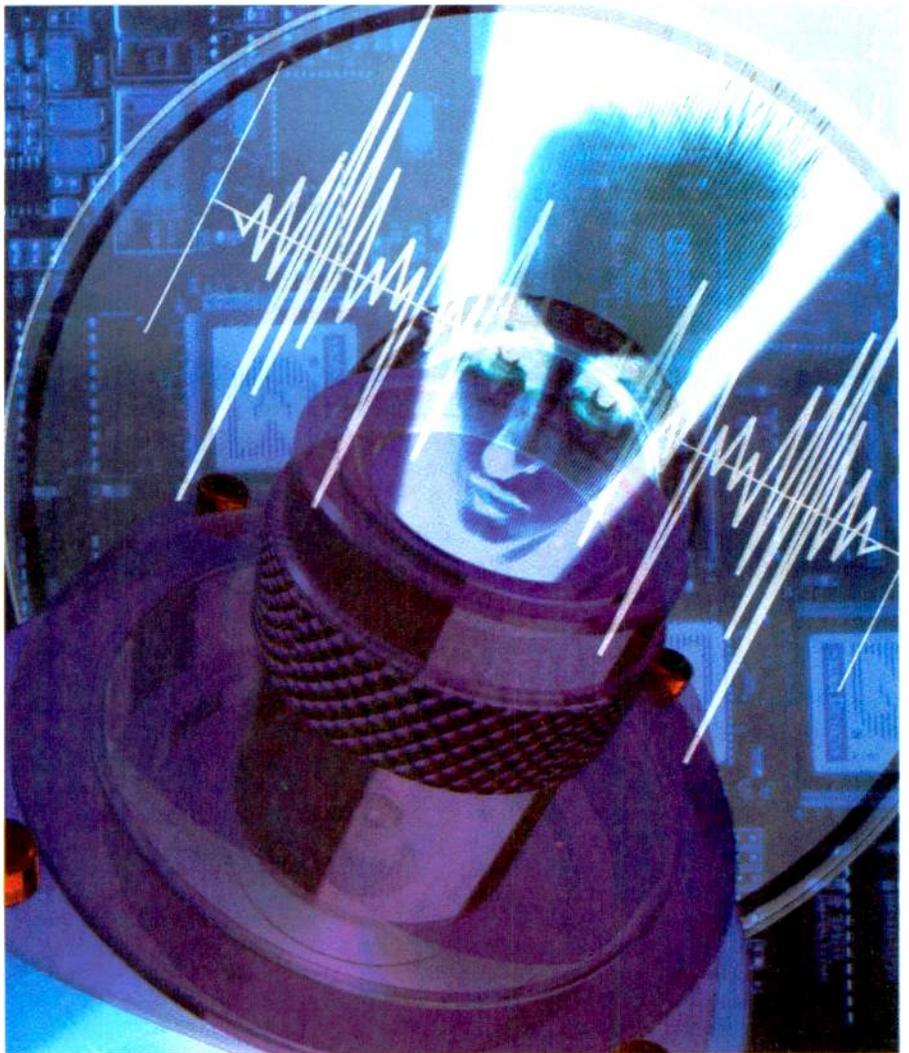One source predicts that video CD sales will exceed 16 million by 1998. With films on CD about to hit the shops, George Cole looks at events that led to current video-compression standards.



VIDEO compact disc

This autumn, Panasonic is launching a home audio system with a difference. Called *SC-VC10*, this system will include a new type of compact-disc machine with the ability to play conventional audio *and* video CDs – which store over an hour of digital full-motion video, or *fmv*.

Video CD is a cross-platform system whose software can be played on domestic players, such as Compact Disc Interactive equipment, computer games consoles such as Commodore's *Amiga CD32*, and desktop PCs. Consumer electronics companies hope video CD will boost sales of compact-disc players, while computer companies think that the ability to play full-length movies on your PC or games machine will prove appealing.

Video CD is not the first CD-based format to offer pictures or even video. The compact-disc Digital Audio Red Book standard, set by Sony and Philips in the late 1970s, **Fig. 1**, makes provision for a CD plus graphics, CD+G, system.

Around 97% of the data stored on an audio CD is for music and error correction. Sub-codes containing control information take up the remaining 3%. These sub-codes are called P, Q, R, S, T, U, V and W. The first two, P and Q, are used for features such as track identification and track time, while R-W are set aside for graphics.

There is space for up to 1500 graphic ele-

ments, each with a display size of 288 by 192 pixels. The graphics look like a teletext picture and can display up to 16 colours from a palette of 4096. It takes around 2.5-10 seconds to draw each display, which can also be scrolled off the screen.

Ordinary CD decks ignore sub-codes R to W, but players equipped with a CD+G decoder can display them on any television screen. It was thought that many record companies would make use of the graphics to display song lyrics and artist information, but few bothered.

JVC launched CD+G decoders in the US, Germany and Japan, where they were used for karaoke titles. But few CDs featured graphics.

WEA launched several CD+G discs, some of which can still be found in music shops. A few multimedia players however, among them CD-i decks, also include CD+G decoders.

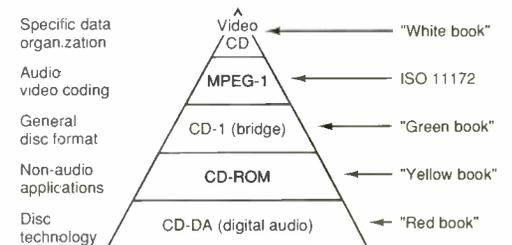


Fig. 1. Video CD technology pyramid.

In 1985, Sony and Philips launched the cd-rom, or Yellow Book standard, which enables a CD to store over 600M-byte of data. This data may be in the form of sound, text or pictures. Although a cd-rom can store over 250,000 pages of text, it can only hold a small amount of uncompressed digital video.

A video frame uses around 800K-byte of data and tv systems like PAL display 25 frames a second to create the illusion of motion. Simple mathematics shows that a CD could only store less than a minute of digital video. Another problem is that CD transfer rate is only 1.5M-bit/s, which is far too slow for displaying 25 frames a second.

In 1987, Philips announced Compact Disc Video, CDV, which stored analogue video and 16-bit pcm audio on the same disc. A 12cm CDV disc stored six minutes of video and sound, plus a further 20 minutes of audio. Philips hoped that CDV would appeal to music buyers, but the format flopped.

Practical CD video – almost

During the same year, researchers from RCA's David Sarnoff Laboratories in New Jersey astounded the world by displaying a CD which held over an hour of digital full-motion video. Called DVI, for Digital Video Interactive, the system which made it possible used powerful algorithms to reduce a 800K-byte frame to just 5K-byte. DVI works by comparing each frame and only coding the differences. It also analyses a frame for repetitive or redundant information. This might be large areas of the same colour, such as sea or sky.

DVI was a fine technical achievement, but the complex number crunching needed meant that it took a super computer over a day to compress an hour of video. What is more, playback DVI boards designed for desktop PCs initially cost thousands of dollars.

Moving pictures through the window

In 1988, the CD-i Green Book standard was set. Originally, the CD-i specification included motion video, which played video running at around 15 frames per second in a small

The other video CD

At the 1993 Midem music festival, Monmouth-based Nimbus Technology and Engineering created a stir by showing two compact discs holding over an hour of MPEG-1 video.

Playable on many conventional CD decks, the first of these discs held 79 minutes of video. The second held 135 minutes of full-motion video. Nimbus said that this too could be played on ordinary CD decks, albeit with a small adjustment to the laser system.

Both long playing CDs were made possible by a new mastering system developed by NTE and called video CD. The company planned to launch add-on MPEG-1 decoders priced at around £100. These would include a CL-450 MPEG-1 chip set designed by C-Cube Microsystems and link directly into the digital output socket of a CD player.

NTE said that roughly one third of the world's 120 million CD decks had a digital output connection and that such a socket was becoming a

window on the screen. At the time Philips said that it was not practical to include full-motion video.

A development in May of 1988 forced Philips to change its mind. Jointly, the International Standards Organisation and International Electrotechnical Commission set up the Moving Picture Experts Group. MPEG, to establish a world standard for digital video. The group included representatives from computer, consumer electronics and telecommunications companies.

In 1989, Philips announced that CD-i would include digital video based on the MPEG standard and hoped to launch the first CD-i players with full-motion video capability. But the first MPEG standard, MPEG-1, was not set until November 1992 – a year after CD-i was launched in North America. As a result, the first decks had space for a plug-in full-motion video cartridge to hold the MPEG chipset.

In January 1993, Nimbus Technology and Engineering demonstrated a system capable of storing over an hour of MPEG-1 video on a CD and offered it to music, film and video companies; there is more on this in the inset panel.

Born from karaoke

On 29 June 1993 however, JVC, Philips, Sony and Matsushita – owner of Panasonic, Technics and JVC – announced the video CD format. It was covered by a new standard

standard feature on most new machines. By plugging the decoder into their tv set, users could watch video movies on their audio CD player.

Although the development caused excitement worldwide, Philips stemmed the fervour by claiming that Nimbus's long-playing discs broke the CD standard and would not play on all audio decks.

Nimbus decided to press ahead with its 79-minute disc – which was within the Red Book standard. The company offered an MPEG-1 compression service to film and video companies, charging \$100 per minute of video material. It also sold a couple of its new mastering systems to China.

But the announcement of the 'new' video CD shocked NTE. Although it claimed that many Hollywood film companies preferred its system, NTE's alternative became significantly less attractive. Earlier this year, NTE was still demonstrating its system to Hollywood, but there is no sign of any software company backing it.

known as the White Book. Video CD is based on another standard known as Karaoke CD, which is a sub-set of CD-i. Karaoke CD was developed by Philips and JVC.

Video CD is designed for linear video programmes, such as music videos, and stores up to 74 minutes of MPEG-1 video and audio on a CD. There are two specifications for PAL and NTSC systems, shown in the table, although all video CDs will play on all video CD decks.

Initially, the announcement stated that video CDs would play on a variety of player formats. These included CD-i decks with an add-on full-motion-video cartridge, dedicated video CD players, PCs with a MPEG card and cd-rom drive and modified audio CD decks with an add-on video CD decoder.

News that modified audio CD decks could be used caused confusion. It suggested that owners of existing CD decks could upgrade to video CD with an add-on decoder. But this is not the case.

Video CD uses a CD-ROM-XA 'bridge disc', which includes a header telling the player that it contains computer data. If you try playing an XA disc in most music CD decks, the audio output is muted to protect the speakers from damaging white noise. Philips has since confirmed that it will not market add-on decoder boxes.

In August 1993, the basic specifications for video CD were released, with news of two optional features. One of these is for display-

Video CD software specifications

Parameter	Video system	
	NTSC	PAL
Coding Method	MPEG-1	MPEG-1
Resolution (pixel)	352h x 240v	352h x 288v
Frame rate (Hz)	29.97	25
Pel aspect ratio	1.0950	0.9157
Bit rate (bit/sec)	1151.929k	1151.929k
	Audio	
Coding method	MPEG - 1	LAYER-II
Sampling rate (Hz)	44.1k	
Bit rate (bit/sec)	224k	
Emphasis	ON or OFF	
Mode	Dual channel or stereo	

ing still pictures, which can be in standard resolution, at 353 by 288 pixels, or high resolution with 704 by 480 pixels.

It is also possible to put control codes on video CDs for branching interactive programmes used for educational or training programmes and the like. In January 1994, the first video CD standard, known as version 1.1, was set.

Better than VHS

Video CD offers 'better than VHS' picture quality and titles can also include widescreen pictures and Dolby Surround sound. A number of electronics companies have shown video CD players, including Panasonic, Sony, Goldstar, Samsung and Fisher. These machines will run video and audio CDs, but not CD-i or cd-rom titles. They will also offer video-recorder type features such as still frame and picture search.

Home multimedia formats CD-i and 3DO also support video CD and Commodore has launched a £200 add-on decoder for its Amiga CD32 system. Atari is promising the same for its Jaguar games system, while US company ReelMagic has launched a MPEG-1 video card for PCs, priced £400. Video CD software supporters include Polygram, BMG, Warner, Paramount and MGM/UA.

But video CD has not been without its problems. One of these is the confusion caused by Philips, which has launched a number of movies on CD. The films are part of a deal with Paramount, announced in autumn 1993, which involves the launch of 50 Paramount movies on CD-i over the next two years. However, the first movies to appear were not

video CD discs, but dedicated CD-i titles.

Philips says the Paramount deal was struck before the video CD announcement and there was no time to convert its video encoders. Philips has since switched its mastering system over to White Book encoding. This means that there are now two types of CD-i movies: those which only play on CD-i decks and those which play on CD-i and video CD machines.

Another problem has been caused by the difference between the CD-i and video CD standards. The Green Book standard defines a picture 384 pixels wide, compared with 352 pixels for the White Book. The result is that when a video CD is played in a CD-i deck, there are thin black bands at the sides of the picture.

Initial video CD titles also looked slightly distorted in CD-i players because of the difference between the 15MHz clock speed of CD-i and video CD, which was set at 13.5MHz. Philips has since adapted the CD-i full-motion video cartridge which now automatically changes the clock speed, depending on the type of disc being played.

Commercial constraints

Other problems have been commercial. Different frame rates, line numbers and colour encoding systems used for PAL and NTSC television formats mean that VHS tapes and laser discs bought in the US will not play in most PAL machines.

Film companies use these differences to negotiate separate deals in PAL and NTSC territories and stagger release dates. Most movies appear on video in the US months

MPEG video compression

There are several MPEG standards under development. MPEG-1, now known as ISO 11172, is optimised for storage media, such as CD. The idea was to develop a digital video system whose data rate was below the CD's 1.5M-bit/s ceiling.

The data rate of MPEG-1 video is approximately 1.2M-bit/s, with 224K-bit/s allocated for the audio. MPEG-1 video is also being used for asymmetrical digital subscriber loop, ADSL, systems used by telephone video-on-demand services. This enables full motion video to be sent down narrow-band copper telephone wires into homes. MPEG-1 picture quality is claimed to be better than VHS, and in some cases can approach Super VHS.

The MPEG-2 standard is designed for data rates of 2-15M-bit/s and aimed at digital broadcast services,

including HDTV. A new generation of cd-roms will also use MPEG-2 to offer even better picture quality. MPEG-3 was originally designed for HDTV, but its work is now part of MPEG-2. MPEG-4 will be aimed at low bit-rate transmission systems, such as video phones, where the data rate is in tens of kilobits/sec.

Note that MPEG is concerned with the organisation and synchronisation of the output digital bit stream. It does not define the encoding algorithms used to compress the audio and video. This leaves companies free to develop their own algorithms and opens the way for improved compression. It also explains why some MPEG-1 pictures look much better than others.

Additionally, MPEG does not define what scrambling and encryption systems companies may wish to use, so there are likely to be many different conditional access systems on the market.

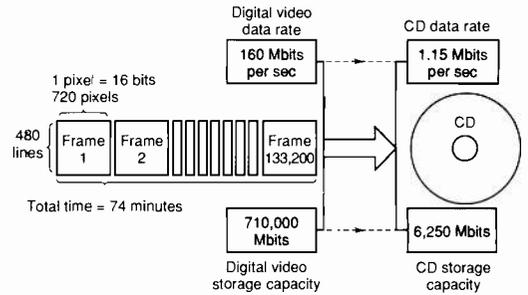


Fig. 2. The video encoding challenge – storing a 710G-bit film on a half-gigabit CD.

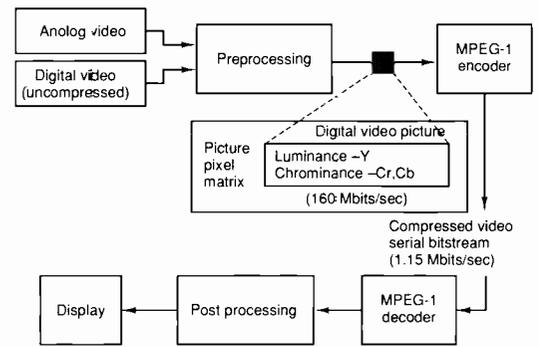


Fig. 3. Video encoding/decoding scheme for the MPEG-1 standard.

before they reach Europe. But video CD breaks this barrier and discs can be bought and used anywhere.

The only caveat to this is that discs designed for NTSC display a letterbox picture when played in a PAL machine. This is because PAL pictures have 288 lines, compared with 240 lines for NTSC; in PAL, these lines are repeated sequentially to produce a full display. As a result of the line difference, PAL pictures look stretched on an NTSC video CD player.

In practice, the letterbox effect is not too obtrusive and most people find it acceptable – especially if it means they can watch a movie long before its UK release date.

Film companies have insisted on separate mastering for PAL and NTSC titles. They want their stars to 'always look their best'. Earlier this year, Paramount began inserting blocking codes into its titles to stop NTSC discs being played in PAL machines. A compromise has now been reached. European viewers playing an NTSC video CD see a warning at the start of the disc stating that the title is designed for NTSC.

Parasonic's first UK video CD system, the SC-VC10, will cost around £800. Most movies on video CD will be on two or three discs, although carousel players, which store several or more discs are promised. Also promised are portable video CD decks with liquid-crystal video screens. Next year, Philips is expected to announce a new CD standard offering longer playing time and better picture quality.

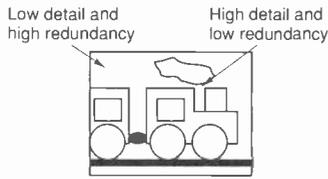


Fig. 4. In video compression, redundancy in individual pictures is exploited.

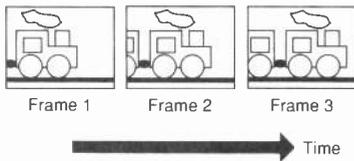


Fig. 5. There is also redundancy in sequences of pictures that can be removed to save memory.

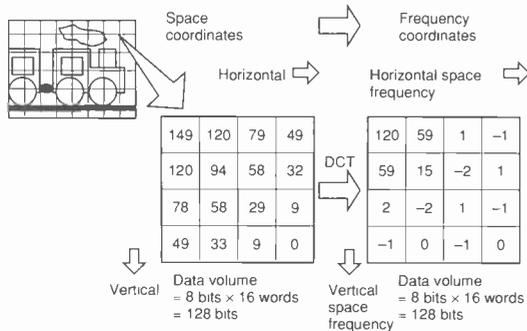


Fig. 6. The process used to sort out redundant data is known as discrete cosine transform, or dct.

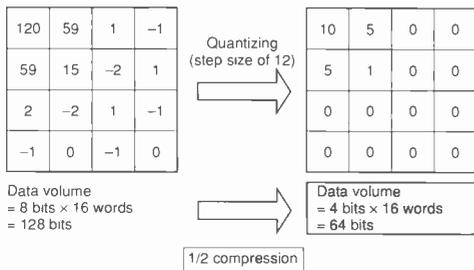


Fig. 7. Here, quantizing the dct components involves scaling down by a factor of 12.

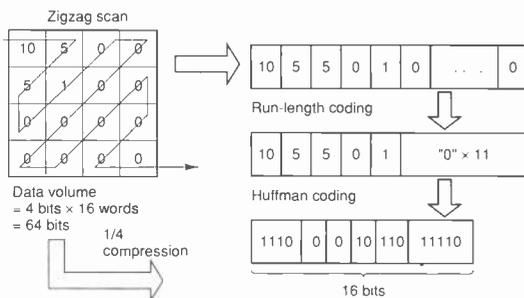


Fig. 8. Variable-length coding involves scanning the pattern in a zig-zag to produce a bit stream.



Panasonic predicts that by 1998, world sales of video CD players could be well over 16 million

Video companies find video CD attractive because it costs around \$1 to press a CD – compared with \$3 for duplicating a tape. Video CDs will cost around £16 for a single disc and £20 for a double-disc set. Panasonic says consumers will like video CD because the discs are non-wearing and offer fast access.

Panasonic predicts that total worldwide sales of video CD players will reach 300,000 this year, rising to 16.4 million by 1998. However, the company does not see video CD replacing the domestic video recorder, which offers longer playing times, masses of cheap software – and recordability. Indeed, Panasonic is a supporter of a new home digital vcr format called dvr. However, the company says that video CD should make audio-only CD players obsolete by the end of the decade.

MPEG technology breakdown

Storing over an hour of digital video on a CD is difficult, as Fig. 2 implies.

Figure 3 shows the general encoding/decoding scheme. The process starts with a high-quality analogue or video source which is pre-processed to obtain a Y/C video signal. This is fed to the encoder where it is compressed then multiplexed with the audio stream.

Also added to the data stream are graphics, such as logos and copyright messages, and control codes for chapter selection, etc. In the player, the MPEG-1 decoder decompresses the audio and video. Post processing is used to produce a display output.

Currently, MPEG-1 encoders cost between £50,000 and £100,000, but prices are expected to fall rapidly. Encoding costs around £90 per minute, so a 90-minute movie can be mastered for around £8000 – which is relatively cheap. The video CD mastering process is shown in Fig. 15.

MPEG exploits redundancy within a frame and between each frame, Figs 4, 5. There are large areas of repetitive detail in the locomotive image. In addition, the short time interval between each frame of 1/25s means that there

is little change between successive frames.

The process used to sort out the redundant data is known as discrete cosine transform, dct. First, an eight-by-eight segment of pixels, called a block, is analysed and each pixel is assigned a number which represents its luminance value, Fig. 6. Discrete cosine transform is used to produce a set of numbers representing the spatial frequency. This is the speed at which the luminance value changes between adjacent pixels. The new set of numbers are known as output coefficients.

Within the dct matrix, the top left number, in this case 120, is most important. It represents the average luminance value for the area being analysed. The 120 looks high for the average value because in this example the values have been scaled down by a factor of 8 rather than 16, for simplicity's sake.

The small values of 1 and -1 indicate that there are no fast changes in brightness from pixel to pixel. Note that at this stage we have still not reduced the amount of data. It is still 128 bits, comprising 8 bits by 16 words.

During compression, the first stage involves the quantization of the dct values, Fig. 7. In this example, the numbers are scaled down by a factor of 12. This means we now need four, rather than eight, bits to code each word, halving the amount of data.

Variable length coding is used in the next stage, Fig. 8. Here, the output coefficients are scanned in a zig-zag fashion to produce a string of bits. Zig-zagging is used because the numbers furthest away from the average value are more likely to have the lowest luminance value. Visually, this makes them least important.

A long string of zeros is usually produced by this process. The next step is to use Huffman coding. The shortest length code is assigned to the most frequent data value and the longest length code for the least frequent data value.

A long string of zeros can also be represented by a small number of bits. This reduces the data by a factor of four. These processes are also applied to the colour signal data.

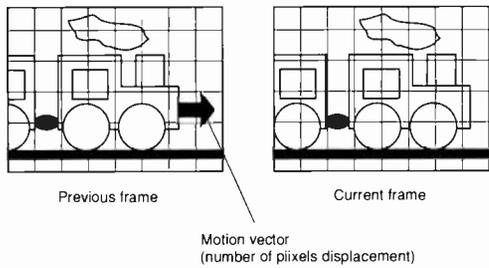


Fig. 9. Further compression is possible by analysing motion over successive frames.


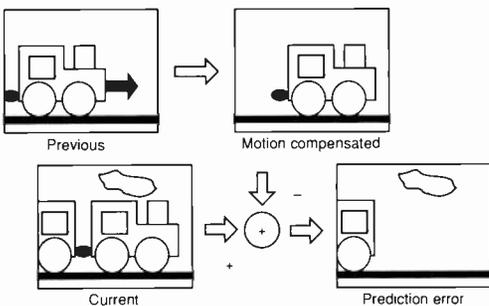


Fig. 10. The image of a moving train need only be stored once, together with a motion vector.

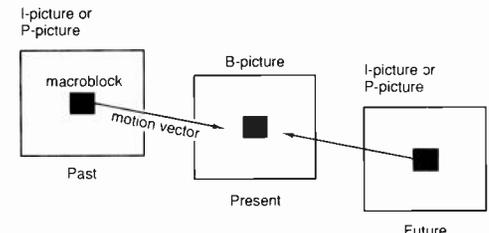

Encoding method:
Bidirectional interpolation

Fig. 11. Encoding a bidirectional picture involves interpolating from a non-compensated I reference frame and a predictive P frame.

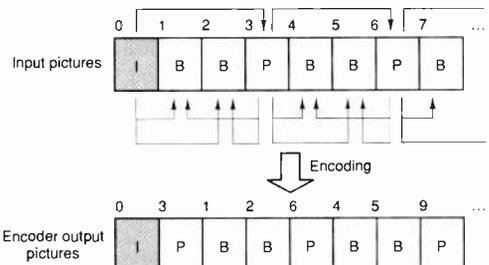


Fig. 12. Video CD picture organisation. Since B frames take longest to encode, output frames are shuffled by the encoder.

Another compression process, namely motion detection and compensation, analyses differences between frames. Figure 9 shows a train moving across a screen. If detail of the engine has already been encoded in the previous frame the only further information needed is the number of pixels moved in the current frame. This is known as the displacement value or motion vector, and requires far less coding.

Fig. 13. Video CD decoding elements. I frames are sent via the top route while B and P frames travel the lower path.



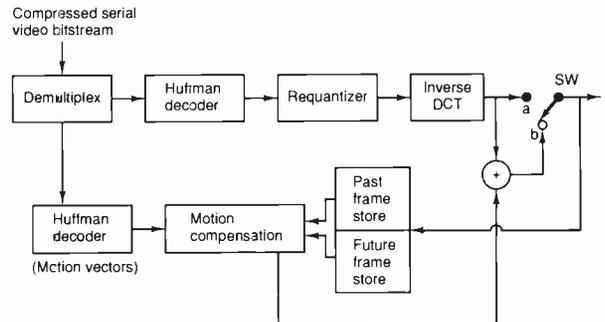


Fig. 14. In the player, a switch routes data depending on whether the disc is audio or video.

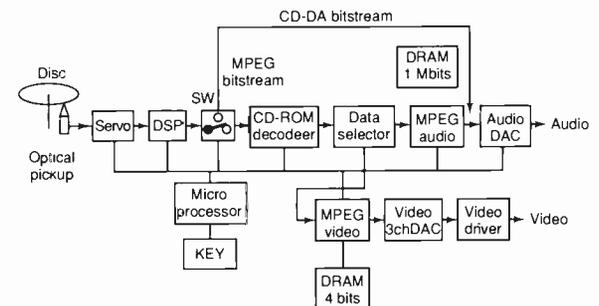

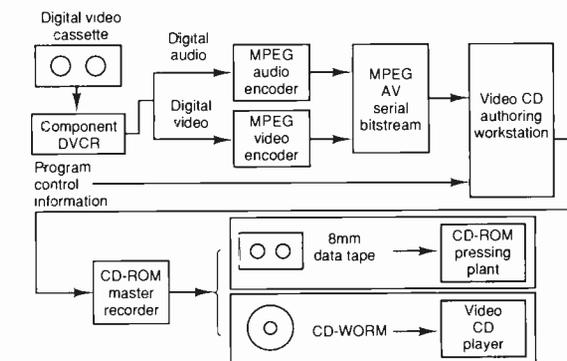Video CD mastering combines encoding and decoding technologies.



Motion vectors are produced by analysing the frames before and after the current frame. This works by storing the frames in memory and calculating the displacement values.

The current frame may also contain new information – part of the first carriage in this case – which is known as the prediction error, Fig. 10. This is coded using dct and added to the motion compensated frame.

There are three types of frame involved in the compression process, Fig. 11. The I frame is the reference frame and no motion compensation is applied to this. The P or predictive frames are produced by motion compensated process. Bi-directional or B frames are produced by an interpolation method which uses the motion vectors from an I and P frame or two P frames.

This process combines blocks of data known as macroblocks from both the I and P frames to create an average value. Macroblocks comprise four luminance and two colour blocks.

Figure 12 shows how the frames are organ-

ised by the encoder. The B frames produce the largest data compression, but take the longest to encode. For this reason, output frames are shuffled by the encoder to increase speed.

Video CD uses an MPEG audio format known as Layer-II. This has a bit rate of 224k-bit/s. It gives stereo or dual channel sound and represents a compression ratio of 6.3 when compared with CD audio.

MPEG uses a coding system similar to the Precision Adaptive Sub-band Coding, PASC, process used by the digital compact cassette. Audio is sampled at 44.1kHz, split into 32 frequency sub-bands, and analysed. Frequencies which are hidden or masked are discarded to reduce the amount of data.

Elements of the the video-CD decoder are shown in Fig. 13. I frames are sent via the top route, while B and P frames follow the bottom route. A switch detects each type of frame.

Figure 14 is a block diagram of a video CD player. The switch here detects whether the machine is playing an audio or video CD. ■

DESIGNING FOR NOISE IMMUNITY

Under certain circumstances, it is possible to recover at least an approximation of data that has become corrupted by noise. However recovery techniques should be only used as a last resort.

Lord Rutherford once advised, "If your experiment needs statistics – think of a better one." In this instance the 'better experiment' relies on preventing the noise from corrupting the data in the first place.

Sensor buffering

In most data acquisition systems, the most vulnerable element will be the sensor itself. Sensors often need some form of excitation, or drive. Noise at this node is often transferred to the output, possibly as a multiplicative distortion.

Every inch of extra cable – shielded or not – between your sensor and its processing electronics is a further reduction in signal integrity. One solution is to insert a sensor interface buffer as close to the sensor as physically possible. This interface should produce any sensor drive

In passing from its source to a data acquisition system, a low-level transducer signal inevitably picks up noise. There are ways of recovering signals from noise, as described in last month's issue, but here, Dave Robinson looks at a better alternative – building in noise immunity.

needed, amplify sensor output and convert the information into a robust transmittable form.

Fortunately modern electronics make the design of sensor buffers straightforward. They can be very compact, and can be designed to consume very little power. Fig 1.

Power for sensor buffers

Powering these buffers can be a problem; there are three methods that generally work well:

- battery power
- remote power and dc/dc converters
- local mains with isolated communication links.

Battery power offers many advantages. Each buffer unit can be totally isolated. Noise generation mechanisms such as earth loops are much easier to handle.


Using cmos devices, a small battery with regulation electronics can provide months of trouble free running without maintenance. This is, however also the major disadvantage. Batteries do expire, and at fairly unpredictable times. Two questions need answering—does the buffer enclosure facilitate battery changes and will the system function if one sensor becomes inoperative? Rechargeable batteries, perhaps charged from solar cells, can solve many problems.

If power has to be transferred from the central controller some distance from the sensor buffer, considerable noise can be picked up on the power lines. As zero volts often acts as the signal reference point, noise picked up on this line can prove troublesome.

One excellent solution is to use the transmitted power as input to an isolated output dc-to-dc converter within the sensor buffer unit, Fig 2. In this way, the isolated zero volts of the converter output and system zero volts need not be brought together until the signal is safely back into your central control system.

An alternative, ingenious and very popular method of powering remote sensors is the so called 4-20mA current loop. This forms a

Fig. 1. To ensure that a low-level signal from a remote sensor can be received at a distance with integrity, an excellent solution is to introduce a buffer subsystem as close to the sensor as possible.

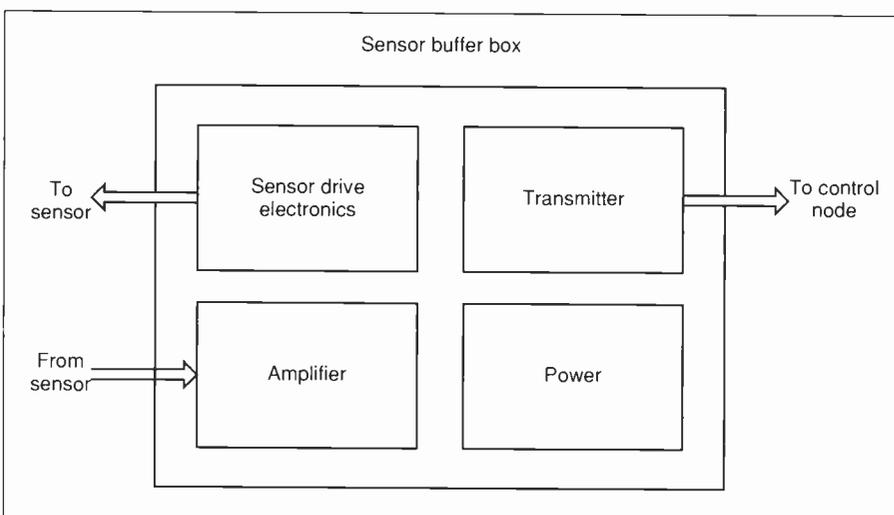

complete two wire power distribution and communication system. Power is provided on the loop by the control unit. The sensor circuitry at the far end essentially modulates the current flowing in the loop, according to the parameter being measured.

Since data is communicated by switching current in the loop between 4 and 20mA, there is always at least 4mA available on the loop for powering the transducer circuitry. This system works extremely well; it is fairly immune to noise pickup and is supported by most of the major manufacturers in the field.

Powering the buffer and the central control node from their own local mains supplies – which may be a fair distance apart – is problematical, **Fig 3**.

In my experience, this configuration has been the cause of a great deal of heartache – mainly caused by the varying earth potentials. Connecting the signal earths of the two systems results in what can be quite large and noisy currents flowing through the earth wire.

The easiest safe method of powering the remote nodes from their local mains is to use completely isolated data transfer between the nodes and the control node. Options here include, telemetry, optical-fibre links and opto-isolator with copper cabling.

Sensor drive signals

Where appropriate, drive signals depend on the type of sensor you are using.

A thermocouple for example, does not need any drive. Platinum resistance thermometers normally require a dc supply, as do a strain gauge bridges.

With dc-excited sensors similar to prts and strain gauges, it is worth considering the advantages to be gained from using an ac excitation signal instead. Frequency-selective amplifiers, lock in amplifiers, phase sensitive detectors and so called box-car integrators are electronic amplifiers designed to produce a dc value. Amplitude of this value is directly proportional to input signal whose frequency and phase are equal to the reference clock provided to the amplifier, **Fig 4**.

Suitable ac-to-dc converters can easily be made from switched-input amplifiers. Exciting the sensor with a known frequency modulates the sensor output signal with the same frequency. Any change in signal level anywhere else in the spectrum is entirely due to noise, and can therefore be ignored – a process that the 'lock-in' amplifier does superbly.

The lock in amplifier is driven from the same oscillator as is driving the sensor. It automatically follows any frequency drift in the excitation generator, allowing a quite crude oscillator to be used. This is better than using a straightforward filter to isolate the signal, as this would require a much more stable frequency standard. Note that the speed of your oscillator should be substantially faster than the maximum rate of change that you are expecting from your signal.

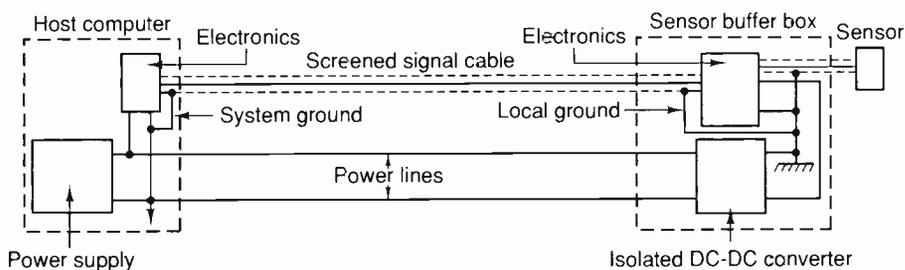


Fig. 2. Powering a sensor buffer from a host can cause grounding problems. One solution is to regenerate clean power supplies using isolated dc-to-dc converters within the sensor buffer unit.

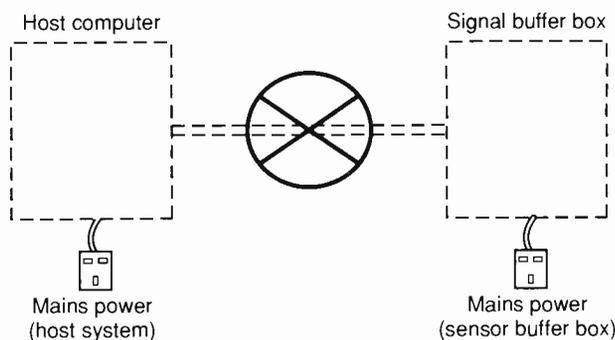


Fig. 3. When the host and remote signal buffer have independent mains-derived power supplies, the two are connected via their earths. If the two are also linked by a signal earth ground loops will inevitably cause problems.

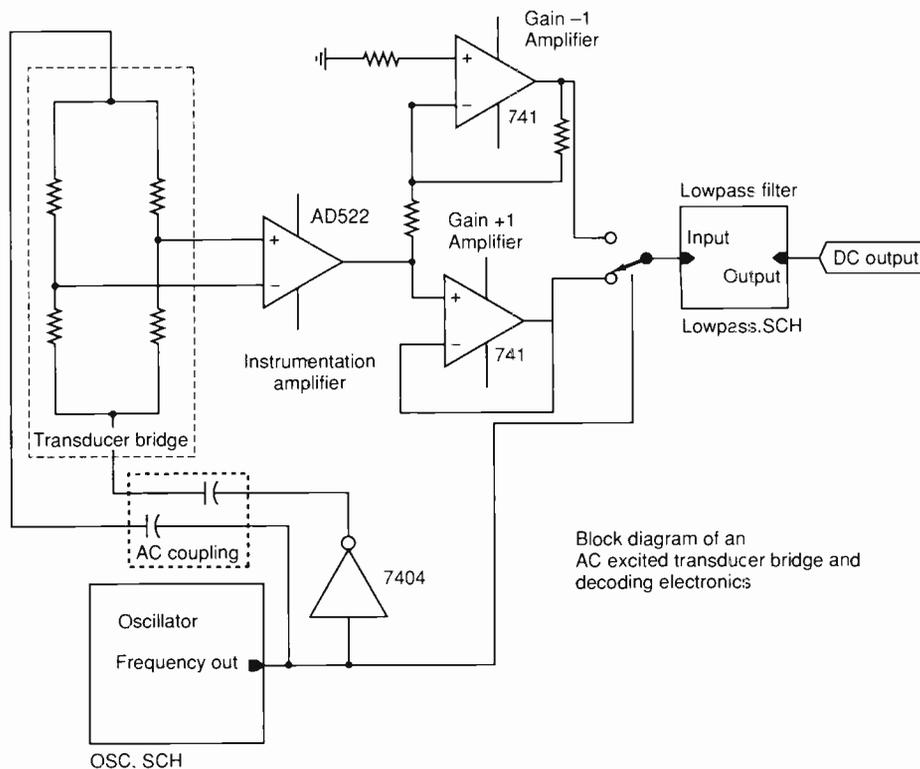


Fig. 4. With certain types of transducer, noise problems can be reduced by exciting the sensor with an ac signal. At the receiving end, a frequency-selective amplifier driven by the exciter clock makes sure that unwanted signals are rejected.

Data protocols

After amplifying and decoding sensor output, the buffer unit has to convert the signal into a format suitable for transfer to the central control node – a crucial task.

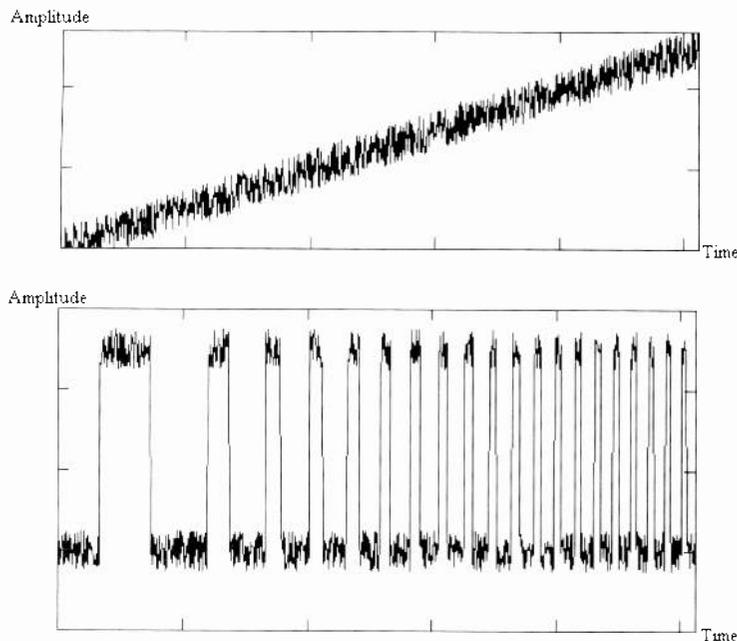


Fig. 5. In a purely analogue system, the ramp's detail is obscured by noise. Converting the clean ramp to frequency-modulated format reduces the effects of noise.

Transducer types

Transducer is a general name for electronic components that interact with the real world. They fall into two key categories, namely input and output transducers.

Output transducers take an electrical signal and convert it to some form of non-electrical output. Examples are loudspeakers, which convert an electric signal into an acoustic one, and solenoids, which convert between electricity and movement. Output transducers are usually called actuators.

Input transducers – the main subject of this article – take some form of non electrical input and produce an electrically measurable parameter change. Input transducers are called sensors. Sensors have been designed to use changes in virtual every conceivable electrical parameter. Although far from exhaustive, the following list outlines some of the more common types.

Change in charge:

Pyroelectric infrared detectors
Microphones

Change in current:

Geiger Müller detector
Photodiode
Photomultiplier
Smoke detectors

Change in voltage:

thermocouple
photodiode

Change in resistance:

strain gauges
thermistors
platinum resistance thermometers
light dependent resistor
position measuring potentiometer

Change in inductance:

position LVDT
metal detector

Change in capacitance:

accelerometers
microphones

Sensors fall into two categories. One is direct output sensors, which produce a measurable electrical effect representing the parameter being measured. A thermocouple is a simple example of this type of sensor. It produces an output voltage which is a direct function of the temperature difference between the so called hot and cold junctions.

The other category of sensor requires some form of drive or stimulus which is modified or modulated by the parameter being measured. Resistive sensors usually fall into this category. In almost all cases, the signals provided by the sensors are very low level, and need to be preprocessed prior to being digitised for digital processing.

What are the criteria? Obviously the transmission should be more immune to interference and noise pickup than simply transmitting the raw sensor data. The first option is to send the amplified analogue output down a wire. Assuming that noise picked up has a fixed amplitude, then there must be a value of gain for which the signal-to-noise ratio becomes acceptable.

Screening the cable helps to diminish noise pickup, as does using a differential format. Differential encoding produces two signals. Difference between the two signals is proportional to the amplified sensor signal. Provided that the conductors follow similar paths to the control node, then any pickup should be almost identical on both cables.

Feeding the resulting differential signals into a differential amplifier results in recovery of the original signal. Noise on the other hand, being common mode, is rejected. Again screening this double cable is a sensible precaution.

The multiplex disadvantage

Now all that remains is to interface the data into a data-acquisition board. This is true where one sensor is concerned, but consider what is needed if data is being acquired from more than one source.

In certain cases, a data-acquisition card with input multiplexer may be suitable. This is especially so if the data has been transferred using a low noise protocol such as current-loop technology.

Consider the following situation however, involving 16 remote sensors. These are interrogated at the same sample rate. This means that during any complete multiplexer cycle, each of the sensors is only being looked at for a sixteenth of the total time.

In other words, 93.75% of the data from the sensor is wasted. If some way of using this lost data could be found then the square-root law shows that signal-to-noise ratio could be increased substantially. From this argument you can see that the major drawback in the use of a simple signal multiplexer is that it succeeds in decreasing our potential signal-to-noise ratio by a factor proportional to the square root of the number of channels on the multiplexer. For the above simple example, the factor is four. So what is the solution? Until recently the only answer would have been to use frequency modulation.

Frequency modulation

There is much to commend frequency modulation. To implement it, each sensor buffer is fitted with a device known as a voltage-to-frequency converter. These are very accurate

voltage-controlled oscillators. Their output amplitude remains fixed. Frequency of the output signal on the other hand is directly proportional to input voltage – in this case the amplified sensor output. Once frequency modulated, the signal is transmitted directly to the acquisition system.

Being essentially digital, the fm signal is easily transmitted via an optical fibre, ensuring no noise pickup and complete isolation between the buffer and control node. Even if the cheaper option of screened electrical cable is opted for, isolation can still be accomplished using a standard opto-isolator.

Noise immunity provided by this technique comes from two directions: the first can be seen from Fig 5. In the top diagram, the ramp illustrates what an amplified and noise-contaminated analogue signal might look like on arriving at the control node. Although general shape of the ramp is clear, any fine detail is lost in the noise.

A fragment of a frequency-modulated waveform being transmitted down exactly the same transmission cable is shown in the second diagram. Its statistical noise corruption is identical. Removing the noise from the first waveform is not a trivial operation, relying on the techniques covered in last month's issue. Removing it from the second however is very simple.

The second advantage of fm stems from the way that the frequency encoded information is demodulated. This can be implemented via several devices, among them frequency-to-voltage converters and digital frequency integrators.

Frequency-to-voltage converters are complementary to voltage-to-frequency converters. In essence the voltage-to-converter, transmission line and frequency-to-voltage converter are transparent. Any change in voltage at the input produces a proportional change in voltage at the output. Noise corruption affects the amplitude of the signal. Because the information travelling down the transmission line is encoded as a frequency change, the signal output is virtually identical to the signal input.

Another efficient way of reconstructing the data is via a digital frequency integrator. It has the advantage that it removes the need for any analogue to digital converters at the control node end. Incoming frequency modulation is simply allowed to increment a counter for a fixed period of time. The faster the frequency, the higher the count.

At the end of the integration period, the count reached is directly proportional to the average voltage at the input of the voltage-to-frequency converter. If this integration period is made equal to the sample period, the accumulated count is a highly suitable format for applying averaging to the incoming data. Because the technique is immune from noise pickup on the transmission line, it helps to remove the noise already corrupting your sensor reading before it reaches the sensor buffer. As the resulting count is already in digital form, its interface to the control computer becomes trivial.

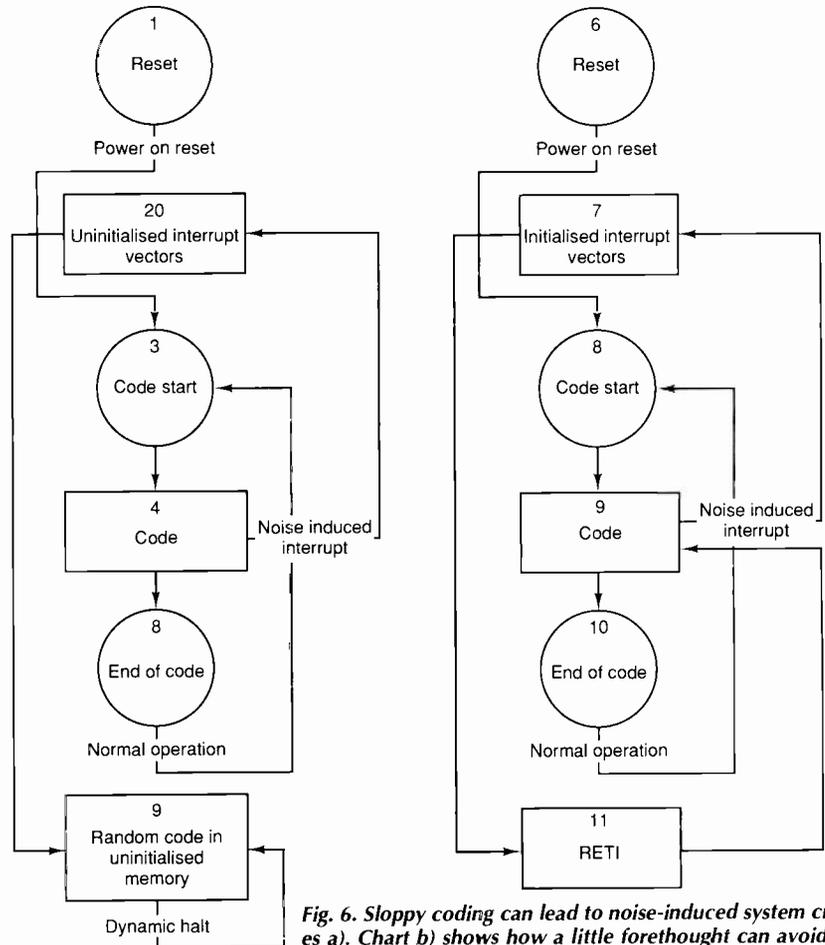


Fig. 6. Sloppy coding can lead to noise-induced system crashes a). Chart b) shows how a little forethought can avoid this problem.

Intelligent buffers

Powerful yet low power microcontrollers and microprocessors have considerably changed the nature of data acquisition. It is now possible to build in intelligence directly into the sensor buffer unit. This opens up options like applying sophisticated preprocessing to your sensor data locally. Preprocessing is application dependent but might well include removing noise from sensor input, sensor linearisation and temperature compensation.

Inserting intelligence at this position expands your options but it can also introduce pitfalls. To avoid them, make sure that any local power supplies are clean. If you have to receive the power from a remote source, then regenerate the rails via isolated dc-to-dc converters and use copious decoupling. Also use separate power planes to distribute power, as opposed to simple tracking.

On the logic-signal side, make sure that any unused interrupt lines and dma requests are strapped in their inactive states using pull up resistors. Do not leave them floating. Ensure that interrupt handling routines are included for all unused interrupt lines. These should comprise at least a return from interrupt instruction, even though you have tied the input line inactive, Fig 6. Problems caused by noise-induced interrupts to a non-existent inter-

rupt handler can be very difficult to detect.

Make sure that the reset line is filtered against transients. Include hardware so that the processor can perform a cold reset to all distributed elements of the system under software control. This is essential for restarting a multi-sensor system synchronously.

Include hardware and software to perform a watchdog function. When running normally, the software outputs periodic pulses that are detected by hardware. If the software runs out of control after a noise induced excursion, the watchdog pulses stop and the hardware causes a reset, bringing the system back under control.

Fill all unused program memory with non-operation instructions. This avoids the possibility of having an accidental 'dynamic halt' or similar instruction due to random bit patterns left in the prom.

When writing your serial communications software, do not rely on serial information getting through even at RS232 levels; expect your messages to become corrupted. Include some form of error checking, and handshake between the sensor buffer box and control node. Also consider using a synchronous protocol. These often automatically handle cyclic redundancy checking, etc. Both Motorola and Hitachi produce cost-effective micros with built in support for this. ■

COMPUTER ICs

8742 1 SHOT	£8	8742 WIPED	£5
TMS320	£5	TMS320 1 SHOT	£3
AM27C020-125L1 SURFACE MOUNT EPROM USED/WIPED	£1.50		
MM16450 UART CHIP	£5 ea		
MM16550 UART CHIP few only	£12 ea		
P8271 BBC DISC CONTROLLER CHIP EX EQPT	£25		
SA45050 TELETEXT CHIP EX EQPT	£5		
2817A-20 (2Kx8) EEPROM ex eqpt	£2		
D41256C-15 256Kx1 PULLS	9 FOR £5		
80C31 MICRO	£2		
P8749H MICRO	£5		
D8751-8 NEW	£10		
MK48202-20 ZERO POWER RAM EQUIV 6116LP	£4		
NEW 4164-15	£1		
USED 41256-15	£1		
USED 4164-15	60p		
BBC VIDEO ULA	£10		
8051 MICRO	£1.25		
8 x 4164 SIP MODULE NEW	£8		
FLOPPY DISC CONTROLLER CHIPS 1771	£16		
FLOPPY DISC CONTROLLER CHIPS 1772	£17.50		
68000-8 PROCESSOR NEW	£6		
HD6384-8	£5		
ALL USED EPROMS ERASED AND BLANK CHECKED			
2716-45 USED	£2 100/£1		
2732-45 USED	£2 100/£1		
2764-30 USED	£2 100/£1.60		
27C256-30 USED	£2		
27C512 USED	£3.50		
1702 EPROM EX EQPT	£5		
2114 EX EQPT 50p 4116 EX EQPT	70p		
6264-15 8k STATIC RAM	£2		
GR281 NON VOLATILE RAM EQUIV 6116	£5		
Z80A SIO-C	£1.25		
90387-16 CPU PROCESSOR (OK WITH 25MHz 386)	£35		
7126 3 1/2 DIGIT LCD DRIVER CHIP	£2 ea		
2816A-30 HOUSE MARKED	£2		
USED TMS2532JL	£2.50	2708 USED	£2
TMS77C82 USED/WIPED	£5		
HM6167LP-8	65p		
M27C 4001-15	£8		
68000-10 PROCESSOR	£6		

REGULATORS

LM338K	£6
LM323K 5V 3A PLASTIC	£2
LM323K 5VA METAL	£3
SANKEN STR451 USED IN AMSTRAD MONITORS	£5
78H12ASC 12V 5A	£5
LM317H T05 CAN	£1
LM317T PLASTIC TO220 variable	£1
LM317 METAL	£2.20
7812 METAL 12V 1A	£1
7805/12/15/24	25p
7905/12/15/24	25p
CA3085 T099 variable reg	2/£1

CRYSTAL OSCILLATORS

2M4576 3M686 4.5M0 5M76 6M144 7M000 7M3728 8M000	
12M000 14M3181 17M6256 16M257 18M000 20M000 23M587	
24M000 25M175 27M0 27M036 28M322 32M000 35M4816	
40M000 44M4444 44M900 48M000 64M000 1M000 1M8432	
4M000 10M000 16M000 18M432000 19M0500 20M0500	
38M10000 56M6092 76M1 84M0	£1.50 each

CRYSTALS

4M0256 10M368 17M6256 18M432 25M000 28M4694 31M4696	
48M000 55M500 111M80 112M80 114M318 114M691 1M0	
1M8 432 2M000 2M4576 2M77 3M00 3M2768 3M579545	
3M58564 3M93216 4M000 4M19304 4M433619 4M608 4M9152	
5M000 5M0688 6M000 6M400 8M000 8M488 9M8304 10M240	
10M245 10M70000 11M000 12M000 13M000 13M270 14M000	
14M381818 15M000 16M000 16M5888 17M000 20M000	
21M300 21M855 22M1184 24M000 34M368 36M75625	
36M7875 36M78125 36M79375 36M80625 36M81875	
36M83125 36M84375 38M900 49M504 54M19166 54M7416	
57M75833 60M000 69M545 69M550 6N 26M995 RD27M045	
OR27M095 YW27M145 GN27M195 BL27M245 3M225	£1 each

TRANSISTORS

MPSA92	10/£1
2N2907A	10/£1
BC477, BC488	10/£1
BC107 BCY70 PREFORMED LEADS	10/£1
full spec	£1 £4/100 £30/1000
BC557, BC238C, BC308B	£1/30 £3.50/100
2N3819 FETS short leads	4/£1

POWER TRANSISTORS

OC29	£1.35 ea
P POWER FET IRF9531 8A 60V	3/£1
N POWER FET IRF531 8A 60V	2/£1
2SC1520 sim BF259	3/£1 100/£22
TIP 141/2 £1 ea TIP 112 42B	2/£1
SE9301 100V 1DA DARL SIM TIP121	2/£1
PLASTIC 3055 OR 2955 equiv 50p	100/£35
BUZ31 POWER FET TO-220 20V 12.5A	2/£1

TEXTOL ZIF SOCKETS

28 PIN USED	£3	40 PIN NEW	£10
SINGLE IN LINE 32 WAY CAN BE GANGED FOR USE WITH ANY DUAL IN LINE DEVICES ... COUPLING SUPPLIED	2/£1.50		

QUARTZ HALOGEN LAMPS

12V 50watt LAMP TYPE M312	£1 ea	HOLDERS 60p ea
24V 150 WATTS LAMP TYPE A1/215	£2.50 each	

MISCELLANEOUS

MINIATURE FERRITE MAGNETS 4x4x3mm	10/£1
ALPS MOTORISED DUAL 47K LOG pots with spindle, works on 6v-12v	£1.50 ea
TL071 LO NOISE OP AMP	5 for £1

TL081 OP AMP	4 for £1
4700u0 25v SPRAGUE 36D	£3.50 £2
12 way dll sw	£3 for £1
10NF 63V X7R PHILIPS SURFACE MOUNT 160K available	£30/4000 box
SWITCHED MODE PSU 40 WATT UNCASED OTY AVAILABLE + 5v 5A, +12V 2A, 12V 500mA FLOATING	£9.95 (£2)
330nF 10% 250V X2 AC RATED PHILIPS	£20/100
220R 2.5W WIREWOUND RESISTOR 60K AVAILABLE	£50/1000

CMOS 555 TIMERS	2/£1
2/3 AA LITHIUM cells as used in compact cameras	2/£1.50
ICM7126CPL CMOS 3 1/2 DIGIT LCD DRIVER CHIP	£2 ea
36 CORE 7/0.2mm OVERALL SCREENED	£50/100m
LITHIUM CELL 1/2 AA SIZE	2 FOR £1
PASSIVE INFRA RED SENSOR CHIP + MIRROR + CIRCUIT	£2 each

EUROCARD 21-SLOT BACK PLANE 96/96-WAY "PROTONIC 24 VARIBUS" 16.7"x5" FIBREGLASS MULTILAYER PRH PCB	£25 ea
EUROCARD 96-WAY EXTENDER BOARD 290 x 100mm	£10 ea

"PROTONIC 24" c/w 2 SUPPORT ARMS/EJECTORS	
DIN 41612 96-WAY A/B/C SOCKET PCB RIGHT ANGLE	£1.30
DIN 41612 96-WAY A/B/C SOCKET WIRE WRAP PINS	£1.30
DIN 41612 64-WAY A/C SOCKET WIRE WRAP PINS	£1
DIN 41612 64-WAY A/C PLUG PCB RIGHT ANGLE	£1
DIN 41612 64-WAY A/B SOCKET WIRE WRAP (2-ROW BODY)	£1

BT PLUG + LEAD	3/£1
13A MOULDED PLUG + 2m lead	£1
MIN. TOGGLE SWITCH 1 POLE c/o PCB type	5/£1
LCD MODULE sim. LM018 but needs 150 to 250V AC for display	£10
40x2 characters 182 x 35 x 13mm	£10
TL431 2.5 to 36V TO92 ADJ. SHUNT REG.	2/£1
6-32 UNC 5/16 POZI PAN SCREWS	£1/100
NUTS	£1.25/100
PUSH SWITCH CHANGEOVER	2/£1
RS232 SERIAL CABLE D25 WAY MALE CONNECTORS	£5.90 ea (£1.30)

25 FEET LONG, 15 PINS WIRE BRAID + FOIL SCREENS	£6.50
LCD DISPLAY sim Hitachi LM016L	£30
AMERICAN 2/3 PIN CHASSIS SOCKET	2/£1
WIRE ENDED FUSES 0.25A	30/£1
NEW ULTRASONIC TRANSDUCERS 32kHz	£2/pr

Also available 28 slot vari-bus backplane same size + Price	
POWERFUL SMALL CYLINDRICAL MAGNETS	3/£1
BNC 500MHZ SCREENED CHASSIS SOCKET	2/£1
SMALL MICROWAVE DIODES AE1 OC1026A	2/£1
D.I.L. SWITCHES 10-WAY £1 8-WAY 80p 4/5/6-WAY 80p	20/£1
180VOLT 11WATT ZENERS also 12V & 75v	10/£1
MIN GLASS NEONS	10/£1
RELAY 5V 2-pole changeover looks like RS 355-741 marked STC 47W80st	£1 ea
MINIATURE CO-AX FREE PLUG RS 456-071	2/£1
MINIATURE CO-AX PCB SKT RS 456-093	2/£1
PCB WITH 2N2646 UNIJUNCTION WITH 12V 4-POLE RELAY	£1

400 MEGOHM THICK FILM RESISTORS	4/£1
STRAIN GAUGES 40 ohm Foil type polyester backed balco grid alloy	£1.50 ea 10+ £1
ELECTRET MICROPHONE INSERT	£0.90
Linear Hall effect IC Micro Switch no 613 SS4 sim RS 304-267	£2.50 100+ £1.50

HALL EFFECT IC UGS3040 + magnet	£1
OSCILLOSCOPE PROBE SWITCHED x1 x10	£12
1 pole 12-way rotary switch	4/£1
AUDIO ICS LM380 LM386 TDA 2003	£1 ea
555 TIMERS £1 741 OP AMP	6/£1
ZN414 AM RADIO CHIP	80p
COAX PLUGS nice ones	4/£1
COAX BACK TO BACK JOINERS	3/£1
4x4 MEMBRANE KEYBOARD	£1.50
INDUCTOR 20uH 1.5A	5/£1
1.25" PANEL FUSEHOLDERS	3/£1
CHROMED STEEL HINGES 1.45x1" OPEN	£1 each
12V 1.2W small w/lamps fit most modern cars	10/£1
STEREO CASSETTE HEAD	£2
MONO CASS. HEAD £1 ERASE HEAD	50p
THERMAL CUT OUTS 50 77 85 120°C	£1 ea
THERMAL FUSES 220°C/121°C 240V 15A	5/£1
TRANSISTOR MOUNTING PADS TO-5/T0-18	£3/1000
TO-3 TRANSISTOR COVERS	10/£1
PCB PINS FIT 0.1" VERO	200/£1
TO-220 micas + bushes	10/50p 100/£2
TO-3 micas + bushes	15/£1
Large heat shrink sleeving pack	£2
IEC chassis plug filter 10A	£3
POTS SHORT SPINDLES 2K5 10K 25K 1M 2M5	4/£1
40k U/S TRANSDUCERS EX-EQPT NO DATA	£1/pr
LM335Z 10MV/degree C	£1
LM234Z CONST. CURRENT I.C.	£1
BNC TO ANM BINDING POST SIM RS 455-961	£1
MIN PCB POWER RELAYS 10.5v COIL 6A CONTACTS 1 p pole c/o	£1

AVEL-LINDBERG MOULDED TRANSFORMER TYPE OB10 15+15V 10VA QTY. AVAILABLE	£2 ea
BANDOLIETED COMPONENTS ASSORTED Rs, Cs, ZENERS	£5/1000
LCD MODULE 16 CHAR. X 1 LINE (SIMILAR TO HITACHI LM10)	£5
KYNAR WIRE WRAP WIRE	£1/REEL
OPH1264A 10kV OPTO ISOLATOR	£1.35 ea 100+ £1 ea
'LOVE STORY' CLOCKWORK MUSICAL BOX MECHANISM MADE BY SANKYO	£1 ea
Telephone cable clips with hardened pins	500/£2

DIODES AND RECTIFIERS	
A115M 3A 600V FAST RECOVERY DIODE	4/£1
1N5407 3A 1000V	8/£1
1N4148	100/£1.50
1N4004 SD 4 1A 300V	100/£3
1N5401 3A 100V	10/£1
BA158 1A 400V fast recovery	100/£3

BY127 1200V 1.2A	10/£1
BY254 800V 3A	8/£1
BY255 1300V 3A	6/£1
6A 100V SMIAR MR751	4/£1
1A 600V BRIDGE RECTIFIER	4/£1
4A 100V BRIDGE	3/£1
6A 100V BRIDGE	2/£1
10A 200V BRIDGE	£1.50
25A 200 V BRIDGE £2	10/£18
25A 400V BRIDGE £2.50	10/£22
2KBPO2 IN LINE 2A 200V BRIDGE REC	8/£1

SCRS

PULSE TRANSFORMERS 1:1+1	£1.25
2P4M EQUIV C107D	3/£1
TICV106D 800ma 400C SCR 3/£1	100/£15
MEL21 PROG. UNIJUNCTION	3/£1

TRIACS

NEC TRIAC AC08F 8A 600V T0220	5/£2 100/£30
TXAL225 8A 500V 5mA GATE	2/£1 100/£35
BTA 08-400 ISO TAB 400V 5mA GATE	90p
TRIAL2230D 30A 400V ISOLATED STUD	£5 ea
TRIAL 1A 800V T3C81T 16k AVAILABLE	5 FOR £1 £15/100

CONNECTORS

D25 IDC PLUG OR SOCKET	£1.25
34-way card edge IDCONNECTOR (disk drive type)	£1.25
CENTRONICS 36 WAY IDC PLUG	£2.50
CENTRONICS 36 WAY IDC SKT	£4.00
BBC TO CENTRONICS PRINTER LEAD 1.5M	£3
CENTRONICS 36 WAY PLUG SOLDER TYPE	£4
USED CENTRONICS 36W PLUG + SKT	£3
14 WAY IDC BLOCK HEADER SKT	5/£1

PHOTO DEVICES

HI BRIGHTNESS LEDS COX24 RED	5/£1
SLOTTED OPTO-SWITCH OPCOA OPB815	£1.30
2N5777	50p
TIL81 PHOTO TRANSISTOR	£1
TIL38 INFRA RED LED	5/£1
4N25, OP12252 OPTO ISOLATOR	50p
PHOTO DIODE 50P	6/£2
MEL12 (PHOTO DARLINGTON BASE n/c)	50p
LED'S RED 3 or 5mm 12/£1	100/£6
LED'S GREEN OR YELLOW 10/£1	100/£6
FLASHING RED OR GREEN LED 50p	100/£40
HIGH SPEED MEDIUM AREA PHOTODIODE RS651-995	£10 ea

STC NTC BEAD THERMISTORS

G22 220R, G13 1K, G23 2K, G24 20K, G54 50K, G25 200K, RES 20°C DIRECTLY HEATED TYPE	£1 ea
FS22B NTC BEAD INSIDE END OF 1" GLASS PROBE RES 20°C DIRECT	£1 ea
A13 DIRECTLY HEATED BEAD THERMISTOR 1k res. ideal for audio Wien Bridge Oscillator	£2 ea

CERMET MULTI TURN PRESETS 3/4"

10R 20R 100R 200R 250R 500R 2K 2K2 2K5 5K 10K 47K 50K 100K 200K 500K 2M	£1 ea
---	-------

IC SOCKETS

14/16/18/20/24/28/40-WAY DIL SKTS	£1 per TUBE
8-WAY DIL SKTS	£2 per TUBE
32-WAY TURNED PIN SKTS, 7k available	3 for £1
SIMM SOCKET FOR 2x30-WAY SIMMS	£1

POLYESTER/POLYCARB CAPS

330nF 10% 250V AC X2 RATED PHILIPS TYPE 330	£20/100
100n, 220n 63V 5mm	20/£1 100/£3
1n/3n/5n/6n/8n/10n 1% 63V 10mm	100/£5
10n/15n/22n/33n/47n/66n 10mm rad	100/£5.10
100n 250V radial 10mm	100/£3
100n 600V Sprague axial 10/£1	100/£5 (£1)
2u2 160V rad 22mm, 2u2 100V rad 15mm	100/£10
10n/33n/47n 250V AC x rated 15mm	10/£1
1u 600V MIXED DIELECTRIC	50p ea
1u0 100V rad 15mm, 1u0 22mm rad	100/£6

RF BITS

SAW FILTERS SW662/SW661 PLESSEY SIGNAL TECHNOLOGY 379.5 MHZ	£1.50 ea **NEW
F3X286 FERRITE RING ID 5mm OD 10mm	10 for £1
ASTECH UM1233 UHF VIDEO MODULATORS (NO SOUND) 1250 STOCK	£1.50 **NEW
MARCONI MICROWAVE DIODES TYPES DC2929, DC2962	£1 ea
DC 4229/F2	£1 ea
XTAL FILTERS 21M4 55M0	£2 ea
ALL TRIMMERS	3 for 50p
VIOLET	5-105pF
YELLOW 5-65pF RED 10-110pF GREY 5-25pF	
SMALL MULLARD 2 to 22pF	3 FOR 50p £10/100
TRANSISTORS 2N4427, 2N3866, 2N5109	80p ea.


CERAMIC FILTERS 4M5/6M/9M/10M7	60p ea
FEED THRU CERAMIC CAPS 1000pF	10/£1
SL610	£5
6 VOLT TELETYPE RELAYS 2 POLE CHANGEOVER (BFY51 TRANSISTOR CAN SIZE)	£2
2N2222 METAL	5/£1
P2N2222A PLASTIC	10/£1
2N2369A	5/£1
VN10KM	4/£1

PLESSEY ICS EX-STOCK

SL350G SL360G SL362C SL403D SL423A	
SL521B SL523C SL541B SL850C SL1021A	
SP8655 SP8719DG	

MONOLITHIC CERAMIC CAPACITORS

10n 50V 2.5mm	100/£4.50
100n 50V 2.5mm or 5mm	100/£6
100n ax short leads	100/£3

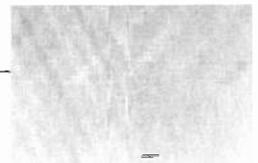

New maps for Smith's world

The Smith chart is the rf engineer's best friend. Ian White reviews Z-Match for Windows, the new Smith-chart program from Number One Systems.

The Smith chart is a visual way of designing and understanding impedance transformations in networks and transmission lines. Designed for pencil and paper it remains a powerful design tool; whatever you can draw on a paper chart, you can also draw on a computer screen.

The programming challenge is to keep all the paper chart's good features and then to add facilities unique to the computerised version. Although previous versions of Number One Systems' Z-Match software for dos came close to those objectives, Z-Match for Windows has made it.

On the screen

The main display is divided into two areas, the Smith chart on the right and the control and information panel on the left (Fig. 1). You draw on the chart in the usual Windows fashion using the mouse. Buttons on the left-hand panel control the main functions, so you seldom need to pull down the menus from the top of the screen. The non-linear scales that used to be the bane of the paper chart are replaced by precise numerical displays, linked to the position of the mouse cursor on the display.

The Smith chart has always been essentially a visual design aid (see the sidebar for an explanation of how the chart works). You draw lines and curves corresponding to your design ideas, and watch what happens to the circuit impedances and other parameters. Quite frequently you need to back-track to an earlier point and reconsider what to do next or even throw away the existing chart and start again with a clean sheet. The software makes good use of the Windows environment to provide these facilities and more.

A cross-shaped flashing cursor represents the current operating point for dragging and dropping around the display using the mouse. Cursor movement can be either free or constrained to follow an arc of constant R. X or VSWR away from its starting point, something you could

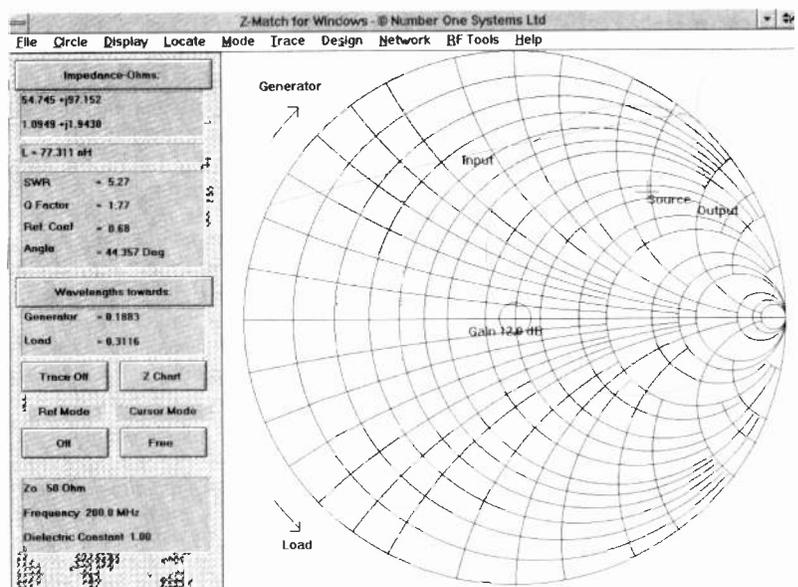


Fig. 1. Z-Match for Windows displays its power with a complicated Smith chart, showing stability and gain circles. Note the cross-shaped cursor over the point marked Source; the panel at the left of the screen displays a range of information about the cursor location, including its absolute and normalized impedance. Quick-change buttons control the most used features of the chart.

not do on a paper chart without first drawing the relevant arc. Whenever you move the cursor, numerical displays of nine parameters are very rapidly updated once again, a facility unique to a computerised Smith chart.

Alternatively you can type in an explicit impedance and the cursor will go there. If you want to leave a permanent mark at any cursor position, simply double-click the mouse button.

For back-tracking and erasing mistakes, *Z-Match for Windows* has an undo function which successively removes objects you had drawn on the chart and restores the cursor to its previous position.

The final requirements to replace the basic paper Smith chart are somewhere to file your work for later retrieval, a waste-basket and an endless supply of clean charts. Windows' familiar File menu provides these functions using Save, Save As, Open and New and of course you can always send a chart to the Windows system printer. Together, all these features provide a good simulation of the familiar paper-and-pencil environment.

Many other functions are accessible through the menu system. For example, several of the numerical displays make use of the system reference frequency (in MHz), the reference impedance Z_0 and the velocity factor of the transmission line, any of which can be changed using the Display - Parameters sub-menu. In addition, buttons in the left-hand panel provide shortcuts to the most useful charting functions.

The software makes two of the most difficult Smith chart operations simple. You can convert with a single click between impedance and admittance charts (see sidebar), allowing the addition of admittances in parallel just as easily as impedances in series. The whole chart flips, leaving the cursor exactly where it was on the screen while maintaining your trace of previous movements. Two clicks draws a unit conductance circle on an impedance chart, or a unit-resistance circle on an admittance chart.

To understand what it was like without these aids, imagine navigating using two road-maps, one showing

only major roads and the other showing only minor roads. You could manage it with practice, but you wouldn't ever want to! These features of the software banish one of the most confusing aspects of the paper Smith chart.

The other difficult routine operation is impedance renormalization which occurs on moving from one system impedance to another. The software offers two ways of doing this. Either you can type in a new system reference impedance Z_0 (and optionally have the cursor position recalculated) or you can specify any cursor location as the new reference impedance; all subsequent cursor movements and displays are referenced to this location on the chart. It is easy to alternate between two different reference impedances.

Advanced functions

A regular use of the Smith chart is to design impedance matching networks, starting from some arbitrary impedance and usually ending at the reference impedance Z_0 in the centre of the chart. The technique is to work your way in towards the centre by adding reactances in series or in parallel.

Reactance in series is added by moving along a constant-resistance line on the impedance chart, while reactance in parallel is added by moving along a constant-conductance line on the admittance chart. In many practical cases the quickest route home is via a point further out towards the periphery of the chart. All this is straightforward in *Z-Match for Windows*, but the software also has a special network synthesis function which draws the circuit diagram of the network you have designed.

Smith chart refresher

Any impedance can be represented as $R \pm jX$ where R is the resistive or "real" component and X is the reactive component, positive for inductance and negative for capacitance. Although you can plot R and X on conventional rectangular coordinates, it can be difficult to represent the very low and very high values that occur in transmission-line calculations.

The problem of very low and high impedances is solved by two techniques: normalization and logarithmic axes. When working in a system that has a defined

standard impedance Z_0 , for example a transmission-line impedance of 50Ω , it is useful to normalize all impedances, so that R becomes R/Z_0 and X becomes X/Z_0 . Thus a normalized impedance of $2 + j1.5$ represents $100 + j75\Omega$ in a 50Ω system.

Logarithmic resistance and reactance scales are possible because real-life rf resistances and reactances do not truly reach either zero or infinity.


Fig. A shows a logarithmic resistance-reactance plot using rectangular axes, with a single "zero-to-infinity" scale for resistance

and two mirror-image scales for positive and negative reactances. The system reference impedance Z_0 falls in the centre of the normalized plot, at $1 + j0$.

What happens if you plot all impedances corresponding to a voltage standing wave ratio vswr of say 2.0 on this diagram? The two relevant points on the normalized resistance axis are $2.0 + j0$ and $0.5 + j0$, and these are equidistant from the origin because the scale is logarithmic. The two corresponding points on the normalized reactance axis are $1 + j0.71$ and $1 - j0.71$. If we scale the axes appropriately, these four points can be made to lie on a circle.

Moving around this constant vswr circle, one complete revolution will pass through all possible combinations of resistance and reactance that produce a vswr of 2, equivalent to having travelled a half-wave along a transmission line.

Unfortunately the angular scale is not linear: $1 + j0.71$ represents a phase angle of 35° rather than 90° as it appears on Fig. A. The genius of Phillip Smith was to realise what happens when the straight-line reactance axes of Fig. A are bent around to form two half-circles whose "infinity" ends join together at the right of the chart. Figure A has become transformed to Fig. B, a Smith chart. Remarkably, the vswr circle remains a circle, but its phase-angle scale

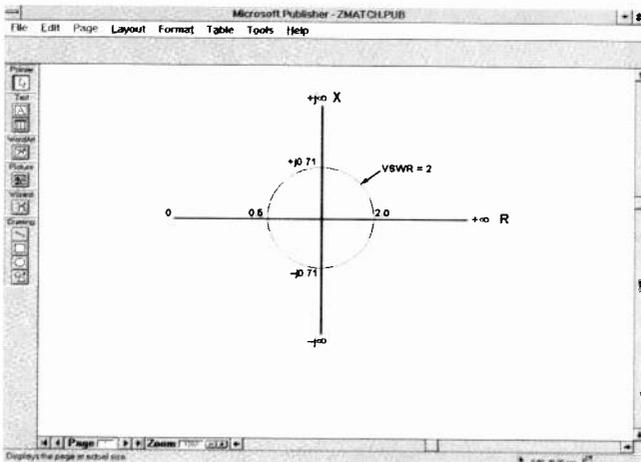

A) One way to represent all practicable impedances $R \pm jX$ on two rectangular axes. All combinations of resistance and reactance that have a normalized voltage standing wave ratio of 2.0 will fall on the constant-VSWR circle. To transform this diagram into a Smith chart Figure B, bend the two reactance axes round so that all three "infinity" points meet at the right-hand end of the resistance axis.

The resulting netlist can be saved in a file format compatible with Number One Systems' *Analyser* nodal analysis software. Similarly you can read in results files from *Analyser* and have *Z-Match* plot them in Smith chart form.

S-parameters are widely used in rf design, and the review software also handles them. Device data may be entered either manually or from files (the package contains the Motorola device library in industry-standard S2P format). It will interpolate frequency dependent file data to the desired frequency, and gives an immediate indication whether the device is stable at a selected frequency. It can then go on to calculate stability circles, source and load impedances, etc.

In Figure 1 the program has calculated and plotted the input and output stability circles (the stable area is towards the middle of the chart), a constant-gain circle for a user selected value of 12dB, and a suitable source impedance. You can then go on to match this impedance using the network synthesis function described earlier.

Off the map

The information panel beside the Smith chart can display its data in several alternative forms, avoiding the need for routine interconversions. In addition there is an RF Tools menu offering interconversions between power and voltage ratios, dB and dBm; and between VSWR, reflection coefficient and return loss. The same menu also offers reactance and resonance calculations, and a designer for simple transmission-line transformers to match any arbitrary impedance to Z_0 .

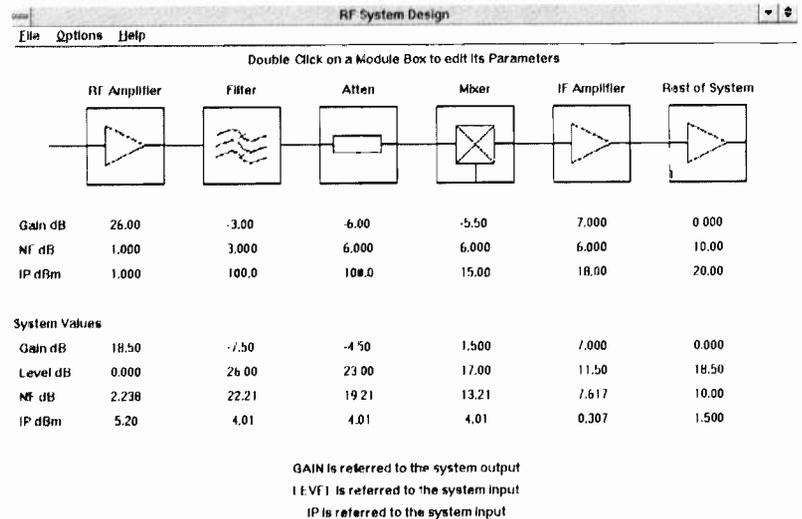


Fig. 2. The receiver noise figure and intermodulation calculator from the rf Tools menu. The top three rows of data refer to the individual modules in the block diagram drawn above. The bottom four rows show how the cascaded stages interact to produce the overall system performance. Double-click on any module box to alter its data, and the whole display is automatically recalculated.

has now become linear. What is more, the entire Smith chart can be constructed from one horizontal straight line and a series of simple arcs and circles.

The horizontal diameter still represents pure resistance, ranging from zero to infinity with $R=1$ at the centre of the chart. Lines of constant resistance are circles, crossing the horizontal diameter at normalized values of $R=0.5, 1, 2$ and so on. R is zero all around the periphery of the chart, except at the "infinity" point where all the constant- R circles meet tangentially. Positive reactances lie above the horizontal diameter, negative reactances below. Lines of constant reactance are arcs of circles, mirror-imaged above and below the diameter and all converging on the "infinity" point. Figure B shows all these characteristics.


Thus you can plot any practicable impedance on a Smith chart, and watch how it changes as you travel on a constant-vswr circle along the transmission line. Anticlockwise is forwards towards the load, clockwise is backwards towards the generator, and a full revolution of the chart represents 180° along the line, in other words a half wavelength.

What happens if you add an inductance in series with an impedance already plotted? You move along a constant-resistance circle

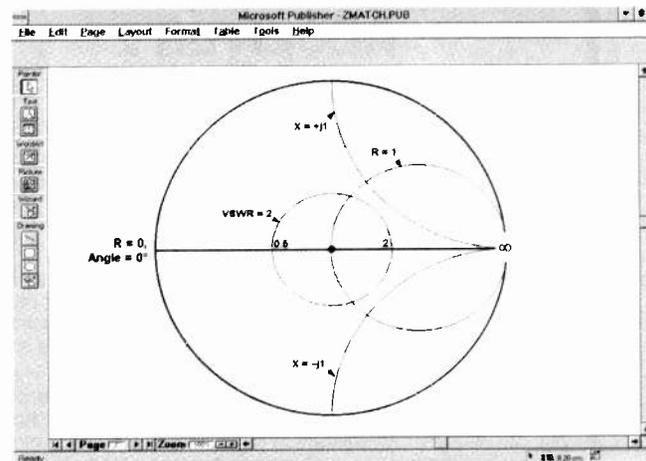B) A basic Smith chart, showing the same constant-VSWR circle as Figure A. The horizontal resistance axis is still the same, and all other components consist of simple arcs and circles. To convert this impedance chart into an admittance chart, mirror-image it from right to left. The Smith chart is the rf design engineer's best friend. Once you know your way around, it provides a convenient and simple way of solving all manner of problems of impedance transformation, amplifier design and stability analysis. Here's how it works.

into the region of higher inductive reactance. How much has the phase angle changed as a result? Draw straight lines out from the centre of the circle through your origin and destination points, and measure the angle between them not forgetting that every 1° on the chart represents 0.5° along the transmission line.

Once you know how to read the map, there are yet more wonders in Smith's World. Thanks to its logarithmic scaling, the Smith chart works equally well as an admittance $1/Z$ chart, which opens the way



to dealing with impedances added in parallel. Changes of characteristic impedance are handled very easily; you can either renormalize all the plotted impedances; or else take advantage of the fact that a constant-vswr circle can be centred anywhere on the chart and will still remain a true circle. This latter property opens yet further paths to the analysis of amplifier stability and noise figure, both of which can be represented using constant-value circles.

Although receiver noise and intermodulation calculations are not directly related to Smith charts, it is useful to have these facilities to hand. Fig. 2 shows how the concept is implemented in *Z-Match for Windows*. Double-click on the box representing a module in the block diagram and a window opens, into which you can enter data relevant to that module. On closing the window, the software recomputes the noise and intermodulation performance of the whole system. Noise performance can be displayed as either noise figure (dB) or noise temperature (K). This Windows "applet" has its own File menu with facilities to save and retrieve designs, and to print out the block diagrams and results.

The package

The software comes with a thorough and well-written 125-page manual, and installation from the single program disk is quick and straightforward. The Motorola device library comes on a second disk, and need not be permanently installed.

Even if you start out knowing very little about Smith charts, the manual gives an extensive explanation of the concepts followed by worked examples to introduce you to the software implementation. Lack of experience may even be an advantage, because experienced Smith chart users may need to unlearn some cherished techniques that were actually geared to the inadequacies of the paper chart.

In spite of a price which may deter amateurs, *Z-Match for Windows* could easily make itself indispensable to any professional rf design engineer. ■

SYSTEM REQUIREMENTS

286, 386 or 486-based PC (at least 16MHz 386SX preferred)
 Coprocessor is used if available
 Graphics display and monitor (at least colour VGA preferred)
 Mouse
 Windows 3.0 or later, under DOS 3.0 or later
 3.5in 1.44MB floppy disk drive
 1MB hard disk space (program will run from floppy disk)

PRICE

Price £245.00 + VAT (upgrade from Z-Match for dos £50.00 + VAT)

SUPPLIER DETAILS

Number One Systems Ltd, Harding Way, Somersham Road, St Ives, Cambridgeshire PE17 4WR. Telephone 0480 461778, fax 0480 494042.

**BROADCAST MONITOR RECEIVER 2
 150kHz-30MHz**



We have taken the synthesised all mode FRG8800 communications receiver and made over 30 modifications to provide a receiver for rebroadcast purposes or checking transmitter performance as well as being suited to communications use and news gathering from international short wave stations.

The modifications include four additional circuit boards providing *Rechargeable memory and clock back-up *Balanced Audio line output *Reduced AM distortion *Buffered IF output for monitoring transmitted modulation envelope on an oscilloscope *Mains safety improvements.

The receiver is available in free standing or rack mounting form and all the original microprocessor features are retained. The new AM system achieves exceptionally low distortion: THD, 200Hz-6kHz at 90% modulation -44dB, 0.6% (originally 20dB, 10%).

*Advanced Active Aerial 4kHz-30MHz *PPM10 In-vision PPM and chart recorder *Twin Twin PPM Rack and Box Units *Stabilizers and Fixed Shift Circuit Boards for howl reduction *10 Outlet Distribution Amplifier 4 *Stereo Variable Emphasis Limiter 3 *Stereo Disc Amplifier 4 *Peak Deviation Meter *PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and movements *Broadcast Stereo Coders

SURREY ELECTRONICS LTD

The Forge, Lucks Green, Cranleigh,
 Surrey GU6 7BG.

Telephone: 0483 275997. Fax: 276477

**ADVERTISERS
 PLEASE NOTE**

For all your future

enquiries on

advertising rates,

please contact

Malcolm Wells on:

Tel: 081-652 3620

Fax: 081-652 8956

APPLICATIONS

Please mention *Electronics World + Wireless World* when seeking further information.


Low power PWM with programmable shutdown

Combined features of the *UCC1570* family of pulse width modulators are low power and high-speed operation. Typical start-up current is $85\mu\text{A}$, running current is 1mA , and the device can drive a power mosfet at up to 500kHz . Peak gate drive current is 1A .


As this circuit diagram from the *1570* family preliminary data sheet shows, the device is intended for use in switching supplies. It is optimised for isolated designs with primary side control and a voltage mode feedback loop.

Made in bimos technology, the three versions in the range have a low start up current requirement. This allows efficient off-line starting with a bootstrapped low-voltage supply. Voltage feedforward provides fast and accurate response to wide line voltage variation without the noise sensitivity associated with current-mode control.

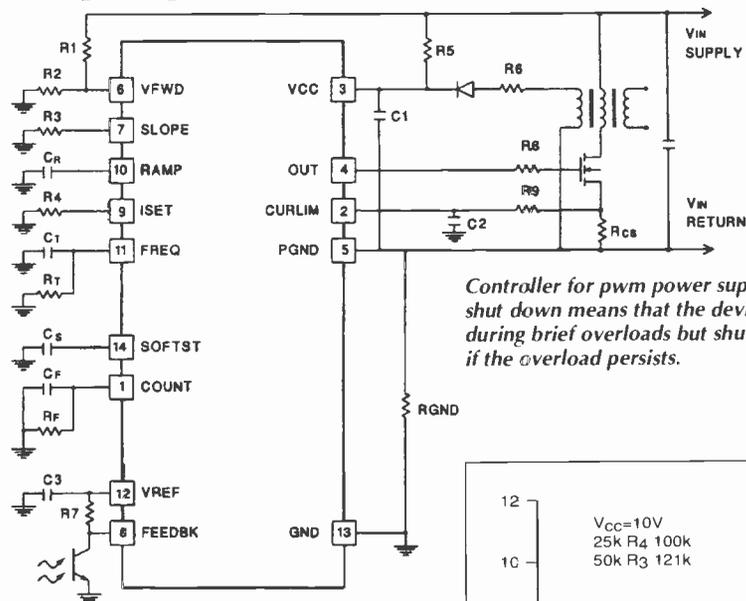
Fast current limiting is included with the ability to latch off after a programmable



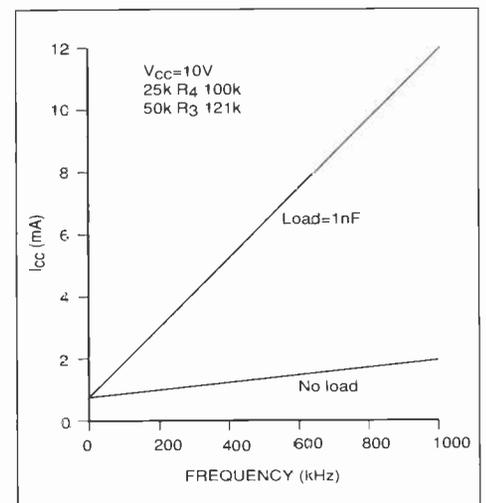Controller for pwm power supplies. Fault-counting shut down means that the device stays operational during brief overloads but shuts down completely if the overload persists.



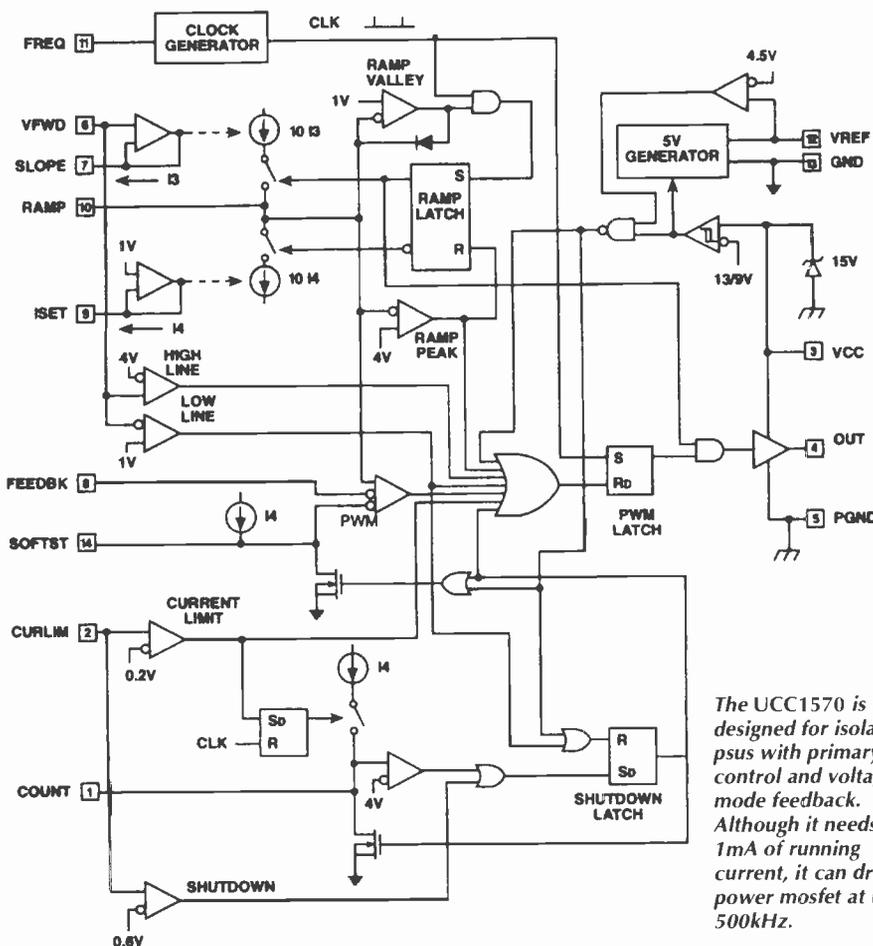Current versus frequency for the UCC1570 pwm controller while in operating mode shows that little current is needed to operate the device – even at high switching speeds and with high mosfet gate capacitance.



The UCC1570 is designed for isolated psus with primary-side control and voltage-mode feedback. Although it needs only 1mA of running current, it can drive a power mosfet at up to 500kHz.

number of repetitive faults has occurred. This enables the power supply to withstand a temporary overload, while still shutting down in the event of a permanent fault.

A built-in maximum duty-cycle clamp is programmable between 20% to 80%. Line voltage sensing is enhanced by the provision of a programmable window of allowable operation. Further facilities offered by the devices are an optocoupler interface and fault latch-off or automatic-restart options.

Notes on how to calculate the components shown are included in the data sheet.

Unitrode UK Ltd, 6 Creswell Park, Blackheath, London SE3 9RD. Tel. 081 318 1431, fax 081 318 2549.

Video selection for broadcast industry

Signal routing and buffering circuits for video feature in Maxim's *Analog Design Guide 3/8*.

In the oscillograph, input versus output is shown for a 180MHz video buffer with guaranteed 0.99V/V gain over its temperature range of -40 to 85°C. This buffer, the MAX405, has a differential phase and gain errors of 0.01° and 0.03%. In addition, it holds its gain with loads as low as 50Ω. Suitable for driving NTSC, PAL or SECAM, the device operates from ±5V supplies and has a slew rate of 650V/μs.

For the eight-by-four crosspoint switch shown, Maxim claims the highest integration and precision in the industry.


Operating at 100MHz and handling 'broadcast-quality' video, the MAX458 and 459 switches incorporate a digital control interface and output buffers. In the 458, these four buffers are unity gain while in the 459 they have a gain of 2. This extra gain is for driving 150Ω back-terminated cable directly, without needing feedback resistors. Phase error is 0.06° while differential gain error is 0.03%.

One of eight video channels is selectable via the MAX440. It has a 160MHz response, 250V/μs slew rate and can switch a pixel in 15ns. Differential gain and phase errors are 0.03° and 0.04% respectively. There are also four and two-channel versions of this switch.



The final circuit is a four-pole, two-way switch for selecting rgb video and sync from two sources. Output swing, provided by buffers with a gain of 2, is ±2V with a 50Ω load and the device operates up to 100MHz.

Other video circuits in the note cover triple and quad 100MHz buffers with no external feedback and a 250MHz no-feedback video amplifier with a slew rate of 850V/μs.

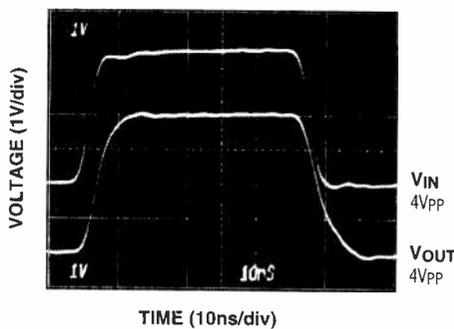
Maxim Integrated Products, 21C
Horseshoe Park, Pangbourne, Reading
RG8 7JW. Tel. 0734 845255, fax 0734 843863.



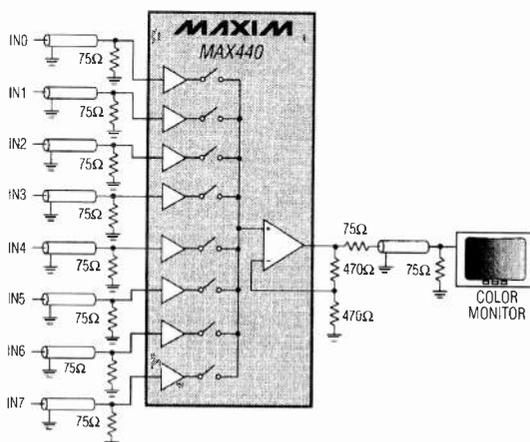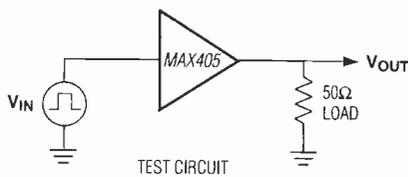
With a differential phase error of 0.01° and a gain error of 0.03%, the MAX405 buffers video up to 180MHz and provides 0.99V/V gain over its full temperature range.



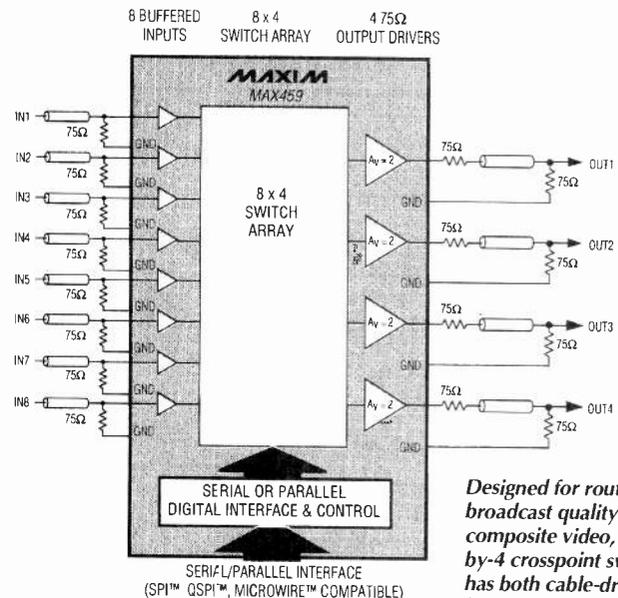Useful in applications such as selecting surveillance camera sources, the MAX440 eight-way switch has pin-selectable frequency compensation and operates to 160MHz.



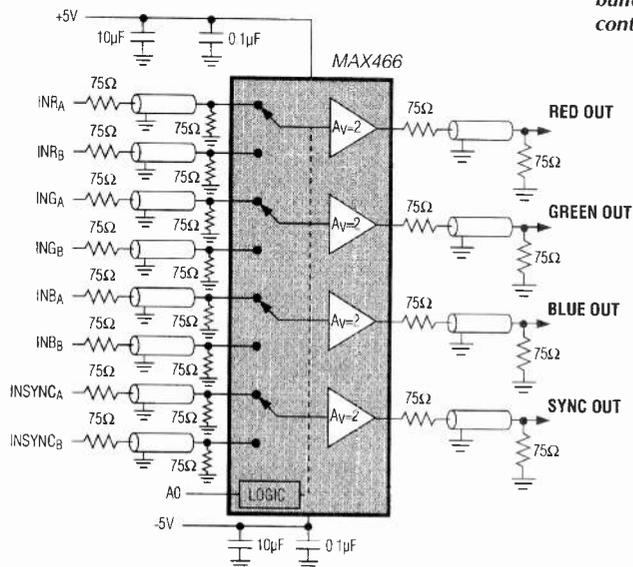Designed for routing broadcast quality composite video, this 8-by-4 crosspoint switch has both cable-drive buffers and digital control interface.



The MAX466, intended for switching between two RGB-plus-sync sources, has 100MHz 6dB buffer amplifiers capable of driving ±2V into a 75Ω load.

Integrated frontend devices for DECT

Three ICs designed to simplify and miniaturise DECT-compatible equipment have been introduced by Motorola.


These application diagrams are from device data sheets for the new devices, namely the *MRFIC1801*, *1803* and *1804*. The *1801* is a 1.8GHz antenna switch, the *1803* an up-converter, and the *1804* a combined INA and down-mixer.

Also suitable for the Japan Personal Handy Phone standard, JPHP, and other personal communication systems, all three devices are produced in surface-mount packaging. They operate from 85° down to -30°C, rendering them suitable for all-weather use.

With the exception of the antenna switch, which can run from a rail up to 5.5V, operation is from a single 2.7-3.3V supply. Combined consumption of both converters is typically just over 100mW, while current needed for the antenna switch is 300µA in transmit mode, or 50µA when receiving.

Transmission insertion loss of the *1801* antenna switch is typically 0.75dB, while the 1dB compression point is quoted as 29dBm. Capable of operating at frequencies from 1.5 to 2.5GHz, the switch is activated via a simple on/off logic input and exhibits 22dB transmit to receive isolation.

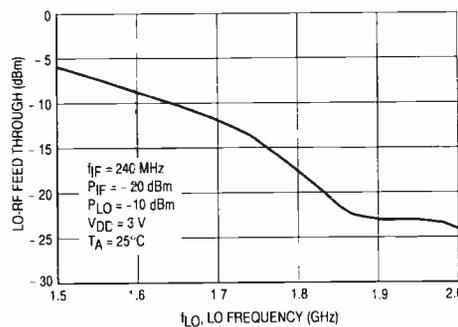
Incorporated in the *1803* up-converter are an active up-mixer, exciter amplifier and



Local oscillator versus rf feedthrough for the 1803 1.8GHz up-converter.

local-oscillator buffer amplifier. The device provides 10dB intermediate-to-radio-frequency conversion gain and has a usable frequency range of 1.7 to 2.5GHz.

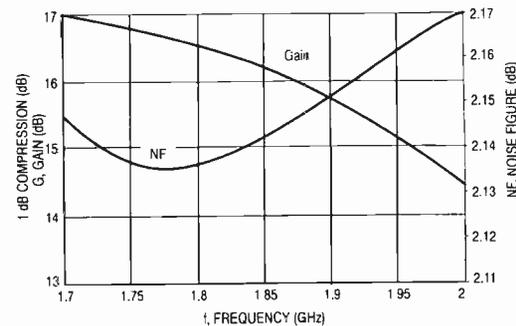
Within the *1804* is an rf amplifier with a 2.3dB noise figure and providing 14dB gain. The mixer section provides 4dB of gain, with



Gain and noise of the 1804 DECT low-noise amplifier versus frequency.


typically 13dB noise. Usable frequency range of the device is 1.8 to 1.925GHz.

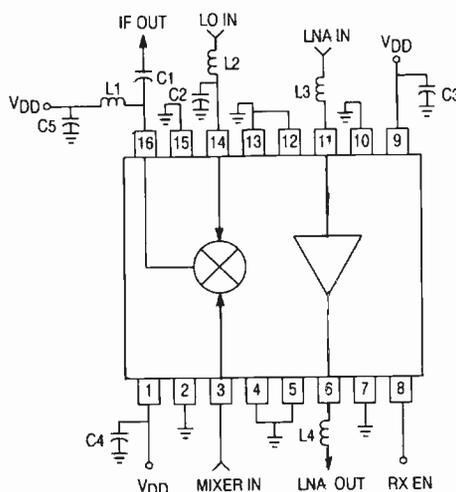Motorola European Literature Centre, 88 Tanners Drive, Blakelands, Milton Keynes MK14 5BP. Tel. 0908 614614, fax 0908 618650.



- C1 12 pF (110 MHz) or 7.5 pF (240 MHz)
- C2 0.8 pF
- C3, C4 100 pF
- C5 1000 pF
- L1 82 nH (110 MHz) or 15 nH (240 MHz)
- L2 8.2 nH
- L3, L4 0.3 nH (Microstrip)

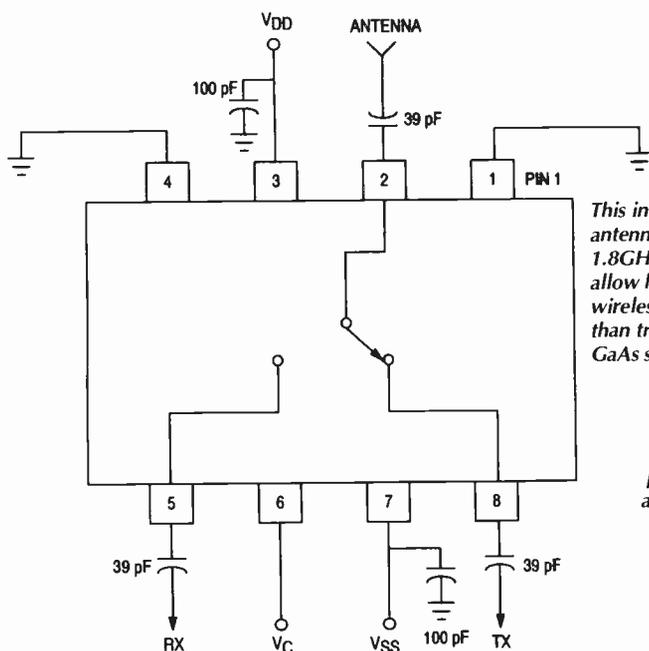
Complementary to the 1803 up-converter, the 8104 integrated DECT lna and down-mixer has a 0.9dB mixer input intercept point and needs only -5dBm of local-oscillator power. Components are for 110 and 240MHz IFs.



- C1 470 pF
- C2 100 pF
- C3 0.1 µF (optional)

This integrated antenna switch for 1.8GHz is said to allow higher power wireless systems than traditional GaAs switches.

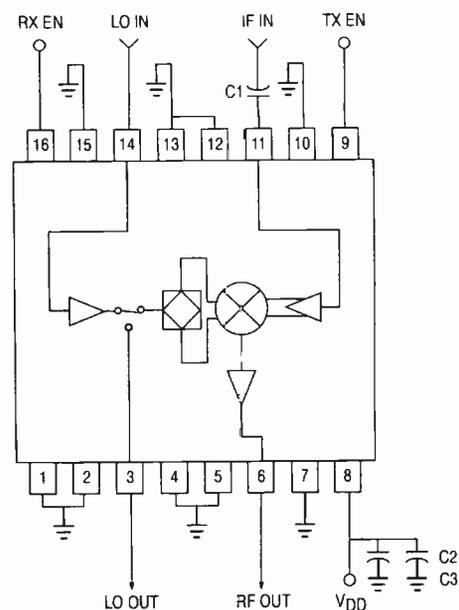Combined within this up-converter for DECT and other personal communication systems are an active up-mixer, an exciter amplifier and local-oscillator buffer. No external baluns are needed and the IF, LO and RF ports are matched to 50Ω.



Micropower op-amp for 2.7V supplies

These circuits are designs based on a new op-amp from National Semiconductor. Called the *LMC6572*, this IC is optimised for low-voltage and battery-powered applications involving supplies down to 2.7V.


To obtain a rail-to-rail output swing at low supply voltages and relatively high loads, the unity-gain output buffer traditionally found in ICs has been abandoned. Instead, output is taken directly from an integrator. This is said to provide low output impedance combined with high gain.

Feed-forward techniques are used to maintain stability over a wider range of operating conditions than is usual for micropower op-amps. Ultra-low-power op-


amps are normally very slow. This device has a 0.22MHz gain-bandwidth product together with a typical slew rate of 90V/ms given a 2.7V supply.

There is a quad version of the *LM6572* dual op-amp called the *LM6574*. In the joint *6572/6574* data sheet, there is further information on how the devices are compensated for input capacitance and capacitive loading. There is also further text on pcb layout for high-impedance circuitry.

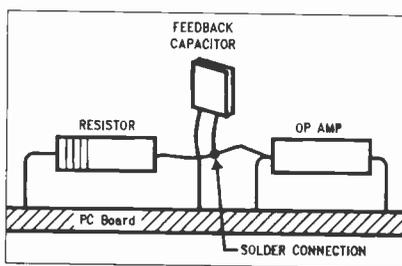National Semiconductor, The Maple, Kembrey Park, Swindon, Wiltshire SN2 6UT, Tel. 0793 614141, fax 0793 697522



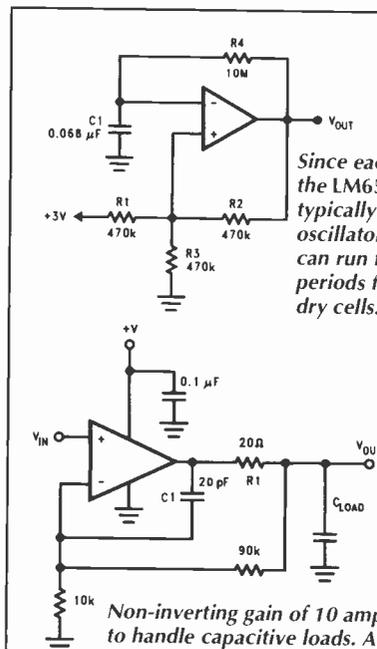can often be outweighed by the improvement in guarding performance



Since each op-amp in the *LM6572* consumes typically 40µA, a 1Hz oscillator such as this can run for long periods from two small dry cells.

Non-inverting gain of 10 amplifier designed to handle capacitive loads. A feedback-loop pole induces phase lag at the op-amp's unity-gain crossover frequency. This results in oscillation or underdamped response when driving capacitive loads - a problem solved here by the addition of a few passive components.

Air improves op-amp guarding

Most op-amp application information prescribes making guard rings for high-impedance op-amp inputs from a ring of pcb copper. According to the *LM6572* data sheet, guarding is improved using air insulation.

To implement air insulation, the IC input pin concerned is bent away from the pcb. Components are then soldered directly to the pin. NS admits that some of the advantages of using a pcb are lost, but says that these



8 CAVANS WAY,
BINLEY INDUSTRIAL ESTATE,
COVENTRY CV3 2SF
Tel: 0203 650702
Fax: 0203 650773
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

OSCILLOSCOPES

Gould 400 - 20MHz D.S.O. 100 Ms/s	£1000
Gould OS4000, OS4200, OS4200, OS4020, OS245	from £125
Nicolet 3091 - 4 channel low frequency D.S.O.	£250
Gould 4035 - 20MHz digital storage	£600
Gould 4050 - 35MHz digital storage	£750
Gould 5110 - 100MHz intelligent oscilloscope	£950
Hewlett Packard 1707A, 1707B - 75MHz dual ch.	from £275
Hewlett Packard 1740A, 1741A, 1744A, 100MHz dual ch	from £350
Hewlett Packard 182C - 100MHz 4 ch.	£350
Hitchel V-422 - 40MHz dual ch.	£300
Nicolet 3091 - Low freq D.S.O.	£1100
Nicolet 4094 - 20MHz D.S.O. dual ch.	£500
Tektronix 2201 - 20MHz D.S.O. dual ch.	£675
Tektronix 2215 - 60MHz dual ch.	£425
Tektronix 2215 - 60MHz dual ch.	£450
Tektronix 2230 - 100MHz digital storage	£1650
Tektronix 2235 - 100MHz dual ch. (portable)	£800
Tektronix 2246 - 100MHz 4 channel (as new)	£995
Tektronix 2335 - 100MHz dual ch. (portable)	£750
Tektronix 465/465B - 100MHz dual ch.	from £350
Tektronix 475 - 200MHz dual ch.	£450
Tektronix 7313, 7603, 7613, 7623, 7633, 100MHz 4 ch.	from £300
Tektronix 7704 - 250MHz 4 ch.	from £650
Tektronix 7834/7844 - 40MHz 4 ch.	from £750
Tektronix 7904 - 500MHz	from £850
Philips 3206, 3211, 3212, 3217, 3226, 3240, 3243, 3244, 3261, 3262 (2ch + 4ch)	from £125 to £350
Solartron Schlumberger CD1740 - 20MHz 4 ch.	£250

Other scopes available too

SPECTRUM ANALYSERS

Alltech 727 - 20GHz	£2200
Hewlett Packard 3580A - 5Hz - 50kHz	£1250
Hewlett Packard 3582A - 25kHz analyser, dual channel	£2500
Hewlett Packard 8590A - 10MHz - 1.5GHz (as new)	£4500
Hewlett Packard 8590B - 9kHz - 1.8GHz	£4750
Hewlett Packard 8754A - Network Analyser 4 - 1300MHz	£3500
Hewlett Packard 182T with 8559A (10MHz - 21GHz)	£3750
Hewlett Packard 4953 Protocol analyser	£2500
Marconi 2370 - 110MHz	£1250
Rohde & Schwarz - SWOB 5 Polyskop 0.1 - 1300MHz	£2750
Tektronix 7L18 with 7603 mainframe (1.5-18GHz)	£4500
Tektronix 492 - 21GHz	£5500
Texscan AL51A - 1GHz	£1300

MISCELLANEOUS

Anritsu ML93B/ML92B Optical power meter with sensor	£2000
Anritsu ME538C Microwave system analyser (Rx + Tx)	£3500
B&K 2511 - 1621 Vibration test set	£2000
B&K 2511 Vibration meter	£1500
B&K 2515 Vibration analyser	£4500

Dranzet 305 Phase meter	£250
Dymar 1585 AF Power meter	£175
Dymar 2085 AF Power meter	£200
Farnell RB 1030-35 Electronic load 1kW	£450
Farnell AMB Automatic modulation meter	£150
Farnell 2081 RF Power meter	POA
Farnell SS6520 Sig. Gen. 10 - 520MHz	£900
Farnell TT5520 Transmitter test set	£900
Farnell SG1B Sig. Gen. interface	£900
Feedback TWG300 Test waveform generator	£200
Fischer Betascope 2040/2060 Coating thickness computer & non destructive coating measurement instrument & many jigs and extras	all for £2000
Fluke 5200A Programmable AC calibrator	POA
Fluke 8010A Digital multimeter	£125
Fluke 8922A True RMS voltmeter	POA
Fluke 95020 Current shunt - FTM - Fast transient monitor	POA
Gay Milano FTMIC/FTM3C - FTM - Fast transient monitor	£250
General Rad 1658 LCR Digibridge	£250
Hewlett Packard 1807B Display unit with 8755B swept. amp. an.	£350
Hewlett Packard 436A Power meter + 8481A sensor	£175
Hewlett Packard 3200B VHF oscillator, 10-500MHz	£150
Hewlett Packard 3400A RMS voltmeter	£250
Hewlett Packard 3403C True RMS voltmeter	£175
Hewlett Packard 3406A Broadband sampling voltmeter	£350
Hewlett Packard 3437A System voltmeter	£200
Hewlett Packard 3438A Digital multimeter	£100
Hewlett Packard 3476A Digital multimeter, 4 wire system, 1EEE	£650
Hewlett Packard 3490 Digital multimeter	POA
Hewlett Packard 3702B/3705A/3710A/3716A Microwave link analyser	£1500
Hewlett Packard 3730A Down converter (with 3736A or 3737A)	£200
Hewlett Packard 3760/3761 Data gen + error detector	each £300
Hewlett Packard 3762/3763 Data gen + error detector	each £350
Hewlett Packard 3779A Channel selector	£250
Hewlett Packard 3779A Primary multiplex analyser	£800
Hewlett Packard 400E/F AC voltmeter	£150
Hewlett Packard 4193A Vector impedance meter	£3500
Hewlett Packard 4204A Oscillator 10Hz - 1MHz	£250
Hewlett Packard 435A Power meter (less sensor)	£350
Hewlett Packard 456A AC current probe	POA
Hewlett Packard 415E SWR meter	£275
Hewlett Packard 5335A Universal counter with 1EEE	£1800
Hewlett Packard 5342A Microwave freq. count. 18GHz	£1500
Hewlett Packard 59501B HP IB isolated D/A power supply programmer	£150
Hewlett Packard 6181C D.C. current source	£150
Hewlett Packard 7402 Recorder with 17401A x 2 plug-ins	£300
Hewlett Packard 8005B Pulse generator	£250
Hewlett Packard 8011A Pulse gen. 0.1Hz - 20MHz	£500
Hewlett Packard 8012B Pulse generator	£750
Hewlett Packard 8013B Pulse gen. 1Hz - 50MHz	£500
Hewlett Packard 8406A Frequency comb. generator	£450
Hewlett Packard 8443A Tracking gen./counter with 1EEE	£700
Hewlett Packard 8445B Automatic presetter 110MHz	£350
Hewlett Packard 8601A 110MHz Gen./swapper	£500
Hewlett Packard 8620C Sweep oscillator mainframe	£650
Hewlett Packard 8654B 10 - 520MHz Sig. Gen.	£400
Hewlett Packard 8750A Storage normaliser	£250
Hewlett Packard 938A Freq. doubler	£825
Hewlett Packard 9640B with opt 001	£400
Kelthley 197 20MHz with 1EEE	£400
Lyons PG73N/PG75/PG2B/PG Pulse generator	from £225

Marconi 2019A 80kHz - 1040MHz sig. gen.	£1850
Marconi 2022D 10kHz - 1GHz sig. gen.	£1950
Marconi 2306 Programmable interface	£500
Marconi 2337 Automatic dist. meter	POA
Marconi 2356 20MHz level oscillator	£300
Marconi 2432A 500MHz digital freq. meter	£200
Marconi 2830 Multiplex tester	£1250
Marconi 2831 Channel access switch	£500
Marconi 6920 Power sensor	£400
Philips PM 2525 Multimeter WF 1EEE	£850
Philips PM 5167 10MHz functiongen.	£400
Philips PM 5190 LF synthesizer w/HP GPIB	£800
Philips 5390 1GHz signal gen.	£1250
Philips PM 5519 Colour TV pattern gen.	£600
Philips PM 5716 Pulse generator high freq. mos	£650
Philips PM 6672 1GHz timer/counter WF 1EEE	£500
Philips PM 8272 XYT chart recorder	£350
Photodyne N90 Fibre optic attenuator	£800
Projectina CH9345 Microscope	£350
Racal Dana 202 Logic analyser + 68000 disassembler	£250
Racal Dana 3100 40-130MHz synthesiser	£750
Racal Dana 5002 Wideband level meter	£650
Racal Dana 5003 Digital m/meter	£150
Racal Dana 9000 Microprocessing timer/count. 52MHz	£250
Racal Dana 9081 Modulation meter	£225
Racal Dana 9081 Synth. sig. gen. 520MHz	£550
Racal Dana 9084 Synth. sig. gen. 104MHz	£450
Racal Dana 9242D Programmable PSU 25V-2A	£300
Racal Dana 9246S Programmable PSU 25V-10A	£400
Racal Dana 9303 True RMS/RF level meter	£650
Racal Dana 9341 LCR databridge	£250
Racal Dana 9500 Universal timer/counter 100MHz	£200
Racal Dana 9917 UHF frequency meter 560MHz	£175
Racal Dana 9919 UHF frequency meter 1GHz	£275
Rohde & Schwarz BN36711 Digital Q meter	£400
Solartron Schlumb 1170 Freq. response analyser	£500
Tektronix TMS03, SG503, PG506, TG501 Scope calibrator	£2200
Tektronix 834 Data comms analyser	£500
W&G SPM12 Level meter 200Hz-6MHz	£500
W&G PS12 Level generator 200Hz-6MHz	£500
Watanabe WTR213 3 pen plotter	£250
Wavetek 157 Programmable waveform synthesiser	£300
Wayne Kerr B424/N LCR Component meter set	£200
Weiler D800/D801 Desoldering station	£175
Weiler D900 Desoldering station	£150
Wiltron 352 Low freq. differential input phase meter	£350

SPECIAL OFFERS - Phoenix 5500A Telecoms analyser, ex. demo, as new with 12 months calibration + 12 months guarantee fitted with V24 interface. A variety of interface options available - Ring/Fax for details. Navtel 9440 Protocol analyser, ex. demo, as new £8000 new - cost now £3500. Navtel 9410 PCB based protocol analyser ex. demo, as new £3000 new - cost now £1500.


MANY MORE ITEMS AVAILABLE - SEND LARGE S.A.E. FOR LIST OF EQUIPMENT ALL EQUIPMENT IS USED - WITH 30 DAYS GUARANTEE. PLEASE CHECK FOR AVAILABILITY BEFORE ORDERING - CARRIAGE & VAT TO BE ADDED TO ALL GOODS

Next Month *September* issue

On Sale August 25


Free to all UK readers: The latest Zetex power transistor technology in their world famous E-Line package. We are giving away two top quality ZTX689B devices. Each 20V npn transistor is capable of passing 3A continuous current, 8A peak, with a low saturation voltage – just 0.5V at 1A. The current gain of these small devices is outstanding: a guaranteed minimum of 400 at 2A collector current.

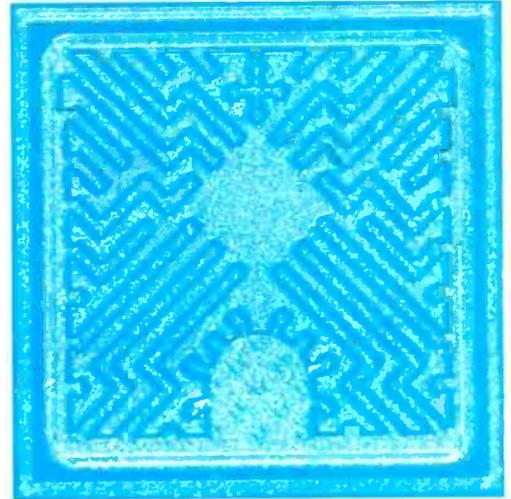In the same issue: Circuits for rms conversion. There are only two types of circuit which will measure the power content of a signal directly. You can either amplify it and use the resulting output to heat a thermocouple, or you can process the signal with a root mean square algorithm. Danny Ayers tells all.



FREE with *October* issue

On Sale September 29

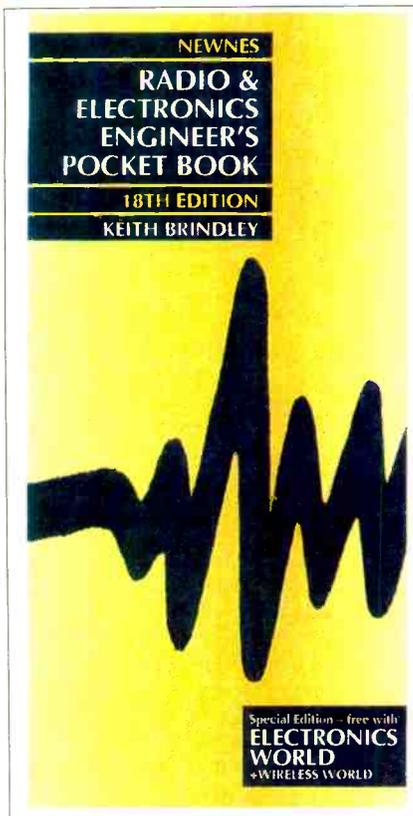

The Radio & Electronic Engineer's Pocket Book. This is a special edition edited to include the most frequently needed and up to date information for electronics engineers. If you work with applied electronics, then you will need this book.

In the same issue: Work with International Rectifier's latest power control chip using a sample device supplied through the magazine and enter our free design competition.

To My Newsagent

Please reserve the September 1994 issue of Electronics World and every issue until further notice.
I will collect/please deliver to...

Name

Address

.....

.....

.....

Imagine a semiconductor technology which delivers VLSI density from transistors with a transition frequency greater than 100GHz, yet costs virtually no more to process than standard cmos. The new silicon-germanium IC manufacturing process suggests that it might just deserve the hyperbole "the most significant development in electronics since cmos".

Jon Mosely investigates.

Silicon-germanium: the integrated future?


In essence, silicon-germanium (or SiGe) is a slightly tweaked silicon process, that improves both the gain and the speed of transistors. In fact, it is fast enough to replace gallium arsenide in most commercial applications, including digital cellular telephones and wireless lans (frequencies up to 3GHz). Finally, as a silicon process, it can be made inexpensively on existing process lines and may easily be integrated with conventional circuits such as sub-micron vlsi cmos.

This means that a single chip cellphone, integrating DSP, mixed-signal and rf stage into one chip, is quite conceivable. Better still, it could be quite affordable.

More specifically, the first results published have included heterojunction bipolar transistors with f_T as high as 110GHz, almost twice those reported for any conventional silicon process and comparable to GaAs. Perhaps as importantly, the beta-early voltage product (βV_{ce}) of these transistors is an impressive 48,000. This measures the quality of a current source, a key property of an analogue circuit; to be useful for precision tasks the product must reach at least into the thousands). In other words, the speed has not been achieved at the expense of having worthwhile devices.

To give an idea of just how radical this leap in performance is Fig. 1 is a graph of the fastest Si transistors reported anywhere; and shows how much faster SiGe is.

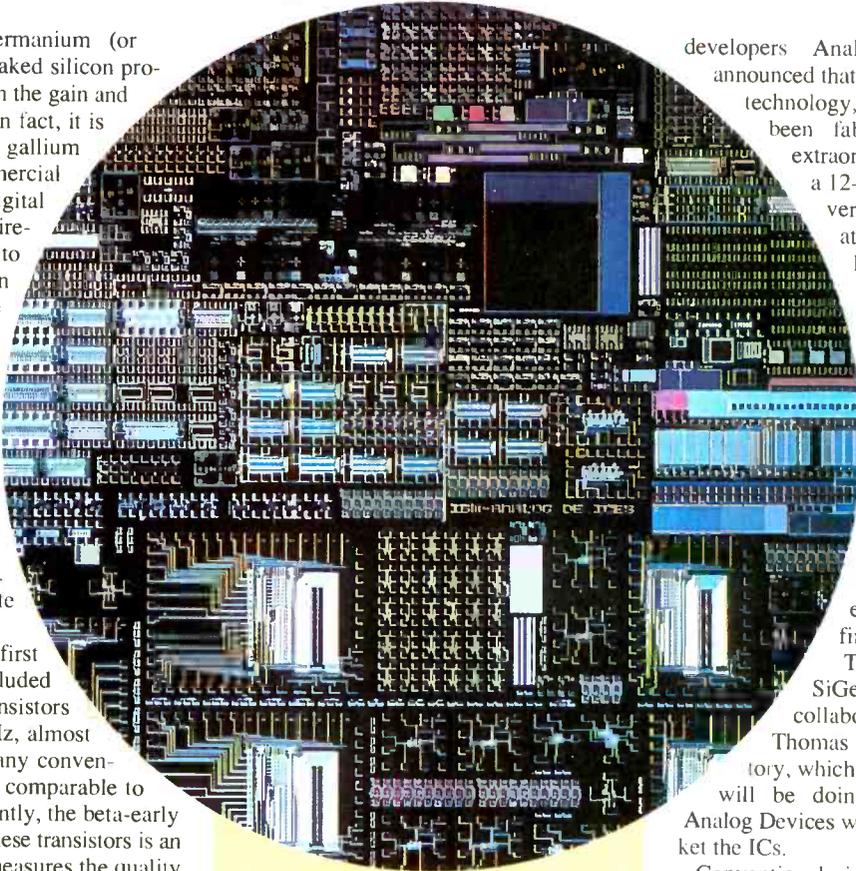The technology has been discussed for a few years, but became real when joint process



"This is about two and a half times faster than the fastest commercially available silicon DAC"

developers Analog Devices and IBM announced that not only was SiGe a viable technology, but that a complex IC had been fabricated which delivered extraordinary results. The part was a 12-bit digital to analogue converter which could be clocked at 1GHz, and drew less than 1W. This is about two and a half times faster than the fastest commercially available silicon DAC.

The fact that an IC of such density (3000 devices) had been made, and reportedly with high yields, obviously made SiGe a lot more than a vague possibility or laboratory curiosity, and the further results that have emerged since seem to confirm its potential.

The commercialisation of SiGe technology results from a collaboration between IBM's Thomas J Watson research laboratory, which developed the process and will be doing the manufacture, and Analog Devices which designs and will market the ICs.

Conventional circuits are made with pure silicon/silicon junctions (homojunctions); adding a second material (in this case a silicon/germanium alloy) forms a heterojunction, with a natural electric field generated where the two different materials meet. By controlling the concentration of germanium, a graded junction can be built (Fig. 2) with a profile that affects the properties of the transistor, increasing both gain and speed. This bandgap engineering improves device performance. Germanium has a smaller bandgap than silicon; introducing a small amount of it reduces

• 75 GHz f_T in non-self-aligned SiGe HBT (1990)
 -2x better than Si BJT!

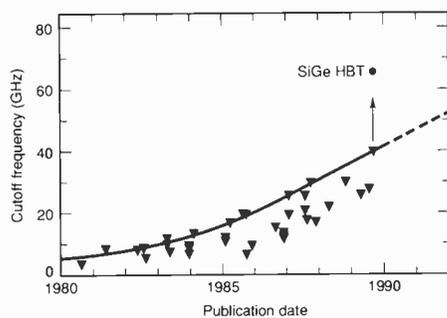


Fig. 1. Trends in cut off frequency. SiGe is a huge leap in speed over the fastest Si transistors reported.


the transistor's base bandgap and increases electron injection, increasing gain, B. The increased gain allows a more heavily doped base, lowering the base resistance. Finally, the bandgap can be controlled to generate an electric field as great as 30,000V/cm across the base, accelerating the electrons and reducing their transit time through the transistor.

In effect, the heterojunction 'tilts' the circuit, forming a slope down which electrons can slide more quickly than before. This reduces the energy and time required to move from one side of the junction to the other. Some engineers have referred to the addition of germanium as 'electron grease' since it eases the movement of the particles.

The concept has been known since the 50s, but the difficult part has been in successfully fabricating a heterojunction. Although silicon and germanium share the same crystal structure, their lattice spacings differ: Ge's is 4% greater than that of Si. If the pure materials were simply deposited together, this mismatch would cause strain, forming defects and preventing circuits from operating. By analogy, if a nut and bolt are of different screw pitches it may be possible to force a match, but the threads will be stripped. This mismatch frustrated engineers trying to build SiGe heterojunction devices.

The answer was developed by Dr Bernard

Fig. 2. SiGe HBT Band Diagram. The germanium is implanted across the base of the transistor, with concentration rising toward the collector. This graded junction causes a drift field which accelerates electrons through the transistor.

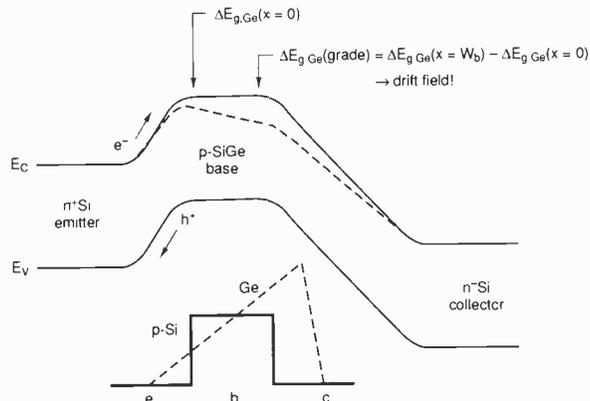

- Oxide deposition and planarization
- W damascene stud formation
- AlCu metal re

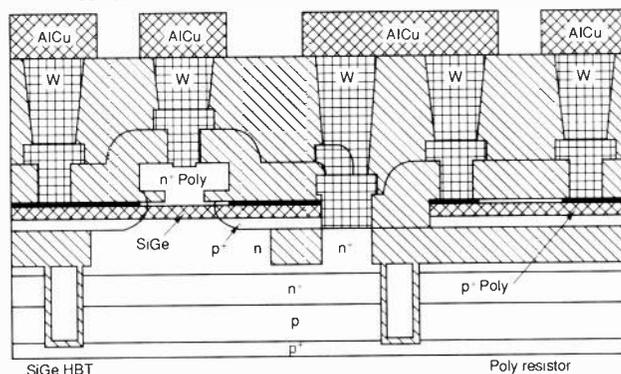


Fig. 3. The structure of an SiGe HBT

Myerson, IBM Research Fellow who leads the IBM SiGe team.

The approach uses a silicon-germanium alloy, which has a lattice spacing part-way between the two substances, reducing the mismatch and strain. As a result, the heterojunction can be made between the pure silicon and the alloy without defects, although the lattice is still under some stress.

The junction is built up with low temperature ultra high vacuum chemical vapour deposition (UHV/CVD), which uses a mixture of gases to leave a thin, highly controlled, layer of atoms on top of a silicon substrate. Conventionally CVD requires high tempera-

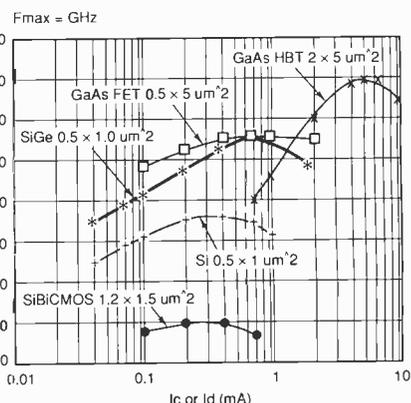
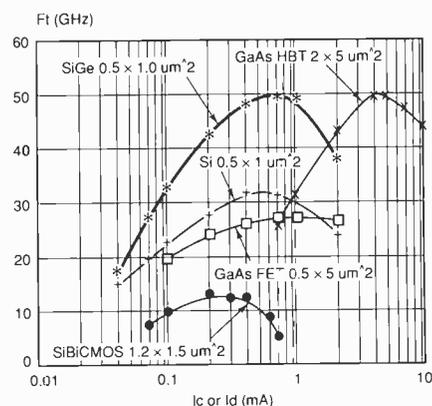


Fig. 4 and 5 show the transition frequency (FT) and maximum oscillation frequency (Fmax) of the SiGe HBTs and compares this to alternative processes.

Table 1. Test results for competing rf technologies

	SiGe HBT ADI/IBM	Si BJT IBM	AlGaAs/GaAs HBT Hitachi	GaAs mesfet M/A-COM	Si BJT bicmos
Device minimum size (μm)	0.5 x 1	0.5 x 1	2 x 5	0.5 x 5	1.2 x 1.5
BV_{CEO}/BV_{DS} (V)	4	4	15	8	6
f_T (GHz)	50	32	50	30	13
F_{max} (GHz)	55	35	70	60	11
G_{max} (dB)	@2GHz: 28	24	19	20	17
	@10GHz: 16	11	13	13	1
NF min (dB)	@2GHz: 0.5	-	1.5	0.3	-
	@10GHz: 0.9	-	-	0.9	-
-1dB p_{out} (dB)	9	9	6	12	9
Added efficiency (%) @3V	70	-	60 @5V	70	40
$1/f_{corner}$ (kHz)	0.1-1	0.1-1	1-10	10,000	0.1-1

Source: Kerrmarec et al, IEEE MTT-S, San Diego May 23-25 1994

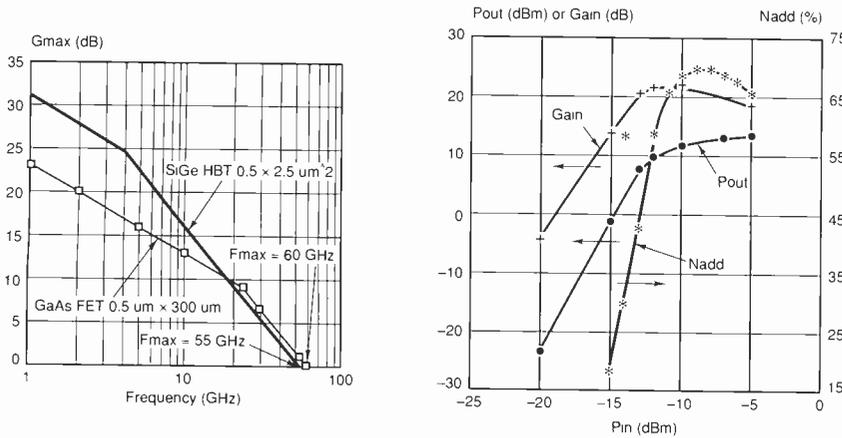


Fig. 6 and 7 show the gain and efficiency of the SiGe HBTs and compares this to alternative processes.

- Highest published level of SiGe HBT integration achieved to date
- 2854 SiGe HBT's
- 1465 polysilicon resistors
- 2 levels of metallization

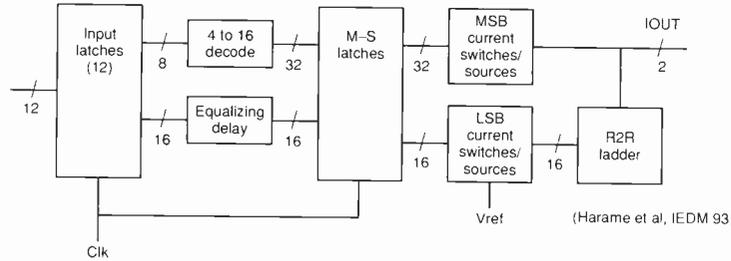


Fig. 8. 12-bit 1GHz digital to analogue converter: block diagram.

- Multiplexed between all 1's and all 0's at the input

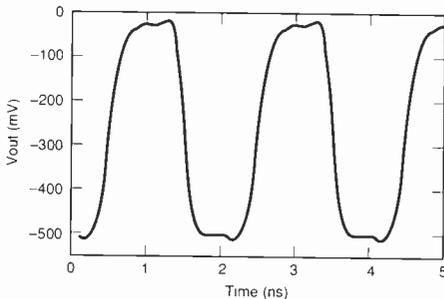


Fig. 9. 12-bit 1GHz digital to analogue converter: output waveform.

"The key fact of SiGe is not merely its speed, but that such speed can be achieved from a standard silicon process using existing equipment"

tures, but this will not work for SiGe, as the strained material will fail. By developing their own innovative CVD process machinery, Dr Myerson and his team were able to perform the deposition at temperatures low enough for the circuit to endure.

Figure 3 shows the structure of a complete SiGe HBT. While researchers outside IBM (including Motorola, M/A-COM, NEC and Daimler Benz) are also working on SiGe, they are achieving fewer devices and lower yields. In addition, most are working on classic mesa structures, which are incompatible with conventional processing techniques.

The first devices were fabricated in 1989, and even those trial parts achieved speeds more than twice of the fastest comparable silicon device (f_T of 75GHz). More recent results have achieved even higher speeds – f_T up to 117GHz.

Figures 4 and 5 show the transition frequency and maximum oscillation frequency (f_{max}) of SiGe HBTs and compares this to alternative processes.

Not only are these fast transistors, they are also exceptional analogue transistors. Their βV_A is at least an order of magnitude better than the fast silicon processes used today. The βV_A of a low voltage, high speed silicon device would typically be under 1000 compared to the 48,000 achieved by SiGe.

The gain and noise performance are also good: 25dB gain at 2GHz with a corresponding noise figure of 0.5dB at 2GHz and low 1/f noise. Finally, the process seems to achieve good efficiency (critically important for portable and battery powered equipment), with

a 70% power added efficiency at 900MHz and operation from either 3V or 1.5V supplies. (Figs 6 and 7)

SiGe transistors are comparable in speed to gallium arsenide mesfets or HBTs. However, unlike GaAs, the SiGe devices have a very low 1/f corner frequency – between 100Hz and 1kHz – allowing them to be used for dc coupled amplifiers or zero IF down converters.

There are some aspects which are difficult to determine about a technology which has hardly moved out of the conference circuit. One concern is reliability. Due to the strain in the lattice, it is possible that devices will not cope well with radiation or high temperatures. However, this is only speculation – the experimental results have not been revealed.

Breakdown voltage – just 4V between collector/base – may be more problematic. This allows a maximum swing of just 8V. While adequate for low power signal processing or receiver circuits, it looks very low when discussing a power amplifier. Even for battery powered systems, the power amplifier still needs a good voltage swing and 8V is marginal. When you consider battery over-voltage or antenna mismatch, it is probable that an rf PA design would not be practical in SiGe.

Commercially, the key fact of SiGe is not merely its speed, but that such speed can be achieved from a standard silicon process using existing equipment and compatible conventional cmos. IBM will be manufacturing the new devices on a full-size 8in wafer line. As a result the volumes and economies of scale are immense.


Because the process is based upon a silicon substrate, it is easy to combine it with conventional circuits: for example sub-micron cmos. This would allow single chip cellular radios using SiGe for the front end radio stage, and cmos for the complex digital and mixed-signal stages.

The first SiGe product will be a version of the dac, and this will be available at the end of the year. Apparently, it is now being sampled for use in a fibre to the kerb application in Eastern Europe; a number of channels are combined and digitised before being sent down a fibre-optic link at rates of 9Gbits/s. At the kerbside they are received and fed into the 12-bit dac, to produce a 750MHz bandwidth analogue signal. Figure 8 shows the block diagram while Fig. 9 gives the output waveform for toggling between 0 and full scale at a rate of 1GHz. Incidentally, the dac may be faster than 1GHz but, at the time these results were released, that was the maximum speed of the available test equipment!

Subsequent commercial products are likely to be highly integrated blocks for use in wireless systems, perhaps even complete rf transceivers in a chip. This would combine up-and down-converters, frequency synthesisers, mixers and amplifiers into a single block.

Silicon germanium has the potential to redefine high speed semiconductors. The only question is when it will be solid enough for an appearance in catalogues? ■

Applying crystals

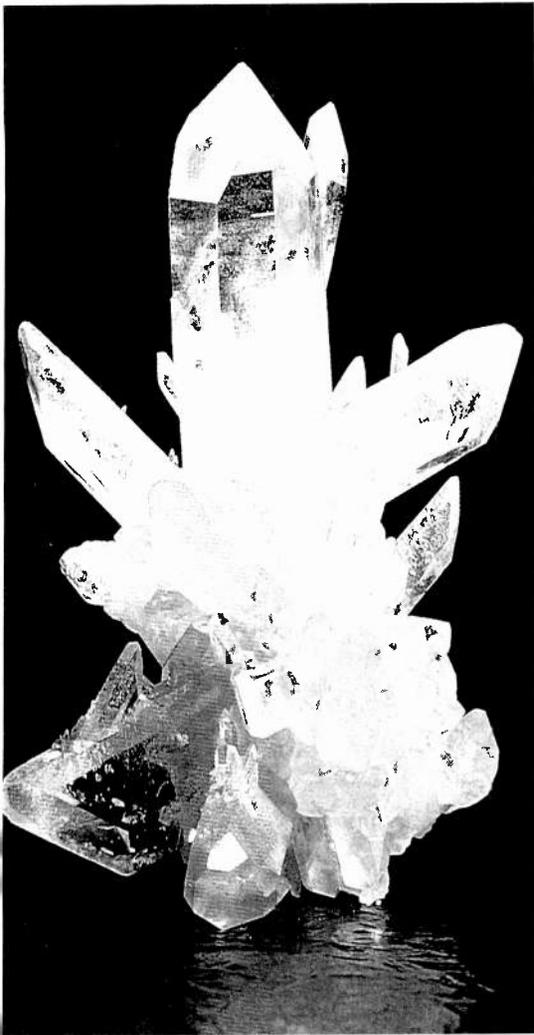

This round up of general-purpose crystal oscillator designs – both discrete component and logic-gate based – satisfies frequency generation requirements from kilohertz to 200MHz. By Martin Eccles.

Quartz crystals used for time keeping and frequency references combine three key features – extremely high Q, small physical size relative to alternative timing devices with the same performance, and excellent temperature stability.

Frequency stability of a crystal is limited in the short term by its temperature coefficient and in the long term by ageing. Quartz crystals with an AT cut generally provide the best temperature coefficient and usually have stability tolerances of $\pm 0.0025\%$ or $\pm 0.005\%$ from -55 to 105°C .

Between 1 and 200MHz, AT-cut crystals are normally chosen. They represent the best compromise between temperature stability and frequency accuracy and frequency pulling capability. Above around 27MHz however, AT crystals are normally only available for use in overtone mode. This is restrictive since overtone oscillators are more difficult to design and are prone to spurious responses. Fig. 1.

Recently, BT-cut crystals have been developed to overcome the overtone problem.

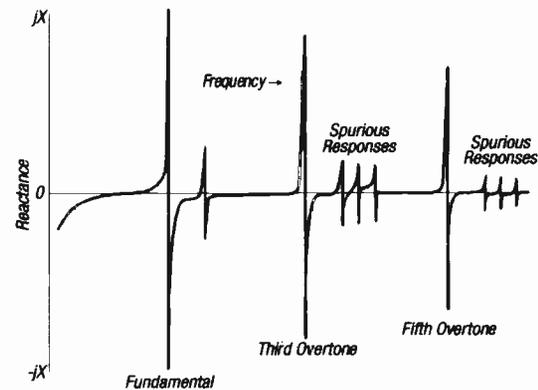


Fig. 1. Operating a crystal at an overtone of its fundamental is tricky. The oscillator circuit needs to be carefully designed to make sure that the spurious response points have no influence on the final output signal.

These operate in fundamental mode up to 46MHz – almost double the frequency of traditional AT-cut alternatives. In addition, the BT-cut devices can operate in overtone mode.

Load capacitance and frequency pulling

Near a crystal's resonant frequency, lowering capacitive loading on the device increases its output and frequency, Fig. 2. In addition to any external loading, the crystal has its own shunt capacitance, C_0 , which is typically between 3 and 15pF. When making calculations, this capacitance should be added to that of the load.

Figure 3 shows how far the frequency of a typical crystal can be pulled by changing its load capacitance. The degree of pulling for a given configuration is obtained by:

$$\frac{C_1 10^6}{2(C_0 + C_L)^2}$$

Free quartz-crystal

In an exclusive offer to *Electronics World & Wireless World* readers, specialist quartz crystal manufacturer IQD is giving away designer's packs comprising four popular crystals and data.

By simply filling in and returning the reply card located between pages 672 and 673

designer's pack

Sample pack parts

Part	Description	Package	Cut	Use and typical circuit
A160K	15MHz	HC49/4H	AT	Microprocessor clocking, Fig 6
A123A	4194.304kHz	HC49	AT	Timers and RTCs, Fig. 14 lower
A103A	32.7680kHz	3X8	Tuning fork	Clocks/watches, Figs 13 & 14 lower
A166A	32MHz	HC49	AT 3rd o/t	Microprocessor clocking, Fig. 7

of this issue, the first 300 readers responding will receive this designer's pack – completely free of charge.

Please note that all correspondence relating to the offer should be directed to IQD. The company's address is given at the end of this article.

where C_1 is motional capacitance, G_L is load capacitance and C_0 is shunt capacitance. Typical values for motional and inherent shunt capacitances are shown in **Table 1**.

All crystals operate at series resonance. The term parallel resonant is often used to describe a crystal designed to handle a high load

impedance across its terminals. Series resonance exists within the crystal, whereas parallel resonance exists only as a crystal measurement phenomenon.

Using quartz crystals

For a circuit to oscillate, it has to have both positive feedback and a loop gain greater than unity. Without any other frequency-sensitive elements in its oscillator circuit, a crystal will oscillate in its fundamental mode. Frequency dependent components need to be added to the circuit to force the crystal to oscillate at an overtone.

Closing an oscillator's feedback loop causes sine wave oscillations which gradually build up, clip, and approach a square wave as the circuit overloads. Crystal oscillators can usually provide either a sine or square wave. The driving signal is usually a square wave while the crystal output is always a sine wave. Either of these waveforms can form the output.

Below 150kHz. Because equivalent series resistance of a crystal is high at low frequencies, high amplifier gain is needed. In **Fig. 4**, which is optimised for 50kHz, the gain problem is solved using dual cascaded common-emitter stages.

Two diodes limit crystal drive level to avoid damage, while tuning in the middle transistor's collector adds selectivity. For parallel resonance, the adjustable capacitor provides calibration. For series calibration, replace the trimmer with 1nF and trim via the inductor.

150 to 550kHz. For this frequency range, DC and CT-cut crystals are normally used with a selective amplifier to suppress unwanted modes. **Fig. 5**. Initially, the crystal is shorted and frequency is adjusted to near the crystal frequency via the inductor. Afterwards, the inductor can be used for trimming.

Series-resonance is preferable but a parallel-resonant device can be used if the first capacitor is replaced by one with a value equal to the crystal load capacitance.

0.95 to 21MHz. Circuitry in **Fig. 6** is designed for high-stability AT-cut crystals calibrated at parallel resonance and operating in fundamental mode.

15 to 105MHz. At higher frequencies, crystals specially designed to oscillate at their overtones are mainly used. Examples of third and fifth overtone oscillators are shown in **Figs 7**

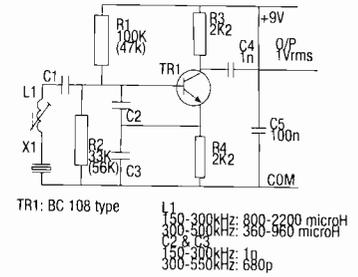


Fig. 5. Relative to circuitry needed for oscillators working at under 150kHz, this circuit for 150 to 550kHz is much simpler.

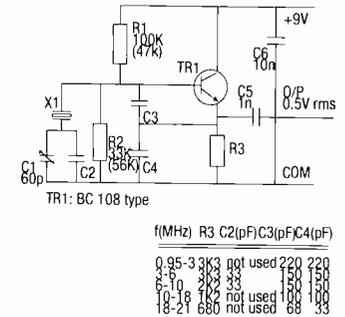


Fig. 6. Designed for use with high-stability AT-cut crystals, this oscillator operates between 0.95 and 21MHz.

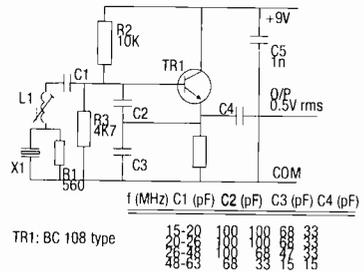


Fig. 7. Third-overtone crystal oscillator configuration for frequencies from 15 to 63MHz.

& 8 respectively. The first example handles crystals from 15 to 63MHz while the second is suitable for 50 to 105MHz. As with **Fig. 5**, the crystal is initially shorted and the oscillator set to run as near as possible to the crystal frequency via the inductor. After removing the short, the inductor can be used for trimming.

By adding a tuned circuit at twice or three times the crystal frequency in the transistor's

Table 1. Using motional and inherent shunt capacitances of a crystal, it is possible to work out how far the device's frequency can be pulled.

Frequency (MHz)	Vibration mode	C_1 (fF)	C_0 (pF)
1 to 2	fundamental	5-8	3
2-4	fundamental	6-12	3
4-6.5	fundamental	8-20	5
6.5-30	fundamental	16-25	6
21-150	3rd o/tone	1-2.5	6
60-150	5th o/tone	<0.7	6
85-210	7th o/tone	<0.4	6

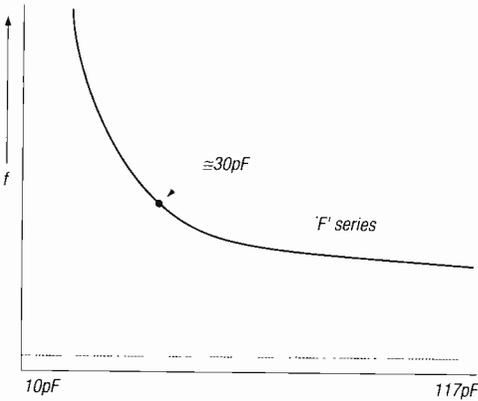


Fig. 2. Lowering capacitive loading on a crystal increases its output frequency.

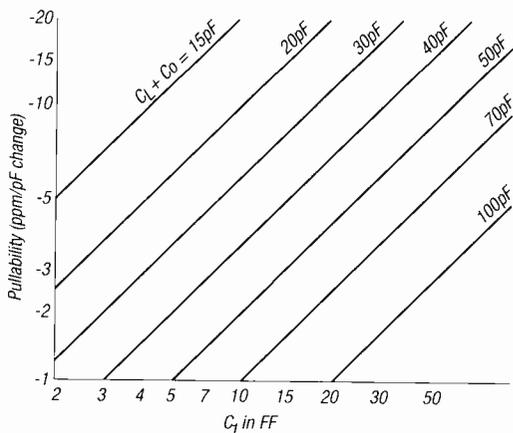


Fig. 3. When estimating how far a crystal's frequency can be pulled by changing its load capacitance, C_L , both package shunt capacitance, C_0 , and motional capacitance C_1 need to be taken into account.

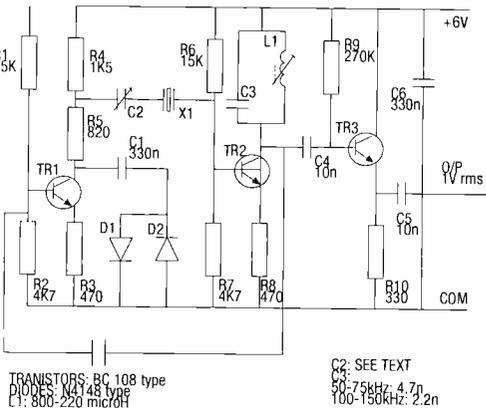


Fig. 4. At frequencies below 150kHz, equivalent series resistance of a crystal is high so oscillator circuits need to have a high gain.

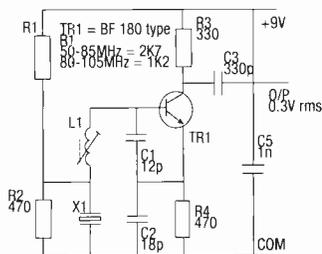


Fig. 8. By driving a crystal into its fifth overtone mode, this oscillator circuit extends useful frequency range to cover 50 to 105MHz.

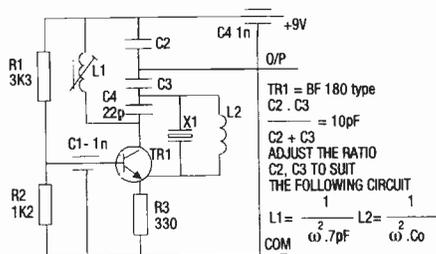


Fig. 9. Above 105MHz, stray capacitances make designing a reliable oscillator difficult. To help prevent oscillation not controlled by the crystal, this circuit uses a small inductor in parallel with the crystal to tune out its static capacitance.


Crystal characteristics

A crystal's equivalent circuit is shown below. Series combination R_1 , C_1 and L_1 represent the quartz while C_0 is shunt capacitance of the electrodes in parallel with capacitance of the can.

Reactance versus frequency is also shown. Resonant frequency F_s is given by;

$$F_s = \frac{1}{2\pi\sqrt{L_1C_1}}$$

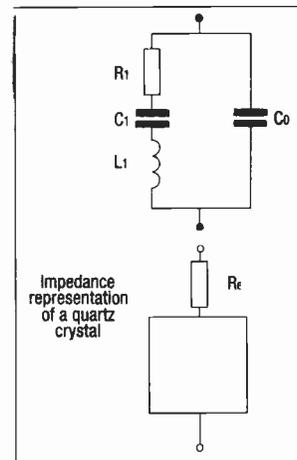where F_s is series resonant frequency in hertz, L_1 is motional arm inductance in henries and C_1 is motional arm capacitance in farads.



Typical crystal parameters

Parameter	200kHz Fundamental	2MHz	30MHz 3rd o/tone	90MHz 5th o/tone
R_1	2k Ω	100 Ω	20 Ω	40 Ω
L_1	27H	520mH	11mH	6mH
C_1	0.024pF	0.012pF	0.0026pF	0.0005pF
C_0	9pF	4pF	6pF	4pF
Q	18x10 ³	18x10 ³	18x10 ³	18x10 ³

collector, it is possible to extract harmonics of the crystal frequency. This is a simple and economical way of making a vhf oscillator.

Above 105MHz. Reactance from stray circuit capacitances can make high-frequency oscillators difficult to design. In the solution shown in Fig. 9, a small inductor is added over the crystal to compensate for its inherent capacitance, which may cause undesirable effects. Tuning is carried out via the other inductor or by inserting a variable reactance in series with the crystal.

20-200MHz. Parasitics can be eliminated by using an oscillator relying on the crystal's harmonics. Figure 10 a) is such an example for operation at around 20MHz. In it, the crystal is tapped into the capacitive side of the LC tank.

Four signal diodes provide base biasing. Emitter output driving the crystal is 25 Ω while the crystal load is around 35 Ω . Figures 10 b,c) show values needed to make the same circuit operate at 50 and 100MHz respectively.

Oscillators from logic gates

Designs for oscillators using standard ttl logic gates as their active components are shown in Fig. 11. With nand gates, unused inputs should be tied to the positive rail while with nor gates spare inputs should be grounded.

In Figs 11 a,b), for frequencies of less than 1MHz and 1-4MHz respectively, the fixed capacitors are best determined experimentally; the dotted component may not be needed at all. Figure 11 c) is for frequencies from 4 to 14MHz.

Jitter can be a problem in ttl-based oscillators due to random phase shift within the IC. In addition, the relatively high crystal drive

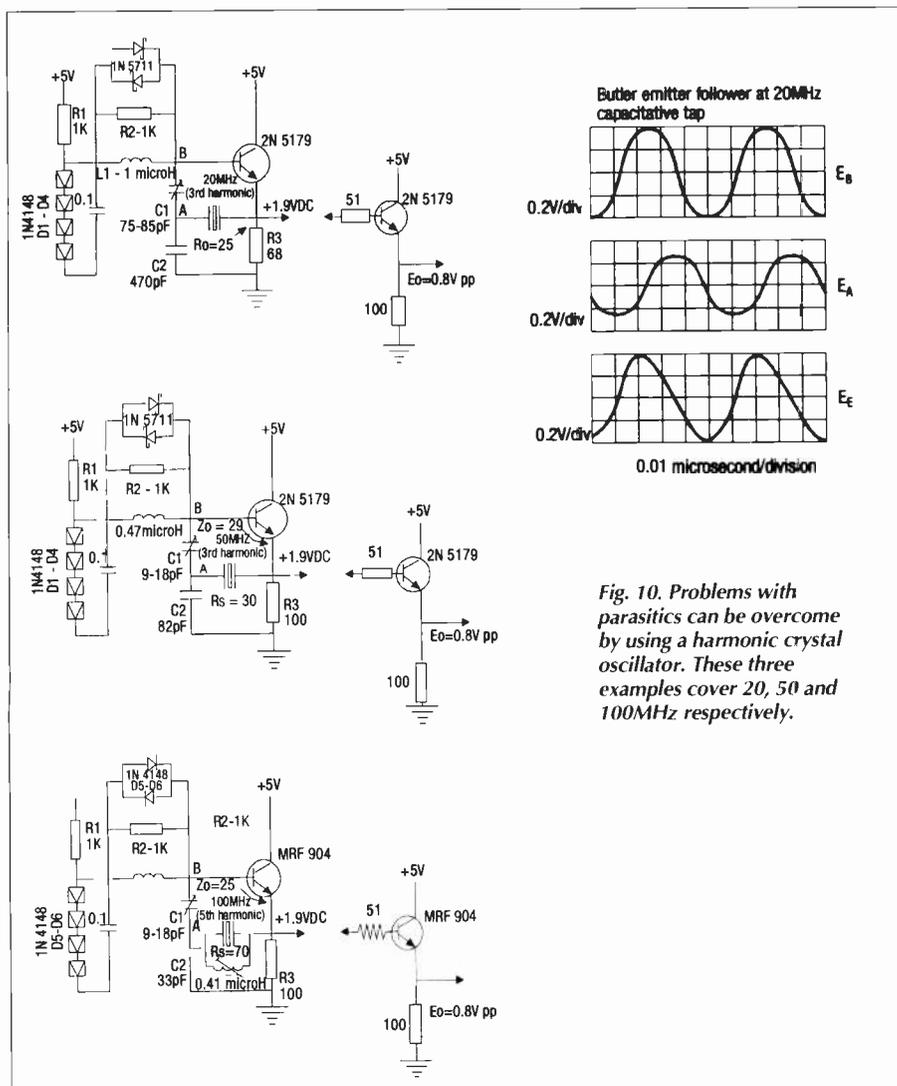


Fig. 10. Problems with parasitics can be overcome by using a harmonic crystal oscillator. These three examples cover 20, 50 and 100MHz respectively.

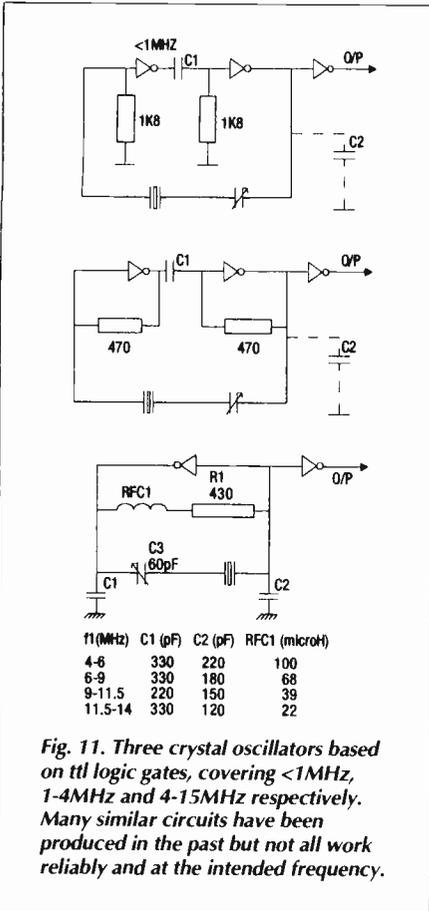


Fig. 11. Three crystal oscillators based on ttl logic gates, covering <math>< 1\text{MHz}</math>, 1-4MHz and 4-15MHz respectively. Many similar circuits have been produced in the past but not all work reliably and at the intended frequency.

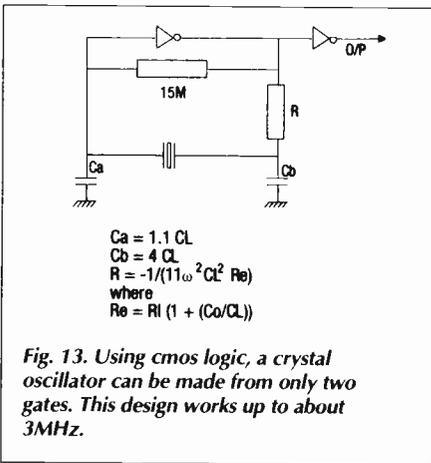


Fig. 13. Using cmos logic, a crystal oscillator can be made from only two gates. This design works up to about 3MHz.

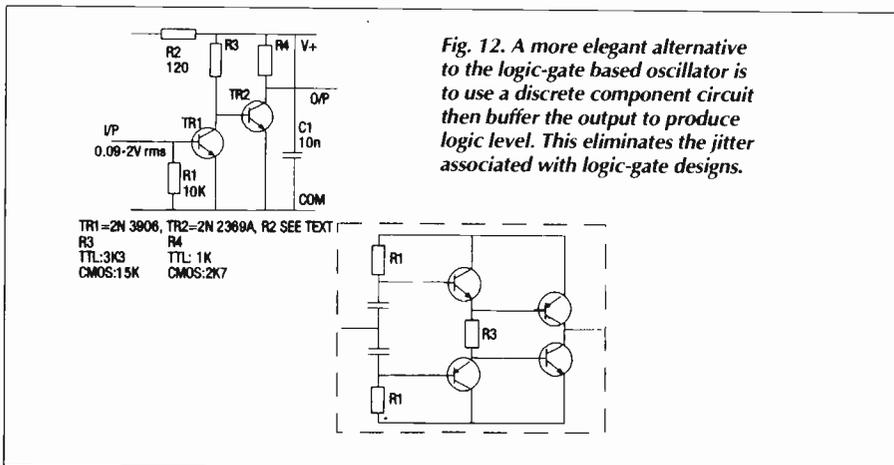


Fig. 12. A more elegant alternative to the logic-gate based oscillator is to use a discrete component circuit then buffer the output to produce logic level. This eliminates the jitter associated with logic-gate designs.

level can affect long-term stability. A discrete component oscillator followed by a buffer such as those in Fig. 12 provides better stability.

In the first buffer, the resistor in the supply rail decouples the oscillator stage. The complementary buffer has more active components but offers faster switching and improved capacitive load driving. Note that drive level from some of the preceding discrete component oscillators may need reducing to interface to these buffers.

Cmos oscillators

A typical cmos gate oscillator with the crystal forming part of a pi network is shown in Fig. 13. This design will work up to 3MHz but values found via the formulas on the diagram may need adjusting to take account of stray capacitance due to component layout. Resistor R is expressed in terms of crystal load capacitance C_L and its equivalent series resistance at parallel resonance R_e .

For operation above 3MHz, resistor R is omitted and the crystal connected directly between the inverter input and output. Low values of crystal load capacitance, of say 12pF, and/or a high supply voltage may be needed for reliable operation.

Reducing power

Timing, clock and calendar circuits often rely on battery-powered frequency references. As a result, power consumption of the frequency reference is important.

Two commonly used timing crystals, both implemented in oscillators designed around a single logic gate, are shown in Fig. 14. Given a 5V supply, the 4000 series cmos gate with a 32kHz watch crystal consumes only 30µA. For the same supply, the HC gate alternative increases current to 1300µA, mainly due to its higher switching frequency.

Even though the HC circuit appears much worse in terms of power consumption, it can still provide significant advantages in battery-powered applications – in addition to the benefits of its higher operating frequency.

Firstly, during tests based on a National Semiconductor 74HC4060 device, oscillation started at 1.1V. The traditional cmos 4060 needs 3V. And at 1.5V, the HC-based oscilla-

tor consumed less than 5µA, Table 2. As a bonus, the HC produced much faster edges than the 4000-series IC.

Supply (V)	Consumption (µA)	
	CD4060	74HC4060
1.1	-	2.3
1.5	-	4.8
2	-	34.9
2.5	-	117
3	7	256
3.5	7	449
4	9	687.3
4.5	20	979
5	31	1325
5.5	46	1712
6	65	2148
8	180	-
10	362	-
12	603	-
14	895	-
16	1252	-

tor consumed less than 5µA, Table 2. As a bonus, the HC produced much faster edges than the 4000-series IC.

Frequency of a tuning fork watch crystal has a significant negative temperature coefficient. In a watch, this is of little consequence since human body temperature remains constant, but there are many applications where temperature coefficient does matter.

Using a more stable higher frequency crystal and dividing it down circumvents this

Inside the can

Crystal resonators rely on the piezoelectric effect of quartz.

Applying stress to a quartz crystal produces an electric charge perpendicular to the stress.

Conversely, applying an electric field causes the crystal to deflect mechanically.

In a quartz crystal resonator, a sliver of quartz is placed between two electrodes that apply the field. An ac signal applied to the electrodes causes the resonator to vibrate. When the frequency of the signal is near a mechanical resonance point of the quartz, amplitude of the vibrations becomes very large.

Resonant vibration of the quartz produces a sinusoidal electric field controlling the effective impedance between the electrodes. This impedance is strongly dependent on the excitation frequency and possesses an extremely high Q.

Fig. 14. Two timing circuits – one using a watch crystal and one a crystal with a frequency often used for real-time clocks. Although the high-speed CMOS circuit consumes more power with a 5V supply, it can have benefits in battery circuits since it operates down to 1.5V. It is also significantly more stable.

problem. With a faster crystal, it is quite easy to achieve stability of ± 10 ppm over between 0 to 50°C.

To reduce current flowing around the circuit, low-power oscillators are designed with a relatively small crystal load of typically 12pF. Using a 74HC4060, the circuit shown consumes about 2.4mA at 5V. It will start reliably with a 1.5V supply, at which point the circuit draws about 360µA.

In both circuits, NPO or COG dielectric capacitors should be used in the network around the crystal because of their low temperature coefficient.

Crystal source

Crystals suitable for all the applications described in this article – and most other quartz crystal applications – can be obtained from IQD at Station Road, Crewkerne, Somerset TA18 7AR. Tel. 0460 74433, fax 0460 72578. IQD also supplied the information upon which this article is based.


Suitable crystals for use in this circuit are IQC types A103A, A103B, A103D and A103E.

Other low frequency tuning fork type crystals should also work in this circuit although some component changes may be required.


Suitable crystal for use in this circuit is IQD type A123A. Other parallel resonant crystals (between 4.0 MHz and 20.0 MHz) could be used providing the other component values are altered to suit the load capacity of the crystal.

Series resistor R3 would generally not be required for crystals 8.0 MHz and higher in frequency.

32.768 KHz watch crystal circuit

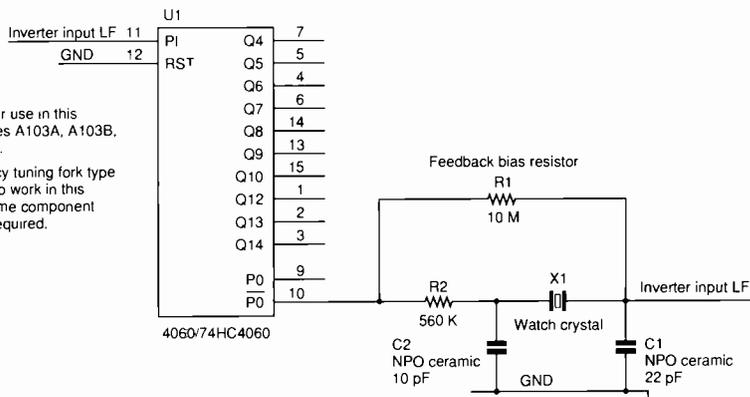

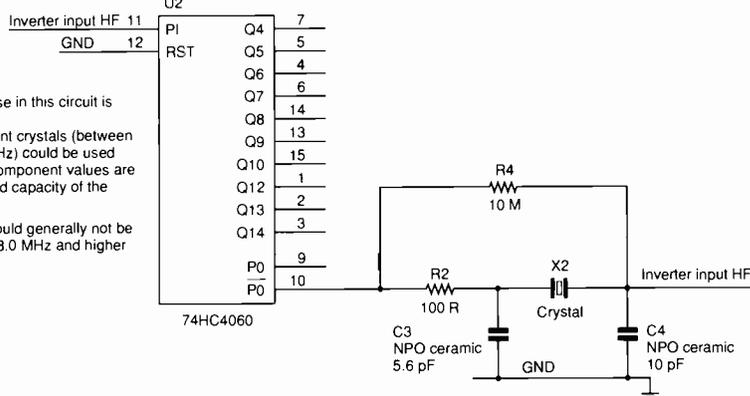4.194304 MHz at cut timing crystal circuit



M & B RADIO (LEEDS)

THE NORTH'S LEADING USED TEST/EQUIPMENT DEALER

SIGNAL GENERATORS

MARCONI 2018 80KHZ TO 520MHZ SYNTHESIZED.....	£750
MARCONI 2008 10KHZ TO 520MHZ INC RF PROBE KIT.....	£300
MARCONI 2015 2171 SYNCHRONIZER 10MHZ TO 520MHZ.....	£125
MARCONI 2016 1200HZ TO 120MHZ AM/FM.....	£200
MARCONI 2015 10MHZ TO 520MHZ AM/FM.....	£195
HP8683D 2.3GHZ TO 13GHZ OPT001/003 SOLID STATE GENERATOR.....	£4750
HP3336A SYNTHESIZER/LEVEL GENERATOR.....	£650
HP8640A 500KHZ TO 512MHZ OPT001.....	£550
HP8620C SWEEPER MAINFRAMES (AS NEW).....	£200
HP8620C/86220A RF PLUG-IN 10MHZ TO 1300MHZ.....	£1200
HP8620C/86290B RF PLUG-IN 2GHZ TO 18.6GHZ.....	£2750
HP4204A 10KHZ TO 1MHZ OSCILLATOR.....	£250
FARNELL SSG520 10MHZ TO 520KHZ SYNTHESIZED.....	£400
POLRAD 1106E1 1.8GHZ TO 4.6GHZ WITH MODULATOR.....	£400
GIGA GR1101A 12GHZ TO 18GHZ PULSE GENERATOR (AS NEW).....	£750
SAYROSA MA30 FREQUENCY OSCILLATOR 10HZ TO 0KHZ.....	£200
RHODES S SCHWARZ SMC1 4.8GHZ TO 12.6GHZ.....	£450
ADRETT 20230A 1MHZ SYNTHESIZED SOURCE.....	£195
HP8672A SYNTHESIZED SIGNAL GENERATOR 2GHZ TO 18GHZ.....	£6200
HP3586A SELECTIVE LEVEL METER 50HZ TO 32.5MHZ.....	£1850

SPECTRUM ANALYSERS

HP8903A 20HZ TO 100KHZ AUDIO ANALYSER.....	£3000
HP8565A 10MHZ TO 22GHZ SPECTRUM ANALYSER.....	£4250
B&K 2033 1HZ TO 20KHZ AUDIO ANALYSER.....	£2750
HP3581A WAVE ANALYSER 1SHZ TO 50KHZ (AS NEW).....	£850
HP3582A 0.02HZ TO 25.5KHZ DUAL CHANNEL AUDIO ANALYSER.....	£2000
HP8558B 10MHZ TO 1500MHZ WITH 1821 MAINFRAME.....	£3000
HP141T 8552B/8553B 110MHZ WITH 8443A TRACKING GENERATOR.....	£2000
HP141T 8552A/8554B 100KHZ TO 1250MHZ (AS NEW).....	£1250
HP141T 8555A/8552B 10MHZ TO 18GHZ SPECTRUM ANALYSER SUPPLIED WITH ADDITIONAL HP8553B 1KHZ TO 110MHZ RF PLUG-IN.....	£2000
HP8444A TRACKING GENERATOR OPT058.....	£1500
HP8553B 1HZ TO 110MHZ LATE MODEL ANALYSER PLUG-INS.....	£200
WAYNE KERR RA200 FREQUENCY RESPONSE ANALYSER.....	£400
HP3580A 5KHZ TO 50KHZ AUDIO ANALYSER.....	£1500
HP3581C SELECTIVE VOLT-METER 1SHZ TO 50KHZ.....	£750
TEKSCAN AL51 4MHZ TO 1000MHZ ANALYSER.....	£750
EATON 2075B NOISE GAIN ANALYSER 10MHZ TO 2GHZ.....	£2000

OSCILLOSCOPES

TEKTRONIX 2445A 150MHZ 4 CHANNEL.....	£1550
TEKTRONIX 2445 150MHZ 2 CHANNEL.....	£1300
TEKTRONIX 2213 60MHZ 2 CHANNEL.....	£325
TEKTRONIX 2215 60MHZ 2 CHANNEL.....	£400
PHILIPS 3305 35MHZ DIGITAL STORAGE.....	£2550
GOULD 5110 100MHZ INTELLIGENT OSCILLOSCOPE.....	£750
GOULD O5300 20MHZ 2 CHANNEL.....	£175
LEADER LB024L 40MHZ DELAYED SWEEP.....	£325
TEKTRONIX SC504/TM503/DM501 PORTABLE 80MHZ SCOPE/DVM IN.....	£600
TEKTRONIX 475 200MHZ DUAL TRACE.....	£400
TEKTRONIX 465 100MHZ DUAL TRACE.....	£345
TEKTRONIX 465B 100MHZ OSCILLOSCOPE.....	£400
TEKTRONIX 464 100MHZ STORAGE.....	£395
HP1228B 275MHZ MICROPROCESSOR CAL MEASUREMENTS (AS NEW).....	£700

TEKTRONIX 2633/7A26/7A13/7B53 200MHZ 4 CHANNEL STORAGE.....

TEKTRONIX 7403/7A26/7A13/7B53A 1GHZ OSCILLOSCOPE.....	£600
PHILIPS PM327 50MHZ 2 CHANNEL DELAYED TIMEBASE.....	£375
IWAT SUI S5412 100MHZ 4 CHANNEL CURSOR READOUT.....	£900
KIKUSUI C06 B00 100MHZ 3 CHANNEL.....	£500
NICOLET 4094A DIGITAL OSCILLOSCOPE (TO CLEAR).....	£250
GOULD O5400 10MHZ DIGITAL STORAGE.....	£195
GOULD O5250 10MHZ 2 CHANNEL.....	£95
TEKTRONIX 7704/7A13/7A26/7B15/7B53A 4 CHANNEL.....	£500
TEKTRONIX 5103/5B10/5A20/5A20N OSCILLOSCOPE.....	£250

TEST EQUIPMENT

TEKTRONIX 521A PAL VECTOR SCOPE.....	£750
TEKTRONIX 141H PAL GENERATOR SPGI/ITK5.....	£1750
SYSTEMS VIDEO 2360 COMPONENT VIDEO GENERATOR.....	£1500
PHILIPS PM567 PAL VECTOR SCOPE.....	£750
HP5005A SIGNATURE MULTIMETER.....	£495
BRUEL & KJAER 2511 VIBRATION METER.....	£750
BRUEL & KJAER 2203 PRECISION SOUND LEVEL METER/WB0812.....	£450
FILTER.....	£450
BRUEL & KJAER 1022 BEAT FREQUENCY OSCILLATOR.....	£200
BRUEL & KJAER 4709 FREQUENCY RESPONSE ANALYSER.....	£250
BRUEL & KJAER 2305 LEVEL RECORDER.....	£225
EFRAIM RPT ATOMIC FREQUENCY STANDARD.....	£2500
HP179A PRIMARY MULTIPLEX ANALYSER.....	£600
HP3780A PATTERN GENERATOR/ERROR DETECTOR.....	£350
HP3762A DATA GENERATOR.....	£350
HP3468D DIGITAL MULTIMETER LCD.....	£200
HP3466A DIGITAL MULTIMETER LED.....	£200
HP8750A STORAGE NORMAUSER.....	£395
HP875A VECTOR VOLT-METER & ACCESSORIES 1000HZ.....	£650
HP3400A TRUE RMS VOLT-METER ANALOGUE.....	£145
HP3403C TRUE RMS VOLT-METER DIGITAL.....	£150
HP3466A BROADBAND SAMPING VOLT-METER.....	£225
HP1481A TRUE RMS AMPLIFIER.....	£300
HP1467A POWER SPLITTER 18GHZ (NEW).....	£500
HP10529A LOGIC COMPARATOR.....	£85
HP394A VARIABLE ATTENUATOR 1GHZ TO 2GHZ.....	£85
HP334A DISTORTION METER OPT H15.....	£250
HP5325A 825MHZ FREQUENCY COUNTER.....	£125
MARCONI 2300E MODULATION METER 1200MHZ.....	£300
MARCONI 2331 A DISTORTION FACTOR METER.....	£200
MARCONI 2432 160MHZ FREQUENCY COUNTER.....	£150
MARCONI 2432A 360MHZ FREQUENCY COUNTER.....	£200
MARCONI 2404 ELECTRONIC VOLT-METER 1500MHZ.....	£45
MARCONI 2403 RF MILLIVOLT METER 1500MHZ.....	£95
MARCONI 2110/4 TV LINEAR DISTORTION ANALYSER.....	£600
MARCONI 2K13 TEST LINE GENERATOR + INSERTOR.....	£600
MARCONI 2114A INSERTION SIGNAL GENERATOR.....	£600
MARCONI 2106 PROGRAMMABLE INTERFACE UNIT.....	£450
MARCONI 2700 LCR BRIDGE BATTERY.....	prices from £25
FARNELL RB1030/35 ELECTRONIC LOAD.....	£495
FARNELL T05 3D TRIPLE OUTPUT DIGITAL PSU.....	£225
FARNELL L50/500mA POWER SUPPLY.....	£95
FARNELL RB1030/35 ELECTRONIC LOAD.....	£495
FARNELL B30/20 POWER SUPPLY 0-30 VOLT 20 AMP.....	£100
FARNELL L5126 RF AMPLIFIER 1.5MHZ TO 520MHZ.....	£155
FARNELL T78 TRUE RMS SAMPING RF METER (AS NEW) 1 GHZ.....	£350
FLUKE 3330B PROG CONSTANT CURRENT/VOLTAGE CALIBRATOR.....	£750
FLUKE 1000A/1000V COMPACTOR.....	£295
ROTEK AC/OC PRECISION CALIBRATOR.....	£650
EXACT 334 PRECISION CURRENT CALIBRATOR.....	£195

BALLANTINE 6125C PROG TIME/AMPLITUDE TESTSET.....

BALLANTINE 590521A UNIVERSAL TEST SYSTEM.....	£500
AVO RM215 L2 AC/DC BREAKDOWN/IONISATION TESTER.....	£300
ALITECH 5332-11 CALIBRATOR 1HP355C/HF355D ATTENUATORS.....	£400
BIRD TENULINE 8343 100W 6DB ATTENUATORS (NEW).....	£100
BIRD TERMINAL B18 80W COAXIAL RESISTOR.....	£85
NARDE 7697 150W 6DB ATTENUATORS.....	£65
NARDE 4200 150 DB DIRECTIONAL COUPLER 460MHZ TO 950MHZ.....	£100
NARDE 3021 B-DIRECTIONAL COUPLER 1GHZ TO 4GHZ.....	£250
KEMO DP1 PHASE METER 1HZ TO 100KHZ (NEW).....	£150
IWATS J1 SC7104 10HZ TO 1000MHZ FREQUENCY COUNTER.....	£235
RACAL 9009 MODULATION METER 30MHZ TO 1500 MHZ.....	£275
RACAL 9903 50MHZ TIMER COUNTER.....	£95
RACAL 9904M 50MHZ TIMER COUNTER.....	£145
RACAL 9915 10HZ TO 120MHZ FREQUENCY COUNTER.....	£150
RACAL 9919 10HZ TO 100MHZ FREQUENCY COUNTER.....	£300
RACAL DANA 1900 520MHZ MICRO PROCESSING TIMER COUNTER.....	£500
RACAL DANA 1998 10HZ TO 1300MHZ FREQ/TIMER COUNTER.....	£250
RACAL 9009 MODULATION METER 30MHZ TO 1500 MHZ.....	£275
RACAL 9903 50MHZ TIMER COUNTER.....	£95
RACAL DANA 9303 TRUE RMS RF LEVEL METER.....	£200
RACAL DANA 488 IEEE STD BUS ANALYSER.....	£200
RACAL DANA 9302 RF MILLIVOLT METER 10KHZ TO 1500MHZ.....	£400
RACAL DANA 1002 THERMAL PRINTER.....	£150
WAYNE KERR CT 496 LCR BRIDGE BATTERY PORTABLE.....	£95
PHILIPS PM8252A DUAL PEN RECORDER.....	£295
DANA 32085 AF POWER METER.....	£200
TEKTRONIX 528A VIDEO WAVEFORM MONITOR.....	£300
TEKTRONIX 138 LOGIC ANALYSER 32 CHANNEL 20MHZ.....	£400
TEKTRONIX 318 LOGIC ANALYSER 16 CHANNEL 50MHZ.....	£450
SIEMENS U2333 PSOPHOMETER (NEW).....	£500
SIEMENS D2108 LEVEL METER 200HZ TO 30MHZ.....	£650
SIEMENS W2108 LEVEL OSCILLATOR 30MHZ.....	£650
WANE EL & GOLTERMAN P519 LEVEL METER 50HZ TO 25MHZ.....	£650
SAYROSA AMH AUTOMATIC MODULATION METER 2GHZ.....	£200
BRUEL & KJAER 2425 ELECTRONIC VOLT-METER 0.5HZ TO 500KHZ.....	£195
DRANETZ 626A MAINS DISTURBANCE ANALYSER FITTED WITH 6036 interface/602A dc monitor/6001 line analyzer/6006 ac monitor/6020 broadband rf monitor.....	£1250
SCHLUMBERGER 7702 DIGITAL TRANSMISSION ANALYSER.....	£1250
MARCONI 4950A/4950A POWER METER 10MHZ TO 30GHZ.....	£85
MARCONI 4953A VSWR INDICATOR.....	£495
HP432A/478A RF POWER METER 10MHZ TO 10GHZ.....	£400
HP435A/482H RF POWER METER 10KHZ TO 42GHZ.....	£850
HP435B/481H RF POWER METER 100KHZ TO 42GHZ.....	£850
HP435B/481A RF POWER METER 10MHZ TO 18GHZ.....	£1000
HP436A DIGITAL POWER METER.....	£650
HP447D AMPLIFIER 0.1MHZ TO 1300MHZ.....	£500
HP432A CRYSTAL DETECTOR.....	£150
SCD RF AMPLIFIER 10MHZ TO 1000MHZ 10 WATT 46DB.....	£1000
BIRD COAXIAL ATTENUATOR 500W 30db.....	£200

BULK PURCHASE SPECIALS


BECKMAN DM110 DIGITAL MULTIMETERS WITH CASE/PROBES.....	£50
SOLARTRON 7045 HIGH SPECIFICATION BENCH DVM.....	£60
TEKTRONIX PAL METER.....	£40
BIRD 43 THRU LINE WATTMETERS.....	£75
SIEMENS PD08M2 PORTABLE LCD RADIATION METER (NEW).....	£45
EX GERMAN ARMY PORTABLE RADIATION METERS.....	£35

ALL PRICES PLUS VAT AND CARRIAGE - ALL EQUIPMENT SUPPLIED WITH 30 DAYS WARRANTY

86 Bishopgate Street, Leeds LS1 4BB
Tel: (0532) 435649 Fax: (0532) 426881

CIRCLE NO. 118 ON REPLY CARD

BOOKS TO BUY

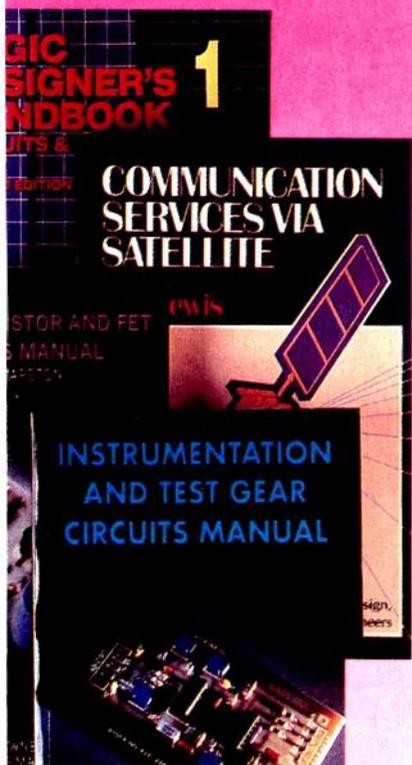

Programmable Logic Handbook

Geoff Bostock

Logic circuit designers are increasingly turning to programmable logic devices as a means of solving problems. This book, for the established electronics engineer, student and technician, is a thorough introduction to programmable logic. Geoff Bostock will take you to a level where you, as a designer, can take full advantage of the growing product range of ASICs and other self-programmable arrays used in computer and control systems. Paperback 256 pages.

Price £19.95 0 7506 0808 0

Understand Electrical and Electronic Maths

Owen Bishop

People who find maths difficult often have, as a result, difficulty

in grasping electrical and electronics theory. This book has been written to help such students to understand the mathematical principles underlying their subject so that they can go on with confidence to tackle problems in practical circuits. Paperback 256 pages.

Price £14.95 0 7506 0924 9

CIRCUIT MANUALS

Ray Marston

A series of books dealing with their subjects in an easy-to-read and non-mathematical manner, presenting the reader with many practical applications and circuits. They are specifically written, for the design engineer, technician and the experimenter, as well as the electronics student and amateur. All the titles are written by Ray Marston, a freelance electronics design engineer and international writer.

Op-amp Circuits Manual

Paperback 224 pages

Price £13.95 0 434 912077

Audio IC Circuits Manual

Paperback 168 pages

Price £13.95 0 434 912107

CMOS Circuits Manual

Paperback 192 pages

Price £13.95 0 434 912123

Electronic Alarm Circuits Manual

Paperback 144 pages

Price £13.95 0 7506 00640

Timer/Generator Circuits Manual

Paperback 224 pages

Price £13.95 0 434 912913

Diode, Transistor and FET Circuits Manual

Paperback 240 pages

Price £13.95 0 7506 0228 7

Instrumentation and Test Gear Circuits Manual

Ray Marston

Modern instrumentation and test gear circuits of value to the industrial, commercial, or amateur electronic engineer or designer make up this book. Almost 500 outstandingly useful and carefully selected practical circuits are in here. This is one book you must have if you need access to practical working circuits ranging from simple attenuators and bridges to complex digital panel meters, waveform generators, and scope trace doublers. Paperback 400 pages.

Price £16.95 0 7506 0758 0

Logic Designers Handbook

Andrew Parr

Easy to read, but none the less thorough, this book on digital circuits is for use by students and engineers and provides an accessible source of data on devices in the TTL and CMOS families. It's a 'Designers Handbook' that will live on the designer's bench rather than on the bookshelf. The basic theory is explained and then supported with specific practical examples. Paperback 488 pages.

Price £25.00 0 7506 0535 9

Digital Audio and Compact Disc Technology

Luc Baert, Luc Theunissen & Guido Vergut

Essential reading for audio engineers, students and hi-fi enthusiasts. A clear and easy-to-follow introduction and includes a technical description of DAT (digital audio tape). Contents includes principles of digital signal processing, sampling, quantization, A/D conversion systems, codes for digital magnetic recording, principles of error correction, the compact disc, CD encoding, optoelectronics and the optical block, servo circuits in CD players, signal processing, digital audio recording systems, PCM, Video 8, R-DAT and S-DAT. Paperback 240 pages.

Price £16.95 0 7506 0614 2

NEWNES POCKET BOOKS

A series of handy, inexpensive, pocket sized books to be kept by your side and used every day. Their size makes them an ideal 'travelling' companion as well.

Newnes Electronics Engineer's Pocket Book

Keith Brindley

Hardback 319 pages

Price £12.95 0 7506 0937 0

Newnes Electronics Assembly Pocket Book

Keith Brindley

Hardback 304 pages

Price £10.95 0 7506 0222 8

Newnes Television and Video Engineer's Pocket Book

Eugene Trundle

Hardback 384 pages

Price £12.95 0 7506 0677 0

Newnes Circuit Calculations Pocket Book

T Davies

Hardback 300 pages

Price £10.95 0 7506 0195 7

Newnes Data Communications Pocket Book

Michael Tooley

Hardback 192 pages

Price £12.95 0 7506 0427 1

Newnes Telecommunications Pocket Book

JE Varrall & EA Edis

Hardback 400 pages

Price £12.95 0 7506 0307 0

Newnes Z80 Pocket Book

Chris Roberts

Hardback 185 pages

Price £12.95 0 7506 0308 9

Newnes 68000 Pocket Book

Mike Tooley

Hardback 257 pages

Price £12.95 0 7506 0309 7

Newnes Electrical Pocket Book

21st edition

E A Parr

Paperback 526 pages

£12.95 0 7506 05138

Newnes Electric Circuits Pocket Book Linear IC

Ray Marston

Hardback 336 pages

Price £12.95 0 7506 0132 9

Newnes Guide to Satellite TV

D J Stephenson

A practical guide, without excessive theory of mathematics, to the installation and servicing of satellite TV receiving equipment for those professionally employed in the aerial rigging/TV trades. Hardback 256 pages.

Price £17.95 0 7506 0215 5

Newnes Practical RF Handbook

Ian Hickman

Pressure on the RF spectrum has never been greater and it's people with knowledge and skills of RF design who are now in demand in the electronics industry to design, produce, maintain and use equipment capable of working in this crowded environment. This practical introduction to modern RF circuit design will equip you with the necessary RF knowledge and skills to enable you to compete effectively in the industry. Paperback 320 pages.

Price £16.95 0 7506 0871 4

Troubleshooting Analog Circuits

R A Pease

Bob Pease is one of the legends of analog design. Over the years, he's developed techniques and methods to expedite the often-difficult tasks of debugging and

troubleshooting analog circuits. Now, Bob has compiled his 'battle-tested' methods in the pages of this book. Based on his immensely popular series in EDN Magazine, the book contains a wealth of new material and advice for Digital/Analog electronics engineers on using simple equipment to troubleshoot. Paperback 217 pages.

Price £14.95 0 7506 16326

PC-Based Instrumentation and Control
M Tooley

Do you need information to enable you to select the necessary hardware and software to implement a wide range of practical PC-based instrumentation and control systems? Then this book is for you. Paperback 320 pages.

Price £14.95 0 7506 1631 8

Electronic Circuits Handbook
M Tooley

Provides you with a unique collection of practical working circuits together with supporting information so that circuits can be produced in the shortest possible time and without recourse to theoretical texts. Paperback 345 pages.

Price £24.95 0 7506 0750 5

Communication Services via Satellite
G E Lewis

DBS is already with us, and will create a series of new technical problems for engineers/technicians in television and communication services. This book gives you the solutions to these problems by:

explaining how the system functions; describing several actual systems and giving several analyses and design rules. You can't afford to be without this invaluable technology update if you're a systems design engineer, service engineer or technician. Paperback 400 pages.

Price £25.00 0 7506 0437 9

Digital Logic Design
Brian Holdsworth

As one of the most successful and well established electronics textbooks on digital logic design, this book reflects recent developments in the digital fields. The book also covers new functional logic symbols and logic design using MSI and programmable logic arrays. Paperback 448 pages.

Price £19. 50 0 7506 0501 4

The Circuit Designers Companion
T Williams

This compendium of practical wisdom concerning the real-world aspects of electronic circuit design is invaluable for linear and digital designers alike. Hardback 320 pages.

Price £25 00 0 7506 1142 1

Credit card orders accepted by phone
081 652 3614

Return to: Lorraine Spindler, Room L333, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

Please supply the following titles:

Qty	Title	ISBN	Price
_____	Programmable Logic Handbook	07506 0808 0	19.95
_____	Understanding Electrical & Elec Maths	07506 0924 9	14.95
_____	Op-amp Circuits Manual	0434 912077	13.95
_____	Audio IC Circuits Manual	0434 912107	13.95
_____	CMOS Circuit Manual	0434 912123	13.95
_____	Electronic Alarm Circuits Manual	07506 0064 0	13.95
_____	Power Control Circuits Manual	07506 06908	13.95
_____	Timer/Generator Circuits Manual	0434 91291 3	13.95
_____	Diode, Transistor & FET Circuits Man	07506 0228 7	13.95
_____	Instrumentation & Test Gear Circuits Man	07506 0758 0	16.95
_____	Logic Designers Handbook	07506 0535 9	25.00
_____	Digital Audio and Compact Disc	07506 0614 2	16.95
_____	Newnes Elec Engineers Pkt Bk	0 7506 0937 0	12.95
_____	Newnes Elec Assembly Pk Bk	07506 0222 8	10.95
_____	Newnes TV and Video Eng Pkt Bk	07506 0677 0	12.95
_____	Newnes Circuit Calculations Pkt Bk	07506 0427 1	10.95
_____	Newnes Data Communications Pkt Bk	07506 0308 9	12.95
_____	Newnes Telecommunications Pkt Bk	07506 0307 0	12.95
_____	Newnes Z80 Pkt Bk	07506 0538 9	12.95
_____	Newnes 68000 Pkt Bk	07506 0309 7	12.95
_____	Newnes Electrical Pk Bk	07506 05138	12.95
_____	Newnes Electric Circuits Pocket Bk	07506 0132 9	12.95
_____	Newnes Guide to Satellite TV	07506 0215 5	17.95
_____	Newnes Practical RF Handbook	07506 0871 4	16.95
_____	Troubleshooting Analog Circuits	07506 16326	14.95
_____	PC-Based Instrumentation and Control	07506 1631 8	14.95
_____	Electronic Circuits Handbook	07506 0750 5	24.95
_____	Communication Services via Satellite	07506 0437 9	25.00
_____	Digital Logic Design	07506 05014	19.50

PLEASE ADD £2.50 FOR POSTAGE _____
Add VAT at local rate _____
NB ZERO RATE FOR UK & EIRE _____ TOTAL _____

Business purchase: Please send me the books listed with an invoice. I will arrange for my company to pay the accompanying invoice within 30 days. I will attach my business card/letterhead and have signed the form below.
Guarantee: If you are not completely satisfied, books may be returned within 30 days in a resaleable condition for a full refund.

Remittance enclosed £ _____
Cheques should be made payable to **Reed Book Services Ltd.**
Please debit my credit card as follows:

Access/Master Barclay/Visa Amex Diners

Credit Card No. _____ Exp date _____

NAME (Please print) _____

ORGANISATION _____

STREET _____

TOWN _____

COUNTY _____ POST CODE _____ COUNTRY _____


DATE _____ TELEPHONE NUMBER _____

SIGNATURE _____

T3000

VAT RATES
6% Belgium, 25% Denmark, 5.5% France, 7% Gemany, 4% Greece, 4% Italy, 3% Luxembourg, 6% Netherlands, 5% Portugal, 3% Spain. FOR COMPANIES REGISTERED FOR VAT, PLEASE SUPPLY YOUR REGISTRATION NUMBER BELOW (customers outside the EEC should leave this part blank)
VAT NO. _____

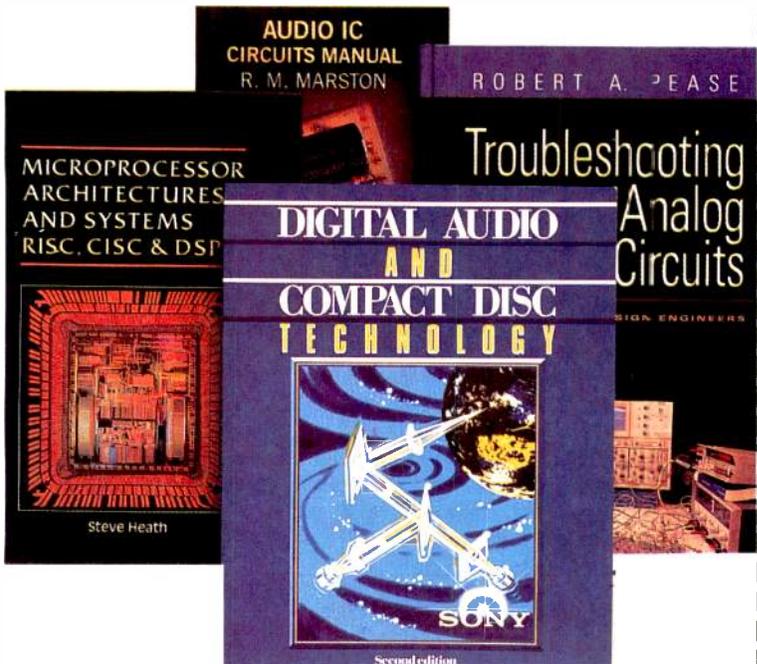
If in the UK please allow 28 days for delivery. All prices are correct at time of going to press but may be subject to change.
Please delete as appropriate. I do/do not wish to recieve further details about books, journals and information services.
Reed Business Publishing - Registered Office - Quadrant Hse The Quadrant Sutton Surrey SM2 5AS Registered in England 151537



New wave

MICROWAVES

5: oscillator and amplifier devices

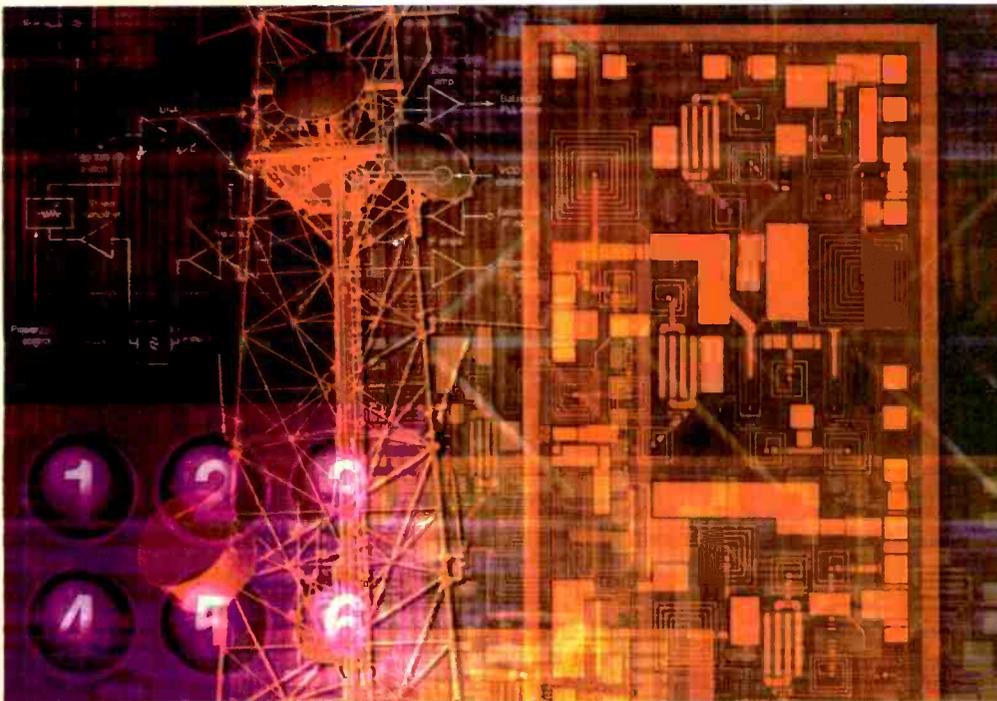

The GaAs mesfet and its derivatives provide the active element of choice in low noise and medium power amplifier designs to 30GHz. However, new technologies look increasingly attractive. Most exploit the features of the heterostructure. Mike Hosking reports on the new wave of semiconductor devices.

**Mike Hosking is a lecturer in telecommunications and microwaves at the University of Portsmouth.*

Gunn and impatt devices, once the main active components for microwave power generation, are now being relegated to millimetre wave and high power operation. The competition has come from mesfet technology, particularly high electron mobility transistor (hemt) and the pseudo-morphic hemt or phemt.

These devices take over from the silicon BJT in the overlapping technology band between 2GHz and 4GHz and offer low noise, good efficiency and medium power levels up to the millimetre wave region and beyond (>30GHz). In recent years, a further contender has appeared on the technology stage: the GaAs heterojunction bipolar transistor (HBT). This possesses many of the advantages of the Si BJT: notably low phase noise, high power-added efficiency and a medium power output; but translated in frequency through the microwave and into the millimetre bands.

Frequency multiplication, as a means of signal generation, is not now widely used except when very low phase noise is needed. One particular technique of interest uses a device called a step recovery diode as a harmonic

generator and is used in certain local oscillator and instrumentation applications.

Microwave transistors

Starting at the lower end of the microwave region, the silicon BJT dominates amplifier and oscillator technology. Low phase noise and optimal power-added efficiency are essential to PCS mobile phone equipment. The BJT can easily and reliably provide several watts of output power at greater than 30% efficiency in the 960MHz to 1400MHz bands. BiCMOS, relevant to the signal processing stages of these systems, combines bipolar speed with CMOS complexity.

Si BJT technology can also generate several hundred watts from a single transistor amplifier at around 1GHz. Solid state radars using hundreds of such high power modules, have been successfully integrated into antenna arrays for L-band operation (between 1GHz and 2GHz).

Construction of the microwave Si BJT, Fig. 1a, is not so different from its lower frequency counterpart and consists of a very highly doped n-type emitter, a p-type base region of

small width ($\approx 1\mu\text{m}$) and a low resistance n-type collector contact. Although operation is possible at frequencies above 10GHz, for most practical purposes the BJT is technology limited to below about 4GHz. Electron transit time from the emitter-base junction to the collector sets the upper frequency limit, but the length of this region cannot be made arbitrarily narrow because of voltage breakdown and power handling.

As the mobility of electrons in silicon is greater than that of holes, microwave transistors are always n-p-n types with electrons as the majority carriers. The maximum frequency of oscillation is a function of the time constant created between collector-base capacitance and base resistance. Interdigital geometry for the base-emitter junction, Fig. 1b, allows an increase in current by the increase in emitter periphery, without increasing the capacitance.

The BJT exhibits low phase noise, generally many times better than that which can be achieved with fet technology. The phones used in PCS, typically have an rf subsystem as shown in Fig. 2, where the same voltage con-

trolled oscillator is used to generate the data-modulated, up-converted carrier as well as the LO for the receiver. With the emphasis on spectrum conservation and a likely change from FM and FSK to high order (16 to 64 state) QAM modulation, phase noise performance is vital. This assures the Si BJT a place in the design of power amplifiers for these systems.

Mesfet devices

The GaAs mesfet dominates low noise amplifier and medium power amplifier applications from microwave to millimetric frequencies. It has revolutionised the performance of DBS receivers and is replacing the travelling wave tube in satellite transponders.

At microwave frequencies, the rectifying junction of the fet is a metal-semiconductor interface of Schottky barrier type, Fig 3a.

Electrons in the n-type GaAs diffuse into the metal to form a barrier potential and leave behind a region of high resistance containing few free carriers: the depletion region. Minority carriers play little part in the operation of the junction and, thus, there are virtually no charge storage effects. This allows the junction to switch from conducting to non-conducting states at microwave and millimetre wave frequencies.

Like conventional fets, a reverse bias applied between the gate and source will increase the height of the depletion region until it equals that of the channel, thus pinching-off the current between drain and source. Hence, this is a means of controlling output current and of applying modulation. The mesfet is a transit time device in that the cut-off frequency is determined by the saturation velocity of the electrons and by the time taken to traverse the gate length, *L*. Thus GaAs, with its higher mobility is preferred to silicon for microwave fets.

A 1µm gate length allows operation up to 10GHz and present lithography can achieve 0.1µm resolution, resulting in achievable operating frequencies of 60GHz and higher. At around 10GHz, a chip-only noise figure of less than 1dB could be expected, with a gain

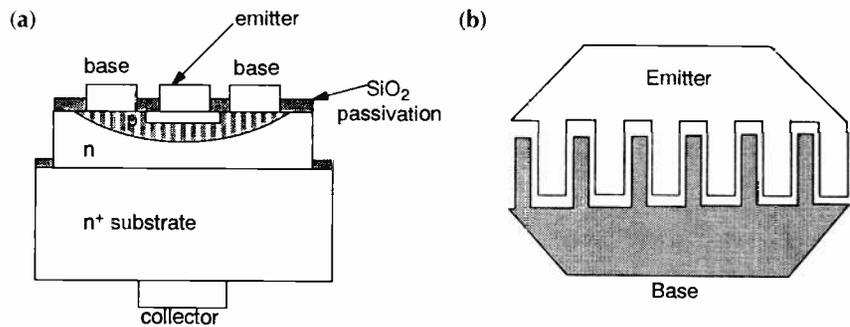


Fig. 1. Basic structure of the silicon bipolar transistor (a) with (b) the general type of interdigitated emitter which allows the current to be increased without a corresponding increase in capacitance.

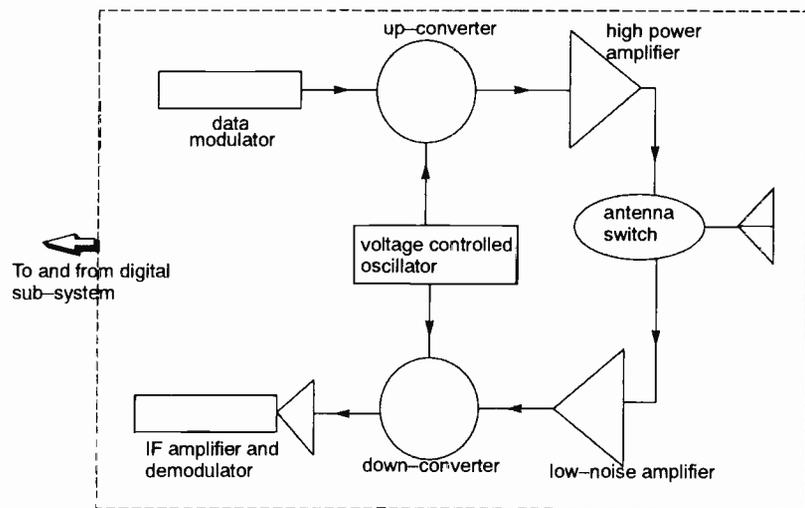


Fig. 2. Typical rf section of a PCS communicator. Different technologies are being used to produce highly optimised devices for each of the major components.

of about 12dB. As a power device, several hundred milliwatts with power-added efficiency greater than 25% could be provided at the same frequency.

Heterojunctions

Two variants of the classic mesfet device, the hemt and pHEMT, extend the mesfet operating envelope. Fig. 3b shows the construction profile of the hemt for comparison with the standard mesfet. The device is still a FET with

regard to its method of operation but, instead of the n-type GaAs channel, the hemt has a thinner (≈500Å) layer of highly doped, n-type AlGaAs grown onto an even thinner (≈40Å) undoped AlGaAs layer. This, in turn is grown onto the normal undoped GaAs buffer layer ≈1µm thick. The key operational difference is that the donor atoms lie in the AlGaAs layer which has an energy band gap of 1.72eV compared with the 1.42eV band gap of GaAs. This creates what is called a potential well of 0.3eV and, when electrons enter the gate channel from the source contact, they are drawn to this energy well and form a narrow sheet of charge. This sheet lies as a thin (<100Å) layer on the GaAs side of the junction, as shown, and is referred to as a two-dimensional electron gas (2-DEG).

In a mesfet, the current fills the whole width of the gate channel defined by the extent of the depletion region. Hence, electrons in the hemt are travelling in the undoped GaAs

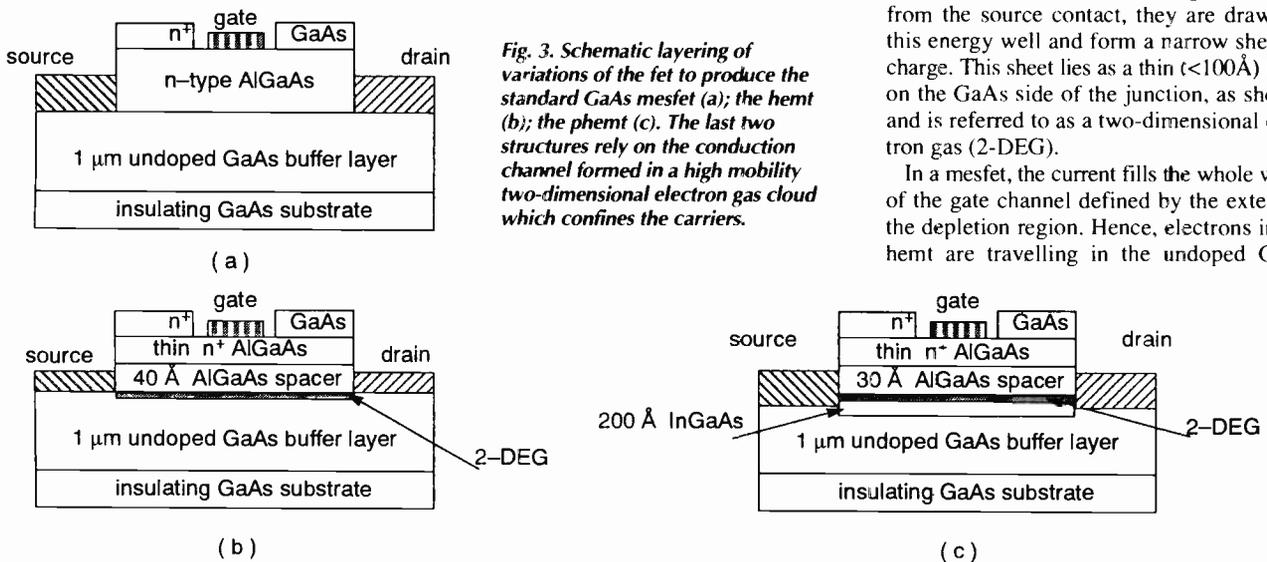


Fig. 3. Schematic layering of variations of the fet to produce the standard GaAs mesfet (a); the hemt (b); the pHEMT (c). The last two structures rely on the conduction channel formed in a high mobility two-dimensional electron gas cloud which confines the carriers.

which contains virtually no donor atoms in this thin electron gas layer. They experience no impurity scattering, with the result that mobility is increased three-fold over that of the GaAs mesfet with a corresponding improvement in performance. About 0.5dB noise figure at 10dB gain could be obtained at around 10GHz and cut-off frequencies well above 100GHz have been achieved. The hemt is also well suited to power applications: Texas Instruments, for example, offers a device delivering over 5W at about 40% efficiency around 10GHz using 0.5µm geometry.

Further improvements to performance can be obtained by modification to the device structure, Fig. 3c. For a sub-micron gate length, the current gain-bandwidth product (f_{max}) of the hemt is approximately given by:

$$f_{max} = \frac{V_t}{2\pi l} \text{ Hz}$$

where V_t is the transit velocity of electrons under the gate and l is the gate length. Thus, a material having a higher electron velocity will contribute directly to a higher frequency of operation.

InGaAs has a peak electron velocity over 30% greater than GaAs and, in the phemt, a thin ($\approx 200\text{\AA}$) layer is introduced on top of the GaAs buffer layer. The two dimensional gas penetrates this higher velocity region and, in fact, is additionally confined by the 0.17eV energy band gap of this material. The structure

is called 'pseudomorphic' because there is a slight mismatch between the lattice structure of InGaAs and the GaAs buffer layer. With careful control of the layer thickness, the strain of this mismatch can be accommodated by the InGaAs lattice which distorts to 'mirror' the GaAs structure. Hence, 'pseudomorphic'.

The result of these device modifications are incentives for a higher frequency of operation ($f_{max} > 200\text{GHz}$) and lower noise figure ($< 1\text{dB}$ at 20GHz) with efficiencies around 30%. Phemts have been commercially available for several years, but development is continuous and performance increases steadily.

There is also development effort being spent on the manufacture of hemt devices using InP instead of GaAs to deliver higher frequencies and lower noise. Operation to 300GHz is predicted and Hughes in the USA has already space qualified a 1.2dB noise figure InP hemt at 60GHz. Cooling of fet devices to liquid nitrogen temperatures of 77K results in general noise figure improvement. However, the hemt and phemt structures perform exceptionally well and noise figures similar to those only obtainable at present with cooled masers are predicted from InP.

Bipolar heterojunctions

The latest in microwave transistors is the GaAs heterojunction bipolar device which offers hundreds of milliwatts at 40 to 50% efficiency at millimetric frequencies. The ver-

tical topology of the HBT means that the emphasis on lithography can be relaxed; 2µm geometry is typical, c.f. fet structure.

Transit time is determined by layer thickness and doping: a simpler and higher-yield process. Fig. 4 shows one structure of the HBT, with the epitaxial layer hierarchy grown upon the collector substrate. The base-collector junction is GaAs, but the main difference from the BJT lies in the base material, typically of n-type AlGaAs. The electron mobility in this material is greater than that of GaAs (and much greater than silicon) thereby increasing the frequency of operation.

Perhaps more importantly the base region of the HBT may be much more heavily doped than the emitter, thereby reducing base resistance and reducing the base-emitter capacitance. The wide bandgap of the emitter prevents hole injection from the base. Also, high current capability is possible as the whole of the emitter area conducts uniformly. Thus, all the desirable features of the Si BJT are translated to higher frequencies (4 to 40GHz at present).

The vertical process technology also circumvents the surface defect limitations of the fet resulting in superior phase noise performance. As an example, Class AB operation at 10GHz has produced in excess of 55% power added efficiency with greater than 10dB gain and a power output of greater than 300 mW.

Both mesfet and HBT devices are themselves compatible with monolithic technology, leading to integrated low noise or high power amplifiers with optimised performance.

Step recovery multiplication

Although largely replaced by fundamental oscillators, one method, used in instrumentation to generate marker frequencies and local oscillator signals, uses the step recovery diode (SRD or snap varactor). It requires simple circuit design and only a single frequency input; the output comprises pure harmonics of the input.

The efficiency of this process is proportional to $1/n$, where n is the harmonic number, whereas the normal varactor multiplier using its non-linear capacitance as the multiplying mechanism has an efficiency proportional to $1/n^2$. Thus, the comb generator is suited to high-order multiplication and can give outputs of 10's of milliwatts, or more, into the millimetre band at about 30GHz.

At frequencies below 10GHz, several watts of output are possible. Multiplication factors up to 10 are typical and efficiency, depending upon n and frequency, can exceed 65%.

The SRD itself is made from silicon and its doping profile is of the p-i-n form shown in Fig. 5, where the intrinsic layer is relatively thin and the exact grading of the p-i junction is crucial to performance.

Successful operation depends upon the charge storage properties of the diode and silicon is preferred because of its minority carrier lifetime. This is the time for which the carrier will remain in its free state before recombination: in Si this can be made to be similar to

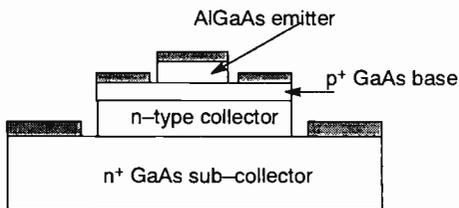


Fig. 4. Structure of the heterojunction bipolar transistor. The key to its high frequency and low noise performance lies in the AlGaAs layer and the high doping possible of the base region.

Fig. 5. Basic structure and equivalent circuit of the step recovery diode under different bias conditions. Unlike the normal p-i-n diode, there is no intermediate impedance state.

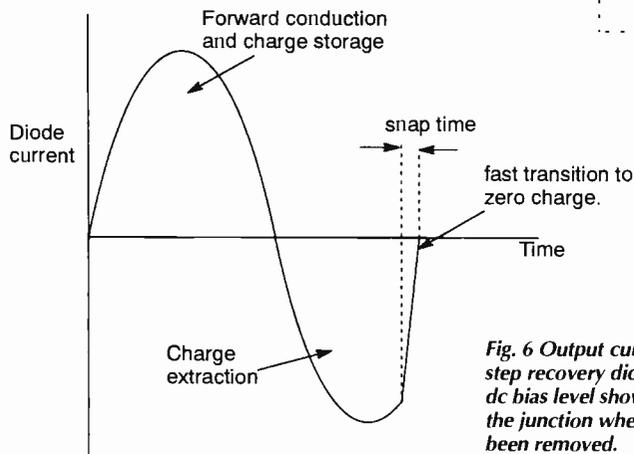
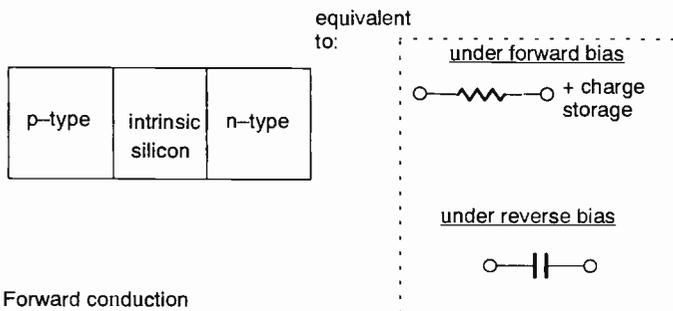


Fig. 6 Output current waveform of the step recovery diode superimposed on a dc bias level showing the snap action of the junction when all the charge has been removed.

period of the input rf cycle.

The diode of Fig. 5 has two extreme states under conditions of bias: forward bias will inject charge into the i-region and the SRD will appear as a low-value resistance. Reverse bias will remove charge leaving, essentially, a parallel-plate capacitance. However, for the duration of the carrier lifetime, there will be a transitory state of charge storage which is the basis of the SRD mechanism. Fig. 6 shows the condition where the SRD is forward biased to just below its conduction threshold (0.6V > 1.0V) and an input RF waveform is superimposed.

During the positive half cycle, the SRD is driven into conduction and the output current will essentially follow the rf input. The i-region fills with electrons and holes. As the input waveform goes negative, charge injection will cease; however, conduction will continue as the i-region charge can still be removed because it has been 'stored' due to the long carrier lifetime. There will come a point, though, in the negative cycle when all charge has been removed and the diode will change state to its high impedance (capacitive) state. The essence of the SRD principle is that this change of state occurs very rapidly: typically in tens of picoseconds and thus appears as a fast, transient spike.

Figure 7 shows a typical comb generator circuit using the SRD. The diode is inductively driven by the input waveform. In some high frequency designs the impulse inductor

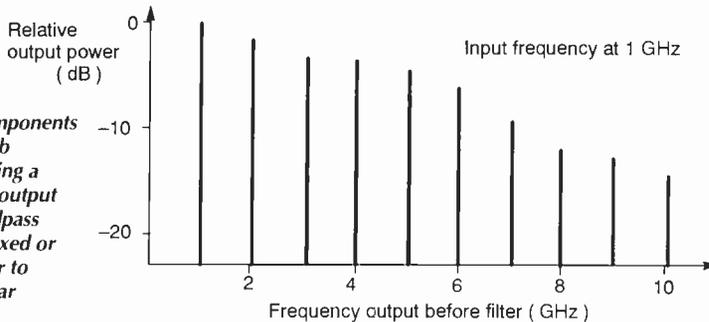
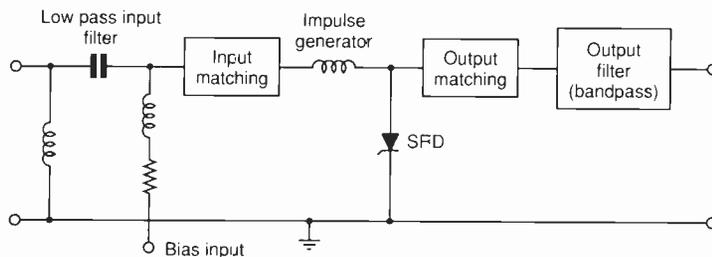


Fig. 7. Main components of the SRD comb generator showing a typical spectral output comb. The bandpass filter could be fixed or variable in order to select a particular harmonic.

can be the actual package inductance. During the charge-extraction portion of the rf cycle, energy builds up in this inductance and then, when the diode snaps into its rapid impedance change, the energy in this transient shock excites the output circuit (usually a length of transmission line) into resonance. This produces a comb of harmonics of the input frequency each input cycle. The final output stage is often a bandpass filter, selecting a par-

ticular harmonic. The output frequency spectrum and stability matches that of the input source. If this is a low-noise, high quality oscillator, then so too will be the output. Input frequencies cannot be too low in frequency and typically range from 250 MHz to 10GHz, depending upon the required output range. ■

Next month: circuits and methods for tuning and stabilising microwave sources.

SEETRAX CAE - RANGER - PCB DESIGN

Ranger1 £100


- * Schematic capture linked to PCB
- * Parts and wiring list entry
- * Outline (footprint) library editor
- * Manual board layout
- * Full design rule checker
- * Back annotation (linked to schematic)
- * Power, memory and signal autorouter - £50

Ranger2 £599

- All the features of Ranger1 plus
- * Gate & pin swapping (linked to schematic)
- * Track highlighting
- * Auto track necking
- * Copper flood fill
- * Power planes (heat-relief & anti-pads)
- * Rip-up & retry autorouter

Ranger3 £3500

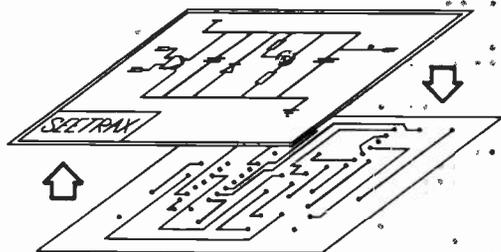- All the features of Ranger2 plus
- * UNIX or DOS versions
- * 1 Micron resolution and angles to 1/10th degree
- * Hierarchical or flat schematic
- * Unlimited design size
- * Any-shaped pad
- * Split power planes
- * Optional on-line DRC
- * 100% rip-up & retry, push & shove autorouter



All systems upward compatible. Trade-in deals available.

Call **Seetrax CAE** for further information/demo packs.
Tel 0705 591037 Fax 0705 599036

Seetrax CAE, Hinton Daubney House, Broadway Lane,
Lovedean, Hampshire, PO8 0SG

All trademarks acknowledged.

Outputs to:

- * 8/9 and 24 pin dot-matrix printers
- * HP Desk/Laser Jet, Canon BJet, Postscript (R3 only)
- * HP-GL, Houston Instruments plotters
- * Gerber photoplotters
- * NC Drill Excellon, Sieb & Meyer
- * AutoCAD DXF

CIRCLE NO. 119 ON REPLY CARD

The transformer ratio arm bridge

Every so often, it becomes worthwhile to reinvent the wheel.

Ian Hickman speculates on a new type of instrumentation based on the age-old bridge measurement technique.

The bridge principle in electrical measurements has been extended far beyond Wheatstone's original application for the measurement of resistance at dc. It has been adapted for measuring inductance, capacitance and even frequency (e.g. Wien bridge).

Bridge methods have largely fallen into disuse, especially for rf measurements. The reason is that each measurement is taken at a spot frequency and involves adjusting two standards for balance. Investigating the variation of impedance or admittance of an unknown with frequency is tedious, involving a large number of spot measurements. It is so much easier to connect the unknown to a network analyser and take an s_{11} measurement covering the frequency range of interest. The answer can be viewed instantly as an angular vector plot versus frequency, or I and Q components, or as a Smith chart display, with the value corresponding to a marker at any desired spot frequency indicated on the screen as a numerical readout.

Often the unknown is not a simple two terminal impedance, but a two port pi network, as in Fig. 1a. Given three independent equations relating the three unknowns to three measured values, the various impedances or admittances can be calculated. So any three of the four s-parameter measurements in Fig. 1b should in theory suffice, permitting the evaluation of the three impedances.

In practice, if Z_1 and Z_3 are low and Z_2 high, the computation will involve the difference of two large quantities, magnifying any measurement errors and may lead to a large margin of error for the calculated value of Z_2 . This is precisely where a particular type of rf bridge, the transformer-ratio-arm-bridge, scores over other methods. The trab was developed during WWII by Mr Gilbert Mayo of the BBC Research Department, and subsequently further developed and marketed by at least two companies in the U.K.

The transformer bridge

Figure 2a shows an rf trab in its simplest form. An rf test signal from a bridge source or signal generator is applied, via a stepdown transformer T_1 , to a calibrated variable standard capacitor C_s and a conductance standard G_x which is effectively variable from $1/R_1$

down to zero by means of the non-inductive calibrated variable resistor R_v . The other ends of these two components are connected to one end of a centre-tapped symmetrical winding on T_2 . The unknown is connected between the output of T_1 and the other end of the centre tapped winding on T_2 . An output winding on T_2 is connected to a bridge detector, which can be any radio receiver covering the band of interest.


In use, C_s and G_x are adjusted until there is no detectable output at the receiver. Balance occurs when the parallel components C_x and G_x of the unknown are equal to the capacitance setting of C_s (marked on its dial) and the effective value of G_x (which is marked on the dial of R_v). Balance occurs as a result of the current flowing via the standards through one half of the balanced symmetrical winding of T_2 equalling the current flowing via the unknown through the other half of the winding. As the number of turns on each half winding are the same, there is no net magnetising force, and consequently no resultant flux on the core. There is thus no voltage induced in the output winding, but equally, there is no voltage appearing across either half of the centre-tapped winding either. Thus T_2 acts as a virtual earth, the significance of which will appear in a moment.

Note that a trab inherently measures Z_2 in terms of an admittance Y_2 , i.e. equivalent components G_x in parallel with B_x . Given the known test frequency, these can be converted to the equivalent series components R_x and X_x using the formulae in Fig. 2b, or using a Smith Chart¹.

As shown in Fig. 2a, the range of the unknown that the bridge can handle is limited to C_x not exceeding the maximum value of C_s , and G_x not higher than $1/R_1$, with no capability at all for measuring either inductance, or negative conductance. This capability can be provided by the modified arrangement of Fig. 2b. Here, the terminals to which the unknown are connected are mounted upon two substantial blocks of metal, firmly bolted together with an insulating film between, to form a capacitance equal to $C_{s\max}/2$. The dial of C_s is now calibrated in positive and negative values of capacitance, with zero occurring where C_s is set at $C_{s\max}/2$; this arrangement was employed in the Wayne Kerr trabs.

Similarly, a resistor of value $2R_1$ can be added in parallel with the unknown terminals, allowing for negative values of conductance and permitting measurements on active devices. The shunt components of resistance (or conductance) and capacitance of the unknown could be read directly from the dials, at any test frequency. Inductance, on the other hand, was read as a negative capacitance. Knowing the test frequency enables the susceptance of the negative capacitance, and hence of the unknown inductive component, to be calculated, from

Fig. 1a) General two port pi network expressed in parallel components.
b) s-parameter measurement of two port pi network

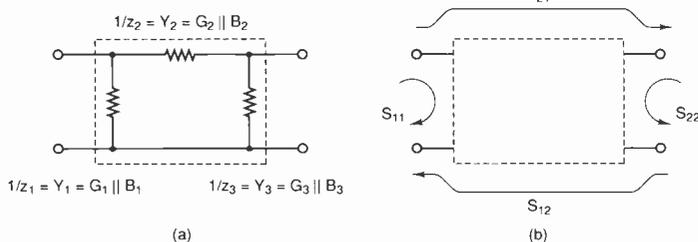

which the value of inductance itself was readily derived.

Although shown with the source connected to T_1 and the detector to T_2 , a trab can be used with the source and detector interchanged, where convenient.

Extended possibilities

Fig. 3 shows how the trab is inherently adapted for three terminal measurements, permitting the accurate measurement of Y_2 whatever the values of Y_1 and Y_3 , by virtue of the bridge's neutral connection. It can be seen that admittance Y_1 shunts the source whilst Y_3 shunts the detector (T_2 is a virtual earth). Thus while Y_1 in particular may reduce bridge sensitivity slightly, neither Y_1 nor Y_3 affects the accuracy of the measurement of Y_2 .

The operation of adaptors which extend the range of a bridge is of interest not only from the electrical point of view, but also because they illustrate the usefulness of the Binomial Theorem, which should really be called "The Engineer's Friend". The LE305, a well specified but low frequency bridge from Hatfield Instruments consisted of two non-inductive 100Ω resistors in a massive metal housing which are interconnected with the common and neutral terminals of the bridge and, by means of a substantial plug, with one of the multiplier terminals associated with T_2 . The unknown to be measured was connected between the junction of the two resistors and the bridge neutral terminal, see Fig. 4. If Z_x is a resistance of 1Ω or less, the current i_1 will be determined virtually solely by R_2 (and the bridge drive voltage at the common terminal). The volt drop e will thus be directly proportional to Z_x , and hence so will the current i_2 delivered to T_2 . If Z_x is zero, i_2 will be zero and bridge balance will be achieved.

As Z_x increases, so R_2 must be advanced, so its dial in fact now reads resistance directly instead of conductance. Similarly, if Z_x is an inductive reactance, the voltage across it and hence i_2 will both be leading and must be balanced by a capacitive current via C_s fed to the opposite side of T_2 .

For an inductive Z_x , as the frequency increases, so will e in Fig. 4, and hence also i_2 . Thus there will be no change in the setting of C_s for balance, so that with the low impedance adaptor in use, it is now inductive unknowns that become independent of frequency, even though they are measured by comparison with a capacitive standard. Furthermore, the unknown is now measured as series components $r+jx$, rather than shunt components $G+jB$. If Z_x is resistive, then the error due to the finite voltage e subtracting from the available bridge drive voltage reaches 2% for $Z_x = 1\Omega$. (The 1% increase in mesh resistance $100\Omega+1\Omega$ results in a 1% decrease in i_1 ; furthermore, the 1Ω unknown is shunted by the second 100Ω resistor, so e is reduced overall by 2%, per the binomial expansion, ignoring second order terms.)

The reactive component of Z_x may be up to 3Ω , since the component of e due to it subtracts from the bridge drive voltage rms-wise, rather than directly.

Automated trab?

A bit of speculation. A self-balancing trab – if such a thing existed – could directly measure the parallel components of susceptance of the series element of a pi network. The drive signal could then be swept, to give an impedance versus frequency display, not unlike a network analyser. For instance, the variable conductance standard formed by R_1 and R_v in Fig. 2 could be replaced by a four quadrant multiplier, with the rf applied to the X port and the control signal to the Y port. The output would thus be adjustable in both amplitude and sign, avoiding the need for selecting one

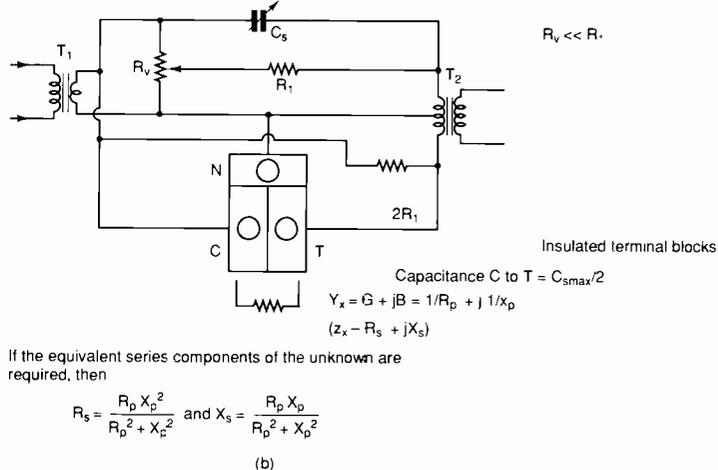
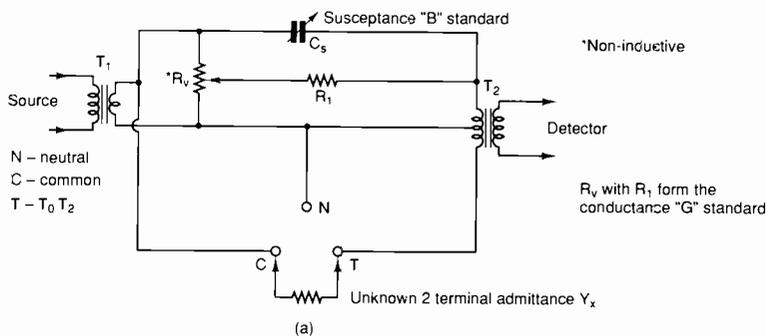


Fig. 2a) In its simplest form, a trab measures only capacitance and conductance (resistance).

b) With modifications, it can also measure negative capacitances (inductance) and negative conductances. Additional circuitry (not shown) is required to permit balancing of the bridge with C_s and R_v set to zero, before connecting the unknown.

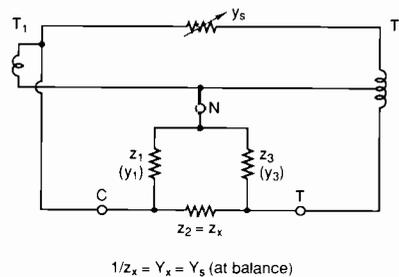


Fig. 3. Circuit showing how a trab is inherently perfectly adapted for three terminal measurements. Admittance Y_1 shunts the source whilst Y_3 shunts the detector (T_2 is a virtual earth). Thus while they may reduce bridge sensitivity slightly, neither affects the accuracy of the measurement of Y_2 .


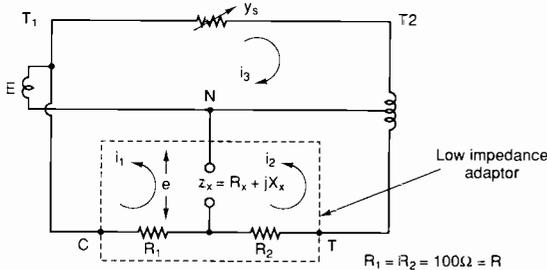


Fig. 4. Showing how a low impedance adaptor not only extends the measurement range of a trab, but also turns conductance into resistance, and capacitive susceptance into inductive reactance and vice versa.


At balance, $Y_s = G + jB = G_s \pm j \omega C_s$
 Then $L_x = C_s R_2^2$ (independent of ω)
 or $C_x = 1/(R_2^2 \omega^2 C_s)$
 and $R_x = G_s R_2^2$

side of T_2 or the other. The bridge output from T_2 would be synchronously detected and the resultant fed back to the Y port of the multiplier to automatically achieve a balance with the conductance of the unknown.

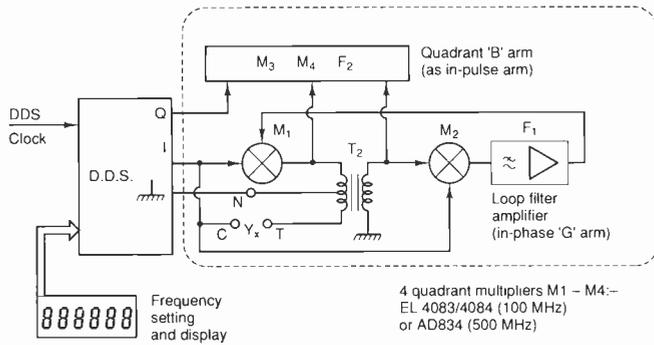
The degree of balance achieved would depend upon the loop gain. The variable susceptance could be obtained from another multiplier instead of C_s , by feeding its X port from a quadrature version of the drive



(a)

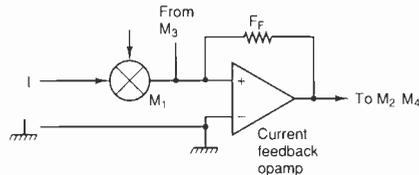

(b)

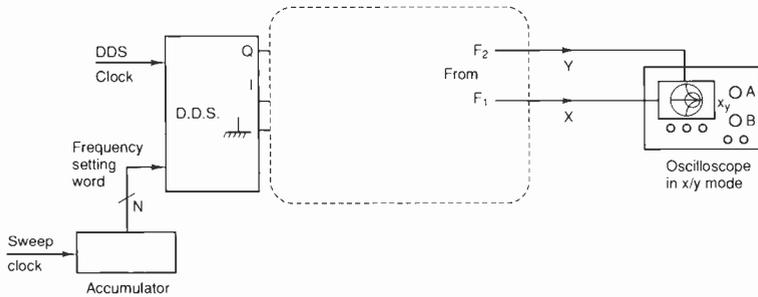

(c)

Fig. 5a) Trab with autobalance facilities
 b) As the multipliers can implement rf outputs of both polarity, i.e. can act as both negative and positive conductance and susceptance standards, T_2 is redundant, and can be replaced by an op-amp virtual earth.
 c) As a), with sweep facility and Smith Chart display.

signal. This requirement is easily met since sine and cosine outputs are available as standard from many direct digital synthesizer chips.

The arrangement might look something like Fig. 5a, where the synchronous detectors could be multipliers identical to those used as the G and B standards, fed through lengths of line to compensate the path-length through the bridge. As the multipliers can implement rf outputs of both polarity, i.e. can act as both negative and positive conductance and susceptance standards, T_2 is in fact redundant. It can be replaced by a current feedback op-amp virtual earth as in Fig. 5b: conveniently the multipliers provide current outputs. Fig. 5c shows how a swept measurement, with Smith Chart display of the unknown as a function of frequency, might be organised.


The only disadvantage of this 'active trab' arrangement is that a very low output impedance buffer is needed to drive the unknown. Any reduction of the I drive voltage due to loading by Z_1 (or indeed Z_2) will affect the conductance standard equally and thus cause no error with this arrangement, it will not correspondingly affect the susceptance standard arm.

Reference

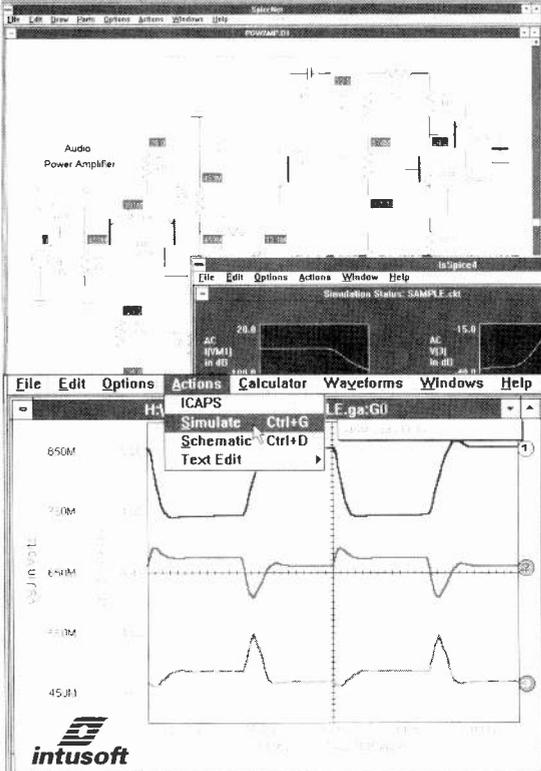1. Ian Hickman, *Design Brief*, EW+WW Oct 93, p972.

Low Cost Analog Simulation

ICAP/4Lite - Schematic Entry, SPICE and Waveform Display for £400




ICAP/4Lite, features schematic entry, powerful analog and mixed signal simulation, and extensive device libraries, all integrated in one easy to use environment. With ICAP/4Lite you can simulate all types of designs including Power, ASIC, RF, Mixed Mode, Control Systems, and Mixed Technologies.

Forget those other low cost and not quite SPICE systems. They cannot compare to ICAP/4Lite...

- **SPICE 3F based Simulator** - AC, DC, Transient, Temperature, Operating Point
- **UNLIMITED CIRCUIT SIZE**
- **Integrated Schematic Entry**
- **High Performance 32-bit Simulator**
- **Real time waveform display**
- **Over 500 Device Models Included**
- **Inexpensive upgrade path**
- **Windows and Windows NT**
- **Works w/other schematic entry programs**
- **Affordable Prices - £400**

Call or write for free information to:
 Technology Sources Ltd
 Falmouth Avenue
 NEWMARKET, Suffolk CB8 0LZ, UK

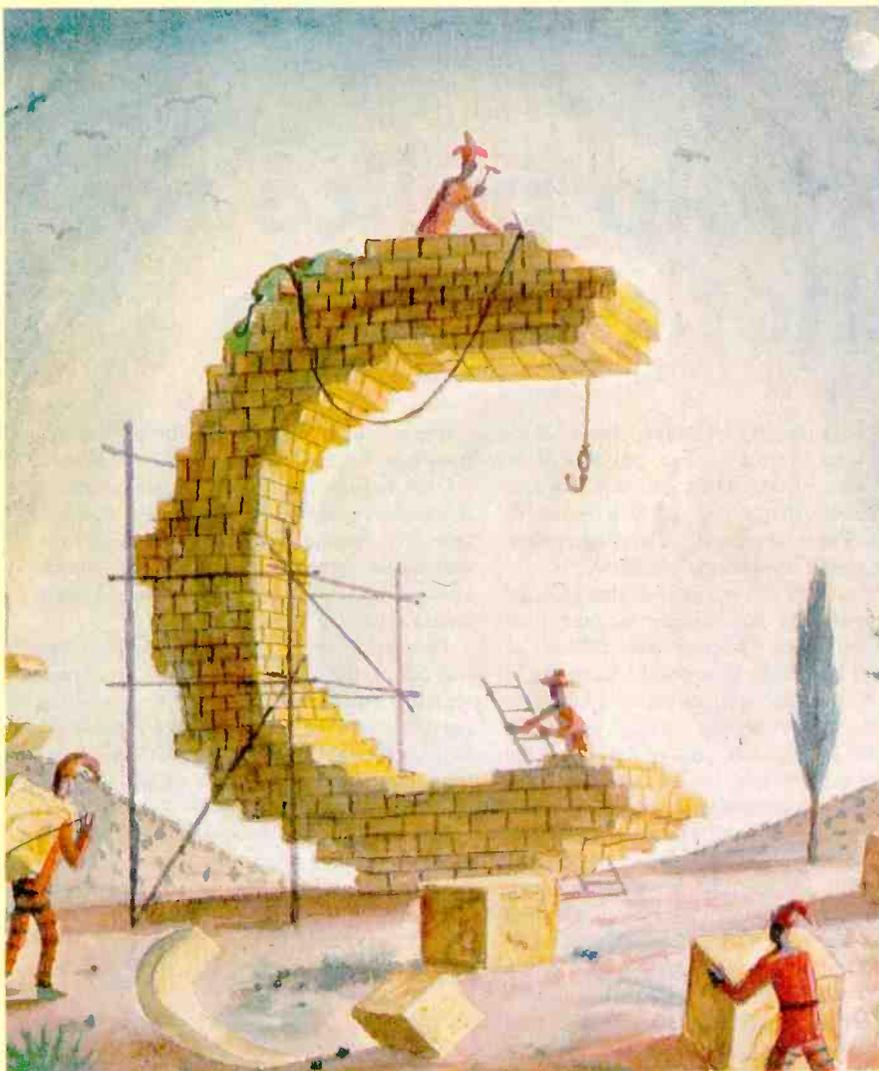Ph: 0638-561460
 Intl +44-638-561460
 Fax: 0638-561721
 Intl +44-638-561721



INTERFACING WITH C

by
HOWARD HUTCHINGS

Interfacing with C can be obtained from Lorraine Spindler, Room L333, Quadrant House, The Quadrant, Sutton, Surrey SM5 2AS.

Please make cheques for £14.95 (which includes postage and packing) payable to Reed Business Publishing Group.

Alternatively, you can telephone your order, quoting a credit card number. Telephone 081-652 3614.

A disk containing all the example listings used in this book is available at £29.96. Please specify size required.

C HERE!

If you have followed our series on the use of the C programming language, then you will recognise its value to the practising engineer.

But, rather than turning up old issues of the journal to check your design for a digital filter, why not have all the articles collected together in one book, *Interfacing with C*?

The book is a storehouse of information that will be of lasting value to anyone involved in the design of filters, A-to-D conversion, convolution, Fourier and many other applications, with not a soldering iron in sight.

To complement the published series, Howard Hutchings has written additional chapters on D-to-A and A-to-D conversion, waveform synthesis and audio special effects, including echo and reverberation. An appendix provides a "getting started" introduction to the running of the many programs scattered throughout the book.


This is a practical guide to real-time programming, the programs provided having been tested and proved. It is a distillation of the teaching of computer-assisted engineering at Humberside Polytechnic, at which Dr Hutchings is a senior lecturer.

Source code listings for the programs described in the book are available on disk.

Electronics help police to see the genetic picture

Britain's police are shortly set to make substantially more use of DNA fingerprinting in human identification. Tom Ivall explains how instrumentation is developing to make the process more practical.

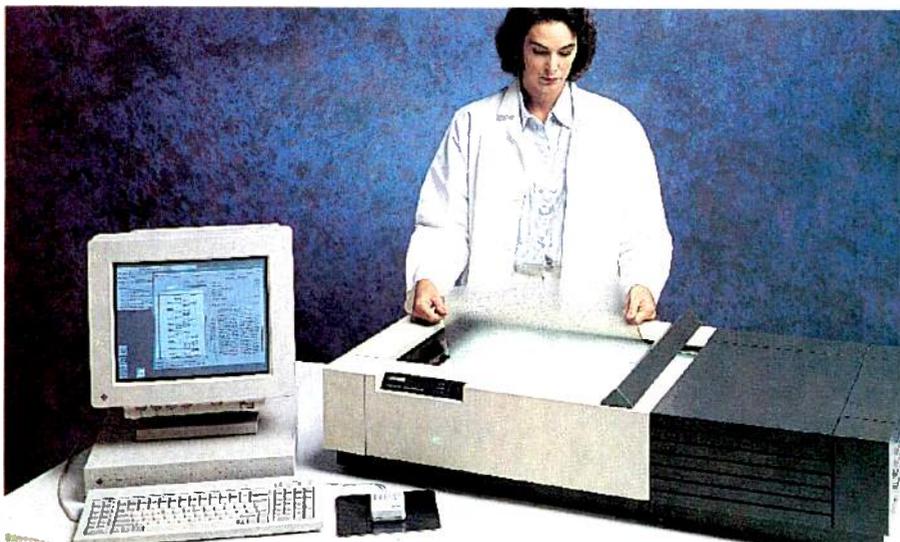Automated scanner made by Bio-Rad Laboratories. The GS Gene Reader scans autoradiograph films for DNA sequence analysis. Digitised images and a corresponding list of base letters are displayed on the workstation screen.



Under the latest Criminal Justice Bill, soon to become law, police will be able to take DNA samples, without consent, from anyone arrested for a recordable offence. The resulting molecular 'fingerprints' will be stored in a national database.

DNA testing for forensic and other identification purposes has already become well established since professor Alec Jeffreys of Leicester University invented the technique in 1985. Now public and commercial laboratories provide it as a service – though in the UK, Cellmark Diagnostics, part of Zeneca, is the only commercial lab.

The US government meanwhile, takes and holds samples from all its military personnel. Legal challenges have been made to the technique. But its validity is now accepted, because every individual has certain inherited patterns within the DNA molecule which are, for practical purposes, unique – better than 1 in 10^{12} – except for identical twins.

Only the methodology is being refined, with electronics and computers automating some of the processes.

Obtaining a DNA fingerprint


The technology for DNA fingerprinting is based on electrophoresis. In addition, optical scanning, digitisation and data analysis are used to map and list both the numbers and

sequences of the highly significant nitrogenous bases in the DNA molecule (see box).

DNA fingerprints are images derived from a molecular pattern in the body's cells. The patterns are composed of short sequences of base molecules, typically 20 bases long, which keep on repeating consecutively along a DNA strand at particular locations.

Two factors make the pattern specific to an individual: the number of repeats at a given location and hence the overall length of the repeating section, normally in the range 4000 to 20,000 base pairs; and the particular locations on the DNA molecule at which these repetitions occur.

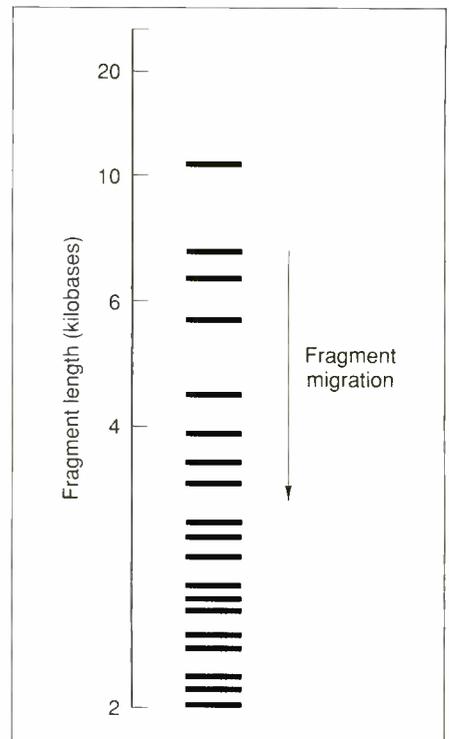Both features vary enormously from person to person and are inherited – so are useful for paternity investigations – but are not part of the functional genes.



DNA fingerprint, resembling a bar code, is an autoradiograph taken from an electrophoresis separation. Each dark band represents probe-selected DNA fragments of a particular length, measured in number of base molecules. The pattern is specific to an individual.

Key to detection

Detecting the molecular pattern is a little like probing an unknown lock with a known key to see if it fits. The probe is a short length of single-strand DNA with a known sequence of bases, derived by cloning from a human source. It will fit any complementary sequence on a single strand of the DNA being tested, so 'recognising' it in a process called hybridisation. The repeating sections detected are subsequently translated into an image by sorting the repeating sections into their different lengths. Then a purified solution of the DNA sample – commonly obtained from blood, saliva, hair roots or semen – is treated with one or more enzymes to cut the double-helix molecules at points on each side of the repeating section. The enzymes recognise particular,

short, base-pair sequences of the DNA and bind to them, slicing the duplex DNA at or near these positions.

The resulting assortment of fragments is placed in an electrophoresis cell and separated according to length (see box). A continuous distribution of fragment lengths is the outcome, from about 200 base pairs (bp) to 20kbp or more, along a 'lane' in the electrophoresis gel. Only those fragments containing the wanted repeat sections have to be identified.

Sodium hydroxide is used to split the DNA into single strands, then the gel is dried and its distribution of fragments is transferred to a solid support – normally a nylon membrane – by a process called Southern blotting.

The membrane is exposed for several hours

to a solution containing the probe, which is radioactively labelled. Binding occurs between the probe and only those lengths of separated-DNA-fragments which include the repeating sections.

X-ray film exposed to the membrane produces an autoradiograph (arg), and detected fragment lengths with their radioactive labelling stand out as a pattern of dark bands on the developed film. This is the fingerprint.

The process does not identify the actual locations of the repeating sections on the molecule. A different method detects repeat lengths at single, chosen molecule locations and produces only two bands on the arg. The first, multi-locus form is used mainly for paternity tests while the second, single-locus type, is used mainly for forensic work.

Structure of human DNA

DNA, or deoxyribonucleic acid, exists in most cells of living organisms – from single-celled bacteria to multicellular animals. In the nuclei of human cells, with proteins, it forms the substance of our 46 chromosomes, and carries the genes for the copying process when cells divide and proliferate to grow and repair the body.

Its form is polymeric, consisting of a long chain of smaller molecules of four distinct types called nucleotides. In a single human cell the total length is about 2m. Each nucleotide comprises three yet smaller molecules: a sugar ring, a phosphate group and a nitrogenous base formed from carbon, hydrogen, oxygen, nitrogen and phosphorus.

The four nucleotides have different nitrogenous bases – adenine (A), thymine (T), cytosine (C) and guanine (G) – and it is these that form the 'symbols' of the genetic and DNA fingerprinting information through their changing sequence along the structure.

The DNA molecule, the famous double helix can be likened to a twisted rope ladder. The two sides of the ladder are made up of alternating, covalently-bonded sugar and phosphate molecules from the nucleotides: the rungs are pairs of bases.

There are about 6×10^9 of these base-pairs in the DNA of a human cell. A complete 360° turn of the double helix is about ten base-pairs and 3.4nm long.

Base A always pairs with base T, and C with G, so the two halves of the ladder – single strands of the molecule – are complementary. The complementary bases are held together by relatively weak hydrogen bonds, allowing easy chemical separation of the two strands.

A single existing strand of DNA forms a template for a new, complementary strand to be synthesised onto it. This template also allows short segments of single-strand DNA from other sources to chemically bind to parts of it (hybridisation).

Called probes, such external segments with known base sequences are used in DNA fingerprinting to detect patterns of base sequences at different locations on the human molecule.

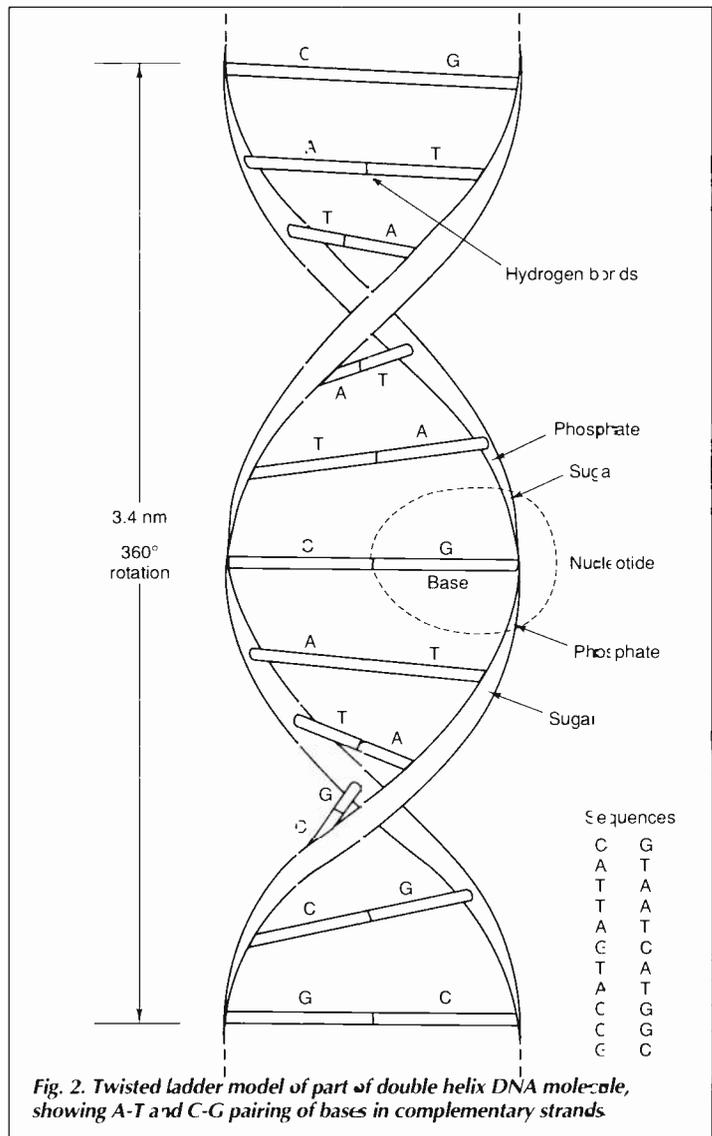


Fig. 2. Twisted ladder model of part of double helix DNA molecule, showing A-T and C-G pairing of bases in complementary strands

Electronic interpretation

Electronic scanning of the electrophoresis bands speeds up the interpretation process, reduces subjective errors in reading and produces data suitable for computer processing and analysis.

Scanning can be used directly on the fingerprints themselves but also, with a different electrophoresis separation, in sequence analysis, to find the A-G-C-T base sequences (see

box) in DNA samples and probes.

For fingerprint args the scanning system is essentially a digital densitometer. A video camera or linear ccd array scans the image and the resulting signals are digitised. One FBI system uses a quantisation of 512 by 480 pixels and 256 grey levels.

ARG bands are fuzzy and of varying density (not sharp as in the figure) so the information obtained is a profile of density against distance along the arg. From the peaks in this

profile an associated pc derives the positions of the bands and calculates the corresponding DNA fragment lengths.

Software can also locate the lane boundaries, correct image distortion, control the digitisation, perform statistical analysis, display data and graphics on the pc screen and finally control disk storage and/or transfer of data to a database.

Sequence analysis

DNA sequence analysis sometimes requires scanning systems to work on arg films and sometimes directly on electrophoresis gels. The biochemical reactions for determining base sequence involve four sets of copies of the DNA, each a gradually lengthening fragment ending on one of A-G-C-T. A four-well electrophoresis cell separates the fragments on the same gel, producing a succession of bands in each lane, A bands in one, G in another, C and T. From the relative distances of these bands along their four lanes, a continuing sequence of bases can be read off such as GTATGCCAT...

Electrophoresis bands are then scanned, translated into letters and then data transferred into a computer for processing and storage. The reader uses a 1728-element ccd linear array to scan arg films with a resolution of 50µm. Variable speed scanning improves resolution where the bands are closely spaced, economising on computer memory when high resolution is not needed.

CCD signals are digitised and transferred to a Sun Sparc workstation where pattern recognition software identifies lanes, corrects errors and translates into base letters. The workstation screen displays a four-lane band pattern and alongside it a list of the corresponding sequence of base letters. Reading and processing at a rate of about 50 bases/min are possible.

Sequence-analysis instruments aim at high accuracy as well as speed, eliminating the arg stage and possible reading errors by sensing the electrophoresis gel directly. They also work in real time by detecting fragment lengths and translating them into base letters while electrophoresis is proceeding.

Reaction products are combined and electrophoresed in a single gel lane, sandwiched between glass plates, and each is labelled with a fluorescent material of distinct emission wavelength.

As the DNA fragments thus identified approach the end of the 25cm lane they are illuminated by an argon ion laser beam, exciting the fluorophores so they emit light of different colours, a wavelength for each DNA base. A lens collects the light and focuses it through an optical bandpass filter, one for each colour, onto a photomultiplier tube. As electrophoresis proceeds, the pmt signal, a succession of peaks, is a-to-d converted and the resulting data is processed and translated into a sequence of DNA base letters. The complete optical system mechanically traverses up to 24 such single lanes, scanning them in succession. ■

Electrophoresis

Electrophoresis separates colloidal particles by size. Here the particles are different length fragments of DNA and are made to migrate through an electrolyte solution by applying an electric field.

Each fragment carries a net charge, resulting from its own molecular composition and the ions in the electrolyte. The moving force on each fragment is proportional to the product of the net charge and the electric field strength.

Rate of migration, the electrophoretic mobility, is measured as velocity per unit field strength. It depends partly on a potential difference, determined by the electrolyte, between the outside of the ion layer bonded to the fragment and parts of the electrolyte some distance away.

Other variables affecting it are viscosity and dielectric strength of the solution.

Mobility is directly proportional to the net charge on the fragment and inversely proportional to its size – smaller fragments travel faster.


But free liquid does not allow stable separation of fragments. So the electrolyte is supported in a porous medium, a slab of gel impregnated with the liquid. Fragments migrate through the gel pores when a voltage is applied across the slab through electrolyte reservoirs. Resolution of size separation is increased, because the gel acts like a mechanical sieve, allowing the shorter fragments through easily but retarding the longer ones.

When the electric field is switched off the DNA fragments end up distributed according to length at various distances along the gel.

In commercial systems the gel, made from agarose or polyacrylamide, is about 1mm thick and mounted either horizontally or vertically. At one end is a well, into which the purified DNA solution is placed. The electrolyte is chosen for its hydrogen ion concentration (pH) and acts as a buffer solution, to keep the pH relatively constant. DNA fragments have a net negative charge and are therefore attracted towards the anode electrode.

Voltages range from 30V to 100V for DNA fingerprinting, or up to about 3000V for DNA sequence analysis. Time required for separation is normally several hours. Using a number of wells in the gel enables different DNA samples to be electrophoresed simultaneously for comparison, forming parallel electrophoresis lanes in the gel.

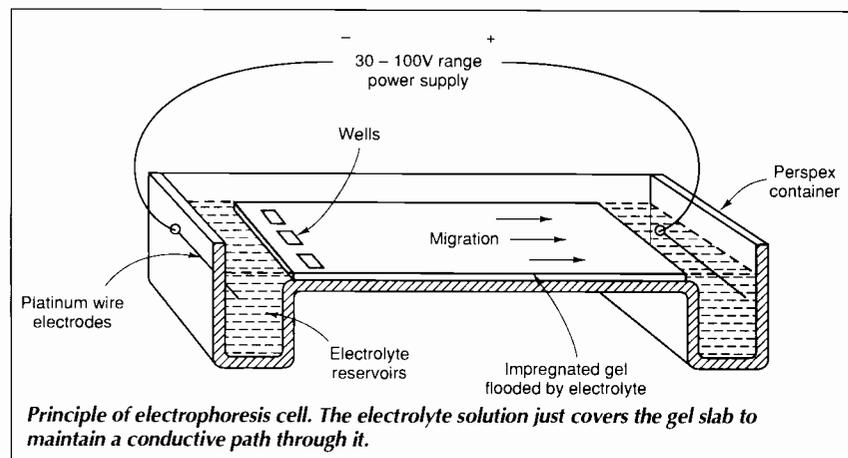Resolution of larger DNA fragments (above 100kb) can be improved by periodically reversing the electric field and hence direction of migration. Typically the cyclic forward:reverse time ratio is 3:1 and times can be anything from seconds to hours. Programmable pulse generators are used for this purpose.



£1 BARGAIN PACKS

In fact...cheaper than £1 because if you buy 10 you can choose one other and receive it free!

- 1 x 12v Stepper Motor. 7.5 degree. Order Ref: 910.
- 1 x 10 pack Screwdrivers. Order Ref: 909.
- 2 x 5 amp Pull Cord Ceiling Switches. Brown. Order Ref: 921.
- 5 x reels Insulation Tape. Order Ref: 911.
- 4 x 14mm Ball-races. Order Ref: 912.
- 2 x Cord Grip Switch lamp Holders. Order Ref: 913.
- 1 x DC Voltage Reducer. 12v-6v. Order Ref: 916.
- 1 x 10 amp 40v Bridge Rectifier. Order Ref: 889.
- Lightweight Stereo Headphones. Moving coil so superior sound. Order Ref: 896.
- 2 x 25W Crossovers. For 4ohm loudspeakers. Order Ref: 22.
- 2 x Nicad Constant Current Chargers. Easily adaptable to charge almost any nicad battery. Order Ref: 30.
- 18v-0-18v 10va Mains Transformer. Order Ref: 813.
- 2 x White Plastic Boxes. With lids, approx. 3" cube. Lid has square hole through the centre so these are ideal for light operated switch. Order Ref: 132.
- 2 x Reed Relay Kits. You get 8 reed switches and 2 coil sets. Order Ref: 148.
- 12v-0-12v 6va Mains Transformer. PCB mounting. Order Ref: 938.
- 1 x Big Pull Solenoid. Mains operated. Has 1/2" pull. Order Ref: 871.
- 1 x Big Push Solenoid. Mains operated. Has 1/2" push. Order Ref: 872.
- 1 x Mini Mono Amp. 3W into 4 ohm speaker or 1W into 8 ohm. Order Ref: 495.
- 1 x Mini Stereo 1W Amp. Order Ref: 870.
- 15v DC 150ma PSU. Nicely cased. Order Ref: 942.
- 1 x In-Flight Stereo Unit is a stereo amp. Has two most useful mini moving coil speakers. Made for BOAC passengers. Order Ref: 29.
- 1 x 0-1mA Panel Meter. Full vision fact 70mm square. Scaled 0-100. Order Ref: 756.
- 2 x Lithium Batteries. 2.5V penlight size. Order Ref: 874.
- 2 x 3m Telephone Leads. With BT flat plug. Ideal for phone extensions, fax, etc. Order Ref: 552.
- 1 x 12V Solenoid. Has good 1/2" pull or could push if modified. Order Ref: 232.
- 4 x In-Flex Switches. With neon on/off lights, saves leaving things switched on. Order Ref: 7.
- 2 x 6V 1A Mains Transformers. Upright mounting with fixing clamps. Order Ref: 9.
- 2 x Humidity Switches. As the air becomes damper, the membrane stretches and operates a micro switch. Order Ref: 32.
- 5 x 13A Rocker Switch. Three tags so on/off, or changeover with centre off. Order Ref: 42.
- Mini Cassette Motor. 9v. Order Ref: 944.
- 1 x Suck or Blow-Operated Pressure Switch. Or it can be operated by any low pressure variation such as water level in tanks. Order Ref: 67.
- 1 x 6V 750mA Power Supply. Nicely cased with mains input and 6V output lead. Order Ref: 103A.
- 2 x Stripper Boards. Each contains a 400V 2A bridge rectifier and 14 other diodes and rectifiers as well as dozens of condensers, etc. Order Ref: 120.
- 12 Very Fine Drills. For PCB boards etc. Normal cost about 80p each. Order Ref: 128.
- 5 x Motors for Model Aeroplanes. Spin to start so needs no switch. Order Ref: 134.
- 6 x Microphone Inserts. Magnetic 400 ohm, also act as speakers. Order Ref: 139.
- 6 x Neon Indicators. In panel mounting holders with lens. Order Ref: 180.
- 1 x In-Flex Solderstat. Keeps your soldering iron etc always at the ready. Order Ref: 196.
- 1 x Mains Solenoid. Very powerful as 1/2" pull, or could push if modified. Order Ref: 199.
- 1 x Electric Clock. Mains operated. Put this in a box and you need never be late. Order Ref: 211.
- 4 x 12V Alarms. Makes a noise about as loud as a car horn. All brand new. Order Ref: 221.
- 2 x (6"x4") Speakers. 16 ohm 5 watts, so can be joined in parallel to make a high wattage column. Order Ref: 243.
- 1 x Panostat. Controls output of boiling ring from simmer up to boil. Order Ref: 252.
- 2 x Oblong Push Switches. For bell or chimes, these can switch mains up to 5A so could be foot switch if fitted in pattress. Order Ref: 263.
- 50 x Mixed Silicon Diodes. Order Ref: 293.
- 1 x 6 Digit Mains Operated Counter. Standard size but counts in even numbers. Order Ref: 28.
- 2 x 6V Operated Reed Relays. One normally on, other normally closed. Order Ref: 48.
- 1 x Cabinet Lock. With two keys. Order Ref: 55.
- 6 1/2" 8 ohm 5 watt Speaker. Order Ref: 824.
- 1 x Shaded Pole Mains Motor. 3/4" stack, so quite powerful. Order Ref: 85.
- 2 x 5 Aluminium Fan Blades. Could be fitted to the above motor. Order Ref: 86.
- 1 x Case. 3 1/2"x2 1/4"x1 1/4" with 13A socket pins. Order Ref: 845.
- 2 x Cases. 2 1/2"x2 1/4"x1 1/4" with 13A pins. Order Ref: 565.
- 4 x Luminous Rocker Switches. 10A mains. Order Ref: 793.
- 4 x Different Standard V3 Micro Switches. Order Ref: 340.
- 4 x Different Sub Min Micro Switches. Order Ref: 313.

BARGAINS GALORE

- Speed Controller for 12v DC Motors. Suitable for motors with horse power's up to one third and drawing currents up to 30A. Gives very good control and speed. Uses mosfets and is based on a well tried circuit which appeared in the *Model Engineer* some time ago. The complete kit with case and on/off switch is available, price £18. Order Ref: 18PB.
 - Ex-British Telecom Insulation Tester Offer. We have a quantity of these that are slightly faulty. There has been no attempt at repairing them. They are not missing any parts so should be repairable. The moving coil movement is in perfect working order so even if you cannot repair the instrument to perform all its original functions, you would be able to use it for another instrument that you need. We supply a circuit diagram of the instrument and chances are that you will find the fault and be able to repair it. Price of the instrument with circuit diagram is £3. Order Ref: 3P176.
 - Fig 8 Flex. Fig. 8 flat white pvc, flexible with .4 sq. mm cores. Ideal for speaker extensions and bell circuits. Also adequately insulated for mains lighting. 50m coil £2. Order Ref: 2P345. 12m coil £1. Order Ref: 1014.
 - Friedland Undermode Bell. Their ref: 792. A loud ring but very neat, 3" diameter, complete with wall fixing screws, £4. Order Ref: 4P75.
 - 12v 10amp Switch Mode Power Supply. For only £9.50 and a little bit of work because you have to convert our 135W PSU. Modifications are relatively simple - we supply instructions. Simply order PSU Ref: 9.5P2 and request modification details. Price still £9.50.
 - Are you making Mini Bugs? We can offer the ideal box. White plastic without any decoration or printing. This has an on/off switch in the top left-hand corner and a hole just above to take a telescopic or wire aerial. The case is large enough to take a PP3 battery and a PCB and when finished it will have a really professional look. Box with switch £1. Order Ref: 1006. Size approximately 4"x3"x1 1/2" thick and its cover is held by four screws.
 - Siren/Horn/Hooter/Klaxon. It isn't any of these - it does the same job but is quite nice to look at and could even be described as ornamental. It is Swiss made and in a grey plastic case, could be free standing or screwed down indoors or out. It is mains driven and when switched on it makes a shocking noise (its loudness is adjustable). You could switch it on to scare an intruder or arrange for your burglar alarm to do the same. Price £5. Order Ref: 5P226.
 - Medicine Cupboard Alarm. Or it could be used to warn when any cupboard door is opened. The light shining on the unit makes the bell ring. Completely built and really cased, requires only a battery. £3. Order Ref: 3P155.
 - Don't Let It Overflow! Be it bath, sink, cellar, sump or any other thing that could flood. This device will tell you when the water has risen to the pre-set level. Adjust the lever quite a useful range. Neatly cased for wall mounting, ready to work when battery fitted. £3. Order Ref: 3P154.
 - Very Powerful Mains Motor. With extra long (2 1/2") shafts extending out each side. Makes it ideal for a reversing arrangement for: as you know, shaded pole motors are not reversible. £3. Order Ref: 3P157.
 - Solar Panel Bargain. Gives 3v at 200mA. Order Ref: 2P324.
- £1 Super Bargain**

12V axial fan for only £1, ideal for equipment cooling, brand new, made by West German company. Brushless so virtually everlasting. Needs simple transistor drive circuit, we include diagram. Only £1. Order Ref: 919. When we supply this we will include a list of approximately 800 of our other £1 bargains.
- 40W-250W Light Dimmers. On standard plate or put directly in place of flush switch. Available in colours, green, red, blue and yellow. £2.50, Order Ref: 2.5P9. Or on standard 3x3 cream metal switch plate, £3. Order Ref: 3P174.
 - 45A Double Pole Mains Switch. Mounted on a 6x3 1/2 aluminium plate, beautifully finished in gold, with pilot light. Top quality, made with MEM, £2. Order Ref: 2F316.
 - Amstrad 3" Disk Drive. Brand new and standard replacement for many Amstrad and other machines. £20, Order Ref: 20P28.
 - Touch Dimmers 40W-250W. No knob to turn, just finger on front plate, will give more, or less light, or off. Silver plate on white background, right size to replace normal switch £5, Order Ref: 5P230.
- Motorize that Trolley!**

You could with Sinclair C5 1/3rd hp
12v battery motor
Still available, price £21. Order Ref: 21P1
- 12/24 DC Solenoid. The construction of this is such that it will push or pull. With 24V this is terrifically powerful but is still quite good at 12V. £1. Order Ref: 877.
 - Don't Stand Out In The Cold Our 12m telephone extension lead has a flat BT socket one end and flat BT plug other end. £2. Order Ref: 2P338.
 - 20W 5" 4 Ohm Speaker mounted on baffle with front grille, £3. Order Ref: 3P145. Matching 4 ohm 20W tweeter on separate baffle. £1.50, Order Ref: 1.5P9.
- LCD 3 1/2" Digit Panel Meter**

This is a multi range voltmeter/ammeter using the A-D converter chip 7106 to provide 5 ranges each of volts and amps. Supplied with full data sheet. Special snip price of £12. Order Ref: 12P19.
- Telephone Extension Wire 4 core correctly colour coded, intended for permanent extensions, 25m coil, £2. Order Ref: 2P339.
 - High Power Switch Mode PSU. Normal mains input, 3 outputs: +12V at 4A, +5V at 16A and -12V at 1/2A. Completely enclosed in plated steel case. Brand new. Our special offer price of £9.50, Order Ref: 9.5P1.
 - Philips 9" High Resolution Monitor. Black and white in metal frame for easy mounting. Brand new, still in maker's packing, offered at less than price of tube alone, only £15, Order Ref: 15P1.
 - High Current AC Mains Relay This has a 230v coil and changeover switch rated at 15A with PCB mounting with clear plastic cover. £1. Order Ref: 965.

BARGAINS GALORE

- Ultra Thin Drills, actually 0.3mm. To buy these regular costs a fortune. However, these are packed in half dozens and the price to you is £1 per pack. Order Ref: 797B.
 - You Can Stand On It! Made to house GPO telephone equipment, this box is extremely tough and would be ideal for keeping your small tools in, internal size approx. 10 1/2"x4 1/2"x5 1/2" high. Complete with carrying strap, price £2. Order Ref: 2P283B.
 - Ultra Sonic Transducers. Two metal cased units, one transmits, one receives. Built to operate around 40kHz. Price £1.50 the pair, Order Ref: 1.5P/4.
 - Power Supply with Extras. Mains input is fused and filtered and the 12V DC output is voltage regulated. Intended for high class equipment, this is mounted on a PCB and, also mounted on the board but easily removed, are two 12V relays and piezo sounder, £3. Order Ref: 3P80B.
 - Insulation Tester with Multimeter. Internally generates voltages which enable you to read insulation directly in megohms. The multimeter has four ranges, AC/DC volts, 3 ranges DC milliamperes, 3 ranges resistance and 5 amp range. These instruments are ex-British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50, yours for only £7.50 with leads, carrying case £2 extra. Order Ref: 7.5P/4.
 - Mains Isolation Transformer. Stops you getting "to earth" shocks. 230V in and 230V out. 150 watt. £7.50, Order Ref: 7.5P/5 and a 250W version is £10, Order Ref: 10P97.
 - Mains 230V Fan. Best make "PAPST", 4 1/2" square, metal blades, £8, Order Ref: 8P8.
 - 2MW Laser. Helium neon by Philips, full spec. £30, Order Ref: 30P1. Power supply for this in kit form with case is £15, Order Ref: 15P16, or in larger case to house tube as well £18, Order Ref: 18P2. The larger unit, made up, tested and ready to use, complete with laser tube £69, Order Ref: 69P1.
 - 12v Bohm speaker, only £1.50 and waterproof.
 - Solar Charger. Holds 4AA nicads and recharges these in 8 hours, in very neat plastic case £6, Order Ref: 6P3.
 - Ferrite Aerial Rod. 8" long x 3/8" diameter, made by Mullard. Complete with two coils, 2 for £1, Order Ref: 832P.
 - Air Spaced Trimmer Caps. 2-20pf, ideal for precision tuning UHF circuits, 4 for £1, Order Ref: 818B.
 - Modem Amstrad FM240. As new condition but customer return, so you may need to fault find. £6, Order Ref: 6P34.
 - Amstrad Fower Unit. 13.5V at 1.9A or 12V at 2A enclosed and with leads and output plug, normal mains input £6, Order Ref: 6P23.
 - 80W Mains Transformer. Two available, good quality, both with normal primaries and upright mounting, one is 20V 4A, Order Ref: 3P106, the other 40V 2A, Order Ref: 3P107, only £3 each.
 - Project Box. Size approx. 8"x4"x4 1/2" metal, sprayed grey, louvred ends for ventilation otherwise undrilled. Made for GPO so best quality, only £3 each, Order Ref: 3P74.
 - Sentinel Component Board. Amongst hundred of other parts, this has 15 ICs, all plug in so do not need soldering. Cost well over £100, yours for £4, Order Ref: 4P67.
 - Sinclair 9" 2.1A Power Supply. Made to operate the 138K Spectrum Plus 2, cased with input and output leads. Originally listed at around £15, are brand new, our price is only £3, Order Ref: 3P151.
 - Experimenting with Valves. Don't spend a fortune on a mains transformer, we can supply one with standard mains input and secs. of 250-0-250V at 75mA and 6.3V at 3A, £5, Order Ref: 5P167.
 - 15W 8 Ohm 8" Speaker & 3" Tweeter. Made for a discontinued high quality music centre, gives real hi-fi and only £4 per pair, Order Ref: 4P57.
 - Water Pump. Very powerful, mains operated, £10, Order Ref: 10P71.
 - 0-1mA Full Vision Panel Meter. 2 3/4" square, scaled 0-100 but scale easily removed for re-writing, £1 each, Order Ref: 756.
 - VU Meter. Illuminate this from behind becomes on/off indicator as well, 1 1/2" square, 75 each, Order Ref: 366.
 - Amstrad Keyboard Model K85. This is a most comprehensive keyboard, having over 100 keys including, of course, full numerical and qwerty. Brand new, still in maker's packing, £5, Order Ref: 5P202.
 - 1 RPM Motor. This is only 2W so will not cost much to run. Speed is ideal for revolving mirrors or lights. £2, Order Ref: 2P328.
 - Unusual Solenoid. Solenoids normally have to be energised to pull in and hold the core, this is a disadvantage where the appliance is left on for most of the time. We now have magnetic solenoids which hold the core until a voltage is applied to release it. £2, Order Ref: 2P327.
 - Mains Filter. Resin impregnated, nicely cased, pcb mounting. £2, Order Ref: 2P315.
 - 200VA Mains Transformer. Secondary voltages 8v-0-8v. So you could have 16v at 12A or 8v at 25A. Could be ideal for car starter charger, soil heating, spot welding, carbon rod welding or driving high powered amplifiers etc. £15, Order Ref: 15P51.
- Prices include VAT. Send cheque/postal order or ring and quote credit card number. Add £3 post and packing. Orders over £25 post free.

**M&B ELECTRICAL
SUPPLIES LTD**
Pilgrim Works (Dept. WW),
Stairbridge Lane, Bolney,
Sussex RH17 5PA
Telephone (0444) 881965 -
phone for Fax
Callers to 12 Boundary Road,
Hove, Sussex

NEW LOW PRICE - NEW COLOUR HP141T SPECTRUM ANALYSERS TESTED

- HP141T + 8552A or B IF - 8553B RF - 1kHz - 110Mc/s - A IF £600 or B IF - £700.**
HP141T + 8552A or B IF - 8554B RF - 100kHz - 1250Mc/s - A IF £800 or B IF - £900.
HP141T + 8552A or B IF - 8555A RF - 10Mc/s - 18GHz - A IF £1400 or B IF - £1600. The mixer in this unit costs £1000, we test every one for correct gain before despatch.
HP141T + 8552A or B IF - 8556A RF - 20Hz - 300kHz - A IF £600 or B IF - £700.

HP ANZ UNITS AVAILABLE SEPARATELY NEW COLOUR - TESTED

- HP141T Mainframe - £350 - 8552A IF - £200 - 8552B IF - £300 - 8553B RF - 1kHz - 110Mc/s - £200 - 8554B RF - 100kHz - 1250Mc/s - £400. 8555A RF - 10Mc/s - 18GHz - £1000. 8556A RF - 20Hz - 300kHz - £250.**
HP8443A Tracking Generator Counter - 100kHz - 110Mc/s - £300 - £400.
HP8445B Tracking Pre-selector DC - 18GHz - £400 - £600 or HP8445A - £250.
HP8444A Tracking Generator - £750 - 1300Mc/s.
HP8444A Opt 059 Tracking Generator - £1000 - 1500Mc/s.

SPECIAL OFFER - 14 ONLY HP140T (NON-STORAGE)

- Mainframe Plus 8552A IF Plug-In Plus 8556A RF Plug-In 20Hz - 300kHz Plus 8553B RF Plug-In 1kHz - 110Mc/s. Tested with instructions - £700.**

Marconi TF2008 - AM-FM signal generator - also sweeper - 10Kc/s - 510Mc/s - from £250 - tested to £400 as new with manual - probe kit in wooden carrying box.
 HP Frequency comb generator type 8406 - £400.
 HP Vector Voltmeter type 8405A - £400 to £600 - old or new colour.
 HP Sweep Oscillators type 8690 A & B + plug-ins from 10Mc/s to 18GHz also 18-40GHz. P.O.R..
 HP Network Analyzer type 8407A + 8412A + 8501A - 100Kc/s - 110Mc/s - £500 - £1000.
 HP Amplifier type 8447A - 1.400Mc/s £200 - HP8447F. 1-1300Mc/s £400.
 HP Frequency Counter type 5340A - 18GHz £1000 - rear output £800.
 HP 8410 - A - B - C Network Analyzer 110Mc/s to 12GHz or 18GHz - plus most other units and displays used in this set-up - 8411a - 8412 - 8413 - 8414 - 8418 - 8740 - 8741 - 8742 - 8743 - 8746 - 8650. From £1000.
 Rcal/Dana 9301A - 9302 RF Millivoltmeter - 1.5-2GHz - £250-£400.
 Rcal/Dana Counters 9915M - 9916 - 9917 - 9921 - £150 to £450. Fitted FX standards.
 Rcal/Dana Modulation Meter type 9009 - 8Mc/s - 1.5GHz - £250.
 Marconi RCL Bridge type TF2700 - £150.
 Marconi/Saunders Signal Sources type - 6058B - 6070A - 6055A - 6059A - 6057A - 6056 - £250-£350. 400Mc/s to 18GHz.
 Marconi TF1245 Circuit Magnification meter + 1246 & 1247 Oscillators - £100-£300.
 Marconi microwave 6600A sweep osc., mainframe with 6650 PI - 18-26.5GHz or 6651 PI - 26.5-40GHz - £1000 or PI only £600. MF only £250.
 Marconi distortion meter type TF2331 - £150. TF2331A - 200.
 Tektronix Plug-Ins 7A13 - 7A14 - 7A18 - 7A24 - 7A26 - 7A11 - 7M11 - 7S11 - 7D10 - 7S12 - S1 - S2 - S6 - S52 - PG506 - SC504 - SG502 - SG503 - SG504 - DC503 - DC508 - DD501 - WR501 - DM501A - FG501A - TG501 - PG502 - DC505A - FG504 - 7B80 + 85-7B92A
 Gould J3B test oscillator + manual - £200.
 Tektronix Mainframes - 7603 - 7623A - 7613 - 7704A - 7844 - 7904 - TM501 - TM503 - TM506 - 7904 - 7834 - 7104 - 7623 - 7633.
 Alltech 757 Spectrum Analyser - 001 22GHz - Digital storage - readout - £2000.
 Marconi 6155A Signal Source - 1 to 2GHz - LED readout - £400.
 Barr & Stroud Variable filter EF3 0.1Hz - 100Kc/s + high pass + low pass - £150.
 Marconi TF2163S attenuator - 1GHz. £200.
 Farnell power unit H60/50 - £400 tested. H60/25 - £250.
 Rcal/Dana 9300 RMS voltmeter - £250.
 HP 8750A storage normalizer - £400 with lead + S.A or N.A Interface.
 Marconi TF2330 or TF2330A wave analysers - £100-£150.
 Rcal/Dana signal generator 9082 - 1.5-520Mc/s - £500.
 Rcal/Dana signal generator 9082H - 1.5-520Mc/s - £600.
 Tektronix - 7S14 - 7T11 - 7S11 - 7S12 - S1 - S2 - S39 - S47 - S51 - S52 - S53 - 7M11.
 Marconi mod meters type TF2304 - £250.
 HP 5065A rubidium vapour FX standard - £2.5k.
 Systron Donner counter type 6054B - 20Mc/s - 24GHz - LED readout - £1k.
 Rcal/Dana 9083 signal source - two tone - £250.
 Systron Donner - signal generator 1702 - synthesized to 1GHz - AM/FM - £600.
 Tektronix TM515 mainframe + TM5006 mainframe - £450 - £850.
 Rhodes & Schwartz power signal generator SLRD-280 - 2750Mc/s - £250-£600.
 Ball Efratom rubidium standard PT256B-FRKL - £1000.
 Farnell electronic load type RB1030-35 - £350.
 Rcal/Dana counters - 9904 - 9905 - 9906 - 9915 - 9916 - 9917 - 9921 - 50Mc/s - 3GHz - £100-£450 - all fitted with FX standards.
 HP4815A RF vector impedance meter c/w probe - £500-£600.
 Marconi TF2092 noise receiver. A, B or C plus filters - £100-£350.

Marconi TF2091 noise generator. A, B or C plus filters - £100-£350.
 HP180TR, HP182T mainframes £300-£500.
 Fluke 8506A thermal RMS digital multimeter. £400.
 Philips panoramic receiver type PM7900 - 1 to 20GHz - £400.
 Marconi 6700A sweep oscillator + 6730A - 1 to 2GHz - £500.
 HP8505A network ANZ + 8503A S parameter test set + 8501A normalizer - £4k.
 Rcal/Dana VLF frequency standard equipment. Tracer receiver type 900A + difference meter type 527E + rubidium standard type 9475 - £2750.
 HP signal generators type 626 - 628 - frequency 10GHz - 21GHz.
 HP 432A - 435A or B - 436A - power meters + powerheads - Mc/s - 40GHz - £200-£1000.
 Bradley oscilloscope calibrator type 192 - £600.
 Barr & Stroud variable filter EF3 0.1Hz - 100Kc/s + high pass + low pass - £150.
 Marconi TF2370 spectrum ANZ - 110Mc/s - £900.
 Marconi TF2370 spectrum ANZ + TK2375 FX extender 1250Mc/s + 1st gen - £1.5k.
 HP8614A signal generator 800Mc/s - 2.4GHz, new colour £400.
 HP8616A signal gen 1.8GHz - 4.5GHz, new colour £400.
 HP 3325A syn function gen 20Mc/s - £1500.
 HP 3336A or B syn level generator - £500-£600.
 HP 3586B or C selective level meter - £750-£1000.
 HP 3575A gain phase meter 1Hz - 13Mc/s - £400.
 HP 8671A syn microwave 2 - 6.2GHz - £2k.
 HP 8683D S/G microwave 2.3 - 13GHz - opt 001 - 003 - £4.5k.
 HP 8660 A-B-C syn S/G. AM + FM + 10Kc/s to 110Mc/s PI - 1Mc/s to 1300Mc/s - 1Mc/s to 2500Mc/s - £750-£2800.
 HP 8640B S/G AM-FM 512Mc/s or 1024Mc/s. Opt 001 or 002 or 003 - £800-£1250.
 HP 8656A S/G AM-FM 0.1 - 990Mc/s - £1500.
 HP 8622B Sweep PI - 01 - 2.4GHz + ATT - £1750.
 HP 8629A Sweep PI - 2 - 18GHz - £1000.
 HP 86290B Sweep PI - 2 - 18GHz - £1250.
 HP 86 Series PI's in stock - splitband from 10Mc/s - 18.6GHz - £250-£1k.
 HP 8620C Mainframe - £250. IEEE - £500.
 HP 8615A Programmable signal source - 1MHz - 50Mc/s - opt 002 - £1k.
 HP 8601A Sweep generator. 1 - 110Mc/s - £300.
 HP 4261A LCR meter + 16038A test leads - £400.
 HP 4271B LCR meter 1MHz digital meter + 16063A test adaptor - £850.
 HP 4342A Q meter 22kHz - 70Mc/s 16462A - qty of 10 inductors - £850.
 HP 3488A HP - IB switch control unit - £500 + control modules various - £175 each.
 HP 3561A Dynamic signal ANZ - £3k.
 HP 8160A 50Mc/s programmable pulse generator - £1400.
 HP 853A MF ANZ + 8558B - 0.1 - 1500Mc/s - £2500.
 HP 8349A Microwave Amp 2 - 20GHz Solid state - £1500.
 HP 3585A Analyser 20Hz - 40Mc/s - £4k.
 HP 8569B Analyser. 01 - 22GHz - £5k.
 HP 3580A Analyser 5Hz - 50kHz - £1k.
 HP 1980B Oscilloscope measurement system - £600.
 HP 3455A Digital voltmeter - £500.
 HP 3437A System voltmeter - £300.
 HP 3581C Selective voltmeter - £500.
 HP 5370A Universal time interval counter - £450.
 HP 5335A Universal counter - 200Mc/s - £500.
 HP 5328A Universal counter - 500Mc/s - £250.
 HP 6034A System power supply - 0 - 60V - 0 - 10 amps - £500.
 HP 3960A 3964A Instrumentation tape recorders - £300-£500.
 HP 5150A Thermal printer - £250.
 HP 1645A Data error analyser - £150.
 HP 4437A Attenuator - £150.
 HP 3717A 70Mc/s modulator - £400.
 HP 3710A - 3715A - 3716A - 3702B - 3703B - 3705A - 3711A - 3791B - 3712A - 3793B microwave link analyser - P.O.R.
 HP 3730A + B RF down converter - P.O.R.
 HP 3552A Transmission test set - £400.
 HP 3763A Error detector - £500.
 HP 3764A Digital transmission analyser - £600.
 HP 3770A Amp delay distortion analyser - £400.
 HP 3780A Pattern generator detector - £400.
 HP 3781A Pattern generator - £400.
 HP 3781B Pattern generator (bell) - £300.
 HP 3782A Error detector - £400.
 HP 3782B Error detector (bell) - £300.
 HP 3785A Jitter generator + receiver - £750-£1k.
 HP 8006A Word generator - £100-£150.
 HP 8016A Word generator - £250.
 HP 8170A Logic pattern generator - £500.
 HP 59401A Bus system analyser - £350.
 HP 59500A Multiprogrammer HP - IB - £300.
 Philips PM5390 RF syn - 0.1 - 1GHz - AM + FM - £1250.
 Philips PM5519 Colour T.V. pattern generator - £250.
 S.A. Spectral Dynamics SD345 spectrascope - £2500.
 Tektronix R7912 Transient waveform digitizer - programmable - £400.
 Tektronix 496 Analyzer 1kHz - 1.8GHz - £3.5k.
 Tektronix TR503 + TM503 tracking generator 0.1 - 1.8GHz - £1k - or TR502.
 Tektronix 576 Curve tracer + adaptors - £900.
 Tektronix 577 Curve tracer + adaptors - £900.
 Tektronix 1502/1503 TDR cable test set - £1000.
 Tektronix 7L5 LF analyser - 0 - 5Mc/s - £800. OPT 25 - £1000.
 Tektronix AM503 Current probe + TM501 m/frame - £1000.
 Tektronix SC501 - SC502 - SC503 - SC504 oscilloscopes - £75-£350.
 Tektronix 465 - 465B - 475 - 2213A - 2215 - 2225 - 2235 - 2245 - £250-£1000.
 Kikusui 100Mc/s Oscilloscope COS6100M - £350.
 Farnell PSG520 Signal generator - £400.
 Nicolet 3091 LF oscilloscope - £1000.
 Rcal 1991 - 1992 - 1988 - 1300Mc/s counters - £500-£900.
 Tek 2445 150Mc/s oscilloscope - £1400.
 Fluke 80K-40 High voltage probe in case - BN - £100.
 Rcal Recorders - Store 4 - 4D - 7 - 14 channels in stock - £250 - £500.
 Rcal Store Horse Recorder & control - £400-£750 Tested.
 EIP 545 microwave 18GHz counter - £1200.
 Fluke 510A AC ref standard - 400Hz - £200.
 Fluke 355A DC voltage standard - £300.
 Schlumberger 5229 Oscilloscope - 500Mc/s - £500.
 Solartron 1170 FX response ANZ - LED display - £280.
 Wiltron 610D Sweep Generator + 6124C PI - 4 - 8GHz - £400.
 Wiltron 610D Sweep Generator + 61084D PI - 1Mc/s - 1500Mc/s - £500.
 Time Electronics 9814 Voltage calibrator - £750.
 Time Electronics 9811 Programmable resistance - £600.
 Time Electronics 2004 D.C. voltage standard - £1000.
 HP 8699B Sweep PI YIG oscillator .01 - 4GHz - £300. 8690B MF - £250. Both £500.
 Schlumberger 1250 Frequency response ANZ - £2500.
 Dummy Loads & power att up to 2.5 kilowatts FX up to 18GHz - microwave parts new and ex equip - relays - attenuators - switches - waveguides - Yigs - SMA-APC7 plugs - adaptors, etc.
 B&K Items in stock - ask for list.
 W&G Items in stock - ask for list.
 Power Supplies Heavy duty + bench in stock - Farnell - HP - Weir - Thurlby - Rcal etc. Ask for list.

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. SAE FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS. AVAILABILITY OR PRICE CHANGE. VAT AND CARRIAGE EXTRA
 ITEMS MARKED TESTED HAVE 30 DAY WARRANTY. WANTED: TEST EQUIPMENT-VALVES-PLUGS AND SOCKETS-SYNCRS-TRANSMITTING AND RECEIVING EQUIPMENT ETC.

Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. No: (0274) 684007. Fax: 651160



NEW PRODUCTS CLASSIFIED

Please quote "Electronics World + Wireless World" when seeking further information

ACTIVE

Asics

Cost-effective asics. Although small asics are out of fashion, they can be much cheaper to develop. Accordingly, Sharp has a special deal on asics with up to 2000 gates, which will handle glue logic, pals and eplds in one chip. Minimum quantity is 5000 pieces and the typical once-only cost is around £10000, design time being 1-4 weeks. Hero Electronics Ltd. Tel., 0525 4055015; fax, 0525 402383.

A-to-d and d-to-a converters

Eighth-order 100kHz lp filter. *LTC1066-1* by Linear Technology is an eighth-order, pin-selectable, elliptical or linear-phase low-pass filter that offers up to 100kHz cut-off and 14-bit dc gain linearity. It has a 94dB signal:noise ratio and is suitable for use as an anti-aliasing or smoothing filter in 12 or 14-bit data acquisition. The device is clock-tunable from 10Hz to 100kHz; clock:cut-off frequency ratio is 50 and the input is sampled twice to reduce the risk of aliasing. Ripple in the pass band is ± 0.15 dB and there is 80dB of stop band attenuation at 2.3 times cut-off. Linear Technology (UK) Ltd. Tel., 0276 677676; fax, 0276 64851.

Delta-sigma modulator. Crystal Semiconductor offers the *CS5321* 24-bit, fourth-order, 256-times-oversampled delta-sigma modulator for seismic and general scientific measurement. Its dynamic range is 123dB with a -118 dB distortion level at 256x, and the device dissipates 70mW per channel - modulator and filter. A switched-capacitor architecture minimises the effects of clock jitter without the use of vcocs and plls. Crystal Semiconductor Corporation. Tel., 0101 512 442 7555; fax, 0101 5512 445 7581.

Discrete active devices

SM power mosfets. Motorola's *MiniMOS* surface-mounted, high-density, n- and p-channel and complementary power mosfets feature 200m Ω or less on-resistance, achieved by laying down six million cells per square inch. The body diode has a shorter and softer recovery time and less stored charge, generating less noise during switching when compared with previous mosfets. They are rated at 50, 30, 20 and 12V breakdown and have a gate/source voltage of 2.7V, at which voltage on-

resistance is constant. Motorola Ltd. Tel., 0908 614614; fax, 0908 618650.

Linear integrated circuits

100MHz video switches. A series of two-channel, 100MHz video buffers from Maxim, the *MAX463/4/5/6*, are single-chip devices containing video switches that switch between two rgb sources or rgb+sync. in less than 20ns, directly driving ± 2.5 V into 75 Ω back-terminated cables. *MAX463/464* buffers have fixed unity gain, the others a fixed gain of 2 for 75 Ω back-terminated use. A shutdown mode reduces current and also tri-states the output to allow multiple switches to be in parallel. Cross-talk is better than 60dB. Maxim Integrated Products UK Ltd. Tel., 0734 845255; fax, 0734 843863.

First pHEMT amplifier. H-P says its *MGA-86576* is the first commercial low-noise amplifier to use a GaAs pHEMT, which is to say pseudomorphic high electron mobility transistor. Although similar in concept to silicon microwave ICs, the new device extends frequency to over 8GHz and reduces a front-end component count from two mesfets and 20 components to one *MGA-86576* and three components. Noise figure is 1.6dB, 4GHz gain 23dB. Hewlett-Packard Ltd. Tel. 0344 362277; fax, 0344 362269.

Subscriber loop circuits. New ICs from AT&T for subscriber loop use include the *T7256*, which offers all the functions of a Basic Rate ISDN termination, and a family of subscriber loop interface circuits (*ATTL7554/7561/7564*) from a versatile solution for short-loop analogue use. The four slices provide independent adjustment of open-loop voltage, feed resistance and current limit and the ISDN interface performs

all network termination functions without a microprocessor. AT&T Microelectronics. Tel., 0732 742999; fax, 0732 741221.

V.32bis chipset. The *CL-MD1414BA* three-chip set from Cirrus Logic is claimed to be the first to offer a high-performance data, fax and voice modem and a sound card, needing only an external 32kbyte sram. All popular standards are supported, including V.32bis, CCITT v 32, V.22bis, Bell 212A and 103 for data and CCITT V.17, V.29, V.27ter and V.21 ch2 for fax. Users may dial from a keyboard and use a headset for voice. Cirrus Logic Inc. (USA) 0101 510 623 8300; fax, 0101 510 226 2240.

'Fastest' op-amp. Analog claims the industry speed record for its *AD8091* 800MHz op-amp, which achieves this performance on 5mA from ± 5 V. It is meant mainly for video application providing 0.1dB gain flatness to 100MHz, 0.01% differential gain error at a gain of 2 into 150 Ω , 1200V/ μ s slewing and a 10ns settling time for a 2V step to within 0.1%. Worst harmonic component at 20MHz is at -60 dB and voltage noise at 10kHz is 1.8nV/ $\sqrt{\text{Hz}}$. The device will drive up to six 75 Ω cables. Analog Devices Ltd. Tel, 0932 253320; fax, 0932 247411.

Zero-drift op-amp. The *LTC1152* low-power op-amp by Linear takes rail-to-rail input and produces rail-to-rail output swings, even into heavy loads. It is unity-gain stable into 2000pF with no extra components and one extra C enables it to drive unlimited capacitive loads. Offset voltage is 1 μ V, offset drift 10nV/ $^{\circ}$ C, cmrr and power supply rejection are 130dB and 120dB and open-loop gain 130dB. Low frequency noise is kept to 2 μ V pk-pk, and GB product is 1MHz. Linear Technology (UK) Ltd. Tel., 0276 677376; fax, 0276 64851.

Gilbert-cell array. Harris's *HFA3101* is a low-cost, silicon Gilbert-cell array intended in the main for rf mixing and amplification use up to 2.5GHz. Power gain-bandwidth product is 5GHz and the transistor f_T is 10GHz. Harris claims for it low cost, easier design and lower power consumption than discrete components and GaAs chips. Transistor noise figure is 2.5dB into 50 Ω . Spice models and rf-specific scattering parameters are available. Harris Semiconductor UK. Tel., 0276 686886; fax, 0276 682323.

Logic building blocks

Fast bus switch. Cypress's *CYBUS3384* bus switch is a Fast Cmos Technology (FCT) bus switch for bidirectional data transfer between multiple buses or between 5V and 3.3V devices. Propagation delay is less than 250ns. FCT devices are also available as FCT-T types with ttl output, or as FCT2-T with 25 Ω terminating resistors to further reduce ground bounce. Ambar Components Ltd. Tel., 0844 261144; fax, 0844 261789.

Fast changeover camera.

Pearpoint's *P328* dual-sensor ccd-based camera can switch between colour and intensified-image modes in less than 1.5s, also switching rapidly between zones with greatly differing illumination levels. The changeover block has the two sensors back-to-back on the same axis, a gain limiter ensuring that the intensified-image sensor is not exposed to high light levels to prolong its life. The image intensifier has a gain of 90, so that real-time video is produced in levels down to 10 $^{-3}$ lux, the eht unit being built in. PAL, NTSC and S-Video signals are available. Pearpoint Ltd. Tel., 0420 489901; fax, 0420 477597



NEW PRODUCTS CLASSIFIED

Please quote "Electronics World + Wireless World" when seeking further information

Clock recovery chip. AD802-155BF from Analog is a clock recovery and data retiming device at rates of up to 155.52Mbit/s. It uses frequency lock for acquisition and tracking and phase lock for close, low-jitter tracking, needing only a single external capacitor. Lock is maintained through a 240-bit transitionless data run. The device tracks the SONET OC-3 standard jitter-tolerance mask and its jitter bandwidth is 130kHz. Analog Devices Ltd. Tel, 0932 253320; fax, 0932 247401.

Memory chips

Flash/EEPROM. SST's Superflash is a 128K by 8 CMOS memory chip combining the reliability of an EEPROM with the small size of the Superflash memory cell. The new technique uses thick oxide tunnelling to increase endurance and eliminate the over-erasing associated with the thin tunnel oxide process. Erasing is by sector, taking less than 10ms to erase and rewrite a page sector and there is software and hardware write protection. No 12V supply is needed. Ambar Components Ltd. Tel., 0844 261144; fax, 0844 261789.

Microprocessors and controllers

Improved PIC16C54. An improved version of Microchip's PIC16C54 8-bit microcontroller uses a 0.9µm double-layer metal wafer process and is powered by a single lithium battery. It is a risc-like device operating at up to 20MHz and with a fuse configurator to select RC timing circuits and crystal/resonator clock options. Memory is 512 words of EPROM for program and 256 bytes of static RAM for data. Peripherals include an 8-bit clock/counter with a programmable prescaler, watchdog timer and 12 I/O lines with individual directional control. Current drain in sleep mode is 4µA. Arizona Microchip Technology Ltd. Tel., 0628 850303; fax, 0628 850178.

Risc i486 replacement. The Rab2it chipset from NEC enables the i486 processor to be replaced by a risc chip, providing a link between the NEC VR4X00 processors and the PC bus and between processor and conventional or synchronous DRAM. Currently available are the i/o controller and a memory controller; the third device – to provide a direct connection to Rambus DRAM – will be made available later this year. The 3.3V or 5V i/o controller handles DMA and interrupt requests from PC AT systems and can be used with VR 4200/4400PC/4400SC processors. NEC Electronics (UK) Ltd. Tel., 0908 691133; fax, 0908 670290.

Mixed-signal ICs

Forward-thinking teletext chip. MV1817 is a GEC Plessey teletext decoder that captures and stores in DRAM up to 256 pages for rapid viewing. It stores all linked pages in the same magazine, ten pages either side of the current one and all page

numbers ending in zero. In the German TOP system, it captures all pages on an index page and will work with the Advanced Header transmissions in Austria and Belgium. Automatic television tuning and video recorder control are also carried out. GEC Plessey Semiconductors Ltd. Tel., 0793 518510; fax, 0793 518582.

100Mbyte/s Fibre Channel. AT&T is to sample two ICs that meet the Fibre Channel physical interface for 100Mbyte/s data transfer in networked computer groups and for connecting peripherals. DA204/5 chips use less than 5W from 5V and provide the retiming, transmit and receive functions for 1Gbit/s products now under development by Ancor and Finisar in America. AT&T Microelectronics. Tel., 0732 742999; fax, 0732 741221.

Overvoltage protector. Harris's SP721 is a low-cost discharge/overvoltage protector, capable of handling six inputs, including microprocessor I/O and buses, from voltages up to 15kV. It switches in 6ns and takes up to 2A of peak current, triggering when the voltage on positive or negative lines increases by more than one diode drop and returning to normal operation after the transient disappears. Normally, the device appears as 3pF input capacitance and draws 1nA leakage. Voltage range is 4.5-30V dc. Harris Semiconductor UK. Tel., 0276 686886; fax, 0276 682323.

Game sound generator. For the games market, Yamaha offers the YM2280 eight-channel sound generator, which takes a 4-bit ADPCM input or 8/16-bit linear PCM to produce the eight channels. It samples at up to 44.1kHz maximum or 172Hz minimum, an external address space 16Mbyte being available for waveform data in ROM or SRAM. Also on offer is the YAC513 D-to-A converter and the YSS225 effects processor, which samples up to 48kHz and has a delay

time of 1.5s. Polar Electronics. Tel., 0525 377093; fax, 0525 378367.

Optical devices

Laser diode modulation head. The AVX-SRB module by Avtech is a bias-T modulation head, which combines the dc output of a laser diode driver with an rf modulation input in the 10MHz-1.5GHz range to drive 3-pin and 4-pin laser diodes, which fit into a socket in the head. A current of 0-500mA is applied to the laser diode, maximum rf input power being 100mW for 125mA pk-pk current swing about the dc bias current. The module mates with heat sinks and coolers and takes laser diode drivers by Seastar. Lyons Instruments Ltd. Tel., 0992 768888; fax, 0992 788000.

Multi-chip leds. Multi-chip leds in the EBT range can be used as direct replacements for panel-mounting incandescent lamps. The devices consist of several led chips bonded directly onto a substrate, conferring better resistance to shock, no surge, longer life and lower heat when compared to filament lamps. Devices with 4, 6 or 8 chips are produced in red, yellow or green with a choice of series or parallel connections. EAO-Highland Electronics Ltd. Tel., 0444 236000; fax, 0444 236641.

Oscillators

Surface-mounted oscillators. Contained in a plastic package measuring 13 by 9.8 by 1.7mm, IQD's IQXO-50 series of surface-mount oscillators work in the 1-70MHz range, with frequency stabilities of ±100ppm or ±50ppm, including load, supply and temperature (0-70°C) variations. All are described in a new Data Book, now available. IQD Ltd. Tel., 0460 77155; fax, 0460 72578.

Power semiconductors

Isolated Hexfets. Low gate-charge Hexfets from IR are now in a fully isolated TO-220 FullPak, which

guarantees 2.5kV rms isolation, its thermal resistance comparing well with other methods of isolation. First FullPak parts are 400-600V types with the same current and resistance characteristics as Hexfets, but having a gate charge reduced from 63nC to 39nC, Miller capacitance from 120pF to 18pF and input C down to 1100pF. International Rectifier. Tel., 0883 713215; fax, 0883 714234.

Pulse transformer/mosfet interface. HV400MJ/883 takes its input directly from a pulse transformer and drives a power mosfet at switching rates up to 300kHz, or about three times the usual frequency obtained without the use of fairly complicated discrete circuitry. Harris's IC is a 6A device for use as a power switch building block for high and low-side switches, secondary-side regulators and synchronous rectifiers, driving capacitive loads in the 5-100nF range. Two pins allow independent control of rise and fall times. Harris Semiconductor UK. Tel., 0276 686886; fax, 0276 682323.

High-current IGBT. The MG600Q1US41 from Toshiba is a 1200V, 600A insulated-gate bipolar transistor with only 20nH inductance between positive and negative terminals, its gates being protected by integrated back-to-back zeners. Saturation voltage with a resistive load is 3V and current fall time 200ns. A signal-collector terminal allows simple desaturation detection. Toshiba Electronics (UK) Ltd. Tel., 0276 694600; fax, 0276 691583.

Micropower regulator. Cherry's CS-8101 linear voltage regulator takes only 70µA of quiescent power (50µV in sleep mode), drops out at 5.2V to give a 5V output and provides a microprocessor reset pin, keyed from the output, valid down to 1V output voltage. The device is protected against ESD, overvoltage, shorts, thermal runaway and reversed battery, and is pin-compatible with the National Semiconductor LP2950/51. Clere Electronics Ltd. Tel., 0635 298574; fax, 0635 297717.

PASSIVE


Passive components

Ceramic resonators. Ceramic resonators provided with built-in capacitors, ZTS components from Integrity Technology Corp. cover the 2-12MHz frequency range. Capacitors are either 30pF connected for TTL use or 100pF for CMOS. Frequency tolerance is ±0.3% per year. Integrity Technology Corporation. Tel., (USA) 0101408 262-8640; fax, 0101408 262-1680.

Improved electrolytics. Nichicon's WT range of surface-mounted electrolytic capacitors now handle up to 60mA ripple current at 100µF and 10-16V operating voltage. Load life is 32000h at 55°C, range is 0.1-100µF and working voltages 1-50V. The

Function generator.

With a frequency range of 0.1MHz-10MHz, Fluke's PM5138A synthesised function generator provides up to 40V pk-pk protected output into either 50Ω or 600Ω. Seven standard waveforms are produced and an arbitrary one that can be created on a PC using Fluke's AnyWave software, and down-loaded on the optional IEEE488 or RS232 interface. Waveforms can also be captured on a digital oscilloscope and directly transferred to the PM5138A. Modulation includes AM, FM, PSK, burst, gating and linear or log sweep. Fluke UK Ltd. Tel., 0923 240511; fax, 0923 225067.

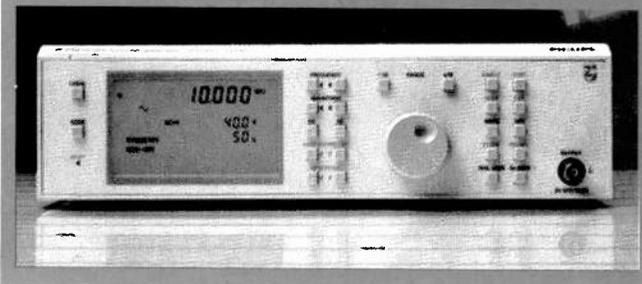

range measures 5.5mm high and diameters are 3-6.3mm. Nichicon (Europe) Ltd. Tel., 0276 685393; fax, 0276 686531.

Ceramic resonators. In five package styles, ceramic resonators by Panasonic cover the 3.58-35MHz frequency range. There are two ranges of leaded components, all with a height off-board of 5mm and three of chips, two of which stand 2.5mm high and the third 1.8mm. All are based on PCM ceramics and can be supplied as general-purpose types or with integral capacitors. Tolerance is down to $\pm 0.3\%$ and ten-year drift to -0.1% . Panasonic Industrial (Europe) Ltd. Tel., 0344 863444; fax, 0344 861656.

SM ceramic C sample kits. Eight surface-mounting sample kits for Philips's 0603, 0805 and 1206 standard and microwave capacitors are now available, containing representative samples with rated voltages of 63V for the microwave types and 63/20V for the standards. A variety of terminations and capacitor characteristics is presented. Gothic Crellon Ltd. Tel., 0734 788878; fax, 0734 776095.


Dielectric filter. AVX announces the PDFC series of dielectric filters meant for use in telecomms, particularly in the DECT sector. Frequency range is 1.8-2GHz, insertion loss 3dB and, for compatibility with the newest equipment, size is 6.5 by 5.5 by 3mm. Filters to provide lower insertion loss and improved stop-band attenuation are available to order. AVX Ltd. Tel., 0252 336868; fax, 0252 346643.

Connectors and cabling

Sealed BNC. From Bulgin, a range of sealed connectors that incorporate 50 Ω or 75 Ω bnc inserts and that can be assembled into any of the five *Mini Buccaneer* bodies to provide sealing to IP66, BS5490:1977. Dust caps preserve the connectors' invulnerability to dust and moisture when the connectors are separated. A brochure of *Buccaneer* sealed products is available. Gothic Crellon Ltd. Tel., 0734 788878; fax, 0734 776095.

PCMCIA memory. Fujitsu's FCN 560H PCMCIA memory cards connectors are single and double types for mounting 68-pole memory boards on PCs, conforming to JEIDA/PCMCIA I and II standards. They come with straight or right-angled pins, with or without an ejector and with polarisation. Resistance of the gold-plated pins is 40m Ω maximum. Electrospeed. Tel., 0703 644555; fax, 0703 610282.

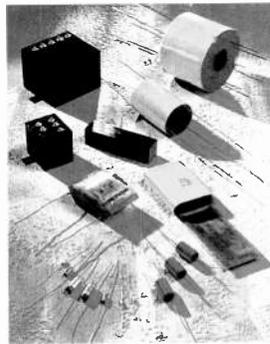Eurocard connectors. The range of Siemens DIN41612 connectors is now available from Quiller. They are in two parts and come with contact ratings up to 5A and rf types, meeting all major standards. Also available is a range of press-fit connectors with a highly compliant press-fit zone to give good connection with low insertion



Custom capacitors. Suflex Capacitors has a new custom design and manufacture service for prototype and short runs as well as production quantities. Plastic-film components can be produced in polypropylene, polycarbonate, polyester and polystyrene in values from picofarads to microfarads and with working voltages up to 30kV. Customers specify size, shape, encapsulation a fixing method. Suflex Capacitors Ltd. Tel., 0633 615511; fax, 0633 613583.

and extraction forces. Through-hole and wire-wrap versions are made and the connectors meet IEC 352-S. Quiller Switches Ltd. Tel., 0202 417744; fax, 0202 421255.

Shielded ribbon connectors. High-density mini delta ribbon (mcr) board-mounted plug connectors from 3M in the 101 series are for internal and external i/o use where small size, emi/rfi shielding and electrostatic discharge before mating are needed. The 101 is a right-angled through-hole-mounted plug in staggered four-row form on a 0.05in by 0.075in matrix and is a miniature version of the standard D ribbon or Centronics connectors, being rated at 500 insertions/withdrawals. It is available in 20, 26, 36 and 50-way versions. 3M United Kingdom plc. Tel., 0344 858000; fax, 0344 858753.

Filters

Coaxial filters. Three diameters of coaxial filter by Atlantic Microwave cover the 30-5000MHz frequency range in band-pass or low-pass form. Depending on the number of sections, they offer a 70dB rejection with low insertion loss and 1.5:1 vswr. Band-pass units with 2-12 sections can be specified at 50 Ω , 75 Ω or 100 Ω and with pass bands of 1-10% of centre frequency. Unit size is 9.5-19mm diameter and 50-450mm in length. Atlantic Microwave Ltd. Tel., 0376 550220; fax, 0376 552145.

Hardware

Instrument cases. Serpac general-purpose cases are intended for almost anything from test instrument enclosures to computer interfaces, having a precision fit, a textured finish

and prices down to £1.50. These ABS boxes are in two types: the *i* series with a recessed top for membrane keypads and the standard series with a flat top. OKW Enclosures Ltd. Tel., 0489 538858; fax, 0489 583836.

Pocket boxes. These boxes by OKW feature IP65 sealing, a recessed top to take membrane keypads and a battery compartment to avoid the use of the less reliable battery clips often found in this type of case. They are in flame-retardant ABS and come in three sizes from 85 by 46 by 16mm to 120 by 65 by 22 mm. Internal pcb mountings are provided and belt clips, emc protection and silk-screening are offered. OKW Enclosures Ltd. Tel., 0489 538858; fax, 0489 583836.

Compact keyboard. Providing the full recommended 3mm travel, Cherry's G34-4100 low-profile, compact keyboard is said by the company to be the smallest: standard keyboard available, its enclosure measuring 23.5mm by 281 mm by 131.5mm. There is an enclosed version with tilt feet and a model supplied without the housing. Mechanical keyswitches do not deteriorate with time and temperature and keycaps are available for most languages. Cherry Electrical Products Ltd. Tel., 0582 763100; fax, 0582 768883.

Instrumentation

High-current probe. A current probe for use with multimeters and oscilloscopes, the PR1000-1 from Lem Heme, uses Hall effect to measure currents up to 1000A peak at frequencies up to 10MHz to an accuracy of $\pm 1\%$ of reading $\pm 0.5A$. Output is 1mV/A. Lem Heme Ltd. Tel., 0695 20535; fax, 0695 50279.

Disturbance analysers. Avo's PDA2 power disturbance analyser will now show pulse direction as well as amplitude and duration, using a current sensor kit. By placing the analyser at several points, the user can determine whether, for example, noise pulses come from the equipment or from the mains. The two-channel instrument evaluates disturbances on single and three-phase, 400Hz and dc supplies, results being shown on an lcd or built-in plotter. An RS232 port enables remote control and data downloading. Avo International Ltd. Tel., 0304 202620; fax, 0304 207342.

Panel meters. The 30-model *Select* range of panel meters from Sifam is in five groups containing voltage and current meters, process meters, rate and frequency monitors, batch counters and temperature indicators. Display is by red or green leds and the user can set the instrument up and protect the setting by a password or two concealed buttons. Sifam Ltd. Tel., 0803 613822; fax, 0803 613926.


IR monitor. New from the Raytex range of non-contact infrared temperature measuring instrumentation, the *Thermalert 30* is

a universal monitor to work with the Raytel T series of sensing heads in the -50 to $3000^{\circ}C$ range. Features include variable emissivity and peak/valley hold for sampling temperature of objects on a conveyor belt while ignoring the belt temperature. Objects down to 1mm can be measured as well as those at long distance and laser sighting heads are on offer. Calex Electronics Ltd. Tel., 0525 373178; fax, 0525 851319.

True-rms oscilloscope. TTI's *Scopemaster* range of lcd oscilloscopes now includes the SM630, which offers five measurement functions, including the indication of true-rms quantities. It functions as digital storage oscilloscope, digital multimeter, data logger, counter/timer and serial data analyser. Bandwidth of the dso is 20MHz, with a maximum sampling rate of 20Msample/s, roll mode down to 200s/div. and repetitive sampling to 2.5ns resolution. The 3000-count dmm provides ac and dc current and voltage scales, R, continuity and diode test and the logger stores up to 1000 readings. Thurlby Thandar Instruments Ltd. Tel., 0480 412451; fax, 0480 450409.

Literature

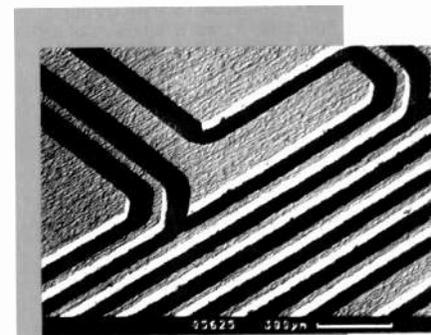Pressure sensors. Motorola has revised its data book on microprocessor-compatible pressure sensor devices, which contains data sheets and application notes describing interfaces to users' circuitry, together with information on evaluation boards. Motorola Inc. Tel., 0908 614614; fax, 0908 618650.



Production equipment
Laser PCB machining. Tracks CAD Systems has a laboratory pcb machining tool, the LPKF, which can cut seven conductor paths between two IC pads, leaving 40 μm isolation channels, cutting with a resolution of 1 μm to an accuracy of 2 μm . It cuts standard FR4 or copper-coated ceramic material, producing clean, square edges. Services needed are power, compressed air and water - no clean room necessary. Tracks CAD Systems Ltd. Tel., 0344 55046; fax, 0344 860547.

NEW PRODUCTS CLASSIFIED

Please quote "Electronics World + Wireless World" when seeking further information

Materials

UV coating. A new type of ultraviolet conformal coating has been introduced by Intertronics which cures as well in shadows as it does in direct uv light. *Dymax Darc Cure* cures in a few seconds throughout the entire coating by means of a post-cure reaction with air, without the use of aqueous or chemical accelerators. The coatings are free of solvent and ozone-depleting chemicals and can be inspected under black light. Intertronics Ltd. Tel., 0865 842842; fax, 0865 842172.

Power supplies

Low-profile transformers. Clairtronic's new low-profile encapsulated power transformers cover the 3-50VA range from the now harmonised mains input of 230V. All produce two outputs, which may be connected in serial or parallel and there is one-time thermal fusing. Materials used are flame-retardant to UL 94VO. Clairtronic Ltd. Tel., 0753 692022; fax, 0753 535096.

600mA dc-to-dc converter. From a two-cell input, Linear's *LT1302* converter supplies 5V at up to 600mA at 87% efficiency. Quiescent current is 200µA, reduced to 15µA at logic-controlled shutdown. The internal n-p-n power switch can handle over 2A and switch at 400kHz, so that small components can be used. Micro Call Ltd. Tel., 0844 261939; fax, 0844 261678.

Efficient step-up converters. *MAX856/7/8/9* are current-limited, step-up dc-to-dc converters claimed by Maxim to offer the world's best combination of efficiency (85% at 100mA), low quiescent current (25µA) and low shutdown current (1µA). *MAX856/8* accept a 0.8-6V input and produce a pin-selected 3.3V or 5V output, while *MAX857/9* give adjustable output between 2.7V and 6V. Maxim Integrated Products UK Ltd. Tel., 0734 845255; fax, 0734 843863.

120W UPS. *BI-UPS*, which is short for built-in uninterruptible power supplies, is a range of 120W ac supplies from Magnum that are able to supply 17in colour monitors in battery backup mode. The units protect themselves and other equipment against a whole range of supply line disturbances in compliance with UL1449, and give backup for 30min during blackouts. If the ac supply drops below 82% of nominal, the ups switches to battery backup. Magnum Power Solutions Ltd. Tel., 0236 433325; fax, 0236 427366.

Dc-to-dc converters. A new range of converters from Schroff includes an extended pluggable type for use with SELV circuits. There four in/out ranges from 8.5-18V to 80-160V, with 5V, 12V, 15V and 24V outputs, single, dual or triple at 25W, 60W or 120W. Overvoltage and short-circuit protection is provided on inputs and outputs. Schroff UK Ltd. Tel., 0442 240471; fax, 0442 213508.

Wide-range dc-to-dc converters. Single-output *UWR* and dual-output *BWR* 10W and 20W converters take an input range of 4.6-13.2V in an operating temperature range of -25°C to 105°C. Outputs are 3.3, 5, 12, 15 and ±15V and sizes are 2 by 1 by 0.375in in the 10W type and 2 by 2 by 0.45in for the 20W version. The pwm techniques adopted confer 84% efficiency and 200µs transient response. There is overvoltage shutdown and i/o isolation of 500V dc. Datel (UK) Ltd. Tel., 0256 880444; fax, 0256 880706.

Radio communications products

RF cable. SMC's range of cables includes the UR67, which gives a loss at 150MHz of 9.3dB/100m and at 2000MHz 53dB. *10F-SFB* exhibits 3.8dB loss at 150MHz and 16.8dB at 2000MHz. South Midlands Communications Ltd. Tel., 0703 255111; fax, 0703 263507.

Switches and relays

Automotive relays. *SAM* relays from Selectronic are compact and offer 15V dc 20A, 24V dc 15A switching current for use in vehicle control systems. The standard *SAM* single-pole device measures 17 by 12 by 16.1mm, the two-pole type comprising two of those in one package. Ambient temperature range is -25°C to 80°C. Selectronic Ltd. Tel., 0993 778000; fax, 0993 772512.

Transducers and sensors

Load washer. Control Transducers has the *Model LW-M* load washer, temperature-compensated and

hermetically sealed to measure bolt stresses, axial thrust, static, dynamic and clamping forces. Ranges are 300-150,000kg and comes in sizes from 34mm diameter, 26mm thick. Creep is ±0.2% fsd over four hours, repeatability ±0.1%, non-linearity and hysteresis better than ±0.2%. With a bridge impedance of 350Ω, sensitivity is 2mV/V. Control Transducers. Tel., 0234 217704; fax, 0234 217083.

COMPUTER

Computer board-level products

Single-board computer. The *Octagon PC-425* is a single-board computer for embedding in systems needing only limited i/o. It uses a 386/25 cpu and 387 co-processor (486 at the moment on special offer). Features include dos 5.0 in rom, four silicon disks giving 2.2Mbyte, keyboard connector and speaker, COM1 and COM2 ports with jumpered RS232, RS422 and opto-isolated RS485 interfaces and a rack for opto-isolated i/o modules accepting digital and analogue modules. Gothic Crellon Ltd. Tel., 0734 788878; fax, 0734 776095.

Data acquisition boards. Two more in the *200 series* of data acquisition boards are introduced by Amplicon Liveline. *PC234* has four channels of bipolar analogue voltage output at 16bit resolution, a four-wire voltage sensing circuit on each channel eliminating load and cable resistance errors. It provides four-quadrant d/a multiplication. *PC224* gives 16 bipolar channels with an independent ground line taken to source. Both give

sequential or simultaneous update on all channels and features included are internal clock, external clock source, three programmable counters and an external trigger. Programs can be written in Quick Basic, Turbo Pascal and C/C++. Amplicon Liveline Ltd. Tel., 0800 525 335 (free); fax, 0273 570215.

Data communications

Single-cable video, audio and data. Stand-alone or rack-mounted optical-fibre transmitters and receivers by Fiber Options are intended for cctv, carrying two-way video, audio and data by fm on one 50m or 62.5m cable. A typical application would be in remote camera control, where pan/tilt-zoom, windscreen wiper and heater are controllable by RS232, RS422 or TTL levels and the audio and video go to the control centre on the same link. Auriga (Europe) plc. Tel., 0908 274200; fax, 0908 378998.


Development and evaluation

83CL782 development. Ashling Microsystems has a new development system for the Philips *83CL782* low-power microcontroller family, based on an 8051 core and used in cordless telephones, DECT, pagers and portable GPS. The Ashling system provides real-time, non-intrusive emulation of all devices and package styles in the family and source-level debugging under Windows 3.1 is available for all the 8051 languages. Ashling Microsystems Ltd. Tel., 010353-61-334466; fax, 010353-61-334477.

Embedded bios v2.0. The General Software Inc. Embedded bios is a rom bios development kit with full feature support for the Intel 386EX processor in embedded designs. The new kit has support for PCMCIA, Intel Flash, Intel System Management Mode (SMM), synchronous serial i/o, watchdog timer, power management and the on-chip 386EX processor devices. There is a disassembler and debugger for hardware drivers and v2.0 also includes standard desktop PC AT bios functions such as Post, cmos support, setup screen, protected mode, PC AT keyboard support, serial and parallel i/o, floppy and IDE drives, clock and video functions. Great Western Instruments Ltd. Tel., 0272 860400; fax, 0272 860401.

PowerPC compilers for Power Mac.

Motorola's *PowerPC C, C++ and Fortran microprocessor compilers* are to be ported to Apple's Power Macintosh range of computers, where they will be compatible with the *Macintosh Programmers' Workshop* development environment. There are also plans to do the same for the *Metrowerks CodeWarrior* environment, so that users will be able to use Motorola's compilers without having to adopt a new development environment. Both projects are to be completed this year. Motorola Inc. Tel., 0908 614614; fax, 0908 618650.

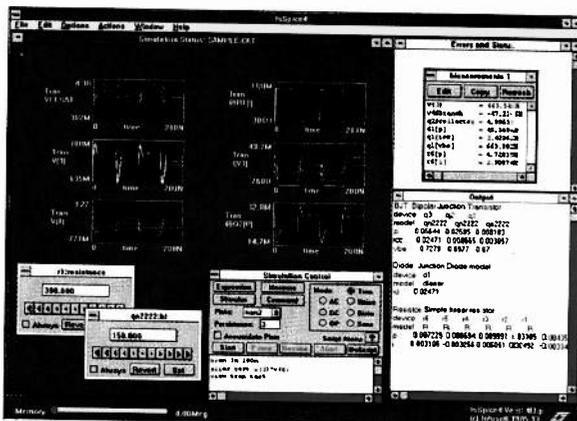

Software

Interactive Spice. *ICAP/4 Virtual Circuit Design Lab* from Intusoft is a circuit simulation system that is completely interactive, integrating schematic entry, the new *IsSPICE4* simulator, libraries and graphical waveform analysis. It runs under Windows 3.1X, NT and 4.0. When *IsSPICE4* is started, the user may examine the design by running different analyses, changing circuit values and measuring the results, without having to close and restart the simulator and alter the Spice input netlist. A cross-probing tool allows the display of waveforms on the circuit diagram and the interactive stimulus mode enables the user to sweep any number of component or parameter values to compare circuit performance. Technology Services Ltd. Tel. 0638 561460, fax C638 561721.

Surplus always wanted for cash!


THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

LOW COST PC's - ALL EXPANDABLE - ALL PC COMPATIBLE

THE OFFER OF 1994!

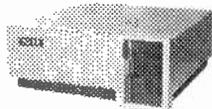


SPECIAL BUY
AT 286
40Mb HD + 3Mb Ram

LIMITED QUANTITY only of these 12Mhz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k x 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!
Order as HIGRADE 286 **ONLY £169.00 (E)**

Optional Fitted extras: VGA graphics card	£29.00
1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb)	£32.95
NE2000 Ethernet (thick, thin or twisted) network card	£49.00

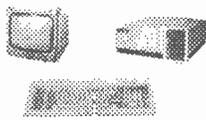PC SCOOP
COMPLETE
COLOUR SYSTEM
ONLY £99.00



A massive bulk purchase enables us to bring you a COMPLETE ready to run colour PC system at an unheard of price! The Display Electronics PC99 system comprises of fully compatible and expandable XT PC with 256k of RAM, 5 1/4" 360k floppy disk drive, 12" CGA colour monitor, standard 84 key keyboard, MS DOS and all connecting cables - just plug in and go!! Ideal students, schools or anybody wishing to learn the world of PC's on an ultra low budget. Don't miss this opportunity. Fully guaranteed for 90 Days.
Order as PC99COL **£99.00 (E)**

Optional Fitted extras: 640k RAM	£29.00
2nd floppy drive, specify 5 1/4" 360k or 3 1/2" 720k	£29.95
Above prices for PC99 offer ONLY.	



Computer Controlled Laser Video Disk Player

One of the most amazing surplus deals that we've been able to offer you! The Philips VP410 LaserVision player, in as new condition, unit features full computer control. Plays standard 12" LaserVision disks with startling visual and audio quality in two channel stereo or mono. When controlled by a computer, it may also be used as a versatile high quality storage / retrieval medium. It will play back either LaserVision CAV (active play) or CLV (Long Play) discs (which covers most types of commercially available video discs). Some of the many features of this incredible machine are:
RS-232 INTERFACE RGB / COMPOSITE VIDEO OUTPUT
BNC+SCART INTERFACE PAL / RGB DECODER
IR+WIRED REMOTE CONTROL FAST RANDOM ACCESS

SPECIAL PURCHASE Only **£399.00 (F)**

FLOPPY DISK DRIVES 3.5" - 8"


5.25" from £22.95 - 3.5" from £24.95
Massive purchases of standard 5.25" and 3.5" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3.5" supported on your PC).
3.5" Panasonic JU363/4 720K or equivalent **£24.95 (B)**
3.5" Mitsubishi MF355C-L 1.4 Meg. Laptops only * **£26.95 (B)**
3.5" Mitsubishi MF355C-D 1.4 Meg. Non Laptop **£29.95 (B)**
5.25" Teac FD-55GFR 1.2 Meg **£29.95 (B)**
5.25" BRAND NEW Mitsubishi MF501B 360K **£22.95 (B)**
* Data cable included in price.
Shugart 800/801 8" SS refurbished & tested **£195.00 (E)**
Shugart 851 8" double sided refurbished & tested **£250.00 (E)**
Mitsubishi M2894-63 8" sided switchable NEW **£250.00 (E)**
Mitsubishi M2896-63-02U 8" DS slimline NEW **£285.00 (E)**
Dual 8" drives with 2 mbyte capacity housed in a smart case with built in power supply. Ideal as exterior drives! **£499.00 (F)**

HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte of hard disk storage! Full industry standard SMD interface. Ultra hi speed data transfer and access time, replaces Fujitsu equivalent model, complete with manual. Only **£299.00 (E)**
3.5" FUJI FK-309-26 20mb MFM I/F RFE **£59.95 (C)**
3.5" CONNER CP3024 20 mb IDE I/F (or equiv) RFE **£69.95 (C)**
3.5" CONNER CP3044 40mb IDE I/F (or equiv) RFE **£99.00 (C)**
3.5" RODIME R03057S 45mb SCSI I/F (Mac & Acorn) **£99.00 (C)**
5.25" MINISCARTE 3425 20mb MFM I/F (or equiv) RFE **£49.95 (C)**
5.25" SEAGATE ST-238R 30 mb RLL I/F Return **£69.95 (C)**
5.25" CDC 94205-51 40mb HM MFM I/F RFE tested **£89.95 (C)**
5" FUJITSU M2322K 160Mb SMD I/F RFE tested **£195.00 (E)**
Hard disc controllers for MFM, IDE, SCSI, RLL etc. from **£16.95**

THE AMAZING TELEBOX

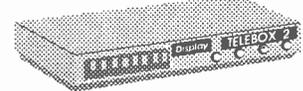Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by manufacturers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD and many more. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

TELEBOX ST for composite video input type monitors **£32.95**
TELEBOX STL as ST but with integral speaker **£36.50**
TELEBOX MB Multiband VHF-UHF-Cable-Hyperband tuner **£69.95**
For overseas PAL versions state 5.5 or 6mhz sound specification.
*For cable / hyperband reception Telebox MB should be connected to cable type socket. Shipping code on all Teleboxes is (B)

FANS & BLOWERS

MITSUBISHI MMF-06D12DL 60 x 25 mm 12v DC **£4.95 10 / £42**
MITSUBISHI MMF-09B12DH 92 x 25 mm 12v DC **£5.95 10 / £53**
PANCAKE 12-3.5 92 x 18 mm 12v DC **£7.95 10 / £69**
EX-EQUIP 120 x 38mm AC fans - tested specify 110 or 240 v **£6.95**
EX-EQUIP 80 x 38mm AC fans - tested specify 110 or 240 v **£5.95**
VERO rack mount 1U x 1 1/2" fan tray specify 110 or 240v **£49.95**
IMHOF B26 1900 rmt mt 3U x 19" Blower 110/240v NEW **£75.95**
Shipping on all fans (A), Blowers (B). **50,000 Fans Ex Stock CALL**

IC's TRANSISTORS DIODES

OBSOLETE - SHORT SUPPLY - BULK
5,000,000 items EX STOCK
For MAJOR SAVINGS - SAE or CALL FOR LATEST LIST

Issue 12 of Display News now available - send large SAE - PACKED with bargains!



LONDON SHOP
Open Mon-Sat 9:00-5:30
215 Whitehorse Lane
South Norwood
LONDON SE25

DISTEL © The Original
FREE On line Database
Info on 1000's of items
V21, V22, V22 BIS
081 679 1888

ALL MAIL & OFFICES
Open Mon-Fri 9:00-5:30
Dep: WW - 32 Biggin Way
Upper Norwood
LONDON SE19 3XF

ALL ENQUIRIES
081 679 4414
FAX 081 679 1927



ESTABLISHED 25 YEARS

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Carriage charges A)=£3, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. Scotland surcharge CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1994. E & O E.

CIRCLE NO. 123 ON REPLY CARD

VIDEO MONITOR SPECIALS

Superb quality 14" FOREFRONT MTS-9600 SVGA Multisync. Multisync monitor, 0.28" dot pitch with resolution of 1024 x 768. The multi mode inp. it allows direct connection to a host of computers including IBM PCs or CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES etc. The H version will also function with the ATARI in all modes inc HI RES monochrome. Complete with 'text' switching for WP use. Syncs down to 15 kHz. Supplied in EXCELLENT little used condition with full 90 day guarantee.
Order as MTS-9600 / H for ATARI **£159.00 (E)**
All modes as above Order as MTS-9600 / S **£139.00 (E)**
ELECTROHOME ECM-12115BU 12" VGA multi/sync monitor with resolution 640 x 480. Multi input selection; 9pin CGA/EGA; 15 pin VGA or 5 BNC connectors. 0.31 pitch. Compatible with PCs, Amiga, Atari and others. In good used condition (possible minor screen burns). 90 day guarantee. **£99.00 (E)**
KME 10" high definition colour monitors. Nice tight 0.28" dot pitch for superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn, Archimedes & BBC. Measures only 13.5" x 12" x 11". Only **£125 (E)**
Good used condition. 90 day guarantee.
KME 10" as above for PC EGA standard **£145.00 (E)**
NEC CGA 12" colour IBM-PC compatible. High quality ex-equipment fully tested with a 90 day guarantee. In an attractive two tone ribbed grey plastic case measuring 15" L x 13" W x 12" H. The front cosmetic bezel has been removed for contractual reasons. **Only £49.00 (E)**

20" 22" and 26" AV SPECIALS
Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound inputs. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.
20"....£135 22"....£155 26"....£185 (F)
9" Mono cased, Black & White for CCTV Used / Tested **£49.00 (C)**

DC POWER SUPPLIES

10,000 Power Supplies Ex Stock
Call for info / list
Power One SPL200-5200P 200 watt (250 w peak). Semi open frame giving +5v 35A, -5v 1.5A, +12v 4A (8A peak), -12v 1.5A, +24v 4A (6A peak). All outputs fully regulated with over voltage protection on the +5v output. AC input selectable for 110/240 vac. Dims 13" x 5" x 2.5". Fully guaranteed RFE. **£85.00 (B)**
Power One SPL130. 130 watts. Selectable for 12v (4A) or 24 v (2A). 5v @ 20A, +12v @ 1.5A. Switch mode. New. **£59.95 (B)**
Astec AC-8151 40 watts. Switch mode. +5v @ 2.5A, +12v @ 2A, -12v @ 0.1A, 6-1/4" x 4" x 1-3/4" RFE tested **£22.95 (C)**
Lambda LYS-12 200 watt switch mode. +12V DC @ 29A semi enclosed, 10" x 5" x 5". RFE and fully tested. **£59.95 (C)**
Conver AC130. 130 watt hi-grade VDE spec. Switch mode. +5v @ 15A, +5v @ 1A, +12v @ 6A, 27 x 12.5 x 6.5 cms. New. **£49.95 (C)**
Boshart 13090. 200 watt. Ideal for drives & system. +5v @ 6A +12v @ 2.5A, -12v @ 0.5A, -5v @ 0.5A. **£29.95 (C)**
Farnell G6/40A. Switch mode. 5v @ 40A. Encased **£95.00 (C)**

SPECIAL INTEREST

Zeta 3220-05 A0 4 pen HPGL RS232 fast drum plotter **£21.00**
Avitel VDA-3100 Video Distribution Amps, 1 ir 92 out **£75**
Trio 0-18 vdc bench PSU, 30 amps. New **£70**
Fujitsu M3041 600 LPM band printer **£295.00**
Andrews LARG 6 m Satellite Dish + mount (For Voyager!) **£950**
RED TOP IR Heat seeking missile (not armed!!) **PJA**
Rhode & Schwarz S8UBF TV test transmitter 25-1000mhz. complete with SBTf2 Modulator **£5995**
Tektronix 1L30 Spectrum analyzer plug in **£330**
Thurlby LA 160B logic analyser **£375**
GEC 1.5kw 400 Hz 3 phase power source **£950**
Brush 2Kw 400 Hz 3 phase frequency converter **£850**
Anton Pillar 75 kW 300 Hz 3 phase frequency converter **POA**
Newton Derby 70 KW 400 Hz 3 phase frequency converter **POA**
Nikon PL-2 Projection lens meter/scope **£750**
Sekonic SD 150H 18 channel digital Hybrid chart recorder **£1395**
HP 7580A A1 8 pen HPGL high speed drum plotter **£1350**
Kenwood DA-3501 CD tester, laser pickup drum plotter **£350**
Computer MCA1613APC 16mm auto iris lenses 'C' mount **£125**
Seaward PAT 2000 dual voltage computerised PAT tester **£585**

19" RACK CABINETS

Superb quality 6 foot 40u Virtually New, Ultra Smart Less than Half Price!
Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have

ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in bays
Overall dimensions are: 77-1/2" H x 32-1/2" D x 22" W. Order as:
Rack 1 Complete with removable side panels. **£295.00 (G)**
Rack 2 Rack, Less side panels **£175.00 (G)**

Over 400 racks in all sizes from stock!
Call with your requirements.

LOW COST RAM UPGRADES

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disk supplied. In good used condition fully tested and guaranteed.
Win lows compatible. Order as: ABOVE CARD **£59.95 (A1)**
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data.
Order as: XT RAM UPG. 256k **£32.95 (A1)**
512k **£38.95 (A1)**
1 MEG x 9 SIMM 9 chip 120ns only **£29.95 (A1)**

No Break Uninterruptible PSU's

Brand new and boxed 230 volts 1 KVA uninterruptible power supply from system from Densel. Model MUD 1085-AHB. Complete with sealed lead acid batteries in matching case. Approx time from interrupt is 15 minutes. Complete with full manual.
Order as: MUD 1 **£575.00 (G)**
EMERSON ACCUCARD UPS, brand new 8 Bit half length PC compatible card for all IBM XT/AT compatibles. Card provides DC power to all internal system components in the event of power supply failure - The Accusaver software provided uses only 6k of base RAM - ac automatically copies all system, expanded and video memory to the hard disk in the event of loss of power. When power is returned the machine is returned to the exact status when the power failed!
The unit features full self diagnostics on boot and is supplied with full fitting instructions and manual. Normal price **£189.00**
Only £99.00 (B) or 2 for £195 (C)

Digital filters simplified

With DSP replacing analogue equivalents in almost all areas of electronics, digital filters are becoming increasingly important. Bob Lawlor* looks at how a field-programmable gate array can simplify the design of both infinite and finite-impulse response filters.

There are two types of digital filter, one with finite-impulse response, FIR, the other with infinite-impulse response, IIR. A digital FIR filter is a discrete-time filter. Any sample of its output sequence is equal to a weighted sum of a finite number of past and present samples of the input sequence.

Mathematically an n-tap FIR filter is expressed as,

$$y(k) = \sum_{j=0}^{n-1} c_j x(k-j)$$

where $x(k)$ and $y(k)$ represent the input and output sequences respectively and represents the filter coefficients.

Figure 1 shows an FIR filter block diagram. The τ -boxes represent unit sample delays. Sampling frequency depends on the application. For example an audio system might warrant up to 40k samples per second while the standard sampling frequency for video is 13.5M samples per second. How many bits there are in each sample also depends on the application, hi-fi audio being typically sixteen bits and video eight bits.

Filter coefficients, c_0, c_1 , etc. multiply or weight the delay outputs. Resulting product terms are summed together to form the filtered output data sequence, $y(k)$. The name finite-impulse response is derived from the fact that an impulse injected into the input will cause the output to become active, i.e. non-zero, for

only a finite duration.


A key advantage of FIR filters is that they can be designed to have a linear phase characteristic, Fig. 2(a). This means that if the input signal to the FIR filter has more than one frequency component – and most real signals have a wide spread of frequencies – then in passing through the filter, all frequency components undergo the same delay.

For example, if the two frequency components of Fig. 2(b) each undergo delay T , the phase change of the higher frequency component is proportionally greater than that of the lower frequency component. If on the other hand the phase characteristic is non-linear, then different frequencies undergo different delays, causing so-called phase distortion.

The ear is extremely sensitive to phase distortion which would occur if the audio signal was processed by a filter having a non-linear phase characteristic. In a composite video signal, the colour information is coded in the phase of the subcarrier, so phase distortion appears as colour distortion.

IIR digital filters

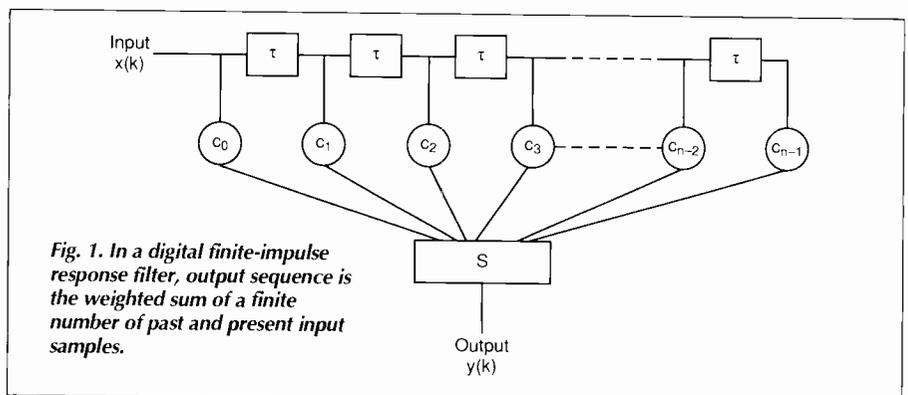A digital infinite-impulse response filter is a discrete-time filter. Any sample of its output sequence is equal to a weighted sum of a finite number of past and present samples of the input sequence, and also of the past output samples.



*Bob Lawlor was the winner of our December 1992 competition, sponsored by Xilinx. He was a senior R&D engineer with Sony, and has recently established his own DSP consultancy.

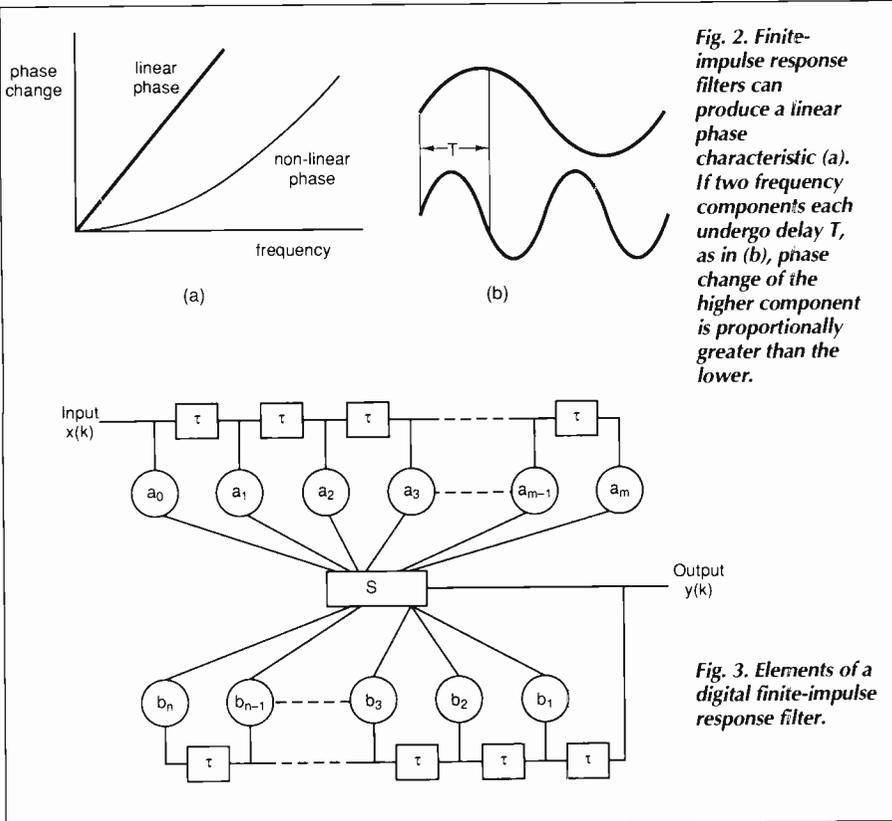


Fig. 2. Finite-impulse response filters can produce a linear phase characteristic (a). If two frequency components each undergo delay T, as in (b), phase change of the higher component is proportionally greater than the lower.

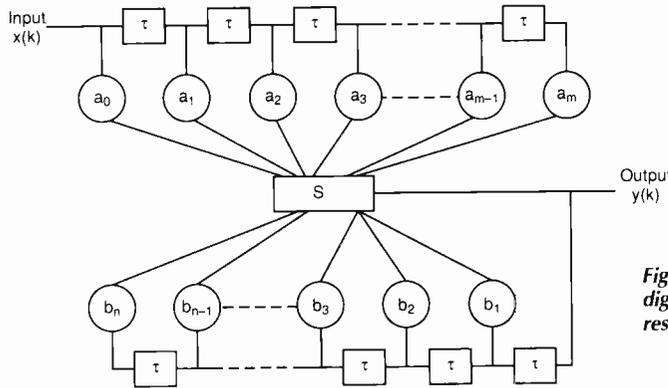


Fig. 3. Elements of a digital finite-impulse response filter.

Mathematically this can be expressed as,

$$y(k) = \sum_{j=0}^m a_j x(k-j) - \sum_{j=0}^n b_j y(k-j)$$

where again x(k) and y(k) represent the input and output sequences respectively. There are now two sets of filter coefficients, namely the feed forward coefficients, a_j, and the feedback coefficients, b_j.

The name infinite-impulse response comes from the fact that an impulse injected into the input can cause the output to remain active for

an infinite duration. Inclusion of previous output samples in the present output sample computation is called feedback. For this reason IIR filters are often referred to as recursive filters and FIR filters as non-recursive.

An advantage of IIR filters is that they generally require less hardware than their FIR counterparts. For most applications however, this advantage is outweighed by their non-linear phase characteristic.

Video application

In decoding composite video to component

RGB, an FIR bandpass filter centred on the subcarrier frequency, and a video field rate FIR comb filter combine to produce very high quality separation of the luminance and chrominance data. Subcarrier frequency is 4.43MHz for PAL, digital video is sampled at 13.5MHz and the video field rate is 50Hz.

This results in a much clearer picture than is possible with conventional TV sets, Fig 6. This type of video decoding is used in the professional video industry, for example in the Sony BVX100 digital decoder.

Each of the FIR filters and the subtractor can be implemented readily using a single Xilinx FPGA. The 50Hz FIR comb filter would need two external field stores, but so also would other implementations.

Since the Xilinx FPGAs are so easily reprogrammable the FIR filter transfer functions can be changed on a field by field basis. This is very useful in adaptive signal processing applications.

Implementing the FIR filter

In Fig 1, values of coefficients c₀, c₁...c_{n-1}, determine the filter characteristics¹. Being readily reprogrammed, the Xilinx FPGAs makes changing the resolution to suit the application easy. A prototype filter for example could be implemented with relatively low resolution. At the pre-production stage, resolution could then be increased to enhance overall system quality. Existing asic general-purpose FIR filters are mostly fixed in terms of resolution.

In order to control round-off error, the multiplier outputs must be kept at full resolution. If for example the coefficients are n-bit numbers, then the multiplier outputs should be 2n-bit numbers. The final rounding to n bits will be done at the summer output.

In most cases the filter response needed is symmetrical so that c₀=c_{n-1}, c₁=c_{n-2}, etc. This means that by adding the relevant delay out-

EXAMPLE 1: AUDIO FIR FILTER APPLICATION

A popular technique used for both audio and video data compression is sub-band coding. This involves splitting the audio spectrum into bands, Figs 4, 5 using a number of FIR bandpass filters. Next the different filter outputs are quantized

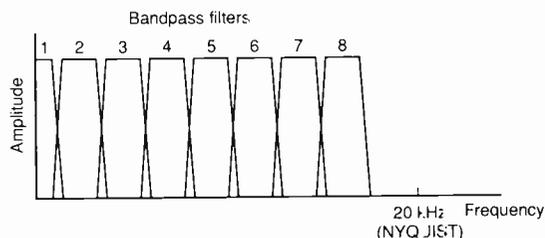


Fig. 4. Spectral segmentation FIR bandpass responses for audio sub-band coding

with different resolutions, i.e. bits per sample. Lower frequency bands are generally given a higher number of bits per sample than higher frequency bands.

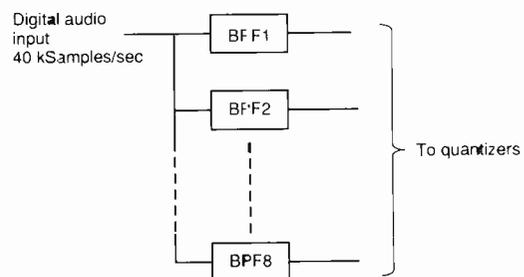


Fig. 5. finite-impulse response bandpass filters used at audio sub-band coder front end. These filters can be implemented in Xilinx FPGAs.

puts before the coefficient multiplication stage, the number of multipliers required is reduced from $2n+1$ to $n+1$.

Also, using general purpose multipliers to realise the required filter response as indicated in Fig. 1 can introduce redundancy. By using a shift-and-add technique, a Xilinx FPGA can remove this redundancy allowing a much more efficient implementation of the required FIR filter.

Shifting-and-adding

Consider an 8-bit two's complement number:

$$s \ b_7 \ b_6 \ b_5 \ b_4 \ b_3 \ b_2 \ b_1$$

This consists of a sign-bit, s , and seven other bits b_{7-1} . To multiply this number by a half, it is necessary only to shift it one place to the right, duplicating the sign-bit:

$$s \ s \ b_7 \ b_6 \ b_5 \ b_4 \ b_3 \ b_2 \ b_1$$

If the original number is thought of as having a range of -128 (10000000_2) to $+127$ (01111111_2) in integer steps, then the shifted number has a possible range of -64 (11000000_2) to $+63.5$ (00111111_2) in half integer steps.

By shifting the original number two places to the right, you effectively multiply it by a quarter. The sum of these two shifted numbers is therefore equal to the original number multiplied by three quarters. This process of shifting and adding can be continued to implement the product of any two digital numbers.

There is no requirement for CLBs in the shifting process because it is inherent in the routing. As a result, each multiplication can be implemented with adders alone. Extra delays in the form of D-type flip-flops may be needed between the addition stages, depending on the coefficient value and the sampling frequency.

Clearly, the coefficient value determines the number of addition stages necessary to implement the product. Each logic one in the coefficient binary representation represents an adder input in hardware terms. The fewer the number of ones, the lower the hardware requirement. This is why $1/2$ (01000000_2) and $1/4$ (00100000_2), assuming a range of -1 to $+127/128$, are convenient coefficients.

A coefficient like 01111111_2 is not as difficult as it may appear because it can be implemented as its two's complement inverse (10000001_2). The resulting product is then inverted before being fed to the final summer.

One way to guarantee convenient coefficients is as follows. Firstly design the filter using a standard filter design technique such as the Remez Exchange Algorithm¹. This will produce 'not-necessarily-convenient' coefficients in terms of ease of implementation by a shift-and-add technique. It does however minimise the deviation from the desired ideal filter specification. Secondly, carrying out a discrete space search around these coefficients to produce a convenient set of coefficients. These keep deviation from the desired ideal filter

specification within a specified tolerance.

The greater the number of coefficients, the more difficult it becomes to find a set of convenient coefficients. An easy way around this using a Xilinx FPGA is to implement the desired filter as a cascade connection of smaller filters, i.e. with fewer taps. When two or more FIR filters are cascaded, the resulting transfer function is equal to the product of the individual transfer functions.

For example, the bandpass filter transfer function of Fig 7(c) could be implemented as a cascade connection of a lowpass filter, Fig 7(a) and a highpass filter, Fig 7(b). The relatively undemanding transfer functions of the low- and highpass filters make it easy to find convenient coefficients for their shift-and-add implementation in the FPGA.

If a sharper bandpass transfer function were required, the above filter could simply be cascaded with an identical version of itself, Fig 7(d). As the individual filters in the cascade chain are relatively simple, a large number of them can be incorporated into a single Xilinx FPGA device, yielding a complex overall transfer function. ■

Glossary

- ASIC** application specific IC.
- BPF** bandpass filter
- CLB** configurable logic block, a functional element from which the user's logic is constructed.
- DAT** digital audio tape
- DCC** digital compact cassette
- DSP** digital signal processing
- FIR** finite-impulse response
- FPGA** field programmable gate array
- HPF** highpass filter
- IIR** infinite impulse filter
- LPF** lowpass filter
- PAL** phase alternate line
- RGB** red green blue

Reference

1. Rabiner, L. R. and Gold, B., *Theory and Application of Digital Signal Processing*, Prentice-Hall.

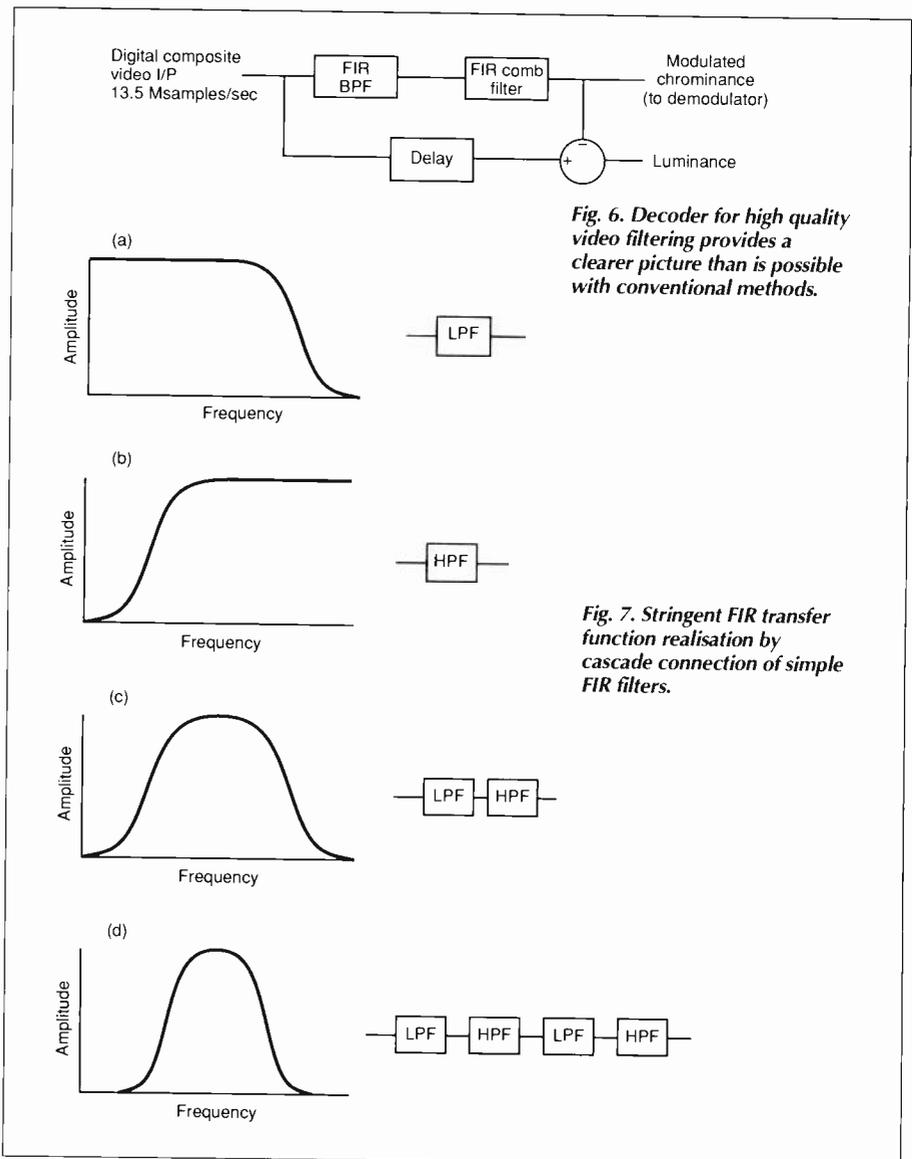


Fig. 6. Decoder for high quality video filtering provides a clearer picture than is possible with conventional methods.

Fig. 7. Stringent FIR transfer function realisation by cascade connection of simple FIR filters.

ELECTRONIC ENGINEERS REFERENCE BOOK

6th Edition
F F Mazda

This reference book is divided into five parts: techniques, physical phenomena, materials and components; electronic design and applications. The sixth edition was updated throughout to take into account changes in standards and materials as well as advances in techniques, and was expanded to include new chapters on surface mount technology, hardware and software design techniques, semi-custom electronics and data communications.

Fraidoon Mazda has worked in the electronics and telecommunications industry for over twenty years, and is currently Product and Operations Manager, Generic Network Management, with Northern Telecom. He is the author of six technical books (translated into four languages) and the editor of the Communications Engineers Reference Book published by Butterworth-Heinemann.

CONTENTS:
Techniques
Trigonometric functions and general formulae;

Calculus; Series and transforms; Matrices and determinants; Electric circuit theory; Statistics. **Physical Phenomena**
Quantities and units; Electricity; Light; Radiation; The ionosphere and troposphere. **Materials and components** Resistive materials and components; Dielectric materials and components; Magnetic materials; Inductors and transformers; Relays; Piezoelectric materials and components; Connectors; Printed circuits; Power sources; Discrete semiconductor devices; Microwave semiconductor devices; Optical digital integrated circuits; Linear integrated circuits; Semiconductor memories; Microprocessors; Application-specific integrated circuits; Electron microscopy; Digital design; Software engineering; Digital systems analysis; Control systems; Antennas and arrays; Noise management in electronic hardware; Noise and communication; Computer aided design; Television and sound broadcasting. **Applications**
Communication satellites; Point-to-point communication; Fibre-optic communication; The integrated services digital network (ISDN); Local area networks; Radar systems Computers and their application; Videotape recording; Office communications; Medical electronics.

1006 pages PAPERBACK ISBN 07506 0809 9
£42.50 (inc post & packaging)

Please return to: Lorraine Spindler, Room L333,
Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

ELECTRONICS ENGINEER'S REFERENCE BOOK

6th Edition



Edited by F F Mazda

- * Now available to Electronics World & Wireless World readers in paperback.
- * Expert coverage of all aspects of electronics
- * Over 50 contributors
- * For electronic engineers, technicians and students

Please supply me — copies of the **ELECTRONIC ENGINEERS REFERENCE BOOK (ISBN 07506 0809 9) @ £42.50 (INC POST & PACKAGING)**

Add VAT at local rate _____
NB ZERO RATE FOR UK & EIRE TOTAL _____

Business purchase: Please send me the books listed with an invoice. I will arrange for my company to pay the accompanying invoice within 30 days. I will attach my business card/letterhead and have signed the form below.

Guarantee: If you are not completely satisfied, books may be returned within 30 days in a resalable condition for a full refund.

Remittance enclosed £ _____
Cheques should be made payable to **Reed Book Services Ltd.**

Please debit my credit card as follows:

Access/Master _____ Barclay/Visa _____
Amex _____ Diners _____

Credit Card No. _____ Exp date _____

NAME (Please print) _____

ORGANISATION _____

STREET _____

TOWN _____

COUNTY _____ POST CODE _____

COUNTRY _____

DATE _____ TELEPHONE NUMBER _____

SIGNATURE _____

T3000

VAT RATES

6% Belgium, 25% Denmark, 5.5% France, 7% Germany, 4% Greece, 4% Italy, 3% Luxembourg, 6% Netherlands, 5% Portugal, 3% Spain. FOR COMPANIES REGISTERED FOR VAT, PLEASE SUPPLY YOUR REGISTRATION NUMBER BELOW (customers outside the EEC should leave this part blank)
VAT NO. _____

If in the UK please allow 28 days for delivery. All prices are correct at time of going to press but may be subject to change.

Please delete as appropriate. I do/do not wish to receive further details about books, journals and information services.

Credit card orders
accepted by phone.
Call 081 652 3614.

CIRCUIT IDEAS

SEND YOUR CIRCUIT IDEAS TO THE EDITOR, ELECTRONICS WORLD, QUADRANT HOUSE, THE QUADRANT, SUTTON, SURREY SM2 5AS

Do you have an original circuit idea for publication? We are giving £100 cash for the month's top design. Other authors will receive £25 cash for each circuit idea published. We are looking for ingenuity in the use of modern components.


£100 WINNER

Single-pot polarity and gain adjustment

Using the 2:1 gain difference between inverting and non-inverting operational amplifiers, one control varies the output between a replica of the input and an inverted version, both being at unity gain.

Its uses include audio processing in which, used with a bucket-brigade delay element, it will allow the positions and amplitudes of the peaks and nulls of a comb filter to be adjusted.

Ben Sullivan
Waterlooville
Hampshire

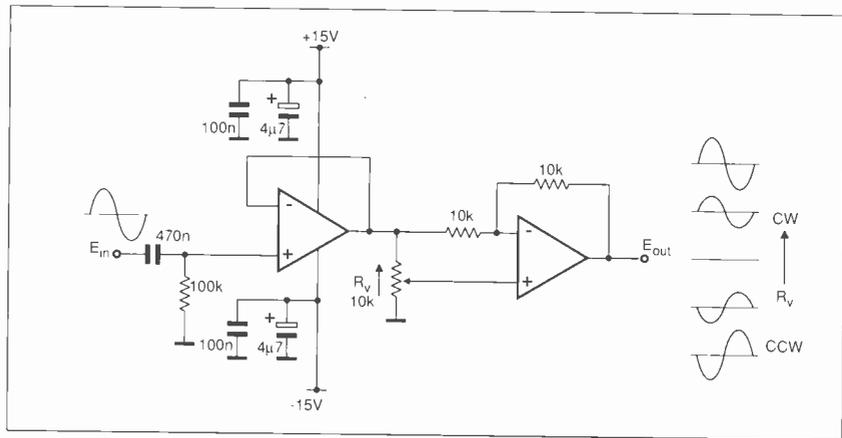

Potentiometer R_v varies output from inverted to non-inverted version of the input at unity gain.

Full-wave rectifier uses single amplifier



Incorporating an op-amp, one diode and a fet, this rectifier is linear down to less than 1mV, assuming that the op-amp's input voltage offset is compensated. Performance depends on input amplitude, being around 20% down at 1kHz and 50mV input.

On a negative half-cycle, the p-channel fet is open-circuit and the result is a unity-gain inverter. With a positive half-cycle, the fet

conducts in reverse mode due to the presence of the large open-loop signal on its gate and the signal appears at the output.

Giuseppe Faini
Milan
Italy

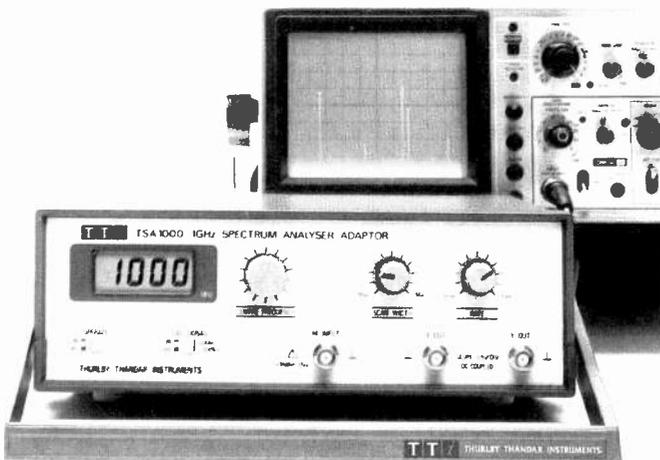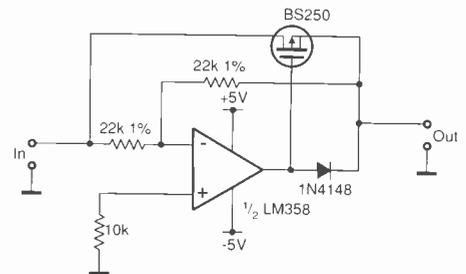Simple, but accurate full-wave rectifier, linear down to less than 1mV.



YOU COULD BE USING A 1GHz SPECTRUM ANALYSER ADAPTOR!

Got a good idea? Then this Thurlby-Thandar Instruments TSA1000 spectrum analyser adaptor could be yours.

Covering the frequency range 400kHz to over 1GHz with a logarithmic display range of 70dB \pm 1.5dB, it turns a basic oscilloscope into a precision spectrum analyser with digital readout calibration.

Recognising the importance of good design, TTI will be giving away one of these excellent instruments every six months to the best circuit idea published in the preceding period until further notice. This incentive will be in addition to our £100 monthly star author's fee together with £25 for all other ideas published.


Our judging criteria are ingenuity and originality in the use of modern components with simplicity particularly valued.

Frequency doubler

TTL square waves at the input to the 74LS123 dual monostable multivibrator produce output pulses at double the input frequency. 1N4148 switching diodes Or together the outputs on pins 5 and 13, the two square-wave inputs having triggered the two monostables on opposite edges. Output pulse width is 3.3µs with 10kΩ and 470pF timing components according to the timing equation, pulse width = 0.7CR. Since the package introduces 50pF residual capacitance and since R must lie between 5kΩ and 260kΩ, the practical minimum pulse width is around 350ns.

The process can be continued by driving a similar circuit with this output.

Mike McGlinchy
Mount View
California
USA

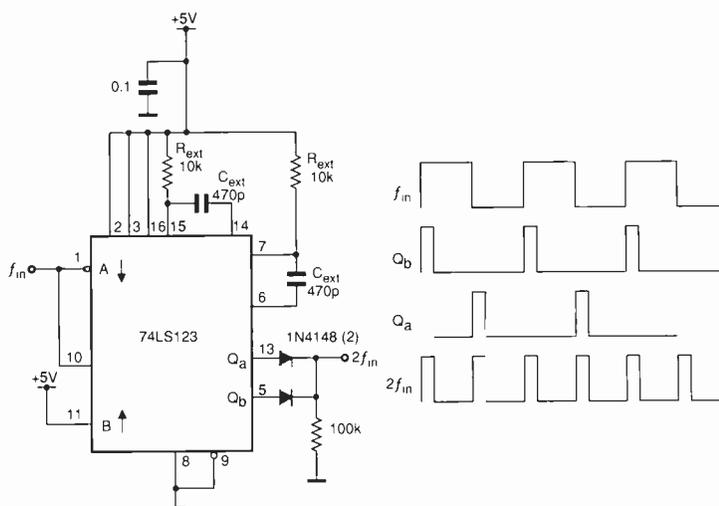

TTL pulse-frequency doubler for operation up to about 2.5MHz with a pulse width of 350ns minimum.

Low-level crossover is maximally flat

High and low frequency outputs from this low-level crossover network, Fig. 1, are in maximally flat, two-pole Butterworth form with 12dB/octave final slopes.

Output curves shown indicate that the amplifier is active mainly around the crossover frequency – in this case, 1kHz. Values shown are in ohms and farads, the crossover being at $\omega=1$. Since input and output of the amplifier are dc-blocked, the practical circuit can use a single supply with the non-inverting input biased to half the supply voltage. A snag is the lowish input and high output impedances, but a practical circuit would include means of correcting them.

Analysing the circuit of Fig. 2 shows the basic section, which gives 12dB/octave, but which cannot be maximally flat. Figure 3 is more or less the same circuit with gain; resistors and capacitors are of equal value.

Since the desired transmission is

$$T = \frac{1}{p^2 + p\sqrt{2} + 1}$$

where $p = j\omega$, assume a 1V output and work backwards to make the input

$$e_{in} = p^2 + p\sqrt{2} + 1.$$

From Fig. 3

$$e_{in} = 1 + pA + A[p + p(1 + pA + pB)]$$

$$e_{in} = 1 + 3pA + p^2(A^2 + AB)$$

so

$$3A = \sqrt{2} \quad \text{and} \quad A^2 + AB = 1$$

or

$$A = \frac{\sqrt{2}}{3} \quad \text{and} \quad B = \frac{7}{3\sqrt{2}}$$

Amplifier output is in bandpass form with its centre frequency $\omega=1$. The high-pass circuit using that voltage is added to the low-pass section to form the complete crossover.

Actual component values for the circuit are calculated as follows, and given $f=1\text{kHz}$ and $C=4\text{nF}$

$$R_1 = \frac{3}{\sqrt{2}} \times \frac{1}{2\pi fC} = 71.83\text{k}\Omega$$

$$R_2 = \frac{7}{3\sqrt{2}} \times \frac{1}{2\pi fC} = 55.87\text{k}\Omega$$

$$R_3 = \frac{\sqrt{2}}{3} \times \frac{1}{2\pi fC} = 15.96\text{k}\Omega$$

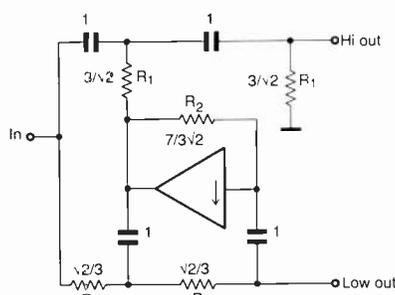


Fig. 1. Low-level crossover circuit with values normalised to $\omega=1$, components in ohms and farads.

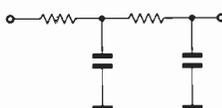


Fig. 2. Basic lowpass circuit, which needs gain for maximal flatness.

The circuit was built using an LF356 op amp although a better device should be used for serious applications. The response departs from the theoretical only by the component tolerances used in the actual circuit.

McKenny W Egerton jr
Owing Mills
Maryland
USA

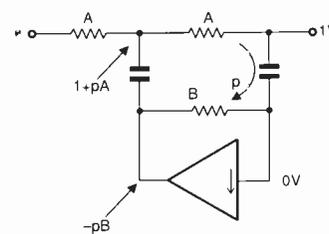


Fig. 3. Resulting lowpass section.

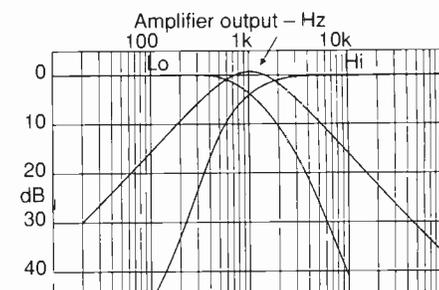


Fig. 4. Output characteristic of final circuit. Amplifier takes part mainly around crossover frequency.


Grounded-load current pump

Improvements on the Howland current source proposed by Steele and Green¹ demand close resistor matching to avoid gross error². This circuit needs no matching.

The source uses two zener diodes as voltage regulators, the control voltage V_c thereby generated riding over the feedback voltage. Output voltage is the sum of load voltage and V_c , which gives a constant V_c across the sense resistor R_s , load current therefore being V_c/R_s . Lower-voltage zeners are preferable in this circuit.

Ashwani Karnal

Bhaba Atomic Research Centre
Jammu
India

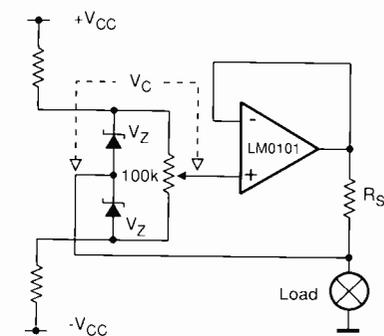

Current source poses no resistor-matching problems.

References

1. Steele, J & Green, T. Tame, *Those Versatile Current-Source Circuits*. *Electronic Design*, Oct. 15, 1992.
2. Baker C B. *Current Source Saves Resistors*. *Electronic Design*, June 25, 1992.

Disabled person's television remote controller


Adapting a remote control unit for use by someone with limited hand movement, this circuit steps through the four channels and standby in response to pressure on an elbow-operated microswitch. Output fets are in parallel with the controller buttons, so that the controller is still operable in its normal mode.

Half the dual monostable IC_{1a} debounces the microswitch, clocks the 4017 decoded decade counter and triggers the second monostable to produce a 0.5s pulse, simulating a button press. Decoded outputs from the 4017 are buffered in the tri-state 4503 hex. buffer and used to drive the button fets.

Since power for the adaptor comes from the controller, decoupling must prevent current spikes from the transmitter led clocking the counter.

C Drinkwater

Wotton-under-Edge
Gloucestershire

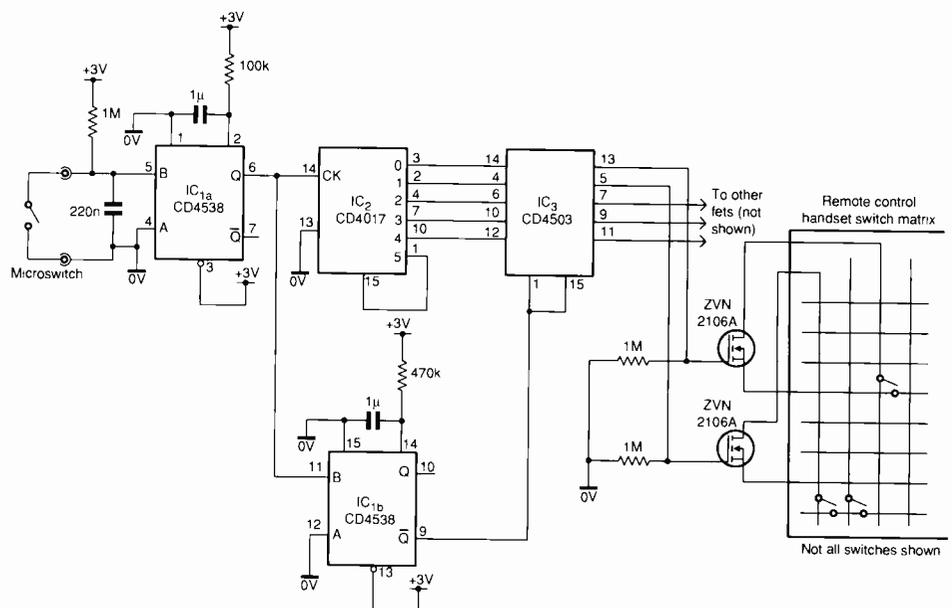

Disabled person's tv controller adaptor, operated by microswitch to step through channels and standby.

Linear optocoupler cancels errors

Using a dual optocoupler and an instrumentation amplifier, this isolation amplifier is linear and operates well above the cut-off frequency of much more expensive commercial devices.


To achieve a linear transfer function, the leds in the optocoupler are run in series at 1mA, the resulting differential signal appearing at the collectors of the transistors $Tr_{1,2}$ with virtually all errors cancelled out. Variable R_7 corrects for any offset. A useful feature of the 6N136 is that it has a screen between

input and output.

The required circuit gain is obtained by setting R_g , gain being $1+50/R_g$. As shown, the total circuit gain is unity, but optocouplers do vary.

A triangular waveform at 500Hz showed no measurable distortion at up to 2.5V and 2% at $\pm 8V$. As regards frequency, a $\pm 1V$ input gave a -3dB point of 150kHz. Input impedance is around 8k Ω , but a buffer could easily be used.

CJD Catto
Cambridge

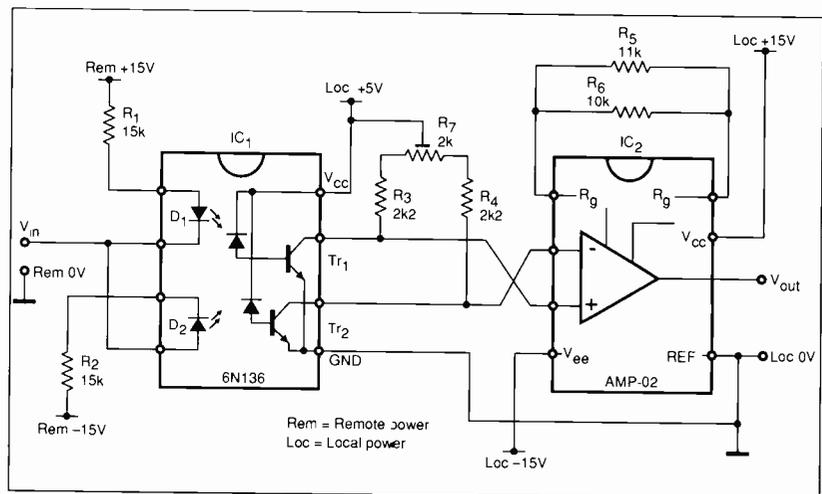

Low-cost, but linear and wide-band, optically isolated amplifier. Running leds differentially cancels out errors.

Current-biased Class-B output stage

Since, unlike the old germanium types, silicon power transistors do not need low-impedance sources to take account of thermal leakage effects, it seems strange that modern designs still appear to provide the low impedance. Indeed, the use of voltage sources can give rise to trouble due to amplification of thermal effects. This design uses current sources.

No bias adjustment is needed and R_x/R_y are chosen to suit the supply rails, in this case $\pm 20V$ to give 20W into 8 Ω . It is interesting that quiescent current increases as the power supply falls, reaching a maximum of 120mA at $\pm 12V$, which is small enough to avoid latch-up. This effect may eliminate crossover effects as output current peaks. Short-circuit protection is applied to the BC213/183 current mirrors by means of the diodes.


The circuit possesses some voltage gain, so that an op-amp or even the output of a personal stereo will drive it to full power.

The type of Darlington output device with built-in bias resistance is unsuitable for this application.

Anon

Rotherham
South Yorkshire

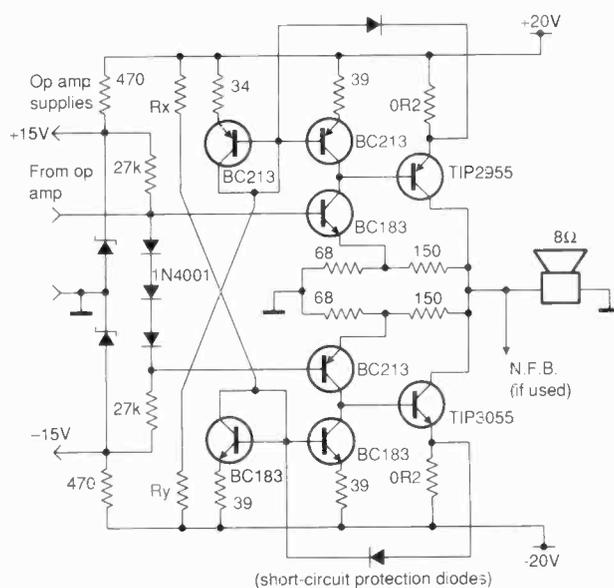Would this contributor please send his full name and address to our editorial offices? Ed.



Silicon audio power output stage, using current drive to the output transistors and needing no bias adjustment.


PCBs for Douglas Self's power amplifier series

Circuit boards for Douglas Self's high-performance power amplifier are now available via *EW+WW*.

Detailed on page 139 of the February issue, Douglas Self's state-of-the-art power amplifier is the culmination of ideas from one of the most detailed studies of power amplifier design ever published in a monthly magazine. Capable of delivering up to 100W into 8 Ω , the amplifier features a distortion figure of 0.0015% at 50W and is designed around a new approach to feedback.

Designed by Douglas himself, the fibreglass boards have silk-screened component IDs and solder masking to minimise the possibility of shorts. Sold in pairs, the boards are supplied with additional detailed constructional notes.

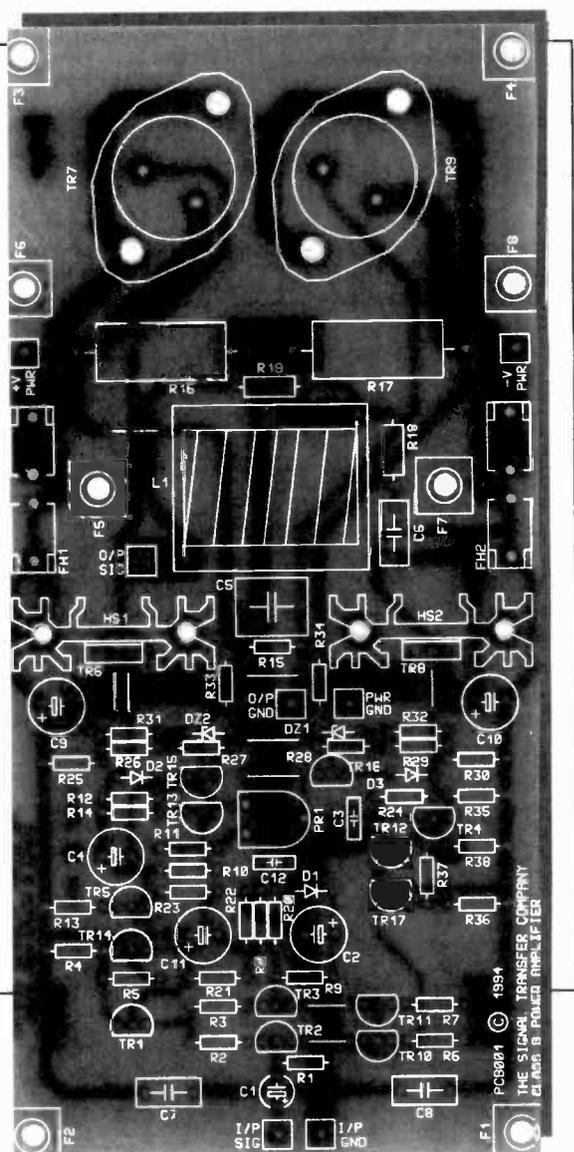Each board pair costs £45, which includes VAT and postage, UK and overseas. Credit card orders can be placed 24 hours on 081-652 8956. Alternatively, send a postal order or cheque made payable to Reed Business Publishing to *EW+WW*, The Quadrant, Sutton, Surrey SM2 5AS.



LETTERS

Critical response

I cannot agree with Graham Maynard's rather vague analysis of class A and B amplifiers (*Letters*, June). Apart from anything else, I don't care for the way he, at a critical point in the argument, turns "conceivably" into allegedly solid fact in the next sentence. Back emfs from reactive loads do not cause detectable intermodulation¹ and even if they did, a higher feedback factor would surely reduce rather than increase the effect. As far as I know, no-one has ever argued that nfb does not effectively reduce amplifier output impedance. To go on and state as another fact that higher levels of nfb cause "audible confusion" (whatever that is, presumably some sort of distortion) is simply wrong.

Using nfb to correct an amplifier with second-harmonic distortion creates third and higher-order products that did not exist before. Baxandall² brilliantly demonstrated this, showing that these higher products have a maximum value for very low amounts of nfb (say 2-10dB) and that as nfb is increased to more practical levels (like 30dB) the level of all the higher products decreases. The result is surely a powerful argument against the use of low nfb factors.

As for the sliding-bias scheme, I can hardly comment as Maynard's diagram seems to have been misdrawn: Tr_8 , the driver for Tr_9 , has disappeared, so the drive to Tr_9 is now in the wrong phase. Worse still,

Tr_9 is turned hard on via the two diodes and the only result of building the circuit as shown will be a loud bang as two power transistors lay down their lives to protect the ht fuses.

Turning to Marcel van de Gevel's comments (*Letters*, May) concerning control of quiescent currents, I agree completely. But I would mildly point out that I specifically mentioned "harmonic AB", which gives the long, smooth device-to-device transition he describes, in Part 5 of the series. I also gave a reference to the intriguing work of F A Thus, and I do have well-thumbed copies of all the other references he quotes. The trouble with these schemes as they currently exist is that they depend on IC techniques such as matched and collector-area-scaled bjts. A discrete component version would no doubt be possible, but it would need to be designed from the ground up and would represent a serious piece of research work – not something that can be dealt with as an adjunct to a larger article. Anyone care to have a go? (An approximation to harmonic AB can be achieved by eliminating the usual output emitter-resistors; crossover gain variations are less, but still exist, and there is a clear and present danger of thermal runaway.)

I am sorry that Chris Bulman (*Letters*, May) finds my class-A quiescent regulator inelegantly intrusive; surely it can't be too bad, having only three transistors, and not even being in the direct signal path? At least it is effective.

As far as I can determine from re-

reading the 1969 article, John Linsley Hood's psu is essentially constant-voltage, though with that voltage rather uncertainly determined by transistor B, as indeed is the amplifier quiescent current (I_q). If this psu really does play an important role in protecting against thermal runaway in the amplifier then I would suggest that the amplifier design could possibly be improved. It hardly counts as an effective method of I_q control.

Since the matter has been aired, I may as well report my own experiences with this design. With an I_q of 1.25A, the I_{hd} at 10W/8Ω and 1kHz was 0.25%, which I found rather discouraging. The output transistors are not driven so as to give pure push-pull action, and the sum of output-device currents (which in true push-pull is virtually constant over a cycle) varies by more than 40% (see *PSpice* plot).

The logic behind de-coupled amplifiers is not obscure. Reservoir capacitors are simply storage elements, and have no direct effect on the amplifier output. That is (or should be) in the iron grip of a hefty negative feedback factor, and immune to ht rail influence. In contrast, an output capacitor handles the signal after the nfb has controlled it, and so any capacitor-distortion it may generate at I_f is passed on untouched to the loudspeakers.

Any de-coupled amp must have a dependable offset-protection system. I can only admire the breath-taking audacity of Mr Bulman's scheme for cooling output transistors by making them boil water. One might object to the pedestrian grounds that the junction-case thermal resistance of even the heftiest TO3 transistors is a 0.7°C/W and so observing a 200°C junction temp maximum reduces the permissible power dissipation from 250 to 70W. I might also point out that elevated temperatures degrade reliability – however this is to detract from the grand sweep of the concept.

Since the transistor cases appear to be in actual contact with the water, there are presumably four electrically-isolated boiling tanks, two for each channel, each with their own condensers and circulating pumps. The arrangement will make for an impressive-looking piece of equipment, reminiscent of the engine-room of a medium-sized steam-tug. Deionised water could be used to minimise conduction – but this is not the ideal basis for a good cup of tea. I cannot resist speculating on the software used to test the system. Handel's Water Music is an

obvious choice; tapes of steam radio might be even more appropriate.

Douglas Self
Forest Gate
London

References

1. Cordell, R. *Interface Intermodulation in Amplifiers*, *Wireless World*, Feb 1983, p.30.
2. Baxandall, P. *Audio Power Amplifier Design: Part 5*, *Wireless World*, Dec 1978, p.56.

Beach buff

Alan Dyke's criticism of audio mysticism makes sense – except for his reference to sand-filled speaker stands, of which I have just bought a pair.

Producing stands with hollow vertical supports is presumably cheaper than using solid stock which would be better and heavier. So filling them with something to facilitate coupling the base of the cabinet to floor, in view of the powerful magnet and coil action of the main drivers, makes sense.

Liquid, especially water, would actually transmit sound vibrations faster than in air. Sand is freely available at low cost – especially if you are near a beach as I am.

Spikes through the carpet pile to floor complete the set-up, and are necessary when using the new D Self amp, of which mine must be one of the first examples.

Hugh Haines
Sunderland

Small world

H G Groenevelt seems not to appreciate the difference between a theory and a theorem. There is all the difference in the world. Maybe that accounts for his confusion.


R H Pearson
Lincs

Amnesty appeal

Mu'taz Qutlabi is an electrical engineer with Aleppo Electricity Company. He is 38, married with one child, and this July sees his 12th year of imprisonment as a Syrian Prisoner of Conscience.

Mu'taz, detained in Damascus, is just one of thousands of political prisoners held in Syria without charge or trial, for their peacefully held beliefs. Many are detained under emergency legislation in force since 1963, suspending all constitutional protection against abuse by the state. Others have been held for more than 20 years, face torture – routine in Syria – and are denied the chance to challenge the

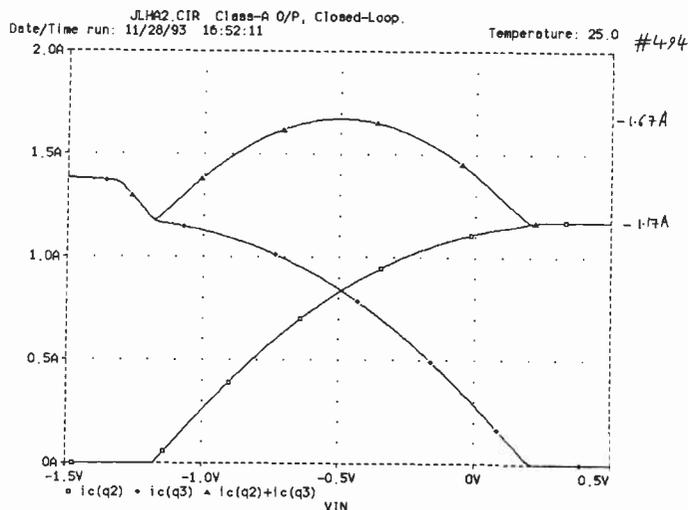PSpice plots of output device currents for the complete closed-loop amplifier. The plots in Part 8 of Self's Distortion in Power Amplifiers series were all done open-loop.



legality of their detention.

Mu'taz is being held at Fir' Amn al-Dawla prison, and Amnesty International is calling upon the Syrian authorities to release him immediately. Every letter of support helps. Please write saying you have read about his case. Courteous letters in English should be sent to: His Excellency, President Hafez al Assad, Presidential Palace, Abu Rummaneh, Al-rashid Street, Damascus, Syrian Arab Republic.
Paul Horvath
Rochdale Amnesty
Lancs

Hidden meaning

Unfortunately a short paragraph is missing in my article *Optoelectronics by design* (EW WW, May 1994, pp. 364-369). The box titled 'Units and meanings' should conclude with two equations relating to the presented drawings (Fig. d, middle and bottom).

The equations regarding proximity sensors should read:

$$U_T = S.R.G.I_c[\tan(\omega)/d]^2 \quad \dots(4)$$

where ω is the transmitter diode half power angle and d is the distance to a large object, and,

$$U_T = S.R.G.I_c[r/d^2]^2 \quad \dots(5)$$


where r is the radius of a small object at distance d .

The final part of the article refers to a calculation based on equation (4).

Tore Arne Nielsen
Denmark

Graphic example

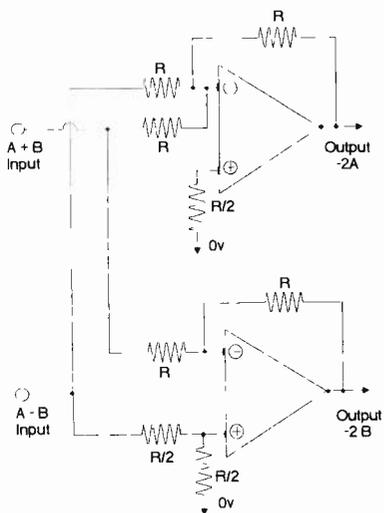In my article on Arnold Sugden (EW+WW, pp. 486-487) a small error appeared in the published version of the matrix. Please would you publish a correction so my colleagues at Keele will continue to talk to me?



Incidentally, as one who is still climbing the steep learning curve of *Windows* after no problems whatsoever with the delightfully simple gui of the Atari, why on earth didn't Bill Gates produce a fully integrated dos with gui? Now, of course, he cannot; it would kill *Windows* stone dead.

Reg Williamson
Staffs

Gates didn't, but another company did. It's called the Amiga... Ed.

IC - can you?

Can any EW+WW reader help me find a superseded integrated circuit?

I have a Rohde & Schwarz test unit called an smpu, manufactured about 17-18 years ago. It is a radio-set test assembly for testing mobile radio transceivers up to 500MHz. I use it for testing radios provided by my club for communications at motor sport events.

No payment is received for the work which is really part of my hobby. So I can not justify spending large amounts of money on repair. The unit is a fine piece of test equipment and most components are bog-standard garden-variety. Unfortunately, the microprocessor has died. It is an Intel 4004, a very early four-bit micro which does not appear to be available at traditional Australian component suppliers.

Rohde & Schwarz can supply the device - for A\$450! While I can understand the need to charge this amount to cover the cost of storing this chip for 20 years, I still can not afford it.

What I am hoping for is that somewhere out there is a hoarder like me, who has a box full of Intel 4004s just gathering dust.

If any one can help I would be most appreciative.

David Ireland,
77 Vahland Avenue
Riverton
Western Australia, 6148.
Tel: 61 9 457 2733
Fax: 61 9 326 6669

Decoding US actions

I found Robert Schifreen's article on the DES data encryption standard (*Big Brother's protection racket*, EW+WW, May, p.388) very interesting. Back in October 1998 I recall an *IEEE Review* claiming that the US National Security Agency was withdrawing its support for the NBS Data Encryption Standard - introduced in 1977 because: "The tools of attack are that much stronger now". It makes the proposed US legislation to outlaw DES quite puzzling.

TJ Wynn
Newport

Calling cable suppliers...

I cannot help but think that there is rather more involved than logic and mere engineering principles when discussing sound reproduction.

My hearing is bad, cutting off at around 8kHz, and I am by no means musical so I will leave the esoterics of subjective testing to those who believe themselves so qualified. But I would suggest that those really interested should perform proper double-blind tests on a reasonably large number of people, as psychologists do. Whether imperfect electrolytics and other components cause audible distortion or not seems a moot point.

Over the last 25 years I have designed something like 3000 separate items: from a 25kA rectifier to a vhf synthesised transceiver, and including a few audio systems. When involved with the audio projects, I remember looking at response curves of the loudspeakers, as published by manufacturers. All those that I saw resembled a cross-section of the Himalayas.

While I well appreciate the difference between amplitude variations and (harmonic) distortion and non-linearity, I cannot really see the point in aiming for an amplifier chain THD of 0.0001% with existing transducers. Perhaps someone could comment on the linearity, or lack thereof, of a coil moving in the magnetic field of a loudspeaker?

My guess is that the flux density is not totally uniform across the entire gap: so the deflection of the coil will not be a perfect reflection of the drive current. This of course will lead to distortion, most likely a reduction in amplitude of the peak of the wave (assuming the flux decreases towards the edge of the gap).

I have no idea what happens to the cone of the speaker when driven by complex waveforms, but would imagine that it would make an interesting study. What I would like to know is the figure for transducer linearity, both at the microphone and loudspeaker ends of the chain.

With these figures, one could then determine what level of amplifier distortion was acceptably small, and what was ridiculous.

As electronic design is a creative art, there is always the drive to achieve the ultimate, the perfect, or in the case of audio circuits, zero distortion. But, as all of those involved in design know, one must maintain a sense of reality, and know when it is time to shoot the engineer.

Perhaps an EW+WW reader familiar with loudspeaker and microphone performance could respond with some hard facts concerning transducer linearity?

Until such time, I don't think I'll be buying any silver loudspeaker cables.

Charles Frizell
Harare

...to prove a difference

Gold-plated speaker cables, silver-plated, platinum-plated etc... isn't it apparent that we professional engineers are starting to behave like amateurs. Neither the Yes nor No fraternity can produce irrefutable evidence that their beliefs are correct. I say 'beliefs' because without proof, that is what they must remain.

The continuing dialogue echoes the heated discussions that took place, many years ago, when the particular attributes of moving-iron and balanced-armature loudspeakers were compared. But that was resolved with the introduction of the moving-coil loudspeaker which quickly killed off the two warring factions.

There might be individuals who honestly believe they can detect a difference when special cables are used. But there are also far more audiophiles who declare that claim to be a load of rubbish.

I accept that 'might' does not necessarily mean 'right' any more than it did for the flat earth proponents of years ago. But until we have proof one way or the other, we are all just flogging a dead horse.

Logic tells us there should be no difference. Perhaps our logic is wrong, although I thought we were involved in a science more exact than most. Ramblings on the subject suggest we are actually a bunch of dabblers.

We should drop the perhapses and maybes and shut-up until someone produces proof either way. Could a supplier help by publishing details of test procedures? Come-on all you special cable manufacturers out there. Tell us the secret of your product. Or did I hear you say you do not have patent cover, or a registered design, or have not been granted a Kitemark?

RL Tufft
Thirsk

USING RF TRANSISTORS

Combined efforts bring power pay-offs

Splitting a signal to provide multiple inputs for several amplifier modules then recombining the result is an obvious way of boosting power output. Norm Dye and Helge Granberg describe different possible combiner/splitter configurations and show why they all have a place in the designer's portfolio. From the book RF Transistors: principles and practical applications.

When the required power output exceeds the capabilities of a single power amplifier, multiple stages or "modules" can be combined to produce the required result.

A splitter – simply a lower-powered version of a combiner used in reverse – divides the input signal into multiple equal amplitude outputs. These are applied to the inputs of each

module. The power combiner then recombines the module outputs ready for feeding into a single load.

Combiners are closely related to wide-band transformers in design and construction – the main difference is how the lines or windings are connected (power splitters have the same configuration, so need not be treated separately).

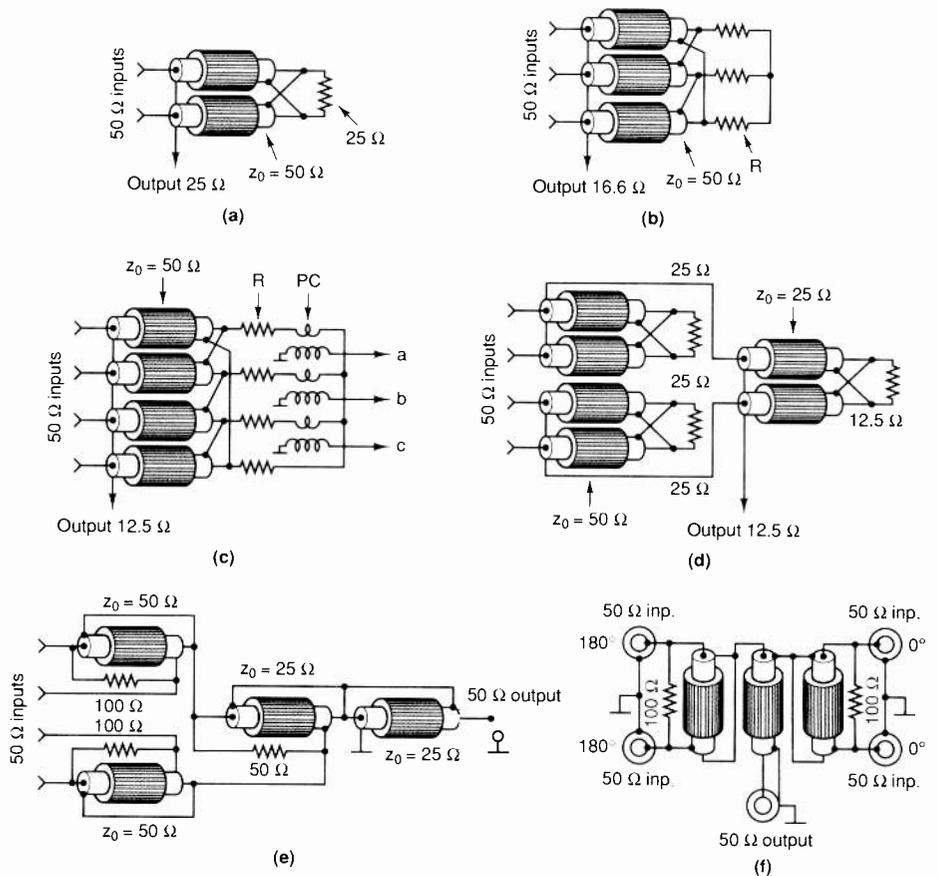


Fig. 1. a), b) and c) represent straight in-phase combiners. Even and odd numbers of input ports are possible with them. d) and e) are staggered or "totem pole" structures, which are adaptable only to even numbers of ports. f) is a 180° combiner that requires no step-up transformer into 50Ω. Note that step-up transformers are not shown for a), b), c) and d).

Wideband power combiners need to have low insertion loss over the required bandwidth; provide isolation (minimum coupling) between the input ports, and show low return loss at the input ports over the required bandwidth.

Their operating bandwidth should be wide too – or wider than the amplifier modules or they will restrict the overall bandwidth of the combined amplifiers.

Several different types of power combiners are available, each having advantages regarding frequency spectrum, bandwidth and other preferred features.

Four main combiner types

Zero degree device: ideally there will be no phase shift between the input ports and the combined output. The device can be designed for even or odd number inputs up to a practical limit. Practical frequency range is up to about 500MHz. These combiners are most common at lower frequencies because of their versatility and straight forward design.

180° device: the two input ports or sets of input ports are 180° out of phase. The device is only applicable to even numbers of inputs: eg 2, 4, etc. Out-of-phase characteristic must be taken into account when designing the input power splitter. Practical frequency range is up to about 100MHz.

90° hybrid: two port unit having, by nature, a narrower bandwidth than the above configurations. The device is applicable from low frequencies to microwaves in proper design configurations.

“Wilkinson combiner”: relatively narrow bandwidth characteristics, but simple and inexpensive. The practical frequency range can be up to microwaves (1-2GHz).

The input power-splitter must be of the same type as the output combiner. An in-phase splitter used with a 180° combiner for example would produce zero combined output power, since the outputs from each amplifier module would cancel.

In-phase and 180° combiners

Transmission line techniques are commonly used in in-phase and 180° power combiners to produce lowest losses and widest bandwidths.

One primary function of an rf power combiner is to provide port-to-port isolation – 30dB is typical and acceptable. By this, the output of one amplifier module will be sufficiently isolated from the others. If a failure in one occurs, the remaining amplifiers will not be affected and will still be operating into the original load impedance. Amplitude unbalance is usually created by a completely disabled module (the “source” for the combiner) or, sometimes, more than one disabled source. Power output with various numbers of disabled sources can be calculated as:

$$P_{out} = (P/N)N_1$$

where *P* is the total power of operative sources, *N* is the total number of initial sources and *N*₁ is the number of operative sources.



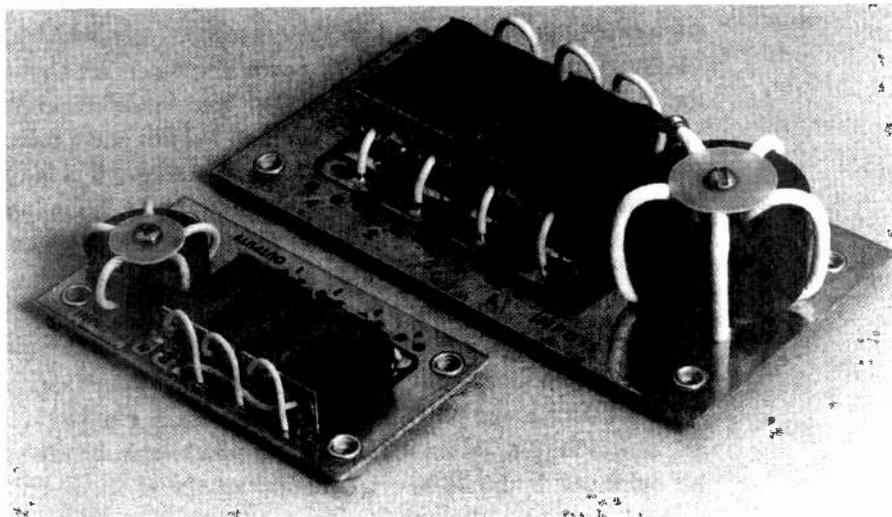
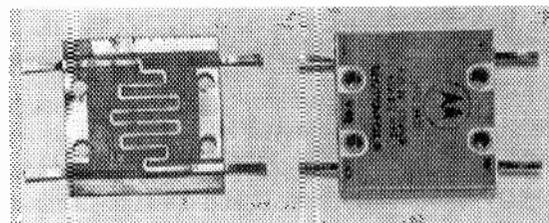


Fig. 2. Commercial four-port splitter-combiner for use at 1.6-20MHz and power levels up to 1kW. The device is of the type shown in Fig. 1c but the combiner lacks the power pick-up coils. The 50Ω lines are realised by metal tubes with a proper size of insulated conductor threaded through the tube, reducing construction costs. Note the compactness of the units, where the step-up transformer is right next to the combiner structure.

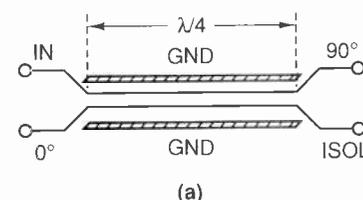

(a)

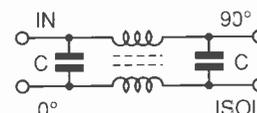

(c)

Fig. 3. The line hybrid, a) and b), is widely used at vhf and uhf since it can be made compact by folding the lines. Its lumped constant equivalent is shown in 3c. The complete uhf coupler has dimensions of approximately 38mm square and 3.5mm thick.

(eg, two-way carbon type) threaded through the toroids.

RF voltages in the secondaries – generated by the unbalance due to a module failure – can then be rectified and processed to operate the shut-down circuitry. If the *a*, *b* and *c* outputs (Fig. 1c) are kept separated, each one can be made to operate an indicator, showing which module has failed. Resistor (*R*) values are not critical, since the power will be shut-off within a millisecond or so making the load mismatch unimportant.

But, for operation under reduced power conditions, the balancing resistors must handle continuous power levels. Here high-power resistors must be used that can be heat sunk, and that are “floating”, with the resistor ele-

For example, in a four-port system designed to deliver 1kW with 250W modules, with one module disabled power output would be (750/4)3 = 562W. The difference power of 188W would be dissipated in the balancing resistors, dividing according to the type of combiner. In a straight zero-degree combiner (Figs. 1a, 1b, and 1c) all resistors are of equal value and the power dissipated in each would be (188/3) = 62.5W in a four port system.

In a two-port combiner system having a maximum output power *P*_{max} if one amplifier fails the output power will decrease to a value 6dB below *P*_{max}. Half the power loss is due to lack of power from the disabled module and an additional 3dB is lost because the power from the remaining module now divides equally between the balancing resistor and the output load.

In this case the balancing resistor must dissipate 1/4 of the original *P*_{max}.

Values of the balancing resistors depend on the number of combiner ports and how many ports are assumed disabled at one time (as can be seen in the expression for *P*_{out} given above). Sometimes these resistors, which must be of the non-inductive type, are referred as dump loads since power due to phase- or amplitude-unbalance is directed to them. In most cases even if one module fails, the system is forced into a shut-down mode. So the balancing resistors do not have to dissipate significant power.

In the failure detection method using pick-up coils (Fig. 1c) the signal pick-up coils (pc) can be small toroids wound with multiple turns of wire. These can form the secondaries for rf voltage step-up transformers whose primaries are the leads of the balancing resistors

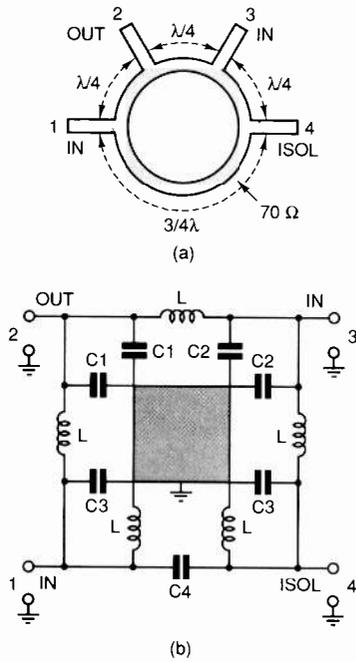


Fig. 4. Ring hybrid (a) and its lumped equivalent (b). In b, C1 and C2 can be paralleled into single units twice the value.

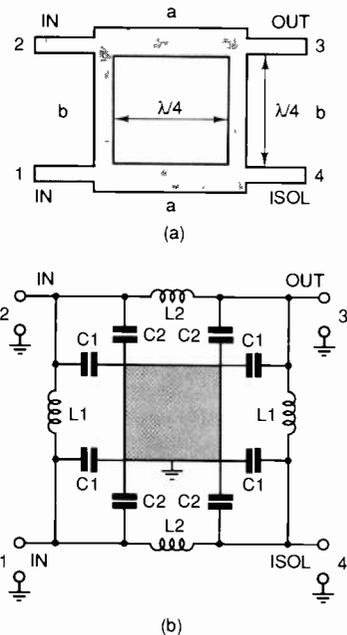


Fig. 5. The branch line hybrid (a) and its lumped equivalent (b). As in the ring hybrid equivalent, the paralleled capacitors (C1 and C2) can be combined into single units.

ment electrically isolated from its mounting structure.

In the event of a failure of one module (which is the most common case), the balancing resistor values can be determined from the formula:

$$R = Z_{in}/N$$

where N is the number of input ports.

Values of 25, 16.6, and 12.5Ω result for two, three and four-port combiners (Figs. 1a, 1b and 1c).

Examples of 180° power combiners include a "totem pole" structure (Fig. 1e) and a system consisting of a pair of two port hybrids and a balun (Fig. 1f).

Comparing the 180° and in-phase combiners shows that the 180° type can be superior in input vswr, but that the latter has better port-to-port isolation characteristics.

In cascaded or totem pole structures, the balancing resistor values follow the values of the two-port hybrids and transmission line transformers.

It is possible to design a system that does not require a step-up transformer (Fig. 1f). Its simplicity is attractive compared to other four-port combiners. The number of transmission lines can be halved and the lack of the 4:1 step-up transformer means bandwidth characteristics are enhanced – though this combiner is covered by a US patent.

Impedance ratios such as 2:1 and 3:1 can be implemented with a 4:1 transformer wound with coaxial cable where the corresponding taps are made to the coax braid. Improved performance over wider bandwidths is possible with fractional-integer equal-delay transformers.

In a commercially available four-port splitter-combiner (Fig. 2) intended for use at 1.6-30MHz and up to power levels of 1kW, port-to-port isolation figures of 27-40dB have been measured on both the in-phase and 180° combiners over a bandwidth of several octaves.

Several manufacturers make high power combiners for use at frequencies up to uhf, but most units are housed in enclosures with connectors and do not suit many designers because of physical outlines or cost.

90° hybrids

One class of hybrid that is a variation of the two-port is the quadrature, and quadrature-couplers can be realised in several different forms.

A quadrature combiner usually refers to a passive device with one input port, two output ports (or vice versa) separated by 90° phase, and an isolated port.

Some networks that can be considered as quadrature couplers are:

- Line hybrid (Fig. 3);
- 3λ/2 ring coupler (commonly known as rat-race, Fig. 4);
- branch coupler, widely used in small signal mixer circuitry but also applicable to use as a power combiner (Fig. 5);
- Wilkinson combiner, consisting of a series of λ/4 transmission lines (Fig. 6). Though not a quadrature coupler like those mentioned above, it is included because all four types are based on the principle of a delay generated by a quarter wavelength transmission line.

Line hybrids

The line hybrid (Fig. 3a), one of the most common combiners used in the vhf and uhf

frequency ranges, consists of two transmission lines (microstrip) of λ/4 in length separated by a dielectric. In addition the structure is sandwiched between two ground planes, again separated by a dielectric.

The mutual impedance between the two lines is designated as Z_{even} , whereas the impedance from the lines to ground is designated as Z_{odd} . Z_{even} is the impedance controlling the coupling coefficient between the lines and is typically $Z_{in}/2$. Then Z_{odd} must be calculated for a value that gives:

$$\sqrt{(Z_{even} \times Z_{odd})} = Z_{in}(50\Omega).$$

If $Z_{even} = 25\Omega$ as in this case, then Z_{odd} must be 100Ω for $Z_{in} = \sqrt{(2.5 \times 10^3)} = 50\Omega$. The Z_{even} and Z_{odd} values can be modified for greater isolation or extended bandwidth, but the $\sqrt{(Z_{even} \times Z_{odd})}$ relationship is always valid.

Typical bandwidths of these couplers are about 15% with 1:1.5 vswr and port-to-port isolation ranging from 20 to 30dB.

In the past, dielectric materials were Teflon-fibreglass (dielectric constant around 2.5) or epoxy-fibreglass (5). Low values of dielectric constants limited the couplers to a lowest practical frequency of approximately 175MHz, though even at these frequencies the couplers were bulky.

Today, advances in dielectrics have brought materials with dielectric constants of 10 or higher, making lower frequency couplers more practical.

To realise any kind of a practical size or shape factor, the lines are usually folded several times (Fig. 3b) and the total electrical length calculated for $l/4$ according to the dielectric constant of the medium.

A variation of the line combiner, designed with lumped constant elements for use at low frequencies, would behave much like its counterpart, the stripline quadrature hybrid. In a true representation of the stripline design, capacitors (C in Fig. 3c) should be split and their centre taps grounded to simulate Z_{odd} . Z_{even} would be determined by the mutual line impedance and the electrical length of the line, which should also be λ/4.

In practice, the transmission line can be made of twisted enamelled wires or two lengths of low impedance coaxial cable with their braids connected together and floating. The centre conductors are left to form two symmetrical lines.

Another adaptation, especially suited to low frequency use, is Fisher's hybrid (resembling more closely the hybrid shown in Fig. 3c). Very tight coupling between the lines is required, and line physical lengths need not be λ/4 since they are electrically lengthened by the presence of the magnetic medium. C depends on the line coupling coefficient and may not be necessary at all in some cases.

The phase relationship is the same as in the stripline hybrid and port isolations are comparable too. Bandwidth achievable depends on line inductance – and so properties of the magnetic core – as well as the line mutual capacitance (coupling). But using the tech-

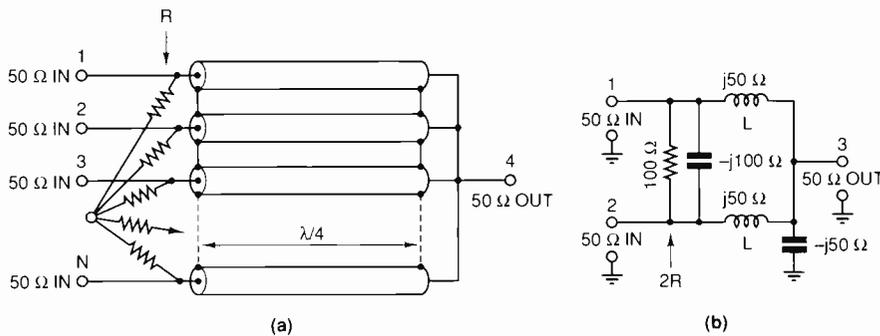


Fig. 6. Wilkinson combiner (a) and its lumped equivalent (b). In practice b) may not be feasible for more than two input ports.

niques described, it may be possible to develop quadrature hybrids for wider bandwidths than the 10-15% normally attributed to this type of coupler.

Ring hybrids

The hybrid ring, $(3/2)\lambda$ hybrid or "rat race" (Fig. 4) as it is commonly called is a directional coupler that can be used to sample rf power travelling in different directions. As a result, it is also adaptable for mixer, power splitter, and combiner applications.

Construction is usually with microstrip transmission lines, a technique that limits use to about 1000MHz and above. Coaxial cable designs can extend the frequency range down to 200-300MHz, but such structures become bulky.

A simple hybrid ring consists of a transmission line in which input, output and isolation ports are connected in four places. If the Z_{in} impedances of these ports are 50Ω , characteristic impedance of the transmission-line ring is:

$$Z_0 = \sqrt{(Z_{in}^2 N)}$$

where N is the number of active ports is 2, then,

$$Z_0 = \sqrt{(5 \times 10^3)} = 70.7\Omega$$

Each of the four ports is separated by quarter-wavelength sections making the remaining part of the ring three-quarter wavelengths – so the total circumference is 1.5 wavelengths.

The hybrid ring is commonly used as a power splitter or combiner. If a signal is applied to port 1 (Fig. 4a), power will be equally divided between ports 2 and 4 and their phase relationship will be 180° .

On the other hand, power incident at port 2 will also be equally divided between ports 1 and 3. But the two output signals will be of similar phase.

When port 2 is used as the input in a combiner, any power reflected at output port 3, due to a mismatch, arrives at the other output port 1 by two paths.

One signal travels a half-wavelength in a counter clockwise rotation from port 3, and the clockwise signal appears at port 1 delayed by a full wavelength. The half wave difference in arrival, and equal path loss results in cancellation of the two signals at port 4, with total cancellation resulting in highest port-to-port isolation. The reflected signal from any mismatch at port 3 arrives at port 4, in phase from both circular paths, where it is dissipated. This port is designated as the isolation port, where a termination absorbs any power due to the unbalance between output ports.

The input signal from port 2 cancels at port 4 because the two-way paths differ by a half wavelength. Advantages of a ring hybrid include simplicity of construction and a reasonable tolerance for variations in line impedance. In addition, the power at the output ports can be adjusted by varying the impedances of the interconnecting lines.

A simple hybrid ring can provide a good match and excellent isolation over a 8-10% bandwidth.

Ring hybrids can also be designed with lumped constant elements – extending low frequency response to audio frequencies.

Deriving a lumped-circuit equivalent is simple and entails replacing each length of transmission line by its pi equivalent (Fig. 4b). Three pi networks represent the $\lambda/4$ sections, namely C_3-L-C_1 , C_1-L-C_2 and C_2-L-C_3 . The lowest branch – $L-C_4-L$ – forms the $3/2 \lambda$ section.

Since all capacitors will be of equal value, C_1 and C_2 can be paralleled into a single unit, $2 \times C_1$ and $2 \times C_2$ respectively. All branches must have a Z_0 of $Z_{in}\sqrt{2}$ or 70.7Ω as the line sections in the microstrip design. All inductors in the circuit are also of equal value, calculated as:

$$L = \epsilon Z_{in}\sqrt{2}/2\pi f_0 \text{ and } C = 1/(2\pi f_0 Z_{in}\sqrt{2})$$

For example, designing a lumped constant ring combiner for a frequency of 100MHz. Then:

$$L = 70.7/628 = 0.11\mu\text{H and}$$

$$C = 1/(628 \times 70.7) = 22.5\text{pF.}$$

Capacitors C_1 s and C_2 s combined would then be 45pF each. The isolation and insertion loss characteristics are greatly dependent on component tolerances, loss factors (Q), and symmetry of the total structure. Typical numbers for 100MHz are 20-25dB and 0.4-0.45dB respectively.

Testing splitters and combiners

Multiple port configurations make the performance of splitters and combiners difficult to test. But a possible method is to terminate all outputs except one and make the measurements between the one unterminated output and the single input port. Each output port would be sequentially tested, revealing the amount of insertion loss, return loss, and the phase angle over the desired frequency spectrum.

To test isolation characteristics between the output ports, the input and all output ports but two should be terminated. Isolation can then be measured between all output ports by sequentially switching terminations and active ports.

One quick test would be to connect all the multiple output ports together (back-to-back), leaving two open ports compatible with a standard 50Ω system – though this would not provide information on port-to-port isolation characteristics of the output.

These test methods are applicable to most types of splitter or combiner. Testing can be carried out with a network analyser or an rf test station consisting of a signal source, load, and appropriate means for measuring forward and reflected power. The rf test station is probably the more accurate of the two methods, since the subject devices can be driven with a more realistic level of rf. In either case, the

amount of return loss, insertion loss and also, in the case of the network analyser, the phase relationship can be found

Phase error can be as much as 25° , but this would still create only a 0.22dB loss. Phase errors of around 10° – typical maximums – have negligible effect.

Influence of source amplitudes are also exaggerated. In a two port system, a 50% difference in source power outputs produces only an approximate 0.2dB loss in the combined output.

Figures may vary depending on the type of combiner, but we can conclude that, in practice, the effect of amplitude unbalance between the input ports of a combiner (especially with a failed source) is far more dominant than the phase relationship.

Branch line couplers

Branch line couplers are the easiest types to construct – most often as two-branch, 3dB units (Fig. 5a). The main transmission line is coupled to a branch line by two quarter-wave lines, each spaced a quarter-wave apart. Simple microstrip configurations can produce coupling values from 3 to 9dB. Used as a power combiner, the device acts as a quadrature coupler with output signals 90° out of phase.

Overall bandwidth of branch-line couplers is rather narrow compared to the hybrid rings. Bandwidth can be increased by adding more branches, though this is not popular because additional branches have higher impedances, and as well as increased losses, the microstrip tolerances become critical.

The use of transformer sections in the main lines results in characteristic impedances of the branch lines equal to those of the input and output arms. The impedance of these transformer sections (*a* in Fig. 5a), also called main lines, can be figured as:

$$Z_0 = \sqrt{(Z_{in} \times Z_{out}/2)}$$

For a 50Ω system:

$$Z_0 = \sqrt{(50 \times 50/2)} = 35.4\Omega.$$

Impedance of the branch lines (*b* in Fig. 5a) will be 50Ω too.

Both the hybrid ring and the branch line coupler are very versatile devices. With the ring coupler, impedance transformation is possible by varying the characteristic impedances of the λ/4 line sections.

Similarly the transformer or the main line impedance can be varied in a branch-line coupler, producing impedance transformation between the input and output ports. Though this function may only be necessary when devices are used for non-power-splitting combining applications such as mixers.

The branch-line coupler is physically smaller than the hybrid ring since its loop periphery measures only one full wavelength. But its practical low-frequency limit is in the low microwave region. Construction using coiled coaxial lines would bring the lowest practical frequency into the 150-200MHz region. Lower frequency versions can be realised with lumped element designs (Fig. 5b) where the principle is the same as with the hybrid ring: each λ/4 transmission line section is replaced by a πLC network. In the hybrid ring equivalent, there are three such networks. The branch-line equivalent requires four, two for 35.4Ω impedance and two for 50Ω. Using the formula to calculate component values for 100MHz, the 35.4Ω branches (*a*) will be:

$$L = 35.4/628 = 56nH$$

and:

$$C = 1/(628 \times 35.4) = 45pF.$$

Similarly the 50Ω branches (*b*) are *L* = 80nH and *C* = 32pF. The combined capacitances (*C*₁

+ *C*₂) will be 45 + 32pF = 78pF. Component tolerances are critical.

Wilkinson couplers

One other power combiner that uses quarter wave transmission lines is the Wilkinson hybrid, though it should not really be called a hybrid since that describes a device with two input or output ports.

The Wilkinson coupler is a reciprocal network and sums *N* coherent sources to a common port, all in one step. Any number of ports can be designed for (Fig. 6a) and so it is commonly called an *N*-way coupler.

In a similar way to other types of combiners, the device can be used for power splitting as well as combining. But unlike quadrature hybrids, all inputs are in equal phase relative to the output, but create a delay of 90°. Since the line length between any two ports is λ/2, the power arriving at each port is 180° out of phase with the power from any other port and so cancels, providing isolation between inputs.

The port-to-port isolation and vswr are theoretically perfect at mid-band (where the lines provide a 90° phase shift) and degrade at frequencies away from band centre. In practice the amount of isolation and the vswr are primarily dependent on the phase relationship (line impedance and length) of the transmission lines.

Typical numbers for the isolation are 20-25dB and for the vswr, 1.2:1. The balancing resistors (*R*) have an important role in that they serve to help isolate and match the input ports. Normally they would not dissipate power, but any unbalance between input ports would result in power dissipation by them.

With two-port combiners, if the power to one input port is completely lost due to a failure of an amplifier module, then half of the power output from the remaining module will be dissipated in the balancing resistor. This is the case with all two-port combiners described. (Refer to straight in-phase combiners and Fig. 1c where a system shut-off under the condition of an amplifier failure is described).

Perfect output-port amplitude-balance (due to its symmetry) is a benefit of the Wilkinson coupler, with equal phases at all of its input ports.

Chief advantage for high power applications stems from the series of combined balancing resistors. Perfect isolation requires completely non-inductive resistors, which must be heat-sunk.

Overall, the Wilkinson *N*-way combiner – constructed with coaxial, stripline, or microstrip transmission lines – offers a relatively low cost method of combining several signals with a fair amount of isolation and low vswr.

Bandwidth of operation is relatively narrow, compared with 90° hybrids. For bandwidths wider than 15-20%, multiple lines of appropriate lengths can be cascaded, with stepped characteristic impedances for an optimum design with Chebyshev response. But the method will add to line *IR* losses, and may

only be practical up to three-four sections. For *N* number of input ports, the line impedances are calculated as: $Z_0 = \sqrt{(Z_{in}^2/N)}$. So the *Z*₀ for a two-port system is 70.7Ω; for a three port system, 86.6Ω; for a four port system 100Ω, and so on. The balancing resistor values (which are equal) can be obtained as: $R = Z_0^2/NZ_{in}$.

Operation of a lumped equivalent of a two-port Wilkinson power combiner (Fig. 6b) is based on the same principle as the ring and branch-line coupler equivalents – that the λ/4 sections are simulated with π networks. The two 50Ω balancing resistors have been combined into a single 100Ω unit because the centre tap is “floating.”

Similarly, the *C*s between the input ports have been combined to a -j100Ω reactance, since it is not necessary for their centre tap to be grounded. The reactances shown can be converted to required values of capacitance and inductance for the centre of the operating frequency band.

The lumped constant version of the Wilkinson combiner works well, with comparable isolation and vswr characteristics to its transmission line counterpart. But component tolerances must be kept within 1-2%. ■

Radio Frequency Transistors
Principles and Practical Applications
Norm Dye and Helge Granberg

Norm Dye is Motorola's product planning manager in the Semiconductor Products Sector, and Helge Granberg is Member of Technical Staff, Radio Frequency Power Group (Semiconductor Products) at Motorola. Their *rf* transistors book includes practical examples from the frequency spectrum from 2MHz to microwaves, with special emphasis on the uhf frequencies.

RF Transistors: Principles and practical applications is available by postal application to room L333 EW+WW, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.

Cheques made payable to Reed Books Services. Credit card orders accepted by phone (081 652 3614).

288pp **HARDBACK** 07506 9059 3 Cost £19.95 + Postage £2.50


Finally an upgradeable PCB CAD system to suit any budget ...

Board Capture

BoardCapture - Schematic Capture

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

£395

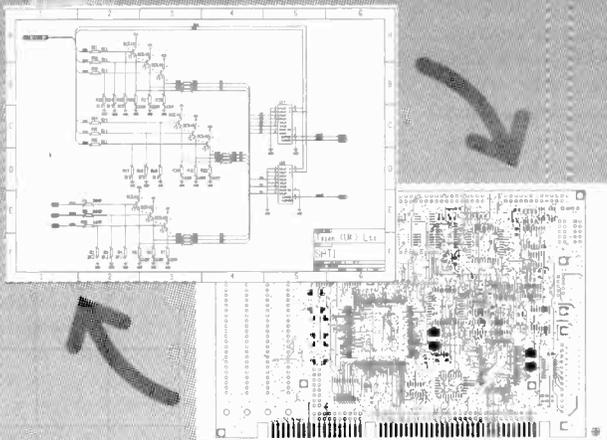

BoardMaker

BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

£95

BoardMaker2 - Advanced level

- All the features of BoardMaker1 plus
- Full netlist support - OrCad, Schema, Tango, CadStar
- Full Design Rule Checking - mechanical & electrical
- Top down modification from the schematic
- Component renamer with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC

£295

NEW

BoardRouter

BoardRouter - Gridless autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

£200

Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphics, Roland & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill / Annotated drill drawings (BM2)



Call for info or full evaluation kit
Tsien (UK) Limited
Tel (0354) 695959
Fax (0354) 695957



tsien

Tsien (UK) Ltd, Aylshay House, Wenny Road, Chalfont, Cambridge CB11 3UT

All trademarks acknowledged

CIRCLE NO. 124 ON REPLY CARD

FREE TO SUBSCRIBERS

Electronics World offers you the chance to advertise **ABSOLUTELY FREE OF CHARGE!**

Simply write your ad in the form below, using one word per box, up to a maximum of twenty words (remember to include your telephone number as one word). You must include your latest mailing label with your form, as this **free** offer applies to private subscribers only. Your ad will be placed in the first available issue.

This offer applies to private sales of electrical and electronic equipment only.

Trade advertisers should call **Malcolm Wells on 081-652 8355**

All adverts will be placed as soon as possible. However, we are unable to guarantee insertion dates. We regret that we are unable to enter into correspondence with readers using this service, we also reserve the right to reject adverts which do not fulfil the terms of this offer.

Please send your completed forms to:

Free Classified Offer: Electronics World, L333, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

Measurement of rf power at the milliwatt level

It is sometimes necessary to measure rf power at the milliwatt level. This usually requires the use of expensive equipment and the achieved accuracy depends on the standard of calibration. In this note, Nick Wheeler describes an inexpensive thermal device which can be calibrated with dc and has good overload capability.

The Analog Devices AD590 is a two-terminal current regulator with the property of passing a current which increases linearly at the rate of $1\mu\text{A}/^\circ\text{C}$, independent of supply voltage, over range of 4 to 30V.

The device is in a TO-52 case similar in size to a TO-18 miniature metal can. This case has a gold-plated base through which the two active leads pass, together with a third lead connected to the case.

The AD590 is specified for storage up to 155°C and for 10s lead soldering temperature at 300°C . Typical low melting-point solder melts at 179°C .

It proved easy, and apparently non-destructive, to solder two 100Ω chip resistors to the gold-plated base. The gold plating facilitates this. These form a relatively non-inductive 50Ω load when connected in parallel, which is fed by length of RG-402 semi-rigid microwave coaxial cable.

The outer conductor of the coax is soldered to the case pin of the AD590. The two leads of the AD590 need to be decoupled by chip capacitors as close in as possible, to prevent rf pickup.

At typical laboratory temperature, the device will draw about $295\mu\text{A}$; the specification is $298.2\mu\text{A}$ at 25°C . On test, a sample drew $291.2\mu\text{A}$ at an ambient level of 20°C . This corresponds to a nominal 18.7°C . As the maximum calibration error is $\pm 1^\circ\text{C}$ and the measurement was at the 1% accuracy level, this was satisfactory. On applying one volt to the

50Ω load, the current increased by $4\mu\text{A}$. A volt across 50Ω dissipates 20mW .


This simple form of the instrument measures small difference between two large quantities. This is bad practice.

By using two sensors in a differential circuit derived from the Analog Devices databook, and applying the signal to one of them, measurements may be made to the milliwatt level. The devices should be made as similar as possible and mounted in a draught-proof enclosure, thermally insulated from each other but otherwise identical in relation to the environment. I used foam polystyrene to achieve this.

On transferring the signal input from one sensor to the other, a large output of reversed polarity should result. It is most unlikely to be identical. Both devices should be calibrated with dc at inputs up to 200mW . The resulting calibration curves are non-linear, falling off at higher inputs. This is because the heat loss from a heated object is proportional to the square of its temperature above ambient.

This is not a quick-response system. About 90% of the final reading is reached in a minute. Also note that a series of readings should start with the lowest input. Otherwise time must be allowed for cooling off between measurements.

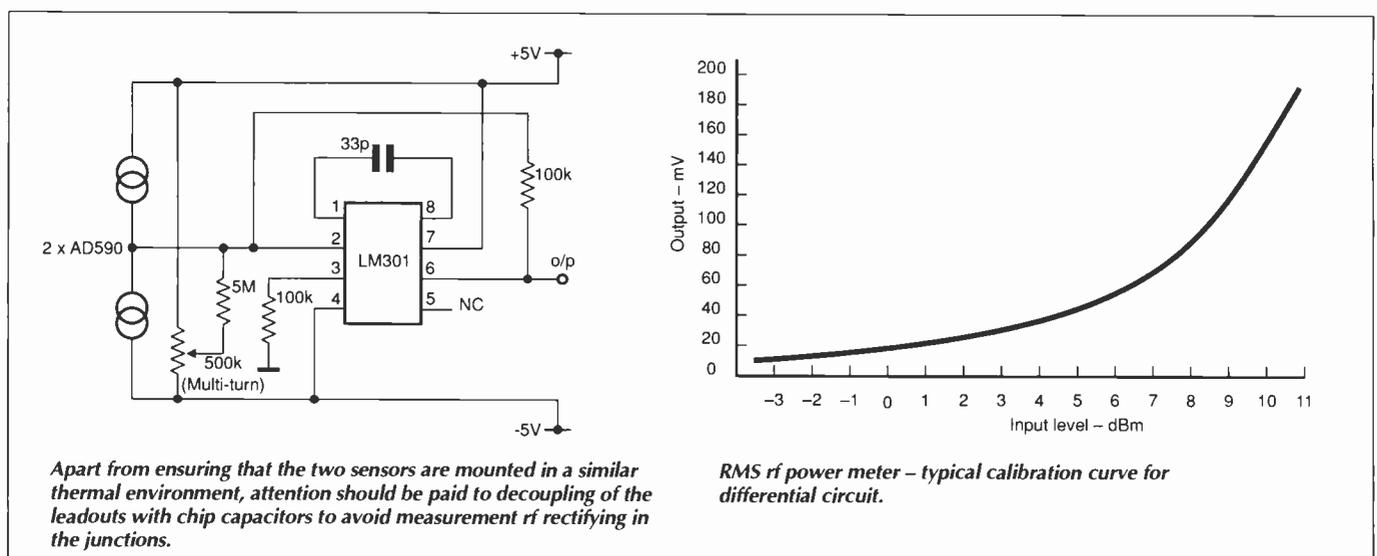Also note that when measuring rf, this is a true rms measurement. Measurements made at 50MHz using a good 100MHz oscilloscope to determine the applied voltage corresponded to the dc calibration within a few percent. ■



CLASSIFIED

TEL 081 652 3620

FAX 081 652 8956

ARTICLES WANTED

WE WANT TO BUY !!

IN VIEW OF THE EXREMELY RAPID CHANGE TAKING PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTITIES OF COMPONENTS BECOME REDUNDANT. WE ARE CASH PURCHASERS OF SUCH MATERIALS AND WOULD APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE. WE PAY TOP PRICES AND COLLECT.

**R.HENSON LTD.
21 Lodge Lane, N.Finchley,
London N12 8JG.
5 Mins, from Tally Ho Corner.
TELEPHONE
081-445-2713/0749
FAX 081-445-5702.**

ARTICLES FOR SALE



Cooke International SUPPLIER OF QUALITY USED TEST INSTRUMENTS

ANALYSERS, BRIDGES, CALIBRATORS,
VOLTMETERS, GENERATORS, OSCILLOSCOPES,
POWER METERS, ETC. **ALWAYS AVAILABLE**

ORIGINAL SERVICE MANUALS FOR SALE
COPIES ALSO AVAILABLE

EXPORT, TRADE AND U.K. ENQUIRIES WELCOME,
SEND LARGE "A3" S.A.E. + 50P POSTAGE FOR LISTS
OF EQUIPMENT AND MANUALS.

ALL PRICES EXCLUDE VAT AND CARRIAGE
DISCOUNT FOR BULK ORDERS SHIPPING ARRANGED

OPEN MONDAY-FRIDAY 9AM-5PM

Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham,
Bognor Regis, West Sussex, PO22 0EB

Tel: (+44) 0243 545111/2 Fax: (+44) 0243 542457

HIGH END TEST & COMMUNICATIONS
EQUIPMENT PURCHASED

CIRCLE NO. 133 ON REPLY CARD

ARTICLES FOR SALE

VALVES AND CRTs

ONE MILLION ITEMS IN STOCK INCLUDING MAGNETRONS,
KYLSTRONS, VALVE SOCKETS FOR AUDIO RECEIVING
TRANSMITTING, OBSOLETE BRANDS SUCH AS MULLARD, GEC A
SPECIALITY. ALSO HUGE STOCKS OF RUSSIAN AND SOVTEK ITEMS.
ASK FOR OUR 40-PAGE VALVE CATALOGUE OR CRT CATALOGUE.

VALVES WANTED FOR CASH

ESPECIALLY KT66, KT77, KT88, PX4, PX25, VALVE HI-FIs e.g. QUAD,
LEAK, GARRARD 301. IF POSSIBLE SEND WRITTEN LIST.

BILLINGTON EXPORT LTD

1E GILLMANS IND EST, BILLINGSHURST, SUSSEX RH14 9EZ
CALLERS STRICTLY BY APPOINTMENT ONLY
TEL: 0403 784961 FAX: 0403 783519
MINIMUM ORDER £50.00 PLUS VAT

TURN YOUR SURPLUS TRANSISTORS, ICS ETC, INTO CASH

Immediate settlement.
We also welcome the opportunity to
quote for complete factory clearance.
Contact:
COLES-HARDING & CO, Unit 58,
Queens Road, Wisbech, Cambs. PE13 2PQ
ESTABLISHED OVER 15 YEARS
Buyers of Surplus Inventory
Tel: 0945 584188 Fax: 0945 475216

TOP PRICES PAID

For all your valves, tubes,
semi conductors and IC's.

Langrex Supplies Ltd,
1, Langroy Road, Croydon,
Surrey, CRO 2QP
TEL: 081 684 1166
FAX 081 684 3056

ARTICLES WANTED

STEWART OF READING

110 WYKEHAM ROAD,
READING, RG6 1PL.
TEL. 0734 268041
FAX: 0734 351696

TOP PRICES PAID FOR ALL
TYPES OF SURPLUS TEST
EQUIPMENT, COMPUTER
EQUIPMENT,
COMPONENTS, etc.
ANY QUANTITYT

103

WANTED

Test equipment, receivers, valves,
transmitters, components, cable
and electronic scrap and quantity.
Prompt service and cash.

M & B RADIO
86 Bishopgate Street,
Leeds LS1 4BB
Tel: 0532 435649
Fax: 0532 426881

9956

WANTED

High-end Test, Communication &
Computer Equipment. Top prices paid.

Please send or fax your offer to:

Steigerwald GmbH
Neusserstrasse 9, 80807 Munich
South Germany
Tel: 01049 89 3615833
Fax: 01049 89 3615899

WANTED

Receivers, Transmitters, Test
Equipment, Components, Cable
and Electronic, Scrap, Boxes,
PCB's, Plugs and Sockets,
Computers, Edge Connectors.

TOP PRICES PAID FOR ALL TYPES OF
ELECTRONICS EQUIPMENT

A.R. Sinclair, Electronics, Stockholders,
2 Normans Lane, Rabley Heath, Welwyn,
Herts AL6 9TQ. Telephone: 0438 812 193.
Mobile: 0860 214302. Fax: 0438 812 387
Telephone: 0763 246939


780

**TO ADVERTISE HERE:
TEL: 081-652 3620**

ELECTRONIC UPDATE

Contact Malcolm Wells on
081-652 3620

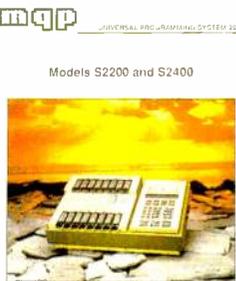A regular advertising feature enabling
readers to obtain more information
on companies' products or services.




mqp
UNIVERSAL PROGRAMMING SYSTEM 2000

Models S2200 and S2400

Gang and Set Programmers for
24, 28 & 32 pin EPROMs, EEPROMs,
FLASH, Emulators and OTPs up to 8M bit.

The system 2000 is an ideal programmer for the production environment. Fast programming results in high throughput and rigorous verification leads to improved quality control. Single key functions and checks against misoperation facilitates its use by unskilled staff.

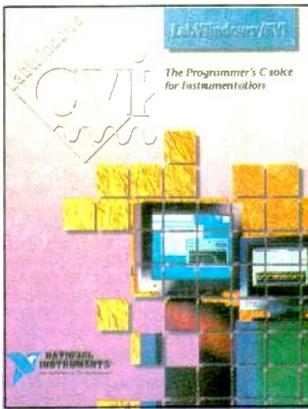MQP ELECTRONICS LTD.
Tel: 0666 825146
Fax: 0666 825141
CIRCLE NO. 142 ON REPLY CARD




LabWindows/CVI
Brochure

The Programmer's Cookbook
for Instrumentation

NATIONAL INSTRUMENTS

The LabWindows/CVI Brochure, from National Instruments, explains how users can build instrumentation applications on Windows PCs and Sun SPARCstations using the ANSI C programming language and LabWindows/CVI data acquisition, analysis, and presentation libraries.

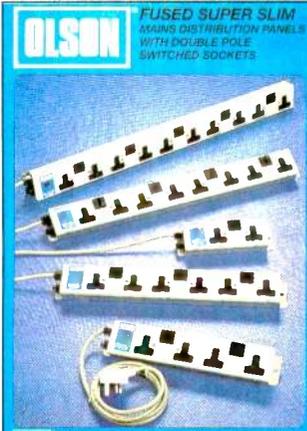NATIONAL INSTRUMENTS
For further information
FREEPHONE 0800 289877
CIRCLE NO. 146 ON REPLY CARD



OLSON FUSED SUPER SLIM
MAINS DISTRIBUTION PANELS
WITH DOUBLE POLE
SWITCHED SOCKETS


OLSON ELECTRONICS LIMITED

OLSON ELECTRONICS LIMITED is a leading manufacturer in the field of mains distribution panels of every shape and size to suit a variety of needs. For use in Broadcasting, Computing, Data Communications, Defence, Education, Finance, Health etc. All panels are manufactured to BS5733, BRITISH AMERICAN, FRENCH, GERMAN CEE22/IEC and many other sockets. Most countries catered for.

All panels are available ex-stock and can be bought direct from OLSON.

Olson Electronics Limited
Tel: 081 885 2884
Fax: 081 885 2496
CIRCLE NO. 143 ON REPLY CARD

SPICE A/D Simulation

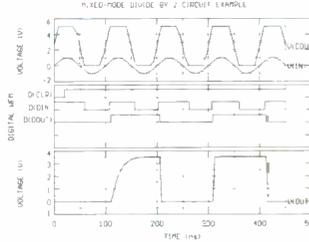

- Mixed Analogue and Digital
- All SPICE 2G6 analyses
- Behavioural Modelling
- Graphical post-processor
- FREE 10 transistor version
- 640K version £395
- 32 bit extd. mem. ver. £695
- Schematic front-end £149

To receive your FREE working evaluation version just send a 1.44MB HD 3.5in disk to: EW+WW Offer, CRaG Systems, 8 Shakespeare Rd, Thatcham, Newbury, Berks RG13 4DG, Tel (0635) 873670

CIRCLE NO. 147 ON REPLY CARD



ENGINEERING & SCIENTIFIC PC


Total Solution for PC-based Industrial and Lab Automation

ADANTECH

The new 230 page 1994 PC-LAB catalogue covers an extensive range of PC-based data acquisition, measurement, control, and interface plug-in cards plus supporting software packages for engineering & scientific applications. Also includes 19" rack mounting industrial PCS, custom OEM PC chassis and associated sub-systems.

Please contact integrated measurement systems for a free catalogue copy.

Tel: (0703) 771143
Fax: (0703) 704301

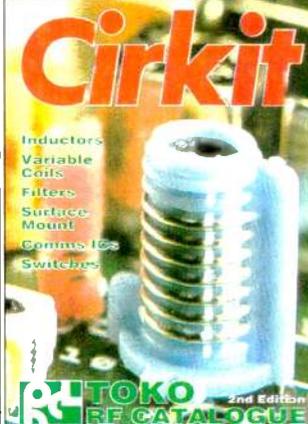

Cirkit

Inductors
Variable Coils
Filters
Surface Mount
Comms ICs
Switches


TOKO RF CATALOGUE 2nd Edition

2nd EDITION TOKO RF CATALOGUE

Cirkit have just published the 2nd Edition of the Toko RF Catalogue, featuring details of Tokos' extensive range of RF coils, inductors, filters and comms ICs.

The 128 page catalogue includes many new products such as:
Surface mount high current inductors, surface mount multilayer inductors, helical filters at 2.5GHz and a new section of push button and tact switches.

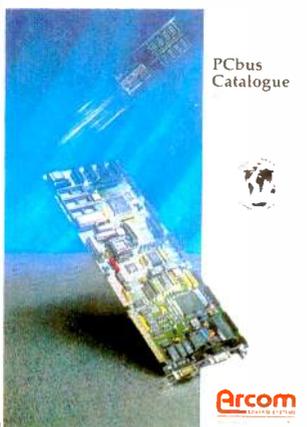Cirkit Distribution Ltd, Park Lane, Broxbourne, Herts, EN10 7NQ
Tel: (0992) 441306
Fax: (0992) 441306
CIRCLE NO. 148 ON REPLY CARD



PCbus Catalogue

Arcom

INDUSTRIAL PCs

Arcom's PChus range is expressly developed for embedded control and data acquisition, providing high integrity industrial solutions with:

- * full range of CPU and I/O functions
- * industrial EMC enclosures
- * mezzanine bus expansion
- * industry standard signal conditioning
- * Windows I/O drivers with predictable performance.

Arcom Control Systems makes plug-together PC solutions for industry a reality!

Please forward all enquiries to Alan Timmins at: Arcom Control Systems Ltd, Units 8-10 Clifton Road, Cambridge CB1 4WH, UK. Tel: + 44 (0)233 411200 Fax: 410457



£295.00 + vat

High Speed EPROM & FLASH Programming from your PC

- Programs EPROMs to 4 Mbits/32-pins
- Superfast 8, 16 & 32-bit programming
- Approved algorithms
- Menu driven software included
- Sophisticated editor functions
- Easy file management
- FREE demo disk available

Stag Programmers Limited
Marinfield Welwyn Garden City, Hertfordshire, AL7 1JT UK
Tel: (0707) 332148
Fax: (0707) 371503

CIRCLE NO. 149 ON REPLY CARD

High Speed EPROM & FLASH Programming from your PC

- Programs EPROMs to 4 Mbits/32-pins
- Superfast 8, 16 & 32-bit programming
- Approved algorithms
- Menu driven software included
- Sophisticated editor functions
- Easy file management
- FREE demo disk available

Stag Programmers Limited
Marinfield Welwyn Garden City, Hertfordshire, AL7 1JT UK
Tel: (0707) 332148
Fax: (0707) 371503

CIRCLE NO. 149 ON REPLY CARD

SPECTRUM ANALYSERS




- IFRA7550 1GHz portable analyser w tracking gen op £4500
- IFRA8000 2.46Hz version of above £5250
- HP3580A 5Hz-50kHz audio spectrum analyser £1500
- HP3582A dual-channel 25kHz analyser
- HP3585A 20Hz-40MHz GPIB analyser
- MARCONI TF2370 110MHz

ADVANTEST TR4133A 199kHz-200GHz Hi-spec spectrum analyser £8500

MARCONI INSTRUMENTS

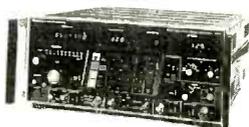- 2019 AM/FM synthesized signal generator 80kHz-1GHz £1750
- 2019A as above, improved spec £1950



- 2828A/2829 digital simulator/analyser £1000
- 2830 multiplex tester £1500
- 6059A signal source 12-18GHz £750
- 6460/6420 power meter 10MHz-12.4GHz 0.3uW-10mW
- 6460/6423 power meter 10MHz-12.4GHz 0.3mW-3W
- 6700B sweep oscillator 8-12.4GHz & 12.4-18GHz
- 6912 power sensor 30kHz-4.2GHz for above series
- 893B audio power meter
- QA2805A PCM regenerator test set
- TF2910/4 non-linear distortion (video) analyser
- TF2914A TV insertion signal analyser
- TF2910 TV interval timer

RALFE · ELECTRONICS

36 EASTCOTE LANE, S. HARROW, MIDDLESEX HA2 8DB
TEL: 081-422 3593. FAX: 081-423 4009

**NOW
IN
40th
YEAR**



DISTRIBUZIONE E ASSISTENZA, ITALY: TLC RADIO, ROMA (06)871 90254

TEST EQUIPMENT

- ANRITSU ME518A PCM portable error rate test set £2500
- BRUEL & KJAER 2511 vibration meter set/1621 filter £2250
- BRUEL & KJAER 2307 level recorder £1000
- BRUEL & KJAER 2317 portable level recorder £1850
- BRUEL & KJAER 1618 band pass filter £750
- BRUEL & KJAER 3513 portable vibration analyser £3500
- BRUEL & KJAER 2515 vibration analyser £5000
- AVO RM215L-2 insulation & breakdown tester £650
- DATRON 1065 digital multimeter £750
- DRANETZ 626 mains disturbance analyser/2 x PA-6001 £750
- DRANETZ 606-3 line disturbance analyser £275
- KEITHLEY 192 programmable dmm £400
- MAURY MICROWAVE 8650E TNC-calibration kit £1500
- NAGRA IV - SJ tape recorder £2000

TEKTRONIC CSA803A COMMUNICATIONS SIGNAL ANALYSER

- As new, supplied with IxSD22 head £22000 each
- TEKTRONIX 1503C/3/4/5 fdr cable tester £3,250

MUCH MORE, FULLY RE-FURBISHED, FULLY GUARANTEED TEST EQUIPMENT AVAILABLE FROM STOCK. PLEASE REQUEST OUR CURRENT LISTINGS. WE CAN FAX LISTS & SHIP GOODS WORLD-WIDE. HIGH-END EQUIPMENT ALWAYS WANTED FOR STOCK.

■ CALL US NOW ■

- RACAL 9008 automatic modulation meter £325. 9009 £300
- RACAL 9082 synthesized AM/FM sig'gen' 5-520MHz £800
- RACAL 9300 RMS voltmeter - 80dB to +50db £325
- RACAL 9341 LCR databridge component tester £350
- RACAL-DANA 9302 RF milli-voltmeter 1.5GHz £450
- RACAL-DANA 9303 level meter, digital £1000
- ROBERTS & ARMSTRONG lio-cable end-out measure unit £500
- TEKTRONIX J16 digital photometer £250
- TEKTRONIX 1503C/03/04/05/06 TDR cable tester £3250
- WAVETEX 2000 0-1400MHz sweep generator £750
- WAYNE KERR B905 automatic precision bridge £950

HEWLETT PACKARD



- 331A distortion meter £200
- 339A distortion meter £1500
- 3457A digital multimeter £1250
- 3335A synthesizer/level generator with option 01 £2500

- 3336A level generator £2000
- 3552A transmission test set £1250
- 3586A selective level meter £2500
- 415E swr meter £350
- 4274A multi-frequency (100Hz-100kHz) LCR component meter £4000
- 4275A multi-frequency LCR component meter £5000
- 432A/478A microwave power meter 10MHz-10GHz £400
- 432A/R486A uwave power meter 26.5-40GHz (waveguide) £600
- 5005B signature multi-meter, programmable £500
- 54501A digitising oscilloscope 100MHz 10MS/s £1500
- 6253A dual power supply 0-20V 0-3A twice £225
- 6825A bipolar power supply/amp -20 to +20vdc 0-1A £350
- 70300A tracking generator plug-in unit £2000
- 70907A external mixer for 70000-ser spectrum analyser £1750
- 7035B X-Y single pen analogue chart recorder £350
- 8011A pulse generator 0.1Hz-20MHz £500
- 816A slotted line 1.8-18GHz with carriage 809C & 447B £500
- 8350B sweep generator main-frame £2250
- 8405A vector voltmeter, voltage & phase to 1000MHz £950
- 8620C sweep generator, many plug-in units available £call
- 8671A synthesized signal generator 2-6.2GHz £2500

8753C with 85046A NETWORK ANALYSERS

with S-PARAMETER TEST SET as new, calibrated, £22500

PLEASE NOTE: ALL OUR EQUIPMENT IS NOW OPERATION-VERIFICATION TESTED BEFORE DESPATCH BY INDEPENDENT LABORATORY

We would be pleased to handle all grades of calibration or NAMAS certification by same laboratory at cost price. All items covered by our 90-day parts and labour guarantee and 7-day Right to Refuse (money back) warranty.

ALL PRICES SUBJECT TO ADDITIONAL VAT AND CARRIAGE

CIRCLE NO. 125 ON REPLY CARD

INDEX TO ADVERTISERS

	<i>PAGE</i>		<i>PAGE</i>
Anchor Surplus Ltd	621	MQP Electronics	618
BK Electronics	629	Number One Systems	629
Bull Electrical	636	Pico Technology	618
Dataman Designs	BC	Powerware	635
Display Electronics Ltd	683	Ralfe Electronics	704
Field Electric Ltd	629	Research Communications	625
Halcyon Electronics Ltd	625	Seetrax Ltd	669
John Morrison	635	Stewart of Reading	635
John's Radio	678	Surrey Electronics	650
JPG Electronics	625	Technology Sources Ltd	672
Kestral Electronics	618	Tektronix	IFC
Keytronics	646	Telnet	654
M & B Electrical	677	Tsien Ltd	699
M B Radio (Leeds)	663	Ultimate Technology	IBC


FROM CONCEPT TO ARTWORK IN 1 DAY




Your design ideas are quickly captured using the ULTIcap schematic design Tool. ULTIcap uses REAL-TIME checks to prevent logic errors. Schematic editing is painless; simply click your start and end points and ULTIcap automatically wires them for you. ULTIcap's auto snap to pin and auto junction features ensure your netlist is complete, thereby relieving you of tedious netlist checking.




ULTIshell, the integrated user interface, makes sure all your design information is transferred correctly from ULTIcap to ULTIboard. Good manual placement tools are vital to the progress of your design, therefore ULTIboard gives you a powerful suite of REAL-TIME functions such as, FORCE VECTORS, RATS NEST RECONNECT and DENSITY HISTOGRAMS. Pin and gate swapping allows you to further optimise your layout.

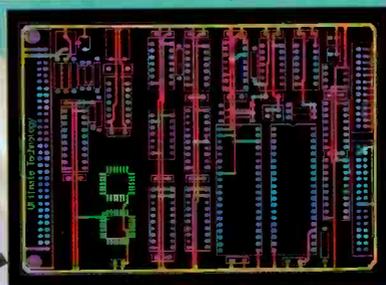

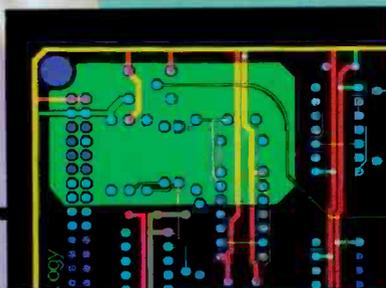
Now you can quickly route your critical tracks. ULTIboard's REAL-TIME DESIGN RULE CHECK will not allow you to make illegal connections or violate your design rules. ULTIboard's powerful TRACE SHOVE, and REROUTE-WHILE-MOVE algorithms guarantee that any manual track editing is flawless. Blind and buried vias and surface mount designs are fully supported.



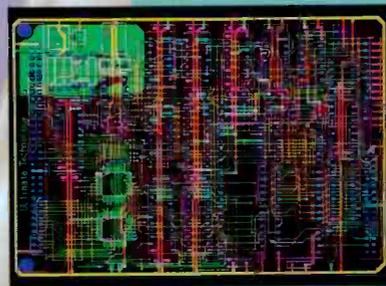If you need partial ground planes, then with the Dos extended board systems you can automatically create copper polygons simply by drawing the outline. The polygon is then filled with copper of the desired net, all correct pins are connected to the polygon with thermal relief connections and user defined gaps are respected around all other pads and tracks.



ULTIboard's autorouter allows you to control which parts of your board are autorouted, either selected nets, or a component, or a window of the board, or the whole board. ULTIboard's intelligent router uses copper sharing techniques to minimise route lengths. Automatic via minimisation reduces the number of vias to decrease production costs. The autorouter will handle up to 32 layers, as well as single sided routing.

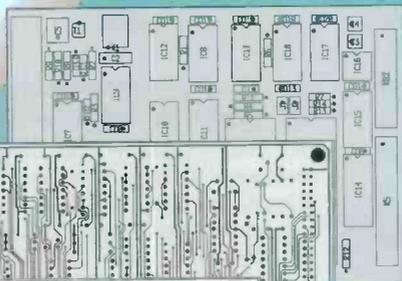

ULTIboard's backannotation automatically updates your ULTIcap schematic with any pin and gate swaps or component renumbering. Finally, your design is post processed to generate pen / photo plots, dot matrix/laser or postscript prints and custom drill files.

CIRCLE NO. 100 ON REPLY CARD

NEW


ULTIboard/ULTIcap evaluation system:

- all features of the bigger versions
- full set of manuals
- design capacity 350 pins

Price incl. S & H, excl. VAT:

£75

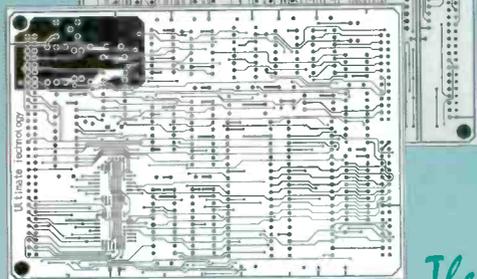Purchase price is 100% credited when upgrading to a bigger version. • Also suitable for study & hobby



ULTIboard PCB Design/ULTIcap Schematic Design Systems are available in low-cost DOS versions, fully compatible with and upgradable to the 16 and 32 bit DOS-extended and UNIX versions, featuring unlimited design capacity.

The European quality alternative

ULTICAP + ULTIBOARD = MAXIMUM PRODUCTIVITY

I want it. What does it do?

- ✓ **8-BIT EPROM**
- ✓ **16-BIT EPROM***
- ✓ **EEPROM**
- ✓ **SERIAL EEPROM***
- ✓ **FLASH**
- ✓ **PIC***
- ✓ **8751***
- ✓ **EMULATION**
- ✓ **FREE UPGRADES**
- ✓ **TOTALLY HANDHELD**
- ✓ **3 YEAR GUARANTEE**
- ✓ **AVAILABLE TODAY!**

**Requires optional modules.*

A 32 pin ZIF socket programs a huge library of EPROMs, EEPROMs and FLASH devices up to 8Mbit. And our unique user loadable Library means that new parts can be added quickly, and at no cost. All software upgrades are free and available for 24hr download from our high speed bulletin boards.

Emulation

See your code running before committing yourself to an EPROM. With S4's powerful and easy-to-use internal emulation system, download your code to S4, press 'EMULATE', and your target system runs in real time as if an EPROM was plugged in to the socket. Use S4's 'EDIT' command to make minor alterations to your code and see the changes happen *immediately* - just one reason why S4 is used by the world's car manufacturers to develop advanced engine management systems in real time! With S4 emulation there's no need for trailing cables or external power sources; earth loop problems are a thing of the past. S4 even emulates RAM.

Remote Control

As well as being totally stand alone and self contained, S4 can be operated remotely via it's serial port at speeds up to 115,200 Baud. We supply you with a FREE disk containing custom terminal software and a pop-up TSR communications utility.

The Company

Dataman has been designing and selling innovative programmers world-wide for over 15

years. As well as having sales and support offices in both the UK and the USA, we supply the world demand for our products via a network of approved dealers stretching from Norway to Australia.

The Package

S4 comes complete with mains charger, emulation leads, comprehensive manual, PC software and a spare library ROM; there are no hidden extras to buy. Upgrading S4's device library is free, does not involve costly internal ROM upgrades and technical support is free for life. Only S4 comes with a three year guarantee.

Availability

S4 is always in stock and we ship worldwide on a daily basis. Call now for delivery TOMORROW. Bona-fide UK customers can try S4 for thirty days without risk. 16,000 users can't be wrong!



Only **£495**
plus VAT
4 Mbit upgrade £39
plus VAT
Full 30 day money
back guarantee!

Size:
186 x 111 x 46mm
Weight: 315g

DATAMAN
Dataman Programmers Ltd

Credit card hotline:
0300 320719
for same-day dispatch

