

**EW+WW exclusive - 30% off virtual instruments**

# ELECTRONICS WORLD

Denmark DKr. 65.00  
Germany DM 15.00  
Greece Dra.950  
Holland Dfl. 14  
Italy L. 8000  
IR £3.30  
Singapore S\$12.60  
Spain Pts. 750  
USA \$4.94

A REED BUSINESS PUBLICATION  
SOR DISTRIBUTION

## + WIRELESS WORLD

September 1995 £2.10

**Analogue design  
for a single-rail**

**New audio  
power  
solution**

**MicroCap 5  
reviewed**

**Nulling coil  
interaction**

**Analogue  
filters**

**Alternative  
balanced  
amplifier**

**Analysing  
fm noise**



**20% discount - audio analyser UK launch**



9 770959 833011

# MICROMASTER LV PROGRAMMER



**APPROVED**

by major manufacturers including

**AMD  
MICROCHIP  
ATMEL**

from only

**£495**

THE ONLY PROGRAMMERS  
WITH TRUE 3 VOLT SUPPORT

## The Only True 3V and 5V Universal Programmers

ICE Technology's universal programming solutions are designed with the future in mind. In addition to their comprehensive, ever widening device support, they are the only programmers ready to **correctly** programme and verify 3 volt devices NOW. Operating from battery or mains power, they are flexible enough for any programming needs.

The Speedmaster LV and Micromaster LV have been rigorously tested and **approved** by some of the most well known names in semiconductor manufacturing today, something that very few programmers can claim, especially at this price level!

Not only that, we give free software upgrades so you can dial up our bulletin board any time for the very latest in device support.

Speedmaster LV and Micromaster LV - they're everything you'll need for programming, chip testing and ROM emulation, now and in the future.

### Speedmaster LV £495

Programmes 3 and 5V devices including memory, programmable logic and 8748/51 series micros. Complete with parallel port cable, software, re-charger and documentation.

### 8 bit Emulator card £125

Expansion card for Speedmaster LV/ Micromaster LV containing 8 bit wide ROM/ RAM emulator. Emulates 3V and 5V devices. Includes cable and software. Configuration: 128K x 8 expandable to 512K by 8.

### Micromaster LV £625

As above plus support for over 130 different Microcontrollers, without adaptors, including PICs, 89C51, 68HC705/711, ST6, Z8 etc.

### 16 bit Emulator card £195

As above but containing 16 bit ROM/RAM emulator. Configuration: 128K by 16, 256K by 8, 2 by 128K 8, expandable to 512K by 16/1024K by 8.

## FEATURES

- Widest ever device support including EPROMs, EEPROMs, Flash, Serial PROMs, BROMs, PALs, MACH, MAX, MAPL, PEELs, EPLDs, Microcontrollers etc.
- Correct programming and verification of 3 volt devices.
- Approved by major manufacturers.
- High speed: programmes and verifies National 27C512 in under 11 seconds.
- Full range of adaptors available for up to 84 pins.
- Connects directly to parallel port - no PC cards needed.
- Built in chiptester for 7400, 4000, DRAM, SRAM.
- Lightweight and mains or battery operation.
- FREE software device support upgrades via bulletin board.
- Next day delivery.

For a copy of our catalogue giving full details of programmers, emulators, erasers, adaptors and logic analysers call, fax or dial the BBS numbers below.



ICE Technology Ltd. Penistone Court, Station Buildings,  
Penistone, South Yorkshire, UK S30 6HG  
Tel: +44 (0)1226 767404 Fax: +44 (0)1226 370434  
BBS: +44 (0)1226 761181 (14400, 8N1)

CIRCLE NO. 101 ON REPLY CARD



## CONTENTS

### 728 DESIGNING WITH A SINGLE RAIL

Design expert Walt Jung presents analogue solutions for systems where only a single, low-voltage supply is available.

### 736 ADD SENSES TO YOUR PC

By plugging a small module into your LPT port, you can log data, count frequency or even analyse spectra.

### 746 A NEW SLANT ON AN OLD ANGLE

Irving Gottlieb looks at an early solution to the problem of adjacent coil interaction.

### 749 A NEW BALANCED VIEW

Steve Winder discusses a new approach to twisted-pair coupling.

### 751 SQUARE LAW RULES IN AUDIO POWER

The 'difference of two squares' concept offers significant linearity benefits when applied to audio power, as Ian Hegglin explains.

### 758 RECORDING ON DEMAND

An electronic aid for reducing the tedium of note taking, designed by François Steenkeste

### 762 FEW COMPLIMENTS FOR NON-COMPLEMENTS

Douglas Self has been analysing Bengt Olsson's work on non-complementary power amplifiers.

### 767 MIXED MODE MODELLING

The latest release of MicroCap features mixed-mode circuit modelling. But it is now also confined to Windows. Ben Duncan asks "is this a feature or a drawback?"

### 783 PREDICTING FM NOISE EFFECTS

Everyone knows that noise affects integrity in fm data communications – but by how much?

### 787 ASP AND FILTERING

In the Design Brief series, Ian Hickman looks at the benefits of using analogue signal processing in filter applications.

## REGULARS

### 715 COMMENT

The industry we never had.

### 716 NEWS

Road toll trials, pcb shortage, new gas sensor, surround sound from two speakers.

### 721 RESEARCH NOTES

Flying robot success, magnetic train breakthrough, live on the net, remote surgery.

### 740 APPLICATIONS

Video-speed a-to-d conversion with no s&h, RS232 with 1 $\mu$ A standby, power mosfet driving.

### 770 LETTERS

Arguments for terrestrial digital tv, EMI on planes, dynamos and audio design debate.

### 792 CIRCUIT IDEAS


Remote resistance measurement  
30W power amplifier, Milliohm meter, HF vco, Isolated thermometer amplifier, Median filter, Q-meter oscillator, Am detector with gain, Better squarewaves, Temperature monitor.

### 799 NEW PRODUCTS


Pick of the month – classified for convenience.



Cover – Hashim Akib

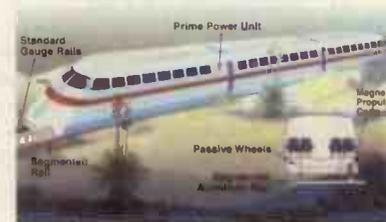

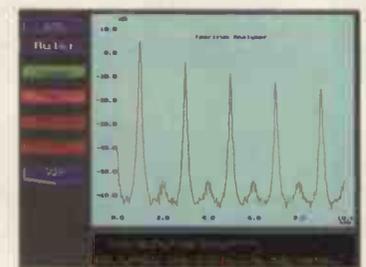Development of a high-speed, magnetically powered train that does not levitate, is inexpensive, and can run on already-laid track – page 721.



### Special reader discount of 30%

Plug a Pico module into the LPT port and turn your pc into a spectrum analyser, 'scope, f-meter, dvm or data logger. EW+WW is offering two such modules. See page 736.

An electro-acoustic measurement system for £750 – representing a 20% discount exclusively for EW+WW readers. Turn to page 780.



Eight motorway tolling systems are about to be tested, starting next summer on a stretch of the M3, page 716.

**Next month:** Probe for measuring mosfet switching losses, Triple stepper motor controller, Very fast power amplifier for instrumentation, Hybrid valve amp, Analysis circuits from energy use.  
**Free – Circuit Ideas Pocket Book Part III**  
**OCTOBER ISSUE – ON SALE 28 SEPTEMBER**

**"moving from schematic to layout  
could not be easier"**

Electronics World & Wireless World Jan 1995

**PRO+ now  
with SPICE  
file export  
& SpiceAge  
DDE Link!**

## quickroute 3.0

Integrated Schematic and PCB  
Design for Windows 3.1

**DESIGNER £99**


\*Schematic & PCB Drawing \*1/2 layer auto-router \*Supports Windows printers/plotters \*Full set of libraries \*Clipboard support \*Designer Special (manual on disk) also available.

**PRO £199**


\*Schematic & PCB Design \*Schematic Capture \*Integrated Rats-Nest Generation \*1-8 layer Auto-router (faster than Designer) \*Net-List Export \*Supports Windows printers/plotters \*CAD-CAM outputs.

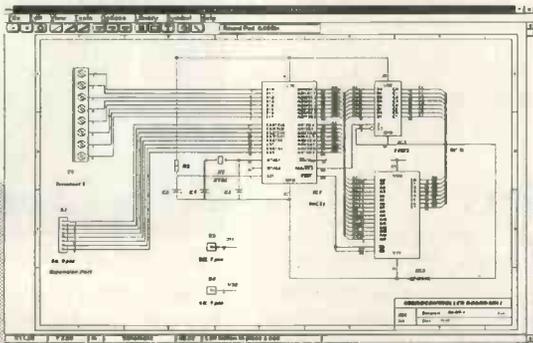**PRO+ £299**

As the PRO but also includes \*Advanced Schematic Capture (Busses, Power rails, etc) \*Larger Schematic & PCB Designs \*Gerber file IMPORT for File Exchange \*Extended libraries (CMOS, SMT, etc) \*SPICE Export \*SpiceAge DDE Link



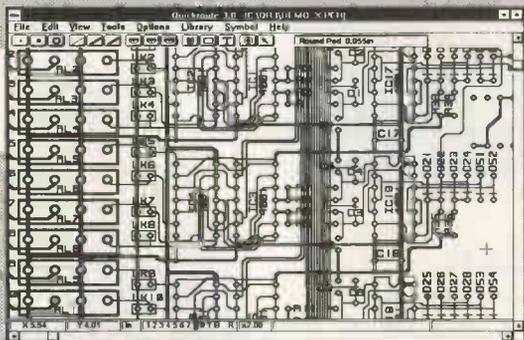Busses & power rails handled using Global Nets on PRO+



Integrated Schematic & PCB Design.

Quickroute Systems Ltd., 14 Ley Lane, Marple Bridge,  
Stockport, SK6 5DD, U.K.

**Tel/Fax 0161 449 7101**

\*Prices exclude P+P and V.A.T. \*VISA/MasterCard  
Accepted \*Network versions available.

**FREE  
Demo  
Pack  
Available.**

CIRCLE NO. 104 ON REPLY CARD

# KENWOOD

**TEST & MEASURING INSTRUMENTS  
A SUPERB RANGE OF OVER 100  
QUALITY INSTRUMENTS.**

Available from  
**B.K. ELECTRONICS**



FM-AM Signal Generators \* Colour Pattern  
Generators \* Video Signal Analyser \* Video  
Timing Analyser \* Video Noise Meter  
\* Distortion Meter \* Waveform Monitors  
\* Vectorscopes \* Audio Generators \* Wow and Flutter  
Meters \* Electronic Voltmeters  
\* Digital Multimeters \* Function Generators  
\* Frequency Counters \* Bus Analyser  
\* Resistance Attenuator \* Oscilloscopes \* Fully  
Programmable Digital Storage Oscilloscopes  
\* Regulated D.C. Power Supplies

A free, 50 page colour brochure, including price  
list, is available on request. Please make your  
request on company headed notepaper, by post  
or by fax, to:

**B.K. ELECTRONICS**  
Unit 1 Comet Way,  
SOUTHEND-ON-SEA,  
Essex, SS2 6TR.  
Tel: 01702-627572  
Fax: 01702-420243



## Orbit 48 Mobile Programmer

Everything you need in one... No gimmicks...  
No adaptors... No after thoughts! The latest in  
design and technology from a company  
that understands and cares

- Designed to program EPROMs, EEPROMs, FLASH, Serial EEPROMs, and Micro-controllers as standard (without fragile adaptor add-ons)
  - Optional PLD docking module
  - The latest in emulation techniques that others try to copy (including 8 & 16 bit devices)
  - 16 Mbits RAM with expansion to 64 Mbits
  - 8 16 and 32 bit formats
  - Real Windows & DOS environments
- STAG PROGRAMMERS**  
Europe's largest programmer manufacturer

call today on +44 (0)1707 332148  
or fax +44 (0)1707 371503 for further information

All trade marks are acknowledged and respected

CIRCLE NO. 105 ON REPLY CARD

**EDITOR**

Martin Eccles  
0181 652 3128

**EDITORIAL ASSISTANT**

Rob Allcock  
0181 652 8638

**CONSULTANTS**

Jonathan Campbell  
Philip Darrington  
Frank Ogden

**DESIGN & PRODUCTION**

Alan Kerr

**EDITORIAL ADMINISTRATION**

Jackie Lowe  
0181-652 3614

**E-MAIL ORDERS**

jackie.lowe@rbp.co.uk

**ADVERTISEMENT MANAGER**

Richard Napier  
0181-652 3620

**DISPLAY SALES EXECUTIVE**

Malcolm Wells  
0181-652 3620

**ADVERTISING PRODUCTION**

Christina Budd  
0181-652 8355

**PUBLISHER**

Mick Elliott

**EDITORIAL FAX**

0181-652 8956

**CLASSIFIED FAX**

0181-652 8956

**SUBSCRIPTION HOTLINE**

01622 721666  
Quote ref INJ

**SUBSCRIPTION QUERIES**

01444 445566

**NEWSTRADE DISTRIBUTION**

David G. Sanders  
0181 652 8171

**BACK ISSUES**

Available at £2.50

ISSN 0959-8332



## The industry we never had

During the industrial revolution members of the aristocracy wishing to spend an inheritance building a steam powered car or a flying machine could always find an artisan to assist them. Around this relationship, Britain's industries prospered and a number of Lord & Blacksmith Ltds became world leaders.

In the early nineteen eighties it seemed history might repeat itself. University professors scoured the countryside looking for someone to turn their designs – half of which were never committed to paper – into working instruments.

We were on our way – a few winners; personal computers, digital effects consoles – the new industrial age.

But earlier this year one of the last major subcontractors – Race – limped off the pitch.

What went wrong? It wasn't, as some suggest, that we let the industry slide Eastwards. More the case there was no real industry in the first place.

Praise open the casing of modern consumer electronics products. For all their functionality, you'll usually find a chip count of one at the most. Why aren't British engineers assembling these products? Because no-one is assembling them. There's someone standing next to the machine which makes them, but the skill needed for this is minimal. In the production of a single chip device the most complicated operation is getting Parcel Force to deliver the components.

Who are the losers? For one, any electronic assembly company which was going for growth in the late eighties. Then there's the component supplier who expanded out of a shop between the shoe repairer and the gent's hairdressers to end its life as a 'For Sale' sign stuck on a warehouse next to a motorway intersection. And of course there's the financier who gave a whole new meaning to the term solder sucker.

The part of the industry which remains is the low-volume, high-quality sector. The bulk of the low value work travels around the world like a Mexican Wave. It seemed it



would settle next to the chip manufactures in Japan or Taiwan but its on the move again. China, Africa who knows where labour will be cheap next year. The functionality of the chip will increase, perhaps to the level of serial input and output, with a massive number of uncommitted gates in between. The minimal skill needed to glue this to power rails on a pcb can be found anywhere – to do it in Britain is a waste of a resource.

Although Britain did hang on too long, today's view of the world is more realistic. It's no longer just the university Professor who wants a circuit built, but Siemens who need chips designed. If all the action is in the chip itself then is this such a bad thing? It takes the skill of an artisan to prototype a pcb and, as the rest of the world is telling us, these skills are also needed to develop integrated circuits.

Peter Kruger,  
flames@flames.cityscape.co.uk

*Electronics World + Wireless World* is published monthly. By post, current issue £2.25, back issues (if available) £2.50. Orders, payments and general correspondence to L333, Electronics World + Wireless World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Tlx:892984 REED BP G. Cheques should be made payable to Reed Business Publishing Group.

Newstrade: Distributed by Marketforce (UK) Ltd, 247 Tottenham Court Road London W1P 0AU 0171 261-5108. Subscriptions: Quadrant Subscription Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address. Subscription rates 1 year (normal rate) £30 UK and £43 outside UK.

USA: \$52.00 airmail. Reed Business Publishing (USA), Subscriptions office, 205 E. 42nd Street, NY 10117.

Overseas advertising agents: France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 205 E. 42nd Street, NY 10117. Telephone (212) 867-2080. Tlx 23827.

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. 2nd class postage paid at Rahway NJ Postmaster. Send address changes to above.

Printed by BPCC Magazines (Carlisle) Ltd, Newtown Trading Estate, Carlisle, Cumbria, CA2 7NR  
Typeset by Wace Publication Imaging 2-4 Powerscroft Road, Sidcup, Kent DA14 5DT

©Reed Business Publishing Ltd 1995 ISSN 0959 8332

## Decision on road toll trials

The Government has finally made a decision to go ahead with trialling the electronic toll collection systems with eight of the original 29 bidding consortia.

The chosen consortia are ANT Bosch, Autolink UK, EuroPassage, GEC-Marconi, Tollstar and Tollway proposing microwave-based systems; EasyToll with a system based on global positioning satellite navigation; and Siemens Traffic Controls developing an infra-red two-way communication system.

The consortia will initially carry out trials next summer at the Transport Research Laboratory in Berkshire, followed by tests on a section of the M3 near Basingstoke.

If any of the systems prove successful they may be installed on UK motorways in the next century.



Although the basic in-vehicle unit may cost around £50, more expensive units will be available which will

provide information such as route guidance, weather and congestion details.

*Eight motorway tolling systems are about to be tested, starting next summer on a stretch of the M3.*

## Computers look back

A team at Tokyo University has built a prototype computer-based system for analysing facial expressions to determine human feelings like joy, anger and sorrow.

The position of 21 reference points, like nose tip and eyebrow top, are located on the analysed image of the face. These are used to fit the image onto a digital wire-frame face model to 'normalise' the face.

Once done the relative movement of 48 points, some coincident with the

original 21, is analysed.

The analytical software is sophisticated enough to tell the difference between people with un-expressive and over-expressive demeanours and apply a second level of normalisation to account for this.

The current system can identify several basic feelings including happiness, anger, sorrow, surprise and fear. Even the tiny movements in seemingly unexpressive faces are discernable.

A second part of the experiment reconstructs and displays the original facial structure from the emotion information and both sets of normalisation parameters.

Away from conceivable 'big brother' applications, the research could provide the basis of extreme data compression for videophones or allow future computers to communicate with people in a manner closer to normal human interaction.

*Researchers have developed a computer system for recognising facial expressions. Even tiny movements in seemingly unexpressive faces are recognisable.*



## Circuit board shortage affects UK users

A world shortage of printed-circuit board laminate is putting US firms out of business and is threatening UK producers already struggling with severe allocations.

Circuit board makers are being told that a system of rationing is being considered by the laminators because of the shortage of woven glass yarn.

David Heywood, technical manager with the German laminate company ISOLA Werke, advises board makers to "plan their usage and keep their laminate suppliers informed".

Heywood added: "The problem is

world scarcity of the spun glass yarn from which FR4 laminate board is made. European manufacturers of yarn have not been investing in looms that make it.

The situation is exacerbated by the decline in the pound against other major European currencies.

Brian Haken, director of the UK pcb trade association, PCIF, said: "pcb makers face a difficulty in passing on laminate price rises to OEMs, and OEMs for their part, expect year-on-year unit cost reductions."

## New technique reduces rf chip count

US firm TRW has developed a chip fabrication process that could reduce the number of rf chips in mobile phones and other wireless equipment.

The technology allows, for the first time, the fabrication of both high electron mobility transistors – hemts – and heterojunction bipolar transistors – hbts – on the same substrate.

The technology is currently being employed in a satellite programme, but could be offered to other equipment makers. Dwight Streit, a spokesman for TRW, said: "There has been no decision yet to sell combined technology chips to other OEMs but it would give us a tremendous

advantage when bidding for new business."

Hemts are the output devices in many rf power amplifiers, but are too noisy for receiver input stages where hbts are favoured. Hbts are, in turn, not linear enough for optimised output stages.

But putting both hemts and hbts on the same chip means the hbts, which are relatively fragile, are normally damaged by the thermal cycling required to fabricate hemts.

TRW's solution has been in two parts; first it has progressively developed more robust hbt materials and second, it has designed a process that protects the hbts while hemts are grown.

The resultant devices have the same characteristics as separately grown transistors.

A spin-off is that the control circuits required by hemts can be made with on-chip hbts rather than off-chip silicon.

In the process, the hbt layers are epitaxially grown and then selectively etched to form the hbt transistors. A silicon nitride protective film is then laid down.

The hemt layers are then grown. Selective etching then removes the unwanted hemt material. So far, the process has proved successful with GaAs and InP substrates.

Steve Bush, *Electronics Weekly*

*Field-emission displays offer many of the benefits of cathode ray tube displays but are thinner, lighter and use less power.*

## Motorola joins display technology alliance

Motorola is to develop flat panel displays based on field emission technology – FED – and has joined the PixTech alliance of companies developing screens based on the technology.

Motorola and the other members of PixTech, which includes Texas Instruments, Raytheon and Futaba, are betting that the FED based screens will result in cheaper and better quality colour flat panel displays.


"We're working on the technology for next generation displays," said Pete Shinyeda, Motorola vice president and general manager of Motorola's Flat Panel Display Division. "This technology will make it possible to manufacture displays

that are bigger yet lighter and thinner, brighter yet more efficient, and are capable of full motion and colour."

Shinyeda predicts that FED based displays will find a wide range of applications in portable computers, cellular phones and video games systems.

FED displays offer many of the same benefits of cathode ray tube displays but are thinner, lighter and use less power.

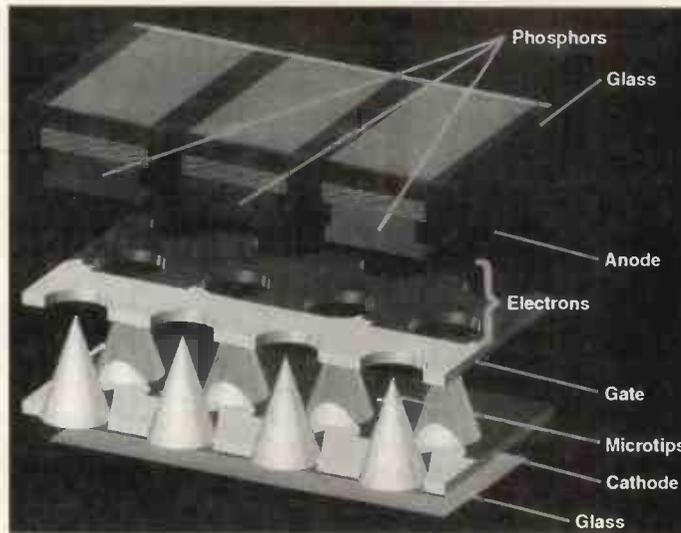Instead of a single cathode ray source, FED relies on hundreds of cathode ray sources for each pixel. Such displays should be easier to manufacture than active matrix liquid crystal displays which suffer from relatively poor production yields because of their complexity.



## Three US companies battle for unified memory first

Three US firms are working towards being the first to market with pc core logic chipsets which support the proposed unified memory architecture, reducing the amount of dynamic ram required in pcs.

Next month pc chipset specialist OPTi will announce a two-chip design which the company claims will remove the need for 32Mbyte of frame buffer d-ram in Pentium pcs resulting in a \$60 cost saving.

By the end of the year, graphics specialist Weitek will be sampling its first single chip memory controller and graphics accelerators, W464 and W564, which will support unified memory designs in 486 and Pentium-class PCs.

VLSI Technology, one of the leading

Pentium chipset suppliers, is expected to introduce its single chip unified memory design, called Coyote, at the turn of the year.

The use of the one block of d-ram for cpu main memory and graphics frame buffer has been made possible by the availability of new forms of high speed synchronous d-ram. As well as saving on a quarter of the memory in a pc with 8Mbyte of ram, chip suppliers are convinced the new designs have implications on the future development of the pc architecture.

OPTi's two-chip design which is being evaluated by the VESA standards body, is seen as a lower cost implementation which will be incorporated into pcs next year.

OPTi is working with market leading

graphics accelerator suppliers S3, Trident and Cirrus logic, to ensure compatibility.

"The approach has the potential to be a *defacto* standard because of the collaborative effort with the graphics vendors," said Prem Talreja, director of marketing for core logic at OPTi, but he admitted there could be a ten percent performance penalty largely due to bus arbitration.

According to Chas Rimpo, at VLSI Technology, the Coyote one chip design, will create no penalty and could enhance performance by running graphics on the 66MHz system bus.

Richard Wilson, *Electronics Weekly*

# One-chip fuzzy controller is low-cost

A reconfigurable microcontroller that executes fuzzy logic control in hardware has been developed by Silicon Valley-based Adaptive Logic. The device, the AL220, is a low cost single chip fuzzy logic processor targeted at the large eight-bit microcontroller market.


In addition to a processing core, the device features on-chip a-to-d and d-to-a converters.

The core performs fuzzy-based control on up to four analogue inputs. It first fuzzifies the input data, processes it based on the chosen rule set – the rules which capture the actions to be performed for given input conditions – before defuzzifying the data to generate output values.

The accompanying Windows-based development tool, called *Insight IIe*,

enables a designer to capture and simulate the fuzzy design. An emulator is also provided, allowing the control algorithm to be linked to the application and be executed in real time. On design completion, the fuzzy rules are programmed into the AL220's on-chip 256x8 eeprom, much in the way a logic array device is programmed.

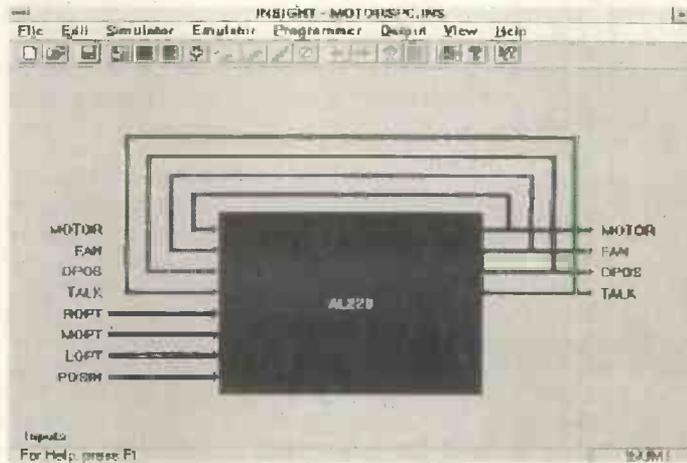The store can hold about 50 rules, with a processing performance of 500,000 rules per second. According to: Adaptive Logic's president, George Schmeer, implementing the algorithm in hardware avoids having to write and debug software using a standard microcontroller. "This reduces development cost and time to market," said Schmeer.



In addition to a fuzzy processing core, the new controller has on-chip a-to-d and d-to-a conversion.

# New surround sound system


JVC has developed a virtual surround sound system called 'Dolby Pro-Logic 3D-Phonic' that creates a surround effect from a Dolby Stereo source using just two front speakers.

The Dolby Pro-Logic Surround decoder and 3D-Phonic processor have been programmed into a single lsi chip. And the first product to use it is a 29in tv retailing at £900 – with other home audio-visual products to follow.

The centre-channel signal is added in equal amounts to the left and right front channels to maintain its central sound image. Because the surround channel signal is mono it requires processing before being added to the left and right channels. Otherwise, it too would seem to come from the centre. This is prevented by reducing the correlation between the signal going to the left channel and that to

the right, together with a degree of phase shifting and retiming between them. The result is the apparent localisation of the surround channel in symmetrical positions on either side of the listener.

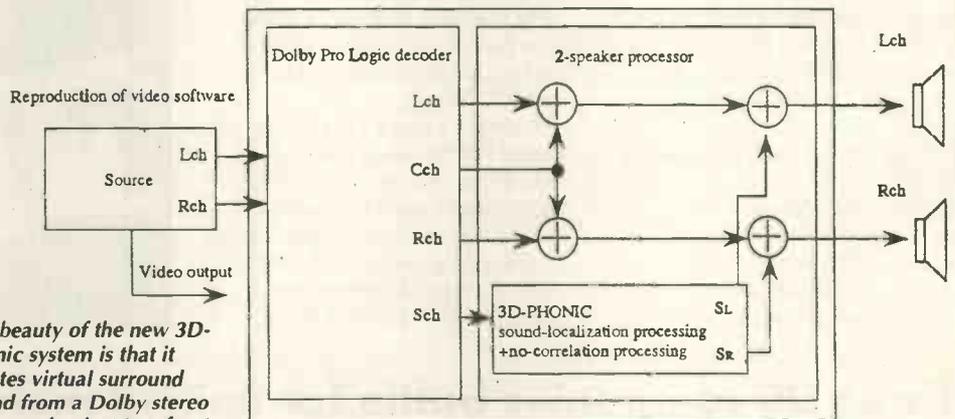Normal stereo and mono are reproduced without processing. While direct audio line outputs from the Pro Logic decoder are included for those who prefer separate front, centre and rear speakers.



The beauty of the new 3D-Phonic system is that it creates virtual surround sound from a Dolby stereo source using just two front speakers.

# Gas sensor breakthrough achieves ten times more sensitivity

Tokyo based Nippon Telegraph and Telephone, NTT, claims to have developed an electronic smell sensor that can detect gas concentrations of a few hundred parts per billion – ten times the sensitivity of conventional sensors.

The sensor consists of an array of eight quartz crystals, each coated with a different organic gas absorption film.

The resonant frequency of each crystal is affected by gas absorption

and is monitored over time. The array is sensitive to a variety of smells and a pc performs pattern recognition to differentiate between

burning smells and others.

The sensing technique can be extended to detect virtually any gas or odour.

# Semiconductor orders up 38%

The computer sector was the main factor in creating demand to exceed supply for semiconductor products for the UK and Eire, reported the Semiconductor Manufacturers' Association (SMA).

This has allowed companies to fill their order books, although there are capacity limitations.

For the year to date, the order intake was 38% higher than last year's, while for billings it was 28% higher. ■

# OLSON<sup>®</sup>

**For all your Power Distribution  
Olson offer a varied  
choice**

**OLSON** Distribution Units

ELECTRONICS LIMITED

**OLSON** DISTRIBUTION PANELS  
FUSED, WITH R.F. FILTER  
AND R.C.D. PROTECTION

ELECTRONICS LIMITED

**OLSON** FUSED WITH RCD  
PROTECTION AND DOUBLE POLE  
WITH SOCKETS

ELECTRONICS LIMITED

**OLSON** 'The Rack Range'  
mains distribution panels  
for 19" rack mounting

ELECTRONICS LIMITED

**OLSON** Office Furniture  
Cable Management  
Manufactured to BS 6396

ELECTRONICS LIMITED

**OLSON** Mains Distribution  
Panels with  
Non Standard Sockets

ELECTRONICS LIMITED

**OLSON** FUSED SUPER SLIM  
MAINS DISTRIBUTION PANELS

ELECTRONICS LIMITED

**OLSON** Earth Leakage  
Distribution  
Units

ELECTRONICS LIMITED

**OLSON** Distribution  
Units

ELECTRONICS LIMITED

**OLSON** PANELS WITH 10AMP  
CEE22/IEC  
SHUTTER SOCKETS  
FUSED, DOUBLE FUSED WITH RCD  
AND R.C.D. PROTECTION

ELECTRONICS LIMITED

**OLSON** 'The Rack Range'  
WITH AMERICAN  
SOCKETS 125V 15A

ELECTRONICS LIMITED

**OLSON** Mains Distribution  
Panels  
INTERNATIONAL RANGE

ELECTRONICS LIMITED

**OLSON** FUSED SUPER SLIM  
WITH ELECTRAK PLUG  
CONDUIT AND DOUBLE  
POLE SWITCHED SOCKETS

ELECTRONICS LIMITED

**OLSON** DATA PROTECTOR  
10 AMP DOUBLE POLE FUSES WITH EARTHLEAK  
CIRCUIT AND OVERCURRENT PROTECTION

ELECTRONICS LIMITED

**OLSON** INDUSTRIAL RANGE  
16 AMP 110V AND 240V  
TO BS 4343/IEC 309

ELECTRONICS LIMITED

**OLSON** Distribution  
Units

ELECTRONICS LIMITED

**OLSON** 19" FAN TRAYS

ELECTRONICS LIMITED

**OLSON** 'The Rack Range'  
CEE22/IEC  
SOCKETS

ELECTRONICS LIMITED

**OLSON** SERVICE PILLAR FOR  
THE OPEN-PLAN OFFICE

ELECTRONICS LIMITED

**OLSON** Distribution  
Units  
FRENCH AND GERMAN STANDARD  
16A AND 20A

ELECTRONICS LIMITED

# M & B RADIO (LEEDS)

THE NORTH'S LEADING USED TEST EQUIPMENT DEALER

<b>OSCILLOSCOPES</b>	FARNELL SSG520 10 MHz-520 MHz synthesized generator	£400	IWATSU SCT104 10 GHz-1000 MHz frequency counter	£275
TEKTRONIX 2225 30 MHz dual trace	RACAL 9081 5 MHz-520 MHz synthesized generator	£450	ROHDE & SCHWARZ EKS R power meter	£600
TEKTRONIX 468 100 MHz digital storage	ADRET 7100D 300 KHz-600 MHz synthesized generator	£500	ROHDE & SCHWARZ ESU2 test receiver 25 MHz-1000 MHz	£1200
TEKTRONIX 475 200 MHz dual trace	SYSTRON DONNER 1702 100 KHz-1000 MHz synthesized generator	£600	EDDYSTONE 1837/2 30 MHz receiver + 1529 FSK unit	£600
TEKTRONIX 434 25 MHz dual trace storage	WILSTRON 610D/501 MHz-1500 MHz sweeper	£1000	RACAL RA17 30 MHz valve receiver	£200
TEKTRONIX SC564/TM504/DM501 80 MHz oscilloscope/multimeter	GIGA GR101A 12 GHz-18 GHz pulse generator (as new)	£650	RACAL RA1218 30 MHz receiver	£300
TEKTRONIX 7000 series oscilloscopes instock phone for prices & details	POLARAD 1106ET 1.8 GHz-4.6 GHz with modulator	£300	RACAL RA1772 30 MHz receiver	£750
TEKTRONIX 5113 dual beam storage mainframe (new)	MARCONI TF2008 10 KHz-510 MHz signal generator/sweeper	£250	RACAL RA1779/MA1 1107 30 MHz receiver	£1500
TEKTRONIX 7128 15 MHz rack mount oscilloscope	MARCONI TF2016 10 KHz-120 MHz signal generator	£195	RACAL 9063 two tone oscillator	£200
TEKTRONIX 212 500 KHz miniscopy	MARCONI TF2016A 10 KHz-120 MHz with rev power trip	£245	RACAL 9009 10 MHz-1500 MHz automatic modulation meter	£250
TEKTRONIX 326 25 MHz miniscopy	MARCONI 6055B 850 GHz-2150 GHz signal source	£225	RACAL 9008 1.5 MHz-2000 MHz automatic modulation meter	£300
BALLANTINE 1022B 25 MHz miniscopy	MARCONI 6056B 2 GHz-4 GHz signal source	£225	SYSTEMS VIDEO 1152/1153 compact 19" waveform monitor	£1500
HP1743A 100 MHz delta measurements	WAVETEK 182A 1 Hz-4 MHz function generator	£195	vectorscope	£600
HP1715A 200 MHz with dvm	EXACT 502LC 1 Hz-5 MHz function generator	£195	PHILIPS PM5567 pal vectorscopes	£600
HP1703A storage oscilloscope	ADRET 2230A 200 Hz-1 MHz synthesized source	£195	PHILIPS PM858A dual pen recorder	£225
PHILIPS 3311 40 MHz digital storage	LINSTEAD G1000 10 MHz synthesized oscillator	£200	SCHLUMBERGER 7702 digital transmission analyser (new)	£750
PHILIPS 3262 100 MHz dual trace	SAYROSA MA30 10 Hz-10 KHz oscillator	£150	SCHLUMBERGER 4010 radio test set	£400
PHILIPS 3240 100 MHz oscilloscope	THANDAR TG503 0.005 MHz-5 pulse/function generator	£225	SCHLUMBERGER 4900 AF/RF measuring unit	£400
PHILIPS 3055 50 MHz dual trace	<b>TEST EQUIPMENT</b>		SCHLUMBERGER AF 405 3 tone generator/modulator	£150
PHILIPS 3217 50 MHz dual trace	TEKTRONIX 1141/PG11/TSG11 Pal video generator	£1500	AMBER 4400A audio test set	£500
PHILIPS 3244 50 MHz 4 channel oscilloscope	TEKTRONIX 145 Pal gen lock test signal generator	£1500	FERROGRAPH RTS 2 audio test set + ATU I	£350
IWATSU SS6122 100 MHz 4 channel with cursors	TEKTRONIX 521A vector scopes	£350	ROD-LN100BVS55 hipot tester	£250
IWATSU SS5710 60 MHz 4 channel	TEKTRONIX 318 50 MHz 16 channel logic analyser	£350	BRANDENBURG 0-30kV/0V power supply	£700
LEADER LBS24L 40 MHz dual trace delayed t/b	TEKTRONIX A892A isolator	£450	WANDEL & GOLTERMAN PSS19 level generator	£650
GOULD 4035 20 MHz digital storage IEEE	TEKTRONIX TM501/DM501 bench multimeter	£125	MARCONI 6950/6910 10 MHz-20 GHz RF power meter	£850
GOULD 1420 20 MHz digital storage	TEKTRONIX P6045 FT differential probe	£250	MARCONI 455A VSWR indicator	£150
GOULD OS4000 10 MHz digital storage	TEKTRONIX P6015 high voltage scope probe	£95	MARCONI 6440/6421 10 MHz-12.4 GHz RF power meter	£250
GOULD OS250B 15 MHz dual trace	HP3468A 5.5 digit multimeter/auto cal (LCD)	£400	MARCONI TF2306 programmable interface unit	£400
<b>SPECTRUM ANALYSERS</b>	HP5004A signature analyser	£150	MARCONI TF2304 modulation meter	£200
TEKTRONIX 492 21 GHz spectrum analyser	HP5005A signature multimeter	£300	MARCONI TF2300B modulation meter	£100
TEKTRONIX 7L12 10 KHz-1.8 GHz + mainframe	HP5005 DC 100 MHz VHF attenuator 50 ohm 1-120db	£100	MARCONI TF2432A 10 Hz-560 MHz frequency counter	£125
BOONTON 1120 20 Hz-100 KHz audio analyser	HP1600A/1607A 32 bit logic analyser	£100	MARCONI TF2404 RF millivoltmeters with probes	£75
HP8903A 20 Hz-100 KHz audio analyser	HP10529A logic comparator	£75	MARCONI TF2913 test line generator/insertor	£250
HP1407/8552B/8553B 1 KHz-110 MHz spectrum analyser	BIRD 43 wattmeter	£100	MARCONI TF2160 20 Hz-20 GHz monitored AF attenuators	£50
HP1417/8552B/8554B 100 KHz-1250 MHz + (8553B)	BIRD 81B ferrite 80 watt coaxial resistor	£150	MARCONI TF23700 LCR meter battery portable	£150
HP1417/8552B/8554A 10 MHz-18 GHz + (8553B)	BIRD 8321 30dB attenuator 50w	£185	EIP 371 18 GHz source locking microwave counter	£950
HP8410/8414A 12 GHz network analyser	BIRD 8329 30dB coaxial attenuator 200w	£500	HP5342A 500 MHz-18 GHz microwave frequency meter OPT001/003	£1500
MARCONI TF2370 30 Hz-110 MHz spectrum analyser	TELEWAVE TW4-200 RF dummy load 50 ohm	£75	HP435B/8481A/8484A/11708A 10 MHz-18 GHz (new/HP case manuals)	£1100
MARCONI TF2370/2373 30 Hz-1250 MHz with frequency converter	EXACT 334 precision current calibrator	£195	HP435B/8481A 10 MHz-18 GHz RF power meter	£800
BRUEL & KJAER 2033 1 Hz-20 KHz audio analyser	FLUKE 103A frequency comparator	£250	HP435A/8482AH 100 KHz-4.2 GHz RF power meter	£550
<b>SIGNAL GENERATORS</b>	FLUKE 3330B prog constant current/voltage calibrator	£450	HP436A digital RF power meters	£650
HP8672 2 GHz-18 GHz synthesized signal generator	BALLANTINE 6125C prog time/amplitude test set	£400	HP3581C 15 Hz-50 KHz selective voltmeter	£600
HP8683D 2.3 GHz-13 GHz OPT 001 003 solid state generator (as new)	ALTECH 333X-11 calibrator (1 HP355C/1 HP355D ATT)	£295	HP4815A RF vector impedance meter with probes	£450
HP8620C/86290B 2 GHz-18 GHz sweeper	KEMO DPI 1 Hz-100 KHz phase meter (new)	£150	HP4951A protocol analyser	£350
HP8620 sweeper mainframes (as new) IEEE	WAYNE KERR CT496 LCR meter battery portable	£75	HP379A primary multiplex analyser	£350
HP3586A 50 Hz-32.5 MHz selective level meter	RADIOMETER TRB11 RLC component comparator	£150	HP3780A pattern generator/error detector	£350
HP3314A 0.001 Hz-19.99 MHz function/waveform generator	POLAR B1000A uP bus tester	£125	HP333A distortion analyser	£295
HP3336B 10 Hz-21 MHz synthesizer/level meter	AYO 215-L2/AC/DC breakdown/ionisation tester	£400	HP3762A data generator	£295
HP3336C 10 Hz-21 MHz synthesizer/level meter	AYO 8 MKS test meters with case/probes	£75	HP11667A DC-18 GHz power splitter (new)	£450
HP8640A 500 KHz-512 MHz signal generator	FARNELL RB 100/25 electronic load	£495	HP11710A down converter	£250
HP8645A 10 MHz-520 MHz signal generator	FARNELL TM8 10 KHz-1000 MHz true RMS sampling voltmeter	£350	HP4610 1 MHz-1000 MHz vector voltmeter	£350
HP8606A comb generator	FARNELL TOPS 3D triple output digital power supply	£195	HP4261A LCR meter	£350
HP8018A serial data generator	SIEMENS U2323 graphometer (new)	£350	HP8750A storage normaliser	£350
HP8007B 10 Hz-100 MHz pulse generator	SIEMENS D2108 200 KHz-30 MHz level oscillator	£350	HP3400A true RMS voltmeter (analogue)	£145
HP8005B 0.3 Hz-20 MHz pulse generator	NARDA 3001 450 MHz-950 MHz directional coupler 10/20/30db	£190	HP3403C true RMS voltmeter (digital)	£195
HP8616A 1.8 GHz-4.5 GHz generator	NARDA 3041 20-500 MHz-1000 MHz directional coupler 20db	£125	HP3406A 10 KHz-1200 MHz RF sampling voltmeter with probes	£200
ROHDE & SCHWARTZ APN62 0.1 Hz-260 KHz LF generator	NARDA 3044B-20 3.7 GHz-8.3 GHz 20db directional coupler	£150	HP3465A 4.5 digit multimeter	£125
(new) FARNELL SSG2000 10 KHz-2000 MHz synthesized generator (as new)	NARDA 3004-10 4 GHz-10 10db directional coupler	£175	HP3466A 4.5 digit autorange multimeter	£200
(new) FARNELL SSG2000 10 KHz-2000 MHz synthesized generator (as new)	NARDA 60132 solid state amplifier 0 GHz-12 GHz	£150	RACAL DANA 9904M 50 MHz universal counter timer	£95
(new) FARNELL DSG2 0.001 Hz-110 KHz synthesized (new)	THURLBY DSAS24 20 MHz digital scope adaptor	£225	RACAL DANA 9916 10 Hz-560 MHz frequency counter	£120
	SAYROSA AMH 1.5 MHz-2 GHz automatic modulation meters	£195	RACAL DANA 9918 10 Hz-560 MHz frequency counter	£195
			RACAL DANA 9919 10 Hz-1100 MHz frequency counter timer	£295
			RACAL DANA 9908 10 Hz-1100 MHz universal counter timer	£400
			RACAL DANA 9921 10 Hz-3000 MHz frequency counter	£400
			RACAL DANA 9916 10 Hz-160 MHz universal counter timer 9 digit	£500
			RACAL DANA 6000 microprocessing digital voltmeter	£250
			RACAL DANA 9232 dual output power supply 0-30 volt 0-2 amp	£150
			BRUEL & KJAER 2283 precision sound level meter/WB0812 filter	£450
			BRUEL & KJAER 2971 phase meter	£450
			BRUEL & KJAER 1022 beat frequency oscillator	£350
			BRUEL & KJAER frequency response analyser	£250
			BRUEL & KJAER 2425 0.5 Hz-500 KHz electronic voltmeter	£225

ALL PRICES PLUS VAT AND CARRIAGE. ALL EQUIPMENT SUPPLIED WITH 30 DAYS WARRANTY

**86 Bishopgate Street, Leeds LS1 4BB**  
**Tel: (0113) 2435649 Fax: (0113) 2426881**

CIRCLE NO. 107 ON REPLY CARD

## Hewlett Packard 8683D



Solid State Microwave  
 Signal Generators  
 2.3-13 GHz Freq' Range  
 Wideband FM for satellite  
 AM/FM & pulse modulation  
 Built in pulse generator  
 Options 001/003 fitted

£2,950 + Carriage + Vat

Supplied fully tested in as new condition. With 30 days parts & labour warranty.

M&B Radio DEALERS IN SURPLUS ELECTRONIC TEST EQUIPMENT

86 BISHOPGATE STREET LEEDS LS1 4BB

TEL: 01132 435649 FAX: 01132 426881

CIRCLE NO. 108 ON REPLY CARD

# RESEARCH NOTES

Jonathan Campbell

## Differential gps brings top honours for flying robot

Students have used a gps technique that can give a positional accuracy of centimetres rather than the usual 10m to win an award for their design of a flying robot. In the Annual Aerial Robotics Competition held in Atlanta at the Georgia Institute of Technology, a team from Stanford University's Aerospace Robotics Laboratory used gps for accurate determination of the position of its flying robot, allowing the robot to navigate a course and carry out some predetermined tasks.

The competition, sponsored by the Association for Unmanned Vehicle Systems (AUVS), requires that flying robots locate six small metal disks scattered in a 2m ring, capture them one at a time, carry each of the disks over a tennis net and drop them into a second 2m ring – all without direct human control.

Stanford's autonomous flying machine was the first entry to use satellite navigation to control movement, with an on-board computer relying on gps to update its position, including altitude, five times per second.

The military gps system was originally designed to limit the

accuracy available to civilian users, but the students used a technique called differential carrier phase gps to provide the computer with position information accurate enough to follow a pre-programmed course.

Their robot helicopter sported four gps antennas, two gps receivers and a 486 computer to control the helicopter's orientation as well as its motion. Precise positions of the boundaries of the competition area, and the location of the starting point, pick-up ring, net and drop-off ring were first determined by the students. Then the on-board computer was programmed to instruct the helicopter to climb to a set altitude; calculate the direction to the pick-up ring; fly to the pick-up ring; drop to the correct altitude so that the pick-up magnets would just drag on the ground; stay in the pick-up area for a few seconds; climb to an altitude high enough so that the magnets would clear the net; calculate the direction to the drop-off ring; and fly to the drop-off ring.

The autonomous flying machine became the first entry not only to hover under control, but also to move to the ring containing the metal disks and pick one up.



On its maiden flight, the Stanford helicopter disqualified itself by picking up two disks, rather than one. On its second effort, it failed to pick up any disks. But on its third try, it successfully picked up a single disk and carried it over the net to the drop-off ring.

However, the first prize for designing an aerial robot that can pick up all six disks and drop them in the ring still remains to be won. So there's still time for a UK team to take the honours next year.

*Differential carrier-phase gps helped Stephen Morris, Bruce Woodley and Andrew Conway from Stanford University position their robot within centimetres rather than metres.*

## High speed magnetic trains are back on the rails

Development of a high-speed, magnetically powered train that does not levitate, is relatively inexpensive to build, and can run on already-laid track could revitalise practical application of magnetic drive technology.

The concept for the train, developed at Sandia National Laboratories, is a spin-off from technology created at Sandia in the late 1980s for the Star Wars programme.

To move the train, pulsed magnets – 30 per 'locomotive' – induce reversed electric currents in a series of aluminum plates bolted to or near the track. The induced currents create their own magnetic fields that oppose those of the train. With the aid of

optical sensors, the fields pulse on just as the magnets pass the midpoint of the aluminum plates, and by repulsion propel the train forward. Plates would be pre-assembled in ladder-like sections – the plates serving as rungs – for fast, cheap bolting to the track. The design is also the basis for the name of the train Seraphim: segmented rail phased induction motor.

Rather than travel suspended by magnetic fields, Seraphim would ride on unpowered wheels made of steel or composite materials, reducing the cost and complexity of the system.


So unlike mag-lev trains under construction in Germany and Japan, the Sandia approach needs no

specially designed track, and permits old-style and new-style trains to travel on the same rails.

Also unlike mag-lev trains, which travel with no engine aboard, the proposed Sandia train would carry its own drive mechanism – a gas turbine that powers on-board electromagnets.

So far, using magnetic coils, a working model has propelled a vertical, two-foot tall aluminum plate along a rail. In less than 4m the plate can reach a speed of 54km/h, demonstrating the potential of the propulsive technique.

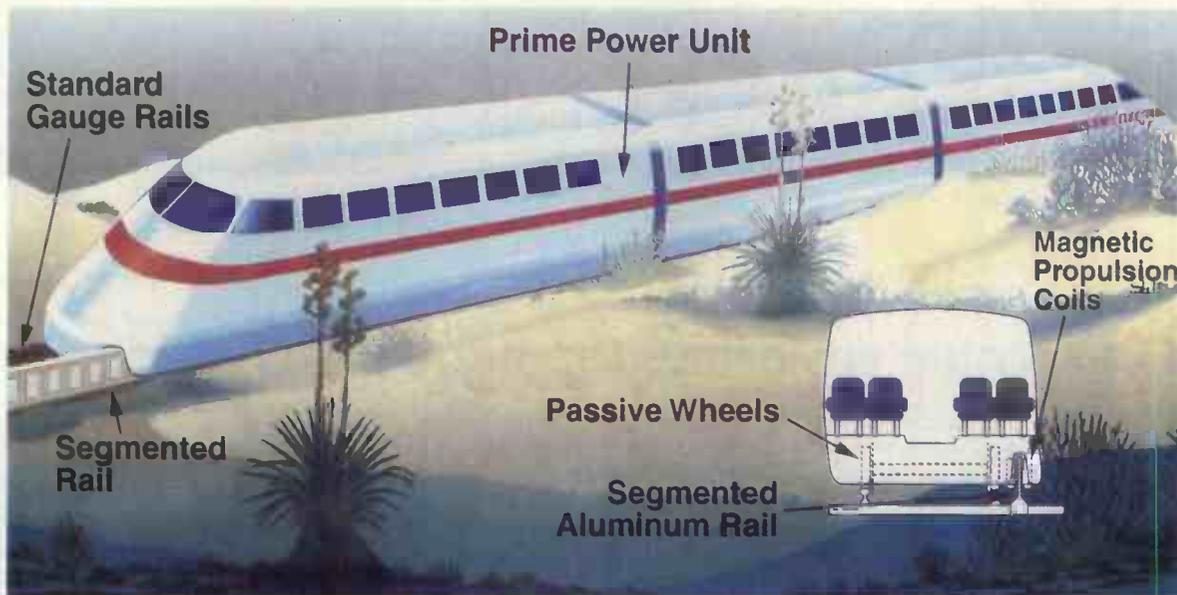The researchers are currently applying for funding to power an actual train to travel at 320km/h. Sandia says the train could achieve



Using available track, Seraphim is powered forward by inducing reversed electric currents in a series of aluminum plates

420km/h, but not on track already laid.

Slow-moving shuttles have used a similar method to achieve speeds of 50km/h. But these trains embed magnetic fields relatively slowly in a neighbouring metal rail to generate a

backward-moving wave of magnetic flux which thrusts the train forward. The Sandia method induces magnetic fields around the edges of a segmented aluminum rail placed along the track, a difference that allows a Seraphim-type train to achieve much higher speeds.

Similarly, experiments with conventional linear induction motors have reached speeds of more than 320km/h, but efficiency suffers at higher speed, while the performance and efficiency of the Sandia engine actually improves with velocity.

## Camera wired up to the world

Any *EW + WW* reader currently planning a romantic trip with a co-traveller who is not their partner – if you get my drift – should avoid Boston, Massachusetts. Or if they should find themselves in Boston, they should avoid Steve Mann.

Fortunately Mr Mann is relatively easy to pick out amongst Bostonians going about their normal business: he will probably have a box of electronics and camera lenses strapped to his head (see pictures).

But if he does see you, then you should be prepared to share your secret – with about 20-odd million

others. Because Steve Mann and his camera are attached to the Internet, and anyone browsing the Internet can see what he sees.

Mann's system is much more than a simple head-mounted camera.

Instead, visual information from the camera is sent directly to one or more remote processors, with a processed version of the visual information then received back at the head-mounted display, as part of a 'visual filter'.

Mann himself is part of the VisMod vision and modelling group in the Media Lab at MIT, and the purpose of the exercise is to stimulate

discussion of everything from visual perception and learning, augmented memory and personal safety/security, through to video postcards – with personal privacy considerations included along the way.

Using the camera system with radio communications, Mann's 'NetCam' can send his visual field anywhere in the world, using the Internet as a communications medium.

So if you want to find out more about how to view Steve Mann's world on the Internet – or want to find where he is so you aren't – contact him at [steve@media.mit.edu](mailto:steve@media.mit.edu).

Steve Mann's NetCam has moved on from just attaching a camera to the head and recording what the head movements point at, leftmost photo. Now what Steve sees is transmitted and processed remotely. As a result Internet browsers can view the world exactly from his perspective.



## Battlefield operation – and not a surgeon in sight

If the makers of *MASH* – the television series that memorably recorded life for a mobile army surgical hospital under fire in the Vietnam war – were to try portray battlefield medicine as it is developing today, things could look a little different. Because one of the key components of combat zone surgery could soon be gone forever: the surgeon.

That's not to say the soldiers will

# ANCHOR SURPLUS Ltd

The Cattle Market Depot  
Nottingham NG2 3GY. UK

Tele: +44 (0115) 986 4902/986 4041

Fax: +44 (0115) 986 4667



## Bruel & Kjoer

Model 2107 Frequency Analyser, 20Hz-20KHz-60 to  
+ 40db 4 Weighting Filters + External **£225**

Model 5587 Spectrum Shaper 125Hz-40KHz in 36 Bands  
Slider Controls **£250**

Model 2304 Level Recorder - 0003-100mm/sec and  
2-1000/sec Write Speed **£175**

## Rohde & Schwarz Model APN-62

Precision Low Frequency Generator 1Hz to 260KHz with  
1Hz res (0.1Hz<20KHz) Balanced/UnBal Outputs Sine-  
Square-Triangle-Sawtooth 100uV-20V Output  
(0.1db resolution) Frequency Sweep 1ms-65 secs  
Level Sweep 2ms-65 secs IEEE488 Option Fitted  
**£995.00**

## Marconi

TF2121 Waveform Generators, 0.001Hz to 100KHz  
50ohm & 600ohm Outputs, Sine Square, Triangle Sawtooth. 0-10V Out.  
+ 100 Phase Output. Cont/Single Shot DC Offset and Level Front/Rear OPs **£250**

## FOR-9

TG160 Alpha Numeric Video Title Generators, Variable Position Variable Bk/White Colour Mask, Parallel Bus **£75**  
VTG22 Video Timers, Year/Month/Date/H/M/s + 0.01sec superimposed on standard Video **£50**

## Fluke

Model 77 LCD Digital MultiMeters inc Protection case. 'Bumper Case', Leads, Probes, Manual Limited Qty Fully Tested  
and Warranted. **ONLY £75**

\*\*\*Also\*\*\* Model 80TK Digital Thermometer Add-Ons for the 77. C°,F°, Cased Manual. **ONLY £50**

## Racal DANA 9000 Series - All fitted High Stability Reference Oscillator

Model 9056/9059M HF Selective Analysers 1Mhz-100Mhz AM FM SSB (Two Tone) Measurements 60db  
Range Wide/Narrow Filters. For Analysis of Radio Transmissions. Few Left **£50**

Model 9904 10Hz to 50Mhz. 7 Digit LED Universal Counter Timer. **NOW ONLY £50**

Model 9914 10Hz to 200Mhz. 8 Digit LED. **NOW ONLY £75**

Model 9915 10Hz to 520Mhz. 8 Digit LED. **NOW ONLY £95**

Model 9916 10Hz to 520Mhz. 8 Digit LED. **NOW ONLY £110**

Model 9919 10Hz to 520Mhz. 8 Digit LED. **NOW ONLY £175**

## Wayne-Kerr

Model B424 Digital Component Meters LCD display of L, C and R (0.1uH 1-2K $\Omega$  0.1pF-20,000uF 1mR-20MR)  
Automatic Selection. Very Easy to Operate. Manual Incl **£75**

## Hewlett Packard

3456A 6.5 digit System Voltmeter 100nV Resolution  
300 Samples/sec 0.0001% Accuracy. HP-IB Option Fitted  
Last Few Available Reduced to  
**Only £495**

3478A 5.5 Digit LCD MultiMeter 100nV 100uOhm Resolution.  
90 readings/sec True RMS with 300KHz B/W & 41 Crest factor  
HP-IB Fitted. Last Few Available Reduced to  
**Only £495**

**OPEN SEVEN DAYS A WEEK**

**Mon-Fri 9am-6pm Sat 8am-4pm Sun 10am-4pm**

**NO APPOINTMENTS NEEDED. CALLERS ALWAYS WELCOME**

**All Prices are Ex VAT & Carriage**

**All items are Fully Tested with Verified Calibration  
and carry our Unique 30 Day Un-Conditional Warranty**



The remote scalpel appears to emerge from the hand controls as the surgeon looks down into the virtual workspace.

no longer be put under the surgeon's knife, simply that the surgeon may be holding it from several miles away through the technique of telepresence.

Remote manipulation has been around for many years, in the handling of dangerous materials for

example, though the interface has not been natural enough to allow a surgeon to work.

But now tests being carried out by SRI International in California (Telepresence Surgery, *IEEE Engineering in Medicine and Biology*, PS Green et al, pp.324-329), are showing that remote surgery is a real possibility. Most recently an operation has been carried out by a surgeon 160m away from the 'patient' - a dummy with a pig's intestines.


The SRI system integrates vision, hearing and manipulation using a surgeon's console and a remote surgical unit.

At the console, the surgeon can look down into a virtual workspace recreated by a 120field/s stereographic video monitor with an lcd shutter - the surgeon wears polarised glasses.

In a remote unit, the patient is viewed by a pair of video cameras and operated on by instruments held by a manipulator. The surgeon sees the instruments as emerging from handles he or she manipulates, and is able to sense the resistance of tissues as they are touched by the instruments and feel the suture as a knot is tied. Sounds are also picked up by stereo mics and relayed to the surgeon through speakers to add to the experience.

So far a telepresence surgery system has been installed in a mobile surgical vehicle with the intention that eventually, wounded soldiers will be placed on its operating table to be operated on remotely, improving immediate trauma care under combat conditions.

Field tests are expected shortly.

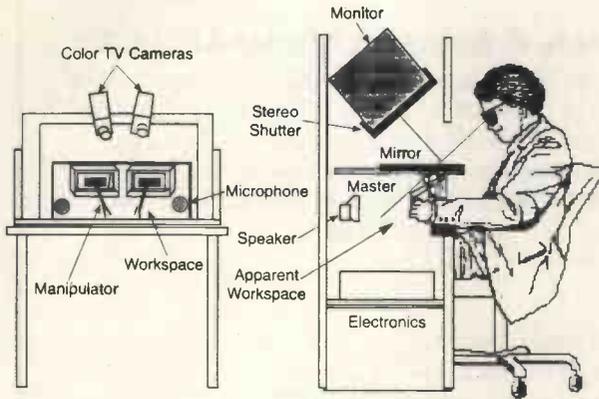

## No image problem for lcds

Photochromic molecules change their molecular shape upon photoradiation - a property that allows light to be used to control the orientation of liquid crystals. Now Tomiki Ikeda and Osamu Tsutsumi at the Research Development Corporation of Japan have developed a liquid crystal system that demonstrates optical switching capabilities significantly faster than any previous liquid crystal. Thermal stability of the system also means it could hold promise as a storage medium for optical images.

Ikeda and Tsutsumi concentrated their investigations on azobenzenes ("Optical switching and image

storage by means of azobenzene liquid crystal films, *Science*, Vol 268, pp.1873-1875).

The attraction of azobenzene is that the trans form of some of its derivatives is rod-like, stabilising the liquid phase, whereas the cis form is bent and destabilises the liquid crystal phase when present. So trans-cis photoisomerisation of azobenzenes in the liquid crystal phase can cause disorganisation of the phase structure.


To carry out their study, very thin films of photochromic liquid crystals (200nm) composed of photosensitive azobenzenes were produced and their photochemical

response investigated.

What the researchers found was that irradiating the films with a laser brought the trans-cis transformation in only 200µs, cutting off light transmission through the crystal two orders of magnitude faster than any system investigated previously.

Similarly, when the film was laser irradiated through a mask, then held at the same temperature in the dark, the resulting image remained unchanged after eight months.

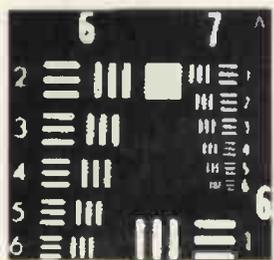The authors believe the properties of thin crystals of azobenzenes could make them ideal for optical switching and image storage.



Photochromic properties of liquid crystals composed of photosensitive azobenzenes could enable them to be used as an optical data storage medium.

## X-ray film bites the dust?

Scientists in the US are in the process of developing a prototype electronic x-ray sensor that could be the next step on the path to filmless x-ray examinations for patients. Developers claim their design differs from other digital radiographic devices that have recently come on the market in that it provides a better spatial resolution for a given sensitivity to x rays. So reduced dosages for examinees would result too.

At the core of the process is an electronic readout device being developed by scientists at Lawrence Berkeley Laboratory and Air Techniques, the US' largest supplier of automatic dental film processors. First application for the technology will be in dental radiography, but researchers say the goal is to make larger digital devices suitable for mammography or heart imaging.

The conventional way to x-ray teeth is with a piece of thick film that is moderately sensitive to x rays. To increase efficiency and lower the required dosage of x rays, the film can be sandwiched between sheets of plastic called intensifying screens. Disadvantage of using the screens is that they scatter radiation, resulting in decreased spatial resolution and accuracy.

But soon, in place of dental film, patients will be closing their mouths around electronic sensors and dentist and patient will be able to watch images coming up on a computer screen seconds after the device is inserted into the mouth. The images will be higher resolution than film images and will be conveniently stored or manipulated. Dental patients will also be exposed to as little as one-tenth of the x-ray radiation they

typically receive now.

The alternative electronic technology, developed at LBL by physicists Victor Perez-Mendez, John Drewery, and graduate student Tao Jing, relies on a light-emitting material, or scintillator.

Vacuum evaporation is used to deposit a scintillator, caesium iodide, on raised pucks dotting the surface of a patterned piece of high-temperature plastic. In the process of evaporation, the caesium iodide forms columns on the plastic pucks. When x rays hit these columns, the material emits light (scintillation) which is partially collimated, and sideways spreading is minimised.

"The net result is that our x-ray-detecting devices are more efficient and more accurate than the commercial Kodak film combination," says Perez-Mendez. ■

TRANSFORMERS FOR  
BALANCED LINES IN HIGH  
PERFORMANCE AUDIO SYSTEMS



E A Sowter Ltd  
PO Box 36 IPSWICH IP1 2EL ENGLAND  
Tel: +44(1)473 252794  
Fax: +44(1)473 236188  
E-Mail: sowter@tcp.co.uk

Design and Manufacture  
of all types of Audio Transformer using  
Nickel and Grain Oriented cores

Free catalogue  
Free technical support service  
Popular types from stock

CIRCLE NO. 109 ON REPLY CARD

COMPONENTS FOR  
GLOBAL POSITIONING SYSTEMS

Our GPS starter pack as featured in the August issue of Electronics World & Wireless World is still available.

The pack includes; Rockwell MicroTracker LP GPS receiver, MicroPulse magnetic mounting antenna, Power supply/serial board, Mains adaptor, serial cable, DC power cable, batteries, reference card, software and manuals - in fact, everything you need to get started. Price £379.

Also, now available, a Vehicle Tracking Developers Kit which includes GPS receiver, modem and software, which via a cellular telephone allows a remote vehicle position to be displayed over AutoRoute plus maps. The pack is available now for £495.

The Rockwell NavCard offers GPS receiver functionality in a PCMCIA II format for only £299. Capable of displaying your position on AutoRoute maps, this receiver is ideal for use with laptop computers. AutoRoute drivers and Windows GPS monitor software, £9.95.

Please add carriage at £13.50 (TNT next day), and VAT to total cost.

GPS Seminar, Basingstoke, September 7th £25, call to book.

**TDC**  
TELECOM DESIGN COMMUNICATIONS LTD

**Telecom Design Communications Ltd**  
Connect House, Stroudley Road,  
Basingstoke, RG24 0UG  
Tel : 01256 332800  
Fax : 01256 332810

CIRCLE NO. 110 ON REPLY CARD



**HATELY ANTENNA  
TECHNOLOGY**

1 Kenfield Place, Aberdeen AB1 7UW. Tel/fax: 01224 316004

**NEWS of the CROSSED FIELD ANTENNA**

THE GROUND PLANE CROSSED FIELD ANTENNA which has been more and more continuously used in development tests for Medium Wave Broadcasting at the Tanta Station in the Nile Delta, is now a permanent feature of Egyptian Broadcasting, reports our colleagues Kabbary and Khattab.

Recently completely re-built, and re-opened at a ceremony with President Mubarak, the GPCFA is now providing a service 16 hours a day on 1.161 MHz for a population of 15 million, using 30kW only. This represents a saving of 66% relative to the earlier 100 kW necessary to give the same signal service area using the now demolished quarter-wave antenna 65 metres in height.

Furthermore, the wider bandwidth of the GPCFA, which is only 8 metres tall mounted on the roof of the single storey transmitter building, is evident to most of the listeners in improved speech quality.

**FUTURE PLANS**

There are more GPCFA projects on stream in Egypt in order to extend both Long Wave and Medium wave services at reduced capital cost and running costs for the parent organisation; the Egyptian Radio and TV Union.


Professional Engineers may phone or circle the card to request a copy of the detailed signal strength report and photo. Patent licences are still available for some countries from our portfolio including US, Europe, Australia, Japan. New patents are filed for the "electrical dual" forms using two currents on separate wires. These have particular advantages in erection simplicity.

Evaluation tests can be performed using the modestly priced Amateur Radio versions available at: GPCFA format £400, Delay-Line format £199, Loop format £250, all prices including UK VAT and postage. Cash with order, or Pro-forma Invoice will be sent.

Proprietor: Maurice C. Hately, MSc FIEE Chartered Electrical Engineer (GM3HAT)

CIRCLE NO. 111 ON REPLY CARD

**EVERYTHING**  
Interactive development,  
**YOU WANT IN**  
easy to learn with  
**A CARD**  
ready-made libraries.  
**COMPUTER**

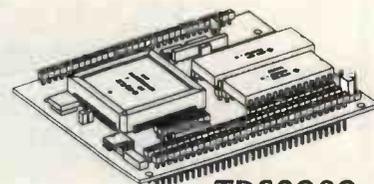

TDS2020



**Triangle Digital  
Services Ltd**  
Tel 0181-539 0285  
Fax 0181-558 8110

**RAPID**  
Graphics and keypad interfaces,  
**APPLICATION**  
35 parallel and 2 serial, clock,  
**DEVELOPMENT**  
10-bit 8-ch A to D, multitasker,  
**IN HIGH LEVEL**  
300µA data logging, PCMCIA.  
**LANGUAGE**

CIRCLE NO. 112 ON REPLY CARD



8 CAVANS WAY,  
BINLEY INDUSTRIAL ESTATE,  
COVENTRY CV3 2SF  
Tel: 01203 650702  
Fax: 01203 650773  
Mobile: 0860 406683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

#### OSCILLOSCOPES

Gould OS4000, OS4200, OS4100, OS1000B	from £125
Gould OS3000 - 40MHz, dual ch.	£250
Gould 4035 - 20MHz digital storage	£600
Gould 4050 - 35MHz digital storage	£750
Gould 5110 - 100MHz intelligent oscilloscope	£275
Hewlett Packard 1707A, 1707B - 75MHz dual ch	from £350
Hewlett Packard 1740A, 1741A, 1744A, 100MHz dual ch	from £350
Hewlett Packard 54201A - 300MHz digitizing	£1750
Hewlett Packard 54100D - 1GHz digitizing	£4950
Hitachi V-212 - 20MHz dual trace	£175
Nicolet 3091 - Low freq D.S.O.	£1100
Philips 3315 - 60MHz D.S.O.	£750
Lecroy 140 - 100MHz D.S.O.	£3250
Tektronix 468 - 100MHz D.S.O.	£800
Tektronix 2213 - 60MHz dual ch	£425
Tektronix 2215 - 60MHz dual ch	£450
Tektronix 2225 - 50MHz dual trace	£450
Tektronix 2235 - 100MHz dual ch. (portable)	£800
Tektronix 2335 - 100MHz dual ch. (portable)	£750
Tektronix 2465B 400MHz 4 channel	£3950
Tektronix 464/466 - 100MHz storage	from £350
Tektronix 465/465B - 100MHz dual ch.	from £350
Tektronix 7313, 7603, 7613, 7623, 7633, 100MHz 4 ch.	from £300
Tektronix 7704 - 250MHz 4 ch.	from £850
Tektronix 7834 with 7B42, 7B80, 7B85 - Plug-Ins (Storage 400MHz)	£1500
Tektronix 7904 - 500MHz	from £850
Tequipment D68 - 50MHz dual ch.	£200
Philips 3206, 3211, 3212, 3217, 3226, 3240, 3243, 3244, 3261, 3262 (2ch + 4 ch)	from £125 to £350
Philips PM293A - 400MHz dual channel	£1950
Hewlett Packard 54501A - 100MHz Digitising - 4 channel	£1950
Tektronix 2236 - 100MHz Dual Trace with Counter/Timer/Dmm	£895
Hwtsu TS 8123 - 100MHz Dig. Storage	£350

Other scopes available too

#### SPECTRUM ANALYSERS

Hewlett Packard 3580A - 5Hz - 50KHz	£995
Hewlett Packard 3582A - 25KHz analyser, dual channel	£2500
Hewlett Packard 182T with 8559A (10MHz - 21GHz)	£3750
Marconi 2370 - 110MHz	£995
Marconi 2371 - 30Hz - 200MHz	£1250
Rohde & Schwarz - SWOB 5 Polyskop 0.1 - 1300MHz	£2500
Schlumberger 1250 - Frequency response analyser	£2500
Alltech 727 - 22 - 4GHz	£2000
Altech 70727 - Tracking Generator for 727 (10KHz - 12.4GHz)	£2000
Texscan AL51A - 1GHz	£850
Tektronix 7L14 with 7603 - Mainframe (1.8GHz)	£2000
Tektronix 7L12 with 7603 mainframe (1.8GHz)	£1500
Tektronix 7L18 with 7603 mainframe (1.8GHz)	£950
Poirard 841-1 10MHz - 18GHz	£1500
Hewlett Packard 35601A - Spectrum Analyser Interface	£1000

## TELNET

Hewlett Packard 8754A Network Analyser - 4 - 1300MHz	£3250
Hewlett Packard 3709B Constellation Analyser with 15709A High Impedance Interface (as new)	£6750

#### MISCELLANEOUS

Anritsu MG642A Pulse pattern generator	£1500
Ballantine 323 True RMS voltmeter	£350
Datalab DL 1080 - Programmable Transient Recorder	£350
Datron 1061 - precision multimeter	£650
Dynagert TP20 - Intelliface tape reel tester, immac cond.	£1950
E.I.P. 331 18Hz frequency counter	£850
E.I.P. 548A - frequency counter (26.5GHz)	£3000
Farnell 2081 R/F Power meter	£350
Farnell TSV70 MkII - Power Supply (70V-5A or 35V-10A)	£225
Ferroglyph RTS2 Audio test set with ATU1	£500
Fluke 5101A - Calibrator AC/DC	£3500
Fluke 5101B - Calibrator AC/OC	£6500
Fluke 5220A - Transconductance Amplifier (20A)	£3000
Heiden 1107 - 30v-10A Programmable power supply (IEEE)	£650
Gould K1000 - 100MHz Logic Analyser with PODS	£350
Hewlett Packard 3325A - 21MHz synthesiser/function gen	£1500
Hewlett Packard 3437A System voltmeter	£350
Hewlett Packard 3438A Digital multimeter	£200
Hewlett Packard 3490A Digital multimeter	£250
Hewlett Packard 3586A - Selective level meter	£1750
Hewlett Packard 3702B/3705A/3710A/3716A Microwave link analyser	£1500
Hewlett Packard 3711A/3712A/3791B/3793B Microwave link analyser	£3500
Hewlett Packard 3475A System voltmeter	£350
Hewlett Packard 3762/3763 Data gen + error detector	each £300
Hewlett Packard 3762/3763 Data gen + error detector	each £350
Hewlett Packard 3775A Channel selector	£250
Hewlett Packard 3779A/3779C Primary multi. analyser	£600/£1000
Hewlett Packard 5150A Thermal printer	£275
Hewlett Packard 5316A - Universal counter HP/IB	£550
Hewlett Packard 5316B - Universal counter HP/IB	£750
Hewlett Packard 5358A - Frequency counter 1GHz (HP/IB) with Opts 001/003/004/005	£995
Hewlett Packard 59501B HP/IB isolated D/A power supply programmer	£150
Hewlett Packard 6181C D.C. current source	£150

Hewlett Packard 6261B Power supply 20V-50A  
DISCOUNT FOR QUANTITIES

Hewlett Packard 7402 Recorder with 17401A x 2 plug-ins	£300
Hewlett Packard 8005B Pulse generator	£250
Hewlett Packard 8011A Pulse gen. 0.1Hz - 20MHz	£500
Hewlett Packard 8152A - optical average power meter	£1250
Hewlett Packard 8158B - optical attenuator with opt's 002 + 001	£1100
Hewlett Packard 8443A Tracking gen/counter with IEEE	£300/£400
Hewlett Packard 8620C Sweep oscillator mainframe	£400
Hewlett Packard 8750A Storage normaliser	£375
Hewlett Packard 3456A Digital voltmeter	£750
Hewlett Packard 8664A - 5.4GHz to 12.5GHz Sig Gen.	£3000
Hewlett Packard 6632A - System Power Supply (HP/IB)	£500
Hewlett Packard 8640B - AM/FM Signal Gen. (512MHz)	£850
Hewlett Packard 8620C Sweep oscillator mainframe	£400
Hewlett Packard 5356A - 18GHz Frequency Converter Head	£450
Hewlett Packard 432A - Power Meter (with 478A Sensor)	£275
Hewlett Packard 435A or B - Power Meter (with 8481A/8484A)	from £750
Hewlett Packard 8662A - (10KHz - 1280MHz) synthesised signal generator	£7950

Hewlett Packard 4953A - protocol analyser	£3500
Hewlett Packard 1630G - logic analyser - 65 channels	£350
Hewlett Packard 5359A - time synthesiser	EP.O.A.
Hewlett Packard 5505A - laser display	EP.O.A.
International Light - IL 1700 research radiometer with Erythral sensor head	£1250
Lyons PG73M/PG75/PG28/PG Pulse generator	from £225
Marconi 2306A - Roganman interface	£500
Marconi 2337A Automatic dist. meter	£150
Marconi 2356 20MHz level oscillator	£300
Marconi 2432A 500MHz digital freq. meter	£200
Marconi 2830 Multiplex tester	£850
Marconi 2831 Channel access switch	£250
Marconi 953B A/V power meter	£295
Marconi 2019A 90KHz - 1040MHz synthesised sig. gen.	£1950
MultiCore 'Vapourure' bench top vapour phase SMD soldering machine (new and unused) (£1100 + new)	£650
Philips PM 5167 10MHz function gen.	£400
Philips PM 5190 LF synthesizer with GPIB	£900
Philips 3551A - logic analyser	EP.O.A.
Phoenix 5500A - telecomms analyser with various interface options	£2500
Racal 9301A True RMS R/F millivoltmeter	£300
Racal Dana 1992 - 1300MHz frequency counter opts 4B+5S	£800
Racal Dana 3100 40 - 130MHz synthesiser	£750
Racal Dana 5002 Wideband level meter	£650
Racal Dana 5003 Digital m/meter	£150
Racal Dana 9000 Microprocessing timer/counter 52MHz	£250
Racal Dana 9081 Synth. sig. gen. 520MHz	£550
Racal Dana 9084 Synth. sig. gen. 104MHz	£450
Racal Dana 9242D Programmable PSU 25V-2A	£300
Racal Dana 9246S Programmable PSU 25V-10A	£400
Racal Dana 9303 True RMS/R/F level meter	£650
Racal Dana 9341 LCR databridge	£250
Racal Dana 9500 Universal timer/counter 100MHz	£200
Racal Dana 9921 3GHz frequency counter	£450
Rohde & Schwarz BN36711 Digital Q meter	£400
Rohde & Schwarz LFM2 Sweep generator 0.02 - 60MHz	£1500
Rohde & Schwarz SCUD Radio code test set	£1500
Rotek 3980A - AC/DC Precision Calibrator with Rotek 350A High Current Adaptor	EP.O.A.
Schlumberger SI 4040 - StabiLock, high accuracy 1GHz radio test set	£5950
Schlumberger 4923 - Radio Code Test Set	£1500
Schlumberger 2720 - 1250MHz Freq. Counter	£600
Systems Video 1258 Waveform analyser + 1255 vector monitor + 1407 differential phase & gain module + 1270 remote control panel	£2250
Syston Donner 6054B or D - 18GHz or 24GHz Freq. Counter	from £900
Tektronix DA599100 Series Logic Analyser	£500
Tektronix - Plug-ins - Many available such as PG508, FG504, SC504, SW503, SG 502 etc	£1750
Tektronix TM203 + AF5101 Arbitrary Function Gen.	£750
Tektronix 1240 Logic Analyser	£600
Time 9811 Programmable resistance	£600
Time 9814 Voltage calibrator	£750
Watanabe WTR211 3 pen plotter	£250
Weller D90 Desoldering station	£150
Wiltron 352 Low freq. differential input phase meter	£350
Wiltron 560 Scalar Network analyser	£800

MANY MORE ITEMS AVAILABLE - SEND  
LARGE S.A.E. FOR LIST OF EQUIPMENT ALL  
EQUIPMENT IS USED - WITH 30 DAYS  
GUARANTEE. PLEASE CHECK FOR AVAILABILITY  
BEFORE ORDERING - CARRIAGE  
& VAT TO BE ADDED TO ALL GOODS

CIRCLE NO. 113 ON REPLY CARD

## BROADCAST MONITOR RECEIVER 2 150kHz-30MHz



We have taken the synthesised all mode FRG8800 communications receiver and made over 30 modifications to provide a receiver for broadcast purposes or checking transmitter performance as well as being suited to communications use and news gathering from international short wave stations.

The modifications include four additional circuit boards providing \*Rechargeable memory and clock back-up \*Balanced Audio line output \*Reduced AM distortion \*Buffered IF output for monitoring transmitted modulation envelope on an oscilloscope \*Mains safety improvements.

The receiver is available in free standing or rack mounting form and all the original microprocessor features are retained. The new AM system achieves exceptionally low distortion: THD, 200Hz-6kHz at 90% modulation -44dB, 0.6% (originally -20dB, 10%).

\*Advanced Active Aerial 4kHz-30MHz \*PPM10 in-vision PPM and chart recorder \*Twin Twin PPM Rack and Box Units \*Stabilizers and Fixed Shift Circuit Boards for howl reduction \*10 Outlet Distribution Amplifier 4 \*Stereo Variable Emphasis Limiter 3 \*Stereo Disc Amplifiers \*Peak Deviation Meter \*PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and movements \*Broadcast Stereo Coders.

### SURREY ELECTRONICS LTD

The Forge, Lucks Green, Cranleigh  
Surrey GU6 7BG  
Telephone: 01483 275997 Fax: 276477

## THE clock for your computer



The ADC-60 brings the accuracy of a time standard to your computer. It provides a data source which can be used by any system which has a serial port such as a PC, MAC or mainframe. The ADC-60 offers improved reliability by using both the British MSF and German DCF time standards. If one of the signals cannot be received the other source will automatically be used.

Other ADC-60 Features include:

- LCD display showing current time and date together with the lock status of the unit.
- Provides GMT or Local time outputs together with the date
- Serial output in ASCII or BCD format
- Includes 2 software packages, the first is a TSR which runs under DOS, the second runs as a minimised window in Microsoft Windows

Contact us today for further information on this superb product

**AMDAT** 4 Northville Road, Northville  
Bristol BS7 0RG  
Tel: 01179 699352 Fax: 01179 872228

CIRCLE NO. 114 ON REPLY CARD

# Best rf article '95

Following the success of 1994's Writers Award, **Electronics World** and **Hewlett-Packard** are launching a new scheme to run from January to December 1995.

Only articles which have an element of rf design will be eligible for consideration by the judging panel. It is hoped that this year's award will focus writer interest on rf engineering in line with the growing importance of radio frequency systems to an increasingly cordless world.

The aim of the award scheme is to locate freelance authors who can bring applied electronics design alive for other people.

Qualifying topics might include direct digital synthesis, microstrip design, application engineering for commercially available rf ICs and modules, receiver design, PLL, frequency generation and rf measurement, wideband circuit design, spread spectrum systems, microstrip and planer aeriels... The list will hopefully be endless.

All articles accepted for publication will be paid for – in the region of several hundred pounds for a typical design feature.

**Win a £4000**  
programmable signal  
generator from  
**Hewlett-Packard**



**The prize for the coming year's award is a £4000 Hewlett-Packard HP8647A 1GHz programmable signal generator. It features GPIB interface, solid state programmable attenuator and built in AM-FM modulation capability.**

*For further details about our quest for the best, call or write to:  
Martin Eccles, Editor, Electronics World,  
Quadrant House, The Quadrant, Sutton,  
Surrey, SM2 5AS  
Tel 081-652 3128*

## Designing with a

## single rail



**Analogue expert  
Walt Jung shows  
how to design  
circuits operating  
from a low-voltage  
single-rail supply  
without  
compromising on  
performance.**

Walt Jung is with Analog Devices Inc.

**T**here is a vast amount of digital circuitry in existence, and much more is emerging. Nearly all of this circuitry operates from a single 5V or 3V rail. Since more and more analogue and digital circuitry is being combined, there has been a rapid rise in the need for analogue circuitry capable of operating from the same low-voltage supply rail as the logic elements.

This collection of applications illustrates low-voltage, low-power design concepts. A variety of stand-alone circuits is presented, each involving single supply and/or low-power circuit design techniques.

#### Low-power, low-dropout references

There are many problems associated with making stable dc voltage references work from 3-5V supplies. Among these are quiescent power consumption and overall power efficiency, the ability to operate down to 3V, low input/output (dropout) capability, and minimum noise output.

Since supplies of less than 7V cannot support zener mode devices, low-voltage references must of necessity be bandgap types. All circuits shown below work at 5V and up, with many operating down to as low as 3V.<sup>1,2</sup>

One of the more difficult designs is simply to get a reference to work well from very low voltages, say 3V. This dictates use of a reference diode of appreciably lower voltage. One solution is a 1.2V reference diode and appropriate low power support circuitry, Fig. 1.

While this circuit appears trivial at first glance, when power drain must be minimised, the options narrow. A low operating current diode is a must for  $D_1$ , and here, an industry standard *AD589*. This 1.235V device has a minimum current of 50 $\mu$ A.

Resistor  $R_1$  sets this current, which is chosen for 50 $\mu$ A at the minimum operating supply. In this case,  $R_1$  operates from supplies down to 2.7V. Obviously, loading on the unbuffered

diode must be minimised, but generally static loads of a few microamps are fine.

Dynamic loads present a larger problem. Usually, a power conscious designer will not want to burn excess current in a reference diode to cater for occasional load changes. Amplifier  $IC_1$  alleviates this problem, buffering the diode so that higher source/sink currents are allowed, with a quiescent current which follows the  $IC_1$  choice from the table.

Without gain scaling resistors  $R_{2,3}$ , output is simply 1.235V; when the resistors are used the output can be set between the reference voltage and the supply rail, assuming a rail-to-rail output swing from  $IC_1$ . Amplifier standby current can be optionally reduced to around 20 $\mu$ A if an *OP193* is used, and the listed devices generally operate from supplies down to 3V – except for the 5V minimum *OP279*.

Available output current is set by the device chosen, which can be as high as 45mA, as indicated in the last column. As noted for all rail-to-rail devices,  $V_{OUT}$  can approach the positive rail within the levels shown at the specified currents.

Power conservation can be a critical issue with references, just as can output dc precision. For such applications, simple, one package fixed voltage references which simply 'drop in' with minimal external circuitry and deliver high accuracy are very attractive.

Two unique features of the three terminal *REF19x* bandgap reference family are low power consumption and shut-down capability. The series allows fixed outputs from 2.048 to 5V, which can be controlled between on and off via a ttl/c-mos power control input,  $V_C$ . It provides a precision reference for the popular voltages as listed in the table of Fig. 2.

The *REF19x* family can be used as a basic three-terminal fixed reference as per the table, simply by linking pins 2 and 3 and operating it as shown. It can also be used as an on/off controlled device, by programming pin 3 high or low, as noted.

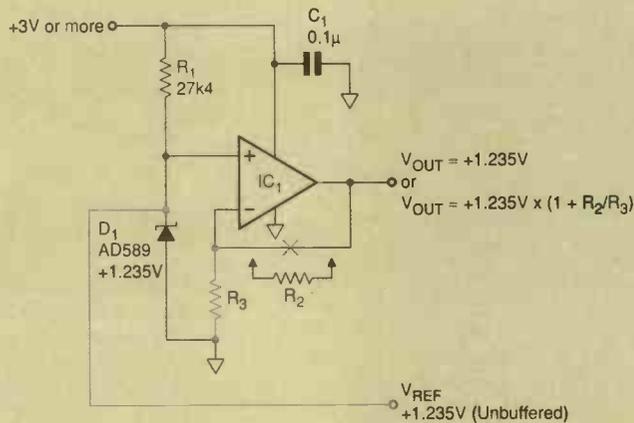


Fig. 1. Rail-to-rail output stage op-amps help design low drop-out voltage references.

Typical device specifications for 5V supply and 25°C ambient.

Device	$I_{q/channel}$ mA	$V_{sat(+)}$ V min@mA	$V_{sat(-)}$ V max@mA	$I_{sc}$ mA min
OP193/293/493	0.017	4.20@1	0.280@1 (typ)	±8
OP295/495	0.150(max)	4.50@1	0.110@1	±11
OP191/291/491	0.300	4.80@2.5	0.075@2.5	±8.75
AD820/822	0.620	4.89@2	0.055@2	±15
OP284/484	1.250(max)	4.85@1	0.125@1	±7.5

worst-case levels down to 4.6V or less.

Figure 4 shows such a regulator using an OP284 plus a low  $R_{ds(on)}$  p-channel mosfet pass device. Low dropout performance is provided by  $Tr_1$ , with a rating of 0.11Ω with a gate drive of 2.7V. This relatively low gate drive allows operation on supplies as low as 3V without compromising overall performance.

The circuit's main voltage-control loop operation is provided by  $IC_{1B}$ , half of the OP284. This voltage control amplifier amplifies the 2.5V reference voltage produced by IC2, a REF192. The regulated output voltage  $V_{OUT}$  is then:

$$V_{OUT} = V_{OUT2} \left[ 1 + \frac{R_2}{R_3} \right]$$

where  $V_{OUT2}$  is generally the  $IC_2$  voltage.

Note that for the lowest  $V_{OUT}$  dc error,  $R_2/R_3$  should be maintained equal to  $R_1$ , as here, and the  $R_{2,3}$  resistors should be stable, close tolerance metal film types. The table suggests  $R_{1,3}$  values for popular output voltages. In general,  $V_{OUT}$  can be anywhere between  $V_{OUT2}$  and the 12V maximum rating of  $Tr_1$ .

While the low-voltage saturation characteristic of  $Tr_1$  is part of the low drop-out key, the other expedient is a low and accurate current-sense comparison. Here this is provided by current-sense amplifier  $IC_{1A}$ , which produces a 20mV reference from 1.235V reference  $D_2$ , and the  $R_7/R_8$  divider. When the product of the output current and sense resistor  $R_{SENSE}$  match this voltage threshold, current control is activated, and  $IC_{1A}$  drives  $Tr_1$ 's gate positive via

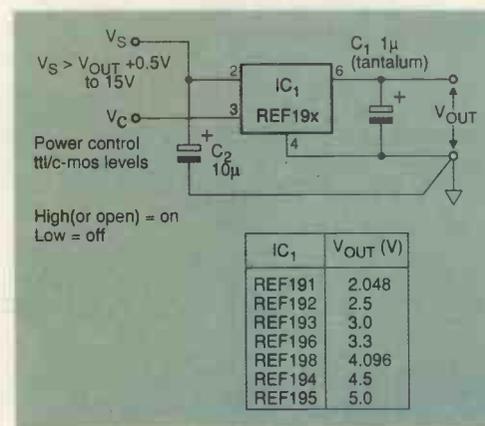


Fig. 2. A voltage reference family with 30mA, low-drop-out features.

In addition to the shutdown capability, the distinguishing functional features are a low dropout of 0.5V at 10mA, and low current drain for both quiescent and shutdown states, at 45 and 15µA maximum, respectively.

When a REF195 is used with inputs in the range 6.3 to 15V for example, it can drive 5V loads at up to 30mA. It also has grade dependent tolerances of ±2 to ±5mV, and maximum temperature coefficients of 5 to 25ppm/°C. Other devices in the series provide comparable accuracy specifications, and all have low dropout features.

To maximise dc accuracy in this circuit, the output lead from  $IC_1$  should be connected directly to the load with short heavy traces, to minimise the impact of IR drops. The common ground terminal, pin 4, is much less critical due to the lower current in this leg. The 1µF output capacitor is part of the device's frequency compensation, and cannot be omitted.

### Regulating with low dropout voltage

By adding a boost transistor to the basic rail-to-rail output low-dropout reference of Fig. 1, output currents of 100mA or more are possible, while still retaining the features of relatively low standby current and low dropout voltage. Figure 3 shows a low dropout regulator with a 800µA standby current, suitable for a variety of outputs at current levels of 100mA or more.

The 100mA output is achieved with a controlled-gain bipolar power transistor for pass device  $Tr_1$ , namely an MJE170. Maximum output current control is provided by limiting base drive to  $Tr_1$  with series resistor  $R_4$ . This limits the base current to about 2mA, so the

maximum  $H_{FE}$  of  $Tr_1$  then allows no more than 500mA, limiting the transistor's short circuit dissipation to safe levels.

Overall, the circuit operates as a follower with gain similar to Fig. 1, so  $V_{OUT}$  has a similar output expression. The circuit is adapted for different voltages simply by programming feedback resistor  $R_2$  via the table. Dropout with a 100mA load is about 200mV, thus a 5V output is maintained for inputs above 5.2V, see table, and  $V_{OUT}$  levels down to 3V are possible.

Step load response of this circuit is quite good, and transient error is only a few millivolts pk-pk for a 30-100mA load change. This is achieved with low effective series resistance switching-type capacitors at input-output, but the circuit also works with conventional electrolytics, albeit with increased transient errors.

If desired, lowest output noise with the AD820 is reached by including the optional reference noise filter,  $R_5/C_1$ . Lower current op-amps can be used for lower standby current, but they may involve a tradeoff of larger transient errors, due to reduced bandwidth.

As noted above, a 'low dropout' regulator is readily implemented with a rail-to-rail output op amps such as those of Fig. 1. This is because their wide output swing makes driving a low saturation voltage pass device simple. Further, it is most useful when the op-amp used also enjoys a rail-rail input feature, as this factor allows high-side current sensing for current limiting.

Typical applications are voltages developed from a 3-9V range system sources, or anywhere where low dropout is required to maximise power efficiency. The 4.5V example here works from 5V nominal sources, with

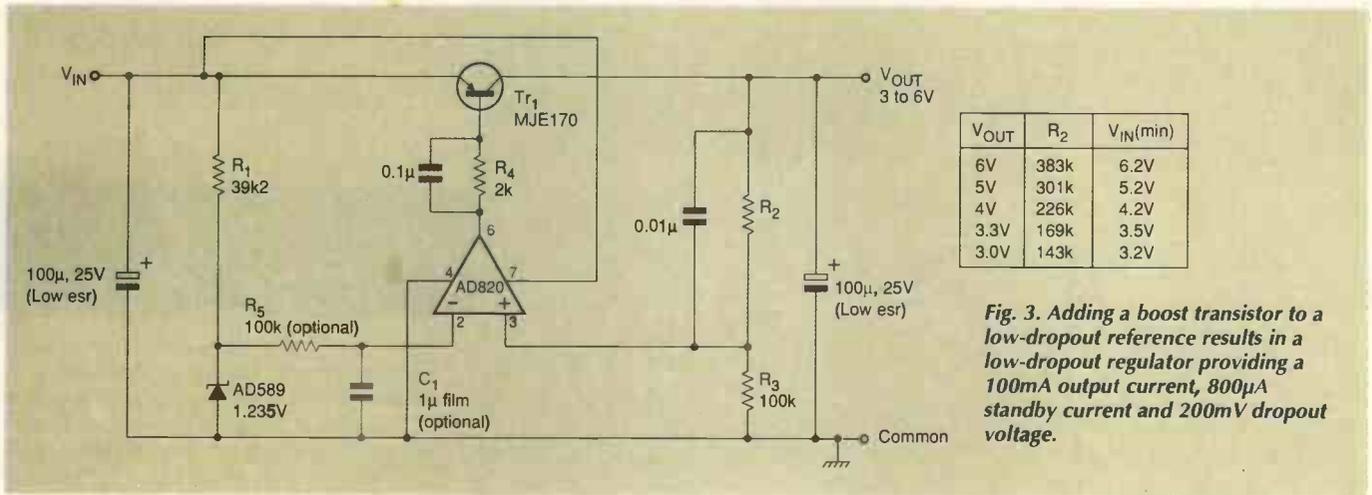


Fig. 3. Adding a boost transistor to a low-dropout reference results in a low-dropout regulator providing a 100mA output current, 800µA standby current and 200mV dropout voltage.

D<sub>1</sub>. Overall circuit operation is then under current mode control, with a current limit I<sub>limit</sub> defined as:

$$I_{limit} = \left[ \frac{V_{R(D2)}}{R_{SENSE}} \right] \cdot \left[ \frac{R_7}{R_7 + R_8} \right]$$

Obviously the comparison voltage should be small, since it becomes a significant portion of the overall dropout voltage. Here the 20mV value used is higher than the typical offset of the OP284, but still reasonably low as a percentage of V<sub>OUT</sub>, at less than 0.5%. For other I<sub>limit</sub> levels, sense resistor R<sub>SENSE</sub> should be set along with R<sub>7,8</sub> to maintain this threshold voltage between 20 and 50mV.

For a 4.5V output version, measured dc output change for a 225mA load change was of the order of a few microvolts, while the dropout voltage at this same current level was about 30mV. Current limit as shown is 400mA, allowing operation at levels up to 300mA or more. While Tr<sub>1</sub> can support currents of several amperes, a practical current rating takes into account this SO-8 device's 2.5W 25°C dissipation. A short-circuit current

of 400mA at an input level of 5V will cause a 2W dissipation in Tr<sub>1</sub>, so other input conditions should be considered carefully in terms of the device's potential overheating. If higher powered devices are used for Q<sub>1</sub>, the circuit will support outputs of tens of amperes as well as the higher V<sub>OUT</sub> levels noted above.

The circuit can be used either as shown for a standard low dropout regulator, or it can also be used with on/off control by applying a logic control voltage V<sub>C</sub> to IC<sub>2</sub>. Note that when the output is off in this circuit, it is still active – i.e., not an open circuit. This is because the off state simply reduces the voltage input to R<sub>1</sub>, leaving the IC<sub>1A/B</sub> amplifiers and Tr<sub>1</sub> still active.

When on/off control is used, resistor R<sub>10</sub> should be used with IC<sub>1</sub>, to speed on-off switching, and to allow the output of the circuit to settle to a nominal zero voltage. Components D<sub>3</sub> and R<sub>11</sub> also aid in speeding up the on-off transition, by providing a dynamic discharge path for C<sub>2</sub>. Transition time from off to on is less than 1ms, while the on-to-off transition is longer, but under 10ms.


4-20 mA current looping

Amplifier devices with outputs that swing close to the negative rail both enhance and simplify the design of 4-20mA current loop transmitters. A case in point is the circuit of Fig. 5. This is a loop-powered strain-gauge sensor where an amplified 50mV full-scale bridge output is calibrated to drive a 4-20mA transmitter output. This is a loop powered circuit, thus the entire signal processing current budget must stay well below the 4mA offset current level – including bridge drive.

Single-supply instrumentation amplifier, or in-amp, IC<sub>1</sub> is an AMP04. It amplifies the bridge signal linearly by a gain G of about 40 times, where gain is determined by R<sub>GAIN</sub>. The AMP04 output swing includes the negative rail, so the 0-50mV bridge signal is amplified to a nominal 0-2V signal referred to the loop common bus, pin 5 of IC<sub>1</sub>. With all device negative supply pins referenced to this bus, the bulk of the loop quiescent current is made to flow into R<sub>6</sub>, plus the external loop and the 100Ω termination, R<sub>LOAD</sub>.

With no output from the bridge, IC<sub>1</sub> output will be at the negative rail. No current then

Fig. 4. Low drop-out voltage regulators are useful for battery applications. This 300mA regulator features high-side current sensing.

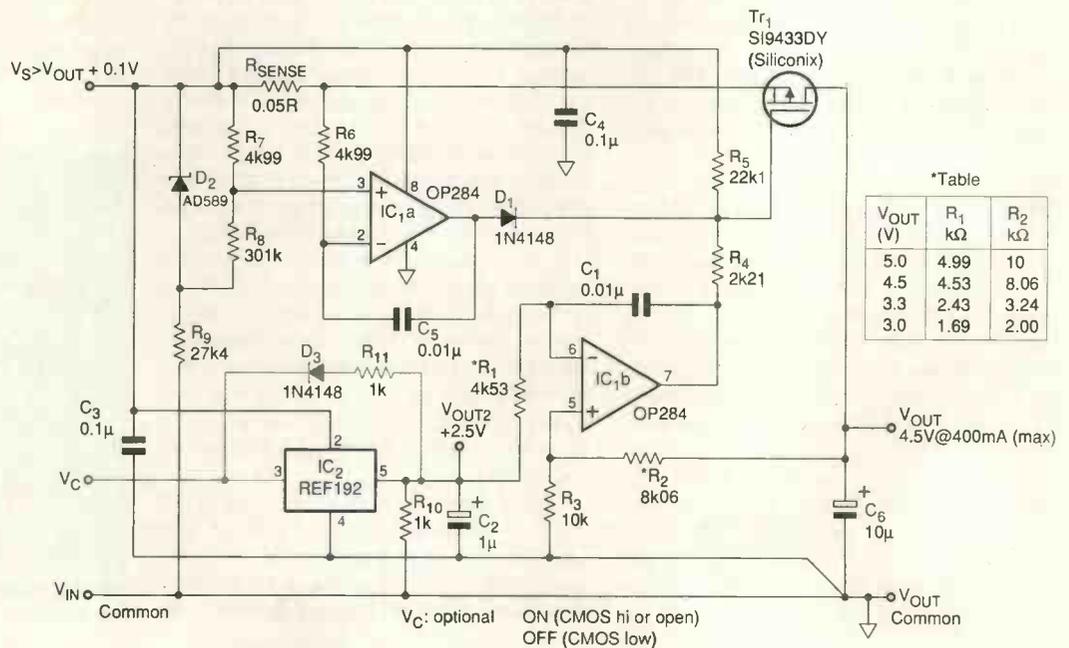

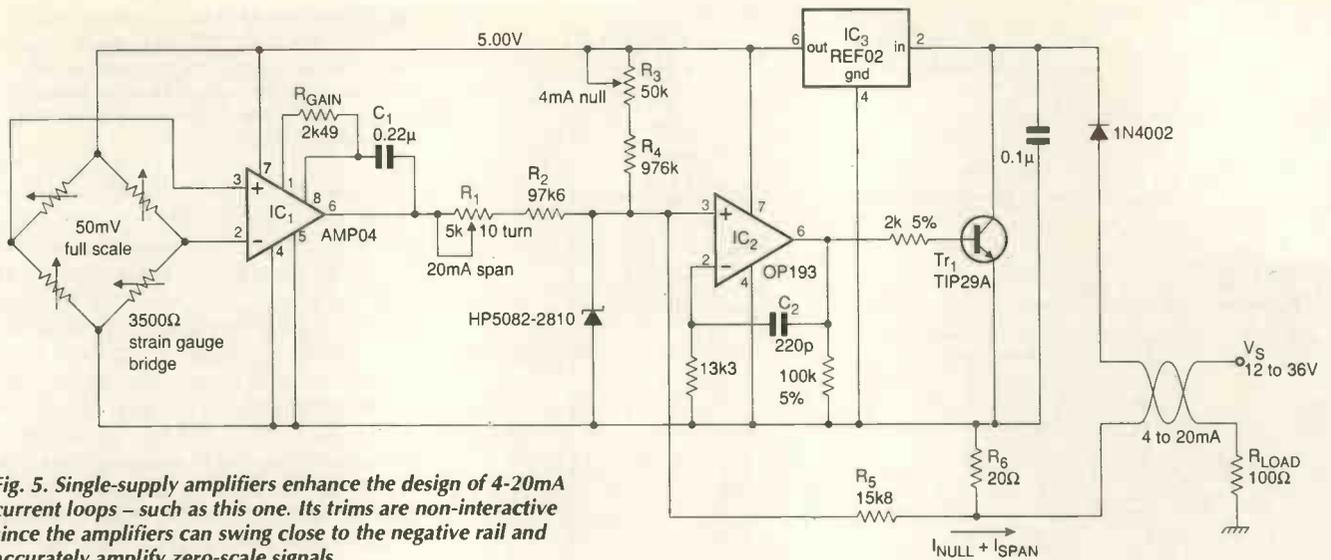


Fig. 5. Single-supply amplifiers enhance the design of 4-20mA current loops – such as this one. Its trims are non-interactive since the amplifiers can swing close to the negative rail and accurately amplify zero-scale signals.

flows into the summing point of IC<sub>2</sub> via R<sub>1,2</sub>, since the summing point is servoed by IC<sub>2</sub> to this same potential. For this zero scale signal condition, the loop is calibrated via R<sub>3</sub> (null) for a 4mA output current, or 0.4V across R<sub>LOAD</sub>. Because current in R<sub>1</sub> is zero for this condition, it has no effect on the null trim, thus making the null/span trims non-interactive.

Resistors R<sub>3,4</sub> effectively appear across the 5V reference voltage from IC<sub>3</sub>, so the current injected is constant and scaled up by loop output summing resistors, R<sub>5,6</sub>. The expression for this current, I<sub>NULL</sub>, is,

$$I_{NULL} \approx \left[ \frac{5}{R_3 + R_4} \right] \left[ \frac{R_5 + R_6}{R_6} \right]$$

where 5 represents the IC<sub>3</sub> reference voltage.

As the system sees a 50mV full-scale bridge output, this is amplified to a 2V level by IC<sub>1</sub>, which then supplies signal current to the IC<sub>2</sub> summing point. Like the reference current through R<sub>3,4</sub>, signal current in R<sub>1,2</sub> is

scaled up by the loop, and appears in R<sub>6</sub> as I<sub>SPAN</sub>, or,

$$I_{SPAN} \approx \left[ \frac{V_{BRIDGE} \times G}{R_1 + R_2} \right] \left[ \frac{R_5 + R_6}{R_6} \right]$$

where V<sub>BRIDGE</sub> is output of the bridge, and G is gain of the AMP04 op-amp. In this case trimming is done via potentiometer R<sub>1</sub> (span) with a 50mV full-scale bridge output, for a 20mA output current (4mA I<sub>NULL</sub> plus 16mA I<sub>SPAN</sub>), or 2V across R<sub>LOAD</sub>.

In this circuit the three active devices and the 3500Ω bridge consumes 3.75mA of current worst case – safely below the 4mA zero scale of the system. Capacitor C<sub>1</sub> provides a 7Hz low pass, to limit noise, while C<sub>2</sub> stabilises the IC<sub>2</sub> output loop.

The 0-16mA I<sub>SPAN</sub> portion of the loop output is conducted by Tr<sub>1</sub>, a TO-220 device. The low drift at typically 0.2µV/°C of the OP193 used at IC<sub>2</sub>, along with the low quiescent power of 15mA, aid overall performance of this circuit.

### Digital-to-analogue on a 5V rail

Most d-to-a converters are designed for dual supply operation. Of those which are not, most work on supplies of 12-15V, as opposed to 5V only. This greatly reduces the component choices available for single +5V supply system power.

Complementary-mos R-2R ladder converters are natural choices for low voltage operation, as many of these units are designed to work on 5V supplies. However, when used in their standard multiplying mode with an inverting output amplifier, they also require a negative supply for the amplifier, in order to output negative voltage with a positive reference. Conversely, if a negative reference is used, the output is positive range. In either case a negative supply is required.

In order to make such a d-to-a converter operate totally unipolarly, it can be turned around and operated in what is known as its inverted, or voltage-output mode. With the IC<sub>1</sub> DAC8043 pinout shown in Fig. 6, in this mode V<sub>REF</sub> input to the ladder becomes the voltage output node, pin 1, and normal I<sub>OUT</sub> node becomes the reference input, pin 3.

This voltage mode c-mos d-to-a converter circuit works on 5V only, using two eight-pin

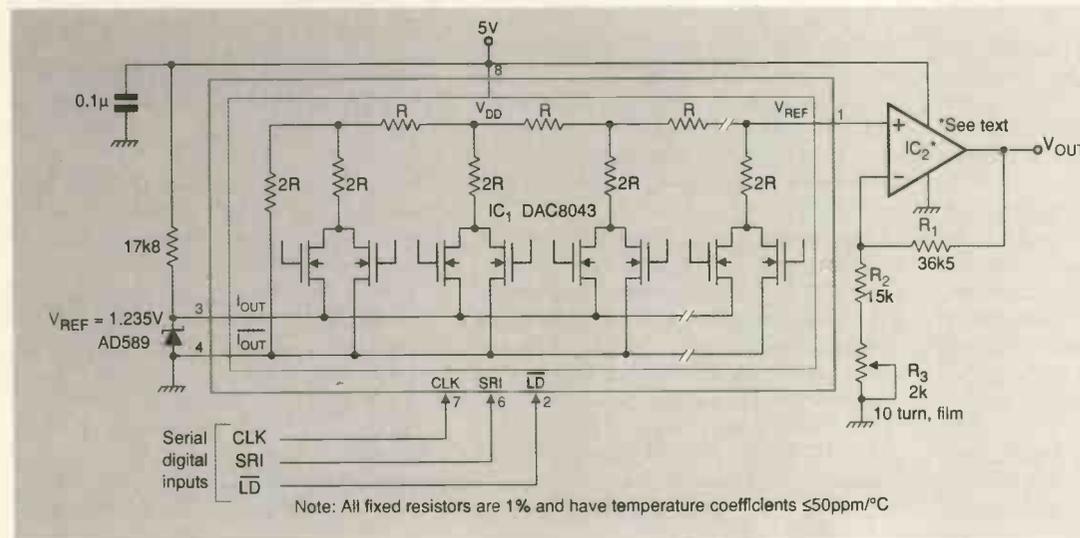


Fig. 6. To run a standard c-mos R/2R ladder d-to-a converter from a single supply rail, you need to operate the converter in its inverted, or voltage-output, mode.

Note: All fixed resistors are 1% and have temperature coefficients ≤50ppm/°C

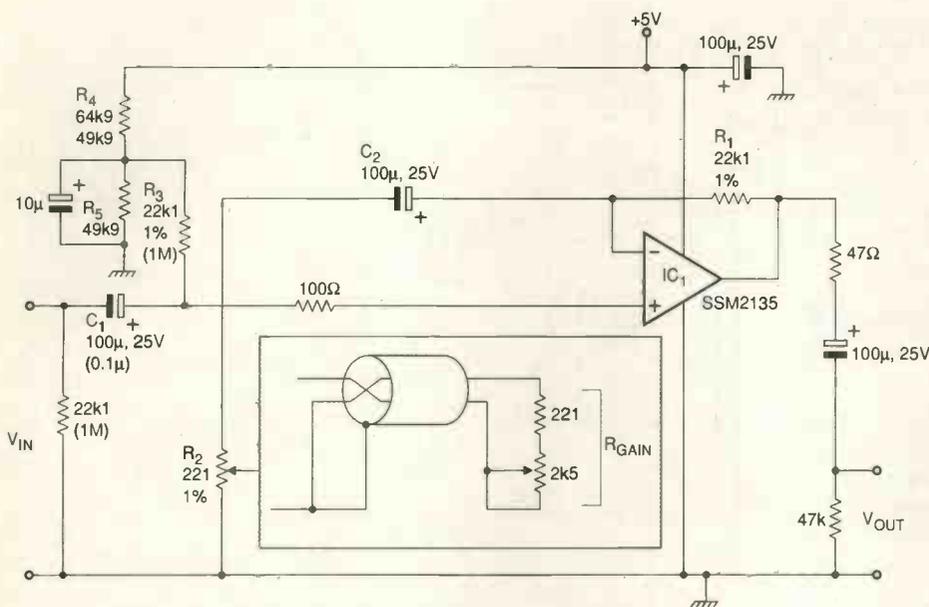


Fig. 7. Devices and circuit topologies make achieving low noise difficult in single-supply designs. One critical design technique is to limit resistor noise using low-noise resistors, or by adding bypass capacitors across them, as this circuit does for  $R_5$ .

ly affected by the choice of  $IC_2$ , and some tradeoffs may be necessary for the best overall choice. Relatively slow response and good overall dc accuracy is possible with the  $OP295$ , or faster response with good but somewhat reduced accuracy with the  $AD820$ .

For a linear  $V_{OUT}$  range of 0 to 4.095V, the amplifier must be a rail-to-rail output stage type such those shown in Fig. 1. The  $OP295$  has a maximum  $V_{OS}$  of 300 $\mu$ V, so the worst case output offset will be about 1mV; with the  $AD820$  this is raised by a factor of 1.67 – optionally nulled if desired. If the low offset  $OP284$  is used, the output offset error can easily be kept below 1lsb.

All amplifiers mentioned can source a 4.095V output on 4.75V, with current as noted in the table of Fig. 1. The rail-to-rail output stages allow linear swings close to ground. For the  $OP295$ , the c-mos output stage allows linear outputs down to within 1mV or lower, while the bipolar output types pull down to about 10mV or lower. Note that the  $R_{1-3}$  gain-set resistances act as a pull-down, as do any external loads to ground.

With the amplifier selection, there is an intrinsic speed/power tradeoff. Settling time using the  $OP295$  is under 150 $\mu$ s, but this can be improved with the  $AD820$  or  $OP284$  to about just a few microseconds, due to their much higher slew rate. The tradeoff here is power; an  $OP295$  channel with the d-to-a converter consumes about 660 $\mu$ A, while the faster  $AD820$  or  $OP284$  use more than 1mA.

Note that the output amplifier function can also be satisfied with more specialised circuitry for specific applications. For example, a buffered amplifier-pass transistor combination such as that used in Fig. 4 allows a programmable power supply with high current output characteristics to be readily implemented, by replacing the fixed reference of that configuration with the voltage variable source from the  $DAC8043$ , pin 1. By choosing the scaling of the buffer amplifier accordingly, a wide range of output swings is possible.

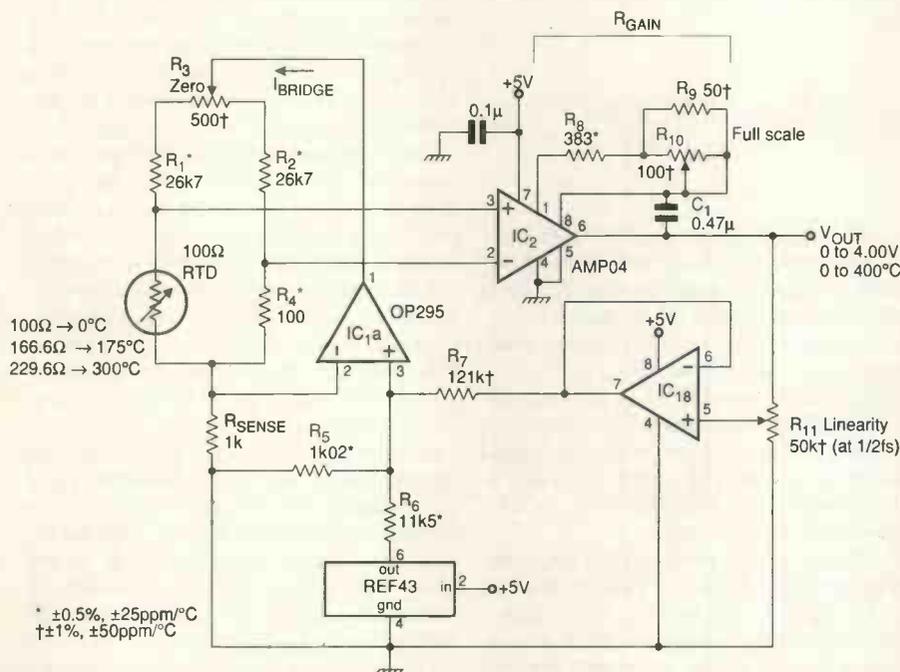


Fig. 8. Overall current drain of this thermometer design is 1.3mA. The circuit yields a 0 to 400°C output working from a 5V supply and 0 to 350°C from a 4.5V supply.

ICs to achieve serial input 12bit operation. It is scaled for a 0-4.095V output range, or 1mV/lsb. Digital inputs are ttl compatible, and the circuit uses a low component count. A number of output amplifiers can be used for  $IC_2$ , as noted below.

While the circuit is clean and straightforward, some application points are noteworthy in the interests of maximising performance. Note that with only a 5V supply, the internal n-mos switches have only 5V- $V_{REF}$  as enhancement voltage, or 3.765V with a 1.235V reference. Therefore 1.3V for  $V_{REF}$  is about as high as can be applied to the d-to-a converter operating in this fashion.

If higher  $V_{REF}$  voltages are used, the mosfet gate drive can become starved, leading to higher on resistance and output voltage non-linearity.

This circuit uses an  $DAC8043$ . Because this

is a 12bit multiplying d-to-a converter, the output voltage will be  $(D/4096) \times V_{REF}$ , where  $D$  is the 12bit digital word ranging from 0-4095. With a  $V_{REF}$  of 1.235V, unbuffered output at pin 1 of  $IC_1$  will be  $(4095/4096) \times 1.235V$  at full scale, or about 1.2347V, which is around 300 $\mu$ V/lsb.

Output amplifier  $IC_2$  brings the overall scale seen at  $V_{OUT}$  up to the desired 1mV/lsb. Gain required of  $IC_2$  for this weighing is about 3.3, and is made variable to trim out tolerances in both  $V_{REF}$  and the gain resistors. Also, for bipolar amplifiers  $IC_2$ , it helps to make the equivalent resistance of the gain divider equal to the d-to-a converter output resistance of around 11k $\Omega$ . This has been done for the  $R_{1-3}$  values shown.

Accuracy at dc, speed and power are strong-

single-supply operation, input and output coupling is of necessity via capacitors, three in the circuit itself and two more for bypassing.

Amplifier  $IC_1$  can be half of an *SSM2135* dual, an *AD820*, or half of an *AD822*, depending on the source impedance. All of these are low noise units suitable for 5V and higher single supply operation.

The *SSM2135* features a  $6nV/\sqrt{Hz}$  input noise, comparable to the popular *5532*, which does not operate optimally on low voltage single supplies. The *AD820/AD822* single/dual types have about  $12.5nV/\sqrt{Hz}$  voltage noise. Current noise of the *SSM2135* is  $0.3pA/\sqrt{Hz}$ , while the *AD820/AD822* current noise is only  $0.8fA/\sqrt{Hz}$ , due to its fet input stage. Thus the *SSM2135* is preferred for source impedances below approximately  $10k\Omega$ , and the *AD820/AD822* are generally better when the source is above  $10k\Omega$ .

To achieve lowest circuit-related noise, the  $IC_1$  gain resistance  $R_2$  is set by design to a value which has a Johnson noise  $1/3$  that of the *SSM2135*, or  $221\Omega$  ( $2nV/\sqrt{Hz}$ ). This step ensures that the noise of the amplifier will dominate at high gains with very low source resistances, rather than the adjoining circuit.

For lowest noise in the surrounding circuit, biasing must also be noiseless, that is free from noise added directly or indirectly by the biasing.<sup>3</sup> This means resistors with dc across them should have low excess noise, or be ac-bypassed. As a result,  $R_{1,5}$ , are metal film types, and  $R_{4,5}$  are bypassed. A 2.2 or 2.5V bias source is provided from  $R_{4,5}$ , which biases the output of  $IC_1$  for optimum swing. In addition,  $C_1$  and  $C_2$  are low esr types.

To provide a low source impedance for lowest noise,  $C_1$  must be larger than if chosen strictly from a time constant point of view ( $100\mu F$ ). Otherwise, current noise from a bipolar amplifier such as the *SSM2135* might produce an equivalent low-frequency voltage noise, across  $C_1$  and  $R_{SOURCE}$ .

Because of the very low current noise and bias current of the *AD820/AD822*, when they are used, this allows the input impedances to be much higher, and  $C_1$  can be correspondingly smaller ( $0.1\mu F$ ). Component values in parentheses apply to an *AD820* or *AD822*.

Gain of the stage as shown is 100 with the fixed value of  $R_2$ . However a remote gain function can be optionally provided by using the variable network,  $R_{GAIN}$ . Bandwidth of this amplifier with the *SSM2135* is about 30kHz at maximum gain, and about 20kHz with the *AD820* or *AD822*.

Apart from the source impedance choice between these two types, there are some power consumption differences; the *SSM2135* draws a quiescent current of 1.45mA/channel, while the *AD820* or *AD822* current is about  $700\mu A$ /channel.

With the two sections of the duals available, the circuit is useful as a low level preamp for multi-media or other 5V supply audio applications. Noise performance will reflect the device chosen for  $IC_1$ , and the relative source impedance. With a shorted input, the *SSM2135* measures an output noise of about

$110\mu V$  rms at a gain of 100, and thd+n was 0.022% at a 1V rms output level into a  $2k\Omega$  load. Under similar conditions, the *AD820* measures about  $200\mu V$  rms with 0.05% thd+n.

### Precision temperature sensing

Many methods of sensing temperature are available, but very high precision on single power supplies remains a challenge.

Figure 8 shows how a precision platinum resistance temperature device, or rtd, can be implemented on a single 5V supply. The rtd bridge is driven with a total regulated  $I_{BRIDGE}$  current of  $200\mu A$ . This minimises the rtd self-heating, by virtue of the  $100\mu A$  excitation. Overall circuit current drain is 1.3mA and the circuit works from supplies of 5V for a 0-400°C output, or down to 4.5V for a 0-350°C range.

The  $200\mu A$   $I_{BRIDGE}$  current passes through  $R_{SENSE}$  and is compared to the 0.2V reference voltage appearing across  $R_5$ . The  $IC_{1A}$  control amplifier is an *OP295*, which easily allows input voltages of 0.2V, and the rail-rail output provides ample headroom to drive the bridge.

At the bridge output, the common mode voltage is around 0.201V – a level difficult to handle for a conventional 5V instrumentation-amp, whether IC or discrete. In this circuit the output is amplified by  $IC_2$ , an *AMP04*. This device has an input common-mode range of 0-3.5V and an output range of 0-4.2V while operating on 5V.

Gains of 1-1000 are set by a single external resistor,  $R_{GAIN}$ . The *AMP04* gain is simply equal to  $100k\Omega/R_{GAIN}$ , so in the case here it is nominally 245. This gain times the bridge output voltage of  $38\mu V/^\circ C$  yields a  $V_{OUT}$  scale factor of  $10mV/^\circ C$ . Capacitor  $C_1$  provides a low-pass filter function in conjunction with the internal *AMP04*  $100k\Omega$  resistor, so the signal is low pass filtered above 3.4Hz.

Several factors are important in the associated circuit for best performance. All critical resistors, marked \*, should be 0.5%,  $\pm 25ppm/^\circ C$  types, or about 100 times better than the rtd temperature coefficient of  $3850ppm/^\circ C$ . Resistors  $R_{1,2}$  in particular should be same batch/same manufacturer units, with  $R_4$  also same manufacturer. These

measures help minimise differential temperature coefficients.

Gain resistor  $R_8$  should have a temperature coefficient which is low with respect to the *AMP04* coefficient of  $50ppm/^\circ C$ . Less critical resistors, market †, with smaller percentage error contributions can be more loosely controlled. All potentiometers should be multiple-turn film types.

The bridge/amplifier combination has a small amount of non-linearity, typically around 0.5%. In comparison, the rtd has a much larger non-linearity, as much as  $6^\circ C$  over a  $400^\circ C$  span, or 1.5%. Fortunately, this non-linearity can be corrected with controlled positive feedback which increases the bridge drive with increasing output. To implement this, a fraction of  $V_{OUT}$  is picked off by  $R_{11}$  (linearity), is buffered by  $IC_{1B}$ , and then is summed with the 0.2V reference voltage via  $R_7$ . With correct adjustment, this feedback cancels the rtd non-linearity.

Calibration is a relatively simple three-step process. First, care must be taken in the setting for  $0^\circ C$ , for the simple reason that the lack of a negative supply prevents this end point going through 0V.

One technique, step 1, is to substitute an exact  $100\Omega$  resistor for the rtd, or place the actual rtd in an ice bath solution, and adjust zero-setting resistor  $R_3$  until  $V_{OUT}$  begins to swing positive. Next, trim  $R_3$  in the reverse direction until  $V_{OUT}$  just stops changing, which should be zero volts.

For full-scale trim, step 2, preset  $R_{11}$  to a midpoint and substitute a  $274.04\Omega$  resistor for the rtd. Then trim  $R_9$  for 4.000V at  $V_{OUT}$ , which represents  $400^\circ C$ . For setting linearity, step 3, substitute a  $175.84\Omega$  resistor for the rtd, and trim  $R_{11}$  for 2.000V at  $V_{OUT}$ . Steps 2 and 3 should be repeated for best accuracy, as they interact.

When fully trimmed, the output errors of the circuit are within  $\pm 0.5^\circ C$  over the 0-400°C range.

### Monitoring current supply

Single supply amplifiers can be arranged to make accurate current monitors in either a negative or positive supply lead. The circuits


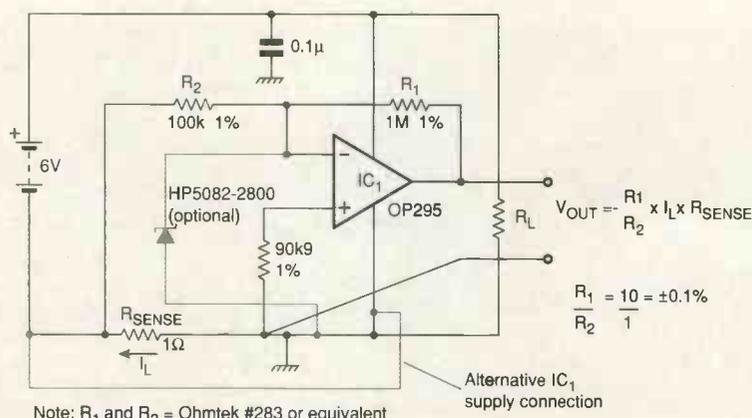


Fig. 9. In this supply-current monitor with negative-rail sensing,  $IC_1$  senses voltage across  $R_{SENSE}$ . Current through  $R_{SENSE}$  is  $I_{LOAD}$ , which equals the total supply current. Resistors  $R_{1,2}$  scale and invert voltage across  $R_{SENSE}$  to produce a positive  $V_{OUT}$ .

Fig. 10. In this positive-rail sensing supply-current monitor, IC<sub>1</sub> senses voltage across R<sub>SENSE</sub>. Voltage across R<sub>1</sub> is forced equal, and R<sub>1,2</sub> scale output voltage. The transistor shifts level and produces ground-referred output V<sub>OUT</sub>.

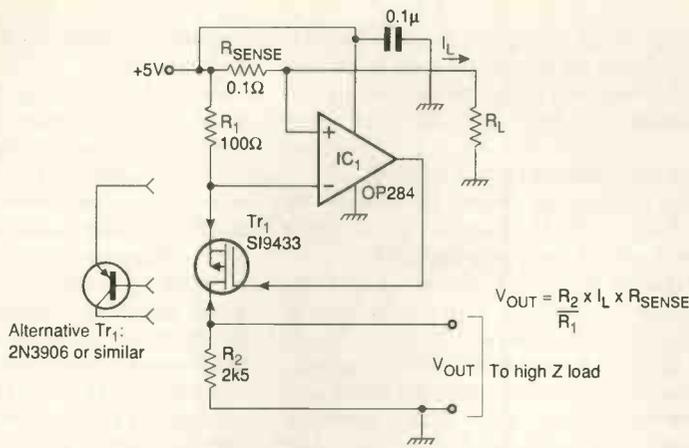

below deliver output voltages directly proportional to load current and positive with respect to supply ground. They are adaptable for wide operating current ranges.

An easy way to monitor negative rail supply current with a single supply amplifier is shown in Fig. 9. Here IC<sub>1</sub> is a section of an OP295 arranged to sense voltage drop across R<sub>SENSE</sub> in the negative supply lead. Current through R<sub>SENSE</sub> is I<sub>L</sub> – the total supply current. Resistors R<sub>1,2</sub> scale and invert the voltage across R<sub>SENSE</sub>, producing a positive output, V<sub>OUT</sub>.

Because of the ability of IC<sub>1</sub> to sense inputs close to its negative supply rail and a rail-rail output capability, the circuit responds linearly to small currents down to a V<sub>OUT</sub> level of a few millivolts. Current-to-voltage conversion scaling is set by the choice of resistor R<sub>SENSE</sub> plus the R<sub>1</sub>/R<sub>2</sub> ratio, producing 10mV/mA or 1V=100mA output scale factor as shown here.

Resistor R<sub>SENSE</sub> is adjusted proportionally for other scale factors, such as 0.1Ω for 1mV/mA, 0.01Ω for 0.1mV/mA, etc. Full scale will be essentially dictated by the supply voltage. For example the 6V supply shown allows currents to be monitored up to 600mA. Resistors R<sub>1,2</sub> should be ratio matched for lowest gain error, and stable types should be used for both these and R<sub>SENSE</sub>.

For highest performance, some other factors should be considered. For low power losses and sense errors, drop across R<sub>SENSE</sub> should be

100mV or less. As shown, the relatively low 160μA/channel OP295 supply current is part of I<sub>L</sub>, but it can be alternately bypassed around R<sub>SENSE</sub> if needed. A Schottky diode clamp is suggested for IC<sub>1</sub>, if input transients can take the summing point 0.3V or more below ground.

The circuit of Fig. 10 allows positive rail sensing, by placing the R<sub>SENSE</sub> resistor in series with the positive rail to be monitored, such as +5V, etc. This requires an op-amp which can operate with common-mode inputs near the positive rail, such as the OP284 shown for IC<sub>1</sub>.

This circuit uses the op-amp plus a high current gain transistor such as Tr<sub>1</sub> to sense the drop across R<sub>SENSE</sub>, which the loop duplicates as an equal drop across R<sub>1</sub>. With the connection of a high gain Tr<sub>1</sub> as a follower, the drain current is then equal to the current in R<sub>1</sub>. Output, V<sub>OUT</sub>, is then proportional to I<sub>L</sub>, and referred to the common end of R<sub>2</sub>, or ground.

Interestingly, the overall expression for V<sub>OUT</sub> follows the same form as that of Fig. 9. In this case, with 0.1Ω for R<sub>SENSE</sub> and R<sub>1,2</sub> as shown, the sensitivity is set up as 2.5V/A.

Caveats similar to those of Fig. 9 apply to selecting R<sub>SENSE</sub> for a full scale drop of less than 0.1V, and the general precision of R<sub>1,2</sub>. The op-amp should also have a low offset voltages, which is true in the case of the OP284. Additional caveats apply to the gain of Tr<sub>1</sub>, which ideally should be a mosfet such

as the low threshold device listed.

Since the effective β of an fet is near infinite, the entire current passing through R<sub>1</sub> also passes through R<sub>2</sub>, and develops an accurate output. Note that since this is a current output, R<sub>2</sub> can be returned to a remote load for best accuracy.

At the expense of accuracy, the circuit can be simplified by substituting a high-gain PNP transistor such as the 2N3906 for Tr<sub>1</sub>. Note that since the output of this circuit is unbuffered, any shunt resistance across R<sub>2</sub> will change the overall scale factor. Therefore V<sub>OUT</sub> should drive a high impedance input such as a buffer stage, or a non-loading a-to-d converter input.

**A composite instrumentation-amp**

As noted earlier, high performance linear circuits operating from 5V and lower supplies are common in many modern designs. While there are many precision rail-to-rail op amps, plus some good single-rail compatible in-amps such as the AMP04 (above), it is generally true that achieving the very highest levels of performance today requires the use of devices expressly designed for conventional dual-supply operation.

It may seem a contradiction in terms to make such a statement, however, as will seen, clever interfacing allows such a precision dual supply device to provide accurate, high dynamic range outputs while operating on a single 5V supply.<sup>4,5</sup>

A technique allowing high precision with single-rail operation takes advantage of the fact that popular transducers such as strain gauge bridges provide an output signal which is naturally centred around the mid-point of the excitation voltage. When the supply rail is used as excitation for these bridge type circuits, the inputs of the signal conditioning in-amp then see a common-mode voltage equal to half the rail voltage.

For single 5V rail operation, this implies a common-mode level of 2.5V, which the amplifier sees as equal to a common-mode voltage of zero when operated on ±2.5V supplies. What is needed to implement this type of system is an in-amp 'front end' which has very high precision on a 5V supply, plus an

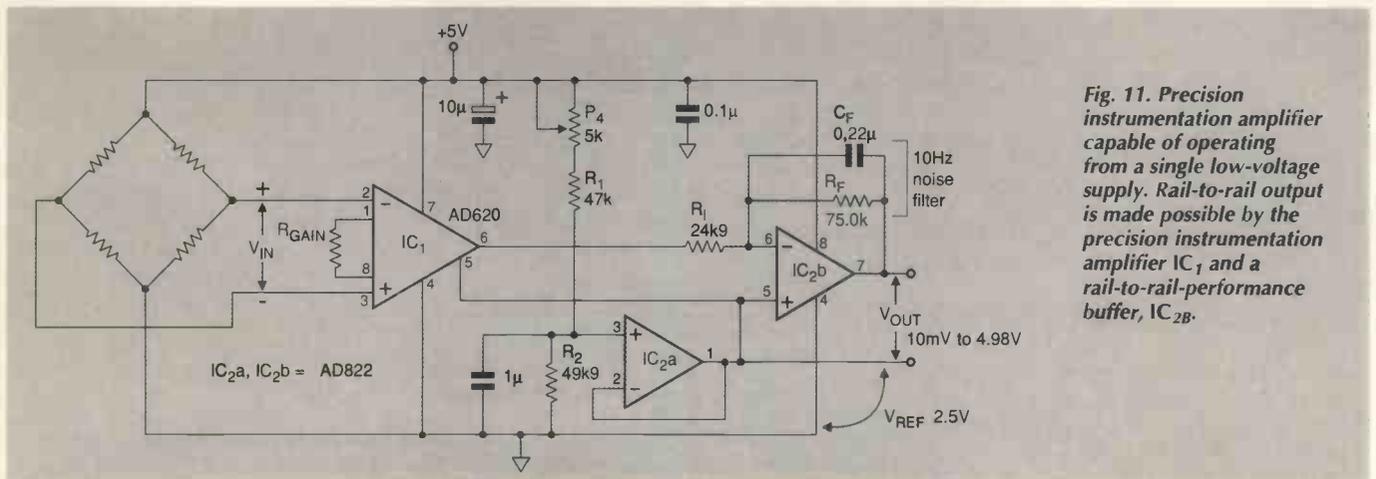


Fig. 11. Precision instrumentation amplifier capable of operating from a single low-voltage supply. Rail-to-rail output is made possible by the precision instrumentation amplifier IC<sub>1</sub> and a rail-to-rail-performance buffer, IC<sub>2B</sub>.

output buffer stage which can be set up to provide rail-to-rail output. This greatly enhances overall dynamic range and dc precision.

Fig. 11 shows such a high performance in-amp which operates from a single +5V rail, and senses signals from a bridge. The circuit uses the AD620 IC in-amp for the input stage, IC<sub>1</sub>. It also uses a dual IC for the second stage, IC<sub>2A,B</sub> – sections of an AD822. The IC<sub>2B</sub> stage is used for voltage scaling and buffering, providing a rail-to-rail output swing. The stage around IC<sub>2A</sub> is a unity-gain buffer for V<sub>REF</sub>, which drives the reference input of IC<sub>1</sub> and also provides an 'elevated ground' potential for circuits following.

Resistors R<sub>1,2</sub> form a voltage divider, nominally splitting the supply rail to around 2.5V, with optional adjustment via trimmer P<sub>1</sub>. This voltage is applied to the input of IC<sub>2A</sub>, using the fet input AD822, thus providing buffering and a low-impedance source for the AD620's output reference port at pin 5. Note that a low source resistance here is critical to maintain high common-mode rejection, so this buffer stage is important.

The other half of IC<sub>2</sub> is connected as a fixed inverting gain stage which scales the signal by a factor of three. This guarantees that a 5V pk-pk or 'rail-to-rail' output from the IC<sub>2B</sub> stage will only need a 1.67V pk-pk drive from IC<sub>1</sub>. This output swing is well within the AD620's capability, which in turn ensures highly linear operation from the IC<sub>1</sub> stage.

As is noted in the diagram, V<sub>OUT</sub> is referenced to V<sub>REF</sub>, as opposed to power ground.

The active V<sub>OUT</sub> range of 0.01-4.98V on a 5V supply essentially means the circuit processes outputs of up to ±2.5V linearly with respect to the +2.5V elevated ground. Over an operating gain range of 10-1000 and the rail-rail signal swing noted, the linearity of this composite in-amp is better than 0.005%.

Gain G of the composite amplifier is the product of the IC<sub>1</sub> and IC<sub>2B</sub> stage gains, or simply,

$$G = \left[ \frac{49.4k\Omega}{R_{GAIN}} + 1 \right] \left[ \frac{R_F}{R_I} \right]$$

In this expression the 49.4kΩ value is an internal resistance of the AD620. Resistors R<sub>F</sub> and R<sub>I</sub> are the resistances around the IC<sub>2B</sub> gain stage, and R<sub>GAIN</sub> is the user selected gain set resistor connected between pins 1-8 of IC<sub>1</sub>. With a fixed gain of 3 in stage IC<sub>2B</sub>, it turns out that standard 1% values for R<sub>GAIN</sub> allow convenient overall gains, such as 21.5kΩ ⇒ G=10, 1.53kΩ ⇒ G=100, etc.

In this +5V powered application, the total input common-mode voltage applied to the inputs of the AD620 can be in the range of +2.1V to +3.7V for full rated performance. Operating this circuit then at an overall gain of 10, the common-mode input voltage span is such that the inputs can readily accommodate the required 0.5Vpk-pk signal centred about a nominal 2.5V level.

The inverting configuration was chosen for the output buffer to facilitate system output offset voltage adjustment by summing cur-

rents into the buffer's feedback summing node. These offset currents can be provided by an external d-to-a converter, or from a resistor connected to a reference voltage.

The AD822 rail-to-rail output stage exhibits a very clean transient response, not shown, and a small-signal bandwidth over 100kHz for gain configurations up to 300.

To reduce noise effects, an optional capacitor C<sub>F</sub> is recommended in this IC<sub>2B</sub> stage. This forms a simple low pass filter in conjunction with R<sub>F</sub>, with the values shown placing the corner frequency at 10Hz. Also, to help minimise the effects of high frequency input-stage rectification, additional common-mode filtering can be used prior to the IC<sub>1</sub> inputs. ■

#### References

1. Walt Kester & ADI Staff, 'Practical Analog Design Techniques', Analog Devices Seminar Notes, 1995.
2. Walt Jung, 'Low Dropout References and Regulators', within Chapter 9 of Ref 1.
3. Motchenbacher, F. Fitchen, 'Low-Noise Electronic Design', Wiley, New York, 1973.
4. Lew Counts, Product Line Director, Advanced Linear Products, Analog Devices, Inc., personal communication, 1995.
5. Adolfo Garcia, 'Single Supply Amplifiers', Chapter 1 within Ref 1.
6. C. Kitchin and L. Counts, 'Instrumentation Amplifier Application Guide', Analog Devices, Inc., 1991.

## THE COMPLETE EMC EMISSIONS TEST KIT

All you need for effective pre-qualification  
EMC testing



The EMC regulations will be in force by the end of 1995! Pre-qualification testing has been acknowledged as a sensible and effective strategy for reducing timescales and costs involved with compliance. The RF-Kxx range of test kits provides all you need to test for all RF emissions, conducted and radiated, over the range 10KHz to 500MHz.

#### Specific features include:

- Compliance to relevant CISPR specifications
- PC interface and software
- Precise frequency analysis
- Comparison against limits

#### All kits include:

- Powerful RF Spectrum Analyser
- Broadband pre-amplifier
- Near field probe set (E&H)
- Far field antenna and stand
- All necessary cables
- Definitive text book – EMC for Designers



#### Options:

- LISN for mains conducted measurement
- Serial link and software for PC

#### The complete kit for:

- Checking existing products
- Refining circuit and screening design
- Location of hot spots and leaks
- Monitoring of problem frequencies
- Pass the formal test first time round
- Documenting results for Technical files
- Monitoring production performance

Prices for complete kits start from under £2000

RING FOR COMPLETE DETAILS LAPLACE INSTRUMENTS LTD TEL: 01692 500777 FAX: 01692 406177



# Add senses to

Plugging into a pc printer port, these two a-to-d converter interfaces provide a simple and economical way of providing virtual instrumentation and data logging.

Virtual instruments – computer based test instruments – comprise two main components. One is interface hardware connecting to the computer and the other software that simulates the functions of the instrument. By simply changing the software, the computer can become an oscilloscope, voltmeter or spectrum analyser.

Consider three different test instruments - a digital storage scope, spectrum analyser and a logic analyser. Although they all perform different functions, each of these expensive items contain much of the same inside – a display, keypad, processor and power supply.


Rather than buy three separate displays, three keypads and three power supplies, it makes sense to use those you already have in your computer. All the hardware you need to buy is a data acquisition interface.

With a disk drive to save waveforms and a printer already connected, virtual instruments give additional advantages.

The division between data logging and virtual instrumentation is fuzzy. Often the same hardware can be used for both. The *ADC-11* described here was designed primarily for data logging with *PicoLog* software, but it can also be used with *PicoScope* software to create a simple oscilloscope. Similarly the *ADC-100* was designed as a virtual instrument using *PicoScope*, but can also be used as a data logger with *PicoLog*.
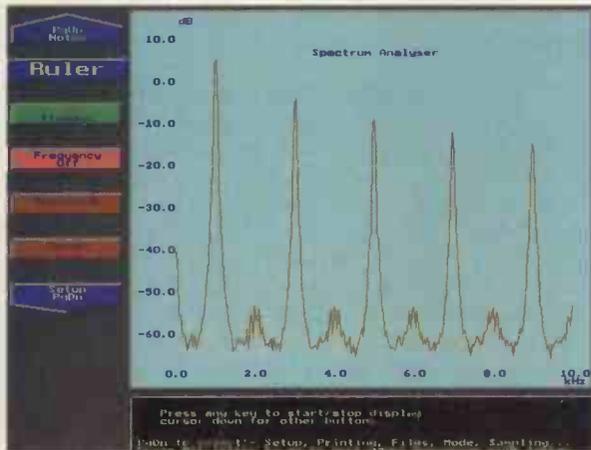
## Pico data converters

Most data acquisition devices are plug in cards. Pico devices differ in that they plug directly into either the serial or parallel port, depending on the model, and require no power supply. This means that they can be installed in seconds and are ideal for use with portable personal computers.



Software for creating a spectrum analyser is primarily designed for use with the faster *ADC-100*, but it can also be applied with the *ADC-11* to form a simple oscilloscope, frequency counter, voltmeter and spectrum analyser.

Available software includes *PicoScope* for use as a Virtual Instrument and *PicoLog* for datalogging. For users wanting to write their own software, C, Pascal, Visual Basic and Windows DLL drivers are supplied as standard.

## Data logging with the *ADC-11*

The *ADC-11* provides eleven channels of analogue input in a case slightly larger than a matchbox. Each channel accepts inputs in the range 0 to 2.5V and provides a resolution of 1 part in 1023, i.e. 10bits.

Basic accuracy of the device is 1% and it can take up to 15,000 samples a second. A digital output is also available for control/alarm functions, which can alternatively provide power for sensors such as thermistors.

## The *ADC-100* virtual Instrument

The *ADC-100* has been described as 'a complete electronics lab in your pc'. With the supplied *PicoScope* software, you can use your pc to emulate the following instruments:

- dual-channel storage oscilloscope, 100 $\mu$ s/div to 5s/div
- XY mode oscilloscope
- spectrum analyser, 0-50kHz
- voltmeter, ac/dc or dB
- frequency meter, 0-30kHz.

Plugging directly into a pc parallel port, the *ADC-100* offers both a high sampling rate of 100kHz and a high resolution of 12bits. Nine input ranges, providing  $\pm 50$ mV to  $\pm 20$ V full scale, enable the unit to be directly connected to a wide range of signals.

As well as its use as a general purpose laboratory instrument, the *ADC-100* has proved

popular in many diverse fields. For example they are used in garages for tracing faults in modern car electronics, ie ignition, fuel injector and ABS circuits. In addition, they prove invaluable to audio engineers as the spectrum analyser covers the whole audible range.

Spectrum-analyser capabilities of the *ADC-100* a-to-d converter together with the *PicoScope* software are illustrated above. This same software also turns the pc into a dual-channel or XY-mode oscilloscope, voltmeter or frequency counter. The spectrum analyser display shows harmonics of a square wave.

## Battery discharge

An example of simply measuring a voltage is plotting the discharge curve of one or more batteries. This is often used as a test to see if rechargeable batteries are coming to the end of their useful life, or to compare the capacity of two different types.

For this example two different types of 6V mobile phone batteries were fully charged, then discharged, while being monitored by the *ADC-11*. *PicoLog* software was used to show a real time graph of the discharge.

The attenuator needed is shown, together with a graph of the results. Resistor  $R_1$  is used as a load resistor to discharge the battery while  $R_{2,3}$  form a

# your PC



## Monitoring temperature

Temperature is the most commonly measured 'real world' signal in data logging. The *ADC-11* works well with either thermistors or semiconductor sensors. For a thermistor, only a simple potential divider circuit is needed.

A common semiconductor temperature sensor is National Semiconductors *LM35*, which gives an output of 10mV/°C. As its power requirements are low, it can be powered using the *ADC-11*'s digital output. With an *ADC-11*, you can measure temperatures in the range 2°C to 110°C with an accuracy of better than 1°C.

An optional terminal board for the *ADC-11* has space for an *LM35* to allow quick and easy connection. Once connection is made, the *PicoLog* software can display and record the temperature. The circuit for connecting the *LM35* to the *ADC-11* is shown.

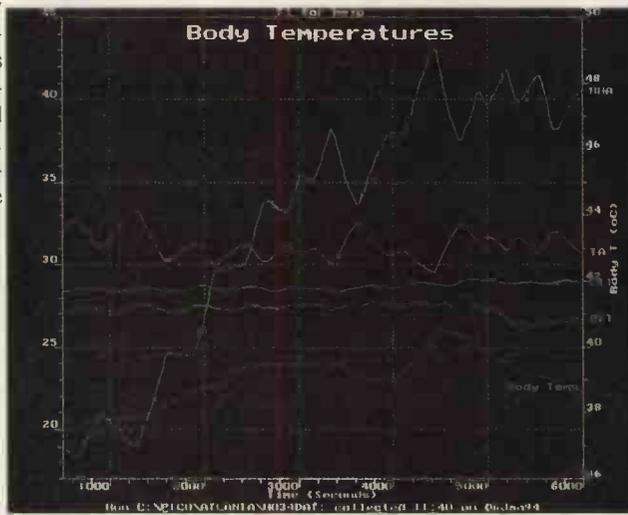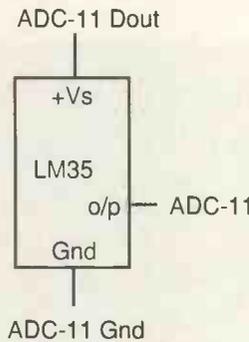*Monitoring body temperature on the pc is simply a matter of plugging the a-to-d converter into the printer port and wiring in a sensor.*




## Current loop sensing

Most industrial sensors have current-loop outputs. Normally these are 4-20mA loops. A value of 4mA corresponds to a zero signal and 20mA corresponds to full scale.

Currents below 4mA or above 20mA signal error conditions, such as a failed sensor or broken wire. *PicoLog*'s alarm functions can be used to give warning of these. Current loops are used rather than voltage signals as they are less subject to electrical noise and unaffected by cable length.


The easiest way to monitor a current is to measure the voltage developed across a resistor inserted into the circuit. Here, a 120Ω resistor allows currents just over 20mA to be monitored. Remember that the *ADC-11*'s 0V is effectively mains earth, assuming a mains powered pc. As a result, check with the sensor manufacturer whether it is permissible to ground part of the current loop.

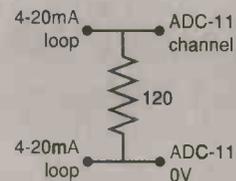*In 4-20mA loop systems, appearance of currents below 4 or above 20mA signal an error condition. Via one resistor, Pico allows 4-20mA monitoring on the pc, together with an alarm trigger when currents above 20mA are detected.*



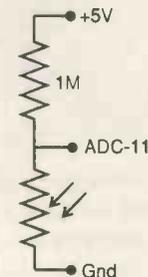
## Detecting light levels

Light levels can be measured simply by connecting an *ORP12* or similar light-dependent resistor. In bright light, this device has a resistance of a few hundred ohms, so the voltage fed into the *ADC-11* is very low. In total darkness the resistance rises to several megaohms causing voltage to rise.



*An ORP12 or similar connected to the pc via the a-to-d interface allows a wide spread of light level to monitored at low cost.*

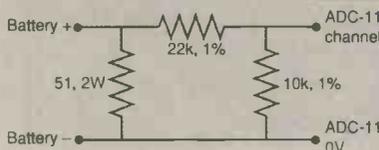simple potential divider to increase the *ADC-11* input range from 2.5V to 8V. The plot shows that the nickel-metal-hydride battery, although much smaller than the nickel-cadmium battery, has virtually the same capacity.



*Monitoring battery charge or discharge is simply a matter of connecting the battery terminals to the a-to-d converter via a suitable potential divider.*

## Converting humidity to frequency


Two types of humidity sensor are available – resistive and capacitive. Resistive sensors are easier to use but tend to be less accurate.

The interface shown is based on a Phillips capacitive sensor, part no 2322 691 90001. If a c-mos 555 timer is used, the circuit can be powered from the ADC-11 digital output. Alternatively, an external 5V supply is required.


PicoLog software supplied with the ADC-11 has the ability to record the frequency of the input signal. This is useful for sensors that generate pulse outputs such as flow sensors or for car engine rev/min measurement.

The humidity sensor is used as the timing capacitor in a standard 555 circuit. Output is a square wave whose frequency is related to humidity. Response of the humidity sensor is non linear, so a lookup table is required to convert frequency to a humidity proportionally.

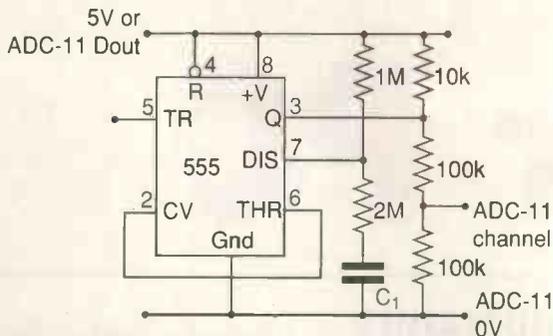The photograph on the right shows a plot from PicoLog displaying humidity, temperature and light levels from the described circuits.



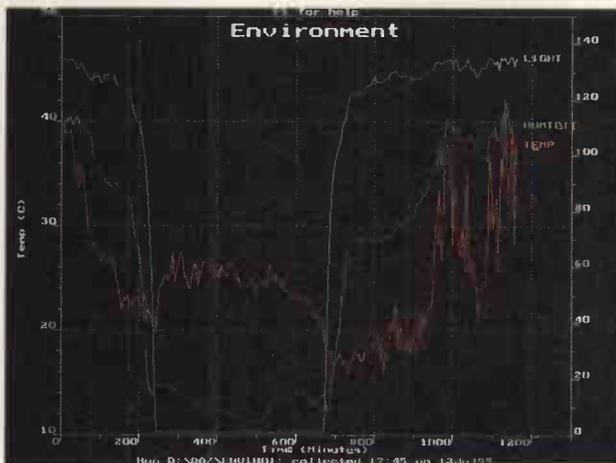Capacitive humidity sensors are more difficult to use than resistive ones, but, they are also more accurate. This one changes output frequency of the astable timer for subsequent detection on the pc via the ADC-11.



Bringing together three of the sensors described here produces a versatile but low-cost data-logging system.

## Exclusive EW+WW reader special

30% discount on printer-port data loggers and virtual instruments

The Pico Technology ADC-11 and ADC-100 are versatile a-to-d converters for the PC – outlined in this issue. These printer-port plug-ins are supplied complete with software and have a normal list price of £95 and £219 respectively, exclusive of VAT and postage. While stocks last, EW+WW readers can obtain the ADC-11 for only £66.50, and the ADC-100 for £153.30, excluding VAT and postage.



ADC-11 has eleven analogue input channels and takes up to 15000 samples a second. It plugs directly into the pc printer port. This 10bit converter takes inputs in the range 0 to 2.5V and has a digital alarm output. Data-logging software is supplied with the ADC-11 as standard.

### Order form

Please Send me:

\_\_\_ ADC-11 @ £66.50                    £  
 \_\_\_ ADC-100 @ £153.30                £

### Postage and packing

(UK)    £ 2.00  
 (overseas)                                 £ 5.50

VAT(17.5%if applicable)                £

**Total**                                        £

Please make cheques/POs payable to Reed Business Publishing Group and send to EW+ WW, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Credit card orders, including address, card type, number and expiry date can be faxed on 0181-652 8956, or e-mailed via jackie.lowe@rbp.co.uk



ADC-100 is a high-performance 100kHz sampling a-to-d converter that plugs into the pc printer port via its supplied lead. Resolution is 12 bits and nine input ranges cover 50mV to 20V full-scale. Each unit is shipped complete with virtual instrument software for turning your pc into a spectrum analyser, frequency counter, dvm or storage oscilloscope. Data-logging software is also included.

Surplus always wanted for cash!

# THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS


Surplus always wanted for cash!

## LOW COST PC's - ALL EXPANDABLE - ALL PC COMPATIBLE

### SPECIAL BUY

AT 286

40Mb HD + 3Mb Ram

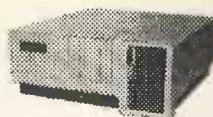


LIMITED QUANTITY only of these 12MHz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!  
Order as HIGRADE 286 **ONLY £149.00 (E)**  
CALL FOR QTY DISCOUNTS

Optional Fitted extras: VGA graphics card	£29.00
1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb)	£24.95
NE2000 Ethernet (thick, thin or twisted) network card	£49.00

### PC SCOOP

COMPLETE  
COLOUR SYSTEM  
ONLY £79.00

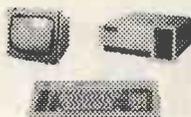

A massive bulk purchase enables us to bring you a COMPLETE ready to run colour PC system at an unheard of price! The Display Electronics PC99 system comprises of fully compatible and expandable XT PC with 256k of RAM, 5 1/4" 360k floppy disk drive, 12" CGA colour monitor, standard 84 key keyboard, MS DOS and all connecting cables - Just plug in and go!! Ideal students, schools or anybody wishing to learn the world of PC's on an ultra low budget. Don't miss this opportunity. Good used condition - Fully guaranteed for 90 Days. £79.00 (E)  
Order as PC99COL

Optional Fitted extras: 640k RAM	£29.00
2nd floppy drive, specify 5 1/4" 360k or 3 1/2" 720k	£29.95

Above prices for PC99 offer ONLY.

## 19" RACK CABINETS

Superb quality 6 foot 40U  
Virtually New, Ultra Smart  
Less than Half Price!



Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:

OPT Rack 1 Complete with removable side panels.	£335.00 (G)
OPT Rack 2 Rack, Less side panels	£225.00 (G)

## 32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features full slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W)



Sold at LESS than a third of makers price !!

A superb buy at only £195.00 (G)

Over 1000 racks in all sizes 19" 22" & 24" 3 to 44 U. Available from stock !!  
Call with your requirements.

## TOUCH SCREEN SYSTEM

The ultimate in 'Touch Screen Technology' made by the experts - MicroTouch - but sold at a price below cost !! System consists of a flat translucent glass laminated panel measuring 29.5 x 23.5 cm connected to an electronic controller PCB. The controller produces a standard serial RS232 or TTL output which continuously gives simple serial data containing positional X & Y co-ordinates as to where a finger is touching the panel - as the finger moves, the data instantly changes. The X & Y information is given at an incredible matrix resolution of 1024 x 1024 positions over the entire screen size !! A host of available translation software enables direct connection to a PC for a myriad of applications including: control panels, pointing devices, POS systems, controllers for the disabled or computer un-trained etc. Imagine using your finger with 'Windows', instead of a mouse !! (a driver is indeed available !!) The applications for this amazing product are only limited by your imagination!! Complete system including Controller, Power Supply and Data supplied at an incredible price of only: £145.00 (B)  
Full MICROTOUCH Software Support Pack and Manuals for IBM compatible PC's £20.95 RFE - Tested

## LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible.  
Order as: ABOVE CARD £59.95 (A1)  
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data.  
Order as: XT RAM UG. 256k. £32.95 or 512k £38.95 (A1)

### SIMM SPECIALS

1 MB x 9 SIMM 9 chip 120ns	Only £19.50 (A1)
1 MB x 9 SIMM 3 chip 80 ns	£23.50 or 70ns £26.00 (A1)
1 MB x 9 SIMM 9 chip 80 ns	£22.50 or 70ns £28.00 (A1)
4 MB 70 ns 72 pin SIMM with parity	Only £105.00 (A1)

SPECIAL OFFER - INTEL 486-DX33 CPU £79.99 (A1)

## PHILIPS - LOW COST PRINTERS

A masterpiece of engineering, the PHILIPS model NMS 1436 fully featured MULTIMODE matrix printer packs a host of features into a unit weighing just over 4kg and measuring only 40 x 12 x 28 Cml Fully Epson compatible with adjustable paper tractor which accepts upto 9.5" sprocket fed paper and adjusts down to handle the smallest letters. The 9 needle head produces Near Letter Quality in a host of fonts and type sizes and in draft mode 'whizzes' along at 120 characters per second! Many other features include most European character sets, IBM, EPSON, MSX & Prestel emulations. Good used condition, IBM Cable £6.95  
Only £49.95 (B)

## FLOPPY DISK DRIVES 3 1/2" - 8"

5 1/4" from £22.95 - 3 1/2" from £24.95

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported on your PC).

3 1/2" Panasonic JU363/4 720K or equivalent	£24.95 (B)
3 1/2" Mitsubishi MF355C-L. 1.4 Meg. Laptops only*	£36.95 (B)
3 1/2" Mitsubishi MF355C-D. 1.4 Meg. Non laptop	£29.95 (B)
5 1/4" Teac FD-55GFR 1.2 Meg	£29.95 (B)
5 1/4" BRAND NEW Mitsubishi MF501B 360K	£22.95 (B)

* Data cable included in price.	
Shugart 800/801 8" SS refurbished & tested	£195.00 (E)
Shugart 851 8" double sided refurbished & tested	£250.00 (E)
Mitsubishi M2894-63 8" double sided NEW	£275.00 (E)
Mitsubishi M2896-63 8" DS slimline NEW	£285.00 (E)

Dual 8" drives with 2 mbyte capacity housed in a smart case with built in power supply. Ideal as exterior drive! £499.00 (F)

## HARD DISK DRIVES


End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte of hard disk storage! Full Industry standard SMD interface. Ultra hi speed data transfer and access time, replaces Fujitsu equivalent model. Complete with manual. Only £299.00 (E)

3 1/2" FUJI FK-309-26 20mb MFM I/F RFE	£59.95 (C)
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE	£69.95 (C)
3 1/2" CONNER CP3044 40mb IDE I/F (or equiv.) RFE	£89.00 (C)
3 1/2" RODIME R03057S 45mb SCSI I/F (Mac & Acorn)	£99.00 (C)
5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE	£49.95 (C)
5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb	£69.95 (C)
5 1/4" CJD 94205-51 40mb HH MFM I/F RFE tested	£69.95 (C)
8" FUJITSU M2322K 160Mb SMD I/F RFE tested	£195.00 (E)

Hard disc controllers for MFM, IDE, SCSI, RLL etc. from £16.95
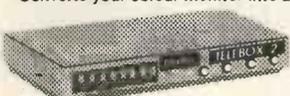
## THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers\* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable off air UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. TELEBOX ST for composite video input type monitors £34.95  
TELEBOX STL as ST but with integral speaker £37.50  
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95  
For overseas PAL versions state 5.5 or 6 mhz sound specification. \*For cable / hyperband reception Telebox MB should be connected to a cable type system. Shipping code on all Teleboxes is (B)

## FANS & BLOWERS

MITSUBISHI MMF-D6D12DL 60x60x25 mm 12v DC	£4.95 10 / £42
MITSUBISHI MMF-09B12DH 92x92x25 mm 12v DC	£5.95 10 / £53
PANCAICE 12-3.5 92x92x18 mm 12v DC	£7.95 10 / £69
EX-EQUIP 120 x 38mm AC fans - tested specify 110 or 240 v	£6.95
EX-EQUIP 80 x 38mm AC fans - tested specify 110 or 240 v	£5.95
WERO rack mount 1U x 19" fan tray specify 110 or 240v	£45.95 (B)
IMHO B26 1900 rack mnt 3U x 19" Blower 110/240v NEW	£79.95

Shipping on all fans (A), Blowers (B), 50,000 Fans Ex Stock CALL

## IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK

5,000,000 items EX STOCK

For MAJOR SAVINGS - Send SAE or CALL FOR LATEST LIST

Issue 13 of Display News now available - send large SAE - PACKED with bargains!



**LONDON SHOP**  
Open Mon - Sat 9:00 - 5:30  
215 Whitehorse Lane  
South Norwood  
On 68A Bus Route  
N. Thornton Heath &  
Selhurst Park SR Rail Stations

**ALL MAIL & OFFICES**  
Open Mon-Fri 9.00-5.30  
Dept WW. 32 Biggin Way  
London Norwood  
Upper SE19 3XF

**NEW DISTEL ©**  
The Original  
FREE On line Database  
Info on 15,000+ stock items!  
COMING SOON !!

**ALL ENQUIRIES**  
**0181 679 4414**  
FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bond Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL! Scotland surcharge CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1995. E & O.E 6/5

# APPLICATIONS

Please mention Electronics World + Wireless World when seeking further information

## Converting at video-speed without s&h circuitry

This high speed a-to-d flash converter is based on the *VP0158* from Gec Plessey, which requires no preceding sample and hold stage. Operating from a single 5V supply, the device is capable of digitising analogue signals with frequencies up to the Nyquist limit at a conversion rate of 25MHz.

Output data is available in four possible 8-bit formats, selectable via two digital control inputs, giving either true or inverted code in binary or offset twos' complement.

The typical application circuit shown is designed to accept a 1V pk-pk signal. Conditioning circuitry level shifts and multiplies the input signal to provide the converter's recommended 2V pk-pk drive

signal, biased at 4.0V for optimum performance.

The analogue input amplifier, an *AD842* or similar, should be a wideband, high slew rate op-amp since it drives the  $A_{in}$  inputs directly. This device provides the necessary gain, offset and low impedance drive. A stable voltage level is needed for both input offset and gain control, in this case provided by a *REF12Z* micro-power reference.


The *VP1058* requires an external clock applied to the CONV input to determine the conversion sampling rate. This input synchronises the sampling, conversion and output stages of the devices.

Features of the chip include a 60MHz

-3dB analogue input bandwidth, ttl compatible, digital i/o, and low power consumption of typically 670mW.

This application is taken from the digital video section of GEC Plessey's new *Digital video & digital signal processing IC handbook*. Further sections in the book cover dsp building blocks, algorithm-specific dsp chips and video compression.

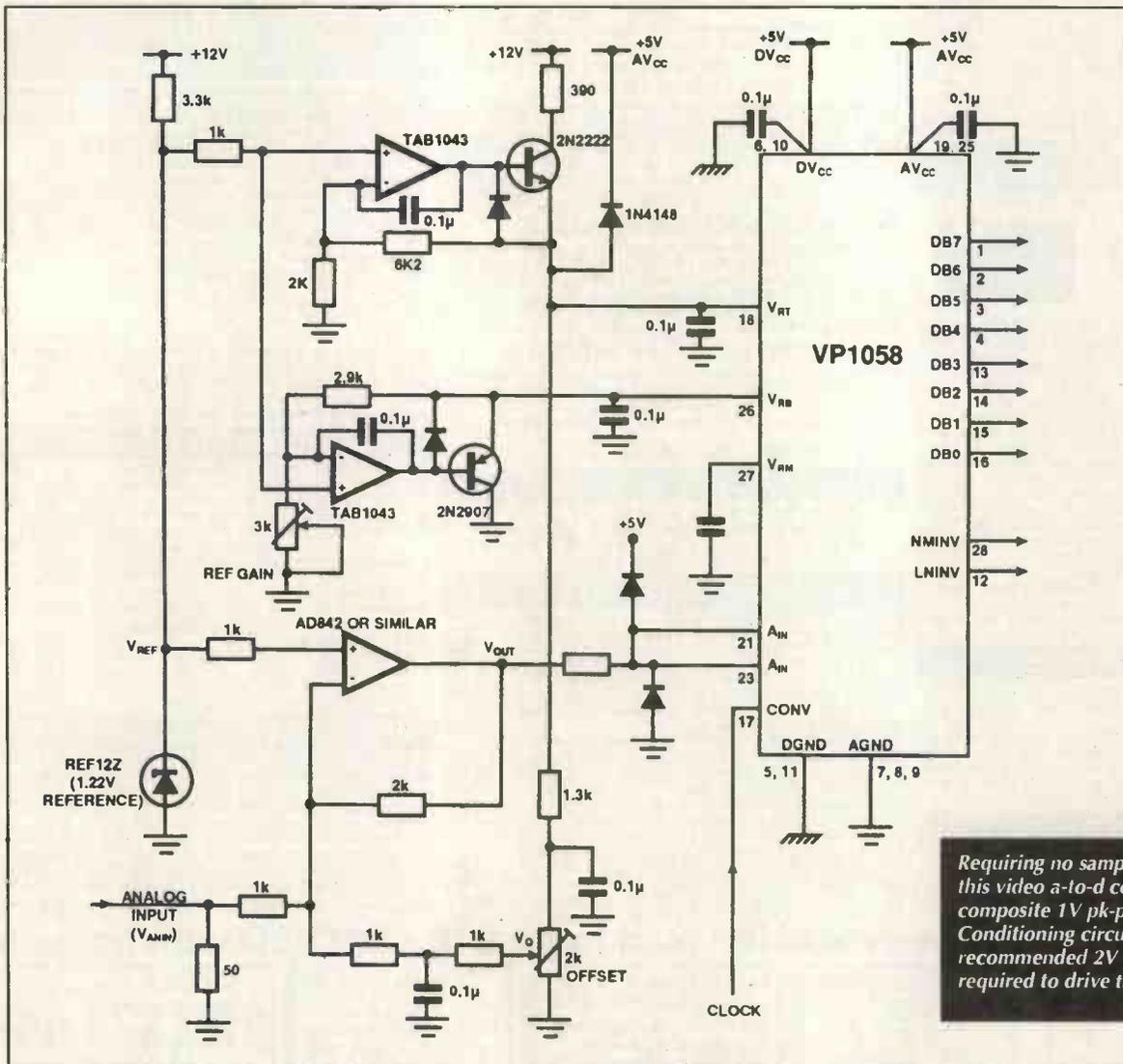*GEC Plessey Semiconductors, Unit 1, Crompton Road, Groundwell Industrial Estate, Swindon, Wiltshire, SN2 5AF. Tel 01793 518527/518566, fax 01793 518582.*



# GRANDATA LTD

K.P. HOUSE, UNIT 15, POP IN COMMERCIAL CENTRE,  
SOUTHWAY, WEMBLEY, MIDDLESEX, ENGLAND HA9 0HB

Telephone: 0181-900 2329 Fax: 0181-903 6126

OPEN Monday to Saturday.

Times: Mon-Fri 9.00-5.30 Sat 9.00-2.00

PLEASE PHONE US FOR TYPE NOT LISTED HERE AS WE ARE  
HOLDING 30,000 ITEMS AND QUOTATIONS ARE GIVEN FOR  
LARGE QUANTITIES

Please send £1 P&P and VAT at 17.5%. Govt, Colleges, etc.  
Orders accepted. Please allow 7 days for delivery. Prices quoted  
are subject to stock availability and may be changed without notice.  
TV and video parts sold as replacement parts.

Access & Visa Card accepted

WE STOCK TV AND VIDEO SPARES, JAPANESE TRANSISTORS AND  
TDA SERIES. PLEASE RING US FOR FURTHER INFORMATION.

## TRANSISTORS

Part	Price	Part	Price	Part	Price	Part	Price	Part	Price	Part	Price	Part	Price	Part	Price
AA532	9p	BD265	45p	BFY90	45p	MJ2501	100p	2N2102	50p	7815	25p	TIC236D	85p	AN315	210p
AC107	40p	BD267	45p	BLY48	85p	MJ2955	55p	2N2218A	24p	7818	25p	12A400V		AN316	350p
AC125	30p	BD269	45p	BR100	14p	MJ3000	100p	2N2219A	24p	7824	25p	TIC246D	105p	AN360	100p
AC126	30p	BD278	45p	BR103	37p	MJ3001	100p	2N2221	23p	7905	25p	16A400V		AN362	140p
AC127	30p	BD311	100p	BR303	85p	MJE29A	30p	2N2222	23p	7906	30p	TIC253D	190p	AN366	150p
AC128K	40p	BD314	100p	BS74	33p	MJE30A	30p	2N2369	15p	7908	30p	20A400V		AN368	150p
AC141K	45p	BD315	150p	BSX20	15p	MJE340	25p	2N2484	15p	7912	30p	TIC263D	205p	AN3312	350p
AC176	22p	BD317	150p	BT100A	70p	MJE350	80p	2N2646	40p	7915	30p	25A400V		AN3821K	600p
ACY18	48p	BD331	40p	BT106	180p	MJE520	30p	2N2904	20p	7918	30p			AN3822K	600p
ACY19	48p	BD332	40p	BT108	150p	MJE520	30p	2N2905	20p	7924	30p			AN3900K	300p
AD149	60p	BD333	40p	BT119	100p	MPB112	45p	2N2906	18p	7924	30p			AN3991K	400p
AF125	50p	BD362	60p	BT146	99p	MPSA06	15p	2N2907	18p	7924	30p			AN5256	150p
AF139	30p	BD370	30p	BTY79	140p	MPSA13	15p	2N3019	28p	7924	30p			AN5033	400p
AF239	30p	BD371	30p	BU105	80p	MPSA20	15p	2N3053	18p	7924	30p			AN5132	250p
BB1058	18p	BD410	50p	BU108	100p	MPSA42	15p	2N3054	18p	7924	30p			AN5150	400p
BB2058	24p	BD433	30p	BU110	90p	MPSA47	15p	2N3055	38p	7924	30p			AN5150	400p
BC107	8p	BD434	30p	BU111	100p	MPSA92	20p	2N3055	38p	7924	30p			AN5150	400p
BC108	8p	BD435	30p	BU122	60p	MPSA93	20p	2N3072	9p	7912	35p			AN5262	175p
BC109	8p	BD437	28p	BU126	65p	MR510	35p	2N3703	9p	7915	35p			AN5265	80p
BC140	20p	BD438	36p	BU180	100p	MR856	36p	2N3704	9p	LM309K	100p			AN5352	600p
BC142	20p	BD439	36p	BU184	100p	OC28	350p	2N3705	9p	LM317T	100p			AN5411	450p
BC143	20p	BD440	36p	BU204	65p	OC29	250p	2N3707	18p	LM323K	350p			AN5421	150p
BC147	8p	BD441	40p	BU205	70p	OC35	350p	2N3707	18p	79H08K	800p			CA3130S	420p
BC149	8p	BD443	40p	BU206	70p	OC36	250p	2N3710	12p	79H12K	70p			CA3134E	200p
BC159	8p	BD534	38p	BU208	70p	OC45	50p	2N3711	12p	79H8K	800p			BT106	180p
BC160	30p	BD535	38p	BU208A	75p	OC200	180p	2N3771	85p	BT119	100p			AN5520	550p
BC171	10p	BD536	38p	BU208AT	200p	R2008B	100p	2N3772	90p	17088	200p			AN5521	100p
BC172	10p	BD537	40p	BU208D	130p	R2010A	100p	2N3773	100p	17089	200p			AN5612	200p
BC177	14p	BD538	40p	BU209	40p	S2000A3	175p	2N3799	18p	17127	200p			AN5613	200p
BC178	14p	BD643	50p	BU225	120p	S2000AF	175p	2N3819	28p	15R00H	230p			AN5615	300p
BC179	14p	BD645	50p	BU226	120p	S2055A	175p	2N3903	11p	15R5R	230p			AN5620	250p
BC182	7p	BD647	50p	BU312	90p	S2055AF	200p	2N3906	11p	SG26A	800p			AN5622	275p
BC182L	7p	BD649	50p	BU325	55p	S2530A	100p	2N4031	25p	SG613	1500p			AN5625	400p
BC183	7p	BD675	40p	BU326A	75p	S2800M	72p	2N4401	12p	AN5712	180p			AN5722	140p
BC183L	7p	BD676	40p	BU406	60p	TIP29	25p	2N4403	12p	AN5720	160p			AN5730	160p
BC184	7p	BD677	38p	BU406D	85p	TIP29A	22p	2N5061	20p	AN5732	120p			AN5732	120p
BC184L	7p	BD678	40p	BU407	55p	TIP29C	25p	2N5088	20p	AN5735	120p			AN5735	120p
BC212	7p	BD679	40p	BU407D	55p	TIP29E	25p	2N5192	20p	AN5753	120p			AN5753	120p
BC212L	7p	BD680	40p	BU408	60p	TIP30	25p	2N5241	500p	AN5753	120p			AN5753	120p
BC213	7p	BD681	45p	BU408D	75p	TIP30C	25p	2N5245	45p	AN5790	240p			AN5790	240p
BC213L	7p	BD682	45p	BU409	65p	TIP31A	22p	2N5294	30p	AN5790	240p			AN5790	240p
BC214	7p	BD705	50p	BU426A	70p	TIP31C	22p	2N5294	30p	AN5790	240p			AN5790	240p
BC214L	7p	BD707	50p	BU500	100p	TIP32	24p	2N5448	12p	AN5790	240p			AN5790	240p
BC237	7p	BD709	50p	BU505	90p	TIP32A	21p	2N6107	40p	AN5790	240p			AN5790	240p
BC238	7p	BD711	50p	BU505D	90p	TIP32C	21p	2N6292	40p	AN5790	240p			AN5790	240p
BC239	7p	BD736	50p	BU505DF	90p	TIP33	50p	2N6385	120p	AN5790	240p			AN5790	240p
BC300	20p	BD826	50p	BU506	100p	TIP33C	60p	2N6403	160p	AN5790	240p			AN5790	240p
BC301	20p	BD828	50p	BU506D	70p	TIP34	50p			AN5790	240p			AN5790	240p
BC302	20p	BD839	55p	BU506DF	120p	TIP34C	60p			AN5790	240p			AN5790	240p
BC303	20p	BD897	50p	BU508A	70p	TIP35C	65p			AN5790	240p			AN5790	240p
BC304	25p	BD899	50p	BU508AF	95p	TIP36C	65p			AN5790	240p			AN5790	240p
BC327	7p	BD977	50p	BU508D	75p	TIP41A	20p			AN5790	240p			AN5790	240p
BC328	7p	BD978	50p	BU508DF	115p	TIP41C	22p			AN5790	240p			AN5790	240p
BC337	7p	BDX33	60p	BU508V	110p	TIP42	20p			AN5790	240p			AN5790	240p
BC338	7p	BDW24	55p	BU508VF	100p	TIP42C	20p			AN5790	240p			AN5790	240p
BC441	28p	BDW93	50p	BU526	75p	TIP47	40p			AN5790	240p			AN5790	240p
BC446	8p	BDW94	50p	BU536	100p	TIP48	40p			AN5790	240p			AN5790	240p
BC477	18p	BDY92	100p	BU546	125p	TIP50	60p			AN5790	240p			AN5790	240p
BC516	22p	BF137	35p	BU608	120p	TIP51	80p			AN5790	240p			AN5790	240p
BC537	25p	BF161	30p	BU626	120p	TIP52	80p			AN5790	240p			AN5790	240p
BC546	8p	BF181	30p	BU705	120p	TIP54	80p			AN5790	240p			AN5790	240p
BC547	8p	BF183	20p	BU706DF	175p	TIP105	65p			AN5790	240p			AN5790	240p
BC548	8p	BF195	7p	BU706F	150p	TIP106	65p			AN5790	240p			AN5790	240p
BC549	8p	BF199	8p	BU801	70p	TIP107	65p			AN5790	240p			AN5790	240p
BC550	8p	BF200	16p	BU806	70p	TIP110	40p			AN5790	240p			AN5790	240p
BC556	8p	BF225	30p	BU807	60p	TIP111	40p			AN5790	240p			AN5790	240p
BC557	8p	BF240	18p	BU902	110p	TIP112	35p			AN5790	240p			AN5790	240p
BC558	8p	BF245	25p	BU903	110p	TIP112H	35p			AN5790	240p			AN5790	240p
BC559	8p	BF254	15p	BU920	110p	TIP115	30p			AN5790	240p			AN5790	240p
BC560	8p	BF255	12p	BU922	110p	TIP116	30p			AN5790	240p			AN5790	240p
BC637	20p	BF256	18p	BU930	130p	TIP117	30p			AN5790	240p			AN5790	240p
BC639	20p	BF257	18p	BU2508A	130p	TIP120	30p			AN5790	240p			AN5790	240p
BC647	20p	BF259	18p	BU2508D	130p	TIP120A	35p			AN5790	240p			AN5790	240p
BCY33	200p	BF262	25p	BU2508F	130p	TIP122	30p			AN5790	240p			AN5790	240p
BCY34	200p	BF270	18p	BU2508DF	150p	TIP125	30p			AN5790	240p			AN5790	240p
BCY70	16p	BF273	15p	BU2520AF	225p	TIP126	40p			AN5790	240p			AN5790	240p
BCY71	16p	BF311	21p	BU2520DF	225p	TIP127	35p			AN5790	240p			AN5790	240p
BCY72	16p	BF336	20p	BU2525AF	325p	TIP130	30p			AN5790	240p			AN5790	240p
BD115	16p	BF337	20p	BUH515	290p	TIP131	30p			AN5790	240p			AN5790	240p
BD124P	50p	BF338	20p	BU111AF	55p	TIP132	30p			AN5790	240p			AN5790	240p
BD131	25p	BF362	30p	BU112	55p	TIP141	65p			AN5790	240p			AN5790	240p
BD132	25p	BF367	13p	BU156A	75p	TIP142	75p			AN5790	240p			AN5790	240p
BD133	50p	BF371	17p	BU18	80p	TIP145	50p			AN5790	240p			AN5790	240p
BD135	20p	BF421	18p	BU18AF	80p	TIP146	70p			AN5790	240p			AN5790	240p
BD136	20p	BF422	18p	BU18V	150p	TIP147	80p			AN5790	240p			AN5790	240p
BD137	20p	BF423	25p	BUX10	210p	TIP150	90p			AN5790	240p			AN5790	240p
BD138	20p	BF455	12p	BUX12	150p	TIP151	60p								

# 60A half bridge draws milliampere quiescent

Modules and other paralleled mos-gated power transistors often present difficulties in gate-drive circuit design.

Most mos gate drivers provide large peak output currents, acceptable for most applications. However, when driving large loads of many paralleled devices, excess power dissipation may become an issue when switching above a few tens of kilohertz. International rectifiers design tip 92-2 outlines a way of alleviating this problem by using a current buffer.

Figure 1 shows a typical circuit for a high input impedance power buffer. It delivers 8A peak output but draws only negligible quiescent current. Transistors Q<sub>1,2</sub> are low current drivers for Q<sub>3,4</sub> which can be sized to suit peak output current requirements.


When the input changes state the 100Ω resistor limits the resulting current of Q<sub>1,2</sub>. In its new state, the driver transistor discharges the gate capacitance of the conducting output transistor, forcing it into off-state.

The gate of the other output transistor charges through the resistor. Turn-on is delayed by the RC time constant formed by the resistor and the input capacitance of the output transistor.

The configuration of Fig. 2 employs two power buffers in conjunction with a IR2110 half-bridge driver, which combine to create a high-current half-bridge circuit.

Each buffer receives its drive signal from the IR2110. They in turn drive an insulated-gate bipolar transistor module with a total gate charge, Q<sub>G</sub>, of typically 600nC. The modules switch an inductive load current of 60A. It is possible to use lower voltage power mosfets ie 60V. However, the large reduction in R<sub>DS(on)</sub> causes a great deal of noise and ringing in the circuit due to a rise in large peak currents.

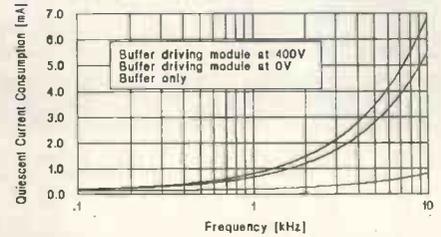*International Rectifier, Hurst green, Oxted, Surrey RH8 9BB, UK.  
Tel 44 883 713 215, fax 716 093.*



Quiescent current of the 2110 rises with increasing frequency, but even at 10kHz, the figure is still under 7mA.

Fig. 1. This high input impedance current buffer delivers 8A peak output yet draws negligible quiescent current.


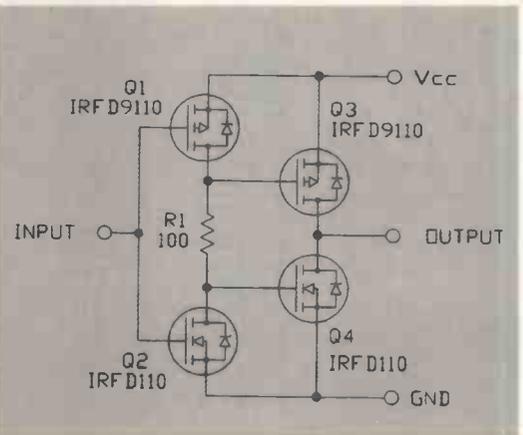


Fig. 2. Two power buffers with an IR2110 driver combine to create a high-current half-bridge power driver for 60A IGBT modules.

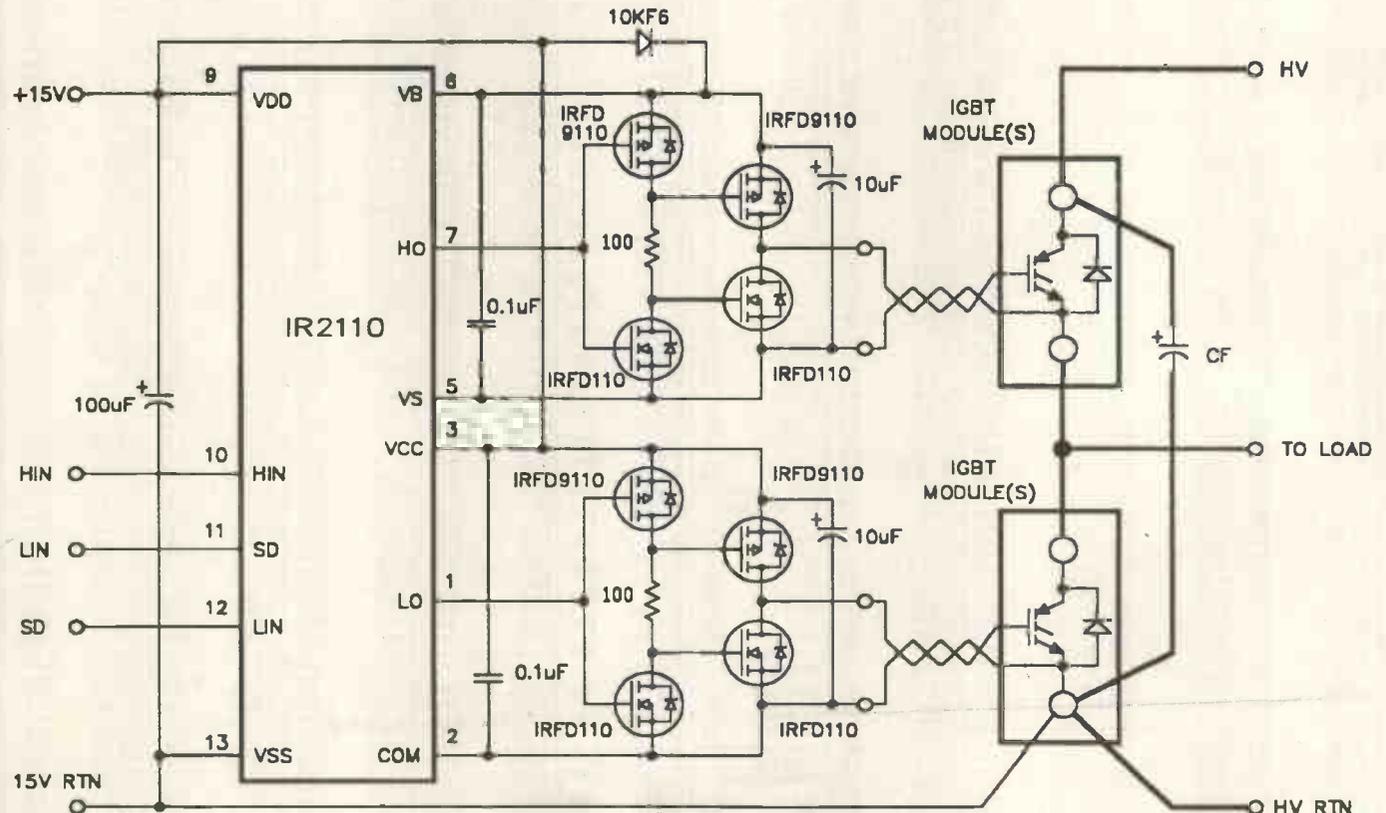

# SMD Power.

Or where to find the widest selection of power SMDs at the lowest cost/amp.




Small as they are, our power SMDs save you more than just board space. They save you time. And money. With the best price-performance ratio from the widest choice of SMDs available.

All off the shelf. All under one roof. And value-priced at the lowest cost/amp. From HEXFET® power MOSFETs and IGBTs to their drivers, the IR2100 Series. And, of course, Schottkys.

You'll find no other power SMDs so closely matched in features and capabilities. But don't take our word for it.

You'll be surprised at what you save.

*Available now at key IR distributors.*

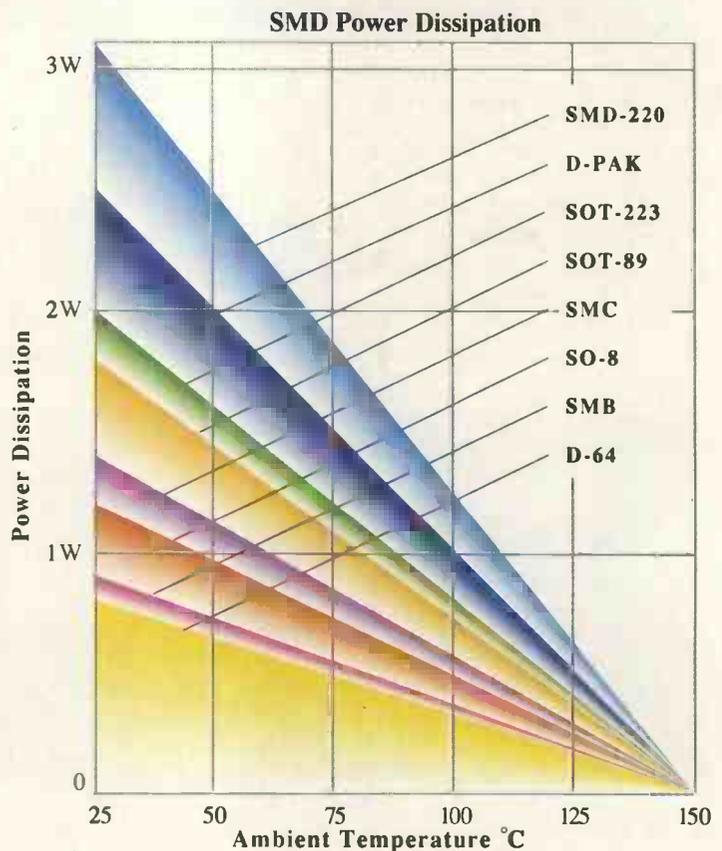

**IR International Rectifier**

WORLD HEADQUARTERS: 233 KANSAS ST., EL SEGUNDO, CA 90245, USA 310-322-3331, FAX 310-322-3332, TELEX 66-4464. EUROPEAN HEADQUARTERS: HURST GREEN, OXTED, SURREY RH8 9BB, ENGLAND, (01883) 713215, FAX (01883) 714234

CIRCLE NO. 118 ON REPLY CARD

# Autoshutdown reduces RS232 standby current to 1µA

Maxim's eighth edition of the *Interface Analogue Design Guide* outlines a new invention that automatically reduces standby power of an RS232 interface to 1µA.

Reducing supply current is a critical factor for extending battery life in any hand held device. Ideally any idle RS232 IC should draw no supply current without degrading performance or increasing cost. With this new invention, the IC draws only 1µA, providing the device is not connected to an operating RS232 system.

Called Autoshutdown the scheme involves

monitoring the RS232 receiver inputs. If no valid RS232 level is present, the IC automatically turns the device on/off, rather than relying on independent software commands to perform the shut-down.

This device is claimed to save 1000 times the supply current relative to other RS232 devices. It is said to be suitable for any hand held system – regardless of the complexity of software.

The RS232 IC is available in four versions. Each has different characteristics suited to different applications. These

include varying data rates, a choice of operating supply ranges and a selection of transmitters/receiver permutations.

Maxim Integrated Products(UK) Ltd.  
Unit 3, Theale Technology Centre, Station Rd  
Theale, Berkshire RG7 4XX, Tel 01734 303388, fax 01734 305577.

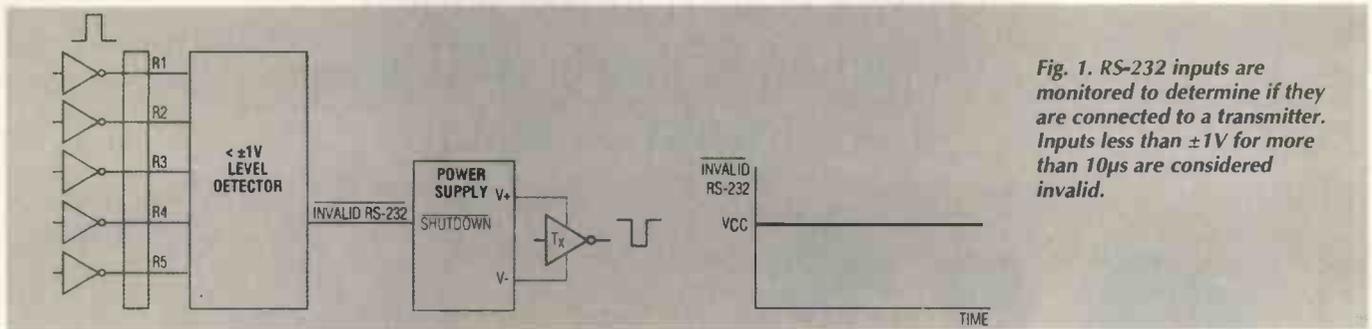


Fig. 1. RS-232 inputs are monitored to determine if they are connected to a transmitter. Inputs less than  $\pm 1V$  for more than 10µs are considered invalid.

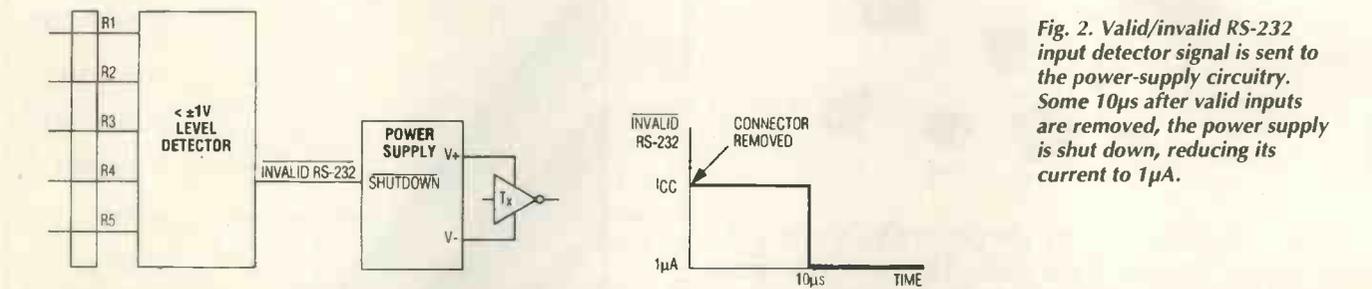


Fig. 2. Valid/invalid RS-232 input detector signal is sent to the power-supply circuitry. Some 10µs after valid inputs are removed, the power supply is shut down, reducing its current to 1µA.

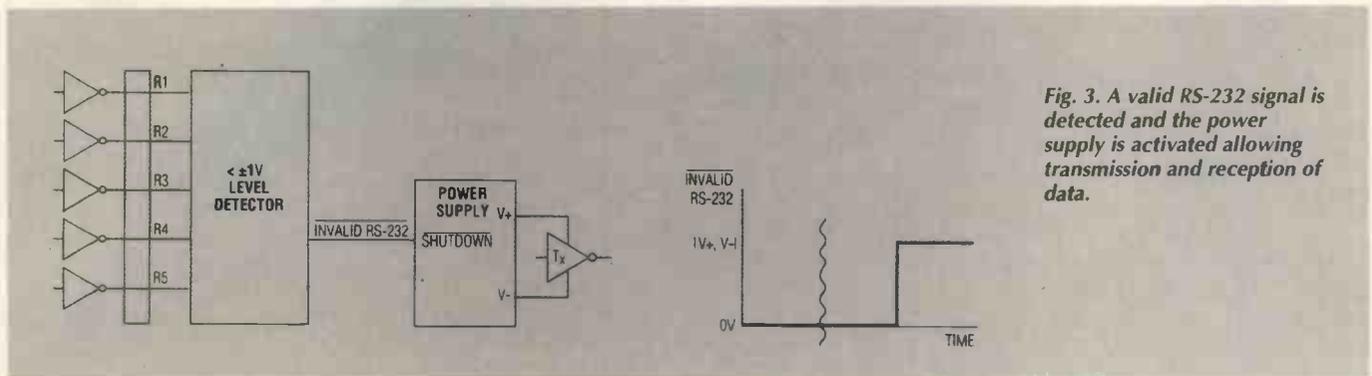


Fig. 3. A valid RS-232 signal is detected and the power supply is activated allowing transmission and reception of data.

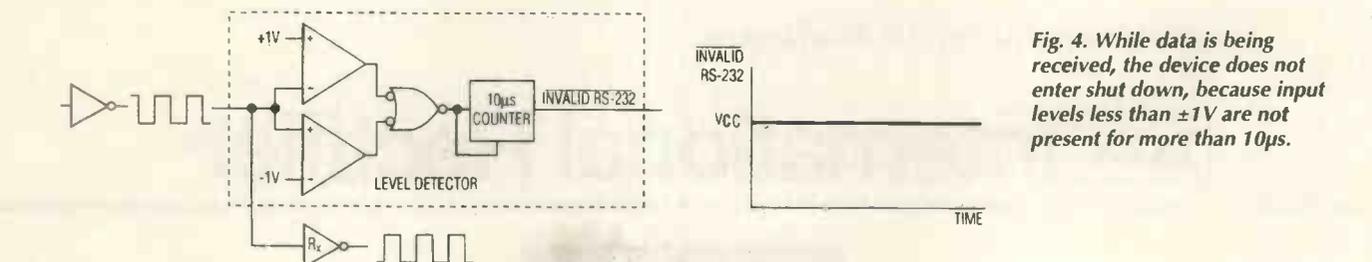


Fig. 4. While data is being received, the device does not enter shut down, because input levels less than  $\pm 1V$  are not present for more than 10µs.


# A NEW FORCE IN LOW COST PORTABLE PROGRAMMERS

The L5000 can program or emulate either a single 8 bit eprom, a pair of 8 bit eproms or a 40 pin - 16 bit - eprom.

## YOU GET MORE WITH THE L5000!

- ★ Approved algorithms, as used in our gang programmers, for eproms & flash.
- ★ Programs up to 2M devices in one pass. Ram expandable to 8M bits.
- ★ Settings for numerous micros from Hitachi, NEC and Toshiba.
- ★ Use stand-alone or with a PC using bi-directional RS232, or Centronics ports. No internal card needed for portable PCs.
- ★ Batch file facility for repetitive operations.
- ★ Full set programming facilities including editing in words or bytes.
- ★ Optional facilities to program 40 pin eproms and/or 8751 micros.
- ★ Emulation of either a single 8 bit eprom, a 16 bit pair of 8 bit eproms or a single 40 pin eprom. You can even emulate ram.


TEN DAY  
TRIAL OFFER

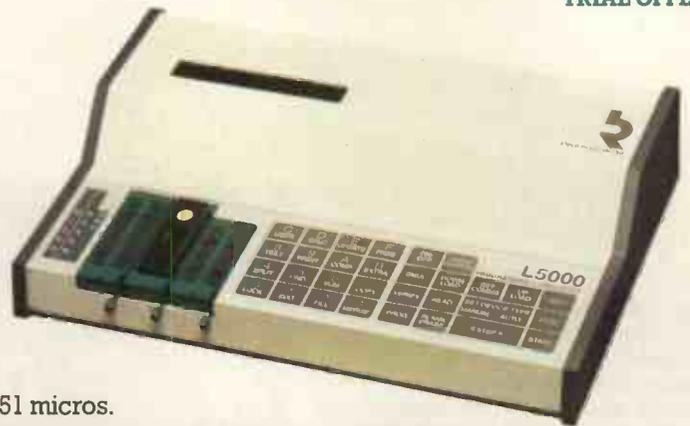

The L5000 already caters for tomorrow's devices. For example, the 2M user ram is twice the size normally found in most small programmers and it can be expanded to 8M bits for the largest 32 pin devices. Adequate ram saves multiple downloads and the need to program in blocks. The L5000 also has additional hardware to support sector protect/unprotect on flash devices such as 29F010/040.

LLOYD RESEARCH LTD.,  
7 & 7A Brook Lane,  
Warsash,  
Southampton SO31 9FH.

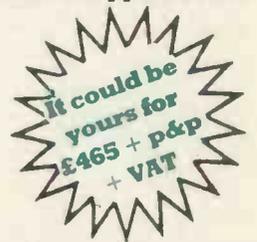Enquiries and credit card orders:  
Tel: +44 (0) 1489 574040  
Fax: +44 (0) 1489 885853



**EXPORT SALES AND DISTRIBUTOR ENQUIRIES WELCOME**

CIRCLE NO. 119 ON REPLY CARD

## DEVELOPMENT AND PRODUCTION SOLUTIONS

- Gang Programmers
- Package Converters
- Development Programmers
- Development Tools
- Universal Cross Assembler
- Emulator Pods + Adapters



IRELAND 1-2800395  
GERMANY 089/4602071  
NORWAY 0702-17890  
ITALY 02 92 10 35 54  
FRANCE 1 69 30 13 79  
SWEDEN 08 590 321 85  
Also from ELECTROSPEED UK




**mqp** ELECTRONICS Ltd  
Park Road Centre, Malmesbury, Wiltshire SN16 0BX UK  
Tel: 01 666 825146 Fax: 01 666 825141  
e/mail 100447.1124@compuserve.com

Ask for Free  
Information Pack  
and Demonstration  
Discs

CIRCLE NO. 120 ON REPLY CARD

**Fig. 1. Rear View of the Fada Neutrodyne trf radio showing its inclined coil arrangement. In conjunction with Hazeltine neutralisation circuits, this physical layout enabled stable rf amplification over the whole broadcast band. Prior to practical and cost-effective super-heterodyne sets, the Neutrodyne represented state-of-the-art technology. It flourished during the 1923-26 time frame.**

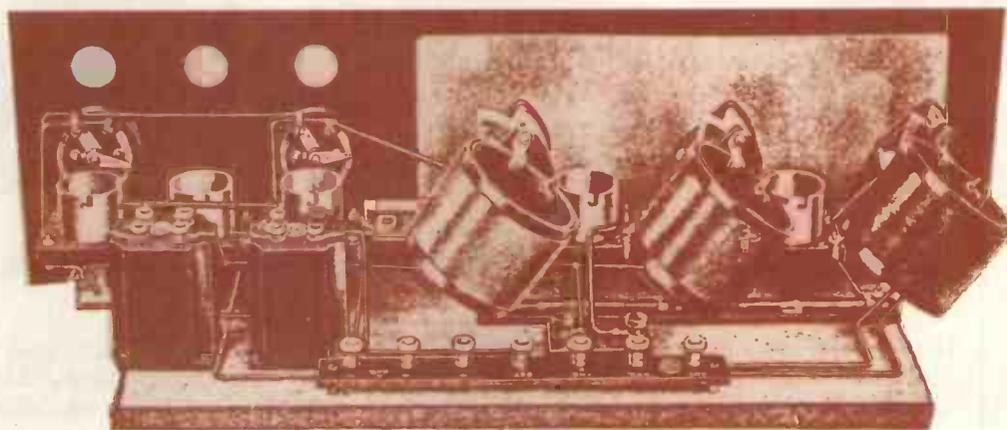

# A new slant on an old angle

**Irving Gottlieb has been looking at the Neutrodyne – a receiver that achieved high gain without suffering from oscillation due to stray coil coupling. “Why is this simple solution not in use today?” he asks.**

**O**scillation caused by stray coupling between tuned circuits is a common problem in multi-stage rf and if amplifiers that need to be constructed in a small space.

Toroidal inductors help reduce the tendency towards oscillation. Alternatively, cylindrical-shaped inductors can be mounted so that they are mutually perpendicular to one another. A third approach stems from the Neutrodyne technique used in early battery radios in vacuum-tube tuned radio-frequency, trf, circuits.

This method arranges the coils at a slant with respect to the horizontal. The ‘magic’ angle used was  $54.7^\circ$  – the tangent of which happens to be the square-root of two. Electromagnetic coupling was surprisingly scarce between any two of the coils, the layout of which is shown in Fig. 1.

You might be tempted to analyse the existence of this coupling null mathematically, but calculations turn out to be extremely complex. Subsequently, best results accrue from empirical work.

The angle is not sacred. Variations of plus or minus several degrees produce similar results. The reason for this is that the angle is a function of wire size, winding length, coil shape and coil spacing. Other variables tend to creep in with regard to proximity effects.

However, the null is attainable over a wide


range of dimensions and circumstances. A useful aspect of the phenomenon is that it is not frequency-sensitive. In old radio sets, near-zero couplings held good over the entire broadcast band.

A straightforward way to implement this technique is to use coils whose diameter and winding length are about the same. This coil configuration also tends to yield optimum Q. Spacing between coils of about-one coil-radius appears to work best. Closer spacing can be accommodated, but the null then becomes more critical to adjust. This is probably due to capacitive coupling.

Electromagnetic isolation provided by this strange scheme does not tie in with our everyday experience of tuned circuits. You might expect strong coupling, for instance somewhere between that due to axial alignment and that caused by perpendicular orientation of the coils. However, with an rf generator, oscilloscope, and a pair of resonant coils, you can easily observe that energy transfer neatly nulls when the coils are positioned approximately as prescribed.

Surely, this is a useful phenomenon – one that has probably been overlooked in modern electronics because of the many more exciting advances that have captured our interests. After researching many radio and engineering tests, even contemporary ones of

Fig. 2. Magnetic flux lines threading through a coil 'slanted' for zero-coupling. Under the null conditions, the coil-conductors are cut symmetrically by both downward and upward-sloping flux lines. A net cancellation of induced voltage takes place so that there is no effective electromagnetic induction. Zero-coupling achieved in this way prevented unwanted feedback in the Neutrodyne radio receiver.

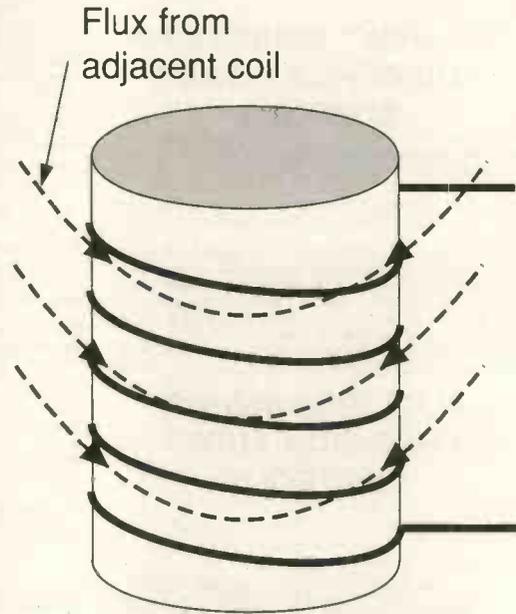

the Neutrodyne, I met with frustration and disappointment. I could find no explanation of this cause and effect relationship. In seeking an analysis from engineers, most of them viewed the situation as a paradox. Here, however, appears to be a feasible solution.

In Fig. 2, you can see lines of magnetic flux threading through a coil. The flux emanates from an adjacent coil and it is assumed that the 'magic angle' exists between the coils.

Note the symmetry of the downward and upward-sloping flux lines. This certainly implies electromagnetically induced emfs in the coil conductors. However, because of the alluded symmetry, these emfs cancel. This is tantamount to zero coupling between the coils.

If the angle is different from the 'magic' one, either the upward or downward slope lines will predominate and a net emf will then manifest. Bear in mind that it is the component of the magnetic lines that 'cut' the coil conductors at right angles that counts. If you mentally rotate the coil with respect to the magnetic lines, the notion of the 'magic' angle is driven home.

Professor Hazeltine was a brilliant mathematician. It appears that he deduced this invention from theoretical considerations. For our purposes, the descriptive account tendered here should suffice for useful results.


From a number of experiments, I would suggest mounting the coils in such a way as to allow a few degrees of angular adjustment. You can then build a high-gain amplifier channel in a small space and carefully adjust the coil slants so as to optimise stability. In doing so, you can compensate for various stray feedback paths since the coil adjustments allow small amounts of negative feedback. ■

# PROTEUS

The Complete Electronics Design System

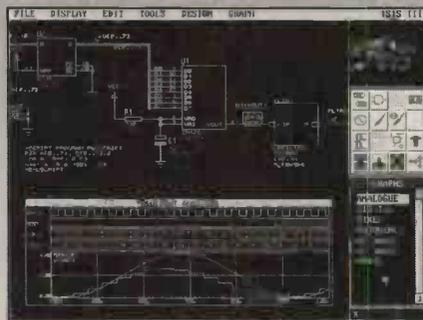
## Schematic Capture

- Easy to Use Graphical Interface.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and PCB design.


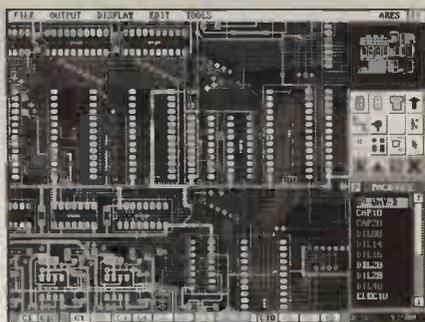
## Simulation

- Non-Linear & Linear Analogue Simulation.
- Event driven Digital Simulation with modelling language.
- Partitioned simulation of large designs with multiple analogue & digital sections.
- Graphs displayed directly on the schematic.



## PCB Design

- Multi-Layer and SMT support.
- Unlimited Design Capacity.
- Full DRC and Connectivity Checking.
- Advanced Multi-Strategy Autorouting.
- Output to printers, plotters, Postscript, Gerber, DXF and DTP bitmaps.
- Gerber View and Import capability.

Write, phone or fax for your free demo disk, or ask about our full evaluation kit.

labcenter  
Electronics

53-55 Main St, Grassington, N Yorks, BD23 5AA  
Tel: 01756 753440 Fax: 01756 752857



# HART AUDIO KITS - YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

Hart Audio Kits and factory assembled units use the unique combination of circuit designs by the renowned John Linsley Hood, the very best audiophile components, and our own engineering expertise, to give you unbeatable performance and unbelievable value for money. We have always led the field for easy home construction to professional standards, even in the sixties we were using easily assembled printed circuits when Heathkit in America were still using tagboards. Many years of experience and innovation, going back to the early Dinsdale and Bailey classics gives us incomparable design background in the needs of the home constructor. This simply means that building a Hart kit is a real pleasure, resulting in a piece of equipment that not only saves you money but you will be proud to own. Why not buy the reprints and construction manual for the kit you are interested in to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase.

## K1100 AUDIO DESIGN 80 WATT POWER AMPLIFIER.



This fantastic John Linsley Hood designed amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hi-fi system. This kit is your way to get UK performance at bargain basement prices. Unique design features such as fully FET stabilised power supplies give this amplifier World Class performance with startling clarity and transparency of sound, allied to the famous HART quality of components and ease of construction.

Useful options are a stereo LED power meter and a versatile passive front end giving switched inputs, with ALPS precision Blue Velvet low-noise volume and balance controls. Construction is very simple and enjoyable with all the difficult work done for you, even the wiring is pre-terminated, ready for instant use! All versions are available with Standard components or specially selected Super Audiophile components at £29.50 extra per channel, plus £2.40 if you want to include Gold Plated speaker terminals.

K1100B Complete STANDARD Amplifier Kit.....	£395.21
A1100B Factory Assembled.....	£499.21
K1100SC Complete SLAVE Amplifier Kit.....	£333.62
A1100SC Factory Assembled.....	£422.62
K1100M Complete MONOBLOC Amplifier Kit.....	£261.20
A1100M Factory Assembled.....	£329.20
RLH11 Reprints of latest Amplifier articles.....	£1.80
K1100CM Construction Manual with full parts lists.....	£5.50

## "CHIARA" SINGLE ENDED



## CLASS "A" HEADPHONE AMPLIFIER.

This unit provides a high quality headphone output for 'stand alone' use or to supplement those many power amplifiers that do not have a headphone facility. Easily installed with special link-through feature the unit draws its power from our new Andante Ultra High Quality linear toroidal supply. Housed in the neat, black finished, Hart minibox it features the wide frequency response, low-distortion and 'musicality' that one associates with designs from the renowned John Linsley Hood. Pre-terminated interconnecting leads and PCB mounted sockets prevent supply polarity reversal and on-board diagnostics provide visual indication of supply line integrity. Volume and balance controls are Alps "Blue Velvet" components. Very easily built, even by beginners, since all components fit directly on the single printed circuit board. The kit has very detailed instructions, and even comes with a complementary roll of Hart audiograde silver solder. It can also be supplied factory assembled and tested. Selling for less than the total cost of all the components, if they were bought separately, this unit represents incredible value for money and makes an attractive and harmonious addition to any hi-fi system.

K2100 Complete Kit.....	£109.50
K2100SA Series Audiophile version with selected audiophile components.....	£112.46
A2100SA Series Audiophile version, factory Assembled.....	£149.46
K3565 "Andante" Power Supply Kit to suit "Chiara".....	£85.42
K3565 Power Supply, Factory Assembled.....	£128.42
CM2100 Construction Manual.....	£2.50
SPECIAL OFFER. Both units together, Kit Form.....	£184.92
Factory Assembled and Tested.....	£267.88

## "Andante" SERIES 20VA AUDIOPHILE POWER SUPPLIES

Specially designed for exacting audio use requiring absolute minimum noise, low hum field and total freedom from mechanical noise this unit is a logical development from our highly successful 1550 series.

Utilising linear technology throughout for smoothness and musicality makes it the perfect partner for any module requiring fully stabilised ±15v supplies.

Two versions are available. K3550 has 2 ±15v supplies and a single 15v for relays etc. and can be used with our K1400 preamp and our K1450 RIAA pickup preamp, as well as other useful modules soon to be introduced. The K3565 is identical in appearance but only has the ±15v lighter current supply for use with the K1450 RIAA pickup pre amplifier or "Chiara" headphone amplifier.

K3550 Full Supply with all outputs.....	£93.75
K3565 Power Supply for K1450 & K2100.....	£85.42

## ALPS "Blue Velvet" PRECISION AUDIO CONTROLS.



Now you can throw out those noisy ill-matched carbon pots and replace with the famous Hart exclusive ALPS "Blue Velvet" range components only used selectively in the very top flight of World class amplifiers. The improvement in track accuracy and matching really is incredible giving better tonal balance between channels and rock solid image stability. Motonised versions have 5v DC motor.

**MANUAL POTENTIOMETERS**

2-Gang 100K Lin.....	£15.67
2-Gang 10K, 50K or 100K Log.....	£16.40
2-Gang 10K Stereo Balance, zero crosstalk and zero centre loss.....	£17.48

**MOTORIZED POTENTIOMETERS**

2-Gang 20K Log Volume Control.....	£26.20
2-Gang 10K RD Stereo Balance, zero crosstalk and less than 10% loss in centre position.....	£26.98

## TECHNICAL BOOKSHELF

NEW! Another Classic by John Linsley Hood. "AUDIO ELECTRONICS" Following the enormous ongoing success of his "Art of Linear Electronics" the latest offering is the all-new edition of "Audio Electronics", now entirely re-written by the master himself. Underlying audio techniques and equipment is a world of electronics that determines the quality of sound. For anyone involved in designing, adapting or using digital or analogue audio equipment understanding electronics leads to far greater control over the reproduced sound. The subjects covered include tape recording, tuners, power output stages, digital audio, test instruments and loudspeaker crossover systems. John's lifetime of experience and personal innovation in this field allow him to apply his gift of being so familiar with his subject that he can write clearly about it and make it both interesting and comprehensible to the reader. Containing 240 pages and over 250 line illustrations this new book represents great value for money at only.....£18.99\*

## "THE ART OF LINEAR ELECTRONICS."

The definitive linear electronics and audio book by John Linsley Hood. This 300+ page book will give you an unparalleled insight into the workings of all types of audio circuits. Learn how to read circuit diagrams and understand amplifiers and how they are designed to give the best sound. The virtues and vices of passive and active components are examined and there are separate sections covering power supplies and the sources of noise and hum. As one would expect from this writer the history and derivation of audio amplifier circuitry have an entire chapter, as does test and measurement equipment. Copiously illustrated this book is incredible value for the amount of information it contains on the much neglected field of linear, as opposed to digital, electronics. Indeed it must be destined to become the standard reference for all who work, or are interested in, this field. Latest reprinted edition with extended index. 1994 344 Pages. 247 x 190. 1Kg. 0-7506-0868-4.....£16.95\*

"DIGITAL AUDIO AND COMPACT DISC TECHNOLOGY" 0-7506-0614-2.....£17.95\*

INTRODUCING DIGITAL AUDIO CD, DAT AND SAMPLING. ISBN 1870775 22 8.....£7.95

"THE ART OF SOLDERING" 0-85935-324-3, 0.....£3.95

"TOWERS' INTERNATIONAL TRANSISTOR SELECTOR" 0-572-01062-1.....£19.95\*

"AUDIO" F.A. Wilson. BP111.....£3.95

"HOW TO USE OSCILLOSCOPES & OTHER TEST EQUIPMENT" R.A. Penfold. BP267.....£3.50

"THE LOUDSPEAKER DESIGN COOKBOOK" Vance Dickason.....£22.95\*

(4th Edn.) 0-9624-191-7-6.....£22.95\*

ELECTROSTATIC LOUDSPEAKER DESIGN AND CONSTRUCTION Ronald Wagner. BKT6.....£18.95

"AN INTRODUCTION TO LOUDSPEAKERS & ENCLOSURE DESIGN" V. Capel. BP256.....£2.95

"LOUDSPEAKERS FOR MUSICIANS" BP297.....£3.95

"THE HART PRINTED CIRCUIT BOARD CONSTRUCTION GUIDE.".....£2.50

## VALVE & EARLY CLASSIC BOOKS

THE VTL BOOK David Manley BKV1.....£17.95

LOUDSPEAKERS; THE WHY AND HOW OF GOOD REPRODUCTION. G. Briggs. 1949 0-9624-1913-3.....£8.95

MULLARD TUBE CIRCUITS FOR AUDIO AMPLIFIERS BKA27.....£13.95

"THE WILLIAMSON AMPLIFIER." 0-9624-1918-4.....£6.95

AN APPROACH TO AUDIO FREQUENCY AMPLIFIER DESIGN. GEC 1957, 1-882580-05-2.....£18.95

AUDIO ANTHOLOGIES, articles from Audio Engineering. Six volumes covering the days when audio was young and valves were king. BKAA3/1 to 6. All.....£13.95 each.

"A SIMPLE CLASS A AMPLIFIER" J.L. Linsley Hood M.I.E.E. 1969. RLH12.....£2.50

Postage on all books, unless starred, is only £1.50 per book, maximum £4.50 for any number, any size! Starred items are heavy books costing.....£2.50 to send.

No waiting! All listed books are normally in stock.

SPECIAL OFFER. All book orders over £15 will receive a FREE John Linsley Hood monograph entitled "Digital versus Analogue, Black Disks or Silver?"

## SPECIAL OFFER PRECISION Triple Purpose TEST CASSETTE TC1D.

Are you sure your tape recorder is set up to give its best? Our latest triple purpose test cassette checks the three most important tape parameters without test equipment. Ideal when fitting new heads. A professional quality, digitally mastered test tape at a price anyone can afford. Test Cassette TC1D. Our price only.....£9.99.



## HC80 Replacement Stereo Cassette Head.

The excellent performance of modern cassette recorders depends totally on the quality of the R/P head. Even the slightest amount of wear can impair the frequency response and distortion levels. Our HC80 is atop quality head from one of the foremost manufacturers in Japan, easily fitted to most standard stereo recorders (except Sony) and will transform the performance over a worn head. Only the fact that we buy these in vast quantities enables us to offer them at the amazing price of only £11.70 each or 2 for £17.60. We also stock a range of other heads, including "T" reel-to-reel stereo heads.

## SOLDERING

The size of modern components makes the right soldering equipment essential for good results. Everything we offer we actually use in our own workshop. See our Lists for the full range. 845-820 XS240 ANTEX 240v 25w Soldering Iron. This is the ideal Multi-purpose iron as the bit is designed to totally surround the element giving the best heat transfer. This excellent design also means that although it is small and handy enough for modern components its heating capacity is better than larger irons of conventional construction. Excellent Value.....£9.93

845-080 ST4 Lightweight Soldering Iron Stand. This has provision for the classic damp sponge for bit wiping.....£3.95

## HART SUPER AUDIOGRADE SILVER SOLDER.

Hart Super Audiograde Silver Solder has been specially formulated for the serious audiophile. Not only does it give beautiful easy-to-make joints but it is designed to melt at normal soldering temperatures avoiding the possibility of thermal damage to components or the need for special high temperature irons. A very low residue flux makes perfect joints easy but eliminates the need for board cleaning after assembly.

845-007 3mtrs 22SWG in Hart Mini Tube.....	£3.90
845-008 100g. Reel Special Valve Grade, 20swg.....	£12.90
845-009 100g. Reel PCB Grade, 22swg.....	£14.75
845-110 100g Reel Superfine 24swg for ultra precise control and easy working.....	£21.45

QUALITY AUDIO KITS

24 hr. SALES LINE (01691) 652894

ALL PRICES INCLUDE UK/EC VAT



CIRCLE NO. 122 ON REPLY CARD

Steve Winder presents a new approach to providing a balanced amplifier output for twisted-pair transmission lines. Using the supply pins of an op-amp as a combined supply and line-connection point, this scheme eliminates the need for a line-coupling transformer at the remote end.

# A new balanced view

Readings from sensors in remote locations are often sent to the base station via an amplifier feeding a twisted pair. The amplifier can be powered locally by battery or mains supply. Most often, though, there is a dc feed from the base station.

If only one cable pair is available, the dc feed must use the same pair as the signal. Line transmission requires a balanced output and, if local power is available, there are two methods of providing it,

- using two amplifiers connected to the same source. One amplifier is inverting and the other is non-inverting. Any signal applied to the input will produce two outputs which are anti-phase – and balanced – and so can be connected to the two wires of the twisted pair.
- driving a transformer from an amplifier's output. The secondary winding of the transformer will be balanced and suitable for connection to the transmission line.

When local power is unavailable the second configuration can be used, but using a transformer with split secondary windings and as shown in Fig. 1. These windings are capacitively coupled to allow the ac signal to pass through both of them in series.

Direct-current feed from the base station travels along the pair and can be taken from across the coupling capacitor to the amplifier's power connections. Unfortunately the line coupling transformer is bulky and is difficult to design because of the dc flowing through its windings.

I have found an alternative to using the transformer is to apply the line directly across the amplifier's power supply pins, as shown in Fig. 2. At the base station, dc power is fed into

the line using a split primary transformer. The two halves of the primary winding are capacitively coupled so that ac signals pass through the transformer.

A dc supply for the amplifier is fed through the primary windings and down the twisted pair. At the sensor, the twisted pair is connected across the amplifier power supply pins. The amplifier output is loaded by a resistor to produce a change in current flow from the supply when signals are applied at the input.

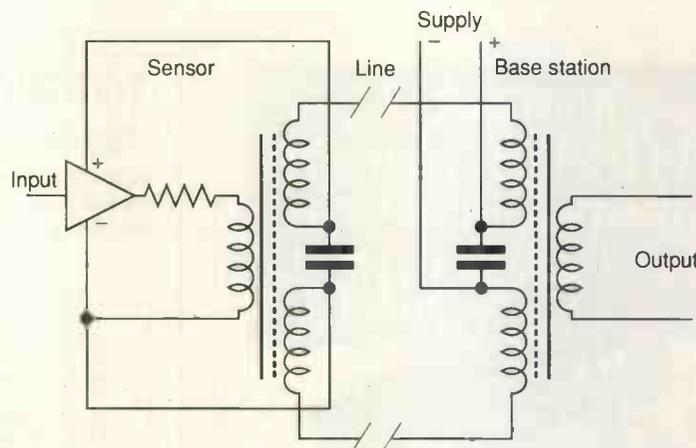


Fig. 1. Impedance analysis of transformer-coupled balanced i/o system. Windings are capacitively coupled to allow the ac signal to pass through them in series.

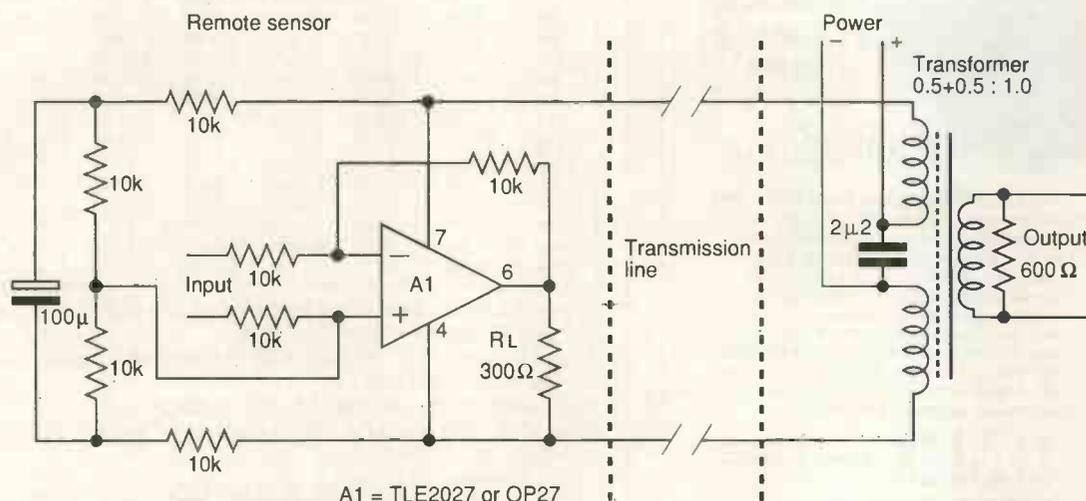


Fig. 2. In this alternative to the conventional transformer-coupled balanced system, the line is applied directly across the amplifier's power supply pins.

A1 = TLE2027 or OP27

To make the impedance of the remote sensor equal to 600Ω it is necessary to use a 300Ω load at the amplifier. The reason for the load resistor value being half that of the line impedance follows.

Consider an ac signal applied to the transformer output. As the potential of the positive supply rail rises, the negative rail will fall, relative to the mid-rail voltage. The ac voltage from the negative rail to the mid-point will be half the total voltage change. This same voltage appears across the load since it is connected between the negative rail and the output of the amplifier which is at mid-rail potential. Thus only half the ac voltage appears across the load, so only half the current flows through it and the effective impedance of the amplifier seen from the transformer is doubled. This is illustrated in Fig. 3.

This scheme requires a decoupled mid-rail supply to be generated locally, but this is simple to achieve using a few resistors and a capacitor; as shown in Fig. 4.

Thévenin's theorem can be used to analyse the circuit. Potential at the centre of the resistor chain is  $V/2$ . The source impedance is approximately equal to  $R$ , relative to the power supply rails. This is because the power rails are much lower in impedance than  $R$  – actually about 300Ω – and so signals applied to the centre of the resistor chain have two

Fig. 3. Analysis shows that only half the ac voltage appears across the load so only half the current flows through it. As a result, effective impedance of the amplifier seen from the transformer is doubled.


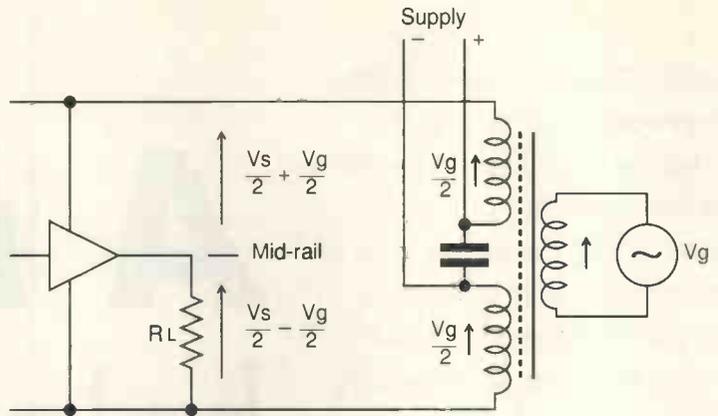


Fig. 4. Achieving a local decoupled mid-supply rail is easy, using a few resistors and a capacitor.

parallel paths to the 0V rail, both  $2R$ .

The decoupling capacitor does not affect the impedance because an equal ac potential appears at each terminal. In theory, signals on the power supply rails are balanced and the centre of the resistor chain should have no ac component present. The decoupling capacitor should not be needed. In practice tolerances in the resistor values result in small ac signals reaching the mid-point unless a decoupling capacitor is present.

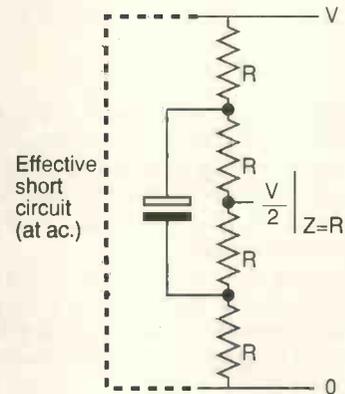

**The MICRO MODULE**  
**A NEW LOW COST controller**  
 that gives you customisation  
 for as little as **£95** one off

**For users of PCs, 8051 & 68000**

**and that's just the half of it!..**

**FEATURES**

- 16/32 bit 68307 CPU for fast operation
- Up to 1 Mbyte of EPROM space onboard
- Up to 512Kbyte SRAM space onboard
- 32 Kbyte SRAM fitted as standard
- RS232 serial with RS485 option
- MODBUS & other protocols supported
- Up to 22 digital I/O channels
- 2 timer/counter/match registers
- I<sup>2</sup>C port or Mbus & Watch dog facilities
- Large Proto-typing area for user circuits
- Up to 5 chip selects available
- Program in C, C++, Modula-2 & Assembler
- Real Time multitasking Operating System
- OS9 or MINOS with free run time license option
- Manufacturing available even in low volumes
- A full range of other Controllers available

**P.C. 'C' STARTER PACK AT ONLY £295 + VAT**

The Micro Module will reduce development time for quick turnaround products/projects and with the P.C. 'C' Starter pack allow you to start coding your application immediately, all drivers and libraries are supplied as standard along with MINOS the real time operating system all ready to run from power on. The 'C' Starter pack includes: A Micro Module with 128 Kbyte SRAM, PSU, Cables, Manuals, C compiler, Debug monitor ROM, Terminal program, Downloader, a single copy of MINOS. Extensive example software, and free unlimited technical support all for £295 + VAT.

**GMS** Cambridge Microprocessor Systems Limited  
 Unit 17-18, Zone 'D', Chelmsford Road Ind. Est., Great Dunmow, Essex, U.K. CM6 1XG  
 Phone 01371 875644 Fax 01371 876077

**TOROIDAL TRANSFORMERS**

High Quality Low Prices

In addition to our standard range we will be pleased to quote for your special requirements.



**PRICE LIST**

VA	Mail Order	Quantity Price Excluding VAT & Carriage				
		2+	10+	25+	50+	100+
15	14.59	10.21	7.69	5.69	5.52	5.35
30	16.04	11.23	8.45	6.25	6.06	5.89
50	17.83	12.48	9.40	9.95	6.74	6.53
60	18.02	12.61	9.49	7.02	6.82	6.61
80	17.98	12.60	9.49	7.02	6.81	6.60
100	21.07	14.74	11.11	8.21	7.96	7.72
120	21.54	15.08	11.35	8.39	8.15	7.89
150	25.98	18.19	13.70	10.12	9.82	9.53
160	23.83	16.68	12.56	9.28	9.00	8.73
225	30.10	21.07	15.87	11.73	11.39	11.04
300	34.32	24.02	18.09	13.38	12.98	12.58
400	46.19	32.32	24.35	17.99	17.47	16.94
500	50.48	35.34	26.61	19.67	19.09	18.51
625	53.09	41.36	31.14	23.02	21.24	20.57
750	58.39	44.23	33.30	24.62	23.89	23.17
1000	78.80	55.16	41.54	30.70	29.80	28.89
1200	82.45	57.72	43.46	32.12	31.17	30.23
1500	105.10	73.63	55.40	40.94	39.74	38.53
2000	114.45	96.13	72.39	53.51	51.93	50.36
2500	163.04	114.13	85.94	63.51	61.64	59.79

These prices are for 240volt primary and two equal secondaries with 8" colour coded fly leads.

Each transformer is supplied with a mounting kit (steel dish washer pads, nut and bolt)

Mail order prices include vat and postage.

Please do not hesitate to telephone or write with your particular requirements.



**Airlink Sales Co**

16 Knight Street, Sawbridgeworth, Herts CM21 9AT  
 Tel: 01279 600139 Fax: 01279 726379

# Square law rules in AUDIO POWER

**To the best of Ian Hegglin's knowledge, the difference of two squares concept has never been used in audio power amplifiers, but as this work shows, there are significant linearity benefits to reap.**

**M**ichael Williams' article<sup>1</sup> shows how the difference of two squares – D2S – produces a linear output from a pair of fets, forming the basis for a perfect linear amplifier. This approach has never been intentionally applied to class AB amplifiers to reduce distortion. The reason is probably the inherent difficulty in obtaining conjugate gain characteristics in the crossover region to prevent crossover distortion<sup>2,3</sup>.

Newly developed circuit techniques could solve this problem, and put the square-law to work in high power audio amplifiers. Experimental results demonstrate the effectiveness of these techniques, but first a look at the underlying theory.

## Crossover distortion in class AB

Class-AB is most widely used due to efficiency and lower cost relative to class-A, but class-AB generates more distortion than class-A. Distortion from class-AB is mainly crossover related and cannot be eliminated by trimming. Negative feedback has difficulty reducing crossover distortion in the high audio range, where there is generally less feedback available for distortion reduction<sup>4</sup>.

Our ears are more sensitive to frequencies in the 1-5kHz range, so crossover distortion is probably a more noticeable type of distortion. It is difficult to design out, and not easy to reduce using negative feedback.

The crossover distortion problem of class-AB power amplifiers is essentially that each of the two output devices must operate in two different modes. Firstly, each device must have constant gain at high currents, but secondly they must have a variable gain in the crossover region where both devices contribute to output current, Fig. 1. The ideal transfer function for no distortion is a straight

line, Fig. 1a. Gain is represented by the slope of the line which is constant, Fig. 1b. Both devices conduct in the crossover region between  $-V_1$  and  $+V_1$ . The gain of each device must sum to a constant value in the crossover region and the total gain must also match the gain outside the crossover region.

With symmetrical components, the gain of each device when  $V_{in}$  is zero must be exactly 50% for a sum of 100%. These requirements give a family of possible symmetrical gain functions that result in zero crossover distortion. A constant rate of change of gain, Fig. 1b, gives the square-law  $V-I$  transfer curve Fig. 1c. This can be found from the gain function by integrating upwards from  $-V_1$  for the positive conducting device and down from  $V_1$  for the other.

An alternative gain function which satisfies the 50% gain requirement and is symmetrical about  $V_{in}=0$  is shown in Fig. 1d. At low currents, fets show exponential deviation from square-law<sup>5</sup>, resulting in a gain curve that is initially exponential. This gives a rounded gain function at low current, Fig. 1d. This suggests it may not be necessary for a fet to show perfect square-law characteristics at low currents to give perfect linearity, provided that the gain curve can be made symmetrical. This should be possible by altering the shape of the top end transition, ie below  $\pm V_1$ .

Classical bipolar and fet class AB stages do not meet these requirements. Figure 1e shows significant gain non-linearity<sup>6</sup> in and near the crossover region. Gain is 32 with a variation of  $-4$ , representing a 13% change when biased for minimum distortion.

Gain error results from one transistor turning off before the other has reached constant gain. Resistors in the emitters cause the gain to flatten at high currents, but the transition occurs

over far too wide a range. Figure 1f is the  $V-I$  transfer function for  $\pm 1V$  input, giving  $\pm 32V$  output and  $\pm 4A$  peak into  $8\Omega$ .

The difference between the line having average gain, i.e. about 31, and the output line results in the distortion component. The error voltage is about 500mV pk-pk, or 200mV rms, with total harmonic distortion of about 1%. If this stage were reconfigured as a unity-gain follower, the action of local feedback would reduce total harmonic distortion to 0.03%.

## More feedback

Negative feedback usually reduces crossover distortion. Due to increasing phase change with frequency, a limit must be put on the amount of negative feedback<sup>4</sup>. In particular, the gain of the feedback loop plus the amplifier must be under unity at the frequency where  $180^\circ$  phase shift occurs. This prevents oscillation and likely destruction of the output transistors.

The  $180^\circ$  phase shift represents a complete phase reversal, turning negative feedback into positive feedback. If the gain  $\geq 1$  at the frequency where  $180^\circ$  shift occurs, the circuit will oscillate. Ideally the gain should fall below 0.7 at the  $180^\circ$  point to give a well-damped response to a square wave.

Load impedance variations have an effect on the loop gain-phase relationship. Capacitive loading from speaker leads and speakers adds phase shift to the output and therefore to the feedback signal<sup>4</sup>. Most output stages are unity-gain follower types with 100% local feedback. These are more sensitive to loading than output stages that have less than 100% feedback and have a gain above unity.

An appropriately designed Zobel network usually overcomes this problem. Generally a

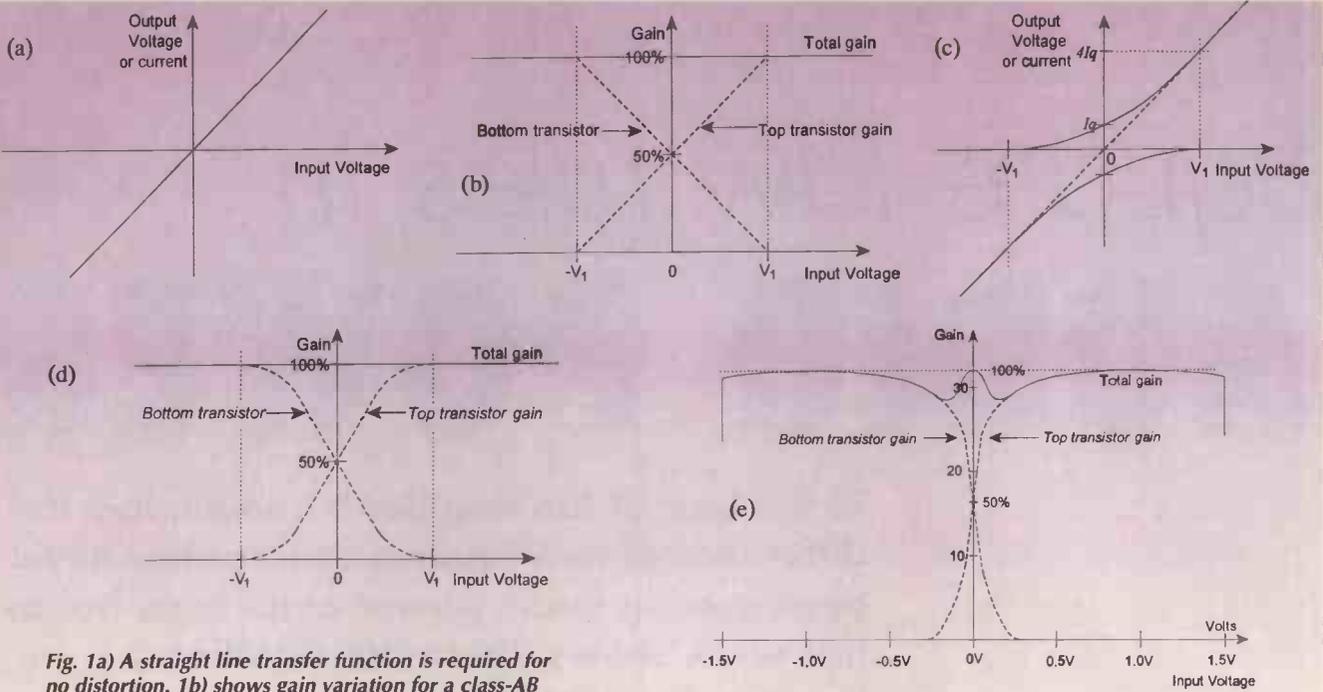


Fig. 1a) A straight line transfer function is required for no distortion. 1b) shows gain variation for a class-AB output stage. Voltage  $V_1$  to  $-V_1$  is the crossover region. Individual gains in the crossover region need to sum to a constant value. In 1c), the transfer functions required for Fig.1b are square-laws in the crossover region and linear beyond. 1d) shows an alternative gain function that also gives no crossover distortion. Both curves must have odd symmetry about the y-axis. In 1e), gain linearity of a bipolar common emitter output stage is shown. Assymetry makes it impossible to eliminate distortion, based on Self's Fig. 8 ref. 6. Transfer function for the bipolar common emitter output stage Fig.1e is shown in 1f). Difference between the average gain of 31 and the output is the distortion component.

conservative amount of global feedback is used to remove any possibility of oscillation.

Using fets as square-law devices, it should be possible to reduce the amounts of feedback required to a level that eliminates complications caused by loading – making amplifier design easier.

The ideal circuit should also be highly efficient – preferably as high as class AB – to minimise cost. Any distortion should consist mainly of a few low-order harmonics rather than the high variety<sup>9</sup>.

Our ears are more sensitive to high-order odd harmonics produced by crossover distortion – particularly if they lie in the sensitive hearing region. Ivor Brown suggests the multiplicity of high order harmonics from crossover distortion reduces spatial definition<sup>8</sup>.

### Differencing two squares

Michael William's article<sup>1</sup> explains the principle of differencing two squares – D2S – also known as 'Curvilinear class-A'. By definition, D2S is class-A since both devices are always conducting. However, the mode of operation shown in Fig. 1c is class-AB – a different class from D2S which I call 'Square-law class-AB'. Only one device conducts when the

input swing exceeds  $\pm V_1$ .

As Williams points out, D2S has the advantage of a lower quiescent current than class-A per output watt. Heat dissipated at idle  $P_q$ , is  $\frac{1}{2}I_{pk}V_{cc}$ , since the quiescent current is set at a quarter of the peak output current ( $I_q = I_{pk}/4$ ).

For split supply rails of  $\pm V_{cc}$ , quiescent power dissipation  $P_q$  is  $2V_{cc}I_q$ , which is  $\frac{1}{2}I_{pk}V_{cc}$ . Neglecting saturation and ripple voltages, this is the same as the output power rating.

Saturation and ripple voltages, say 2V for saturation and  $2V_{rms}$  ripple ( $6V_{p-p}$ ), cause dissipation to rise by 10%. Both conventional class-A and D2S require this same margin which means practical class-A push-pull amplifiers dissipate twice the power of the D2S amplifier per output watt. For class-AB, dissipation peaks at half full power, dissipating typically the same amount as heat. As a result, maximum dissipation is  $\frac{1}{2}$  of maximum output power, so D2S dissipates twice the power of class-AB.

The maximum possible sinewave efficiency for D2S, as detailed in the appendix, is 75%, compared to 50% for push-pull class-A and 78.5% for class-B. Since the efficiency of D2S and class-AB are almost the same, their power

supply rating is likewise. As a result, D2S offers a substantial cost advantage over other types of class-A due to its high efficiency – effectively the same as class-B. Requiring only a larger heatsink D2S is slightly more expensive than class-AB.

Operating in class-A using D2S, rather than class-AB, crossover distortion can be avoided completely at little extra cost. Distortion components are mainly second and third harmonics. Due to component mismatch most of the second harmonic can be trimmed by equalising the gain difference. Third harmonics can be compensated by gain drop in the fet. Trimming these errors can be considered a form of *feed-forward* error correction, relying on the stability of the other parameters to maintain linearity after set-up.

Most amplifiers already require the setting of one preset at manufacture, so another should not be a serious disadvantage.

### Implementing the concept

Douglas Self<sup>6</sup> explored a power-fet square-law circuit (Self's Fig. 2) but found the range for the square-law only extended over a disappointing 80mA range of output current. This circuit was class-AB with only one device

conducting at high currents.

Examining the *V-I* transfer curves of Self's Fig. 10, you can see that considerable local feedback is applied to the fets. About 1V appears across the 0.22Ω source resistors at 5A with 1.5V input. This amount of feedback kills the square-law relationship – even at low currents. Reducing or eliminating these resistors increases the useful square-law current range.

The design example described in the panel shows that *IRF540/9540* power fets could achieve class-A power levels of 100W with distortion as low as 0.0005%, without trimming. This appears possible even with a 12% fet gain drop at peaks, and a 16% mismatch. It suggests that ultra low distortion D2S amplifiers are not only possible, but cheaper than other class-A amplifiers.

**Class AB square-law circuits**

The circuit of Fig. 2 was constructed to evaluate power fets for class-AB. It is similar to Self's Fig. 2 evaluation circuit<sup>6</sup>, minus source resistors.

Driver transistors *Tr*<sub>3,4</sub> provide level shifting for the fets as well as biasing and voltage gain. Unlike conventional class-AB driver circuits the emitters are not coupled. This gives a wider crossover region – wider than the fets' range ±*V*<sub>1</sub>. Effectively, the power fets are open loop, ie they have no source resistors, apart from a small amount of voltage feedback used to trim the higher gain half for symmetry.

Figure 3 shows triangle wave input and output voltages. Supply is reduced to ±22V so saturation can be seen. Open-loop linearity is maintained up to within a few volts of saturation.

Traces are offset by 0.47V to aid trimming. Vertical differences represent the output error voltage.

Deviation of about 0.2V<sub>pp</sub> appears at the ends, covering about 1/4 of the time. Since total harmonic distortion is the ratio of rms error voltage to rms output voltage, the rms error voltage can be calculated using,

$$V_{RMS} = \frac{V_{pp}}{2\sqrt{2}} \sqrt{\frac{t}{T}}$$

where *t/T* is the duty cycle. In this case error voltage is 35mV rms for 12V<sub>rms</sub> output voltage, giving 0.3% thd open loop. Open loop measurements are shown in Table 1.

**Table 1. Open-loop performance of amplifier based on difference of two squares principle. Phase shift was 180° with 8Ω load at 10kHz.**

Load	bias	thd	gain
8Ω	250mA	0.3%	20
4Ω	500mA	0.5%	15
8Ω	500mA	0.5%	30

Fets used here have a 7A/140V rating and *R*<sub>DSon</sub> of 1Ω. Measurement showed their gate thresholds were very low and quiescent voltage across *R*<sub>7,8</sub> was only 1.1V and -0.75V for a quiescent current of 250mA. These fets are still capable of delivering high currents efficiently since gate voltages in this circuit can swing up to 2/3 of the supply voltage, limited

**Efficiency in D2S class-A**

Equations in this panel describe efficiency in D2S class-A using two square-laws.

With a sinewave input each fet has a current waveform given by,

$$I(x) = \frac{I_{pk}}{4} (\sin x + 1)^2$$

$$I_{ave} = \frac{1}{\pi} \int_{-\frac{\pi}{2}}^{\frac{\pi}{2}} \frac{I_{pk}}{4} (\sin x + 1)^2 dx$$

$$\therefore I_{ave} = \frac{3I_{pk}}{8}$$

for each half,


$$P_{in} = 2I_{ave}V_{cc} = \frac{3}{4}I_{pk}V_{cc}$$

and,


$$P_{out} = \frac{V_{pk}I_{pk}}{2} = \frac{(V_{cc} - V_{sat})I_{pk}}{2}$$

$$\therefore \eta = \frac{P_{out}}{P_{in}} = \frac{3}{4}I_{pk} \left(1 - \frac{V_{sat}}{V_{cc}}\right)$$


Maximum possible sinewave efficiency is 75% with *V*<sub>sat</sub> at 0. When *V*<sub>sat</sub> is 5V and *V*<sub>cc</sub> is 35V, efficiency is 64%.

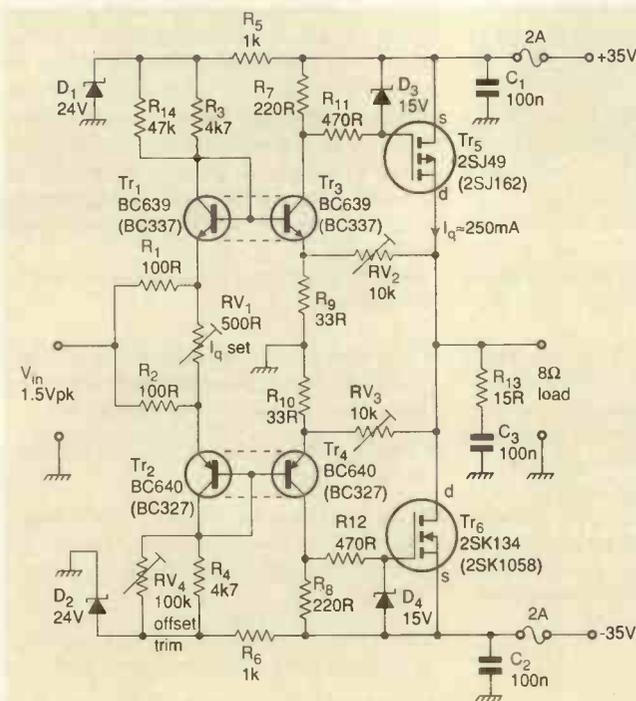

**Fig. 2. Class AB output stage with power fets operating as approximate square-law devices in the crossover region with correction provided by increasing gain of the driver transistors.**

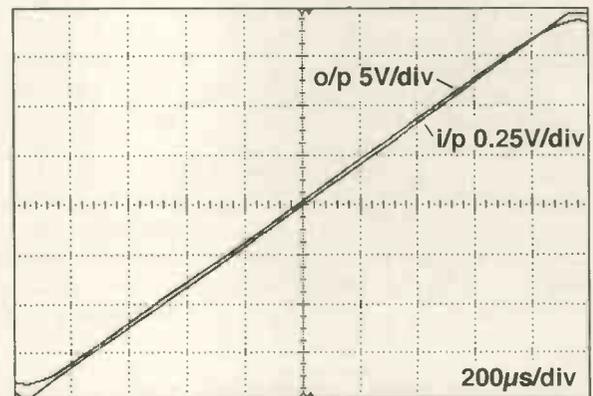

**Fig. 3. Output of circuit of Fig. 2 with a triangle wave input shown for comparison.**

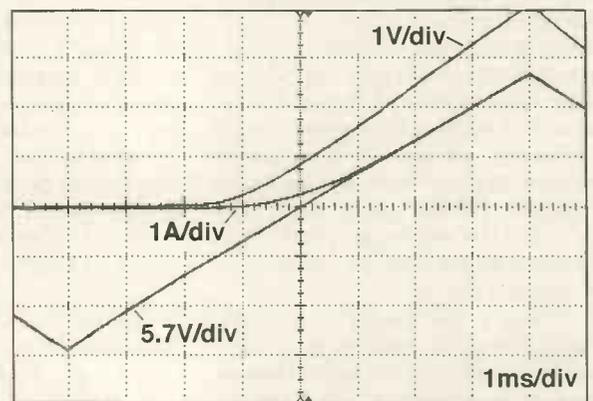

**Fig. 4. Curves for Fig. 2 with output voltage, *Tr*<sub>3</sub> current and gate voltage show square-law region, linear region and non-linear gain of driver used to compensate for fet gain drop.**

# A 100W D2S fet amplifier

For 100W continuous into 8Ω, output swing is ±40V peak at ±5A peak. For D2S, quiescent current must be set at 1/4 I<sub>pk</sub>, or 1.25A.

Peak input voltage V<sub>1</sub> can be calculated for a specified distortion level as follows. Velocity saturation<sup>5</sup> causes a reduction in output current at high current, causing gain compression.

Assuming matched fets, there is no second harmonic, but there is mostly third harmonic distortion for which,

$$D_3 = \frac{\delta^+ + \delta^-}{24}$$

(eq. 12 of ref. 11).

With velocity saturation,

$$I_D(\theta) = \frac{\beta(V_G - V_T)^2}{2[1 + \theta(V_G - V_T)]}$$

Taking the ratio of current with saturation velocity to the ideal current gives

$$\frac{I_D(\theta)}{I_{D(ideal)}} \cong 1 - \theta(V_G - V_T).$$

This shows the gain compression factor Δ≡θ(V<sub>G</sub>-V<sub>T</sub>). For, say, 1% of third-harmonic at full power using the equation for D<sub>3</sub>, with δ<sup>+</sup>δ<sup>+</sup>=δ<sup>-</sup>=ΔG, gives ΔG=0.12. Using a typical value for θ of 0.1V<sup>-1</sup>, peak gate rise V<sub>G</sub>-V<sub>T</sub> is 1V. This means that V<sub>in</sub> is ±0.5V<sub>pk</sub>.

With a 3V threshold voltage, the fets would need to be biased<sup>5</sup> at 4V, reducing by 6mV/°C. Since peak current is 5A with a gate rise of 1V, the fet requires a gain of 5A/V. The minimum value of β, calculated from g<sub>fs</sub>=β(V<sub>G</sub>-V<sub>T</sub>), is 5A/V<sup>2</sup>.

For an IRF540, β can be found from the data sheet V-I transfer curves by plotting √I<sub>D</sub> against V<sub>G</sub> using,

$$slope = \sqrt{\frac{\beta}{2}}$$

This yields a β of 11A/V<sup>2</sup> with V<sub>T</sub> at 3V for both the IRF540 and IRF640.

Their complements, the IRF9540 and 9640, typically have betas that are 25% lower. This means they are suitable for a 100W D2S class-A amplifier with 1% thd, open loop.

Fet gain mismatch causes the gains at each end to be different, giving mainly second harmonic distortion, calculated from,

$$D_2 = \frac{\delta^+ - \delta^-}{8}$$

(eq. 12a of ref. 11). A mismatch of 8% adds 1% second harmonic distortion. Total open loop distortion is 1.4%,

$$D_T = \sqrt{D_2^2 + D_3^2}$$

Open-loop voltage gain is calculated from A<sub>V</sub>=G<sub>fs</sub>R<sub>L</sub>=80 where the overall gain G<sub>fs</sub> is the same as the g<sub>fs</sub> calculated above at the end points. Distortion of this output stage can be compared to other unity gain output stages using the relationship,

$$D = \frac{D_{ol}}{1 + \beta A_{ol}}$$

where β is 1 for 100% feedback.

With a gain of 80 and 1.4% open loop distortion, the equivalent unity gain distortion is 0.02%. Similarly, a gain drop of 20% with a gain of 80 is equivalent to a drop of 0.3% at unity gain. Douglas Self's class-A output stage (Fig. 3 of ref. 10) shows a gain drop of 0.3% at 70% output swing at 30W, giving 0.0012% thd at 20kHz with 30dB global-feedback factor, also at 20kHz.

by zeners. For a low saturation voltage of say 3V, the fets would be restricted to 3A (50W average) but linearity is still good up to 5A allowing 100W average into 8Ω, making them cost effective.

To measure fet current, a 0.1Ω sensing resistor was placed in the supply rail, with no noticeable effect on linearity. Figure 4 shows fet current with output voltage using a triangle wave input after trimming for best linearity. The output voltage is vernier scaled until this curve merges with the current trace. This allows square law and linear regions to be clearly seen in the top transistor similar to the curves shown in Fig. 1c.

Gate voltage is also displayed at 1V/div. The current waveform appears to be a square-law within the crossover region and outside the gain it is reasonably linear. The square-law crossover region covers an input swing of ±0.8V. The quiescent current of 220mA was stable with temperature on a 1°C/W heatsink.

Current at the end of crossover region is about 0.8A – four times I<sub>q</sub> – indicating square-law operation.

Gain of the driver transistor can be measured from the gate voltage waveform. It doubles from -V<sub>1</sub> to +V<sub>1</sub>. Increasing the gain of the driver transistors offsets the fet gain drop due to velocity saturation within the square-law region, resulting in a near ideal square-law relationship. At V<sub>1</sub> the fet has gone linear<sup>5</sup>. This demonstrates that the falling gain of fets is not an obstacle for the square-law principle.

Theory<sup>5</sup> shows gain falls by 50% at high currents. Using,

$$G_{fs} = \sqrt{2\beta I_D} - 3\theta I_D$$

the gain peaks at,

$$G_{fs} = \frac{\beta}{60}$$

where,

$$I_D = \frac{\beta}{18\theta^2}$$

This is half the gain of the ideal fet where θ is 0 and velocity saturation does not occur. It is possible to calculate the beta required for a given amplifier, given θ of say 0.11, using β=18θ<sup>2</sup>I<sub>D</sub>, where I<sub>D</sub> is the output current at the inflection point (G<sub>fs</sub> maxima, where the V-I plot curves backwards). Current I<sub>D</sub> is therefore arbitrary. It simply depends on how much of the rated capacity of the fet is to be used.

A useful technique to find θ and β from data sheets that give the G<sub>fs</sub> versus I<sub>D</sub> curve, that shows a peak is,

$$\beta = \frac{2G_{pk}^2}{I_{pk}}$$

and,

$$\theta = \frac{G_{pk}}{3I_{pk}}$$

G<sub>pk</sub> and I<sub>pk</sub> are G<sub>fs</sub> and I<sub>D</sub> at the maxima.

Values of R<sub>7,8</sub> were altered to suit the amount of compensation required for a particular fet and operating current range. Increasing bias voltage gives less gain compensation for higher gate bias voltages of modern power fets. I expect equations can be found to calculate resistor values from β, θ, peak I<sub>D</sub>, etc.

Interestingly, the slow gain change of bipolar class-AB circuits – the cause of crossover distortion – is advantageous in offsetting the slow gain change of the fets from square-law to linear. Modern op-amps with output swings of ±10V can be used to drive output stages if they have voltage gain. For example, the OPA627, although expensive, can give distortion figures as low as 0.0003%<sup>12</sup> with a gain of 3 and the NE5534 can give almost as good performance<sup>13</sup> at lower cost. They can provide suitable slew rates, and more importantly, reduce component count. They are probably not more widely used in this type of application because the usual starting point in a design is with a voltage follower, unity gain, output stage.

Other advantages of using output stages with gain are:

- Improved output stage stability due to lower feedback factor. This makes it easier to ensure less than unity loop gain at 180°.
- Higher efficiency due to lower saturation voltage.
- Biasing current can be derived from a regulated/filtered supply, improving power supply rejection and its resulting effect on distortion.
- Slew rate required for the driving amplifier is reduced due to the output stage gain.
- Driver transistors only need to be rated at half the supply voltage.
- Output is a current source so current limiting can be performed by simply limiting input voltage swing using diodes.

**Another square-law circuit**

The circuit of Fig. 5 uses 74HCU04 cmos inverters as drivers for the bipolar output transistors. In this arrangement ambient temperature variations need not affect linearity, whereas changes in load cannot.

C-mos inverters provide well matched complementary fets, readily available and cheap. When the six inverters in a HCU04 are paralleled, 120mA can be safely handled, at which point the gain drops by 10%. This is sufficient to drive a bipolar power transistor for 5A output, given a beta of 50 at 5A.

For six HCU04 inverters in parallel, fet parameters are  $\beta=50\text{mA/V}^2$ ,  $V_T=0.8\text{V}$  and  $\theta=0.12(\text{V}^{-1})$ . Matching of p and n beta values was within a few percent. Devices with the same date mark had almost identical betas, although the threshold voltages of p fets were typically 80mV higher than n fets for those tested.

The HCU04 runs from 5V. Figure 5 uses a level shifter with one HCU04 driving both sides to increase voltage swing.

Figure 6a shows an alternative circuit giving lower distortion by using n fets for better matching. Here  $Tr_{7,9}$  are acting as virtual complements.

Gain matching of each half is achieved with  $RV_{2,3}$  in series with small signal diodes  $D_{5,6}$ . This compensation method is effective, allowing large gain variations in bipolar transistors as well as partly linearising beta fall-off in the bipolar transistors above 1A.

Usually, the output transistors have a resistor directly across the base-emitter terminals to remove base leakage current and speed up turn off. These resistors are not used in this application. This is due to the fact they cause unacceptable non-linear gain at low currents.


One solution to prevent thermal run-away is to keep the transistors cool with a larger heatsink. An alternative is the circuit of Fig. 6b. Temperature sensing diodes  $D_{7,8}$  can be soldered to a lug held by the TO3 bolt to the case of  $Tr_{5,6}$ . High-gain transistors  $Tr_{11,12}$ , with  $\beta \geq 300$  across the base-emitter terminals, remove the temperature-dependent leakage current and prevent thermal run-away allowing minimal heatsinks.

In Fig. 5, fets  $Tr_{7,8}$  are used as a bias voltage generator. They maintain a constant bias current through fets  $Tr_{9,10}$  since current through  $Tr_{7,8}$  is mirrored into  $Tr_{9,10}$  independent of ambient temperature changes. Impedance of the bias generator is small compared to  $R_{5,6}$  supplying the bias, being  $1/g_{fs}$  where  $g_{fs}$  is  $\sqrt{2\beta/I_D}$  or  $100\Omega$  since  $I_D$  is 1mA.

With a low impedance voltage drive there is little incremental drop across the bias generator as the input voltage varies. Since the input voltage swing is only  $\pm 2\text{V}$ , resistors  $R_{5,6}$  can be used rather than active current sources to set the bias current.

Power supply ripple rejection is about 30dB, with zeners  $D_{3,4}$  providing another 30dB. Transistors  $Tr_{1,2}$  compensate for temperature change in  $Tr_{3,4}$  since they are coupled thermally. Higher power versions will require a heatsink. Tests on the 50W version were done

**Fig. 5. This class AB amplifier uses complementary mosfets in the emitters of the drivers to give accurate square-law current differencing in the crossover region and a linear gain outside the crossover region.**

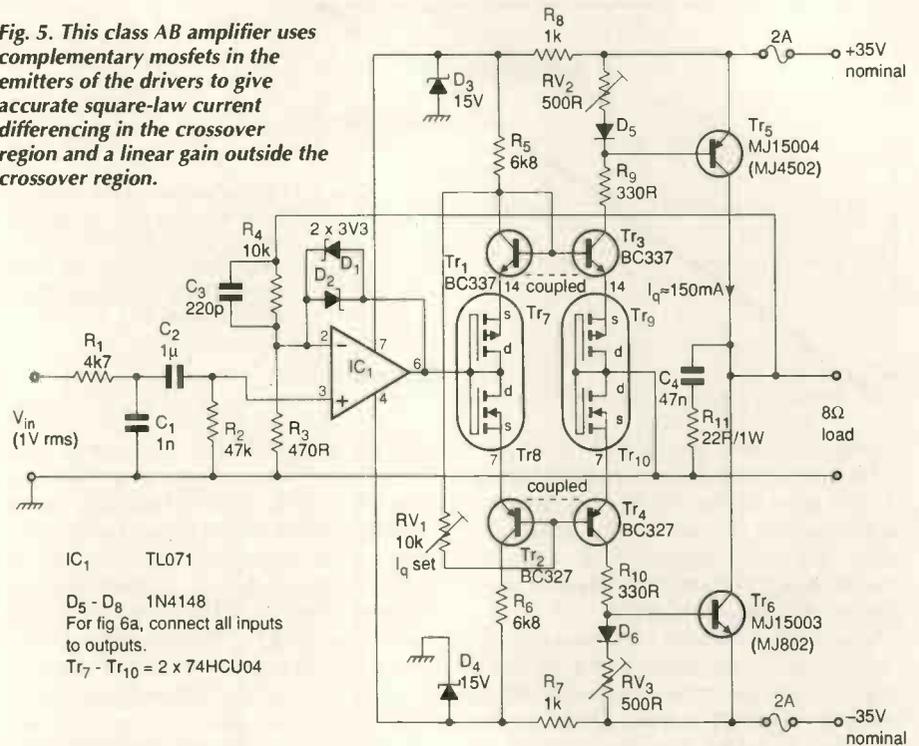

IC<sub>1</sub> TL071  
 D<sub>5</sub> - D<sub>6</sub> 1N4148  
 For fig 6a, connect all inputs to outputs.  
 Tr<sub>7</sub> - Tr<sub>10</sub> = 2 x 74HCU04

without this heatsink.

Transistors  $Tr_{3,4}$  act as voltage followers. Input voltage is transferred to the gates of  $Tr_{9,10}$ . The resulting drain currents are level shifted by  $Tr_{3,4}$  to drive the output transistors. Resistors  $R_{9,10}$  limit the output current for output shorts to prevent secondary breakdown. At a  $V_{ce}$  of 50V, the  $I_{SB}$  rating for these transistors is 4A.


Resistors  $R_{9,10}$  can be calculated assuming a beta of 50 at 4A. As a result, base current is 80mA so 30V across  $R_{9,10}$  requires 330Ω resistors. These resistors also reduce dissipation in the drivers, allowing free-standing TO92 devices for a 50W version. Transistors  $Tr_{5,6}$  have gains of 110 and 80 respectively at 1A, both falling to 50 at 5A. MJ15003/4s were used because of availability, but the MJ802/MJ4502 pair is a better choice for a 50W version with similar  $I_{SB}$  ratings at half the cost.

Typically, the bias voltage for optimum bias of 150mA was 1.7V in Fig. 5, with 785mV across n-channel fet  $Tr_8$  and 863mV across the p-channel fet  $Tr_9$  - a difference of 83mV.


This is attributed to differences in the p-n threshold voltages. It was found to cause one side to finish its square-law before the other and so give non-linearities toward the ends of the crossover region. These could not be trimmed out since the fets are internally coupled.

Using all n-channel fets for  $Tr_{7-10}$ , Fig. 6a, the bias voltages were to within 6mV and non-linearity in the crossover region was removable by trimming the quiescent current.

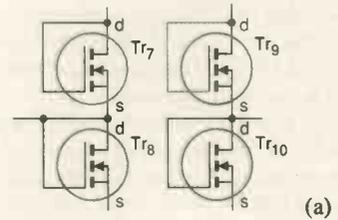Digital meters were used in a static test to accurately measure Fig. 5's  $V-I$  transfer function at each half of the collectors of  $Tr_{3,4}$  before the output stage. Plotting the results manually showed surprisingly linearity to meter accuracy of  $\pm 0.1\%$  right up to 100mA.



(a)

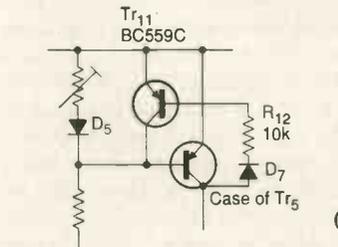

(b)

**Fig. 6a) Alternative arrangement for  $Tr_{7-10}$  giving better matching. Transistors  $Tr_{7,8}$  are virtual complements. Use four 74HCU04s for  $Tr_{7-10}$ . Source is pin 7. Leave pin 14 floating.**

**Fig. 6b) Collector-base leakage current compensation circuit to prevent thermal runaway in  $Tr_5$ . A similar circuit is used for  $Tr_6$ , not shown.**

However, the gain of each half was different, at 69mA/V and -64mA/V. This is compensated for in this circuit using  $RV_{2,3}$ .

Points where the fets change from square-law to linear were considerably different - from 20mA upwards and -25mA downwards. Another plot of  $\sqrt{I_D}$  versus  $V_{in}$  showed the square-law relationship was accurate up to the 20/25mA points.

The reason for the abrupt change from square-law to linear required for class-AB is not yet fully understood. It may be caused by pinch-off, where the fet changes from current

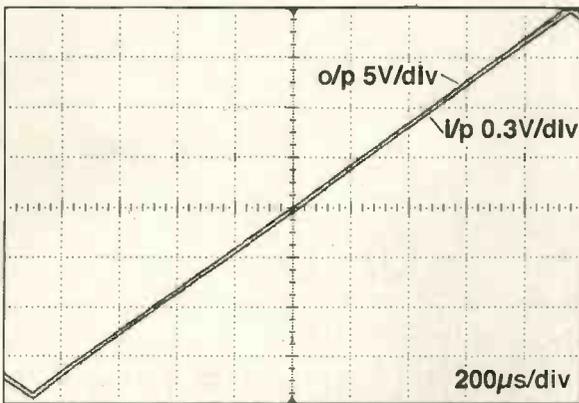


Fig. 7. Output of circuit of Fig. 5 but all n-fets (Fig. 6a) with a triangle wave input shown for comparison. It shows the open loop linearity before applying global feedback.

saturation to resistive mode as  $I_D$  increases.

Dynamic testing of the output stage of Fig. 5, after trimming for best linearity showed a 0.2V deviation over  $\pm 20V$ . When plotted, the static test also showed 0.2V deviation. Distortion at 500Hz was 0.3% when the swing reached 60% of the full output.

Most of the harmonics were third and fifth order. Voltage gain was 13 with an  $8\Omega$  resistive load. Full power bandwidth was 70kHz, and gain-bandwidth product 1MHz. Second harmonic switching distortion, seen on an oscilloscope as differences in the bandwidth of the output transistors, reached a maximum of 3% at 10kHz and 33V pk-pk, first noticeable at 2kHz. At 5kHz distortion is 1%.

The negative side is the slower half and generally has the higher gain. This allows a  $10\Omega$  resistor in parallel with a  $1\mu F$  capacitor to be added in series with the emitter of  $Tr_4$  to give lead compensation to the slower half. This allows switching asymmetry to be almost cancelled over the audio range, giving similar open-loop distortion levels to the power fet circuit of Fig. 2. In closed-loop the power fet circuit can achieve lower distortion due to higher open-loop gain and bandwidth.

Modification Fig. 6a reduced total harmonic distortion after trimming by a factor of 3 to 0.1% at 500Hz. Figure 7 shows the open-loop transfer curve. Based on the static test, remaining non-linearity is probably due to the bipolar output transistors. There was only a slight temperature induced change in linearity, observed between idle and running continuously at maximum power.

Load impedance changes did not have any noticeable affect on linearity for the same output current swing. Without collector-base leakage compensation, quiescent current through the output transistors would rise from 150mA of optimum bias, to 230mA after running at full power for some time. This variation does not affect linearity.

Circuit Fig. 6a has demonstrated that a stable 0.1% thd can be achieved up to 2kHz open loop with a gain of 13 using readily available non-selected parts. Closed-loop distortion could not be measured with the HP54601A using FFT. Closed loop thd however is expected to be 0.001% at 1kHz and 0.006% at 20kHz. This assumes an TL071 providing about 40dB feedback at 20kHz.

In closed loop,  $C_3$  provides some phase

advance above 70kHz – the output stage roll-off point – keeping the loop phase less than  $180^\circ$  until the gain has fallen below unity.

Using similar transistors in a complementary feedback-pair output stage, Self's Fig. 8 class-AB amplifier of reference 2 shows distortion reaching 0.01% at 20kHz, using a 37dB feedback factor at 20kHz. This he attributes mainly to crossover and switching distortion.

With a 37dB feedback factor, output stage distortion can be calculated to be 0.7% with optimal biasing – 50 times higher than the 0.014% expected from an optimally biased complementary-feedback pair<sup>14</sup>. Presumably the 0.7% figure is mostly due to switching distortion and not component mismatch. The emitter resistors determine gain matching at high current – not the transistors.

The fet output stage is expected to give 0.001% thd at 20kHz since it has higher gain and wider bandwidth allowing a higher feedback factor at 20kHz. It is also expected to match the class-A design of 0.0012% at 20kHz by Self<sup>10,4</sup> with a similar spread of low order harmonics.

### Setting optimum bias

I developed a straightforward technique for setting optimum biasing using an oscilloscope and triangle wave source. The alignment is carried out with an open loop by connecting a  $100\mu F$  capacitor across  $D_1$ . Trimming is best achieved at about 50% of the maximum output swing by applying about 1.5V peak triangle wave with an  $8\Omega$  resistive load.

Display the input and output waveforms together, as Fig. 3. Set  $RV_1$  at zero and  $RV_{2,3}$  at maximum. Raise quiescent current to about 150mA then determine which half shows the lowest slope. If, for example, the lower half has the lower gain then vary  $RV_1$  for best linearity – lower half only. Lastly, reduce  $RV_2$  until the upper half has the same slope as the lower half. The overall line should then be straight.

### Better things yet to come?

The static test showed that given a sufficiently linear current mirror output stage, crossover and high-end gain deviation could go as low as  $\pm 0.1\%$  for open loop class-AB. If this were achieved, the output stage alone could go as low as 0.001% thd with unity gain, since open loop gain  $\geq 10$ . This would be two orders of

magnitude lower than the best possible using classical class-AB circuits.

A technique that gives an output stage excellent linearity has been used in a fast power amplifier<sup>15</sup>. As for bias stability, integrating  $Tr_{1-4}$  and  $Tr_{7-10}$  on the same chip must provide ultimate performance. Integrating can also allow automatic biasing using a slave circuit<sup>16</sup> to monitor linearity and correct any changes.

### In summary

Preliminary results from two different class-AB circuits show the square-law nature of fets can be used to reduce distortion below the levels of classical fet and bipolar output stages. The only drawback is that two presets are used for alignment instead of one, as is normally the case.

It is pleasing to see fets go linear at higher currents in a way that allows near elimination of class-AB crossover distortion. Two different techniques have demonstrated that class-A performance is possible using class-AB – one circuit using power fets over their full current range, and the other using fets driving bipolar power transistors.

Bipolar output-stage bandwidth degrades performance above 2kHz. The power fet output stage is free from switching distortion and allows more feedback at the top audio end giving superior overall performance. These fet based circuits demonstrate that class-A performance need not be traded for class-AB efficiency.


I would like to thank Manawatu Polytechnic, New Zealand for its help in preparing this article. ■

### References

- Williams, M, 'Making a linear difference to square-law fets', *EW+WW*, Jan 94, p. 84.
- Self, D, 'Distortion in Power Amplifiers: Part 5', *EW+WW*, Dec 93, p. 1010.
- Blomley, P, 'New Approach To Class B', *WW*, Feb 71, p. 57.
- Self, D, 'Distortion in power amplifiers: Part 7', *EW+WW*, Feb 94, p. 137.
- Finnegan T, 'Going linear with power mosfets: Part 1', *EW+WW*, Aug 92, p. 637.
- Self, D, 'Common emitter amplifiers', *EW+WW*, July 94, p. 550.
- Brown, I, 'Between amplifier and speaker', *EW+WW*, Feb 95, p. 114.
- Brown, I, 'Feedback and fets in audio power amplifiers', Feb 89, *EW+WW*, p. 126.
- Moir, J, 'Just detectable distortion levels', *WW*, Feb 81, p. 34.
- Self, D, 'Distortion in power amplifiers: Part 8', *EW+WW*, March 94, p. 226.
- Cherry, E, 'Ironing out distortion', *EW+WW*, Jan 95, p14.
- Giesberts, T, '1000-Hz sine wave oscillator', *Elektronika*, Dec 94, p. 5.
- Duncan, B, 'How clean is your op-amp?', *EW+WW*, Jan 93, p. 42.
- Self, D, 'Distortion in power amplifiers: Part 8', *EW+WW*, Nov 93, p933.
- Hegglin, I, 'Fast power amplifier for audio', *EW+WW*, Mar 95, p. 240.
- Park, C, Schaumann, R, 'Design of a 4MHz Analog Integrated CMOS Transconductance-C Bandpass Filter', *IEEE, J. Solid-State Circuits*, Vol 23, No. 4, Aug 88, p. 987-996.
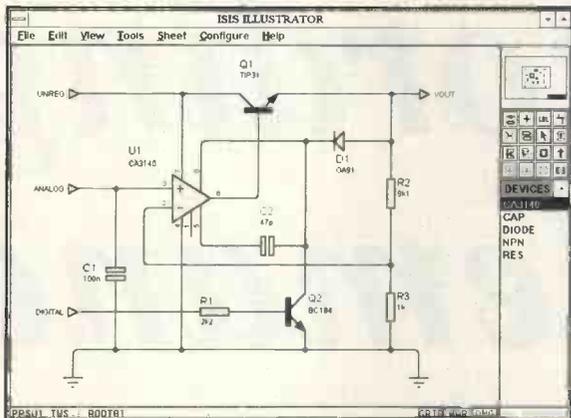
## CADPAK for Windows

CADPAK is especially suited to educational, hobby and small scale schematic and PCB design. CADPAK includes both schematic drawing and 32-bit PCB drafting tools but as an entry level product, there is no netlist link between them.




The schematic drawing module of CADPAK, ISIS Illustrator, enables you to create circuit diagrams like the ones in the magazines.

- Runs under Windows 3.1 making full use of Windows features such as on-line help.
- Full control of appearance including line widths, fill styles, fonts, colours.
- Automatic wire routing & dot placement.
- Fully automatic annotator.
- Complete with device and comprehensive package libraries for both through hole and SMT parts.
- Advanced route editing allows deletion or modification of any section of track.
- Gerber, Excellon and DXF outputs as well as output via Windows drivers. Also includes Gerber viewer.
- Exports diagrams to other applications via the clipboard.
- CADPAK is also available for DOS.

**CADPAK FOR WINDOWS ..... £ 149**  
**CADPAK FOR DOS ..... £ 79**
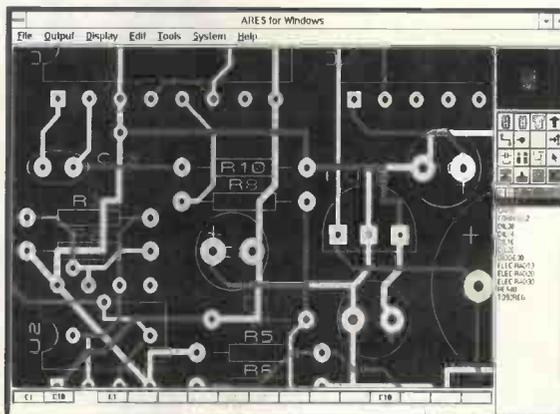
## PROPAK for Windows

PROPAK has all of the features in CADPAK plus netlist based integration, automatic power plane generation and a powerful auto-router. PROPAK includes enough schematic capture and PCB design functionality for all but the most demanding applications.



PROPAK's schematic drawing editor ISIS ILLUSTRATOR+ includes even more features than ISIS ILLUSTRATOR. PROPAK's 32-bit PCB design tool, ARES for Windows, is our most powerful and easy to use yet.

- Multi-sheet and hierarchical designs.
- Netlist link between modules guarantees consistency between schematic and PCB.
- Netlists are also compatible with SPICE-AGE and most other electronics CAD packages.
- Generates a full bill of materials.
- ASCII data import facility.
- Electrical rules and connectivity checkers.
- Ratsnest display with automatic update during placement and routing.
- Multi-strategy autorouter gives high completion rates.
- Power plane generator creates ground planes with ease.
- PROPAK is also available for DOS.

**PROPAK FOR WINDOWS ..... £ 495**  
**PROPAK FOR DOS ..... £ 395**

**Call or fax us today for a demo pack. Please state whether you would like a DOS or Windows pack.**

Prices exclude postage (£5 for UK) and VAT. ISIS ILLUSTRATOR and ARES for Windows are also available separately. All manufacturers trademarks acknowledged.

**labcenter**  
**Electronics**  
 53-55 Main St. Grassington, N. Yorks. BD23 5AA  
 Tel: 01756 753440 Fax: 01756 752857

# Recording on demand

**As a learning aid for advanced students, note taking is only useful to the dextrous. François Steenkeste's delayed recorder is designed to make the alternative - tape recording lessons - a much more efficient process.**

**N**ote-taking is a complex activity requiring listening, thinking, manual dexterity and eyesight. Not everyone takes notes equally well. Visually impaired people for example can be at a distinct disadvantage at university, when note taking skills can make the difference between a pass and a fail.

Tape recordings help, but sorting a few useful ideas from a long speech can be very time consuming.

With the note-taking aid described here, speech is recorded into a rolling buffer memory. When the listener perceives that an important point has been made in the speech, he or she simply presses the record button - after the event.

Unlike a tape recorder, this system records not the real-time speech, but a delayed representation of it. In this way, ideas already spoken can be recorded provided that the button is pressed before the rolling delay has expired.

## Delayed recording details

To obtain a few seconds delay, a digital memory and a-to-d/d-to-a converters are used, Fig. 1. Memory is organised as an endless loop by a memory controller, making it easier to reconstruct the audio-signal after the delay.

Digital information coming from the microphone via the a-to-d converter is sent to ram address  $x$  by the memory controller. During the same sample period, the memory controller reads the bits contained in the ram address  $x+1$ , incrementing the address counter by one ready for the next read/write. These three operations are repeated each sample period.

If the endless loop contains  $n$  addresses, the information stored at address  $x$  will be read  $n$  sample periods later. One complete memory cycle time,  $d$ , is represented by the time taken to sample one converter reading multiplied by the total number of addresses.

The d-to-a converter receives this informa-

tion and sends the corresponding analogue signal towards the magnetic head. Provided the listener operates the remote control before the end of the delay period, the motor turns on and the signal is recorded.

The three switches of Fig. 2 represent analogue multiplexers/demultiplexers. These give access to the recording and playback functions of the recorder. They are controlled by the keyboard via logic. If  $S_{1,2}$  are in position A, the device records. In position B, playback takes effect. Delay position, A, and the normal position, B, are controlled by  $S_3$ .

Playback circuitry is provided by the OKI MSM6310. This device is designed for endless loop recording in eight-bit pulse-code modulation and is used to drive the endless loop.

Three units make up the internal circuit. The input unit comprises a line amplifier, low pass filter and eight-bit a-to-d converter. An eight-bit d-to-a converter followed by a low pass filter forms the output unit. Finally, there is a control unit for one or two dynamic-ram segments. This control unit also drives the remote control, motor and sample frequency.

Delayed recording and repeated playback depend on the remote control. When the operator presses the button, the motor command is given by an output from the MSM6310. In the case of delayed recording, the analogue signal corresponding to the idea spoken  $d$  seconds earlier is recorded on tape.

When the speaker finishes giving relevant information, the listener presses the remote control a second time. After delay  $d$ , the motor is stopped. This avoids losing the last piece of information contained in the endless loop memory.

In the repeat mode, the user operates the remote control in order to re-hear the last seconds of playback. Consequently, the motor is stopped and the memory content is repeated on the loudspeaker until a second action on the remote control turns the motor back on.

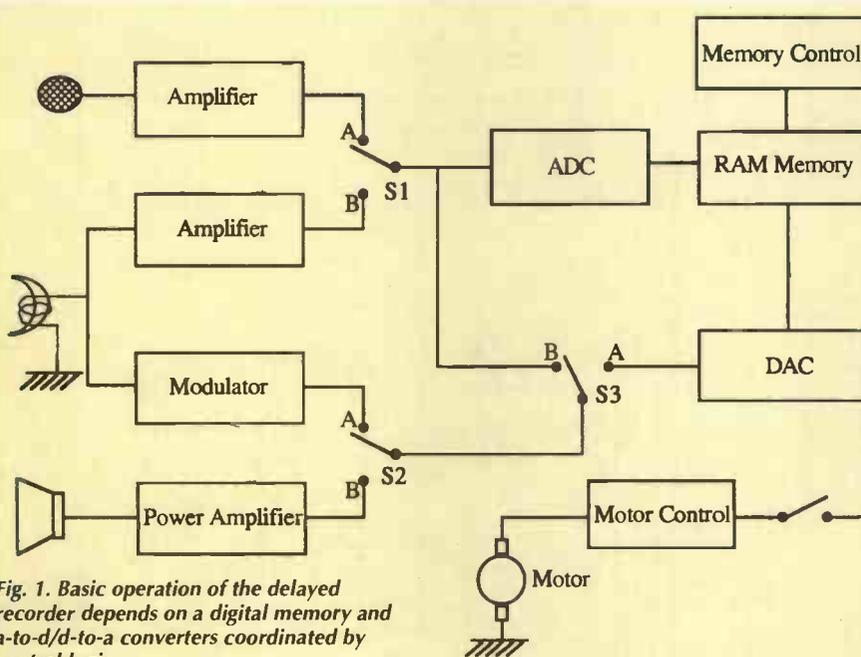


Fig. 1. Basic operation of the delayed recorder depends on a digital memory and a-to-d/d-to-a converters coordinated by control logic.

**Implementing the recorder**

At the heart of this recorder is the *MSM6310* controller, connected to two 256K×1-bit *MSM41256* dynamic rams, Fig. 3. The device controls address lines, column address strobe signals, row address strobe signals and the memory write enable signals.

Double-pole, three-way slide switch *Sw4* allows selection of delay time with a duration of 2, 4 or 8 seconds by controlling both RAMS and FSS inputs. A high level to the RAMS input informs the *MSM6310* IC that an external dynamic ram is connected. When the same level is applied to the FSS input, the crystal frequency of 8MHz is divided by 1024, giving around an 8kHz sampling frequency. If this level is low, the divisor is 512, doubling the sampling frequency.

**Analogue section**

Recording and playback are provided by the analogue section, under control of the *4053B* analogue multiplexer-demultiplexer. When the *Ob4* NOR gate output is low, the microphone's signal is recorded on the tape.

Transistor *Tr6* buffers the built-in microphone signal and feeds an *SL6270* gain controlled pre-amplifier. This IC is designed to accept signals from a low sensitivity microphone and provide a constant output signal for a 50dB input range.

Dynamic range, attack and delay times are controlled by the *R35/C14* network. The signal is amplified by the *MSM6310*, whose 40dB gain is fixed by network *R38/R40*. The amplifier output, AMPO, together with the output of the internal d-to-a converter, DAO, is connected to the analogue multiplexer-demultiplexer. Output of the multiplexer-demultiplexer is linked to the *MSM6310* low-pass filter.

This implementation allows the user to choose between a recording with or without delay, DAO/AMPO. Amplifier *A3* mixes the low-pass filter output with the 33kHz signal of controlled oscillator *A2* and a 50Hz signal from oscillator *A4*.

Oscillator *A4*, controlled by *Sw7*, allows marking of the start of a new recording. The mixed signal is then sent through the *R58/C27* network into magnetic head *H1*. During recording, erase head *H2* and oscillator *A2* are activated by a high level on *R34* and *R51*.

Conversely, in playback mode, the *Ob4* NOR gate output is high. In this instance, the audio signal is supplied by the tape, through the magnetic head *H1*, and amplified by *Tr8*. During playback, this signal's source replaces the microphone in the amplifier chain detailed above. In the same way, during playback, amplifier *A3* output is connected to the *MSC1191* power amplifier and the built-in speaker.

Figures 4 and 5 show the bandwidth of the


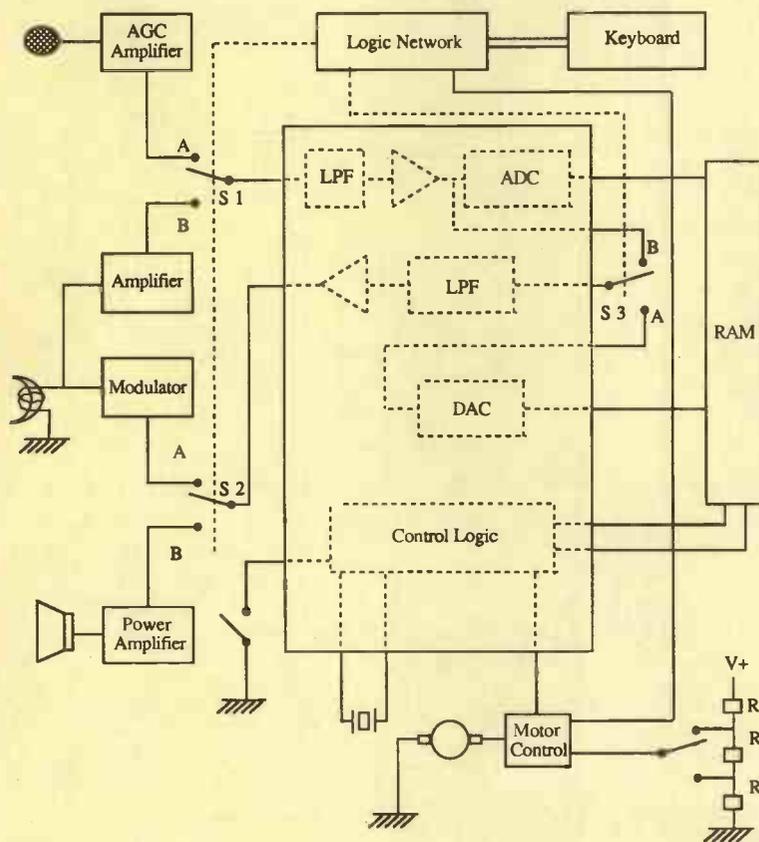


Fig. 2. Delayed/normal recording together with repeat/normal playback functions of the recorder are achieved through analogue multiplexers/demultiplexers controlled via a logic network.

Fig. 3. The MSM6310 - designed for endless loop recording in 8-bit pcm - is the backbone of the delayed voice recorder.

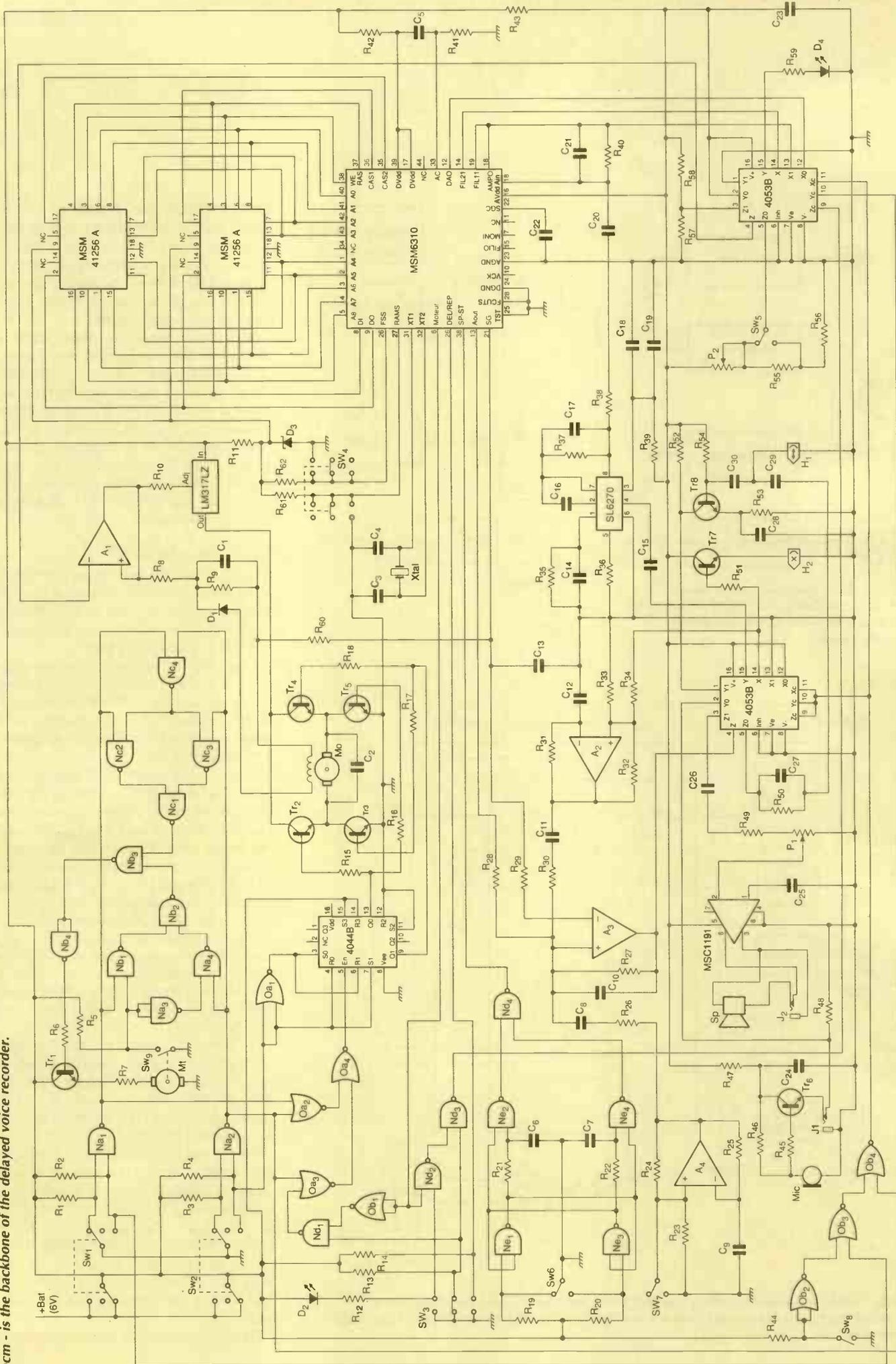

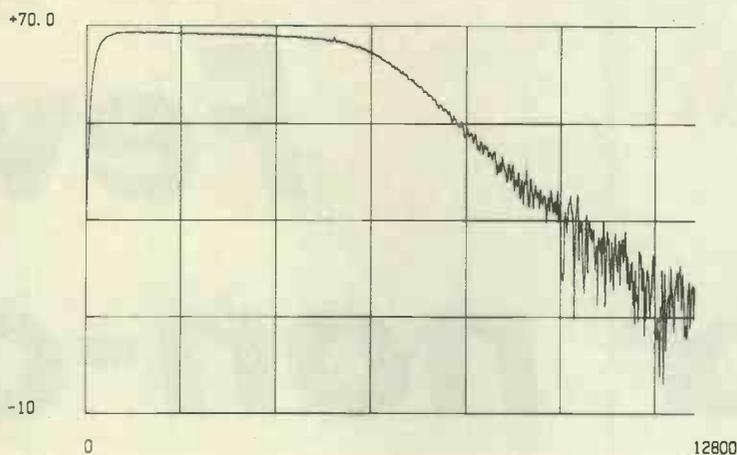


Fig. 4. A 16kHz sampling frequency, with a delay of 2 or 4 seconds, results in a -3dB bandwidth of 270-5600Hz. Horizontal scaling is 2kHz/div and vertical is 20dB/div.

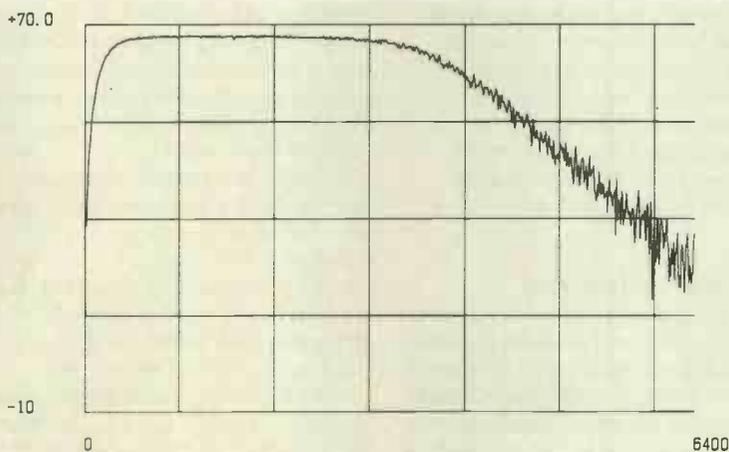


Fig. 5. At eight seconds, sampling frequency falls to 8kHz, resulting in a bandwidth of 260-3450Hz. Horizontal scaling is 1kHz/div while vertical is 20dB/div.

amplification chain between the  $Tr_6$  and AOUT of the  $MSM6310$ . When the delay time is fixed at 2 or 4 seconds, the sampling frequency is 16kHz. This results in a -3dB bandwidth equal to 270-5600Hz, Fig. 4. At 8 seconds, the sampling frequency reduces to 8kHz and the bandwidth to 260-3450Hz, Fig. 5.

**Logic section**

The logic circuitry is designed to drive an electrically-controlled mechanism made by Olympus. The heads are positioned by a dc motor driving a gearwheel and cam. This closes  $Sw_3$  when the magnetic heads are near the tape.

Main functions of the recorder are controlled by slide switches. Playback/record is controlled by  $Sw_1$  and rewind/fast forward by  $Sw_2$ . Output levels of gates  $Na_{1,2}$  and the status of  $Sw_3$  drive the exclusive-or circuit comprising NAND gates  $Na_3$  and  $Nc_4$ .

The tape motor is driven by two three state set-reset latches within the  $4044B$ , connected to transistor network  $Tr_{2,5}$ . Tape direction is indicated by  $Oa_1$ . Control depends on  $Sw_1$ - $Sw_2$  and the 'motor' output of the  $MSM6310$  circuit, through a logic network comprising four two input NOR gates  $Oa_{2,1}$  and  $Nd_1$ .

The motor has an inductive tachymetric generator whose output signal is used to adjust the motor's speed. This signal is compared with a reference voltage from resistor networks  $R_{57}/R_{58}$  or  $P_2/R_{55}/R_{56}$ , by amplifier  $A_1$ .

This amplifier controls the  $LM317$  adjustable regulator.

Network  $R_{57}/R_{58}$  indicates fast forward and rewind. The two-position slide switch  $Sw_5$  allows the user to choose the tape speed of 2.4cm/s or 1.2cm/s.

Record/playback switch  $Sw_3$  drives the input DEL/REP of the  $MSM6310$  and controls the analogue switch of the  $4053B$  via  $Nd_{2,3}$ . In addition, contact  $Sw_8$  on the microcassette holder detects whether the cassette can be erased. If the cassette's erase-protection tab is broken, gates  $Ob_{2,4}$  prevent the multiplexers/demultiplexers from establishing the recording circuit.

Finally,  $Sw_6$  together with gates  $Nd_4$  and  $Nc_{1,4}$  create the start/stop pulses. These pulses drive the motor output of the  $MSM6310$  during delay and repeat modes.

	Non handicapped	Motor handicapped
Written notes	80%	71%
Recorded notes	-	90%

Table 1. These results show that motor-handicapped students using the delayed recorder take notes more efficiently than non-handicapped students taking notes conventionally.

**Results**

We have tested this recorder with different student groups during their courses. During

the first experiment, motor handicapped pupils used delayed recorders set for four second delay. In addition, non-handicapped pupils aged 13 from the French fifth form took notes.

Approximately a quarter of the lesson was recorded. Pupils who used the recorder took note of 90% of the main information, while the non-handicapped pupils wrote down less than 80% of main information. However, the pupils were not very selective and had difficulty appreciating what could be said in four seconds.

A second experiment took place during the psychology and physiology courses of the Universite de Lille. A blind student recorded his course notes with the delayed recorder. The capacity of the endless loop was set to two seconds.

It was possible for this student to select and record complete sentences without losing the first words. Recording duration lasted less than 50% of the course.

**Initial findings**

Results obtained using a delayed tape recorder have shown that selective recording during courses is practicable. Using prototypes, we reached the following conclusions:

- Due to ram limitations, it is more difficult to take notes with a four-second delay than with two seconds.
- Delayed recording facilitates rapid selection of information.
- Recordings made are shorter than the lessons, reducing the amount of post-analysis needed by the students.

**References**

1. Nguyen, D.D, Steenkeste, F, Moschetto, Y, Sizaire, P, Ledru, C, 'Aide technique a la prise de notes chez les handicapes moteurs : le magnetophone enregistrement differe', *ITBM*, Vol. 8, No 5, 1987, p. 569-577.
2. Steenkeste F, Lesage J.C, Dhelin G, Moschetto Y, 'Un outil pour la prise de notes : le magnetophone a enregistrement differe et a compression temporelle', *ITBM*, Vol. 12, No 2, 1991, p. 213-222.
3. Steenkeste, F, Lesage, J.C, Dhelin, G, Moschetto, Y, 'Delayed recording to facilitate the educational integration of people with disabilities.' *International Journal of Rehabilitation Research*, Vol. 16, No 3, Sep. 1993, p. 239-244.
4. Data book, 'OKI Voice Synthesis LSI', Fourth Edition, Mar. 1992.
5. Professional Products IC Handbook, GEC Plessey Semiconductors, May 1991.

*Douglas Self takes issue with Bengt Olsson's non-complementary power amplifier design, arguing that the two-stage approach is not necessarily simpler or better than the traditional three-stage design.*

# Few for non-co

**B**engt Olsson's most interesting article on quasi-complementary fet output stages<sup>1</sup> prompted me to examine how his proposed configuration works. Investigations showed that his scheme changes not just the output stage but the entire structure of the amplifier, and it presents some intriguing new design problems.

## An alternative architecture

Nearly all audio amplifiers use the conventional architecture I have analysed previously.<sup>2</sup> There are three stages, the first being a transconductance stage, ie differential voltage in/current out, the second is a transimpedance stage ie current in/voltage out and lastly a unity-gain output stage, Fig. 1a.

Clearly, the second stage has to provide all the voltage gain and is therefore formally named the voltage amplifier stage, or vas. This architecture has several advantages. A main benefit is that it is straightforward to arrange things so that the interaction between stages is negligible. For example, there is very little signal voltage at the input to the second stage, due to its current-input nature. This results in very little voltage on the first stage output, which in turn minimises phase-shift and possible Early effect.

In contrast, the architecture presented by Olsson is a two stage amplifier, Fig. 1b. The first stage is once more a transconductance stage, though now without a guaranteed low impedance to accept its output current. The second combines voltage amplifier stage and output stage in one block. It is inherent in this scheme that the voltage amplifier must double as a phase-splitter. This results in two dissimilar signal paths to the output, and it is not at all clear that trying to break this block down further will assist a linearity analysis. The use of a phase-splitting stage harks back to valve amplifier days, when it was essential due to the lack of complementary valve technology.

Since the amount of linearising global feedback available depends upon amplifier open-loop gain, the way in which the stages contribute to this is of great interest. The normal three-stage architecture always has a unity-gain output stage – unless you really want to make life difficult for yourself. As a

result the total forward gain is simply the product of the transconductance of the input stage and the transimpedance of the voltage amplifier stage. Transimpedance is determined solely by the Miller capacitor  $C_{dom}$ , except at very low frequencies<sup>3</sup>.

Typically, the feedback factor at 20kHz will be 25-40dB. It will increase at 6dB per octave with falling frequency until it reaches the dominant pole frequency  $P_1$ , when it flattens out. What matters for the control of distortion is the amount of negative feedback, nfb, available, rather than the open-loop bandwidth, to which it has no direct relationship.

In my *EW+WW* Class-B design, input stage  $g_m$  is about 9mA/V, and  $C_{dom}$  is 100pF, giving a feedback factor of 31dB at 20kHz. In other designs I have used as little as 26dB at the same frequency with good results.

Arranging the compensation of a three-stage amplifier can be relatively simple. Since the pole at the voltage-amplifier stage is already dominant, it can be easily increased to lower the hf negative-feedback factor to whatever level is considered safe. The local negative feedback working on the voltage amplifier has an invaluable linearising effect. I am aware that some consider there are better ways to perform this sort of compensation, but the Miller approach is so far the most stable method in my experience.

## Fewer stages, more complexity?

Paradoxically, a two-stage amplifier may be more complex in its gain structure than a three-stage. Forward gain depends on the input-stage  $g_m$ , the input-stage collector load, and the gain of the output stage, which will be seen to vary in a most unsettling manner with bias and loading. Input-stage collector loading plays a part here since the input stage can not be assumed to be feeding a virtual earth.

Choosing the compensation is also more complex for a two-stage amplifier. The voltage-amplifier/phase-splitter has a significant signal voltage on its input. Usually, the pole-splitting mechanism enhances Nyquist stability by increasing the pole frequency associated with the input stage collector. But because of the relatively high voltage on the voltage-amplifier/phase-splitter, the pole-splitting mechanism is no longer effective.

# compliments mplements

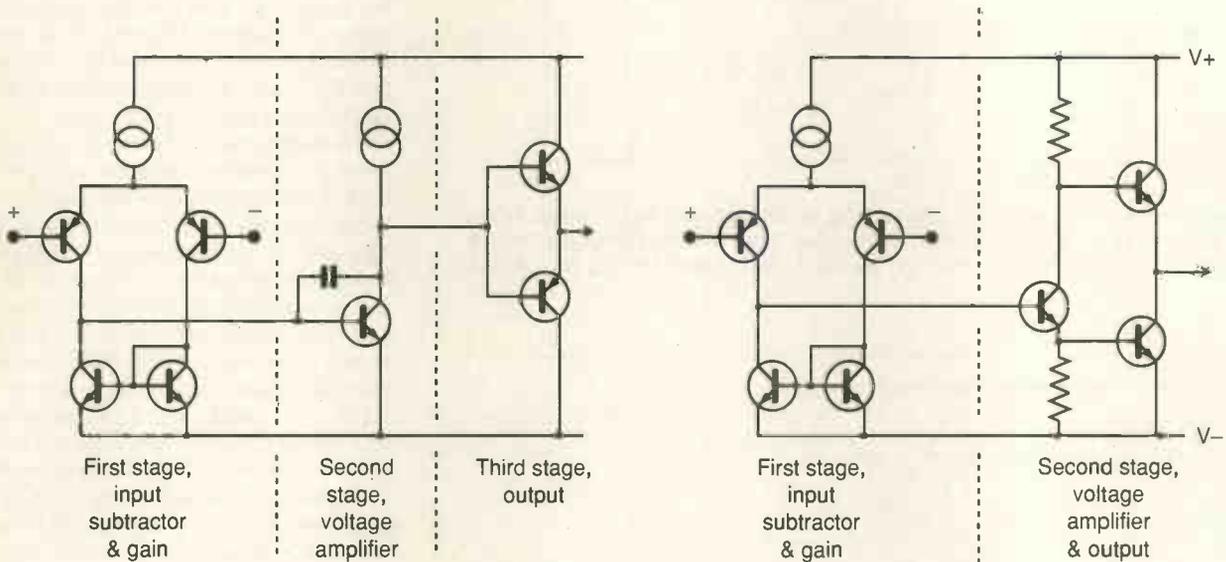


Fig. 1. Conventional three-stage amplifier architecture, and two-stage architecture advocated by Olsson.


This may be why Olsson's circuit uses a cascoded input stage comprising  $Tr_{6,7}$  in his original circuit, Fig. 11. This presents the input device collectors with a low impedance and prevents a significant collector pole. Another valid reason is that it also allows the use of high-beta low- $V_{ce}$  input transistors, which minimise output dc offset due to base current mismatch. This is usually much larger than the dc offset due to  $V_{be}$  mismatch.

Such an input cascode can also improve power-supply rejection as it prevents Early effect from modulating the subtractive action of the input pair.

Simple calculation gives the  $g_m$  of Olsson's amplifier as  $16\text{mA/V}$ , but the effective gain of the next stage seems much more difficult to equate. A full *PSpice* simulation of the complete amplifier with an  $8\Omega$  load shows that the feedback factor is 36dB up to 300Hz. It then rolls off at the usual 6dB/octave, until it passes through 0dB at about 20kHz. This 36dB represents much less feedback than the three-stage version. It indicates that  $C_{dom}$ , notionally connected between drain and gate of  $M_3$ , must be comparatively very large at approximately 3nF.

Specified internal capacitances of  $M_3$  are certainly orders of magnitude larger than those of an equivalent bipolar device – they vary

Fig. 2. Basic fet output stage used for simulations of Figs 3, 4 and 5. Transistors  $M_{1,2}$  are IRF240 and  $M_3$  is IRF710.

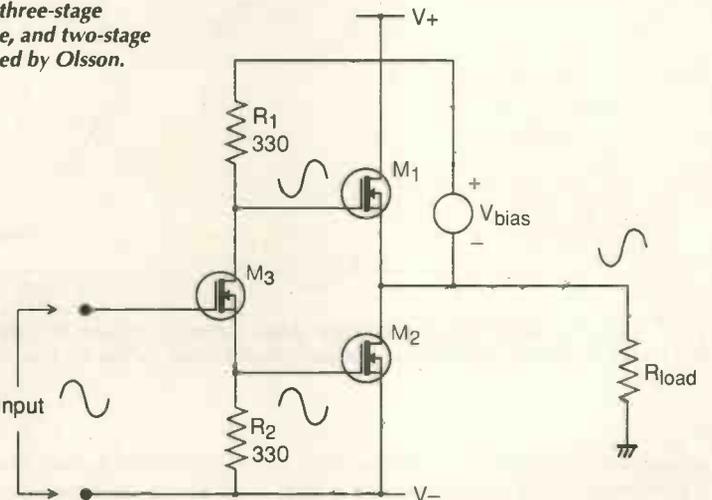

from sample to sample and also with operating conditions such as  $V_{ds}$ . These unwanted variations would appear to make stable and reliable compensation a difficult business.

The low-frequency feedback factor is about 6dB less with a  $4\Omega$  load, due to lower gain in the output stage. However, this variation is much reduced above the dominant pole frequency, as there is then increasing local negative feedback acting in the output stage.

### Devices and desires

In his opening paragraph, Olsson says that the symmetry of complementary transistor output stages is theoretical rather than practical. Presumably he is referring only to power-fets, as suitable pairs of bipolar devices, such as Motorola *MJ802/MJ4502* – old favourites of mine – exhibit excellent symmetry.<sup>4</sup> Admittedly, the two devices are not exact mirror-images, but the asymmetries are small

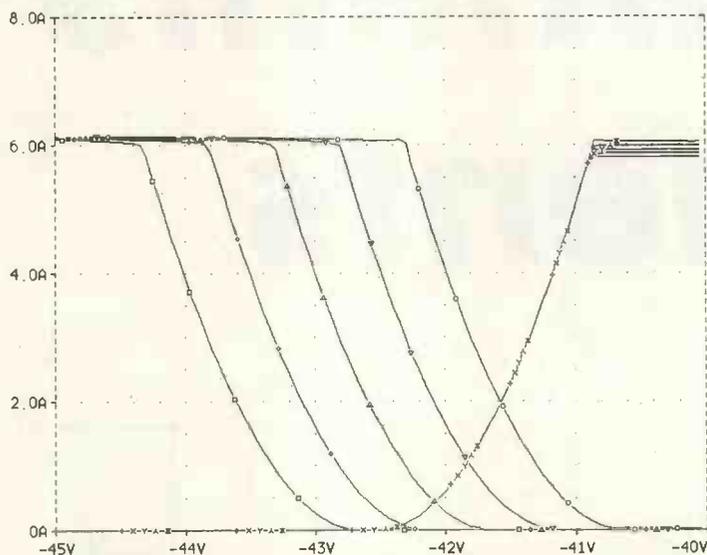


Fig. 3. Drain current in each output fet when driving an 8Ω load, with  $V_{bias}$  stepped. As  $V_{bias}$  increases the  $I_d(M_1)$  line moves to the right and overlaps more with the  $I_d(M_2)$  line. In each case symmetry exists about the intersection of the two  $I_d$  lines. Values for  $V_{bias}$  are 7.5, 8, 8.5, 9 and 9.5V.

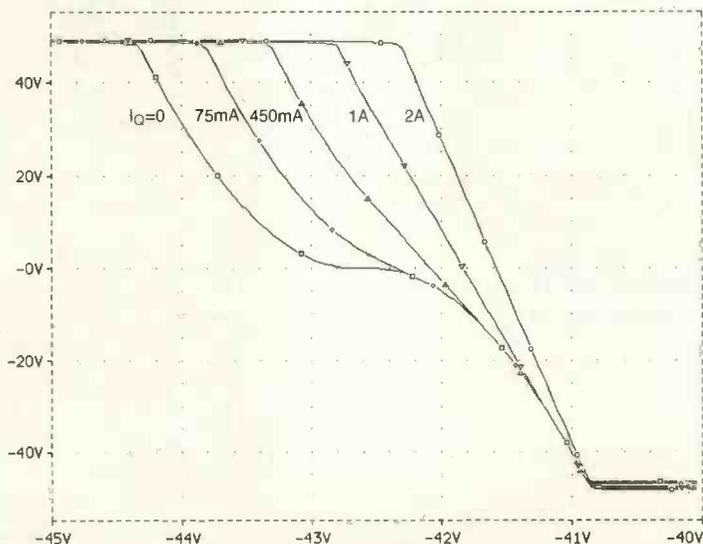


Fig. 4. Output transfer functions for stepped bias voltage. For lower bias, the characteristic is sigmoidal – S-shaped, unlike a conventional Class-B stage. Values for  $V_{bias}$  are 7.5, 8, 8.5, 9 and 9.5V.

enough for even-order harmonic generation in the output stage to be negligible. This is surely what counts.

This symmetry does not hold for power-fets however, and so it may be that some of Olsson's concern with symmetry flows from an initial decision to use fets. I find it difficult to understand why power fets in particular suffer from so many mis-statements. It is still confidently held that fets are more linear than bipolars, although the opposite is certainly the case when the two types of device are used in normal Class-B output stages.

Similarly, fet robustness is often exaggerated, the devices being prone to summary explosion under serious parasitic oscillation. Mercifully bipolars are not. In particular, I find it hard to understand Olsson's contention that fet parameters are predictable – they are notorious for being anything but.

From one manufacturer's data, namely Harris, the  $V_{gs}$  for the IRF240 varies between 2 and 4V for an  $I_d$  of 250μA – a range of two to one. In contrast the  $V_{be}/I_c$  relation in bipolars is fixed by a mathematical equation for a given transistor type. The exponential rela-

tionship may be regarded as more non-linear than the partially-square-law fet  $V_{gs}/I_d$  relationship but it is dependable, and gives a much higher transconductance. This can always be traded for linearity by introducing local negative feedback.

**Output considerations**

Figure 2 shows the basic output configuration I have investigated. I have not examined the 'anti-saturation' schemes intended to provide the output fets with extra gate drive.

My first discovery is that the voltage-amplifier stage/phase-splitter does not have to be a fet. Replacing it with a bipolar junction transistor, for example MPSA92, gives almost identical results. I have used  $M_{1,2}$  etc rather than  $Tr_{1,2}$  for fet designations as this preserves consistency with the PSpice output.

This output stage configuration is totally different in operation from the conventional Class-B stages discussed in reference 1. It is a hybrid common-drain/common-source configuration, or, in bipolar speak, a common-collector/common-emitter (cc-ce) stage. In this sort of output, the upper emitter-follower has a common-emitter active-load. This load may or may not deliver an appropriate current into the node it shares with the upper device.

The input-voltage/output-current relationship for the upper and lower devices will be different, as a result of the two dissimilar paths to the output. This means that while such a stage can always be biased into Class-A by increasing the quiescent enough<sup>5</sup> there is every likelihood that it will be an inefficient kind of Class-A. It will deviate seriously from the constant-sum-of-currents condition that distinguishes classical Class-A.<sup>6</sup>

Lower quiescents tend to give a depressing-ly non-linear and asymmetrical Class-AB. In general there is no equivalent at all to standard Class-B, where the symmetry of the configuration – rather than anything else – allows both output devices to be biased to the edge of conduction simultaneously.

In general, cc-ce stages generate large amounts of even-order distortion, due to their inherent asymmetry. I appreciate however that avoiding this is one of the prime purposes of Olsson's circuit.

In Fig. 2, the position of  $V_{bias}$  causes a form of bootstrapping, and I can confirm that driving it from the output is essential to make the scheme work.

Figure 3 shows drain current in each output fet when driving an 8Ω load, with  $V_{bias}$  stepped, as simulated by PSpice. Compared with conventional Class-B, the drain currents cross over smoothly. This seems intuitively a good idea, and has been recommended by several writers, but in fact a smooth-looking current crossover does not guarantee a linear composite gain characteristic.

Figure 4 shows the input/output characteristic for the stage. You can see that the lower

$V_{bias}$  levels produce a sigmoidal transfer function, with gain falling off in the crossover region. This gross output distortion is much greater than that given by a normal Class-AB stage. It suggests that it is only practical to run the stage in full Class-A, see the straight line at the right of the plot. I do not recall a mention of this point in the original article.

Quiescent current needed to achieve this is about 2A. The desirability of Class-A operation is reinforced by the incremental gain plot in Fig. 5. It is clear that the gain variations are serious for lower  $V_{bias}$ , and do not augur well for the closed-loop distortion performance. Only the rightmost Class-A gain characteristic has a clear flat portion over its operational range.

It is true that the drain currents in this stage are symmetrical – but the quiescent required to remove the sharp-eared 'Batman' effect in Fig. 5 is so high that the amplifier is working entirely in Class-A. The symmetry of the circuit means only that when distortion is produced, it will be predominantly odd-order, which is not normally considered a good thing from the subjective point of view. To keep the stage linear into  $4\Omega$  loads would demand a quiescent of 2.9A. It is interesting that this is not twice the current for the  $8\Omega$  case.

There are other significant differences from the usual voltage-follower configuration, which if nothing else has a stage gain reliably close to unity. Olsson's output stage gain varies with  $V_{bias}$  adjustment – even when in Class-A – and also varies strongly with load impedance. This would seem to make reliable compensation a difficult business, but in the complete amplifier this variation is probably only significant below the dominant-pole frequency  $P_1$ .

Figure 6 is a comparison between the Olsson configuration and three conventional stages, all biased to drive an  $8\Omega$  load in Class-A. Traces 1 and 2, at the top, are bipolar-emitter follower and complementary-feedback-pair stages. These produce the usual linearity and close approach to unity gain.

The curved lower trace, 4, is a conventional complementary fet output. Trace 3 is the Olsson stage, with its gain of about 65 times normalised to fit in between the other curves. It shows stronger curvature than the bipolar stages, and despite everything, is actually less symmetrical than the usual output stages. I think this is inherent in the circuit's lack of symmetry about the output line.

I hope this article is a fair analysis of the proposed configuration, and that I have not made any serious misinterpretations of Mr Olsson's intentions. I also trust that it will not be taken as purely destructive criticism, for that is not my intention. I have to conclude that the configuration appears to require a very high quiescent current for linear operation, and has only a limited amount of negative feed-

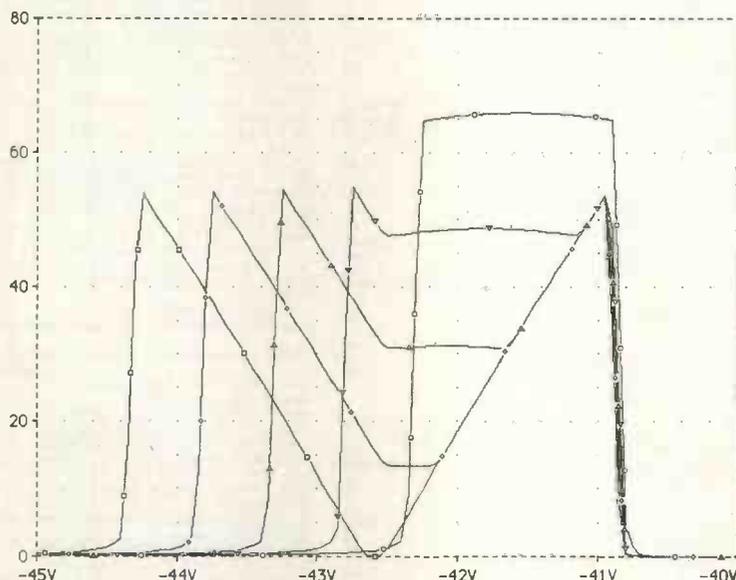


Fig. 5. Incremental gain plot for the Olsson stage, with  $V_{bias}$  stepped. The -AB mode (curve B) shows serious gain variations and therefore poor linearity.

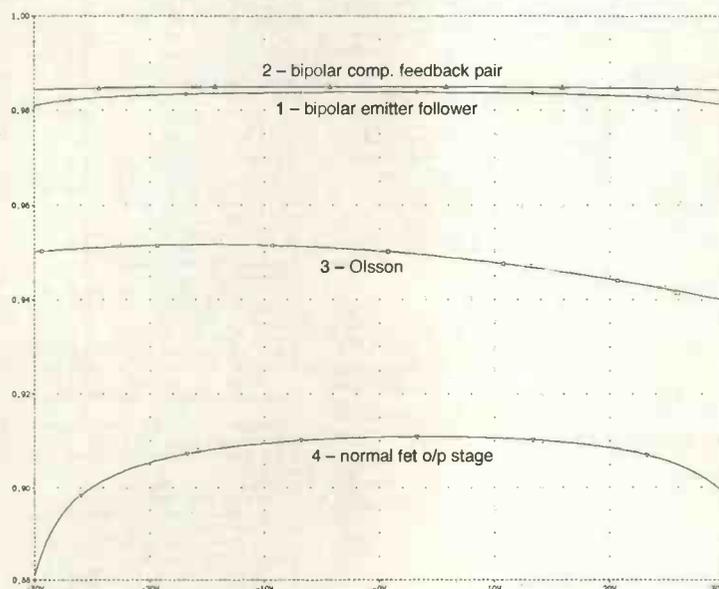


Fig. 6. Curve 3 shows incremental gain for the Olsson stage, driving  $8\Omega$  in Class-A. Equivalent plots for conventional Class-A bipolar emitter follower (curve 1), bipolar complementary feedback pair (curve 2) and a normal complementary fet stage (curve 4) are shown for comparison.

back available to correct output stage distortions. Any deeper investigation would need to be encouraged by some promise that the Olsson configuration can deliver substantial benefits, and as far as my analysis goes, this does not seem likely. ■

#### References

1. Olsson, B., 'Better audio from non-complements?' *EW+WW*, Dec. 1994 pp. 988-992.

2. Self, D, 'Distortion in power amplifiers: Pt 1' *EW+WW*, Aug. 1993.
3. Self, D, 'Distortion in power amplifiers: Pt 3' *EW+WW*, Oct. 1993.
4. Self, D, 'Distortion in power amplifiers: Pt 4' *EW+WW*, Nov. 1993.
5. Hood, J L, 'Simple Class-A amplifier.' *Wireless World*, Apr. 1969.
6. Self, D, 'Distortion in power amplifiers: Pt 7' *EW+WW*, Mar. 1994.

## COMPUTER ICs

TMS 9900L-40 PULLS	£20 ea
S9900 NEW AMD EQUIVALENT	£30 ea
TMS 9901L-40 PULLS	£20 ea
MC6802 PROCESSOR	£2 ea
TMS320	£5
TMS320 1 SHOT	£3
AM27C020-125L1 SURFACE MOUNT EPROM USED/WIPED	£1.50
MM16450 UART CHIP	£5 ea
P8271 BBC DISC CONTROLLER CHIP EX EOPT	£25
2817A-20 (2Kx8) EEPROM ex eqpt	£2
D41256-15 256Kx1 PULLS	9 FOR £5
80C31 MICRO	£2
P8749H MICRO	£5
D8751-8 NEW	£10
NK48202-20 ZERO POWER RAM EQUIV 6116LP	£1
NEW 4164-4	£4
USED 41256-15	£1
USED 4164-15	60p
BBC VIDEO ULA	£10
8051 MICRO	£1.25
8 x 4164 SIP MODULE NEW	£8
FLOPPY DISC CONTROLLER CHIPS 1771	£16
FLOPPY DISC CONTROLLER CHIPS 1772	£17.50
68000-8 PROCESSOR NEW	£6
HDE384-6	£5
ALL USED EPROMS ERASED AND BLANK CHECKED	
2718-45 USED	£2 100/£1
2732-45 USED	£2 100/£1
2764-30 USED	£2 100/£1
2764-30 USED	£2 100/£1
27C256-30 USED	£2
27C512 USED	£2.50
1702 EPROM EX EOPT	£5
2114 EX EOPT 50p 4116 EX EOPT	70p
6264-15 8K STATIC RAM	£2
GR281 NON VOLATILE RAM EQUIV 6116	£5
Z80A SIO-C	£1.25
7126 3 1/2 DIGIT LCD DRIVER CHIP	£2 ea
2816A-30 HOUSE MARKED	£2
USED TMS2532JL	£2.50
2708 USED	£2
HM6167LP-8	65p
68000-10 PROCESSOR	£5
8255-5	£1
2114 CMOS (PCA 5114)	£1.60
M27C4001-12 USED/WIPED 4M EPROM	£5
WD16C550-PC UART	£9

## REGULATORS

LM338K	£6
LM323K 5V 3A PLASTIC	£3
LM323K 5V 3A METAL	£3
LM350K (VARIABLE 3A)	£3 **NEW
78H12ASC 12V 5A	£1
LM317H T05 CAN	£1
LM317T PLASTIC TO220 variable	£1
LM317 METAL	£2.20
7812 METAL 12V 1A	£1
7805/12/15/24	30p
7905/12/15/24	30p
CA3085 T099 variable reg.	2/£1
78HGASC+79HGASC REGULATORS	£30 ea
LM123 ST93 5V 3A T03 REGS	£3 ea
UC3524AN SWITCHING REGULATOR IC	60p

## CRYSTAL OSCILLATORS

2M4576 3M6864 5M0 5M76 6M144 7M000 7M3728 8M000 12M000 14M3181 17M6256 18M2571 19M000 20M000 23M4572 24M000 25M1175 27M0 27M035 28M322 32M000 33M3330 35M4816 40M000 44M4444 44M900 48M000 64M000 1M000 1M8432 4M000 10M000 16M000 18M432000 19M0500 20M0500 38M10000 56M6092 76M1 84M0	£1.50 ea
---	----------

## CRYSTALS

4M0256 10M368 17M6256 18M432 25M000 28M4694 31M4696 48M000 55M500 111M80 112M80 114M318 114M80 1M0 1M8432 2M000 2M4576 2M77 3M00 3M2768 3M579545 3M58564 3M93216 4M000 4M19304 4M433619 4M608 4M9152 5M000 5M0688 6M0000 6M400 8M000 8M488 9M8304 10M240 10M245 10M7000 11M000 12M000 13M000 13M270 14M000 14M381818 15M000 16M000 16M8888 17M000 20M000 21M300 21M855 22M1184 24M000 34M368 36M75625 36M76875 36M78125 36M79375 36M80625 36M81875 36M83125 36M84375 38M900 49M504 54M19166 54M7416 57M75833 60M000 69M545 69M550 69M550 26M995 69M7M045 0R27M095 YW27M145 GN27M195 BL27M245 3M225	£1 ea
--	-------

## TRANSISTORS

MPS432	10/£1
2N2907A	10/£1
BC477, BC488	10/£1
BC107 BCY70 PREFORMED LEADS	
full spec.	£1 £4/100 £30/1000
BC557, BC238C, BC308B	£1/30 £3.50/100
2N3819 FETS short leads	4/£1
2N2907 PLASTIC CROPPED	£1/15 £4/100

## POWER TRANSISTORS

OC29	£1.35 ea
P POWER FET IRF9531 8A 60V	3/£1
N POWER FET IRF531 8A 60V	2/£1
2SC1520 sim BF259	3/£1 100/£22
TIP 141/2 £1 ea TIP 112/48B	2/£1
SE9301 100V 1DA DARL SIM TIP121	2/£1
PLASTIC 3055 OR 2955 equiv 50p	100/£35
BUZ31 POWER FET TO-220 200V 12.5A	2/£1

## TEXTBOOK ZIF SOCKETS

28 PIN USED	£3
40 PIN NEW	£10
SINGLE IN LINE 32 WAY CAN BE GANGED FOR USE WITH ANY DUAL IN LINE DEVICES . . . COUPLING SUPPLIED	2/£1.50

## MISCELLANEOUS

2 VOLT 920 A/hr LEAD ACID CELLS, UNUSED, UNFILLED 18" HIGH 12" x 7", WEIGHT 48kg each, RUBBERISED CASE, GAULTEDED TUBULAR PLATE CONSTRUCTION, FOR DEEP CYCLE, HIGH CURRENT USE, MADE FOR BRITISH NAVY, 800 CELLS AVAILABLE, PHONE FOR PRICING ALSO AVAILABLE FILLED & CHARGED	
Narrow angle infra red emitter LED55C	2/£1
UM61 16M-2L surface mount 1000 available	£1
Z80B PIO 7000 available £1 each, qty. price	30/50p
CNY65 OPTO ISOL 3000 available	50p

OPTO ICS also available TLP550 TLP666GF	
68 way PLCC SKT 1500 available	£1 each
100 way PLCC SKT 100 available	£1.50 each
1250pF POSTAGE STAMP COMPRESSION TRIMMER	£1
XL930C54P-3 serial Eprom 10,700 available	£1.600/lot, £25/100, £1/3
LM324 (Quad 741)	4/£1
MINIATURE FERRITE MAGNETS 4x4x3mm	10/£1
TL071 LO NOISE OP AMP	5 for £1
TL081 OP AMP	4 for £1
47000u 25v SPRAGUE 360	£2.50 (£2)
12 way dll sw	£3 for £1
10NF 63V X7R PHILIPS SURFACE MOUNT 100K available	£30/4000
SWITCHED MODE PSU 40 WATT UNCASED QTY. AVAILABLE + 5v 5A, +12V 2A, 12V 500mA FLOATING	
220R 2.5W WIREWOUND RESISTOR 60K AVAILABLE	£50/1000

CMOS 555 TIMERS	2/£1
2/3 AA LITHIUM cells as used in compact cameras	2/£1.50
ICM7126CPL CMOS 3 1/2 DIGIT LCD DRIVER CHIP	£2 ea
LITHIUM CELL 1/2 AA SIZE	2 FOR £1
PASSIVE INFRA RED SENSOR CHIP + MIRROR + CIRCUIT	£2 ea
EUROCARD 28-SLOT BACK PLANE 96/96-WAY	£25 ea
*PHOTONIC 24 VARIBUS* 16.7"x5" FIBREGLASS MULTILAYER PCB	
EUROCARD 96-WAY EXTENDER BOARD	£10 ea
290x100mm	
DIN 41612 96-WAY A/B/C SOCKET PCB RIGHT ANGLE	£1.30
DIN 41612 96-WAY A/B/C SOCKET WIRE WRAP PINS	£1.30
OIN 41612 64-WAY A/C SOCKET WIRE WRAP PINS	£1
DIN 41612 64-WAY A/C PLUG PCB RIGHT ANGLE	£1
DIN 41612 64-WAY A/B SOCKET WIRE WRAP (2-ROW BODY)	£1
BT PLUG+LEAD	3/£1
MIN. TOGGLE SWITCH 1 POLE c/o PCB type	5/£1
LCD MODULE sim. LM018 but needs 150 to 250V AC for display	£10
40x2 characters 182 x35x13mm	£1/100
6-32 UNC 5/16 POZI PAN SCREWS	£1.25/100
NUTS	2/£1
PUSH SWITCH CHANGEOVER	2/£1
RS232 SERIAL CABLE D25 WAY MALE CONNECTORS	£5.90 ea (£1.30)
25 FEET LONG, 15 PINS WIRED BRAID + FOIL SCREENS	
INMAC LIST PRICE	£30

AMERICAN 2/3 PIN CHASSIS SOCKET	2/£1
WIRE ENDED FUSES 0.25A	30/£1
NEW ULTRASONIC TRANSDUCERS 32kHz	£2/pr
POWERFUL SMALL CYLINDRICAL MAGNETS	3/£1
BNC 50OHM SCREENED CHASSIS SOCKET	2/£1
SMALL MICROVAE DIODES AE1 OC1026A	2/£1
D.I.L. SWITCHES 10-WAY £1 8-WAY 80p 4/5/6-WAY	80p
180VOLT 1WATT ZENERS also 12V & 75V	20/£1
MIN GLASS NEONS	10/£1
RELAY 5V 2-pole changeover looks like RS 355-741 marked STO 47W80st	£1 ea
MINIATURE CO-AX FREE PLUG RS 456-071	2/£1
MINIATURE CO-AX PCB SKT RS 456-093	2/£1
PCB WITH 2N2646 UNIJUNCTION WITH 12V 4-POLE RELAY	£1
400 MEGOHM THICK FILM RESISTORS	4/£1
STRAIN GAUGES 40 ohm Foil type polyester backed balco grid alloy	£1.50 ea 10+ £1
ELECTRET MICROPHONE INSERT	2/£1
Linear Hall effect IC Micro Switch no 613 SS4 sim RS 304-267	£2.50 100+ £1.50

HALL EFFECT IC UGS3040 + magnel.	4/£1
1 pole 12-way rotary switch	4/£1
AUDIO ICS LM380 LM386	£1 ea
555 TIMERS £1 741 OP AMP	6/£1
2N414 AM RADIO CHIP	80p
COAX PLUGS nice ones	4/£1
COAX BACK TO BACK JOINERS	3/£1
INDUCTOR 20µH 1.5A	5/£1
1.25" PANEL FUSEHOLDERS	3/£1
12V 1.2w small w/leads fit most modern cars	10/£1
STEREO CASSETTE HEAD	£2
MONO CASS. HEAD £1 ERASE HEAD	50p
THERMAL CUT OUTS 50 77 85 120°C	£1 ea
THERMAL FUSES 220°C/121°C 240V 15A	5/£1
TRANSISTOR MOUNTING PADS TO 50-T0-18	£3/1000
T0-3 TRANSISTOR COVERS	10/£1
PCB PINS FIT 0.1" VERO	200/£1
TO-220 micas + bushes	10/50p 100/£2
TO-3 micas + bushes	15/£1
Large heat shrink sleeving pack	£2
IEC chassis plug filter 10A	£3
POTS SHORT SPINDLES 2K5 10K 25K 1M 25M5	4/£1
40k U/S TRANSDUCERS EX-EOPT NO DATA	£1/pr
LM3352 10MV/degree C	£1
LM234Z CONST. CURRENT I.C.	£1
BNC TO 4MM BINDING POST SIM RS 455-961	£1
MIN PCB POWER RELAYS 10.5v COIL 6A CONTACTS 1 pole c/o	£1

BANDOLIERY COMPONENTS ASSORTED RS, Cs, ZENERS	£5/1000
LCD MODULE 16 CHAR. X 1 LINE (SIMILAR TO HITACHI LM10)	£5
OP1254A 10kV OPTO ISOLATOR	£1.35 ea 100+ £1 ea
'LOVE STORY' CLOCKWORK MUSICAL BOX MECHANISM	£1 ea
MADE BY SANKYO	£1 ea
Telephone cable clips with hardened pins	500/£2
10,000µF 16V PCB TYPE 30mm DIAx31mm	2/£1
EC CHASSIS FUSED PLUG B-LEE L2728	3/£1
2A CERAMIC FUSE 1.25" QB	10/£1
46 WAY IDC RIBBON CABLE 100 FOOT REEL	£5 + CARR
20mm PCB FUSEHOLDER	5/£1
IEC CHASSIS FUSED PLUG B-LEE L2728	3/£1
ASTEC MODULATOR VIDEO + SOUND UM1287	£2.25
BARGRAPH DISPLAY 8 RED LEDS	£1.50
NE567 PHASE LOCKED LOOP	2/£1
NE564	£1
P8749H USED WIPED	£1
TL084	4/£1
IR2432 SHARP 12 LED VU BAR GRAPH DRIVER	£1.25

DIODES AND RECTIFIERS	
A115M 3A 800V FAST RECOVERY DIODE	4/£1
1N5407 3A 1000V	8/£1
1N4148	100/£1.50
1N4004 5D4 1A 300V	100/£3
1N5401 3A 100V	10/£1
1N5819L 20K Ex stock	1000+10p **NEW
BA158 1A 400V fast recovery	100/£3
BY254 800V 3A	8/£1

BY255 1300V 3A	6/£1
6A 100V SIMILAR RECTIFIER	4/£1
1A 600V BRIDGE REF51	4/£1
4A 100V BRIDGE	3/£1
6A 100V BRIDGE	2/£1
10A 200V BRIDGE	10/£1.50
25A 200 V BRIDGE £2	£1.50
25A 400V BRIDGE £2.50	10/£2.50
2KBPO2 IN LINE 2A 200V BRIDGE REC	8/£1
BY297	10/£1

PULSE TRANSFORMERS 1:1+1	£1.25
TICV106D 800mA 400C SCR 3/£1	100/£15
MEU21 PROG UNIJUNCTION	3/£1

NEC TRIAC AC08F 8A 600V T0220	5/£2 4/£1
TXAL225 8A 500V 5mA GATE	2/£1 100/£35
BTA 08-400 ISO TAB 400V 5mA GATE	90p
TRAL2230D 30A 400V ISOLATED STUD	£5 ea
TRIAC 1A 800V T1C381T 16k AVAILABLE	5 FOR £1 100/£100

## CONNECTIONS

D25 IDC PLUG OR SOCKET	£1
34-way card edge IDCCONNECTOR (disk drive type)	£1.25
CENTRONICS 36 WAY IDC PLUG	£2.50
CENTRONICS 36 WAY IDC SKT	£4.00
BBC TO CENTRONICS PRINTER LEAD 1.5M	£3
CENTRONICS 36 WAY PLUG SOLDER TYPE	£4
USED CENTRONICS 36W PLUG+SKT	£3
14 WAY IDC BLOCK HEADER SKT	5/£1

## CONNECTORS

D25 IDC PLUG OR SOCKET	£1
34-way card edge IDCCONNECTOR (disk drive type)	£1.25
CENTRONICS 36 WAY IDC PLUG	£2.50
CENTRONICS 36 WAY IDC SKT	£4.00
BBC TO CENTRONICS PRINTER LEAD 1.5M	£3
CENTRONICS 36 WAY PLUG SOLDER TYPE	£4
USED CENTRONICS 36W PLUG+SKT	£3
14 WAY IDC BLOCK HEADER SKT	5/£1

## PHOTO DEVICES

HI BRIGHTNESS LEDS COX24 RED	5/£1
SLOTTED OPTO-SWITCH OPCOA OPB815	£1.30
2N577	50p
TL181 PHOTO TRANSISTOR	£1
TL138 INFRA RED LED	5/£1
4N25, OP1252 OPTO ISOLATOR	50p
PHOTO DIODE 50P	6/£2
MEL12 (PHOTO DARLINGTON BASE n/c)	50p
LED's RED 3 or 5mm 12/£1	100/£6
LED's GREEN OR YELLOW 10/£1	100/£6
FLASHING RED LED 5mm 50p	100/£40
HIGH SPEED MEDIUM AREA PHOTODIODE RS651-995	£10 ea

## STC NTC BEAD THERMISTORS

G22 220R, G13 1K, G23 2K, G24 20K, G54 50K, G25 200K, RES 20°C DIRECTLY HEATED TYPE	£1 ea
FS22B NTC BEAD INSIDE END OF 1" GLASS PROBE RES 20°C 200R	£1 ea
A13 DIRECTLY HEATED BEAD THERMISTOR 1k res. ideal for audio Wien Bridge Oscillator	£2 ea

## CERMET MULTI TURN PRESETS 3/4"

10R 20R 100R 200R 250R 500R 2K 2K2 2K5 5K 10K 47K 50K 100K 200K 500K 2M	50p ea
---	--------

## IC SOCKETS

14/16/18/20/24/28/40-WAY DIL SKTS	£1 per TUBE
8-WAY DIL SKTS	£2 per TUBE
32-WAY TURNED PIN SKTS	3 for £1
SIMM SOCKET FOR 2x30-way SIMMS	£1

## POLYESTER/POLYCARB CAPS

330nF 10% 250V AC X2 RATED PHILIPS TYPE 330	£20/100
100n, 220n 63V 5mm	20/£1 100/£3
10n 15n 22n 33n 47n 66n 10mm rad	100/£3.50
100n 250V radial 10mm	100/£3
100n 600V Sprague axial 10/£1	100/£10
2µ2 160V rad 22mm, 2µ2 100V rad 15mm	100/£10
10n 33n 47n 250V AC x rated 15mm	10/£1
1µ 600V MIXED DIELECTRIC	50p ea
1µ 100V rad 15mm, 1µ 22mm rad	100/£6
0.22µ 250V AC X2 RATING	4/£1
0.22µ 900V	4/£1

## RFB BITS

SAW FILTERS SW662/SW661 PLESSEY SIGNAL TECHNOLOGY 379.5 MHz	£1.50 ea
FX3288 FERRITE RING ID 5mm OD 10mm	10 for £1
ASTEC UM1233 UHF VIDEO MODULATORS (NO SOUND) 1250 STOCK	£1.50
MARCONI MICROWAVE DIODES TYPES DC2929, DC2962, DC4229F1/2	£1 EA
XTAL FILTERS 21M4 55M0	£2 ea
ALL TRIMMERS	3 for 50p
VIOLET	5-105pF
YELLOW 5-65pF RED 10-110pF GREY 5-25pF	
SMALL MULLARD 2 to 22pF	3 FOR 50p 100/£10
TRANSISTORS 2N4427, 2N3866	80p ea
CERAMIC FILTERS 4M5/6M/9M/10M7	60p ea
FEED THRU CERAMIC CAPS 1000pF	10/£1
SL610	£5
6 VOLT TELETYPE RELAYS 2 POLE CHANGEOVER	£2
(BFY51 TRANSISTOR CAN SIZE)	
2N2222 METAL	5/£1
P2N2222A PLASTIC	10/£1
2N2369A	5/£1
VN10KM	4/£1

## MONOLITHIC CERAMIC CAPACITORS

10n 50V 2.5mm	100/£4.50
100n 50V 2.5mm or 5mm	100/£6
100n ax short leads	100/£3
100n ax long leads	100/£5
100n 50V dll package 0.3" rad.	100/£8
1µF 50v 5mm	£6/100

## QUARTZ HALOGEN LAMPS

12V 50watt LAMP TYPE M312	£1 ea HOLDERS 60p ea
6V 50watt</	

The latest update of the longest established pc-based circuit simulator now analyses mixed-mode designs, but was making *MicroCap V* compatible only with Windows also a step forward? Ben Duncan wonders.

# Mixed-mode modelling

Previous generations of *MicroCAP* have had all the benefits of a 'windows-like' environment in dos. One of the keynotes of *MicroCAP-V*, or *MC5*, is that it is written in 32-bit code and runs under Windows. This brings the advantages of select-your-own typefaces, ease of screen grabbing, pasting simulation schematics and graphs into other programs. It also makes printer control more coherent.

However, it also has the penalty of needing 8MB of memory to run what only needed 4MB under dos. This is in addition to Windows' existing problems of flakey double click and an excessive reliance on mouse selection. There is also presently an incompatibility between Microsoft's own mouse and drivers and Win 32s. This driver upgrades Windows 3.1+ to 32 bits.

Another keynote is an event-driven digital logic engine. Using PSpice syntax, many users won't need to relearn anything. The promise of seamless digital/analog modelling seems a very good reason for buying *MC5*.

## Digital features

Digital analysis is outside my domain, but I can outline the new version's essentials. *MicroCAP-5* has about 75% of the digital models in PSpice. Each program's libraries can be read by the other. PSpice can read *MC5* text circuit files or alternatively, *MC5* can read most PSpice files. Analogue and digital circuits can be freely mixed, either in *MC5* schematics or in Spice text file circuits.

## System requirements

Windows 3.1 + optional Win 32s – when debugged – Absolute minimum 33MHz AT PC with 386-DX, dos 5, and 8Mbyte ram. However 16MB is recommended.

Digital nodes, like analogue ones, are numbered automatically and can be referenced by any legal name. On schematics they are in square boxes, whereas analogue node boxes are clearly distinguished by radiusing. Interfacing between analogue and digital nodes and *vice versa* can be automatic, with hard one, zero or fuzzier R, F, X levels.

To enable tri-state and multiple open-collector outputs to be accurately modelled, six digital states are allowed, each with different strengths and levels. Device input/output models provide impedance and switching time data. These determine output strength with wire-ORed parts.

Loading, inertial and transport delays are covered. Path commands identify and list gates in paths as well as calculating and showing each paths delay. They can be 'point-to-end', 'point-to-point' or 'show all paths'.

Delays can be minimum, typical, maximum, or the worst case minimum-maximum, creating a realistic ambiguity region. Equally, timing hazards, for example convergence or cumulative ambiguity hazards, can also be modelled.

Digital powering is automatically provided for a given logic family. There are over 1200 digital parts. Primitives include *plas* and multibit d-to-a/a-to-d converters. Bistable devices may be both edge and level triggered, and gated latches similarly *srf* and *ditch* types. Digital stimuli can originate from a generator or a file. Generator form can create virtually any waveform.

## Analogue developments

There is a number of small additions to the analogue features in the new version, mostly concerning analysis. Temperature modelling abilities of *MC5* – previously a relatively a weak spot – have since caught up with other high-end Spice-based programs. Now, *measured*, *absolute*, *local* and *global* temperature settings are all handled.

Unfortunately, *MC5* follows the obscure nomenclature of Spice. For example, the 'absolute' temperature would be

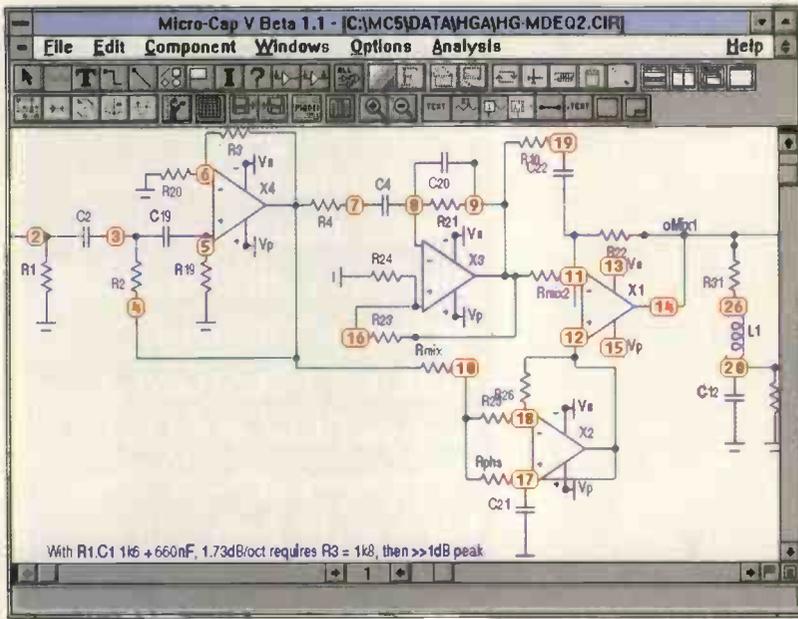


Fig. 1. Fragment of a filter system, converted from MC4. Only the psu macro – two batteries – had to be replaced to get it to run ‘as was’. With the Beta copy tested, some text labels have shifted to overlap, but in any event, MC5 allows all part labels to be moved freely. Note the icons above the schematic and help screen below.

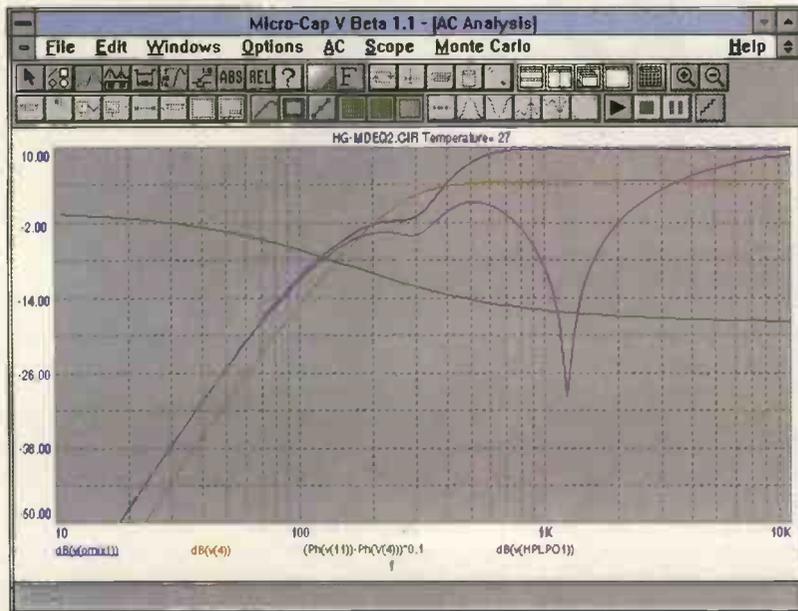


Fig. 2. An example of four simultaneous ac plots. Any mixture of ac operators may be employed, provided a common scale is realisable. Here the green graph is phase and the others are amplitude. Any number of plots are allowed in theory but there are only sixteen colour choices. The new cursor function is annotating the approximate 34dB difference between one plot and the dip of another.

better named a ‘solo’ temperature, as it is independent from the others, including the default global temperature. The ‘measured’ setting is not used in simulation. Instead it re-normalises spice parameters when measured at other than the fixed, nominal 27°C.

In stepping, it is now easier to enter model parameters like BF – as opposed to simple part values with enhanced control. With the default ‘public’ library, each part shares its model parameters with others using the same model name.

If, as before, you wanted to step one BC337 transistor’s  $\beta$ , among other BC337’s in your circuit, you would normally have to rename it ‘Tr<sub>3</sub>’ or some other legal and previously unused name. However, using the ‘private’ option when initially drawing a schematic, only a given part’s parameters are stepped.

With MC5, the only part that cannot now be stepped, excepting the various tabular sources, is the transformer. This can be replaced though through mutualled inductors which are steppable. When a relatively subtle parameter, say the ‘vaf’ of one transistor in many, is being stepped, a new command line enables it to be plotted on the analysis screen. This allows you to verify whether it is being stepped or Monte-Carlo processed.

After analysis, cursors can now provide approximate auto measurement on the screen between any pair of horizontal or vertical data points, Fig. 2. To ensure multiplot clarity in black and white printouts, six types of graphic primitives can be placed on the graph, for instance a diamond.

When analysing, any number of simultaneous plots can now in theory be specified. This can have its creative uses such as mass parallel plotting of circuit alternatives. Reviewing the beta software version I could only get four plot colours to run, Fig. 2, but readers can rely on Spectrum Software meeting their specification on release.

Inductor and core modelling has been changed from using a ‘mutual’ statement to the spice format, using the ‘K’ device. This is straightforward – core data as MC4, with turns as the inductor parameter. Micro-CAP and PSpice appear to be the only pc simulators using the advanced Jiles-Atherton magnetics model.

In the model editor I found a ‘revert’ function, something every good program should have. In the event of a data entry disaster it puts everything back to where it was at the start of a session. The manual continues in the MicroCAP tradition of being unusually well written, if somewhat terse. It contains a useful chapter on solving bad convergence. If MC5 runs like its predecessor then this chapter will not be needed often.

Reliable and fuss-free conversion of the tens of thousands of MC4 files to the MC5 format is vital. I tested a variety of different circuits and found this was the case with just one exception – all macros had to be partly re-created manually. MC4 macros should not need re-creating in the released version – a ‘merge’ command should auto-convert them. This is something of a nuisance, especially, if like me you have dozens of standard macros, such as a psu that appears in nearly every schematic needing conversion. Still, it is far better than having to convert parts of thousands of MC4 files individually.

The first version MicroCAP appeared 14 years ago, making this package the longest surviving pc simulator. It is also the most friendly of the £1k-£10k packages as far as it is 100% seamless – compared with similarly costly pc simulators that comprise a Spice core with a schematic editor and other functions bolted on as an afterthought.

For the intuitive user, MC5 largely avoids the counter-intuitive jargon of spice-land. A battery is called a battery. ■

### Software sourcing

Manufacturer – Spectrum Software, 1021 S.Wolfe Rd, Sunnyvale, CA 94086, USA. UK distributors, Rainbow Software, phone or fax 0181 295 4500, Datech, 0181 308 1800, fax 308 0802. A demonstration disk is available.

# SEETRAX CAE RANGER PCB DESIGN

WITH COOPER & CHYAN AUTOROUTER

RANGER3 - DOS £2500  
- Windows\NT £2900

Hierarchical or flat schematic linked to artwork.  
Unlimited design size. 1 micron resolution  
Any shaped pad, definable outline library  
Pin, gate & outline swapping - auto back annotation  
Split power planes, switchable on - line DRC

**COOPER & CHYAN SPECCTRA**  
autorouter (SP2)

Inputs: OrCAD, Cadstar,  
PCAD, AutoCAD DXF

Outputs: Postscript, Windows bit map

R2 & R3 Outputs: 8/9 & 24 pin printers, HP  
Desk & Laser Jet, Cannon Bubble Jet,  
HP-GL, Gerber,  
NC Drill, AutoCAD DXF

RANGER2 £150

Upto 8 pages of schematic linked to artwork  
Gate & pin swapping - automatic back annotation  
Copper flood fill, Power planes, Track necking,  
Curved tracks, Clearance checking,  
Simultaneous multi-layer auto-router

RANGER2 UTILITIES £250

COOPER & CHYAN SPECCTRA auto-router (SPI)  
Gerber-in viewer, AutoCAD DXF in & out

UPGRADE YOUR PCB PACKAGE  
TO RANGER2 £60


TRADE IN YOUR EXISTING PACKAGE TODAY

Seetrax CAE, Hinton Daubnay House, Broadway Lane, Lovedean, Hants, PO8 0SG  
Call 01705 591037 or Fax 01705 599036 + VAT & P.P.

CIRCLE NO. 126 ON REPLY CARD

All Trademarks Acknowledged


## COMPONENTS & SYSTEMS FROM IOSIS

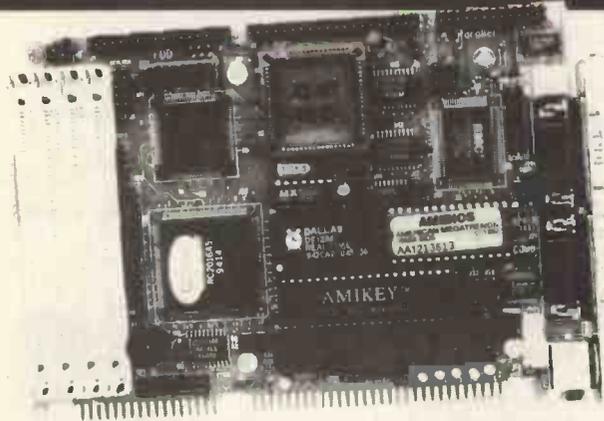

**INDUSTRIAL SPEC COMPONENTS AND SYSTEMS**  
386SX-40 All-in-one CPU Board on PC half card from  
£215. Requires only display adapter and RAM to complete  
the core of a PC-compatible system. PC/104 or ISA bus  
expansion. PC/104 display adapter from £135. Desktop LCD  
mono VGA monitor with display adapter and passive back-  
plane from £499. Please enquire for complete systems.  
Prices exclude VAT and carriage.

2c Chandos Road, Redland, Bristol BS6 6PE, UK  
Tel: 0117 973 0435 Fax: 0117 923 7295

CIRCLE NO. 127 ON REPLY CARD

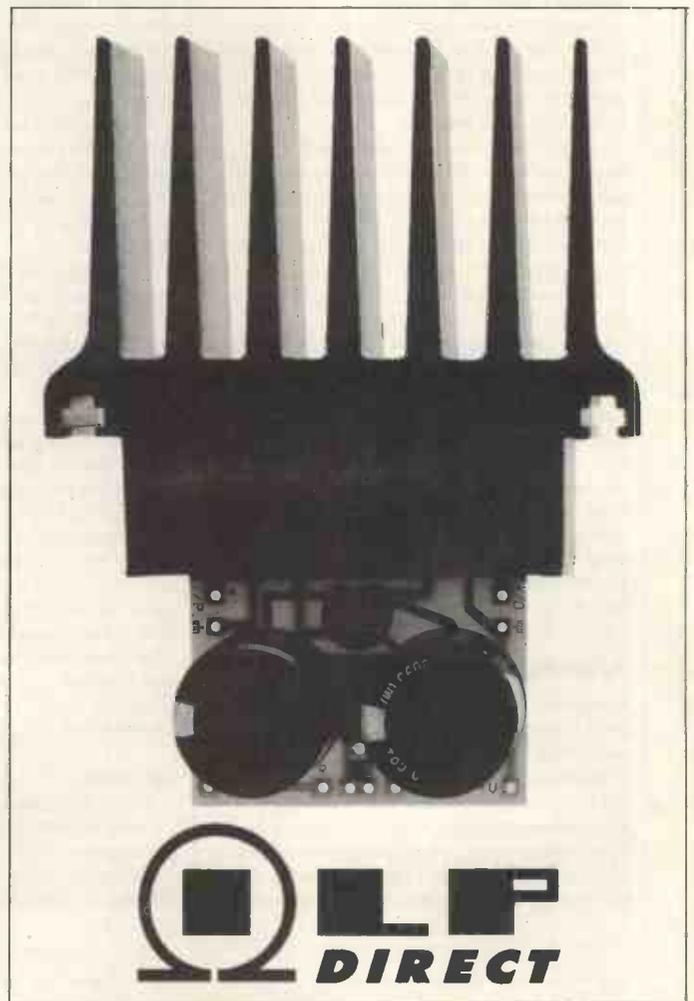

CIRCLE NO. 128 ON REPLY CARD

# LETTERS

Letters to "Electronics World" Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

## Earth grounds for digital tv

Your editorial in the July edition debating the pros and cons of various means of digital television delivery was stimulating as usual.

Digital television may well be available first via satellite and cable systems, but we are of the view that digital terrestrial television still has a major part to play – particularly for universal service and the delivery of regional and local services, and for tv sets where access to satellite or cable is either inconvenient or impossible.

Your assertion that "there is absolutely no reason to run digital tv from land based transmitters" is a conclusion with which we could not agree. Estimates for the percentage of population able to erect antennas and receive satellite television services directly vary between 80-95%, depending on source.

It ought to be easy to accept that not every home in the country can erect a dish in a suitable position. As a result, it is impossible for geostationary satellites ever to achieve the 99.5% penetration of the current analogue services. There are

also planning constraints on the erection of dishes which might well apply even to the smaller dishes that will most probably be practicable for digital satellite tv.

The benefits of digital terrestrial are that it can reach houses other technologies cannot reach; that it provides a more attractive route for local and regional television; and that if early tests prove correct, it can deliver a robust service to set top aerials for portable reception and second and third sets in the home which do not have access to the main satellite/cable delivery point.

Your point about the amount of spectrum occupied by television broadcasting is well made, but I suspect few of your readers would be enthusiastic if we were to relocate domestic television to an alternative slot in the spectrum at short notice and everyone had to buy converter boxes or new televisions and a new aerial.

However, our long strategy is to free up a portion of the spectrum currently used for terrestrial television broadcasting for other applications. This might include mobile tv which opens up another

## Speakers and dynamos, mismatching and reluctance

In the May issue, Jeff Macaulay remarked that moving-coil loudspeakers are somewhat crass devices that lose 99% of the applied energy in copper losses. In the June issue a correspondent complained that his cycle dynamo achieved constant output by being very inefficient.

Both are wrong. Loudspeakers are lossy mainly because of the mismatch between the cone and the surrounding air, which of course can be changed by the use of a horn, which makes efficiency is much higher.

As a permanent-magnet alternator, the cycle dynamo suffers from the field generated by the rotor when a lagging current is drawn. This current bucks the voltage generated in the way a series inductance would.

In power engineering, the equivalent inductance is called synchronous reactance. You cannot design it out. I reckon if you short circuit the machine at any speed, it will circulate sufficient current internally to nul the internal magnetic field at its peaks. But this current will be the same regardless of speed, except that the idea must fail at some low speed.

So you have something akin to a constant-current machine operating over a range of speeds. Bulbs in the circuit are constant-current devices too, so if they have different ideas about the magnitude of the current, problems occur. As a result, if I manufactured cycle dynamos I would try to obtain a precisely defined output from them.

In the interests of better lighting, I think manufacturers should produce a large dynamo.  
**Bernard Jones,**  
London

## Alternate dynamo

In response to Steve Bush's letter in the June issue concerning bicycle dynamos, I would like to pass on the results of my research.

The bicycle dynamo is not a dynamo at all, since a dynamo is a dc machine. It is actually a single-phase alternator.<sup>1,2</sup> Electrically it looks like an ac voltage source whose voltage and frequency are linearly proportional to speed; in series with the resistance and inductance of the windings.

A motor vehicle alternator has a field winding whose current can be varied to vary the magnetic field, and thus the output. The cycle dynamo on the other hand has a permanent magnet, and cannot be regulated. At high speeds, the inductance dominates. As its reactance is also linearly proportional to speed, the output is a crude constant current source. This is as close to regulation as it can manage. Unloaded ac output can exceed 100V rms.

In order to extract maximum power, the dynamo must be run at the lowest possible current. Additionally, advantage must be taken of the high unloaded output voltage. Rectification schemes that take large, short current pulses such as a simple diode and capacitor will not work however. This is due to the inductance limiting  $dI/dt$ .

A power factor corrector IC may be worth trying. In simple terms, a higher power output ought to be possible by using a higher voltage lamp with the same current rating as the original, at the expense of reduced brightness at lower speed.

Cycle lamps seem to manage an efficiency of about 5 lumens per watt. Leds vary from about 1lm/W to 30lm/W, but are usually quoted in candelas. Convert to lumens by multiplying by  $2\pi(1-\cos\phi)$  where  $\phi$  is the half angle of the output beam.

Rear lamp red leds capable of out-performing the filament lamp are reasonably common, but yellow leds for front lights are not. There are a few ultra-bright yellow types available from Hewlett-Packard (RS 826-723 and 823-717).

Filament-lamp brightness is proportional to the cube of applied voltage, current to the square root, and life inversely to the twelfth power,<sup>3</sup> but longer for an ac supply. Lower voltage lamps have thicker filaments, and therefore better mechanical shock resistance.

**Ian Benton**  
Ilkeston  
Derbyshire

## References

1. Smith, RJ, 'Circuits, Devices and Systems', Chapter 4, ISBN 0-471-80516-5
2. Admiralty 'Examples in Electrical Calculations', Chapter 24, HMSO B.R.158
3. Oshino Lamps catalogue

## Steve replies...

I agree with both correspondents that dynamos are simple constant-current ac machines, but I suspect the laminations of the stator are deliberately thick to reduce output voltage by increasing eddy currents at high speed. This technique is certainly used in the alternators of cheap motorcycles.

Using higher voltage bulbs does therefore work, but the physical effort required to produce a certain power output is disproportionately large. After a few lunch times wrestling with a propped-up bike, a handful of dynamos and an AVO, I have determined the following:


- A series capacitance in the circuit increases the output, probably by series resonance with the dynamo inductance. Selection of the value can produce an extra watt.

- No cycle dynamo has magnetics that are efficient enough to produce 6W without unacceptable physical effort – whatever electronics are fitted.

The next step is to try a different machine, perhaps a rare-earth, three-phase brushless dc motor, which should look like a 'star' wound generator (has anyone got one that I can experiment with?).

Note that 12Ω is the standard load used in BS bicycle specifications.


**Steve bush,**  
Epsom

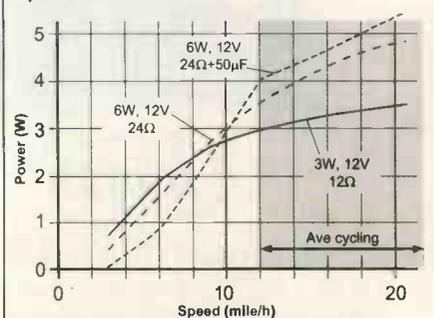

**Output versus loading for a Soubitez dynamo. British Standard loading is 12Ω but 24Ω with a series capacitor produced better results. Plots were produced using an average reading ac voltmeter so there will be some errors due to distortion of the waveforms involved.**


# Electronic Designs Right First Time?

## Schematic Design

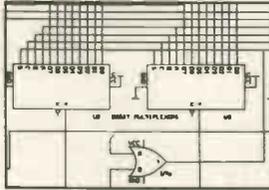


Create your schematics quickly and efficiently using EASY-PC Professional. Areas of the circuit can be highlighted on screen and simulated automatically using PULSAR, ANALYSER III and Z-MATCH our simulation and design programs.


## Digital and Analogue Simulation

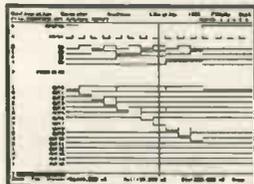

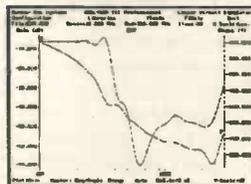Modify the configuration and change component values until the required performance is achieved.



## PCB Design

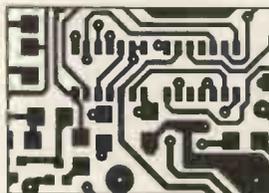

The design, complete with connectivity, can then be translated into the PCB. The connectivity and design rules can be checked automatically to ensure that the PCB matches the schematic. And with LAYAN the Parasitic effects of the PCB can be included in the Analogue Simulation



## Affordable Electronics CAD

<b>EASY-PC:</b> Entry level PCB and Sch. CAD.	<b>\$195.00</b>	<b>£98.00</b>
<b>EASY-PC Professional:</b> Schematic Capture and PCB CAD. Links directly to ANALYSER III, LAYAN and PULSAR.	<b>\$375.00</b>	<b>£195.00</b>
<b>PULSAR:</b> Digital Circuit Simulator ~ 1500 gate capacity.	<b>\$195.00</b>	<b>£98.00</b>
<b>ANALYSER III:</b> Linear Analogue Circuit Simulator ~ 130 node capability	<b>\$195.00</b>	<b>£98.00</b>
<b>LAYAN:</b> New Electro-magnetic layout Simulator. Include board parasitics in your Analogue simulations.	<b>\$950.00</b>	<b>£495.00</b>
<b>Z-MATCH for Windows:</b> Windows based Smith-Chart program for RF Engineers.	<b>\$475.00</b>	<b>£245.00</b>
<b>FILTECH:</b> Active and Passive Filter Design	<b>\$275.00</b>	<b>£145.00</b>
<i>We operate a no penalty upgrade policy. Technical support is FREE FOR LIFE. Special prices for Education</i>		US\$ prices include Post and Packing
		Sterling Prices exclude P&P and VAT.

## Number One Systems

Ref WW, Harding Way, St. Ives, Huntingdon, Cambs. PE17 4WR, UK.

For Full Information Please Write, Phone or Fax.

**Tel: +44 (0) 1480 461778**

**Fax: +44 (0) 1480 494042**


CIRCLE NO. 129 ON REPLY CARD


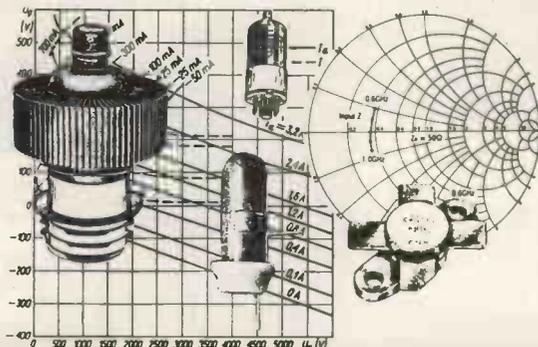
# CHELMER VALVE COMPANY

*If you need Valves/Tubes or RF Power Transistors e.t.c. ... then try us!*

We have vast stocks, widespread sources and 33 years specialist experience in meeting our customers requirements.



*Tuned to the needs of the Professional User*

Chelmer Valve Company, 130 New London Road, Chelmsford, Essex CM2 0RG, England

**44-01245-355296/265865**

Fax: 44-01245-490064

CIRCLE NO. 130 ON REPLY CARD



CIRCLE NO. 131 ON REPLY CARD

homet's nest of diverging views about the benefits, practicability and desirability of mobile television!  
**Adrian Grilli,**  
*Director of Broadcasting Services, Radiocommunications Agency, London*

### Give them a chance

Frank Ogden's leader Jobs for the Boys (July 1995) was, as usual, a model of clear prose – reasonably factual with an unmistakable conclusion. Regrettably that conclusion was wholly wrong.

Lord Thomson, when he chaired the IBA, argued in its latter days for "change with continuity" in broadcasting. That was in the late eighties when the ITV system was due for radical overhaul and the IBA, itself about to be disbanded.

My union BECTU, which represents all broadcasting, film and theatre categories, including NTL and BBC transmission staff, agrees that continuity is a vitally necessary concomitant of change. The existing terrestrial transmission networks should provide that continuity between analogue and digital transmission, for the sake of viewers, listeners and programme makers.

Satellite and cable delivery are playing an increasing role. However it is clear that neither separately nor together can they soon replace

terrestrial transmission – if ever.

That durable and reliable system, comprising the hundreds of sites owned by BBC, and NTL, and importantly operated by highly trained and qualified engineering staff will remain the main delivery system for decades to come.

To deny BBC and NTL any role in digital broadcasting would be both wrong and shortsighted. Both organisations are developing commercial activity in telecommunications. If their core businesses of television and radio transmission were restricted both would be hard pressed to maintain and grow those increasingly important sectors.

Do not hasten the end of BBC and NTL – they both have an important role still to play.

**Brian Marsh,**  
*National Organiser BECTU*

### Emi still not understood...

Dr Walton's letter, EMI Still Not Understood, *EW+WW*, July 1995, took its theme from a newspaper article which contained unsubstantiated statements. I would therefore like to take this opportunity of putting the record straight and allaying Dr Walton's concerns.

Aviation authorities and industry have, for many years, recognised that

aircraft and their systems need to be protected against the effects of electro magnetic interference, EMI. Sources of EMI generated within the aircraft can be non-intentional or intentional as in the case of the aircraft's own high power communication transmitters. The required protection is demonstrated by ensuring that aircraft and their systems are qualified to electro magnetic compatibility, EMC, standards appropriate to aviation operations. These standards, which were written in conjunction with aviation industry experts, have been continuously updated as the level of understanding of EMC and the possibility and consequences of EMI have increased. As a result of the application of these standards, aircraft and their systems have continued to demonstrate a high level of immunity to EMI.

The issue of interference to aircraft systems by portable electronic devices, PEDs, is one which it is correct to become concerned about. There have been a number of reports of interference with aircraft navigation systems (but not with flight critical systems as inferred in the newspaper article), which were investigated but could not be substantiated. For this reason, aviation authorities have adopted a cautious approach and many have imposed a ban on the use of PEDs

### Seeking failure

Can anyone help? I am researching the cause and consequences of equipment failure and I am interested in hearing from readers who have first hand knowledge of specific instances. I would like any failure details of electronics, mechanisms, structures, software or procedures.

Photographs, reports etc would be much appreciated particularly if the failure resulted in serious mishap which might have been avoided.

All letters will be acknowledged.  
**Bob Collins,** 1 Church Street, The Square, Wimborne Minster, Dorset BH21 1JH.

during certain phases of flight. However, they are not content with such a simplistic approach and are currently researching the issue to determine if PEDs are capable of emitting sufficient power to cause airborne system disruption and how any electromagnetic coupling between PEDs and airborne systems could occur.

In the same way that airborne inter/intra-system EMC issues have been recognised as a potential problem, so has lightning. To this end, aviation authorities also require that aircraft and their systems demonstrate immunity to the effects of electromagnetic energy generated

# Measure & Record Temperature on your PC.


Pico's **NEW TC-08** is a 8 channel thermocouple to PC converter. Supplied with PicoLog datalogging software it is designed to allow simple yet accurate temperature recording onto a computer.

TC-08 has provision for up to 8 thermocouples -B,E,J,K,R,S and T types. For type K the resolution over -270°C to +1300°C is better than 0.1°C and accurate to ±0.1°C.


**NEW from Pico TC-08 £ 199.00**

complete with PicoLog, software drivers and connecting cable. A range of thermocouple probes is available.

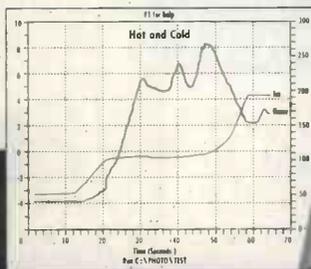**Call for your Guide on 'Virtual Instrumentation' and Release your PC Potential.**



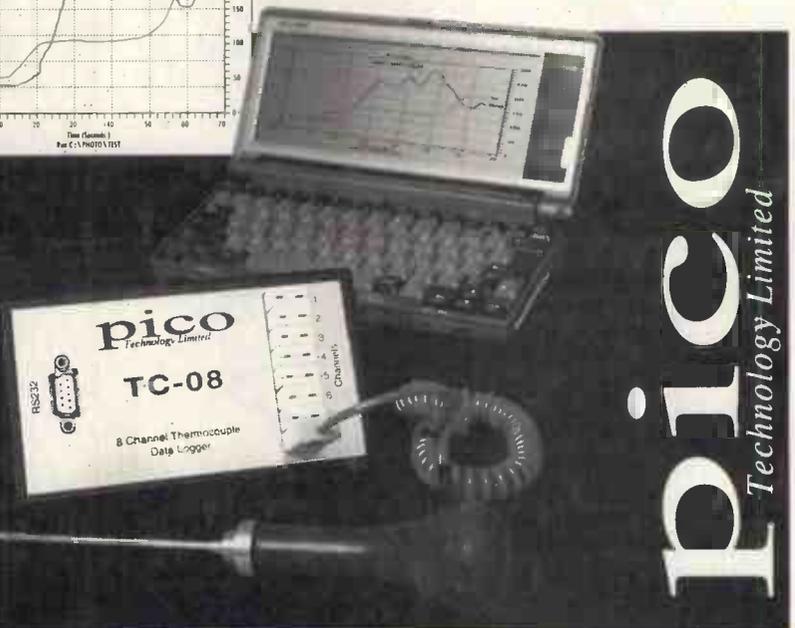**PicoLog** Advanced data logging software. Samples can be taken every second or as slow as one per hour and displayed in real time.



Pico Technology Ltd. Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ UK.

Tel: 01954 - 211716 Fax: 01954 - 211880




Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT. Carriage Overseas £9

CIRCLE NO. 132 ON REPLY CARD

**When Performance is more important than size:-**  
two new re-programmable BASIC Stamp Computers.



**BS1-IC**  
8 I/O lines  
up to 100 program lines  
2,000 lines/sec  
Comms to 2400 baud  
**£29** single price

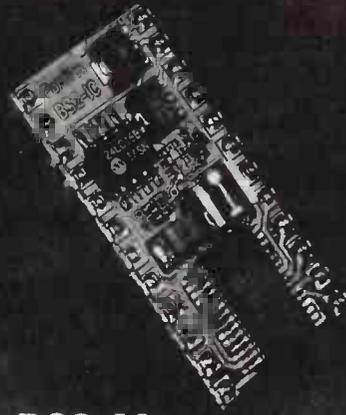


**BS2-IC**  
16 I/O lines  
up to 600 program lines  
10,000 lines/sec  
Comms to 9600 baud  
**£49** single price

Programming package £66

Milford Instruments Tel 01977 683665 Fax 01977 681465

CIRCLE NO. 133 ON REPLY CARD

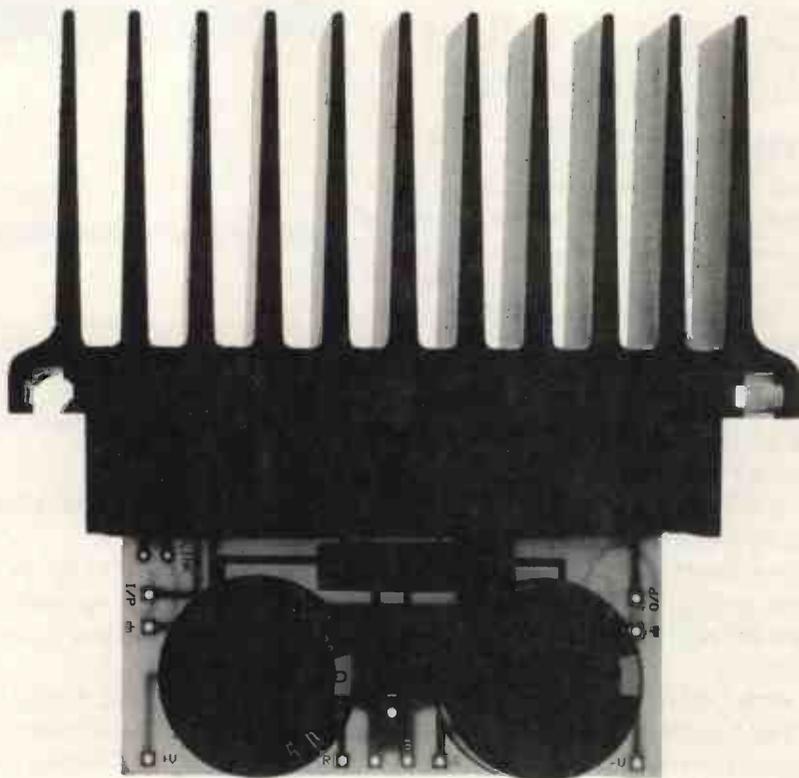

**NEW**  
**SUPERB QUALITY**  
**RANGE**

**AUDIO**  
**LEADING EDGE**  
**MODULES**

**ILP ELECTRONICS LTD WINCHEAP**  
**CANTERBURY KENT CT1 3RB U.K.**



**TELEPHONE +44 (0)1227 454778**  
**FACSIMILE +44 (0)1227 450507**

CIRCLE NO. 134 ON REPLY CARD

by lightning. Again, these requirements are written against aviation industry standards.

Considering the issue of how airborne systems withstand the electromagnetic 'explosion' of lightning but not the electromagnetic 'whisper' of PEDs, remember that the 'explosion' takes place outside of the Faraday cage provided by the aircraft fuselage.

With regard to the possibility of terrorist attack, modern aircraft and their systems are even now under 'attack' by high power external rf sources such as commercial broadcast transmitters, satellite communication transmitters and surveillance radars, which generate very high electromagnetic fields. Again, aviation authorities have recognised this problem and, in conjunction with aviation industry experts, have developed design and test criteria for aircraft and their systems to ensure they remain immune to such rf illuminations. These design and certification criteria should also ensure the immunity of flight critical systems to potential terrorist activity, be it generated by an on-board suicide 'emitter', or a source outside the aircraft.

**C F. Phelan**

Head of Avionics and Electrical Systems Group, CAA

## ...nor are analogue systems

Dr David Walton writing about the laptop computer ban in airplanes (Letters, July issue) may well be an expert on digital systems and the electromagnetic compatibility rules needed to make those systems work safely. But he is not aware of the analogue systems used in avionics.

Radio beacons and instrument landing systems (ILS) are analogue. They rely on fixed land-based transmitters continuously sending waves - on clean channels - to airborne receivers.

These waves are modulated and/or beam-formed so that airplanes using directional antennas and/or discriminating detectors can find their way safely towards the next beacon. In the axis of the landing runway the safe glide path for touching down on the right spot of the runway can be found. This allows manoeuvres to start many miles away from beacons through heavy clouds or fog.

Lightning interference may well hide such weak oncoming vhf radio waves, but only for very short durations. Proper operation relies on continuous heading or path searching and keeping, except during lightning pulses. A lightning

pulse cannot set any data bit. It is an insignificant transient type of interference which can be filtered out at any step in the process.

Most terrorists do not want to be inside the airplane they want to destroy. They also want a reliable means of destroying an airplane, which is not simple. A jammer near an airport would have to be on the right frequency, which is easy. But in order to go unnoticed long enough to lead an airplane to a crash, the transmitter also needs to radiate the right power with the right antenna beams - very unlikely.

Conversely, weak but continuous interference - any harmonic of a local oscillator or computer clock for example - from aboard the airplane can impair the operation of the ILS, if this interference is within the radio channel. The problem is especially acute when the signal is radiated by whip antenna or mouse cord. Under worst-case conditions, the interference goes unnoticed, but the instrument on the dashboard gives continuous false bearing or glide angle that can result in collision or crash.

So the best way to prevent terrorist attacks against ILS is still the ban of computers, radios, etc in airplanes.

**Louis Aubree,**

Nantes,  
France

## Self reacting

I must admit I was disappointed in Ivor Brown's example of negative feedback operation (Letters, June 95) as it seems likely to add to the confusion that exists in some minds between open-loop bandwidth and slew rate. He says "limited open-loop bandwidth prevents the feedback signal from immediately following the system input." This is not true unless the amplifier has been pushed into slew-limit.

No linear circuit can introduce a pure-time delay; the output must begin to respond at once, even if it takes a long time to respond fully. In the typical amplifier the dominant pole capacitor introduces a 90° phase shift between input pair and output at all but the lowest frequencies; this is not in any way the same thing as a time delay. The phrase "delayed feedback" is sometimes used to describe this situation, and it is a wretchedly inaccurate term; if you really delay feedback to a power amplifier, it will turn into the proverbial power oscillator as sure as night follows day.

I agree with Ivor that the amount of negative feedback applied should be maximised at all audio frequencies, and to my mind the only limit on this is the requirement for hf stability; the point at issue is how to go about it.


## The new schematic capture program Geswin (GESECA for Windows™) adds more than a pretty face to SpiceAge. Upgrade for £100+ VAT\*

- Geswin DDE links with SpiceAge to provide instant circuit editing. Because this link enables SpiceAge to retain all its simulation settings, the schematic (produced by Geswin) is uncluttered so that you can create clean drawings that may be clipboarded into your other Windows applications.
- You can clipboard sections of your netlist from SpiceAge back into Geswin's attribute Inspector if you wish to use patches of existing circuits.
- Geswin has inherited GESECA's speed and ease of use. You will find it's best-loved "bucket of bits" components' store waiting for your instant use from a special self-replenishing window.
- The SpiceAge component library has been expanded and re-drawn into "stubbies". The new symbols allow more components to fit within a given screen area without compromising clarity.
- Multiple windows allow you to scratch pad your designs (simulating as you work) and clipboard them into a fair copy window.
- File compatible with GESECA: schematics and components from GESECA may be read.
- Comprehensive HELP provides reference material; tutorial style manual reassures you of your own intuition.
- Geswin automatically invokes (or switches to) SpiceAge; you can also invoke Geswin from SpiceAge.

Please contact Those Engineers Ltd, 31 Birkbeck Road, LONDON NW7 4BP.

Tel 0181-906 0155, FAX 0181-906 0969.

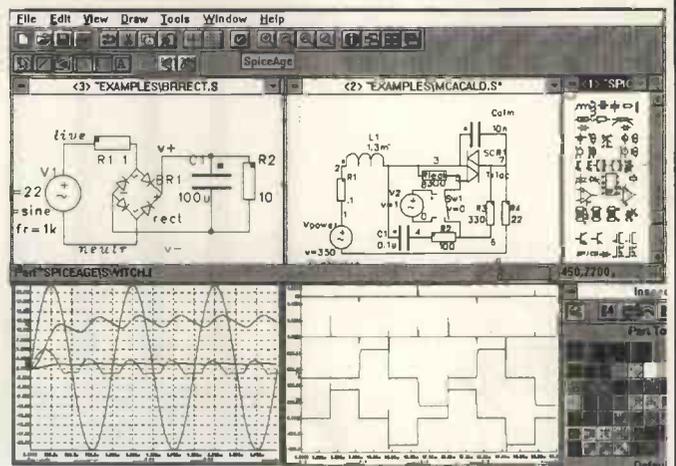
\*upgrade price from GESECA; £295 + VAT new



Those  
Engineers Ltd



CIRCLE NO. 135 ON REPLY CARD

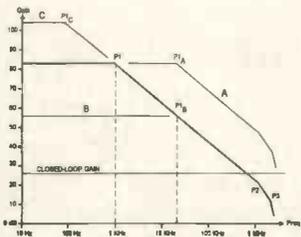

Open and closed-loop gain for a typical generic power amplifier with closed-loop gain set at 26dB.

The heavy line in the diagram shows the open and closed-loop gain for a typical generic amplifier; closed-loop gain is set at +26dB as usual. The second and third poles P2 & 3 are just beyond the intersection of the two gain lines, so the curves close on each other at no more than 6dB/octave and Nyquist stability is obtained. Dominant pole P1 is a 1kHz. Below this frequency the open-loop gain curve levels out the feedback factor becomes constant.

So, supposing we want to increase the negative feedback to a maximum. What can be done? Clearly, if our target is a constant negative feedback factor across the audio band, which appears superficially attractive, the P1 must be increased to 20kHz, and we can claim 'high open-loop bandwidth'. This can be done in two ways: firstly we can increase the

open-loop gain at hf by decreasing the compensation capacitor so that we get curve A with P1A at 20kHz; but this also lifts P2 & 3 above the unity loop-gain level and we get a power oscillator and the tweeters explode.

Alternatively we can reduce the open-loop gain at low frequencies, by shunting the compensation capacitor with a resistor, giving curve B with P1B at 20kHz once more. This will be stable, and may look nice on a graph, but seriously reduces the amount of feedback at low frequencies, gives much more distortion than necessary, and badly degrades ripple rejection.<sup>1</sup> Neither A nor B is acceptable.

I hold that the amount of feedback should be truly maximised, as said before. The open-loop gain is therefore left alone in the falling 6dB/octave region, where it is already maximal if we stick to this slope. Instead the flat low-frequency region is raised to give curve C, which has a lot more negative feedback at low frequencies than the original. This is simply done either by cascading or adding a beta-enhancing emitter-follower to the voltage amplifier stage!<sup>1</sup> This in turn pushes the new dominant pole PIC down to a much lower frequency, possibly as low as sub-10Hz, but so what? We have only altered linear gains in various parts of the circuit, and have not affected the non-linear limit

phenomenon of slew rate at all. I have calculated this, simulated it, measured it and even built a special amplifier where P1 could be varied with a knob on the front panel, so I'm pretty sure of my ground here.

The only way to increase the amount of negative feedback applied above that shown in curve C is to make the compensation more complex, so that we are not confined to a 6dB/octave gain roll-off. In the form of two-pole compensation in the second reference, the gain is held constant up to a higher frequency, before rolling off more quickly; the key to stability is that the slope reduces to 6dB/octave before the Nyquist gain intersection is reached.

To say it once more; open-loop bandwidth and slew rate are nothing to do with each other. High-gain op-amps with sub-1Hz bandwidths and blindingly fast slewing are as common as the grass (if somewhat less cheap) and if that doesn't demonstrate the point beyond doubt then I really don't know what will.

In his letter Ivor also stigmatises sinewaves as steady-state signals, which is presumably meant to imply that they are in some way particularly easy for an amplifier to handle. Since sinewaves have an unending series of non-zero differentials, 'steady' hardly comes into it. I know of no evidence that sinewaves of randomly varying


amplitude would provide a more searching test of amplifier competence.

I think this view must be the result of anthropomorphic thinking about amplifiers; twenty sinewaves of different frequencies may be conceptually more complex to us, but to an amplifier it resolves to a single instantaneous voltage that must be increased in amplitude. An amplitude. An amplifier has no perspective on the signal arriving at its input, but must take it as it comes; one might also say, 'the amplifier has no memory' by analogy with the roulette wheel.

To remind us that a distortion analyser is incapable of distinguishing between Bartok and Bon Jovi is not really necessary; why ever should it mimic the human brain? I don't want a machine to enjoy music for me so that I don't have to do it...

1. Self, D, 'Distortion off the rails' *EW+WW* Mar 1995, p210
2. Self, D, 'Distortion in Power amplifiers' *EW+WW* Feb 1994, p140.
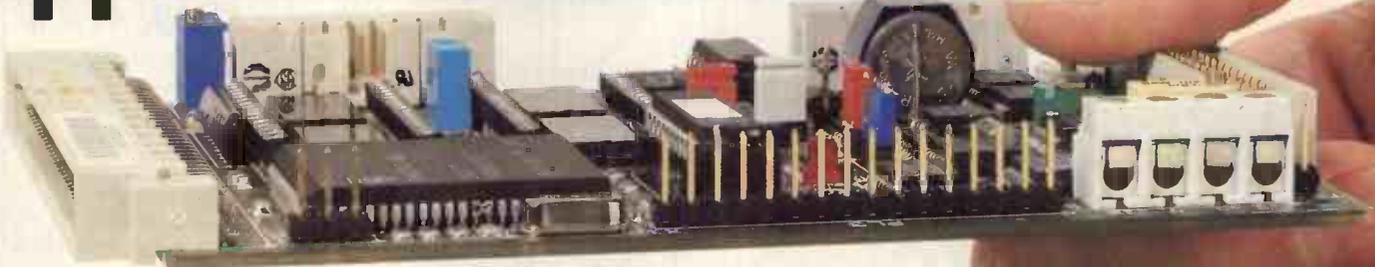
# The power to take BIG applications on board!



## The NEW CMS Mini-Module

### A UNIQUE LOW COST HIGHLY DEVELOPED MODULE

The Mini-Module is a small 100 x 118 mm all CMOS microcontroller containing a 32 bit microprocessor, 32 digital I/O, 4 analogue in, 1 analogue out, direct output to LCD displays, keyboard input, serial port, 1°C port, 512k EPROM space, 128K SRAM, RTC, Timers, plus much more. The board, on its own, or in combination with other peripheral cards, is capable of outstanding performance.

The programming environment is very simple to use. When connected to an IBM PC, programs can be written from

most word processors and can be downloaded into the module. The module will compile the program into very fast executable code.

- PROGRAM IN C, C++ OR MODULA-2.
- CHOICE OF OPERATING SYSTEMS OS9 68K OR MINOS.
- IDEAL FOR ONE OFF APPLICATIONS
- EASY TO USE, VERY FAST DEVELOPMENT.


The Mini-Module provides the complete solution to many applications and can be customised or expanded to suit your needs.

# CMS

**Cambridge Microprocessor  
Systems Limited**

Unit 17-18, Zone 'D', Chelmsford Road Ind. Est.,  
Great Dunmow, Essex, UK. CM6 1XG  
Phone 0371 875644 FAX 0371 876077

# Programming Solutions

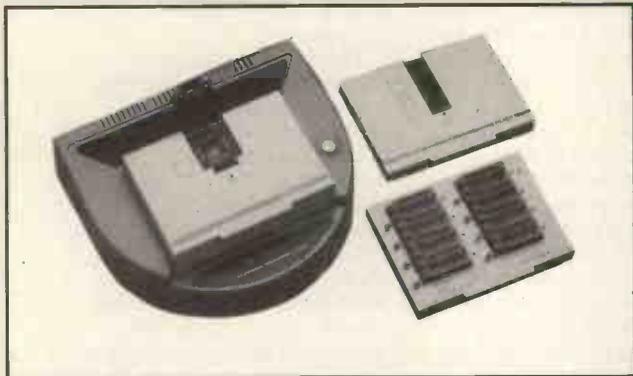

## Universal Programmer

- ◆ Uses standard pc printer port works with notebook and handbook pc's
- ◆ Pin driver expansion can drive up to 256 pins.
- ◆ Supports over 2000 IC's - 3 and 5 volt devices. EPROMs, E<sup>2</sup>PROMs, Bipolars, Flash, Serial EPROMs over 150 microcontrollers, WSI/Philips PSDs, PLDs, EPLDs, PEELs, PALs, GALs, FPGAs including MACH, MAX, MAPL & Xilinx parts
- ◆ Universal DIL (up to 48 pins), PLCC and gang PACs
- ◆ Powerful full colour menu driven software.
- ◆ Approved by AMD, TI, NatSemi, etc...
- ◆ Tests TTL, CMOS and SRAM devices (including SIMMS)

ONLY  
**£595**

## Multi-Device Programmer

- ◆ EPROMs, E<sup>2</sup>PROMs, Flash EPROMs, Serial E<sup>2</sup>PROMs, PLDs, GALs, PEELs, EPLDs, MACHs & WSI PSDs Micros - Intel, Microchip, Motorola, Zilog
- ◆ Fast programming algorithms.
- ◆ Connects direct to pc printer port.
- ◆ Simple full colour software.
- ◆ No expensive adapters.

ONLY  
**£325**

Prices exclude VAT & Delivery

## Eprom Programmer

EPROMs, E<sup>2</sup>PROMs, Flash and 8748/51 micros.  
Fast programming algorithms. Simple colour menu operation.

ONLY  
**£139**

EMULATORS • SIMULATORS • COMPILERS • ASSEMBLERS  
PROGRAMMERS • 8051 8085 Z8 68020 77C82 80C552  
320C25 68HC11 6301 6502 87C751 65816 Z80 6809  
PIC 7720 MIPS etc.

**SMART**  
COMMUNICATIONS

2 Field End • Arkley • Barnet • Herts • EN5 3EZ • England

Telephone +44 (0)181 441 3890 Fax +44 (0)181 441 1843

CIRCLE NO. 137 ON REPLY CARD



## JPG Electronics

High quality stepping motor kits (all including stepping motors) 'Comstep' independent control of 2 stepping motors by PC (Via the parallel port) with 2 motors and software ..... Kit £67.00  
Ready built ..... £99.00  
Software support and 4 digital inputs kit ..... £27.00  
Power interface 4A kit ..... £36.00  
Power interface 8A kit ..... £46.00  
Stepper kit 4 (manual control) includes 200 step stepping motor and control circuit ..... £23.00  
We are now stocking a range of stepping motors and kits to drive them, please ask for the stepping motor data sheet for full information.  
Inventor toroidal transformers 225VA 10.5-0-10.5 primary 0-260-285 secondary ..... £29.95  
LEDs 3mm or 5mm red or green ..... 7p each  
Yellow ..... 11p each  
Cable ties, 1p each, £5.95 per 1000, £49.50 per 10,000  
High quality photo resist copper clad epoxy glass boards  
Dimensions single sided double sided  
3x4 inches £1.95 £1.25  
4x8 inches £2.75 £2.99  
6x12 inches £6.20  
12x12 inches £12.25  
Rechargeable Batteries  
AA (HP7) 500mAh ..... £0.99  
AA 500mAh with solder tags ..... £1.55  
AA 700mAh ..... £1.75  
C(HPI) 1.8AH ..... £2.20  
C2AH with solder tags ..... £3.60  
D(HPI) 1.2AH ..... £2.60  
D4AH with solder tags ..... £4.95  
Sub C with solder tags ..... £1.55  
1/3 AA with tags (Phillips CTV) ..... £1.95  
AAA (HP16) 180mAh ..... £1.75  
Standard charger charges 4 AA cells in 5 hours or 4Cs or Ds in 12-14 hours + 1xPP3 (1, 2, 3 or 4 cells may be charged at a time) ..... £5.95  
High power charger as above but charges the Cs and Ds in 5 hours. AAs, Cs and Ds must be charged in 2s or 4s ..... £10.95  
Nickel Metal Hydride AA cells high capacity with no memory. If charged at 100ma and discharged at 250ma or less 1100mAh capacity (lower capacity for high discharge rates) ..... £3.75  
1100mAh ..... £3.75  
Special offers, please check for availability.  
Stick of 4 4x2x16mm Nicad batteries 171x16mm dia with red & black leads 4.8v ..... £5.95  
115V AC 80V DC motor 4x22mm shaft 50mm dia x 60 long body (excluding the shaft) it has a replaceable thermal fuse and brushes ..... £4.95 each (£3.95 100+)  
7 segment common anode led display 12mm £0.45  
LM557K T03 case variable regulator ..... £1.95  
GaAs FET low leakage current S8873 ..... £12.95 each (£9.95 10+, £7.95 100+)  
BS250 P channel mosfet ..... £0.45  
BC550 transistor ..... £3.95 per 100  
74LS05 hex inverter ..... £10.00 per 100  
Used 8748 Microcontroller ..... £3.50


SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet ..... £1.95  
AM27502 ..... £1.25 each (90p 100+)  
CD4007UB ..... 10p 100+ (6p 1000+)  
Sinclair light gun terminated with a jack plug and PPS chip gives a signal when pointed at 50Hz flickering light with output wave form chart ..... £6.00  
DC-DC convertor Reliability model V12P5 12v In 5v 200ma out 500v input to output Isolation with data ..... £4.95 each or pack of 10 £39.50  
Hour counter used 7 digit 240V AC 50Hz ..... £1.45  
QWERTY keyboard 58 key good quality switches new ..... £6.00  
Airpax A82909-C large stepping motor 14v 7.5 step 27ohm 68mm dia body 6.3mm shaft ..... £8.95 or £200.00 for a box of 30  
Polyester capacitors box type 22.5mm lead pitch  
0.9uf 250vdc 18p each 14p...100+ 9p...1000+ 1uf 250vdc ..... 20p each  
15p...100+ 10p...1000+ ..... 15p each  
1uf 50v bipolar electrolytic axial leads ..... 40p each  
0.22uf 250v polyester axial leads ..... 15p each  
100+ ..... 7.5p 100+  
Polypropylene 1uf 400vdc (Wima MKP10) 27.5mm pitch 32x29x17mm case ..... 75p each  
60p 100+  
Philips 125 series solid aluminium axial leads - 35uf 10v & 2.2uf 40v ..... 25p 100+  
Philips 108 series long life 22uf 63v axial ..... 15p 1000+  
Multilayer AVX ceramic capacitors all 5mm pitch 100v 100pF, 150pF, 220pF, 10,000pF (10n) ..... £138.00 for 5  
10p each 5p...100+ 3.5p...1000+  
500pF compression trimmer ..... 60p  
40 uf 370vac motor start capacitor (dielectric type containing no pcb's) ..... £5.95 or £49.50 for 10  
Solid carbon resistors very low inductance ideal for RF circuits - 27ohm 2W, 68ohm 2W ..... 25p each 15p each 100+  
We have a range of 0.25w 0.5w 1w and 2w solid carbon resistors, please send SAE for list  
P.C. 100W PSU (Intel part 201035-001) with standard motherboard and 5 disk drive connectors, fan and mains Inlet/outlet connectors on back and switch on the side (top for tower case) dims 212x149x149mm excluding switch ..... £138.00 for 5  
MX180 Digital multimeter 17 ranges 1000vdc 750vac 2mohm 200mA transistor Hfe 9v and 1.5v battery test ..... £12.95  
AMD 27256-3 Eproms ..... £2.00 each £1.25/100+  
DIP switch 3PC0 12 pin (ERG SDC-3-025) 60p each 40p...100+  
Disk drive boxes for 5.25 disk drive with room for a power supply, light grey plastic, 67x268x247mm ..... £7.95 or £49.50 for 10  
Hand held ultrasonic remote control ..... £3.95  
CV2486 gas relay, 30x10mm dia with 3 wire terminals, will also work as a neon light ..... 20p each £7.50 per 100

All products advertised are new and unused unless otherwise stated.  
Wide range of CMOS TTL 74HC 74F Linear Translators kits. Rechargeable batteries, capacitors, tools etc always in stock. Please add £1.95 towards p&p. VAT included in all prices.

JPG Electronics, 276-278 Chatsworth Road, Chesterfield S40 2BH  
Access/Visa (01246) 211202 Fax: 550959 Callers welcome

CIRCLE NO. 138 ON REPLY CARD

## CROSSWARE

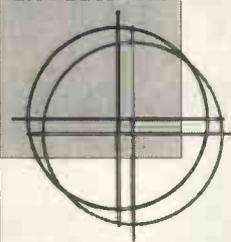

CROSS DEVELOPMENT  
SOFTWARE TOOLS FOR THE PC

**8051 C • ASSEMBLY**  
• **SIMULATION**

FULLY SUPPORTED  
QUALITY SOFTWARE

### > 8051 C Compiler (DOS)

An optimising C compiler with full support for floating point arithmetic, interrupts, embedded assembler, linking and relocation, IEEB695 debug output. Includes a complete relocatable cross assembler.  
Price: £349.00

### > 8051 Cross Assembler (DOS)

Available in two variants: absolute and relocatable. The relocatable assembler allows you to flexibly link and locate your program into 8051 address space and generates IEEB695 debug output for symbolic information (ideal for use with our simulator). The absolute assembler is easy to use and creates final 8051 code from a single assembler source file.  
Prices: Relocatable £169.00, Absolute £99.00

### > 8051 Simulator (Microsoft Windows)

Watch your program run on your PC. Set breakpoints, single step, trace, watch and modify memory and SFR's. Generate interrupts, run the timers, serial port and parallel ports. All without a single piece of 8051 hardware. Works with any 8051 assembler or compiler that generates Intel hex, OMF51, IEEB695 or binary output. Uses debug information in OMF51 and IEEB695 files to create a symbolic disassembly of your program.  
Price: £148.00

Further information from: (prices exclude VAT and delivery)

CROSSWARE PRODUCTS  
St John's Innovation Centre, Cowley Road, Cambridge, CB4 4WS, UK  
Tel: +44 (0) 1223 421263, Fax: +44 (0) 1223 421006  
BBS: +44 (0) 1223 421207 (8-N-1), Internet: sales@crossware.com

CIRCLE NO. 139 ON REPLY CARD

# Embedded PC POWER

Need a tough  
PC for an  
industrial  
application?



Arcom's SCIMX, on the rugged single-Eurocard STEbus, provides unprecedented power and flexibility: 486SLC performance, full PC-AT compatibility, over 10Mbytes of RAM and Flash EPROM, and three local expansion routes!

It's a real breakthrough for embedded DOS/Windows developers -  
call for details:

**STEbus**

**Arcom**  
CONTROL SYSTEMS LTD

Tel: (0223) 411200 Fax: 410457

CIRCLE NO. 140 ON REPLY CARD

# RADIO MODEM


- ★ MPT 1329 licence exempt.
- ★ Range 10– 20km in free space or 1km in buildings.
- ★ Half duplex asynchronous transmission at 4800/9600 bits/sec.
- ★ Serial interface with baud rates of 1200, 2400, 4800 and 9600.
- ★ 4K of buffer memory.
- ★ Predictor/corrector error checking.
- ★ Automatic repeater mode to extend range.
- ★ Station addressable.
- ★ Analogue and digital interfaces.
- ★ Low power battery operation.




**Warwick Industrial Electronics Ltd**  
The Manor Aston Flamville  
Leicestershire  
Tel: 01455 233616 Fax: 01455 233179

CIRCLE NO. 141 ON REPLY CARD


IF YOU'VE GOT ONE OF THESE

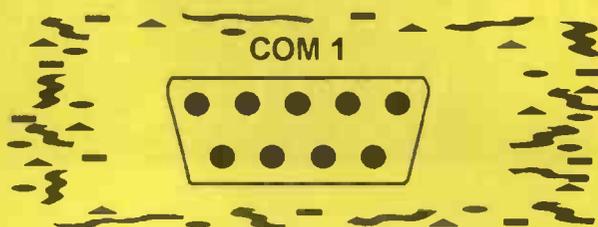

AND ONE OF THESE

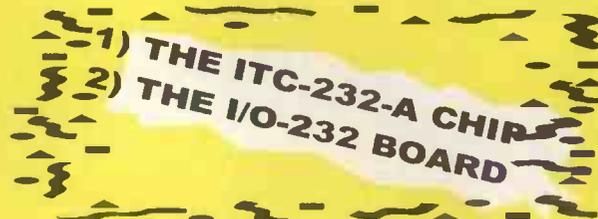

DRIVE ALL OF THESE

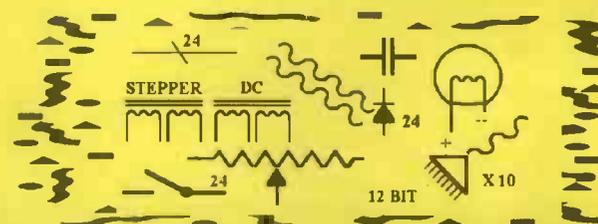


AND SENSE ALL OF THESE



USING ONLY ONE OF THESE



AND NONE OF THIS

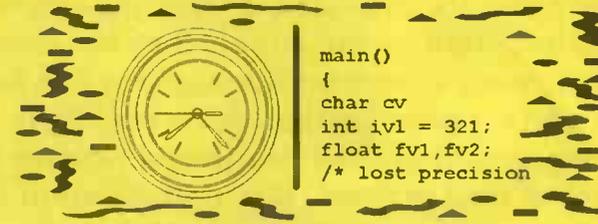

£300 TO JUST £30

TIMELY TECHNOLOGY LIMITED  
TEL : 01536 791269. FAX : 01536 790730  
MILLBANK, KETTERING ROAD  
LITTLE CRANSLEY, NORTHANTS NN14 1PJ

CIRCLE NO. 142 ON REPLY CARD

# INTERFACING WITH C



HOWARD HUTCHINGS

If you have followed our series on the use of the C programming language, then you will recognise its value to the practising engineer.

The book is a storehouse of information that will be of lasting value to anyone involved in the design of filters, A-to-D conversion, convolution, fourier and many other applications, with not a soldering iron in sight.

To complement the published series, Howard Hutchings has written additional chapters on D-to-A and A-to-D conversion, waveform synthesis and audio special effects, including echo and reverberation. An appendix provides a 'getting started' introduction to the running of the many programs scattered throughout the book.

This is a practical guide to real-time programming. The programs having been tested and proved. It is a distillation of the teaching of computer-assisted engineering at Humberside Polytechnic, at which Dr Hutchings is a senior lecturer.



A disk containing all the example listings used in this book is available, Please specify size required

Please supply \_\_\_\_\_ copies of  
**INTERFACING WITH C** Price **£14.95**  
Please supply \_\_\_\_\_ copies of  
**Disk containing all the example listings** £15.00.

Remittance enclosed £ \_\_\_\_\_

**Interfacing with C can be obtained from Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS**

Cheques should be made payable to  
Reed Business Publishing Group Ltd

Please debit my credit card as follows:  
Access/Master    Barclay/Visa    Amex    Diners

Credit Card No. \_\_\_\_\_

Exp date \_\_\_\_\_

NAME (Please print) \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

POST CODE \_\_\_\_\_

DATE \_\_\_\_\_ TELE \_\_\_\_\_

SIGNATURE \_\_\_\_\_

VAT NO. \_\_\_\_\_


If in the UK please allow 28 days for delivery. All prices are correct at time of going to press but may be subject to change.

**Credit card orders  
accepted by phone.  
Call 0181 652 3614.**

# STOP! Just Take Two Steps to do Your Measurement



## TiePieSCOPE

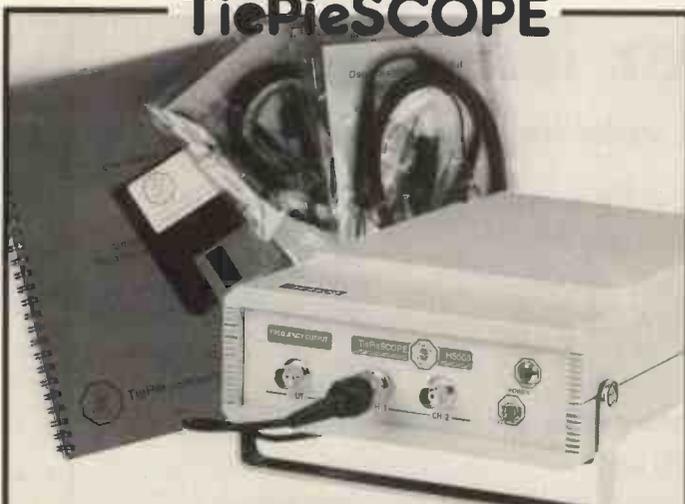

**HS508 Complete set  
for £ 597.00**

You can simply plug the new TiePieSCOPE - HS508 into the parallel port of your portable or desktop PC. With the advanced software, you can use this two channel, 8 bits, 50 MHz measuring instrument as a fast digital storage oscilloscope, including a lot more features than a single oscilloscope! Moreover, the TiePieSCOPE - HS508 contains a multiple display voltmeter (up to 5 MHz true RMS), a spectrum analyzer with an harmonic distortion meter and a transient recorder for recording a variety of signals. The TiePieSCOPE - HS508 is supplied complete with user manual, software, and two probes.

Call now for a free demo diskette and our catalog!!

### TiePie engineering (UK)

✉ 28. Stephenson Rd, Industrial Est., ST. IVES, CAMBS PE17 4WJ  
Tel.: (01480) 460028 - Fax: (01480) 460340

### TiePie engineering, The Netherlands

✉ P.O. Box 115, 8900 AC LEEUWARDEN  
📍 Batterserreed 2, 9023 AR JORWERD


Tel.: (31) 5106 9238 - Fax: (31) 5106 9704

# 20% discount – Electro-acoustic measurement system for under £750

Until 30 September, *EW+WW* can obtain 20% discount on Clio – a pc-based electro-acoustic measurement system that operates under pc control. Normally, this system costs £938.83 including vat, but readers can obtain the system at the special price of £749.90 fully inclusive.

Manufactured by Audiomatica, Clio is a complete electro-acoustic measurement system combining several instruments for testing at audio frequencies. The system is designed to work as a precision a-to-d/d-to-a audio front end for your pc. It is capable of generating pre-defined stimuli, for example sine, square, burst, and noise signals etc, analysing signals present at its inputs both in frequency and time domains – the wide range of programmable output attenuation and input gain allows interface to the outer world.

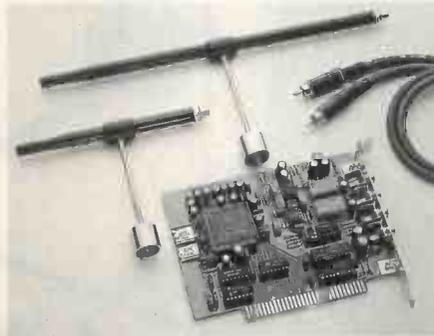The system is supplied with Windows like, mouse orientated pc software.



This offer is open to readers in the UK only until end September 1995. For more information, contact DBS Audio at P.O. Box 91, Bury St Edmunds, Suffolk IP30 0NF. Tel 01284 828926, fax 01284 828026. Make cheques payable to DBS Audio and send to the above address or post/fax your order with Visa or Access card type plus card-holder address, card number and expiry date.

Reviewed in *EW+WW*,  
August 1995, p. 656  
'AF analysis via the pc'

## 20% discount – exclusive to *EW+WW* readers


Item	Normal price	<i>EW+WW</i> discount price
Clio base system	£938.83	£749.90 fully inclusive
Clio mic. 02	£175.07	£163.90 fully inclusive
Base system + mic	£1113.90	£913.80 fully inclusive

## Next month's issue

Free with the October issue
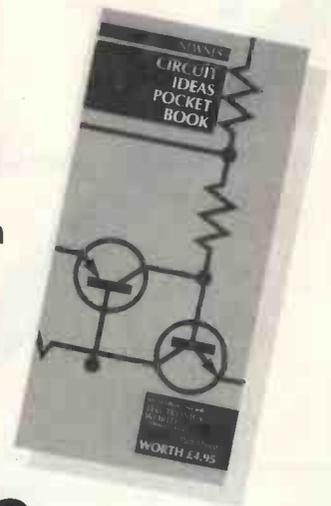
### Cover-mounted Circuit Ideas Pocket Book – Part III


Worth £4.95, this book is a compilation of circuit ideas from *EW+WW* brought together in handy pocket-reference format. Among the ideas are improved solutions to existing problems and methods for saving costs or components, but also many unique electronic designs.



## Free with November issue
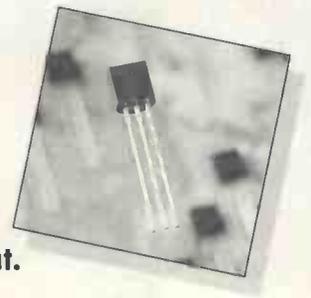
### Cover-mounted TO-92 three-terminal voltage regulator

Manufactured by Zetex, this high-performance 5V regulator is similar to the industry standard 78L05, except that it has a quiescent current of around 350µA as opposed to 2-3mA. In addition, it has double the output current, at 200mA, and improved line and load regulation.



**Remember... you can reserve your copy of *Electronics World* with your local newsagent. Simply fill in the card in the magazine to guarantee your monthly copy.**

**SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK**

HP New Colour Spectrum Analysers  
 HP141T+8552B IF + 8553B RF - 1KHz-110Mc/s - £700.  
 HP141T+8552B IF + 8554B RF - 100KHz-1250Mc/s - £900.  
 HP141T+8552B IF + 8556A RF - 20Hz-300KHz - £700.  
 Special Offer just in from MOD Qty 40 HP8555A RF Units 10Mc/s - 18GHzS.  
 HP141T+8552B IF + 8555A 10Mc/s-18GHzS - £1200.  
 HP ANZ Units Available separately - New Colours - Tested  
 HP141T Mainframe - £350.  
 HP8552B IF - £300.  
 HP8553B RF 1KHz to 110Mc/s - £200.  
 HP8554B RF 100KHz to 1250Mc/s - £500.  
 HP8555A RF 10Mc/s to 18GHzS - £800.  
 HP8556A RF 20Hz to 300KHzS - £250.  
 HP8443A Tracking Generator Counter 100KHz-110Mc/s - £300.  
 HP8445B Tracking Preselctor DC to 18GHz - £350.  
 HP3580A 5Hz - 50KHz ANZ - £750 - £1000.  
 HP3582A .02Hz to 25.6KHz - £2k.  
 HP8568A 100Hz-1500Mc/s ANZ - £6k.  
 HP8569B 10Mc/s-22GHz ANZ - £6k.  
 HP Mixers are available for the above ANZ's to 40GHz  
 TEK 492 - 50KHz - 18GHz Opt 1+2 - £4k-£4.2k.  
 TEK 492 - 50KHz - 18GHz Opt 1+2+3 - £4.5k.  
 TEK 492P - 50KHz - 21 GHz Opt 1+2+3 - £5k.  
 TEK 494AP 1KCs - 21 GHz - £7k.  
 TEK 496P 1KHz-1.8GHz - £4k.  
 TEK 5L4N 0-100KHz - £400.  
 TEK 7L5 + L1 - 20Hz-5Mc/s - £700.  
 TEK 7L5 + L3 - Opt 25 Tracking Gen - £900.  
 TEK 7L12 - 100KHz-1800Mc/s - £1000.  
 TEK 7L18 - 1.5-60GHzS - £1500.  
 TEK 491 10Mc/s-12.4GHzS-40GHzS - £750. 12.4GHzS-40GHzS with Mixers.  
 Tektronix Mixers are available for above ANZ to 60GHzS  
 Systron Donner 763 Spectrum ANZ + 4745B Preselctor .01-18GHz + Two Mixers 18-40GHz in Transit Case - £3k.  
 HP8673D Signal Generator .05-26.5GHz - £20k.  
 Systron Donner 1618B Microwave AM FM Synthesizer 50Mc/s 2-18GHzS  
 R&S SWP Sweep Generator Synthesizer AM FM 24-2500Mc/s - £3.5k.  
 ADRETT 3310A FX Synthesizer 300Hz-60Mc/s - £600.  
 HP8640A Signal Generators - 1024Mc/s - AM FM - £800.  
 HP3717A 70Mc/s Modulator - Demodulator - £500.  
 HP8651A RF Oscillator 22KCs - 22Mc/s.  
 HP5316B Universal Counter A+B.  
 HP6002A Power Unit 0-5V 0-10A 200W.  
 HP6825A Bipolar Power Supply Amplifier.  
 HP461A-465A-467A Amplifiers.  
 HP81519A Optical Receiver DC-400Mc/s.  
 HP Plotters 7470A-7475A.  
 HP3770A Amplitude Delay Distortion ANZ.  
 HP3770B Telephone Line Analyser.  
 HP8182A Data Analyser.  
 HP59401A Bus System Analyser.  
 HP6260B Power Unit 0-10V 0-100 Amps.  
 HP3782A Error Detector.  
 HP3781A Pattern Generator.  
 HP3730A+3737A Down Converter Oscillator 3.5-6.5GHz.  
 HP Microwave Amps 491-492-493-494-495-1GHz-12.4GHz - £250.  
 HP105B Quartz Oscillator - £400.  
 HP5087A Distribution Amplifier.  
 HP6034A System Power Supply 0-60V 0-10A-200W - £500.  
 HP6131C Digital Voltage Source + 100V 1/2 Amp.  
 HP4275A Multi Frequency L.C.R. Meter.  
 HP3779A Primary Multiplex Analyser.  
 HP3779C Primary Multiplex Analyser.  
 HP8150A Optical Signal Source.  
 HP1630G Logic Analyser.  
 HP5316A Universal Counter A+B.  
 HP5335A Universal Counter A+B+C.  
 HP59501B Isolated Power Supply Programmer.  
 HP8901A Modulation Meter AM - FM - also 8901B.  
 HP5370A Universal Time Interval Counter.  
 Marconi TF2370 - 30Hz-110Mc/s 750HM Output (2 BNC Sockets + Resistor for 500HM MOD with Marconi MOD Sheet supplied - £650.  
 Marconi TF2370 30Hz-110Mc/s 50 ohm Output - £750.  
 Marconi TF2370 as above but late type - £850.  
 Marconi TF2370 as above but late type Brown Case - £1000.  
 Marconi TF2374 Zero Loss Probe - £200.  
 Marconi TF2440 Microwave Counter - 20GHz - £1500.  
 Marconi TF2442 Microwave Counter - 26.5GHz - £2k.  
 Marconi TF2305 Modulation Meter - £2.3k.  
 Rascal/Dana 2101 Microwave Counter - 10Hz-20GHz - £2k.  
 Rascal/Dana 1250-1261 Universal Switch Controller + 200Mc/s PI Cards.  
 Rascal/Dana 9303 True RMS Levelmeter + Head - £450. IFFE - £500.  
 TEKA6902A also A6902B Isolator - £300-£400.  
 TEK 1240 Logic Analyser - £400.  
 TEK FG5010 Programmable Function Generator 20Mc/s - £600.  
 TEK2465A 350Mc/s Oscilloscope - £2.5k + probes - £150 each.  
 TEK CT-5 High Current Transformer Probe - £250.  
 TEK J16 Digital Photometer + J6523-2 Luminance Probe - £300.  
 TEK J16 Digital Photometer + J6503 Luminance Probe - £250.  
 ROTEK 320 Calibrator + 350 High Current Adaptor AC-DC - £500.  
 FLUKE 5102B AC-DC Calibrator - £4k.  
 FLUKE 1120A IEE - 488 Translator - £250.  
 Tinsley Standard Cell Battery 5644B - £500.  
 Tinsley Transportable Voltage Reference - £500.  
 FLUKE Y520 Current Shunt - £150.  
 HP745A+746A AC Calibrator - £600.  
 HP8080A MF + 8091A 1GHz Rate Generator + 8092A Delay Generator + Two 8093A 1GHz Amps + 15400A - £800.  
 HP54200A Digitizing Oscilloscope.  
 HP11729B Carrier Noise Test Set .01-18GHz - LEF - £2000.  
 HP3311A Function Generator - £300.  
 Marconi TF2008 - AM-FM signal generator - also sweeper - 10Kcs - 510Mc/s - from £250 - tested to £400 as new with manual - probe kit in wooden carrying box.  
 HP Frequency comb generator type 8406 - £400.  
 HP Vector Voltmeter type 8405A - £400 new colour.  
 HP Sweep Oscillators type 8690 A & B + plug-ins from 10Mc/s to 18GHz also 18-40GHz. P.O.R..  
 HP Network Analyzer type 8407A + 8412A + 8501A - 100Kcs - 110Mc/s - £500 - £1000.  
 HP Amplifier type 8447A - 1-400Mc/s £200 - HP8447A Dual - £300.  
 HP Frequency Counter type 5340A - 18GHz £1000 - rear output £800.  
 HP 8410 - A - B - C Network Analyzer 110Mc/s to 12GHz or 18GHz - plus most other units and displays used in this set-up - 8411a - 8412 - 8413 - 8414 - 8418 - 8740 - 8741 - 8742 - 8743 - 8746 - 8650. From £1000.  
 Rascal/Dana 9301A - 9302 RF Millivoltmeter - 1.5-2GHz - £250-£400.  
 Rascal/Dana Modulation Meter type 9009 - 8Mc/s - 1.5GHz - £250.  
 Marconi RCL Bridge type TF2700 - £150.  
 Marconi/Saunders Signal Sources type - 6058B - 6070A - 6055A - 6059A - 6057A - 6056 - £250-£350. 400Mc/s to 18GHz.  
 Marconi TF1245 Circuit Magnification meter + 1246 & 1247 Oscillators - £100-£300.  
 Marconi microwave 6600A sweep osc., mainframes with 6650 PI - 18-26.5GHz or 6651 PI - 26.5-40GHz - £1000 or PI only £600. MF only £250.  
 Marconi distortion meter type TF2331 - £150. TF2331A - £200.  
 Tektronix Plug-Ins 7A13 - 7A14 - 7A18 - 7A24 - 7A26 - 7A11 - 7M11 - 7S11 - 7D10 - 7S12 - S1 - S2 - S6 - S52 - PG506 - SC504 - SG502 - SG503 - SG504 - DC503 - DC508 - DD501 - WR501 - DM501A - FG501A - TG501 - PG502 - DC505A - FG504 - 7B80 + 85-7B92A  
 Gould J3B test oscillator + manual - £150.  
 Tektronix Mainframes - 7603 - 7623A - 7613 - 7704A - 7844 - 7904 - TM501 - TM503 - TM506 - 7904A - 7834 - 7623 - 7633.  
 Marconi 6155A Signal Source - 1 to 2GHz - LED readout - £400.  
 Barr & Stroud Variable filter EF3.0.1Hz - 100Kcs + high pass + low pass - £150.  
 Marconi TF2163S attenuator - 1GHz. £200.  
 Farnell power unit H60/50 - £400 tested. H60/25 - £250.  
 Rascal/Dana 9300 RMS voltmeter - £250.  
 HP 8750A storage normalizer - £400 with lead + S.A or N.A Interface.  
 Marconi TF2330 - or TF2330A wave analysers - £100-£150.  
 Tektronix - 7514 - 7T11 - 7S11 - 7S12 - S1 - S2 - S39 - S47 - S51 - S52 - S53 - 7M11.  
 Marconi mod meters type TF2304 - £250.  
 HP 5065A rubidium vapour FX standard - £1.5k.  
 Systron Donner counter type 6054B - 20Mc/s - 24GHz - LED readout - £1k.  
 Rascal/Dana 9083 signal source - two tone - £250.  
 Systron Donner - signal generator 1702 - synthesized to 1GHz - AM/FM - £600.  
 Tektronix TM515 mainframe + TM5006 mainframe - £450 - £850.  
 Farnell electronic load type RB1030-35 - £350.  
 Rascal/Dana counters - 9904 - 9905 - 9906 - 9915 - 9916 - 9917 - 9921 - 50Mc/s - 3GHz - £100-£450 - all fitted with FX standards.  
 HP4815A RF vector impedance meter c/w probe - £500-£600.  
 Marconi TF2092 noise receiver. A, B or C plus filters - £100-£350.  
 Marconi TF2091 noise generator. A, B or C plus filters - £100-£350.  
 Marconi 2017 S/G 10KHz - 1024MHz.  
 HP180TR, HP182T mainframes £300-£500.  
 Philips panoramic receiver type PM750 - 1 to 20GHz - £400.  
 Marconi 6700A sweep oscillator + 18GHz PI's available.  
 HP8505A network ANZ + 8503A S parameter test set + 8501A normalizer - £4k.  
 HP8505 network ANZ 8505 + 8501A + 8503A.  
 Rascal/Dana VLF frequency standard equipment. Tracer receiver type 900A + difference meter type 527E + rubidium standard type 9475 - £2750.  
 HP signal generators type 626 - 628 - frequency 10GHz - 21GHz.  
 HP 432A - 435A or B - 436A - power meters + powerheads - Mc/s - 40GHz - £200-£1000.  
 Bradley oscilloscope calibrator type 192 - £600.  
 HP8614A signal generator 800Mc/s - 2.4GHz. new colour £400.  
 HP8616A signal gen 1.8GHz - 4.5GHz. new colour £400.  
 HP 3325A syn function gen 20Mc/s - £1500.  
 HP 3336A or B syn level generator - £500-£600.  
 HP 3586B or C selective level meter - £750-£1000.  
 HP 3575A gain phase meter 1Hz - 13Mc/s - £400.  
 HP 8683D S/G microwave 2.3 - 13GHz - opt 001 - 003 - £4.5k.  
 HP 8660 A-B-C syn S/G. AM + FM + 10Kcs to 110Mc/s PI - 1Mc/s to 1300Mc/s - 1Mc/s to 2600Mc/s - £500-£2000.  
 HP 8640B S/G AM-FM 512Mc/s or 1024Mc/s. Opt 001 or 002 or 003 - £800-£1250.  
 HP 86222BX Sweep PI - 01 - 2.4GHz + ATT - £1750.  
 HP 8629A Sweep PI - 2 - 18GHz - £1000.  
 HP 86290B Sweep PI - 2 - 18GHz - £1250.  
 HP 86 Series PI's in stock - splitband from 10Mc/s - 18.6GHz - £250-£1k.  
 HP 8620C Mainframe - £250. IEEE - £500.  
 HP 8615A Programmable signal source - 1MHz - 50Mc/s - opt 002 - £1k.  
 HP 8601A Sweep generator .1 - 110Mc/s - £300.  
 HP 3488A HP - IB switch control unit - £500 + control modules various - £175 each.  
 HP 8160A 50Mc/s programmable pulse generator - £1000.  
 HP 853A MF ANZ - £1.5k.  
 HP 8349A Microwave Amp 2 - 20GHz Solid state - £1500  
 HP 3585A Analyser 20Hz - 40Mc/s - £4k.  
 HP 8569B Analyser .01 - 22GHz - £5k.  
 HP 3580A Analyser 5Hz - 50kHz - £1k.  
 HP 1980B Oscilloscope measurement system - £600.  
 HP 3455A Digital voltmeter - £500.  
 HP 3437A Digital voltmeter - £300.  
 HP 3581C Selective voltmeter - £250.  
 HP 6370A Universal time interval counter - £450.  
 HP 5335A Universal counter - 200Mc/s - £500.  
 HP 5328A Universal counter - 500Mc/s - £250.  
 HP 6034A System power supply - 0 - 60V - 0 - 10 amps - £500.  
 HP 5150A Thermal printer - £250.  
 HP 1645A Data error analyser - £150.  
 HP 4437A Attenuator - £150.  
 HP 3717A 70Mc/s modulator - £400.  
 HP 3710A - 3715A - 3716A - 3702B - 3703B - 3705A - 3711A - 3791B - 3712A - 3793B microwave link analyser - P.O.R.  
 HP 3730A + B RF down converter - P.O.R.  
 HP 3552A Transmission test set - £400.  
 HP 3763A Error detector - £500.  
 HP 3764A Digital transmission analyser - £600.  
 HP 3770A Amp delay distortion analyser - £400.  
 HP 3780A Pattern generator detector - £400.  
 HP 3781A Pattern generator - £400.  
 HP 3781B Pattern generator (bell) - £300.  
 HP 3782A Error detector - £400.  
 HP 3782B Error detector (bell) - £300.  
 HP 3785A Jitter generator + receiver - £750-£1k.  
 HP 8006A Word generator - £100-£150.  
 HP 8016A Word generator - £250.  
 HP 8170A Logic pattern generator - £500.  
 HP 59401A Bus system analyser - £350.  
 HP 59500A Multiprogrammer HP - IB - £300.  
 Philips PM5390 RF syn - 0.1 - 1GHz - AM + FM - £1000.  
 S.A. Spectral Dynamics SD345 spectroscope 111 - LF ANZ - £1500.  
 Tektronix R7912 Transient waveform digitizer - programmable - £400.  
 Tektronix TR503 + TM503 tracking generator 0.1 - 1.8GHz - £1k - or TR502.  
 Tektronix 576 Curve tracer + adaptors - £300.  
 Tektronix 577 Curve tracer + adaptors - £900.  
 Tektronix 1502/1503 TDR cable test set - £1000.  
 Tektronix AM503 Current probe + TM501 m/frame - £1000.  
 Tektronix SC501 - SC502 - SC503 - SC504 oscilloscopes - £75-£350.  
 Tektronix 465 - 465B - 475 - 2213A - 2215 - 2225 - 2235 - 2245 - 2246 - £250-£1000.  
 Kikusui 100Mc/s Oscilloscope COS6100M - £350.  
 Nicolet 3091 LF oscilloscope - £400.  
 Rascal 1991 - 1992 - 1988 - 1300Mc/s counters - £500-£900.  
 Fluke 80K-40 High voltage probe in case - BN - £100.  
 Rascal Recorders - Store 4 - 4D - 7 - 14 channels in stock - £250 - £500.  
 Rascal Store Horse Recorder & control - £400-£750 Tested.  
 EIP 545 microwave 18GHz counter - £1200.  
 Fluke 510A AC ref standard - 400Hz - £200.  
 Fluke 355A DC voltage standard - £300.  
 Wiltron 610D Sweep Generator + 6124C PI - 4 - 8GHz - £400.  
 Wiltron 610D Sweep Generator + 61084D PI - 1Mc/s - 1500Mc/s - £500.  
 Time Electronics 9814 Voltage calibrator - £750.  
 Time Electronics 9811 Programmable resistance - £600.  
 Time Electronics 2004 D.C. voltage standard - £1000.  
 HP 8699B Sweep PI YIG oscillator .01 - 4GHz - £300. 8690B MF - £250. Both £150.  
 Schlumberger 1250 Frequency response ANZ - £1500.  
 Dummy Loads & power att to 2.5 kilowatts FX up to 18GHz - microwave parts new and ex equip - relays - attenuators - switches - waveguides - Vigs - SMA - APC7 plugs - adaptors.  
 B&K items in stock - ask for list.  
 W&G items in stock - ask for list.  
 Power Supplies Heavy duty + bench in stock - Farnell - HP - Weir - Thurlby - Rascal etc. Ask for list.

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. SAE FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS, AVAILABILITY OR PRICE CHANGE. VAT AND CARRIAGE EXTRA  
 ITEMS MARKED TESTED HAVE 30 DAY WARRANTY. WANTED: TEST EQUIPMENT-VALVES-PLUGS AND SOCKETS-SYNCRDS-TRANSMITTING AND RECEIVING EQUIPMENT ETC.

**Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. No: (01274) 684007. Fax: 651160**

**CIRCLE NO. 144 ON REPLY CARD**


Finally an upgradeable PCB CAD system to suit any budget ...

# Board Capture

## BoardCapture - Schematic Capture

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

**£395**

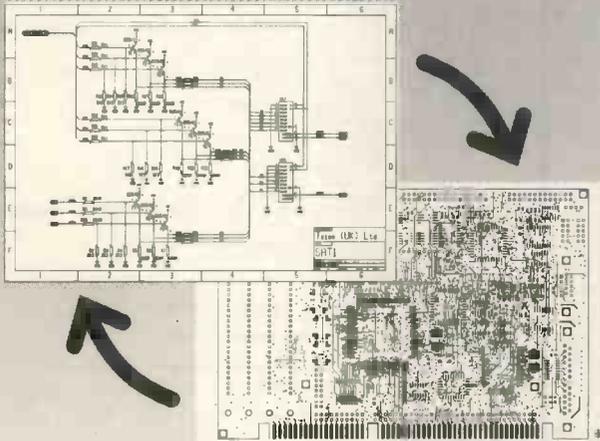

# Board Maker

## BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

**£95**

## BoardMaker2 - Advanced level

- All the features of BoardMaker1 plus
- Full netlist support - OrCad, Schema, Tango, CadStar
- Full Design Rule Checking - mechanical & electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC

**£395**

# Board Router

## BoardRouter - Gridless autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

**£200**

## Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec, Roland & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill / Annotated drill drawings (BM2)

Contact Tsien for further information on  
Tel 01354 695959  
Fax 01354 695957



**tsien**

Tsien (UK) Ltd Aylesby House Wenny Road Chatteris Cambridge PE16 6UT

All trademarks acknowledged

CIRCLE NO. 145 ON REPLY CARD

# KESTREL ELECTRONIC COMPONENTS LTD

- ☆ All items guaranteed to manufacturers' spec.
- ☆ Many other items available.

'Exclusive of V.A.T. and post and package'

	1+	100+		1+	100+
27C64-15	2.60	1.80	628128LP-85	8.30	7.20
27C128-15	2.40	1.80	62256LP10	3.00	2.60
27C256-15	2.20	1.70	6264LP-10	2.10	1.45
27C512-15	2.20	1.70	MM58274CN	4.90	3.75
27C010-15	3.95	2.80	ULN2003A	0.43	0.30
27C020-15	6.00	4.25	7805	0.32	0.25
27C040-15	8.60	6.45	MAX232	1.35	0.88
80C31-12	2.10	1.65	7406	0.35	0.23
8255AC-2	2.00	1.45	7407	0.35	0.23
Z80A CPU	1.80	1.00	74HC244	0.35	0.24
LM386N-3	0.50	0.35	74HC245	0.35	0.24
75176BP	1.35	0.85	74HC373	0.35	0.25
68w PLCC skt	0.90	0.70	74HC374	0.32	0.25

74LS, 74HC, 74HCT Series available

Phone for full price list

All memory prices are fluctuating daily, please phone to confirm prices

178 Brighton Road,  
Purley, Surrey CR8 4HA

Tel: 0181-668 7522. Fax: 0181-668 4190.

CIRCLE NO. 146 ON REPLY CARD

## 'OFF-AIR' FREQUENCY STANDARD



Variants from  
**£195+VAT**

- ★ Provides 10MHz, 5MHz & 1MHz
- ★ Use it for calibrating equipment that relies on quartz crystals, TCXOs, VXCOs, oven crystals
- ★ Phase locks to DROITWICH (rubidium controlled and traceable to NPL)
- ★ For ADDED VALUE also phase locks to ALLOUIS (cesium controlled and traceable to OP - French eq to NPL)
- ★ British designed and British manufactured
- ★ Options available include enhanced receiver, sine wave outputs and 13MHz output for GSM. Prices on application.

Output frequencies - 10MHz, 5MHz, 1MHz  
Short term stability - better than  $1 \times 10^{-9}$  (1 sec)  
Typical -  $4 \times 10^{-9}$  (1 sec)  
Long term - tends to  $2 \times 10^{-12}$  (1000 sec)  
Call for 'Off-Air' Standard list

## TEST EQUIPMENT

We are well known for our quality, new and used Test Equipment. Our list is extensive, the following will give some idea of our range and prices:

TIME 404S Precision mV source	£95	FEEDBACK SSO603 1MHz sine/square oscillator	£125
TIME 2003N DCV Pot/Cal, 0-10V, null, etc	£249	FEEDBACK DPM609 10Hz-100kHz phase meter	£125
TIME 2004 DC Volt standard 0.005%	£945	TEKTRONIX 2215 60MHz dual trace, dual delay T/B	£450
TRACOR B90A 60kHz/75kHz tracking Fx	£95	TEKTRONIX 2455 300MHz 4 trace, dual delay T/B	£1950
FLUKE 8012A 3.5 digit led, ac/dc/V/I/Ω	£149	GOULD OS3000A 40MHz dual trace, dual delay T/B	£249
FLUKE 8600A 3.5 digit led, ac/dc/V/I/Ω	£59	HITACHI V222 20MHz dual trace, TV Trig	£249
KEITHLEY 197A 4.5 digit led, ac/dc to 1kV	£149	MARCONI TF2370 100MHz spectrum analyser	£995
ADVANCE VM78 ac 1mV to 300V, up to 1MHz	£25	ADRETE 740A 0.1MHz-1.2GHz sig. gen. AM/FM/PM	£1450
MARCONI TF2600B video vm 300V, to 10MHz	£75	FLUKE 931B AC rms/differential voltmeter, 0-1kV ac	£95
MARCONI TF2183 DC to 1GHz attenuator	£195	BRYANS BS272 2 pen 10cm/min to 10mm/hr	£95
E.V. EV4020A NTSC V/scope	£395	GOULD 2400 8 pen 5mm/sec to 200mm/min	£125
LEADER LG396 NTSC pattern generator	£395	VIGILANT SR532 10kHz-30MHz, AM/CW/SSB, PLL	£1250
PHILIPS 5509 PAL pattern generator	£195	VIGILANT SR510 10kHz-30MHz, AM/CW/SSB, PLL	£750
PHILIPS PM5716 pulse generator	£495	EDDYSTONE EC10 150kHz to 30MHz, AM/CW/SSB	£125
PHILIPS PM5134 function generator	£1495	RACAL RA17 0.5 to 30MHz AM/CW/SSB/NL	£149
MARCONI TF2700 universal LCR bridge	£195	DRAKE MN2700 ATU/PSU	£380
AVO CZ457/5 component comparator	£95	DIGITAL LNO3 Serial Laser Printer	£249
PHILIPS 8833 Mk 2 RBG, comp, sound	£99	DIGITAL MicroVAX II 9 V T220 terminals, Hubs, S/W	£POA

Call for Equipment list



**HALCYON ELECTRONICS**



423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR  
SHOP HOURS 9-5.30 MON-SAT. TEL 0181-542 6383. FAX 0181-542 0340

CIRCLE NO. 147 ON REPLY CARD

# Predicting fm

# NOISE

# NOISE

## effects

**W**hy fm? Frequency modulation, carrying data, audio or television, is very popular. Its advantages are,

- bandwidth is controlled simply by adjusting deviation to set spectral occupancy. A minimum of twice the highest baseband modulating frequency is needed.
- constant envelope – no amplitude component – means a linear transmitter is unnecessary; frequency multipliers can be used with no distortion to the signal. Carrier harmonics must be filtered out in the usual way.
- hardware implementation is straight forward. Only amplitude modulation with super-regenerative demodulation provides a simpler option.

Noise level is independent of deviation. As a result, signal-to-noise ratio can be improved arbitrarily by simply increasing deviation, and hence the signal level in the numerator of the s-n ratio. Limits to this are firstly regulatory.

Increased deviation widens occupied rf bandwidth according to Carsons's rule (of thumb), which gives bandwidth as twice highest modulating frequency plus the peak to peak deviation.

In the UK, the Radiocommunications Agency – part of the DTI – issues performance specifications called 'MPTs'. These include limits of adjacent channel power, spectral occupancy etc. In principle, increasing deviation will incur a greater cost as rf spectrum is auctioned off.

Secondly as deviation is increased a technical difficulty arises; the threshold effect destroys the integrity of the fm system and no useful output is produced. The margin above threshold is an important operational system parameter.

*Everyone knows that noise affects integrity in fm data communications – but by how much? Simon Day discusses the problem.*


### Improving performance

With deviation set according to the criteria above, the system quality – s-to-n ratio – can only be improved by reducing the noise level.

Many factors contribute, including received carrier level, the noise figure of the receiver rf front end, baseband filtering after demodulation and transmitter modulator residual fm, i.e. ssb phase noise. De-emphasis and local oscillator residual fm also play a role.

A key receiver parameter, which does not affect noise level directly, is receiver IF

*Fig. 1. This fm-if spectrum of carrier entering a demodulator shows that components far away from the carrier are removed by baseband filtering.*

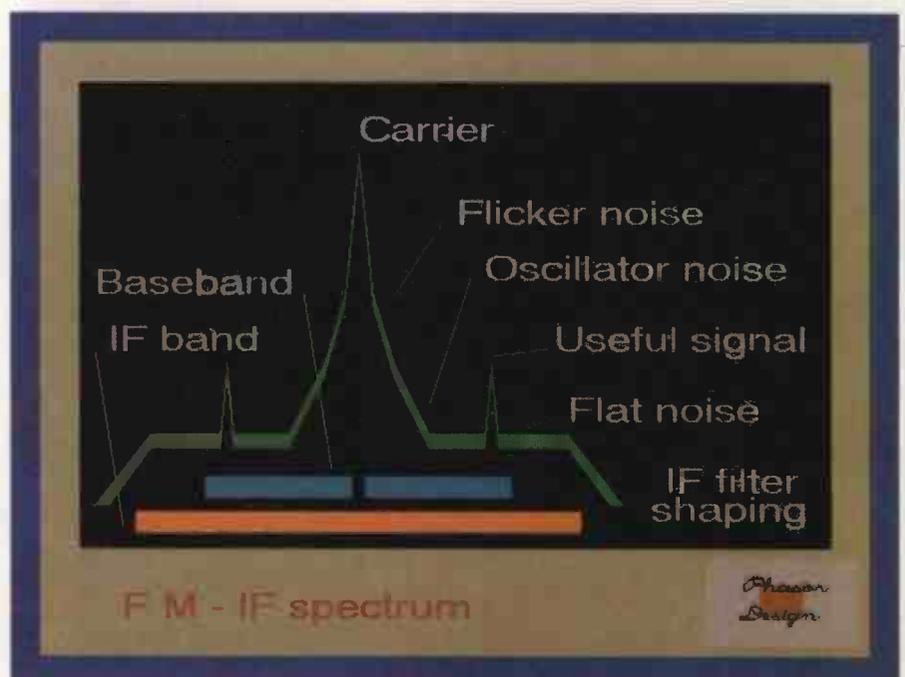

**Software availability**


*FM Noise Analysis* is available from Phasor Design at 16 Blenheim Way, Market Harborough, Leicestershire LE16 7LQ. Tel. 01858 432148, fax 432109. It is priced at £119 excluding VAT.

bandwidth when above threshold.

Two additional factors relate to the measurement of noise. In audio and video systems, standard weighting networks are used. These modify the noise frequency distribution to represent the way noise is perceived by the ear or eye. The weighting networks may have gain so actually increasing the noise level. Mainly, rms detection is used to meter noise; audio systems are an exception, where average reading detection was promoted by Dolby

Fig. 2. Phasor diagram – geometrical representation of a noise element, top photo.

Fig. 3. Graphical output of the spectrum analyser connected to a receiver output – part of a typical satellite-television simulation.

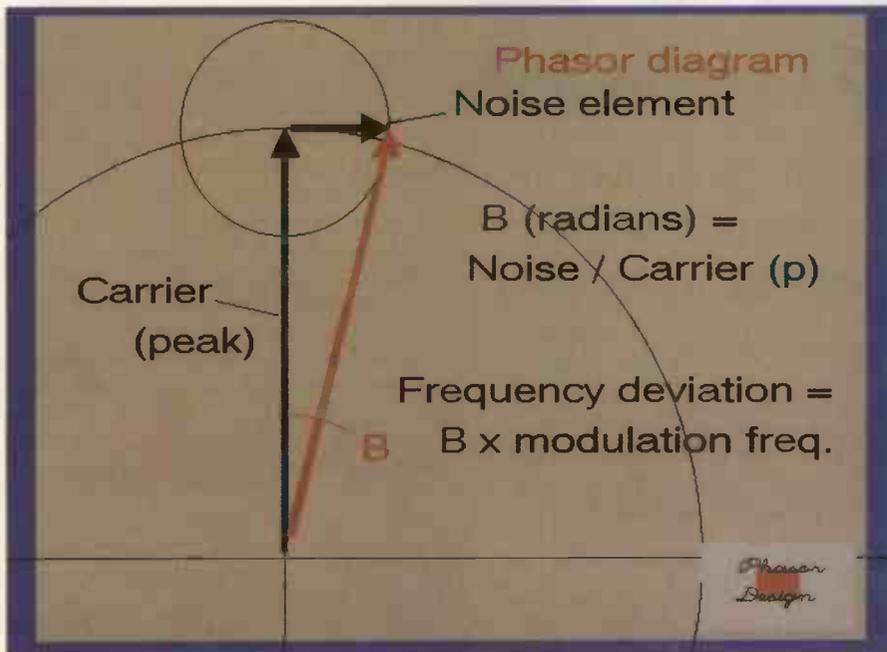

Laboratories. This seems to have been accepted for domestic equipment; broadcast and professional noise measurements often use the CCIR 468-4 quasi-peak method which is accepted as reading about 5dB higher than rms.

**Modelling noise**

Fundamentally noise arises because the pure carrier becomes embedded in unwanted elements. These are resolved by the fm demodulator as baseband voltages. These elements are either noise sidebands originating in oscillators or 'link noise' caused by the carrier falling to the noise floor. Figure 1 shows the situation entering the demodulator.

An important difference between oscillator and link noise – not visible in the IF spectrum – is the coherence between lower and upper sidebands. Most oscillators have little amplitude modulation noise so coherence exists. Link noise has no coherence and so half of this noise power is rejected by the fm receiver which is insensitive to amplitude modulation.

A geometrical representation of one noise element is illustrated in Fig. 2. The claim that IF bandwidth is not a factor above threshold is supported by Fig. 1 – the IF spectrum – which shows the noise components far away from the carrier are removed by baseband filtering.

**CAD tools**

A pc application called *FM Noise Analysis* from Phasor Design brings all these points together to predict s-to-n ratio in real systems. Figure 3 is the graphical output forming a detailed simulation of the spectrum analyser connected to the receiver output.

FM system deficiencies can be quickly resolved by comparing experimental and predicted spectra. Signal-to-noise ratio is calculated by numerical integration and displayed, along with probability of a bit error for an fsk system.

A typical satellite television simulation is shown in Fig. 3; emphasis to CCIR Rec.405 for system I, and 200ns weighting are included along with transmitter and receiver oscillator noise contributions.

*FM Noise Analysis* is a software tool specifically developed to help engineers get the best from fm systems. Its design philosophy is to minimise learning time and provide a direct and clear way for the engineer to simulate and verify the noise performance of their communications system. It is based on actual engineering experience of optimising frequency modulated systems operating between 1MHz and 18GHz. ■

**PC requirements**

- PC with 640K main memory
- Dos 3.1 or higher
- Printer port (for software key)
- In addition, VGA monitor with colour printer are recommended.

# LOW COST DEVELOPMENT SYSTEM

ECAL comprises a versatile relocatable assembler with integral editor which runs about ten times faster than typical assemblers. Support includes 4, 8, 16 & 32 bit processor families including 75X, 6502, 6809, 68HC05/11, 8031/51, H8-300, 78K, PICs, ST6 & Z80/180, 68000, 80C196, H8-500 & Z280.

ECAL is either available for a single processor family or all families.

Single processor version £295  
Multiprocessor version.... £395

Overseas  
distributors  
required

**OEMA Ltd.,**


7 & 7A Brook Lane,

Warsash,

Southampton SO31 9FH

Tel: 01489 571300

Fax: 01489 885853

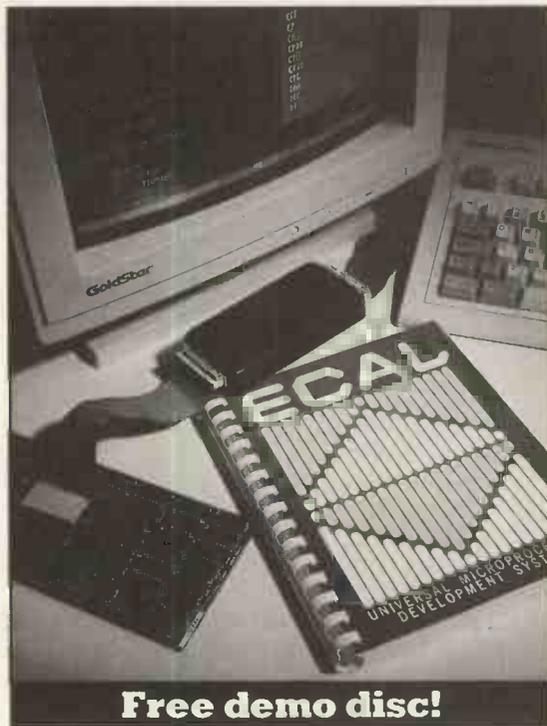

**Free demo disc!**

The PC based ECAL hardware emulator is fully integrated with the assembler. Connection is made to the target through the eeprom socket so a single pod can support all processors. Facilities include windows for the inspection or change of registers or memory. You can even watch your program executing at source level!

Download time is about two seconds!

Pods can be daisy-chained for 16/32 bit systems.

Applications include software development, hardware debug, test and, finally, teaching about micro-controllers in education.

ECAL emulator ..... £475

**Quantity discounts of up to 50% make ECAL software ideal for education.**

CIRCLE NO. 148 ON REPLY CARD

## LANGREX SUPPLIES LTD

PHONE 0181 684 1166  
DISTRIBUTORS OF ELECTRONIC VALVES  
TUBES, SEMICONDUCTORS AND I.C.S.  
1 MAYO ROAD • CROYDON • SURREY CR0 2QP  
24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS

PHONE	FAX
0181 684 1166	0181 684 3056
AZ31	5.00
CBL31	£12.50
CL33	10.00
DY86/7	1.50
E88CC Mull	8.50
E180F	3.50
E810F	22.00
E8BC80	2.00
EB91	1.50
EBF80	1.50
EBF89	1.50
E8L31	15.00
ECC33	7.50
ECC35	7.50
ECC81	3.00
ECC82	3.00
ECC83	3.50
ECC85	3.50
ECC88 Mull	6.00
ECC91	2.00
ECC90	1.50
ECN35	3.50
ECN42	3.50
ECN81	3.00
ECN80	1.50
ECN82	3.00
ECN83	3.00
ECN83 Mull	3.50
ECN85	3.50
ECN86 Mull	25.00
EF37A	3.50
EF39	2.75
EF40	5.00
EF41	3.50
EF42	4.50
EF80	1.50
EF85	1.50
EF86	7.50
EF91	2.00
EF92	2.50
EF183	2.00
EF184	2.00
EL32	2.50
EL33	10.00
EL34 Siemens	8.00
EL36	4.00
EL41	3.50
EL80	25.00
EL81	5.00
EL84	2.25
EL84 Mull	6.00
EL86	2.75
EL91	3.00
EL95	2.00
EL360	18.50
EL509	12.00
EM34	15.00
EM81	4.00
EM84	4.00
EM87	4.00
EN91 Mull	7.50
EY51	1.50
EY86	1.75
EY88	1.75
EY81	3.50
EY82	3.50
EY83	3.50
EY84	3.50
EY85	3.50
EY86	3.50
EY87	3.50
EY88	3.50
EY89	3.50
EY90	3.50
EY91	3.50
EY92	3.50
EY93	3.50
EY94	3.50
EY95	3.50
EY96	3.50
EY97	3.50
EY98	3.50
EY99	3.50
EY00	3.50
EY01	3.50
EY02	3.50
EY03	3.50
EY04	3.50
EY05	3.50
EY06	3.50
EY07	3.50
EY08	3.50
EY09	3.50
EY10	3.50
EY11	3.50
EY12	3.50
EY99	3.50
EY00	3.50
EY01	3.50
EY02	3.50
EY03	3.50
EY04	3.50
EY05	3.50
EY06	3.50
EY07	3.50
EY08	3.50
EY09	3.50
EY10	3.50
EY11	3.50
EY12	3.50
EY99	3.50
EY00	3.50
EY01	3.50
EY02	3.50
EY03	3.50
EY04	3.50
EY05	3.50
EY06	3.50
EY07	3.50
EY08	3.50
EY09	3.50
EY10	3.50
EY11	3.50
EY12	3.50
EY99	3.50
EY00	3.50
EY01	3.50
EY02	3.50
EY03	3.50
EY04	3.50
EY05	3.50
EY06	3.50
EY07	3.50
EY08	3.50
EY09	3.50
EY10	3.50
EY11	3.50
EY12	3.50
EY13	3.50
EY14	3.50
EY15	3.50
EY16	3.50
EY17	3.50
EY18	3.50
EY19	3.50
EY20	3.50
EY21	3.50
EY22	3.50
EY23	3.50
EY24	3.50
EY25	3.50
EY26	3.50
EY27	3.50
EY28	3.50
EY29	3.50
EY30	3.50
EY31	3.50
EY32	3.50
EY33	3.50
EY34	3.50
EY35	3.50
EY36	3.50
EY37	3.5

# TELFORD ELECTRONICS

## OSCILLOSCOPES

Gold OS250A 15MHz Dual Trace	£120
SE Labs 111 18MHz Dual Trace	£85
Tequipment D1011R 10MHz Dual Trace	£75
Tequipment DM63 50MHz 4 Trace storage	£150
Trio CS1586A 20MHz Dual Trace	£150
Cosser C00150 35MHz Dual Trace	£95
HP 740A 100MHz Dual Trace/storage	£150
HP180A - 180MHz + 1821A 50MHz	£150
HP1742A 100MHz Dual Trace/storage	£150
Tektronik 453 100MHz Dual Trace	£150
Tektronik 465 100MHz Delay sweep/Dual Trace	£375
Tektronik 7854 c/w 7511 plug-in/7111 fitted with S1 sampling head 1GHz	£1600
Tektronik 7834 c/w 7925 c2 + 7829A c2 200MHz	£900

## OTHER SCOPES AVAILABLE

<b>SIGNAL GENERATORS</b>	
HP8548 10-50MHz	£400
HP8544 10-50MHz	£350
HP8614A 0.8-2.4GHz signal generator	£300
HP8616A 1.8-4.5GHz signal generator	£400
Marconi TF2015 AM/FM 10MHz-110MHz	£165
Marconi TF2016 AM/FM 10Hz-110MHz	£170
Marconi TF2019 80kHz-1040MHz	£1900
Racal 9081 50MHz synthesized	£480
Racal 9082 1.5-50MHz synthesized	£500
Wavetek 3000 1-50MHz	£250
Wavetek 183 sweep/modulation 20MHz	£380
Wavetek 184 30MHz Sweep generator	£300

## LF OSCILLATORS

Gold J3B 10Hz-100kHz sine/square wave metered: very low distortion	£150
HP4200A 10Hz-1MHz	£150
HP3200B VHF Oscillator	£220
HP851B Test Oscillator	£125
HP203A Variable phase LF generator	£50
Advance M1E 1.5-50MHz sine/square 200u/20V	£300
Radford LD04 Low distortion Oscillator	£300
Radford LDMS22 Low distortion measuring set	£300
Global Specialities 20MHz pulse/LF generator Type: 8201 GPIB	£90A
Philips PM513Z function generator 0.1Hz-2MHz AS NEW	£350
Philips PM5715 pulse generator 1Hz-50MHz	£750
Adnet Type: Z238	£50
Rhode & Schwarz Type: SU7	£200

## POWER SUPPLIES

Farnell TSV70 MIX 0-70V/5A 0-350V/0-10A	£200
Farnell TS70 MIX 0-70V/5A 0-350V/0-10A	£250
HP5111A DC 0-20V 0-1A	£70
HP6291A DC 0-40V 0-5A	£100
HP6281B DC 0-20V 0-50A	£700
HP8002A DC 0-50V 0-10A 200W	£700
HP6298B DC 0-30V 0-0.1A	£75
Lambda PDA22A PM regulated, DC 0-40V/1A x2	£100
Henden Type: 110A/16 0-16V 0-20A	£90A

VARIOUS SWITCH MODE POWER SUPPLIES & HY TRANSFORMERS IN STOCK - PLEASE PHONE

## CALIBRATION EQUIPMENT

Haven temperature calibrator 0785 oil/water bath	£500
Haven thermal i.s. thermocouple simulator/calibrator	£600
Time CD millivolt pot source Model 494M c/w DC current source Model 505	£250
Leader LDC785 Soper calibrator AS NEW	£1200
Casekla W.B.G.T.	£200
PPM 411F Current reference	£250
Cropico resistance standards various in stock from	£75
N. Tinsley resistance bridge Type: 5/61	£750
Bradley AC calibrator type: 1238	£90A
Bradley LF generator digital type: 235	£250
Bradley DC calibrator type: 1238 c/w 126B	£150
Keithley Picocommeter type: 417	£250
Wallace & Tiernan precision pneumatic calibrator	£300
Schwarzbeck HF interference measuring receiver 850Hz-30MHz	£700
Microline telemetry receiver c/w spectrum display unit 2.2-2.3GHz	£700

## DIGITAL & ANALOGUE MULTIMETERS

Avo 8 HKS - 8 c/w case, leads, prods etc. (c/w Cal cert MPL)	From £85
Solartron 7845 4.5 digit bench multimeter battery mains	£50
Avo DA116	£50
Fluke 8000A	£45

## FREQUENCY COUNTERS

HP5342A Microwave 18GHz	£1,400
HP5308A 75MHz counter/timer	£100
HP5305A 110MHz counter	£275
Marconi TF2431 200MHz digital frequency counter	£150
Marconi TF2438 500MHz universal counter/timer	£250
Marconi TF2440 20GHz	£1,300
EIP Type: 331 Microwave 25MHz-18GHz	£850
Racal 9904M 50MHz	£100
Racal 9913 10Hz-200MHz Fitted FX standard	£125
Racal 9914 10Hz-500MHz Fitted FX standard	£125
Racal 9915M 10Hz-500MHz Fitted FX standard	£125
Racal 9916 10Hz-500MHz Fitted FX standard	£125
Racal 9917A 10Hz-560MHz Fitted FX standard	£195
Racal 1992 1300MHz	£700
Syrstron Donner 8054B microwave counter 20Hz-18GHz	£850

## REEL TO REEL RECORDERS

Nagra T instrumentation tape recorder	£1,200
Nagra E mono single speed (1/2")	£350
Nagra 1VS-J stereo	£500
HP3964A instrumentation recorder	£600
Racal 4DS	£500
Racal 7DS	£700
EPDA	£90A
Racal Wordsafe 8 track	£100
Dixiphone 2x tape decks	£75
Racal ICR recorder	£100
SE Labs eight-hour	£100
Uher 4200/4400 in stock from	£125

## TRANSMITTING EQUIPMENT

Racal TA1885 Auto tuned HF transmitter freq. 1.6-30MHz 1KW output	£90A
Racal TA1800 HF linear amplifier freq. 2-30MHz 10KW output ALL MODE OP.	£90A
Pye T300AM 68-174MHz 300W output	£350
Redifon GA484 400W solid state amplifier c/w 1KW aerial filter unit/drive unit, PSU	£350
Harris ATU type: 601A 1-30MHz 1KW AS NEW	£650

## MISCELLANEOUS

Datalab D11080 programmable transient recorder	£300
Tektronix 1912 10MHz Storage scope	£175
Roxel AC/DC Precision Calibrator	£300
Racal 9084 Synthesized generator c/w GPIB Interface 9934A (As new condition)	£700
hwatsu SS-5418A Synchroscope DC-40MHz	£350
Roland drafting plotter A2 DPX-2200 Various interfaces: 8 pen	£1200
Roland DG X-Y plotter A3 DXY-980A Various interfaces: 8 pen	£375
Krohn-Hite Filter Model 3202F	£150
Cabletron Systems MR-9800 c/w Lanview Multiport Ethernet/IEEE 802.3 Repeater	£90A
Cabletron Systems FR-3000 c/w Lanview Fibreoptic/IEEE 802.3 Repeater Unit	£90A
Avritsu Channel Selector MS120A	£90A
Bruel & Kjaer Vibration programmer ZH100	£90A
Watkins & Johnson Microwave Tuning Frame MH102A 4-8GHz	£250
Watkins & Johnson Frequency Extender FE2.4.5A 2-4.5GHz	£275
Watkins & Johnson Demodulator DM112.5	£450
Watkins & Johnson (C2) Frequency Extender Unit FE1.4.5A 0.95-2GHz + 2-4.5GHz	£500
Watkins & Johnson Signal Monitor SM9403A	£400
Sullivan Automatic Component Analyzer AC5555	£90A
Yew Digital AC Power Meter 2503	£90A
Alitech Noise Monitor	£90A
Minolta TV Colour Analyzer c/w Probe TV2140	£1250
Phoenix Telecommunications Analyzer 5500A	£90A
2nd Unit, Phoenix 5500-MSU 5500-200	£90A
5500-555 5500A-828	£90A
3rd Unit, Phoenix Control Module 5500-200 + 5500A-828	£90A

The above 3 items come as one unit	£90A
Comex 48-48 Audio Switch Matrix 921B-1	£1200
HP8684B Signal Generator 5-4.125GHz	£3000
Marconi Power Meter 6360 c/w RF Head 6310 10MHz-20GHz	£1100
Racal Dana 1998 Frequency Counter 10Hz-1.3GHz	£900
Racal Dana 9303 True RMS Level Meter c/w Sensing Head 20Hz	£650
EIP Frequency Counter 545 10Hz-18GHz	£1250
Tektronix 78120 Programmable Digitizer	£90A
Bird Tenuline Coaxial Attenuator 30dB 500W 50ohm Model 8325	£90A
Brand New Boxes £200 VARIOUS OTHERS IN STOCK - PLEASE ASK	£90A

## MICROWAVE COAXIAL SWITCHES

"W" Type connectors, R.L.C. Model S-2799	£45
2KW @ 100MHz - 400W @ 5GHz	£40
Teledyne SMA connectors, Model CS38S16	£40
22GHz 1 in - 6 out	£40

## FLEXIBLE COAXIAL CABLE

Can21 size 1/8" 50 ohm approx. 1200M available (NEW)	£90A
<b>SPECIAL OFFER WHILE STOCKS LAST</b>	
HP180 50MHz Dual Trace/Delay timebase with probes	£150

**AN EXTENSIVE RANGE OF TEST EQUIPMENT IS AVAILABLE. PLEASE SEND FOR OUR NEW CATALOGUE**  
 Postage and packing must be added. Please phone for price. VAT @ 17 1/2% to be added to all orders. Please send large SAE for details.  
**Telford Electronics, Old Officers Mess, Hoo Farm, Humbers Lane, Horton, Telford TF6 6DJ**  
**Tel: 01952 605451 Fax: 01952 677978**

CIRCLE NO. 151 ON REPLY CARD



## Mid-Summer Madness

**Our catalogue WAS £2.50 NOW FREE** only the cost of a stamp or a phone call

LARGE RANGE OF COMPONENTS AND ACCESSORIES FROM THE FAR EAST TO THE WESTERN HEMISPHERE INCLUDING TRANSISTORS, SPEAKERS, TOOLS, TEST EQUIPMENT AND MUCH, MUCH MORE

**THINK COMPONENTS - THINK CRICKLEWOOD**

**INC. £30 WORTH OF VOUCHERS**

Please send me a copy of the 1995 Cricklewood Catalogue.

Name.....  
 Address.....  
 EWW

Cricklewood Electronics Ltd, 40-42 Cricklewood Broadway, London NW2 3ET. Tel: 0181-450 0995 Fax: 0181-208 1441

CIRCLE NO. 152 ON REPLY CARD

## HEWLETT PACKARD HP71B

As easy to use as a calculator but as powerful as a computer

**BARCODE READER**  
 Smart wand  
 - Automatically recognises and decodes all major bar-code standards.



- A powerful set of basic functions, statements and operators - over 230 in all - many larger computers don't have a set of basic instructions in this complete.
- Advanced statistics functions enabling computations on up to 15 independent variables.
- Recursive subprograms and user defined functions.
- An advanced internal file system for storing programs and data - the HP71 has continuous memory - when you turn the computer off it retains programs and data.
- A keyboard that can be easily customised for your specific application.
- HP-1L interface pre-installed to create a system that can print, plot, store, retrieve and display information. Control or read instruments or speak to other computers, 5000 bytes/sec. Built In ROM includes 46 separate commands. Interface to HP-1L, HP-1B, RS232C, GPIO or series 80.

These are second user systems ex DHSS are fully tested and working but have no programming (THAT IS UP TO YOU)

HP71B ..... £29.95  
 Bar-code Reader ..... £12.95  
 AC Power Supply ..... £4.95  
 (Works from batteries normally)  
 Keyboard Overlay ..... £1.00  
 (Limited quantities)  
 Unknown Program - Memory Modules ..... £3.00  
 (Limited quantities)  
 Complete kit of HP71B, Bar-code Reader and power supply ..... £39.50  
 (Prices include VAT - delivery £3.00)  
 (Currently selling in USA for US\$500)  
 Allow 7 days for delivery

**SPECIAL OFFER**  
 Buy 2 Kits For £59.00

**Other products at give-away prices**  
 Numeric keypad for 'AT' computer  
**£5 + £2 Carriage** (Carriage FREE if ordered with above).

**INTERCONNECTIONS LTD**  
 Unit 51, InShops, Wellington Centre, Aldershot, Hants GU11 5DB  
 Tel: (01252) 341900 Fax: (01293) 822786

CIRCLE NO. 153 ON REPLY CARD

# Asp and filtering

Continuing his review of analogue signal-processing techniques, Ian Hickman looks at filters and allows digits to make their appearance.

If preservation of the detailed shape of the wanted waveform is important, then some care in choice of filter type is important.

**Low-pass.** For any given order of filter, a Butterworth type gives faster cutoff above the pass-band than a Bessel filter, but it causes ringing on a pulse type of waveform. Figure 1a) compares the response of eight-pole Bessel and Butterworth filters, both with a 10kHz cut-off frequency, to a 3kHz square-wave input.

**High-pass.** These can improve the wanted signal-to-noise ratio in the same way as low-pass filters; for example, to reject mains hum, and its harmonics also, if a higher cut-off frequency is acceptable. However, whereas a suitable low-pass filter type such as Bessel will not cause any ringing or overshoot on a square wave or step function, overshoot seems to be an inherent feature of all high-pass filters of order higher than the first.

Figure 1b) shows a high-pass CR circuit with a step-function input applied, giving the well known decaying output, down to just 37% ( $100/e$ ) of the input after a time interval equal to CR seconds. A series of similar sections are cascaded after the first, giving a high-pass filter with five coincident poles on the real (negative) axis. This is not a good filter design, having an even 'softer' cut-off than a five-pole Bessel, being 15dB down at the 'cut-off' frequency of  $f_c = 1/(2\pi CR)$ , but it aptly illustrates the point.

Figure 1c) shows the response at the output of each stage. As, initially, the input to the sec-

ond stage is positive, its output decays towards zero, opening up an increasing gap between second stage input and output voltages, as shown. When the output voltage of the second stage reaches zero, its input voltage is still falling, causing the output voltage to reverse sign, eventually dying away to zero from below the axis.

A similar argument applies to the third stage except that, as the second stage output finally dies away from a negative value, the third stage output is pushed back across the baseline, dying away from a smaller positive value. If Fig. 1c) were replotted to an expanded vertical, it would be more easily seen that the  $n$ th stage output crosses the zero voltage baseline ( $n-1$ ) times.

Coincident-pole high-pass filter are minimum-phase types, but if you go to a non-minimum phase design, you can have a high-pass filter with a squarer, sharper cut-off than Bessel, but still with constant group delay. Such filters were originally designed for band-pass applications<sup>1</sup>, but the design was extended to high-pass types<sup>2</sup>.


An interesting alternative to the high-pass


filter is the synthesis of a high-pass response by subtracting the output of a low-pass filter from the original signal. At very low frequencies where the output of the low-pass filter is identical to its input, the result is no signal, while at very high frequencies where the output of the low-pass filter is zero, the input signal simply constitutes the output signal.

Less than satisfactory is the part in-between, where the output of the low-pass filter is at an intermediate amplitude and phase-shifted to boot, resulting in partial cancellation, and a slow transition from the stop-band to the pass-band. Nevertheless, the arrangement is attractive, as its implementation calls for a low-pass filter rather than a high-pass type, giving one the choice of a much wider range of ready-made integrated filter circuits.




Such a high-pass filter is illustrated in Fig. 2a,b), which also shows its limitations. For an 8-pole Bessel filter, the attenuation at the cut-off frequency has risen to 3dB and the phase shift has reached 180°. Consequently, the fundamental component of the square wave coming through the low-pass path does not cancel out the same component via the flat path;

Fig. 1a). A 3kHz squarewave (A) emerges from a 10kHz bandwidth, 8-pole Bessel low-pass filter (B) with its edges slowed down B, but otherwise unscathed. By comparison, a similar filter with Butterworth characteristic (C) causes marked ringing. This would be even more pronounced with Chebychev or elliptic Cauer filters. At (b), a 5-pole, high-pass filter consisting of five cascaded, first-order stages, with a step-function input. c) shows the response at each of the five outputs, showing that the  $n$ th output crosses the zero voltage baseline  $n-1$  times.

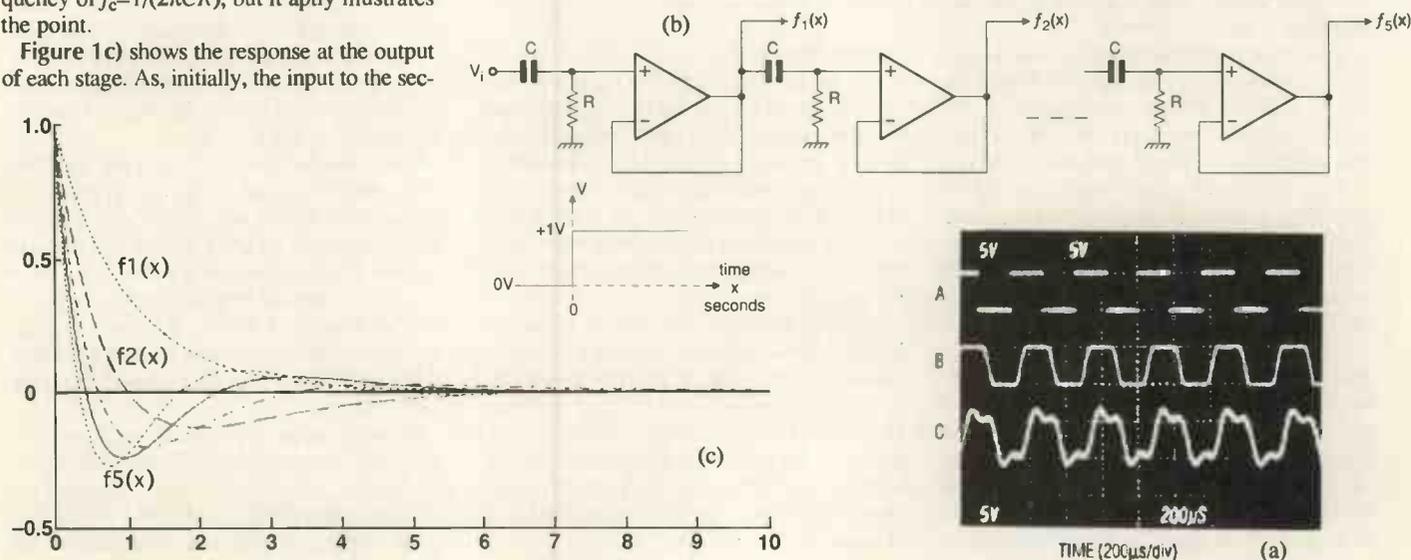

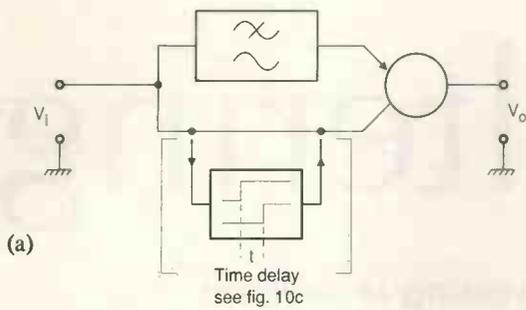

**Fig. 2a).** High-pass response implemented with a low-pass filter. Circuit b) is a filter as in a). Low-pass filter was a MAX292 8-pole Bessel type with its internal clock set for 1kHz cut-off. 1kHz squarewave at c) is applied to high-pass filter b). Far from cancelling out the fundamental of the square wave via the flat path, the component via the low-pass filter actually adds to it, since phase shift through the filter is 180°. By 2kHz, phase shift at d) is 360°, but there is little signal left via the low-pass path, so the overall output is nearly square.

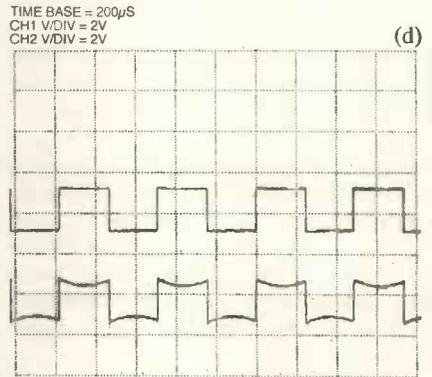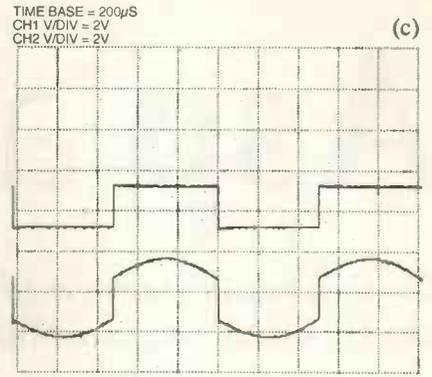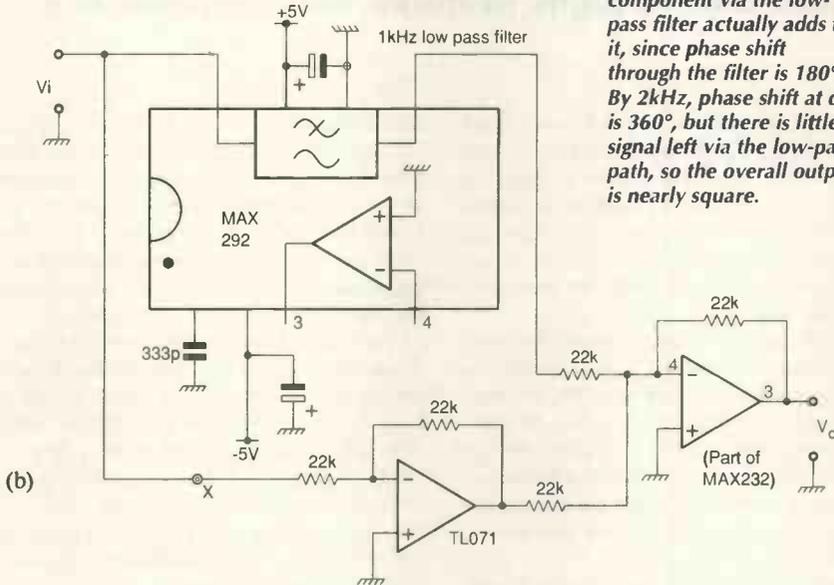

indeed, due to the 180° phase shift, it adds to it, as in Fig. 2c).

An eight-pole Bessel filter has constant group delay (phase shift proportional to frequency) well past the cut-off frequency, almost up to twice that frequency – in fact the data sheet for the MAX292 used in the circuit of Fig. 2b) shows it as completely flat to 2fc. Consequently, at that frequency the phase shift through the low-pass path has reached 360° and the signal via the low-pass path is again subtracting from that via the flat path. However, the signal is by now much attenuated so the flat top of the square wave is by now only slightly dented, as in Fig. 2d), and quite flat at 3fc and upwards.

This simple high-pass filter also has a limited performance at low frequencies. Figure 3a) shows a 100Hz square wave applied to the basic low-pass filter, upper trace, and its output, lower trace. Bessel response shows no ringing, but there is clearly a finite time delay through the filter. Subtracting the two waveforms allows the edges of the input through to the output before the low-pass filter output arrives to cancel the rest of each half cycle of the square wave. Fig. 3b) shows the result.

Figure 3c) shows the effect of inserting a pure frequency independent time delay, implemented using a bucket-brigade device, bbd, of which more later, into the flat path at the point labelled X in Fig. 2b). In this case the bbd clock frequency is too low, giving too long a delay, with the result that the Bessel low-pass filter output now leads the broad-band signal

via the flat path – compare Figs. 3b,c).

Increasing the bbd clock frequency just sufficiently reduces the delay to site the edge of the delayed square wave in the middle of the rise time of the low-pass filter output, Fig. 3d). Whereas the lower trace in b clearly contains a component at 100Hz, together with harmonics of that frequency, the lower trace in d is virtually devoid of any 100Hz component.

This is confirmed by the spectrum of the lower trace of Fig. 3d), shown in Fig. 3e), covering 0-5000Hz. At frequencies above about 2kHz, the harmonics of the square wave roll off at the rate expected and attenuation at 100Hz is well over 40dB.

**Comb filters**

It may happen that interfering signals lie within the bandwidth occupied by a wanted signal, a typical example being mains hum and its harmonics. All is not lost; it may be possible to remove the interference, whilst keeping most if not all of the signal energy, by using a comb filter – a filter with a series of notches at nfo, where fo is the frequency of the lowest notch, and n=1, 2, 3, etc.

A useful device in this context is the bbd, mentioned earlier, which subjects a signal to a time delay, the value of which is determined by the frequency of a clock signal applied to the device. Having experimented with such a device in the past to produce artificial reverberation in connection with an electronic organ, I unearthed the breadboard, the circuit of which is shown in Fig. 4a).

As shown, the circuit ran at the very low clock frequency of about 8kHz, limiting the useful bandwidth to about 2kHz. Maximum delay provided at the output tap (stage 3328) was about 200ms, and the circuit had provision for adding in contributions from any or all of the intermediate taps, at various strengths, by means of the six-way dil switch SWB. Delays at the intermediate taps, stage 386, stage 662, etc, as a fraction of the maximum delay, are all chosen to be irrational numbers to simulate the various reflection delays and resulting eigentones in a large building.

To extend the maximum delay to one or more seconds, I used a similar arrangement of select-on-test resistors and dil switch in the path via IC1d,c,b. Output v01 consists of the input signal plus selected, delayed versions summed at the virtual earth input of IC1d and added to the direct signal. For the purposes of simulated reverberation, I found it best to recirculate solely via the maximum delay, tap 3328, adding different delays only at SWB, the input of the output path to v02 via IC1a, IC2b.

I used the MN3011 bbd chip, RS No. 631-294, which is a pmos device and is thus rated to operate between a Vss of 0V and a Vdd of -15V, although for convenience it is usual to operate it from a positive supply, as shown in Fig. 4a. It needs a two-phase clock, which was provided by the CD4011, IC4. Any overlap should be limited to within 3V of the positive rail, a condition which the circuit shown very nearly met.

Op-amp inputs are referred to a nominal midpoint voltage adjusted by the 220kΩ pot., which was set for minimum distortion on maximum amplitude signals. The 100kΩ pot. at the output of IC1d permits adjustment of the

degree of recirculation, and hence of the length of reverberation.

Naturally, if advanced too far, the loop gain exceeds unity and the circuit oscillates.

**Comb notch filter**

I modified the bbd circuit to run as a comb notch filter, by combining the signal with a delayed and inverted version of itself, but without any recirculation of the signal via IC<sub>1d</sub> and using the first tap, stage 396 output, to give a delay of 25ms. Thus a sine wave at 40Hz would be delayed by exactly one cycle, and when inverted and added to the original signal, should cancel it completely.

The same should apply at 80Hz, 120Hz, etc, whilst at 20Hz, 60Hz, 100Hz, where the delay is 180 degrees, the inverted delayed signal will add to the original and give a 6dB increase in amplitude.

This is illustrated in Fig. 4b), where the broad pass-bands are generally 20dB above the narrow stop-bands or notches; greater notch depth can be achieved by careful adjustment of the gains in the direct and the delayed inverted channels. Reduced amplitude of the lowest-frequency pass-band, centred on 20Hz, is due to the 100nF coupling capacitor at the input.

A filter with a series of narrow notches can be used to remove mains hum and its harmonics from a signal, while leaving much of the wanted signal energy. If the wanted signal happened to be at 20Hz and/or any of its odd harmonics, it would be passed by the filter in its entirety, completely unscathed.

This arrangement, with a comb spacing of 10.125kHz and known as the 'tête bêche' (head to toe) system, was used years ago to distribute two black-and-white television pictures over cable in urban areas; the two programmes occupied the same bandwidth, but one with its carrier at the bottom of the band and the other at the top.

Carrier frequencies were set so that the line frequencies interleaved, there being negligible energy except in the immediate vicinity of each line frequency harmonic in normal picture content. Appropriate filters separated the one signal from the other, there being but two programmes to choose from in those days.

**Selective comb-pass filter**

If the inverted delayed channel signal is removed and a portion of the delayed signal is added back into the original signal, by closing one of the switches in SW<sub>A</sub>, what were previously notches now correspond to frequencies where the delayed signal is in phase with the original, giving a series of peaks. Midway between each pair of peaks, the delayed signal is in antiphase with the original, so the output is reduced.

When the degree of recirculation is increased to the point where  $V_{out}/V_{in}$  at the peaks almost reaches infinity, the gain via the bbd and IC<sub>1d</sub> must be very nearly unity, since we can almost do without the input entirely. In this condition, the gain at the intermediate points must be 0.5. This follows necessarily,

since  $V_o$  equals  $V_{in}$  minus the delayed version, and the gain via the delayed path has been set to unity; the only solution to the equation  $x=1-x$  is  $x=0.5$ .

Such a selective comb-pass filter was set up using the circuit of Fig. 4a) by selecting the stage-396 tap output at pin 9 of IC<sub>3</sub> with dil switch SW<sub>A</sub>, the resistor from there to IC<sub>1d</sub> input having been changed to 150kΩ. With the pot. at the output of IC<sub>1d</sub> advanced until the circuit almost oscillated, the frequency response  $V_{in}$  to  $V_{out}$  was as in Fig. 4c). The uniformity of the peaks, from about 330Hz upwards, is remarkable.

Roll-off below this frequency is due to the effect of the 10nF coupling capacitor at the input of IC<sub>1d</sub>, which is much more pronounced on the peaks than on the troughs, where the feedback via the delay is negative, nicely illustrating how positive feedback emphasises variations, while negative feedback flattens them out.

I selected the capacitor during the earlier synthetic reverberation experiments, to avoid boominess – a realistic reverberation effect does not require an extended frequency response, in either the treble or the bass.

Where the wanted signal and its harmonics are at a known frequency, you can use a selective comb-pass filter by setting the bbd clock frequency so that the peaks pick out the wanted signal components, substantially reducing the system bandwidth and cutting out much of any broadband noise which may be present. However, carried to extremes, the narrow bandwidth of the peaks means that very rapid changes in the wanted signal cannot be accurately followed.

**Bbd strips noise**

An interesting alternative is to use a selective comb-pass filter not to pick out the wanted signal from the interference, but to pick out the interference from the wanted signal. You then subtract the interference from the original mixture of signal and interference, leaving just the signal. This application is feasible where the interference is an unvarying waveform or, in signal-processing jargon, the interference is a 'stationary' signal.

Before trying out this scheme, suggested by




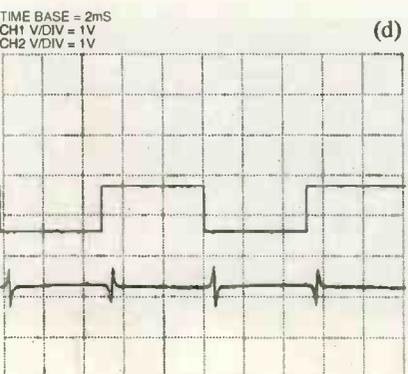
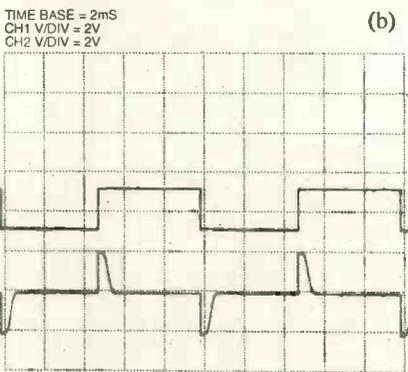


Fig. 3a). A 100Hz squarewave applied to the basic low-pass filter of Fig. 2a), upper trace and its output, lower trace. Bessel response shows no ringing, but there is a finite time delay through the filter. Due to the time delay, the simple high-pass scheme of Fig. 2a&b) lets the edges of the input through before the low-pass filter output arrives b) to cancel the rest of each half cycle of the squarewave. Adding time delay c) in the flat path is in this case excessive, as the low-pass filter output now leads the squarewave coming through the flat path. With just the right delay, d) shows the direct and low-pass signals arrive at the output at the same time. e) Spectrum of the lower trace in d) illustrates that there is hardly any 100Hz component.

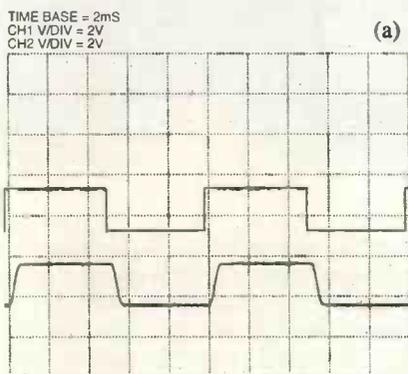

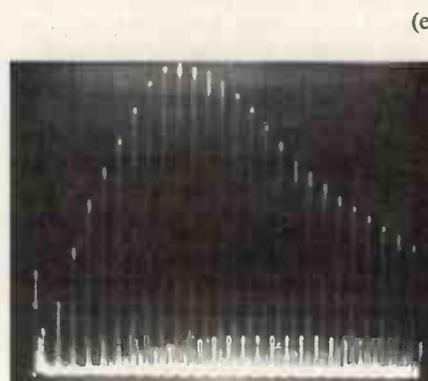

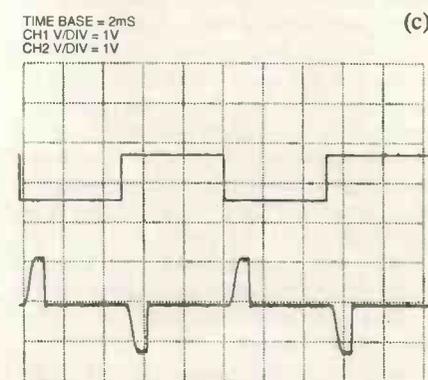

Do you have an original circuit idea for publication? We are giving **£100** cash for the month's top design. Additional authors will receive **£25** cash for each circuit idea published. We are looking for ingenuity in the use of modern components.

## Hf voltage-controlled oscillator

Three h-cmos inverters in a 74HC04 form a ring oscillator whose frequency varies with a 1.5-5.5V control voltage that alters gate delays, frequency varying as  $1/6$ . One amplifier and an output buffer used alone – the top half of the circuit – produce a square wave, but the rest of the circuit takes the square wave and turns it into a sinusoidal output.



All three phases from the ring oscillator combine in the three further inverters to give a stepped, triangular output, which passes through the variable cut-off, low-pass RC filter. Cut-off frequency of the filter automatically tracks the oscillator frequency

by means of the feedback loop consisting of a peak detector and amplifier driving the pin diode.

Short-term output frequency variations show a random element and one related to the mains frequency, both 1kHz wide and of about the same amplitude and both worse below 2MHz. Temperature variation is around 0.5%/°C at 10MHz for the free-running oscillator – a small problem in the intended synthesiser application.

**Giuseppe Faini**  
Milan  
Italy

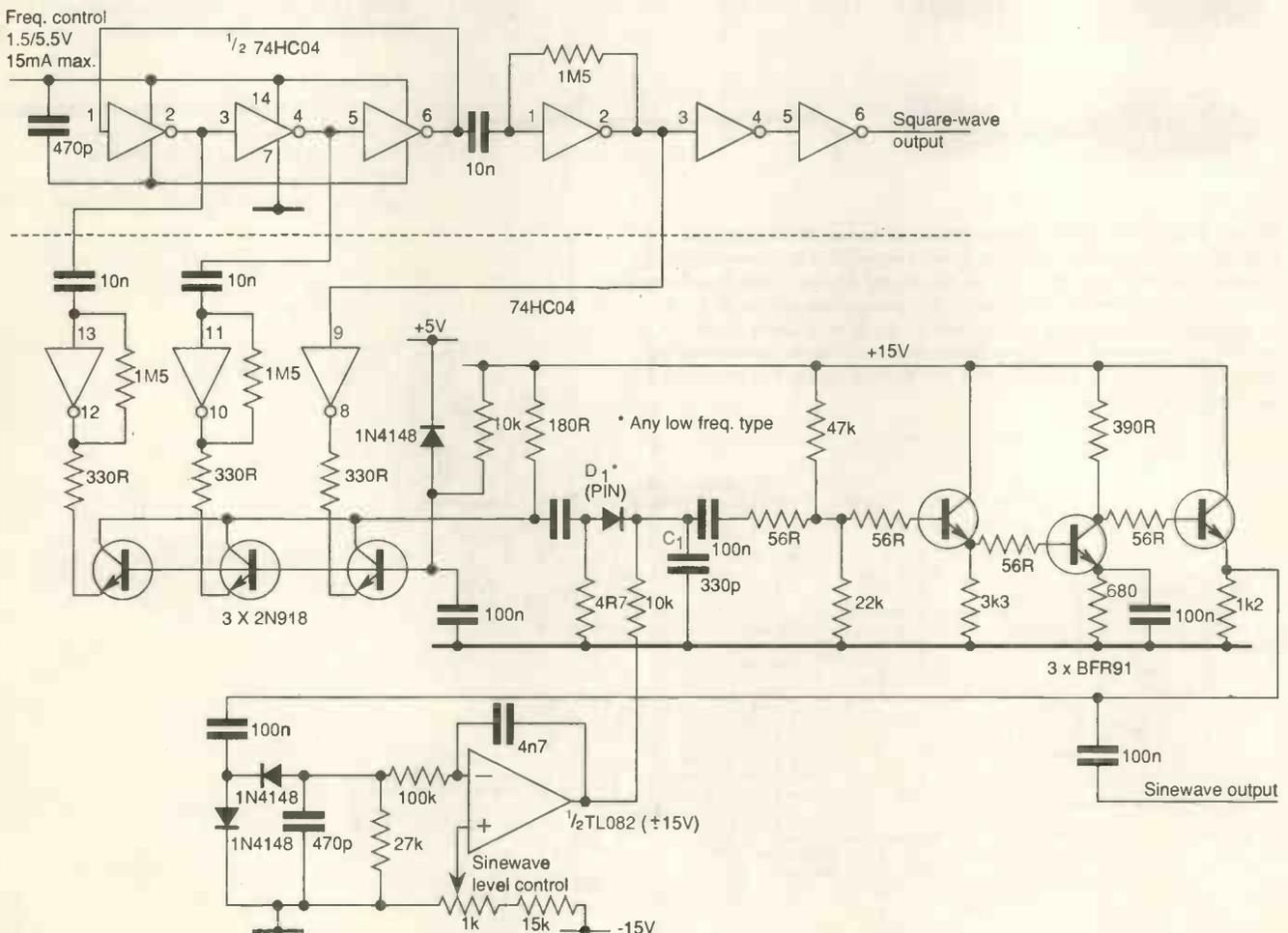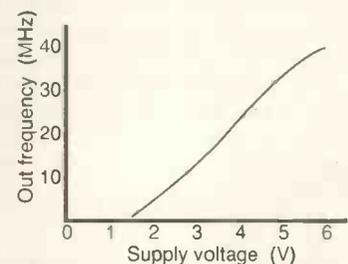*This variable-frequency oscillator spans 2-40MHz for a direct control voltage input of 1.5V to 5.5V, producing both sine and square wave outputs.*



## YOU COULD BE USING A 1GHz SPECTRUM ANALYSER ADAPTOR!

Got a good idea? Then this Thurlby-Thandar Instruments TSA1000 spectrum analyser adaptor could be yours.

Covering the frequency range 400kHz to over 1GHz with a logarithmic display range of 70dB  $\pm$ 1.5dB, it turns a basic oscilloscope into a precision spectrum analyser with digital readout calibration.

Recognising the importance of good design, TTI will be giving away one of these excellent instruments every six months to the best circuit idea published in the preceding period until further notice. This incentive will be in addition to our £100 monthly star author's fee, together with £25 for all other ideas published.

Our judging criteria are ingenuity and originality in the use of modern components – with simplicity particularly valued.



## Thermometer amplifier provides isolation

At the core of the circuit is an *HCPL7800* optical isolation amplifier, taking its input from an *AD594* or *AD595* thermocouple amplifier for J and K sensors respectively, which also drives an open-circuit indicator led. Potential divider  $R_{3,4}$  must be calculated to present less than  $\pm 200\text{mV}$  to the isolator, the values shown giving an output of  $32\text{mV}/^\circ\text{C}$ .


An *AMP 03* differential amplifier provides

a single-ended output to a low-pass filter cutting off at 10Hz or whatever frequency is needed for the application.

If the *HCPL7800* is hard to obtain, the Burr-Brown *ISO130P* is a pin-compatible alternative and the *AMP 03* can also be replaced by the *INA105KP*.

Alex Birkett  
London SE 22

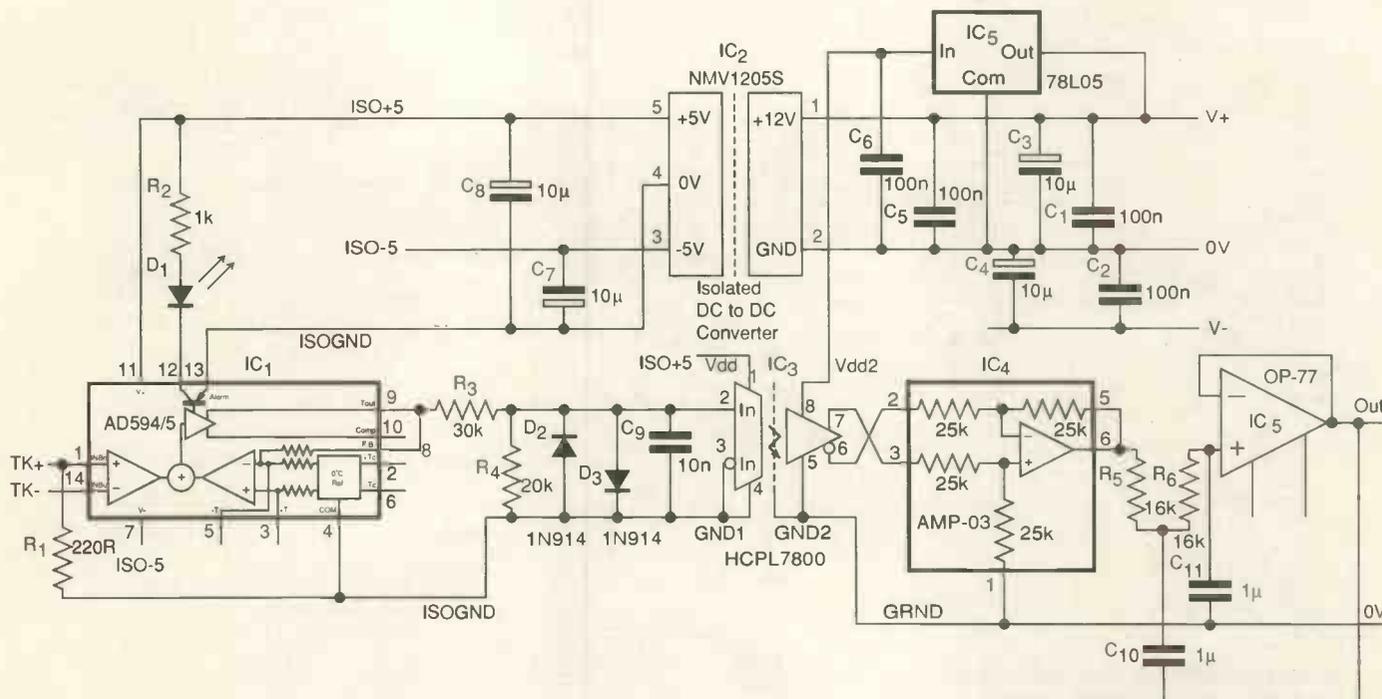Complete circuit of a  $32\text{mV}/^\circ\text{C}$  isolated thermometer, which covers  $0\text{--}50^\circ\text{C}$  or a range set by the values of two resistors.



# Remote multichannel resistance measurement

This low-power circuit measures the value of remote resistive sensors using any type of connection such as wire, infrared or ultrasonics; I use a vhf radio link. With a *UMC UM3758-108AM* encoder/decoder, it is possible to transmit 8-bit data combined with 10 address bits. Depending upon the logical level on the mode input, the circuit acts as a decoder or encoder. In this application, the address bits are hard-wired high and the measuring resolution is limited to 6-bit, for reasons explained later.

In encoder mode, the Tx/Rx pin transmits the address/data information as long as power is supplied. A built-in RC oscillator, with only two external components ( $R_9, C_9$ ) is used as a clock; matching of the encoder/decoder's oscillator frequencies is not very critical and 5% resistors are sufficient.

Serial data is supplied to the Rx input in decoder mode, where it is examined bit by bit as received. Only if two successive address/data combinations match is data transferred to the output data pins  $D_{1-8}$ , which latch the data until the next valid data is being received. The Tx/Rx out pin switches low if data matches, returning high after two successive unmatched address words.

System timing is controlled by  $IC_1$ , a *74HC4060*. The positive-going edge of the  $Q_5$  output of  $IC_1$  triggers an enable

signal, the duration of which is adjustable by  $P_1$  about every 60s, depending upon  $R_1, R_2, C_1$ . At the start of this enable time, the counter in  $IC_4$  is reset to 0 by the positive-going edge of the oscillator enable signal via  $C_3, R_4$ . Diode  $D_8$  gates the  $IC_4$  clock signal, pulling down the clock input to disable counting. During the enable time, a sensor-dependent count is reached on the outputs  $Q_{4-9}$ . Be careful to avoid overflow, by selecting the right combination between the enable time and the  $IC_4$  oscillator frequency, which depends on the sensor used.

At the end of the oscillator enable time, the down-going edge of  $IC_{5b}$  Q output triggers  $IC_{5a}$  to switch on the power supply for both the *UM3758* and the transmitter. To be sure that a minimum of three address/data codes are transmitted, the transmitter on time, adjustable by  $P_2$ , is 250-300ms. Raising the *UM3758* oscillator frequency makes it possible to use an even shorter transmitter time, but bear in mind that the receiver must be capable of detecting this signal. A low-loss, dual P-channel mosfet, a Siliconix *SI9933DY* with  $R_{gs} < 0.2\Omega$ , switches the transmitter/encoder supply.

To prevent any current flow through the data input of  $IC_2$  when it is powered down, the counter outputs of  $IC_4$  are connected via diodes  $D_{1-6}$ . Because of the internal architecture of the *UM3758*, an open input will be seen as logical 1, so there is no need to use pull-up resistors.

Logic levels of data bits D7 and D8 are


user selectable to allow the use of four transmitters on the same frequency without changing decoder address lines in the receiver. A small difference in transmitting interval will prevent most of the interference when more than one transmitter is used.

Powered by a 3.6V lithium cell, the transmitter logic draws less than 100µA, transmitting current depending upon the type of transmitter used, although overall power consumption is still low because of the short transmitting time. A telemetry system based on this design has been in use by our institute since early 1994 to study activity and feeding behaviour of the red deer. As the resistive element we use an electrolytic tilt sensor. I built the circuit using surface-mounted components but, except for the *SI9933DY*, they are also available in through-hole form.

**Willem van der Veer**  
Institute for Forestry and Nature Research  
Wageningen  
The Netherlands.

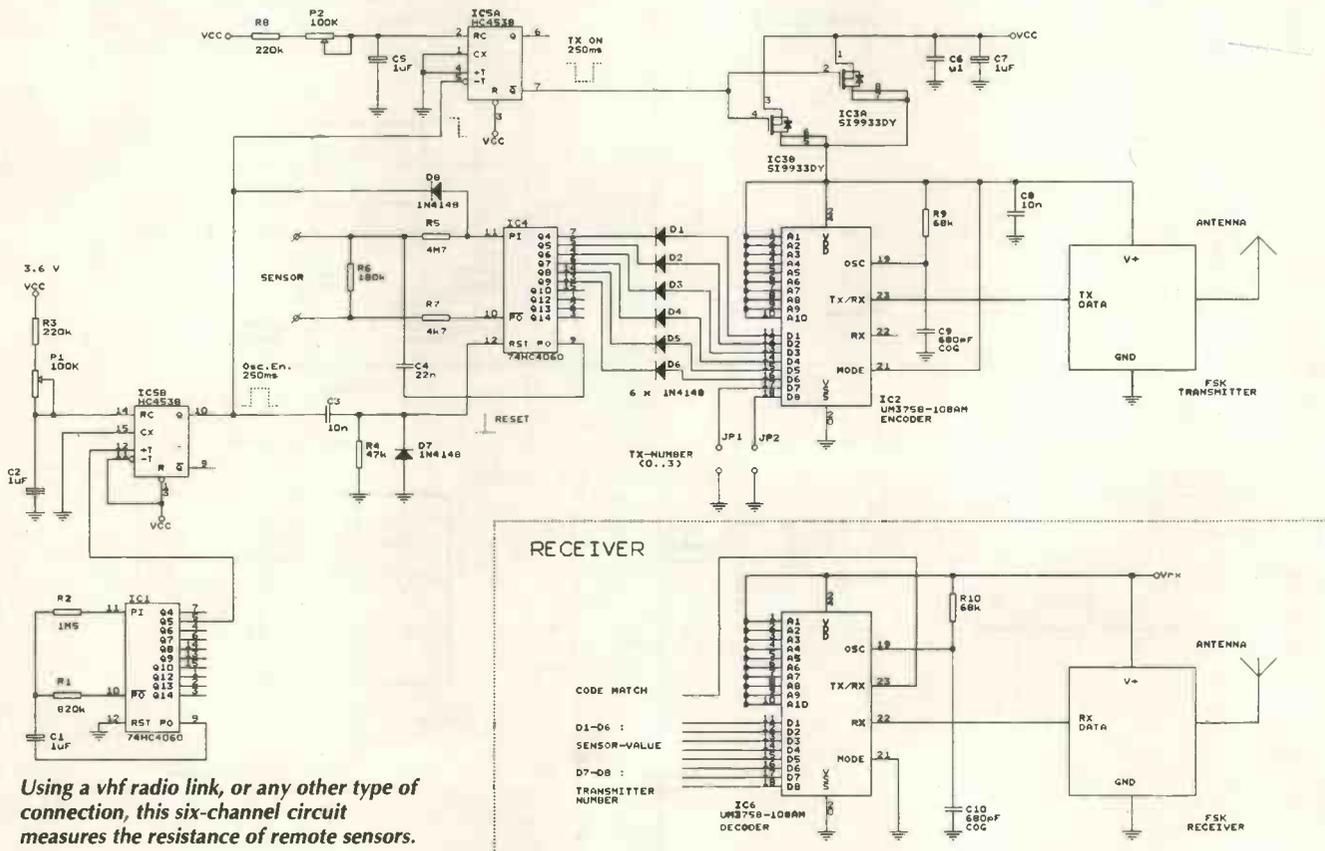
**References**

- UM3758* series data sheet, UMC Europe, Amsterdam, The Netherlands. Telephone: 0031-20-6970766.
- Little Foot series manual, Siliconix Ltd, Newbury, Berks RG14 5UX. Tel. 01344-485757.



£100 WINNER

## Dvm to milliohm meter

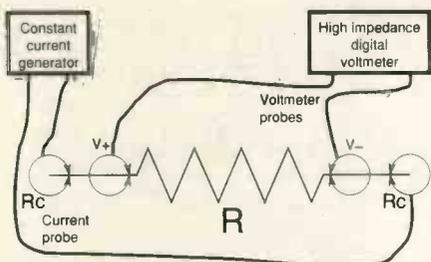

Digital voltmeter adaptor enables it to measure down to 1mΩ by forcing a constant current through the circuit and separating the voltage measurement.

High and variable probe contact resistance set a lower limit to the resistance measurement facility when a digital meter is used in the normal way to supply a current and to measure the consequent voltage drop across the resistor. Resolution is also commonly 100mΩ which is, again, limiting.

The diagram, top left, shows an alternative method in which contact resistance plays no part. A constant, higher than normal, current

is supplied separately and the voltage read by the dvm, whose probes must be directly across the resistance to be measured. Input current of a high input-impedance dvm is negligible compared to the 100mA in the measuring circuit. Resistance is the voltage reading multiplied by 10, i.e. 100mV=1Ω.


In the practical circuit below, the voltage regulator LM317T functions as a constant-current generator, output being set by R<sub>3</sub>; a good milliammeter or a precision resistor

carrying the current will be needed to adjust the current.

Filter R<sub>2</sub>C<sub>2</sub> reduces error in the dc-reading millivoltmeter, or a 9V battery may be used.

One shorted turn in a transformer showed up as a reading of 3973mΩ against the 4035mΩ of a functioning unit and it was salutary to see that the resistance of a spliced solid wire was 30mΩ, while when soldered its resistance was 1mΩ. Leads can be of any length, so long as the whole loop does not exceed 10Ω.

Douglas A Kohl  
Osseo  
Minnesota, USA

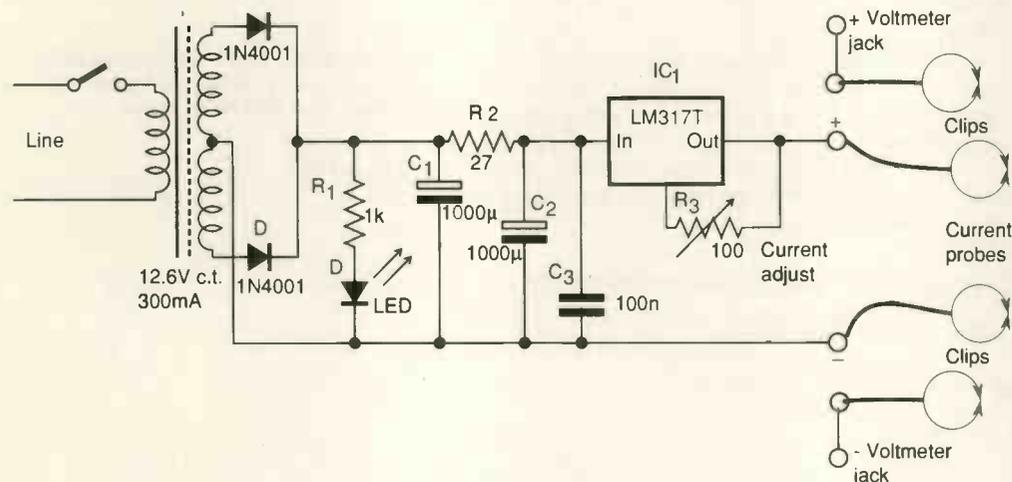

## Median filter for spike reduction


This type of filter finds the median level of an analogue signal, that being the level that is exceeded 50% of the time. Filters of this type reduce spikes while maintaining edges of a waveform.

An LM339 comparator changes state when the input crosses the median level, forcing the LM324 integrator to ramp the fed-back median level in a positive or negative direction at around 12000V/s. Transients are therefore limited to this speed.


Set the probability level by applying a dc level of say V<sub>cc</sub>/2 at the input, and adjusting the pot until the square wave V<sub>e</sub> has a unity m:s ratio – setting V<sub>e</sub> to a 3:1 ratio makes the filter determine the upper quartile of the input, etc.

At the output, a continuous 60kHz, 0.1Vpk-pk triangle wave appears, determined by the RC feedback filter; a faster comparator and op-amp would determine the triangle wave by hysteresis, rather than by the filter. Filter the triangle out or leave it as dither for succeeding stages.

W Gray  
Farnborough  
Hampshire.

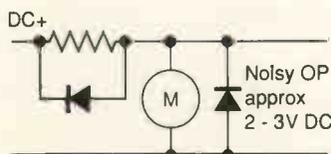

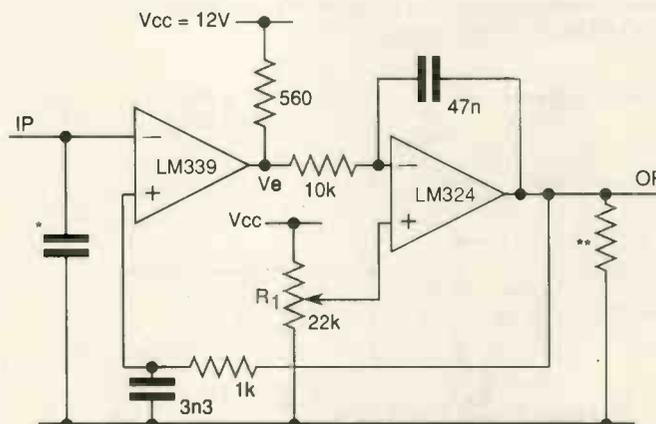Median filter removes overshoot spikes to leave fast edges. Test circuit, left, demonstrates filter by producing spiky signals.



\* = 10n, only needed during calibration, to prevent jitter  
\*\* = 1k load, only needed if op-amp is LM324


# Q-meter oscillator

Although simple in design, this 100kHz-2MHz oscillator provides a variable-amplitude output at low distortion and is suitable for use as the oscillator in a Q-meter, other types of instrument or in communications.

Tail current in the differential pair switches between collector loads on alternate half cycles, the load to  $Tr_2$  consisting of the LC tank circuit. Voltage across the tank is fed back by way of  $R_{1,2}$  to the buffer  $Tr_3$  to complete the feedback loop. Symmetry is maintained by  $Tr_4$  and its components.

Current mirror  $Tr_{5,6}$  drives the tail current, which is made variable by  $VR_1$  to vary output amplitude and which can be monitored by the voltage on  $Tr_6$  emitter or the switching waveform on  $Tr_1$  collector. The tank circuit provides a filtering action on the square current waveform to give less than 1% distortion even at low Q values. Square waves at  $Tr_1$  collector may be useful as synchronisation to other circuits.

On a 12V supply, output swing before

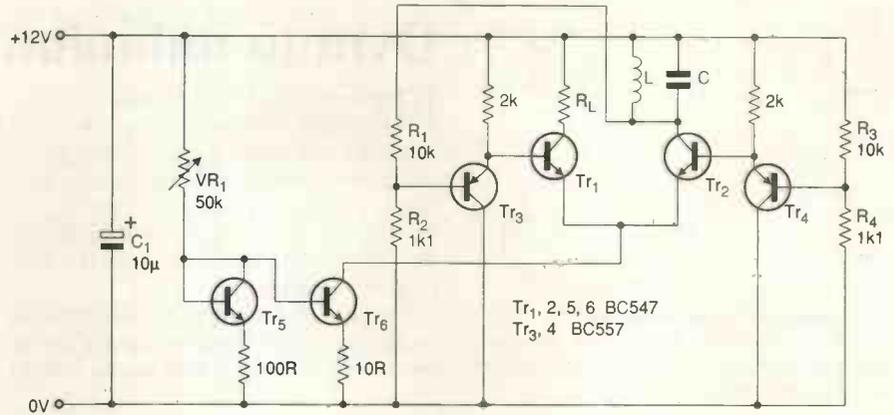

clipping is 20Vpk-pk, approximately symmetrical about the positive supply rail. If the oscillator is to be used in a measuring instrument, loading of the feedback circuit should be considered. An unknown L can be calculated from the frequency and known resonating capacitance.

$$R_d = V_{pk-pk} / 1.27 I_{pk-pk} \text{ (dynamic resistance)}$$

$$Q = R_d / (6.28 f_o L),$$

$$\text{where } L = 1 / C(6.28 f_o)^2$$

Simple oscillator, which nevertheless offers variable output to 20Vpk-pk, at under 1% distortion, from 100kHz to 2MHz.

M J Hutchings  
Salisbury  
Wiltshire

# Level-shifter generates square waves

Fig. 2. Single gate generator offers a wide range of frequency and mark:space ratios.

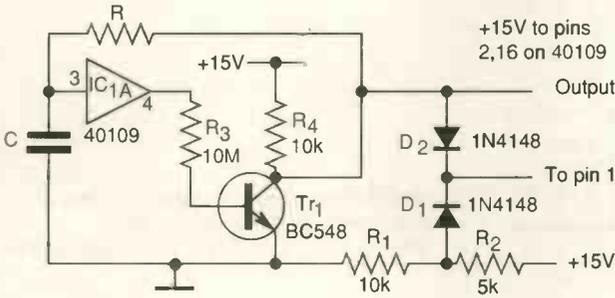


Fig. 3. Enhancement of square wave generator Fig. 2 includes adjustments for frequency and mark:space ratio.

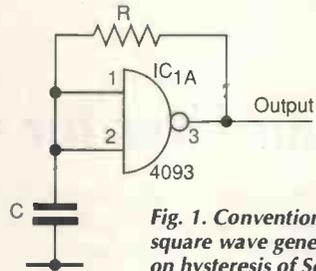
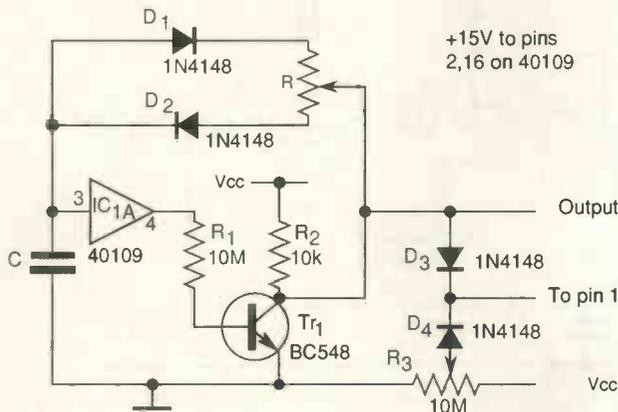


Fig. 1. Conventional single gate square wave generator relies on hysteresis of Schmitt nands

Single-gate square-wave generators often use the hysteresis of Schmitt nands, Fig. 1 to change state. This one uses a 40109 level shifter that offers access to both  $V_{cc}$  and  $V_{dd}$  on separate pins.

In Fig. 2, initially, C is discharged, the output of the 40109 is low, the transistor is off and circuit output is at around 15V. Point B is 10V and, since  $D_1$  is reverse-biased and  $D_2$  forward-biased,  $V_{cc}$  to the ic (pin 1) is at about 15V. The capacitor starts to charge through R and when it reaches 7.5V the output of the ic goes high, the transistor conducts and the output goes low.

Diode  $D_1$  is now forward-biased,  $D_2$  reverse-biased and  $V_{cc}$  about 10V, after which the cycle repeats. Mark:space ratio is 1:1, since the capacitor charges and discharges through the same resistor.

Figure 3 shows a developed circuit with adjustments for frequency and mark:space ratio.

V B Oleinik  
Kaliningrad  
Moscow Region  
Russia

# Am detector with gain


Since the square of a number, positive or negative, is always positive, a squaring circuit inverts the negative half cycle of a signal and forms a detector for am.

This squarer is an analogue multiplier with both inputs connected together so that the output is proportional to the square of the instantaneous input, the multiplier operating in a continuous mode, unlike the switching mechanism of a diode. Op-amp IC<sub>2</sub> converts the balanced output of the multiplier to an unbalanced output at low impedance.

Gain is set by the values of  $R_{x,y}$ , the smaller the values, the greater the gain. With the values shown, voltage gain is 40 and bandwidth 100MHz. At 30% modulation depth, second-harmonic content of the output is 7.5%.

**Peter Goodson**  
Bracknell  
Berkshire

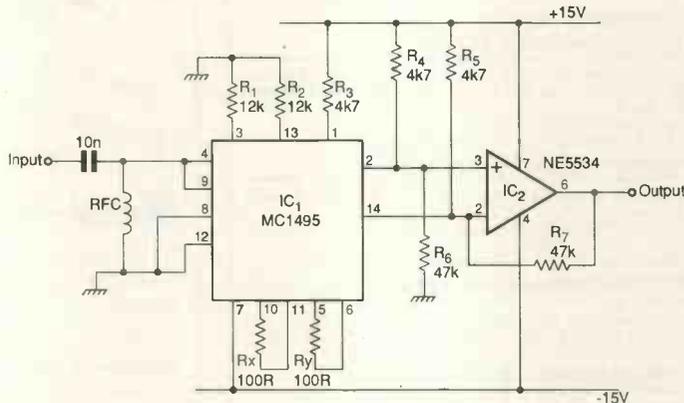Analogue multiplier with common inputs acts as am demodulator, with a gain of 40.




# Two-wire connection for both power and signal

A current-feedback amplifier in this thermistor circuit allows the use of a single-ended supply for both voltage offset and bias.


Current to the amplifier inverting input maintains a constant sum determined by the voltage at pin 3 and the current in  $R_b$ . Gain resistor  $R_f$  therefore sees the output voltage change inversely with thermistor current, the op-amp voltage comparator switching state as its input exceeds the voltage on its pin 2. Hysteresis current through  $R_{hyst}$  goes to the summing node via the 2N2907, used as a diode, since hysteresis feedback current is only 1.5µA/°C; a led indicates the state of the comparator. The 42.2kΩ resistor linearises the thermistor between 10°C and 30°C. Output of the current-feedback amplifier is 2-7Vdc.

Used as a remote monitor, the circuit was supplied by an ICL7663SCPA low dropout regulator, which supplied 18mA with the led on and 9mA with it off, so that sensing this step gave a system taking power and sending signal over the same two wires.

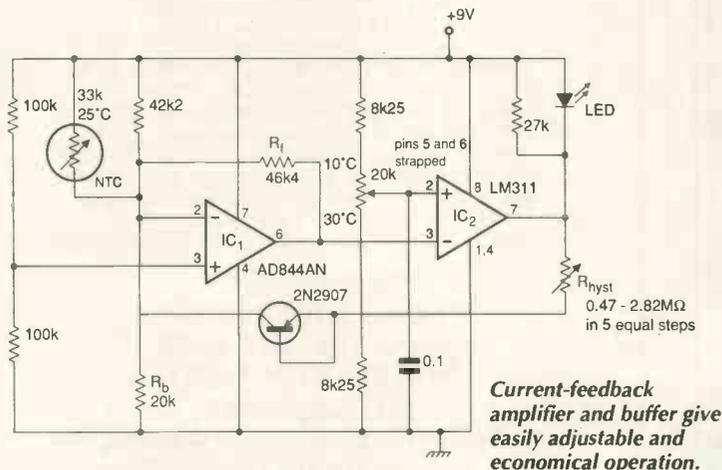**John A Haase**  
Colorado State University  
USA



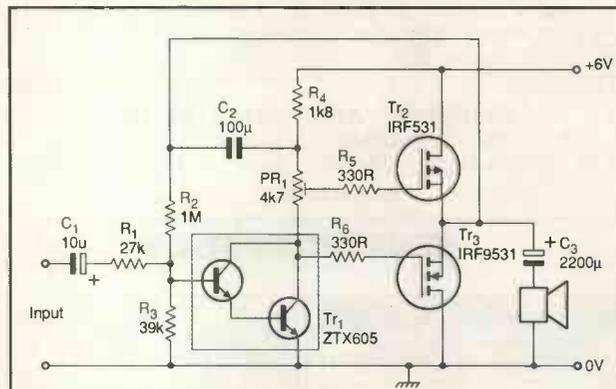Current-feedback amplifier and buffer give easily adjustable and economical operation.



Very simple 30W audio power amplifier offers a 50kHz bandwidth and 0.1% total harmonic distortion at 30W. Unusually, the circuit operates with a single supply rail.

# Simple 30W power amplifier

Using a shunt driver stage eliminates much of the complexity normally associated with audio power amplifiers, while retaining a reasonable performance in terms of its -3dB bandwidth at 10Hz-52kHz and thd of under 0.1% at 30W and 1kHz.

As driver, a Zetex 605 is convenient, but discrete transistors can, of course, be used. Bootstrapping from the output to the junction of the collector-load components by way of  $C_2$  increases the output swing and reduces the effect of mains ripple.

Overall direct feedback is applied via  $R_2$  and  $R_3$  can be selected to cope with different supply voltages, its value being determined by  $1.2 \times 10^6 / 2V+$ . For a change in closed-loop voltage gain, vary  $R_1$ . Gain is set by  $R_2/R_1$ .

**J Macaulay**  
Chichester,  
Sussex.

# JOHN MORRISON

## Hardware & Software Design Specialist

Smart Card/Programmer & PIC16C84 Programmer £79.95

On board ISO7816 Socket (Videocrypt, GSM etc). Software Runs on an IBMPC allowing the operator to send data to and receive data from an ISO7816 Smart Card. Can also be used to program Smart Card emulator (PIC Cards) cards used in the Satellite TV trade. Includes a software suite allowing the operator to successfully manipulate data on many of the popular Smart Cards. Requires an external power supply of 15-20V AC or DC (optional extra £8.50).

**PIC Programmer 16C54-55-56-67-71 & 84 £89.95**

Programs all 18/28 Pin PIC Microchips. Read Write & Copy PIC devices including data memory & configuration fuses where applicable. Interfaces to Centronics port in IBMPC. High quality board with ZIF Socket. Includes software suite for PIC 18/28 pin devices. Requires an external power supply 15-20V AC or DC (optional extra £8.50).

**PIC In Circuit Emulator Std £79.95**

A low cost in circuit emulator for the 18 pin PIC chips (No A to D). Operates via the printer port, the emulator appears as a real PIC to the system with Oscill and RTCC in-out. Runs in real time on the IBMPC, speed is dependent on PC speed but will be between 1ms and 80µs. NOW SUPPLIED WITH A FULL SUITE OF DEVELOPMENT SOFTWARE. Allows the operator to write and test code before committing to a real Pic, saving development cost & time.

**PIC In Circuit Emulator Professional £159.95**

In Circuit Emulator for PIC 16C54-55-56-57-71 & 84. Replaces all 18 or 28 pin PICs. All ports are Bi directional, Oscill output, RTCC Input. Onn board A to D converter for PIC16C71. NOW SUPPLIED WITH A FULL SUITE OF DEVELOPMENT SOFTWARE, manual, connecting leads & headers, ASM examples, and hardware circuit ideas. Allows the operator to write and test code before committing to a real Pic, saving development cost & time.

**MEGAPROM EPROM Programmer £99.95**

Handles EPROM EPROM & FLASH memory. From 2K 2716 - 8Mg 27C080. Runs on ALL IBMPC compatibles, Note books and Laptops via the Centronics port using a standard printer cable. High quality PCB Inc ZIF socket. Requires an external power supply 15-20V AC or DC (optional extra £8.50).

**EPROM Emulator £69.95**

Works on ANY computer with a Centronics printer port. Data sent to the printer appears as ROM on the target board EPROM socket. Emulates 1Kb to 32Kb (27C256) ROMs. Very fast download, supplied with development software. Allows the operator to write and test code before committing to a real Pic, saving development cost & time.

**DEVELOPMENT SOFTWARE £19.95**

Develop software on your IBMPC for other Microprocessors, controllers, PIC's etc. Fully integrated Text Editor, Assembler, Disassembler and Simulator. Code can be downloaded directly to your EPROM EMULATOR. Supplied with sample ASM files and user documentation. Available for:- MC8051/52/552 MCS8048/49 PIC16C71/84 PIC16C54/55/56/57 HD63/6809 R6502

Please add £1.75 P&P

12 Month Component Failure Warranty

### CROWN HILL ASSOCIATES LIMITED

P.O. BOX 845, WATERBEACH, CAMBRIDGE CB4 9JS

FAX: 01223 441645 TEL: 0956 700017 BBS: 0956 700018

VISA MASTERCARD ACCESS

CIRCLE NO. 154 ON REPLY CARD

# Radio Data Modems

Range 2-3km  
Free Communications  
User-friendly PC interface  
Selectable channels  
Flexible Hand-shaking  
Unit Addressing

Faster operation: up to 9600 baud  
New synthesised radio  
5 Diagnostics LEDs  
Licence exempt to MPT 1329

## Now - with even more features!

In addition to the wide range of features currently available, the model 2ASx now offers a **repeater function** and a **rapid response interface** which virtually eliminates turnaround time associated with devices such as data loggers.

In keeping with our policy of being ever responsive to the requirements of our wide-ranging customer base, this enhanced specification is in direct response to your requests.

### NEW! Telemetry pictures by radio.

Using the proven, licence-exempt Radio Data Modems, we now offer 4 or 8 camera modules which can be used 2 to 3 km away. Screen refresh is every 4 to 6 seconds and up to 4 scenes can be viewed simultaneously on screen.

Please call, fax or write for further details.



Sole UK Distributor: XL Systems Ltd  
High Warren House, Tandridge Road  
Worthington, Surrey CR6 9LS.  
Tel: 01883 622778, Fax: 01883 626991

CIRCLE NO. 155 ON REPLY CARD

### WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 7000 SERIES OSCILLOSCOPES AVAILABLE FROM £200. PLUG-INS SOLD SEPARATELY

TEKTRONIX TA5475 4 Channel 100MHz Delay Sweep Cursors	£1300
TEKTRONIX TA5455 Dual Trace 60MHz Delay Cursors	£900
TEKTRONIX 2455 4 Channel 30MHz Delay Sweep Cursors	£1950
TEKTRONIX 2245A 4 Channel 100MHz Cursors/Volts/etc	£1250
TEKTRONIX 2235 Dual Trace 100MHz Delay Sweep	£750
TEKTRONIX 485 Dual Trace 50MHz Delay Sweep	£750
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep	£500
TEKTRONIX 465 Dual Trace 100MHz Delay	£400
H.P. 1740A Dual Trace 100MHz Delay Sweep	£350
TEKTRONIX 2215 Dual Trace 60MHz Delay Sweep	£250
TEKTRONIX 455 Dual Trace 50MHz Delay Sweep	£400
PHILIPS PM3217 Dual Trace 30MHz Delay Sweep	£400
WITACH V223 Dual Trace 20MHz Delay Sweep	£250
GOULD OS1100 Dual Trace 30MHz Delay Sweep	£240
BECKMAN 9020 Dual Trace 20MHz Delay Sweep	£240
KUNITSU SS5702 Dual Trace 20MHz	£200
KUNITSU SS5504 Dual Trace 25MHz	£220
GOULD OS300 Dual Trace 20MHz (No handle)	£180
BLACK STAR 1502 Dual Trace 15MHz Mains Battery	£200
GOULD 4030 Dual Trace 20MHz Digital Storage Cursors	£350
GOULD OS4020 Dual Trace 10MHz Digital Storage	£250
GOULD 4100 Dual Trace 10MHz Dig Storage/T-X-Y Modes	£225
GOULD OS4000 Dual Trace 10MHz Digital Storage	£200
H.P. 1741A Dual Trace 100MHz Analog Storage	£400

THIS IS JUST A SAMPLE. MANY OTHERS AVAILABLE

EATON/ALTECH 380K11 Syn Sig Gen 1-2000MHz with PM3602 AM/FM Phase Mod.	P.O.B.
MARCONI 7019 Syn AM/FM Sig Gen 80kHz-100MHz	£1900
MARCONI 2018 Syn AM/FM Sig Gen 80kHz-520MHz	£2500
H.P. 8620C Sweep Osc 5-12.4GHz or 8-12.4GHz	£350
H.P. 8620D Sweep Oscillator Main Frame only	£200
RACAL 5081 Syn AM/FM Sig Gen 5-520MHz	£450
FARWELL SS620 Syn AM/FM Sig Gen 10-520MHz	£400
MARCONI TF2337 Automatic Distortion Meter	£200
MARCONI TF2334 Distortion Factor Meter 20Hz-20kHz 0.05% Un-used	£225
MARCONI TF8338 Audio Power Meter 0-10W	£250
MARCONI TF2163 Attenuator DC-1GHz	£100
H.P. 8495B Attenuator DC-18GHz 0-11dB in Steps	£350
HAYFIELD Z105 Attenuator 50 Ohm	£75
TEKTRONIX TDR1502	£1250
R&S Video Noise Meter UPSF2 with UPSF2E 40-Hz-10MHz	£1500
R&S Video Analyser Type UHF	£900

### BRUEL & KJOER EQUIPMENT AVAILABLE PLEASE ENQUIRE

SPECTRUM ANALYSERS	
H.P. A7550 Synthesised 10Hz	£4000
H.P. 8555A 0.01-22GHz	£4000
H.P. 3580A 5Hz-50kHz	£800
ANDO AC8281 with AC8211 1700MHz	£1500
POLARON 641-1 10MHz-180MHz	£1000
H.P. 182 with 8558B 100kHz-1500MHz	from £1500
H.P. 141T with 8558A & 8552B 100kHz-18GHz	£1700
H.P. 141T with 8558A & 8552B 500kHz-1500MHz	£1200
H.P. 141T with 8558A & 8552A 10Hz-100MHz	£800
H.P. 141T MAIN FRAMES ONLY. GOOD TUBES.	£225
MARCONI TF2370 30kHz-110MHz	£1200
TEKTRONIX 711 with Main Frame 100kHz-1800MHz	£1200
TEKTRONIX 715 with Main Frame 20MHz-5MHz	£1000

H.P. 5341A Frequency Counter 50MHz 1.5Hz LED	£300
RACAL 1998 Frequency Counter 1.3GHz (Options GPIB & High Stab)	£900
MARCONI 2437 Universal Counter/Timer DC-100MHz 8 digit	£175
MARCONI 2430A Frequency Counter 10Hz-60MHz 8 digit	£125
RACAL 9916 Frequency Counter 10Hz-520MHz	£175
BLACK STAR Meleor 100 Frequency counter 100MHz	£100
DATRON 1055 5 1/2 digit Autocal Multimeter with AC/DC/Ohms. IEEE	£600
H.P. 3435A 3 1/2 digit Multimeter AC/DC/Ohms/Current. LED.	£180
SOLARTRON 7065 6 1/2 digit Microprocessor Voltmeter AC/DC/Ohms/Auto.	£400
SOLARTRON 7045 4 1/2 digit Multimeter Volts/Amps/Ohms	£80
THANDAR 1504 4 1/2 digit True RMS Multimeter with Adaptor.	£100
THANDAR 1503 4 1/2 digit Multimeter with Adaptor	£75
H.P. 3310A Func Gen 0.005Hz-5MHz Sine/Sq/Tri/Pulse/Ramp/DC	£200
WAVETEK 182A Func Gen 0.004Hz-4MHz Sine/Sq/Tri/DC/TTL Pulse etc	£225
WAVETEK 184 Sweep Func Gen Sine/Sq/Tri/Pulse/Ramp/TTL Pulse etc	£250
THANDAR TG501 Func Gen 0.005Hz-5MHz Sine/Sq/Tri/Pulse/etc	£175
GOULD J35 Sine Square Oscillator 10Hz-100kHz	£150
FEEDBACK FG600 Sine/Sq/Tri 0.01Hz-100kHz	£60
H.R. SMITH ANTENNA TEST SET Type 12-602-4L	£2000
LINDS LAL M28 Audio Analyser	£500
UNIDIM CPS01 Audio Analyser	£350
PHILIPS PM5565 Waveform Monitor	£300
PHILIPS PM8917 Video Line Selector	£200
FERRUGRAM R152 Recorder Test Set	£250
REMO Dual Variable Filter VDF10 1Hz-10kHz	£200
RACAL Instrumentation Recorder Type Store 40Hz	£350
RACAL Instrumentation Recorder Type Store 70S	£500
NAERA IV-S1 Tape Recorder	£350
ANA Oscilloscope and Noise Meter F212	£400
LEADER LS216 Signal Generator	£450
MARCONI TF2700 Universal Bridge. Battery Operated	from £150
MARCONI TF131A Universal LCR Bridge 0.1%	£125
WYME KEAR 8424 Digital Component Meter LCR	£700
HEALTHYTR 1B RLC Bridge	£60
SORENSEN DCR600-4 50-600 Volts 0-4 5Amps.	£100
H.P. 6288 0-40 Volts, 0-30 Amps	£500
FARWELL 1030 0-30 Volts, 0-100 Amps, Metered	£800
FARWELL 830 10 30 Volts, 10 Amps Variable	£150
FARWELL L30 0-30 Volts, 0-5 Amps, 2 Meters	£150
FARWELL L30E 0-30 Volts, 0-5 Amps, Metered	£100
FARWELL L30C 0-30 Volts, 0-2 Amp, Metered	£80
FARWELL L30D 0-30 Volts, 0-1 Amp, Metered	£60
FARWELL L30E 0-30 Volts, 0-1 Amp, Metered	£35
BRANDENBURG Alpha Series 2 Modes 2702 15KV	£300
BRANDENBURG Model 4228 7-70V Metered	£200

MANY OTHER POWER SUPPLIES AVAILABLE

### NEW EQUIPMENT

HAMEG OSCILLOSCOPE HM1095 Triple Trace 100MHz Delay Timebase	£847
HAMEG OSCILLOSCOPE HM604 Dual Trace 50MHz Delay Sweep	£853
HAMEG OSCILLOSCOPE HM303 Dual Trace 30MHz Component Tester	£452
HAMEG OSCILLOSCOPE HM205 3 Dual Trace 20MHz Digital Storage	£677
All other models available-all oscilloscopes supplied with 2 probes	
BLACK STAR EQUIPMENT (P&P all units £5)	
APOLLO 10-100MHz Counter/Timer Ratio/Period/Time interval etc	£234
APOLLO 100-100MHz (As above with more functions)	£372
METRO 100 FREQUENCY COUNTER 100MHz	£119
METRO 600 FREQUENCY COUNTER 600MHz	£145
METRO 1000 FREQUENCY COUNTER 1000Hz	£149
METRO 1000 FUNCTION GEN 1Hz-500kHz Sine/Sq/Tri	£185
ORION COLOUR BAR GENERATOR Pal/TV Video	£243
All other Black Star Equipment available	
OSCILLOSCOPE PROBES Switchable x1 x10 (P&P £3)	£13

Used Equipment - GUARANTEED. Manuals supplied if possible. This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.

## STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Telephone: (01734) 268041. Fax: (01734) 351696

Callers Welcome 9am-5.30pm Monday to Friday (until 8pm Thursday)

CIRCLE NO. 156 ON REPLY CARD

# Literature Components Equipment

- Spectrum Analyser Tek 7623A/7L18 - £3,500
- Spectrum Analyser Tek 7623A/7L13 - £2,200
- Spectrum Analyser Marconi 2370 - £1,500
- Spectrum Analyser HP141T/8554B - £1,500
- Spectrum Analyser HP141T/8555A - £2,500
- Digital Storage Hameg 205-2 - £550
- Digital Storage Iwatsu 6121A (Cursors) - £700
- Digital Storage Gould 4035 - £500
- Tek 465 Scope - £350
- Tek 475 Scope - £450
- Philips PM3215 Scope - £250
- HP 1740A Scope - £350
- Hameg 203-6 Scope - £250
- Thandar TF200 Frequency Counter - £100
- Gould J3B Oscillator - £200
- Dranitz 626/6003 Mains Monitor - £550
- HP 4952A/002 Protocol Analyser - £2,700
- HP 4954A High Speed Protocol - £2,750
- HP 3773A/001 Data Com Analyser - £4,000
- HP 4957A/001 Protocol Analyser - £4,200

WE BUY WE SELL

USED ELECTRONIC TEST INSTRUMENTS

For further details:

Phone: 0181 813 9946

Fax: 0181 574 2339

Mobile: 0374 759984

At LCE, Unit 5,  
Southall Enterprise Centre,  
Bridge Road, Southall,  
Middlesex UB2 4AR, England

CIRCLE NO. 157 ON REPLY CARD

# NEW PRODUCTS CLASSIFIED

Please quote "Electronics World + Wireless World" when seeking further information

## ACTIVE

### A-to-d and d-to-a converters

**Multi-channel d-to-as.** Dual and single channel, 8-bit digital-to-analogue converters newly introduced by SPT offer high speed and low power consumption. *SPT5100* processes 20Mword/s while dissipating 70mW and the *SPT5110* 30Mword/s at 135mW. Both are intended for use in colour graphics applications. Signal Processing Technologies Inc. Tel., 01932 254904; fax, 01932 254903.

**Triple 8-bit d-to-a.** Meant for use in video and graphics, Raytheon's *TMC3503* restructures analogue rgb video from the digital form and drives graphics monitors directly. It has single-ended current outputs, takes in SYNC\ and BLANK\ inputs and has a separate current source to add separate sync. pulses to the green d-to-a converter output. Three speed


grades give 30, 50 and 80Mpixels/s. An input takes all three converters to maximum value to give reference white for calibration or display. METL. Tel., 01844 278781; fax, 01844 278746.

**Video d-to-as.** Digital-to-analogue converters in the Signal Processing Technology *SPT1018/1019/5140* family offer conversion rates of 165/275/400 million words/s and 8-bit resolution. For video, features include sync., blank, reference white and bright inputs and analogue video output to drive doubly terminated 50 $\Omega$  or 75 $\Omega$  loads to standard RS-343-A and RS-170 video levels. There is a feed-through pin to allow registered or unregistered operation between video control inputs and data; in registered mode, composite functions are latched to the pixel data to prevent screen-edge distortion. Ambar Cascom Ltd. Tel., 0296 434141; fax, 01296 29670.
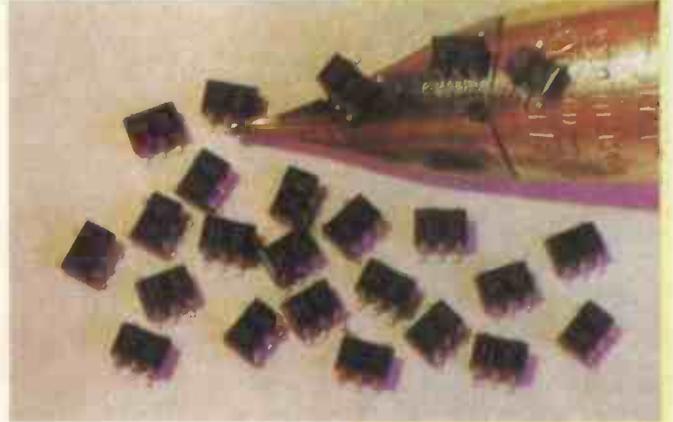
### Digital signal processors

**Two from Motorola.** New from Motorola, the *DSP56005*, a 24-bit digital signal processor with 4608-word program memory and five pulse-width modulators. These features, together with its thin quad flat pack, points the device at industrial control and magneto-optical disk drives and allows the single chip to replace two in many applications such as motor control. A peripheral-select pin eliminates external decoding logic. Also announced is a speeded-up version of the *DSP56002* 24-bit dsp, now running at 80MHz and 40Mips. Motorola Semiconductors. Tel., 01355 565000; fax, 01355 234582.

**DSP boards.** Borens offers a range of three digital signal-processing boards that use TI's *TMS320Cxx* dsp processors: *Model 250* has the 'C25; the *Model 310* the floating-point 'C31;



and the *Model 5000* with the 'C51. Each board contains the processor, analogue i/o subsystem with up to eight channels and a set of software development tools including dsp assembler, debugger and pc interface function library. Application software supplied includes data acquisition and display, FFT analysis and filtering. Borens Signal Processing. Tel., 01483 740138; fax, 01483 740136.

### Embedded processor

TI's *TMS320C57S* digital signal processor is a lower-cost version of the earlier 'LC57 and is intended for embedding into mobile radio, navigation comms equipment and similar applications. Its 40mips operating speed is combined with 7Kword of ram, a zero-overhead buffered serial port and a 'glueless' host-port interface to enable the device to handle the large amounts of data i/o for communications without overinvolving the dsp processor; it eliminates the need for the dsp cpu to service real-time data-frame interrupts from system i/o peripherals such as codecs or a-to-d converters. The device accepts both 5V and 3.3V supplies. SR Communications (Texas Instruments). Tel., 0181 692 7575; fax, 0181 692 8057.

### Linear integrated circuits

**DSL driver/receiver.** *SLIDE* by Elantec is an analogue IC meant for digital subscriber line application. It is a complete differential driver and receiver containing two twisted-pair telephone line drivers and two receiver amplifiers, and will drive differential 45V pk-pk signals at 2MHz into a 200 $\Omega$  load. Output distortion is -60dB at full 2MHz output and a typical receiver distortion is -73dB at 15Vpk-pk. Supply is  $\pm 5V$  to  $\pm 15V$ . METL. Tel., 01844 278781; fax, 01844 278746.

**2.5GHz buffer amplifier.** *RF2301* is a wide-band GaAs mesfet buffer for use

**Single-gate cmos.** Toshiba extends its series of very high-speed, low-noise cmos with the *TC7SH Logic MOS* single-gate series, comprising Nand, Nor and inverters; the USV package measures 2-by-2.1mm, 0.9mm thick. Propagation delay is 3ns and noise is the same as in slower members of the family. Input protection allows the use of 5V and 3.3V supplies without the need for voltage matching. Toshiba Electronics Europe Ltd. Tel., 001 49 211 52 96-392; fax, 001 49 211 52 96-400.

at frequencies in the 300MHz-2.5GHz range and beyond. Reverse isolation is -50dB and output power 5dBm, so that the device is useful in buffering signal sources to impedance changes or as a transmitter driver. A single 2.7-6V supply is needed and current consumption is 18mA for 17dB total gain. Anglia Microwaves Ltd. Tel., 01277 630000; fax, 01277 631111.

### Logic

**3V logic for hand-holds.** Hitachi's new high-speed 3V logic elements in the *HD74LV* range are all designed for use on 2.7-3.6V supplies and use only 20 $\mu A$  quiescent current. They complement devices in the *HD74LVC* series and can often be used with them. Zener diodes at the inputs offer protection against es discharge. Propagation delays vary in the 14-30ns range, input capacitance being under 7pF. Eiger Technologies Ltd. Tel., 01925 626626; fax, 01925 626600.


### Memory chips

**Dual fifos.** For cost and space reduction of around 50%, IDT's 18-bit *Dual Sync fifos* contain two independent devices in one package. Although independent, the fifos may be used together with no glue logic, in parallel for extra width or cascaded for more depth; packages can also be

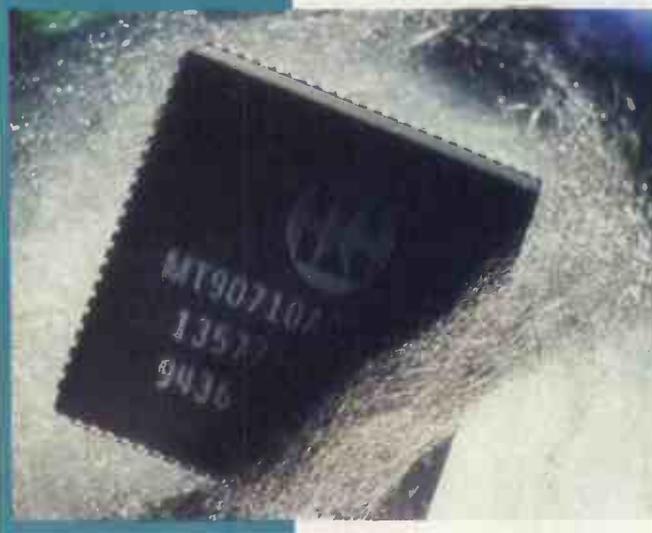
### Multiplexer links

8x2Mbit/s data nets.

Made by Mitel, the *MT90710* high-speed isosynchronous multiplexer provides point-to-point data transfer between up to eight S-bus links. These links are multiplexed onto a single 20Mbit/s line. The device connects with standard fibre-optic interfaces to form a complete photo-electric conversion circuit. Mitel Semiconductor, Tel., 01291 430000, fax, 01291 436389.



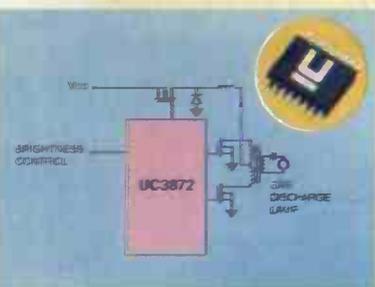Please quote "Electronics World + Wireless World" when seeking further information



**Lamp ballast controller.**

Optimised for driving cold-cathode fluorescent, neon and other gas-discharge lamps, Unirode's UCx872 series lamp-ballast ICs are resonant switching types. Since the resonant converter produces a sinusoidal lamp-drive output, switching losses and emi are minimised. Lamp intensity is adjusted via a buck regulator, synchronised to the external power stage's resonant frequency. When disabled, the device draws 1µA, making it suitable for battery-power applications. Supply for the di1, soic or plcc versions is 4.5 to 24V. Unirode, Tel., 0181 318 1431; fax, 0181 318 2549.

used in parallel or serially. Ability to store and retrieve data from two sources simultaneously makes the devices ideal for matching data rates in a multiprocessor system. Integrated Device Technology. Tel., 01372 363734; fax, 01372 378851.

**Tough memory card.** Raymond Engineering's *Sentinel* memory card is ATA PCMCIA-compatible and comes in capacities from 5Mbyte to 40Mbyte. It is hermetically sealed in a stainless-steel case and is thereby resistant to 1500g shock, 20g vibration, altitudes up to 80,000ft, humidity, immersion, condensation, temperature and emi. While the cards can be inserted into an ordinary PCMCIA slot, there is a Sentinel interface unit with a sealed access door and standard bus to provide extra security. Controller and all software is contained in the card. Ambar Components Ltd. Tel., 01844 261144; fax, 01844 261789.

**Microprocessors and controllers**

**32-bit microcontrollers.** GPS announces its range of 32-bit embedded controllers, for which it sees an immediate application in the communications field. *Butterfly*, *Spider* and *Mantis* incorporate the ARM7 risc processor core with a number of peripherals and support facilities on chip to give small, low-cost and low-power devices. Entry level to this range of livestock is the *Butterfly*, which has two uarts, a two-channel dma and a programmable interface. In addition to power management, flexible interfacing, timer/counters and programmable interrupt control. *Spider* also offers an on-chip V.2.1 PCMCIA slave interface, a four-channel dma controller with

programmable source and destination devices and a uart. Most extensive is the *Mantis*, which is *Spider*-like except that it has a 16bit peripheral interface and two uarts. There is a new software development toolkit and the first fully Windows-based debugger for the ARM processor, common to all three. Operating speeds are 15-30MHz, depending on type and voltage supply. GEC Plessey Semiconductors Ltd. Tel., 01793 518510; fax, 01793 518582.

**Bright Sparc.** When this appears, Sun is due to have its *UltraSPARC* risc processor available in quantity. The new 64-bit chip runs at 143MHz and 167MHz and has on-chip multimedia support. Its data throughput is 1.3Gbyte/s and the Visual instruction set allows it to run at 1.67Gop/s. Texas Instruments make the device, which is packaged in a 521-pin ball grid array. Sun Microsystems Ltd. Tel., 01276 451440; fax, 01276 451287.

**3D graphics.** Yamaha's YGV612 (RPA2) is a 3D graphics device that supports full texture mapping at 150Kpolygons/s for 3D, 50-pixel triangles and which will allow complete 3D accelerator boards to be sold for under £200. This is the second device in the *Virtuality* series and has dram frame buffer support, a glueless PCIbus interface and a 30MHz video d-to-a converter. It is compatible with Yamaha's earlier rendering polygon accelerator, the YGV611, and performs Gouraud shading, hidden surface removal, video capture and bit block transfer. Polar Electronics. Tel., 01525 377093; fax, 01525 378367.

**Pentium for portables.** Intel introduces the 90MHz *Pentium Processor Mobile Advantage*, intended for use in notebook and smaller computers, with a 3.3V interface to the outside world and 2.9V internal operation. Features include a package 'thinner than a dime', however thin that is, and an on-chip power-down circuit to rest the cache and floating-point unit when they are not needed. Intel Corporation UK Ltd. Tel., 01793 696000; fax, 01793 430763.

**Oscillators**

**Controlled-crystal oscillators.** M-tron's *MTET-1* is a ±1ppm oscillator responding to an external frequency control voltage. For an input of 0-5V, frequency varies by 5ppm in the frequency range 10-20MHz. Output is ttl/cmos-compatible and required power either 5V or 12V. Shielding by an all-metal welded case minimises radiation. Semi-Dice (UK) Ltd. Tel., 01494 714010; fax, 01494 712400.

**Programmable logic arrays**

**MAX developments.** Altera's MAX 7000S family of programmable logic devices is compatible in pinout and programming files with MAX 7000/7000E families, but now has in-system programming and JTAG

boundary-scan testing. In-system programming eliminates the handling of devices during programming, since they can be board mounted in the normal way and programmed *in situ* with no risk of lead damage; the process of up-grading the design is also eased. Altera UK Ltd. Tel., 01628 488811; fax, 01628 890078.

**Power semiconductors**

**Power mosfets.** Power mosfets made by IXYS can now be specified in TO-247, which allows the devices to be surface-mounted to a pcb, having gull-wing leads and also the back of the package plated with lead/tin matte finish. Currently, there are three mosfets and four igbts with this option, denoted by an 'S' after the number. IXYS Corporation. Tel., (USA) 001 408 982 0700; fax, 001 408 496 0670.

**PASSIVE**

**Communications equipment**

**Telephone chip.** An fsk demodulator, the *Exar 2211*, is used by Nortel in a new telephone offering multistandard calling line identification. The *C9316* telephone has an lcd to guide the

**Rf/microwave test set.** Portable rf and microwave test sets by Marconi Instruments in the 6200B series are developed from the 6200A instruments and are meant for use by field engineers working on mobile and cellular radio antennas and associated links - a situation in which the ability of the 6200B MTS to measure both return loss and real-time fault location to within 0.1% of the distance range is of particular value. New on these instruments is the 6240 fault locator which measures return loss and location from a single port. Features of the instrument include a scalar network analyser, a synthesised sweep generator, power meter and frequency counter. Frequency coverage of the five instruments in the series is 10MHz-40GHz. Up to 200 traces can be stored on a 3.5in dos-compatible disk for later import to a pc. Marconi Instruments Ltd. Tel., 01727 859292; fax, 01727 857481.

user through call logging, call duration timing and incoming caller's name and number. Using the Exar chip has allowed the identification process to be held in software, simplifying the telephone hardware and rendering it compatible with all known international standards. Nortel Europe. Tel., 0162 8812050.

**Connectors and cabling**

**Dimm sockets.** Dual-in-line memory-module sockets from Robinson Nugent use a dual readout format to give an effective doubling of package density in a single-density area, a form used in workstations but not, until now, in pcs. Features include 60-cycle life, vertical entry, resistance to shock and vibration and a method of ejecting the modules. The 8byte socket has 168 positions and keying for 3.3V and 5V srams and drums. Robinson Nugent (Europe) Ltd. Tel., 01256 842626; fax, 01256 842673.

**Displays**


**High-temp., high duty-ratio lcds.** GEC-Marconi's Hirst-LCD has been able to combine a duty ratio of 1:240 with an 80°C operating temperature in new stn lcds to make them usable for military, automotive and outdoor use. These displays use the company's 270° twist technique to give high contrast and wide viewing angle. GEC-Marconi Materials Technology Ltd. Tel., 01327 350581; fax, 01327 353410.

**Stn colour displays.** Sanyo has a range of colour and monochrome supertwist nematic lcds, using chip-on-glass and chip-on-board techniques. *LMCF53/G53* are 11.4in and 14in vga colour modules, *LMFK53* is a 10.3in replacement with 800-by-600 resolution for pcs and *LMAE55* is a 9in vga monochrome type. All these dual-scan displays give high brightness and use a low-power backlight, the colour models having colour filters for better contrast and viewing angle. Anders Electronics plc. Tel., 0171 3887171; fax, 0171 3872951.

**Pcb indicators.** Three leds in one housing save board space and provide a more consistent alignment than separate leds. Dialight's *570 Series* uses three 2mm leds in red, green or yellow, and the 6.84mm distance from front to first lead conforms to DIN 41494. Viewing angle is ±19° and the units are in black epoxy to improve contrast.



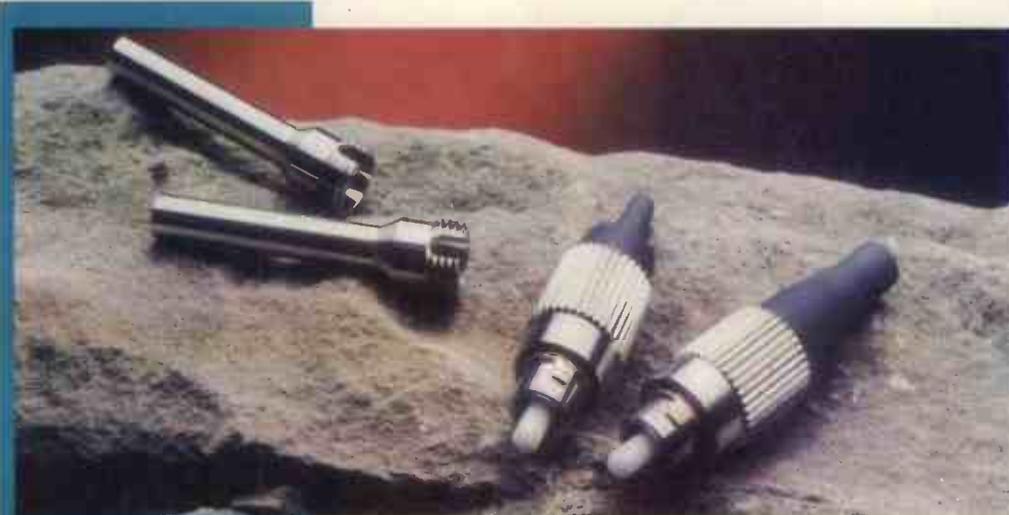Please quote "Electronics World + Wireless World" when seeking further information



**Optical-fibre connector.** Transradio announces the *FCPC monobloc*, a one-piece optical-fibre connector combining easy termination and a tuning optimisation facility. Connectors come fully assembled with the specified optical ferrule. Cable retention is provided by a standard crimp on the aramid yarn. Cable assemblies by Transradio's termination facility offer <math>< 50\text{dB}</math> reflectance and <math>< 0.15\text{dB}</math> insertion loss. Transradio Ltd. Tel., 0181 997 8880; fax, 0181 997 0116.

Operating frequency for all three filters is 0-400Hz. BLP Components Ltd. Tel., 01638 665161; fax, 01638 660718.

### Hardware

**Screened racks.** Barton's range of screened racks is extended to include a unit with a -70dB performance at 1GHz. It takes internal rack fittings from most rack component makers, meeting EMC regulations comfortably. Largest is a 42-unit 19in model and there are standard fan tray mountings, ventilation, castors or adjustable feet and, as options, glass doors and a two-tone finish. Barton Engineering and Export Ltd. Tel., 01227 272141; fax, 01227 771653.

loads when driven by the outputs of 8 or 16-bit microprocessors, primarily in avionics equipment; wire links configure the device for Intel or Motorola processors. Outputs drive at least two 40mA incandescent lamps and higher loads are possible by



**Clamp-on induced current meter.** HI-3702 *Clamp-on Induced Current Meter* by Holaday measures rf induced current in ankles and arms in the 3kHz-110MHz range at 1mA-1A, complying with ANSI C95 1-1992. To avoid perturbing the rf field, the readout and control unit is coupled by optical fibre and can be held in a belt case for hands-free use. It is intended for measurements in rf welding, induction heating, broadcast and aerial locations. Holaday Industries. Tel., 01628 478155; fax, 01628 476781.

### Instrumentation

**Camera testing.** Optest VT-C1 from the Israeli company Genop is a modular, computer-controlled test station for the electronic and optical testing of camera systems, including monochrome and colour video, intensified ccds and slow-scan ccds, using a uniform light source and calibrated reticle in an enclosure. Computer control using the Windows-based software supplied provides automatic, integrated performance of a set of complex tests that usually require many separate instruments and do not give the documentation and analysis this system provides. Optilas Ltd. Tel., 01908 221123; fax, 01908 221110.

**Semiconductor tester.** Now in its fifth generation, Testronics's 201C *Discrete Semiconductor Test System* is mainly intended for use in manufacturing. Depending on device type and test parameters, throughput is 3-10 times faster than in earlier instruments, a new 16bit data converter and a new Windows-based programming language being responsible for the speed increase. Instrumentation Test & Measurement Ltd. Tel., 01202 872771; fax, 01202 871052.

### Interfaces

**Avionics switching interface.** DDL's DD-01616 consists of 16 circuits switching lamp, solenoid or actuator

paralleling the switches; lamp life is extended by the controlled turn-on/off times. Short-circuit protection copes with inrush current but trips on working overcurrent, and comparators sense overcurrent or absence of current. Data Device Corporation. Tel., 01635 40158; fax, 01635 32264.

**Network interface.** A 16-bit Ethernet 10Base2/BNC adaptor card from MPS is for use with PC XT/AT computers and is Novell NE2000 Ethernet adaptor-compatible. It has a BNC connector for the thin coaxial Ethernet interface and 15-pin D connector for AUI interface so that any Ethernet segment may be connected by means of an external transceiver. MPS Electronics. Tel., 01702 554171; fax, 01702 553935.

### Literature

**Allegro/Sanken.** Allegro Microsystems Europe has a 16-page short catalogue listing Allegro and Sanken semiconductors. Allegro's mixed-signal devices and Sanken's power ICs and discrete components are all listed and categories include regulators and power management, leds, diodes, power devices, motor

**Dual-measurement dmm.** Model 1705 from Thurlby Thandar is a bench digital multimeter that allows the measurement of two different signals simultaneously. There are both main and secondary displays: the latter is used to show the secondary range in addition to the measurement units; to display a measurement in two different units such as volts and dBm; to display the result of a calculated function; measuring and displaying two aspects of one signal such as alternating and direct voltage; and measuring and displaying two different signals. Basically, the instrument is a 4.5-digit multimeter showing 10,000 counts and with a resolution of 10 $\mu$ V, 10m $\Omega$  and 0.1 $\mu$ A. Autoranging is used on most functions with manual selection if required. Response to ac is true rms and the attenuator is highly accurate in the audio band, giving wide-band response to prevent errors when measuring switching waveforms. Many calculated functions are provided and there is a 100-step data logger. Thurlby Thandar Instruments Ltd. Tel., 01480 412451; fax, 01480 450409.



Dialight. Tel., 01638 662317; fax, 01638 560455.

**SVGA lcd.** Toshiba's LTM10C035 is a liquid-crystal display to svga resolution of 800-by-600 pixels and measuring 10.4in diagonally. The active-matrix thin-film transistor technique gives a pixel size of 0.264 by 0.264mm and a response time of 50ms. An internal oxide layer and anti-glare surface improve contrast and cut reflection to 2% at a 550nm wavelength. A single fluorescent lamp takes only 3.5mA. Toshiba Electronics Europe Ltd. Tel., 001 49 211 52 96-392; fax, 001 49 211 52 96-400.

**800 by 600 lcd.** For its P1000 series of 100MHz Pentium notebooks, Tadpole Technology has introduced the option of an active-matrix, thin-film transistor display supporting 800-by-600 graphics. The P1000G, for example, combines the 256-colour display, the Pentium, 256K second-level cache and 128Mbyte of memory, to run applications such as cad, modelling and multimedia, normally found on desk-top equipment. Tadpole Technology. Tel., 01223 428200; fax., 01223 428201.

### Filters

**Emc filter.** Pcb-mounted mains filter by Belling Lee, the SF3010, is a compact device handling up to 250Vac at 1A, 2A or 6A and measuring 20-by-25 by 25mm.

Please quote "Electronics World + Wireless World" when seeking further information

drivers and sensors. Allegro MicroSystems Inc. Tel., 01932 253355; fax, 01932 246622.

**Automotive semiconductors.** Toshiba offers a brochure on semiconductor devices for the automotive industry, including controllers, bipolar devices, lgbtbs and power modules, logic, diodes, leds and optical-fibre connectors. Toshiba Electronics UK Ltd. Tel., 01276 694600; fax, 01276 694800.

**Switches.** Switches by the C&K Clayton/Unimax division are described in a new catalogue from Roxburgh. In 220 pages, the publication covers additions to the range such as camlocks, switchlocks and rotary, rocker, pushbutton and slider types, most being approved and certified by the relevant authorities. A section on the possible combinations of features, 'Build-a switch', is included, complete with specifications, materials, drawings and ratings. Roxburgh Electronics Ltd. Tel., 01724 281770; fax, 01724 281650.

BLP. Crellon can let you have a 22-page catalogue of the offerings

available from BLP Components, including Belling Lee filters, connectors and fuses; PED solenoids and relays; and Dialight optoelectronics products. Gothic Crellon Ltd. Tel., 01734 788878; fax, 01734 776095.

**Pcb repair.** A manual on the repair and rework of printed-circuit boards by Circuit Repair Corp. is available from Intertronics. In more than 200 pages, it describes step-by-step procedures, base material and conductor repair and rework and plated-through hole repair. The work also comes on floppy disk in AmiPro and Word. Price for the manual is £44; for the disk, £444. Intertronics Ltd. Tel., 01865 842842; fax, 01865 842172.

**Subminiature switches.** Cherry has a brochure describing a range of small switches for low-power circuits, the *Type DB*. They conform to DIN 41636 sizes and come in normally open, normally closed or changeover form, versions handling 5A or 10A at 250Vac and 0.1A at 125Vac. Various actuators are available, including rollers, as are terminal types, and contacts are in silver/nickel or gold crosspoint. Cherry Electrical Products Ltd. Tel., 01582 763100; fax, 01582 768883.

**Production equipment**

**Lead-forming tool.** Fancort Industries offers the *F-1F/2FLEX* two-sided universal gull-wing lead former for surface-mounting flatpacks and quadpacks to any footprint, controlling the finished stand-off height to within ±0.002in. All dimensions, such as foot length, shoulder length and radii are adjustable and the tool fits the Fancort *5000-1* floating anvil press which uses an electronic system to maintain stand-off height. The tool handles both sides of a component simultaneously and, as an option, there is a loader. Production Equipment Sales Ltd. Tel., 01323 811694; fax, 01323 811528.

**Power supplies**

**Power trays.** *PT series* 19-in power trays by XP are improved and extended. They provide completely packaged power for all XP supplies and dc-to-dc converters in heights from 1U in 360 or 500mm depths. Many combinations of ac and/or dc input can be accommodated, depending on the selection of psu or converters and many combinations of output to customer requirements. XP plc. Tel., 01734 845515; fax, 01734 843423.

**3V regulators.** Allegro's *A818x* series of low drop-out voltage regulators now contains devices with a fixed 3V output giving up to 150mA at an input/output differential of under 150mV. Current used in the device itself is 65µA normally, 1µA when sleeping. Rated input is 0-10V, over which range stabilisation is within 30mV. Thermal protection is provided and there is a ttl-compatible enable



**OS9-to-pc link.** Version 3 of BVM's *Pclink* enables full two-way transparent network access with on-the-fly conversion and resource sharing between OS-9 real-time machines and pcs running under dos or windows. A main advantage is that OS-9 developers can make use of the well established text editors and compilers available for windows. One new feature is OS-9 access to network file servers by linking into a client pc then communicating transparently with the server using normal pc networking software. Print spooling is also supported. BVM, Tel., 01489 783589, fax, 01489 780144.

input. Flint Distribution. Tel., 01530 510333; fax, 01530 510275.

**SM dc-to-dc converters.** Calex has a range of surface-mounted dc-to-dc converters handling up to 15W. *SD* single-output series of units gives 5V and 3.3V output from inputs of 6.5-15.5V dc and 4.5-6V dc. Output noise is under 40mVpk-pk, Stabilisation 1.7% and regulation 0.2%. The units occupy 2-by-0.75in, and are 0.5in high. Calex Electronics Ltd. Tel., 01525 373178; fax, 01525 851319.

**Switches and relays**

**Current trip amplifier.** Foxtam Controls offers the *11WRI/T* 1-20mA trip amplifier, which provides trip current monitoring with or without latching. It is in a plug-in housing, which also carries separate trip-level and hysteresis controls, relay status indication and adjustable start-up inhibit delay timer. Models to suit a range of ac supplies are available. Foxtam Controls Ltd. Tel., 0161 626 5316; fax, 0161 627 0929.

**Transducers and sensors**

**Shaft encoder.** Low-cost shaft encoders from Control Transducers, the *DP* series are easy to install devices for use as feedback and positioning controls in industrial

machinery. The 16 models in the series are non-contacting, optical types with resolutions from 96 to 2048 lines per revolution. Diameter is from 1in, mounting is by a single hole and the units are of low torque design, coping with continuous speeds of up to 10,000rev/min. Optional accessories include a line driver, cables, a variable power supply and various ICs. Control Transducers. Tel., 01234 217704; fax, 01234 217083.

**Thermal imaging.** Vero's *Thermochromic Heat Imaging* board provides a hardware method of determining a system's thermal characteristics, rather than software modelling. Boards coated with thermal ink are placed in a slot or near the object of interest, different colours appearing at various temperatures, a detectable change in colour occurring every 1°C. Eurocard, Futurebus and a universal size are available and there is a transparent front panel. In popular sizes to allow the realistic airflow while the boards are examined. Electrospeed. Tel., 01703 644555; fax, 01703 610282.

**Tilt sensor.** Using the force-balance principle, the *ES-256 Series* of inclinometers from Control Transducers is both extremely accurate and resistant to hostile conditions. Linear output of ±5V over full-scale ranges from ±5.75° to ±90° needs a single 10.5-28V supply, non-linearity being ±0.05%, repeatability ±0.005%, resolution 0.001% and operating temperature -40°C to 85°C. A stainless steel case protects the instruments and there is a variety of damping, insulation and connection options. Control Transducers. Tel., 01234 217704; fax, 01234 217083.

**Data communications**

**PCI data highway.** Myriad Solutions announces the *Q-Card*, which uses the National Semiconductor *QuickRing* data streaming controller to provide a peak data rate between nodes of 200Mbyte/s and will receive



**Remote switching.** Transmitter and receiver modules by Wood and Douglas allow up to ten different functions, such as lighting, irrigation, alarms, to be controlled over radio links of up to 15km. The *RTC450* 500mW transmitter has a four or ten function relay controller and is normally fitted with a quarter-wave antenna, with other types as options. Data receiver *RRC450* has the corresponding number of contacts rated at 1A at 240V ac. Both units are in Surtel-type enclosures, protected to IP65 standard. Supply is 12Vdc at 150mA. Wood and Douglas Ltd. Tel., 01734 811444; fax, 01734 811567.

and transmit data at the PCbus limiting bandwidth of 132Mbyte/s as either PCI master or slave. Cards plug into any PCI-based computer and give a means of linking computers to other computers and peripherals. Software to allow the cards to be incorporated into applications is provided. Myriad Solutions. Tel., 01223 421181; fax, 01223 421228.

**Power-line transformers.**

Transformers by Etal in the P28xx range have been designed for use in the linking of equipment that uses the mains wiring to carry high-frequency signals. Transformers for this duty have not commonly been made to close tolerance, with the result that the electronics has had to cope expensively with the variations. These


transformers are more closely controlled and cover four bands between 40kHz and 148.5kHz, each conforming to EN60950 and EN50065-1. Etal Electronic Techniques Ltd. Tel., 01473 611422; fax, 01473 611919.

# COMPUTER

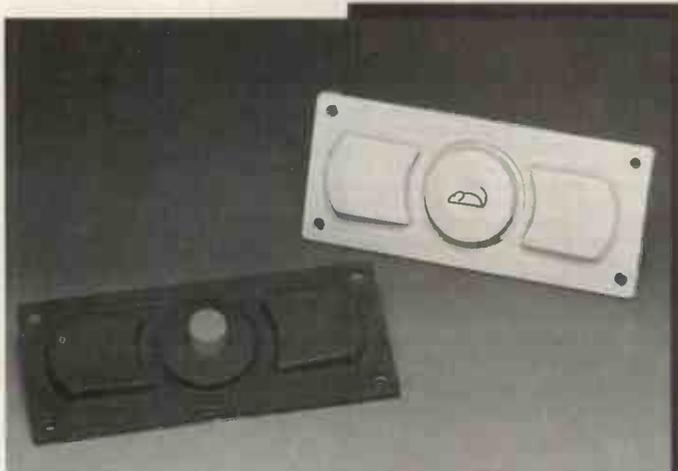**Software**

**Data acquisition.** Additions to Amplicon's *LABTech Notebook* to make version 8 are operation under windows, FFT analysis of real and complex waveforms, real-time vision gui and sound support and interfacing to spreadsheets by dde or streaming to hard disk at up to 1MHz. Flexibility in the software is preserved from earlier versions and remote control over networks is a feature: for example, Notebook can be run on one machine and be controlled and have its output monitored on another. Amplicon Liveline Ltd. Tel., 0800 525 335 (free); fax, 01273 570215.

**Dsp development.** *DSP Blockset* by Cambridge Controls is claimed to be the first to combine dsp algorithm development with real time prototyping and implementation. It is an extension of the *Simulink* non-linear simulator and is used with the *Matlab* environment. There is a library of over 100 basic dsp operations and the software converts point-by-point data samples to data vectors. An optional feature converts block diagrams to portable, ANSI C code to run on any programmable floating-point dsp equipment. The package runs on 486 pcs under windows, on Mac 68000 and *Power Macs* and on most Unix workstations. Cambridge Control Ltd. Tel., 01223 423200; fax, 01223 423255.



**Telecoms simulator.** *Saber Telecommunications Simulation Package* combines a library of telecoms building blocks with the latest version 3.4 of the *Saber* mixed-signal simulator to form a design and analysis tool for people working on analogue and digital cellular and landline systems. Component models and templates are programmable in MAST, *Saber's* own language, and can be enhanced or used as a starting point for a user's own model, models in C, Fortran and Spice also being usable. For analysis, *Saber* now includes features such as Smith and Nichols chart display and eye diagrams to show digital signal degradation. Analogy Europe. Tel., 01793 432286; fax, 01793 488098.


**EMI analysis.** Version 2.0 of *Quiet*, the electromagnetic interference analysis tool by Quad Design, is now available. Predicting electric and magnetic field intensities from boards, the package now includes a 3-D simulation engine to provide better

**Sealable mouse.** With a mounting depth of only 6mm, *Interlink's MicroModule* mice are sealable and suitable for industrial applications and heavily used commercial environments such as information kiosks. There are two options, one providing button cursor pointing control, the other with a mini joystick. Both versions offer two-button click control. *Interlink Electronics*, Tel., 805 484 8855, fax, 805 484 8989.

simulation of, for example, common-mode current and radiation in cables. Further, since the use of multiple boards distorts the predicted performance of a single one, a new facility predicts the effects of shielding and scattering for the whole structure. The package also handles enclosure resonance. *Quad Design*. Tel., 01344 306166; fax, 01344 304747.

**Notepads.** As a replacement for sticky bits of yellow paper, *ScreenMagic* offers *Stick-ups*, which is a note-taking and keeping facility for windows. It has a great number of clever features, one of which is voice entry, assuming you have bought the sound card and microphone. Drag-and-drop is operative, so that notes can be attached to other documents, and an instant save feature avoids the need to type file names. Additionally, alarms will wake you up at meeting time or provide 'continuous animated reminders'. *Guildsoft Ltd.* Tel., 01752 895100; fax, 01752 894833.

**Fuzzy toolkit HI-FLAG** is a development toolkit for fuzzy logic from the Swiss company *Hiware AG*. Design, simulation and debugging elements of the development have a graphic user interface and fuzzy objects – the variables and inference objects – are freely movable in the screen design area, properties being edited by double-clicking and groups of objects being placed in different debugging windows to make create methods. The simulator allows any input function to be mapped into the system and simulated and complex fuzzy systems can be designed by integrating non-fuzzy functions into the fuzzy design. Output is C or optimised assembler code for the target processor – for the *68HC16* now and then for all *Motorola* mcu series of embedded controllers. *Pentica Systems Ltd.* Tel., 01734 792101; fax, 01734 774081.

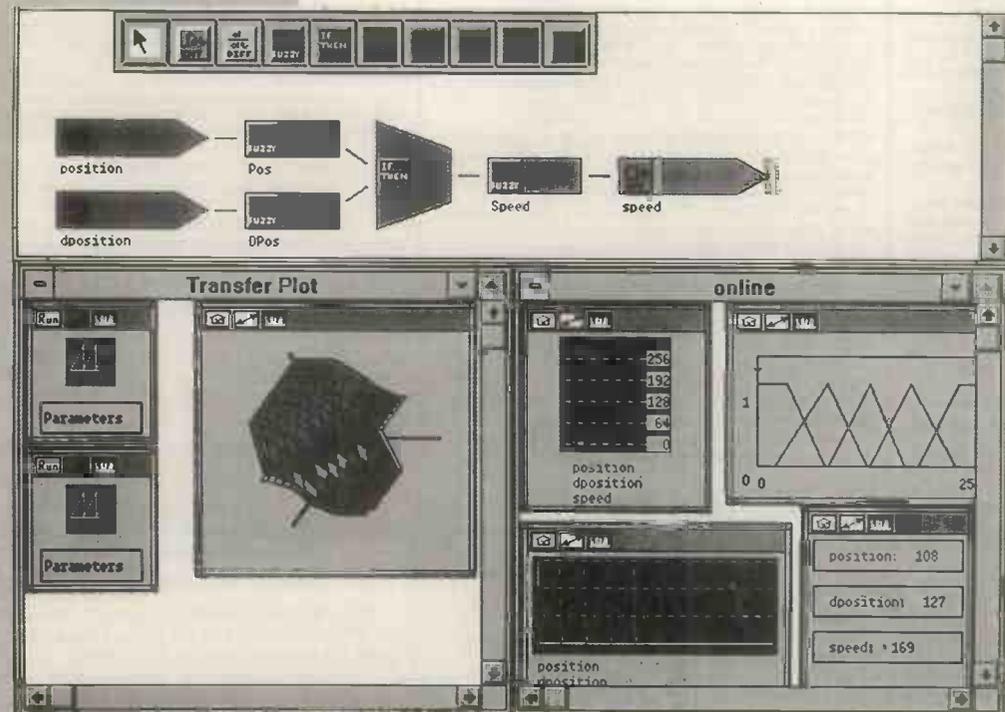

# BULL CLEAROUT SALE

**WIRELESS VIDEO BUG KIT** Transmits video and audio signals from a miniature CCTV camera (included) to any standard television! All the components including a PP3 battery will fit into a cigarette packet with the lens requiring a hole about 3mm diameter. Supplied with telescopic aerial but a piece of wire about 4" long will still give a range of up to 100 metres. A single PP3 will probably give less than 1 hours operating time. £99 REF EP79. (probably not licensable!)

**GOT AN EXPENSIVE BIKE?** You need one of our bottle alarms, they look like a standard water bottle, but open the top, insert a key to activate a motion sensor alarm built inside. Fits all standard bottle carriers, supplied with two keys. SALE PRICE £7.99 REF SA32.

**GOT AN EXPENSIVE ANYTHING?** You need one of our cased vibration alarms, keyswitch operated, fully cased just fit it to anything from videos to caravans, provides a years protection from 1 PP3 battery, UK made. SALE PRICE £4.99 REF SA33.

**DAMAGED ANSWER PHONES** These are probably beyond repair so they are just £4.99 each. Mainly response 200 machines. REF SA30.

**COMMODORE GAMES CONSOLES** Just a few of these left to clear at £5 ref SA31. Condition unknown.

**COMPUTER DISC CLEAROUT** We are left with a lot of software packs that need clearing so we are selling at disc value only! 50 discs for £4, that's just 8p each (our choice of discs) SALE PRICE £4 REF EP66

**IBM PS2 MODEL 160Z CASE AND POWER SUPPLY** Complete with fan etc and 200 watt power supply. SALE PRICE £9.95 REF EP67

**DELL PC POWER SUPPLIES** 145 watt, +5, -5, +12, -12, 150x150x85mm complete with switch, flyleads and IEC socket. SALE PRICE £9.99 ref EP55

**1.44 DISC DRIVES** Standard PC 3.5" drives but returns so they will need attention SALE PRICE £4.99 ref EP68

**1.2 DISC DRIVES** Standard 5.25" drives but returns so they will need attention SALE PRICE £4.99 ref EP69

**PP3 NICADS** New and unused but some storage marks. SALE PRICE £4.99 ref EP52

**SOLAR PANELS** 3v output with two flyleads, 100x60 mm pack of 10 SALE PRICE £8.99 ref EP56

**DELL PC POWER SUPPLIES** (Customer returns) Standard PC psu's complete with fly leads, case and fan, pack of two psus SALE PRICE £5 FOR TWO!! ref EP61

**GASHOBS AND OVENS** Brand new gas appliances, perfect for small flats etc. Basic 3 burner hob SALE PRICE £24.99 ref EP72. Basic small built in oven SALE PRICE £79 ref EP73

**BITS AND BOBS** We have a quantity of cased modems, multiplexers etc different specs but ideal strippers. SALE PRICE £4 each ref EP63

**RED EYE SECURITY PROTECTOR** 1,000 watt outdoor PIR switch SALE PRICE £9.99 ref EP57

**ENERGY BANK KIT** 100 6"x6" 6v 100mA panels, 100 diodes, connection details etc. £69.95 ref EP112.

**CCTV CAMERA MODULES** 46X70X29mm, 30 grams, 12v 100mA, auto electronic shutter, 3.6mm F2 lens, CCIR, 512x492 pixels, video outputs 1v p-p (75 ohm). Works directly into a scart or video input on a tv or video. IR sensitive. £79.95 ref EP137.

**IR LAMP KIT** Suitable for the above camera enables the camera to be used in total darkness! £5.99 ref EP138.

**PASTEL ACCOUNTS SOFTWARE**, does everything for all sizes of businesses, includes wordprocessor, report writer, windowing, networkable up to 10 stations, multiple cash books etc. 200 page comprehensive manual, 90 days free technical support (0345-326009 try before you buy!) Current retail price is £129, SALE PRICE £9.95 ref SA12. SAVE £120!!

**MINI MICRO FANS** 12V 1.5" sq SALE PRICE £2. Ref SA13.

**REUSEABLE HEAT PACKS**. Ideal for fishermen, outdoor enthusiasts elderly or infirm, warming food, drinks etc, defrosting pipes etc. reusable up to 10 times, lasts for up to 8 hours per go, 2,000wh energy, gets up to 90 degC. SALE PRICE £9.95 REF SA29

**12V ZAMP LAPTOP** psu's 110x55x40mm (includes standard IEC socket) and 2m lead with plug, 100-240v IP. SALE PRICE £6.99 REF SA15.

**PC CONTROLLED 4 CHANNEL TIMER** Control (on/off times etc) up to 4 items (8A 240v each) with this kit. Complete with software, relays, PCB etc. £25.99 REF 95/26

**COMPLETE PC 300 WATT UPS SYSTEM** Top of the range UPS system providing protection for your computer system and valuable software against mains power fluctuations and cuts. New and boxed, UK made Provides up to 5 mins running time in the event of complete power failure to allow you to run your system down correctly. SALE PRICE JUST £99.00.

**SOLAR PATH LIGHTS** Low energy walklights powered by the sun built in PIR so they work when you walk past. Includes solar panel & rechargeable bat. SALE PRICE £19.99 REF EP62

**BIG BROTHER PSU** Cased PSU, 6v 2A output, 2m o/p lead, 1.5m Input lead, UK made, 220v. SALE PRICE £4.99 REF EP7

**WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA?** We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is a certificate enabling you to reproduce the manuals as much as you like! SALE PRICE £14 REF EP74

**RACAL MODEM BONANZA!** 1 Racal MPS1223 1200/75 modem, telephone lead, mains lead, manual and comms software, the cheapest way onto the net all for just £13 ref DEC13.

**3mw LASER POINTER**. Supplied in kit form, complete with power adjuster, 1.5mw and beam emergence adjuster. Runs on 2 AAA batteries. Produces thin red beam. Ideal for levels, gun sights, experiments etc. Cheapest in the UK! Just £39.95 ref DEC48 TRADE PRICE £28 MIN 10 PIECES

**RADIO PAGERS** Brand new, UK made pocket pagers clearance price is just £4.99 each 100x40x15mm packed with bits! Ref SEP5.

**BULL TENS UNIT** Fully built and tested TENS (Transcutaneous Electrical Nerve Stimulation) unit, complete with electrodes and full instructions. TENS is used for the relief of pain etc in up to 70% of sufferers. Drug free pain relief, safe and easy to use, can be used in conjunction with analgesics etc. £49 Ref TEN/1

**COMPUTER R8232 TERMINALS. (LIBERTY)** Excellent quality modem units, (like wyse 50,s) 2xRS232, 20 function keys, 50 thro to 38,400 baud, menu driven port, screen, cursor, and keyboard setup menus (18 menu's). £29 REF NOV4.

**PC PAL VGA TO TV CONVERTER** Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and s/ware. Ideal for laptops or a cheap upgrade. Supplied in kit form for home assembly. SALE PRICE £25 REF SA34

**EMERGENCY LIGHTING UNIT** Complete unit with 2 double bulb floodlights, built in charger and auto switch. Fully cased, 6v 8AH lead acid req'd. (secondhand) £4 ref MAG4P11.

**SWINGFIRE GUIDED MISSILE WIRE**. 4,200 metre reel of ultra thin 4 core insulated cable, 28lbs breaking strain, less than 1mm thick! Ideal alarms, intercoms, fishing, dolls house's etc. SALE PRICE £13.99 ref EP51

**ELECTRIC CAR WINDOW DE-ICERS** Complete with cable, plug etc SALE PRICE JUST £4.99 REF SA28

**ASTEC SWITCHED MODE PSU** BM41012 Gives +5 @ 3.75A, +12 @ 1.5A, -12 @ 4A. 230/110, cased, BM41012. £5.99 ref AUG6P3.

**AUTO SUNCHARGER** 155x300mm solar panel with diode and 3 metre lead fitted with a cigarr plug. 12v 2watt. SALE PRICE £8.99 REF SA25.

**TOP QUALITY CENTRIFUGAL MAINS MOTORS SALE PRICE 2 FOR JUST £2.60 REF SA38**

**ECLATRON FLASH TUBE** As used in police car flashing lights etc, full spec supplied, 60-100 flashes a min. SALE PRICE £8.99 REF SA15.

**24v AC 96WATT** Cased power supply. New. SALE PRICE JUST £9.99 REF SA40

**MILITARY SPEC GEIGER COUNTERS** Unused anstraightfrom Her majesty's forces. SALE PRICE £44 REF SA16

**MICRODRIVE STRIPPERS** Small cased tape drives ideal for stripping, lots of useful goodies including a smart case, and lots of components. SALE PRICE JUST £4.99 FOR FIVE REF SA26

**SOLAR POWER LAB SPECIAL** You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit SALE PRICE JUST £4.99 REF SA27

**RGB/CGA/EGA/TTL COLOUR MONITORS** 12" in good condition. Back anodised metal case. SALE PRICE £49 REF SA16

**SWITCHED MODE PSU** ex equip, 60w +5v @ 5A, -5v @ 5A, +12v @ 2A, -12v @ 5A 120/220v cased 245x88x55mm IEC input socket £6.99 REF MAG7P1

**PLUG IN ACORN PSU** 19v AC 14w, £2.99 REF MAG3P10

**POWER SUPPLY** fully cased with mains and o/p leads 17v DC 900mA output. Bargain price £5.99 ref MAG6P9

**ACORN ARCHIMEDES PSU +5v @ 4.4A.** on/off sw uncased, selectable mains input, 145x100x45mm SALE PRICE £4.99 REF SA1

**13.8V 1.9A psu** cased with leads. Just £9.99 REF MAG10P3

**PPC MODEM CARDS**. These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud dial up unit complete with leads. Clearance price is £5 REF: MAG5P1

**200 WATT INVERTER** Converts 10-15v DC into either 110v or 240v AC. Fully cased 115x36x156mm, complete with heavy duty power lead, cigarr plug, AC outlet socket. Auto overload shutdown, auto short circuit shut down, auto input over voltage shutdown, auto input under voltage shut down (with audible alarm), auto temp control, unit shuts down if overheated and sounds audible alarm. Fused reversed polarity protected, output frequency within 2%, voltage within 10%. A well built unit at a keen price. Just £64.99 ref AUG65.

**UNIVERSAL SPEED CONTROLLER KIT** Designed by us for the C5 motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

**COMPUTER COMMUNICATIONS PACK** Kit contains 100m of 6 core cable, 100 cable clips, 2 line drivers with RS232 interfaces and all connectors etc. Ideal low cost method of communicating between PC's over a long distance. Complete kit £8.99.

**ELECTRIC MOTOR KIT** Comprehensive educational kit including all you need to build an electric motor. £9.99 ref MAR10P4.

**VIEWDATA SYSTEMS** made by Phillips, complete with internal 1200/75 modem, keyboard, psu etc RGB and composite outputs, menu driven, autodialler etc. SALE PRICE £12.99 REF SA18

**AIR RIFLES .22As** used by the Chinese army for training purposes, so there is a lot about! £39.95 Ref EF78. 500 pellets £4.50 ref EF80.

**PLUG IN POWER SUPPLY SALE FROM £1.60** Plugs in to 13A socket with output lead, three types available, 9vdc 150mA E1.50 ref SA19, 9vdc 200mA E2.00 ref SA20, 6.5vdc 500mA E2 ref SA21.

**VIDEO SENDER UNIT**. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £15 REF: MAG15 12v psu is £5 extra REF: MAG5P2

**\*SOME OF OUR PRODUCTS MAY BE UNLICKENSABLE IN THE UK**

## BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.  
BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE  
WITH ORDER PLUS 43 POST PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERY PHONE ORDERS  
WELCOME FACIES VISA, SWITCH, AMERICAN EXPRESS

TEL: 01273 203500

FAX 01273 323077

**\*FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

**\*MINIATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range up to 2kmin open country. Units measure 22x52x155mm. Including cases and earp'ces. 2xPP3 req'd. £30.00 pr. REF: MAG30

**FUTURE PC POWER SUPPLIES** These are 295x135x60mm, 4 drive connectors 1 mother board connector. 150watt, 12v fan, IEC inlet and on/off switch. SALE PRICE £7.99 REF SA 22

**\*FM TRANSMITTER KIT** housed in a standard working 13A adapter! the bug runs directly off the mains so lasts forever why pay £700? or price is £15 REF: EF62 Transmits to any FM radio (this is in kit form with full instructions.)

**\*FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

**TALKING COINBOX STRIPPER COMPLETE WITH COIN SLOT MECHANISMS** originally made to retail at £79 each, these units are designed to convert an ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? SALE PRICE JUST £2.50 REF SA23

**GAT AIR PISTOL PACK** Complete with pistol, darts and pellets £12.95 REF EF82 extra pellets (500) £4.50 ref EF80.

**6"x12" AMORPHOUS SOLAR PANEL** 12v 155x310mm 130mA. SALE PRICE £4.99 REF SA24.

**FIBRE OPTIC CABLE BUMPER PACK** 10 metres for £4.99 ref MAG5P13 Ideal for experimenters! 30 m for £12.99 ref MAG13P1

**MIXED GOODIES PACK. BOX OF MIXED COMPONENTS**  
WEIGHING 2 KILOS YOURS FOR JUST £3.99

**SIDE LEVER .177 AIR RIFLE** Superb, low priced general purpose rifle, 18" tapered, rifled barrel, fully adjustable open sights, wooden stock, very accurate with low recoil, 41". £39.95 ref R/3

**4X28 TELESCOPIC SIGHTS** Suitable for all air rifles, ground lenses, good light gathering properties. £19.95 ref R/7.

**RATTLE BACKS** Interesting things these, small piece of solid perspex like material that if you try to spin it on the desk it only spins one way! In fact if you spin it the 'wrong' way it stops of its own accord and goes back the other way! £1.99 ref GI/J01.

**GYROSCOPES** Remember these? well we have found a company that still manufactures these popular scientific toys, perfect gift or for educational use etc. £6 ref EP70

**EDIBLE LONGFLICE CANDLES** Made from Oleo Beef Stearin so you can eat them in an emergency alternatively, you could just light them! Each candle burns for approx 10 hours. 2 for £2.99 ref O/N326.

**HYPOTHERMIA SPACE BLANKET** 215x150cm aluminised foil blanket, reflects more than 90% of body heat. Also suitable for the construction of two way mirrors! £3.99 each ref O/L041.

**LENSTATIC RANGER COMPASS** Oil filled capsule, strong metal case, large luminous points. Slight line with magnifying viewer. 50mm dia, 86gm. £10.99 ref O/K604.

**RECHARGE ORDINARY BATTERIES UP TO 10 TIMES!** With the Battery Wizard! Uses the latest pulse wave charge system to charge all popular brands of ordinary batteries AAA, AA, C, D, four at a time! Led system shows when batteries are charged, automatically rejects unsuitable cells, complete with mains adaptor. BS approved. Price is £21.95 ref EP31.

**TALKING WATCH** Yes, it actually tells you the time at the press of a button. Also features a voice alarm that wakes you up and tells you what the time is! Lithium cell included. £7.99 ref EP26.

**PHOTOGRAPHIC RADAR TRAPS CAN COST YOU YOUR LICENCE!** The new multiband 2000 radar detector can prevent even the most responsible of drivers from losing their licence! Adjustable audible alarm with 8 flashing leds gives instant warning of radar zones. Detects X, K, and Ka bands, 3 mile range, 'over the hill' 'around bends' and 'rear trap' facilities, micro size just 4.25"x2.5"x.75". Can pay for itself in just one day! £79.95 ref EP3.

**SNOREBUSTER!** A small wristwatch style device that detects the noise of snoring and instantly produces a stimulation to the wrist of the snorer without waking them. The bio feedback effectively prevents future bouts of snoring, thus reducing Snorebuster to only occasional use. 10 of 1,000's sold. £24.99 ref LA15999.

**WORLDS SMALLEST TAPELESS MEMO PEN!** Not only is the a smart pen but will record 20 seconds of memos etc. No more scratching about for scraps of paper! £39.99 ref AA21381.

**ELECTRIC TYRE INFLATOR** High power micro air compressor inflates tyres, airbeds footballs etc. Includes pressure gauge. £14.99 ref J8231.

**MAMOD STEAM ENGINE SP2** Powerful compact model steam engine complete with fuel etc. £39.95 ref SP2.

**SANYO NICAD PACKS** 120mmx14mm 4.8v 270 mA/h suitable for cordless phones etc. Pack of 2 just £5 ref EP78.

## WE BUY SURPLUS STOCK FOR CASH FREE CATALOGUE

1995 100 PAGE CATALOGUE NOW AVAILABLE, 45P STAMP OR FREE WITH ORDER.

## PORTABLE RADIATION DETECTOR WITH NEW COMPUTER INTERFACE 59

A Hand held personal Gamma and X Ray detector. This unit contains two Geiger Tubes, has a 4 digit LCD display with a Piezo speaker, giving an audio visual indication. The unit detects high energy electromagnetic quanta with an energy from 30K eV to over 1.2M eV and a measuring range of 5-9999 UR/h or 10-99990 Nr/h. ref NOV18

# CLASSIFIED

TEL 0181 652 3620

FAX 0181 652 8956

## ARTICLES FOR SALE





### SUPPLIER OF QUALITY USED TEST INSTRUMENTS



**CONTACT**

### Cooke International


ELECTRONIC TEST & MEASURING INSTRUMENTS  
Unit Four, Fordingbridge Site, Main Road, Barnham, Bognor Regis, West Sussex, PO22 0EB  
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

**CIRCLE NO. 159 ON REPLY CARD**





### OPERATING & SERVICE MANUALS

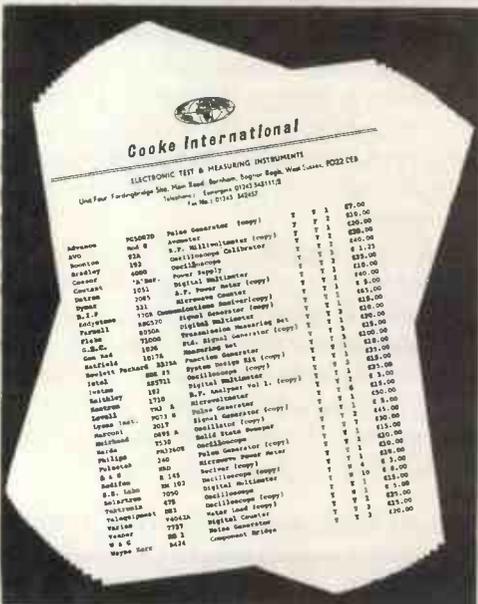

**CONTACT**

### Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS  
Unit Four, Fordingbridge Site, Main Road, Barnham, Bognor Regis, West Sussex, PO22 0EB  
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

**CIRCLE NO. 160 ON REPLY CARD**

# INDEX TO ADVERTISERS

	PAGE		PAGE		PAGE
Airlink Sales Co	750	Interconnections	786	Quickroute Systems Ltd	714
Anchor Surplus	723	International Rectifiers	743	Ralfe Electronics	808
Andat	726	IOSIS	769	Seetrex Ltd	769
Arcom	777	Johns Radio	781	Smart	776
BK Electronics	714	JPG	776	Sowter	725
Bull Electrical	804	Kestrel Electronic Components	782	Stag	714
CMS	750 & 775	Keytronics	766	Stewart of Reading	798
Chelmer Valve Co	771	Labcentre	747 & 757	Surrey Electronics	726
Cricklewood Electronics	786	Langrex	785	TDC	725
Crossware Products	776	Laplace	735	Telford Electronics	786
Dataman	OBC	LCE	798	Telnet	726
Display Electronics Ltd	739	Lloyd Research Ltd	745	Those Engineers	774
Field Electric Ltd	785	MB	720	TLE Die	779
Grandata Ltd	741	MQP	745	Timely Technology	777
Halcyon Electronics	782	John Morrison	798	Triangle	725
Hart Electronic Kits Ltd	748	Number One Systems	771	Tsien Ltd	782
Hateley Antenna Technology	725	Olsen	719	Ultimate	IBC
ICE Technology	IFC	OEMA	785	Warwick	777
ILP	769, 771 & 773	Pico	772	XL Systems	798

# CLASSIFIED

TEL 0181 652 3620

FAX 0181 652 8956

## RECRUITMENT

### Audio Design Engineer

Cloud Electronics is a respected manufacturer of purpose designed equipment for the Reproduced Sound and Entertainment marketplace worldwide. The cornerstones on which we have built our success are excellence in design, integrity in engineering, reliability in performance and in maintaining a close relationship with our customers, before, during and after sales. The resulting growth in the Company and the expansion of our product range has created a vacancy within our R & D department.

The successful applicant will work alongside the Technical Director, in a multitasking role. Accordingly, we are seeking a multi-skilled person with experience in audio design and D.S.P. who has a genuine passion for audio electronics and who can fully utilise the excellent facilities placed at his/her disposal. We offer an attractive salary package, commensurate with experience and a friendly, purposeful environment. This is an exceptional opportunity for an exceptional candidate. If you feel you are that person, contact:-

**Cloud Electronics Limited** 140 Staniforth Road, Sheffield, S9 3HF

## VALVES

### ELECTRONICS VALVES & SEMICONDUCTORS

Phone for a most  
courteous quotation

We are one of the largest  
stockists of valves etc,  
in the U.K.

### COLOMOR ELECTRONICS LTD

170 Goldhawk Road,  
London W12 8HJ  
England.

Tel: 0181 743 0899  
Fax: 0181 749 3934

## COMPLETE



### NOW IS THE CHANCE TO GET INTO TELEVISION

Complete, one of London's leading video editing companies require a keen electronics enthusiast to join their engineering team as a Junior assistant. He/She will help with all aspects of day to day engineering and project work. Please apply in writing only with CV to:

Richard Whitaker, Complete Facilities, Silingsby Place, Long Acre,  
London WC2E 9AB.

## ARTICLES WANTED

### WANTED!!

Top prices paid for your test equipment made by HEWLETT-PACKARD, MARCONI, FLUKE, TEKTRONIX, BOONTON, ROHDE & SCHWARZ etc.

From Europe's No. 1 Test Equipment Leader

**ROSENKRANZ-ELEKTRONIK, AXEL ROSENKRANZ  
GROSS GERAUER WEG 55, 64295 DARMSTADT/GERMANY**

Phone: 0049-6151-3998-0 Fax: 0049-6151-3998-18

### CONTACT US NOW!

You are looking for test equipment? More than 10,000 units in stock for immediate delivery. Call or fax for our new 100 page catalogue

— today —

**\*\* WHAT WE DON'T HAVE YOU DON'T NEED \*\***

### WANTED

High-end Test Equipment, only brand names as Hewlett-Packard, Tektronix, Rhode & Schwarz, Marconi etc. Top prices paid. Please send or fax your offer to:

### HTB ELEKTRONIK

Alter Apeler Weg 5,  
27619 Schiffdorf, West Germany

TEL: 01049 4706 7044  
FAX: 01049 4706 7049

### WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap and quantity. Prompt service and cash.

**M & B RADIO**  
86 Bishopgate Street,  
Leeds LS1 4BB

Tel: 0113 2435649  
Fax: 0113 2426881

9956

## ARTICLES WANTED

### WE WANT TO BUY !!

**IN VIEW OF THE EXREMELY  
RAPID CHANGE TAKING PLACE  
IN THE ELECTRONICS  
INDUSTRY, LARGE QUANTITIES  
OF COMPONENTS BECOME  
REDUNDANT. WE ARE CASH  
PURCHASERS OF SUCH  
MATERIALS AND WOULD  
APPRECIATE A TELEPHONE  
CALL OR A LIST IF AVAILABLE.  
WE PAY TOP PRICES AND  
COLLECT.**

**R.HENSON LTD.**

**21 Lodge Lane, N.Finchley,  
London N12 8JG.**

**5 Mins, from Tally Ho Corner.**

**TELEPHONE**

**081-445-2713/0749**

**FAX 081-445-5702.**

# CLASSIFIED

TEL 0181 652 3620

FAX 0181 652 8956

## ARTICLES WANTED

### TOP PRICES PAID

For all your valves, tubes, semi conductors and IC's.

**Langrex Supplies Limited**  
1, Mayo Road,  
Croydon,  
Surrey CR0 2QP

TEL:  
**0181-684 1166**  
FAX:  
**0181-684 3056**

### FOR SALE PHOTOPLOTTER & FILM PROCESSOR

EXCELLENT CONDITION  
QED 400 A2 Photoplotter c/w an  
AGFA Rapiline 66 Film Processor,  
Chemicals and Film.  
**£4950 ono**  
Tel: Brian Richards at Monitor  
01562 825556

## FREE CLASSIFIED

FOR SALE, AVO8 MK7. Virtually unused, £160. Tel: (01224) 822693.

**TEKTRONIX MODULES 7A26, 7A18, 7B85, 7B80, 7B50A:** Fully tested. Sensible offers please. Ian Stirling, Cottaracre Star. Fife KY7 6LA. 01592 757384.

**WANTED:** pre-war television. Jac Janssen, Hogeham 117D, NL-5104JD Dongen, Netherlands. Tel: (eves) 01031 1623 18158. Fax (office): 01031 13 624664.

**WANTED:** TEKTRONIX Plug in module. Type AA501 Distortion analyser. Also SG505 oscillator. Phone: G. E. Gillard 0115 9846116.

**WANTED:** Agent/spy radio sets. All periods. SOE/SAS/SSTR-SOVJET etc. German W.W.2 radios. OZ8RO. R. Otterstad, Høsterkøbvej 10, DK-3460 Birkerød, Denmark. Tel: 4281 5205.

**WANTED:** TUBE for Solartron CD1400 oscilloscope, type SE5/2A. Poole 01202 602722.

FOR SALE: Dranetz phase meter, 2Hz - 700 KHz, 0.01 degrees resolution, good for filters, crossovers etc. £350 ono. Tel: Mike 01483 487189 (eves).

SALE OR SWOP for CD-Rom drive. Perkin Elmer, infra-red spect potometer, infragraph H1200, working. Phone 01273 553505.

FOR SALE: EWWW 1980 to 1994. Offers. Phone: Tony - 01276 66155 - evenings.

**WANTED:** pre-war television. Jac Janssen, Hogeham 117D, NL-5104JD Dongen, Netherlands. Tel: 01031 1623 18158. Fax (office): 01031 13 624664. Thanks!

## DISTRIBUTORS

AN5521	1.35	STK4352	6.20	STRD6008	10.00	TEA2026C	4.50
AN5732	1.40	STK4372	5.65	TA7227	1.85	TEA5170	1.40
AN6327	9.85	STK4803	7.05	TA7271	2.50	TUA2000-4	4.25
AN6677	8.50	STK4843	7.05	TA7280	2.25	U884B	2.35
BA5114	1.55	STK5315	5.85	TA7281	2.20	U4606B	5.50
BA6218	1.85	STK5332	1.80	TA7698	5.00	UAA1008	3.00
BA6219	1.20	STK5338	3.25	TA8200	3.50	UPC1178	1.05
HA11423	1.65	STK5361	4.15	TA8210	3.00	UPC1182H	5.15
HA13119	2.50	STK5372	2.85	TA8214	3.00	UPC1278H	2.20
KA6210	4.99	STR5372H	4.15	TA8215	3.00	UPC1420	4.50
LA3220	0.60	STK5412	3.75	TA8205	3.95	UPD1937	3.00
LA4183	1.35	STK5471	3.85	TA8659	13.00	25A814	0.71
LA4445	1.90	STK5490	4.95	TA75339	0.75	25A839	1.40
LA4495	1.40	STK6732	14.00	TD A1908A	2.00	25A1062	1.00
LA4588	2.55	STK7226	7.50	TDA2170	3.00	BU426A	1.10
LA7835	2.35	STK7308	4.05	TDA2270	2.50	BU500	2.45
LB1416	2.25	STK7348	4.05	TDA3562A-TFK	3.25	BU506D	1.50
LM301	0.25	STK7356	4.75	TDA3562A-SG	3.00	BU508A(PHIL)	0.80
LM317T	1.50	STK7404	6.50	TDA3645	8.00	BU508AF(PHI)	1.00
M491BB1	4.75	STK73410	5.15	TDA3650	8.99	BU508DF(PHI)	1.25
M494BB1	6.75	STK73410/2	5.95	TDA3850	18.99	BU806A	1.40
M51393	5.95	STR73605	4.50	TDA4400	1.75	BU807	0.85
M58655	3.30	STR441	14.75	TDA4505A	4.10	BU908	1.15
MB3730	1.70	STR451	25.00	TDA4505B	4.10	BU932	1.50
MB3756	8.00	STR3125	5.50	TDA4505E	4.00	BUK444/500	2.15
STK078	6.00	STR4211	5.50	TD A4505M	6.80	BUK454/600	1.95
STK435	4.00	STR4090	11.15	TD A4505K	6.15	BUT11A	0.70
STK461	6.00	STR20005	5.00	TDA4660	4.50	BUT11AF(PHI)	1.20
STK2250	7.45	STR40090	4.00	TDA4950	1.40	BUT11F	1.20
STK4121/2	7.00	STR50103A	3.85	TDA5660P	2.50	BUT12A	1.10
STK4141/2	5.50	STR54041	3.75	TD A7072	3.99	BUT12AF	1.10
STK4142/2	6.50	STR58041	3.75	TDA8370	14.00	BUT56A	0.80
STK4162/2	6.25	STR80001	6.00	TD A8405	8.00	BUT76A	1.05
STK4171/2	8.10	STR1706	4.75	TD A8732	5.95	BUV48C	3.10
STK4191/2	8.50	STRD1806	4.50	TEA2018A	1.50	BUW13	1.50

When you have been let down by the rest come and try us for fast friendly service. Ask for our full, comprehensive catalogue, FREE OF CHARGE



Please phone us for the types not listed. Please add 60p post & packing and then add 17.5% VAT to the total. Callers by appointment only.

## J.J. COMPONENTS

63 THE CHASE, EDGWARE,  
MIDDX. HA8 5DN, ENGLAND

Hotline No: 081-381 1700/081-952 4641  
Free fax orderline ONLY: 0800 318498  
General Fax: 081-381 1700

## ADD VALUE AND CREDIBILITY WITH REPRINTS


Multiple copies of your articles and advertisements published in this magazine make ideal promotional material for sales literature, exhibition handouts, direct mail, new product launches, distributor promotions, Public Relations etc.

You can add your own artwork and copy, utilise the front cover of this magazine, include your list of distributors, and/or your latest advertisement/s. Reasonably priced reprints can be tailor-made to your own specific requirements or simply reprinted in their original form. (Minimum order number 250)

For a FREE quotation please telephone Jan Crowther now on: 0181-652 8229 or fax: 0181-652 3978

Reprint Services, Reed Business Publishing,  
Room 1006, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS, England

**SPECTRUM ANALYSERS**

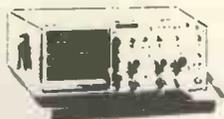

IFR MODEL A-7550 1GHz portable with inbuilt tracking gen & IEEE ops £5000  
 HP141T 18GHz system (8552B, 8555A) £2000  
 HP3580A 5Hz - 50kHz audio frequency spectrum analyser £1500  
 HP3582A audio frequency ft analyser dual-channel £2500  
 HP8557A 350MHz (opt 01 75C) (requires mainframe) £1000  
 HP8591E 1.8GHz synthesized £call us  
 HP8568A high-specification 1.5GHz spectrum analyser £7500  
 MARCONI 2386 100Hz-26.5GHz (in 1Hz steps) £15000  
 TEKTRONIX 492 22GHz spectrum analyser GPIB + options 1/23 £6000

**MARCONI INSTRUMENTS**



2019A synthesized AM/FM signal generator 80kHz - 1040MHz £2000  
 2305 modulation analyser 50kHz - 2.3GHz £3000  
 2828A/2829 digital simulator/analyser  
 2955 mobile radio test set WITH TACS ADAPTER  
 2386 spectrum analyser, superb specification, 100Hz-26.5GHz  
 6460/6421 power meter & sensor 10MHz-12.4GHz  
 6500 amplitude analyser c/w 2c 6514 waveguide detectors £2500  
 6960 microwave power meter with 6910 power sensor 10MHz-20GHz £1000  
 OA2805A pam regenerator test set £750  
 TF29104 non-linear distortion (video) test set £500  
 TF2910 TV interval timer £250

**RALFE · ELECTRONICS**

36 EASTCOTE LANE, S. HARROW, MIDDLESEX HA2 8DB  
 TEL: 0181-422 3593. FAX: 0181-423 4009

NOW IN 40th YEAR



DISTRIBUZIONE E ASSISTENZA, ITALY: TLC RADIO, ROMA (06) 871 90254

**TEST EQUIPMENT**

APLAB TIS115/230/500 transverter 115/230V in/out, 50/60/400Hz, 500VA £650  
 BRUEL & KJAER 2511 vibration meter (file set 1621 filter) £2000  
 BRUEL & KJAER 2317 portable level recorder £1500  
 BRUEL & KJAER 2635 charge amplifier £950  
 BRUEL & KJAER 2609 measuring amplifier £750  
 BRUEL & KJAER 2308 analogue X-Y pen recorder £750  
 BRUEL & KJAER 2639 preamplifier £275  
 DATRON 1065 digital multimeter £500  
 HITACHI V509 50MHz portable battery powered oscilloscope (includes batts) £550  
 KIKUSUI 8520 frequency response analyser 20Hz-200KHz £750  
 NARDA bi-directional coaxial coupler 1-4GHz £250

**HEWLETT PACKARD**



TEKTRONIX PG502 250MHz pulse generator (requires TM-series mainframe) £750  
 WAYNE KERR SR268 source & detector £350

1640B serial data analyser £500  
 339A distortion meter £1750  
 3325B function generator £3000  
 3400A voltmeter, analogue 10Hz-10MHz £250  
 3456A digital multimeter £750  
 3580A audio frequency spectrum analyser £1500  
 3581C selective voltmeter £1250  
 3586A selective level meter £2000  
 4140B pA/meter, DC voltage source £3250  
 415E swr meter £200  
 4275A multi-frequency lcr meter £4000  
 432A/R486A uWave power meter waveguide 26-40GHz £500  
 435B microwave power meter (analogue) (requires sensor) £500  
 4951C protocol analyser with 18179A pod £1250  
 5334A 100MHz frequency counter £2000  
 5335A 200MHz frequency counter w ops 20 & 40 £2500  
 6012A power supply 0-60V 0-50A 1000W £650  
 6033A system power supply 0-20V 0-30A £1250  
 6038A system power supply 0-60V 0-10A £1250  
 6253A dual power supply 0-20V 0-1A twice £250  
 6443B power supply 0-120V 0-2.5A £400  
 6625A bipolar power supply/amplifier -20V to +20V, 0-1A £350  
 8011A pulse generator 0.1Hz-20MHz £500  
 8444A tracking generator with option 059 £1500  
 8754A H26 2600MHz network analyser c/w S-parameter set £4000  
 8568A spectrum analyser 100Hz-1.5GHz £7500  
 8656B synthesized signal generator 0.1-990MHz AM/FM £2900  
 8901A modulation analyser with option 02/010 £3500

**ralfe electronics exclusively a professional T&M**

★★ HP8754A 4-1300MHz NETWORK ANALYSER with ★★  
 8748A S-Parameter test set £3500  
 ★★ HP8970A noise figure meter £4000 ★★  
 ★★ HP54100A 1GHz digitizing oscilloscope £1750 ★★  
 ★★ MARCONI 2955 MOBILE RADIO TEST SET ★★  
 with cellular TACS adapter £4000

£500 PHILIPS PE1647 power supply 0-75V, 0-14A £250  
 £4000 PHILIPS PM5519 video pattern generator £350  
 £1500 PHILIPS PM8272 2-channel recorder £750  
 £350 RACAL-DANA 1992 frequency counter 1.3GHz IEEE option £700  
 £2500 SCHLUMBERGER 1250 frequency response analyser £3000  
 £1000 SCHLUMBERGER 4040 communications test set, many options included £5000  
 £750 TEKTRONIX 1503C tdr with battery & printer options £3250  
 £500 TEKTRONIX P6303 scope probes NEW 250MHz X10/X10 with readout pin £500a  
 £250 TEKTRONIX transistor curve tracer type 577 with standard test fixture £1500

PLEASE NOTE: ALL OUR EQUIPMENT IS NOW OPERATION-VERIFICATION TESTED BEFORE DESPATCH BY INDEPENDENT LABORATORY

We would be pleased to handle all grades of calibration or NAMAS certification by same laboratory at cost price. All items covered by our 90-day parts and labour guarantee and 7-day 'Right to Refuse' (money back) warranty.

ALL PRICES SUBJECT TO ADDITIONAL VAT AND CARRIAGE

CIRCLE NO. 161 ON REPLY CARD

**ELECTRONIC UPDATE**

Contact Malcolm Wells on 0181-652 3620

A regular advertising feature enabling readers to obtain more information on companies' products or services.

**flint SMD**  
 9th Edition

**I DON'T BELIEVE IT!**

This new 264 page Guide to SMDs now includes 64 pages of SM Connector Systems from AMP, JAE, Molex, Hirose, Oxley, Cinch and Sumitomo and mainly from stock as well.

Not only that but it's bulging with new SMDs from over 30 franchises which now include Panasonic. What an incredibly useful publication.

I had better ring 01530 510333 for my copy before they run out!

CIRCLE NO. 162 ON REPLY CARD

**IEEE 488.2**  
 Instrument Control

**(GPIB BROCHURE) IEEE 488.2 INSTRUMENT CONTROL**  
 Eight page brochure covers GPIB interfaces, support products, accessories, and software. Includes information on IEEE 488.2-compatible interfaces for your desktop PC, Macintosh or workstation, as well as the PCMCIA-GPIB interface, for notebook or laptop computers. These interfaces feature the TNT4882 and 4882C ASICs, which are also described. Application software and software drivers for numerous operating systems are discussed, in addition to the new HS488 high-speed GPIB handshake protocol.  
**NATIONAL INSTRUMENTS**  
 For further information Freephone 0800 28987.

CIRCLE NO. 163 ON REPLY CARD

**1995 MASTER PRODUCT CATALOGUE**  
 BRAIN BOXES  
 ISO 9001

**1995 MASTER PRODUCT CATALOGUE NOW OUT!**

Test and instrument control solutions. 48 pages of full description and technical data on our own range of solutions to your PC and PS2 interfacing problems: IEEE488 (GPIB) \* DIO \* Timer/Counters \* RS232 \* RS422/485 \* A/D \* D/A \* plus Opto Isolated versions. New Parallel/Serial RS232. Opto Dual RS232. Motion Control. Converter and Repeater for 1995!  
 ISO 9001 Quality guarantee ✓  
 UK design and manufacture ✓  
 36 month no-quibble warranty ✓  
 Telephone hotline support ✓  
 Competitive pricing on the page ✓  
 Intelligent solutions & friendly service ✓

**BRAIN BOXES**  
 Unif 3f Wavertree Boulevard South  
 Wavertree Technology Park  
 Liverpool L7 9PF  
 Tel: 0151 220 2500 Fax: 0151 252 0446

CIRCLE NO. 164 ON REPLY CARD

**PC-ADH24**  
 24 Channel 12-Bit Analog Input Card with DMA & Interrupts

- 24 differential input channels
- 13 bit AD converter
- 100 KHz throughput
- 128K & 512K memory buffers
- Unib-polar four voltage inputs
- Intermittent amplifier inputs
- Programmable gain of 1, 2.5, 5 or 10 V/V
- Maximum resolution - 1.2uV
- User programmable
- Full PC/XT/AT & compatibles
- Software Drivers for Windows, Basic, Assembly, Turbo Pascal & C/C++
- Comprehensive Technical Manual
- Free Applications Manual
- Free Technical Support
- Three Year Warranty
- Designed & Manufactured in the UK
- Operates from Standby State & 5V Standby Gate

Bede Technology  
 27a Lonsdale Court, Bude Industrial Estate, Bude, Cornwall TR11 3JH  
 Tel: 0200 474 000 Fax: 0200 474 004


**DATA ACQUISITION & CONTROL FOR PCs**

Bede Technology provide a wide range of products for PC/XT/AT Compatibles:  
 ★ Plug-in Data Acquisition and Control Cards and Software.  
 ★ Industrial PCs and Single Board Computers.  
 ★ Parallel/Serial Interfaces.  
 Products offer: \*Excellent Quality \*Three Year Warranty \*Made in the UK \*Free Technical Support.  
 For a free catalogue and demo disks call (0191) 4280353 or fax (0191) 4282904.

Bede Technology  
 Tel: (0191) 4280353. Fax (0191) 4282904

CIRCLE NO. 165 ON REPLY CARD

# PCB Design Contest

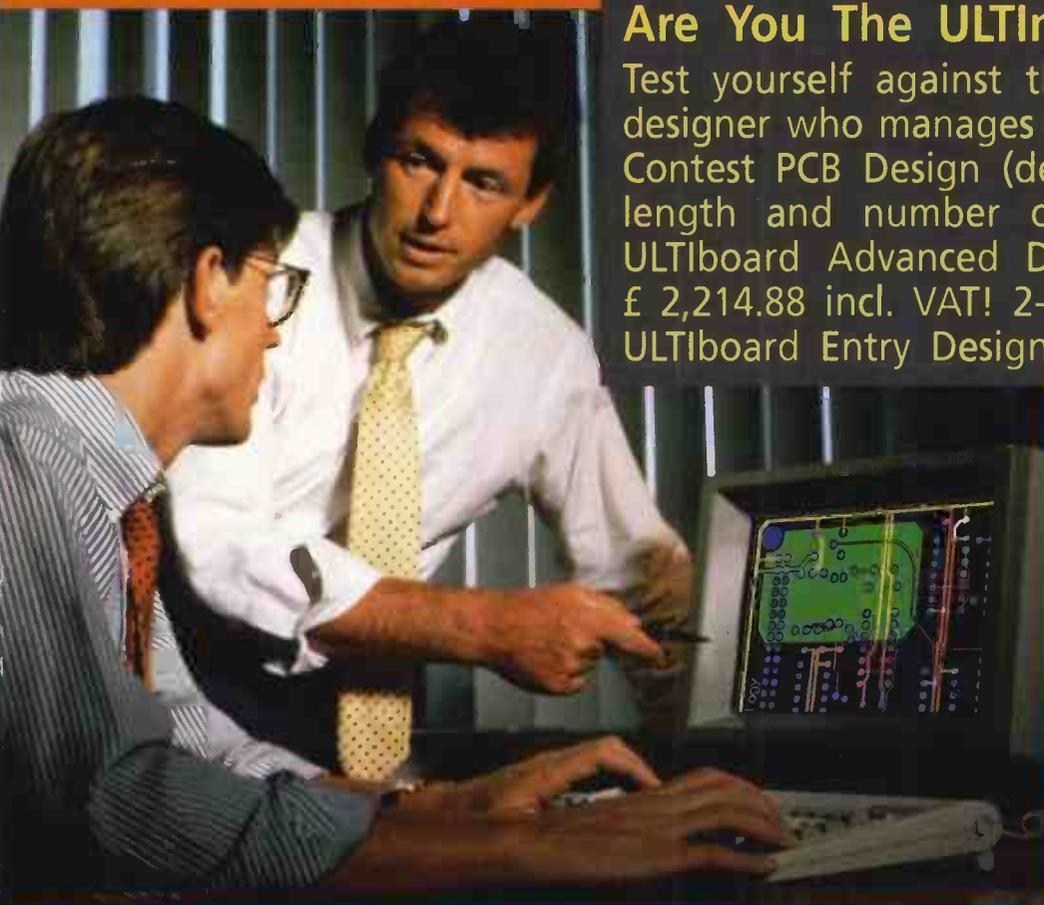

## Are You The ULTimate PCB Designer?

Test yourself against the best in the UK! The designer who manages to make the best quality Contest PCB Design (determined by total trace length and number of vias) will receive an ULTiboard Advanced Designer, valued at over £ 2,214.88 incl. VAT! 2-10 prize winners win an ULTiboard Entry Designer valued at £ 1,521.63.

Competition Entries will be judged by an independent jury, consisting of experts in the field of electronic design and production. So that we can judge your design, contenders need to provide us with:

- an ULTiboard ddf file or
- a Gerber (photoplot) file of any PCB Design System plus printouts that clearly show trace widths, pad sizes number of vias and total trace length. The contest closes on 1st Nov, 1995. The 10 Winners will be personally informed, and the results published. No correspondence will be entered into and the judges decision is final!

The contest design may be perfectly designed with the ULTiboard Challenger Lite a 32 bit Schematic Entry and PCB Layout Tool with a design capacity of 500 pins. This Version includes an internal gridless autorouter, that routes by nets, component or block.

Minimum Hardware requirements are: 80386 (SX), 2 Mb RAM and Colour VGA. No Purchase is required to enter the competition and all employees & distributors of ULTimate Technology are excluded. For those who wish to purchase their own PCB Design System the 32 bit Challenger Lite is available on special offer for a limited period only.

### Special Offer!

**Challenger Lite £150 + £10 Delivery and VAT**  
Please order by Credit Card, Tel: 01734 812030 or Send a Cheque for £188 to: ULTimate Technology Ltd. 2 Bacchus House, Calleva Park, Aldermaston. Berks RG7 4QW

## ENTRY FORM

Please fax or send back this form (one design per entrant only) to ULTimate Technology (UK) Ltd, 2 Bacchus House, Calleva Park, Aldermaston, Berkshire RG7 4QW England, Fax: 01734 815323

Name : \_\_\_\_\_

Address : \_\_\_\_\_  
\_\_\_\_\_

Daytime Tel : \_\_\_\_\_

Design Tool Used : \_\_\_\_\_

Please send me a competition pack including: Net List on floppy disk and paper and design rules (minimum trace widths & clearances, pad and via sizes) etc.

**ULTICAP + ULTIBOARD = MAXIMUM PRODUCTIVITY**

CIRCLE NO. 102 ON REPLY CARD

**ULTIMATE**  
TECHNOLOGY


Corporate Headquarters: tel.: (+31) 2159 - 44444  
Energistraat 36 • 1411 AT Naarden fax: (+31) 2159 - 43345  
The Netherlands

For further information enter 63

UK/Ireland Sales-Office: tel.: 01734 - 812030  
2 Bacchus House • Calleva Park fax: 01734 - 815323  
Aldermaston Berkshire • RG7 4QW

Credit card holders - call now for special bundle deals.

# The handiest programmer on earth

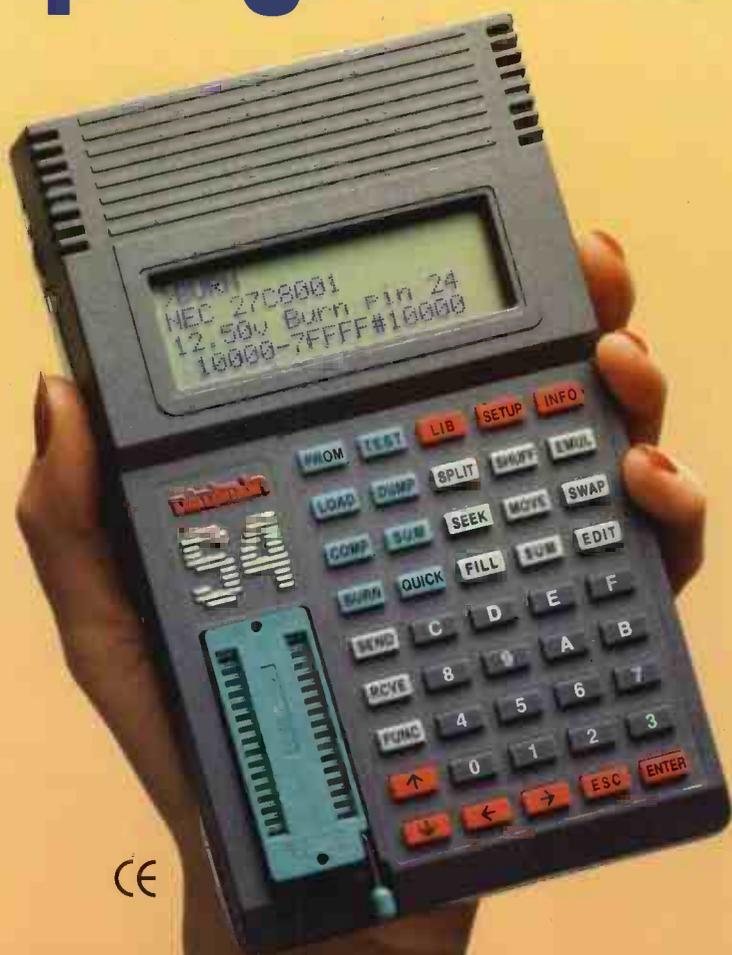

CE

## Here's why:

- Totally handheld programmer/emulator manufactured in the UK
- Fast approved programming algorithms; eg program and verify: National 27C512 in 16 seconds, AMD 29F010 in only 90 seconds
- EPROMs to 16Mbit, 5v, 12v and BOOT-BLOCK FLASH, EEPROMS and PEROMS
- Three year parts and labour guarantee
- Full 24 byte on-screen editor
- Continuous programming whilst charging (nonstop operation)
- Designer case - feels as good as it looks
- Big, easy-view 80 character supertwist LCD
- Optional modules available to program PIC (all 16/17 series), 8751, 16-bit EPROMs, MROM-EPROM, 16-bit FLASH, Toshiba 4-bit, Hitachi H8, SERIAL EEPROMS
- Optional sockets for programming and emulating PLCC devices

CIRCLE NO. 103 ON REPLY CARD

FREE software upgrades for life

FREE emulation leads

FREE Windows and DOS software

only **£495** plus VAT

**3 year guarantee**  
**30 day free trial**

4Mbit upgrade only £39 plus VAT

S4's 32 pin ZIF socket programs a huge library of 8 and 16-bit EPROMs, EEPROMS, FLASH, PICs and other popular microcontrollers using manufacturers approved algorithms.

Dataman *never* charge for updates or technical support, a vital factor in determining a cost-effective programming solution for the years ahead. Upgrading your S4's device library couldn't be simpler. As well as our high speed bulletin boards, we also offer full Internet access to our Home Page which contains all the latest software as well as hints and tips.

**Built-in emulation** enables you to see your code *before* committing yourself to an EPROM.

Load your program from an EPROM or download code from your PC into S4's memory. Plug S4's emulation lead into the target system, press the emulation key and run the system. Changes can be made using S4's powerful editor, and you can re-run the code to test and confirm changes. When the code is proved to be working, it can then be programmed to a fresh ROM.

**The S4 Package** comes complete with mains charger, emulation leads, organiser-style instruction manual, Windows and DOS terminal software *and* a three year guarantee.

**S4 is always available** off the shelf and we ship worldwide on a daily basis. Call now for delivery tomorrow.

Bona-fide UK customers can try S4 for thirty days without risk. 24,000 engineers worldwide can't be wrong!

**DATAMAN**  
**Dataman Programmiers Ltd**

Station Road, Malden Newton,  
Dorset DT2 0AE, UK

Tel: 01300 320719 Fax: 01300 321012

Telex: 418442 BBS: 01300 321095

Modem: V.34/V.FC/V.32bis

22 Lake Beauty Drive, Suite 101  
Orlando, FL 32806, USA

Tel: (407) 649-3335 Fax: (407) 649-3310

BBS: (407) 649-3159 24hr

Modem: V.34/V.FC/V.32bis

Via the Internet:

Home Page: <http://www.dataman.com>

FTP access: [ftp.dataman.com](ftp://ftp.dataman.com)

Email: [sales@dataman.com](mailto:sales@dataman.com)



CREDIT CARD

HOTLINE 01300 320719

for same-day dispatch



DATAMAN PROGRAMMERS