Havan W. Samz

HANDBOOK OF ELECTRONIC TABLES & FORMULAS

Compiled and Edited by

DONALD HERRINGTON and STANLEY MEACHAM

Members, Howard W. Sams Engineering Staff

HOWARD W. SAMS & CO., INC.
THE BOBBS-MERRILL COMPANY, INC.

Indianapolis • New York

SECOND EDITION

FIRST PRINTING — FEBRUARY, 1962 SECOND PRINTING — DECEMBER, 1962 THIRD PRINTING — MARCH, 1964 FOURTH PRINTING — OCTOBER, 1964

FIRST EDITION
FIRST PRINTING — NOVEMBER, 1959
SECOND PRINTING — JULY, 1960

HANDBOOK OF ELECTRONIC TABLES AND FORMULAS

Copyright © 1959, 1962, and 1964 by Howard W. Sams & Co., Inc., Indianapolis 6, Indiana. Printed in the United States of America.

Reproduction or use, without express permission, of editorial or pictorial content, in any manner, is prohibited. No patent liability is assumed with respect to the use of the information contained herein.

Library of Congress Catalog Card Number: 62-12659

PREFACE

In the Preface to the first edition of this book, published in November, 1959, we asked for recommendations of additional items to consider for inclusion in a future edition. Many suggestions were received and considered; most of them are incorporated in this volume. Hence, this book contains the information which users of the first edition—engineers, technicians, students, experimenters, and hobbyists—have told us they would like to have in a comprehensive one-stop edition.

The basic formulas and laws, so important in all branches of electronics, are given in Part One. Also included are nomographs to speed up the solution of problems involving Ohm's law, power, parallel resistance, and reactance.

Useful, but hard to remember constants, and standards which have been established by the government or industry, are included in Part Two. The comprehensive Table of Conversion Factors is especially helpful in electronic computations.

Part Three contains symbols and codes which have been adopted over the years. The latest semiconductor information is included, to keep you abreast of this rapidly expanding field.

Items of particular interest to electronics service technicians are included in Part Four. Data most often used in circuit design work are given in Part Five. The filter and attenuator configurations and formulas are particularly useful to service technicians and design engineers.

Mathematical tables, formulas, and other information are presented in Part Six. Binary numbers and an introduction to Boolean algebra—the tools of the computer field—are also included in this section. Many items of a miscellaneous nature are included in Part Seven.

No effort has been spared to make this revised handbook of maximum value to anyone, in any branch of electronics. Once again your comments, criticisms, and recommendations for additional data you would like to see included in a future edition, will be welcomed.

1 Mans

January, 1962

TABLE OF CONTENTS

Secti					1 age
	ELECTRONICS FORMULAS				
1.	Ohm's Law for Direct Current				
2.	DC Power				. 11
3.	Ohm's Law Nomograph				. 13
4.	Kirchhoff's Laws				. 13
5.	Resistance				. 14
6.	Capacitance				. 17
7.	Inductance				. 19
8.	Q Factor				. 22
9.	Resonance				. 22
10.	Admittance				. 22
11.	Susceptance				. 23
12.	Conductance				. 23
13.	Energy Units				. 24
14.	Reactance				
15.	Impedance				
16.	Ohm's Law for Alternating Curr	ent .			. 33
17.	Average, Rms, Peak, and Peak-to	o-Peak	Volta	ge	
	and Current				. 34
18.	Power Factor				
19.	Time Constants				
20.	Transformer Formulas				. 37
21.	Voltage Regulation				
22.	DC Meter Formulas				
23.	Frequency and Wavelength .				. 41
24.	Transmission-Line Formulas .				. 43
25.	Modulation Formulas				. 44
26.	Decibels and Volume Units				
	CONSTANTS AND STA	NDAF	RDS		
27.	Dielectric Constants of Materials				. 51
28.	Conversion Factors				. 52
29.	Metric Prefixes				. 57
30.	Standard Frequencies and Time	Signal	S .		. 59
31.	Frequency and Operating Power	Toler	ances		. 65
32.	Commercial Operator Licenses				
33.	Amateur Operator Privileges .				

TABLE OF CONTENTS

Sect							Page
34.	Amateur ("Ham") Bands						71
35.	Types of Emission						74
36.	Television Channel Frequencies						74
37.	Television Signal Standards						74
38.	Audio Frequency Standards						74
39.	Television Signal Standards Audio Frequency Standards Radio Frequency Standards						74
	SYMBOLS AND COD	ES					
40.	International Q Signals						80
41.	"10" Signals	•	•	•	•	•	81
42.	"10" Signals	•	٠	•	•		
43.	Greek Alphabet	•	•	•	•		
44.	Electronic Symbols and Abbreviati	ions	•	•	•		
45.	Semiconductor Abbreviations	OIIS	•	•			
46.	Semiconductor Abbreviations EIA Transformer Color Codes .		•	•			
47.	Resistor and Capacitor Color Codes		•	•	•		
48.	Electronic Schematic Symbols .	<i>.</i>	•	•	•	•	88
		٠	•	•	•	•	00
	SERVICE AND INSTALLATI	ON	D	ΑT	A		
49.	Coaxial Cable Characteristics						95
50.	Test-Pattern Interpretation					•	96
51.	Classes of Vacuum-Tube Operation	1 .			·	•	99
52 .	Miniatura Lamp Data						101
53.	Gas-Filled Lamp Data						102
54 .	Light Properties of Color TV			•	•	•	104
55.	Relay Rewinding Data			Ċ	•	•	107
56 .	Speaker Connections	·	•	•	•	•	108
57.	Speaker Connections	·	•	•	•	•	110
58.	Types of Screw Heads		•	Ċ	•	•	111
59.	Types of Screw Heads Resistance of Metals and Alloys .	·	•	•	•	•	111
60.	Copper-Wire Table			Ċ	•	•	111
			•	٠	·	•	
	DEGLOW DAMA						
01	DESIGN DATA						
61.	Vacuum-Tube Formulas	•					114
62.	Transistor Formulas		•				114
63.	Three-Phase Power Formulas						116
64.	Coil Windings						117
65. 66.	Filter Formulas						

TABLE OF CONTENTS

Secti	on]	Page
	MATHEMATICAL TABLE	ES	Al	ND	F	OR	MU	LA	S	
67.	Mathematical Constants									135
68.	Mathematical Symbols .									135
69.	Decimal Equivalents of Fr	act	ion	S						136
70.	Powers of 10									137
71.	Operation of the Slide Rule									140
72.	Algebraic Operations .									144
73.	Geometric Formulas									146
74 .	Trigonometric Functions					•				150
75 .	Binary Numbers									157
76 .	Fundamentals of Boolean	\lg	ebr	a						160
77.	Common Logarithms .									162
	MISCELLANE	ΩTI	ום ו	D 4	ТΑ					
78.	Power Consumption of Ho	me	EI	ect.	rica	¥1				1771
	Equipment	•	٠	•	٠	•	•	•	•	170
79 .	Temperature Conversion									174
80.	Characteristics of the Eler									174
81.	Measures and Weights .									176
82.	Metric Equivalents									177
83.	Winds									178
84.	Weight of Water									179
85.	Hydraulic Equations .									179
86.	Miscellaneous			•	•	•	٠	•	•	179
INI	DEX									183

LIST OF TABLES

Table		Page
I	Average, Rms, Peak, and Peak-to-Peak Values	34
II	Time Constants versus Per Cent of Voltage or	0.
	Current	36
III	Decibel Table	48
IV	Dielectric Constants of Materials	51
V	Conversion Factors	52
VI	Metric Prenxes	57
VII	Metric Conversion Table Other Standards Stations	58
VIII	Other Standards Stations	66
IX	LF and VLF Stations	66
X	Power Limits of Citizens-Band Stations	68
ΧI	Frequency Tolerances of Citizens-Band	UG
	Stations	68
XII	"Ham" Bands	71
XIII	Types of Emission	72
XIV	Frequency Classification	79
XV	Q Signals	80
XVI	"10" Signals	81
XVII	Greek Alphabet	82
XVIII	Coaxial Cable Characteristics	95
XIX	3.51 1 1	102
XX		102
XXI	External Resistances Needed for Gas-Filled	100
	Lamps	104
XXII	Lamps	110
XXIII	Machine Screw and Drill Sizes	111
XXIV	Copper Wire Table	119
XXV	K Factors for Calculating Attenuator Loss	129
XXVI	Decimal Equivalents of Fractions	136
XXVII		151
XXVIII	Natural Trigonometric Functions	152
XXIX	Powers of 2	158
XXX	Basic Rules of Symbolic Logic	161
XXXI	Summary of Logical Statements	162
XXXII	Common Logarithms	167
IIIXXX	Common Logarithms	-01
	Equipment	171
XXXIV	Characteristics of the Elements	174
XXXV	Wind Designations	178

Electronics Formulas and Laws

1. OHM'S LAW FOR DIRECT CURRENT

All substances offer some obstruction to the flow of current. Ohm's law states that the current which flows is directly proportional to the applied voltage and inversely proportional to the resistance. Thus:

$$I = \frac{E}{R}$$

$$E = IR$$

$$R = \frac{E}{I}$$

$$Fig. 1$$

where.

I is the current in amperes, E is the voltage in volts,

R is the resistance in ohms.

2. DC POWER

The power P expended in load resistance R when current I flows under a voltage pressure E can be determined by the formulas:

$$P = EI$$

$$P = I^2R$$

$$P = \frac{E^2}{R}$$

where,

P is the power expressed in watts, E is the voltage in volts, I is the current in amperes, R is the resistance in ohms.

Ohm's Law Nomograph

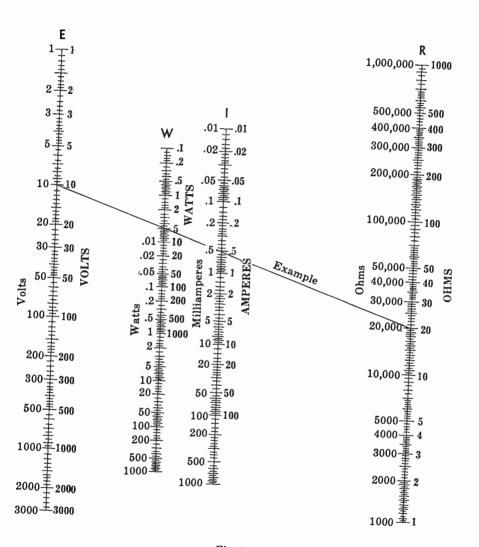


Fig. 2

3. OHM'S LAW NOMOGRAPH


The nomograph on the preceding page is a convenient way of solving most Ohm's law and DC power problems. If two values are known, the two unknown values can be determined by placing a straightedge across the two known values and reading the unknown values at the points where the straightedge crosses the appropriate scales. The figures in bold face (on the right side of all scales) cover one range of given values, and the figures in light face (on the left side) cover another range. For a given problem, all values must be read in either the bold- or light-face figures.

Example—What is the value of a resistor if a 10-volt drop is measured across it and a current of 500 milliamperes (.5 ampere) is flowing through it? What is the power dissipated by the resistor?

ANSWER: The value of the resistor is 20 ohms. The power dissipated in the resistor is 5 watts.

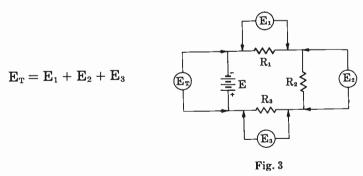4. KIRCHHOFF'S LAWS

Kirchhoff's voltage law states: "The sum of the voltage drops around a DC series circuit equals the source or applied voltage. In other words, disregarding losses due to the wire resistance:



where,

 \mathbf{E}_{T} is the source voltage,

 E_1 , E_2 , and E_3 are the voltage drops across the individual resistors.

Kirchhoff's current law states: "The current flowing toward a point in a circuit must equal the current flowing away from that point." Hence, if a circuit is broken up into several parallel paths, the sum of the currents through the individual paths must equal the current flowing to the point where the circuit branches, or:

$$I_T = I_1 + I_2 + I_3$$

$$= \underbrace{I_1}_{E} E \quad R_1$$

$$= \underbrace{R_2}_{E} \quad R_3$$

$$= \underbrace{R_3}_{E}$$


$$= \underbrace{R_1}_{E} \quad R_2$$

$$= \underbrace{R_3}_{E}$$

where,

 $I_{\rm T}$ is the total current flowing through the circuit, $I_{\rm 1},~I_{\rm 2},$ and $I_{\rm 3}$ are the currents flowing through the individual branches.

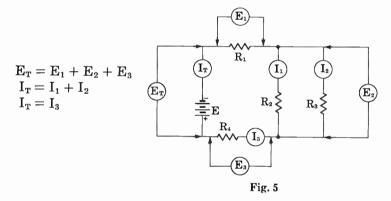In a series-parallel circuit, the relationships are as follows:



5. RESISTANCE

The following formulas can be used for calculating the total resistance in a circuit.

Resistors in series (Fig. 6):

$$R_T = R_1 + R_2 + R_3 + \dots$$

$$R_T = R_1 + R_2 + R_3 + \dots$$

$$R_1 = R_2 + R_3$$
Fig. 6

Resistors in parallel (Fig. 7):

$$R_{T} = \frac{1}{\frac{1}{R_{1}} + \frac{1}{R_{2}} + \frac{1}{R_{3}} + \dots}$$

$$R_{T} = \frac{1}{\frac{1}{R_{1}} + \frac{1}{R_{2}} + \frac{1}{R_{3}} + \dots}$$

$$R_{1} = \frac{R_{1}}{R_{2}}$$

$$R_{2} = \frac{R_{3}}{R_{3}}$$
Fig. 7

Two resistors in parallel (Fig. 8):

$$R_{T} = \frac{R_{1} \times R_{2}}{R_{1} + R_{2}}$$

$$R_{1}$$

$$R_{2}$$

$$R_{2}$$
Fig. 8

where,

 R_T is the total resistance of the circuit, R_1 , R_2 , and R_3 are the values of the individual resistors.

The equivalent value of resistors in parallel can be solved with the nomograph given in Fig. 9. Place a straightedge across the points on scale R_1 and R_2 where the known value resistors fall. The point at which the straightedge crosses the R_T scale will show the total resistance of the two resistors in parallel. If three resistors are in parallel, first find the equivalent resistance of two of the resistors, then consider this value as being in parallel with the remaining resistor.

If the total resistance needed is known, the straightedge can be placed at this value on the $R_{\mathtt{T}}$ scale and rotated to find the various combinations of values on the $R_{\mathtt{1}}$ and $R_{\mathtt{2}}$ scales which will produce the needed value.

Scales R_{1Y} and R_{TY} are used with the R_1 scale when the values of the known resistors differ greatly. The range of the nomograph can be increased by multiplying the values of all scales by 10, 100, 1,000, or more, as required.

Parallel Resistance Nomograph

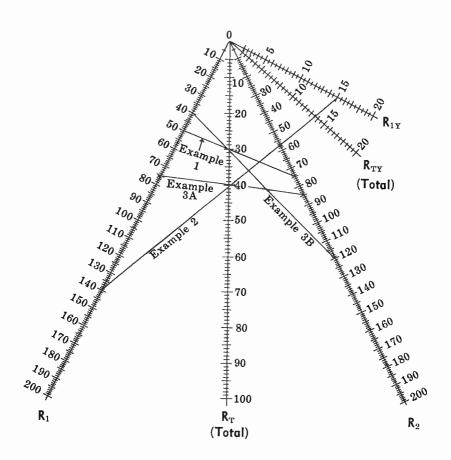


Fig. 9

Example 1—What is the total resistance of a 50-ohm and a 75-ohm resistor in parallel.

ANSWER: 30 ohms.

Example 2—What is the total resistance of a 1,500-ohm and a 14,000-ohm resistor in parallel?

ANSWER: 1,355 ohms. (Use R_{ι} and $R_{\iota\tau}$ scales; read answer on $R_{\tau\tau}$ scale.)

Example 3—What is the total resistance of a 75-ohm, an 85-ohm, and a 120-ohm resistor in parallel?

ANSWER: 30 ohms. (First, consider the 75-ohm and 85-ohm resistors, which will give 40 ohms; then consider this 40 ohms and the 120-ohm resistor, which will give 30 ohms.)

6. CAPACITANCE

(A) Total Capacitance

The following formulas can be used for calculating the total capacitance in a circuit.

Capacitors in parallel (Fig. 10):

$$C_T=C_1+C_2+C_3+\ldots$$

Capacitors in series (Fig. 11):


$$C_{T} = \frac{1}{\frac{1}{C_{1}} + \frac{1}{C_{2}} + \frac{1}{C_{3}} + \dots}$$

$$C_{T} = \frac{1}{\frac{1}{C_{1}} + \frac{1}{C_{2}} + \frac{1}{C_{3}} + \dots}$$

$$C_{1} = \frac{C_{2}}{C_{3}}$$
Fig. 11

Two capacitors in series (Fig. 12):
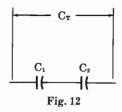
$$C_{T} = \frac{C_1 \times C_2}{C_1 + C_2}$$



where,

 C_T is the total capacitance in a circuit, C_1 , C_2 , and C_3 are the values of the individual capacitors.

The parallel-resistance nomograph in § 5 can also be used to determine the total capacitance of capacitors in series.

The capacitance of a parallel-plate capacitor is determined by:

$$\mathrm{C} = 0.2235 \, \frac{\mathrm{KA}}{\mathrm{d}} (\mathrm{N} - 1)$$

where,

C is the capacitance in micromicrofarads,

K is the dielectric constant,*

A is the area of one plate in square inches,

d is the thickness of the dielectric in inches,

N is the number of plates.

(B) Charge Stored

The charge stored in a capacitor is determined by:

$$Q = CE$$

where,

Q is the charge, in coulombs,

C is the capacitance in farads,

E is the voltage impressed across the capacitor.

(C) Energy Stored

The energy stored in a capacitor can be determined by:

$$W = \frac{CE^2}{2}$$

where,

W is the energy in joules (watt-seconds),


C is the capacitance in farads,

E is the applied voltage in volts.

^{*} For a list of dielectric constants of materials, see § 27.

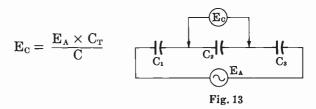(D) Voltage Across Series Capacitors

When an AC voltage is applied across a group of capacitors connected in series (Fig. 13), the voltage drop across the combination is, of course, equal to the applied voltage. The drop across each individual capacitor is inversely proportional to its capacitance. The drop across any capacitor in a group of series capacitors is calculated by the formula:



where,

 E_C is the voltage across the individual capacitor in the series $(C_1, C_2, \text{ or } C_3)$,

 E_A is the applied voltage,

 C_{T} is the total capacitance of the series combination,

C is the capacitance of the individual capacitor under consideration.

Note: C_T and C may be in any unit of measurement as long as the unit selected is the same for both.

7. INDUCTANCE

The following formulas can be used for calculating the total inductance in a circuit.

Inductors in series (with no mutual inductance) (Fig. 14):

$$L_{T} = L_{1} + L_{2} + L_{3} + \dots$$

$$L_{1} \qquad L_{2} \qquad L_{3}$$

$$L_{1} \qquad L_{2} \qquad L_{3}$$
Fig. 14

Inductors in parallel (with no mutual inductance) (Fig. 15):

$$L_{\mathrm{T}} = rac{1}{rac{1}{L_{1}} + rac{1}{L_{2}} + rac{1}{L_{3}} + \dots }$$

Two inductors in parallel (with no mutual inductance) (Fig. 16):

$$L_{\mathrm{T}} = \frac{L_1 \times L_2}{L_1 + L_2}$$

where,

Fig. 16

 $L_{\rm T}$ is the total inductance of the circuit,

 L_1 , L_2 , and L_3 are the inductances of the individual inductors (coils).

The parallel-resistance nomograph in § 5 can also be used to determine the total inductance of inductors in parallel.

(A) Mutual Inductance

The mutual inductance of two coils with fields interacting can be determined by:

$$M = \frac{L_{\text{A}} - L_{\text{B}}}{4}$$

where.

M is the mutual inductance expressed in the same unit as $L_{\mathtt{A}}$ and $L_{\mathtt{B}}$,

 L_A is the total inductance of coils L_1 and L_2 with fields aiding,

 L_B is the total inductance of coils L_1 and L_2 with fields opposing.

(B) Coupled Inductance

The coupled inductance can be determined by the following formulas.

In parallel, with fields aiding:

$$m L_{T} = rac{1}{rac{1}{L_{1} + M} + rac{1}{L_{2} + M}}$$

In parallel, with fields opposing:

$$m L_{T} = rac{1}{rac{1}{L_{1} - M} + rac{1}{L_{2} - M}}$$

In series, with fields aiding:

$$L_T = L_1 + L_2 + 2M$$

In series, with fields opposing:

$$L_T = L_1 + L_2 - 2M$$

where.

 L_{T} is the total inductance, L_{1} and L_{2} are the inductances of the individual coils, M is the mutual inductance.

(C) Coupling Coefficient

When two coils are inductively coupled to give transformer action, the coupling coefficient is determined by:

$$K = \frac{M}{\sqrt{L_1 L_2}}$$

where,

K is the coupling coefficient, M is the mutual inductance, L_1 and L_2 are the inductances of the two coils.

(D) Energy Stored

The energy stored in an inductor can be determined by:

$$W=\frac{LI^2}{2}$$

where,

W is the energy in joules (watt-seconds), L is the inductance in henries, I is the current in amperes.

8. Q FACTOR

The ratio of reactance to resistance is known as the Q factor. It can be determined by the following formulas.

For a coil wherein R and L are in series:

$$Q = \frac{\omega L}{R}$$

For a capacitor wherein R and C are in series:

$$Q = \frac{1}{\omega RC}$$

For a capacitor wherein R and C are in parallel:

$$Q = \omega RC$$

where.

Q is a ratio expressing the factor of merit,

 ω equals $2\pi f$,

L is the inductance in henries.

R is the resistance in ohms,

C is the capacitance in farads.

9. RESONANCE

The resonant frequency, or the frequency at which the reactances of the circuit add up to zero $(X_L = X_C)$, is determined by the formula:

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$

where.

f_R is the resonant frequency in cycles per second,

L is the inductance in henries,

C is the capacitance in farads.

The resonant frequency of various combinations of inductance and capacitance can also be obtained from the reactance charts in § 14. Simply lay a straightedge across the values of inductance and capacitance, and read the resonant frequency from the frequency scale of the chart.

10. ADMITTANCE

The measure of the ease with which alternating current flows in a circuit is the admittance of the circuit.

Admittance of a series circuit is given by:

$$Y = \frac{1}{\sqrt{R^2 + X^2}}$$

Admittance is also expressed as the reciprocal of impedance; thus:

$$Y = \frac{1}{Z}$$

where,

Y is the admittance in mhos, R is the resistance in ohms, X is the reactance in ohms, Z is the impedance in ohms.

11. SUSCEPTANCE

The susceptance of a series circuit is given by:

$$B = \frac{X}{R^2 + X^2}$$

When the resistance is zero, susceptance becomes the reciprocal of reactance; thus:

$$B = \frac{1}{X}$$

where.

B is the susceptance in mhos, X is the reactance in ohms, R is the resistance in ohms.

12. CONDUCTANCE

Conductance is the measure of the ability of a component to conduct electricity. Conductance for DC circuits is expressed as the reciprocal of resistance; therefore:

$$G = \frac{1}{R}$$

where,

G is the conductance in mhos, R is the resistance in ohms.

Ohm's law formulas when conductance is considered are:

$$I = EG$$

$$G = \frac{I}{E}$$

$$E = \frac{I}{G}$$

where,

I is the current in amperes, E is the voltage in volts, G is the conductance in mhos, R is the resistance in ohms.

13. ENERGY UNITS

Energy is the capacity or ability to do work. The joule is a unit of energy. One joule is the amount of energy required to maintain a current of one ampere for one second through a resistance of one ohm. It is equivalent to a watt-second. The watt-hour is the practical unit of energy; 3600 watt-seconds equals one watt-hour. The number of watt-hours is calculated:

Watt-hours =
$$P \times T$$

where,

P is the power in watts,

T is the time in hours the power is dissipated.

See § 6 for the energy stored in a capacitor, and § 7 for the energy stored in an inductor.

14. REACTANCE

The opposition to the flow of alternating current by the inductance or capacitance of a component or circuit is called the reactance.

(A) Capacitive Reactance

The reactance of a capacitor may be calculated by the formula:

$$X_{\rm C} = \frac{1}{2\pi f C}$$

where,

X_C is the reactance in ohms, f is the frequency in cycles per second, C is the capacitance in farads.

(B) Inductive Reactance

The reactance of an inductor may be calculated by the formula:

$$X_L = 2\pi f L$$

where,

X₁, is the reactance in ohms, f is the frequency in cycles per second, L is the inductance in henries.

(C) Reactance Charts

Charts for determining unknown values of reactance, inductance, capacitance, and frequency are given on the following pages. The chart in Fig. 17A covers 1 to 1,000 cycles, Fig. 17B covers 1 to 1,000 kilocycles, and Fig. 17C covers 1 to 1,000 megacycles.

To find the amount of reactance of a capacitor at a given frequency, lay the straightedge across the capacitor value and the frequency. Then read the reactance from the reactance scale. By extending the line, the value of an inductance which will give the same reactance can be obtained.

Since $X_C = X_L$ at resonance, by laying the straightedge across the capacitance and inductance values, the resonant frequency of the combination can be determined.

Example—If the frequency is 10 cycles per second and the capacitance is 50 mfd, what is the reactance of the capacitor? What value of inductance will give this same reactance?

ANSWER: The reactance is 310 ohms. The inductance needed to produce this same reactance is 5 henries. Thus, it follows that a 50-mfd capacitor and a 5-henry choke are resonant at 10 cps. [Place the straightedge, on the proper chart (Fig. 17A), across 10 cps and 50 mfd. Read the values indicated on the reactance and inductance scales.]

15. IMPEDANCE

The basic formulas for calculating the total impedance are as follows.

For parallel circuits:

$$Z = \frac{1}{\sqrt{G^2 + B^2}}$$

Reactance Chart — 1 cps to 1 kc

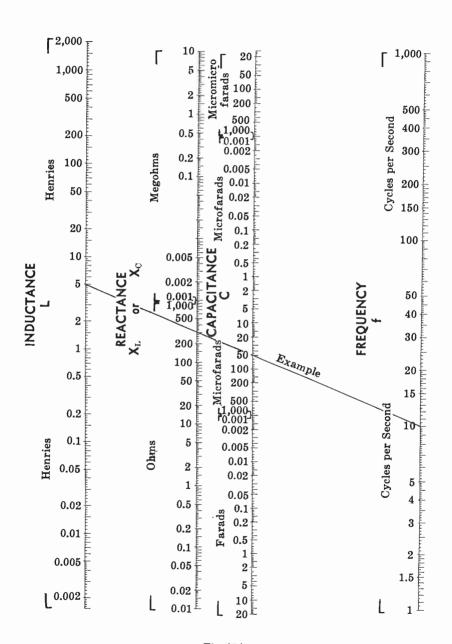


Fig. 17A

Reactance Chart — 1 kc to 1 mc

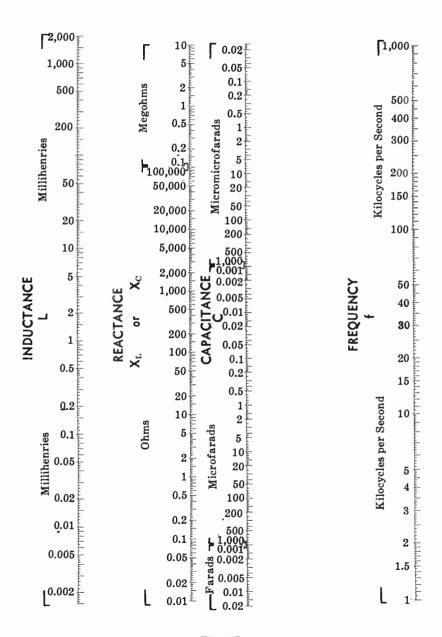


Fig. 17B

Reactance Chart — 1 mc to 1,000 mc

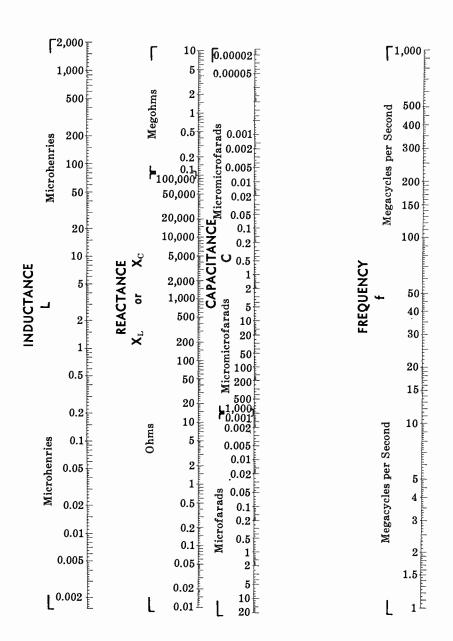


Fig. 17C

For series circuits:

$$Z = \sqrt{R^2 + X^2}$$

where,

Z is the total impedance.

G is the total conductance or the reciprocal of the total parallel resistance,

B is the total susceptance,

R is the total resistance,

X is the total reactance.

The following formulas can be used to find the impedance of the various combinations of inductance, capacitance, and resistance.

For a single resistance (Fig. 18):

$$Z = R$$
 $\theta = 0^{\circ}$

R
Fig. 18

For resistances in series (Fig. 19):

$$Z=R_1+R_2+R_3+\ldots$$
 $\theta=0^\circ$ R_1 R_2 R_3 Fig. 19

For a single inductance (Fig. 20):

For inductances in series (with no mutual inductance) (Fig. 21):

$$Z = X_{L_1} + X_{L_2} + X_{L_3} + \dots$$
 $\theta = 90^{\circ}$
 L_1
 L_2
 L_3
Fig. 21

For a single capacitance (Fig. 22):

$$Z = X_{C}$$
 $\theta = 90^{\circ}$

C
Fig. 22

For capacitances in series (Fig. 23):

$$Z = X_{C_1} + X_{C_2} + X_{C_3} + \dots$$

$$\theta = 90^{\circ}$$

$$C_1 \quad C_2 \quad C_3$$

$$Fig. 23$$

For resistance and inductance in series (Fig. 24):

$$Z = \sqrt{R^2 + X_L^2}$$

$$\theta = \arctan \frac{X_L}{R}$$
 Fig. 24

For resistance and capacitance in series (Fig. 25):

$$Z = \sqrt{R^2 + X_c^2}$$
 $\theta = \arctan \frac{X_c}{R}$
 R
 $Fig. 25$

For inductance and capacitance in series (Fig. 26):


When X_L is larger than X_C

$$\mathbf{Z} = \mathbf{X_L} - \mathbf{X_C}$$

When X_c is larger than X_L

$$Z = X_C - X_L$$

 $\theta = 0^\circ$ when $X_L = X_C$

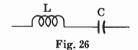

For resistance, inductance, and capacitance in series (Fig. 27):

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\theta = \arctan \frac{X_L - X_C}{R}$$

$$R$$
Fig. 27

For resistances in parallel (Fig. 28):

$$Z = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

$$\theta = 0^{\circ}$$

$$R_z$$

$$R_s$$

$$R_s$$

$$R_s$$

$$R_s$$

$$R_s$$

$$R_s$$

For inductances in parallel (with no mutual inductance) (Fig. 29):

$$Z = \frac{1}{\frac{1}{X_{L_1}} + \frac{1}{X_{L_2}} + \frac{1}{X_{L_3}} + \dots$$

$$\theta = 90^{\circ}$$

$$L_3$$

$$Fig. 29$$

For capacitances in parallel (Fig. 30):

$$Z = \frac{1}{\frac{1}{X_{C_1}} + \frac{1}{X_{C_2}} + \frac{1}{X_{C_3}} + \dots$$

$$\theta = 90^{\circ}$$

$$C_1$$

$$C_2$$

$$C_3$$

$$C_3$$
Fig. 30

For resistance and inductance in parallel (Fig. 31):

$$Z = \frac{RX_L}{\sqrt{R^2 + X_L^2}}$$

$$\theta = \arctan \frac{R}{X_L}$$
Fig. 31

For capacitance and resistance in parallel (Fig. 32):

$$Z = \frac{RX_{C}}{\sqrt{R^{2} + X_{C}^{2}}}$$

$$\theta = \arctan \frac{R}{X_{C}}$$

$$Fig. 32$$

For capacitance and inductance in parallel (Fig. 33):

When X_L is larger than X_C :

$$Z = \frac{X_L X_C}{\overline{X_L - X_C}}$$
When X_C is larger than X_L :
$$Z = \frac{X_C X_L}{\overline{X_C - X_L}}$$

$$\theta = 0^{\circ} \text{ when } X_L = X_C$$

For inductance, capacitance, and resistance in parallel (Fig. 34):

$$Z = \frac{RX_LX_C}{\sqrt{X_L^2 X_C^2 + R^2(X_L - X_C)}}^2$$

$$\theta = \arctan \frac{R(X_L - X_C)}{X_LX_C}$$

$$R$$

$$C$$

$$C$$

$$Fig. 34$$

For inductance and series resistance in parallel with resistance (Fig. 35):

$$Z = R_2 \sqrt{\frac{R_1^2 + X_L^2}{(R_1 + R_2)^2 + X_L^2}}$$

$$\theta = \arctan \frac{X_L R_2}{R_1^2 + X_L^2 + R_1 R_2}$$
Fig. 35

For inductance and series resistance in parallel with capacitance (Fig. 36):

$$Z = X_C \sqrt{\frac{R^2 + X_L^2}{R^2 + (X_L - X_C)^2}}$$

$$\theta = \arctan \frac{X_L(X_C - X_L) - R^2}{RX_C}$$

$$Fig. 36$$

For capacitance and series resistance in parallel with inductance and series resistance (Fig. 37):

ductance and series resistance (Fig. 37): L
$$Z = \sqrt{\frac{(R_1^2 + X_L^2) (R_2^2 + X_C^2)}{(R_1 + R_2)^2 + (X_L - X_C)^2}}$$

$$X_L (R_2^2 + X_C^2) - X_C (R_1^2 + X_L^2)$$
Fig. 37

 $\theta = \arctan \frac{X_{L} \ (R_{2}{}^{2} + X_{C}{}^{2}) \ - X_{C} \ (R_{1}{}^{2} + X_{L}{}^{2})}{R_{1} \ (R_{2}{}^{2} + X_{C}{}^{2}) \ + R_{2} \ (R_{1}{}^{2} + X_{L}{}^{2})}$

where.

Z is the impedance in ohms,

R is the resistance in ohms, L is the inductance in henries,

 X_L is the inductive reactance in ohms,

X_c is the capacitive reactance in ohms,

 θ is the phase angle in degrees by which the current leads the voltage in a capacitive circuit or lags the voltage in an inductive circuit. 0° indicates an in-phase condition.

16. OHM'S LAW FOR ALTERNATING CURRENT

The fundamental Ohm's law formulas for alternating current are given by:

$$E = IZ$$

$$I = \frac{E}{Z}$$

$$Z = \frac{E}{I}$$
Fig. 38

where,

E is the voltage in volts, I is the current in amperes, Z is the impedance in ohms.

The power expended in an AC circuit is calculated by the formula:

$$P = EI \cos \theta$$

where,

P is the power in watts, E is the voltage in volts, I is the current in amperes, θ is the phase angle in degrees.

The phase angle is the difference in degrees by which the current leads or lags the voltage in a reactive circuit. In a series circuit, the phase angle is determined by the formula:

$$\theta = \arctan \frac{X}{R}$$

where,

X is the inductive or capacitive reactance in ohms, R is the nonreactive resistance in ohms.

Therefore:

For a purely resistive circuit:

$$heta = 0^{\circ}$$
 $\cos \theta = 1$
 $P = EI$

For a resonant circuit:

$$\theta = 0^{\circ}$$
 $\cos \theta = 1$
 $P = EI$

For a purely reactive circuit:

$$\theta = 90^{\circ}$$

$$\cos \theta = 0$$

$$P = 0$$

17. AVERAGE, RMS, PEAK, AND PEAK-TO-PEAK VOLTAGE AND CURRENT

The following table can be used to convert sinusoidal voltage (or current) values from one method of measurement to another. To use the table, first find the given type of reading in the left-hand column, then find the desired type of reading across the top of the table. To convert the given value to the desired value, multiply the given value by the factor listed under the desired value.

Example—What factor must peak voltage be multiplied by to obtain rms voltage?

ANSWER: .707.

Table I. Average, Rms, Peak, and Peak-to-Peak Values

Given	Multiplying Factor To Get							
Value	Average	Rms	Peak	Peak-to-Peak				
Average	_	1.11	1.57	3.14				
Rms	0.9	_	1.414	2.828				
Peak	0.637	0.707	_	2.0				
Peak-to-Peak	0,32	0.3535	0.5					

18. POWER FACTOR

Power factor is the ratio of true power to apparent power in an alternating circuit. Thus:

$$pf = \frac{P_T}{P_A} = \frac{EI \cos \theta}{EI}$$

$$= \cos \theta$$
Fig. 39

where,

pf is the power factor, P_T is the true power in watts, P_A is the apparent power in volt-amperes, EI $\cos \theta$ is the true power in watts, EI is the apparent power in volt-amperes.

Therefore:

For a purely resistive circuit:

$$\theta = 0^{\circ}$$
pf = 1

For a resonant circuit:

$$\theta = 0^{\circ}$$
pf = 1

For a purely reactive circuit:

$$\theta = 90^{\circ}$$
pf = 0

19. TIME CONSTANTS

A certain amount of time is required, after a DC voltage has been applied to an R-C or R-L circuit, before the capacitor can charge or the current can build up to a portion of the full value. This time is called the time constant of the circuit. However, the time constant is not the time required for the voltage or current to reach the full value; instead, it is the time required to reach 63.2% of full value. During the next time constant, the capacitor is charged or the current builds


up to 63.2% of the remaining difference, or to 86.5% of the full value. Table II gives the per cent of full charge on a capacitor, or current buildup in an inductance after each time constant. Theoretically, the charge on the capacitor, or the current through the coil, can never reach 100%. However, it is usually considered to be 100% after five time constants.

o. G						
No. of Time Constants	% Charge or Buildup	% Discharge or Decay				
1	63.2	36.8				
2	86.5	13.5				
3	95.0	5.0				
4	98.2	1.8				
5	99.3	0.7				

Table II. Time Constants versus Per Cent of Voltage or Current

Likewise, when the voltage source is removed, the capacitor will discharge or the current will decay 63.2%, or to 36.8% of full value during the first time constant. Table II also gives the per cent of full voltage after each time constant for discharge of a capacitor or decay of the current through a coil.

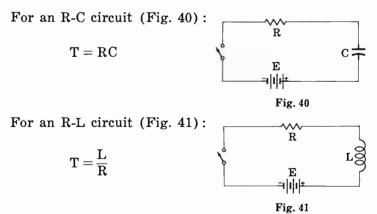The time per time constant is calculated as follows.



where,

T is the time in seconds,

R is the resistance in ohms,

C is the capacitance in farads,

L is the inductance in henries.

In addition, the values can also be expressed by the following relationships:

${f T}$	\mathbf{R}	${f C}$ or ${f L}$
seconds	megohms	microfarads
seconds	megohms	microhenries
microseconds	ohms	microfarads
microseconds	megohms	micromicrofarads
microseconds	ohms	microhenries

20. TRANSFORMER FORMULAS

In a transformer, the relationships between the number of turns in the primary and secondary, the voltage across each winding, and the current through the windings are expressed by the equations:

$$\frac{E_{\scriptscriptstyle p}}{E_{\scriptscriptstyle s}} = \frac{N_{\scriptscriptstyle p}}{N_{\scriptscriptstyle s}} \hspace{1cm} \text{and} \hspace{1cm} \frac{E_{\scriptscriptstyle p}}{E_{\scriptscriptstyle s}} = \frac{I_{\scriptscriptstyle s}}{I_{\scriptscriptstyle p}}$$

By rearranging these equations, any unknown can be determined from the following formulas:

$$\begin{split} E_{p} &= \frac{E_{s}N_{p}}{N_{s}} = \frac{E_{s}I_{s}}{I_{p}} \\ E_{s} &= \frac{E_{p}N_{s}}{N_{p}} = \frac{E_{p}I_{p}}{I_{s}} \\ N_{p} &= \frac{E_{p}N_{s}}{E_{s}} = \frac{N_{s}I_{s}}{I_{p}} \\ N_{s} &= \frac{E_{s}N_{p}}{E_{p}} = \frac{N_{p}I_{p}}{I_{s}} \\ I_{p} &= \frac{E_{s}I_{s}}{E_{p}} = \frac{N_{s}I_{s}}{N_{p}} \\ I_{s} &= \frac{E_{p}I_{p}}{E_{s}} = \frac{N_{p}I_{p}}{N_{s}} \end{split}$$

The turns ratio of a transformer is determined by the following formulas:

For a step-up transformer:

$$T = \frac{N_s}{N_p}$$

For a step-down transformer:

$$T = \frac{N_{\rm p}}{N_{\rm s}}$$

The impedance ratio of a transformer is determined by:

$$Z = T^2$$

The impedance of an unknown winding is determined by the following:

For a step-up transformer:

$$Z_p = \frac{Z_s}{Z}$$

$$Z_s = Z \times Z_p$$

For a step-down transformer:

$$\begin{split} Z_p &= Z \times Z_s \\ Z_s &= \frac{Z_p}{Z} \end{split}$$

where,

 E_p is the voltage across the primary winding, E_s is the voltage across the secondary winding, N_p is the number of turns in the primary winding, N_s is the number of turns in the secondary winding, I_p is the current through the primary winding, I_s is the current through the secondary winding, I_s is the turns ratio, I_s is the impedance ratio, I_s is the impedance of the primary winding, I_s is the impedance of the secondary winding, I_s is the impedance of the secondary winding.

21. VOLTAGE REGULATION

When a load is connected to a power supply, the output voltage drops because more current flows through the resistive elements of the power supply. Voltage regulation is a measure of how much the voltage drops and is usually expressed as a percentage. It is determined by the following formula:


$$\% R = \frac{E_1 - E_2}{E_2} \times 100$$

where,

%R is the voltage regulation in per cent, E_1 is the no-load voltage, E_2 is the voltage under load.

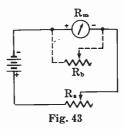22. DC METER FORMULAS

The basic instrument for testing current and voltage is the moving-coil meter. The meter can be either a DC milliammeter or a DC microammeter. A series resistor converts the meter to a DC voltmeter, and a parallel resistor converts the meter to a DC ammeter. The resistance of the meter movement is determined first, as follows. Connect a suitable variable resistor R_a and a battery as shown in Fig. 43. Adjust resistor R_a until full-scale deflection is obtained. Then connect a variable resistor R_b in parallel with the meter, and adjust R_b until half-scale deflection is obtained. Disconnect



 $R_{\mbox{\tiny b}}$ and measure its resistance. The measured value is the resistance of the meter movement.

(A) Voltage Multipliers

$$R = \frac{E_s}{I_s} - R_m$$

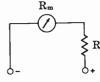



Fig. 44

where,

R is the multiplier resistance in ohms, E_s is the full-scale reading in volts, I_s is the full-scale reading in amperes, R_m is the meter resistance in ohms.

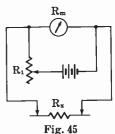(B) Shunt-type Ohmmeter for Low Resistance

$$R_{\mathbf{X}} = R_{\mathbf{m}} \frac{I_2}{I_1 - I_2}$$



where,

R_x is the unknown resistance,

R_m is the meter resistance in ohms,


 I_1 is the current reading with probes open,

I₂ is the current reading with probes connected across unknown resistor,

R₁ is a variable resistance for current limiting to keep meter adjusted for full-scale reading with probes open.

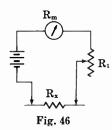(C) Series-type Ohmmeter for High Resistance

$$R_X = (R_1 + R_m) \frac{I_1 - I_2}{I_2}$$



where,

Rx is the unknown resistance,

R₁ is a variable resistance adjusted for full-scale reading with probes shorted together,

R_m is the meter resistance in ohms,

 I_1 is the current reading with probes shorted,

I₂ is the current reading with unknown resistor connected.

(D) Ammeter Shunts

$$R = \frac{R_m}{N-1} \! = \! \frac{I_m \; R_m}{I_s}$$



Fig. 47

where,

R is the resistance of the shunt, $R_{\rm m}$ is the meter resistance in ohms, N is the scale multiplication factor, $I_{\rm m}$ is the meter current, $I_{\rm s}$ is the shunt current.

(E) Ammeter With Multirange Shunt

$$R_2 = \frac{(R_1 + R_2) + R_m}{N}$$

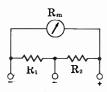


Fig. 48

where,

R₂ is the intermediate value in ohms,

 $R_1 + R_2$ is the total shunt resistance for lowest full-scale reading,

R_m is the meter resistance in ohms, N is the scale multiplication factor.

23. FREQUENCY AND WAVELENGTH

(A) Formulas

Since the frequency is the number of complete cycles per second and since radio waves travel at a fixed speed, it follows that a complete cycle occupies a given distance in space. The distance between two corresponding parts of two waves (the two positive or negative crests or the points where the two waves cross the zero axis in a given direction) constitutes the wavelength. If either the frequency or the wavelength is known, the other can be computed as follows:

$$f = \frac{300,000}{\lambda}$$
$$\lambda = \frac{300,000}{f}$$

where,

f is the frequency in kilocycles, λ is the wavelength in meters.

If it is desired to calculate the wavelength in feet, the following formulas should be used:


$$f = \frac{984,000}{\lambda}$$
$$\lambda = \frac{984,000}{f}$$

where,

f is the frequency in kilocycles, λ is the wavelength in feet.

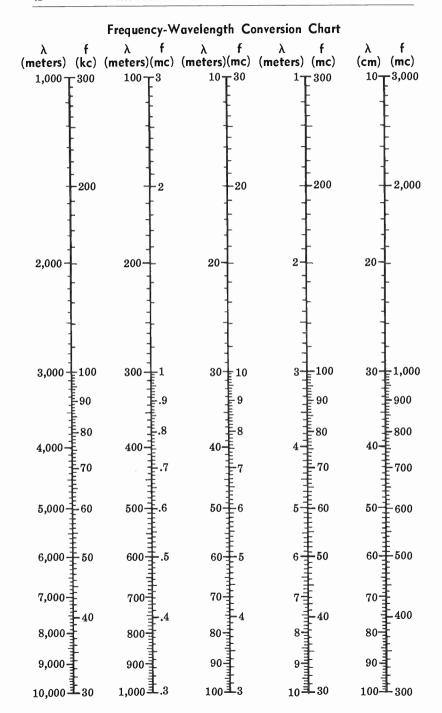(B) Conversion Chart

The wavelength of any frequency from 30 kc to 3000 mc can be read directly from the chart in Fig. 49. Likewise, if the wavelength is known, the corresponding frequency can be obtained from the chart for wavelengths from 10 centimeters to 1000 meters. To use the chart, merely find the



known value (either frequency or wavelength) on one of the scales, and then read the corresponding value from the opposite side of the scale.

Example—What is the wavelength of a 4-mc signal?

ANSWER: 75 meters. (Find 4 mc on the third scale from the left. Opposite 4 mc on the frequency scale we find 75 meters on the wavelength scale.)

24. TRANSMISSION-LINE FORMULAS

The characteristic impedance of a transmission line is defined as the input impedance of a line of the same configuration and dimensions but of infinite length. When a line of finite length is terminated with an impedance equal to its own characteristic impedance, the line is said to be matched.

(A) Coaxial Line

The characteristic impedance of a coaxial line is given by:

$$Z_{o} = \frac{138}{\sqrt{k}} \log \frac{D}{d}$$

where.

Z_o is the characteristic impedance,

D is the inside diameter of the outer conductor,

d is the outside diameter of the inner conductor expressed in the same units as D,

k is the dielectric constant of the insulating material* (k equals 1 for dry air).

The attenuation of coaxial line in decibels per foot can be determined by the formula:

$$a = \frac{4.6 \sqrt{f} (D + d)}{D \times d \left(\log \frac{D}{d}\right)} \times 10^{-6}$$

where.

a is the attenuation in decibels per foot of line,

f is the frequency in megacycles,

D is the inside diameter of the outer conductor in inches, d is the outside diameter of the inner conductor in inches.

^{*} For a list of dielectric constants of materials, see § 27.

(B) Parallel-Conductor Line

The characteristic impedance of parallel-conductor line (twin-lead) is determined by the formula:

$$Z_{o} = \frac{276}{\sqrt{k}} \log \frac{2D}{d}$$

$$\downarrow D$$

where,

Zo is the characteristic impedance,

D is the center-to-center distance between conductors, d is the diameter of the conductors in the same units as D, k is the dielectric constant of the insulating material between conductors* (k equals 1 for dry air).

25. MODULATION FORMULAS

(A) Amplitude Modulation

The amount of modulation of an amplitude-modulated carrier is referred to as the percentage of modulation. It can be determined by the following formulas:

$$\% M = \frac{E_{c} - E_{T}}{2E_{AV}} \times 100$$
or,
 $\% M = \frac{E_{c} - E_{T}}{E_{c} + E_{T}} \times 100$



Fig. 52

where,

%M is the percentage of modulation,

 \dot{E}_{c} is the amplitude of the crest of the modulated carrier, E_{T} is the amplitude of the trough of the modulated carrier, E_{AV} is the average amplitude of the modulated carrier.

Also, the percentage of modulation can be determined by applying the modulated carrier wave to the vertical plates and the modulating voltage wave to the horizontal plates of an oscilloscope. This produces a trapezoidal wave, as shown in Fig. 53. The dimensions A and B are proportional to the crest and trough amplitudes, respectively. The percentage

^{*} For a list of dielectric constants of materials, see § 27.

of modulation can be determined by measuring the height of A and B, and using the formula:

$$\%M = \frac{A - B}{A + B} \times 100$$



Fig. 53

where,

%M is the percentage of modulation, A and B are the dimensions measured in Fig. 53.

The sideband power of an AM carrier is determined by:

$$P_{\scriptscriptstyle SB} = \frac{\%\,M^2}{2} \times P_{\scriptscriptstyle C}$$

The total radiated power is the sum of the carrier and the radiated powers:

$$P_{\rm T} = P_{\rm SB} + P_{\rm C}$$

where,

 P_{sr} is the sideband power (includes both sidebands), %M is the percentage of modulation,

P_c is the carrier power,

P_T is the total radiated power.

Note: The carrier power does not change with modulation.

(B) Frequency Modulation

In a frequency-modulated carrier, the amount the carrier frequency changes is determined by the amplitude of the modulating signal, and the number of times the changes occur per second is determined by the frequency of the modulating signal.

The percentage of modulation of an FM carrier can be computed from:

$$\%M = \frac{\Delta f}{\Delta f \text{ for } 100\%M} \times 100$$

where,

%M is the percentage of modulation,

Af is the change in frequency, or the deviation,

Af for 100% M is the change in frequency for a 100% modulated carrier. (For commercial FM, 75 kc; for television sound, 25 kc; and for two-way radio, 15 kc.)

The modulation index of an FM carrier is determined by:

$$M = \frac{f_\text{d}}{f_\text{a}}$$

where,

M is the modulation index.

 f_d is the deviation in frequency, f_a is the modulating audio frequency in the same units as f_d.

26. DECIBELS AND VOLUME UNITS

(A) Equations

The number of decibels corresponding to a given power ratio is 10 times the common logarithm of the ratio. Thus:

$$db = 10 \log \frac{P_2}{P_1}$$

The number of decibels corresponding to a given voltage or current ratio is 20 times the common logarithm of the ratio. Thus, when the impedances across which the signals are being measured are equal, the equations are:

$$db = 20 \log \frac{E_2}{E_1}$$

$$db = 20 \log \frac{I_2}{I_1}$$

If the impedances across which the signals are measured are not equal, the equations become:

$$\begin{split} \text{db} &= 20 \, \log \frac{E_2 \sqrt{Z_1}}{E_1 \sqrt{Z_2}} \\ \text{db} &= 20 \, \log \frac{I_2 \sqrt{Z_2}}{I_1 \sqrt{Z_1}} \end{split}$$

(B) Reference Levels

The decibel is not an absolute value; it is a means of stating the ratio of a level to a certain reference level. Usually, when no reference level is given, it is 6 millivolts across a 500-ohm impedance. However, the reference level should be stated whenever a value in db's is given. Other units, which do have specific reference levels, have been established. Some of the more common are:

dbk -1 kilowatt

dbm -1 milliwatt, 600 ohms

dby -1 volt

dbw ---1 watt

dbvg -voltage gain

dbrap—decibels above a reference acoustical power of 10^{-16} watts

VU —1 milliwatt, 600 ohms (complex waveforms varying in both amplitude and frequency).

(C) Decibel Table

The decibel table on the following pages lists most of the current, voltage, and power ratios encountered, with their decibel values. If a db value is not listed and it is desired to find the corresponding ratio, first subtract one of the given values from the unlisted value (select a value so the remainder will also be listed). Then multiply the ratios given in the chart for each value. To convert a ratio which is not given in the table to a db value, first factor the ratio so that each factor will be a listed value; then find the db equivalents for each factor and add them.

Example 1—Find the db equivalent of a power ratio of .631.

ANSWER: 2-db loss.

Example 2-Find the current ratio corresponding to a gain of 43 db.

ANSWER: 141. [First find the current ratio for 40 db (100); then find the current ratio for 3 db (1.41). Multiplying, $100 \times 1.41 = 141$.]

Example 3—Find the db value corresponding to a voltage ratio of 150.

ANSWER: 43.5. [First factor 150 into 1.5×100 . The db value for a voltage ratio of 100 is 40; the db value for a voltage ratio of 1.5 is 3.5 (approximately). Therefore, the db value for a voltage ratio is 40 + 3.5 or 43.5 db.]

Table III. Decibel Table (0 to 10.9 Db)

		ent or e Ratio	Power	Ratio		Curre Voltage		Power	Ratio
DЬ	Gain	Loss	Gain	Loss	DЬ	Gain	Loss	Gain	Loss
0	1.000	1.0000	1.000	1.0000	5.5	1.884	.5309	3.548	.2818
.1	1.012	.9886	1.023	.9772	5.6	1.905	.5248	3.631	.2754
.2	1.023	.9772	1.047	.9550	5.7	1.928	.5188	3.715	.2692
.3	1.035	.9661	1.072	.9333	5.8	1.950	.5129	3.802	.2630
.4	1.047	.9550	1.096	.9120	5.9	1.972	.5070	3.890	.2570
.5	1.059	.9441	1.122	.8913	6.0	1.995	.5012	3.981	.2512
.6	1.072	.9333	1.148	.8710	6.1	2.018	.4955	4.074	.2455
.7	1.084	.9226	1.175	.8511	6.2	2.042	.4898	4.169	.2399
.8	1.096	,9120	1.202	.8318	6.3	2.065	.4842	4.266	.2344
.9	1.109	.9016	1.230	.8128	6.4	2.089	.4786	4.365	.2291
1.0	1.122	.8913	1.259	.7943	6.5	2.113	.4732	4.467	.2239
1.1	1.135	.8810	1.288	.7762	6.6	2,138	.4677	4.571	.2188
1.2	1.148	.8710	1.318	.7586	6.7	2.163	.4624	4.677	.2138
1.3	1.161	.8610	1.349	.7413	6.8	2.188	.4571	4.786	.2089
1.4	1.175	.8511	1.380	.7244	6.9	2.213	.4519	4.898 5.012	.2042 .1995
1.5	1.189	.8414	1.413	.7079	7.0	2.239	.4467 .4416	5.129	.1950
1.6	1.202	.8318	1.445	.6918 .6761	7.1 7.2	2.291	.4365	5.248	.1905
1.7	1.216	.8222	1.479	.6607	7.2	2.291	.4305	5.370	.1862
1.8	1.230	.8128 .8035	1.549	.6457	7.4	2.344	.4266	5.495	.1820
	ł .				7.5	2.371	.4217	5.623	.1778
2.0	1.259	.7943	1.585	.6310	7.5	2.399	.4169	5.754	.1738
2.1	1.274	.7852	1.622	.6166 .6026	7.7	2.427	.4121	5.888	.1698
2.2	1.288	.7762 .7674	1.660	.5888	7.8	2.455	.4074	6.026	.1660
2.3	1.303	.7586	1.738	.5754	7.9	2.483	.4027	6.166	.1622
2.4	1.334	.7499	1.778	.5623	8.0	2.512	.3981	6.310	.1585
2.6	1.349	.7413	1.820	.5495	8.1	2.541	.3936	6.457	.1549
2.7	1.365	.7328	1.862	.5370	8.2	2.570	.3890	6.607	.1514
2.8	1.380	.7244	1.905	.5248	8.3	2.600	.3846	6.761	.1479
2.9	1.396	.7161	1.950	.5129	8.4	2.630	.3802	6.918	.1445
3.0	1.413	.7079	1.995	.5012	8.5	2.661	.3758	7.079	.1413
3.1	1.429	.6998	2.042	.4898	8.6	2.692	.3715	7.244	.1380
3.2	1.445	.6918	2.089	.4786	8.7	2.723	.3673	7.413	.1349
3.3	1.462	.6839	2.138	.4677	8.8	1	.3631	7.586	.1318
3.4	1.479	.6761	2.188	.4571	8.9	2.786	.3589	7.762	.1288
3.5	1.496	.6683	2.239	.4467	9.0	2.818	.3548	7.943	.1259
3.6	1.514	.6607	2.291	.4365	9.1	2.851	.3508	8.128	.1230
3.7	1.531	.6531	2.344	.4266	9.2		.3467	8.318	.1202
3.8	1.549	.6457	2.399	.4169	9.3	2.917	.3428	8.511	.1175
3.9	1.567	.6383	2.455	.4074	9.4	1	.3388	8.710	.1148
4.0	1.585	.6310	2.512	.3981	9.5		.3350	8.913	.1122
4.1	1.603	.6237	2.570	.3890	9.6	1	.3311	9.120	.1096
4.2	1.622	.6166	2.630	.3802	9.7		.3273	9.333	.1072
4.3		.6095	2.692	.3715	9.8		.3236	9.550	.1047
4.4		.6026	2.754	.3631	9.9		.3199	9,772	.1023
4.5	1.679	.5957	2.818	.3548	10.0		.3162	10.000	.1000
4.6	1.698	.5888	2.884	.3467	10.1		.3126	10.23	.09772
4.7	1.718	.5821	2.951	.3388	10.2		.3055	10.47	.09333
4.8		.5754	3.020	.3311	10.3	1	.3020	10.72	.09333
4.9		.5689	3.090	.3236	10.4	1	1	1	1
5.0		.5623	3.162	.3162	10.5		.2985	11.22	.08913
5.1	1.799	.5559	3.236	.3090	10.6		.2951	11.48	.08511
5.2		.5495	3.311	.3020	10.7	1	.2884	12.02	.08318
5.3	1.841	.5433	3.388	.2951		3.508		12.30	.08128

Table III. Decibel Table—(Cont'd) (11.0 to 19.9 Db)

	Curre					Curre Voltage		Power	Patio
	Voltage	Ratio	Power	Ratio	- 1				
Db	Gain	Loss	Gain	Loss	Db	Gain	Loss	Gain	Loss
11.0	3.548	.2818	12.59	.07943	15.5	5.957	.1679	35.48	.02818
11.1	3.589	.2786	12.88	.07762	15.6	6.026	.1660	36.31	.02754
11.2	3.631	.2754	13.18	.07586	15.7	6.095	.1641	37.15	.02692
11.3	3.673	.2723	13.49	.07413	15.8	6.166	.1622	38.02	.02630
11.4	3.715	.2692	13.80	.07244	15.9	6.237	.1603	38.90	.02570
11.5	3.758	.2661	14.13	.07079	16.0	6.310	.1585	39.81	.02512
11.6	3.802	.2630	14.45	.06918	16.1	6.383	.1567	40.74	.02455
11.7	3.846	.2600	14.79	.06761	16.2	6.457	.1549	41.69	.02399
11.8	3.890	.2570	15.14	.06607	16.3	6.531	.1531	42.66	.02344
11.9	3.936	.2541	15.49	.06457	16.4	6.607	.1514	43.65	.02291
12.0	3.981	.2512	15.85	.06310	16.5	6.683	.1496	44.67	.02239
12.1	4.027	.2483	16.22	.06166	16.6	6.761	.1479	45.71	.02188
12.2	4.074	.2455	16.60	.06026	16.7	6.839	.1462	46.77	.02138
12.3	4.121	.2427	16.98	.05888	16.8	6.918	.1445	47.86	.02089
12.4	4.169	.2399	17.38	.05754	16.9	6.998	.1429	48.98	.02042
12.5	4.217	.2371	17.78	.05623	17.0	7.079	.1413	50.12	.01995
12.6	4.266	.2344	18.20	.05495	17.1	7.161	.1396	51.29	.01950
12.7	4.315	.2317	18.62	.05370	17.2	7.244	.1380	52.48	.01905
12.8	4.365	.2291	19.05	.05248	17.3	7.328	.1365	53.70	.01862
12.9	4.416	.2265	19.50	.05129	17.4	7.413	.1349	54.95	.01820
13.0	4.467	.2239	19.95	.05012	17.5	7.499	.1334	56.23	.01778
13.1	4.519	.2213	20.42	.04898	17.6	7.586	.1318	57.54	.01738
13.2	4.571	.2188	20.89	.04786	17.7	7.674	.1303	58.88	.01698
13.3	4.624	.2163		.04677	17.8	7.762	.1288	60.26	.01660
13.4	4.677	.2138	21.88	.04571	17.9		.1274	1	.01622
13.5	4.732	.2113	22.39	.04467	18.0		.1259		.01585
13.6	4.786	.2089		.04365	18.1		.1245		
13.7	4.842	.2065		.04266	18.2		.1230		.01514
13.8	4.898	.2042		.04169	18.3		.1216		.01479
13.9	4.955	.2018		.04074	18.4		.1202		.01445
14.0	5.012	.1995		.03981	18.5		.1189		.01413
14.1	5.070	.1972		.03890	18.6		.1175		.01380
14.2	5.129	.1950		.03802	18.7		.1161		.01349
14.3		.1928		.03715	18.8		.1148		.01318
14.4		.1905		.03631	18.9		.1135		.01288
14.5		.1884		.03548	19.0		.1122		.01259
14.6		.1862		.03467	19.1		.1109		.01230
14.7		.1841		.03388	19.2		.1096		.01202
14.8		.1820		.03311	19.3		.1084		.01175
14.9		.1799	1	.03236	19.4	1	.1072	1	.01148
15.0		.1778		.03162	19.5		.1059		.01122
15.1	5.689	.1758		.03090	19.6		.1047		.01096
15.2	5.754	.1738		.03020	19.7		.1035		.01072
15.3	5.821	.1718		.02951	19.8		.1023		.01047
15.4	5.888	.1698	34.67	.02884	19.9	9.886	.1012	97.72	.01023
		\perp			<u> </u>				

Note: For values from 20 to 180 db, see next page.

Table III. Decibel Table—(Cont'd) (20 to 180 Db)

	Current or V	oltage Ratio	Power	Ratio
DЬ	Gain	Loss	Gain	Loss
20.0	10.00	0.1000	100.00	0.01000
25.0	17.78	0.0562	3.162 X 10 ²	3.162 X 10 ⁻³
30.0	31.62	0.0316	10 ³	10-3
35.0	56.23	0.0178	3.162 X 10 ³	3.162 X 10 ⁻⁴
40.0	100.00	0.0100	104	10-4
45.0	177.8	0.0056	3.162 X 10 ⁴	3.162 X 10 ⁻⁵
50.0	316.2	0.0032	105	10-5
55.0	562.3	0.0018	3.162 X 10 ⁵	3.162 X 10 ⁻⁶
60.0	10 ³	10-3	10"	10-6
65.0	1.778 X 10 ³	5.623 X 10 ⁻⁴	3.162 X 10 ⁸	3.162 X 10 ⁻⁷
70.0	3.162 X 10 ³	3.162 X 10 ⁻⁴	107	10-7
75.0	5.623 X 10 ³	1.78 X 10 ⁻⁴	3.162 X 10 ⁷	3.162 X 10 ⁻⁸
80.0	104	10-4	10 ⁸	10-8
85.0	1.778 X 10 ⁴	5.623 X 10 ⁻⁵	3.162 X 10 ⁸	3.162 X 10 ⁻⁹
90.0	3.162 X 10 ⁴	3.162 X 10 ⁻⁵	10°	10-9
95.0	5.632 X 10 ⁴	1.78 X 10⁻⁵	3.162 X 10 ⁹	3.162 X 10 ⁻¹⁰
100.0	10 ⁵	10⁻⁵	1010	10-10
110.0	3.162 X 10 ⁵	3.162 X 10 ⁻⁶	1011	10-11
120.0	10 ⁶	10 ⁻⁶	1012	10-12
130.0	3.162 X 10 ⁶	3.162 X 10 ⁻⁷	1013	10-13
140.0	107	10-7	1014	10-14
150.0	3.162 X 10 ⁷	3.162 X 10 ⁻⁸	1015	10-15
160.0	10 ⁸	10 ⁻⁸	1010	10-16
170.0	3.162 X 10 ⁸	3.162 X 10 ⁻⁹	1017	10-17
180.0	10 ₈	10-9	10 ¹⁸	10 ⁻¹⁸

Constants and Standards

27. DIELECTRIC CONSTANTS OF MATERIALS

The dielectric constants of most materials vary for different temperatures and frequencies. Likewise, small differences in the composition of materials will cause differences in the dielectric constants. A list of materials, and the approximate range (where available) of their dielectric constants, are given in Table IV. The values shown are accurate enough for most applications. The dielectric constants of some materials (such as quartz, Styrofoam, and Teflon) do not change appreciably with frequency.

Table IV. Dielectric Constants of Materials

Material	Dielectric Constant (Approx.)	Material	Dielectric Constant (Approx.)
Air	1.0	Nylon	3.4-22.4
Amber	2.6-2.7	Pæper (dry)	1.5-3.0
Bakelite (asbestos base)	5.0-22	Paper (paraffin coated)	2.5-4.0
Bakelite (mica filled)	4.5-4.8	Paraffin (solid)	2.0-3.0
Beeswax	2.4-2.8	Plexiglass	2.6-3.5
Cambric (varnished)	4.0	Palyethylene	2.3
Celluloid	4.0	Polystyrene	2.4-3.0
Cellulose Acetate	3.1-4.5	Porcelain (dry process)	5.0-5.5
Durite	4.7-5.1	Parcelain (wet process)	5.8-6.5
Ebonite	2.7	Quartz	5.0
Fiber	5.0	Quartz (fused)	3.78
Formica	3.6-6.0	Rubber (hard)	2.0-4.0
Glass (electrical)	3.8-14.5	Ruby Mica	5.4
Glass (photographic)	7.5	Shellac (natural)	2.9-3.9
Glass (Pyrex)	4.6-5.0	Sificone (glass) (molding)	3.2-4.7
Glass (window)	7.6	Silicone (glass) (laminate)	3.7-4.3
Gutta Percha	2.4-2.6	Slate	7.0
Isolantite	6.1	Steatite (ceramic)	5.2-6.3
Lucite	2.5	Steatite (low loss)	4.4
Mica (electrical)	4.0-9.0	Styrofoam	1.03
Mica (clear India)	7.5	Teflon	2.1
Mica (filled phenolic)	4.2-5.2	Vaseline	2.16
Micarta	3.2-5.5	Vinylite	2.7-7.5
Mycalex	7.3-9.3	Water (distilled)	34-78
Neoprene	4.0-6.7	Wood (dry)	1.4-2.9

28. CONVERSION FACTORS

The following table lists the multiplying factors necessary to convert from one unit of measure to another, and vice versa. To use the table, locate the unit of measure you are converting from or the one you are converting to in the first column. Opposite this listing are the multiplying factors for converting either unit of measure to the other unit of measure.

Table V. Conversion Factors

To Convert	Into	Multiply by	Conversely, Multiply by
Acres	Square feet	4.356 X 10 ⁴	2.296 X 10 ⁻⁵
Acres	Square meters	4047	2.471 X 10 ⁻⁴
Acres	Square miles	1.5625 X 10 ⁻³	640
Amperes	Microamperes	10 ⁶	10 ⁻⁶
Amperes	Micromicroamperes	10 ¹²	10 ⁻¹²
Amperes Ampere-hours Ampere-turns Ampere-turns per cm.	Milliamperes	10 ³	10 ⁻³
	Coulombs	3600	2.778 X 10 ⁻⁴
	Gilberts	1.257	0.7958
	Ampere-turns per in.	2.54	0.3937
Angstrom units	Inches	3.937 X 10 ⁻⁹	2.54 X 10 ^N
Angstrom units	Meters	10 ⁻¹⁰	10 ¹⁰
Bars	Atmospheres	9.870 X 10 ⁻⁷	1.0133
Bars	Dynes per sq. cm.	10 ⁶	10 ⁻⁶
Bars	Pounds per sq. in.	14.504	6.8947 X 10 ⁻²
Btu	Ergs	1.0548 X 10 ¹⁰	9.486 X 10 ⁻¹¹
Btu	Foot-pounds	778.3	1.285 X 10 ⁻³
Btu	Joules	1054.8	9.480 X 10 ⁻⁴
Btu	Kilogram-calories	0.252	3.969
Btu per hour	Horsepower-hours	3.929 X 10 ⁻⁴	2545
Bushels Calories, gram Centigrade Centigrade	Cubic feet Joules Celsius Fahrenheit	1.2445 4.185 1 (°C X 9/5) + 32 = °F	0.8036 0.2389 1 (°F - 32) X 5/9 = °C
Centigrade	Kelvin	°C + 273.1 = °K	°K — 273.1
Chains (surveyor's)	Feet	66	1.515 X 10 ⁻²
Circular mils	Square centimeters	5.067 X 10 ⁻⁶	1.973 X 10 ⁵
Circular mils	Square mils	0.7854	1.273
Cubic feet	Gallons (liq. U.S.)	7.481	0.1337
Cubic feet	Liters	28.32	3.531 X 10 ⁻²
Cubic inches	Cubic centimeters	16.39	6.102 X 10 ⁻²
Cubic inches	Cubic feet	5.787 X 10 ⁻⁴	1728
Cubic inches	Cubic meters	1.639 X 10 ⁻⁵	6.102 X 10 ⁴
Cubic inches Cubic meters Cubic meters Cycles Cycles	Gallons (liq. U.S.)	4.329 X 10 ⁻³	231
	Cubic feet	35.31	2.832 X 10 ⁻²
	Cubic yards	1.308	0.7646
	Kilocycles	10 ⁻³	10 ³
	Megacycles	10 ⁻⁶	10 ⁶

Table V. Conversion Factors—(Cont'd)

To Convert	Into	Multiply by	Conversely, Multiply by
D (1-)	Mils	17.45	5.73 X 10 ⁻²
Degrees (angle)		1.745 X 10 ⁻²	57.3
Degrees (angle)	Radians	2.248 X 10 ⁻⁶	4.448 X 10 ⁵
Dynes	Pounds	7.376 X 10 ⁻⁸	1.356 X 10 ⁷
Ergs	Foot-pounds		°R-459.58=°
Fahrenheit	Rankine	°F+459.58=°R	.,
Faradays	Ampere-hours	26.8	3.731 X 10 ⁻²
Farads	Microfarads	10 ⁶	10 ⁻⁶
Farads	Micromicrofarads	1012	10-12
Farads	Millifarads	10^{3}	10-3
Fathoms	Feet	6	0.16667
Feet	Centimeters	30.48	3.281 X 10 ⁻²
Feet	Meters	0.3048	3.281
Feet	Mils	1.2 X 10 ⁴	8.333 X 10 ⁻⁵
	Gram-centimeters	1.383 X 10 ⁴	1.235 X 10 ⁻⁵
Foot-pounds	Horsepower-hours	5.05 X 10 ⁻⁷	1.98 X 10 ⁶
Foot-pound's			
Foot-pounds	Kilogram-meters	0.1383	7.233 2.655 X 10 ⁶
Foot-pounds	Kilowatt-hours	3.766 X 10 ⁻⁷	2.000 X 10
Foot-pounds	Ounce-inches	192	5.208 X 10 ⁻³
Gallons (liq. U.S.)	Cubic meters	3.785 X 10 ⁻³	264.2
Gallons (liq. U.S.)	Gallons (liq. Br. Imp.)	0.8327	1.201
Gausses	Lines per sq. cm.	1.0	1.0
Gausses	Lines per sq. in.	6.452	0.155
Gausses	Webers per sq. in.	6.452 X 10 ^{-™}	1.55 X 10 ⁷
Grams	Dynes	980.7	1.02 X 10 ⁻³
Grams	Grains	15.43	6.481 X 10 ⁻²
Grams	Ounces (avdp.)	3.527 X 10 ⁻²	28.35
	Poundals	7.093 X 10 ⁻²	14.1
Grams	Pounds per in.	5.6 X 10 ⁻⁸	178.6
Grams per cm.		3.613 X 10 ⁻²	27.68
Grams per cu. cm.	Pounds per cu. in.		10-6
Henries	Microhenries	106	1
Henries	Millihenries	10³	10-3
Horsepower	Btu per minute	42.418	2.357 X 10 ⁻²
Horsepower	Foot-lbs. per minute	3.3 X 10 ⁴	3.03 X 10 ⁻⁵
Horsepower	Foot-lbs. per second	550	1.182 X 10 ⁻³
Horsepower	Horsepower (metric)	1.014	0.9863
Horsepower	Kilowatts	0.746	1.341
Inches	Centimeters	2.54	0.3937
Inches	Feet	8.333 X 10 ⁻²	12
Inches	Meters	2.54 X 10 ⁻²	39.37
Inches	Miles	1.578 X 10 ⁻⁵	6.336 X 10 ⁴
Inches	Mils	10 ⁸	10-3
Inches	Yards	2.778 X 10 ⁻²	36
Joules	Foot-pounds	0.7376	1.356
Joules	Ergs	107	10-7
Joules	Watt-hours	2.778 X 10 ⁻⁴	3600
Kilograms	Tonnes	10 ³	10 ⁻⁸
Kilograms	Tons (long)	9.842 X 10 ⁻⁴	1016
Kilograms	Tons (short)	1,102 X 10 ⁻³	907.2
Kilograms	Pounds (avdp.)	2.205	0.4536
Kilograms per sq.	Pounds per sq. feet	0,2048	4.882
meter	7 contas per sq. reel		1
	T.		-

Table V. Conversion Factors—(Cont'd)

To Convert	Into	Multiply by	Conversely, Multiply by
Kilometers	Feet	3281	3.408 X 10 ⁻⁴
Kilometers	Inches	3.937 X 10 ⁴	2.54 X 10 ⁻⁵
Kilometers	Light years	1.0567 X 10 ⁻¹³	9.4637 X 10 ¹²
Kilometers per hr.	Feet per minute	54.68	1.829 X 10 ⁻²
Kilometers per hr.	Knots	0.5396	1.8532
Kilowatt-hours	Btu	3413	2.93 X 10 ⁻⁴
Kilowatt-hours	Foot-pounds	2.655 X 10 ⁶	3.766 X 10 ⁻⁷
Kilowatt-hours	Joules	3.6 X 10 ⁶	2.778 X 10 ⁻⁷
Kilowatt-hours	Horsepower-hours	1.341	0.7457
Kilowatt-hours	Pounds water evap- orated from and at 212°F,	3.53	0.284
Kilowatt-hours	Watt-hours	10 ³	10 ⁻³
Knots	Feet per second	1.688	0.5 92 5
Knots	Meters per minute	30.87	0.0324
Knots	Miles per hour	1.1508	0.869
Lamberts	Candles per sq. cm.	0.3183	3.142
Lamberts	Candles per sq. in.	2.054	0.4869
Leagues	Miles	3	0.33
Links	Chains	0.01	100
Links (surveyor's)	Inches Bushels (dry U.S.) Cubic centimeters Cubic meters Cubic inches	7.92	0.1263
Liters		2.838 X 10 ⁻²	35.24
Liters		10 ³	10 ⁻³
Liters		10 ⁻³	10 ³
Liters		61.02	1.639 X 10 ⁻²
Liters	Gallons (liq. U.S.)	0.2642	3.785
Liters	Pints (liq. U.S.)	2.113	0.4732
Log _E N	Log₁₀ N	0.4343	2.303
Lumens per sq. ft.	Foot-candles	1	1
Lux	Foot-candles	0.0929	10.764
Maxwells Maxwells Maxwells Meters Meters	Kilolines Megalines Webers Centimeters Feet	10 ⁻³ 10 ⁻⁶ 10 ⁻⁸ 10 ³ 3.28	10 ⁸ 10 ⁸ 10 ⁻² 30.48 X 10 ⁻²
Meters	Inches	39.37	2.54 X 10 ⁻²
Meters	Kilometers	10 ⁻³	10 ³
Meters	Miles	6.214 X 10 ⁻⁴	1609.35
Meters	Yards	1.094	0.9144
Meters per minute	Feet per minute	3.281	0.3048
Meters per minute	Kilometers per hour	0.06	16.67
Mhos	Micromhos	10 ⁶	10 ⁻⁶
Mhos	Millimhos	10 ³	10 ⁻³
Microfarads	Micromicrofarads	10 ⁶	10 ⁻⁶
Miles (nautical)	Feet	6076.1	1.646 X 10 ⁻⁴
Miles (nautical) Miles (statute) Miles (statute) Miles (statute) Miles (statute)	Meters	1852	5.4 X 10 ⁻⁴
	Feet	5280	1.894 X 10 ⁻⁴
	Kilometers	1.609	0.6214
	Light years	1.691 X 10 ⁻¹⁸	5.88 X 10 ¹²
	Miles (nautical)	0.869	1.1508

Table V. Conversion Factors—(Cont'd)

To Convert	Into	Multiply by	Conversely, Multiply by
Miles (statute) Miles per hour	Yards Feet per minute	1760 88 1.467	5.6818 X 10 ⁻⁴ 1.136 X 10 ⁻² 0.6818
Miles per hour Miles per hour Miles per hour	Feet per second Kilometers per hour Knots	1.609 0.8684	0.6214 1.152
Milliamperes Millihenries Millimeters Millimeters Millimeters	Microamperes Microhenries Centimeters Inches Microns	10 ³ 10 ³ 0.1 3.937 X 10 ⁻² 10 ³	10 ⁻³ 10 ⁻³ 10 25.4 10 ⁻³
Millivolts Mils Minutes (angle) Nepers Newtons	Microvolts Minutes Degrees Decibels Dynes	10 ³ 3.438 1.666 X 10 ⁻² 8.686 10 ⁵	10 ⁻³ 0.2909 60 0.1151 10 ⁻⁵
Newtons Ohms Ohms Ohms Ohms	Pounds (avdp.) Milliohms Micro-ohms Micromicro-ohms Megohms	0.2248 10 ³ 10 ⁶ 10 ¹²	4.448 10 ⁻³ 10 ⁻⁶ 10 ⁻¹² 10 ⁶
Ohms Ohms per foot Ounces (fluid) Ounces (avdp.) Picofarad	Ohms (International) Ohms per meter Quarts Pounds Micromicrofarad	0.99948 0.3048 3.125 X 10 ⁻² 6.25 X 10 ⁻²	1.00052 3.281 32 16 1
Pints Pounds (force) Pounds carbon oxidized	Quarts (liq. U.S.) Newtons Btu	0.50 4.4482 14,544	2 0.2288 6.88 X 10 ⁻⁵
Pounds carbon oxidized	Horsepower-hours	5.705	0.175
Pounds carbon oxidized Pounds of water	Kilowatt-hours Cubic feet	4.254 1.603 X 10 ⁻²	0.235 62.38
(dist.) Pounds of water	Gallons	0.1198	8.347
(dist.) Pounds per sq. in. Poundals Poundals	Dynes per sq. cm. Dynes Pounds (avdp.)	6.8946 X 10 ⁴ 1.383 X 10 ⁴ 3.108 X 10 ⁻²	1.450 X 10 ⁻⁵ 7.233 X 10 ⁻⁶ 32.17
Quadrants Quadrants Radians Radians Radians	Degrees Radians Mils Minutes Seconds	90 1.5708 10 ⁸ 3.438 X 10 ⁸ 2.06265 X 10 ⁵	11.111 X 10 ⁻² 0.637 10 ⁻³ 2.909 X 10 ⁻⁴ 4.848 X 10 ⁻⁶
Rods Rods Rods Rpm Rpm	Feet Miles Yards Degrees per second Radians per second	16.5 3.125 X 10 ⁻³ 5.5 6.0 0.1047	6.061 X 10 ⁻² 320 0.1818 0.1667 9.549

Table V. Conversion Factors—(Cont'd)

To Convert	Into	Multiply by	Conversely, Multiply by
Rpm	Rps	1.667 X 10 ⁻²	60
Square feet	Acres	2.296 X 10 ⁻⁵	43,560
Square feet	Square centimeters	929.034	1.076 X 10 ⁻³
Square feet	Square inches	144	6.944 X 10 ⁻³
Square feet	Square meters	9.29 X 10 ⁻²	10.764
Square feet	Square miles	3.587 X 10 ⁻⁸	27.88 X 10 ⁶
Square feet	Square yards	11.11 X 10 ⁻²	9
Square inches	Circular mils	1.273 X 10°	7.854 X 10 ⁻⁷
Square inches	Square centimeters	6.452	0.155
Square inches	Square mils	10 ⁶	10-6
Square inches	Square millimeters	645.2	1.55 X 10 ⁻³
Square kilometers	Square miles	0.3861	2.59
Square meters	Square yards	1.196	0.8361
Square miles	Acres	640	1.562 X 10 ⁻³
Square miles	Square yards	3.098 X 10 ⁶	3.228 X 10 ⁻⁷
Square millimeters	Circular mils	1973	5.067 X 10 ⁻⁴
Square millimeters	Square centimeters	.01	100
Square mils	Circular mils	1.273	0.7854
Tons (long)	Pounds (avdp.)	2240	4.464 X 10 ⁻⁴
Tons (short)	Pounds	2,000	5 X 10 ⁻⁴
Tonnes	Pounds	2204.63	4.536 X 10 ⁻⁴
Varas	Feet	2.7777	0.36
Volts	Kilovolts	10-3	10 ³
Volts	Microvolts	10 ⁶	10-4
Volts	Millivolts	10 ³	10-3
Watts	Btu per hour	3.413	0.293
Watts	Btu per minute	5.689 X 10 ⁻²	17.58
Watts	Ergs per second	107	10-7
Watts	Foot-lbs per minute	44.26	2.26 X 10 ⁻²
Watts	Foot-lbs per second	0.7378	1.356
Watts	Horsepower	1.341 X 10 ⁻³	746
Watts	Kilogram-calories per minute	1.433 X 10 ⁻²	69.77
Watts	Kilowatts	10-3	10 ³
Watts	Microwatts	10 ⁶	10-6
Watts	Milliwatts	10 ³	10-3
Watt-seconds	Joules	1	1
Webers	Maxwells	10 ⁸	10-8
Webers per sq. meter	Gausses	10⁴	10-4
Yards	Feet	3	.3333
Yards	Varas	1.08	0.9259

29. METRIC PREFIXES

(A) Unit Prefixes

The metric system, whereby a different prefix is assigned for each order of magnitude, is particularly suited for electronic values. In 1958 the International Committee on Weights and Measures assigned prefixes for the ninth and twelfth orders of magnitude (both positive and negative). (See Table VI.) This system eliminates the cumbersome double prefixes (micromicro-," "kilomega-," etc. In 1959 the National Bureau of Standards began using these terms; however, acceptance by industry in the United States has been slow, particularly in using the newer term "picofarad" instead of "micromicrofarad."

Prefix Abbreviation **Abbreviation** Multiple Multiple Prefix 1012 Т 10-1 deci-Ы tera- 10^{-2} 109 G centigiga- 10^{-3} milli-106 megam 10⁻⁶ 10⁴ micromyria-My μ 10-9 10^{3} kilo-Κ nano-10-12 10^{2} hecto-Н picoр D 10 deka-

Table VI. Metric Prefixes

(B) Conversion Table

Table VII gives the number of places, and the direction, the decimal point must be moved to convert from one metric notation to another. The value labeled "units" is the basic unit of measurement—e.g., ohms, farads, etc. To use the chart, find the desired value in the left-hand column; then follow the horizontal line across to the column with the prefix in which the original value is stated. The number and arrow at this point indicate the number of places and the direction the decimal point must be moved to change the original value to the desired value.

Table VII. Metric Conversion Table

Desired						Ori	ginal Valu	e						
Value	Tera-	Giga-	Mega-	Myria-	Kilo-	Hecto-	Deka-	Units	Deci-	Centi-	Milli-	Micro-	Nano-	Pico-
Tera-		← 3	← 6	← 8	← 9	←10	←11	←12	←13	←14	←15	← 18	←2 1	←24
Giga-	3→		← 3	← 5	← 6	← 7	← 8	← 9	←10	←11	←12	←15	←18	←21
Mega-	6→	3→		← 2	← 3	← 4	← 5	← 6	← 7	← 8	← 9	←12	←15	←18
Myria-	8→	5→	2→		← 1	← 2	← 3	← 4	← 5	← 6	← 7	← 10	←13	←16
Kilo-	9→	6→	3→	1→		← 1	← 2	← 3	← 4	← 5	← 6	← 9	←12	←15
Hecto-	10→	7→	4>	2→	1→		← 1	← 2	← з	← 4	← 5	← 8	← 11	←14
Deka-	11→	8→	5→	3→	2→	1→		← 1	← 2	← 3	← 4	← 7	←10	←13
Units	12→	9→	6→	4>	3→	2→	1→		← 1	← 2	← 3	← 6	← 9	←12
Deci-	13→	10→	7→	5→	4→	3→	2→	1→		← 1	← 2	← 5	← 8	←11
Centi-	14→	11→	8→	6→	5→	4>	3→	2→	1→		← 1	← 4	← 7	←10
Milli-	15→	12→	9→	7→	6→	5→	4->	3→	2→	1→		← 3	← 6	← 9
Micro-	18→	15→	12→	10→	9→	8→	7→	6→	5→	4->	3→		← 3	← 6
Nano-	21→	18→	15→	13→	12→	11→	10→	9→	8→	7→	6→	3→		← 3
Pico-	24→	21→	18→	16→	15→	14→	13→	12→	11→	10→	9->	6→	3→	

30. STANDARD FREQUENCIES AND TIME SIGNALS

(A) WWV and WWVH

Time signals, audio frequencies, and a 36-digit binary timing code are broadcast continuously day and night from WWV, operated by the National Bureau of Standards near Washington, D.C. The WWV broadcast frequencies are 2.5, 5, 10, 15, 20, and 25 megacycles; and its modulation consists of 1-cps pulses and 440- and 600-cps tones. A similar station, WWVH, is located at Maui, Hawaii. It broadcasts on frequencies of 5, 10, and 15 megacycles.

Signals from WWV and WWVH are coordinated with Stations GBR and MSF at Rugby, England, and Station NBA in the Canal Zone. This coordination provides a more uniform system of time and frequency transmissions throughout the world. It also aids in the solution of many scientific and technical problems such as radiocommunications, geodesy, and tracking of artificial satellites.

WWV is silent for a four-minute period beginning approximately 45 minutes after each hour. The WWVH transmissions are silent for a four-minute period beginning approximately 15 minutes after the hour, and for 34 minutes beginning at 1900 Universal Time.

The frequencies transmitted from WWV and WWVH are accurate to within 1 part in 10 billion.


The drawing in Fig. 54 shows a breakdown of the transmissions during each hour. Each small division represents 1 minute; each large division, 5 minutes.

The audio-frequency signals are transmitted from WWV for precisely two minutes at the beginning of each five-minute period except at the beginning of each hour, when the transmission is for three minutes, and at 45 minutes after the hour when WWV is silent. The audio-frequency signal from WWVH is for precisely three minutes during the periods indicated in Fig. 54.

The timing code (a 36-bit, 100-pulses-per-second code carried on 1,000-cps modulation) is broadcast for one-minute intervals, 10 times per hour. This timing code is indicated by the shaded area in Fig. 54, and immediately follows the 440-and 600-cps modulation except at the beginning of each hour. The 440- and 600-cps modulations are alternated as shown in Fig. 54.

The code is binary-coded decimal (BCD), as shown in Fig. 55, and contains the time-of-year information (in Universal Time) in seconds, minutes, hours, and days. The code consists of nine binary groups each second, as shown in Fig. 55A. The groups appear in the following order: two groups for seconds, two for minutes, two for hours, and three for day of year. The expanded drawing at the bottom of Fig. 55A shows the make-up of the pulse code. A "0" pulse is 2 milliseconds long (or 2 cycles at 1,000 cps), and the "1" pulse is 6 milliseconds (6 cycles at 1,000 cps). The code is locked in phase with the frequency and time signals.

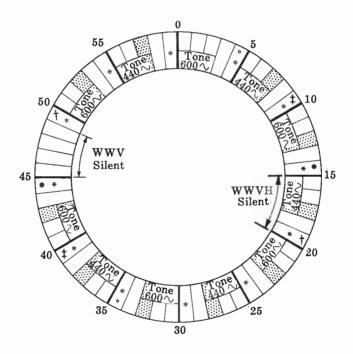A complete time frame is 1 second. Fig. 55B shows the make-up of a typical time code. The time code is amplitude-



- * One Minute Announcement interval (See Fig. 56).
- † North Atlantic Propagation Notice-WWV.
- 1 North Pacific Propagation Notice--WWVH.
- ° IWDS Warning-WWV.
- IWDS Warning-WWVH.

WWVH Silent Between 1900 and 1934 Universal Time

Fig. 54

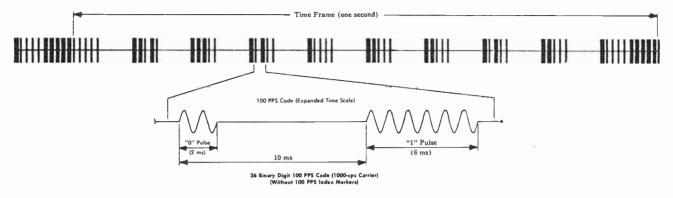


Fig. 55A

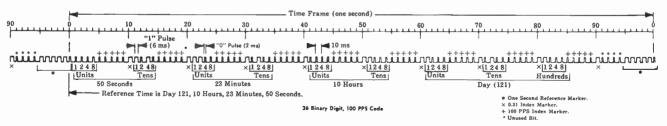


Fig. 55B

modulated on 1,000 cps. The leading edge of the time-code pulses coincide with the zero axis of the positive-going 1,000-cps signal. The least significant binary group and least significant binary digit in each group occur first. The binary groups follow the 1-second reference marker. The start time occurs at the leading edge of all pulses.

The BCD contains a 100-per-second clocking rate, 10-per-second index markers, and 1-per-second reference markers. The 1,000-cps signal is locked to the code pulses so that millisecond resolution can be obtained easily.

The 10-per-second index markers consist of "1" pulses preceding each code group except at the beginning of the second, where there is a "0" pulse.

Each second begins at the leading edge of the "0" pulse, as shown in Fig. 55.

The 1-second reference marker is made up of five "1" pulses followed by a "0" pulse.

The code is spaced so that it follows each of the 10-persecond index markers. The last index marker is followed by an unused four-bit group of "0" pulses immediately preceding the 1-second reference marker.


A five-millisecond pulse spaced at intervals of one second is also transmitted. The pulse transmitted by WWV consists of five cycles of a 1,000-cycle tone. The pulse transmitted by WWVH consists of six cycles of a 1,200-cycle tone. The 440- and 600-cps tone signal is interrupted for .04 second for each seconds pulse. The pulse starts .01 second after commencement of the interruption, and resumes .025 second after the pulse. For identification, the fifty-ninth second pulse is omitted, and the zero-second pulse is followed by another pulse 100 milliseconds later.

A voice announcement of Eastern Standard Time and call letters is given each five minutes from station WWV. This is followed by a telegraph-code announcement of Universal Time and another voice announcement of Eastern Standard Time. WWVH broadcasts call letters and Universal Time (UT) in telegraphic code only. The time given is the time at the resumption of the tone.

The drawing in Fig. 56 shows a breakdown of the transmissions during the one-minute announcement intervals marked with an asterisk (*) in Fig. 54. Each division on this drawing represents one second.

During announcement intervals at 19½ and 49½ minutes past every hour, propagation notices applying to transmission paths over the North Atlantic are transmitted from WWV. Similar forecasts for the North Pacific are transmitted from WWVH, during announcement intervals, at 9.4 and 39.4 minutes after the hour.

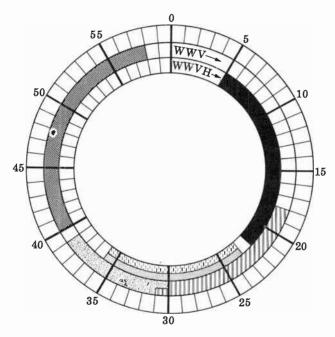These notices, in telegraphic code, consist of a letter followed by a number. The letter signifies the propagation conditions at the time of the broadcast. The following designations are used:



- Universal Time and Call Letters (Code).
- IWDS Warning (Code) WWV. (4.3 and 34.3 Minutes After Hour Only.)
- North Pacific Propagation Forecast. (Approx. 9.4 and 39.4 Minutes After Hour Only.)
- IWDS Warning (Code) WWVH. (Approx. 14.4 and 44.4 Minutes After Hour Only.)
- North Atlantic Propagation Forecast. (19.5 and 49.5 Minutes After Hour Only.)
- Call Letters and EST (Voice) UT (Code) EST (Voice).

 Fig. 56

N-Normal U-Unsettled W-Disturbance

The number following the letter applies to expected propagation conditions during the subsequent 6 or more hours. The following designations are used:

1—Useless 4—Poor to Fair 7—Good
2—Very Poor 5—Fair 8—Very good
3—Poor 6—Fair to Good 9—Excellent

At 4.3 and 34.3 minutes past the hour on WWV, and at approximately 14.4 and 44.4 minutes past the hour on WWVH, the IWDS (International World Day Service) warning is broadcast. This message reveals to experimenters in radio, geophysical, and solar sciences the content of the warning message issued at 1600 UT by the world warning agency on days when an outstanding geophysical event has occurred during the preceding 24 hours. This message is first broadcast at 1604.3 UT on WWV and at 1714.4 UT on WWVH.

If the IWDS warning declares an alert, the letters AGI AAAA are broadcast very slowly in code. This means that a significant magnetic storm has started or that an outstanding auroral display or increase in cosmic-ray flux has been reported or observed.

If a special world interval is in progress, the code letters AGI are followed by three extra-long dashes. This again indicates that an alert has been declared and that the geophysical activity is of sufficient interest to warrant special attention and intensified observations. Special world intervals usually last two or three days.

When there is no "state of alert" or "special world interval" in progress, the letters AGI EEEEE are broadcast.

(B) CHU

The Dominion Observatory at Ottawa, Canada, broadcasts time signals which can be heard throughout the North American continent and many other parts of the world. The frequencies are 3,330, 7,335, and 14,670 kc, and the transmission is continuous on all frequencies. The 3,330-kc transmitter has a power of 0.75 kw and the other two, 3 kw.

The frequencies are synthesized from a 100-kc crystal oscillator which is maintained accurate to within a few parts

in one billion. The "seconds" pips are also derived from this same oscillator and consist of 200 cycles of a 1,000-cps tone.

The "seconds" pips are broadcast continuously except for the 29th and the 51st through 59th pips, which are omitted each minute. In addition, the 1st to 29th pips are omitted during the first minute of the hour. The beginning of the pip marks the exact second. The zero pip has a duration of 0.5 second instead of the 0.2 second of the other pips.

During the first half-minute of each hour, CHU CANADA CHU is transmitted in code.

A voice announcement of the time is given each minute during the 10-second interval between the 50th and 60th second when the pips are omitted. The announcement is as follows: "CHU, Dominion Observatory Canada, Eastern Standard Time, _____ hours, ____ minutes." The time given refers to the beginning of the minute pip which follows, and is on the 24-hour system.

(C) Other Standards Stations

Throughout the world, there are many other stations which broadcast similar data. Table VIII lists some of them, and other data about stations operating on the standards frequencies. Table IX lists some other stations in the LF and VLF bands which broadcast similar data, but not on the frequencies assigned for standard-frequency operation.

31. FREQUENCY AND OPERATING POWER TOLERANCES

(A) AM Broadcast

The operating frequency tolerance of each station shall be maintained within ± 20 cycles of the assigned frequency.

The operating power of each AM broadcast station shall be maintained as near as practicable to the licensed power and shall not exceed the limits of 5 per cent above and 10 per cent below the licensed power except in emergencies.

(B) FM Broadcast

Operating frequency tolerance of each station shall be maintained within $\pm 2,000$ cycles of the assigned center frequency.

Table VIII. Other Standards Stations

Call Sign	Location	Carrier Freq. (mc)	Modulation (cps)	Power (kw)
ATA	New Delhi, India	10	1; 1000	1.0
FFH	Paris, France	2.5; 5; 10	1; 440; 1000	0.3
HBN	Neuchatel, Switzerland	2,5; 5	1; 500	0.5
IAM	Rome, Italy	5	1; 440; 600; 1000	1,0
IBF	Turin, Italy	5	1; 440; 1000	0.3
JJY	Tokyo, Japan	2.5; 5; 10; 15	1; 440; 1000	2.0
LOL	Buenos Aires, Argentina	2.5; 5; 10; 15; 20; 25	1; 440; 1000	2,0
MSF	Rugby, England	2.5; 5; 10	1; 1000	0.5
OMA	Prague, Czechoslovakia	2,5	1; 1000	1.0
ZLFS	Lower Hutt, New Zealand	2.5		0.03
ZUO	Olifantsfontein, South Africa	5	1	4.0
WWVL	Fort Collins, Colorado	20 kc		1.0

Table IX. LF and VLF Stations

Call Sign	Location	Carrier Freq. (kc)	Modulation (cps)	Power (kw)
WWVB	Fort Collins, Colorado	60		5
DCF77	Federal German Republic	77,5	1; 200; 440	12
OMA	Czechoslovakia	50		5
GBR	Rugby, England	16		300
MSF	Rugby, England	60	1; 1000	10
NBA	Canal Zone (U. S. Navy)	18	1	100

The operating power of each station shall be maintained as near as practicable to the authorized operating power and shall not exceed the limits of 5 per cent above and 10 per cent below the authorized power except in emergencies.

(C) TV Broadcast

The carrier frequency of the visual transmitter shall be maintained within $\pm 1,000$ cycles of the authorized carrier frequency.

The center frequency of the aural transmitter shall be maintained 4.5 megacycles $\pm 1,000$ cycles above the visual carrier frequency.

The peak power shall be monitored by a peak-reading device which reads proportionally to voltages, current, or power in the radio-frequency line. The operating power as so monitored shall be maintained as near as practicable to the authorized operating power and shall not exceed the limits of 10 per cent above and 20 per cent below the authorized power except in emergencies.

The operating power of the aural transmitter shall be maintained as near as practicable to the authorized operating power, and shall not exceed the limits of 10 per cent above and 20 per cent below the authorized power except in emergencies.

(D) Industrial Radio Service

The carrier frequency of stations operating below 220 megacycles in the Industrial Radio Service shall be maintained within $\pm .01\%$ of the authorized power for stations of 3 watts or less, and $\pm .005\%$ for stations with an authorized power of more than 3 watts. The frequency tolerance of Industrial Radio Service stations operating between 220 and 1,000 megacycles is specified in the station authorization.

(E) Citizens-Band Radio

The maximum plate power input to the anode (plate) circuit of the electron tube or tubes which supply energy to the radiating system of a station in this service shall not exceed the values given in Table X.

Class of Station	Maximum Plate Power Input (Watts)
Α	60
В	5
С	5*
D	5

Table X. Power Limits of Citizens-Band Stations

The carrier frequency of a station in this service shall be maintained within the percentages of authorized frequency given in Table XI.

Table XI. Frequency Tolerances of Citizens-Band Stations

	Maximum Authorized Plate Power Input Class (Watts)	Frequency Tolerance %	
Class		Fixed and Base	Mobile
Α	3 or less	.001	.005
Α	Over 3	.001	.001
В	3 or less		.5
В	Over 3		.3
С	5 or less*		.005
С	Over 5 (27,255 mc only)		.005
D	5 or less		.005

^{*} Class-C stations which have a plate power input of 3 watts or less and are used solely for remote control of objects or devices by radio (other than devices used solely as a means of attracting attention) are permitted a frequency tolerance of 0.01%.

32. COMMERCIAL OPERATOR LICENSES

The classes of commercial radio operator licenses issued by the Federal Communications Commission are classified basically as radiotelegraph and radiotelephone licenses.

(A) Examination Elements

Written examinations are composed of questions from various categories called elements. These elements, and the types of questions in each, are:

^{*} A maximum plate power input of 30 watts is permitted on 27.255 mc only.

- Element 1. Basic Law. Provisions of laws, treaties, and regulations with which every operator should be familiar.
- Element 2. Basic Operating Practice. Radio operating procedures and practices generally followed or required in communicating by means of radiotelephone stations.
- Element 3. Basic Radiotelephone. Technical, legal, and other matters applicable to the operation of radiotelephone stations other than broadcast.
- Element 4. Advanced Radiotelephone. Advanced technical, legal, and other matters particularly applicable to the operation of the various classes of broadcast stations.
- Element 5. Radiotelegraph Operating Practice. Radio operating procedure and practices generally followed or required in communicating by means of radiotelegraph stations primarily other than in the maritime mobile services of public correspondences.
- Element 6. Advanced Radiotelegraph. Technical, legal, and other matters applicable to the operation of all classes of radiotelegraph stations, including operating procedures and practices in the maritime mobile services of public correspondences, and associated matters such as radionavigational aids, message traffic routing and accounting, etc.
- Element 7. Aircraft Radiotelegraph. Basic theory and practice in the operation of radiocommunications and radionavigational systems aboard aircraft.
- Element 8. Ship Radar Techniques. Specialized theory and practice applicable to the proper installation, servicing, and maintenance of ship radar equipment in general use for marine navigational purposes.

(B) Examination Requirements

Applicants for licenses must be able to transmit and receive spoken messages in English, and be able to pass the examination elements required for the license. The requirements for the various licenses are:

- 1. Radiotelephone second-class operator licenses. Written examination elements 1, 2, and 3.
- 2. Radiotelephone first-class operator licenses. Written examination elements 1, 2, 3, and 4.
- 3. Radiotelegraph second-class operator license. Transmitting and receiving code test of 16 code groups per minute. Written examination elements 1, 2, 5, and 6.
- 4. Radiotelegraph first-class operator license. Transmitting and receiving code test of 25 words per minute in conversational language and 20 groups per minute in code. Written examination elements 1, 2, 5, and 6.
- 5. Radiotelephone third-class operator permit. Written examination elements 1 and 2.
- 6. Radiotelegraph third-class operator permit. Transmitting and receiving code test of 16 code groups per minute. Written examination elements 1, 2, and 5.

33. AMATEUR OPERATOR PRIVILEGES

(A) Examination Elements

Examinations for amateur operator privileges are composed of questions from various categories, called elements. The various elements and their requirements are:

- Element 1(A): Beginner's Code Test. Code test at 5 words per minute.
- Element 1(B): General Code Test. Code test at 13 words per minute.
- Element 1(C): Expert's Code Test. Code test at 20 words per minute.
- Element 2: Basic Amateur Practice. Amateur radio operation and apparatus, including radiotelephone and radiotelegraph.
- Element 3(A): Basic Law. Rules and regulations essential to beginners' operation, including sufficient elementary radio theory to understand these rules.
- Element 3(B): General Regulations. Provisions of treaties, statutes, and rules and regulations affecting all amateur stations and operators.
- Element 4(B): Advanced Amateur Practice. Advanced radio theory and operation applicable to mod-

ern amateur techniques, including—but not limited to—radiotelephony, radiotelegraphy, and transmission of energy for (1) measurements and observations applied to propagation, (2) radio control of remote objects, and (3) similar experimental purposes.

(B) Examination Requirements

Applicants for original licenses will be required to pass examinations as follows:

- 1. Amateur Extra Class. Elements 1(C), 2, 3(B), and 4(B).
- 2. General Class. Elements 1(B), 2, and 3(B).
- 3. Conditional Class. Elements 1(B), 2, and 3(B).
- 4. Technician Class. Elements 1(A), 2, and 3(B).
- 5. Novice Class. Elements 1(A) and 3(A).

Note: Examinations for licenses (1) and (2) above must be given by an FCC examiner. The examinations for licenses (3), (4), and (5) are taken by mail, under the supervision of a volunteer examiner.

34. AMATEUR ("HAM") BANDS

The various bands of frequencies used by amateur radio operators ("hams") are usually referred to in meters instead of the actual frequencies. The number of meters approximates the wavelength at the band of frequencies being designated. The meter bands and their frequency limits are given in Table XII. (Note: Frequencies between 220 and 225 mc are sometimes referred to as 1½ meters, and between 420 and 450 meters as ¾ meter.)

Band	Frequency (mc)
80 Meters	3.5-4.0
40 Meters	7.0-7.3
20 Meters	14.0—14.35
15 Meters	21.0—21.45
10 Meters	28.0-29.7
6 Meters	50—54
2 Meters	144—148

Table XII. "Ham" Bands

Table XIII. Types of Emission

Type of Modulation	Type of Transmission	Supplementary Characteristics	Symbol
1. Amplitude	Absence of any modulation	_	A0
	Telegraphy without the use of modulating audio frequency (on-off keying)		A1
	Telegraphy by the keying of a modulating audio frequency or frequencies or by the keying of the modulated emission (special case: an unkeyed modulated emission)		A2
		Double sideband, full carrier	А3
	Telephony	Single sideband, reduced carrier	A3a
		Two independent sidebands, reduced car- rier	A3b
	Facsimile		A4
	Television		A5
	Composite transmissions, and cases not covered by the above		А9
	Composite transmissions	Reduced carrier	A9c
modulated Telegraphy without t	Absence of any modulation		FO
	Telegraphy without the use of modulating audio frequency (frequency shift keying)		FI

	Telegraphy by the keying of a modulating audio frequency or audio frequencies or by the keying of the modulated emission (special case: an unkeyed emission modulated by audio frequency)		F2
	Telephony		F3
	Facsimile		F4
	Television		F5
	Composite transmissions and cases not covered by the above		F9
3. Pulsed emissions	Absence of any modulation carrying information		PO
	Telegraphy without the use of modulating audio frequency		Pl
	Telegraphy by the keying of a modulating audio frequency or of the modulated pulse (special case: an unkeyed modulated pulse)	Audio frequency or frequencies modulat- ing the pulse in amplitude	P2d
		Audio frequency or frequencies modulat- ing the width of the pulse	P2c
		Audio frequency or frequencies modulating the phase (or position) of the pulse	P2f
	Telephony	Amplitude-modulated pulse	P3d
		Width-modulated pulse	P3e
		Phase-(or position-) modulated pulse	P3f
	Composite transmissions and cases not covered by the above		P9

35. TYPES OF EMISSIONS.

Emissions are classified according to their modulation, type of transmission, and supplementary characteristics. These classifications are given in Table XIII on pages 72 and 73. When a full designation of the emissions—including bandwidth—is necessary, the symbols in Table XIII are prefixed by a number indicating the bandwidth in kilocycles. Below 10 kc, this number is given to two significant figures.

36. TELEVISION CHANNEL FREQUENCIES

The chart in Fig. 57 (page 75) lists the frequency limits of all television channels and the frequency of the picture and sound carriers of each channel.

37. TELEVISION SIGNAL STANDARDS

The signal standards for television broadcasting are given in Figs. 58A and B (pages 76 and 77). Note: The standards given here are for color transmission. For monochrome transmission, the standards are the same except the color burst signal is omitted. Also, for color the vertical and horizontal scanning frequencies are 59.94 and 15,734.264 cps, respectively; for monochrome they are 60 and 15,750 cps.

38. AUDIO-FREQUENCY SPECTRUM

The audio-frequency spectrum is generally accepted as extending from 15 cps to 20,000 cps. Fig. 60 (page 79) gives the frequencies for each tone of the standard keyboard, based on the current musical pitch of A=440 cps. Fig. 59 (page 78) shows the frequency range of various musical instruments and of other sounds. The frequency range shown for each sound is the range needed for faithful reproduction, and includes the fundamental frequency and the necessary harmonic frequencies. The frequency range of the human ear, and the various broadcasting and recording media, are also included in Fig. 59.

39. RADIO-FREQUENCY SPECTRUM

(A) Frequency Classification

The radio-frequency spectrum from 3 kc to 3,000,000 mc is divided into the various bands (shown in Table XIV on page 78) for easier identification.

Television Channel Frequencies


			- 1010	57151011 Q 111		- reque	10103	-14
		Channel No.	Freq. Limits	P 543.25 \$ 547.75	26	542	P 717.25 \$ 721.75 55	_ 716
	55,25		54	P 549.25	27	548	P 723,25 E ≰	— 722
S	59.75	2	60	\$ 553.75 P 555,25		554		728
P S	61.25 65.75	3		\$ 559.75	28	560	s 733.75 3/	734
P	67.25 71.75	4	- 66	P 561.25 \$ 565.75	29	566	s 739.75 38	— 740
	71.73	***	72	P 567.25 \$ 571.75	30		P 741.25 \$ 745.75 59	— 746
_			76	P 573,25 \$ 577.75	31	572	P 747.25 S 751.75 60	
P S	77.25 81.75	5	82	P 579.25	32	578	P 753.25 🗸 🕇	— 752
P	83.25 87.75	6	- 88	\$ 583.75 P 585.25		- 584		— 758
			. 00	s 589.75	33	- 590	F 759.25 S 763.75 62 P 765.25 63	764
P	175.25	_	174	P 591.25 \$ 595.75	34	- 596	s 769.75 03	770
S	179.75	7	- 180	P 597.25 S 601.75	35	- 602	P 771.25 \$ 775.75 64	776
P S	181.25 185.75	8	186	P 603.25 \$ 607.75	36		P 777.25 \$ 781,75 65	
P	187.25 191.75	9	192	P 609.25	37	- 608	P 783,25 🚜	782
P	193.25 197.75	10		\$ 613.75 P 615.25	38	- 614	P 789.25 47	788
P	199.25	11	- 198	\$ 619.75 P 621.25		- 620		794
S P	203.75		- 204	\$ 625.75	39	- 626	s 799.75 OB	800
S	209.75	12	- 210	P 627.25 \$ 631.75	40	- 632	P 801.25 \$ 805.75 69	806
5	211.25 215.75	13	- 216	P 633.25 \$ 637.75	41		P 807.25 \$ 811.75 70	
				P 639.25 S 643.75	42	- 638	P 813.25 S 817.75 71	
P	471.25	14	- 470	P 645,25	43	- 644	P 819.25 72	818
S P	475.75 477.25		476	\$ 649.75 P 651.25		- 650		024
SP	481.75	15	482	\$ 655.75	44	- 656	s 829.75 / 3	030
<u>S</u>	483.25 487.75	16	- 488	s 661.75	45	- 662	P 831.25 S 835.75 74	836
P	489.25 493.75	17	_ 494	P 663.25 S 667.75	46	- 668	P 837.25 S 841.75 75	842
P	495.25 499.75	18		P 669.25 \$ 673.75	47		P 843.25 \$ 847.75 76	
P	501.25	19	_ 500	P 675.25	48	_ 674	P 849.25 77	040
S P	505.75 507.25		_ 506	\$ 679.75 P 681.25		- 680	3 033.73	834
SP	511.75	20	_ 512	\$ 685.75 P 687.25	49	- 686	s 859.75	000
S	513,25 517,75	21	_ 518	s 691.75	50	_ 692	s 865.75) 866
P	519.25 523.75	22	_ 524	P 693.25 \$ 697.75	51	698	P 867.25 \$ 871.75	872
P	525.25 529.75	23		P 699.25 \$ 703.75	52		P 873.25 \$ 877.75	
P	531.25	24	_ 530	P 705.25	53	_ 704	P 879.25 Q 7	0/0)
S P	535.75 537.25		_ 536	\$ 709.75 P 711.25	54	_ 710	3 000:70 ==	004
<u>s</u>	541.75	25	_ 542	\$ 715.75	34	_ 716	P 885.25 \$ 889.75	890


P = Picture Carrier Freq.

s = Sound Carrier Freq.

All frequencies in mc.

Fig. 57

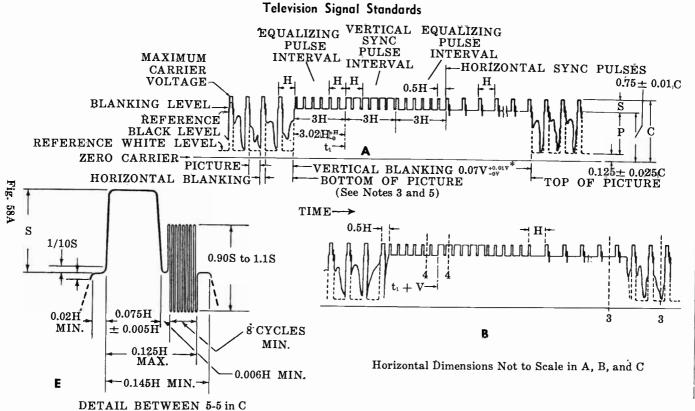

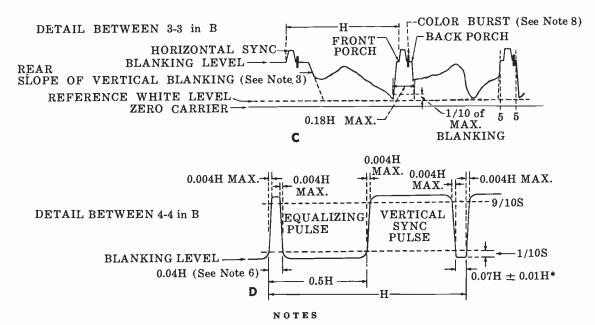

- 1. H = Time from start of one line to start of next line.
- 2. V = Time from start of one field to start of next field.
- Leading and trailing edges of vertical blanking should be complete in less than 0.1H.
- Leading and trailing slopes of horizontal blanking must be steep enough to preserve minimum and maximum values of (x + y) and (z) under all conditions of picture content.
- Dimensions marked with asterisk indicate that tolerances given are permitted only for long time variations and not for successive cycles.
- 6. Equalizing pulse area shall be between 0.45 and 0.5 of area of a horizontal sync pulse.
- 7. Color burst follows each horizontal pulse, but is omitted following the equalizing pulses and during the broad vertical pulses.

- 8. Color burst to be omitted during monochrome transmissions.
- The burst frequency shall be 3.579545 mc. The tolerance on the frequency shall be ±0.0003% with a maximum rate of change of frequency not to exceed 1/10 cycle per second per second.
- The horizontal scanning frequency shall be 2/455 times the burst frequency.
- 11. The dimensions specified for the burst determine the times of starting and stopping the burst but not its phase. The color burst consists of amplitude modulation of a continuous sine wave.
- 12. Dimension "P" represents the peak excursion of the luminance signal at blanking level but does not include the chrominance signal. Dimension "S" is the sync amplitude above blanking level. Dimension "C" is the peak carrier amplitude.

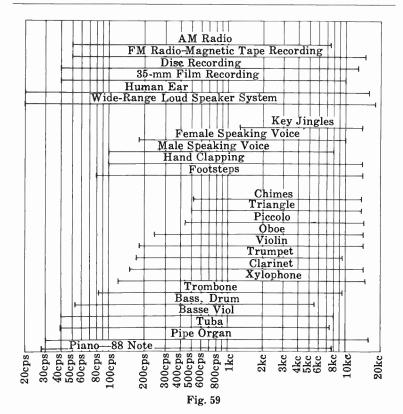


Table XIV. Frequency Classification

Frequency	Band No.	Classification	Abbreviation
3–30 kc	4	Very low frequencies	VLF
30–300 kc	5	Low frequencies	LF
300–3000 kc	6	Medium frequencies	MF
3-30 mc	7	High frequencies	HF
30-300 mc	8	Very high frequencies	VHF
300-3000 mc	9	Ultrahigh frequencies	UHF
3000-30,000 mc	10	Super-high frequencies	SHF
30,000-300,000 mc	11	Extremely high frequencies	EHF
300,000–3,000,000 mc	12		

(B) FCC Allocations

The FCC allocations for the various services between 10 kc and 100,000 mc are given in Fig. 61A and B (located on the fold-out page between pages 180 and 181.

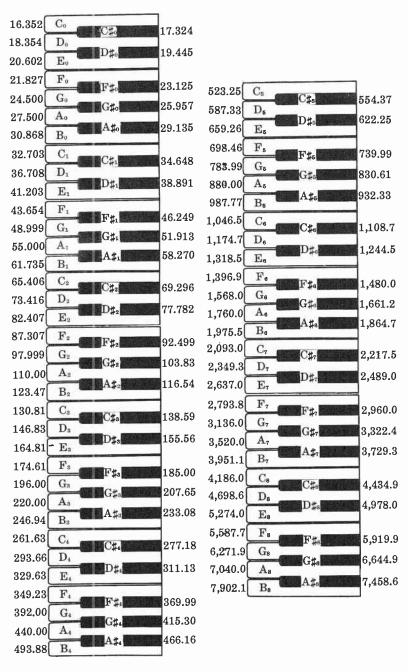


Fig. 60

Symbols and Codes

40. INTERNATIONAL Q SIGNALS

The international Q signals were first adopted to enable ships at sea to communicate with each other or to foreign shores without experiencing language difficulties. The signals consist of a series of three-letter groups starting with Q and having the same meaning in all languages. Today, Q signals serve as a convenient means of abbreviation in communications between amateurs. Each Q signal has both an affirmative and an interrogative meaning. The question is designated by the addition of the question mark after the Q signal. The most common Q signals are listed in Table XV.

Table XV. Q Signals

Signal	Question	Answer or Advice
QRG	Will you tell me my exact frequency?	Your exact frequency is kc (or mc).
QRH	Does my frequency vary?	Your frequency varies.
QRK	What is the readability of my signals?	The readability of your signals is
QRM	Are you being interfered with?	I am being interfered with.
QRN	Are you troubled by static?	I am troubled by static.
QRO	Shall I increase power?	Increase power.
QRP	Shall I decrease power?	Decrease power.
QRQ	Shall I send faster?	Send faster.
QRS	Shall I send more slowly?	Send more slowly (words per minute).
QRT	Shall I stop sending?	Stop sending.
QRU	Have you anything for me?	I have nothing for you.
QRV	Are you ready?	I am ready.
QRX	When will you call again?	I will call you again at hours [on kc (or mc)].
QSA	What is the strength of my signals?	The strength of your signals is
QSB	Are my signals fading?	Your signals are fading.
QSL	Can you acknowledge receipt?	I am acknowledging receipt.
QSM	Shall I repeat the last message I sent you?	Repeat the last message you have sent me.
QSO	Can you communicate with direct or by relay?	I can communicate with direct (or by relay through).
QSV	Shall I send a series of V's?	Send a series of V's.
QSY	Shall I change to transmission on another frequency?	Change to transmission on another frequency [or on kc (or mc)].
QSZ	Shall I send each word or group twice?	Send each word or group twice.
QTH	What is your location?	My location is

41. "10" SIGNALS

The abbreviations based on the number 10 plus a suffix was originally used for communication between police units. Now they are often used in other forms of two-way communications. The most common signals are given in Table XVI.

Table XVI. "10" Signals

Signal	Meaning	Signal	Meaning
10-1	Unable to copy	10.27	Operator on duty
10-2	Signal good	10-30	Does not conform to rules
10-3	Affirmative-granted-will do	10-33	Emergency traffic this station
10-5	Relay	10-36	Confidential information
10-6	Busy	10-41	Beginning tour of duty
10-7	Off the air	10-42	Ending tour of duty
10-8	On the air	10-44	Message received by all con-
10-9	Repeat	1	cerned
10-10	On detail, but subject to call	10-60	What is next number?
10-11	Remain in service	10-61	CW traffic
10-12	Visitors or officials present	10-62	Teletype traffic
10-13	Weather and road conditions	10-63	Any answer our number
10-14	Correct time	10-64	Message for local delivery
10-16	Pick up ()	10-65	Net message assignment
10-17	Urgent—rush present detail	10-66	Cancellation
10-18	Anything for us?	10-67	Clear for net message
10-19	Nothing for you	10-68	Dispatch information
10-20	Location	10-88	Advise present phone number
10-21	Call by telephone	1	of
10-22	Reporting in person to	10-91	Too weak; talk closer to mike
10-23	Arrived at scene	10-92	Too loud; talk farther from mike
10-24	Finished with last assignment	10-93	Frequency check
10-25	Disregard last information	10-94	Give a test

42. THE INTERNATIONAL CODE

Α		M		Y	
В		N		${f Z}$	
\mathbf{C}		O		1	
D		P		2	
\mathbf{E}		Q		3	
\mathbf{F}		\mathbf{R}		4	
G		\mathbf{S}		5	
Н		\mathbf{T}	-	6	
Ι		U		7	
J		V		8	
K		W		9	
L		\mathbf{X}		0	
Qu	estion Mark · ·		Period · - ·		_
Er			Comma		
Wa			End of Messa	ge	

43. GREEK ALPHABET

The Greek alphabet is given in Table XVII. The items for which each letter is a symbol are also listed. The small Greek letter is the symbol for all the items listed unless a capital letter is indicated (cap).

Table XVII. Greek Alphabet

Letter			
Small	Capital	Name	Designates
α	A	Alpha	Angles, coefficients, attenuation constant, absorption factor, area.
β	В	Beta	Angles, coefficients, phase constant.
γ	Г	Gamma	Specific quantity, angles, electrical conductivity, propagation constant, complex propagation constant (cap).
δ	Δ	Delta	Density, angles, increment or decre- ment (cap or small), determinant (cap), permittivity (cap).
ε	E	Epsilon	Dielectric constant, permittivity, base of natural (Napierian) logarithms, electric intensity.
\$	Z	Zeta	Co-ordinate, coefficients.
η	н	Eta	Intrinsic impedance, efficiency, sur- face charge density, hysteresis, co- ordinates.
θ	θ	Theta	Angular phase displacement, time constant, reluctance, angles.
L	1	lota	Unit vector.
κ	K	Kappa	Susceptibility, coupling coefficient.
λ	Λ	Lambda	Wavelength, attenuation constant, permeance (cap).
μ	M	Μυ	Prefix <i>micro</i> -, permeability, amplification factor.
ν	N	Nυ	Reluctivity, frequency.
ξ	Ξ	Xi	Co-ordinates.
0	0	Omicron	
π	TT	Pi	3.1416 (circumference divided by diameter).
ρ	Р	Rho	Resistivity, volume charge density, co-ordinates.
σ	Σ	Sigma	Surface charge density, complex propagation constant, electrical conductivity, leakage coefficient, sign of summation (cap).
τ	T	Tau	Time constant, volume resistivity, time-phase displacement, transmis- sion factor, density.
υ	Υ	Upsilon	

Table XVII.	Greek	Alphabet—	(Cont	'd)
-------------	-------	-----------	-------	-----

Le	tter							
Small	Capital	Name	Designates					
φ	Ф	Phi	Magnetic flux, angles, scalar potential (cap).					
x	x	Chi	Electric susceptibility, angles.					
ψ	Ψ	Psi	Dielectric flux, phase difference, co- ordinates, angles.					
ω Ω		Omega	Angular velocity $(2\pi f)$, resistance in ohms (cap), solid angles (cap).					

44. ELECTRONIC SYMBOLS AND ABBREVIATIONS*

A—Ammeter; ampere; area

a-Ampere

AC, a.c., a-c, ac-Alternating current

AF, a.f., a-f, af-Audio frequency

AFC, afc-Automatic frequency control

AGC, agc—Automatic gain control

AM, am-Amplitude modulation

Amp, amp., Amps, amps.—Ampere; amperes

Ant, ant.—Antenna

AVC, a.v.c., avc—Automatic volume con-

B-Susceptance

b---Magnetic flux density

BC, bc-Broadcast

BFO, bfo-Beat-frequency oscillator

C-Capacitance; capacitor

°C—Degrees Celsius or centigrade

cm---Centimeter

cps-Cycles per second

CW, cw-Continuous wave

db---Decibels

DC, d.c., d-c, dc-Direct current

d.c.c., dcc—Double cotton-covered

DPDT, d.p.d.t., dpdt—Double-pole, double-throw

DPST, d.p.s.t., dpst—Double-pole, single-

d.s.c., dsc-Double silk-covered

E, e—Voltage

e.c., ec-Enamel-covered

EMF, emf-Electromotive force

ERP-Effective radiated power

F. f---Farad

f-Frequency

°F-Degrees Fahrenheit

FM, f.m., fm-Frequency modulation

G—Conductance

G_m, gm, g_m—Mutual conductance

GCT-Greenwich Civil Time

gnd-Ground

H, h-Henry

HF, h.f., h-f, hf-High frequency

hp—Horsepower

hy.—Henry

I---Current

IF, i.f., i-f, if-Intermediate frequency

ips-Inches per second

j—Joule; an imaginary number; an operator to rotate a vector quantity 90° counterclockwise

K—X 1000; dielectric constant; a numerical value that does not change during a given period

k-Dielectric constant

KC, kc-Kilocycle

kv-Kilovolt

kva—Kilovolt ampere

KW, kw-Kilowatt

KWH, kwh-Kilowatt hour

L-Inductance; inductor

I-Lenath

LF, I.f., I-f, If—Low frequency

M-Mutual inductance; × 1000

m---Meter

ma-Milliampere

^{*} For Greek letters used as symbols (such as Ω , ω , and ψ), see the Greek alphabet in § 43.

MC, Mc, mc-Megacycle

mcw-Modulated continuous wave

meg-Megohm

MF, m.f., m-f, mf-Medium frequency

mf, mfd-Microfarad

mh-Millihenry

mm--Millimeter

mmf, mmfd-Micromicrofarad

mv-Millivolt (sometimes microvolt)

mw-Milliwatt (sometimes microwatt)

NC-No connection

OD—Outside diameter

P-Power

pf-Power factor

p-p-Peak-to-peak

Q—Merit of a coil or capacitor; quantity of electricity

R-Resistance: resistor

RC, R-C-Product of resistance time ca-

pacitance; resistor-capacitor

RF, r.f., r-f, rf—Radio frequency

RFC—Radio-frequency choke coil

rms-Root mean square

rpm-Revolutions per minute

s.c.c., scc-Single cotton-covered

s.c.e., sce—Single cotton ename!

sec-Second; secondary

s.s.c., ssc—Single silk-covered

SHF; s.h.f., shf-Super-high frequencies

SW, sw-Short wave

t-Time

T-Temperature

trf-Tuned radio frequency

UHF, uhf-Ultrahigh frequencies

V, v-Volt; voltmeter

VHF, vhf-Very high frequencies

VOM, vom-Volt-ohm-milliammeter

VTVM, vtvm—Vacuum-tube voltmeter

VU-Volume unit

W-Watt; work

w—Watt

wh, whr-Watt-hour

X-Reactance

X₁—Capacitive reactance

X1.-Inductive reactance

Y-Admittance

Z—Impedance

μa-Microampere

μf --- Microfarad

μ**h**—Microhenry

μμf---Micromicrofarad

√—Cycles per second

45. SEMICONDUCTOR ABBREVIATIONS

The following symbols and abbreviations have been adopted as standard by the Electronic Industries Association (EIA) and the National Electrical Manufacturers Association (NEMA).

B, b—Base electrode for units employing a single base

b₁, **b**₂, etc.—Base electrodes for more than one base

BV_{GBO}—Breakdown voltage, collector to base, emitter open

BV_{CEO}—Breakdown voltage, collector to emitter, base open

BV_{ORB}—Breakdown voltage, collector to emitter, with specified resistance between base and emitter

BV_{CRS}—Breakdown voltage, collector to emitter, with base short-circuited to emitter **BV**_{EBO}—Breakdown voltage, emitter to base, collector open

BV_R-Breakdown voltage, reverse

C, c-Collector electrode

C16-Input capacitance (common base)

Cic-Input capacitance (common collector)

Cie-Input capacitance (common emitter)

Cub-Output capacitance (common base)

C_{oc}—Output capacitance (common collector)

Coe—Output capacitance (common emitter)

E, e-Emitter electrode

- fhfb—Small-signal, short-circuit, forwardcurrent, transfer-ratio cutoff frequency (common base)
- fhre—Small-signal, short-circuit, forwardcurrent, transfer-ratio cutoff frequency (common collector)
- fhfe—Small-signal, short-circuit, forward-current, transfer-ratio cutoff frequency (common emitter)
- $f_{\rm max}{-}{\sf Maximum}$ frequency of oscillation $G_{\rm PB}{-}{\sf Large\text{-}signal}$ average power gain
- (common base)
- G_{pb} —Small-signal average power gain (common base)
- $G_{\rm PC}$ —Large-signal average power gain (common collector)
- G_{pe} —Small-signal average power gain (common collector)
- **G**_{PE}—Large-signal average power gain (common emitter)
- G_{pe} —Small-signal average power gain (common emitter)
- h_{FB}—Static value of the forward-current transfer ratio (common base)
- h_{fb}—Small-signal, short-circuit, forwardcurrent transfer ratio (common base)
- hFC-Static value of the forward-current transfer ratio (common collector)
- hte—Small-signal, short-circuit, forwardcurrent transfer ratio (common collector)
- h_{FE}—Static value of the forward-current transfer ratio (common emitter)
- h_{fe} —Small-signal, short-circuit, forward-current transfer ratio (common emitter)
- h_{IB}—Static value of the input resistance (common base)
- h_{1b}—Small-signal value of short-circuit input impedance (common base)
- h_{IC}—Static value of the input resistance (common collector)
- hie-Small-signal value of short-circuit input impedance (common emitter)
- h_{IE}—Static value of the input resistance (common emitter)
- hie—Small-signal value of short-circuit input impedance (common emitter)
- h_{1e} (real)—Real part of small-signal value of short-circuit input impedance (common emitter)

- hob-Static value of open-circuit output conductance (common base)
- hob—Small-signal value of open-circuit output admittance (common base)
- hoc-Static value of open-circuit output conductance (common collector)
- hoc-Small-signal value of open-circuit output admittance (common collector)
- h_{0E}—Static value of open-circuit output conductance (common emitter)
- hoe—Small-signal value of open-circuit output admittance (common emitter)
- h_{rb}—Small-signal value of open-circuit, reverse-voltage transfer ratio (common base)
- h_{re}—Small-signal value of open-circuit, reverse-voltage transfer ratio (common collector)
- h_{re}—Small-signal value of open-circuit, reverse-voltage transfer ratio (common emitter)
- i—Intrinsic region of a device (where neither holes nor electrons predominate)
- In-Base current (DC)
- In-Base current (rms)
- in-Base current (instantaneous)
- Ic-Collector current (DC)
- I_c—Collector current (rms)
 i_c—Collector current (instantaneous)
- I_{CRO}—Collector cutoff current (DC), emitter open
- I_{CEO} -Collector cutoff current (DC), base
- I_{CER}—Collector cutoff current (DC), with specified resistance between base and emitter
- Icex-Collector current (DC), with specified circuit between base and emitter
- I_{CES}—Collector cutoff current (DC), with base short-circuited to emitter
- IE-Emitter current (DC)
- Ie-Emitter current (rms)
- ie-Emitter current (instantaneous)
- $I_{\rm EBO}$ -Emitter cutoff current (DC), collector open
- Ir-Forward current (DC)
- ir-Forward current (instantaneous)
- In-Average output (rectified) current
- In-Reverse current (DC)

i_R-Reverse current (instantaneous)

K_e-Thermal derating factor

Le-Conversion loss

N, n-Region of a device where electrons are the majority carriers

NF-Noise figure

P, p—Region of a device where holes are the majority carriers

PRE—Total power input (DC or average) to the base electrode with respect to the emitter electrode

pne—Total power input (instantaneous) to the base electrode with respect to the emitter electrode

Pos—Total power input (DC or average) to the collector electrode with respect to the base electrode

pce—Total power input (instantaneous) to to the collector electrode with respect to the base electrode

Pee-Total power input (DC or average) to the collector electrode with respect to the emitter electrode

pcε—Total power input (instantaneous) to the collector electrode with respect to the emitter electrode

 $P_{\rm EB}$ -Total power input (DC or average) to the emitter electrode with respect to the base electrode

PER—Total power input (instantaneous) to the emitter electrode with respect to the base electrode

 P_{1B} —Large-signal input power (common base)

P_{1b}—Small-signal input power (common base)

Pro—Large-signal input power (common collector)

Pic-Small-signal input power (common collector)

Pie—Large-signal input power (common emitter)

P1e—Small-signal input power (common emitter)

PoB-Large-signal output power (common hase)

Pob—Small-signal output power (common base)

Poc-Large-signal output power (common collector)

Poc-Small-signal output power (common collector)

Poe-Large-signal output power (common emitter)

Poe—Small-signal output power (common emitter)

 P_T —Total power input (DC or average) to all electrodes

p_T—Total power input (instantaneous) to all electrodes

R_R-External base resistance

Rc-External collector resistance

res (sat)—Collector-to-emitter saturation resistance

RE-External emitter resistance

R₁.—Load resistance

T—Temperature

T_A-Ambient temperature

To-Case temperature

ta-Delay time

tr-Fall time

tr-Forward recovery time

T_J-Junction temperature

Topr-Operating temperature

tp-Pulse time

tr-Rise time

trr-Reverse recovery time

t_s—Storage time

 T_{stg} —Storage temperature

tw-Pulse average time

θ-Thermal resistance

θ_{J-A}—Thermal resistance, junction-toambient

 $\theta_{ extsf{J-C}}$ —Thermal resistance, junction-to-case

VBR-Base supply voltage (DC)

V_{BC}—Base-to-collector voltage (DC)

V_{be}-Base-to-collector voltage (rms)

V_{bc}—Base-to-collector voltage (instantaneous)

VBB-Base-to-emitter voltage (DC)

V_{be}-Base-to-emitter voltage (rms)

Vbe—Base-to-emitter voltage (instantaneous)

V_{CB}—Collector-to-base voltage (DC)

V_{cb}-Collector-to-base voltage (rms)

v_{cb}—collector-to-base voltage (instantaneous)

Vcc-Collector supply voltage (DC)

VCE-Collector-to-emitter voltage (DC)

 V_{ce} —Collector-to-emitter voltage (rms)

v_{ce}—Collector-to-emitter voltage (instantaneous)

V_{CE} (sat)—Collector-to-emitter saturation voltage

VEB-Emitter-to-base voltage (DC)

Veb-Emitter-to-base voltage (rms)

v_{eb}—Emitter-to-base voltage (instantaneous)

V_{EC}-Emitter-to-collector voltage (DC)

Ver-Emitter-to-collector voltage (rms)

vec—Emitter-to-collector voltage (instantaneous)

VEE-Emitter supply voltage (DC)

V_F-Forward voltage (DC)

v_F-Forward voltage (instantaneous)

VCBF-DC open-circuit voltage (floating potential) between collector and base, with emitter biased in reverse direction with respect to base

V_{ECF}—DC open-circuit voltage (floating potential) between emitter and collector, with base biased in reverse direction with respect to collector

 V_{RT} —Reach-through voltage


V_R-Reverse voltage (DC)

v_R-Reverse voltage (instantaneous)


46. EIA TRANSFORMER COLOR CODE

The following diagrams illustrate the color code for transformers recommended by the EIA.


(A) Power Transformers

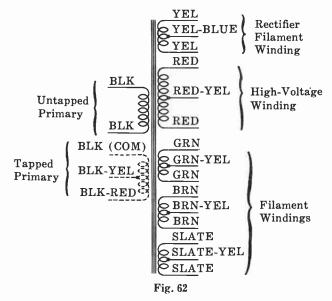

(B) IF Transformers

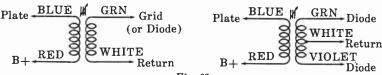



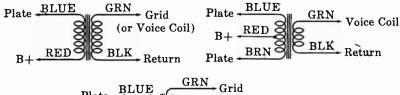

47. RESISTOR AND CAPACITOR COLOR CODES

The present method and some of the older methods of color-coding resistors and capacitors are given in Figs. 65A and B (pages 89 and 90).

48. ELECTRONIC SCHEMATIC SYMBOLS

The most common schematic symbols are illustrated in Figs. 66A, B, C, and D (pages 91, 92, 93, and 94).

89

		MC	DI DED MI	CA CAPACITOR	CODES								MOLDED PAR	ER CAPACI	FOR CODES	
		****		ity Given In MA									(Capaci	ty Given In	MMF)	
			MULTI-	Ity orver min		ASS OR			_						MOLDED PAPER TU	
	COLOR		PLIER	TOLERANCE		CTERISTIC			1 1	OLOR	DIGIT	MULTI- PLIER	TOLERANCE	_		gnificant
	BLACK	0	1	20%		A	-			ACK	O	1	20%	//	, 2nd∫ Fi	gures
1	BROWN	1 2	10	1% 2%		B C				NWO	1	10		//	MI	itlplier
	ORANGE	3	1000	3%		D D	Ì		RI		2	100		//.		lerance
	YELLOW	4	10000	""	1	E				RANGE	3	1000			W W CI L	
	GREEN	5		5%(EIA)		F(JAN) G(JAN)				REEN	5	100000	5%			
	BLUE	7				G(JAN)	-			JUE	6	1000000		/	lst -	Significant
	-GRAY	8				I(EIA) J(EIA)	1			OLET	7 8			Indicates O		Voltage Figures
	WHITE	9		F. (7. 1. 1. 1. 1. 1. 1. 1. 1. 1. 1. 1. 1. 1.		J(EIA)				HITE	9		10%	Foil . May B		, Figures
	GOLD		.1 .01	5%(JAN) 10%						DLD			5%	Either End.		Two Zeros To Sig-
	DEVER			10.0						LVER	Į		10%	Also Be Inc	dicated By nific	cant Voltage Fig-
10	lass or chars	cterist	lc denotes	specifications o	f design i	nvolving Q factors	3,			COTO	ì		50.0			. One Band Indi-
14	mperature co	efficie	nts, and o	roduction test re	quiremen	its.	1		-				i			s Voltage Ratings
A	llaxial lead m or ±1.0 MMF	ica cap	acitors ha	ve a voltage rati:	ng of 300,	500, or 1000 volts	i.							Or Black St	tripe. Und	er 1000 Volts.
F	MOLDED- IN			$\overline{}$	<u> </u>		-				T			1		E T.C. TUBULAR
L		ERAMI		LEAD	TYP	OGRAPHICALLY	MARKED CERAMICS			JA	TER -	TOLEF 10MMF	OVER	{	·CERA	
	•		st \Signii	Geant						DE.		or LESS	10MMF			- 1st Significant - 2nd Figures
	/		nd Figur	res						C		±0.25MMF			//_	- Ziigi rigures - Multiplier
	//	Ñ	Aultiplier	-		/— Temp	Temperature Coefficient			E		±0.5MMF	±1%		///_	- Tolerance
.	///	/	Tolerand	e l		Capacity				i		±2.0MMF	±2%		-n-///	
; J.				-	-	NTSO SUPUSING			J			±5% ±10%			J))	
- 1	CHRRN	H	Tempera	tura	1		Tolerance			l K			±20%			Coeff. Multiplier
			Coefficie											1	T. C. 'Sig	gnificant Figure
\vdash																
-	COL	OR BAN	D SYSTE	M			RES	ISTOR CODES (RESISTA	NCE GIV	EN IN C	HMS)		-		BODY-END-DOT	
- 1			na Tes	gnificant						_	mot			-		-1st Significant
			– 150 (3) – 2nd! Fi			COLOR BLACK	DIGIT 0	MULTIPLIER	TOLERANCE				1	/ ,	-2nd∫ Figures	
- 1		//	— Zilgj ri — Multipl			BROWN	1	10		±1%	,			1	m 69 58	•
	/	1/	— Tolerar			RED	2	100		±2%						1
- 1						ORANGE YELLOW	3	1000 10000		±3% GMV					-0 0-	- Multiplier
	<u> </u>	g .	-			GREEN	5	100000		±5%	(EIA Al	ternate)	1		1	- Tolerance
- 1	E	BH PI		Ì		BLUE	6	1000000		±6%				-	BODY - END BA	
			VIOLET	7	10000000 .01 (EIA Alternate)		±12	1/2%*		ì		BODI - END BA	1st Significant			
	Resistors With Black Body Color Are		WHITE	9	.1 (EIA Alternate)		±109	EIA A	lternate)				2nd Figures			
- 1	Composition, Non-Insulated. Go		GOLD		.1 (JAN and EIA Prefe		±5%	(JAN an	d (EIA Pre	(erred)		/ 7	and ugues			
	Resistors With Colored Bodies Are			SILVER NO COLOR		.01 (JAN and EIA Prei	errea)	±109		nu EIA PTe				J _		
- 1	Composition	n, insi	ılated.					d minimum value, or -0	100% tol					1	F	Maria (4.5-11-)
Į	Wire-Wour	d Resi	stors Hav	e The 1st		13, 6, 12	1/2, and	30% are ASA 40, 20, 10,	and 5 ste	p tolera	nces.				\	- Multiplier
	Digit Color	Band [Wire-Wound Resistors Have The 1st Digit Color Band Double Width.													- Tolerance

Resistor

and

Capacitor

Color

Codes

(Cont'd

Fig.

65 H

Electronic Schematic Symbols

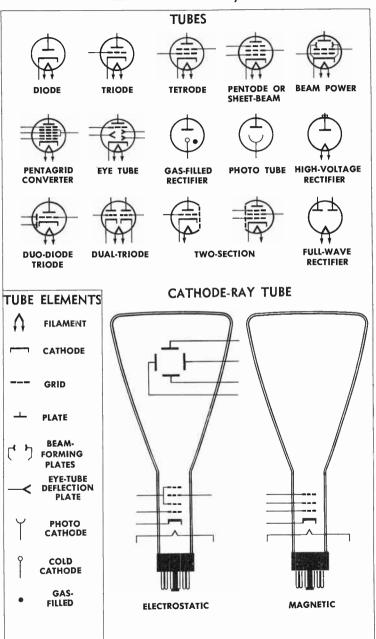


Fig. 66A

Electronic Schematic Symbols—(Cont'd)

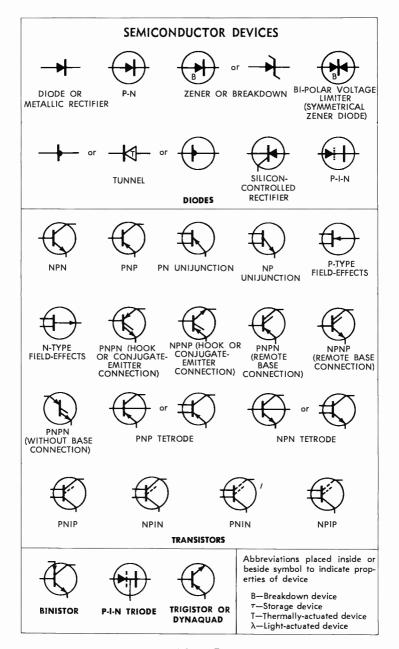


Fig. 66B

Electronic Schematic Symbols—(Cont'd)

COMPUTER SYMBOLS	BATTERIES
A	# =
$\frac{B}{B}$ $A \cdot B$ $A \cdot B$ $A \cdot B$	ONE-CELL
AND GATE OR GATE NOT GATE	¥UUUV⊫
	MULTICELL
PIEZOELECTRIC CRYSTALS WIRING	GROUNDS
卓 /	
FREQUENCY Monaural Stereo WIRES WIRES	= <i>/////</i>
DETERMINING PHONO CARTRIDGES CONNECTED CROSSING RESISTORS	
-mmmll-l	
FIXED VARIABLE TAPPED	TEMPERATURE
CAPACITORS	LAMPS
 ÷ ÷ ÷ * * • • • • • • • • •	
Non- SPARK	
FIFCTROLYTICS	ILAMENT NEON
INDUCTORS FUSES	METERS
	Q
	AMMETER VOLTMETER
AIR POWDERED- IRON VARIABLE CORE IRON CORE CORE	-GALVANOMETER MILLIAMMETER
TRANSFORMERS	-MICROAMMETER
TRANSFORMERS	אל אל
	IggI
	Täet
VARIABLE AUTO- POWER AIR CORE IRON CORE CORE TRANSFORMER	IF
SPEAKERS	LECTRO-
	STATIC
Field 9	TRANSDUCER
PM EM ELECTRO- GENERAL DYNAMIC STATIC	-
Jiane	

Fig. 66C

Electronic Schematic Symbols—(Cont'd)

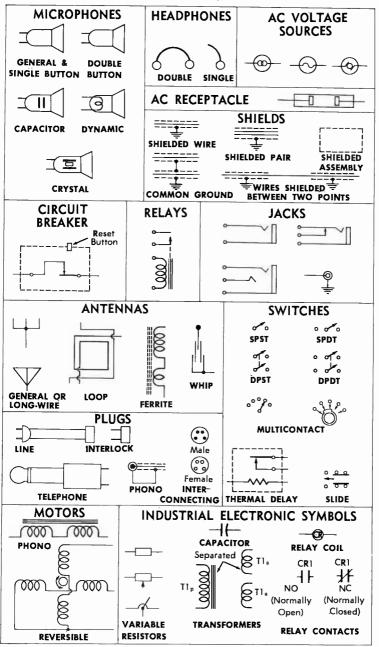


Fig. 66D

Service and Installation Data

49. COAXIAL CABLE CHARACTERISTICS

Table XVIII lists the most frequently-used coaxial cables. The electrical specifications include the impedance in ohms, capacitance in micromicrofarads per foot, attenuation in db per 100 feet, and the outside diameter. (See page 43 for formulas.)

Table XVIII. Coaxial Cable Characteristics

Туре		Cap.		Att	enual	tion—d	b per 10	00 ft.	
RG	Imp.	(mmf	Diam.	1	10	100	400	1000	
/υ	(ohms)	perft.)	(inches)	m¢	mc	m¢	mc	mc	REMARKS
5	52.5	28.5	.332	.21	.77	2.9	6.5	11.5	Small, double braid
5A	50	29	.328	.16	.66	2.4	5.25	8.8	Small, low loss
6	76	20	.332	.21	.78	2.9	6.5	11,2	IF & video
8	52	29.5	.405	.16	.55	2.0	4.5	8,5	General purpose
9	51	30	.420	.12	.47	1.9	4.4	8.5	General purpose
9A	51	30	.420	.16	.59	2.3	5.2	8.6	Stable attenuation
11	75	20.5	.405	.18	.62	2.2	4.7	8.2	Community TV
13	74	20.5	.420	.18	.62	2.2	4.7	8.2	IF
14	52	29.5	.545	.10	.38	1.5	3.5	6.0	RF power
16	52	29.5	.630		—		—	-	RF power
17	52·	29.5	.870	.06	.24	.95	2.4	4.4	RF power
19	52	29.5	1.120	.04	.17	.68	1.28	3.5	Low-loss RF
21	53	29	.332	1.4	4.4	14.0	29.0	46.0	Attenuating cable
22	95	16	.405	.41	1,3	4.3	8.8	_	Twin conductors
23	125	12	.65 X .945	_	.4	1.7		—	Twin conductors (balanced)
25	48	50	.565			_		_	Pulse
26	48	50	.525	_					Pulse
27	48	50	.675						Pulse
28	48	50	.805		l —		l —	—	Pulse
33	51	30	.470		—	—			Pulse
34	71	21.5	.625	.065	.29	1.3	3.3	6.0	Flexible, medium
35	71	21.5	.945	.064	.22	.85	2.3	4.2	Low-loss video
36	69	22	1.180	_	—	l —		l —	
41	67.5	27	.425	_	—	<u> </u>		_	Special twist
54A	58	26.5	.250	.18	.74	3.1	6.7	11.5	Flexible, small

Table XVIII. Coaxial Cable Characteristics—(Cont'd)

Туре		Cap.		A	tenua	tion—c			
RG	Imp.	(mmf	Diam.	1	10	100	400	1000	1
/U	(ohms)	perft.)	(inches)	mc	mc	mc	mc	mc	REMARKS
55	53.5	28.5	.206	.36	1.3	4.8	10.4	17.0	Flexible, small
56	l —	l —	.535	l —	l —	_	_	I —	Pulse
57	95	17	.625	81.	.71	3.0	7.3	13.0	Twin conductors
58	53.5	30	.195	.38	1.4	5.2	11.2	20.0	General purpose
58A	50	30	.195	.42	1.6	6.2	14.0	24.0	Test leads
59	73	21	.242	.30	1.1	3.8	8.5	14.0	TV lead-in
60	50	_	.425	_	_		_		Pulse cable
61	500	_	_	—	—	—	—	—	Special 500-ohm
62	93	13.5	.242	.25	.83	2.7	5.6	9.0	twin-lead
		10.5		.23	.03	2.7	3.0	9.0	Low capacity, small
63	125	10	.405	.19	.61	2.0	4.0	6.3	Low capacity
64 65	48	50	.495	—	-	1 —	—	—	Pulse
71	950 93	44 13.5	.405 .250					_	Coaxial delay line
77	48	50	.415	.25	.83	2.7	5.6	9.0	Low capacity, small
	40	30	.415	_	_	-	_	_	Pulse
78	48	50	.385	_	_	_	_	<u> </u>	Pu!se
87A	50	29.5	.425	.13	.52	2.0	4.4	7.6	Teflon dielectric
88 101	48 75	50	.490	_	_		_	-	Pulse
101	140	_	.588	_	_		_	-	
102	140	_	1.088	_	_	_	-	_	
108	76	25	.245		_	_	_	_	Twin conductors
114	185	6.5	.405	-	_		—	_	Extra flexible
117	50	29	.730	.05	.20	.85	2.0	3.6	Teflon & Fiberglas
119	50	29	.470		_				Teflon & Fiberglas
122	50	29.3	.160	.40	1.70	7.0	16.5	29.0	
126	50	29	.290	3.20	9.0	25.0	47.0	72.0	Teflon & Fiberglas
140	73	21	.242	.33	1.03	3.3	6.9	11.7	Teflon & Fiberglas
141	50	29	.195	.35	1.12	3.8	8.0		Teflon & Fiberglas
142	50	29	.206	.35	1.12	3.8	8.0	13.8	Teflon & Fiberglas
143	50	29	.325	.24	.77	2.5	5.3	9.0	Teflon & Fiberglas
144	72	21	.395	.16	.53	1.8	3.9	7.0	Teflon & Fiberglas
174	50	30	.10	_	_	-	19.0		Miniature coaxial
	_								

50. TEST-PATTERN INTERPRETATION

The Indian Head test pattern in Fig. 67 is transmitted by many TV stations and is also used in the flying-spot scanner type of video pattern generators. In addition, many of the features of this pattern are incorporated in the individual test patterns of TV stations. The test pattern is a quick and accurate way of checking receiver adjustments and operating conditions.

In the following explanation, the significance of each point indicated by an arrow and letter on the test pattern is

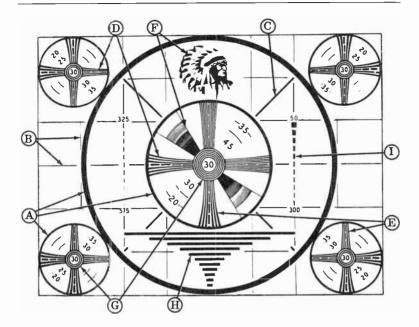


Fig. 67

explained. For example, the letter A indicates the circles at each corner and the two circles in the center of the pattern.

A. The six circles serve as a check for the adjustment of the Height, Width, Vertical Linearity, Horizontal Linearity, and Horizontal Drive controls and the ion-trap magnets, as well as the over-all operation of the vertical, horizontal, and power-supply circuits. All circles should be round and should not overlap the sides of the picture tube by more than three-fourths of an inch.

- B. The eight squares along the horizontal axis and the six squares along the vertical axis indicate the standard aspect ratio of 4:3. These squares serve as a check for rectangular distortion caused by misadjusted or missing anti-pincushion magnets or by defects in the deflection yoke.
- C. The four diagonal lines are used to check interlace. Poor interlace due to improper operation of the vertical-oscillator circuit will make the lines appear jagged.
- D. The horizontal wedges located at each corner and in the center of the pattern serve as a check of the vertical resolution and interlace. Note the point where the horizontal lines are no longer clear and straight. The breaks in the

center line indicate 50-line intervals. That is, starting from the left (on the center and left-hand wedges), the first break indicates vertical resolution of 150 lines; the others, 200, 250, 300, and 350. The first break to the right of the center circles indicates 500 lines, then 450, 400, 350, and 300. The wedges at the top and bottom of the right side of the pattern give the same information except that the wedge is reversed. The numbers (20, 30, 35, and 45) between the vertical and horizontal wedges in each circle indicate these vertical resolution check points, with the last zero omitted.

E. The vertical wedges at each corner and at the center of the pattern indicate the horizontal resolution. Hence, they serve as a check on all video-amplifying circuits and alignment. Note the point where the vertical lines are no longer clear. Each break in the center line of the vertical wedge indicates 50 lines, as explained for D. The horizontal resolution can be converted to bandwidth by dividing the number of lines by 80. For example, if the lines are no longer clear at the 300-line point, the bandwidth equals 300 divided by 80, or 3.75 mc.

F. The two diagonal wedges and the Indian head indicate the contrast ratio. Therefore, they can be used to check the adjustment of the Contrast, Brightness, and AGC controls, as well as the video-amplifying and picture-tube circuits. When video-amplifier and picture-tube circuits are operating properly and the controls are properly adjusted, four degrees of shading should be observed, ranging from black at the center to light gray at the outermost point on the wedge.

G. The bull's-eyes at each corner and at the center of the pattern indicate receiver focus. Hence, they serve to check the adjustment of the focusing device or, if electromagnetic focusing is employed, of the low-voltage power supply.

H. The eleven horizontal bars represent half cycles of square-wave signals, and are used to check the low-frequency response or phase shift of the receiver. The bars, from top to bottom, represent the following video signals: 19 kc, 28 kc, 38 kc, 56 kc, 75 kc, 113 kc, 150 kc, 225 kc, 300 kc, 450 kc, and 600 kc. If the low-frequency response is satisfactory, the bars will be sharply defined. However, if the receiver has poor low-frequency response due to a defect in the video-amplifier circuit or misadjustment of the Fine

Tuning, Contrast, or AGC controls, the bars will have trailing black or white edges.

I. The single resolution lines at each side of the center circle represent the width of a single line ranging from 50 to 575 lines, in steps of 25. These lines are used to check for ringing in the video amplifier at frequencies from approximately 600 kc to 7 mc. When ringing occurs at any frequency, the resolution line corresponding to that frequency will be repeated several times at evenly spaced intervals. To convert the resolution lines to the frequency, divide the number of lines by 80, as explained in the foregoing for E.

51. CLASSES OF VACUUM-TUBE OPERATION

Class-A amplifiers are biased so that the AC input signal is on the linear portion of their characteristic curve, as shown in Fig. 68.

The output signal is a faithful reproduction of the input signal. The only difference is in the amplification. Plate current flows at all times in a Class-A amplifier. Class-A amplifiers are used in audio or other applications where distortion cannot be tolerated. Their efficiency is around 20 to $25\,\%$.

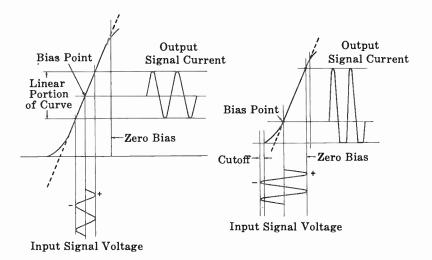


Fig. 68

Fig. 69

Class-AB amplifiers are biased as shown in Fig. 69. Here, plate current will flow more than one half but less than a full cycle. Higher plate voltages and currents can be employed than for Class-A amplifiers because the increased negative grid bias will hold the plate current within the plate-dissipation rating. For this reason, more power output can be obtained from Class-AB operation. Class-AB amplifiers may be operated either single-ended or in push-pull.

Class-AB amplifiers are subdivided into two classes, AB_1 and AB_2 . In a Class-AB₁ amplifier, no grid current will flow.

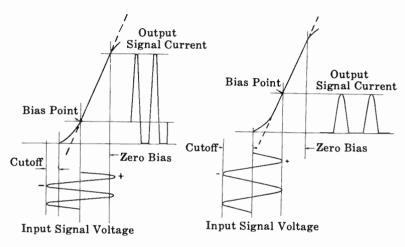


Fig. 70 Fig. 71

That is, the peak signal voltage applied to each grid is never greater than the negative grid bias; therefore, the grid is never driven positive. In a Class-AB₂ amplifier, grid current will flow because the peak signal is greater than the negative grid bias and the grid is driven positive during a portion of the cycle, as shown in Fig. 70. The efficiency of Class-AB amplifiers varies from 40 to 75%, depending on the bias voltage.

Class-B amplifiers are biased at or near cutoff, as shown in Fig. 71. When on exciting grid voltage is applied, plate current is near zero; therefore, it will flow only during approximately half of a cycle. Because plate current flows for only one half the cycle, Class-B amplifiers must be operated in push-pull. More power can be obtained from Class-B amplifiers than from Class-A or Class-AB amplifiers without

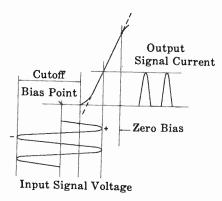


Fig. 72

excessive plate dissipation. The efficiency of Class-B amplifiers is around 40 to $60\,\%$.

Class-C amplifiers are biased below cutoff, as shown in Fig. 72. Therefore, plate current flows for less than half of a cycle. More power can be obtained from Class-C than Class-B amplifiers. Usually, Class-C amplifiers are used in a selective-tuned circuit, such as those employed in RF amplifiers. The high distortion, characteristic of Class-C amplifiers, is overcome by the flywheel effect of the tuned circuits. The efficiency of Class-C amplifiers is around 50 to 80%.

52. MINIATURE LAMP DATA

Table XIX (page 102) lists the most common miniature lamps and their characteristics. The outline drawings for each lamp are given in Fig. 73 below.

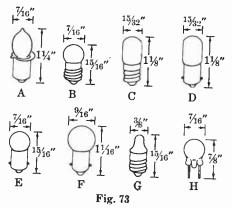


Table XIX. Miniature Lamp Data

Lamp No. Volts Am		Amps	Bead s Color Base		Bulb Type	Fig. No	
PR2	2.4	0.50	Blue	rl	D 011	 	
PR3	3.6	0.50	Green	Flange	B-31/2	A	
PR4	2.3	0.27	Yellow	Flange	B-31/2	A	
PR6	2.5	0.30	Brown	Flange	B-31/2	A	
PR12	5.95	0.50		Flange	B-31/2	A	
	3.73	0.50	White	Flange	B-31/2	A	
12	6.3	0.15		2-Pin	G-31/2	Н	
13	3.8	0.30	Green	Screw	G-31/2	B	
14	2.5	0.30	Blue	Screw	G-31/2	В	
40	6.3	0.15	Brown	Screw	T-31/4	C	
41	2.5	0.50	White	Screw	T-31/4	c	
40					1-3 74		
42	3.2	0.35*	Green	Screw	T-31/4		
43	2.5	0.50	White	Bayonet	T-31/4 .	D	
44	6.3	0.25	Blue	Bayonet	T-31/4	D	
45	3.2	0.35†	Green†	Bayonet	T-31/4	D	
46	6.3	0.25	Blue	Screw	T-31/4‡	l c	
47	6.3	0.15	Brown	Bayonet	T-31/4	D	
48	2.0	0.06	Pink	Screw	T-31/4	c	
49	2.0	0.06	Pink	Bayonet	T-31/4	D	
50	6.3	0.20	White	Screw	G-31/2	В	
51	6.3	0.20	White	Bayonet	G-31/2	E	
				22,01101	0-372	C	
55	6.3	0.40	White	Bayonet	G-41/2	F	
57	14.0	0.24	White	Bayonet	G-41/2	F	
112	1.1	0.22	Pink	Screw	rew TL-3		
222	2.2	0.25	White	Screw	TL-3	G	
233	2.3	0.27	Purple	Screw G-31/2		В	
291	2.9	0.17	White	Screw	T-31/4	С	
292	2.9	0.17	White	Screw	T-31/4	Č	
1490	3.2	0.16	White	Bayonet			
1891	14.0	0.23	Pink	Bayonet	T-31/4	D D	
1892	14.0	0.12	White	Screw	T-31/4	c	

‡ Frosted.

53. GAS-FILLED LAMP DATA

The characteristics of the more common gas-filled lamps are given in Table XX. The value of external resistance needed for operation with circuit voltages from 110 to 600 volts is given in Table XXI.

^{*} Some brands are .50 amp.
† Some brands are .50 amp and white bead.

Table XX. Gas-Filled Lamps

Number	Hours of Average Useful Life*	Type Gas	Max. Length In inches	Base	Amps	Volts	Watts
AR-1	3.000	Argon	3 1/2	Medium Screw	0.018	110-125	2
AR-3	1,000	Argon	1 5/8	Cand. Screw	0.0035	110-125	1/4
AR-4	1,000	Argon	1 1/2	Double-Contact Bayonet	0.0035	110-125	1/4
NE-2	Over 25,000	Neon	1 1/16‡	Unbased	0.003	110-125	1/25
NE-2A	Over 25,000	Neon	27/32‡	Unbased	0.003	110-125	1/25
NE-17	5,000	Neon	1 1/2	Double-Contact Bayonet§	0.002	110-125	1/4
NE-17	10,000	Neon	2 1/4	Medium Screw§	0.012	110-125	1
NE-32	10,000	Neon	2 1/16	Double-Contact Bayonet§	0.012	110-125	1
NE-34	8,000	Neon	3 1/2	Medium Screw	0.018	110-125	2
NE-40	8,000	Neon	3 1/2	Medium Screw§	0.030	110-125	3
NE-45	Over 7,500	Neon	1 5/8	Cand. Screw	0.002	110-125	1/4
NE-48	Over 7,500	Neon	1 1/2	Double-Contact Bayonet	0.002	110-125	1/4
NE-51	Over 15,000	Neon	1 3/16	Miniature Bayonet	0.0003	110-125	1/25
NE-56	10,000	Neon	2 1/4	Medium Screw§	0.005	220-250	1
NE-57	5,000	Neon	1 5/8	Cand. Screw§	0.002	110-125	1/4
NE-58	Over 7,500	Neon	1 5/8	Cand. Screw	0.002	220-250	1/2

^{*} Life on DC is approximately 60% of AC values.

[†] For 110-125V operation.

[‡] The dimension is for glass only.

[§] On DC circuits the base should be negative.

Type	110-125V	220-300V	300-375V	375-450V	450-600V
AR-1	Included in Base	10,000	18,000	24,000	30,000
AR-3	Included in Base	68,000	91,000	150,000	160,000
AR-4	15,000	82,000	100,000	160,000	180,000
NE-2	200,000	750,000	1,000,000	1,200,000	1,600,000
NE-2A	200,000	750,000	1,000,000	1,200,000	1,600,000
NE-17	30,000	110,000	150,000	180,000	240,000
NE-30	Included in Base	10,000	20,000	24,000	36,000
NE-32	7,500	18,000	27,000	33,000	43,000
NE-34	Included in Base	9,100	13,000	16,000	22,000
NE-40	Included in Base	6,200	8,200	11,000	16,000
NE-45	Included in Base	82,000	120,000	150,000	200,000
NE-48	30,000	110,000	150,000	180,000	240,000
NE-51 NE-56 NE-57 NE-58	200,000 Included in Base Included in Base Included in Base	750,000 82,000	1,000,000	1,200,000	1,600,000

Table XXI. External Resistances Needed For Gas-Filled Lamps

54. LIGHT PROPERTIES OF COLOR TV


When we speak of light, we usually think of light coming from the sun or the light emitted from some artificial lighting source, such as electrical lighting. This light is referred to as direct light. Another type of light is indirect or reflected light, which is given off by an object when direct light strikes it. The difference between these two types of light is that the indirect light depends upon the direct light. When light is not shining upon an object, no light will be given off unless the object contains self-luminating properties.

White light is made up of different colors. This composition can be shown by passing light through a prism. The light spectrum is broken up into its constituent wavelengths, each representing a different color. The ability to disperse the light by a prism stems from the fact that light of shorter wavelengths travels slower through glass than does light of longer wavelengths. The spectrum ranges from violet on the lower end to red on the upper end. In between fall blue, green, yellow, and orange. A total of six distinct colors are visible when white light passes through a prism. Since the colors of the spectrum pass gradually from one to the other, the theoretical number of colors becomes infinite.

There are three color attributes used to describe any one color or to differentiate between several colors. These are (1) hue, (2) saturation, and (3) brightness. Hue is the quality used to identify any color under consideration, such as red, blue, or yellow. Saturation is a measure of the absence of dilution by white light, and can be expressed with such terms as rich, deep, vivid, or pure. Brightness defines the amount of light energy contained within a given color.

Color may be produced by either of two processes. When working with paint pigments, the subtractive process is employed. The other process of mixing colors is called the additive process. This process is used in color television. The colors in the additive process do not depend upon an incident light source. Self-luminous properties are characteristic of the additive colors. Phosphorescent signs which glow in the dark are good examples of this process. Cathoderay tubes contain self-luminance properties; so it is only logical that the additive process would be employed in color television.

The three primaries for the additive process of color mixing are red, green, and blue. Two requirements for the primary colors are that each primary must be different and that the combination of any two primaries must not be capable of producing the third. Red, green, and blue were chosen for the additive primaries because they fulfilled these requirements and because it was determined that the greatest number of colors could be produced by the combination of these three colors.

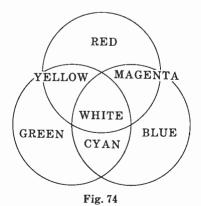

The three additive primaries used in color television are shown in Fig. 74. From the illustration we can see that by mixing colors in certain proportions, we can obtain the following:

Red + Green = Yellow
Red + Blue = Magenta
Blue + Green = Cyan
Yellow + Blue = White
Cyan + Red = White
Magenta + Green = White
Red + Blue + Green = White
Cyan + Magenta + Yellow = White

It is not necessary to overlap the primary colors in the additive process to produce a different color. They may be placed close to each other, and at a certain viewing distance the two colors will blend and produce the new color.

To be compatible, the composite color signal must contain a complete black-and-white signal to which an additional signal is added to convey the color information. The black-and-white signal (also called the luminance signal) carries all the information pertaining to the brightness of the scene being televised, by means of amplitude modulation of the carrier envelope. The other color attributes—hue and saturation—are carried by the color signal.

To keep the color signal from interfering with black-and-white reception of the composite color signal, the color information is included within the 4.25-mc video band by an interleaving process. This process is possible because the energy of the luminance signal concentrates at specific intervals in the frequency spectrum. The spaces between these intervals are relatively void of energy, and the energy of the chrominance signal can be caused to concentrate in these spaces.

The color or chrominance signal is conveyed by means of a subcarrier at 3.579 megacycles. This frequency was chosen so that the interleaving process could be accomplished. This chrominance signal is modulated in both phase and amplitude. A change in the phase of this signal represents a change in the hue of the scene, and a change in amplitude

represents a change of color saturation. A color sync signal which keeps the receiver circuits synchronized to the color information is included in the composite signal. This signal is placed on the "back porch" of the horizontal blanking pedestal and is transmitted at a fixed or reference phase. This signal is known as the "color burst" signal.

55. RELAY REWINDING DATA

The following nomograph can be used if it is desired to rewind a relay for operation on a different voltage. To calculate the wire size needed for operation on the desired voltage, first lay a straightedge across the points where the present voltage and the desired voltage appear on the first

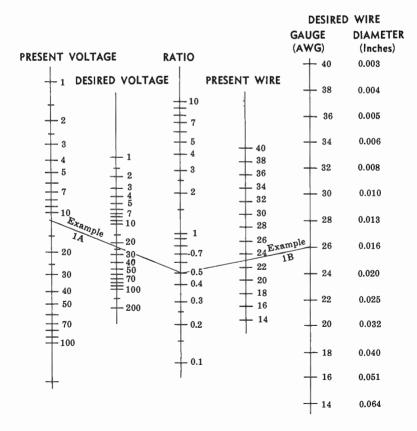


Fig. 75

two columns, and note the point where the straightedge intersects the ratio column. Then lay the straightedge across this point on the ratio column and the present wire gauge column. Read the wire gauge needed for the desired voltage from the fifth column. Directly opposite this point, the wire diameter (in inches) is also given.

Example—What size wire is needed to rewind a relay wound with No. 23 wire and designed for 12-volt operation, for operation on 24 volts?

ANSWER: No. 26 (0.0159 inch diameter). [First lay the straightedge across 12 in the first column and 24 in the second column. Note the point where the straightedge crosses the third column (.5), and lay the straightedge across this point and across 23 on the fourth column. Read the desired size from the fifth and sixth columns.]

56. SPEAKER CONNECTIONS

The following diagrams show the proper connection methods for single- or multiple-speaker operation.

(A) Single Speaker

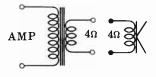


Fig. 76

(B) Two Speakers in Series

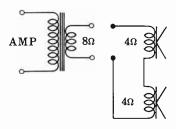


Fig. 77

(C) Speakers in Parallel

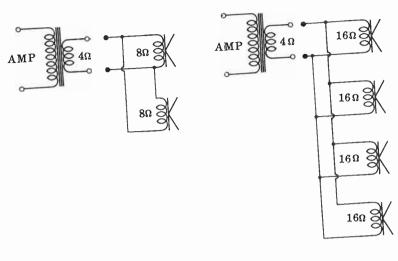


Fig. 78

(D) 70.7-Volt Hook-up Using Matching Transformers

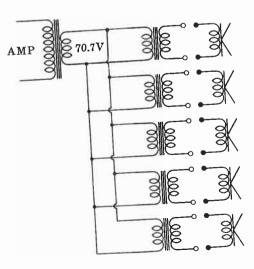


Fig. 79

57. MACHINE SCREW AND DRILL SIZES

The most common screw sizes and threads, together with the tap and clearance drill sizes, are given in Table XXII. The number listed under the "Type" column is actually a combination of the screw size and the number of threads per inch. For example, a No. 6-32 screw denotes a size No. 6 screw with 32 threads per inch.

Table XXII. Machine Screw and Drill Sizes

Туре	Tap Drill	Clearance Drill	Туре	Tap Drill	Clearance Dril	
1-64 1-72 2-56 2-64 3-48 3-56 4-40	53 53 50 50 47 45 43	47 47 42 42 36 36 36	10-24 10-32 12-24 12-28 1/4-20	25 21 16 14 7	13/64 13/64 7/32 7/32 17/64	
4-48 5-40 5-44	42 38 37	31 29 29	5/16-18 5/16-24 3/8-16 3/8-24	F 1 5/16 Q	21/64 21/64 25/64 25/64	
6-32 6-40 8-32 8-36	36 33 29 29	25 25 16 16	7/16-14 7/16-20 1/2-13 1/2-20	U 25/64 27/64 29/64	29/64 29/64 33/64 33/64	

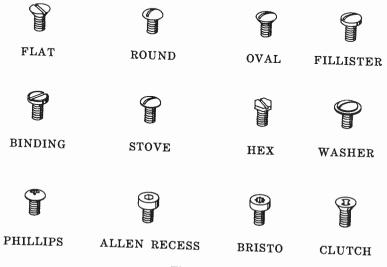


Fig. 80

58. TYPES OF SCREW HEADS

The most common types of screw heads are listed and illustrated in Fig. 80 on the preceding page.

59. RESISTANCE OF METALS AND ALLOYS

The resistance for a given length of wire is determined by:

$$R = \frac{KL}{d^2}$$

where.

R is the resistance, in ohms, of the length of wire.

K is the resistance, in ohms per circular mil foot, of the material.

L is the length of the wire in feet,

d is the diameter of the wire in mils.

The resistance, in ohms per circular mil foot, of many of the materials used for conductors or heating elements is given in Table XXIII. The resistance shown is for 20°C (68°F).

Table	XXIII.	Resistance	of	Metals	and	Alloys
-------	--------	------------	----	--------	-----	--------

Material	Symbol	Resistance (ohms per cir. mil foot)
Nichrome	Ni-Fe-Cr	675
Nichrome V	Ni-Cr	650
Manganese Nickel	Ni-Mu	85
Pure Nickel	Ni	60
High Brass	Cu-Zn	50
Commercial Bronze	Cu-Zn	25
Platinum	Pt	63.8
Iron	Fe	60.14
Zinc	Zn	35.58
Molybdenum	Мо	34.27
Tungsten	w	33.22
Aluminum	AI	16.06
Gold	Αu	14.55
Copper	Cu	10.37
Silver	Ag	9.796

60. COPPER WIRE TABLE

Copper wire sizes ranging from American wire gauge (B & S) 0000 to 40 are listed in Table XXIV (pages 112 and 113). The turns per linear inch, diameter, area in circular mils, current-carrying capacity, feet per pound, and resistance per 1000 feet are included in the table.

Table XXIV. Copper Wire Table

AWG B & S		Turns Per	Linear Inch		Diameter	Circular	Current Carrying Capacity @700 CM	Feet Per Lb.	Ohms Per
Gauge	Enamel	D.C.C.	s.c.c.	Nylon	(Inches)	Mils	Per Amp	(Bare)	1,000 Ft. @ 20°C
0000	_		_	_	.4600	211,600	302.3	1.561	0.04901
000	-		_	_	.4096	167,800	239.7	1.968	0.06180
00		_	_		.3648	133,100	190.1	2.482	0.07793
0	_	_	-	_	.3249	105,500	150.7	3.130	0.09827
1	_	3.3	3.3	_	.2893	83,690	119.6	3.947	0.1239
2	-	3.6	3.8	_	.2576	66,370	94.8	4.977	0.1563
3	_	4.0	4.2	_	.2294	52,640	75.2	6.276	0.1970
4	<u> </u>	4.5	4.7	_	.2043	41,740	59.6	7.914	0.2485
5	_	5.0	5.2	_	.1819	33,100	47.3	9.980	0.3133
6	_	5.6	5.9	_	.1620	26,250	37.5	12.58	0.3951
7	_	6.2	6.5	_	.1443	20,820	29.7	15.87	0.4982
8	7.6	7.1	7.4	_	.1285	16,510	23.6	20.01	0.6282
9	8.6	7.8	8.2	_	.1144	13,090	18.7	25.23	0.7921
10	9.6	8.9	9.3	_	.1019	10,380	14.8	31.82	0.9989
11	10.7	9.8	10.3	_	.09074	8,234	11.8	40.12	1.260
12	12.0	10.9	11.5	_	.08081	6,530	9.33	50.5 9	1.588
13	13.5	12.0	12.8	_	.07196	5,178	7.40	63.80	2.003
14	15.0	13.8	14.2	14.9	.06408	4,107	5.87	80.44	2.525
15	16.8	14.7	15.8	_	.05707	3,257	4.65	101.4	3.184

113

1		i	ı						1
16	18.9	16.4	17.9	18.6	.05082	2,583	3.69	127.9	4.016
17	21,2	18.1	19.9	<u> </u>	.04526	2,048	2.93	161.3	5.064
18	23.6	19.8	22.0	23.2	.04030	1,624	2.32	203.4	6.385
19	26.4	21.8	24.4	_	.03589	1,288	1.84	256.5	8.051
20	29.4	23.8	27.0	28.9	.03196	1,022	1.46	323.4	10.15
21	33.1	26.0	29.8	_	.02846	810.1	1.16	407.8	12.80
22	37.0	30.0	34.1	36.0	.02535	642.4	.918	514.2	16.14
23	41.3	31.6	37.6	_	.02257	509.5	.728	648.4	20.36
24	46.3	35.6	41.5	44.7	.02010	404.0	.577	817.7	25.67
25	51.7	38.6	45.6	_	.01790	320.4	.458	1,031	32.37
26	58.0	41.8	50.2	55.7	.01594	254.1	.363	1,300	40.81
27	64.9	45.0	55.0	_	.01420	201.5	.288	1,639	51.47
28	72.7	48.5	60.2	69.4	.01264	159.8	.228	2,067	64.90
29	81.6	51.8	65.4	_	.01126	126.7	.181	2,607	81.83
30	90.5	55.5	71.5	86.2	.01003	100.5	.144	3,287	103.2
31	101.0	59.2	77.5	_	.008928	79.70	.114	4,145	130.1
32	113.0	62.6	83.6	106.0	.007950	63,21	.090	5,227	164.1
33	127.0	66.3	90.3	_	.007080	50.13	.072	6,591	206.9
34	143.0	70.0	97.0	133.0	.006305	39.75	.057	8,310	260.9
35	158.0	73.5	104.0	_	.005615	31.52	.045	10,480	329.0
36	175.0	77.0	111.0	167.0	.005000	25.00	.036	13,210	414.8
37	198.0	80.3	118.0		.004453	19.83	.028	16,660	523.1
38	224.0	83.6	126.0	206.0	.003965	15.72	.022	21,010	659.6
39	248.0	86.6	133.0	_	.003531	12.47	.018	26,500	831.8
40	282.0	89.7	140.0	263.0	.003145	9.89	.014	33,410	1,049.0

Design Data

61. VACUUM-TUBE FORMULAS

The following formulas can be used to calculate the vacuum-tube properties listed.

Amplification factor:

$$\mu = \frac{\Delta E_p}{\Delta E_g}$$
 (with I_p constant)

AC (dynamic) plate resistance:

$$r_p = \frac{\Delta E_p}{\Delta I_p}$$
 (with E_g constant)

Mutual conductance (transconductance):

$$g_m = \frac{\Delta I_p}{\Delta E_g}$$
 (with E_p constant)

Gain of an amplifier stage:

$$Gain = \mu \frac{R_L}{R_L + r_n}$$

where,

 μ is the amplification factor, Δ is the variation or change in value, E_p is the plate voltage in volts, E_g is the grid voltage in volts, I_p is the plate current in amperes, R_L is the plate-load resistance in ohms, r_p is the AC plate resistance in ohms, g_m is the mutual conductance in mhos.

62. TRANSISTOR FORMULAS

The following formulas can be used to calculate the transistor properties listed.

Input Resistance:

$$R_{i} = \frac{\Delta V_{i}}{\Delta I_{i}}$$

Current Gain:

$$A_{\rm i} = \frac{\Delta I_c}{\Delta I_b}$$
 (with V_c constant)

Voltage Gain:

$$A_{\rm v} = \frac{\Delta V_{\rm c}}{\Delta V_{\rm h}}$$
 (with $I_{\rm c}$ constant)

Output 'Resistance:

$$R_o = \frac{\Delta V_o}{\Delta I_o}$$

Power Gain:

$$A_{p} = \frac{\Delta P_{o}}{\Delta P_{i}}$$

The current gain of the common-base configuration is alpha:

$$_{\alpha}=\frac{\Delta I_{c}}{\Delta I_{e}}\text{(with }V_{c}\text{ constant)}$$

The current gain of the common emitter is beta:

$$\beta = \frac{\Delta I_c}{\Delta I_b}$$
 (with V_c constant)

A direct relationship exists between the alpha and beta of a transistor:

$$a = \frac{\beta}{1+\beta} \qquad \beta = \frac{a}{1-a}$$

where,

a is the current gain of a common-base configuration,

 A_v is the voltage gain,

Ai is the current gain,

 A_p is the power gain, β is the current gain in a common-emitter configuration,


 I_b is the base current,

Ic is the collector current,

 $I_{\rm c}$ is the emitter current, $I_{\rm i}$ is the input current, $I_{\rm o}$ is the output current, $P_{\rm i}$ is the input power, $P_{\rm o}$ is the output power, $R_{\rm i}$ is the input resistance, $R_{\rm o}$ is the output resistance, $V_{\rm b}$ is the base voltage, $V_{\rm c}$ is the collector voltage, $V_{\rm i}$ is the input voltage, $V_{\rm o}$ is the output voltage.

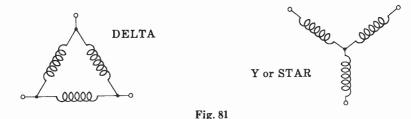63. THREE-PHASE POWER FORMULAS

In a three-phase system, there are three voltages, each separated by a phase difference of 120° : The power-supply input transformers may be connected in either a delta or a Y (star). Fig. 81 shows how the terminals are placed in relationship to the coils. In the delta connection, there is one coil between each pair of terminals; and in the Y connection, there are two. The voltage between two terminals of the Y-connected coil is equal to $\sqrt{3}$ times the voltage across one winding.



The formulas for determining the voltage across the secondary winding for each of the four possible connections are as follows:

 Δ to Y:

$$\mathbf{E}_{\mathrm{s}} = \mathbf{E}_{\mathrm{p}} \times \mathbf{N} \times \sqrt{3}$$

Y to Δ :

$$E_{\rm s} = \frac{E_{\rm p} \times N}{\sqrt{3}}$$

 Δ to Δ :

$$\mathbf{E}_{s}=\mathbf{E}_{\nu}\times N$$

Y to Y:

$$E_{\rm s}=E_{\nu}\times N$$

where,

Es is the secondary voltage, \overline{E}_{ν} is the primary voltage, N is the turns ratio.

64. COIL WINDINGS

(A) Single-Layer Coils

The inductance of single-layer coils can be calculated to an accuracy of approximately 1% with the formula:

$$L = \frac{(N \times A)^2}{9A + 10B}$$
Fig. 82

To find the number of turns required for a single-layer coil with a given inductance, the foregoing formula is rearranged as follows:

$$N = \frac{\sqrt{L(9A + 10B)}}{A}$$

where.

L is the inductance in microhenries,

N is the number of turns,

A is the mean radius in inches,

B is the length of the coil in inches.

(B) Multilayer Coils

The inductance of a multilayer coil of rectangular cross section can be computed from the formula:

$$L = \frac{0.8 (N \times A)^2}{6A + 9B + 10C}$$

$$C \downarrow B \downarrow A$$

$$A \downarrow B \downarrow A$$
Fig. 83

where,

L is the inductance in microhenries,

N is the number of turns,

A is the mean radius in inches,

B is the length of the coil in inches,

C is the depth of the coil in inches.

(C) Single-Layer Coil Chart

The chart on the following page provides an easy method for determining either the inductance or the number of turns for single-layer coils. When the length of the winding, the diameter, and the number of turns of the coil are known, the inductance can be found by placing a straightedge from the "Turns" scale to the "Ratio" (diameter ÷ length) scale and noting the point where the straightedge intersects the "Axis" scale. Then lay the straightedge from the point of intersection of the "Axis" scale to the "Diameter" scale. The point at which this line intersects the "Inductance" scale indicates the inductance (in microhenries) of the coil. The number of turns can be determined by reversing the procedure.

After finding the number of turns, consult the wire table in § 60 to determine the size of wire to be used.

Example—What is the inductance of a single-layer coil having 80 turns wound to 4 inches in length on a coil form 2 inches in diameter?

ANSWER: 130 microhenries. (First lay the straightedge as indicated by the line labeled "Example 1A." Then lay the straightedge as indicated by the line labeled "Example 1B.")

65. FILTER FORMULAS

(A) Constant-k Filters

A constant-k filter presents an impedance match to the line at only one frequency, and a mismatch at all others. The three basic configurations are the T, L (half-section), and pi.

A constant-k low-pass filter will pass frequencies below and attenuate those above a set frequency. Fig. 85 gives the circuit configurations, attenuation characteristics, and impedance characteristics of the three types of constant-k lowpass filters.

The attenuation of the L section is equal to half that of the T or pi sections. The impedance of the filter is equal to

Single-Layer Coil Chart


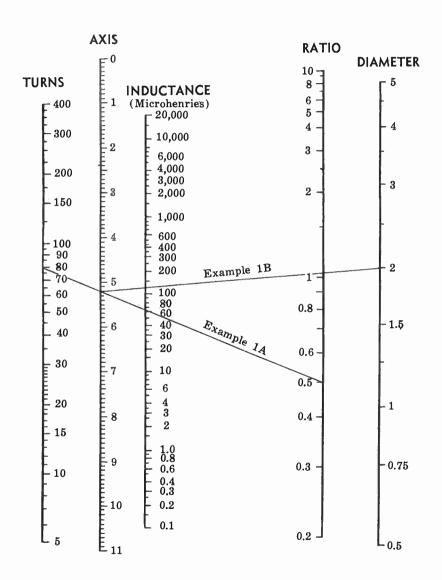


Fig. 84

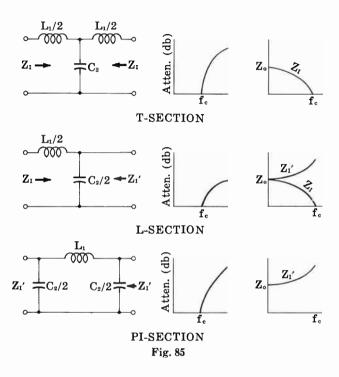
the characteristic impedance of the line (Z_o) at zero frequency only. For all other frequencies, the input and output impedance of the filter are equal to Z_I or $Z_{I'}$, as shown in Fig. 85.



The values for L_1 , C_2 , Z_0 , and f_c can be computed from the following formulas:

$$egin{aligned} \mathbf{L}_1 &= rac{\mathbf{Z}_o}{\pi \mathbf{f}_c} \ \mathbf{C}_2 &= rac{1}{\pi \mathbf{f}_c \mathbf{Z}_o} \ \mathbf{Z}_o &= \sqrt{rac{\mathbf{L}_1}{\mathbf{C}_2}} \ \mathbf{f}_c &= rac{1}{\pi \sqrt{\mathbf{L}_1 \mathbf{C}_2}} \end{aligned}$$

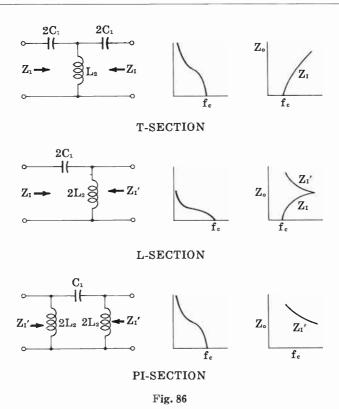The values computed for L_1 and C_2 must be divided in half, where specified in Fig. 85. That is, the coils in the T




and L sections, and the capacitors in the L and pi sections, are equal to one-half the computed value.


A high-pass filter will pass all frequencies above and attenuate all those below a set frequency.

The circuit configurations, attenuation characteristics, and impedance characteristics of constant-k high-pass filters are given in Fig. 86. The formulas for computing L_2 , C_1 , Z_0 , and f_c are as follows:

$$egin{aligned} \mathbf{L}_{2} &= rac{\mathbf{Z}_{\mathrm{o}}}{4\pi\mathbf{f}_{\mathrm{c}}} \ \mathbf{C}_{1} &= rac{1}{4\pi\mathbf{f}_{\mathrm{c}}\mathbf{Z}_{\mathrm{o}}} \ \mathbf{Z}_{\mathrm{o}} &= \sqrt{rac{\mathbf{L}_{2}}{\mathbf{C}_{1}}} \ \mathbf{f}_{\mathrm{c}} &= rac{1}{4\pi\sqrt{\mathbf{L}_{2}\mathbf{C}_{1}}} \end{aligned}$$

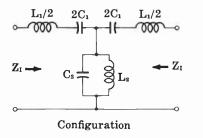Notice that the values computed for C in the foregoing formulas must be doubled in the T and L sections. Likewise, the value computed for L must be doubled in the L and pi sections.



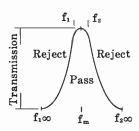

Transmission Characteristics


Fig. 87


Bandpass filters will pass frequencies of a certain band and reject all others. The configuration and the transmission characteristics for a constant-k bandpass filter are given in Fig. 87. The formulas for computing the various values are:

$$egin{aligned} \mathrm{L}_1 &= rac{\mathrm{Z}_{\mathrm{o}}}{\pi (\mathrm{f}_2 - \mathrm{f}_1)} \ \mathrm{L}_2 &= rac{(\mathrm{f}_2 - \mathrm{f}_1)}{4\pi \mathrm{f}_1 \mathrm{f}_2} \ \mathrm{C}_1 &= rac{(\mathrm{f}_2 - \mathrm{f}_1)}{4\pi \mathrm{f}_1 \mathrm{f}_2 \mathrm{Z}_{\mathrm{o}}} \ \mathrm{C}_2 &= rac{1}{\pi (\mathrm{f}_2 - \mathrm{f}_1)} \mathrm{Z}_{\mathrm{o}} \ \mathrm{f}_{\mathrm{m}} &= \sqrt{\mathrm{f}_1 \mathrm{f}_2} = rac{1}{2\pi \sqrt{\mathrm{L}_1 \mathrm{C}_1}} = rac{1}{2\pi \sqrt{\mathrm{L}_2 \mathrm{C}_2}} \ \mathrm{Z}_{\mathrm{o}} &= \sqrt{rac{\mathrm{L}_1}{\mathrm{C}_2}} &= \sqrt{rac{\mathrm{L}_2}{\mathrm{C}_1}} \end{aligned}$$

As before, some values must be doubled or halved, as shown in Fig. 87.

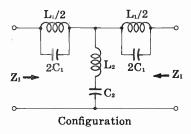A band-rejection filter will reject a certain band of frequencies and pass all others. The configuration and the transmission characteristics of a constant-k band-rejection filter



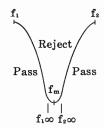

Transmission Characteristics

Fig. 88

are given in Fig. 88. The formulas for computing the component values, frequencies, and line impedance are:

$$\begin{split} L_1 &= \frac{(f_2 - f_1)}{\pi f_1 f_2} \\ L_2 &= \frac{Z_o}{4\pi (f_2 - f_1)} \\ C_1 &= \frac{1}{4\pi (f_2 - f_1)} Z_o \\ C_2 &= \frac{(f_2 - f_1)}{\pi f_1 f_2 Z_o} \\ f_m &= \sqrt{f_1 f_2} = \frac{1}{2\pi \sqrt{L_1 C_1}} = \frac{1}{2\pi \sqrt{L_2 C_2}} \\ Z_o &= \sqrt{\frac{L_1}{C_2}} = \sqrt{\frac{L_2}{C_1}} \end{split}$$

where,

 L_1 and L_2 are the inductances of the coils in henries,

C₁ and C₂ are the capacitances of the capacitors in farads, f₁ and f₂ are the frequencies at the edge of the passband, in cycles per second,


 $f_{\rm m}$ is the frequency at the center of the passband, in cycles per second,

 $f_1 \infty$ and $f_2 \infty$ are the frequencies of infinite attenuation, in cycles per second,

Z_o is the line impedance in ohms.

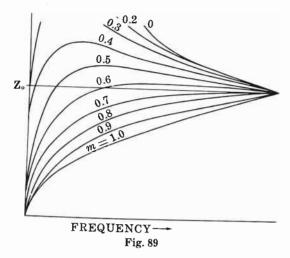(B) M-Derived Filters

In an m-derived filter, the designer can control either the impedance or the attenuation characteristics. The values are first computed as for a constant-k filter and then modified by an algebraic expression containing the constant m. The



term m will be a positive number between zero and one, and its value governs the characteristics of the filter.

Two frequencies—the cutoff and the frequency of infinite attenuation—are involved in the design of m-derived filters. By selecting the proper value for m, it is possible to control the spacing between the two frequencies. Fig. 89 shows the effect which different values of m have on the impedance

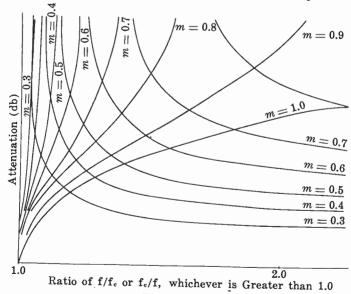


Fig. 90

characteristics. Note that the best impedance match is obtained when m is equal to 0.6; hence this value is usually employed.

The attenuation characteristics for the various values of m are given in Fig. 90. The attenuation rises to maximum and then drops on all curves. This graph applies to both lowand high-pass filters.

The value of m is determined from the formulas:

$$m = \sqrt{1 - \left(\frac{\mathbf{f}_c}{\mathbf{f}_{\infty}}\right)^2}$$

or,

$$m = \sqrt{1 - \left(\frac{f_{\infty}}{f_{o}}\right)^{2}}$$

Select the formula which will give a positive number.

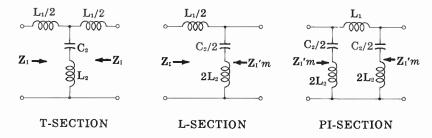


Fig. 91

The configurations for m-derived filters are classified as either series or shunt. Those for the series m-derived low-pass filters are given in Fig. 91. The formulas are as follows:

$$egin{aligned} \mathbf{L}_1 &= m \; \left(rac{\mathbf{Z}_o}{2\pi\mathbf{f}_c}
ight) \ \mathbf{L}_2 &= \left(rac{1-m^2}{4m}
ight) \left(rac{\mathbf{Z}_o}{2\pi\mathbf{f}_c}
ight) \ \mathbf{C}_2 &= m \; \left(rac{1}{\pi\mathbf{f}_c}\mathbf{Z}_o
ight) \end{aligned}$$

For a series m-derived high-pass filter (Fig. 92), the formulas are:

$${
m L}_2 = rac{\left(rac{{
m Z}_{
m o}}{4\pi{
m f}_{
m c}}
ight)}{m}$$

$$\begin{aligned} \mathrm{C}_1 &= \frac{\left(\frac{1}{4\pi\mathrm{f_c}\mathrm{Z_o}}\right)}{m} \\ \mathrm{C}_2 &= \left(\frac{4m}{1-m^2}\right) \left(\frac{1}{4\pi\mathrm{f_c}\mathrm{Z_o}}\right) \end{aligned}$$

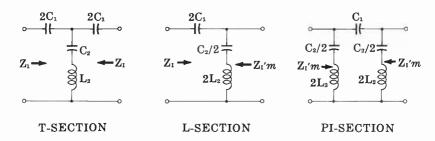


Fig. 92

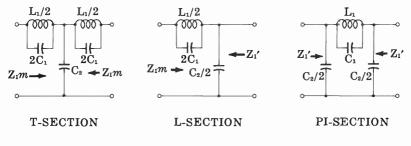


Fig. 93

The configurations for shunt m-derived low-pass filters are given in Fig. 93. The formulas for computing the component values are:

$$egin{aligned} \mathbf{L_1} &= m \left(rac{\mathbf{Z_o}}{\pi \mathbf{f_c}}
ight) \ \mathbf{C_1} &= \left(rac{1-m^2}{4m}
ight) \left(rac{1}{\pi \mathbf{f_c} \mathbf{Z_o}}
ight) \ \mathbf{C_2} &= m \left(rac{1}{\pi \mathbf{f_c} \mathbf{Z_o}}
ight) \end{aligned}$$

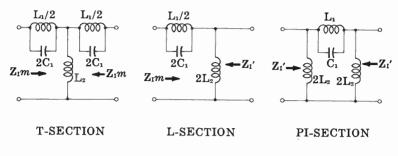


Fig. 94

For shunt m-derived high-pass filters (Fig. 94), the formulas are:

$$egin{align} \mathbf{L}_1 &= \left(rac{4m}{1-m^2}
ight) \, \left(rac{\mathbf{Z}_{
m o}}{4\pi\mathbf{f}_{
m c}}
ight) \ \mathbf{L}_2 &= rac{\left(rac{\mathbf{Z}_{
m o}}{4\pi\mathbf{f}_{
m c}}
ight)}{m} \ \mathbf{C}_1 &= rac{\left(rac{1}{4\pi\mathbf{f}_{
m c}}\mathbf{Z}_{
m o}
ight)}{m} \end{array}$$

where,

 L_1 and L_2 are the inductances of the coils in henries, C_1 and C_2 are the capacitances of the capacitors in farads, m is a constant between 0 and 1, Z_0 is the line impedance in ohms, f_c is the cutoff frequency in cycles per second.


66. ATTENUATOR FORMULAS

(A) General

An attenuator is an arrangement of noninductive resistors used in an electrical circuit to reduce the audio- or radiosignal strength without introducing distortion. The resistors may be fixed or variable. Attenuators can be designed to work between equal or unequal impedances; hence, they are often used as impedance-matching networks.

Any attenuator working between unequal impedances must introduce a certain minimum loss. These values are given in the graph of Fig. 95. The impedance ratio is the input impedance divided by the output impedance, or vice versa—whichever gives a value of more than one.

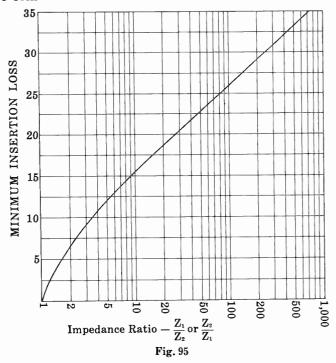A factor is used in the calculation of resistor values in attenuator networks. Called K, it is the ratio of current, voltage, or power corresponding to a given value of attenuation in decibels. Table XXV gives the value of "K" for the more common loss values.




The four steps in the design of a pad are: (1) Determine the type of network required. (2) If impedances are unequal, calculate the ratio of input to output impedance (or output to input impedance) and refer to Fig. 95 for the minimum loss value. (3) From Table XXV find the value of K for the desired loss. (4) Calculate the resistor values, using the following formulas.

db	К	db	К	db	К	db	К
.05	1.0058	9.5	2.9854	29.0	28.184	49.0	281.84
1 .1	1.0116	10.0	3.1623	30.0	31.623	50.0	316.23
.5	1.0593	11.0	3.5481	31.0	35.481	51.0	354.81
1.0	1.1220	12.0	3.9811	32.0	39.811	52.0	398.11
1.5	1.1885	13.0	4.4668	33.0	44.668	54.0	501.19
2.0	1.2589	14.0	5.0119	34.0	50.119	55.0	562.34
2.5	1,3335	15.0	5.6234	35.0	56.234	56.0	630.96
3.0	1.4125	16.0	6.3096	36.0	63.096	57.0	707.95
3.5	1.4962	17.0	7.0795	37.0	70.795	58.0	794.33
4.0	1.5849	18.0	7.9433	38.0	79.433	60.0	1000.0
4.5	1.6788	19.0	8.9125	39.0	89.125	65.0	1778.3
5.0	1.7783	20.0	10.0000	40.0	100.000	70.0	3162.3
5.5	1.8837	21.0	11.2202	41.0	112.202	75.0	5623.4
6.0	1.9953	22.0	12.589	42.0	125.89	80.0	10,000
6.5	2.1135	23.0	14.125	43.0	141.25	85.0	17,783
7.0	2.2387	24.0	15.849	44.0	158.49	90.0	31,623
7.5	2.3714	25.0	17.783	45.0	177.83	95.0	56,234
8.0	2.5119	26.0	19.953	46.0	199.53	100.0	10 ⁶
8.5	2.6607	27.0	22.387	47.0	223.87		
9.0	2.8184	28.0	25.119	48.0	251.19		

Table XXV. K Factors for Calculating Attenuator Loss

(B) Combining or Dividing Network

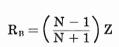

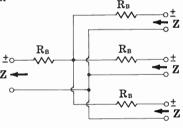



Fig. 96

where,

 $R_{\rm B}$ is the resistance of the building-out resistors in ohms, N is the number of circuits fed by the source impedance, Z is the source impedance in ohms.

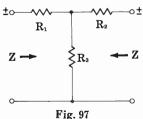
(C) T-Type Attenuator (Between Equal Impedances)

$$R_1$$
 and $R_2=\left(\frac{K-1}{K+1}\right)Z$
$$R_3=\left(\frac{K}{K^2-1}\right)2Z$$



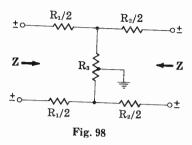(D) H-Type Attenuator (Balanced-T Attenuator)

Calculate the values for R_1 , R_2 , and R_3 as for an unbalanced T-attenuator (Fig. 97). Then halve the values of R_1 and R_2 , as shown in Fig. 98. The tap on R_3 is exactly in the center.



(E) Taper Pad (T-Type Attenuator Between Unequal Impedances)

$$R_1 = Z_1 \left(\frac{K^2 + 1}{K^2 - 1}\right) - 2\sqrt{Z_1 Z_2} \left(\frac{K}{K^2 - 1}\right) \xrightarrow{\text{± 0}} R_1 \xrightarrow{\text{R_2}} e^{\pm \frac{1}{K^2 - 1}}$$


$$R_2 = Z_2 \left(\frac{K^2 + 1}{K^2 - 1}\right) - 2\sqrt{Z_1 Z_2} \left(\frac{K}{K^2 - 1}\right) \xrightarrow{\text{Z_1}} R_2 \xrightarrow{\text{Z_2}} R_3 = 2\sqrt{Z_1 Z_2} \left(\frac{K}{K^2 - 1}\right)$$

$$Fig. 99$$

where,

 \mathbf{Z}_1 is the larger impedance.


(F) Bridged-T Attenuator (Unbalanced)

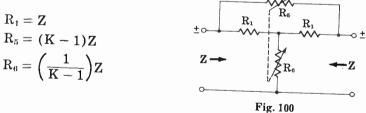

 ${
m R}_5$ and ${
m R}_6$ are connected to a common shaft, and each varies inversely in value with respect to the other.

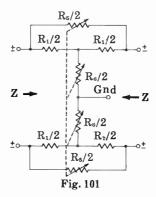(G) Balanced Bridged-T Attenuator

Calculate the values for R_1 , R_5 , and R_6 as for an unbalanced bridged-T attenuator (Fig. 100). Then halve the values as shown in Fig. 101.



(H) L-Type Attenuators

An L-type attenuator can supply an impedance match in only one direction. If the impedances it works out of and into are unequal, it can be made to match either—but not both—impedances. The arrows in the following illustrations indicate the direction of impedance match.

Between equal impedances and with the impedance match in the direction of the series arm:

$$R_{1} = Z\left(\frac{K-1}{K}\right)$$

$$R_{2} = Z\left(\frac{1}{K-1}\right)$$

$$\stackrel{\pm \circ \qquad R_{1}}{\longleftarrow}$$

$$Z \longrightarrow \qquad R_{2} \nearrow \qquad Z$$

$$\stackrel{\bullet}{\longrightarrow}$$
Fig. 102

Between equal impedances and with the impedance match in the direction of the shunt arm:

$$R_{1} = Z (K-1)$$

$$R_{2} = Z \left(\frac{K}{K-1}\right)$$

$$z$$

$$Fig. 103$$

Between unequal impedances and with the impedance match toward the larger value:

$$R_{1} = \left(\frac{Z_{1}}{S}\right) \left(\frac{KS - 1}{K}\right)$$

$$R_{2} = \left(\frac{Z_{1}}{S}\right) \left(\frac{1}{K - S}\right)$$

$$Z_{1} \longrightarrow R_{2}$$

$$Z_{2}$$

$$Z_{3} \longrightarrow R_{2}$$

$$Z_{4} \longrightarrow R_{2}$$

$$Z_{5} \longrightarrow R_{2}$$

$$Z_{7} \longrightarrow R_{2}$$

$$Z_{8} \longrightarrow R_{2}$$

$$Z_{1} \longrightarrow R_{2}$$

$$Z_{2} \longrightarrow R_{3}$$

$$Z_{4} \longrightarrow R_{4}$$

$$Z_{5} \longrightarrow R_{5}$$

$$Z_{7} \longrightarrow R_{2}$$

$$Z_{8} \longrightarrow R_{1}$$

$$Z_{1} \longrightarrow R_{2}$$

$$Z_{2} \longrightarrow R_{3}$$

$$Z_{4} \longrightarrow R_{4}$$

$$Z_{5} \longrightarrow R_{5}$$

$$Z_{7} \longrightarrow R_{7}$$

$$Z_{8} \longrightarrow R_{7}$$

Between unequal impedances and with the impedance match toward the smaller value:

$$R_{1} = \left(\frac{Z_{1}}{S}\right) (K - S)$$

$$R_{2} = \left(\frac{Z_{1}}{S}\right) \left(\frac{K}{KS - 1}\right)$$
where,
$$S \text{ equals } \sqrt{\frac{Z_{1}}{Z_{2}}}$$

$$\sum_{i} R_{2} + \sum_{i} R_{2}$$
Fig. 105

(I) Pi-Type Attenuator (Between Equal Impedances)

$$R_{1} = Z\left(\frac{K+1}{K-1}\right)$$

$$L_{2} = \left(\frac{Z}{2}\right)\left(\frac{K^{2}-1}{K}\right)$$

$$Z \longrightarrow R_{1}$$

$$R_{2} = \left(\frac{Z}{2}\right)\left(\frac{K^{2}-1}{K}\right)$$

$$Z \longrightarrow R_{1}$$

$$R_{2} = \left(\frac{Z}{2}\right)\left(\frac{K^{2}-1}{K}\right)$$

(J) Pi-Type Attenuator (Between Unequal Impedances)

$$R_1 = Z_1 \left(\frac{K^2 - 1}{K^2 - 2KS + 1} \right)$$

$$R_2 = \left(\frac{\sqrt{Z_1 Z_2}}{2} \right) \left(\frac{K^2 - 1}{K} \right)$$


$$R_3 = Z_2 \left(\frac{K^2 - 1}{K_2 - 2\frac{K}{S} + 1} \right)$$

$$Z_1 \longrightarrow \{R_1, R_3\} \longrightarrow Z_2$$
where,

S equals $\sqrt{\frac{Z_1}{Z_2}}$

(K) O-Type Attenuators

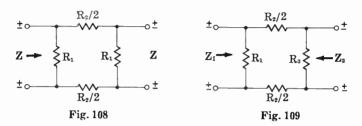Calculate the values for a pi-type attenuator (Figs. 106 and 107), then halve the values for the series resistors as shown in Figs. 108 (balanced) and 109 (unbalanced).



(L) U-Type Attenuator

For impedance match in the direction of the series arms:

$$R_{1} = \left(\frac{Z_{1}}{2S}\right) \left(\frac{KS - 1}{K}\right)$$

$$Z_{1} \longrightarrow \begin{bmatrix} X_{1} & X_{2} & X_{1} & X_{2} & X_{2} & X_{3} & X_{4} & X_{4}$$

For impedance match in the direction of the shunt arm:

where,

The arrows indicate the direction of the impedance match,

S equals
$$\sqrt{\frac{\overline{Z_1}}{\overline{Z_2}}}$$

(M) Lattice-Type Attenuator

$$R_1 = \left(\frac{K-1}{K+1}\right) Z$$

$$R_2 = \left(\frac{K+1}{K-1}\right) Z$$

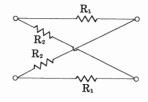


Fig. 112

(N) Ladder-Type Attenuator

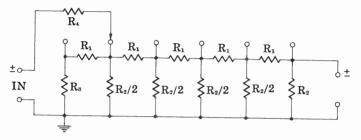


Fig. 113

$$\begin{aligned} R_1 &= \left(\frac{K^2 - 1}{2K}\right) Z \\ R_2 &= \left(\frac{K + 1}{K - 1}\right) Z \\ R_3 &= \frac{R_2 \times Z}{R_2 + Z} \\ R_4 &= \frac{Z}{2} \\ Z_{in} &= Z_{out} \end{aligned}$$

where,

K depends on the loss per step-not on the total loss.

Mathematical Tables and Formulas

67. MATHEMATICAL CONSTANTS

O/. 141/4111=11111	
$_{\pi}=3.1416$	$(2\pi)^2 = 39.4786$
$\pi^2 = 9.8696$	$4\pi=12.5664$
$\pi^3 = 31.0063$	$\frac{\pi}{2} = 1.5708$
$\frac{1}{\pi} = 0.3183$	$\frac{\sqrt{\pi}}{2} = 1.2533$
$\frac{1}{\pi^2} = 0.1013$	$\sqrt{2} = 1.4142$
$\frac{1}{\pi^3} = 0.0323$	$\sqrt{3} = 1.7321$
$\sqrt[n]{\pi} = 1.7725$	$\frac{1}{\sqrt{2}} = 0.7071$
$\frac{1}{\sqrt{ au}} = 0.5642$	$\frac{1}{\sqrt{3}} = 0.5773$
$\frac{1}{2\pi} = 0.1592$	$\log \pi = 0.4971$
<i>21</i> 1	$\log \pi^2 = 0.9943$
$\left(\frac{1}{2\pi}\right)^2 = 0.0253$	$\log\sqrt{\pi} = 0.2486$
$2_{\pi}=6.2832$	$\log\frac{\pi}{2} = 0.1961$

68. MATHEMATICAL SYMBOLS

× or · Multiplied by.
÷ Divided by.
= Equals.
† Does not equal.
+ Positive, add, and plus.
- Negative, subtract, and minus.
> Is greater than.

- < Is less than.
- ± Plus or minus.
- **■** Identical with.
- ... Therefore.
 - || Parallel to.
- ∠ Angle.
- ✓ Is much less than.
- > Is much greater than.

- ≥ Equal to or greater than.
- \leq Equal to or less than.
- 1 Perpendicular to.
- |n| Absolute value of n.
- Is approximately equal to.
- $\sqrt{}$ Square root.

69. DECIMAL EQUIVALENTS OF FRACTIONS

The decimal equivalents to four places of fractions by 64ths are given in Table XXVI.

Table XXVI. Decimal Equivalents of Fractions

	Fraction			Decimal		Fractio	n	_	Decimal
3/64	1/32			0.0156 0.0313 0.0469	33/64 35/64	17/32			0.5156 0.5313 0.5469
5/64 7/64	3/32	1/16	1/8	0.0625 0.0781 0.0938 0.1094 0.1250	37/64 39/64	19/32	9/16	5/8	0.5625 0.5781 0.5938 0.6094 0.6250
9/64	5/32	3/16		0.1406 0.1563 0.1719 0.1875 0.2031	41/64 43/64 45/64	21/32	11/16		0.6406 0.6563 0.6719 0.6875
15/64	7/32		1/4	0.2188 0.2344 0.2500 0.2656	47/64	23/32		3/4	0.7031 0.7188 0.7344 0.7500
19/64	9/32	5/16		0.2813 0.2969 0.3125 0.3281	51/64	25/32	13/16		0.7656 0.7813 0.7969 0.8125 0.8281
23/64	11/32		3/8	0.3438 0.3594 0.3750 0.3906	55/64	27/32		7/8	0.8438 0.8594 0.8750
27/64	13/32	7/16		0.4906 0.4063 0.4219 0.4375 0.4531	57/64 59/64 61/64	29/32	15/16		0.8906 0.9063 0.9219 0.9375
31/64	15/32		1/2	0.4688 0.4844 0.5000	63/64	31/32		1	0.9531 0.9688 0.9844 1.0000

70. POWERS OF TEN

(A) Exponent Determination

Large numbers can be simplified by using powers of ten. For example, some of the multiples of ten from 1 to 1,000,000, with their equivalents in powers of ten are:

$$1 = 10^{0*}$$

$$10 = 10^{1}$$

$$100 = 10^{2}$$

$$1000 = 10^{3}$$

$$10,000 = 10^{4}$$

$$100,000 = 10^{5}$$

$$1,000,000 = 10^{6}$$

Likewise, powers of ten can be used to simplify decimal expressions. Some of the submultiples of ten from 0.1 to 0.000001, with their equivalents in powers of ten are:

$$0.1 = 10^{-1}$$

$$0.01 = 10^{-2}$$

$$0.001 = 10^{-3}$$

$$0.0001 = 10^{-4}$$

$$0.00001 = 10^{-5}$$

$$0.000001 = 10^{-6}$$

Any whole number can be expressed as a smaller whole number, and any decimal can be expressed as a whole number, by moving the decimal point to the left or right and expressing the number as a power of ten. If the decimal point is moved to the left, the power is positive and is equal to the number of places the decimal point was moved. If the decimal point is moved to the right, the power is negative and is equal to the number of places the decimal point was moved.

For example:

$$123 = 1.23 \times 10^{2}$$
 $456.7 = 4.567 \times 10^{2}$
 $78,900 = 78.9 \times 10^{3}$
 $0.00012 = 1.2 \times 10^{-4}$
 $0.0345 = 34.5 \times 10^{-3}$
 $.678 = 67.8 \times 10^{-2}$

^{*} Any number to the zero power is 1.

(B) Addition and Subtraction

To add or subtract using powers of ten, first convert all numbers to the same power of ten. The numbers can then be added or subtracted, and the answer will be in the same power of ten. For example:

$$\begin{array}{c} 9.32\times 10^2+17.63 & \times 10^3+297=?\\ 9.32\times 10^2=0.932 & \times 10^3\\ 17.63\times 10^3=17.630\times 10^3\\ &297=\underbrace{0.297\times 10^3}_{18.859\times 10^3}=18,859\\ 18.47\times 10^2-1.59 & \times 10^3=?\\ 18.47\times 10^2=1.847\times 10^3\\ 1.59\times 10^3=\underbrace{1.590\times 10^3}_{.257\times 10^3}=257 \end{array}$$

(C) Multiplication

To multiply using powers of ten, add the exponents. Thus:

$$1000 \times 3721 = 10^{3} \times 37.21 \times 10^{2}$$

$$= 37.21 \times 10^{3+2}$$

$$= 37.21 \times 10^{5}$$

$$= 3,721,000$$

$$225 \times .00723 = 2.25 \times 10^{2} \times 7.23 \times 10^{-3}$$

$$= 2.25 \times 7.23 \times 10^{2+(-3)}$$

$$= 2.25 \times 7.23 \times 10^{-1}$$

$$= 16.2675 \times 10^{-1}$$

$$= 1.62675$$

(D) Division

To divide using powers of ten, subtract the exponent of the denominator from the exponent of the numerator. Thus:

$$\frac{10^5}{10^3} = 10^{5-3}$$
$$= 10^2$$
$$= 100$$

$$\begin{aligned} \frac{72,600}{.002} &= \frac{72.6 \times 10^3}{2 \times 10^{-3}} \\ &= \frac{72.6 \times 10^{3+3}}{2} \\ &= 36.3 \times 10^6 \\ &= 36,300,000. \end{aligned}$$

(E) Combination Multiplication and Division

Problems involving a combination of multiplication and division can be solved using powers of ten by multiplying and dividing, as called for, until the problem is completed. For example:

$$\frac{3900 \times .007 \times 420}{142,000 \times .00005} = \frac{3.9 \times 10^3 \times 7 \times 10^{-3} \times 4.2 \times 10^2}{1.42 \times 10^5 \times 5 \times 10^{-5}}$$

$$= \frac{3.9 \times 7 \times 4.2 \times 10^2}{1.42 \times 5}$$

$$= \frac{114.66 \times 10^2}{7.1}$$

$$= 16.1493 \times 10^2$$

$$= 1614.93$$

(F) Reciprocal

To take the reciprocal of a number using powers of ten, first (if necessary) state the number so the decimal point precedes the first significant figure of the number. Then divide this number into 1. The power of 10 in the answer will be the same value as in the original number, but will have the opposite sign. For example:

Reciprocal of
$$400 = \frac{1}{400}$$

$$\frac{1}{400} = \frac{1}{.4 \times 10^{3}}$$

$$= 2.5 \times 10^{-3}$$

$$= .0025$$
Reciprocal of $.0025 = \frac{1}{.0025}$

$$\frac{1}{.0025} = \frac{1}{.25 \times 10^{-2}}$$

$$= 4 \times 10^{2}$$

$$= 400$$

(G) Square and Square Root

To square a number using powers of ten, multiply the number by itself, and double the exponent. Thus:

$$(7 \times 10^{3})^{2} = 49 \times 10^{6}$$

= 49,000,000
 $(9.2 \times 10^{-4})^{2} = 84.64 \times 10^{-8}$
= .0000008464

To extract the square root of a number using powers of ten, do the opposite. (If the number is an odd power of 10, first convert it to an even power of ten.) Extract the square root of the number, and divide the power of ten by 2. Thus:

$$\sqrt{36 \times 10^{10}} = 6 \times 10^{5}
= 600,000
\sqrt{5.72 \times 10^{3}} = \sqrt{57.2 \times 10^{2}}
= 7.56 \times 10
= 75.6$$

71. OPERATION OF THE SLIDE RULE

The slide rule (Fig. 114) is an instrument designed to perform mathematical calculations with a high degree of accuracy. For example, the common 10-inch slide rule has an accuracy of one-tenth of one per cent. Operations such as multiplication, division, extraction of square and cube roots, and finding trigonometric functions such as sine, cosine, and tangent can all be performed on the slide rule.

There are six scales on the front of the slide rule. The letter A, in the upper left-hand corner of the body, denotes the A scale. On the left side of the slide, the letters B, CI, and C denote their respective scales. The letters D and K, at the lower left corner of the body, indicate these scales.

	Α	CHARLES BRILING CO MADE W USA	
2403	B	1 2 3 4 5 6 7 8 9 1 2 3 4 5 6 7 8 9 1 2 3 4 5 6 7 8 9 1	2
%	С		WADE
	D K	1 2 3 4 5 6 7 8 9 2 3 3 4 5 6 7 8 9 2 3 3 4 5 6 7 8 9 3 3 3 4 5 6 7 8 9 3 3 3 4 5 6 7 8 9 3 3 3 3 4 5 6 7 8 9 3 3 3 3 3 3 3 3 3 3 3 3 3 3 3 3 3 3	-

Fig. 114

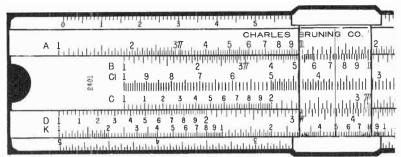


Fig. 115

The number 1 on the left end of the slide is called the left index, and the number 1 on the right end is the right index.

The C and D scales, which are identical, are used for multiplication and division. As a sample problem in multiplication, let us multiply 136 by 27. First place the left index of the slide on 136 on the D scale. Then slide the runner to 27 on the C scale, and read your answer (3672) on the D scale, as shown in Fig. 115.

Notice that the slide rule is accurate to three places, as illustrated by the sample problem. The fourth number can be estimated close enough for practical purposes.

As a sample problem in division, let us divide 390 by 0.7. Place the runner on 390 on the D scale; then push the slide to the left until 7 on the C scale is over the 390, as shown in Fig. 116. Finally, place the runner at the right index, and read the answer (557) on the D scale.

The CI, or reciprocal, scale is the same as the C scale except its numbers increase from right to left. Hence, any number on the CI scale is the reciprocal of the number directly below it on the C scale. The CI scale can be used with


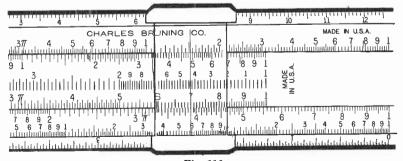


Fig. 116

the C and D scales for multiplication and division, including problems involving several multiplication and division operations in sequence.

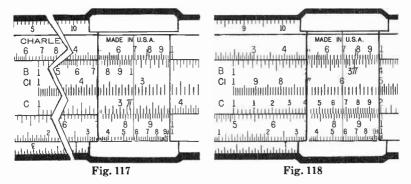As a sample problem in multiplication, take $26 \times 32 \times 6$. Place the left index of the slide on 26 of the D scale. Then slide the runner to 32 on the C scale, as shown in Fig. 117. Multiplying by 6 is the same as dividing by the reciprocal of 6. To do this, place the 6 on the CI scale under the hairline of the runner (Fig. 118), and read the answer (4992) under the left index.



The A and B scales, which are identical, are located on the upper portion of the body and slide. The A and/or B scales are used with the C and/or D scales for finding the square or square root of a number.

Example problem: Find the square root of 625. First place the runner at 625 on the A scale. Then read the answer (25) on the D scale (Fig. 119).

The slide rule can be used for finding the square root of the sum of two squares, as you might wish to do if you were

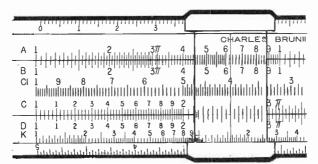


Fig. 119

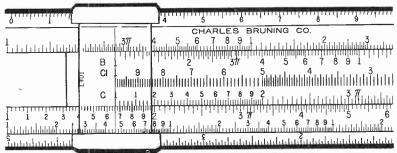


Fig. 120

solving a right triangle. For example, if the two sides of a right triangle are 3 and 5, find the hypotenuse in the following manner:

Divide the 5 by the 3, by placing 3 on the C scale opposite 5 on the D scale. Square the quotient by reading 2.78 on the A scale opposite the left index of the B scale (Fig. 120). Mentally add 1 to get 3.78, and set the left index of the B scale to 3.78 on the A scale. Extract the square root by going to the D scale and reading 1.945 opposite the C index mark. Without changing the slide, multiply by 3 (the number by which you originally divided) to obtain the answer (5.83) on the D scale (Fig. 121).

The K scale is used with the D scale for finding the cube and cube root. Each number on the K scale is equal to the cube of the number above it on the D scale. Conversely, to extract the cube root of a number, set the runner to this number on the K scale, and read the cube root on the D scale.

The back of the slide is shown in Fig. 122. On it are the sine, log, and tangent scales. The sine scale is at the top and is designated by the letter S on the right side of the

մասևավասիամասիա <u>ն</u> ուրանուրանուրանուր	Monthe
CHARLES BRUNING CO.	MADE IN U.S
	3 4 5 6 7
C1 1 2 3 4 5 6 7 8 9 2	
3 4 5 6 7 8 9 1 1001001 111111111111111111111111111	
	<u> </u>

Fig. 121

slide. The log scale, designated by the letter L, is in the middle; and the tangent scale, designated by the letter T, is at the bottom.

The "inch" and "centimeter" scales on the rule are only a convenience—they are not used in any slide-rule operations.

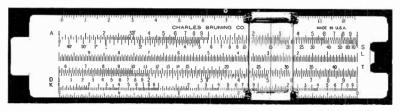


Fig. 122

72. ALGEBRAIC OPERATIONS

(A) Transposition of Terms

The following rules apply to the transposition of terms in algebraic equations:

If
$$A = \frac{B}{C}$$
, then:
 $B = AC$
 $C = \frac{B}{A}$
If $\frac{A}{B} = \frac{C}{D}$, then:
 $A = \frac{BC}{D}$
 $C = \frac{AD}{C}$
 $C = \frac{AD}{A}$

$$\begin{split} \text{If A} &= \frac{1}{D\sqrt{BC}} \text{, then:} \\ &A^2 = \frac{1}{D^2 \, BC} \\ &B = \frac{1}{D^2 \, A^2 \, C} \\ &C = \frac{1}{D^2 \, A^2 \, B} \\ &D = \frac{1}{A\sqrt{BC}} \end{split}$$

$$\text{If A} &= \sqrt{B^2 + C^2} \text{, then:} \\ &A^2 = B^2 + C^2 \\ &B = \sqrt{A^2 - C^2} \\ &C = \sqrt{A^2 - B^2} \end{split}$$

(B) Laws of Exponents

A power of a fraction is equal to that power of the numerator divided by the same power of the denominator.

$$\left(\frac{\mathbf{a}}{\mathbf{b}}\right)^{\mathbf{x}} = \frac{\mathbf{a}^{\mathbf{x}}}{\mathbf{b}^{\mathbf{x}}}$$

The product of two powers of the same base is also a power of that base; the exponent of the product is equal to the sum of the exponents of the two factors.

$$\mathbf{a}^{\mathbf{x}} \cdot \mathbf{a}^{\mathbf{y}} = \mathbf{a}^{\mathbf{x} + \mathbf{y}}$$

The quotient of two powers of the same base is also a power of that base; the exponent of the quotient is equal to the numerator exponent minus the denominator exponent.

$$\frac{\mathbf{a}^{\mathbf{x}}}{\mathbf{a}^{\mathbf{z}}} = \mathbf{a}^{\mathbf{x}-\mathbf{z}}$$

The power of a power of a base is also a power of that base; the exponent of the product is equal to the product of the exponents.

$$(\mathbf{a}^{\mathbf{x}})^{\mathbf{y}} = \mathbf{a}^{\mathbf{x}\mathbf{y}}$$

A negative exponent of a base is equal to the reciprocal of that base, with a positive exponent numerically equal to the original exponent.

$$\mathbf{a}^{-\mathbf{x}} = \frac{1}{\mathbf{a}^{\mathbf{x}}}$$

A fractional exponent indicates that the base should be raised to the power indicated by the numerator of the fraction; the root indicated by the denominator should then be extracted.

$$a^{\frac{x}{y}} = \sqrt[y]{a^x}$$

A root of a fraction is equal to the identical root of the numerator divided by the identical root of the denominator.

$$\sqrt[x]{\frac{a}{b}} = \frac{\sqrt[x]{a}}{\sqrt{b}}$$

A root of a product is equal to the product of the roots of the individual factors.

$$\sqrt[x]{ab} = \sqrt[x]{a} \times \sqrt[x]{b}$$

(C) Quadratic Equation

The general quadratic equation:

$$ax^2 + bx + c = 0$$

may be solved by:

$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

73. GEOMETRIC FORMULAS

(A) Triangle

area (A) =
$$\frac{bh}{2}$$



(B) Square

area
$$(A) = b^2$$



Fig. 124

(C) Rectangle

$$area(A) = ab$$



Fig. 125

(D) Parallelogram

$$area(A) = ah$$

(E) Trapezoid

area (A) =
$$\frac{h}{2}$$
(a + b)

(F) Trapezium

area (A) =
$$\frac{1}{2}$$
 [b(H+h)
+ ah + cH]

(G) Regular Pentagon

area (A) =
$$1.720 a^2$$

(H) Regular Hexagon

area (A) =
$$2.598 a^2$$

(I) Regular Octagon

area (A) =
$$4.828 a^2$$

(J) Circle

circumference (C) =
$$2\pi R$$

= πD
area (A) = πR^2



Fig. 126



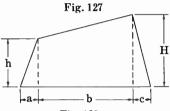


Fig. 128



Fig. 129



Fig. 130



Fig. 131



Fig. 132

(K) Segment

chord (c) =
$$\sqrt{4(2hR-h^2)}$$
 area (A) = $\pi R^2 \left(\frac{\theta}{360}\right) - \left(\frac{c(R-h)}{2}\right)$



Fig. 133

(L) Sector

area (A) =
$$\frac{bR}{2}$$

= $\pi R^2 \left(\frac{\theta}{360}\right)$



Fig. 134

(M) Circular Ring

area (A) =
$$\pi(R^2-r^2)$$

= 7854 (D²-d²)

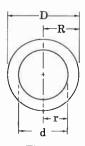


Fig. 135

(N) Ellipse

circumference (C) =
$$\pi$$
(a+b)
$$\frac{64-3\left(\frac{b-a}{b+a}\right)^4}{64-16\left(\frac{b-a}{b+a}\right)^2}$$

area (A) =
$$\pi ab$$

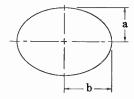


Fig. 136

(O) Sphere

area (A) =
$$4\pi R^2$$

= πD^2
volume (V) = $\frac{4}{3}\pi R^3$
= $1/6\pi D^3$

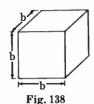


Fig. 137

(P) Cube

area (A) =
$$6b^2$$


volume (V) = b^3



(Q) Rectangular Solid

area
$$(A) = 2 (ab + bc + ac)$$

volume $(V) = abc$

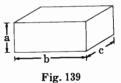

(R) Cone

area (A) =
$$\pi RS$$

= $\pi R \sqrt{R^2 + h^2}$
volume (V) = $\frac{\pi R^2 h}{3}$
= 1.047R²h
= 0.2618D²h

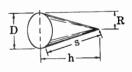


Fig. 140

(S) Cylinder

cylindrical surface =
$$\pi Dh$$

total surface = $2\pi R (R+h)$
volume (V) = $\pi R^2 h$
= $\frac{c^2 h}{4\pi}$

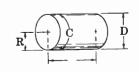


Fig. 141

(T) Ring of Rectangular Cross Section

volume (V) =
$$\frac{\pi c}{4}$$
 (D²-d²)
$$= \left(\frac{D+d}{2}\right)_{\pi}bc$$

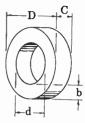


Fig. 142

(U) Torus (Ring of Circular Cross Section)

$$egin{aligned} ext{total surface} &= 4\pi^2 R r \ &= \pi^2 D d \end{aligned} \ ext{volume (V)} &= 2\pi^2 R imes r^2 \ &= 2.463 D imes d^2 \end{aligned}$$

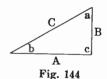


Fig. 143

74. TRIGONOMETRIC FUNCTIONS

(A) Plane Trigonometry

In any right triangle, the values in Table XXVII are valid if we let:



- a equal the acute angle formed by the hypotenuse and the altitude leg,
- b equal the acute angle formed by the hypotenuse and the base leg,

A equal the side adjacent to $\angle b$ and opposite $\angle a$,

B equal the side opposite \angle b and adjacent to \angle a,

C equal the hypotenuse.

Known		Formulas f	or Unknown	Values of	
Values	A	В	С	∠b	∠a
A & B			$\sqrt{A^3 + B^2}$	arc tan BA	arc tan AB
A & C		$\sqrt{C^2-A^2}$		arc cos A/C	arc sin A/C
A & ∠b		A tan ∠b	A cos ∠b		9 0° — ∠b
A & ∠a		A tan ∠a	A sin ∠a	90° — ∠a	
B & C	$\sqrt{C^2 - B^2}$			arc sin B	$arc cos \frac{B}{C}$
B & ∠b	B B tan ∠b		B sin ∠b		90° — ∠b
B & ∠a	B tan ∠a		B cos ∠a	90° — ∠a	
C&∠b	C cos ∠b	C sin ∠b			90° — ∠b
C & ∠a	C sin ∠a	C cos ∠a		90° — ∠a	

Table XXVII. Trigonometric Formulas

The expression "arc sin" or "sin'" indicates an angle whose sine is. . . . Similarly, "arc tan" or "tan'" indicates the angle whose tangent is . . . , etc.

(B) Table of Trigonometric Functions

Table XXVIII gives the natural sines, cosines, tangents, and cotangents of angles. To find these values for angles from 0° to 45°, use the headings at the top of the table and the degree listings in the left-hand column. For angles from 45° to 90°, use the headings at the bottom of the table and the degree listings in the right-hand column. Note: Read the degree listings in the right-hand column from bottom to top; thus, the 10′ listing directly above 89° signifies 89° 10′.

Table XXVIII. Natural Trigonometric Functions

Degrees	Sin	Cos	Tan	Cot	
0° 00′	0.0000	1,0000	0.0000	00	90° 00'
0° 00′ 0.0000 10 .0029 20 .0058 30 .0087 40 .0116 50 .0145 1° 00′ 0.0175 10 .0204 20 .0233 30 .0262 40 .0291 50 .0320 2° 00′ .0.0349 10 .0378 20 .0407 30 .0436 40 .0445 50 .0494 3° 00′ 0.0523 10 .0552 20 .0581 30 .0610 40 .0640 50 .0669 4° 00′ 0.0698 10 .0727 20 .0756 30 .0785 40 .0814 50 .0929 30 .09581 40 .0929 30				50	
0° 00′ 0.0000 1 1.0000 1 0.0000 20029 343.77 20 .0058 1 1.0000 .0058 171.89 343.77 30 .0087 1 1.0000 .0087 114.59 171.89 40 .0116 .9999 .0145 68.750 .016 85.940 .016 85.940 50 .0145 .9999 .0145 68.750 .0175 57.290 .0204 49.104 20 .0233 .9997 .0233 342.964 .0204 49.104 .0204 49.104 20 .0233 .9997 .0262 38.188 .0224 .994 .0291 34.368 .0291 .34.368 .0291 .34.368 50 .0320 .9995 .0320 31.242 .0291 .0407 .0291 34.368 .0291 .0407 .0291 34.368 50 .0320 .9995 .0320 31.242 .0320 .9995 .0320 31.242 2° .00′ .0.0349 .9994 .0.049 .0.049 .0.049 .0.049 .0.0407 .9992 .0.0407 .0.049	40				
30					30
			1		20
0° 00′	10				
0° 00′ 0.0000 1.0000 0.0000 ∞ 90 10 .0029 1.0000 .0029 343.77 90 20 .0058 1.0000 .0058 171.89 30 114.59 340 10116 .9999 .0116 85.940 50 10145 .9999 .01145 68.750 89 68.750 10 .0204 .9998 .02175 57.290 89 89 .0204 49.104 49.104 20 .0233 .9997 .0224 49.104 20 .0233 .9997 .0262 38.188 <	89° 00′				
10	.0204	.9998	.0204	49.104	50
0° 00′ 0.0000 1.0000 0.0009 343.77 9 20 .0058 1.0000 .0029 343.77 9 30 .0087 1.0000 .0087 171.89 30 .0087 1.0000 .0087 114.59 40 .0116 .9999 .0116 68.750 1° 00′ 0.0175 .0.9998 .0.0175 57.290 8 10 .0204 .9998 .0204 49.104 20.116 29.997 .0262 38.188 40.0291 .9996 .0291 34.368 34.368 34.368 34.368 34.368 34.368 34.368 34.368 34.368 36.36 8.36	40				
0° 00′ 0.0000 1.0000 0.0009 343.77 20 .0058 1.0000 .0029 343.77 20 .0058 1.0000 .0087 171.89 30 .0087 1.0000 .0087 171.89 40 .0116 .9999 .0145 68.750 1° 00′ 0.0175 .9998 .0204 49.104 20 .0233 .9997 .0262 38.188 40 .0221 .9998 .0204 49.104 20 .0233 .9997 .0262 38.188 40 .0221 .9996 .0221 34.368 30 .0252 .9997 .0262 38.188 40 .0221 .9996 .0221 34.368 30 .0340 .9999 .0320 .31242 2° .00′ .0378 .9993 .0378 26.432 20 .0407 .99992 .0407 24.542 30 </td <td>30</td>	30				
40	.0291	.9996	.0291	34.368	20
50	.0320	.9995	.0320		10
2° 00'	0.0349	0.9994	0.0349	28.636	88° 00'
10	.0378	.9993	.0378	26,432	50
20	.0407	.9992	.0407	24.542	40
30	.0436	.9990	.0437	22,904	30
40	.0465	.9989	.0466	21,470	20
0° 00′ 0.0000 1.0000 10 .0029 1.0000 20 .0058 1.0000 30 .0087 1.0000 40 .0116 .9999 50 .0145 .9999 10 .0204 .9998 20 .0233 .9997 30 .0262 .9997 40 .0291 .9996 50 .0320 .9995 2° 00′ 0.0349 0.9994 10 .0378 .9993 20 .0407 .9992 30 .0436 .9990 40 .0465 .9989 50 .0494 .9988 3° 00′ 0.0523 0.9986 10 .0552 .9985 20 .0581 .9981 30 .0610 .9981 4° 00′ 0.0698 0.9976 10 .0727 .9974			10		
3° 00′	0.0523	0.9986	0.0524	19.081	87° 00′
	.0552	.9985	.0553	18.075	50
	.0581	.9983	.0582	17.169	40
30	.0610	.9981	.0612	16.350	30
	.0640	.9980	.0641	15.605	20
50	.0669	.9978	.0670	14.924	10
		0.9976	0.0699	14.301	86° 00′
		.9974	.0729	13.727	50
		.9971	.0758	13.197	40
			.0787	12.706	30
	.0814	.9967	.0816	12.251	20
	.0843	.9964	.0846	11.826	10
1					85° 00′
					50
					40
					30
					20 10
J					
1					84° 00′
					50
			1 1		40
0° 00′ 0.0000 10 .0029 20 .0058 30 .0087 40 .0116 50 .0145 1° 00′ 0.0175 10 .0204 20 .0233 30 .0262 40 .0291 50 .0320 2° 00′ .0.0349 10 .0378 20 .0407 30 .0436 40 .0465 50 .0494 3° 00′ 0.0523 10 .0552 20 .0581 30 .0610 40 .0640 50 .0669 4° 00′ 0.0698 10 .0727 20 .0756 30 .0785 40 .0814 50 .0843 5° 00′ 0.0872 10 .0901				30	
					20 10
					83° 00′
		_			
					50
					40
					30
					20 10
	Cos	Sin		Tan	Degrees

Table XXVIII. Natural Trigonometric Functions—(Cont'd)

8° 00' 0.1392 0.9903 0.1405 7.1154 82° 00' 10 .1421 .9899 1.445 6.9682 50 20 .1449 .9894 .1465 6.8269 40 30 .1478 .9890 .1455 6.6912 30 40 .1507 .9886 .1524 6.5606 20 50 .1536 .9881 .1554 6.5006 20 50 .1533 .9872 .1614 6.1970 50 10 .1593 .9872 .1614 6.1970 50 20 .1622 .9868 .1644 6.0844 6.0844 30 .1650 .9863 .1673 5.9758 30 40 .1679 .9853 .1703 5.8708 20 10° .00' 0.1765 .9843 .1793 5.5764 50 20 .1794 .9838 .1823 5.3955 30 30	Degrees	Sin	Cos	Tan	Cot	
10	8° 00'	0.1392	0.9903	0.1405	7.1154	82° 00'
20	10		.9899		1	
30	20					
40 .1507 .9886 .1524 6.5606 20 50 .1536 .9881 .1554 6.4348 10 9° 00' 0.1564 0.9877 0.1584 6.4348 81° 00' 10 .1593 .9872 .1614 6.1970 50 20 20 .1622 .9868 .1644 6.0844 40 30 .1679 .9858 .1703 5.9788 30 40 .1679 .9858 .1703 5.8708 20 10 .17765 .9843 .1733 5.7694 10 10° .1794 .9838 .1823 5.4845 40 .8853 .1833 5.3955 30 20 .1794 .9838 .1823 5.3955 30 4845 40 .1851 .9827 .1883 5.3995 30 18 18 30 .18 19 9811 .1974 5.0658 50 20 .1944 5.1446	30				1	1
50 .1536 .9881 .1554 6.4348 10 9° 00' 0.1564 0.9877 0.1584 6.3138 81° 00' 10 .1593 .9872 .1614 6.1970 50 20 .1622 .9868 .1673 5.9758 30 40 .1679 .9858 .1703 5.8708 20 50 .1708 .9853 .1733 5.7694 10 10° 00' 0.1736 .9848 0.1763 5.6713 80° 00' 10 .1765 .9843 .1793 5.5764 40 20 .1794 .9838 .1823 5.3955 30 30 .1822 .9833 .1853 5.3955 30 40 .1851 .9827 .1883 5.3995 20 50 .1880 .9822 .1914 5.0658 4 20 .1965 .9805 .2004 4.9894 40 30	40					
10	50	I				1
10	9° 00'	0.1564	0.9877	0.1584	6 2120	810 001
10						
30						
40 .1679 .9858 .1703 5.8708 20 50 .1708 .9853 .1733 5.7694 10 10° 00° 0.1736 .9848 0.1763 5.6713 80° 00° 10 .1765 .9843 .1823 5.4845 40 20 .1794 .9838 .1823 5.4845 40 30 .1822 .9833 .1853 5.3955 30 40 .1851 .9827 .1883 5.3093 20 50 .1880 .9822 .1914 5.2257 10 11° 00° 0.1908 0.9816 0.1944 5.1446 79° 00° 10 .1937 .9811 .1974 5.0658 50 20 .1965 .9805 .2004 4.9894 40 30 .1994 .9799 .2035 4.9152 30 40 .2022 .9793 .2065 4.8430 20 50 .2			1			
50 .1708 9853 .1733 5.7694 10 10° 00′ 0.1736 0.9848 0.1763 5.6713 80° 00′ 10 .1765 .9843 .1793 5.5764 50 20 .1794 .9838 .1823 5.4845 40 30 .1822 .9833 .1853 5.3953 30 40 .1851 .9827 .1883 5.3093 20 50 .1880 .9822 .1914 5.2257 10 11° 00′ 0.1908 0.9816 0.1944 5.1446 79° 00 10 .1937 .9811 .1974 5.0658 50 20 .1965 .9805 .2004 4.9894 40 30 .1994 .9799 .2035 4.9152 30 40 .2022 .9793 .2065 4.8430 20 12° 00′ 0.2079 0.9781 0.2126 4.7046 78° 00′ 12° 00′<	1				1	
10			1	4		
10	10° 00'	0.1736	0.0848	0.1763	5 6712	80° 00'
20 1.794 .9838 .1823 5.4845 40 30 .1822 .9833 .1853 5.3955 30 40 .1851 .9827 .1883 5.3093 20 50 .1880 .9822 .1914 5.2257 10 11° 00° 0.1908 0.9816 0.1944 5.1446 79° 00° 10 .1937 .9811 .1974 5.0658 50 20 .1965 .9805 .2004 4.9894 40 30 .1994 .9799 .2035 4.9152 30 40 .2022 .9793 .2065 4.8430 20 50 .2051 .9787 .2095 4.7729 10 12° 00° 0.2079 0.9781 0.2126 4.7046 78° 00° 10 .2136 .9775 .2156 4.6382 50 20 .2136 .9763 .2217 4.5107 30 40 .						
30		1				1
40 .1851 .9827 .1883 5.3093 20 50 .1880 .9822 .1914 5.2257 10 11° 00′ 0.1908 0.9816 0.1944 5.1446 79° 00′ 10 .1937 .9811 .1974 5.0658 50 20 .1965 .9805 .2004 4.9894 40 30 .1994 .9799 .2035 4.9152 30 40 .2022 .9793 .2065 4.8430 20 50 .2051 .9787 .2095 4.7729 10 12° 00′ 0.2079 0.9781 0.2126 4.7046 78° 00′ 10 .2108 .9775 .2156 4.6382 50 20 .2136 .9769 .2186 4.5736 40 30 .2164 .9763 .2217 4.4494 20 40 .2193 .9757 .2247 4.4494 20 30 .						1
50 .1880 .9822 .1914 5.2257 10 11° 00′ 0.1908 0.9816 0.1944 5.1446 79° 00′ 10 .1937 .9811 .1974 5.0658 50 20 .1965 .9805 .2004 4.9894 40 30 .1994 .9799 .2035 4.9152 30 40 .2022 .9793 .2065 4.8430 20 50 .2051 .9787 .2095 4.7729 10 12° 00′ 0.2079 0.9781 0.2126 4.7046 78° 00′ 10 .2108 .9775 .2156 4.6382 50 20 .2136 .9769 .2186 4.5736 40 30 .2164 .9763 .2217 4.5107 30 40 .2193 .9757 .2247 4.4494 20 50 .2221 .9750 .2278 4.3897 10 13° 00′						
11° 00′						
10]			1	5.2257	
20 .1965 .9805 .2004 4,9894 40 30 .1994 .9799 .2035 4,9152 30 40 .2022 .9793 .2065 4,8430 20 50 .2051 .9787 .2095 4,7729 10 12° 00' 0.2079 0.9781 0.2126 4,7046 78° 00' 10 .2108 .9775 .2156 4,6382 50 20 .2136 .9769 .2186 4,5736 40 30 .2164 .9763 .2217 4,5107 30 40 .2193 .9757 .2247 4,4494 20 50 .2221 .9750 .2278 4,3897 10 13° 00' 0.2250 0.9744 0.2309 4,3315 77° 00' 10 .2278 .9737 .2339 4,2747 50 20 .2363 .9717 .2432 4,1126 20 20 </td <td></td> <td></td> <td>0.9816</td> <td>0.1944</td> <td>5.1446</td> <td>79° 00′</td>			0.9816	0.1944	5.1446	79° 00′
30				.1974	5.0658	50
40		.1965	.9805		4.9894	40
50 .2051 .9787 .2095 4.7729 10 12° 00' 0.2079 0.9781 0.2126 4.7046 78° 00' 10 .2108 .9775 .2156 4.6382 50 20 .2136 .9769 .2186 4.5736 40 30 .2164 .9763 .2217 4.5107 30 40 .2193 .9757 .2247 4.4494 20 50 .2221 .9750 .2278 4.3897 10 13° 00' 0.2250 0.9744 0.2309 4.3315 77° 00' 10 .2278 .9737 .2339 4.2747 50 20 .2306 .9730 .2370 4.2193 40 30 .2334 .9724 .2401 4.1653 30 40 .2363 .9717 .2432 4.1126 20 50 .2391 .9710 .2462 4.0611 10 14° 00'		.1994	.9799	.2035	4.9152	30
12° 00' 0.2079 0.9781 0.2126 4.7046 78° 00' 10 .2108 .9775 .2156 4.6382 50 20 .2136 .9769 .2186 4.5736 40 30 .2164 .9763 .2217 4.5107 30 40 .2193 .9757 .2247 4.4494 20 50 .2221 .9750 .2278 4.3897 10 13° 00' 0.2250 0.9744 0.2309 4.3315 77° 00' 10 .2278 .9737 .2339 4.2747 50 20 .2306 .9730 .2370 4.2193 40 30 .2334 .9724 .2401 4.1653 30 40 .2363 .9717 .2432 4.1126 20 50 .2391 .9710 .2462 4.0611 10 14° 00' 0.2419 0.9703 0.2493 4.0108 76° 00' 10			.9793	.2065	4.8430	20
10 .2108 .9775 .2156 4.6382 50 20 .2136 .9769 .2186 4.5736 40 30 .2164 .9763 .2217 4.5107 30 40 .2193 .9757 .2247 4.4494 20 50 .2221 .9750 .2278 4.3897 10 13° 00' 0.2250 0.9744 0.2309 4.3315 77° 00' 10 .2278 .9737 .2339 4.2747 50 20 .2306 .9730 .2370 4.2193 40 30 .2334 .9724 .2401 4.1653 30 40 .2363 .9717 .2432 4.1126 20 50 .2391 .9710 .2462 4.0611 10 14° 00' 0.2419 0.9703 0.2493 4.0108 76° 00' 10 .2447 .9696 .2524 3.9617 50 20 </td <td>50</td> <td>.2051</td> <td>.9787</td> <td>.2095</td> <td>4.7729</td> <td>10</td>	50	.2051	.9787	.2095	4.7729	10
20 .2136 .9769 .2186 4.5736 40 30 .2164 .9763 .2217 4.5107 30 40 .2193 .9757 .2247 4.4494 20 50 .2221 .9750 .2278 4.3897 10 13° 00' 0.2250 0.9744 0.2309 4.3315 77° 00' 10 .2278 .9737 .2339 4.2747 50 20 .2306 .9730 .2370 4.2193 40 30 .2334 .9724 .2401 4.1653 30 40 .2363 .9717 .2432 4.1126 20 50 .2391 .9710 .2462 4.0611 10 14° 00' 0.2419 0.9703 0.2493 4.0108 76° 00' 10 .2447 .9696 .2524 3.9617 50 20 .2476 .9689 .2555 3.9136 40 30 .			0.9781	0.2126	4.7046	78° 00'
30		.2108	.9775	.2156	4.6382	50
40		.2136	.9769	.2186	4.5736	40
50 .2221 .9750 .2278 4.3897 10 13° 00' 0.2250 0.9744 0.2309 4.3315 77° 00' 10 .2278 .9737 .2339 4.2747 50 20 .2306 .9730 .2370 4.2193 40 30 .2334 .9724 .2401 4.1653 30 40 .2363 .9717 .2432 4.1126 20 50 .2391 .9710 .2462 4.0611 10 14° 00' 0.2419 0.9703 0.2493 4.0108 76° 00' 10 .2447 .9696 .2524 3.9617 50 20 .2476 .9689 .2555 3.9136 40 30 .2504 .9681 .2586 3.8667 30 40 .2532 .9674 .2617 3.8208 20 50 .2560 .9667 .2648 3.7760 10 15° 00'		.2164	.9763	.2217	4.5107	30
13° 00' 0.2250 0.9744 0.2309 4.3315 77° 00' 10 .2278 .9737 .2339 4.2747 50 20 .2306 .9730 .2370 4.2193 40 30 .2334 .9724 .2401 4.1653 30 40 .2363 .9717 .2432 4.1126 20 50 .2391 .9710 .2462 4.0611 10 14° 00' 0.2419 0.9703 0.2493 4.0108 76° 00' 10 .2447 .9696 .2524 3.9617 50 20 .2476 .9689 .2555 3.9136 40 30 .2504 .9681 .2586 3.8667 30 40 .2532 .9674 .2617 3.8208 20 50 .2560 .9667 .2648 3.7760 10 15° 00' 0.2588 0.9659 0.2679 3.7321 75° 00' 10			.9757	.2247	4.4494	20
10 .2278 .9737 .2339 4.2747 50 20 .2306 .9730 .2370 4.2193 40 30 .2334 .9724 .2401 4.1653 30 40 .2363 .9717 .2432 4.1126 20 50 .2391 .9710 .2462 4.0611 10 14° 00′ 0.2419 0.9703 0.2493 4.0108 76° 00′ 10 .2447 .9696 .2524 3.9617 50 20 .2476 .9689 .2555 3.9136 40 30 .2504 .9681 .2586 3.8667 30 40 .2532 .9674 .2617 3.8208 20 50 .2560 .9667 .2648 3.7760 10 15° 00′ 0.2588 0.9659 0.2679 3.7321 75° 00′ 10 .2644 .9644 .2742 3.6470 40 30 .2672 .9636 .2773 3.6059 30 40 .2700 .9628 .2805 3.5656 20 50 .2728 .9621 .2836 3.5261 10	50	.2221	.9750	.2278	4.3897	10
20 .2306 .9730 .2370 4.2193 40 30 .2334 .9724 .2401 4.1653 30 40 .2363 .9717 .2432 4.1126 20 50 .2391 .9710 .2462 4.0611 10 14° 00′ 0.2419 0.9703 0.2493 4.0108 76° 00′ 10 .2447 .9696 .2524 3.9617 50 20 .2476 .9689 .2555 3.9136 40 30 .2504 .9681 .2586 3.8667 30 40 .2532 .9674 .2617 3.8208 20 50 .2560 .9667 .2648 3.7760 10 15° 00′ 0.2588 0.9659 0.2679 3.7321 75° 00′ 10 .2616 .9652 .2711 3.6891 50 20 .2644 .9644 .2742 3.6470 40 30 .	1					77° 00′
30					4.2747	50
40 .2363 .9717 .2432 4.1126 20 .50 .2391 .9710 .2462 4.0611 10 .2462 .2624 .0611 .10 .2462 .2624 .0611 .10 .2447 .9696 .2524 3.9617 .50 .20 .2476 .9689 .2555 3.9136 .40 .30 .2504 .9681 .2586 3.8667 .30 .40 .2532 .9674 .2617 3.8208 .20 .50 .2560 .9667 .2648 3.7760 .10 .2616 .9652 .2711 3.6891 .50 .2644 .9644 .2742 3.6470 .40 .30 .2672 .9636 .2773 3.6059 .30 .2672 .9636 .2773 3.6059 .30 .2728 .9621 .2836 3.5261 .10						40
50 .2391 .9710 .2462 4.0611 10 14° 00′ 0.2419 0.9703 0.2493 4.0108 76° 00′ 10 .2447 .9696 .2524 3.9617 50 20 .2476 .9689 .2555 3.9136 40 30 .2504 .9681 .2586 3.8667 30 40 .2532 .9674 .2617 3.8208 20 50 .2560 .9667 .2648 3.7760 10 15° 00′ 0.2588 0.9659 0.2679 3.7321 75° 00′ 10 .2616 .9652 .2711 3.6891 50 20 .2644 .9644 .2742 3.6470 40 30 .2672 .9636 .2773 3.6059 30 40 .2700 .9628 .2805 3.5656 20 50 .2728 .9621 .2836 3.5261 10					4.1653	30
14° 00′ 0.2419 0.9703 0.2493 4.0108 76° 00′ 10 .2447 .9696 .2524 3.9617 50 20 .2476 .9689 .2555 3.9136 40 30 .2504 .9681 .2586 3.8667 30 40 .2532 .9674 .2617 3.8208 20 50 .2560 .9667 .2648 3.7760 10 15° 00′ 0.2588 0.9659 0.2679 3.7321 75° 00′ 10 .2616 .9652 .2711 3.6891 50 20 .2644 .9644 .2742 3.6470 40 30 .2672 .9636 .2773 3.6059 30 40 .2700 .9628 .2805 3.5656 20 50 .2728 .9621 .2836 3.5261 10	1			l .	4.1126	20
10	50	.2391	.9710	.2462	4.0611	10
20 .2476 .9689 .2555 3.9136 40 30 .2504 .9681 .2586 3.8667 30 40 .2532 .9674 .2617 3.8208 20 50 .2560 .9667 .2648 3.7760 10 15° 00' 0.2588 0.9659 0.2679 3.7321 75° 00' 10 .2616 .9652 .2711 3.6891 50 20 .2644 .9644 .2742 3.6470 40 30 .2672 .9636 .2773 3.6059 30 40 .2700 .9628 .2805 3.5656 20 50 .2728 .9621 .2836 3.5261 10	1		0.9703	0.2493	4.0108	76° 00′
30 .2504 .9681 .2586 3.8667 30 40 .2532 .9674 .2617 3.8208 20 50 .2560 .9667 .2648 3.7760 10 15° 00' 0.2588 0.9659 0.2679 3.7321 75° 00' 10 .2616 .9652 .2711 3.6891 50 20 .2644 .9644 .2742 3.6470 40 30 .2672 .9636 .2773 3.6059 30 40 .2700 .9628 .2805 3.5656 20 50 .2728 .9621 .2836 3.5261 10			1		3.9617	50
40 .2532 .9674 .2617 3.8208 20 50 .2560 .9667 .2648 3.7760 10 15° 00' 0.2588 0.9659 0.2679 3.7321 75° 00' 10 .2616 .9652 .2711 3.6891 50 20 .2644 .9644 .2742 3.6470 40 30 .2672 .9636 .2773 3.6059 30 40 .2700 .9628 .2805 3.5656 20 50 .2728 .9621 .2836 3.5261 10					3.9136	40
50 .2560 .9667 .2648 3,7760 10 15° 00′ 0.2588 0.9659 0.2679 3,7321 75° 00′ 10 .2616 .9652 .2711 3.6891 50 20 .2644 .9644 .2742 3.6470 40 30 .2672 .9636 .2773 3.6059 30 40 .2700 .9628 .2805 3.5656 20 50 .2728 .9621 .2836 3.5261 10					3.8667	30
15° 00' 0.2588 0.9659 0.2679 3.7321 75° 00' 10 .2616 .9652 .2711 3.6891 50 20 .2644 .9644 .2742 3.6470 40 30 .2672 .9636 .2773 3.6059 30 40 .2700 .9628 .2805 3.5656 20 50 .2728 .9621 .2836 3.5261 10		1	1	.2617	3.8208	20
10 .2616 .9652 .2711 3.6891 50 20 .2644 .9644 .2742 3.6470 40 30 .2672 .9636 .2773 3.6059 30 40 .2700 .9628 .2805 3.5656 20 50 .2728 .9621 .2836 3.5261 10	50	.2560	.9667	.2648	3,7760	10
20 .2644 .9644 .2742 3.6470 40 30 .2672 .9636 .2773 3.6059 30 40 .2700 .9628 .2805 3.5656 20 50 .2728 .9621 .2836 3.5261 10			0.9659	0.2679	3.7321	75° 00′
30 2672 .9636 .2773 3.6059 30 40 .2700 .9628 .2805 3.5656 20 50 .2728 .9621 .2836 3.5261 10			.9652		3.6891	50
40 .2700 .9628 .2805 3.5656 20 50 .2728 .9621 .2836 3.5261 10			.9644	.2742	3.6470	40
50 .2728 .9621 .2836 3.5261 10		ľ	.9636	.2773	3.6059	30
				.2805	3.5656	20
Cos Sin Cot Tan Degrees	50	.2728	.9621	.2836	3.5261	10
		Cos	Sin	Cot	Tan	Degrees

 $\label{thm:continuous} \textbf{Table XXVIII.} \quad \textbf{Natural Trigonometric Functions} \textbf{--} (\textbf{Cont'd})$

Degrees	5:				
Degrees	Sin	Cos	Tan	Cot	
16° 00′	0.2756	0.9613	0.2867	3,4874	74° 00′
	1	.9605	.2899		50
		.9596	.2931	_	40
		.9588	.2962	3.3759	30
16° 00′ 0.2756 10 0.9613 2784 20 0.9613 2899 3.4495 20 0.2812 2996 2931 3.4124 30 3.4874 3.4124 3.4124 3.01 2888 3.9580 3.9572 3.026 3.3052 3.4874 3.4124 3.4124 3.4124 3.4124 3.4124 3.4124 3.4125 3.4124 3.4124 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4124 3.4125 3.4124 3.4125 3.4124 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4124 3.4125 3.4121 3.4124 3.4124 3.4125 3.4121 3.4125 3.4	20				
16° 00′ 0.2756 0.9613 0.2867 3.4874 10 .2784 .9605 .2899 3.4495 20 .2812 .9596 .2931 3.4124 30 .2840 .9588 .2962 3.3759 40 .2868 .9580 .2994 3.3402 50 .2896 .9572 .3026 3.3052 17° 00° 0.2924 0.9563 0.3057 3.27C7 10 .2952 .9555 .3089 3.2371 30 .3007 .9537 .3153 3.1716 40 .3035 .9528 .3185 3.1397 30 .3062 .9520 .3217 3.1084 18° 00° 0.3090 .0,9511 0.3249 3.0777 10 .3118 .9502 .3221 3.0475 20 .3145 .9492 .3314 3.0178 30 .3173 .9483 .3346 2.9887 <	10				
	1		0.3057	3.2707	73° 00′
			.3089	3.2371	50
16° 00'	40				
16° 00'	30				
			.3185	3.1397	20
16° 00′ 0.2756 0.9613 0.2867 3.4874 10 .2784 .9605 .2899 3.4495 20 .2812 .9596 .2931 3.4124 30 .2840 .9588 .2962 3.3759 40 .2868 .9580 .2994 3.3402 50 .2896 .9572 .3026 3.3052 17° 00′ 0.2924 0.9563 0.3057 3.27C? 10 .2952 .9555 .3089 3.2371 30 .3007 .9537 .3153 3.1716 40 .3035 .9528 .3185 3.1397 30 .3062 .9520 .3217 3.1084 18° 00′ 0.3090 0.9511 0.3249 3.0777 30 .3173 .9483 .3346 2.9887 40 .3228 .9465 .3411 2.9319 19° 00′ .0.3256 .0.9455 0.3443 2	10				
		1	0.3249	3.0777	72° 00'
16° 00' 0.2756 0.9613 0.2867 3.4874 2.2637 2.284 .9605 .2899 3.4495 2.2812 .9596 .2931 3.4124 3.0 .2868 .9588 .2962 3.3759 4.0 .2868 .9580 .2994 3.3402 3.0552 3.062 .9572 .3026 3.0552 3.052 3.		50			
				3.0178	40
				2.9887	30
					20
	.3228	.9465	.3411	2.9319	10
		0.9455	0.3443	2.9042	71° 00′
		.9446	.3476		50
16° 00′ 0.2756 0.9613 0.2867 3.4874 20 .2812 .9596 .2931 3.4124 30 .2840 .9588 .2962 3.3759 40 .2868 .9580 .2994 3.3402 50 .2896 .9572 .3026 3.3052 17° 00′ 0.2924 0.9563 0.3057 3.27C7 10 .2952 .9555 .3089 3.2371 30 .3007 .9537 .3153 3.1716 40 .3035 .9528 .3185 3.1397 50 .3062 .9520 .3217 3.1084 18° 00′ 0.3090 .0,9511 0.3249 .3077 10 .3118 .9502 .3281 3.0475 30 .3173 .9483 .3346 2,9887 30 .3173 .9483 .3346 2,9887 30 .3228 .9465 .3411 2,9319 19° 00′	40				
10	30				
30 .2840 .9588 .2962 3.3759 50 .2896 .9580 .2994 3.3402 50 .2896 .9572 .3026 3.3052 17° 00′ 0.2924 0.9563 0.3057 3.27C2 10 .2952 .9555 .3089 3.2371 20 .2979 .9546 .3121 3.2041 30 .3007 .9537 .3153 3.1716 40 .3035 .9528 .3185 3.1397 50 .3062 .9520 .3217 3.1084 18° 00′ 0.3090 0.9511 0.3249 3.0475 30 .3118 .9502 .3281 3.0475 30 .3173 .9483 .3346 2.9887 40 .3201 .9474 .3378 2.9600 50 .3228 .9465 .3411 2.9319 19° 00′ 0.3256 0.9455 0.3443 2.9042 <t< td=""><td>20</td></t<>	20				
	.3393	.9407	.3607	2.7725	10
		0.9397	0.3640	2.7475	70° 00'
			.3673	2.7228	50
17° 00' 0.2924 0.9563 0.3 10 2.952 .9555 3 20 .2979 .9546 .3 30 .3007 .9537 .3 40 .3035 .9528 .3 50 .3062 .9520 .3 10 .3118 .9502 .3 20 .3145 .9492 .3 30 .3173 .9483 .3 40 .3201 .9474 .33 40 .3201 .9474 .33 40 .3228 .9465 .34 19° 00' 0.3256 0.9455 0.34 20 .3311 .9436 .35 30 .3338 .9426 .35 30 .3338 .9426 .35 30 .3348 .9437 .36 20° 00' 0.3420 0.9397 0.36 20° .3448 .9387	.3706	2.6985	40		
			.3739	2.6746	30
			.3772	2.6511	20
	.3557	.9346	.3805	2.6279	10
(0.3839	2.6051	69° 00'
16° 00' 0.2756 0.9613 0.2867 3.4874 10 2.784 .9605 .2899 3.4495 3.492 3.0 .2812 .9596 .2991 3.4124 30 .2840 .9588 .2962 3.3759 40 .2868 .9580 .2994 3.3402 3.3053 3.3052 3.3053 3.3052 3.3053 3.3053 3.3153 3.1716 3.3063 3.3052 3.3217 3.1084 3.3062 3.9528 3.3185 3.1397 3.3062 3.9528 3.3185 3.1397 3.3062 3.9528 3.3185 3.30475 3.318 3.0475 3.318 3.0475 3.318 3.0475 3.314 3.0178 3.0184 3.0178 3.0184 3.0178 3.0184 3.0178 3.0184 3.0188 3.0188 3.0188 3.0188 3.0188 3.0188 3.0188 3.01		50			
			.3906	2.5605	40
1			.3939	2.5386	30
				2.5172	20
	.3/19	.9283	.4006	2.4960	10
			0.4040	2.4751	68° 00'
			.4074	2.4545	50
10 .3448 .9387 .3643 2.7428 20 .3475 .9377 .3706 2.6985 30 .3502 .9367 .3739 2.6746 40 .3529 .9356 .3772 2.6511 50 .3557 .9346 .3805 2.6279 21° 00′ 0.3584 0.9336 0.3839 2.6051 10 .3611 .9325 .3872 2.5826 20 .3638 .9315 .3906 2.5605 30 .3665 .9304 .3939 2.5386 40 .3692 .9293 .3973 2.5172 50 .3719 .9283 .4006 2.4751 20° .03746 0.9272 0.4040 2.4751 20 .3800 .9250 .4108 2.4342 20 .3800 .9250 .4108 2.4342 30 .3827 .9239 .4142 2.4142 40 .3854			40		
40		30			
40 .3035 .9528 .3185 3.1397 3.1084 18° 00° 0.3090 0.9511 0.3249 3.0777 72° 10 .3118 .9502 .3281 3.0475 3.0475 30 .3173 .9483 .3346 2.9887 40 30 .3173 .9483 .3346 2.9887 40 50 .3228 .9465 .3411 2.9319 71° 19° 00° 0.3256 0.9455 0.3443 2.9042 71° 10 .3283 .9446 .3476 2.8770 20° .3311 .9436 .3508 2.8502 30 .3338 .9426 .3541 2.8239 40 .3365 .9417 .3574 2.7980 .3607 2.7725 20° .3448 .9387 .3607 2.7475 70° 10 .3448 .9387 .3673 2.7228 2.6746 2.6985 30 .3557 .9346 .3805 2.6679 2.6746 <td< td=""><td>20</td></td<>	20				
10	10				
17° 00′ 0.2924 10 2.2952 20 2.2979 30 3.007 40 3.035 50 3.062 18° 00′ 0.3090 10 3118 20 3145 30 3173 40 3201 50 3228 19° 00′ 0.3256 10 3283 20 3311 30 3383 40 3365 50 3393 20° 00′ 0.3420 10 3448 20 3475 30 3502 40 3529 50 3557 21° 00′ 0.3584 10 3611 20 3638 30 3665 40 3692 50 3719 22° 00′ 0.3746 10 3773 20 3800 30 3827 40 3854 50 3881 23° 00′ 0.3907 10 3934 20 3961 30 3937 20 3987 40 .4014 50 .4041		0.4245	2.3559	67° 00′	
10	50				
16° 00′ 0.2756 0.9613 0.2867 3.4874 3.00 2.2812 9.596 2.991 3.4124 3.00 2.2840 9.588 2.962 3.3759 3.405 3.00 2.2868 9.580 2.994 3.3402 3.0052 3.007 3.007 9.537 3.153 3.1716 3.0041 3.0035 9.528 3.185 3.1397 3.0062 9.9502 3.217 3.1084 3.0062 9.9502 3.217 3.1084 3.007 3.0062 9.9502 3.281 3.0475 3.0475 3.0178 3.018 3.0178 3.018 3.0178 3.018	40				
16° 00' 0.2756 0.9613 0.2867 3.4874 10 .2784 .9605 .2899 3.4495 20 .2812 .9596 .2931 3.4124 30 .2840 .9588 .2962 3.3759 40 .2868 .9580 .2994 3.3402 50 .2896 .9572 .3026 3.3052 17° 00' 0.2924 0.9563 0.3057 3.27C2 10 .2952 .9555 .3089 3.2371 30 .3007 .9537 .3153 3.1716 30 .3007 .9537 .3153 3.1716 40 .3035 .9528 .3185 3.1397 30 .3062 .9520 .3217 3.1084 18° 00' 0.3090 0.9511 0.3249 3.0777 10 .3118 .9502 .3214 3.0475 30 .3173 .9483 .3346 2.9887 30	30				
					20
50	.4041	.9147	.4417	2.2637	10

Table XXVIII. Natural Trigonometric Functions—(Cont'd)

Degrees	Sin	Cos	Tan	Cot			
		0.0105	0.4452	2.2460	66° 00′		
24° 00′					50		
10	Sin Cos Tan Cot 0.4067 0.9135 0.4452 2.2460 4.094 .9124 .4487 2.2286 1.4120 .9112 .4522 2.2113 2.14173 .9088 .4592 2.1775 3.4200 .9075 .4628 2.1609 3.4253 .9051 .4699 2.1283 3.0 .4279 .9038 .4734 2.1123 3.0 .4279 .9038 .4770 2.0965 3.0 .4279 .9038 .4734 2.1123 3.0 .4279 .9038 .4770 2.0965 3.0 .4279 .9038 .4770 2.0965 3.0 .4279 .9038 .4770 2.0965 3.0 .4331 .9013 .4806 2.0809 3.0 .4348 .0.8988 0.4877 2.0553 3.0 .4410 .8975 .4913 2.0353 3.0 .44410				40		
	.4120	Cos Tan Cot 0.9135 0.4452 2.2460 66° .9124 .4487 2.2286 .9112 .4522 2.2113 .9100 .4557 2.1943 .9088 .4592 2.1775 .9088 .4592 2.1775 .9075 .4628 2.1609 .9075 .4628 2.1609 .1283 .9051 .4699 2.1283 .9038 .4734 2.1123 .9038 .4770 2.0965 .9013 .4806 2.0809 .8962 .4970 2.0965 .9013 .4806 2.0809 .8975 .4913 2.0353 64° .8975 .4913 2.0353 .64° .8949 .4986 2.0057 8 8936 .5022 1.9912 .8949 .4986 2.0057 8 8893 .5022 1.9912 .8949 .4986 2.0057 8 .8936 .5022 1.9912 .8949 .4986 2.0057 .8876 .5243		30			
	Grees Sin Cos Tan Cet ° 00' 0.4067 0.9135 0.4452 2.244 10 .4094 .9124 .4487 2.228 20 .4120 .9112 .4522 2.21 30 .4147 .9100 .4557 2.19 40 .4173 .9088 .4592 2.17 50 .4200 .9075 .4628 2.16 10 .4253 .9051 .4699 2.12 20 .4279 .9038 .4734 2.11 30 .4305 .9026 .4770 2.09 40 .4331 .9013 .4806 2.06 40 .4331 .9013 .4806 2.06 40 .4331 .9013 .4806 2.06 40 .4384 0.8988 0.4877 2.05 20 .4436 .8962 .4950 2.07 30 .4646 .8949 .			20			
Degrees Sin 24° 00′ 10 .4067 .4094 .4120 .30 .4147 .40 .4173 .50 .4200 .4226 .20 .4279 .30 .4305 .40 .4331 .50 .4358 .40 .4318 .50 .4358 .4358 .4358 .4358 .4358 .4462 .40 .4488 .50 .4514 .4410 .20 .4436 .30 .4462 .40 .4488 .50 .4514 .4566 .20 .4592 .30 .4617 .40 .4643 .50 .4669 .4720 .30 .4774 .40 .4795 .50 .482 .4792 .50 .482 .4792 .50 .482 .489 .30 .492 .49 .495 .50 .497 .30° .00′ 0.500 .500 .40 .510 .500 .500 .500 .500 .500 .500 .50		.9088	.4592				
20			.4628	2.1609	10		
	0.4226	0.9063	0.4663	2.1445	65° 00′		
			.4699	2.1283	50		
			4734	2.1123	40		
				2.0965	30		
				2.0809	20		
40					10		
50	.4358	.9001	.4841				
26° 00′	0.4384				64° 00′ 50		
	.4410	.8975			40		
		.8962			30		
		.8949					
			.5022	22 2.2460 2.2286 2.2113 2.1943 2.1943 2.1943 2.1775 28 2.1609 63 2.1445 99 2.1283 34 2.1123 70 2.0965 06 2.0809 441 2.0655 377 2.0503 3750 2.0204 2.0057 3.20353 2.0353 2.0353 2.0353 2.0353 2.0204 2.096 2.097 3.20353 2.0	20		
	1			1.9768	10		
	1	0.8910	0.5095	1.9626	63° 00′		
				1.9486	50		
10					40		
20	1	1	1	I .	30		
30	.4617	1 '			20		
40	.4643				10		
50	.4669	.8843	.5280	1.0940			
000 001	0.4695	0.8829	0.5317		62° 00′		
			.5354		50 40		
			.0010				
				1.8418	30		
• • •				1.8291	20		
				1.8165	10		
-			0.5543	1.8040	61° 00′		
29°_ 00′					50		
	.4874				40		
	.4899				30		
	.4924				20		
	.4950	.8689			10		
		.8675	.5735	1./43/			
200 001	0.5000	0.8660			60° 00′		
• • • • • • • • • • • • • • • • • • • •			.5812		50		
			.5851		40		
				1.6977	30		
_				1.6864	20		
ı				1.6753	10		
			0.4000	1 6643	59° 00		
					50		
10	.5175	.8557		1	40		
20	.5200	.8542			30		
30	.5225	.8526			20		
40	.5250	.8511			10		
50	.5275	.8496	-6208	1.0107			
	Cos	Sin	C-4	Tan	Degree		

Table XXVIII. Natural Trigonometric Functions—(Cont'd)

Degrees	Sin	Cos	Tan	Cot					
32° 00′	0.5299	0.8480	0.4040						
10	.5324	.8465	0.6249	,					
20	.5348	.8450	.6289	1					
30	.5373	.8434	.6330	1,	40				
40	.5398		.6371	1.5697	30				
50	.5422	.8418	.6412	1.5597	20				
		.8403	.6453	1.5497	10				
33° 00′ 10	0.5446	0.8387	0.6494	1.5399	57° 00'				
20	.5471	.8371	.6536	1.5301	50				
	.5495	.8355	.6577	1.5204	40				
30	.5519	.8339	.6619	1.5108					
40	.5544	.8323	.6661	1.5013	30				
50	.5568	.8307	.6703	1.4919	20 10				
34° 00′	0.5592	0.8290	1	1	1				
10	.5616	.8274	0.6745	1.4826	56° 00'				
20	.5640	.8258	.6787	1.4733	50				
30	.5664	.8241	.6830 1.4641 .6873 1.4550 .6916 1.4460						
40	.5688			1.4550	30				
50	.5712	.8225		1.4460	20				
	1	.8208	.6959	1.4370	10				
35° 00′	0.5736	0.8192	0.7002	1.4281	==0 ==:				
10	.5760	.8175	.7046	1.4193	55° 00′				
20	.5783	.8158	.7089		50				
30	.5807	.8141	.7133	1.4106	40				
40	.5831	.8124		1.4019	30				
50	.5854	.8107	.7177 .7221	1.3934	20				
36° 00'	0.5070			1.3848	10				
10	0.5878	0.8090	0.7265	1.3764	54° 00′				
20	.5901	.8073	.7310	1.3680	50				
30	.5925	.8056	.7355	1.3597	40				
	.5948	.8039	.7400	1.3514	1				
40	.5972	.8021	.7445	1.3432	30				
50	.5995	.8004	.7490	1.3351	20 10				
37° 00′	.6018	.7986	.7536	1.3270	1 1				
10	.6041	.7969	.7581	1.32/0	53° 00′				
20	.6065	.7951	.7627		50				
30	.6088	.7934	.7673	1.3111	40				
40	.6111	.7916	I	1.3032	30				
50	.6134	.7898	.7720 .7766	1.2954	20				
38° 00'	0.4157			1.2876	10				
10	0.6157	0.7880	0.7813	1.2799	52° 00'				
20	.6180	.7862	.7860	1.2723	50				
30	.6202	.7844	.7907	1.2647	40				
	.6225	.7826	.7954	1.2572	30				
40	.6248	.7808	.8002	1.2497	20				
50	.6271	.7790	.8050	1.2423	10				
39° 00′	0.6293	0.7771	0.8098	1.2349					
10	.6316	.7753	.8146		51° 00′				
20	.6338	.7735	.8195	1.2276	50				
30	.6361	.7716		1.2203	40				
40	.6383	.7698	.8243	1.2131	30				
50	.6406	.7679	.8292 .8342	1.2059	20				
			.0342	1.1988	10				
	Cos	Sin							

Degrees	Sin	Cos	Tan	Cot	
40° 00′	0.6428	0.7660	0.8391	1.1918	50° 00′
10	.6450	.7642	.8441	1.1847	50
20	.6472	.7623	.8491	1.1778	40
30	.6494	.7604	.8541	1.1708	30
40	.6517	.7585	.8591	1.1640	20
50	.6539	.7566	.8642	1.1571	10
41° 00′	0.6561	0.7547	0.8693	1,1504	49° 00′
10	.6583	.7528	.8744	1.1436	50
20	.6604	.7509	.8796	1.1369	40
30	.6626	.7490	.8847	1.1303	30
40	.6648	.7470	.8899	1.1237	20
50	.6670	.7451	.8952	1.1171	10
42° 00′	0.6691	0.7431	0.9004	1.1106	48° 00′
10	.6713	.7412	.9057	1.1041	50
20	.6734	.7392	.9110	1.0977	40
30	.6756	.7373	.9163	1.0913	30
40	.6777	.7353	.9217	1.0850	20
50	.6799	.7333	.9271	1.0786	10
43° 00′	0.6820	0.7314	0.9325	1.0724	47° 00′
10	.6841	.7294	.9380	1.0661	50
20	.6862	.7274	.9435	1.0599	40
30	.6884	.7254	.9490	1.0538	30
40	.6905	.7234	.9545	1.0477	20
50	.6926	.7214	.9601	1.0416	10
44° 00′	0.6947	0.7193	0.9657	1.0355	46° 00′
10	.6967	.7173	.9713	1.0295	50
20	.6988	.7163	. 9 770	1.0235	40
30	.7009	.7133	.9827	1.0176	30
40	.7030	.7112	.9884	1.0117	20
50	.7050	.7092	.9942	1.0058	10
45° 00′	0.7071	0.7071	1.0000	1.0000	45° 00′
	Cos	Sin	Cot	Tan	Degrees

Table XXVIII. Natural Trigonometric Functions—(Cont'd)

75. BINARY NUMBERS

(A) Binary Digits

In the binary system of numbers, there are only two digits —0 and 1. All numbers are written as successive powers of 2. Actually, in the decimal system, all numbers are written as successive powers of 10, although we don't normally think of them in this way. For example, decimal 3487 is actually:

$$3 \times 10^{3} = 3000$$

$$4 \times 10^{2} = 400$$

$$8 \times 10^{1} = 80$$

$$7 \times 10^{0} = 7$$

$$3487$$

With binary numbers, a like system is used except the base (radix) is 2 instead of 10. For example, the binary numbers corresponding to decimal numbers 0 through 10 are 0, 1, 10, 11, 100, 101, 111, 1000, 1001, 1010. Each number is written as a succession of powers of 2. For example, binary 1010 actually means:

$$1 \times 2^3 = 8$$
$$+1 \times 2^1 = 2$$
$$10$$

The powers of 2, from 0 to 20, are given in Table XXIX. Thus, to write a number above decimal 1,048,056 using binary numbers requires a minimum of 21 digits!

Power	Decimal	Power	Decimal	Power	Decimal
20	1	27	128	214	16,384
21	2	2 ⁸	256	215	32,768
22	4	2 ⁹	512	21 ^G	65,536
2 ³	8	210	1,024	217	131,072
24	16	211	2,048	218	262,144
25	32	212	4,096	219	524,288
2 ⁶	64	213	8,192	2 ²⁰	1,048,576

Table XXIX. Powers of 2

(B) Conversion

To convert from binary to decimal or from decimal to binary, you could use Table XXIX and compute the equivalent in the other numbering system as was done in the previous section. However, there are simpler methods. To convert from decimal to binary, successively divide the decimal number by 2. Write down a 1 if there is a remainder and a 0 if not, until the division gives a 0. For example, to convert decimal 22 to binary:

$$\begin{array}{ccc} 2)22 \\ 2)11 & R = 0 \\ 2) \overline{5} & R = 1 \\ 2) \overline{2} & R = 1 \\ 2) \overline{1} & R = 0 \\ \hline 0 & R = 1 \end{array}$$

The least significant figure is at the top; thus, the binary number corresponding to decimal 22 is 10110.

To convert from binary to decimal, take the first binary digit, double it, and add your answer to the second digit. Write this sum under the second digit. Then double this number, add it to the third digit, and write the sum under the third digit. Continue this process up to and including the last digit, as follows:

The number under the last digit (45) is the decimal equivalent of binary 101101.

(C) Addition

Binary addition has only four rules:

Following these rules, any binary number can be added. Thus:

$$\frac{1011}{110}$$

$$\frac{110}{10001}$$

To simplify the carry when 1 + 1 = 10, place the carry under the next digit. Then add the partial total and the carries, as follows:

$$\begin{array}{r}
111101 \\
10110 \\
\hline
101011 \\
1 1 \\
\hline
1010011
\end{array}$$

(D) Subtraction

Binary numbers can be subtracted directly, as follows:

$$\frac{-1111}{1000}$$

However, a simpler method is to complement the subtracted number and add. In the binary system, a number is

complemented by merely changing all 0's to 1's and all 1's to 0's and adding 1 to the final digit. Thus:

$$\frac{1111}{-0111}$$
 complemented $\frac{1111}{+1001}$

The first digit in the answer is disregarded. Hence, the answer is 1000 (decimal 8), the same as before.

(E) Multiplication

Binary multiplication is similar to decimal multiplication. All products are the same as in decimal multiplication. That is:

$$0 \times 0 = 0$$
$$1 \times 0 = 0$$
$$1 \times 1 = 1$$

To multiply 1011 by 101:

$$\begin{array}{r}
1011 \\
0101 \\
\hline
1011 \\
0000 \\
1011 \\
\hline
110111
\end{array}$$

(F) Division

Binary division is similar to decimal division. Thus, to divide 1101001 by 101:

76. FUNDAMENTALS OF BOOLEAN ALGEBRA

Boolean algebra is based on symbolic logic, which states that an idea must be either true or false—it can be nothing else. The symbols A, B, and C are used to designate the various conditions (or computer inputs). Two connectives—AND and OR—express the relationship between two statements.

OR is the logical equivalent of a parallel switch circuit. That is, a statement is true if any switch is closed, or if they are all closed. OR is symbolized by a + sign. Thus, "A OR B" is written "A + B."

AND is the logical equivalent of a series switch circuit—all switches must be closed to satisfy the condition. AND is symbolized by a multiplication sign $(A \cdot B)$ or no sign at all. For example, $A \cdot B$ and AB both mean A AND B. The various symbols are given in Table XXX. Table XXXI summarizes the various logical statements, explains their meanings, and shows the equivalent switch circuit for the statement.

Table XXX. Basic Rules of Symbolic Logic

Symbol	Logic	Switch	Meanin g	Circuit
1	True	Closed	The statement is true, the circuit is closed.	
0	False	Open	The statement is false, the circuit is open.	
•	Series	A and B	A is in series with B.	A B
+	Parallel	A or B	A is in parallel with B.	A B B
A or A'	Not A		Opposite of A (If A = 0, $\overline{A} = 1$; if A = 1, $\overline{A} = 0$).	

Logic	Meaning	Circuit
0.0 = 0	An open in series with an open is open.	
0•1 = 0	An open in series with a closed is open.	0000
1•1 = 1	A closed in series with a closed is closed.	-0+0-0+0
$A \cdot \overline{A} = 0$	A switch in series with its negation is open.	
0+0=0	An open in parallel with an open is open.	
0 + 1 = 1	An open in parallel with a closed is closed.	
1+1=1	A closed in parallel with a closed is closed.	
A + Ā = 1	A switch in parallel with its negation is closed.	A Ā

Table XXXI. Summary of Logical Statements

77. COMMON LOGARITHMS

The logarithm of a quantity is the power to which a given number (base) must be raised in order to equal that quantity. Thus, any number may be used as the base. The most common system is the base 10. Logarithms with the base 10 are known as common, or Briggs, logarithms; they are written log₁₀, or simply log. When the base is omitted, the base 10 is understood.

A common logarithm of a given number is the number which, when applied to the number 10 as an exponent, will produce the given number. Thus, 2 is the common logarithm of 100, since 10^2 equals 100; 3 is the logarithm of 1000, since 10^3 equals 1000, etc. From this we can see that the logarithm of any number except a whole number power of 10 consists of a whole number and a decimal fraction.

(A) Characteristic of a Logarithm

The whole-number portion of a logarithm is called the characteristic. The characteristic of a whole number, or of

a whole number and a fraction, has a positive value equal to one less than the number of digits preceding the decimal point. The characteristic of a decimal fraction has a negative value equal to one more than the number of zeros immediately following the decimal point. The characteristics of numbers between .0001 and 99,999 are:

Numbers	Characteristic
.0001 to .0009	-4
.001 to .009	-3
.01 to .09	-2
.1 to .9	-1
1 to 9	0
10 to 99	1
100 to 999	2
1,000 to 9,999	3
10,000 to 99,999	4

(B) Use of Logarithm Table

The mantissa, or decimal-fraction portion, of a logarithm is obtained from Table XXXII. To find the mantissa for the logarithm of any number, locate the first two figures of the number in the left-hand column (N); then, in the column under the third figure of the number, the mantissa for that number will be found.

For example, to find the logarithm of 6673, first locate 66 in the left-hand column (N); then follow across to the column numbered 7. The mantissa for 667 (.8241) is located at this point. The characteristic for the logarithm of 6673 is 3. Therefore, the logarithm of 6670 is 3.8241. For most computations, greater accuracy will not be required.

If accuracy to four places is desired, the columns labeled *Proportional Parts* may be used. These columns list the numbers to be added to the logarithm to obtain four-place accuracy. In the foregoing, we obtained the logarithm for 6670 (3.8241), but we wanted the logarithm for 6673; therefore, we use the *proportional parts* column to find the proportional part for 3. This is 2. Therefore, the logarithm for 6673 is 3.8241 plus .0002, or 3.8243.

The mantissa of a logarithm is usually positive, whereas a characteristic may be either positive or negative. The total logarithm is the sum of the mantissa and the characteristic.

Thus, the mantissa of .0234 is .3692, and the characteristic is -2. The total logarithm is -2 + .3692, or -1.6308. A negative logarithm is difficult to use; therefore, it is more convenient to convert the logarithm to a positive number. This is possible by adding 10, or a multiple thereof, to the characteristic when it is negative, and compensating for this by indicating the subtraction of 10 from the entire logarithm. Thus, the logarithm of .0234 would be written 8.3692 - 10, since -2 + .3692 equals 8 + .3692 - 10. This logarithm may now be used like any other positive logarithm, except that the -10 must be considered in determining the characteristic of the answer.

(C) Antilogarithms

An antilogarithm (abbreviated antilog or log^{-1}) is a number corresponding to a given logarithm. To find an antilog, locate in the logarithm table the mantissa closest to that of the given logarithm. Record the number in the N column directly opposite the mantissa located, and annex to this the number on the top line immediately above the mantissa. Next determine where the decimal point is located, by counting off the number of places indicated by the characteristic. Starting between the first and second digits, count to the right if the characteristic is positive, and to the left if it is negative. If greater accuracy is desired, the $proportional\ parts$ columns of the logarithm table can be used, in the same manner described in the foregoing for finding the mantissa.

To find the antilog of 3.4548, locate 4548 in the table. Then read the first two figures of the antilog from the N column (28) and the third figure directly above the mantissa (5). Thus, the three figures of the antilog are 285. Locate the decimal point by counting off three places to the right, from the point between the 2 and the 8, to obtain 2850.0—the antilog of 3.4548.

In the foregoing example, if the logarithm had been -2 + .4548, the procedure would have been the same except for the location of the decimal point. The decimal point in this example would be located by starting at the point between the 2 and the 8, and counting two places to the left to obtain 0.0285—the antilog of -2 + .4548.

(D) Multiplication

Numbers are multiplied by adding their logarithms and finding the antilog of the sum. For example, to multiply 682×497 , proceed as follows:

$$\log N = \log 682 + \log 497$$

$$\log 682 = 2.8338$$

$$+ \log 497 = \underline{2.6964}$$

$$\log N = \overline{5.5302}$$
antilog 5.5302 = 339,000.

To multiply $.02 \times .03 \times .5$, proceed as follows:

$$\log N = \log .02 + \log .03 + \log .5$$

$$\log .02 = -2 + .3010 = 8.3010 - 10$$

$$+ \log .03 = -2 + .4771 = 8.4771 - 10$$

$$+ \log .5 = -1 + .6990 = 9.6990 - 10$$

$$\log N = 26.4771 - 30$$

$$= -4 + .4771$$
antilog $-4 + .4771 = .0003$

(E) Division

Numbers are divided by subtracting the logarithm of the divisor from the logarithm of the dividend, and finding the antilog of the difference. For example, to divide 39,200 by 27.2, proceed as follows:

$$\log N = \log 39,200 - \log 27.2$$

$$\log 39,200 = 4.5933$$

$$-\log 27.2 = \underbrace{1.4346}_{00}$$

$$\log N = 3.1587$$
antilog 3.1587 = 1441

To divide .3 by .007, proceed as follows:

$$\log N = \log .3 - \log .007$$

$$\log .3 = -1 + .4771 = 9.4771 - 10$$

$$-\log .007 = -3 + .8451 = \underline{7.8451 - 10}$$

$$\log N = \underline{1.6320 - 0}$$
antilog 1.6320 = 42.86

(F) Raising to Powers

A given number can be raised to any power by multiplying the logarithm of the given number by the power to which the number is to be raised, and finding the antilog of the product. For example, to raise 39.7 to the third power, proceed as follows:

$$\log N = \log 39.7 \times 3$$

 $\log 39.7 = 1.5988$
 $\log N = 1.5988 \times 3$
 $= 4.7964$
antilog $4.7964 = 62,570$

(G) Extracting Roots

Any root can be extracted from a given number by dividing the logarithm of the given number by the index of the root, and finding the antilog of the quotient. For example, to extract the cube root of 149, proceed as follows:

$$\log N = \log 149 \div 3$$

 $\log 149 = 2.1732$
 $\log N = 2.1732 \div 3$
 $= 0.7244$
antilog $0.7244 = 5.301$

Table XXXII. Common Logarithms

													P	ropor	tional	Parts	5		
N	0	1	2	3	4	5	6	7	8	9	1	2	3	4	5	6	7	8	9
					0170	0212	0253	0294	0334	0374	4	8	12	17	21	25	29	33	37
10	0000	0043	0086	0128	0170		0645	0682	0719	0755	4	8	-11	15	19	23	26	30	34
11	0414	0453	0492	0531	0569	0607	1004	1038	1072	1106	3	7	10	14	17	21	24	28	31
12	0792	0828	0864	0899	0934	0969	1335	1367	1399	1430	3	6	10	13	16	19	23	26	29
13	1139	1173	1206	1239	1271	1303	1644	1673	1703	1732	3	6	9	12	15	18	21	24	27
14	1461	1492	1523	1553	1584	1614	1044	10/3						11	14	17	20	22	25
15	1761	1790	1818	1847	1875	1903	1931	1959	1987	2014	3	6	8	lii	13	16	18	21	24
16	2041	2068	2095	2122	2148	2175	2201	2227	2253	2279	3	5	7	10	12	15	17	20	22
17	2304	2330	2355	2380	2405	2430	2455	2480	2504	2529	2	5		9	12	14	16	19	21
18	2553	2577	2601	2625	2648	2672	2695	2718	2742	2765	2	5	7	9	11	13	16	18	20
19	2788	2810	2833	2856	2878	2900	2923	2945	2967	2989	. 2	4	7	9	''		1		1
17	2/00	2010		}			3139	3160	3181	3201	2	4	6	8	11	13	15	17	19
20	3010	3032	3054	3075	3096	3118		3365	3385	3404	2	4	6	8	10	12	14	16	18
21	3222	3243	3263	3284	3304	3324	3345	3560	3579	3598	2	4	6	8	10	12	14	15	17
22	3424	3444	3464	3483	3502	3522	3541	3747	3766	3784	2	4	6	7	9	11	13	15	17
23	3617	3636	3655	3674	3692	3711	3729	3927	3945	3962	2	4	5	7	9	11	12	14	16
24	3802	3820	3838	3856	3874	3892	3909	3927	Į.	Į.	1		_	-	9	10	12	14	13
	3979	3997	4014	4031	4048	4065	4082	4099	4116	4133	2	3	5	7	8	10	111	13	l i
25	1	4166	4183	4200	4216	4232	4249	4265	4281	4298	2	3	5	7	1 -	9	111	13	l i
26	4150	4330	4346	4362	4378	4393	4409	4425	4440	4456	2	3	5	6	8	9	111	12	l i
27	4314	4487	4502	4518	4533	4548	4564	4579	4594	4609	2	3	5	6	8		10	12	li
28	4472	4487	4654	4669	4683	4698	4713	4728	4742	4757	1	3	4	6	7	9	10		1
29	4624	4039	4054				1057	4871	4886	4900	1	3	4	6	7	9	10	11	1.
30	4771	4786	4800	4814	4829	4843	4857	5011	5024	5038	l i	3	4	6	7	8	10	11	1
31	4914	4928	4942	4955	4969	4983	4997	5145	5159	5172	l i	3	4	5	7	8	9	11	1
32	5051	5065	5079	5092	5105	5119	5132	5276	5289	5302	li	3	4	5	6	8	9	10	1
33	5185	5198	5211	5224	5237	5250	5263		5416	5428	li	3	4	5	6	8	9	10	1
34	5315	5328	5340	5353	5366	5378	5391	5403	3410	3420	+ ÷	+	+-	+	5	6	7	8	
	+						6	7	8	9	1	2	3					1 3	
N	0	1	2	3	4	5		1 '						Prop	ortion	ai rai	T 1 5		

Table XXXII. Common Logarithms—(Cont'd)

N	0	١,	2	3										Propo	rtion	l Dar	-	_	
		<u> </u>			4	5	6	7	8	9	1	2	3	4	5	6	7	8	9
35	5441	5453	5465	5478	5490	5502	5514	5527	5539	5551	١,	2	4	+-	1	<u> </u>	 	-	-
36	5563	5575	5587	5599	5611	5623	5635	5647	5658	5670	;	2	4	5	6	7	9	10	11
37	5682	5694	5705	5717	5729	5740	5752	5763	5775	5786	;	2	3		6	7	8	10	11
38	5798	5809	5821	5832	5843	5855	5866	5877	5888	5899	;	2	3	5	6	7	8	9	10
39	5911	5922	5 9 33	5944	5955	5966	5977	5988	5999	6010	l i	2	3	4	6 5	7 7	8	9	10
40	6021	6031	6042	6053	6064	6075	6085	6096	6107	6117	,	2	3		1	1 -	-	1	'
41	6128	6138	6149	6160	6170	6180	6191	6201	6212	6222	;	2	3	4	5	6	8	9	10
42	6232	6243	6253	6263	6274	6284	6294	6304	6314	6325	1 ;	2	3	4	5	6	7	8	9
43	6335	6345	6355	6365	6375	6385	6395	6405	6415	6425	1 :	2	3	4	5	6	7	8	9
44	6435	6444	6454	6464	6474	6484	6493	6503	6513	6522	li	2	3	4	5	6	7	8 8	9
45	6532	6542	6551	6561	6571	6580	6590	6599	6609	6618	1	2	3	'	-	-] -	1
46	6628	6637	6646	6656	6665	6675	6684	6693	6702	6712	;	2	3	4	5	6	7	8	9
47	6721	6730	6739	6749	6758	6767	6776	6785	6794	6803	1 ;	2	3	4	5	6	7	7	8
48	6812	6821	6830	6839	6848	6857	6866	6875	6884	6893	;	2	3	4	5	5	6	7	8
49	6902	6911	6920	6928	6937	6946	6955	6964	6972	6981	l i	2	3	4	4	5	6	7	8
50	6990	6998	7007	7016	7024	7033	7042	7050	7059	7067	١,	2	-			-	•		_
51	7076	7084	7093	7101	7110	7118	7126	7135	7143	7152	;	2	3	3	4	5	6	7	8
52	7160	7168	7177	7185	7193	7202	7210	7218	7226	7235	;	2			4	5	6	7	8
53	7243	7251	7259	7267	7275	7284	7292	7300	7308	7316	;	2	2 2	3	4	5	6	7	7
54	7324	7332	7340	7348	7356	7364	7372	7380	7388	7396	li	2	2	3	4	5 5	6	6	7
55	7404	7412	7419	7427	7435	7443	7451	7459	7466	7474	;	-	-	-	·	-			_
56	7482	7490	7497	7505	7513	7520	7528	7536	7543	7551	;	2	2	3	4	5	5	6	7
57	7559	7566	7574	7582	7589	7597	7604	7612	7619	7627		2	2	3	4	5	5	6	7
58	7634	7642	7649	7657	7664	7672	7679	7686	7694	7701		2	2	3	4	5	5	6	7
59	7709	7716	7723	7731	7738	7745	7752	7760	7767	7774	1	1	2 2	3	4 4	4	5	6	7 7
N	0	1	2	3	4	5		-			1	2	3	4	5	6	7	8	9
			_	٠ '	7	9	6	7	8	9				ropor					

Table XXXII. Common Logarithms—(Cont'd)

				-	Table :	XXXII.	Commo	n Logai	rithms—	-(Cont'd	1)								-
													Pre	oport	ional	Parts			
N	0	1	2	3	4	5	6	7	8	9	1	2	3	4	5	6	7	8	6
N							7005	7832	7839	7846	1	1	2	3	4	4	5	6	6
60	7782	7789	7796	7803	7810	7818	7825 7896	7903	7910	7917	1	1	2	3	4	4 4	5	6	6
	7853	7860	7868	7875	7882	7889		7973	7980	7987	1	1	2	3	3		5	5	6
61	7924	7931	7938	7945	7952	7959	7966	8041	8048	8055	1	1	2	3	3	4	5	5	6
62	7993	8000	8007	8014	8021	8028	8035	8109	8116	8122	1	1	2	3	3	4	2	٦	•
63		8069	8075	8082	8089	8096	8102	8109			1	٠, ١	2	3	3	4	5	5	6
64	8062	0007	- 1		8156	8162	8169	8176	8182	8189	!		2	3	3	4	5	5	6
65	8129	8136	8142	8149		8228	8235	8241	8248	8254	!		2	3	3	4	5	5	6
66	8195	8202	8209	8215	8222	8293	8299	8306	8312	8319		!		3	3	4	4	5	6
67	8261	8267	8274	8280	8287	8357	8363	8370	8376	8382	1 1	!	2	2	3	4	4	5	6
68	8325	8331	8338	8344	8351		8426	8432	8439	8445	1	'	2	2	"	1		_	
69	8388	8395	8401	8407	8414	8420	0420	'		8506	1	1 1	2	2	3	4	4	5	6
07	1			8470	8476	8482	8488	8494	8500		;	i	2	2	3	4	4	5	5
70	8451	8457	8463	8531	8537	8543	8549	8555	8561	8567	1 :	1 ; 1	2	2	3	4	4	5	5
71	8513	8519	8525		8597	8603	8609	8615	8621	8627	1 ;	1 ; 1	2	2	3	4	4	5	5
72	8573	8579	8585	8591	8657	8663	8669	8675	.8681	8686	;	1 ;	2	2	3	4	4	5	5
73	8633	8639	8645	8651		8722	8727	8733	8739	8745	1 1	1 '		-	-		١.	-	5
74	8692	8698	8704	8710	8716		1	0701	8797	8802	1	1	2	2	3	3	4	5	5
' '		2754	8762	8768	8774	8779	8785	8791	8854	8859	1 1	1	2	2	3	3	4	1 -	5
75	8751	8756	8820	8825	8831	8837	8842	8848		8915	l i	1	2	2	3	3	4	4	
76	8808	8814	8876	8882	8887	8893	8899	8904	8910	8971	li	l i	2	2	3	3	4	4	5
77	8865	8871		8938	8943	8949	8954	8960	8965	9025	l i	l i	2	2	3	3	4	4	5
78	8921	8927	8932	8993	8998	9004	9009	9015	9020	9023	'		-		1 2	3	4	4	5
79	8976	8982	8987	0773		1	9063	9069	9074	9079	1	1	2	2	3	3	4	4	5
00	9031	9036	9042	9047	9053	9058		9122	9128	9133	1	1	2	2	3		4	4	5
80	9085	9090	9096	9101	9106	9112	9117	9175	9180	9186	1	1	2	2	3	3		4	5
81	,	9143	9149	9154	9159	9165	9170	9227	9232	9238	1	1	2	2	3	1 -	4	4	5
82	9138	9196	9201	9206	9212	9217	9222		9284	9289	1	1	2	2	3	3	4	4	1
83	9191	9196	9253	9258	9263	9269	9274	9279	7204	1,207	+	2	3	4	5	6	7	8	9
84	7243	1240			+			7	8	9	-	1 2				nal Pa	rts		
, N	0	1	2	3	4	5	6	1 ′						rrop	0.110				
N								orld Radio History											

Table XXXII. Common Logarithms—(Cont'd)

N	0	,	2	3	4	5		7		8 9	l	Proportional Parts								
	L	<u> </u>					•	′	•	,	1	2	3	4	5	6	7	8	9	
85	9294	9299	9304	9309	9315	9320	9325	9330	9335	9340	1	ı	2	2	3	3	4	4	5	
86	9345	9350	9355	9360	9365	9370	9375	9380	9385	9390	li	l i	2	2	3	3	4	4	5	
87	9395	9400	9405	9410	9415	9420	9425	9430	9435	9440	Ιò	l i	l ī	2	2	3	3	4	4	
88	9445	9450	9455	9460	9465	9469	9474	9479	9484	9489	l o	ĺi	Ιi	2	2	3	3	4	Δ	
89	9494	9499	9504	9509	9513	9518	9523	9528	9533	9538	ő	i	ī	2	2	3	3	4	4	
90	9542	9547	9552	9557	9562	9566	9571	9576	9581	9586	0	ı	1	2	2	3	3	4	4	
91	9590	9595	9600	9605	9609	9614	9619	9624	9628	9633	اة	i	Ιi	2	2	3	3	4	4	
92	9638	9643	9647	9652	9657	9661	9666	9671	9675	9680	0	i	Ιi	2	2	3	3	4	4	
93	9685	9689	9694	9699	9703	9708	9713	9717	9722	9727	0	i	l i	2	2	3	3	4	4	
94	9731	9736	9741	9745	9750	9754	9759	9763	9768	9773	ō	i	i	2	2	3	3	4	4	
95	9777	9782	9786	9791	9795	9800	9805	9809	9814	9818	0	ı	l ı	2	2	3	3	4	4	
96	9823	9827	9832	9836	9841	9845	9850	9854	9859	9863	0	i	Ιi	2	2	3	3	4	4	
97	9868	9872	9877	9881	9886	9890	9894	9899	9903	9908	l ŏ l	i	l i	2	2	3	3	4	4	
98	9912	9917	9921	9926	9930	9934	9939	9943	9948	9952	o l	i	i	2	2	3	3	4	4	
99	9956	9961	9965	9969	9974	9978	9983	9987	9991	9996	ő	i	i	2	2	3	3	3	4	
N	0	,	2	3	4	5	6	7	8	9	1	2	3	4	5	6	7	8	9	
.,	"			3	4	3	°	′	8	7			Р	ropo	rtiona	l Part	s			

Miscellaneous

78. POWER CONSUMPTION OF HOME ELECTRICAL EQUIPMENT

The power consumption for many items of home electrical equipment by an average family is given in Table XXXIII. The approximate usage of each item is also listed where applicable.

Table XXXIII. Power Consumption of Home Electrical Equipment

ltem	Approx. Kwh per Month	Remarks
DI I (() ()	15	8 hr. per day (used 7 mo.)
Blanket (automatic) Clock	11/2	, , , , , , , , , , , , , , , , , , ,
Coffee Maker	15	25 hr. per mo.
Dishwasher	25	11/2 washings per day
Dryer (clothes)	50	10 hr. per mo. (family of 4)
Fan (10-inch)	1	25 hr. per mo.
Food Freezer	40	8 cu. ft.
Garbage Disposal Unit	3/4	4 min. per day
Iron	6	12 hr. per mo.
Ironer	10	10 hr. per mo. (family of 4)
Lighting	65	
Mixer	3/4	5 hr. per mo.
Oil Furnace (not including cir-		(000 500 (()))
culator fan)	30	(200-500 KW-hours per year)
Radio	10	130 hr. per mo.
Range	90	(Family of 4)
Refrigerator	22	8 cu. ft.
Roaster	12	16 hr. per mo.
Sandwich Grill	4	5 hr. per mo.
Sewing Machine	1	
Television	18	90 hr. per mo.
Toaster	3	3 hr. per mo.
Vacuum Cleaner (upright)	21/4	6 hr. per mo.
Vacuum Cleaner (tank)	31/4	6 hr. per mo.
Washer (wringer-type)	2	12 hr. per mo. (family of 4)
Washer (automatic)	3	12 hr. per mo. (family of 4)
Water Heater	350	(Family of 4)
Water Heater	350	(raminy or 4)

79. TEMPERATURE CONVERSION

The nomograph in Fig. 145 can be used to convert from degrees Fahrenheit to degrees Celsius (or vice versa) for any temperature between absolute zero and 540°F. (281°C). The term Celsius was officially adopted, in place of centigrade, by international agreement in 1948; however, acceptance of the new term has been slow in Europe, and still slower in the United States. Actually, Celsius and centigrade scales differ slightly—the Celsius scale is based on 0° at the triple point of water (.01°C), and centigrade has 0° at the freezing point of water. For all practical purposes, though, the two terms are interchangeable.

Two absolute temperature scales are also in use. The Fahrenheit absolute scale is called the Rankine—0° Rankine equals -459.67° Fahrenheit. The Celsius absolute scale is the Kelvin—0° Kelvin equals -273.16° Celsius (or centigrade).

The following formulas can be used to convert from any temperature to the other:

Temperature Nomograph

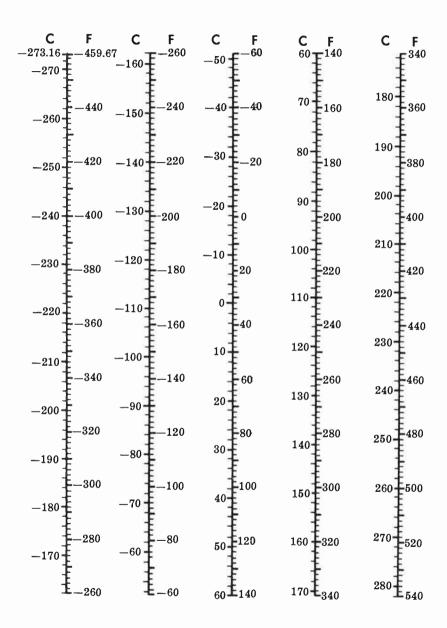


Fig. 145

80. CHARACTERISTICS OF THE ELEMENTS

A list of all the known elements (103) is given in Table XXXIV. The symbol, atomic number, and atomic weight are included for each element. Where known, the melting and boiling point of each element is also given. A value shown in parentheses indicates the value is approximated; the asterisk (*) indicates the mass number of the longest-lived of the known available forms of the element, usually synthetic; < indicates the value may be lower; > indicates the value may be higher.

Table XXXIV. Characteristics of the Elements

Element	Symbol	Atomic Number	Atomic Weight	Melting Point °C	Boiling Point °C
Actinium	Ac	89	*227		
Aluminum	AI	13	26.97	660.1	1800
Americium	Am	95	*243	000.1	1800
Antimony	Sb	51	121.76	630.5	1380
Argon	A	18	39.944	—189.2	— 185.7
Arsenic	As	33	74.91	(820)	615
Astatine	At	85	*210	(020)	013
Barium	Ba	56	137.36	850	1140
Berkelium	Bk	97	*249	0.50	1140
Beryllium	Be	4	9.013	1350	(1500)
· ·	00	7	7.013	1330	(1500)
Bismuth	Bi	83	209.00	271.3	1450
Boron	В	5	10.82	2300	2550
Bromine	Br	35	79.916	-7.2	58.8
Cadmium	Cq	48	112.41	320.9	766
Calcium	Ca	20	40.08	810	1170
Californium	Cf	98	*249		
Carbon	С	6	12.01	>3500	(4200)
Cerium	Ce	58	140.13	640	1400
Cesium	Cs	55	132.91	28	670
Chlorine	CI	17	35.457	-101.6	—34.7
Chromium	Cr	24	52.01	1615	2200
Cobalt	Co	27	58.94	1492	3000
Copper	Cu	29	63.54	1083	2300
Curium	Cm	96	247	1000	2500
Dysprosium	Dy	66	162.46		
Einsteinium	E	99	*254		
Erbium	Ēr 1	68	167.2		
Europium	Eu	63	152.0		
Fermium	Fm	100	*255		
Fluorine	F	9	19.00	-223	-187
Francium	Fr	87	*223		
Gadolinium	Gd	64	156.9		
Gallium	Ga	31	69.72	29.7	>1400
Germanium	Ge	32	72.60		>1600
Gold	Au	79	197.0	958.5	(2700)
- July	70	/7	197.0	1063	2600

Table XXXIV. Characteristics of the Elements—(Cont'd)

Element	Symbol	Atomic Number	Atomic Weight	Melting Point °C	Boiling Point °C
Halfnium Helium	Hf He	72 2 67	178.6 4.003 164.94	1500 <-271.4	(>3200) -268.94
Holmium Hydrogen Indium	Ho H In	1 49	1.0080	—259.14 155	-252.8 >1450
lodine Iridium Iron Krypton Lanthanum	l Ir Fe Kr La	53 77 26 36 57	126.91 192.2 55.85 83.8 138.92	113.5 2443 1533 —169 826	184.35 (>4800) 3000 —151.8 1800
Lawrencium Lead Lithium Lutetium Magnesium	Lw Pb Li Lu Mg	103 82 3 71 12	207.21 6.940 174.99 24.32	327.4 186 ———————————————————————————————————	1620 >1200
Manganese Mendelevium Mercury Molybdenum Neodymium	Mn Mv Hg Mo Nd	25 101 80 42 60	54.94 *256 200.61 95.95 144.27	1260 —38.87 2620 840	356.9 3700
Neon Neptunium Nickel Niobium Nitrogen	Ne Np Ni Nb N	10 93 28 41 7	20.183 *237 58.69 92.91 14.008	-248.67 639 1453 2500 -209.86	2900 3200 195.81
Nobelium Osmium Oxygen Palladium Phosphorus	No Os O Pd P	102 76 8 46 15	251 190.2 16.000 106.7 30.975	2700 218.4 1552 44.1	(>5300) -183 2200 280
Platinum Plutonium Polonium Potassium Praseodymium	Pt Pu Po K Pr	78 94 84 19 59	195.23 242 210 39.100 140.92	1769 ————————————————————————————————————	760
Promethium Protactinium Radium Radon Rhenium	Pm Pa Ra Rn Re	61 91 88 86 75	*145 *231 226.05 222 186.31	960 —110 (3000)	1140
Rhodium Rubidium Ruthenium Samarium Scandium	Rh Rb Ru Sm Sc	45 37 44 62 21	102.91 85.48 101.1 150.43 44.96	1960 38.5 2500 >1300 1200	>2500 700 >2700 (2400)
Selenium Silicon Silver Sodium Strontium	Se Si Ag Na Sr	34 14 47 11 38	78.96 28.09 107.880 22.997 87.63	220 1420 960.8 97.5 800	688 2600 1950 880 1150

Table	XXXIV.	Characteristics	of	the	Elements—	-(Cont	' d)
	, , , , , , , ,	endidetensiles	٠.		-1011101113	100111	4/

Element	Symbol	Atomic Number	Atomic Weight	Melting Point °C	Boiling Point °C
Sulfur	s	16	32.066	113-119	444.6
Tantalum	Ta	73	180.95	3005	(>4100)
Technetium	Tc	43	*99		
Tellurium	Te	52	127.61	452	1390
Terbium	Tb	65	158.93	327	
Thallium	TI	81	204.39	303.5	1650
Thorium	Th	90	232.12	1845	>3000
Thulium	Tm	69	168.94		3500
Tin	Sn	50	118.70	231.9	2260
Titanium	Ti Ti	22	47.90	1820	(>3000)
Tungsten	l w	74	183.92	3380	5900
Uranium	l u	92	238.07	1133	
Vanadium	V	23	50,95	1735	(3000)
Xenon	Xe	54	131.3	-140	109.1
Ytterbium	Yb	70	173.04		
Yttrium	Y	39	88.92	1490	(2500)
Zinc	Zn	30	65.38	419.47	907
Zirconium	Zr	40	91.22	1750	>2900

81. MEASURES AND WEIGHTS

(A) Linear Measure

1 inch	= 1000 mils	1 furlong = 40 rods
1 hand	= 4 inches	1 statute mile = 8 furlongs
1 foot	= 12 inches	1 statute mile = 5,280 feet
1' yard	= 3 feet	1 nautical mile = 6076.1 feet
1 fathor	= 6 feet	1 nautical mile = 1.1508 statute miles
1 rod	51/2 yards	1 league - 3 miles

(B) Square Measure

1 sq. foot	= 144 sq. inches	1 township	= 6 miles sq. (36 sq. miles)
1 sq. yard	= 9 sq. feet	l acre	=160 sq. rods
1 sq. rod	== 301/4 sq. yards	l acre	== 43,560 sq. feet
1 section (of land)	= 1 sq. mile	1 sq. mile	== 640 acres

(C) Volume Measure

1 cu. foot = 1,728 cu. inches	1 cu. yard = 27 cu. feet
1 US gallon 2	31 cu inchae

(D) Liquid Measure

1 pint	= 4 gills	1 barrel	= 311/2 gallons
1 quart	= 2 pints	1 hogshea	d = 2 barrels (63 gallons)
1 gallon	= 4 quarts	1 tun	= 252 gallons
1 barrel (petroleum	n) = 42 gallons		

(E) Dry Measure

```
1 bushel = 4 pecks = 2150.419 cu. in.
1 quart == 2 pints == 67.2006 cu. in.
                                       1 barrel = 2.381 bushels = 7056 cu. in.
1 peck = 8 quarts = 537.605 cu. in.
```

(F) Avoirdupois Weight

(For other than drugs, gold, silver, etc.)

```
I hundredweight (cwt.) == 4 quarters
1 dram (dr.) == 27.3437 grains*
                                                              == 20 cwts.
                                       I ton (tn.)
1 ounce (oz.) == 16 drams
                                                             == 2000 pounds
1 pound (lb.) == 16 ounces
                                        1 short ton
                                                              == 2240 pounds
                                        I long ton
1 quarter = 25 pounds
```

1 pound avdp. = 7000 grains = 453.59 grams = 1.2153 pounds troy

(G) Troy Weight

```
(For gold, silver, etc.)
```

I ounce troy (oz.t.) == 20 pennyweights 1 pennyweight (dwt.) == 24 grains*

1 pound troy (lb.t.) = 12 ounces troy = 240 pennyweights = 5760 grains

(H) Apothecaries' Weight

(For drugs)

```
I dram apoth. (dr. ap.) == 3 scruples
1 scruple (s. ap.) == 20 grains*
```

I ounce apoth. (oz. ap.) == 8 drams apoth.

I pound apoth. (lb. ap.) = 12 ounces apoth. = 96 drams apoth. = 288 scruples == 5760 drams

82. METRIC EQUIVALENTS

(A) Length

```
= 2.5400 centimeters (cm.)
                                    1 inch
1 centimeter = 0.3937 inch
                                                   = 0.3048 meter
                                    1 foot
           == 3.2808 feet
1 meter
                                                   = 0.9144 meter
                                    1 yard
            = 1.0936 yards
1 meter
                                    1 mile (statute) == 1.6093 kilometers (km.)
1 kilometer = 0.6214 miles
```

(B) Area

```
1 sq. inch = 6.4516 sq. cm.
1 sq. cm. = 0.1550 sq. inch
                                          1 sq. foot = 0.0929 sq. meter
1 sq. meter = 10.7639 sq. feet
                                          1 sq. yard == 0.8361 sq. meter
1 sq. meter = 1.1960 sq. yards
                                                     == 0.4047 hectare
1 hectare = 2.4710 acres
                                          1 sq. mile = 2.5900 sq. km.
1 sq. km. = 0.3861 sq. mile
```

^{*} The grain is the same in avoirdupois, troy, and apothecaries' weights.

(C) Volume

 1 cu. cm.
 = 0.0610 cu. inch
 1 cu. inch = 16.3872 cu. cm.

 1 cu. meter = 35.3145 cu. feet
 1 cu. foot = 0.0283 cu. meter

 1 cu. meter = 1.3079 cu. yards
 1 cu. yard = 0.7646 cu. meter

(D) Capacity

1 liter = 61.0250 cu. inches
1 liter = 0.9081 quart (dry)
1 liter = 0.0353 cu. feet
1 liter = 0.2642 gallon (U.S.)
1 liter = 0.0284 bushel (U.S.)
1 liter = 1000.027 cu. cm.
1 liter = 1.056 quarts (liquid)
1 liter = 3.9081 quart (dry)
1 liter = 2.2046 pounds of water @ 4° C
1 cu. inch = 0.0164 liter
1 cu. foot = 28.3162 liters
1 gallon = 3.7853 liters
1 bushel = 35.2383 liters

(E) Weight

1 gram	== 15.4324 grains	1 grain	== 0.0648 gram
1 gram	= 0.0353 ounce avdp.	1 ounce (avdp.) = 28.3495 grams
1 kg.	= 2.2046 pounds avdp.		.) == 0.4536 kg.
1 kg.	= 0.0011 ton (short)	1 ton (short)	== 907.1848 kg.
1 ton (metric	c) = 1.1023 tons (short)	1 ton (short)	= 0.9072 ton (metric)
1 ton (metric	:) == 0.9842 ton (long)	1 ton (long)	= 1.0160 ton (metric)

(F) Pressure

1 kg. per sq. cm. = 14.223 lbs. per sq. inch
1 lb. per sq. inch = 0.0703 kg. per sq. cm.
1 kg. per sq. meter = 0.2048 lb. per sq. foot
1 lb. per sq. foot = 4.8824 kg. per sq. meter
1 kg. per sq. cm. = 0.9678 normal atmosphere
1 normal atmosphere = 1.0332 kg. per sq. cm.
1 normal atmosphere = 1.01325 bars
1 normal atmosphere = 14.696 lbs. per sq. inch

83. WINDS

Table XXXV. Wind Designations

Designation	Miles per hour	Designation	Miles per hour
Calm	Less than 1	Moderate gale	32 to 38
Light air	1 to 3	Fresh gale	39 to 46
Light breeze	4 to 7	Strong gale	47 to 54
Gentle breeze	8 to 12	Whole gale	55 to 63
Moderate breeze	13 to 18	Storm	64 to 72
Fresh breeze	19 to 24	Hurricane	Above 72
Strong breeze	25 to 31		

84. WEIGHT OF WATER

1 cubic inch	= .0360 pound	1 imperial gallon	== 10.0 pounds
12 cubic inches	= .433 pound	11.2 imperial gallons	= 112.0 pounds
1 cubic foot	= 62.4 pounds	224 imperial gallons	= 2240.0 pounds
1 cubic foot	= 7.48052 U.S. gallons	1 U.S. gallon	= 8.33 pounds
1.8 cubic feet	== 112.0 pounds	13.45 U.S. gallons	= 112.0 pounds
35.96 cubic feet	== 2240.0 pounds	269.0 U.S. gallons	= 2240.0 pounds

85. HYDRAULIC EQUATIONS

Lbs. per sq. in. = $0.434 \times \text{head}$ of water in feet Head in feet = $2.31 \times \text{lbs}$, per sq. inch

Approximate loss of head due to friction in clean iron pipes is:

$$\frac{0.02 \times L \times V^2}{64.4D}$$
 ft.

where,

L is the length of pipe in feet,

V is the velocity of flow in foot-pounds per second,

D is the diameter in feet.

In calculating the total head to be pumped against, it is common to consider this value as being equal to the sum of the friction head and the actual head.

$$Horsepower of waterfall = \frac{62 \times A \times V \times H}{33,000}$$

where,

A is the cross section of water in square feet,

V is the velocity of flow in foot-pounds per minute,

H is the head of fall in feet.

86. MISCELLANEOUS

(A) Falling Object

The speed acquired by a falling object is determined by the formula:

$$V = 32t$$

where,

V is the velocity in feet per second, t is the time in seconds.

The distance traveled by a falling object is determined by the formula:

$$d = 16t^{2}$$

where.

d is the distance traveled in feet, t is the time in seconds.

(B) Speed of Sound

The speed of sound through air at 0°C. is usually considered to be 1087.42 feet per second, and at normal temperature, 1130 feet per second. The speed of sound through any given temperature of air is determined by the formula:

$$V = \frac{1087 \sqrt{(273 + t)}}{16.52}$$

where,

V is the speed in feet per second, t is the temperature in degrees Celsius.

(C) Cost of Operation

The cost per hour of operation of an electrical device is determined by the formula:

$$C = \frac{Wtc}{1000}$$

where.

C is the cost per hour of operation, W is the wattage of the device, t is the time in hours, c is the cost per kilowatt hour of electricity.


(D) Conversion of Matter Into Energy

The conversion of matter into energy (Einstein's theorem) is expressed by:

$$E = mc^2$$

where,

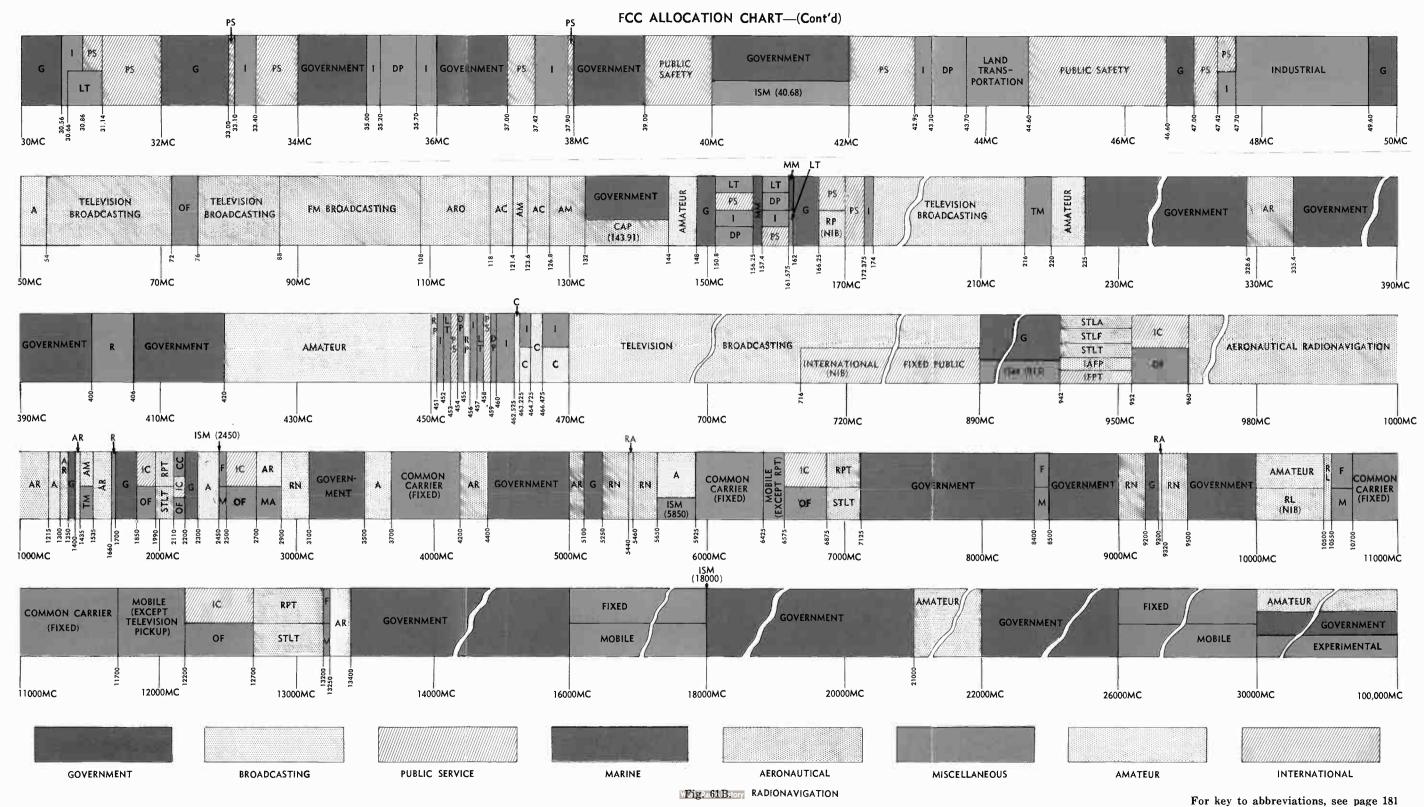E is the energy in ergs, m is the mass of the matter in grams, c is the speed of light in centimeters per second ($c^2 = 9.10^{20}$).



Key to Abbreviations for FCC Allocation Chart

A-Amateur

AC-Airdrome Control

AF—Aeronautical Fixed

AFF-Aviation (Flight Test and Aeronautical Fixed Only)

AM---Aeronautical Mobile

AR-Aeronautical Radionavigation

ARO—Aeronautical Radionavigation (Omnidirectional Radio Range)

C-Citizens Radio

CC—Common Carrier

CAP-Civil Air Patrol (Land and Mobile)

DP—Domestic Public

F-Fixed

FA-Fixed (Alaska)

FAP-Fixed (Alaska and Puerto Rico)

G—Government

II—Industrial

IAF---International Aeronautical Fixed

IAFP-International Aeronautical Fixed (Alaska, Hawaii, and U.S. Possessions)

IB-International Broadcasting

IC-International Control

IFP-International Fixed Public

IFPT-International Fixed Public (Puerto Rico and Virgin Islands)

ISM---Industrial, Scientific, and Medical

Equipment

LT-Land Transportation

M-Mobile

MA-Meteorological Aids

MM-Maritime Mobile

MMCP-Maritime Mobile Coastal Tele-

phony

MMCT---Maritime Mobile Coastal Tele-

graphy

MMDCP-Maritime Mobile Distress and Calling (Telephony)

19 377

MMDCT-Maritime Mobile Distress and Calling (Telegraphy)

MMIP-Maritime Mobile (Intership Telephony)

MMSCP-Maritime Mobile Ship Calling (Telephony)

MMSCT-Maritime Mobile Ship Calling (Telegraphy)

MMSP-Maritime Mobile Ship (Telephony)

MMST---Maritime Mobile Ship (Telegraphy)

MMT-Maritime Mobile (Telegraphy)

MRDF-Maritime Radionavigation (Radio Direction Finding)

(NIB)—Noninterference Basis

OF-Operational Fixed

P---Police

PS-Public Safety

R-Radiosonde

RA-Racon

RL—Radiolocation

RN-Radionavigation

RNAL—Radionavigation (Aeronautical and

Land)

RP-Remote Pickup

RPT-Remote Pickup (Television)

SF-Standard Frequency

STLA---Studio Transmitter Link (AM Broadcast)


STLF-Studio Transmitter Link

(FM Broadcast)

STLT---Studio Transmitter Link (Television)

TM-Telemetering

 Allocations Shown Are Current Through November, 1961.



INDEX

A	Area—cont'd
A scale, slide rule, 142	of hexagon, 147 of octagon, 147
Abbreviations, electronic, 83-84	of parallelogram, 147
frequency bands, 78	of pentagon, 147
metric prefixes, 57	of rectangle, 146
semiconductor terms, 84-87	of rectangular solid, 149
Absolute zero, 172	of sector, 148
Absorption factor, 82 AC, Ohm's law for, 33 AC circuits, power factor of, 35 power in, 33-34	of segment, 148
AC circuits, power factor of, 35	of sphere, 149 of square, 146
power in, 33-34	of trapezium, 147
AC plate resistance, vacuum tube, 114	of trapezoid, 147
Acres, 52, 55, 176, 177	of triangle, 146
Actinium, 174	symbol for, 82
Addition, using binary numbers, 159 using powers of 10, 138	Arsenic, 174
Admittance, abbreviation for, 84	Argon, 174 Astatine, 174
definition of, 22	ATA, 66
formula for, 23	Atmospheres, normal, 178
Air, dielectric constant of, 51	Atomic number, 174
Algebra, Boolean, 160-162	Atomic weight, 174
Algebraic equations, transposition of,	Attenuation, coaxial line, 43
144-145 Algebraic operations, 144-145	Attenuation characteristics, constant-K fil-
Allocations, FCC, 78	ters, 120-121 m-derived filters, 123-124
Alloys, resistance of, 111	Attenuation constant, 82
Alpha, of transistor, 115	Attenuation constant, 82 Attenuator, bridged-T, 130-131
Alphabet, Greek, 81-82	characteristics of, 127-128
Alternating current, abbreviation for, 83	formulas, 127-134 H-type, 129
Ohm's law for, 33-34	H-type, 129
Aluminum, characteristics of, 174 resistance of, 111	L-type, 131-132 ladder, 134
AM broadcast stations, 65	lattice, 133
AM carrier, percentage of modulation,	O-type, 133
44-45	pi-type, 132
sideband power, 45	purpose of, 127
Amateur bands, 71 Amateur operator privileges, 70-71	T-type, 129-130 taper pad, 130
examination requirements, 71	U-type, 133
Amber, dielectric constant of, 51	Audio frequency, abbreviation for, 83
Americium, 174	Audio frequency, abbreviation for, 83 spectrum, 74, 79
Ammeter, abbreviation for, 83	Audio output transformer, color code for,
shunts, 40-41	88
Ampere, abbreviation for, 83 -hours, 52	Automatic frequency control, 83 Automatic gain control, 83
-turns, per cm., 52	Automatic volume control, 83
per in., 52	Average voltage or current, 34
Amperes, 52	Avoirdupois weight, 177
Amplification factor, formula for, 114	_
symbol for, 82	В
Amplifier, stage gain of, 114 Amplitude modulation, 44-45, 72	B scale, slide rule, 142
abbreviation for, 83	Bakelite, dielectric constant of, 51
AND gate, 161	Band-rejection filter, 122-123
symbol for, 93	Bandpass filter, 122
Angles, 82-83	Bands, amateur, 71
Angstrom units, 52	radio-frequency spectrum, 74-78
Angular phase displacement, 82 Angular velocity, 83	Barium, 174 Barrel, 176, 177
Antenna, abbreviation for, 83	Bars, 52, 178
symbols for, 94	Battery, 93
Antilogarithms, 164	Beam-power tube, symbol for, 91
Antimony, 174	Beat-frequency oscillator, 83
Apothecaries' weight, 177 Apparent power, 35	Beeswax, dielectric constant of, 51
Area, abbreviation for, 83	Berkelium, 174 Beryllium, 174
metric equivalents, 177	Beta, of transistor, 115
of circle, 147	Binary numbers, 157-160
of circular ring, 148	addition of, 159
of cone, 149	conversion to decimal, 158-159
of cube, 149	division of, 160
of cylinder, 149 of ellipse, 148	multiplication of, 160 subtraction of, 159-160

Binistor, 92
Bipolar voltage limiter, 92
Bismuth, 174
Blanket, power consumption of, 171
Boolean algebra, 160-162
Boron, 174
Brass, resistance of, 111
Breakdown diode, 92
Bridged-T attenuator, 130-131
Briggs logarithms, 160
Brightness, definition of, 105
Broadcast, 83
Bromine, 174
Btu, 52, 54, 55
per hour, 52, 56
per minute, 53, 56
Burst, color, 107
Bushels, 52, 177, 178

C

C scale, slide rule, 141 Cable, coaxial, characteristics of, 95-96 Cadmium, 174 Calcium, 174 Californium, 174 Calories, gram, 52 Cambric, dielectric constant of, 51 Candles, per sq. cm., 54
per sq. in., 54
Capacitance, 33
series, impedance of, 30
total, 17-18 Capacitive reactance, 84 Capacitive reactance, 84 Capacitor, abbreviation for, 83 change stored in, 18 color codes, 88, 89-90 energy stored in, 18 parallel-plate, 18 Q-factor of, 22 reactance of, 25 series, voltage across, 19 symbols for, 93 Capacity, metric equivalents, 178 Carbon, 174 Cartridges, phono, 93 Cathode-ray tubes, 91 Cell, 93 Celluloid, dielectric constant of, 51 Cellulose acetate, dielectric constant of, 51 Celsius, 172-173 abbreviation for, 83 conversion of, 52, 172-173 Centi-, 57-58 Centin, 5/-58
Centigrade, 172-173
abbreviation for, 83
conversion of, 52, 172-173
Centimeter, 177
abbreviation for, 83
conversion of, 53, 55 conversion of, 53, 55
Cerium, 174
Cesium, 174
Chains, 52, 54
Characteristic curve, vacuum tubes, 99
Characteristic impedance, coaxial line, 43
definition of, 43
parallel-conductor line, 14
Characteristics, of elements, 174-176
of logarithm, 162-163
Charge, of R-C circuit, 35-36
Charge stored, in capacitor, 18
Chemical elements, characteristics of,
174-176 Chlorine, 174 Chord, of segment, 148 Chrominance signal, 106-107 Chromium, 174 CHU, 64 CI scale, slide rule, 141-142 Circle, area of, 147 circumference of, 147 Circuit breaker, 94 Circular mils, 52, 56

Circular ring, area of, 148 Circumference, of circle, 147 of ellipse, 148 Citizens-band radio, 67-68 Class-A operation, vacuum tubes, 99 Class-AB operation, vacuum tubes, 100 Class-B operation, vacuum tubes, 100-101 Class-C operation, vacuum tubes, 101 Classes, of vacuum-tube operation, 99-101 Classification, radio frequencies, 78 types of emission, 72-74 Cleaner, vacuum, power consumption of, Clearance-drill sizes, 110 Clock, power consumption of, 171 Clothes dryer, power consumption of, Coaxial cable, characteristics of, 95-96 formulas for, 43 Cobalt, 174 Code, international, 81 time signals, 59-64 Codes color, capacitors, 88, 89-90 resistor, 88, 89-90 transformer, 87-88 Coefficients, 82 Coffeemaker, power consumption of, 171 Coil; also see inductor coupling coefficient of, 21 Q-factor of, 22 symbols for, 93 Coil windings, multilayer, 117-118 single-layer, 117 Siligic-layer, 11: Color codes, capacitors, 88, 89-90 resistors, 88, 89 transformer, 87-88 Color TV, light properties of, 104-107 Combining network 199 Color TV, light properties of, 104-10 Combining network, 129 Commercial operator licenses, 68-69 requirements for, 69-70 Common logarithms, 162-170 antilogarithms, 164 characteristic of, 162-163 division using, 165-166 mantissa of, 163 multiplication using, 165 nowers. raising to using, 166 powers, raising to using, roots, extracting using, 166 table of, 167-170 use of, 163-164 Computer symbols, 93 Conductance, 23 abbreviation for, 83 Ohm's law formulas with, 24 Cone, area of, 148 volume of, 149 Configurations, impedance of, 25, 29-33 phase angle of, 29-33 Constant-k filters, 118, 120-123 Constants, mathematical, 135 dielectric, 51 Conversion, binary to decimal, 158-159 decimal to binary, 158-159 matter into energy, 180 Conversion chart, frequency-wavelength, 41-43 Conversion factors, 52-56 Conversion table, metric prefixes, 57-58 Co-ordinates, 82, 83 Copper, 174
resistance of, 111
Copper-wire table, 111-113
Cost of operation, electrical appliance, 180
Coulombs, 52 Coupled inductance, 20-21 Coupling coefficient, coils, 21 symbol for, 82 Crystals, 93 Cube, area of, 149 of number, using slide rule, 143 volume, of, 149 Cube root, using slide rule, 143 Cubic centimeters, 52, 178

Cubic foot, 52, 55, 176, 178 Cubic inch, 52, 178 Cubic meter, 52, 53, 178 Cubic yard, 52, 176, 178 Current, abbreviation for, 83 AC circuit, 33 average, 34 peak, 34 peak-to-peak, 34 rms, 34 Current gain, in decibels, 46-50 Current ratio, 46-50 Curium, 174 Cycles, 52 Cycles per second, 83, 84 Cylinder, surface area, of, 149 volume of, 149

D scale, slide rule, 141 db, 46-47 db loss, attenuators, 128-129 dbk, 47 dbm. 47 dbrap, 47 dbv, 47 dbvg, 47 dbw, 47 DCF77, 66 DC meter formulas, 39-41 DC power, 11 Deci-, 57-58 Decibel, abbreviation for, 83 equations, 46 reference levels, 46-47 table, 47-50 Decibels, conversion to nepers, 55 Decimal equivalents, 136
Decimal expressions, as powers of 10, 137 Decrement, 82 Degrees, 53, 55 per second, 55 Deka-, 57-58 Delta connection, three-phase power, 116 Density, 82 Determinant, 82 Dial lamps, 101-102 Dielectric constant, abbreviation for, 83 of materials, 51 symbol for, 82 Dielectric flux, 83 Diode, crystal, 92 tube, 91 Direct current; also see DC abbreviation for, 83 Ohm's law for, 11 Dishwasher, power consumption of, 171 Disposal, power consumption of, 171 Dividing network, 129 Division, using binary numbers, 160 using logarithms, 165-166 using powers of 10, 138-139 using slide rule, 141, 142 Dominion Observatory, 64-65 Dram, 177 Drill sizes, 110 Dry measure, 176 Dryer, clothes, power consumption of, 171 Durite, dielectric constant of, 51 Dynaquad, 92 Dynes, 53, 55 per sq. cm., 55 Dysprosium, 174

E

Ear, human, frequency range of, 74 Ebonite, dielectric constant of, 51 Effective radiated power, 83 Efficiency, 82 Einsteinium, 174

Einstein's theorem, 180 Electric intensity, 82 Electrical, conductivity, 82 equipment, power consumption of, 171 susceptibility, 83 Electromotive force, 83 Electron-eye tube, 91 Electronic, abbreviations, 83-84 schematic symbols, 88, 91-94 Elements, characteristics of, 174-176 commercial operator license, 68-69 Ellipse, area of, 148 circumference of, 148
Emission, types of, 72-74
Energy, definition of, 24
stored, in capacitor, 18 in inductor, 21 units, formulas for, 24 Equations, decibel, 46 hydraulic, 179 quadratic, 146 transposition of terms in, 144-145 Erbium, 174 Ergs, 53 per second, 56 Europium, 174 Examination requirements, amateur operator, 70-71 commercial operator, 69-70 Exponents, determination of, 137 fractional, 146 laws of, 145-146 negative, 145

F

Fahrenheit, 172-173 abbreviation for, 83 conversion of, 52, 53 Falling object, distance traveled, 180 speed of, 179 Fan, power consumption of, 171 Farad, 83 Faradays, 53 Farads, 53 Fathom, 53, 176 FCC allocations, 78 Feet, 52-56, 176, 17 per minute, 54, 55 per second, 54, 55 Fermium, 174 FFH, 66 Fiber, dielectric constant of, 51 Filters, constant-k, 118, 120-123 m-derived, 123-127 Fluorine, 174 FM broadcast stations, frequency and power tolerances, 65, 67 Foot, 176 Foot-lbs., 53, 54 per minute, 53, 56 per second, 53, 56 Formica, dielectric constant of, 51 Formulas, AC plate resistance, 114 admittance, 22-23 ammeter shunt, 40-41 amplification factor, 114 amplitude modulation, 44, 45 attenuator, 127-134 band-rejection filters, 122-123 bandpass filter, 122 bridged-T attenuator, 130-131 capacitance, 17-18 capacitive reactance, 24 charge stored, in capacitor, 18 coaxial line, 43 coil windings, 117 conductance, 23 constant-k filters, 118, 120-123 cost of operation, electrical appliance. 180 coupled inductance, 20-21 coupling coefficient, 21

Formulas—cont'd current, 11, 13-14	Formulas—cont'd
Current, 11, 13-14 DC meter, 39-41	voltage
decibels 46	across series capacitors, 19 multiplier, DC meter, 39
Einstein's theorem, 180	regulation, 38
Einstein's theorem, 180 energy stored, in capacitor, 18 in inductor, 21	watt-hours, 24
in inductor, 21	watt-hours, 24 wavelength and frequency, 41
energy units, 24	r ractional exponents, 146
falling object, 179-180 filters, 118, 120-127	Fractions, decimal equivalents of, 136
frequency and wavelength 41	powers of, 145 Francium, 174
frequency and wavelength, 41 frequency modulation, 45	Freezer, power consumption of, 171
geometric, 146-150	Freezer, power consumption of, 171 Frequencies, television channels, 74-75
H-type attenuator, 129	rrequency, abbreviation for, 83
high-pass filter, 121-122, 125, 127 horsepower of waterfall, 179	definition of, 41
hydraulic equations, 179	formula for, 41 modulation, 72-73
inductance, coupled, 20-21	abbreviation for, 83
mutual, 20	modulation index, 46
inductive reactance, 25	percentage of modulation, 45 musical notes, 74, 78 range, musical instruments, 74, 79
inductors, 19-20	musical notes, 74, 78
impedance, 25, 29-33 ratio, 38	resonant, 22
transformer windings, 38 Kirchhoff's laws, 13-14 L-section filter, 118, 120-122, 125-127	spectrum sudio- 74 79
Kirchhoff's laws, 13-14	spectrum, audio-, 74, 79 radio-, 74, 78 standard, 59-66
L-section filter, 118, 120-122, 125-127	standard, 59-66
D-type attenuator, 191-192	symbol for, 82
ladder-type attenuator, 134	tolerances, AM broadcast stations, 65
low-pass filters, 118, 120-121, 125-126	TV broadcast stations, 65
lattice-type attenuator, 133 low-pass filters, 118, 120-121, 125-126 m-derived filters, 123-127	FM broadcast stations, 65 TV broadcast stations, 67 Industrial Radio Service, 67
mensuration, 146-150	Citizens-band radio, 67-68
meter, DC, 39-41 modulation, AM, 44-45	-wavelength conversion chart, 41-43
FM, 45-46	Functions
percentage of, 44-45	trigonometric, 150-157 on slide rule, 140, 143-144
mutual conductance, 114	Furlong, 176
mutual conductance, 114 mutual inductance, 20 O-type attenuator, 133	Furnace, oil, power consumption of, 171
O-type attenuator, 133	Fuses, symbols for, 93
ohmmeter, 39-41 Ohm's law, 11	
AC circuits, 33	G
considering conductance, 24	G
considering conductance, 24 parallel circuit, impedance of, 25	Gadolinium, 174
parallel-conductor lines, 44	Gadolinium, 174 Gain, in decibels, 46-50
percentage of modulation, 44-45 phase angle, 33	transistor circuits, 115
pi-section filter, 118, 120-129, 125-127	Gallium, 174 Gallons, British imperial, 53, 179 U. S., 52, 53, 55, 176, 178 Garbage dispersal power consumption of
pi-section filter, 118, 120-122, 125-127 pi-type attenuators, 133	U. S., 52, 53, 55, 176, 178
	Carbage disposar, power consumption of,
DC circuits, 11 radiated, AM, 45 sideband, AM, 45	C (N 171
radiated, AM, 45	Gas-filled lamps, 102-104 Gas-filled tubes, symbols for, 91 Gausses, 53, 56
power factor, 35	Gausses 53 56
Q-factor, 22	GBR, 59, 66
radiated power, AM, 45	Geometric formulas, 146-150
reactance, capacitive, 24 inductive, 25	Geophysical alert, 64 Germanium, 174
	Germanium, 174
resistance, 11	Giga-, 57-58 Gilberts, 52
resonant frequency, 22 regulation, voltage, 38 series circuit, impedance of, 29 series-type chumeter, 41	Gills, 176
series circuit, impedance of, 29	Glass, dielectric constant of, 51
out too type ommitteer, tr	Glass, dielectric constant of, 51 Gold, characteristics of, 174
shunt-type ohmmeter, 39-40	resistance of, 111
sideband power, AM, 45 sound, speed of, 180	Grains, 53, 178 Gram-centimeters, 52
stage gain, 114	Gram-centimeters, 53 Grams, 53, 178
stored energy, in capacitor, 18 in inductor, 21	Grams, 53, 178 per cm., 53
in inductor, 21	per cu. cm., 53
susceptance, 23	Greek alphabet, 82-83 Greenwich Civil Time, abbreviation for, 83 Grill, power consumption of, 171
T-section filter, 118, 120-122, 125-127 T-type attenuator, 129-130	Greenwich Civil Time, abbreviation for, 83
taper-pads, 130	Ground, abbreviation for, 83
temperature conversion, 172-173	symbols for, 93
three-phase power, 116-117	Gutta Percha, dielectric constant of, 51
time constant, 36	·
transformer, 37-38 transistor, 114-116	TT
transistor, 114-116 transmission line, 43-44	H
transmission line, 43-44 trigonometric, 151	H-type attenuator, 129
turns ratio, transformer, 37-38	Halfnium, 175
U-type attenuator, 133	Hand, 176 HBN, 66
vacuum-tube, 114 voltage, 11, 13	HBN, 66 Headphones, 94
	ALLEMPHONES, 5%

Heads, screw, types of, 110-111
Heater, power consumption of, 171
Hectare, 177
Hecto-, 57-58
Helium, 175
Henries, abbreviation for, 83
conversion of, 53
Hexagon, area of, 147
High frequency, 83
High-pass filters, constant-k, 121-122
m-derived, 125, 127
Hogshead, 176
Holmium, 175
Horsepower, abbreviation for, 83
conversion of, 53, 56
hours, 52, 53, 54, 55
metric, 53
of waterfall, 179
Hue, definition of, 105
Hundredweight, 177
Hydraulic equations, 179
Hydrogen, 175
Hypotenuse, solving for, 143
Hysteresis, symbol for, 82

I

IAM, 66 IBF, 66 Iff transformer, color code for, 87 Impedance, 25, 29-33 abbreviation for, 84 AC circuit, 33 capacitive circuit, 29, 30, 31 characteristics, constant-k filter, 120-121 m-derived filters, 124-125 inductance and capacitance, 30, 31 inductive circuit, 29, 31 parallel circuit, 25 ratio, transformer, 38 resistance and capacitance, 30, 31, 32 resistance and inductance, 30, 31, 32 resistance inductance and capacitance, 30, 32 resistive circuit, 29, 30 series circuit, 29 transformer winding, 38 Imperial gallon, 179 Inches, 52-55, 176, 177 Inches per second, 83 Increment, 82 Index, modulation, 46 slide rule, 141 Indian-head test pattern, 96-99 Indium, 175 Inductance, abbreviation for, 83 coupled, 20-21 mutual, 20 series, impedance of, 29 total, 19-20 Inductive reactance, 84 Inductor; also see coil abbreviation for, 83 energy stored in, 21 energy stored in, 21 reactance of, 25 symbols for, 93 Industrial electronic symbols, 94 Industrial Radio Service, 67 Input resistance, transistor, 115 Intermediate frequency, abbreviation for, 83 International code, 81 International World Day Service, 64 Intrinsic impedance, 82 Iodine, 175 Iridium, 175 Iron, 175 electric, power consumption of, 171 resistance of, 111 Ironer, power consumption of, 171 Isolantite, dielectric constant of, 51 IWDS, 64

J

Jacks, 94 JJY, 66 Joules, 18 abbreviation for, 83 conversion of, 52, 53, 54, 56 definition of, 24

K

K-factor, attenuators, 128-129 K scale, slide rule, 143 Kelvin, 172 conversion of, 52 Keyboard, frequencies of notes, 74, 79 Kilo-, 57-58 Kilocycles, abbreviation for, 83 conversion of, 52 Kilograms, 53, 178 Kilogram calories, 52 per minute, 56
Kilograms per sq. meter, 53
Kilometers, 54, 177
per hour, 54, 55 Kilovolt ampere, abbreviation for, 83 Kilovolts, abbreviation for, 83 conversion of, 56 Kilowatt hours, 54, 55 Kilowatts, abbreviation for, 83 conversion of, 53, 56 Kirchhoff's laws, 13-14 Knots, 54, 55 Krypton, 175

L L scale, slide rule, 144 L-section filter, 118, 120-122, 125-127 L-type attenuator, 131-132 Ladder-type attenuator, 134 Lamberts, 54 Lamps, gas-filled, 102-104 miniature, 101-102 symbols for, 93 Lanthanum, 175 Lattice-type attenuator, 134 Lawrencium, 175 Law Ohm's, AC circuits, 33 considering conductance, 24 DC, 11 nomograph, 12-13 Kirchhoff's, 13-14 Laws of exponents, 145-146 Lead, 175 Leagues, 54, 176 Length, abbreviation for, 83 metric equivalents, 177 Level, reference, 46-47 Licenses, commercial operator, 68-69 Light, properties of, 104 Light years, 54 Lighting, home, power consumption of, 171 Linear measure, 176 Lines per sq. cm., 53 Lines per sq. in., 53 Links, 54 Liquid measure, 176 Lithium, 175 Liters, 52, 54, 178 Loge, 54 Log scale, slide rule, 144 Logarithms common, 162-170 antilogarithms, 164 characteristic of, 162-163 division using, 165-166 mantissa of, 163 multiplication using, 165 powers, raising to with, 166

1

Logarithms-cont'd common roots, extracting using, 166 table of, 167-170 use of, 163-164 Naperian, 82 Logic, symbolic, 160-162 Logical statements, summary of, 162 LOL, 66 Loss, in decibels, 46-50 Low frequency, 83 Low pass filter, constant-K, 118, 120-121 m-derived, 125, 126 Lucite, dielectric constant of, 51 Lumens per sq. ft., 54 Luminance signal, 106 Lutetium, 175 Lux, 54

M

m-derived filters, 123-127 Magnesium, 175
Magnetic flux, 83
Magnetic flux density, 83
Machine screw sizes, 110 Manganese, 175
Manganese nickel, 111
Mantissa, of logarithms, 163
Mathematical constants, 135 Mathematical symbols, 135-136 Maxwells, 54, 56 Measures, 176-177 Medium frequency, 84 Mega-, 57-58 Megacycle, abbreviation for, 84 conversion of, 52 Megohm, abbreviation for, 84 conversion of, 55 Mendelevium, 175 Mensuration formulas, 146-150 Mercury, 175 Metallic rectifier, 92 Metals, resistance of, 111 Meter, 177 Meter, abbreviation for, 83 DC, formulas for, 39-41 bc, formulas for, 59-41 symbols for, 93 Meters, 53, 54 per minute, 54 Metric equivalents, area, 177 capacity, 178 length, 178 pressure, 178 volume, 178 weight, 178 Metric prefixes, 57-58 Mhos, 54 Mica, dielectric constant of, 51 Micarta, dielectric constant of, 51 Micro-, 57-58 Microampere, abbreviation for, 84 conversion of, 52, 55 Microfarad, abbreviation for, 84 conversion of, 53, 54 Microhenry, abbreviation for, 84 conversion of, 53, 55 Micromhos, 54 Micromicroamperes, 52 Micromicrofarad, abbreviation for, 84 conversion of, 53, 54, 55 Micromicro-ohms, 55 Microns, 55 Micro-ohms, 55 Microphone, symbols for, 93 Microvolts, 55 Microwatts, 56 Mile, nautical, 54, 176 statute, 53, 54, 176, 177 Miles per hour, 55 Milli, 57-58 Milliampere, abbreviation for, 83 conversion of, 52, 55 Millifarads, 53

Millihenries, abbreviation for, 84 conversion of, 53, 55 Millimeter, abbreviation for, 84 conversion of, 55 Millimhos, 54 Milliohms, 55 Millivolts, abbreviation for, 84 conversion of, 55, 56 Milliwatts, abbreviation for, 84 conversion of, 56 Mils, 53, 54, 55, 176 Miniature lamps, 101-102 Minimum loss, attenuators, 128 Minutes, angular, 55 Mixer, power consumption of, 171 MSF, 59, 66 Modulated continuous wave, 84 Modulation, amplitude, 44-45, 72 frequency, 45-46 percentage of modulation, 45 index, 46 Molybdenum, characteristics of, 175 resistance of, 111 Morse code, 81 Motors, symbols for, 94 Movement, meter, determining resistance of, 39 Moving coil meter, 39 Moving coil meter, 39
Multiplication, using binary numbers, 160
using logarithms, 165
using powers of 10, 138, 139
using slide rule, 141, 142
Multiplier, voltage, DC meter, 39
Musical notes, frequency of, 74, 79
Mutual perdustrose abbuviction for 82 Mutual conductance, abbreviation for, 83 formula for, 114 Mutual inductance, 20 abbreviation for, 83 Mycalex, dielectric constant of, 51 Myria-, 57-58

N

Nano-, 57-58 Naperian logarithms, 82 Natural logarithms, 82 Nautical mile, 176 NBA, 59, 66 Negative exponents, 145 Neodymium, 175 Neon, 175 Nepers, 55 Neptunium, 175 Neoprene, dielectric constant of, 51 Network, combining, 129 Newtons, 55 Nichrome, resistance of, 111 Nickel, characteristics of, 175 resistance of, 111 Niobium, 175 Nitrogen, 175 No connection, abbreviation for, 84 Nobelium, 175 Nomograph, Ohm's law, 12-13 parallel resistance, 15-17 parallel inductance, 20 relay rewinding, 107-108 resonant frequency, 22 series capacitance, 18 single-layer coils, 118-119 temperature conversion, 173 Normal atmospheres, 178 NOT gate, 93 Notes, musical, frequency of, 74, 79 Notes, musical, frequency of, 74 Numbers, as powers of 10, 137 atomic, 174 binary, 157-160 zero power of, 137 Nylon, dielectric constant of, 51

O-type attenuator, 133

Ostoron and of 147	
Octagon, area of, 147 Ohms, 55	Pounds, 53, 55, 56, 177, 178
international, 55	carbon oxidized, 55 of water, 55, 178
law, AC circuits, 33-34	per in., 53
considering conductance, 24 DC, 11	
nomograph, 12-13	per sq. ft., 53 per sq. in., 55 Poundals, 53, 55
per foot, 55	Poundals, 53, 55
per meter, 55 symbol for, 83	Power, abbreviation for, 84
Ohmmeter, series-type, 40	AC circuit, 33
shunt-type, 39-40	consumption, electrical equipment, 171 DC, 11
OMA, 66	factor, 35
Operator license, commercial, 68-70	abbreviation for 84
OR gate, 162 symbol for, 93	in decibels, 46-50 radiated, AM, 45
Osmium, 175	ratio, 46-50
Ounce inches, 53	sideband, AM carrier, 45
Ounces, 53, 55, 177, 178 Output resistance transistor circuits, 115	three-phase, 116-117 tolerances, AM broadcast stations, 65
Outside diameter, 84	EM broadenst stations, 65
Oxygen, 175	FM broadcast stations, 67 TV broadcast stations, 67
	industrial Radio Service, 67
P	Citizens Radio Service, 67-68
Г	transformer, color code for, 87 Powers, of fractions, 145
Pad, attenuator, 128	of 2, 158
Palladium, 175	of 10, 137-140
Paper, dielectric constant of, 51 Paraffin, dielectric constant of, 51	product of, 145 quotient of, 145
Parallel circuit, current through, 13-14	quotient of, 145 raising to, 166
Parallel circuit, current through, 13-14 Parallel circuit, impedance of, 25 Parallel conductor line of	Praseodymium, 175
a an electron ductor line, characteristic im-	Prefixes, metric, 57-58
pedance of, 44 Parallel resistance, nomograph for, 15-17	Pressure, metric equivalents, 178
Parallelogram, area of, 147	Primary colors, 105-106 Promethium, 175
Peak voltage or current, 34	Propagation constants, 82
Peak-to-peak, abbreviation for, 84	Propagation constants, 82 Propagation forecast, WWV and WWVH
voltage or current, 34 Peck, 177	03-04
Pennyweight 177	Protactinium, 175 Pulsed emissions, 73
Pentagon, area of, 147	- widea cirrissions, 10
Pentagon, area of, 147 Pentagon, area of, 147 Pentagrid converter, symbol for, 91 Pentode tube, symbol for, 91 Percentage of modulation 44	
Percentage of modulation, 44-45	Q
Permeability, symbol for, 82	Q-factor, 22
refineance, symbol for, x2	Q-signals, 80
Permittivity, symbol for, 82 Phase angle, 29-33	Quadrants, 55
AC circuit, 33-34	Quadratic equation, 146 Quarter, 177
capacitive circuit, 29, 30, 31	Quarts, 55, 176, 177, 178
inductance and capacitance, 31, 32 inductive circuit, 29, 31	Quartz, dielectric constant of, 51
resistance and canacitance 30 31 32	
resistance and capacitance, 30, 31, 32 resistance and inductance, 30, 31, 32	R
resistance inductance and canacitance	
30, 32 resistive circuit, 29, 30	Radians, 53, 55
Phase constant, 82	per second, 55 Radiated power 45
Phase difference, 83	Radiated power, 45 Radio, power consumption of, 171
Phono cartridges, 93	Radio Frequency, abbreviation for, 84
Phosphorus, 175 Phototube, 91 Picarion 61	choke coll, 84
I I-Section filter, IIX, IZU-IZZ 125-127	spectrum, 74, 78 Radium, 175
Pi-type attenuator, 132 Pico-, 57-58	Radon, 175
Pico-, 57-58 Picofarad, 55, 57	Range, power consumption of, 171
Picture carrier, TV channels, 75	Rankine temperature, 53, 172
Pints, 176	Ratio, current, 46-50 impedance, transformer, 38
conversion of, 55	power, 46-50
Plane trigonometry, 150 Plate resistance, AC, vacuum tube, 114 Platinum characteristics of 177	voltage, 46-50
Platinum, characteristics of, 175	Reactance, 24-28 abbreviation for, 84
resistance of, [1]	capacitive, 24
Plexiglass, dielectric constant of, 51	capacitive, 24 charts, 25, 26-28
Plugs, 94 Plutonium, 175	definition of, 24
P-N Diode, 92	inductive, 25 Reactive circuit, nower factor for 25
Polyethylene, dielectric constant of, 51	Reactive circuit, power factor for, 35 power in, 34
Polonium, 175	Reciprocal, using powers of 10, 139
Polystyrene, dielectric constant of, 51 Porcelain, dielectric constant of, 51	using slide rule, 141
Potassium, 175	Rectangle, area of, 146 Rectangular solid, area of, 148
Potentiometer, 93	volume of, 148

Reference levels, 46-47	Sarias aircuit impadance of 80
Refrigerator, nower consumption of 171	Series circuit, impedance of, 29 voltage drops around, 13
Refrigerator, power consumption of, 171 Regulation, voltage, 38	Series m-derived filters, 125-126
Relay, rewinding data, 107-108	70 7-volt line speaker connections 100
symbol for, 94	70.7-volt line, speaker connections, 109 Sewing machine, power consumption of,
Reluctance, 82	171
Reluctivity, 82	Sheet-beam tube, 91
Reluctivity, 82 Resistance, abbreviation for, 84	Shellac, dielectric constant of, 51
-capacitance circuit, time constant of,	Short wave, 84
36	Shunt m-derived filters, 126-127
copper-wire, 112-113	Shunts, ammeter, 40-41
external, gas-filled lamps, 102-104	Sideband power, AM carrier 45
-inductance circuit, time constant of, 36	Sideband power, AM carrier, 45 Signal standards, TV broadcasting,
measuring of, 39-40	74. 76-77
metals and alloys, 111	74, 76-77 Signals, Q, 80 Signals, "10," 81
parallel, 15	Signals, "10," 81
nomograph, 15-17	Silicon, 175
impedance of, 30	-controlled rectifier, 92
series, 14	Silicone, dielectric constant of, 51
impedance of, 29	Silver, characteristics of, 175
Resistive circuit, phase angle of, 34	resistance of, 111 Sine scale, slide rule, 143
power factor of, 35	Sine scale, slide rule, 143
power in, 34 Resistivity, 82	Single-layer coils, formulas for, 117
Resistivity, 82	nomograph, 118-119
Resistor, abbreviation for, 84	Sinusoidal voltage, 34
color codes, 88, 89	State, dielectric constant of, 51
symbols for, 93	Slide rule, operation of, 140-144
Resonance, formula for, 22	Sodium, 175
L-C circuit, 25	Solid angles, 83
Resonant circuit, power factor for, 35 power in, 34	Sound, speed of, 180 Sound carrier, TV channels, 75
Resonant frequency, formula for, 22	Speakers connection of 100 100
Revolutions per minute, 84	Speakers, connection of, 108-109 symbol for, 93
Rewinding, relays, 107-108	Specific quantity 82
Rewinding, relays, 107-108 Rhenium, 175	Spectrum color 104
Rhodium, 175	frequency, 74 78
Right triangle, solving for, 143	Specific quantity, 82 Spectrum, color, 104 frequency, 74, 78 Speed, of falling objects, 179
Right triangle, solving for, 143 Ring, area of, 148	of sound, 180
of circular cross section, surface area,	Sphere, area of, 149
150	volume of, 149
volume, 150	Square, area of, 146
of rectangular cross section, volume of,	Square centimeter, 52, 55, 177
150	Square centimeter, 52, 55, 177 Square foot, 52, 56, 176, 177 Square inch, 56, 177
Rms voltage or current, 34	Square inch, 56, 177
Roaster, power consumption of, 171 Rods, 55, 176	Sauare kilometer, 56, 177
Rods, 55, 176	Square measure, 176 Square meter, 52, 56, 177 Square mile, 52, 56, 176
Root, cube, using slide rule, 143	Square meter, 52, 56, 177
extracting, using logarithms, 166	Square mile, 52, 56, 176
of fraction, 146 of product, 146	Square millimeter, 56
source using slide rule 142 142	Square mils, 52, 56 Square rod, 176
square, using slide rule, 142-143 using powers of 10, 140	Square rod, 176
Root mean square, 84	Square root, using powers of 10, 140 using slide rule, 142-143 Square yard, 56, 176, 177
Rpm. 55, 56	Source verd 56 176 177
Rpm, 55, 56 Rps, 56	Squaring using noward of 10 140
Rubber, dielectric constant of, 51	Squaring, using powers of 10, 140 Standard frequency signals, 59-66
Rubidium, 175	Standard time signals, 59-66
Ruby mica, dielectric constant of, 51	Standards, television signal, 74, 76-77
Ruthenium, 175	Star connection, three phase power, 116
	Stations, standard, 59-66
	Statute mile, 176, 177
S	Steatite, dielectric constant of, 51
o	Stored energy, capacitor, 18
S scale, slide rule, 143-144	inductor, 21 Strontium, 175
Samarium, 175	Strontium, 175
Saturation, color, definition of, 105 Scalar potential, 83	Styrafoam, dielectric constant of, 51
Scalar potential, 83	Subtraction, using binary numbers, 159-160
Scales, slide rule, 140	using powers of 10, 138 Sulfur, 176
Scandium, 175	Sulfur, 176
Scanning frequencies, TV, 74 Schematic symbols, 88, 91-94	Summation, sign of, 82
Schematic symbols, 88, 91-94	Super-high frequencies, 84
Screw, machine, sizes of, 110	Surface charge density, 82
Screw heads, types of, 110-111	Susceptance, abbreviation for, 83
Secondary 84	formula for, 23
Scruple, 177 Secondary, 84 Seconds, abbreviations for, 84	Susceptibility, 82
conversion of, 55	Symbolic logic, 160-162
Section, 176	Symbols, atomic elements, 174-176 computer, 93
Sector, area of, 148	Greek alphabet, 81-82
Segment, area of, 148	mathematical 135-136
chord of, 148	mathematical, 135-136 schematic, 88, 91-94
Selenium, 175	semiconductors, 92
Semiconductor, symbols, 92	vacuum tube, 91
terms, abbreviations for, 84-87	Switches, 94

T	Tube, classes of operation, 99-101
T scale, slide rule, 144	vacuum, formulas for, 114 Tun, 176
T-section filter, 118, 120-122, 125-127 T-type attenuator, 129-130 Table, decibel, 47-50	Tuned radio frequency, 84
Table, decibel, 47-50	Tungsten, characteristics of, 176 resistance of, 111
Tangent scale, slide rule, 144 Tantalum, 176	Tunnel diode, 92 Turns ratio, transformer, 37-38
Tap-drill sizes, 110	TV, color, light properties of, 104-107 TV broadcast stations, frequency and
Taper pad, 130 Technetium, 176	TV broadcast stations, frequency and power tolerances, 67
Teflon, dielectric constant of, 51 Television: see TV	power tolerances, 67 TV Channel frequencies, 74-75
Television; sce TV Tellurium, 176	TV receivers, power consumption of, 171 TV signal standards, 74, 76-77
Temperature, abbreviation of, 84 conversion of, 172	Twin lead, characteristic impedance of, 44 2, powers of, 158
Systems of measurement 179	Types of emission, 72-74
Ten, powers of, 137-140 "10" signals, 81	\mathbf{U}
Tera-, 57-58 Terbium, 176	U-type attenuator, 133
Terms, transposition of, 144-145	Ultrahigh frequency, 84
Test pattern, interpretation of, 96-99 Tetrode tube, 91	Unit vector, 82 Uranium, 176
Thallium, 176 Theorem, Einstein's, 180	
Thorium, 176	V
Three-phase power formulas, 116-117 Thulium, 176	Vacuum cleaner, power consumption of,
Time, 84 Time constants, 35-37	Vacuum-tube, classes of operation, 99-101
symbol for, 82	symbols for, 91 formulas, 114
Time-phase displacement, 82 Time signals, standard, 59-66	formulas, 114 Vacuum-tube voltmeter, 84 Vanadium, 176
11n, 176	Varas, 56
Titanium, 176 Toaster, power consumption of, 171	Vaseline, dielectric constant of, 51 Velocity, of falling object, 179
Tolerance frequency, AM broadcast stations, 65	very nigh frequencies, 84
FM broadcast stations, 67	Vinylite, dielectric constant of, 51 Volt, 56, 84
Industrial Radio Service 67	-amperes, 35 Volt-ohm-milliampere, 84
Citizens Radio Service, 67-68 power, AM broadcast stations, 65	voltage, abbreviation for, 83
FM Droadcast stations 67	AC circuit, 33 across series capacitor, 19
TV broadcast stations, 67 Industrial Radio Service, 67	average 34
Citizens Radio Service, 67-68 Ton, conversion of, 53, 56	gain, in decibels, 46-50 multipliers, DC meters, 39
metric, 178	peak, 34 peak-to-peak, 34
metric, 178 U.S., 177, 178 Tonnes, 53, 56	ratio, 46-50 rms, 34
Torus, surface area, 150	Voltmeter, 84
volume of, 150 Total inductance, 19-20	Volume, metric equivalents, 178 of cone, 149
Township, 176	of cube, 149
Transconductance, formula for, 114 Transducer, 93	of cylinder, 149 of rectangular solid, 148
Transformer, color codes, 87-88 coupling coefficient between windings 21	OI ring of circular cross section 150
coupling coefficient between windings, 21 symbols for, 93 Transistors, symbols for, 92	of ring of rectangular cross section, 150 of sphere, 149
Transistor formulas, 114-116	Volume charge density, 82 Volume measures, 176
Transmission characteristics, bandpass fil- ter, 122	Volume resistivity, 82
ter, 122 band-rejection filter, 122-123 Transmission factor, 82	Volume unit, 46-47 abbreviation for, 84
Transmitters, AM, 44-45	VU, 47
FM, 45-46 Transposition of terms, 144-145	W
Trapezoid, area of, 147	Washer, power consumption of, 171
Trapezium, area of, 147 Triangle, area of, 146	Water, dielectric constant of, 51 weight of, 179
right, solving for, 143 solving for, 150	water heater, power consumption of 171
Trigistor, 92	Watts, 11, 35 abbreviation for, 84
Trigonometric formulas, 151 Trigonometric functions, 150	conversion of, 56 Watt-hours, 24
on slide rule, 140, 143-144	abbreviation for, 84
Trigonometry, plane, 150	conversion of, 53, 54 Watt seconds, 24
Triode tube, 91	conversion of, 56
Troy weight, 177 True power, 35	Wavelength, definition of, 41 formula for, 41

Wavelength—cont'd
-frequency conversion chart, 41-43
symbol for, 82
Webers, 56
Webers per sq. in., 53
Webers per sq. meter, 56
Weights, 177
apothecaries', 177
atomic, 174
avoirdupois, 177
metric equivalents, 178
troy, 177
Windings, transformer, 37
Winds, designations of, 178
Wire, resistance of, 111
Wire table, copper, 111-113
Wood, dielectric constant of, 51
Work, 24
abbreviation for, 84
WWV, 59-64
WWVB, 66
WWVH, 59-64
WWVL, 66

X

Xenon, 176

Y

Y connection, three-phase power, 116 Yard, 53-56, 176, 177 Ytterbium, 176 Yttrium, 176

 \mathbf{z}

Zener diode, 92
Zero, absolute, 172
Zero power, of number, 137
Zinc, 176
resistance of, 111
Zirconium, 176
ZLFS, 66
ZUO, 66



