

ADVANCED TECHNOLOGY LOUDSPEAKER

GOLD DOME PIEZO-ELECTRIC TWEETER
HIGH DEFINITION AEROGEL MIDRANGE
HIGH DEFINITION AEROGEL BASS

ADVANCED AUDIO
TEST PACKAGE - AT
BUDGET PRICE!
WE TEST LIBERTY
AUDIOSUITE

TURE PREMICE CORRECOK

ELECTRONIC UN ERSAL

MANUEL ELECTRONIC UN ERSAL

LETTERS AND Q&A

FREE D.I.Y. SUPPLEMENT No. 16

World Radio History

Hart Audio Kits - Your Value for Money Route to Ultimate Hi-Fi

2 Penylan Mill, Oswestry, Shropshire, England SY 10 9AF phone Oswestry (01691) 652894

Hart Audi. Kith and factory isoumbiled at its use his my best suit aphilic composition a racit designs by the renound John Linsley Hood to the you unbitable perform not

the halo mays led the "d for usy hor construct on to profession is a identis, in an in this size of more using easily assumbled on ited oricults when Healthist in America were shi using abounds! It in years of expenence and in overion going back to the early and Bally less as gives us incomparable design expiritise in the needs of the harm constructor. The current range of Hart kits is designed to give you all the components of audio exp for a matching rise




K1100 AUDIO DESIGN 80 WATT POWER AMPLIFIER

This fantastic John Linsley Hood designed amplifier is the flagship of our nino and the rhouse to your until a hill sys in This kins your way to get £K performance at barg in basem int prices. Unique design to the esturb is hully FET it to have point supplies give his amplified Class political countries with shifting clarify and transparency 'so rd, ad to it to our HART quality of complete and as of construct a Use't loptions are a simple LED point in the second reduction of the second re sy tiched inputs, with ALPS precision Blue Verilla and allowing and length controls Construction is very semple and enjoyable with all the difficult work done for you, even the runng is pre-learn nated mady lie instant use. All recisions are available with Standard componints or spicially and led Supe Audiophilic componints at £29.60 extra problem in plus £2.40 if you and to include Gold Plated spice in min.

K1100B Complex STAN OARD Ample of	£395.21
A1100B Factory Assembled	£499.21
#1100SC Complete SLAVE Amplifier Kit. £.	£333.62:
A1100SC Factory Assembled	£422.62
K1100M Complet. AIO OBLOC Amount Kit.	£261.20
A1100M Factory Assembled	£329.29
RLH10 Reponts of let of Ampli of articles	£2.70
K1100CM Construction Manual with will parts lists	£4.50

K1400 AUDIOPHILE PREAMPLIFIER. A versalile ultra high quality preamp with no less than senin inputs, all switched by sealed high quality relays. Separate tape output selection. Class: "A" haraphone output for two phones. Lo-Z long line drive facility.

Standard Kit	£343.49
K1400T Kit was Tri range tone controls	£398.41

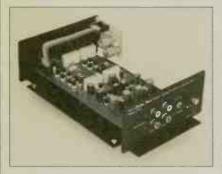

K1450 MAGNETIC PICKUP PREAMPLIFIER KIT features a totally discrete component implementation with the superior sound of the Shurit Feedback concept. High quality components filling to an advanced double under printed oricult bound make this a product at earing edit of chrobyly had our in be proud to own Me. 11 ss with our sup by step instructions it is very easy and satisfying to assemble. The higher current commitment on of this unit means that it is best po-med by our new Andante Audio Po-e. Supply, itself an admirced piece of technology in a matching case. This supplies the superbly smoothed and stabilised supply times needed by my sets the preampth of and features a felly profeed. Hi-grade toroidal transformer, long with a special limited still earthing system for hum me n The K1450 is suit bill lot all moring coil and muring magnatiti risduo is is

and as each could recommended for, and will extract the very best from the modern generation of low output high quality moving coil transducers This magnificent kill, comes complife with all parts ready to assumble in-ide the fully in shind 228 x 134 x 63 mm case. Comes with full easy to to ow. ristructions as will as the Hart Guide to PCB Construction we win from a enough Hart Audiograph Silver Solder to construct your




"CHIARA" SINGLE ENDED CLASS "A" HEADPHONE AMPLIFIER.

First Module to appear in our new "2000 Range" of kits. This in provides a high quality 'phone output for those many amplifiers that do not have one. Easily installed with special into prough lacily the unit draws its power from our new Andon's Ultra High Quility toro de suppry. Housed in the need black in shed, Hint - box - it is new of In quancy response, to ad-distortion and musically have associates with designs from the nine and John Linsley Hacd. Pre form as ed into anothing leads and PCB mounted soo ats print sugar po'r ty minsal and on-hourd it amounts provide visual and our on of Lappy Ramby Volume of billing contaits in the Billing come into Very assly by Le in by begin is incent compounts if dischy of the site in pair of circuit board and there is no con-int on it wining whatsour. The I the way of the led instructions and even comes with a roll of Hint and ograde silver sold in It can also be supplied factory assembled and lested. Selling for less than the foil it cost of all the companies if they were bought sup ratify, this unit regres into incredible value for money nd mailes en a rec' and harmo ous did a lo my hifi syst :

K21 Como Kit	£109.50
K2100SA Series Audiophili is of this selected wheth composits	£112.46

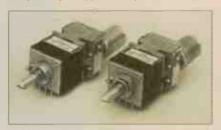Why not buy the reprints and construction manual for the ful you are interested in to see how easy it is to build your own equipment the HART way. The FULL cost can be credited



ALPS Blue Velimi" PRECISION AUDIO CONTROLS.

MANUAL POTENTIOMETERS

sponge for bit wiping

Now you can throw out those no sy ill mulched carbon pots and replace with the real hish components only used seed by in the very top fight of World class amplifiers. The improvem in in tracil accurry and much a re-fit is inheal ble giving better tone balance between channels and rock solid and state and

2-Gung 10K Sp. " Ballance and cross than and and countre loss. MOTURISED POTENTIOMETERS 2-Gung 20K Log Volume Control 2-Gung 10K RD Spaceal Balance, zero crosstank and less than 10% loss in centre position. SOLDERING The size of mod im campo and the right solid approximation of sessits. Everything a country and a size in our own were shops! Seriou Lass for the full range.	2-Gang 100K Lin	£15.67
MOTORISED POTENTIONIETERS 2-Gang 20M Log Volume Control 2-Gang 10M RD Special Balance, zero crosstalik and less than 10% loss in centre position SOLDERING The size of modium composition of the right solid to a process of the right solid to the full range.	2-Gang 10K 50K or 100K Log	£16.40
2-Gang 20M Log Volume Control 2-Gang 10M RD Spaceal Belance, zero crosstalk and less than 10% loss in centre position SOLDERING The size of modi im camput in the light sold in the process of the right sold in the process of the right sold in the full lange.	2-Gong 10K Sp + Balance zero crosst and a rolo of	re loss £17.48
2-Gung 10K RD Spacial Balance, zero crosstalk and less than 10 % loss in centre position £26.9 SOLDERING The size of mod im campo file of the right sold in the provided results Elergy ing the control of the right sold in the full range.	MOTORISED POTENTIOMETERS	
position SOLDERING The size of mod in campo the right sold to provide	2-Gang 20K Log Volume Control	£26.28
SOLDERING The size of mod in composition is the light solds by process for good results Everything use of a size in the full range.	2-Geng 10K RD Special Balance, zero crosstalk and less to	han 10% loss in centre
SOLDERING The size of mod in comparing the right solding primes of large good results Everything use of a size of the full range.	pos "en	£26.98
The size of mode in composition is the right sold in a profession of good results. Everything is a surface of a surface of the full range.		
results Everything a summary in a summary in a summary in a summary in the full range.	SDLDERING	
full range	The size of mod in companion the right sold in	gr pmm' ss " i for good
	results Everything to the state of the nour own wo	n shops! Ser ou Lists for the
BAS 990 VC240 ANTEV 240, 25 a Coldrego from This is the ideal Mail or many year	full range	
	845-820 XS240 ANTEX 240v 25w Soldering Iron This is	the ideal Mall ourses from as
the bit is dies and to lotally surround in formal along in best had broade. This		
eige at de an in me in his mont in sme ind high in the min		

HART SUPER AUDIOGRADE SILVER SOLDER

845-090 ST4 Lightweight Soldering Iron Stand. This has provision for the class c dam

companies straing capacity strain large rows of continues

Hint Sup A diograde Silver Solder has been specially formulaed for the silver audiophile. Not only does it give beautiful easy to main into hit is designed to min at norm I sold ring temperatures are directly the possibility I farmal dismage to components or the need for special high temperature irons. A very easy but alim hates the need for board cleaning after its

845-007	7 3 rtrs 2251 °G in Hart N n Tutle	£3.
845-008	8 100g Anal Special Valve Grade, 20swg.	£12.90
845-009	9 100g Princision PCB Grade, 22sing	£14.75
845-110	0 100g Reel Superline 24s for ultra precise control and	easy working £21.45

PRINTED CIRCUIT BOARD SOLDERING PRACTICE KIT.

Uns, re whether you can construct a HART hit? this is you chance to try! Your HART

Printing Circui Board Soldering Practic K. cornes in his man of medium components a type... Hert quilly PCB a roll of incorned yinds of solution of the structures it in the list the cost who is uncertain of his orinded his, about a put tougher and sold a printed circuit to try their hand at min min cost. The instructions explain the right technique and ou de even an absolute beginner through the seven now desinting, but in fact very simple, art of making a good soldered joint Excellent elux for money at mily.

TECHNICAL BOOKSHELF

MEW! "AUD ELECTRO CS" And now, ho off the press, yet anothe class c from the pen of John Lins'ey Hood. Following the enarmous oncoming success of his "Art of Linear Electronics" his latust or ening is the "I-m" of an of "Audio Electronics", now entirely re-initial by the moster his self

Underlying aid some as and equipment is sent of factor as to disquality of sound. For impone in a lind in discovery dupting or using digital or analogue audio equipment understanding l'ectro artificial la rigre di contro o la reproduced

The subject correct natival tape recording terms policy output strains diagrams did less instracts is ad laudapa crosso systems Johns to the pin not and person innoving in this lid law him to reply his a lat by so law are this sub, of that he can write clearly about it and make it both interesting and comprehensible to the reade-Containing 240 peaces and over 250 line illustrations this new book in prison's ment value for money a only

"THE ART OF LINEAR ELECTRONICS."

Summar V sun + h H d Si - Solder

The district Embers seemed and bon by "renormed in" Linsby Hood This 300+ pupe bon will give you an unperall individually into exactings of all types of audio circuits. Learn how to read circuit disor min and understand amplifies and how they e designed to g. " but sould. The little and loos I pass and clin companings are < m ild and thirte are separate silvers . Ing point upp is indivisional of no die As a out put o the er of heavy address of a ampling to the particular of the earn entire chap it, as do less and musicipal into guipming Copius this hook is incredible allo for the amount information it contains on the min hing and hind of linear, as opposed to digital, electronics indused it must be destined to be a made and and a roce loss of who and or are in eached in this finite 1994 344 Proes 247 : 190 1Kg 0-7506-0868-4

"BIGITAL AUDIO AND COMPACT DISC TECHNOLOGY"	
0-7506-0614-2	£17.95*
INTRODUCING DIGITAL AUTHO CD. DAT AND SAMPLING.	
ISBN 1870775 22 8	£7.95
"THE ART OF SOLDERING" 0-85935-324 3 0	£3.95
"TOWERS' INTERNATIONAL TRANSISTOR SELECTOR"	23.30
0-572-01062-1	£19.95°
"AUGGO" F.A Wilson BP111	£3.95
"HOW TO USE OSCILLOSCOPES & OTHER TEST EQUIPMENT" F	A Peniold BP267
£3.50	
"THE LOUDSPEAKER DESIGN COURBOOK" Vance Dickason (4th.	Edn.) 0-9624-191-
7-6	£22.95°
ELECTROSTATIC LOURSPEAKER DESIGN AND CONSTRUCTION	Ronald Wasse
BKT6	£18.95
"AN INTRODUCTION TO LOUDSPEAKERS & ENCLOSURE DESIGN	
V Can. BP256	£2.95
"LOUDSPEAKERS FOR MUSICIANS" BP297.	£3.95
THE HART PRINTED CHICUIT BOARD CONSTRUCTION GUIDE."	In's is included

VALVE & EARLY CLASSIC BOOKS	
THE VTL BROW David Manley BKVT1 £	17.95
LOUDSPEAKERS; THE WHY AND NOW OF GOOD REPRODUCTION. G Bright	1949
0-9624 1913 3	£8.95
MULLARO TUBE ORICUITS FOR AURIO AMPLIFIERS	
BKAA27	13.95
THE WILLIAMSGN AMPLIFIER." 0-9624-1918-4.	26.95
AN APPROACH TO AUDIO FREQUENCY AMPLIFIER DESIGN. GEC 1957, 1-	882580
05-2 £	18.95

\$7.50

FREE with all are plant out but is malable separately.

when and o was young and valves were king!. BKAA3/1 to 6 All £13 95 each "A SIMPLE CLASS A AMPLIFIER" J.L. Linsley Hood M.L.E. 1969. RLH12. £2.50

Postage on all books, unless starred, is only £1.50 per book meaning £4.50 for ny number any size! Starred items are heavy books costing £250 to send He waiting!. All listed books are normally in stock!.

Send or phone for your copy of our FREE list of these and many other Kits & Components. Enquires from Overseas customers are equally welcome, but PLEASE send 2 IRCs if you want a list sent surface post, or 5 for Airmail. Ordering is easy. Just write or telephone, your requirements to sample the friendly and efficient HART services. Payment by cheque, cash or credit card. A telephoned order with your credit card number will get your order on its way to you THAT DAY Please add part cost of carriage and insurance as follows: INLAND Orders up to £20 - £1.50, Order over £20 - £3.50. Express Courier, next working day £10. OVERSEAS - Please see the ordering information with our lists.

OUALITY AUDIO KIT 24hrs SALES LINE 01691 652894

ALL PRICES **INCLUDE** UK/EC VAT

£9.93



D.I.Y. Supplement

Contents

KIT NEWS

All the new kits, components, drive units and services for the DIYer. Find out what the latest components and technology can offer.

WORLD AUDIO DESIGN KLS6

A new top-end loudspeaker design using Audax's latest and very special piezo electric gold-dome tweeter, together with their High Definition Aerogel drive units.

LIBERTY AUDIOSUITE

A new audio CAD package from Liberty Instruments, who also make the IMP system. Audiosuite is a more advanced package including many extra features useful to DIY audiophiles.

18

BOOK REVIEWS

TUBE PREAMP COOKBOOK

Allen Wright cooks up numerous valve preamplifiers for the DIY hi-fi enthusiast.

23

ELECTRONIC UNIVERSAL VADE MECUM

Published in Poland, the Electronic Universal Vade Mecum is a reference data book containing application notes and working conditions for over 5,500 valve types.

25

The only place to write to for design and build advice on all aspects of audio Our experts will answer your questions and steer you in the right direction.

All of the

directly

blishing Ltd and World Audlo Design Ltd accept no responsibility for accident of injury sprojects in this supplement have gone through rigourous listening and test procedures.

Audie Publishing Led and World Audio Design Led accept no responsibility for accident of

Audio Design Ltd.

arising from the construction or use of any of the designs published. The performance and specification of these projects can only be guaranteed on kits bought

All rights to the designs are reserved by World Audio Design Ltd. They are published for single use by private individuals. They are not to be used for commercial gain without prior

Connect the dots.



Introducing The Parts Connection's first complete DIY kit: the Assemblage DAC-1 Digital Processor.

It comes in a small package (24cm x 5cm x 18cm chassis), but packs a big punch and a very musical sound. Designed for the rookie or first time kit builder, the only tools required are a pencil tip soldering iron, a screw driver, a wrench, a pair of electronics pliers, and a wire stripper or hobby knife. With only 21 solder joints and a handful of nuts and bolts, this kit goes together in one evening (typically about an hour). It's as easy as connecting the dots.

The parts quality is top notch. The board comes assembled and tested, implementing the Burr Brown 1702 DAC, a Crystal 8412 input receiver, an NPC 5813 digital filter, Analog Device's AD844 and 847 op amps and a custom potted toroidal power transformer.

At \$449 US, the Assemblage DAC-1 offers an outstanding value in digital conversion and comes with a Satisfaction Guarantee (return it with-

in 30 days of purchase for a full refund) and an Assembly Guarantee (if you can't get it running, we will!). We challenge you to find a DAC anywhere near this price with better measured performance, component quality, and most importantly, sound quality. Call us for more specific information on the performance or construction features.

To order the DAC-1 kit or to order The Parts Connection 1994 Catalog (for £3), full of a lot of other exciting stuff (including a \$10 US discount coupon good on your first order over \$100 US), send us your request and mailing address - or call with credit card information.



2790 Brighton Road, Oakville, Ontario, Canada L6H 5T4
Telephone 0101-905- 829-5858 Facsimile 0101-905-829-5388

Toll Free Order Line 1-800-769-0747 (U.S. & Canada only)

TECHNICAL & GENERAL

THE ORIGINAL TURNTABLE SPECIALIST

for the Great Classical Tumtable, Arms, Cartridges, Styli
CONNOISSEUR GARRARD GOLDRING LENCO
ORTOFON SHURE S.M.E. THORENS WATTS

All available Genuine spares and our own re-manufacture obsolete parts
Servicing and Overhauls, to original technical specifications.

NO ILLUSORY 'IMPROVEMENT' NO DUBIOUS OR HARMFUL 'MODIFICATIONS'

Remedial Services available

Cartridge and styli, correct radius dismond, for early recording - 78s & Lps

TECHNICAL & GENERAL

P.O. Box 53 Crowborough, East Sussex TN6 2BY Tel: 01892 65 45 34

MPROVED STEREO DECODER FOR MONO VALVE TUNERS

Now with revised impedance matching, for wider separation, fuller bass and extended treble.

Experience REAL stereo from your Troughline, Quad, RCA, Rogers, etc. Just connect this great sounding decoder to the multiplex output from your mono tuner. Available as a mains powered boxed unit, or an easily assembled kit of parts, or a fully aligned module only. No special tuner alignment needed.

Complete unit £48.50. Kit £28.50. Assembled module £12.50. (Inc. P&P)

STUDIO

Nanjivey Terrace, St Ives, Cornwall, TR26 1BQ. Tel: (01736) 798393

AUDIO ENGINEERING

Our "type 15" is a medium-priced high performance 6 kilo single-ended output transformer, as used on our "musician" amplifier.

But with a series /parallel primary section, user set for a 300B or EL34/KT88/6550 output valve to match a 8 ohm. With 130 milliamps DC. flowing through the primary the frequency response is level from well below 15 hz. to above 40 khz., with or without feedback. Thus allowing the accurate reproduction of large scale orchestral works with a large dynamic range.

The "type 15" has been used successfully as a replacement upgrade for various commercial amplifiers, and is now available for home constructors wishing to build their own amplifiers.

They are handwound in matched pairs, tested and guaranteed for one year. Priced at £180.00 per pair including carriage, insurance and VAT.

And of course our fully welded 1.5mm. mild steel blank chassis, the most popular sizes being ...

400mm. x 300mm. x 65mm, @ £30.00 each.

400mm. x 230mm. x 50mm. @ £50.00 per pair.

For more details on these and other items please send sae to P.J. Perry

AUDIO ENGINEERING
57 Lyndhurst Drive, Leyton, London E10 6JB

Tel: 0181 558 4266

KIT NEWS

NEW VOICE COIL

Audio Amateur Publications have just announced the June '95 relaunch of Voice Coil, a periodical for the loudspeaker industry. The 12-16 page monthly issues of Voice Coil will now include product reviews, show reports, industry events and more.

Audio Amateur Publications PO Box 576, Peterborough, 합 02458-0576 Fax: (603) 924 9467

STUDIO 12 UPGRADE DECODER

Studio 12 have been working on a couple of tweaks to improve the performance of their stereo decoder. These involve removing the input capacitor and direct coupling the tuner to pin 2 of the module via a new $1M\Omega$ potentiometer and increasing the values of the capacitors in each output leg to 10µF. Still having the decoder I built for the review in Supplement 15, I decided to give these new tweaks a go See my column on page 69 of the main issue. DB Studio 12 12 Nanjivey Terrace, St Ives, Cornwall TR26 IBO TO 01736 798393

NEW VALVE PREAMPLIFIER FROM MAPLIN

Maplin have recently introduced a new valve preamplifier to go with their Millennium valve power amplifier. The Newton is available in a number of different forms, a full spec version including RIAA phono stage and tone controls coming in at £119.97.

Full articles describing the design and construction of the Newton preamplifier can be found in issues 85 and 86 of Electronics, The Maplin Magazine.

ELECTRONICS FOR BEGINNERS

Written by Keith Brindley, Starting Electronics provides an important

introduction for the newcomer to electronics. With a practical approach this book available from Maplin is intended to give a thorough grounding in all of the basics.

Maplin Electronics
P. O. Box 3,
Rayleigh,
Essex SS6 8LR
20 01702 554161

SILVER WIRE SALE

If you're looking for top quality cable for DIY interconnects and 'speaker cable, give Audio-Links a call. Why? They're offering a range of solid silver wires from 0.2mm to 2mm diameter at special sale prices until the 31st July or until stocks clear.

Audio-Links
7 Fairmont Crescent,
Scunthorpe,
N. Lincolnshire DW16
IEL
12 01724 870432

WESTERN ELECTRIC 300B IS BACK

Westrex Corp. is planning to re-release the WE 300B triode valve, regarded by many as the best 300B ever made. It is said that the new WE 300Bs will be made using the same original tooling, materials and manufacturing processes, the only difference will be the date code. Availability is expected to be September '95. The Parts Connection in Canada are already advertising the WE 300B in the main issue of Hi-Fi World, price \$350.

The Parts Connection 2790 Brighton Road,


Oakville, Ontario, Canada L6H 5T4 & 905 829 5858

NEW CATALOGUE FROM CRICKLEWOOD

Cricklewood Electronics have just finished their latest catalogue of electronic components and hardware. It includes loudspeaker drive units, books, audio grade polypropylene capacitors up to 100µF from Ansar, projects cases, valves, power supplies and more. Call to get your copy.

Cricklewood Electronics
40-42 Cricklewood Broadway,
London NW2 3ET

© 0181 450 0995

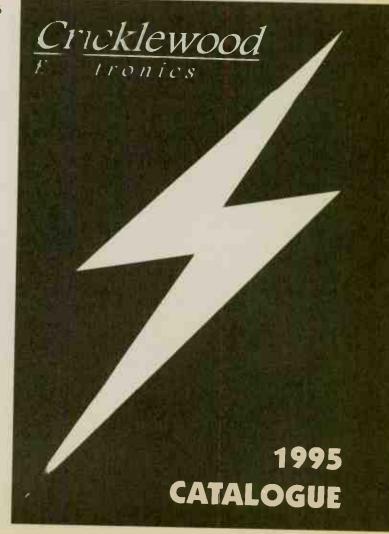



Get on our list to get closer to this list.

- MIT MultiCap Wonder Cap Kimber Kap Solo Hovland MusiCap Solen Siemens
- Wima Holco Rel-Cap Draloric IRC Allen-Bradley Jensen Resista Vishay Mills
- Caddock Matsushita TKD Noble Cardas Kimber Kable van den Hul Discovery
- Audioquest MIT Alps Boums Shallco Elma Electroswitch Nichicon Gold Aero
- RAM Mallory Panasonic HFQ Nichicon Elna N.O.S. Ruby Tubes UltraAnalog
- Burr-Brown Crystal Linear Technology Analog Devices Edison Price Motorola UCC
- International Rectifier Hitachi MagneQuest Sonic Frontiers Pearl Tube Sockets
- WBT Neutrik Sound Coat Curcio Audio Engineering Assemblage and other kits And it's growing and growing. To order The Parts Connection 1995 Catalog & Resource

Guide, send £7 and mailing information. You'll also receive a Discount Coupon worth \$10 off a purchase over \$100 or \$25 off a purchase over \$250" as well as The Breadboard bulletin to keep you updated on our latest news, information and growth spurts.



or \$10 US, or credit card information catalogue discounts are in US Do are

THE PARTS CONNECTION

2790 Brighton Road, Oakville Ontario, Canada L6H 5T4

Toll Free Order Line 1-800-769-0747 (U.S. & Canada only)

Tel (905) 829-5858 Fax (905) 829-5388





BORBELY AUDIO Germany

The FET specialists...

ACTIVE CROSSOVER KITS

Class-A, discrete JEFT cascode circuitry. Balanced & single-ended input/output. 2- and 3-ways loudspeaker systems. 1st, 2nd, 3rd and 4th order network.

We also offer KITs for high-end preamps, Class-A MOSFET power amps and audiophile components.

Please send two International Replay Coupons (available at your post office) for our price list and information leaflet. We accept VISA/MC.

BORBELY AUDIO

Melchior Fanger Str. 34A 82205 Gilching Germany

Tel: +49/8105/5291 Fax: +49/8105/24605

The AP ELECTRONICS Route to Musical Happiness

EXPERIMENT

With Sometink custom designed mains cables By changing resistors and capacitors With large power supplies

With large power supplies
By applying simple modifications to improve your circuits
By bypossing high value capacitors with higher quality lower values
With mechanical damping of mechanical parts and electrical encits
LEARY

From your experiments
The leatures which give the best sound quality.
From knowledge gained through reading AP PERFORM INCL ALDIO

MODIFY

Use the knowledge gained from experimentation And from tips published in AP PERFORMANCE ACDIO

To rebuild your own amplifiers
To improve the sound quality of your system
To get greater enjoyment from your layourite music

BUILD

DESIGN

Design the equipment of your dreams Make your dream come true with parts purchased from AP LLECTRONICS

A P E L E C T R O V I C S Audiophile Parts at Affordable Price 1995 CATALOGUE now available - £4.95 (or FRFL with your next \$40 + order)

PERFORMANCE The Journal of High Performance Audio Construction 1995 Subscription (4 issues) -95 (overseas 910) Please make cheque payable to AUDIOKIIS

timessages recorded when imattended - please give full details HOTHMETOR FREE TECHNICAL ADMGE - TEL 01332-67 (929)

9-10am Mondays-Sundays

Derwent Business Centre, Clarke Street, derby DC1 2Bt fel: + 14-1332-674929 Tax: +11-1332-298836

The Tube Preamp CookBook by Allen Wright

An in-depth pragmatic discussion of tube preamp designs based on 30 years of experience of design, development and manufacture of state of the art tube equipment. Packed with diagrams, schematics and ideas, it's a goldmine for tube enthusiasts & constructors at all levels.

"full of secrets, some of which I am surprised you gave away you tell it like it is, debunking myths regarding all aspects of audio..." JH, professional electronics engineer, USA

You've seen the reviews - this is where you can buy it. Choose your most convenient agent - all accept VISA/MC & cheques in their local currency.

Prices: UK £20 - US\$29.50 - DM49.50 - AUS\$49.50

Vacuum State Electronics (UK) United TV & Video PO Box 4016, Pangbourne Reading RG8 8UA Fax 01734 845933


12436 Moorpark Street Studio City, CA91604 Tel/fax (818) 752 0785

Allen Wright/Allgäuer Einstein Str. 129 D-81675 Munich Tel/fax ++49-89-477415

Class One Productions PO Box 145 Woy Woy Australia 2256 Fax ++61 43 411129

Email orders cleared through Compuserve 100240,2562

VACUUM STATE ELECTRONICS

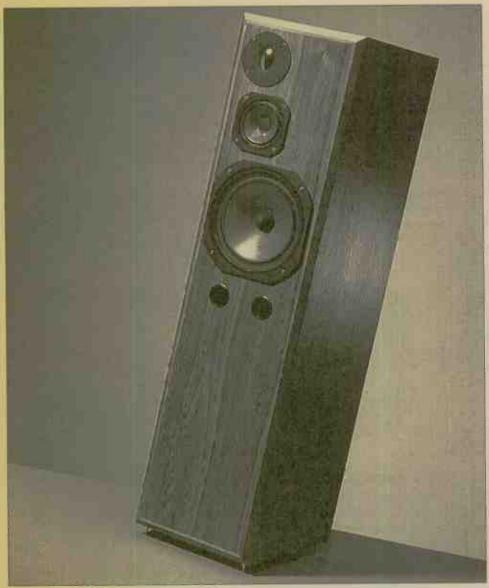

KLS6

A UNIQUE HIGH TECHNOLOGY LOUDSPEAKER DESIGNED BY DOMINIC BAKER.

If you're looking for a top-end loudspeaker capable of rivaling the very best commercial designs, without having to shell out a four-figure sum, our new KLS6 design may be just the thing for you. It uses state-of-the-art technology in its drivers, combined with a simple, but highly effective cabinet design and a minimalist crossover, which together offer the highest performance possible.

Looking around at the loudspeaker market, you could be forgiven for thinking that things haven't advanced much over the last twenty years. Modern loudspeakers still use paper and plastic cones, and the conventional two-way bass reflex system is still the most common, by far. For a truly high performance design, using modern materials with a higher performance is important, but the penalty here is cost.

DIY is the only answer.

The drivers used in KLS6 are some of the best money can buy; if they were incorporated into a commercial design they would be prohibitively expensive. But for all of you keen DIYers, these drivers, when used in a well designed and engineered system, will rival loudspeakers costing five times as much as KLS6 - or more!

Briefly, KLS6 uses Audax's super new gold piezo-electric tweeter for outstanding clarity and transient response, a High Definition Aerogel (HDA) midrange driver, mounted on a simple open baffle to completely eliminate cabinet colouration, and a powerful 8inch HDA bass driver in an efficient bass reflex system for deep, taut and powerful lows. With such high quality drivers and a well engineered cabinet and crossover, the results are nothing short of breathtaking.

KLS6 is aimed at audiophiles using well matched and set up hi-fi systems. It is a very revealing loudspeaker, designed to resolve as much detail as possible, whilst being free of colouration. These days, sophisticated hi-fi systems can provide fantastic musical results, but all too often the end performance is let down by the loudspeakers, because they are still a long way behind what a good source and amplifier are capable of resolving. KLS6 will get the very best from your system, and has been designed to be compatible with a wide


range of equipment, valve, solid-state, zero feedback, etc.

This 'speaker's high 90dB sensitivity and smooth impedance means it will always get the very best out of partnering equipment. It's not just valve amplifiers that benefit from high sensitivity loudspeakers, the less power it takes to drive the 'speakers, the less distortion your amplifier will produce and the smoother it will sound.

KLS6 ADVANCED TECHNOLOGY LOUDSPEAKER

THE DRIVE UNITS

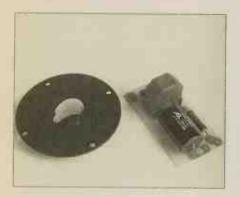For KLS6 we have necessarily chosen to use some of the most advanced drivers available. They aren't cheap of course, but this is not a budget design; it's a top quality loudspeaker system capable of revealing as much as possible from a well sorted high-end system. The drivers are far too expensive to be used in commercial products.



THE TWEETER

Although expensive, Audax's HD-3P piezo electric gold dome tweeter offers state-of-the-art technology and performance. This unit uses a piezo electric polymer film, coated on both sides with pure gold and clamped to an elliptical ring former. The dome shape of the HD-3P is formed by a pressurised gas chamber behind the diaphragm.

The HD-3P uses no magnet or voice coil, the signal is applied to the gold deposit on either side of the dome and this makes it flex in proportion to the signal. Sound waves are produced by this motion. Because the HD-3P tweeter has no moving parts its moving mass is approximately twenty times lower than a conventional 20mm dome tweeter, giving it unmatched transient ability.

The sound quality from the HD-P3 is similar in character to an electrostatic or ribbon tweeter. It is clear, open and extended, as well as being extremely fast and detailed.




THE MIDRANGE DRIVER

Because the HD-3P tweeter only reaches down to 5kHz or so a very high quality midrange driver capable of smoothly extending at least this far upwards is needed. Audax's HM100ZO, a

small dedicated midrange unit, is ideal for the purpose. It uses a High Definition Aerogel cone, which is light and consequently fast, giving super detail and a crisp and open quality well suited to the HD-3P.

High Definition Aerogel is another Audax innovation. It's made from a controlled matrix of acrylic polymer gel, in which a carefully optimised proportion of Carbon and Kevlar fibres are embedded. It is light and stiff, with good internal damping properties.

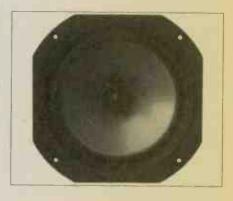
HDA has a smooth, neutral and highly detailed sound, making it ideal for top-end systems. The HM100Z0 uses a die cast chassis, which is ideal for DIY constructors, because it's near impossible to over-tighten screws and twist the chassis, which can misalign a voice coil.



THE BASS DRIVER

For powerful and taut bass an 8inch HDA driver with a powerful magnet assembly was chosen. By using HDA for the bass - the same cone material as the midrange driver - there is no character change between the two, making for a cohesive sound. The cone is extremely light and stiff for fast and detailed bass, and again comes on a die cast chassis for strength and rigidity.

AUDAX HD-3P TWEETER

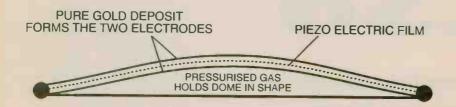


THE CROSSOVER

Audax's HD-3P tweeter comes complete with its own dedicated crossover and matching transformer. As supplied, it comes set with a -3dB lower roll-off point at 6kHz, and a sensitivity of 89dB. This turned out to be ideal for

matching with the HM100Z0 midrange unit, as Audax suggested.

The crossover for KLS6 was kept as simple as possible to ensure maximum sensitivity and detail; fewer components means lower selective signal losses. The HM100Z0 HDA

Midrange/Treble Response

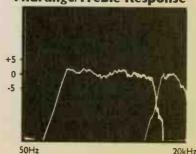


midrange driver rolls off around 6kHz where the HD-3P tweeter takes over.

The

KLS6 ADVANCED TECHNOLOGY LOUDSPEAKER

nidrange driver is fed from a 3rd order rossover filter at its upper cut-off point, comprising one capacitor and two nductors. This filter operates at 6kHz, colling off frequencies above this point to avoid cone break up, giving a smooth

Midrange/Bass Response

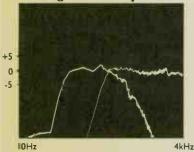

Measuring near field (less than I m from the baffle) the midrange and bass drivers overlap. Because the midrange driver is mounted on an open baffle though, further back in the listening position some of the lower midrange will cancel out to give a flat response.

and accurate response. Most midrange drivers get no further than 3kHz, by the way; this one manages one octave more.


Because the HDA midrange unit is mounted on an open baffle, its low response will start to roll off at -6dB/octave, due to phase cancellation, where the baffle radius is half a wavelength; imagine the front wave reaching around (in effect) to cancel the rear output. The baffle radius of KLS6 is equivalent to 400mm, so cancellation will occur at wavelengths of 800mm or more. This corresponds to a frequency of 426Hz, causing the midrange to gently roll-off below this frequency. A series capacitor increases the roll-off rate to 12dB/octave (2nd order) to improve power handling by limiting the amount of bass this driver must cope with. It also matches into the 2ndorder roll off rate of the bass unit properly.

Below this the powerful 8inch HDA bass unit is fed from a 2nd order low-pass filter This driver is reflex loaded

by a large 40litre cabinet to ensure bass reaches down low enough to produce the deepest fundamentals.


To smooth the 'speaker's electrical impedance, and to reduce output a little from the midrange and treble in order to match the bass unit, an L-pad attenuator is used, which employs just three resistors.

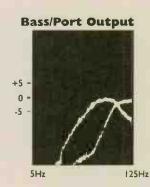Of course, for best results KLS6 uses Solen polypropylene capacitors throughout, and all inductors are high quality air-core types.




Output from the port extends bass low to 28Hz (-3dB), 22Hz (-6dB).

CROSSOVER CIRCUIT

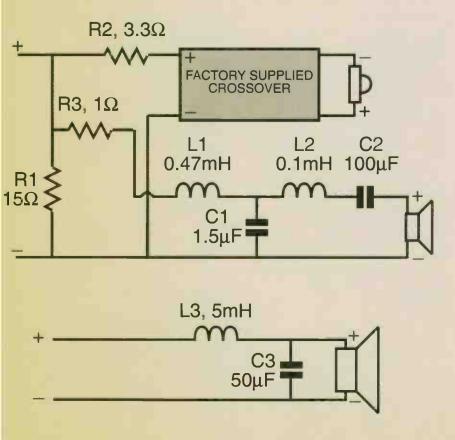

CROSSOVER FIXING

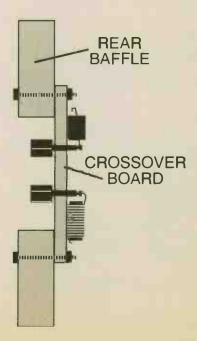

KIT & COMPONENT SUPPLIERS

LOUDSPEAKER KIT SUPPLIERS

Falcon DIY Speakers Falcon Electronics, Tabor House, Mulbarton, Norfolk NR14 8|T. Tel. 01508 578272 Falcon sell kits, drive units and crossover components and have a large range of books and back issues of kit magazines. Please send large SAE (36p) for free pnce

The Speaker Co. Unit 9, Waterside Mill, Waterside, Macclesfield, Cheshire. SKII 7HG. Tel: 0625 500507 The largest range of speaker drive units and accessories stocked for the speaker builder. Plus a range of speaker kits designed exclusively for The Speaker Company MLSSA test facility available, phone for an appointment Our prices can not be beaten

9 Skew Bridge Close, Wootton Bassett, Swindon, Wilts. SN4 7DW. Tel: 0793 848437.

Loudspeaker cabinet kits are the speciality of 'AUDIOCAB'' Whether you are prototyping your own loudspeakers or working to a design published in Hi-Fi World, including the KLS3, "AUDIOCAB" will produce a bespoke kit to your specification. "Biscuit jointing" is used to ensure perfect alignment of adjacent panels and cabinets are dry assembled and sanded before dispatch. David Barfield, propnetor, says "no pnor expenence of woodworking will be required to build our kits and achieve a professional finish." Kits will normally be supplied in 25mm unfinished MDF but any finish is available and designs are usually enhanced by the use of mouldings to escape from the normal 'square box'. Ready built cabinets can also be specified Professional, trade and retail enquines are nvited

Wilmslow Audio

Wellington Close, Parkgate Trading Estate, Knutsford, Cheshire WA16 8DX Tel. 0565 650605 Fax. 0565 650080

Extensive range of drive units and over 30 different designs of self-assembly kit. Two 'ATC' kits now available. Drive units include those from KEF, Dynaudio. Audax, SEAS, Peerless, Scanspeak and Morel Everything required for the loudspeaker builder and four dem rooms to listen to the kits in built-up form. Two new kits from Morel - one 3 litre, magnetically shielded, one 11 litre book shelf.

IPL Acoustics 2 Laverton Road, Westbury Wilts BA13 3RS, Tel. 0373 823333

IPL supply a range of eight speaker kits using drive units from SEAS, Morel, Audax, Visaton etc. including four transmission lines to suit all room sizes. We also supply a full range of drive units, capacitors, and cabinet accesones as well as silver plated P.T.F.E. insulated

DBS Audio

PO Box 91, Bury St Edmunds, Suffolk IP30 ONF. Tel. 0284 828926

Sole authorised supplier of DBS loudspeaker kits designed by Dave Bernman. The acclaimed DBS6 kit includes Morel tweeters and custom built woofers, plus top quality pre-assembled crossover and components

UPLIFTING SOUNDS - Tel: 0121 777 4196

Offers assistance in the design and construction of loudspeakers and audio furniture. From innovative to stylistic talk through your ideas with an enthusiast and choose your own level of involvement.

VALVE AND OUPUT TRANSFORMER SUPPLIERS

P.V. Tubes 104 Abbey Street, Accrington, Lancs. BB5 1EE Tel. 0254 236521/232611 24 hrs a/p. Fax.

or all your electronic components. Valves are new in branded boxes and matched pairs areavailable. Pls call for types and prices. We are closed all day Wednesday. Vintage Valves, PO Box 147, Station A, Vancouver B.C. Canada, U6C 2M3. Fax (604) 876 5876.

Dynaco, Sherwood, Scott, The Fisher, McIntosh Eico. Harmon Kardon, Heath, Altec Stromberg- Carbon Many vintage parts and equipment available on request

Wilson Valves 28 Banks Ave., Golcar, Huddersfield, West Yorks HD7 4LZ. Tel. 0484 654650/420774, Fax. 0484 655699.

Mail order. Call us to find out more about out extensive range of valves Over 1,000 different types stocked. S.A.E for list. (Please mark for Dept. HFW).

Langrex Supplies Ltd I Mayo Road, Croydon, Surrey CRO 2QP

Tel. 081 684 1166 or fax. 081 684 3056

One of the largest distributors of electronic valves, tubes and semi-conductors in the UK by onginal UK and USA manufacturers. Obsolete types are a speciality Telephone or fax for an immediate quotation

Billington Export Ltd. IE Gillmans Trading Est., Billingshurst West Sussex RH14 9EZ Tel. 01403 784961 or Fax. 01403 783519

Billington Export Ltd. holds large stocks of audio valves including many obsolete brands such as Mullard, GEC Bnmar etc as well as Sovtek, Thermionic Gold Brand and the recently introduced Billington Gold range Also Cathode Ray Tubes (eg used in Marantz tuner 10B). 50 page catalogue available, tel or fax for a quotation. Minimum order £50.00 UK, £100 export

PM Components

Springhead Enterprise Park Springhead Road, Gravesend, Kent DATT 3HD . Tel. 0474 560521

P.M. Components Ltd are the specialist component company for High End Audio enthusiasts. We have a design and manufacturing base for audio valves and associated products and have a capability to produce custom tubes for major manufacturers. Our 70 page catalogue is available at £2.50 including U.K. postage. P.M. Components are major stockists for Golden Dragon, Mullard, GEC and Teonex valves and have a vast archive of vintage tubes gathered from every manufacturer in the world

Chelmer Valve Company 130 New London Road, Chelmsford, Essex CM2 0RG. Tel 0245 265865 Fax. 0245 490064. Supplier of premium range of audio valves, other valves and components also available (Please see our ad on outside back cover of this supplement).

RESTORATION

GT Audio 5 Upper Road,

Higher Denham, Bucks UB9 5EJ. Tel. 0895 833099 Professional repair/restoration of all hi-fi including classic and vintage equipment. Supplier of very high quality electronic components, in particular types which are difficult to source Onginal valves available, i.e. Mullard, Bnmar, GEC, GE, RCA, Sylvania etc.

COMPONENT SUPPLIERS

Hart Electronic Kits Ltd Penylan Mill, Oswestry, Shropshire SY10 9AF 24 Hr sales/enquiries. Tel. 0691 652894

A range of Audiophile kits for 80 watt Power Amplifiers, Tuners, Pre-Amps and Moving Coil/Moving Magnet RIAA Pickup Preamps. All kits are fully engineered, with our thirty years design expenence, for easy constructions from circuits by John Lindsey Hood, the most respected designer in the field. Send for lists.

V.R.R. 30 Melbourne Ave, Worthing, BN12 4RT, Tel: 01903 501158 Vintage Radio Restoration

We can provide mains transformers, chokes and singleended or push/pull output transformers as well as silver cable, paper-in-oil capacitors and other goodies all at reasonable pnces

Our 30w monoblock short kit is only £2991

AP Electronics 20 Derwent Centre, Clarke Street, Derby, DEI 2BU

Check out the AP ELECTRONICS 1994 catalogue. It's free with every order of over £40.00 or can be purchased for a £495 cheque payable to 'AUDIOKITS' Over 80 pages include pre and power amplifier kits. high grade audiophile resistors, capacitors and semiconductors, audio and mains cables, gold and modium plated connectors and COMPONENT NOTES on using high grade parts. A quarterly newsletter 'AP PERFORMANCE AUDIO' has been recently launched and your first issue is free.

RushAudio 126 Station Rd., Tempsford, Sandy SG19 2AY, Tel. 01767 640779 Fax. 01767

RushAudio stock high quality British made polypropylene capacitors (630V dc) ideal for PSU applications. 30uF (100mm x 50mm dia.) £22; 40uF (100 x 63) £27, 50uF (100 x 63) £32; 100uF (125 x 76) £55. Carnage: 1 capacitor £2; 2 - £4, 3 or more £6 Unfortunately VAT is extra on total of goods plus camage Cheque with order apperciated for prompt delivery.

Audio-Links

7 Fairmont Crescent, Scunthorpe, South Humberside DN16 IEL. Tel. 0724 870432

Vast range of highest quality electronic components and accessones for the D.I.Y. enthusiast. A wide range of components aimed at the hobbyist competitive VAT incl. prices, mail order and a friendly service. Open Mon-Thurs 9.15-6.00, Fnday 9.15-5.00 and Sat's

V Chassis Company PO Box 36, Letchworth Hertfordshire SG6 2UR Tel/Fax: 01462 671594

Suppliers of high quality classic style welded Aluminium chassis, designed for DIY Audiophile constructors. Our modular chassis is also very suited to semiconductor pre/power amplifier applications. Check out our PTFE sheet at £24 inc per sheet 150x30x5mm. Please send 38p A4 SAE for details.

Russ Andrews Audiophile Components Edge Bank House, Skelsmergh Kendal, Westmorland, LAS 9AS Tel. 01539 823247 Fax. 01539 823317

World leading supplier of the highest quality premium grade components. If you want the very best sounding resistors, capacitors, inductors. Volume controls, wire etc send for our 1994/95 Catalogue We also have a range of our own design of amplifiers, preamp, speakers and CD players built with our components. To receive your copy of our new 1994/95 Catalogue and a £5 discount coupon usable on your first order over £50, just mail, phone or fax the address above. together with £3 or \$5 US or your credit card information.

VINTAGE DIY

Loricraft Audio

4 Big Lane, Goose Green, Lambourn, Berks RG16 7SQ. Tel. 0488 72267 Specialist restoration of 301's and 401's using genuine

spares and re-manufactured parts to onginal pristine standards in our newly built workshops designed pnmanly for these purposes.

CLASSIC TURNTABLES

Technical & General P.O. Box 53, Crowborough, East Sussex TN6 2BY. Tel. 0892 654534.

The original specialist source of spares, restorations and overhauls for the classic turntables. Years of actual expenence and comprehensive range of parts (onginals and re-manufactures), manuals, ancillanes, No dubious 'improvements' - no harmful 'modifications' Our specialities: Connoisseur, Garrard; Goldning; Lenco; S.M.E.; Thorens; Watts; Ortofon; Shure: Cartidges and styli for 78s, Mono LPs, Stereo LPs.

THE CABINET

To get the very best out of the expensive drivers used in KLS6, the cabinet is a little different to that of most designs, including our own to date. It doesn't use concrete, plastics, exotic materials, or even a complex internal structure. Instead it is extremely simple, but devastatingly effective.

So what is this special cabinet construction? Well, because the HM100Z0 midrange driver uses a stiff cone surround it lends itself particularly well to use on an open baffle. Rather than invest in overly elaborate cabinet materials, why not do away with cabinet problems in one go? In one fell swoop, standing waves, reflections from the rear wall and other horrid things that make up "box colourations". As a result, an open baffle design such as this goes a long way towards achieving electrostatic-like neutrality and lack of colouration. The sound is open, with


great stage depth and width, and because there is no body of air acting like a spring behind the driver, transients are crisp and clean. Our design is essentially a cabinet with the back left off, the front and the sides giving the necessary distance required between front and rear of the cone for full output down to the bass crossover point. This also allows the front of the cabinet to be kept as narrow as possible, improving image definition, a property we are careful to nurture.


Behind the driver the cabinet is lined with soft carpet felt and lightly filled with long hair wool. In addition, a curtain of felt is hung at the back of the open box to ensure that as much of the rear radiation as possible is absorbed. So, KLS6 possesses the see-through clarity of a true open baffle 'speaker, but it absorbs a significant amount of the rear radiation which would otherwise reflect off a rear wall and compromise imaging.

It is a simple idea, but one that gets the very best from the drivers by removing from the cabinets unwanted contributions to their efforts. When you are spending so much for top quality drivers, this only makes sense.

In the bass, to keep the size of the cabinet domestically acceptable (an open baffle bass system designed to reach down to 40Hz would need a baffle diameter of 14ft!) efficient bass reflex loading is used. Carefully tuned, this gives excellent bass quality, together with high efficiency.

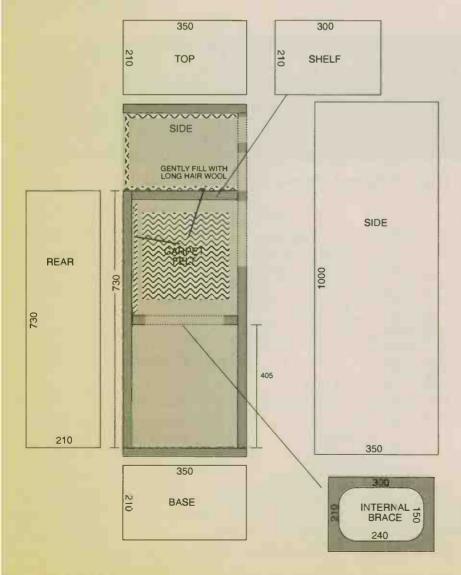The result of combining the latest technology, super quality drivers, with a cabinet designed to get the very best from them and a well designed, simple crossover using high quality components is quite something. It shows just what an amazingly high level of performance is possible from a loudspeaker nowadays, when cost is not allowed to restrict drive unit quality.



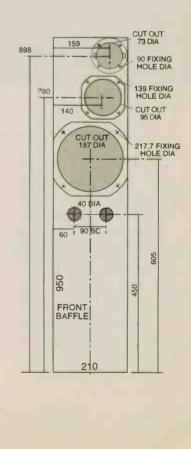

WHY LET THE SIGHT LET DOWN THE SOUND?

Introducing a choice of 'Modern Classic' or 'Modular' Chassis designs, created for the VALVE AUDIOPHILE constructor.

Crafted from thick gauge aluminium, ready for the finish of your choice!

Other materials and custom services are available upon request.

PRICES FROM £69.00 inc VAT



C H A S S I S C O M P A N Y

Send A4 SAE for details to: VCC, P.O BOX 36, LETCHWORTH, HERTS. SG6 2UR

LANGREX SUPPLIES LTD

DISTRIBUTORS OF ELECTRONIC VALVES, TUBES AND SEMI-CONDUCTORS AND I.C.S.

PHONE 1 MAYO ROAD • CROYDON • SURREY CRO 2QP

0181 684 1166 24 HOURS EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS

FAX 0181 684 3056

A selection of our stocks of New Original Mullard - Brimar audio types made in UK.

STANDARD TYPES		SPE	CIAL QU	ALITY TYPES	
ECC81 MULLARD ECC82 MULLARD ECC88 MULLARD ECH81 MULLARD ECL82 MULLARD ECL86 MULLARD EF86 MULLARD	6.00 6.00 3.00 3.50 3.50 7.50	E88CC - GOLD PIN M E88CC SIEMENS GOI E188CC - GOLD PIN M ECC81 - M8162 / CV ECC81 - 6201 / GOL ECC82 - M8136 / CV ECC83 - M8137 / CV	ULLARD D PIN MULLARD 4024 MUI D PIN MUL 4003 MUI 4004 BRIA	LARD LARD LARD AAR	8.50 8.50 8.50 6.50 8.50 6.50
GZ32 MULLARD GZ32 MULLARD GZ34 MULLARD 6SL7GT BRIMAR 6SN7GT BRIMAR 6V6GT BRIMAR	15.00 4.50 4.50	5 R4GY RCA 6 FQ7/6CG7 SYL 6L6GC GE 6L6WGB SYL 12AX7A GE	6.00 7.50 12.50 10.00 7.00	12BY7A GE 6146B GE 6550A GE 7027A GE 7581A SYL	7.00 15.00 20.00 17.50 15.00

MANY OTHER BRANDS AVAILABLE

THESE ARE A SELECTION FROM OUR STOCK OF OVER 6000 TYPES. PLEASE CALL OR FAX AN IMMEDIATE QUOTATION ON ANY TYPES NOT LISTED. WE ARE ONE OF THE LARGEST DISTRIBUTORS OF VALVES IN THE UK. SAME DAY DESPATCH VISA/ACCESS ACCEPTABLE. OBSOLETE TYPE A SPECIALITY.

OPEN TO CALLERS MON.-FRI. 9AM - 4PM. CLOSED SATURDAY
P&P 1-3 VALVES £2.00, 4-6 VALVES £3.00 17.5% VAT TO TOTAL INC P+P



KLS6 CONSTRUCTION

The cabinets for KLS6 are made from 25mm MDF, which gives a very solid, inert enclosure. It is easier and far quicker to cut all holes for drive units, ports, terminal dish, etc, before you start to glue the cabinet together. It also reduces the amount of dust inside the cabinets which can find its way into the open voice coils of the drive units.

The plans below show the general construction. The speakers can conveniently be built up on one side panel, laid flat. After the front, rear, top and bottom panels are glued into position, I put on the other side panel and held it down with weights until the glue set. Remember to do a dry run first to check that all the panels fit snugly together. In my case, even though the MDF was cut by a professional woodworker, it had to be sanded to size for a perfect fit.

Using Evostick Resin-W, apply the glue to the edges of the panels. They can then be slid into place, their 25mm thickness being enough to stand steady without panel pins. Any excess glue that oozes from the joins can be wiped away lightly with a damp cloth.

To ensure the panels are firmly pressed together, either place suitable heavy implements on top of the cabinet, or use thick, stretchy carpet tape wrapped around the cabinet to pull the pieces together. After this last step, check that the cabinet is square and that all the sides are square. The glue should still be wet enough to allow the panels to be gently pushed into line.

Once the glue is dry - overnight is normally enough for it to reach full strength - the cabinets are ready for their internal damping to be fixed into place. Carpet felt should be glued to each of the surfaces in the open baffle midrange chamber with a curtain hanging down at the back, and onto the sides and back of the main bass enclosure. As a finishing touch, I cut a neat square of black felt and glued it over the back of the open baffle chamber. Make sure you have finished wiring up first though, and that everything works, otherwise you will have to tear it off and start again.

The whole cabinet, including the open baffle midrange enclosure, is then lightly stuffed with long hair wool, to further absorb reflections and reduce the effects of standing waves. The long hair wool normally comes in knotted bundles, tease it out gently for best effect. Of course, you are free to experiment with other forms of panel treatment: BAF and Deflex pads for example. But we find that the combination of soft carpet felt glued to the panels together with long hair wool stuffing to be extremely good, as well as being cost effective.

Mount the crossover as shown in the diagram below. Because inductors, being magnetic components, have a field around them, they need to be spaced well apart and at right angles to each other to minimise inductive coupling. Again, a recommended layout is shown below. The components can be fixed to the crossover board with PVA glue, but I find a hot-melt glue gun holds them in place just as well, but the glue is more easily removable.

The wires for the midrange and treble unit have to pass through a small hole in the open baffle midrange chamber. It is very important to seal this hole either with hot-melt glue or PVA. The drive units can now be soldered to these wires and screwed into the front baffle. The tweeter should have wires attached using slide-on terminals to prevent heat damage from a soldering iron. A foam gasket made from draft excluder (you can get it in any hardware shop) should be stuck to the rear of the drive unit frames where they mate with the cabinet, to give a good air-tight seal.

WARNING!

The dust you get when working with MDF is carcinogenic. If you are going to make the cabinets yourself, purchase a good mask that covers your mouth and nose and work in a well ventilated area. Otherwise get a professional woodworker who will have appropriate safety equipment to cut the panels for you.

TESTING

A simple test to reduce the risk of any damage to your amplifier when you first plug in, is to check the impedance of the loudspeaker using a simple multimeter. Using the resistance setting they should measure around 5.2Ω across the terminals. This simple test will indicate a short with a reading below 1Ω .

TWEAKING KLS6

There are several tweaks that will affect the overall sound of this loudspeaker. Firstly, the reflex ports can be made either longer or shorter to change the box tuning. Making the ports longer moves the tuning frequency downwards, giving a flatter and deeper bass response. But this will tend to excite small rooms, resulting in a boomy or overblown sound. In smaller rooms the ports should be shortened, which reduces bass depth and peaks bass up higher, but gives greater subjective speed and punch.

Spiking the cabinets to the floor with a suitable spike kit will improve bass definition too. Spike kits are available from most kit loudspeaker suppliers and from stand manufacturers such as Apollo and Target.

More precise treble can be had by gluing a thin piece of soft foam or felt cloth around the tweeter to restrict surface waves and refraction from the front of the cabinet, and also to reduce dispersion angle, lessening off-axis treble energy that will bounce back off walls and ceiling. Images will come into better focus as a result.

Being a three-way speaker, KLS6 can be either single, bi or tri-wired. We'd recommend bi-wiring, connecting the tweeter and midrange together and driving the bass with a separate cable run. But for those with plenty of spare cable around, tri-wiring will bring a subtle improvement.

Good quality internal cable should be used to connect the crossover to the drive units. I used silver plated copper, which combines the sweetness of silver with the weight and power of a solid core copper cable. Because of the small quantity used it makes sense to use silver solder for all connections. We do not advise you to solder the wires to the tweeter however, as a touch too much heat will damage them, and replacement is costly.

Cricklewood Electronics Ltd

You don't have to spend a fortune on High Quality Valves Our valves are manufactured to a very high standard and compare favourably to brand names costing much more.

Good vaives at a	conomical on	ces	
ECC81	4.50	EL 84	4.50
ECC82	4.50	GZ34	7.50
ECC83	4.50	6L6G	6.50
EF 86	4.50	6V6GT	4.50
EL 34	8.50		

PAP £3.50 +VAT up to 6 valves

- Superseund Axial Polypropylene Capacitors

 Extremely low distortion

 Detailed acoustic properties
- High purity tinned copper leads Tight wound thick dielectric for resonance elimination
- Low dissipation factor
- * All units proof voltage tested at 150% rated voltage for 15 mins

TOO NO TELLOO FORES	yo 101 10 111113	
	Price	£
Tol + - 5%	250v	400v
100nF	0.85	1.00
220nF	0.85	1.00
470nF	0.85	1.00
1uF	1.00	1.25
2u2	1.35	1.50
3u3	1.50	1.75
4u7	1.75	2.00
6u8	2.25	2.50
108	3.00	3.50
15u	4.00	4.50
22u	6.25	6.95
25u	6.25	6.95
50u	10.00	11.00
75u	15.00	17.00
100u	19.00	21.00
125u	20.00	22.00

P&P £2.50 +VAT ini antigrappiene capacitors, signal level. Tolerance +-

2.5%					
		Price			Price
47pF	630V	.50	1nF	250V	.65
68pF	630V	.50	1.5nF	250V	.65
100pF	630V	.50	2.2nF	250V	.65

150pF	400V	.50	4.7nF	160V	.65
220pF	400V	.50	10nF	63V	.75
330pF	400V	.50	22nF	160V	.85
470pF	400V	.65	47nF	160V	1.00
680nF	4001/	60			

High quality 400V Axial Polyester capacitor very suitable for

replacing these is va	irve (a soner) a	mps. sperance	← 187b
1nF	.50	68nF	.75
1.5nF	.50	100nF	.75
2.2nF	.50	150nF	.75
3.3nF	.50	220nF	.85
4.7nF	.65	330nF	1.00
10nF	.65	470nF	1.00
15nF	.65	680nF	1.25
22nF	.65	1nF	1.50
33nF	.65	1.5nF	2.00
47nF	.65	2.2nF	2.55

Hiff Cohle

111111 0-010			
ZS18	Heavy Duty Ultrasupple	Neoprene Oxyge	n free single
screened	cable 6.5mm OD. 20/0.1	mm	£1.25 per metre
Z\$36	Red & Blue marked Fig.	8 cable, High den	sity braid stereo
screened	4mm x 2 00		£1.25 per metre
ZL79	79 strand Fig.8 speaker	cable.	
White wit	th black marker 25A max		0.25 per metre
ZL69	189 strand Fig.8 speaks	er cabie. Transpar	ent. Square &
around p	rofile		£1.25 per metre

Gold plated Low cost RCA Phono plugs & leads

PPG2	pair gold plated phono plugs with spring cable stra	in relief.
For cable	sizes up to 5.8mm Only	per pair
PPG3	as above for cable up to 8mm. Only £1.65	per pair
LPPX	Low cost phono lead with 2 gold plated phono plug	S
moulded	on each end of 1.2 metres stereo screen cable	
Only		£1.25
LPPV	as above but 5M cable Only	£2.95
LPPG	High quality 4mm red & blue marked stereo screen	ed cable
800mm	iong with 2 gold plated phone plugs each end Only	£3.95

Post & packing on Phone plus & cable £2.50. Please add VAT to all price We stock a vast range of power transistors, deales & ICs, cable connectors, or nts. 1995 Catalogue due january £2.50

Cricklewood Electronics Ltd 40 Cricklewood Broadway London MW2 3ET Tel: 081 452 0161, 081 450 0995 Fax: 081 208 1441



AUDIO DINKS

SUPPLIERS OF HIGHEST QUALITY COMPONENTS

eq.

Elna Cerafine 10,000µF/80V £20.00

Sfernice Potentiometers

Double sided P.T.F.E. Boards

Polypropylene Capacitors 47pF -120µF 99.99% Pure Silver Wire - 1/2 Price

TEL: 01724 870432

Mon. to Sat. 10am - 7pm

AUDIO LINKS

7 Fairmont Crescent, Scunthorpe North Lincolinshire, DN16 1EL

Liberty Audiosuite

a new standard in PC Audio Measurement and Analysis Systems

advanced....powerful....practical....£495

- * MLS and Gated Sinewave testing, with real phase angle
- * Amplitude, Impedance and Phase Angle vs frequency
- * Thiele/Small parameters
- * Waterfall plots and Energy vs Time displays
- * Distortion Analyser, Dual Channel Oscilloscope
- * Spectrum Analyser,..... Cepstral Analysis,.... and more...

You provide the PC (a 486DX is best) and amplifier

I supply the LAUD software + manual, the assembled mic/probe preamp and probes, the ECHO soundcard, a calibrated microphone, and all the cables ready for easy "plug and go", plus fax/ telephone support and advice for best use of this very sophisticated but easy to use system.

To order, or for more details, call Tony Seaford at

MARTON MUSIC 01282-773198



Sowter Transformers have been used by the Professional Audio Market throughout the world for at least the last twenty - five years.

Using modern technology and Computer Aided Design we are now able to offer a complete design and manufacture service.

Our current lists show a range of over 50 output, 70 power transformers and nearly 30 chokes.

E.A. SOWTER LTD P.O. BOX 36, Ipswich IP1 2EL SEND S.A.E. FOR DETAILS Tel: 0473 252794, Fax: 0473 236188

SOUND QUALITY

Having used a pair of exotic Sony carbon fibre coned monitors for a good long time, I've a general distaste for paper and plastic cones. So to date, one of my favourite loudspeaker designs has been KLS3. But along comes a design to put even this to shame.

Carbon-fibre cones, for all their strengths, have a tendency to sound 'dry'. Of course, this can be excused in the light of what else they can do, but here's a 'speaker that needs no excuses. With KLS6, you get the uncanny sensation of not hearing the drivers working. They are outstandingly neutral and clear, superbly cohesive from bass to treble and have deliciously sweet, tactile high frequencies thanks to that gold piezo-electric tweeter.

Teenage Fanclub's 'About You' is a severe test of any 'speaker - a super clean, bright recording which shows up any nasties with a vengeance. But KLS6 delivered a near-electrostatic

smoothness, yet with the subtlest of rhythmic and dynamic inflections brought into sharp relief. The HDA midrange acquitted itself very well indeed, sounding even smoother than the carbon fibre equivalent in KLS-3, while bringing a greater palette of tonal colours.

But it wasn't until Rimsky Korsakov's Scheherazade (Chicago Symphony Orchestra/Daniel Barenboim) found its way into the Da Capo CD player that KLS6's full talents became obvious. String tone was just about the best I've heard on a moving coil loudspeaker, totally devoid of grain or hardness. Imaging was excellent, but not quite in the gasp-inducing KEF/Tannoy point source league. KLS6 is weakest in the bass, where it can't quite match the outstanding performance higher up, being merely 'very good', with a tight, clean, tuneful punch devoid of boxiness.

David Price

PARTS LIST

Drive Uni

Tweeter Audax HD 3P
Midrange Audax HM100Z0
Bass Audax HM210Z0

Cros over

Twenter crossover factory-supplied with Audax HD-3P.

RI	15Ω/5W
R2	3 3Ω/5W
R3	1Ω/5W
CI	1.5µF Solen
C2	F/100V Alcap بر
C3	50 JF/100V Alcap
LI	0.47mH air core 0.502DCR
L2	0. mH air core 0.2ΩDCR
L3	5mH air core 1.302DCR

Reflex ports

38mm diameter x 85mm length.

MEASURED PERFORMANCE

The third-octave frequency response plot below shows the smooth and flat response of KLS6 through the midrange and treble. Upper treble is rolled off slightly which ensures a smooth and pleasant balance with CD.


Between 200-400Hz there is a lift in the response (+4dB) where the midrange and bass are overlapping in the near field. Further back in the listening position the response will flatten out due to cancellation around the open baffle midrange. There is still a slight lift left in this area in the far field, but this serves to add a pleasant warmth to the sound. A dryer balance can be engineered if desired by increasing the capacitor on the bass crossover network to 100µF.

The HD-3P tweeter is a 4Ω driver, and the HDA drivers' impedance falls to around 5Ω in places, making overall impedance a low 6Ω . However, impedance varies little across the audio bandlessentially residing between 4-8 Ω , so is smooth enough to match well with zero feedback amplifiers such as our 300B. If they are used with a valve amplifier


though best matching will be with the 4Ω tap selected

Again the HD-3P tweeter has an influence on the overall sensitivity possible, being an 89dB driver. Sensitivity measured at I'm using a nominal watt (2.83V) pink noise signal was 89dB, sensitive enough to be used with amplifiers capable of producing 20watts or more. **DB**

Frequency Response

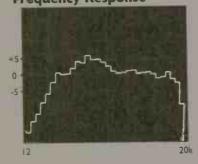

Impedance

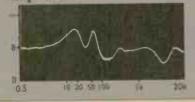


WARNING

Be extremely careful wher screwing drive units in and out of the cabinets. One slip with a screw driver and they're useless. We recommend using cross head screws or Allen bolts which reduce the chance of this happening.

Do not try and solder wires to the terminals on the tweeter. They are fragile and easily damaged and the fine wires connecting the diaphragm will vaporise, rendering the unit useless. Use small, push-on receptacle clips.

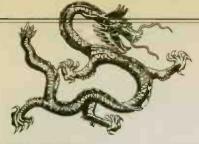A KIT OF PARTS FOR
KLS6 WILL SHORTLY
BE AVAILABLE,
PLEASE CALL WORLD
AUDIO DESIGN FOR
DETAILS
TEL: 0171 289 3533



Golden Dragon

RF.	ΤΔΙΙ	PR	ICE	LIST	
1116			IUL	LIVI	

Golden Dragon Pre-Amplifier Tubes	Singles
6AQ8/ECC85	£6.50
12AT7A/E81CC/ECC81	£6.95
12AU7A/E82CC/ECC82	£6.95
12AX7A/E88CC/ECC83	£6.95
6DJ8/E88CC/ECC88	£10.95
6SN7GT/ECC33	£8.95

Special Quality Golden Dragon Pre-AmplifierTubes

E81CC-01 Gold Pins Low Microphony Low Noise £10.50
E82CC-01 Gold Pins Low Microphony Low Noise £10.50
E83CC-01 Gold Pins Low Microphony Low Noise £9.50
E88CC-01 Gold Pins Low Microphony Low Noise £14.50

Golden Dragon Triodes

	Singles	Pairs	Quads
2A3 4PIN	£22.50	£50.00	£100.00
2A3 OCTAL	£22.50	£50.00	£100.00
211	£28.50	£60.00	£120.00
811A	£11.50	£25.00	£50.00
845	£36.50	£75.00	£150.00
805	£36.50	£75.00	£150.00

Golden Dragon 300B Range

	Singles	Pairs	Quads
300B Super	£79.00	£160.00	£320.00
4.300B	£84.00	£170.00	£340.00
4.300BLX Super	£124.00	£250.00	£500.00

Please enquire of any tube types not listed. We have an inventory of over 2,500 different types in stock.

Golden Dragon Power Tubes

	Pairs	Quads	Octets
EL34/6CA7	£25.00	£50.00	£100.00
E34L	£29.95	£60.00	£120.00
EL84	£8.95	£19.00	£38.00
E84L	£12.50	£25.00	£50.00
6L6WGB/588	1 £25.00	£50.00	£100.00
KT66	£25.95	£52.00	£104.00
KT88 Mar Designa	£57.95	£116.00	£232.00
KT88 Super	£67.95	£136.00	£272.00
6L6GC	£19.95	£40.00	280.00
6550A	£42.95	£86.00	£172.00
6550A Specia	(Guld Paris)		
	£64.95	£130.00	£260.00
50CA10	£84.95	£170.00	£340.00
807	£25.00	£50.00	£100.00

Ceramic Sockets and Hardware

	Standard	Gold	Plated
Locking 4 Pin			
(300B etc.)	£6.95		£15.00
4 Pin UX4 (300B etc.	£2.5		£3.50
Jumbo (211 etc.)	£12.50		£25.00
Octal Chassis			
(EL34 etc.)	£1.25		£3.50
Octal PCB (EL34 etc.)	£1.25		£3.50
B9A Chassis (pre am	p) £1.25		£2.50
B9A PCB (pre amp)	£1.25		£2.50
Screening Can & Skir	t (pre amp)	£8.50
Damping Can (pre an			£4.50
Power Valve Retainer	(ÉL34 etc.)	£5.50

	Golden \	Dragon
	NEW ***	NEW
	KT66 Super	£65.00 pair
	KT90	£65.00 pair
	KT90 LX	£75.00 pair
ı	274B	£14.50 each
	350B	£29.95 pair

Carriage charge £2.50 on any U.K order. Cash with order or Visa - Mastercard accepted. 24 Hour Answerphone Service.

We have a vast range of tubes available from manufacturers all over the world including rare and vintage types. A 70 page booklet of valves available is updated monthly and can be provided at a cost of £2.50 per copy including U.K postage or you may telephone our Sales Desk for a prompt quotation. Prices exclude VAT. Please add VAT at 17.5%.

A selection from our stock of over 2,500 different audio quality valves. Please enquire for items not listed

ECC81	BRIMAR	4.50	M8162/ECC81	MULLARD	8.50	65 5 0A	TEONEX	12.50
ECC82	GE	4.50	M8137/ECC83	MULLARD	24.00	12AT6	BRIMAR	2.50
ECL82	TEONEX	3.50	OA2WA	TEONEX	4.50	12AV6	RCA	2.50
ECC83	TEONEX	3.50	PCC88	BRIMAR	3.50	12BA6	WESTINGHOUSE	3.50
ECC85	TEONEX	3.50	PL36	MAZDA	3.50	12BH7A	USA	12.00
ECC88	TEONEX	4.50	PL519	THORN	5.95	12E1	STC	15.00
ECC88	BRIMAR	4.50	TT100	GEC	65.00	13D3	BRIMAR	6.50
ECF82	RCA	3.50	U19	GEC	8.50	85A2	MULLARD	6.50
ECL86	TEONEX	3.50	UCC85	MULLARD	3.50	300B	TEONEX	50.00
EF86	TEONEX	4.50	2A3	TEONEX	15.00	807	TEONEX	6.50
EF804S	TELEFUNKEN	36.00	5Y3WGTA	SYLVANIA	4.50	1625	RCA	6.50
EL34	TEONEX	6.50	5V4G	BRIMAR	3.50	5687	USA	6.50
EL86	MULLARD	4.50	6AG7	RCA	3.50	5814A	GE	5.50
EL504	TEONEX	3.50	6A7G	RCA	8.50	5881	USSR	6.50
EL519	PHILIPS	15.00	6B4G	TEONEX	29.50	6072A	USA	8.95
GZ32	MULLARD	8.50	6C8G	RCA	3.50	6146B	TEONEX	8.50
GZ37	MULLARD	4.50	6K7G	RCA	3.50	6158	BRIMAR	6.50
GZ34	TEONEX	5.50	6L6GC	TEONEX	4.50	6189	SYLVANIA	4.95
G237	GEC	5.50	6SN7GT	TEONEX	4.50	6189W	GE	5.95
KT66	TEONEX	6.50	6V6 G	RCA	6.50	6201	GE	6.50
KT88	TEONEX	12.50	6V6GT	TEONEX	4.50	6463	UNITED	7.50
M8136/ECC8	2 MULLARD	8.50	6X4	TEONEX	4.50	6870	BRIMAR	11.50

EXPORT WELCOME CARRIAGE AT COST

P.M. COMPONENTS LTD., Springhead Enterprise Park, Springhead Road, Gravesend, Kent DA11 8HD, England Sales Desk Tel: 01474 560521. Fax: 01474 333762

BD ELECTRONICS

9 SCRIPTION GILL, BRANDON, DURHAM, DH7 8BQ TEL/FAX: 0191 3780193

TANGO OUTPUT TRANSFORMERS (THE HEART OF THE WORLDS BEST AMPLIFIERS) SECONDARY IMP 4,8,16 OHMS

MODEL NO.	WATTS	P.IMP	FREQ. RESPONSE	APPLICATION	PRICE
X-10S SE	40W	10K /70mA	20Hz - 55KHz -20B	211, 845, VT4C	713.00
X-2.7S SE	40W	2.7K / 100mA	15Hz - 80KHz -2dB	300B, 2A3	678.00
XE60-2.5 SE	30W	2.5K / 90mA	20Hz -100KHz -2dB	300B, 2A3	455.00
X-3.5P PP	120W	3.5K	4Hz - 100KHz -1dB	300B, KT88,	678.00
XE 60-5 PP	60W	5K	4Hz - 80KHz -1dB	6L6GC, KT88,	480.00
XE 60 3.5 PP	60W	3 5K	4Hz - 100KHz -1dB	EL 34, 6550A	455.00

TAMURA TRANSFORMERS

SECONDARY IMP. ALL 16, 8 & 4 OHMS EXCEPT F2004 16,8 OHMS

MODE	L NO.	WATTS	P.IMP	FREQ. RESPONSE	APPLICATION	PRICE
F2004	SE	8W	5K / 100mA	30Hz - 80KHz -2dB	PX25, PX25A, DA-30, 50	340.00
F2007	SE	10W	3K / 100mA	10Hz - 60KHz -2dB	300B, 2A3	340.00
F2020	PP	50W	3.5K	10Hz - 100KHz -2dB	300B, EL34, KT66	385.00
F2021	PP	50W	5K	10Hz - 80KHz -2dB	KT88, 6L6GC, 6550A	385.00

MAGNEQUEST TRANSFORMERS

WOUND WITH OXYGEN FREE COPPER)

MACHEOUEST TRANSFORMERS (HAND

ı	SECONDAIT INT. NEE 10, 6 4 4 GIIMS EXCEL I I ESCO 10,0 GIIMS								
ı	MODEL I	NO.	WATTS	P.IMP	FREQ. RESPONSE	APPLICATION	PRICE		
ĺ	OS025	SE	25W	2K5/60mA	30Hz - 20KHz -1dB	300B, 2A3	215.00		
۱	DS050	SE	25W	5K/40mA	30Hz - 20KHz - 1dB	PX25, PX25A, DA-30	215.00		
ı	05 025	SE	25W	2K5/60mA	30Hz - 20KHz -1dB	3908, 2A3	755.00		
ı	QS025 HAS	JPRATE	D CORE AND	WOUND WITH	HIGH PURITY SILVER WIRE A	ND KIMBER SILVER LEADOU	пs		
۱	FS030	SE	40W	3K5/60mA	30Hz - 20KHz - 1dB	300B	340 00		
ı	FS045	SE	50W	3K/60mA	30Hz - 20KHz - 1dB	3008, 2A3	465.00		
ı	FS006	PSE	40W	1K25/120mA	30Hz - 20Hz - 1dB	300B, 2A3 (PARALLELL SE)	340.00		

BLACKGATE CAPACITORS OTHER VALUES AVAILABLE

VALUE		SERIES	APPLICATION	PRICE
471 × 2	50°V	SKZ	VALVE PSU	52.50
100u × 2	SUBV	SKZ	VALVE PSU	82 00
2200 F	100V	BG N	VERY LOW ESR. NON POLARISED, USE IN	230.00
4700 F	35V	BG N	PAIRS IN L-CANCEL PAIR CONFIGURATION	110.00
1080uF	25V	BG NX	FOR VERY LOW MOISE	22.50
680	35V	BG NX	POWER SUPPLIES	24.50

MISCELLANEOUS

VV - 308 POWER TRIODE (NEW 3006)	High Vacuum, Ula max 550v, la max 100mA, Guarantee 2K Hrs./ 1 yr	264.00
ZOW TOZZO Metal Film Non Industive Resistors	OR22 OR47 1R.2R2.3R3 4R7 10R 22R 33R 47R	3 45
	100R 220R 330R 470R 1K,2K2,4K7,10K,15K	3.45

ADD 22.50 DELIVERY AND THEN VAT TO ORDERS
RING FOR FULL CATALOGUE OF HIG GRADE AUDIO COMPONENTS, NEUTRIK, DELTRON, LARGE SELECTION OF GOLD PLATED CONNECTORS XLR, PHONO, 4 mm., MULTICONTACT. SEMICONDUCTORS, SOLDER, ETC.

TECHNICAL & GENERAL


Some Nece	ssitles - From the Original Classic Tu	rntable Specia	alists
Connolsseur			P&P
	BD1/2 Drive Belt	9.85	1.85
	BD1/2 Motor Suspension kit	13.75	2.25
	SAU,2 Headshell	16.75	2.55
	SAU.2 Connecting lead	15.95	3.55
Garrard	Standard Models		
	Wired arm tubes	from 12.75	2.55
	Cartridge carriers (sliders)	9.25	1.85
	Idler Wheels	9.85	2.25
	301/401 Transcription Mode/s	0.00	
	Original Thrust pad assembly	9.80	2.25
		2.95	1.85
	Onginal Idler tension spring		
	Original Speed control disc - 401	13.75	2.20
	Xeroxcopy Owners Manual 301 incl. full size		
	mounting template	7.35	1.85
	Xeroxcopy Owners Manual 401 incl. full size		
	mounting template	5.20	1.85
	Replacement Intermediate grive wheel	19.95	2.85
	Replacement 301 control knobs On-Off/Speed		
	select	pair 20.25	2.55
	Replacement 301 suppressor unit	5.65	2.25
	Replacement 301 motor pulley (-2%), (-1%),		
	(Std), (+1%)	each 12.65	2.25
	Replacement 301 Chrome plated mounting	04011 12.00	
	bolts	set 3.70	1.85
	Recommended Lubrication set - early 301	301 0.70	1.00
	or 301/401 (specify)	5.20	1.85
		5.20	1.00
Goldring/Lend		40.00	2.05
	Idler wheel (lock-nut or clip fixing)	19.95	2.85
	Arm Pivot bearings with instructions	7.85	1.85
	Spindle/Main bearing assembly complete	22.85	3.85
	Headshells	from 21.95	2.55
	Instruction books	from 4.20	1.85
Thorens .			
	TD.124 series		
	Idler wheel	19.95	2 85
	Drive belt	9.85	1 85
	Chassis spring suspension		
	(replaces 'mushrooms')	13.85	2.55
	150/160 series		
	Drive belt	9.85	1.85
	Suspension springs (-1%), (Std),(+1%)	set 10.85	2.55
	Suspension bushes	set 12.50	2.25
		from 16.90	2.55
C-all Mant D	Armboards for most models	110111 10.50	2.55
	ustbugs/Parastats/ (spares incl. Preener wicks)	24 1.0	
Carringes and	styli for 78s & Mono LPs in addition to current	Steleo FL	

TECHNICAL & GENERAL PO Box 53. Crowborough, E.Sussex. TN6 2BY Tel:- 01892 654534




256 PAGES! TONS OF VINTAGE AUDIO GEAR! 1000'S OF N.O.S. TUBES! DOZENS OF NEW & VINTAGE OUTPUT AND POWER TRANSFORMERS! 100'S OF RARE OLD MANUALS, CATALOGS

AND BOOKS ABOUT TUBE ELECTRONICS & EARLY HI-FI! ALSO COMPLETE AMP KITS, TUBE TESTERS, HARD TO FIND HIGH VOLTAGE SIGNAL AND POWER SUPPLY CAPACITORS, TUBE SOCKETS, KOOL MICS, TUBE GUITAR AMPS, MUCH MOY big Jam Bonus, Ya`ll! in THIS EDITION WE FEATURE SIMPLIFIED PICTORIAL PLANS FOR MAKIN' WESTERN ELECTRIC MODEL 91 STYLE 300B SINGLE-ENDED MONOBLOCKS! IF YOU'VE ALWAYS WANTED TO BUILD YOUR OWN AMPS BUT FEEL INTIMIDATED BY SCARY 'SCHEMATIC ONLY PLANS, THEN THIS ONE'S FOR YOU! TO ORDER YOUR COPY OF THE ANGELA INSTRUMENTS 1995 CATALOG, MAIL US A CHECK/M.O. FOR 38 OR CALL/FAX WITH VISA/MC NUMBER & EXPIRY DATE, ANGELA INSTRUMENTS, 10830 GUILFORD ROAD, SUITE 309, ANNAPOLIS JUNCTION, MARYLAND 20701, USA. PHONE (301) 725-04-51 FAX (301) 725-8823

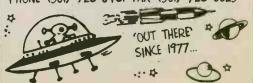

AUGUST 1995

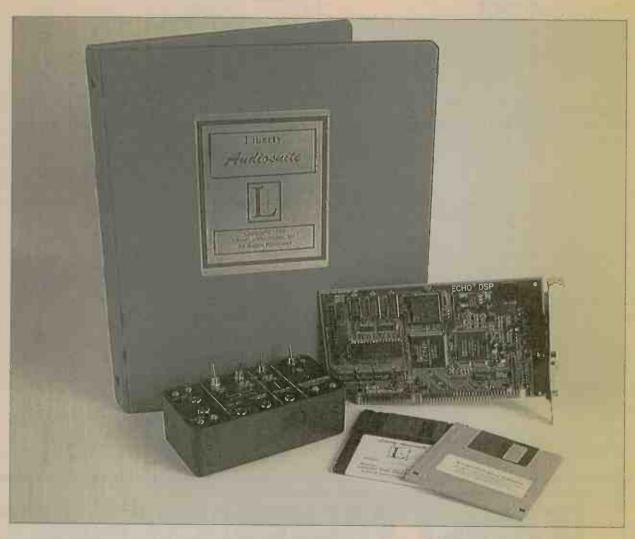

LIBERTY AUDIOSUITE - ADVANCED 'SPEAKER MEASUREMENT

Here's a complex but affordable loudspeaker measurement system.

Dominic Baker revs up his PC.

Ithough many home designed projects work well and give a satisfactory sound, getting truly top class results takes more understanding and involvement. A thorough knowledge of theory, good experience to sort the important from the (subjectively) superfluous and, finally, the ability to analyse performance by measurement are all crucial. What I'm reviewing here is a

measurement package that is deeply complex at a theoretical level, yet at the same time absurdly cheap by current standards, as far as test equipment goes, that is. It all comes down to the plummeting cost of digital processing (e.g. computers).

Nowadays, FFT analysers are becoming available at prices of less than £1000, providing you already have a powerful PC computer to do the

number crunching. That's what I'm testing here: something so powerful and sophisticated that it's a bit breathtaking. There are two snags: it's slow to use compared to dedicated industrial test instruments like our own Hewlett Packard 3561A FFT, and it relies on concepts that are obscure for those not versed in maths and measurement principles. This Liberty Audiosuite is no digital AVO. You might be able to afford it; beware that you can understand it.

The handbook is written in unusually friendly and informal prose; it's a good effort. Yet the concepts it must cover are so broad ranging and measurement-specific that some prior

knowledge is virtually a must. If you haven't mastered the difference between time and frequency domains, there's a lot to take on board here, and not all of it is explained. For example, the instrument has two channels, but cross-analysis using maths processing is barely mentioned and no explanation is provided of window properties.

The package is aimed strongly at loudspeaker measurement and has some fantastic powers, such as L/C determination from impedance and phase angle information (something we do manually), as well as Thiele-Small parameter analysis of drive units. Although the A/D processor is 16-bit, and the dynamic range in theory 96dB, reckon on a useable 80dB minimum in

practice, because of Soundcard limitations Maximum bandwidth is 22kHz and both X & Y axes are scaleable in lin. or log. form. Zoom analysis is not possible, only baseband, but four 'windows' are provided: None (for a clean pulse), Blackman, Hamming and Bingham, the last three offering progressively less weighting on a 'continuous' signal, and useable full or just with trailing edge smoothing. Cumulative decay spectra can be shown (waterfall plots), Energy-Time curves and even the Hilbert Transform can be applied. The two channels can be multiplied or divided against each other, which can be enormously useful for comparative (difference) analyses, a technique we use in tape testing, for

example, to derive a relative frequency response.

All this is impressive modern day stuff capable of placing enormous analysis power in an owner's hands. Yet as the power of modern day digital measuring systems increase, so does their theoretical complexity. It's important to bear in mind that at heart the Liberty Audiosuite is a seriously complex piece of kit by any standards and no handbook in the world, however well written, will ever makes its abilities easy to understand and exploit. Apart from this proviso, the Liberty Audiosuite package offers signal processing power as advanced as anything available today, but at a knockdown price (see p21).

Liberty's Audiosuite CAD package is essentially a collection of audio test instruments all controllable from within one package. The use of a Soundcard means that a wide range of test signals can be generated and then analysed by various different software systems, making Audiosuite highly flexible. The instruments that are included in Audiosuite are as follows.

MLS/FFT - Essentially an up-rated version of Liberty's well known and popular IMP loudspeaker test system, MLS/FFT uses the Soundcard to generate the test signal rather than a dedicated IMP module. MLS is a sophisticated variation of impulse response testing. A pseudo-random noise signal subjects the item under test to every frequency in the audio band at the same instant. The 'time domain' plot that Audiosuite then generates can be transformed, through calculation by the computer, into frequency response and phase information.

This section is very similar in operation to IMP, but with improvements made to both the measurement accuracy and graphical display. For a more detailed explanation of how MLS works, see the review on IMP in Supplement 13.

SINE - This instrument is similar to MLS, but uses a gated or continuous sine wave test signal. The sine wave signal is set to a chosen frequency and a

measurement is taken which will reveal phase (gated sine) and magnitude.

Obviously, if you were measuring a loudspeaker you would have to plot many points to build up a useful response curve, but SINE does have more energy at low frequencies and consequently better signal-to-noise ratio.

SINE - The sine instrument has a gated facility, which injects a sine wave into the loudspeaker and takes a measurement before any of the reflections from the room have a chance to reach the microphone. This is a very accurate way of measuring exactly what the loudspeaker is doing, without being influenced by the room, at least down to a certain frequency determined by the room dimensions.

SCOPE - A real-time, digital, dualchannel triggered oscilloscope instrument, combined with a sinewave and squarewave generator. The Oscilloscope is AC coupled, so can't be used to measure DC voltage levels. Both the oscilloscope and the signal generator are band limited to 22kHz, because of the use of a soundcard. The display is shown in a 'join-the-dots' format, because SCOPE samples the input signal rather than continuously monitors it as an analogue 'scope does. So where the horizontal scale gets close to the sampling rate set, the waveform displayed will be very jagged. Because of

this care needs to be taken when interpreting the SCOPE's display. The sampling rate can be set between 5.12kHz and 48kHz.

SPEC_AN - This is an FFT based spectrum analyser and matching white noise generator. The spectrum is displayed at multiples of the sample rate, divided by sample size. A useful feature of SPEC_AN is the ability to perform power averaging of the spectrum. This average power level across a spectrum, measured at different microphone positions, can be used to determine the typical or average response of an audio system within a room.

DIST_AN - Harmonic distortion analyser with low distortion sinewave source. This instrument is used for measuring and observing the characteristics of distortion that a piece of equipment produces. DIST_AN will analyse harmonics from second through to ninth, and measure the THD percentage relative to the fundamental applied. It can be used to measure amplifiers and other electronic equipment as well as loudspeakers.

DIST_AN also includes a feature called 'Visualizer'. The Visualizer measures the THD and displays a plot of the waveform tested. At low distortion levels the plot would be indistinguishable from a sinewave, but the Visualizer allows you to 'turn up' the distortion to make its effect on the sine wave visible.



Jaguar Standard Kit

This kit contains everything you need to build the speakers except the cabinets.

2 x RCF L5/090 Bass mid drivers, 2 x RCF TWT/E Titanium dome Tweeters, assembled Bi-wired crossovers, 2 x F 469
F Bi-wire connection panels, I metre A101 wadding, 6 x FT
57 Fo damping panels, 2 x reflex tubes, 8 x Grill studs, Speaker cloth, Full set of instructions and plans.

Deluxe Kit

As above but includes cabinet kits machined from 25mm MDF fully rebated for ease of construction.

Tornado Standard Kit £275pr

This kit contains everything you need to build the speakers

2 x RCF L6/090 Bass mid drivers, 2 x RCF TWT/E Titanium dome 1weeters, assembled Bi-wired crossovers, 2 x F 469 F Bi-wire connection panels, 2.5 metres A101 wadding, 12 x FT 57 Fo damping panels, 4 x retlex tubes, 8 x Grill studs, Speaker cloth, Full set of instructions and plans

Deluxe Kit

£385pr

As above but includes cabinet kits machined from 25 mm MDF fully rebated for ease of construction

RPD 10

10" Precision Devices Bass driver coupled with a 1" compress on driver and CD horn with a high quality passive crossover and Deflex panels. This speaker has ultimate precise reproductionof all types of music. Trapezoidal cabinet

HPD 10

As above but with horn loaded cabinet for ultra low bass reproduction which leaves nothing to the imagination Cabinets come assembled due to the complexity of the

101 MONITOR

This speaker is well known to all. It uses KEF drive units B101 B and T27 A combined in a small infinite baffle cabinet of only 7 Litres with a high quality crossover Incorporating electronic protection S-stop this is one best near field monitors available built in 25mm MDF



This speaker combines the latest of the new technologies from Morel and Spectra Dynamics. Available only as a Deluxe kit and contains everything you will require to build a superb set of monitors



A small infinite baffle trapezoidal cabinet with a top mounted MOREL neodiniyum dome tweeter and 5' bass mid unit. This Speaker has amazing imaging and should be placed close to the wall to achieve optimum results.

Stockists of


- · ALTAI · ALTEC LANSING · AUDAX · BAD ·
- CELESTION DESIGN REFERENCE EMINENCE •
- · KEF · MACROM · MOREL · MOTOROLA ·
- PRECISION DEVICES RCF RCL SEAS SPECTRA DYNAMICS • VOLT •



Deflex panels and Magnapads from Spectra Dynamics are an important feature to some of

cur kits. These revolutionary products in loudspeaker technology are a vast leap forward over the use of other damping materials and contribute greatly to the

standard panel

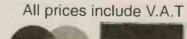



BUILDING THE AUDIOSUITE PREAMP

I chose the kit version of Audiosuite, which entails building the main preamplifier where the probes and microphone are connected yourself. It is very quick and simple to build, all of the components being mounted on one good quality printed circuit board (PCB).

I had the very first version of the build instructions, but although I managed to complete a working preamp first time, there are a few areas that would benefit from attention. The instructions rightly suggest that you solder all resistors to the board first. These are least sensitive to excessive heat, and being low height components shouldn't get in the way later on. I use a thick foam 'dishcloth' under the board which ensures the components are pushed tight against the PCB surface.

At this stage, it is very wise to also solder in an IC socket for UI, a quad CMOS op-amp. It is suggested that this static sensitive device can be carefully

soldered to the board after the resistors and capacitors. But I found it almost impossible to get the damn thing in without dropping it several times trying to get it past the closely packed surrounding resistors/capacitors. Solder in a suitable IC socket, and gently plug it in last - it's much easier and safer.


Another small point worth attention I discovered when fitting capacitors CI-3. The one that sits closest to J4, a PCB mounting phono socket, is too wide and doesn't fit. Luckily I had a $330\mu F$ electrolytic in my parts bin with a taller, slimmer can, and it fitted just fine.

A small note also needs to be included in the instructions on how to fit the LED. I had to scour the RS catalogue to remind myself that the short lead is the cathode before I could work out which way it went, a simple sketch would remove any confusion for novice builders.

Lastly, when you install the four toggle switches, I found the best way was to start by screwing them into their

correct location on the front panel. This holds them in perfect alignment, and the PCB can then be guided onto the switches from behind to ensure that the two line up. This saves having to bend the pins to get the switches through the front panel mounting holes.

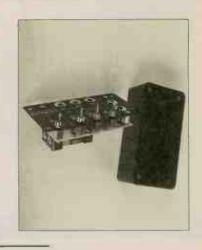The preamp took me around 40minutes to complete, and it worked first time which, given the above, shows how clear and easy-to-follow the instructions are.



SETTING UP AUDIOSUITE

The version of Audiosuite supplied by Bill Waslo of Liberty Instruments came complete with an Echo DSP Soundcard. Before you even start to install Audiosuite to your PC, it is best to install the soundcard and ensure that it is working properly. The Echo Soundcard I was using came with clear installation instructions.

Once you are sure the Soundcard is properly connected and running, Audiosuite can be installed. Again, this is a simple process, helped by clear instructions and on-screen prompts.

A little note about the hardware you will need is necessary at this point. Your PC will need to be a 386, 486 or Pentium with at least 4MB of memory and a VGA/SVGA monitor and mouse. This is quite a heavy spec. so older PCs may well have to be upgraded before Audiosuite can be used. Audiosuite needs a Personal Sound Architecture DSP type soundcard. These include: Orchid Soundwave 32 (or 32 Plus) and Gamewave 32 Plus, Cardinal Digital Sound Pro 16, Wearnes Beethoven 16-DSP, Adaptec DSP, Paradise DSP16 and Echo DSP.

Once installed, you will need to

calibrate Audiosuite for the microphone and the gain of the Soundcard and preamp you are using. This is fairly straightforward if you are using a calibrated microphone. If you are using your own preamp and microphone, the procedure is a little more complex. I won't go into it here, other than to say that it is possible, allowing meaningful, sensitive measurements to be made.

To measure hi-fi equipment you will need to make up your own special test leads. You will also need to make up the two probe leads, which need a phono plug at one end, and your choice of probe at the other.

For testing loudspeakers you will need an accurate microphone or one with a calibration chart. This, once loaded into Audiosuite, compensates for the microphone's response to give near 'perfect' accuracy. The output from the Soundcard is fed to an amplifier, which drives the loudspeaker. You can use your existing hi-fi amplifier for this, but Audiosuite must be used with an amplifier that has its negative terminal at ground potential (earth), so bridged amplifiers and many valve amplifiers are not acceptable.

CONCLUSION

Audiosuite is a very well put together package. The manual is excellent, with plenty of pictures and diagrams to help you set the system up and get measuring quickly. In the next Supplement, No.17, free with the October issue of Hi-Fi World, I will explain more about the individual instruments within Audiosuite and give examples of how they can be used to develop your own designs. Liberty have also just added a new feature to Audiosuite's repertoire under the MLS instrument, called Cepstral Analysis. This is used to detect the presence of echoes or reflections in the response of a loudspeaker, such as those caused by grilles or the edges of a loudspeaker baffle. More on this in the next Supplement.

Liberty Audiosuite £310
Echo soundcard £150
Complete with Echo soundcard,
calibrated mike + probes £495
Available from: Marton Music, 5
Masterson Ave, Read, Burnley, Lancs.
BB12 7PL. Tel: 01282 773198

SPEAKER KITS FROM IPL ACOUSTICS

Over a 8 year period I.P.L. ACOUSTICS have developed a range of high quality speaker kits, using the best units from SEAS, MOREL, AUDAX, and I.P.L. and have produced a comprehensive range of speakers which will compete with the most expensive of commercial designs.


All speakers have biwired crossover kits containing high quality components and terminals.

TRANSMISSION LINE




PLUS KIT£331.00 TOTAL KIT£446.00

FIVE **TRANSMISSION** LINE KITS

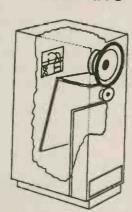

TRANSMISSION LINE PLUS KITS£166.00 -

 



S3TLM METAL TRANSMISSION LINE



PLUS KITS£166.00 TOTAL KIT£225.00



TOTAL KIT£250.00



PLUS KIT£216.50 TOTAL KIT £289.50

PRE-VENEERED CABINET KITS NOW AVAILABLE. Carriage charge extra on all kits

If you would like further details please send large SAE with 36p stamp for PAGE SPEAKER BUILDING CATALOGUE, comprising VALUABLE ADVICE on DESIGNING, BUILDING, and TESTING speakers and full technical specifications including response curves of eight kits, drive units, and details of SPECIALIST CABLES and ACCESSORIES. KITS FOR A.V. USE NOW AVAILABLE.

I.P.L. Acoustics, 2 Laverton Road, Westbury, Wiltshire, BA13 3RS. Tel: 01373 823333



Vacuum Tubes for Audio Are Back!

Glass Audio brings together yesterday's tube with today's improved components, voltage control, and the exciting new Soviet tubes, to make smooth sound in your livingroom possible again!


YES!

Please send my first issue of Glass Audio. I'll pay just \$45.00 for six issues (1 year); \$80.00 for 12 issues (2 years) of the best information on tubes to be found anywhere. I understand that my satisfaction is guaranteed!

Name	
Street & Number	
City	Postal Code
Country	REMIT IN US \$ DRAWN ON A US BANK ONLY. PRICE GOOD THROUGH DECEMBER 31, 1995
	We Accept MC/VISA.

Glass Audio

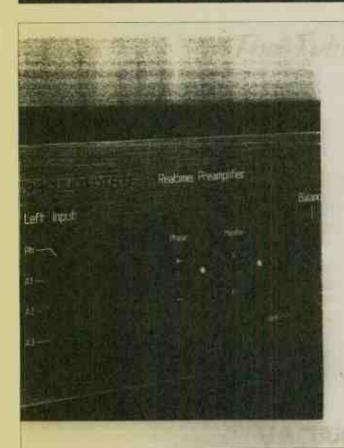PO Box 176, Dept. HFWS, Peterborough, NH 03458-0176 USA Phone: (603) 924-9464 or FAX 24 hours a day (603) 924-9467



The Tube Preamp CookBook

Allen Wright

First Edition

VACUUM STATE ELECTRONICS

TUBE PREAMP COOKBOOK -

reviewed by tube-meister Andy Grove

print, hand-drawn diagrams and a rather unusual widthways layout. It progresses from author Allen Wright's basic philosophies on audio design to complete preamp circuits marketed under the Vacuum State Electronics brand.

Allen's intuitive grasp of the subject allows him to explain in everyday language, rather than trying to make arguments look impressive with reams of unnecessary mathematics or abstruse gobbledegook. However, this book could cause a few problems for both those "new to electronics", as well as boys from the old school. It is assumed the reader already has a strong grasp of electronic theory and will understand why some of the unusual modifications work.

This is the only book I know which dares to take audio design onto a more metaphysical plane. Most like-minded thinkers either keep their knowledge a closely guarded secret or are too afraid of criticism to voice their opinions. There are plenty of cranks about spewing pseudoscience, but here the information presented is derived from solid reasoning and experimentation, albeit with a modest sprinkling of fairy dust.

Allen gives examples of human perception beyond the mechanics of eyes and ears, states his Basic Philosophies and then heads off into outer space at Warp Factor 9. His 'Building Blocks' section covers just about everything you need to know about what goes into an amplifier and even gives advice on selecting valves.

The following section is where steam will start to issue from some people's ears. Here, the reader is led through the 'Circuit Modules' Allen uses, starting off with the simple common cathode stage right up to fully differential mu followers, RIAA e.q. networks and choke input power supplies, with advice on the sonic qualities of each. Again, it is assumed the reader will not need to be nurse-maided through each circuit block; the emphasis is on the audio application, so electrical details are left to you.

Next, Allen leads the reader through the reasoning behind his 'Super Reg' shunt regulator, the differences between series and shunt types, why the shunt is superior, finally giving the outline of the Super Reg.

Using a more practical approach, he then gives examples of classic preamps and possible mods and improvements to them, illustrating different approaches to preamp

design and the good and bad points of each. He goes on to cover the development of two earlier preamp designs, describing the mistakes and discoveries he made and passing his experience on to the reader.

In the penultimate chapter he shows how to fully "hot rod" valve circuits, giving a modification checklist and useful advice on the modification procedure. The last section covers the development of two considerably more complex preamps. Full circuits are also given for those who want to produce clones.

Overall The Tube Preamp Cookbook is an excellent, if somewhat wacky look at audio design. The emphasis is definitely on sound quality rather than outright specifications, but all the same, sonic improvements are brought about by better electrical performance.


There are some mistakes in the book: for example the 12B4 valve is listed as a "12 volt heater octal base 2A3". It is in fact a B9A-based indirectly heated TV triode, nothing like a 2A3. The reader has to be aware of small hiccups like this, and take into account that this is only one person's view of the world.

I thoroughly recommend this book to anyone interested in either modifying or building valve equipment. It's a worthwhile addition to any library on the black art of valve audio

Russ Andrews Audiophile Equipment

announcing our

NEW Junior Integrated Amplifier

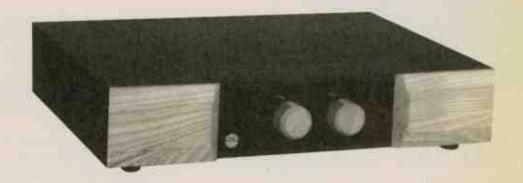

When I collected one of our 2 box Integrated Amplifiers from a home demonstration, the slightly distraught lady said;

"I'm so disappointed; I can't afford to buy it and you're going to take it away."

So we have responded to the challenge with our NEW one-box Junior Integrated Amplifier for £1,250.00 inc. VAT! Problem solved.

This musical and affordable masterpiece, can be auditioned at our Listening Rooms at Kendal, London (phone Jim on 0181 697 4912), at Birmingham (phone Dave on 0121 382 8615), and of course, in your own home.

Phone us for full details.



Russ Andrews Turntable Accessories Limited

Edge Bank House, Skelsmergh, Kendal, Westmorland, LAS 9AS, England Tel: 01539 823247 Fax: 01539 823317

oday valve data books are becoming rare and sought after. Valve suppliers often have no data or only "one line" of basic characteristics which can only really be used as a guide. Colomor Electronics have taken the initiative and reprinted a very comprehensive data book - Electronic Universal Vade Mecum, the first of a two-volume set; the second part is as yet unavailable.

Vade Mecum (Latin for General Guide) is a Polish book but the data is presented in pictorial and symbolic format that is very easy to interpret. The two indexes at the front of the book are arranged in alpha-numerical orders, one uses Roman (e.g. English) and the other Cyrillic (e.g. Greek or Russian) script, so finding the particular valve in question is quick and easy.

The valves are arranged into sections of similar types, so when you are looking at the data for one particular valve you are in exactly the right section to examine possible alternatives, although equivalents aren't always listed. Basic "one liner" information is presented in clear tables listing principle electrical characteristics, manufacturer and so on, with more detailed information below. Where abbreviations and symbols are used their meaning is usually obvious. If not, you can turn to one of the glossaries in the front of the book for an explanation. There are seven of these glossaries, each in a different language, including English, German and Russian.

Full characteristic curves are given for the more common valves and are very clearly presented. Compared with original data from manufacturers like General Electric or Mullard though, the graphs are small and have rather large graduations, making precise graphical analyses difficult. For very accurate design work it may still be necessary to get the original manufacturers data.

Other useful charts are given in some cases, for example distortion versus power for output valves or conversion conductance versus anode current for hexodes and heptodes intended for mixer use. Physical parameters such as base type, pin-out and physical dimensions are given, usually with an outline drawing showing the overall shape.


Unfortunately, because this book is about 'receiving valves', the meatiest

output valve you are likely to find is the 6550 (yawnarama) or maybe the ELI 56 (?). There are no big triodes or transmitter pentodes whatsoever. I think most people will find the power valve section rather disappointing, although there are the old faithfuls like EL34 and KT66. The mansize valves like 211, 828 or even 300B etc. are sadly absent: I assume these will be in the second volume, as and when it becomes available.

The book, although expensive, really

is essential, unless you already have a very comprehensive library of valve data. Even then Vade Mecum contains some very strange Russian and European types which I haven't seen data on before. The overall quality of the book is excellent, bound in a cherry red leather effect finish with gold lettering. Inside the printing and paper are first class. This is not a workshop data manual, more a library reference book which, I'm sure, will become classic. I hope Volume 2 comes out soon

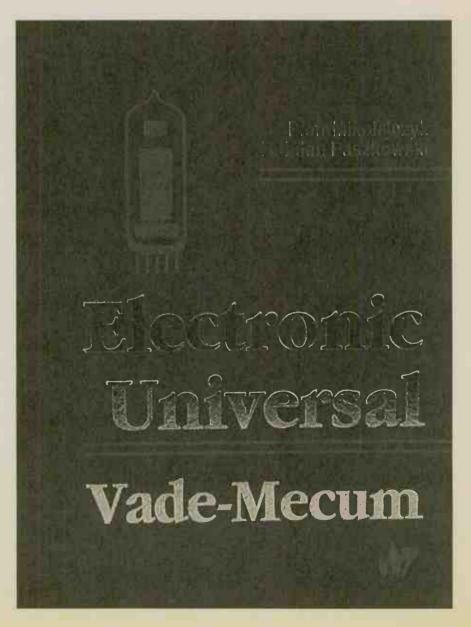ELECTRONIC UNIVERSAL VADE MECUM reviewed by Andy Grove



STATION SOUNDS

W O R T H I N G
DOWN PLATFORM WORTHING STATION SUSSEX

FOR A SELECTION OF VALVE AMPLIFIERS AND OTHER OLDER QUALITY EQUIPMENT

VALVE AMPLIFIERS (COMBOS AND HI-FI)
OVERHAULED AT SENSIBLE RATES

Valve and other equipment always wanted FISHER • RADFORD • RICHARDSON • QUAD • EMIKERR-McINTOSH • BEAM-ECHO • DYNACO • B&W TANNOY • DYNATRON • and anything interesting

I also have a selection of DIY items.

SINGLE AMPS, SPEAKERS, TURNTABLES ETC..

Including usual stock:

TANNOYS • GARRARD • PYE • LEAK • RADFORD • AUDIO
INNOVATION • FISHER • DYNACO • ROGERS •
HEATHKIT ETC..

l also stock manufacturers line ends and ex-demo models - please ring for details

MIKE POINTER

0903 39980

Evenings 0903 213192

sjs electroacoustics

New fon '95:

interstage transformers more output transformers valve phono stage kit

We are proud to announce our new interstage coupling transformers. These carefully designed and built products are in responce to requests from our customers for quality transformers with which to drive output valves. The transformers have a wide flat frequency response and excellent sonic characteristics. The two initial designs have been based around using the following valve types for drivers: 5687, E182CC, 417A, parallel ECC82. Designed around a 15mA primary current, approx 3K5 anode impedence and slight step up ratios, they can be used with a large range of output valves, including: 211, 845, 300B, 6080, 2A3 etc. We currently have available:

it101	1:1.5 ratio for SE output	£158 per pair
it102	1:1 ratio for SE output	£148 per pair
it201	1:1.5 + 1.5 for PP output	£168 per pair
it202	1:1 + 1 for PP output	£159per pair

We also have new additions to our range of high quality output transformers.

type se107	primary Z 2K5	max dc 70mA	max power 20W	suggested valve type 6080	price (inc) £48.18
Push Pull	Output Trans	sformers			
type pp 108 pp 108 pp 110	a to a Z 3K3 5K0 6K0	max dc 70mA 100mA 70mA	max power 20W 30W 25W	suggested valve type 6080 300B 5881	£58.95 £64.87 £59.87

All the above can be supplied fully shrouded, open frame or drop through as required. Please enquire about any requirements not listed here. A large range of mains transformers and power supply chokes is also available. Full "sets" for amplifiers can be supplied:

Set 1: suitable for a push-pull 5881 kit: 2xOTX, 1xChoke, 1xMains for £190
Set 2: suitable for a push-pull 300B kit: 2xOTX, 2xChoke,2xinterstage, 1xMains for £
Set 3: suitable for a single ended 300B kit: 2xOTX, 1xChoke, 1xMains for £220

We also supply a full range of quality parts including: Black Gates caps, polypropelene power supply caps, Vitamin Q caps, silver wire, resistors, speakers, Alps pots, advice and lots more.....

Finally we will have a valve phono stage kit available for late February, this will be an excellent MM to line level phono stage, with optical MC stepup transformers. The full kit will include pcb, components, casework, valves and shipping; and will sell for only £360 for the mm version.

Export and Trade Enquires welcome.
For further information and a catalogue send an A4 or A5 SSAE (38p) to:

sjs electroacoustics Ben-Dor, Lumb Carr Rd, Holcombe, Bury, BL8 4NN.

KIT BUILDING SERVICE

If you want to own one of the many kits available today, but are unsure of building it yourself, I will build it for you, at reasonable cost.

DAN HI FI ENGINEER ULEY 0181 470 9795

RESTORATION OF CLASSIC EQUIPMENT

SUITABLY QUALIFIED ELECTRONICS ENGINEER (DEGREE/MAES) WITH OVER 40 YEARS EXPERIENCE AND SPECIALIST KNOWLEDGE OF QUAD, RADFORD, LEAK, ROGERS, AND ARMSTRONG, ETC. EXTENSIVE WORKSHOP FACILITIES ENABLE ORIGINAL STANDARDS ACCOMPANIED BY DETAILED REPORTS OF WORK CARRIED OUT. CLIENTS WILL HEAR THEIR APPARATUS DEMONSTRATED PRIOR TO THEIR DEPARTURE. AVAILABLE 7 DAYS PER WEEK

CIRCUIT DATA ON OFFER (SEND SAE FOR LIST)
TEL 0181 504 5467
WOODFORD, ESSEX



D.I.Y. Letters

EARTH EXPLORER

would very much appreciate vour advice about earthing and alectricity supply safety. I am using a pair of old (late 1950s) valve power-amps that have ecently been renovated by RATA (original circuit diagram enclosed). I like the sound generally, but a persistent problem has been the relatively quiet, but annoying hum which was reduced by the renovation, but not eliminated.

The interconnects I mainly use are the pseudo-balanced configuration-type described in the October supplement; I have also tried Tandy interconnects that Eric Braithwaite enthused about for valve amps last year and find no difference as regards the hum problem. I have experimented with the use of different power sockets (one for each amp/both from the same 4-way socket etc.) which has some effect, but have

discovered recently that disconnecting the earth lead at the mains (13amp) plug for each amplifier brings about almost a complete 'cure' (the residual hum is only audible very close to the loudspeakers, and for any normal listening position is below the ambient noise level).

In normal operation there are no 'live' points on the amp, so eliminating the earthing seems quite safe. As part of the renovation (mainly new passive components) a small magnetic circuit breaker was put in to replace the mains fuse and act as a switch (when I had the mains amps they had no on/off switch). I expect the circuit breaker to handle the problem on the mains side of the power supply transformer, but presumably a potential risk is a failure in the HT line making the chassis live - is that

I assume the hum is


associated with an earth loop and the mains supply of my house which has conventional ring main wiring and, I believe, permanent multiple earthing (PME) wiring at the electricity supply company's junction box i.e. the earth circuits in the house are connected to the neutral (return) lead to the sub-station.

Rewiring the house is not a realistic option, but would a different kind of earthing of the power amp chassis, or providing a guard be possible moves? Currently I am putting up with the hum (i.e, earth wires are re-connected), but any thoughts, or suggestions which would justify my 'cure' would be very welcome Guy Woolley, Thurgarton, Notts.


Sounds like you've got a classic hum loop problem.
There are two sources.

Most common is that of

multiple earths and recirculating earth currents. This occurs when a system is earthed to the mains through two components, in your case preamp and power amp, which are also earthed together through the signal lead ground, forming a loop. As you've found, breaking the loop (anywhere, but in your case at the mains plug) stops the hum. The usual solution is to use an 'earth lift' resistor (i.e. resistor in the earth lead) - see diagram. It goes between the incoming mains earth and the amplifier.

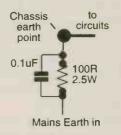

The other less well understood source of hum comes from an induction loop. This is formed when signal and return are separated to form a loop, which will pick up hum when close to a mains transformer. We've found left and right signal leads from preamp to power amp. will cause hum when drawn apart to form a loop, when a mains transformer is nearby that is. In amplifiers, signal and return wires must not be separated, but run alongside each other, as our diagram shows. NK

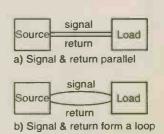

DIGITAL UPGRADE

My Arcam 170.3 CD transport doesn't have a XLR AES/EBU


AUGUST 1995

(RS422) digital output. An easy way to work with this format without modifying your CD transport is to build an external RS422 driver with phono input and a RS422 receiver with phono output. The 74HCU04 (see schematic) is used as a signal buffer with 75Ω impedance (S/PDIF format). The RS422 driver is capable of driving a balanced 110Ω cable (AES/EBU format). The driver is built into a small box with phono input. The AES/EBU cable is attached without any plugs to the RS422 receiver box. This box has a 75Ω phono output. External power supply must be capable of supplying +5V/300 mA DC. The RS422 IC's are made by National Semiconductor and perfectly made for this application. The AES/EBU cable I use is made by Gotham, I don't have any experience with other AES/EBU cables. Comparison between several digital 75Ω cables and the Gotham AES/EBU cable using the RS422, I find the sound a bit more relaxing and open. By the way this RS422 set is not a copy of the Audio Alchemy DST (Data Stream Transceiver). W. de Haan Leiden,

Mike Martindale, Chief Designer, Arcam says -

The Netherlands.

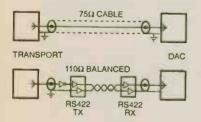Your reader is suggesting extra electronics be used at the sending and receiving end of the digitial



connection between transport and DAC. There are two reasons for this: 1) An assumption that a balanced AES/EBU cable is going to sound better than a

75 Ω cable and -2) A balanced connection will break the earth path

return line between between the two units.

These are reasonable things to consider, but it is a complicated way of going about things. Undoubtedly, it will sound different than a straight 75Ω cable and this may be taken as sonding 'better'. Personally, I would be more inclined to spend my money and time making up experimental 75 Ω leads from wire samples and evaluating them! MM

STICKY SUBJECT

1. Hi-fi manufacturers use an aluminium glue which apparently produces joints as strong as the metal itself. For example Linn assemble the Ekos in such a way. Where can I buy such glues? 2. In the last issue in his article on stereo, Noel Keywood had

an illustration in which 'speakers were turned inwards about 45degrees rather than facing fully forwards. The instructions that accompanied my Ruark Talisman IIs says all Ruarks should be positioned facing fully front on. Please ask him to discuss this aspect of positioning speakers in a later article. (He said he was writing a series on the subject). Thanks.

John Williams London.

Linn did not want to divulge the name of their aluminium adhesive, identifying it only as an Epoxy Resin. We suggest you trawl through the ever fascinating Electromail catalogue, price £4.99 ('phone 01536-204555), where you can get anything RS Components sells to industry - which seems to be everything, including hifi digital-to-analogue convertor evaluation

boards and valves, amongst a sea of special adhesives. How about 2-ton Clear Epoxy, an "extremely strong water resistant adhesive that bonds nonferrous metals", RS-price £3.50, or Plastic Welder that has "high shear, peel and impact strength over a wide range of temperature", price £5.60. Then there's Loctite Structural Adhesive 326 at £18.56, fast drying and for close fitting metal surfaces, or Loctite Multibond 330 at £9.16. The list is enormous.

On the matter of 'speaker orientation, I have to admit that my diagram was a representation, not drawn to convey exact angles. However, there's quite a lot in this topic, so here goes.

Broadly speaking, some tweeters, especially those that fire through a port or horn, like KEF Uni-O. Tannoy Dual-Concentric

_etter of

BUILDING A VOIGT TRACTRIX


I applaud your intention to examine the design of good but cheap audio equipment. It did seem to be a pity that whilst your sensitive speakers could be built for a little over £200 the 4W amplifier designed to power them cost £385. Would the Mullard 3W amplifier provide the basis for development into a good modern design, much as you have based K5881 from the Mullard 20W design? It has the advantage of a low component count, which reduces need to compromise on component quality. It is also sensitive (100mV for 3W). Would this permit design of a simple dedicated preamp for


moving magnet cartridges, powered from the main amplifier to keep down cost? The Mullard 3W has been praised on a number of occasions in your columns and a project of this type would seem to be consistent with your aims.


In D.I.Y. Supplement 11, Andy Grove presented a simple design method for the Voigt Tractrix horn but is clearly afraid of the difficulty of building one. I suggest he should look at the method of joining large profiled sheets of plywood which was invented by the designers of the Mirrorclass dinghy. The hull of this boat is made from four 10ft long plywood panels forming the bottom and sides, with two smaller panels for the bow and

stern.

These panels are first stitched together with short lengths of copper wire, inserted from the outside through holes drilled along the edges to be mated. These are twisted- together on the inside with pliers, drawing the plywood panels together. When all the panels have been joined in this manner, a strip of woven glass-fibre tape is bonded along the outside of the joint with resin. Once this has cured, the twisted wires on the inside of the joint are cut off, flush with the surface of the panel. A second length of tape is then bonded along the inside of the joint. The resultant joint is very strong and will be air-

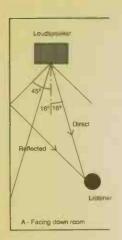

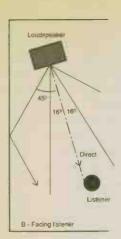

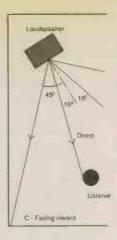

and Tonigen ribbon tweeter, all give a smoother frequency response off-axis, our measurements show. This is because on-axis, left/right mechanical symmetry results in cancellation effects. They should be positioned so as not to point directly at listeners (diagram B). In this circumstance, manufacturers usually advise users to point the 'speaker straight down the

room (A). This puts the listener, in my diagram, 16degrees (anti-clockwise) off-axis.

This situation faced me with the Heybrook Sextets, even though differences between listening on and off axis are small. I pointed the speakers straight down my lounge, as in A, and got a more muddled and vague soundstage than B. This was perplexing, because this particular room, in a

flat on short term
rental so acoustic
treatment is out, has
never provided the
excellent results of
our in-house
listening room. I
knew from
experience the
Heybrooks could
sound a lot better,
but moving them to
A from B made a
poor situation
worse.

I reasoned that if the Sextets were swung further inward (C), rather than outward, such that I sat 16degrees off-axis still, but this time clockwise, less treble energy would reach the nearside wall and more would be directed to the far side wall. Travelling further, it would experience greater attenuation, making far wall reflections less of a problem. The diagrams show how an imaginary loudspeaker

with a 32degree (+/-16°) listening window and a 90degree (+/-45°) total forward radiation angle can be swung through 32degrees with no change in perceived forward radiation pattern (i.e. frequency response) to the listener, but a significantly different radiation pattern into the room. Facing down the room (A) directs much more treble energy to the near wall, which bounces off to give a lot of reflected energy. The key point is that reflected sound from a wall is very "dirty", having a ragged frequency response caused by selective absorption. For a clean sound, the listener shouldn't be in a strong reflected sound field, or it should be diffused by a randomly varying surface.

My scheme worked better than I could have hoped, giving the sort of pin sharp imaging to which I'm

The Month

tight. A square piece of MDF can be screwed and taped in the throat for mounting the driver and a stiffening batten pinned and glued along each side of the method of fabricating large plywood structures is simple, if tedious, not requiring any great skill in woodworking. Would Andy, with a patient helper, care to have a go? **David Andrews** Cheltenham, Glos.

Most of the cost of both valve amplifiers and loudspeakers lies in their casework. The sensitive 'speaker cost little because we don't supply cabinets, not even in flat pack form. The 4W valve

amp on the other hand has expensive transformers and chassis. A 3W amplifier like the Mullard would be no different price wise, except with much cheaper casework andlor transformers. Maplin's Millenium (based on the Mullard 5-20) costs £200, but for this you get thin, unpunched aluminium casework and the smallest transformers vossible.

This well illustrates the compromises that must be juggled with. We have in truth been working on a low cost kit valve amplifier for some time now, output 40 watts per channel. Hopefully, the design will published in DIY

Supplement No17, with our October 1995 issue. This was brewed up in direct response to reader's requests.

We aren't so much "scared" of horn 'speakers as limited by time and budget. Andy is incredibly busy designing and developing products to demanding schedules, as well as answering queries, etc. We work on those things that are likely to appeal to most people. A proper horn loudspeaker is luge, very awkward to handle but of limited appeal we feel. I hope we can tackle such things in the future, but right now I'm afraid it isn't possible (like the valve synthesiser tuner I dream of!). NK



WIN A MAPLIN SOLDERING IRON KIT COMPLETE WITH A LENGTH OF SILVER SOLDER

The writer of the most interesting DIY letter each month will receive a superb Maplin soldering iron, stand, booklet on good soldering practice and a length of high quality silver solder. Write in to: Hi-Fi World DIY letters, 64 Castellain Rd, Maida Vale, London W9 1EX.

addicted. The amount of benefit will depend upon room width, wall characteristics (i.e. reflective or absorptive) and speaker dispersion characteristics. All the same, it appears to me that toeing-in heavily is more likely to give good imaging than pointing a 'speaker straight down the room. NK

AN ACTIVE APPROACH

Firstly, thanks for a most informative and worthwhile magazine. It's a refreshing change to find a mag actually concerned with its readers and what they want - not just a platform for the latest 'black box' release.

I'm an avid DIY'er, and am hoping you can point me in the right direction for my latest project: first optimising for bi-amping then building an active cross-over for my system.


This currently consists of an Audiolab 8000CDM and DAC, Mark Levinson MLI pre-amp, Plinius SA100 (Class A, 100 watts per channel) transistor amp driving the bass with a somewhat modified Leak Stereo 20 on the high end. Speakers are Lambert 300Ts: built locally, utilising 2 Tonigen tweeters and 4 bass midrange drivers in parallel, in a 2-way configuration.

As noted, the Stereo 20 has been partially modified, all bar the power caps being changed for Wimas and the input slugged to match the power amp. Is it possible to optimise it for high frequency response? Likewise, can it be modified to run in Triode mode, and is this advisable?

The next step will be to look at an active crossover. Unfortunately, the only Hi-Fi World edition I've missed (ever!) is the April edition with your active crossover! Are back-copies of the article available, or alternatively, where would you suggest I look to develop a design? My

speakers are electrically 2-way, with a crossover point at 4 kHz. Slope rates are 6 dB/octave on the woofers, 12 dB/octave on the tweeters.

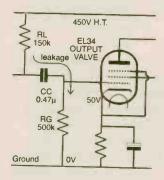On a different note, some topic suggestions for future articles: how about an article on resistor and capacitor types that could be used in upgrades - for example, when



A leaky coupling capacitor could cause the grid to became positively biased, burning out the valve.

should electrolytics be replaced with similar - (say) Black Gates, when should polypropylenes and/or other varieties be used, etc. Likewise, precision metal film verses wirewound resistors and comparisons/scoring of 'audiophile' ICs and transistors etc. What about a piece on valve symbols, their meanings, pin recognition and numbering systems?

All of my (woefully inadequate I'm sure) valve knowledge comes from avid reading of your magazine and supplements. Even so, I'm in the dark about many of the basics: while I don't have a problem reading and interpreting 'modern' circuit diagrams, none of the valve symbols (and functions) were covered at School or Tech.

I realise I've asked a lot in a long and fairly boring letter: my apologies! I've been reading your magazine since it first appeared and have watched with interest the increase in the number of copies at the local newsagents. You certainly have a loyal following here at the other end of the world (even though we have to wire 180 degrees out of phase from your circuits to allow for our inverted orientation and compensate for frequency time delays due to the 4-month delivery time!)

It's great to see that a little time and patience can result in substantial improvements on 'the latest and greatest' - and that others like yourselves have enough time and patience to show us 'plebs how. Keep up the good work: after the last few years, I feel like I know the team personally!

Darl Singh

Auckland,

Putting an active crossover ahead of the Leak Stereo 20 will remove all low frequencies from it and this in itself will give the amplifier a much easier time. We generally do not recommend you do anything to any old valve amp. other than restore it, although to be realistic if the casework is shot -damaged or rusty perhaps -then mods aren't sacriligious.

New Zealand.

Replacing the capacitors with Solen audio-grade polypropylene or, better sounding, modern Jensen (Denmark) paperand-oils from Audionote (UK) (Tel: 01273-220511/Fax: 01273-731498), will clean things up. However, because of the variable nature of the beast, some paper-and-oils can be leaky. Ideally, you need to check that current leakage isn't altering d.c. conditions after installation, especially with critical coupling capacitors (see diagram) where just 0.2mA would bias the grid positive (i.e. above the 50V on the cathode), cause the anode to glow red and the valve to burn out. These capacitors sound gorgeous however: gloriously sweet, yet with beautifully damped, dark inter-transient silences.

Don't rip out every

capacitor at once though; change just a few at a time and listen. Subjective component selection is a matter of achieving balance; filling an amp with metal film resistiors, paper-and-oils or polyprops. can swing its character too far in one direction, so be careful.

Putting a solid-state active crossover in front of a valve amplifier seems a bit contradictory to us purists, although it isn't so bad since valves always seem to add in their character even after solidstate has done its worst, although they can't retrieve what has been lost. My own recommendation for solid-state crossover design is Don Lancaster's renowned Active Filter Cookbook, published by Howard Sams & Co, Indianapolis, Indiana 46268, USA. The Modern Book Co., 19-21 Praed Street, London W2 1NP (Tel: 0171 402 9176/Fax: 0171 724 5736) can supply this mail order to you. If you want the circuit of an active valve crossover, contact Old Colony Sound Lab, P.O. Box 243, Peterborough, New Hampshire NH 03458 (Tel: (603) 924 6371/Fax: (603) 924 9467. I spotted this fairly amazing idea in one of their publications, so you will probably be looking at a book purchase here.

We'd love to do basic theory articles, but are desperately short of space at present. I think you ought to put your head into The Art of Linear Electronics, by John Linsley Hood, a new book that - unusually - covers valves as well as all other things audio. See page 101 in the main issue.

I hope all this is of some help to you. I thought they invented CD for New Zealand 'cos records kept falling off the turntables. NK



Long known as specialists in rare tube brands, Billington Export provides a line of premium-grade valves to fill the increasing demand for hard-to-find tubes! BILLINGTON GOLD features specially tested valves selected for long life, low microphony and low noise. Versions with gold plated pins are available. BILLINGTON GOLD brand comes from a variety of countries around the world. We have carefully chosen the best manufacturer for each type, with an

emphasis on the highest audio quality and product reliability. We stock one million valves including: BRIMAR, GE USA, GEC UK, MAZDA, MULLARD, RCA, RUSSIAN/SOVTEK/SVETLANA, SYLVANIA, TESLA, THERMIONIC, TUNGSRAM and other rare brands, as well as sockets and CRTs.

BILLINGTON GOLD

2A3	1550
6L6GC	6.45
12AX7	5.25
300B	60.00
811A	12.00
845	33.00
6550A	11.50
E81CC	5.25
E81CC-01	9.50
E82CC	4.50
E82CC-01	8.50
E83CC-01	8.50
E88CC	7.50
ECC81	5.25
ECC82	4.50
ECC83	5.25
ECC88	6.90
EL34	9.95
EL84	3.60
KT66	9.50
KT88	18.50

RARE BRANDS

3AMP1A Tungsram Hungary	32 40	6550A GE USA	33.00
5C-450A STC UK	259.35	CV4003 Mullard UK	POA
5R4GY USA	POA	CV4004 Brimar UK	POA
5Y3GT RCA	3.90	CV4024 Mullard UK	POA
6BH6 RCA	2.48	DG7-32 Tungsram Hungary	32.48
6L6WGB Sylvania	15.00	ECC81 Mullard UK (CV4024)	POA
6V6GT STC UK	POA	ECC82 Mullard UK (CV4003)	POA
12BH7A GE	11.40	ECC83/ECC803S Tesla	13.13
12E1 STC/ITT UK	POA	EF86 GEC UK (CV4085)	POA
13E1 STC UK	135.00	GZ32 Mazda	8.00
85A2 Mullard	5.93	GZ37/CV378 Mullard UK	POA
807 USA	POA	KT90 Yugoslavian	45.00
5687WA RCA	6.45	PL519 ECG Philips	5.95

YUGOSLAVIAN / ETC

6CG7 Yugoslavian	6.75	ECC83 Yugoslavian	3.09
6X4W Raytheon USA	3.60	ECC85 Tungsram	3.30
5751 (USE ECC83)		ECL86 Tungsram	3.45
6336A Penta USA	58.50	KT90 Yugoslavian	45.00

RUSSIAN/SVETLANA

6AS7G	4.50
6B4G	27.00
ECL82	2.25
SV811-3	22.75
SV811-10	22.75
Try us for ALL	Russian/Svetlana valves

SOVTEK

5U4G	3.60	ECC83/12AX7WB	3.50
6L6WGC	6.00	EF86	POA
6SL7GT	2.50	EL34G	6.20
6SN7GT	4.95	EL84	1.99
12AX7WA	3.50	GZ34	5.40
12AX7WB	3.50	GZ34/5Y3GT	2.90
5881/6L6WGC	6 00		

CHINESE

300B Silvertone	60.00
ECC88	3.90
EL34	7.00

SOCKETS

Jumbo 4-Pin for 211,845,etc	11.50
Jumbo 4-Pin, Gold Plated for 211	24.00
UX4 for 2A3, 300B, 811A, etc.	2.25
UX4 Large Locking Type for 300B	6.00
B5 UK	POA
UX5 McMurdo UK for 807	3.60
B7A for 6C33CB	3.23
B7G McMurdo UK, chassis, skirted	0.72
813 Ceramic	15.00
Octal McMurdo UK	1.20
Octal PCB, nylon	2.70
Octal PCB, foreign	1.20
B9A for ECC83, EL34, EF86, etc, suitable for pre-am	nps: -
- Ceramic, skirted, chassis, screening can;	
Chinese	1.20
Russian	0.90
- PCB, gold pins	2.40
B9D Magnoval, chassis, for PL519	2.25

We supply sockets for all valves listed in this advertisement

TOPCAPS

For	2C34,	807 etc	1.20
For	12E1,	5B-254M, PL519	3.60

MATCHED TESTING

£2.00 Per Valve (£4.00 per pair)

All items in stock at time of going to press. Prices in GB Pounds and subject to fluctuation: please check before placing your order.

We stock over 3000 valve types and 400 types of CRT. Please ask for our free 50 page catalogue of valves and/or our CRT catalogue.

Payment is accepted by:

ACCESS, AMERICAN EXPRESS, DEBIT CARD, JCB, MASTERCARD, VISA, Bankers Draft, Bank Telex, Eurocheque and Cheque (UK only)

MINIMUM ORDER: UK £50.00 + VAT & Carriage. Export £100.00 (US \$150.00) + Carriage



1E GILLMANS TRADING ESTATE
BILLINGSHURST
WEST SUSSEX RH14 9EZ UK
TEL: (0)1403 784961 FAX: (0)1403 783519
VISITORS STRICTLY BY APPOINTMENT PLEASE



CHELMER VALVE COMPANY

for High Quality Audio Valves

We offer below a selection of our CVC PREMIUM range of audio valves. These CVC BRAND valves are from selected world wide sources, processed in our special facility to provide low noise/hum/microphony PRE-AMP valves and POWER VALVES burnt-in for improved stability and reliability. Use this sheet as your order form. If you require matched pairs, quads or octets etc. Please allow £1.00 extra per valve for this service and mark alongside the valve type number 'M2,M4, M8' etc as required.

Price list and Order Form for CVC PREMIUM Audio Valves							
PRE-AMP VALVES				RECTIFIERS	Unit Price	Qty	Total Price
FGG01 #46 + ===	Unit Price	Qty	Total Price	EZ80	4.00	4.3	rotal Trice
ECC81/12AT7WA	5.00			EZ81	4.25		
ECC82/12AU7WA	4.50			GZ32	7.00		
ECC83/12AX7WA	5.00			GZ33	7.00	1	
ECC85	5.00	1		GZ34	6.00		1
ECC88	4.50			GZ37	6.00		
ECF82	5.00			5U4G			
ECL82	5.00			5V4GT	5.00		
ECL86	5.00			5Y3GT	4.00		
EF86	4.50			5Z4GT	3.50		
E80F Gold Pin	9.00			32401	3.50		
E81CC Gold Pin	6.20			SOCKETS ETC			
E82CC Gold Pin	6.20				Unit Price	Qty	Total Price
E83CC Gold Pin	6.20			B9A (Chassis or PCB)	1.60		1
E88CC Gold Pin	7.20			B9A (Ch or PCB) Gold	3.00		
6EU7	6.00			Octal (Ch or PCB)	1.80		
6SL7GT				Octal (Ch or PCB) Gold	4.20		
6SN7GT	4.00			4 Pin (For 2A3, 300B)	3.30		
6922	4.50			4 Pin Jumbo (For 211 Etc.)	11.00		
7025	5.00			4 Pin Jumbo Gold (For 211 Etc.)	15.00		
1023	6.20			5 Pin (For 807)	3.00		
POWER VALVES				7 Pin (For6C33C-B)	4.50		
EL34/6CA7	Unit Price	Qty	Total Price	Screening Can (For ECC83 Etc.)	2.00		
	7.50		1	Anode Connecter (For 807 Etc.)	1.50		
EL34 (Large Din)	8.50			Anode Connecter (For PL519 Etc.	1.60		
EL84/6BQ5 E84L/7189A	4.00			Retainer (For 6L6WGC Etc.)	2.00		
KT66	5.50						
	9.20						
KT77	12.00						
KT88	12.50			MATCHING CHARGES	£		
KT88 (Gold Special)	19.80			POST & PACKING (UK)	£3.00		
2A3 (4 or 8 Pin)	14.50			TOTAL EXC VAT			
211	22.00		1		£		
300B	50.50			VAT @ 17.5% (UK/EEC ONL			
6C33C-B	27.00			TOTAL TO PAY	£		
6L6GC	6.50						
6L6WGC/5881	8.00			Di			
6V6GT	5.00			Please make cheques payable to:			
6080	12.00			'CHELMER VALVE COMPANY	or pay by		1
6146B	10.20			ACCESS/MASTERCARD/VISA	Please give de	tails:	
6336A	46.00						
6550A	11.00						
6550WA	13.50						
6550WB	13.50			SIGNATURE: EXI	P. DATE:		
7581A	11.00			NAME:			
807	8.00			ADDRESS:		*******	
811A	10.50						
812A	34.00			***************************************			
845	30.00						
Total carried forward	20.00			Po	ost Code:		
VALUE ARENE STREET							

VALVE AMPLIFIERS SOUND BETTER STILL WITH CVC PREMIUM VALVES!
130 New London Road, Chelmsford, Essex. CM2 0RG. Tel: 01245 355296/265865 Fax: 01245 490064