

ELECTRONICS

Australia

with **CB and HI-FI NEWS**

NOVEMBER, 1977

AUST \$1.25* NZ \$1.25

SPECIAL OFFER ON 18-CHANNEL SSB CB RIG!

TV LISTENING AID * 5V/10A POWER SUPPLY



**INVENTORY CONTROL &
QUALITY TESTS AT TANDY**

**BONUS INSIDE:
TANDY'S 132 PAGE
'78 CATALOG**


**MORE THAN A CHAIN OF
STORES: STORY INSIDE**



WAY OUT FRONT BECAUSE THEY'RE WAY OUT FRONT



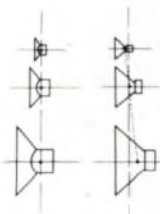SONY'S NEW G SERIES SPEAKERS. WE LINED UP THE SOUND SOURCES—NOT THE SPEAKER EDGES—TO GET THE EDGE ON THE FRONT-NAME SPEAKERS.



have found the answers:

First spring water. Like good whisky, good cone papers depend on the purity of the water used in making them. So we built an entirely new factory at Kofu at the base of Mt. Fuji where we can get all the spring water we need. Next there was the use of carbon fibre in our speaker cone paper. It's very strong and light. So our speakers are more efficient. And the carbon fibre prevents the cone from bending out of shape in the high frequency range. Moreover it doesn't resonate much. Which cuts out unwanted vibration.

We admit it, for years our front name reputation in audio and video hasn't quite been matched by our speakers.

So in 1972 we began a total new research programme specifically designed to put our speakers where all of our other stereo components have long been—out front.

After years of research and development our engineers

Then so does our use of a cast basket rather than a cheap stamped one. Finally our big breakthrough came by breaking through the standard idea of simply attaching the front of each speaker to the baffle board.

By moving our woofer and mid-range forward to a position where the sound waves originate in the same line, we aligned them acoustically. The result is transparently smooth and deep sound over the entire audio frequency range.

It's a sound that specifications alone cannot describe. But some of the toughest critics in the whole audio world can. They heard our new G Series speakers first at the last Japan Stereo Components Contest. Result? They awarded Sony the "Grand Prix".

Now hear this: The new Sony G Series speakers have arrived at your dealers. Listen to them and you'll hear just how beautiful five years' research can sound.

SONY®

Research makes the difference.

ELECTRONICS

Australia

Australia's largest selling electronics & hi-fi magazine

On sale the first Monday of each month

VOL. 39 No. 8

NOVEMBER, 1977



This month's issue carries a bonus 132-page Tandy Electronics catalog. You'll find it following p48.



This attractive 18-channel AM/SSB CB rig is currently on special offer to EA readers. You can find out how it performs on p58, and how to buy it on p54.

On the cover

Our cover pictures this month illustrate two of the behind-the-scenes activities of chain store electronics retailing: stock inventory and products acceptance testing. (Pictures courtesy Tandy International Electronics).

FEATURES

RADIO STATION CHY COFFS HARBOUR <i>Cable radio success story</i>	10
TANDY: MORE THAN JUST A CHAIN OF STORES <i>Servicing is important too</i>	14
THE MEASUREMENT CHALLENGE IN ELECTRONIC TECHNOLOGY	18

HIFI NEWS & REVIEWS

HIFI NEWS <i>BASF tape for Japanese cassette decks</i>	27
ONE MAN BAND! <i>Fantastic new music synthesiser</i>	32
REVIEW <i>Mitsubishi DA-F10 FM-AM tuner</i>	37
REVIEW <i>Standard PM-403W stereo amplifier</i>	41

THE AUSTRALIAN CB SCENE

AM CB TRANSCEIVER FROM SHARP <i>A review of the CB-800A</i>	51
CB OPERATING CONVENTIONS <i>Useful list of CB jargon and code</i>	52
CB BOOK REVIEW <i>A look at some of the literature available</i>	56
CHIBA 18-CHANNEL AM/SSB TRANSCEIVER <i>This rig's on special offer</i>	58
PHILIPS UHF PROTOTYPE <i>A brief preview of what's to come</i>	61

PROJECTS & CIRCUITS

SIMPLE MIXER FOR PICK-UP & MICROPHONE <i>Add commentary to your home movies!</i>	44
REMOTE TV HEADPHONES <i>Simple unit eliminates trailing cords</i>	62
HOW TO DESIGN TRANSISTOR HEATSINKS — <i>and keep your cool</i>	66
HOW TO CHARGE NICAD BATTERIES <i>Build this simple charger</i>	75
ELECTRONIC SCANNER FOR ORGANS <i>Simulates rotating speaker systems</i>	82
MINI BRUTE <i>5V/10A power supply for microcomputers</i>	92
TEST TONE GENERATOR <i>Checks out AM, FM and SSB transmitters</i>	100


COLUMNS

EDITORIAL	3
FORUM <i>Have a pleasant evening if you can</i>	22
THE SERVICEMAN <i>Detecting intermittents needs time and patience</i>	80
RECORD REVIEWS <i>Classical</i>	109
RECORD REVIEWS <i>Devotional, popular, jazz</i>	113
THE AMATEUR BANDS <i>What does the future hold?</i>	127
SHORTWAVE SCENE <i>World Administrative Radio Conference</i>	131

DEPARTMENTS

NEWS HIGHLIGHTS — 4/CIRCUIT AND DESIGN IDEAS — 71/LETTERS TO THE EDITOR — 91/MICROCOMPUTER NEWS & PRODUCTS — 98/BOOKS & LITERATURE — 118/NEW PRODUCTS — 121/INFORMATION CENTRE — 133/MARKETPLACE — 134/INDEX TO ADVERTISERS — 136/NOTES & ERRATA — 133
--

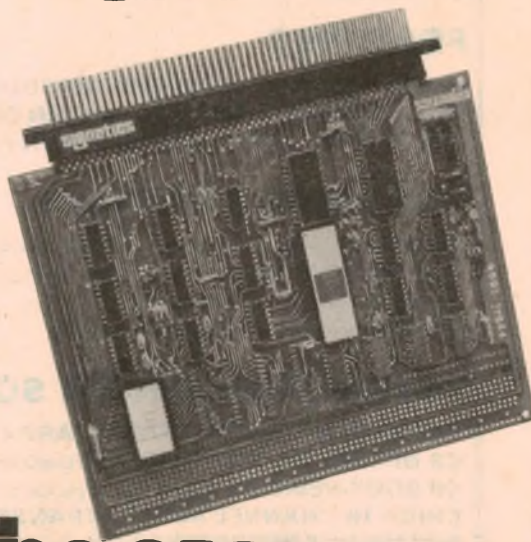ADAPTABLE BOARD COMPUTER PROTOTYPING CARD.



Two easy steps:
Plug in, Hook up
+ 5 volts, ground, and
a teletype,...and you're
in business!

Here is a short
list of features.

- 1 K BYTES ROM (PIPBUG EDITOR AND LOADER) BOARD EXPANDABLE TO 2 K BYTES ROM/PROM
- 512 BYTES RAM (2112B - 256 x 4 STATIC NMOS RAMS) BOARD EXPANDABLE TO 1 K BYTES OF RAM
- ON BOARD TTL CLOCK
- TWO - 8 BIT PARALLEL B1/D1 I/O PORTS
- RS232/TTY SERIAL I/O PORT

**The easy way
to start in
Microprocessors**

- CONNECTOR SUPPLIED
- AVAILABLE PRE-ASSEMBLED AND TESTED - 2650 PC1500 OR IN KIT FORM - 2650 KT9500

Ask your local
Philips stockist to

show you the 2650 PC1500 Adaptable Board Computer Prototyping Card, and get an easy start in Microprocessors.

PHILIPS ELECTRONIC
COMPONENTS & MATERIALS,
P.O. Box 50, Lane Cove, 2066.
Sydney 427 0888,
Melbourne 699 0300, Brisbane 277 3332
Adelaide 223 4022, Perth 65 4199.



Electronic
Components
and Materials

PHILIPS



Editorial Viewpoint

Is Herman Huyer merely sounding off?

A recent issue of "Australian Financial Review" highlighted a speech by Mr H. D. Huyer, chairman and managing director of Philips Industries Holdings Ltd. In it, he drew attention to the erosion of the local electronics industry and called for a positive statement of Government policy on which the industry could decide to reinvest or phase itself out.

He has said as much before and there may be a tendency for some to dismiss it on the basis that Huyer is "sounding off" again; or crying wolf; or merely lamenting the changing fortunes of electronics manufacturers in general, and of Philips in particular.

Frankly, we don't go along with any such light dismissal of what was said. If Mr Huyer appears to be "sounding off" the explanation is not that he has said it too often, but that he tends to be a rather lone voice crying in the electronic wilderness. Where are all the others?

Unfortunately, many of those whose voices should be heard are no longer in the industry — having been the victims of the very erosion to which Mr Huyer refers. And it is rather whimsical that the forum for the remark should have been provided by the Institution of Radio and Electronics Engineers, a group which all too eloquently reflects the change. By and large, the once strong array of commercial engineers has gone, and the Institution's meetings and committees are dominated by academics and public servants. If they lament the "good old days" at all, they do so from the security of their own Government-funded ivory towers!

Perhaps the industry was over-protected, complacent and due for a shake-up; perhaps there were good reasons to encourage the influx of manufactured goods from Asia, to bring down prices and to encourage two-way trading. But the resulting policies, which have been pursued by both the major parties, have cut employment in the industry by half and, more than that, caused a massive switch in skills from making to selling.

It is true that there is some compensating activity in areas of high technology but we have become progressively more dependent on Asian suppliers for everyday bits and pieces, and for everyday items of manufactured goods. Is the Government going to reverse the trend, arrest it at some point, or merely allow it to run its course, to the extinction of all local grass-roots knowhow?

As Mr Huyer pointed out: technology is not something a nation can suddenly decide to recover. It is a reservoir of knowhow constantly being built up in a body of people trained in a particular profession, assimilating techniques as they become available and passing from generation to generation.

W. N. Williams

EDITOR-IN-CHIEF

Neville Williams
M.I.R.E.E. (Aust.) (VK2XV)

EDITOR

Jamieson Rowe
B.A. (Sydney), B.Sc. (Technology, NSW)
M.I.R.E.E. (Aust.) (VK2ZLO/T)

ASSISTANT EDITOR

Philip Watson
A.M.I.R.E.E. (Aust.) (VK2ZPW)

SCIENCE FEATURES

Greg Swain, B.Sc. (Hons. Sydney)

PRODUCT REVIEWS

Leo Simpson

TECHNICAL PROJECTS

David Edwards, B.E. (Hons. Tasmania)
Ian Pogson (VK2AZN/T)

GRAPHICS

Robert Flynn

PRODUCTION

Danny Hooper

ADVERTISING MANAGER

Selwyn Sayers

CIRCULATION MANAGER

Alan Parker

Registered for posting as a periodical — Category B.

Printed by Magazine Printers Pty Ltd, of Regent Street, Sydney and Masterprint Pty Ltd of Dubbo, NSW, for Sungravure Pty Ltd, of Regent St, Sydney.

*Recommended and maximum price only.

Editorial Office

57-59 Regent St, Sydney 2008
Phone 699 3622

Postal Address: PO Box 163, Beaconsfield 2014.

Advertising Offices

Sydney — 57-59 Regent St, Sydney 2008
Phone 699 3622

Representative: Narcisco Pimental
Melbourne — 392 Little Collins St, Melbourne,
3000. Phone 67 3131

Representative: Keith Watts.

Adelaide — Charles F. Brown & Associates Ltd,
168 Melbourne St, North Adelaide 5006

Representative: Tom Duffy, 267 4377.

Perth — 454 Murray Street, Perth 6000

Representative: Jack Hansen, 21 8217.

Subscriptions

Subscription Dept, John Fairfax & Sons Ltd, GPO
Box 506, Sydney 2001. Enquiries: Harry Dale,
Phone 663 3911, ext 342

Circulation Office

21 Morley Ave, Rosebery, Sydney 2018
Phone 663 3911


Distribution

Distributed in NSW by Sungravure Pty Ltd, 57-59
Regent St, Sydney; in Victoria by Sungravure Pty
Ltd, 392 Little Collins Street, Melbourne; in South
Australia by Sungravure Pty Ltd, 101-105

Weymouth St, Adelaide; in Western Australia by
Sungravure Pty Ltd, 454 Murray Street, Perth; in
Queensland by Gordon and Gotch (A'asia) Ltd; in
Tasmania by Ingle Distributors, 93 Macquarie St,
Hobart; in New Zealand by Gordon and Gotch (NZ)
Ltd, Adelaide Rd, Wellington

Copyright. All rights reserved

Devices or arrangements shown or described
herein may embody patents. Information is fur-
nished without responsibility for its use and
without prejudice for patent rights. All
manuscripts, photographs and other material sub-
mitted to Electronics Australia for publication must
be accompanied by a stamped, addressed
envelope. Contributions are submitted at the
sender's risk, and responsibility for loss cannot be
accepted by Electronics Australia.

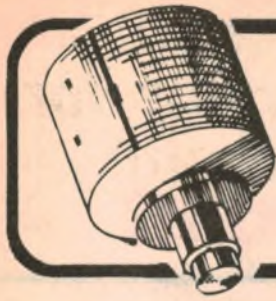

News Highlights



Computerland stores opening in Sydney, Melbourne

Little more than a year ago, a new type of retail store appeared in the USA: the computer store, specialising in hobby computers and small business systems. Since then, the stores have multiplied in a most dramatic way, with some 300 in operation throughout the USA by May this year.

One of the fastest-growing groups of stores is the Computerland chain, which is due to have around 60 stores operating by the end of this year. Operated on a franchise basis, they were started in September last year by Edward E. Faber, under the "Computer Shack" banner.

Now president of the renamed Computerland Corporation, Edward Faber has had more than 20 years' experience in the computer business. Just before launching his chain of stores, he was sales manager of Imsai, one of the pioneers in hobby computer manufacturing.

The big advantage of franchise chains like Computerland is that as a group they can buy from the manufacturers in bulk. This allows the stores to sell the products at a price significantly lower than if they were buying individually, while still being able to provide the degree of back-up service required in selling this type of product.

Starting this month, these advantages will be available to computer hobbyists and small users in Australia. The first Computerland store is opening in Sydney, right in the heart of the central business district. The location is the ground floor of a brand new building at 55 Clarence Street, and the store will have a layout and product inventory almost identical with the US stores.

A second store is due to be operating in Melbourne by Christmas, and if all goes well, there will be Computerland stores in all capital cities by the end of next year. In effect, the Computerland chain is being extended to cover Australia.

The stores will be carrying just about all of the major brand names: Apple Computer, Cromemco, DEC, Diablo, Hazeltine, Icom, Imsai, Lear Siegler, National Semiconductor, North Star, Texas Instruments, Vector Graphics and many more; also an array of tools, books and other items. And they'll be



A Computerland staff member helping customers plan their system. Pictured at right is Mr Rudi Hoess, the man behind Computerland in Australia.

offering systems planning advice, software help and service back-up.

The man behind Computerland in Australia is managing director Rudi Hoess, who with his wife also runs Electronic Concepts Pty Ltd. Like Edward Faber in the USA, Rudi Hoess has considerable experience in the computer industry. He is also very experienced in marketing high-technology consumer



goods, like calculators, digital watches and security alarms.

Based on his knowledge of the Australian market, and on insights gained from many trips to the USA, Rudi Hoess is confident that the Computerland concept will be just as successful here. If he's right, the future looks bright not just for Computerland, but for Australian computer hobbyists and small businesses as well. (J.R.)

... and we get our own Silicon Valley(s), too

Just as this issue went to press, it was announced that Cema Electronics has opened two new computer stores under the name "Silicon Valley". One of the new Silicon Valley stores is in the Sydney suburb of St Leonards, and the other in the Melbourne suburb of Richmond.

The stores are described as "professional computer stores", and are carrying a wide of microprocessor kits and associated products from manufacturers such as Motorola, Texas Instruments, AMI, Intel, National Semiconductor, Fairchild, Synertek, Burroughs and Philips. They will also be carrying a range of computer hobby magazines, such as Byte, Interface, and Kilobaud, and a broad selection of electronics components for the hobbyist and engineer — components like

RAMs, ROMs and PROMs, UARTs, multiplexers and CMOS and TTL ICs.

The stores will also be providing supporting software and in-store programming services, provided by a team of experts with a broad background in microprocessor applications. And while the stores are designed to appeal particularly to the professional and advanced hobbyist, beginners will also be made welcome.

The motto used in the stores' opening advertising neatly plays on the fact that most microprocessor components are made in the "silicon valley" area just south of San Francisco: "Build your own computer with components from Silicon Valley."

You'll find the Silicon Valley stores at 23 Chandos Street, St Leonards, and at 380 Bridge Road, Richmond.

High-speed silicon switch — controls 20,000 amps!

Small silicon wafers capable of switching at rates above a million amperes in a millionth of a second may be one of the keys to the development of laser-activated thermonuclear fusion.

The Westinghouse Research and Development Center in Pittsburgh, Pennsylvania, is testing a major candidate for this high-speed switching task — a Light Activated Silicon Switch (LASS).

This experimental solid-state device is triggered with a pulse of infrared radiation, which provides very fast and efficient turn-on of a large semiconductor area. With light pipes, an array of light-activated switches could be simultaneously operated with a single infrared pulse.

To test the capability of the LASS device, a special test apparatus was constructed at the Westinghouse Research Center. The silicon device

has demonstrated peak current pulses of 20,000 amperes, switched on at rates of 40,000 amperes per microsecond, and sustained for about 40 microseconds.

To give an indication of the development still required to satisfy the fusion application, the switching apparatus required to control a fusion-inducing laser will have to handle more than 10,000 times the power being switched today by this single LASS device.

The laser-initiated fusion concept considers the use of intense pulses of laser beams to rapidly compress small pellets of fusionable material to super-high densities and thermonuclear ignition. Present studies suggest that efficient (about 5 per cent) visible light lasers delivering about 10^{15} peak watts in less than 10^{-9} second at repetition rates of 10 to 100 pulses per second would probably be required for an operable fusion power plant.

Newcastle dealership for Dick Smith



A full Dick Smith Electronics dealership, D.G.E. Systems Pty Ltd, has opened in Newcastle. The new store is situated at 103 Broadmeadow Rd, Broadmeadow (telephone 69 1625), and is part of a growing chain of Dick Smith stores and dealerships.

Managers of the new store are Geoff Linthorne and Dave McCauley. Dick Smith Electronics is prepared to discuss the opening of dealerships for any large centre in Australia, and interested persons should contact Gary Johnston in Sydney on (02) 439 5311.

W-F entertains the press



EA Editor Jim Rowe (left) listens to Kenneth D. Boyce of Intel Corporation, USA, at a recent luncheon arranged by Warburton-Franki for the technical press. Boyce was in Australia for W-F to talk on recent developments at Intel in the microprocessor and semiconductor fields.

Flight simulator for TAA

Redifon Flight Simulation Ltd of West Sussex, England, is to build a Boeing 727 flight simulator worth over \$3 million for Trans Australia Airlines (TAA). The recent deal completes a hat-trick for Redifon, who now have three B727 flight simulators under construction. The other two are for Iraq Airways and Braniff International.

The TAA simulator will incorporate a six degrees of freedom motion system and the latest Redifon Computer Generated Image (CGI) visual system —

Novoview SP1 — which provides dusk and night scenes for occupants of the flight deck. The on-board instructor's station will have advanced visual display units providing aircraft track and approach positions, as well as exercise control facilities. At the off-board instructional station, a similar display will provide data for an Air Traffic Control Instructor.

The simulator will be completed by mid-1979 and will be installed at the airline's flight training centre at Essendon.

Polish up your metrics, says Board!

The Metric Conversion Board has asked newspapers, magazines, radio and television to polish up their use of the metric system now that Australia's conversion program has reached such an advanced stage.

The Board has been approaching the various news organisations and broadcasting networks asking them to improve their metric usage so that it complies with the International System (SI) that Australia is adopting, and to ensure that the use of imperial units in broadcast and published material ceases as soon as possible.

The MCB's Director of Public Relations, Mr Gavin Handley, praised the co-operative and progressive approach adopted by the media towards metrication in the past seven years. He

said the early use of metric units by the media helped to influence public acceptance of the new system.

The follow-up action was designed to eliminate inconsistencies and confusion resulting from having to cope with two measurement systems. Achieving this would undoubtedly help the public in assimilating metric concepts.

An MCB publication "Guidelines for Metric Reporting" has been distributed to all sections of the media, and provides practical information to help journalists convert from imperial to metric measurements, and also to avoid the pitfalls of incorrect usage. There are also sections in the booklet to assist specialist writers, e.g. for sport, motor-ing, finance and shipping and rural industries.

Teletext for the deaf

Computer portrait!

Advances in electronics promise a fuller life for the deaf and blind, with devices that give them new means of communication.

The introduction of "teletext", in which requested information is displayed on the home television screen, will be of particular value to the deaf and hard of hearing. This has been pioneered in Britain, where a group of researchers and engineers have now got together to form a charitable organisation, called Deaf-fax, with the aim of providing teletext units for deaf people.

These units can be fitted to an ordinary television receiver and allow the user to pick up the new information services which are being run by the British Broadcasting Corporation and the Independent Broadcasting Authority, as well as the telephone linked service to be set up by the British Post Office. Deaf-fax hopes to be able to provide the deaf with the teletext service at a nominal rent by using volunteers to assemble the units.

New Association

Seven major suppliers of video equipment have formed the Video Suppliers' Association to improve the availability of information to retailers and the public generally on video equipment in Australia.

The inaugural president of the new association is Mr Bob McCallum, General Manager of AWA Rediffusion. According to Mr McCallum, the association was formed following a decision by suppliers to pool information on video equipment.



This portrait of EA Editor-in-Chief Neville Williams is not a photograph. Instead, it is a computer portrait, drawn by a computer in a London department store during his recent overseas trip. The time taken by the computer? — less than half a minute!

Help save our sound heritage . . .

Have you ever thought what happens to old records, to important radio broadcasts or to tapes of personal reminiscences? For instance, in October 1890, at the Centenary Hall in Sydney, several leading politicians and stage personalities recorded their voices on "Mr Edison's Improved Phonograph".

What did Nellie Stewart sing? We don't know. Nobody thought to preserve those fragile cylinders. They would be priceless today, but they were just a novelty then.

Despite what has already been lost, there are in Australia a number of important private sound collections, while the Sound Archive of the National Library in Canberra has been

entrusted with the custody of some 260,000 records donated by individuals and institutions, and purchased from its special budget.

In addition to these discs, there are some 4,000 tapes and 4,000 cylinders — the lot amassed in just four years of operation.

But the National Library's Sound Archive is facing a serious crisis. It has inadequate staffing, inadequate premises, inadequate facilities and an inadequate purchasing budget.

The Archive is tucked away in a corner of the 4th floor of the Library, its third location in four years. Less than 10 per cent of the collection is housed on suitable shelving and only five per cent is catalogued. The rest is lumped waist-high in boxes and

cartons in odd corners of the building and — worse — over 200,000 discs are stacked outside the library in a leaky storage shed.

Recording equipment is also hopelessly inadequate.

To help the Archive, a group called the Friends of the National Sound Archive has been formed. The aim is to promote the collection, preservation, documentation and accessibility of Australia's sound heritage.

The group is planning regular meetings in all states, and will be publishing a newsletter. You can become a member by sending \$5 to the Secretary, Friends of the National Sound Archive, Box 4037, Melbourne 3001.

Electronics is where it's all happening

...if you're into it you've got it made!

It's the world's fastest growing industry... with new discoveries...new products every day. And, every day, there are more jobs...bigger salaries...better opportunities...for people who are trained.

You can be part of this boom now by training with International Correspondence Schools. Learn to design, build, install, test, control and maintain modern electronic equipment...from your own colour TV or hi-fi set to a digital computer.

Your career opportunities are limitless...in broadcasting, industry, the military, aerospace programs, medical science and communications. With your enthusiasm and ICS tuition, a well paid job and a secure future in electronics is well within your grasp.

How do I get into it? ICS have put together a FREE Electronics Career Folder. It tells you all about the many courses open to you including Communications and Broadcasting, Industrial Electronics, Computer Servicing and Audio/Radio Servicing...courses endorsed by the Television and Electronics Technicians Institute of Australia. Post the coupon and the career folder will be on its way to you without obligation. Don't wait another minute...progress won't. The big developments in electronics are happening now and the demand for skilled people is growing all the time.

Special Colour TV repair course. Colour TV is booming all over Australia, beyond the expectations of all the manufacturers, resulting in a shortage of qualified people to fill the service gap.

You could make a successful career in this growing field with the help of the ICS School of TV Servicing. You can benefit by this course - all you need is the enthusiasm to learn and enjoy rewarding work.

Your ICS course could be a start of an exciting new career or you can use your new-found knowledge to earn extra money in your spare time.

This special course is endorsed by the Television and Electronics Technicians Institute of Australia.

Send the coupon today. It could be the first step in an exciting new future for you.



Find out how you can be where it's all happening - in Electronics. Fill in the coupon and post today!

**ICS Home Study
...your passport
to success in life!**

Your invitation to join the thousands of successful ICS graduates.

To: International Correspondence Schools
400 Pacific Highway, Crows Nest, NSW. 2065
18-20 Collins Street, Melbourne VIC. 3000
182 Wakefield Street, Wellington, N.Z.

27 4550

YES!

Please send me, entirely without obligation, a copy of the:

- ICS Electronics Career Guidance Kit
- ICS Colour TV Servicing Career Guidance Kit.

MR/MRS/MISS _____

ADDRESS _____

POST CODE _____

PRESENT OCCUPATION _____

AGE _____

Take the first step -
Fill in and mail this coupon today!

ICS

PKB54430

Books

MAKE GREAT CHRISTMAS PRESENTS...




COURSE IN RADIO FUNDAMENTALS. Want to progress up to amateur radio? Learn how your CB works? Find out with this valuable reference. Cat B-2202 .. \$5.50

HINTS & KINKS Great for ideas! Amateur, Cber or experimenter. Save time & money. Cat B-2206 .. \$3.75



NEW! 1977 AMATEUR RADIO CALL BOOK. Official listing from P&T gives all calls plus lots of info. Cat B-2259 ..\$2.85

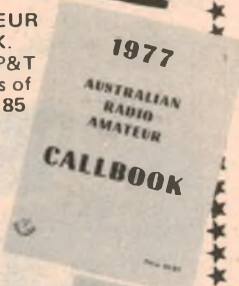HAM RADIO OPERATING GUIDE. Another value text. Ideal for novices or old hands! Everything you need. Cat B-2208 .. \$6.90




FOREIGN CALL BOOK Into DX? find out who you're talking to. A must for QSL addresses. Cat B-2262 .. \$18.00



US CALL BOOK All the names & calls the other (foreign) book misses out on! Talk to the W's & K's. Cat B-2260 .. \$18.00

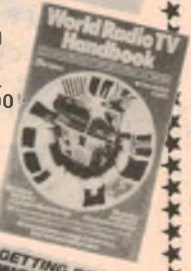WORLD RADIO TV H'BOOK Here's one for the SWL. All stations around the world. Most authoritative available. Cat B-2080 .. \$12.90




TEST EQUIPMENT FOR THE RADIO AMATEUR. You might know theory, but do you know your test gear. RSGB publication. Cat B-2048 .. \$6.50



GETTING INTO MICRO-PROCESSORS. New from Electronics Australia. Examine this fascinating new science. Cat B-2350 .. \$4.50



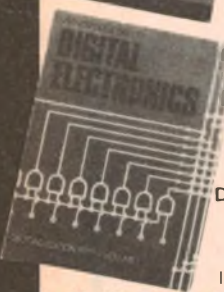DIGITAL ELECTRONICS. New from EA — up-dated and enlarged. Features modern IC theory, starts at first principles. Cat B-3622 .. \$3.00



NOW HERE'S A SWITCH...



Come home to a warm bed... turn the lights on... make a cuppa before you wake up...

You can with this great little time switch! Lets you turn an appliance or circuit on and off

twice a day. You can easily change the times, too. Fully self contained, portable. Handles up to 2400 watts (3-bar radiator).

The Autoset is made by Smith's (now there's a familiar name) so you know it's quality.

Save money — don't waste electricity when it's not needed. Let the Autoset turn the wasteful appliance off until you want it on again.

\$44⁹⁵

Cat X-1118

DON'T FORGET OUR INCREDIBLE RANGE OF ELECTRONICS AND HOBBYIST'S TOOLS... THEY MAKE IDEAL XMAS PRESENTS!!!

NOW IN! EASY ELECTRONICS VOL 2. Cat B-3630 .. \$2.50

TI SR52 Programmable

SAVE NEAR \$60.00!!!! That's right — the SR52 is now reduced way, way down. More than a calculator — the SR52 is a mathematician's dream. But it's more than a number cruncher, too — scientists, businessmen, analysts, statisticians, students — all benefit from the SR52's unique computing ability. Use TI's pre-programmed cars or program your own.

Each SR52 comes with a very comprehensive manual plus a FREE AC adaptor. Incredible machine — the tool of the future at today's — no, yesterday's prices.



NOW ONLY \$240⁰⁰

Cat. Q — 3724

OR \$213.64 TAX FREE


OPENING SOON IN MELBOURNE CITY — 399 LONSDALE ST — NEAR MYERS

DICK SMITH ELECTRONICS GROUP

SYDNEY - 125 York St. Ph: 29 1126.
 GORE HILL - 162 Pacific Hwy. Ph: 439 5311.
 BANKSTOWN - 361 Hume Hwy. Ph: 709 6600.
 PARRAMATTA - 30 Grose St. Ph: 683 1133.
 MELBOURNE - 656 Bridge Rd. Richmond. Ph: 42 1614.
 BRISBANE - 166 Logan Rd. Buranda. Ph: 391 6233.
 MAIL ORDERS: PO. Box 747, Crows Nest. NSW. 2065. Ph: 439 5311.

THE

AUSTRALIAN COMPANY

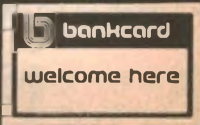

Postage & packing extra.

Dont take chances...

Is a life worth

4⁴⁹

Most electrocutions are caused by 'experts' wiring their own cords & power points. Now there is a way to check your wiring and make sure you have not created a hazard — this great little power point & cord tester. Plug it in — observe the light pattern. You know straight away if it is ok or not.

YOU COULD SAVE A LIFE — MAYBE EVEN YOUR OWN!
Cat P-5300

cheap cheap

NO, WE HAVEN'T GONE INTO THE CANARY BUSIN-

ESS (though Dick once sold white mice ...)

Look at these 'prized' IC's for extra special value ...

CT7001 Clock Chip. Long valued by experimenters — has prov. for date, alarm, snooze — circuits are available on request. Save now. Cat Z-6821 .. was \$8.90 ...
A BARGAIN AT \$6.50

2112 Memory chip: Suits Mini-scamp. Incredible special for logic experiments. Cat Z-9304. \$4.00
SAVE MONEY — BUY NOW!!!!



TEMPEST

Cassette Recorder

Wow! AC AND DC portable cassette recorder with beaut new styling — comes complete with in-built condenser microphone and carry strap. Even has a DIN socket for all the Volkswagen drivers! At our price it's a great buy. Cat A-4092 \$39.95

CMOS: 25C IMPROVED noise cancel microphone

That's right! 74C02 CMOS ICs are just 25c each! Who'd of thought it possible! Get you 74C02's from Dick while they last! But quickly! Cat Z-5412 25c!!

Dick's done it again! The new model of his famous noise cancelling microphone looks the same as before, but is better! Instead of two inserts, the new model uses a single insert which is acoustically balanced to really stamp out noise! Ideal for all CB, amateur or PA applications.

same low 99c price

C-1105

scamp: save \$12!

Dick feels generous at Christmas — and Christmas is almost here. Save now on the Scamp microprocessor kit. Learn all about logic electronics. Cat Z-9200 \$82.90

NEW...

Here is the ideal gift for all budding CBers!

'10-4, Good Buddy' is a 12 inch L.P. record describing all aspects of CB radio, including codes and jargon. The ideal complement to Dick's own CB book (see below).

\$6.99 THAT'S A BIG 10-4!!

D-9200



Hey! How about this:

89.50 save \$25.50



D-1433

NEW

It's Dick Smith's Handbook of Australian CB Radio ...

The only CB book written for the Australian CB scene. All you want to know about CB radio in this country. Even has the latest in CB rigs. Codes, channels, jargon, and much more. Foreword by Mr CB — C.W. McCall!

IDEAL CHRISTMAS PRESENT!
Cat B-2325

3.95



This is unbelievable value!!! Last month we introduced the new Hi-gain II AM set — at \$115.00. That was fantastic value for such a fine rig. The demand took us completely by surprise, so we air-lifted in another shipment to satisfy the need. And the best part: these are actually cheaper than the last shipment. Dick's quantity buying has paid off again — and you get the benefits. While they last, these incredible Hi-gain II AM rigs are only \$89.50. But be warned — we cannot guarantee this price once this shipment is sold out. Better be quick!

SAVESAVESAVESAVESAVESAVESAVESAVESAVESAVESAVESAVE!

Dick Smith products are available from all these dealers — right across Australia. Dealer prices may, in some cases, be slightly higher to cover transport costs. The Dick Smith warranty and parts back up applies to all products bought from authorized dealers. **LOOK FOR THIS SIGN:**

AUTHORISED



Dick Smith

CB DEALER

DICK SMITH DEALERS: Armidale: 72 1895, Griffith: 62 1577, Newcastle: 69 1222, Orange: 62 6491, Tamworth: 66 1363, Bendigo: 43 1977, Geelong: 94 408, Palm Beach: 34 1248, Maryborough: 21 4559, Elizabeth St: 255 2249, Port Adelaide: 47 3688, Prospect: 44 5835, Perth: 328 1599, Devonport: 24 4216, Hobart: 34 8232, Wivenhoe: 31 2560, Alice Springs: 52 1713, Darwin: 81 3491, Canberra: 80 4307, Mt Gambier: 256 404, Bathurst: 31 1200, Bega: 22 090, Bourke: 72 2129, Bowral: 61 1861, Condobolin: 95 2625, Coolah: 84, Cooma Nth: 32 709, Coonamble: 22 1877, Cootamundra: 42 1682, Dubbo: 82 3793, Dubbo: 82 2377, Finley: 83 1611, Forbes: 52 2300, Forster: 561, Glen Innes: 1219, Gloucester: 571 1152, Gosford: 24 4644, Goulburn: 21 5440, Grenfell: 43 1733, Gunnedah: 42 0222, Inverell: 22 2443, Jindabyne: 62 112, Kurri Kurri: 37 2141, Laurieaton: 599 060, Lavington: 21 6058, Leon: 53 2081, Lismore: 21 3741, Lismore: 21 3189, Lithgow: 51 2563, Milparinka: 4, Mudgee: 72 1413, Nowra: 23 628, Peak Hill: 31, Rylstone: 77, Shell Harbour: 95 1175, St. Grafton: 42 3400, Sydney: 31 0673, Taree: 52 1488, Tullamore: 75, Wagga: 21 2125, Walgett: 243, Wellington: 1002, West Gosford: 24 1768, West Wyalong: 424, Wollongong: 29 2254, Wollongong: 29 5876, Drouin: 25 1342, Horsham: 82 3724, Mildura: 23 2438, Mildura: 23 4432, Sale: 44 2677, Shepparton: 21 9006, Wangaratta: 21 5907, Warrnambool: 62 4070, Biloela: 26 126, Bundaberg: 724 263, Cairns: 54 1035, Dalby: 62 2389, Edmonton: 55 4235, Gladstone: 72 3949, Gympie: 82 1327, Lota: 396 9010, Margate: 284 2341, Mackay: 511 211, Miles: 118, Nambour: 411 100, Proserpine: 45 1071, Rockhampton: 27 4004, Toowoomba: 32 3766, Townsville: 79 8844, Victoria Pt: 207 7308, Adelaide: 223 6539, Cleve: 99, Narrung: 11, Peterborough: 307, Port Lincoln: 82 1981, Renmark: 86 6682, Wallaroo: 211 017, Whyalla: 455 766, Yorketown: 29, Bunbury: 212 777, Carnarvon: 411 362, Claremont: 862 433, Kalgoorlie: 21 1906, Paraburdoo: 895 200, x 368, Port Headland: 732 504, St. Fremantle: 355 875, Tom Price: RMDodson, Waroona: 331 595, Avoca: 842-166, Launceston: 31 5688, Launceston: 31 5815, New Norfolk: 612 553, Triabunna: 57 3135, Darwin: 81 5411.

CHY— cable radio success story

Cable radio has been well established in Britain, Europe and the United States for some years now. However, many readers will be surprised to learn that a cable radio station has been operating successfully in Australia for the last four years. The station, Radio CHY, is run by senior high school students, and has had a significant impact on the small north coast town of Coffs Harbour in NSW. Here we tell the story of Radio CHY.

The Sydney Opera House and Radio CHY, Coffs Harbour, have one thing in common — they both grew out of a hole in the ground. Above that level the similarity ends. The footings for CHY were dug in 3½ hours on Saturday, 12th August, 1972, and measured just six metres long by two metres wide.

How did it all begin?

Captain John Townsend of the Salvation Army and his family were on holidays in Brisbane when a letter arrived from Salvation Army Headquarters advising that they were to leave Gladstone in Central Queensland and take up a new appointment in Northern NSW by the end of January 1972. Sent to take command of the Salvation Army in the rapidly developing town of Coffs

Harbour the captain had no thoughts of building a radio station.

During his first few months in Coffs Harbour, Townsend established a "Space Club" for boys and girls of primary school age. One night the children were invited to bring their favourite records from home to play "radio" by pretending to be disc jockeys. The experiment proved so overwhelmingly successful that the captain decided to build a small room at the rear of the Salvation Army property to be used as a "Communications Laboratory".

The proposal seemed straightforward enough to the Salvation Army Property Board and approval was given to erect a two-storey building using voluntary labour.

It seemed a pity to devote so much

time and energy to a "Communications Building" that lacked an audience with which to communicate. Townsend recalled that Telecom telephone lines were used in Sydney for the distribution of "piped-music" programs. Why not employ the same system for a student radio station?

A letter, setting out the proposal, was dispatched to the Postmaster-General. The matter was duly considered by the Department and the Australian Broadcasting Control Board, and approval given to operate the service subject to certain conditions, viz:

- (a) the service not carrying advertising material; and
- (b) the preparation of a properly engineered proposal by the Salvation Army in association with the Post Office.

The government "green light" had been given!

As the building began to take shape an approach was made to the English Master of Coffs Harbour High School, Ed Gormley, to gauge his reaction to the proposal that secondary school students be invited to run a landline radio station. (By this time Townsend had realised that the project was way beyond the capacity of primary school students.)

Gormley realised that the idea had exciting possibilities. He took the matter up with the Department of Education and was delighted when they agreed to release students from school for one half day per month to participate in CHY. Another milestone had been laid!

It is true to say that CHY owes much

About radio station CHY . . .

- Radio CHY is the first cable radio station to gain official approval to operate;
- The program is fed by Telecom line to the Coffs Harbour telephone exchange after suitable compression and line isolation;
- The signal at the exchange end goes into a "splitting amplifier" which allows distribution of the program to subscribers;
- CHY operates 16 hours per day, seven days a week, 52 weeks a year. Broadcasting commences at 6.00 am and ceases at 10.00 pm;
- Over 100 secondary school students provide the announcing team needed to maintain the high level of program output;
- CHY is in the business of training announcers. To ensure that there is an adequate supply of qualified announcers, a training program is continuously operated.

of its origin to the enthusiasm of a small group of students from Coffs Harbour High School. Brought together to form the nucleus of the station, they quickly set about to fan life into the project.

The first step was to swell meagre finances by holding an "Announcethon" in the window of Waltons department store. Andrew Couchman felt tired but triumphant when he emerged from the store after clocking up 50 hours of nonstop announcing.

The students worked tirelessly for seven months with the result that the nation's first student-run cable radio station was officially opened on 1st December, 1973.

Enter Rodney Swansborough. Swansborough was a member of the English staff of Orara High School when approached by John Townsend to join CHY. Motivated by curiosity and the challenge of a unique innovation, he readily accepted the invitation to spend his spare time in CHY.

Swansborough's knowledge and understanding of students proved advantageous. He quickly came to the rescue when a crisis developed over the allocation of student announcing shifts. Some students were being grossly overworked. A vigorous recruitment campaign was set in motion and a disaster averted.

Community goodwill and generosity had provided the basic capital resources that covered a vacant patch of grass with a broadcasting studio. However, the immediate challenge facing the management of CHY was how to develop a legitimate means of funding that would provide for the day-to-day operational expenses of the station.

The Broadcasting Control Board had insisted that the station should not broadcast advertisements. Fortunately the Control Board, with customary thoroughness, had defined "advertising" in one of their Program Standard's publications. Section 37 of "Television Programme Standards" (1970) stated: "The term advertisement does not include the brief announcement of a sponsor's name and business at the beginning and end of a program which is scheduled for a duration of not less than 15 minutes . . ."

It provided the solution to CHY's fund-raising dilemma. The Board and Telecom gave approval for the station to broadcast sponsorship announcements, and this has remained the means for the raising of revenue ever since.

Technical problems retarded the early growth of the network. Prior to the opening of the station Telecom had introduced stringent regulations governing the attachment of electrically powered equipment to Departmental landlines. In order to comply with these regulations CHY had



Student announcer Linda Hill in CHY's main production studio.

"In theory CHY is a student-run cable radio station. In reality it is a composite of personalities, a friendly meeting place . . . and a direct stimulus for heads filled with ideas."

—student announcer Milli Nord

to design a protective interface unit and gain approval to connect it across Telecom lines.

The Department was sympathetic to the plight of the student broadcasters and managed to locate an engineer named Trevor Smith who accepted the challenge and designed a satisfactory unit, appropriately called a "Smithlab". The CHY kids hailed him as an instant hero. Six months after the official opening additional listening outlets were added to the Network.

Technical help came from other quarters, too. Paul Linsley was in Albury when he first heard about CHY. He hitch-hiked to Coffs Harbour and placed his technical skills at the disposal of the station. Two Sydney radio stations (2SM and 2UE) had previously donated valve-powered AWA Consolettes to CHY, but it took the patience and ingenuity of Paul Linsley to adapt them to CHY's needs. Paul

stayed in Coffs for about nine months and proved a great asset to the station.

The government wasn't to be outdone either.


"We've got the grant" said Rod Swansborough as he put down the telephone, his face covered with a \$25,000 grin. The Australian Government Karmel Schools Commission had approved an Innovations Grant to CHY. These funds opened the way for CHY to be technically refitted with modern broadcasting equipment. The grant also provided for the establishment of an "Educational Network" which would link all schools in Coffs Harbour to their private network for the transmission of locally produced educational programs.

The station had come of age!

This (second) network is available to the schools within Coffs Harbour during school hours. The s

ل.ب.ب.ا

top
forte

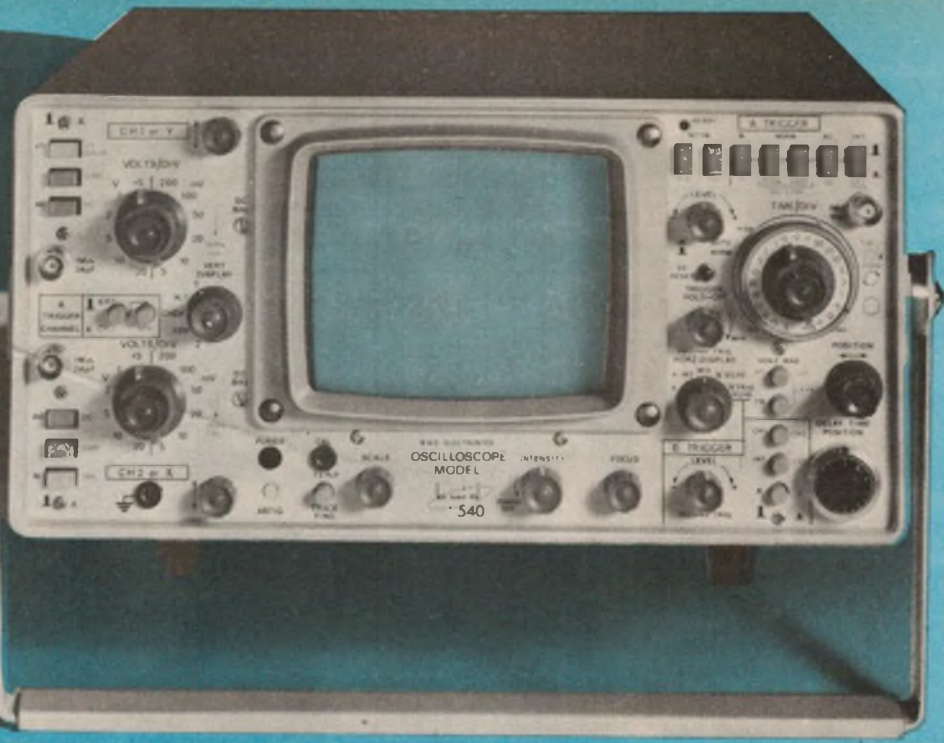

BWD540
Dual Trace
DC-100MHz -3db
5mV sensitivity
5nSec. sweep speed

*Computers, μ -Processors,
Research and development,
Field service*



BWD539D
Dual Trace
DC-20MHz -3db
5mV sensitivity

*Colour TV,
C.B. Radio,
 μ -Processors,
Video & audio
recording.*



BWD504
DC-6MHz
10mV sensitivity

*Education,
Hobbyists,
X-Y monitor*

BWD
ELECTRONICS
PTY. LTD.

Miles Street, Mulgrave, Victoria, 3170
Telephone 561 2888. Telex 35115

- N.S.W. Amalgamated Wireless (A'asia) Ltd., Sydney. Phone 888 8111
- QLD. Warburton Franki (Brisbane) Pty. Ltd., Phone 52 7255
- S.A. Protronics Pty. Ltd., Adelaide. Phone 51 4713
Rogers Electronics, Adelaide. Phone 42 6666
- W.A. Cairns Instrument Services, Perth. Phone 25 3144
- TAS. Associated Agencies Pty. Ltd., Hobart. Phone 23 1843

CHY — cable radio success story

currently connected to the network receive programs via the CHY studios and have all participated at some stage in their production. The Second Network is able to involve every school child in Coffs Harbour and environs in CHY's activities and make available to them the station's professional studio and recording facilities, its extensive record library, plus the experience and expertise of the CHY personnel.

Excursions from schools throughout the North Coast region are conducted regularly through the CHY complex. CHY staff also visit the schools within the Coffs Harbour area as well as travelling further afield offering advice to other schools and groups interested in setting up similar projects.

By the end of 1974 CHY had grown from infancy to late adolescence. The Salvation Army reviewed the progress of the station and came to the conclusion that it was impossible for John Townsend to run both the station and the Corps (Parish). They decided that another officer should be sent to run the Corps and that Townsend be appointed full-time to Radio CHY.

Following the implementation of the Karmel Schools Commission Grant the NSW Department of Education assessed the educational potential of CHY and decided to appoint a secondary school teacher to supervise all student and educational activity. Rod Swansborough, an obvious choice, got the job. The stage was now set for real growth and consolidation.

The need for additional full-time staff became very obvious early in 1976 but it wasn't until later in the year that the much needed help arrived. The mild-mannered Ian Stevenson, complete with technical skills and an analytical mind, vocationally adopted CHY and within a short space of time had the technical facilities of the place finely tuned. And Bronwyn Bell, vivacious and indefatigable, moved out of Coffs Harbour High School with the ink still wet on her School Certificate to turn her part-time job as student Program Manager into a full-time career.

The extent to which Radio CHY has been accepted as an integral part of the life of Coffs Harbour is self-evident from the number of landlines now extending into business and recreational premises in the town — over 30 at last count. Included are theatres, shopping malls, seven motels, supermarkets, pharmacies, small businesses, and even a banana packing shed!



A student announcer broadcasting from the window of Walton's Department Store, Coffs Harbour. CHY has been well accepted by the business community.



The record library provides an ideal setting for programming discussions.

Yet the future of CHY remains clouded in doubt. The substantial costs associated with the installation of cable into private homes impose severe limitations on the natural growth of the network. CHY listeners cannot understand why the station does not broadcast like a conventional radio station. One of the continuing disappointments of the students involved with CHY is that they are unable to listen to the station at home.

Radio CHY's quest for an "on-air" broadcasting licence has been plagued with broken promises and bureaucratic ineptitude. Both Labor and Liberal Governments have recognised the

value and viability of this community-media operation, having on many occasions conveyed their support to the CHY management for the acquisition of a Broadcasting Licence for CHY.

As a result Radio CHY has been on "stand-by" for the past three years ready to commence broadcasting. CHY has the necessary administrative and programming experience, technical equipment, and proven financial viability, as well as wide local community support. All it now awaits is a decision from the Federal Government and the Licensing authorities.



TANDY: more than just a chain of stores

by PHILIP WATSON

When most people invest in a piece of electronic equipment they tend to take it for granted that the firm from whom they bought it will stand by the product — provide a warranty period, service facilities, and a stock of spare parts. But is such an assumption always valid? And when it is, do they ever stop to think about the organisation behind such back-up facilities?

It is true that most organisations will stand by the product they sell, if only for the reason that they are jealous of their good name and reputation; the reputation on which they depend for continued custom. But it is unwise to automatically assume that any product you buy is so protected. The wise buyer will make sure that such protection is spelled out in detail.

This is particularly important when items are offered at "bargain" prices by organisations of doubtful background. One of the ways to offer a lower than normal price is to simply retail the items with little or no back-up; doubtful warranty in the event of premature failure, and no provision for spare parts or service facilities when these are needed.

The simple fact is that providing such services costs money, and this cost is inevitably reflected in the price of the product. So, we can have a cheap product without any back-up, or a

more expensive one with back-up; most people prefer the latter.

To get some idea of what is involved in providing such back-up facilities, we accepted an invitation to visit the head office of the Tandy organisation in the Sydney suburb of Rydalmere, NSW, and inspect their service and spare parts facilities.

The Tandy organisation commenced operation in November 1973 with three stores, and has since experienced a remarkable growth rate. It now has 109 stores throughout Australia, and is still expanding. The stores carry a large range of electronic items, from minor components and accessories to audio amplifiers, receivers, transceivers, tape recorders, etc.

All the items they sell carry a warranty. In the case of major items, the warranty details are included in the owner's manual. In the case of minor items it is an automatic 90-day warranty, the details of which are normally dis-

played on a poster in every Tandy store.

Their warranty, incidentally, is virtually worldwide. If a customer purchases a Tandy product in say, England, while on an overseas tour and, on arriving back in Australia, finds that it needs attention, then this will be available at the nearest Tandy store. All that is necessary is to produce the sales docket from the store where it was purchased.

Our visit was organised by Mr Gordon Heyes, quality control manager for Tandy in Australia. And, as we quickly learned, his department is concerned with a lot more than simply ensuring that a product can be serviced after the customer receives it. In fact, as the term "quality control" implies, the primary aim of the department is almost the opposite: to ensure that the customer doesn't need service after he or she buys the product. But if service is needed, they are fully equipped to provide it.



Opposite page: Mr Tomo Yamamoto is Tandy's resident electronics engineer. Using this well equipped test bay he checks the quality of each shipment from Asian contractors. Above left: Part of the computer system which is about to take over the stock and other routine records of the quality



control department. Above right: Spare parts by the thousand! This is just one of several large component storage bays used to back up the warranty and service facilities. An effective stock control system provides immediate access to any component.

While about half of Tandy's products are manufactured in one of the company's 16 factories located around the world, certain items such as audio equipment, receivers, transceivers, etc, are made under contract by other manufacturers, mainly in Asia. And this is where the quality control starts — with the drafting of specifications and letting of the contract to a particular manufacturer.

Before such a manufacturer is given the go-ahead for large scale production he is first required to make a number of sample models. These will vary slightly, according to the market for which they are intended — i.e., USA, Europe, Australia, etc. Mains operated devices, for example, intended for the European or Australian markets must be suitable for 220V to 250V operation, rather than 110V as in the USA. Also frequency conscious devices such as turntables must be suitable for 50Hz rather than 60Hz.

Over and above that, Australia, and most European countries, have very strict standards for mains operated appliances. In Australia, for example, appliance transformers are required to use double bobbins to separate the primary and secondary windings, in the interest of maximum safety.

The power cord must also conform to local requirements. If it is a two wire cord it will be accepted only if the insulation of the appliance itself meets the necessary requirements. Otherwise a three wire cord must be fitted and, in either case, must be terminated in a standard three pin plug.

One of these samples is sent to each area and, in fact, one arrived in Mr Heyes' office while he was explaining this procedure to us. It was a very attractive portable stereo cassette recorder with AM/FM tuner, which the company plans to market as soon as all tests are completed.

This sample had already been evaluated by a Tandy engineer on duty at the contractor's factory, and his written report accompanied the sample. It amounted to several pages of performance figures, reports, comments, etc.

As well as the electrical performance tests it would have been submitted to extremes of temperature in ovens and refrigerators, far exceeding those likely to be encountered in practice. It would also have been given a vibration test and a drop test, the latter in the type of transport package normally employed.

At this point, the firm might be excused if they accepted the findings of their overseas engineers, and simply evaluated the product on its general appeal to the local market. In fact, the entire electrical performance will be checked, as will its mechanical condition following the journey from overseas.

For this purpose a very comprehensive test bay has been set up, equipped with a high performance CRO, audio generator, HF generator, VHF generator, UHF generator, meters, etc, to enable the local test engineer to match the tests made by his opposite number overseas.

To facilitate communication with Asian contractors, Tandy employs a Japanese engineer to conduct or supervise these tests. This helps overcome language barriers which can otherwise create quite serious problems where complex technical matters have to be discussed.

Mains operated equipment will also be voluntarily submitted to the appropriate Australian power supply authorities to ensure that it meets their safety specifications.

When this model has been fully evaluated a report is sent back to the contractor and the Tandy engineer, who supervises whatever modifications are required.

The next step is a trial production run, the previous models having been constructed by skilled technicians rather than normal production line staff. Such a production run may involve 20 or 30 units, and a small quantity is sent to each market area. Australia, for example, may get five units.

Again these are evaluated, this time to detect any problems arising from mass production techniques. Only when this batch is given a clean bill of health is the contractor given the go-ahead for a full scale production run.

During the production run the Tandy engineer remains on location and continually checks samples taken at random from stock waiting to be shipped. Naturally, any fault pattern which emerges can be quickly rectified and, if it is sufficiently serious, stocks can be frozen until all units are checked.



COMMUNICATION ENGINEERS

Local designers and manufacturers of antennas and related products for HF, VHF, and UHF Bands.

- * We specialise in citizen band antennas.
- * Range of mobile and marine helicals.
- * Marine antenna, no groundplane required.
- * Range of base station antenna.
- * and accessories.

POLAR ELECTRONIC INDUSTRIES


5 Advantage Road, Highett, Vic. 3190. Phone: 95-7405

S.A. (STD) (08) 264-5540
W.A. (STD) (092) 25-5722

DISCOVER the exciting world of EXPLORATION!



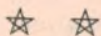See our spectacular display of telescopes, binoculars, microscopes, weather equipment, build-it-yourself kits, books, charts and atlases.



Send 45c to Dept. C, Box 568,
Crows Nest, 2065
for a complete informative catalogue.

Astro-Optical Supplies Pty. Ltd.

11 CLARKE STREET CROWS NEST, SYDNEY N.S.W. 2065 PH. 43 4360
200 BOHRKE STREET MID CITY ARCADE, MELBOURNE, VIC. PH. 663 2761

TANDY SERVICE

When a shipment finally arrives in Australia it is subject to yet another check. This is a random check involving, initially, about 10 per cent of the shipment. The amount of subsequent checking depends very largely on the result of this check. If it was 100 per cent correct, for example, there would be little point in further checks. But if a serious fault pattern emerges, it may be necessary to check all stocks.

In such an event the necessary corrections would normally be made by the quality control department's staff, with the cost being met by the contractor. If the volume of work involved should be beyond the capacity of the local staff to cope with it in a reasonable time the contractor may elect to send out the necessary staff, rather than recall the entire shipment.

Incidentally, these checks are not concerned only with the performance and condition of the equipment itself — the whole package is evaluated. A missing owner's manual or accessory can be just as frustrating to the customer, and as embarrassing to the quality control department, as a major technical fault.

Nor is the quality of the owner's manual itself taken for granted. We have all encountered manuals written in what has come to be known as "Asian English", quaint combinations of English words which at times can be almost meaningless.

I raised this point, and Gordon Heyes' answer was to pick a manual at random from a nearby stock shelf and say, "Here, see for yourself." A quick check was enough to convince me that, regardless of who drafted the text in the first place, it had been edited by someone with a full command of English.

At this point one may fairly ask just how effective this overall checking system is in practice. Does it mean, for example, that a customer can never get a faulty appliance? Gordon Heyes is the first to admit that such a claim would be quite unrealistic. "But," he claims, "putting aside nuisance calls, such as the customer pressing the wrong buttons, we do keep our warranty claims under one per cent. In fact, if we experienced a figure of one per cent, it would set the alarm bells ringing, because we would know something serious was wrong."

Of course not all service calls are under warranty or imply faulty design or workmanship. Some things, like tape recorder heads, drive belts, etc, wear out in the normal course of events. Also equipment is damaged, either by mechanical or electrical abuse. When these problems occur, the owner is naturally concerned about getting his gear going again.

And this is where the other end of the quality control department takes over. It is in fact a service department in its own right, but there are significant advantages in having it under the one administrative control. Among other things, it provides a valuable source of information concerning any distinct fault patterns which might occur, and which should be fed back to the production line. Gordon Heyes feels that too rigid separation of departments can inhibit such feedback.

Another aspect of the service end of the department is maintaining a stock of spare parts, without which any service department would grind to a halt. This is a significant operation in itself, involving many racks of shelves and many thousands of bins, all carrying individual spares. The bins must be effectively indexed to provide immediate access to a particular part, and an extensive stock control system is needed to keep them supplied.

Again, according to Gordon Heyes, there are advantages in a single administration. One example is the need to regularly re-order spare parts, keeping in mind the conflicting requirements that, on the hand it is undesirable to carry more stock than is strictly necessary but, on the other hand, important to maintain enough for immediate needs.

The service department provides the most valid information as to the rate at which particular spares are being used, plus any additional information regarding the quality of the spares, or the possible need for modifications in some instances.

Spares are dispatched with each new shipment of appliances, the proportion of individual items being based on experience gathered from the previous shipments. Normally this is sufficient to provide adequate stocks but, understandably, there is sometimes a run on a particular component, such that it is in danger of running out before the next shipment.

In such cases a telex message would be dispatched to the company's head office in Forth Worth, Texas, and the items would be dispatched by air freight. However, there have been situations where the department has stripped down brand-new appliances to provide a stock of urgently needed spares, rather than subject their customers to undue delays.

Talking of spare parts raised the inevitable question as to how long such spares can be stocked for a particular model. "Our policy," said Gordon Heyes, "is to stock spare parts for at least five years after our last shipment of a particular model. Sometimes this is outside our control, as when a manufacturer goes out of business prematurely, but it is our policy and we do our best to follow it."

The service department proper con-



One of several well equipped booths which form the service section of the quality control department. In this case the technician is working on a cassette tape deck, but the next job may involve the output stage of a transceiver.

sists of several well equipped test booths, plus the necessary inwards and outwards departments, clerical staff, etc. It handles all the service for NSW, and there are similar departments in Brisbane and Melbourne.

In the event that a customer needs service, whether under warranty or not, he need only take the device to his nearest Tandy store, preferably the one from which he bought it. All the details of the complaint are noted on a suitable docket and the device forwarded to the Rydalmere depot.

At the same time the store concerned can give the customer a fair estimate of what the repair will cost, assuming it is no longer under warranty. Tandy employ a novel flat rate labour costing system, whereby the labour cost is a fixed amount for any particular piece of equipment. This is regardless of the time actually taken for the job; if it turns out to be a stinker, that is the company's bad luck. Hopefully, the next one will be a pushover!

The minimum labour charge under this scheme is \$7.50, and the maximum charge, for the most complex piece of equipment currently on their list, is about \$17. To this will be added the cost of any components which need to be replaced and, while this charge is not completely predictable, it is more often than not quite modest.

After being serviced at Rydalmere the equipment is returned to the shop from which it came, and the customer is advised by telephone that it is ready.

At this point of our discussion I could not resist raising one point. In any system like this the line of communication between the customer, and the service mechanic on the bench, tends to be stretched to its limit. Suppose the fault is intermittent, or environmental, and does not show up on the bench?

I was assured that everyone was well aware of this risk, and that they are geared to avoid it. At the store end of the line the staff are trained to elicit as

much information as possible from the customer concerning the symptoms, and these are recorded on the service docket.

At the service bench end of the line the technicians are trained to watch for just this problem. If the symptoms they observe on the bench do not seem to tally with those on the docket, or if they can find no fault, then the customer must be contacted with the request for further details of the symptoms. If necessary, arrangements can be made for him to demonstrate the symptoms at some mutually convenient site.

Earlier we mentioned the need for an effective stock control system to maintain the spare parts at an adequate level. In addition, there is a fair amount of clerical work required in any service department, including the costing of components and labour for each job, interdepartmental billing, and so on.

To date this has all been done by hand. However, the department has now grown to the point where it would be more economical to computerise the system. In fact, the computer already exists within the Rydalmere head office complex, where it is used for the much bigger jobs of main stock control, accounting, payroll records, etc. It can also be connected into the Forth Worth computer in Texas, via an international circuit, for exchange of information.

So plans are now under way to bring the quality control department into the computer system. It will obviously involve a fair amount of work to transfer everything to computer records, while ensuring that the flexibility of the department's current working systems — which have proved themselves — are not impaired. But Gordon Heyes is confident that it can be done and that it will significantly improve the efficiency of the department.

One of the jobs, for example, will be to provide an automatic ordering system. It will monitor the inventory

level and, when a predetermined minimum quantity is reached, it will print out a purchase instruction.

And, of course, the computer is an ideal device to provide the kind of statistical information which is so valuable in a department of this kind; the rate at which individual spares are being used (is there a weakness in a particular component, about which the contractors should be informed?), the rate at which particular products are being repaired under warranty (again, is there a pattern?), or even the effect which seasonal changes have on service demands, for whatever such information may be worth.


One thing it won't replace, however, is the enthusiasm and team spirit which operates within the department, and of which Gordon Heyes is justifiably proud. "Our job," he said, "is to ensure that Tandy has satisfied customers. If a customer has a complaint, we will bend over backwards to put it right whatever is wrong. And, while our warranty spells out strict legal conditions, for our own protection, we are not above exercising our discretion in borderline cases, or where a strict interpretation is obviously inappropriate.

"In fact," he went on, "this department is not even expected to show a profit; more usually, it runs at a loss. The service it provides is part of what the customer pays for when he buys the product."

On the technical side it is obvious that most of the staff have a genuine interest in electronics over and above their job. Most of them have an amateur radio licence at one level or another, and others are studying for their licence. And although that may not automatically guarantee a good technician, it isn't a bad place to start from.

According to Gordon Heyes, each technician is expected to be able to tackle any of their appliances, and to be equally at home with the mechanics of a tape deck or the output stage of a transmitter. On the other hand, they are not above pooling their knowledge and experience should a particularly sticky problem arise. If necessary, the Japanese engineer can be called on for additional assistance.

From all this there is little doubt that the Tandy organisation takes its responsibilities to its customers seriously; certainly as seriously as most other organisations, and possibly more seriously than some. And not only because it stands behind its product after it is sold but, as much as anything, because it strives to make such after sales service unnecessary — though no less available for all that.

So next time you contemplate a "bargain" price think carefully about what you will get for your money. Buying from a reputable organisation may cost a little more, but it could mean a lot more in real value. 

The Measurement Challenge

In Electronic Technology

Rapidly advancing semiconductor technology has outdistanced traditional measurement technology. Now for a variety of safety, economic and technological reasons, new measurement techniques must be developed for the semiconductor industry. For the US, the development of new techniques is vitally important if the country is not to lose its military and economic ascendancy.

by **JUDSON C. FRENCH***

Is the United States losing its technological leadership? That question is being raised frequently. At the EASCON meeting of the Institute of Electrical and Electronics Engineers last fall, a panel of experts concluded that the country is in serious danger of doing so. Their examples of US failures to be competitive internationally in the manufacture of certain electronic components and circuits were startling.

*Chief of the Electronic Technology Division, NBS Institute for Applied Technology.

Many other leaders in industry and government have expressed similar concern not only about the loss of technological leadership, but also about the loss of economic and military leadership, both dependent on technological ascendancy. For example, members of management in 13 electronics companies unanimously agreed that a problem exists—a problem not in creativity but in how to make things better from a standpoint of productivity and quality. They cited semiconductor technology as one area requiring careful attention.


One of the major factors in the expansion of electronics into industrial, consumer, and government application is the rapid development of semiconductor components on which most electronic "systems," from cardiac pacemakers to computer networks, now depend. Active electron devices, such as semiconductors, largely make possible, and also limit, the capabilities of such systems. As go components, so goes the system.

Silicon-based semiconductors have been the pacesetters for years and will continue to be so for the foreseeable future. Other technologies are important in special cases, but comments involving silicon devices as an example will apply equally well to them.

The measurement problem in this field can be summed up by saying that despite (or perhaps because of) the sophistication of semiconductor technology, the measurement methods available to control materials and equipment as they enter and are used on a production line, and the measurement methods to characterize the finished product, are all too often not sufficient to meet the needs of the supplier or the customer. Semiconductor technology has outdistanced traditional metrology (measurement technology). This is true across the board, from chemical measurements, through dimensional metrology, to electrical tests.

Hundreds of companies confront this problem to an increasing extent in US industry. Manufacturers of products as diverse as computers, cameras, automobiles, cardiac pacemakers, and electronic instruments now make these semiconductor components in-house for economic and competitive reasons. These companies must interface with the thousand suppliers of materials and equipment needed for semiconductor manufacture and must control the manufacture of their own products and characterize them, perhaps even more carefully than must the merchant manufacturers of devices.

Many persons today are familiar with

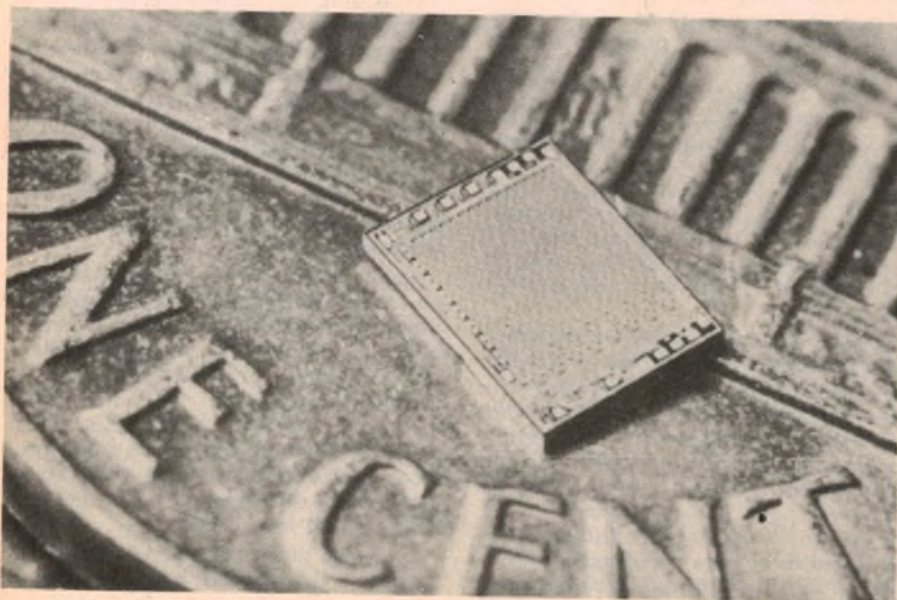

This tiny semiconductor is a complex maze of transistors on a single integrated circuit chip. Rapid advances in the design of integrated semiconductor devices like this have made today's computers possible.

the development of tiny, complex integrated circuits that contain thousands of individual transistors on a silicon chip only a few millimetres square. These devices already require crystal purity and perfection, purity of processing gases and chemicals, and dimensional controls for photolithographic processes far beyond those of other production processes. In insulating oxide layers or in active regions of silicon, quantitative identification of dopants and contaminants, in the parts-per-million to parts-per-billion range, and of their distribution over fractional micrometer dimensions are required. Most of the physics of a device takes place within a micrometer or so of the surface!


In the future, the dimensions of entire transistors will approach a wavelength of light to meet, for example, computer requirements for increased speed and reduced power consumption in each logic function. The metal-oxide-silicon transistor of the future may have less than 200 dopant atoms in its 150 nanometer-long control channel. It may be manufactured using electron beam exposures of new polymer materials to define working areas, with its dopants introduced by ion implantation techniques. The control measurements for all of these processes must be economically feasible on a manufacturing line.

But there are already problems with the control measurements, even today before these extremes in design requirements are reached. Successive, even alternate silicon wafers in a single diffusion run may have high or zero yield of devices, for unknown reasons. Processes which are more art than science go out of control and, lacking quantitative control over the materials involved and the processes themselves, the panic button is pushed.

An enormous amount of frantic empiricism begins as the lost art is redeveloped and the process re-established. Procurement experts write specifications on hermeticity and water vapour content of devices, for example to achieve reliability, but satisfactory test methods are not available. Those responsible for safety in large systems complain that there is no adequate way to electrically test individual elements in complex microcircuits such as microprocessors. And so it goes.

These are not simply matters of routine economic significance, hopefully to be solved by each company as a normal cost of doing business. They mean more to the US as a whole, and to the taxpayer than that. Not only are they of concern with respect to US international technological leadership, but they are of concern to military and civilian users of electronics.

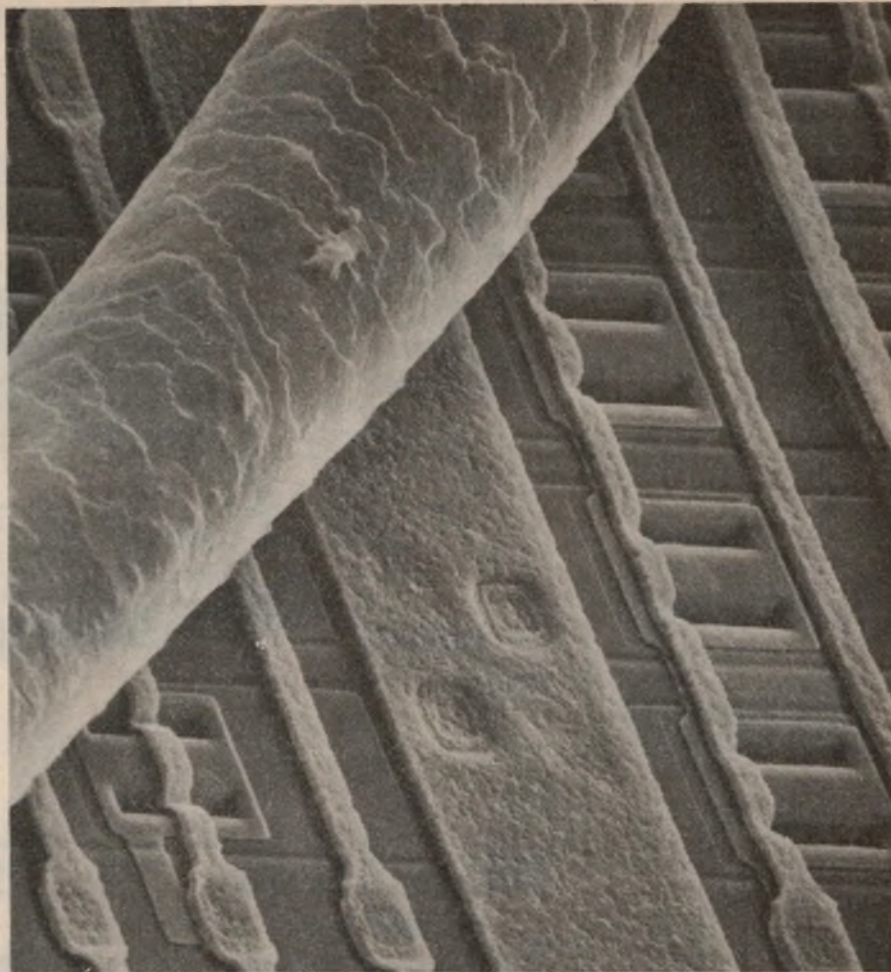The Department of Defense (DoD), long a leader in understanding the advances to be gained from the use of electronics, is much concerned about the cost of doing business with a high depen-



This photograph graphically illustrates the measurement problems of modern electronic technology. Shown are computer memory transistors so small that eight of them on an integrated circuit will fit in the cross-section of a human hair. Electron microscope photo (10,000 times enlargement) shows the V-shaped third-dimension of the VMOS transistor process. (Photo courtesy of American Microsystems Incorporated, Santa Clara, California.)

dence on electronics. Electronic maintenance costs the Pentagon over \$5 billion per year. Accident costs have risen as the result of failures of increasingly complex computers and components. DoD's ability to purchase custom, reliable devices to provide the competitive edge it requires for US national defense had led it to conclude that new attention must be given to improve measurement methods in manufacturing processes for two primary reasons: so that reliability can be built into devices made in the large quantities that provide economy-of-scale, and so that devices can be designed and built in modest quantities and still be both reliable and affordable.

The significance of similar problems in the civilian sector is only beginning to be appreciated. There the impact will be felt in the ability, safety, and economy of such large-scale applications as automobile electronics, computer controlled systems, and medical instrumentation.

Instruments that are meaningful, repeatable, and economical are needed for control on the production line. They

must be backed up by specifications and tests and standards covering the material and equipment coming into the line, and they must be followed by screening tests on the finished product and by incoming inspection by the customer. Everyone claims to know all this and even to practice it. So what is the problem?

Three points can be made in answering this question.

The first is that some practical measurement needs cannot be met because basic quantitative measurement technology is not available, even in standards or research laboratories.

As an example, consider the control that is necessary of dopants and contaminants in the micrometer-sized working region of a transistor. Quantitative measurements, backed up by standards, are not available to provide this information, despite the advent of powerful qualitative methods such as ion microprobes and other surface analysis tools.


The Electronic Technology Division of NBS is attempting to provide a start in this direction, in work supported by the

TEST INSTRUMENTS



CO-1303D 75mm OSCILLOSCOPE

★ Now with 5MHz bandwidth. ★

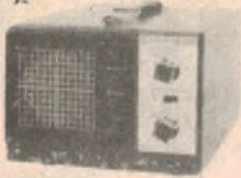


- 75mm CRT
- DC-5MHz/10mV
- Compact & lightweight

• SPECIFICATIONS

Bandwidth: DC to 5MHz (-3dB)
Deflection: 10mV/div
factor
Attenuator: 1, 1/10, 1/100
Input R.C.: 1M Ω , 35pF
Sweep range: 10Hz to 100kHz
Phosphor: P31

SG-402 RF SIGNAL GENERATOR

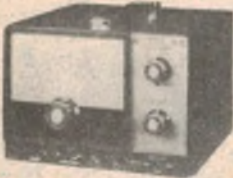

- Wide frequency range
- Compact
- Amplitude modulation facility

• SPECIFICATIONS

Frequency range: 100kHz to 30MHz
in 6 ranges
Output voltage: 0.1 V rms
Int. Mod: 400Hz, 40% modulation
Ext. mod: 1.5V rms, 50Hz to 10kHz

AG-202A CR OSCILLATOR



- Wide frequency range
- Sine and square wave signals
- High output stabilized voltage

• SPECIFICATIONS

Frequency range: 20Hz to 200kHz
in 4 ranges
Output impedance: 600 Ω
Output voltage: Sine wave 10V rms, Square wave 10V p-p

15MHz

CS1560A

If you need more bandwidth-

The 15MHz dual trace

★ In fact we found the CS-1560 a delight to drive and use. It has the full 15MHz bandwidth available at deflections up to 10mV/div and maximum sensitivity of 10mV/div. Traces are bright and sharp and cm. Traces with fast risetimes are easily viewed. The whole unit appears to be a well-conceived piece of equipment. We can recommend it for laboratory or hobby use. E.A. Dec. 75. ★



CS-1560A

130mm DUAL TRACE TRIGGERED SWEEP OSCILLOSCOPE

- 130mm CRT
- DC 15MHz/10mV
- Automatic sweep (AUTO FREE RUN)
- Display modes (CH1 CH2 DUAL ADD SUB)
- Full sensitivity X-Y operation

• SPECIFICATIONS

Bandwidth: DC to 15MHz (-3dB)
Deflection: 10mV/div to 20V/div
factor
Input R.C.: 1M Ω , 22pF
Rise time: 23nsec
Overshoot: Better than 3%
Sweep time: 0.5 μ s/div to 0.5s/div
Magnifier: $\times 5$
Linearity: Better than 3%

Calibrator: 1Vpp (1kHz square wave)
Intensity modulation: More than 20Vpp
Phosphor: P31
Power: AC 100/120/220/240V 50/60Hz 23W
Dimensions: W260 x H190 x D385 (mm)
Weight: 8.4kg

BEST VALUE

10MHz CS1562 Dual Trace, Triggered Sweep

CS-1562

130mm DUAL TRACE TRIGGERED SWEEP OSCILLOSCOPE

• SPECIFICATIONS

Bandwidth: DC to 10MHz (-3dB)
Deflection: 10mV/div to 20V/div
factor
Input R.C.: 1M Ω , 22pF
Rise time: 35nsec
Overshoot: Better than 3%
Sweep time: 1 μ s/div to 0.5s/div
Magnifier: $\times 5$
Linearity: Better than 3%

Calibrator: 1Vpp (AC line freq. square wave)
Intensity modulation: Less than 5Vpp
Phosphor: P31
Power: AC 100/120/230/240V 50/60Hz 20W
Dimensions: W260 x H190 x D375 (mm)
Weight: 8.0kg

CS-1559

130mm TRIGGERED SWEEP OSCILLOSCOPE 10MHz Single



30MHz CS1570 ANOTHER SENSIBLY PRICED SCOPE

CS-1570

130mm DUAL TRACE TRIGGERED SWEEP OSCILLOSCOPE

• SPECIFICATIONS

Bandwidth: DC to 30MHz (-3dB)
Deflection: 5mV/div to 5V/div
factor
Input R.C.: 1M Ω , 24pF
Rise time: 11.7nsec
Overshoot: Better than 3%
Signal delay: 160nsec
Polarity: CH2 can be inverted
Sweep time: 0.2 μ s/div to 0.5s/div
Magnifier: $\times 5$
Linearity: Better than 3%

- 130mm mesh PDA
- DC 30MHz/5mV
- Delay time
- Auto level triggering
- Display modes (CH1 CH2 DUAL ADD)
- Trigger modes (AC, LF, Re, HF, Re) DC

Calibrator: 0.5Vpp (1kHz square wave)
Intensity modulation: More than 5Vpp
Phosphor: P31
Power: AC 100/120/220/240V 50/60Hz 25W
Dimensions: W260 x H190 x D375 (mm)
Weight: 8.5kg

MODEL 1040 CB



- Greatly simplifies all CB transceiver servicing.
- Checks complete CB transceiver performance in minutes.
- Checks AM and SSB
- No complex hookups or calculations required.
- Test results displayed on direct reading meters.
- Only one hookup required for all tests.
- Eliminates need for special equipment.
- Increases your CB service profit by saving you time.

Call in for a demonstration at leading electronics stores or the Australian agents - Parameters Pty. Ltd.
Sydney: 68 Alexander St., Crows Nest, 2065 Tel: 439 3288
Melbourne: 53 Governor Rd., Mordialloc 3195 Tel: 90 7444

SERVICEMASTER

MODEL 1827 30MHz FREQUENCY COUNTER

- 30MHz reading guaranteed. 50MHz typical-
- Full 6-digit display with range switch allows 8-digit accuracy.
- 1Hz resolution—even at 30MHz and beyond.
- Completely portable for use anywhere.
- Exclusive battery saver features auto-shutoff of display to reduce battery drain.



- Operates on AA size batteries, AC with optional charger/adaptor or 12VDC with optional power cord/adaptor.
- Complete range of optional accessories for unequalled versatility.

PARAMETERS PTY LTD

The Measurement Challenge

DoD's Advanced Research Projects Agency (ARPA) that is aimed at providing artifacts of known chemical content. These materials are produced in a silicon matrix by the same photolithographic processes and ion implantation used in making semiconductor devices. They are defined in content by independent analytical means (neutron activation) applied to companion samples.

The second point is that some practical needs are not being met because of gaps in the traceability chain, gaps which may occur near either end of the chain—on the production line or at NBS.

As an example of the former, consider the use of a test instrument duly calibrated by the in-house standards laboratory and traceable to the standard volt. The rub is that a fixture has been added by the user between the instrument and the device he is testing, and he and his customer cannot understand why they always disagree. What is lacking is some standard artifact for checking out the whole measurement system.


As an example of a break in the chain occurring at NBS, take the measurement of linewidths in a photomask used in patterning the structures in a semiconductor device. Five to twenty steps in the manufacture of a device require photomasks. Absolute dimensions on each mask, uniformity across a mask, and registration of the image on the device structure from masking step to masking step are required to tolerances of the order of fractions of a wavelength of light. Poor control of line width can adversely affect device yield. It certainly can effect marketplace exchanges of photomasks. Several million photomasks are used a year by semiconductor device manufacturers, and untold millions of masking operations are performed.

Photomasks are sold by over two dozen small companies to device manufacturers. Photomasks are also made and used by the device maker and exchanged between the in-house maker and user. In either case the problem is similar: inability to agree on the measurements because the measurements cannot be standardized yet. What is needed now is a measurement standard for line width of one micrometer plus or minus 50 nanometers and the optical technology for properly using it.

Soon, the need will be for fractional micrometer standards. NBS has not been able to make these measurements. Line separations, yes; linewidths, no. But the Bureau will be able to do so soon. In a cooperative program, initiated by the Electronic Technology Division and carried out by this and two other NBS

MICROMETRE CALIBRATION ARTIFACT

Dimensions in micrometres

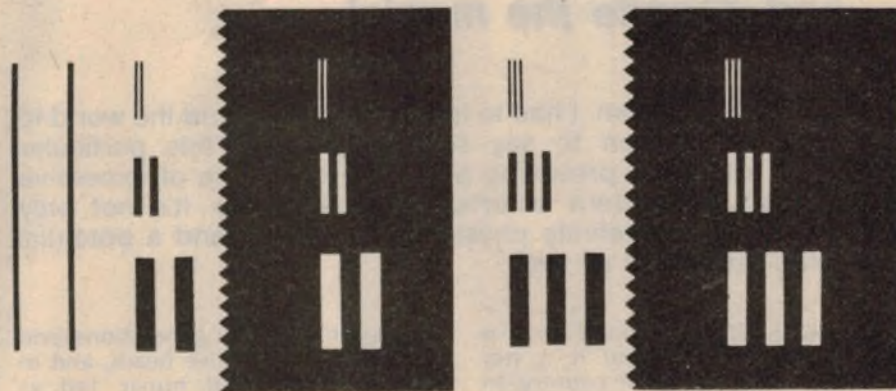

Schematic of NBS artifact for calibrating optical-microscope systems for measuring line widths.

Divisions (Mechanics and Optical Physics), improvements in optical measurement understanding and procedures have been developed and artifacts in the micrometer range are expected to be available this year on a trial basis, with the fractional micrometer standards to follow.

The third point is that some practical needs are not being met because external influences on the measurement instrument, or sensory transducer are ignored, either inadvertently or because there is no available way to take them into consideration (usually for lack of information about the problem). The problem here is that calibrations are typically conducted under laboratory conditions that bear little resemblance to the real world environment of vibration, thermal transients, magnetic fields, and so on.

There are as many examples from semiconductor process control or in other types of manufacturing process control that could be used to demonstrate this point, but consider a totally different field this time: the case of some high-quality, high-priced pressure transducers for flight-test instrumentation. Suspecting that these devices might be affected by thermal transients to which they are occasionally exposed in use, a simple, quick screening test to check for such sensitivity has been developed. This work was done in the Electronic Technology Division at the request of the

DoD Range Commanders Council. Using this new method to test representative devices of several types including strain gauge and crystal-based transducers, it was found that apparent pressure shifts of 0.4 percent to 400 percent of full scale were observed solely as the result of thermal pulses with an energy density of 1.8 joules per square centimetre.

It has become abundantly clear that electronics is presenting a challenge to metrologists and is demonstrating an increasingly important need for advancements in the development and practice of practical, on-line measurements for a variety of social and economic reasons. Research is needed, to be sure; new methods and standards are required; and greater care is required in using the instruments that exist and have been calibrated in the traditional way.

NBS is responding to this challenge and need in its electronic technology program, where the goals are to develop cost-effective measurement technology for commerce (to specify electronic materials and devices), for industry (to control electronic device fabrication processes), and for government (to improve economy in procurement and application of electronic components and the systems which use them). ☺

Reprinted from Dimensions, Journal of the National Bureau of Standards, Washington DC.



Forum

Conducted by Neville Williams

Have a pleasant evening if you can — and despite the music!

Strange as it may seem, I had to travel halfway around the world to generate the emotion to say something about this particular subject — about the prevailing and quite crazy use of excessive sound levels in modern entertainment situations. It's not only unnecessary but a definite physiological hazard, and a potential psychological hazard as well.

The use of very high sound levels is not new, of course, and it is not confined to any particular country. In Australia, as elsewhere, we've grown accustomed to the idea of "pop" concerts and discotheques, where sound levels are used which are not far short of the pain threshold, even for people without any apparent limitations on their hearing.

For people who do have hearing limitations — and they are fairly numerous — sound levels approaching or exceeding their pain threshold can lead to tension, headaches and nausea. Logically, such people should avoid high sound level situations, but they don't always have that simple option.

From a technical viewpoint, the design and production of high-power, high-quality audio equipment is a highly interesting subject and what is available today is a tribute to the skills of those involved. But, as in many other areas, the products of advanced technology are not necessarily in line with the best interests of the community.

If one protests, in a practical situation, that the audience could hear the proceedings perfectly well at a much lower sound level, one is likely to be regarded as old-fashioned and obviously not "with it". The amplification is not there simply to make the "music" clearly audible, one discovers; it's an essential ingredient in the total psychological impact. It's part of the process of "turning the audience on"!

To settle for merely adequate amplification would be akin to turning off the psychedelic display and relying on merely adequate lighting.

Dare I suggest that it might also expose the basic mediocrity of many performers?

So, we in the older generations tend to shake our respective heads, and to write off the loud music fad as something peculiar to youth; as something that they'll get over as they grow older. The chances are that they won't, but we'll say more about that presently!

Being in no way a pop fan, excesses have not affected me directly but the members of my family and other acquaintances are frequently the victims of what I believe is a spillover from the pop scene: the excessive sound level that is encountered nowadays in ordinary film theatres — not just for special films, but for literally every film!

Someone, as a treat, decides to take the children or the grandchildren to see a film that will interest them, only to come home again complaining of a



Sungravure staff artist Brian Evans: "Any resemblance between the cartoon characters and people living or dead is entirely intentional!"

headache from the roof-lifting sound level from a string of cartoons, and main-feature characters that are made to shout rather than talk.

Why?

Do projectionists and managers no longer slip occasionally into the auditorium to listen to the sound they are feeding to the patrons? What has happened to the old-fashioned "too-loud too-soft" button that we once relied on?

Do they imagine that every performance should follow the lead of the pop scene and belt the ears off theatre patrons?

Or are the projectionists and staff in modern multi-cinema complexes so isolated from the dramatic content of any one presentation that they merely roll the film and turn the sound up to some habitual setting, thereafter "letting 'er rip"?

Frankly, I'm not sure what the cause is. I'm complaining here about the end result, as it affects so many theatre patrons.

However, what directly inspired this present outburst was neither a pop concern nor a film presentation but an ethnic style concert of the type staged nightly wherever tourists tend to concentrate overseas.

A couple of such concerts during my recent jaunt were entirely successful as, for example, a night cruise on the lake at Lucerne in Switzerland — a balmy evening, a pleasant meal, and entertainment by Swiss nationals presenting their own style of music and dancing. It was a happy and spontaneous performance, with just enough amplification to make it all clearly audible above the incidental noise aboard the boat. Everyone went back to the hotel relaxed and happy.

Much the same remarks applied to a Tyrolean evening at the Adambrau restaurant at Innsbruck in Austria — a somewhat tougher battle between the presentation and a packed audience, but with amplification used sensibly and effectively, nevertheless.

What a contrast to an evening of Italian style music at Le Torre restaurant on the outskirts of Rome. It started off in promising fashion, with as many dishes and as much wine as the guests felt inclined to consume. Within a very short time, there was a hum of friendly conversation in a variety of languages.

But suddenly, around 9 pm, the atmosphere was shattered by the loudest noise I've been subjected to in many a long day. I've sat through orchestral concerts, organ recitals and many over-enthusiastic hi-fi demonstrations, and my ears are not easily overloaded. But I cannot recall any other occasion on which they have been so obviously "pumped" by sheer sound pressure. There were grimaces, startled looks and at least two people near me clapped their hands over their ears in a vain effort to shut out the din.

If the intention was to silence the conversation, it certainly succeeded!

I stood it for about five minutes and then, with a couple of others, simply walked out and spent the next hour in the relative peace of the adjoining garden, where the goings-on were still plainly audible.

Around 10 o'clock the musicians abandoned the stage and the microphones and played their music from the floor, amongst the tables. Even without amplification, their accordions, fiddles and powerful Italian voices were very loud in the confined space, but at least they were natural.

Then why the grotesque degree of amplification for the initial performance? If it was supposed to enhance its appeal, I can only say that it had precisely the reverse effect on me. All the Mediterranean romance of the particular kind of music was sacrificed in the multi-decibel blare.

No less disturbing to me was the unquestioning acceptance of the entertainment by the rest of the audience. When prompted, some of them agreed later that the music had been too loud and that they had enjoyed the second part much better than the first. But they had simply carried on with the food and the wine, as if excessively loud sound was an integral and necessary part of the evening's entertainment.

I fear that this general attitude is widespread. So often, people in charge of sound systems seem to ignore the niceties of presentation and pour on the sound, with all the delicacy of filling a wineglass from a bucket! Worse, the audience accepts and puts up with it, as the way things are now done.

By coincidence, one of the people at my table who was conscious of the situation was the personnel officer for an Australian company which currently has on its staff about 80 apprentices and trainees, mainly involved in machining and fitting. Each year, every one of this staff group undergoes a hearing test, as a monitor for possible hearing damage occasioned by noise in the machine shop.

According to the personnel officer, 35 of the group are currently showing a definite and progressive hearing loss, but here's the crunch: every one of the number so affected regularly attends pop concerts and/or discos. Those that don't have retained normal hearing, despite the noise in their work environment.

Which brings me back to the point I made earlier: We may philosophise about young people and assume that they will get over their fad for very loud sound. They may tire of it, for sure, but it may well leave its mark in the way of impaired hearing for the rest of their lives because all the evidence I've come across suggests that the damage is irreversible.

These are days when we hear a lot about consumerism, environment and protection of the community. There are

Can you afford not to know about microprocessors?

Six years ago, microprocessors and microcomputers were little more than dreams in the minds of research engineers and science fiction writers. Now they are changing the whole face of electronics. The change is happening so fast that overseas it is being called an explosion, a revolution. What are these new devices, and why are they having such a dramatic impact? Whether you're a professional or a hobbyist, you really need to know.

This book will help you find out what the revolution is all about:



\$4.50 from newsagents, bookstores, electronic suppliers and also from Electronics Australia, Box 163, P.O. Beaconsfield, NSW 2014. (Post and packing 60c extra.)

**The beginning
of
beautiful music.**



Micro Seiki turntables.

A sophisticated range of direct drive and belt drive turntables.

Excellence of materials, meticulous workmanship, attention to minute engineering details...

A combination to produce impressive overall performance in sound reproduction.

Indeed, the beginning of beautiful music.

The Micro Seiki DD-30


The new DD-30 features fully automatic, electronically controlled tone arm lift and return. The risk of mechanical failure is, thus, eliminated.

The unique floating suspension system of the DD-30 ensures crisp, clean sound. Direct drive from the DC servo motor results in wow and flutter of less than 0.03% WRMS.

The DD-30, one of the superb Micro Seiki range.

Select from belt driven models MB-10 and MB-15, direct drive models DD-20, DD-30 and DD-40. Ask for a demonstration soon.

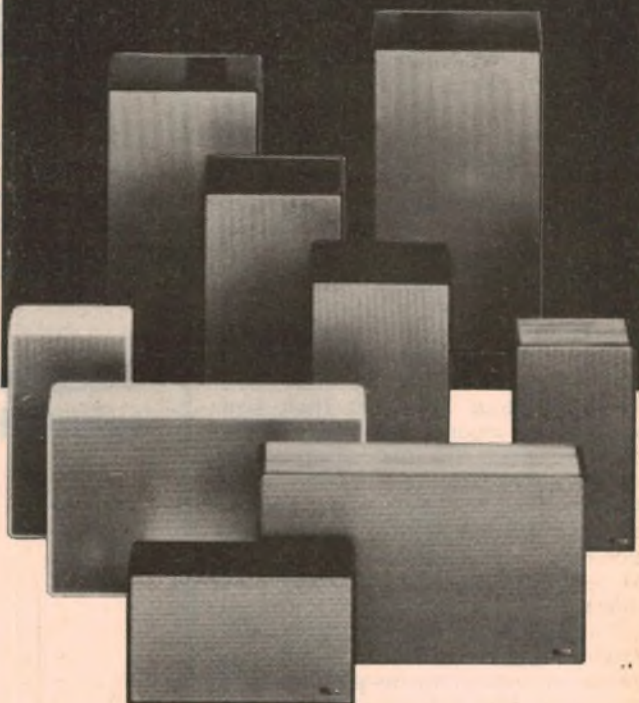**The greatest
range of sound
from the
smallest of enclosures.**



Canton speakers. For value, none better.

Canton sets new standards in compact domestic enclosures. Among the smallest on the market, Canton are built to high specifications and their sound is superb.

The Canton range of Hi-Fi loudspeakers includes seven units: The LE250 is the smallest at 30 x 17.5 x 13 cm with an RMS rating of 40 watts. The LE900 is the largest - 58.5 x 31.5 x 27 cm - with an RMS rating of 90 watts.

And, Canton make the components as well as the speakers.

So, quality is controlled from beginning to completion.

Canton. Stunning sound and value that can't be bettered in its class.

PA39CMS

Distributed by

PHOTIMPOR

MELBOURNE ADELAIDE BRISBANE PERTH SYDNEY

For descriptive literature and specifications, send a 30c stamp to Qualitron Industries Division of Photimport (Australia) Pty. Ltd. Head Office: 69 Nicholson Street, East Brunswick, Victoria, 3057, Australia. Telephone: 380 6922.

FORUM: Have a pleasant evening if you can . . .

limits on motor car exhaust emission and the noise patterns of aircraft; the intake of drugs and tobacco is discouraged; a variety of food and medicinal ingredients have been questioned because of their potential harmful effects and spirited arguments are raging about uranium and radioactive wastes.

Then what about giving some attention to sound level at various forms of entertainment, which must inevitably be making inroads into the hearing acuity of everyone exposed to it!

I suspect that it may have psychological effects as well, at least to the extent of adding to the tensions and the fatigue that seems to be the lot of modern society.

How delicious and novel it is to get away into the stillness and peace of the countryside. Perhaps the contrast seems all the greater because we make it so — or allow it to be so — by creating and tolerating sound levels far in excess of necessity at other times.

Some may contend, of course, that high, loud sound levels have long been a feature of symphonic concerts and grand organ recitals, so why all the fuss now?

It's a fair question and I, for one, will never forget the enormous level that Marcell Dupre released from the Sydney Town Hall organ in a performance of "The Marseillaise". It was sheer sonic exhilaration, all the more so because it lasted only for a very short time. Had he played the whole concert in that fashion, it would have been tasteless and intolerable but, in fact, The Marseillaise was followed by items that ranged all the way down the decibel scale to the sounds of the most remote and delicate pipes. Sonically, a delicious sweet.

While I am on the audio bandwagon, I may as well take a sideswipe at the many people who are seemingly embarrassed by relative silence; who seem to assume that people are automatically made happier by being subjected to background music competing in level with whatever else is going on at the time.

The attitude is as firmly established in Australia as anywhere else but, in tripping around Europe, I was exposed to it more frequently than happens in my usual routine.

At home, my own inclination is to be quite selective, as distinct from others who allegedly work best and study best against a program from the local "top 40" radio station. If the radio, TV or record player is turned on, I tend to assume that the intention is to listen or to watch, and that talk should be limited to brief, pertinent comment. If the emphasis is to be on conversation, then let's turn off the distractions.

Back to public situations: one may typically be riding on a tour bus, watching the scenery, chatting quietly or even dozing if there is not too much to hold the attention. Suddenly, the driver or the tour guide gets worried that the passengers may be bored — and on goes a tape to make them happy again. A few may indeed respond, if it happens to be their kind of music and they want to listen rather than talk or doze — but the rest just put up with the intrusion, too timid or too polite to indicate disapproval.

Tour boats have their own sonic pattern. You are welcomed aboard to the sound of music played through spray-proof horn loudspeakers; music superficially appropriate to time and place and heard through the chatter of people trying to work out where they should go and where they should sit.

Later, the indifferent quality music gives way to an indifferent quality taped announcement about this or that; then click and the music takes over again until next time. Hopefully, somewhere on the boat, there will be a spot where the announcements can be heard but where the music is faint enough to be ignored!

And, finally, to the many restaurants, where the customer's ears are subjected to a mix of music, talking, walking and the rattle of utensils.

I have mixed memories of a sidewalk cafe in Florence which I visited on a couple of occasions, because it offered a most generous serve of the most delicious strawberries, cream and ice cream that I've ever tasted. Unfortunately, the gastronomic pleasure was compromised by the noise of patrons and passers-by, which was at such a level that one could converse only with difficulty. But the customers still got music with their strawberries — turned up sufficiently to compete with the already loud noise.

After all that carry-on, it may seem strange to say that I don't mind low-level background music of the deliberately bland type which one hears in elevators, waiting rooms and such like, although I prefer silence when involved in any kind of work requiring mental concentration.

The whole point of such music is that it is played only in relatively quiet areas, and at such level, and with such deliberately restricted dynamics that one can as readily ignore it as listen to it. Once it is turned up louder than that, or is required to combat high ambient noise, I'll join the ranks of protesters!

A horrible thought: I wonder if there really are ranks of protesters or am I the only one who has strong ideas about super-loud amplification and the make-people-happy-with-music cult?

I'd like to hear what others think about it.

printed circuits

- Accurately machine printed / etched
- Phenolic & fibreglass-gold / tin plated
- Special manufacturers' packs of 10
- EA R & H ET Philips Mullard available
- Specials to your drawing
- POSTAGE small 60c large \$ 1 00

	8	8	8
ET604	2.50	ET5857/R	3.00
ET713	3.00	ASC11	2.80
77TS9	3.00	ET603	3.00
ET134	2.60	77AL8	2.50
77DVM9	2.80	ET065	2.20
ET067	2.20	ET063	2.50
ET072	2.50	ET085	2.00
ET485	2.80	ET484	3.00
ET481M	2.50	ET582B	2.60
ET547	2.50	ET317	2.50
77D7	2.50	77B7	2.80
77UP6	3.50	77TY7	2.80
ET631/2	4.50	ET481PS	3.00
ET444S	3.00	ET316	2.50
ET548	3.20	77TY6	2.50
77PTY7	2.80	77PY6	2.50
77E05	3.50	77PNE5	2.50
ET081	2.20	ET062	2.50
ET632U	4.00	ET632	7.00
77CC4	3.00	77UP2	3.00
ET632C	8.00	ET632B	6.50
77UT2	3.00	77F18	2.50
ET633FR	6.00	77UT2	3.00
ET632P	2.50	ET632M	7.50
ET482A	6.50	76CL12	2.50
76B4	2.60	ET480PS	2.50
ET631	7.00	ET630	2.20
ET064	2.00	ET445	2.20
ET448A	2.20	ET448	2.80
ET111B	2.20	ET068	2.00
ET044	2.00	ET043	2.00
ET111R	2.50	ET111D	6.00
ET544	2.50	76PC9	4.40
ET602	6.50	ET446	2.50
ET111A	7.50	ET543B	2.50
ET445	2.50	ET241	2.80
ET1780A	3.00	ET541	2.50
76S7	2.50	76M17	2.50
76SS6	3.00	76SW4	2.00
76M5	2.50	76VG5	5.00
76VG5	5.00	76M5	2.50
ET708	2.50	ET740A	4.50
ET514	2.50	ET707A	2.50
ET706	2.50	ET130	2.50
76T2	2.50	76A03	2.50
76E02	5.50	75SWILA/Bgr	4.00
75PC12	2.50	EA70F1	2.80
ET514	2.50	ET129	2.50
ET439	3.00	ET420G	2.50
ET123A	2.50	ET119	2.60
75L11	2.50	ET438	2.50
75F12	2.80	ET1124	2.50
75CL9	2.50	75PC12	2.50
ET120	2.50	ET118	2.50
ET704	2.50	ET500	2.50
75R7	3.00	75CD7	2.50
75TU10	3.50	75FE5	2.50
75TU9	3.50	ET533A-B	2.50
ET400	2.50	75WJ3	2.50
ET529B	3.30	ET529A	4.50
ET801R	2.80	ET801P	2.50
75EM8	2.50	75SD4	2.50
ET414E	2.50	ET41402	3.20
ET314	2.50	ET116	2.50
EBK1	3.00	ET520	2.50
75D1	2.50	74MX120	3.50
74MX120B	3.20	74MX12A	2.80
ET527	2.50	ET428	2.80
ET530	2.50	ET427	2.50
74MX8	2.50	74EM9	2.50
ET429	2.60	EBX	5.00
EBP	5.00	EBM	5.00
ET635	2.80	77UP11	6.50
ET383	2.50	ET071	2.20
ET083	2.20	ET084	2.50
ET581	2.50	ET582A	3.00
ET5712	2.50	77DL7	6.00
770BF7	3.20	ET444M	2.00
ET444M	2.00	ET549A	2.50
HMS276	6.00	ET133	2.60
77UP5	8.50	ET546	2.50
ET546	2.50	ET77Y4	2.50
ET132	2.50	ET632A	6.50
77F1A	3.20	ET633	6.00
ET480B	2.80	ET480	2.80
ET1066	2.20	ET804	2.80
ET111C	2.00	ET061	2.00
76M19	3.50	76M47	2.80
76X10	2.80	ET533A C	3.00
ET543A	2.50	ET180B	2.50
ET444	2.50	76LM5	2.50
76R4	2.50	76R4	2.50
ET740B	3.50	76G3	2.50
ET707B	2.50	76RT3	3.00
76RS1	2.50	76S34	2.50
ET28	2.50	ET123B	2.50
ET122	3.00	75V12	2.50
ET121	2.50	ET122	3.00
ET117A-B	2.80	ET121	2.50
75T19	2.50	75T19	2.50
75FM5	2.50	75T19	2.50
75TU8	5.00	ET440	4.50
ET532	2.50	ET532	2.50
ET702	2.50	EBST	3.00
75A01	2.50	75A01	2.50
ET430	2.50	EB8	3.00
ET312	3.00	ET312	3.00
74MX12C	2.60	ET701	2.50
ET701	2.50	ET313	2.50
ET428	2.80	ET428	2.50
74TU8	2.50	74TU8	2.50
EB10T	5.00	EB10T	5.00
F80	5.00	F80	5.00

ALL SILICON 30/60w PA PORTABLE AMPLIFIER

6 1/2" W x 3 1/2" H x 8 1/2" D 12—16V two inputs 5 & 100mV 15 ohm output No. 763D Also 125 250 500 ohm output No. 763A All \$70 each For 240V operation \$33 extra. Freight collect.

COILS and IF's 1/2" x 1/2" x 2" H RF CHOKES Plus post 80c

381 AIR 2.5mh 50ma—Pya 70c
381 IRON 10uh to 1.000uh 25ma 70c


FILTERS 27 Line filter 2 814 29 Line filter 10/20amp \$37.50 Plus Post \$1.50

MAIL cheque or money order (add postage) direct to —

RCS radio pty ltd
651 FOREST RD BEXLEY
NSW 2207 587 3491

This data is meaningless!

CALIBRATION PERFORMANCE DATA



STANTON

Each Stanton 681 Triple-E is calibrated individually and the information below applies specifically to your pickup and stylus.

CALIBRATIONS:

Frequency Response: 10 Hz to 12,000 Hz $\frac{1}{2}$ dB
 10 Hz to 17,000 Hz $\frac{1}{2}$ dB
 17,000 Hz to 22,000 Hz $\frac{1}{2}$ dB

Output: 0.65 mv per cm per second


CALIBRATION CONDITIONS:

a) Load resistance for measured response: 47,000 Ohms
 b) Cable capacitance for measured response: 275 pf
 c) Calibration temperature 72 °F
 d) Calibration at 1 grams tracking force

SPECIFICATIONS:

1. Channel separation: 35 @ 1,000 Hz
 2. Recommended tracking force: $3/4$ to $1 1/2$ grams
 3. Cartridge D.C. resistance: 1268 ohms
 4. Cartridge inductance: 904 mH

*Does not apply to D6810 or D6827 Styli
 **All play back conditions must be optimized to meet above information.

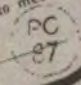Serial No. $E0318$ Inspector's Stamp 

6801-9350-01 3-74

if... This data is meaningless if your STANTON 681EEE Calibration Standard Cartridge is not fitted with a genuine STANTON stylus (type D6800EEE).

Every STANTON 681EEE Cartridge is individually calibrated using a STANTON D6800EEE stylus. The finest equipment in the world is used for this calibration and this is your guarantee of performance. Naturally you cannot get the same performance if you fit any other type of stylus. STANTON styli are the result of intensive use of STANTON'S own Scanning Electron Beam Microscope which is used to examine styli tips at up to 20,000 times magnification to reveal minute blemishes in the highly polished surface which could ultimately lead to distortion and cumulatively significant record wear. Conventional high powered microscopes are hopelessly inadequate for such a task.



Protect your performance guarantee, and your records. Insist on Genuine Stanton Replacement Styli for your Stanton Cartridges.

Sole Australian Distributors

 **LEROYA INDUSTRIES PTY**

Head Office, W.A.: 156 Railway Pde., Leederville 6007. Phone 381 2930.
 N.S.W. Office: 100 Walker St., North Sydney. 2060. Phone 922 4037.
 VICTORIA Office: 103 Pelham St., Carlton. 3053. Phone 347 7620.

LER 195



Hi Fi News

BASF TAPE FOR JAPANESE DECKS

With dealers' shelves already overstocked with cassette brands and types, why should a European-based manufacturer — BASF — decide to release a new line expressly designed for Japanese style recorders? Is it a sales gimmick or a move based on sound technical reasons?

by NEVILLE WILLIAMS

While BASF, like any other company, is not adverse to using any new angle which will help market its products, tape applications engineer Klaus Goetz explained to me the reason for his company's decision with considerable conviction and enthusiasm — this over a pleasant meal one evening in a restaurant beneath a ruined castle in the rural heart of West Germany.

I must say that, if one has to spend an evening talking technicalities, it would be difficult to nominate a more conducive environment!

From the very outset, Klaus Goetz emphasised, Philips of Eindhoven — the company which fathered the compact cassette — has been most keen to safeguard the cassette's basic compatibility as it found wider and wider application. It involved dimensions, traverse speed, track configuration, &c, all aimed at ensuring that any cassette from any source would be playable on any machine.

It was logical to assume that there would be cheap recorders and elaborate recorders, and that performance ceilings would rise with continuing research but Philips were determined to see that their cassette story would not be a replay of what was then happening to open reel tape, with the multiplicity of speeds, reel sizes and track configurations.

Because of their control of patents and their influence over the product, Philips were able to secure this basic compatibility, and this has been a powerful factor in the acceptance of the compact cassette in the domestic market. It has largely taken over from other forms of cassette, from cartridge and reel systems and remains unthreatened — so far — by the more recent Elcaset.

As part of the standardisation, Philips encouraged the use of magnetic tape

having a particular value of coercivity — a parameter which indicates the amount of magnetic energy necessary to return the particles on the tape from a full, permanently magnetised state to zero magnetisation. In turn, it indicates the amount of high frequency magnetic bias necessary to swing the particles through a full magnetic hysteresis loop.


The first figure chosen is expressed on the accompanying graph as 26 kAmp/metre and, using this as a guide, equipment manufacturers could design their electronics and their recording heads to provide the optimum level of bias for (hopefully) all cassette tapes, irrespective of manufacturer.

In broad terms, HF bias is conventionally set at a level which approximates or slightly exceeds that which secures the highest level of recording on the tape at middle frequencies. If the bias is allowed to rise significantly above this level, there will be a progressive loss at the high frequency end of the audio spectrum, as recorded and played back.

If the bias amplitude is too low, the high frequency response will tend to be exaggerated relative to the middle frequencies, with a further tendency to increased distortion on the signal, overall.

As the manufacture of cassette tape was progressively refined, manufacturers came to accept as optimum a slightly lower figure of coercivity and bias — expressed as 24 kAmp/metre — and this is currently the basis of the European standards: DIN reference tape BASF TPLH super, batch T3085 (high density iron oxide).

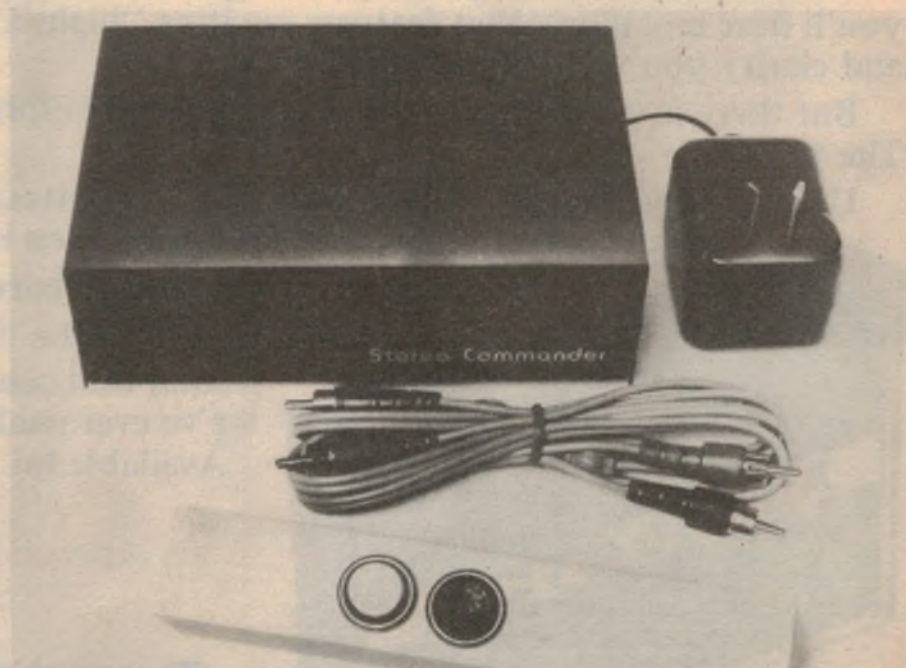This represents predominantly European thinking but, as it happens, the cassette market nowadays is dominated



With this Australian-developed "Stereo Commander" unit, hifi enthusiasts can control the volume level from their sound system from the listening position. The Commander receiver, operating from the AC mains or a 12V supply, is positioned near the amplifier and is cut into the signal circuit by means of the sockets found at the rear of most modern systems. It controls the sound level in response to supersonic (40kHz) impulses from a hand-held transmitter. Normal range is about six metres but this can be increased with the aid of an extra microphone attached to the supersonic receiver. Price, complete with power supply and patch cords, is quoted as "less than \$170". Although credited to Remote Control Systems Aust. Pty Ltd, inquiries should be directed to Insound Pty Ltd, cnr West and Hayberry Streets, Crows Nest, NSW.

OUR SECOND BEST IS BETTER THAN MOST OTHERS' FIRST BEST.

TDK's AD (Acoustic Dynamic) is one of the world's finest cassette tapes but not the best cassette tape made by TDK.

Our SA (Super Avilyn) has the edge but that's only if you're using the special bias/equalisation setting on your tape deck.

However, if you're using the normal or standard setting, you'll have to settle for AD – second best.

Chances are you won't find anything better or with more consistent sound quality for decks with normal tape selector settings (or no selector switch at all). In other words, even if you don't own extravagant equipment, with AD you can still hear extravagant sound reproduction.

You see, because of AD's superior dynamic range at the critical high end, you'll hear any music that features exciting "highs", with amazing brilliance and clarity you won't get from any other tape.

But there is something else you should hear before you try TDK's AD. The price.

Unlike other so-called "super premium" cassettes, AD's price is down-to-earth (that should make AD sound even better).

There's just no comparison between ours and what others consider to be their best. So try the

second best cassette we've ever made – AD.

Available in: C45

C60

C90

C120



 **TDK** [®] **AD**
(Acoustic Dynamic)

SOLE AUSTRALIAN AGENTS:
CONVOY INTERNATIONAL PTY LTD
4 DOWLING ST WOOLLOOMOOLOO 2011
TEL 357 2444 TELEX AA23111

by Japanese not European manufacturers — and they apparently have their own ideas about coercivity and bias levels!

For one reason or another, they have released tape after tape with a coercivity figure well above the European "24" standard and therefore requiring, theoretically, some increase in the level of high frequency bias. At the same time, there has been a tendency to edge up the bias level in Japanese recorders and both factors have operated to the disadvantage of their European competitors.

Thus the operator of a European standard machine may decide to try a highly promoted Japanese tape, without realising that it will be under-biased on his recorder. He is much less likely to notice a subtle increase in distortion than he is an added brightness due to a rising treble response. And, for many users, "brighter" has to mean "better", so the European tape suffers by comparison.

Conversely, the user of a recorder having a high bias may try a European or other tape with DIN standard (lower) coercivity. The tape will be over-biased, leading to a loss of treble response, and the conclusion that the tape is of inherently poorer quality.

Having become progressively more aware of the problem, BASF decided that they had no choice but to add to their range a tape more in keeping with current "average" Japanese (and/or Asian) practice. But, as Klaus Goetz explained to me, that is where their problems began. What was the Asian average?

There followed a lengthy research exercise, involving the purchase of sample cassettes from around the world markets in an attempt to secure representative tapes being sold by competitive companies. These were tested, compared and averaged to reveal a considerable spread in the measured figures of coercivity. Some tapes were only modestly above the European standard but others were way above it and well on the way to the standard for chromium dioxide tape.

The resulting distribution curve and a parallel study of Japanese recorders suggested that the mean lay in the region of 28 kAmp/metre and this is the figure which BASF chose as a desirable one for its new "Japanese compatible" tape cassettes.

A press release just to hand from BASF United Kingdom Ltd says that the new tape uses cobalt treated iron oxide particles and requires ideally an increase in the HF bias setting by between 1.5 and 2dB above the European DIN standard.

It also makes the point that a likely penalty of increasing the coercivity of a tape is a rise in the noise level. BASF claim that they have been able to keep the noise level of their higher coercivity tape to the same figure as for their normal LH Super: 50dB (DIN original) or

NEW CASSETTE DECK FROM TOSHIBA-EMI




Designed to integrate with their SB series amplifiers, SA receivers and ST tuners, Toshiba-EMI's new PC-3060 front loading cassette deck has many attractive features. Specifications are excellent and it has provision for Dolby recording and for normal tapes, chromium dioxide and ferro-chromium. The transport controls provide all the usual facilities but can provide, as well, automatic replay, review and cueing. For further information: Toshiba-EMI (Australia) Pty Ltd, 16 Mars Road, Lane Cove, NSW 2066.

58dB (IEC) and a signal-noise ratio of 53.5 (DIN original) or 61.5dB (IEC) — both figures based on mono track technique without Dolby. BASF claim that these figures are not bettered by any other iron oxide formulation currently available. Super LHI also shows a 1dB improvement in the high frequency area compared with LH super.

may not be optimum for each and every Japanese cassette deck — any more than a given rival tape — but BASF's Klaus Goetz is convinced that it is spot in the middle of the coercivity distribution curve, as measured.

Advance samples of the tape are being made available currently for assessment by key consumers but it is not likely to be available for general release in Australia until the first quarter of 1978, on present indications.


Its new tape, BASF "ferro super LHI",

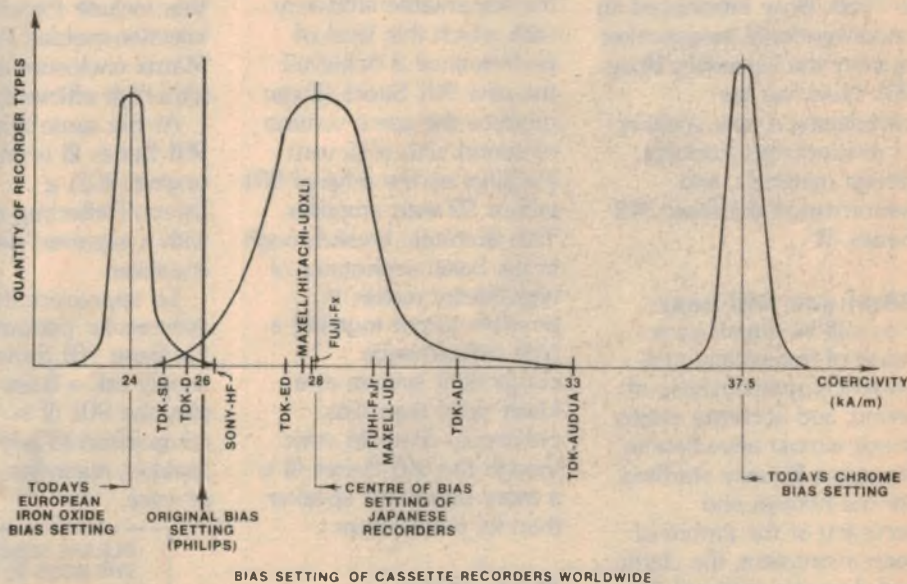

BIAS SETTING OF CASSETTE RECORDERS WORLDWIDE

Copied from data made available to "Electronics Australia" by BASF engineers in Germany, this diagram shows the divergence and spread of Japanese cassette tapes, in terms of coercivity, relative to the European DIN standard and practice. BASF's new ferro super LHI tape sits right in the centre of the Japanese curve. Incidentally, the unit kA/m replaces the older term Oersteds.

A speaker unlike any other

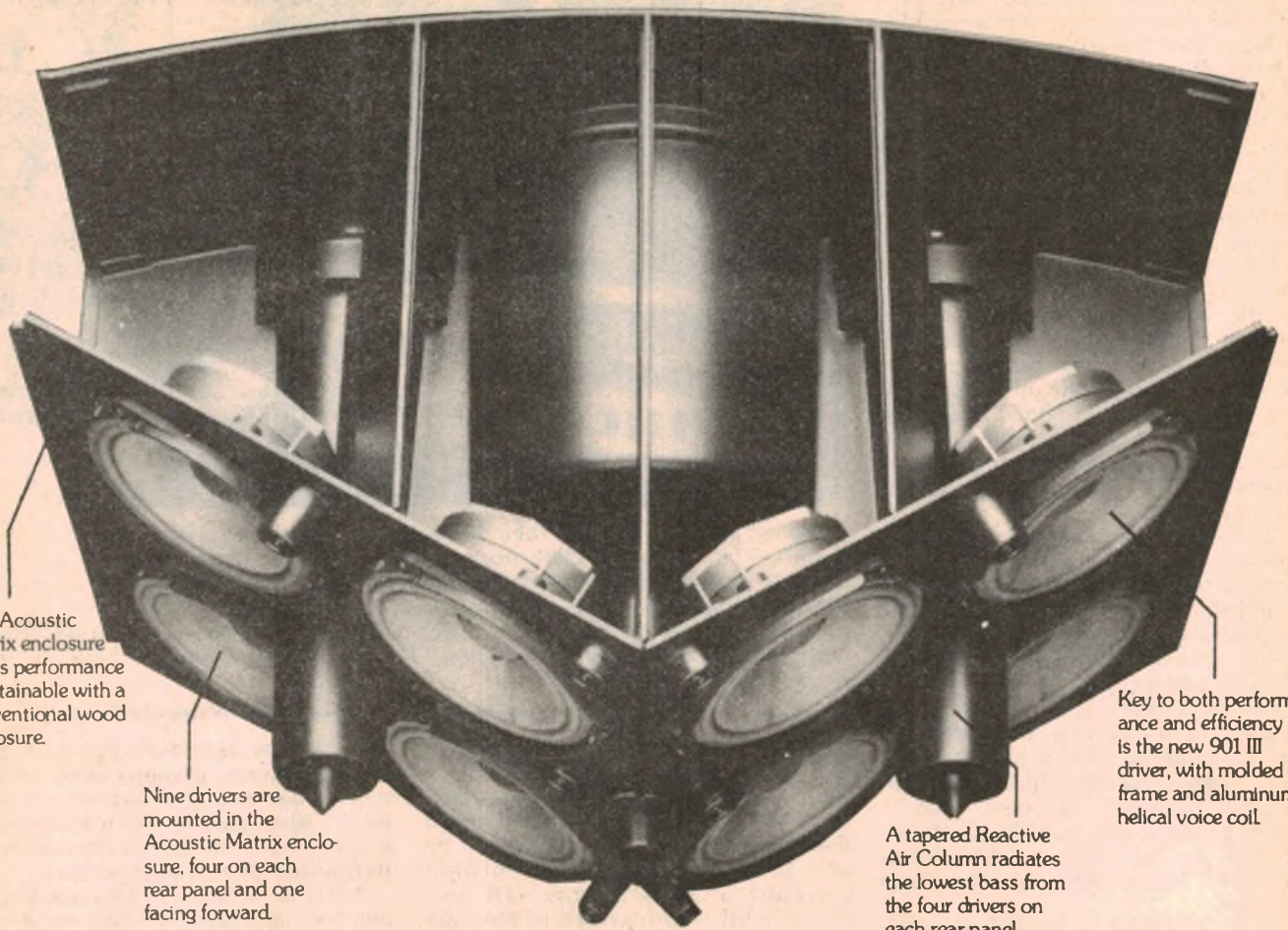

The Acoustic Matrix enclosure yields performance unattainable with a conventional wood enclosure.

Nine drivers are mounted in the Acoustic Matrix enclosure, four on each rear panel and one facing forward.

Key to both performance and efficiency is the new 901 III driver, with molded frame and aluminum helical voice coil.

A tapered Reactive Air Column radiates the lowest bass from the four drivers on each rear panel.

Introducing the Bose 901 Series III.

In 1968, Bose introduced an unconventional loudspeaker system: the legendary Bose 901. Now, we are introducing a new speaker of revolutionary concept, design materials, and performance: the Bose 901 Series III.

What you will hear.

You will be struck by a sense of immediacy and presence, spaciousness of sound, and accurate stereo image almost anywhere in the room. Equally startling are the realism and accuracy of the timbre of each instrument, the clarity and dynamic range of the deepest bass notes, and the precise definition of individual instruments.

Efficiency

Most dramatic, however, is the remarkable efficiency with which this level of performance is achieved: the new 901 Series III can produce the same volume of sound with a 15 watt amplifier as the original 901 with a 50 watt amplifier. This dramatic breakthrough in the basic economics of high-fidelity makes it possible to put together a high performance component system at a lower price than was previously possible, even though the 901 Series III is a more expensive speaker than its predecessor.

Technology

Spectacular performance and efficiency are the results of proven Bose

design concepts and technological innovations that include the unique, injection-molded Acoustic Matrix enclosure and a new, ultra-high efficiency driver.

At the same time, the 901 Series III is (as is the original 901), a Direct/Reflecting speaker with a separate electronic equalizer.

To appreciate the spectacular performance of the Bose 901 Series III, simply ask a Bose dealer to play the 901 III in comparison to any other speaker, regardless of size or price.

We submit that the 901 Series III provides more value in concepts, materials and performance than any other loudspeaker.



BOSE

PLEASE SEND ME THE 16 PAGE COLOUR BROCHURE ON THE BOSE 901 SERIES III

Name

Address

State Postcode

TO: W. C. WEDDERSPOON PTY. LTD.
3 FORD ST., GREENACRE, NSW 2190
PHONE: 642-3993

AUSTRALIAN DISTRIBUTORS

HIFI NEWS — continued

A new chromium dioxide cassette tape is also projected for 1978 and, when it appears, BASF customers will have the choice of four state-of-the-art tapes which should effectively cover present day needs:

- BASF ferro super LH (24 kAmp/m) optimised for European DIN standard recorders.
- BASF ferro super LHI, especially intended for Japanese recorders having higher than normal standard bias.
- BASF ferrochrome to suit recorders which have the appropriate bias and compensation provisions.
- BASF Chromdioxid super, conforming to the DIN standard for chromium dioxide tape.

YAMAHA-ROSE MUSIC PTY LTD was awarded one of only two Gold Stylus awards by the Federation of Australian Radio Broadcasters in recognition of the company's advertising campaign on Yamaha P.A. and mixer equipment. On air just before last Christmas, the adverts were written by Tony Fisher of Mullins, Clarke & Ralph (Vic.) Pty Ltd and spoken by Geoff Cox of 3DB.

HACO DISTRIBUTING AGENCIES, Australian distributors for "National", "Panasonic" and "Technics" products, were also the recipients of an advertising Gold award, this time from the manufacturer in Japan: the Matsushita Electric Industrial Company. The commercial was one which featured the editors of several Australian industry journals (see "Electronics Australia" for September 1976). It was devised by Tony Surtees of Quinlan Mitchell Malanot and Stott and narrated by TV personality Barrie Freedman.

ZEPHYR PRODUCTS of 70 Batesford Road, Chadstone, Victoria, announce that they have reached an agreement with Plessey Australia Ltd, which gives Zephyr sole distribution rights in Victoria for the recently announced range of Garrard turntables. Included is a high quality direct drive unit and various belt-drive models, variously featuring automatic, semi-automatic and repeat play, some with tangential tracking tone arms. They are presented in modular form, with teak bases and tinted acrylic dust covers.

In addition to the Garrard range, Zephyr will also distribute a new range of Plessey loudspeakers, manufactured in the first instance by Foster/Fostex. Exhibited earlier in the year by Plessey, the range includes domestic woofers, mid-range and tweeters, plus general purpose speakers and others designed expressly for musical instrument use.

Zephyr also distribute well known audio products such as Altec Lansing, JBL, KEF, QUAD, RCF, Radford and Auditec.



HARMAN AUSTRALIA PTY LTD announce that they have taken over the responsibility for the importation, distribution and service of Ortofon high quality and professional record playing components. Ortofon have previously been represented in Australia by Simon Gray Ltd and Rank Australia, but the new arrangement follows naturally from the acquisition of Ortofon by Harman International Industries Inc. Situated in Copenhagen, Ortofon Manufacturing A/S is well known for the manufacture of moving high quality coil cartridges, pickup arms and head amplifiers, as well as for cutting heads and amplifiers used for the production of disc recordings. "Ortofon" joins other well known names in Harman Australia's stable: JBL, Harman/Kardon, Chuo Electric (record players), Tokyo (CEC), Dynaco Inc., Bolivar Speaker Works, Tocord (cables), and White (instruments).

EMI (AUSTRALIA) LTD have advised their distributors that sales of 8-track cartridges have dropped to a level where it is no longer economical for the company to continue manufacture.

They envisaged that current stocks would not last beyond October so that, by the time you read this, 8-track cartridges on the EMI (Australia) label will belong to history, except for a few odd ones remaining on dealers' shelves.

ROSE MUSIC PTY LTD of 17/33 Market Street, South Melbourne 3205, feel that they have a Yamaha turntable available to suit every hi-fi need — and wallet! Recently added to their range, the YP211 sells for a modest \$245 but features slim styling, automatic controls, static balance arm, antiskating, cueing and gold-plated headshell contacts. It is covered by a 3-year parts and labour warranty.

The YP511, retailing for \$319, uses an 8-pole D servomotor to drive a 1.6kg turntable. Wow and flutter are down to a miserly 0.04% (WRMS). Operation is simple.

VFS SOUND, specialising in top of the range equipment has opened on the 4th floor of 106 Goulburn Street, Sydney (entrance round the corner in Nithsdale Street). You can ring manager Vic Forstman on Sydney 61-2589.

AIWA (Eye-ee-wah is the way it sounds in Australia) received a bonus in the huge Consumer Electronics Show at Chicago when their AD-6800 cassette deck was selected by a panel of independent judges for display in the special Design and Engineering Exhibit — the only cassette deck so chosen. With advanced engineering and specifications, it employs double needle meters which react to both peak and V.U. functions, plus advance circuitry to set the bias for overall flat frequency response. Details of this deck, plus its companions AD-6550 and AD-6400, can be obtained from AIWA (Australia) Pty Ltd, 14 Gertrude Street, Arncliffe, NSW.



NEW NESSEL

PROFESSIONAL SERIES

15" LOUDSPEAKER



MODEL SL 1502

This speaker is suitable for musical amplifying systems, PA, sound reinforcement, discos etc.

- Voice coil diameter 4"
- Magnet structure weighing 9 kilos
- Cone resonance 55 Hz
- Power handling 150 WATTS **\$125.00**

TRADE ENQUIRIES WELCOME

AVAILABLE FROM
NESSEL AUDIO

9 NELLBERN ROAD, MOORABBIN EAST, VIC. 3189. PHONE 95 95 10



At last it's a reality! Electronics has created the

One Man Band

In the picture above, Roland Amplification Manager, Gerry Stoll, puts the new Roland Guitar Synthesizer through its paces. Almost all the equipment shown is involved in the performance and he really does sound like a complete combo!

by LEO SIMPSON

As I sit and type I am trying to establish in perspective a fabulous new musical instrument. Having just attended an overwhelming personal demonstration lasting several hours, the potential of the new instrument seems enormous. It greatly increases the scope of musicians, and could rewrite the rulebook for recording studios.

These days people have become used to the sight of keyboard-controlled synthesizers as part of pop groups or modern jazz combos. Often they are featured in conjunction with electronic organ or electric piano. At the same time, people have come to expect certain types of sound from synthesizers. Some

would say it has become stereotyped. To a large extent, that would seem to be true.

At the same time, the role of the guitarist in these pop groups and combos has diminished in importance. But the status of the guitarist could once again become pre-eminent with the introduction of this new instrument from Roland.

At first sight, the Roland GS-500 does not look very different from any other deluxe solid-body guitar. Any other fine guitar in this context means a custom-made Gibson or Fender Stratocaster, which may cost up in the region of \$1000.

In keeping with the presentation of other deluxe guitars, the Roland GS-500 has a highly polished mahogany body, a specially designed maple neck and an ebony fingerboard. But apart from having a few more switches and knobs than usual, the appearance is certainly not out of the ordinary.

In fact, the first demonstration unit was lost for a period and the local Roland people went through a trying time worrying about the fact that it was unique and "unfloggable". Finally, it was returned, in exchange for a reward.

Closer examination of the GS-500 reveals quite a few special features in addition to those found on normal gui-

tars. For use as a standard guitar, the GS-500 has a set of six "humbucking" pickups (each pickup has two coils which are connected so as to cancel hum). Associated with the pickups is a three-position equaliser switch which provides settings for "soft", "hard" or "acoustic" sound. The latter term refers to the sound quality of an "acoustic" guitar.

Also associated with the normal guitar pickups is the tone control and volume control which are grouped together with the equaliser switch.

All the other controls and switches on the GS-500 are associated with the synthesizer functions.

The synthesizer functions are not controlled by the humbucking pickups. Instead, set close to the bridge, there is another set of pickups which look very like 1/4-inch tape heads. Apparently there is a magnet system underneath the strings (between the humbucking pickups and the fingerboard) which enables the "tape" heads to produce an output signal which is related to string vibration.

The tape heads have been placed close to the bridge so that each tape head produces output only from its designated string. This is important when the guitarist engages in "pitch bending" whereby the strings are pulled across the fingerboard to produce upward changes in pitch. If the heads were further away from the bridge the strings could be pulled across to adjacent heads, and this could upset the string identification which triggers various synthesizer functions.

Really, the heart of the system is not the guitar but the companion GR-500 synthesizer which, in addition to the overriding controls on the guitar, has a mass of controls of its own.

Basically the GR-500 has five independent sound producing sections. Each section has its own output which may be directed to any of three separate channels, plus a "Mix out" channel for connection to a single amplifier.

The mixing and selection of each or all of the five sound producing sections is controlled by the knobs and switches on the guitar itself.

As with each other section of the GR-500 synthesizer, the guitar section is threshold conscious and has a LED which lights to show that this particular section is presently operating. The idea behind the threshold for each section is that the guitarist can control the output of sounds from each of the five sections merely by plucking the strings more heavily or softly as the case may be.

The first control section on the GR-500 synthesizer is in fact the guitar output. This may be switched on or off by a three position switch on the guitar which provides for the following functions: Guitar only, Synthesizer only and Guitar plus synthesizer. The guitar control panel on the synthesizer features a single slider



This impressive Roland guitar and accompanying synthesizer can drive a little or lot of equipment to produce some exciting and complex sounds. It vastly increases the potential capabilities of one musician.

knob which is marked "equaliser". We assume this is a variable bandpass filter.

The second section of the GR-500 is the "polyensemble". This comprises an envelope generator with separate controls for attack, decay, sustain and four voicing mixers (woodwinds, reeds, brass and strings). These voices, which are all pitch-related to the notes struck by the guitar, can simulate violins, brass ensembles, harpsichord and even the human voice. It is quite uncanny to see the guitarist plucking strings and yet producing bowed violin notes! Even more mind-bending is the sight of the guitarist applying string vibrato to these bowed violin notes (which were actually produced by plucking the guitar strings) in exactly the same way as a violinist would.

At the same time, he can alternate bet-


ween guitar and violin (or any other or all of the "voices" in the poly-ensemble section) merely by varying the intensity of his string plucking. Or, he can use the appropriate switch to provide the same mode jumping.

Lest the system seem too, too clever we should remark that all the synthesizer functions are monophonic in operation, as are most synthesizers. But there is more to the system. Far more!

Now consider the Bass section on the GR-500. This also has an envelope generator with controls for attack, decay and sustain. There are also three voicing mixers which enable simulation of string bass, tuba and other bass instruments. It also has a "Last Note Priority" facility and a string selector.

The string selector allows the bass accompaniment to be applied to all

Roland Guitar Synthesizer

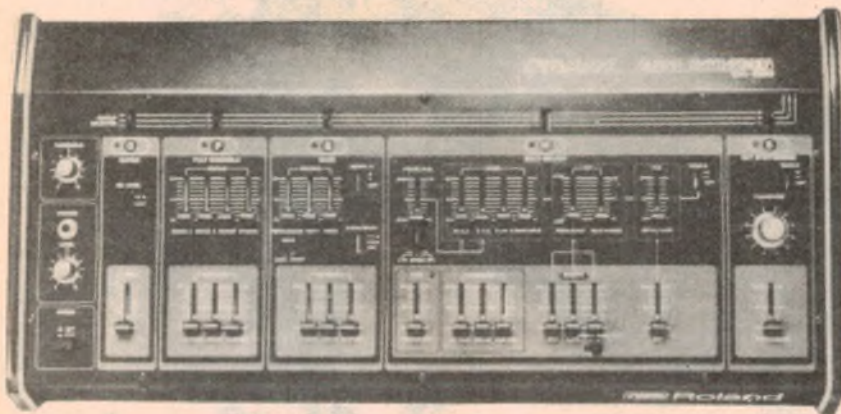

strings: 1/2/3/4/5/6; 3 strings: 4/5/6 or 2 strings: 5/6. In the last case, for example, the guitarist can play a melody on all strings but the GR-500 bass accompaniment only chimes in for the lowest two strings. Again, the bass accompaniment produced by the GR-500 can have string vibrato applied to it in the same way as the previous section.

"Last note priority" refers to a system designed to take out the last picked note by suppressing the succeeding note in down-stroke picking. For example, when string 5 is picked after string 6, the note produced by string 6 is suppressed at the exact moment string 5 is picked. String 5 will in turn be suppressed when another string is picked. The last note priority system applies only to those strings designated by the string selector.

Fourth section of the GR-500 is the Solo Melody section. This is very much like a conventional synthesizer with envelope controls, voltage controlled filter, voicing mixer, pulse width modulation and a low frequency oscillator (for scanning the voltage controlled filter).

As with the Bass section, the Solo-Melody section has the last note priority system, a 2-position touch sensitive switch which allows intonation and a LED which shows that the section is actually operating.

The last section provides controls and outputs for an external synthesizer which may also be hooked via a tape echo system.

In total, the GS-500 and accompanying GR-500 synthesizer can drive up to five separate amplifiers and loudspeaker systems, when working at its maximum potential. Where less equipment is available, the guitar/synthesizer can drive just one amplifier and loudspeaker system.

If all this seems like an immensely

complicated system, I can assure the reader that he has gained but a modest impression. When actually demonstrated it is overwhelming, both in terms of the amount of equipment involved and the sheer volume and variety of sound produced.

One wonders how the musician using the system would feel. Is he still a soloist? Maybe not. He may think of himself as a duo, trio, quartet or quintet. And as far as the musical effect is concerned he would be right. Maybe when musicians begin to master the complications and potential of this new instrument system there will be a lot of incredible new music, and more than a few schizophrenic musos!

Alternatively, the musician might develop a persecution complex (or he may even go paranoid). After all, every time he strikes a note, all these other guys seem to chime in unison. What will the Musicians Union of Australia say about it all?

There are some interesting implications for recording studios too. Presently, many pop groups use multiple track recording and dubbing to add in as many instruments and effects as they can obtain. This can be a laborious and time consuming process which can result in a mediocre final result, as far as the sound quality is concerned.

Using the Roland guitar/synthesizer, one, two or three musicians can provide a wealth of musical effects, all at the one sitting and possibly only having to use a 4-track recorder rather than a costly eight or sixteen track machine.

And in a market where the sky can be the limit as far as equipment is concerned, the projected price of the Roland GS/GR-500 seems quite reasonable. It is expected to be under \$2000, with the exact figure depending on whether import duty will be applicable. ☺

AVAILABLE FROM:

I.C.S.
16 GERTRUDE STREET
ARNCLIFFE 597 1444

DISTRIBUTORS:

NORTH

J.A. SEVERN
50 BAMBARA
CRESCENT
BEECROFT 869 1058

SOUTH

BRYAN CATT
INDUSTRIES
105 MIRANDA ROAD
MIRANDA 524 4425

EAST

RADIO DESPATCH
869 GEORGE STREET
SYDNEY 211 0191

WEST

ELECTRONIC
ENTHUSIASTS
EMPORIUM
7-10 JOYCE STREET
PENDLE HILL
636 6222

DISTRIBUTORS FOR THE ELECTRONIC INDUSTRY

Are you aware??

We offer Top Brand Products at market prices with one of the largest product ranges available from a single source of supply.

PRODUCTS AVAILABLE AS LISTED:

Semi-conductors

DELCO
ELCOMA
GENERAL ELECTRIC
INTERMETAL
ITT
NATIONAL (NS)
NEC (RECTIFIERS)
R.C.A.
SANYO
SIGNETICS
T.I.

Passives

A.E.E.
BEYSCHLAG
BOURNES
ELCOMA
ERIE
ITT
SOANAR
SPRAGUE

Electro-Mechanic

ALCO
AUGAT
CANNON
ITT
J.A.E.
JEAN RENAUD
NATIONAL (RELAY)
POMONA
ROTRON
SWITCHCRAFT
T.I. (IC SOCKETS)
THERMALLOY

Instant Component Service

16 GERTRUDE STREET, ARNCLIFFE

THE ADC CARTRIDGE CAUSES NO PERCEIVABLE WEAR OVER THE LIFE OF A RECORD.

The tests show that the ADC XLM-MKII cartridge causes no perceivable wear until after 60 plays. Industry sources estimate the "life of a record" (the average number of times a record is played) to be 40 to 50 plays.

A series of tests conducted by a leading independent audio-testing laboratory prove it* Other cartridge manufacturers may talk about less record wear, but ADC has proven no wear over the

average life of a record.

The reason for this is our unique patented design. It's patent #3294405.

We call it the "induced magnet" cartridge.

Most cartridges are designed so that a heavy magnet is part of the moving system.

The ADC XLM-MKII is

different, because our engineers found a way to detach the magnet and reposition it above the stylus, so the stylus applies less pressure against the groove.

Less pressure means less wear.

The fact is, of all the leading brands, ADC cartridges have the lowest mass moving system you can buy. That means better sound and superior performance.

The XLM frequency response is exceptionally flat, from 15Hz to 24KHz ± 1.5 dB. And for the ultimate in stereo reproduction, it has a minimum of 28dB of channel separation.

Think about it. In the long run you'll probably spend more on your record collection than you will on your whole stereo system. So it makes sense to buy a cartridge with proof that it makes your records sound better and helps them to live longer. The ADC low mass cartridge.

Unbelievable.

THE ADC LOW MASS CARTRIDGE.


IT HELPS YOUR RECORDS LIVE LONGER.



A BSR COMPANY

BSR (A'asia) Pty. Ltd.,
Anne Street, St. Mary's, NSW 2760.


THE PROOF:

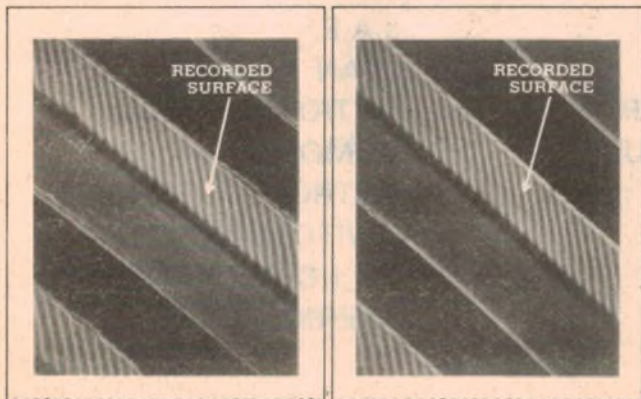


This is a photomicrograph of a 20kHz record groove that has never been played before.

This is a photomicrograph of a similar 20kHz record groove played 75 times with an ADC XLM-MKII cartridge. As you can see there is no difference.

THE DIFFERENCE:

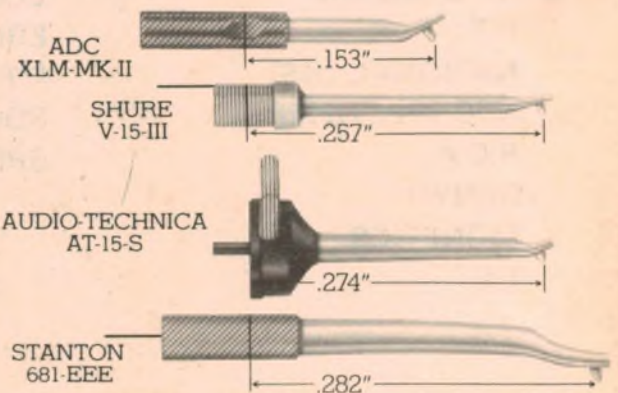

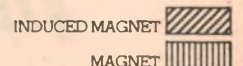The way to get the most accurate reproduction of sound is to lower the total effective mass of the moving parts of the stylus. And that's exactly what our engineers did. In fact, of all the leading brands, ADC cartridges have the lowest mass moving system you can buy.



* CBS Technology Center Project 1108: Record Wear Test Program. Performed for Audio Dynamics Corporation. December 1976.

COMPTON BSR137

Mitsubishi DA-F10 FM-AM tuner

Mitsubishi is a new name to the Australian high fidelity market. This long-established Japanese manufacturer is introducing a range of premium equipment typified by the tuner reviewed here. The Mitsubishi DA-F10 is an AM/FM-stereo tuner with excellent specifications, and is one of the few tuners on the market with a selectivity switch.

Housed in a fairly bulky case, the Mitsubishi DA-F10 has styling which looks very "technical" without being overcrowded with knobs and gee-gaws. The front panel is finished in brushed aluminium while the dial, meters, handles and top cover have a semi-gloss charcoal finish. Case dimensions are 425 x 170 x 280mm (W x H x D), including handles and real projections. Mass is 7.5kg. Clearance of about 195mm is required at the rear of the tuner to allow the AM rod antenna to be fully swung out if necessary for good reception.

Controls are fairly simple and are well labelled so that their purpose is self evident. The Selector knob has four positions: AM, FM auto, FM mono and FM mono/muting off. In the auto and mono modes of FM reception the muting threshold is just under 10 microvolts. Signals smaller than this figure can be received by switching the selector to "FM mono/muting off".

The Mitsubishi DA-F10 is one of few tuners which can boast a "selectivity" switch. In the narrow selectivity setting the tuner has improved suppression of adjacent channel interference, which is presently not a problem in Australia. However, the selectivity switch is still a most worthwhile feature because it is associated with improved figures for distortion and separation between channels (when set to the wide selectivity setting).

A circular dial within a rectangular frame gives an unusual touch to the styling. The FM portion of the dial is provided with 200kHz calibrations, while the AM calibrations are almost non-existent. Does that indicate Mitsubishi's comparative attitudes to FM and AM? The answer would seem to be yes.

Like most other manufacturers of FM/AM tuners, Mitsubishi have quite vague specifications for the AM section and neglect to mention the frequency response at all. Needless to say, the AM performance is good enough to recognise a tune, but not enough to get excited about.

On the rear panel there are three pairs of RCA sockets which provide

fixed and variable stereo outputs, plus output signals for a Multipath display on an oscilloscope. Terminals are provided for FM antenna connection via 75 ohm coax cable or 300 ohm ribbon, AM long-wire antenna and ground. Our sample was fitted with two-core flex and and two-pin plug.

characteristics are very similar to those obtained with many other premium quality units. We were not able to confirm Mitsubishi's figures for ultimate signal-to-noise ratio, which were 70dB in stereo and 75dB in mono. Our results were 68dB in mono and 64.5dB in stereo.

Limiting was complete at 3 microvolts input. Note that while the measured ultimate signal-to-noise ratios are not the highest we have measured, the Quieting slope, ie, the rate at which the tuner approaches its ultimate S/N ratio, was comparable to the best tuners we have tested.

Response of the signal strength



We hope that units sold to the public are fitted with the correct three-core flex and three-pin mains plug.


Removing the top cover reveals an uncluttered internal layout with all components readily accessible. Access to the PC boards is easily gained by removing the underside panel. Semiconductor complement is five integrated circuits, 38 transistors and 19 diodes.

Much of the tuner's performance is displayed in the two graphs accompanying this review. The Quieting

meter is also shown of the graph of the Quieting characteristics. From this it can be seen that the meter circuitry appears to be saturated for signals of 200uV and beyond. While this is not a very progressive response it could be argued that the meter tells you all you need to know. After all, for signals of 200uV and above the tuner has reached its ultimate signal to noise ratio.

The other graph displays the frequency response and excellent separation between channels when operated in the wide selectivity mode. In fact,

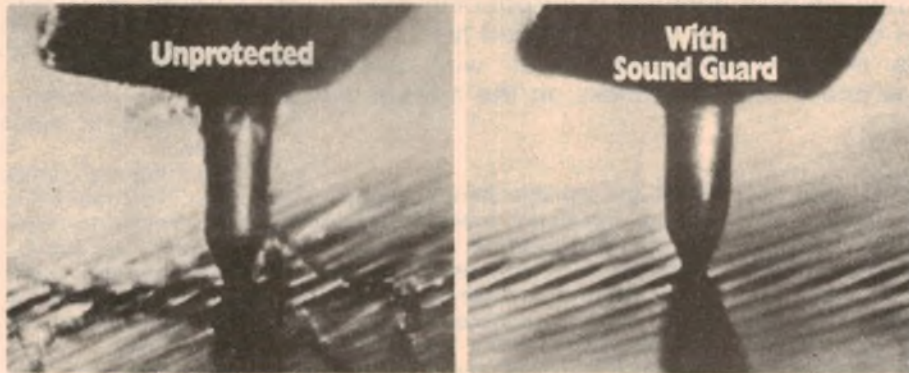If you can see a difference, imagine what you'll hear.



Magnified, you can see record vinyl wearing away.

With same magnification, record vinyl shows no wear.

You're looking at the solution to one of the oldest problems in audio—how to protect records from wear, while at the same time preserving full fidelity.

It's called Sound Guard,* and it's remarkable.

Independent tests show that discs treated with Sound


distortion as "mint condition" discs played once.

A by-product of dry lubricants developed for aerospace applications, Sound Guard preservative is so smooth it reduces friction, yet so thin (less than 0.000003") it leaves even the most fragile groove modulations unaffected.

Len Feldman in *Radio Electronics* reports "At last!

The long awaited record-care product has arrived. It preserves frequency response

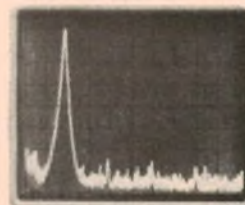
in a kit complete with a non-aerosol pump sprayer and



Test record played first time.



After 100 plays without Sound Guard.

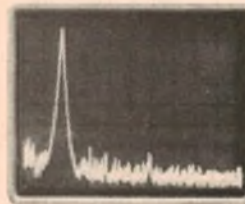

Identical test record after 100 plays with Sound Guard.

Guard preservative played 100 times display the same full amplitude at all frequencies and the same absence of surface noise and harmonic

while reducing distortion and surface noise." It's effective and safe for all discs, from precious old 78's to the newest LP's.

Sound Guard preservative,

velvet buffing pad, is available in audio and record outlets.


Sound Guard keeps your good sounds sounding good.



*Sound Guard is Ball Corporation's trademark for its record preservative. Copyright © Ball Corporation, 1976.

Sound Guard is distributed throughout Australia by
LEROYA INDUSTRIES PTY

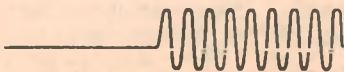Head Office, W.A.: 156 Railway Pde., Leederville 6007. Phone 381 2930.
N.S.W. Office: 100 Walker St., North Sydney 2060. Phone 922 4037.
VICTORIA Office: 103 Pelham St., Carlton 3053. Phone 347 7620.



MITSUBISHI DA-F10 TUNER

this is only the second tuner we have tested to date which has turned in separation figures in excess of 50dB. Even in the narrow selectivity mode the separation figures are quite adequate, at 30dB or more over most of the audio range.

Frequency response was quoted as 30Hz to 15kHz ± 1 dB. We measured it as 20Hz to 15kHz within $\pm 0, -2$ dB in both mono and stereo.

19kHz suppression was 65dB down while 38kHz suppression was greater than 70dB. Readers may wonder how we managed to produce these two figures when the ultimate signal-to-noise ratio in stereo was in fact higher than 65dB (ie. worse). The answer is quite simple. A large component of the residual noise of the DA-F10 is hum. We measured the 19kHz level by first passing the residual noise through a high-pass filter to remove the hum and other low frequency components.




As might be expected from the fine calibrations of the FM portion of the dial, calibration accuracy is very good and would appear to be within better than 25kHz over the whole tuning range.

Harmonic distortion is quoted for both wide and narrow selectivity settings, but the modulating frequency and modulation level are not specified. For the narrow selectivity mode, we obtained mono distortion readings of 0.25% at 100Hz, 0.22% at 1kHz and 0.4% at 6kHz; while in stereo the respective readings were 1%, 0.8% and 0.4%. Switching to wide selectivity gives a slight improvement to the mono distortion figures and a very worthwhile improvement to the stereo figures. In mono we measured 0.23% at 100Hz, 0.18% at 1kHz and 0.29% at 6kHz. In stereo mode, the respective figures were 0.5% at 100Hz, 0.4% at 1kHz and 0.3% at 6kHz. These figures are not as good as those quoted by Mitsubishi, but are still quite creditable.

We listened to the DA-F10 process program material from FM stations and from our own "off-air" music signals via our FM generator and found the sound reproduction very good. The tuner mutes and unmutes without "pops" or other transients and tuning is not very critical — provided the "lock" and "stereo" indicators are alight you are virtually assured of excellent sound.

Overall, the Mitsubishi DA-F10 is an impressive new contender in the hifi market and one which must be considered by those desiring a unit capable of premium performance. Recommended retail price is \$347.00.

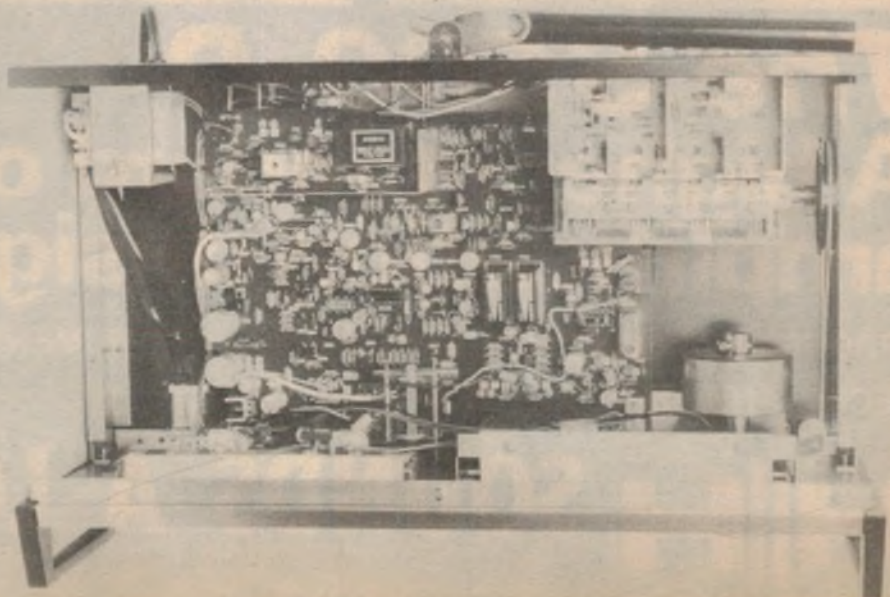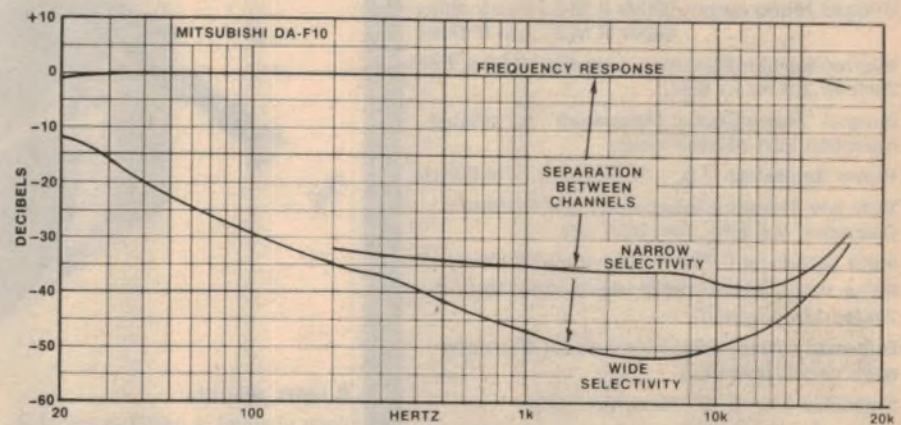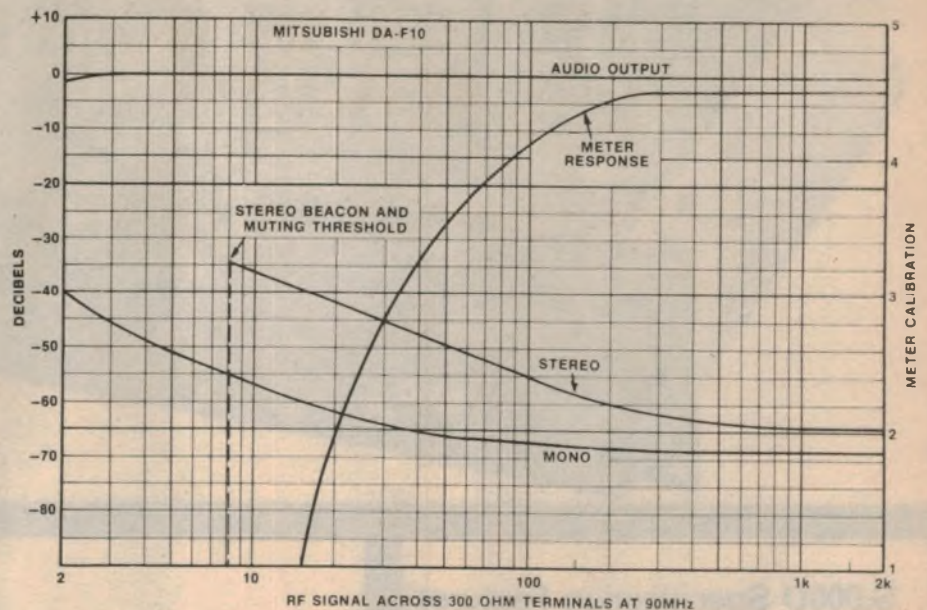Further information can be obtained from hifi retailers or from the Australian distributors AWA-Thorn Sales Pty Ltd, 348 Victoria Road, Rydalmere, NSW 2116. (L.D.S.)




Meet the New Leader....



S.500D Specification Features

- * Power output 340W R.M.S. into 4 ohms
500W R.M.S. into 2.5 ohms
- * Bridged Mono output 900W R.M.S. into 5 ohms
640W R.M.S. into 8 ohms
- * Intermodulation Distortion Less than 0.02% from 20Hz to 20KHz F1 60Hz.
- * Integral "Force Cooled Dissipators" for reliable operation into adverse loads.
- * Power Bandwidth +0, -1dB from D.C. to 20KHz.
- * Very low Transient Intermodulation Distortion. Restricted rise time, fast slew rate.
- * Input sensitivity 0.75V for 300W into 4 ohms.
- * Noise 105dB Below 180W into 8 ohms 10Hz to 20KHz. Unweighted.
- * Elaborate system protection against short and open circuit operation
- * Small size 3½" x 19" Rack mounting.
- * 1KVA Toroidal power supply providing 55 joules of energy.

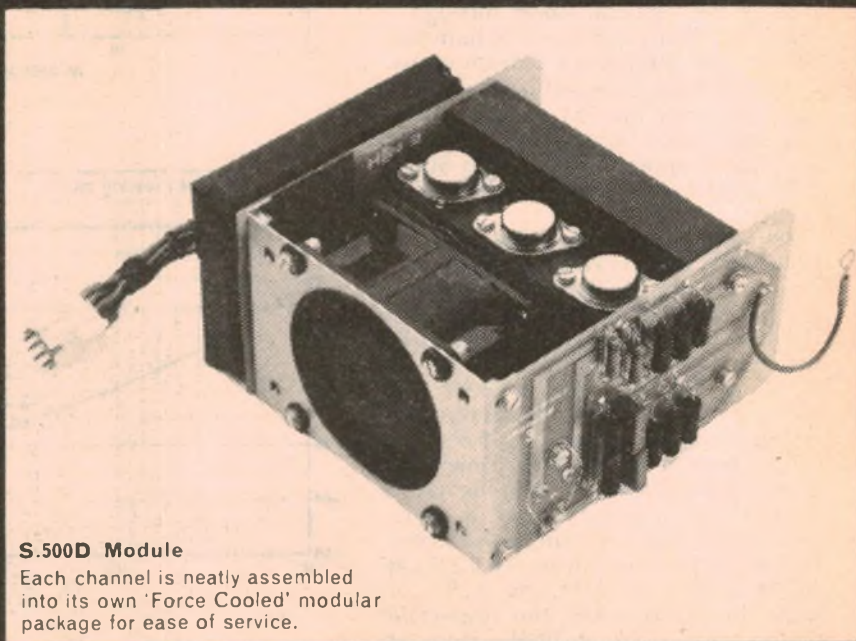

S.500D Module

Each channel is neatly assembled into its own 'Force Cooled' modular package for ease of service.

The S500-D

A higher standard of power amplification design

- PROFESSIONAL POWER AMPLIFIERS • INSTRUMENT AMPLIFIERS • P.A. SYSTEMS
- ECHO AND EFFECTS UNITS • MIXERS



SOUNDS A LOT BETTER

Literature available from the Australian Distributors:
W. C. WEDDERSPOON PTY. LTD., 3 FORD ST., GREENACRE, N.S.W. 2190
PHONE: 642-3993; 642-2595

Standard PM-403W stereo amplifier

Bargains are rare in the hifi market. Whether or not you regard this Standard PM-403W amplifier as high fidelity is up to you, but there is no denying that it is a bargain. It has all the usual control facilities and a rating of 12 watts per channel into 8-ohm loads.

Measuring 340 x 100 x 200mm (WxHxD) and with mass 3.6kg, the Standard PM-403W has a neat extruded aluminium front panel and a wraparound timber case with simulated wood veneer. It is supplied fitted with three-core mains flex and three-pin mains plug.

Five knobs and four push-buttons provide the control facilities. The three-position selector gives a choice of three signal sources: phono, tuner and auxiliary, while the "tape monitor" push-button allows selection of a cassette or tape recorder.

The loudspeaker selector pushbutton gives a choice of two pairs of loudspeakers, "main" and "remote". Plugging in a pair of headphones switches off the "main" loudspeakers if they happen to be selected.

With the exception of the headphone socket, all signal inputs and outputs are DIN sockets. Four 2-pin DIN sockets provide the loudspeaker connections while the inputs are made via 5-pin sockets.

A slider switch on the rear panel converts the phono input to suit a ceramic cartridge instead of a magnetic type. Since this merely inserts a large series resistor into the input circuit of each channel, it is hardly likely to provide accurate equalisation for a ceramic cartridge. However, this should not worry many prospective buyers, as magnetic cartridges are now available at very reasonable prices and provide a far superior result.

Removing the four rubber feet allows the chassis to be withdrawn from the timber case. Most of the circuitry is accommodated on one PC board, with the plastic power transistors clamped to a common heatsink bracket. Access to the copper side of the PCB is via a large cutout in the chassis. Most of the wiring is neat and tidy, although we would prefer to see the mains switch and its connections a little less exposed.

With a semiconductor complement of 18 transistors and 10 diodes the circuit of the amplifier can be described as simple. The power amplifiers use six transistors each, with quasi-complementary output stages and capacitive coupling to the loudspeakers. The output capacitor is incorporated in the feedback network so that the damping factor at low frequencies is high.

The RIAA preamplifiers each use two transistors in a direct-coupled configuration while the tone control circuit uses a single transistor as a common-emitter amplifier to make up the losses in the passive RC networks.

In fact, the overall circuit configuration of the Standard PM-403W is very similar to some of the most popular high fidelity amplifiers of a few years ago, which in terms of 1977 dollars (September 1977, that is) cost a whole lot more.


Our measurements confirmed the specifications of the PM-403W in most respects. We measured power at 10 watts per channel into 8-ohm loads, with one or both channels driven. Harmonic distortion at this power level was 0.7% at 10kHz, 0.4% at 1kHz and 0.35% at 100Hz. Under the same conditions, separation between channels was 45dB at 10kHz and better than 60dB at 1kHz and 100Hz.

Into 4-ohm load, we measured 14.5 watts into a single channel and 12 watts with both channels driven. Harmonic distortion at full power at 1kHz into 4 ohm-loads was about 1.5%.

Phono sensitivity was 2.8mV for full power at 1kHz and the overload threshold ranged from 80mV at low volume control settings to 40mV at high settings (at 1kHz). Phono signal to noise ratio was 64dB with respect to full power and an input signal of 10mV at 1kHz, with a typical cartridge connected. Translated, that means the amplifier is reasonably quiet.

Other parameters tested satisfactorily. Listening tests confirmed that the performance was good and that the power was adequate in typical rooms with loudspeakers of reasonable efficiency.

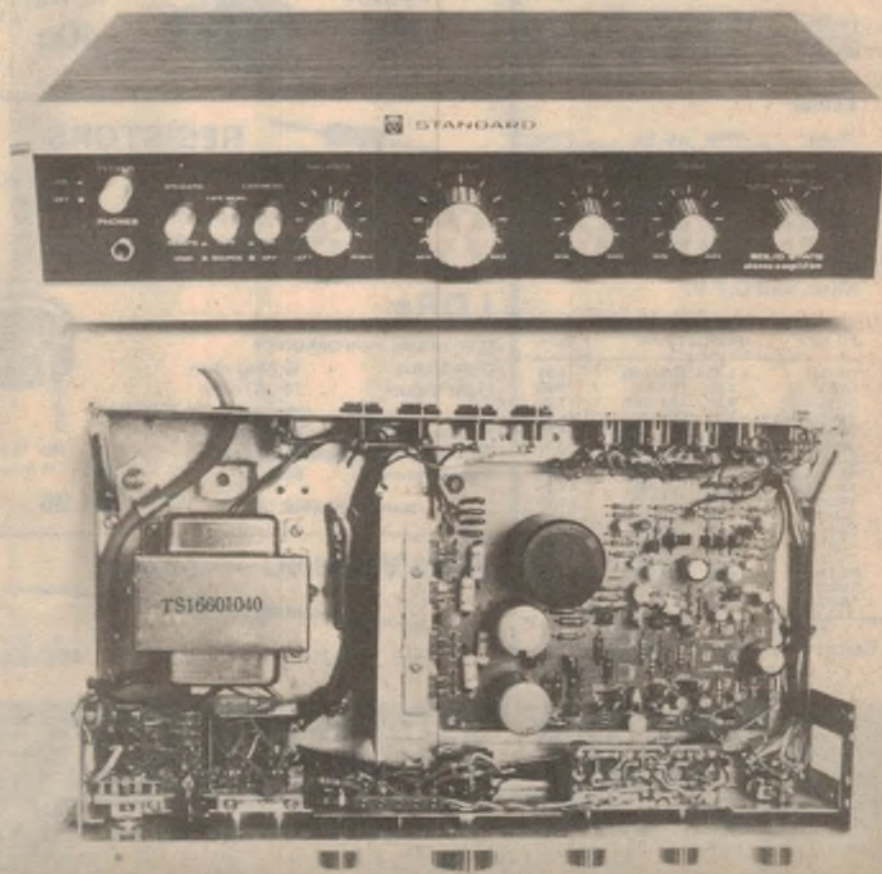In summary, our impressions of this neat and compact amplifier were very favourable. And at the bargain price of \$59, how can you go wrong? Rush out and get on the queue at Classic Radio, 245 Parramatta Road, Haberfield, NSW 2045. (L.D.S.)



T.T.L.

I.C. No.	Price	I.C. No.	Price
SN7400N	44	SN7473N	85
SN7401N	44	SN7474N	90
SN7402N	44	SN7475N	1 10
SN7403N	44	SN7476N	1 10
SN7404N	44	SN7483AN	1 65
SN7405N	44	SN7486N	75
SN7407N	75	SN7490AN	90
SN7408N	44	SN7492AN	85
SN7410N	44	SN7483AN	85
SN7412N	44	SN7495AN	1 50
SN7413N	90	SN7496N	1 90
SN7420N	44	SN74107N	75
SN7430N	44	SN74121N	79
SN7432N	65	SN74122N	95
SN7437N	75	SN74123N	1 10
SN7442N	1 10	SN74141N	2 88
SN7447AN	1 65	SN74145N	1 95
SN7448AN	1 55	SN74154N	2 10
SN7454N	44	SN74192N	2 10
SN7460N	45	SN74193N	2 10
SN7472N	75	SN74199N	3 75

C./M.O.S.

I.C. No.	Price	I.C. No.	Price
TP4001AN	44	TP4024AN	1 25
TP4007AN	44	TP4027AN	1 16
TP4011AN	44	TP4028AN	1 85
TP4012AN	44	TP4043AN	1 95
TP4013AN	1 16	TP4049AN	1 10
TP4015AN	1 95	TP4050AN	1m10
TP4016AN	1 16	TP4051AN	1 85
TP4017AN	2 10	TP4304AN	1 65
TP4018AN	2 65	TP4306AN	1 65
TP4022AN	1 99	TP45B1AN	5 50
TP4023AN	44	TP45B2AN	1 95

Audio Amplifiers

I.C. No.	Price	I.C. No.	Price
SN76001N	1 42	SN76023N	2 65
SN76005N	2 25	UPC 1025H	2 50

Clock Chips


I.C. No.	Price	I.C. No.	Price
MM5314	5 80	TMS3834	8 75

Linear

I.C. No.	Price	I.C. No.	Price
LM381	3 48	SN72723L	1 20
SN72301AP	99	SN72723N	1 20
SN72555P	95	SN72741L	60
SN72709L	99	SN72741P	60
SN72709P	95	SN72747N	95
SN72710	1 17	SN72748N	80

Misc. and C.T.V.

I.C. No.	Price	I.C. No.	Price
HA1125	3 20	TBA5500	6 33
LM2917M	2 50	TBA560	7 20
SN76226D	2 20	TBA560C	7 20
SN76227N 07	2 58	TBA720A	4 75
SN76231N	2 10	TBA730	4 50
SN76533N	3 85	TBA750A	4 50
SN76570N	2 35	TBA750BQ	4 50
SN76666N	1 41	TBA760	4 25
TA7070P	4 50	TBA900	5 25
TA7074P	5 35	TBA920	5 75
TA7173P	9 10	TCA270S	5 20
TAA300	4 50	TDA2620	6 50
TAA574	5 50	TDA2630	10 50
TAA630S	4 50	TMS6011NC	9 77
TBA240B	4 50	UPC30C	1 50
TBA520	4 75	UPC574J	1 30
TBA530	4 25		

Spun-Aluminium Knobs  Only **80c**

Plugs and Sockets

CB



PL259 ONLY \$1.29




SO239 ONLY \$1.30

1 metre Patch Cord **PC258 \$4.50**

Dip Switch


16 pin dual in-line switch. Fits into 16 pin DIL socket.

\$2.25

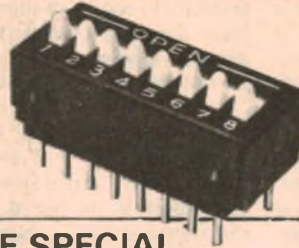

PLASTIC CASE SPECIAL

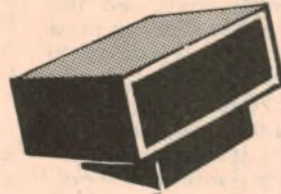As used in many clock projects. Has sold at double this price before. You'll have to be in quick for this one.



\$3.75


Quality IC Sockets

14-way **35c**



16-way **40c**

RESISTORS

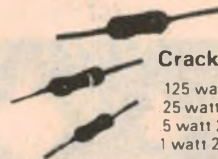

Cracked carbon

125 watt 2.7 ohm - 2.2 meg
25 watt 2.2 ohm - 10 meg.
5 watt 2.2 ohm - 10 meg.
1 watt 2.2 ohm - 2.2 meg.

1-9 10-99 mixed
4c 3c 2c
4c 3c 2c
5c 4c 3c
6c 5c 4c

LDRs

ELECTRICAL PERFORMANCE


Dark Value 10 Meg ohm
Light Value 75.300 ohm (measured at 1000 lux)
Recovery Rate 200k/ohms
Permissible Voltage 150 Vpeak
Capacitance 6pF



Dia 14 mm
H. 9 mm

Similar to ORP12 **Only \$1.95**

WIREWOUND — 2 watt

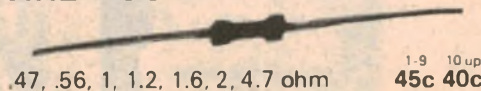


.47, .56, 1, 1.2, 1.6, 2, 4.7 ohm

1-9 10 up
45c 40c

Capacitor Corner

Disc Ceramic — 50 volt

2m2 3 3 4 7 6 8 8 2 10 15 22
33 47 68 82 100 150 220 330
470 1K, 2K2 3K3 4K7 10K, 22K.
47K pfd
100K 25V

1-9 10 up

11c 8c
16c 14c

Polyester and Foil — 250 volt

001 0015 0022 0033 0047
0068
01 012 015 027 033 039
047 mfd
056 068 082 mfd
1 12 15 22 mfd
27 33 .47 mfd

1-9 10 up
18c 15c
22c 18c
25c 20c
35c 30c
40c 35c

Mylar 50 volt

.01 mfd **10c** each



HAVE YOU SENT IN YOUR COUPONS FOR THE FREE SAMPLES ON PAGE 44 OF THE 'DAVRED CATALOGUE'?

Transistors

AC125	95c	BF185	80c
AC126	55c	BF259	\$1 20
AC127	75c	BF337	\$1 30
AC128	75c	BF594	42c
AC187	80c	BF595	42c
AC188	85c	BFR40	61c
AC187-01/188-01	\$1 36	BFR80	61c
AC187-01	65c	BFT43	75c
AC188 01	75c	BFY51	70c
AD149	\$2 20	BSX21	95c
AD161/62 pair	\$3 00	BU105	\$4 95
AD161	\$1 70	BU108	\$4 25
AD162	\$1 50	BU126	\$3 45
AF106	\$1 60	BU208	\$4 20
AF125	\$1 30	E1222	\$1 50
AF126	\$1 30	E5386	50c
BC107B	24c	SP8385	\$2 20
BC108B	24c	TIP29A	77c
BC108C	24c	TIP30A	88c
BC109B	24c	TIP31A	91c
BC142	\$1 05	TIP32A	95c
BC143	\$1 10	TIP33A	\$1 27
BC158B	30c	TIP34A	\$1 46
BC177B	25c	TIP35A	\$2 20
BC178B	25c	TIP36A	\$3 06
BC179B	45c	TIP41A	\$1 15
BC182B	25c	TIP42A	\$1 30
BC182L	25c	TIP49	\$1 32
BC182LB	25c	TIP53	\$3 53
BC183B	25c	TIP120	\$1 99
BC183L	33c	TIP125	\$2 12
BC183LB	38c	TIP2955	\$1 46
BC183LC	33c	TIP3055	\$1 10
BC184B	25c	TIS62A	60c
BC184C	25c	TIS63A	60c
BC184L	32c	TIS64A	55c
BC184LC	33c	TIS91	55c
BC212B	21c	TIS92	55c
BC212L	25c	TIS93	55c
BC213B	21c	2N1304	65c
BC213L	21c	2N1305	65c
BC214B	30c	2N1307	95c
BC547	30c	2N3053	60c
BC548	30c	2N3055	\$1 25
BC549	30c	2N3702	45c
BC557	30c	2N3703	40c
BC558 or B	30c	2N3704	40c
BD139	90c	2N3707	45c
BD140	90c	2N3903	48c
BF173	90c	2N3904	50c
BF179	\$1 10	2N3906	50c

DAVRED ELECTRONICS PTY. LTD.

104-106 King Street Newtown Sydney Australia P.O. Box 317 Newtown, N.S.W. 2042.

THE NEW BREED IN ELECTRONICS SERVICE

Telephone 516-3544

Crystal Sockets

Small. Suitable for all CB projects. Hurry! ONLY 25c




20K TRANSISTOR POTS — WING

12 mm dia. 10c ea.


STYLII SPECIAL

Double Diamond

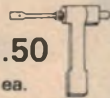B.S.R. ST2 ST10a. **\$2.50**
ST15a. ST17a. ea.



L.E.D. BEZELS

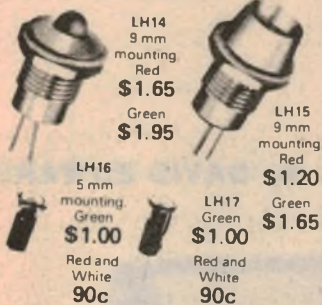

LH14
9 mm
mounting
Red
\$1.65
Green
\$1.95

LH15
9 mm
mounting
Red
\$1.20
Green
\$1.65

LH16
5 mm
mounting
Green
\$1.00
Red and
White
90c

LH17
Green
Red and
White
\$1.00
90c

Insulated Battery Clips



CL4

These won't last long. 10 mm wide jaws. black PVC cover only. Only 12c ea.


Plastic Mini-Box



Tough little black box ideal for TV games controls, small projects. 40 x 29 x 15 mm. PB1 LOOK Only 18c ea.

C.B. HAND HELD BH15 BATTERY HOLDER

Holds 8 penlight cells to give total 12V. Suitable for use with our UM3 rechargeables.

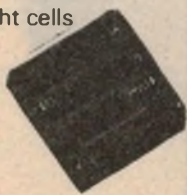

ONLY 95c.

BATTERY SPECIAL

Japanese 006P (equiv. 216). Here's value and quality **65c each**
Japanese AAA **30c ea.** (anc)

Thank you very much for the tremendous response


Thanks to the customers who have written in advising that they would not be without their 'New Davred Electronics Catalogue' and how they are amazed at the service they have received from our 'mail Order Department'. They also advise that they are continually using the semi-conductor specification pages, electronic symbol guides, and component technical information scattered throughout.

Not only is it the most up-to-date electronic catalogue of its kind, but also it has one of the largest ranges of 'build your own kits' and electronic components, at the most competitive prices in Australia.

Even though 'Electronics Today International' printed more copies of the issue containing the 'Davred Catalogue' you may have found they were sold out, so we suggest that you write now using the coupon below to receive your copy as stocks will definitely not last long.

Morse Keys

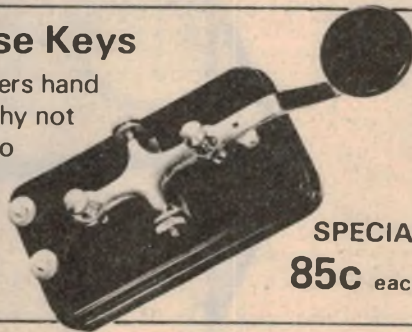Beginners hand key. Why not buy two for the kids.



SPECIAL 85c each

Stereo Magnetic Pre-amps!

Scoop buy. Uses std. 216 battery. **Only 100 left \$4.75**

Housed in handy little box. Has 5 pin din lead to plug into amp 5 pin socket from cartridge.

Mail Order Instructions

Minimum P. P \$1.00
Orders over \$9.99 must include additional postal charges (see right)

ADDITIONAL POSTAL CHARGES

Order value	Charge
\$5 — \$9.99	Nil
\$10 — \$24.99	\$0.50
\$25 — \$49.99	\$1.50
\$50 — \$99.99	\$2.50
\$100 or more	\$4.00

PLUGS AND SOCKETS

P85	Auto Cigar Plugs	60c
P7	3 pin moulded Plug	25c
S7	3 pin moulded Socket	20c
P14	3 pin Din Plug	48c
P15	5 pin Din Plug	55c
S15	5 pin Din Socket	35c
P27	Insulated Phono Plug	25c
P33	2 pin AC Adpt. Plug	35c
S33	2 pin AC Adpt. Socket	70c
P37	2.1 mm DC Adpt. Plug	30c
P38	2.5 mm DC Adpt. Plug	30c
P45	6.5 mm std. Jack Plug	55c
P51	Std. Stereo Jack Plug	55c
P62	3.5 mm Min. Phone Plug	30c

SWITCHES

SW24	SPST Toggle	65c
SW18	DPDT Slide	35c
SW45	SPST Min. Toggle	\$1.10
SW50	SPST Sub Min. Toggle	75c
SAS-1	Proximity Switch	\$1.90
Complete with magnet		
SW16	Min. Push-on	35c
SW55	Push-on Irrid. end	70c

Rechargeable Batteries

Top brand Ni-Cad for radios, tape recorders, and all other projects

		1-9	10 up
UM3	Penlight	\$1.65	\$1.45
UM2	C size	\$3.50	\$3.20
UM1-3500	D size	\$7.25	\$7.00
NU-1200			
mA H	D size	\$3.25	\$3.00

CHARGING UNITS

At last charging units for all sizes of Ni-Cads for +ve and -ve polarity and regulated charge. **4V supply required.**

NC1	(fits UM3 batteries)	\$3.40
NC2	(fits UM2 batteries)	\$4.25
NC3	(fits UM1 batteries)	\$4.59

Metric Screws and Nuts

A wide range of metric sizes are now available to suit many applications. These have been exceptionally hard to get but now a fully comprehensive range is available.

Sizes as follows:

- 1.7 x 4 mm PPH.
- 2 x 5 mm PPH Philips Flat Head.
- 2 x 6 mm PRH Philips Pan Head.
- 2.6 x 5 mm PBH Philips Binding Head.
- 2.6 x 8 mm SRH.
- 3 x 5 mm PRH.
- 3 x 8 mm PRH Philips Round Head.
- 3 x 15 mm PRH.
- 3 x 18 mm PRH.
- 2.6 mm Hex Nuts.
- 3 mm Hex Nuts.



95c per pkt of 25

2.6 x 40 mm PPH with nuts. Pkts. of 10 sets **\$1.20c**

Davred Electronics Pty. Ltd
P.O. Box 317, Newtown, Sydney, Australia 2042

I enclose 50c to cover postage. Please send the 1977/8 Electronic Catalogue.

TO: Name
Address
Postcode

DAVRED ELECTRONICS PTY. LTD.

104-106 King Street Newtown Sydney Australia P.O. Box 317 Newtown, N.S.W. 2042.
THE NEW BREED IN ELECTRONICS SERVICE Telephone 516-3544

Simple mixer for pick-up and microphone

The little mixer unit described in this article will enable you to mix together a high level source such as the output from a record player or a tape recorder, and a low level source such as a microphone. It can be very handy for generating home movie soundtracks and can also be used as a microphone preamplifier for use with hi-fi amplifiers lacking such facilities.

by DAVID EDWARDS

The incentive for this project arose out of a need to mix a microphone with a high level source, to generate the soundtrack for a home movie. But it soon became obvious that a simple mixer capable of meeting these requirements could also be used in a variety of other situations.

For instance, the unit could be used to mix a microphone signal with a high level audio signal, making it possible to "sing along" with records or tapes. Other uses which come to mind include adding an identification (verbally) to computer programs or RTTY messages stored on cassettes, and in adding personal comments to your own recordings.

As you can see from the photographs, the mixer is constructed in a small low-cost metal case. The one used for the prototype measures 150 x 100 x 60mm, and has an aluminium chassis with a steel lid. It was kindly supplied by Dick Smith Electronics Pty Ltd. We elected to power the unit with a battery, both on the grounds of cost and to minimise any possible hum problems.

Readers are referred to the accompanying table for a list of the pertinent specifications of the prototype.

Turning now to the circuit diagram, we can discuss the operation of the circuit. The microphone preamplifier is implemented with a two stage DC coupled pair. DC feedback from the emitter of the second transistor is used to bias the input transistor, while the gain is set by the ratio of the 100k feedback resistor and the effective AC impedance in the emitter of the input transistor.

The collector load of the input transistor is decoupled by a 22 μ F bypass capacitor, while a 1k/47pF low-pass filter is used at the input to eliminate possible RF interference.



For use with high impedance microphones, the marked components are deleted. This gives a nominal gain of 56. For use with low impedance microphones, higher gain is required, and this is achieved by reducing the AC feedback with the marked components. This gives a nominal gain of 250.


The transistors we have specified have the required gain and noise performance to achieve very close to the nominal gains. Only electrically equivalent types such as BC109s, should be used as substitutes.

A shorting type of input connector has been used for the microphone connector, in order to minimise the input

noise when no microphone is connected. We used one of the 3.5mm dia. jack sockets, as this suits the majority of currently available microphones supplied with movie cameras, projectors and cassette recorders.

The microphone preamplifier is intended to work with dynamic microphones of either the low or high impedance type, as were commonly supplied with the cheaper cassette recorders before the introduction of electret microphones. It will also work well with separate electret microphones having an output impedance of around 2k ohms.

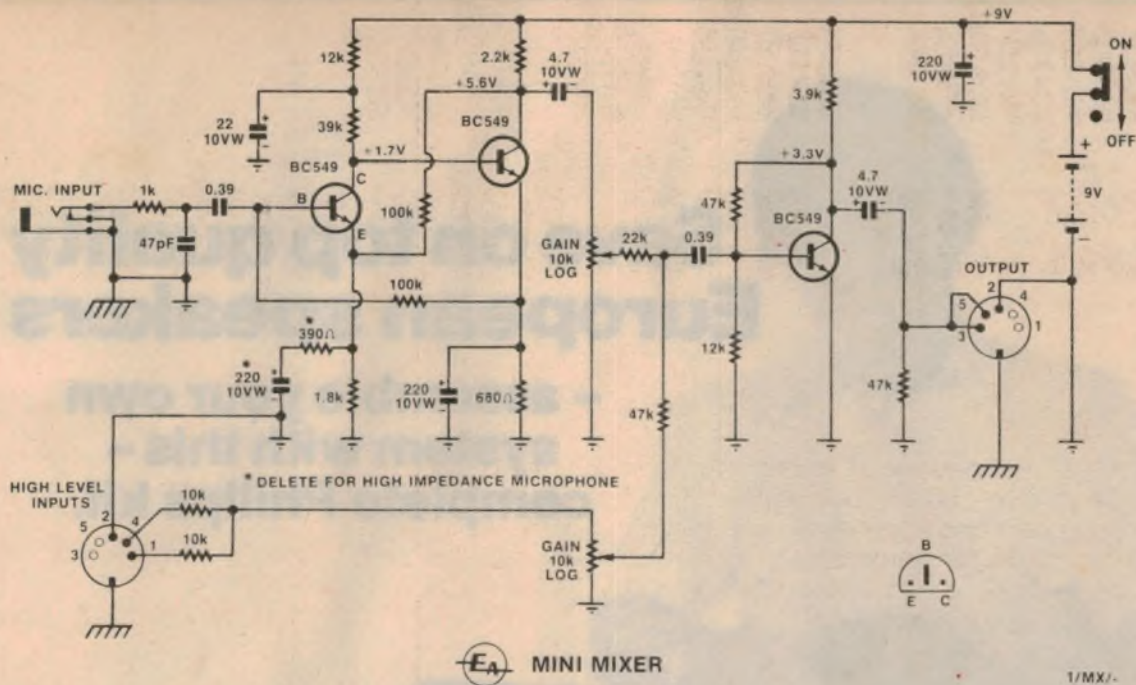No amplification is provided for the high level inputs. Provision is made for



Our circuit is suitable for both high impedance and low impedance microphones.

stereo inputs, which are mixed together passively by 10k mixing resistors. The high level inputs are connected to the circuit via a 5 pin DIN socket, wired so that the mixer unit will be electrically equivalent to a tape recorder, so that it may be connected to an amplifier via a standard DIN cord.

Two 10k logarithmic potentiometers are used to control the levels of the two inputs. The outputs from these controls are mixed in a simple virtual earth mixer. The gain of each channel can be varied by changing the input resistor. We do not recommend that the 22k resistor used for the microphone channel be changed, although in some cases it may be advantageous to lower the 47k high level resistor to 22k in order to increase the gain in this channel.

For the prototype, we provided a separate DIN socket for the output, as this suited the purposes we had in mind. However, for use with hi-fi amplifiers the output could be connected to pins 3 and 5 of the input socket, so that only one cord would be required to connect to the amplifier.

Connection to the amplifier would then be via the tape recorder sockets, and the mixer unit would be switched into circuit using the tape monitor switch.

A miniature slide switch was used for the power switch, with a 220uF electrolytic capacitor in parallel with the battery to ensure a low supply impedance. The DC voltages noted on the circuit were measured with a high impedance voltmeter, with a supply voltage of 9V. They should be taken as representative values only.

A battery voltage of 7V was taken as

the design point for the DC bias calculations, so that reasonable performance would be obtained over a wide range of battery voltages. Testing of the prototype confirmed that performance was essentially constant from 6 to 9V.

Construction of the unit should be very simple, as all components are contained on a single printed circuit board, coded 77mx11. This measures 96 x 87mm, and is supported in the case by the connections to the pots and the on/off switch.

Commence construction by fitting the input and output connectors, and

the controls to the box. Use the PCB as a guide to position the latter components, remembering to leave a clearance at the top of the box for the connectors. Fit the controls to the box, and then solder short lengths of tinned copper wire to their connecting lugs, and put the assembly aside for the moment.

Now fit all the components to the PCB. Ensure that the polarity conscious components, such as capacitors and transistors are fitted correctly. Use PCB pins to make the connections to the board for the battery lead and the input

SPECIFICATIONS

POWER REQUIREMENTS

9V at 3mA (Eveready No. 216 or similar battery)

Estimated battery life: in excess of 150 hours

OUTPUT CHARACTERISTICS

Nominal output voltage: 100mV RMS

Maximum output voltage: 2V RMS
Frequency response: 20Hz to 200kHz at -1dB points

Nominal output load: 10k ohms or greater

LOW IMPEDANCE MICROPHONE INPUT

Input impedance: 100k ohms
Sensitivity: 0.2mV for nominal output

Input overload: 6mV at 1kHz
Signal to noise ratio: -36dB below

nominal output and with S/C input
Distortion: masked by residual noise but less than 0.4% at 1kHz

ALTERNATIVE HIGH IMPEDANCE MICROPHONE INPUT

Input impedance: 100k ohms
Sensitivity: 1mV for nominal output
Input overload: 40mV at 1kHz
Signal to noise ratio: -40dB below nominal output and with S/C input
Distortion: masked by residual noise but less than 0.1% at 1kHz

HIGH LEVEL INPUT

Input impedance: 15k ohms
Sensitivity: 250mV for rated output
Input overload: 5V at 1kHz
Signal to noise ratio: -45dB below nominal output and with S/C input
Distortion: less than 0.04% at 1kHz




Save on top quality European speakers

- assemble your own system with this - complete Philips kit.

All you need is a couple of hours, a pair of scissors and a screwdriver.



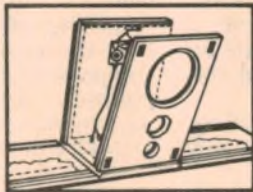
1 Screw the crossover networks to the baffle boards.



2 Apply glue to the case and fit baffle boards in grooves.



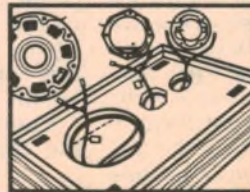3 Wrap sides of case around baffle board.



4 Insert speakers in holes and screw into position.



5 Clip fascia panel in place.



By assembling these Philips speaker kits yourself you can either save yourself a packet on what you were expecting to pay - or achieve a much higher quality system for the same money.

No need to make excuses about not being an electrician. These kits are complete. All components are genuine Philips units. Every part is ready to install. Every step is covered in simple illustrated stages. It's as easy as assembling a simple model kit from a hobby shop.

Now simply connect up to your amplifier and turntable and you're in business. For information about your nearest dealer contact your state office or send in this coupon.

**Sydney 42 1261, 42 0361, Melbourne 699 0300
Brisbane 44 2471, Adelaide 223 4022
Perth 654 199**

**Philips
Electronic Components and Materials,
P.O. Box 50, Lane Cove, N.S.W. 2066.**
Please send me details on your High Fidelity Loudspeaker kits.

Name _____

Address _____

Postcode _____




**Electronic
Components
and Materials**


PHILIPS

153.0193

Mixer for pick-up and microphone

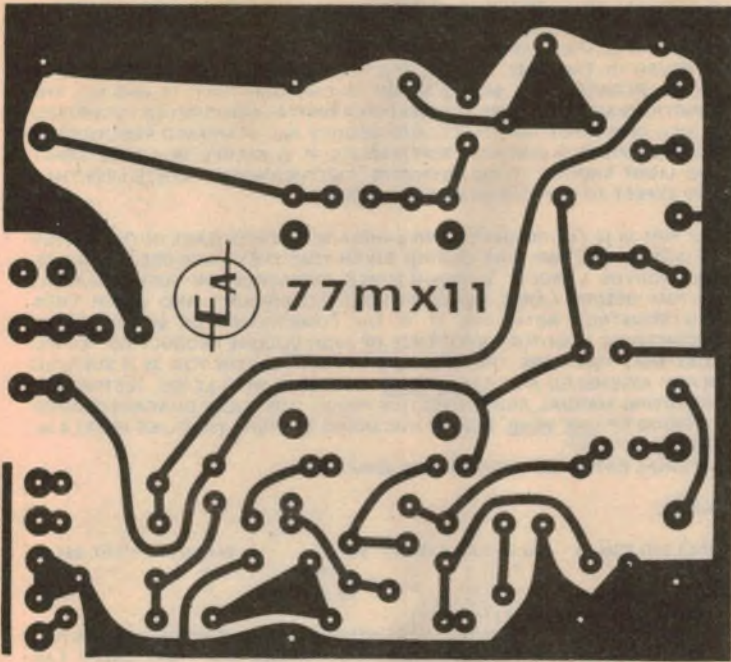

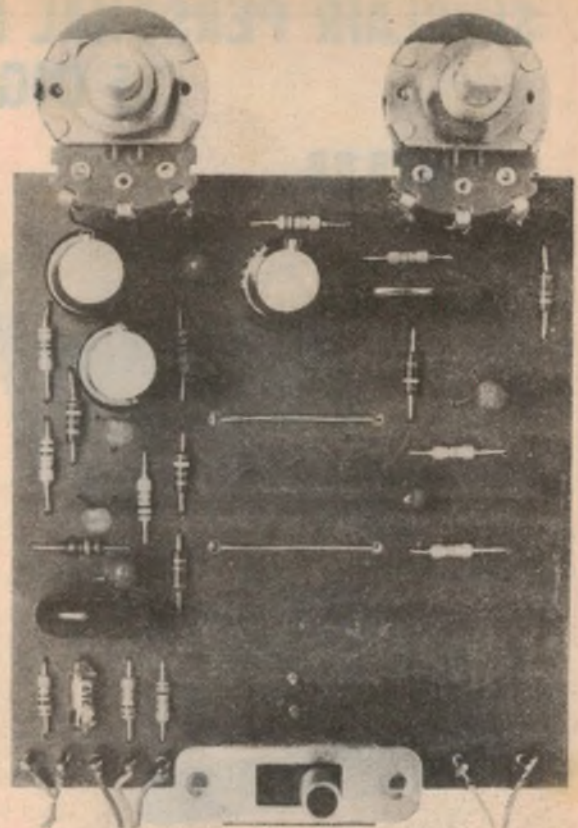Actual size reproduction of the PCB pattern.



Top: the assembled board. Below: the component overlay.

PARTS LIST

- 3 BC549 or equivalent low noise/high gain NPN silicon transistors
- 1 printed circuit board, coded 77mx11, 96 x 87mm
- 1 metal case, 150 x 100 x 60mm, see text

- 2 10k logarithmic potentiometers
- 2 knobs to suit
- 1 miniature slide switch
- 2 5-pin 180 degree DIN sockets
- 1 miniature earphone socket
- 1 216 type 9V battery and clip to suit

CAPACITORS

- 3 220uF 10VW electrolytics
- 1 22uF 10VW electrolytic
- 2 4.7uF 10VW electrolytics

- 2 0.39uF polyester
- 1 47pF ceramic or polystyrene


RESISTORS (all 1/4W)

- 2 100k, 3 47k, 1 39k, 1 22k, 2 12k, 2 10k, 1 3.9k, 1 2.2k, 1 1.8k, 1 1k, 1 680 ohm, 1 390 ohm

MISCELLANEOUS

Solder, tinned copper wire, hookup wire, machine screws and nuts, cardboard or insulating tape.

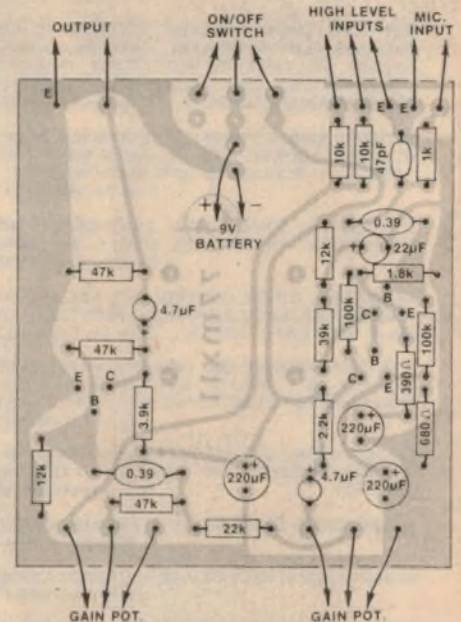NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Components with higher ratings may generally be used provided they are physically compatible.



and output connections.

The battery is mounted on the copper side of the board, but remember to insulate the tracks underneath it with a piece of cardboard or insulating tape. Fix the battery to the board using string or tinned copper wire, using the four holes provided. At this stage, do not connect the battery clip to the battery.

Ordinary hookup wire can be used for the input and output connectors, provided the leads are kept short, and the input and output leads separated.

This is facilitated by the pattern on the board. Once all these leads have been fitted, offer the PCB up to the controls, feeding the tinned copper wire through the appropriate holes.

After checking that the board is positioned correctly, solder all the connections, and clip off the excess wire lengths. If at a later stage it is required to obtain access to the top of the board, this can be achieved by removing the controls from the top of the case.

Testing of the unit consists of trying it out, giving all controls, inputs and

switches a quick operational test. If the unit fails to operate correctly, check the DC voltages marked on the circuit diagram, and try to isolate the faulty section. Then check for incorrectly soldered joints, wrong components, or faulty components.

In conclusion, the only point to watch is that you remember to turn the unit off when it is not in use, in order to prolong the battery life. Provided you keep this in mind, you should be able to look forward to many hours of happy mixing.

SINCLAIR PERSONAL DIGITAL MULTIMETER PDM 35

3.5 DIGIT RESOLUTION

\$60.00



NOW ANYONE CAN AFFORD A DIGITAL MULTIMETER. THOSE WHO MAKE ELECTRICAL MEASUREMENTS KNOW THE ADVANTAGES OF USING A DIGITAL METER: QUICK, CLEAR READINGS, HIGH ACCURACY AND RESOLUTION, HIGH INPUT IMPEDANCE AND FREEDOM FROM PARALLEX READING ERRORS. HOWEVER IN THE PAST, DIGITAL MULTIMETERS WERE COSTLY, BULKY AND MAINS OPERATED. THE SINCLAIR PDM 35 CHANGES THAT. IT HAS ALL THE FUNCTIONS AND FEATURES YOU NEED IN A DIGITAL MULTIMETER, STANDARD 10 MEG OHM INPUT IMPEDANCE AND BESIDES ALL STANDARD FUNCTIONS IT ALSO PROVIDES 5 JUNCTION TEST RANGES. IT IS PACKED IN A CASE SMALL AND LIGHT ENOUGH TO GO ANYWHERE. FURTHERMORE IT COSTS LESS THAN YOU EXPECT TO PAY FOR AN ANALOGUE METER.

THE PDM 35 IS THE RESULT OF SINCLAIR'S 6 YEAR EXPERIENCE IN THE DESIGN OF DIGITAL MULTIMETERS, DURING WHICH TIME THEY HAVE BECOME ONE OF THE WORLD'S LARGEST MANUFACTURERS PIONEERING IN SUCH AREAS AS CUSTOM DESIGN, LARGE SCALE INTEGRATED CIRCUITS AND LASER TRIMMED RESISTOR NETWORKS. IT IS THE COMBINATION OF SOPHISTICATED ENGINEERING WITH THE EXPERIENCE OF HIGH VOLUME PRODUCTION TECHNIQUES THAT HAS MADE THIS PRICEBREAK POSSIBLE. THE PDM 35 IS SUPPLIED READY ASSEMBLED AND CALIBRATED, COMPLETE WITH LEADS, TEST PROBES, OPERATING MANUAL AND PROTECTIVE POUCH. IT IS FULLY GUARANTEED FOR A PERIOD OF ONE YEAR. WEIGHT INCLUDING BATTERY (SUPPLIED FREE) 8 oz. SIZE: 6" x 3" x 1 1/2"
OPTIONAL EXTRA: AC ADAPTOR AND 30KV PROBE.

PRICES:

SINCLAIR PDM 35	SALES TAX EXEMPT	\$60.00	SALES TAX PAID	\$66.00
AC ADAPTOR	" "	9.00	" "	9.60
30 KV PROBE	" "	39.50	" "	44.60

Post, pack & insurance \$2.50 per order.

10% DISCOUNT FOR 10 OR MORE UNITS. STUDENTS WHO REQUIRE A METER FOR THEIR STUDIES CAN PURCHASE THIS UNIT SALES TAX FREE. SALES TAX EXEMPTION CERTIFICATE IS AVAILABLE FROM W.H.K.

GZF 1201 CMOS 4-DECADE COUNTER IC CONTAINS 4-RESETTABLE DECADES PLUS OVERFLOW, LATCHES, CARRY OUTPUTS FROM EACH DECADE, MULTIPLEXED BCD OUTPUT, 15 MICRO AMP STATIC CURRENT CONSUMPTION, CAN BE CASCADED, OPERATES FROM 5 TO 10 VOLTS, TTL COMPATIBLE OUTPUTS. Sales Tax exempt \$10.95 Sales Tax paid \$12.60

INTERSIL 8038CC FUNCTION GENERATOR /VCO, PRODUCES SIMULTANEOUS SINE, SQUARE AND TRIANGLE WAVE OUTPUTS FROM 0.001Hz TO 1 MHz. WITH 20 PAGES OF APPLICATION NOTES. Sales Tax exempt \$5.50 Sales Tax paid \$6.33

S187 DIGITAL FREQUENCY SYNTHESIZER WITH MORE THAN 500,000 SELECTABLE FREQUENCIES, SINGLE 10V SUPPLY, WITH DATA SHEETS. Sales Tax exempt \$18.50 Sales Tax paid \$21.28

4-CHANNEL TOUCH CONTROL IC's SAS 5605 for 1st 4-CHANNELS AND SAS5705 FOR EACH 4-CHANNEL ADDITION OUTPUT CURRENT UP TO 25mA. WITH DATA SHEETS. Sales Tax Exempt \$3.80 ea Sales Tax paid \$4.85

UAA170 ANALOGUE LED DRIVER (DRIVES 16 LED'S) CAN BE CASCADED WITH UP TO 7 UAA170 WITH DATA SHEETS AND VARIOUS CIRCUIT DIAGRAMS FOR ELECTRONIC THERMOMETER ETC. Sales Tax exempt \$2.78 Sales Tax paid \$3.20

SAJ205 STAIRCASE VOLTAGE GENERATOR & SAJ410 7-STAGE FREQUENCY DIVIDER FOR ELECTRONIC ORGANS, WITH DATA SHEETS BOTH IC'S Sales Tax exempt \$9.22 Sales Tax paid \$10.60

TCA955 SPEED CONTROLLER IC incl. APPLICATION NOTES Sales Tax exempt \$2.43 Sales Tax paid \$2.80

SBV566 HALL EFFECT DEVICE incl. APPLICATION NOTES Sales Tax exempt \$3.04 Sales Tax paid \$3.50

FP30L 100E MAGNETO RESISTOR incl. APPLICATION NOTES Sales Tax exempt \$2.43 Sales Tax paid \$2.80

SAS201 MAGNETICALLY CONTROLLED SWITCH (4-pin IC) incl. APPLICATION NOTES Sales Tax exempt \$3.04 Sales Tax paid \$3.50

INTERSIL ICM7045 STOPWATCH IC AS USED IN CRONUS 2 STOPWATCHES, TIMES FROM 0.01 SEC TO 24 HOURS, FUNCTIONS: STANDARD START/STOP, TAYLOR, SEQUENTIAL, SPLIT and EVENT TIME OUT, ONLY CRYSTAL, TRIMMER, DISPLAY AND SWITCHES ARE REQUIRED. ICM 7045, CRYSTAL, TRIMMER & APPLICATION NOTES TO CLEAR Sales Tax exempt \$29.57 Sales Tax paid \$34.00

INTERSIL ICM7205 STOPWATCH IC, FUNCTIONS: STANDARD SPLIT, CUMULATIVE TAYLOR/SEQUENTIAL, TIMES FROM 0.01SEC TO 1 HOUR, AS USED IN CRONUS 1 STOPWATCH. ICM7205 IC, CRYSTAL, TRIMMER & APPLICATION NOTES TO CLEAR Sales Tax exempt \$25.22 Sales Tax paid \$29.00

HIGH BRIGHTNESS LED DISPLAYS TO SUIT, 8 REQUIRED FOR ICM7045 AND 6 REQUIRED FOR THE ICM7205, EA. Sales T. ex \$1.00, S.T. paid \$1.15

INFRA-RED KIT CONSISTING OF 6 INFRA-RED LED'S, INFRA-RED RECEIVER plus 23 PAGES OF APPLICATION NOTES AND VARIOUS CIRCUITS FOR AM AND FM SOUND

Sales Tax exempt \$9.50 Sales Tax paid \$11.00

LD 470 GREEN, LD480 YELLOW LED ARRAY (10 LED'S)

Sales Tax exempt 2.43 Sales Tax paid \$2.80

LD 460 RED LED ARRAY (10 LED'S)

Sales Tax exempt \$1.83 Sales Tax paid \$2.10

FIBER OPTICS, LIGHT IS TRANSMITTED (MODULATED WITH SOUND IF YOU WISH) THROUGH PLASTIC FIBER WITH APPLICATION NOTES 10 ft. 0.040"

Sales Tax exempt \$2.00 Sales Tax paid \$2.30

5ft. 0.060"

Sales Tax exempt \$2.00 Sales Tax paid \$2.30

FIBER OPTIC KIT GB-1 contains several hundred feet of Fibers with notes

Sales Tax exempt \$3.47 Sales Tax paid \$4.00

SILICON NPN PHOTO DARLINGTON TRANSISTOR IDEAL FOR FIBER OPTIC EXPERIMENTS 25V, 250mA max. Sales T. ex \$1.48 Sales T. paid 1.70

BAG of 10 LED'S MIXED WITH DATA SHEET

Sales Tax exempt \$1.57 Sales Tax paid \$1.80

TV CHALLENGER 3000 TO CLEAR 4 GAME incl. AC ADAPTOR \$44.00

TV CHALLENGER 3000 WITH 6 GAMES incl. AC ADAPTOR \$49.50

ELECTRONIC RIFLE TO SUIT \$34.40 (suitable for all games based on the AY-3-8500 CHIP, SHOOTING DISTANCE UP TO 35 feet.

COMMODORE

SR-4148R 48 KEY, 14 DIGIT SCIENTIFIC NOTATION CALCULATOR WITH RECHARGEABLE NI CAD BATTERIES & CHARGER TO CLEAR Sales Tax exempt \$28.26 Sales Tax paid \$32.50

SR4190R 106 FUNCTION PRE-PROGRAMMED SCIENTIFIC CALCULATOR SEE E/A PAGE 104 SEPTEMBER 77 REVIEW FOR DETAILS. TO CLEAR Sales Tax exempt \$54.50 Sales Tax paid \$62.68

COMING SOON: COMMODORE COMPUTER SYSTEM PET 2001 WITH 4K BYTES OF RAM, 12K BYTES OF ROM CONTAINING BASIC AND OPERATING SYSTEM, VIDEO DISPLAY, 43 KEY KEYBOARD, CASSETTE MEMORY INPUT/OUTPUT VIA HEWLETT-PACKARD INTERFACE BUS ETC. AUSTRALIAN PRICE AROUND \$700.00

ONE USED ASR33 TELETYPE WITH STAND, PAPER PUNCH & READER IN VERY GOOD CONDITION PLUS MANUALS \$650.00 FREIGHT COLLECT

POST, PACK & INSURANCE ON ALL ITEMS \$3.50 EXCESS REFUNDED

W.H.K. ELECTRONIC & SCIENTIFIC INSTRUMENTATION
2 GUM ROAD, ST. ALBANS 3021 VIC
PHONE (03) 396 3742 TELEX AA33321

DO IT YOURSELF - LABELS, PC/BOARDS, TRANSFERS

THE EASY, LOW COST WAY TO MAKE YOUR OWN LABELS, PRINTED CIRCUIT BOARDS AND RUB-OFF TRANSFERS. ONE STEP FROM ART TO NEGATIVE - ONE STEP FROM NEGATIVE TO POSITIVE. NO DARKROOM IS REQUIRED. SHARP LINE DRAWINGS MAY BE REPRODUCED DIRECTLY FOR GOOD - LOOKING REVERSE BACKGROUND NAMEPLATES, AND THE SELF - ADHESIVE FEATURE PERMITS APPLICATION WITHOUT NUTS, BOLTS OR OTHER UNSIGHTLY FASTENERS.

NOW W.H.K. HAS A NEW TOOL FOR ENGINEERS, LAYOUT - ARTISTS, ARCHITECTS, DRAFTSMEN, ILLUSTRATORS AND MANY OTHERS, CALLED THE I.N.T. (IMAGE'N TRANSFER) MATERIAL.

TRANSFER MATERIAL ISN'T NEW. PRE - IMAGED SHEETS OF RUB - ON TRANSFER LETTERS, NUMBERS, AND SYMBOLS HAVE BEEN "WORK - A - DAY TOOLS" FOR YEARS. NOW MAKE YOUR OWN TRANSFER SHEETS THAT STAY ON AND WILL NOT CHIP, FLAKE, CRACK OR PEEL UNDER MOST CONDITIONS. ONCE APPLIED, IMAGES ARE HIGHLY RESISTANT TO ABRASION. MAKE YOUR OWN PC BOARD SYMBOLS, DISPLAY/SIGNS, WORDS, LETTERS IN ANY STYLE AND SIZE. MAKE AS MANY SHEETS AS NEEDED WHEN YOU NEED THEM. ONLY ONE CHEMICAL IS REQUIRED. I.N.T. MAINTAINS PHOTOGRAPHIC CLARITY. LINE ART, 85 LINE HALFTONES, AND TYPOGRAPHY CAN BE TRANSFERRED AND USED AS CAMERA-READY ART.



CENTURION MARK III TANK

guns and mounted on caterpillar tracks, capable of traversing rough terrain. Rare metallic element of vanadium group, a very

PHOTOCOPY OF ORIGINAL ON PLAIN PAPER




CENTURION MARK III TANK

guns and mounted on caterpillar tracks, capable of traversing rough terrain. Rare metallic element of vanadium group, a very

NEGATIVE MASTER ON REVERSING FILM




POSITIVE GREEN LABEL

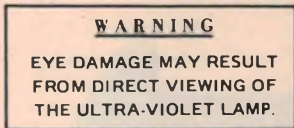

ORIGINAL TYPED ON PLAIN PAPER



NEGATIVE MASTER ON REVERSING FILM

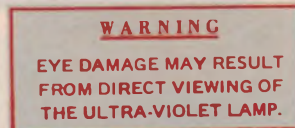


POSITIVE ON RED ALUMINUM LABEL




RED PLASTIC LABEL




VIDEO GAME LABEL ON BLACK ALUMINUM LABEL

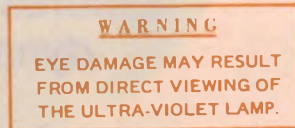

POSITIVE MASTER ON REVERSING FILM

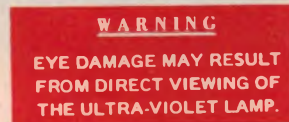

NEGATIVE RED PLASTIC LABEL

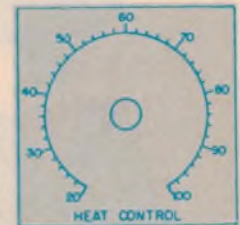

DIAL FACE ON BLUE ALUMINUM LABEL



IMAGE TRANSFER MATERIAL




POSITIVE & NEGATIVE ON BLUE PLASTIC LABEL




YELLOW PLASTIC LABEL



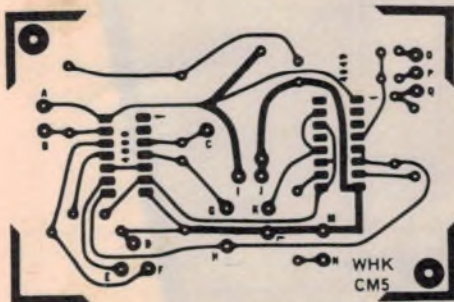POSITIVE & NEGATIVE ON GREEN PLASTIC LABEL



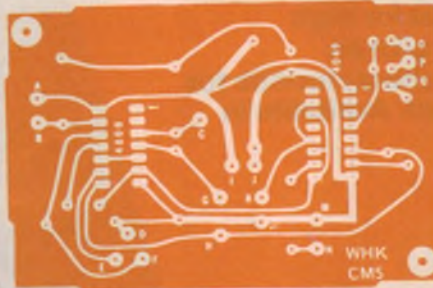PC BOARD ARTWORK ON PLAIN PAPER (PENCIL OR INK IS SUITABLE)



NEGATIVE MASTER ON REVERSING FILM




DEVELOPED PC BOARD - READY TO ETCH


AVAILABLE FROM W.H.K.: SELF-ADHESIVE METAL & PLASTIC LABEL MATERIAL IN THE FOLLOWING: BLUE ON WHITE PLASTIC, GREEN ON WHITE PLASTIC, RED ON WHITE PLASTIC, BLACK ON TRANSPARENT PLASTIC, BLACK ON YELLOW PLASTIC, BLACK ON WHITE PLASTIC, BLUE ON ALUMINUM, RED ON ALUMINUM, BLACK ON ALUMINUM, REVERSING FILM. SIZES UP TO 24" x 48". IMAGE TRANSFER MATERIAL, DEVELOPER, CLEAR COATINGS, GREY SCALES, PRE-SENSITISED SINGLE & DOUBLE SIDED PC BOARDS, VARIOUS UV LIGHT SOURCES, INCLUDING A FULLY AUTOMATIC LAMP, EXPOSURE TIMERS, ETCHANTS, ETCHANT TANKS WITH AGITATION AND HEATER, RESIST STRIPPER, ELECTROLESS GOLD & TIN PLATING SOLUTIONS ETC.

NOTE: W.H.K. CAN MANUFACTURE SELF-ADHESIVE LABELS, AND TRANSFERS FROM YOUR HANDWRITTEN TEXT (WE HAVE AN IBM ELECTRONIC COMPOSER FOR TYPESETTING). ALSO AVAILABLE FINISHED P/C BOARDS FROM YOUR ARTWORK. WRITE FOR OUR FREE 16 PAGE CATALOGUE ON PHOTO-SENSITISED PRODUCTS. PLEASE INCLUDE \$0.40 TO COVER POSTAGE.

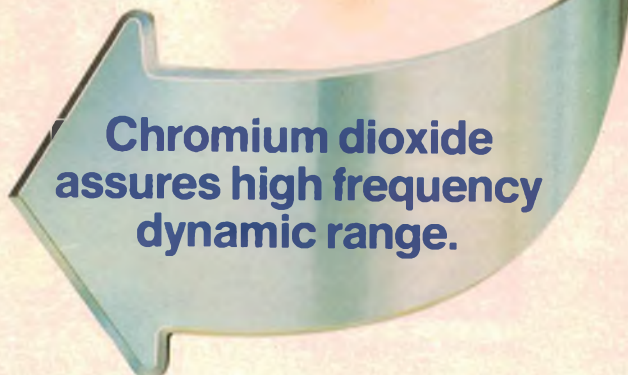W.H.K. ELECTRONIC & SCIENTIFIC INSTRUMENTATION
2 GUM ROAD, ST. ALBANS 3021, Vic.
PHONE (03) 396 3742 TELEX AA33321



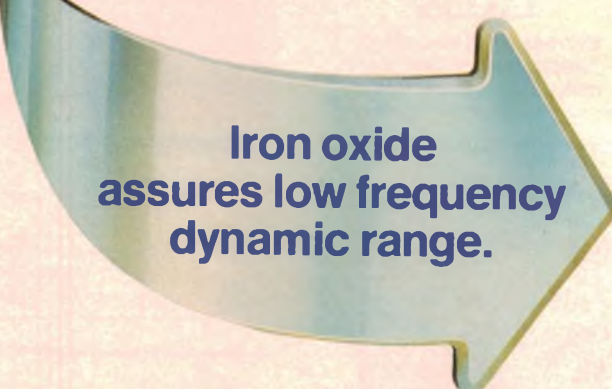**Chromium dioxide
assures high frequency
dynamic range.**



**Iron oxide
assures low frequency
dynamic range.**

AGFA CARAT


The superb dual layer tape.

Truly a technical triumph—Agfa CARAT combines two magnetic layers in one tape. The lower layer is highly sensitive iron oxide that is specially designed for low frequencies. Above is a layer of chromium dioxide whose optimum output level is ideal for high frequencies. Together they give an extraordinarily high replay characteristic for high quality audio equipment. Available in C48, C60 and C90.



°Registered trademark of Agfa-Gevaert
Antwerp/Leverkusen.

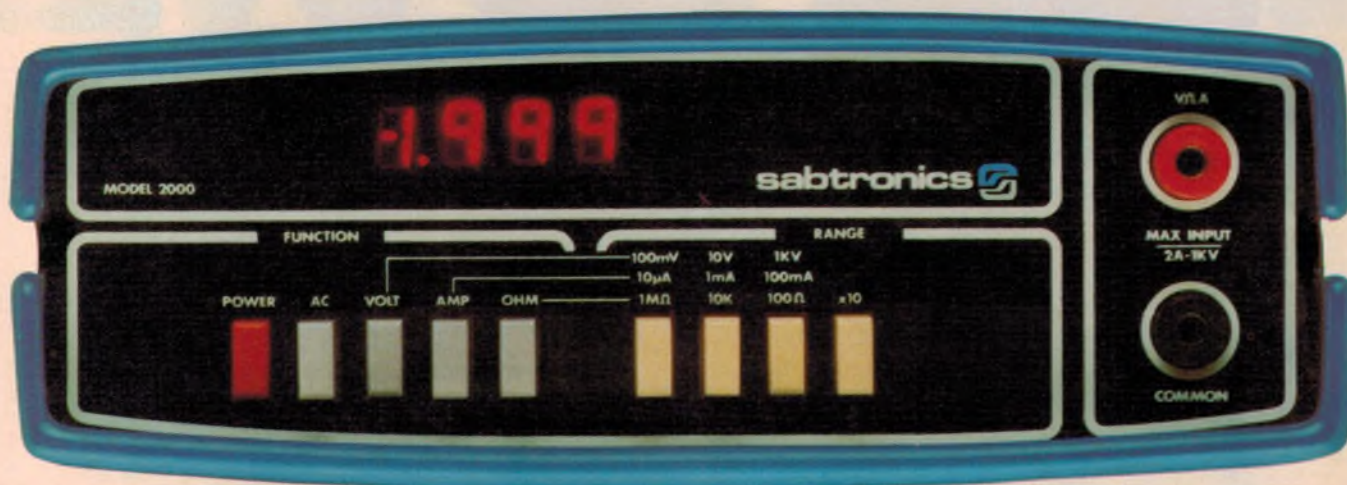Chances are, someone you know just bought a professional 3½ digit DMM kit for less than \$70.



Thousands of people have already bought the Sabtronics Model 2000 for two main reasons. First, its incredible accuracy, range and professional features. And second, the incredibly low price of \$69.95.

People everywhere appreciate this bench/portable multi-meter. They depend on its basic DCV accuracy of 0.1% ± 1 digit, its readings to ±1999 and its five functions giving 28 ranges, overload protection and 100% overrange.

The 2000 is automatically appealing to hobbyist and professional alike. With automatic overrange indication, automatic polarity, even automatic zeroing.

Best of all, it's easy to assemble. All the parts you'll need, including the high-impact case, come right along with the clear, step-by-step instructions.

The result is a professional quality 3½ digit DMM that you could have paid a lot more than \$69.95 for, possibly receiving a lot less. But this one's from Sabtronics, specialists in digital technology.

Maybe you should order yours before you turn the page.



Made in U.S.A.

sabtronics

INTERNATIONAL

P.O. Box 64683 Dallas, Texas 75206 (214) 369-7310

SPECIFICATIONS:

DC volts in 5 ranges: 100µV to 1000V
 AC volts in 5 ranges: 100µV to 1000V
 DC current in 6 ranges: 10nA to 2A
 AC current in 6 ranges: 10nA to 2A
 Resistance in 6 ranges: 1Ω to 20MΩ
 Input Impedance: 10MΩ
 Display: 9mm (36") LED
 Power requirements: 4.5 VDC to 6.5 VDC
 (4 "C" cells - not included)
 Size: 8"W x 6.5"D x 3.0"H
 (203W x 165D x 76H mm)

ORDERING INFORMATION

The prices as listed are in Australian dollars and do not include any tax or duty which may be levied upon receipt of the goods. Please send remittance in the form of a Bank Draft for an equivalent amount in U.S. dollars. If an International Postal Money Order is used, include original receipt with order to insure prompt shipment.

**TO: Sabtronics International,
 P.O. Box 64683, Dallas, TX 75206, U.S.A.**

Please send via insured airmail:—

_____ (qty) Model 2000 DMM kit(s)

@ A \$69.95 each _____ subtotal

Insurance, postage and handling:

A\$9.00 per unit _____ subtotal

Amount enclosed A\$ _____ *TOTAL

Please print or typewrite

Name _____

Address _____

City _____

*I have enclosed the U.S. dollar equivalent of the A\$ total.

Hear no evil

Today's standards in hi fi insist on components with the highest standards of performance. JVC's speaker range is not only designed to give you this faultless reproduction, but is designed to be extremely durable as well. Years of research have ensured that all JVC speakers — whether they be omni-directional, bass reflex — together with the different types of speaker used,

meet the most discriminating needs. The special materials selected in the construction of the domes, for instance, is the very finest available, and no expense has been spared at any stage of manufacture. Extensive research into sound and sound projection has also proved itself worldwide — in competition with many other brands of less critical construction. JVC — you can hear clearly now.



SK44

SK55

SK33



the right choice

For details on all JVC Hi Fi Equipment, write to: JVC Advisory Service, P.O. Box 49, Kensington, N.S.W. 2033.



ELECTRONICS TRAINING IN TODAY'S AIR FORCE.



If you're aged between 17 and 34 and you're into radio equipment, navigation aids, computers, radar and advanced telecommunications equipment, the Air Force can train you as a radio technician.

You'll work with people your own age on good pay — \$9,936 per year on completion of training. You'll have the chance to travel, and a secure future.

And, when in due course you leave the Air Force, there are tremendous opportunities in civilian life. Training is free, so is medical, dental and optical care, and you'll be eligible for a low interest housing loan, after 3 years.

So if you're between 17 and 34 on entry, an Australian citizen, and meet our nationality requirements and have good results in English, Maths and Science, give the Air Force a call.

Your future's in your hands.

Brisbane: 226 2626, Townsville: 71 3191,
 Sydney: 212 1011, Newcastle: 2 5476,
 Wollongong: 28 6492, Wagga: 21 1100,
 Canberra: 47 6530, Melbourne: 61 3731,
 Hobart: 34 7077, Adelaide: 223 2891,
 Perth: 22 4355.

To RAAF Careers Officer, GPO Box XYZ (Insert your nearest Capital City and Postcode) Please send me full details about electronics training in today's Air Force.

Name _____

Address _____

Date of Birth _____

State _____ Postcode _____

**YOUR FUTURE'S
 IN TODAY'S AIR FORCE.**

RG55.FP57

Auth by Director-General Recruiting, Dept Defence

SSB/AM

POWER SUPPLY

**HUGE
4AMP
PEAK**



FULLY
APPROVED BY
THE
ELECTRICITY
AUTHORITY.

- * Sufficient peak current rating for ALL rigs — including SSB models!
- * High 13.8Volt output — not just 12.6Volts
- * Gives higher transmit power.
- * Has power switch on front panel.
- * Output connectors are out of sight on rear.
- * Fully fuse protected for safety. You know if something goes wrong!
- * Finished in the latest 'black is beautiful' style.
- * Service guaranteed — Designed for Australia!!!

LOOK ~
SWITCH ON FRONT PANEL

**WHY PAY \$49.50
OURS IS ONLY
\$39.50**

Don't get caught with a CB power supply that isn't up to the job! Most supplies are rated at between 1 and 2 Amps. Fine — but what they don't tell you is their peak rating. A CB supply has to be able to handle high peak currents — especially for SSB. This supply has a huge 4A peak reserve — more than enough! And watch out too for supplies with electronic protection. For CB use, the best protection is the good, old fashioned fuse! If something goes wrong, you know about it — and the supply can't re-set itself to do more damage! The third point to watch out for is the price. We've seen supplies around for \$45 — \$49 — \$55 and more. And they have no more to offer than this one. In fact, many offer less! Look at our price again. Just \$39.50. It's almost the price of a kit you make up yourself — but it's complete and ready to go. Just plug it in!
THE SOUTHERN STAR CB POWER SUPPLY FROM DICK SMITH — perfect for your CB radio!

Cat M-9545

DICK SMITH ELECTRONICS GROUP

SYDNEY - 125 York St. Ph: 29 1126.
GORE HILL - 162 Pacific Hwy. Ph: 439 5311.
BANKSTOWN - 361 Hume Hwy. Ph: 709 6600.
PARRAMATTA - 30 Grose St. Ph: 683 1133.
MELBOURNE - 656 Bridge Rd. Richmond. Ph: 42 1614.
399 Lonsdale St., City. Ph 67 9834
BRISBANE - 166 Logan Rd. Buranda. Ph: 391 6233.

THE AUSTRALIAN COMPANY.

Mail Orders: Box 747, Crows Nest. NSW.
Postage and packing is extra!
We have a network of dealers across Australia.



The Australian CB SCENE

AN AM CB TRANSCEIVER FROM SHARP AUSTRALIA

Compact, neat and modern in design, the CB-800A is the Sharp Corporation's answer for the CBer who wants an AM transceiver which will fit neatly into the family car.

Most obvious feature of the CB-800A is the uncalibrated channel selector knob and the LED readout in the window alongside, which indicates clearly the channel to which the transceiver is tuned. Rotating the knob brings the numbers up, in turn, with two points of note: on the emergency frequency (USA channel 9) the digit flashes to warn the user that there is something special about that setting; secondly, when the public address function is invoked, any digit being displayed in the window is replaced by the letters "PA".

Also visible through the window is a signal and RF power meter but, unlike the LED readout, it is really too small to be of much use to a mobile operator.

There is a volume control knob, with a supplementary "power off" function, and a squelch control.

An ANL switch invokes the automatic noise limiter function, while a "Delta" switch shifts the receiver tuning from channel centre frequency to plus or minus 1kHz. The microphone plugs



into the front panel, while antenna, power, PA and extension speaker connections are at the rear.

The receiver is a dual conversion superhet, employing 3 crystals and a phase locked loop to ensure frequency stability, with intermediate frequencies at 11.275MHz and 455 kHz. Selectivity is quoted as 6dB down at ± 3 kHz, and 50dB down at ± 10 kHz. Power output is rated at 3W and input sensitivity 0.7 μ V for 10dB signal/noise ratio, with 30% modulation at 1000Hz.

The transmitter also uses a phase locked loop for frequency control and includes modulation limiter circuitry to

ensure maximum "talk power". Input is set nominally for 5W, harmonic suppression is 50dB, and output is coupled to antenna at the usual 50 ohms impedance.

On test, the receiver sensitivity was never in doubt, with the receiver's own limits far below the natural noise and interference ambient on any CB channel. The ANL switch tended merely to soften the noise spikes under these congested conditions, and the Delta switch had only a minor effect. Both controls would probably come into their own, however, for out-of-town use.

The squelch operated smoothly and effectively with the possible difference that it was less abrupt than usual, tending to act more as a severe mute for signals just below the threshold.

If we had any criticism at all, it would be that the channel change, while mechanically very smooth, did produce some noise output from the speaker; a minor point, however.

Tested into a dummy load, the transmitter produced very close to 4W RF output with about 13.6V applied and monitoring under these conditions indicated, full, clean modulation. If the unit appeals, its performance in practice should be right up to expectations for an AM CB transceiver.

Recommended retail price for the CB-800A is \$149.95. For further details: Sharp Corporation of Australia Pty Ltd, 64-80 Seville St, Fairfield, NSW or P.O. Box 233, Fairfield 2165; tel: (02) 728 9111. (W.N.W.)

Remember the "EVERSHARP" pencil?

There was a time when the trade name "Eversharp" was so familiar that people used it to refer to any propelling pencil. What few people know is that it dates back to 1915 and is the word from which the 65-year-old Sharp Corporation presently derives its name.

Since then, the Sharp Corporation has moved heavily into electronics and can claim a long list of industry "firsts":

- 1953 — Mass production of Japanese TV.
- 1962 — Mass production of microwave ovens.
- 1963 — Mass produced solar batteries.

1964 — Solid-state desk top calculator.

1965 — 19in. colour TV receiver.

1971 — "Compet" calculator passes the million mark; first IC colour TV marketed; Sharp Australia established.

1974 — Mini calculator with memory.

1976 — Ultra-thin (7mm) calculator.

The story does not end there and the company is still "looking sharp", with a super-slim (5mm) calculator, and no protruding keys, liquid crystal display and an audible input check.

And there's a line of cassette radios bristling with all modern facilities.

CB OPERATING CONVENTIONS

FREQUENCIES: Australian v. USA 23-channel

Aust. Ch.	Freq. (MHz)	USA Ch.	Aust. Ch.	Freq. (MHz)	USA Ch.
—	26.965	1	9	27.115	13
—	26.975	2	10	27.125	14
—	26.985	3	11	27.135	15
—	27.005	4	12	27.155	16
1	27.015	5	13	27.165	17
2	27.025	6	14	27.175	18
3	27.035	7	15	27.185	19
4	27.055	8	16	27.195	—
5	27.065	9	17	27.205	20
—	27.075	10	—	27.215	21
6	27.085	11	18	27.225	22
7	27.095	—	—	27.255	23
8	27.105	12			

FREQUENCIES: USA, Extension to 40 Channel

Channel	Freq. (MHz)	Channel	Freq. (MHz)	Channel	Freq. (MHz)
24	27.235	30	27.305	36	27.365
25	27.245	31	27.315	37	27.375
26	27.265	32	27.325	38	27.385
27	27.275	33	27.335	39	27.395
28	27.285	34	27.345	40	27.405
29	27.295	35	27.355		

THE "10" SIGNAL CODE

CODE MEANING

- 10-1 Receiving you poorly.
 10-2 Receiving you well.
 10-3 Channel in use.
 10-4 Message received.
 10-5 Relay message.
 10-6 Busy. Can't talk now.
 10-7 Out of service. Going off air.
 10-8 Back in service after shut-down.
 10-9 Repeat message.
 10-10 Was 10-6. Now on call.
 10-11 Talking too rapidly.
 10-12 Visitors are present.
 10-13 Advise weather, road conditions.
 10-14 Time by the clock.
 10-17 Important business.
 10-18 Anything for us?
 10-19 Return to base.
 10-20 My location is:
 10-21 Contact me by phone
 10-22 Make personal contact with:
 10-23 Stand by.
 10-24 Assignment completed.
 10-25 Contact another station by radio.
 10-26 Disregard last transmission.
 10-27 I am moving to channel.
 10-28 Proper station identification.
 10-29 Time is up for contact.
 10-30 Violates regulations.
 10-31 No longer in violation of regs.
 10-32 I will advise re signal readability.
 10-33 Emergency traffic at this station.
 10-34 In trouble; need help.
 10-35 Matter of urgency but cannot discuss it by radio.

- 10-36 Transmission or event is scheduled for:
 10-37 Send tow truck.
 10-38 Injuries; send ambulance.
 10-39 Your message was delivered.
 10-41 Moved to another channel.
 10-42 Traffic accident at:
 10-43 Traffic congestion at:
 10-44 I have a message for:
 10-45 Stations on this channel please identify.
 10-50 Break.
 10-62 Unable to copy; use phone.
 10-63 Net directed to:
 10-64 Net clear.
 10-70 Fire at:
 10-84 My telephone number is:
 10-85 My address is:
 10-89 Radio repairman needed at:
 10-92 Your xmitter needs adjusting.
 10-94 Please give me a long count.
 10-100 Rest stop.

PHONETIC ALPHABET

- | | |
|-----------|------------|
| A—ALFA | N—NOVEMBER |
| B—BRAVO | O—OSCAR |
| C—CHARLIE | P—PAPA |
| D—DELTA | Q—QUEBEC |
| E—ECHO | R—ROMEO |
| F—FOXTROT | S—SIERRA |
| G—GOLF | T—TANGO |
| H—HOTEL | U—UNIFORM |
| I—INDIA | V—VICTOR |
| J—JULIETT | W—WHISKEY |
| K—KILO | X—X-RAY |
| L—LIMA | Y—YANKEE |
| M—MIKE | Z—ZULU |

R-S SIGNAL REPORTS

READABILITY

- 1—Unreadable.
 2—Barely readable, occasional words distinguishable.
 3—Readable with difficulty.
 4—Readable with little difficulty.
 5—Perfectly readable.

SIGNAL STRENGTH

- 1—Faint signals barely perceptible.
 2—Very weak signals.
 3—Weak signals.
 4—Fair signals.
 5—Fairly good signals.
 6—Good signals.
 7—Moderately strong signals.
 8—Strong signals.
 9—Extremely strong signals.

THE "Q" CODE

The Q code was originally devised as a means of speeding up communication between operators using Morse Code. A Q-code letter group may serve as a statement or it may be posed as a question — in Morse Code simply by adding to it a question mark.

Q-code letter groups have tended to carry over to speech communication as jargon, needlessly displacing plain language words.

Listed below are the Q-code letter groups most likely to crop up as jargon in speech transmissions.

- QRM** Your transmission is being interfered with. Is my transmission . . . ?
QRN My reception is marred by static. Is your reception being marred . . . ?
QRO Please increase your power (if possible). Shall I increase power?
QRP Please reduce your power (if possible). Shall I reduce power?
QRT Stop sending (or transmitting). Shall I stop sending or transmitting?
QRV I am ready. Are you ready?
QRX I will call you again at . . . (time) on . . . (freq). Will you call me again . . . ?
QRZ You are being called by . . . on . . . (freq). Who is calling me?
QSL I will acknowledge receipt (by card, etc). Will you acknowledge receipt?
QSO I can communicate with . . . Can you communicate with . . . ?
QSP I will relay to . . . Will you relay to . . . ?
QSY I will change frequency to . . . Can you change frequency to . . . ?
QTH My location (more commonly home station address) is . . . What is yours . . . ?
QRT The time is . . . What is the correct time?

AMAZING CB SALE! AEGIS-MBL OFFER YOU THE BEST FOR LESS.

AEGIS-MBL offer you CB with 3 months warranty and service backup by fully qualified and experienced technicians to protect your investment.

We've been in the communications business for over thirty years. Let our specialists advise you on the right choice of rig and accessories.



Midland 13-892

World famous market leader SSB AM unit with RF gain control, dual detectors tone switch and clarifier which doubles as continuously variable delta tune. Was \$299.50.

Now only **\$249.00**

Midland 13-886 (below)

Dramatic modern styling combined with top class performance makes this the choice for an AM home base station. Wired for 240V, has inbuilt SWR meter. Use the handset for private conversation, switch to loudspeaker when required. Outstanding value at

\$189.50



Tram Diamond 40

Most advanced AM rig on market. 52 semi-conductor devices to reject noise and adjacent channel interference. Has mic. gain control, delta tune and inbuilt SWR meter. Was \$169.00.


Now only **\$139.00**



Johnson Viking 352D

The ultimate in high level AM/SSB performance. Crystal lattice filtering rejects adjacent channel interference and a fully automatic noise limiter assures clean, clear reception. Built in microphone compressor and full allowable power ensure strong, crisp transmissions. Originally selling at \$268.00.

Now only **\$229.00**

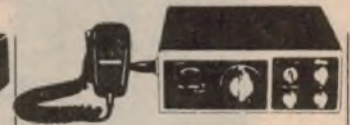

Hy-gain V

Review in June CB Australia magazine said "Outstanding in functional design and operation". SSB/AM with RF gain control, automatic noise limiter, noise blanker. Was \$279.50.

Now only **\$239.50**

Other models in stock

Including Bengal, Pace, Tasc, Finetone, Kraco, Unimetrics, Roberts, Xtal, Electrophone 18 Channel Write, phone or call for further details. Special discounts to clubs, social organisations, etc. Trade enquiries welcome.

Full range of accessories

includes mobile antennas, base antennas, SWR bridges, TVI filters, Co-Ax cable and fittings, PA speakers, Mic compressors, RF amplifiers.



AEGIS-MBL

347 Darebin Road, Thornbury, Vic. 3071
Telephone 49 1017 or 49 6792 Open 9-4 p.m. Saturdays



Please supply urgently (Brand name) _____ CB unit @ \$ _____

I enclose \$4.50 to cover packing and freight \$ _____

or Please forward freight payable by Comet. TOTAL \$ _____

I enclose cheque / money order to the value of \$ _____

Please charge my Bank Card. Number _____ Expiry Date _____

Name _____ Signature _____

Address _____

Postcode _____ 888 3904

When you're read Single Side Band-i



**ONLY
\$229.95**

**PLUS \$5.00
POST AND
HANDLING**

Why for the ultimate investment in CHIBA CB

THE DISCRIMINATING BUYER WILL ALWAYS LOOK FOR FIRST-CLASS, DEPENDABLE PERFORMANCE... THAT'S CHIBA

Why not move up to the ultimate — the Chiba 18 channel AM SSB unit offering many of the finest CB features in Australia today.

Designed for Australian conditions, the Chiba has 54 channels (18 channels AM and 18 each in Upper Side Band and Lower Side Band). In addition a full 12 watts PEP of SSB output power. Also 4 watts AM output power. Fits in a compact unit 203mm x 60mm x 232mm deep.

Large, clear, backlit dial shows exactly the channel you're tuned to. 18 upper or 18 lower SSB modes or 18 AM channels. Well designed, functional S RF meter shows the precise incoming signal strength together with the relative transmitting power available.

LOOK AT THESE GREAT FEATURES:

- **INTEGRATED CIRCUIT BALANCED MODULATOR:** Leaders in the SSB generation with this development
- **INTEGRATED CURRENT MIXER:** Gives stability and reliability with fewer parts
- **INTEGRATED CIRCUIT SPEECH PROCESSOR:** Plus ALC, gives you maximum speaking volume on AM or SSB
- **SEPARATE RF TRANSISTOR HEAT DISSIPATOR:** Ensures even better performance and reliability

- **NEW CLARIFIER CONTROL:** Enhances clarity of reception on every channel and simplifies speedy adjustment from one mode to another. Adjusts SSB receiver frequencies, converts to AM variable fine tuning
- **STRONG, MODERN, SOLID STATE CIRCUITRY:** Dependable chassis ensures reliable relay switching
- **DUAL CONVERSION RECEIVER:** 4 Ceramic filters for AM and one mechanical filter for SSB gives better SSB reception plus superior overall selectivity
- **SPECIAL PA AUDIO CIRCUIT:** This special integrated circuit PA Amplifier at the push of a button

PLUS ALL THESE IMPROVED FEATURES:

TX operating light, full size mike, bracket and 12 volt DC cord, automatic noise limiter with built-in amplified automatic gain control circuit reduce noise together, external speaker with PA speaker jacks.

Chiba Communications Industries, Inc. of Japan, employs over 1000 people. 1976 sales were in excess of US\$85 million. It's good to know that your purchase is backed by a highly responsible financially stable Company.

Chiba pioneered the PPL developments in CB and will continue through its innovative research and development to be a world leader in personal communications.



CHIBA

Another fine quality product marketed by
Chiba Communications (Aust) Pty Ltd.

HOW TO ORDER: Fill in BOTH sections of the coupon. In each section print your name and full postal address in BLOCK letters. Cut the entire coupon out around the dotted line. Send it with your money order or crossed cheque to this Magazine's Mail Order Department Offer No 162/77, PO Box 4000, GPO, Sydney 2001. Cheques should be endorsed on the back with the sender's name and address and made payable to this magazine. This offer is open to readers in Australia only. Please allow four weeks for delivery.

THIS MAGAZINE'S CHIBA CB RADIO
OFFER No. 162/77.

NAME

ADDRESS

STATE

POSTCODE

Please send me

(state quantity)

I enclose my cheque, postal/money order to the value of

\$

The Australian CB SCENE

What you've always wanted to know . . .

CBer's HANDY MANUAL. Published 1976 by Tab Books, Blue Ridge Summit, Pa, USA. Stiff paper covers, 48 pages 215mm x 139mm, mainly text. Price in Australia \$2.75.

Only about 20 of the 48 pages in this little book are of direct interest to Australian CBers. Twelve pages or so are devoted to getting the best out of your mobile CB rig, and a couple pages to "10" code expressions. There's a page of "Q" code terms and four pages of CB jargon, much of which seems to have been imported from the USA, along with the CB concept. As the publishers explain: the book doesn't contain all the expressions you'll hear but it will help you start talking to the "natives"—a neat way of putting it!

The rest of the book is a reprint of the FCC 1976 (23-channel) regulations covering CB radio in the USA and, while some may be interested to reading the many pages of small print, they are not the rules which apply in Australia, which have yet to be spelt out in detail. So it's back to those first twenty pages!

Our copy of the book came from Technical Book & Magazine Company, 289-299 Swanston St, Melbourne, 3000. (W.N.W.)

☆☆☆

CB RADIO OPERATOR'S GUIDE 2nd Edition, by Robert M. Brown and Paul L. Dorweiler. Fourth printing, published February 1977 by TAB Books. Stiff paper cover, 256 pages 215mm x 136mm, freely illustrated by photographs and diagrams. Price in Australia \$8.50.

If you want to know all about the Citizen's Band Radio Service in the USA, this very recent publication will tell you a great deal of it! Chapter 1, "Introduction to CB Radio" really sells the concept. Chapter 2 and a 50-page appendix explain the US licencing system which, of course, does not apply here. Chapters 3 and 4 on equipment discuss what is available in the USA but would apply obliquely to the local scene.

The chapter on antennas could be helpful—provided you don't start erect-



ing high-gain beams—but other material on coaxial cable and connectors, installation, optimising your station and simple troubleshooting would all be applicable.

There is a chapter also on CB and Public Service which may point the way to its possible future role in Australia. In short, if you're hungry for background information on CB radio, this book will be read with interest.

Our copy came from Technical Book & Magazine Co, 289-299 Swanston St, Melbourne, 3000. (W.N.W.)

☆☆☆

CBer's HANDBOOK OF SIMPLE HOBBY PROJECTS by Robert M. Brown. Published 1976 by TAB Books. Stiff paper covers, 168 pages 208mm x 130mm, illustrated by circuit diagrams. Price in Australia \$5.50.


I must confess to being intrigued by the title of this book and by the index

CITIZENS BAND ANTENNAS

QUALITY **SCALAR** ANTENNAS ARE
DESIGNED AND MANUFACTURED IN AUSTRALIA

MOBILE, MARINE, BASE STATION

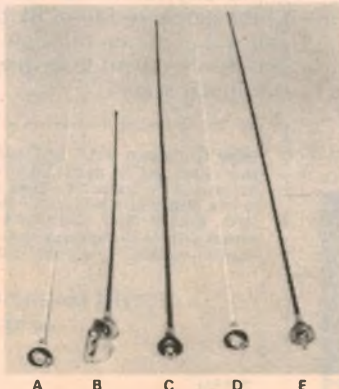Scalar Citizen Band Whip Antennas are designed to provide efficient performance with reduced length. Either helical, centre or top loading on fibreglass rods. They are available for vehicle or marine installations on standard, or marine base, or for gutter or for trunk lid mounting.



TYPES ILLUSTRATED

- A) CB 1220 42" Centre Loaded.
- B) CB 1120 30" Centre Loaded.
- C) CB 1420 60" Helical.
- D) CB 1520 60" Helical / Sector / Top Loaded.
- E) CB 1320 60" Centre Loaded.

A WIDE RANGE OF SCALAR CB ANTENNAS (FROM 30" TO 108" LONG) AND ACCESSORIES ARE AVAILABLE FROM LEADING RETAILERS AND DISTRIBUTORS THROUGHOUT AUSTRALIA.

TRADE ENQUIRIES WELCOME

SCALAR INDUSTRIES PTY. LTD.

COMMUNICATION ANTENNA ENGINEERS.

18 SHELLEY AVENUE, KILSYTH, VICTORIA, 3137.

TELEPHONE: 725-9677 Cables: Welkin Telex: AA 34341

N S W 20 THE STRAND, PENSHURST, 2222. Telephone: 570-1392
QLD (STD 07) 371-5677 WA (STD 092) 57-1555 SA (STD 08) 42-6666



The Australian CB SCENE

list of 114 projects for CBers. Because CB equipment is supposed to be type approved, in America as in Australia, it is not all that open to modification or additions; how then could one possibly dream up 114 CB gadgets?

Looking through the pages, the question was answered—to this reviewer's satisfaction, at least! Had I had to vet the material before publication, I would have rejected a large proportion of the gadgets there and then. The tally would have been much, much smaller!

There are home-made transmitters (illegal?) and elementary receivers which I suspect would radiate. There are a number of microphone preamplifiers and other gadgetry supposed to increase talk power; they may also simultaneously overmodulate and/or distort and cause splatter! I doubt that some of the gadgets would work at all, like a neon bulb TVI detector and a noise limiter involving a neon bulb across the speaker voice coil.

Dubious also are some of the antennas and associated gadgetry, including a diplexer which would feed some of a CB transmitter energy to the domestic TV antenna and the rest to the input circuit of the TV set itself! For sure, some readers may find a use for some of the other ideas but don't blame me if you are disillusioned. In short, a book I definitely would not recommend.

Our copy came from Technical Book & Magazine Co, 289-299 Swanston St, Melbourne, 3000. (W.N.W.)

☆☆☆

PICTORIAL GUIDE TO CB RADIO INSTALLATION & REPAIR. By Forest Belt. Published 1973 by TAB Books. Stiff paper covers, 256 pages 215mm x 137mm, freely illustrated by photographs. Price in Australia \$8.50.

In the preface, the author stresses that there are three kinds of CB equipment repair: by do-it-yourselfers, by technicians who lack appropriate facilities and, lastly, by a relatively small number of technicians who have the appropriate experience and equipment. He remarks that the first two groups often end up with maladjusted transmitters and a heritage of radiated interference—this based on the American experience.

His aim here is to encourage technicians to be better informed about CB radio, and this is certainly appropriate to the Australian scene right now. Accordingly, the first five chapters cover such subjects as installing CB base stations, CB base antennas, coax cables, and CB mobiles, including antennas. At least half the space is taken up by pictures and, while some of the material has to be dis-

counted as appropriate only to the US scene, the general problems are graphically illustrated.

The remaining five chapters deal with the service and instrumentation of CB transceivers, with individual coverage of transmitters, receivers, SSB circuitry and frequency synthesizers. Two of the chapters cover bench and field servicing.

While all this could be read with great interest by any technically inclined CBER, the target audience is primarily that of professional technicians and, for them, a book like this would be an excellent starting place. Our copy came from the Technical Book & Magazine Co, 289-299 Swanston St, Melbourne, 3000. (W.N.W.)

☆☆☆

PRACTICAL CB RADIO TROUBLE-SHOOTING & REPAIR by David F. Norman. Published 1975 by TAB Books. Stiff paper covers, 237 pages, 210mm x 130mm, illustrated by circuits and pictures. Price in Australia \$8.50.

In some ways, this would be a companion book, rather than an alternative to "Pictorial Guide . . ." reviewed earlier, because the approach is quite different. It opens with two chapters on the origin and applications of CB radio and, while the story relates strictly to the USA, it does provide an interesting summary.

Chapter 3, some 38 pages long, gives quite an extensive coverage of CB antennas and, while the more elaborate types would not be permitted in Australia, there is a lot of useful background to the types that are. Chapter 5 also has something to say on antennas and anyone planning to get involved in CB radio repair should find this useful reading.

The chapters on equipment and facilities and for CB service, and on CB troubleshooting are fairly routine material, which shows its age by sundry references to valve stages. An appendix at the rear contains data and typical circuits, but this portion of the book—the last 50 odd pages—would have little relevance to Australia in 1977.

Of the two books on servicing, I'd much rather have Forest Belt's "Pictorial Guide . . ." but this present one could provide useful back-up reading.

Our copy came from Technical Book & Magazine Company, 289-999 Swanston St, Melbourne, 3000. (W.N.W.)

M/W Station Guide

The Australian Radio DX Club advise that they have a new publication titled "Medium Wave Guide" listing all m/w stations in Australia, New Zealand and Papua New Guinea known to be in operation on August 10, 1977. Frequency, power and schedules are given, and space is provided to permit possible additions and alterations. Price of the 17-page publication is \$1.00 and orders should be directed to: 3 Kadana Street, Oak Park, Victoria 3046.

TRADE ENQUIRIES WELCOME

**DIRECT FROM
MANUFACTURER**

DX ½ WAVE BASE STATION
ANTENNAS
5ft HELICAL WHIPS
¼ WAVE MOBILE ANTENNAS

CB HARDWARE

PL 259s, SO 239s, 3 & 4 Pin
Plugs, etc., etc.

**WE ARE SEEKING
COUNTRY AND
INTERSTATE AGENTS**

APPLY IN WRITING TO:

DX PRODUCTS

P.O. BOX 386
HEALESVILLE, VIC. 3777



FRG-7 SYNTHESIZED RECEIVER

for
Amateurs,
Novices,
and
Short-Wave
Listeners.




TECHNICAL DATA

- Electronic Band Changing.
- 0.5 — 29.9 MHz. Continuous Coverage.
- Uses Wadley Loop (drift cancellation circuit) to derive synthesized heterodyne oscillator signal.
- LSB, USB, AM and CW.
- Frequency Readout better than 10 KHz (readable to 5 KHz).
- Stability within 500 Hz during any 30 minute period after warmup.
- Better than 0.7 μ V for 10 dB S + N/NSSB and CW.
Better than 2 μ V for 10 dB S + N/N AM.
- Selectivity \pm 3 KHz at -6 dB, \pm 7 KHz at -50 dB.
- Input Impedance, high 0.5 — 1.6 MHz.
50-75 Ohm 1.6 — 29.9 MHz.
- 234V AC 50-60Hz or 12V DC (external or internal 8 dry cell).
- Size 340 mm x 153 mm x 285 mm.

FRG-7 \$338

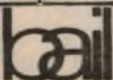Above prices include S.T. Prices and specifications subject to change.



60 Shannon St., Box Hill North
Vic. 3129
Ph 89 2213

Lafayette))

27MHz two-way



**5 WATT 6 CHANNEL
'MICRO 66'**

From the Lafayette Radio Electronics Corporation of U.S.A. Lafayette transceivers embody features which have made them world famous. 1,000's in use throughout Australia, 100,000's world-wide. Government, industrial, marine, sports and farm applications testify to their versatility and rugged reliability.



All units Telecom
Type Approved (Licence
Required)

**Lafayette are 2-way
specialists. Full range 27MHz
crystals, antennas, auxiliary
equipment available!**

Dealer enquiries invited

Lafayette))

the Communicators
LAFAYETTE ELECTRONICS
Div. of Electron Tube Distributors P/L
94 ST. KILDA RD., ST. KILDA
Victoria 3182. Tel. 94 6036

The Australian CB SCENE

18-CH AM/SSB FROM CHIBA AUST.



Heralding the shape of things to come, a new Chiba 18-channel CB transceiver has just been announced, especially produced for the Australian market. Designated as model 69A, it offers full AM and SSB facilities on the 18 channels designated for use in this country.

First impression of the new Chiba transceiver is of a slim, modern unit — an impression largely resulting from the orderly layout of controls on the front panel. Push-buttons along the top select the PA/CB function, AM, USB (upper sideband) and LSB (lower sideband). They lead into a relatively easy-to-read meter indicating "S" points for receive and comparative power for transmit.

Immediately beneath the meter and providing visual balance is the Chiba nameplate and, alongside that, knobs for Clarifier, Squelch and Volume, with the microphone socket in the lower left-hand corner.

At the right-hand end of the panel, illuminated from behind, is the channel selector, with a transmit indicator LED at the bottom right-hand corner.

The 69A is of average size for an AM/sideband transceiver: 250mm wide, 56mm high and 232mm deep, not including knobs at the front or connections at the rear — the latter comprising a 50-ohm antenna outlet, 12V supply socket, and jacks for external CB speaker and PA speaker. The overall finish is in black wrinkle lacquer with chrome plated controls and trim.

Removal of four screws allows the covers to be slipped off, giving ready access to both sides of the PC board on which the vast majority of the components are mounted. Construction appears to be open and conventional.

According to the specifications, the

circuit configuration also appears to follow along modern lines, the receiver being a double-change superhet, fully solid-state, with intermediate frequencies at 10.695MHz and 455kHz, and channel frequencies controlled by a phase-locked loop. Sensitivity for signal/noise ratio of 10dB is quoted as 0.7uV for AM and 0.2uV for SSB. Audio response is from 300 to 2,200Hz and rated audio power output 4W.

Conforming to normal CB regulation limits, the transmitter is rated to deliver 4W output on AM and 12W PEP on SSB, both into a 50-ohm load. Under normal conditions of use, modulation should be greater than 75%, and spurious emission more than 60dB below the main signal.

Connected to a normal 5/8-wave base station antenna, the 69A gave a commendable performance in receive mode with, perhaps, one peculiarity which warrants a mention: with the squelch fully open, the gain after the volume control in the receiver under test was such as to produce a residual hiss with the control right off. It might not have been audible under other than quiet conditions and did not affect normal operation, but we would have preferred it otherwise.

In transmit mode, into a dummy load, the power output appeared to conform closely to expectations and, to judge by a monitor receiver, was characterised by firm, clean modulation.

The Australian CB SCENE

CHIBA 18-CH AM/SSB — continued

The distributors are confident that the 69A transceiver will gain Australian type approval but official testing of all CB transceivers was being delayed, at the time of writing, by an industrial dispute affecting the licensing authority.

The 69A is being handled in Australia by a subsidiary company of Chiba (see EA for September, page 39) but inquiries should now be addressed to 12 Terracotta Drive, Blackburn, Vic. 3130.

(In fact, the 69A is being made the subject of an attractive introductory offer directly to readers of "Electronics Australia". Readers wishing to take advantage of this offer should study the advertisement elsewhere in this issue.)

CB AT THE C.E. SHOW



George Tillett, a well known hifi writer and a frequent contributor to "Electronics Australia", recently visited the Chicago Consumer Electronics Show and had the following to say about the CB radio exhibits:

As far as CB was concerned, there were some very mixed feelings: for one thing, sales of the new 40-channel models have not been as high as expected, partly because there is a huge backlog of something like three or four million 23-channel models left to sell. Consequently, prices of both 23-channel and 40-channel models have been ruthlessly cut!

On the other hand, companies like SBE and Texas Instruments have just introduced expensive and sophisticated models using MPU (microprocessor unit) technology with keyboard tuning, programmable memory, fast and slow scanning, emergency channel override and other facilities. The TI model is a SSB unit and all the controls are in a small hand-held unit which looks just like a calculator. Readouts show the channel number, sideband mode and signal strength.

Hy-gain also make use of MPU circuitry in their Model 16 which has all the controls plus the loudspeaker built into a neat hand-held unit. Two push-buttons control the volume level and there are digital readouts for channel numbers, RF output power and the time!

The transceiver illustrated above is the Aircommand CB-640 40-channel model with LED indicators for channel number and metering, channel 9 scan, and SWR indicator.

One of the intriguing spin-offs of the CB boom is the increased interest in amateur radio in the USA. The ARRL reports that the licence figures now stand at 375,000 with 50,000 non-amateurs now enrolled in radio training courses.

Convert your CB into a base station




Power your rig direct from mains electricity with an SEC approved power supply.

These small portable units provide a factory-set 13.8V DC regulated output for maximum transmitting power.

High performance integrated circuitry guarantees clean, hum-free reception. Quick-connect terminals facilitate rapid changeover from static-mobile-static operation.

ARLEC CB radio power supplies

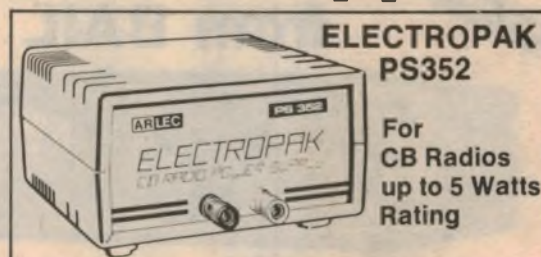

**ELECTROPAK
PS352**

For
CB Radios
up to 5 Watts
Rating

1.8 Amp peak capability. Automatic overload protection.
1.0 Amp continuous output. Size: 140 x 80 x 133mm



**SIDEBAND 4
PS353**

For CB
Radios up
to 15 Watts
Rating

4 Amp peak capability. Automatic overload protection.
2 Amp continuous output. Size: 140 x 80 x 133mm

See them at your local CB Store or write to
A&R Electronic Equipment Co. Pty. Ltd. for further details

A+R ELECTRONIC EQUIPMENT CO. PTY. LTD.

A MEMBER OF THE A+R-SOANAR ELECTRONICS GROUP
SALES OFFICES

30 Lexton Road, Box Hill, Vic., 3128
Australia. Telex 32286

VICTORIA: 89 0661
N.S.W.: 78 0281
S. AUST.: 51 6981
QUEENSLAND: 52 5421
W. AUST.: 81 5500



HERE!

Plug this frequency counter into 240V AC or 12V DC and count up to 750 MHz.



Get 7 digit direct readout with high visibility 1/2" LED's 50 ohm and 1Mohm protected inputs. Switchable 1 MHz low pass filter on the input. High stability internal time base, self check function and many more cost saving features.

The DFM 600 from Scientific Electronics is easy to use and easy to read — its low cost, coupled with high performance and versatility make it the ideal frequency counter for applications ranging from production line testing, calibration, education, frequency monitoring to telecommunications and 2 way radio and video servicing.

The DFM 600 offers 240V or 12V DC operation. Counts up 750MHz. 50 ohm and 1 Mohm protected inputs. High stability internal time base. 7 Digit Direct Readout with Zero blanking. Switchable 1MHz Low pass filter on input. Self check function. 25 mV Sensitivity (high z input only). External oscillator input. Ratio measurement capability. Attenuators on input x1x10x100. Display update (gate) indicator. Overrange indicator.

Also available is the DFM 100, this is priced even lower than the 600 but still enjoys many of its excellent features — including 240V or 12V DC operation.

Designed and manufactured in Australia by:

Scientific Electronics



42 Barry Street, Bayswater, Victoria, 3153. Telephone: 729 3688. Contact these distributors for prices and data — Victoria, Electro Technics, 699 2716 N.S.W. Electronic Developments, 51 7007. S.A. Graphic Electronic Industries, 42 6655. Qld. Fred Hoe and Sons, 277 4311. W.A. W.J. Moncrieff Pty. Ltd. 325 5722.



CB Transceivers from BAIL



GTX-3336

Delux AM 23 Channel transceiver featuring built-in range boost modulation, Automatic Noise Limiter, and Modulation indicator \$89

GTX-3325

Delux SSB/AM 23 Channel transceiver featuring built-in Range Boost Modulation, FET RF amplifier for high receiver sensitivity, Noise Blanker, RF gain control and large S-meter 15 watts PEP SSB, 5 watts AM \$269



also available from BAIL ELECTRONICS QUALITY BASE STATION & MOBILE ANTENNAS

The original ASAHI "Million V1" 1/2 wave "Ringo" 3.75 dB base station antenna, still only \$52. (Illustrated at left)

HIDAKA VS 10 GH 5/8 wave, 4.25 db 27/28 MHz, very rugged construction, 9ft radials, excellent value at \$65.

ASAHI TD-1 "twin-trucker" phased twin mobile whips, \$39 the set complete with mounts and co-ax harness.

HIDAKA VS-11cm three element heavy duty beam \$89.



Plus mobile whips: Mag-mount, Gutter clip, Helicals, Motorised CB/AM/FM combinations. Also, antenna mounts, SWR meters, test sets, Low-pass TVI filters, Linear amplifiers, etc., etc.

TRADE ENQUIRIES WELCOME. Above prices include S.T. Freight and Insurance is extra. 90-day warranty. Prices and specifications subject to change. Note all Transmitting Equipment requires a Licence.



ELECTRONIC SERVICES

60 Shannon St., Box Hill North, Vic., 3129. Phone 89 2213
Distributors in all states and N.T.

The Australian CB SCENE

PHILIPS UHF PROTOTYPE

Following the announcement that they would be entering the UHF CB field, (E.A. Sept. p37) Philips have taken the further step of exhibiting their first production prototype and confirming the price at "about \$300".

Designated as type FM320, the new transceiver is scheduled to go on sale in January next and should prove a boon to those who need 2-way CB-style communication — but not of the kind which presently characterises the 27MHz band.

Reception conditions on UHF will tend to be much quieter and more hassle-free for a variety of reasons. With little or no "skip" at these frequencies, local point-point communication will not be cluttered by distant signals or "DX" activities; atmospheric, ignition and other man-made noise will be much less troublesome; and there will be 40 channels over which to distribute the local traffic.

This much is an outcome of the use of a higher frequency band but Philips point out that, in addition, the move to UHF will make possible the use of frequency modulation in place of amplitude modulation or SSB, giving a further protection against noise, heterodyne effects and cross-talk. The standard of communication will approach more closely that of established 2-way radio services.

Another very significant bonus flowing from the use of UHF FM will be the reduction of interference radiated into neighbouring TV receivers, hifi systems and other electronic equipment. As in America, this has already reached the hassle stage in Australia.

Philips list a variety of features for their forthcoming FM320 transceiver including such things as:

- 40 channels provided;
- Digital channel display;
- Electronic channel change with variable stepping rate.

DELTA BASE CB RADIO of East Bentleigh, Vic, are manufacturing half-wave base station antennas under the new trade name of DX Products, at Healesville, Vic. They are also manufacturing 5ft helicals, bases to suit helicals and, as well, they distribute a wide range of CB hardware. Trade inquiries should be directed to DX Products, PO Box 386, Healesville, Vic 377.


- Instant return to a preferred channel;
- 5-watt RF output;
- 2-watt audio output;
- Microswitch operated push-to-talk.

CREST AUSTRALIA: Following a meeting in September, the National Headquarters of CREST (Citizens Radio Emergency Service Teams) Australia is to be located in Canberra. Information regarding CREST should, in future, be sought through the National Secretary, David T. Wynn, at 157 Blamey Crescent, Campbell 2061.

Other office bearers elected were: National Director, Bill Payne, 10 Davis St, Glebe 2037; National Operations Director, John A. White, 86 Schlich St, Yarralumla 2600; National Treasurer,

Jan Kuwahata, 36 Tobalum Rd, Balgowlah 2093. Also recognised was the Immediate Past National Operations Director, currently Dermot Lynch, 170 Enmore Rd, Enmore 2042; tel 02 519 1772.

IN THE USA, CB licence applications to the FCC rose to 3.25 million in the first half of 1977, up more than 10% from the 2.93 million filed in the first half of 1976, a record year for CB radio sales and licence applications. Approximately 11 million licences have been granted by the FCC since it began licensing CB in 1958, over half of them in the last 18 months, according to the Electronic Industries Association. EIA staff vice president John Sodolski estimates that "by 1980 there will be more than 50 million mobile citizens' radios in use in the US — approximately one in every other car — in addition to 15 million to 20 million base stations."

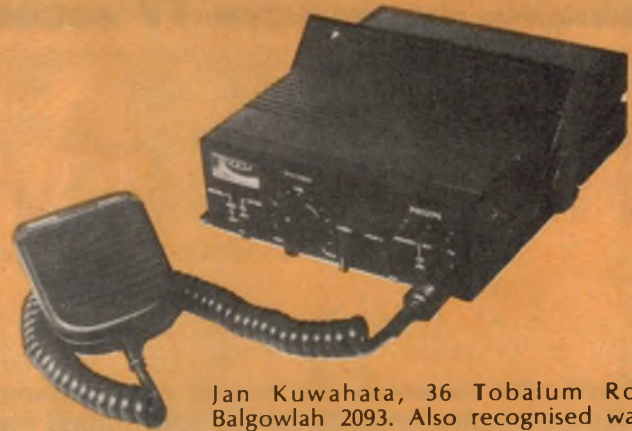

From out of the blue comes a dramatic improvement in CB from Telex, the aviation communications experts.

Exclusive Double-Header feature allows use as a conventional power mike or a superior, noise-cancelling power mike.

Patented design fits every hand — the same style used by pilots around the world.

Unique aircraft-type front mount eliminates mike tumbling. Mike comes off the bracket in the talk position.

Built-in variable gain power amplifier.

Made in U.S.A.

The first "loud and clear" CB mike.

**The Pilot People
TELEX
COMMUNICATIONS, INC.**

Unique Telex CB-73 Double-Header — power mike with switchable noise-cancelling mode.

Puts you through loud — thanks to the power mike — and clear — thanks to the special noise-cancelling mode. Built-in integrated circuit amplifier maximizes "talk power" without distortion. In high noise environment, switch to unique noise-cancelling mode. Try it. You'll get the message — loud and clear.

<p>AUDIO TELEX COMMUNICATIONS PTY. LTD.</p>	<p>SYDNEY 54-56 Alfred Street, Milsons Point 2061 Telephone: 929-9848</p>
	<p>MELBOURNE 828 Glenferrie Road, Hawthorne 3122 Telephone: 819-2363</p>

Simple, inexpensive TV accessory:

Remote TV headphones

If you like to watch TV late at night without disturbing other members of the household, this little gadget may be just what you are looking for. You listen to the TV sound using either an earphone or a pair of headphones, without being tied to the TV by a bothersome cord. No modifications are required to the TV set, and the unit is simple and economical to construct.

by **DAVID EDWARDS**

The unit to be described in this article also has a use as a TV hearing aid for people who are hard of hearing. With slight modifications, it is possible to arrange for such people to hear the TV sound channel at a level higher than would normally exist in the room. Of course, this could be done simply with headphones alone, but normally this requires the listener to be "tethered" to the set.

With the unit described here sound information from the TV is transmitted to a self contained receiver unit by magnetic induction. To do this, a loop of wire is required around the perimeter of the room in which the device is to operate. This loop is fed with the required audio signal, and generates a magnetic field in the interior of the loop whose intensity varies with the audio information.

The receiver consists simply of a second loop, whose output is fed into a

suitable voltage and power amplifier. In order to improve the efficiency of energy transfer, while keeping the receiving loop to small dimensions, it is wound around a section of ferrite rod. This enables the complete receiver to be housed in a small mini-box, measuring only 83 x 54 x 29mm.

The circuit details of the receiver are shown in the accompanying circuit diagram. The pickup coil consists of five layers of 30 B & S enamelled copper wire, wound on a 75mm length of 9.5mm (3/8") ferrite rod. The exact number of turns is not critical, and neither is the size of the wire used.

We have used an LM380 integrated circuit as the amplifier, as this gives a simple, reliable unit, using a minimum of parts. These devices have a fixed gain of 34dB, and are capable of driving an 8 ohm speaker or headphone directly. The output is short circuit proof, and incorporates thermal limiting. Either an 8 or 14 pin package is available.

We have tailored the input and output coupling capacitor values to limit the low frequency response of the receiver. This is required because of the large amounts of 50 and 100Hz hum

and ripple which tends to be picked up by the loop. The 100pF capacitor connected between the inputs also rolls off the high frequency response above 5kHz, to prevent any stray 15625Hz TV line frequency signal from being passed to the headphones.


We have used tantalum capacitors for the supply decoupling and bypass units, as these are usually smaller than their aluminium counterparts. Power is supplied by a 9V battery, one of the 216 type units. A small slider switch is used as an on/off switch.

Construction of the unit should be within the capabilities of the average enthusiast, and does not require any specialized tools. We made up the transmitter loop using a 15 metre

PARTS LIST

- 1 LM380N or LM380N-8 audio amplifier
- 1 47uF 6.3VW tantalum electrolytic capacitor
- 1 33uF 10VW tantalum electrolytic capacitor
- 1 4.7uF 35VW tantalum electrolytic capacitor
- 1 0.0022uF polyester capacitor
- 1 100pF ceramic or polystyrene capacitor
- 1 length of 9.5mm (3/8") dia. ferrite rod
- 1 earphone socket
- 1 9V miniature battery and clip to suit
- 1 plastic minibox, 83 x 54 x 29mm
- 1 miniature slide switch
- 1 length of multiconductor cable Veroboard, solder, 30 B & S enamelled copper wire, insulation tape, hookup wire.

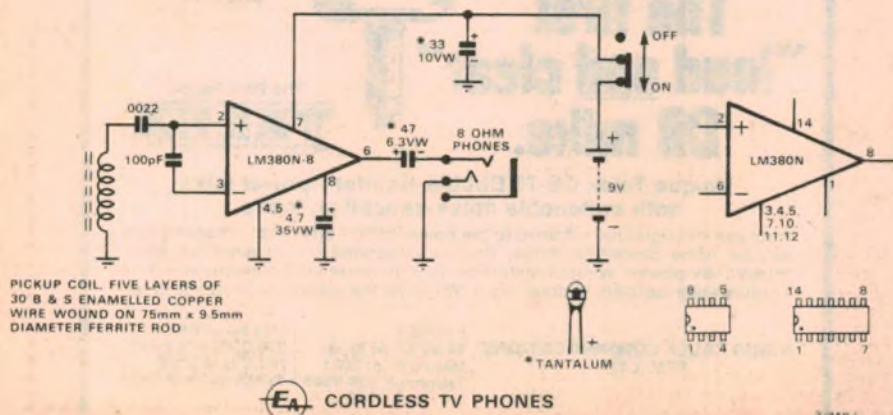BELOW: The circuit diagram of the receiver unit. Note the different pin connections of the two LM380 devices currently available.





length of six-way cable. This enables a six turn loop to be obtained fairly easily.

The accompanying photograph shows how we used a small piece of Veroboard to terminate the cable, and to facilitate the connection of the separate wires into a loop. When we had completed the loop wiring, we were pleasantly surprised to discover that the total loop impedance was about 8 ohms. This meant that no series resistor was required to match the loop into the TV receiver loudspeaker voice-coil circuit.

Alternatives to the type of cable we used include rainbow cable or telephone cable. The important parameter to consider when purchasing cable is the effective cost per metre. In other words, 12-way telephone cable at 60 cents/metre has an equivalent cost of 5 cents/metre, as against plain hookup wire at 8 cents/metre.

For permanent installations, the best place for the cable is behind skirting boards, under carpet, or even under the floor-boards. Check the resistance of the completed cable, and if it is less than 8 ohms, add sufficient resistance to bring the total resistance up to this value. Then fit a suitable cord and plug to the free ends of the loop, so that you can plug it into the earphone socket of your TV or radio.

The first step in the construction of the receiver is to cut the ferrite rod to the correct length, if you have not been able to purchase it already cut. Instead of using a new rod, it is possible to use an old aerial rod from a transistor radio. The existing coil may be pressed into service, although you will still require extra turns.



-that's where the money is!

Stott's course is totally comprehensive — and includes both sophisticated electronic equipment and project materials you need to gain a thorough understanding of servicing techniques.

Divided into three self-contained sections, the course covers:

Part 1 — Introduction to Electronics (theory and practice)

Part 2 — Monochrome Television Receivers

Part 3 — Colour Television, including processing circuitry, service techniques, fault tracing and trouble shooting techniques.

Like all Stott's courses, you work with your own instructor who is an expert in this exciting and rewarding field, at your own pace, in your own home.


If you are a beginner, Stott's will teach you everything you need to know concerning television principles and receiver circuitry.

If you are already working in the field, or have completed some studies in electronics, you may be eligible to enter the course at an advanced stage. Whether your aim is to enter the TV service industry or whether you wish to gain a thorough understanding of television theory and servicing as an aid to sales experience, this is the course which will help you make it!

Other electronics courses offered by Stott's include:

Digital Electronics — AM Radio Receivers —

Radio for Amateurs — Amateur Operator's Certificate

EA 11.77	STC28
	
TECHNICAL CORRESPONDENCE COLLEGE The name to trust in correspondence education Please send me, without obligation, full details of the following courses:	
(please PRINT)	
Stott's undertake that no sales counsellor will visit	
Mr., Mrs., Miss	Age
Address	
Postcode	
159 Flinders Lane, Melbourne, 3000. Tel: 63 5583	66 King William St., Kent Town, S.A., 5067. Tel: 42 5798
383 George Street, Sydney, 2000. Tel: 29 2445	89 St. George's Terrace, Perth, 6000. Tel: 22 5481
290 Adelaide Street, Brisbane, 4000. Tel: 31 1627	P.O. Box 3396, Singapore 1

The Swamper II

UNIQUE CB BASE ANTENNA

EXCLUSIVE! Highly efficient and attractive capacitive top hat — lowers angle of radiation and means your signal gets further!

EXCLUSIVE! Commercial quality aluminium tubing. Antenna extends to over 5.4 metres — wind survival rating in excess of 130km/h.

EXCLUSIVE! Unique self-locking collars for instant erection or dismantling. Simply slide the section up and turn the collar. That's it!

EXCLUSIVE! Full half wave antenna gives 3.75 dB of gain. No ground plane needed!

EXCLUSIVE! All components and hardware come on a single card pack with full instructions. Extra easy for assembly — nothing to disappear out of a bag!

EXCLUSIVE! Base of antenna is at DC ground potential to minimise static and induced noise interference!

EXCLUSIVE! Bottom of antenna just slips over our standard 1½in TV mast pipe. Instant and cheap method of erecting your antenna!

VALUE PLUS!

Complete with 50' co-ax cable with pre-soldered plugs, and full mounting instructions.



Here it is: the Swamper II. A brilliant new concept in CB base station antennas. And you'll find it only at Dick Smith stores and dealers.

No more fiddling with holes that don't line up; no more losing the screws or stripping the threads; no more juggling a 20 foot length of unwieldy antenna against a howling southerly!

The Swamper II is so simple to erect. Just pull out the telescoping sections and lock. That's it. And it's ring fed for easy SWRing. And it fits over a TV mast pipe!

But don't just use it as a base — use it on a van or camper. Drive along with it collapsed, when you get to the site you're on the air in seconds!

We could go on and on describing the virtues of this incredible antenna. But better than that, find out for yourself. At just \$69.00 it's a bargain. Remember with this antenna alone you get 50 feet of co-ax with pre-soldered plugs all in the one price. That's usually worth at least \$11.00 more — and then you have to solder them on!

Have a look at this exciting antenna today — at your nearest Dick Smith store or dealer. You won't be sorry!

ALL THIS FOR ONLY \$69⁰⁰

Cat D-4428


DICK SMITH ELECTRONICS GROUP

SYDNEY - 125 York St. Ph: 29 1126.
 GORE HILL - 162 Pacific Hwy. Ph: 439 5311.
 BANKSTOWN - 361 Hume Hwy. Ph: 709 6600.
 PARRAMATTA - 30 Grose St. Ph: 683 1133.
 MELBOURNE - 656 Bridge Rd. Richmond. Ph: 42 1614.
 399 Lonsdale St., City. Ph 67 9834
 BRISBANE - 166 Logan Rd. Buranda. Ph: 391 6233.


THE AUSTRALIAN COMPANY.

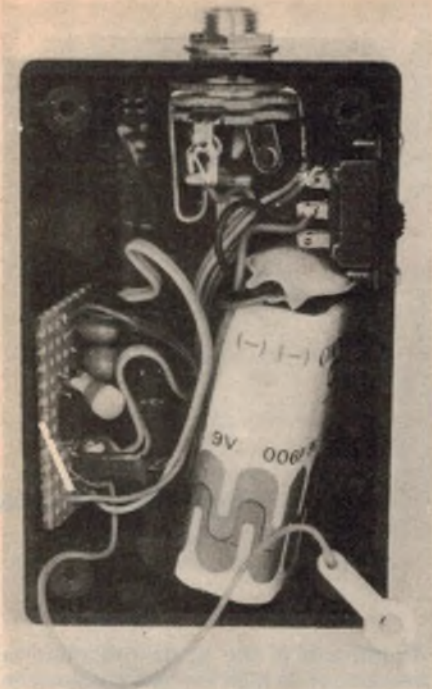Mail Orders: Box 747, Crows Nest, NSW.
 Postage and packing is extra!
 We have a network of dealers across Australia.





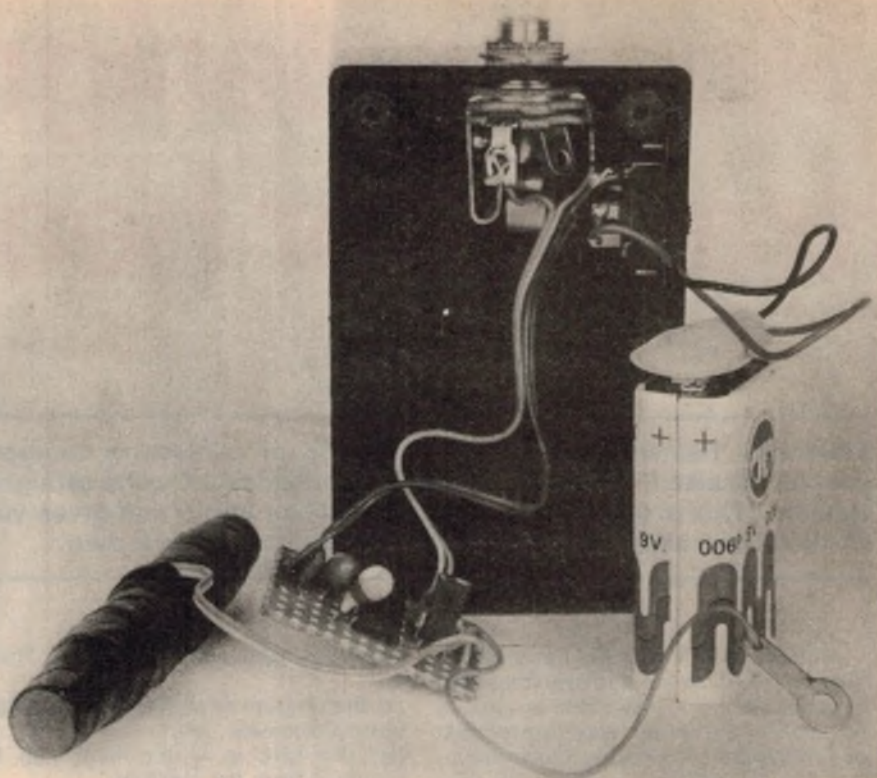ABOVE and RIGHT: These two photographs show how the various components are fitted into the case.



To cut the rod, use a three cornered file to make a nick round the circumference, and then simply snap it in two. You will find that it will snap where the nick is. The wire can be wound onto the rod by hand, but this is very tedious. A better way is to use an electric or hand drill.

We used a two speed electric drill with a 9.5mm ($\frac{3}{8}$ ") chuck, along with a drill speed control. A suitable speed control was described in the July 1976 issue (File No. 2/PC/22). Clamp the drill to your bench, or in your vyce, and adjust the speed control to a very low speed (with the drill set for low speed as well!).

Anchor the start of the winding to the rod with a small piece of insulation tape, and then turn on the drill and commence to feed the wire onto the rod. Use an even tension, and make sure that the turns are wound on evenly, so that the second and subsequent layers will go on easily. When the fifth layer is complete, anchor the end with more tape, and then completely cover the coil with a layer or two of tape.

If you wish, you can solder the coil ends to short pieces of hookup wire, and then tape the joints thoroughly to the rod. This will provide a strong mechanical joint, and prevent the thin winding wire from breaking.

The LM380 is mounted on a small piece of Veroboard, along with the associated capacitors. The circuit diagram shows the connections for the two packages available. The smaller package cannot supply as much output power as the larger one, but is recommended on the grounds of cost,


as it supplies ample power for headphones.

Use the photographs as a guide to the placement of the components, as there is not much room in the box. The headphone socket is mounted at one end, with the power switch near it. The rod lays along one side, with the Veroboard assembly lying at an angle over it. The battery is laid along the other side, near the power switch.

The aluminium lid of the box should be connected to the negative side of the battery, as otherwise spurious sounds are produced when it is touched. To test the completed system, simply try using it. With the volume control on the sound source set at a normal listening level, and the loop energised, sound should be heard in the phones whenever the receiver is inside the area of the loop. Note that the ferrite rod in



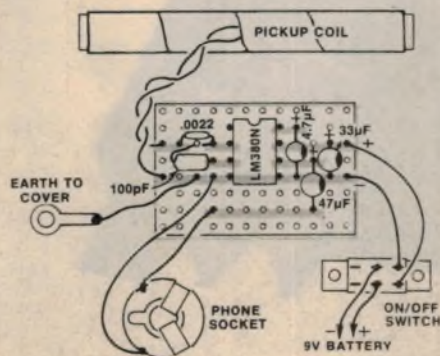ABOVE: This photograph shows how we terminated the transmitter loop onto a small piece of Veroboard.



ABOVE: Use this diagram to aid the placement of components on the Veroboard. A different layout is required for the 14-pin package.

the receiver must be held perpendicular to the plane of the transmitter loop, for maximum pickup.

The volume of the received sound can be varied by varying the volume of the TV or radio driving the transmitter loop. If required, a volume control can be fitted to the receiver by inserting a 500 ohm potentiometer in series with the phone jack.

If it is required to drive the transmitter loop at the same time as the TV speaker, it will be necessary to connect the loop in series with the speaker. To do this will most likely require modifications to the set, and these should only be attempted by those qualified to do so.

Finally, we would like to point out that more than one receiver unit can be used with a single transmitter loop. ☺

How to design transistor heatsinks

Transistor heatsink design is something of a mystery to most people, despite the fact that the basic principles are quite straightforward. This article explains how heatsinks work, and gives you all the information necessary to design and select your own.

by GREG SWAIN

An understanding of the basic principles involved in heat dissipation and heatsink design is important to anyone involved in the design and construction of semiconductor circuits. Semiconductors are temperature sensitive devices and, to ensure reliable circuit operation, care must be taken to ensure that circuit temperatures do not exceed certain critical limits.

The primary limitation on the power handling capability of any semiconductor device is the maximum temperature at which the device junctions will continue to operate normally. This maximum temperature depends on the semiconductor material used, and for silicon may run as high as 200°C.

The actual temperature that the junction will reach in circuit operation

depends mainly on two factors. These are:

- (a) the amount of power being dissipated in the device; and
- (b) the rate at which heat can be removed from the junction.

More specifically, the temperature reached by the junction of a diode or transistor is the sum of the ambient temperature and the rise due to generated heat energy. And the temperature rise due to the heat generated depends upon the ease with which the heat may be dispersed away to the ambient. The easier it can flow away, the lower the temperature rise of the device, and vice-versa.

The heat removal process can be made more efficient by mounting the device on a metal dissipator or "heatsink".

Aluminium is the preferred material because of its high thermal conductivity and light weight. Heat energy is then transferred from the device case to the heatsink by conduction and removed from the heatsink itself by conduction, radiation and convection.

One way of thinking of a heatsink is to consider it as a thermal impedance matching device. The small device case represents a relatively high thermal impedance, while the ambient surroundings represent a very low impedance. The coupling between the two without a heatsink is thus rather poor, due to the mismatch.


To explain further, it is easier for heat energy to be transferred from the device to the heatsink and thence to the surrounding air than it is for heat energy to be transferred directly from the device to the air. The closer the impedance match, the more efficient the heat removal process, and the lower the device temperature.

In practice, the thermal impedance depends on the design and size of the heatsink. As a general rule of thumb, the larger the heatsink, the lower its thermal impedance. Obviously, there is a practical limit to the size of heatsink that can be employed, and the problem facing the equipment designer is one of finding the correct heatsink for the job on hand.


The most convenient way of describing the relationship between temperature rise and the ease with which heat can be removed from a device is to use an electrical analogy. By equating temperature rise with voltage and heat energy flow with current, then the relationship which links the two can be considered as "resistance"—or, in this case, thermal resistance.

We can now link these three factors into the thermal equivalent of Ohm's Law:
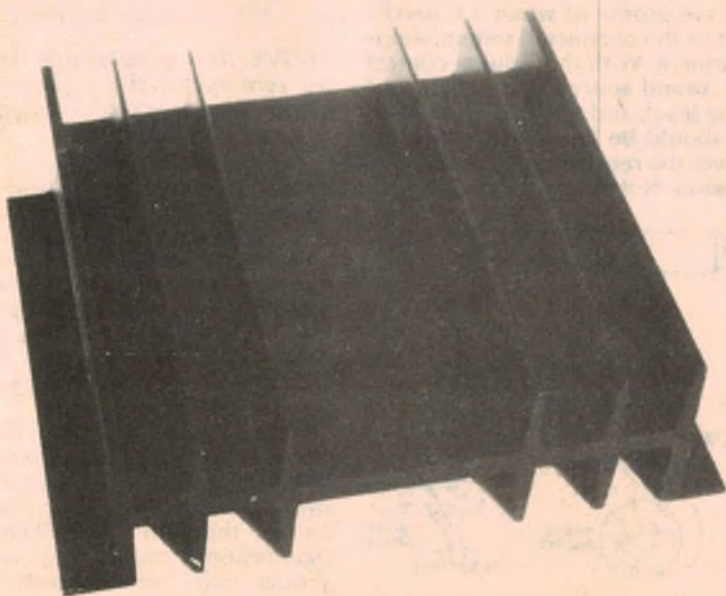
$$T = P \times K \dots \dots \dots \text{Eqn (1)}$$



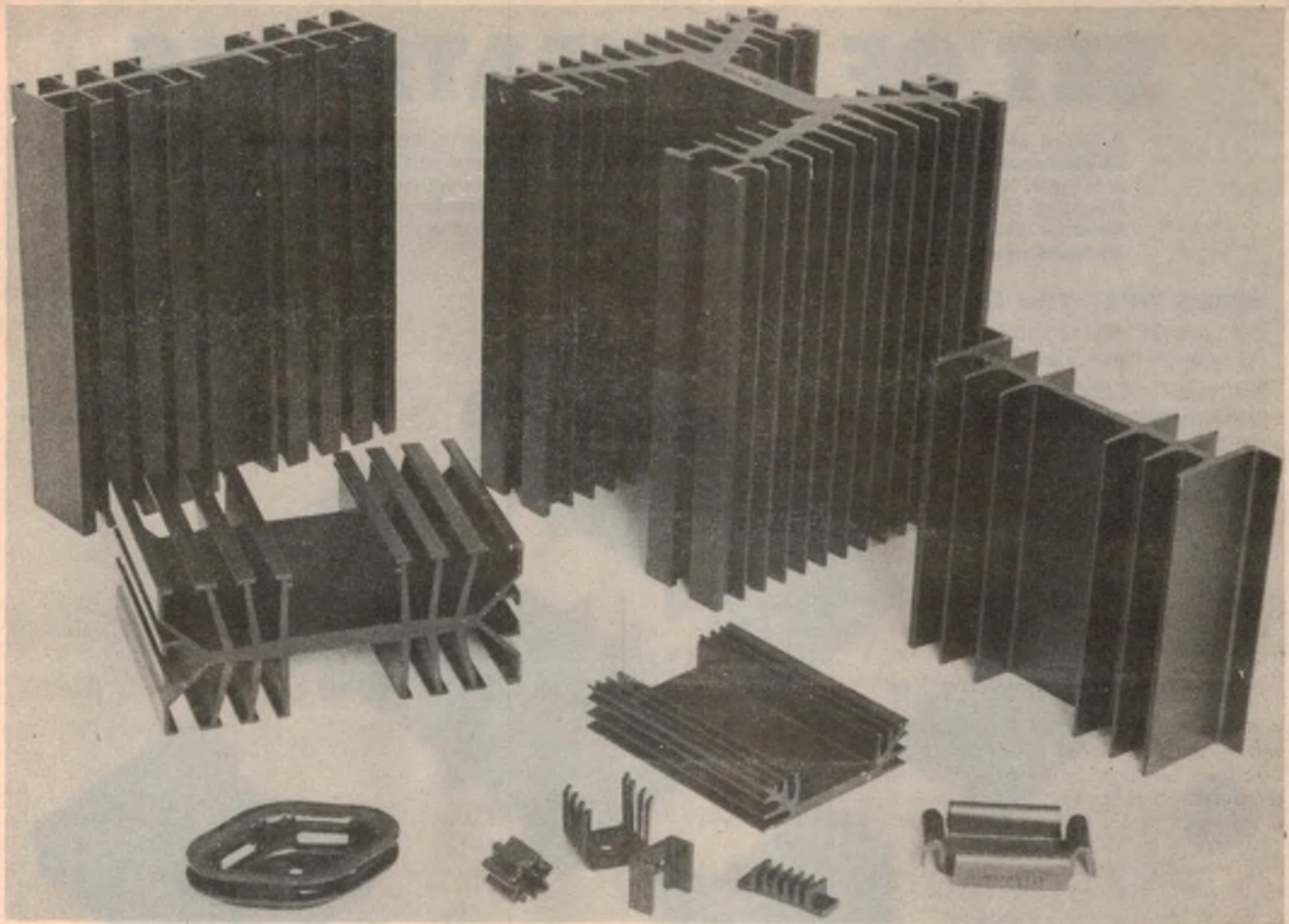76mm length P-type heatsink from Redpoint. Thermal resistance is 2.8°C/W.



A selection of heatsinks from the Redpoint range. Thermal ratings are specified by the manufacturer.

where T is the temperature rise, P is the heat energy flow, and K is the thermal resistance.

The actual operating temperature of our diode or transistor junction can thus be calculated by simply adding the product of heat flow and thermal resistance to the ambient temperature:

$T_j = P_{diss} \times K_{j-a} + T_a$ Eqn (2)
 where T_j is the junction temperature in degrees C, P_{diss} is the heat flow (equal to the power being dissipated in watts), K_{j-a} is the total thermal resistance between the junction and the ambient, and T_a is the ambient temperature (also in degrees C).

The total thermal resistance K_{j-a} has a value which depends on several factors. These include the size of the device junction, the method of mounting within the case of the device, the type of heatsink used (if any), and the method of removing heat energy from the heatsink. In practice, the total thermal resistance K_{j-a} can be considered to be the sum of a number of different thermal resistances.

Once again, a simple electrical analogy can be used to illustrate this last point. This is shown in Fig. 1 which gives an equivalent circuit for the thermal resistance between the junction and the ambient:

$K_{j-a} = K_{j-c} + K_{c-s} + K_{s-a}$ Eqn (3)
 where K_{j-c} is the thermal resistance between junction and case, K_{c-s} is the thermal resistance between case and heatsink, and K_{s-a} is the thermal resistance between the heatsink and air.

Eqns (2) and (3) are the basic equations from which we can readily calculate our heatsink requirements. The maximum allowable power dissipation for a device is specified by the manufacturer, as is the maximum junction temperature T_j (or alternatively the junction-to-case thermal resistance). The ambient temperature for which the equipment is intended is known by the designer.

Note that maximum power dissipation is usually specified for a case temperature of 25°C. This is because the device manufacturer has no way of knowing what type of heatsink will be used with the device. The above equations allow the user to calculate the extent to which the device must be derated for higher case temperatures.

The case-to-heatsink thermal resistance K_{c-s} depends upon the way the device is mounted on the heatsink. If the device is properly mounted on the heatsink, and no insulating material is used between the two, the heatsink will be at

the same temperature as the device case and K_{c-s} will be effectively zero. More often than not though, the device case must be electrically insulated from the heatsink material, and for this purpose a thin mica washer is normally used.

A thickness of about .002" of mica is generally considered adequate for insulation, resulting in a value of about 0.5°C/W for K_{c-s} . A thin smear of silicone grease is usually applied to both sides of the mica washer before mounting in order to improve the thermal bonding.

The problem of choosing an ap-

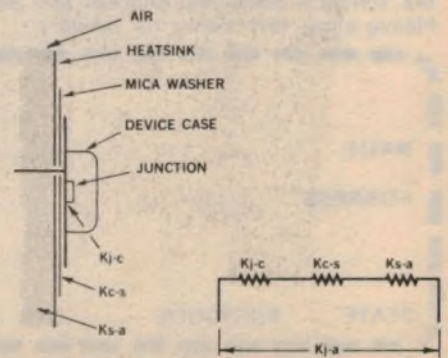


FIG. 1


SET OF 12 HEATSINKS

If you're an experimenter, technician or radio amateur building up electronic equipment, this bargain pack of well-known "Redpoint" heatsinks for transistors and other semiconductor devices is for you. It offers 12 heatsinks, selected from those most often used, and together with a jar of mounting compound — at a price much lower than you'd normally have to pay. All have the standard black matt finish, for optimum heat dissipation, and the PCB types are drilled for standard device mounting.

HERE'S WHAT YOU GET:

- 2 x type 2P (extruded TO-3 size, 3.4°C/watt)
- 1 x type 2Y (extruded TO-3 size, 6.20°C/watt)
- 2 x type TV3 (TO-3 size, 7.2°C/watt)
- 2 x type TV 4 (TO-126 size, 17°C/watt)
- 5 x type 5F (clip-on TO-5, 50°C/watt)
- 1 x jar of mounting compound

**SPECIAL OFFER
TO OUR
READERS**

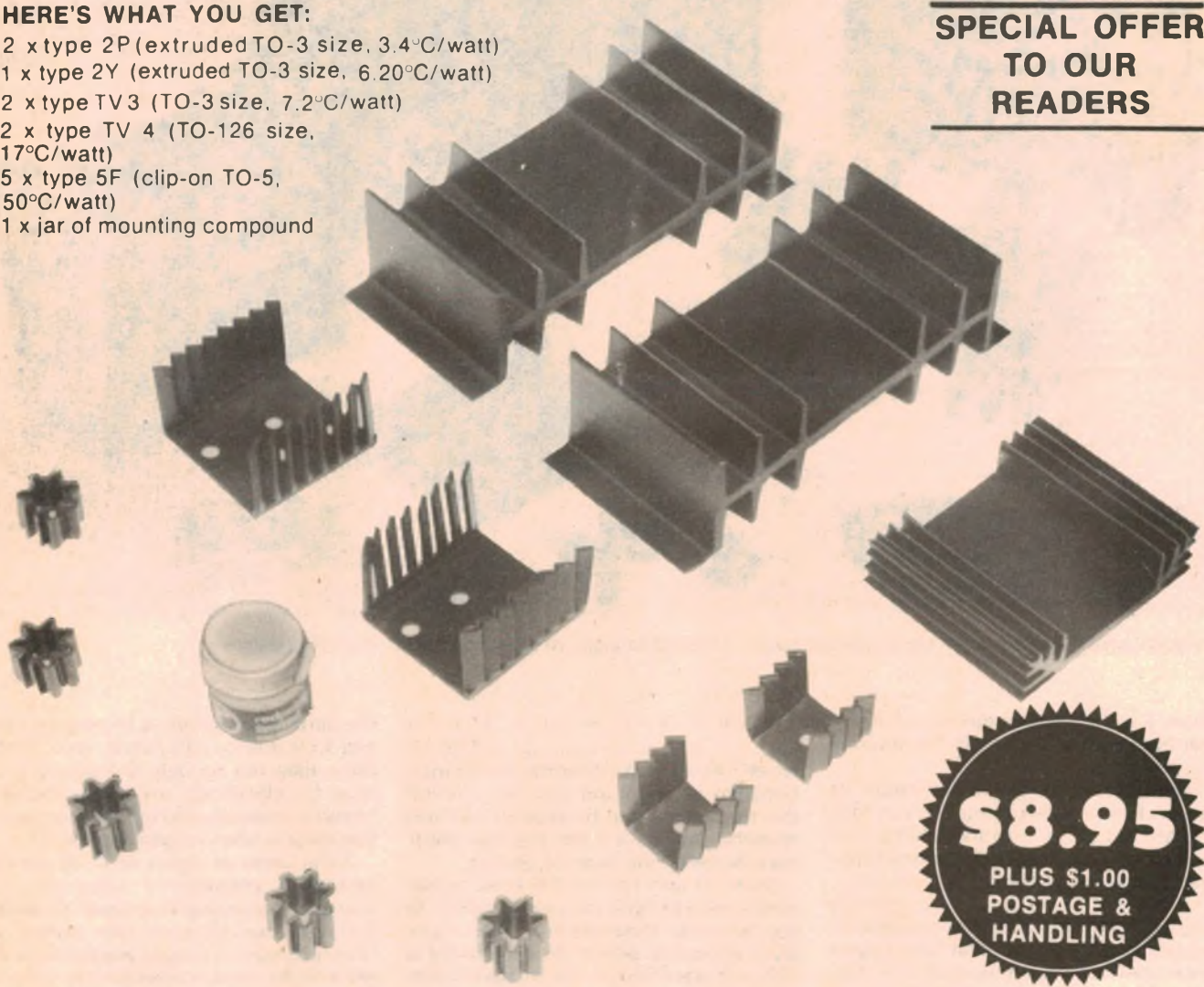

\$8.95
PLUS \$1.00
POSTAGE &
HANDLING

HOW TO ORDER: Fill in BOTH sections of the coupon. In each section print your name and full postal address in BLOCK letters. Cut the entire coupon out around the dotted line. Send it with your money order or crossed cheque to this Magazine's Mail Order Department Offer No. 160/77. PO Box 4000, GPO Sydney 2000. Cheques should be endorsed on the back with the sender's name and address and made payable to this magazine. This offer is open to readers in Australia only. Please allow four weeks for delivery.

This Magazine's Heatsinks Offer No. 160/77

NAME

NAME

ADDRESS

ADDRESS

STATE

POSTCODE

Please send me (state quantity)

EA 11 77

STATE POSTCODE QTY.....

I enclose my postal/money order to the value of \$

How to design transistor heatsinks . . .

appropriate heatsink for a given design situation thus reduces to one of determining the maximum allowable heatsink-to-air thermal resistance K_{s-a} . This we can do by combining equations (2) and (3) to get an expression for K_{s-a} :

$$K_{s-a} = (T_j - T_a) / P_{diss} - K_{j-c} - K_{c-s} \quad \text{Eqn (4)}$$

The use of this formula can best be illustrated by working through a simple example. Consider a transistor (eg 2N3055) with a rated P_{diss} of 115W at a case temperature of $T_c = 25^\circ\text{C}$ and K_{j-c} of 1.52°C/W , operated on a heatsink in an ambient air temperature of up to 35°C . We wish to design a suitable heatsink to enable us to dissipate 20 watts in the transistor junction.

The maximum T_j for this device would be $1.52 \times 115 + 25 = 200^\circ\text{C}$. The maximum K_{s-a} we could allow for the heatsink would thus be:

$$\begin{aligned} K_{s-a} &= (200 - 35) / 20 - (1.52 + 0.5) \\ &= 8.25 - 2.02 \\ &= 6.23^\circ\text{C/W} \end{aligned}$$

This assumes the use of a mica washer between the case of the device and the heatsink, with a thermal resistance of 0.5°C/W .

We can now go further by calculating the temperature differentials across various parts of the thermal circuit of our example, and thus the temperatures reached by the heatsink and the device case. The temperature reached by the heatsink is given by $T_s = (P_{diss} \times K_{s-a}) + T_a = (20 \times 6.23) + 35 = 159.6^\circ\text{C}$. Similarly, the temperature reached by the device case will be $T_c = (P_{diss} \times K_{c-s}) + T_s = (20 \times 0.5) + 159.6 = 169.6^\circ\text{C}$.

In a practical situation, the calculated K_{s-a} value would be derated in order to provide a safe operating margin. For example, our calculated K_{s-a} value of 6.23°C/W could be derated by choosing a heatsink with a K_{s-a} rating of, say, 4.2°C/W .

Again, in a practical situation, there may be a maximum heatsink or device case temperature which is tolerable from a design aspect. This will be particularly so in those instances where the heatsink is exposed to the equipment user, and the temperature must be limited for safety reasons. A situation familiar to most readers is when the series-pass regulator transistor of a bench power supply is bolted to an exposed heatsink, or to the metal case.


Let's now assume that under normal load and regulation conditions, our regulator transistor (2N3055) dissipates 10 watts. And let's also assume that, for safety reasons, the maximum permissible case temperature of the device is 60°C , and that the ambient temperature is 35°C . What is the maximum K_{s-a} for a heatsink that will satisfy these conditions?

The first step is to calculate the temperature of the heatsink. Now $T_c = (P_{diss} \times K_{c-s}) + T_s$ which gives $T_s = 60 - 5 = 55^\circ\text{C}$. Also, $T_s = (P_{diss} \times K_{s-a}) + T_a$, which on rearranging gives $K_{s-a} = (T_s - T_a) / P_{diss} = (55 - 35) / 10 = 2^\circ\text{C/W}$.

There are several types of heatsink in common use. Among the most popular are flat vertical plates, flat horizontal plates, and finned vertical extrusions. The equipment chassis often makes a convenient heatsink. The thermal characteristics of commercially produced heatsinks are normally specified by the manufacturer.

The accompanying photographs show a variety of finned heatsinks from the popular Redpoint range, together with some K_{s-a} ratings. From these the reader will readily appreciate that quite hefty heatsinks are required if temperatures are to be kept low, even for moderate power dissipation.

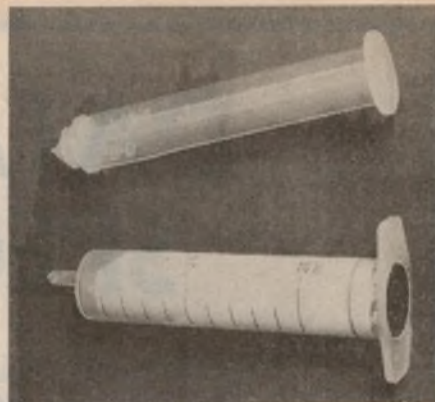The Redpoint range, by the way, is distributed by General Electronic Services Pty Ltd, 99 Alexander St, Crows Nest 2065. The most popular types from the



Silicone grease, packaged in a syringe-like tube for ease of application.



Redpoint TV4 heatsink. Thermal resistance is 17°C/W .

range are available through electronics retail outlets.

For many situations though, it is unnecessary to resort to the expense of commercial heatsinks. Adequate heatsinks can often be made by the hobbyist or home constructor out of sheet aluminium. Table 1 shows the K_{s-a} to be expected from various sizes of 18G aluminium sheet.

The figures quoted assume a central mounting position for the device and free air circulation around the heatsink. Other gauges may of course be used, the thinner gauges increasing the thermal resistance and the thicker gauges reducing it. For 24G material about 1°C/W should be added to the figures shown, whereas for 14G material 0.5°C/W can be subtracted.

Note that the ratio of width to height of the heatsink should not exceed 2:1.

The table also highlights the advantages of vertical mounting and putting a flat black finish on the heatsink. A word of caution about painting a heatsink, though. Make sure that the thinnest possible coating is used, as the paint can act as an insulator around the heatsink if applied too thickly. This will result in a K_{s-a} which is higher than the untreated aluminium, defeating the whole purpose of the operation.

Table 1: Thermal Resistance of heatsinks in $^\circ\text{C/W}$

AREA (sq. cms)	HORIZONTAL PLAIN	HORIZONTAL BLACK	VERTICAL PLAIN	VERTICAL BLACK
13	52	27	45	25
26	27	15	23	14
39	18	10.5	15	11
52	14	8.5	13	7.5
65	12	7	11	6.5
97	9	5.5	7.5	5
129	7	4.5	6.5	4
194	5.5	4	5	3.5
260	4.5	3.5	4	3.25
323	4	3	3.5	3

DATA PRECISION SPECIAL OFFER

Over the past four years, KENNEDY ELECTRONICS has been promoting the Data Precision range of digital instruments in the traditional areas of Research, Laboratories, Educational Facilities, etc. We have been successful, in fact so successful that Data Precision has enjoyed a growth rate far in excess of its targets. Some of this growth has stemmed from our sales.

Over the years, we have neglected you, the hobbyist and now for two months, we have a special offer on the three models listed below.

MODEL 245



- One of the most popular 4½ digit DMM ever made.
- It measures AC volts, DC volts, AC current, DC current and Resistance with .005% resolution
- Basic Accuracy $\pm .05\%$ with 100% overrange
- Line and battery operation at no additional cost
- PRICE \$260.00 Plus Sales Tax.

MODEL 175



- 3½ Digit Battery and Line Portable DMM
- 32 Range versatility: DC and AC volts, DC and AC Current, Hi and Lo excitation resistance
- Basic Accuracy 0.1% with 100% overrange
- True Laboratory performance and quality
- PRICE \$155.00 Plus Sales Tax. (Stand \$20.00 extra).

MODEL 5740



- 100MHz Multifunction Digital Counter
- 7 Digit Resolution (1 Part in 10⁷)
- Frequency 5Hz to 100MHz
- Single Period 1 to 200,000.0 Microsec.
- Period Average 999,999 to 99,999,999 Microsec.
- Totalizing and time Interval
- PRICE \$265.00 Plus Sales Tax.

KENNEDY ELECTRONICS PTY LTD

142 HIGHBURY ROAD, BURWOOD, VICTORIA 3125


TELEPHONE: MELBOURNE (03) 288 7100. SYDNEY (02) 439 3954
ADELAIDE (08) 223 2420. BRISBANE (071) 44 1259

Circuit & Design Ideas

Conducted by Ian Pogson

Interesting circuit ideas and design notes selected from technical literature, reader contributions and staff jottings. As they have not necessarily been tested in our laboratory, responsibility cannot be accepted. Your contributions are welcome, and will be paid for if used.

Video ball game sound addition

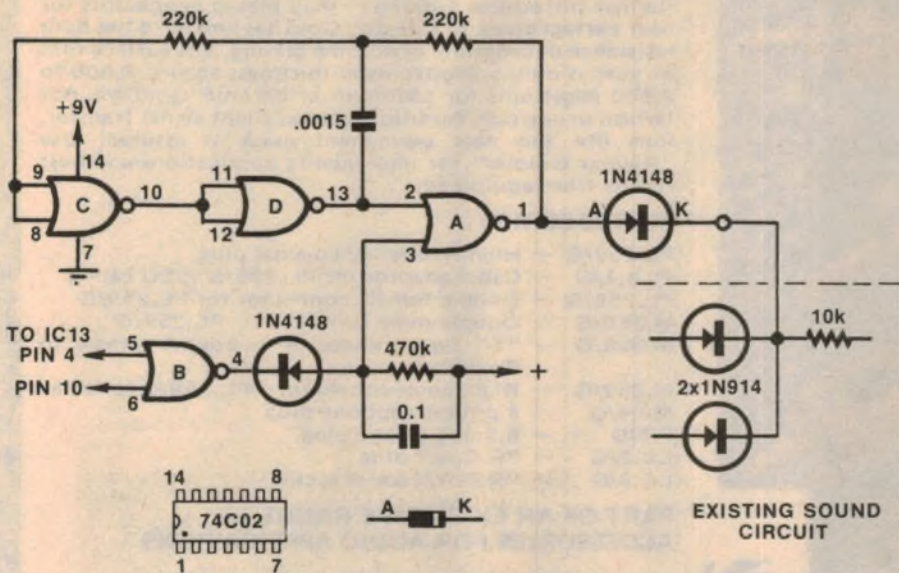

The Video Ball Game, described in May, 1976, and the add-on unit for sound, in November 1976, both work

very well, the sound providing added realism. The sound unit, however, did not incorporate a provision for sound

when the ball bounces off the top and bottom walls. The circuit shown here provides this facility without modification to either of the previously published circuits.

The oscillator (gates A, C, D) is gated on when gate B detects coincidence between the ball and either the upper or lower walls. This pulse is inverted and stretched by the RC network at the output of gate B. The diode ensures that the capacitor is charged only via the 470k resistor.

Constructional layout is not critical but the usual precautions regarding the handling of CMOS devices should be observed. Power should NOT be applied until pins 5 and 6 of the IC are properly connected to the Video Ball Game (pins 4 and 10 of IC13). I used 1/4W resistors and "greencap" capacitors.


(By Mr P. M. Jardine, 31A Queen Street, Caloundra, Qld 4551.)

RF operated aerial switch

This aerial switch offers good isolation and negligible attenuation without the use of high voltage bias supplies. The unit is simply connected into the aerial lead and no connections are made to the receiver or transmitter power supplies.

When an RF signal appears in the dummy load, a sample is picked up by the coil, rectified, and used to turn on the transistor circuit. The relay then changes to transmit. When the RF ceases the discharge of C produces a small delay so that the relay only switches at the beginning and end of a CW transmission. The switch to transmit is rapid and a 100uF x 15k produces a delay of two seconds when switching to receive.

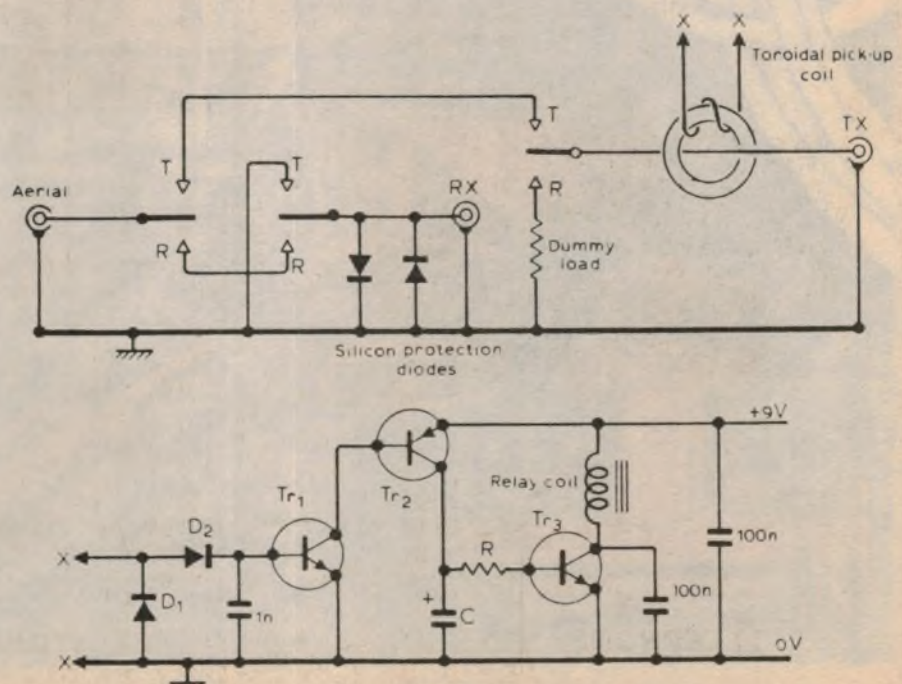The few turns on a toroid is sufficient for a pickup coil with an output of 1W. In the receive condition the circuit requires only 30uA so a battery can be left in circuit. With short leads and the unit mounted in a screened case, the circuit functions from 1.8MHz. The transistors are general purpose silicon types but D1 and D2 should be germanium. (By I. Braithwaite, in "Wireless World".)



GOLDIES

RALMAR INTRODUCES GOLDIES

Ralmar introduces Goldies — gold plated connectors for near perfect electron transfer. Gold has one third the bulk resistance of cadmium or chrome plating. The surface film of gold is only 5 angstroms in thickness against 1,000 to 2,000 angstroms for cadmium or chrome. Gold will not tarnish or corrode. Additional to excellent signal transfer, long life and near permanent usage is assured. Use "Ralmar Goldies" for high quality applications and best results from equipment.

IN THIS SERIES

- PL.259/G — High frequency co-axial plug.
- PLA.1/G — Cable adaptor for PL.259/G (58U cable)
- PL.258/G — Double female connector for PL.259/G
- M.258/G — Double male connector — PL.259/G
- M.358/G — "T" type connector — double female to PL.259/G
- M.359/G — Right angle connector — PL.259/G to female
- MP.4/G — 4 pin microphone plug
- P.4/G — 6.3 mm phone plug
- LC.2/G — "R.C.A." plug
- LC.3/G — "R.C.A." panel socket


PART OF AN EXTENSIVE RANGE OF ACCESSORIES FOR AUDIO APPLICATIONS



RALMAR AGENCIES PTY. LTD.

23 ATCHISON STREET, ST. LEONARDS, N.S.W. 2065
PHONES: (02) 439-4352, 439 6174 TELEX AA 22523

Door chime inhibitor

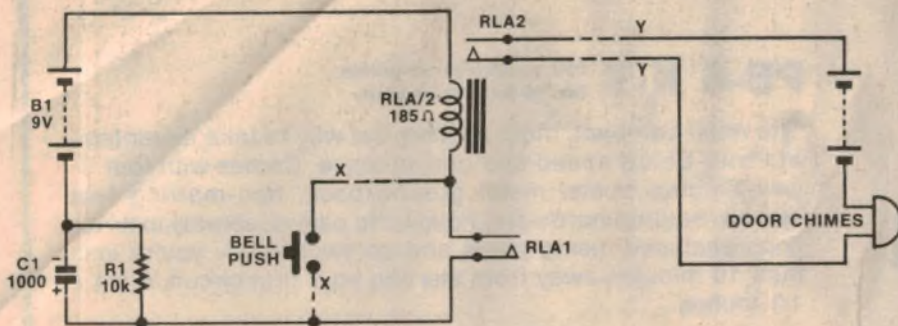

The unit to be described was designed to thwart the efforts of those bent on destroying the author's sanity. There are various ways of abusing door chimes—all of them annoying. Since most door chimes are loud enough to be heard with just one "ding-dong", the following circuit was devised and which allows only one "ding-dong". Further pressing of the button will give no results until about 20 seconds have elapsed.

The circuit consists of a general purpose relay, a resistor of about 10k and an electrolytic capacitor of about 1000uF. On pressing the bell-push, the relay is energised and the capacitor begins to charge up from the 9V supply. This charging current falls off as the capacitor charges and, typically, takes about one

second for the relay to drop out to its original state.

The relay switches the chimes via RLA2, which remains closed just long enough to give the initial ding-dong. If this time is too short or too long, a different value of electrolytic capacitor can be tried, or a different relay used. A higher value of capacitor will give a long ding-dong, while a smaller value will give a shortening effect.

Further operation of the bell-push will fail to work the chimes because the capacitor will be left in a charged state and cannot be charged further and so will not allow sufficient current to flow to energise the relay. Under such conditions the capacitor would take a long time to discharge sufficiently to render

the circuit operational again and so a resistor of 10k is placed across it.

If it is required to shorten or lengthen the time, a lower or higher value resistor could be used, but a more flexible arrangement is to use a small preset variable resistor of about 100k, which could be adjusted to give the desired time factor.

Another feature of the circuit is that even a very short press of the bell-push will give a full ding-dong. This is because a second set of contacts (RLA1) on the relay short circuits the bell-push while the relay is energised.


Basic operation may be checked, without connecting the unit to the chimes, by listening to the clicking of the relay. Final checking and setting up may be done by making the necessary connections to points X-X and Y-Y, as shown in the circuit.

(From "Everyday Electronics".)

Note on car battery monitor

In Circuit & Design Ideas for September 1977, the resistor values for the Car Battery Monitor were omitted. They are: R1, R3, 10k ¼W; R2, R4, R5, 1k ½W; R6, R7, 2.7k ¼W; VR1, VR2, 10k trimpot. My apologies for omitting this vital information.

Oscillators using 555 devices

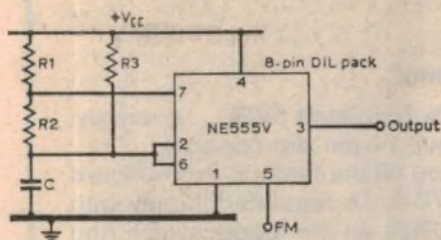

Many circuits have been published using the well known 555 timer IC as an oscillator, but nowhere does there seem to be any mention of the fact that under certain conditions 555 oscillators do not!

Generally, this malfunction seems to occur when the supply is switched on, although once persuaded to oscillate they carry on quite happily. A couple of years ago, after a colleague and I spent several days trying to get to the bottom of this problem, I telephoned the makers. They obviously knew about the problem, described the reason for the failure to oscillate, and suggested cures. The condition results from the design

of one of the voltage comparators and could be changed by a single change in chip layout; in fact the LM555 from National Semiconductor appears to incorporate this change but apparently those from other manufacturers do not.

The recommended cure by the makers was to put a diode or high-value resistor in series with the connection to pin 2 of the 8-lead DIL pack. Although the timing error drift of the basic 555 is quoted as 50ppm/°C, adding such a diode ruins the otherwise good temperature stability, not the most helpful of suggestions!

To retain the good stability and yet ensure a ready start, I have devised the circuit as shown. To ensure that the oscillator starts every time, R2 and R3 are chosen so that the potential at pins 2 and 6 exceeds 0.5V even when the transistor connected to pin 7 is saturated. The formulae for frequency of oscillation and duty ratio are, however, rather more involved than the simple ones quoted for the conventional circuit.

(By Richard J. Harris, G30TK, in "Radio Communication".)

RADIO DESPATCH SERVICES

869 GEORGE STREET, SYDNEY 2000
NEAR RAILWAY SQUARE

- Obsolete Project instrument bones, rectangular and sloping front.
- Lupe MkII Stylii viewer.
- DM95 C.B. Dynamic Microphone omni-Direct
- MH40 Magnetic C.B. Microphone holder.
- MH25 Screw on clip C.B. Microphone holder.
- HL1 Hot line filter C.B. car ignition suppressor
- ACR PS353 Sideband — 4 C.B. Power Supply, wide range of BNC & UHF Connectors for C.B. use.
- Universal 883E Electronic Digital Display Clock Radio
- Timeband Digital watches and alarm clocks.
- AD-TDK cassettes in 45 & 90 minutes
- National and Sanyo "AA" Penlite rechargeable cells. Special price \$1.65 ea
- Large range of relays and sockets
- Supertone walkie talkie sets ideal gift
- Car radio/cassette & car cassette units
- E.A. & E.T.I. project P.C. boards stocked

TV Aerials accessories and installation kits available for colour or black and white sets

Open Mon. to Fri 8.00a.m. to 5.30p.m.
Saturday 8.00a.m. to 11.45a.m.
TRUST R.D.S.

CONTINENTAL SPECIALTIES CORPORATION



PROTO-BOARD®

SOLDERLESS BREADBOARD SYSTEMS



PB-6 KIT

630 solderless tie-points
Six 14-pin dip capacity

The most compact, most economical way to take advantage of Proto-Board speed and convenience. Comes with four 5-way binding posts, metal ground/base, non-marring feet and all required hardware. Follow the easy assembly instructions enclosed, using pliers and screwdriver — you're less than 10 minutes away from starting your first circuit. 6 x 4 x 1.1 inches.

PB-102

1240 solderless tie-points
Twelve 14-pin dip capacity

For experimenters with needs for larger breadboarding capacity, we offer the PB-102. In a relatively compact space, it offers twice the capacity of the PB-6. Excellent for intermediate digital needs, more complex audio circuits and a wide variety of other projects. 7.4 x 4.5 x 1.1 inches.

PB-103

2250 solderless tie-points
Twenty-four 14-pin dip capacity

For advanced experimenters with larger projects in mind. Over 81% more capacity than the PB-102. Great flexibility is provided by 10 distribution buses and a roomy layout. PB-103 gives you three breadboarding sockets, bus strips, plus four 5-way binding posts, all mounted on a rigid, heavy-duty metal ground/base plate, with non-marring feet. Lets you build calculators, interfaces, complex switching circuits, networks, etc. with ease. 9 x 6 x 1.1 inches.



PB-203

2250 solderless tie-points
Twenty-four 14-pin dip capacity

Proto-Board flexibility plus built-in 1% regulated 5VDC, 1A supply, 2250 solderless tie-points. Twenty-four 14-pin dip capacity. The ultimate in proto-testing. Gives you all the famous Proto-Board features, plus a short-proof, fused 5VDC, 1A regulated supply with only 10 mV ripple and noise at 0.5A. Flick on the toggle switch (the pilot light indicates power), and you're ready to go on. Power is supplied via two of the four 5-way binding posts on the PB-203's top panel. PB-203 gives you enough capacity for large projects, plus the proper voltage for most digital ICs. 9.75 x 6.6 x 3.25 inches.



GENERAL ELECTRONIC SERVICES PTY LTD

99 Alexander Street, Crows Nest, NSW 2065

Telephone: 439-2488

Adelaide 42-6655; Brisbane 277-4311; Canberra 95-6811, 82-3581; Melbourne 598-9207; Newcastle 69-1222; Perth 25-5722.

How to charge nickel-cadmium batteries

The increasing use of nickel-cadmium batteries in tape recorders, calculators, flash units, etc, has created a growing interest in the characteristics of these batteries and, in particular, how they should be charged. This article discusses the charging requirements and describes a simple charger.

by PHILIP WATSON

A frequent request in our mail is for a charger "suitable for nickel-cadmium batteries"; usually without any additional information as to the voltage or capacity of the battery concerned. The implication seems to be that a charger for nickel-cadmium batteries needs to have some special characteristic and that, once this is provided, the charger automatically becomes suitable for any nickel-cadmium battery.

As is usually the case, there is an element of truth behind these ideas, but also a lot of misunderstanding. To put the record straight, let us take a brief look at the nickel-cadmium cell, and its charging requirements.

A nickel-cadmium cell, regardless of size, has a nominal voltage of 1.2 over most of its discharge cycle. When being charged, and at the prescribed rate, this will rise to about 1.5V at the end of charge. This will drop to about 1.3V after the charger is disconnected, and to 1.2V on load.

The first consideration, as with any battery, is the charging rate. If this is excessive, the battery can be damaged. The rule for nickel-cadmium batteries is quite simple: they should be charged at not more than the 10-hour rate. This is the rate which, in theory, should fully charge them in 10 hours.


A typical example is the "AA" size cell with a capacity of 450 milliamp-hours, which should be charged at 45mA. And, because the charging function is not one hundred per cent efficient, the actual charging time is 14 hours. This rule, a charging current equal to one tenth of the capacity figure for 14 hours, can be used for any nickel-cadmium battery.

The next consideration is more or less peculiar to the nickel-cadmium battery, although it is practised a good deal, largely by default, on other types of batteries. This is the requirement to provide a constant-current charging characteristic. As the term implies, this simply means that the charging rate

should remain essentially constant over the whole charging period.

When a battery is charged in this way the voltage will vary over the charging period. In any particular set-up the voltage can be used, with a little experience, to give at least a rough indication of progress of the charging cycle.

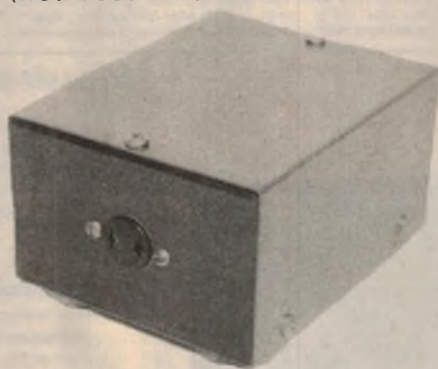The opposite to this characteristic (not recommended for nickel-



Several small boxes will suit the charger, that shown being the Davred No. 2. Note the two-pin polarised bracket.

cadmium batteries) is constant-voltage charging. As the term implies, it means maintaining an essentially constant voltage across the battery terminals for the whole of the charging period.

This method results in a varying current rate over the charging period. Again, it is possible, with experience, to judge progress of the charging cycle by the current flow.

The advantage of constant-voltage charging is that the charge rate is high at the beginning of the charge, when the battery is flat, and tapers off to little more than a trickle as the battery approaches full charge.

When the battery is flat most of the energy fed into it is usefully employed in changing the chemical composition of the plates, and very little is wasted as heat or gas — two conditions which

damage a battery.

As the battery approaches full charge a lesser proportion of the charging energy can be usefully employed, so it is necessary to reduce the charge rate to avoid excessive heat and gas. By charging at a (correct) constant voltage this reduction or "tapering" of the current occurs automatically. (This method is sometimes called "tapered charging".)

The main advantage is that the battery is charged in the shortest possible time, consistent with good battery life. It is particularly suitable for lead acid batteries and, in fact, the modern automotive regulator system simulates this condition, at least within the current capability of the generator or alternator.

On the other hand, as already noted, this method is not suitable for the nickel-cadmium battery. As with all batteries, there will be some temperature rise at the end of charge and, in the case of the nickel-cadmium cell, this causes the voltage of the battery to drop slightly.

Since the charge rate is a function, among other things, of the battery voltage, such a drop will cause an increase in charge rate. This will raise the temperature still further, cause a further voltage drop, greater charging current, etc, in a vicious circle or thermal runaway condition which can damage the battery.

In practice most simple chargers, particularly those used for large batteries, fall somewhere in between the constant-voltage and constant-current concept. Usually, it is sufficient to ensure that the charging rate at the end of charge is not excessive, after which its behaviour over the rest of the period is simply accepted.


Providing a constant-voltage or constant-current characteristic obviously involves something rather more elaborate than a basic charger circuit. Of the two, constant-voltage is probably the more difficult to provide but this is of little interest for this exercise.

The simplest way to provide a sub-



Digital Test Instruments

HEATHKIT
WESTON
ASAHI

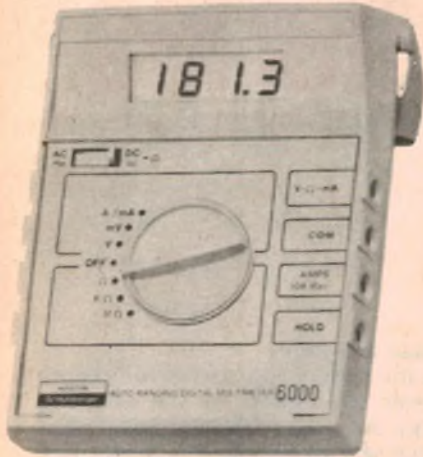

Model 6000 Autoranging Digital Multimeter

Standard Features:-

- Autoranging
- Long life Liquid Crystal Display
- Portable
- LSI microcircuitry
- Patented Dual Slope integration*
- More than 200 hours battery life


The Weston Model 6000 Autoranging Digital Multimeter combines the accuracy and convenience of automatic digital measurements and the economy and broad range coverage of conventional VOM's. This rugged, compact portable instrument is equally suited to bench measurements and field service applications. Two inexpensive 9 volt "transistor" batteries provide more than 200 hours of operation, and automatic circuitry warns of the need for fresh batteries during the final 8-10 hours of operation.

The sophisticated operating characteristics of the Model 6000 have been achieved at modest cost through recent technological advances. Laser-trimmed resistor networks are used instead of costly precision resistors, and the complex electronics required for the Model 6000 operating cycle have been implemented as custom LSI microcircuitry for minimum cost and optimum reliability. A specially-developed liquid crystal display employs new materials which eliminate earlier LCD failure modes, resulting in a long-life, high reliability display which yields highly legible readings in any practical work environment.

Model 6000 versatility is enhanced by the "Display Hold" feature, which allows a given reading to be retained indefinitely. Thus measurements in hazardous or crowded circuitry may be made with full operator attention devoted to probe placement and the probes subsequently withdrawn before reading the display. The "Hold" input may be controlled by an optional probe or user-furnished SPST switching. Other accessories are available for the measurement of DC voltages to 50 kV, R.F. voltage in the 0-30 v./10kHz-50MHz range, and high level AC currents to 200 amperes. Moreover, the 100 millivolt ranges are compatible with conventional switchboard shunts, and the 0-10 ampere range is ideal for monitoring current transformer outputs.

The calculator case styling of the Model 6000 permits maximum versatility and convenience. The carrying handle folds forward as a protective display cover, and may be folded fully back to serve as a tilt stand for convenient bench top viewing the color-coded range plate may be removed to provide access to the input fuse and batteries, as well as calibration adjustments. Routine operation requires only the selection of appropriate units of measure and AC or DC mode. Auto zeroing and autoranging circuitry eliminate other user adjustments for fast, convenient measurements at maximum accuracy.

Model 6000 \$299.00

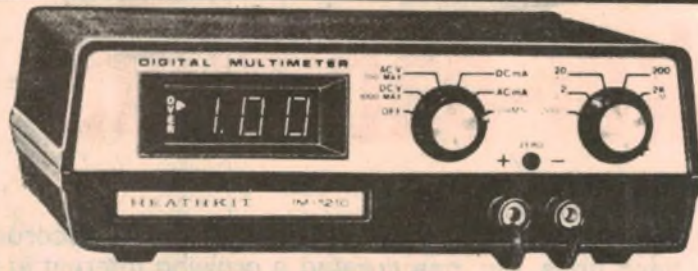

Heathkit Low Cost Bench Digital Multimeter

Here's a low-cost, high performance DMM that hams, hobbyists and service techs have been waiting for. Its full-function capability even includes AC voltage measurements up to 700 volts. Has four overlapping AC & DC voltage & current ranges and five resistance ranges. And it's hard to find better accuracy at a price this low: 1% on DC volts, 1½% on AC volts and AC/DC current, and 1½% on resistance. Lighted front-panel indicators show overrange, + and - DC voltages and current at a glance.

A solid-state design uses IC circuitry for a clear non-blanking 2½-digit display with automatic decimal positioning. Its ease of operation makes it a pleasure to use for both beginners and advanced technicians. The easy assembly makes it a great project for student electronics labs. And the exclusive Heath built in calibration standards are all that's needed for initial and periodic adjustments.

Features overload protection on all ranges, 240 VAC operation, isolated floating ground, attractive heavy-duty case to withstand rugged use, universal banana jack inputs for easy testing of all types of electronic equipment.

Kit IM-1210.

\$104.50

IM-1212 SPECIFICATIONS: Functions: DC volts, DC current, AC volts, AC current, Ohms. Ranges (Full-Scale): DC volts: 0-2, 20, 200, 1,000 V, DC current: 0-2, 20, 200, 2,000 mA; AC volts: 0-2, 20, 200, 700 V rms (50 Hz to 10 kHz); AC current: 0-2, 20, 200, 2,000 mA rms (50 Hz to 10 kHz); Ohms: 0-200, 2K, 20K, 200K, 2M ohms. Overrange: 25% on all functions, within maximum input limits. Maximum Input: 3 amperes into AC or DC mA, and Ohms (fuse protected) 700 VAC rms into Volts (except 2V range: 250 VAC rms), 1,000 VDC into Volts (except 2V range: 350 VDC). Input may be floated 1000 VDC (700 VAC) above earth ground. Resolution (Low Range): Volts 10 mV, Current 10µA, Ohms 1 ohm. Display: 2½-digit 7-segment, planar, LED (light emitting diode) with overrange and negative-input indicators. Accuracy (Full Scale, ±1 Digit): DC volts: ±1% DC current: ±1.5% AC volts: ±1.5% AC current: ±2% Ohms: ±1.5%. Input Impedance: 1 megohm on all voltage ranges, 2.1-volt drop maximum on current ranges (except 2.5-volt drop on 2,000 mA range). Sample Rate: Line frequency. Display Settling Time: Less than 10 seconds on DC volts and DC current, and less than 3.0 seconds on AC volts, AC current, and ohms; to within 5 counts. Power Requirements: 200-270 VAC 50 Hz, 8 watts. Fuse Requirements: Input 3AG 3-ampere Line (¼-ampere slow blow for 240 VAC). Dimensions (overall): 3.00" H x 8.69" W x 10.54" D (7.62 cm high, 22.07 cm wide, 26.77 cm deep). Weight: 3.3 pounds (1.5 kg).

NOTE: The Multimeter requires a warmup time of 30 minutes to meet specifications.

Model MV-550 Digital Tester

Outline

This is a digital tester incorporating dual slope integration. It has multiple-purpose functions. DC voltage and current, AC voltage and current, and resistance can be measured over a wide range. The use of CMOS L.S.I. has resulted in a compact, light weight tester with low power consumption, characterized by high performance, reliability and low price.

Features

- Wide applications**
The instrument has wide application in the measurement of DC, current, voltage, and resistance, and AC current and voltage.
- Automatic polarity**
Input signals can be measured irrespective of input polarity.
- Easy handling**
Range selection and operation are similar to those of analog circuit testers. The instrument utilizes two input terminals common to each measurement.
- Unlimited instrument attitude**
The instrument is so designed that instrument attitude has no effect on performance.
- High accuracy and low cost**
- Compact and light weight**
The instrument utilizes CMOS L.S.I. in the circuitry and LED (Light Emitting Diode) for scale reading. This design concept reduces power consumption, and provides a compact, light-weight instrument with high reliability.

Model MV-550 \$224.00



ORDER BY COUPON NOW OR COME TO OUR SHOWROOM

Please send me the kit / unit of my choice. My cheque for \$ _____ is enclosed plus \$2.50 for package and post.

Name

Model 6000

Address


Kit IM-1210

..... P / Code

Model MV-550

Send to: W. F. Heathkit Centre
220 Park St., South Melb. 3205. Phone: 699-4999

WF 911/77

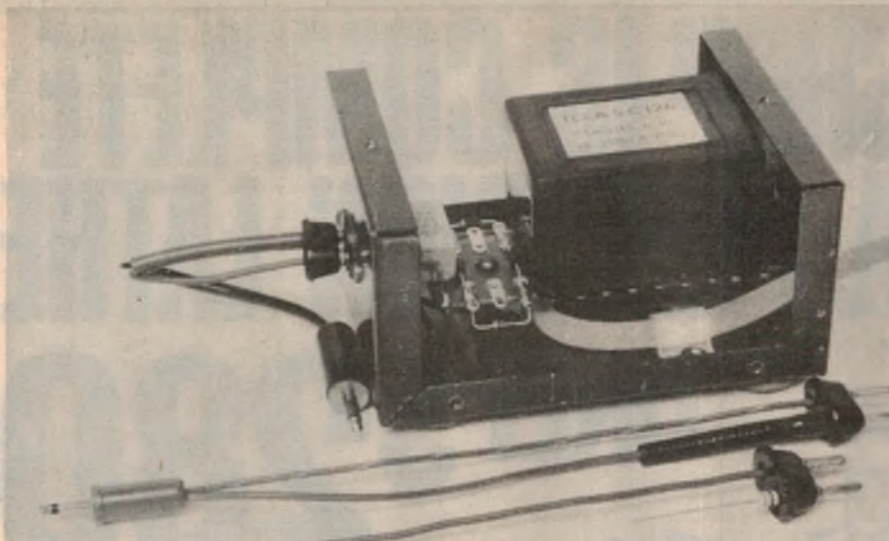

The simple layout of the charger is obvious in this picture. A battery lead is plugged into the charger and a second one is alongside it. A third one, partially completed, shows how the resistor is accommodated in the plug.

stantially constant current is to start with a charging voltage a good deal higher than we require, then use a lot of resistance in series with this supply to control the current. With a lot of resistance in circuit minor variations in battery voltage (which also oppose the flow of current) become relatively insignificant.

The objection to this arrangement is the waste energy, in the form of heat, which must be dissipated. To provide a reasonably constant current flow we need to start with at least twice the voltage required, which means that we will waste as much energy heating the resistor as we will use to charge the battery.


This problem is not serious for small batteries, such as the "AA" type used in calculators, small flash guns, etc. Four such cells would require approximately 6V to charge them and if we provided twice this and developed 6V across the dropping resistor, this latter would have to dissipate less than 0.3W.

Even a tape recorder using, say, five "C" cells is still a reasonable proposition. On the basis of a 7.5V battery, a charge rate of 180mA, and 7.5V developed across the resistor, the latter would still dissipate only a little over 1.3W.

The next size cell, the "D", needs to be charged at 400mA and, assuming a similar number of cells, would call for a series resistor dissipating 3W; enough to be embarrassing in many configurations.

Fortunately, most of the interest in nickel-cadmium applications involves the smaller cells, making it relatively simple to provide a satisfactory charger.

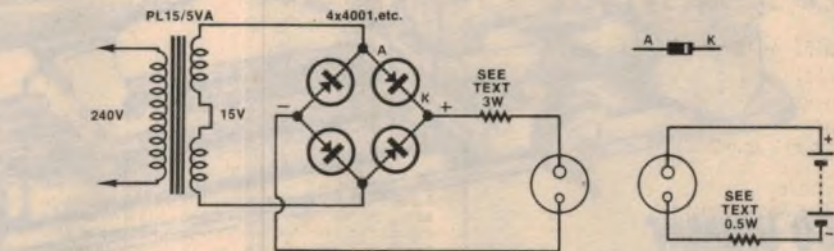In practice, it is possible to design a charger which can be made quite versatile and able to serve a wide variety of cell sizes and combinations. This is done by budgeting, initially, for the highest voltage and highest current likely to be required; say five "C" size cells (as used in a typical tape recorder)



 Ni-Cd BATTERY CHARGER

2/BC/-

The circuit is extremely simple and calls for very little comment. Almost any power diodes with a 1A or higher rating will be more than adequate, even when using the larger transformer to charge quite large cells.

needing 7.5V at 180mA.

Such a charger could then be used to charge any battery of fewer or smaller cells up to, and even beyond, the five cell arrangement. All that is required is to increase the current determining resistance until the required charge rate is provided.

There are a number of ways of arranging this in practice. One method, used commercially, is to provide a multi-position switch giving a number of pre-selected charge rates, typical of commonly used cell sizes.

Another arrangement, which the author has used, is to provide a separate charging lead for each appliance or battery pack, this lead containing the necessary additional resistance to suit the battery concerned. The charger is fitted with a two-pin polarized socket, into which the appropriate lead is plugged. The other end of the lead carries whatever plug is needed for the particular appliance and, if necessary, can be tagged to identify the appliance.

To reduce the physical size and dissipation of the resistor in the lead, part of the total resistance can be inside the charger. Normally, this would be the amount required for the largest battery. In most cases this will keep the individual lead resistors within the ½W

rating, and facilitate fitting them to one or other of the plugs.

The charger we are about to describe is based on these ideas, and is built around components readily available on the local market. It can use one of several transformers designed to deliver 15V AC at between about 300mA and 1A. On the basis of a five cell battery (7.5V at full charge) this will provide at least twice the required voltage.

The transformer we actually used was the Ferguson type PL15/5. This has two secondary windings, each delivering 7.5V at 330mA. They can be connected in parallel to provide 7.5V at 660mA, or in series to provide 15V at 330mA. We used the latter connection.

An alternative transformer is the type DSE2155 from Dick Smith. This has a variety of tappings from 6.3 to 15V at 1A. It is physically a little larger than the Ferguson model, but would still fit in the case we selected. The higher current rating could be an advantage where larger cell sizes, such as the "D", were involved.

The case can be any one of several simple two-piece sheet metal boxes which are readily available. We used one from Davred, known as their No. 2 box, which measures 105mm x 82mm x 54mm. Other boxes having similar


PARTS LIST

- 1 transformer; 240V primary, 15V secondary. (Ferguson PL15/5, DSE 2155, or similar.)
- 1 metal box, approx 100mm x 80mm x 55mm (Davred No. 2 or similar)
- 1 miniature tag strip, 13 pairs of tags
- 4 silicon power diodes, 1A
- 2 ½in spacers, tapped ¼ Whit
- 1 2 pin polarised plug and socket (McMurdo or similar)
- 1 3W resistor and other resistors, as needed. See text.
- 3 core power cable, cable clamp, 3 pin power plug, hook up wire, nuts and bolts, rubber feet, etc.

NO WORKSHOP IS COMPLETE WITHOUT A PRECISION LATHE

ONLY \$280


SAVE \$35

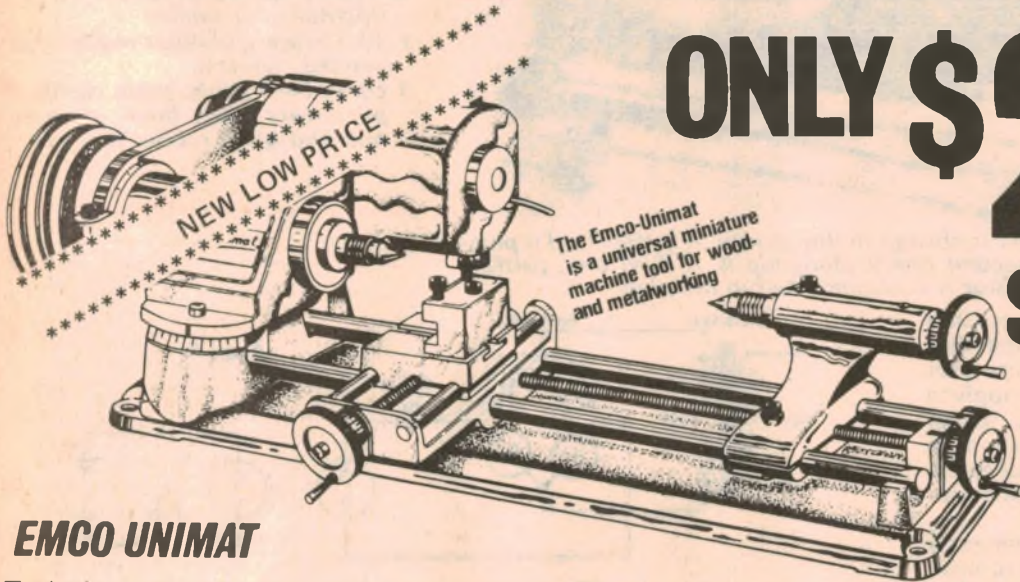

NEW LOW PRICE

The Emco-Unimat is a universal miniature machine tool for wood- and metalworking

SUPPLIED WITH THESE EXTRAS

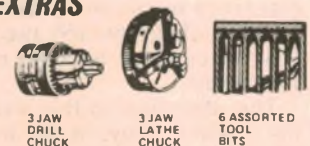


EMCO UNIMAT

The basic unit alone together with the motor and attachments (a 3 jaw lathe chuck, a 3 jaw drill chuck and 6 assorted tool bits which are supplied) permits a large number of operations irrespective of whether the component is made of balsa wood, tool steel or one of the modern plastics. The Unimat will give you the professional finish and accuracy you want — at a fraction of the cost of a 'normal' lathe. And you don't have to have a spare room for it — the Unimat is small enough to fit in anywhere!
 Cat. T — 6010 ... Including Lathe Chuck, Drill Chuck, Basic Lathe and Six Assorted Tool Bits\$280

THE HOBBY KIT FOR THE ENTHUSIASTIC HOBBYIST

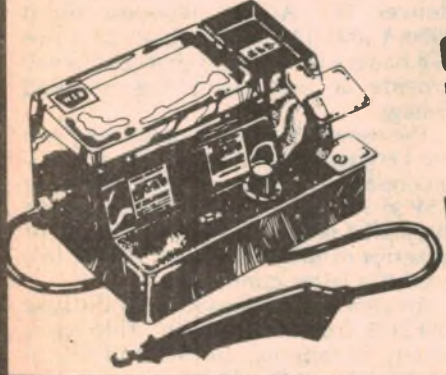CONVERSION KIT to give your Unimat even greater versatility !
 Includes 3 GRINDING WHEELS — GRINDING WHEEL GUARD — VERTICAL COLUMN AND ACCESS FOR DRILLING AND MILLING — SET OF 8 MILLING AND DRILLING TOOLS.
 Cat. T — 6011\$99.00 **\$99**



SAVE \$15
~~\$125~~
NOW ONLY \$110

The hobby centre kit is everything the hobbyist or model-maker needs. Double insulated for safety. Speed control for versatility. No hobbyist should be without this machine.

COMPLETE KIT INCLUDES:—Bench Grinder and Disc Sander — 5" x 6 1/2" x 9" compact base unit with built in storage area. 3" 60 Grit High Speed Grinding Wheel — Tool Rest — Eye Shield — Spark Arrestor — Small Parts Tray — 2" Sanding Disc Plate — 3 assorted 2" Sanding Discs — Calibrated Adjustable Tool Rest — Allen Wrench. High Speed Hand Grinder With 36" of Flexible Shaft — 2 Double Ended Wrenches. 39 Piece Accessory Kit — 9 Mounted Emery Wheels — 1 Dressing Stone — 2 Hi-Speed Rotary Files — 2 Mounting Arbors — 2 Felt Pol. Wheels — 1 Drum Sander — 3 Sanding Drums — 1 Polishing Wheel — 10 Sanding Discs — 1 Drill Bit — 2 Nylon Brushes — Plastic Carry Box. 40 Page "HOW TO DO IT" Book.
 Cat. T — 6020\$110.00

DICK SMITH ELECTRONICS GROUP

PARRAMATTA — 30 Grose St, Parramatta.
 SYDNEY — 125 York St, Ph. 29 1126
 BANKSTOWN — 361 Hume Hwy, Ph. 709 6600
 GORE HILL — 162 Pacific Hwy, Ph. 439 5311
 MELBOURNE — 399 Lonsdale St., Ph 67 9834
 MELBOURNE — 656 Bridge Rd, Richmond Ph. 42 1614
 BRISBANE — 166 Logan Rd, Buranda. Ph. 391 6233

MAIL ORDERS:
 Box 747, Crows Nest, NSW. 2065. Ph. 439 5311
SHOP HOURS
 Mon to Fri: 9AM — 5.30PM
 Sat: 9AM 12 noon
 (Bris. Sat: 8.30AM — 11.30AM)

POSTAGE/PACKING CHARGES		
ORDER VALUE	CHARGE	
\$5	\$9 99	\$1 00
\$10	\$24 99	\$2 00
\$25	\$49 99	\$3 00
\$50	\$99 99	\$4 00
\$100 or more		\$5 50



ALSO AVAILABLE AT DEALERS THROUGHOUT AUSTRALIA

dimensions should be quite suitable.

The Ferguson transformer is designed for printed board mounting, but a printed board could not be justified for a simple project like this. We used a short length (13 terminals) of 28mm wide tag board. The tags are spaced about 6mm apart and about 19mm between the rows. These dimensions are fortunate, because they match up almost exactly, in both directions, with the terminal pins on the transformer.

All that is necessary is to bend the two inner terminal pins of the secondary windings flat against the transformer case and lying beside one another. Soldered together they complete the series connection and, at the same time, allow the transformer to lie flat on the tag board. All the other pins will pass through the tag board holes and can be soldered.

The tag board is supported on two 1/2in long brass spacers, tapped 1/8in Whitworth, secured to the bottom of the box. The length of the strip is such that four pairs of tags protrude beyond the transformer at the secondary end. These support the four diodes in a bridge configuration, and the main series resistor.

The power cable is secured with a plastic cable clamp and passes through the box via a grommited hole. The earth lead (green, or green and yellow) is terminated on a solder lug clamped under the spacer at the primary end of the transformer.

The output is via a 2-pin polarised plug and socket, such as the McMurdo type which we used. Where resistance has to be added to the lead, a 1/2W resistor may be partly buried in the hole in the base of the plug. A short length of insulating tubing can be pushed over it to protect its junction with the lead.

(To facilitate fitting plastic tubing over the resistor, try soaking the tubing in lacquer thinners for a few hours. This tends to both soften and expand it. After fitting it will shrink to its normal size as it dries.)

Many appliances have a socket intended either to permit charging or to permit a power pack to be used. In the latter case the internal battery is normally disconnected when the plug is inserted, but it is usually a simple matter to bridge the appropriate terminals on the socket so that the battery remains connected, and can be charged via this socket.

(Note: It is risky to operate the appliance in this mode. If the battery should be accidentally disconnected, due to a faulty contact, an excessive voltage could be applied to the appliance, with possible damage.)

The amount of resistance needed for any particular battery can be determined experimentally, but a preliminary calculation will help, and can be quite accurate. Using Ohm's law, simply divide the voltage to be

RESISTANCE TABLE

Size	Capacity	Charge Rate	1 cell	2 cells	4 cells	5 cells
N	150mAH	15mA	900	800	600	500
AA	450mAH	45mA	300	270	200	166
Sub C	1.2AH	120mA	112	100	75	62
C	1.8AH	180mA	75	66	50	42
D	4AH	400mA	33	30	22	18

The figures in the four right hand columns indicate the total resistance (in ohms) required for a particular combination of cells. As indicated in the text some of this resistance is best located inside the charger. Note that not all cells of the same physical size have the same capacity or charge rate. In all cases the instructions on the cell should be followed.

developed across the resistor by the charging current required. For example: five "C" cells require 7.5V at 180mA. Assuming a supply voltage of 15, 7.5V needs to be developed across the resistor. Divided by 0.18A, this gives 42 ohms. Assuming this was the largest battery to be charged, this resistor would be fitted internally and should have at least a 3W rating.

To charge 4 "AA" cells at 45mA add 150 ohms in the external lead or, for two cells, add 220 ohms. An even smaller battery is a very small 9V type,



An alternative transformer, available from Dick Smith. It would be suitable for charging rates up to 1 amp.

similar to the type 216 carbon-zinc battery. This can be readily accommodated and requires a lead resistor of 620 ohms.

For those who may be dubious about their ability to perform these calculations we have prepared a table showing calculated values for typical cell combinations.

These values should be checked experimentally and, if any small adjustment is required, this is best done when the battery is fully charged. Variation in current over the charging period should not be more than about 10%.

Finally, the box should be fitted with four rubber feet to protect any surfaces on which it may be placed.

For those not familiar with battery charging in general, or nickel-cadmium types in particular, it will help to get the "feel" of the battery and charger if the voltage is monitored during charging, at least for the first few times the battery is charged.

The voltage should rise slowly over the charging period and the battery may be regarded as fully charged when it reaches between 1.4 and 1.5 volts per cell, or when the voltage shows no appreciable rise over a period of, say, one hour. This provides a useful indication where the exact condition of the battery is uncertain when it is placed on charge.

In fact, the voltage may actually fall slightly, as already explained. This may be discernable on an ordinary voltmeter if the pointer is well up the scale, but calls for careful observation. An expanded scale voltmeter is better, while a digital voltmeter is better still. But, even without these refined versions, voltage measurement is still a most useful guide to the progress of the charge.



**The
NEW
American
900 Series
ASTATIC
MICROPHONES**



Outstanding for —

- ☆ Professional entertainers.
- ☆ Stage & Studio
- ☆ Broadcasting.


950
Extended linear response

952
Contoured response creating that desired articulation

AVAILABLE IN BOTH LZ & HZ

NOMIS ELECTRONICS PTY. LTD.
689 SOUTH ROAD,
BLACK FOREST SA (08) 293 4896
And these suppliers

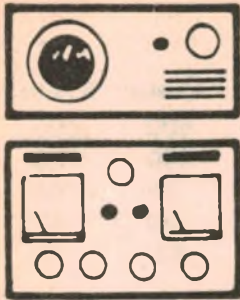N.S.W. Martin de Launay, Sydney—29 5834; Newcastle—2 4741; Wagga—21 4644; Wollongong—28 6020; QLD Martin de Launay Brisbane—52 8467; SA Neil Muller Adelaide—74 1162; Mt Gambier, SESB Services—25 5970; WA Atkins Carlyle Perth—22 0191; NT Veneman & Wyatt Darwin—81 3491; VIC JES Electronic Components Melbourne—88 5282



The Serviceman

Detecting intermittents needs time and patience

Taking things for granted is probably the most common single mistake of which we, as servicemen, are guilty. And, while it is easy to be wise after the event, it is one of the lessons which experience should teach us. My main story this month is a typical example.

The story concerns a valve type monochrome TV set, in which the main complaint was intermittent rolling, mainly on Channel 2, according to the customer. (I always treat such information with a certain amount of caution; in many cases the trouble appears to be worse on one channel simply because that is the customer's favourite channel!)

More important was the information that the set would sometimes go for days, or even weeks, without a sign of trouble. Then it would go all temperamental and slip a frame every few minutes for hours at a time — not a situation calculated to encourage relaxed and enjoyable viewing.

Naturally this was no job for the customer's lounge room. Intermittent faults need all the facilities which can be provided in the workshop, including time; time to let the set run and for the fault to show up.

On the bench the set decided it was not going to misbehave; a not uncommon situation with intermittents. So I simply set it up at one end of the bench and made a few routine measurements while it was working correctly. Such information can be vitally important when the fault does appear.

This set used one half of a 6Y9 twin pentode as the video amplifier, with the other half as the gated AGC stage. Signals from the plate of the video amplifier went to the cathode of the picture tube and to the sync separator stage, a 6CS6.

I concentrated on this latter stage, making voltage measurements and CRO pattern observations, and comparing these with the maker's circuit data. As far as I could see, everything was as it should be so I left the set running with the CRO connected to the sync separator input and a VTVM on the plate.

The set ran for several hours without missing a beat, while I busied myself with other jobs. Then it started to slip frames, and I dropped what I was doing

and made a quick check on the CRO and meter.

The meter wasn't much help, but the CRO indicated that the sync pulses were varying in height quite significantly and, when they dropped low enough the picture would start to slip a frame, or even roll continuously.

Before I could do much more the fault vanished again, and nothing I could do would restore it. So I simply moved the VTVM to monitor the plate of the video amplifier stage, and went back to the other jobs.

Over the next couple of days the fault came and went in its own capricious manner, with yours truly taking every opportunity to narrow down the fault area. It didn't take me long to suspect the video amplifier. For one thing the CRO indicated that the sync pulses coming out of it were quite unreliable when the fault was present, though they remained constant at the grid. At the same time the voltages around this stage were kicking up and down in a quite unpredictable manner.

The first thing I did was to replace the valve, choosing a time when the fault was present. The fault vanished as the new valve warmed up, but I have been caught too many times to put much faith in such an occurrence. Sure enough, some time later the fault appeared again, ruling out that possibility.

Convinced that it was in the video stage I began a systematic examination of all associated components — screen resistor, cathode resistor, associated bypasses, and so on. None of this was to any avail; as far as I could test them all the components were above suspicion, yet I was convinced that the fault was in this stage.

Having reached such an impasse, I just sat and looked at the wiring, hoping for some inspiration. And that is just what I did get. This set was one of the relatively few designs, during the valve era, which used printed boards and the 6Y9 socket was an appropriate type

mounted on the board.

I began to examine it closely and, when I came to the screen pin of the socket, I thought I detected a faint dark ring between the pin and the solder. A check with a jeweller's glass confirmed my suspicion; the pin was sitting in a little hollow of solder which barely touched it in one or two places, but had obviously never wetted it.

I confirmed the situation by exerting gentle pressure on the pin with an insulated prod and established that I could make the fault come and go at will. That was proof enough, and I knew that another intermittent was about to bite the dust.

In fact, I kept the set for another day, just to make sure, but there was never any real doubt in my mind. When it ran the whole day without even blinking, I returned it to the customer. A follow-up call a couple of weeks later confirmed that it was still behaving.

In some ways this fault was almost a routine one, as intermittents go, but there are a few points worth noting. One was the length of time that the set had been in the field, probably 10 years at least, during which time it performed without trouble until the last few months. This is not unusual with dry joints, in fact they almost invariably show up in old equipment and, I suspect, probably result in a significant number of such old units being written off as having reached the end of their useful life.

Another point is that we invariably get caught when we take too much for granted. How often do we trace a voltage up to a socket and take it for granted that, from there on, all is well. Most times it is, of course, but when all else fails don't forget that sockets, of all kinds, can fail.

This next story concerns a technician employed by a colleague. He passes it on in the hope that it may avoid a similar situation and, perhaps, a fatality.

The technician concerned made a house call to a colour TV set, the complaint being no picture or sound. He removed the rear cover from the set, checked an appropriate point for HT, and found there was none. Suspecting the switch mode power supply, he decided to try a spare one which he

carried as part of his kit. He unplugged the leads, removed the protective hardware, and slid the power supply out of its casing.

The next instant he received a terrific "belt" and the power supply fell from his grasp onto the lid of his toolbox, printed side downwards. There was a bright flash and a loud bang, as the printed board made contact with the toolbox lid. The whole thing happened in a split second.

After regaining his composure, the technician examined the power supply for possible damage. The first casualty was a 2A fuse in the line going from the rectifiers and filter capacitor to the collector of the chopper transistor. He also noticed that several components in that area had blackened soldered joints with most of the solder removed.

So he set to work cleaning and resoldering the suspect joints on the board. After completing this, he again tried the supply in the set, and this time it worked.

Whether the blown fuse was the original cause of the trouble, or whether it blew when the filter capacitor discharged, he will never know, nor will he know if another fault, such as a dry joint, was the real cause of the trouble, as this incident happened about a month ago, and the set is still working. One thing is for sure however: the technician is a sadder but wiser man for his experience.

This illustrates the dangers involved in careless handling of these units. The main filter capacitors can range in value from 200 to 400 μ F and can be charged to something like the peak of the mains voltage: typically 325V.

Years ago, when I was a young lad in a factory, it was customary to play practical jokes with charged capacitors. By a kind of unwritten law we limited our activities to the 0.5 μ F variety; they were quite large enough to deliver an unpleasant shock, yet not so large as to involve any kind of risk.

In spite of the unwritten law, however, I was caught a couple of times with 8 μ F electrolytics and anyone who has experienced it will confirm that they can deliver a very nasty wallop. Yet this would be a mere tickle compared with the jolt from even 200 μ F which, in the right circumstances, could possibly be fatal.

Before working on these power supplies, discharge the main filter capacitors through a resistive load. A unit made from a household electric light globe, a suitable lampholder and a pair of well insulated test prods is satisfactory. Above all — be careful. Your first slip may well be your last.

And, to finish off, here is another brief thought on the matter of safety.

A colleague rang me the other day in a mild panic. It seemed that he had bought a roll of three core power cable, with the idea of replacing some

appliance cords that had seen better days, only to discover that the conventional red, green and black wires had been replaced with blue, brown, and green with a yellow trace.

"I've heard about an alternative colour code," he confided "but this is the first time I have had to use it. Just what are the equivalent colours?"

I had to admit that I couldn't quote them off the cuff either, but I seemed to remember that I had filed a pamphlet issued by the NSW Electricity Commission. Sure enough, a few minutes' digging brought it to light and I was able to pass the information on to him.

But do you know what the alternative colours are?

In fact, they are sufficiently logical to make them reasonably easy to remember, if one really puts one's mind to it. Fairly obviously, the green with a yellow stripe, replaces the old plain green. The old red is replaced by the colour which most nearly resembles it, i.e., the brown, and the old black is replaced by the colour closest to it — the blue.

Also, it appears that there is a variation on the pattern for the earth lead. In some cases the yellow stripe is straight, in others it has a spiral pattern. Either arrangement is correct.

So there it is and you had better make a note of it; it looks as though progress (?) is catching up with us.

New!

Multiform AudioLarm

Who could ask for anything more...

You asked for it, an electronic audible signal for every need. Created by Floyd Bell Associates Inc. (USA), these units offer continuous tone, beeping and warble alarm modes via the proven reliability of solid state circuitry.

Audiolarm is a rugged, compact, inexpensive audible alarm primarily designed for the volume OEM market.

Nine standard models are available from stock, each backed by the fail-safe reliability of all Floyd Bell products.

Operating voltage ranges are 3-16V, 5-16V and 5-30V.

Terminals are either colour coded wires, quick connect or printed circuit, while mounting is simplified to the extreme with permanent, self adhesive washers on some models.

New Multiform AudioLarm backed by C&K reputation... consider the advantages.




Four housing configurations.
Four mounting styles.



Three terminal systems.
Three voltage ranges.
Three alarm modes.



Two body depths.

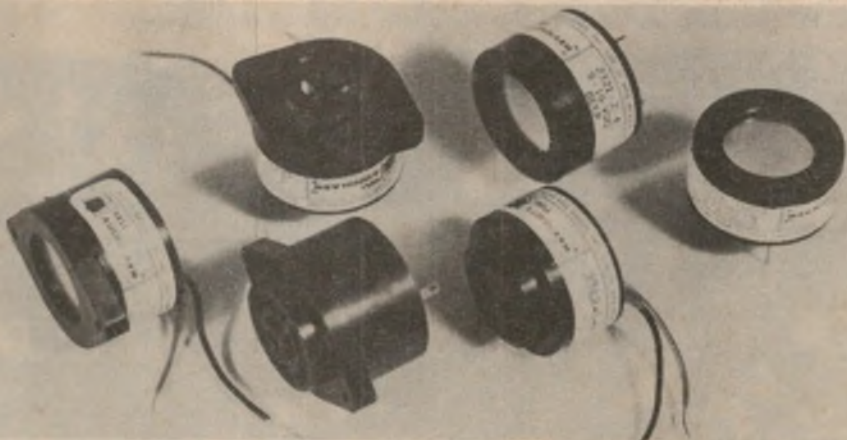

C&K Electronics (Aust.) Pty Limited

Office 2/6 McFarlane Street Merrylands NSW 2160
PO Box 101 Merrylands 2160 Telephone 682 3144

Agents: Melbourne 885282/Adelaide 269 2544/Brisbane 36 1277/Perth 687111

Obligation-free and comprehensive data is yours for the asking.

Electronic scanner

In order to overcome the mechanical problems associated with rotating loudspeaker systems for electronic organs, we have devised this all-electronic device for simulating both the fast and slow speeds usually provided with the mechanical systems.

by IAN POGSON

Over the past couple of decades or so, the electronic organ has gained tremendous popularity in private homes as well as its increasing use in public halls and churches. However, a great majority of electronic organs generate the tones from either one master oscillator, or 12 top octave oscillators — and then divide down with mathematical precision to all the lower octaves. Because of this the sound can be rather bland and uninteresting.

By contrast, every note from a pipe organ comes from an individual pipe, toned to its correct nominal frequency. No matter how well the tuning is done there are slight errors, due to the tuning procedure itself as well as changes in weather and other conditions. Rather than being a problem, provided that the errors are not too great, this situation gives a sound with subtle multiple random beats. This is generally

pleasing to the ear and adds considerable interest to the music produced on the particular instrument.

In order to remedy the deficiency of tonal interest in electronic organs, manufacturers have resorted to a number of different methods. In a few cases, the makers have elected to use a separate oscillator for every note. However, with this system, there may be upwards of 60 separate oscillators and when tuning becomes necessary, the task is a formidable one.

Apart from this approach, other techniques used include artificial reverberation, electronically produced vibrato, and some type of mechanically arranged rotating loudspeaker or reflector system.

It is the mechanically rotating loudspeaker system which claims our particular attention here. This system is generally arranged by adjustment of an


electric motor and pulley drive arrangement to give two speeds. The higher speed gives about seven revolutions per second, or a little over 400 revolutions per minute. The low speed is often about one tenth of this figure, or about 40 revolutions per minute.

The higher speed gives a deep throbbing tremolo effect, often associated with the theatre organ of years gone by. The low speed is somewhat more subtle in its effect and is inclined to give the illusion of the tones being slightly off precise tune, together with that "rolling" sound which some of us have experienced when in some of the large cathedrals in Europe and elsewhere.

Suffice it to say that either effect can be very useful when associated with the appropriate type of music. Having established the desirability of a system giving these effects, as borne out by the fact that very large numbers of electronic organs have been fitted with these devices in the past, let us take a closer look at the subject.

If your organ is fitted with a rotating speaker system, well and good. However, there are some organs which are not so fitted and the owner may wish to add one of these devices. There

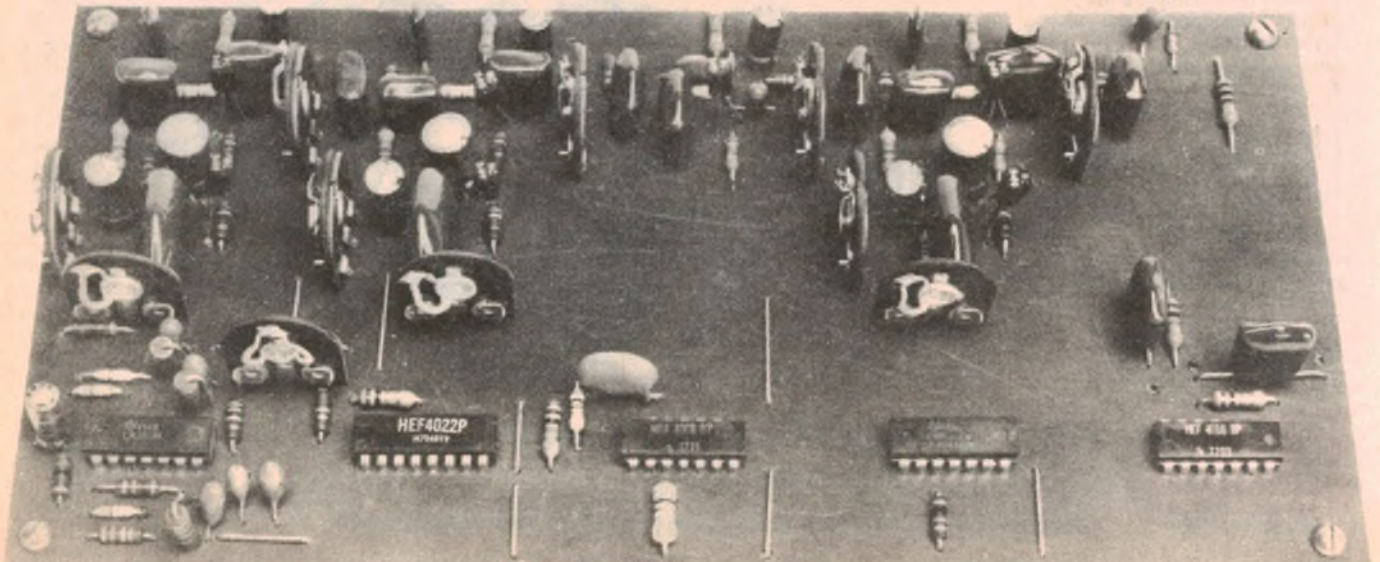A single PC board accommodates the complete circuit of the scanner.



for organs

is also the second situation where an organ may or may not be fitted with a rotating speaker system, and the owner may wish to provide an external "tone cabinet" for one reason or another. He may wish to have a rotating speaker system included in the external cabinet.

In either case, without going into details of the construction of an external cabinet, with its amplifiers and speakers, one is faced with the need to make up a largely mechanical device, with its need for perhaps a couple of suitable electric motors, pulleys and the necessity to change from one speed to another. Quite a daunting prospect, coupled with the fact that unless the mechanics are very good indeed, when in operation there will be an unacceptable amount of rumble and other noise.

Another characteristic which generally accompanies the mechanical rotating speaker is the rather lengthy time it takes to change from one speed to the other. This has been exploited in some kinds of popular music but in the main, it is a feature which most of us could do without.

For a couple of years or so, I have been thinking over the idea of simulating the rotating speaker effect by electronic means. Some preliminary experiments were tried, using electronic switching of three or four speakers sequentially, from the output of an amplifier. These were not very successful due to the high audio power levels involved. An alternative seemed to be to do the switching or whatever at low level and have as many amplifiers as speakers. At first sight this seemed to be a rather expensive way of doing it and there the matter rested.

Just recently, the idea was raised again and while it still seemed rather extravagant to use a number of audio amplifiers, it also still seemed to be a feasible way of approaching the problem. Talks with Editor Jim Rowe and David Edwards resulted in a number of ideas being put forward for trial. After culling out those which did not measure up, the idea of doing the whole circuit along digital lines was investigated at some length.

In short, the basic scanning system proved to be very successful but there were difficult problems associated with using digital techniques for the actual

audio modulating process. It could have been done no doubt, but the complexity appeared to be getting out of hand.

As a result, we reverted to the idea of using conventional analog techniques for the modulating process. This explains the "hybrid" arrangement of digital and analog circuitry to achieve our purpose.

Initially, the idea was to use four channels with a 90° modulation shift from one to the next, sequentially, thus giving a similar effect to a rotating speaker. This would be fine but if we could use only three channels with a 120° shift instead, still achieving the wanted result, then the saving would be substantial. Checks showed this to be satisfactory and so this is the method which we have adopted.

Let us look at the circuit to see how it is done. One section of an LM3900 quad amplifier is wired as a two speed oscillator. The square wave output from the oscillator becomes the clock input to a 4022 CMOS IC, which is a divide-by-8 counter/divider with 8 decoded outputs.

The 4022 is wired to divide by 6. Each of the 6 outputs used remains high for one full clock cycle. This means that the driving oscillator must run at a frequency six times the wanted cycle of events from the outputs of the 4022.

Three R-S flipflops are made up from two 4001 CMOS quadruple 2-input NOR gates. The remaining two gates are left unused. The six outputs of the 4022 are used to toggle the flipflops. Every third 4022 output toggles a particular flipflop and the sequence of events results in the flipflops being triggered at 120° intervals. This gives three square-wave signals with the wanted 120° phase separation.

The square wave output of each of the flipflops drives an integrator which uses the remaining three sections of the 3900 IC. The output from each of the integrators is a triangular wave form, again each one being 120° away from the next one.

The triangular waves are used to drive three modulator circuits. Although the ideal waveform for this purpose would be a sine wave, the triangular wave approximates a sine wave and does the job quite well. Although it would be possible to filter

PARTS LIST

- 1 Printed board, 204m x 101m, code 77sc11
- 1 LM3900 quad amplifier IC
- 1 4022 CMOS counter/divider IC
- 2 4001 CMOS quad 2-input gate ICs
- 1 4016 CMOS quad bilateral switch IC
- 7 Transistors, BC549, BC209, BC109
- 1 Zener diode, BZX79C12

RESISTORS

($\frac{1}{2}$ W unless stated otherwise)

- | | |
|---------------|----------------|
| 2 1k | 1 22k trimpot |
| 3 1.8k | 3 100k |
| 3 2.2k | 3 100k trimpot |
| 4 2.7k | 1 220k trimpot |
| 3 3.3k | 1 330k |
| 3 4.7k | 1 470k |
| 8 5.6k | 3 820k |
| 4 10k | 4 1M |
| 6 10k trimpot | 4 2.7M |
| 5 22k | 3 4.7M |

CAPACITORS


- 1 100pF polystyrene or ceramic
- 3 .01uF 200V greencap
- 13 0.1uF 200V greencap
- 3 0.33uF 200V greencap
- 4 0.47uF 35VW tantalum
- 1 1uF 35VW tantalum
- 2 4.7uF 35VW tantalum
- 5 10uF 10VW electrolytic
- 3 47uF 6.3VW electrolytic
- 3 100uF 6.3VW electrolytic

Note: Resistor wattage ratings and capacitor voltage ratings are those used on the prototype. Components with higher ratings may generally be used providing they are physically compatible. Components with lower ratings may also be used in some cases, providing the ratings are not exceeded.

the triangular wave to a sine wave, we did not find this to be necessary.

The modulation system consists of three modulated amplifiers each of which processes the signal from the organ generators. Bipolar transistors are used here, with a potentially large amount of degeneration in the form of a large value of unbypassed emitter resistor. Modulation is achieved by introducing variable bypassing of the emitter resistor and this is done with another bipolar transistor performing the function of a variable resistor in series with the bypass capacitor.

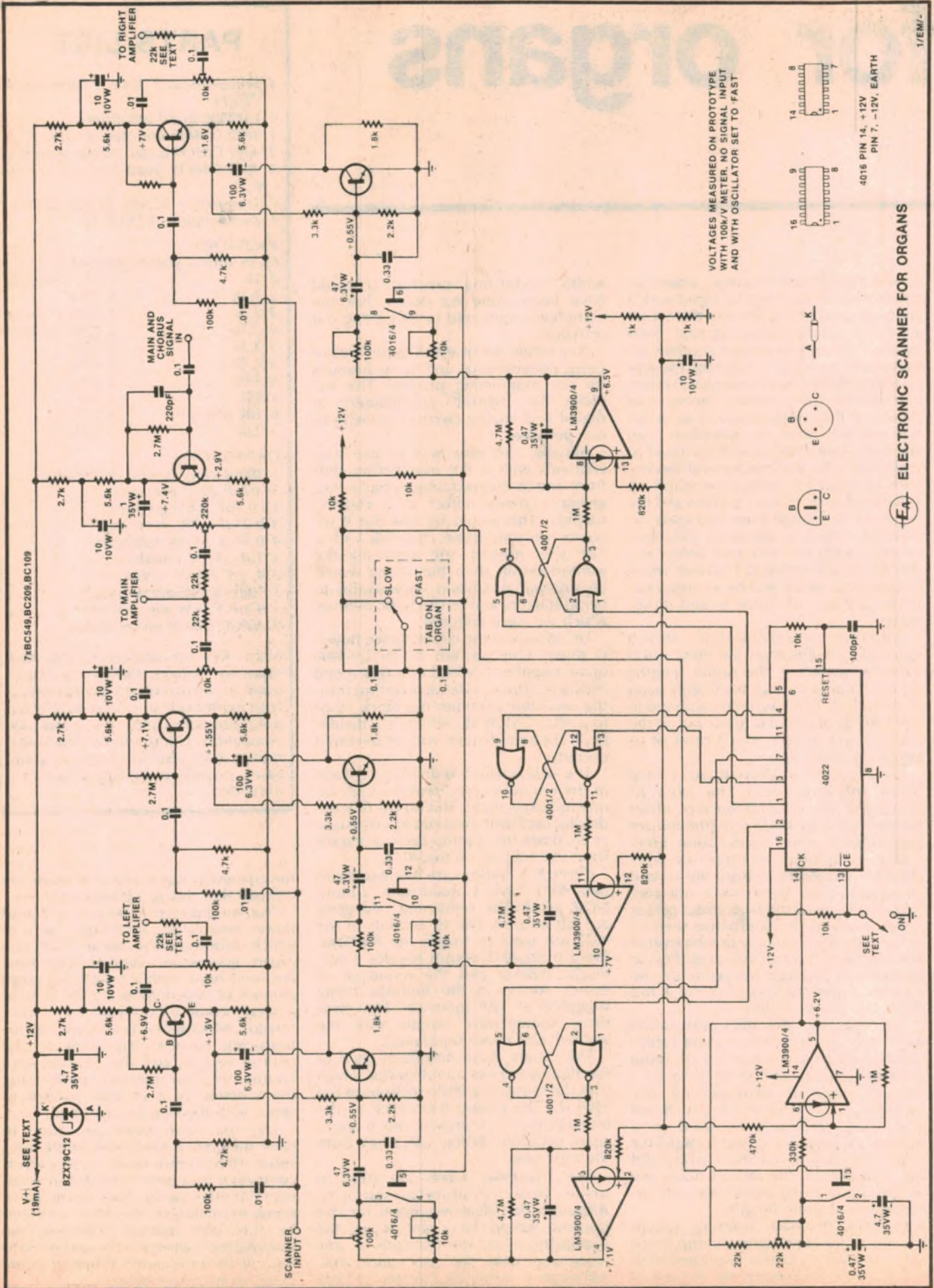
The triangular waves are used to drive the base of each modulating transistor. The amount of drive for each is controlled by a potentiometer in series with the drive signal. Also, the negative going excursion of the drive is limited by the 1.8k resistor shunting the modulating transistor. This avoids cutting off the modulated amplifier in the event of excessive drive.



ELECTRONIC SCANNER FOR ORGANS

1/EMI-

Electronic scanner for organs

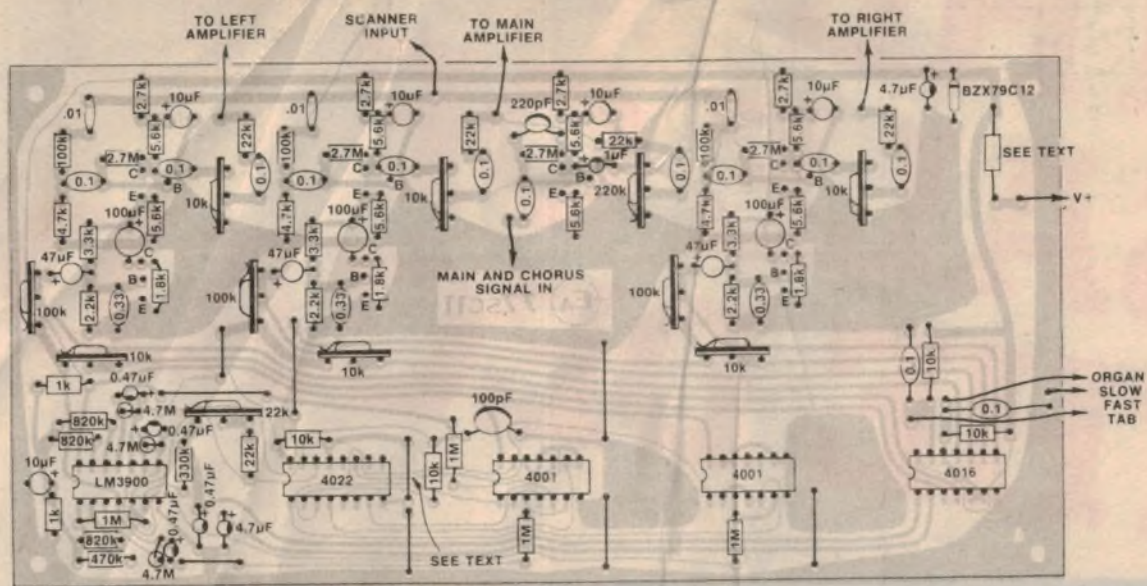

Component overlay diagram for the PC board. The CMOS ICs should be fitted last.

The higher speed is made variable by means of a 22k trimpot in the oscillator circuit. The low speed is achieved by switching in an extra capacitor across the existing one in the oscillator. The low speed is not made separately variable, as it is generally accepted that small changes are not necessary.

Speed switching is done by means of a type 4016 CMOS quad bilateral switch. One section of this switch is used to switch the capacitor in the oscillator. The three remaining sections are used to switch in trimpots to control the amount of drive to the modulators. In turn, the switches may be controlled by the tab normally used for this purpose on the console of the organ. If such a tab is not available, then a single pole changeover switch will serve for this function.

An extra stage, also using a bipolar transistor has been provided. Its main purpose is to provide phase inversion for the "main" and "chorus" signals, to balance the inversion of the signals passed through the scanner stages. Also, the outputs of the scanner and phase inverter are brought together via two 22k isolating resistors.

Provision has been made to stop the scanner action if this is desired. A switch appears on the circuit diagram at pin 13 of the 4022 IC. This is replaced with a link on the board if the facility is not wanted.

Power requirement for the complete unit is quite modest, being 12V at about 19mA. A 12V zener diode has been provided on the board, with a place for a series dropping resistor. The value of the resistor will have to be calculated to meet individual requirements. In addition to the 19mA or so taken by the unit, an extra 5mA or so should be allowed for the zener diode. A round figure of 25mA could be assumed.

So much for the circuit and a broad outline as to how it works. Use of the device will depend upon the requirements of the individual and the particular organ with which it is to be used.

Basically, a signal which is not intended to be passed through the scanner will be fed into the "main & chorus signal in", via the phase inverter and then into the main amplifier. Signals which are to be processed by the scanner will be fed to the "scanner input", which is then fed in parallel into the three modulated amplifiers, the outputs being affected by the fast or slow scanning accordingly. Each of the three outputs from the scanner must be fed into a separate amplifier, although one of these may normally be the main amplifier.

The scanner circuit is intended to be fitted into the signal lines immediately before it is fed into the audio amplifiers. Although the various stages in the scanner circuitry have some gain, preset potentiometers are provided so that the net gain can be adjusted to about unity.

It will be necessary for each installa-

tion to be treated individually, as there are many variations on the way the signals are routed, according to the ideas of the manufacturers. As a basic rule, all percussion effects will be fed via the main amplifier path, avoiding any vibrato or scanning. Some organs provide for a separation of the voices, only allowing tibias or flutes through the rotating speaker. On the other hand, many makers direct all voices, except percussions, through the rotating speaker. Obviously, this is one for you to sort out for yourself.


The complete circuit, except for power supply which may be obtained from a suitable point on the organ itself, is contained on one printed circuit board. The size, 204mm x 101mm, has been kept to a minimum so that it may be fitted into the organ with a minimum of space problems. Construction is reasonably straightforward and anyone familiar with building equipment on PCBs should be able to build it up successfully.

Apart from the circuit diagram, there is also a layout diagram which should make the job quite easy as far as component location is concerned. The usual precautions should be taken when soldering, not to overheat vital components, consistent with care to make sure that there are no dry joints. Polarities of components, such as electrolytic capacitors, transistors and diodes should be carefully observed.

It is generally good practice to mount the smallest components first, such as resistors, followed progressively with the larger components. There are nine


Facing page: 5 integrated circuits and 6 transistors are used in the circuit of the new scanner.

THE SALE OF THE DECADE

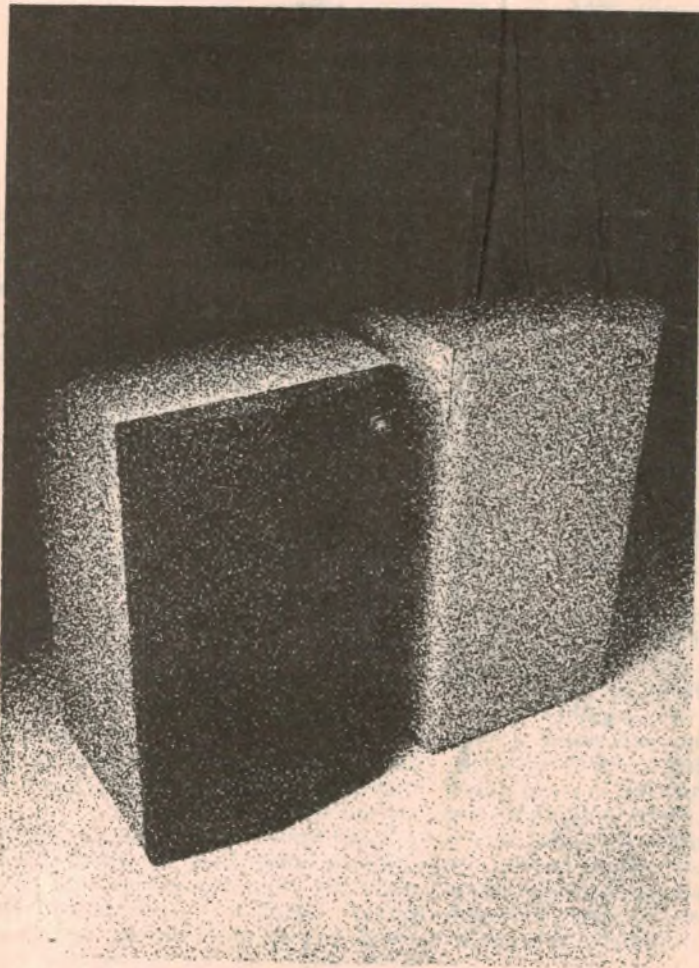

It's official: From NOW until December 31st, or until stocks are sold, a *limited* number of JBL L26 and L36 Decades will be available from your JBL Audio Specialist Dealer . . . at a **Reduced Price!**

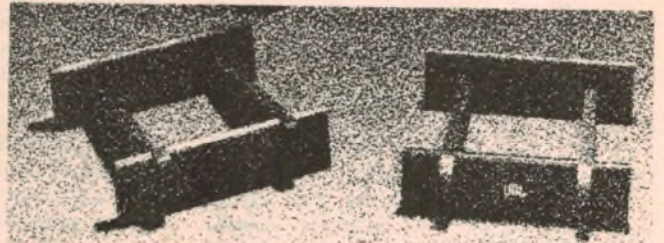With every pair of Decades purchased during the Sale, you will receive **Free**, a pair of JBL Speaker Stands.



Available at your JBL Dealer
... **NOW!**

Distributed by—
HARMAN AUSTRALIA PTY. LTD.,
P.O. Box 6, BROOKVALE, N.S.W. 2100
Telephone: (02) 939 2922



Electronic scanner for organs

links on the board and these should be fitted at the same time as the resistors. If you wish to use the on/off scan switching, then the appropriate link will be omitted and arrangements made for wiring in a suitable switch.

The last items to be fitted will be the five ICs. Apart from the LM3900, the rest are CMOS devices and care must be taken when fitting them. Leave each IC in its protective package until it is to be fitted. Then the soldering iron should have a clip lead from its barrel and in turn, clipped to the earth copper on the board. In addition to this electrical precaution, it will be noted that the spaces between pin connections on the ICs are very close. Considerable care must be taken when soldering, using a small iron bit, to ensure that no adjacent points are bridged with solder.

Having finished the board assembly, there will be still one resistor missing. This is the dropping resistor between the external supply voltage and the 12V zener diode. The unit is designed to operate from a 12V supply at a current of about 19-20mA. If you have a 12V supply available, then the dropping resistor and zener diode will not be needed and the supply may be fed in at the +12V zener diode point.

Most of us will not be fortunate enough to have a 12V supply available. One possible source which may be used is the supply to the main power amplifier. If it is a single supply, the voltage may be between 48 and 60V. If the supply is a balanced one, then there may be plus and minus 24 to 30V. The positive supply must be used.

Having determined the actual positive supply voltage, we then have to calculate the value of the dropping resistor. Assuming a current drain of 20mA and allowing an extra 5mA for the zener diode, we have a total current of 25mA. As an example, suppose that we have a 60V amplifier supply which we can draw on. The voltage drop across the resistor will be 60V-12V, which equals 48V. By Ohm's law, the resistor will be $48/.025$, which comes to 1920 ohms. The nearest preferred value is 1.8k, the result being that there will be somewhat more than 5mA flowing through the zener diode — but it will be still well within the dissipation rating.

Now the dissipation of the 1.8k resistor must be considered. With a voltage drop of 48V, the power dissipation will be $48^2/1800$, which comes to 1.28W. A 2W resistor would do, but it would not be conservative enough for long periods of use and so a 5W resistor would be the wise choice.

If you are fortunate enough to have available a CRO and an audio

generator, you may make preliminary checks and adjustments to the scanner before it is fitted into the organ. By doing this, it will become clearer as to how the device works.

To make the preliminary checks, proceed as follows. Set all trimpots to mid-position, except the 10k and 220k units feeding the main amplifier via the 22k resistors. Set the latter two trimpots to full level. Apply power to the unit via the calculated dropping resistor. Check that the voltage across the zener diode is 12V and that the zener diode and the dropping resistor are showing no signs of distress. Other voltages may be checked and compared with those marked on the circuit, as read from the prototype. Your voltages should be close to those on the circuit.

Set the audio generator to about 400Hz and at an output level between about 200 and 500mV RMS and feed it into the "main & chorus signal in". Check the output "to main amplifier" on the CRO and a clean signal should be observed. Now connect the generator to the "scanner input". With the CRO still on the same output point and with the modulation set to "fast", the modulation envelope should be observed. If necessary, adjust the timebase so that the envelope can be viewed properly. The envelope will be triangular rather than sinusoidal in shape.

At this point, a preliminary adjustment of the modulation depth may be made on this channel. Adjust the 10k trimpot in the base circuit of the modulating transistor for this channel. It will not be possible to drive the stage sufficiently to cause cutoff of modulation, due to the limiting effect of the 1.8k shunting resistor. However, a "flattening" of the negative excursion of modulation will be observed when too much drive is applied. The correct adjustment is just before the onset of flattening. Note the minimum level on the CRO.

Now switch to "slow" and adjust the corresponding 100k trimpot for the same minimum level as previously observed for the fast condition. Return to the fast position and retouch the 10k trimpot to give the same condition as previously. The right and left channels may be adjusted in the same way as just outlined.

In cases where a CRO and an audio generator are not available, the unit may be set up quite satisfactorily by audible means. A little more time and care may be needed but after all, it is the ear which must be satisfied!

The scanner board will have to be connected into the organ signal lines to be adjusted audibly. Obviously, it will

Turn page for . . .

THE TANDY ELECTRONICS

1978 CATALOG

132 pages
crammed with
bargains . . .

- ☆ Hifi equipment
- ☆ Kits and components
- ☆ CB transceivers
- ☆ Car radios

Plus lots more!

Advertised goods are available from over 100 Tandy Electronics stores throughout Australia, or by mail order.

also need to be connected up after it has been tested with a CRO and audio generator. In either event, consideration should be given to the location of the board. This may be dictated by available space and shortness of signal leads. If the leads can be kept short, say 10 to 15cm or so, then with the rather high signal levels usually available, shielding of the signal leads may not be necessary. On the other hand, with much longer leads, it would be wise to run them in shielded cable.

With the board in place and connected up, before making adjustments, turn the four output potentiometers (three 10k and one 220k) right down. A situation should be simulated where the maximum sound level is likely to be demanded of the organ. This means something like "all stops out", with say the bottom C pedal and a chord played by each hand. Under these conditions, and with other tabs set so that the scanner is not in use, bring up the 220k potentiometer until the volume is as loud as you are likely to require, or just before distortion occurs. This will be the setting against which the scanner levels will be set.

The following adjustments can be a little tricky but as I mentioned before, the ear is the final judge. Earlier, I suggested that all preset potentiometers, except those controlling output levels, be set to mid-position. Now set the scanner to "slow". With the "main" channel volume as the reference, advance the 10k potentiometer which feeds the "main" amplifier and set the volume a little lower than the reference. At this point, a multimeter with a low AC volts range would be useful.

Check the voltage across the voice coil of the appropriate speaker and note the reading. Because of the scanning effect, the voltage will waver between two values. Set the right and left trimpots, with the meter across the respective voice coils, to give the same range of readings. If you do not have a meter available, then an audible estimation of the levels will have to be made.

With the levels now set to equal values, the overall sound level of the slow scan output should be about equal to the "main" or reference output. If necessary, an adjustment slightly higher or lower may need to be made on all three output levels.

At this point, you may wish to vary the depth of the slow scan modulation. This can be done by adjusting the three 10k trimpots controlling the drive to the modulator stages.


Now switch to "fast" scan. The volume levels should not need any adjustment, but you may wish to alter the depth of the modulation. To get the maximum effect, the three 10k trimpots for adjusting the modulation depth should be advanced as far as possible, consistent with a tolerable level of

"pumping" from the three speakers when no signal is being passed. However, you may settle for a modulation depth which falls short of any audible pumping of the speakers.

The actual speed of the fast scan should be fairly close with the 22k trimpot set to its mid-position. However, it may now be adjusted to the speed which suits you best. This normally

comes to somewhere between about 400 and 420 beats per minute.

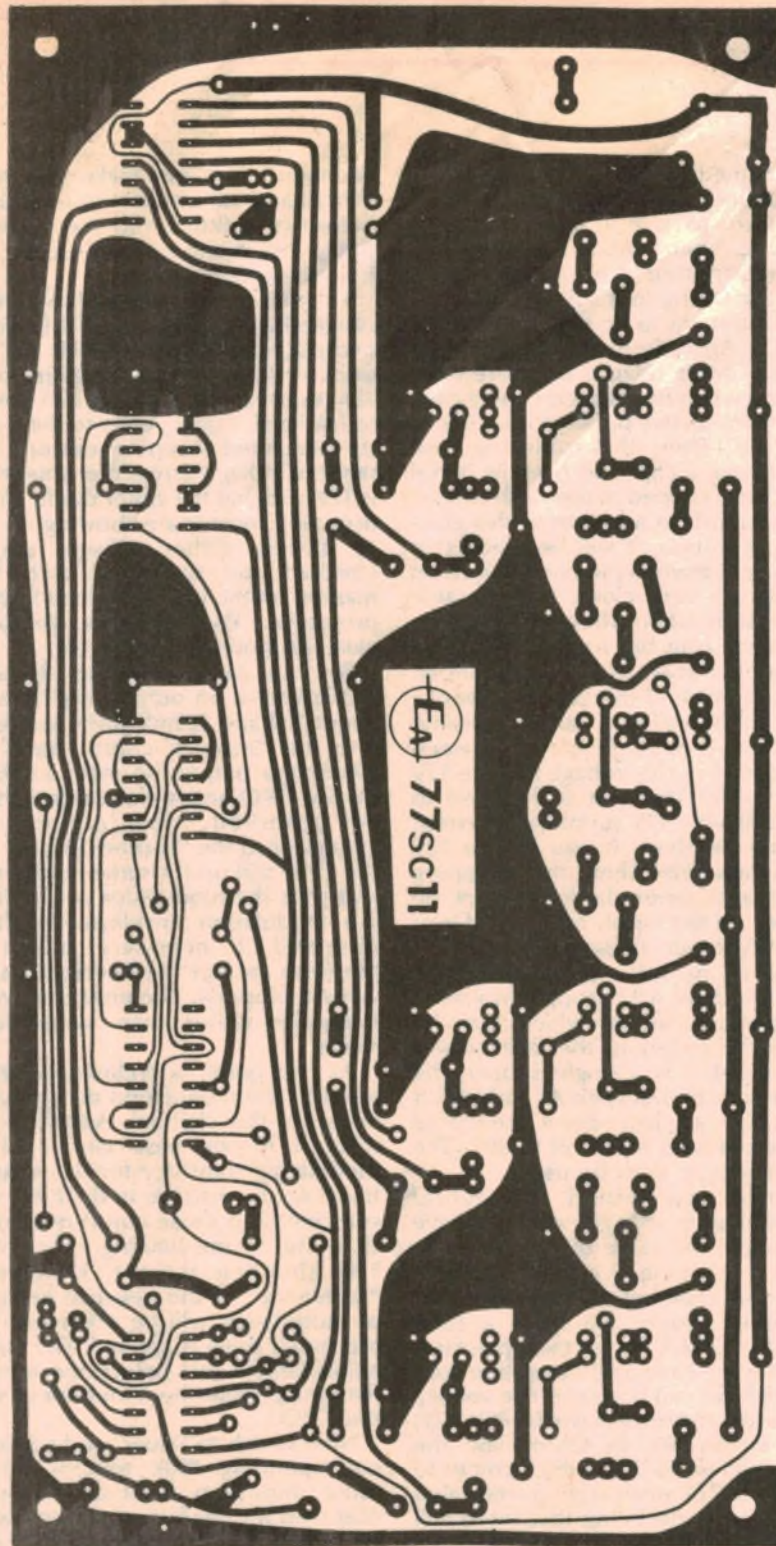The foregoing description of the adjustment and application for the scanner should be sufficient for the scanner going satisfactorily. No attempt has been made to treat the theme fully, as the variations in application and personal taste are so diverse as to make this impossible. 2



Actual size reproduction of the PC pattern.

Where to buy printed boards etc

One of the most frequent requests we receive from readers concerns the availability of printed circuit boards for our projects. To a lesser degree they also enquire about chassis and etched panels.

Some readers imagine that we manufacture and distribute boards. Others appear to believe that these are available only from special sources. We do not manufacture or distribute any of these items, or any other components. But we are concerned that our readers should be able to buy these parts with no more difficulty than the other components used in a project. When a project is ready for publication we distribute drawings of printed boards, chassis, and front panels to a number of manufacturers who have requested this information.

These manufacturers are then in a position to supply these items to any distributor who requires them or, in some cases, direct to the public. On this basis you should be able to obtain these items from the same distributor who supplies your resistors, capacitors, transistors and other routine components. If he does not have them in stock he should have no difficulty obtaining them to order.

However, for the benefit of those readers who may have difficulty in obtaining these items, for one reason or another, we list below those manufacturers who are currently on our mailing list. If all else fails they should be able to either supply you direct, or advise which distributors are holding stocks.

PRINTED BOARDS

Applied Technology Pty Ltd
109 Hunter Street,
Hornsby, NSW 2077

Bespoke Metalwork
42c Sydenham Road,
Brookvale, NSW 2100

BKX Electronic Supply Service
PO Box 787,
Potts Point, NSW 2011

"Cirprint"
PO Box 165,
Bentley, WA 6102

David J. Reid NZ Ltd
PO Box 2630,
Auckland, NZ

E. H. Earl Ltd
PO Box 834,
Wellington, NZ

Jemal Products
120 Briggs Street,
Welshpool, WA 6106

Mini Tech Manufacturing Co. Ltd
PO Box 9194,
Newmarket, NZ

Neosonic Electronics
PO Box 50,
North Strathpine, Qld 4500

Printed Circuits Ltd
PO Box 4248,
Christchurch, NZ

RCS Radio Pty Ltd
651 Forest Road,
Bexley, NSW 2207

Statronics Pty Ltd
103 Hunter Street,
Hornsby, NSW 2077

CHASSIS

Bespoke Metalwork
42c Sydenham Road,
Brookvale, NSW 2100

Coin Selectors Pty Ltd
PO Box 203,
Narrabeen, NSW 2101

Cowper Sheetmetal & Engineering
11 Cowper Street,
Granville, NSW 2142

ETCHED PANELS

Bespoke Metalwork
42c Sydenham Road,
Brookvale, NSW 2100

Cowper Sheetmetal & Engineering
11 Cowper Street,
Granville, NSW 2142

Jemal Products
120 Briggs Street,
Welshpool, WA 6106

As a spin-off from the drawings we prepare for the trade, we can also supply copies for our readers (price \$2.00). Those with access to metal working or etching facilities can take advantage of this to "roll their own".

However, beginners should be aware that this may not always be the most economical approach. To the cost of drawings must be added the cost of raw materials, wastage, etc, plus the disappointment which comes from a job which may fall short of professional standards.

As a general rule it costs very little more to buy the ready made product, saves a lot of time, and results in a much more satisfying end result.

DANDY ELECTRONIC DISCOUNTS

(CHEAPEST IN TOWN)

508 BRIDGE ROAD, RICHMOND, VIC. 3121
Tel. After Hours: 799-1869

Resistors from 1c. Switches from 30c.
Capacitors from 3c. Coils from 20c.
Electrolytics from 5c. Trimmers from 10c.
Knobs from 3c.

SPEAKERS (Wide range, e.g.)

Twin/Cone 8" 8 OHMS \$5.50.

Twin/Cone 5" 8 OHMS \$3.00

Twin/Cone 5" 15 OHMS \$3.00

Balance Meters \$1.50. Transformers from 60c.
Coaxial Cable 75 OHMS 13c per metre. Hook-
up Wire 4c per metre. A/C Leads 3 Core 45c.
A/C Leads 2 Core 30c. Slider Pots single 20c
dual 40c. Acrylic Lid 15"x23" \$2.00. TV Aerials
\$2.50. Transistors from 15c. Baffles (Cut Outs)
from 60c. Speaker Cloth \$1.50 per yard. Heat
Sinks from 5c. Earth Strips from 10c.
Suppressors — various. TV Tuners B/W, EHT
Coils, Deflection Coils, Sockets (Speaker), Din
Sockets (Globe Sockets), Globes — various
from 10c. Lugs — various. Fuses — various.
Trim Pots — various. Sanyo Tape Bands
Special 80c. Formers — various.

**MAIL ORDERS AND TRADE
ENQUIRIES WELCOME**

**OUR MOTTO
CHEAPEST IN TOWN**

Mon.-Thurs. 9 am-5.30 pm
Fri. 9 am-7 pm. Sat. 9 am-12 noon.

COWPER SHEETMETAL WORK FOR THE ELECTRONICS INDUSTRY

**E.A. VIDEO DATA
TERMINAL CASES
MINI-SCAMP
MICROCOMPUTER**

C.S. 108 & 216 Hobby Boxes

108 x 108 x 50 + + 216 x 108 x 50

Inquiries welcome on
Cases and Panels

Rack Mounting Chassis

Chassis & Covers

Vented Transformer Cases

General Sheetmetal & Welding

**COWPER SHEETMETAL
& ENG.**


11 COWPER STREET
GRANVILLE N.S.W. 2142

PHONE 637 8736 (S.T.D. 02)

(A Division of The Star Delta Co. P/L)

Understanding Digital Electronics

New teach-yourself courses

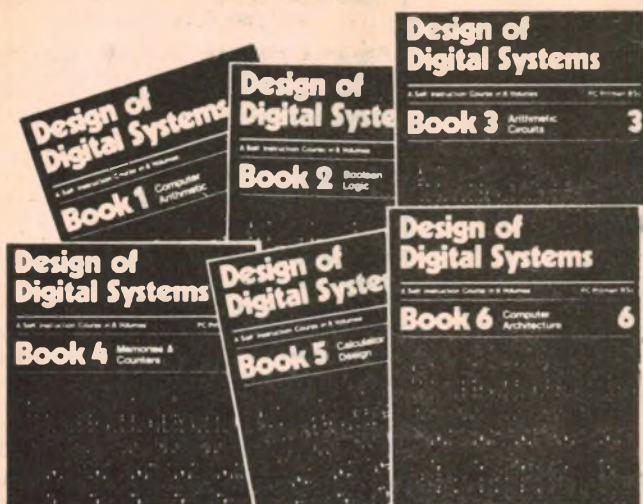

Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes — each 11-1/2" x 8-1/4" are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers.

The contents of Design of Digital Systems include:

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division

Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three state and wired logic

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure

Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input / output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing



Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed though the student should have an aptitude for logical thought. It consists of four volumes — each 11-1/2" x 8-1/4" — and serves as an introduction to the subject of digital electronics. Everyone can learn from it — designer, executive, scientist, student, engineer

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your automobile speed and gas consumption; you could be calling people by entering their name into a telephone which would automatically look up their number and dial it for you

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

The six volumes of Design of Digital Systems cost only: **\$19⁸⁸**

And the four volumes of Digital Computer Logic and Electronics cost only: **\$14⁸⁸**

But if you buy both courses, the total cost is only: **\$29⁹⁰**

a saving of over: **\$5⁰⁰**

SEVEN DAY MONEY-BACK GUARANTEE: If you are not satisfied with your Cambridge course, return it within 7 days for a full refund.

To order your books, complete the order form below and send it together with your cheque or money order to J. S. & A. National Sales Group, 128 Hawthorn Road, Caulfield, Vic. 3162.

To: **J. S. & A. NATIONAL SALES GROUP**
128 HAWTHORN ROAD, CAULFIELD, 3162. TEL: 528 6243

Please send me:

..... Sets of Design of Digital Systems \$19.88

..... Sets of Digital Computer Logic & Electronics \$14.88

..... Sets of both courses \$29.90

..... Shipping and handling per set \$3.50

Enclosed is cheque/money order payable to J. S. & A. National Sales Group.

Total: \$

Name

Address

City

State

Postcode

Please allow 3-4 weeks for delivery.



Letters to the editor

All is not lost, however. JBL will introduce a "domesticated" 4301, the L19, early next year in the European market. The L19 will arrive in the JBL specialist dealerships during February or March, 1978, right around Australia. Trevan C. Johns, Sales Manager, Harman Australia Pty Ltd.

Loudspeaker review

Thank you for your magazine's very fair review of the JBL 4301 Broadcast Monitors (EA, September 1977, p.35).

We find it absolutely necessary to correct some wrong inferences drawn in the conclusion of the article, however. The author commenced the article by choosing to evaluate the 4301s as he would a pair of hifi speakers, and this is, of course, very valid. The conclusion of the review, however, gives the impression that JBL describes the 4301 as a "Broadcast Monitor" as some sort of gimmick to induce the public to hold them in a higher esteem than is their due, and buy for this reason.

Perhaps this criticism is rightly founded, in view of the well known tendency for the term "monitor loudspeaker" to be rather loosely hung on quite a few devices that would never be seriously considered for professional monitoring.

The 4301s were submitted as Broad-

cast Monitors for the primary interest of your readers in the broadcasting industry, however. JBL introduced the model 4301 at the Audio Engineering Society Exhibition in Los Angeles in May this year. The 4301s are not offered for sale to the hi-fi dealerships. JBL has a very strict policy on this point, and professional series transducers are distributed through a separate dealer network to hifi products.

At this time there are over 1600 JBL monitors used professionally in Australia. The ABC has approximately 300, alone. The price and size of the JBL Monitor Systems exclude them from most living rooms, and there is a waiting period on most of the seven models. However, in recognition of the growing number of home recording studio enthusiasts, we market JBL Professional Monitor Systems through three hifi dealers. ENCEL ELECTRONICS, Melbourne, CONVOY TECHNOCENTRE, Sydney and PACIFIC STEREO, Manuka, ACT, subject to availability.


Laser surgery

It is with some interest that I read your leading article in the August issue on "Laser Surgery in Australia". I am writing to enter a mild protest at the failure of your reporter to include in the article reasonable mention of the pioneering use of the laser in surgery in New South Wales by the surgeons at Sydney Hospital.

The surgical Laser was installed at Sydney Hospital six months prior to installation at the Children's Hospital and at least 10 times more surgery has been performed at Sydney Hospital than at the Children's Hospital. A far wider variety of operations has also been performed at Sydney Hospital. It might have been expected that the pioneering experience obtained by the surgeons at Sydney Hospital would be the basis for an article on laser surgery in your magazine.

W. H. McCarthy, FRACS, M.Ed.,
Associate Professor of Surgery,
Sydney Hospital.

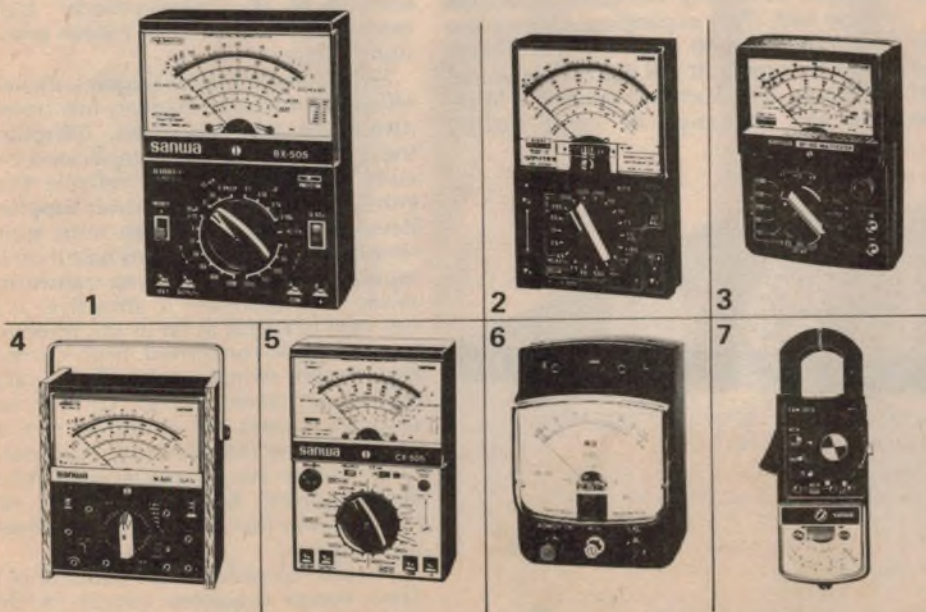Sanwa precision circuit testers — Big on features. Bigger on selection.



1. BX-505

- Fast-response, 24 μ A movement — fuse & diode protected with high resolution factor (0.4 μ A/scale division)
- Revised scale marking — intermediate readings readily determined

2. U-60D

- 44 μ A movement — quality performance, diode protected
- Stable ACV measurement — solid-state rectifier & enlarged frequency coverage

3. SP-10D

- Easy operation — multiposition rotary selector switch & well-lighted scale
- Stable ACV measurement — durable diode rectifier

4. N-501

- 2 μ A suspension movement — 0.05mA/1mV resolution
- Double protection — fuse & Si diode

5. CX-505

- 16.5 μ A movement — varistor protected & 50k Ω /V for DC
- Capacitor tester — push-button operation with solid-state oscillator built in

6. PDM-500 (Insulation Tester)

- Battery operated — 3 small-size 1.5V batteries built in
- Push-button operation — pointer calibration & insulation test

7. CAM-201S (Clamp Meter)


- Measuring ranges 15-60-300A — 500V — 50k Ω
- Meter protection diode provided



WARBURTON FRANKI

ADELAIDE 356-7333 BRISBANE 52-7255 HOBART 23-1841
MELBOURNE 699-4999 PERTH 65-7000 SYDNEY 648-1711
WELLINGTON, N.Z. 698-272

sanwa
MULTITESTERS

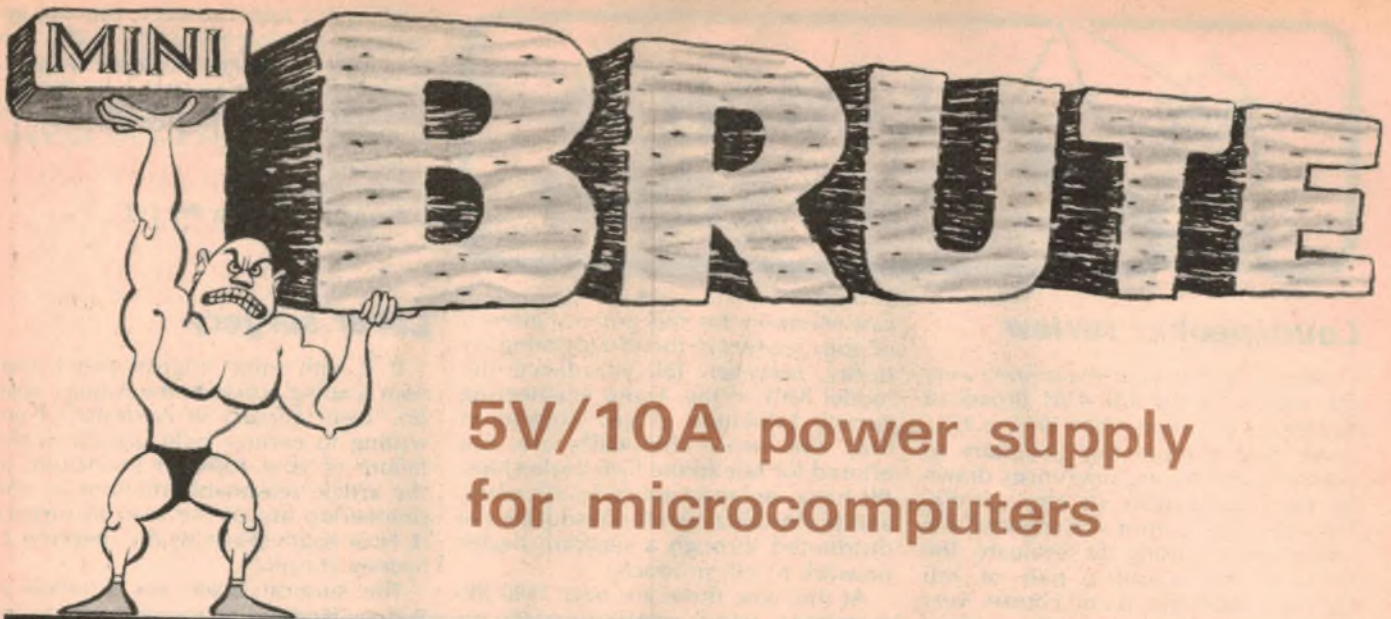

5V/10A power supply for microcomputers

by **LEO SIMPSON**

Intended for the heavy current drain of a microcomputer with expanded memory and peripheral interfacing, this little "brute-force" supply is much simpler in approach than the elegant switch-mode designs but provides a highly regulated five volts at up to 10 amps. It uses readily available components, is short circuit proof and has optional crowbar protection.

Anyone who becomes involved with hobby computing quickly discovers that there is an apparently universal tendency for hobby computer systems to "grow". They might start as baby systems, but before long you are adding extra memory, interfacing circuitry for this peripheral or that, some more memory, and so on.

And with this growth, the power drain inevitably goes up. Even though the drain is really very low compared with early computers, thanks to the

MOS technology used to make modern microprocessors and memories, it soon rises to a point where one's small original power supply becomes embarrassed.


Generally most of the current drain is associated with the +5 volt power supply. So to help computer hobbyists cope with their expanding systems, we have decided to produce this heavy-duty 5V supply. It will deliver a nominal 10 amps, which should satisfy the likely current demands of most hobby

systems — at least for a while!


A major problem to be faced in the design of a high current supply is that of efficiency and the inversely related parameter, heat dissipation. For this reason, many commercially designed regulated power supplies these days tend to be the "switch-mode" type, most commonly seen in colour television receivers.

Switch-mode power supplies are very efficient and have relatively low power dissipation and low mass. Offsetting these advantages are complicated circuits which can be less reliable than conventional regulated power supplies. Recently, there have been some quite simple and elegant designs based on IC regulators driving switching transistors. While this approach is attractive, it is not very practical as far as the hobbyist in Australia is concerned. High-current high-speed switching transistors and their accompanying high current fast recovery diodes are almost as rare as rocking-horse manure, and correspondingly expensive. A special inductor is also required. Reluctantly, then, we had to admit that some other approach was required.

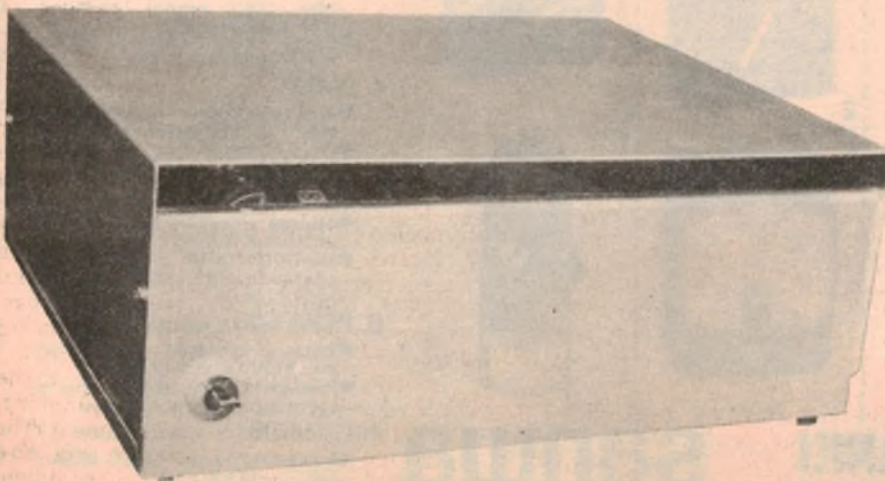We also considered the concept of a Triac based regulator circuit in the primary of a power transformer, with feedback from the low voltage output to the Triac control circuitry. This would have the advantage of reasonable efficiency, but the gloss



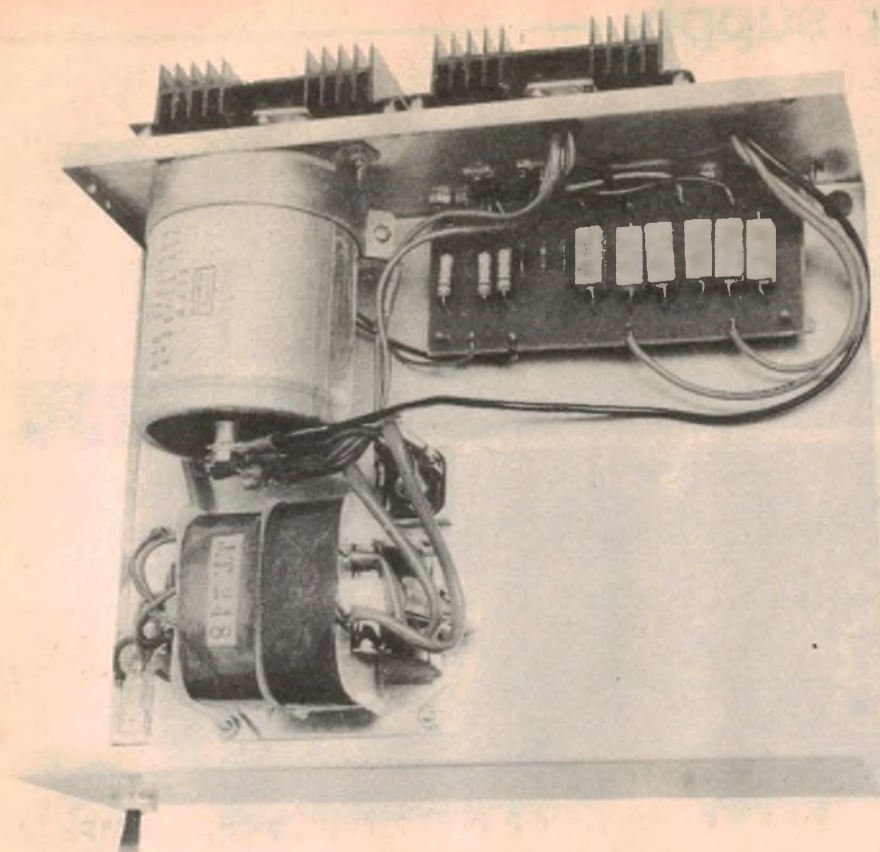Not pretty, as befits a brute. The cover is raised to aid ventilation.



Relatively few components are involved, considering the high performance of the supply. The blank area can be used for our cassette interface board.

went off the idea when calculations indicated the large amount of filter capacitance required to achieve low ripple on the output. Half a dozen computer-grade electrolytic capacitors would make a sizable debit in most hobbyist's bank accounts!

Eventually, we decided upon the circuit featured here. It uses the old "tried and proven" series regulator in a souped-up circuit. The circuit is not original, but is based on an Application Note in the National Semiconductor "Voltage Regulator Handbook".

This supply has the advantage of using components which are readily available in Australia, and an overall cost which is quite reasonable considering the performance. There is but one disadvantage — heat dissipation. When supplying that highly regulated five volts at 10 amps (50 watts) the circuit dissipates between 60 and 70 watts. As a result, it gets stinking hot!

But before you toss this magazine aside, read a little further. Lest we paint too bad a picture, let us assure you that the component ratings are not exceeded. This can be hard for many people to accept. After all, everyone knows that valves are supposed to get hot, but transistors are supposed to stay cucumber cool. Well that need not be so; in fact they can run very hot indeed, and quite reliably.

Refer now to the circuit diagram. Basically, it is a current sharing arrange-

ment with a three-terminal 5V IC regulator providing about 10% of the current and the other 90% being provided by Tr2 and Tr3.

The front half of the circuit is quite conventional, with the low voltage transformer secondary being rectified by a silicon bridge rectifier to feed a big fat electrolytic capacitor which provides about 10 to 12 volts DC. From there, the DC is split into three paths. Assuming a 10 amp load, about 1 amp goes to the 5V IC regulator via a diode and two 1 ohm/1W resistors in parallel. About 0.5 amp goes to Tr1 via the 1 ohm/1W resistor, and about 8.5 amps goes to the collectors of Tr2 and Tr3.

The current sharing mechanism works as follows. The current drawn by the IC regulator produces a voltage drop in the 0.5-ohm resistance produced by the two 1 ohm resistors in parallel. This forward biases Tr1, which by emitter follower action draws enough current to balance the drop across the 0.5-ohm resistance with that across its 1-ohm emitter resistance. The diode is used to balance out the base-emitter voltage of the transistor.

Tr1 then supplies base current to Tr2 and Tr3. The current gain of Tr2 and Tr3 then determines how much of the total current they supply to the load. In most cases, Tr2 and Tr3 will supply adequate current to the load so that the IC is handling less than 1 amp when the total load current is 10 amps. In a few cases it

PARTS LIST

- 1 aluminium case, 18 SWG, 285 x 230 x 90mm
- 1 PC board, 140 x 60mm, coded 77ps11
- 1 transformer with secondary 11V at 10A DC
- 1 SPST mains toggle switch
- 1 12-way insulated terminal strip
- 2 double-sided heatsinks, 102 x 75mm

SEMICONDUCTORS

- 1 LM340T-5 or μ A7805 5V IC regulator
- 1 TIP32 PNP transistor
- 2 2N3055 NPN transistors
- 1 1N4001 silicon 1 amp diode
- 1 1N5408 or equivalent 3 amp silicon diode
- 1 PB40 or equivalent 25 amp bridge rectifier

RESISTORS

- 3 x 100 ohms/1/2W, 3 x 1 ohm/1W
- 6 x 0.56 ohm/5W

CAPACITORS

- 1 33000 μ F at 16V or more, or
- 3 5600 μ F/40V (see text)
- 1 x 4.7 μ F/35VW tantalum electrolytic

MISCELLANEOUS

- 4 rubber feet, 4 PCB supports (Richco), 8 6mm metal spacers, 2 grommets, 2 TO-3 sockets, mounting hardware for TO-3 transistors, heatsink compound, 6 Utilux quick-connectors, 7 crimp spade lugs plus crimping tool, mains cord and three-pin plug, mains cord clamp, solder lug, 4mm auto cable, screws, nuts, lockwashers, solder.

may be necessary to shunt the 1 ohm feed resistor to Tr1 to increase the current drive to Tr2 and Tr3.


The emitter resistors of Tr2 and Tr3 ensure that they each supply approximately the same current, to share the load.

The current sharing mechanism described above makes it possible for the IC regulator to closely control the voltage applied to the load, at currents far above its normal rating. If the voltage across the load tends to rise above the nominal 5V output of the regulator, the regulator tends to shut down slightly and, via the current sharing mechanism, shuts down Tr2 and Tr3 by the appropriate amount.

Similarly, if the voltage applied to the load tends to drop below the nominal 5V, the regulator tends to draw a little more current to make up the difference, and Tr2 and Tr3 are driven just a little harder to do their share.

Just how effective is this system of

5V/10A power supply

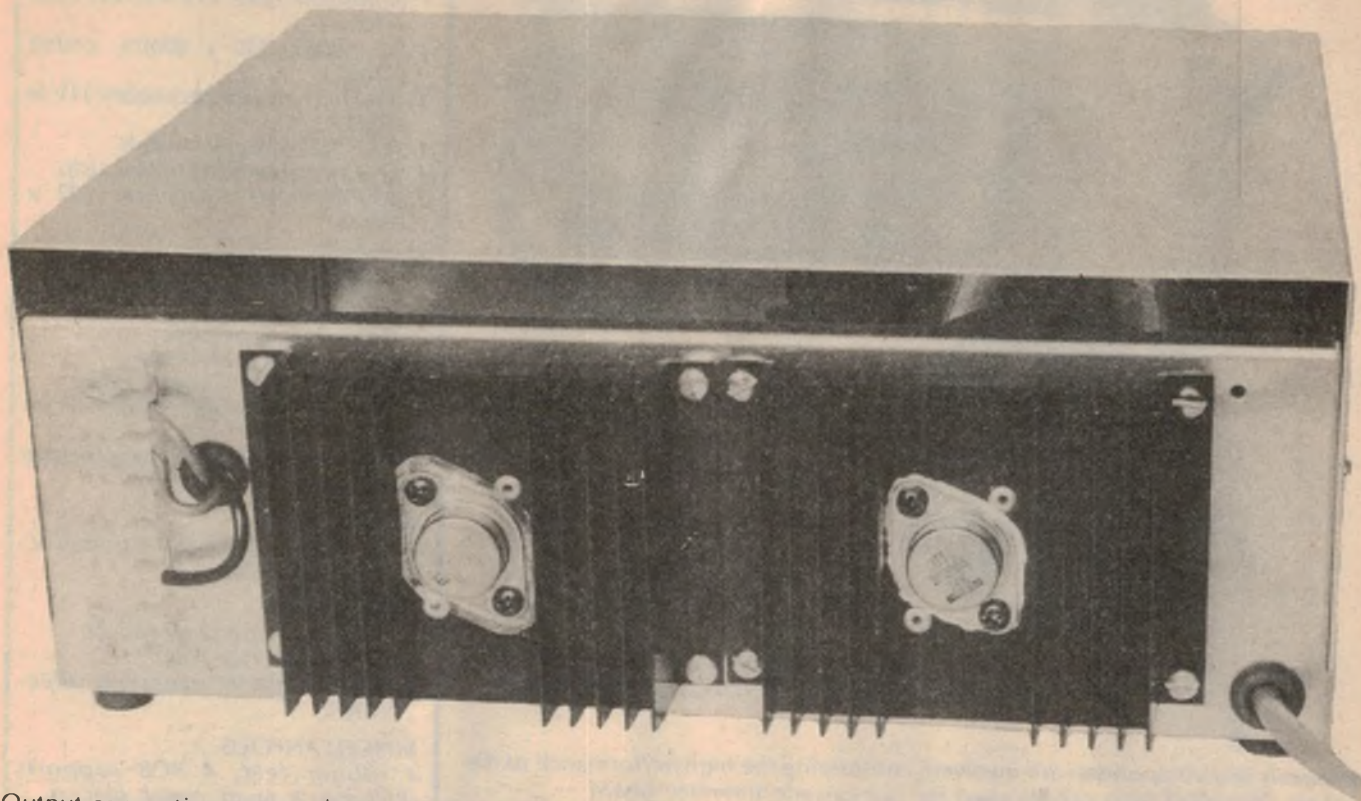

Output connections are made via an insulated terminal strip.

voltage regulation? With our prototype, the change in output voltage from no load to full load (10 amps) is only 8 millivolts. Hum and noise on the output are less than 2 millivolts peak-to-peak at full load. Line regulation, with mains voltage changing from 264V to 216V, is less than 3 millivolts. These figures are more than adequate for the job.

There are three 100 ohm resistors in the circuit to ensure that the IC regulator maintains full control right down to zero load current. The 100 ohm resistors across the base-emitter junctions of the transistors ensure that they do not turn on harder than required, while the 100 ohm resistor across the output ensures a 50 milliamp

output current whether or not an external load is connected.

A 4.7 μ F tantalum capacitor is connected across the input to the IC regulator to ensure stability. Capacitors are not required across the output for stability, although they can be added to improve transient response. In any case, it can be assumed that most circuitry with which this power supply will be used will have supply bypass capacitors.

By virtue of the IC regulator and the current sharing mechanism already referred to, the power supply is protected against short circuits. The IC has two protection mechanisms, "safe operating area" and thermal limiting. The first limits the current to control the power dissipation, while thermal limiting monitors the chip temperature and shuts down the output to prevent overheating.

This system of protection is effective only for short term overloads. Long term overloads will damage not only the regulator circuit but also the bridge rectifier and transformer. If this possibility is likely a 15 amp fuse should

be connected in series with the regulator circuitry. More about protection later in this article.


Our prototype was assembled into an aluminium case with dimensions 285 x 230 x 90 mm. This case is almost identical to that for the Miniscamp project described in May 1977, and was kindly supplied by Bespoke Metalwork.

The power transformer was made by Jones Transformers and is designated JT-248. It is based on the same hardware as the C-core transformer used in the Playmaster Forty-Forty. As such, the C-core enables a modest overall size with very good inherent regulation.


An EDI Minibridge, type PB40, was employed as the bridge rectifier. It has a rating of 25 amps continuous, which is necessary if it is to withstand short circuit conditions.

We used a 33000 μ F computer-grade electrolytic for the main filter capacitor. However, depending on your usual sources of supply, computer grade electrolytics may be expensive and may be hard to get. Some constructors will be able to salvage capacitors from old computer gear.

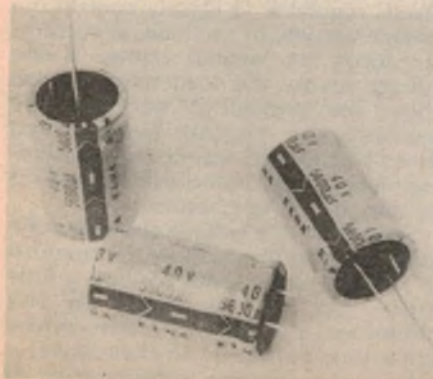For those without these resources, there is an alternative in a new capacitor from Elna, distributed by Soanar Electronics Pty Ltd. It is a PCB mounting type with value of 5600 μ F/40VW and ripple rating of 4.3 amps. Three of these capacitors con-



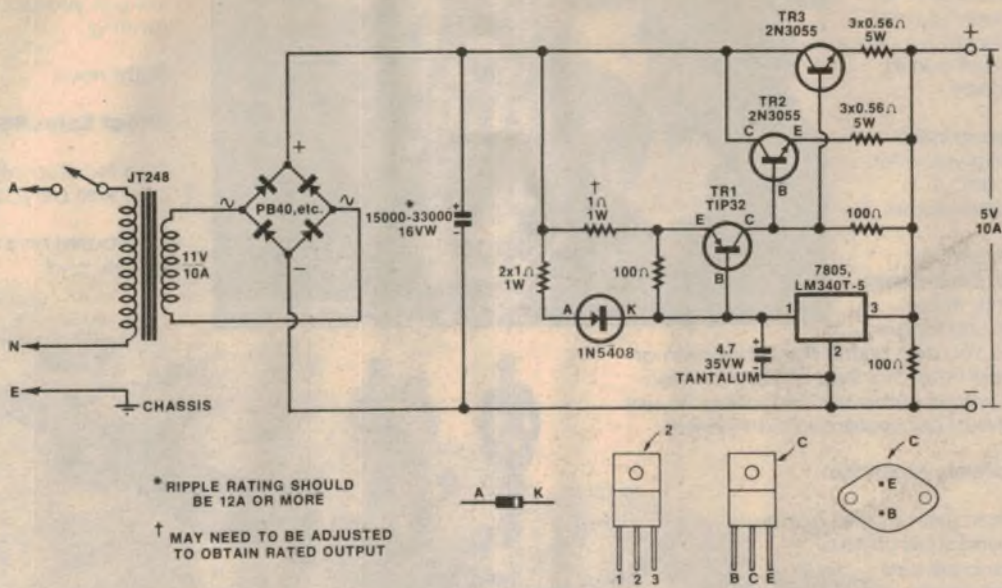Three of these 5600 μ F/40VW electrolytics from Elna can provide the main filter capacitance for the power supply. Each has a ripple rating of 4.3 amps.



EA 5V/10A MICROCOMPUTER POWER SUPPLY

2/PS/-

Most of the smaller components are mounted on the PCB which simplifies the wiring.


nected in parallel will be adequate for this application.

All the remaining components, with the exception of Tr2 and Tr3, are mounted on a PCB measuring 140 x 60mm, designated type 77ps11. Both the 5V regulator (uA7805 or LM340T-5) and Tr1 (TIP32) are accommodated at the edge of the PCB so that they can be thermally connected to the chassis for heat dissipation.

Both the IC regulator and the TIP32 have the TO-220 style encapsulation. The heatsink tab of the TIP32 must be isolated from chassis and, if the power supply is required to have an electrically floating output, the same applies to the heatsink tab of the IC regulator. At the time of writing we were unable to obtain TO-220 mounting hardware but we were able to "gimmick up" a suitable mounting using mounting hardware for a TO-3 transistor.

There is provision on the PC board for a variety of combinations of resistors for the Tr2/Tr3 emitter resistances. We used three 0.56 ohm 5 watt resistors in parallel per output transistor, and any substitute combination should have roughly the same resultant resistance and total power rating. If the power rating seems excessive, remember that the resistors must be able to withstand short-circuit currents of up to about 20 amps total.

Mount the resistors so that they are

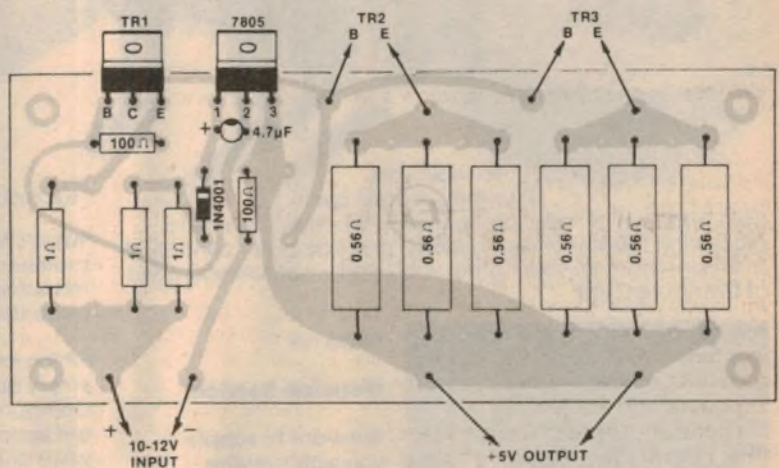

This crimping kit plus the Utilux connectors helps make rugged and reliable connections to the bridge rectifier, main filter capacitor and mains switch.

Rated G

The Best Game in Town.

Welcome to ComputerLand. An incredible adventure into the world of personal computers. A one-of-a-kind shopping experience.

Each ComputerLand store presents everything you ever wanted to know about computers. And then some.

Take our Game Room, for starters. You'll find excitement for the whole family in our endless variety of challenging computer games. You can battle the Klingons in an out-of-this-world game of Star Trek. Create an electronic work of art with a computer controlled TV. Test your skill in a game of computerized hangman.

You can even plot your biorhythm.

But we're more than just fun and games. Each ComputerLand store offers a knowledgeable and personable staff of professionals



And if your system breaks down, our in-store service department will get you back up and running.

Right now!

Great Selection.

Your first stop at ComputerLand may well be your last stop.

ComputerLand offers the finest quality and



largest selection of all the major brand names. Like Apple Computer, Cromemco, DEC, Diablo, Hazeltine, ICOM, IMSAI, Lear Siegler, National Semiconductor, North Star, Texas Instruments, Vector Graphics and more.

to serve you.

Plus the greatest available selection of micro components. Whether it's a data processing system for your business or a computer controlled sprinkler system for your home, you'll find whatever you need at ComputerLand.

Plus a complete inventory of tools, books and accessories.

What's more, at ComputerLand, we deal in product. Not promises. Our inventory is on our own shelves. Rather than the manufacturer's. So you can take delivery on tomorrow's components today.



Read on.

Genuine Service.

We want to supply you with the one system that's right. Rather than a complete system that isn't. Or a limited system that is.

That's why, at ComputerLand, you deal with real professionals who are also real people. People who speak your language

... in addition to BASIC, COBOL or FORTRAN.

People, in short, who can offer both the novice and the old hand the same expert guidance in selecting the optimum system he or she needs.

Yet, assisting in the purchase is only the beginning of ComputerLand's service. If the kit you bought requires a little more do-it-yourself than you yourself can do, we provide assembly assistance.

If that complex program proves to be just that, we provide programming assistance.

Which means, simply put, that at ComputerLand, you get exactly what you want.

Exactly when you want it.

Be Our Guest.

Begin with the grand tour of our exhibit areas. "Test-drive" any of our individual systems.



Then tell us your needs. We'll sit down and talk about the system that's right for you. It's as easy as that at ComputerLand.


The great computer store. RATED G.

Call or write for the address of the ComputerLand store nearest you. Franchise opportunities available.

ComputerLand™

55 Clarence St, Sydney 2000. Tel. 29 3753.

5V/10A power supply

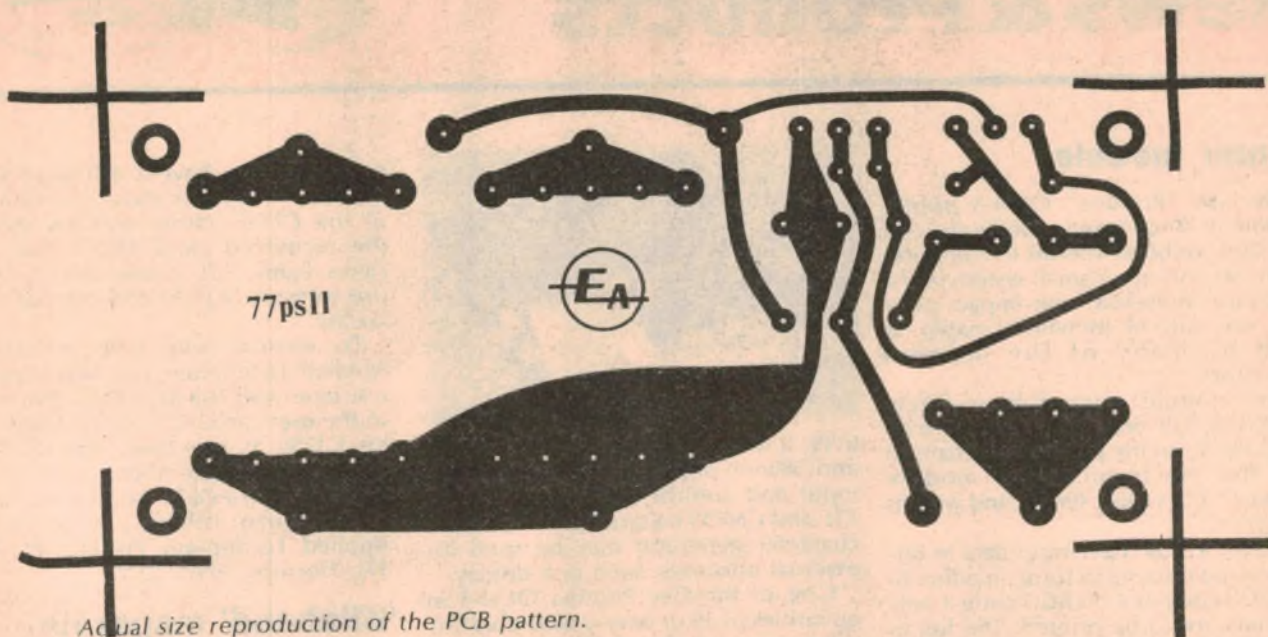

Actual size reproduction of the PCB pattern.

about 3mm clear of the PCB. This is to prevent the resistors from scorching the PCB in the event of an overload.

We used double-sided heatsinks for the output transistors. The heatsinks are spaced away from the rear of the chassis using 6mm metal spacers. We recommend TO-3 sockets for mounting the output transistors. Use a mica washer and heatsink compound for each transistor.

Use heavy duty insulated cable for all high current wiring. The type we used is known in the trade as "4mm auto cable". Connections to the filter

capacitor were made with the aid of crimped spade lugs, while connections to the bridge rectifier and mains switch were via Utilux push-on "quick-connectors".

Ventilation of the case is assisted by raising the lid so that there is a gap of about 8mm along the bottom of either side, and about 18mm at the top along front and back.

All of the components for this project should be available in due course from Dick Smith Electronics.

Now a few words about power dissipation and overvoltage protection. In


spite of reasonable emissivity obtained with the double-sided heatsinks, the output transistors and indeed the whole unit will become very hot when operated at full load. Normally, the output transistors and the bridge rectifier will run at about 75 to 80 degrees Celsius (case temperature). If it is necessary to operate with elevated ambient temperatures (40°C or above) or with mains voltage above 250V AC, it would be wise to run the unit with reduced loading (say 8 amps) or arrange fan cooling.

For those who worry for the safety of their equipment in the case of power supply failure which increases the 5V rail, we have designed an over-voltage protection circuit. This has been proved on the bench but was not incorporated into the prototype.

The circuit monitors the output of the regulator and if the voltage rises above 6.2V (depends on the tolerance of the zener diode) it trips an SCR. The SCR energises a heavy duty relay which blows a 15 amp fuse in series with the regulator.

The relay we used was a heavy duty automotive type with suitable coil and contact ratings. Horn relays are strictly not suitable, as they are designed for intermittent use only. Headlight relays are suitable.

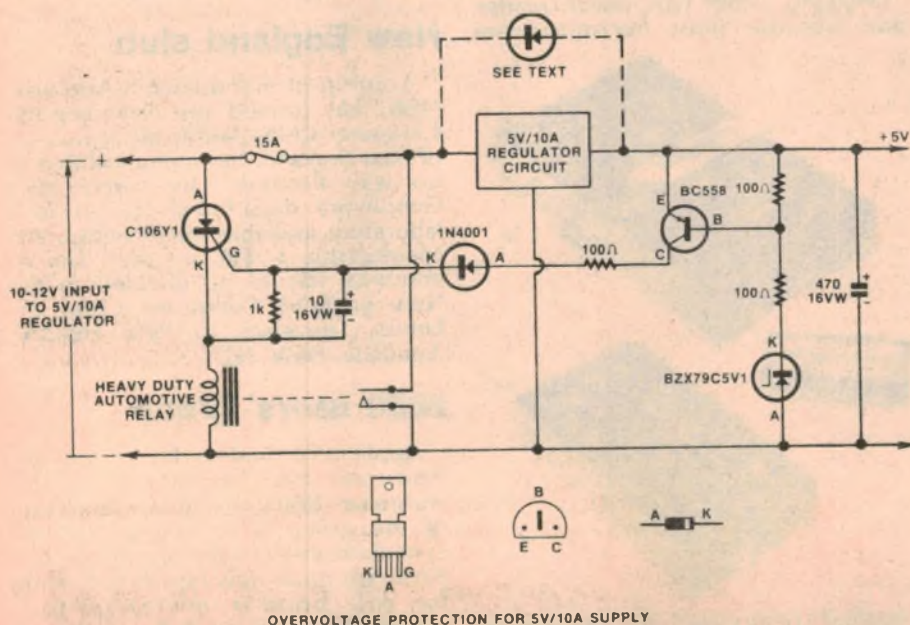The diode shown dotted on the circuit is intended to discharge external capacitors when the crowbar operates, and thus protect the IC regulator. According to the ratings of the IC regulators used, the diode should not be necessary. Nervous types who wish to install it should use a heavy duty automotive type such as the BYX21L/200.



OVERVOLTAGE PROTECTION FOR 5V/10A SUPPLY

This optional circuit will protect external equipment in the case of a breakdown in the power supply.

Microcomputer News & Products



Printer module

The Gay "Printina" OEM-S printer module is a compact, moderate-cost unit likely to be of interest to computer hobbyists and other small system users. It features noiseless, non-impact printing, on rolls of metallised paper as used by many of the modern calculators.

The module comprises a single printed-circuit board assembly, which integrates both the printing mechanism and the electronics. The module measures 180 x 110 x 40mm, and weighs 330 grams.

The printer accepts input data in bit-parallel, column serial form, in either 6-bit ASCII code or 4-bit BCD code if only numbers are to be printed. The full 6-bit ASCII character set of 64 characters is available. Printing is via a 7-electrode sliding head, giving standard 5x7 matrix characters. Printing speed is 1.2 lines per second, with typical lines of 24 characters.

The printer module runs from a single DC power supply of either 5V or



6-8V. It draws 150mA in standby mode, and 500mA peak when printing. Data input and control input levels are all TTL and CMOS compatible. The inbuilt character generator may be used for external purposes, such as a display.

Cost of the Gay Printina OEM-S in quantities of 16 or over is \$293 plus tax.

Enquiries to the Australian agents, Arlunya Pty Ltd, PO Box 113, Balwyn, Victoria 3103.

Cassette interface

The Applied Technology CT750 Cassette Interface has proved to be a popular peripheral for the computer hobbyist. Since its release in May 1977, demand has outpaced supply. Applied Technology has now rescheduled a faster production to keep pace.

As most users have found, the major advantage of the CT750 is that although it operates at the 300 baud "Kansas City" standard, it can be readily used at other speeds. In fact at 110 baud it virtually imitates the action of a "Teletype" paper tape punch/reader, and because most microprocessor

evaluation kits have a 110 baud serial interface this is the most common use of the CT750. Other features include the recovered clock (300 baud), LED status lights, TTL carrier detect signal (for software search) and internal clock facility.

To ensure long term reliability Applied Technology can now supply a test tape with full aligning instructions so the user can check the calibration of his CT750 at any time. The CT750 is available in assembled and tested form and carries a 12 months' warranty.

For more information contact Applied Technology Pty Ltd, PO Box 311, Hornsby, NSW 2077.

'Kilobaud' magazine

Although it commenced publication in only January this year, "Kilobaud" magazine has grown very rapidly and is now regarded by many as second only to "Byte" among the US computer hobby magazines. Like Byte, it carries many articles on custom hardware and interfacing.

Local hobbyists will no doubt be interested to know that Kilobaud is now being imported and distributed by the Byte Shop, at 17 Arawatta St, Carnegie, Victoria.

The cost per issue is \$3.50, which includes air mail postage from the USA. Back issues are available.

Enquiries to The Byte Shop, PO Box 156, Carnegie, Victoria 3163.

New England club

A group of enthusiasts in Armidale, NSW, has formed the New England Computer Club. Base is the University of New England, but membership is in no way limited. The University's Geophysics department has made a laboratory available for meetings, etc. Membership is \$10 per year, and all enquiries should be directed to the New England Computer Club, c/- Union, University of New England, Armidale, NSW 2351.

2650 users' group

Applied Technology Pty Ltd has announced the formation of the Australian 2650 users' group. Main aim of the group is to arrange for the systematic interchange of software and hardware notes now rapidly appearing for this popular microprocessor. Applied Technology will donate its own considerable software base to the group and Philips-Elcoma have agreed



Applied Technology CT750 Cassette Interface with cassette player and test tape.

kilobaud
The Small Computer Magazine

AN EXCITING NEW MAGAZINE
COVERING ALL
MICROPROCESSORS.

AVAILABLE FROM:

**MELBOURNE'S
BYTE SHOP**

at \$3.50 per issue

(Price includes Air Mail from USA)

Current Issue No. 11, Vol. 1
Back Issues available to No. 1,
Vol. 1

Please make subscription payable to

'BYTE'

P.O. Box 156, Carnegie, Vic. 3163.

SONTRON INSTRUMENTS

17 Arawatta Street
Carnegie, Vic. 3163


Tel.: 568-0642 or 569-7867

to make available all publicly released material.

At present a major software competition has been announced in the USA and a similar competition is planned for Australia to highlight the possibilities of the 2650.

For more information contact Applied Technology Pty Ltd, PO Box 311, Hornsby, NSW 2077.

Stackable RAM planes

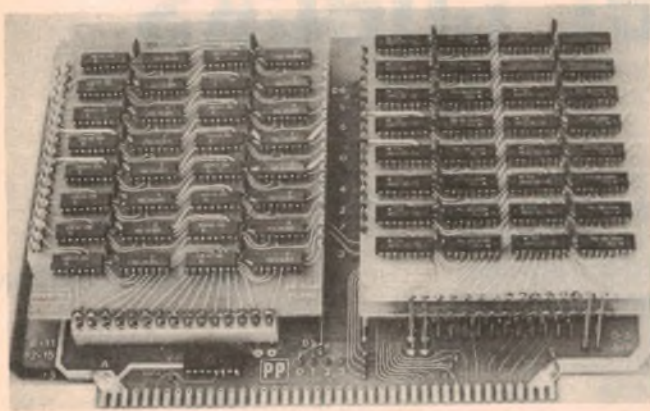

Pennywise Peripherals are now able to supply "RAM Plane" memory kits, based on 2102 static memory chips. The kits are based on a stackable printed circuit board module — the actual RAM Plane — which takes up to 32 chips to provide 4k bytes of memory. Each 1k byte segment on the PCB may be separately selected. The RAM Plane PCB is available by itself, or as part of a complete kit.

The firm also has a memory mother board, capable of accepting up to 4 RAM Plane cards to provide up to 16k of memory. The mother board has dual address buffers, decoding, data latches and receivers, and is especially designed to run off either a 6800 or 8080 system. The picture above shows a mother board with three RAM planes — one mounted via Molex sockets, and the other two simply via connecting wires.

RAM Plane PCBs sell for \$15.75 each; complete kits for \$89.30. The mother board comes as a kit for \$37.60. These prices include sales tax and postage within Australia, but sockets are extra. Enquiries to Pennywise Peripherals, 19 Suemar Street, Mulgrave, Victoria 3170.

Home computer from Tandy

The latest entry to the consumer computer market in the USA is the Tandy Corporation, which has just released a complete microcomputer system based on the Zilog Z-80 microprocessor. Called the TRS-80, the system is being marketed under the "Radio Shack" brand name, through selected stores in Tandy's chain of 5000 outlets.

The TRS-80 comes complete, not as a kit. It consists of four items: a keyboard/computer unit, a 30cm video display, a power supply and a data cassette recorder. Within the keyboard/computer unit is 4k bytes of dynamic RAM, 4k bytes of ROM, and a cassette interface. The ROM has a resident interpreter for BASIC programming, capable of handling floating-point arithmetic and numeric, array and string variables.

Price of this basic system in the USA is a very attractive \$599.95, with the keyboard/computer unit also available alone for \$400. A memory expansion option is also available, which expands the ROM to 12k bytes and the RAM to 16k bytes for an extra \$280.

On the software side, the TRS-80 comes with a cassette of computer games. Applications packages for business, education, home and personal finance are available, at between \$5 and \$20 each. Various peripherals are also coming — including a mini floppy disc and a printer.

As it stands, the TRS-80 is not directly suitable for Australia, but apparently Tandy is working on that, too.

CAE computer art
and education

ARE PROUD TO BE APPOINTED
DISTRIBUTORS FOR CROMEMCO
(T.M.)



Sequence from Cromemco's KALEIDOSCOPE software. This program runs without keyboard entry, gives you stunning color display.

As a **SPECIAL**
INTRODUCTORY OFFER
we have reduced the price of the Z-2
Mainframe

CROMEMCO MODULES AVAILABLE*

4 MHz CPU Card with Z 80 microprocessor	16 K Prom Card
4 K Ram Card	D/A and A/D interface
16 K Ram Card with bank select (Memory access time 200 nanoseconds)	TV Art digital interface
Bytesaver	TV Dazzler (needs only 2 K memory)
	Z-2D Disc Computer System
	Z-1 computer mainframe.

CROMEMCO SOFTWARE INCLUDES:

3 K Control Basic Monitor	16 K Basic
Resident Operating System assembler	Z-80 Macro Assembler
	Fortran IV
	Dazzler Games

***ALL CROMEMCO MODULES ARE S 100 BUS COMPATIBLE**

A bonus for established operators. Our software division is looking for debugged programmes for publication.

Send \$1.00 for catalogue and price list (refundable against purchases). Clubs note that we offer quantity discounts. Schools write for time sharing system (up to eight users). We provide full back up service on modules. Finance is available to purchasers.

Direct all replies to:
**COMPUTER ART AND
EDUCATION**

P.O. BOX 147, CROYDON, VIC. 3136
2 STEPHEN CRESCENT, CROYDON, VIC.
3136

Test tone generator for transmitter checks

Here is a handy test tone generator for checking the performance of AM, FM and SSB transmitters—and CB transceivers. It can also be used for setting up tape recorders and noise limiting systems. It provides either a single 1000Hz tone, or a 500/2400Hz two-tone signal, and output coupling may be either acoustic or electrical.

by IAN POGSON

There are many instances where a source of sine wave audio tone is required to make tests and measurements. The tone source to be described here has its main application for modulation testing of AM, FM and SSB transmitters and transceivers, but should also be useful for testing and setting up various pieces of audio gear.

For AM and FM transmitters (and transceivers), a single tone is required and 1kHz is a frequency commonly used. For SSB mode tests, a two-tone source is required and our unit provides for a composite tone consisting of 500Hz and 2.4kHz.

This unit should be useful to technicians who have the task of checking commercial communications equipment, including that for the Citizens

Radio Service. Also, amateurs will find it of use for checking either commercial or "home brew" equipment.

Where commercial equipment is to be tested with the tone facilities, ideally the tone(s) should be fed into the unit from the electrical output point. This may necessitate making up a test jig whereby a plug which fits the microphone input is suitably wired to cope with any push-to-talk facility, as well as feeding in the tone to the audio system. The other end of the cable will be fitted with a plug mating with the outlet provided on the Tone Source.

On the other hand, there may be reasons why it may not be convenient to feed the tone in electrically, either for test purposes, or for using the tone for MCW transmission purposes. We have there-

fore provided an alternative: using the transmitter's normal microphone, placed over the loudspeaker provided. For single tone use this method may normally be used quite satisfactorily. However, due to problems associated with the frequency response of the miniature speaker, combined with the microphone, it is not likely that this approach will be satisfactory for two-tone testing.

A look over the circuit should help to make the overall concept somewhat clearer. The basis of the unit is three sine wave oscillators, one each on 1kHz, 500Hz and 2.4kHz. These oscillators are identical except for frequency determining resistor values. The oscillators are based on the Wien bridge circuit, and use the 741 op-amp IC.


A .047 μ F capacitor in series with two resistors in parallel, and this in turn in series with another .047 μ F capacitor in parallel with two more resistors in parallel, constitute a Wien network in the positive feedback path. Two OA91 diodes in parallel with opposite polarities, in series with a 4.7k trimpot and a 5.6k resistor form the negative feedback circuit. Crossover distortion from the OA91 diodes is virtually eliminated by shunting them with a 1.2k resistor. A single power supply is made possible by adding a voltage divider consisting of two 1k resistors across the supply, with the junction forming the reference point.

Output from each oscillator is taken via a .047 μ F blocking capacitor, in series with a 390k resistor. The output from the 1kHz oscillator is taken to one pole of a selector switch. The outputs of the other two oscillators are tied together and taken to the other pole of the selector switch.

A 100k linear potentiometer follows the selector switch, as a level control. Output from the level control goes to the input of an LM380 audio amplifier IC. A 47k resistor is added across the + and



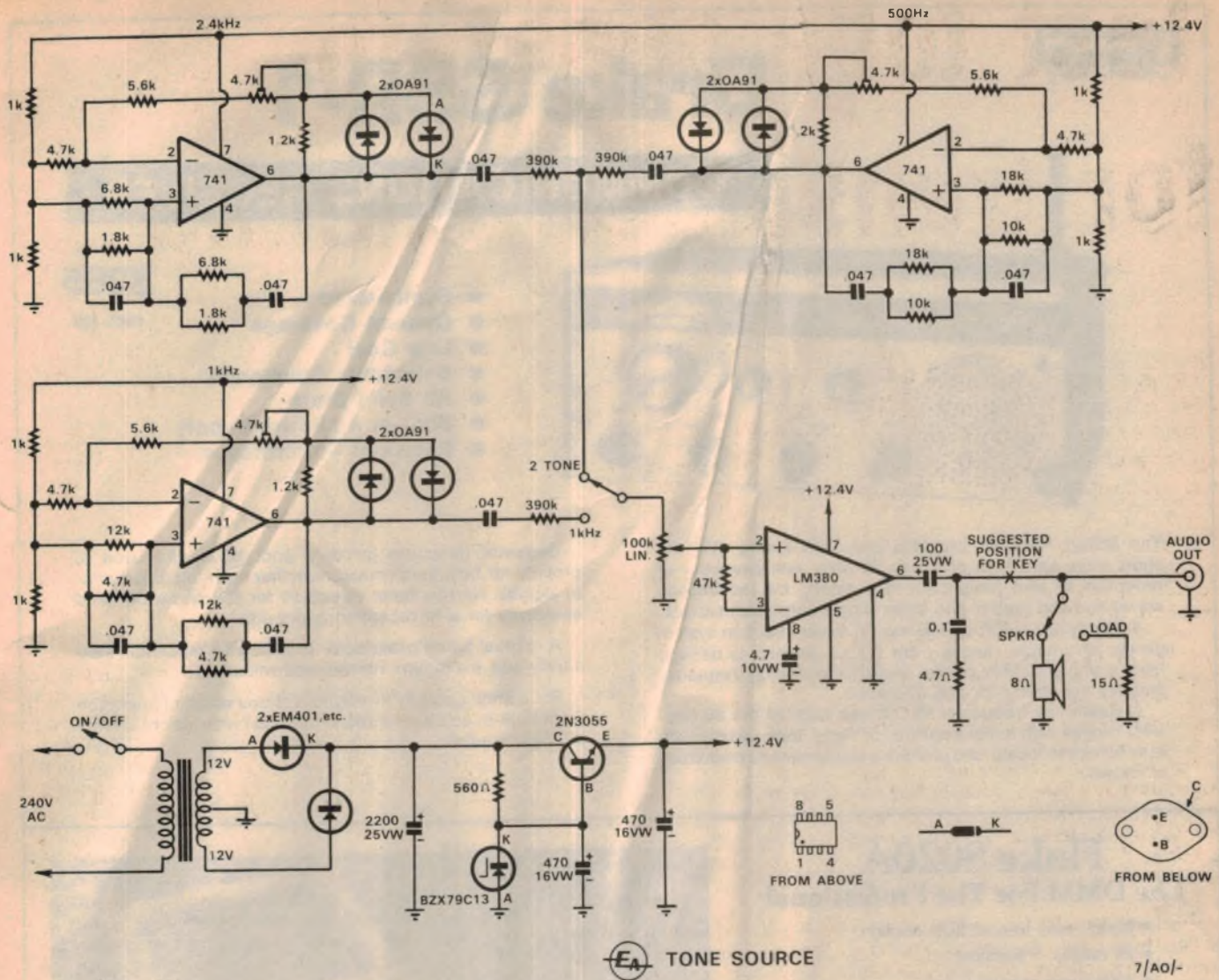The completed prototype provides either a single 1000Hz tone or a 500/2400Hz two tone signal. Coupling may be either acoustic or electrical.



—E_A TONE SOURCE

7/AO/-

— inputs to reduce sensitivity. Levels are adjusted to give a nominal audio output of about 100mW, which is adequate for our purpose. A stabilising network consisting of a 0.1µF capacitor and a 4.7 ohm resistor in series is connected across the amplifier output.

The amplifier output goes straight to an output socket as well as to a toggle selector switch. The switch selects either the loudspeaker or a resistive load. Heat sinking for the audio amplifier IC is via pins 4 and 5, to the earth copper on the printed board. Provided that the power output is kept to 100mW or so, this amount of heat sinking should be quite sufficient.

The power supply is a conventional type of series regulated circuit. Rectification is full wave, using two silicon diodes and a centre tapped transformer secondary winding. The series regulating transistor is a 2N3055 with its base referenced to a 13V zener diode. This provides a nominal regulated output at 12.4V. Adequate filtering is provided with one 2200µF and two 470µF electrolytic capacitors.

It may be questioned as to why such

a large power transistor is used for the series regulator when only a modest amount of current and power has to be handled. The reasons are that the 2N3055 is readily available, the price is low and even if the output should be short circuited, it is not likely to damage the 2N3055.

A few comments on components may be helpful. Resistors, capacitors, diodes, switches, the transistor and ICs are all readily available items and should present no problems. The printed circuit board should be available through normal components outlets. However, if any trouble is experienced in getting a board, no doubt they will be available directly from a number of manufacturers. Our board was kindly supplied by RCS Radio Pty Ltd in Sydney and supplies may be obtained from this source.

The power transformer is one of the regular catalog lines (PL24/5A) made by Ferguson Transformers Pty Ltd in Sydney. The printed circuit board is made to take this particular transformer but it may be possible to fit one of another make. Supplies of the Ferguson type should be available through the usual outlets.

The box with its aluminium panel is imported by Dick Smith Electronics and supplies are available from this source. Alternatively, your local supplier may be able to get one from Dick Smith for you. The same comments apply for the speaker. On the other hand, similar speakers should be available from other suppliers. Although we have specified the 51mm size, there is room on the panel for the 57mm size if one is more readily available.

Assembly of the unit is fairly straightforward but a few comments may be helpful. When fitting the components to the printed board, it is a good idea to start with the smaller items, such as resistors, diodes and the smaller capacitors. When soldering, it is important to make good soldered joints without overheating the components. To this end, a small but adequately hot soldering iron is required. Also, items requiring it should be orientated with respect to the correct polarity. This applies to diodes, electrolytic capacitors and ICs.

There are different schools of thought relating to the use or not of sockets for the ICs. There are arguments both ways

Drake SSR-1

COMMUNICATIONS RECEIVER



\$265

Incl. tax

- Synthesized
- General Coverage
- Low Cost
- Selectable Sidebands
- All Solid State
- Built-in Ac Power Supply
- Excellent Performance

The SSR-1 Receiver provides precision tuning over the short wave spectrum of 0.5 to 30 MHz with capability of reception of a-m (amplitude modulated), cw (continuous wave) and ssb (upper and lower single sideband) signals.

A synthesized/drift-cancelling 1st mixer injection system giving 30 tunable ranges from 0.5 to 30 MHz is derived from a single 10 MHz crystal oscillator providing frequency stability necessary for ssb operation.

A stable low frequency VFO tunes each of the 30 one-MHz ranges with a dial accuracy of better than 5 kHz which is sufficient to locate and identify a station whose frequency is known.

Separate detectors (product and diode) are used to provide for best performance whether listening to ssb or a-m signals. Narrow band selectivity for ssb and wide band selectivity for a-m reception is provided.

A manual tuned preselector provides for maximum sensitivity and maximum interference rejection.

Solid state circuitry throughout allows efficient operation from built-in ac power supply, internal batteries or external 12 V-dc source.

Fluke 8020A The DMM For The Professional

- Large, easy-to-read LCD display
- 26 ranges, 7 functions
- 2000-count resolution
- Leakage measurements to 10,000 M Ω
- Hi/Low power ohms
- Ten times more accurate than quality analog meters
- 10 M Ω input resistance, ACV and DCV
- Inexpensive 9V battery
- 200-hour battery life
- Low battery indicator
- Meets Mil-spec shock, vibration
- Three-way overload protection
- Autozero, autopolarity
- One-hand operation
- Single custom CMOS LSI chip
- Only 47 parts mean reliability
- Only 3 calibration adjustments
- Recessed input jacks and battery jack for operator protection
- One-year calibration and warranty
- Worldwide service
- Tilt bail for bench use

\$179

Excl. tax



ELMEASCO

Instruments Pty. Ltd.

Post Office Box 30, Concord, New South Wales, 2137.
Telephone: 738-2888

Melbourne: Post Office Box 107, Mt. Waverley, Vic., 3149. Phone: 233-4044
Adelaide: 42-6666 Brisbane: 392-2884 Perth: 325-3144

Tone generator


and the final choice is up to the builder. However, provided that the builder is sufficiently experienced in soldering, we consider that it is a better proposition to solder the ICs straight to the board.

With the smaller items fixed to the board, the larger items such as the electrolytics can follow, finishing with the power transformer. Leads from the board to such items as the switches, level control speaker, and audio output socket should be provided. The appropriate items may also be soldered to the leads in a temporary fashion, so that the unit may be tested and set up before being finally fitted to its box. The three leads of the power cord should also be connected up, without the run to the on/off switch on the panel.

Before proceeding further, a thorough check should be made to make sure that all items are in their proper place and correctly orientated. When you are satisfied that all is well, the unit is ready for testing. A word of warning at this point is to draw attention to the fact that the mains supply is terminated on the board. Precautions must be taken to ensure that accidental contact with these terminations is not possible—perhaps a piece of insulation tape stuck over the copper pads.

In order to carry out the testing procedure, a CRO is needed, preferably one that is calibrated. If it is not calibrated, then a high impedance AC voltmeter will be needed as well.

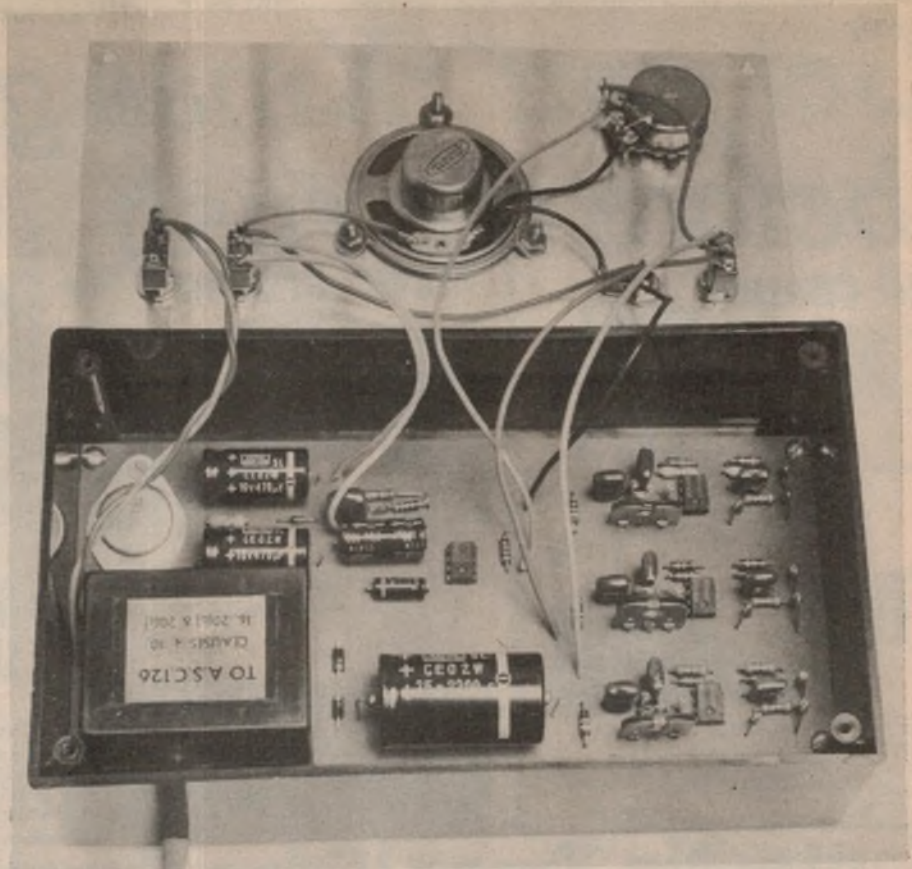Before switching on, set the three 4.7k trimpots to mid-position and the 100k level control right off. Switch on and measure DC voltage between the emitter of the 2N3055 and earth. It should be nominally 12.4V, although it is likely to depart from this value due to spreads in the zener diode. With a 5% tolerance




This internal view shows the prototype with wiring completed.

zener diode, the departure from the nominal 12.4V would be 0.65V either way.

To set up the oscillators, connect the probe of the CRO between the junction of the .047 μ F capacitor and the 390k resistor of the 1kHz oscillator. If there is no signal on the CRO the 4.7k trimpot should be rotated to increase its resistance, until a signal appears on the CRO. Now proceed to adjust the trimpot to get a signal which is 2V peak-to-peak. If the CRO is not calibrated, then an AC voltmeter should be connected in parallel with the CRO and the meter should read

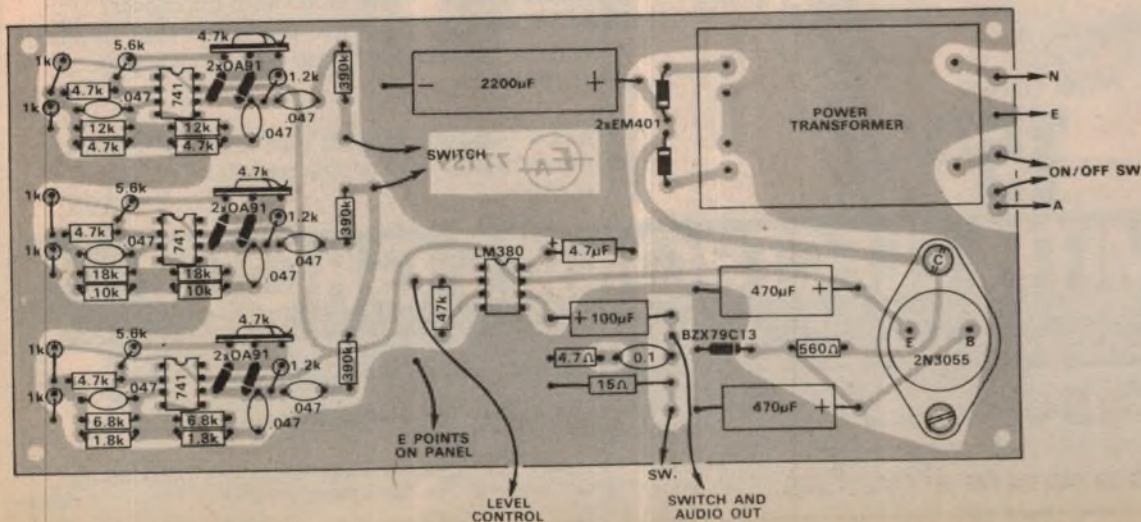0.7V RMS. Each of the other two oscillators should now be set up in the same way as for the first one.

It will have been noticed earlier that there are two pairs of parallel resistors in each oscillator. This has been done so that a suitable value of resistance can be arrived at to give the three nominal frequencies. For most practical purposes the frequencies obtained will be quite satisfactory. However, if you have a frequency counter and you wish to bring the frequencies closer to the nominal values, then this may be done by changing the appropriate resistors.




The component overlay diagram shows the PC board viewed from the component side.

Get your Xmas goodies before the rush




cb corner

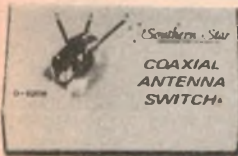

CO-ax switch
1175

New design antenna switch. Allows you to swap between antennas for best DX! Suits PL-259 plugs.
Cat D-5206 \$11.75

Filter
\$1050

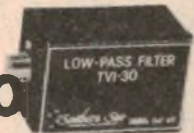

Cure your TVI troubles. As Cbers, TV interference can put you off air. Ensure your signals are clean with a low pass filter. Cheap insurance!
Cat D-7082 \$10.50

car stereo



auto reverse **\$115**

That's right! An automatic reversing car cassette for only \$130.00! Incredible value, high fidelity machine will really do your cassettes proud! You can select the program by pressing a button, or let it get to the end of the tape and the unit does it for you!
Cat. A-6486 \$115.00
(speakers not included)

SEE DICK SMITH FOR ALL YOUR CHRISTMAS GIFT IDEAS - EVERYTHING FOR THE HOBBYIST FROM COMPONENTS TO COMPUTERS, FROM TAGSTRIPS TO TOOLS - ALL AT EXTRA VALUE PRICES!

How about a bit of 'light' reading?



What do you give someone who wants to know more about a subject: A good book, of course. Here's a really authoritative book: An introduction to microcomputers. A whopping 1207 pages crammed with the good oil!
Cat B-2342

1950

1207 pages!



Here's the first volume of the above book. Real value for the novice computer brain!
Cat B-2340 . . . \$12.50

1250

Fantastic Xmas Video Game Bargains...

Greatest Kit value ever . . . The ETI 408 Video Game Kit is now being supplied with the fantastic AY-38550 IC which allows up & down as well as back & forth movement of bats!

This, plus the special price, makes the ETI 408 video game kit an ideal christmas gift. Keep the family amused over the long holidays ahead!

Has ON-SCREEN SCORING & SOUND!
NEVER BEFORE AT THIS PRICE!

Cat K-3432

47⁵⁰

Chips

We still have a few AY-38500 ICs in stock, at a VERY SPECIAL PRICE! They were \$19.75 each - NOW ONLY

Fish

Sorry - sold out.

15⁷⁵



FREE: Full details for converting your old video game to two-way bat control. Just ask!

Convert your old TV game to full TWO-WAY BAT CONTROL!!!!

First the bad news - your old TV game is out of date. New advances in IC technology have meant that TV games now have two-way bat control for more realism.

Now the good news. You can easily convert your old TV game to two-way bat control simply by replacing the IC with a new type. Pin-for-pin substitution - no more soldering or new components. Add a joystick pot to allow two-way movement and the job's finished.

THE PARTS YOU NEED:

- AY-38550 IC Direct substitution for the old AY-38500. Cat Z-6850 \$17.75 (Normally \$19.75 - save \$2.00 until Christmas!)
- JOY STICK POTS. Gives two-way action in an ingenious mechanical combination of two conventional pots. Cat R-1976 \$4.75

PRINTED CIRCUIT BOARD (just in case you've damaged the old one or wish to start again!)

Cat H-8605 \$3.50

DICK SMITH ELECTRONICS GROUP

SYDNEY - 125 York St. Ph: 29 1126.

GORE HILL - 162 Pacific Hwy. Ph: 439 5311.

BANKSTOWN - 361 Hume Hwy. Ph: 709 6600.

PARRAMATTA - 30 Grose St. Ph: 683 1133.

MELBOURNE - 656 Bridge Rd. Richmond. Ph: 42 1614.

399 Lonsdale St., City. Ph 67-9834

BRISBANE - 166 Logan Rd. Buranda. Ph: 391 6233.

THE AUSTRALIAN COMPANY.



Mail Orders: Box 747, Crows Nest, NSW.

Postage and packing is extra!

We have a network of dealers across Australia.

Tone generator

With the adjusting and setting up completed, the components may be fixed to the aluminium panel. The level control, switches and audio output socket each require one hole for mounting. However, the small speaker may either have one large opening about 40mm in diameter, or several small holes about 3/16in diameter may be drilled in a pattern to allow the sound from the cone. I prefer the latter at it provides some protection for the cone.

As there are no mounting holes provided on the miniature speaker, an alternative method must be used to fix it to the panel. Perhaps the most primitive method would be to glue it to the panel. Another way is to make up three small brackets which can be screwed to the panel, as well as forming clamps for the edge of the speaker frame. Possibly the easiest and a very satisfactory way is to drill three screw clearance holes in the panel, equally around and close to the edge of the speaker frame. Then with three screws, with washers and nuts, the speaker is secured in place.


So that a microphone may be placed face down, facing the cone of the speaker, some sort of padding is required between the two items. A piece of foam plastic or rubber about 13mm thick is ideal. There is no need to cut a hole to let the sound through from the speaker, as the foam is remarkably transparent in this regard. With the foam cut to size, it may be fixed in place with some rubber cement.

The foam padding which we used was a piece of scrap which happened to be handy. However, if you do not have a suitable piece already, then it should be possible to get some at one of the many shops selling foam in all shapes and sizes, such as Clark Rubber Stores Ltd in the Sydney area.

The unit should now be ready to be fitted to the box. The board is stood off the bottom of the box with four spacers, 1/2in length and tapped to 1/8in Whitworth. Four holes are required in the bottom of the box for mounting. Another hole is needed on one side of the box to pass the power flex. Immediately on the inside, the flex should be clamped and the leads are then terminated on the printed board, the circuit including the on/off toggle switch on the panel.

No wiring details are given for the interconnections to the items on the panel but there should be no problems here, as it is quite easy to wire them according to the circuit.


Some comments on the possible uses and applications of the Tone Source may be helpful. Firstly, there are two possible ways of taking off the signal, as already mentioned. Perhaps the simplest way is to use the microphone and speaker combination but as pointed out earlier, this has limitations as far as SSB testing is concerned. Fortunately, it is not difficult to make up a small cable with plugs to suit, along with a PTT switch. By this method, the microphone and speaker are eliminated and all methods of use may be done in this way.

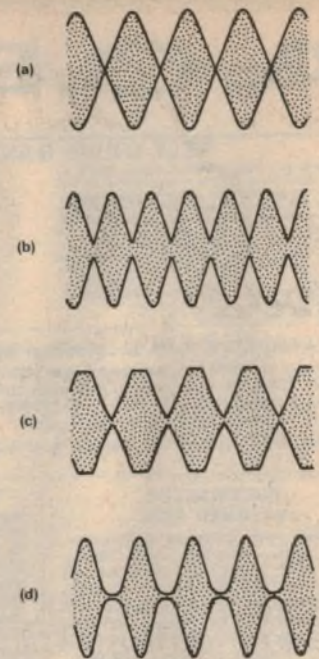

These patterns show what the signal could look like after passing through the transmitter, as viewed on a CRO. Refer to the text for an explanation of each.

When using the microphone and speaker method, the level required for proper modulation may be readily adjusted with the level control provided on the unit. However, when using the direct electrical takeoff, it may be a little difficult to set the level control precisely at the low level required. If this should be the case, then another potentiometer could be introduced into the cable assembly which is made up. Between the

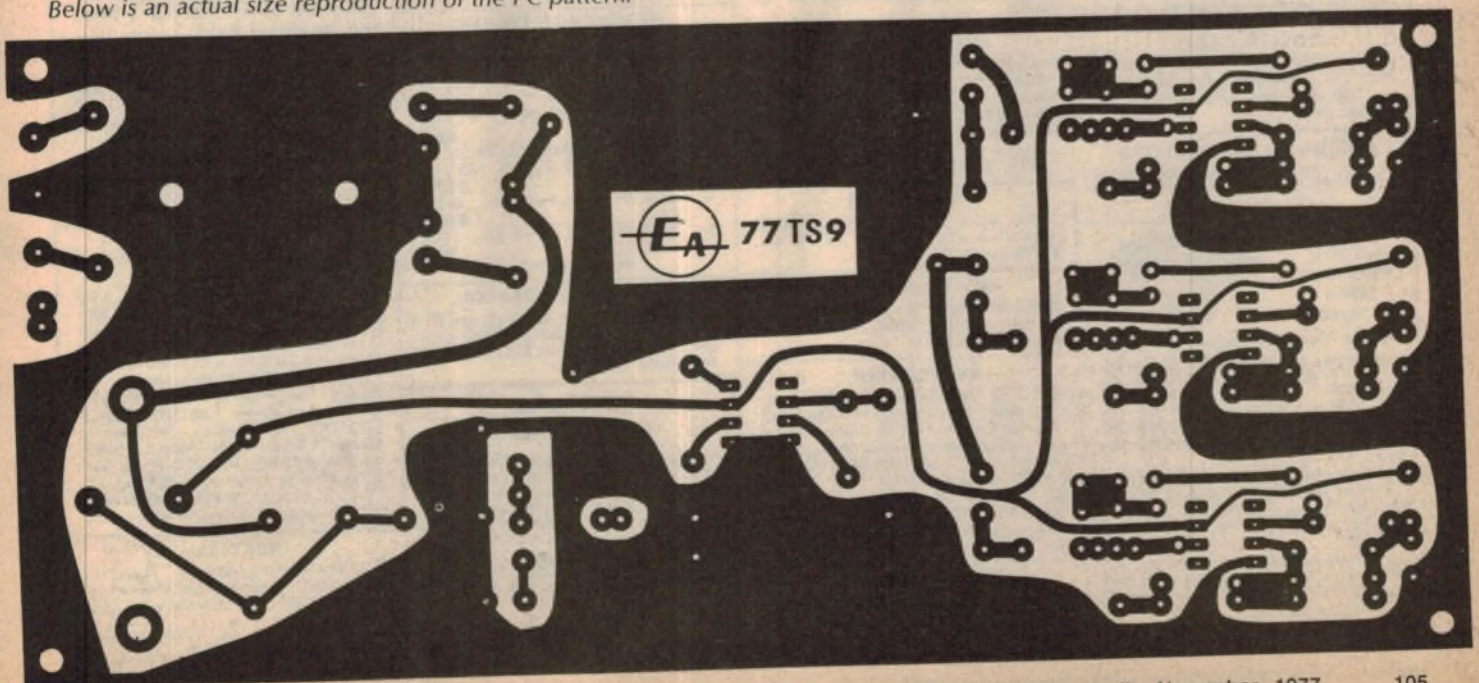Below is an actual size reproduction of the PC pattern.



BELT DRIVE GARRARD 35SB

An outstanding high performance 2 speed 33 1/2 or 45 r.p.m. stereo record player mounted in sleek limber base with tinted perspex cover. Features—auto repeating Viscous damped cue and pause control. Calibrated bias compensator adjustable to match stylus force. Low-mass tone-arm with adjustable counter-weight. Ball bearing pivots. Deep formed aluminium platter, dia 280mm 240v 50Hz synchro-Lab motor Wow and flutter 0.16% Rumble din A—39dB Din B—59dB. Min tracking force 1.5gms. Sonotone V100 magnetic cartridge with diamond stylus. Size 428 x 385 x 168mm. Limited stocks only p.p. \$5.50 Interstate \$8.50 FDN Rail Air Road



ONLY \$125.00

GARRARD MODEL 82

A superb 3-speed transcription changer/player. Auto/manual operation 4 pole magnetically shielded syn motor. Resiliently mounted. Counter-balanced. Elegant tone arm with slide-in cartridge carrier calibrated Antiskate. 265mm (10 1/2") Aluminium platter. Cue and pause control. Cartridge tilting lever. Magnetic cartridge diamond stylus. Size 375 x 335 x 170mm (14 1/4" x 13 1/4" x 6 1/4") 4.5kg (10lb) \$57.00 pp \$2.50 Interstate \$3.50. Base and Perspex Cover with hinges. Teak or walnut \$35.00. Freight NSW \$4.50 Interstate \$6.50.



PLAYMASTER 3-4IL Loudspeaker System

30 watts of excellent hi-fi. Beautiful teak or walnut veneered cabinets. Driven by the mighty 8-30 Woofer Smooth 6-25 mid-range Super sensitive Philips AD0160/T8 Tweeter. Specially designed frequency divider network.



\$199.00 PAIR Weight 40kg Dispatch Aust wide.

PLAYMASTER 40+40 STEREO AMPLIFIER

GREAT HI FI PERFORMER TOP VALUE



Quality components C-core transformer. Easy to build. Full instructions and circuit. Complete kit \$109.95. Fully constructed, guaranteed \$135.00. Freight, NSW \$3.50. Interstate, \$5.50.

PLAYMASTER SPEAKER KITS

Complete with Crossover components, grille cloth, innerbond tubes, instructions. 3-45 L Kit 8-30 Bass 6J Mid Philips AD0160 T8 Tweeter WT 4.5kg \$57.00. 3-41 L Kit 8-30 Bass 625 Mid Philips AD0160 TS Tweeter WT 5kg \$67.00. MV50 Kit 10-40 Bass 625 Mid 2X XJ3 Tweeters WT 5.5kg \$78.00.

MAGNAVOX SPEAKERS

Model 10/40 8 ohms 40w rms 30-8000Hz \$25.95
Model 8/30 8 ohms 30w rms 30-8000Hz \$19.00
Model 8wr 8 ohms 16w rms 30-16000Hz \$12.95
Model 6wr 8 ohms 16w rms 30-16000Hz \$12.40
Model 6/25 8 ohms 25w rms 45-6000Hz \$16.95
Dome XJ3 8/15 ohms 25w rms 2-20kHz \$9.35
6J 8 ohms 10w 80-7000Hz \$8.95 p.p. \$2.50 Interstate \$3.50

FM WIRELESS MICROPHONE

Cardioid Electret condenser type. Transmitting freq. range 88-106MHz. freq dev +75KHz. Field S. 50uV/MAT 50ft. \$27.95 pp. 80c



PHILIPS 80 WATTS

1" Dome Tweeter AD0161 T8 Resonance 1000Hz Freq 2000-22,000Hz \$14.95 each or \$27.50 Pair P.P. \$2.50 AD0160 T8 40 Watt \$13.60 ea or \$24.60 pair

CB COMMUNICATION EQUIPMENT TOP QUALITY • WARRANTY • AFTER SALES SERVICE

S.W.R. — POWER METER

Dual Meters Directional couple. Type 50-239 Coax Sockets Max Power 1kw Freq. Range 3.5-150MHz Imp 50 ohms \$24.50. Send SAE for Tech Specs. pp. \$1.50

SUPER PANTHER AT A SUPER PRICE

send SAE for tech data and quote.



BSR RECORD CHANGER



New Model C129 240V 50Hz 3 speeds 2 spindles Auto Manual operation. Cue lever. Stereo Ceramic cartridge \$20.00 p.p. \$2.50

GRILLE CLOTH MATERIAL

a1 quality 60in wide \$12.00 per metre. Send SAE for free samples

GOLDRING

ni-fi moving magnet stereo cartridge model E570 with diamond conical stylus Freq 15-25000Hz Output 5MV Ch bal 1.5dB at 100Hz Ch sep 20dB at 1000Hz Imp 3500 ohms at 1000Hz Tracking 1-2.5 grms 1/2in mounting \$8.50 pp 50c. Model E570 with diamond stylus and spare elliptical diamond stylus. Output 9MV, freq 10-30000Hz \$14.50 pp 50c

GOLD PLATED CONNECTORS FOR C-B

Suitable for installations to 200MHz. PL-259/G plug \$2.40. PLA 1/G adaptor for 58U 1/4in dia coax cable 70c. PL 258/G double female joiner \$1.60. M 258/G double male joiner \$2.40. M 358/G "T" type double female and one male \$3.95. M 359/G right angle male to female \$3.60 pp 50c

PYE SPECIAL

mobile C-B Antenna. 5ft helical. Extra strong. Not too whippy. Ready to mount, including base 12ft 52 ohm coax cable. PL-259 plug \$24.50 plus freight



PLESSEY ROLA

speaker special 12in 30W RMS. Model C12P/150 ohms. Two types available. Hi-fi cone. resonance 35/45Hz. Freq 7000Hz. Guitar cone. Resonance 70/80Hz. Freq 7000Hz \$15.00 pp \$2.50

AVO 8 MULTIMETER MOVEMENT

brand new replacement \$19.50 pp \$2.50

C-B POWER SUPPLY KIT

big saving & easy to build

10-13.8Vdc adjustable. 2 1/2A. Cont 4 1/2A surge. Sturdy vented metal case. Component screened f'glass PC board. Instructions circuit \$34.50 pp \$2.50

REFLEX HORNS

8inx5in ohms 15x \$24.95. 7 1/2inx4 1/2in 8 ohms 5W \$22.95. Each has mounting bracket. 5 1/2in round all metal anodised reflex trumpet, with adjustable swivel bracket. 8 ohms 8W \$6.95 pp 90c

FAIRCHILD TRANSISTORS

Type 2N 3054 10 for \$5.00 pp. 50c

POWER CABLE

250Vac. 7.5 amp 2 core. 23/0076 Black PVC sheathed. 25c per yd \$12.00 per 100 yds. Often used for hi-power speaker cable

AWA TV SPARES


last offer. End of stock. Valves, 4KG5, 6GS7, 10 for \$3.00. 6BM8, 6GV8 6 for \$3.00. 13 ch Solid State Matsushita TV tuner. \$8.00 pp \$1.00. 13 ch Value Tuner (6GK5 6GS7). \$2.00 pp \$1.00. 2in b/w CP/110 picture tube type 310. CF84A \$9.50 pp \$3.50

HI VOLTAGE POWER TRANSFORMERS

all 240V 50Hz primary.
1. 415-0-415V-180MA. 2x6.3V-1.6A 1x6.3V-3A \$12.50
2. 325-0-325V-200MA 6.3V-8A 5V-3A \$8.50
3. 0-285V-250MA. 2x34.2V-1A 6.2V-4.5A 6.3V-1A. 25V-1A \$10.00
4. 225-0-225V-250MA. 6.3V-8A \$10.00
5. 2x12.5V-1.8A 6.3V-5A. 110V-1.8A \$8.50
PLUS FREIGHT

SWR. POWER FIELD STRENGTH METER

\$20.50 pp \$1.50

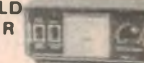

SANYO CADNICA

rechargeable battery Super special, Type A Penlight. Four for \$3.00 pp 75c.

TEST EQUIPMENT AT DISCOUNT PRICES

leader Audio Gen LAG26 20Hz-200kHz Sine/sq wave. \$132.00. LSG 16 RF Gen 100 kHz-100MHz, on harmonics 300MHz Int/ext mod. Output 0.1VRMS \$80.00. LDM 815 TR Dip Meter 1.5-250MHz with coils. \$88.00. Also available. Pal Pattern Gen. TV-FM Swam Gen. POA University USG-20M RF Gen. 120kHz-130MHz (Fund) 500MHz Harmonics RF output 100MV/100UV. Audio output 400Hz. Int mod \$75.00. UAG-22D Audio Gen. 20Hz-200kHz sin/sq wave. \$82.00. TE-15 GDO 440kHz-280MHz. \$62.00 plus freight. Send SAE for full technical data

SERVICE

Moderate Charges — Repairs Guaranteed. Radios, Tape Recorders, Cassettes, CB Rigs, PA Guitar Amps, Stereos, etc

AWA E-TONE 100 Watts RMS

15" Speaker



General purpose speaker for guitar, organ, bass guitar. PA cast aluminium frame. Cone type, straight ribbed, integrated surround 2" VC Dia magnet Wt. 13 1/2lb Flux 13,000 Gauss. Total Flux 236,000 Maxwells Freq. 40-5000Hz Imp 8 ohms Net wt 21lb \$99.00 Fon. Road, Rail, Air
12" twin cone 50 watts rms Freq. 50-15,000Hz V C Dia. 1 1/2" Magnet Wt 5lb. Net Wt 7 1/2lb. For vocals, amplified acoustic instruments 8 or 15 ohms \$49.00.
12" single cone 60 watts RMS Freq. 40-7000Hz V C Dia. 2" Mag Wt 6.6lb Net Wt 10lb. for guitar, organ, bass guitar, 8 or 15 ohms \$49.00.
P.P. NSW \$4.50 Interstate \$6.50

BEAT THE HEAT

With a new ceiling fan, motor speed control unit included 240V 50Hz \$13.00 Fon. Road, Rail, Air

TV BOOSTER

A VHF TV FM amplifier designed to improve reception especially in fringe areas (suitable for colour). 1 to 3 sets may be operated off the one aerial through the booster Gain. 1 set. 10&B54—88MHz 6.5&B174—216MHz 2 sets. 5&B54 88, 2&B174/216. 3 sets, no signal loss Noise 5&B54/88, 8.5&B174/216 Imp. 300 ohms 240 50Hz operation \$23.75 p.p. \$1.50

YAESU MUSEN FRG-7 Communication Receiver

These are the very latest model. Send SAE for specs and our low, low quote.

SERVICEMAN SPECIAL

Isolation transformer for bench use 6" x 6" x 6" Wt. 25lb Input 240V 50Hz output 250, 260, 275V at 500Va \$15.00 Fon. Road, Rail

EX-MUZAC PA AMPLIFIERS

240 Vac 50Hz operation. In good working order and condition guaranteed. Model 908A Hi. Imp Input (provision for Lo Imp. Mic. Transformer, but not supplied) 2 x KT66 output valves. Output Imp. 500, 125, 4 Ohms. Power 10 Watts. \$35.00. Model 920A Hi. Imp. Input 2 x KT66 output valves, output. 600, 250, 150, 4 ohms, 70V line. Power 20 watts \$45.00 FON By Road, Rail, Air.

WE REGRET THAT PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE.

Tone generator

If you wish to make use of the single tone for MCW use, then either method of takeoff may be used. In this particular case, by using the microphone and speaker method, there is a ready means of monitoring one's own transmission. The tone may be keyed by breaking the lead from the junction of the 100uF and the 0.1uF capacitors and the switch and "audio out" socket, and inserting the key in this line.

Use of the single tone for testing amplitude modulation may be achieved equally well by using either electrical or acoustic output from the Tone Source. The usual methods may be used, taking some of the output from the transmitter and feeding it into the Y plates of the CRO. Then the CRO timebase will be set to a suitable rate, thus giving the usual modulation envelope pattern. Alternatively, some audio may be taken from the modulator output and fed into the Z plates of the CRO. This gives a vertical line on the CRO when the carrier is unmodulated, changing to a triangle for 100% modulation. Either of the above patterns will deviate from the norm if there is some sort of distortion on the signal.

Modulation tests for the SSB mode are somewhat more involved than tests for the AM mode. A single tone may be used to check the performance of the final linear amplifier at peak signal conditions. However, this does not give any indication of the actual linearity of the amplifier. To do this, a two-tone audio signal is used. Two well-separated frequencies are chosen and when mixed together, form a beat with its characteristic pattern, at a rate corresponding to the difference between the two frequencies. The top one of the four patterns shown indicates what this looks like on the CRO when the CRO timebase is correctly adjusted.

The two tone frequencies which we have chosen are at 500Hz and 2400Hz. These will give a beat or repetition rate at 1900Hz. With the timebase on the CRO set to about one fifth of 1900 in terms of sweeps across the face of the tube, you will get the pattern as shown in the top figure.

Perhaps it would be well to mention at this stage that in cases where the actual bandwidth of the transmitter is less than 2400Hz, then a lower frequency may be chosen. As an example, 800Hz and 1800Hz are sometimes used.

Let us take a look at the rest of the patterns shown and what they mean when viewed on a CRO, after the signal has passed through the transmitter. As mentioned earlier, the top signal is as generated by the Tone Source and if this is the

PARTS LIST


- | | | |
|--|--|-----------------------------|
| 1 Zippy box 196mm x 113mm x 60mm | 1 0.1uF 100V greencap | |
| 3 Miniature toggle switches, SPDT | 1 4.7uF 10VW electro | |
| 1 RCA single hole mounting coax socket | 1 100uF 25VW electro | |
| 1 100k linear potentiometer | 2 470uF 16VW electro | |
| 1 Knob | 1 2200uF 25VW electro | |
| 1 Miniature speaker, 51mm diameter, 8 ohms | RESISTORS (½W unless stated otherwise) | |
| 1 Printed board 190mm x 86mm, code 77T59 | 1 4.7 ohms | 2 6.8k |
| 4 Spacers ½in long tapped ½in Whitworth | 1 15 ohms | 2 10k |
| 4 Rubber feet for box | 1 560 ohms | 2 12k |
| 1 Foam plastic pad 107mm long x 60mm wide x 13mm thick | 6 1k | 2 18k |
| 1 3-core power cord 2 metres | 3 1.2k | 1 47k |
| 1 3-pin plug | 2 1.8k | 1 100k linear potentiometer |
| 3 ICs, 741 8-pin DIL | 5 4.7k | 3 390k |
| 1 IC, LM380 8-pin DIL | 3 4.7k trimpot | |
| 1 Transistor 2N3055 | 3 5.6k | |
| 6 Diodes OA91 or similar | MISCELLANEOUS | |
| 1 Zener diode BZX79C13 | Hookup wire, solder, screws, nuts, clamp for power flex. | |
| 2 Power diodes EM401 or similar | NOTE: Resistor wattage ratings and capacitor voltage ratings are those used on the prototype. Components with higher ratings may generally be used, providing they are physically compatible. Components with lower ratings may generally be used, providing ratings are not exceeded. | |
| 1 Power transformer, Ferguson PL24/5VA | | |
| CAPACITORS | | |
| 9 .047uF 100V greencap | | |

pattern also which emerges from the transmitter, then the transmitter is correctly adjusted. The second is due to a fault in the generator, in that the two tones are not equal in amplitude. This should be put right before further tests are undertaken.

The third pattern shows a considerable amount of clipping, due to excessive drive. The fourth pattern indicates that the bias applied to the linear amplifier is wrong and should be adjusted to get the "X" type of crossover as shown in the top pattern.

While it is outside the scope of this article to describe a full test setup for SSB transmitters, a brief description of what is normally required may be helpful. As already indicated, the two tone signal is injected into the microphone input of the

transmitter. The output of the transmitter is fed into a dummy load to suit the transmitter with regard to impedance and power rating. In the line between the transmitter and dummy load is inserted a pickup device so that a small amount of the signal may be tapped off and fed into a tuning unit, tuned to the output frequency of the transmitter.

 The usual procedure then is to connect the output of the tuned circuit across the vertical deflection plates of the CRO. However, with many modern CROs, the facility to gain access to the vertical plates is lacking. Presumably in these circumstances, and provided that the CRO vertical amplifier has sufficient bandwidth, the output of the tuned circuit could be fed to the vertical amplifier input of the CRO. 

BASIC ELECTRONICS

Basic Electronics, now in its fifth edition, is almost certainly the most widely used manual on electronic fundamentals in Australia. It is used by radio clubs, in secondary schools & colleges, and in WIA youth radio clubs. Begins with the electron, introduces and explains components and circuit concepts, and progresses through radio, audio techniques, servicing, test instruments, etc. If you've always wanted to become involved in Electronics, but have been scared off by the mysteries involved, let Basic Electronics explain them to you.

\$3.00 plus 60c p & p

FUNDAMENTALS OF SOLID STATE

Fundamentals of Solid State provides a wealth of information on the structure, principles, operation and applications of Solid State devices. It begins with atomic theory. Successive chapters cover: diode types; unijunction, field-effect and bipolar transistors; thyristor devices; device fabrication; and microcircuits. A glossary of terms and an index complete the 120 pp book. Adopted as a text by many colleges, Fundamentals of Solid State is ideal for amateur, hobbyist, engineer and student.

\$3.00 plus 60c p & p

Electronics Australia, Box 163, Beaconsfield, NSW 2014.

M.R. ACOUSTICS

P.O. Box 110, Albion, Brisbane 4010,
present the quality range of QED audio accessories from the U.K.

SPEAKER CONTROL CONSOLE

This stylish console provides control over two pairs of headphones and up to four pairs of speakers, any combination of which can be selected without the risk of damaging an expensive amplifier. (See specification.) Being suitable for either surface or flush mounting, the speaker control console will provide the answer to your multi speaker home installation problems.



Technical Specifications

Size (mm): 130 x 100 x 50
Colour: White panel with surface mounting box
Switches: Rocker Type
Current Rating: 5 amps (150 watts RMS)
Headphone Outlets: 1/4" Stereo Jack sockets
Loading: Using 8 ohm speakers the impedance never falls below 4 ohm

Termination: Screw Terminal (Wire entry through underside of box)
Mounting: Surface or Flush (Screws supplied)
Wiring: Independent earth
Functions: 16 combinations of pairs of speakers. All speakers can be turned off without damaging the amplifier.

\$35 each R.R.P.

TAPE SWITCHING UNIT

Many amplifiers have facilities for connecting only one tape recorder. Now, with the addition of this new tape switching unit, three compatible tape decks (whether reel to reel, cassette or cartridge) can be connected and operated without having to change leads by hand.

The controls provided allow for inter-recording between machines as well as playback and record from either. Simultaneous recording onto all three machines is also possible. Monitoring can be from the source or via the monitor output socket fitted to most tape decks. Fitted with 5 pin DIN sockets.



SIZE (mm) 130 x 100 x 50

\$32 each R.R.P.

SPEAKER MOUNTING BRACKETS

● Specifically designed for mounting lightweight speakers ● Can be "locked" in correct position after fitting ● Precision made (Black etch stove finish) ● Easy and safe to fit ● Complete with screws and rawlplugs

Advantages of using Mounting Brackets

- (1) Isolating speakers from each other and the rest of the Hi-Fi system can reduce the risk of acoustic feedback and unwanted shelf resonances.
- (2) Speaker angle can be adjusted to obtain the best stereo image.
- (3) As the Brackets cannot be seen when in use, there are fewer restrictions as to where speakers can be mounted.



SIZE 127mm x 51mm (CLOSED)

\$13 pair R.R.P.

SPECIFICATIONS —

Horizontal Movement: Up to 130 degrees **Maximum Loading:** 15lb (7kg)
Material: 16 SW G (Steel Plate). Finish: Black Etch Stove

DISC SWITCHING UNIT

Very few amplifiers have facilities for connecting two record player decks (with magnetic cartridges). The Disc Switching Unit enables two such decks to be connected and controlled without changing leads by hand, suitable for wall mounting and fitted with professional quality phono sockets.

Technical specification

Size (mm): 100 x 65 x 50
Colour: White panel with black surface mounting box
Switch: 2 position rotary

Termination: 6 off phono sockets professional quality
Connecting leads: A total of three ohono to phono leads are required.



\$21 each R.R.P.

LIGHT SWITCH SUPPRESSOR

Radio frequency interference generated by domestic light switches and reproduced via the audio system in the form of "clicks" etc, can now be overcome simply and quickly by using the Light Switch Suppressor, easy to fit — no soldering! Supplied in display pack complete with full instructions — one suppressor required for each light switch.

Please note: When used for suppressing fluorescent lights, the suppressor should not be fitted to the light switch but to the mains input terminal block on the light itself.

\$3.50 each R.R.P.



Input Comparator/Output Comparator

These Comparators have been designed to provide an economic and reliable means of comparing record decks, tape decks, amplifiers and loudspeakers. The separate input and output units allow for a greater freedom of choice when deciding what facilities are required.



Input Comparator specification

Tape Inputs: Six
Disc Inputs: Six
Amplifiers: Six
Sockets: 5 way 180 degree professional quality DIN sockets
Case Size (mm): 432 x 127 x 64
Case Finish: Anodised aluminium panels with extruded sections. Black leather textured PVC top. Supplied with rubber feet
Wiring: Fully screened

Output Comparator specification

Amplifiers: Six
Speakers: Twelve Pairs
Sockets: 2-way DIN
Case size (mm): 432 x 127 x 64
Case Finish: Same as Input Comparator
Wiring: Independent earth

Trade enquires — price on application

SPEAKER VOLUME CONTROL

Order code 4/3 & 4/4*

The Speaker Volume Control has been designed to provide "in-room" control over the volume of an additional pair of speakers remote from the main amplifier. This product is particularly suitable for persons requiring speakers in several rooms, whilst still being able to control each pair individually. It is also possible to turn off this control without affecting any others.

Technical specification

Size (mm): 130 x 100 x 50
Colour: White panel with black surface mounting box
Switches: 5 position rotary
Power rating: 40 watts RMS
Loading: Constant impedance

Termination: Screw Terminal (wire entry through underside of box)
Mounting: Surface or Flush
Wiring: Independent earth

*Use model 4/3 for 8 ohm speakers and 4/4 for 4 ohm speakers.



\$39 each R.R.P.


CABLE CLIPS

This range of self adhesive cable clips provides the ideal answer to securing cables of up to 19.00mm dia. They are quick, neat and easy to use.

The adhesive used is strong, long lasting and acts instantly. The polyethylene pad also provides a high level of insulation.

Technical specification

Clips per pack	Order code	Base size	Maximum cable dia.
30	13/1	11 x 16mm	6mm
20	13/2	15 x 19mm	10mm
15	13/3	12 x 26mm	12.7mm
12	13/4	16 x 26mm	19mm

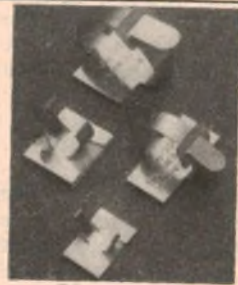

Packs \$2.08 each R.R.P.

QUADRAPHONIC SYNTHESISER

This "surround sound" adaptor attempts to provide some impression of the missing ambience present at all live performances. This information, normally lost when using conventional two channel stereo equipment, is present on all stereo programmes, whether disc, tape or radio.

The rear blend control featured in this unit allows complete control of the directional information between the rear speakers, resulting in a much improved spatial sound and a closer approach to realism.

Connecting simply to the output of most stereo amplifiers, the QED Synthesiser provides, with the addition of two speakers, that extra dimension felt when attending a live performance.



SIZE (mm) 130 x 100 x 50
\$32 each R.R.P.

A new product due by approximately end of the year —

A six-outlet mains distribution unit with mains interference suppressor built in. Suppressor operates on all outlets with total power of 1500 watts (6.3 amps). Australian plug and sockets fitted, and lead is 2 1/2 metres long. This neat and effective unit, comprising black box with white panel and sockets, measures only 200mm x 130mm x 90mm. R.R.P. expected to be \$43.

Available from Hi-Fi stores or direct from M.R. ACOUSTICS
Add 50c pack and post for Light Switch Suppressor, \$1 for each other item. Extra 50c gives certified mail insurance cover. Trade enquiries welcomed.

Classical Recordings

Reviewed by Julian Russell



Elgar — Overture in the South

ELGAR — Overture In The South (Alasio). VAUGHAN WILLIAMS — Fantasia on a Theme by Thomas Tallis. Overture The Wasps. Bournemouth Symphony Orchestra conducted by Constantin Silvestri. HMV Greensleeve Stereo Issue ESD7013.

To many, the name Bournemouth Symphony Orchestra might well suggest an English seaside band playing on a pier on a summer afternoon. Nothing could be further from the truth.

Oldtimers still talk of it being quite good back in the distant days of Dan Godfrey. But under the incumbency of the Rumanian conductor, the late Silvestri, it developed into an orchestra any Australian capital city might well be proud of. Those who heard his sumptuous recording of Rimsky-Korsakov's "Scheherazade" some years ago will remember the players' glowing sound and the conductor's delightful freewheeling style. They will not be disappointed with this budget priced issue of the same combination in the items listed above.

Silvestri, though Rumanian, was in complete sympathy with Elgar's music and those who remember Elgar's own style when conducting will recall that he was by no means a reticent director, especially of his own music. Silvestri starts "In The South" with just the right jauntiness and follows it with a theme so Elgarian that though it was inspired by the Italian scene it was unquestionably an Italy seen through English eyes as, of course, it was intended to be.

It is hard to understand why this fine overture is comparatively neglected in favour of the no better but just as beautiful "Cockaigne Overture", so popular with England's ex-Prime Minister, Edward Heath. All the first desk players are excellent and I must add a special word of praise for Cedric Morgan's lovely viola solo.

Silvestri moves without effort from the dolce far niente Italian atmosphere to the passage descriptive of the departed glory of the ancient Roman Empire. During the work the viola solo calls up a picture of the composer lying relaxed in the unaccustomed sunshine. The orchestration is of course magnifi-

cent especially in Elgar's characteristically magnificent scoring for the brass.

There are many treasures in this work and if some of them owe allegiance to Richard Strauss, there are many that are true Elgar. The sound is fine and resonant. By the way I must mention that on my pressing the labels had somehow got stuck on the wrong sides — not a very worrying error if you happen to know the pieces played.

In Vaughan Williams' great "Tallis Variations", Silvestri shows just the same understanding of this composer as he does of Elgar. Here is a performance I praised very highly when it was first issued some years ago. It has spaciousness and majesty, and I still react to it with the same enthusiasm.

Despite the conductor's markedly

HAYDN — Symphony No. 95 in C Minor. Symphony No. 101 in D Major (The Clock). Fritz Reiner and his Symphony Orchestra. RCA Stereo AGL1-1275.

This is another "recreation" of a 1964 recording, though in this Reiner uses what is described as "His Symphony Orchestra". There is no explanation in the sleeve notes as to who the players were or any account of its founding.

But whoever they were they were very good. Tonally I found this disc a shade more modern sounding than the one reviewed above, perhaps because of the lighter scoring and also the improvement in the original engineering which was produced some eight years after the Brahms Third.

Reiner's readings of both the Haydn Symphonies are very stylish indeed. Their dynamic proportions are always kept within the bounds of the composer's 18th century orchestration. His phrasing is a total delight and I can't imagine anyone guessing that the disc was remade from a 13-year-old original.

Some parts of "The Clock" sound as delicate as some of the very best contemporary engineering. Also Reiner, whenever he sets a tempo, as in the "Clock Symphony", sticks to it tenaciously. Any slight variation he introduces is due to logic and impeccable taste. True this metronomic beat is what

romantic temperament it is none the less a noble reading and it would be difficult to imagine two more different personalities than the mercurial Silvestri's and the granitic Vaughan Williams'. Yet if you follow Silvestri's passionate interpretation with a score you will see that he takes surprisingly few liberties. I am sure grand old VW would have loved it. At any rate it moved me deeply.

The acoustics are fine and it is worthy to appreciate that, while the Elgar was recorded in the Bournemouth Winter Garden, Winchester Cathedral was chosen for the Tallis. The Cathedral has exactly the right resonance and reproduces superbly identification of the three separate string groups.

But the same praise would be out of place for the performance of the overture "The Wasps". Here resonance and reverberation are very much out of place. Add to this Silvestri's unusually fast tempo and I found myself wondering why I enjoyed it so much. The piece is marked *allegro vivace* but Silvestri's speed is much closer to a *presto*, though he does spread the music out grandly in the slow middle section!

The combination of this speed and the reverberation makes some of the loud passages sound confused and the echos of the final chords sound simply silly. However, don't be put off by the faults of this comparatively minor piece, but enjoy instead the pleasure of listening to the two main ones.

has given the first movement of "The Clock Symphony" its nickname.

If you want to quibble the last two chords are not attacked quite as un-animously as they might be. A pity, but you'd have to be pretty churlish to complain. Throughout both symphonies, the dynamic variations are always decorative enough to rivet admiring attention.

There is a tendency to treat Haydn's symphonies nowadays, especially his later ones, rather more weightily than Reiner does. But, to me, Reiner strikes just the right medium. I admit that others might think Reiner's treatment a trifle too dainty but none could challenge his perfect judgement of contrasts and tempos. This, too, is issued at a budget price and I consider it a great bargain.

☆ ☆ ☆

BRAHMS — Symphony No. 3 in F Major. Chicago Symphony Orchestra conducted by Fritz Reiner. RCA Stereo AGL1-1280.

This is a remastered reissue of a performance recorded back in 1958, and a very good job has been made of it. The sound is very clear and usually well balanced though the strings are a bit wiry. There is no surface noise to betray its origin. I found I got the best result

FRESH 1977 STOCK ELECTROS

1000 MFD	10volt	10 for \$1
47uF	35v	10 for \$1
47uF	16v	10 for \$1
47uF	200v	5 for \$1
47uF	25v	5 for \$1
220uF	10v	10 for \$1
0.39uF	160v	10 for \$1
500 MFD	12v	5 for \$1
70 MFD	45vac	5 for \$1
47uF	160v	5 for \$1
6.8uF	1500v	10 for \$1
15uF	400v	5 for \$1

PHILIPS MONO PICK-UP CARTRIDGES \$3.50

POWER TRANSFORMERS

60 MIL 240V 245 ASIDE 6.3 \$5.
80 MIL 240V 245 ASIDE 6.3 \$6



SPEAKER TRANSFORMERS

7000 to 15/OHMS \$1.75
1200 to 15/OHMS \$1.75
7000 to 3.5 OHMS \$2.50

TRANSISTOR 7 RADIO

Complete with 3 1/2 inch speaker
No cabinet \$3.95

PHILIPS 110 DEG EHT
TRANSFORMERS \$10

B.S.R. CERAMIC STEREO \$5
Pick up Cartridges Universal Type

LEVEL AND BALANCE METERS



12,000 ohm 10Q Microamps \$2

SLIDE POTS 50k 4 for \$2

Special miniature transistor pots
10k 4 for \$1

Special miniature tuning condensers
for transistor radio 2 for \$1

SOLID STATE 10 WATTS

PER CHANNEL
Stereo Amplifiers complete except
power supply \$10

PHILIPS
110 DEG
YOKES \$10



POTS

1/2 Meg switch 50 cents
10K switch 50 cents. 1 Meg 50
cents. 1/2 Meg 50 cents. 100K
switch 50 cents. 250K 50 cents.
7500K 50 cents. 25K 50 cents.
Dual concentric 500K 1 Meg \$1.
Dual concentric 50K 25K \$1. 1
Meg Dual ganged log \$1. 1/2 Meg
dual ganged double pole switch \$1.
2 Meg dual ganged Lin \$1. 1 Meg
dual concentric \$1. 500K min 4 for
\$1. 10K min 4 for \$1.

SPECIAL

25 mixed transistors and diodes \$2



SUPER SPECIAL OUTPUT TRANSISTORS

AD 161
162 K5 \$2.50 A PAIR

SLIDE SWITCHES

4 mixed types 4 for \$1

SLIDE POTS 250K 4 for \$1
1 Meg 4 for \$1

MICROPHONES
plug and lead \$2.50



GRAMOPHONE MOTOR
and Turntable 3 speed \$3

SPECIAL PICTURE TUBES

17 inch 90° new
\$10.00

POWER DIODES
0A636 1000 v 50 cents

VU
METER
\$3.00 pair

Gramophone
Motor & Pickup
B.S.R. 4 Speed
\$7.95



BASE AND PERSPEX TOP

for record player
Size 17 1/2 x 13 1/2
x 6 1/4 \$10
Pack & post \$2.50. Interstate \$3.50



CONVERGENCE BOARDS
for Colour T.V. Complete \$4

PICK UP ARM

balanced
complete
with ceramic
cartridge \$9



SPEAKER
CABINET includ-
ing 2 dual cone
speakers, 6 1/2
inch 10watts
RMS \$16. Size
16 1/2 x 10 1/4 x 8.
Pack & post Inter-
state \$5 a pair,
NSW \$3.00.



Super
Special
Record
Player
\$12



VALVE
TYPE
13 CHANNEL



SPEAKER SPECIAL
2 1/2 INCH 8/Ohm 2 for \$1.

SPEAKER AND
CABINET
Size 10 x 7 1/4 x 4 \$4
incl 6 x 4 speaker

PHILIPS TV TUNERS
Transistor NT3032
\$10



POWER TRANSFORMER
300 mil 240 volt: 115; 110: 6.3 \$5

POWER LEADS

for tape recorders,
etc 75 cents



CAR RADIO

push button
tuner \$3



TELESCOPIC AERIALS

\$1.50

3 position
push button switch
50 cents



POWER TRANSFORMER
240 volt, 180 volt, 6.3 V 40/mil
\$2.50

BARGAINS BARGAINS BARGAINS BARGAINS

Hook up wire 30 mixed colours \$1.
250 mixed screws with self tappers, bolts,
nuts, etc. \$1.25 + postage 50c.
100 mixed radio TV knobs including fine
tune & channel change \$5.00
1/2 meg double pole switch pots 50c.

Mixed pots 30 including ganged & con-
centric \$5.

Morganite & IRC 33 useful valves fresh
stock \$2.00 + postage 50c.

Slide switch 3 position 50 cents

50 ohm Pots ideal for ext. Speakers 50
cents. Transistor and Driver Speaker
Transformers \$1.00 pair. Ferrite Rods 6 1/2
x 1/2 inch 50 cents.

Pots 30 mixed values including ganged
and concentric \$5

In Line Fuse Holders 20 cents Stereo
Speaker Wire 12 cents yard

100 Mixed TV and Radio Knobs including
Fine Tune and Channel Change \$5

Car radio suppressor condenser 30
cents.

Special—Stereo Amplifier 3 watts per
channel RMS. 240 volt bass & treble
boost controls. Includes fancy chrome
face plate \$10.

Electros 3 in one 100-25-40,
24-250-300, 50-250-300 75 cents.

Screw in 6 Volt Pilot Lights \$1.50 for 10
Plug-in type 10 for \$1.00

3.5 to 3.5 Jack Plugs 7h Shielded Cable
75 cents. 6.5 to 3.5 Jack Plugs 7h
Shielded Cable 75 cents.

Mixed Tag Strips 50 cents for Dozen

Special Fancy chrome knobs. Ideal for
amplifiers. 5 for \$1

Tape Recorder Heads Transistor—Top
quality suit most recorders \$5.00.

Jack Plug Sockets 6.5 mm 35 cents.

Morganite and IRC resistors 33 values \$2
per 100 pack and post 45c.

Philips Gramo Motor and Pickup 4 Speed
6 Volt \$7.75

Crossover Condensers 2 mld 60 cents.

Crystal Microphone Inserts \$1.00

Microphone Transformers 50 cents.

Switch Wafers: 11 position 20 cents

Perspex tops for record players size
12 x 8 1/2 x 3 1/4 \$1.50

Pots 50k 50 cents: 1M 50 cents.

Tape Spools: 7 inch 75 cents. 1/2 Meg
Double Pole Switch Pots 50 cents

Coaxial TV Feeder Cable 75 ohm 30 cents
yard.

Jack Plugs 6.5 mm 50 cents. 3.5 mm 25
cents. R.C.A. Plugs 25 cents.

Hook Up Wire 30 mixed colours lengths
\$1 bag.

Speaker 4 pin plugs 15 cents. 25 mixed
and 5 and 10 Watt resistors \$2.00.

250 mixed screws BSA. Whit self-tapper
bolts, nuts, etc. \$1.25 bag plus 40c
post.

TV Aerials Complete Range Hills Color
\$12 to \$60.

Car radio aerials, lockdown, top quality
extended 1600 mm \$4.50.

Electros 3-in-one 20 400 450 10.

400. 450. 75. 50. 65 \$1.00

Power Transformer 60 mil 240 volt 36
volt Centre tap 6.3 winding \$5.

Mics Dynamic 10k \$3.50

Valve Sockets: 7 or 9 pin 10 cents Octal
10 cents

6.3 winding \$5 small power transformer
240v. 220v and 22v windings \$3.

Pilot Lights: 24 volt screw-in, 10 for
\$1.50

Ferrite Rods 6 inch 50. 9 x 1/2 75 cents.

Pots: 10K ganged log 50 cents. 1 Meg
ganged log \$1.25; 1/2 Meg ganged log
\$1.25; 2 Meg ganged log \$1.25;

2 Meg double pole switch \$1.50.

Sharp TV Flyback Transformers 8 FT 604
\$7.00

Miniature Speaker Transformers, drive
and output \$1.00 pair.

Heat Sinks 4x2 1 1/4 \$1.50

Speaker Transformers 7000 to 15 ohm
\$1.75

Slide Pots 250 K 4 for \$1.

SPEAKERS SPEAKERS SPEAKERS

6 1/2 inch Dual Cone 4 ohm
4 x 2 8 ohm
Special 12 inch dual cone MSP TACX 8 ohm
8 TACX 8 ohm
6 x 9 inch 8 or 15 ohm
5 x 7 inch 8 or 15 ohm
6 1/2 inch 8 or 15 ohm
8 x 4 8 or 15 ohm
6 x 4 8 or 15 ohm
5 x 4 15 ohm
4 inch 8 ohm
5 inch Tweeters 8 ohm

\$5.00 6 inch Dual Cone Tweeters
\$1.50 5 inch Magnavox Dual Cone 8 inch 27 ohm
\$8.00 Magnavox midrange 5 inch dual cone
\$8.00 MSP 6 x 7 inch 3 1/2 ohm
\$6.00 Magnavox 5 inch 15 ohm
\$5.00 MSP 2 1/2 inch 8 ohm
\$4.50 Magnavox 6 inch 4 ohm 8 Watt
\$4.50 Magnavox 5 inch 15 ohm
\$3.50 Philips Gramophone Motor & Pickup 6 volt
\$2.50 Magnavox 6 inch 3 1/2 ohm
\$2.75 Magnavox 6 x 3 8 ohm
\$3.50 Magnavox 4 ohm 5 x 3

\$6.00 MSP 4 x 2 5 ohm
\$6.00 MSP 6 x 4 47 ohm
\$8.00 ROLA 6 x 7 47 ohm
\$4.00 ROLA 6 x 9 47 ohm
\$4.00 Magnavox 5 inch 8 ohm
\$5.00 Magnavox 6 x 9 inch 3 1/2 ohm
\$4.00 Magnavox 5 inch mid range 8 ohm
\$5.00 Magnavox 10 inch dual cone 15 ohm
\$3.50 MSP 4 or 5 inch 3 1/2 ohm
\$2.00 2 1/2 inch 33 ohm
\$2.50 5 x 4 35 ohm
\$2.50 6 x 4 8 or 15 ohm

\$2.50
\$3.50
\$6.00
\$6.00
\$4.00
\$4.00
\$5.00
\$6.00
\$10.00
\$3.50
\$2.00
\$3.50
\$2.50

on my equipment by reducing the highs and boosting the bass a little!

Reiner pushes the first movement along a little faster than is usual, though this might logically be argued to be in keeping with the dramatic statement of the first bars. However, in the quieter parts he shows no reluctance to remove the pressure. All through the symphony the Chicago, which Reiner did so much to improve during his fairly long stay with them, play very well indeed. However, despite the skill of its remastering it sounds a trifle thin compared with more recent recordings.

Reiner's insistence on clarity does away with the lumpiness of some of Brahms' scoring under the batons of other — and more recent — conductors. He establishes quite a different mood in his tender treatment of the following Andante but he takes the third movement much more like the previous one than the scherzo Brahms intended. It is smoother and without the rumbustiousness of Brahms' other scherzos.

Here I must mention the solo horn's lovely contribution, though all the first desk men are fine. He produces that remote, almost mysterious tone which I, having had my musical education in England, admire so much.

The finale is entirely satisfactory and, importantly, this new series of reissues, more of which I will review later, are put out at a budget price. Don't expect too much lusciousness or bloom, despite the skill of the remastering. Still, it serves very well indeed to remind one what a fine conductor Reiner was — and how quickly he seems to have been forgotten.

☆ ☆ ☆

RESPIGHI — The Pines of Rome. The Fountains of Rome. Minneapolis Symphony Orchestra conducted by Antal Dorati. Philips Stereo (Universo Series) 6582 015.

"The Fountains of Rome" has had a good innings since it was composed in 1817. If you're a regular concert-goer you'll be bound to hear it somewhere or other at least once a year.

The number of recordings sold by various companies must now run into pop figures. It was a favorite showpiece with the various overseas conductors who visited here to conduct the newly formed ABC Symphony Orchestra during the early 1930s. Indeed, back in those days, many of the audiences thought it daringly modern, and at least one old Sydney critic wrote of it as merely cacophonous and had one of his sons state in print that "I have nothing but contempt for the music of Bartok."

Those were the days!

The sleeve notes on this issue contain some interesting facts about the composer. He wrote 10 operas — all forgotten and most of them never

receiving more than one or two performances in his native Italy. He studied in Russia with Rimsky-Korsakov — hence his brilliant scoring — and with Max Bruch in Berlin, yet his orchestrations of these two suites are more Straussian in style than either of the two first-named masters. And he was a violinist in a string quartet which toured America where some of his operas had a stillborn performance!

In the "Pines of Rome" he was the first composer to introduce a recording of a nightingale's song into the orchestra — a 78, of course, inaudible unless grossly amplified. In the same work he introduced into the same orchestra four buccine — ancient Roman curly trumpets that I have only ever seen in giant Hollywood historical films.

His scoring of the "Fountains" is more modest — a more or less conventional symphony orchestra.

The continuing popularity of these two suites is easily explained — they are easy to listen to, melodious, and graceful when played by most good orchestras and conductors. Above all both suites are picturesque in what has been called a picture postcard sense.

The first delicate movement is followed dramatically by the superb gushing of the "Triton Fountain at Noon", a real waterfall in music. By the way when I saw the Triton fountain there was only an unimpressive squirt coming out of it. Dorati seems to me to hurry this movement unnecessarily though I still listen to most of it with a good deal of enjoyment. And in the last item, "The Medici Fountain at Sunset", the luscious melody is decorated with birdsongs, bells and other crepuscular sounds.

Though it is a frankly romantic work, Dorati takes it all classically, carefully avoiding any Italianate extravagances. And the sound is really fine.

In "The Pines" I like best his two least exuberant middle movements. The first movement — the "Borghese Garden" — pays strong allegiance to very early Stravinsky. "The Apian Way" sequence is marked by the steady distance-consuming marching step of the ancient Roman legions with a triumphal return to Rome to finish. With modern recording techniques the nightingale's song in the pines is now easily audible.

Both suites seem to have outlived many other popular pieces of the period. To mention only two:

Dohnanyi's "Variations on a Nursery Tune" and Falla's "Nights in the Gardens of Spain".

This issue is worthy of continuing Respighi's popularity in this field, though in my opinion other works of his such as "The Birds" and his arrangement of Rossini tunes in the ballet "Boutique Fantasque" deserve equal popularity.

☆ ☆ ☆

BACH J. S. — Six Partitas for Cembalo played by Stanislav Heller. Christophorus-Verlag Stereo BWV825-830. (Two discs.)

Last month I reviewed a disc with a label new to me — SFP. This month I have received another new label — Christophorus-Verlag from Germany. SFP is, by the way, French. The new issue offers "Six Partitas for Cembalo" by J. S. Bach. But before I go on I had perhaps better explain that the word cembalo can be used to describe very different instruments. In Hungary it is used as the name for a stringed instrument, rather like a big zither but with a heavier tone and struck by hand-held, felt-covered hammers. This is best known in Australia for its use in the Hary Janos Suite of Kodaly.

During the 18th century the word was frequently used in Europe to indicate a figured bass. In Italy it is a dulcimer and, in a slightly different form, cembalum, it is a jews' harp, that twanging device held between the teeth and which is neither a harp nor, so far as I can discover, Jewish. In this Christophorus issue it simply means harpsichord.

The six partitas here are recorded very clearly on a more than usually full-toned instrument. Stanislav Heller's Bach is very stylish without being mannered.

There is, alas, no space here to review all six separately but I can assure you that all are excellently played, expressive and technically immaculate. Changes of registration are used with discretion and unflinching good taste. In order to display their variety they are not recorded in numerical order, and unless you are a German scholar, you will find no information in the sleeve notes, which are in that language without an English translation. The two discs make a very high class production which can hold its own with any other of these six partitas.


GETTING INTO
MICROPROCESSORS



GETTING INTO MICROPROCESSORS

This book will help you find out what the revolution is all about . . .

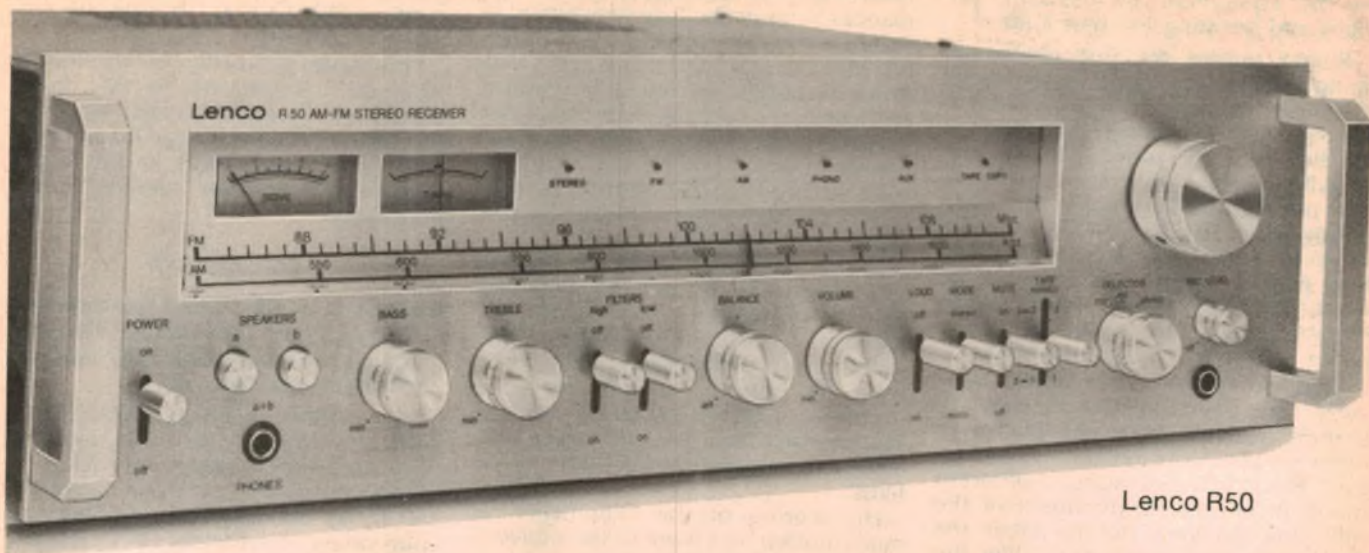Available from newsagents, electronic suppliers and also "Electronics Australia", 57 Regent St. Sydney. PRICE \$4.50 OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield 2014. PRICE \$5.10.



Lenco R50

Rely on Lenco, if you can't be at the concert hall.

Swiss engineered to reproduce the music the way you want to hear it. The way it was played. Lenco. Precision equipment for the discerning enthusiast. And the next best thing to being where the music was.

The Lenco R50

One of an excellent range of amplifiers, tuners and receivers ... including the T30 AM/FM stereo tuner, the A50 stereo amplifier and the R25 receiver. The Lenco R50 is designed and engineered to provide AM/FM reception and beautiful quality stereo amplification in **one** unit.
Power: 40w x 40w RMS at 8 ohm.
Frequency: 10-40,000 Hz.
FM sensitivity: 1.8 mV.
Stereo separation: 40 dB.
Weight: 13 Kg.
Size: 490 x 132 x 320 mm.



Lenco C2003

The Lenco C2003

A cassette deck to satisfy even a music pro. Swiss engineered 3 head 2 capstan direct drive. Modern design and a host of advanced technical features to make a concert hall of your HiFi room.



Lenco L-833DD

The Lenco L-833DD

The first direct-drive turntable with contactless high-frequency auto-stop. A top ranking, HiFi turntable. Gimbal-suspended tone-arm with excellent geometry. High-frequency electronic auto-stop switches off the turntable and lifts tone-arm. Simply superb. The L-830 has all the same excellent features except the high-frequency auto-stop.

Distributed by

PHOTIMPOR

MELBOURNE ADELAIDE BRISBANE PERTH SYDNEY

For descriptive literature, send a 30c stamp to **Qualitron Industries Division** of Photimport (Australia) Pty. Ltd.
 Head Office: 69 Nicholson Street, East Brunswick, Victoria, 3057, Australia. Phone: 380 6922

PA37L



Lighter Side

Reviews of other recordings

Devotional Records

JESUS OF NAZARETH. Original soundtrack, composed and conducted by Maurice Jarre. The National Philharmonic Orchestra. Stereo, Astor SPLP-1498.

I was in two minds whether this album should be included in the devotional section but I guess that, if it is sought out, it will be mainly by people who will come to associate it with the film. At the time of writing, I can judge the content of the film only by the title, the jacket notes which speak of the dedication of those who produced it, and the track titles which suggest a traditional portrayal of the life of Christ:

Jesus Of Nazareth — Annunciation — Three Kings — Baptism — Jairus' Daughter — Jerusalem — Salome — The Beatitudes — Miracle Of The Fish — Crucifixion — Resurrection.

The music itself is traditional orchestral sound — restrained, melodic, thematic and obviously related to the visual, with the "Salome" theme being unmistakable. On side two the "Beatitudes" are recited with considerable feeling against an orchestral background by Robert Powell, who plays the part of Jesus. It confirms the nature of the album and, for many, will be the most played track.

The quality and surface of the recording are well up to standard and, if you get to see the film, and like the portrayal, this soundtrack recording should help you to retain the image. (W.N.W.)

☆ ☆ ☆

JOY IN THE MORNING. Ernie Rettino & Debby Kerner. Stereo, Maranatha HS777/19. (From S. John Bacon Pty Ltd, 12-13 Windsor Av, Mt Waverley, Vic 3149.)

"Joy in the Morning" is the title of this album and it is the conviction that these two young people are trying to convey in their songs: All Day Song — Mary Magdalene — In The Morning — The Wa Wa Song — Song of Solomon — Seek And Ye Shall Find Him — Motherless Child — He's Got The Whole World In His Hands — I Finally Appreciate — Shine On.

Most of the songs are their own compositions, ranging in style from a well

performed soft rock sound to the quiet and intimate, but appealing predominantly to the teen/twenties group.

Singing, for the most part, in close harmony, diction is average — not clear enough to follow every word but sufficient to convey the main message of the lyrics and the sincerity of the performance as a whole.

Recording quality and the pressing itself are well up to standard. (W.N.W.)

☆ ☆ ☆

SOMETIMES ALLELUIA. The Sonlight Orchestra. Stereo, Myrrh MSA-6560. (From Sacred Productions Aust, 181 Clarence St, Sydney and other capitals.)

Conventionally, those "Jesus Songs", as the jacket notes describe them, the work of contemporary Gospel composers, are belted out by rock singers and rock groups, presumably to the delight of the "now" generation.

On this album, 10 such numbers are presented in purely orchestral form, with the lyrics printed on the sleeve to

remind you what they're all about: I Can't Wait — Prince Song — You Got The Power — Sometimes Alleluia — Searchlight — I Am Your Servant — Say "I Do" — For Those Tears I Died — Clean Before My Lord — It Took A Carpenter.

While guitars are prominent enough to remind the listener of the derivation of the music, the arrangements and orchestration plus ye olde world cover design are obviously intended to convey the thought that modern Gospel can parade quite successfully in period costume. It's a novel idea and one that may interest Gospel groups who may want to develop a compromise format.

But let me sound a note of warning to hifi fans. Maybe it's the acoustics, or the recording equipment and/or the number of amplified instruments but the Sonlight Orchestra has a very "middly" sound here, that is evident from the very first groove. Fortunately, the sound is otherwise clean, as is the surface of the pressing, but it lacks boomp and it lacks sparkle. A pity. (W.N.W.)

Instrumental, Vocal and Humour

LAWRENCE WELK. Interfusion L252281. Festival release.

If TV themes are your bag, played by a big and competent orchestra, then this is the record for you, with twelve title tracks from American shows: Nadia's Theme from 'The Young And The Restless' — Baretta's Theme — Paloma Blanca — Feelings — Theme from 'Swat' — Champagne Time — 'Johnny' Theme — Star Trek — Love Will Keep Us Together — The Hustle — Making Our Dreams Come True — Happy Days.

The quality and big band sound are excellent, far better than the usual run of sound track records. (N.J.M.)

☆ ☆ ☆

FORTYMANIA. M7 Stereo MLR-190.

If the music of the forties is your bag, this disc would be a good way to grab a sample of both big band and vocal sound from that decade. Recorded in England at the Pye studios, it

features such English artists as: Dennis Lotis — Rosemary Squires — The Polka Dots — Joan Baxter — The Mike Sammes Singers — The Al Saxon Big Band and the Richomd String Orchestra.

The 40 titles would take a page of their own, so a sample: In The Mood — Sentimental Journey — 12th Street Rag — Lazy River — Blue Moon — April Showers — Baby It's Cold Outside — Don't Get Around Much Any More.

The quality is excellent and the sleeve notes give a rundown on the artists who made each hit their own. Some of the arrangements lack a little of the sparkle of the original but this would be a small price to pay. (N.J.M.)

☆ ☆ ☆

JONAH JONES, GLEN GRAY QUARTET and the Cas Loma Orchestra. Capital Encore VMP 1008. EMI Release.

If like me you're old enough to remember the big bands of yesteryear you will really dig the musical offerings on this record. Trumpeter Jonah Jones puts everything into 12 tracks of

SPECIAL PURCHASE

NEW STANDARD PM-403 W-24 WATT STEREO AMPLIFIER AT LESS THAN TRADE PRICE

MANUFACTURED BY STANDARD RADIO CORPORATION — A MAJOR JAPANESE ELECTRONIC MANUFACTURER.



\$59.00 plus post & packing

NSW \$3.50
VIC., QLD, SA \$5.00
WA, TAS. \$6.50 (Reg. post \$2.00 extra)

SPECIFICATIONS:

Continuous power 12 watts R.M.S. per channel at 8ohms. (24 watts) at 1KHz
Harmonic distortion at 1KHz 0.5% to 10 watts
Power bandwidth 20-20,000Hz at 8ohms
Frequency response 15-40,000Hz
Signal to noise ratio Aux. 70db Mag. 60db.
Bass control ± 10 db at 100Hz Treble control ± 10 db at 10,000Hz
Input sensitivity Mag. 2.5mv, Cer. 150mv. Aux 100mv, Tape 500mv.
● TAPE MONITOR SWITCH ● LOUDNESS CONTROL ● SPEAKER SELECTOR SWITCH
● HEADPHONE JACK ● SEPARATE BASS & TREBLE CONTROLS ● BALANCE CONTROL
Dimensions 13 1/2" by 8" by 4" high SUPPLIED IN WALNUT FINISHED CABINET WITH OPERATION INSTRUCTIONS & SCHEMATIC DIAGRAM

READ REVIEW ON THE STANDARD PM-403W AMPLIFIER IN THIS ISSUE OF E.A.

SPECIAL PACKAGE OFFER

STANDARD PM -403W AMPLIFIER — TWO GOODMAN-FOSTER SPEAKER KITS AND B.S.R. STANDARD CHANGER WITH CERAMIC CARTRIDGE **\$145.00.**

(Cabinets for speakers and changer not supplied.) Freight and packing extra per rail or air freight.

NEW B.S.R. & GARRARD RECORD CHANGERS — ROLA & GOODMAN SPEAKERS AT A FRACTION OF LIST PRICE

NEW STANDARD B.S.R. C123 RECORD CHANGERS

\$20.00



Fully automatic turntable plays up to six records automatically and single records automatically or manually as required. 11" turntable. Bias compensation. Cue & pause control. Record speeds 331/3, 45 and 78 rev./min. Finished in black with

silver trim. Player and changer spindles supplied. Fitted with ceramic cartridge. Post & packing extra. NSW \$2.70; Vic., Qld, SA \$3.70; WA \$4.70 (registered post \$2 extra if required).

GARRARD M.82

\$57.00 TRANSCRIPTION CHANGER

Supplied with Goldring Magnetic Cartridge with Diamond Stylus. Post & packing (Reg. post) NSW \$3.60, Vic., SA, Qld \$4.74, Tas \$5.50, WA & NT \$5.80.



GARRARD CC10A RECORD CHANGER \$14.75

Fitted with a Sonatone Garrard Ceramic Cartridge Sapphire Stylus supplied with template and instructions. Post & Packing: NSW \$2.50. Inter. \$3.50.

BASE & PERSPEX COVERS AVAILABLE IN TEAK & WALNUT FINISH

NEW GOODMAN-FOSTER 3-WAY 4 SPEAKER HI-FI SYSTEM

Frequency Range 45 to 22,000 cycles. Power rating 25 watt. Imp-8ohms. Supplied in kit form (less cabinet) each kit comprises two English Goodmans 8" bass units. Foster 5" mid range. Foster 1" dome tweeter crossover components (condensers and inductance) innabond, speaker fabric and plans of cabinet. Cabinet dimensions 23"x13"x10". Post & Packing extra: NSW \$2.70, Vic., SA, Qld \$4.70, WA 5.70. (Registered Post \$2.00 extra if required) cabinets available.

\$39.00 PER KIT

NEW ROLA C12PX 12" HI-FI SPEAKERS

Rola twin cone Hi-Fi speakers. Freq. range 40 to 13,000 cycles power rating 30 watts. Imp-8ohms. Post & Packing: NSW \$2.50. Interstate \$3.50.

\$16.50

A.W.A.-MSP-Foster Hi-Fi 3-way Speaker System

\$29.00 per kit

Frequency Range 40-20,000 cycles. Power rating 20 watts RMS Imp 8ohms. Supplied in kit form (less cabinet). Each kit comprises A.W.A. 8 WAC8. 8" base unit. Foster 5" mid range. Foster 1" dome tweeter. Crossover components innabond speaker fabric and cabinet plans. Post and Packing. NSW \$3.00, Vic., SA, Qld \$4.00, Tas. \$5.00, WA \$6.50.

Cabinet dimensions 23"x13"x10"

PLAYMASTER-MAGNAVOX HI-FI SPEAKER SYSTEMS 3-WAY

3-45-L

AS FEATURED IN ELECTRONICS AUST. APRIL '75
Complete kit of parts for above system including speakers, Magnavox 8-30 Bass Unit, 6J Mid Range Phillips ADO160/T8 Dome Tweeter, crossover components 6" and 3" tubes, speaker silk and innabond (less cabinet). **\$57.00 PER KIT.**

3-41-L

AS FEATURED IN ELECTRONICS AUST. JUNE '76
As above but using the new Magnavox 6-25 Mid Range in place of the 6J with additional crossover components. **\$65.00 PER KIT.**

Freight and packing extra per pass, rail or air freight.

CLASSIC RADIO IS A DISTRIBUTOR FOR FOSTER LOUDSPEAKERS

NEW MAGNAVOX — MV50 — 50 WATT SPEAKER SYSTEMS

As featured in Feb. 1976 Issue of Electronics Today
Complete kit of parts (less cabinet) comprising Magnavox 10-40 10" bass unit. 625 mid range 6" two XJ3 dome tweeters, crossover network, innabond, speaker silk and plans of cabinet.

\$78.00 freight extra
per rail or air freight.
Cabinet available.

PER KIT

CLASSIC RADIO

245 PARRAMATTA RD, HABERFIELD 2045. PHONES 798-7145, 798-6507.

THE LIGHTER SIDE

superlative quality that would put the disc into the "demo" class.

The titles: Baubles Bangles and Beads — Echoes Of Harlem — Two O'Clock Jump — I Can't Get Started — Boy Meets Horn — Hot Lips — After You're Gone — West End Blues — Ciribiribin — Tenderly — Sugar Blues — Apollo Jumps.

One curious thing about this disc is the amount of pre-echo preceding each track. I doubt if the Casa Loma Orchestra has the original performers, as it has been around for a long time. (N.J.M.)

☆ ☆ ☆

CARRIE. Original Motion Picture Sound Track. United Artists L36133. Festival release.

It is still a puzzle to me why the motion picture industry persists in releasing sound track recordings of nearly every film made, particularly in the case of a film like "Carrie" where, judging by the press comments, so much depends on visual effects.

The first side could be best described as fairly typical movie schmaltz with titles like: "I Never Dreamed Someone Like You Could Love Someone Like Me" and "At The Prom" but side two carries more "interesting" titles as: Bucket Of Blood — School In Flames — Mother At The Top Of The Stairs — Collapse Of Carrie's Home.

The basic story line is that of a fairly plain American schoolgirl who tormented by her fellow pupils and a deranged mother, takes her revenge by her exercise of the gift of telekinesis; like Uri Geller only more so, with rather horrifying results! (N.J.M.)

☆ ☆ ☆

SCOTT JOPLIN. Music from the Original Motion Picture Soundtrack. MCA Records, stereo MCA 2098.

Those who enjoyed the music in the film of the life of Scott Joplin now have the opportunity to purchase a good memento. The recording quality is good, particularly so since it is a film sound track. Most of the music arrangements are for piano with orchestral backing.

Some of the Scott Joplin tunes featured are as follows: Maple Leaf Rag — The Entertainer — Solace — Pleasant Moments — Peacherine Rag — Weeping Willow — Wall Street Rag — Heliotrope Bouquet. (L.D.S.)

☆ ☆ ☆

CAL TJADER AT GRACE CATHEDRAL. Fantasy 36198. Festival release.

After reading the promo leaflet with this record, one gets the impression that Cal Tjader has been around in the music scene for some time, working as a percussionist for people like Dave Brubeck and George Shearing. The



CARPENTERS—LIVE AT THE PALLADIUM. CARPENTERS. A & M Records. L 36201. Festival release.

On this record, Richard and Karen present a very smooth and professional show. The first side shows off very well their many and varied talents, while the second side is almost wholly composed of one large medley of their most famous hits.

Apart from the clapping, this next side is very enjoyable. On the technical side, the recording is excellent, except that I found out how much modern vinyl records will flex when I tried to get it off my turntable. It looked like I had the two edges about 150 mm above the platter bar before it freed itself from the spindle. (D.W.E.)

venue for this enjoyable recording session was the Grace Cathedral in San Francisco, about a year ago, the occasion being a charity concert.

Most of the tracks have a strong latin feeling about them and side one is taken with two long tracks; I Showed Them — Bluesology; side two starts with Black Orpheus Medley, followed by an exciting version of the old standard "Body And Soul" and "Theme". The ambience of a live performance is captured nicely but there is the occasional trace of acoustic overload of the system. However, overall, the quality is good. (N.J.M.)

☆ ☆ ☆

REFLECTIONS OF LOVE. Roger Whitaker EMI Records Ltd EMC 3140. Stereo.

The relaxed easy style of Roger Whitaker will be well known to many readers by now, particularly since his memorable love song "The Last Farewell". On this album, the love theme of "The Last Farewell" is continued with this collection of twelve songs, some Roger Whitaker's own compositions.

The track titles are: It's Your Love — Before She Breaks My Heart — Indian Lady — Time — My World — Say My Goodbye's To The Rain — Here We Stand — Summer Days — Pretty Bird Of Love

— All The Way To Richmond — Let Me Be Your Sun — New Love.

My reaction — pleasant, easy-on-the-ear listening. Recording quality is excellent. (G.S.)

☆ ☆ ☆

25 OF THE WORLD'S GREATEST LOVE SONGS. The London Strings. M7, stereo MLR 191.

Lush strings lull your spirits and create the atmosphere for romance. If that is your wish then this fine album will fit the bill. The arrangements are pleasant without being too saccharine and the recording quality is good.

Some of the 25 tunes featured are as follows: Where Do I Begin — Love Me Tender — Strangers In The Night — A Lover's Interlude — Speak Softly Love — Yesterday. (L.D.S.)

☆ ☆ ☆

CARA MIA. The Disco Sound of Paul Delicato. M7 stereo MLF 153

If you are a fan of Tom Jones, Engelbert Humperdinck or even Lovelace Watkins, then high voltage vocalist Paul Delicato is certain to have tremendous appeal. His is the sort of record you slap on the turntable to send you ripping through the chores or to get people on their feet and dancing at a party. Like those singers above Paul Delicato has the range and vitality to set up almost any song. And he is backed with some excellent arrangements.

Recording quality is not marvellous but the standard of performance makes up for that. A good buy.

Ten tunes are featured, two in medley form: Cara Mia — It's the Same Old Song — Happy Together — What Becomes Of The Brokenhearted — I Can't Make It All Alone — Lean On Me — I Couldn't Live Without Your Love — Just Enough To Keep Me Hangin' On — Baby Face — You Must Have Been A Beautiful Baby — Spirit Of America. (L.D.S.)

☆ ☆ ☆

SHAMAL. Gong. Virgin Records L 35871. Festival release.

Gong rely heavily on a wide range of instruments to produce an interesting jazz-rock sound which at times can be most impressive.

Particularly ear catching are the vastly contrasting "Cat In Clark's Shoes", which assaults the listener with a host of sounds, and the moody, flute dominated "Mandrake". The remaining tracks are more routine.

In terms of quality the record was quite clean, although a small amount of surface noise could be detected on my copy. (D.W.E.)

☆ ☆ ☆

SIDE SHOW. Barry Biggs. M7 Stereo MLF 168.

Barry Biggs is a Jamaican singer with a voice that almost ranges up to a soprano on twelve pleasant love ballads including: Side Show — You Are My Life — Goodnight My Love — Work All Day

NOW. GREAT FOR THE PRICE OF GOOD.

There are a lot of good loudspeakers around these days. Especially if you're going to pay \$300 or \$500. Some are pretty good. Some are really good.

But good isn't great. Introducing Bolivar Speaker Works. We make two loudspeakers. Both are 3-way bookshelf systems. One is \$468, the other \$358. Both are really efficient. (Twice as efficient as the current leader in that price range.) You won't need a big receiver to get a big sound. The enclosures are the same kind used for expensive loudspeakers, but we finished them in a warm-toned vinyl. No fancy wood veneers. We put the money in the sound. Come listen to Bolivar. Then listen to any other speaker that costs about the same. You'll buy Bolivar.



Bolivar Speaker Works

Your nearest Bolivar dealer? That's easy. Write Bolivar Speaker Works
P.O. Box 6, Brookvale 2100, N.S.W. or phone 939 2922

LIGHTER SIDE

—You'll Never Get To Heaven — Sweetest Little Thing — That Girl I Knew — Your Kiss Is Sweet — The Road Is Rough.

Barry Biggs started off in show-biz as a sound recordist and cameraman with the Jamaican Broadcasting Corporation and has had wide experience in Europe and the USA as well as Great Britain. His high voice may not be to every taste but it is at least a change! (N.J.M.)

☆ ☆ ☆

THE BIG BAD ROCK GUITAR OF GLEN CAMPBELL.

Capitol stereo VMP 1006.

Big bad rock guitar of Glen Campbell? Improbable though it may seem, Glen Campbell does not sing a note on this album. Instead, as suggested by the title, he plays lead guitar in a rock group who play in very much the same style as the Ventures. It makes lively listening, whether you are jiving or just foot-tapping.

There are 12 tracks in all: Walk, Don't Run — Ticket To Ride — Steve's Shuck — Spanish Shades — The Lonely Arranger — The James Bond Theme — It's Not Unusual — King Of The Road — Sassy — Mr Tambourine Man — Spring Mist — Beef Jerky. (L.D.S.)

☆ ☆ ☆

KENNY BALL AND HIS JAZZ MEN.

Saturday at The Mill. Spiral MLF-183 M7 release.

Kenny Ball fans will enjoy this light-hearted romp in the jazz idiom with 11 titles: Saturday Night At The Mill — Sunday — Sweet Painted Lady — Feline Stomp — Them There Eyes — You Can't Get To Heaven By Living Like Hell — Lady Of Spain — I've Got Plenty O'Nuttin — Taint What You Do — Lilli Marlene — Down By The River. Some of the lyrics will cause a raised eyebrow or two.

The band: Kenny Ball, trumpet, flugel horn, vocals; Andy Cooper, clarinet saxophone, vocals; Ted Baldwin, banjo, guitar, vocals; Vic Pitt, bass, bass guitar; John Parker, piano; Ron Bowden, drums. Quality, excellent. (N.J.M.)

☆ ☆ ☆

ROCK AND RHYTHM.

Raymond Lefevre and his Orchestra. Barclay L-36217 Festival release.

Raymond Lefevre is one of that international breed of band leaders that produces a bright sound rendition of all the recent hits, the sound that some people call 'wallpaper' music. Perhaps the description is a little unkind because, as a background to social pleasantries, these discs can't be beaten. The quality is excellent.

The titles: Fly Robin Fly — Yesterday — A Whiter Shade Of Pale — S.O.S. — Oh Happy Day — Mississippi — Raindrops Keep Falling On My Head — The Hustle — Soul Coaxing — Charly Brown — El Condo Pasa — Save Your Kisses For Me — Bridge Over Troubled Water — Africa. (N.J.M.)

☆ ☆ ☆


WES MONTGOMERY, MOVIN'.

Milestone L-45735-6 Festival release.

This two record album of the late, great Wes Montgomery would be required listening for anyone with a liking for jazz guitar at its best. It was originally recorded in two sessions in 1960 and 1962 and remastered in 1977 with extensive sleeve notes and a full rundown on the backing personnel.

There is a total of 13 tracks, with: MOVIN' Along — I Don't Stand A Ghost Of A Chance With You — Tune-Up — Body and Soul — So Do It — Says You — Sandu — Full House — I've Grown Accustomed To Her Face — Blue'n'Boogie — Cariba — Come Rain Or Come Shine — S.O.S. The quality overall is very good; an album to be enjoyed. (N.J.M.)

PRODUCT OF THE MONTH

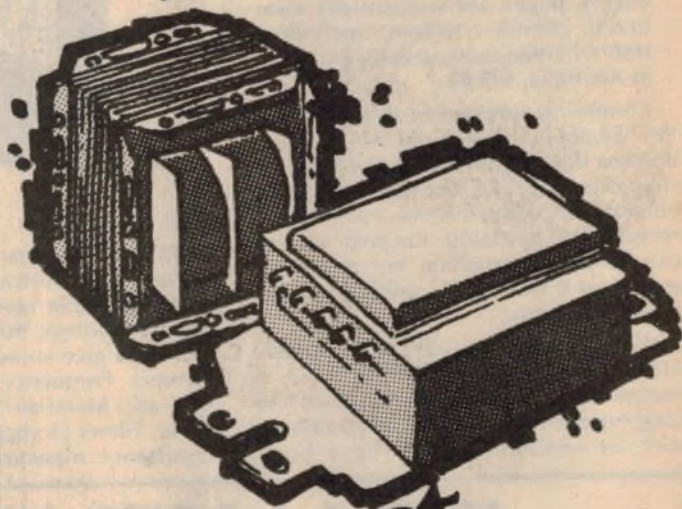

low cost
transformers
• easy to install
• low profile

Distributors of Electronic Components to Industry



ELECTRONIC
ENTHUSIASTS
EMPORIUM

SHOPS 2 & 3 POST OFFICE ARCADE • JOYCE STREET
PENDLE HILL • NSW 2145 • TELEPHONE 636 6222



Books & Literature

Reference tome

REFERENCE DATA FOR RADIO ENGINEERS. Sixth Edition, first printing, 1965. Published by ITT and Howard W. Sams & Co Inc. Hard covers, pages not sequentially numbered, 240mm x 160mm, freely illustrated by diagrams, graphs, etc. Price in Australia, \$40.05.

Commonly referred to in the USA as the "Engineer's Bible", this ITT publication has been around since 1943 and has sold something like 450,000 copies of the editions preceding this one. Now further revised and up-dated, the sixth edition can hardly be anything but a notable work and a worthwhile addition to any reference library.

With the pages in each chapter separately numbered, it would take a mathematical exercise to nominate the total number but they are all crammed with information and add up a book



about 6cm thick.

With 48 chapters in all, plus a huge 46-page index, it would take more space than is available here merely to list the chapter headings; but the following summary may give some idea of the scope covered: Frequency data; Units, constant, etc; Materials; Components; Networks; Filters (4 chapters); Attenuators; Impedance measurements; Magnetic

reactors, amplifiers, filters; Electron tubes & circuits; Semiconductors & circuits; Optoelectronics; Modulation; Propagation, waveguides, transmission lines, antennas; Noise & interference; Broadcasting, etc; Radar; Space; Optical communications; Nuclear physics; Quantum electronics; Computers; Information theory; Statistics; Reliability; Fourier; Maxwell; Equations & Tables.

In describing the contents, it is perhaps appropriate to emphasise the words in the title "Reference Data". There is a fair amount of descriptive text in the book but is there mainly to provide continuity for the actual reference data—tables, graphs, circuits and so on: all the data which busy engineers and undergraduates may need to refer to in a hurry, without having to search through half the books in the library. And, as will be apparent from the listing earlier, the range of subjects is very wide.

So there it is: a book compiled primarily for engineers; a book to refer to rather than to read; packed with an enormous range of data.

Our review copy from Prentice-Hall of Australia Pty Ltd, P.O. Box 151 Brookvale, NSW, 2100. (W.N.W.)

Programming micros

MICROPROCESSOR - MICROPROGRAMMING HANDBOOK, first edition (second printing), by Brice Ward. Published by TAB Books, USA, 1976. Soft Covers, 130 x 210 mm, 293pp, many diagrams and tables. Recommended retail price \$9.75.

This book would be an invaluable aid to those with a grounding in electronics who wish to learn about the new and expanding field of microprocessors and their programming. The introductory chapters give the reader a good grounding in microprocessor fundamentals. The text progresses from background information to a discussion of basic computer and microprocessor structure, architecture and systems.

The first four chapters are concerned with this basic material, while the next four chapters are concerned with actual systems. In order, the actual systems covered are the MCS-4, the MCS-40 (4004 and 4040), and the MCS-80 (8080), all from the Intel Corporation, and the MC6800, from Motorola Semiconductor Products.

The remaining four chapters are concerned with the various types of memory systems in common use, and with microprogramming. This latter subject accounts for most of the last main section of the book. Sample programs are given in both machine and assembly languages.

The back of the book contains a list of common computer terminology abbreviations and a glossary, as well as a list of microprocessor manufacturers and a comparison of their products, and a list of the MCS-80 support family.

KED-1 LASER KIT

available from

LASER ELECTRONICS PTY. LTD.

Although we design and manufacture over 60 Lasers and Laser Systems, and have done for over 10 years, we could be accused of not catering for the needs of those who wish to "Do-it-Yourself".

The KED-1 kit is the third Laser construction project we have been responsible for in conjunction with Electronics Australia in eight years.

This time we got portable with a 12V D.C. Laser.

Cost including Mailing— **\$180.00** plus \$18 Sales Tax (if applicable)

Complete Kits of Parts including the Laser Tube and Instruction Manual available from

LASER ELECTRONICS PTY. LTD.

P.O. BOX 359, SOUTHPORT, QLD., 4215

PHONE: (075) 32-1699. TELEX: 41225

W.A. AGENT — TISCO 74 PTY. LTD.

SUBIACO, PERTH. PHONE: 381-6000

In conclusion, while it must be said that the book is somewhat biased towards the earlier microprocessors, this should not detract from its value to the student. The opening chapters contain much valuable information which is applicable to any microprocessor system, while most of the principles covered in the remainder of the book are also applicable to any microprocessor.

Review copies came from the Technical Book and Magazine Company Pty Ltd, 289-299 Swanston Street, Melbourne Vic. 3000, and also from Dick Smith Electronics Pty Ltd, PO Box 747 Crows Nest, NSW 2065. (D.W.E.)

Tape recorders

NEWNES TAPE RECORDER SERVICING MANUAL, Second Edition, Volume 1. Edited by John Gardner, MAES, MBKS, Ass. ISTC. Published by Newnes-Butterworths, London. Hard covers, 207 pages, 245mm x 185mm, freely illustrated by drawings and photographs. Price in Australia \$17.50.

Whatever value this book may have in Britain, I cannot imagine it appealing to too many people in Australia, apart from those who are really involved in—and dedicated to—the repair of all and sundry tape players.

This volume number 1 is devoted to domestic tape equipment, mainly open-reelers and mono cassette machines, of brands far more common in Britain than in Australia, and released during the years 1968-1970. The brands include: Abba, Beocord, Elizabethan, Ferguson, Fidelity, Grundig, ITT, Kenwood, Marconiphone, Philips, Sanyo, Sony, Tandberg and Uher.

A few of the machines represented might still be giving good service in Australia but many others would either be little known or getting to long in the tooth to warrant extensive service.

But, if you are involved in this field and need all the information you can get, you'll find reproduced in this book as much circuitry and mechanical data as the author could reasonably extract from the manufacturers' service sheets. We understand that Volume 2, which we did not see, covers models released during the years 1971-4. Our review copy came from Butterworths, 586 Pacific Highway, Chatswood, NSW, 2067. (W.N.W.)

a basic library for electronics enthusiasts

FUNDAMENTALS OF SOLID STATE

\$3.00 + 60c P&P

DIGITAL ELECTRONICS

\$3.00 + 60c P&P

BASIC ELECTRONICS

\$3.00 + 60c P&P

Electronics Australia,

Box 163, Beaconsfield, NSW 2014.

BOOKS

NEW — NEW — NEW

Latest editions of some of the most popular books on the subject:

R.S.G.B. Handbook (New edition) Volume 1	\$21.10
R.S.G.B. Handbook (New edition) Volume 2	\$18.40
A.R.R.L. Ham Operating Guide	\$7.20
A.R.R.L. Electronics Data Book	\$7.20
Reference Data for Radio Engineers (New edition) I.T.T.	\$37.50
Radio Handbook (William I. Orr) 20th Edition	\$24.40
World Radio TV Handbook 1977	\$11.95
Weather Satellite Handbook (Dr R. E. Taggart)	\$4.95
How To Build Proximity Detectors and Metal Locators (John Potter Shields)	\$6.35
Building and Installing Electronic Intrusion Alarms (John E. Cunningham)	\$6.35
Australian Electrical Wiring Theory and Practice (Pethebridge & Williams)	\$11.10
Australian Radio Amateur Callbook 1977	\$2.85

New Books:

Advanced Applications for Pocket Calculators (Jack Gilbert)	\$8.50
Master Handbook of Digital Logic Applications (William L. Hunter)	\$10.95
111 Digital and Linear IC Projects (Don Tuite)	\$8.50
"Miniwatt" Technical Data — Valves, Picture Tubes, Semi-conductor Devices (7th Edition)	\$7.50
Unique IC OP-AMP Applications (Walter C. Jung)	\$7.00
IC OP-AMP Cookbook (Walter C. Jung)	\$17.80
TTL Cookbook (Lancaster)	\$12.25
TV Typewriter Cookbook (Lancaster)	\$14.20
RTL Cookbook (Lancaster)	\$6.60
CMOS Cookbook (Lancaster) 1st Edition, 1977	\$13.50
Active Filter Cookbook (Lancaster)	\$19.00
IC Timer Cookbook (Jung)	\$13.50
Transistor Specifications Manual, 8th Edition	\$9.50
Transistor Substitution Handbook, New Edition	\$6.75
International Transistor Selector (T.D. Towers)	\$6.95
Master Tube Substitution Handbook (Tab Books)	\$7.00
Modern Crystal Sets — Fully Illustrated Step by Step (R. H. Warring) See and Make Series	\$4.95
Electronic Organs (Norman H. Crowhurst) Volume 3	\$9.35
1977 Australian Radio Amateur Callbook (ARRL)	\$2.85
Solid State Design for the Radio Amateur (ARRL)	\$14.20
Australian Electrical Wiring Theory and Practice (Pethebridge & Williams)	\$11.10

CB Radio Books:

CBer's How-To Book (Leo G. Sands)	\$6.95
Citizen's Band Radio (Allan Lytel) Revised 2nd Ed.	\$6.95
Easi-Guide to CB Radio for Truckers (Forest H. Belt)	\$4.95
Pictorial Guide to CB Radio Installation & Repair (Forest Belt)	\$8.50
CB Radio Operating Procedures (D. Hicks)	\$5.50
CB Radio Servicing Guide (Leo G. Sands)	\$7.00
How To Protect Your CB Rig (F. Mims)	\$5.05
Easi-Guide to Citizen's Band Radio (Forest H. Belt)	\$4.95
CB Radio Construction Projects (Len Buckwalter)	\$5.60
Citizen's Band Radio Handbook (David E. Hicks)	\$8.50
Questions & Answers About CB Operations (Leo G. Sands)	\$5.30
CB Radio Operator's Guide (2nd Edition) (Robert M. Brown & Paul L. Dorweiler)	\$8.50
From CB to Ham Beginner (J. S. Stanley)	\$6.95
CBer's Handbook of Simple Hobby Projects — 114 Tested Performance Improvers (Robert M. Brown)	\$5.50
Practical CB Radio Troubleshooting and Repair (David F. Norman)	\$8.50
The Big Dummies Guide to CB Radio	\$2.95
The Best Book on CB — Includes all 40 Channels & 1977 Regulations (Evan Herbert)	\$6.25
CB Bible — The Complete Guide to Citizen's Band 2-way Radio	\$6.95
The Wonderful Wacky World of CB Radio	\$5.95
The "Official" CB Slangue Language Dictionary (Lanie Dills)	\$2.95
How To Select and Install CB Antennas (Staff of CB Test Labs)	\$6.95
The Truth about CB Antennas (William I. Orr)	\$9.40

MICROCOMPUTERS/MICROPROCESSORS

Books:	
Programming Microprocessors (M. W. McMurrin)	\$9.75
Microprocessors: Technology, Architecture and Applications (Daniel R. McGlynn)	\$18.80
Microprocessors (Electronics Book Series)	\$17.65
Microcomputers/Microprocessing Hardware Software & Application (Hilburn & Julich)	\$29.50
Minicomputer Systems Organization and Programming (PDP 11) (Eckhouse)	\$25.80

Prices Subject to Alteration

For Mail Orders please add: 80c Local \$1.50 Interstate

McGILL'S AUTHORISED NEWSAGENCY PTY. LTD.

187 Elizabeth Street, Melbourne.

Phone: 60 1475-6-7

Just some of the books from the biggest range of radio and electronics books in Australia.

If the book you require is not listed below, it can be ordered from us.

Minicomputer Systems: Structure, Implementation & Application (C. Weitzman)	\$29.55
Microcomputer Primer (Waite & Pardee)	\$10.75
Minicomputers for Engineers and Scientists (G. Korn)	\$33.15
SC/MP Microprocessor Applications Handbook (National)	\$7.20
How to Buy and Use Minicomputers and Microcomputers (W. Barden, Jr.)	\$13.50
Microprocessing/Microprogramming Handbook (B. Ward)	\$9.75
101 Basic Computer Games (D. Ahl)	\$10.60

American Radio Relay League Publications:

Hints and Kinks for the Radio Amateur	\$4.25
The Radio Amateur's VHF Manual	\$7.20
A.R.R.L. Antenna Handbook	\$8.00
Understanding Amateur Radio	\$7.20
The Radio Amateur's Licence Manual	\$2.55
How To Become a Radio Amateur	\$2.55
A Course in Radio Fundamentals	\$5.60
Special Communications Techniques for the Radio Amateur	\$5.60
FM & Repeater for the Radio Amateur	\$7.20
Single Sideband for the Radio Amateur	\$7.20
Ham Radio Operating Guide	\$7.20
Electronics Data Book	\$7.20

Howard W. Sams Publications:

Understanding IC Operational Amplifiers (Melen & Garland)	\$5.60
Know Your Oscilloscope (P. Smith)	\$7.00
TV Servicing Guide — Arranged by Trouble Symptoms (Leslie D. Deane & Calvin C. Young, Jr.)	\$6.50
Electric Guitar Amplifier Handbook (Jack Darr)	\$10.20
Transistor Fundamentals — A Programmed Learning Course Volume 1 — Basic Semiconductor & Circuit Principles (Robert J. Brite)	\$7.15
Transistor Fundamentals — A Programmed Learning Course Volume 2 — Basic Transistor Circuits (Charles A. Pike)	\$7.15
Transistor Fundamentals — A Programmed Learning Course Volume 3 — Electronic Equipment Circuits (Martin Gersten)	\$7.15
Transistor Fundamentals — A Programmed Learning Course Volume 4 — Digital & Special Circuits (Louis Schweitzer & Reginald H. Peniston)	\$7.15

RCA Publications:

Electro-Optics Handbook	\$8.30
Linear Integrated Circuits	\$3.75
Understanding CMOS	\$2.85
Solid State Servicing — Hi-Fi, Tape, Records, AM/FM Mono, Stereo, TV B&W Colour	\$6.60
Designer's Handbook — Solid State Power Circuits	\$11.25
RC 30 — Receiving Tube Manual	\$4.50
SC 16 — Solid State Devices Manual (New Edition of RCA Transistor Manual)	\$7.50
RCA Power Devices (RCA Solid State)	\$7.95
RCA Integrated Circuits (RCA Solid State)	\$7.95

Other Titles:

Sound System Engineering (Don & Carolyn Davis)	\$26.95
Servicing with the Oscilloscope — 2nd Edition (Gordon J. King)	\$11.20
Slow Scan Television Handbook (Miller & Taggart)	\$7.90
Amateur Radio Techniques — 5th Edition (Pat Hawker) (R.S.G.B. Publication)	\$10.15
73 Dipole and Long-Wire Antennas (Edward M. Noll)	\$7.15
73 Vertical, Beam and Triangle Antennas (Noll)	\$7.15
Basic Television — Principles & Servicing — 4th Edition (Bernard Grob)	\$14.60
New Edition — Soft Cover	\$15.00
Basic Electronics — 4th Edition (Bernard Grob) New Edition	\$15.00
PAL Colour Television for Servicemen (W.C. Cook)	\$15.00
Pin-Point TV Troubles in 10 Minutes — Check Charts — New TV Trouble Shooting Techniques	\$8.50
Pin-Point Transistor Troubles in 12 Minutes — Check Charts — New Transistor Trouble-Shooting Techniques	\$8.50
Pickups and Loudspeakers — How To Choose and Use (John Earl)	\$8.25
Manual of Sound Recording — 2nd Edition (John Aldred)	\$10.25
Electronic Calculators (H. Edward Roberts)	\$7.60
Getting the Most out of Your Electronic Calculator (William L. Hunter)	\$6.95
99 Ways to Know and Use Your Electronic Calculator (Sams Publication)	\$7.15


Direct Disposals

EST. 31 yrs.

Phone 52 4833
 SEND 50c FOR 20 PAGE CATALOGUE
 MAIL ORDERS TO P O BOX 165 VALLEY BRIS O

14 Duncan Street, The Valley
 36 Helen Street, The Valley
 Parcel Post Rates
 Articles to 1 lb 60c anywhere in Australia
 Articles over 1 lb to max 44lb
 Old Basic \$1 05 plus 05c every 2 lb or part of N.S.W. & ACT
 Basic \$1 75 plus 25c every 2 lb or part of Vic. S.A. W.A. N.T. & Tas.
 Basic \$1 80 plus 45c every 2 lb or part of.

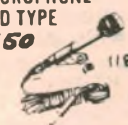UNI DIRECTIONAL DYNAMIC MICROPHONE CARDIOID TYPE
\$17.50



Features dual impedance — 600 ohm and 50K ohm netted ball head, on/off switch, stand holder, 20ft cable. Extremely wide range frequency response. This microphone has the unique facility of shutting out unwanted noise originating from the opposite direction of the microphone due to its uni-directional polar pick-up pattern. Exceptional value!

Fantastic Purchase! CONDENSER MICROPHONES




\$29.50

One of the finest made. Used by the B.B.C. in their outside broadcast. Our huge direct import just arrived makes this price possible. Freq. response 30—16,000 HZ; impedance 600 ohms; output level — 68 DB at 1,000 HZ; Polar pattern uni-directional (cardioid). Max sound level 125 DB. 20ft of shielded cable and on-off switch. Complete with battery. Us \$45.



46 RANGE MULTIMETER
\$32.95

50,000 ohms per volt to 1000 volts AC & DC in 46 ranges. Built in overload protection.



WOODS BLOWERS

Made in England. 240 volts A.C. .3 Amp. 2800 r.p.m. Originally made for computers and of excellent workmanship. Fan has FOURTEEN blades

\$22.50 5 lb.



LIFE MULTITESTER
 EXCLUSIVE IMPORT!
\$9.95

LIFE compact portable meter is ideal for home school or lab. Accuracy combined with wide view color coded scale. Make it ideal for field use. Precision meter movement & complete with test leads & ball. SPECIFICATIONS: AC VOLTS 0-100 0-250 0-500 0-1000 DC VOLTS 0-100 0-500 0-1000 OHMS 0-100 0-500 0-1000



PLANNAIR

6 Blade Fans made in the U.K. with capacitor start. 240 volts A.C. 5" Diameter.

Single units **\$17.95** 4 lb.
 Double units in Bracket **\$35.00** 8 lb.



240V EXTRACTOR FANS \$5.95

12 MONTHS GUARANTEE

Brand new English 240 volt A.C. mains operated fans. Make ideal extractor fans for kitchens, caravans and other domestic and light industrial purposes. Continuously rated, smooth, silent-running induction motor, 4 000 r.p.m., balanced 3-bladed, 6 1/2" fan. Size 6 1/2" dia. x 4" deep



AC ADAPTOR



POWER PACK
 (Dispense with costly dry batteries).

For all Recorders, Cassette Players, Radios and Electronic Calculators of low D.C. Voltage. Fitted with selector switch to give 6, 7 1/2 and 9 volts D.C. at 300 Milliamp. Plugs directly into 240 volt A.C. Approved by electrical authorities and guaranteed for 12 months. Complete with co-axial cable and adaptor plug with four different adaptors to suit most models

12 ozs. PRICE **\$10.50**



1/2 HP "DELCO" MOTOR
240V AC \$45

500 to 10,000 RPM Fully ball bearing, controlled by speed control. Gives full control. New in cartons 12lb. Good for 3 months. Special 3" pulley EXTRA \$5.75. Speed control EXTRA \$29.50. These are one of the latest ENGLISH developments in 240V AC motors have tremendous applications in workshops, coil winding machines, pumps, drills, lathes, test machinery etc. 1,000's of other uses. The speed control is the latest electronic type completely enclosed with fine adjustment of RPM. Motor can be supplied with instructions for making your own speed control. \$45 12lb

SPECIAL OFFER


Package Deal. 30 large Computer Boards with a wealth of Transistors, Diodes, Resistors, Heat Sinks etc. \$10.00. Post \$2.50.

DON'T MISS THIS CHANCE




CAR STEREO SPEAKERS
\$7.50 PAIR

Top quality 5" x 5 watt, for rear shelf or door. 12H of lead each. Super special price! 500 to clear.



"FRACMO" MOTOR \$35
 240V AC 1/2hp. 6000 r.p.m. 1.7 amps. fan cooled, cont. duty shaft at each end, 3/8" x 1" Fully ball bearing brush type. Beautifully made in England. Brand new 10lb.




Multi-Speed MAINS MOTOR
240V AC \$4.95

Exceptionally robust, brush-type, series wound motor

Six speeds: 500, 850, 1,100, 8,000, 12,000 and 15,000 r.p.m.



1/2 HP "DELCO" MOTOR
240V AC \$45



BRAND NEW VOLTMETERS & AMPMETERS 12oz.

Beautifully made. Moving coil, extremely accurate. Brand new 1977 models in cartons. Save \$4 each.

0-60 volt D.C. voltmeters in two volt divisions **\$9.50**
 60-0-60 D.C. AMPMETERS IN 2 AMP DIVS WITH INBUILT SHUNT **\$11.50**




FRESNEL LENSES
\$4.50

12 in. sq. x 1 mm. thick. f.l. 13, 1/2 in.

Precision worked in thin optical plastic and providing large area magnification equivalent to expensive glass lenses. Fine optical quality permits use as solar furnace elements, condensers, image magnifiers, light intensifiers, overhead and back projection optics, camera image brighteners (disco scenes). Use our low RPM geared motors to drive these

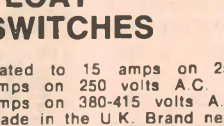Box. Double Fresnel Lenses (condenser) same size as above **\$7.50** 256 1lb.



FLOAT SWITCHES

Rated to 15 amps on 250 volts on 250 volts A.C. 10 amps on 380-415 volts A.C. Made in the U.K. Brand new. Adjustable between 7" to 16"

\$5.95 8 oz.



GEARBOXES — 60 to 1 REDUCTION

Beautifully made in the U.K. and in excellent condition. Size across base — 3 3/4"

\$12.50 2 lb.



BRAND NEW VOLTMETERS & AMPMETERS 12oz.

Beautifully made. Moving coil, extremely accurate. Brand new 1977 models in cartons. Save \$4 each.

0-60 volt D.C. voltmeters in two volt divisions **\$9.50**
 60-0-60 D.C. AMPMETERS IN 2 AMP DIVS WITH INBUILT SHUNT **\$11.50**




brand New 40-Piece TAP & DIE SETS — \$23.50

40 piece stock and dies covering the full range S.A.E. and WHIT. in the one box. TUNGSTEN STEEL 1/8" 1/2". Complete with 7/16" stock, tap wrench, tap holder, pitch gauge, driver—in strong metal case. A bargain. 31b



Drop Forged Tempered Chrome Steel Brand New 32-Piece SOCKET SETS — \$7.95


Full range S.A.E.: 3/16" to 7/16" with 1/4" screw drive, 13/32" to 5/8" with hexagon drive, 7/16" to 15/16" with 1/2" hexagon drive. Socket sets are complete with 2 "L" handles, 2 reversible ratchet handles, three-piece adaptor, flex-handle plug wrench, tommy bar and 1/4" universal screwdriver fitting. 3 extension bars complete in strong metal case—a bargain, usually twice this price. 51b.



HEAVY DUTY BATTERY CHARGERS

• Charges 6V and 12V Batteries overnight • High 4-amp. charge rate • 12 mths. written GUARANTEE.

\$29.50



GENERAL ELECTRIC TIME CLOCKS

240 volts A.C. Switching rated at 25 amps. 6000 watts. Has very accurate continuous duty electric clock with stop start setting in the 12 hour range — also 1 hour range. Ideal for stop/start lights, radios, pumps, motors (up to 6 h.p.). Also use as very accurate clock. Brand New. Size 5" x 3" x 2".

\$7.95 1 lb.

New Products

Compact digital multimeter has LED readout

The B & K Precision Model 2800 Digital Multimeter can measure DC and AC voltage and current, along with DC resistance. It has a high input impedance on all voltage ranges, and features a 3½-digit 7mm high LED readout. With automatic offset correction and automatic polarity switching, it offers simple range interpretation and high resolution.

The unit is mounted in an attractive yellow and black plastic case measuring 110 x 160 x 50mm. At the top of the case is an on/off slide switch, with the display underneath it. Two rotary switches are provided at the bottom of the case, one used as a function selector and the other for range. Recessed banana sockets are provided for connection of the test leads, which are supplied with the unit.

Four DC voltage ranges are provided, with nominal full scale readings of 2, 20, 200 and 2000V. A point to watch is that on the 2000V range, the maximum voltage allowable is only 1500V. Accuracy is quoted as $\pm 0.5\%$ of reading, $\pm 0.25\%$ of full scale and ± 1 LSD on the three lowest ranges, with the highest range having approximately half this accuracy.

Four AC voltage ranges are provided, with nominal full scale readings of 2, 20, 200 and 2000V. Average reading circuitry is used, calibrated to read the RMS value of a pure sine wave. The frequency response is quoted as being from 50 to 400Hz. The quoted accuracy is substantially the same as that on the DC ranges. On the highest range, maximum allowable voltage is 1000V.

The input impedance on all voltage ranges is 10 megohms, while overload protection is provided up to 1500VDC or (DC + AC) peak.

Four direct current ranges are provided, with full scale readings of 2, 20, 200 and 2000mA. Quoted accuracy is $\pm 1\%$ of reading, $\pm 0.5\%$ of full scale and ± 1 LSD on the three lower ranges, with the top range having approximately half this accuracy.

As with the voltage ranges, the AC current ranges are similar to the DC current ranges. The current ranges are protected by a fuse (accessible from the



front of the instrument) and by diodes. The nominal voltage drop across the input terminals is 200mV DC or RMS on the three lower ranges, and 700mV DC or RMS on the upper range.

Six ohms ranges are provided, with full scale readings of 200 ohms, 2000 ohms, 20 kilohms, 200 kilohms, 2 megohm and 20 megohm. Test currents are 1mA on the two lowest ranges, 10 μ A on the middle two ranges, and 100nA on the highest ranges. Full scale voltage applied to the test resistor is 0.2V on the 200 ohm, 20 kilohm and 2 megohm ranges, and 2V on the remaining ranges.

Since three of the ohms ranges apply a maximum voltage to the test resistor of 200mV or less (and this is indicated

on the front panel by a H/L ohms indicator), it is possible to perform in circuit tests where there are semiconductor junctions shunting the test resistor.

Similarly, the high ohms positions can be used to make out of circuit tests of semiconductors, in a similar manner to the way in which forward and reverse bias tests are performed with a conventional multimeter.

Overrange indications are provided on all ranges by the display flashing 1999. Negative readings are indicated by a minus sign, with the absence of this implying a positive reading. The settling time for all ranges and functions is typically 0.7 seconds. Power is supplied by four "C" size cells.

These can be either carbon-zinc or alkaline, or rechargeable nickel-cadmium types. An optional charger/converter is available for this last type. A comprehensive instruction manual and circuit diagram is supplied.

In conclusion, the B & K Precision 2800 digital multimeter appears to be a well-designed and constructed test instrument, which would be equally at home in a professional or amateur/hobby test room. It is distributed in Australia by Parameters Pty Ltd, of 68 Alexander Street, Crows Nest 2065. Recommended price is \$131 plus 15% sales tax if applicable. (D.W.E.)

Flattened actuator for toggle switches

C & K Components Inc., USA, is now offering yet another toggle configuration to help improve panel appearance and function.

The new toggle, P4, is a short, flattened actuator, available as an option on any of C & K's 1 pole through 4 pole toggle switches. Dimensions are 8.13mm x 4.19mm at its largest diameter.

P4 features C & K's unique anti-rotation rivet pin. This pin secures the toggle to the bushing and assures true linear toggle motion.

Further information is available from C & K Electronics (Australia) Pty Ltd, PO Box 101, Merrylands, NSW 2160.

LEADER TEST INSTRUMENTS


STEREO

LBO-552

5" Horizontal, Dual Trace/
Dual Chan. Oscilloscope

WITH SIMULTANEOUS LEFT/RIGHT
WAVEFORM DISPLAY

A solid state achievement that makes audio testing, on-line quality control and general purpose measurements easier than ever. Features a horizontal dual trace/dual channel format that lets you view two independent signals simultaneously and side-by-side on a bright CRT display. Perfect for inspecting and aligning the most sophisticated stereo equipment, the LBO-552 also provides a single channel input for conventional readout. Sensitivity is 20mVp-p/cm; Vert. B'width is DC or 2Hz to 2.5MHz. Sweep speeds are from 10Hz to 100KHz in 4 ranges with input impedance 1MΩ shunted by 40pF.
250mm h x 180 w x 380 d; 6.5kg.

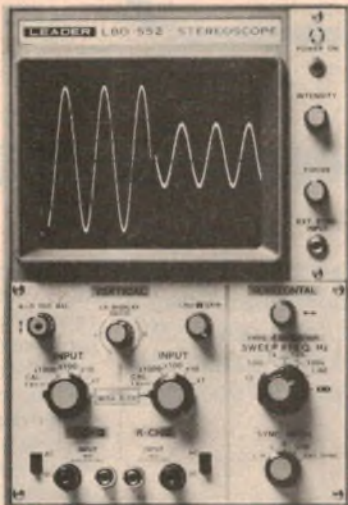

LMV-186A

Dual Chan./
Dual Pointer

AC Millivolt Meter

Check stereo signal quality, especially where a big difference exists in two points. This instrument uses identical switches and amplifiers in each channel to operate without crosstalk effects. Measuring range is 100μV to 300V, 12 steps. It has two dB scales: an easy-to-read meter face; 2 scale readings; built-in dual amplifier output. Accuracy is ±2% full scale (1KHz). Channels operate individually, or in common at ch. 2. Scale calibration reads effective values. With input cable 240V/50Hz.
150mm h x 200 w x 250 d; 3.5kg.



WARBURTON FRANKI

- ADELAIDE 356-7333 • BRISBANE 52-7255 • HOBART 23-1841
- MELBOURNE 699-4999 • PERTH 65-7000 • SYDNEY 648-1711
- AUCKLAND N.Z. 360-154 • WELLINGTON N.Z. 698-272



VIDEO TECHNICS

2ND FLOOR, TELFORD TRUST BUILDING, 79-85 OXFORD STREET, BONDI JUNCTION, NSW 2022. PH. 387 2555.

3RD FLOOR, EQUITABLE LIFE BUILDING, 301 CORONATION DRIVE, BRISBANE 4064. PH. 361 257.

FOCUS INTENSIFIER



Announcing our video focus intensifier to improve the playback quality of all VCR system video recorders.

This consists of a small circuit board which fits inside the VCR (Philips etc.)

This circuit detects a change in picture contrast and inserts a transient—in effect an extra—signal at this point, which crispens the image. The effect if the size of this transient is adequate is to recover lost sharpness, and the principle is indeed very effective. Full fitting instructions included.

\$39.00 + P.P.

VIDEO EQUIPMENT—Sony, Akai, Portopacks. Also agents for J.V.C. and National. All formats and brands Colour and BW RECORDERS, EDITORS, GENERATORS AND BLANK VIDEO TAPE AVAILABLE. New and used equipment Trade and terms. Specials. We have several BW Portopacks traded on colour sets.



COLOUR TV TUNER

VIDEO TECHNICS
COLOUR TV TUNER MODEL HD6709

- Record one channel while watching another
- No modification required to existing television sets
- Will record while TV set is off
- Usable with any video recorder BW or Colour with an RF output which means this tuner allows video recording of TV programs and playback through aerial input of TV set. **\$295.00 + P.P.**

SPECIAL CLOCK TIMERS

Can be set to switch equipment up to 4 days ahead.



Starting time accurate to a second
\$195 + P.P.

You'll never have to miss a favourite TV programme—whatever you're doing



PHILIPS

N 1502 \$1.145

N 1512 \$1,350 with video camera input

Will receive and record all Aust. channels. Stocks now available \$1.145 incl. S.T. Shipped anywhere in Australia freight on.

FRANCHISEES REQUIRED FOR S.A., W.A., VICTORIA AND TASMANIA

Wide band, variable persistence, storage oscilloscope

BWD Electronics Pty Ltd, has now added the Model BWD 845, high sensitivity, wide band, portable, variable persistence, storage oscilloscope to its extensive oscilloscope range.


This model incorporates a wide range of storage modes, has high sensitivity (1mV), 30MHz bandwidth vertical amplifiers, wide range delayed or mixed time base with comprehensive trigger facilities, and can be either mains or battery powered.

The BWD 845 provides two operating conditions for the storage mode — fast and normal. By writing in the fast mode then switching to normal, storage times up to 50 minutes are available depending on background level. Additional signals can of course be stored at any time during this period.

Maximum writing speed is specified at 1usec/div but speeds up to 5 div/usec can be achieved over most of the screen. Repetitive displays can extend the writing speed to the bandwidth limit of the oscilloscope.

Many storage scopes offer only a limited pretrigger period before the CRT fades positive, when attempting to store single shot transients. The BWD 845 incorporates an Auto Store facility to hold the CRT in the erase mode. This extends the waiting period to several hours before the time base is triggered, writes the display, then automatically switches to store.

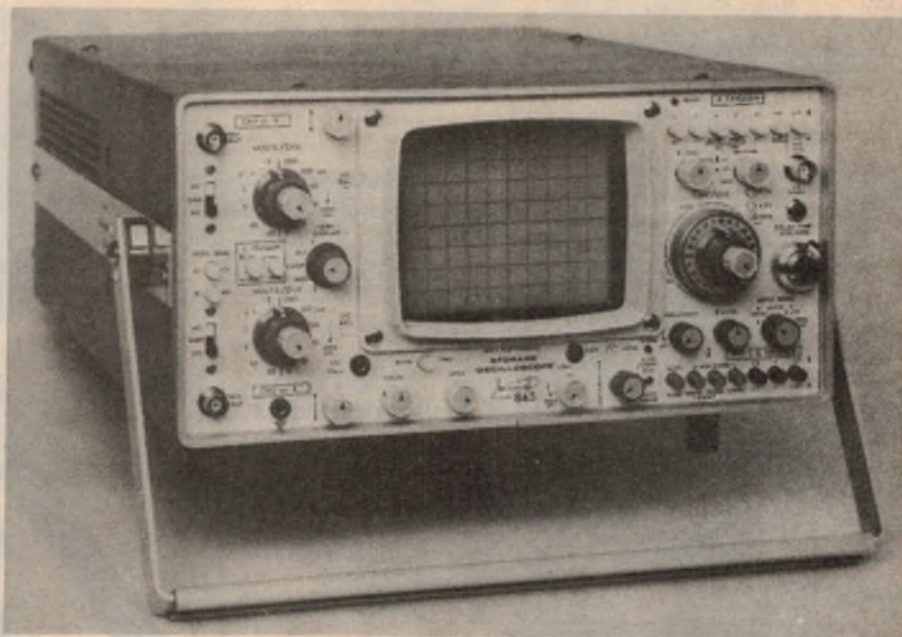Another feature is the Auto Write, View and Erase cycle which continuously erases the display, then awaits for a signal to be written, switches to view for approximately four seconds, then erases and the cycle repeats.




In addition to providing a high performance instrument, BWD Electronics has given considerable attention to internal mechanical design to provide ease of alignment and servicing. Circuits are based on thick film networks, and standard readily available integrated circuits and discrete components.

The attractive cabinet design with colour co-ordinated controls incorporates a carrying handle and provision for battery pack and front panel protective cover fitting. A range of accessories is available to further extend its versatility.

Further details are available from BWD Electronics Pty Ltd, Miles Street, Mulgrave, Victoria 3170.

Prototyping aid

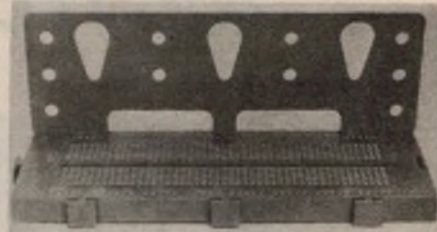Dick Smith Electronics has submitted for review a sample of the Bimboard prototyping aid. It is intended for use with integrated circuits, but can also be used successfully with discrete components.



The breadboard consists of two sections, the base section which performs the interconnections, and a clip-on plastic backplate which can be used to mount controls, switches and terminals. The base section contains two rows of contacts, each row being divided into columns of five contacts. There are 47 pairs of columns.

In addition, there are rows of contacts at the top and bottom of the assembly, which are intended to be used for power supply rails. Each individual socket is capable of accepting wires with diameters between 0.25mm and 0.85mm, and can carry a current of 1 amp.

Each Bimboard is fitted with lugs on all four edges, which enable separate units to be coupled together to form a larger unit. They are available from Dick Smith Electronics Pty Ltd, and have a recommended retail price of \$22.50. (D.W.E.).

"Bin Boxes" for component storage

Efficient and convenient component storage is a common problem, whether it be for the individual in his workshop or the businessman on his stock shelves. A neat and economical solution to this problem is offered in the form of "Bin Boxes" — stout corrugated cardboard containers specifically designed for just this application.

Bin Boxes are made by Corrugated Paper Manufacturing Co Pty Ltd, of Leichhardt NSW and are available from Radio Despatch Service, 869 George Street, Sydney. Radio Despatch are stocking four sizes, three of which are illustrated. These are the models 1000 (230 x 100 x 100mm), 2000 (300 x 50 x 110mm), and 4000 (300 x 150 x 110mm). The model 3000 measures 300 x 110 x 100mm.


The boxes are supplied flat but are easily folded into their final shape and



lock together quite rigidly.

Recommended prices (one off) are: Model 1000 37c; Model 2000 42c; Model 3000 45c; Model 4000 56c plus 15 per cent sales tax where applicable. Radio Despatch anticipate that prices for quantity orders (above 25, mixed sizes) should be substantially lower.

Soldering printed circuits?

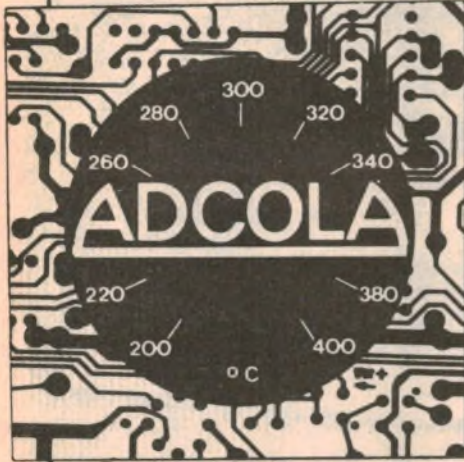

The Duotemp protects circuits and components at a cost far lower than soldering tools with automatic temperature control.

- Correct soldering temperature for printed circuits.
- Fast heat-up and heat recovery.
- Power boost for long sequences or heavy joints.

From your electronic parts supplier
or enquire from
ADCOLA PRODUCTS

Melbourne, 848 3777. Sydney, 709 5293.
Brisbane, 52 3166. Adelaide, 42 6655.
Hobart, 34 2233. Launceston, 31 2511.
Perth, 81 5500

A77



THE PUSH BUTTON . . .


The Duotemp soldering tool will idle all day on half-wave AC without overheating. A touch of the button converts it to full wave, instantly doubling the thermal capacity.

DUOTEMP

AVAILABLE IN 240V AC & 24V AC

MODEL D30	3mm tip
MODEL D50	5mm tip
MODEL D65	6.5mm tip

AUDITEC A-SERIES AMPLIFIERS

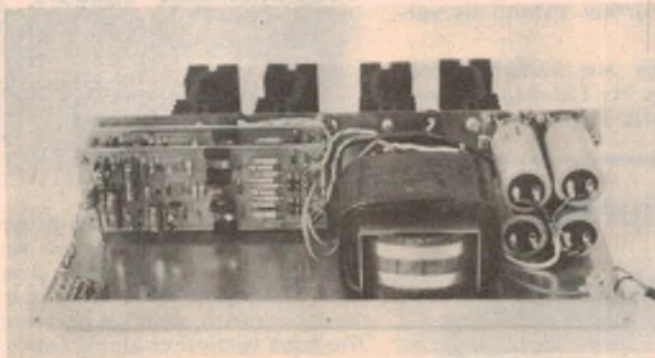

**THE A-SERIES ARE
NO-FRILLS BASIC POWER AMPLIFIERS
READY TO CONNECT TO YOUR
PREAMPLIFIERS OR MIXER
AND LOUSPEAKERS**

**AVAILABLE IN 1 x 100 WATT (1A009, 1A033)
2 x 100 WATT (2A009, 2A033)
1 x 200 WATT (1A027)**

AGENTS:

MELBOURNE: Zephyr Products. Phone 568 2922
BRISBANE: Delsound Pty Ltd. Phone 229 6155
ADELAIDE: Nell Muller Pty Ltd. Phone 74 1162
BUNDABERG: Bundaberg Hi-Fi. Phone 71 3176
CANBERRA: Musique Boutique. Phone 82 2553
PERTH: Willis Trading Co Pty Ltd. Phone 21 7609
TAMWORTH: Hi-Fi Gallery. Phone 65 7788
MARYBOROUGH (QLD): Keller Electronics. Phone 21 4559
ROCKHAMPTON (QLD): Premier Sound. Phone 28 2701
SURFERS PARADISE (QLD): Beno's Musical Supplies. Phone 38 1568
WHYALLA (S.A.): Audiolab Sales. Phone 45 7755
DARWIN: Darwin Communications Systems. Phone 85 3184
ALICE SPRINGS: Farmer & Davies Electronics. Phone 52 2967

FOR DESCRIPTIVE LEAFLETS ON THESE AMPLIFIERS
CALL, PHONE OR WRITE TO:

AUDITEC AUSTRALIA PTY LTD
10 WAITARA AVENUE, WAITARA, N.S.W. 2077
PHONE: 48 4116

(PACIFIC HIGHWAY SIDE OF WAITARA STATION)


Roll your own 1kVA power transformer!

Designed for experimental work, this power transformer has an unusual and unique design feature — it lets you determine the output voltage by winding on your own secondary (or secondaries).

Rated at a hefty 1kVA, the new transformer measures a bulky 240 x 185 x 120mm (H x W x D). The unit features a primary winding wound on a large toroidal core, fully encapsulated in epoxy and enclosed in a heavy duty, high impact plastic case for safety. Mounting feet and a carrying handle are fitted to the case.

The user winds the secondary (or secondaries) himself, a feature which enables the secondary voltage to be tailored to requirements. Each turn through the toroid core gives 1V, the only precautions necessary being to ensure that the secondary winding is capable of carrying the required current and that the transformer rating is not exceeded.

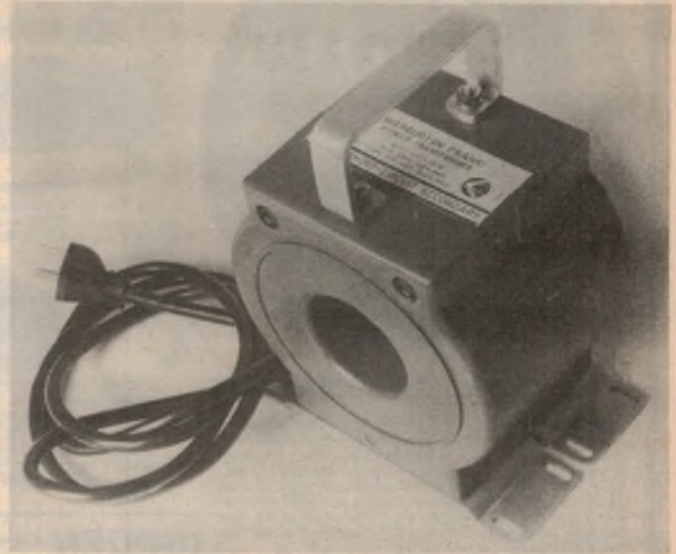The unit is expected to sell for less than \$100. For further information contact Warburton-Franki Pty Ltd, 372 Eastern Valley Way, Chatswood 2067.



Key-operated switch



A range of Yale key operated security switches is now available from C & K Australia.

Switch type KMS (pictured) is available with a double pole mains switch and carries a rating of 4A at 250V AC or 10A at 12V AC. The unit has a two-position 60° movement, and the key may be trapped or withdrawable in either position. Alternatively, a spring return or non-latching style can be provided.

Switch type KRA allows for the stacking of switch wafers at the rear of the mechanism, giving a maximum number of six positions at 60° indexing. This offers the same circuit flexibility as a multi-pole multi-bank rotary switch.

The lock mechanism is a Yale 5-disc type supplied with two keys and offering 200 different key combinations.

Enquiries to C & K Electronics (Aust.) Pty Ltd, PO Box 101 Merrylands 2160.

Name change

MS Components Pty Ltd has advised that the company has now changed name to Sheridan Electronics Pty Ltd. The company will continue trading at 164-166 Redfern St, Redfern 2016. A wide range of electronic components and equipment is offered.

Nutdriver set for service work

The Cooper Tool Group, Albury, now has available the PS-120 Xcelite nutdriver set for electronic and service engineers.

The set consists of 10 small nutdrivers and a torque amplifier. The torque amplifier handle slips over the nutdriver handles to provide a larger gripping surface, extended reach and increased driving power.

Nut sizes catered for by the PS-120 nutdriver set range from 3/32-inch to 3/8-inch. The complete set is contained in a convenient plastic carrying case, as pictured.



Readers requiring further information should contact The Cooper Tool Group, Nurigong Street, Albury, NSW 2640.

TRANSFORMERS:

12 or 24 Volt Range: Primaries 220/240 volts

Ref.	12v Amps	24v Amps	Wt. Gms	Secondary Windings	Price \$
242	300MA	150MA	198	0.12V at 150 MA x 2	2.25
111	0.5	0.25	283	0.12V at 0.25A x 2	3.25
213	1.0	0.5	425	0.12V at 0.5A x 2	4.00
71	2	1	793	0.12V at 1A x 2	6.00
18	4	2	1020	0.12V at 2A x 2	7.50
70	6	3	1538	0.12V at 3A x 2	11.50
108	8	4	2268	0.12V at 4A x 2	12.50
116	12	6	2722	0.12V at 6A x 2	14.00
115	20	10	5300	0.12V at 10A x 2	20.25

30 Volt Range: Primaries 220/240 volts
Voltages obtainable 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30 or 12.0-12 or 15.0-15.

Ref.	Amps	Wt. Gms	Secondary Taps	Price \$
112	0.5	623	0.12-15-20-24-30	5.00
79	1	737	0.12-15-20-24-30	6.25
3	2	1361	0.12-15-20-24-30	8.50
21	4	2600	0.12-15-20-24-30	10.50
89	10	5670	0.12-15-20-24-30	21.75

50 Volt Range: Primaries 220/240 volts
Voltages obtainable 6, 7, 8, 10, 14, 15, 17, 19, 21, 25, 31, 33, 40, 50 or 25.0-25.

Ref.	Amps	Wt.	Secondary Taps	Price \$
102	0.5	737	0.19-25-33-40-50 V	7.00
103	1	1304	0.19-25-33-40-50 V	8.00
104	2	2485	0.19-25-33-40-50 V	10.50
105	3	3176	0.19-25-33-40-50 V	12.50
106	4	4100	0.19-25-33-40-50 V	15.00
107	6	5444	0.19-25-33-40-50 V	22.00

60 Volt Range: Primaries 220/240 volts
Voltages obtainable 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24.0-24 or 30.0-30.

Ref.	Amps	Wt.	Secondary Taps	Price \$
124	0.5	737	0.24-30-40-48-60 V	6.50
126	1	1361	0.24-30-40-48-60 V	8.00
127	2	2485	0.24-30-40-48-60 V	10.50
125	3	4083	0.24-30-40-48-60 V	15.50
40	5	5670	0.24-30-40-48-60 V	21.00

Miniature transformers with across: Primaries 220/240 volts

Ref.	MA	Wt. Gms	Voltage	Price \$
238	200	85	3.0/3	2.50
212	1A, 1A	595	0.6/0.6	3.50
13	100	113	9.0/9	2.50
236	330/330	198	0.9/0.9	2.50
207	500/500	566	0.8-9/0.8-9	3.25
205	500/600	1077	0.15-20/0.15-20	6.00
214	300/300	623	0.20/0.20	4.00
221	700/1000	737	20-12/0.12/20	6.50
206	1A, 1A	1204	0.15-20/0.15-20	9.00
203	500/500	822	0.15-27/0.15-27	8.50
204	1A, 1A	1417	0.15-27/0.15-27	12.00

Battery Charger Types: Primaries 220/240 volts Secondary 2v, 6v, 12v DC (Rectified)

Ref.	AMPS	Wt. Gms	Price \$
45	1.5	737	6.00
5	4.0	1474	8.50
86	6.0	2608	11.50
146	8.0	3175	13.00
147	10	4082	15.00

Prices do not include postage or packing. Assess postage to your address using weights given and add 10% of postage rate for packing. Unless quoting sales tax number add 15% to order cost.


DOUGLAS TRANSFORMERS, BOX 23, COORANBONG, NSW. 2265.

Personal Callers: 477 Freemans Drive, Cooranbong Telephone (049) 77 1431.



...TOPS FOR HAM GEAR

DISTRIBUTORS OF QUALITY ICOM PRODUCTS

 

IC225 2m fm synthesised with programmable matrix. ICOM quality with back-up technical support. Price \$279.



WARNING: The law requires that a licence be held for all transmitting equipment. Purchasers may be asked to produce a licence when buying equipment.

HANDY ICOM PORTABLES

IC202 2m ssb/cw	\$199
IC502 6m ssb/cw	\$219
IC215 2m fm	\$199
BC-20 nicad pack	\$57
IC50L 10w linear 6m	\$98
IC20L 10w linear 2m	\$98
Rubber Ducky for IC215	\$13

... It's just the beginning.

At VICOM we provide a whole World of communications products including CB, Military and Amateur Radio, our speciality. VICOM didn't reach the top without providing Amateurs in Australia with the technical back-up and support demanded in marketing specialised sophisticated commercial equipment. Come and see our wide range of transceivers and accessories and receive some of that friendly personalised service for which VICOM has become famous!



Yaesu FT101E transceiver 160-10m including speech processor, VICOM 90 day warranty. Price \$839



The TS820S from VICOM is the rig that is the talk of the Ham bands. Too many built-in features to list here! What a rig and only \$990 complete with digital display! Many accessories available to increase your operating pleasure and station versatility.



ATLAS 350-XL

The ATLAS 350-XL from VICOM is the new, all solid state ssb transceiver, 350w pep input with coverage 160 thru 10 metres. Plug in options include digital display, auxiliary VFO and auxiliary oscillator. Superb selectivity for which ATLAS have become famous.

ROTATORS

ART3000C Heavy Duty with 240v con box	\$199
ART9000 Super Heavy Duty 240v con box	\$478
CDE CD44 medium duty 240v control box	\$192
CDE AR22XL light duty 240v control box	\$109
8 core cable per meter	\$1.40



VICOM brings the VFO revolution to you with the IC245 mobile 144 thru 148MHz transceiver. The IC245 features accurate tuning over 50 detent steps, digital display in 5KHz steps, modes: fm, ssb (with optional adapter only) and cw. Carrier suppression better than 40dB. TX output 10w fm. Comes complete with mic, bracket, manual and VICOM 90 day warranty.



ICOM IC-245



ICOM IC211 2m fm transceiver. The new IC211 from VICOM is the last word in digital 2m, all-mode transceivers. Fully synthesised in 100Hz or 5KHz steps, has dual tracking, optically coupled VFOs with 7 digit LED readout. One knob controls all frequencies. Modes fm, usb, lsb, cw. Internal 240vac and 13.8vdc power supply. Comes complete with VICOM 90 day warranty, freight and insurance.

UNIDEN the best value



The fabulous UNIDEN 2020 p11 transceiver offers separate usb, lsb and cw 8-pole filters as STANDARD and 6146Bs in the final with screen grid voltage stabilisation for minimum distortion products. Features pcbs and even the front panel can be swung out for easy servicing! A comprehensive range of spare parts is available together with back-up service support. Overseas this rig sells for at least \$65 more than the FT101E! Compare the features of the UNIDEN 2020 with other HF transceivers and you'll quickly be convinced that it offers the best value!

Popular VC2 SWR meter operates 3-150 MHz with power measurement 12/120 watts. Will handle up to 1000 watts. 50 ohms impedance, twin meters. A bargain!

VC2 SWR \$38

ANTENNAS

BASE & MOBILE

Space 2m 1/4 wave model 42S, complete with assembly	\$14
Space 2m 5/8 wave model 82D, complete with assembly	\$26
Lindenow 5/8 wave quality 2m (incl base)	\$26
Ringo Ranger ARX 2 for 2m	\$45

VHF/UHF BEAM ANTENNAS

JAYBEAM	
5Y/2M 2m 5el 7.8dBd gain	\$29
8Y/2M 2m 8el 9.5dBd gain	\$35
10Y/2M 10el 11.4dBd gain	\$59
10XY/2M crossed yagi 11.3dBd	\$68
D8/70cm twin 8el 12.3dBd	\$48
PBM18/70cm 18el 70cm 14.9dBd	\$59
MBM88/70cm 88el 70cm 18.5dBd	\$75
MBM48/70cm 48el 70cm 14.5dBd	\$59



Why take the gamble. All rigs sold by VICOM are given a thorough pre-delivery check-out supported by technical expertise and well equipped workshops. Spare parts are available too.

PARABOLIC DISH ANTENNA

For 430 and 1296MHz	\$349
---------------------	-------

MORSE KEYS

Economy model KH70E	\$19
Operator model HK70E	\$20
Deluxe model HK70Z	\$35
Electronic Keyer EK103	\$159
Manipulator MK701	\$38

RECEIVERS

Yaesu-Musen FRG-7	\$325
Barlow-Wadley with FM	\$339
NRD 505 Professional	\$2499

TRAP DIPOLES

AL48DXN 40/80 metres	\$49
AL24DXN 20/40 metres	\$47
MIDY VN 80 thru 10 m	\$65

BALUNS

AS BL (Asahi) for beams	\$30
BN-86 (Hy Grain) for beams	\$30
BL50A 50 ohms, 4kW model	\$24
BL70A 70 ohms, 4kW model	\$24



The FL2100B linear uses two rugged 572B carbon plate tubes in class B grounded grid circuit with individually tuned input coils for each band. Covers 80 thru 10 metres at 1200W pep input. Price \$524.

FL-2100B linear amplifier



TS220S the transceiver that has made the Kenwood name near and dear to amateur operators around the World. Reliability is the name of the rig in capital letters! 160 metres thru 10 metres with many built-in features.



The new HAL KSR3000 send/receive RTTY terminal including keyboard and video display, features scrolling, continuous, word or line transmission and firmware for word wrap-around and blankfill. Handles Baudot and ASC11 (8-level) with a screen size up to 1152 chs. List price \$1499. Write (including SAE) for complete specifications.

A whole world of communications products.

VICOM

Head Office & Mail orders—

139 AUBURN RD. AUBURN. VIC. 3123
 Phone: (03) 82.5398, (03) 813.2355 Telex: AA30566
 Adelaide (437981) Brisbane (3844480)
 Canberra (823581) Perth (4633232)

Direction: Russell J. Kelly VK3NT
 Peter D. Williams VK3IZ

The Amateur Bands

by Pierce Healy, VK2APQ



What does the future hold?

This month's notes feature a message written on behalf of the WIA federal executive, concerning CB radio, which every amateur would be wise to consider at length. Also included are details of an amateur radio seminar and the usual club notes.

Will the current loss of the 11 metre band to the CB radio service actually result in a future gain for amateur radio in Australia?

This seems to be a topical subject discussed among amateurs. Here are some points for consideration. From the Wireless Institute of Australia federal executive headquarters came a copy of the main QSP for the October 1977 issue of the WIA magazine *Amateur Radio*.

Under the caption "CB — What Now?" Michael Owen, VK3KI, writes on behalf of the federal executive.

"Legal CB is a fact of life.

"Amateurs have 'temporarily' lost the 11 metre band. We say 'temporarily' not because we do not accept the sincerity of the Minister and his advisers (we do), but because we doubt the practicability of clearing that band when the time comes.

"The Institute believes that there are grounds for legitimate criticism of the way the issue has been handled and also that there are some very valuable potential advantages for the amateur service arising from the introduction of CB.

"Let's make our criticism clear. Quite apart from the loss of the 11 metre band, bad enough in itself, there are features that make that loss worse.

"The Institute argued that novices should be allowed to use the 10 metre band. The Department insisted on allocating the 11 metre band. So novices set themselves up on 11 metres only to be told to shift back to the very band the Institute had proposed all along. Many amateurs have expressed concern that might seem to have become right. Meanwhile, the law abiding amateur sees legitimate request after request piling up in some bottomless Departmental pending tray.

"The Institute does not criticize CB as such. It does, however, see recent history as a sorry story of Departmental procrastination, bungling and ineptitude.

"In fact, the Institute sees the introduction of CB as an important phase in the growth of amateur radio in Australia. Most CBers want to be law abiding. There are a few that have shown themselves to be irresponsible, to say the least, but the same criticism could be levelled at some (though very few) amateurs.

"For many, CB is the first introduction to radio communication. Many have found quickly how much more the amateur can do. They aspire to become amateurs, first novices, then full licensees. That is no new discovery on our part. The APRI has embarked on a program of seeking to attract CBers to amateur ranks. Many individual clubs in Australia have already started to do that, too.

"The numbers of amateurs in the USA and the membership of ARRL has grown thanks, in part, to CB. We say 'in part' because the other part has been the active encouragement of converts by

ARRL and US amateurs. The message for us is clear. We are not at war with CB radio. We want CBers to upgrade to amateur radio.

"We should make one point clear. It was suggested that CB could be introduced in Australia as a fourth kind of amateur licence, without code, and with no more proficiency than the ability to know which knob to turn. The Institute rejects that flatly. That is pulling the amateur service the wrong way — we hope that CBers want to become amateurs. If amateurs become CBers the whole foundation for the amateur service is lost. We have privilege, yes, but that is privilege that has been earned, individually and collectively.

"So let's sum up what the Institute says about CB and the wider implications of recent history. We have made our point about the manner in which CB has been introduced. We take that point further. With the introduction of CB we have seen a significant area of deregulation. The Institute has, we believe, acted with responsibility and restraint. We urge amateurs individually to do the same. But that should not be the basis for the Department to pretend that amateurs can be ignored. It is now up to the Department to show that it can be responsive to the highly disciplined and law-abiding group constituting the amateurs of this country.

"Our next point is this. There is a law governing the use of radio frequency. We have seen that law not enforced, but ignored. The Institute sees real need for new legislation, capable of proper enforcement, dealing, for example, harshly with hoax distress calls and the like. That law should be enforced. Curbs in government spending are not a matter on which the Institute makes any general comment. It does make the specific comment that law enforcement should not be curtailed for reasons of economy. The law must be a law that does not inhibit the legitimate use of radio frequency by pettifogging regulation, but does enable easier control of illegitimate use of radio frequency. Unnecessary regulation imposes a cost burden on the administrator and licensee, and may be self-defeating in that restriction without reason will never achieve acceptance.

"Our final point is this. We welcome the introduction of CB radio as a vast reservoir of potential amateurs. Many, we know, will be content to use what they now have. Others will, for the very reasons that led them into CB, seek to widen their horizons by becoming amateurs.

"We will be very foolish indeed if we do anything less than offering these people the tullest encouragement to upgrade to amateur radio."

In Sydney NSW some amateurs who were operating on the 11 metre band prior to the introduction of CB radio are now operating on this band as CBers within the regulations. They have formed the Amateur and Citizens' Radio Club

(VKCB Club). They are using the words "Amateur Radio" in lieu of the "VK" prefix to their amateur call sign. The aim is to give example on good operating techniques as well as helping the newcomer who is having equipment problems or the CBer who wants to know more about amateur radio.

The stated philosophy of the VKCB club is that it recognises the interest in amateur radio among the CBers as well as assisting CBers to become amateurs they are also assisting the on air community in the use of radio as a communication medium.

The club aims to affiliate with the Wireless Institute of Australia and its Youth Radio Scheme and the NCRA, and will attempt to organise national involvement of amateurs and CBers.

Membership requirements for those not holding an amateur licence include a five-hour training session by one of the club's instructors. On qualifying, such members will be allocated a call sign — Amateur Radio followed by the standard state number and a numerical suffix, eg. for NSW — Amateur Radio 2 001.

The secretary is Sam Voron, VK2BVS, 2 Griffith Avenue, Roseville, who provided this information.

AMATEUR RADIO SEMINAR

A seminar with the theme "Antennas and Propagation", organised by the Frankston and Mornington Peninsula Amateur Radio Club, will be held over the weekend 19th and 20th November, 1977. The venue is the Prince of Wales Hotel, St Kilda, Melbourne.

The club is interested in encouraging delegates from interstate and country areas and is subsidising the accommodation costs, limited to 30 interstate, on a first come first served basis.

FAMPARC Seminar program details:

Saturday —

- 9.00-10.15 Registration.
- 9.45-10.10 Coffee and conversation.
- Morning session:
- 10.15-10.45 Introduction and opening "WARC and You" Michael Owen, VK3KI.
- 11.00-11.40 "Design of Long Yagi Antennas for VHF and UHF" Les Jenkins, VK3ZBJ.
- 12.00-12.40 "Construction and Applications of Parabolic Reflectors" Ray Naughton, VK3ATN.
- 1.00- 1.55 Lunch
- Afternoon Session:
- 2.00 2.40 "Meaningful Antenna Measurements" Peter Cousins, VK3BFG.
- 3.00- 3.30 "Antenna Requirements for Earth Satellite Communications" John Sved, VK3ZVZ.
- 3.40- 4.00 Coffee break.
- 4.00- 4.40 "HF Propagation and Amateur Radio" Earl Russell, VK3BER & Associate.
- End of session.
- Dinner.

Sunday —

- 10.30-11.00 Wireless Institute Broadcast.
- Coffee.
- 11.15-11.50 "Emergency HF Antenna Systems" Harold Hepburn, VK3AFQ.
- 12.05-12.45 "Vehicle Mounted Antennas for HF Operation" Peter Williams, VK3IZ.
- 1.00- 1.55 Lunch.
- 2.00- 3.00 General discussion and question session — closing remarks, etc.
- End of seminar.

Two package deals are available to interstate delegates —

Package 1 includes: Two nights' accommodation, twin share basis. Morning and afternoon tea, both days. Lunch, both days. Dinner, Saturday night. Also bound copy of papers. Cost \$44.00.

Package 2 includes: One night accommodation, twin share basis; plus other items as above. Cost \$38.00.

Packages on a non-resident basis are available for local delegates. Package 3 as for package 1. Cost \$35.00. Package 4 — Saturday only includes: Dinner Saturday night; morning and afternoon tea and lunch. Package 5 includes: Morning and afternoon tea and lunch Sunday only.

As official carrier for the FAMPARC Seminar,

Radio clubs and other organisations, as well as individual amateur operators, are cordially invited to submit news and notes of their activities for inclusion in these columns. Photographs will be published when of sufficient general interest, and where space permits. All material should be sent to Pierce Healy at 69 Taylor Street, Bankstown 2200.

AMATEUR BANDS

ANSETT Airlines offers a personalised service and personnel at their major city offices will be fully conversant with all aspects of this meeting.

Delegates who intend to travel by air should check air fares and flight times with their local Ansett contact and forward air fare and registration fee to:

Seminar Secretary, PO Box 38, Frankston, Vic. 3199, together with the following details: Name, address, phone No., call sign, flight No., time.

RADIO CLUB NEWS

LADIES AMATEUR RADIO ASSOCIATION: LARA has just celebrated its second birthday. Those Victorian members strong and foolhardy enough to brave the cold weather, ventured up to Cherokee on Mt Macedon where a birthday cake and barbecued burnt offerings were consumed.

LARA holds a regular weekly net on Monday evenings at 8.00 pm EST (8.30 pm during daylight saving time) on 3.65MHz.

Ladies interested in amateur radio may contact LARA through the net or the secretary, c/- 412 Brunswick Street, Fitzroy, Vic. 3065.

TOWNSVILLE AMATEUR RADIO CLUB: The third biennial North Queensland Convention held over the weekend 23rd-24th July, 1977, at the Hermit Park School, Townsville, was a great success.

The official opening was conducted by the Mayor of Townsville, Alderman P. Tucker. In his speech Alderman Tucker said he was very much aware that the Townsville Radio Club and amateur radio operators throughout North Queensland have a very high standing in their communities. Their specialist skills are very important to North Queensland in times of disaster, particularly when storms like cyclone Althea threaten the Queensland coast.

The convention program provided an interesting weekend for amateurs as well as for wives and families.

A highlight was the visit to the James Cook

University, as guests of Professor James Ward and his associates Dr Mal Heron, Mr Stuart Bayliss and Dr Graeme Hicks. Speaking briefly on the subjects to be covered, Professor Ward mentioned ocean radar and the electrical activities associated with cyclones.

Other subjects were VLF work associated with the Americans at North West Cape in West Australia, the means to explore from 60 metres down, VNG work on 12MHz from Victoria to Townsville (results of which are being computerised), satellite cloud pictures, defraction patterns, laser experiments, whip antennas, polarimeter and ionospheric.

Saturday evening was a social night with a smorgasbord and presentation of prizes. There was a barbecue lunch on Sunday, and visitors were treated to a display by the Townsville Highland Band and some of their young dancers.

Visitors included Dave Laurie, VK4DT president of the Queensland division WIA and Mark Churton, ZL1TB from New Zealand.

It was pleasing to receive a note from the convention convener, Graham Sargent, VK4ZGB who commented: "Undoubtedly quite a few visitors to the convention came as a result of reading about it in your 'Electronics Australia' column."

GOLD COAST RADIO CLUB: At a recent meeting it was decided that future fox-hunts will carry a perpetual trophy for both first and last prizes. The next hunt has been organised for Sunday, 13th November, 1977, starting at 9.30 am from the Main Place shopping centre at Broadbeach.

A nice gesture has been made in relation to the GCRC general meeting to be held on the second Friday in November, as notified in the GCRC newsletter.

"As there is a member of the club who, due to health reasons, cannot attend our meetings, it is with great pleasure that arrangements have been made to take the meeting to Don's place.

"We trust that as many members as possible will try to attend as Don will get a great kick out of it."

The member is Don Soraghan, VK2PU, who lives just across the Queensland border at Kingscliff, NSW.

DARWIN AMATEUR RADIO CLUB: The president, Graham Vayro VK8CEC, reports that the novice licence scheme operated by the club appears to be working well and he has finally seen reward for many hours spent restoring outpost and marine radios for novice use. The AM/CW net is well attended and they are proud that Darwin is probably the only place where a new novice licensee can at least get on the air with a club owned AM/CW transceiver with no personal financial outlay.

On Sunday, 12th June, 1977, the club provided communications for the Darwin Annual Beer Can Regatta. The exercise was a success and certainly contributed greatly to the success of the regatta.

Three things were achieved. First and most important was the public relations aspect. It was a good start in placing amateur radio back in the public eye in its true context. Secondly, as a WICEN exercise, valuable experience was gained in what would appear to be a simple matter of operating portable, handling messages and maintain net discipline. Thirdly, the opportunity was provided for new members to gain experience.

SUMMERLAND RADIO CLUB: Two classes are in progress for the novice examinations and an invitation is extended to those wishing to increase their knowledge to attend club meetings held on Fridays at 7.30 pm in St Peters Church of England Hall, Ballina Road, Goonellabah, NSW.

Warwick Ford, VK2ZLD has colour TV operating in the 70cm band with 150 watts of video and inter-carrier sound. The transmitter, converter, video mixers, effects generator and sound gear are all home built. The colour camera is a commercial valve type. Very good results and coverage are achieved.

MID SOUTH COAST AMATEUR RADIO CLUB: This club was formed about one year ago for the main purpose of establishing a repeater on 144MHz to serve the Princes Highway and pleasure resorts along the coast from Kiama to Narooma. At present their repeater, VK2RMU, is operating on Channel 2 from a temporary location at Milton.

The club has established an access point for the Mt Ginini repeater (VK1RGI on Channel 7) for use by those travelling through Ulladulla. This is a beam antenna at the side of the road with a length of feeder to connect to equipment in a car.

Amateur operators wishing to make use of this facility should contact the secretary, Doug Allen, VK2YDA, 1 Geoffrey Street, Ulladulla, NSW 2539. Telephone (044) 55-2394. Club membership totals around 50, scattered from Sydney to south of Narooma and westwards to Canberra. A club net, 'Lyrebird net', runs on Channel 2 repeater VK2RUMU each Wednesday evening at 8.30 pm.

ILLAWARRA AMATEUR RADIO SOCIETY: The VK2AMW moonbounce (EME) tests for July were made on the 27th with WA2VWL, YV5ZZ, W5FF and XE1RY. Although VK2AMW echoes were 6dB to 7dB above noise none of the scheduled stations appeared. K3NSS was heard on 432.015MHz and later on 432.010MHz with signal strength up to 15dB above noise. This big signal came from a 25.5 metre dish antenna at the US Naval communica-

BRIGHT STAR CRYSTALS PTY LTD

35 EILEEN ROAD CLAYTON VICTORIA 546 5076
(ALL MAIL TO - P O. BOX 42 SPRINGVALE, VIC. 3171)

**MAY WE REMIND YOU
THAT BRIGHT STAR CRYSTALS
HAVE MORE THAN 36 YEARS
EXPERIENCE IN**



**WATCH CRYSTALS 32.768 KHz
NOW AVAILABLE
MADE IN AUSTRALIA**

HOSE & EQUIPMENT CO. PTY. LTD. SYDNEY. PHONE 666-8144

COMMUNICATION SYSTEMS
PERTH. PHONE 76 2566

FRED HOE & SONS PTY. LTD.
BRISBANE PHONE 47 4311

ROGERS ELECTRONICS
ADELAIDE PHONE 42 6666

DILMOND INSTRUMENTS
HOBART PHONE 47 9077

SO YOU WANT TO BE A RADIO AMATEUR?

To achieve this aim, why not undertake one of the Courses conducted by the Wireless Institute of Australia? Established in 1910 to further the interests of Amateur Radio, the Institute is well qualified to assist you to your goal. Correspondence Courses are available at any time. Personal classes commence in February each year.

For further information write to

**THE COURSE SUPERVISOR,
W.I.A.
14 ATCHISON STREET,
CROWS NEST, N.S.W. 2065**

tion Station in Washington DC.

Repairs to the antenna dish surface were made during August and the main part of the Clavin feed system was made and installed. Initial tests showed little improvement in gain, but the required impedance matching arrangement has yet to be installed to give the lowest SWR.

An E-M-E test scheduled for the 2nd September, 1977, resulted in a contact being made with F2TU with "M" reports both ways. The other station scheduled for tests, SM2BFBK, was not heard.

The committee of the IARC has decided to assist the WIA with WARC 79 expenses, and has organised a guessing competition. The first prize is a single beam CRO-Trio CO1303D with a 75cm tube and is good to 5MHz.

Second prize is a Texas Instruments programmable calculator and third prize a Texas Instruments digital watch.

Entry fee is \$1.00 with a maximum of 1000 tickets. Details from the secretary, PO Box 1838, Wollongong, NSW 2500.

WEST AUSTRALIAN VHF GROUP (INC): Office-bearers elected at the annual general meeting in July 1977 are: Rod Henderson, VK6RH — president; Bob Pine, VK6ZFY — vice-president; Peter Morgan, VK6ZEG — secretary; Jack Zeffert — treasurer; committee — Ron Fisher, VK6PR; Tom Berg, VK6ZAF; Gill Weaver, VK6YL Graham Grieve, VK6ZDO — materials officer; Danny Robinson, VK6TZ — beacon officer; David Laws, VK6DS — Librarian and Wireless Hill resident.

Wireless Hill Museum committee — Wally Howse, VK6KZ; Jack Sullivan, VK6ZFO; Tom Berg, VK6ZAF.

A comprehensive tentative program and timetable have been drawn up for the Wireless Hill Museum project. Two dates have been fixed, opening in August-September 1979 and budgetary submission for 1978-79 for the Melville City Council in March 1978.

WESTLAKES RADIO CLUB: The WRC conducts a club net each Friday night from 6.00 pm to 7.30 pm around 3565kHz. This net allows members from all around Australia to meet each other. The club equipment is a TS520S under the guiding hand of Dave McKie, VK2BWK and second operator Eric Brockbank, VK2ZOP. An 80 metre dipole antenna 18 metres high is used and an average of around 20 join the net. The club call sign is VK2ATZ.

Another net is conducted each Wednesday evening at 8.00 pm on 28.55MHz by Michael, VK2AMJ, using the call VK2ATZ/P.

A broadcast on each Monday evening at 6.30 pm on 3565kHz is intended as an information net. If you have any questions about the club or any activity, join in and enquire.

The popular "Manual of Questions and Answers for the Novice Licence" has been expanded and is now in its fifth edition.

It is published by the WRC as an educational service to novice licence candidates and course instructors. There are now more than 3000 copies in circulation in Australia, and it is available from the Westlakes Radio Club, PO Box 1, Teralba, NSW 2284. The cost is \$3.50 post paid. Ten or more cost \$3.00 a copy, postage paid.

IONOSPHERIC PREDICTIONS FOR NOVEMBER

Reproduced below are radio propagation graphs based on information supplied by the Ionospheric Prediction Service Division of the Department of Science. The graphs are based on the limits set by the MUF (Maximum Usable Frequency) and the ALF (Absorption Limiting Frequency). Black bonds indicate periods when circuit is open.

7MHz EAST		01 02 03 04 05 06 07 08 09 10 11 12 13 14 15 16 17 18 19 20 21 22 23																							
EAST AUST TO BARBADOS (SR)																									
JOHANNESBURG																									
MUMURDO SOUND																									
NEW DELHI																									
NEW YORK																									
RIO DE JANEIRO																									
TOKYO																									
VANCOUVER																									
WELLINGTON																									
WEST AFRICA																									
WEST EUROPE (SR)																									
WEST EUROPE (IR)																									
ADELAIDE TO SYDNEY																									
BRISBANE TO MELBOURNE																									
PERTH																									
SYDNEY																									
DARWIN TO SYDNEY																									
MELBOURNE TO PERTH																									
SYDNEY																									
14MHz GMT		15 16 17 18 19 20 21 22 23 24 01 02 03 04 05 06 07 08 09 10 11 12 13																							
EAST AUST TO BARBADOS (SR)																									
JOHANNESBURG																									
MUMURDO SOUND																									
NEW DELHI																									
NEW YORK																									
RIO DE JANEIRO																									
TOKYO																									
VANCOUVER																									
WELLINGTON																									
WEST AFRICA																									
WEST EUROPE (SR)																									
WEST EUROPE (IR)																									
ADELAIDE TO SYDNEY																									
BRISBANE TO MELBOURNE																									
PERTH																									
SYDNEY																									
DARWIN TO SYDNEY																									
MELBOURNE TO PERTH																									
SYDNEY																									
21MHz EAST		01 02 03 04 05 06 07 08 09 10 11 12 13 14 15 16 17 18 19 20 21 22 23																							
EAST AUST TO BARBADOS (SR)																									
JOHANNESBURG																									
MUMURDO SOUND																									
NEW DELHI																									
NEW YORK																									
RIO DE JANEIRO																									
TOKYO																									
VANCOUVER																									
WELLINGTON																									
WEST AFRICA																									
WEST EUROPE (SR)																									
WEST EUROPE (IR)																									
ADELAIDE TO SYDNEY																									
BRISBANE TO MELBOURNE																									
PERTH																									
SYDNEY																									
DARWIN TO SYDNEY																									
MELBOURNE TO PERTH																									
SYDNEY																									

YRS TRIAL EXAMINATION

Trial examinations conducted by the WIA Youth Radio Scheme have greatly assisted candidates for the P&T Department's novice licence. The following report received from John Kolm, VK3YJK, YRS examiner in Victoria, may assist candidates in avoiding pitfalls. This is an abbreviated report of statistical information compiled with the aid of a computer. The full report has been published in the YRS magazine "Zero Beat".

"The April 1977 trial novice exam was the first to be conducted by the YRS in Victoria. It has been a great success and will be repeated bi-annually from now; the next trial exam is scheduled for April 1978.

"There were 61 candidates. The pass rates were

as follows —

"Theory section: 46%; regulations section: 48%; telegraphy section: 19%.

"Only 15% of candidates passed in all sections. This low pass rate was largely caused by the high failure rate in telegraphy receiving.

"Theory scores ranged between 28 and 96, with a mean value of 64.9. Facility values (percentage correct on each item) ranged between 15% and 92%. The weakest area was the section on AC circuits, especially reactance and resonance which were not well understood.

"Regulations scores ranged between 20 and 97, with a mean value of 66.2. Facility values ranged between 30% and 98%, the weakest area was the section on the "Q" code. This should be remedied, since the "Q" code questions are heavily weighted.

Realtime QUARTZ

1/100 of a second accuracy chronograph-LCD Watches

THE PRECISE MODERN DIGITAL TIMEPIECE WITH A TOTAL OF 13 FUNCTIONS PLUS NIGHT LIGHT. IDEALLY SUITED FOR USE IN SPORTING, SCIENCE, INDUSTRY, OR WHEREVER ACCURACY AND ELEGANCE ARE DESIRED.

Chan Merchandising Co. Pty Ltd

SYDNEY:
111 RESERVOIR STREET,
SURRY HILLS 2010
TEL. (02) 211 4660

NEWCASTLE:
906 CASSON AVENUE,
MT. HUTTON, NSW 2290
TEL. (049) 48 9676 (Sat. & Sun.)

featuring:
*hr/min/sec/month/
date/day
*30 seconds correction
*start, stop, reset, lap
time, instant time
freeze, memory recall
*back light
*four-year calendar
*2 battery system
*module thickness: 5mm
*one year guarantee

\$ **99** Free
P & P



AN OPEN LETTER FROM DICK SMITH ...


WIA CALL BOOKS

NOW AVAILABLE

Cat B 2259 \$2.85

YAESU FRG-7

\$328.00

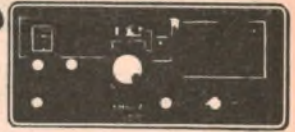

The ultimate in a general coverage receiver — continuous tuning from 550kHz to 30MHz, fully synthesised for ultra stable reception in AM, SSB or CW modes. Sensitivity is better than 0.25µV (SSB) for 10dB S+N/N. Uses the famous 'Wadley Loop' principle; operates from 240V mains or 12V battery. 52 ohm antenna. **A really incredible receiver! Cat D-2850.**

KENWOOD QUALITY TS600A



\$650 value

MAGNIFICENT KENWOOD TS600A ALL-MODE 6m TRANSCEIVER
This transceiver is all you could want for the 6 metre band. It covers the band in 20 channels (5 crystals), and covers it in style: SSB, FM, CW, AM! You can't be left out of a QSO because your gear hasn't got that mode! Complete unit with built-in power supply, speaker plus microphone. **Cat D-3106 \$650.00**

Amateur band linear amps



\$299

Cat D-2544

(Left) This one covers 40, 20 & 10 metres, 200W input from just 3W of drive! Also has RF preamp: switching is RF actuated. 240V AC operated. **Cat D-2544 \$299.00**
(Also available) 10 metre linear, 12V DC, 50W from 3W drive (also works on 11m) **Cat D-2545 \$189.00**

Dear fellow amateurs, Do you ever get the feeling that amateurs are getting a raw deal? It seems to me that every man and his dog are suddenly becoming amateur gear experts. There are countless back-yard operators offering amateur gear at 'bargain' prices. On face value, it looks like a really good deal. But look a bit closer and you find it's not quite all it could be. Half the time the gear is sold without any warranty — and if there is a warranty, the seller has neither the expertise nor equipment to effect it. My service department is one of the largest around. I'm proud to say that when a product is bought from one of my stores or dealers, the full resources of my organisation are behind that sale. So next time you see a bargain and are tempted to buy, stop and think. Can the seller offer you as much as I can? Over to you ... '73's.

Dick Smith
VK2ZJP

DICK SMITH ELECTRONICS GROUP

SYDNEY
125 York St.
CITY
Ph 29-1126

SYDNEY
361 Hume Hwy.
BANKSTOWN
Ph 709-6600

SYDNEY
162 Pacific Hwy.
GORE HILL
Ph 439-5311

SYDNEY
30 Grose St.
PARRAMATTA
Ph 683-1133

MELBOURNE
656 Bridge Rd.
RICHMOND
Ph 42-1614

MELBOURNE
399 Lonsdale St.
CITY
Ph 67-9834

BRISBANE
166 Logan Rd.
BURANDA.
Ph 391-6233

MAIL ORDERS
PO Box 747,
CROWS NEST 2065.
Ph 439-5311.



Post & Pack extra!

ELECTROCRAFT PTY. LTD.

Distributors of Belling Lee, Channel Master, Ecrafft, Hills, HI-Q, Lab Gear, Kingray, Matchmaster Largest Television range of aerial equipment in Sydney

106A Hampden Rd.
Artarmon, 2064
Phone 411-2989

TELEVISION AERIALS, DISTRIBUTION AMPLIFIERS, EQUIPMENT AND ACCESSORIES WHOLESALE, TRADE AND RETAIL SUPPLIED.

NEW FROM ECRAFT A range of Medium & High gain R.F. DISTRIBUTION Amplifiers, suitable for all TV & FM Radio transmissions within the VHF & UHF Bands 1 to V.

APPLICATION Suitable for small home unit, showroom or household type installations. D16 & D25 amplifiers have good signal to noise ratio. As such this makes them suitable as a booster in semi-fringe or fringe areas.

1.75 D16 16 dB gain \$45.90 1.75 D25 25 dB gain \$53.55

All type coaxial cables in stock from 30c per yd 50 ohm—75 ohm

HILLS	ANTENNAS	CH's	\$
CA16	High gain phased array	Multi	44.36
215/2710	8 EL	Multi	24.42
2010/2710	Airways	Multi	56.26
E.F.C. 1	75 ohm for colour	Multi	31.43
E.F.C. 2	75 ohm for colour	Multi	41.70
E.F.C. 3/24	75 ohm for colour	Multi	60.64
E.F.C. 4/24	75 ohm for colour	Multi	76.30
207/45A		4 & 5A	31.47

CHANNEL MASTER

3110	2 EL Coloray	12 to 11	27.96
3111	6 EL Super Coloray	Multi	41.98
315	2 EL City VEE	0 to 11	15.68
3615A	9 EL Crossfire	Multi	43.64
3614A	13 EL Crossfire	Multi	54.69
3613A	17 EL Crossfire	Multi	68.17
3612A	21 EL Crossfire	Multi	78.54
3610A	24 EL Crossfire	Multi	99.84
3617A	28 EL Crossfire	Multi	125.73

HILLS FM ANTENNAS

FM1	300 ohm		9.39
FM3	75 ohm		18.27

CHANNEL MASTER FM ANTENNAS

700 FM 8 EL	300 ohm		19.68
200 FM 2 EL	300 ohm		8.31

MATCHMASTER FM ANTENNAS

FMG	300 ohm		11.95
FMG/2	300 ohm		18.30
FMG/6	Fringe area 300 ohm		40.93

COBRA 132 \$350.00 AM/SSB Delta Tune P.A. Extension Speaker Facility Illuminated Channel Indicator and Metre. R.F. MIC Gain Control. N.B. Switch. Auto Noise Limiter. **Sensitivity:** AM 0.5µV or better. SSB 0.25µV or better. **Selectivity:** 6dB at 4kHz. 50dB at 20kHz. 6dB at 2 kHz. 60dB at 5kHz. **Audio Output:** 3.5 watts typical



THE COBRA 26 \$120.00

The Cobra 26 is called "The Performance Radio" because professional drivers prefer the 26's top rated features and performance. Just check this list. Switchable noise limiting (ANL), RF gain control, Delta Tune, illuminated Power/S meter, adjustable squelch, PA output, detachable dynamic mike and much more.

The Cobra 26 operates at maximum legal power and critical sensitivities. What it really means to you is more enjoyable use of your CB operation. See for yourself why the Cobra 26 is the standard of comparison in the Citizens Band two-way radio industry. *No matter what the conditions, the Cobra 26 punches through loud and clear.*

A big voice in a small package. The Cobra 19M \$110.00.

If you've ever heard a Cobra 26, you'll know it's hard to believe all that talk-power is legal. Cobra found the way to make their radios really talk and still obey the rules. Now you can talk just as loud and far with a smaller package. Cobra 19M is thin and narrow enough to mount conveniently in any car, even the latest subcompacts. And the 19M has other features you'd expect from a Cobra, such as a plug-in dynamic mike, external speaker jack, and now, even an illuminated RF/signals metre. The Cobra 19M has the same receiver sensitivity and selectivity as its big brother. Cobra 26. It has an efficient automatic noise limiter too, you'll hear clearly in the heart of heavy traffic. Dimensions 1½" H x 5¼" W x 8" D. Power Output: Factory adjusted to 4 watts legal maximum. Modulation 100%. Sensitivity: Less than 1.0µV for 10dB (S+N)/N. Selectivity dB—6dB at 4kHz. 40dB at 20kHz. Image Rejection—30dB. IF Rejection—80dB. Audio Output: 2.5 watts into 8 ohms.

CB AERIALS

ASIC 5ft Fibreglass vertical helical whip aerial with base (Guard Mount) complete with 12ft cable & plug \$26.73

5ft Helical home base aerial for mast mounting \$33

CB2600 Gutter Clamp aerial complete with lead & plug \$20.70.

ALL TYPES OF

HARDWARE IN STOCK Wall Brackets, Chimney Mounts, J Brackets, Guy Rings & Guy Wire, Masts from 8ft to 50ft ETC.

Shortwave Scene

by Arthur Cushen, MBE



Radio amateurs and shortwave listeners will be looking forward to the meeting of the World Administrative Radio Conference in Geneva in 1979 when there is every possibility of the bands being extended for these two hobbies.

Due to heavy congestion in the shortwave broadcasting bands, shortwave broadcasters hope for band extensions, and so do the maritime mobile services, as well as the radio amateurs.

According to the World Radio and Television Newsletter their hopes are high due to the transfer of traffic from the fixed services in the high frequency bands towards satellite repeaters. As fixed services are allotted some 48 per cent of the total HF spectrum, it seems well possible for them to give up some frequency space in favour of the other services.

Shortwave broadcasters hope for a doubling of frequency space, achieved by doubling each shortwave broadcasting band, except the 25MHz band. Many shortwave broadcasters are of the opinion that the 41 and 60 metre band should be allotted on a worldwide basis.

Since 1959, the year of the last World Administrative Radio Conference, the growth of international shortwave broadcasting has been steady, and many new nations either have a shortwave service or are in the process of building one. All these new services deserve a place in the bands, and to achieve this the experts have calculated that the frequency space allocated to shortwave broadcasting needs to grow from a total of 2350kHz to about 4700kHz.

SYNCHRONISED TRANSMISSIONS

Radio New Zealand has two synchronised frequencies. The Whangarei station 1YX operates on 830kHz and carries the National program and recently the Kaitia station, formerly on 1010kHz, was also moved to 830kHz. Also 1ZN Whangarei moved from 970kHz and 1ZK Kaitia from 1440kHz so that both are now operating on 1010kHz.

Synchronised transmissions were introduced by 1XX Radio Whakatane on 1240kHz.

In Australia at present only two stations are synchronised on medium wave. These are 4QO Eidsvoll and 4QB Maryborough on 910kHz which carry the ABC program. The New Zealand experiment is new and results in the release of two further frequencies in the congested medium wave band, with 1050 and 1440kHz now being free. There are plans however to move 2ZP New Plymouth from 1370 to 1050kHz, while Radio Auckland has moved to 1330kHz from 1590kHz.

KOREAN EXPANSION

Pyongyang Radio in North Korea has expanded its broadcast and some new frequencies are now being used. One of the best received is 11780kHz which has French 0800-0950GMT, Korean 1000-1100GMT and Chinese 1100-1300GMT. There are many broadcasts in English. The transmissions best heard in this area are 0600-0750GMT on 9420 and 11531kHz; 0800-0950 on 9420 and 11531kHz; and 2000-2150 on 3560, 6575 and 9420kHz.

Notes from readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill, NZ. All times are GMT; add nine hours for West Aust. summer time, 11 hours for East Aust. summer time and 13 hours for NZ daylight time.

RED CROSS TESTS

The final test from the Red Cross Radio at Geneva using the facilities of the Swiss Broadcasting Corporation is scheduled for November 21, 23 and 25 and will be broadcast on 7210kHz. The times of broadcast are 0600-0700 1130-1230, 1700-1800, 2200-2300GMT.

On Monday the broadcast will be in English, Wednesday in French and German, and Friday in Spanish and Arabic. Reports are appreciated on these tests, and should be addressed to the Radio Division, International Committee of the Red Cross, Geneva, Switzerland.

NEW LAOS SCHEDULE

A verification letter in English and a complete schedule have been received after 20 months from National Radio of Laos, Vientiane. According to the covering letter the old Philips 25kW transmitters have been replaced by two transmitters of 10kW from a Chinese manufacturer. One is used for shortwave transmissions on 7145kHz and the other is for standby operation. The Director-General of Radio Laos, Mr Chaleun Vongsam-Ang, is anxious to receive reception reports.

The schedule of the External Service which operates on 1030 and 7145kHz is 2300-0130, 0400-0630 and 1130-1430GMT, with English news bulletins and program at 0100, 0600 and 1330GMT.

The Internal Service is broadcast on 640 and 6130kHz, 2230-0200, 0400-0700, and 0900-1530GMT with all local programming.

RADIO ETHIOPIA

Radio Ethiopia at Addis Ababa has been heard on 9610kHz opening at 0400GMT. The station has an interval signal followed by a march, then time signals, and an announcement introducing the relay of the domestic program.

The Voice of Revolutionary Ethiopia, which uses the transmitters of the former ETLF, has been heard on a new frequency 6010kHz, as well as 7180kHz. The broadcasts in English are now 1500-1600GMT. The transmission opens at 1200GMT and during the hour long broadcast in English, news headlines are featured at 1500GMT and a full news bulletin at 1530GMT. The frequency of 6010kHz replaces the old channel of 6015kHz.

RECENT VERIFICATIONS

BOLIVIA: Radio Tropicico, which operates on 4775kHz, uses 1500W and closes at 0400GMT, has confirmed our reception with an attractive postcard. The call sign CP120 is assigned to this frequency. The station address is Radio Tropicico, Trinidad, Beni, Bolivia. The verification card was signed by Carlos Avila Alberdi.

FRENCH GUYANA: Radio Cayenne has verified our reception on 4972kHz with a card from Radio France Region 3. The card lists the shortwave frequencies as 3385 and 6170kHz (both 4kW), and 4972kHz with 1kW. The station was heard opening at 0930GMT on 4972kHz. The address is F.R.3 — B.P. 336, 97305 Cayenne, French Guyana.

NEW ZEALAND SCHEDULE

The Shortwave Service of Radio New Zealand is operating at new times due to the fact that daylight time was introduced into New Zealand on October 29. This means that all programs are heard an hour earlier by overseas listeners. New Zealand does not adjust its broadcasts to remain with GMT, and as the programs are a relay of the internal service they are broadcast at this earlier hour. This schedule is effective up to March 5, 1978.

Broadcasts to the Pacific are: 1800-2215GMT, 11960kHz; 2230-0250, 17710; 0300-0530, 11705; 0545-1030, 11780; 1800-0715, 15130; and to Australia 0730-1030, 11780kHz.

The DX World program will now be heard at 0915GMT on the first Sunday of each month and the Mailbox session at the same time on the third Sunday of each month during the period of daylight time in New Zealand.

LISTENING BRIEFS EUROPE

BULGARIA: Radio Sofia is now using two frequencies in the 31 metre band for its English transmission to the United Kingdom 2130-2200GMT. The new frequency of 9530kHz provides the best signal, but reception on 9745kHz is also fair, though both frequencies suffer from interference.

ROMANIA: Radio Bucharest is using 5990kHz for its service to North America in English at 0400GMT. The reception in this area has been fair, though signals are spoiled at 0420GMT by Rome Radio which opens on the same channel. This transmission will be best on the higher frequencies during our summer months.

AFRICA

CAMEROON: Radio Yaounde was recently observed on 4925kHz around 1900GMT with announcements in French, but this frequency has been replaced by 4850kHz which is heard at the same time. According to Peter Bunn in Melbourne, reporting in Australian DXers Calling, the station was heard from 2000-2200GMT. This new channel of 4850kHz is also observed as parallel to 4972kHz, the latter channel continuing transmission until the station closes at 2300GMT.

AMERICAS

BRAZIL: Radio Nacional, Brazilia, has returned to the shortwave bands and is operating on 11780kHz, 1900-2400GMT. The transmitter which formerly carried the broadcast to Europe on this frequency with English at 2100GMT was suspended from this operation in order to carry a program into the Amazon area, which was receiving strong signals from overseas stations, but a poor service from inside Brazil.

DOMINICAN REPUBLIC: Radio Clarin at Santo Domingo has introduced a second broadcast in English, and this is heard at 2130GMT. This transmission is for Europe and broadcast on 11700kHz. According to Sweden DXers a service to the United States is still transmitted at 2330GMT and the station plans to issue a verification card.

ASIA

PHILIPPINES: Radio Veritas has been heard on 11955kHz with an English program 1400-1500GMT. The station plays popular music on Saturday at 1412GMT and has a news bulletin at 1430GMT. The station address is Radio Veritas Overseas, PO Box 939, Manila, Philippines.

OCEANIA

COOK ISLANDS: Radio Raratonga has been observed on 9695kHz closing at 0834GMT, according to John Mainland of Wellington, NZ. There is some interference on the frequency from the French radio, which is also using the frequency at this time. Recently the station moved from 3265 to 5045kHz. Douglas Doull of Auckland, NZ, advises that they have a new address, PO Box 126, Avarua, Raratonga.

AUSTRALIA: Radio Australia has altered its program format on 5995kHz and now broadcasts to the Solomon Islands, New Hebrides and New Caledonia from 0700-0845GMT. Mark Shiell, Renown Park, SA, advises that at 0855GMT the station resumes its English transmission following the special service to the South Pacific.

ZOOM FOCUSING MICROSCOPES 900X

\$23.95
Battery
and
Mirror
illuminated
Zoom
1200X
Similar To Above
\$35.00

A. \$1.70. B. \$2.25. C. \$2.40. D. \$2.65

P.M.G. TYPE TELEPHONES

Standard desk type with magneto bell calling device. Range 30 miles. Uses standard batteries at each phone. Any number can be connected together on single line.

\$35.00
(2 TELEPHONE SETS)

\$2 Cartage to Rail Freight payable at nearest attended Railway Station

FOUR CHANNEL VHF TRANSCEIVER

125 to 140 M/hz 28 volt DC operated AM single crystal locks both TX and RX on same channel complete with generator.

\$33.00

EX ABC MAGNETIC RECORDING TAPES 1/4" PROFESSIONAL QUALITY

5" x 600' \$1.50
7" x 1200' \$2.75
10 1/2" x 2400' \$5.95

P & P A \$1.10. B \$2.00. C \$2.25. D \$2.25

MINI-TOGGLE SWITCHES MIYAMA

SPST 3A 75c
SPDT 3A 95c
DPDT 3A \$1.25
SPDT Centre-Off 10A \$1.25
DPDT Centre-Off 10A \$1.65
Please add postage

No. 62 TRANSCEIVER

With headphones accessories etc
\$60

TELEPHONE WIRE

1 mile twin (2 miles) genuine ex-Army Don B perfect condition \$35 per drum \$2.00 cartage to rail freight payable at destination.

RCA 77DX MICROPHONES

PROFESSIONAL QUALITY \$75
P & P A. \$1.80 B. \$3.50 C. \$4.55
D. \$4.55

MORSE KEY | MORSE KEY BUZZERS
\$1.75 | \$4.25
Post 40c | Post 60c

KAISE MULTIMETERS

A compact and handy tester for workshop or lab where quick circuit checks are required

DC Volts 2.5 to 1,000V (20,000 OHMS per volt) AC Volts 10 to 1,000V (10,000 OHMS per volt) DC Current 50 UA 25 MA 250 MA Resistance 40 K OHM 4 MEG OHM Decibels minus 20 DB plus 62 DB complete with instructions only \$23.95 Ea. P.O. \$1.05. Multimeter similar to above 30,000 OHMS per volt \$29.50 P.P. \$1.05

Only \$17.25 ea Post \$1.05

BENDIX PIONEER

Drift Sight
Type B3
\$250.00

4 DIGIT RELAY COUNTERS

50 volt DC, suit slot car Lap counters, etc.
\$1.28 each P & P 60c.

NIBBLING TOOL

Cuts sheet metal like a punch and die. Trims, notches and cuts to any size or shape over 7.16inch.

ONLY \$12.50
Post \$1.10

NIFE CELLS

1.2 Volt, fully charged. 4in x 3in x 1in 4 AH
\$1.50 each P & P 80c

5" CRO TUBE 5 BPI \$6.50 each

Post A \$1.40. B. \$2.25. C \$2.70. D \$3.45

HANDY SIGNAL INJECTOR

Produces an Audio Signal in rich harmonics. Ideal for Sig Tracing in A.F., I.F., and R.F. circuits. Powered by 4 Penlight Batteries with On Off Switch and indicator lamp. Size 1 1/2" Diam 5" Long Only
\$8.95 Post \$1.10

POSTAGE KEY:

A: NSW
B: Vic Old SA
C: NT, Tas.
D: WA

VALVES

BRAND NEW	6BM8	\$1.80	
	6GV8	\$1.50	
65N7GT	95c	CV850	\$1.50
5U4G	95c	1H6G	75c
EF50	75c	832	\$5.00
5Y3	\$2.25	6X4	\$1.80
2x7	75c	VR65	75c
	P & P 40c		

ARTILLERY DIAL SIGHTS MK2

Can also be adapted as a Dumpy Level or as base for a telescope has full 360° 5/16" diam. gunmetal rotating circle. Adjustable elevation and depression. Has top grade 3/4" diam. object lens. F.L. 10" with cross hairs. eyepiece 1/2" right angle prism.—height 10"—weight 3 1/2 kgs. With leather carrying case. Original cost \$300
Our Special only \$27.50
P & P A. \$1.95. B. \$4.25. C. \$5.90. D. \$5.90

ZOOM SPOTTING SCOPES

30x30
LENGTH 12 1/2". HEIGHT
10"
WEIGHT 1 1/4 lb.
\$27.50

60x60
Length: 22in
Height: 18in
Weight: 2kg
\$59.50



High grade coated lenses. Ideal for pistol and rifle ranges or general viewing. Zooms in from very low to high powers. Complete with tripods.

POST: A \$1.70. B \$2.25. C \$2.40. D \$2.65.

TELESCOPES

25 x 30 \$7.95
P & P A \$1.70 B \$2.25
C \$2.40 D \$2.65

SPY TELESCOPES

8 x 17 mag size of a rifle cartridge extends to 8" Only \$5.95 each post 60c

BINOCULARS

PRISMATIC Coated Lenses Brand new. Complete with case.

8 x 30	\$32.50	P&P	
7 x 50	\$43.95	A	\$1.65
10 x 50	\$44.95	B	\$2.75
12 x 50	\$46.00	C	\$3.20
20 x 50	\$47.50	D	\$3.20

SMALL CLIP-ON POCKET TELESCOPE

15X \$5.20 Post 60c

RECEIVER No. 210

2.16 M/cs \$65
Transmitter No. 11 suits 210 \$35
24 volt Power supply to suit above \$15
Or complete station with Headphones, Mic. Morse Key. Antenna \$110

SOLENOIDS

Plunger Type 24V 300MA. Suit electric camera control. miniature trains radio, etc.

\$2.50 P & P 20c
200 MA 24 volt. 1/2in push movement.
\$2.50 P & P 20c.

SELSYN MOTORS MAGSLIP

RECEIVERS 2" MK2 \$5.50

TRANSMITTER 3" MK2 \$15.00

Post Packing A. \$1.75 B. \$2.75 C. \$2.75 D. \$3.65

3000 TYPE RELAYS

P.M.G. 200ohms — 1'500ohm
Coils \$2.50 each P & P 60c

P.M.G. TYPE KEY SWITCHES.

75c P & P 20c

Coscor Double Beam Oscilloscope 1035.
Tested. \$150.00

AIRCRAFT INSTRUMENTS

Directional Gyros
AN5735-1 Air Operated
Dimensions 6inx5inx5in
Weight 2kgs
\$35

Sperry Artificial Horizon.
AN5736-1 Air Operated
Dimensions: Length 9in;
Diam 4 1/2in.
\$45

Slip and Turn Indicators
Electric. Type Mk. 12.
24Vdc.

Dimensions: Length 6 1/2in.
Diam 3 1/4in.
Weight: 1kg
\$17.50.
P & P A \$1.60. B \$2.50. C \$2.75. D \$2.75.

TRANSCEIVERS Ex Army

No C42 set 36 to 60 MHz with 24V power supply, headphone, mic, leads etc **\$65.00**

No C45 set 23 to 38 MHz with headphones, mic. 24V power supply etc **\$95.00**

\$1.00 cartage to rail, freight payable at nearest railway station

EX-ARMY TWO-WAY FM RADIOS



1 2 WATTS OUTPUT SUPERHET
PRC9 AND 9A 27 to 39 M/HZ
PRC10 AND 10A 38 to 55 M/HZ
WITH HANDSET ANTENNA \$25 EA
Battery \$3.50 extra. Harness \$4.50 extra
\$2 Cartage to Rail. Freight payable at nearest attended Railway Station.

16MM SOUND PROJECTORS IN GOOD WORKING ORDER

240 volts operated. Complete with Speaker and Amplifier

CINEVOX \$150.00
BELL & HOWELL \$250.00
SIEMENS \$375.00

\$1 Cartage to Rail. Freight payable at nearest attended Railway Station.

CB RADIOS

PMG Approved. Famous Pony Brand on 27 Meg.
7 transistor model \$55 per set of two (hand held)
11 transistor model 1 watt (hand held) \$72 ea
5 watt 6 channel \$99 ea
Post A \$1.65 B \$2.75 C \$3.20 D \$3.20.

"KAISE"

Trans-Match Ham Tester SWR, RF Power, Modulation Percentage, Relative Field Strength. \$45.00 P & P A \$1.65. B \$2.75. C \$3.20. D \$3.20

"KAISE"

SK-100 Multimeter 100,000 ohms per volt, 12 Amps. AC or DC. \$52.
P & P A \$1.65. B \$2.75. C \$3.20. D \$3.20

Deitch Bros.

70 OXFORD STREET, SYDNEY 2010

SORRY NO C O D

INFORMATION CENTRE

200MHz DFM: I have constructed the 200MHz Digital Frequency Meter described in March 1977 and managed to get the unit operational with relative ease. However, I have struck some problems which I hope you can solve for me.

What loading effect, if any, would this unit have on RF and oscillator circuits when used on the highest range? The input impedance is quoted as 75 ohms shunted with 50pF. If there is a loading effect can it be predicted and allowed for?

No information on the construction of suitable probes was discussed. I require assistance here. Can the buffered output of the crystal be used to align the DFM? Is there any way that this unit can be interfaced with a voltage-to-frequency converter and thus be used as a digital voltmeter?

I have had problems with the LED readouts, having three failures (faulty segments) in as many weeks. This could be only an isolated case but, I feel, worthy of your notice.

Despite all precautions taken, I am still getting multiplex hash — a sort of tone interrupted and changing in pitch every two seconds. This is only evident when making measurements in the front end of an FM receiving circuit. (R.D., Corio, Vic.)

● The loading effect of any electronic measuring instrument depends on the ratio of its input impedance to that of the circuit or device being measured. For minimum loading, the impedance of the measuring instrument should always be higher than that of the circuit being measured. In your case, the loading effect of the DFM on VHF oscillator and "front-end" circuits could be severe, to the point where they malfunction.

Most work with DFMs does not require special probes so we have not designed any. The output of the crystal cannot be used to calibrate the DFM — another reference must be used. A voltage-to-frequency converter plus a DFM can be regarded as the basis of a

Notes & Errata

ALL WAVE TWO (Yearbook 1976/77, File No. 4/TR2/5): The lug connecting the 100uF, 0.1uF and 0.22uF capacitors should be connected to the adjacent earth terminal.

CORRECTION: The Nessel Audio advertisement published on page 34 of the October issue, the price of the SL1502 speaker should have been shown as \$125.

DVM, but we do not regard the idea as a practical proposition for this particular instrument.

Your problem of multiplex hash breaking into an FM front-end is to be expected. These are very sensitive circuits, requiring only a few microvolts of signal for normal operation. You would have to go to very great lengths to reduce the hash below this level.

CDI: I would appreciate some advice concerning your CDI system published in July 1975. A friend of mine and I both have this CDI in our cars. Last summer we both had trouble with them. The unit appears to switch itself off in hot weather at high engine revs (in a four cylinder car) of 4000 rpm or more — especially, although not necessarily, under much load. It will not cut out if the engine is simply revved up in neutral. The ambient temperature needs to be around 37 to 39 degrees Celsius before this happens.

When it cuts out, it does so only for a second or so and then switches back on, then off again and so on. It almost certainly does not appear to be an EHT breakdown (coil, etc.). Both units are mounted in the coolest spot possible under the bonnet. Both units are supplied with the full 12 volts. As summer is coming around again, we would appreciate an answer on this one. (B.R., Glen Osmond, SA.)

● First, we must point out that in the case of an EHT breakdown, it is often not possible to give a clear diagnosis on the basis of engine behaviour when not under load. The fact that the engine is revving freely can mask misfiring. However, more often than not, the engine does not misbehave when not under load.

If you are unable to complete an "Electronics Australia" project because you missed out on your regular issue, we can usually provide emergency assistance on the following basis:

PHOTOSTAT COPIES: \$2 per project, or \$2 per part where a project spreads over multiple issues. Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries.

METALWORK DYELINES: Available for most projects at \$2 each, showing dimensions, holes, cutouts, etc., but no wiring details.

PRINTED BOARD PATTERNS: Dyeline transparencies, actual size but of limited contrast: \$2. Specify positive or negative. We do not sell PC boards.

REPLIES BY POST: Limited to advice concerning projects published within the past two years. Charge \$2. We cannot provide lengthy answers, undertake special research or discuss design changes.

When the engine is under load the cylinder pressures are much higher and therefore the ignition voltage of the spark plugs is considerably higher. Combined with the fact that you are running the CDI from the full 12 volts (which can be as much as 15 volts with the engine at high revs) there is a greatly increased likelihood of EHT breakdown. Still, you may be right. It might not be an EHT breakdown.

Fortunately, the CDI has no way of knowing whether the engine is under load or not. So if it is going to misbehave it is just as likely to do so when the engine is not under load. This means that the CDI can be checked with the engine revving in neutral. A caution here though: Revving an engine to high speed while in neutral runs the risk of putting a piston through the block.

Having said all that, the best way to diagnose a problem in the CDI is to monitor the oscillation at the collector of one of the transistors with the aid of an oscilloscope. Failing this, use a multimeter to monitor the DC output from the inverter — this may or may not show the fault. If the CDI does have a temperature sensitive fault, it is likely to be caused by the SCR or one of the transistors.

AMPLIFIER HUM: I would like to know why my Playmaster 40/40 hums when the leads from the turntable are applied to the phono inputs $\frac{1}{2}$. Is it possible to add high and low filters, and a loudness control to the amplifier? (A.M., Mentone, Vic.)

● A likely explanation is that there is an "earth loop" created when you connect the turntable. This could be because the input cable shields are connected to the earth wire of the turntable mains cord. If you break this connection, a cure should result.

Some people have also found hum due to the fact that the headphone socket was not isolated from chassis, as recommended in the January 1977 issue on the Playmaster Twin 40W.

BACK NUMBERS: Available only until our stocks are exhausted. Within three months of publication, face value. Four months and older, if available, \$2. Post and packing 60c per issue extra.

OTHER QUERIES: Technical queries outside the scope of "Replies by Post" may be submitted without fee, for reply in the magazine, at the discretion of the Editor.

COMMERCIAL SURPLUS EQUIPMENT: No information can be supplied.

COMPONENTS: We do not deal in electronic components. Prices, specifications, etc., should be sought from advertisers or agents.

REMITTANCES: Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

ADDRESS: All requests to the Assistant Editor, "Electronics Australia", Box 163, Beaconsfield, 2014.

LANTHUR ELECTRONICS

69 Buchanan Avenue, North Balwyn, (P.O. Box 162), Vic. 3104. Ph. 859 4061.

SPEED CONTROLLER KITS

For all brush type AC/DC 240 volt motors. Regulates down to stop with no loss of torque. Especially hand tools, lathes, potters wheels etc.
Five amp (1200 watt) size **\$10.25**
Ten amp (2400 watt) size **\$10.95**
Price includes postage.

LAMP DIMMER KITS

Will control incandescent lamps from full to out.
Five amp (1200 watt) size **\$7.50**
Ten amp (2400 watt) size **\$8.50**
Available with rotary or slider type control. Price inc postage.

PLASTIC CABINET

Suitable for above speed controller or lamp dimmer **\$1.75**

ALUMINIUM CABINET

As above **\$2.95**

BATTERY CHARGER KITS

For charging 12 volt wet batteries at 2 amps. Contains transformer, bridge rectifier, ballast resistor and circuit **\$10.25**
Plus postage \$2 (Surplus refunded)
Aluminium cabinet to suit **\$3.95**

BATTERY SAVER KITS

Will supply DC voltages from 6 to 15. Contains tapped transformer, bridge rectifier, filter cap and circuit.
One amp size **\$8.95**
Two amp size **\$16.95**
Plus postage \$2.50 (Surplus refunded)
Aluminium cabinet to suit. One amp **\$3.95**
Aluminium cabinet to suit. Two amp **\$4.75**

SPECIAL

2N3055 TO3 Case, ITT brand 2 for \$2.00, 5 for \$4.50.

INSTRUMENT BOXES

Plastic with aluminium lid.
Approx. size 125mm x 65mm x 40mm **\$1.75**
Approx. size 155mm x 90mm x 50mm **\$2.00**

POTENTIOMETERS

Tab mount 10k linear with 20mm plastic shaft
5 for **\$1.50**
10 for **\$2.50**

SPEAKERS

2 1/4" 8ohm 2 for **\$3.50**

TRIACS

15 amp, 400 piv, with matching diac. Per pair **\$3.25**

ELECTROLYTIC CONDENSERS

Pigtail 1000/25 and 470/63 2 for **\$1.75**
Above prices include postage.

THE VALVELESS WORLD

has been postponed indefinitely. Until then we will continue to serve you with the most extensive range of electron tubes. If you are looking for an electron tube or a semiconductor you will find it at:

Adrian Michell's TELEVISION REPLACEMENTS

Rear 139 Union Road, Surrey Hills, Vic. 3127. Phone 89-1019.

Marketplace

FOR SALE

TELEPRINTING SPECIALS: Mod. 15 Mint cond. \$90. Very good \$70. Good \$50. Mod. 15 Keyboard Perforator \$40. Mod. 14 T.D. \$30. FRXD4 Reperf. Trans. Dist. \$30. Paper Rolls 12 for \$18. 11/16 Tape 20 for \$18. Creed 7B Teleprinter \$80. Send for price list. Ex Gov. Goods. Photo Medical, Electrical, Scientific gear. All goods sent freight on anywhere plus packing. Studio 20 Sales. 367 Bourke St., Darlinghurst 2010. Phone 31 3383.

DON'T READ THIS if you've got no cents. So you're a big game bargain hunter, off alone into the jungle of electronics, armed only with a soldering iron. Don't be taken for a ride — send for our free guide. SSAE appreciated (small okay). Take along our wild stock list as a guide which includes choice game such as 2c resistors, 6c electrolytics, 6c 1N4148 (\$4.50/100, \$38/K), 15c zeners, 35c SCRs, 65c triacs, 35c diacs, and many others worth bagging. We'll bag 'em for you — as many as you like for only 40c postage allowance. No minimum quota either. We operate a genuine same day turnaround service. **DIGGERMAN ELECTRONICS**, Box 33, Coramba 2466.

SUPER SPECIALS: 1 RH Metal glaze G.L.P. or G.L. 1/2 watt resistors 2.5 cents each or 2 cents each over 100 mixed 555 timers. mDip 50 cents each or 10 for \$4.50. 2N3055 at 90 cents each. BC107 8-9 at 20 cents each. PN3566 at 25 cents each. BD 135-bd140 60 cents each. uA741 mDip 40 cents each. uA723 14 pin 50 cents each. Large RED LEDs 25c each. C.B. Regulators uA78CB 13.8v. at 2 Amps \$2.90 each. uA7805-7812-7815 +v, +v, +15v. 1 Amp Regulators at a SPECIAL price of \$1.90 each. We stock FAIRCHILD components and in every order we include a price list of other discounted components. Package and postage 40 cents. Send cheque or postal order to: Rod Irving Electronics, P.O. Box 135, Northcote, Vic. 3070.

TRANSCEIVER-YAESU FT 75B-SSB/CW 5 band-80/10m-matching AC and DC power supplies — comprehensive accessories and spares — new condition — \$450 ono — Alan Kitchener, 75 Brunswick Street, Fitzroy 3065. Ph. 419 7055.

FOR THE MUSIC LOVER AND ELECTRONICS ENTHUSIAST: Bohm Electronic Organs for superior sound and competitive prices. Now available in Do-it-yourself kit form. Write or phone today for information. Bohm Electronic Organs (Aust.), WE Herrmann, 54 Ambrie Crescent, Harrisfield, 3174 (Vic.). Tel. (06) 546 1461 (H), (06) 341 2329 (Bus).

NOVICE EA TRANSMITTER \$85. EA 130 Receiver \$75. EA Video Game \$65. ETI XHATCH Gen \$40. Kenwood TS600 \$600. Vox \$20. N. Mattick Hargraves 2850.

TV GAMES I.C. AY 3 8500. Scoop purchase of manufacturers surplus \$12 each plus \$1 post & packing. \$10 each in lots of 10 or more. Once only offer so get in quick. A.E. Cooling Electronics, 6 Trimmer Road, Elizabeth South 5112.

DISPLAY ADVERTISEMENTS IN MARKETPLACE are available in sizes from a minimum of 2cm x 1 col rated at \$11 per col cm.

CLASSIFIED RATES \$2 per line per insertion payable in advance. Minimum two lines.

CLOSING DATE is six weeks prior to the on-sale date. Issues are on sale the first Monday of each month.

ADDRESS all classified orders, copy, enquiries, etc., to: The Advertising Manager, **ELECTRONICS Australia**, Box 162, Beaconsfield 2014.

RESISTORS AND CAPACITORS: Resistors all E12 values. 1/4 watt carbon film, 10 ohm to 1 meg 2 cents each. I.R.H. G.L. 1/2 or G.L.P. 1/2 watt Metal glaze 10 ohm — 470k 3 cents each or 2.5 cents over 250. 1 watt 1 ohm to 1k 6 cents each or 5 cents over 100. **PACKS STANDARD PACK** contains 5 each of E12 values in ranges shown. **COMPUTER PACK** contains quantities based on general usage. 1/2 watt 285 resistors \$7.00. 1/4 watt 305 resistors \$5.90. **CAPACITORS ELECTROLYTIC** single ended up-rights. Mfd 35 v.w. 1. 2. 2. 3.3. 4.7. 10. 22. 10 cents each. 33.47. 15 cents. 25 v.w. 100. 16 cents each. 220. 25 cents each. 470. 35 cents. Polyester Green-caps 100 v.w. 001. 0022. 0033. 0047. 0056. 0068. 7 cents each. 01. 022. 033. 047. 056. 068. 082. 10 cents each. 1. 22. 13 cents each. **Poly Pack** 5 cents of these values \$6.00. 75 capacitors. Other components see E.A. June 1976. All components brand new from manufacturers or agents. Each value of component individually packed. Post and packing included in all orders over \$6.50. For orders less than \$6.50 add 40 cents for post and packing. 5% discount on orders over \$35.00. 10% discount on orders over \$75.00. Send orders to **RAM ELECTRONICS**, 575 Sydney Road, Seaford, N.S.W. 2092. Please send cheque or money order.

HIGH QUALITY CASSETTE TAPES: Wholesale price min. ten C60. SA9.50 postpaid. Free sample! La Selle Co. Salyingpun, P.O. Box 20359, Hong Kong.

TRIO 9R-S9DS Communications Receiver. Mint condition. 55 — 30 MHz — \$160 — (062) 41 2951.

POST FREE BARGAINS: Surplus untested semiconductors, transistors 10 for 50 cents, diodes 30 for 50 cents. Low cost B & W Television parts. Send 18 cent stamp for full lists including our C.B. gear. Nalco Mail Order, 15 Grove Street, Eastwood 2122.

SHORTWAVE ENTHUSIASTS — DXERS: You need the Australian Radio DX Club. Now in its 13th year of operation, the monthly magazine covers the SW & MW spectrums. For full details, including information on club services, write enclosing 20c stamp to ARDXC, N.S.W. enquiries to P.O. Box 250, Mona Vale, N.S.W. 2103. S.A. enquiries to 12 High St., Cheltenham, S.A. 5014, all others to P.O. Box 67, Hightett, Vic. 3190.

SWTPC SWTPC SWTPC: Computer Kits in Australia. MP.68 complete unit with 4K memory and Serial Interface. For further technical details ring **PARIS RADIO ELECTRONICS** 02-31 3273 or send S.A.E. at 7A Burton St. Darlinghurst 2010.

WANTED

USED YAESU FRG-7 RECEIVER, must be in mint condition. R. Redberger, 12 Aquarium Dr. Hemmant, Qld 4174.

FREE

14 PAGE ILLUSTRATED CATALOGUE

OF

TOP QUALITY ELECTRONIC COMPONENTS — TTL, CMOS, LINEAR, TRANSISTORS, ZENER, CAPACITORS, POTS RESISTORS, ETC. SURPRISE YOURSELF WITH OUR DISCOUNT PRICES.

Just write to:

Linear Electronics,
P.O. BOX 254, PUNCHBOWL, 2196

ELECTRONICS AUSTRALIA
DIGITAL FREQUENCY
METER KIT
20MHz \$82.00
200MHz \$89.50

HIGH STABILITY CRYSTAL (see below) Prepunched aluminium chassis with black "Marviplate" cover. "Polaroid" front panel, lettered. Fibreglass P.C. Boards with component overlay

All high quality components (Fairchild, National, A @ R etc) B.N.C. socket (Amphenol) standard — U.H.F. type available on request. Instructions included.

Further details — E.A. March 1977.
Separate Components available — 3.579545 MHz Crystal, cold welded HC18/u holder 30 p.p.m. — 10° to +60°C (from 25°C) \$8.00, post free. Fairchild 95H90 \$9.50 post free. Prices include Sales Tax.

Postage and Packing (buyer's risk)
 N.S.W. \$2, Interstate \$4

Registration charge \$2

COMET — 50c, packing free insur.
 Sydney \$2, Melbourne, Brisbane \$7

J.R. COMPONENTS


P.O. BOX 128 EASTWOOD,
 N.S.W. 2122
 PHONE (02) 85 3976

If you program microprocessors, these sheets are for you

Writing microprocessor programs on blank or plain ruled paper is messy and time consuming. To make the job easier, Electronics Australia has produced these custom-designed programming sheets for use with virtually any microprocessor system. The sheets feature columns for a 4-digit address, up to six digits of instruction code or data, labels, mnemonics, and comments. There is space for 46 lines per sheet, and the sheets are provided with space for program title, date and sheet number. They are also punched for filing in a standard ring binder. All for less than 5 cents per sheet, posted!

PRICED AT \$2.00 FOR 50 SHEETS
 (plus 40c for postage anywhere in Australia)

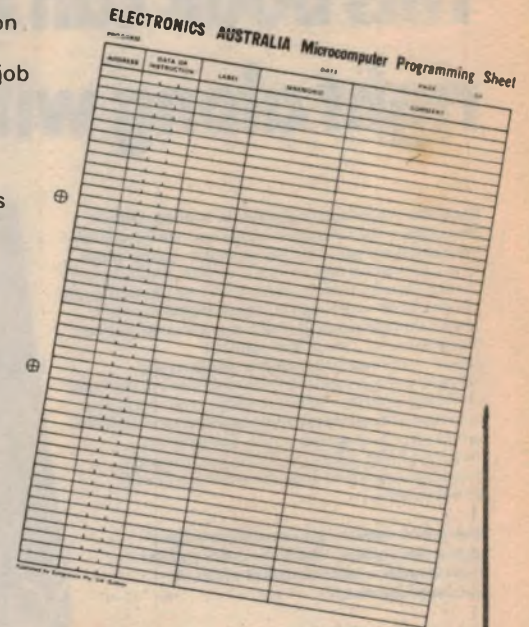Available only from Electronics Australia,
 57 Regent St., Sydney (P.O. Box 163, Beaconsfield, NSW 2014)



SPEAKER BONANZA

4D/8 4 inch, 8 ohm, 4 watt, general purpose speaker. Suitable for simple alarms, and sirens. Supplied with many of our kits.
 \$3.25 each or 10 for \$28.00.

3D/16 5 inch, 15 ohm, 3 1/2 watt, general purpose speaker. Very efficient, ideal for using in small transistor projects.
 \$3.50 each or 10 for \$30.00.

64D/8 Oval speaker, 3 1/2 watt, low cost but very efficient speaker.
 \$3.75 each or 10 for \$30.00.

CRMX/8 8 inch, 8 ohm, 6 watt, wide range twin cone speaker. Useful in many situations requiring high quality, but low cost.
 \$6.00 each or 10 for \$50.00.

96D/8 Oval, 8 ohm, 6 watt, general purpose speaker. Can also be used as a car type replacement speaker.
 \$4.00 each or 10 for \$36.00.

30W RMS 12 INCH

PLESSEY C12P SPEAKERS 8 and 15 ohm available. A steal at this price. Suitable for guitar, PA and HiFi use. Price includes P&P.
16.00

10% DISCOUNT

This discount is applicable on any order of the above speakers totalling more than \$100.00.

ETI 804

ETI804 TELEVISION GAME \$ 49.50
 This kit includes the new games chip that has both vertical and horizontal movement. To use it pen pots are required and these are included in this kit.
 AT 3 8550 chip and two pen pots \$ 23.50

6 DIGIT COUNTER

SIX DIGIT COUNTER, DISPLAY AND TOTALIZER IC CHIP. CASE SUPPLIED, IN LOGICAL POSITION TO CUSTOMER'S 7 + 200V SOURCES, FREQUENCY, THERMAL RESISTANCE AND COMPASSION. SEVEN SEGMENT OUTPUT.

MS2033 0.27" PIN DATA..... \$19.50
 612A MS2033 1" READOUTS..... \$10.00
 612C MS2000 1.5" READOUTS..... \$11.00

VU METER 1.80

VU METER 4 cm square. Black face, white and red scale suitable for back lighting. Fantastic value while they last.

KITS AND PARTS MAY EA

27 MHz. PREAMPLIFIER KIT \$19.50
 77pre5 board \$ 1.30

DIGITAL QUARTZ CLOCK M4M002B \$37.50

GAS ANALYSER MARINE KIT \$27.50
 AUTO KIT \$27.50
 PORTABLE KIT \$17.50
 813 TGS \$10.50
 813 TGS \$10.50

KITTY MODULATOR KIT (NO CASE) \$ 7.50
 LM3900 \$ 1.25
 77cxy8 board \$ 1.50

MINISCAMP \$ 3.50
 77up5 board \$ 1.10
 SPDT toggle \$ 1.40

JUNE

TUNABLE RF PREAMPLIFIER KIT \$27.50
 77pre5 board \$ 1.30

DOAL REGULATED SUPPLY KIT \$27.50
 LM340T-5 \$ 2.25
 LM320T-12 \$ 3.75

760 LARGE MOS KEYSER KIT "C" \$ 8.95
 MOS KEYSER KIT \$ 6.95
 77eo5 board \$ 2.25
 4016 \$ 72c
 4024 \$ 1.12

LARGER MINISCAMP EXTENSION \$ 2.20
 77up6 board

JULY

10 GHz. RADAR BURGLAR ALARM KIT \$ 69.50
 require \$ 1.60

DWELL METER KIT \$ 21.50
 LM2917N IC \$ 3.95
 77d7 board \$ 1.20

DIGITAL LOGIC TRAINER KIT (NO CASE) \$ 49.50
 77dlc7 & front \$ 9.50

KITTY REGENERATOR AND SPEED CONV. KIT \$ 27.50
 81883 IC \$ 12.50
 77c1y7 board \$ 1.80
 power supply \$ 6.95

EA CDI 18.50

Complete kit with prewound secondary coil. High quality components and undrilled metalwork. Buy now for easy winter starting and running.

EA SQ 29.00

This is the three I.C. SQ decoder kit as featured in EA February 1977. Complete with board, rotary pots and IC's. No case or power supply. This is a very popular kit. See below for conversion kit.

ELECTROKITS

JUMBO 7 SEGMENT DISPLAY \$8.00

THIS CONSISTS OF A BOARD, TWENTY TWO LARGE LEADS AND A SEVEN SEGMENT DRIVER. IT IS IDEAL WHERE LARGE BUT BRIGHT DISPLAYS ARE REQUIRED. APPROXIMATELY THREE CENTIMETRES HIGH.

STEAM WHISTLE KIT \$8.00

THE PITCH OF THE NOTE CAN BE VARIED, OPERATION OF THE SOUND CAN BE MADE WITH LAMP'S SINCE THE UNIT IS SWITCHED BY A LIGHT DEPENDENT RESISTOR.

STEAM TRAIN SOUND KIT \$ 8.00

THE RHYTHM OF THE SOUND IS REGULATED AUTOMATICALLY AND IS PRACTICALLY PROPORTIONAL TO THE SPEED OF THE TRAIN. THIS UNIT REQUIRES AN AMPLIFIER.

BASIC 1WATT KIT \$ 5.00

AMPLIFIER AND MIXER FOR ABOVE SOUNDS, OR FOR USE IN ANY GENERAL PURPOSE APPLICATION REQUIRING A LOW BUT USEFUL AUDIO AMPLIFIER. SPEAKER NOT SUPPLIED.

DIGITAL REV COUNTER KIT \$12.00

DEIGNED TO MEASURE THE SPEED OF A CAR ENGINE IN RPM WITH TWO DIGIT READOUT. THIS ALLOWS MEASUREMENT AT AN ACCURACY OF BETTER THAN ONE PERCENT. THE CASE IS NOT SUPPLIED.

Electronics Supply Service

WE REGRET THAT IT IS SOMETIMES NECESSARY TO ALTER PRICES WITHOUT NOTICE

POSTAL ADDRESS :
 SKY ELECTRONICS SUPPLY SERVICE,
 PO BOX 787, POTTS POINT,
 SYDNEY, 2011.

MAIL ORDER.....MINIMUM.....\$8.00.
 PACK AND POST.....FREE IN AUSTRALIA.
 TELEPHONE ENQUIRIES.....(02) 358 2420.

179 VICTORIA ST., KINGS CROSS N.S.W. 2011


Electronics is going digital. This book can help YOU go right along with it:

Electronic equipment now plays an important role in almost every field of human endeavour. And every day, more and more electronic equipment is "going digital". Even professional engineers and technicians find it hard to keep pace. In order to understand new developments, you need a good grounding in basic digital concepts, and *An Introduction to Digital Electronics* can give you that grounding. Tens of thousands of people—engineers, technicians, students and hobbyists—have used the first two editions of this book to find out what the digital revolution is all about. The new third edition has been fully rewritten and updated, to make it of even greater value. The author is Jamieson Rowe, Editor of "Electronics Australia" magazine, a qualified engineer and experienced technical writer.

You don't need any previous knowledge of digital electronics—the book starts you right from scratch, and covers all of the basic concepts you need.

PRICE \$3.00

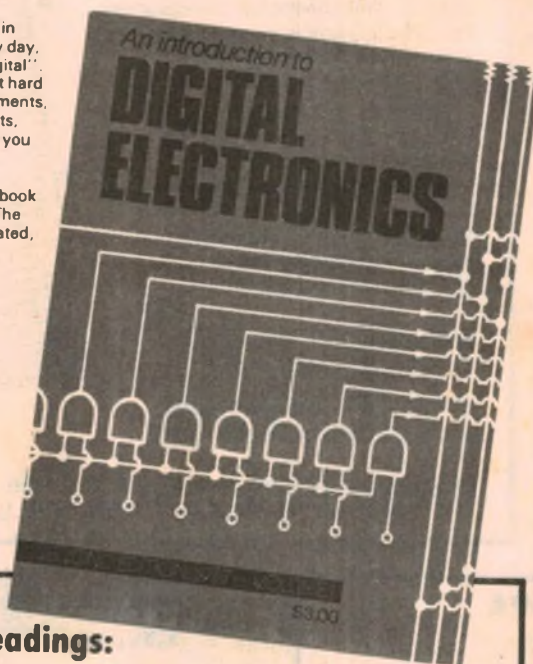Available from newsagents, bookstores, electronic suppliers and also from "Electronics Australia", Box 163, P.O. Beaconsfield 2014. (Post and packing 60c).



Here are the chapter headings:

- | | |
|--------------------------------|---------------------------|
| 1. Signals, circuits and logic | 10. Flipflops in counters |
| 2. Basic logic elements | 11. Encoding and decoding |
| 3. Logic circuit "families" | 12. Basic readout devices |
| 4. Logic convention and laws | 13. Multiplexing |
| 5. Logic design: theory | 14. Binary arithmetic |
| 6. Logic design: practice | 15. Arithmetic circuits |
| 7. Numbers, data & codes | 16. Timing & control |
| 8. The flipflop family | Glossary of terms |
| 9. Flipflops in registers | |

TIME CLOCKS SANGAMO



LESS
DAY OMIT
DEVICE
\$13.50

WITH
DAY OMIT
DEVICE
\$16.00

240V 50 cs
15A Contacts

Used tested and guaranteed
PACK & POST N.S.W. \$2.00
Vic. & Qld. \$2.50, W.A. \$3.00

CLOCK DISPOSAL CO.
P.O. Box 147
LINDFIELD, N.S.W. 2070

ELECTRONICS Australia

EVERY MONTH FROM YOUR NEWSAGENT

- Articles which will keep you up to date in this fascinating world of electronics.
- Constructional details for a never ending variety of do it yourself electronic projects.
- How it-works features explaining electronic equipment and theory in uncomplicated terms.
- Up to the minute information on new recordings, new products and books, short-wave listening and amateur band activities.

Australia's largest selling electronics and HiFi magazine

Advertising Index

A & R Soanar Group	59
Ace Radio	106
Aegis Pty Ltd	53
Agfa Gevaert Ltd colour insert between	48-49
Adcola Products Pty Ltd	124
Astro-Optical Supplies Pty Ltd	16
Audio Télex Communications Pty Ltd	61
Auditec Australia	124
Australian Government Recruiting	49
BKX Electronics Supply Service	135
Bail Electronic Services	57, 60
BSR Hi-Fi Equipment	36
Bright Star Crystals Pty Ltd	128
BWD Electronics Pty Ltd	12
C & R Electronics	81
Chan Merchandising	129
Chapman L. E.	110
Classic Radio	114
Clock Disposal Co.	136
Computer Art & Education	99
Convoy International Pty Ltd	28
Cowper Sheetmetal & Engineering	89
Dandy Electronic Discounts	89
Davred Electronics	42, 43
Deitch Bros.	132
Delta Base CB Radio	57
Dick Smith Electronics Group	8, 9, 50, 64, 78, 104, 130
Direct Disposals Trading Co.	120
Douglas Transformers	125
Electrocraft Pty Ltd	130
Electronic Concepts	96
Electronic Enthusiasts Emporium	117
Elmeasco Instruments Pty Ltd	102
General Electronic Services Pty Ltd	74
Haco Distributing Agencies	OBC
Hagemeyer (Aust)	IBC,
colour insert between	48-49
Harman Australia Pty Ltd	86, 116
Instant Component Service	34, 35
International Correspondence Schools	7
JR Components	135
Kenelec Systems	70
Lafayette Electronics	58
Lanthur Electronics	134
Laser Electronics Pty Ltd	118
Leroya Industries Pty Ltd	26, 38
Linear Electronics	134
M.R. Acoustics	108
McGills Newsagency Pty Ltd	119
Nessel Audio	31
Nomis Electronics Pty Ltd	79
Parameters Pty Ltd	20
Philips	2, 4, 6
Photimport	24, 112
Polar Electronics	16
Ralmar "Goldies"	72
RCS Radio	25
Radio Despatch Service	73
Sabtronics International	
colour insert between	48-49
Sanwa Electric Instruments	91
Scalar Industries Pty Ltd	56
Scientific Electronics	60
Sontron Instruments	98
Sony Kemtron Pty Ltd	IFC
Stotts Technical College	63
Sungravure Pty Ltd	54, 55, 68
Tandy International Electronics	
catalog between	88-89
Television Replacement	134
Unitrex of Australia Pty Ltd	90
Vicom International	126
Video Technics	122
Warburton Franki Ltd	76, 122
Wedderspoon W. C.	30, 40
WHK Electronics	48, colour insert between 48-49
Wireless Institute of Australia	128

WHY YOUR NEXT CASSETTE SHOULD BE A MAXELL UD



3 THE SHELL — Even the best tape can get mangled in a poorly constructed shell. That's why Maxell protects its tape with a precisely constructed shell, made of lasting heavy-duty plastic.

No fixed guide posts are used. Instead Maxell uses nylon rollers on stainless steel pins thus eliminating the major cause of skipping, jumping and unwinding.

A tough teflon (not waxed paper) slip sheet keeps the tape pack tight and flat. No more bent or nicked tape to ruin your recording.

Maxell doesn't use a welded seal, but puts the cassette together with precision screws. Result — Maxell doesn't jam.



1 THE RESEARCH — More than twenty years ago, Maxell produced their first reel of magnetic tape. At that time, Maxell made a commitment to produce and sell only the finest magnetic products their technology could create.


That commitment still stands today.

2 THE TAPE — This continuous research has led to the development of the Maxell UD (ultra dynamic) cassette. A tape that has a coating of super-fine PX gamma ferric oxide particles with an extra smooth mirror-finish surface.

All of this adds up to high output, low noise, distortion free performance and a dynamic range equaling that of open reel tapes.

4 THE LEADER — A leader tape that has a four function purpose.

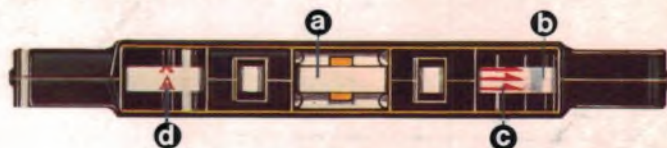- a) Non-abrasive head cleaning leader (cleans recording head for 5 secs.).
- b) 5 second cueing line (recording function starts 5 seconds after the line appears).
- c) Arrows indicating direction of tape travel.
- d) A/B side mark (indicates which side is ready for play).



Now you know why your next cassette should be a Maxell UD (ultra dynamic).

maxell®

The sound expert's cassette. UD available in C60, C90 and C120.
Distributed by **Hagemeyer (Australasia) B.V.** Branches in all States.

TECHNICS PRESENTS ITS CREDENTIALS.



The amazing waveform fidelity of Technics linear phase 2-way speaker systems is now almost legendary. To achieve sound that is virtually indistinguishable from the original, Technics research developed the linear phase system by adopting high performance, wide range units in a unique network configuration and ideal positional location.

With the Technics SB-4500 comes a similar system—priced to suit the economy minded. It retains the essential crisp transparency of sound all the way through the audio spectrum, easily handling peak power of up to 75 watts.

Technics also offer the SB-5000 and SB-6000 linear phase speaker systems for high fidelity components of compatible quality and performance.

SB-4500

- Extra wide-range 25 cm cone-type woofer.
- 6 cm wide-range edgeless cone tweeter eliminates edge resonance and so reduces distortion • 75 watts peak power input.
- 92.5 dB/W (1 m) sound pressure level.

SB-5000

- Wide range 25 cm woofer.
- 6 cm wide-range edgeless cone tweeter delivers a crisp transparency of high frequency sound • 75 watts peak power input.
- 93.5 dB/W (1 m) sound pressure level.

SB-6000

- 30 cm woofer gives low distortion from super-low frequencies through the midrange.
- 3.2 cm dome tweeter gives high efficiency and low distortion.
- 100 watts peak power input • 93 dB/W (1 m) sound pressure level.



For a National Technics catalogue please write to:
National Technics Advisory Service, P.O. Box 49, Kensington, N.S.W. 2033



Technics

hi-fi