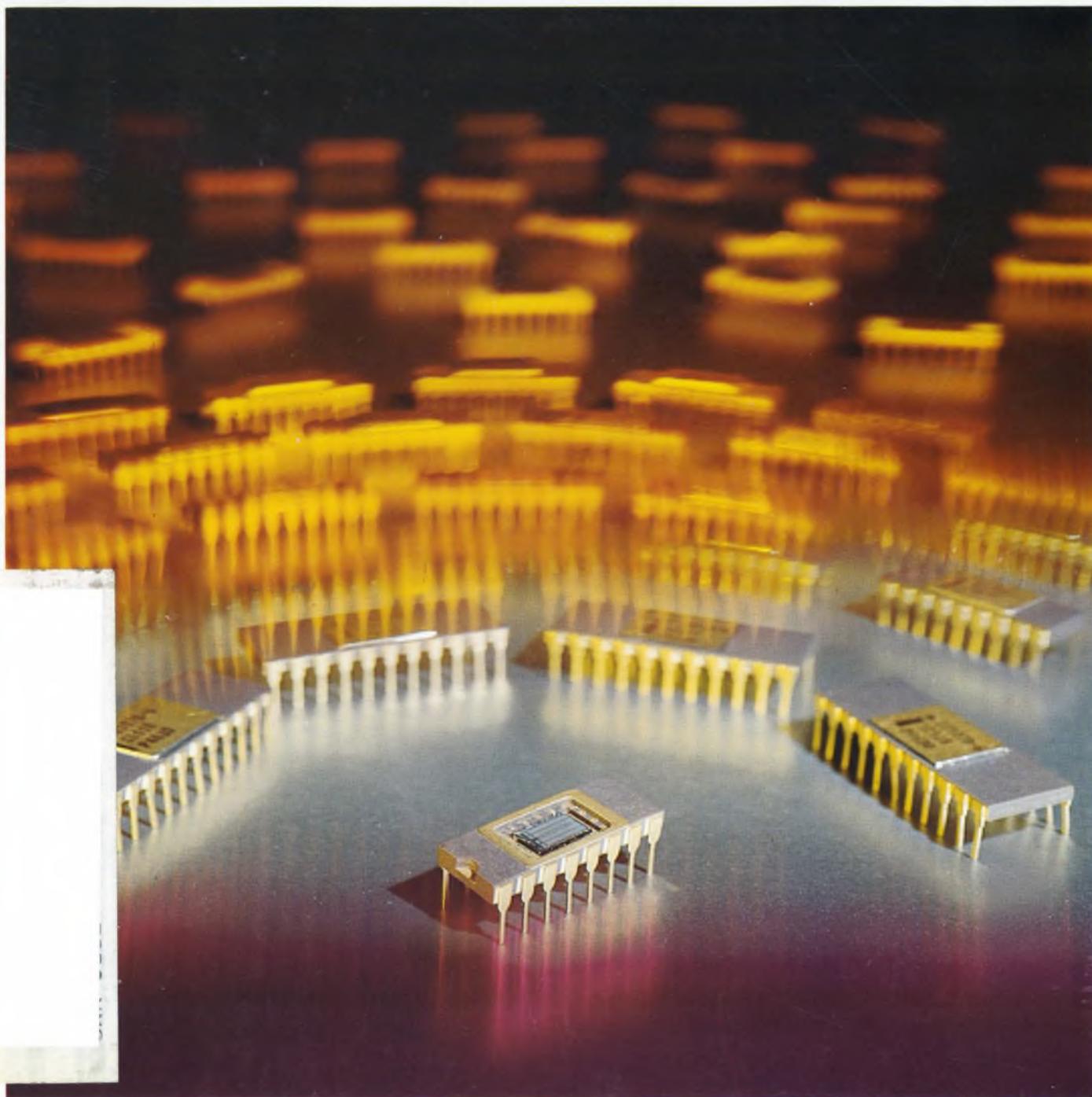


The first 16-k bit MOS RAM achieves the highest capacity for random-access memories, with no sacrifice in speed. The IC has an access time of 250 ns,

or about that of current 4-k bit units. And the new memory uses the 16-pin package of some 4-k versions, simplifying expansion of present systems. See p. 101.





BOURNS®
New, Low-Cost
Cermet
Trimming
Potentiometer
outperforms
the other
"small-change"
models!

Bourns super cermet performance delivers again. Our new Model 3352 trimming potentiometer handles more power . . . takes more shock and vibration . . . has a lower CRV . . . and is easier to set than, for example, the "Model 91". Naturally, Bourns super cermet performance is comparably priced. You can depend on it.

The 3352 is a 3/8" diameter, single-turn device with an easy (but stable) three-way thumbwheel adjust. It can be wave-soldered, and withstands board washing processes with minimal (1%) TR shift. The 3352 is available TODAY in a variety of pin styles to suit your requirements.

Compare performance . . . specify Bourns Model 3352. For complete details, contact your local Bourns representative . . . or the factory direct.

COMPARE PERFORMANCE

| | Model 3352 | Beckman Model 91 |
|-------------------------|------------------------|--------------------|
| Power | .75 watts at 40°C | .5 watts at 40°C |
| Electrical Angle | 230° | 180° |
| Adjustability | ±0.05% | ±0.05% |
| Torque | 5 oz.-in. max. | 6 oz.-in. |
| Shock | 100G's max. ±2% VRS | 50G's no VRS spec. |
| Vibration | 30G's max. ±2% VRS | 10G's no VRS spec. |
| Contact Resistance Var. | 1% | 2% |
| Rotational Life | 200 cycles | 200 cycles |
| Temp. Range | -55°C to +125°C | -55°C to +125°C |





*Nobody knows more about
trimming potentiometers than we do*



TRIMPOT PRODUCTS DIVISION • 1200 COLUMBIA AVE., RIVERSIDE, CALIF. 92507

Hot-molded resistors provide low temperature coefficient and unmatched reliability.

The Resistance Temperature Coefficient of Allen-Bradley hot-molded fixed resistors is typically less than 200 PPM over the entire resistor range shown in the normal equipment operating temperature of +15°C to +75°C. Excellent RTC ratings have always been an Allen-Bradley benefit. And consistency of Allen-Bradley resistors means repeatable results and tight performance patterns. Allen-Bradley resistors offer the **lowest cost—on the board—**where it counts!

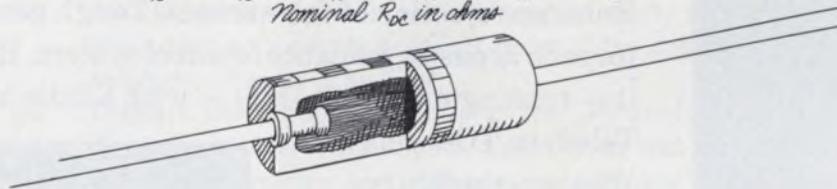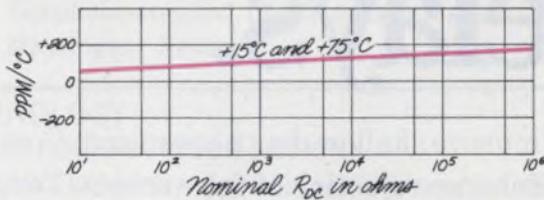

Reliability

is unsurpassed. Over 700 million unit test hours without a single failure.

No coatings

Insulation and resistance element integrally molded into one solid structure.

Pulse handling


characteristics offer outstanding protection against surges and transients.

Quality in the best tradition.



ALLEN-BRADLEY
Electronics Division
Milwaukee, Wisconsin 53204

We unknot wire problems

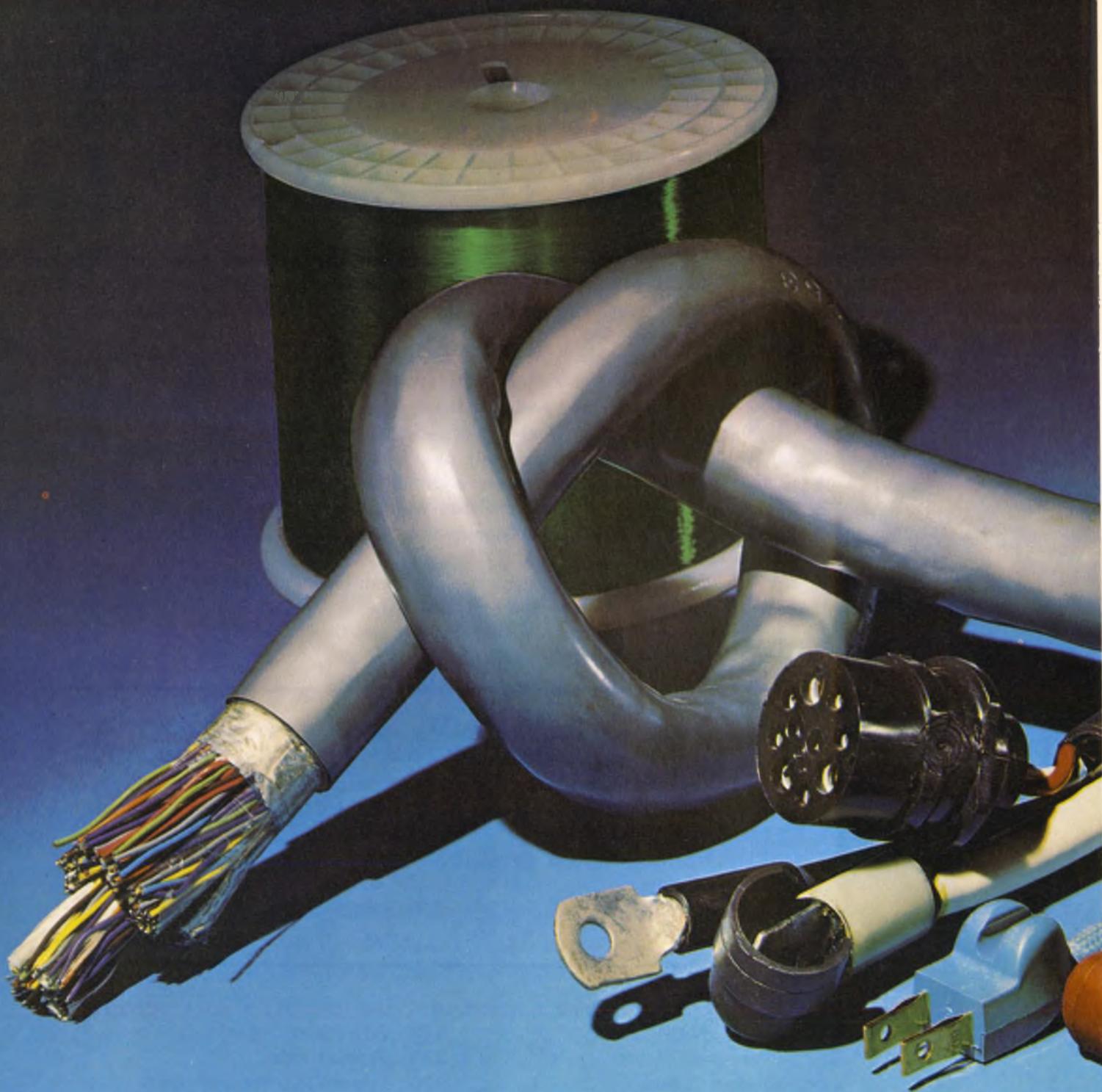

BELDEN 

...new ideas for moving electrical energy

Knotty problems in wire, cable, and cords can pop up at any stage of a project. Hopefully, they arise early in design. Oftentimes, they surface later. This can put an unexpected crimp in your product's profit or performance.

We're ready to offer backup help in performance, design, processing, assembly, installations, and ordering. Whatever wire and cable application idea you put on paper, Belden can help put life into it! Our total engineering approach to your problems can identify and analyze the "knots" before they tie up a major project.

If you have problems involving electrical parameters, space, compatibility, human

engineering, color coordination, precision, materials, fabrication, processing, put-ups, installation, Belden has the ability to engineer reliability and ease of assembly into wire, cable, and cords without letting costs run wild due to over-engineering.

When we can't get out the "kinks" using standards, we'll innovate a solution for your problem. We're here with service and multi-plant facilities that can meet your demands. Need answers? Phone:


(312) 986-1600, Electrical Division

(317) 966-6681, Electronic Division

(312) 887-1800, Transportation Division

Or, write Belden Corporation, 2000 South Batavia Ave., Geneva, Illinois 60134.

H-4-4A

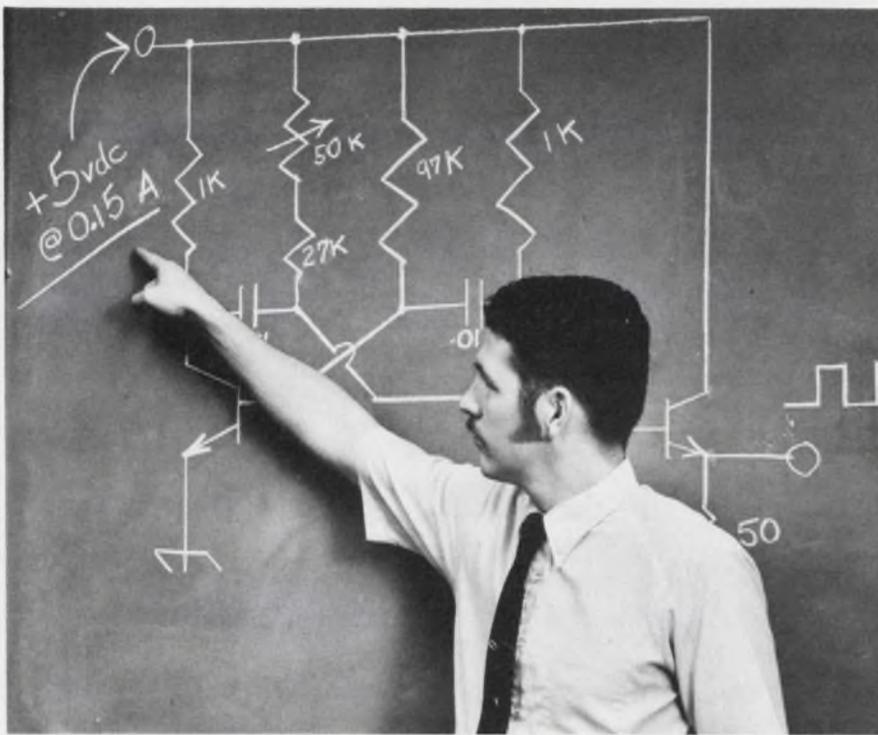

How to Design Your Power Supply for \$66

You get the *complete schematic diagram, and parts list* with operating and installation instructions when you spend \$66 for an Abbott Model "RN" power supply. Two years in development, this model represents the latest state of the art in power module design. It features close regulation (0.1%), low ripple (0.02%), automatic short circuit and complimentary overvoltage protection and continuous operation in a 160°F ambient.

Abbott Engineers followed specific design criteria in engineering these modules. First, the electrical design was carefully engineered to insure that all components operate well within their limits, under "worst case" operating conditions. Second, the thermal design, including case construction, was carefully made to insure that the maximum temperature limits of all components are never exceeded. Then the size and weight of these modules were controlled to a minimum, without sacrificing reliability. Finally these units were thoroughly tested to make certain that all design and performance specifications were met.

So, you can build your own power supply using our schematic diagram if you want to—but we think we can build it more

Please see pages 1037-1056 Volume 1 of your 1975-76 EEM (ELECTRONIC ENGINEERS MASTER Catalog) or pages 612-620 Volume 2 of your 1975-76 GOLD BOOK for complete information on Abbott Modules.

Send for our new 60 page FREE catalog.

reliably and for less cost, simply because we have been doing it for ten years. Put our power supply in your system first and try it. Examine its performance. We think you will be pleasantly surprised at the quality, adherence to specifications, and the reliability you find in the Abbott Model "RN".

Any output voltage from 5 to 100 volts DC with current from 0.15 to 20 amperes is available. *Many of the popular voltages are carried in stock for immediate delivery.* Please call us for attractive O.E.M. discount prices.

Abbott also manufactures 3,000 other models of power supplies with output voltages from 5.0 to 740 volts DC and with output currents from 2 milliamperes to 20 amperes. They are all listed *with prices* in the new Abbott catalog with various inputs:

- 60 A to DC
- 400 A to DC
- 28 VDC to DC
- 28 VDC to 400 A
- 12-38 VDC to 60 A

Sr. Vice President, Publisher
Peter Coley

Editors

Editorial Offices
50 Essex St.
Rochelle Park, NJ 07662
(201) 843-0550
TWX: 710-990-5071
Cable: Haydenpubs Rochellepark

Editor-in-Chief George Rostky

Managing Editors:

Ralph Dobriner
Michael Elphick

Associate Editors:

Dave Bursky
Samuel Derman
Morris Grossman
John F. Mason
Stanley Runyon
Michael Shunfenthal
Edward A. Torrero

Contributing Editors:

Peter N. Budzilovich, John Kessler
Alberto Socolovsky, Nathan Sussman

Editorial Field Offices

East

Jim McDermott, Eastern Editor
P.O. Box 272
Easthampton, MA 01027
(413) 527-3632

West

David N. Kaye, Senior Western Editor
8939 S. Sepulveda Blvd., Suite 510
Los Angeles, CA 90045
(213) 641-6544
TWX: 1-910-328-7240

Jim Gold, Western Editor

1454 Burrell Court
San Jose, CA 95126
(408) 246-6094

Editorial Production

Marjorie A. Duffy, Production Editor
Tom Collins, Copy Editor

Art

Art Director, William Kelly
Richard Luce, Anthony J. Fischetto

Production

Manager, Dollie S. Viebig
Helen De Polo, Anne Molfetas

Circulation

Manager, Barbara Freundlich
Trish Edelmann, Gene M. Corrado

Information Retrieval

Peggy Long

Advertising Promotion

Paul K. Hogue

Promotion, Creative Layouts

Manager, Albert B. Stempel
Maxine Correal, Nancy Gordon

abbott

transistor

LABORATORIES, INCORPORATED
general offices eastern office

5200 W. Jefferson Blvd./Los Angeles 90016
(213) 936-8185 Telex: 69-1398

1224 Anderson Ave./Fort Lee, N.J. 07024
(201) 224-6900 Telex: 13-5332

"SEE US AT ELECTRO '76 I.E.E.E. SHOW IN BOSTON, BOOTH NO. 2112"

CIRCLE NUMBER 5

Across the Desk

Bit-error rate analysis needed

The article "Squeeze More Data into Mag Tape," by Messrs. Bentley and Varsos (ED No. 21, Oct. 11, 1975, p. 76) should have included a more substantial analysis of the high bit-error rate associated with Miller encoding in a bandwidth-limited (tape recording) application. Such an exhaustive analysis is included in a paper by W. N. Waggener of EMR-Schlumberger titled "Optimum Detection of Delay Modulation."

The introduction of the paper states, "The performance of delay modulation (DM) has been widely misunderstood. The small low-frequency content and a sharply peaked spectrum at about 0.4 bit rate has led potential users to conclude that DM is an efficient coding technique."

Such a conclusion is unwarranted and, in fact, the performance of DM is 3.5 dB poorer than NRZ using an optimum detection bandwidth of twice that of NRZ. If the bandwidth of DM is limited to the spectral region less than the bit rate, a considerable penalty in bit error performance is paid. This seems to contradict the article by Messrs. Bentley and Varsos.

W. D. Lewis

Computer Systems Specialist
General Dynamics
Data Systems Services

Authors reply

The analytical paper referred to by Mr. Lewis has been reviewed with interest and appears to be highly pertinent to the subject ma-

terial. We greatly appreciate his letter, especially in directing our attention to this analytical study.

Our article, though, in no way contradicts or confirms the result of Mr. Waggener's study. For recording applications, where output signal-to-noise ratios greater than 20 dB are experienced in practice, bit-error rates (BERs) better than 10^{-6} are attainable even under the most pessimistic performance curve of Waggener's analysis. This is in agreement with the claims of BER performance, as stated in our article.

The 10^{-6} BER performance has been previously reported in reference 2 of our article, and in other new references that have been published more recently. These are listed here for your information:

1. Breikss, Ivars P., "High-Density Data Recording," *IEEE Spectrum*, May, 1975, pp. 58-62.

2. Jensen, T. A., and Starkey, M., "80 MBPS Recording," *Digital Design*, September, 1974, pp. 28-35.

S. G. Varsos

Engineer Principal

Lockheed Electronics Co.
16811 El Camino Real
Houston, TX 77058


Beating the standard set for HP-25

The programmable pocket calculator truly provides the scientist and engineer of today with a personal computer. The presently available calculators are comparable in computing power to the early full-scale computers. It will be interesting to watch for parallelisms in development.

The absolute machine language

(continued on page 8)

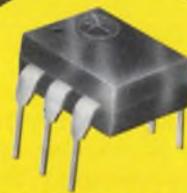Electronic Design welcomes the opinions of its readers on the issues raised in the magazine's editorial columns. Address letters to Managing Editor, Electronic Design, 50 Essex St. Rochelle Park, N.J. 07662. Try to keep letters under 200 words. Letters must be signed. Names will be withheld on request.



5 kV ISOLATION
"DIP"
Isolators

OPTRON OPTICALLY COUPLED ISOLATORS

NEW HIGH ISOLATION VOLTAGE
"DIP" SERIES OFFERS
HIGH TRANSFER RATIO

Now, OPTRON provides a 5 kV isolation voltage capability for its standard six pin plastic dual-in-line isolators. A new, unique internal design allows high voltage isolation while still maintaining a high current transfer ratio. The 5 kV DC or 3750 rms AC feature is available for all devices in OPTRON's popular OPI 2100 and OPI 3100 series.

OPTRON's extended "DIP" series includes JEDEC types 4N25 through 4N38A, features complete interchangeability with popular industry types and provides an inexpensive coupler for every application. Devices are available with isolation voltages of 1500, 2500 or 5000 volts with minimum current transfer ratios ranging from 2.0 to 500%.

OPTRON's "DIP" and a full line of other isolator packages with isolation voltages to 50 kV provide the versatility required for maximum electrical and mechanical design flexibility.

1.5 kV isolation with 60% current transfer ratio. Phototransistor base lead available. Hermetic TO-5 package.



OPI 102



OPI 110

10 kV isolation and 40% current transfer ratio. 4 μ sec switching time in low cost miniature plastic package.

Detailed technical information on "DIP" and other isolators as well as all OPTRON optoelectronic products... chips, discrete components, assemblies, and PC board arrays... is available from your nearest OPTRON sales representative or the factory direct.



OPTRON, INC.

1201 Tappan Circle
Carrollton, Texas 75006, U.S.A.
214/242-6571 • TELEX-73-0701
TWX-910-860-5958

ACROSS THE DESK

(continued from page 7)

programming in the early computer days emphasized minimization of the number of machine cycles and storage locations used. As execution and storage got faster and cheaper, especially relative to the labor component of programming, economic considerations changed the factors to be minimized. As a result, higher level languages became popular.

Modern programmable pocket calculators have limited speed, limited program and data storage, and are programmed in machine language. We are back to counting and minimizing the number of locations used and instructions executed. Since these programs are often entered from the keyboard by highly trained personnel, the number of keystrokes needed to enter the program should also be minimized.

The HP-25 is a popular calculator of this class, and since a book of application programs comes with it, there is a standard to try to beat. Here is a program that calculates the factorial and that is used the same way as the one in the book, but consists of fewer instruction entered in fewer keystrokes—and runs faster. Both versions use one data storage register.

```
STO 0
1
—
STO × 0
1
f × ≠ y
GTO 03
RCL 0
GTO 00
```

Can some other reader beat this?

Henry E. Schaffer
Professor of Genetics

North Carolina State University
Box 5487
Raleigh, NC 27607

D for diode is recommended

Reference Mr. Thomas' letter "An 'Excellent' Guide to Miniature Relays" (ED No. 22, Oct. 25, 1975, p. 7), perhaps I might express the hope that the use of the designa-

tion CR be abandoned for diodes.

Not only does it suffer from the disadvantage of obscurity in this context (D is admirably clear and not used, so far as I am aware, for any other circuit element) but CR is needed for "contactor," for which it is regularly used by electrical engineers to distinguish contactors from low-power supervisor-and-control relays (RL).

Please therefore continue to use the common sense D for diode and perhaps we may hope that one day the American National Standards Institute terminology will be amended to conform to what is a natural and therefore preferable usage.

W. Lyons

Jt. Managing Director

Claude Lyons Ltd.
Ware Rd., Hoddesdon
Herts, EN11 9DX
United Kingdom

Misplaced Caption Dept.



Come seven, we spec it at 7 dB.

Sorry. That's Bartolomé Esteban Murillo's "Street Arabs," which hangs in the Alte Pinakothek in Munich.

Need for kits with an understandable program

I want to commend ELECTRONIC DESIGN for bringing out two fine articles relating to microprocessors. In the January 5, 1976 issue (ED No. 1), on page 46 there is the ED special report on microprocessors,

and the even more interesting article on page 96, "Incorporate a Calculator Chip," relating to use of a calculator chip in a number-processing data system.

It is certain that both of these articles will go far to advance the microprocessor concept, not only for controlling systems, but for mathematical calculations involved in doing so.

For example, a calculator-microprocessor combination could be designed to orient a flat-plate mirror, one of many to be used for concentrating solar heat onto a boiler to generate megawatts of electrical energy. Solar energy thus should go a long way toward solving the energy crisis now facing humanity.

The Altair system, as pointed out in the microprocessor article, is operable using Basic. Many of us engineers know how to use Basic but have difficulties understanding assembly languages as offered in the simple microprocessor kits. Hence, there is an urgent need for putting these kits together with understandable programs for ease in arranging I/O interfaces.

For that reason, the article on the calculator chip was particularly appealing. For instance, calculator kits are available from a number of sources. One could assemble such a "pocket calculator," modify it in the direction of process controlling, and at the same time learn some very good fundamentals of microprocessor use.

Robert H. Weitbrecht

Vice President, Research & Development

Applied Communications Corp.
P.O. Box 555
Belmont, CA 94002

A matter of fact

Thank you for your enlightening editorial in the January 5, 1976 issue of ELECTRONIC DESIGN. Irrespective of whether a different consultant would have altered the course of history, I would like to know if the progeny of the Czar and the Czarina should in fact have been identified as Czardines.

Robert E. Bilby

Manager Marketing Services
Weston Instruments
614 Frelinghuysen Ave.
Newark, NJ 07114




MEASUREMENT COMPUTATION

innovations from Hewlett-Packard

NEWS

MARCH 1976

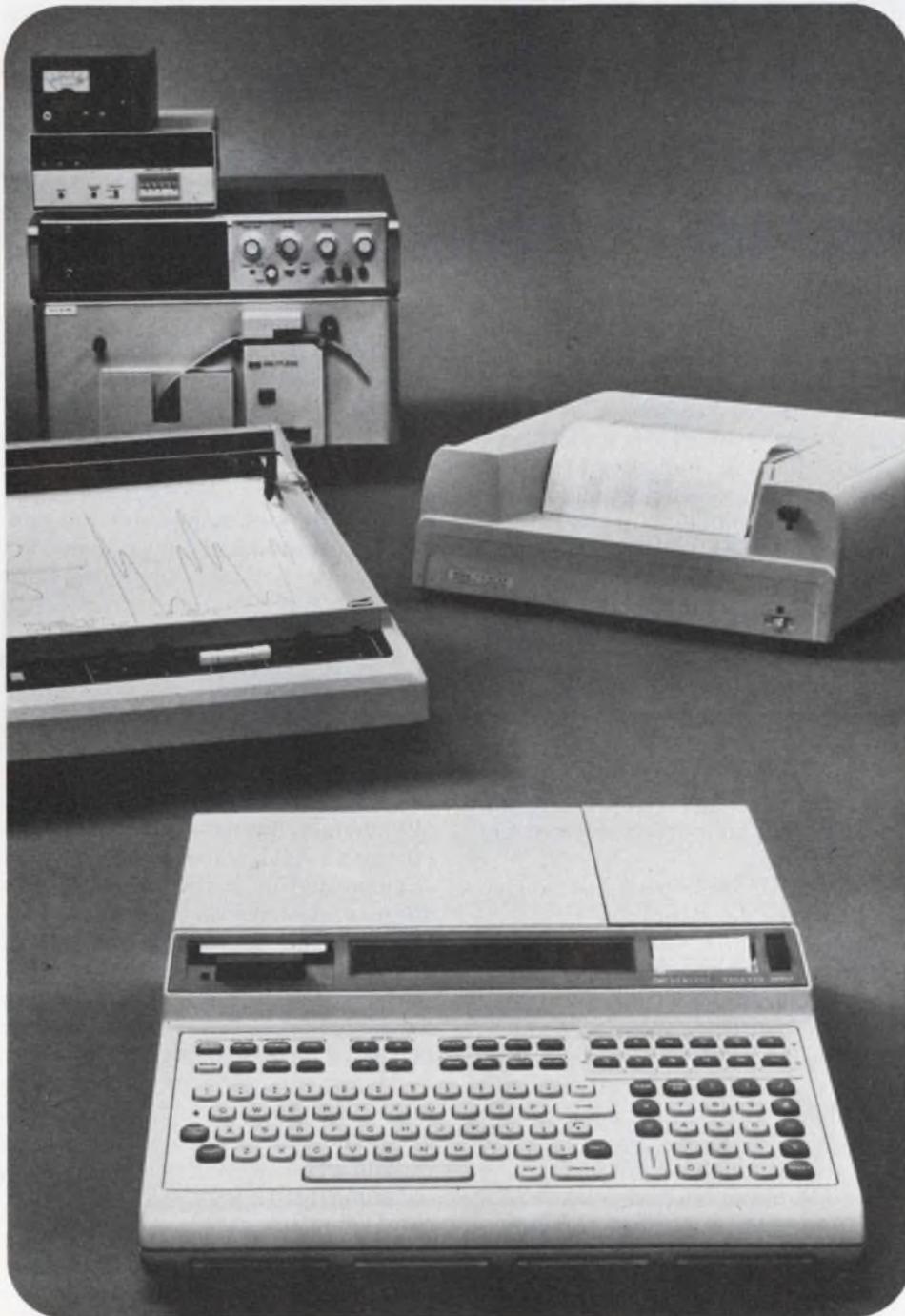

in this issue

One reading per second
with new LCR Meter

New low forward-voltage
microwave diodes

Multi-family logic probe
with lamp display

HP's 9825A powerful new desktop computing system

Because of special features and high speed, the 9825A can compute, handle peripherals, and control instruments, all effectively at the same time.

Combining calculator and mini-computer features, HP's new 9825A offers you a "personal" computer oriented toward the solution of problems in the fields of engineering, research and statistics.

The 9825A has a combination of features never before found on a desktop calculator. With the *live keyboard*, the user can examine and change program variables, perform complex calculations, call subroutines, and record and list programs while the 9825 is performing other operations.

A few more exciting features of this new calculator: *Multidimensional arrays*

(continued on second page)

New fully automatic LCR meter measures inductance, capacitance, and resistance over wider range

Measurements of capacitors, inductors and resistors have been speeded up to rates as high as one reading per second with HP's new 4261A LCR Meter. Auto-ranging and automatic selection of measurement equivalent circuits in C/D, L/D and R modes makes the 4261A LCR meter ideal for testing components used in electronic equipment ranging from stereophonic gear to lab-grade test instrumentation.

Applications such as the measurement of stray capacitance of cables, printed circuit board materials and other components become routine with the 4261A. To facilitate the wide variety of applications, the 4261A will be available with three options: BCD, remote control, and an interface for HP 9800 series calculators via the HP Interface Bus (HP-IB) (IEEE Standard 488-1975).

Capacitance measurement capability is in eight ranges from 0.1 pF to 19.00 mF. Inductance can be measured in seven ranges from 0.1 μ H to 1900 henries; resistance in eight ranges from 1 milliohm to 19 megohms. Dissipation factors of 0 to approximately 1.900 can be made with the 4261A. Measurements are made at 1 kHz for general applications and at 120 Hz for electrolytic capacitors. Accuracy is typically 0.2% of reading.

For details, check D on the HP Reply Card.



Automatic measurement is now possible for the parameters of semiconductors, pulse transformers, filter coils, electrolytic and film capacitors, or to determine the internal resistance of a dry cell or an electrolysis liquid.

New multi-family Logic Probe has built-in pulse memory, low price



Easy-to-use, simple, and rugged, the probe provides a highly effective solution to digital troubleshooting problems.

Troubleshooting of mixed logic families is now faster and more economical than ever before, thanks to HP's new 545A multi-family Logic Probe.

At the flick of a switch, the HP 545A Logic Probe changes to test most positive logic families including TTL and CMOS. An unambiguous single lamp display in the probe tip quickly indicates logic HIGH, LOW, bad level, pulses or pulse trains. Yet, this rugged overload-protected probe costs one-half the price of previous multi-family probes.

The 545A also has a separate built-in pulse memory with its own indicator lamp to catch those elusive pulses and transitions that occur when you're not there to watch. Use of the pulse memory in no way interferes with probe operation as there's an independent memory display circuit.

The 15 μ A/15pF input hardly loads your circuits, yet gives pulse train response to 80 MHz for TTL, 40 MHz for CMOS, and pulse width response to 10 ns.

HP's versatile new "grabber" connectors are provided so you can power the probe using IC test clips, test pins, or you can connect to power pins on an IC with little chance of shorting to an adjacent pin. The probe operates from a wide voltage range—3 to 18 Vdc—and in the TTL mode offers standard TTL logic thresholds over supply ranges from 4.5 to 15 Vdc.

Circle B on the HP Reply Card for your 545A data sheet.

New calculator/controller with outstanding interface capability

(continued from first page)

allow you to organize data logically, thus saving program space and execution time. *Memory load and record* allows you to suspend processing, store the complete contents of memory on tape—including programs, data, and pointers—for continuation later on.

Direct memory access (DMA) is yours with input speeds up to 400,000 16-bit words per second. Memory is expandable in 8K bytes to 32K bytes. Each bi-directional tape cartridge can store 250K bytes with an average access time of 6 seconds.

Accuracy to 12 digits with a dynamic range of 10^{-99} to 10^{99} and an internal calculation range of 10^{-511} to 10^{511} provides you with outstanding arithmetical capabilities.

Because of the 9825's vectored *priority* interrupt capability, available in the Extended I/O ROM, the calculator can act as a controller for several instruments or peripherals which require attention at unpredictable rates or times. Besides being used as a controller for instrumentation systems, it can also be used for pilot process control applications, remote data collection and production control.

As a controller, the 9825 can handle up to 45 measuring instruments simultaneously through its three I/O slots.

Three optional interface cards are available: one for 16-bit parallel data, one for BCD devices, and a third—the HP-Interface Bus—for instruments that conform to IEEE Standard 488-1975.

Upper and lower case alphanumeric are now available on both the 32-character LED display and the 16-character thermal printer.

The 9825's high level programming language (HPL) offers you power and efficiency for handling complex formulas and equations. HPL handles subroutine nesting and flags, and allows 26 simple and 26 array variables.

With all this versatility and speed and weighing just 12 kg. (26 lbs), the 9825 can legitimately be considered a portable computer.

For your free copy of the 16-page 9825A brochure, check O on the HP Reply Card.

Economical pulse generators for TTL, CMOS, ECL, and educational applications

HP's broad family of high quality pulse generators includes a cost-effective pulser for every performance level and application. Model 8011A, for example, is HP's lowest cost pulse generator. Its 16V amplitude and 20 MHz repetition rate are perfect for the requirements of CMOS and TTL logic design. The pulse burst option (001) helps you speed logic debugging by letting you rapidly generate a precise pulse burst just by dialing the desired length on thumbwheel switches. The 8011A's low cost of ownership also makes it an ideal choice for education applications. The logical, easy-to-use panel control layout, and short circuit proof output minimize familiarization and downtime—important benefits in student labs.

Models 8012B and 8013B are versatile, general-purpose units which provide



Meeting the requirements of digital logic laboratories, these pulse generators are extremely flexible with panel controls designed for easy operation.

you additional pulse parameter control for more complex testing applications. The 50 MHz, $\pm 10V$ performance of these models is ideal for TTL and basic ECL applications. The 8012B is HP's lowest cost 50 Hz pulser with variable rise and fall times. The 8013B has fixed transition times less than 3.5 ns

and also provides simultaneous positive and negative outputs useful in analog applications.

For literature, check L on the HP Reply Card.

Precision Constant Current sources give output useful to microampere region



With a constant current source in the lab, you can:

- Evaluate reverse breakdown and forward V-I characteristics of PN junctions
- Measure silicon wafer resistivity and contact resistance
- Test relays, meters, potentiometers, and electrolytic capacitors
- Aid in coulometric titration and precision electroplating
- Determine dynamic and incremental impedance of devices

HP constant current sources supply precisely-regulated (30 ppm) dc current. Three models cover a range of ratings from 1 μA to 0.5A.

You can adjust the constant current output with the high resolution (0.02%) front panel control, or you can program the output current anywhere over an

entire range with an external voltage or resistance. The maximum voltage compliance can also be set with a voltage limit control or by external programming.

These supplies have no output capacitor. Output capacitance is minimized to reduce stored energy at the high impedance output, which along with specialized circuitry, reduces current transients in rapidly changing loads.

A separate monitoring terminal allows external voltage measurement without degrading constant current performance.

For technical data sheet, check J on the HP Reply Card.

Precision performance, low price, small size, and light weight combine to make these supplies useful as general purpose laboratory constant current sources for semiconductor circuit development and component evaluation.

The "Time Standard" Company offers a wide choice of proven precision frequency standards

Hewlett-Packard frequency/time standards in the HP Measurement Standards Lab in Santa Clara, Calif. contribute timekeeping data regularly to both the U.S. Naval Observatory and the U.S. Bureau of Standards.



As a leading manufacturer of cesium, rubidium and quartz standards, we at Hewlett-Packard offer you 35 years of frequency standards experience to help you make an optimum choice.

We can be of special help since many of our several thousands of frequency standards in the field are used in the most reliability demanding areas. These include LORAN C and OMEGA navigation, space vehicle tracking and guidance, satellite communication and basic timekeeping in numerous standards labs and observatories throughout the world.

One of the following precision frequency standards should meet your applications needs.

HP 5061A Cesium Standard

- Primary frequency standard with 7×10^{-12} accuracy (with high performance tube, 0° to 50°C)
 - Proven reliability (MTBF in excess of 40,000 hours)
- Your best choice for superior performance and reliability.

HP 5062C Cesium Standard

- Primary frequency standard with 3×10^{-11} accuracy (-28° to +65°C)
 - Fast warmup (20 min. at -28°C)
 - Rugged construction (passed 400 lb. hammer blow test)
- Your best choice for harsh environments such as mobile naviga-

tion and communications systems.

HP 5065A Rubidium Standard

- Compact and light weight
- Long term stability less than 1×10^{-11} /month
- Short term stability less than 5×10^{-13} , 100 sec. averaging

Your best choice for a secondary atomic standard at a considerably lower price.

HP 105A/B Quartz Oscillator

- High performance economical frequency standard
- Excellent short term stability and spectral purity
- Aging rate less than 5×10^{-10} /day

Your best choice when excellent stability and versatility are needed at lowest cost.

HP 10544A Ovenized Component Oscillator

- Fast warmup
- Excellent aging rate at low cost (less than 5×10^{-10} /day)
- Rugged, compact, reliable

Your best choice for integrating into test and measurement equipment or communication and navigation systems.

For data sheets on all of these instruments, please check F on the HP Reply Card.

New Application Note for Low Input Current, High Gain Isolators

Optically coupled isolators are useful in applications where large common mode signals are encountered. Examples are: line receivers, logic isolation, power lines, medical equipment and telephone lines. This Application Note 951-1 has at least one example in each of these areas for the 5082-4370 series high CTR isolators.

HP's 5082-4370 series isolators contain a high gain, high speed photodetector that provides a minimum current transfer ratio (CTR) of 300% at input currents of 1.6 mA for the -4370 and 400% at 0.5 mA for the -4371. The excellent low input current CTR enables these devices to be used in applications where low power consumption is required and those applications that do not provide sufficient input current for other isolators.

For your free copy, check Q on the HP Reply Card.


HP offers new monolithic LED chips for watch industry

The HP 5082-7800 series are common cathode monolithic chips designed for hybrid applications. Chips are available in seven segment, nine segment, and one digit fonts. Colons are available in discrete or monolithic form.

Four character sizes with a common cathode are available: 53 mil, 80 mil, 100 mil and 120 mil. These are easy to read, MOS compatible and offer an excellent aesthetic appearance.


The chips are packaged on vinyl film or in waffle packages.

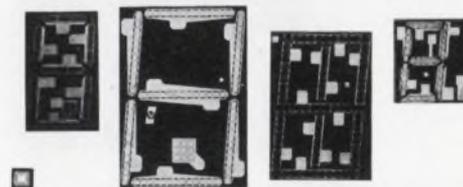For detailed specific technical data, check I on the HP Reply Card.



New low power chips are 100% electrically tested, before shipment, to a high HP standard criteria.

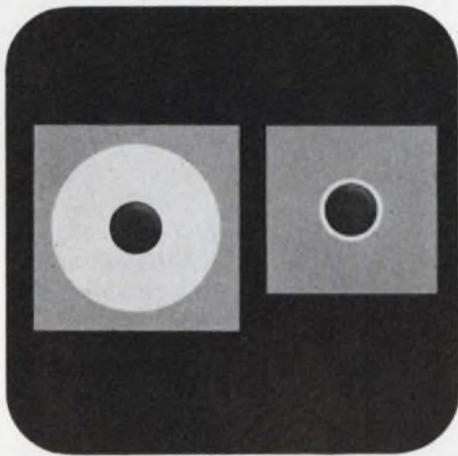New Metal-Insulator-Semiconductor capacitors for microwave IC's



Magnified view of new MIS chip capacitor with oxide-nitride insulator yielding superior reliability.

These new 5082-0900 MIS chip capacitors have been designed for shunt rf bypassing and series dc blocking in amplifiers, oscillators, switches, limiters, mixers and modulators.

Eleven units are offered in the 0.5 to 45 pF range. Capacitance tolerance is $\pm 15\%$. Tolerances to $\pm 5\%$ and values in the 45 to 100 pF range are available on special order. Minimum breakdown voltage for units from 0.5 to 2.0 pF is 250 V; 5.0 to 15 pF—150V; units from 20 to 45 pF—100 volts.

In the MIS structure, the metal is gold, the insulator is silicon nitride over silicon dioxide, and the semiconductor material is silicon.

For a technical data sheet, check G on the HP Reply Card.


Low V_F Schottky mixer diodes for better matching and lower noise

Low forward-voltage equivalents of HP's microwave Schottky diode line are now available. A rating of 200 to 300 millivolts forward drop versus the conventional millivolt droppage of 400 to 500 millivolts is now available in a total of 23 devices including chips, beam leads and quad configurations.

Intended primarily for mixer applications, the low V_F diodes are closer to a 50 ohm impedance than standard Schottky mixer diodes, resulting in lower VSWR over the band. At lower levels of I.o. power, the impedance is equivalent to standard units, a property useful in starved local oscillator mixers.


This new forward voltage rating applies to the following series of components:
 5082-2229 beam lead mixer diodes
 5082-2231 hermetic microstrip quads
 5082-2271 broadband microstrip quads
 5082-2285 hermetic single chip coax packages
 5082-2765 hermetic single chip microstrip packages
 5082-2774 broadband single chip microstrip packages

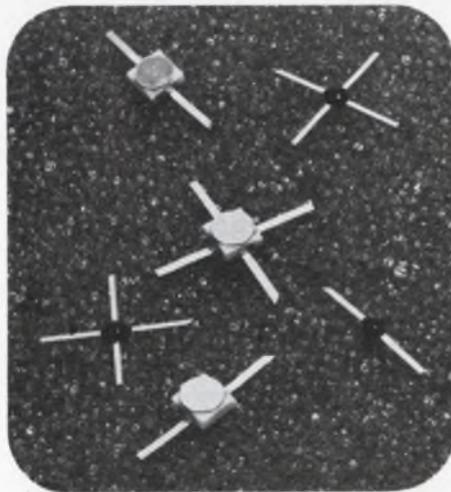For data sheets describing the above products, check H on the HP Reply Card.



Noise figure of low V_F diodes is typically less than 6 dB at 9 GHz for power levels ranging from -5 dBm to +5 dBm.

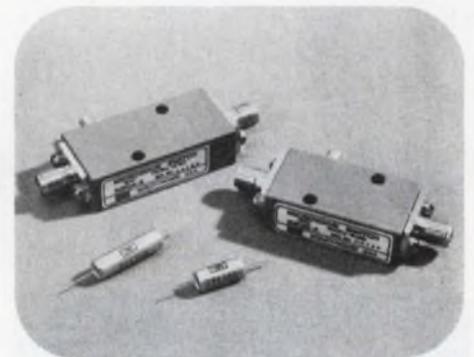Insertion loss reduced by 20% in new SPST microwave switches



These SPST switches use PIN diodes in shunt across a 50 ohm transmission line. Control current for the 33132A/33632A is 30 mA for the 33134A/33634A is 200 mA.

Two new SPST microwave switches reduce insertion loss in X-Band and Ku-Band by 20% over currently available types. The HP 33130 series are complete switches, with RF connector, bias circuits, and built-in dc returns. Model 33132A is a complete 2-diode switch with insertion loss of 1.8 dB max from 12.0 to 18.0 GHz.

The Model 33134A is a complete 4-diode switch with insertion loss of 2.3 dB maximum over the same frequency range.

The basis of the HP SPST switch product line is the coaxial module. The 33600 series module is optimized for low insertion loss with high isolation. The modules are available with either two or four diodes. Three diode units are available on special order.

For a technical data sheet on the 33130 and 33630 Series switches, check P on the HP Reply Card.

A new ultra-low distortion analyzer gives you readings to -90 dB

The Hewlett-Packard 4333A Distortion Analyzer measures total harmonic distortion down to 0.01% full scale at 41 spot frequencies, each variable over a range of more than $\pm 8\%$.

The new 4333A gives you $\pm 3\%$ accuracy over its entire 10 Hz to 100 kHz range.

The 4333A is easy to use. Automatic fundamental nulling reduces critical manual nulling operations. Select your measurement range in 10 dB steps and read distortion directly on the large, clearly marked panel meter. A front-

panel monitor output lets you conveniently analyze the harmonic distortion using a scope or recorder.

A high sensitivity voltmeter mode offers 13 ranges in 10 dB steps; range is from 100 μV to 100 V rms full scale.


When you need believable amplifier or oscillator distortion measurements, rely on the 4333A.

For more information, check E on the HP Reply Card.



New distortion analyzer with distortion input sensitivity of 1 Vrms for 100% set level reference.

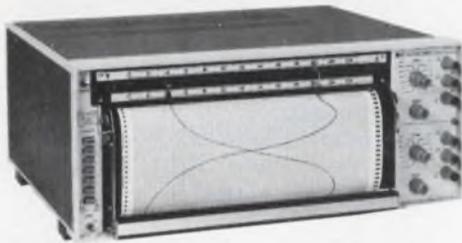Inkless writing for HP strip chart recorders



New thermal writing option produces a crisp, uniform trace.

For the first time, thermal writing is available for a series of Hewlett-Packard strip-chart recorders. Models 7130A and 7131A, one and two-pen, 10-inch OEM recorders can be equipped with thermal writing pens and event markers for long-term, unattended operation. Models 7132A and 7133A, laboratory versions, can be similarly equipped.

Each thermal tip contains a temperature sensing element used to maintain a constant tip temperature. The tip

temperature is therefore independent of ambient temperature, paper speed, etc.

Designated Option 054, the inkless system includes beryllium-tipped pens designed to last the lifetime of the instrument. Recordings are of high contrast and are easy to read.

For more details, check K on the HP Reply Card.

New Application Note helps match microwave frequency counters to measurement requirements


At one time there weren't many microwave frequency counters from which to choose. Now, there are a variety of these counters available with varying degrees of sophistication in design and measurement capability. The new Hewlett-Packard Application Note 144, "Understanding Microwave Frequency Measurement" discusses tradeoffs between microwave frequency counter designs which merit consideration when choosing a counter for a particular application.

The Application Note discusses in detail considerations of measurement

speed, accuracy, dynamic range, and tolerance to modulations and unwanted noise on the signal for each of the three common down-conversion techniques: prescale, heterodyne, and transfer oscillator. It also suggests other useful considerations such as input characteristics, sensitivity, and input/output structure.

The booklet should prove useful to the microwave engineer in selecting a frequency counter to meet his needs.

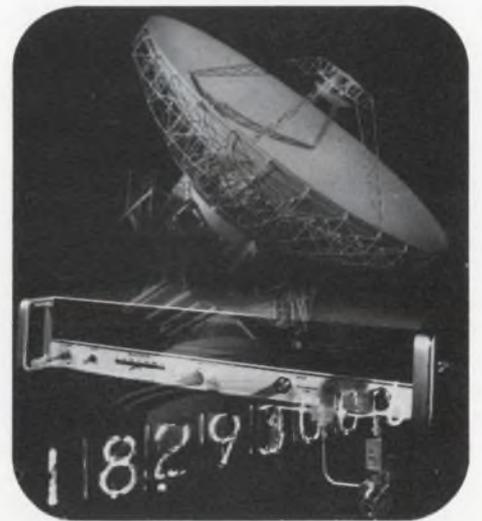
For your free copy of this Application Note, check N on the HP Reply Card.



The successful 5340A Frequency Counter represents one of several designs described in the new AN 144, "Understanding Microwave Frequency Measurement".

HP high resolution CRT displays for OEM applications

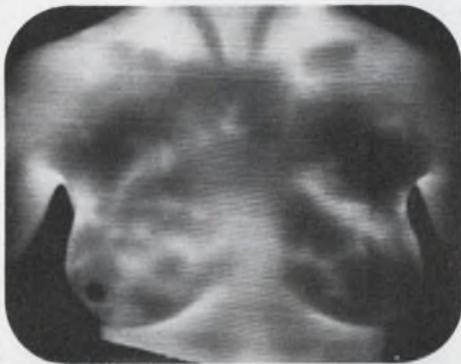
The CRTs in these displays have a totally new design, optimized exclusively for information display and to reproduce fine image detail with superior contrast and uniformity.



Stable light output for long scan periods permits time exposure photograph to paint a picture of body temperature versus location in a medical thermography application.


Hewlett-Packard's Models 1332A, 1333A, and 1335A CRT displays are designed to provide excellent images in all types of OEM systems. Applications for these displays include spectrum, network and chemical analyzers, nuclear medicine, medical thermographic ultrasound, and automatic test systems, among others.

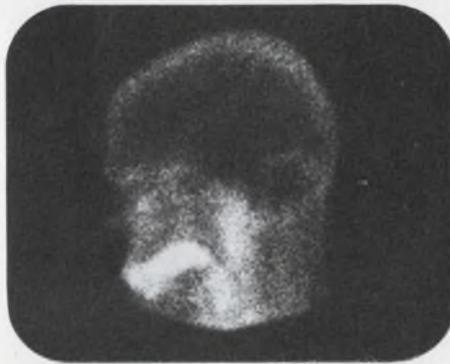Model 1332A is designed for the OEM that has both visual and some photographic requirements. CRT display parameters are optimized for such a combined application including large 9.6×11.9 cm viewing area. Display brightness is such that it can be viewed in high ambient light conditions while maintaining resolution and gray shades for photographic work.



The 1333A CRT is optimized for photographic image quality with a wide range of gray shades, contrast, and uniformity as shown in this high resolution gamma camera brain scan.

Model 1333A is designed specifically for applications in which photographic recording of displays is the major factor. The small spot size of 0.20 mm offers exceptional image quality that makes evaluation of photographs easier and more accurate. A specified light output uniformity assures that the display information is an accurate representation of the input signals. The high resolution CRT display qualities make the 1333A ideal for recording rapid sequence dynamic studies in nuclear medicine and for capturing transient displays in ultrasound work. The 8×10 cm screen can be reproduced on Polaroid® film with very little optic reduction which allows the use of almost 1:1 optics and minimizes design difficulties encountered when using enlarging or reducing optics.

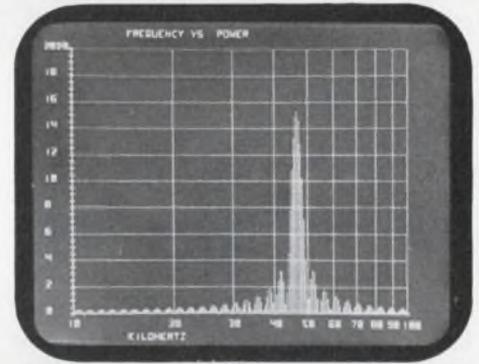

Fine image detail and a well-focused spot at all intensity levels make the 1335A ideal for use in Spectrum, Fourier, Network, and Chemical analysis as well as automatic test systems.

For applications requiring variable persistence and storage, the 1335A offers exceptional uniformity needed in OEM medical and instrumentation systems. The variable persistence mode can be used to eliminate flicker on some presentations with the ability to increase persistence to match the refresh rate. In the storage mode, resolution is over 20 lines per cm (50 lines per in.) permitting the retention of sharp details. For maximum flexibility, any operating mode—erase, store, write, conventional, or variable persistence—can be selected with manual front panel controls, remote program inputs, or a combination of both.

For detailed specifications on these CRT displays, Check C on the HP Reply Card.

Buy the HP-65 now* and get \$195 worth of proven software FREE

During this special promotion, purchasers of Hewlett-Packard's HP-65 fully programmable pocket calculator will receive FREE with the calculator, a \$195 coupon for the delivery of 4 Application Pacs and 5 Users' Library Programs of their choice. The promotion runs through April 30, 1976.

There are 14 Application Pacs currently available in electrical engineering, finance, mathematics, statistics, medicine, navigation, aviation, surveying, machine design, stress analysis and chemical engineering. You may choose any four of these Pacs, each containing up to 40 pre-recorded programs from that particular discipline.

In addition, each purchaser will be able to choose five of 15 popular programs from the HP-65 Users' Library of contributed programs. Each of these programs includes a complete keystroke listing, user instructions and supporting documentation. The entire library listing, available to HP-65 owners, contains more than 4000 contributed programs.


Software is the difference that sets our HP-65 Fully Programmable apart from all other calculators. This hardware/software combination permits the HP-65 to remain the most versatile hand-held computing system available. Like a computer, the HP-65 memorizes programs of any size that are fed into



it on tiny magnetic cards, 100 program steps to a card. With just a few keystrokes by the user, it executes the program and gives the answer to complex problems with an accuracy of up to 10 digits. Five User Definable keys plus 51 preprogrammed functions and operations plus a superior editing capability add up to "a great deal".

Call, toll-free, 800-538-7922 (in Calif. 800-662-9862) for an HP dealer near you so that you can take advantage of this special \$195 software offer before April 30, 1976.

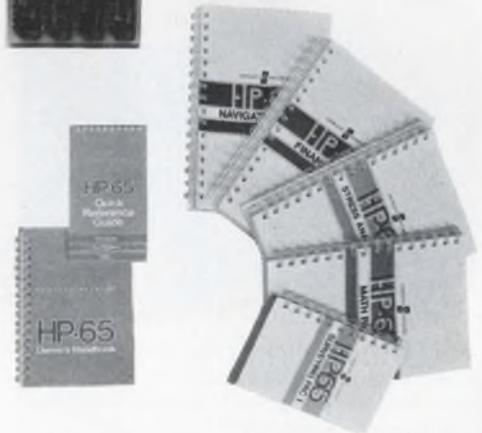For descriptive literature only, check A on the HP Reply Card.




*Offer valid until April 30, 1976 in continental U.S.A., Alaska and Hawaii.



East-4 Choke Cherry Road, Rockville, MD 20850
Ph. (301) 948-6370.
South-P.O. Box 28234, Atlanta, GA 30328,
Ph. (404) 434-4000.
Midwest-5500 Howard Street, Skokie, IL 60076,
Ph. (312) 677-0400.
West-3939 Lankershim Blvd, North Hollywood, CA
91604, Ph. (213) 877-1282.
Europe-P.O. Box 349, CH-1217 Meyrin 1, Geneva,
Switzerland, Ph. (022) 41 54 00.
Canada-6877 Goreway Drive, Mississauga, Ontario,
L4V 1L9, Ph. (416) 678-9430.
Japan-Yokogawa-Hewlett-Packard Ltd., Ohashi
Bldg., 59-1 Yoyogi, 1-chome, Shibuya-ku,
Tokyo 151, Ph. 03-370-2281/92.

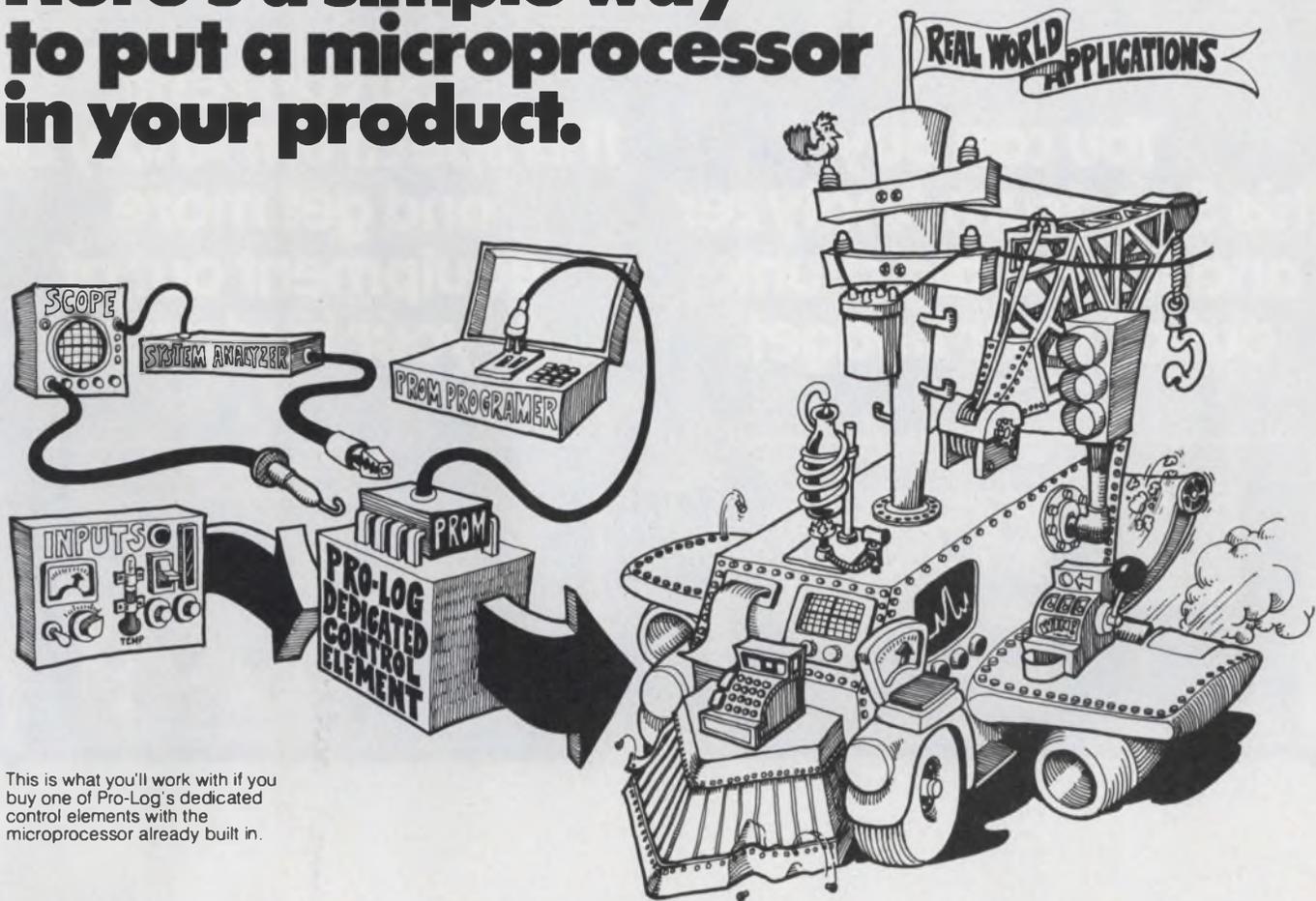Here's a simple way to put a microprocessor in your product.



This is what you'll work with if you buy one of Pro-Log's dedicated control elements with the microprocessor already built in.

Buy a dedicated control element, for all practical purposes a black box, with a microprocessor already built in.

We've developed subsystems using microprocessors. They come in modular configurations readily expandable to meet your product requirements. You hardwire them directly to relay contacts, switches, push buttons, displays or other real-world devices. They give you all the capabilities of a microprocessor with none of the headaches. And we deliver them in a matter of weeks.

When you use our subsystems, we give you the kind of production and documentation assistance that results in a product your present manufacturing people can build and your present service force can support.

And system design stays with the design engineer.

Plus, we give you something more, a free set of plans and a second source.

Order 250 subsystems and we'll throw in free non-exclusive manufacturing rights and a complete set of manufacturing and assembly plans allowing you to build your own hardware, relying on us as an established and dependable second source.

We make everything you need to design with microprocessors.

Our starter sets include a microprocessor subsystem, a Series 90 PROM programmer, a microprocessor system analyzer, plus all associated hardware. 4-bit sets cost around \$3,000, 8-bit sets around \$3,500, a substantial savings over what you'd pay if you purchased all these items separately.

We have education too.

Our half-day introductory seminar takes a hard look at the function of microprocessors in real-world applications.


Our three-day hands-on design course teaches engineers how to formulate, program and use microprocessor modules.

Our free booklet, "The Microprocessor User's Guide" answers all your questions.

It explains what a microprocessor is, what it's capable of doing, what criteria you need to evaluate the ones on the market and how Pro-Log can help you put them to best use. Write for your copy.

To show how much Pro-Log can save you both in time and money, consider this. We've got a one-card 4004-based system called the PLS-401A. It includes a microprocessor; crystal controlled clock; 16 lines of TTL input; 16 lines of TTL output; sockets for 1024 words of program memory; 80-character RAM and built-in power-on reset. It costs only \$99 in quantities above 500 (\$175 in quantities of 10.) How long would it take, and what would it cost you to design and build something in-house that could do the same job?

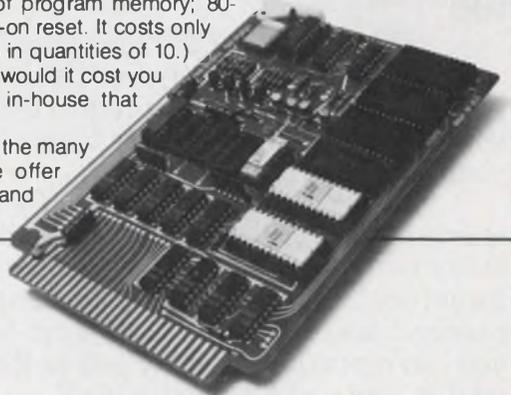And this is just one example of the many microprocessor subsystems we offer using 4004, 4040, 8008, 8080, and 6800 microprocessors.



PRO-LOG CORPORATION
2411 Garden Road
Monterey, CA 93940
Telephone (408) 372-4593
TWX 910-360-7082

CIRCLE NUMBER 7

**You can buy
this Spectrum Analyzer
and take a big chunk
out of your budget.**

**You can rent
this Spectrum Analyzer
and get more
equipment out of
your budget.**



Even the best equipment budget can only go so far. And at the price you pay for electronic test equipment nowadays, that's not very far at all.

Unless you rent your equipment from REI.

When you rent from us, there's no large cash outlay. You pay only for the time you have your instruments, and you return them when you're through. So you never have to spend your money on idle equipment.

Getting more for your money is just one reason for renting from REI. Immediate delivery is another. We have over \$10 million in inventory in fully stocked centers around the country. And, when you have short-term needs, you can rent equipment for just as long as you need it, and make it pay for itself.

REI stocks over 8,000 fully checked-out test instruments, and they're ready whenever you are. For the full story on renting, as well as our low prices, send in the coupon for prompt delivery of our free illustrated catalog . . . or call us now for your immediate requirements.

Rental Electronics, Inc.
99 Hartwell Avenue, Lexington, Mass. 02173
Please send me your free instrument rental catalog:

Name _____ Title _____

Company _____

Address _____

City _____ State _____ Zip _____

Tel. Number _____

Rental Electronics, Inc. 

A PERSCO LEASING COMPANY

Burlington, MA (617) 273-2770 • Gaithersburg, MD (301) 948-0620 • Oakland, NJ (201) 337-3757 • Ft. Lauderdale, FL (305) 771-3500
• Des Plaines, IL (312) 827-6670 • Dallas, TX (214) 661-8082 • Mountain View, CA (415) 968-8845 • Anaheim, CA (714) 879-0561
• Rexdale, Ontario (PLC Leasing Ltd.) (416) 677-7513

See us at Booth #2702 at Electro 76 May 11-14 Bicentennial IEEE Show in Boston

CIRCLE NUMBER 8

MARCH 29, 1976

Data General's μ P-based mini extends its Nova line

A downward-compatible minicomputer system based on a 16-bit microprocessor has been announced by Data General. Known as the microNova family, the system is available as a full minicomputer, a single central-processing-unit board with 4-k words of memory or as individual CPU, memory and support chips.

"An original-equipment manufacturer can start out with a fully packaged microNova minicomputer, then integrate downward into microNova boards or chips as his development time or product volume allow, without having to re-design hardware or software," says Engineering Vice President Carl Carman.

Since the microNova is completely software-compatible with the company's line of Nova minicomputers an extensive library of software already exists to support the new family.

Included among major competitors who have introduced their own compatible families of μ Cs through full minicomputers are Digital Equipment Corp., with the LSI-11; Texas Instruments with the 990 Series. Of course, there are several suppliers of monolithic 16-bit MOS chips—notably General Instrument and National Semiconductor.

"In a way, each of these products can satisfy a part of the market," says Data General's Herb Richman, "but in other ways they fall short because they're lacking in product-line breadth, software or other forms of support."

All of the microNova chips are produced by Data General at its plant in Sunnyvale, CA. The CPU has common address and data pins and is designed for use with the company's 20-pin dynamic RAMs. Separate refresh circuitry is not required by the CPU because it has an integral refresh cycle.



The microNova family consists of chip set, board computer and fully packaged minicomputer.

There are two separate serial I/O lines on the chip and a real-time clock. Other chips available to complete the system are an I/O controller to decode a 16-Mb/s data stream for communication with peripheral devices, address-buffer elements, data-line buffers and memory-sense amplifier/buffer chips.

The microNova minicomputer is available fully packaged with a separate calculator-like control panel attached to the main unit by a long flexible cable. Nine-slot and 18-slot versions, each slot having 32-k memory capacity, allow plenty of program storage.

In a complete system including the microNova minicomputer, diskette and ASCII terminal, development software is available at no extra cost.

Software such as a disc operating system, text editor, Fortran IV compiler, assembler, relocatable loader and symbolic debugger provide complete support for developing anything from a fully customized system to a dedicated system using the chip set.

The CPU chip mN601 sells for \$225 (single quantities) and \$95

(500 quantities); the microNova CPU/4k single-board minicomputer with 4-k words of memory costs \$950 (single quantities).

CIRCLE NO. 319

Listen to the sound: the part is corroding

It used to be that listening to corrosion was like watching grass grow. A sensitive electronic listening device can now tune in on corrosion and catch it red-handed. The computer controlled instrument can locate and measure corrosion deep within the bowels of a piece of machinery, inside the wing of an aircraft or even inside an integrated circuit package.

"We look at it as an acoustic previewing of failures," says Allen Green, general manager of Acoustic Emission Technology Corp. in Sacramento, CA. Corrosion is a chemical reaction that usually gives off a minute amount of hydrogen gas. The gas bubbles off like boiling water. The bubbling action gives off a very small level of sound that can be detected in the 100-kHz to 2-MHz window in the ultrasonic spectrum. By listening with an extremely sensitive receiver to the acoustic energy in that portion of the spectrum, corrosion can be detected in a non-destructive way before a failure occurs.

A single piezoelectric sensor is first placed on the item of interest. The signal from the sensor is connected to a preamplifier with an rms noise threshold of about 800 nV, then filtered so specific octave-wide bands of frequencies are looked at individually.

When a sound is detected, additional sensors are placed on the item of interest and readings are taken by each. An LSI-2 computer from Computer Automation, Irvine, CA, analyzes the data from the sensors and, by triangulation, calculates the exact position of the corrosion.

If the signal is too small for an accurate reading, the part can be heated. Green notes that a 10 to 18-F increase in temperature doubles the reaction rate of the corrosion and, therefore, also doubles the level of the sound given off.

When multiple sensors are used the propagation of the reaction

can be plotted by the computer as a function of time.

Lockheed-California Co. in Burbank, CA, is using the equipment for structural analysis of aircraft.

The equipment can detect micrograms of loose material inside integrated circuit packages, Green says. He notes that the technique has been used to find the cause of failures where X-rays and other methods failed.

An improved Schottky diode tests for ozone

Chemical elements that are believed to be responsible for depleting the earth's atmospheric ozone layer can now be detected more precisely using an improved Schottky-barrier diode.

These chemicals in the stratosphere signal their presence by emitting electromagnetic radiation of very precisely defined frequencies (in the 115-to-118-GHz and 183-to-184-GHz ranges).

The improved, low-noise diode developed by Dr. Robert Mattauca, Associate Professor of Electrical Engineering at the University of Virginia, Charlottesville, VA, is used as a millimeter-wave mixer in a sensitive receiver to detect these frequencies.

Tests to measure trace gases like N₂O and ozone have already been conducted by sensitive receivers in aircraft using these new diodes up to 40,000 ft. More tests are scheduled for June.

The diodes, measuring only 10⁻⁴ in. in diameter, are formed on a single gallium arsenide chip 5 × 10 mils in area and 5 mils thick. The small size of the diodes allows a large number of them to be placed on a single chip, although only one of them is actually used as the mixer.

Color-TV picture tube is better and cheaper

A color-TV picture tube that can be manufactured by a fully automated facility has been developed by Zenith Radio and Corning Glass. The tube will cost 20% less to produce and have improved performance.

The tube is built with a deflection angle of 100°, which "provides a desirable combination of styling, power consumption and picture quality advantages," according to Joseph P. Fiore, Zenith's vice president of manufacturing and co-inventor of the Chromacolor picture tube.

The depth of the tube was reduced 2-1/2 in. Resolution was improved by using a smaller electron-beam spot size. And power consumption was held down because the 100° tube uses the same deflection-drive power components used in a 90° unit.

The tube is built with a striped, negative-guard-band phosphor screen. A slot-aperture mask assembly designed by Zenith engineers reduces mask weight by over 2 lb and eliminates the glass skirt around the edge of the faceplate. The aperture mask is held rigid by studs in the four corners of the faceplate panel.

Multistage mask-forming dies are used to accomplish a stable, self-supporting mask that eliminates the conventional frame.

Mask-mounting studs may be precision-located and cemented to the inside face of the tube by an automated process said to be simpler than the stud-mounting and alignment system currently used.

The same mounting studs may be used for automatic precision alignment of the faceplate to the funnel. That eliminates the requirement for precision alignment fixtures now used during the tube-sealing operation. The technique is said to increase alignment accuracy and improve production yields.

The mask is built with an integral electron shield to protect the screen from stray or overscanned electrons. This eliminates the need for a separate shield.

"One of the most important features of the design," Fiore adds, "is the ease of mask insertion and removal. Automation of these operations is now possible using simple equipment."

Zenith is banking on the new picture tube to remain competitive with foreign set makers, which have doubled their share of the market in the past four years.

The company plans to manufacture about 200,000 of the tubes this year.

Army opens \$40-million missile flight simulator

A complex of simulators that can recreate virtually any man-made or natural phenomena that a missile might encounter in flight has been opened at the Army's Redstone Arsenal, Huntsville, AL. The \$40-million facility will be used by all branches of the military and their contractors in the design, development and evaluation of missile systems. It will also provide a tool for analyzing foreign weapons.

The three-story, 75,000 ft² Advanced Simulation Center consists of three environmental simulation systems (infrared, electro-optical and radio frequency) and a hybrid computer complex to tie them together.

The center enables a designer to test sensors, guidance-and-control components and flight hardware. Simulations are performed across a wide frequency spectrum, from near ultraviolet through microwave, with expansion capabilities inherent in the design.

One simulator accommodates missiles with sensor systems operating in both the 0.2 to 0.4 and 1.0 to 5.0-micron bands. The sensors are controlled by a hybrid computer in six degrees-of-freedom while the target is being acquired.

The gimballed flight table provides pitch, yaw and roll movements to the sensor airframe. A target generator simulates a variety of target background combinations, including tailpipes, plumes, flares and fuselages in single or multiple displays against clear, clouded, overcast or sunlit skies.

These combinations are then displayed in azimuth, elevation, range and aspect by the target projection subsystem through a folded optical network, a display arm and a display mirror. Simulation capability ranges from open-loop component evaluation to closed-loop total-system simulation.

"Millions of dollars each year will be saved in research and development and actual flight tests," according to an Army spokesman. The center will also reduce significantly the time and manpower required to develop a missile system.

We saw your microprocessor

coming. So we designed an entire family of socket homes for it. Socket cards for card file mounting, and we've even got the card files. Socket boards for LSI mounting in frames, drawers, and racks,

and we've even got the frames, drawers, and racks. Our socket cards, the 3D Series, come with built-in test points, a ceramic monolithic bypass capacitor

at each socket, and solder tab connection to pins on LSI chips. Our socket boards, the 2D Series,

offer a good selection of socket complements, and are compatible with other boards for hybrid installations. We also offer automated wiring service. We're ready for you.



EECO

PACKAGING/SWITCHES/READERS

1441 East Chestnut Avenue, Santa Ana, California 92701 Phone 714/835-6000
Also stocked and serviced in North America by G. S. Marshall, R-A-E, Zentronics.

Ceralam® Chips. When you're on the outside looking in.

If you're looking at ways to put more capacitance into a microcircuit, look into Ceralam chips. Because they're ceramic, they have the volumetric efficiency necessary for microcircuit applications. So you can package a lot of capacitance. Even when you're short on space. Because they're made by the leader in multilayer technology, AVX chips deliver the performance needed in your

most demanding applications. They're tested for physical, electrical, environmental characteristics repeatedly during production. Qualified to AVX's demanding specifications. So you can adhere to yours.

Ceralam chips also make bonding easy. They're available in a variety of terminating materials, so you won't have to introduce changes into existing designs. And they

can be supplied with special terminations. Like AVX's exclusive alloy NiGuard®. A material that eliminates the need for preforms and wire bonding. And prevents base metal bleed through and silver migration.

If you've been looking around for the right kind of capacitors for your microcircuit designs, settle on Ceralam chips. They'll make an insider out of you.

AVX: The Insiders

AVX Ceramics, P.O. Box 867, Myrtle Beach, SC 29577 (803) 448-3191 TWX: 810-661-2252
Olean, NY (716) 372-6611 TWX: 510-245-2815

Specifications

*10 physical sizes
Capacitance Range:
1pf to 1.5 mfd
Voltages:
100, 50, 25
Three temperature
characteristics
Four available
terminations*




AVX Distributors: Cramer Electronics, Inc./Elmar-Liberty Electronics
Jaco Electronics, Inc./Newark Electronics/Texas Instrument Supply

CIRCLE NUMBER 10

Motorola Turns On 4K RAM Availability

We keep hearing of 4K RAM delivery problems, particularly with popular 16-pin types. Well, forget that. With Motorola's totally turned-on 4K RAM production at the Austin, Texas facility, availability is the word for 4Ks. Availability of the 16-pin MCM6604 and the 22-pin MCM6605A.

Let Motorola eliminate the 4K RAM hassle for you, today . . . and with inflation beating low prices, at that.

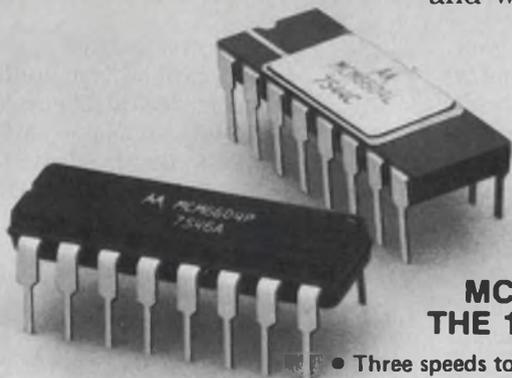

**MCM6604—
THE 16-PIN 4K**

- Three speeds to choose from
- Recognized industry standard
- Directly replaces 2104, MK4096, 4096, S4096
- Small package optimizes system density



MCM6605A — THE 22-PIN 4K

- 2.5 mW standby . . . Ideal for battery backup
- Three speed choices — down to 150 ns
- Alternate sourced by IM7505 Series
- Documented Reliability — Ask us for a copy

Motorola Semiconductor Products Inc., MOS Memory Marketing,
3501 Ed Bluestein Avenue, Austin, Texas 78721

COME AND GET 'EM...FROM THESE AUTHORIZED MOTOROLA DISTRIBUTORS

| | | | | | |
|------------------------------|---------------------------------|----------------|-------------------------------|------------------------------------|----------------|
| ALABAMA, Huntsville | Hall-Mark Electronics | (205) 837-8700 | NEW JERSEY, Pennsauken | Radio Electric Service Co. | (609) 662-4000 |
| ALABAMA, Huntsville | Hamilton/Avnet Electronics | (205) 533-1170 | NEW JERSEY, Saddle Brook | Arrow Electronics | (201) 797-5800 |
| ARIZONA, Phoenix | Hamilton/Avnet Electronics | (602) 275-7851 | NEW JERSEY, Somerset | Schweber Electronics | (201) 469-6008 |
| ARIZONA, Phoenix | Liberty Electronics/Arizona | (602) 257-1272 | NEW MEXICO, Albuquerque | Hamilton/Avnet Electronics | (505) 765-1500 |
| CALIFORNIA, El Segundo | Liberty Electronics Corp. | (213) 322-8100 | NEW YORK, Farmingdale | Arrow Electronics | (516) 694-6800 |
| CALIFORNIA, Irvine | Cramer/Los Angeles | (213) 771-8300 | NEW YORK, Hauppauge, L.I. | Cramer/Long Island | (516) 231-5600 |
| CALIFORNIA, Los Angeles | Hamilton Electro Sales | (213) 558-2121 | NEW YORK, Rochester | Cramer/Rochester | (716) 275-0300 |
| CALIFORNIA, Mountain View | Eimar Electronics, Inc. | (415) 961-3611 | NEW YORK, Rochester | Hamilton/Avnet Electronics | (716) 442-7820 |
| CALIFORNIA, Mountain View | Hamilton/Avnet Electronics | (415) 961-7000 | NEW YORK, Rochester | Schweber Electronics | (716) 461-4000 |
| CALIFORNIA, San Diego | Hamilton/Avnet Electronics | (714) 279-2421 | NEW YORK, East Syracuse | Cramer/Syracuse | (315) 437-6671 |
| CALIFORNIA, San Diego | Liberty Electronics/San Diego | (714) 565-9111 | NEW YORK, East Syracuse | Hamilton/Avnet Electronics | (315) 437-2642 |
| CALIFORNIA, Sunnyvale | Cramer/San Francisco | (408) 739-3011 | NEW YORK, Westbury, L.I. | Hamilton/Avnet Electronics | (516) 333-5800 |
| COLORADO, Commerce City | Eimar Electronics, Inc. | (303) 287-9611 | NEW YORK, Westbury, L.I. | Schweber Electronics | (516) 334-7474 |
| COLORADO, Denver | Hamilton/Avnet Electronics | (303) 534-1212 | NEW YORK, Woodbury, L.I. | Harvey Electronics | (516) 921-8700 |
| CONNECTICUT, Danbury | Schweber Electronics | (203) 792-3500 | NORTH CAROLINA, Winston-Salem | Cramer/Winston-Salem | (919) 725-8711 |
| CONNECTICUT, Georgetown | Hamilton/Avnet Electronics | (203) 762-0361 | OHIO, Beachwood | Schweber Electronics | (216) 464-2970 |
| CONNECTICUT, North Haven | Cramer/Connecticut | (203) 239-5641 | OHIO, Cleveland | Hamilton/Avnet Electronics | (216) 461-1400 |
| FLORIDA, Hollywood | Hamilton/Avnet Electronics | (305) 925-5401 | OHIO, Cleveland | Pioneer-Standard Electronics, Inc. | (216) 587-3600 |
| FLORIDA, Hollywood | Schweber Electronics | (305) 927-0511 | OHIO, Dayton | Hamilton/Avnet Electronics | (513) 433-0610 |
| FLORIDA, Orlando | Cramer/Orlando | (305) 894-1511 | OHIO, Dayton | Pioneer/Dayton | (513) 236-9900 |
| GEORGIA, Atlanta | Cramer/Atlanta | (404) 448-9050 | OHIO, Solon | Cramer/Cleveland | (216) 248-8400 |
| GEORGIA, Norcross | Hamilton/Avnet Electronics | (404) 448-0800 | OKLAHOMA, Tulsa | Hall-Mark Electronics | (918) 835-8458 |
| ILLINOIS, Chicago | Newark Electronics Corp. | (312) 638-4411 | PENNSYLVANIA, Philadelphia | Pioneer/Philadelphia | (215) 674-5710 |
| ILLINOIS, Chicago | Semiconductor Specialists, Inc. | (312) 279-1000 | PENNSYLVANIA, Pittsburgh | Pioneer/Pittsburgh | (412) 782-2300 |
| ILLINOIS, Elk Grove Village | Schweber Electronics | (312) 593-2740 | SOUTH CAROLINA, Columbia | Dixie Radio Supply Company, Inc. | (803) 779-5332 |
| ILLINOIS, Mt. Prospect | Cramer/Chicago | (312) 593-8230 | TEXAS, Dallas | Hall-Mark Electronics Corp. | (214) 231-6111 |
| ILLINOIS, Schiller Park | Hamilton/Avnet Electronics | (312) 678-6310 | TEXAS, Dallas | Hamilton/Avnet Electronics | (214) 661-8661 |
| INDIANA, Indianapolis | Graham Electronics Supply, Inc. | (317) 634-8202 | TEXAS, Dallas | Schweber Electronics | (214) 661-5010 |
| INDIANA, Indianapolis | Pioneer/Indianapolis | (317) 849-7300 | TEXAS, Dallas | Sterling Electronics | (214) 357-9131 |
| KANSAS, Lenexa | Hall-Mark Electronics | (913) 888-4747 | TEXAS, El Paso | Midland Speciality Co. | (915) 533-9555 |
| KANSAS, Lenexa | Hamilton/Avnet Electronics | (913) 888-8900 | TEXAS, Houston | Hall-Mark Electronics | (713) 781-6100 |
| MARYLAND, Rockville | Cramer/Washington | (301) 948-0110 | TEXAS, Houston | Hamilton/Avnet Electronics | (713) 526-4561 |
| MARYLAND, Gaithersburg | Pioneer/Washington Electronics | (301) 948-0710 | TEXAS, Houston | Sterling Electronics, Inc. | (713) 627-9800 |
| MARYLAND, Hanover | Hamilton/Avnet Electronics | (301) 796-5000 | UTAH, Salt Lake City | Cramer/Utah | (801) 487-4131 |
| MARYLAND, Rockville | Schweber Electronics | (301) 881-3300 | UTAH, Salt Lake City | Hamilton/Avnet Electronics | (801) 262-8451 |
| MARYLAND, Savage | Pytronic Industries, Inc. | (301) 792-7000 | WASHINGTON, Bellevue | Hamilton/Avnet Electronics | (206) 746-8750 |
| MASSACHUSETTS, Burlington | Hamilton/Avnet Electronics | (617) 273-2120 | WASHINGTON, Seattle | Almac/Strom Electronics | (206) 763-2300 |
| MASSACHUSETTS, Lexington | Harvey Electronics | (617) 861-9200 | WASHINGTON, Seattle | Liberty Electronics Corp. | (206) 763-8200 |
| MASSACHUSETTS, Newton Centre | Cramer Electronics, Inc. | (617) 969-7700 | | | |
| MASSACHUSETTS, Waltham | Schweber Electronics | (617) 890-8484 | CANADA | | |
| MICHIGAN, Detroit | RS Electronics | (313) 491-1012 | CALGARY, T2E 6L7 Alta | Varah's Electric | (403) 276-8818 |
| MICHIGAN, Livonia | Hamilton/Avnet Electronics | (313) 522-4700 | EDMONTON, Alta | Bowtek Electric | (403) 426-1072 |
| MICHIGAN, Livonia | Pioneer/Detroit | (313) 525-1800 | LONDON, Ont. | CM Peterson Co. Ltd. | (519) 434-3204 |
| MINNESOTA, Eden Prairie | Schweber Electronics | (612) 941-5200 | MISSISSAUGA, Ont. | Hamilton/Avnet | (416) 677-7432 |
| MINNESOTA, Edina | Cramer/Minneapolis | (612) 835-7811 | OTTAWA, Ont. | Zenitronics, Ltd. | (613) 238-6411 |
| MINNESOTA, Edina | Hamilton/Avnet Electronics | (612) 941-3801 | OTTAWA, K2C 2B4 Ont. | Hamilton/Avnet Int'l. Ltd. | (613) 262-1700 |
| MISSOURI, Hazelwood | Hamilton/Avnet Electronics | (314) 731-1144 | ST. LAURENT, P.O. H4S 1G2 | Hamilton/Avnet | (514) 331-6443 |
| MISSOURI, St. Louis | Hall-Mark Electronics | (314) 291-5350 | TORONTO, Ont. | Zenitronics, Ltd. | (416) 787-1271 |
| NEW JERSEY, Cedar Grove | Hamilton/Avnet Electronics | (201) 239-0800 | TOWN OF MOUNT ROYAL, P.O. | Zenitronics, Ltd. | (514) 735-5361 |
| NEW JERSEY, Cherry Hill | Cramer/Pennsylvania | (609) 424-5993 | VANCOUVER, B.C. | Bowtek Electric | (604) 736-1141 |
| NEW JERSEY, Mt. Laurel | Hamilton/Avnet Electronics | (609) 234-2133 | VANCOUVER, B.C. | Varah's | (604) 873-3211 |
| NEW JERSEY, Moorestown | Arrow Electronics | (609) 235-1900 | WINNIPEG, Man. | Bowtek Electric | (204) 786-7521 |



MOTOROLA MOS

—where 4K RAM means availability

AT THE INTERNATIONAL SOLID-STATE CIRCUITS CONFERENCE

Dynamic RAMs reach 16-k density —and touch off a memory battle

"Users are being dragged kicking and screaming into the 16-k race without first getting really good 4-ks."

That statement was voiced by one participant in the 1976 International Solid-State Circuits Conference in Philadelphia. It was echoed repeatedly by memory-system designers and even by some memory manufacturers.

The occasion was the unveiling of the first 16,384-bit dynamic MOS RAM, an Intel development soon to reach the market (see

product feature in this issue, p. 101). But users and manufacturers alike were far from unanimous on Intel's claim that its approach was the right one. Dissent came especially on the matter of an output-data latch, the number of refresh cycles and the chip's power dissipation.

In a private meeting organized by J. Reese Brown, a Burroughs senior staff engineer, users and vendors clashed over the relative merits of Intel's new n-channel memory. Also contested were other approaches to be used by other memory makers, most of whom plan a 16-k entry by year's end.

For memory users, the ominous


lack of agreement signified a new round of frustrations not unlike those that many feel still envelop present 4096-bit dynamic MOS RAMs (see "4-k RAM Race Still Wide Open as Designers Try Different Paths," ED No. 6, Mar. 15, 1975, p. 26).

The 16-k bit RAM battle

At the heart of the 16-k-RAM debate is the extent to which different manufacturers seek to duplicate some of the features of current 4-k RAMs housed in 16-pin DIPs.

This kind of package for 16-k RAMs is one of the few areas of

Edward A. Torrero
Associate Editor

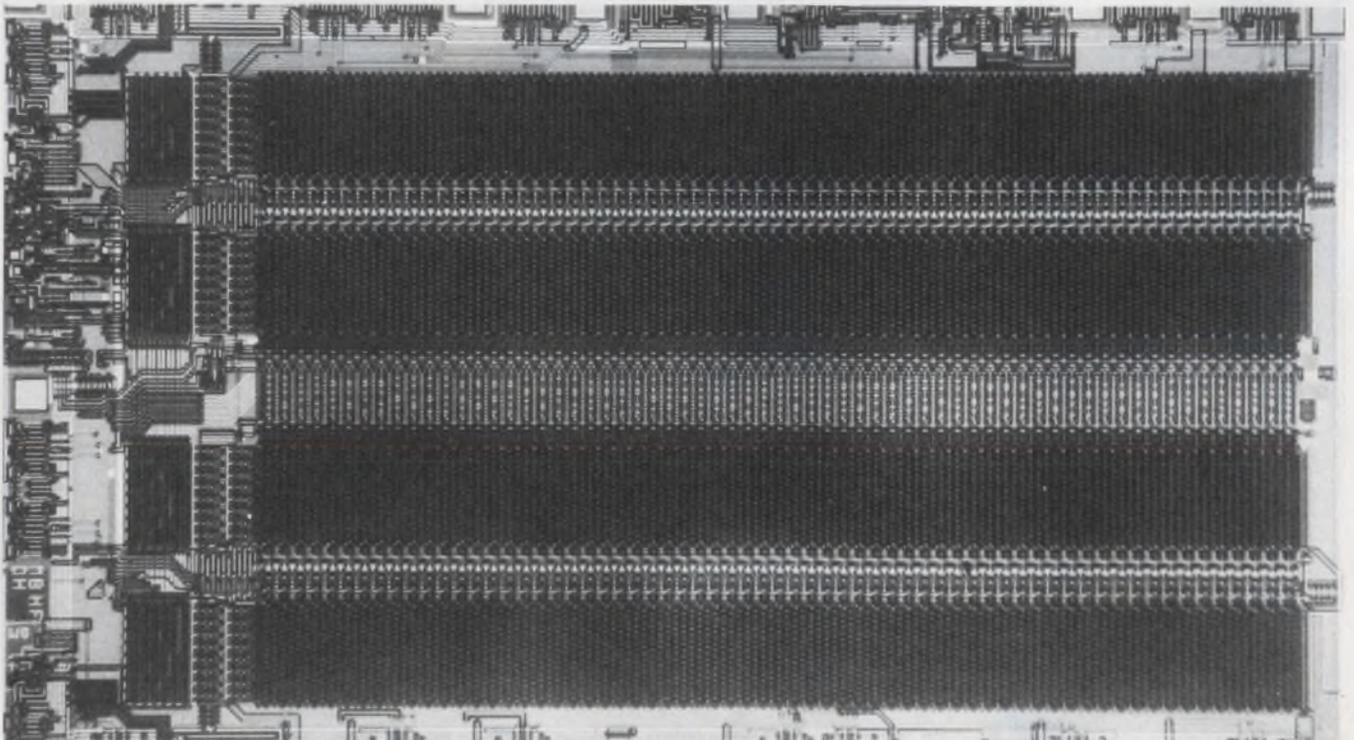

A 16,384 × 1-bit n-channel MOS dynamic RAM employs single-transistor cells and two-layer polysilicon

technology. Intel's 2116 replaces the Chip Select of 16-pin 4-k RAMs with a seventh address pin.

NEW SIMPSON

SERIES 2850 DIGITAL PANEL METER



NOW... at the right price...
a single DPM for popular
domestic and IEC/DIN cutouts



STANDARD CUTOUT
1.682" x 3.622"
(42.72 mm x 92 mm)



IEC/DIN CUTOUT
1.77" x 3.622"
(45 mm x 92 mm)



OTHER DOMESTIC CUTOUT
1.682" x 3.92"
(42.72 mm x 99.57 mm)

- 3½ digit readout
- Automatic zero and polarity
- 0.1% of reading accuracy
- BCD output is standard
- Input/output edge connector included
- Highly reliable LSI circuitry
- Choice of 120/240 VAC, 50-400 Hz or 5 VDC operation
- OEM quantity prices available upon request.

ORDER FROM YOUR ELECTRONICS DISTRIBUTOR

Model 2850 120/240 VAC input; 0.55" planar gas discharge display complete with panel mounting clips, edge connector and manual. **\$138**

Model 2851 5 VDC input, 0.55" planar gas discharge display complete with panel mounting clips, edge connector and manual. **\$138**

Model 2852 120/240 VAC input, 0.43" LED display complete with panel mounting clips, edge connector and manual. **\$138**

Model 2853 5 VDC input, 0.43" LED display complete with panel mounting clips, edge connector and manual. **\$138**

STOCK DC CURRENT RANGES: 20 & 200 μ A; 2, 20 & 200 mA
STOCK DC VOLTAGE RANGES: 200 mV; 2, 20 & 200 V
OTHER RANGES ON SPECIAL ORDER



SIMPSON ELECTRIC COMPANY

853 Dundee Avenue, Elgin, Illinois 60120 • (312) 697-2260

CABLE: SIMELCO • Telex: 72-2416

IN CANADA: Bach-Simpson, Ltd., London, Ontario



IN ENGLAND: Bach-Simpson (U.K.) Ltd., Wadebridge, Cornwall

IN INDIA: Ruttonsha-Simpson Private, Ltd., Vikhroli, Bombay

KATY INDUSTRIES



INDUSTRIAL
EQUIPMENT
GROUP

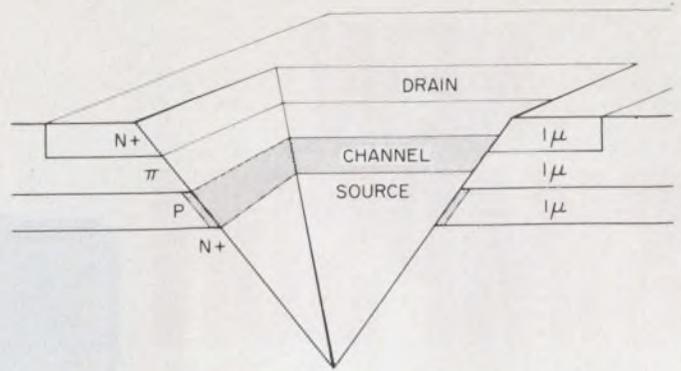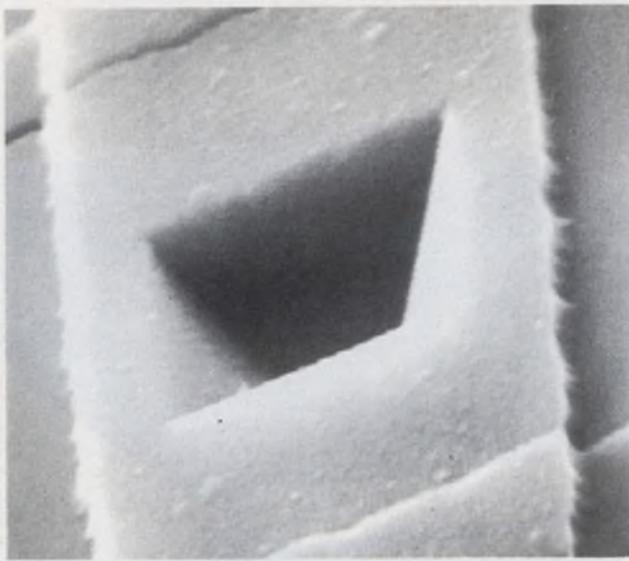

VMOS transistors—vertical n-channel MOS devices formed on the face of a V-groove—form the basis of a developmental 16-k bit ROM from American Microsystems. The 5-V VMOS ROM has a worst-case access of 200 ns, compared with over 500 ns for equivalent ROMs that use conventional techniques.

agreement: it is used by Intel for its 16-k RAM, the 2116. However, companies like Nippon and Hitachi (which presented a late paper on its developmental 16-k RAM) and possibly Texas Instruments (which didn't participate in the general discussions) are among those thought to be planning an 18 or 22-pin package.

The acknowledged model for the 16-pin package is Mostek's. The company pioneered the 16-pin package for 4-k RAMs. Sockets designed for that package can readily accommodate the similarly packaged, though higher-density, 16-k memory. This is done by abolishing Chip Select (CS) in favor of an extra address line (A_6) supporting two address bits—as in Intel's 2116.

However, the 2116 also incorporates a special output latch like that found on early Mostek 4-k RAMs. That simple latch represents one of the major points of dispute. Unlike a standard latch, the Mostek version maintains data in a Valid state right into a succeeding memory cycle.

"For a chip designer," said Richard Foss, president of Mosaid in Canada, "that latch violates one of the golden rules, that each cycle should be considered a separate entity. If in the next cycle, you have to worry about what happened in the last cycle, you can't re-standardize. It's a no-no for testing."

Moreover, the use of Chip Select was one way to clear the output latch in the 4-k RAM. But Chip

Select isn't available on 16-k RAMs going into 16-pin packages. Device selection is now an additional function of either the column-address strobe ($\overline{\text{CAS}}$) signal, which determines the vertical cells to be accessed, or the row-address strobe (RAS), which pinpoints horizontal cells.

Refresh woes

The absence of Chip Select can be a particularly acute problem for existing 4-k-RAM-based systems that refresh the dynamic memories with hidden, or "transparent," techniques. The techniques make use of the fact that not all memory elements are accessed at the same time, and are ideal for large memory systems, such as those employed by Honeywell.

While some of the elements are activated by row and column-address signals, other elements have their column-address signals cut off, and are refreshed by RAS . The so-called $\overline{\text{RAS}}$ -only refresh isn't possible with a memory chip that contains the output latch.

"With a data-out latch, you have to provide $\overline{\text{CAS}}$ to all chips whether you want to or not in order to turn off the data-out from a previously accessed chip," said Paul Schroeder, Mostek's senior design engineer in charge of 16-k RAM development.

"All of the things you need to do to get around this are extremely unpleasant. They're not the kind of things a system designer really wants to do."

For Intel, a strong argument for the latch is that it exists on current 4-k RAMs. Company spokesmen make much of the fact that they can replace the 4-ks in a customer's board with 16-k-RAM samples. The board then works just as if the memories had not been replaced.

Although the 16-k RAMs function as 4-ks—only one quadrant is used—the customer can perform most of his testing. He can check pattern sensitivities, access times and power dissipation. And with an extra address line, he can multiply storage capacity by four.

"I think the customer has been done a disservice by this debate," said David House, Intel's component applications manager. The decision of some manufacturers to drop the latch on their 16-ks, according to House, was a poor business decision, rather than an obvious engineering decision.



"It's definitely not clear that the output latch should not be there."

For the great bulk of applications, an output latch on the 16-k RAM presents no problem, observes House. In fact most memory systems can be readily designed to accommodate both a memory chip with the latch and a memory chip without one.

Such a system must be able to sample data when the clocks are in a Valid state, so that the latchless part works, and must not depend on the output being in a high-impedance state—so that the memory with the latch, like Intel's 2116,

SQUEEZE PLAY.

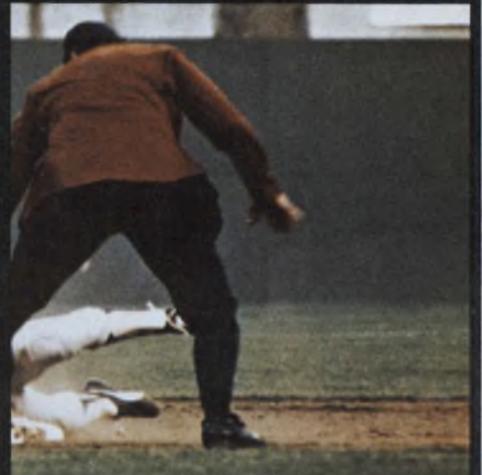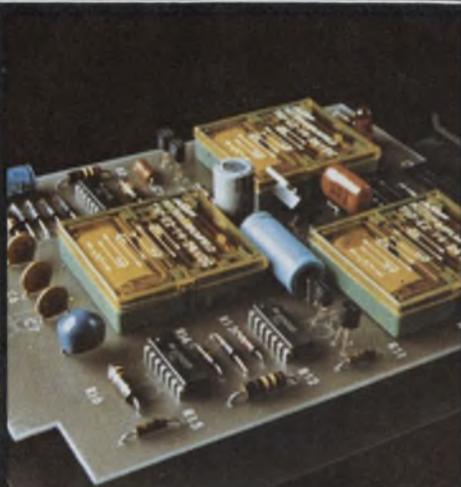T10 relays by P&B let you mount your pc boards on 0.5" centers. They work in tight spots like a pro.



T10s are only 0.375" high. The lowest profile 3 amp relay in the Potter & Brumfield line.

They provide 0.1 to 3 amp switching @ 28V DC in 2, 4, and 6 pole models. Coil ratings are 6, 12, 24, and 48V DC. Permissive make, gold-flashed silver contacts are noted for low contact bounce, long operating life. Bifurcated contacts for low level switching are also available.

These relays are compatible with TTL and CMOS peripheral driver ICs, and TTL and CMOS buffers wired for current sharing. Ideal for telecommunications, copy and reproduction machines as well as computers and peripheral equipment.


Put a squeeze play on costs. Prices are as compact as the relays themselves.

For full information on the T10 series and all P&B relays, see your Potter & Brumfield sales representative or P&B Pro Shop distributor. Or, contact Potter & Brumfield Division AMF Incorporated, Princeton, Indiana 47671. Telephone: 812/385-5251.

European address: Electrical Products Group, AMF International Limited, AMF House, Whitby Road, Bristol B54 4AZ, England. Telephone: (0272) 778383, Telex: 449481, AMMAFOCO, BRSTL.



Go with the Pros and you can't go wrong.

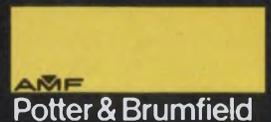

can also work.

Most manufacturers declined to detail how they would design their 16-k RAM chip, although American Microsystems indicated it would follow Intel's lead in building a 16-k version of Mostek's early 4-k RAM.

Mostek, however, was adamant in its opposition to the kind of latch it originally inflicted on the industry. The Mostek 16-k RAM, which could be announced as early as midyear, will have a data latch, but one that can be cleared at the end of a memory cycle, when $\overline{\text{CAS}}$ goes high.

The benefits are many. Now a $\overline{\text{CAS}}$ signal can be used as a separate Chip Select and to simplify the expansion of speed-enhancing page-mode systems. Multiple 16-ks are accessed with a $\overline{\text{RAS}}$ pulse, and a $\overline{\text{CAS}}$ is applied only to those chips from which outputs are needed. Further, the memory chip can be used in systems that call for transparent refresh.

Another point of controversy is the number of refresh cycles. If compatibility with 4-k RAMs were the sole consideration, the number of refresh cycles would be 64 every 2 ms.

The Intel 16-k RAM allows either 64 or 128 cycles in the 2-ms refresh interval. The memory naturally takes 128 cycles, because of its 128

\times 128-element layout. However, internal logic can reduce the refresh requirement to 64 when signalled to do so by a special overlapping of $\overline{\text{CAS}}$ and $\overline{\text{RAS}}$.

For system designers, 64 cycles would seem to be better than 128. The reduced refresh requirement leads to a somewhat simpler design and to lessened "dead" time.

Critics argue, though, that with a 64-cycle refresh, twice as many sense amps are active than there would be with 128 cycles. The additional amps increase power dissipation.

"Chip temperature could rise by 10 C," said Foss. "If it does, never mind the data sheets, you may have to refresh twice as often, because the chip is that much hotter."

Further, the 2116 has a total of 64 cells on each sense amp, and a total of 256 space-consuming sense amps on the 145×235 -mil die—close to the maximum size that will sit in a 16-pin DIP, "without using a shoehorn," as one expert put it.

When the refresh requirement is solely 128 cycles, a smaller chip can be built with just 128 cells on each sense amp and a total of 128 sense amps—the approach planned by Mostek.

The result, according to Mostek's Schroeder, will be a chip measuring about 28,000 square mils, com-

pared with 34,000 for the 2116. And the Mostek version will specify its slowest access at 250 ns—which is the top speed for the 2116.

"I expect the highest speed to be 200 ns early in the game," Schroeder said, "and faster units will appear later."

Dissipating power

The 2116's power dissipation was another point of concern. Although the memory was said to consume substantially less power/bit than a 4-k RAM did, the 2116's over-all dissipation was about the same—officially under 3/4 W. For some, the value was too high.

"The arithmetic I've gone through," Schroeder said, "makes me expect that parts having dissipations over 1/2 W tend to have a high junction temperature. If it rises by no more than 10 C, I would be surprised."

That rise could spell trouble for the refresh interval. Published specs don't always take into account the rise in junction temperature. One way to make the spec more meaningful, according to Schroeder, is for manufacturers to test refresh interval with internal junction temperatures at 100 C or higher, and to provide curves of ambient temperature and air flow as functions of cycle rate. ■■

Lack of standards slows progress of analog interfacing for μP systems

Despite impressive advances in the design of monolithic analog-to-digital converters, widespread use of microprocessors in analog systems may be stymied, an expert warned, unless the industry acts immediately to standardize converter hardware.

The call for action came from Hermann Schmid, a consultant for General Electric. Schmid summed up the problem during a panel discussion on "Problems of Analog Interface in Microprocessor-Based

Michael Elphick
Managing Editor

Systems" at the ISSCC.

"There must be hundreds of a/d and d/a converters on the market," he said, "but have you ever tried to find a second source for one of them?"

Few circuits are pin-compatible, Schmid added, and they come in all sorts of shapes and sizes and with various voltage requirements. And when you try to interface them with μPs you run into still further problems.

To be useful, the analog interface device should be address selectable, have on-board latches, and

have three-state digital outputs for direct connection to the μP 's bus, Schmid said.

"Standardization is difficult and we shouldn't underestimate the magnitude of the task," warned Schmid. "But, it must be done. The IEEE interface-bus standard for instruments is an excellent example of what is possible."

Most panelists agreed there was an urgent need for standards. Tom Harper of National Semiconductor said system designers he's worked with seem to be using μPs primarily to reduce their parts count.


SC/MP... A MICROPROCESSOR SO SIMPLE AND INEXPENSIVE, IT'S ENOUGH TO MAKE ANY MACHINE THINK.

The "Simple Cheap Microprocessor." At less than ten bucks apiece in volume, it makes microprocessor technology practical where it's never made sense before. In products like meters,

It requires a minimum number of components and support chips.

Yet it gives you advantages that can't be found in many expensive microprocessors. Like an on-chip clock. Serial I/O ports that are TTL-compatible. Static operation. Bus allocation for multi-processor system design. Plus built-in, programmable DELAY instruction.

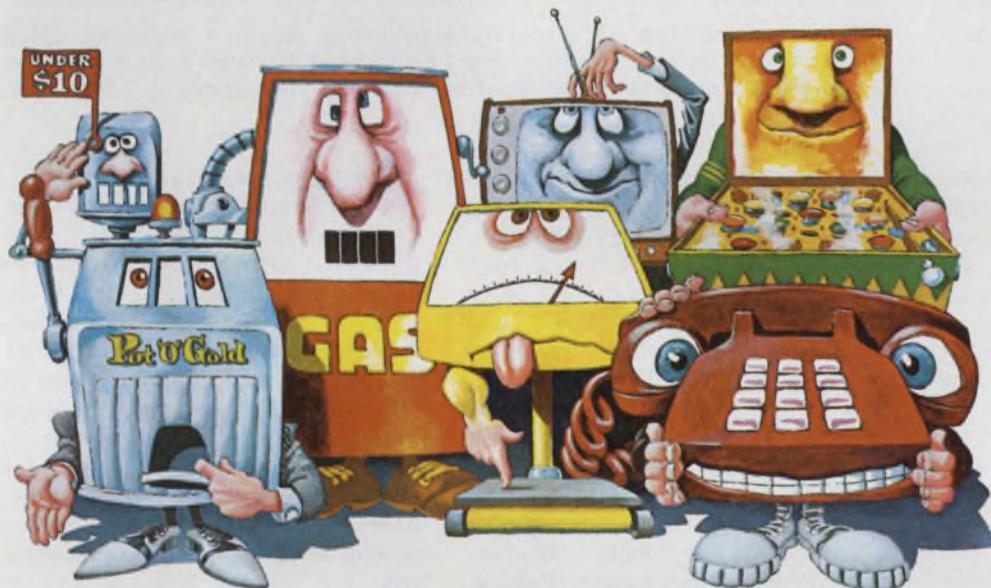It's on your distributor's shelf right now. For technical description of the chip and a complete data sheet, send us the coupon below.



gas pumps, traffic-light controls, pinball machines, medical electronics, TV games, scales, motor controls, telephones, home appliances.

A whole world of machines and men has been waiting for such a thing.

Well, thanks to National, SC/MP is here now.

And it's not just the cheapest, least-complicated microprocessor on the market. It's also one of the most capable.

It shortens design time because of its architecture, and its ability to interface with standard memories and standard peripheral components.

If this thing catches on (and at less than \$10 a copy, it's got to), who knows where it could lead?

To stuffed dogs that tell shaggy people-stories?

National Semiconductor Corporation
 2900 Semiconductor Drive
 Santa Clara, California 95051

Gentlemen:
 SC/MP, eh? I'd like to see that Technical Description, data sheet and a sales brochure:

Name _____ Title _____

Company _____

Address _____

City _____ State _____ Zip _____

National Semiconductor

Ask your distributor for our SC/MP Evaluation Kit.

When substantial hardware is needed for analog interfacing it defeats the purpose of using a μP .

Microprocessor manufacturers may start to include analog-interface circuitry on the μP chips, and system designers may start to replace external hardware with software algorithms, he warned, unless converter manufacturers act quickly to supply compact standardized hardware at low cost.

"Converter manufacturers aren't merely competing with each other," explained Harper. "The real competition is software."

Panelists also agreed that the standardization task would be Herculean. Since it would be practically impossible to standardize the software aspects of analog interfacing without standards for the μPs themselves, Schmid urged the industry to begin with hardware standardization and resolve software problems later.

Even in the hardware area, though, prospects for standardization appeared bleak. While most panelists agreed on the need for addressing capability and three-state TTL digital signals, the panel was sharply divided on the basic question of whether digital data should be handled serially or in parallel.


The hardware's getting better

Although standardization remains elusive, papers presented at the conference showed that IC manufacturers have licked several other problems that tended to restrict use of μPs in analog systems. A/d and d/a converters no longer need to be expensive, slow, inaccurate and bulky.

IC designers proved at this year's conference that most of the traditional constraints have been overcome. It's now possible to build single-chip a/d converters using just about any popular circuit configuration.

Among the developmental a/d converters described at the conference were circuits using CMOS, PMOS and bipolar-LSI processing. Circuit techniques used included dual-slope integration, successive approximation and high-speed parallel conversion.

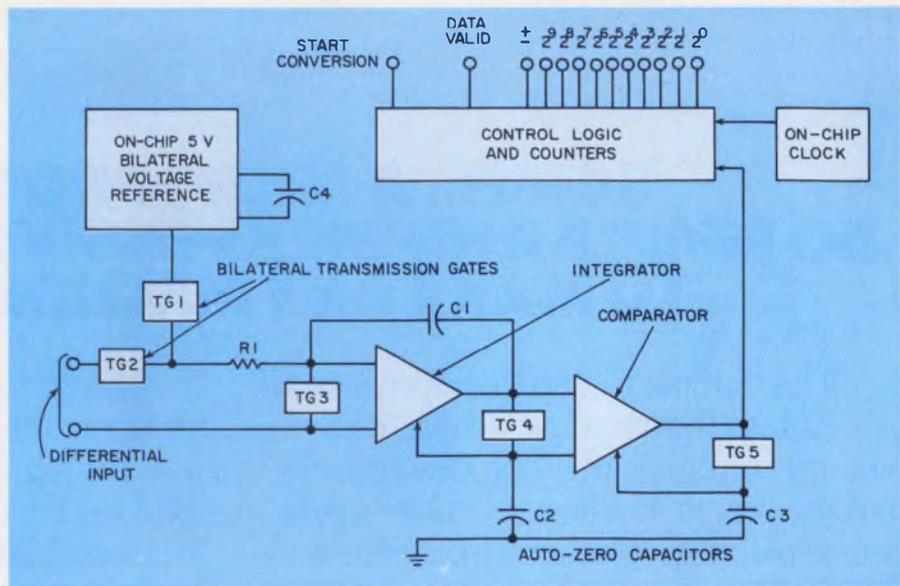Perhaps the most impressive a/d converter described at the confer-



Dual-slope integration is the conversion technique used in a monolithic CMOS a/d converter designed by RCA. The 11-bit circuit includes a clock oscillator and a reference source. It operates from a single-ended supply of 4.5 to 15 V.

ence was a successive-approximation circuit, from TRW Systems, that combines speed with accuracy. The 10-bit bipolar-LSI circuit achieves a sampling rate of 5 MHz while consuming only 2.7 W.

Linearity of the basic circuit is 0.4 LSB, but can be improved to less than 0.2 LSB by laser trimming of the chip's thin-film resistors. The only external circuitry needed is a reference source and a clock oscillator. (For a block diagram and more complete description of this circuit, see "Fastest Monolithic 10-bit A/d Device Has 200-ns Conversion Time," ED 5, March 1, 1976, p. 20.)

Although the Systems Group of TRW traditionally doesn't sell components, the company may market the converter circuit later in the year, according to David Breuer, who presented the paper.

Even higher conversion speeds are achieved in a bipolar a/d converter described by Robert Nordstrom of Tektronix. This circuit uses a parallel-conversion technique to achieve a conversion rate of 100 MHz, and the 4-bit chip has sufficient accuracy for use in an 8-bit converter.

The circuit consists essentially of 16 high-speed comparators and a 4-bit binary encoder, integrated on a single chip. A separate resistor network was used for the prototype, which was built primarily to demonstrate the feasibility of inte-

grating the comparators.

Other manufacturers have demonstrated that it's possible to deposit and trim thin-film resistors on a silicon chip, so it should be possible to build a complete monolithic converter based on this design. Each comparator cell consists of only 15 transistors, and standard high-frequency IC processing is used to achieve an f_T of 3 GHz for the transistors. The bit lines deliver ECL levels, but dissipation is only 32 mW for each comparator cell.

MOS shows progress, too

Bipolar circuits won the speed race at ISSCC, but some solid gains were also made in MOS. Of course, for a/d converters, MOS offers the advantages of low cost, high circuit density and low power dissipation. But until recently designers found it difficult to achieve the required performance in the analog portion of a/d converters that employed MOS throughout.

Most designers compromised on a two-chip arrangement, using MOS for the digital portion and bipolar circuitry for the analog section. Now, however, the analog design problems seem to be licked. Three companies announced single-chip MOS converters at the conference—two use CMOS, while one uses PMOS.

One of the CMOS circuits was

“No, we ordered a ten-buck DAC!”

O.K., friends, here it is, our DAC-03 monolithic D/A converter. 10-bits, 10 bucks. Lowest cost unit you can find that contains all necessary functions: precision voltage reference, current sources, current steering logic, R-2R resistor ladder network, and a high speed internally compensated op amp.

You save dollars, pounds and p.c. board real estate. And you get guaranteed key specs at no extra charge.


Add it all up—price, performance, and PMI's history of delivering more monolithic DACs than all other manufacturers combined. Then ask for data sheets on our DAC line.

You won't have to look anywhere else for the DAC you need; the buck stops here.

Precision Monolithics, Inc.,
1500 Space Park Drive,
Santa Clara, CA 95050
(408) 246-9222. TWX 910-
338-0528. Cable MONO.



CIRCLE NUMBER 15

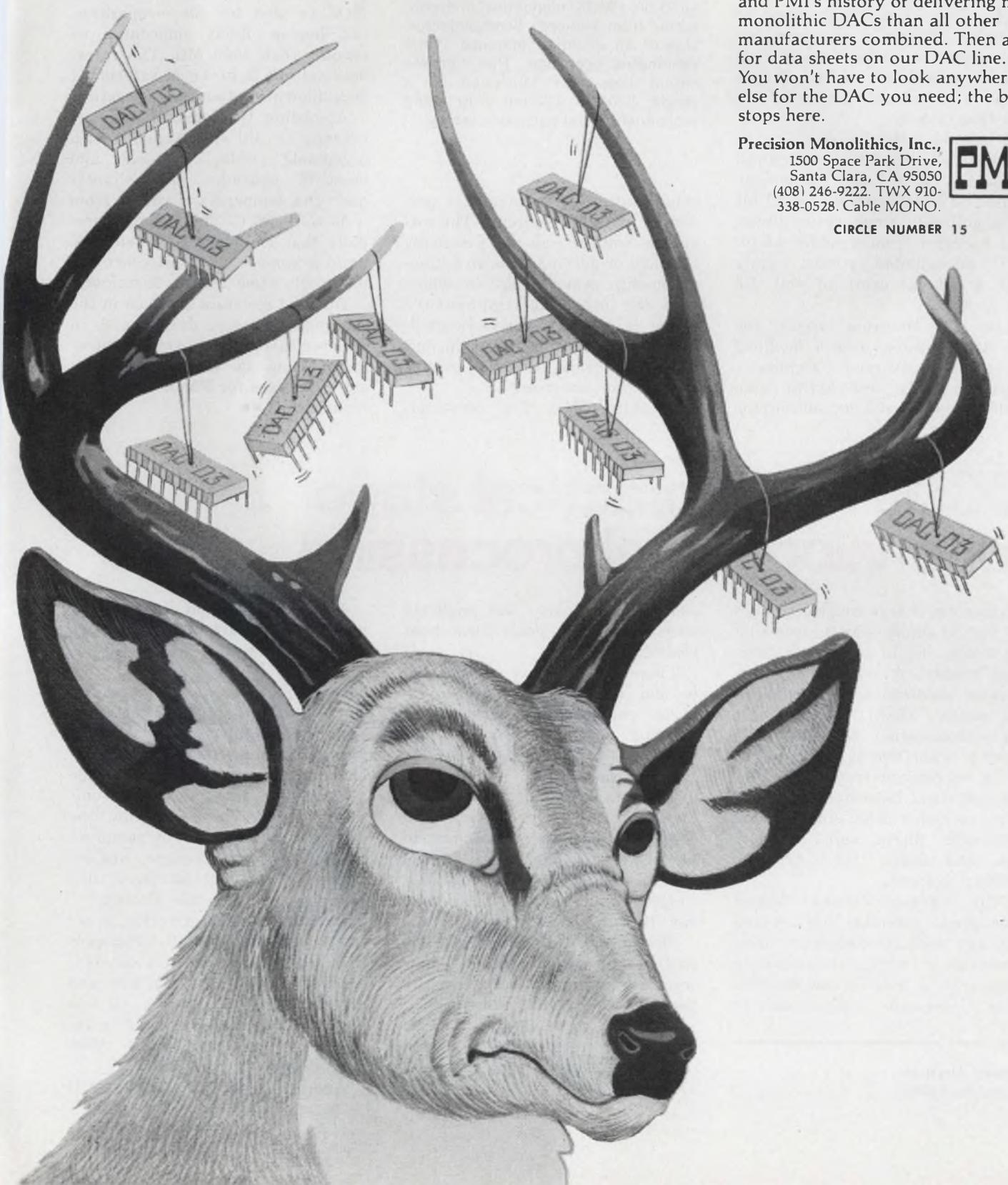


described by Robert Huntington of Motorola Semiconductor Products. His 3-1/2-digit a/d converter provides autopolarity and automatic-zero functions.

Also, it compensates itself for op-amp offsets and the comparator threshold. As a result, the modified dual-slope circuit holds its 0.05% full-scale accuracy over a temperature range of -50 to +75 C and eliminates the need for manual adjustments.

The single-chip circuit needs no precision off-chip components, but does require a couple of noncritical capacitors and a resistor. Power-supply requirements are ± 5 V at less than 2 mA.

A second CMOS a/d converter was described by Andrew Dingwall of RCA's Solid State Technology Center. The circuit is an 11-bit autostabilized single-chip design that operates from a single 4.5-to-15-V unregulated power supply with a current drain of only 1.2 mA at 5 V.

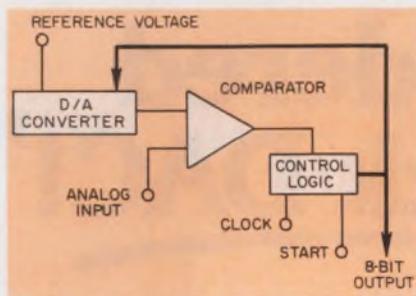Like the Motorola circuit, the RCA version uses a modified dual-slope conversion technique. Single-supply operation was achieved by use of a current-mirror



Successive approximation provides a typical conversion time of 20 μ s in an 8-bit PMOS monolithic a/d converter from National Semiconductor. Use of an external reference allows ratiometric operation. The complete circuit has been fabricated on a single 120 \times 123-mil chip using p-channel, metal-gate, processing.

configuration in the amplifier portion of the CMOS circuit. The reference voltage can be externally supplied or derived from an optional on-chip zener diode—in which case the operating-temperature range is reduced. The clock oscillator is included on the chip, but some noncritical, external passive components are needed.

A third MOS a/d converter,

using p-channel, metal-gate processing, was described by Adib Hamadé. He now works in Iraq, but designed the single-chip 8-bit converter while working for National Semiconductor in the U.S.

The circuit employs a successive-approximation conversion technique to yield a typical conversion time of 20 μ s. The 120 \times 123-mil PMOS chip includes a d/a converter, a comparator, control logic and three-state output buffers. Because MOS is used for the comparator, the analog input impedance is greater than 1000 M Ω . The reference voltage is provided externally, thus allowing ratiometric operation.

According to Hamadé, the unit exhibits 1/4-bit step linearity with acceptable production yield, and linearity degrades only slightly over the temperature range from -55 to +125 C. The designer predicts that it should be possible to build a monolithic 10-bit converter using the same circuit techniques.

Diffused resistors are used in the inherently low-cost design, and, in a clever layout trick, small protrusions from the resistor diffusion act as sources for PMOS switching transistors. ■■

CCDs reach practical stage for analog signal processing

Applying charge-coupled devices (CCDs) to analog-signal processing has finally begun to achieve practical results. A variety of user-oriented hardware was described at last month's ISSCC.

The application concept—introduced a scant two years ago—has begun to emerge from university and industrial laboratories in such forms as video delay lines, analog transversal filters, signal correlators, and lenses for ultrasonic imaging systems.

CCD signal-processing devices offer great potential for lowered cost and reduced complexity over present-day signal-processing equipment. A host of new markets (plus increased competition in

some existing ones) was predicted once these cost goals have been realized.

These devices have passed well beyond the feasibility stage, experts emphasized. As evidence, working specifications for CCD-based hardware were given for such characteristics as linearity, distortion, dynamic range and bandwidth.

"What the engineer wants to know now is whether it's good enough for his application," said Carlo Sequin of Bell Labs, Murray Hill, NJ.

"Engineers don't just think of a CCD as an isolated device. They want a working black box that can perform a particular function."

David Wen of Fairchild, Palo Alto, CA, introduced one of several of these CCD-implemented units, a video-delay line.

The Fairchild delay line serves a number of important needs of the video industry, Wen explained.

One use is for television time-base correction, which is needed when the TV signal is obtained from a video tape or disc. Any existing irregularities in the mechanism that drives the disc or tape reels results in timing-synchronization errors. The CCD delay line can correct the errors by sampling the signal at one frequency and re-transmitting it at another, thus changing the effective timing.

Currently, such correction is accomplished by digital techniques that require a/d and d/a converters to transfer the signal into and out of the digital domain. All this very elaborate hardware can be replaced by just one CCD, Wen pointed out.

Another application for the CCD

Samuel Derman
Associate Editor

Good news from Hughes:

Now you can actually reduce system cost by using our hybrid microcircuit modules.

If you're designing circuits that have to be both cost-effective and high in reliability, it will probably pay you to talk with us.

We've developed a system for condensing circuit requirements into the most efficient hybrid packages possible. And we can help you reduce size and weight as well as manufacturing costs.

Here's how we do it: We design the hybrid circuits, develop the prototypes, manufacture custom components, then assemble, test, and guarantee the total hybrid package. We make both thick film and thin film hybrids. We use hermetically-sealed metal and ceramic packages. And we make custom MOS devices and bipolar chips right here in-house.

We produce hybrid modules in volume quantities at competitive prices, as well as small quantities for product development.

Result: Now you can work with the one company best equipped and experienced to handle your job from concept through production.

We must be doing a lot of things right, because we're one of the leading producers of custom hybrid circuits.

So when it comes to hybrids, call on Hughes. Especially if quality is as important as price. Write for additional information: 500 Superior Avenue, Newport Beach, CA 92663, Att'n. Hybrid Dept. Or call (714) 548-0671, ext. 204.

HUGHES

HUGHES AIRCRAFT COMPANY
MICROELECTRONIC
PRODUCTS DIVISION



delay line is in separating color from black and white in a composite TV signal.

The Fairchild CCD delay line consists of two independent 455-element buried-channel CCD shift registers, complete with transport clocks and input and output terminals, all on a die measuring 79 × 84 mils. The unit has a bandwidth of 4 to 5 MHz, a dynamic range of about 55 dB and nonlinearity of 3 percent or less. Only two external clocks are required.

The output signal of one register can be directly connected to the input terminal of the other to obtain a 910-element delay capable of storing a complete horizontal line of standard television transmission (63.55 μs) with a sampling rate of 14.32 MHz. The device is assembled into a standard 16-lead DIP.

The delay line will become available "very soon," Wen reported. The price for single units will initially be somewhere in the \$100 to \$200 range, with the projected price eventually dropping to less than five dollars each for quantity lots. The current price of an equivalent standard delay line is \$700 to \$800.

CCDs filter baseband data

An analog CCD transversal filter for baseband data filtering was described by Marvin White, advisory engineer at Westinghouse Advanced Technology Laboratories, Baltimore, MD.

A CCD transversal filter consists basically of a tapped CCD delay line. At each tap the signal

leaves the delay line and passes through a separate variable resistance. Finally, the delayed signals, from each tap, are summed.

Since each resistance can be varied independently, the result is a summation of weighted signals. Any desired filter characteristic can be synthesized by this means. This is a powerful design tool, White explained, because it allows the designer to control a filter's amplitude and phase characteristics independently. In conventional passive filters the amplitude and phase are unavoidably related.

Even more important, said White, the individual resistances can be varied electrically, and the weighting factors can be continuously upgraded in accordance with some specified algorithm. This process, known as adaptive filtering, offers the possibility of enormous improvement in signal-to-noise ratio in such diverse areas as radar reception, echo suppression in satellite communications, and biomedical electronics. For example, it can remove 60 Hz noise from electrocardiogram signals, or separate the heartbeats of fetus and mother.

White provided the following figures for the filter: total harmonic distortion of 0.3 percent for a 1.5-V p-p 1-kHz input signal and a sampling frequency of 16.7 kHz.

White explained that a unique design feature of this device is the use of a floating-clock electrode sensor that provides nondestructive readout (at each tap point) of the CCD delay-line signal. The unit combines both bipolar and MOS technology with the CCD delay line

—the first time such a combination has been realized on a single chip.

Completion of the entire system must await the integration of the adaptive-filter algorithm on the chip, White said.

CCDs convolute analog inputs

Patrick Bosshart, an electrical-engineering graduate student at MIT, described an integrated-circuit analog correlator that uses CCDs. An analog correlator performs the convolution of two arbitrary analog input functions and can replace some complex digital systems that do the same job. The CCD correlator, however, uses fewer components and costs less to manufacture.

The device, based on a master's thesis project, was designed by Bosshart and fabricated at Texas Instruments.

The level of performance is high enough to allow the correlator to be used in applications in audio and video-signal processing and in adaptive filtering Bosshart reported.

Potential improvements in ultrasound technology for both medical and industrial applications using a cascade CCD were described by John Short of Stanford University, Stanford, CA.

This device uses CCD delay lines to equalize the total (electronic plus acoustic) propagation time for a set of ultrasonic transducers.

The CCD "lens" has been built and tested and has been shown to produce a resolution near the theoretical maximum for an array of 1.5-MHz transducers. ■■

Telephone-oriented LSI finds tough going despite reported advances

The role of standard IC products—and particularly microprocessors—in the multi-billion-dollar telephone industry appears cloudy.

Despite LSI-circuit innovations described at the 1976 ISSCC, a panel discussion on the future impact of such circuits brought

out controversies surrounding new semiconductor developments. It also underscored the long, rocky road ICs must travel before finding acceptance in telephone equipment.

Papers described at the conference covered three major areas in telephony: coder/decoders (codex), compressor/expanders (compandors) and crosspoint switches.

One switch unveiled at the meeting is notable for having its control circuits, which can interface directly with a microprocessor, integrated on the same chip as the crosspoint array.


Microprocessor control may indeed be an attractive feature. But the question is, can the microprocessor, or any of the other communications circuits described at

Stanley Runyon
Associate Editor

the conference, find a prominent niche in an industry famous for its caution. If some of the panelists and audience at the informal discussion have their way, the answer is "no."

Although John C. McDonald, vice president of research and engineering for the Vidar Div. of TRW, Mountain View, CA, projected a \$3 billion market for LSI/MSI circuits in telephone networks by 1990, others took a different view:

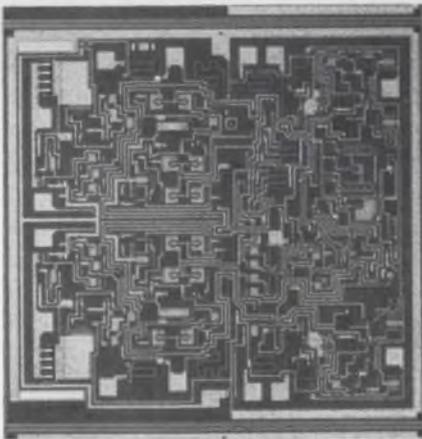John Rhodes, organizer and moderator of the session, and a technical member of the board of Pye-TMC, a supplier of phone equipment in Wilts, England, stated



An 88 × 92-mil analog compandor uses ion implantation and matched components to achieve low drift, high accuracy.

flatly that "processing and microprocessors are not for telephony." Rhodes apparently meant off-the-shelf silicon products, not custom LSI, of which he proclaimed himself a proponent. Asked to define "custom LSI" Rhodes replied: "It's an IC designed by an engineer who knows the telephone business."

Winners and losers

McDonald, on the other hand, told of considerable success with standard ICs, and of disasters with custom circuits. His formula for success: 100 to 500 FITs (failures in 10^9 hours), availability for 20 years or more, and, of course, low price.

Attendees and panelists immediately polarized, lining up on either the custom or standard-product side. While this appeared

NOW— A FAIL-SAFE SOLID-STATE RELAY

Most solid-state relays have a nasty tendency to stick in the "on" condition if a voltage or current surge hits them. And, if the triac fails to fire, many even burn up and become the unfortunate cause of catastrophic system failures.

Not ours.

A unique combination of dv/dt snubber, fusible-link protection, and an oversized triac makes the new optically-coupled Heinemann SSRs fail-safe. Now, the worst thing that can happen to your system is the simple need to replace the relay. That's a lot better than having to reprogram your entire control sequence, isn't it?



We make our new SSRs for either zero-voltage or non-zero-voltage switching, and both types are rated for maximum ac load currents of 5A or 10A. Any control voltage from 3Vdc to 32Vdc; all models compatible with TTL, DTL, and CMOS logic.

And you have a choice of solder-pin, quick-on, and screw terminals.

Talk with Bob Kusek (609-882-4800) or write for further information. Heinemann Electric Company, Brunswick Pike, Trenton, NJ 08602.

HEINEMANN

We keep you out of trouble.

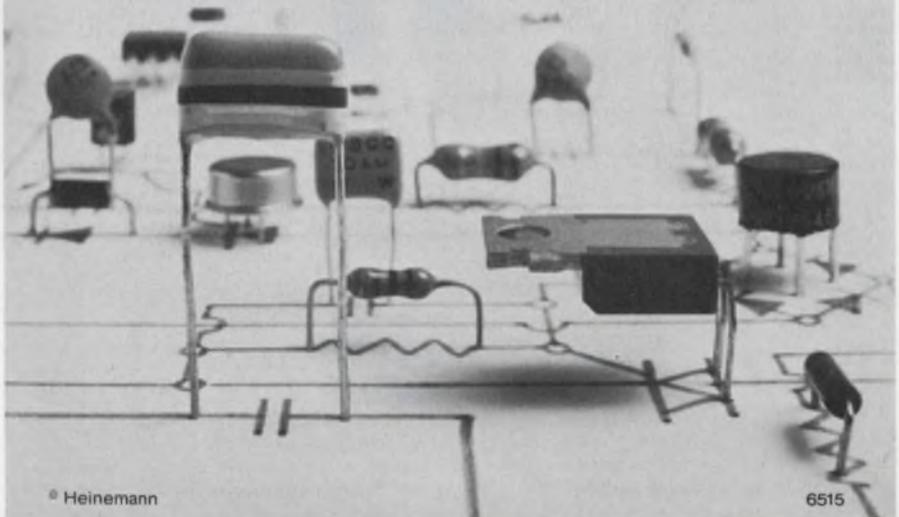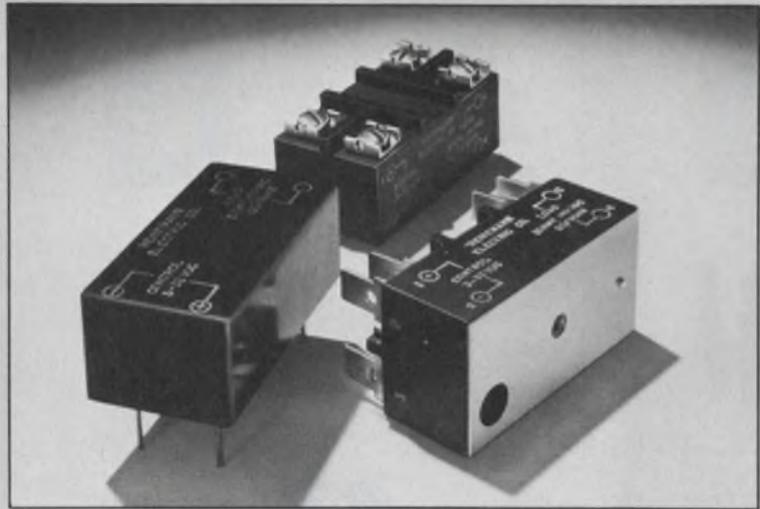

© Heinemann

6515

CIRCLE NUMBER 17

SAVE WEAR AND TEAR ON YOUR CIRCUITS, YOUR NERVES AND YOUR BUDGET.

Proto-Clip™: Foolproof, short-proof, power-on DIP in-circuit testing.


Wherever you use DIP's, you need CSC Proto-Clips.** The clip-on, short-proof way to bring leads up from crowded circuit boards, for fast signal-tracing, testing, signal injection ... even wiring unused circuits into existing boards. Unique gripping teeth (see inset) provide slip-proof connections for test-equipment probes ... free your hands for other work. High-impact plastic construction eliminates troublesome springs and pivots; molded

flexible web insures positive operation for thousands of tests; non-corroding nickel-silver contacts give simultaneous, low-resistance connections to all IC leads.

Proto-Clips are available with or without cable for 14-, 16- and 24-pin DIP's.

Best of all, Proto-Clips are inexpensive!

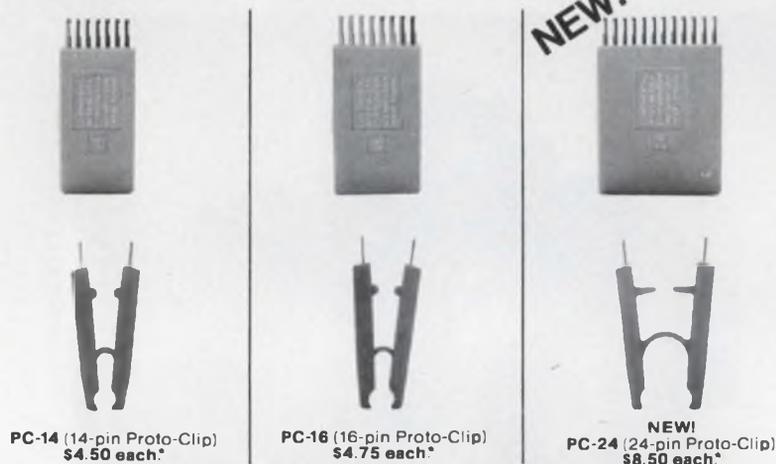For more information, write for our full product catalog and distributor list.



| | Cable length inches | Price Single clip | Each Dual clip |
|--------|---------------------|-------------------|----------------|
| PC-14- | 12 | 7.50 | 14.50 |
| PC-14- | 18 | 7.75 | 14.75 |
| PC-14- | 24 | 8.00 | 15.00 |
| PC-14- | 30 | 8.25 | 15.25 |
| PC-14- | 36 | 8.50 | 15.50 |
| PC-16- | 12 | 8.25 | 15.75 |
| PC-16- | 18 | 8.50 | 16.00 |
| PC-16- | 24 | 8.75 | 16.25 |
| PC-16- | 30 | 9.00 | 16.50 |
| PC-16- | 36 | 9.25 | 16.75 |
| PC-24- | 12 | 12.00 | 25.00 |
| PC-24- | 18 | 12.25 | 25.25 |
| PC-24- | 24 | 12.50 | 25.50 |
| PC-24- | 30 | 12.75 | 25.75 |
| PC-24- | 36 | 13.00 | 26.00 |



NEW!
PROTO-CLIPS WITH
PREWIRED CABLES.

Factory assembled and tested, Proto-Clips with prewired cables simplify a wide variety of jobs. Like simplifying IC connections to other IC's, other boards, test fixtures, even interconnecting Proto-Boards. Available with connectors at one or both ends, cables are rated to 150V and 105°C. Conductors are #28 AWG stranded conductors with PVC insulation.

Note: S= Single Clip D= Dual Clips
When ordering include Part No. — Cable Length—Single (S) or Dual (D) Clips.

CONTINENTAL SPECIALTIES CORPORATION



44 Kendall Street Box 1942 New Haven, CT 06509 203-624-3103 TWX 710-465-1227
West Coast Office: Box 7809, San Francisco, CA 94119 415-421-8872 TWX 910-372-7992
Canada: Len Finkler Ltd., Ontario

© 1975 Continental Specialties Corp.

*Manufacturer's recommended retail
**U.S. Pat. No. 3,914,007

CIRCLE NUMBER 18

to be the key issue of the session, the debate actually surfaced as a clash between two giant but antithetical industries—the slow moving telephone establishment and the quick-turnover semiconductor houses.

Just how quickly semiconductor technology can respond to a specific job is demonstrated by the advances outlined at the conference.

In a paper on an all-MOS, compounded PCM voice encoder, John P. Tsvividis of the University of California, Berkeley, CA, described a partially integrated MOS chip that meets Bell System specifications for signal-to-distortion ratio, gain tracking, single-frequency distortion and idle-channel noise.

Tsvividis explained that the chip, fabricated as metal-gate, n-channel MOS, satisfies a commonly used companding algorithm (μ -255) that uses a 15-segment approximation of the nonlinear curve. Thus the s/n ratio is optimized for digital voice transmission.

Analog is king in telephony

Most existing telephone equipment, however, still operates in the analog domain. To improve the s/n ratio of analog transmission, companding remains the traditional technique. Here, a 2-dB change in input level is compressed into a 1-dB variation for transmission, and an expander restores the 2-dB excursion at the receiving end.

A monolithic compandor was described by Craig Todd of Signetics. As he pointed out, discrete compandors require many components, and so often suffer from excessive temperature drift. The bipolar IC, however, uses ion-implanted resistors and matched IC components, so that the required low-level tracking, distortion and temperature stability are realized without costly external trimming.

The untrimmed distortion of the IC compandor, Todd stated, is 0.5 percent, and the gain change from -40 to 70°C is only ± 0.2 dB. Another benefit: low power consumption—just 4 mA are drawn at a V_{cc} ranging from 6 to 18 V.

In the third important application area—that of switching—two ICs that were described met the challenge of low distortion, low loss and low crosstalk. Though

electromechanical relays aptly fulfill these requirements, solid-state crosspoints are potentially more reliable, switch much faster than relays and need far less power.

The first IC—outlined by Willy Sansen of Catholic University, Heverlee, Belgium, is an active, bipolar 4×4 crosspoint with a low r_{on} -area product (1.7 to 2.5 Ω -mm²), with low sensitivity to line spikes, and needing no coupling transformers or capacitors.

In operation, the pass transistor of the switch is biased in its active region—instead of the linear region—and the device gain is arranged in a feedback loop to reduce the ON resistance and cut losses. Insertion loss of the switch is as low as 0.1 dB, and ON dissipation is fairly high—80 mW—compared with that of other solid-state methods.


Switching plus digital control

In another approach, Thomas Cauge of Signetics told of a DMOS crosspoint array in which control circuitry was integrated on the same chip. Configured as an 8×2 unbalanced network, the switch ON resistance is cut by a factor of three to five over that of conventional MOS that uses the same area.

Cauge listed both the typical crosstalk and OFF isolation of the DMOS switch as -105 dB, and typical ON resistance as 12Ω at a V_{cc} of 15 V. He noted that the TTL/CMOS compatibility of the chip and the single 15-V supply needed are features designed expressly for microprocessor interfacing. ■■

Papers, anyone?

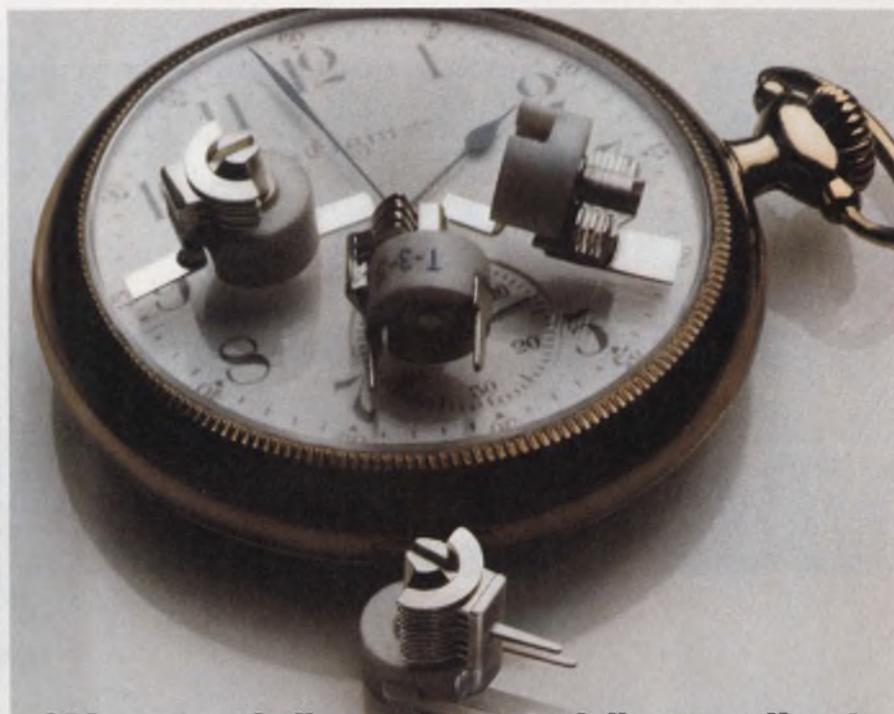A complete digest of the papers presented at the International Solid-State Circuits Conference is available at \$20 for IEEE members and \$30 for nonmembers. Write to: International Solid-State Circuits Conference, Philadelphia Section IEEE Office, Moore School of Electrical Engineering, University of Pennsylvania, Philadelphia, PA 19174.



We can deliver the world's smallest 180° air variable capacitors. On time.

And since we're nice people, we don't even charge much for them. So if you have an application that calls for a sub-miniature capacitor that you can "tweak" to a specific frequency, these Johnson trimmers are ideal.

You can choose from either PC or stripline mount, either vertical or horizontal tuning. These Type "T" capacitors are about one-third the size of the familiar type "U" capacitors, so you can save space, cut costs and insure improved performance in the most compact electronic equipment.

Rotors and stators are precision-machined from solid brass extrusions, resulting in exceptional stability and uniformity. High Q—typically 2000 at 150 MHz. Temperature coefficient is a low plus 30 ± 15 ppm/°C. High torque ($1\frac{1}{2}$ to 8 oz./inches) holds rotor securely under vibration. They're designed to meet or exceed EIA-RS 204 and MIL Standard 202C Methods 204A and 201A.

In short, these capacitors may be just what you've been looking for. It'll only cost you a stamp to get more information. And if you give us your phone number, we'll call you and send free samples after we have clarified your application.

E. F. JOHNSON COMPANY
3305 Tenth Ave. S.W. / Waseca, MN. 56093


- Please send me technical information on the type T.
 - Also, include information on your entire line of variable capacitors.
 - I want test samples. Please call me at _____
- NAME _____
TITLE _____
FIRM _____




ADDRESS _____
CITY _____ STATE _____ ZIP _____

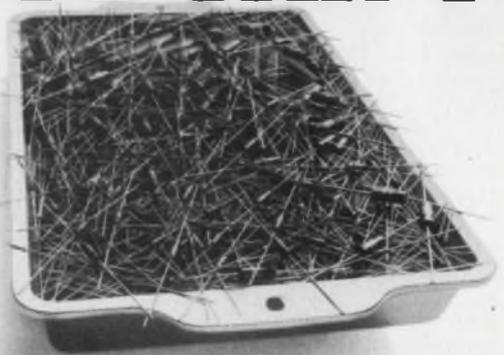E. F. JOHNSON COMPANY

FOR STABILITY YOU CAN'T GET FROM THE BROWN 'N SERVE VARIETY...



YOU NEED CARBON FILM RESISTORS FROM

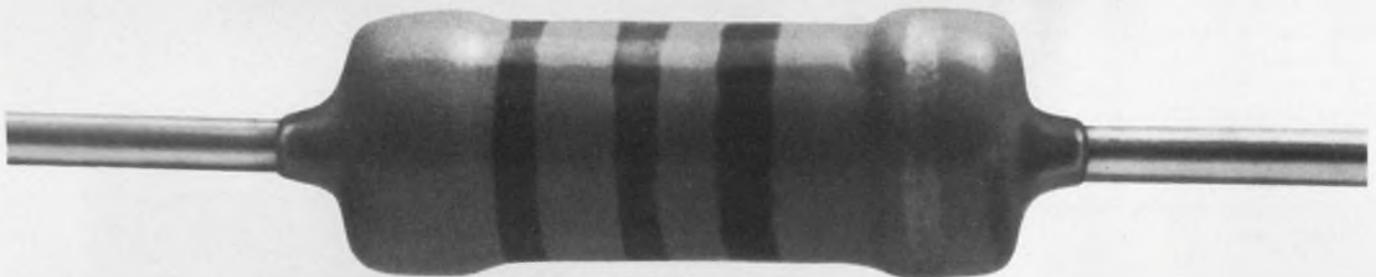

MEPCO/ELECTRA

Carbon comp resistors, like a lot of modern foods, have to be popped into the oven before they're ready for use. But right there, the similarity ends. Because while "brown 'n serve" type foods mean convenience, there's certainly nothing convenient about baking resistors so they'll perform in a circuit with halfway decent stability.

Let's get serious. If you *really* want stability—built-in, all-climate stability—switch over to the high performance, low cost carbon film resistors from Mepco/Electra. Here's why: Under humidity testing, carbon film resistors, will change a maximum of 3% while carbon comps will change anywhere from 5 to 15%. Your circuit operates more reliably with carbon film resistors, and you need no designed-in compensations for future climatic changes.

The temperature coefficient of carbon film resistors is -300 ± 70 PPM/ $^{\circ}$ C while carbon comps can be anywhere between $+1000$ and -500 PPM/ $^{\circ}$ C. Carbon films give you a more precise circuit

over a broad temperature range. There's no need to put the accuracy burden on other parts, and you'll be able to cut down sharply on costs.

Carbon film resistors are calibrated to value during manufacture and offered in ± 2 and $\pm 5\%$ tolerances, while carbon comps are culled to provide tolerances of ± 5 , ± 10 and $\pm 20\%$. There's less drift, greater precision with carbon film resistors, and you'll require less critical characteristics in other circuit parts.

The decision is clear. Mepco/Electra carbon film resistors can give you the high stability, high reliability performance at low cost that carbon comp resistors can't deliver at any cost. If anyone tells you otherwise, it's only a half-baked theory!

For further technical data and samples contact your nearest representative for top quality Mepco/Electra products.

Columbia Road, Morristown, N.J. 07960
(201) 539-2000



CIRCLE NUMBER 20

OUR CUP RUNNETH OVER

Thanks.

Since we offered our UGLY MUG™ we've been flooded with quotation requests and we love it. If you're one of the engineers that got one of our quotes, you probably love it too.

Because we're the company that makes the modular dc supplies that solve 90% of your computer peripheral and instrumentation problems for as little as 53¢/watt, 16 voltages up to 28V and currents to 100A; $\pm 0.1\%$ regulation, ripple-and-noise; remote sensing; spike suppression; fold-back current limiting; and 120/240V inputs. All standard features, not high-cost options.


And we've got a complete custom capability that can give you 4, 5 or more outputs, with increased currents and higher voltages. Provide power sequencing and failure detection. Or even build you a complete UPS. And none of it costs much more—or takes much longer—than our standard supplies.

If you missed all this the first time around, you've still got a second chance: just send us an RFQ with "UGLY LIVES" scrawled, scribbled or typed across it and we'll get back to you with a quote and a free UGLY MUG.

But do it now—this has got to be the best offer you've seen all day.

Elexon Power Systems 
3131 S. Standard Ave., Santa Ana, CA 92705 714/979-4440

CIRCLE NUMBER 21

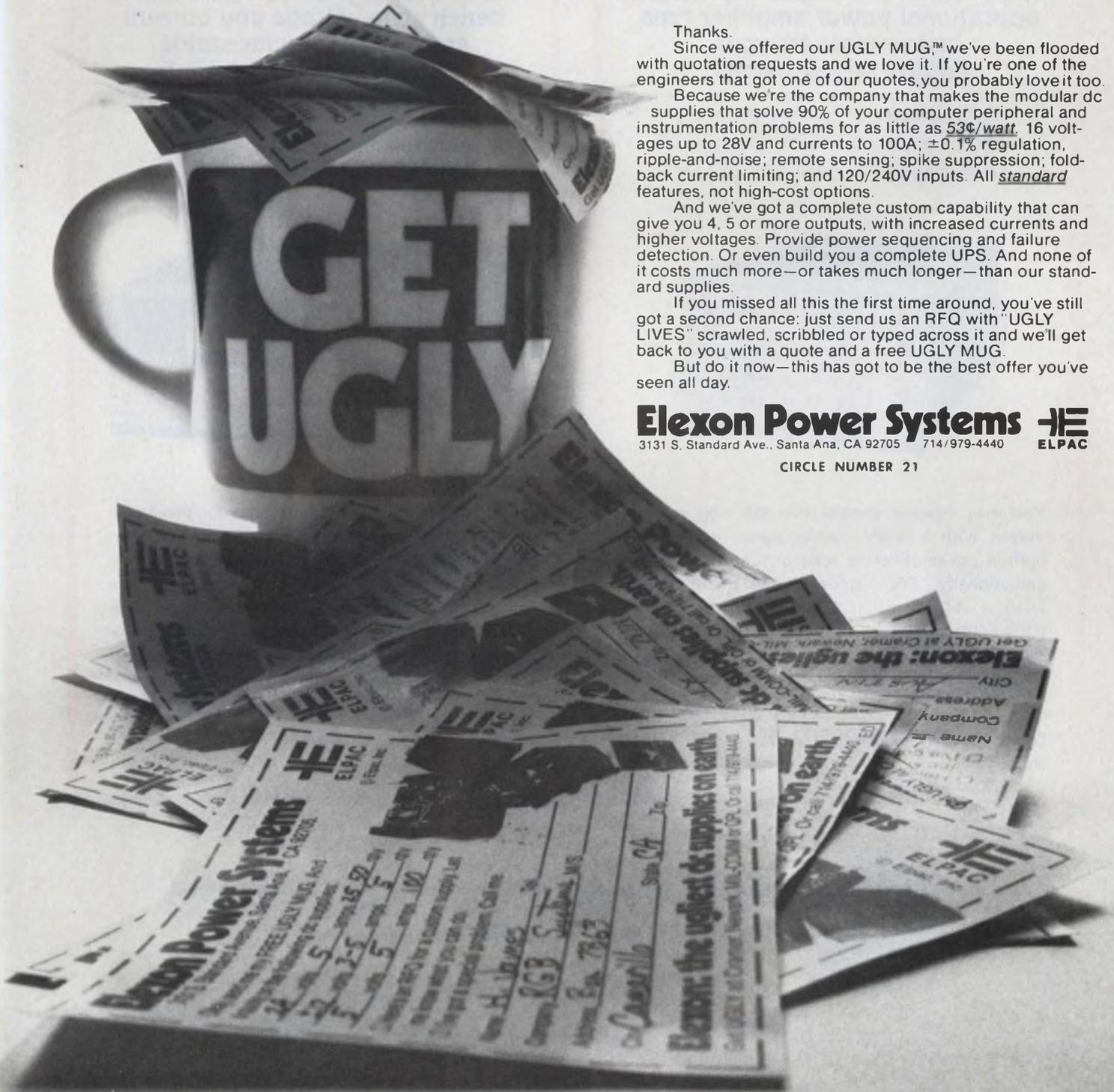

for your HIGH VOLTAGE NEEDS KEPCO offers a choice:

OPS

group IXB

High Speed (no output capacitor) operational power amplifier-type instruments for your control requirements

- OPS 500B: 0–500V @ 40 mA
- OPS 1000B: 0–1000V @ 20 mA
- OPS 2000B: 0–2000V @ 10 mA



You may exercise control over the high voltage output with a 0–5V control signal, or use the built-in pre-amplifier to scale or sum your inputs operationally. The output follows input signals with a 100 μ sec programming time constant (OPS 500B). Current limit is both adjustable and electrically programmable.

- Slew Rate Limit 1 V/ μ sec.
- Gain 10^6 V/V
- Offset Voltage (for Load) <10 μ V
- Noise 0.01% of E_o or 15 mV rms

APH

AUTOMATIC CROSSOVER

Conventionally filtered (low noise) bench style voltage and current stabilizers for your stable high voltage requirements

- APH 500B: 0–500V @ 40 mA
- APH 1000B: 0–1000V @ 20 mA
- APH 2000B: 0–2000V @ 10 mA



Control voltage with a 10-turn precision panel control (or program like the OPS). Another 10-turn panel control adjusts the output current. LED annunciators signal operation in either voltage mode or current modes. A built-in "uncommitted pre-amplifier" is available for scaling or summing programming inputs. Output is monitored on a pair of 2½" meters.

- Stabilization (for Load) <0.005%
- 8-hour Drift <0.01%
- Noise <1 mV rms

Write Dept.
FG-05



Kepeco high voltage power supplies are designed with your needs in mind. Our Catalog describes models ranging up to 5000 volts; up to 200 watts and includes both unipolar and bipolar instruments.

with KEPCO you're in control!

Washington Report

NASA to develop hand-carried satellite ground terminals

The National Aeronautics and Space Administration is developing a technology base to support a new family of communication satellites for the 1980s. Trends indicate that both fixed and mobile terminals will be smaller and cheaper, and that many will be hand-carried.

The new services would aid in search and rescue and in disaster warning, would collect environmental data from thousands of floating or fixed unattended platforms throughout the world and would offer such capabilities as two-way video and voice transmissions.

NASA will continue research in high-power transmitters and in sensitive receivers. Another component of interest is an antenna that has commandable, adaptive beam contouring for confining transmissions to selected geographic areas.

Because of the growing demand for frequency allocations and the steadily aggravated spectrum crowding on lower frequencies, NASA will maintain current efforts to alleviate overcrowding, while also pursuing a long-range interest in opening up higher frequencies in the spectrum, which are still unused.

Lasers gain status in energy program

The Energy Research and Development Administration has realigned its laser and electron-beam fusion programs and its laser-isotope separation program in recognition of the increasing importance of lasers in the energy field.

Both were formerly under ERDA's Division of Military Applications. Now laser and electron-beam fusion programs will come under a newly created Division of Laser Fusion. Laser isotope separation programs move over to the Division of Nuclear Research and Application as part of ERDA's long-range plan for nuclear fuel enrichment.

ERDA has received proposals for four enrichment projects from private industry, both for building the conventional gaseous-diffusion plants, and for building plants that would use the newer centrifuge approach. But the agency has announced interest in an enrichment approach—laser isotope separation—that might have an even lower cost. Its goal is construction of a laser-enrichment plant by late 1980s.

Patent system may be overhauled

Inventors shouldn't get their hopes up too soon, but reform of the nation's patent system is on the way. Patents in the future may cost less to gain, less to maintain, be less susceptible to challenge because they'll

be better validated, and have a better image around the world.

These are some of the heralded benefits of S. 2255, "The Patent Act of 1975," which sailed through the Senate so quickly on Feb. 26 that opponents were caught flatfooted. The bill was passed by a voice vote, without any debate, and sent to the House. Angry protests are expected from such groups as the organized patent bar and the furor will likely produce intensive hearings in the House.

Basically, the reform measure doesn't change any of the substantive portions of the 1836 law. While the patent system was codified in 1952, there have not been significant changes in 140 years, notes Sen. Philip Hart (D-MI), a prime sponsor.

He says the bill will update the present antiquated administrative setup, provide for a more rigorous examination by the Patent and Trademark Office of patent requests, and require greater disclosure of prior art to that office by the applicant. Included in the measure are provisions for lowering and deferring fees to private inventors and small businesses.

Government's contracting procedures to be streamlined

The powerful Senate Operations Committee is now considering landmark legislation that would overhaul the Federal government's \$70 billion a year contracting activities.

Introduced by Sen. Lawton Chiles (D-FL), S. 3005, "Federal Acquisition Act of 1976," is designed to legislate changes recommended by the Commission on Government Procurement that couldn't be made administratively.

The bill "directly seeks to substitute effective competition for regulation" and is aimed at relieving a wide range of government surveillance, "but only where effective competition is at work," Chiles says.

A key provision requires the Office of Federal Procurement Policy to establish a single, simplified set of regulations to cover all agencies of the Federal government by meshing regulations generated by the Armed Services Act and the Federal Property Act.

Other titles in the bill define the proper circumstances for agency use of acquisition procedures by competitive sealed bids, competitive negotiations (with an exception for single-source procurements) and acquisition by competitive small-purchase procedures.

Capital Capsules: NASA's Nimbus 6 meteorological research satellite gets a new task this summer—tracking a Model-T Ford in the American Bicentennial Around-the-World Auto Race, an enactment of the Great Race of 1908. A 30-pound electronic package will be carried by a 1914 Model T to transmit the ground speed of the moving car to the Random Access Measurement System carried by the pole-to-pole orbiting satellite. . . . The Air Force has issued requests for proposals to 31 small business firms for a **dual-bank radar beacon transponder set (AN/TPN-28)**. The self-contained, portable 30-pound units are for forward air controllers. Contract award is set for midyear. The Air Force will buy 12 preproduction and 800 operational sets with the Marine Corps slated to get 340 of them. . . . The Navy has awarded Norden Div. of United Technology a development contract for a **lightweight, high-frequency transceiver for shipboard use**. The millimeter-wave communicator weighs 5 lb and offers voice, video or data transmissions over distances of up to 20 miles. Its narrow beamwidth minimizes interception.

Dialight sees a need:

Need: A new computer-grade switch at a price you can afford.

LOW COST • COMPUTER GRADE QUALITY • DESIGN FLEXIBILITY • GOLD OR SILVER CONTACTS • CHOICE OF TERMINALS • MOMENTARY OR ALTERNATE SWITCHING ACTIONS • SPDT, DPDT • DESIGNED TO MEET UL SPECIFICATIONS • UNIFORM FRONT PANEL APPEARANCE AND REAR PROJECTION • MATCHING INDICATOR LIGHT • FRONT MOUNTING SNAP-IN BEZELS—4 SIZES/SHAPES TO CHOOSE FROM • REAR MOUNTING SWITCH WITH ANTI-ROTATION FEATURE • CHOICE OF OVER 200 CAP SHAPES, SIZES AND COLORS • CHOICE OF ENGRAVED, HOT STAMPED OR REPLACEABLE LEGENDS.

Dialight's low cost 554 series switches are available in a wide selection of rear panel and front bezel mounting types. Switches are available with silver or gold contacts for wide range of applications; operating life is 250,000 operations.

Fingertip grips permit easy cap removal . . .

lamp replacement is from front of panel . . . no special tools needed.

Caps are available with or without underlying color filter in 5/8" and 3/4" square, 5/8" x 3/4" and 3/4" x 1" rectangles. At Dialight it's your choice because we see your need.

DIALIGHT

Dialight, A North American Philips Company
203 Harrison Place, Brooklyn, N. Y. 11237
(212) 497-7600

CIRCLE NUMBER 23




\$1.65
EACH

P/N 554-1121
(1K PRICING)

See
Dialight

TEXAS INSTRUMENTS SUPPORT, SOFTWARE

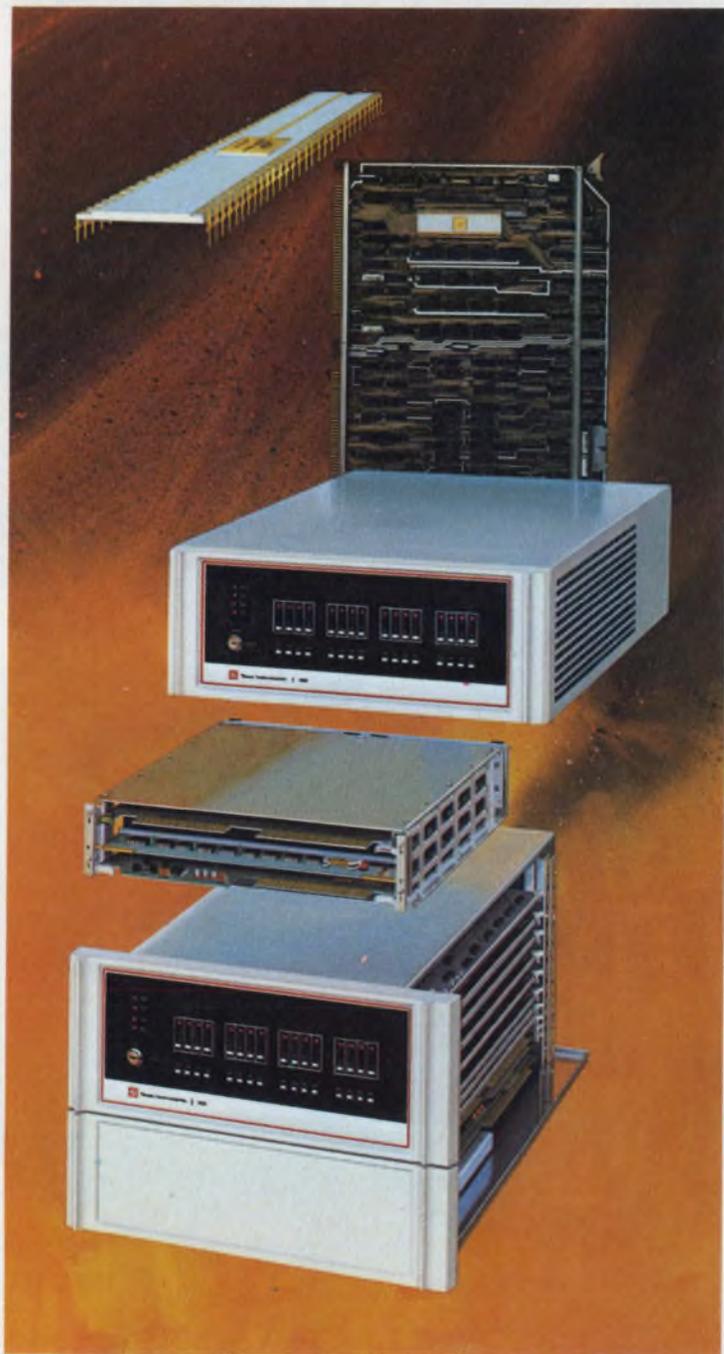

The TI 990 computer family has all the ingredients.

The TI concept of what a computer family should be goes beyond producing the most reliable and cost-effective hardware around. To us, that's basic. The extra dimension is usability, and this means software and support.

The TI 990 computer family has all the ingredients. We make every member of the family ourselves, and we make them all software compatible from bottom to top.

Complete software libraries, as well as memory-resident and disc-based operating systems, support real-time and multi-tasking operations. We offer FORTRAN, COBOL and BASIC languages. Cross-support on timesharing networks allows early development of your own applications programs.

The TMS 9900 Microprocessor... The Technology Leader

The advanced capabilities of the 990 family result from a TI milestone in MOS technology... the TMS 9900 single-chip, 16-bit microprocessor. With its high-speed interrupt capability, hardware multiply-and-divide, and versatile instruction set, the TMS 9900 delivers the kind of computing power you'd expect from a 16-bit TTL computer. And it's the best microprocessor going for terminals, machine monitoring and control, and many other applications.

Because the TMS 9900 provides the instruction set for the new 990/4 microcomputer and 990/10 minicomputer, software developed for the low-end computers will be compatible with the higher performance models... and with a minimum of interface and software adaptation.

Versatile Operating Systems

The TX990 Executive Operating System Software uses either the 990/4 or 990/10 computer for low-cost multi-task control, requiring a minimum of peripheral support. The modular construction of TX990 allows users to select only the functions required for efficient memory usage, leaving more memory availa-

UMENTS HAS RE AND HARDWARE.

ble for application software.

The 990/10 Disc System Software accents the mass-storage, random-access features of the disc with extensive file management and the multi-tasking features of the DX10 Operating System. The system software package includes a multi-pass 990 assembler, link editor, interactive source editor, and numerous other utilities that support easy implementation of application programs.

Flexible Packaged Systems

TI offers two packaged program development systems and a prototyping system for the user who needs his own stand-alone system for software and firmware development of application programs.

These packaged systems provide a flexible method of implementing early project development. These include the low-priced 990/4 Program Development System and the powerful 990/10 Program Development System. The 990/10 system combines the power of the 990/10 minicomputer with the disc-based DX10 operating system and an extensive set of software development tools. The standard package includes the 990/10 minicomputer with 64K bytes of error-correcting memory, ROM loader and diagnostics, 3.1-million byte removable disc kit with accompanying peripherals, and a complete software development package. And, at \$24,500, this system costs at least 20% less than comparable equipment from other manufacturers.

For developing firmware modules, there is a \$5950 prototyping system which includes a 990/4 computer with 16K bytes of memory and programmer's front panel, and a "Silent 700*" twin-cassette ASR data terminal. Also, an optional PROM programming kit is available for



developing read-only memory.

In addition, we provide a wide variety of program development utilities for the 990 family. There is communications software that supports either synchronous or asynchronous data transmission, and can operate with the TX990 or the DX10.

Support from the start

We offer complete training and applications assistance, plus a nationwide service network backed by TI-CARE[†], our remote diagnostic, service dispatching and real-time field service management information system.

For more information, call your nearest TI office or write Texas Instruments Incorporated, P.O. Box 1444, M/S 784, Houston, Texas 77001.

Or, phone Computer Equipment Marketing at (512) 258-5121.



See the 990 Family at the Computer Caravan and NCC.

Arlington, Va. (703) 527-2800 • Atlanta, Ga. (404) 458-7791 • Boston, Ma. (617) 890-7400 • Chicago, Il. (312) 671-0300 • Clark, Nj. (201) 574-9800 • Cleveland, Oh. (216) 464-4990 • Costa Mesa, Ca. (714) 540-7311 • Dallas, Tx. (214) 238-5318 • Dayton, Oh. (513) 253-6128 • Denver, Co. (303) 751-1780 • Detroit, Mi. (313) 353-0830 • El Segundo, Ca. (213) 973-2571 • Hamden, Ct. (203) 281-0074 • Houston, Tx. (713) 494-5115 • Indianapolis, In. (317) 248-8555 • Milwaukee, Wi. (414) 475-1690 • Minneapolis, Mn. (612) 835-5711 • Mobile, Al. (205) 344-8082 • Philadelphia, Pa. (215) 628-3434 • Phoenix, Az. (602) 249-1313 • San Francisco, Ca. (415) 392-0229 • Seattle, Wa. (206) 455-1711 • St. Louis, Mo. (314) 569-0801 • Sunnyvale, Ca. (408) 732-1840 • Winter Park, Fl. (305) 644-3535 • Amstelveen, Holland 020-456256 • Bedford, England 0234-58701 • Beirut, Lebanon 452010 • Bruxelles, Belgium 733 96 24 • Cheshire, England 061-442-8448 • Copenhagen, Denmark 01/91 74 00 • Essen, Germany 0201/20916 • Frankfurt, Germany 0611/39/90/61 • Freising, Germany 08161/801 • Helsinki, Finland 90 408 300 • Milan, Italy 02 688/8051 • Montreal, Canada (514) 341-5224 • Nice, France (93) 20 01 01 • Oslo, Norway 02-68 94 87 • Paris, France (1) 630-2343 • Rome, Italy 839 4792 • Slough, England 0753-33411 • Stockholm, Sweden 62 71 59/62 71 65 • Sydney, Australia 831-2555 • Tokyo, Japan (03) 402-6181 • Toronto, Canada (416) 889-7373 • Vancouver, B.C. (604) 689-8017

TEXAS INSTRUMENTS
INCORPORATED

*Trademark of Texas Instruments

†Service Mark of Texas Instruments

CIRCLE NUMBER 24

How to Win at the Microprocessor Game



Today everyone wants to get into the game. But the stakes are high and the rules just aren't very clear.

Now the M-8 Educator tips the odds in your favor by providing in one versatile package everything you need to write and evaluate programs for the F-8 microprocessor. Or use it as a stand-alone control system or operate it as a data terminal. No matter what your application you win with the M-8 Educator.

Software Development. The M-8 Educator's highly flexibly resident monitor contains user callable subroutines for I/O, memory interrogation, and program development. Standard memory is 4K bytes static RAM expandable to 16K bytes per board (system expandable to 64K bytes). An optional E-PROM card contains a CRA (Conversational Resident Assembler) with space for an additional 5K bytes of user-definable memory.


The program is entered on the ASCII-encoded, Hall-effect keyboard in easily-learned F-8 assembly language and the high-resolution, 12 inch diagonal, CRT gives a 64 character by 31 line display. For the hard copy a 110 baud, 20ma. loop, TTY I/O is provided.

Industrial/Process Control. The M-8 Educator's Bus Extension Module provides

a powerful interface capability for a wide variety of user applications. Available at the 86-line card edge connector are power, address lines, data bus, all important system control lines, and four, 8-bit parallel, TTL-compatible I/O ports. From plastics manufacturing to medical instrumentation the M-8 Educator holds a winning hand.

Data Communications. Matrix Mode operation (selected via rear-panel switch) disables the self-addressed write operation of the CRT display module. Display refresh memory is then assigned a 2K byte address block on the F-8 system bus. This capability allows the user to treat the CRT as a matrix of "display cells", each with a unique address, providing virtually total freedom in display format and control response, all in software.

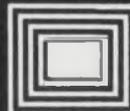The ante? That's the best part. Only \$1895 complete with hardware and programming manuals. Delivery is stock to 3 weeks ARO. So whatever your application game call and raise Don Cartner at 913/492-7350. He'll be happy to deal you in. Technical Communications, Inc., P.O. Box 306, Olathe, Ks. 66061.



TECH-COM

M-8 Educator, CRA, and Matrix Mode are registered trademarks of Technical Communications, Inc.

Microprocessor Design

Diagnostic instrument simplifies μ P-system testing and debugging

The first diagnostic instrument to combine the features of both logic analyzers and μ C-development systems can be used to simplify 8-bit μ P-system testing and debugging. Called the MPA-1 Microprocessor Analyzer, it is produced by Motorola Data Products (455 E. North Ave., Carol Stream, IL 60187. 312-690-1400).

The MPA-1 cabinet and display typically works in conjunction with a 40-pin IC test clip that clamps over the μ P DIP package to lift address and data signals directly from the DIP mounting pins. The analyzer captures 32-word segments of program execution and displays the information on a 9-in. CRT screen.

Words are shown directly in hexadecimal form, which allows direct comparison with written program instructions, without the need for manual binary-to-hexadecimal translation. Each hex word consists of four characters of address, plus two characters of associated data-bus information.

By using individual probe buffers, the instrument can interface directly with the



following: the 8080 from Intel, Advanced Micro Devices, Texas Instruments and NEC; the PPS-4 from Rockwell; the 6800 from Motorola and American Microsystems; the 6500 from MOS Technology and Synertek; and Motorola's

(continued on page 50)

Full microcomputer comes complete with power supply

A ready-to-use, μ P-based microcomputer, the Micro 68, comes complete with its own integral power supply and 16-button keyboard. A 6-digit LED display and 128 words of RAM are also included. The Micro 68 is built around the Motorola/AMI 6800 μ P, costs \$430 and was developed by Electronic Product Associates (1157 Vega St., San Diego, CA 92110. 714-276-8911).

In addition, the 512 John Bug PROM that's included contains all the software necessary to load programs easily, inspect and edit them as necessary, insert break points for debugging, and to execute them. Memory expansion to 64 k and full 16-bit I/O can be accomplished through edge connectors.

The Micro 68 comes in a hardwood cabinet with a transparent smoked-plexiglass lid and measures 9 x 16 x 2 in. Delivery is from stock.



CIRCLE NO. 552

MICROPROCESSOR DESIGN

(continued from page 49)

Exorciser system.

The MPA-1 has three basic operating modes. In the Start Display mode, the instrument monitors program execution starting with the trigger-word address and adding the next 31 words in their order of execution. This allows the tracing of program flow, algorithms, interrupt-handling and I/O routines.

In the End Display mode, the MPA-1 can work backwards from illegal operations to track down the source of hardware and software errors. And in the Free Run mode, continuous address and data information are displayed to locate hardware faults and program hang-ups. The instrument can be stopped in this mode; program execution can then be retraced to the source of a mistake.

Other features include Start Delayed Triggering, in which the 32-word display can be delayed digitally up to 65-k clock pulses. This feature allows examination of the inner workings of loops, the results of subroutine

calls and other uses in which desired data does not immediately follow the trigger word.

End Delayed triggering, with a delay of 16 clock cycles, provides a before-and-after display in which the trigger word appears in the center of the 32-word block, allowing simultaneous examination of both preceding and following μ P activity.

Besides the IC test clip, the instrument is furnished with a standard 40-pin connector and a 40-conductor cable. Also, at the rear of the MPA-1 cabinet, two plugs allow access to address-recognition and buffered-clock signals for external counter or oscilloscope triggering.

The MPA-1 package, complete with all three probe connectors plus a choice of one of the available probe buffers, is priced at \$2985. Additional probe buffers cost \$100 each. The MPA-1 cabinet measures 8 × 13 × 12 in. and weighs 24 lb.

CIRCLE NO. 551

Low-cost cross-assembler runs on IBM 360/370

A cross-assembler for the 8080 μ P, designed to run on an IBM 360/370, is claimed to provide a low-cost alternative to the Intel MAC80 assembler available through time-sharing vendors. The MASM80 program is written in Fortran/BAL and executes its operations in under 100 k of memory.

Well Test Data (P.O. Box 7081, Kansas City, MO 64113. 816-444-5519) is offering a source deck and documentation set for \$55. Extra features of the MASM80 include direct punching of BNPF decks for PROM programming, object code listing in both octal and hex, and ASCII constant generation with the parity bit either set or reset.

CIRCLE NO. 553

μ P emulator offers fourfold increase in throughput

A microprocessor emulator that has from two to four times the throughput of the 8080 μ P but is completely software-compatible has been designed by Technology Marketing Inc. (3170 Red Hill Ave., Costa Mesa, CA 92626. 714-979-1100).

Called the TMI 8080E, the emulator consists of 79 multiple-sourced ICs and occupies less than 80 in.² of circuit board area. It requires just 180 ns for a machine cycle and is not as rigidly limited as the 8080 μ P, in regard to memory timing.

A substantial advantage of the TMI 8080E, according to the firm, is that the 8080E can drive 10 TTL loads instead of the single-TTL load that can be driven by the 8080. In a system, this improvement in drive capability means that a large 64-k × 8-bit memory can be built into the system along with eight I/O modules, without additional buffering.

(continued on page 52)



Announcing a giant reduction in the Nova line.

You're looking at a whole new family of NOVA[®] computers. microNOVA. A microprocessor chip, a microcomputer board and a complete MOS mini-computer. All based on the little thing on the tip of the finger.

mN601. The microNOVA CPU.

It's a full-blown, 16-bit NOVA computer. Manufactured by Data General. And fully supported by NOVA software.

And it's not a NOVA computer in name only. This chip has all the NOVA registers, internal data paths and computational elements. The NOVA multifunction instruction set. The NOVA multiple addressing modes. And the NOVA 3 hardware stacking. Plus things that used to be NOVA options: multiply/divide, real-time clock and power fail/auto restart. All standard at no additional cost.

The difference is, all that NOVA has been reduced to a single chip that measures only 225 mils by 244 mils.

Which was no small accomplishment.

For those who need more than a chip, there's the microNOVA computer-on-a-board. A complete, fully-buffered microcomputer that comes with 2K or 4K words of RAM on a single 7½" by 9½" board. You can add on more RAM in either 4K or

8K increments, or PROM boards with up to 4K words. Plus terminal interfaces, general purpose interfacing boards, card frame, power supply and PROM burner.

And for those who need more than a board, there's a fully-packaged 4K word MOS microNOVA mini. It comes with power supply and turnkey console. In 9 and 18 slot versions. Into which you can place as much as 32K words of RAM or PROM. And still have plenty of room left over for I/O.

There's even a microNOVA system specifically for program development. A complete system, with dual diskette drive, terminal and our RDOS-compatible Disc Operating System. Or you can use a Nova 3 system with RDOS. The best development software you can get.

And no matter which microNOVA product you get, you get to use NOVA software like FORTRAN IV. Software that's in use in over 20,000 installations all over the world. So you know it's going to work right the day you get it.

Want to know something else?

Call our toll free number.

800-225-9497.

microNOVA

Nova is a registered trademark of Data General Corporation.

DataGeneral

• Data General, Route 9, Southboro, Mass. 01772 (617) 485-9100. Data General (Canada) Ltd., Ontario.

Data General Europe, 15 Rue Le Sueur, Paris 75116, France. Data General Australia, Melbourne (03) 82-1361/Sydney (02) 908-1366.


(continued from page 50)

The emulator can cut system size when clock, bus driver, memory and input/output modules are added to the basic 8080 IC. The TMI 8080E single-board processor replaces the 8080 μ P, the 8228 controller and bus driver, the 8224 clock generator, the 8216 bus drivers, and the associated circuitry.

The price of the emulator starts at \$1200 for a single-unit purchase, and prices drop to \$200 in production quantities. Delivery time is 6 to 8 weeks.

CIRCLE NO. 554

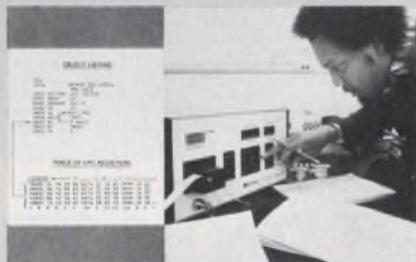System development tool works with PPS-8 μ Ps



The Assembler, a system-development tool, can help debug and develop 8-bit PPS (parallel-processing system) microcomputers. The new design aid permits real-time software check-out of systems with peripherals, and makes possible generation of ROM mask codes and encoding of PROMs and EAROMs for the field testing of prototypes.

Designated the PPS-8MP, the instrument comes complete with software and comprehensive programming and operating manuals. It costs \$3450 and was developed by Rockwell (3310 Miraloma Ave., P.O. Box 3669, Anaheim, CA 92803. 714-632-1650).

PPS-8MP software consists of a ROM-resident supervisory program that provides utility and debugging functions, and RAM-resident assembly and text-editing programs.

The assembly and text-editing software is supplied on tape and is loaded into the machine's RAM with a TTY, a TI 733 ASR tape reader, or an optional high-speed reader. Memory can be expanded in 2-k-byte increments to a total of 16-k bytes by internally adding RAM or EAROM modules. Even more memory can be added by using an optional bus extender or 8-k byte RAM module.

CIRCLE NO. 555

8080-compatible microcomputer uses bipolar logic for speed

Up to four times the speed of typical 8080 μ P-based systems is offered by a new bipolar-based microcomputer, the System 80. It is fully compatible with the 8080 μ P, can be purchased with either core or semiconductor memory and has an extended addressing capability of up to 1 megabyte of memory. The μ C is made by Electronic Memories and Magnetics (12621 Chadron Ave., Hawthorne, CA 90250. 213-664-9881).


Inside the System 80 is an asynchronous, MSI central processor, a minimum of 16-k, 8-bit words of read/write memory, a direct-memory-access (DMA) capability, a ROM bootstrap loader, an RS-232-C2 interface, an operator's panel and a five-slot chassis that measures 5.25-in. high and has an integral power supply.

Three basic speed/memory configurations are available: the first is a core memory with a 650-ns cycle time; the second is an NMOS semiconductor memory with a 450-ns cycle time; and the third version is a high-speed NMOS unit with a 180-ns cycle time. Memory capacities range from 16 to 64-k bytes on a single board. This approach allows the user to set up a complete 256-k byte system in a 7-in. chassis.

Basic system prices begin at \$4150 for 16-k bytes of core memory or \$4500 for 32-k bytes of semiconductor memory. Other semiconductor based systems offer 64-k bytes for \$5650, 256-k bytes for \$14,000 and 1-M byte for \$44,000. System 80s are available from stock.

CIRCLE NO. 556

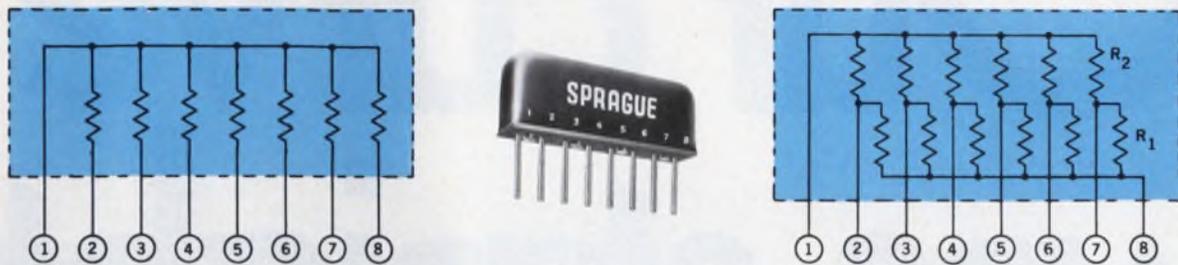NOW! SINGLE IN-LINE RESISTOR NETWORKS WITH IMPROVED PERFORMANCE



BOARDABLE AND AFFORDABLE

Low Cost and **High Density Configuration** are only two of the features of Sprague Type 216C Metanet® Resistor Networks. Now, you can also enjoy the benefits of improved power dissipation, better temperature coefficient of resistance, and closer standard resistance tolerance.

Save Board Space. Single in-line design permits vertical installation, which allows more units to be seated in less space. This mounting style also results in improved high-frequency performance and significant in-place cost reduction.

Better TCR. Typical temperature coefficient of resistance is within ± 200 ppm/°C, cutting previous allowable limit almost in half.

Up-graded Power Dissipation. Individual terminating, pull-up/pull-down, and interface networks are capable of dissipating 250 mW per resistor at 70°C, an increase of 100% over previous designs.

Closer Resistance Tolerance. Standard resistance tolerance for each resistor is $\pm 2\%$, with other tolerances between $\pm 1\%$ and $\pm 5\%$ available on special order.

Proven Product Line. Sprague has more than fifteen years of experience in the development and manufacture of precision thick-film resistor networks, which include individual terminating, pull-up/pull-down, interface, and dual terminating designs.

*For complete technical data, write for Engineering Bulletin 7041A to:
Technical Literature Service, Sprague Electric Co.,
347 Marshall Street, North Adams, Mass. 01247.*


THE BROAD-LINE PRODUCER OF ELECTRONIC PARTS

CIRCLE NUMBER 27



Our curve was straight.

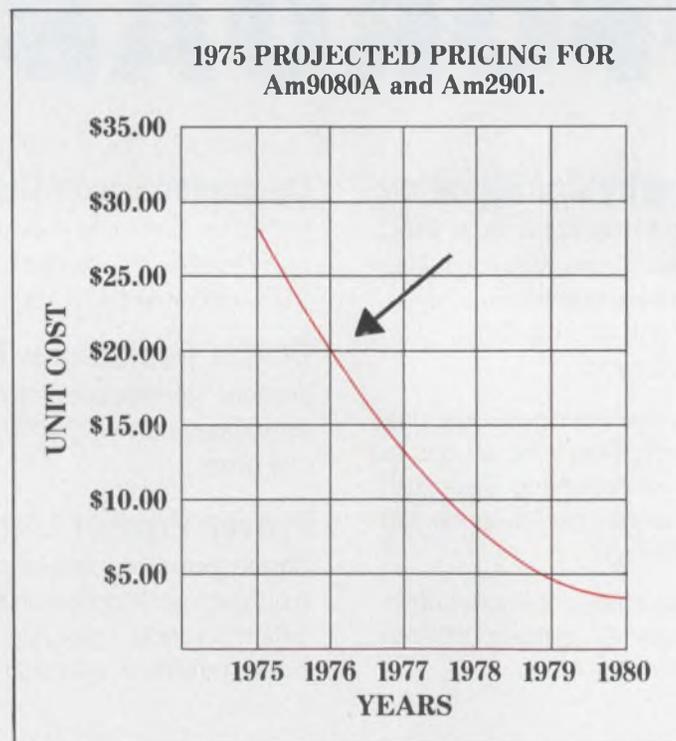Advanced Micro Devices announces the 100-piece price for the Am9080A and Am2901: \$21.00.
Just like we said.



Last year, we predicted the price would be just over \$20.00. We even drew a curve. Now it's happened. And that's only the beginning. Look:

Am9080A. It's built with an advanced ion-implanted, n-channel, silicon-gate process that permits versions with speeds to 250 nanoseconds cycle time (one microsecond instruction time). Our low power (800mW maximum) gives you cooler running systems, less power drain and better reliability. The superior output drive (3.2mA @ 0.4V) gives increased design flexibility and improved margins.

Am2901. It's bipolar, for systems that rely on

high speed. It can do a 16-bit register-to-register add in just 145 nanoseconds. It has 16 working registers in a cycle-saving, two-address architecture, and is controlled by nine instruction lines that permit it to do almost anything you can think of.

Another thing. Advanced Micro Devices offers a full line of support circuits for either unit—support circuits that optimize your system, not compromise it.

Whether you can best use the MOS Am9080A or the bipolar Am2901, you can now do it for less. \$21.00 in 100-piece quantities.

Just like the curve said.

Am9080A System Circuits

| AMD Part Number | Description | Availability |
|--|---|---------------|
| CPU | | |
| Am9080A/-2/-1/-4 | Speeds to 250 nsec 0 to 70°C | In Dist Stock |
| Am9080A/-2 | Speeds to 380 nsec -55 to +125°C | In Dist Stock |
| Static Read/Write Random Access Memories | | |
| Am9101A/B/C/D | 256 x 4 Speeds to 250 nsec | In Dist Stock |
| Am9101A/B/C | 256 x 4 Speeds to 300 nsec | In Dist Stock |
| Am9102A/B/C/D | 1K x 1 Speeds to 250 nsec | In Dist Stock |
| Am9102A/B/C | 1K x 1 Speeds to 300 nsec | In Dist Stock |
| Am9111A/B/C/D | 256 x 4 Speeds to 250 nsec | In Dist Stock |
| Am9111A/B/C | 256 x 4 Speeds to 300 nsec | In Dist Stock |
| Am9112A/B/C/D | 256 x 4 Speeds to 250 nsec | In Dist Stock |
| Am9112A/B/C | 256 x 4 Speeds to 300 nsec | In Dist Stock |
| Am9130A/B/C/E | 1024 x 4 Speeds to 200 nsec | In Dist Stock |
| Am9140A/B/C/E | 4096 x 1 Speeds to 200 nsec | In Dist Stock |
| Dynamic Read/Write Random Access Memories | | |
| Am9050C/D/E | 4K x 1 Speeds to 200 nsec | In Dist Stock |
| Am9060C/D/E | 4K x 1 Speeds to 200 nsec | In Dist Stock |
| Mask Programmable Read-Only Memories | | |
| Am9208/B/C/D | 1K x 8 Speeds to 250 nsec | Available Now |
| Am9214 | 512 x 8 mask programmed Speeds to 500 nsec | Available Now |
| Am9216B/C | 2K x 8 mask programmed Speeds to 300 nsec | Available Now |
| Erasable Read-Only Memories | | |
| Am9702 | 256 x 8 Speeds to 1.0 μsec | In Dist Stock |
| Am1702A | 256 x 8 Speeds to 1.0 μsec | In Dist Stock |
| Am2708 | 1024 x 8 Speeds to 450 μsec | 2nd Q 1976 |

| AMD Part Number | Description | Availability |
|--|-----------------------------------|---------------|
| Processor System Support Circuits | | |
| Am8212 | 8-bit I/O Port | In Dist Stock |
| Am8224 | Clock Generator | In Dist Stock |
| Am8228 | System Controller | 2nd Q 1976 |
| Am8216/26 | Bus Transceiver | 2nd Q 1976 |
| Am25LS138 | 1 of 8 Decoder | In Dist Stock |
| Am9555 | Programmable Peripheral Interface | 2nd Q 1976 |
| Am9551 | Serial Communications Interface | 2nd Q 1976 |
| CPU: 9080A = 480 nsec -2= 380 nsec -1= 320 nsec -4= 250 nsec Mem: A= 500 nsec B= 400 nsec C= 300 nsec D= 250 nsec E= 200 nsec | | |

Am2900 System Circuits

| AMD Part Number | Description | Availability |
|------------------|---|---------------|
| Am2901 | 4-Bit Microprocessor Slice | In Dist Stock |
| Am2902 | Carry Lookahead Chip | In Dist Stock |
| Am2905 | 4-Bit Transceiver For Open Collector Bus | In Dist Stock |
| Am2906 | 4-Bit Transceiver For Open Collector Bus With Parity Generator/Checker | In Dist Stock |
| Am2907 | 4-Bit Transceiver For Open Collector Bus With Single Data Input | In Dist Stock |
| Am2909 | Microprogram Sequencer | In Dist Stock |
| Am2911 | Minimicroprogram Sequencer | 2nd Q 1976 |
| Am2914 | 8-Level Priority Interrupt | 3rd Q 1976 |
| Am2915 | 4-Bit Transceiver For Three-State Bus | 2nd Q 1976 |
| Am2916 | 4-Bit Transceiver For Three-State Bus With Parity Generator/Checker | 2nd Q 1976 |
| Am2917 | 4-Bit Transceiver For Three-State Bus With Single Data Input | 2nd Q 1976 |
| Am2918 | 1 By 2 Port Register | In Dist Stock |
| Am2919 | Priority Interrupt Expander | 2nd Q 1976 |
| Am2950/51 | 256-Bit RAM Open Collector Or Three-State | In Dist Stock |
| Am2952 | 1024-Bit RAM Open Collector | 2nd Q 1976 |
| Am2954/55 | 16-Word By 4-Bit Two Address Register Stack Open Collector or Three-State | 2nd Q 1976 |
| Am2970/71 | 256 By 4 PROM's With Open Collector or Three-State Outputs | In Dist Stock |


Advanced Microprocessors



Advanced Micro Devices • 901 Thompson Place, Sunnyvale, California 94086 • Telephone (408) 732-2400

Distributed nationally by Hamilton/Avnet, Cramer and Schwaber Electronics

CIRCLE NUMBER 28

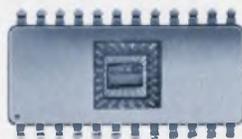

There is no more accurate 12-bit A/D converter on the market ... and it's monolithic.

Differential and overall linearity within $\frac{1}{2}$ LSB. Inherently monotonic operation (and no missing codes). Immunity to noise transients. They all add up to unusually high accuracy for our 8702, a single chip, 12-bit CMOS A/D converter.

The 8702 has some other important advantages, too. CMOS technology means very low power dissipation — typically less than 20 mW. It is easy to use; no active auxiliary components are needed. And its latched parallel outputs are



ideal for inputting to microprocessors or other digital logic.

Compared to modules, the 8702 offers immediate significant cost savings plus the prospect of even

greater future economies due to its monolithic construction. And the savings in PCB real estate go without saying.

The 8702 comes in a 24-pin ceramic DIP. 8 and 10 bit versions are also available. Call or write for the full details today.

TELEDYNE SEMICONDUCTOR

1300 Terra Bella Avenue, Mountain View, California 94043 Tel: (415) 968-9241 TWX: 910-379-6494 Telex: 34-8416

SALES OFFICES:

DOMESTIC: Salem, N.H. (603) 893-9551; Stony Brook, N.Y. (516) 751-5640; Des Plaines, IL (312) 299-6196; Los Angeles, CA (213) 826-6639; Mountain View, CA (415) 968-9241 • INTERNATIONAL: Hounslow, Middlesex, England (44) 01-897-2503; Tiengen, West Germany 7741-5066; Wiesbaden, West Germany 06121-39171; Kowloon, Hong Kong 3-240122; Tokyo, Japan 03-405-5738

CIRCLE NUMBER 29

If I don't know it, it ain't so

A friend of mine had intermittent claudication—a blood-vessel constriction that afflicts many heavy smokers and often leads to amputation. He took massive doses of vitamins and was cured. Another fellow's kidney stones were eliminated by vitamins. And vitamins helped other friends with ailments like high blood pressure, high cholesterol, low energy, headaches, colds, bleeding gums and bursitis.

The average doctor, or the American Medical Association, or the Food and Drug Administration will likely tell you that beyond the nutrition you get in a reasonably balanced diet, vitamins don't really help. Their attitude seems to be that vitamin-deficiency diseases have been licked; nobody gets scurvy or beri-beri anymore; a massive vitamin deficiency can hurt you, but a less-than-massive deficiency has no effect.

If you ask about people who've been helped by vitamins, you get a stock answer; they probably would have gotten better anyway. But what they really mean is probably this: The authorities don't support it, so it can't be so.

And that attitude is too common. Most of us too quickly say, "That can't work. I never heard of it." Even in a profession where we take pride in our creativity, we remain conservative. We shy away from the untried—from material we didn't learn in school or books, and from ideas that don't carry the seal of authority.

It's unfortunate that a powerful precedent for this attitude is set by doctors—whose wisdom and infallibility many of us regard with awe. Doctors, when they don't kill their mistakes, often forget them. For many years they ridiculed the idea that thalidomide could be dangerous. Then overwhelming evidence showed that it mangled unborn babies. And for years the Food and Drug Administration insisted that Red No. 2, which appears innocuously on labels as "artificial coloring," is harmless. The FDA finally conceded that the stuff—widely used in foods, drugs and cosmetics—can cause cancer.

If prestigious authorities like medical doctors and the FDA scoff at ideas that differ from the accepted "wisdom," shouldn't we? Should we cling always to what's safe? Or should we sometimes break away and accept the scorn of authorities?



A handwritten signature in dark ink, which appears to read "George Rostky". The signature is fluid and cursive.

GEORGE ROSTKY
Editor-in-Chief

FOCUS

on
Microprocessors


While diversity usually makes a designer's life easier, with microprocessors it can make comparison—not to mention selection—more difficult than ever.

A wide diversity of architectures, support circuits and design aids from available μ Ps should make it a whole lot easier to pick the right micro. But because microprocessor-based systems must be programmed like conventional computers, you must think of software as well as hardware. Grappling with the intricacies of either could keep you working evenings and weekends, especially since the use of different micros entails different tradeoffs between hardware and software.

Further, the problems of selection may not be helped much by the burgeoning application literature offered with "computers on a chip." You could end up with documentation up to your eyeballs only to discover that key specifications have been inflated or even omitted or that some important characteristics—like operating speed—can't be extrapolated from the mountain of data. Adding to the problems, manufacturers' promotional material may elevate a selling point into an unwarranted selection factor. The prices of microprocessor, or CPU (central processing unit), chips are a case in point.

Manufacturers note that the high-flying 8080 μ P, for example, can be purchased now for about \$20 in production quantities—quite a drop from its initial price of several hundred dollars. For very high quantities, you can get the price under \$10.

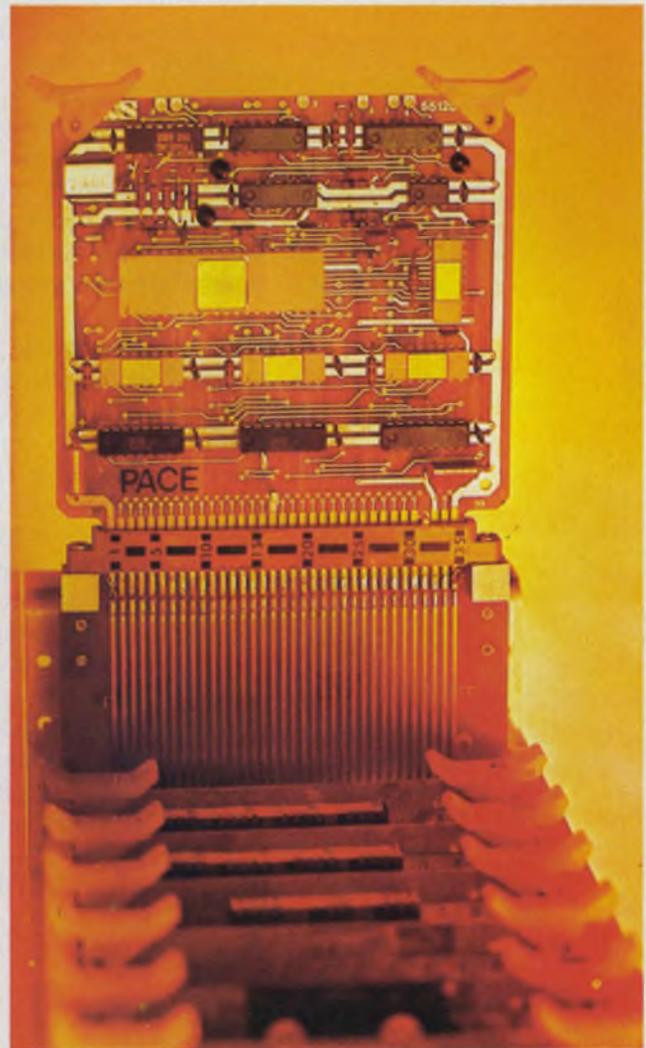But a CPU chip itself is about as useful as a pet rock. For a complete, operating μ C (microcomputer), you must add peripheral and interface circuits, as well as memory. A simple μ C-



A data-processing controller resides on a PC board measuring only 4-1/2 x 4-1/2 in. The board combines National Semiconductor's Pace (the first single-chip 16-bit μ P) with sense amplifiers, hex buffers, a crystal oscillator and clock drivers.

Edward A. Torrero
Associate Editor


based controller could require at least 25 extra chips surrounding the processor. The cost of the additional components exceeds the price of the CPU by a wide margin. Moreover, a package of system components having an attractively priced CPU may have an over-all cost that's higher than one that doesn't.

Whatever the system hardware's cost, it is likely to be dwarfed by the soaring cost of μC software, which can range from hundreds of dollars to thousands for the finished system. For a \$30 μP , such software has been known to cost more than \$65,000.

Of course, your software development is a "one shot" expense that can be amortized over the life of the product—assuming it is a successful one. But should you decide to switch micros, you won't be able to transfer a design using the first μP 's software to the second. The experience gain-



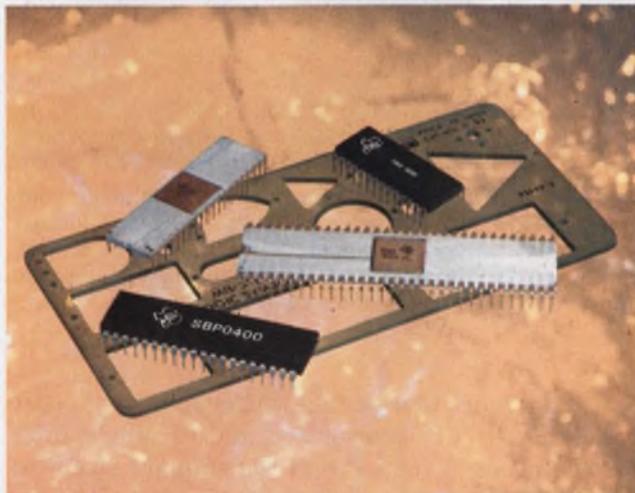The most advanced development system for micros, Intel's MDS (microcomputer development system), features in-circuit emulation. The capability permits early fault and error isolation in system prototypes. MDS includes floppy-disc storage and a CRT terminal, and allows the setting of breakpoints symbolically.



A single-chip 16-bit μP is the latest offering from Texas Instruments' growing line of microprocessor products. The new TMS 9900 μP is upward compatible in software with other members of the 990 processor family, which includes a minicomputer.

ed from one μP can't be applied to another. Different micros come with different software capabilities, hardware requirements and design aids. That first costly system may have to be scrapped completely.

μP products and technologies: a mixed bag

Microprocessors and related circuits can be obtained in a variety of technologies and product forms. Older micros employ p-channel MOS (PMOS) and offer 4, 8 and 16-bit word lengths. The bulk of present MOS micros uses speed-enhancing n-channel MOS (NMOS) for 8-bit units and specifies a basic cycle time of about 2 μs . More recently, NMOS has been applied to 16-bit μP s and power-saving complementary-MOS (CMOS) has been used to build 8 and 12-bit μP s.

Product forms encompass just about anything you'd care to ask for, from a sack of parts to a μP -based minicomputer. At the simplest level, you can purchase a set of chips that include the CPU, special interface ICs and, generally, special memories. If you don't want to be bothered testing, mounting and interconnecting the chips, you can purchase a logic board instead. The μP -based board comes fully wired and ready to run, although at the very least you generally have to provide system-test equipment and a power supply.

At the high end of the price ladder are complete μP -based development systems, such as Intel's MDS (microcomputer development system), Motorola's Exorciser and National Semiconductor's IMP-16. These units constitute sophisticated hardware/software design aids that offer the conveniences and peripherals associated with minicomputers—at prices to match. A basic system starts at about \$5000 and rapidly escalates to about \$10,000 if you decide to use such system peripherals as a floppy-disc operating system, video terminal and PROM programmer.

Currently the most popular product form for microprocessors is the do-it-yourself kit. Priced at \$500 or less, the μP kit offers designers—especially the growing number of newcomers—an inexpensive and fairly painless way to get a μP system up and running.

However, like the microprocessors they are built around, kits may not live up to all the claims made for them. Ideally a kit should be easy to use and allow some system prototyping. But whether the kit actually does these things often reveals what was left out to keep prices low, even better than it reflects what was put in. The old adage, "you get what you pay for," might well be applied here.

One kit may be priced significantly lower than another, though both use the same microprocessor

and offer about the same features. Sometimes the difference in price is due to the use of less expensive ICs in the lower-priced model. These ICs exhibit temperature and voltage limitations that aren't necessarily bad for home experiments, but which could prove disastrous in an industrial environment.

All kits require hand-assembly for program entry. Instructions must be entered one bit at a time, though some units feature hex or octal-code entry, thereby shortening the number of times you have to move a switch or press a button. Manual assembly may not be a problem if your program isn't longer than a few hundred words. But it rapidly becomes unwieldy for a program any longer than that—assuming the kit has sufficient memory to store it.

What you can prototype with a kit depends largely on how much memory comes with it. Capacity ranges from 256 bytes up to 8-k, though most units don't have more than about 1-k of storage. The capacity is sufficient for simple systems.

But storage capacity can easily become a problem for applications that need 1000 or more words of code—like a computer-peripheral controller. Moreover, long programs can't be debugged easily. A hand-assembled program that has errors has to be redone completely, unless spaces (No Op instructions) have been left in the program for corrections.

The most serious problem arises when the set of components doesn't come with adequate monitor and debug programs. A monitor program provides the means to drive a control panel or operate the system through a teletypewriter. A debug program lets you single-step the system one instruction at a time, examine memory, and insert breakpoints. Typically, the monitor and debug programs are combined in ROM and offered as firmware.

Without these essential programs, that μP system does little more than talk to itself. Of course, monitor/debug software can be developed. But presumably you bought a kit because you wanted to learn about microprocessors the easy way.


Chip sets reduce package count

Newer μP -chip sets have overcome one of the most serious shortcomings of early μP s—the need for a host of supporting chips to interface with peripheral devices, data-communication lines and even the μP 's own memory. The first 8-bit μP and the only one for about two years—Intel's 8008—required 20 or so additional standard-TTL circuits to make it work.

Constrained primarily by the limitations of an 18-pin package, the 8008 needed the following: registers to address memory, either ROM or



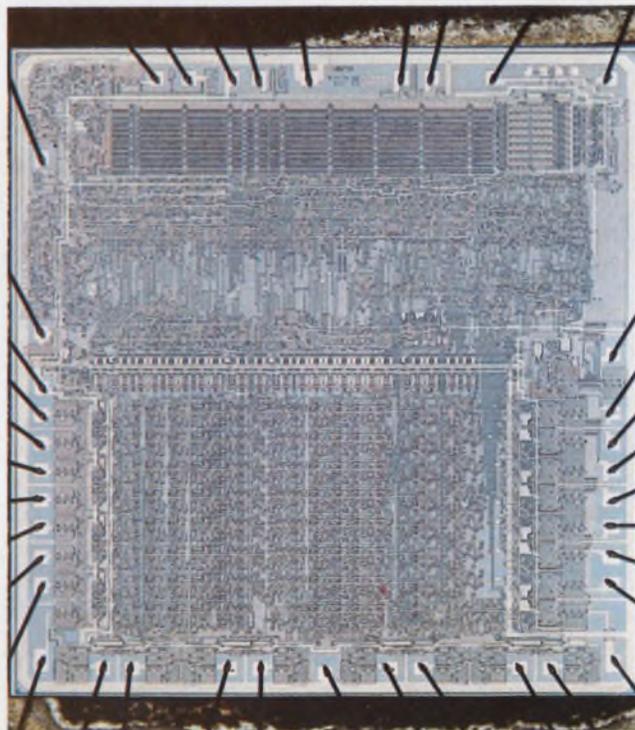Features often associated with minis combine with the ease-of-use of other programmable controllers in the Eptak industrial-control system from Eagle Signal. The system uses the 8080 μP .



The 6800 μP forms the nucleus of an 8-bit microcomputer chip set that includes a peripheral-interface adapter and an asynchronous-communications interface circuit. Introduced by Motorola, the chips have been alternate-sourced by American Microsystems and Hitachi.

RAM; decoders to interface with memories; other ICs to handle μP information and to synchronize the operation of the μP and the support circuits; clock circuits; and a number of interface ICs, depending on the application. For example, in a multichannel data-communications application, each channel requires an asynchronous receiver/transmitter and associated interface ICs.

Now improved μ Ps like Intel's 8080, Motorola's 6800 and Fairchild's F8 have come along. Special LSI peripheral and memory circuits match and enhance the μ Ps they support. Together with improvements in the CPU chips, the resulting chip sets constitute minimal-chip configurations that can drastically reduce package count while improving performance.

But even new chip sets may not be all they seem. Some manufacturers stress the fact that their μ P systems can run from TTL levels of 5 V and ground. However, more than a single supply may be needed if you decide to use such memories as some of the new 4-k dynamic RAMs, or some PROMs. Also, you'll need another supply if you want to hook up a device that spits out ASCII characters, or more simply, if you try to provide the μ P's demanding clock requirements with conventional circuitry.

Expansion can present other problems. Since many chip sets employ nonstandard memories, you're limited in the choice of storage elements, even though the manufacturer claims that any memory works well with the μ P—including core, though that admission may have to be pulled out of a semiconductor manufacturer. In some cases, you can use the memory of your choice, but only after you've added special memory-interface ICs to your "minimal" chip system. And if the memory is static, you might use a different interface chip than the one for a refresh-hungry dynamic memory.

Further, several chip sets employ mask-programmable ROMs for program storage. These can be found in such MOS μ Ps as those that employ bit-slice configurations, as well as those that incorporate the control memory within the CPU circuits. In such cases, your system-development time will have to include the manufacturer's turn-around time for ROM mask programming.

An obvious time-saving solution would be to employ PROMs, especially the erasable kind, as a growing number of designers are now doing. But again, these components can entail additional circuitry and power supplies.

For situations that do entail additional circuits, manufacturers provide an ever expanding line of package-saving MSI (medium-scale-integration) circuits. Unlike key LSI peripherals, though, the MSI units aren't always an economical buy. You do save on, say, a complex data-communications chip or a direct-memory-access controller that replaces 10 or more standard-TTL circuits, but you won't always save with an MSI component that replaces just a few standard packages. The best bet is carefully to select the components you want in a manufacturer's μ P family and consider making up the rest with standard TTL.


Shop around, too, for the best price tag on the

same component. It wasn't always possible to do so when μ Ps were virtually sole-source products and typically were offered only as part of complete chip-package orders and only when you purchased the associated memory from the same IC manufacturer. That practice has since died down, mainly because of falling memory prices. But several designers report they still encounter it. If you find this problem, go to an alternate source.

Avoid specification pitfalls

Though microprocessors are far too complex to be characterized by a simple data sheet, specifications for μ Ps do abound. Ideally one should be able to use the published data to make a selection. However, spec sheets don't always reveal what a μ P will do, or how it will react in your application.

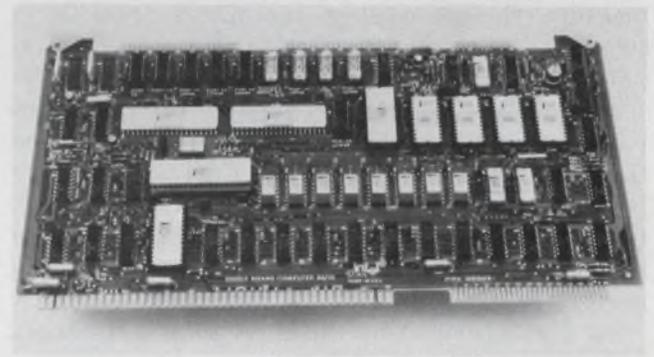A widely omitted spec is noise immunity, even



A single-board microcomputer based on the 8080—Intel's SBC 80/10—features 48 lines of programmable I/O. The board includes 4-k bytes of ROM and 1-k byte of EPROM.

though manufacturers promote their products as ideal for use in industrial equipment. For some μ Ps, the omission may be intentional. A comparison between input levels for peripheral circuits and the address-output levels of the μ P may show little or no protection against unwanted transients.

However high noise immunity specs can be expected from newer microprocessors. For example, CMOS μ Ps from Harris Semiconductor, Intersil and RCA excel in noise immunity—a forte of the low-power technology.

If you don't have the noise immunity needed, you'll quickly discover the fact when you move from a clean, noise-free bench to a production environment. Of course, the problem can be overcome with simple level shifters and pull-up resistors. These components are cheap, but they do take up valuable board space and drive up power dissipation.

Another spec that's hard to find is the length of time the μ P will hold data from a memory

after Write signals have dropped. Some memories, especially the most inexpensive, can't work with a μP unless they hold data for, say, 100 ns. Too low a hold time results in data loss. Without the hold-time spec, memories added to the system may have to be selected by trial and error.

Speed specs confuse

Of the specs that are generally published, few are more numerous than the ones offered as a measure of a microprocessor's operating speed. A typical data sheet specifies a basic cycle (or microcycle) time, state time, clock rate, execution time, interrupt time, and time to add two decimal numbers, among other "times." Paradoxically, none of these nor any combination gives either a complete measure of a μP 's computing speed, or fully tells how much work the μP can do in a unit of time.

Consider cycle time—possibly the most useless measure, though most of the others could lay a strong claim to that distinction. Many microcomputer operations require several cycles to be performed. This is especially true of the more powerful instructions, which take far more time than the basic cycle indicates. Further, it's very possible for one μP with a seemingly high clock rate to perform a fundamental operation—like register-to-register add—more slowly than it is performed in a unit with a slower clock.

In a comparison of different μP s, differences in architecture and chip design tend to minimize the importance of specs like clock rate and cycle time. Moreover, all of these time specs don't measure such critical times as the over-all time needed to perform important routines. Not accounted for are additional delays, particularly those needed to obtain information from memory.

For example, one spec sheet says that a Call instruction for a subroutine takes about 11 states for execution. Since each state takes about $1/2 \mu\text{s}$, the Call instruction should be completed in less than $6 \mu\text{s}$. However, memory must be referred to five times before the instruction is completed, and each reference typically adds an additional state time since few memories are sufficiently fast. So a Call can easily take significantly longer than expected.

Often the number of instructions is spotlighted as an indication of the μP 's prowess. There are several reasons why this emphasis can lead to fallacious comparisons. A number simply doesn't reveal what instructions are available for data movement and manipulation, for decision and control, or for I/O operations.

Nor does a number tell which instructions are single or multibyte in length. Double-byte instructions take twice the memory of single-byte



One of the first development systems to use the 8080, Process Computer Systems' Micropac 80/A simplifies the design of controllers for industrial equipment.

instructions. And missing instructions can always be made up with additional hardware or with software routines, although the latter sacrifices speed. Further, a μP that features a number of addressing modes allows tighter and more efficient coding than a μP with more limited addressing capabilities.

Sometimes the number of available μP instructions depends on which page of the applications manual you're reading—because the manufacturer has multiplied instructions. The multiplying factor may be the number of addressing modes or the number of registers (in, say, a load-to-register operation), or the number of conditions (for example, those on which a branch may occur). Other multiplying factors may be used, so that one or more parts of the original instruction set might be multiplied several times.

Improved instruction sets do come with longer-word-length μP s and with advanced versions of older units. For example, 16-bit models can handle multiplication or division with a single instruction. In 8-bit μP s, these functions call for either subroutines or special circuitry.

Further, advanced μP s offer the original instruction set of a predecessor, and more powerful instructions, too. However this "software compatibility" doesn't allow routine upgrading of systems by chip replacement. And a pin-compatible higher-speed version of a μP doesn't produce a faster, more efficient system unless there are some design changes first. In general, expect to redesign if you want to employ the new hardware/software tradeoffs efficiently.

Programming ease: a key selection factor

A microprocessor's instruction set and architecture determine one of the most frequently stressed selection factors—programming ease.

Programming can be very time consuming. Various estimates place the number of lines of "shippable" code that a programmer can write in a day at less than 20 because of the time needed to write the program, run it, and then to debug,

check and finally document the code.

However, microprocessor-chip designers are constrained by limitations of technology and packaging; their chips must fit into a package no larger than a 40 or 42-pin DIP. As a result, each μ P reflects a very different series of compromises and tradeoffs. Though each manufacturer says his μ P is easy to program, the programmer is actually both helped and hindered by each μ P. The degree of each depends on the specific application involved.

For example, one μ P's instruction set may seem to be quite complete. It has a fine complement of test and branch instructions, all the logic instructions you need and all the memory-reference instructions you could possibly require.

But the μ P doesn't allow program-relative addressing, though most other addressing modes are available. If you are writing a large program—as more and more microcomputer designers are—you can't easily relocate a ROM-based program from one memory-address space to another. So design changes may require a redoing of the program.


Another μ P may allow the memory-addressing mode as well as indirect and indexed addressing, but at the expense of no direct addressing—the most common type. In this case, you'll be able to move programs around, but you won't be able to address all of memory without detouring through the index register.

Benchmarks get mixed reviews

One solution to the problem of comparing chaotically different μ Ps is the use of benchmarks. In theory, these short test routines show how well different μ Ps perform critical tasks, like moving data from one part of memory to another. These software tests, adherents argue, provide a quick and easy short-cut to the one obvious but unwieldy solution: writing complete, optimized programs for different μ Ps and comparing results.

In practice, though, different benchmarks from different μ P manufacturers show that each has a better product than anyone else. And a benchmark test that puts one μ P on top of the heap can be modified ever so slightly so that the pace-setting μ P loses out to others. For example, one manufacturer provides a benchmark test that shows its unit is the best mover of data in a μ P's memory. But if that pace-setting micro must also deal with an interrupt during data-move operations, it falls far behind the pack.

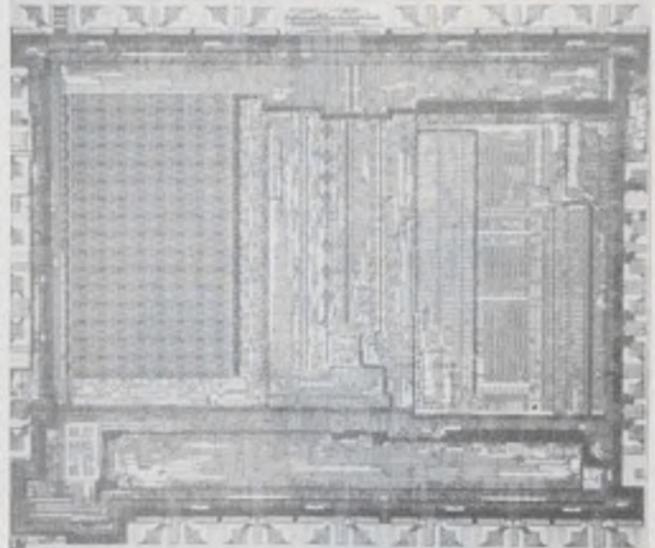Benchmarks designed for one particular architecture can be thoroughly ineffective for another. If you're doing a job that requires 16 bits of precision for the job, then a 16-bit μ P will out-dis-



The F8 two-chip set consists of a CPU and a program-storage unit. The CPU (above) contains a 64-byte scratchpad, eliminating the need for RAM in many applications. When needed, though, external RAM can be added to an F8 system. Introduced by Fairchild, the F8 is also available from Mostek.

tance 8-bit versions. When many different operations need to be performed a multiregister μ P will outperform one with fewer available registers. For any model, no software test reveals the hardware side of the story—the required support circuits and necessary power supplies, for example.

And for a number of applications, benchmark tests may be just plain meaningless. In a host of μ P applications, the micro may spend much of its time waiting for some external event, like the closing of a switch or the pressing of a button, that can take milliseconds just for the contact bounce to die down. A test that merely compares sub-millisecond operating speeds has little relevance to this problem.

Still, benchmarking provides meaningful results when used to compare two slightly different versions of the same system. The difference might be the use of a somewhat altered μ P, or a modified I/O scheme. In other cases, design the benchmark to the specific application or task at hand. If you're presented with comparative benchmark tests, be sure they are specified completely. ■■

Need more information?

For additional information on specific products, circle the appropriate information retrieval numbers. For data sheets on many microprocessor and related products, consult ELECTRONIC DESIGN's GOLD BOOK.

AEG-Telefunken, 6 Frankfurt 70, AEG-Hochhaus, Germany.
Circle No. 501

(continued on page 64)



Nurl-Loc® ...4-way problem solver


Warp . . . only the patented Nurl-Loc® design, with 500% more gripping surface, eliminates panel warp by spreading stress.

Spin . . . gear-locking action guaranteed not to rotate during wrapping.

Tear . . . replace terminals up to 3 times without tearing or crazing panel.

Snap . . . no brittle pins to break. Accurate true position without pin straightening.

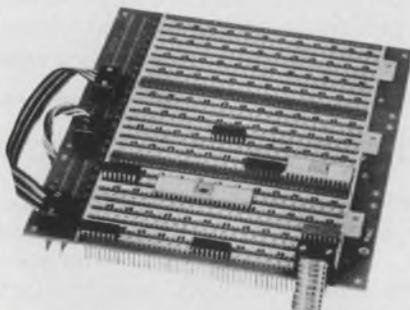Interested? Call Allan Klepper (401) 769-3800 or contact Electronic Molding Corp., 96 Mill Street, Woonsocket, Rhode Island 02895.



CIRCLE NUMBER 30

(continued from page 63)

- Adaptive Systems, P.O. Box 1481, Pompano Beach, FL 33061. (305) 942-4000. **Circle No. 502**
- Advanced Memory Systems, 1275 Hammerwood, Sunnyvale, CA 94086. (408) 734-4330. **Circle No. 503**
- Advanced Micro Devices, 901 Thompson Pl., Sunnyvale, CA 94086. (408) 732-2400. **Circle No. 504**
- American Microsystems, 3800 Homestead Rd., Santa Clara, CA 95051. (408) 246-0330. **Circle No. 505**
- Applied Computing Technology, 17961 Sky Park Circle, Irvine, CA 92707. (714) 557-9972. **Circle No. 506**
- Burroughs, P.O. Box 517, Paoli, PA 19301. (215) 648-2000. **Circle No. 507**
- Computer Automation, 18651 Von Karman Ave., Irvine, CA 92664. (714) 833-8830. **Circle No. 508**
- Comstar Microcomputers, Warner & Swasey, 30300 Solon Industrial Pkwy., Solon, OH 44139. (216) 368-6200. **Circle No. 509**
- Data Works, 9748 Cozycroft Ave., Chatsworth, CA 91311. (213) 998-8985. **Circle No. 510**
- Digital Equipment Corp., 146 Main St., Maynard, MA 01754. (617) 897-5111. **Circle No. 511**
- Eagle Signal Industrial Controls Div., Gulf and Western, 736 Federal St., Davenport, IA 52803. (319) 326-8101. **Circle No. 512**
- Electronic Arrays, 550 E. Middlefield Rd., Mountain View, CA 94043. (415) 964-4321. **Circle No. 513**
- Essex International, 564 Alpha Dr., Pittsburgh, PA 15238. (412) 782-0200. **Circle No. 514**
- Fairchild Semiconductor, 1725 Technology Dr., San Jose, CA 95110. (408) 998-0123. **Circle No. 515**
- Fujitsu, 2-chome 6-1, Chiyoda-ku Tokyo, Japan. **Circle No. 516**
- General Automation, 1055 S. East St., Anaheim, CA 92803. (714) 778-4800. **Circle No. 517**
- General Instrument, 600 W. John St., Hicksville, NY 11802. (516) 733-3000. **Circle No. 518**
- Harris Semiconductor, P.O. Box 883, Melbourne, FL 32901. (305) 727-5407. **Circle No. 519**
- Hitachi, 23-15 6-Chome, Minamiohi, Shinagawa-ku, Japan. **Circle No. 546**
- Intel, 3065 Bowers Ave., Santa Clara, CA 95051. (408) 246-7501. **Circle No. 520**
- Intersil, 10900 N. Tantau Ave., Cupertino, CA 95014. (408) 257-5450. **Circle No. 521**
- Martin Research, 1825 S. Halsted St., Chicago, IL 60608. (312) 829-6932. **Circle No. 522**
- Microcomputer Associates, P.O. Box 304, Cupertino, CA 95014. (408) 226-3191. **Circle No. 523**
- MITS, 6328 Linn Ave., Albuquerque, NM 87108. (505) 265-7553. **Circle No. 524**
- Monroe Calculator Co., 550 Central Ave., Orange, NJ 07051. (201) 673-6600. **Circle No. 525**
- MOS Technology, 950 Rittenhouse Rd., Norristown, PA 19401. (215) 666-7950. **Circle No. 526**
- Mostek, 1215 W. Crosby Rd., Carrollton, TX 75006. (214) 242-0444. **Circle No. 527**
- Motorola Semiconductor, 5005 E. McDowell Rd., Phoenix, AZ 85036. (602) 244-3465. **Circle No. 528**
- Multisonics, 3300 Crow Canyon Rd., P.O. Box 350, San Ramon, CA 94583. (415) 837-8111. **Circle No. 529**
- NEC Microcomputers, 5 Militia Dr., Lexington, MA 02173. (617) 862-6410. **Circle No. 530**
- National Semiconductor, 2900 Semiconductor Dr., Santa Clara, CA 95051. (408) 732-5000. **Circle No. 531**
- Panafacom, P.O. Box 4637, Mountain View, CA 94040. **Circle No. 532**
- Plessey Microsystems, 1674 McGaw Ave., Santa Ana, CA 92705. (714) 540-9979. **Circle No. 533**
- Process Computers Systems, 5467 Hill 23 Dr., Flint, MI 48507. (313) 767-8920. **Circle No. 534**
- Pro-Log, 852 Airport Rd., Monterey, CA 93940. (408) 372-4593. **Circle No. 535**
- RCA, Route 202, Somerville, NJ 08876. (201) 722-3200. **Circle No. 536**
- Rockwell International, Microelectronic Device Div., P.O. Box 3669, Anaheim, CA 92803. (714) 632-2321. **Circle No. 537**
- SEMI, Div. of EM&M, 3883 N. 28 Ave., Phoenix, AZ 85017. (602) 263-0202. **Circle No. 538**
- Signetics, 811 E. Arques Ave., Sunnyvale, CA 94086. (408) 739-7700. **Circle No. 539**
- Synertek, 3050 Coronado Dr., Santa Clara, CA 95051. (408) 241-4300. **Circle No. 540**
- Teledyne Systems, 19601 N. Nordhoff St., Northridge, CA 91324. (213) 886-2211. **Circle No. 541**
- Texas Instruments, P.O. Box 1443, Houston, TX 77001. (713) 494-5115. **Circle No. 542**
- Toshiba Transistor Works, 1-Komukai, Toshiba-Cho, Kawasaki-Chi, Japan. **Circle No. 543**
- Western Digital, 19242 Red Hill Ave., Newport Beach, CA 92663. (714) 557-3550. **Circle No. 544**
- Zilog, 170 State St., Los Altos, CA 94022. (415) 941-5055. **Circle No. 545**

Out of almost 30,000 flexible circuits...

This circuit is critical in the operation of a sophisticated plasma display unit. Somebody else said they could make it cheaper.

They did. And the customer's reject rate shot up over 1000 times.

Now, BMC is producing it again with the same reliability as before. Sure, it's costing our customer a little more at the beginning. But, he saves a lot in the end.

Because after almost 20 years of experience in flexible circuitry we know what it takes to build in reliability. Like almost constant inspection.

We inspect the raw materials. The photo sensitized laminate. The imaged laminate. The plated circuit. The coverlay. The finished circuit.

Every step of the way skilled BMC craftsmen have written specifications that must be met. Extra care and attention that may cost a little more.

But, we can show you at least one customer who thinks it's worth every penny. Wouldn't you pay a little more for that kind of reliability?

For more information, contact Ed Dugan, Circuits Division, (612) 228-6371.

245 EAST 6TH STREET
ST. PAUL, MN 55101
612 - 228-6371

BUCKBEE-MEARS COMPANY
bmc

CIRCLE NUMBER 31

only 4 were rejects.




Still the best and most versatile low-cost multiturn pot available!



THE SPECTROL MODEL 534

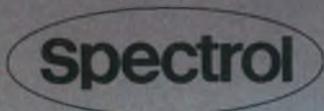Standard, 10-turn, wirewound Model 534 — 100-piece price, \$4.75. Also offered as standard, 5 and 3-turn models. Send for a data sheet, or call for a quote.




SPECTROL ELECTRONICS GROUP

UNITED STATES Spectrol Electronics Corporation 17070 E. Gale Avenue, City of Industry, Calif. 91745, U.S.A. • (213) 964-6565 • TWX (910) 584-1314

UNITED KINGDOM Spectrol Reliance Ltd. Drakes Way, Swindon, Wiltshire, England • Swindon 21351 • TELEX: 44692

ITALY SP Elettronica spa Via Carlo Pisacane 7, 20016 Pero (Milan) Italy • 35 30 241 • TELEX: 36091

MOS KIM-1 microcomputer system

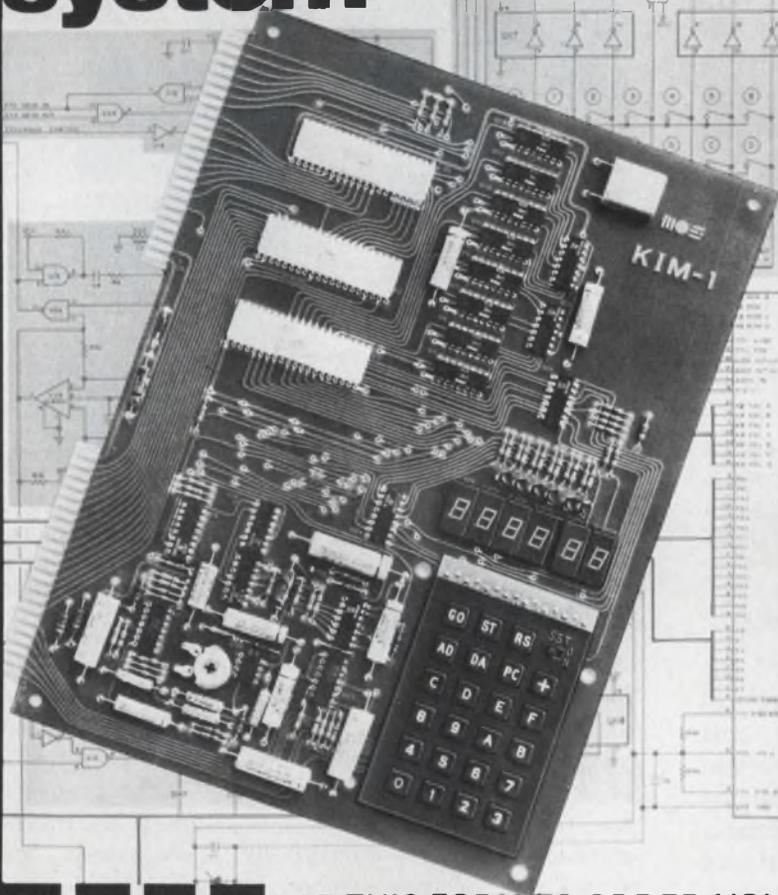

- A COMPLETE MICROCOMPUTER
- ONLY \$245
- NOT A KIT!
 - FULLY ASSEMBLED
 - FULLY TESTED
 - FULLY WARRANTED
- OPERATES WITH
 - KEYBOARD & DISPLAY
 - AUDIO CASSETTE
 - TTY
- KIM-1 INCLUDES
 - HARDWARE
 - KIM-1 MODULE WITH
 - 6502 μ P ARRAY
 - 6530 ARRAY (2)
 - 1 K BYTE RAM
 - 15 I/O PINS
 - SOFTWARE
 - MONITOR PROGRAMS (STORED IN 2048 ROM BYTES)
 - FULL DOCUMENTATION
 - KIM-1 USER MANUAL
 - SYSTEM SCHEMATIC
 - 6500 HARDWARE MANUAL
 - 6500 PROGRAMMING MANUAL
 - 6500 PROGRAMMER'S REFERENCE CARD

USE THIS FORM TO ORDER YOUR KIM-1 TODAY!

ED3

Send to:



MOS TECHNOLOGY, INC.
KIM-1, 950 Rittenhouse Rd.
Norristown, PA 19401

Please ship me _____ KIM-1 Systems at a cost of \$245.00 per system plus \$4.50 for shipping, handling and insurance (U.S. and Canada only) PA residents add 6% sales tax.

(International sales subject to U.S. Commodity Control Regulations.
Add \$20.00 per system for shipping and handling of international orders.)

My check or money order is enclosed for \$ _____

Name _____

Address _____

City _____ State _____ Zip _____

CIRCLE NUMBER 33

Displays don't trouble 8-bit μ P's. The μ P's easily provide information for displays as diverse as simple digital types and data-demanding video terminals.

The data-handling capabilities of 8-bit microprocessors are both versatile and flexible enough to interface with displays that run the gamut from simple seven-segment digital types to complex CRT terminals.

A seven-segment digital display requires only infrequent updating, and when it is updated, very little information actually transfers to the display. A video-display terminal must be updated—or refreshed—very frequently (unless a storage tube is used), and that entails a large amount of data.

Data can be transferred from buffer memory to a display by various methods. The simplest is a software-controlled transfer, which uses minimal peripheral-interface hardware. However, the software approach may turn out to be the slowest one when performed on the usual macroprogram level. Higher data rates can be obtained through microprogramming.


A completely hardwired direct-memory-access (DMA) approach achieves the highest throughputs. A microprocessor like the IMP-8 (Fig. 1) allows these and other data-transfer methods.

Treat the display as a standard peripheral device

When you use the 8-bit microprocessor,^{1,2} the display should be treated as a standard peripheral unit that attaches to the μ P's bus in the same way that memory does. The IMP-8 instruction set contains no instructions specifically intended for peripheral operations. All peripheral transactions with the CPU are performed by standard memory-reference instructions, like Load Accumulator from memory and Store Accumulator in memory.

Two basic software-control methods—loop and in-line—may be employed on the macroprogram level.

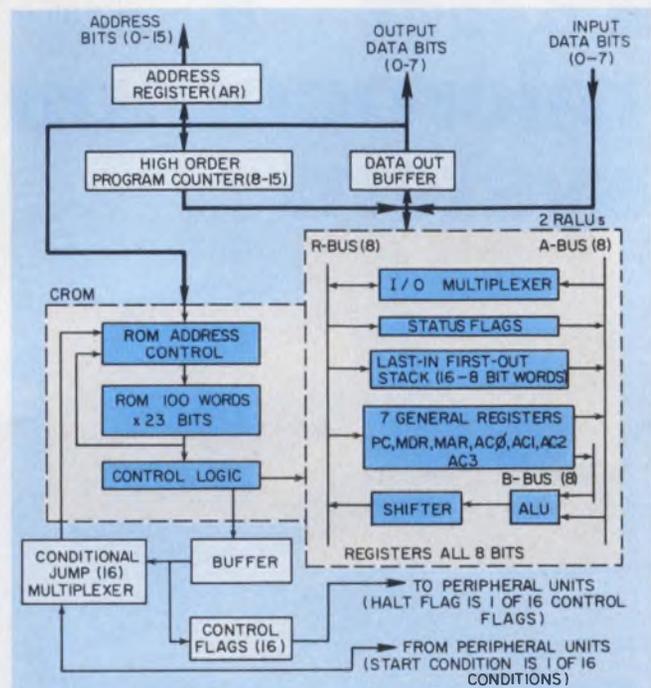The loop method executes a sequence of instructions over and over again (Fig. 2). This method



1. The IMP-8, an 8-bit microprogrammable μ P, employs two 4-bit RALUs (register and arithmetic logic units) and one CROM (control read-only memory). The μ P's instruction set can be changed by modifying the existing CROM or by adding extra CROMs in parallel.

has the advantage that only a few words of code are needed to transfer a large block of data from memory to the peripheral. However, to keep track of the buffer word being processed, the pointers for the last-in, first-out stack must be incremented and tested continually. As a result, the actual rate of transmission is relatively slow.

In Fig. 2, BUF1 represents the starting address of the first buffer. AC3, the third accumulator, functions as the index register and increments once for each data word transferred. When AC3 becomes equal to zero, the loop will be terminated and the transfer of a second buffer can begin. For each pass through the loop, four machine instructions must be executed, requiring 44 machine cycles at 1.4 μ s (minimum) per cycle. Hence, one 8-bit word can be transferred every 61.6 μ s.

When only a few data words need be trans-

Roger Thompson, Microprocessor Engineer, National Semiconductor, 2900 Semiconductor Dr., Santa Clara, CA 95051.

ferred to a peripheral, the data rate can be increased about 50 percent by using the in-line method (Fig. 3). This method eliminates the control loop and uses instead a separate Load and Store-instruction pair.


In Fig. 3, BUF1 is again the starting address and AC3 serves as the base index register. The short program increments the displacement value for each Load instruction. The method requires only the execution of two machine instructions for each data transfer, and these two instructions

tical to the structures of other members of the IMP family.³ Each microinstruction specifies the exact function of the ALU and any external logic during that microcycle.

For example,

ADD, AC3,, AC2 CIN

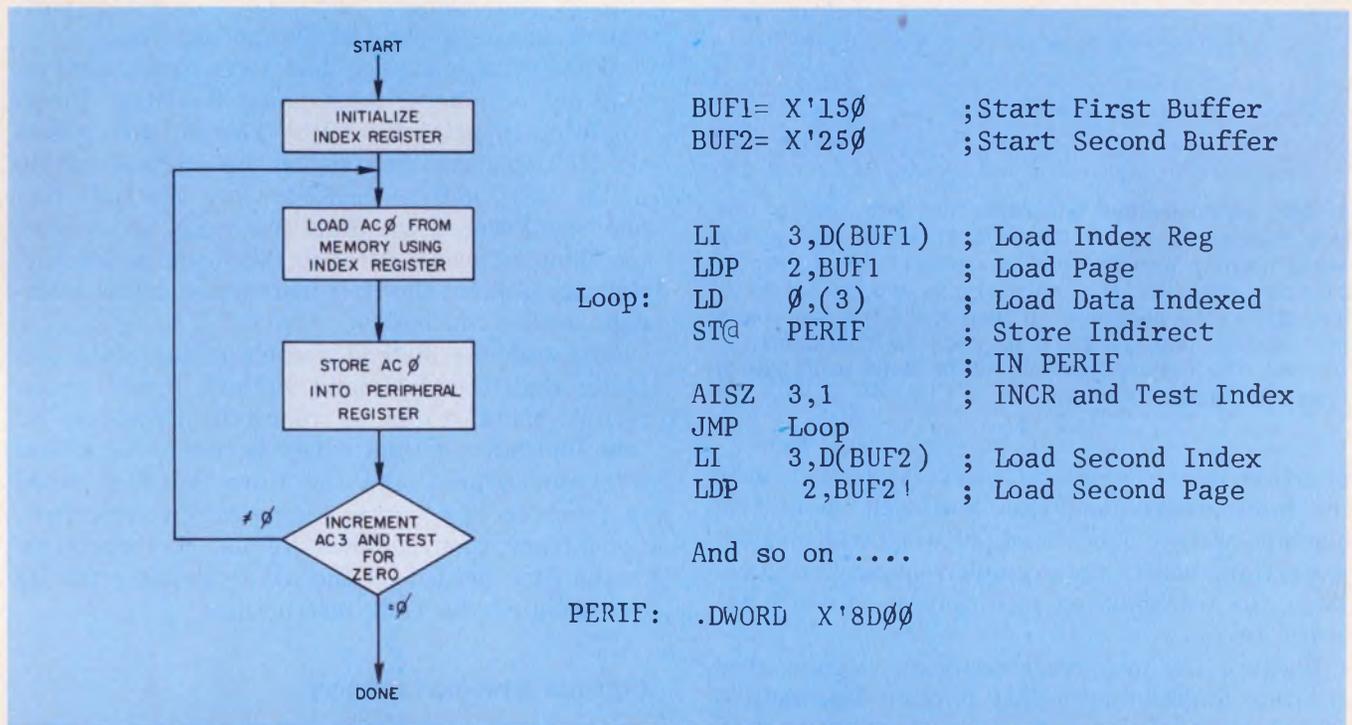specifies an Add operation. The A-bus operand is AC3, and the B-bus operand is undefined—and consequently is interpreted as all zeros. CIN indicates that the result will be incremented. In this example AC2 indicates that the final result



2. The loop method uses only a few words of machine code to transfer an 8-bit word from memory to a peripheral display. However, each transfer takes a lengthy

62 μ s since stack pointers in the RALUs must be continually tested and incremented. A speed-enhancing microprogrammed approach uses the same flow chart.

require only 26 machine cycles at 1.4 μ s per cycle. Hence one 8-bit word can be transferred every 36 μ s. However, the in-line method requires more memory to store the control program than does the loop method.

Microprogramming speeds data transfers

Other techniques for data transfer deal directly with the microprogram that controls the execution of each machine instruction. With the IMP-8 μ P, you can add or delete portions of the microprogram to achieve an altered instruction set.

But microprogramming lengthens development time and costs, and it can entail additional CROMs (control and read-only memories). In general, this approach becomes economical only for high-volume applications.

IMP-8 microprogramming structures are iden-

(after incrementing) will be stored in that accumulator.

Several microinstructions are sequenced together to form a general subroutine. Each subroutine is executed as a response to a fetched and decoded macroinstruction from memory.

A microprogram-loop method like that discussed on the macroprogram level offers several advantages. First, the four-machine-instruction loop is replaced by a single machine instruction. And since all data are transferred within the execution of a single machine instruction, the over-all data rate can be reduced dramatically.

The example in Fig. 4 requires only 9.2 machine cycles per pass through the loop. Since each machine cycle requires only 1.4 μ s, each word transmitted takes just 12.9 μ s. That's about 1/5 the time needed by the macroprogrammed loop.

The in-line method, when applied on the micro-

```
BUF1 = X'150
```

```
LI    3,D(BUF1)  
LDP   2,BUF1
```

```
START:
```

```
LD    0,(3) ;LOAD FIRST WORD  
ST@   PERIF ;SEND TO PERIPHERAL  
LD    0,1(3)  
ST@   PERIF ;SEND SECOND WORD  
LD    0,2(3)  
ST@   PERIF ;SEND THIRD WORD
```

```
AND SO ON .....
```

```
PERIF:.DWORD X'8D00
```

3. The in-line method increases the data rate of the loop method by about 50 percent when only a few words need be transferred. The routine reads a memory location's data into accumulator zero and then outputs that data to the peripheral. It then reads the next memory location and transfers its data to the same peripheral. The routine continues to do so for each pair of Load and Store instructions.

program level, doesn't increase speed much over the microprogrammed-loop approach. Only two machine cycles can be saved per word transmitted. Everything else in the example remains the same. Thus, the transmission rate reduces to one word every 10 μ s.

Because the total microprogram storage area is rather limited for the IMP-8, the in-line method should be employed only for very limited data transfers, even though a comparison between this method and the macroprogram in-line version shows a 3-to-1 speed advantage. It requires only one machine instruction, as opposed to two for each buffer-word transferred.

Hardware-controlled data transfers

In the clock-hold DMA method—a hardware implementation—the requesting peripheral must generate a clock-hold request whenever it requires data (Fig. 5). The request temporarily stops the CPU clocks for a maximum of 10 μ s. During this period, the CPU address buffers are disabled, allowing the requesting peripheral to take control of the address bus.

Data rates are limited to the cycle rate of the memory. For example, with a memory having 1- μ s access, up to 10 words of data could be transferred during a 10- μ s clock-hold period.

Since no software control is needed, the peripheral's request can be serviced in less than 1 machine cycle, or 1.4 μ s. However only a limited

number of data words per request can be transferred; the clocks can be held only for a short period of time each machine cycle.

An interrupt-controlled DMA doesn't rely on a stopping of clocks. Instead, the peripheral requiring data requests a CPU interrupt.

The interrupt must be serviced under program control. First the DMA interrupt-service routine executes a Halt instruction, which sets the CPU Halt flag. This flag and its complement then are used as the appropriate address-buffer enable/disable signals. As was the case with the clock-hold method, data can be transferred at the cycle rate of the memory once the requesting peripheral obtains control of the address bus.

When data exchange has terminated, the requesting peripheral must raise the Start jump-condition input to the CPU. This in turn resets the Halt flag that established the original setting of the CPU address buffers. Once the Halt flag has been lowered, the Start input can be lowered, too. This returns control to the machine instruction that follows the Halt instruction in the interrupt-service routine.

Although the method doesn't handle data any faster than the clock-hold method, it can transfer as many words as required. However, an interrupt-latency time exists between the actual interrupt request and the time the first word is transferred. For the application described, the latency time is about 75 μ s, corresponding to the time needed by the μ P to prepare for its execution of the Halt instruction.

Organize a two-port memory

In all of the examples described, the buffer memory was presumed to be part of the main-system memory. But since data are all that are being transferred, there is no reason for the buffer memory to be organized the same way as the instruction memory. In fact, if the buffer is organized as a two-port memory, high data rates can be sustained for any length of time without the need for a μ P interrupt. This, in turn, would eliminate the interrupt latency time, and allow transfer of data within one machine cycle or 1.4 μ s on the standard IMP-8.

One port performs read-only operations, and is controlled directly by the peripheral. The second port, a write-only, is connected to the main μ P I/O bus.

The μ P generates data and stores it in the buffer memory, from which the peripheral takes data. However, the buffer memory does not acknowledge the transfer to the IMP-8 μ P. After each write operation, the CPU must check the buffer to determine if it is in a DMA mode. Only when the buffer completes a data transfer can the μ P write in new data.

CONTINENTAL CONNECTOR... for economy in connectors



SEND FOR FREE E600 TECHNICAL BOOKLET!

E-conn printed circuit board connectors provide reliable performance at lower cost - flame retardant glass fiber filled Diallyl Phthalate molding material and phosphor bronze contacts with gold plate over nickel. This group also features patented "Bellowform" contacts with choice of solder lugs, dip solder terminals or .025" and .045" square solderless-wrap terminations. Write or phone Continental Connector Corporation for your free booklet: 34-63 56th Street, Woodside, N.Y. 11377; (212) 899-4422.

For the Sales Representative Nearest You, See Our Listings in EEM and Gold Book Directories

CONTINENTAL CONNECTORS

CONTINENTAL CONNECTOR CORPORATION • WOODSIDE, NEW YORK 11377

Brownoutproof:

Often the Difference Between Up and Running or Down and Out.

To smooth out the Ups and Downs of today's utility power, digital design engineers are turning to The Dependables - the family of brownout-proof, switching power supplies that virtually eliminates the effects of utility power variations on equipment reliability.

The Dependables can supply their specified outputs at full load over input voltage ranges of 92 to 138 or 184 to 250 VAC; and, in fact, they'll operate for several minutes at inputs as low as 70 or 140 VAC. If AC input fails completely, the supplies will hold up for 30 milliseconds, allowing orderly system shutdown.


In addition to brownout protection, the Dependables feature:

- 0.1% Combined Line and Load Regulation
- 40,000 Hours+ MTBF, Field Proven
- 0 to 50°C Operating Range at Full Load with 80% Output at 70°C
- U.L. Recognition

For over 17 years, Pioneer Magnetics has been designing, building and delivering switching power supplies. Today, more engineers are considering them. Because tomorrow, utility power isn't going to be any better.

For complete information on our standard and customized switching power supplies, contact: Pioneer Magnetics, Inc. • 1745 Berkeley St. • Santa Monica, CA. 90404 • Tel. (213) 829-3305 • TWX 910-343-6249.

| SINGLE OUTPUT SUPPLIES | | | |
|------------------------|-------------|-------------|-------------|
| MODEL | PM2496 | PM2497 | PM2498 |
| OUTPUT VOLTS | OUTPUT AMPS | OUTPUT AMPS | OUTPUT AMPS |
| 2 | 100 | 200 | 400 |
| 3 | 60 | 100 | 300 |
| 5 | 50 | 100 | 200 |
| 5 | — | 1.50 | 300 |
| 12 | 25 | 60 | 120 |
| 15 | 20 | 50 | 100 |
| 18 | 17 | 45 | 90 |
| 21 | 14 | 38 | 76 |
| 24 | 13 | 33 | 66 |
| SIZE (inches) | 5x8x11 | 5x8x11 | 5x16x11 |

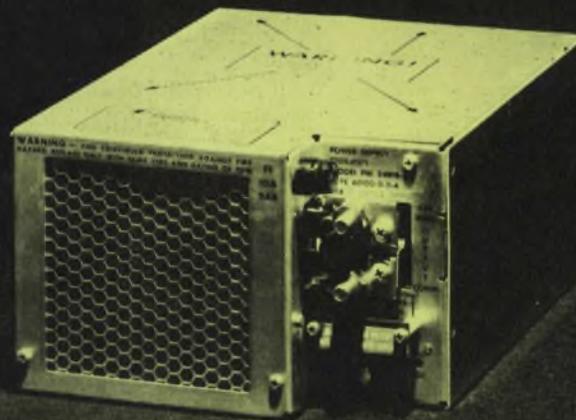

Pioneers in Switching Power Supplies.

Unite μ P hardware and software the easy way. Design a universal test system that checks, debugs or troubleshoots—from breadboard to field.

When you near the end of a μ P-based design and face the problem of joining the nearly completed hardware to the almost finished software, let a universal test system officiate at the final coupling.

Such a test system can be very useful. First, it allows you to communicate with the μ P system through a keyboard. Second, the program can be loaded into a RAM memory from tape generated by either time-sharing or a proprietary development system like Motorola's Exorcisor. Then the μ P system can be operated from the program as stored in the RAM. Third, selected portions of the program can be exercised, and the program modified to perform special tests or system-hardware adjustments. The RAM memory can be tested to ensure that it is operating properly.

A particular advantage in programs with a short turn-around time is that system development and software debugging can proceed on hardware in the breadboard or prototype stage.


Finally, as the system nears completion, it can be operated entirely on its own, but with the test option available in case problems develop.

The test system can still be used for production units even after the μ P product is finished. And when the products are out in the field the test system can serve as a troubleshooting aid, for both hardware and software.

No need to change standard procedure

In developing a μ P system you usually follow a standard sequence of steps: 1. The system requirements are written down in statement form. 2. Algorithms are developed from these statements. 3. Rough code is written and assembled to implement the algorithms. 4. The code is simulated and refined on either a time-sharing system or on a proprietary development system like the Exorcisor or Inteltec.

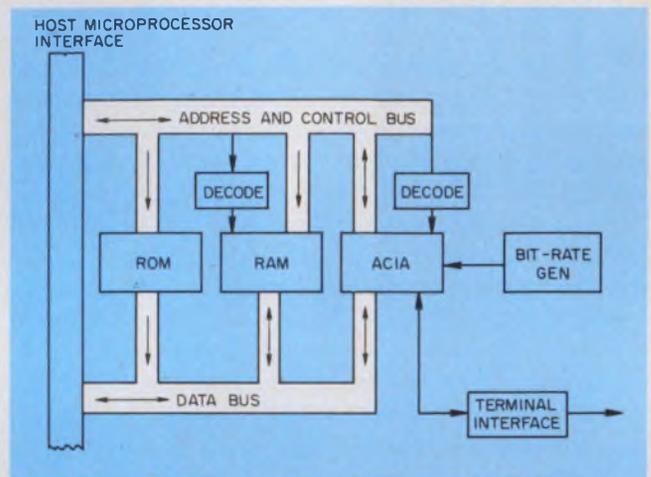Eventually, you must fit the refined program into the hardware system. This ultimate mar-



1. A universal test system consists of a number of LSI and MSI packages. The ROM holds the test program, the RAM acts as a scratchpad, and the ACIA interfaces the terminal with the test system.

riage may not occur until after the system is prototyped. What makes the test system so effective with small μ P systems is that it interfaces with existing hardware without significant modification to that hardware.


Hardware for the test system consists of three LSI packages, four conventional IC packages, an interface connector to the terminal and additional interface connections to the data, address and control buses of the host μ P (Fig. 1).

The LSI packages—all components of the M6800 μ P family—include the Minibug II firmware ROM (this is the same ROM supplied with Motorola's Evaluation Module II), the M6810 RAM as a scratchpad and the M6850 asynchronous communications interface adapter (ACIA) for connection to the terminal.


MSI packages include the MC14411 bit-rate generator, the MC14025 gate package for ACIA address decoding and the MC1489/MC1488 pair, which provides the RS232 interface. If you use a TTY terminal requiring a 20-mA current loop, then a 4N33 optocoupler can act as the interface.

The ROM provides the program that recognizes both requests to perform standard operations and the routines that actually perform

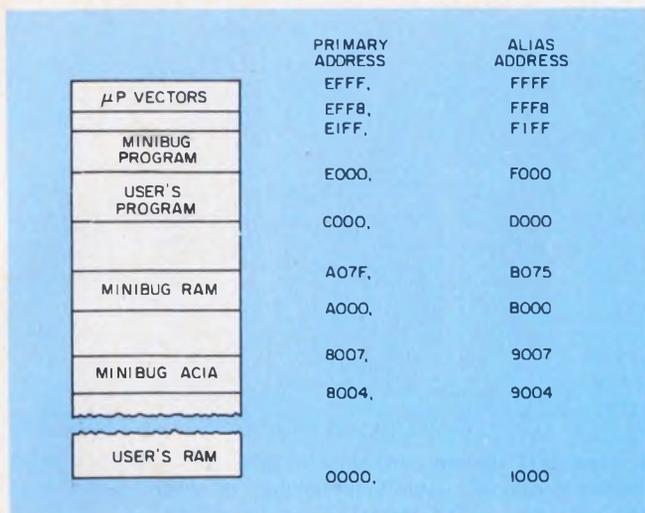Jim Barnes, Senior Project Engineer, and Bert Bergquist, Design Engineer, Motorola Semiconductor Products, 5005 E. McDowell Rd., Phoenix, AZ 85008.



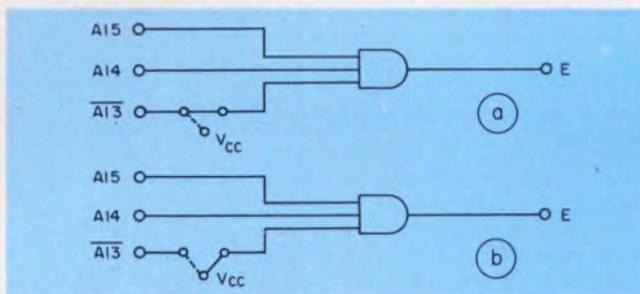2. The memory map shows wired addresses and those used during system start-up.



3. Generation of system-enable signal: in the TEST mode, firmware decodes C to generate an enable signal (a). Without TEST, C or E is decoded (b). Response is to CXXX or FXXX, depending on whether $\overline{A_{13}}$ or V_{cc} is connected.

them. The RAM—in addition to providing dedicated storage areas for stack, target, interrupt and data-enclosing vectors—also contains a small area that can hold limited test routines. Finally, the ACIA provides the serial-to-parallel interface to the terminal.

Connection of the test system is complicated by the μ P-controlled start-up sequence. The μ P's first action is to put all address lines, except A_{15} , at the HIGH level (hexadecimal address FFFE) and then look for the high-order byte of the program's starting address. Next, the μ P puts A_0 HIGH (hex FFFF) and looks for the low-order starting-address byte.

When a program like the Minibug II is used, μ P action must direct a vector to the start of the Minibug II ROM; when the operating system is used alone the same action must point to the start of the system ROM. Similar requirements exist for the interrupt vectors located at FFF8 through FFFD.

Equalizing the addresses

The Minibug ROM is wired to respond to address EXXX, but it must also respond to FXXX at system start-up. To see how this can be accom-

plished, you must interpret these locations in terms of the actual address lines. Hex E and F are equal to binary 1110 and 1111, respectively. The corresponding address line configurations are $A_{15}, A_{14}, A_{13}, \overline{A_{12}}$ and $A_{15}, A_{14}, A_{13}, A_{12}$ respectively.

To make addresses E and F react equally, you need only make A_{12} an X, or a Don't Care. Then the Minibug II ROM—though wired as EXXX—will respond to FXXX.

As shown in Fig. 2, the Minibug II program also reserves AXXX for its RAM and 8XXX for its ACIA. With A_{12} as a Don't Care, the BXXX and 9XXX are unavailable without additional decoding. Since the low-order addresses usually are reserved for peripherals and program RAMs, the CXXX (or DXXX) 2-k byte area is only recommended for programs in small systems; more than 2-k bytes of program call for additional hardware decoding.

When you compare hex F (binary 1111) and hex C (binary 1100), and realize that you have already made A_{12} a Don't Care, you see that F and C differ only in A_{13} . Take advantage of this situation: Hook-up a single-pole, double-throw switch to determine whether the system is in the Minibug II or system-ROM program. Figure 3 shows how to generate the system-enable signal, E. The signal responds to CXXX when $\overline{A_{13}}$ is connected and to either CXXX or FXXX when V_{cc} is connected.

In operation, the system calls those functions that accomplish the desired end. These functions include:

- Read a memory location to a printer.
- Write into any memory location from an external keyboard.
- Write into memory from tape.
- Print a designated section of memory on either printer or tape (with computed checksum).
- Vector to a target program.
- Memory test (five patterns and a walking-bit test).
- Punch and load binary tape.

The memory-test function allows exhaustive testing of any block of memory the designer may designate by use of the M function. The tests are as follows:


- A Walking address.
- B Write FF into all locations and verify.
- C Write AA into all locations and verify.
- D Write 55 into all locations and verify.
- E Write 00 into all locations and verify.
- W Write a single walking bit through the entire memory.

As each test is completed, the corresponding letter is typed—if a test fails, the user knows immediately which one.

The function, "Punch binary tape," allows punching the exact contents of memory on tape

Table 1. Memory examine-and-change sequences

| ENTER (Command) | RESPONSE |
|-----------------------------------|---|
| M | Space |
| XXXX (4 Hex digit memory loc.) | Space XX (2 Hex digit of memory contents.) |
| XX (2 Hex digit of new data.) | |
| C.R. or L.F. or ↑ | 1) C.R. stores data and responds with* 2) L.F. stores data, increments address and opens that location. 3) ↑ stores data, decrements address and opens that location. |

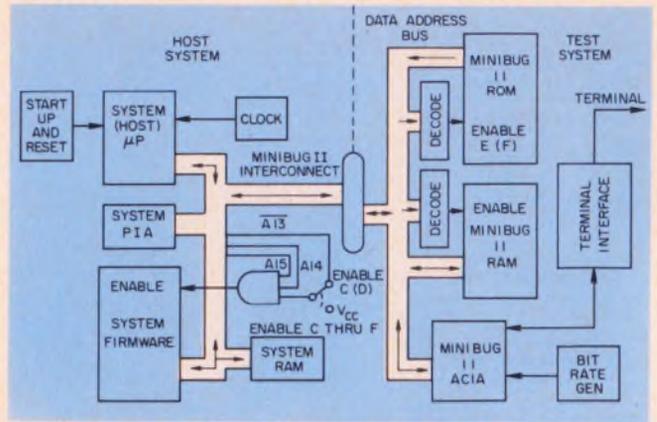

4. How test system connects to host μ P system. Little hardware change usually is needed to interconnect the two systems. A TTY terminal can be used.

Table 2. Test system response and command

| ENTER (Command) | RESPONSE | ENTER | RESPONSE |
|-----------------------------|----------|--|---|
| G | Space | XXXX (4 Hex digit users starting address) | Goes to user's program and executes instruction sequence. |
| DISPLAY REGISTERS | | | |
| R | | | Prints register contents as follows: condition code ACCB ACCA INDEX P COUNTER STACK XX XX XX XXXX XXXX XXXX |
| MEMORY TEST FUNCTION | | | |
| W | Space | | A B C D E W, carriage returns, prints*. |
| PUNCH BINARY TAPE | | | |
| Y | | | Tape is punched, carriage returns and prints*. |
| READ BINARY TAPE | | | |
| Z | | | Memory is read to printer, carriage returns, prints*. |

—no ASCII II conversion is made, as is when talking with a printer. A tape header is generated that includes the word count and starting address. Record length is 256 words. If the record is longer, another header is inserted after each 256-word sector.

The "Read binary tape" function is exactly the inverse of the punch binary tape function—the record is written into memory at the starting address contained in the tape header.

Note that, with the test system, the memory-examine-and-change sequence should be learned first, because this sequence sets up portions of other commands (Table 1).

With the test system and a terminal both properly connected to your system (Fig. 4), and with the power on, a press of the system reset or restart button causes the terminal to respond with a carriage return, line feed and a printed asterisk. The system is now ready to accept commands from the terminal.

To load tape into memory, first load a formatted tape into the terminal and set the tape reader to Auto. Then just enter the command "L" following the asterisk, and the tape is loaded. To print out the memory contents or punch a formatted tape, first enter the high and low-order starting-print address into memory locations A002 and A003. Then enter into locations A004 and A005 the high and low-order END print address. After the asterisk appears, enter the command "P." The response is printout or recording of the formatted data.

To use the program-interrupt sequences, enter the assigned addresses into the test system as follows: at memory locations A001 and A002, the high and low-order hardware-interrupt vector; at A006 and A007, the nonmaskable interrupt; and at A00C and A00D, the software-interrupt vector.

The various commands associated with the user's program are given in Table II. ■■


THE MICROCOMPUTER MEMORY THAT STAYS ON WHEN THE POWER GOES OFF.

Ampex MCM. Microcomputer Core Memory. It retains everything, even in the event of a total power failure. No batteries or other tricks, just the unflappable reliability of magnetic core technology.

Ampex MCM comes complete, with all timing and control, data and address registers, decoding and drive circuits and, of course, your choice of core capacity. You can specify the word length you need from 4 to 18 bits, and storage for 256 to 4096 words, in all popular binary increments.

Modest-capacity MCM modules are complete on a single board; use as many as required to achieve the total capacity you desire. All of them are available with a single connector strip, with pinouts to suit your design.

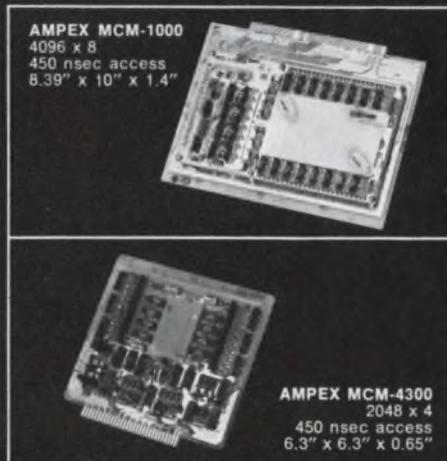
Ask yourself if your microcomputer-based system can afford a program loss due to power interruption. If you answer "no" to that question, then you'll answer "yes" to Ampex MCM modules. They offer the least expensive protection you can buy. When the power goes off, they stay on.



Ampex Memory Products Division
13031 West Jefferson Boulevard
Marina del Rey, CA 90291, 213-821-8933

AMPEX

Darlington that last.

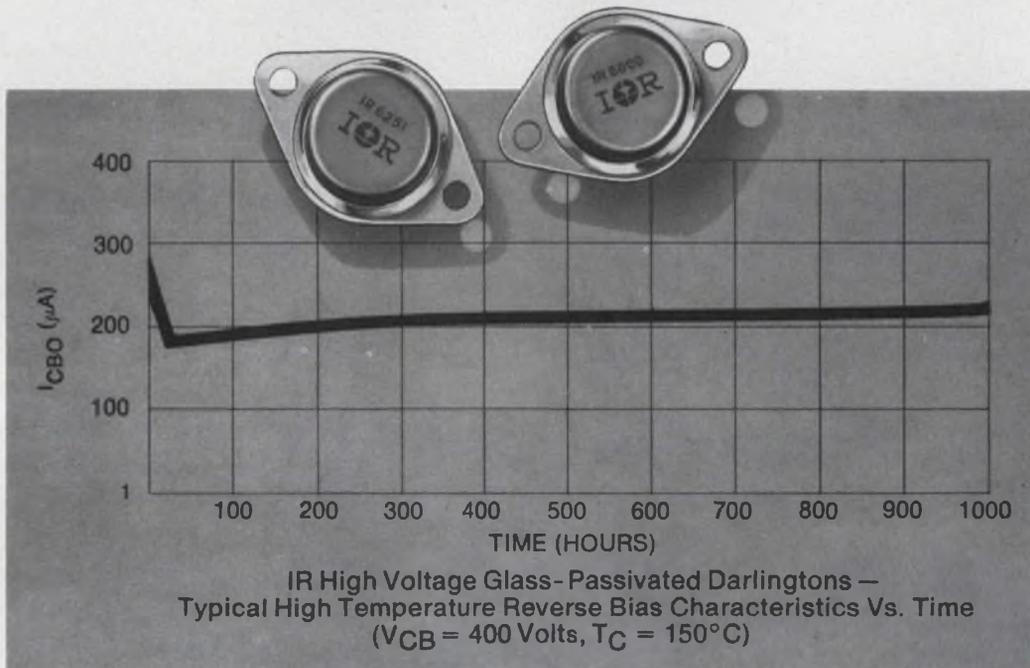

Whether you use Darlington or discretes, without high-temperature stability, you're dead. Failure may be a boon to the aftermarket, but for OEM's it can start something big... and bad.

Stability testing of IR Darlington shows a remarkable 210 microamps leakage after operating 1000 hours at 400 Volts V_{CB} and 150°C ! We don't think anyone can top it with present technology.

It's due to our hard-glass passivation techniques, plus 28 years' experience building high reliability power semiconductor devices.

New 20KHz Series

Our three new series of fast-switching Darlington (using an internal speed-up diode) give you this superb stability, plus the great per-

| Series | Ic Peak | Total max tr/ts/td | V _{CEO(SUS)} |
|--------|---------|--------------------|-----------------------|
| IR6251 | 15A | 3.75µs | 350-450V |
| IR6000 | 20A | 3.90µs | 300-400V |
| IR6060 | 25A | 3.90µs | 300-400V |

3 New Series for 20KHz Switchers.

formance you need for switching power supplies. Like a rise/storage/fall time total that's typically 50% below maximum rating, guaranteed minimum gains, plus lower sats and a wide SOA.

New 900V Darlington Series

While you're getting data, ask about our new super-voltage, 500 to 900Volt $V_{CEO(SUS)}$ devices, and our many other high gain high-voltage series for 5KHz applications.

And if you're thinking of paralleling, ask for our "Paralleling Power Transistors" paper.

It's full of valuable information that can save you a lot of time and money.

Above all, think of our device stability. For more peace of mind... at no extra cost.


International Rectifier



the innovative power people

233 Kansas St., El Segundo, CA 90245, (213) 678-6281

CIRCLE NUMBER 37

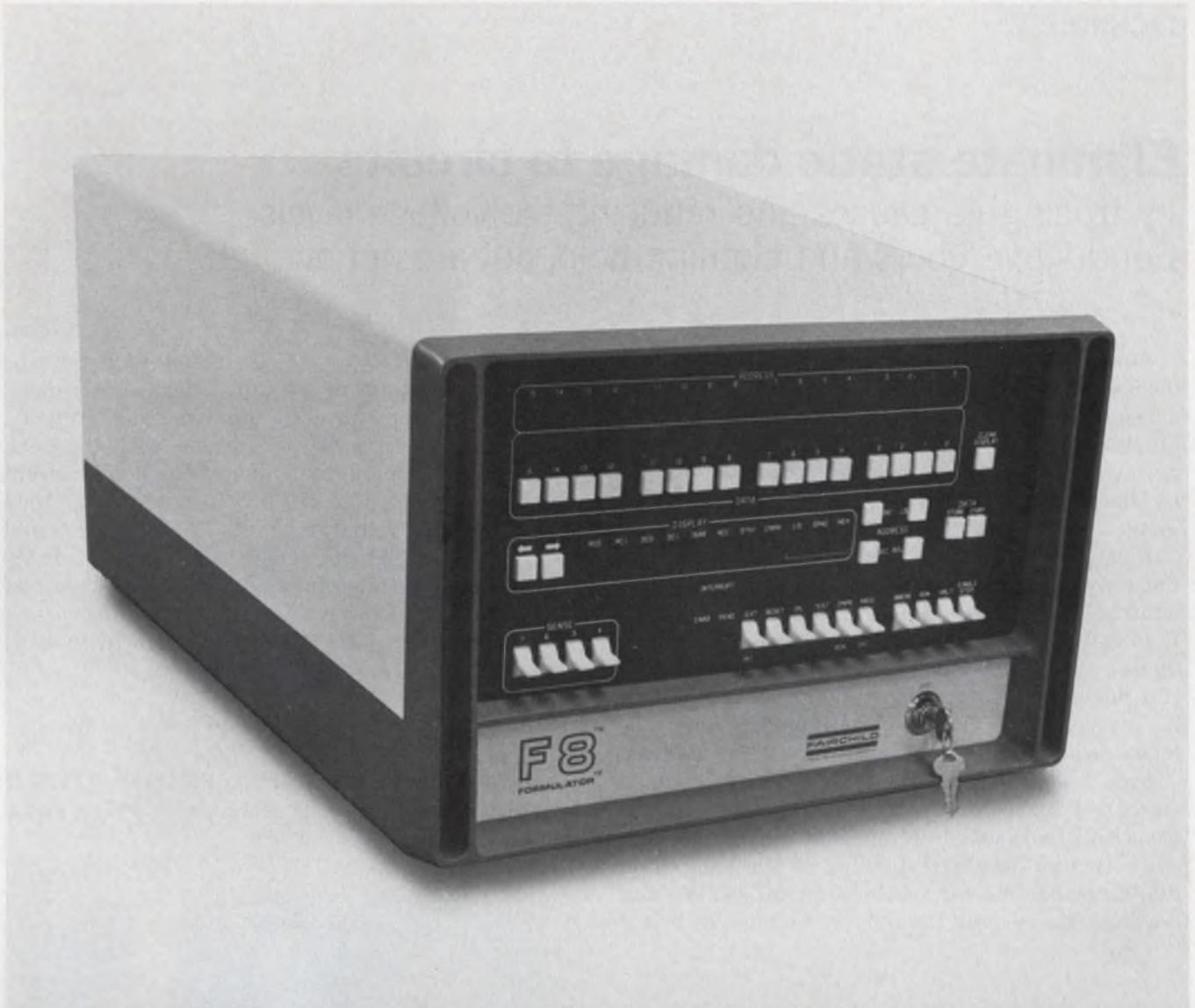

Fairchild's F8 Formulator: It gets you from μ p design to hands-on prototype in half the time.

The Formulator is a powerful new microprocessor development tool that offers you all the design assistance you'll need to develop a microprocessor-based system or product. It saves time by:

1. Eliminating the need for an external system breadboard.
2. Putting your design energy where you need it: On the non-microprocessor circuits and on the operating features of your total product.
3. Providing real-time program execution. The system uses actual F8 I/O components to provide I/O to the system, ensuring an exact reproduction of F8 waveforms and circuit levels.
4. Enabling you to edit, assemble

and debug fast and efficiently.

5. Keeping all the system software resident in the machine while developing your program. No loading and reloading of system software.
6. Providing an intelligent front panel which makes debugging effortless.
7. Letting you examine and alter storage, set hardware breakpoints and single-step the central processor.
8. Providing self-test at the push of a button.

The Formulator can be interfaced with either an HP2644 terminal or an ASR33. Fairchild offers a fully integrated software package including an operating

system complete with monitor, text editor, assembler and debug package.

The Formulator was designed by systems people with reliability and maintainability as a design criteria. Each Formulator is burned in for 120 hours at 120°F prior to shipment. The Formulator can be delivered immediately—lease or rental plans are available. Write for more information to: Fairchild Microsystems Division of Fairchild Camera & Instrument Corporation, 1725 Technology Drive, San Jose, California 95110. Phone (408) 998-0123

FAIRCHILD
MICRO SYSTEMS

CIRCLE NUMBER 38

Eliminate static damage to circuits

by tracing its causes and reducing the voltage levels.
Conductive floors and clothing help, but are not enough.

Static discharges can damage many solid-state devices, but you can prevent this by using an energy-storage model to help minimize the causes of static buildup. Many of the potentially dangerous electrostatic voltage levels are generated by operator movement or assembly-line movement.

Relatively low static-voltage levels can damage not only MOS devices, which are commonly recognized to be static-sensitive, but also junction field-effect transistors, some bipolar devices, diodes, thick-film resistors and other small junction devices. The potential for damage is especially severe in the low-relative-humidity environments usually found in assembly and design areas.

Fig. 1 shows typical static-discharge damage sustained by a 2N3112 JFET. In some circuits the JFET will still function and appear normal, even though localized heating from the static discharge has melted a thin elliptical section and lowered the reverse breakdown voltage to below normal.

Use an energy-storage model

To study the effects of operator-generated static-energy discharge on semiconductor devices, use an energy-storage model of the body (Fig. 2a). The body acts as one plate of a capacitor, C_H , which is in series with the skin and body resistance, R_H . The other plate of the capacitor is formed by the ground.


Published values for C_H range from 100 to 10,000 pF and from 0 to 18 k Ω for R_H , depending upon the measuring method selected.¹⁻¹⁶ To arrive at realistic values for use in this article, the measurement circuit of Fig. 2b was used to compute R_H and C_H from charge and discharge waveforms observed on an oscilloscope.

The test subject was connected to a mercury relay through a wrist strap that had a surface area of 40 sq. cm. First, the subject was charged to a dc potential between 200 and 2000 V, then

discharged through a 1-k Ω resistor. From the discharge waveform, we can determine the peak current, I_p , and the discharge time constant, T_c . The value of I_p is then compared with the peak current I_0 , which is the value of the body current if $R_H = 0$ and $C_H = 270$ pF. R_H and C_H are then calculated and found to be: $R_H = 87$ to 190 Ω and $C_H = 132$ to 190 pF, which compares favorably with earlier results obtained under discharge test conditions.^{8,15} So, for the rest of this discussion, the values $R_H = 100$ Ω and $C_H = 218$ pF will be used.

Determine device sensitivity

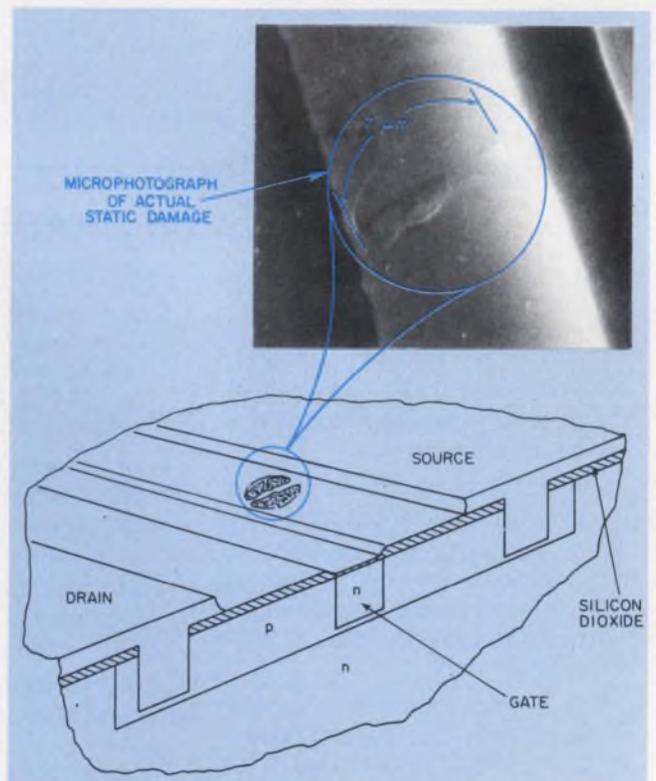Let's see what happens to a 2N4118A JFET if we use these three test methods to judge static discharge damage (Fig. 3):



1. Static damage to a JFET can be caused by voltage discharges into the gate without necessarily destroying the JFET. However, the JFET fails more readily if stressed near its voltage limit.

Whitson J. Kirk Jr., Lane S. Carter and Max L. Waddell, Staff Engineers, Electronic Products Dept., Bendix Corp., P.O. Box 1159, Kansas City, MO 64141.

1. A human-body model charged with a dc power source.
2. A human body charged with static voltage generated by movement.
3. A human body charged with a dc power source.

In each test, C_H was charged to a known voltage and then discharged through the gate-source junction of the JFET. A change in the junction reverse-breakdown voltage at a junction current

breakdown voltage, with no significant change in transconductance or pinch-off voltage. These devices would perform normally for a time in many applications. However, the effects in Fig. 1 resemble the melt transition that results from the second breakdown of a pn junction.¹⁷ And increased current density in the melt region can reduce operating life and power-dissipation capability.^{18,19}

- The resistance in series with the JFET gate

Table 1. Observed effects of JFET test

| Test Conditions ¹ | Device-Failure Voltage Levels ² | | | | | | | | | | |
|---|--|----|-----|-----|-----|-----|-----|------|------|------|-----|
| | 70 | 85 | 100 | 120 | 140 | 160 | 190 | 230 | 270 | 320 | 380 |
| Human-Body Electric Model Direct-Current Charge $R_H = 0, C_H = 97$ $R_H = 0, C_H = 218$ $R_H = 0, C_H = 425$ $R_H = 100, C_H = 218$ | | | | | | | | | | | |
| | | | | | | D | | | D | D | |
| | | | | | CCD | | | | CC | | |
| | | | C | | C | C | D | | | | |
| | | | | | | | D | CCCD | CDDD | CCDD | CC |
| Actual Human Body Movement-Generated Charge Direct-Current Charge | | | | | | | | | | | |
| | | | | | C | D | | | | | D |
| | | | | | DD | C | | C | | | |

Notes:

1. R_H values in ohms, C_H values in picofarads.
2. Each JFET receives one discharge pulse at each test voltage until failure occurs. The letter C indicates catastrophic failure when the reverse breakdown voltage drops to less than 3 V. The letter D indicates degradation when the 5- μ A gate-source reverse breakdown voltage decreases by 50%.

of 5 μ A provides a sensitive indicator of degradation. The results of this experiment are summarized in Table 1. Degradation did not vary appreciably with different discharge sources.


Other results from this experiment include these:

- The discharge levels at which the failure occurred were lower with reverse-breakdown polarity (100 to 380 V) than with forward-conduction polarity (600 to 765 V) on the gate-source junction.


- The capacitance value or energy level influenced, to some extent, the voltage required to degrade the transistor. CMOS circuits with diode protection were also found to be energy-sensitive. Unprotected MOS proved to be voltage-sensitive rather than energy-sensitive.

- Repeated discharge pulses at voltages below the degradation level didn't significantly degrade the device. This indicates that progressive degradation from repeated pulses is minimal. The mean degradation voltage for a 15-sample group that received a single pulse at each voltage was 282 V. Another group of five devices was given 10 pulses at each voltage; these ended up with a mean of 230 V. There was no statistical difference between the two groups.

- Half of the JFETs showed a decrease in

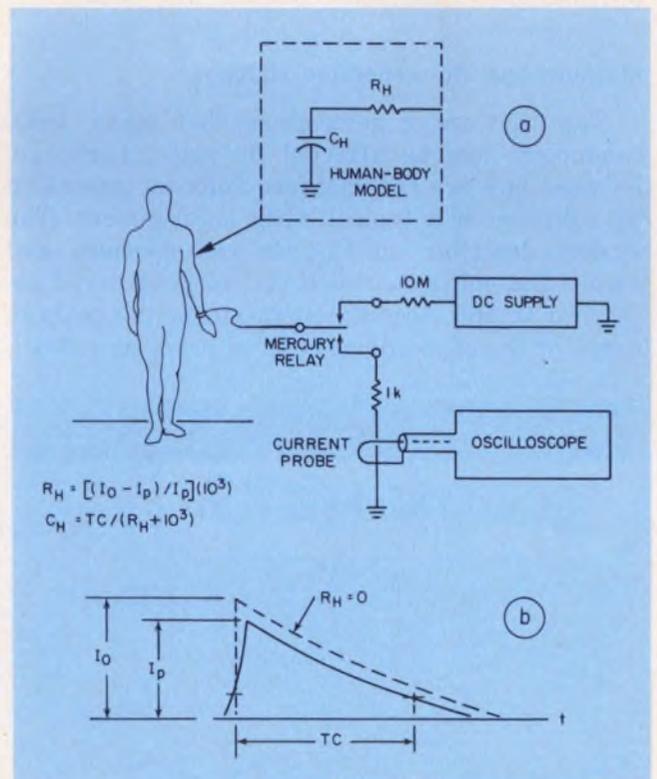

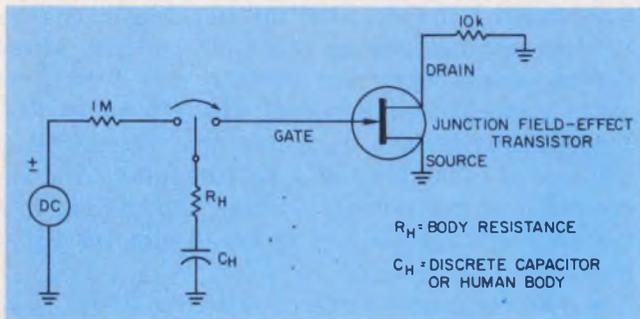2. A model of the human body starts the analysis of how voltages build up (a). By measuring the rise and decay times we can calculate the time constant and thus the values of R_H and C_H (b).



3. The charge-discharge model for the human body indicates how energy is stored from a dc source and then discharged through the small-signal device under test.

limits the current arising from discharging voltages, thereby providing some protection to JFET and CMOS devices. Normal body resistance doesn't sufficiently isolate the device. Series resistances well above 1 MΩ are required for protection against voltages as high as 4 kV.

In another study, several bipolar transistors, some diodes and some FETs were tested with the circuit of Fig. 3. The results are tabulated in Table 2. Initial pulses for MOS devices were 16 V; for all other devices, they were 70 V. If the pulse resulted in no change in the reverse breakdown voltage, the pulse voltage was increased by 20% and the test repeated; the maximum voltage applied was 3 kV. Although FETs proved to be the most sensitive to static discharge, some degradation of the other devices was found.

Measure operator-generated voltages

Now that we've determined that many semiconductors can be affected by static discharge, let's see how we can measure voltages generated by subjects in a typical work environment. The system described in Fig. 4a can measure and record the voltages, and it can respond in 12 μs. Critical to the circuit's operation is the maintenance of the capacitively coupled probe at a fixed,

calibrated distance from the conductive disc connected to the operator.²⁰ A typical voltage output generated by the subject intermittently gliding on an insulated chair and walking across a conductive floor is shown in Fig. 4b.

The floor was of conductive vinyl tile, which has a resistance of 0.95 MΩ.²¹ The chair was insulated with rubber rollers, and the subject was wearing composition-soled street shoes. The relative humidity was 4%. Under these conditions, spikes of 700 V were generated; these can degrade small-junction devices. Although portable static meters and electrostatic voltmeters can measure dc static voltages, they cannot detect rapid transients.²²

After the subject had been monitored for several conditions, the results were summarized (Table 3) and some conclusions drawn:


- With the exceptions noted in the table, peak generated voltages were observed at points where the feet of the subject partly or totally lost contact with the ground plane. This is typical when a reduction in capacitance increases triboelectric voltage.

- Conductive-soled shoes or conductive shoe covers limit voltage generation on a conductive floor to 50 V or so, as long as the shoes remain in contact with the conductive surface.

- When the relative humidity is 45%, a subject's street clothing does not provide a conductive path between the skin and the conductive seat of a chair. (Typical resistance through street clothing was found to be about 10 GΩ).

- Neither conductive shoes on an insulated floor nor insulated street shoes on a conductive floor provide static protection.

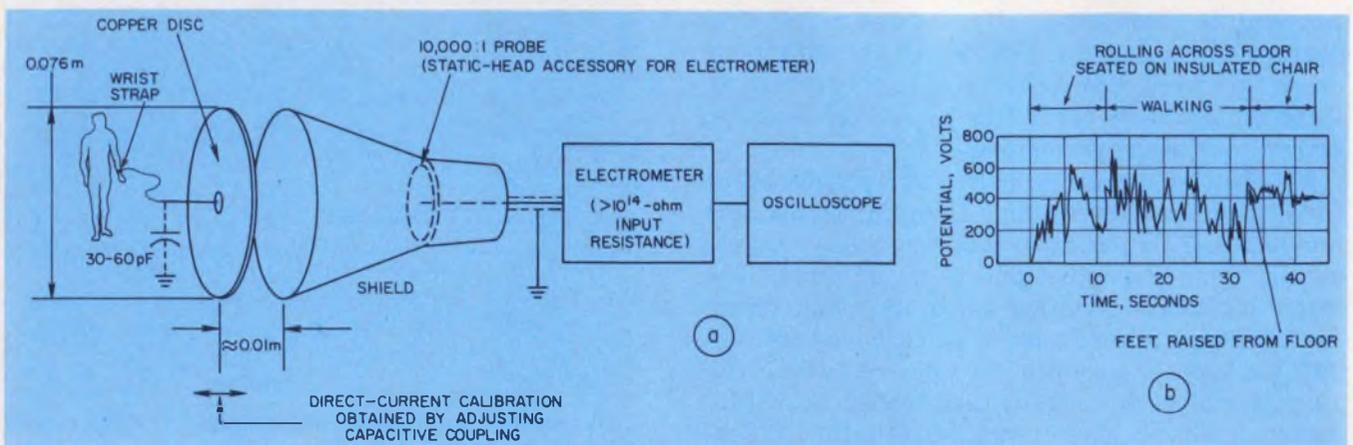The time it takes for a movement-generated charge to dissipate is also important. The graph in Fig. 5 shows how voltage dissipates from a 500-V starting level for a variety of environmental conditions. With conductive shoes, on a conductive floor, the charge on a subject can dissipate in less than 1 ms, which means there



4. To monitor the generated electrostatic voltage, a test set can be built with an electrometer amplifier (a). The

voltage peaks generated by the moving subject can be measured on an oscilloscope (b).

is a good probability that any charges will dissipate before contact is made with a static-sensitive device. The three rates observed with leather street shoes on a conductive floor vary so markedly that this combination cannot be considered reliable. All other conditions studied have even slower discharge rates, though, which makes them even more dangerous.

As seen on the graph, an increase in relative humidity decreases the discharge time for composition-soled shoes on a conductive floor. However, to ensure adequate protection, a relative humidity much higher than 45% would be required, but then the working conditions might become uncomfortable or undesirable for sensitive circuits.

The effect of subject-to-ground shunt resistance on the peak voltage generated is shown in Fig. 6. For the shoe and floor materials tested, any combination of conductive devices that *always* ensures a resistance of less than 10 MΩ between body and ground provides good static protection for MOS devices and an R of less than 100 MΩ for junction devices. Other materials, such as rubber-soled shoes or waxed floors, could produce higher peak voltages, which would then require lower shunt resistances.

Minimize the static hazard

By modifying facilities and process procedures, you can minimize the hazard of static-discharge damage to solid-state devices without requiring an operator to think about being grounded before handling components or assemblies. A wrist strap offers poor grounding protection, at best.

Minimum design requirements for a static-discharge-protected facility include:

- A conductive floor with a resistance in the 25-to-300-kΩ range, tested in accordance with National Fire Protection Association codes. The 1-MΩ upper limit in the codes is marginal; an upper limit of 300 kΩ indicates a more uniform distribution of conductive path and thus lowers peak voltages.

- Conductive shoes with a maximum resistance of 500 kΩ, tested under the same guidelines as the floor.

- Conductive chairs with a maximum resistance of 1 MΩ between the seat and a metal plate under the chair. If a foot rest or rollers are provided, they also must be conductive. (Although the conductivity through an operator's clothing may be low, the presence of the grounded seat reduces voltage amplification when the feet of the operator are lifted from a grounding plane.)

- Conductive foot rests under the table.

To validate reliability, at periodic intervals resistance measurements should be made on each operator at his work station. The operator-to-

Table 2. Typical device degradation threshold

| Device | Test Results | |
|---|-------------------------------|--|
| | Threshold, ¹ volts | Degradation criteria ² |
| Diodes | | 50% drop in V_{Rr} at $I_{Rr} = 5 \mu A$ |
| 1N459 | >3000 | |
| 1N916 | 3000 | |
| TI551 | 450 | |
| 1N4151 | >3000 | |
| Zener Diodes | | 50% drop in V_{Rr} at $I_{Rr} = 5 \mu A$ |
| LVA356 | >3000 | |
| Transistors | | 50% drop in $V_{(BR)CBO}$ at $I_{Rr} = 5 \mu A$ |
| 2N2222 | 1000 | |
| 2N2369A | 460 | |
| 2N2432A | 620 | |
| 2N2540 | 1450 | |
| 2N2907 | 1200 | |
| 2N3117 | 1000 | |
| 2N3570 | 380 | |
| 2N4251 | 460 | |
| 2N4872 | 1200 | |
| 2N5154 | >3000 | |
| Junction Field-Effect Transistors | | 50% drop in $V_{(BR)GSS}$ at $I_{Rr} = 5 \mu A$ |
| 2N2608 | 320 | |
| 2N3112 | 530 | |
| 2N3971 | 160 | |
| 2N4118A | 140 | |
| Metal-Oxide-Semiconductor Transistors | | $I_{Rr} > 5 \mu A$ at $V_{GS} = 22 V$ |
| GI MEM 520c (chip) | 58 | |
| Complementary Metal-Oxide-Semiconductor Integrated Circuits | | > 0.5 μA input at 10 V or > 10% decrease in output voltage across 100-kΩ load |
| RCA CD4001 | 250 | |
| Silicon-Controlled Rectifiers | | 50% increase in I_{CGO} |
| 2N886A | 680 | |
| 2N3030 | 1000 | |

Notes:

1. Reverse-breakdown polarity.

2. Where V_R is the reverse voltage, I_{Rr} the reverse current, $V_{(BR)CBO}$ the collector/base breakdown voltage, I_B the base current, $V_{(BR)GSS}$ the gate/source breakdown, I_G the gate current, V_{GS} the gate/source voltage and I_{CGO} the gate leakage current.

ground resistance is voltage-dependent and cannot safely exceed the limiting protection resistance implied in Fig. 6. A system check like this accounts for the random distribution of conductive particles on both floor and shoes, and should be used to supplement standard floor and shoe-resistance measurements. And don't forget conventional precautionary equipment, such as conductive tabletops, conductive foam packaging and soldering irons with grounded tips.


The spray cleaning of electronic assemblies with

Table 3. Typical generated voltages

| Shoe/Chair Combination | Peak Voltage Generated ¹ | | |
|--|--------------------------------------|--|------------------------------|
| | Conductive Floor I ² | Conductive Floor II ³ | Insulated Floor ⁴ |
| Conductive-Soled Shoes Conductive Chair Insulated Chair | 20 | 100 500 | 700 |
| Leather-Soled Shoes Conductive Chair Insulated Chair | 340 1200 | 370 900 | 600 800 |
| Composition-Soled Shoes (man-made) Conductive Chair Insulated Chair | 500 ⁵ 500 ⁵ | 1100 ⁵ 1100 ⁵ | 1050 ⁵ 1550 |

Notes:

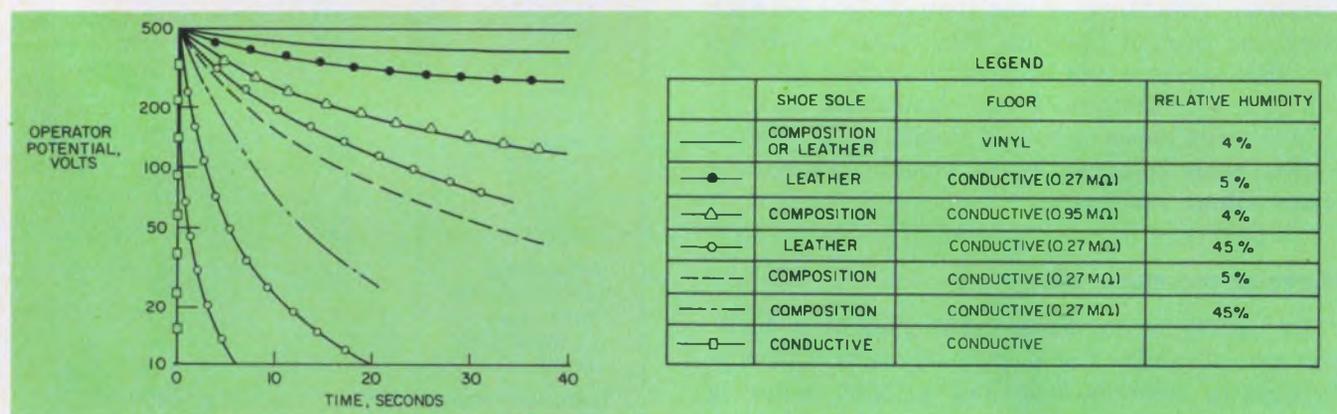1. For an operator walking to chair, sitting down and lifting feet.
2. A conductive tile floor with 0.27-M Ω resistance, relative humidity of 45%, R_o of 0.5 M Ω from operator through conductive shoes and floor to ground, with 1 μ A measuring current.
3. A conductive tile floor with 0.95-M Ω resistance, relative humidity of 4% and R_o of 11 M Ω .
4. Insulated vinyl tile floor and relative humidity of 4%.
5. Peak voltage observed during walking phase of operation.



5. Electrostatically generated voltages decay at a rate that depends upon the relative humidity and the material. Solvent after soldering operations can also generate potentially dangerous electrostatic charges.²³ The polarity and magnitude of the charges is a function of the resistivity of the solvent, the spray rate and the triboelectric voltages or contact potential of the solvent and assembly materials. Assemblies that get this precharge can be damaged if the gate of a JFET is accidentally grounded. The charge, however, must have the proper polarity to impose an excessive reverse-breakdown potential on the gate.

To study the effects of various solvent systems, several solvents that produce positive and negative charges were used to neutralize the voltage on a printed-circuit board.

The PC laminate selected was epoxy glass (Type GH per MIL-P-13949), the spray pressure was 234 kilopascals (34 psig), and the relative humidity was 4%. Table 4 shows some of the compositions studied, and the test results are plotted on the graph of Fig. 7. Mixing a low-resistivity solvent with the normal cleaning solvent results in improved control of charge generation.

The upper limit on solvent volume resistivity

materials in the floor and clothing. Decay times can take several minutes to reach safe levels.

for adequate protection under the test conditions was 50 k Ω -m. Although ethanol was used in the controlled experiments, other low-resistivity polar solvents are equally suitable. ■■

References

1. Lenzlinger, Martin, "Gate Protection of MIS Devices," *IEEE Transactions on Electron Devices*, (Vol. ED-18, No. 4, April, 1971, pp. 249-257.
2. Morse, A.R., comment on paper by W.B. Kouwenhoven and W.R. Milnor, "Field Treatment of Electric Shock Cases I," *AIEE Transactions on Power Apparatus and Systems Part III* Vol. 76, No. 4, April, 1957, pp. 82-87.
3. Lee, Ralph H., "Electrical Safety in Industrial Plants," *IEEE Spectrum*, Vol. 8, No. 6, June, 1971, pp. 51-55.
4. "Using Electrically Operated Equipment Safely With the Monitored Cardiac Patient," Hewlett-Packard Co., Waltham, MA, March, 1970, pp. 22.
5. Molinski, A.E., "Effects of Electricity on the Human Body," *Mining Congress Journal*, Vol. 56, No. 7, July, 1970, pp. 64-68.
6. Friedlander, Gordon D., "Electricity in Hospitals: Elimination of Lethal Hazards," *IEEE Spectrum*, Vol. 8, No. 9, September, 1971, pp. 40-51.
7. Montesi, Louis J., "The Development of a Fixed-Gap Electrostatic Spark Discharge Apparatus for Characterizing Explosives," *Proceedings of the Sixth Symposium on Electroexplosive Devices*, San Francisco, July 8-10, 1969, The Franklin Institute Research Laboratories, Philadelphia, PA. pp. 2-8.1.

Table 4. Cleaning solvent mixtures

| Solvent System | Compositions Studied | | | | | |
|----------------|--------------------------|----------------------------------|-----------|------|------|------|
| | Component | Concentration, percent by volume | | | | |
| A | trichloroethylene | 100.0 | 90.0 | 80.0 | 72.5 | 50.0 |
| | trichlorotrifluoroethane | 0.0 | 6.5 | 13.0 | 17.9 | 32.5 |
| | ethanol | 0.0 | 3.2 | 6.3 | 8.6 | 15.7 |
| | methanol | 0.0 | 0.3 | 0.7 | 1.0 | 1.8 |
| B | tetrachloroethylene | 80.0 | 66.4 | 60.0 | 53.6 | 40.0 |
| | 2-ethoxyethanol | 20.0 | 16.6 | 15.0 | 13.4 | 10.0 |
| | trichlorotrifluoroethane | 0.0 | 11.0 | 16.3 | 21.5 | 32.5 |
| | ethanol | 0.0 | 5.4 | 7.8 | 10.3 | 15.7 |
| | methanol | 0.0 | 0.6 | 0.9 | 1.2 | 1.8 |
| C | trichloroethylene | 59.6 | azeotrope | | | |
| | ethanol (200-proof) | 40.4 | | | | |

8. Petrick, John T., "Discharge of an Electrostatically Charged Human," *Proceedings of the Sixth Symposium on Electroexplosive Devices*, San Francisco, July 8-10, 1969, The Franklin Institute Research Laboratories, Philadelphia, PA, pp. 3-5.1.

9. Silsbee, Francis B., "Static Electricity," *National Bureau of Standards Circular C438*, June 10, 1942, p. 23.

10. Schroeder Jr., C.F., "Energy Transfer in Electrostatic Arcs," *Proceedings of the Fifth Symposium on Electroexplosive Devices*, Philadelphia, June 13-14, 1967, The Franklin Institute Research Laboratories, Philadelphia, PA, pp. 2-5.1.

11. Eichel, F. G., "Electrostatics," *Chemical Engineering*, Vol. 74, No. 6, March 13, 1967, pp. 153-167.

12. Taylor, Boyd C., "Electrostatic-Insensitive Detonator for Precise Synchronization," *Proceedings of the Sixth Symposium on Electroexplosive Devices*, San Francisco, July 8-10, 1969, The Franklin Institute Research Laboratories, Philadelphia, PA, pp. 1-10.1.

13. Pitts, L. D., "Demythologizing Electrostatics," *Proceedings of the Sixth Symposium on Electroexplosive Devices*, San Francisco, July 8-10, 1969, The Franklin Institute Research Laboratories, Philadelphia, PA, pp. 3-7.1.

14. "Static Electricity," *National Fire Codes*, National Fire Protection Association, Boston, 1973-74, Vol. 9, No. 77, p. 144.

15. Tucker, T.J., "Spark Initiation Requirements of a Secondary Explosive," *Annals of the New York Academy of Sciences*, Vol. 152 Article 1, October 28, 1958, pp. 643-653.

16. Hamiter, Jr., L. C., "How Reliable are MOS ICs? As Good as Bipolars, Says NASA," *Electronics*, Vol. 42, No. 13, June 23, 1969, pp. 106-110.

17. Smith, W.B., Pontius, D.H., and Budenstein, P.P., "Second Breakdown and Damage in Junction Devices," *IEEE Transactions on Electron Devices*, Vol. ED-20, No. 8, August, 1973, pp. 731-744.

18. Lumley, R.M. and Neiswender, W.J., "Personnel Grounding: A Case History," *IEEE Transactions on Industry and General Applications*, Vol. IGA-2, No. 5, September/October, 1966, pp. 417-422.


19. Rose, S.E., "Static Electricity Can Cause Bipolar IC Failures," *Evaluation Engineering*, Vol. 10, No. 3, May/June, 1971, pp. 21-24.

20. Nowac, R.J., "How Not to Get a Charge Out of Static Electricity," *Machine Design*, Vol. 43, No. 21, Sept. 2, 1971, pp. 76-80.


21. "Inhalation Anesthetics," *National Fire Codes*, National Fire Protection Association, Boston, 1973-74, Vol. 2, No. 56A, p. 55.

22. Stroh, D. G., "Static Electricity Can Kill Transistors," *Electronics*, Vol. 35, No. 1, Jan. 12, 1962, p. 90.

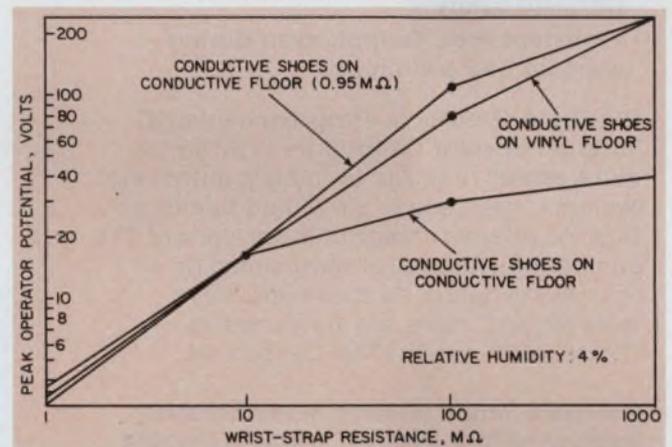23. Hedlund, C.F., "Static and Lightning Protection Grounding," *IEEE Conference Record of 1970 Joint Technical Conference on Industrial and Commercial Power Systems and Electric Space Heating and Air Conditioning*, Institute of Electrical and Electronics Engineers, Document 70C 8-IGA, New York, 1970.



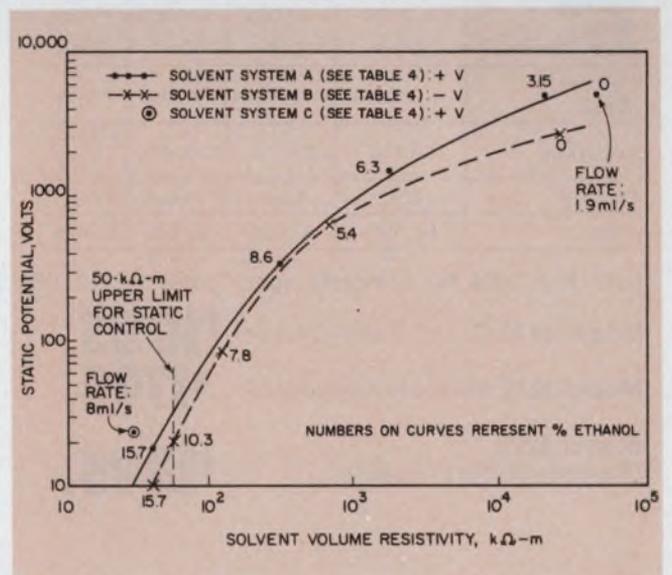6. Operator-to-ground shunt resistance affects the peak voltage generated when the operator walks. As the resistance increases, less and less of the voltage can leak off.



7. Spray cleaning solvents, depending upon their resistivity, can affect static charge generation. Ethanol, with its low resistivity, helps minimize the potential build-up and thus the static damage.

New Programmable Calibrators With Power.

A precision source for Voltage and Current from one instrument!

- Output $\pm 1\mu\text{V}$ to $\pm 200\text{V}$ and $\pm 1\mu\text{A}$ to $\pm 200\text{mA}$.
- Short Circuit Protection on all ranges
- Keyboard Lockout prevents accidental program changes
- Compliance Voltage Limiting for intrinsic safety
- Transient-Free Output, even during start-up and switching.

DigiTec's Precision, Programmable, DC Voltage/Current Calibrators provide the **extra power** required in today's automatic systems. Interface is simplified because DigiTec offers a choice of three types of TTL compatible remote programming or a remote keyboard. All these important features and more are furnished as STANDARD on DigiTec Calibrators.

Compare other leading manufacturers sources with a DigiTec Voltage/Current Calibrator for output and features.

| FEATURES | DIGITEC 3210/3220 | DIGITEC 3110 | SD | EDC |
|---------------------|--------------------|--------------------|-------------------|------------------|
| Remote Programmable | Yes | No | Yes | Yes |
| Voltage Mode | $\pm 200\text{V}$ | $\pm 100\text{V}$ | $\pm 100\text{V}$ | $\pm 10\text{V}$ |
| Max. Current | 200mA | 100mA | 50mA | 50mA |
| Current Mode | $\pm 200\text{mA}$ | $\pm 100\text{mA}$ | None | None |
| Accuracy | 0.01% | 0.01% | 0.008% | 0.005% <10V |
| Display | LED | LED | Nixie | Binary |
| Cost | \$1,595 | \$1,095 | \$2,140 | \$1,925 |

Call Dick Dale for complete specifications (513) 254-6259

Model 3110 (Front Panel Control) **\$1095.**

Model 3210 (Remote Keyboard) . . **\$1795.**

Model 3220 (Remote Programmable) **\$1595.**



Model 3110, front panel controls for general use.



Model 3210/3220, fully programmable by keyboard or system input.




UNITED SYSTEMS CORPORATION

918 Woodley Road • Dayton, Ohio 45403 • Ph: (513) 254-6251 • TWX: (810) 459-1728

These instruments available under GSA contract GS-OOS-27741.

SOMETHING NEW for the
Efficient World of High Frequency Power Switching!

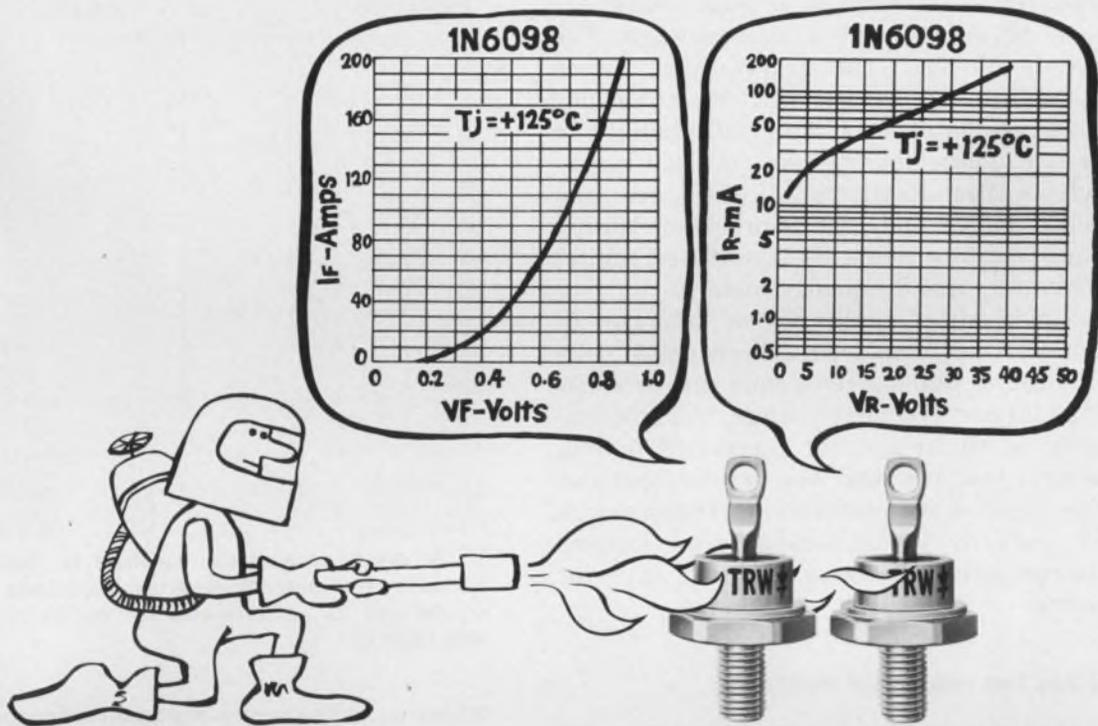OK, you Power Schottkys, the heat's on. Talk!



These new TRW Power Schottkys have quite a story to tell and it starts with the fact that they're JEDEC registered. Then they'll tell you that they let you maintain 50 Amps—typically 0.55 Volt forward drop at a T_j of 125°C . The highest operating junction temperatures, lowest reverse leakage typically less than 200mA @ 40V, 125°C , and highest voltages on the market today. (Yet, for all that, they're competitively priced.)

Yes, TRW's Schottky Diodes are now 1N registered. And they're about to be JAN and JANTX qualified.

Let these new Power Schottkys take your heat, try one in your present circuit or in the circuit you're working on, you'll find out they're not just talk.

| | | | |
|--------|--------|-----|------|
| 1N6095 | 25 AMP | 30V | DO-4 |
| 1N6096 | 25 AMP | 40V | DO-4 |
| 1N6097 | 50 AMP | 30V | DO-5 |
| 1N6098 | 50 AMP | 40V | DO-5 |

If you'd like to hear more about how TRW's Power Schottkys can help you in the design of low-voltage, high-current power supplies, call John Power at (213) 679-4561. Or use the coupon. (These components are available from stock from our distributors.)

TRW Power Semiconductors

An Electronic Components Division of TRW, Inc.,
14520 Aviation Boulevard, Lawndale, California 90260

- Please send me data sheets on TRW's Power Schottky Diodes
- Have a salesman get in touch with me

Name _____

Company Name _____

Position _____

Address _____

City _____

State _____

Zip _____

TRW POWER SEMICONDUCTORS

Need an adjustable crystal oscillator?

With properly proportioned circuit capacitances, a crystal oscillator can be "pulled" over a usefully wide range.

The frequency stability of crystal oscillators is both an advantage and a disadvantage. The advantage is obvious; the disadvantage arises when you wish to deliberately shift the frequency of a crystal oscillator to make small changes in its frequency. These changes are required in circuits such as frequency-modulation systems and phase-locked loops, and where precision timing adjustments must be made, as in watches, digital interval counters and frequency meters.

Various methods of "pulling" the frequency of crystals have been employed. Those using coils or active circuits that emulate coils can be shifted over the largest frequency range, but frequency stability is relatively poor. Inductive pulling elements are unstable, and the crystal operates where the slope of its reactance vs frequency is relatively shallow. Variable-capacitance loading of quartz resonators, however, provides superior performance.

A crystal has two resonance modes

The equivalent circuit of a capacitance-loaded lossless quartz crystal is shown in Fig. 1. The crystal's mechanical inertia is represented by L_1 and its mechanical compliance by C_1 . The electrical capacitance of the crystal and its holder is represented by C_0 and the capacitance of the oscillator's input circuit by C_v .

A crystal can resonate in two modes: a series, and a parallel, or antiresonant, mode. The parallel-mode resonance frequency is slightly higher than the series mode; thus in the parallel mode, the mechanical element of the crystal behaves effectively as an inductive reactance that resonates with the capacitive reactance of C_0 and C_v in parallel.


The reactance of the mechanical element is

$$X_m = \omega L_1 - \frac{1}{\omega C_1} \quad (1)$$

Since

$$C_1 = \frac{1}{\omega_0^2 L_1} \quad (2)$$

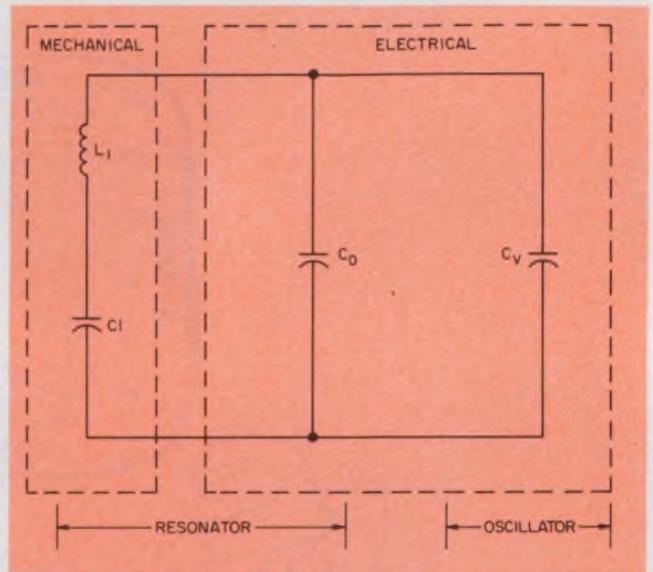Frank W. Noble, Electronics Engineer, Laboratory of Technical Development, National Heart and Lung Institute, Dept. of HEW, Bethesda, MD 20014.



1. A crystal-resonator's mechanical parameters are loaded by the inherent electrical capacitance of C_0 —the crystal and its holder—and the oscillator's input variable capacitor, C_v .

where ω_0 is the series-resonance frequency of the crystal, substituting Eq. 2 into Eq. 1 yields

$$X_m = L_1 \frac{[\omega^2 - \omega_0^2]}{\omega} \quad (3)$$

$$\text{If we let } \omega = \omega_0 + \Delta\omega, \quad (4)$$

$$\text{so that } \omega^2 \approx \omega_0^2 + 2\omega_0 (\Delta\omega), \quad (5)$$

and substitute Eq. 5 into Eq. 3, then

$$X_m \approx 2 L_1 (\Delta\omega), \quad (6)$$

because $\omega \approx \omega_0$.

At parallel resonance, the reactance of the mechanical branch, X_m , equals the reactance of C_0 and C_v in parallel. Thus from Eq. 6,


$$(\Delta\omega) = \frac{1}{2 \omega_0 L_1 (C_0 + C_v)} \quad (7)$$

Substitute Eq. 2 into Eq. 7 and rearrange to get


$$\frac{(\Delta\omega)}{\omega_0} = \frac{(\Delta f)}{f_0} = \frac{\frac{C_1}{C_0}}{2 \left[1 + \frac{C_v}{C_0} \right]} \quad (8)$$

An electromechanical coupling factor, r_o , determined by the crystal cut and method of mounting can be defined as

$$r_o = \frac{C_0}{C_1} \quad (9)$$

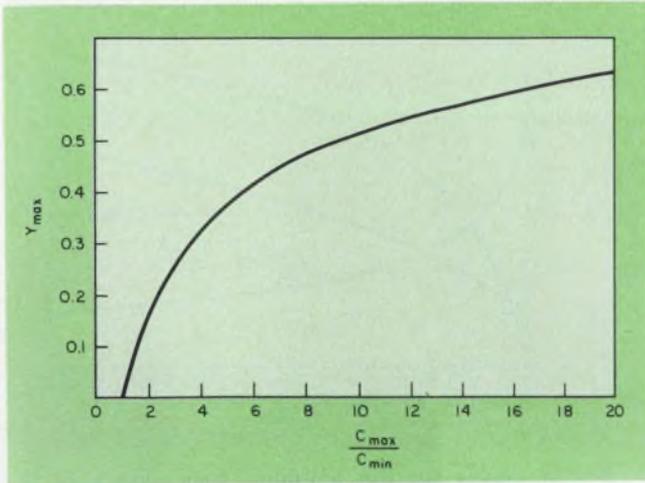

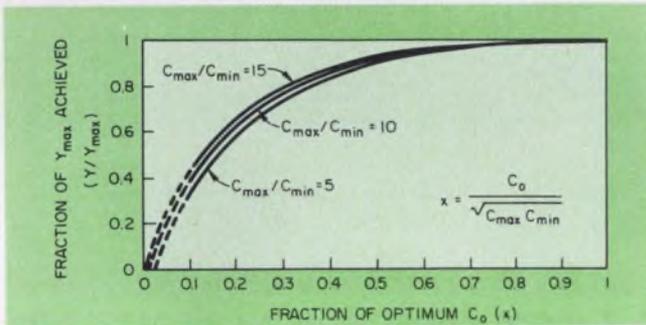2. The maximum possible value of the frequency deviation factor, y , is a function of the ratio C_{\max}/C_{\min} of capacitor C_v and is obtained when $C_o = \sqrt{C_{\max} C_{\min}}$.



3. The fraction of y_{\max} that is attainable when the crystal capacitance, C_o , is not the optimum value is not strongly affected by the C_{\max}/C_{\min} ratio, as shown by varying the ratio over a range of 3:1.

Eq. 8, expressed in kHz/MHz for convenience, can now be written as

$$\frac{(\Delta f)}{f_o} = \frac{500}{r_o \left[1 + \frac{C_v}{C_o} \right]} \text{ kHz/MHz,} \quad (10)$$

or

$$(\Delta f)_{\max} = \frac{500 f_o}{r_o \left[1 + \frac{C_{\min}}{C_o} \right]} \quad (11)$$

and

$$(\Delta f)_{\min} = \frac{500 f_o}{r_o \left[1 + \frac{C_{\max}}{C_o} \right]} \quad (12)$$

Let's define the pulling range, B , as

$$B \equiv (\Delta f)_{\max} - (\Delta f)_{\min}, \quad (13)$$

then

$$\frac{B}{f_o} = \frac{500}{r_o} \left[\frac{1}{1 + \frac{C_{\min}}{C_o}} - \frac{1}{1 + \frac{C_{\max}}{C_o}} \right]. \quad (14)$$

Maximizing the pulling range

To maximize the pulling range, we let the function within the brackets of Eq. 14 equal y and

then differentiate to get

$$\frac{\partial y}{\partial C_o} = \frac{C_{\min}}{[C_o + C_{\min}]^2} - \frac{C_{\max}}{[C_o + C_{\max}]^2}. \quad (15)$$

Setting Eq. 15 to zero and solving, yields the conditions for the maximum pulling range,

$$C_o = \sqrt{C_{\max} C_{\min}}, \quad (16)$$

when C_o is the geometric mean of the C_v extremes. Then

$$y_{\max} = \left[\frac{1}{1 + \sqrt{\frac{C_{\min}}{C_{\max}}}} - \frac{1}{1 + \sqrt{\frac{C_{\max}}{C_{\min}}}} \right]. \quad (17)$$

A plot of Eq. 17 is shown in Fig. 2. However, practical circuits generally yield a smaller pulling range than allowed by Eq. 17, because the C_o for standard crystals is usually too small to satisfy Eq. 16, even when care is taken in the oscillator design.

Calculations show that the value of C_{\max}/C_{\min} does not strongly affect the percentage of y_{\max} that is achievable as C_o is varied below its optimum value as given by Eq. 16.

A practical example

To gain a quantitative "feel" of magnitudes we are dealing with, let

$$C_{\max} = z C_{\min}; \quad (18)$$

thus the optimum value of C_o from Eq. 16 becomes

$$C_o = C_{\min} \sqrt{z} \quad (19)$$

and $C_o = C_{\max} / \sqrt{z}$ (20)

Fig. 4 contains a replot of Fig. 2 along with C_{\min}/C_o and C_{\max}/C_o .

Now we can solve a practical problem: How to achieve 5-kHz deviation from an AT-cut 7-MHz crystal that has $r_o = 250$, $C_o = 5$ pF and $C_{\min} = 7$ pF.

First assume that $C_o = \sqrt{C_{\max} C_{\min}}$ can be achieved. Then from Eqs. 14 and 17,

$$\frac{B}{f_o} = 2y_{\max} = \frac{5}{7} \quad (21)$$

and

$$y_{\max} = 0.357$$

From Fig. 4, scale C we get,

$$\frac{C_{\max}}{C_{\min}} = 4.45;$$

from scale A,

$$\frac{C_{\min}}{C_o} = 0.475, \text{ or } C_{\min} = 2.37 \text{ pF};$$

and from scale B,

$$\frac{C_{\max}}{C_o} = 2.12, \text{ or } C_{\max} = 10.6 \text{ pF.}$$

An oscillator with a C_{\min} as small as 2.37 pF is difficult to achieve; practically, C_{\min} tends to be about 7 pF, even with very careful design. Of course, the optimum condition, $C_o = \sqrt{C_{\max} C_{\min}}$, is therefore not achieved.

Nevertheless, with a C_{\max}/C_{\min} larger than the

Now you can "see" inside your 8080 with the Ramtek MM 80



Develop and debug 8080/8080A hardware and software —

using the real engineering prototype.

Fast and convenient software —

with ROM resident assembler and editor.

Service and debug 8080 systems in the field —

with a sixteen pound package.

Easy program modification during development —

with the PROM programmer.

Get "inside" your 8080 breadboards and know where you are every step of the way —

without building special front panels.

RAMTEK's new MM80 in circuit Emulator plugs directly into a 8080 microprocessor socket with its own 8080, giving you complete system access through a full complement of console commands, front panel controls, displays and probe points. With the MM80, you actually "see" what's going on inside the system.

The programmer can step, trace and breakpoint the software in the real system, and display and alter the 8080 registers, memory and I/O ports even if the user programs are all in ROM.

The MM80 provides a complete control and test center for any system under test. Five scope probe points let you trigger on MI, sync, $\phi 1$, $\phi 2$ signals and specific address references. RAM diagnostic programs are provided. The LED display provides complete processor status information.


For the complete inside story on Ramtek's new MM80, call or write

RAMTEK CORPORATION
THE GRAPHIC DISPLAY COMPANY


**RAMTEK
MICRO MACHINES**
292 Commercial Street
Sunnyvale, CA 94086
Tel: (408) 735-8400
TWX: 910-339-9379

The Ramtek MM80 is available now from Texas Instruments Supply.

CIRCLE NUMBER 41

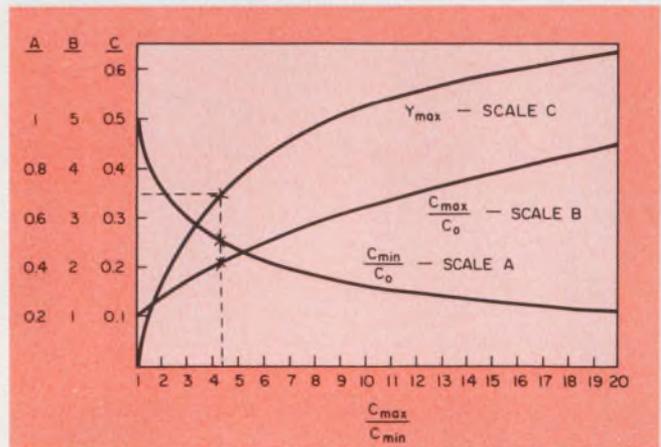

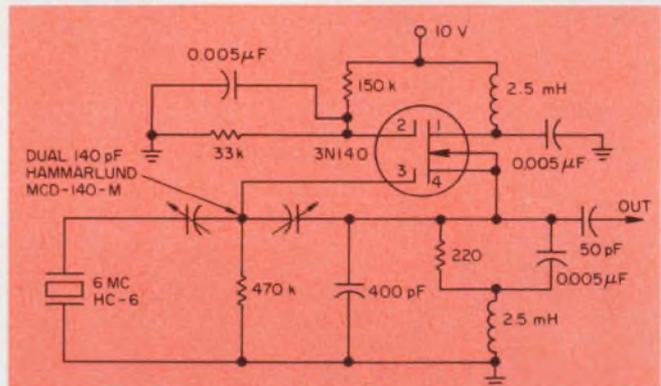4. Design curves for the optimum case, where $C_0 = \sqrt{C_{max} C_{min}}$, can be used to solve practical problems.



5. A practical oscillator circuit that can achieve 5-kHz deviation from a standard 6-MHz, AT-cut, HC-6 crystal resonator uses a dual-air-variable capacitor.

theoretical value 4.45, the deviation range can still be achieved.

Assume that a C_{max}/C_{min} of 10 can be obtained readily; thus $C_{max} = 70$ pF. Then the corresponding y_{max} from Fig. 2 is 0.520 and $B/f_0 = 1.04$, from which the deviation for the 7-MHz crystal results in 7.28 kHz.

Since we need $y = 0.357$, the value of y/y_{max} is 0.686—considerably removed from the optimum condition. With $C_{max} = 70$ pF, the optimum value of C_0 for this oscillator becomes 22.1 pF.

Generally, to achieve optimum conditions for pulling, you should use special crystals that have plated areas larger than twice the diameter for standard crystals.

A practical oscillator circuit is shown in Fig. 5. In the interests of achieving a small minimum value for C_v , the circuit uses a dual-air-variable capacitor with its sections in series.

This configuration reduces the minimum value of C_v by more than half that of a single-capacitor arrangement. Maximum capacitance is also less than half the maximum capacitance of a single capacitor, but this is not important because an adequate C_{max}/C_{min} ratio can readily be achieved with standard components. ■■

Performance and Value through advanced engineering

Model 134

3½ Digit DMM \$189.00

Competitively priced with the best analog meters, the Model 134 provides digital accuracy and an easy-to-read ½ inch digital display. The Model 134 is an ideal, low cost lab or production test instrument.

The Model 134 measures DC volts, AC volts, DC current, AC current and resistance with a basic accuracy of $\pm 0.2\%$ through a total of 22 range scales.

It features auto-decimal positioning, auto-polarity, 100% overranging, high voltage protection circuit, probes and a one year warranty.

The Model 134 is the logical alternative to analog instrumentation at a competitive price.



Model 245

Portable, 4½ Digit DMM \$295.00

Ideal for field use, the Model 245 is a rugged, truly miniature, lab-quality, 5-function instrument featuring a basic DC accuracy of $\pm 0.05\%$, .005% resolution, 100% overranging, equipped with both rechargeable battery pack and battery recharger/line adapter.

Model 245 measures ACV (100 μ V to 500V RMS), DCV (100 μ V to 1000V), Resistance (100 milliohms to 20 Megohms), AC and DC current (1 microamp to 2 Amps). AC voltage/current response, 30 Hz to 50 kHz.

With over 25,000 in the field the Model 245 is still the only pocket-size portable 4½ digit DMM available.



Model 1455

Bench/Portable 4½ Digit DMM \$355.00

Model 1455 — all the virtues of a laboratory bench instrument with the added benefits of complete portability.

A five function multimeter featuring ½" high display, 100% overranging, measures 100 μ V to 1000 VDC, 100 μ V to 500 VAC; resistance 100 milliohms to 20 Megohms; AC and DC current 1 microamp to 2 amps. AC response, 30 Hz to 50 kHz.

Basic accuracy on DCV is $\pm 0.02\%$ reading $\pm 0.01\%$ f.s., ± 1 digit for 6 months. Internal NiCd battery module and recharger.

Model 1450 4½ Digit DMM \$325.00

The same specifications and features as the Model 1455, line operation only.



Model 3400

System/Lab 4½ Digit DMM \$795.00

Model 3400 is the world's most accurate systems/lab 4½-digit multimeter. It is a fully programmable system multimeter and a highly versatile stand-alone, auto-ranging laboratory multimeter. Remote triggering will allow 12 conversions per second.

Full 100% overranging (20,000 counts), basic DCV accuracy of $\pm 0.007\%$ of reading ± 1 L.S.D. for six months, measures from 10 microvolts to 1,000 VDC (ACV from 10 microvolts to 750V RMS), resistance from 10 milliohms to 20 Megohms; AC/DC and DC/DC voltage ratio.



Model 3500

5½ Digit DMM \$995.00

The Model 3500 delivers more features for less money than any other 5½ digit DMM available. It is a full function, autoranging DMM with 6 months basic accuracy of $\pm 0.007\%$ of rdg. $\pm 0.001\%$ f.s. ± 1 L.S.D. Remote ranging and trigger, 20% overrange and ½ inch planar displays.

• DCV 1 μ V to 1000 volts • ACV 1 μ V to 700 volts RMS. 30 Hz to 100 kHz
• Resistance 1 milliohm to 12 Megohms
• 1000 M Ω Input Impedance through 10 VDC • RatiohmTM. Resistance Method 2 and 4 wire. BCD output and voltage ratio are included at no extra cost.



Model 5740

Multifunction Counter \$295.00

Model 5740 measures Frequency, Period, Period Average, Total Events and Elapsed Time.

SPECIFICATIONS: Sinewaves, Square Waves, Pulses, Pulse Pairs, Complex Waves • Frequency: 5 Hz to 100 MHz; 10 ms/100 ms/1 sec./10 sec. gate times, resolution to 0.1 Hz • Period: ½ microsecond to 0.2 sec. • Period Average: 10, 100 and 1000 periods • Total Events: 0 to 9,999,999 (unlimited with "overflow" indicator) • Elapsed Time: 0 to 99,999.99 sec. (27.8 hrs) • Sensitivity to 10mV



For complete information on these and other Data Precision instruments or a demonstration, contact your local Data Precision representative or Data Precision Corporation, Audubon Road, Wakefield, MA. 01880 (617) 246-1600. TELEX (0650) 949341.

DATA PRECISION®
...years ahead

A versatile CMOS circuit changes mode when bias and load are changed

The CMOS circuit of Fig. 1 can perform many electronic functions, depending only on the circuit's applied bias and load. The circuit can be used as an amplifier inverter, amplifier follower, frequency doubler, oscillator, or a multivibrator. Though over 20 such versatile circuits have been developed, the circuit in Fig. 1 is particularly practical, simple and easy to apply. The circuit can also be designed in IC form.

The circuit's functional versatility is made possible by its special I-V characteristics, with analytic properties that satisfy conditions for several electronic functions on the same portion of the I-V plane.


For example, in the I-V plot of Fig. 2, the point $I = 3 \text{ mA}$, $V = 11.2 \text{ V}$ can be obtained when the bias, e , is either 3 or 1 V. At this point, the transconductance, $\partial I / \partial e$, is positive or negative, depending on whether e is 3 or 1 V, respectively. For $\partial I / \partial e > 0$, the circuit can work as an amplifier follower, and for $\partial I / \partial e < 0$, as an inverter.

The circuit is a three-terminal combination of two n-channel and two p-channel MOSTs. The particular choices of depletion-type n-channel


devices, FT 57 and 2N3796, and the 9-V threshold battery for the p-channel FT702 unit determine the curvature of the characteristic curves and the location of the zero-bias curve on the I-V plane (Fig. 2). Further modification of the curves can be obtained by the insertion of another battery in series with the gate of the other FT702.

The circuit operates as a follower amplifier when it is biased at $e = 3 \text{ V}$, $E_R = 15 \text{ V}$ and load resistor, R_L , equals $1.2 \text{ k}\Omega$. With the same R_L and E_R , but with $e = 1 \text{ V}$, the circuit operates as an amplifier inverter. With the load line, where $R_L = 76.2 \Omega$, $E_R = 10.4 \text{ V}$ and $e = 2 \text{ V}$, the circuit is a frequency doubler. But with the same load line and $e = 1 \text{ V}$, the circuit is again an inverter, and with $e = 3 \text{ V}$, a follower.

With load line C, $R_L = 567 \Omega$, $E_R = 5.5 \text{ V}$, and with an appropriate inductor in series with R_L , the circuit behaves as an astable multivibrator when $e = 0$. With an LC circuit connected, the circuit works as a quasi sine-wave oscillator. And when $e = 2, 3$ or -4 V , the circuit works as a monostable multivibrator. The circuit's signal input terminals can be used for trigger pulses.

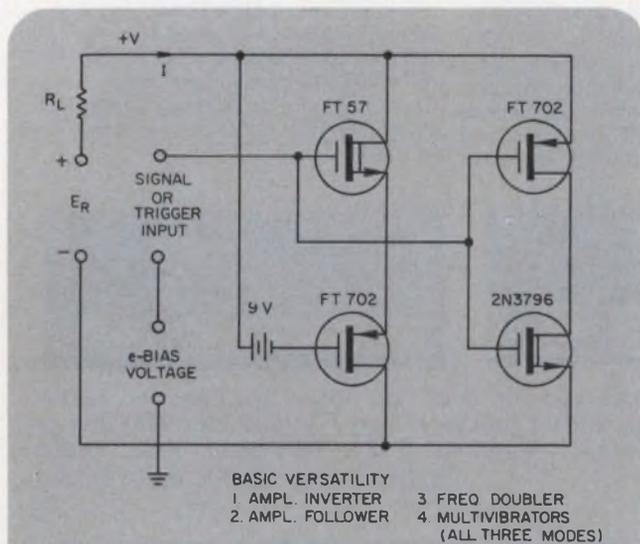

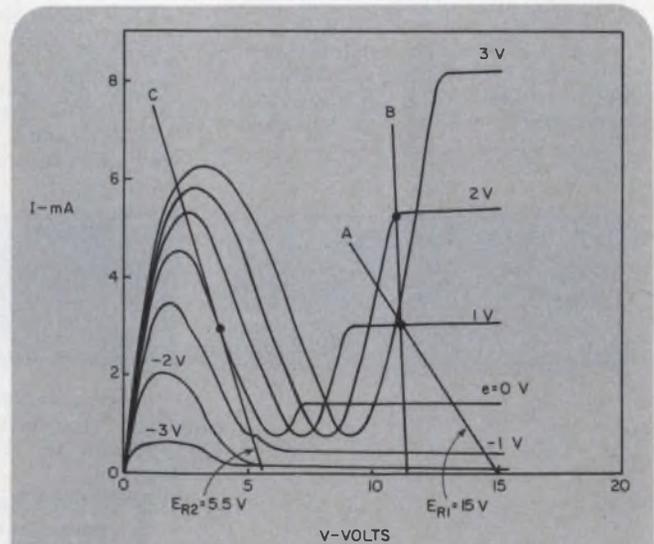1. A circuit made with four CMOS devices becomes a versatile circuit whose properties depend only on the load and bias values.



2. The characteristic curves of the CMOS circuit provide properties for amplification, inversion and multivibrator operation, all on a single I-V plane.

Triplet 310 mini-VOM's fit your hand and your wallet...



only \$51



The high quality Triplet 310 is a little all-in-one VOM. This made in the U.S.A. VOM gets around a lot for half fare. It packs most of the features you'd expect to find only on a meter twice the size and price. It fits in your shirtpocket easily. The small size and its versatility is a boon to field servicemen as well as circuit designers, technicians, electrical maintenance engineers, and the price is right for vocational and hobbyist use.

A newly designed high impact, drop resistant case makes it practically indestructible . . . 20K ohms/volt DC and 5K ohms/volt AC ranges provide plenty of sensitivity for most applications . . . and, there's diode overload protection with a fused R X 1 ohm range. The single range selector switch is a real time saver for reading 0 - 1200 DC or AC volts, 0 - 20 megohms, and 0 - 600 micro-amps or 0 - 600 milliamps at 250 millivolts.

Comes complete with 42" leads, alligator clips, batteries and instruction manual. Accessories triple the versatility of a 310. Adding the Model 10 clamp-on ammeter allows you to measure AC currents easily with one hand.

Visit your local distributor or Mod Center and shake hands with a real bargain.



TRIPLETT
BLUFFTON, OHIO 45817

Triplet. The easy readers

IDEAS FOR DESIGN


It is perhaps easier to follow the circuit's various functions with Fig. 3. This transfer characteristic curve shows the circuit's versatility comprehensively. With $R_L = 5\text{ k}\Omega$, biasing in the AB region makes the circuit an amplifier inverter, and biasing in the BC region makes it a follower. Note that as a follower, the circuit has gain, $\partial V/\partial e > 2$.

The complete loop, ABCDE, traces the circuit's behavior in oscillator and multivibrator applications. Biasing at point B gives frequency doubling, but with $R_L = 5\text{ k}\Omega$, the ABC part of the curve is not symmetrical and would provide a distorted output. To optimize frequency-doubling action, the curve can be made more symmetrical by changes in R_L and the threshold voltage.

Reference

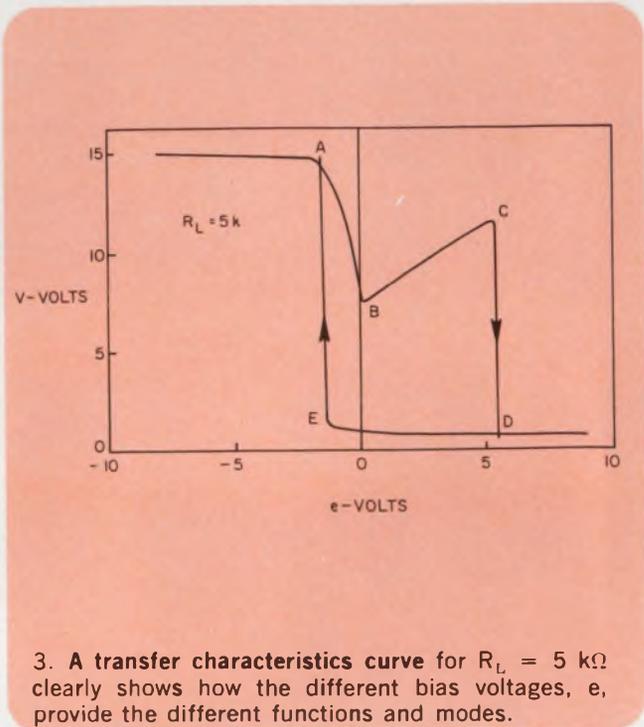1. Lubelfeld, J., "Versatile CMOS Circuits," Air Force Institute of Technology, WPFAB, OH 45433, internal report.

J. Lubelfeld, Dept. of Electrical Engineering, Air Force Institute of Technology, Wright-Patterson AF Base, OH 45433. CIRCLE NO. 311



3. A transfer characteristics curve for $R_L = 5\text{ k}\Omega$ clearly shows how the different bias voltages, e , provide the different functions and modes.


Digital frequency doubler works to 100 kHz

A digital frequency doubler that works from 1 Hz to 100 kHz can be built with only one hex-inverter chip, two diodes and a capacitor (Fig. 1). The circuit requires a square-wave input. To produce an approximately symmetrical output, the capacitor, C, should have a reactance of $1000\ \Omega$ at the input frequency. If symmetry is important, the capacitor may be padded with a series or parallel resistor to provide almost perfect symmetry at the frequency used.

The output circuit includes inverters G_3 , G_4 , G_5 and G_6 that are cross-coupled by diodes D_1 and D_2 . The input signal is split into two components that are phase-shifted 90-degrees from each other with the help of inverters G_1 and G_2 and capacitor C. The two shifted signals are combined to provide a doubled-frequency output.

The circuit is very stable and several stages can be cascaded to a frequency limit of about 100 kHz.

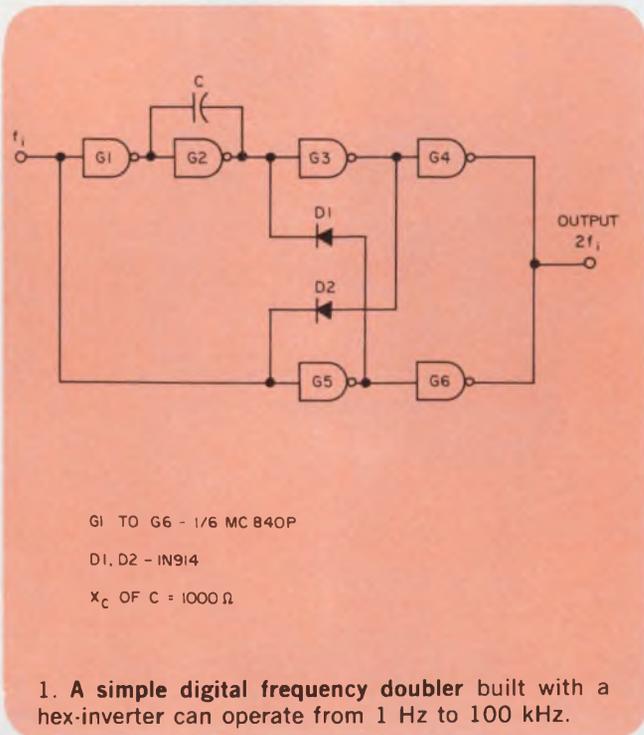Gerald L. Vano, Systems Engineer, Alden Research Foundation, 117 N. Main St., Brockton, MA 02403. CIRCLE NO. 312



G1 TO G6 - 1/6 MC 840P

D1, D2 - 1N914

X_C OF C = $1000\ \Omega$

1. A simple digital frequency doubler built with a hex-inverter can operate from 1 Hz to 100 kHz.

THE HIGH VOLTAGE SUPER GROUP.



| Type | Resistance Range | Power Rating At 70 C | Max Operating Volts | Temp. Coef. Rating (-55 C to +125 C) | Maximum Dimensions (Inches) |
|---|---------------------|----------------------|---------------------|---|---|
| Slim-Mox  | 1 MΩ to 5000 MΩ | 5W | 18,000 V | ±250 ppm | Length 2.08 Height .84 Thickness .860 |
| Mini-Mox  | 100 kΩ to 10,000 MΩ | .25 W to 1.4 W | 1000 V to 5000 V | ±100 ppm to ±1000 ppm | Length .470 to 1.310 Dia. .140 or .165 |
| Divider-Mox  | 4.5 MΩ to 2000 MΩ | 1.5 W to 6.0 W | 7.5 kV to 30kV | ±100 ppm to ±1000 ppm overall TCR Tracking ±25 ppm | Length 2.2 to 5.2 Dia. .345 |
| Maxi-Mox  | 10 kΩ to 5000 MΩ | 1.5 W to 12.5 W | 7.5 kV to 37.5 kV | ±100 ppm to ±500 ppm | Length 1.122 to 5.2 Dia. .310 or .345 |
| Power-Mox  | 20 kΩ to 7000 MΩ | 22.5 W to 45 W | 20 kV to 45 kV | ±100 ppm to ±300 ppm | Length 3.96 to 6.96 Dia. .89 |

MOX resistors from Victoreen. The high voltage experts.

What's your problem? Space? Economy? Stability? Better tolerance? Here's one solution to all of the above. The Victoreen MOX high voltage resistor line.

From Mini-MOX to Power-MOX, you'll find that the people at Victoreen know how to make you happy. We know how to give you resistor performance that allows more design flexibility. And product reliability.

MOX resistors are the high voltage designer's solution to problems caused by other resistors.

The tougher your high voltage resistor requirements, the more you need our advanced, reliable MOX magic.

Send for complete technical data. Write: Victoreen Instrument Division



10101
Woodland
Avenue,
Cleveland,
Ohio 44104

 SELLER-GLOBE CORPORATION

CIRCLE NUMBER 44

High-frequency zero-crossing detector operates beyond 50 MHz

The three sections of an MC10116 ECL receiver when connected in tandem make a sensitive zero-crossing voltage detector that is capable of operation beyond 50 MHz (Fig. 1). Input voltages of this detector may range from 30 mV to 5 V, peak to peak. The zero-cross point does not change by more than 2 ns over this large input range.


The MC10116 chip contains three differential amplifiers, each with a gain of approximately eight; thus the over-all gain of all three stages in tandem is 512. Input biasing is derived from the negative 1.3-V reference-voltage delivered at pin 11 of the chip. This voltage centers the dc of the input amplifier for class-A amplification and maximizes its common-mode-rejection capability.

For input signals less than 100 mV the first

amplifier stage operates in a class-A mode. Larger signals force all stages into a fully switched mode. Propagation time through one stage is about 2 ns in the switched mode, and less in class A. Since only the first stage ever operates in class A, the propagation time difference between the smallest signal, 30 mV, and the largest signal, 5 V, will vary only by the difference between the class-A and switched-mode delays—much less than 2 ns.

The value of input resistors R_1 and R_2 can be chosen to match the line impedance. And the values of the coupling capacitors, C , should be selected in conjunction with R_1 and R_2 to provide the required low-frequency response.

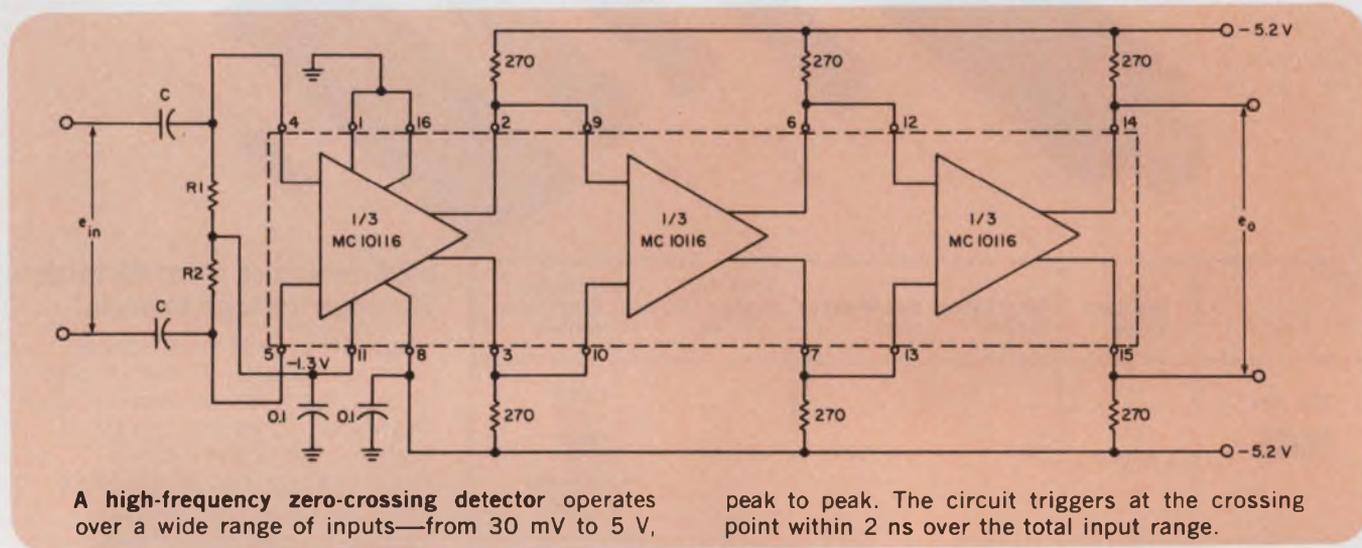William A. Palm, Principal Engineer, Magnetic Peripherals Inc., 7801 Computer Ave., Minneapolis, MN 55435. CIRCLE NO. 313



IFD Winner of November 22, 1975

Douglas Thom, Development Engineer, Novus Div., National Semiconductor Corp., 1177 Kern Ave., Sunnyvale, CA 94086. His idea, "Capacitor Drops Voltage with Little Heat for Low-Cost, Low-Voltage Power Supply" has been voted the Most Valuable of Issue Award.


Vote for the Best idea in this issue by circling the number of your selection on the Information Retrieval Card at the back of this issue.

SEND US YOUR IDEAS FOR DESIGN. You may win a grand total of \$1050 (cash)! Here's how. Submit your IFD describing a new or important circuit or design technique, the clever use of a new component or test equipment, packaging tips, cost-saving ideas to our Ideas for Design editor. Ideas can only be considered for publication if they are submitted exclusively to ELECTRONIC DESIGN. You will receive \$20 for each published idea, \$30 more if it is voted best of issue by our readers. The best-of-issue winners become eligible for the Idea of the Year award of \$1000.

ELECTRONIC DESIGN cannot assume responsibility for circuits shown nor represent freedom from patent infringement.

CANNON® COST CUTTERS:

THE CIRCULAR CONNECTOR

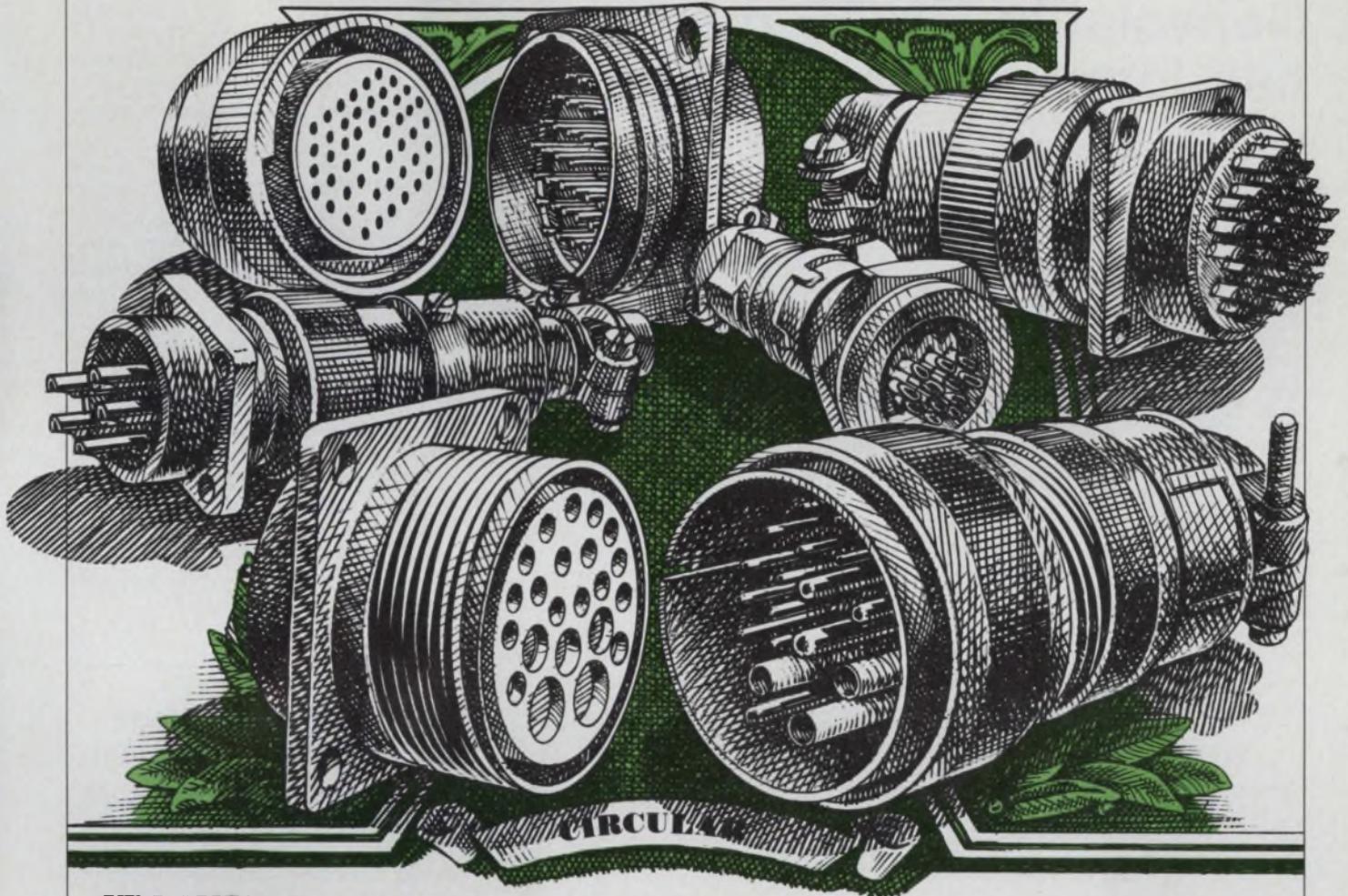

IT LOWERS YOUR TOTAL INSTALLED COST.

What are you looking for today in circular connectors?

Fast delivery, for one thing, so you don't have to carry a lot of inventory. High quality, for another, so you can cut down on rejects and returns. And the exact right connector, too, so you can design more efficiently.

Delivery, quality, selection... they're all part of your total installed cost — your *real* cost. Cannon can lower it.

Why? Because we offer you the largest network of stocking/assembly distributors. The broadest line anywhere. The product with the best reputation for quality in the industry.

After almost sixty years of experience we can proudly say, few products are made as well as Cannon makes circular connectors.

K Series Quick Connect/Disconnect Connector Acme thread • 1-75 contacts • 0-20 wire sizes • Coaxial contacts available.

KO Series Miniature Version of K Series Meets environmental requirements of MIL-C-25955 • Solder contacts • Diecast aluminum shells.

KPT/KPSE (Environment-Resistant) Qualified to MIL-C-26482 • Solder contacts (KPT), crimp contacts (KPSE) • Bayonet coupling.

MC Series Environmental Sub-miniature Connectors Solder contacts • Diecast aluminum shells •

Polychloroprene insulators.

MS Series Connectors to MIL-C-5015 1-100 contacts • Solder termination • Threaded coupling

Applications: Rapid transit • Traffic control • Machine tools • Medical electronics • Recreational vehicles • Business aircraft • Mining machinery and instrumentation.

Today, send for "Cannon Cost Cutters" brochure. Contact ITT Cannon Electric, 666 East Dyer Rd., Santa Ana, California 92702. (714) 557-4700.

**CANNON
ENGINEERING
LOWERS YOUR COSTS.**

CANNON ITT

Nonvolatile MNOS memory has longer operating life

A nonvolatile semiconductor memory that overcomes the short life of the conventional MNOS (metal-nitride-oxide semiconductor) transistor has been revealed by the Tokyo Shibaura Electric Co. in Japan. Because the characteristics of the MNOS transistor deteriorate after each write operation, the lifetime is usually well below 10^6 cycles.

Standard MOS memory cells are combined in the Toshiba memory with MNOS transistors, and in normal operation the MNOS transistors are not used. Data are written into the MNOS transistors only when nonvolatility is essential, such as to protect against data loss in the event of a power failure. Because the MNOS transistors

undergo a minimum number of write cycles their lifetime is increased.

The major drawbacks at present are that ten transistors are required for each memory bit and costs are likely to be higher than if a CMOS RAM with back-up power supply were used. Current work is aimed at improving yield and increasing the level of integration.

A 64×4 -bit array is feasible now but Toshiba hopes to achieve a 1 k-capacity in the next year. The 64×4 RAM can retain data without power for at least one year, has a read access time of less than 500 ns, a write-cycle time of less than $1 \mu\text{s}$ and a power consumption of 600 mW.

Green LED process boosts light output

A new process for producing green light-emitting diodes with luminous intensities of 30 millicandelas at an operating current of 10 mA has been developed by Siemens AG, Erlangen, West Germany. The diodes can operate with up to 60 mA, and at the higher currents the light output is sufficient to illuminate the surroundings.

The first stage in the production of the devices is the direct synthesis of polycrystalline gallium phosphide from pure gallium and phosphorous. This is then converted to monocrystalline GaP on which an n-type GaP layer is grown, at 900 to 1100 C, by means of fusion epitaxy. Further doping with zinc produces the pn junction, which is required for light emission.

640 characters displayed on 40×50 -cm LCD

A large-area liquid-crystal display panel has been jointly developed by Hitachi, Dai Nippon

Tokyo and Asahi Glass. The panel, which measures 40×50 cm, can display 640 characters (Roman

letters, numerals and Japanese kana characters) and can also be used in a computer-graphics mode. The panel, still in an experimental stage, makes use of matrix addressing.

The individual characters are generated from a 9×7 dot matrix. The space between vertical lines is 9 mm, and the space between horizontal lines is 3 mm. Between characters, the space is 18 mm (vertical) \times 100 mm (horizontal).

The liquid-crystal material developed for the panel contains four ionic additives and has an operating temperature range of -10 C to 74 C, a threshold voltage of 6.9 V rms and a cut-off frequency of 3.4 kHz. Contrast ratios up to 25:1 have been obtained for the complete panel operating with a maximum rise time of 1.5 s and fall time of 0.8 s.

Helicopter rotor blade used as radar antenna

A unique radar that uses a helicopter rotor blade as the antenna has been developed by the Electronic Systems Dept. of Ferranti in Edinburgh, Scotland. The antenna is built into one blade of the rotor assembly and wholly contained within the aerofoil section.

Because of the large span of the rotor blade a very narrow beam in azimuth—about $1/2$ degree—is produced. This sharp beam, together with a 50-ns transmitted pulse and an antenna-rotation speed of 240 rpm, results in a 360-degree plan-view radar picture of high resolution.

The rotor-blade radar, called Rodar, is expected to extend the operational capabilities of helicopters. For example, the high definition of the radar will enable small objects, such as survivors at sea, to be rapidly detected in search and rescue operations.

**All the advantages of optical coupling,
plus supersensitivity with high gain, and stability.**

Coupled with a light source, Crystalonics' FOTOFETs provide:

Electrically isolated input and output circuitry, with isolation resistances as high as 10^{15} ;
Capacitances between input and output of less than 0.01 pf;
Signals transferred unilaterally, with no reflection of output signals.

As a replacement for phototransistors, photomultipliers and photodiodes, our FOTOFET is ideal for coupling applications that demand high sensitivity and stability.

The FOTOFET is many times more sensitive than conventional bipolar optical devices, with sensitivity adjustable over ranges up to 10^6 to 1. It produces gain-bandwidths 4 times higher and has a realizable power gain in a solid state device.

The FOTOFET remains stable over the operating temperature range and exhibits a stable gain that will not vary with the level of the light source.

Thus, FOTOFET gives you three marked advantages: isolation, supersensitivity and stability.

And there's a marked advantage in doing business with Crystalonics. For over a decade, we've been helping designers solve their problems. We're known for efficient communications between the designer and our applications engineers. We produce top quality, innovative devices, with you in mind.

Send for our new catalog of FOTOFETs, then order samples.
Or for immediate design assistance, give us a call.

Ask for
Richard Antalik,
our man on
FOTOFETs.




Consider the FOTOFET®

We're at your elbow to ease your design.

 **TELEDYNE
CRYSTALONICS**

147 Sherman Street, Cambridge, Mass. 02140
Tel: (617) 491-1670 • TWX: 710-320-1196

CIRCLE NUMBER 46

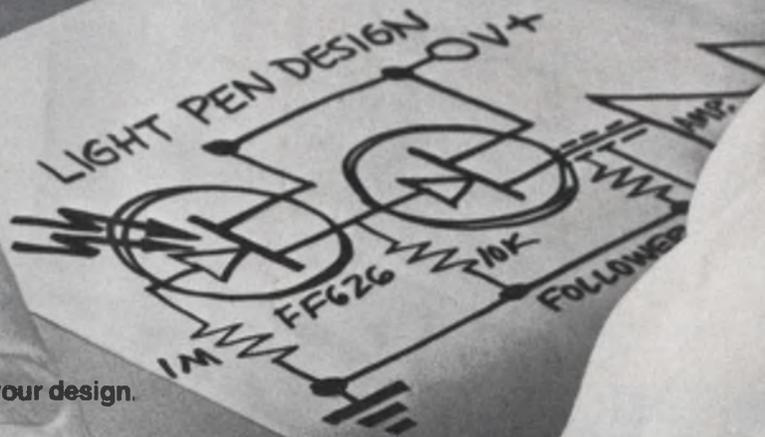

Save Space. Save Weight. Increase Reliability.


Paralleling transistors doesn't pay —not when an inherently rugged single device can do the job far more reliably, using much less space, weight, and at lower total system cost. That's why PowerTech's unique single-chip NPN silicon high-power transistor is the *one way to go*.

Used alone, our space-saving single-chip device eliminates multiple failure sources while reducing the environmental testing costs inherent in parallel arrays. Because of their simplicity they're available off-the-shelf—pre-rated, pre-tested and inventoried to meet virtually any hi-rel JAN and JAN-TX hi-current requirements without custom prices and long

custom waits. For information, application assistance, and free design guide call Sales Engineering, PowerTech, Inc., 9 Baker Court, Clifton, N.J. 07011; (201) 478-6205.


| Type # | (pk.) I_c | V_{CE0} | ($h_{fe} = 10$) $V_{CE} (sat) @ I_c$ |
|------------------|----------------|-----------|---|
| JAN-TX 2N5926 | 90A | 120V | 0.6V @ 50A |
| PT-7511 | 90A | 200V | 0.6V @ 50A |
| JAN-TX 2N5927 | 120A | 120V | 0.6V @ 70A |
| PT-6502 | 200A | 80V | 0.7V @ 100A |
| PT-9502* | 500A | 80V | 0.5V @ 300A |

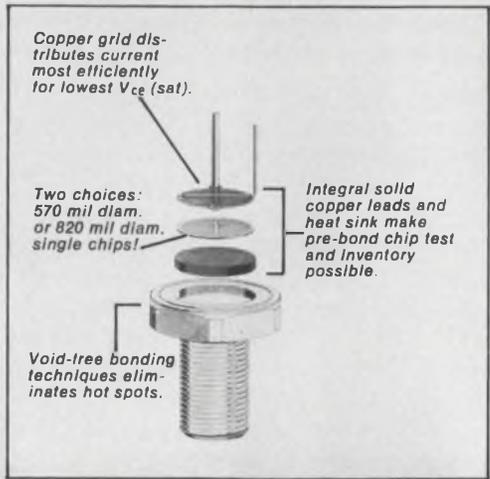350 Watt Power Rating
*625 Watt Power Rating
Guaranteed SOAR




TO UNPARALLEL IS TO SAVE:

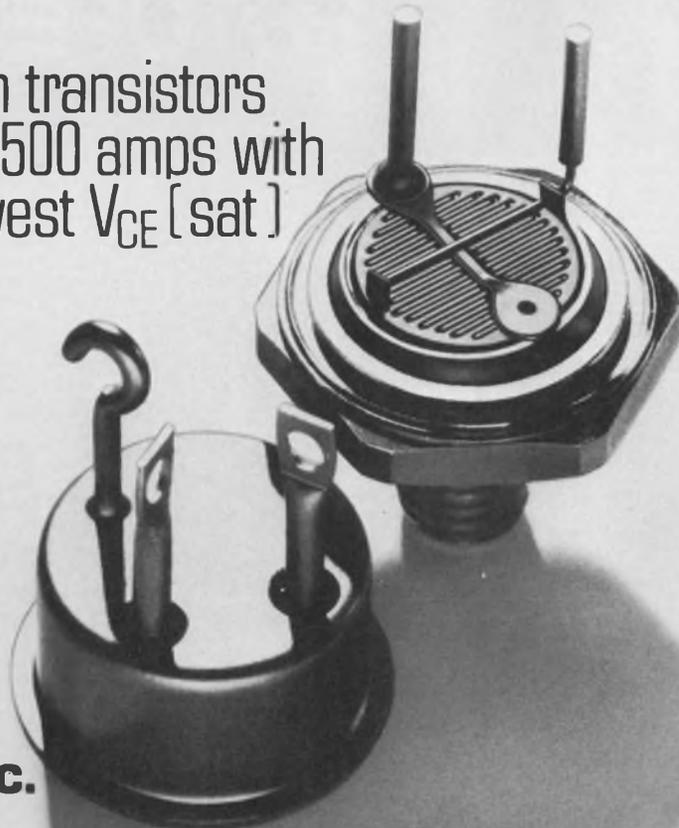Silicon transistors
to 500 amps with
lowest $V_{CE} (sat)$



PowerTech, Inc.
"BIG IDEAS IN
BIG POWER"

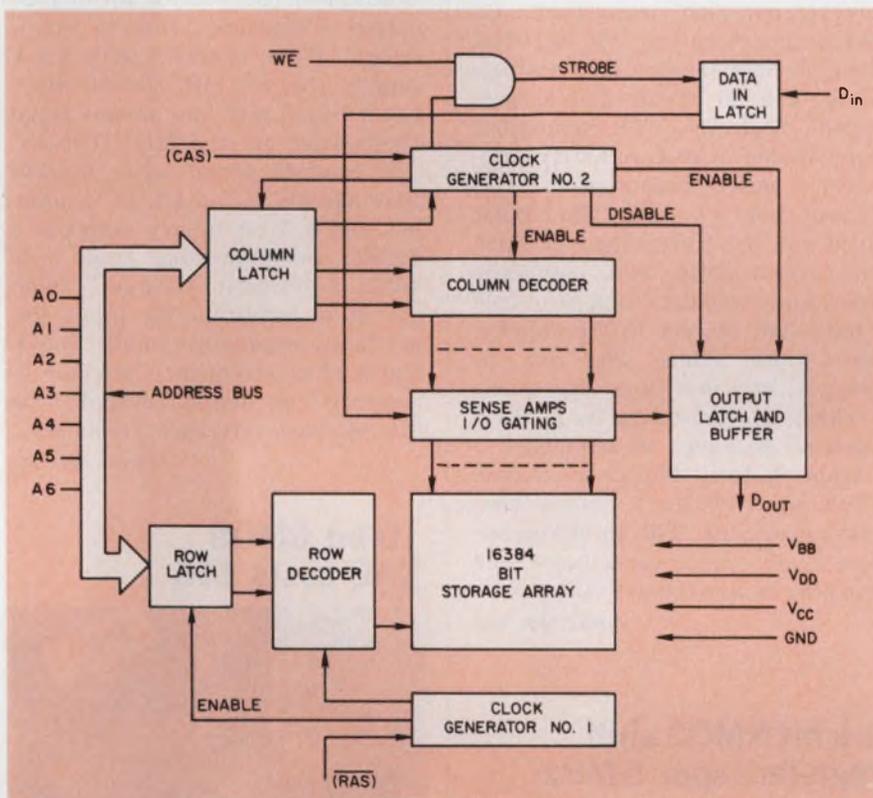16-k bit RAM has the same speed and lower dissipation/bit than 4-k versions




Intel, 3065 Bowers Ave., Santa Clara, CA 95051. (408) 246-7501. P&A: See text.

With the introduction of Intel's 16-k bit NMOS random-access memory—the highest density RAM to date—designers can achieve a 4:1 increase in memory-board density without sacrificing speed and with savings in power.

The new 2116 offers plug compatibility with 4-k dynamic RAMs like the company's 2104. Both units come in 16-pin packages and employ multiplexed addressing. And both specify best access and cycle times of 250 and 375 ns, respectively.

Further, the new semiconductor memory dissipates less than 700 mW in active operation and only 12 mW on standby. Compared with Intel's 4-k RAM, the 2116's power

2116 FUNCTIONAL LAYOUT

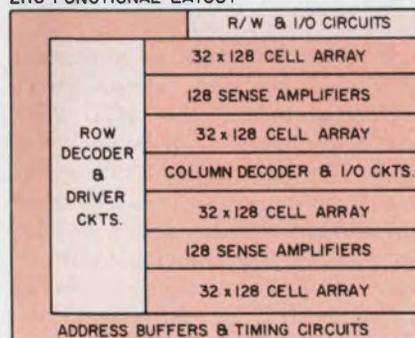

specs represent a reduction in dissipation/bit by a factor of almost four.

Other features shared by both the 16,384-bit and 4096-bit RAMs include operation from power supplies of 5, -5 and 12 V, similar supply-current requirements, and TTL inputs and outputs. Also, they

can both be refreshed in 64 address cycles, and have the same refresh interval requirement of 2 ms.

The pinouts of the two 16-pin RAMs are identical, with one exception: The A_6 address input of the 16-k RAM replaces the chip-select (CS) input of the 4-k RAM. The 2116 has seven address inputs, and the 2104 has six. Other pins are the same: column-address strobe (\overline{CAS}), row-address strobe (\overline{RAS}), write enable (\overline{WE}), three-state data output, data input and supplies.

Intel has also developed the Model 3242 address multiplexer and refresh counter for use with the 16-k RAM. It converts a 14-bit-wide address into the 7-wide multiplexed column and row addresses, and controls either 64-cycle or 128-cycle refresh. (The latter is also possible with the 2116). The 3242 comes in a 28-pin DIP.

The 16-k bit memory employs a single-transistor storage cell and uses the company's n-channel silicon-gate MOS technology. The cell design differs from the 2104 in two major respects: two layers of polysilicon are used for interconnections instead of one, and bit-cell lines are diffused, not deposited metal.

The chip-design changes halve cell area to $13 \times 35 \mu\text{m}$ and reduce cell capacitance to 0.03 pF. The resulting chip measures 145×235 mils, or about 34,000 square mils—only about twice that of some 4-k RAM chips.

Power dissipation has been kept low by several techniques. For example, half the memory is inactive during operation. Also, sense-amplifier load devices are shut off as soon as the write or restore operation is completed.

Though operating as a 16,384 \times 1-bit RAM, the 2116 is divided into

(continued on page 102)

INTEGRATED CIRCUITS

(continued from page 101)

two 8-k RAMs that share a column decoder (see functional layout). Each 8-k RAM has two 32×128 cell arrays, which in turn share 128 sense amplifiers.

In normal operation, A_6 selects one of the two 8-k RAMs, and the other 8-k RAM is kept inactive to conserve power. Address lines A_7 to A_5 and the strobe inputs select the bit in the active half. The strobe inputs drive internal TTL-to-MOS level converters and clock generators, which time internal operations. For increased operating voltage margins, address and data inputs as well as the $\overline{\text{CAS}}$ and $\overline{\text{RAS}}$ inputs, have been augmented with on-chip latches.

A special refresh mode was developed to achieve 64-cycle refresh—the usual amount for a 4-k RAM because of its 64×64 -cell array. The 2116 is typically a 128×128 array, but to require 128 refresh cycles for the 16-k RAM would reduce the availability of memory to the system.

The refresh signal is multiplexed onto the $\overline{\text{CAS}}$ input at the $\overline{\text{RAS}}$ transition. The output then goes to the high-impedance state. A_6 is ignored, and all cells on the selected word line are refreshed in both 8-k RAMs. Thus, 128×2 , or 256 bits, are refreshed simultaneously and only 64 cycles are required. For 128-cycle refreshing, read cycles can be used, or alternatively, the $\overline{\text{RAS}}$ input can be used to control row-by-row refresh.

Intel plans to produce a family of 16-k RAMs based on the 2116 design. Three versions have been specified to date: The standard 2116 has maximum access time of 350 ns and a maximum read or write cycle time of 500 ns. A dash-2 version provides the top access and cycle times (250 and 375-ns maximum). Finally, a dash-4 version offers maximum times of 300 and 425 ns. All of these times are identical to those of similarly labelled Intel 4-k RAMs.

Production quantities of the 16-k RAM are expected by the middle of the year. Initial prices are \$50 for quantities of 50 to 100. Intel says production volumes will reduce 16-k memory costs to 0.1¢/bit by the middle of 1977.

CIRCLE NO. 305

4-k RAMs have 200-ns access

Advanced Micro Devices, 901 Thompson Pl., Sunnyvale, CA 94086. (408) 732-2400. \$15.30 to \$21.60 (100); stock.

A pair of 4096-bit dynamic RAMs features access times to 200 ns and maximum power dissipation of 750 mW (at 0°C). The RAMs are available in a 22-pin package with separate data input/output circuitry—the Am 9060—or in an 18-pin version with common data input/output circuitry—the Am 9050. Both devices require only a single clock, and all inputs and outputs except clock are TTL compatible. The RAMs' input circuitry provides a purely capacitive load, so that during chip-enable transitions, memories don't experience extraneous current surges. Also, both units guarantee zero-data and read-hold times with respect to the chip-enable pulse. Thus data can be changed at same time chip enable is changed, eliminating the need for external packages to accomplish a timing delay. Moreover clocked static-input circuitry reduces timing constraints. The memories offer 20-pF clock capacitance and can sink two-to-three TTL loads.

CIRCLE NO. 306

1-k bit NMOS shift registers spec 5 MHz

Synertek, 3050 Coronado Dr., Santa Clara, CA 95051. (408) 241-4300. \$4.95 to \$11.50 (100-999).

A family of 1024-bit n-channel MOS shift registers provide direct replacements for the AMD 2833 and Signetics 2533 p-channel versions. The new SYP 2533 family uses a 5-V supply, and offers these advantages over the earlier models: no negative power supply required; 50% less power dissipation; speeds up to 5 MHz. A militarized version—SYM 2833—operates over the temperature range of -55 to 125°C, and is guaranteed to 2 MHz.

CIRCLE NO. 307

Fellow we know designed a Citizens Band radio for his Volkswagen. He wanted a phone in his bug.

CMOS synthesizer offers 1021 frequencies




Hughes Microelectronic Products, 500 Superior Ave., Newport Beach, CA 92663. (714) 548-0671. \$8.50 (1000).

A CMOS/LSI digital frequency synthesizer can provide up to 1021 output frequencies from a single crystal. When operated with a 5-V supply, the new HCTR0320 dissipates only 5 mW and accepts input frequencies up to 5 MHz. The circuit consists of an adder/decoder that accepts a 3-digit BCD number and a 7-bit binary number; a divider programmable from 3 to 1023; a "Schmitt Trigger" input circuit to condition the input signal to an acceptable counter input, and a phase/frequency detector to compare the divider output with the external reference frequency.

CIRCLE NO. 308

10-bit CMOS DAC costs \$15

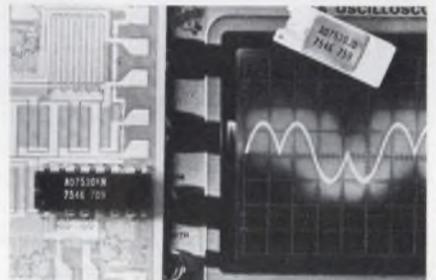


Analog Devices, Route 1 Industrial Park, P.O. Box 280, Norwood, MA 02062. (617) 329-4700.

A monolithic CMOS multiplying d/a converter features 10-bit accuracy, resolution and linearity, and it costs only \$15.00 (in hundreds). The DAC operates from a single 5-to-15-V-dc supply and dissipates only 20 mW, including the ladder network. The unit has a differential nonlinearity tempo of 2 ppm of FSR/°C maximum, gain-error tempo of 10 ppm of FSR/°C maximum and operating temperature range of 0 to 75°C. Output current settles in 500 ns to 0.05% when the DAC switches all digital inputs low to high or high to low with a 10-V reference.

CIRCLE NO. 309

The first
true universal
LED lamp.

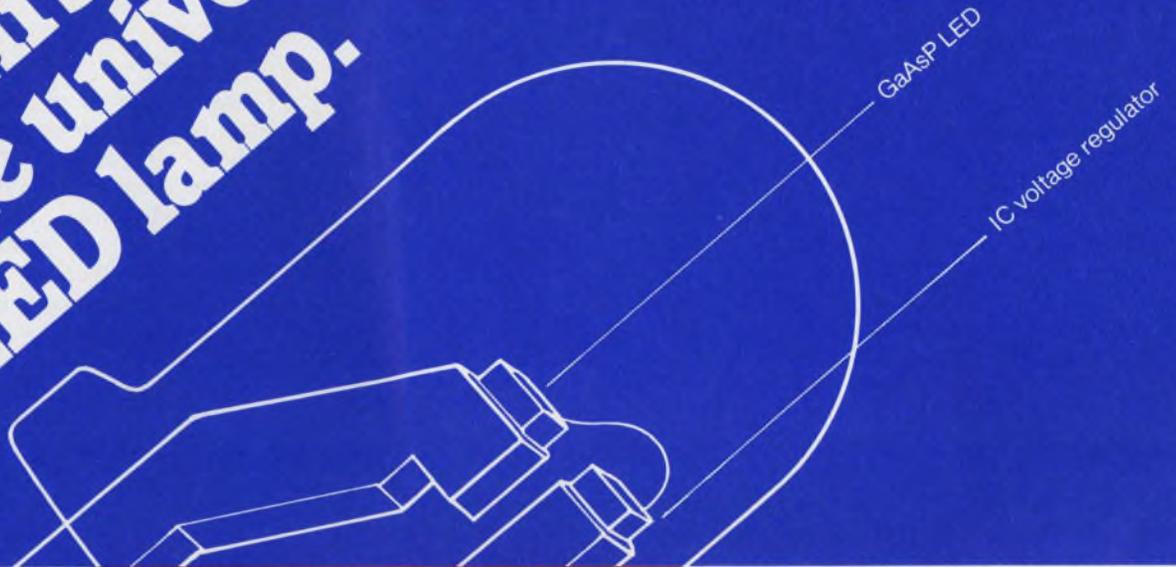

**You get constant brightness
from 4.5v to 12.5v — or even 16v.
And that's not all.**

Good-by resistors.

Good-by brightness fluctuation.

Good-by higher loading costs.

Good-by bigger inventories.

Hello universal lamp. That's what it's all about.

The Constant Brightness Lamp (CBL) is a bright new packaging idea from Litronix. The CBL has an IC voltage regulator built into the lamp so the voltage across the lamp doesn't matter so long as it is within a wide range. You can even take the lamp out of one circuit and put it into another.

The brightness never varies.

Our CBLs operate over three wide voltage ranges between 4.5 and 16 volts. And they plug into any PC board that accepts a T1 or T1 3/4 package. Even existing boards. What could be more convenient!

Price-wise, they make incredible sense. When you consider you don't have the extra costs for resistors, loading, inventory, and overhead, you can get the convenience of CBLs for about the same installed cost as ordinary lamps.

| | | | |
|---------|-------------------|----------------|----------------------------|
| RLC-200 | 20 ma @ 4.5-12.5v | T1 3/4 package | 37¢ in 1000 pc. quantities |
| RLC-201 | 10 ma @ 4.5-16v | T1 3/4 package | 37¢ in 1000 pc. quantities |
| RLC-210 | 10 ma @ 4.5-11v | T1 package | 40¢ in 1000 pc. quantities |

Get turned on. Ask for details on the new Constant Brightness Lamps from Litronix, Inc., 19000 Homestead Road, Cupertino, Calif. 95014. Phone (408) 257-7910. TWX 910-338-0022.

**No wonder
we're No.1
in LEDs**


litronix

Plastic-blade stripper handles multiwire cables

Alpha Wire Corp., 711 Lidgerwood Ave., Elizabeth, NJ 07207. (201) 925-8000. \$39.95 with three blade sets (unit qty).

A new concept in wire stripping, the Alpha plastic-blade stripper, uses blades made of a space-age plastic called Stilan. Its cutting edges are harder than wire insulation, but softer than copper. This allows the blades to strip insulation from a wire or cable without damage to the conductors and without the need for careful selection of the proper sized notch as with a conventional stripper blade.

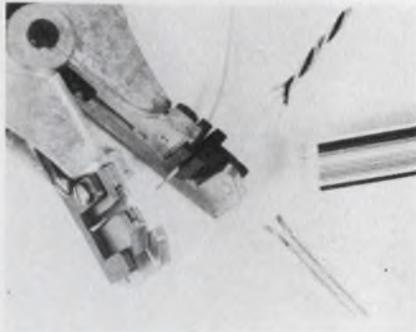The stripper can remove the insulation from multiwire cables such as twisted pairs, flat cables and twin-lead antenna wire in one action without the need to separate the individual wires, and do it as



quickly as from ordinary hook-up wire.

Alpha claims that time studies show the plastic-blade stripper can operate at least 25% faster than models using steel blades. The wires being stripped don't have to be carefully positioned between the stripper blades; a number of different wires can be stripped at the

same time; and the stripper requires no adjustment for wire size, type or number of conductors. Even poorly manufactured wire with off-center conductors is protected against nicks; the plastic blades cut through the insulation, but deform around the conductor.


The stripper can handle any size wire from AWG 12 through 28 with almost any type of insulation—PVC cross-linked polyethylene, rubber, neoprene—except Teflon and Kynar.

Stilan is a patented polymer originally developed for aerospace applications. The cutting edges last up to 50,000 strips on simple hook-up wire. Replacement injector blades slide easily into place. No tools are needed for replacement.

CIRCLE NO. 301

Q. Is there a recorder just for spectrum analyzers?

A.

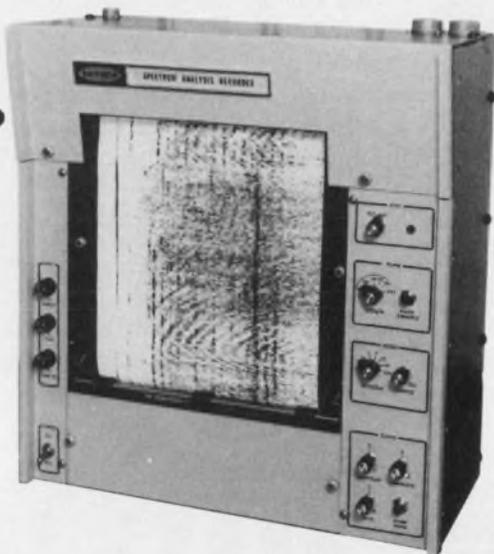

The new 19" rack-mounting SPECTRUM ANALYSIS RECORDER from Raytheon. It's the first dry paper line scanning recorder specifically developed for direct plug-in operation with commercially available spectrum analyzers.

Any new or existing spectrum analyzer equipped with the SAR-097 will have a lot more going for it. Like infinitely variable 100:1 speed range - 5 sec/scan to 50 millise/scan... stylus position encoder... automatic recorder synchronization... computer/analyzer compatibility... high resolution and dynamic range... all-electronic drive. And more.

If you design and build - or buy and use - spectrum analyzers, you don't have to settle for multi-purpose recorders any more. The SAR-097 is here. For full details write the Marketing Manager, Raytheon Company, Ocean Systems Center, Portsmouth, R.I. 02871. (401) 847-8000.



Hand-operated tool cuts and crimps leads

Electronic Production Equipment Co., 6 Kane Industrial Dr., Hudson, MA 01749. (617) 562-9123. \$9.50; stock.

A hand tool, the Model 975, is designed to flush out and crimp component leads. It is lightweight, weighing only 5 oz., and measures 5 in. long. The return-spring is double-coil steel and plastic handles are shaped to fit the palm of the hand comfortably.

CIRCLE NO. 320

Mini transistor sockets handle EIA size devices



Garry Manufacturing, 1010 Jersey Ave., New Brunswick, NJ 08902. (201) 545-2424. From \$0.50; 4 to 6 wks.

Miniature packaging sockets, which will accept standard EIA-size transistors, are available for RO-52, TO-5, TO-18 and in-line transistors, with 3, 4, and 6 pins. Pin circles have either 0.1 or 0.2 in. diameters. The sockets feature closed-entry contacts which resist distortion or damage from misaligned or over-sized leads. Terminal sleeves are brass and the plating is gold over nickel. Socket terminals for most applications are available: printed circuit, turret, solder-pot, and wrapped-wire.


CIRCLE NO. 321

Solvent disintegrates cured epoxy compounds

Hightemp Resins, Inc., 225 Greenwich Ave., Stamford, CT 06902. (203) 325-4124. See text.

Hightemp 5625 can disintegrate cured epoxy compounds. It is non-flammable, noncaustic and non-acidic and will not attack metals. The solvent is available in minimum 10 lb. containers for \$0.75/lb. and in 45 lb. lots for \$0.69/lb.

CIRCLE NO. 322

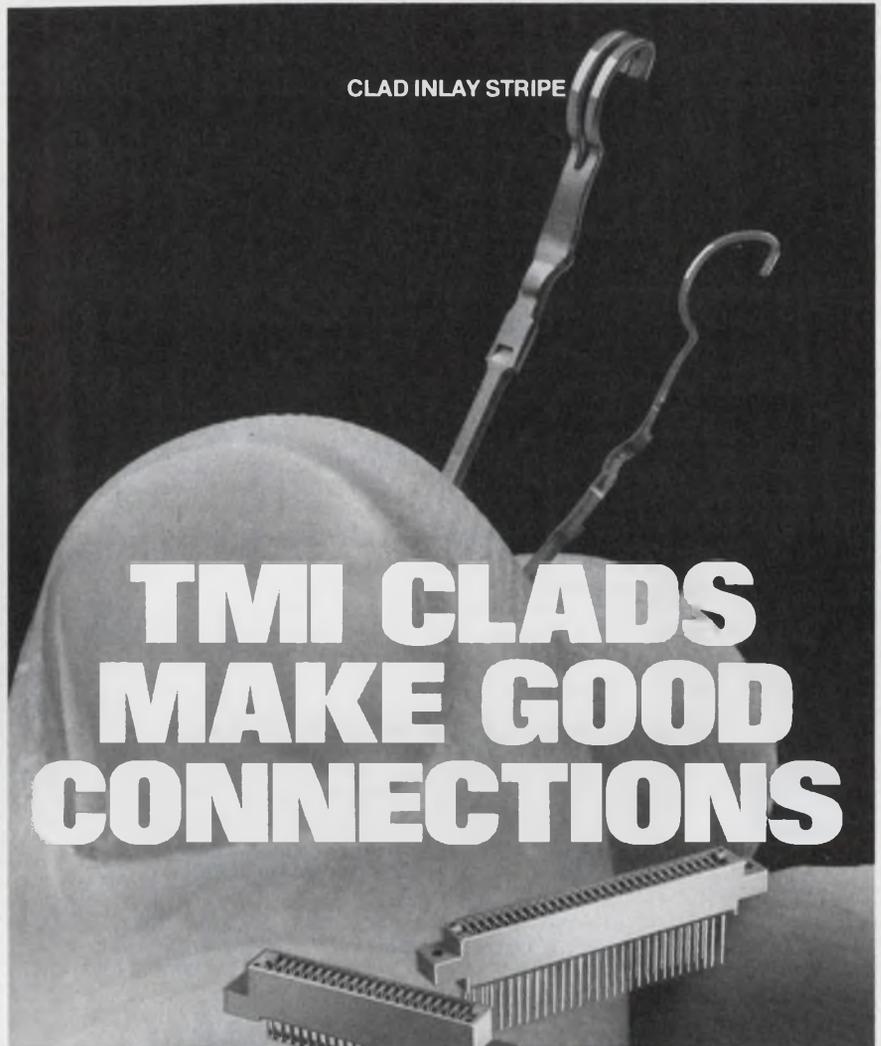

... Good enough for EDAC's PC Edgeboard Connectors, winner of the 1975 Canadian IEEE "Best Component Design" Award. Why did EDAC choose a TMI multi-gauge clad inlay stripe? For some very good reasons:

ECONOMY. It has been a general assumption that clads had to be at least 100 microinches thick. Not so. TMI provides EDAC with a 30 microinch, 18kt gold alloy, clad inlay on CA725 for their PC edgeboard connector. This results in a substantial savings to EDAC because of the minimal thickness of gold required. The 18kt gold alloy replaces 24kt gold for the contact point providing further gold savings and still meeting rigid performance requirements.

FORMABILITY. TMI clad metals permit the stamping and forming of complex bends and shapes without any delamination or flaking of the gold alloy.

DUAL GAUGE. TMI dual gauge allows an .025" thickness for the wire wrap post and .012" for precise leaf spring properties. Dual gauging also permits one source to supply both inlay and dual gauge requirements.

RELIABILITY. The EDAC connector has proven exceptionally reliable for the two years the product has been in service.

If you're interested in making a good connection, contact TMI.



TECHNICAL MATERIALS, INC.

5 Wellington Road, Lincoln, Rhode Island 02865
Telephone: 401 • 728-7200
After July 1, 1976, please dial 401 • 333-1700

CIRCLE NUMBER 51



UNBELIEVABLE!!!!
The Intecolor® 8001
A Complete 8 COLOR
Intelligent CRT
Terminal
\$1,995*

"Complete" Means

- 8080 CPU • 25 Line x 80 Character/Line • 4Kx8 RAM • PROM Software
- Sockets for UV Erasable PROM • 19" Shadow Mask Color CR Tube
- RS232 I/O • Sockets for 64 Special Graphics • Selectable Baud Rates to 9600 Baud • Single Package • 8 Color Monitor • ASCII Set
- Keyboard • Bell • Manual

And you also get the Intecolor® 8001 9 sector Convergence System for ease of set up (3-5 minutes) and stability.

Additional Options Available:

- Roll • Additional RAM to 32K • 48 Line x 80 Characters/Line • Light Pens
- Limited Graphics Mode • Background Color • Special Graphic Characters
- Games

*Quantity 100 (Unit Price \$2,495.)


ISC WILL MAKE A BELIEVER OUT OF YOU!



Intelligent Systems Corp. 4376 Ridge Gate Drive, Duluth, Georgia 30136
 Telephone (404) 449-5961

CIRCLE NUMBER 52

When it comes to value...

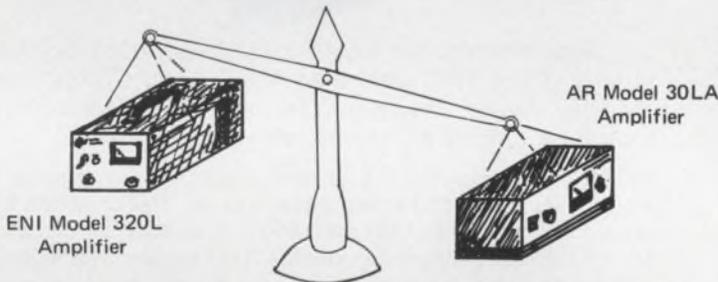

Model 30LA is a HEAVYWEIGHT

Feature-for-feature, the Amplifier Research Model 30LA broadband amplifier outweighs the ENI 320L. This rugged, high performance amplifier provides a minimum 30-watt output from 1-110 MHz. It offers a directional power meter, adjustable gain control, infinite mismatch tolerance, and low harmonic distortion.

If your considering an ENI 320L or any other ENI amplifier, send us the model number. We'll provide you with specifications on a competitive unit.



Amplifier Research
 160 School House Road
 Souderton, Pa. 18964

YOUR BEST SOURCE FOR RF POWER AMPLIFIERS

CIRCLE NUMBER 53

PACKAGING & MATERIALS


Conductive grease helps make RFI-tight case

Emerson & Cuming, Inc., Canton, MA 02021. (617) 828-3300. \$4.70/lb (5 lb and up); stock.

Eccoshield CO is a conductive grease that has a volume resistivity of less than 100 Ω -cm. It can lubricate metal-to-metal sliding contact areas, which require continuous electrical conductive paths. The grease can also ground enclosures, which require lubrication to overcome friction as well as electromagnetic-interference control and rf caulk metal-to-metal joints. Proper shield design and use of Eccoshield CO can produce insertion loss values of 100 dB.

CIRCLE NO. 323

Heavy-duty connectors meet MIL-C-22992E


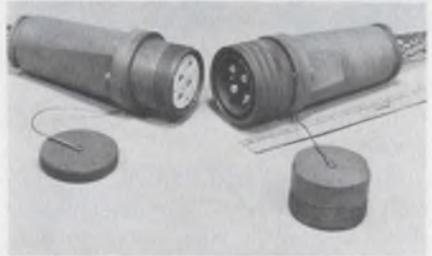


Amphenol Connector, 2801 S. 25th Ave., Broadview, IL 60153. (312) 261-2000. For 100-up quantities: \$100 (mated pair); stock.

A line of multicontact, heavy-duty, waterproof plug and receptacle connectors is fully qualified to latest specifications of MIL-C-22992E, Class L. Shell size 28, 32, 44 and 52 connectors, with current ratings of 40, 60, 100, and 200 A, respectively, are initially available. The power distribution connectors offer several significant features: An arc-suppression chamber within the connector protects users from serious shock hazards, an internal multiple-part environmental sealing mechanism completely waterproofs the assemblies, whether mated or unmated, a built-in five key shell polarization prevents mismatings and an integral safety ground is included in compliance with requirements of OSHA and the National Electrical Code for grounding connectors.

CIRCLE NO. 324

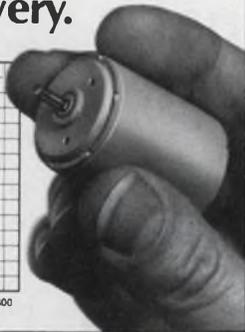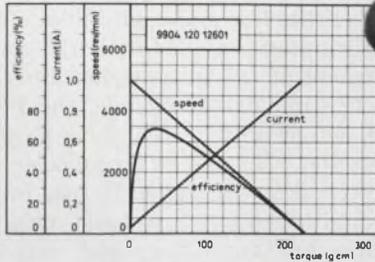**Superior performance...
Significant cost advantages...
Off-the-shelf delivery.**



**Miniature ironless rotor DC motors.
Ideal for cassette drives.**


The typical performance graph shown above speaks for itself. Our miniature ironless rotor 12 VDC motors not only have the desired characteristics for cassette drives, they also offer an important price advantage—under \$10.00 in 500-piece lots. As low as, if not lower than, any competitive motor. Fast, off-the-shelf deliveries, too!

Motor time constant is 23 MS; rotor torque 50 gcm; starting torque 230 gcm. Plus, low noise levels and smooth cog-free operation. The motor can also be ordered with double shaft for use as a tach motor. 24 VDC models also available.

Send for information today!
A. W. HAYDON CO. PRODUCTS

NORTH AMERICAN PHILIPS CONTROLS CORP.

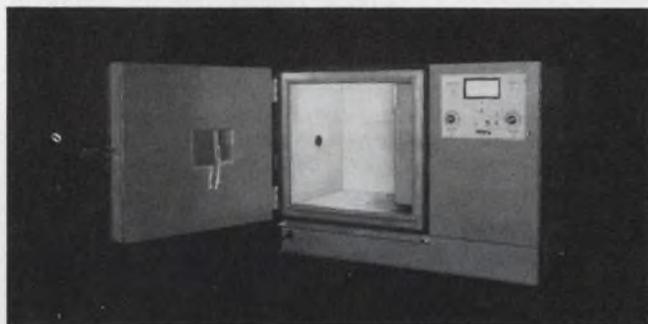Cheshire, Conn. 06410 • (203) 272-0301
CIRCLE NUMBER 54



**BENCHMASTER...
5 CUBIC FEET OF
BENCH-TOP TEST SPACE!**

Economical, portable, and compact, this all-new front-opening temperature and humidity test chamber is only 4 feet wide!

It's extremely versatile, too. Benchmaster offers medium or extreme temperature ranges—with or without humidity. Benchmaster is available in 4 performance variations:

- Model BTH: 0°F to 200°F with humidity
- Model BTR: -30°F to 350°F with humidity
- Model BTR: -100°F to 350°F with humidity
- Model BTC: -100°F to 350°F without humidity

Write for complete information.



1090 Springfield Rd., Union, N.J. 07083 • (201) 686-7870 • (212) 962-0332

CIRCLE NUMBER 55



**There Goes Your Reputation
--Up In Smoke.**

Here's how to protect your product, your customer—and yourself!

Just add MICROTEMP® safety thermal cutoffs to your plans. The millions already in use are your assurance of positive, yet low cost protection against overheating caused by malfunctions in electrical circuits and components.


- compact—diameter, .157"; length, .457" (exclusive of leads)
- economical—priced as low as 9¢
- proved reliable in millions of on-the-job applications
- installation ease—assorted terminations, mounting packages and insulations are available

MICROTEMP is a reliable, accurate, easy to install, "one shot" thermal limiter. Because of its patented design and construction, it won't derate. And, it's unaffected by age or extended use.

Recognized under the Component Program of Underwriters' Laboratories, Inc. UL File #E40667A. CSA and BSI Certificate #5041 approved. Recognized by MITI and VDE. Military approval.

Compare this data:

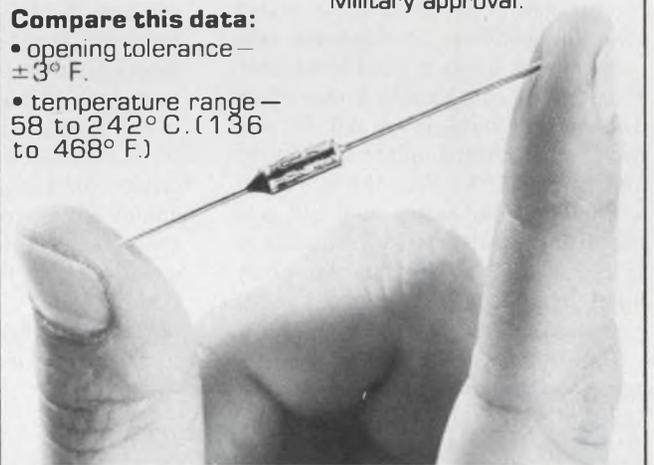- opening tolerance— $\pm 3^\circ$ F.
- temperature range—58 to 242°C. (136 to 468°F.)



For additional information, check the reader service card, or call or write:




MICRO DEVICES CORP.

1881 Southtown Blvd., Dayton, Ohio 45439
Ph: (513) 294-0581 Telex: 28-8087

CIRCLE NUMBER 56

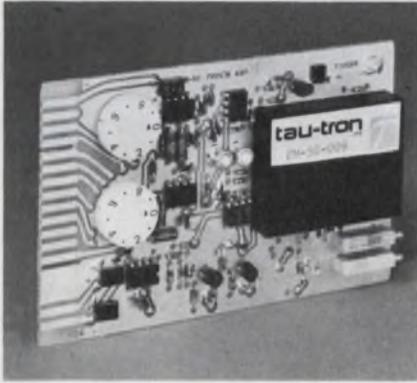Drive lines and discriminate pulses at 50-MHz data rates




Tau-Tron, 11 Esquire Rd., North Billerica, MA 01862. (617) 667-3874. P&A: See text.

High-speed comparators and line drivers for automatic test equipment have been introduced by Tau-Tron. These units can operate at frequencies of over 50 MHz and are available in either printed-circuit mountable modules or complete PC-card assemblies.

The analog-comparator module, the M-AD-10, is a 1 × 1-in. hybrid circuit that can operate as either two independent single-level discriminators or as a dual-level unit. Each input can handle a maximum differential voltage of ±5 V, and has a maximum common input voltage of ±3.5 V. The input resistance for either input is 6 kΩ, and the differential input offset voltage is ±2.5 mV at 100 Ω. An error band of ±2 mV is added by the comparator to the input signal.

Inputs of the M-AD-10 are in-

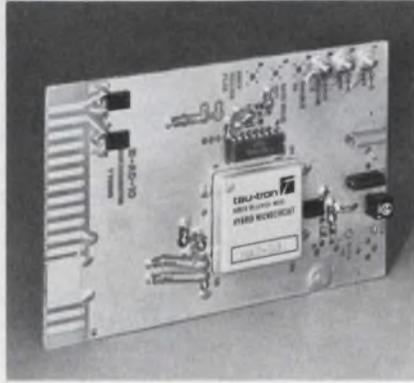

tended for ECL-level signals, as are the outputs. However, the outputs have open-emitter transistors that require external termination.

When operated as two independent comparators, each discriminator has its own threshold adjustment. In the two-level mode, the two data inputs are tied together and the trip points can be set using separate threshold adjusts. Each discriminator also contains a latch that either permits the reference voltage to be compared normally with the input signal, or locks the discriminator output to the existing state of the data.

Switching times are fast—the input-to-output, high-to-low transition, for instance is 10 ns. Latch-enable times are also 10 ns, and the time the strobe line requires to move data to the output is a mere 1 ns.

The discriminator module offers four usable outputs—a channel-1

high output, a channel-2 low output, a gray region output and a discriminator-valid output. The gray-region output lets you know when the voltage levels present at the input lines are somewhere between the low and high limits. The discriminator-valid line is the complement of the gray-region line.

The line-driver module, the PM-50, is a programmable power amplifier that operates at frequencies of better than 50 MHz. It has individual control of input and output-pulse top and input and output-pulse bottom and measures only 1.25 × 2 in. The input is designed for ECL-level signals and is terminated by 50 Ω to -2 V. (50 Ω to ground is available as an option.)

Both the input and output pulse tops and bottoms can be adjusted over a ±2-V range, although ±5-V adjustment ranges are available on the outputs as an option. The amplifier has an input impedance of 10 kΩ and will reproduce the original input signal to within ±20 mV. Rise and fall times for the amplifier are 2 ns, typically, with the total propagation delay reaching only 7 ns.

Signal aberrations on rising or falling edges are guaranteed to be no more than 100 mV pk-pk or 7 percent (whichever is greater) when the module is properly terminated. Output terminations must be specified when the module is ordered, and can be any value between 50 and 100 Ω.

Prices for the modules start at \$350 for the M-AD-10 discriminators and reach \$450 for the amplifier module. Circuit cards with the modules built in range from \$400 to \$585. The cards measure 2.5 × 5 in. Modules and cards are available from stock.

CIRCLE NO. 304

TV ANALOG

ANA, YOU CAN WIN A TRIP TO HAWAII WITH THE RIGHT WORDS. READY?

YES

QUIZ SHOW FINISH THAT TUNE

REPLACE YOUR A/D WITH AN INTECH VFC AND DA DA DA DA...

AHH GOLLY, GEE.

"SORRY! IT'S 'SAVE MONEY,' BUT HERE ARE TWO TICKETS TO THE LODI STRAY DOG CATCHING RODEO."

ANALOG

YOU CAN'T LOSE WITH THE WORLD'S FIRST MONOLITHIC 14-PIN DIP V/FV CONVERTER. EXTERNAL R/C DEFINES PROPORTIONAL FULL SCALE FREQUENCY OUTPUT (TTL, DTL, CMOS COMPATIBLE) THROUGH THE 100 KHZ BAND. 0.05% LINEARITY (0.025% @ 10 KHZ) FOR FULL SCALE INPUT OF 0 TO +10V. USE THE A-8400 AS A F/V FOR A 2-WIRE DATA LINK OR COMBINE IT WITH A BINARY COUNTER FOR A/D ENCODING RATE OF 25 12-BIT CONVERSIONS / SEC.

intech/FMI

282 BROKAW RD. SANTA CLARA, CA 95050 (408) 244 0500


Improved acquisition modules cut costs

Data Translation, 109 Concord St., Framingham, MA 01701. (617) 879-3595. See text; 4 wks.

The DATA X II series of modular data-acquisition systems offers improved specs at lower prices than the company's older DATA X I series. Models DT5720 and DT5740 offer 12-bit resolution and throughput speeds of 50 and 25 kHz at prices of \$575 and \$475, respectively. The modules have three-state outputs, which permit their use with most microcomputer systems. Linearity of the DATA X II series is ± 0.5 LSB over 0 to 70 C and the systems have an accuracy of 0.03% for the full-scale range. All units are housed in $3 \times 4.6 \times 0.375$ in. metal modules.

CIRCLE NO. 325

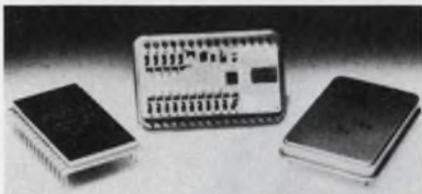Multiplying d/a accepts 13-bit input words



Beckman Instruments, Helipot Div., 2500 Harbor Blvd., Fullerton, CA 92634. (714) 871-4848. From \$100 (100-up); stock.

The 877-69 series of multiplying d/a converters includes units with resolution of up to 13 bits. They have provisions for external ac or dc references for full four-quadrant operation, can handle ac reference frequencies from dc to 10 kHz, and have an MSB inversion input for TWO's complement or offset binary arithmetic options. The 30-pin, dual in-line metal or ceramic packaged devices are available in two accuracy (linearity and gain) code models. Typical accuracy of Model 877-69M-D1 (metal package) is $\pm 0.012\%$ at 25 C, guaranteed to $\pm 0.025\%$ over -55 to $+125$ C, or $\pm 0.05\%$ at 25 C guaranteed to 0.1% for Model 877-69M-D2. Typical accuracy of Model 877-69C-C1 (ceramic package) is $\pm 0.012\%$ at 25 C guaranteed to $\pm 0.025\%$ over -25 to $+85$ C or $\pm 0.05\%$ at 25 C guaranteed to $\pm 0.1\%$ for Model 877-69C-D2.

CIRCLE NO. 326

F-16
CUSTOM HYBRIDS
by **CTI**
will be aboard!

Circuit Technology, Inc.
160 Smith St., Farmingdale, N.Y. 11735
(516) 293-8686 • (213) 374-7446

CIRCLE NUMBER 58

99 and 44/100% reliable.

Our return rate on encapsulated power supplies is less than 1%. This excellent reliability is one of the reasons we're the world's leading manufacturer of encapsulated power supplies.

Like to hear more reasons?

All our power supplies feature internal short circuit protection. All are "triple-tested" before delivery to insure performance. And all have a 24 month warranty.

We offer 49 models with single and dual outputs from

3.6V to 28V, and with output currents from 65mA to 2000mA.

Best of all, the cost is surprisingly low, and delivery is extremely fast.

Want to find out more about our power supplies? Simply circle our number on the Reader Service Card and we'll mail you our new Power Supply Catalog. If you're in a hurry, call us at (305) 974-5500.

 Computer Products, Inc.



Distributors: Los Angeles 213-877-5518/Albuquerque 505-255-2440

1400 N.W. 70th Street, Fort Lauderdale, Florida 33309 • (305) 974-5500, TWX (510) 956-9895

CIRCLE NUMBER 59

Pure Power

IT'S FA

We're st



Stephen J. Scorza
General Manager
NOBEL ELECTRONICS, INC.



Tell us what you think about the GOLD BOOK. (If it's good, we'd like to hear it. If it's bad, we want to improve it.)

NTASTIC!

getting business from Jermyn's catalog pages in the **GOLD BOOK**

"We receive numerous calls and letters, both from the U.S.A. and all over the world, which we can readily ascribe to the **GOLD BOOK**," writes Stephen J. Scorza, General Manager, Nobel Electronics, Inc., New City, New York.

In July 1975, Nobel assumed U.S. stocking, marketing, and sales operations for Jermyn, an English company. (Jermyn manufactures semiconductor hardware: IC and transistor sockets, mounting pads, transi-pads, insulators, and heat sinks.)


"Many of the engineers who contact us refer to specific Jermyn products illustrated in the **GOLD BOOK**, requiring either the standard item or a slightly modified version. A brief phone conversation, followed-up with evaluation samples, is frequently all that is needed to produce the initial order. Now, that's cost-effective selling—and all because the catalog pages serve to qualify readers, making them much stronger prospects.

"The **GOLD BOOK** is a good *selling* tool because it is an extremely good *buying* tool. We use it ourselves to locate new sources of old items and to discover new items that may be useful in design and test."

Because the **GOLD BOOK** goes primarily to *Electronic Design's* audience of specifiers, Jermyn (and now Nobel Electronics) gets the benefit of 78,000 engineers, engineering managers, purchasing agents and distributors throughout the U.S.A., not to mention 13,000 overseas. These are the men who are ready to talk business—the men who have the authority to *buy*.

**ELECTRONIC DESIGN'S GOLD BOOK IS WORKING
...IT'S WORKING FOR READERS...AND IT'S
WORKING FOR ADVERTISERS, TOO.**

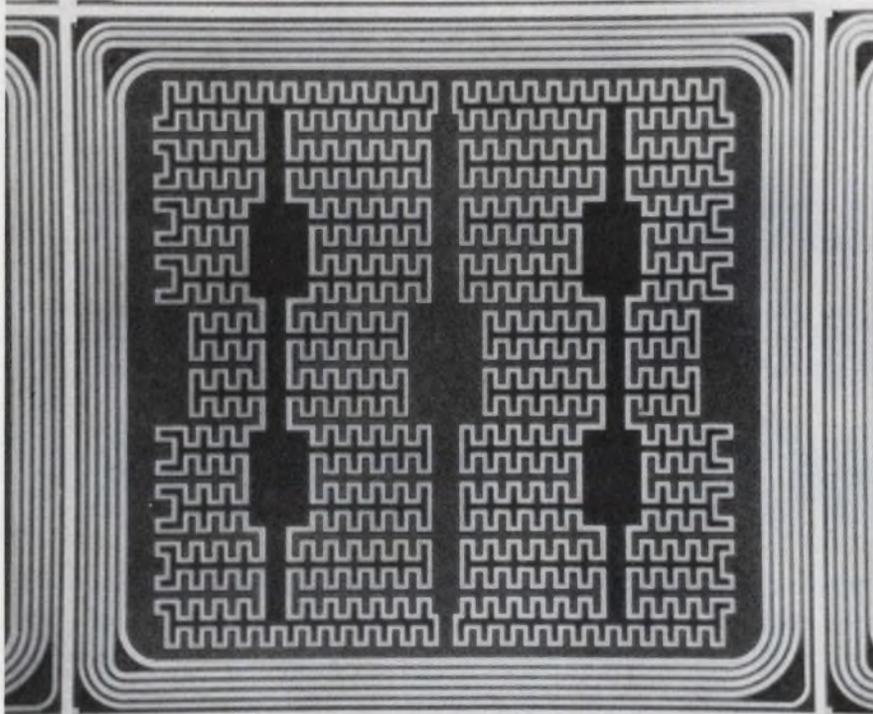10 & 15-A transistors switch fast and have high gain



General Semiconductor Industries, 2001 W. Tenth Pl., Tempe, AZ 85281. (602) 968-3101. See text; up to 1000 pieces available from stock.

The first 10 and 15-A power transistors that have total switching times of less than 1 μ s are available from General Semiconductor Industries. Their dc-current gains are at least 10—a figure most other manufacturers require Darlington configurations to get, and then only at slower speeds.

Of the discrete transistors already on the market, the one that comes closest is the SVT 400-12 from TRW Power Semiconductors (Lawndale, CA). It is a 12-A, 400-V device with a maximum rise time of 0.5 μ s, a maximum storage time of 2 μ s, and a maximum fall time of 0.5 μ s. Its dc-current gain is at least 10.

In comparison, the XGSR15040 from General Semiconductor is a 15-A, 400-V device that has a maximum rise time of 0.07 μ s, a maximum storage time of 0.35 μ s and a maximum fall time of 0.2 μ s.

Minimum dc current gain is also 10. There are also 250, 300 and 350-V versions with the same switching speeds but minimum gains of 20, 15 and 10, respectively.

General Semiconductor's 10-A device has the same gains at 250, 300 and 350-V as the equivalent 15-A versions and are just as fast.

These General Semiconductor transistors all come in a standard TO-3 package. The allowable junction temperature for the transistors ranges from -65 to $+175$ C. Saturation voltage on all of the General Semiconductor devices is no higher than 0.8 V.

Costs, in 100-999 quantities, for the 15-A transistor start at \$14.75 for the 250-V unit and increase to \$20 for the 400-V unit. 10-A device pricing ranges from \$13 for the 250-V unit to \$14.25 for the 350-V unit.


TRW's transistors cost \$8 to \$9 for 100-piece lots.

General Semiconductor

TRW

CIRCLE NO. 302
CIRCLE NO. 303

Varactor tuning diodes have Qs of 12,000

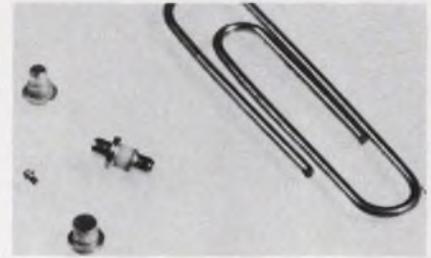


Alpha Industries, 20 Sylvan Rd., Woburn, MA 01801. (617) 935-5150. \$75 to \$98 (small qty.); 15 days.

The DVE4550 series of gallium arsenide tuning varactors has wide tuning ratios and high values of Q. A choice of five standard ceramic/metal packages is available. All diodes are burned-in prior to final measurement. Some of the diode characteristics (when measured at 25 V and 10 μ A) include: capacitance range, 0.4 to 4 pF; Q_{-1} range (at 50 MHz), 4300 to 12,000; Q_{-1} range (at 1 GHz), 215 to 600; and reverse leakage current at 20 V bias, 100 nA.

CIRCLE NO. 327

LED lamps come in many colors

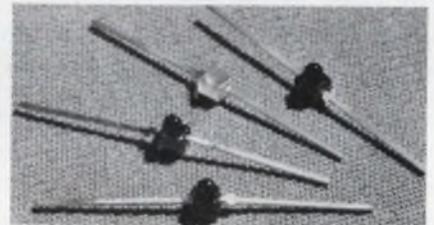


Hewlett-Packard, 1501 Page Mill Rd., Palo Alto, CA 94304. (415) 493-1501. \$0.19 to \$.65 (100-999).

Four new low-cost LEDs in a radial-lead subminiature epoxy package include a red, yellow, green and a high-efficiency red type. They can be mounted in stacked arrays on 2.21-mm centers for high-density applications. A tinted diffused lens for each color provides high on-off contrast with a wide viewing angle. At a forward current of 10 mA, the red HP 5082-4100 has an axial luminous intensity of 0.7 mcd; the red HP 5082-4101, 1 mcd. Forward voltage is 1.6 V. The high efficiency red has an output of 3 mcd at a forward current of 10 mA and forward voltage of 2.2 V.

CIRCLE NO. 328

Behind every good designer is a new Cambion catalog.

Our new giant 747-A general catalog has a 56-page section just on new products introduced since our last big catalog. That's in addition to our familiar products like solder terminals, terminal boards, insulated terminals, coil forms, coils, RF Chokes, connectors, capacitors, IC accessories, hardware and thermo-electrics. You can get one behind you free just by writing: Cambridge Thermionic Corporation, 401 Concord Ave., Cambridge, MA 02138.

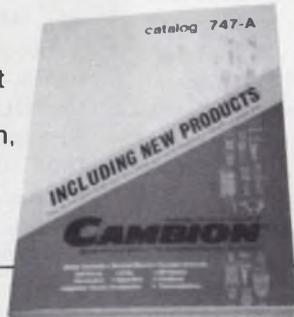

Standardize on

CAMBION

The Guaranteed Electronic Components

CIRCLE NUMBER 61

Facts. The GOULD/Brush 2400 delivers more of them with less fuss, bother and cost than any other oscillograph you can buy.

And it does it on a wide 100mm channel and at a remarkable 30Hz. Available in 2, 3 and 4 channel models with all the Gould exclusives, of course.

For the full Gould 2400 story, write Gould Inc., Instrument Systems Division, 3631 Perkins Avenue, Cleveland, Ohio 44114. Or Gould Allco S.A., 57 rue St. Sauveur, 91160 Ballainvilliers, France.

PHONE FREE (800) 648-4990 FOR BROCHURE.



GOULD

CIRCLE NUMBER 62

ELECTRONIC DESIGN 7, March 29, 1976


POWER

Power you can count
Power you can count on



AILTECH's Model 446 RF Power Signal

Source has an easy-to-read 5 digit frequency counter, with accuracy as high as .002%, power output to 50 watts, full AM-FM capability, and covers a frequency range from 10KHz to 2500MHz with plug-in head versatility. It's just part of a complete line extending up to 8GHz. Universally used for EMC testing, wattmeter calibration, component evaluation, high-power solid-state amplifier design, biological studies and plasma investigations, the Model 446

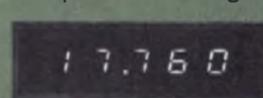

features easy operation and direct indication of forward and reflected power.

For truly turnable precision RF power, consider Model 446. Don't take our word for it, though. With Model 446 you can count it yourself.

We've
Got The
Power

plus a complete line of Noise Figure Instrumentation, Spectrum Analyzers, System Noise Monitors and Frequency Synthesizers.

AILTECH 
A CUTLER-HAMMER COMPANY


WEST COAST • CITY OF INDUSTRY, CA. 91748 • (213) 965-4911
EAST COAST • FARMINGDALE, NEW YORK 11735 • (516) 595-6471
FRANCE • LA GARENNE-COLOMBES • TELEPHONE (01) 780-73-73
UNITED KINGDOM • CROWTHORNE • TELEPHONE 5777
GERMANY • MUNICH • TELEPHONE (089) 5233023
JAPAN • TOKYO • TELEPHONE (404) 8701

FOR DATA CIRCLE NUMBER 271

FOR DEMONSTRATION CIRCLE NUMBER 272

DISCRETE SEMICONDUCTORS

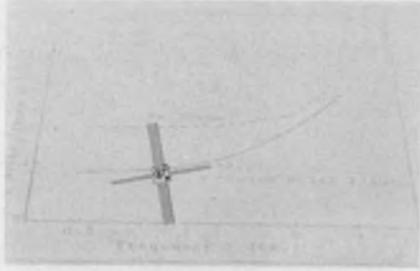Microwave transistors have 1.7 dB of noise



Fujitsu Limited, Syuwaonarimon Building, 1-1 Shinbashi, 6-Chome, Minato-ku, Tokyo 105, Japan.

A microwave low-noise transistor, the FJ203, has noise characteristics of 1 dB at 1 GHz and 1.7 dB at 2 GHz. The transistor is passivated with silicon-nitride film and is housed in a metal/ceramic hermetic package. Specifications of the transistors include: a gain-bandwidth product, f_T , of 8 GHz; a maximum available power gain of 13 dB at $f = 2$ GHz; and a power dissipation of 200 mW, max.

CIRCLE NO. 329

Voltage crowbars handle 3 to 235 A continuous




MCG, 297 Skidmore Rd., Deer Park, NY 11729. (516) 586-5125. From \$3 (1000-up); 2 wks.

The Series LVC-1 dc crowbars switch in less than 10 μ s from an open to a virtual short circuit. Potentially destructive energy from transients, series regulator faults, misadjustments, etc., can be almost eliminated. The crowbars recover when power is momentarily removed. Trip voltages are available from 4.7 to 600 V dc at current levels ranging from 3 to 235 A dc. Temperature range is -55 to 100 C.

CIRCLE NO. 330

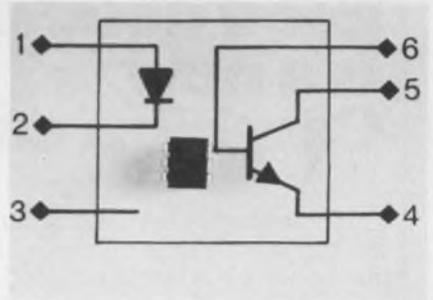Improved opto-isolator replaces earlier version



Energy Electronic Products, 6060 Manchester Ave., Los Angeles, CA 90045. (213) 670-1275. \$0.89 (100-up); stock.

The EL 74 A opto-isolator comes in the same six-pin plastic DIP as the EL 74, which it is replacing. The improved unit has a response time of 2 μ s compared with 20 μ s for the old; a dark current of 50 nA instead of 500 nA; and a breakdown voltage of 30 V instead of 20 V. Current transfer ratio, isolation voltage and isolation resistance are the same as for the older units (35%, 1500 V, and 100 G Ω , respectively).

CIRCLE NO. 331

Power to the μ P



Sola offers DUAL and TRIPLE OUTPUT POWER SUPPLIES for MICROPROCESSORS and accessories: RAM's, PROM's, ROM's, FEPROM's, CLOCKS and IO devices.

All available from your local electronic distributor. At competitive pricing. From a name you can count on—Sola.

Our versatile power supplies offer fully isolated independent outputs for either positive or negative operation. Series or parallel operation. Plus, remote sensing/programming, and complete serviceability. Just call or write for Catalog 647.

For added protection, consider our minicomputer regulators, UPS, and Standby units. Everything you need for MPU power and protection.

Sola Electric, 1717 Busse Road, Elk Grove Village, Ill. 60007 (312) 439-2800.

SOLA ELECTRIC



Think of us as your supply line.

CIRCLE NUMBER 64

DATA PROCESSING


Disc storage multiplexed among four processors

Wang Laboratories, Inc., 836 North St., Tewksbury, MA 01876. (617) 851-4111. \$800: first units, \$500: each of three additional; 2 wks.

Disc-storage units are one of the most expensive elements of any data-processing system, according to Wang. With its new Model 2230MX-A/B disc multiplexer, a user can cut this cost. The multiplexer allows up to four System 2200 processors to share a single disc drive. Access is on a "daisy-chain" basis, with a master controller polling each processor sequentially on an equal-priority basis. All processors sharing the disc have almost concurrent access at all times, since a single access typically requires from 20 to 80 ms to complete.

CIRCLE NO. 332

PROM eraser delivers calibrated UV dose

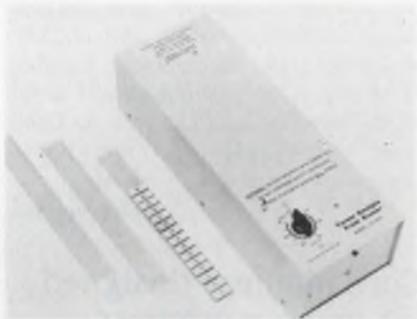

Turner Designs, 2247A Old Middlefield Way, Mountain View, CA 94043. (415) 965-9800. \$295 (unit qty).

The Model 30-000 PROM eraser can deliver the correct UV wavelength and intensity for MM5203Q, 1702A, 2708 and similar type PROMs, and handle as many as 60 simultaneously. Devices are loaded with removable metal trays, which protect the PROMs against electrostatic damage. Operation is controlled by an adjustable timer, calibrated in increments of 1 min. Exposures can be set from very short durations to more than 1 h. Lamp start is automatic. The operator is protected from UV exposure by a door interlock and from ozone by a specially designed lamp envelope.


CIRCLE NO. 333

The Fastest Way: Data Acquisition with μ C.


Throughput rates of 125KHz or 8 μ seconds per channel are now easily accomplished with our DT5710A Data Acquisition Module. Our second-generation DATAX II™ Data Acquisition Module is complete with multiplexer, differential amplifier, sample/hold, 12-bit A/D converter, and all control and programming logic . . . plus TRI-STATE outputs for direct connection to computer busses.

A fast data acquisition front end solves the throughput problem in μ C systems where time is at a premium. DMA systems, FFTs, telecommunications, and large multi-channel systems can also benefit from the DT5710A's throughput of 125,000 channels per second.

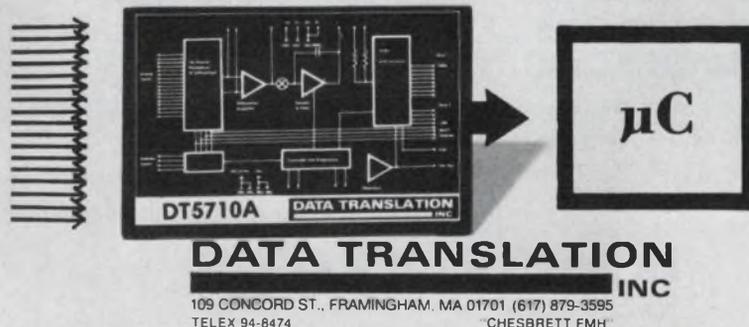Call us at 617/879-3595 for a complete set of applications data.



CIRCLE NUMBER 65

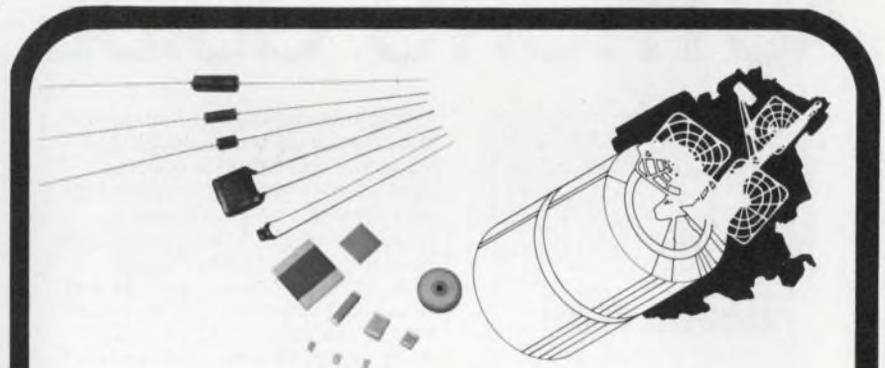

A New High in Stability

Centre Engineering has met the challenge of providing ultra-high reliable sub-miniature ceramic capacitors for the space programs. Now, design engineers in the tele-communications, computer and instrumentation industries can have ceramic capacitors in high volume for low cost applications, using the same processes and manufacturing techniques from Centre Engineering.


Ceramic capacitors are available in 40 various formulations with a capacity range of 1pf to 10mfd. For applications requiring large volume, low cost ceramic capacitors consider Centre Engineering. Catalog available upon request.

CE CENTRE ENGINEERING

2820 E. COLLEGE AVE., STATE COLLEGE, PA. 16801
814-237-0321 - TWX 510-691-2634

CIRCLE NUMBER 66

Free Catalog:

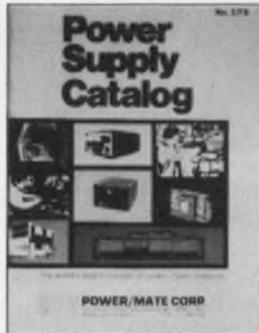

Free advice:

Use Power/Mate power supplies. We'll save you time and money because we make more power supplies for more applications than any other power supply manufacturer in the business.

And that's not all. We'll service you from stock with whatever you need for whatever the job and usually ship it out the

same day.

Power/Mate's building block approach even enables you to design customized power supply systems from off the shelf units.

And everything we sell is unconditionally guaranteed. Call or write for our 84 page catalog today.




POWER/MATE CORP.

World's largest manufacturer of quality power supplies.

514 South River Street/Hackensack, N.J. 07601 / Phone (201) 343-6294 TWX 710-990-5023

CIRCLE NUMBER 68

AUTHOR'S GUIDE

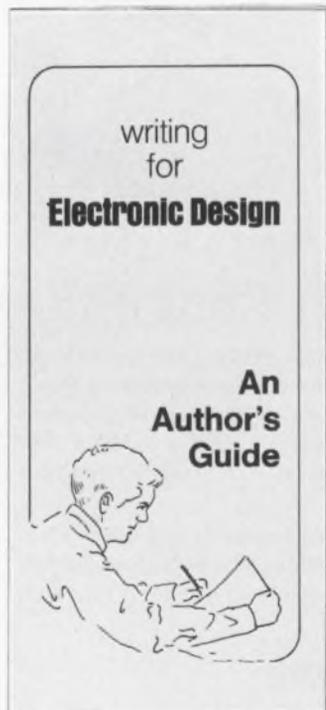

If you've solved a tricky design problem, if you have developed special expertise in a specific area, if you have information that will aid the design process... share it with your fellow engineer-readers of *Electronic Design*.

Articles you have authored not only raise your own professional status, but help build your company image as well. The readers benefit, your company benefits.

To help you prepare material that meets *Electronic Design's* high editorial standards, our editors have prepared a special author's guide entitled "Writing for *Electronic Design*." It covers criteria for acceptability, form, length, writing tips, illustrations, and payment for articles published. It's available without cost.

It's easy to write for *Electronic Design*, but it's often hard to get started. Send for your copy of our Author's Guide today.

Circle No.
895

DATA PROCESSING

2400 lpm printer
sells for \$3000



Houston Instrument, One Houston Square, 8500 Cameron Rd., Austin, TX 78753. (512) 837-2820. See text.

A 2400 line/min printer, Model 8210, sells for only \$3000. Its output is 80-columns wide on 8-1/2-in. paper. Also a 132-column output, which prints on 14-7/8-in. paper at 1400 lines/min sells for \$3785. Their features and performance rival that of \$10,000-to-\$20,000 printers, according to the manufacturer. The features include a full-print line-buffer memory, automatic top-of-form advance, 400-in/min paper-advance speeds, the ability to use both roll and fanfold paper interchangeably, and enough speed to make the printer capable of doing a core dump from a 64 kbyte mini in less than 30 s. Low-cost electrostatic printer paper commonly available is used.

CIRCLE NO. 334

Core memory designed for microcomputers

Ampex Corp., P.O. Box 33, Marina del Rey, CA 90291. (213) 821-8933. \$99.95 (OEM qty).


The MCM-4300 is the second in Ampex' family of microcomputer core memories designed for terminal, peripheral and microprocessor applications. The memory provides a nonvolatile storage of 2048, 1024, 512 or 256 four-bit data words. Applicable to read/modify/write applications, the memory modules provide data access in 450 ns. Only a single uncompensated 5-V power source is required. Each module includes timing and control, data and address registers, decoding and drive circuits and a TTL-negative-true interface. Multiple modules may be combined in parallel for larger capacities.

CIRCLE NO. 335

Thick Film Dual-In-Line Resistor Networks

- Resistor Values: 100 ohm to 10K ohm
- Tolerance: $\pm 2\%$
- TCR: ± 200 ppm/ $^{\circ}\text{C}$
- Package Power Rating: 2.5 watt
- Four popular series:

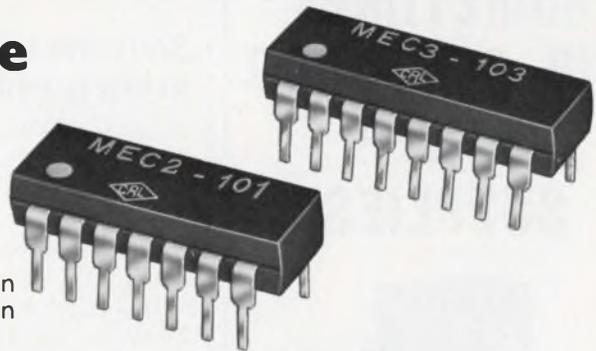MEC1, 13 resistor, 14 pin MEC3, 8 resistor, 16 pin
 MEC2, 7 resistor, 14 pin MEC4, 15 resistor, 16 pin



Now Available For Off-The-Shelf Delivery From Centralab Distributors

Not just another resistor network, these are backed by Centralab's 31 years in thick film microcircuitry. They're proven in use . . . reliable . . . for such typical applications as pull-up and pull-down networks or line terminators. Best of all you can get them fast . . . through our network of over 200 Centralab Distributors. When you think of networks—think of Centralab. Call your Distributor for complete details, prices and delivery.

DISTRIBUTOR PRODUCTS



CENTRALAB

Electronics Division
 GLOBE-UNION INC.

5757 NORTH GREEN BAY AVENUE
 MILWAUKEE, WISCONSIN 53201

CIRCLE NUMBER 69

Rose enclosures. New. Beautiful. Quality. Standards.



Rose Enclosures, made specifically for electronic use, culminate years of design, engineering and production experience. Extra high quality, precision-finished units provide functional protection, easy access, excellent esthetics. Available materials: Lexan, Aluminum, Polyester and ABS. Clear plastic covers with Lexan and ABS. A competitively-priced stock of Rose Enclosures is maintained in Belding, Mich. for immediate shipment. Contact us at (616) 794-0700.

STAHLIN
 BROTHERS, INC.
 Belding, Michigan 48809

CIRCLE NUMBER 70

ELECTRONIC DESIGN 7, March 29, 1976

FAST GUN FOR SALE

RAPID IC INSERTER FROM 'MES' WILL PAY FOR ITSELF WITH INCREASED PRODUCTION.

STICK-A-DIP the first, truly new innovation in manual insertion tools in years. Accepts plastic shipping stick. Eliminates handling of ICs. Uses either 14 or 16 pin ICs mixed. Squeeze trigger until IC leads protrude from nozzle, align into respective holes in printed circuit board and squeeze trigger again, IC ejects into PCB.

STICK-A-DIP is jam-proof, lightweight, projected nozzle for easy alignment. DIP-STICKS permit pre-programming for production and inventory control. STICK-A-DIP #1100. DIP-STICKS #P/N 1101.

Micro Electronic Systems Inc.

8 KEVIN DRIVE, DANBURY, CT 06810 TEL (203) 746-2525

CIRCLE NUMBER 71

SOMETIMES OUR STANDARD POWER SUPPLIES



ARE A LITTLE SPECIAL!

For special electrical and/or mechanical power supply needs, Arnold Magnetics is hard to beat. Our unique modular concept allows us to mix our standard modules with specials to meet custom design requirements. The result is reduced engineering costs, fast deliveries and proven performance. And with over 1200 possible standard configurations a special from someone else may be just another standard for us.

- Single or dual inputs:
115 VAC, 47-500 Hz.
12, 18, 48, 115, 150 VDC.
- Multiple isolated and regulated DC outputs from 4.2 to 300 VDC.
- Line & load regulation to 0.1%.
- Up to 400 watts per output.
- Efficiencies to 85%.
- Completed units provided in tested and encapsulated, conduction cooled packages.

Call or write for more information today!



ARNOLD MAGNETICS CORPORATION

11520 W. Jefferson Blvd.
Culver City, Ca. 90230 • (213) 870-7014

CIRCLE NUMBER 72

COMPONENTS


Sensitive relays come in low-profile package

Gould Inc., Allied Control Div., 100 Relay Rd., Plantsville, CT 06479. (203) 628-9654. From \$3.15 (1 to 24); stock.

The MPCS relays have a 160 mW sensitivity at pull-in. They are available in either a 1-form-C or 2-form-C contact configuration. Either configuration can switch 2 A. The relays are also low-profile units—only 0.415 in. high × 0.6 wide × 1.1 in. long.

CIRCLE NO. 336

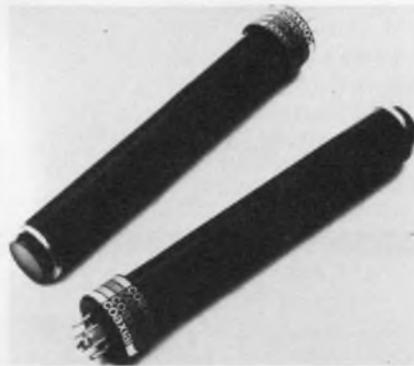Lead-oxide vidicons offer users many plusses




English Electric Valve North America Ltd., 1 America Dr., Cheektowage, NY 14225. (716) 632-5871. \$1925 to \$2200 ea.; stock.

The P8130 series of Leddicon (lead-oxide vidicon) TV camera tubes has five advantages over typical vidicons. Because of its coaxial construction it offers: separate or integral mesh operation, reduced line-scan pickup, operation at any attitude, self-generated or variable-light bias that results in low lag and good dynamic resolution with uniform dark current, and use in virtually any 30-mm-diameter camera. The tubes fit standard, unmodified, 30-mm sockets (such as type 56021) and require a total current of 300 mA for energizing the cathode heater and internal light bias source. The heater voltage of the tube is 6.3 V ±5%, the ratio of capacitance of the signal electrode to that of all other electrodes is 3 pF to 6 pF and the peak spectral response is approximately 500 nm.

CIRCLE NO. 337

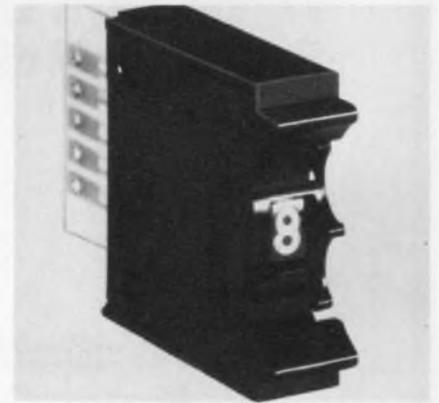Narrow thumbwheel switches cut panel space



Cherry Electrical Products, 3600 Sunset Ave., Waukegan, IL 60085. (312) 689-7702. \$2.15 (2000-up); stock.

A 0.35-in.-wide thumbwheel switch series, the T35, has 0.16-in.-high dial characters. The T35-02A comes in a black-gloss finish and has BCD outputs. The T35 series thumbwheels may be ordered individually or in assemblies of several switches ganged side-by-side. An assembly of 40 switches complete with end caps, uses only 1 × 12 in. of front-panel space.

CIRCLE NO. 338

Bleep to blast with this sound kit



C.A. Briggs, Co., P.O. Box 151, Glenside, PA 19038. (215) 885-2244. \$34.95 (unit qty); stock.

The new Cybersonic designer's kit makes it possible for the designer to listen to and demonstrate a bleep to a blast range of sounds. The 14 sounds that can be produced from the devices and accessories included in the kit provide nominal sound-pressure levels of 65 to 90 dBA at distances of 3 to 10 ft. Current drain is in the range of 3 to 30 mA at the nominal-operating voltage of 12 V dc.

CIRCLE NO. 339



6th international exhibition MESUCORA 76

Measure • Analysis • Control • Testing • Automation

10th-17th JUNE 76 - PARIS

Parc des Expositions
Porte de Versailles (France)

551 groups
of Measurement, Analy-
sis, Control, Regulation and
Automation instruments form in
Paris a

unique confrontation

between the 900 best well-known
manufacturers from 23 Countries.
400 French, 500 Foreign Companies
covering the various techniques :

Acoustic, Automation, Chromatic,
Electronic, Electrotechnic, Flow
Control, Computing, Magnetic,
Nucleonic, Optic, Pneu-
matic, Thermic

Full information for: FRENCH TRADE SHOWS - French Chamber of
Commerce in The United States Inc. 1350 Avenue of the Americas
NEW YORK N.Y. 10019 TEL : (212) 582-4960

CIRCLE NUMBER 73

LOOKING FOR A DISTRIBUTOR NEAR YOU?

Electronic Design's GOLD
BOOK lists 5,700 distributors
with access both alphabetic,
by distributor name, and ge-
ographic by location.


When you need
information . . .

**Electronic Design's
GOLD BOOK
IS THE PLACE
TO LOOK**

NEED A COMPETITIVE EDGE? CHECK OUT WESTON POTS FOR COST DELIVERY • PERFORMANCE

EXAMPLE:

Model #830P

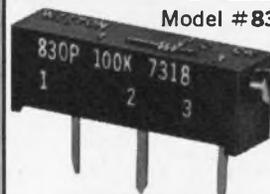

**WESTON
RECTILINEAR
3/4" CERMET
TRIMMER**

PRICE (1000 Piece Orders) **\$.91** EA.

Comparable prices — all sizes — Square
• Round • Cermet • Wirewound

WESTON

Schlumberger

WESTON COMPONENTS
ARCHBALD, PENNSYLVANIA 18403
TEL. (717) 876-1500
TWX 510 656-2902
TELEX 83-7443

CIRCLE NUMBER 74

INSTRUMENTATION

Charge amplifier works over wide range



Kristal Instrument, 2475 Grand Island Blvd., Grand Island, NY 14072. (716) 773-4150. From \$300 to \$975; stock to 2 wks.

Charge amplifier, type 5003, and range selector, type 5423, convert electrical charge signals (100 to 10^6 pC) from piezoelectric transducers into proportional voltages for direct reading on a scope or other indicating instrument. The amplifier comes with three, six or nine ranges, which can be set manually or, optionally, by remote control. Fine adjustment of the individual range is also possible to calibrate the amplifier for a specific transducer.

CIRCLE NO. 340

High-voltage pulser sells for \$965

Instrument Research Company, P.O. Box 231, Lincoln, MA 01773. (617) 897-7647. \$965; 30 days.

Model 941 power pulse generator is priced below \$1000. Featuring an output adjustable to 2 kV at load currents to 1 A, the new unit maintains a clean pulse into an essentially capacitive load. The driver features complementary TTL outputs together with an independent ± 30 -V offset and amplitude capability—a combination which permits driving all logic families directly. The 941 thereby offers four simultaneous outputs together with five modes of operation—single shot, triggered, gates, delayed and normal PRF.

CIRCLE NO. 341

Analog VOMs, move over! Here's a pocket DVM



Sencore, Inc., 3200 Sencore Dr., Sioux Falls, SD 57107. (605) 339-0100. \$124.

Pocket-portable DVM35 takes aim at portable analog VOMs. The unit features three-digit readout, 1% dc voltage accuracy, coupled with $15\text{-M}\Omega$ input impedance. Capabilities include 1-A and $10\text{-M}\Omega$ measurements plus 2000 V dc with a "times two" button on the probe that doubles all voltage ranges for expanded field use, plus increases the input impedance to $30\text{ M}\Omega$. DVM35 weighs only 1 lb with AA-size batteries. It is said to be "drop-proof" and "burn-out-proof."

CIRCLE NO. 342

Sweep generator carries low price tag



Wavetek Indiana, 66 N. 1st Ave., Beech Grove, IN 46107. (317) 783-3221. \$495; 30 days.

Model 1050A sweeper sells for less than \$500. The broadband instrument covers a frequency range of 1 to 400 MHz and has a calibrated rf output of from +10 to -60 dBm. Flatness of ± 0.25 dB is accomplished with p-i-n diode leveling and both harmonic and nonharmonic spurious signals are 30-dB below the output. Sweep linearity is 2%.

CIRCLE NO. 343

Digital temp meter comes in DIN case

Columbia Research Labs, Woodlyn, PA 19094. (215) 532-9464. \$350; 6 wks.

Model DT-103 digital temperature meter is packaged in a DIN-standard case measuring $3.780 \times 1.890 \times 3.750$ in. The instrument displays directly in degrees C or F on a 0.55-in. 3-1/2-digit display. A single platinum resistance probe covers -200 to 500 C. Accuracies range from ± 3 C over the full range to ± 1 C from -100 to 100 C.

CIRCLE NO. 344

Sig gen tunes from 1.5 to 80 MHz in one band



Logimetrics, 121-03 Dupont St., Plainview, NY 11803. (516) 681-4700. \$2275; 60 days.

Model 950A FM-AM signal generator is continuously tunable over the range of 1.5 MHz to 80 MHz. The unit offers direct 5-digit frequency readout and is said to be the lowest priced generator in its class to provide this feature. Calibrated FM deviation of 0 to 10, and 30 kHz is read directly from a meter on the front panel. FM distortion is less than 3%.

CIRCLE NO. 345


PROM copier features hexadecimal key entry

Technitrol, Inc., 1952 E. Allegheny Ave., Philadelphia, PA 19134. (215) 426-9105. \$850.

Model 107K is a new PROM programmer/copier/reader/verifier with hexadecimal keyboard for entry of data and addresses. The unit provides auto-copy between selectable minimum and maximum addresses, programs or lists addresses sequentially or randomly, verifies master to copy while reading or writing, stops on error detect, displays copy data and address in "read," and displays keyboard data and address in "write."

CIRCLE NO. 346

Make the Switch...

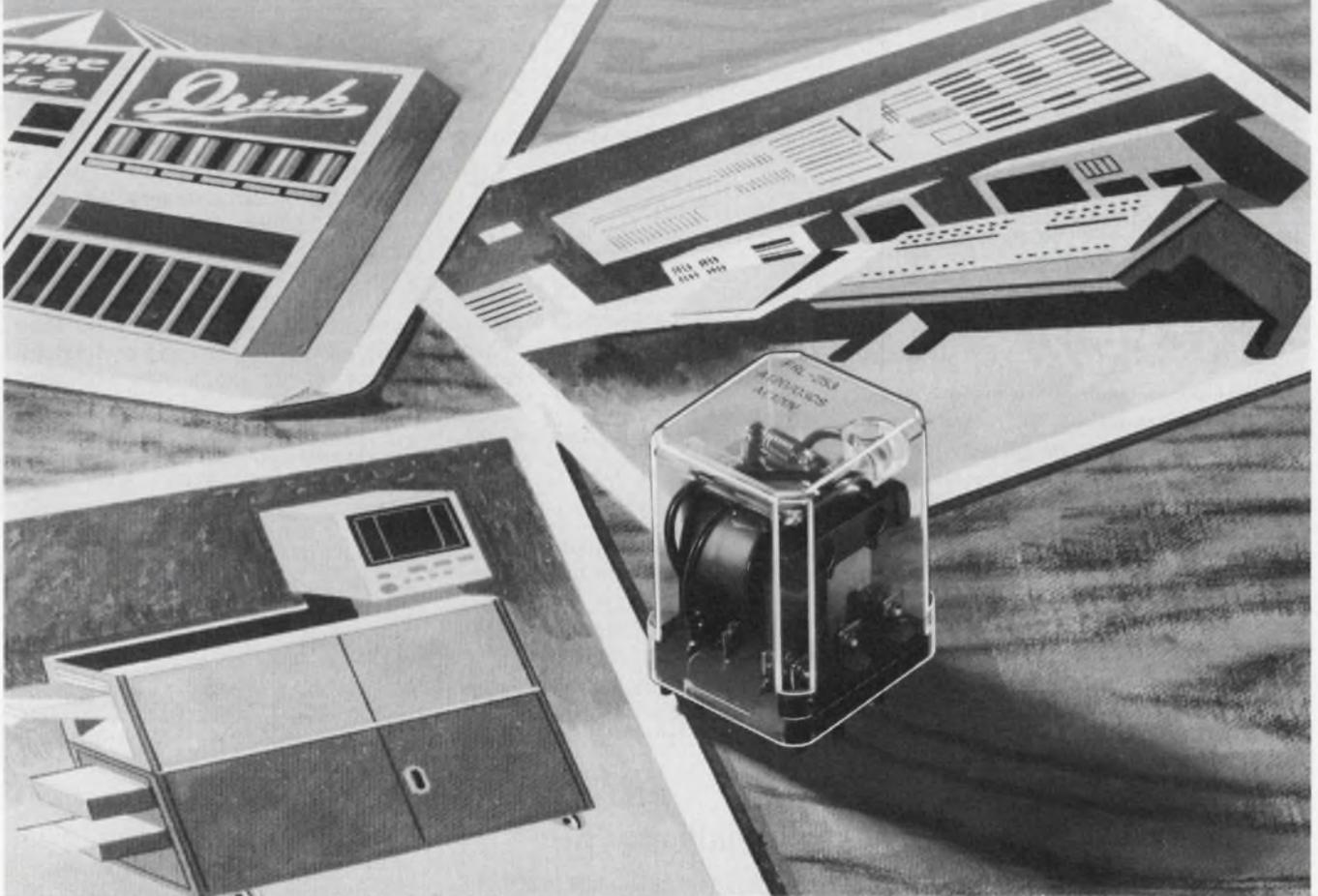

Fujitsu quality miniature power relays

Are you a maker of vending machines, control equipment, business machines, communications gear, or entertainment products? If so, then chances are you're a large consumer of miniature power relays, especially in the up-to-10-amp range. If you think about it for a minute, you're probably willing to consider an alternate source for your relays, if this maker can match the quality and performance of your present source's products, yet at a price that will spell savings for you. Well, now that you've thought about it, take a look at what Fujitsu has to offer.

Fujitsu is now marketing its FRL250-series of top quality miniature power relays. Proven and high performance, the FRL250-series is

available in basic open or enclosed models, delay models, or latching models, and all with the same wide selection of mounting hardware and convenience accessories for top-notch operation to meet your every need. You can choose either DC operation with coils rated at from 6V to 110V or AC operation of from 12V to 240V. Contact arrangements available are from 1 Form C to 3 Form C to provide the widest selection. And, of course, all relays are in full compliance with applicable electrical safety/performance standards.

Fujitsu FRL250-series miniature power relays. They're a proven alternative, fully pin compatible with leading models, and at prices that will make you wonder why you didn't think Fujitsu before.



FUJITSU LIMITED

Communications and Electronics

Marunouchi, Tokyo, Japan

For further information please contact:

■ **Components Division (Head Office):** Syuwa Onarimon Bldg., 1-1 Shinbashi 6-chome Minato-ku, Tokyo 105, Japan. Phone: Tokyo (03) 437-2111. Cable: FUJITSULIMITED TOKYO. Telex: 2422808 FT SIN J. ■ **New York Office:** 680 Fifth Avenue, New York, N.Y. 10019, U.S.A. Phone: (212) 265-5360. Telex: 23 234969. ■ **Fujitsu California, Inc.:** 1135 East Janis Street, Carson, California 90746, U.S.A. Phone: (213) 636-0858, 537-8930. Telex: 230 673387. ■ **London Office:** Norman House, 105/109 Strand, London, W.C. 2, England. Phone: 240-0461/0462. Telex: 51 22305

MAIN PRODUCTS □ Telephone Exchange Equipment □ Carrier Transmission Equipment □ Radio Communication Equipment □ Space Electronics Systems □ Electronic Computers & Peripheral Equipment □ Telegraph & Data Communication Equipment □ Remote Control & Telemetry Equipment □ Electronic Components

CIRCLE NUMBER 76

Step-by-step coverage of defense radar system design . . .

INTRODUCTION TO DEFENSE RADAR SYSTEMS ENGINEERING

James N. Constant

This all-inclusive handbook covers virtually every facet of radar technology that must be mastered in order to design a complete defense radar system. In fact, it concludes with a *step-by-step procedure for specifying and designing a complete radar system for a given application*. Separate chapters cover target characteristics; radar detection; radar receivers; radar system error model; flight of a ballistic missile; ballistic reentry trajectories; trajectory prediction; radar data processing; reflector antennas; and array antennas. Order your 15-day examination copy today! #9194, 344 pages, cloth, illustrated, \$22.95



15-DAY FREE EXAMINATION!



Hayden Book Company, Inc.
50 Essex Street
Rochelle Park, N.J. 07662

- Please send me my copy of INTRODUCTION TO DEFENSE RADAR SYSTEMS ENGINEERING to read and use for 15 days. At the end of that time, I'll send a check or money order for \$22.95, plus postage and handling, or return the book and owe absolutely nothing.
- I want to save money! I have enclosed full amount. Publisher pays postage and handling. I get a complete 15-day money-back guarantee.

Name _____
Firm _____
Address _____
City/State/Zip _____

76-15

Application Notes

Power-supply performance

How to make accurate load regulation measurements by using Kelvin four-terminal connections is covered in a bulletin. Proper metering techniques and line sources as well as thermal environment and difficulties in measuring tempco are discussed. Deltron, North Wales, PA

CIRCLE NO. 347

Audio products

How to use low-frequency wave and spectrum analyzers to measure distortion, frequency response, wow and flutter, signal-to-noise ratio and cross-talk of high-quality audio products are detailed in a 16-page brochure. Hewlett-Packard, Palo Alto, CA

CIRCLE NO. 348

Data-acquisition system

An interfacing scheme used to connect minicomputers to groups of analog transducers and voltage sensors is described in a six-page note. Circuit drawings as well as a full timing diagram for random and sequential channel operation are included. Datel Systems, Canton, MA

CIRCLE NO. 349

Arithmetic subroutine

A comprehensive, powerful new subroutine used to dynamically evaluate arithmetic expressions is described in a 52-page booklet. This subroutine, written using a modern structured programming compiler, is available to the higher order language IBM 370 programmer, enabling him to instantly enhance his system by adding sophisticated arithmetic specification to his user communications. National Institute of Health, Div. of Computer Research and Technology, Bethesda, MD

CIRCLE NO. 350

Vendors Report

Annual and interim reports can provide much more than financial-position information. They often include the first public disclosure of new products, new techniques and new directions of our vendors and customers. Further, they often contain superb analyses of segments of industry that a company serves.

Selected companies with recent reports are listed here with their main electronic products or services. For a copy, circle the indicated number.

Spectra-Strip. Interconnection devices and systems.

CIRCLE NO. 351

Aeronautical Radio (ARINC). Air-ground-air communications service, electronic switching systems and intercity communications.

CIRCLE NO. 352

Franklin Electric. Motors and package-weighing products.

CIRCLE NO. 353

S.R.C. Laboratories. Photomultiplier tubes and fluid-flow inducing devices.

CIRCLE NO. 354

Bliss & Laughlin Industries. Tools and tool kits.

CIRCLE NO. 355

Nashua. Image forming, adhesive and magnetic recording materials.

CIRCLE NO. 356

SRI. Basic and applied research.

CIRCLE NO. 357

Triangle Industries. Electrical products for construction industry, pre-insulated pipe, automatic merchandising machines and music systems, coin-operated phonographs and dollar-bill changers.

CIRCLE NO. 358

Turbodyne. Steam and gas turbine systems and electrical equipment.

CIRCLE NO. 359

Union Carbide. Chemicals and plastics; gases, metals and carbons, and consumer and related products.

CIRCLE NO. 360

Electronic Design

Advertising Sales Staff

Tom W. Carr, Sales Director
Jean Bunfield, Sales Coordinator

Rochelle Park, NJ 07662

Robert W. Gascoigne
Daniel J. Rowland
Thomas P. Barth
George Mortimer
Stan Tessler
50 Essex St.
(201) 843-0550
TWX: 710-990-5071

Philadelphia

Thomas P. Barth
(201) 843-0550

Boston 02178

Gene Pritchard
P.O. Box 379
Belmont, MA 02178
(617) 489-2340

Chicago 60611

Thomas P. Kavooras
Berry Connor, Jr.
Harry Marshall
200 East Ontario
(312) 337-0588

Cleveland

Thomas P. Kavooras
(312) 337-0588

Los Angeles 90045

Stanley I. Ehrenclou
Burt Underwood
Neil Canavin
8939 Sepulveda Blvd.
(213) 641-6544

Texas

Burt Underwood
(213) 641-6544

San Francisco 94040

Robert A. Lukas
3579 Cambridge Lane
Mountain View, CA 94040
(415) 965-2636

London, Amsterdam, Tokyo, Seoul

Malcolm M. Thiele
Wood Cottage, Shurlock Row
Reading RG 10-QE, England
Phone: Shurlock Row 302 & 619
S.T.D. 073 581

Sanders, B. V.
Raadhuisstraat 24
Graft-De Ryp, Holland
Phone: 02997-1303
Telegrams: Euradteam-Amsterdam

Haruki Hirayama
Electronic Media Service
5th Floor, Lila Bldg.,
4-9-8 Roppongi
Minato-ku, Tokyo, Japan
Phone: 402-4556
Cable: Electronicmedia, Tokyo

Mr. O-kyu Park, President
Dongbo Intl Corp.—
World Marketing
C.P.O. Box 4010
Seoul, Korea
Tel. 76-3910/3911
Cable: DONGBO SEOUL
Telex: EBKOREA K27286

ABP

BPA

HEATH

Schlumberger

OSCILLOSCOPES

with MORE VALUE for your dollar

Today's design engineer needs more than just a "visual voltmeter" on his bench. So Heath developed a line of scopes that offers more performance per dollar than the industry has seen in years. There's sure to be a Heath scope for your application...at a price that satisfies the most value-conscious engineer. Compare Heath specs and price before you buy...learn about quality that counts.



New Heath/Schlumberger SO-4550 Dual-Trace Scope

- 10-MHz scope with brighter trace & faster writing speed
- Full mu-metal shield to eliminate display error from electromagnetic interference
- Fully-regulated high voltage power supply

Write for your free copy of our latest

FREE

Assembled Instruments Catalog.

Heath Company
Dept. 511-150
Benton Harbor,
Michigan 49022

Heath/Schlumberger...pioneers in value-proven instrumentation

EK-481



CIRCLE NUMBER 81

Meet the top new analyzer.



Quan-Tech introduces a high-frequency wave and spectrum analyzer with a range of 1 KHz to 1.5 MHz.

The Model 2525 is a new, high performance Wave and Spectrum Analyzer with many features including electronic sweep. This portable unit offers unequalled capabilities for accurate harmonic measurements, fourier amplitude analysis of

complex signals and spectral density analysis of random signals.



Quan-Tech
Division of SCIENTIFIC-ATLANTA, INC.

RANDOLPH PARK WEST, ROUTE 10, RANDOLPH TOWNSHIP, NEW JERSEY 07801
PHONE (201) 361-3100 TWX 710-987-7946

CIRCLE NUMBER 82

New Literature



Thumbwheel switches

Photographs, descriptions, specifications, truth tables and mounting instructions of thumbwheel switches are offered in an eight-page catalog. C&K Components, Watertown, MA

CIRCLE NO. 361

IC sample/hold device

Technical specifications for the Model SHM-IC-1, an integrated circuit sample-and-hold device, are given in a four-page brochure. A general description, block diagram and mechanical specifications are included. Datel Systems, Canton, MA

CIRCLE NO. 362

Power supplies

How you can have your own individual power supply by selecting submodular units is illustrated in a brochure. Output voltages, typical output currents and prices are itemized for each model. Power/Mate, Hackensack, NJ

CIRCLE NO. 363

Measurement systems

A 112-page book contains all published data sheets on the HP 9600 measurement and control systems, networks, software and peripherals. Hewlett-Packard, Palo Alto, CA

CIRCLE NO. 364

Rf transistors

A 16-page rf communications transistor catalog contains product information for both 12 and 28 V devices, at specific frequencies, by application from 2 MHz to 1 GHz. Also included is a competitive package cross-reference and an rf transistor cross-reference. Solid State Scientific, Montgomeryville, PA

CIRCLE NO. 365

Proximity switches

Self-contained industrial proximity switches are highlighted in a 16-page brochure. It contains application drawings, product listings, simplified ordering guides, electrical and operating characteristics, drift and sensitivity charts, circuit diagrams, schematics and mounting dimensions. Micro Switch, Freeport, IL

CIRCLE NO. 366

Digital data processor

The CP70A second generation digital data processor is pictured, described and specified in an eight-page brochure. In-depth discussion is devoted to the nature of and uses for the many standard programs available. California Instruments, San Diego, CA

CIRCLE NO. 367

Discrete semiconductors

A 112-page discrete semiconductor guide contains technical specifications and application data on field-effect transistors, dual field-effect transistors and dual bipolar transistors. The guide groups products by application with a comparison table of key parameters for each device. Intersil, Cupertino, CA

CIRCLE NO. 368

Analog IC designs

"101 Analog IC Designs," a 150-page book, contains practical designs for amplifiers, comparators, current sources, flip-flops, gain control circuits, gates, op amps, oscillators, phase detectors, PLLs, Schmitt-triggers, timers and voltage regulators. The book costs \$3 prepaid. Interdesign, 1255 Reamwood Ave., Sunnyvale, CA 94086

INQUIRE DIRECT

Electronic Design

ELECTRONIC DESIGN's function is:

- To aid progress in the electronics manufacturing industry by promoting good design.
- To give the electronic design engineer concepts and ideas that make his job easier and more productive.
- To provide a central source of timely electronics information.
- To promote communication among members of the electronics engineering community.

Want a subscription? ELECTRONIC DESIGN is sent free to qualified engineers and engineering managers doing design work, supervising design or setting standards in the United States and Western Europe. For a free subscription, use the application form bound in the magazine. If none is included, write to us direct for an application form.

If you do not qualify, you may take out a paid subscription for \$30 a year in the U.S.A., \$40 a year elsewhere. Single copies are \$1.50 each.

If you change your address, send us an old mailing label and your new address; there is generally a postcard for this bound in the magazine. You will have to requalify to continue receiving ELECTRONIC DESIGN free.

The accuracy policy of ELECTRONIC DESIGN is:

- To make diligent efforts to ensure the accuracy of editorial matter.
- To publish prompt corrections whenever inaccuracies are brought to our attention. Corrections appear in "Across the Desk."
- To encourage our readers as responsible members of our business community to report to us misleading or fraudulent advertising.
- To refuse any advertisement deemed to be misleading or fraudulent.

Microfilm copies are available of complete volumes of ELECTRONIC DESIGN at \$19 per volume, beginning with Volume 1, 1952 through Volume 20. Reprints of individual articles may be obtained for \$3.00 each, prepaid (\$.50 for each additional copy of the same article) no matter how long the article. For further details and to place orders, contact the Customer Services Department, University Microfilms, 300 North Zeeb Road, Ann Arbor, Michigan 48106 telephone (313) 761-4700.

Want to contact us? If you have any comments or wish to submit a manuscript or article outline, address your correspondence to:

Editor
ELECTRONIC DESIGN
50 Essex Street
Rochelle Park, N.J. 07662

NOW! PM and SHUNT-WOUND adjustable speed drive systems



CDC-PM describes PM systems, 1/12-1/4 Hp. 12 pages, 32 drawings, photos and tables.



CDC-SH describes shunt-wound systems, 1/50-1/4 Hp. 16 pages, 51 photos, drawings and tables.

... from Bodine and Bodine Distributors

Designed and built by Bodine to give you *perfectly matched* speed/torque control characteristics—provide reliability and performance you might expect only from far more costly and complex systems.



Send for catalogs today.

Bodine Electric Company, 2528 W. Bradley Place, Chicago, IL 60618


CIRCLE NUMBER 77



We offer the following for OEM's producing their own keyboards.

- Keyswitches in 3 sizes for 1/2", 5/8" or 3/4" centers
- Gold Bar mechanical contacts or sealed contacts
- Front panel relampable lighted models
- Single and double pole contacts including NC
- Alternate action models
- Doubleshot molded keytops for 3/4" or 5/8" mounting
- Easy change legend systems
- 100,000 pc. quantity prices as low as \$0.19 each

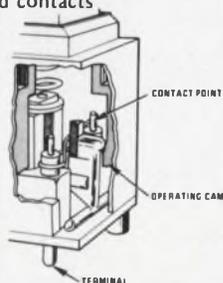Letterhead request or phone call brings free sample switch w/keytop.



MECHANICAL ENTERPRISES, INC.
8000 Forbes Place Springfield, Virginia 22151
(703) 321-8282 TWX 710-832-0942

In Germany - NEUMÜLLER GMBH, MUNICH
In U.K. - TEKDATA Ltd., STOKE-ON-TRENT

CIRCLE NUMBER 78

ELECTRONIC DESIGN 7, March 29, 1976

Bicentennial Issue

Electronic Design 4

200 YEARS OF PROGRESS



\$4

JUST

SUPPLY
LIMITED

We've saved a limited number of copies of the unique 254-page February 16th Bicentennial issue of *Electronic Design*. It traces the historic and technological developments of the electronics industry from the Colonial period to today.

In a message from the White House published in the Bicentennial issue, President Ford commends the issue as "a special part" of our nation's 200th anniversary.

If you'd like an extra copy as a memento of this historic event, we'll be happy to provide it at \$4.

Hurry! When the supply runs out you'll have to wait another hundred years for anything like it!

Bicentennial Issue Electronic Design

Hayden Publishing Company, Inc.
50 Essex St., Rochelle Park, N.J. 07662


Please send me ____ copy (copies) of *Electronic Design's* February 16 Bicentennial issue at \$4 each. I enclose my check for _____.

Name _____

Title _____

Company _____

Address _____

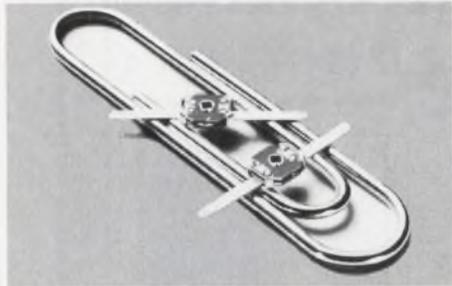

Thin-Trim variable capacitors provide a reliable means of adjusting capacitance without abrasive trimming or interchange of fixed capacitors. Series 9401 has high Q's and a range of capacitance values from 0.2-0.6 pf to 3.0-12.0 pf and 250 WVDC working voltage. Johanson Manufacturing Corporation, Boonton, New Jersey (201) 334-2676.

THIN-TRIM CAPACITORS


181



SYNCHRO TO BCD CONVERTERS: 3 or 4 decade, unipolar or bipolar output, adjustable scale factor, ± 6 or ± 30 minute accuracy, 60 or 400 Hz input, zero offset adjustment, module 2.6 x 3.1 x .82" H. Unit Price from \$395 ea. Other CCC products are Synchro to Digital or DC, Digital or DC to Synchro Converters, Solid State C. T.'s or CDX's, and Absolute Encoders. Send for Free Catalog & Application Notes. Computer Conversions Corp., East Northport, N.Y. 11731 (516) 261-3300.

SYNCHRO TO DIGITAL


184

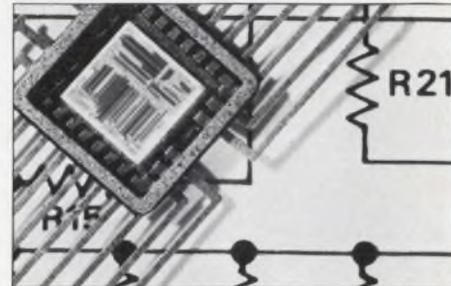

Hi-Rel 12 Bit Ladder Network: Added to the industry's most complete standard ladder network product line is the AD850/U/F/883. The ladder is a 12 bit binary current network for user configured avionics systems where minimum space, weight and reliability are important. Accuracy is $\frac{1}{2}$ LSB of 12 bits. Price is \$50.00 in 100's. Analog Devices, Norwood, Mass. 02062 617-329-4700.

HI-REL 12 BIT LADDER NETWORK

187

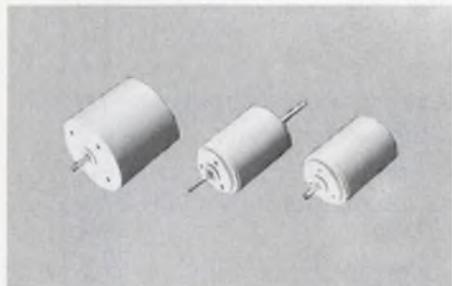

MINIATURE IRONLESS ROTOR DC MOTORS offer efficiencies to 80%, low inertia, rapid response and high starting torque. 24 and 12 VDC models available. Motor time constants are 17 and 23 MS respectively. Rotor torque is 100 and 50 gcm and starting torque 600 and 230 gcm, respectively. 12 VDC units can be ordered with either a single or extended double shaft. Tach versions also available. For reel and capstan drives, chart and pen drives, etc. North American Philips Controls Corp., Cheshire, Conn. 06410. (203) 272-0301.

IRONLESS ROTOR


182



Basic Electricity & Basic Electronics by Van Valkenburgh, Nooger & Neville, Inc. Derived from the COMMON-CORE Training Program initially developed for the U.S. Navy. Thorough, comprehensive coverage. Available in separate paperbacks or cloth volume. Write for FREE brochure. Hayden Book Co., Inc., 50 Essex St., Rochelle Pk, N.J. 07662 (201) 843-0550.

TRAINING TEXT


185

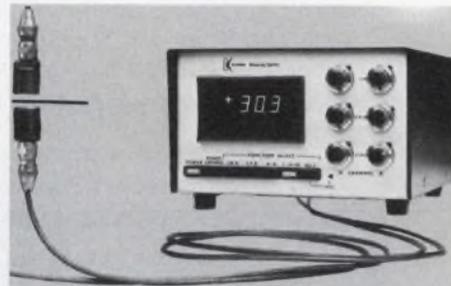

New Electronic Gage, Easy To Use. Thickness, Alignment . . . diameter or deviation measurements, concentricity, orbit tracing, etc. Accuracy up to \pm microinches (\pm 0.001 inch), resolution \pm 10 microinches. Utilizes non-contacting inductive measuring techniques—unaffected by oil, grease, or water. Replaces LVDT, air gage, dial indicator, micrometer, \$1,995. Ask for information on KD-2602-2S. Kaman Sciences Corporation, P.O. Box 7463, Colorado Springs, Colorado 80933. (303) 599-1500

ELECTRONIC GAGE


188

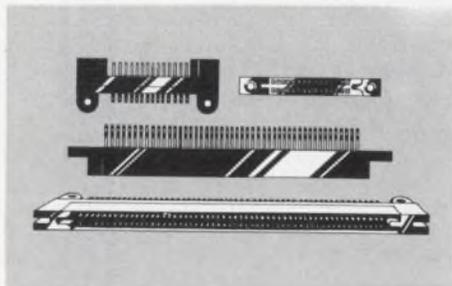

The AMP Box Connector is ideal for systems with up to several hundred contacts. It features an innovative "box" contact design that accepts square, rectangular, round, or formed channel pins. Available in many pin and receptacle configurations and with external keying. From the people who offer technical assistance at its best: AMP Incorporated, Harrisburg, PA (717) 564-0100.

AMP BOX CONNECTOR

183

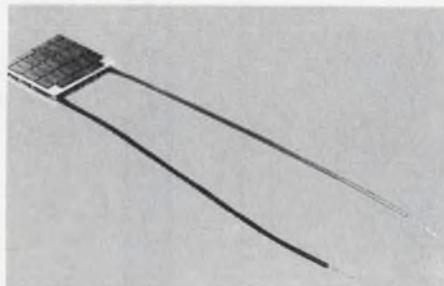

THERMOELECTRIC MODULE, a remarkable value for only \$20 (ppd.), can be used in water coolers, small refrigerators, hot and cold temperature sources, spot cooling for electronic components and other applications. Operates at 3.5 VDC, 8.5 amps, ΔT Max at Qc Zero is 60°C, Th is 50° C, Qc Max. at ΔT Zero is 19 watts, Max. Op. temp is 100° C. Price includes Thermoelectric handbook. CAMBION, 445 Concord Avenue, Cambridge, MA 02138.

THERMOELECTRIC MODULE

186



Model 9201 Power Switch, miniature DPDT toggle is designed to meet international dimensional/electrical specs. Electric life: 25,000 make-and-break cycles at full load. Contact rating: 6 amps with resistive load @ 120 VAC or 28 VDC. Free Engineering Sample on request. C&K Components, Inc., 103 Morse St., Watertown, MA 02172, (617) 962-0800.

POWER SWITCH


189



A Software Library, developed and maintained by users to provide access to the programming efforts of other handheld, programmable calculator users. Viola Grange invites your programs. Contributors receive free the volume in which they are published. Vol 1 is a source containing practical formulae, skillful programming, and imaginative treks into mathematics and engineering. Published quarterly. \$6. The Viola Grange, Rt. 2, Box 965, Estacada, OR 97023

APPLICATIONS PROGRAMS


190

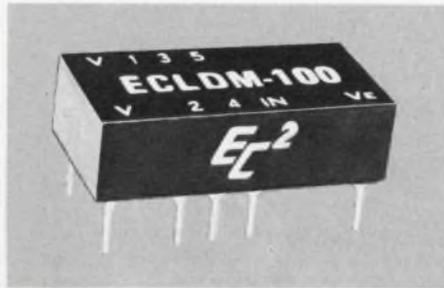

EC's new ECL compatible Logic Delay Module features ECL input and outputs; 16-pin DIP package (.250 high); precise delays from 25ns to 250ns; and with 20% taps—each isolated with 70 ECL dc. fan-out capacity. Engineered Components Company, P.O. Box Y, San Luis Obispo, CA 93406 (805) 544-3800.

ECL LOGIC DELAY MODULE

193

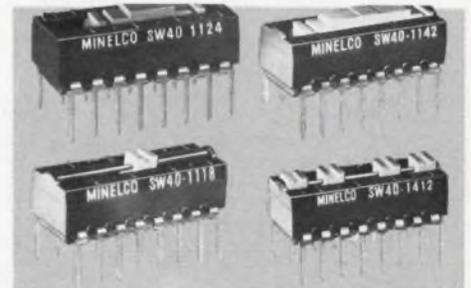

New Multi-Slide, Multi Circuit DIP Switches . . . wide variety of switching combinations. Freq. Range Sel. test pt. monitoring, select on test, atten. level selection, program addressing, cross pt. switching, 2 poles, 4 posit., 4 poles, 2 posit.; 1 pole, 8 posit.; 4 poles 2 posit. (var.) True "break-before-make"; spring-loaded double bearing detent; gold/nickel contact plating; self-cleaning wiping action for consistent performance. Minelco Div., Gen. Time, 135 S. Main St., Thomaston, CT 06787 (203) 283-8261

DIP SWITCHES

196



The **Model 1000 Directional Wattmeter** is an accurate and portable insertion RF wattmeter using plug-in detectors and quick-change RF connectors, which measure forward & reflected CW power. The Model 1000 features a large scale, easily read meter movement. Standard ranges are 5 watts to 10,000 watts; frequency range is 2 to 1,000 MHz. TUCKER ELECTRONICS CO., PO BOX 1050, GARLAND, TEXAS 75040 (800) 527-4642 (In Texas Call (214) 348-8800)

RF WATTMETER

191



Resident COBOL compiler system for the 8080 microprocessor. Runs on any 16K RAM system. With a few exceptions, the level of COBOL offered (relative to ANSI X3.23-1974) is: nucleus level 2, table handling level 2, sequential, relative and indexed I-O level 1, and sort-merge level 1. Reference manual \$6. Also available: complete disk operating system including a powerful job control language, an assembler, a text editor, a debugging system, file utility routines. Mini-Software Inc., Box 7438, Alexandria, VA 22307.

COBOL COMPILER

194

FREE:
from the
NO. 1
SOURCE

Power Supply and DC/DC Converter Catalog

Application Information

- Power Supplies
- DC/DC Converters
- Microprocessor Supplies
- Pricing
- Specifications
- Discounts

SEMICONDUCTOR CIRCUITS, INC.
306 RIVER STREET • HAVERHILL, MASSACHUSETTS 01830
TEL (617) 373-9104

CONVERTER CATALOG


197



Introduction To Defense Radar Systems Engineering. Excellent introduction and practical reference to radar systems design and applications. #9194, 260 pp., \$22.95. Circle the Info Retrieval No. to order 15-day exam copy. When billed, remit or return book with no obligation. Hayden Book Co., 50 Essex St., Rochelle Park, N.J. 07662

RADAR SYSTEMS


192

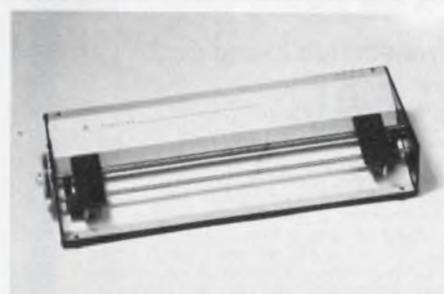

A FORMS FEED TRACTOR slewing at 37 lps with 140 in/oz of torque. Electronic vernier adj. sets TOP OF FORM: quarter, single & double line feed in forward or reverse are standard. Options of PERF. SKIP, PAPER FEED TIME OUT, END OF FORM SENSING & SELECTABLE TOP OF FORM are available. The design assures operating simplicity, long life and trouble free performance in heavy duty operation. TRAKTEX 45 Ryegate Terr. Monroe, Ct. 06468 203-261-9011

FORMS FEED TRACTOR

195

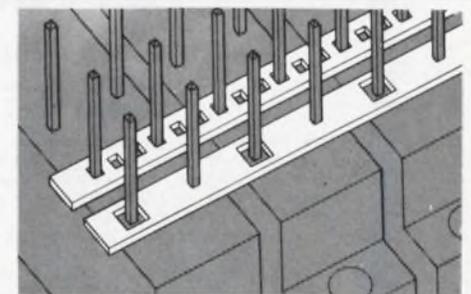

STRIP/BUS BY ROGERS. Low Cost Bussing Systems; easy installation, reliable solder joints; greater pin exposure. Write or call for details. Rogers Corporation, Rogers, CT 06263. Phone (203) 774-9605.

STRIP/BUS

198

Advertiser's Index

| Advertiser | Page |
|--|-----------|
| AMP, Incorporated | 126 |
| AVX Ceramics | 24 |
| Abbott Transistor Laboratories, Inc. | 6 |
| Advanced Micro Devices | 54, 55 |
| Ailtech, A Cutler-Hammer Company | 113 |
| Allen Bradley Co. | 1 |
| Ampex Memory Products Division | 77 |
| Amplifier Research Corporation | 106 |
| Analog Devices, Inc. | 126 |
| Arnold Magnetics Corp. | 118 |
| Belden Corporation | 4, 5 |
| Bodine Electric Company | 125 |
| Bourns, Inc., Trimpot Products Division | Cover II |
| Buckbee Mears Company | 65 |
| C & K Components, Inc. | 126 |
| CTS Corporation | Cover III |
| Cambion | 126 |
| Cambridge Thermionic Corporation | 113 |
| Centre Engineering | 115 |
| Centralab, The Electronics Division of Globe-Union, Inc. | 117 |
| Circuit Technology, Inc. | 109 |
| Computer Conversions Corp. | 126 |
| Computer Products, Inc. | 109 |
| Continental Connector Corporation | 72 |
| Continental Specialties Corporation | 38 |
| Curtis Adams | 127 |
| Data General Corporation | 51 |
| Data Precision Corporation | 91 |

| Advertiser | Page |
|---|---------------|
| Data Translation, Inc. | 115 |
| Dialight, A North American Philips Company | 45 |
| EECO | 23 |
| Electronic Design | 116, 125, 129 |
| Electronic Molding Corporation | 64 |
| Elxon Power Systems | 41 |
| Engineered Components Company | 127 |
| Fairchild Micro Systems Division of Fairchild Camera and Instrument Corporation | 79 |
| Fujitsu Limited | 121 |
| Gold Book, The | 110, 111 |
| Gould Inc., Instrument Systems Division | 113 |
| Hayden Book Company, Inc. | 122, 126, 127 |
| Heath Company | 123 |
| Heinemann Electric Company | 37 |
| Hewlett-Packard | 9 thru 18 |
| Hughes Aircraft Company, Microelectronic Products Division | 35 |
| ITT Cannon, A Division of International Telephone and Telegraph Corporation | 97 |
| Intech, Incorporated | 108 |
| Intelligent Systems Corp. | 106 |
| International Rectifier | 78 |
| Johanson Manufacturing Corp. | 126 |

| Advertiser | Page |
|--|----------|
| Johnson Company, E. F. | 39 |
| Kaman Sciences Corp. | 126 |
| Kepeco, Inc. | 42 |
| Litronix, Inc. | 103 |
| MCG Electronics | 130 |
| Mechanical Enterprises, Inc. | 125 |
| *Membrain Ltd. | 2 |
| Mepco/Electra, Inc. | 40 |
| Mesucora 76 | 119 |
| Micro Devices Corp. | 107 |
| Micro Electronic Systems, Inc. | 117 |
| Minelco Division/General Time Corp. | 127 |
| Mini-Software, Inc. | 127 |
| Monsanto, United Systems Corporation Subsidiary | 86 |
| Mos Technology, Inc. | 67 |
| Motorola Semiconductor Products, Inc. | 25 |
| National Semiconductor Corporation | 31 |
| North American Philips Controls Corp. | 107, 126 |
| Optron, Inc. | 7 |
| *Philips Industries, Electronic Components and Materials Division | 114A |
| *Philips Instrumentation Recording | 114B-C |
| Pioneer Magnetics, Inc. | 73 |
| Potter & Brumfield, Division of AMF, Incorporated | 29 |
| Power/Mate Corp. | 116 |
| Power Tech, Inc. | 100 |
| Precision Monolithics, Incorporated | 33 |
| Pro-Log Corporation | 19 |
| Quan-Tech, Division of Scientific Atlanta, Inc. | 123 |
| RCA Solid State | Cover IV |
| Ramtek Corp. | 90 |
| Raytheon Company, Ocean Systems Center | 104 |
| Rental Electronics, Inc. | 20 |
| *Rifa of Sweden | 114D |
| Rogers Corporation | 127 |
| Semiconductor Circuits, Inc. | 127 |
| Simpson Electric Company | 27 |
| *Sodeco SAIA Ltd. | 20 |
| Sola Electric, Division of Sola Basic Industries | 114 |
| Spectrol Electronics Corporation | 66 |
| Sprague Electric Company | 53 |
| Stahlin Co., Inc. | 117 |
| TRW Power Semiconductors, an Electronic Components Division of TRW, Inc. | 87 |
| Technical Communications, Inc. | 48 |
| Technical Materials, Inc. | 105 |
| Teledyne Crystalonics | 99 |
| Teledyne Relays, A Teledyne Company | 2 |
| Teledyne Semiconductor | 56 |
| Tenney Engineering, Inc. | 107 |
| Texas Instruments, Incorporated | 46, 47 |
| Traktex | 127 |
| Triplett Corporation | 93 |
| Tucker Electronics Co. | 127 |
| United Systems Corporation, A Subsidiary of Monsanto | 86 |
| Victoreen Instrument Division, Sheller-Globe Corporation | 95 |
| Weston Components | 119 |

*Advertisers in non-U.S. edition

classified ad

LINEAR CIRCUIT DESIGN ENGINEER

Want the whole challenge from design to end use?
COME TO EAI...

It's the world's leading producer of analog/hybrid computer systems that's providing this comprehensive opportunity—requiring a BSEE with experience in linear and digital circuit design, with emphasis in the linear area.

Your assignments will cover design, development and testing of precision operational amplifier circuitry as utilized in analog/hybrid computers—inclusive of integrators, multipliers, analog switching matrices, multi-variable function generators, A

to D and D to A converters, sample hold amplifiers and power supplies. In addition, you'll be involved with the end use of circuitry, employing the system of which it is a part.

Position offers fully paid relocation to our corporate headquarters in desirable Jersey Shore area, an excellent starting salary plus full package of company benefits. Write and/or send resume, in confidence, with salary history, to: B. Evenson, Corporate Staffing.



ELECTRONIC ASSOCIATES, INC.

Dept. ED329, West Long Branch, New Jersey 07764
An Affirmative Action Equal Opportunity Employer-Female/Male

MAIL TO:

Electronic Design

P.O. BOX 13803, PHILADELPHIA, PA. 19101

FREE SUBSCRIPTION APPLICATION

Do you wish to receive (continue to receive)

ELECTRONIC DESIGN? Yes No

Date:

Signature: Does not obligate me or my company

I wish to receive (do not wish to receive) other solicitations. Yes No

ALL SUBSCRIBERS: Please fillout completely, the name and address portion, even if the information on your label is the same. (For prompt, accurate processing remember to affix label in the space provided above.) Do not use periods, commas etc.

To qualify please answer all questions carefully. Independent consultants must attach business card.

MR
MS

| | | | | | | | | | |
|-----------|--|--|--|--|------------------|--|--|--|--|
| | | | | | | | | | |
| Area Code | | | | | Office Telephone | | | | |

| | | | |
|--|-------------|--------------------|----------------------|
| 1st Initial | 2nd Initial | Last Name | Title |
| Company Name (Do not abbreviate if possible) | | Division | |
| Parent Company (if subsidiary) (Do not abbreviate if possible) | | | |
| Department | | Internal Mail Code | |
| Company Street Address or P.O. Box No. | | | |
| Company City | | State/Country | Zip Code/Postal Code |
| Home Address | | | |
| Home City | | State/Country | Zip Code/Postal Code |

8 Products you specify or authorize purchase of:
(Check all codes that apply.)

| | |
|--|--|
| <input type="checkbox"/> 1 Resistors and Capacitors | <input type="checkbox"/> 12 Computer Peripherals |
| <input type="checkbox"/> 2 Connectors | <input type="checkbox"/> 13 Computer Components |
| <input type="checkbox"/> 3 Switches and Relays | <input type="checkbox"/> 14 Cabinets and Enclosures |
| <input type="checkbox"/> 4 Function Modules: Op Amps, Converters, etc. | <input type="checkbox"/> 15 Panel Meters, Analog or Digital |
| <input type="checkbox"/> 5 Potentiometers | <input type="checkbox"/> 16 Readout and Display Devices |
| <input type="checkbox"/> 6 Test and Measurement Equipment | <input type="checkbox"/> 17 Rotating Components |
| <input type="checkbox"/> 7 Computers, Medium and Large | <input type="checkbox"/> 18 Cooling Products |
| <input type="checkbox"/> 8 Electronic Power Supplies | <input type="checkbox"/> 19 Printed Circuits |
| <input type="checkbox"/> 9 ICs and Semiconductors | <input type="checkbox"/> 20 Calculators |
| <input type="checkbox"/> 10 Microwave Devices | <input type="checkbox"/> 21 Indicators including LEDs |
| <input type="checkbox"/> 11 Minicomputers | <input type="checkbox"/> 22 Materials, Potting and Stripping |
| | <input type="checkbox"/> 23 Communications Equipment |

7 Please write in box total number (other than self) to be served by this subscription at this address and list individuals and their titles below. If no other person is served please indicate "0" in the box at left.

| Name (Please Print) | Title |
|---------------------|-------|
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |

This questionnaire conforms to the guidelines of the Business Publication Audit of circulation for eliciting comparable data. The publisher reserves the right to serve only those individuals who qualify for a free subscription.
ELECTRONIC DESIGN is sent free to qualified engineers and engineering managers doing work, supervising design or setting the standards in the United States and Western Europe.

9 Do you specify or buy through distributors?
 YES NO

10 Minicomputers at this address:

| | Model | Qty. | Model | Qty. |
|----------------------------|-------|------|-------|------|
| 3 Cincinnati Milacron | | | | |
| C Computer Automation | | | | |
| D Control Data | | | | |
| E Data General | | | | |
| F Digital Equipment | | | | |
| I General Automation | | | | |
| K Hewlett Packard | | | | |
| M Honeywell | | | | |
| O IBM | | | | |
| N Interdata | | | | |
| 7 Microdata | | | | |
| Modular Computer | | | | |
| ROLM | | | | |
| V Systems Engineering Labs | | | | |
| 9 Texas Instruments | | | | |
| x Varian | | | | |
| Other | | | | |

1 Title: (Insert letter)

| | |
|---------------------------------|--------------------|
| A President | J Project Engineer |
| B Vice President | K Senior Engineer |
| C Vice President of Engineering | L Group Leader |
| D Technical Director | M Dept. Head |
| E Chief Engineer | N MTS |
| F Principal Engineer | O Engineer |
| G Research Director | P Consultant |
| H Section Head | R Scientist |
| | S Physicist |

2 Your principal job function: (Insert code)

- General and Corporate Management
- Design and Development Engineering (circuits, components, equipment systems)
- Engineering Services (evaluation, quality control, reliability, standards, test)
- Basic Research
- Manufacturing and Production
- Engineering Assistants (draftsman, lab assistant, technician)
- Purchasing and Procurement
- Marketing including Sales
- Other Personnel (explain)

3 Plant Your own work
The primary end product (or service performed) at your plant, and the product (or service) that is your own work. (Insert code in each box even if the same)

| | |
|---|---|
| A Large Computers | A Large Computers |
| B Mini-Computers | B Mini-Computers |
| C Computer Peripheral Equipment | C Computer Peripheral Equipment |
| D Data Processing Systems (Systems Integration) | D Data Processing Systems (Systems Integration) |
| T Office and Business Machines | T Office and Business Machines |
| E Test, Measurement and Instrumentation Equipment | E Test, Measurement and Instrumentation Equipment |
| F Communications Systems and Equipment | F Communications Systems and Equipment |
| H Navigation and Guidance Systems and Equipment | H Navigation and Guidance Systems and Equipment |
| J Consumer Entertainment Electronic Equipment | J Consumer Entertainment Electronic Equipment |
| G Consumer Electronic Appliances | G Consumer Electronic Appliances |
| N Other Consumer Electronics | N Other Consumer Electronics |
| K Industrial Controls, Systems and Equipment | K Industrial Controls, Systems and Equipment |
| L Components and Sub Assemblies | L Components and Sub Assemblies |
| M Materials and Hardware | M Materials and Hardware |
| O Aircraft, Missiles, Space and Ground Support Equipment | O Aircraft, Missiles, Space and Ground Support Equipment |
| P Oceanography and Support Equipment | P Oceanography and Support Equipment |
| R Medical Electronics | R Medical Electronics |
| U Industrial Companies within the OEM incorporating Electronic Equipment in their end product, not elsewhere classified | U Industrial Companies within the OEM incorporating Electronic Equipment in their end product, not elsewhere classified |
| V Independent Research, Test and Design Laboratory and Consultant. (Only if you are not connected with a manufacturing company.) | V Independent Research, Test and Design Laboratory and Consultant. (Only if you are not connected with a manufacturing company.) |
| X Government Agency and Military | X Government Agency and Military |
| 2 Industrial Companies using and/or incorporating any Electronic products in their manufacturing, research or development activities. | 2 Industrial Companies using and/or incorporating any Electronic products in their manufacturing, research or development activities. |
| 1 Commercial Users of Electronic Equipment | 1 Commercial Users of Electronic Equipment |
| 3 Distributor | 3 Distributor |
| 4 School, University or Library | 4 School, University or Library |
| 5 Other (explain) | 5 Other (explain) |

4 Your design function: (Insert each letter that applies)

- do electronic design or development engineering work
- supervise electronic design or development engineering work
- set standards for, or evaluate electronic design components, systems and materials

5 Your principal responsibility: (Insert code)

| | |
|-------------------------------------|---------------|
| 1 Management other than Engineering | 3 Engineering |
| 2 Engineering Management | |

6 Please estimate: (Insert letter)

The number of electronic engineers at this address:
(A) 1 (B) 2-5 (C) 6-19 (D) 20-49 (E) 50-99
(F) 100-249 (G) 250-499 (H) 500-999 (J) Over 1000

Use this form for Change of Address or New Subscription Only.

For change of address only attach old mailing label here.

Circuit Savers



Here's positive low cost protection for your IC's, transistors, power supplies and pc cards.

The LVC-1A crowbar switches to a short circuit whenever the voltage across it exceeds a specified level.

Any trip voltage level between 4.7V and 200V \pm 10% can be selected. The unit will handle a peak current of 50 Amps (8rms) and 3A continuously. MIL Temperature range. Call Mike Coyle for applications assistance.

Full line of protection modules for every hi-lo voltage/current requirement. Write or call for Catalog 749.

279 Skidmore Road
Deer Park, New York 11729
Telephone: 516 - 586-5125

MCG Electronics

CIRCLE NUMBER 85

Please Help Children Live

Research is our only weapon against childhood cancer.

St. Jude Children's Research Hospital, which is non-sectarian, is the largest childhood cancer research center in the world.

Please join in the fight against childhood cancer.

Send your special gift now.



ST. JUDE CHILDREN'S RESEARCH HOSPITAL

Danny Thomas, Founder

Send contributions to:
MEMPHIS, TENN. 38101

This space donated by publication

Product Index

Information Retrieval Service. New Products, Evaluation Samples (ES), Design Aids (DA), Application Notes (AN), and New Literature (NL) in this issue are listed here with page and Information Retrieval numbers. Reader requests will be promptly processed by computer and mailed to the manufacturer within three days.

| Category | Page | IRN | Category | Page | IRN |
|--------------------------------|------|-----|------------------------------------|------|-----|
| Components | | | RAMs | 102 | 306 |
| capacitors | 39 | 19 | shift registers | 102 | 307 |
| capacitors, ceramic | 115 | 66 | synthesizer | 102 | 308 |
| chips | 24 | 10 | Microprocessor Design | | |
| keyboards | 121 | 78 | assembler, cross | 50 | 553 |
| motors, dc | 107 | 54 | computer, micro | 49 | 552 |
| potentiometers, trimming | 11 | 284 | computer, 8080 | | |
| relay, solid-state | 37 | 17 | compatible | 52 | 556 |
| relays | 29 | 13 | emulator, μ P | 50 | 554 |
| relays, TO-5 | 2 | 3 | instrument | 49 | 551 |
| relays, sensitive | 118 | 336 | microprocessor | 79 | 38 |
| resistor networks | 117 | 69 | microprocessors | 19 | 7 |
| resistors | 1 | 2 | tool, system development | 52 | 555 |
| resistors | 41 | 21 | Modules & Subassemblies | | |
| switch, thumbwheel | 118 | 338 | converters, d/a | 109 | 326 |
| switches | 45 | 23 | custom hybrids | 109 | 58 |
| trimmers | 119 | 74 | data-acquisition system | 115 | 65 |
| trimmers | III | 285 | drive systems | 121 | 77 |
| Data Processing | | | f/v/f converters | 108 | 57 |
| CRT terminal | 106 | 52 | line driver | 108 | 304 |
| emulator, in-circuit | 90 | 41 | microcircuit modules | 35 | 16 |
| memory, μ C | 77 | 36 | subsystems, data-acq. | 109 | 325 |
| memory, core | 116 | 335 | Packaging & Materials | | |
| multiplexer, disc-storage | 115 | 332 | clips | 38 | 18 |
| PROM eraser | 115 | 333 | connectors | 72 | 34 |
| printer | 116 | 334 | connectors, circular | 97 | 45 |
| Discrete Semiconductors | | | connectors, heavy duty | 106 | 324 |
| crowbar, dc | 130 | 85 | electronic comp. catalog | 113 | 61 |
| crowbars, dc voltage | 114 | 330 | flexible circuits | 51 | 26 |
| diodes, varactor | 112 | 327 | gold inlay | 105 | 51 |
| isolator, opto | 114 | 331 | gripper | 64 | 30 |
| isolators | 7 | 6 | insertion tool | 117 | 71 |
| LEDs | 112 | 328 | sockets, transistor | 105 | 321 |
| optical coupler | 99 | 46 | solvent, epoxy | 105 | 322 |
| power Schottkys | 87 | 40 | test chamber | 107 | 55 |
| silicon transistors | 100 | 47 | tool, crimp and cut | 105 | 320 |
| transistors, microwave | 114 | 329 | wire, cable and cord | 5 | 234 |
| transistors, switching | 112 | 302 | wire stripper | 104 | 301 |
| Instrumentation | | | Power Sources | | |
| amplifier, broadband | 106 | 53 | power supplies | 6 | 5 |
| analyzer | 123 | 82 | power supplies | 40 | 20 |
| charge amplifier | 120 | 340 | power supplies | 73 | 35 |
| DPMs | 27 | 12 | power supplies | 109 | 59 |
| oscilloscopes | 123 | 81 | power supplies | 114 | 64 |
| oscillograph | 113 | 62 | digital data processor | 124 | 367 |
| PROM programmer | 120 | 346 | discrete semiconductors | 124 | 368 |
| pocket DVM | 120 | 342 | IC sample/hold device | 124 | 362 |
| pulse generator | 120 | 341 | measurement, control | | |
| rental equipment | 20 | 8 | sys. | 124 | 364 |
| signal generator | 120 | 345 | off-the-shelf power | | |
| sweeper | 120 | 343 | supplies | 124 | 363 |
| temperature meter | 120 | 344 | proximity switches | 124 | 366 |
| VOMs | 93 | 43 | rf transistors | 124 | 365 |
| Integrated Circuits | | | thumbwheel switches | 124 | 361 |
| d/a converters | 25 | 11 | | | |
| DAC | 102 | 309 | | | |
| linear ICs | IV | 286 | | | |
| RAM, 16-k | 101 | 305 | | | |



Million-dollar performance for only a quarter.

Fantastic! Small size, great performance and CTS reliability are only three reasons you should use our NEW series 375 single turn cermet trimmers. The low 25¢ price tag is still another.

CTS 375's, in six popular terminal styles, feature a low ± 100 ppm/ $^{\circ}$ C standard temperature coefficient—throughout the resistance range. Power rating, 1 watt at 40 $^{\circ}$ C; ½ watt at 70 $^{\circ}$ C. CRV of 2%. Settability of .03%.

And the serrated adjustment knob doubles as a dust cover to protect the element from dirt, oil and other contaminants.

It's a lot for so little. But you expect that from a company that's put millions into electronics for industry. For complete information, write **CTS OF BERNE, INC.**, Berne, Indiana 46711 or phone (219) 589-3111.

CTS CORPORATION
ELKHART, INDIANA



A world leader in cermet and variable resistor technology

What's new in solid state...

RCA offers 11 more Gold CHIP LICs at plastic prices.

Now you can replace ceramic with plastic, and get the reliability of ceramic at plastic prices. Eleven new Gold CHIP standards give you 11 new ways to get the cost and reliability benefits of gold plus Chip Hermeticity In Plastic. In all there are 26 Gold CHIP LICs with the reliability that comes from true hermeticity, plus the economy and ruggedness of plastic. The chip's hermetic—and the metalization and leads are all of non-corroding gold. There's no aluminum with its potential problems.

No problems ordering, either. Just call the Gold CHIP specialist at your nearest RCA Solid State distributor. And give him the type numbers of the circuits you need. That's the easy way to get Chip Hermeticity In Plastic. At plastic prices. Or contact RCA.

| | |
|-------------------------------|---|
| Single Operational Amplifiers | CA101AG,* CA107G,* CA201AG,* CA207G,* CA301AG,* CA307G,* CA741CG, CA741G, CA748CG,* CA748G* |
| Dual Operational Amplifiers | CA747CG, CA747G, CA1458G,* CA1558G* |
| Quad Operational Amplifiers | CA124G, CA224G, CA324G, CA3401G* |
| Quad Voltage Comparators | CA139AG, CA139G, CA239AG, CA239G, CA339AG, CA339G |
| 1A N-P-N Transistor Arrays | CA3724G, CA3725G |

*New types

Write: RCA Solid State, Box 3200, Somerville, New Jersey 08876; Ste. Anne de Bellevue 810, Canada; Sunbury-on-Thames, U.K.; Fuji Bldg., Tokyo, Japan.

RCA



RCA. Full house in Linear ICs.