

NEW LOOK — NEW STORIES — NEW DEPARTMENTS

# Popular Electronics

FIFTY CENTS / NOVEMBER 1970

## Light-emitting Diodes for Readout and Communications

DIGITAL READOUT FREQUENCY METER

HAFLER vs SCHEIBER 4 CHANNELS ON DISCS

ELECTRONICS SEEKS AN ANSWER TO CLEAR AIR TURBULENCE

WHAT WAS SO GREAT ABOUT THE "SWEET 16"?



3794061 DRNL A28A302 C  
REG100624HO 0408 A00036  
L DARKNELL JR MAY  
28 ARDEN CT CA 94061  
REDWOOD CITY



# Discover the ease and excitement of learning Electronics with programmed equipment NRI sends you

When you train at home with NRI, you train with your hands as well as your head. You learn the WHY of Electronics, Communications, TV-Radio the NRI pioneering "3-Dimensional" way. NRI training is the result of more than half a century of simplifying, organizing, dramatizing subject matter, and providing personal services unique for a home study school. You get the kind of technical training that gives you priceless confidence as you gain experience equal to many, many months of training on the job.

*NRI—The 53 Year Leader in Electronics Training*



## APPROVED UNDER NEW GI BILL

If you served since January 31, 1955, or are in service, check GI line in postage-free card.



*Earn \$5 or more an hour  
spare or full time in*

## **TV-RADIO SERVICING**

Color Television has arrived. Sales are soaring, along with the continuing popularity of other home entertainment equipment like portable radios, tape recorders, hi-fi sets, phonographs and auto radios. TV-Radio servicing is one of your best routes to spare-time earnings, a good paying job or a business of your own. NRI not only trains you quickly and expertly, but also shows you how to get started in Servicing soon after you enroll, earning as you learn. NRI trains you in today's methods of installing and repairing all Electronic equipment for the home—including booming Color TV. You even build, experiment with and keep to enjoy your own solid-state radio and your choice of black-and-white or Color TV receiver. Like thousands of others, you can be earning \$5 or more an hour extra in spare time starting soon.

## *There's money and success awaiting you in* **BROADCASTING— COMMUNICATIONS**

The experience you gain from intensely practical NRI training in Complete Communications equals as much as two years of training on the job. With NRI, you can train for a choice of careers ranging from mobile, marine and aviation radio to TV broadcasting and space communications. You learn how to install, maintain and operate today's remarkable transmitting and receiving equipment by actually *doing* it. You build and experiment with test equipment, like a VTVM you keep. You build and operate amplifier circuits, transmission line and antenna systems, even build and use a phone-cw transmitter suitable for transmission on the 80-meter amateur band. Whichever of five NRI Communications courses you choose, you prepare for your FCC License exams, and *you must pass your FCC exams or NRI refunds your tuition in full.*

## *Move ahead in America's fast growing industry as* **ELECTRONICS TECHNICIAN**

Electronics touches everyone's lives. This vast field of opportunity is open to you with NRI training. Industrial/Military Electronics training—like all NRI courses—prepares you quickly, thoroughly the practical "hands on" way. You build with, and learn to understand the functions of, today's miracle solid-state components like printed circuits, diodes and transistors. You build and experiment with Electronic circuitry used in automation, data processing, ultrasonics, telemetry. Whatever your interest in Electronics, NRI training can fill your needs. Prove to yourself what nearly a million NRI students could tell you . . . that you get more for your money from NRI. Check the postage-free card and mail it today for your FREE NRI Color Catalog. No salesman will call. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D.C. 20016.

**YOU GET MORE FOR YOUR MONEY FROM NRI** — Build, test, explore, discover. Everything you see here is included in one NRI course—including Color TV. Other courses equally complete. And you'll be surprised at the low tuition costs. Text for text, kit for kit, dollar for dollar—you get more for your money from NRI.



# Popular Electronics

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

## FEATURE ARTICLES

- |  |           |                      |
|--|-----------|----------------------|
| <b>ELECTRONICS GOES CAT CATCHING</b>                                 | <b>29</b> | Webb Garrison        |
| <i>Can air pockets be detected and avoided?</i>                      |           |                      |
| <b>LIGHT-EMITTING DIODES</b>   | <b>35</b> | Forrest M. Mims, III |
| <i>New semiconductors for readout and communication</i>              |           |                      |
| <b>OPPORTUNITY AWARENESS</b>   | <b>44</b> | David L. Heiserman   |
| <i>The sacred club of engineers</i>                                  |           |                      |
| <b>ASSEMBLE AN LED COMMUNICATOR—THE OPTICOM</b>                      | <b>45</b> | Forrest M. Mims, III |
| <i>Invisible light beam gives privacy</i>                            |           |                      |
| <b>ASSEMBLE A DIGITAL MEASUREMENTS LAB</b>                           | <b>51</b> | Dan Meyer            |
| <i>Versatility through modularization</i>                            |           |                      |
| <b>THE NUMBERS GAME</b>  | <b>64</b> | David B. Weems       |
| <i>How many speakers are just enough?</i>                            |           |                      |
| <b>STEREO SCENE</b>  | <b>69</b> | J. Gordon Holt       |
| <i>Four channels from two on discs</i>                               |           |                      |
| <b>THE PRODUCT GALLERY</b>   | <b>76</b> |                      |
| <i>Avanti Astro-Plane Antenna<br/>B &amp; K Cobra 24 Transceiver</i> |           |                      |
| <b>COMMUNICATIONS</b>  | <b>80</b> |                      |
| <i>WWV time booklet available</i>                                    |           |                      |
| <b>SOLID STATE</b>   | <b>82</b> | Lou Garner           |
| <i>Micropower semiconductors</i>                                     |           |                      |

## DEPARTMENTS

- |                                     |            |                   |
|-------------------------------------|------------|-------------------|
| <b>DIRECT &amp; CURRENT</b>         | <b>7</b>   | Oliver P. Ferrell |
| <b>INTERFACE</b>                    | <b>8</b>   |                   |
| <b>NEW LITERATURE</b>               | <b>12</b>  |                   |
| <b>ELECTRONICS LIBRARY</b>          | <b>14</b>  |                   |
| <b>READER SERVICE PAGE</b>          | <b>15</b>  |                   |
| <b>NEW PRODUCTS</b>                 | <b>22</b>  |                   |
| <b>OUT OF TUNE</b>                  | <b>102</b> |                   |
| <i>An Improved Four-Way Flasher</i> |            |                   |

POPULAR ELECTRONICS is indexed  
in the Readers' Guide  
to Periodical Literature

This month's cover photo by  
Justin Kerr

Copyright © 1970 by ZIFF-DAVIS PUBLISHING COMPANY. All rights reserved.

POPULAR ELECTRONICS, November 1970, Volume 33, Number 5, Published monthly at One Park Ave., New York, N.Y. 10016. One year subscription rate for U.S., U.S. Possessions and Canada, \$6.00; all other countries, \$7.00. Second class postage paid at New York, N.Y. and at additional mailing offices. Authorized as second class mail by the Post Office Department, Ottawa, Canada and for payment of postage in cash. Subscription service and Forms 3579; P.O. Box 1090, Flushing, N.Y. 11352. Editorial offices for manuscript contributions, reader inquiries, etc.: One Park Ave., New York, N.Y. 10016.

# Special introductory offer to new members of the ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB

	<p>404/437 <b>SOURCEBOOK OF ELECTRONIC CIRCUITS</b> by J. Markus Pub. price, \$19.75 Club price, \$14.75</p>		<p>A494/754 <b>ENGINEERING MANUAL, 2/e</b> by R. H. Perry Pub. price, \$12.50 Club price, \$10.65</p>
	<p>391/432 <b>DISPLAY SYSTEMS ENGINEERING</b> by H. R. Luxenberg &amp; R. L. Kuehn Pub. price, \$16.50 Club price, \$11.95</p>		<p>A523/401 <b>CHARACTERISTICS AND OPERATION OF MOS FIELD-EFFECT DEVICES</b> by P. Richman Pub. price, \$10.00 Club price, \$8.50</p>
	<p>A286/507 <b>SOLID-STATE ELECTRONICS</b> by R. G. Hibberd Pub. price, \$9.50 Club price, \$7.95</p>		<p>A037/604 <b>DIGITAL LOGIC AND COMPUTER OPERATIONS</b> by Baron &amp; Piccirilli Pub. price, \$14.50 Club price, \$11.95</p>
	<p>389/608 <b>PRINCIPLES OF DATA COMMUNICATION</b> by Lucky, Weldon &amp; Salz Pub. price, \$14.50 Club price, \$11.60</p>		<p>350/434 <b>DIGITAL COMPUTER USER'S HANDBOOK</b> by M. Klerer &amp; C. A. Korn Pub. price, \$27.50 Club price, \$23.35</p>
	<p>A347/506 <b>ELECTRONIC DIGITAL TECHNIQUES</b> by P. M. Kintner Pub. price, \$12.50 Club price, \$10.65</p>		<p>A565/031 <b>AMPLIFIER HANDBOOK</b> by R. F. Shea Pub. price, \$37.50 Club price, \$29.50</p>
			<p>A637/377 <b>TRANSISTOR CIRCUIT DESIGN</b> by Texas Instruments, Inc., Staff Pub. price, \$16.50 Club price, \$13.95</p>
			<p>A126/070 <b>PRINTED CIRCUITS HANDBOOK</b> by C. F. Coombs, Jr. Pub. price, \$17.75 Club price, \$14.95</p>
			<p>A610/037 <b>MODERN COMMUNICATION PRINCIPLES</b> by Stein &amp; Jones Pub. price, \$15.00 Club price, \$12.75</p>
			<p>A259/607 <b>COMMUNICATION SYSTEM ENGINEERING HANDBOOK</b> by D. H. Hamsher Pub. price, \$29.50 Club price, \$24.95</p>

**ANY ONE**  
of these great professional books  
for only **\$1.00**  
VALUES FROM \$9.50 to \$37.50

Special \$1.00 bonus book comes to you with your first club selection

## Save time and money by joining the Electronics and Control Engineers' Book Club

HERE is a professional club designed specifically to meet your day-to-day engineering needs by providing practical books in your field on a regular basis at below publisher prices.

How the Club operates: Basic to the Club's service is its publication, the *Electronics and Control Engineers' Book Club Bulletin*, which brings you news of books in your field. Sent to members without cost, it announces and describes in detail the Club's featured book of the month as well as alternate selections which are available at special members' prices.

When you want to examine the Club's feature of the month, you do nothing. The book will be mailed to you as a regular part of your Club service. If you prefer one of the alternate selections—or if you want no book at all for that month—you notify the Club by returning the convenient card enclosed with each *Bulletin*.

As a Club member, you agree only to the purchase of four books over a two-year period. Considering the many books published annually in your field, there will surely be at least four that you would want to own anyway. By joining the Club, you save both money and the trouble of searching for the best books.

## MAIL THIS COUPON TODAY

ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB  
582 Princeton Road, Hightstown, N.J. 08520

Please enroll me as a member of the Electronics and Control Engineers' Book Club and send me the two books indicated below. I am to receive the bonus for just \$1.00, and my first selection at the special Club price shown. These books are to be shipped on approval, and I may return them both without cost or further obligation. If I decide to keep the books, I agree to purchase as few as four additional books during the next two years at special Club prices (approximately 15% below list).

Write Code No. of  
bonus book  
here

Write Code No. of  
first selection  
here

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

E-33146

# Every record you buy is one more reason to own a Dual.

If you think of your total investment in records — which may be hundreds or even thousands of dollars — we think you'll agree that those records should be handled with the utmost care.

Which brings us to the turntable, the component that handles those precious records. Spinning them on a platter and tracking their fragile grooves with a diamond stylus, the hardest substance known to man.

For many years, serious music lovers have entrusted their records to one make of automatic turntable — Dual. In fact, most professionals (who have access to any equipment) use a Dual in their own stereo component systems. And not always the highest priced mode.

So the question for you to consider isn't which Dual is good enough, but how much more than "good" your turntable has to be.

This question can be answered in our literature, which includes complete reprints of independent test reports. Or at any of our franchised dealers.

**United Audio Products, Inc.,**  
120 So. Columbus Ave., Mt. Vernon,  
New York 10553. 



Dual 1209, \$129.50.  
Other models from \$99.50 to \$175.00.

CIRCLE NO. 31 ON READER SERVICE PAGE

# Popular Electronics

**LAWRENCE SPORN**  
*Publisher*

**OLIVER P. FERRELL**  
*Editor*

**LESLIE SOLOMON**  
*Technical Editor*

**JOHN R. RIGGS**  
*Managing Editor*

**EDWARD I. BUXBAUM**  
*Art Director*

**ALEXANDER W. BURAWA**  
*Associate Editor*

**ANDRE DUZANT**  
*Technical Illustrator*

**PATTI MORGAN**  
*Assistant Editor*

**JUDITH L. HOGAN**  
*Editorial Assistant*

**J. GORDON HOLT**  
**L. E. GARNER, JR.**  
**DAVID L. HEISERMAN**  
*Contributing Editors*

**J. ROYCE RICHARD**  
*Assistant Publisher*

**RICHARD J. HALPERN**  
*Advertising Manager*

**ROBERT UR**  
*Marketing Manager*

**MARGARET DANIELLO**  
*Advertising Service Manager*

**FURMAN H. HEBB**  
*Group Vice President*  
*Electronics and Photographic*

**ZIFF-DAVIS PUBLISHING COMPANY**  
*Editorial and Executive Offices*  
One Park Avenue, New York, New York 10016  
212 679-7200

*Midwestern Office*

The Patis Group, 4761 West Touhy Ave.,  
Lincolnwood, Illinois 60046, 312 679-1100  
GERALD E. WOLFE, DICK POWELL

*Western Office*

9025 Wilshire Boulevard, Beverly Hills, California 90211  
213 CResview 4-0265; BRadshaw 2-1161  
Western Advertising Manager, BUD DEAN

*Japan: James Yagi*

Ishikawa Mansion #4, Sakuragaoka  
Shibuya-ku, Tokyo, 462-2911-3

*Circulation Office*

P.O. Box 1096, Flushing, N.Y. 11352

William Ziff, President

W. Bradford Briggs, Executive Vice President

Hershel B. Sarbin, Senior Vice President

Stanley R. Greenfield, Senior Vice President

Philip Sine, Financial Vice President

Walter S. Mills, Jr., Vice President, Circulation

Phillip T. Heffernan, Vice President, Marketing

Frank Pamerantz, Vice President, Creative Services

Arthur W. Butzow, Vice President, Production

Edward D. Muhlfeld, Vice President, Aviation Division

Irwin Robinson, Vice President, Travel Division

George Morrissey, Vice President

Sydney H. Rogers, Vice President

Ziff-Davis also publishes Airline Management and Marketing Including American Aviation, Boating, Business & Commercial Aviation, Car and Driver, Cycle, Electronics World, Flying, Modern Bride, Popular Photography, Skiing, Skiing Area News, Skiing Trade News, Stereo Review, and Travel Weekly.


Forms 3579 and all subscriptions correspondence should be addressed to POPULAR ELECTRONICS, Circulation Department, P.O. Box 1096, Flushing, N.Y. 11352. Please allow at least six weeks for change of address. Include your old address, as well as new—enclosing if possible an address label from a recent issue.

EDITORIAL CONTRIBUTIONS must be accompanied by return postage and will be handled with reasonable care; however, publisher assumes no responsibility for return or safety of art work, photographs or manuscripts.



Member Audit Bureau  
of Circulations

POPULAR ELECTRONICS

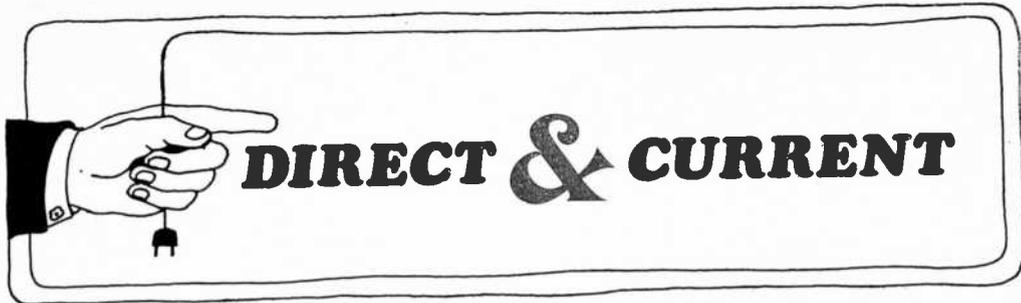

Third in a Monthly Series by **Oliver P. Ferrell**, Editor

## ABOUT READER MAIL

Several years ago, an associate proposed a unique solution to the problem of how to handle reader mail—never answer a single letter! Undoubtedly he was embittered by the seemingly endless flow of letters from POPULAR ELECTRONICS readers.

Trying to answer reader mail is admittedly a moral obligation for the magazine—especially in regard to published material. However, all readers may not be aware that, as much as the staff would like to help solve reader problems, it is frequently impossible. Permit me, on behalf of the staff, a moment to review the problem and explain why some inquiries go unanswered:

**1 Cost.** Answering the average inquiry costs more in manhours than the magazine recoups from a one-year subscription.

**2 Validity.** The average inquiry wants us to change into something else something that has already been published; frequently an incredibly complex redesign of the entire project.

**3 Out of Date.** An amazingly high percentage of inquiries deal with material published 3 to 10 years ago involving projects using components no longer available and lacking substitutions.

**4 Referrals.** The average inquiry is addressed to the author and an answer is expected over the author's signature. Only one out of 20 authors has the time and research facilities to answer reader inquiries; as much as he may appreciate the interest in his work.

**5 Volume.** Last year, POPULAR ELECTRONICS received an average of 900 letters and postcards each month that might be categorized as reader inquiries. (We are not referring here, of course, to the use of the Reader Service Pages.)

In one recent batch of mail, the inquiries included the following samples: design of a recording studio fader console; comparison of various CB transceivers; pleas for free subscriptions; detailed theoretical analysis for a Science Fair project; complaint about absence of Carl & Jerry series; 17 modifications of the "Mini-DVM", 9 requests for clarification of JK flip-flop article; plans for 14 different speaker enclosures; etc., etc.

The above skims the surface of the problem and is written to show that we are aware of the need for a quick advisory service. The staff attempts to answer as many inquiries as time will permit, but those answered are still a fraction of the incoming mail. Any suggestions?

# SAMS BOOKS

ESPECIALLY FOR THE BUILDER

## Hi-Fi Projects for the Hobbyist

Easy-to-build projects include: rumble filter, noise filter, high-gain antenna, transistorized microphone preamp, etc. Also explains how to improve existing high fidelity systems and how to check them out for optimum performance. Order 20222, only... \$2.95

## 101 Easy Ham Radio Projects

A selection of easy-to-build, inexpensive circuits for a variety of worthwhile ham devices. Provides brief descriptions, construction hints, diagrams, and parts lists; includes substitution guide appendix. Order 20674, only..... \$3.95

## ABC's of Electrical Soldering

An invaluable book on the art of soldering—what it is and does, how to make a good connection, how to make solder repairs. Explains solder alloys, fluxes, soldering irons, and instant-heat guns. Order 20627, only..... \$2.95



## 49 Easy Transistor Projects

Provides simple, easy instructions, schematic diagrams, and parts lists for building a-m and fm radios, light relay controls, audio amplifiers, code practice oscillators, and test equipment, using inexpensive parts. Order 20617, only..... \$1.75

## How to Build Electronics Projects

Provides complete description of methods and tools used in construction. Discusses proper circuit layout, metal chassis and panel layout, and drilling and punching. Also includes information on semiconductor and etched-circuit boards construction. Order 20670, only..... \$2.95

## 101 Easy Audio Projects

Furnishes complete instructions for building simple, inexpensive audio projects with the imaginative use of many spare parts found in old radio and TV chassis. Includes intercom systems, wireless microphones, phono and power amplifiers, and a-m tuners. Order 20608, only..... \$3.50

### —HOWARD W. SAMS & CO., INC.—

Order from any Electronic Parts Distributor, or mail to Howard W. Sams & Co., Inc. Dept. PE-110 4300 W. 62nd St., Indianapolis, Ind. 46268

Send the following books: Nos. \_\_\_\_\_ \$ \_\_\_\_\_ enclosed

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE NO. 27 ON READER SERVICE PAGE



# INTERFACE

## THE "NEW LOOK"—PRO AND CON

Congratulations! I had long ago decided that you people thought that your readers were either idiots, senile, or both. I am glad to see you doing articles more ambitious than how to add an S-meter to your radio. I especially like the idea of Hirsch-Houck Laboratories checking out all audio projects. One of my pet peeves has always been the very sketchy, incomplete or nonexistent specifications on preamps and power amps.

Double congratulations to Mr. Holt on the "Stereo Scene." I was beginning to think that I was the only person who considered most American-cut discs not worth buying. I long ago switched to EMI and London pressings. I had also dropped all of my audio-type magazine subscriptions since I was getting weary of reading "good buy" test reports for everybody on the market.

R. T. TAYLOR  
Lincolnton, N.C.

The new format is cold and seems to be a collection of news releases. Missing is the friendliness that we have known for so many years. The typography is excellent, but to this reader it is just plain cold type.

J. A. STAUHS, WA2BNF  
Belleville, N.J.

The new "Product Gallery" makes more sense than reproduction of a lot of slick, insipid press releases from the pen of some brainless continuity writer. Go to it!

C. T. WEATHERFORD, JR.  
Roscoe, N.Y.

The new cover design is sharp, but the editorial content is insipid! POPULAR ELECTRONICS has taken a posture much like the professional journals in electronics. If the September issue is an example of the plans for the future, your magazine is of no more use to me.

W. C. GANSOEC  
Chicago, Ill.

I am pleased with the new look and format, especially the new "Communications" column and your regular column, "The Product Gallery." I feel that POPULAR ELECTRONICS is worth its weight in gold.

R. R. HALL  
Madison, Tenn.

Changed format? Yeah, you've done that all right and apparently changed the po-

# Suddenly we're a household word.



## New Cobra 25 CB Base Station

As if we weren't famous enough already. Now we're a household word.

Why? Because we've come up with everything you've been asking for in a CB radio designed for the home (or for that matter, any place a base station is used). It's called the Cobra 25. You have to see it to believe it. Hear it and you'll be convinced.

Ultramodern new solid state circuit design gives you the biggest talk power in the industry—full 5 watts input, maximum legal output up to 4 watts.

And exclusive Dynabooast speech compression puts your message through crisp and sharp, even when others are garbled and unclear.

The word is spreading fast about the new big talking Cobra 25. Shouldn't you have one for your household or communications center?

See your dealer or write us for complete details.

The ultimate in solid state circuit design with selective dual-conversion superhet receiver. Ceramic filter. New Delta Tune control to reduce off-channel interference. FET's in the critical mixer stage to eliminate cross talk. New integrated circuit (IC) in the IF stage for greatest gain in the smallest space with lifetime dependability. Exclusive Dynabooast speech compression. Separate power and SWR meters. 5 watts input. 100% modulation. PA system. 23 channels with crystals included.

Cobra 25  
\$228.00

**Cobra** 

Product of DYNASCAN CORPORATION  
1801 W. Belle Plaine Chicago, Illinois 60613

## The Biggest Voice in CB Radio

CIRCLE NO. 10 ON READER SERVICE PAGE

tential subscriber group since the entire issue says to me, "To hell with you stupid people, now all of us brilliant electronics M.A.'s and PhD's are going to communicate with all of our brilliant colleagues."

You had a good thing, and, like I said, you blew it!

R. B. ORFORD  
Rochelle, Ill.

The "New Look" is great !!!

JAY CARPENTER  
Berryville, Va.

I must tell you that your "New Look" is a big disappointment. You have apparently decided to eye the well-padded pocketbook of the hobbyist with more money than know-how.

J. FEAGANS  
Tallula, Ill.

To J. Gordon Holt: Welcome! Welcome! At last someone is saying the things I would like to say in the way I would like to say them. Bravo! Don't change a thing!

JACK O'RYAN  
Northfield, Ohio

I have read and subscribed to POPULAR ELECTRONICS for years for two reasons, Hank Bennett's and Herb Brier's columns. Now you simply tell us non-builders to go jump in the lake.

DR. C. SCHWARTZBARD, WB2IWH  
Clifton, N.J.

I congratulate you and your colleagues on the "New Look." I am especially pleased with your entry into the experimental areas of digital and computer equipment. I hope that your "Direct & Current" editorial series will occasionally wax philosophic and deal with the problems related to broadcasting, such as definition, establishments, recognition, maintenance, protection of rights, etc.

N. E. ANDREWS  
Eastontion, N.J.

I have two complaints about your "New Look." First, I like the idea of more unique and sophisticated construction projects, but would like to see one or two simple ones tossed in from time to time.

Secondly, I would like to see Roger Legge's material put back in the magazine.

S. KARKLIN  
Pepper Pike, Ohio

Just received your September issue and I'd just like you to know how much I enjoyed it. I was debating whether or not to continue my subscription after it ran out. Not only do I like the new format style, but also appreciate the new content.

D. R. WARD  
Middlebury, Conn.

I thoroughly detest your "New Look" for it leaves no great interest to the beginning experimenter. I think you should devote at least one project article in each issue to the

*(Continued on page 95)*

# BIG TDK CASSETTE GIVEAWAY



Get two TDK SD cassettes free when you take home a handy 10-pack, either C60SD or C90SD—you pay for eight only! The two free cassettes are our 25% bonus to you—our chance to make you a fan of TDK Super Dynamic tape, the finest available anywhere, by proving that *your ears* will hear the difference. The specially formulated oxide coating and binder extend your recorder's high-frequency response, cut down background noise, increase sound level and reduce distortion. Act while these special 10-for-8 giveaway packs last. This offer expires at midnight, November 30, 1970.



**TDK** World's leader in tape technology since 1932.  
**TDK ELECTRONICS CORP.**

LONG ISLAND CITY, NEW YORK 11103












CIRCLE NO. 30 ON READER SERVICE PAGE

POPULAR ELECTRONICS

# FINCO '70 SERIES

COLOR TV ANTENNAS SPECTRUM

NO VHF VHF STRONG VHF MODERATE VHF WEAK VHF VERY WEAK

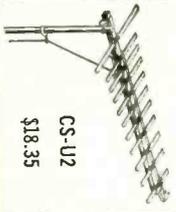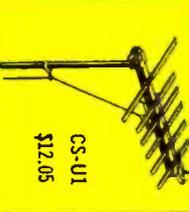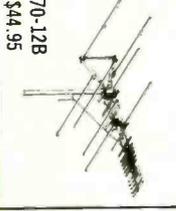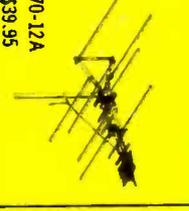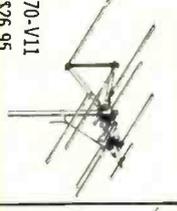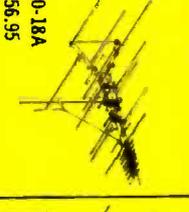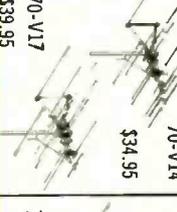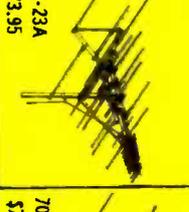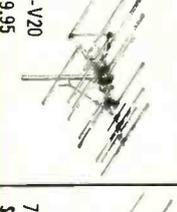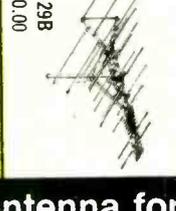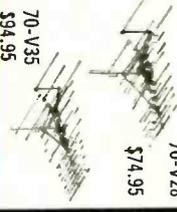UHF VERY WEAK	UHF WEAK	UHF STRONG	NO UHF
 <p>CS-U3 \$26.40</p>	 <p>CS-U2 \$18.35</p>	 <p>CS-U1 \$12.05</p>	<p>All Prices Subject to Change</p>
 <p>70-188B \$62.95</p>	 <p>70-12B \$44.95</p>	 <p>70-12A \$39.95</p>	 <p>70-V11 \$26.95</p>
 <p>70-188 \$62.95</p>	 <p>70-188B \$62.95</p>	 <p>70-18A \$56.95</p>	 <p>70-V14 \$34.95</p>
 <p>70-23B \$80.95</p>	 <p>70-23B \$80.95</p>	 <p>70-23A \$73.95</p>	 <p>70-V20 \$49.95</p>
 <p>70-29B \$100.00</p>	 <p>70-29B \$100.00</p>	 <p>70-23A \$73.95</p>	 <p>70-V35 \$94.95</p>
			 <p>70-V28 \$74.95</p>

NOTE: Each model above is also available with 75 ohm coaxial cable, downlead and compact behind-the-set balun-splitter to match antenna system to proper set terminals.

Select the antenna for your area from this chart

The set choice is yours...  
the antenna choice is **FINCO**

Send for free Catalog 20-556

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_



**THE FINNEY COMPANY**  
34 West Interstate St., Dept. PE-11  
Bedford, Ohio 44146

CIRCLE NO. 14 ON READER SERVICE PAGE



"Semiconductor Device Digest." The 20-page, full-color, illustrated "short form" Digest reflects International Rectifier's in-depth product capability. Devices listed include: SCR's, selenium rectifiers, zener regulators, power logic triacs, high-power silicon rectifiers, silicon rectifier assemblies, light-sensitive devices, etc. Each category of semiconductor devices is presented in compact tables and charts that give ratings, parameters, and other important specifications. An additional feature of the Digest is a complete alphanumeric cross-reference index of individual IR device numbers to the corresponding Digest page.

Circle No. 76 on Reader Service Page 15

To obtain a copy of any of the catalogs or leaflets described below, fill in and mail the Reader Service blank on page 15.


A colorful, six-page brochure available from *Elpa Marketing Industries, Inc.*, covers the entire line of Thorens Transcription Turntables. Listed are the new TD-150 MKII and the full line of TD-125's. The brochure also lists the company's line of turntable bases, dust covers, mounting frames, tonearm mounting boards, and Thorens maintenance equipment. Each item is illustrated and explained.

Circle No. 75 on Reader Service Page 15

All *International Rectifier* semiconductor devices are presented in a new publication titled

A "Quick Delivery Identification" system, featuring a three-level popularity grading guide to automatically forecast the availability and required lead time for major component items, is highlighted in a new 36-page shortform catalog, No. 300B, published by *Ohmite Mfg. Co.* The components described in the catalog include resistors, rheostats/potentiometers, trimmer pots, tap switches, variable transformers, relays, solid-state power controls, r-f chokes and various design aids. The new identification system utilizes *bold-* and light-face type and parentheses to indicate product availability based on nationally exhibited usage patterns. Also available with the catalog is a copy of the "Manufacturer's Price Schedule," No. MS-100.

Circle No. 77 on Reader Service Page 15

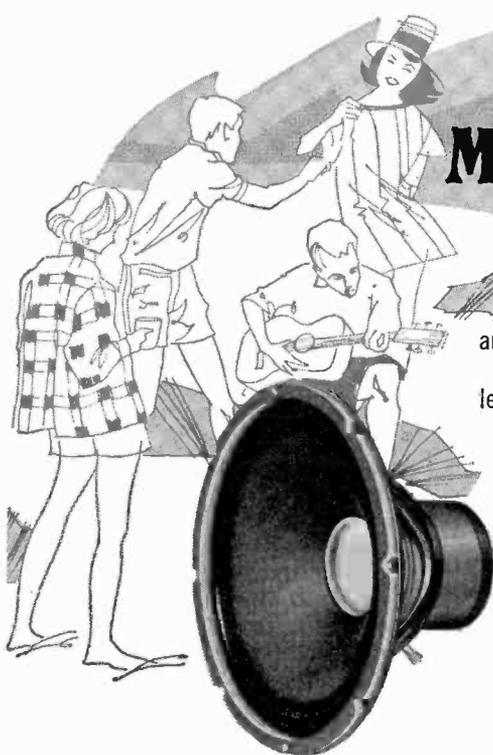

## MAKING "WAVES"

**CADENCE—the musical instrument speakers**

Making better, clearer, amplified sound waves is the **THING** Cadence does... better than anything else in the industry. Cadence Speakers are built to withstand heat from sustained notes at a high power level and the vibrations and stresses which are continually placed upon them. Cadence is guaranteed **one full year** at the power level specified. This proven speaker family has been selected by the manufacturers of most of the world's fine amplified music instruments.


If making beautiful, clear sound waves is your thing, ask for **CADENCE SPEAKERS**.

For complete information and the name of your Cadence Dealer, write:



**UTAH ELECTRONICS DIVISION**  
Utah-American Corporation  
1124 East Franklin Street  
Huntington, Indiana 46750

CIRCLE NO. 32 ON READER SERVICE PAGE

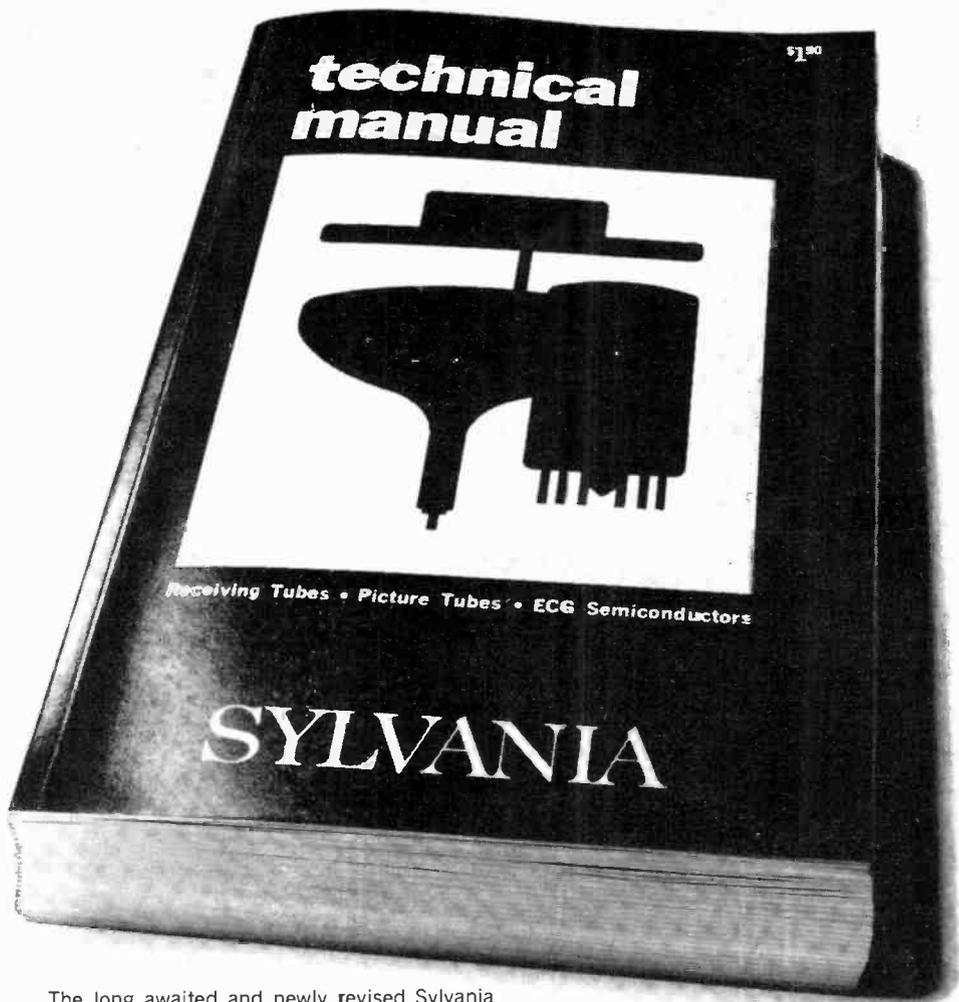

The long awaited and newly revised Sylvania Technical Manual is out. Complete and unexpurgated. The fantasy of every Independent Service Technician. Written anonymously by an agile team of Sylvania engineers. 32,000 components described in breathtaking detail. Including thousands of unretouched diagrams and illustrations. Discover the unspeakable thrill of new color TV Tubes, listed as never before. The ecstasy of 28,000 ECG Semiconductors.

From exotic Deflection Oscillators to a lurid account of Transistors and Rectifiers.


This book has what you want. Components for the man who knows what to do with them.

The 14th Edition of the Sylvania Technical Manual is not available in any bookstore. Your Sylvania Distributor is discreet. Speak to him.

“Electrifying”

**SYLVANIA**  
GENERAL TELEPHONE & ELECTRONICS

## Sinclair PROJECT 60

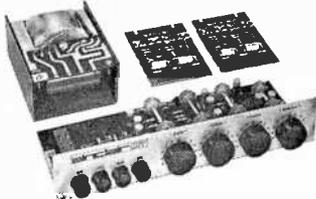

Sinclair Project 60 modules may be used together or separately in home or professional applications requiring high performance at modest cost. Complete

Project 60 systems come supplied with necessary hardware to enable you to easily install the modules in cabinet or enclosure of your choice. The Project 60 modules are fully guaranteed for **TWO YEARS**. A stereo FM tuner will be available shortly. If you have not found the amplifier which meets your installation or performance requirements, the **PROJECT 60 SYSTEM** by Sinclair may be your answer.

The Sinclair Z-30/50 audio amplifier modules are of advanced design, using silicon epitaxial planar transistors for ruggedness and reliability. The Z-50 is basically the same as the Z-30 but uses higher current output transistors. The Z-30/50 may be used in numerous audio applications such as electronic music and instruments, sound reinforcement and laboratory work in addition to home stereo.

**POWER OUTPUT:** Z-30, 15 watts RMS; Z-50, 30 watts RMS; Both into 8 ohm loads.

**FREQUENCY RESPONSE:** 20 Hz\* to 300 KHz  $\pm 1$  db at normal level. \*adjustable to meet installation requirements.

**DISTORTION:** Less than .02% at 1 KHz at any level up to maximum rated output.

**OUTPUT IMPEDANCE:** 3 to over 16 ohms. . . . May be used with electrostatic speakers.

**SENSITIVITY:** 250 mV high impedance.

**OPERATING VOLTAGE:** As low as 8 Vdc with reduced output.

**SIZE:**  $3\frac{1}{2} \times 2\frac{1}{4} \times \frac{1}{2}$  inches

Z-30 \$15.95

Z-50 \$18.95

The Stereo 60 module is a matching unit in performance for use with the Z-30/50 modules but may be used with other amplifiers. The Stereo 60 features low distortion (less than .05%), three inputs, tape output, RIAA equalization within 1 db on magnetic input and operates over a wide voltage range from 9 to 50 Vdc. Size:  $8\frac{1}{4} \times 1\frac{1}{2} \times 4$  inches. \$29.95

The Sinclair **ACTIVE FILTER UNIT** may be used with the Project 60 systems plus specialized applications requiring a continuously variable rumble and scratch filtering system. The AFU uses **SALLEN & KEY** active filter stages to provide rapid rejection of unwanted frequencies (12 db per octave).

**HF FILTER:** Variable 5 KHz to 28 KHz.

**LF FILTER:** Variable 25 Hz to 100 Hz.

**SINCLAIR ACTIVE FILTER UNIT** . . . . . \$20.95

### POWER SUPPLIES

**PZ-5:** A standard 25-30 Vdc supply for use with the Project 60 modules . . . . . \$13.95

**PZ-6:** A regulated supply providing 35 Vdc (adjustable) at 1 1/2 amps for use with Z-30s when maximum RMS power is required . . . . . \$23.95

**PZ-8:** A regulated supply for use with the Z-50 modules only when maximum power is required. 35-50 Vdc at 3 amps (adjustable) . . . . . \$37.95

**SINCLAIR PROJECT 60 SYSTEMS** are available from many dealers. If your dealer does not yet stock Sinclair products, order direct from Audionics.

**AUDIONICS, INC.,**  
9701 S.E. Mill Street, Portland, Oregon 97216

Please ship the following:

- #1 Two Z-30's, PZ-5 and Stereo 60 . . . . . \$74.95
- #2 Two Z-30's, PZ-6 and Stereo 60 . . . . . 84.95
- #3 Two Z-50's, PZ-6 and Stereo 60 . . . . . 90.95
- #4 Two Z-50's, PZ-8 and Stereo 60 . . . . . 104.95


Other \_\_\_\_\_

Name: \_\_\_\_\_

Address: \_\_\_\_\_

City: \_\_\_\_\_ State: \_\_\_\_\_ Zip: \_\_\_\_\_

All shipments F.O.B. Portland, Oregon pe

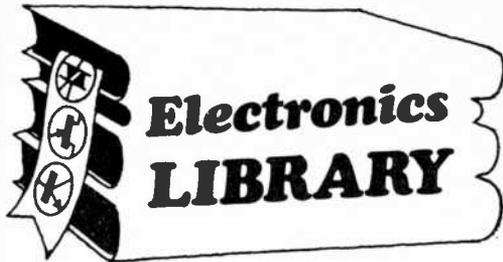

## SEMICONDUCTOR PULSE CIRCUITS WITH EXPERIMENTS

by Brinton B. Mitchell

The technician must have a firm understanding of circuit theory no matter what his position. This book, then, provides the design, analysis, and synthesis information of basic pulse and switching circuits, introducing these circuits in their simplest forms. The text is organized into 20 chapters, each of which presents a typical basic circuit. Circuit discussions include such information as prerequisite theory, a design example, an analysis example, an experiment consisting of a design circuit problem or an analysis circuit problem, and questions covering the material. Throughout the book, the material is geared to a technician level with emphasis on the semiconductor active device as a switch.

Published by Holt, Rinehart and Winston, Inc., 383 Madison Ave., New York, NY 10017. Hard Cover. 379 pages. \$10.50.

## SERVICING MODERN HI-FI SYSTEMS

by Norman Crowhurst

This is a practical guide to repairing such hi-fi items as tuners, amplifiers, receivers, tape recorders, etc. The author develops a rational and logical method of trouble-shooting virtually any type of hi-fi equipment to find the cause of trouble. Beginning with an analysis of modern system design in comparison with older concepts, new servicing techniques required for solid-state devices, test equipment requirements, testing procedures for components, etc., are then introduced. To aid the technician who is constantly faced with a variety of component types, a chapter is devoted entirely to transistor and diode interchangeability. Also, to provide a thorough understanding of the causes of component failure, another chapter is devoted to protection circuits.

Published by TAB Books, Blue Ridge Summit, PA 17214. 224 pages. \$7.95 hardbound; \$4.95 soft cover.

## ELEMENTS OF ELECTRONICS, Third Edition

by H.V. Hickey & W.M. Villines, Jr.

This is an ideal book for technician-level electronics survey courses with a communica-

# Popular Electronics

## READER SERVICE PAGE

### free information service:

Here's an easy and convenient way for you to get additional information about products advertised or mentioned editorially (if it has a "Reader Service Number") in this issue. Just follow the directions below... and the material will be sent to you promptly and free of charge.

**1.** On coupon below, circle the number(s) that corresponds to the key number(s) at the bottom or next to the advertisement or editorial mention that is of interest to you. (Key numbers for advertised products also appear in the Advertisers' Index.) Print or type your name and address on the lines indicated.

**2.** Cut out the coupon and mail it to: POPULAR ELECTRONICS, P.O. Box 8391, Philadelphia, PA 19101.

**note:** If you want to write to the editors of POPULAR ELECTRONICS about an article on any subject that does not have a key number, write to POPULAR ELECTRONICS, One Park Avenue, New York, N.Y. 10016. Inquiries concerning circulation and subscriptions should be sent to POPULAR ELECTRONICS, P.O. Box 1096, Flushing, N.Y. 11352.

Void after December 31, 1970

# Popular Electronics

P.O. BOX 8391  
PHILADELPHIA, PA. 19101

1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20  
21 22 23 24 25 26 27 28 29 30 31 32 33 34 35 36 37 38 39 40  
41 42 43 44 45 46 47 48 49 50 51 52 53 54 55 56 57 58 59 60  
61 62 63 64 65 66 67 68 69 70 71 72 73 74 75 76 77 78 79 80  
81 82 83 84 85 86 87 88 89 90 91 92 93 94 95 96 97 98 99 100

NAME (Print clearly) \_\_\_\_\_


ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP CODE \_\_\_\_\_

11 a

CB gets a first ever from Turner

# FULL MODULATION GUARANTEED

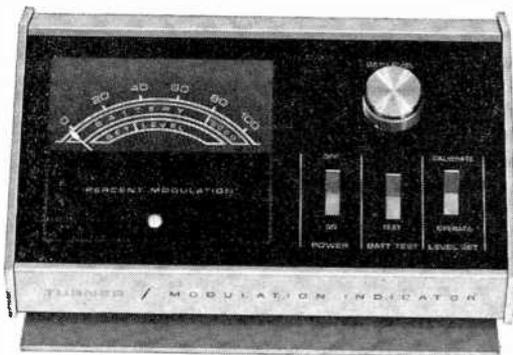

Get the most out of your base rig. Put something new into it. Buy a Turner Modulation Indicator and be sure of full modulation every time. There's no other way to keep a steady eye on your signal. And nothing could be easier to operate. Just work the volume control on your Turner +2 or +3 microphone until the indicator shows 100%. You'll get a clearer signal. You'll send it a lot farther. Buy now. Be among the first to own this handsome instrument with a black-lucite and brushed-aluminum finish. Works with all CB sets, comes with complete operating instructions. Features solid state construction, plug-in installation, self-contained standard 9-volt battery operation. CB users net price \$39.50. Manufactured in the United States by the Turner Company, A Subsidiary of Conrac Corporation, 909 17th Street N.E., Cedar Rapids, Iowa 52402.

## The Turner Company

CIRCLE NO. 33 ON READER SERVICE PAGE

tions emphasis. In its Third Edition, it is one of the few books that provide detailed discussions of both tubes and transistors. One of the special features is the inclusion of a complete and self-contained chapter on the theory, use, and basic circuitry of computers, representing possibly the first time computers have ever been dealt with in an introductory-level textbook. And integrated circuits are explained and detailed coverage is given to thin-film and semiconductor techniques.

*Published by McGraw-Hill Book Co., 330 West 42 St., New York, NY 10036. Hard cover. 709 pages. \$11.95.*

### FILTER SYSTEMS AND DESIGN: ELECTRICAL, MICROWAVE, AND DIGITAL

by Yale Jay Lubkin

Using an informal but basically thorough approach, this book is written to extend the working engineer's knowledge of electrical filters and to provide him with tools he can use immediately. The text presents the fundamental concepts of filters; why and how the various kinds originated; what types of problems they solve; and filter limitations. Some of the concepts developed in this book have never before appeared in print, and, while they are rather advanced in nature, they are nevertheless presented in an understandable manner. Aimed at the engineer with curiosity, a job to do, and not much time in which to do it, the book requires little math sophistication. This book is also suitable for senior and graduate level courses on filter theory or as a supplementary text in courses on network analysis.

*Published by Addison-Wesley Publishing Co., Inc., Reading, MA 01867. Hard cover. 212 pages. \$11.50.*

### THE PHYSICS OF TRANSMISSION LINES AT HIGH AND VERY HIGH FREQUENCIES, Volume 1

by P. Grivet

From the scientific point of view, a transmission line is an unusual structure in which a variety of seemingly contradictory qualities are united. It is especially valuable as a model because it forms a simple, general example in which travelling, standing, pure, and attenuated waves can all be treated clearly and thoroughly using both circuits and field theory. Although these two dissimilar theories are often regarded as antagonistic, the author believes that a harmonious and fruitful association between them is desirable. His general approach in this book is in terms of circuit theory, but he takes care to show the links with field theory. This book will aid physicists, microwave engineers, and electronics engineers who want familiarization with new elements of circuit theory.

*Published by Academic Press, Inc., 111 Fifth Ave., New York, NY 10003. Hard cover. 451 pages. \$22.50.*



## UNIVERSITY JUST MADE YOU A SOUND INSTALLATION EXPERT



**TCS = Totally  
Coordinated Sound  
systems you  
can install yourself.**


University just invented TCS — Totally Coordinated Sound systems so painstakingly pre-engineered *anyone* can install them. Everything you need comes with each system: speakers, amplifiers, microphones, color-coded cables, plus assembly and installation instructions. All pre-engineered, pre-matched, pre-sized, for hundreds of applications.

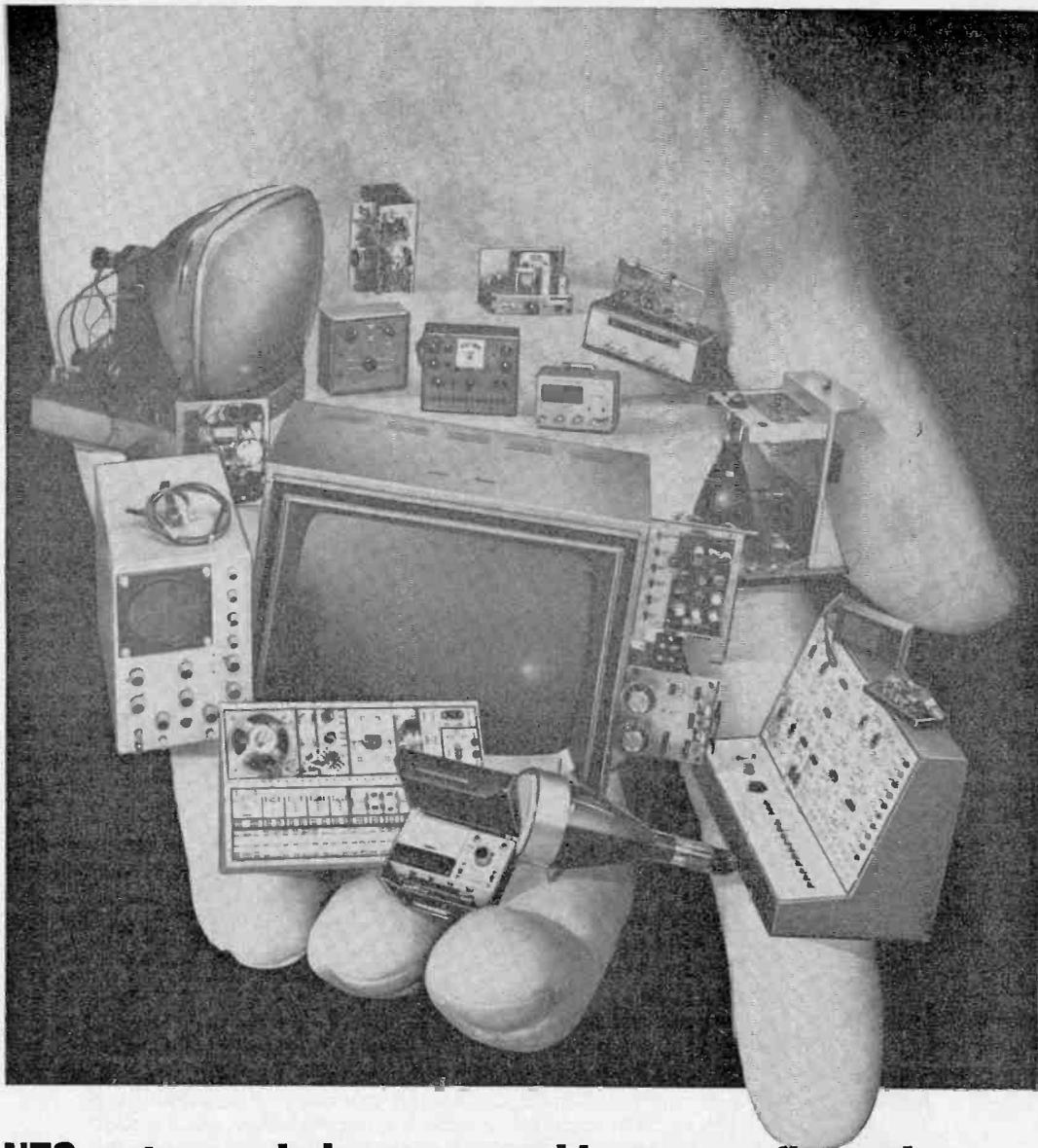***If you can twist a wire, screw a screw, push a plug into a socket — congratulations! University just made you a sound installation expert.***

Write for details today about how you can install your own PA sound system tomorrow.

**UNIVERSITY<sup>®</sup> SOUND**  
A DIVISION OF BOWLING BROTHERS & COMPANY, INC.





## NTS puts a whole new world at your fingertips.

NTS home training can put a whole new way of life in the palm of your hand. A new, exciting job, a much bigger income is now easily within your reach.

NTS training is something special. We provide all the kits you need for the most effective training. National Technical Schools sends kits with every course, and teaches you to build and test a


wide range of professional equipment — the same kind of equipment you'll actually use on the job. That's the NTS "Project Method" — training that's practical and in-depth. You learn everything from fundamentals to the latest innovations. From beginning to end, NTS makes it fascinating and fun to learn this way. And all you need is a little

spare time and an interest in electronics.

Each year, men are moving into important new jobs, or their own businesses, straight out of NTS electronics training. NTS is what's happening to men everywhere. Check the coupon. Take hold of the career you want most. Do it now. No obligation. No salesman will call.

**We pack your electronics course with kits to make your training fast. You'll enjoy every minute of it.**

## NTS COLOR TV SERVICING

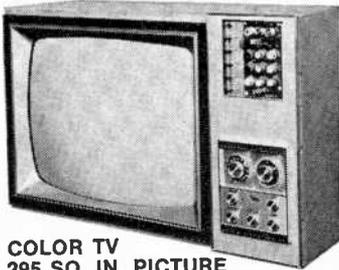


**COLOR TV  
295 SQ. IN. PICTURE**

NTS training provides an easy way to become a professional home-entertainment service technician. You receive a big screen Color TV with many unique features. The unit even includes self servicing equipment that permits you to make all normal test operations. No additional test equipment is needed for adjusting your set. In addition you get an AM-SW radio, Solid-State radio, Field-Effect Transistor Volt-Ohm-meter, and Electronic Tube Tester. You learn about Electronic principles and trouble shooting, hi-fi, multiplex systems, stereo, and color TV servicing.
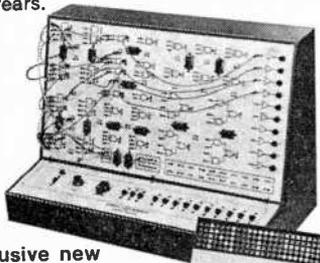
## NTS COMPUTER ELECTRONICS

This is the future. And it's happening now. The number of computers will increase many times in the next few years.



**Exclusive new Compu-Trainer®**

If card is missing check coupon and mail for free color catalog and sample lesson. Now.

### National Technical Schools

4000 S. Figueroa St., Los Angeles, Calif. 90037

Please rush Free Color Catalog and Sample Lesson, plus information on course checked below. No obligation. No salesman will call.



NTS offers a solid grounding in computer operation, wiring, data processing and programming. One of the 10 important kits included is our exclusive Compu-Trainer®. It's a fully operational computer logic trainer — loaded with integrated circuits — the first ever offered in home study. It introduces you quickly to how, what, when and why of computers ... from theory to practical servicing techniques. This unit is capable of performing 50,000 operations per second.

## NTS ELECTRONICS COMMUNICATIONS


Choose from two exciting courses to get into the big-paying fields of transmitting and receiving equipment: (1) The FCC License Course. (2) The Master Course in Electronic Communications (more comprehensive, with Citizens' Band Two-Way-Radio). Either Communications program qualifies you for your FCC First Class Commercial Radio-Telephone License — *NTS assures you will pass this FCC exam within six months after successfully completing your course or your tuition is refunded.* Kits include an Amateur-Phone 6 Meter VHF Transceiver — NTS exclusive, 6 transistor Solid-State Radio, Volt-Ohmmeter (fully transistorized).



**5 Watt AM Transmitter/Receiver**
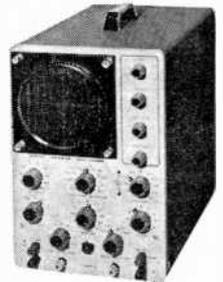
## NTS AUTOMATION/ INDUSTRIAL ELECTRONICS

Let NTS put you into the age of electronic controls. Systems Automation is rapidly becoming the emphasis of modern industry. Your NTS training in automation electronics includes equipment like a 5" wide band Oscilloscope. You also get the new NTS Electronics Lab. It's an exclusive NTS experimental laboratory — a complete workshop that simplifies learning about solid-state, miniature and integrated circuits.



**5" Oscilloscope**

## CLASSROOM TRAINING AT LOS ANGELES

You can take classroom training at Los Angeles in sunny Southern California. NTS occupies a city block with over a million dollars in facilities devoted exclusively to technical training. Check box in coupon.

## NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

4000 South Figueroa Street  
Los Angeles, Calif. 90037, U.S.A.

## APPROVED FOR VETERANS

Accredited Member: National Association of Trade and Technical Schools; National Home Study Council.

- Master Course in Color TV Servicing
- Color TV Servicing
- Master Course in TV & Radio Servicing
- Practical TV & Radio Servicing
- Master Course in Electronic Comm.
- FCC License Course
- Master Course in Electronics Tech.
- Industrial and Automation Electronics
- Computer Electronics
- Basic Electronics


Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

- Check if interested in Veteran Training under new G.I. Bill
- Check if interested only in Classroom Training at Los Angeles

Dept. 205-110

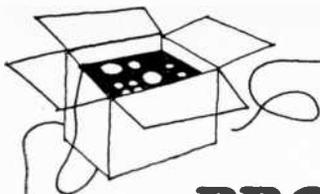

# NEW PRODUCTS

Additional information on products described in this section is available from the manufacturers. Each new product is identified by a corresponding number on the Reader Service Page. To obtain additional information on any of them, circle the number on the Reader Service Page, fill in your name and address, and mail it in accordance with the instructions.

**XCELITE SOCKET WRENCH SET**—An interesting and quite useful innovation in socket wrenches is a new set from *Xcelite Inc.*, in which a plastic-handled nutdriver can also be used as an extension for a reversible ratcheting handle. The ratchet handle (with a fully enclosed mechanism) fits into a socket on top of the plastic driver. A conventional 2" extension fits on the ratchet on either end of the spinner/extension so that the reach of the assembled components can be varied from 1½" to 9¼". Nine sockets have hex sizes from 3/16" through ½". Two dual-purpose sockets, with openings of ¼" and 5/16" fit both square and hex nuts, bolts, pipe plugs, etc. The No. 1001 set comes in a snap-lock molded plastic case.

Circle No. 78 on Reader Service Page 15



**TANDBERG STEREO TAPE DECK**—For those who want a quality tape recorder but are willing to forego some of the frills and doodads to get it at a moderate price, *Tandberg of America, Inc.* has introduced a new Model 3000X. With four heads (record, playback, erase, and crossfield), it operates at 1½, 3¾, or 7½ in/s. For the highest speed, the frequency response is 40 to 20,000 Hz ±2 dB, and wow and flutter are better than 0.07% rms. Crosstalk attenuation at 1000 Hz, stereo, is 50 dB. The crossfield system uses a separate bias head that thoroughly magnetizes and reduces the on-tape recording zone as well as wavelength dependability losses in the function.

Circle No. 79 on Reader Service Page 15

**UNIMETRICS MULTI-BAND RECEIVER**—For the boatman, hunter, or pilot trying to home in on a signal, the Omniband-VI, made by *Unimetrics, Inc.*, has a 180° rotating radio directional finder antenna. The solid-state receiver has six bands: 180-380 kHz (longwave); 540-1600 kHz (standard AM); 1.6-4.0 MHz (AM marine); 88-108 MHz (standard FM); 108-136 MHz (VHF/AM aircraft); 147-174 MHz (VHF/FM marine, weather, public service, etc.). Variable squelch, battery/ac power, 4" speaker, and battery strength indicator are also included.

Circle No. 80 on Reader Service Page 15



**BITRAN DIGITAL READOUTS**—Ready-to-use seven-segment digital readout devices from *Bitran* are available with 2 through 8 digits as well as several special symbols. Model 400 readouts have one side of each lamp common and the other terminated at printed circuit board. Model 500 includes the RCA CD2503E decoder drivers which re-

# Need an 80-db blast?

Actual size



You'll get it from our 1¼-ounce Sonalert® electronic audible signal.

With as little as 6 VDC and 3 ma., Sonalert produces a piercing sound that's hard to ignore. Yet it weighs only a couple of ounces because it's all solid state. Even the transducer is a crystal. This makes Sonalert reliable, efficient and long lasting. And because it's solid state, there's no danger of arcing, no RFI or EMI noise.

Standard units vibrate at a fixed frequency of  $2900 \pm 500$  Hz or  $4500 \pm 500$  Hz depending

® Registered trademark, P. R. Mallory & Co. Inc.

on model. Pulsing, warbling and AC models are also available. The penetrating sound covers a wider area than alarm lights and demands instant action. Examples: electrical overload, computer error, automobile door ajar, headlights-on warning, shipboard, communications alarms, etc.

For an informative 48-page booklet of projects and circuit ideas, write for folder No. 9-406. Address Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., Indianapolis, Indiana 46206.

**MALLORY**

**MALLORY DISTRIBUTOR PRODUCTS COMPANY**

a division of P. R. MALLORY & CO. INC.  
Box 1556, Indianapolis, Indiana 46206. Telephone: 317-636-6363


Batteries • Capacitors • Cassette Tapes • Controls • Resistors • Semiconductors • Sonalert® • Switches • Timers • Vibrators • ICs

CIRCLE NO. 19 ON READER SERVICE PAGE

## NEW PRODUCTS CONTINUED FROM PAGE 22


quire four line BCD inputs (8421 code) DTL or TTL logic level. Model 600 has decoder drivers and a resettable TTL decade up counter. Two-digit unit is 3 $\frac{3}{4}$ " long with 1" added for each additional digit.

Circle No. 81 on Reader Service Page 15

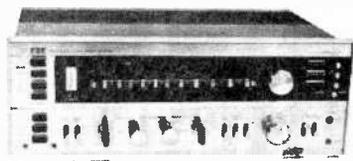

**BRITISH INDUSTRIES HI-FI/STEREO**—New to the United States is the BIC/LUX line of receivers, amplifiers and tuners from *British Industries Co.* Six components are now available: Two AM/FM stereo receivers, an AM/FM stereo amplifier, a stereo amplifier, and two AM/FM stereo tuners. The premium set is Model 71/2R AM/FM stereo receiver which has tuning via computer for complete noise suppression, 4 gang FET cascode varactor tuner, and a "center tune light" to indicate best tuning. Output is 150 watts rms (both channels driven) with a frequency range of 10 to 50,000 Hz and power bandwidth of 15 to 30,000 Hz at a THD of 0.5%  $\pm$  1 dB.

Circle No. 82 on Reader Service Page 15

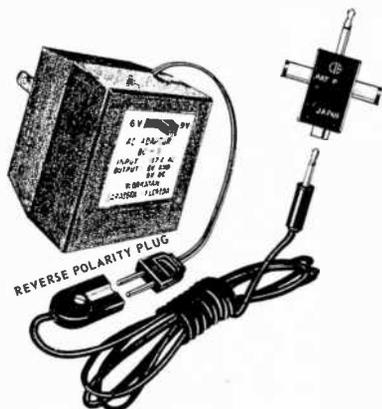


**WORKMAN AC ADAPTER**—Some portable radios and tape recorders require a "plus" dc supply—others take a "negative" supply. The *Workman* Model BC9 AC Adapter has a polarity-reversing plug which makes it usable with any type of system. It also has a four-way plug which makes it compatible with 3.5-mm plugs, 3.5-mm jacks, 2.1-mm coax power plugs, 2.5-mm coax power plugs, and 2.5-mm miniature plugs. Input is 117 volts ac; output either 6 or 9 volts dc.

Circle No. 83 on Reader Service Page 15

**MURA STEREO HEADSET**—Private stereo listening gets a boost with a headset which has volume and tone controls for each ear and a stereo/monaural switch and adjustable padded leatherette headbands. This is Model SP-104 from *Mura Corp.* It also has oversized foam-filled earpieces which completely surround the ear to eliminate external noise and give greater comfort. Other models in the line (SP-103, -102, -101) have, progressively, fewer refinements and, hence, lower costs. All four have a frequency range of 20 to 20,000 Hz and an impedance of 8 ohms. Maximum input of the SP-104 is 300 mW and maximum output is 3 watts.

Circle No. 84 on Reader Service Page 15

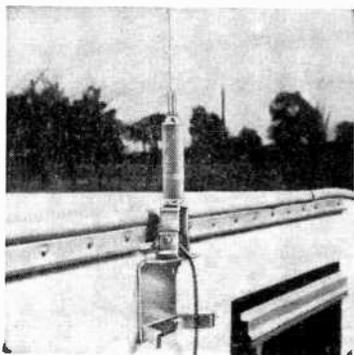

**ANTENNA SPECIALISTS MOBILE CB ANTENNA**—Outdoorsmen who use citizens two-way radio (CB) will welcome the new Model M-189 from *The Antenna Specialists Co.* It can be mounted on almost any level or slanted surface because of a special swivel base and full 90° vertical adjustment. Thus it is easy to install on campers, trailers, trucks, buses, etc. The antenna has a high-efficiency loading coil, is completely weatherproof, and has a tapered stainless steel whip.

Circle No. 85 on Reader Service Page 15


# THE CALECTRO SUPERMARKET

## EVERYTHING IN ELECTRONICS!


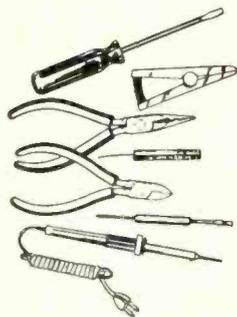
### VARIABLE BALANCE STEREO HEAD PHONE

Unique "Sound Level" control on each earpiece permits adjustment. Frequency range: 20 to 20,000 + cps. 6 1/2' cord with stereo plug. Impedance 4 to 16 ohms. Cat. No. Q4-132 \$17.95 Net



### HOBBYIST'S SOLDERING AND TOOL KIT

Diagonals, long nose pliers, soldering iron and solder, solder aid tool, heat-sink, and screwdriver. An ideal gift item. Cat. No. H3-378 \$7.95 Net.




### TAPE RECORDER MICROPHONE

Outstanding performance on music and speech for the price. Low impedance matches late model solid state recorders. Removable desk stand; 4 1/2' cord with dual plugs that fit most models. Freq. Response: 100-8k Hz. Output: -77 dB, impedance: 200 ohms. Cat. No. Q4-146 \$4.95 Net


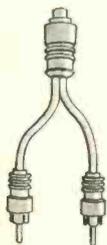
### EXPERIMENTER'S CIRCUIT BOARD KIT

Contains a 3 1/4" x 4" perforated board, 15 terminals (No. J4-636) and 4 mounting feet w/screws. Build small circuits, hobby and science projects, etc. Cat. No. J4-660 \$.98 Net




### AUDIO ADAPTORS

"Y" Audio Adaptor has a phono pin jack on one end and dual pin plug on the other. Cat. No. Q4-288 \$.99 Net


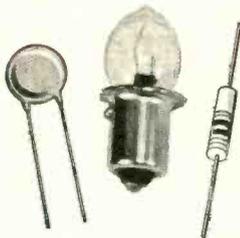
### TWO STATION WIRELESS INTERCOM

Just plug into any electrical outlet. Completely portable. Expand system anytime with additional units. Two unit system complete in display pack. Cat. No. N4-110 \$34.95 Net



### MINIATURE LAMPS

Type PR2 • 2.5 volt • 0.50 amp • Cat. No. E2-430 • Pkg. of 2 \$.29 Net  
Type PR3 • 3.6 volt • 0.50 amp • Cat. No. E2-431 • Pkg. of 2 \$.29 Net

### RESISTORS

Attractively packaged 2 per pack, showing values, color codes and formulas.

### STANDARD 1000 VOLT CAPACITOR

High quality, compact and reliable.



### THE "GC CALECTRO HOBBYIST HANDBOOK"

The "GC Calectro Hobbyist Handbook" is available at your nearest Calectro Electronic Supermarket. One is located near you. WRITE TODAY and we'll rush you the name and address of your nearest Calectro Supermarket.



# CALECTRO

G-C ELECTRONICS  
A DIVISION OF  
HYDROMETALS, INC.



400 SO. WYMAN ST. ROCKFORD, ILLINOIS 61101

# THEY CAN TURN INTO A MULTI-

## ALASKA

Anchorage  
Team Electronics  
404 E. Fireweed Lane  
ARIZONA  
Phoenix  
Black and Ryan  
2545 East Washington St.  
Paris Electronic of Arizona  
310 North Seventh St.  
Yuma  
Yuma Electronics Supply  
4th and Orange Ave.

## ARKANSAS

Fayetteville  
David White Electronics  
117 West Rock St.  
Little Rock  
David White Electronics  
222 Main St.  
Texarkana  
Lavender Electronics  
518-520 East 4th St.  
CALIFORNIA

Burbank  
Electronic City, Inc.  
4001 W. Burbank Blvd.  
Canoga Park  
Sandy's Electronic Supply  
21305 Salicoy St.  
Goleta  
Dow of Goleta  
5857 Hollister St.  
Hollywood  
Yale Radio Electric Company  
6616 Sunset Blvd.  
La Puente  
Klausner Electronics, Inc.  
5418 Fairgrove Ave.  
Los Angeles  
Radio Products Sales  
501 South Hill St.  
RCA Distributing Corporation  
6051 Telegraph Road  
(213) 478-7868  
In Burbank, call (213) 842-8155  
In Culver City, call (213)  
391-6764  
In Glendora, call (213) 963-6817  
In Hawthorne, call (213)  
676-9088  
In Huntington Beach, call (714)  
968-3329  
In Imperial Beach, call (714)  
424-5121  
In La Habra, call (714) 697-6751  
In Lancaster, call (805) 942-8444  
In Pasadena, call (213) 795-5951  
In San Bernardino, call (714)  
889-9777  
In San Diego, call (714) 324-3201  
In Tustin, call (714) 838-1122  
In Van Nuys, call (213) 786-4410  
In Wilmington, call (213)  
835-3293  
In Yucaipa, call (714) 797-1907

Oxnard  
Dow of Oxnard  
921 S. Oxnard Blvd.  
Pasadena  
Dow of Pasadena  
1759 E. Colorado Blvd.  
Sacramento  
Dunlap Electronics  
1800 18th St.  
San Francisco  
Hauer Electronic Supply  
281 Ninth St.  
San Diego  
Dow/Sound City  
3686 El Cajon Blvd.  
Santa Barbara  
Lombard's Electronic Supply  
5152 Hollister Ave.  
Santa Maria  
Lombard's Electronic Supply  
1835 South Broadway  
South Gate  
Mac's Electronics  
3351 Tweedy Blvd.  
Thousand Oaks  
Sandy's Electronic Supply  
369 Hampshire Rd.

## COLORADO

Arvada  
Team Electronics  
Arvada Plaza Shopping Center  
9232 West 58th Avenue  
Boulder  
Burstlein-Applebee Co.  
Basemar Shopping Center  
Colorado Springs  
Team Electronics  
3102 Gomer Ave.  
Denver  
Burstlein-Applebee Co.

## CONNECTICUT

Norwalk  
Arrow Electronics, Inc.  
18 Isaac St.

## DELAWARE

Dover  
Standard Electronics of  
Delaware, Inc.  
1277 So. Governors Ave.  
Wilmington  
Radio Electric Service Co. of  
Delaware  
3601 No. Market St.

## FLORIDA

Tallahassee  
Lafayette Radio Electronics  
Assoc. Store  
Northwood Mall

## ILLINOIS

Chicago  
Allied Electronics Corporation  
2400 W. Washington Blvd.  
Howard Electronic Sales, Inc.  
4573 S. Archer Ave.  
Joseph Electronics, Inc.  
1733 N. Harlem Ave.  
North Central Electronic  
Supply Co.  
3412 W. Bryn Mawr  
Viking Sales Corp.  
8300 W. Addison Street  
Decatur  
Klaus Radio & Electric Co.  
370 E. Cerro Gordo  
Des Plaines  
RCA Distributing Corporation  
424 E. Howard Ave.  
Downers Grove  
Healthki Electronic Center  
224 Ogden Ave.  
Evanston  
Tri-State Electronics Corp.  
707 West Howard St.

LaSalle  
Klaus Radio & Electric Co.  
1055 1st Street

Niles  
Joseph Electronics, Inc.  
8024 N. Milwaukee Ave.  
Peoria  
Klaus Radio & Electric Co.  
8400 N. Pioneer Parkway  
Quincy  
Klaus Radio & Electric Co.  
1101 Broadway

Rock Island  
Team Electronics  
1714 5th Avenue

Waukegan  
Badger Electronics, Inc.  
1105 Washington St.

## INDIANA

Anderson  
Seybert's Electronic Supply  
14 & Main Streets  
Bloomington  
H. A. Williams & Son  
204 South Rogers Street  
Evansville  
Ohio Valley Sound, Inc.  
20 E. Sycamore St.  
Fort Wayne  
Fl. Wayne Electronics Supply, Inc.  
3605 E. Maumes Ave.

Indianapolis  
Graham Electronics-Glendale Inc.  
6101 N. Keystone Ave.  
Graham Electronics Supply, Inc.  
133 S. Pennsylvania St.  
Munier Electronic Supply, Inc.  
3409 E. Washington St.

Jeffersonville  
Moakler Electronics  
500 E. Chestnut St.  
Lafayette  
Lafayette Radio Supply, Inc.  
408 E. North St.

Muncie  
Muncie Electronic Supply, Inc.  
222 North Madison St.  
South Bend  
Radio Distributing Company, Inc.  
1212 South High St.

Terre Haute  
Midwest Supply Electronics, Inc.  
2015 Garfield Ave.  
Vincennes  
Ohio Valley Sound, Inc.  
902 Main St.

## IOWA

Cedar Rapids  
Team Electronics  
216 8th Street, S. E.  
Davenport  
Klaus Radio & Electric Co.  
322 E. 4th St.

## TCR Distributors

1205 East River Drive  
Des Moines  
Radio Trade Supply Co.  
1013-17 High St.

Team Electronics  
1718 6th Ave.  
Dubuque  
Team Electronics  
20 South Main St.

Fort Dodge  
Team Electronics  
2307 5th Ave., South  
Hason City  
Team Electronics  
30 First Avenue, S. W.

Sioux City  
Team Electronics  
2015 4th St.  
Waterloo  
Team Electronics  
1310 Headford Avenue

KANSAS  
Garden City  
Team Electronics  
215 W. Kansas Avenue

Hutchinson  
Acme Radio & TV, Inc.  
313 N. Main  
Team Electronics  
4 South Main St.

Overland Park  
Burstlein-Applebee Co.  
Pittsburg  
Pittsburg Radio Supply  
212 South Broadway

Wichita  
Amateur Radio Equipment Co., Inc.  
203 East Douglas St.  
Team Electronics  
764 North West Street

Team Electronics  
812 S. Woodlawn

KENTUCKY  
Bowling Green  
Randolph, Hale & Meredith, Inc.  
98 State St.  
Louisville  
P. I. Burk's Company, Inc.  
842 South Seventh St.

Peerless Electronics Equipment  
Co.  
1815 So. 7th St.  
Owensboro  
Ohio Valley Sound Inc.  
600 West 3rd St.

LOUISIANA  
Metairie  
Pelican Electronic Supply Co.  
3321 Division St.  
New Orleans  
Southern Radio Supply Co.  
1909 Tulane Ave.

Shreveport  
B & S Electronics, Inc.  
2618 Southern Ave.

MAINE  
Portland  
Commercial Distributors  
8 Somerset St.

MARYLAND  
Aberdeen  
Harco Electronics, Inc.  
Carsins Run - Rt. 22  
Hyattsville  
Mark Electronics, Inc.  
3005 Hamilton St.

Salisbury  
Standard Electronics  
Supply Co., Inc.  
701 Snow Hill Road

MASSACHUSETTS  
Boston  
DeMambo Radio Supply Co.  
1095 Commonwealth Ave.  
A. W. Mayer Co., Inc.  
895 Boylston St.

Sager Electrical Supply Company  
172 High St.  
Brockton  
Ware Radio Supply Corp.  
913 Centre St.

Lynn  
Linn Electronics Supply Co., Inc.  
9R Franklin St.

Melrose  
Melrose Sales Company, Inc.  
166 Tremont St.  
New Bedford  
C. E. Beckman Company  
11-35 Commercial St.

MICHIGAN  
Adrian  
Wedemeyer Electronic Supply Co.  
2921 Treat Road

Ann Arbor  
Wedemeyer Electronic Supply Co.  
2280 Industrial Highway  
Benton Harbor  
Collax Co.  
1485 M-139 Bldg. #2

Clawson  
Radio Supply and  
Engineering Co., Inc.  
1203 West 14 Mile Road  
Detroit

Healthki Electronic Center  
18645 West 8 Mile Road  
Radio Specialties Co., Inc.  
12775 Lyndon

Riss Electronic Supply Co.  
14405 Wyoming Ave.  
Ferndale  
Midway Electronics Supply  
990 West 8 Mile Road

Flint  
Shand Electronics, Inc.  
2401 South Dort Highway  
Jackson  
Wedemeyer Electronic Supply Co.  
1617 E. Michigan Ave.

Lansing  
Wedemeyer Electronic Supply Co.  
800 Merrill Ave.  
Menominee  
Team Electronics  
M & M Plaza, P.O. Box 212

Roseville  
Radio Specialties Co., Inc.  
27882 Grafton Ave.  
Saginaw  
Morley Brothers, Inc.  
475 Holland Road

Wyandotte  
Radio Specialties Co., Inc.  
2833 Fort Street

MINNESOTA  
Duluth  
Team Electronics  
2954 Miller Trunk Hwy.

Eveleth  
Team Electronics  
306-312 Grant Avenue  
Hibbing  
Team Electronics  
112 E. Howard St.

Mankato  
Team Electronics  
Madison East  
Minneapolis  
Team Electronics  
337 E. Hennepin Avenue

Team Electronics  
2640 Hennepin Avenue  
Team Electronics  
6413 Lyndale Ave. South

Team Electronics  
470 29th Avenue S. E.  
Moorhead  
Team Electronics  
115 8th St. South

Rocheater  
Team Electronics  
102 4th Street S. E.  
St. Cloud  
Team Electronics  
117 5th Avenue, South

St. Paul  
Team Electronics  
455 Rice Street  
Team Electronics  
1534 White Bear Avenue

Willmar  
Team Electronics  
920 E. Litchfield

MISSISSIPPI  
Gulfport  
E. A. Helwick Electronics  
2214 25th Ave.

Hattiesburg  
Gillilands Electronics  
216 South Main St.  
Jackson  
Swan Electronics, Inc.  
342 North Gallatin St.

Teague Electronics  
716 S. Gallatin St.

MISSOURI  
Columbia  
Missouri Cable Co., Inc.  
107 North 7th St.

Joplin  
Teleradio, Inc.  
1610 Main St.  
Kansas City  
Burstlein-Applebee Co.

Team Electronics  
10117 State Line Road  
Lee's Summit  
Burstlein-Applebee Co.  
244 North Odham Parkway

# YOUR AM RADIO AND RECEIVER!

**St. Ann**  
Radonics Electronics  
10525 St. Charles Rock Road  
**St. Joseph**  
St. Joseph Radio & Supply Co.  
720 South Ninth St.  
**Sedalia**  
Radio & Television  
Supply Co., Inc.  
321 E. Main St.  
**Springfield**  
Burstin-Applebee Co.  
1904 South Glenstone Blvd.

**MONTANA**  
**Billings**  
Team Electronics  
2501 Grand Avenue  
**Bozeman**  
Team Electronics  
235 West Main Street  
**Great Falls**  
Team Electronics  
718 13th Street, North  
**Missoula**  
Team Electronics  
1805 South Avenue, West

**NEBRASKA**  
**Lincoln**  
Team Electronics  
2055 "O" Street  
**North Platte**  
Corr & Johns Radio &  
TV Supply Co.  
108 E. Front St.  
**Omaha**  
Team Electronics  
3901 Leavenworth St.  
Team Electronics  
12100 West Center Road,  
Bel Air Plaza

**NEVADA**  
**Las Vegas**  
Electronic Supply Company  
1112 So. Casino Center Blvd.  
**NEW HAMPSHIRE**  
**Concord**  
Evans Radio, Inc.  
Box 893

**NEW JERSEY**  
**Atlantic City**  
Radio Electric Service Company  
of N.J.  
452 No. Albany Ave.  
**Berlin**  
Midstate Radio Supply Co.  
157 W. White Horse Pike  
**Bridgeton**  
Midstate Radio Supply Co.  
653 N. Pearl St.  
**Burlington**  
Rein Distributors, Inc.  
Rt. 130 & Wood St.  
**Camden**  
General Radio Supply Co., Inc.  
527 Cooper St.  
Radio Electric Service Co. of Pa.  
211 Market St.  
**Cape May**  
Mylron Electronics Corporation  
1400 Texas Ave.  
**Mt. Holly**  
Radio Electric Service Company  
of N.J.  
192 Rancocas Road  
**Springfield**  
Route Electronics, Inc.  
Echo Plaza—Rt. 22  
**Totowa**  
Arrow Electronics, Inc.  
225 Route 46 W  
**Union City**  
NIDISCO Inc.  
2612 Kennedy Blvd.

**NEW MEXICO**  
**Farmington**  
Lektrotron Supply Co.  
1817 E. 20th St.

**NEW YORK**  
**Belhpage**  
S & R Electronics  
4020 Hempstead Turnpike  
**Buffalo**  
Summit Distributors, Inc.  
916 Main St.  
**Farmingdale**  
Arrow Electronics, Inc.  
900 Route 110  
**Hempstead**  
Electronic Equipment Co., Inc.  
741 Peninsula Blvd.  
Standard Parts Corporation  
277 No. Franklin St.  
**Hornell**  
Hornell Electronics  
266-288 Main St.

**Lindenhurst**  
Barstun Electronics  
26-28 East Sunrise Highway  
**Mineola**  
Arrow Electronics, Inc.  
525 Jericho Turnpike  
**Manuett**  
Arrow Electronics, Inc.  
195 W. Rt. 59  
**New York**  
Arrow Electronics, Inc.  
97 Chambers Street  
Dale Electronics Corp.  
244 West 14th St.  
Harvey Radio Group  
2 West 45th St.  
**Rochester**  
Rochester Radio Supply Co.  
140 West Main St.  
**Troy**  
Trojan Electronic Supply Co., Inc.  
15 Middleburg St.

**NORTH DAKOTA**  
**Bismarck**  
Team Electronics  
2304 East Broadway  
**Grand Forks**  
Team Electronics  
1503 11th Ave. No.  
**Minot**  
Team Electronics  
209 11th Avenue S. W.

**OHIO**  
**Akron**  
Fox Radio Parts Co.  
300 Akron Square Shopping  
Center, 1615 Arlington Street  
**Canton**  
The Electronic Center, Inc.  
1300 North Cherry Ave.  
**Cincinnati**  
Hughes-Peters, Inc.  
4865 Duck Creek Road  
Ohio Appliances, Inc.  
7624 Reinhold Drive  
**Cleveland**  
United Radio, Inc.  
Summit Road & Reinhold Drive  
**Cleveland**  
Fox Audio Center  
3736 Rocky River Drive  
Hughes-Peters, Inc.  
481 East 11th Ave.  
**Main Line**  
Cleveland, Inc.  
1260 East 38th St.

**Columbus**  
Hughes-Peters, Inc.  
481 East 11th Ave.  
Ohio Appliances, Inc.  
1171 West Goodale Blvd.  
**Thompson**  
Electronic  
Supplies, Inc.  
182 East Long St.  
**Whitehead**  
Radio Co.  
124 North Grant Ave.  
**Dayton**  
Ohio Appliances, Inc.  
1611 Troy St.  
The Slots-Friedman Company  
108 N. Jefferson St.  
**Elyria**  
EL-A-Co Electronics, Inc.  
235 Lodi St.  
**Mansfield**  
Fox Radio Parts Co.  
1225 Park Avenue West  
Servex Electronic  
Distributing, Inc.  
775 Springmill Road  
**Marion**  
Servex Electronic  
Distributing, Inc.  
224 N. Prospect St.  
**Perrysburg**  
Main Line Distributors, Inc.  
Wills Day Industrial Park  
**Springfield**  
Eberle's Radio Supply, Inc.  
522 West Main St.  
**Tiffin**  
Hutch & Son  
278 No. Washington  
**Toledo**  
Hillebrand Electronic Supply  
4665 West Bancroft  
**Zanesville**  
Thompson Radio Supplies  
110 South 6th St.

**OKLAHOMA**  
**Muskogee**  
Sooner Radio & TV  
110 C Callahan St.  
**Tulsa**  
Radio, Inc.  
1000 South Main St.  
S & S Radio Supply  
537 South Kenosha

## PENNSYLVANIA

**Allentown**  
RESCO of LV  
425 Hanover Ave.  
**Bradock**  
M. Left Radio Parts Co., Inc.  
225 Braddock Ave.  
**Drexel Hill**  
Kass Electronics Distributors, Inc.  
2502 Township Line Road  
**Easton**  
RESCO of LV  
1700 Northampton St.  
**Elkins Park**  
A. G. Radio Parts Co.  
939 Township Line  
**Erie**  
Mace Electronics  
2631 West 8th Street  
**Hazleton**  
Moyer Electronic Supply Co.  
758 N. Locust St.

**Hyde**  
Clearfield Electronic Supply Co.  
**Washington Ave.**  
Norristown  
Phila Electronics, Inc.  
624 W. Airy St.  
**Philadelphia**  
Herbach & Rademan, Inc.  
401 E. Erie Ave.  
**Phila Electronics, Inc.**  
1225 Vine St.  
Radio Electric Service Co. of Pa.  
6587 Roosevelt Blvd.  
Radio Electric Service Co. of Pa.  
7th and Arch Streets  
**Steinberg Electronics, Inc.**  
233 North 4th St.  
Eugene G. Wile  
218 South 11th St.  
**Pittsburgh**  
Cameroadio Co.  
2801 Liberty Ave.  
**Reading**  
Barbey Electronics  
2300 4th St.  
Upper Darby  
Radio Electric Service Co. of Pa.  
7911 Westchester Pike  
**SOUTH CAROLINA**  
**Charleston**  
Wholesale Radio Supply Co.  
3701 Rivers Ave.  
**Columbia**  
Distie Radio Supply Co.  
1900 Barnwell St.

**SOUTH DAKOTA**  
**Rapid City**  
Team Electronics  
1101 Omaha Street  
**Sioux Falls**  
Team Electronics  
613 West 41st St.  
**Warren**  
Radio Supply  
196 E. 6th St.  
**Watertown**  
Team Electronics  
223 9th Ave. S. E.

**TENNESSEE**  
**Memphis**  
Bluff City Distributing Co.  
234 East Street  
**Nashville**  
Electra Distributing Company  
1914 West End Ave.  
**Union City**  
Bluff City Distributing Co.  
306 South 2nd St.  
**Austin**  
Modern-Electrolex  
914 W. 12th St.  
Sterling Electronics, Inc.  
1712 Lavaca  
**Corpus Christi**  
Modern-Electrolex  
1800 Ayers St.  
**Dallas**  
Adleta Electronics Co.  
1314 Cedar Springs  
Southwest Radio Supply Co.  
1820 N. Harwood St.  
**Greenville**  
Lavender Electronics  
2311 Washington  
**Houston**  
Electrolex  
2300 Richmond Ave.

**Sterling Electronics**  
4201 Southwest Freeway  
Sterling Home Electronics  
3118 Smith  
Sterling Home Electronics  
8404 Winkler Drive  
Lubbock  
Nurn Electric Supply Corp.  
1817 4th St.  
**Odessa**  
Midland Specialty Company  
2101 Andrews Highway  
**Paris**  
Lavender Electronics  
250 South Main St.  
**San Antonio**  
Modern-Electrolex  
910 W. Laurel  
Sterling Electronics, Inc.  
4600 San Pedro Ave.  
**Sherman**  
Lavender Electronics  
308 E. Houston St.  
**Tyler**  
Lavender Electronics  
503 E. Oakwood St.  
**Victoria**  
Modern-Electrolex  
1007 North William

**UTAH**  
**Ogden**  
Ballard Supply Corporation  
3109 Washington Blvd.  
**Salt Lake City**  
Team Electronics  
6237 South Highland Drive

**VIRGINIA**  
**Charlottesville**  
Graves Electronics, Inc.  
1700 Allied St.  
**Norfolk**  
Avec Electronics Corporation  
711 Granby St.  
Priest Electronics, Inc.  
6431 Tidewater Drive  
**Richmond**  
Avec Electronics Corporation  
2002 Staples Mill Road  
**Roanoke**  
H. C. Baker Sales Co., Inc.  
17-19 Franklin Road

**WASHINGTON**  
**Seattle**  
Western Electronics Co.  
717 Dexter Ave. No.

**WEST VIRGINIA**  
**Beckley**  
Halley Electronics, Inc.  
713 South Oakwood Ave.  
**Charleston**  
Electronic Materials Corporation  
1106 Central Ave.  
Mountain Electronics, Inc.  
1605 Fourth Avenue  
**Huntington**  
Electronic Supply, Inc.  
222 7th Avenue  
Van Zandt Supply Company  
1123 4th Avenue

**WISCONSIN**  
**Appleton**  
Team Electronics  
1828 West Wisconsin Avenue  
**Eau Claire**  
Team Electronics  
2321 E. Clairmont Pkwy.  
**Green Bay**  
Team Electronics  
821 Military Road  
**La Crosse**  
Team Electronics  
1505 Losey Blvd. So.

**Madison**  
Team Electronics  
3365 East Washington Avenue  
**Milwaukee**  
Amateur Electronic Supply  
4828 West Fond du Lac Avenue  
Healthkit Electronic Center  
5215 West Fond du Lac Avenue  
**Team Electronics**  
3818 West Fond du Lac Avenue  
**Manitowoc**  
Team Electronics  
1801 Marshall St.  
**Schofield**  
Team Electronics  
725 Grand Avenue

For the facts, turn the page...



Turn any AM radio into a multi-band receiver! Sophisticated in design, but so easy to build, these RCA Integrated Circuit Converter Kits "take you where the action is!" You'll monitor your local police and fire departments, tune into aircraft, ship-to-shore, ham, and even space research stations! Without interconnecting wires. Without interfering with AM reception! And, only \$10.95\* each.

- KC4007 Aircraft IC Converter Kit—tunes any AM radio to 118-136 MHz.
- KC4008 Ham, Government & Space Research IC Converter Kit (134-150 MHz).
- KC4009 Marine, Mobile, Fire, & Police IC Converter Kit (148-164 MHz).
- KC 4010 Police & Fire IC Converter Kit (160-174 MHz).

# NEW RCA IC KITS FOR THE ACTION BANDS

*Also available for home-owners, hobbyists, tape fans and students (from under \$5.00\*):*

- KC4006 Fire Alarm IC Kit.
- KC4005 Intruder Alarm IC Kit.
- KC4001 2-Channel Mixer IC Kit.
- KC4002 Audio Oscillator IC Kit.
- KC4003 Amplifier/Oscillator IC Kit.
- KC4004 9-V Regulated Power Supply IC Kit.
- KC4000 Mike Preamplifier IC Kit.


Plus the KC4500, a handsome, sturdy case for any RCA IC Kit, complete with input and output jacks, switch and hardware!

Now available at any of the distributors listed on the preceding pages.

\*optional distributor resale prices

# RCA

POPULAR ELECTRONICS

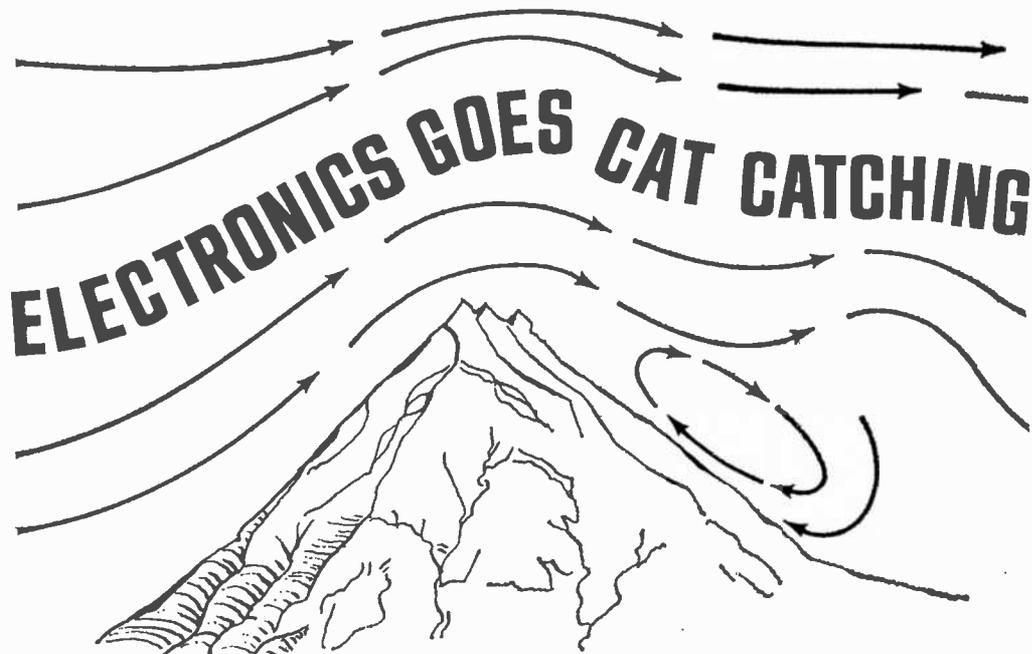

## CAN INFRARED OR LASERS FIND CLEAR AIR TURBULENCES?

**Everyone associated with flying—including the passengers—expects and knows how to avoid air turbulences associated with changes in barometric pressures such as storm centers. Most such disturbances are accompanied by clouds and are visible. Not so with other turbulences which have plagued air travel for years and for which some sort of solution is only now beginning to appear.**

**L**ATE IN WORLD WAR II when first frequently reported by military fliers, jet streams were dismissed by ground-based meteorologists as delusions. Earlier, "air pockets" that aviators of the 1940's said they hit had been chalked up to over-active imaginations.

Now clear air turbulence, or CAT, has mushroomed into the world spotlight. It's definitely linked with jet streams, lee waves created by mountain ranges, and other still-mysterious kinds of turbulence. Even the basic concept of the "air pocket" has been revived—with its label changed to "microcosmic atmospheric cell."

Government agencies, private industry, and research organizations are all trying to zero in on CAT.

Just what is this unseen phenomenon that bears a feline title?

In December, 1966, the U.S. Department of Commerce brought together a National Committee for Clear Air Turbulence. Meteorologists, pilots, physicists, and safety officials immediately found they didn't even agree on a definition of their target. From their parley came an official description: CAT consists of "all turbulence in the free atmosphere of interest in aerospace operations that is not in or adjacent to visible convective activity."


Less precise but more vivid descriptions come from veteran pilots who have had several bouts with severe CAT. One describes the encounter as "like having a pneumatic jack hammer work on your plane." Another says that a jet in the paws of CAT reacts like a car roaring over a cobblestone street at high speed.

Many but not all occurrences of CAT stem from interaction of two different kinds of wind shear. One is horizontal—caused by friction between masses of air moving side by

---

---


BY WEBB GARRISON

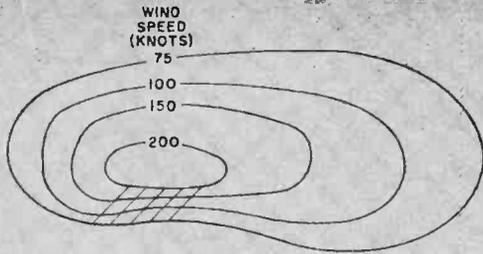

At left is a cross section of the jet stream where different layers of air move in the same direction but at different speeds. Greatest turbulences occur where the layers are close together.

Disturbances occur if two air streams of different temperature and velocity are flowing in different directions, one above the other, such as slow westerlies near ground under jet stream.

### THREE KINDS OF CAT

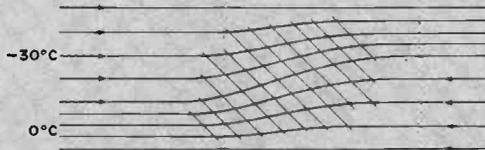

Favorite spot for CAT to hide is on the lee side of mountain ranges. Thus they may be found, for instance, up and down Atlantic Coast, east of Appalachians, and east of Rockies where plains begin.



side at different speeds. The other is vertical and is created by friction between two air masses (again moving at different speeds) that flow in relatively distinct levels, one above the other.

When first recognized to be real rather than imaginary, CAT was thought to be met at altitudes between 20,000 and 40,000 feet. Now it is known to be found as low as 6,000 feet and as high as 80,000.

New interest in it stems partly from the fact that more sophisticated instruments are just now beginning to show how deadly it can be. As late as 1964, it was suspected of having caused some spectacular crashes but had not been convicted. Last year CAT was implicated in at least eleven crashes by civilian planes. Its most formidable threat to military craft is linked with air-to-air refueling operations.

Costly programs aimed at detecting CAT and discovering what forces produce it, and why, aren't based on the relatively few crashes it now causes, however. More and more small planes are being flown by private individuals and corporations. These craft are particularly vulnerable to sudden assaults by CAT.

There's every indication that the supersonic transport (SST) will also be vulnerable in ways different in degree and kind from today's planes. Rapid cycles of vibration are likely to be set up in the SST by choppy jolts and severe lateral gusts that would simply buffet a B-52. Supersonic transports will be especially likely to encounter CAT during climb and descent—roughly 20% of the flight profile. Structural failure can result unless stresses associated with CAT are fully understood and taken into consideration by designers.

As a result the CAT which never purrs has become the subject of an all-out search. Answers are being sought to questions on subjects ranging from the nature of atmospheric energy exchanges to the optimum wavelength at which to capture radiation emitted by CO<sub>2</sub>.

Lacking the hardware produced by today's electronic technology, neither the quest for basic understanding of CAT nor attempts to detect it quickly and accurately could be undertaken.

**Radar Tried First.** Before the existence of CAT as a special meteorological phenomenon was positively established, some searchers

tried to locate it with radar. Their efforts were futile.

A break came in 1962. RCA technicians tracking missiles with C-band radar sets operating above 5,000 MHz noticed that they were getting substantial backscatter on some days when skies were clear. Could these unexpected echoes point to areas where CAT is found?

Working with U.S. Army meteorologists at Fort Monmouth, N.J., engineers added a low-noise amplifier to their radar. Early results made them jubilant; a clear, rapidly changing line on radarscopes seemed to mark the tracks of the CAT.

A press release of this era gloated that "Once they are certain they have cornered CAT, avoiding its dangerous attack will be a simple matter for the careful pilot."

In practice, it has proved to be anything but simple. Part of the difficulty lies in the size of the zone in which CAT hides. It's likely to be 400 to 500 miles long, more than 100 miles wide and two or three miles thick. A typical CAT region, on the other hand, is minute in global terms. It is seldom more than 50 to 100 miles long, 10 to 20 miles wide, and a mere 1,500 to 2,000 feet thick.

Ground-based radars such as the ultrasensitive ones at Wallops Island, Virginia, do pick up clear-air echoes. Such echoes presumably stem from scattering caused by variations in the refractive index and hence point to atmospheric levels associated with CAT.


A world-wide network of radar facilities equal to or better than those on Wallops Island would be necessary for ground-based remote detection of CAT. Even if such a network were available, computer systems with which to retrieve data in time to warn a jet pilot are far in the future. Radar's chief contribution will probably be in the area of basic understanding of CAT rather than location of turbulent areas.

This spring at the National Center for Atmospheric Research, Boulder, Colorado, fine metal chaff was dropped into the path of winds blowing over the mountains. Two Doppler radars, pointed into turbulent areas at different angles, were used to gain data. Physicist Roger Lhermitte hopes eventually to build up a three-dimensional picture of the dynamic structure of the atmosphere in target areas studied.

Outcome of the trial won't be known until all the data have been analyzed. If Lhermitte and his colleagues succeed in finding just how a turbulent area reacts, groundwork for more precise detection will have been laid.

Air-borne radar has proved useless in the search for CAT. No matter how violent its currents may be, clear air includes no solids of sufficient size to register on sets small enough to be mounted in aircraft.

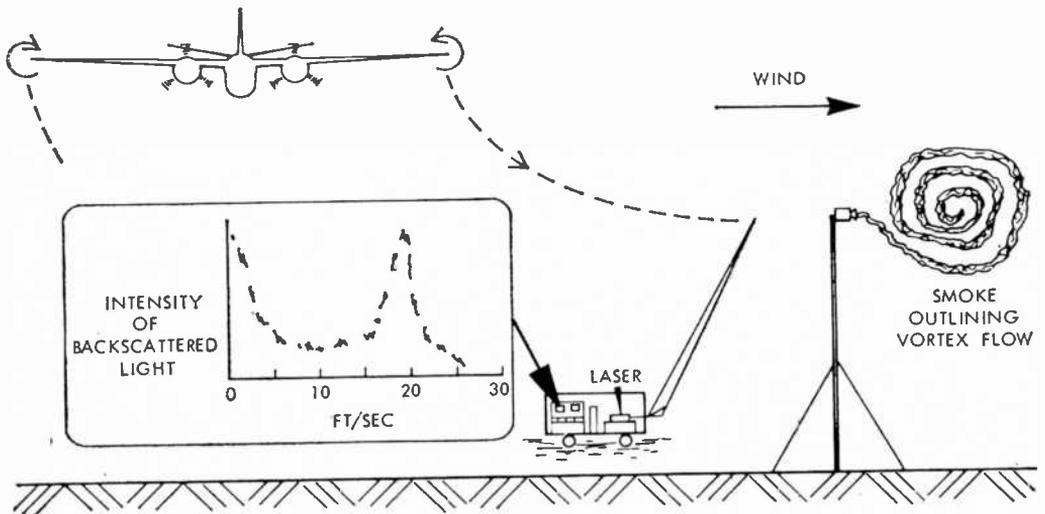**Thermal Sensors Employed.** Many rapidly moving air currents, including the jet streams, vary from the temperature of sur-



Schematic diagram of the laser doppler technique used for remote measurement of wind velocity; trailing vortex detection experiment. Varying wind velocities are one of the chief causes of CAT. (NASA diagram.)

rounding air masses by a few degrees. At least in theory, air-borne infrared sensors should pinpoint such differences—effectively substituting CAT.

North American Aviation and Barnes Engineering Company have tossed their hats in the ring in a race to develop a workable thermal sensor. Both companies had prototype systems in operation by 1967.

Electronics engineer Edward Flint of North American developed a compact infrared sensor suitable for mounting on top of a plane. Capable of scanning 45° on each side of the flight path, the instrument could detect temperature variations of less than one degree Fahrenheit in atmospheric carbon dioxide 20 to 40 miles away.

Using a Canadian T-33 jet trainer, Barnes flight-tested an instrument that used a thermistor bolometer as the sensing element. Scanning was accomplished by means of the rocking etalon assembly of a Fabry-Perot spectrometer.

Both devices worked—up to a point. Each revealed changes of temperature within distant air masses. Neither came anywhere near the then-desired range of 25 miles. Both suffered from a defect that hasn't yet been overcome: the infrared signal is passive. That is, it conveys no information about intensity of turbulence or size of the area affected. Greatly refined and recently patented, the Barnes instrument has logged enough hours on Pan Am and other commercial planes to demonstrate that it can be of great help to pilots.

Stable data were first obtained in May, 1969. That month the Barnes IRCAT was used on two long-distance flights: PA72 from New York to Frankfurt on the 20th; PA ONE from London to New York on the 29th.

In the joint program between Barnes and Pan Am, the approach utilized has been the straight horizontal forward look in the 15-micron CO<sub>2</sub> band of the infrared region at a volume of air ahead of the aircraft. Very recent findings indicate that a "two color" system tuned in to both CO<sub>2</sub> and O<sub>3</sub> would probably give more accurate information about deformation of the tropopause by vertical air mass movement. Before such a system can be put to test, additional new instrumentation will be required.

Range of the best detectors being used at present is far short of that required for an SST cruising at 2000 mph.


**New Role for Laser.** Some pioneer searchers for CAT deliberately rejected attempts at

detection by means of temperature variations. They set out, instead, to find ways by which atmospheric discontinuities may be directly observed. Laser radar, now commonly called lidar (Light Detection And Ranging) seemed to offer intriguing possibilities.

At Stanford Research Institute, M. G. H. Ligda developed pulsed-ruby-laser radar especially for atmospheric research. His system didn't perform as expected, so the Navy awarded Stanford a contract for a more complex one that employed four-headed lidar.

From this instrument and its successors, NASA's Marshall Space Flight Center moved to a laser-Doppler technique. Small particles that are caught up in a turbulent air mass create a Doppler effect by which the frequency of scattered light is shifted a trifle before it returns to a receiver.

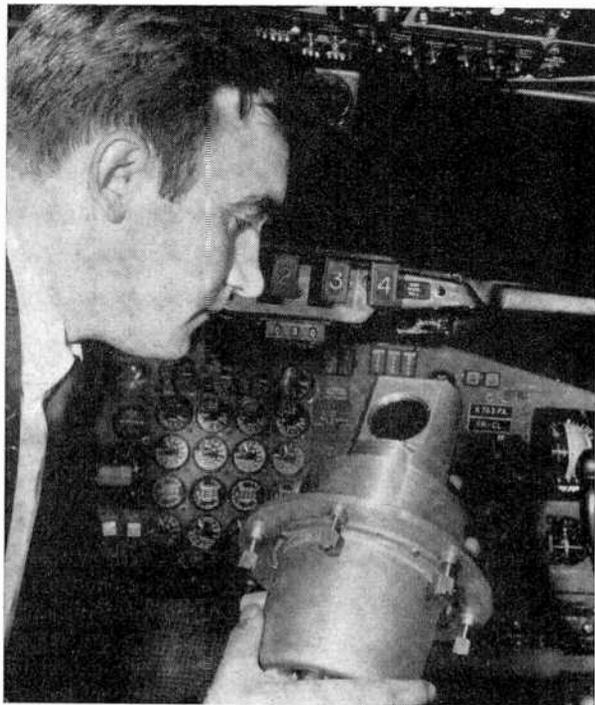At Marshall, physicist Robert M. Huffaker has developed an optical Doppler system which he says has proved itself in feasibility studies. He hopes to have an airborne version in operation early in 1971. The system operates on much the same principle as conventional Doppler radar. Instead of radio frequency, however, it employs a coherent



Sensing head of the Barnes infrared system for spotting CAT in cockpit of a Pan-Am Boeing 707.

Infrared sensor of the Barnes IRCAT is mounted on the top of Pan-Am plane to spot CAT. So far data gathered looks good.



pulse from a carbon dioxide laser. As a result, the resolution of the instrument is about 10,000 times better than that of today's conventional Doppler radar on aircraft. Radiation

employed is at 10.6 microns—out of the visible spectrum.

Most other laser systems aimed at CAT detection have been dismissed, says Huffaker, because they "just would not work." He expects to find the CO<sub>2</sub> laser-Doppler far more effective than "passive" systems that seek to infer turbulence from an indirect measurement such as temperature or intensity of back scattered light.



**Error-producing Factors.** Past experience suggests the possibility or even probability that the latest device aimed at trapping CAT will run into unexpected complicating factors. That has been the case with all equipment produced so far.

At first it was hoped that CAT could be trapped by means of conventional instruments used to measure velocity of ordinary kinds of wind. This approach proved vastly oversimplified: instruments distorted the flow to such an extent that interpretation of results was uncertain even after a plane had passed through CAT in search of data.

Radiosonde networks, extremely useful in many branches of meteorology, proved ineffective with CAT. Because this kind of turbulence is essentially a small-scale phenomenon, it usually eludes the wide-meshed radiosonde network.

Even jet streams have proved uncooperative. Early tests with a heavily instrumented T-33 were scheduled to take place from a base in Alberta, Canada. High-altitude streams are commonly found at this latitude in mid-autumn. However, operations had to be shifted

Low-frequency infrasonic waves, created when energy is released into air by various causes, is used by General Telephone & Electronics and Washington State U. to get data that will find CAT.

to California because the jet stream abruptly changed its course.

Radiometric detection, the most promising technique that has been flight-tested, has its problems, too. Unless temperature inversions are tilted with respect to the sensor, it usually fails to respond to them. Cumulonimbus clouds render present models of the IRCAT blind.

A great many false alarms, some of them produced by exhausts of jets that were miles away, indicated to Barnes engineers that they were using a wavelength too far away from the center of absorption of CO<sub>2</sub>. Now the chosen wavelength is centered at approximately 14.1 microns. This increases attenuation and minimizes detection of phenomena not associated with turbulence—but also shortens the range of the instrument.

Early tests of North American Autonetics' system (infrared) produced a great many false readings. Examination showed that some of them were produced by bodies of insects that splattered on the sensor window during climb and descent.

A relatively small mass of air whose temperature differs from that of air around it may not be sensed by the best infrared equipment now available. That's because the instrument integrates contributions from a volume of air thirty to forty miles ahead of the plane rather than measuring temperature at a given distance. When positive and negative contributions cancel one another, IRCAT can't spot microscale disturbances that are linked with CAT.

Even sharp pitching or banking so that infrared sensors looked toward the ground produced a high percentage of false alarms in early tests. This factor has been largely controlled by use of an automatic deactivation circuit that operates from aircraft attitude gyro signals. After four or five "generations" of refinement, even the best infrared detectors do not meet needs expected to become increasingly urgent as planes become faster.

**Single Solution Unlikely.** No one is absolutely sure that the shock wave ahead of an SST won't destroy the coherence of a laser beam. Growing evidence suggests that even if the laser-Doppler instrument now in development performs as well in flight as in wind tunnels, it probably won't defeat CAT singlehandedly.

Until that instrument or others on the drawing board are operational, the general consensus is that the Barnes IRCAT remains the

most effective detector available. Though it can perform as a remote sensor when clear conditions exist along the flight path, it too has limitations.

Presently, even IRCAT doesn't give navigators a clear picture of how far ahead temperature-linked turbulence is—or how severe it may be. Clouds and haze reduce the optical path length of the IRCAT and cut its range of detection. Under hazy conditions produced by ice the range becomes very short.


To make things worse, CAT probably isn't universally linked with temperature gradients. Atmospheric electrical phenomena, still largely shrouded in mystery, may be associated with many turbulent areas too clear for detection by air-borne radar.

Australian scientists have suggested (but haven't conclusively demonstrated) that, when CAT occurs in a thermally stable environment, gravity waves or Helmholtz waves somehow break down into random turbulent eddies. No detectors now in use are designed to pinpoint energy changes of this sort.


Inflight remote detectors, regardless of type, will probably have to be supplemented by ground-based CAT detectors. Bigger and bigger information networks will have to be developed. Ultimately, a global system continually receiving and rapidly processing data from great numbers of satellite-borne CAT detectors may become essential.

Some of these things are far in the future. But by refining and combining a variety of systems, experts in government and industry hope for a major break-through in the 70's. When it comes, small private craft and big supersonic ones will receive warnings in time to avoid the CAT that strikes from its invisible lair.

—50—

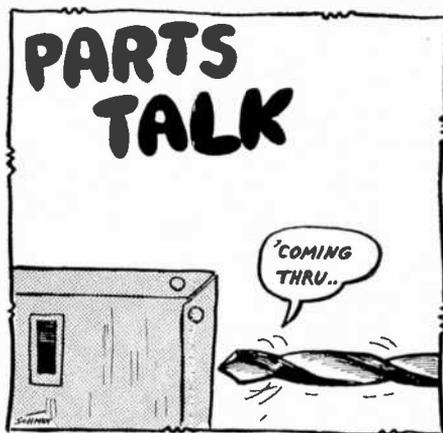

# Light-emitting Diodes

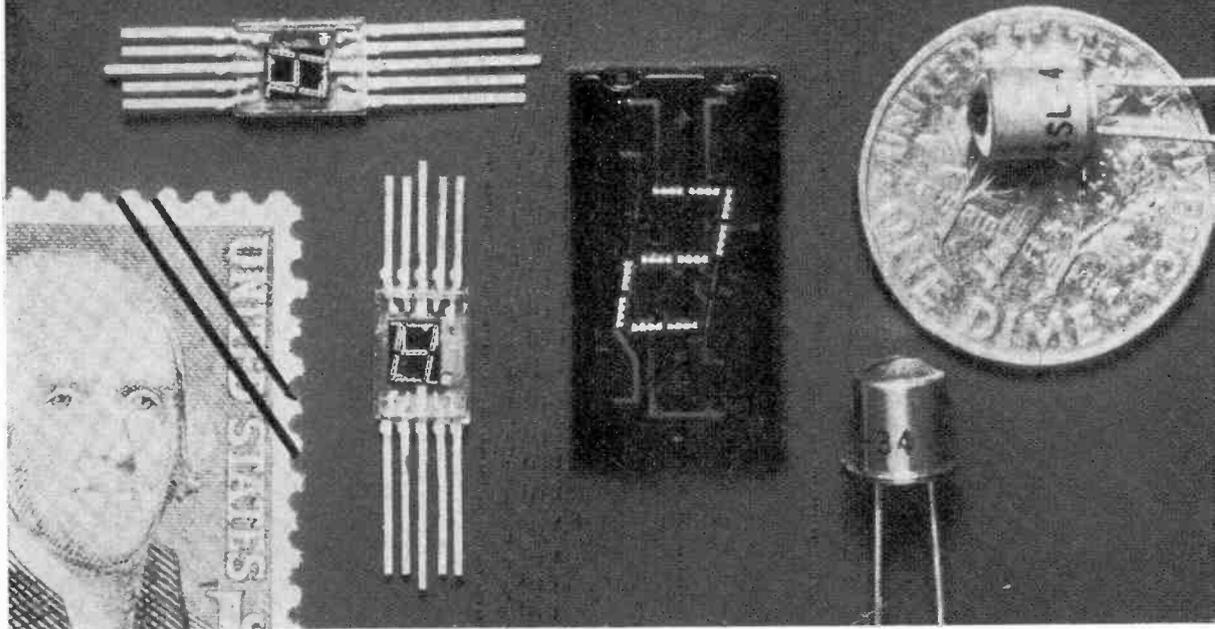

## NEW SEMICONDUCTORS FOR READOUT AND COMMUNICATION

**O**ne of the least known but most fascinating of semiconductor devices is the light-emitting diode (LED). Until quite recently, these devices were too expensive for widespread use; however, technological advances in their fabrication now make possible moderately low prices so that they are attractive to the electronics experimenter.

The first recorded instance of light being generated by a "diode" was in 1907 when H. J. Round touched a pair of battery wires to a crystal of silicon carbide. Much to his surprise, flashes of yellow light were emitted at the contact region of one of the battery wires—he had accidentally discovered the LED. Unfortunately, his discovery was forgotten and not until the early 1950's did scientists once again study semiconductor light emission. At that time several patents were applied for covering LED's made from silicon or germanium—common semiconductor materials. One of these patents not only described the principle of the


LED but listed several fascinating uses for the device. Among them were light-beam communication systems, light "radar", and light-beam alignment devices.

Unlike the 1907 silicon carbide cat whisker diode, the 1950's LED's emitted infrared light (see Fig. 1). The invisible beam was desirable but researchers began a concentrated effort to fabricate LED's in the visible range. The first company to market any kind of LED was Texas Instruments, Inc. Their diodes included infrared emitters made from gallium arsenide (GaAs) and visible emitters made of gallium arsenide phosphide (GaAsP). These diodes were expensive; but their appearance on the commercial market in 1962 whetted the appetites of design engineers—and of course was of great interest to other semiconductor manufacturers. While scientists at IBM and Bell Telephone performed basic research on the devices (especially visible emitters), General Electric, Monsanto, Electro-Nuclear Labora-

---

COVER STORY BY FORREST M. MIMS, III

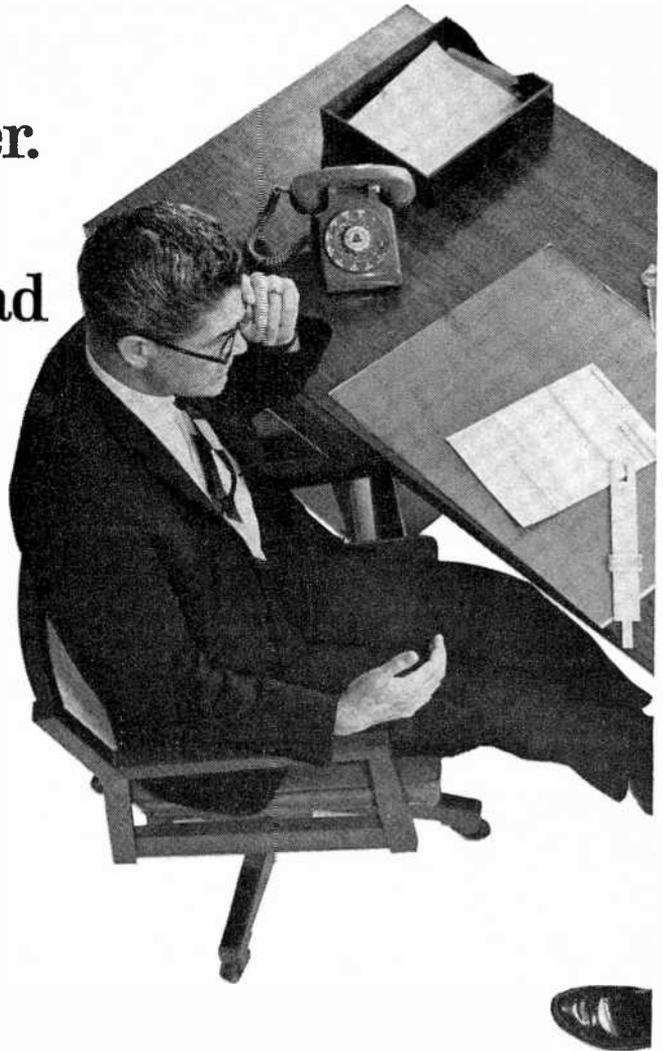**“He’s a good worker.  
I’d promote him  
right now if he had  
more education  
in electronics.”**



## **Could they be talking about you?**

You'll miss a lot of opportunities if you try to get along in the electronics industry without an advanced education. Many doors will be closed to you, and no amount of hard work will open them.

But you can build a rewarding career if you supplement your experience with specialized knowledge of one of the key areas of electronics. As a specialist, you will enjoy security, excellent pay, and the kind of future you want for yourself and your family.

Going back to school isn't easy for a man with a

full-time job and family obligations. But CREI Home Study Programs make it possible for you to get the additional education you need without attending classes. You study at home, at your own pace, on your own schedule. You study with the assurance that what you learn can be applied to the job immediately.

CREI Programs cover all important areas of electronics including communications, radar and sonar, even missile and spacecraft guidance. You're sure to find a program that fits your career objectives.



**IN-DEPTH  
 COVERAGE OF  
 SOLID STATE  
 ELECTRONICS**  
 ...including  
 integrated circuits!

You're eligible for a CREI Program if you work in electronics and have a high school education. Our FREE book gives complete information. Mail postpaid card for your copy. If card is detached, use coupon at right or write: CREI, Dept. 1211A, 3224 16th St., N.W., Washington, D.C. 20010.

**CREI, Home Study Division  
 McGraw-Hill Book Company  
 Dept. 1211A, 3224 Sixteenth Street, N.W.  
 Washington, D.C. 20010**

Please mail me FREE book describing CREI Programs. I am employed in electronics and have a high school education.

NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP CODE \_\_\_\_\_

EMPLOYED BY \_\_\_\_\_

TYPE OF PRESENT WORK \_\_\_\_\_  G.I. BILL

I am interested in


Electronic Engineering Technology  Computers

Space Electronics  Nuclear Engineering Technology

Industrial Automation  NEW! Electronics Systems Engineering

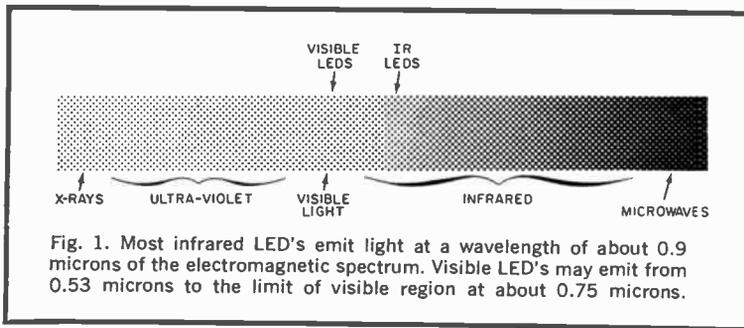**APPROVED FOR TRAINING UNDER NEW G.I. BILL**





tories and others began competing with TI. Since the LED has an almost unlimited lifetime and because of its low operating current, many claims were made for its potential in flat screen television, indicator lamps, night lights, and even as a source of room lighting. The extremely fast modulation capability of the LED made possible several demonstrations of voice communications permitting two parties to converse over a beam of invisible infrared light for clear weather distances of several miles.

**How Does It Do It?** The LED is different from conventional incandescent lamps because the latter give off light as a byproduct of heat. That is, the filament must first be heated to incandescence before light is produced. This, of course, is the reason for placing incandescent filaments in evacuated or gas-filled glass bulbs. If the filament were exposed to oxygen, it would quickly be consumed. Not so with LED's; they operate with or without the presence of air. In fact, the main reason LED's are placed in containers is to protect the rather delicate contact wires. Often, in fact, the LED is simply protected by a layer of clear epoxy which serves both as a protective cover and a lens. Since the LED produces far more light than heat, it is a more efficient source of light than the incandescent lamp.


Production of light by an LED comes under the broad heading of "electro-luminescence." Luminescence describes light produced by means other than incandescence. Since luminescing bodies are generally at the temperature of their environment, they are sometimes referred to as sources of "cold light." Fireflies, many species of fish, rotting wood, marsh gas, and many other objects are sources of luminescent light.

Light from an LED is the result of stimulation by a small electric current. As is the case with all luminescent bodies, the light is a result of sub-atomic events. The cause of these

events may be chemical, as with the firefly, or electrical as with the LED.

**Light Generation.** In the LED, emission of light is called "pn junction luminescence." As shown in Fig. 2, light is emitted at the junction of an LED when electrons which have been stimulated to higher than normal energy levels move across the junction and fall back into their normal places. The energy loss resulting when an electron reoccupies its normal slot in an atom is accompanied by the emission of a photon of light at a wavelength related to the difference in energy between the two bands. Since junction luminescence involves the combination of electrons with holes, physicists often refer to the effect as "recombination radiation."

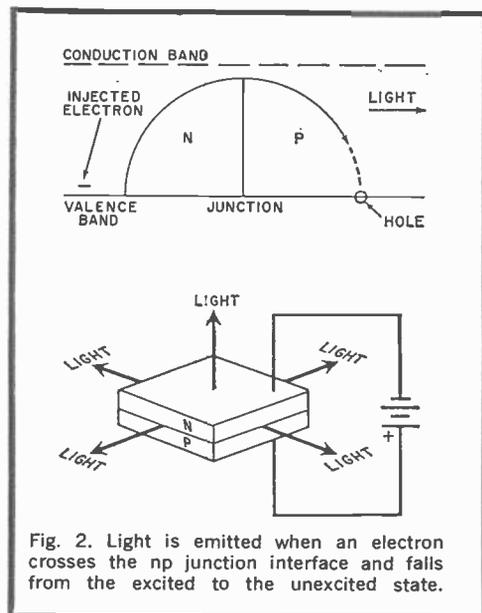The sub-atomic physics of semiconductor light emission can be highly efficient. But the mechanisms of bringing the light to the sur-



face and the application of electrical current to the diode can be terribly inefficient. Sources of inefficiency are:

1. Internal absorption of light within the p or n region of the semiconductor following its emission at the junction.

2. Reabsorption of light which is reflected back into the diode due to the "critical interface" problem.

3. Resistance at the electrical contacts and in the semiconductor.

Many of these inefficiencies have been partially resolved as a result of years of research. Consider, for example, the critical interface problem. Since most semiconductors have a high index of refraction, they tend to reflect light at air-semiconductor interfaces. The effect is similar to that of an observer looking through a glass window and seeing his own reflection as well as objects on the other

side of the window. The effect results in the loss of light that is generated at the junction.

An ingenious solution to the problem was suggested by early research and was first used commercially by Texas Instruments. It consists of forming the light emitting region of the diode into a dome. Since the light is only bent and not reflected back into the diode, all light reaching the surface is emitted (see Fig. 3). Unfortunately, the dome approach does have its drawbacks—the longer path that the light must travel before being emitted causes more internal absorption than in planar emitters. Also, grinding domed diodes is an expensive process.

In an effort to gain the benefits of both planar and domed diodes, many manufacturers now coat planar diodes with a transparent dome of epoxy which essentially serves the same purpose of the semiconductor dome.

### PHYSICS OF LIGHT EMITTING DIODES

Modern atomic physics tells us that electrons within the confines of a particular atom are allowed to occupy only discrete energy levels or bands. Energy levels between the outer two bands, the valence and conduction bands, are separated by a region called the forbidden gap. Under special conditions of doping, an electron may occupy one or more levels within the forbidden gap for relatively brief periods of time. The forbidden gap plays an important role in semiconductor light emission, since transitions from the conduction to the valence band provide the mechanism for photon generation.

An efficient way to cause transitions between the valence and conduction bands is to pump or inject electrons into the n region of a semiconductor diode. If a sufficient number of electrons is injected, the potential barrier at the junction of the n and p regions will be overcome and current will flow through the diode. Having crossed the junction barrier, the injected electrons seek their equilibrium point and drop from their excited position in the conduction band to the valence band. In essence, the electrons drop into holes or regions in a band where there is an electron deficiency.

The act of electrons combining with holes is called recombination and results in the magic of pn junction electroluminescence or light emission. An electron falling from a high to a low level releases the energy which propelled it over the junction as heat, light, or some of each. Heat emission is accompanied by vibrations in the crystal lattice and if

left uncontrolled, results in thermal destruction of the diode. Heat emission predominates in indirect band gap semiconductors such as silicon and germanium. The forbidden gap in such materials permits an electron falling from the conduction to the valence band to loiter briefly at one or more levels. Transitions between the various levels in the forbidden gap may result in either light or heat emission.

It is interesting to note that an ordinary silicon or germanium diode emits a minute quantity of infrared light when forward biased. However, light emission in such diodes is far less efficient than heat production and development of practical semiconductor light emitters followed research with direct band-gap materials.

Gallium arsenide GaAs is normally a direct band-gap material. Since electrons injected into a GaAs diode recombine with holes without pausing at intermediate levels within the forbidden gap, light emission is very efficient and production of heat is generally limited to contact resistance and bulk absorption of some of the emitted light within the semiconductor.

GaAs diodes are so efficient as light emitters that scientists chose them as candidates for early work concerning the feasibility of fabricating semiconductor lasers. In the fall of 1962, researchers at G.E., IBM, and MIT announced almost simultaneously lasers made from specially prepared GaAs diodes. In a future issue of POPULAR ELECTRONICS, the operating principles and characteristics of the diode laser will be described.

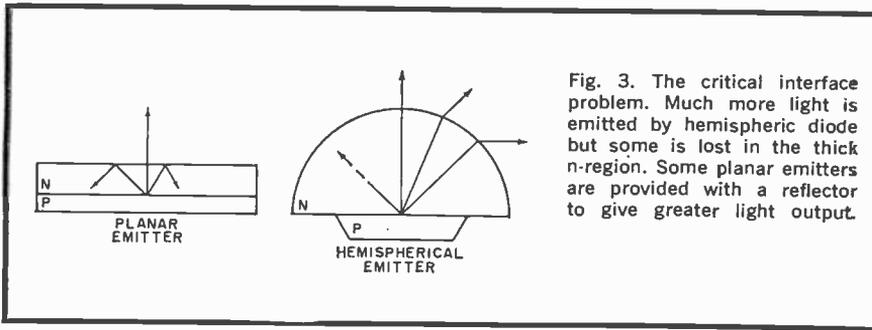


Fig. 3. The critical interface problem. Much more light is emitted by hemispheric diode but some is lost in the thick n-region. Some planar emitters are provided with a reflector to give greater light output.


**How Are They Made?** As mentioned earlier, the LED usually consists of a pn junction of one type of semiconductor, the most common being gallium arsenide. A typical diode may consist of a small wafer of positively charged (p) material in intimate electrical contact with a metal header similar to a transistor case. Before it is mounted on the header, the wafer is given a thin top layer of negatively charged (n) GaAs by either diffusion or epitaxial growth. The p portion of the finished wafer is connected to one of the wire leads of

the header, resulting in a true pn junction diode.

To collect the light output from the wafer in an efficient manner, a metal can with a lens or flat window at one end is welded to the header. The can also serves as protection (see Fig. 4).

**How Are They Used?** Now that we know something about the history, physics, and mechanical construction of the LED, what are its applications other than those found in the lab-

Fig. 4. In practical applications, the LED is mounted within a metal enclosure, similar to a transistor, for mechanical protection. A transparent window permits the light to exit from one end of the enclosure.

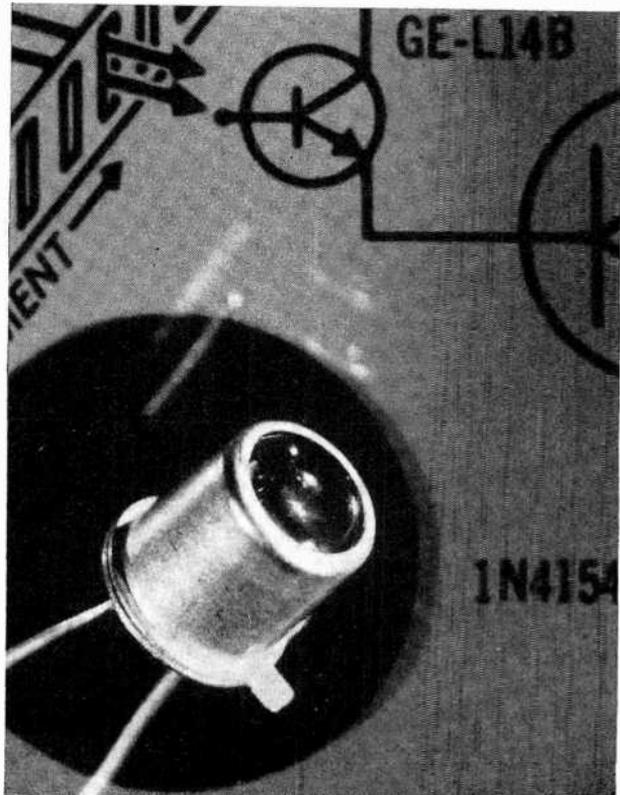

oratory? Especially, how can the experimenter use these tiny sources of "cold light."

An important military use of the LED is as a covert source of illumination for night vision devices. The usefulness of the Army's starlight scope is greatly enhanced by invisible infrared illumination supplied by one or more LED's. Another military use is in covert communications. The Navy, for example, has several types of infrared, line-of-sight LED voice communicators for ship-to-ship and ship-to-shore.

Recently, commercial applications of the LED have been revealed at an unprecedented rate. Several companies are mass producing tiny alpha-numeric displays consisting of arrays of LED's. These displays operate at a much lower voltage than conventional mechanical, incandescent, cathode ray, or gas-discharge displays.

One manufacturer has demonstrated a complete VOM in a probe! Using several of the new numeric displays, the futuristic unit is similar in size to a standard scope probe. Volts

and ohms are read directly from the small light display. The Hamilton Watch Company will market a digital watch using LED numeric displays, and Bell Telephone is hard at work on new types of blue, green, yellow, and red LED's for use in home telephones. Infrared LED's are being used in several types of new intrusion alarms. One company even markets a complete line of LED voice communicators and burglar alarms.

One of the most unusual applications of the infrared LED is as a light source for small mobility aids for the blind. Such devices may eventually be marketed at a price comparable to most hearing aids.

An important result of all these new uses for LED's is a large drop in price. LED's are available for under \$2.50 each in small quantities. This price is competitive with that of miniature, long-life indicator lamps. And of course, the LED offers sturdier packaging, a million-hour lifetime, and far less current consumption.

Only a year ago, the cheapest infrared LED retailed for \$18.00. At least five manufacturers now offer GaAs LED's for under \$7.50. These devices are far more efficient than visible LED's and are therefore usable in experiments in secret communications.

To sum up then, the LED is superior to the conventional filament lamp in the following ways:

1. Response time is extremely fast—most LED's operate in a fraction of a second rise and fall times. Some LED's can reach a speed of 100 MHz.

2. Because it is a solid-state device, an LED has no warm-up time, is completely free of microphonics, is just about impervious to mechanical vibration and other environmental conditions, and is usually of very small size and weight.

3. The LED light output is nearly monochromatic—far from being a laser—but close enough to have most of its light in a relatively narrow bandwidth. This makes it possible to use optical filters to reduce ambient noise.

4. The LED is a low-impedance device with forward characteristics similar to those of a conventional silicon diode and it can be driven from ordinary low-voltage supplies with conventional transistor circuitry.

Elsewhere in this issue you will find a unique construction article for a low-cost LED communicator. Other projects using LED's will appear in future issues.

-50-

#### MORE INFORMATION

For more information about commercial light emitting diodes, write to one of the following manufacturers:

Electro-Nuclear Laboratories  
115 Independence Drive  
Menlo Park, CA 94025

Miniature Lamp Department  
General Electric Company  
Nela Park  
Cleveland, OH 44112

Monsanto Electronic Special Products  
10131 Bubb Road  
Cupertino, CA 95014

Radio Corporation of America  
Electronic Components and Devices  
Harrison, NJ 07029

Texas Instruments  
Semiconductor-Components Division  
Box 5012  
Dallas, TX 75222

Fairchild Semiconductor  
313 Fairchild Drive  
Mountain View, CA 94040

Hewlett-Packard  
1501 Page Mill Road  
Palo Alto, CA 94304

Motorola Semiconductor Products  
Box 20912  
Phoenix, AZ 85036

Sharp Electronics Corporation  
178 Commerce Road  
Carlstadt, NJ 07072

An excellent booklet on LED's is sold by the General Electric Company for \$2.00. Called the "Solid State Lamp Manual," it describes in detail theory, characteristics, and applications.



# OPPORTUNITY AWARENESS



**Thoughtful Reflections On Your Future**

**Eighth in a Monthly Series by David L. Heiserman**

## **The Sacred Club of Engineers**

*I am sick and tired of losing out on good engineering assignments and promotions because I don't have a college degree. Six years ago, I earned an Associate Degree from a two-year technical college. I graduated with honors, but since I don't have a bachelor's or master's, the job openings that I go for seem to be snapped up by junior engineers with 10% of my experience. Sure, I am making a living wage, but I am also at a dead end. How do I break into the sacred club?*

● Since you have kept abreast of the field with specialized home study courses, I must assume that you have no aversion to further scholastic endeavors. Have you attempted to convince your employer to subsidize your college education? Many employers are perfectly willing to give their people time off to attend college classes. Some of them pay part or all of the tuition.

It is an unfortunate situation, but at the moment, it appears easier for employers to screen out people who might not be able to do the job than to test and interview people who might do the job predicated on lesser education, but more experience.

It's sad, but the only way around the problem at this moment is to pick up some more "formal" credentials. Besides getting your bachelor's degree, a fine credential is a Professional Engineer's certificate from your state. Many states don't require Professional Engineers to have a college degree, since they are given an examination—which you should find relatively easy to pass. Also consider membership in the Institute of Electrical and Electronics Engineers and other professional societies.

In his new book, *Education and Jobs: The Great Training Robbery*, Ivar Berg says that an ever increasing percentage of workers spend their time on jobs requiring less formal education than they have. This may be true. Statistics are beginning to show that the

less educated, but more experienced employees have a lower turnover rate and a better aptitude for the job than the over-educated engineer.

## **Which School is Best?**

*I want to take a home-study course in electronics. However, all of the home-study schools claim that they are the best in terms of training, laboratory materials, job placement, etc. Isn't there some way to rate these schools?*

● If you read between the lines in the school advertisements, you will see subtle differences. And, it is because of these differences that it is impossible to objectively "rate" one school above another.


The best electronics home study school for you is the one that has a teaching objective that matches your career goal. You should try to make up your mind exactly what you want to study before contacting the home study schools. Then, write for literature from the schools that advertise lessons to fit your objective. If you have a firm goal in mind, you can narrow down the number of possible schools that can be of any help.

Note that one home study school may emphasize radio and TV repair as its primary teaching objective. Another school will attempt to reach a different kind of student; possibly one already employed in electronics. The course outlined for the latter school may not even mention television. A third school may emphasize communications and may be aiming at helping you get an FCC license.

If you know what you want to study beforehand—which is not as impossible as it may sound—there will be a much smaller chance that you'll be swayed from your conviction by flashy sales literature or the sometimes over-eager sales representative.

As far as a school's business reputation is concerned, you can always depend on a school that has been approved by the National Home Study Council.

-50-

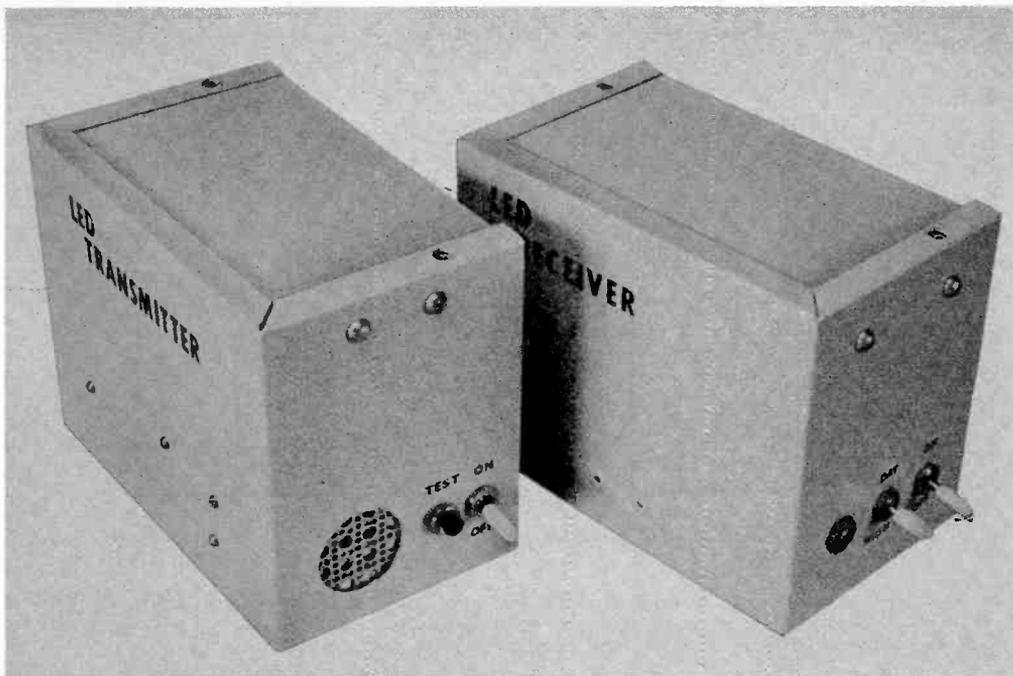

## ASSEMBLE AN LED COMMUNICATOR— **THE OPTICOM**

PRIVATE COMMUNICATIONS VIA  
AN INVISIBLE LIGHT BEAM

**This optical communications system is a very practical and useful application of the light-emitting diode, the theory of operation of which is discussed elsewhere in this issue. The communicator operates at 9400 angstroms and has a range of over 1000' in darkness. Both the transmitter and receiver are simple to build and use relatively easy-to-find components.**

**L**ooking for a totally private, jam-proof, interference-free communications system? Try the "Opticom," the low-cost younger brother of the POPULAR ELECTRONICS Laser Communicator.

Using a light-emitting diode (see the article on page 35) in the transmitter and phototransistor in the receiver, the Opticom is a

voice-modulated infrared optical communicator. It operates at 9400 Angstroms and has a range of over 1000 feet in darkness. The range is considerably less in daylight; but, depending on the angle of the sun and the cloud cover, it can easily reach 100 feet without the use of special filters or light shields.

The key to the amount of range obtainable is in the lenses used at the transmitter and receiver. In the prototype, simple, low-cost lenses were used. Employing a pair of binoculars or a low-cost telescope at each end would greatly increase the operating range.

**Transmitter.** The circuit of the transmitter is shown in Fig. 1. During voice operation, Q1 and Q2 provide amplification and impedance matching between the 20-mV signal from the crystal microphone and Q3. The am-

---

BY FORREST M. MIMS, III AND HENRY E. ROBERTS

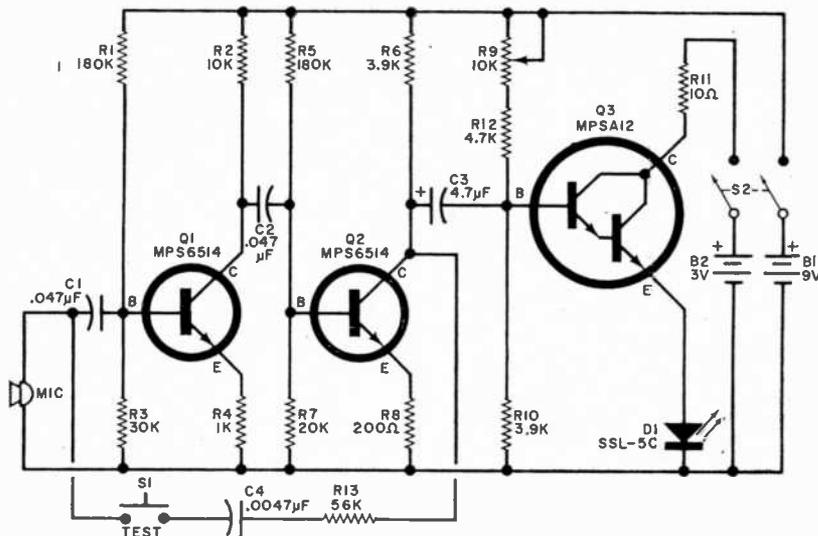


Fig. 1. The LED transmitter consists of a two-stage audio amplifier driving a Darlington modulator. When S1 is depressed, the audio amplifier is converted to an audio oscillator, used for making the original optical setup.

### PARTS LIST TRANSMITTER

- B1—9-volt battery
- B2—Two 1½-volt C cells
- C1, C2—0.047- $\mu$ F, 10-volt capacitor
- C3—4.7 $\mu$ F, 10-volt electrolytic capacitor
- C4—0.0047- $\mu$ F, 10-volt capacitor
- D1—Light-emitting diode (GE SSL-5C)\*
- R1, R5—180,000-ohm, ¼-watt resistor
- R2—10,000-ohm, ¼-watt resistor
- R3—30,000-ohm, ¼-watt resistor
- R4—1000-ohm, ¼-watt resistor
- R6, R10—3900-ohm, ¼-watt resistor
- R7—20,000-ohm, ¼-watt resistor
- R8—200-ohm, ¼-watt resistor
- R9—10,000-ohm, 1-watt potentiometer (Mallory MLC 14L or similar)
- R11—10-ohm, ¼-watt resistor
- R12—4700-ohm, ¼-watt resistor

- R13—56,000-ohm, ¼-watt resistor
- S1—Normally open pushbutton switch
- S2—Dpst slide or toggle switch
- Q1, Q2—MPS6514 or IIEP728 transistor
- Q3—Darlington transistor (Motorola MPSA12)

Misc.—Suitable chassis, miniature crystal microphone, lens, battery holders, battery clips, mounting hardware, cement, wire, solder, etc.

\*Available from Miniature Lamp Department, General Electric Co., P.O. Box 2422, Cleveland, OH 44112, \$7.05, plus postage.



Note—The following are available from MITS, 4809 Palo Duro N.E., Albuquerque, NM 87110: etched and drilled PC board, \$2.50; PC board and all electronic items except switches, microphone, and batteries, \$12.00; complete kit of all parts including lens, chassis, switches, and microphone, \$17.00; all postpaid.

plifier formed by Q1 and Q2 is coupled to provide a low-frequency cutoff to minimize 60-Hz response. Darlington emitter follower Q3 supplies bias current to the LED from B2. Potentiometer R9 provides an unmodulated current-level adjustment for the LED and should be set so that ½ volt is read across R11. From Ohms law, ½ volt across 10 ohms indicates a current level of 50 milliamperes. This is well below the 100-mA capability of the SSL-5C LED without a heat sink.


Tone operation is provided by connecting


the feedback circuit comprised of R13 and C4 to the input of Q1 through S1. With S1 depressed, the amplifier formed by Q1 and Q2 oscillates at about 500 Hz and supplies 100% modulation to the LED.

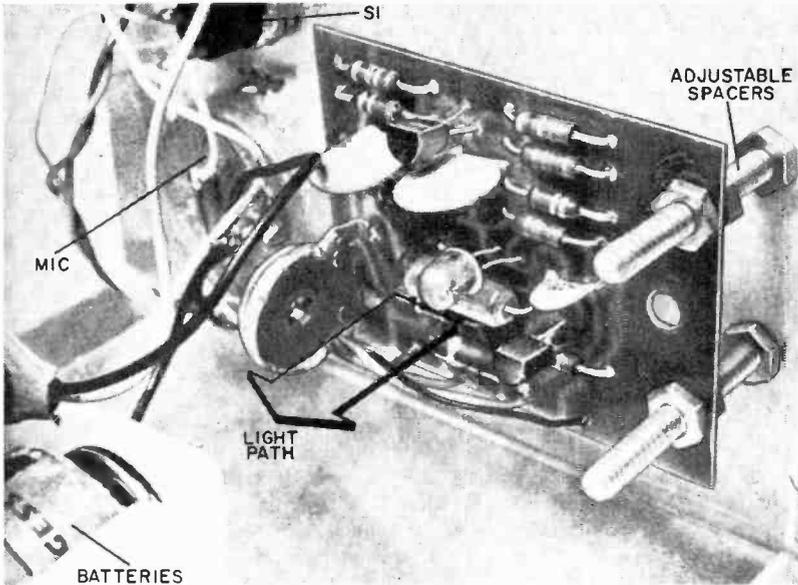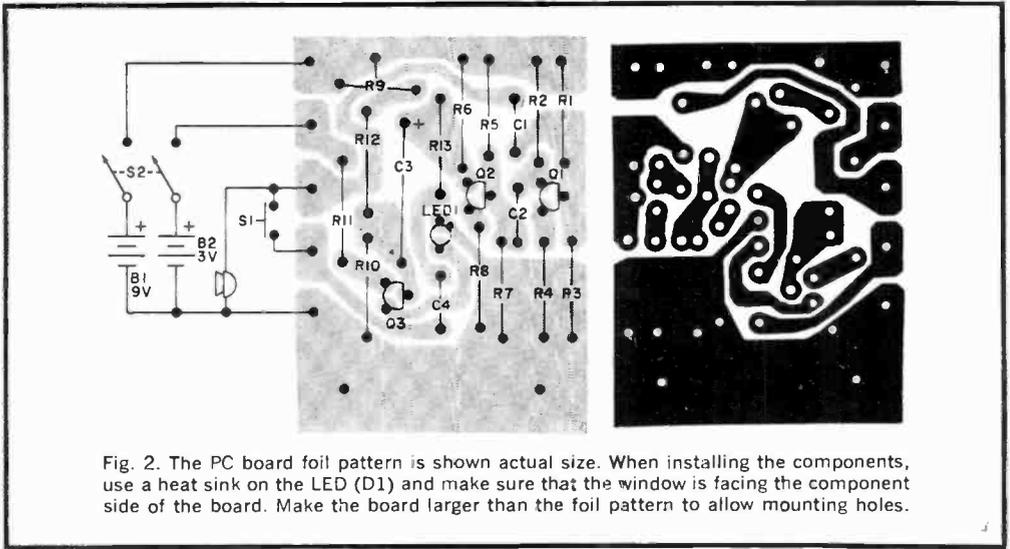The transmitter circuit is assembled on a printed circuit board as shown in Fig. 2. In installing the semiconductors, use care—particularly with the LED, whose leads should have a heat sink attached while soldering. Make sure that the window of the LED is parallel to the PC board.




Assemble the transmitter on four adjustable spacers so that the window of the LED can be placed at the focal point of the lens. When assembling complete chassis be sure to mount the batteries so that they do not obstruct light path between the LED and the lens. Although the prototype has the microphone on chassis, a remote mike can be used. Even S2 can be mike-mounted push-to-talk switch. Oscillator switch S1 is rarely used, so can remain mounted on chassis.

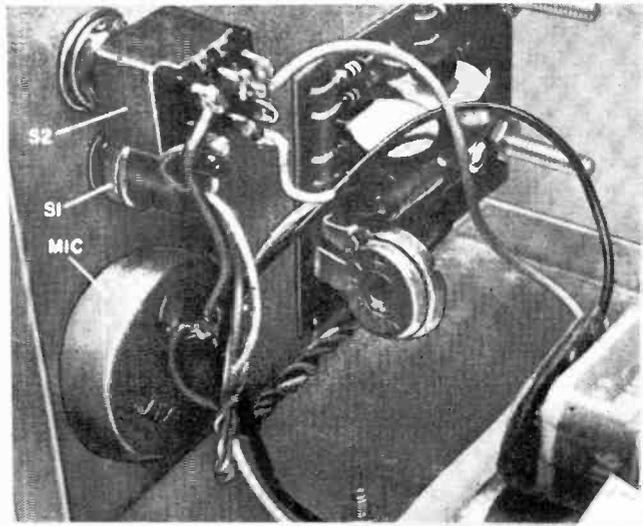

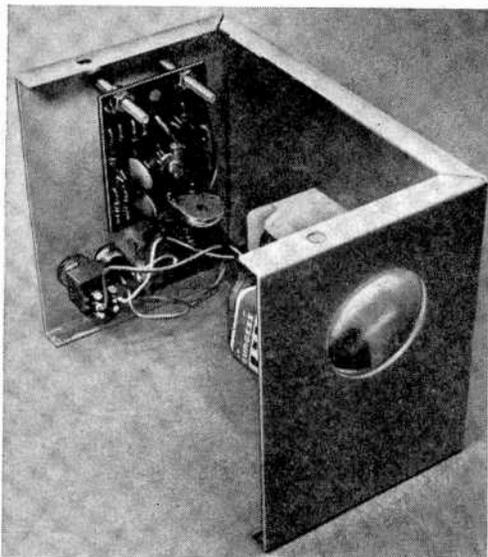

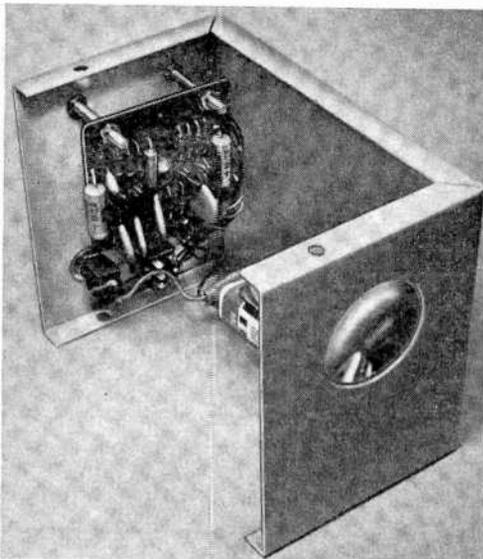In assembling the transmitter, arrange the board and lens mounting so that the LED window is on the center line of the lens. The text explains how to adjust the board to make the lens focus at the window of the light-emitting diode on board.



The receiver must be assembled in a manner similar to the transmitter—with the window of Q1 at the focal point of the lens. In both receiver and transmitter, once the focus has been attained, a drop of cement on screws will prevent slippage.

**Receiver.** A schematic of the receiver circuit is shown in Fig. 3. Phototransistor *Q1* passes a current proportional to the light intensity at its active surface. In essence, light replaces *Q1*'s base lead. Since *Q1* is quite light sensitive, even a moderate level of ambient illumination will drive it into saturation. Transistors *Q2* and *Q3* provide a dynamic load for *Q1*, preventing saturation or cutoff and extending useful daylight receiving range. The FET, *Q4*, matches the high impedance of the detection circuit to the audio amplifier formed by *Q5* and *Q6*. The complete receiver circuit provides a voltage gain of about 400.

A foil pattern and component layout for the receiver printed circuit board are shown in Fig. 4. Be very careful when installing phototransistor *Q1* because it has a plastic package and the leads are fragile. The collector of this transistor is indicated by a small arrow on the bottom. Place the transistor through the 0.175" hole at the center of the receiver board (domed window to the component side), be sure the leads are properly oriented, and then solder them to the correct points. Use a clip-on heat sink when installing all semiconductors.

**Assembly.** Once both boards have been completed and checked for possible wiring errors, the system is ready for packaging. You

can use the arrangement described here or you can strike out on your own. If, for example, you need only a 15-to-20-ft. range, an optical system is not required. All you have to do is aim the two boards at each other, depress the transmitter Test pushbutton, and align the two units. Then release the button and talk.

If you want a night range of up to 1000', you must use a lens at both transmitter and receiver. Obtain two low-cost magnifying lenses at least one inch in diameter and remove the lenses from their housing or frames. Measure the focal length of each lens by placing it in the beam of a fairly distant light source. The sun is ideal, but an overhead lamp, about 10 feet away will do. The focal length is determined by placing the lens at a distance from a piece of white paper so that the smallest recognizable image is displayed on the paper. Measure the distance between the lens center and the paper—this is the focal length. The chassis to be used should be long enough so that, with the lens mounted at one end and the PC board carrying the LED or phototransistor at the other, the distance between the two can be adjusted to the focal length of the lens.

The chassis used must have a cover so that the interior is dark when the system is in use.

Drill four holes for mounting the PC board

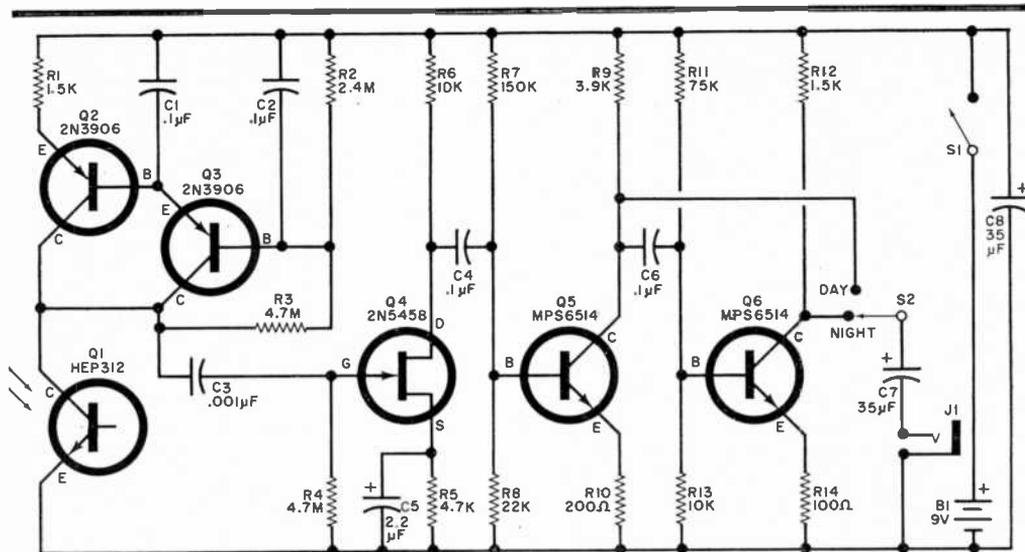


Fig. 3. Consisting of an audio amplifier driven by a phototransistor circuit, the receiver can use either two or three audio stages for day or night operation. There is no actual base connection to Q1 as this function is performed by light from LED.

### PARTS LIST RECEIVER

B1—9-volt battery  
 C1, C2, C4, C6—0.1- $\mu$ F, 10-volt capacitor  
 C3—0.001- $\mu$ F, 10-volt capacitor  
 C5—2.2- $\mu$ F, 10-volt electrolytic capacitor  
 C7, C8—35- $\mu$ F, 10-volt electrolytic capacitor  
 J1—Earphone jack and plug  
 Q1—HEP312 phototransistor  
 Q2, Q3—2N3906 or IIEP715 transistor  
 Q4—2N5458 or IIEP801 FET  
 Q5, Q6—MPS6514 or HEP728 transistor  
 R1, R12—1500-ohm,  $\frac{1}{4}$ -watt resistor  
 R2—2.4-megohm,  $\frac{1}{4}$ -watt resistor  
 R3, R4—4.7-megohm,  $\frac{1}{4}$ -watt resistor  
 R5—4700-ohm,  $\frac{1}{4}$ -watt resistor  
 R6, R13—10,000-ohm,  $\frac{1}{4}$ -watt resistor  
 R7—150,000-ohm,  $\frac{1}{4}$ -watt resistor

R8—22,000-ohm,  $\frac{1}{4}$ -watt resistor  
 R9—3900-ohm,  $\frac{1}{4}$ -watt resistor  
 R10—200-ohm,  $\frac{1}{4}$ -watt resistor  
 R11—75,000-ohm,  $\frac{1}{4}$ -watt resistor  
 R14—100-ohm,  $\frac{1}{4}$ -watt resistor  
 S1—Spst slide or toggle switch  
 S2—Spdt slide or toggle switch  
 Misc.—Suitable chassis, lens, battery connectors, battery clips, mounting, hardware, cement, earphone (250 ohms or more), solder, wire, etc.


Note—The following are available from MITS, 4809 Palo Duro N.E., Albuquerque, NM 87110: etched and drilled PC board, \$2.75; PC board and all electronic items except switches, earphone and batteries, \$11.00; complete kit of all parts including lens, chassis, switches, and earphone, \$15.00; all postpaid.

in one end of the chassis. Temporarily mount the chassis with four screws and nuts to allow for adjustments. Make measurements to determine the location of the center of the light-sensitive semiconductor with respect to its location on the chassis wall.

The center of the lens must be in the same position on the opposite end. Make the hole for the lens about  $\frac{1}{4}$ " smaller in diameter than the lens.

The crystal microphone and two switches for the transmitter are mounted on the same

The lens hole should be slightly smaller than the lens. Use epoxy cement to mount the lens to inside of the chassis to prevent accidental loosening.

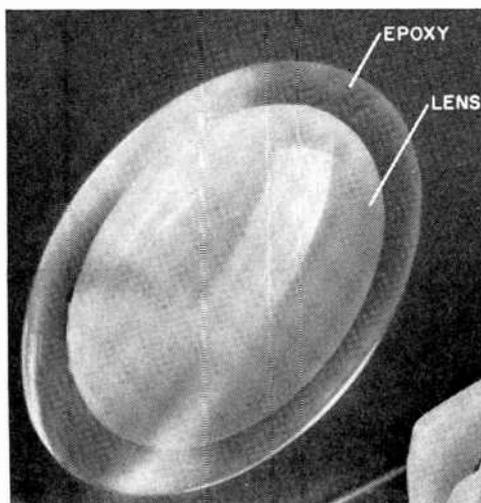

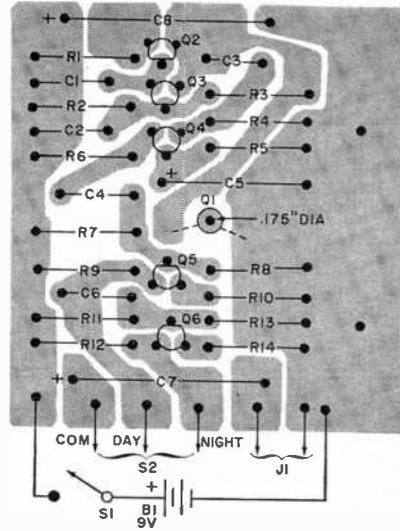
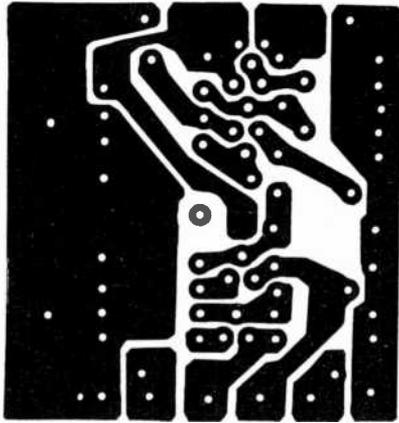



Fig. 4. When mounting Q1 make sure the window is facing the component side of the PC board. Connect collector to the foil that goes to R3 and Q1, and the emitter to the large common foil adjacent to the Q1 hole.

end as the PC board on the transmitter chassis. Cut a clean hole for acoustic access to the microphone, which is cemented to the inside of the chassis. The battery clips are mounted within the chassis, in a location where the batteries do not interfere with the light path from the lens to the LED.

On the receiver chassis use similar locations for the two switches and the earphone jack. Before mounting any components on the

chassis, make sure that all mounting holes have been drilled and deburred; and, if desired, paint the chassis. Mount the PC boards with long screws to permit adjustment of focus. Put nuts on the screws on both sides of the boards to permit making the adjustment and locking the board in place.

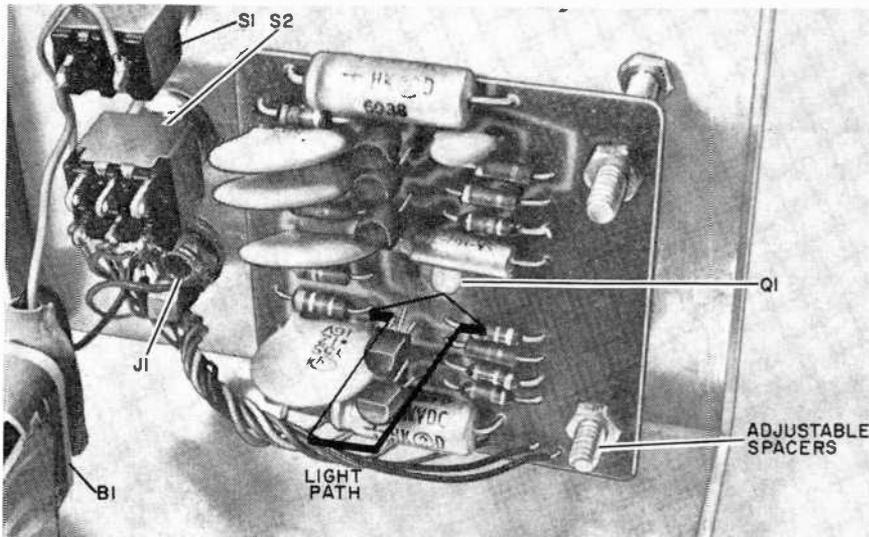When the wiring is complete and before mounting the lenses, test the units by aiming  
(Continued on page 98)



Like transmitter, assemble receiver board on four adjustable spacers so that the window of Q1 is at the focus of the lens. Once again, make sure batteries do not obstruct light.



## ASSEMBLE A

# DIGITAL MEASUREMENTS LAB

MAIN FRAME POWER SUPPLY AND READOUT  
WITH 20-MHz FREQUENCY COUNTER MODULE  
(MORE PLUG-IN MODULES TO COME)

This article is the first in a series on the construction of an integrated, modern, digital readout instrument having a common main frame (with power supply and readout) which is capable of accepting a variety of individual plug-in units. The use of the plug-in module concept makes it possible to have digital test equipment of high accuracy at a very economical cost.

**T**HE PRIMARY PURPOSE of most electronic measuring instruments is to provide a numerical indication of the level or value of the quantity being measured. It matters little whether the measurement is in volts, amperes, ohms, Hz, or elapsed time; only the accuracy of the measurement is important. Since the readout device and the measuring instruments

do not necessarily have to be connected, why not have a "modularized" type of measurement system—with a highly accurate digital readout (with a power supply) on a main frame and measurement modules that can be plugged in?

The "Digital Measurements Lab" is such a system; and its hallmarks are economy, accuracy and flexibility. In this issue of POPULAR ELECTRONICS, are assembly instructions for the main frame, which houses the readout and power supply, and one measurement module, a 20-MHz Frequency Counter. In future articles, other modules, which can be added at little additional cost, will be described. These will include a Dual-Slope Volt-Ohmmeter and a Capacitance Meter.

The Digital Measurements Lab employs

---

---

BY DANIEL MEYER

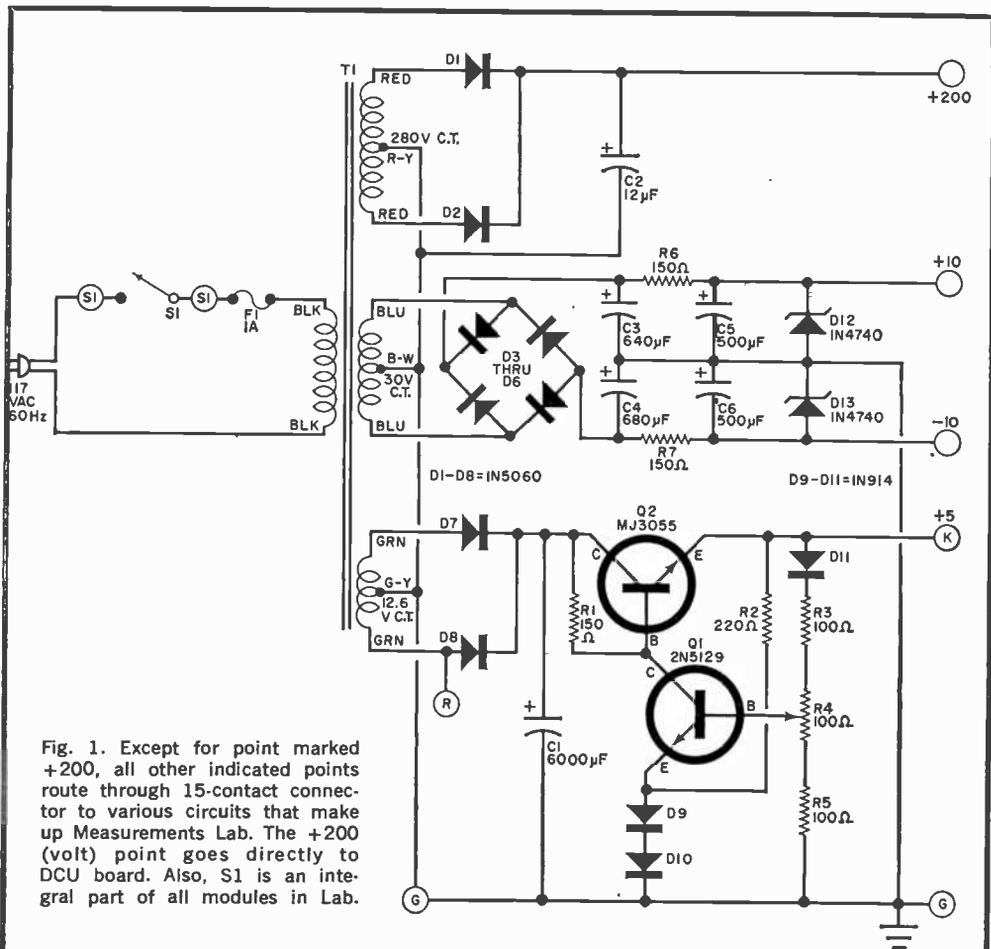


Fig. 1. Except for point marked +200, all other indicated points route through 15-contact connector to various circuits that make up Measurements Lab. The +200 (volt) point goes directly to DCU board. Also, S1 is an integral part of all modules in Lab.

### PARTS LIST MAIN FRAME

- C1—6000- $\mu$ F, 10-volt electrolytic capacitor
- C2—12- $\mu$ F, 250-volt electrolytic capacitor
- C3,C4—640- $\mu$ F, 25-volt electrolytic capacitor
- C5,C6—500- $\mu$ F, 15-volt electrolytic capacitor
- D1-D8—400-PIV, 1-ampere silicon rectifier (1N5060 or similar)
- D9-D11—DHD800 (General Electric) or 1N914 silicon rectifier
- D12,D13—1N4740 zener diode
- F1—1-ampere fuse
- Q1—2N5129 transistor (National Semiconductor or Fairchild)
- Q2—MJ3055 transistor (Motorola)
- R1,R6,R7—150-ohm, 1/2-watt, 10% tolerance resistor
- R2—220-ohm, 1/2-watt, 10% tolerance resistor
- R3,R5—100-ohm, 1/2-watt, 10% tolerance resistor
- R4—100-ohm printed circuit type potentiometer

S1—Spst switch (see Frequency Counter Parts List)

T1—Power transformer (117-volt primary/280-volt, center-tapped (at 20 mA); 30-volt, center-tapped (at 100 mA); and 12.6-volt, center-tapped (at 1.5 ampere) secondaries)

1—"Utilogic" 3 1/2-digit display and counter kit  
Misc.—Main frame chassis and cowling; control knob; power supply printed circuit board; ac line cord and strain relief; fuse holder; 15-contact socket; solid and stranded hookup wire; machine hardware; spacers; solder; etc.

Note—The following items are available from Southwest Technical Products Corp., Box 16297, San Antonio, TX 78216: power supply circuit board No. 170-Pb for \$2.85; complete power supply kit, including board, No. 170-C for \$14.55 plus postage on 4 lb; complete main frame kit, including chassis and cowling, display time control, reset switch, etc., but minus readout assembly, No. 170-CP for \$19.55 plus postage on 8 lb; "Utilogic" display-counter kit No. MNX-1 for \$49.50.

transistor-transistor-logic (TTL) integrated circuits and other modern design techniques to provide maximum accuracy and reliability. The readout system consists of decoders, drivers, and Nixie® neon-glow tubes to provide 3½ decades and, thus, 3-place accuracy.

The cost of the parts for the main frame is estimated at less than \$75; while the Frequency Counter module is about \$42.

**The Main Frame.** The Digital Measurements Lab can be built around almost any type of decimal counting system capable of responding to 20 MHz or more. For example, you can use either of the two decoder/driver systems that have previously appeared in *POPULAR ELECTRONICS* (see "Build Numeric Glow Tube DCU," Feb. 1970 and "Assembling The Popular Electronics Mini DVM," Sept.

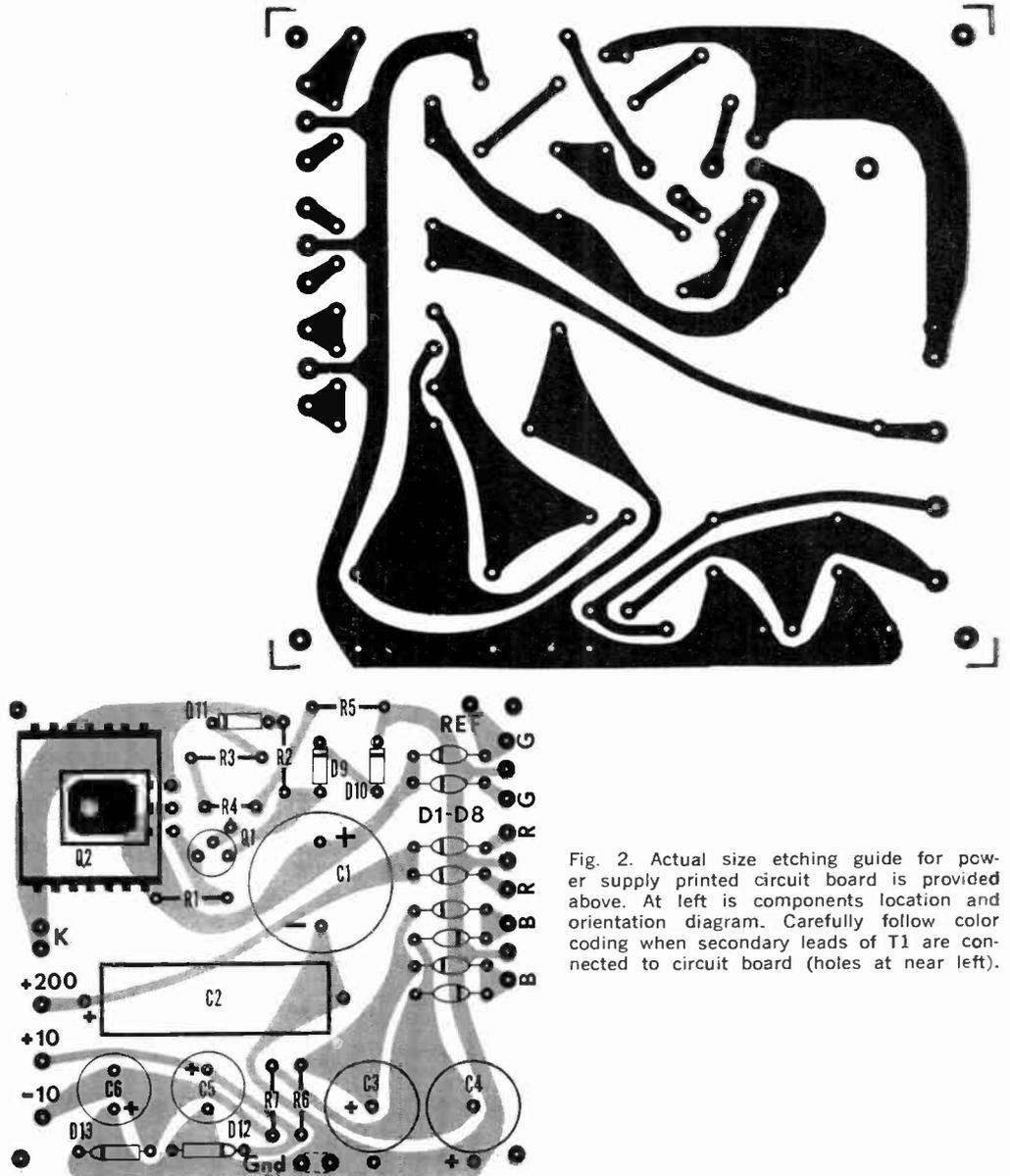


Fig. 2. Actual size etching guide for power supply printed circuit board is provided above. At left is components location and orientation diagram. Carefully follow color coding when secondary leads of T1 are connected to circuit board (holes at near left).

# "CIE training helped pay for my new house," says Eugene Frost of Columbus, Ohio

Gene Frost was "stuck" in low-pay TV repair work. Then two co-workers suggested he take a CIE home study course in electronics. Today he's living in a new house, owns two cars and a color TV set, and holds an important technical job at North American Aviation. If you'd like to get ahead the way he did, read his inspiring story here.



**I**F YOU LIKE ELECTRONICS—and are trapped in a dull, low-paying job—the story of Eugene Frost's success can open your eyes to a good way to get ahead.

Back in 1957, Gene Frost was stalled in a low-pay TV repair job. Before that, he'd driven a cab, repaired washers, rebuilt electric motors, and been a furnace salesman. He'd turned to TV service work in hopes of a better future—but soon found he was stymied there too.

"I'd had lots of TV training," Frost recalls today, "including numerous factory schools and a semester of advanced TV at a college in Dayton. But even so, I was stuck at \$1.50 an hour."

Gene Frost's wife recalls those days all too well. "We were living in a rented double," she says, "at \$25 a month. And there were no modern conveniences."

"We were driving a six-year-old car," adds Mr. Frost, "but we had no choice. No matter what I did, there seemed to be no way to get ahead."

## Learns of CIE

Then one day at the shop, Frost got to talking with two fellow workers who were taking CIE courses... pre-

paring for better jobs by studying electronics at home in their spare time. "They were so well satisfied," Mr. Frost relates, "that I decided to try the course myself."

He was not disappointed. "The lessons," he declares, "were wonderful—well presented and easy to understand. And I liked the relationship with my instructor. He made notes on the work I sent in, giving me a clear explanation of the areas where I had problems. It was even better than taking a course in person because I had plenty of time to read over his comments."

## Studies at Night

"While taking the course from CIE," Mr. Frost continues, "I kept right on with my regular job and studied at night. After graduating, I went on with my TV repair work while looking for an opening where I could put my new training to use."

His opportunity wasn't long in coming. With his CIE training, he qualified for his 2nd Class FCC License, and soon afterward passed the entrance examination at North American Aviation. "You can imagine how I felt," says Mr. Frost. "My new job paid \$228 a month more!"

Currently, Mr. Frost reports, he's an inspector of major electronic systems, checking the work of as many as 18 men. "I don't lift anything heavier than a pencil," he says. "It's pleasant work and work that I feel is important."

## Changes Standard of Living


Gene Frost's wife shares his enthusiasm. "CIE training has changed our standard of living completely," she says.

"Our new house is just one example," chimes in Mr. Frost. "We also have a color TV and two good cars instead of one old one. Now we can get out and enjoy life. Last summer we took a 5,000 mile trip through the West in our new air-conditioned Pontiac."

"No doubt about it," Gene Frost concludes. "My CIE electronics course has really paid off. Every minute and every dollar I spent on it was worth it."
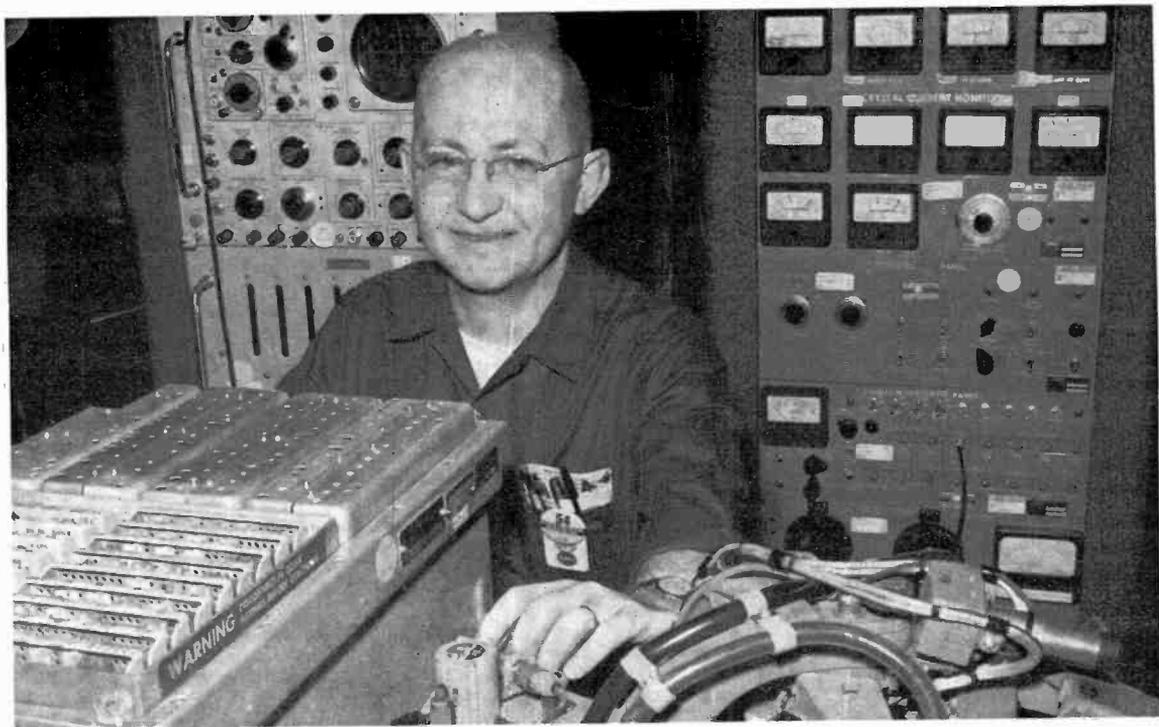
## Why Training is Important

Gene Frost has discovered what many others never learn until it is too late: that to get ahead in electronics today, you need to know more than soldering connections, testing circuits, and



replacing components. You need to really know the fundamentals.

Without such knowledge, you're limited to "thinking with your hands" ... learning by taking things apart and putting them back together. You can never hope to be anything more than a serviceman. And in this kind of work, your pay will stay low because you're competing with every home handyman and part-time basement tinkerer.

But for men with training in the fundamentals of electronics, there are no such limitations. They think with their heads, not their hands. They're qualified for assignments that are far beyond the capacity of the "screw-driver and pliers" repairman.

The future for trained technicians is bright indeed. Thousands of men are desperately needed in virtually every field of electronics, from 2-way mobile radio to computer testing and troubleshooting. And with demands like this, salaries have skyrocketed. Many technicians earn \$8,000, \$10,000, \$12,000 or more a year.

How can you get the training you need to cash in on this booming demand? Gene Frost found the answer in CIE. And so can you.

#### Send for Free Book

Thousands who are advancing their electronics careers started by reading our famous book, "How To Succeed In Electronics." It tells of the many electronics careers open to men with the proper training. And it tells which courses of study best prepare you for the work you want.

If you'd like to get ahead the way Gene Frost did, let us send you this 44-page book free. With

it we'll include our other helpful book, "How To Get A Commercial FCC License." Just fill out and mail the attached card.

If the card is missing, use the coupon below.

#### ENROLL UNDER G.I. BILL

All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1955, or are in service now, check box on reply card for G.I. Bill information.

**CIE** Cleveland Institute of Electronics  
1776 East 17th Street, Cleveland, Ohio 44114

### NEW

#### COLLEGE-LEVEL CAREER COURSE FOR MEN WITH PRIOR EXPERIENCE IN ELECTRONICS

**ELECTRONICS ENGINEERING** ... covers steady-state and transient network theory, solid state physics and circuitry pulse techniques, computer logic and mathematics through calculus. A college-level course for men already working in Electronics.

Cleveland Institute of Electronics  
1776 East 17th Street, Cleveland, Ohio 44114

Please send me without cost or obligation:

1. Your 44-page book "How To Succeed In Electronics" describing the job opportunities in Electronics today, and how your courses can prepare me for them.
2. Your book on "How To Get A Commercial FCC License."

I am especially interested in:

- |  |   |  |
|--|---|--|
| <input type="checkbox"/> Electronics Technology    | <input type="checkbox"/> Broadcast Engineering  | <input type="checkbox"/> First Class FCC License |
| <input type="checkbox"/> Electronic Communications | <input type="checkbox"/> Industrial Electronics | <input type="checkbox"/> Electronics Engineering |

Name \_\_\_\_\_ (Please Print)

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Check here for G.I. Bill information. PE-10

CIRCLE NO. 6 ON READER SERVICE PAGE

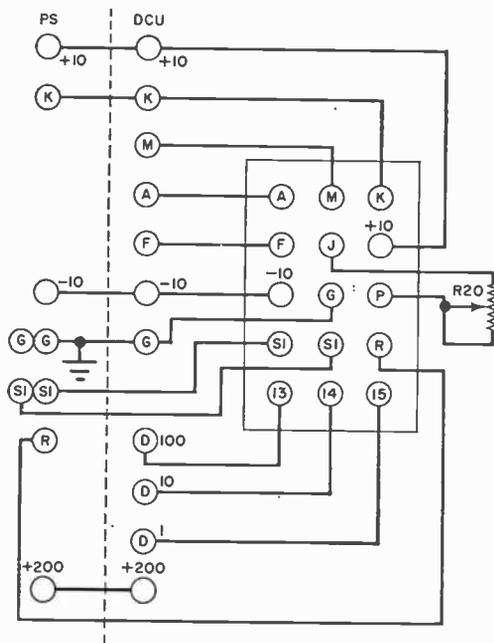


Fig. 3. Power supply (PS) and readout (DCU) boards and 15-contact connector are wired together as shown. Potentiometer R20 is display time control.

1970). However, since the "Utilogie" three-and-a-half-digit display and counter assembly was designed specifically for the Lab's main frame, its use is recommended (see Main Frame Parts List).

The first step in putting together the main frame is to assemble the readout system from the plans provided in a previous issue or with the "Utilogie" kit. Next, assemble the power supply circuit, the schematic diagram for which is shown in Fig. 1, on its printed circuit board. In the event you plan to etch and drill your own circuit board, an actual size etching guide and components location and orientation diagram are given in Fig. 2. When assembling the power supply circuit board, pay close attention to the orientations of the diodes, transistors, and electrolytic capacitors. Use bare #22 hookup wire for the three jumpers.

Once the boards are assembled, they must be wired to each other and to a 15-contact connector. The connector provides a means for routing the signal and power lines to and from the plug-in modules. The wiring procedure is greatly simplified by the fact that all wiring holes in the circuit boards are assigned a letter-code designation. This code is set up so that like letters mate with each other and with the coding on the connector as shown in

Fig. 3. Between the boards, you can use solid hookup wire, but between the boards and connector, it is recommended that you use stranded wire.

After the wiring is completed, bolt the readout circuit board to the chassis with machine hardware and  $\frac{3}{8}$ " spacers. Then use #6 hardware to bolt the power transformer (*T1*) to the floor of the main frame's chassis (see Fig. 4) and temporarily set the power supply board in its appropriate location. Measure the secondary leads from *T1* to their respective holes in the power supply board. Add about an inch to each measurement and trim away any excess lead lengths. Strip away  $\frac{1}{4}$ " of insulation from each lead, push the leads through the holes in the power supply board, and solder them to the foil pattern.

Mount the RATE control and the RESET

### THEORY OF POWER SUPPLY DESIGN




The power supply used in the Digital Measurements Lab and shown schematically in Fig. 1 is designed to provide all of the voltages required by the circuits that make up the Lab. The +200-volt output is used for firing the readout tubes and neon lamps in the multi-decade readout assembly. This output is not critical and is, therefore, unregulated.

The various transistor circuits in the Lab are powered by the +10- and -10-volt outputs which are voltage regulated by zener diodes *D12* and *D13*. For the more critical demands of the IC's, the +5-volt output is derived from a special regulator circuit that maintains the output voltage within 5% of the 5-volt level at point K. The regulator circuit consists of series-pass transistor *Q2* and error amplifier transistor *Q1*. In operation, a sample of the output voltage is applied to the base of *Q1* by the wiper of voltage level control *R4*. If any loading condition attempts to force the output voltage to increase, the base voltage of *Q1* will also increase slightly and cause *Q1* to draw more collector current. The increase in collector current then causes a decrease in the base voltage of *Q2* of sufficient magnitude to maintain the output voltage at its original +5-volt level. If, on the other hand, loading conditions attempt to decrease the output voltage level below 5 volts at point K, the opposite action will occur.

The positive and negative 10-volt outputs are obtained from the bridge rectifier assembly made up of diodes *D3-D6* and filter capacitors *C4-C6*. The +200-volt output is obtained from a separate *T1* secondary winding, diodes *D1* and *D2*, and filter capacitor *C2*.

The  $\pm 5$ -volt output is obtained from a third secondary winding, *D7* and *D8*, and *C1*. Potentiometer *R4* is a voltage level control, capable of varying the output voltage between approximately 4 and 6 volts. This control would normally be set to provide a 5-volt output.

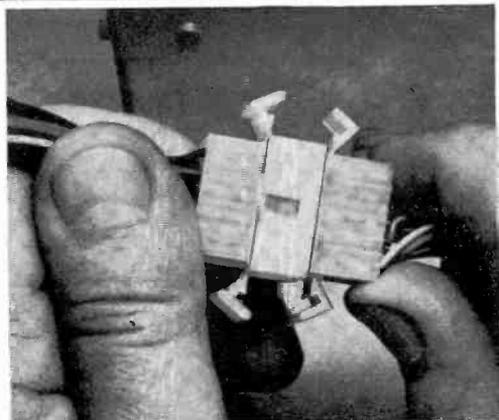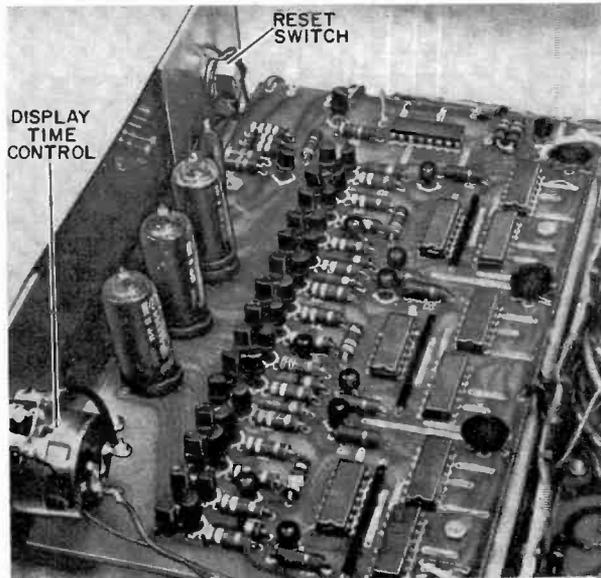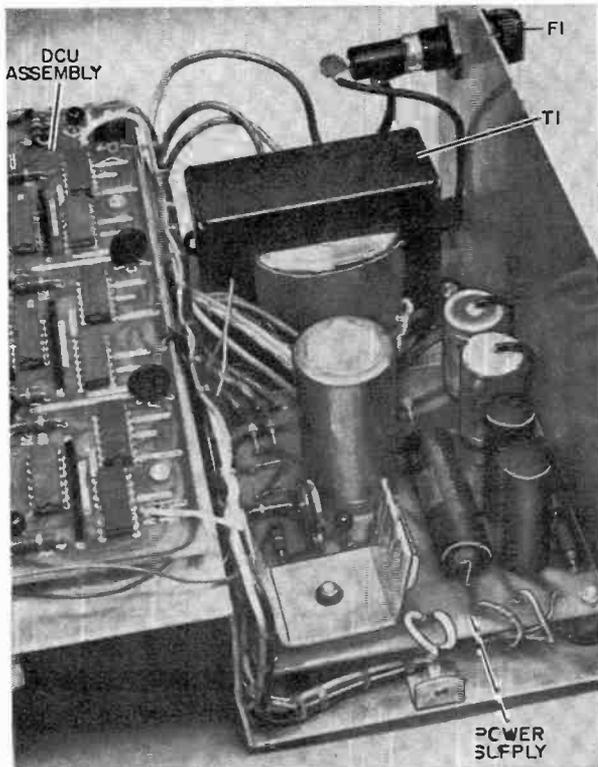Locations of power supply (right) and 3½-digit decoder/driver assembly, reset switch, and display time control (below) are shown mounted on respective sections of main frame chassis.



A 15-contact Molex connector is recommended for use in Digital Measurements Lab for positive electrical contact.

switch on the front panel of the main frame. Then, on the rear apron, mount the fuse holder and pass through its entry hole the ac line cord and fasten it in place with a strain relief. Then finish wiring the power supply primary circuit, referring back to Fig. 1 and Fig. 3 for details.

Solder one end of a length of hookup wire to one of the lugs on the RESET switch; the other end goes to hole M on the DCU board. Cut a length of stranded hookup wire to size, and connect and solder its ends to the same lug on the RESET switch and contact M on the connector. Then connect and solder a final

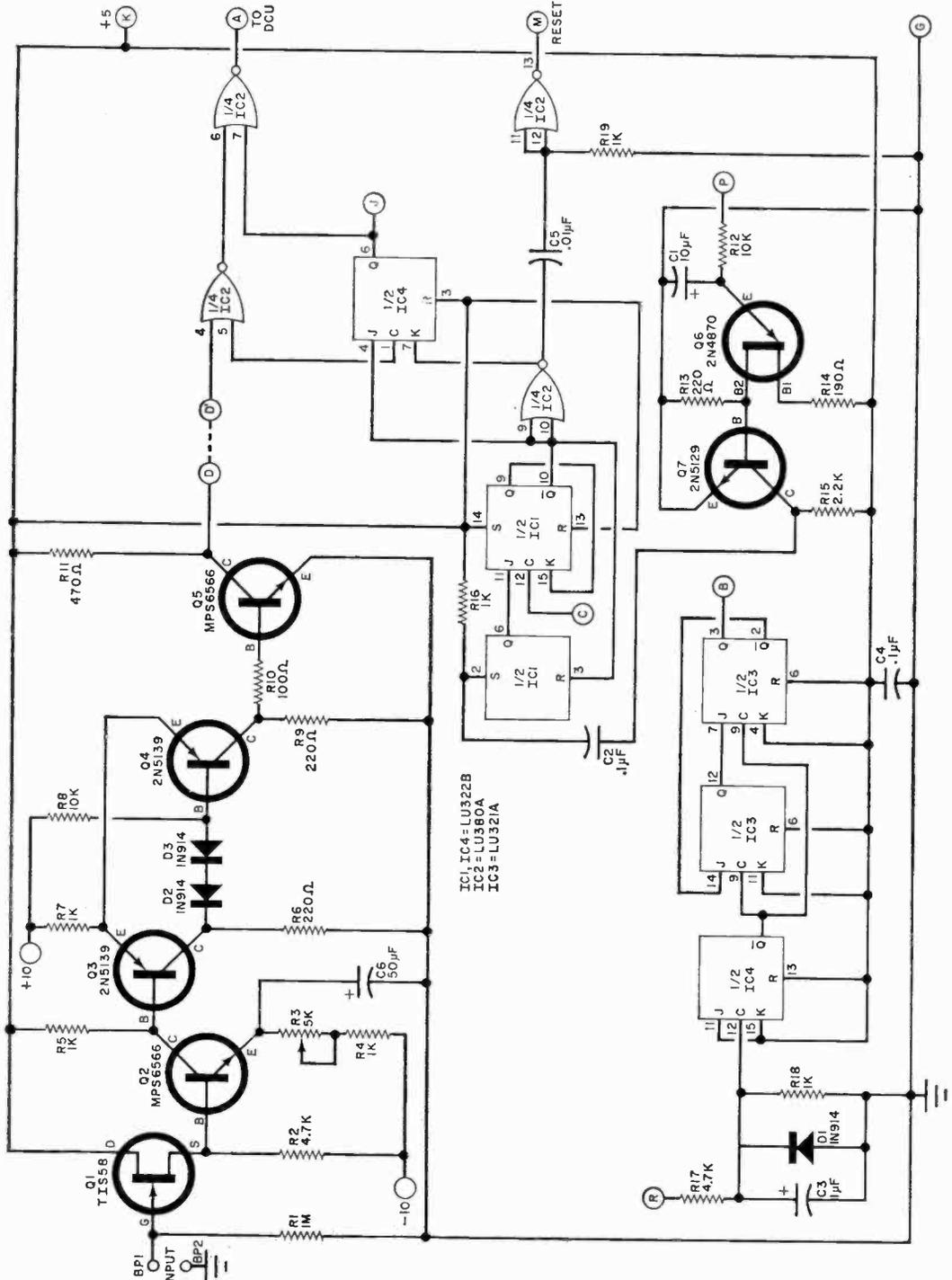


Fig. 5. By connecting D to D' and B to C, basic Time Base circuit shown can provide single 2000-Hz range. To obtain full 20-MHz, five-range capability, Scaler/switching arrangement would be connected to these points.

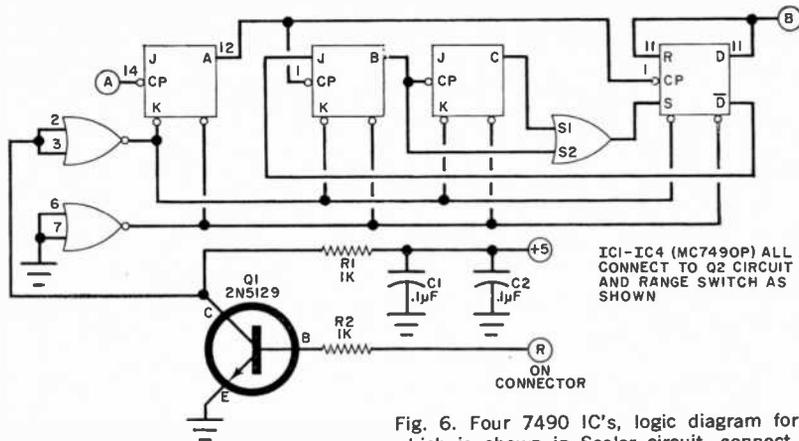


Fig. 6. Four 7490 IC's, logic diagram for only one of which is shown in Scaler circuit, connect to Q1 stage.

length of wire between the free lug of the switch and chassis ground.

Locate the 15-contact connector and pass it through the cutout in the center wall of the main frame's chassis so that it is easily accessible through the plug-in compartment. Then neatly lace together the wiring.

**Testing the Main Frame.** Temporarily connect a jumper wire between the two S1

contacts on the connector (see Fig. 3). Plug the line cord into a convenient 117-volt, 60-Hz ac outlet. Use a voltmeter to check the +10-volt, -10-volt and +200-volt outputs from the power supply. Your readings should be within 10% of these values. Then connect the meter to point K in the power supply and chassis ground and adjust R4 for an exact 5-volt reading.

Now, check the front panel of the main

## PARTS LIST FREQUENCY COUNTER

### Time Base:

BP1, BP2—Five-way binding post (one black, one red)

C1—10- $\mu$ F, 15-volt electrolytic capacitor

C2, C4—0.1- $\mu$ F, 12-volt disc capacitor

C3—1- $\mu$ F, 15-volt electrolytic capacitor

C5—0.01- $\mu$ F, 12-volt disc capacitor

C6—50- $\mu$ F, 15-volt electrolytic capacitor

D1—D3—1N914 diode

IC1, IC4—LU322B integrated circuit (Signetics)

IC2—LU380A integrated circuit (Signetics)

IC3—LU321A integrated circuit (Signetics)

Q1—T1S58 transistor (Texas Instruments)

Q2, Q5—MPS6566 transistor (Motorola)

Q3, Q4—2N5139 transistor (Fairchild)

Q6—2N4870 or 2N4871 unijunction transistor

Q7—2N5129 transistor (Fairchild)

R1—1-Megohm

R2—4700-ohm

R4, R5, R7, R16,

R18, R19—1000-ohm

R6, R9, R13—220-ohm

R8, R12—10,000-ohm

R10—100-ohm

R11—470-ohm

R14—190-ohm

R15—2200-ohm

R17—4700-ohm

All resistors 1/2-watt, 10% tolerance

R3—5000-ohm linear-taper potentiometer

S1—10-position, 4-deck non-shorting rotary switch with spst switch attachment for S1 in power supply

### Scaler:

C1, C2—0.1- $\mu$ F, 10-volt disc capacitor

IC1-IC4—MC7490P integrated circuit (Motorola)

Q1—2N5129 transistor (National Semiconductor or Fairchild)

R1, R2—1000-ohm, 1/2-watt, 10% tolerance resistor

Misc.—Time Base and Scaler printed circuit boards; 33,000-ohm, 1/2-watt, 10% tolerance resistor (see text); control knobs (2): L bracket chassis; 15-contact plug to match SO1 in main frame; 4-40 machine hardware; 1/4"-long spacers (8); solid and stranded hookup wire; solder; etc.

Note—The following items are available from Southwest Technical Products Corp., Box 16297, San Antonio, TX 78216: complete Time Base kit, including circuit board, No. TB-2, for \$17.50; Complete Scaler kit, including circuit board, No. S-410 for \$14.95. both kits plus chassis and 15-contact plug, No. FC-2 for \$34.95 plus postage on 3 lb.

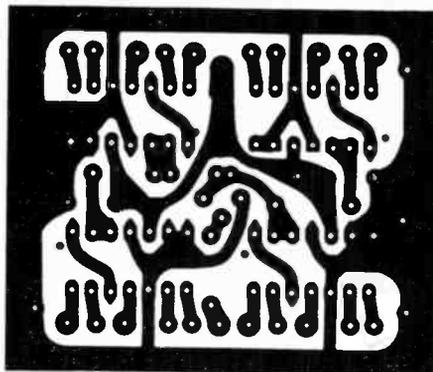
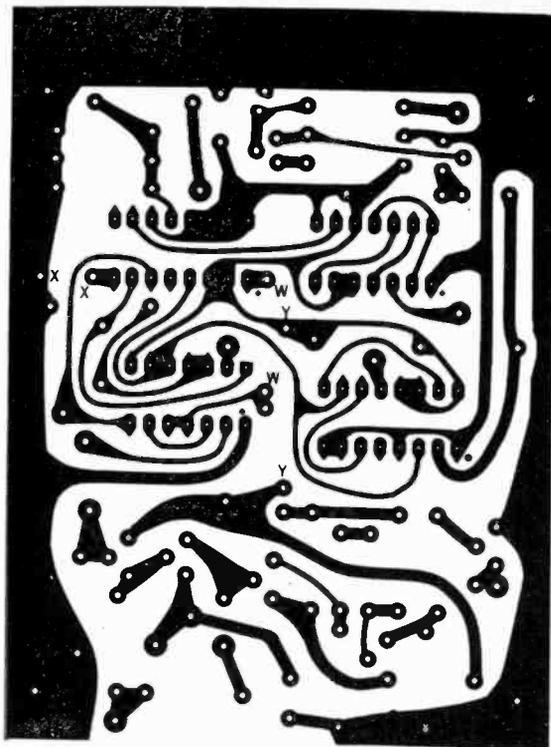


Fig. 7. Actual size etching guides for Time Base and Scaler printed circuit boards are shown at left and above, respectively. Use etching guides to check for solder bridges between closely spaced conductors after all components are soldered to circuit boards.


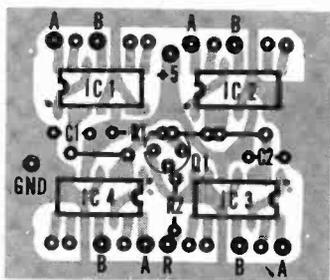


Fig. 8. When mounting electrolytic capacitors, diodes, IC's, and transistors on circuit boards carefully orient them exactly as shown here.

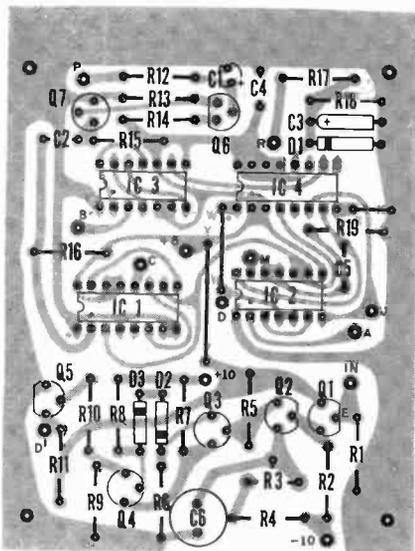


frame; with power applied, the readout tubes and neon lamps should glow. If so, depress and release the RESET switch. If the main frame is operating properly, all tubes should immediately reset to "0". Then set the main frame aside.

**Frequency Counter Module.** As mentioned earlier, the first in the series of integrated plug-in construction plans is a 20-MHz Frequency Counter. The module, employing TTL integrated circuits, consists of two basic

circuit assemblies: one is the Time Base and the other is the Scaler, shown schematically in Fig. 5 and Fig. 6, respectively. For minimum loading on the circuit under test, the counter module is equipped with a high-impedance source-follower field effect transistor input circuit.

The Frequency Counter module has full-scale ranges of 1000 Hz, 10 kHz, 100 kHz, 1 MHz, and 10 MHz with a 100 percent over-range capability. This means that it will count pulses up to a frequency of 19.99 MHz direct-

Fig. 9. Time Base and Scaler connect to each other and main frame via rotary switch and connector assembly. Note legend at lower left of drawing.

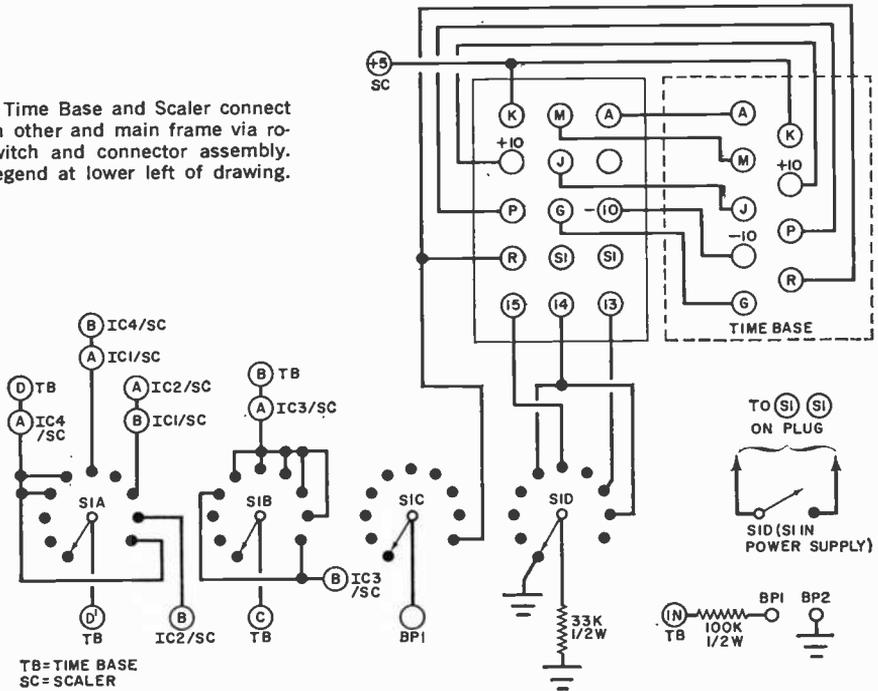

ly when the module is used with the main frame. Also, the counter has a built-in TEST circuit to which you can switch at any time to check the operational status of the Lab.

**Assembling the Module.** The use of integrated circuits in the Time Base and Scaler subassemblies makes it necessary that the cir-  
(Continued on page 96)

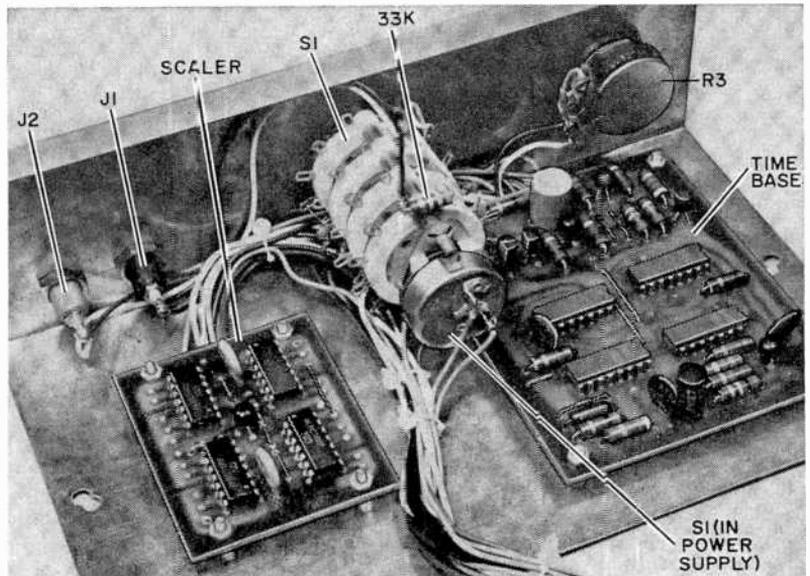


Fig. 10. Time Base and Scaler circuit boards fasten to chassis with 4-40 machine hardware and spacers. A 33,000-ohm resistor ( $\frac{1}{2}$ -watt) is used to limit current through decimal point in readouts. Wires connect to foil sides of boards.



# **THE NUMBERS GAME**

IF FOUR IS BETTER THAN TWO, IS SIXTEEN BETTER THAN EIGHT?

In 1961, **POPULAR ELECTRONICS** turned loose an avalanche and has lived through a storm of brickbats and bouquets. At that time, the "Sweet Sixteen" represented a hi-fi system that many readers wanted to build and find out first hand if the multiple-speaker idea would work. Sometimes it did, many times it didn't. In this article, our specialist on speaker systems tells why.

**T**O THOSE SYMPTOMS of national madness, such as the tulipmania craze in the 1600's, most knowledgeable audio enthusiasts

usually add the multiple-cheap speaker epidemic of the early 1960's. **POPULAR ELECTRONICS**<sup>1,2</sup> instigated the construction of thousands of speaker systems, each containing 16, or more, small 5" permanent magnet speakers. Although the heyday of the craze has abated, hundreds of these systems are still being constructed—usually for the wrong reasons.

According to the builders of the multiple speaker systems, the obvious advantages could be summarized as follows:

A. The system produces noticeably

---

---

BY DAVID B. WEEMS

POPULAR ELECTRONICS

lower distortion because the amplifier power is divided between many speakers.

B. The use of multiple speakers extends the bass range since mutual coupling permits all speaker cones to work together in unison at the lower frequencies.

C. The dips and peaks in the response of individual speakers are averaged out and the overall frequency response of the system is very smooth.

D. The use of small cones in the multiple speaker system insures the generation of a good treble response.

E. The multiple small speaker system does not require a crossover network and thus eliminates phase shift effects.

F. There is a noticeably "bigger" sound due to the expanded area of the source.

G. The multiple small speaker system can be built for a very low dollar figure.

All of the above qualities represent worthy goals. The reasons supporting each goal seem clear and logical. Yet, the manufacturers of high fidelity speaker systems have failed to exploit the use of multiple cheap speakers. It is natural to ask why. A hard look at the various concepts and the advantages claimed for them may disclose the answer.


**Distortion.** The sound output from a loudspeaker is usually not a true representation of the electrical signal input. The production of harmonic and intermodulation distortion are mentioned most often in considering loudspeaker system performance.

Harmonic distortion, frequency doubling, tripling, etc., can be produced in a speaker by either a nonlinear cone suspension or a nonuniform magnetic field surrounding the voice coil. Most speaker cone suspensions exert an increasing force on the cone as the cone moves away from its rest position. By intentional design, the suspension of a high-quality speaker tends to exert the same restoring force on the cone throughout its normal movement range. The magnet and voice coil structure of a good speaker is usually deep enough to always keep the voice coil operating in a field of uniform flux density.

Cheap speakers are made for applications where the normal power handling requirement can be measured in a fraction of a watt. At such sound intensity levels the cone movement—and distortion—is kept within tolerable limits. Since an array divides the power between all speakers, harmonic distortion should not be a major problem in normal use. At the very least, harmonic distortion will generally be lower than if one cheap speaker were used in the system.

However, if the speaker array is used to generate a high level of sound intensity at low frequencies, the cone movement can become excessive—producing distortion. In this case, the nonlinear suspension can be relieved of part of its distortion producing effects by installing the speaker array in a sealed enclosure. The captive air in the enclosure acts as a restoring force and tends to limit cone movement. Unfortunately, the creation of this "pressure box" treatment causes another problem that is discussed later on in this article.

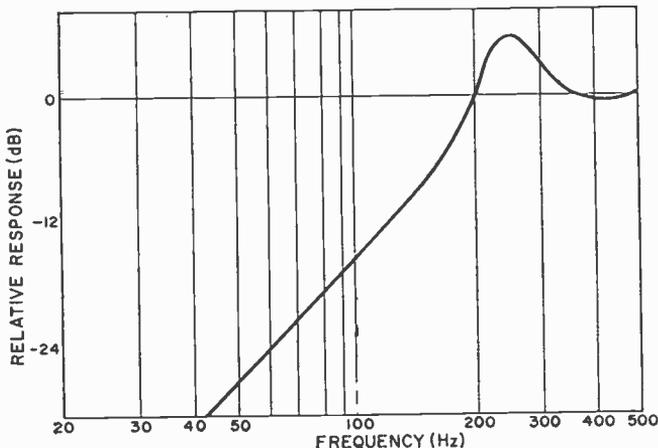**Intermodulation distortion** is the mod-




Generalized response curve of a cheap speaker in a sealed box has a resonance peak at 245 Hz. Amplitude of peak would depend upon speaker and enclosure properties.

ulation of one audio frequency by another audio frequency. Low frequencies can modulate high frequencies when both are being produced by the same speaker. High quality speaker systems reduce intermodulation distortion through the separation of bass and treble ranges. Thus, these two-way or three-way systems are also not as severely limited in their power handling capacity through a limitation of cone movement. Excessive cone movement aggravates and increases intermodulation distortion.

**Bass Response.** The bass response of any speaker falls off below the frequency of the fundamental cone resonance. The frequency of cone resonance is lowered as the compliance and mass of the cone are increased. The simplest and most obvious method of obtaining extended bass response has always been to choose a speaker with a low fundamental cone resonance frequency.


The idea of using a number of speakers to generate low audio frequencies at very high power levels was suggested as early as 1931.<sup>3</sup> Because of this suggestion, there have been claims that mutual coupling extends the bass response to a degree that is limited only by the number of speakers used. However, subsequent to the publication by POPULAR ELECTRONICS of the "Sweet Sixteen" system, James F. Novak<sup>4</sup> presented a mathematical analysis showing that coupling occurs at certain bands of frequencies and that these bands are determined by the separation between individual speakers. For example, when the center-to-center spacing between speakers is less than  $\frac{1}{2}$  wavelength, the air mass offers a reactance to the sound output. For the usual separation—about 6" to 8"—this puts a lower limit of about 200 Hz on the coupling range of an array of small speakers. To lower this frequency, the speakers should be moved farther apart; but confusing the issue, to make the coupling more effective, speakers must be close together.

Besides contending with the problem of spacing between speakers, the builder must also decide whether the enclosure holding the speaker array is to have an open back or be built as a sealed enclosure. Since mutual coupling increases the air load, the effective mass of the speaker cones is increased tending to lower the resonant frequency of the array below that of a single speaker. However, when the array of speakers is mounted in an airtight enclosure, the fundamental resonance of the speaker system is

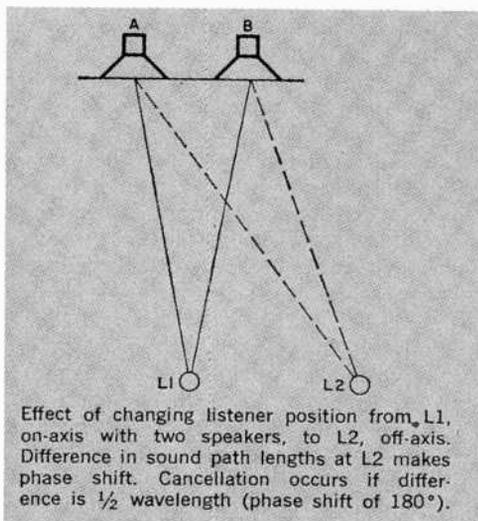

raised. In this trade-off, if the enclosure is small enough to add some restoring force to the cones and reduce distortion, it will also have the effect of raising the array resonance probably far above the original frequency of an individual speaker. Theoretically, a cheap speaker in a sealed enclosure should have its amplitude of peak resonance vary inversely with the damping on the speaker (see illustration). Cheap speakers are notoriously poorly damped, both electrically and mechanically. Of course, the point of resonance can be lowered by omitting the enclosure back, but the distortion increases and the frequency response curve of the speaker system becomes dependent on the shape of the open-backed box.

A large, shallow open-backed box pro-

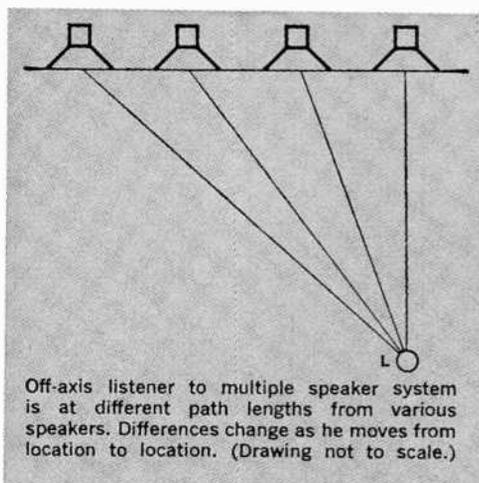

duces less peak amplitudes and more extended response than a small, deep open-backed box. Unless distortion becomes a major problem, the back should always be removed from the enclosure of a multiple cheap speaker system to improve the bass response.

**Synthetic Bass.** Distortion, especially that caused by driving the speakers to the limits of their suspensions or magnetic fields, may produce the illusion of more bass frequency response. Griffiths<sup>5</sup> experimented with electronically induced distortion and seems to have confirmed the existence of this illusion.

In the Griffiths experiment, clipping and distortion, similar to that produced by over-driven cheap speakers, was purposely designed into an audio system with a 200-Hz low-end cutoff. The percentage of distortion was controlled by the listener until the bass was thought to be "equal" to that produced by a low-distortion full-range audio system. Experimental results indicated that most listeners heard more "bass" when the distortion in the filtered system was increased to certain arbitrary values.

Another kind of synthetic bass occurs in speaker systems that have a prominent resonance. A resonant frequency in the upper bass range—say about 250 Hz—may make the system sound full and bassy, although music played through it has a distinct one-note quality. The earliest vacuum-tube amplifier juke boxes were noted for their generous bass response—most of it at one frequency.

Listeners can also be deceived into hearing bass frequency response that isn't there in the first place! A land line telephone system doesn't reproduce the fundamentals of a known voice, but the harmonic structure is recognized by the listener and the ear and brain supply the missing information. This tendency to hear the missing fundamental notes often leads the owner of a miniature transistor radio receiver with a 2" speaker to compliment the product on its "fine tone."

Some types of synthetic bass may sound satisfactory—even impressive—at first hearing. But if the listener becomes accustomed to hearing true fundamental bass response, he won't be happy with synthetic bass again.

**Smooth Response vs Phase Shift.** One of the qualities attributed to the multiple speaker system is that of a smoothed response—considered to be an absolute requirement for high-fidelity sound reproduction. However, many authorities claim that a medium-

range system with a smooth response is preferable to a wide-range system that has numerous peaks and dips in the audio response curve. And, peaks are worse than dips.


It is now well accepted that a speaker's response curve is always smoother when the speaker is operated at a reduced volume level.<sup>6</sup> For example, a 10" full-range speaker may have a high-level response curve embracing the spectrum between 40-20,000 Hz at  $\pm 12.5$  dB. When the input is reduced by 75%, the response curve is within  $\pm 5.0$  dB. Presumably, operating a number of speakers at low volume should flatten the overall response curve. Unfortunately, what sounds good in theory does not produce acceptable results in practice.

The audio enthusiast who has built several multiple-speaker systems soon realizes that the results are fairly unpredictable. A system using only four speakers may sound pretty good, although the builder has a feeling that the sound could be improved. The number of speakers is doubled, but the sound is still not right. The number is doubled again and the system sounds terrible. The faults are numerous, but they are difficult to identify—except for some obvious peaks in the midrange.

The mid-range peaks are due to mutual coupling between speakers. The maximum coupling and boost is at the sound frequency corresponding to a separation of one-quarter wave length. In a multiple-speaker system with center-to-center spacing of 7" to 8", the coupling peak is at about 500 Hz. This peak is insidious and even if not immediately noticeable, makes the system sound "loud" even at low volume levels and eventually proves quite tiring to the listener.

The problem is amplified when speakers are mounted so that there are many identical center-to-center distances and for this reason the square pattern of mounting multiple-speakers is one of the worst possible arrangements. This also helps explain why larger numbers of smaller speakers sometimes sound much worse than a similar system with only four to six speakers.

In addition to the boost in the mid-range by the multiple-speaker system, the same arrangement produces sharply defined peaks and dips at the higher frequencies. These upper-range deviations are noticeable to the listener who is sitting off axis of the system. They occur at frequencies where the sound waves from adjacent speakers reach the listener at various phase angles (see illustrations). Researcher Joel Julie<sup>7</sup> calculated that

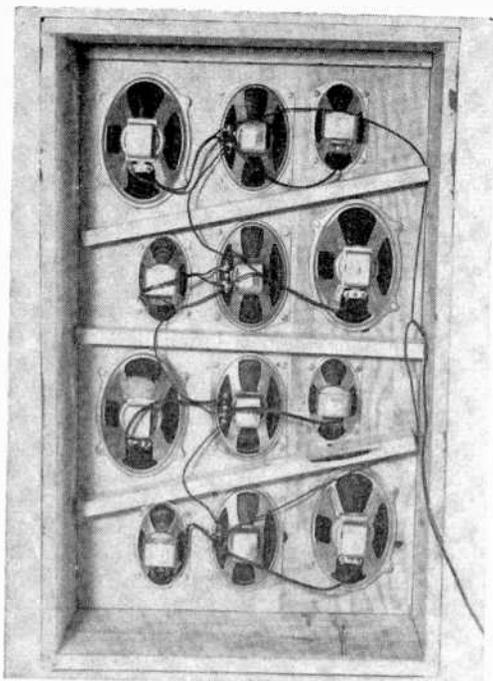

Speakers of different sizes permit unequal spacing between speakers and staggered resonances, alleviating two of worst faults of multiple speaker systems. But problem of restricted fundamental bass response and high-frequency dispersion remains.

for a listener  $10^\circ$  off axis of two speakers separated by center-to-center distance of only 8", the  $180^\circ$  phase shift occurs at 4200 Hz. As the listener moves farther off center, the frequency of cancellation decreases and at  $30^\circ$  it is down to 1650 Hz.

For the two listening positions cited above, the listener would also receive in-phase sound boosting at 8400 Hz and 3300 Hz, respectively. At frequencies other than those specified, the sound waves mix with varying degrees of phase shift and the result is sound-wave phase distortion.

Since the broad results represent what happens with only two speakers, the reader can imagine that the phase interference situation becomes incredibly complex in a multiple-speaker situation.

Phase interference can occur in an ordinary two-speaker woofer-tweeter arrangement, but only at frequencies near the crossover point where both the woofer and tweeter are producing the same tones. Phase shift in crossover networks may be more of a problem than generally recognized, but it could hardly produce the nightmare that is gen-

erated from multiple speakers mounted on a single baffle.

**The Big Sound.** The feeling of spaciousness from a sound source depends, in part at least, upon good dispersion. Large speakers are notoriously directional devices at the higher audio frequencies. At frequencies above that at which the wavelength of the sound is equal to the diameter of the speaker cone, the dispersion is poor. Thus, when several speakers are mounted on a square baffle and all of them reproduce the high audio frequencies, the source is spread over the baffle, and dispersion suffers.

**Cost.** Since the introduction of the "Sweet Sixteen" in the early 1960's, the cost of building such a system now mitigates against its construction. Numerous manufacturers now offer a variety of woofers with resonant frequencies and prices far under comparable models available 10 years ago. Meanwhile, the cost of plywood and other lumber has skyrocketed and when this material cost is added to the price of obtaining 16 speakers, the multiple-speaker array is no longer cheap.


To make such an investment in an essentially cheap speaker system defeats one of the main purposes of assembling a multiple-speaker system.

It would be unfair not to mention in this article that there are useful purposes to be served by multiple speaker systems. Several good-quality woofers in a multiple system will handle far more power with much lower distortion than a single woofer. The use of multiple speakers in a line radiator provides good horizontal dispersion and the omnidirectional speaker system can frequently be used to definite advantage.

The ordinary multiple-speaker system has seen its day. It was a good idea—but, the facts of life are catching up with it. ~~50~~
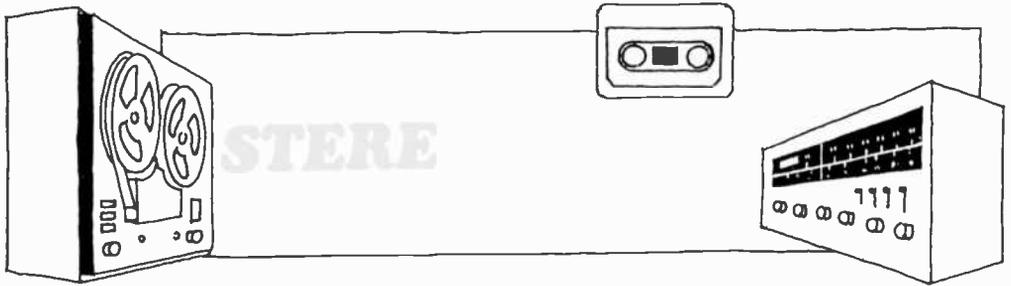
## References

- <sup>1</sup>Jim Kyle, "Sweet Sixteen," *POPULAR ELECTRONICS*, January 1961, p 55.
- <sup>2</sup>David B. Weems, "Build the Mixed Twelve Speaker System," *POPULAR ELECTRONICS*, March 1967, p 74.
- <sup>3</sup>E. W. Kellogg, "Means of Radiating Large Amounts of Low-Frequency Sound," *Journal of the Acoustical Society of America*, July 1931, p 94.
- <sup>4</sup>James F. Novak, "Performance of Series-Parallel Speaker Arrays," *Audio*, September 1961, p 23.
- <sup>5</sup>John D. Griffiths, "Apparent Bass and Nonlinear Distortion," *IEE Transaction on Audio*, July-August 1961, p 117.
- <sup>6</sup>H. A. Hartley, *Audio Design*, Gernsback Library, 1958, p 151.
- <sup>7</sup>Joel Julie, "Minimizing Interference Effects in Tweeters and Tweeter-Woofer Combinations," *IEEE Trans. on Audio*, March-April 1964, p 30.



Third in a Monthly Series by J. Gordon Holt

**F**OUR-CHANNEL STEREO is here. Whether it is here to stay is questionable; but one thing certain is that, the less it costs the consumer, the better are its chances of survival.

Ideally, four-channel stereo should be reproduced using a four-channel tape play-back machine, a four-channel preamplifier, two stereo amplifiers, and four loudspeakers. This will be expensive, even if you are prepared to swap four medium-fi channels for two hi-fi channels. It will also mean a permanent commitment to tape, which is persistently costlier than discs and makes your disc collection obsolete if for no other reason than that you just won't buy anymore discs.

The high cost of four separate channels is not likely to dismay the home equipment manufacturers. But if recording studios and broadcasters have to scrap some of their present equipment and duplicate the rest of it in order to switch to four channels, they will drag their feet; and that, plus consumer resistance, could quash quadrasonics before it ever gets off the ground. Under the circumstances, it is hardly surprising that there is considerable interest in the possibility of going four-channel without having to go all the way.

A number of people are working on ways of reproducing four channels via two channels; and at the time this was written there had been demonstrations of two such systems: one developed by Peter Scheiber and the other promoted by David Hafler of Dynaco—who points out that he did not invent it. (The "Hafler system" and some interesting variations thereof have been in use in some European countries for at least four years.) There will be others demonstrated in the future; and the industry will take careful note of each because one of them may determine the future (or lack of it) of four-channel sound.

The problem facing these designers is that there is simply no way, at any "state of the

art," of making two channels carry as much information as four channels. The thing that offers some hope of success is the fact that, most of the time, the two channels of a stereo pair are not fully "occupied" by program material; and when they are, there is usually a substantial duplication of material in both channels. Thus, the hope is to use the "gaps" between unduplicated signals to carry information for the other two channels or to find a way of preventing material from wasting space.

Both the Scheiber and Hafler systems are based on the latter approach, using matrixing to suppress duplicated material in such a way that a later "comparison" between the channels from which it was removed allows it to be reconstituted. Matrixing, by the way, simply refers to a process whereby differences in the intensity and electrical polarity of two or more signals are used to cancel out unwanted material and strengthen the desired material.

**In the Groove.** The easiest way to visualize how matrixing works in the Scheiber and Hafler systems is in terms of stylus motion in a disc groove. The solid arrows in Fig. 1 show the direction in which the stylus tip vibrates in a conventional two-channel recording, as viewed from the front of the pickup. Modulations in the left and right channels are at a

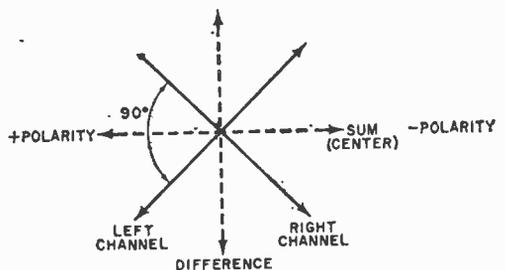


Fig. 1. Stylus motions in two-channel disc groove. Dotted arrows are resultants of left/right axes.

45-degree angle to the horizontal and at right angles to each other. The right-angle relationship is important as it permits the stylus to move along one axis without changing its position along the other axis, to provide theoretically perfect channel separation.

The dotted horizontal arrow in Fig. 1 represents the direction of stylus motion when both stereo channels carry identical in-phase information (that is, both move simultaneously at 45 degrees to left or right). The *average* motion then is horizontal, at 45 degrees to each axis, separation is only 50% and each main channel reproduces half of the resulting signal in-phase. This condition causes the sound to "appear" midway between the side speakers, directly in front of the listener. Normally, it is a "phantom" center, since it seems to be coming from a loudspeaker where there is no loudspeaker, but if a third speaker is connected so as to receive the combined signals from the left and right channels, the resulting "matrixed" signal will appear from that speaker twice as loud as from either side speaker. This effectively derives a third channel from the original two.

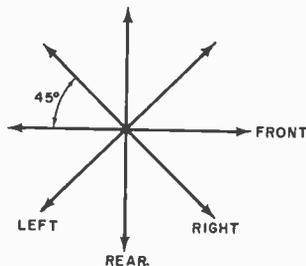


Fig. 2. Hafler system derives signals from sum/difference axes to drive front and rear speakers.

The difference information in a stereo groove comes through as *vertical* modulations (dotted vertical arrow). If a signal is equal in both channels but out of phase, difference (vertical) information will be at a maximum, the front-center adding channel will "see" equal plus and minus polarities, and complete cancellation of the signal will occur. The center speaker will be dead, while the side speakers will each reproduce half of the total signal out of phase.

Now, suppose we add a fourth loudspeaker, connected so as to respond only to difference signals. Equal out-of-phase signals will then be reproduced through that speaker, twice as loud as through the side speakers, while the front center speaker will remain "dead." This is how the Hafler four-channel system works.

Figure 2 shows how these four channels are represented by groove modulations. Note that the front and rear modulations are at right angles to one another (providing 100% potential stereo separation) but adjacent channels are 45 degrees apart so separation between these cannot be better than 50%. Thus, while it is possible for a perfectly balanced signal to cut one channel off completely, the other three channels will continue to be active, and the center one of those will be twice as loud (+3 dB) as the flanking channels. This is enough "separation" to provide a strong impression that the sound is coming from that center speaker, as long as you sit roughly in the middle of a four-speaker rectangle. A closer seat to any one of the three active speakers will make it predominate even when one of the others is 3 dB louder.

**But Is It Compatible?** Mr. Hafler claims that his system is "completely compatible with normal two-channel stereophonic reproduction," which is almost but not quite true. On a two-channel system, a point-source rear signal would emerge out-of-phase from the side speakers, producing the vague kind of imaging normally expected from out-of-phase speakers. This is hardly compatibility. Monophonic playback would be even less satisfactory, since the mixing of the out-of-phase rear signals would cancel them out, neatly eliminating from the music any instruments that were located at the rear of the listener.

There are some definite advantages to the Hafler system, not the least of which is its extreme simplicity. The playback dematrixing of the four channels from two can be done without electronic hardware. All it takes is four (preferably identical) loudspeakers connected as shown in Fig. 3. You can in fact dispense with the front center speaker if the side speakers are able to produce a firm and definite "phantom center" by themselves. The fact that the consumer will not have to buy decoding devices may, however, account for some of the industry's current lack of enthusiasm.

Another nice thing about the Hafler system, at least as far as the consumer is concerned, is that it can be used with some existing two-channel recordings to derive a legitimate rear-ambience signal. The theory here is that any natural ambience, having been reflected several times from the walls and ceiling of the recording hall (upholstered seats minimize floor reflections), has random phasing, of which roughly half at any given moment is out-of-phase energy that will be reproduced

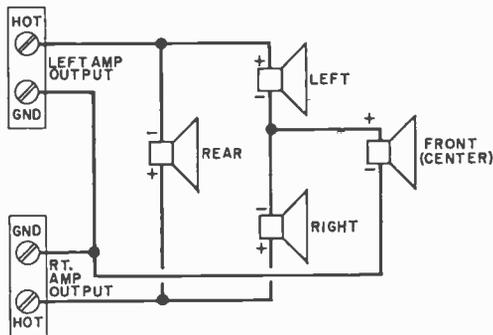


Fig. 3. Dynaco's recommended loudspeaker hook-up for Hafler four-channel playback. All speakers should be identical, and the two stereo channels should be modified to provide 6 dB of separation (unless a separate summing amplifier is used to drive the front center loudspeaker).

by the rear loudspeaker. Because of the limited separation between the rear speaker and the side speakers, some side-channel information comes through the rear speaker along with the ambience, but there is enough pure ambience in many recordings to add an impressive sense of spaciousness to the sound, and to make two-channel reproduction sound disturbingly "flat" by comparison.

As Dave Hafler points out, the effect could be greatly heightened if the recording companies actually added extra out-of-phase ambience to their two-channel recordings, instead of depending on random-phase pickup from their present mike setups. His suggestion has not been met with overt enthusiasm from the major American recording companies, but industry scuttlebutt has it that some European companies are already doing this, and four-channel playback of some recordings (a la Hafler) would seem to confirm this rumor. I have not heard of any disc manufacturer who is making—or even contemplating—four channel ping-pong recordings for Hafler playback, although this would be possible with the separation and compatibility limitations mentioned previously.

Peter Scheiber has not, to my knowledge, made any claims for the compatibility of his system. In fact it is less compatible than the Hafler proposal. The Scheiber system uses exactly the same matrixing procedures as Hafler, but with two significant differences. One of these is shown in Fig. 4, where it will be noted that the stylus axes for the four channels lie midway *between* the axes used by the Hafler system. It is as though the whole arrangement had been rotated  $22\frac{1}{2}$  degrees. This initial phase rotation or "encoding" takes place in a circuit that is a masterpiece of simplicity, involving only a handful of resistors.

**Something Extra.** The dematrixing decoder for the Scheiber system playback does

exactly the same thing in reverse, but because the axes of adjacent channels are at  $45^\circ$  angles to each other, the adjacent-channel separation is no better than from the Hafler system. Scheiber carried things a bit further, though, by adding to the basic decoder circuit a pair of variable-gain control amplifiers and sensing circuits. Now, when a signal is supposed to appear in one channel only, the device senses the very large separation between that channel and the opposite one and automatically shuts off the two adjacent channels where crosstalk is appearing. At the same time, the levels of both the "speaking" channel and its opposite (which has unlimited separation) are increased to overcome the 3-dB dematrixing loss. The control action is almost instantaneous so it can operate selectively within the structural details of a complex signal. "picking out" each cycle and routing it to the proper speaker.


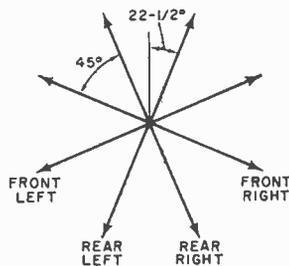


Fig. 4. Scheiber system produces modulation axes  $22\frac{1}{2}^\circ$  rotated from those used in Hafler's system.

Unlike the Hafler system, the Scheiber *can* reproduce four-channel ping-pong effects, and this is in fact its strong point. At the demonstration I attended, I was not able to tell any difference whatsoever between a four-channel tape of ping-pong-times-two material and the Scheiber playback, but I wasn't so sure about how it behaved with more complicated program material. Perhaps complex signals such  
(Continued on page 100)

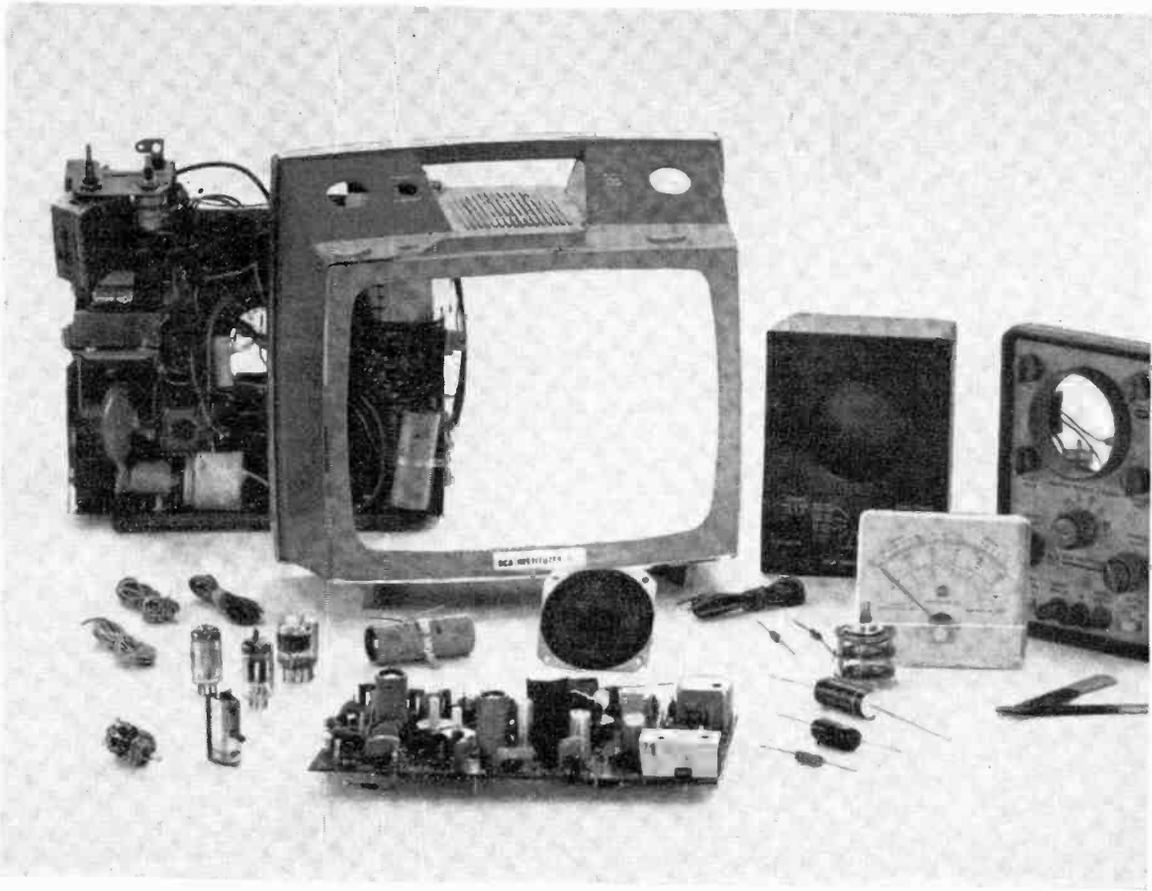

**Look! You get 25 kits...  
more than ever before at no extra  
cost...for your practical "hands-  
on" learning of electronics and  
TV with RCA Institutes Home  
Training! Send postcard today!**





# THE PRODUCT GALLERY

Third in a Monthly Series by "The Reviewer"

**A**S A GENERAL RULE I would prefer not to discuss a couple of allied products in the same column, but the summer months provided the opportunity to take a close look at CB (Citizens Radio Service). As a result, I am devoting much of this column to a CB antenna that has been around for several years and a 5-watt input mobile CB transceiver that apparently typifies current trends in circuit design and performance.

**The Avanti "Astro-Plane."** There is no textbook explanation or analysis of the unusual physical configuration of the Astro-Plane. It is a CB antenna totally unlike every other base station antenna. To a minor extent the Astro-Plane might be thought of as an inverted colinear with vastly shortened radials and a trombone matching section. But even this supposition is not entirely correct, although maximum signal radiation appears to come from the 4' "clear" section beneath the capacity-hat or top-loading radials.

Power to the Astro-Plane is introduced to one leg, is divided at the bottom of the antenna and passes to the other leg going up to the "grounded" side of the coaxial line (gamma matching?) and is balanced in the top-loaded section against the lower section of the antenna. The manufacturer claims a vertically polarized 4.4-dB gain over an isotropic dipole and an SWR of less than 1.4:1.

**Installation.** The Astro-Plane is shipped disassembled in 15 pieces sans supporting mast. The supporting mast section should be at least 12' long in order to provide a 4' clearance between the bottom of the Astro-Plane and all other surrounding objects (metallic tower, other antennas, etc.). A coaxial cable feedline must be provided by the user and should be 52-ohm cable. The manufacturer recommends the use of RG-8/U cable for runs longer than 30-35'.

The smaller diameter cable—RG-58/U—may be used for short runs.

Assembly time will vary according to what provisions you have available for mounting the supporting mast section. Bolting together the Astro-Plane itself will require under one hour and should be done in an open area where supports can be provided to keep the bottom closed loop and the top-loading radials off the ground.

The antenna itself is lightweight (3½ lb) and is physically well-balanced around the supporting mast. Although it doesn't look it, wind loading is minimal and no bending or distortion has been observed at wind gusts up to 40 mi/h.

**On the Air.** Switching over to the Astro-Plane from a colinear produced several immediate surprises. The background noise level took a nose dive, long range (1000-plus miles) skip signals were stronger and close-in skip (400-500 miles) was weaker. The decrease in background noise level was admittedly disturbing and a check was made on the SWR with the following favorable results:


Channel Number	SWR
1	1.5:1
4	1.4:1
7	1.4:1
10	1.35:1
13	1.3:1
16	1.3:1
19	1.25:1
22	1.2:1

Candidly, the exact reason for the reduction in background noise level has not been determined at this writing and may be due to a variety of contributory causes. However, the skip effects appear at first view to verify the manufacturer's claim of greater signal concentration (lower angle of radiation) close to the horizon. The Astro-Plane is strongly polarized vertically and in comparison with other CB antennas seems


to attenuate horizontally polarized signals on the order of 24 to 26 dB.

Mounted at the legal height for CB antennas, signals have been heard on ground wave out to 45 to 50 miles. Sky wave signals (both double-hop sporadic-E and F2 layer) have been heard at distances exceeding 2000 miles. As far as can be determined, the hori-

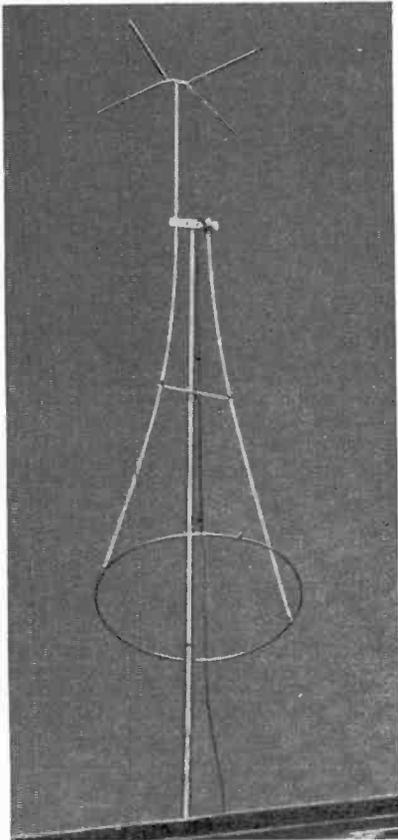
zontal pattern of the Astro-Plane is omnidirectional and the SWR does not change radically when operating the CB base station in a rain shower. After eight weeks of use, I am still pleased with the results and will report further on this antenna during the summer of 1971 after it has been subjected to a winter in the northeastern states.



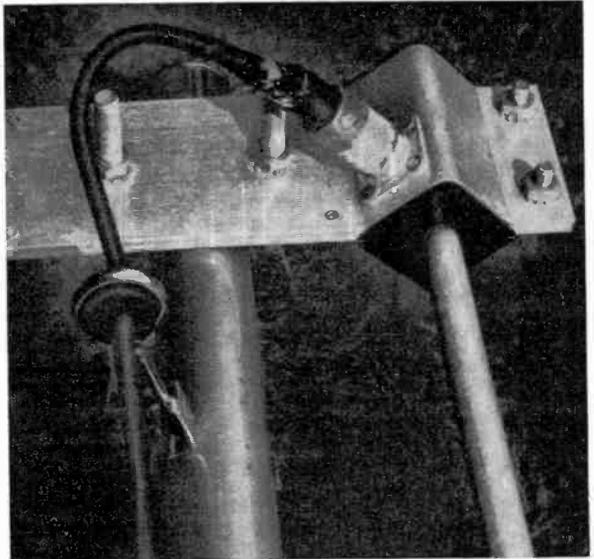The Avanti Astro-Plane may be thought of as inverted colinear with short radials (top, above) and a trombone matching section below. Shortened top-loading radials are made of pre-bent seamless aluminum tubing. Liberal use of lock washers (see photo at right) practically eliminates the possibility of wind or ice loading bending the radials.



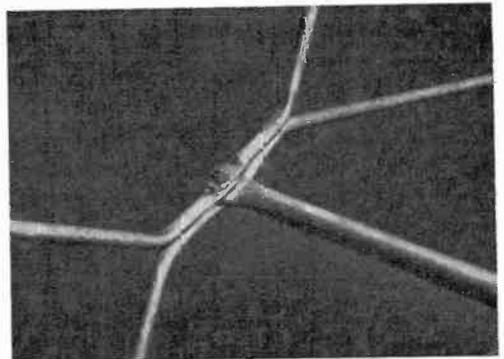Don't forget to caulk coax cable plug when it is attached to the Astro-Plane input connector. The liberal use of caulking prohibits moisture from corroding the silver plating on the connector and keeps it from entering the coaxial cable.



(More Product Gallery overleaf)

## Product Gallery continued

**The B & K Cobra 24.** This CB transceiver (5 watts input) can be operated on any one of the assigned 23 channels. The unit is designed for mobile operation (positive or negative ground—up to 14 volts dc input) and a 117-volt ac power supply is available as an optional extra for \$32.95. The receiver circuit is dual-conversion with a first i-f of 10.595-10.635 MHz and a second i-f of 455 kHz. A ceramic mechanical filter to provide adequate adjacent channel rejection is used in the first 455-kHz i-f stage and an integrated circuit is used in the second stage. The first mixer is a FET, but the r-f stage is a bi-polar transistor.

A full-time series-gate noise limiter is included in the receiver circuit and the squelch is adjustable (see below). The receiver circuit makes use of amplified agc and bootstrap secondary agc to minimize breakup and overloading when in the immediate vicinity of a very strong signal. The transmitter and receiver are fed from a 14-crystal frequency synthesizer with tolerances exceeding FCC requirements. The modulation is hi-level with audio filtering and speech compression—called "Dyna Boost." The output is rated at 3.5 watts into 50 ohms. Antenna loading may be optimized by adjusting one section of the output network (rear panel insulated screw-driver adjustment).

A switch on the front panel disables the transmitter and feeds the modulator audio output to an external PA speaker. The PA volume is adjustable using panel volume control.

**Laboratory Tests.** The Cobra 24 tested by POPULAR ELECTRONICS was equal to or better in terms of sensitivity, selectivity and rejection than the manufacturer's published specifications. Absolute AM sensitivity was 0.5  $\mu$ V for 10-dB (S+N)/N and the squelch threshold operated at the same level. The squelch range is limited (tight) and will not cut off signals exceeding 200  $\mu$ V input.

Selectivity was measured at just under 7 kHz wide at 6 dB down and 18 kHz wide at 60 dB down. On the test model the second i-f had ended up on 452 kHz instead of 455 kHz which resulted in a lopsided adjacent channel rejection equalling the manufacturer's claimed 50-dB rejection on the high-frequency side and over 70-dB rejection on the low frequency side. Rejection of interference possibly breaking through on the first i-f exceeded 90 dB.

The agc characteristic for a variation of r-f input of 80 dB was about 8 dB. This is

within the specifications supplied by the manufacturer who estimates the variation to be  $\pm 5$  dB (?) with an input change of 5  $\mu$ V to 0.5 V.


The measured power output (carrier only, unmodulated) with 13.6 volts dc input was 3.25 watts. Modulation is 100% with absence of clipping and distortion although the built-in compression circuit limits only positive peaks.

**On the Air.** The Cobra 24 was air-tested for several weeks as a mobile unit and performed better than average (if there can be such a thing) CB transceiver. Base-to-mobile transmissions were regularly carried out to distances of 15-plus miles using the Avanti Astro Plane antenna (see above) and the Antenna Specialists M-125 mobile antenna. Modulation from the Cobra 24 as received at the base station was crisp and even a woman's voice appeared to modulate the carrier to 90-100%. The noise limiter in the mobile unit was effective.

Electronically, the Cobra 24 is an example of the circuit refinements now seen in many Japanese top-quality imports. Personally I would have liked to see the addition of delta tuning to clear up reception of the CB's operating slightly off frequency. The thumb wheels on the squelch and volume controls are sufficiently unusual to be a little awkward to handle. Inside the Cobra 24 all parts appear to be well-mounted and presumably the transceiver can withstand road shock for a long time to come.



**Work in Progress.** Quite a few unusual products are scheduled for review in the next few issues. They include the new Heath-kit solid-state color TV, an Ungar IC de-soldering kit, various pieces of test equipment and several audio/stereo items. In addition, I am making up a column of smaller product reviews that will include a couple of things that just barely stay on the right side of the line from being fraudulently advertised. I have been fascinated by ludicrous products and frequently wonder if people really buy things that just couldn't possibly live up to their advertised claims. As much as I detest the idea of giving some people free publicity, I nevertheless feel that it is the purpose of this column to bring some of the phonies to your attention. It'll make interesting reading.

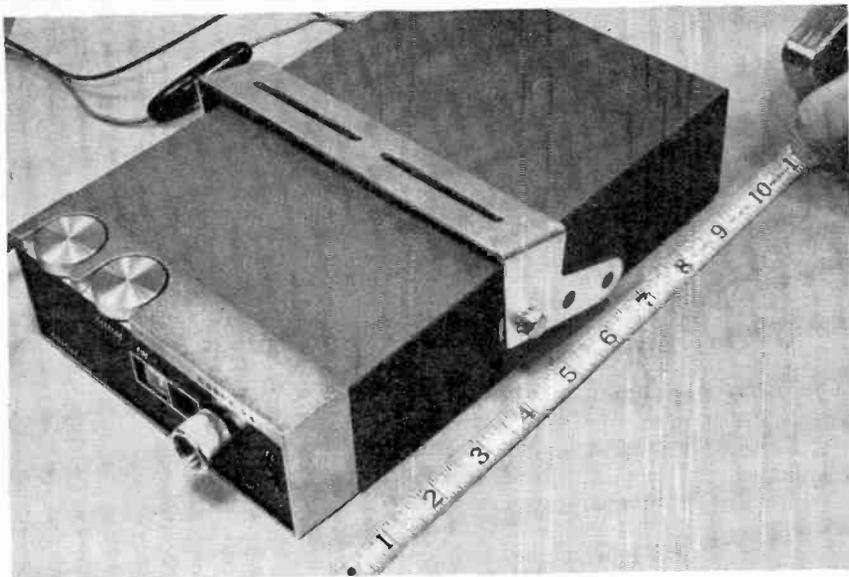My personal thanks to the many readers who wrote suggestions and constructive criticisms. Your letters were answered and your thoughts appreciated.



The Cobra 24 is one of the slightly deeper mobile CB transceivers. This may present a mounting problem in some automobiles. To be on safe side, allow a minimum of 12" (including the coax cable connector) if you don't want a transceiver that projects too far out from under the dashboard of your car.

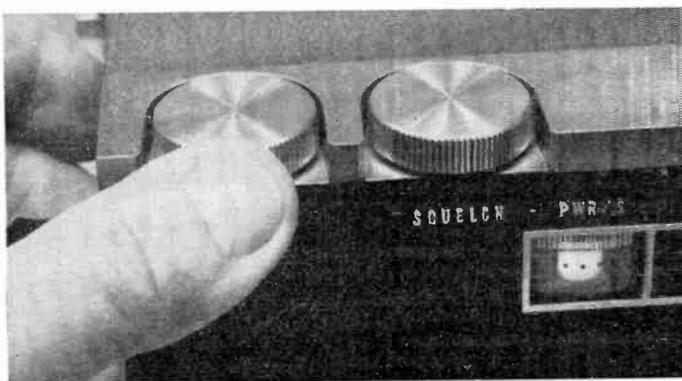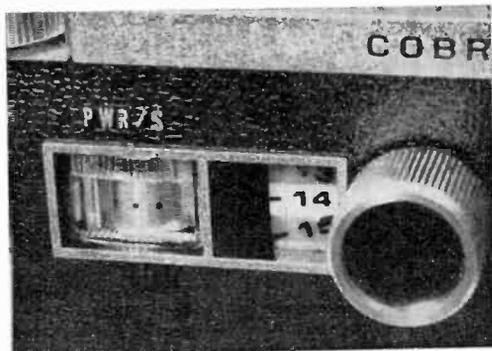Meter indicating incoming signal strength and relative power output is small and uncalibrated. This is of minor importance in mobile operation where visibility is limited and a rough indication is all that is required. However, as a base station, a true, accurate S-meter might be more desirable.



Your reviewer had some mixed feelings about the thumb wheels on the volume and squelch controls. They are unmarked, cannot be reset and require more than a little "getting used to."

**FOR MORE INFORMATION**

Astro Plane—Circle No. 86 on Reader Service Page 15.

Cobra 24—Circle No. 87 on Reader Service Page 15.



# COMMUNICATIONS

## SHORTWAVE LISTENING

**WWV Time Booklet Available**—The 1970 edition of "NBS Frequency and Time Broadcast Services, Radio Stations WWV, WWVH, WWVB, and WWVL" is now available from the Superintendent of Documents, U.S. Government Printing Office, Washington, DC 20402 for 25¢. This 16-page booklet contains detailed information on all the major services provided by the National Bureau of Standards through the WWV chain of stations. Catalog coding for this Special Publication 236 is SD Catalog No. C13.11:236. A copy is invaluable for interpreting the propagation forecast and geophysical alerts.

## CITIZENS RADIO (CB)

**German CB**—Citizens Radio in the Federal German Republic is a farce, according to a first-hand report by Dave Dunwoodie, KDM3144, published in the "7-11 Monitor," Spokane, Washington. Dave says that there are two classes of CB license—one limited to 2 watts input and a second limited to 30 watts input. Licenses are good for one month (!) and you get no callsign, but pay a minimum of \$10 depending on the number of mobile units. All outdoor antennas are illegal and operation on channel 17 is frowned upon since it is supposedly used by the ambulance services. Working skip is legal and you can yak your heart (and pocketbook) away.

## TELEVISION

**TV Channels Go Land Mobile**—The Federal Communications Commission has finalized a new plan to permit sharing of TV channels 14, 15, 16, 17, 18 and 20 with public safety (police/fire), land transportation, industrial and domestic public radio services. Restricted to certain cities (urban areas) the plan permits land mobile operation in the spectrum occupied by TV channels 14 and 15 in New York/northern New Jersey; 14 and 20 in Los Angeles; 15 and 16 in Detroit; 16 and 17 in San Francisco/Oakland; 14 and 16 in Boston; 17 and 18 in Washington; 14 and 18 in Pittsburgh; and 14 and 15 in Cleveland. Allocations for Chicago and Philadelphia are to be made in a few months. TV viewers will now be treated to a hash of public safety signals—as an entertainment bonus.

## SHORTWAVE LISTENING

**Changes at BBC?**—The External Service of the BBC is in for a rough time according to a press report in the London Sunday Telegraph (August 16). International shortwave broadcasting costs about \$28,500,000 per year and the Foreign Office is unhappy about spending that much money without having a bigger say of how it is to be spent and how the External Service is run. Should the Foreign Office put the External Service under its Central Office of Information, the "image" of the BBC's objective news coverage will be lost forever. Shades of Radio Moscow!

## CITIZENS RADIO (CB)

**And in New Zealand**—The information is confusing; but, in response to inquiries about weak phone signals: yes, there is a Citizens Band in New Zealand! The maximum power input is 1 watt and the channels (in numerical order) are: 26,425; 26,450; 26,475; 26,500; 26,525; 26,550; and 26,575 kHz. Sample location prefixes are: AK, Auckland; CH, Christchurch; IN, Invercargill; DN, Dunedin; and WN, Wellington. More specific information about licensing and equipment would be appreciated by the Editors.

## AMATEUR RADIO

**Hamfest Directory**—A Directory of 1971 Hamfests is being prepared by Art Collatz, K9JZM. Distribution will be nationwide. Amateur radio clubs are urged to appoint a representative to notify Art about their hamfest plans by Dec. 1, 1970. Address: Art Collatz, K9JZM, 2127 Market St., Blue Island, IL 60406.

## TELEVISION

**One More Try For Phonevision**—*In late August, the Federal Communications Commission granted Zenith Radio Corporation approval to proceed with its Phonevision system. Zenith Radio and Phonevision (now a misnomer) have been advocating a form of subscription television since 1947. The system was tested over the air via station WHCT (TV), Hartford, Conn. from July 1962 to February 1969. Phonevision is a means of scrambling a TV picture and sound so that it cannot be received via a non-customer's receiver. Subscribers rent a special decoder to unscramble the signal and pay only for those programs that they want to watch—in contrast to cable TV. Zenith radio has given options to RKO General, Teco, Kaiser, and Field Enterprises to use the Phonevision system in selected cities. Subscription-type Phonevision is expected to start in late 1971.*

## SHORTWAVE LISTENING


**Radio Free Europe and Radio Liberty**—There is a strong possibility that both Radio Free Europe and Radio Liberty will discontinue part of their services to eastern Europe within the next few months. The West German government has reportedly made informal inquiries to the United States about cessation of broadcasts until after the 1972 Olympic Games. RFE has cut back on its New York City staff (probably an uncorrelated action) and there are indications that Radio Liberty may reduce its hours of operation. If true, the excessive Soviet block jamming would cease—but heaven help the Communist Chinese when all that surplus jamming equipment is transferred to Siberia.

## BROADCAST BAND

**King David**—*A new pirate AM broadcasting station went on the air at 6:00 a.m. (GMT), September 1. Calling itself "Capital Radio," this pirate is operating several miles off the Netherlands coastline aboard the trawler "King David." The operating frequency is 1115 kHz with 10-kW output power and a daily schedule from 6:00 a.m. to 2:00 p.m. Instead of the top-heavy mast used by many pirate broadcasters—to their grief (see "Radio Hauraki," September issue)—Capital Radio uses a ring-type antenna that is claimed to radiate no sky wave! NRC and IRCA DX'ers take note!*
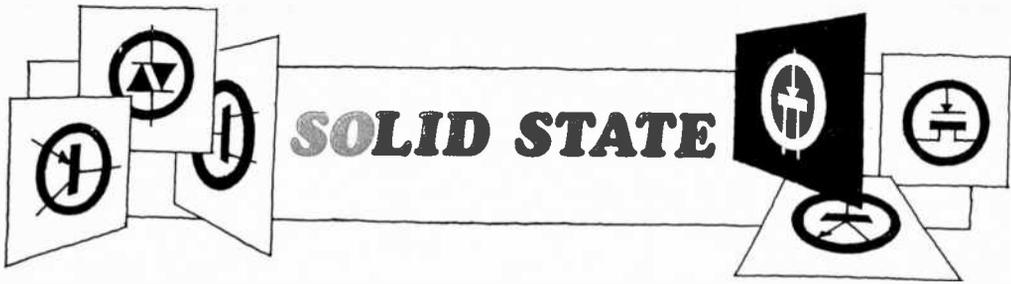
## RESEARCH

**It Looks Like a Boo-Boo**—Broadcasters—both AM and FM—have begun a campaign to force General Motors (Delco Radio Division)  
(Continued on page 102)



One Hundred Seventy-Fourth in a Monthly Series by Lou Garner

**W**ITH ROCK-AND-ROLL enthusiasts demanding multi-hundred-watt amplifiers, industrial engineers needing multi-kilowatt power controls, and communications specialists seeking higher and higher powers at ever-increasing frequencies, it is not surprising that nearly all semiconductors manufacturers are devoting major efforts to creating more powerful solid-state devices. But, it may come as a mild shock that most of these same manufacturers have smaller, but equally devoted, engineering groups assigned to developing devices with minute power requirements.

Actually, absolute power levels are relatively unimportant in most signal-handling, signal-processing, instrumentation, logic and computational applications, except where physical work must be performed. Electromechanical devices such as solenoids, loudspeakers, and motors require substantial power, naturally, as do induction and dielectric heaters, microwave ovens, and ultrasonic cleaners and machine tools. And, of course, relatively high powers may be required for long-distance data transmission and communication to compensate for fairly large line and radiation losses, but information handling circuits do not, in themselves, require much power. After all, one of the most effective of all information processing and control systems, the human brain, is a relatively low-power device.

The development of effective low-power circuits and equipment designs, then, offers a fertile and challenging field for the serious hobbyist wishing to push the state-of-the-art to its lower limits. A *powerless* functioning circuit, while a theoretical ideal, would be a virtual impossibility, but circuits with power requirements measured in the microwatt range are not only theoretically possible, but within practical reach.

An advanced experimenter tackling micropower projects for the first time should find the following guidelines of value:

- Use only low-leakage active and passive devices—i.e., high-quality silicon rather than germanium transistors, and ceramic or mica capacitors instead of electrolytics.

- Where possible, avoid the use of power-robbing bleeder networks.

- Series diode chains rather than resistive voltage dividers are preferred for stage biasing.

- Design for the minimum bandwidth compatible with application requirements.

- Employ series and/or complementary circuits where feasible, and Darlingtons where high gain is needed.

- Use high-value load resistors to achieve maximum gain per stage.

- If practicable, use class B or class C amplifier stages in preference to class A designs.

- Optimize the circuit stage-by-stage.

- Seek the *minimum* output voltage swing consistent with reliable operation in the intended application—that is, don't "overdesign."

On the commercial level, at least two major firms are now offering microwatt IC amplifiers as off-the-shelf products—Fairchild Semiconductor (313 Fairchild Drive, Mountain view, CA 94040) and Solitron Devices, Inc. (Semiconductor Division, 8808 Balboa Ave., San Diego, CA 92123).

A monolithic operational amplifier requiring only 100  $\mu$ W standby power when operated on a  $\pm 3$  volt dc supply, Fairchild's  $\mu$ A735 utilizes a direct-coupled, three-stage circuit featuring twenty-one transistors and sixteen thin-film silicon-chromium resistors. Six of its transistors are diode-connected. The device furnishes an output voltage swing of only  $\pm 1.2$  volts when powered by a low-voltage source, but can supply swings of  $\pm 12$  volts when a  $\pm 15$  volt power source is used. At the higher supply voltage the  $\mu$ A735's standby power is raised to 6 mW. The device's large-signal voltage gain ranges from 20,000 with a low-voltage supply to over 40,000 when higher source voltages are used. As is typical of operational amplifiers, its frequency response is dependent on the type(s) of compensation network used, but a suitable choice of external feedback components will extend the response to over 100 kHz.

Solitron's UC4250 is a general-purpose

operational amplifier designed for use with power supplies of from  $\pm 1$  to  $\pm 18$  volts. With a  $\pm 1$  volt dc source and its quiescent current adjusted to  $10 \mu\text{A}$  the device has a standby power requirement of *only*  $20 \mu\text{W}$ . The UC4250 can furnish a gain of 100,000 into a 10,000-ohm load when operated on a  $\pm 6$  volt supply, with its quiescent current adjusted to  $30 \mu\text{A}$ .

In tests at Solitron, two miniature electronic watch batteries were used to power a square wave oscillator using the UC4250. The circuit's load current checked out at a mere 100 pA, thus indicating that the oscillator should be able to run continuously for 30 months on one set of batteries. Unfortunately, the actual operational battery life is somewhat less, for these small cells have a rated shelf life of only a little over 15 months. The circuit's power drain is so small, then, that its power supply batteries would fail chemically long before they are exhausted electrically. How about that for low power?

Micropower circuits are particularly useful in medical electronics, biological and geophysical telemetry, portable instrumentation, long-term monitoring, and miniature computers. A recent development in another field may make such circuits of even greater value in medical appliances.

Working with selective catalysts, Drs. J. H. Fishman and J. F. Henry at Leeson Corporation's Moos Laboratories Division (Great Neck, N.Y.) have developed experimental fuel cells using human blood as a source of both fuel and oxygen: In practice, two electrodes are immersed directly into the blood stream, one of which reacts with glucose and similar organic materials, the other with oxygen, to produce electric power. The experimental units tested to date yield approx-

imately  $5 \mu\text{W}$  for each square centimeter of electrode area. Although this power yield may be improved considerably as techniques are refined, it is already sufficient to operate circuits comparable to Solitron's UC4250.

Looking to the future, one day we may see implantable solid-state heart pacers and similar aids which are powered by the patient's own blood stream.

Your editors would be interested in hearing of any micropower circuits developed by our readers. If of general interest, we may find a place for it here.

**Reader's Circuit.** A practicing engineer as well as an enthusiastic experimenter, reader Eugene Richardson (310 East Mason Ave., Alexandria, VA 22301) feels that the programmable unijunction transistor, or PUT, has not received the attention it deserves and, therefore, is not as widely used by most hobbyists as are such familiar devices as transistors, SCR's, diodes and conventional unijunctions. As he points out, the PUT is an exceptionally versatile device.

Essentially an anode-gate thyristor, the PUT is functionally equivalent to standard unijunction devices, but has a number of superior features. Its stand-by and holding currents are much lower, its *on* resistance considerably lower, and its peak current rating much higher. Further, its firing threshold can be either programmed or made variable and, in addition, its inherent regenerative action gives it a fast-acting characteristic.

As evidence of the PUT's versatility, Eugene has submitted the sweep/frequency divider circuit illustrated in Fig. 1 for consideration and possible use by other experimenters. Capable of delivering either sawtooth or pulse waveforms, its output can be

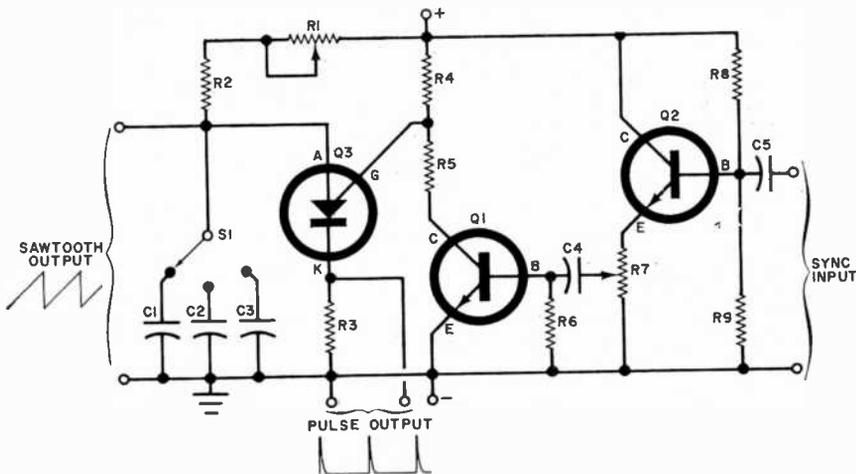


Fig. 1. Programmable unijunction transistor, Q3, is used in sweep/frequency divider circuit to deliver either sawtooth or pulse waveforms synchronized with an external signal.

synchronized with an external signal. He suggests that the circuit can be used as a general purpose waveform or pulse generator or, if preferred, incorporated into other equipment, such as an oscilloscope as a linear sweep, or in a counter as a pulse frequency divider.

In the circuit, the PUT,  $Q3$ , is used as a modified relaxation oscillator, with  $Q1$  serving as a bias control device and emitter-follower  $Q2$  as a sync amplifier/buffer. In operation,  $Q3$ 's anode-cathode capacitor ( $C1$ ,  $C2$ , or  $C3$ .) is slowly charged toward source voltage through a series resistor ( $R1$  and  $R2$ ), forming the leading ramp of a sawtooth waveform. During this period,  $Q3$ 's gate is maintained essentially at source voltage, because  $Q1$ , (part of the gate bias voltage-divider consisting of  $R4$ ,  $R5$  and  $Q1$ 's emitter-collector resistance), is operated without base bias and acts as an open circuit. Under these conditions, the PUT cannot "fire" (i.e., switch to a conducting state).

If, at this time, a positive-going sync pulse is applied to  $Q1$ 's base, the transistor starts conducting, dropping the PUT's gate voltage below its anode voltage and causing it to fire, discharging the anode-cathode capacitor through cathode resistor  $R3$  and develop-

ing a sharp output pulse. With the capacitor discharged,  $Q3$ 's anode voltage drops and the device switches back to a non-conducting state, permitting the cycle to repeat.

For optimum operation, the sync pulse rate should be at a frequency comparable to or higher than the relaxation oscillator's "natural" frequency, as determined by the supply voltage and its anode-cathode RC time constant ( $R1$ - $R2$  and  $C1$ ,  $C2$  or  $C3$ ). In fact, the sync pulse rate may be several times higher than the circuit's natural frequency, for the PUT will not fire until its anode voltage reaches a pre-established peak value. Since the output pulse rate (across  $R3$ ) can be an integral fraction of the sync frequency, the circuit may be used as an effective frequency divider.

In practice,  $S1$  serves as a frequency range control, selecting various capacitor values and thus changing the relaxation oscillator's RC time constant. Similarly, variable resistor  $R1$  acts as a "fine frequency" control. Potentiometer  $R7$  provides an adjustment of sync amplitude.

Eugene has not specified component values for his circuit, indicating that these will be determined by the individual devices used, by the dc supply voltage, by the desired

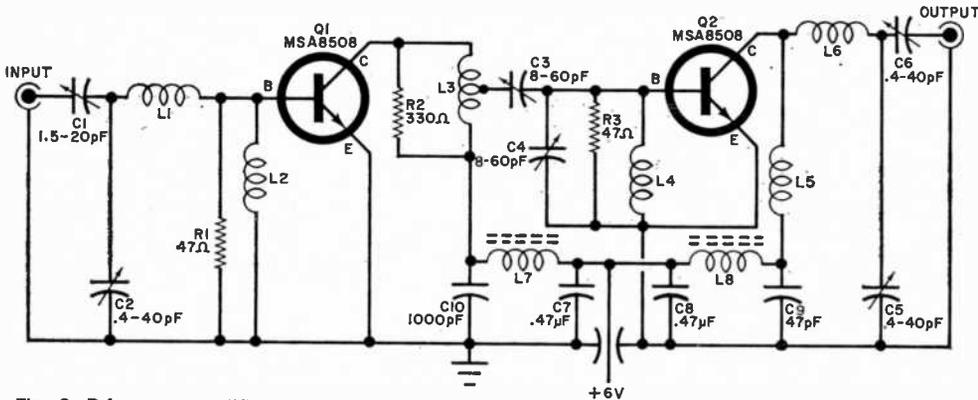


Fig. 2. R-f power amplifier employing npn VHF silicon power transistors can be used in either handheld, base station, or mobile applications. Operating frequency can be changed by varying LC values.





## COMMUNICATIONS RECEIVER

**MODEL SPR-4**  
**\$449<sup>00</sup>**  
**NET**

A general purpose receiver, the SPR-4 may be programmed to suit any interest: SWL, Amateur, Laboratory, Broadcast, Marine Radio, etc. Frequency Coverage: 150-500 KHz plus any (23) 500 KHz ranges, 500 to 30 MHz.

**FEATURES:** ● Linear dial with 1 KHz readout ● 4-pole crystal filter in first IF ● 4-pole LC filter in second IF ● Three bandwidths: 0.4 KHz, 2.4 KHz, and 4.8 KHz for: CW, SSB, AM ● Superior cross-modulation and overload performance ● Power: 120 VAC, 220 VAC, and 12 VDC ● Crystals supplied for LW, BC and seven SW bands ● Built-in speaker ● Notch Filter.

**ACCESSORIES:** 100 KHz calibrator, noise blanker, transceive adapter (T-4XB), DC power cord, loop antenna, crystals for other ranges.

● Direct Frequency Dialing ● All Solid State  
● Programmable Coverage ● FET Circuitry

For more details write: **R. L. DRAKE COMPANY**, 540 Richard St., Miamisburg, Ohio 45342

repetition rate(s) (frequency), and similar factors. However, he has suggested that the PUT can be GE types D13T1 or D13T2, or Motorola types MPU131 to MPU133. The other transistors ( $Q1$ ,  $Q2$ ) should be low-leakage, general purpose npn silicon devices. A relatively low value (under 50 ohms) resistor should be used for  $R3$  to insure a sharp output pulse and short discharge time.

**Manufacturer's Circuit.** Originally designed for operation in the Land Mobile Communications band, the r-f power amplifier circuit in Fig. 2 was abstracted from a brochure published by Fairchild Semiconductor to illustrate the use of their MSA8506-08 series of npn VHF silicon power transistors. Hams should find the circuit of particular interest, for it can be used in either handheld, base station, or mobile applications. A complete transmitter may be assembled by adding a suitable crystal-controlled FM oscillator/buffer, an antenna, and a dc power supply to the basic amplifier. The circuit's center operating frequency (175 MHz) may be shifted to other bands simply by changing its LC component values, although the transistors specified in the design are characterized for optimum performance at from 150 to 175 MHz.

The circuit is a straightforward arrangement with two cascaded npn common-emitter stages,  $Q1$  and  $Q2$ . Broadband coupling is used throughout to insure satisfactory operation with FM signals. Adjustable input ( $C1-C2$ ,  $L1-L2$ ) and output ( $C5-C6$ ,  $L5-L6$ ) networks are included to provide efficient coupling to the driver and antenna, respectively, while a tapped coil,  $L3$ , insures a match of interstage impedances.

Referring to Fig. 2,  $Q1$  and  $Q2$  are Fairchild type MSA8508. Capacitor  $C1$  is a 1.5-20 pF Arco type 402;  $C2$ ,  $C5$ , and  $C6$  are 0.4-40 pF Arco type 403;  $C3$  and  $C4$  are 8-60 pF Arco type 405;  $C7$  and  $C8$  are 0.47  $\mu$ F ceramic discs;  $C9$  a 47 pF mica capacitor; and  $C10$  and  $C11$  are 1000 pF feedthrough types. Resistors  $R1$  and  $R3$  are 47-ohm,  $\frac{1}{4}$ -watt, 5% resistors; while  $R2$  is a 330-ohm,  $\frac{1}{4}$ -watt, 5% unit.

Both hand-wound and commercial coils are used in the amplifier.  $L1$ ,  $L5$  and  $L6$  each consist of 2 turns of #18 wire,  $\frac{1}{4}$ " diameter;  $L3$  consists of 3 turns, #18,  $\frac{1}{4}$ " diameter, with a tap at  $1\frac{1}{2}$  turns;  $L2$  and  $L4$  are 33  $\mu$ H chokes; while  $L7$  and  $L8$  are small ferrite chokes (Ferroxcube #200-10-3B).

In common with most VHF projects, layout and lead dress are reasonably critical. Good r-f wiring practice must be observed

## If you can't come to the world's newest, largest and most exciting electronics department store, we'll mail the store to you!

### Exclusive!

Knight-Kit and Science-Fair Kits.

### Exclusive!

Realistic Lifetime Tubes.

### Exclusive!


Battery-A-Month Club.

World's finest selection of famous brands—in one book!



DIVISION OF TANDY CORP

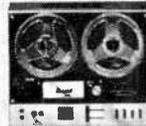New! 1971 Allied Radio Shack Catalog  
460 pages—thousands of electronic values!



Big Choice of Audio Items  
... Factory-Direct Savings!  
Allied TD-1099, 3-Head Stereo Tape Deck. Walnut-grain case. \$179.95

Realistic STA-120. Wideband AM/FET-FM Stereo Receiver. 140 Watts. With case. \$269.95



MAIL COUPON . . . or bring to Allied Radio Shack store.

ALLIED RADIO SHACK, 100 N. Western Avenue, 614  
Chicago, Illinois 60680

Yes! I want your big new 1971 Catalog. I enclose \$1 for mailing and handling (refundable with my first purchase of \$1 or more).

NAME \_\_\_\_\_  
First Middle Last

ADDRESS \_\_\_\_\_  
Street or Route and Box No.

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

I enclose  check  money order  cash.

**WORLD'S LARGEST! OVER 800 STORES IN 48 STATES. SEE YOUR PHONE BOOK.**

# There's Only One

# CB

# ANTENNA FOR YOU...

## HUSTLER

CB MOBILE  
MODEL TLA-27L  
**\$14.95**  
COMPLETE

If you are hard to please—if you want optimum performance—it's the HUSTLER TLA-27-L trunk lip mounted fiberglass antenna—only 48" tall—ready for easy installation: no holes to drill, cable to trim or solder (a Hustler exclusive). Complete, including 17' coax cable with connectors and priced \$4 below—yes four dollars below any similar competitive model.

It's HUSTLER for any requirement—choose from 118 models covering citizens-band, amateur radio and monitoring.

HUSTLER  
EXCLUSIVES

RUSH CATALOG  CB  HAM

NAME \_\_\_\_\_

STREET \_\_\_\_\_

CITY \_\_\_\_\_

ZIP \_\_\_\_\_

**NEW-TRONICS CORP.** 15800 COMMERCE PARK  
BROOK PARK, OHIO 44142

CIRCLE NO. 36 ON READER SERVICE PAGE

## McGEE RADIO Co.

WORLD'S BEST SELECTIONS  
AND LOWEST PRICES

# SPEAKERS

ALMOST EVERY SIZE FROM 1½ TO 18 INCH  
WOOFERS—TWEETERS—CROSSOVERS

MANY HIGH FIDELITY KITS

McGEE'S 176 PAGE 1971 CATALOG

SENT FREE ON REQUEST

### NORELCO HI-FI SPEAKERS

McGEE HAS ADDED A FULL LINE OF NORELCO  
HI-FI SPEAKERS FOR THE SYSTEM BUILDER.

McGee ships orders all over the U.S. When requesting our catalog please give name, address and zip code. Our 41st year in Kansas City. Catalog offers everything for Hi-Fidelity audio P.A. systems. All kinds of microphones. Names such as Shure, Bogen, Electro-Voice, University, Altec, Ampex, G.E. Tubes and Transistors. All kinds of parts. Everything for Educational and Industrial electronics. Write for your catalog today.

**McGEE RADIO CO.—1901—PE**

McGee St., Kansas City, Mo. 64108

CIRCLE NO. 22 ON READER SERVICE PAGE

## SOLID STATE

(Continued from page 85)

when duplicating the circuit, with signal leads kept short and direct and common ground points used in each stage.

According to Fairchild, the basic circuit will deliver 5 watts r-f output when driven by a 200 mW signal and operated on a 6-volt dc source. The design is not critical with respect to either drive or supply voltage, however, and, within reasonable limits, both higher and lower drives as well as dc voltages may be used without changing component values. With a 12-volt power supply and 400 mW drive, for example, the amplifier should deliver over 8 watts.

**R.F. Preamp.** We discovered the schematic illustrated in Fig. 3 in the back of a catalog recently issued by Teledyne Crystalonics (147 Sherman St., Cambridge, Massachusetts 02140). Although relatively simple, the design should have numerous potential applications in r-f instrumentation and communications as a general purpose preamplifier.

Featuring a type CP651 n-channel JFET in a grounded-gate configuration, the preamp could be duplicated easily in a single evening by any hobbyist with average skills. Standard components are used throughout, with *C1* and *C2* small ceramic capacitors, *R1* a half-watt resistor, and *L1* a 2 mH, r-f choke. Inductor *T1* is a 200:50-ohm untuned impedance matching r-f transformer. A 20-volt dc power supply is required, with the unit drawing 30 mA.


Crystalonics indicates that the preamp has a bandwidth extending from 500 kHz to 40 MHz and can furnish 10-dB voltage gain with a dynamic range of 140 dB. It will accept input signals of up to 3 volts p-p and has a noise figure of only 2.5 dB. Its cross-modulation characteristics are quite good. With 1-volt, 3-MHz and 5-MHz test signals, the 3rd order product is down 44 dB, while 0.25-volt signals reduce the 3rd order product to a low -80 dB.

**Device News.** Two new MODEM IC's, the MC1488L and MC1489L, have been announced by Motorola Semiconductor Products, Inc. (P.O. Box 20912, Phoenix, AZ 85036). Supplied in 14-pin dual in-line ceramic packages, both devices are DTL/TTL compatible monolithic integrated circuits designed to provide systems interfacing between communication networks and data terminal equipment. According to the manufacturer, these two new units are the fore-

POPULAR ELECTRONICS

runners of a planned line of MODEM system circuits.

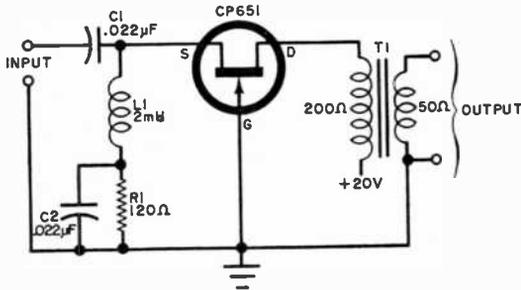
The MC1488L is a quad line driver consisting of four NAND gates: three two-input gates and a single input gate. Its output current is limited to 10 mA to comply with an applicable EIA standard.



The MC1489L is a quad line receiver including four special two-input NAND gates, with each containing three inverting stages. One input of each gate can be used as a response control node, and feedback is provided from the second to the first stage of each. With the response control input open, (Continued on page 94)

Fig. 3. An n-channel JFET in grounded-gate configuration (left) has applications in r-f instrumentation as a general purpose preamp.

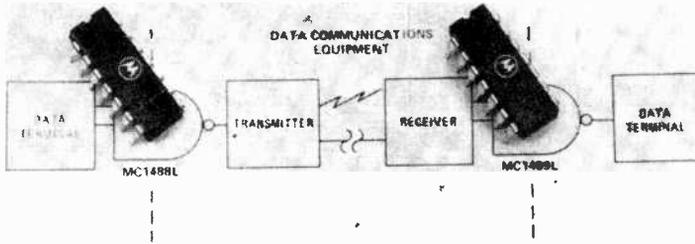New MODEM IC's from Motorola include a quad line driver containing four NAND gates (below left) and a quad line receiver which contains four two-input NAND gates. Both are DTL/TTL.



## If you're switched on to CB, switch up to Courier



### New Traveller II

Sleek and sassy, it's the world's smallest 23 channel CB radio. Instant warm-up, solid-state dependability, 100% modulation. All chrome cabinet and diecast face. One year warranty. **\$139<sup>95</sup>**


### New Classic II

A legend in its own time, it's a sleek mobile rig with equally good base station capabilities. Built-in AC power supply and P.A. function. 23 channels with 100% modulation. Illuminated S meter, slide controls, ANL delta tuning. One year warranty. **\$199<sup>95</sup>**


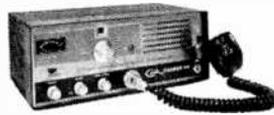
### New Base Station Mike BMT-1

Improve the performance of your CB, AM, FM or SSB transceiver with our base station mike with built-in pre-amp. Only **\$299<sup>5</sup>**



### New Ranger 23

Great performance, great value. Features cascode front end for greater sensitivity, nuvistor mixer for improved S/N ratio and full-time range expand. S-RF meter. Complete with all crystals for 23 channel operation. **\$199<sup>95</sup>**

**Special Offer!**  
17" x 22" CB  
Psychedelic Posters  
In Full Color



Courier Communications  
100 Hoffman Place, Hillside, New Jersey 07205

Please send me more information on:

- Traveller II\*       Classic II\*  
 Ranger 23 Plus       BTM-1 Mike

\* Enclose \$1 each and we'll send you a 17" x 22" full color psychedelic CB poster featuring the sensational new  Classic II  Traveller II (check one or both)

Name .....  
Address .....  
City ..... State ..... Zip .....


Dept. PE-11

# New from Heath...in time

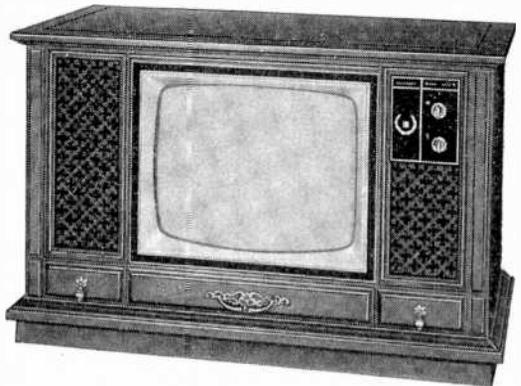
## New Heathkit® solid-state modular color TV

The result of over five years in research and development, these sets represent one of today's greatest color TV values. Here's why: a total of 45 transistors, 55 diodes, 2 silicon controlled rectifiers, 4 IC's containing another 46 transistors and 21 diodes plus 2 tubes (picture and high voltage rectifier) combine to deliver performance and reliability unequalled by any conventional tube set. Other features include: MOSFET VHF tuner; high-gain 3-stage solid-state IF; emitter-follower output; automatic fine tuning; VHF power tuning; built-in degaussing plus manual degaussing coil; automatic chroma control; adjustable noise limiting and gated AGC; "instant-on"... sound instantly, picture in seconds; bonded-face, etched glass picture tubes; adjustable tone control; exclusive hi-fi outputs; and 48-hour factory service facility for modules. The sets are designed to be owner-serviced... the only sets on the market with this exclusive feature. A built-in dot generator, volt-ohm meter, and modular snap-out epoxy circuit boards make routine adjustments and service a snap... virtually eliminating service calls and offering significant savings over the life of the set. It all adds up to the color TV buy of a lifetime in the GR-270 and GR-370... ready now for Christmas giving!

Kit **GR-270**, 227" 20V tube, 114 lbs. .... \$489.95\*  
 Kit **GR-370**, 295" 23V tube, 127 lbs. .... \$559.95\*  
 Kit **GR-370MX**, **GR-370** with RCA matrix tube,  
 127 lbs. .... \$569.95\*



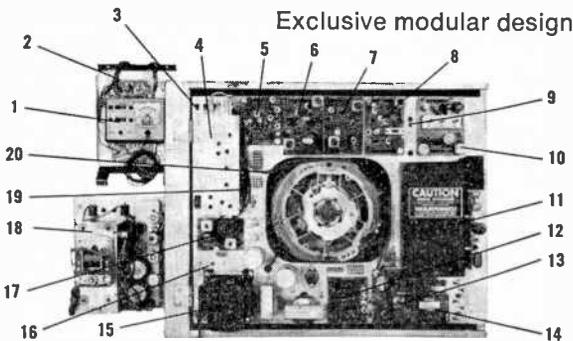- Modular plug-in circuit board construction
- MOSFET VHF tuner and 3-stage IF
- Pushbutton channel advance
- Hi-fi sound outputs — for amplifier
- Designed for owner-servicing




Exclusive modular design

- 1 Exclusive check-out meter
- 2 Tilt-out convergence/secondary control panel
- 3 Gun shorting switches
- 4 3-stage IF assembly
- 5 Plug-in AGC/Sync circuit board
- 6 Plug-in 3.58 MHz oscillator circuit board
- 7 Plug-in Chroma circuit board
- 8 Plug-in Luminance circuit board
- 9 Service and Dots switches
- 10 Plug-in Video Output circuit board
- 11 High voltage power supply
- 12 Plug-in Vertical Oscillator circuit board
- 13 Plug-in Horizontal Oscillator circuit board
- 14 Plug-in Pincushion circuit board
- 15 Conservatively-rated power supply components
- 16 Circuit breaker protection
- 17 Plug-in Sound circuit board
- 18 Master control panel
- 19 Hi-fi sound output
- 20 Plug-in wiring harnesses and connectors for faster assembly

### Choice of factory-assembled cabinets
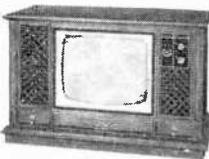
#### 3 models in 295 sq. in.

**Luxurious Mediterranean Cabinet...** factory assembled of fine furniture grade hardwoods and finished in a flawless Mediterranean pecan. Statuary bronze trim handle. 30-1/2" H x 47" W x 17-3/4" D. Assembled **GRA-304-23**, 78 lbs. .... \$129.95\*



**Deluxe Early American Cabinet...** factory assembled of hardwoods & veneers and finished in classic Salem Maple. 29-1/2" H x 37-1/4" W x 19-3/4" D. Assembled **GRA-303-23**, 73 lbs. .... \$114.95\*



**Contemporary Walnut Cabinet...** factory assembled of fine veneers & solids with an oil-rubbed walnut finish. 29-1/2" H x 35-1/4" W x 19-1/4" D. Assembled **GRA-301-23**, 60 lbs. .... \$74.95\*



#### 3 models in 227 sq. in.


**Exciting Mediterranean Cabinet...** assembled using fine furniture techniques and finished in stylish Mediterranean pecan. Accented with statuary bronze handle. 27-1/2" H x 41-1/4" W x 19-1/4" D. Assembled **GRA-202-20**, 85 lbs. .... \$114.95\*



**Contemporary Walnut Cabinet and Base Combination.** Handsome walnut finished cabinet sits on a matching walnut base. Cabinet dimensions 20-1/2" H x 31-1/4" W x 18-3/4" D. Base dimensions 7-3/4" H x 27-3/4" W x 18-3/4" D. Assembled **GRA-203-20** Cabinet, 46 lbs. \$49.95\* **GRS-203-6** above cab. w/matching base, 59 lbs. .... \$59.95\*



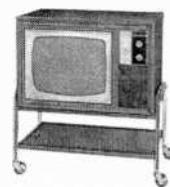**Handy Roll-Around Cart and Cabinet Combination.** Features the **GRA-203-20** walnut cabinet plus a walnut-trimmed wheeled cart with storage shelf. Assembled **GRA-203-20** Cabinet, 46 lbs. \$49.95\* **GRA-204-20** Roll-Around Cart, 19 lbs. .. \$19.95\* **GRS-203-5** Cart & Cabinet Combo, 65 lbs. .... \$59.95\*




# for Christmas giving
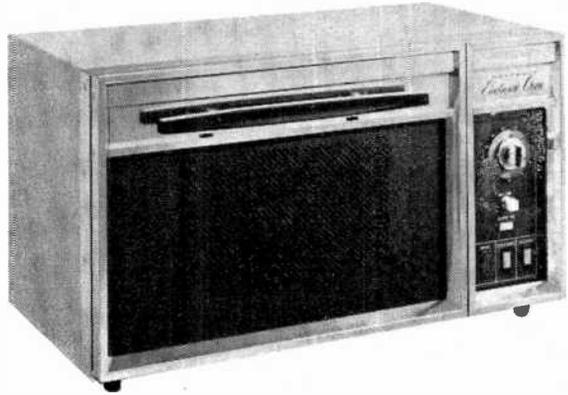
## New Heathkit Electronic Oven

...only \$399.95\*

Now, through the miracle of microwave energy, a cooking revolution that frees you from conventional kitchen drudgery forever!



Imagine a baked potato in 4 minutes; baked beans in a little over 6 minutes; a five-pound roast in 45 minutes. This is the miracle of microwave cooking. And now Heath brings you this modern miracle for the first time in money-saving, easy-to-assemble kit form. For busy families on the go, meal preparation is a matter of minutes. You can cook on china, glass, or even paper dishes since only the food becomes hot. Your cooking dish can be your serving dish. Frozen foods can be defrosted in minutes for quick spur-of-the-moment frozen meals cooked right in their own containers. And there is not the slightest cause for concern about the safety of your Heathkit electronic oven. Exclusive door design prevents microwave leakage from the oven cavity. And with a SAFETY INTERLOCK SYSTEM UNIQUE IN THE INDUSTRY, not only does the oven stop cooking if the door is opened, but the door can't be opened unless the interlock is operating properly. A second independent door interlock is also provided for maximum protection. And all interlock mechanisms are tamperproof. Assembled in accordance with the


manual, the GD-29 meets all the new federal standards for safety and radio interference. No special precautions are required when operating. The Heathkit electronic oven is as safe as your conventional oven! Quality components are used throughout: magnetron tube by Litton, the uncontested leader in the field; avalanche diode circuitry for longer tube life; simplified wiring harness with push-on quick-connectors for reliability and ease of assembly. GD-29 prototypes endured grueling "life-tests" equivalent to over 60 years of continuous service... further assurance of uncompromised reliability. Another feature is portability: the Heathkit electronic oven operates on regular household current. Plug it in anywhere... on a countertop, a wheeled cart, in the kitchen, on the patio, at the cottage... anyplace a grounded 120V AC power outlet is available. Make this a Christmas to remember by putting a Heathkit electronic oven under the tree. It's a gift your wife will thrill to... and a present the whole family will enjoy... meal after meal after meal.

Kit GD-29, 80 lbs. .... \$399.95\*


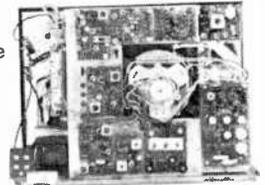
## New Heathkit portable solid-state color TV

- Big set performance, portable convenience
- MOSFET VHF tuner & 3-stage IF
- Modular, self-service design
- 102", 14 V picture tube




What do you do for an encore after you've created the solid-state GR-270 and GR-370 big-screen sets? Simple. Make them portable. That's virtually what's been done in the new Heathkit GR-169 solid-state portable color TV. Heath engineers took the same cool-running solid-state circuitry from the large screen chassis and packaged it in an easy-to-assemble compact chassis... with the same nine plug-in glass epoxy circuit board modules used in the big sets. In fact the only difference is the smaller preassembled horizontal deflection and high voltage power supply. The same MOSFET tuner and high gain 3-stage IF found in the big sets offer superlative color performance. And, as in the larger sets, complete owner-service features are provided by inclusion of built-in dot

generator and degaussing along with an exclusive volt-ohm check-out meter. 48-hour factory service facilities for modules are also provided with the GR-169. Other features include: built-in antennas and connections for external antennas; instant picture and sound; complete secondary controls available behind the hinged door on the front panel; high resolution circuitry for sharp, crisp pictures; adjustable noise limiting to keep external interference to a minimum. If you're looking for big set color fidelity and performance with portable convenience... put the new Heathkit GR-169 on your Christmas shopping list now!

Kit GR-169, 48 lbs. .... \$349.95\*


# New Heath-gift ideas... for

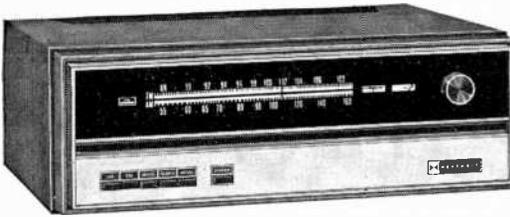
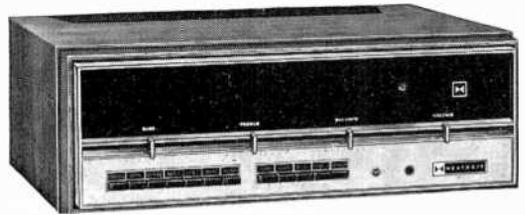
## New Heathkit® AJ-29 AM-FM-FM stereo tuner

This is the feature-packed tuner section of the famous Heathkit AR-29 stereo receiver . . . now available as a stereo "separate." The pre-assembled, factory-aligned FM tuner boasts 1.8 uV sensitivity for whopping station pulling power using FET design for superior overload characteristics. Three IC's in the IF section offer superior AM rejection, hard limiting, temperature stability, and outstanding reliability. Other features include a computer-designed 9-pole L-C filter for greater than 70 dB selectivity; new "blend" and "mute" functions; and a built-in AM rod antenna that swivels for best reception.

Kit AJ-29, 19 lbs., less cabinet . . . . . \$169.95\*  
Assembled AE-19, oiled pecan cab., 9 lbs. . . . . \$19.95\*



## New Heathkit® AA-29 100-watt stereo amplifier

Power-packed amplifier section of the Heathkit AR-29, the AA-29 stereo "separate" marks another milestone in superior Heathkit amplifier design. Its 70-watts of continuous power is more than enough to drive even the most inefficient speaker systems. A massive, fully-regulated and filtered power supply, 4 conservatively heat sunk output transistors and the best IM and harmonic distortion specifications in the industry add up to sound fidelity you never expected to hear outside the theater. Modular plug-in circuit boards make assembly easier . . . snap out in seconds for future servicing.


Kit AA-29, 27 lbs., less cabinet . . . . . \$149.95\*  
Assembled AE-19, oiled pecan cab., 9 lbs. . . . . \$19.95\*



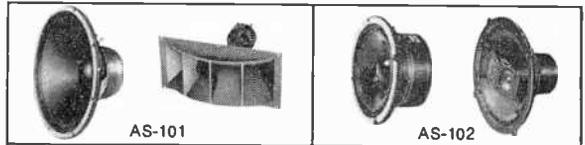
## New Heathkit® floor model speaker systems

In the new Heathkit AS-101 and AS-102 speaker systems, Heath engineers have combined the best of both worlds of sound and beauty. The AS-101 Heath/Altec-Lansing 2-way system features a 15" woofer and sectoral horn delivering from 35 to 22,000 Hz with uncompromising accuracy. The AS-102 Heath/Bozak 3-way system uses a 12" woofer, 6" mid-range, and two 2½" tweeters in an infinite baffle design to produce clean natural reproduction from 40 to 20,000 Hz. Both systems are housed in assembled Mediterranean pecan cabinets, 29½" H x 27¾" W x 19½" D.

Kit AS-101, 53 lbs. . . . . \$259.95\*  
Kit AS-102, 39 lbs. . . . . \$259.95\*



## New Heath stereo equipment credenza

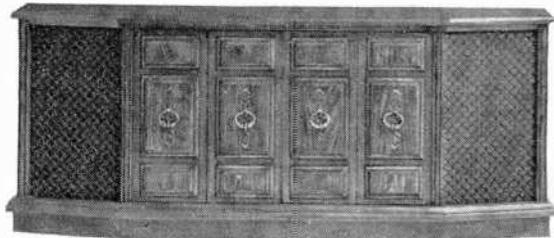

Romantic Mediterranean styling in wife-pleasing one-piece console design . . . yet with plenty of room for your favorite separate stereo components. Six-and-a-half feet of solid craftsmanship executed in North American Hickory veneers and solid oak trim, finished in oiled pecan. Completely assembled and finished, ready for installation of Heath or other components. Speaker enclosures

are ducted port reflex design, pre-cut for 12" speakers. An adjustable shelf has room for stereo receiver, cartridge or cassette tape player or separate tuner and amplifier. Below the shelf is room for your turntable and record storage. Accessory matching drawers on ball bearing slides are available for turntable and tape player.  
Model AE-101, 90 lbs. . . . . \$189.95\*

# home, shop and ham shack

## New Heathkit® IC 15 MHz frequency counter...199.95\*

A highly accurate, low cost frequency meter for anyone requiring accurate frequency measurements. Compare these features to counters selling for over twice this low price: accurate counting, 1 Hz to over 15 MHz; integrated circuitry; automatic trigger level for wide range input without adjustment; five digit readout with Hz/kHz ranges and overrange indicators for eight digit capability; high input impedance; storage circuitry for non-blinking, no-count-up readout; computer-type circuitry, no divider chain adjustment; temperature-compensated crystal time base oscillator; BNC input with cable; double-sided, plated-thru circuit board with sockets; three-wire, removable line cord; heavy-duty aluminum case handle/tilt stand and die cast zinc front panel; no special instruments required for accurate calibration.

Kit IB-101, 7 lbs. ....\$199.95\*



**IB-101 SPECIFICATIONS:** Frequency Range: 1 Hz to greater than 15 MHz. Accuracy:  $\pm 1$  count  $\pm$  time base stability. Gate Times: 1 millisecond or 1 second with automatic reset. Input Characteristics: Sensitivity: 1 Hz to 1 MHz, less than 100 mV rms. 1 MHz to 15 MHz, less than 250 mV rms. After 30 minutes warmup. Trigger Level: Automatic. Impedance: 1 Meg ohm shunted by less than 20 pf. Maximum Input: 200 V rms. DC-1 kHz. Derate at 48 V per frequency decade. TIME BASE: Frequency: 1 MHz, crystal controlled. Aging Rate: Less than 1 PPM/month after 30 days. Temperature: Less than  $\pm 2$  parts in  $10^7$ /degree C. 20 to 35 degrees C after 30 minutes warmup.  $\pm .002\%$  from 0 to 50 degrees C. GENERAL: Readout: 5 digits plus overrange. Temperature Range: Storage: -55 to 80 degrees C. Operating: 0 to 50 degrees C. Power Requirements: 105-125 or 210-250 VAC, 50/60 Hz, 8 watts. Cabinet Dimensions: 8 7/8" W x 3 1/4" H x 9" D not including handle. Net Weight: 4 1/2 lbs.

See these and 300 other  
Heath-gift suggestions at one of the  
following Heathkit Electronic Centers:

Anaheim, Calif. 92805  
330 E. Ball Road

Boston Area  
Wellesley, Mass. 02181  
165 Worcester St.

Chicago, Illinois 60645  
3462-66 W. Devon Ave.

Chicago Area  
Downers Grove, Ill. 60515  
224 Ogden Avenue

Cleveland, Ohio 44129  
5444 Pearl Road

Dallas, Texas 75201  
2715 Ross Avenue

Denver, Colorado 80212  
5940 W. 38th Ave.

Detroit, Michigan 48219  
18645 W. 8 Mile Road

Fair Lawn, N. J. 07410  
35-07 Broadway (Rt. 4)

Houston, Texas 77027  
3705 Westheimer

Los Angeles, Calif. 90007  
2309 S. Flower St.

Milwaukee, Wisc. 53216  
5215 W. Fond du Lac

Minneapolis Area  
Hopkins, Minn. 55343  
101 Shady Oak Road

New York, N.Y. 10036  
35 W. 45th Street

Philadelphia, Pa. 19149  
6318 Roosevelt Blvd.

Pittsburgh, Pa. 15235  
3482 William Penn Highway

St. Louis, Mo. 63123  
9296 Gravois Ave.

San Diego Area  
La Mesa, Calif. 92041  
8363 Center Drive

San Francisco Area  
Redwood City, Calif. 94063  
2001 Middlefield Road

Seattle, Wash. 98121  
2221 Third Avenue

Washington, D. C. Area  
Rockville, Md. 20852  
5542 Nicholson Lane

All Heathkit Electronic Centers are units of Schlumberger Products Corporation.  
Heathkit Electronic Center Prices Slightly Higher.

During 1971, consult Heathkit Catalog Supplements and local newspapers for announcements of new Heathkit Electronic Centers opening in these places:


Long Island Area  
Westbury, New York  
Miami, Florida

San Francisco Area  
El Cerrito, California  
Cincinnati, Ohio

Los Angeles Area  
Woodland Hills, California  
Atlanta, Georgia

Prices listed are factory mail order.  
Retail prices are slightly higher.

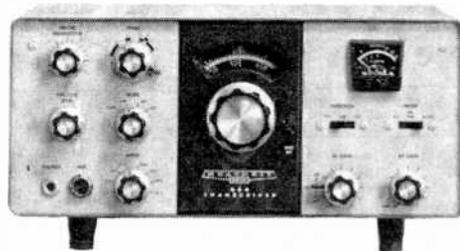... or send for your FREE  
factory mail order catalog



## New Heathkit® HW-101 SSB transceiver

The Hams at Heath have done it again... with an updated version of the Heathkit HW-100, one of the most popular pieces of ham gear on the market! The HW-101 features improved receiver circuitry resulting in better than 0.35 uV sensitivity for 10 dB S+N/N. Image and IF rejection are better than 50 dB. Other improvements are a new 36-to-1 ball-bearing dial drive; new selectable SSB or CW filters and attractive new front-panel styling.

Kit HW-101, 23 lbs. ....\$249.95\*

## New Heathkit wattmeter/SWR bridge



Two switch-selected ranges allow measurement of RF output from 10-200 W and 100-2000 W. Built-in calibrator permits 10% accuracy throughout the 80-10 M ham bands.

Kit HM-102, 3 lbs. ....\$29.95\*



HEATH COMPANY, Dept. 10-11  
Benton Harbor, Michigan 49022

a Schlumberger Company

Enclosed is \$\_\_\_\_\_ plus shipping.

Please send model (s) \_\_\_\_\_

Please send FREE Heathkit Catalog.  Please send Credit Application.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_


State \_\_\_\_\_

Zip \_\_\_\_\_

\*Mail order prices; F.O.B. factory.  
Prices & specifications subject to change without notice. CL-394R

CIRCLE NO. 16 ON READER SERVICE PAGE

## NEW Jensen

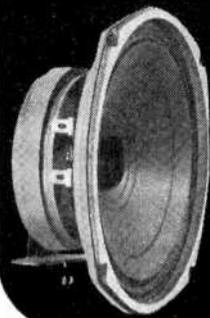

### GENERAL PURPOSE SPEAKER CATALOG

The newest, largest selection of General Purpose, Musical Instrument and Special Application speakers. Anywhere!

Send for your **FREE** copy today!

Send also  Hi-Fi Catalog  
 Commercial Sound Catalog

Jensen Manufacturing Division, The Muter Company  
5655 West 73rd Street • Chicago, Illinois 60638

Name \_\_\_\_\_


Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE NO. 17 ON READER SERVICE PAGE

## SYDMUR

The Last Word in "CD" Ignition Systems

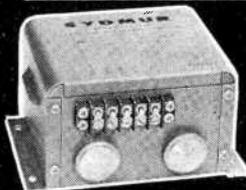

**SAVE MONEY**  
on GAS! COILS!  
SPARK PLUGS!  
TUNE-UPS!

New heavy duty solid state "CD" ignition systems available. Take advantage of the latest technology... get the most out of your car's engine.

- Increased mileage
- Greatly extended spark plug life
- Fast cold weather starting
- Fewer tune ups

Well built, conservatively rated components. Every Sydmur part is pre-tested and guaranteed. The easy to install Sydmur is fully adaptable; 6 or 12 volt systems, positive or negative ground.

Fly-away assembled .....	\$60.00	prepaid
Fly-away kit .....	44.50	prepaid
Compac assembled .....	\$34.75	plus \$1.00 handling
Compac kit .....	24.95	plus \$1.00 handling

Or Build Your Own—Free Instructions!!

Power Transformer plus detailed instructions  
SPC-4 (6 and 12 volt) ..... \$14.95

As described in June 1965 Popular Electronics (New York State residents add sales tax) Recommended by many of the world's leading automotive manufacturers. Send check or money order today.

For free literature and parts list write:

**SYDMUR ELECTRONIC SPECIALTIES**

1268 East 12th Street Brooklyn, NY 11230

CIRCLE NO. 29 ON READER SERVICE PAGE

## SOLID STATE

(Continued from page 87)

the receiver has a typical turn-on threshold of 1.25 volts and a turn-off of 1.00 volts. Thus, a 250-mV hysteresis is provided to prevent possible oscillation from noise occurring during the rise and fall times of a slow input waveform.

Although MODEM circuits are used primarily in data transmission systems, the versatile characteristics of these new Motorola devices could be of real value to all serious experimenters working with digital projects.

A series of six new high-voltage npn transistors is being offered in plastic packages by Fairchild Semiconductor (313 Fairchild Drive, Mountain View, CA 94040). Featuring excellent beta linearity from 1.0 mA to 50 mA, these new units are registered as types 2N5964-65 and 2N5830-33. The first two are supplied in 700 mW dissipation TO-105 packages, the latter four in 310 mW TO-106 packages. All six are complements to the 2N4888-89 pnp types.

Both the input capacitances and the leakage currents of Fairchild's new devices are quite low—only 4 pF maximum capacitance, while leakages are but 10 nA for the 2N5833 and 50 nA for the others in the series. The 2N5833 and 2N5965 operate with an  $V_{CE0}$  of 180 volts while their companion units range in sustaining voltage from 100 to 150 volts.

The TRW Semiconductor Division (14520 Aviation Blvd., Lawndale, CA 90260) has recently announced a number of new high-frequency transistors, including the 2N5773-76 series, the PT6738, and the PT6729. Of these, the 2N5773-76 series is a family of four broadband transistors for use in the 200- to 500-MHz range; power output levels range from 1.5 watts for the 2N5773 to 40 watts for the 2N5776.

A new SSB transistor furnishing 30 watts PEP across the 1.5-to-18-MHz band, the PT6738 has a power gain of 13 dB, with its intermodulation distortion guaranteed at -30 dB or better. Designed for operation on a 28-volt dc source, the unit is packaged in a TO-59 case.

The type PT6729 is claimed to be industry's most powerful 150-MHz communications transistor. Delivering 120 watts r-f power output with 6 dB gain when operated on a 28-volt dc power supply, this new device is packaged in a 4-lead diamond configuration case.

That concludes our Solid State story for November... until next month and the Holiday Season, keep cool.

—Lou

POPULAR ELECTRONICS

## INTERFACE

(Continued from page 10)

serious beginner with a limited budget.

C. JAROSZ  
Baltimore, Md.

Congratulations on your "New Look." The upgrading is a welcome change and seems to signal increased confidence on your part in your readership.

R. BUNGER  
Los Angeles, Ca.

It must have been coincidence that I picked up your "New Look" September issue and found it so interesting. Probably very few of your readers were aware of Olson's live orchestra/filter test and I was particularly happy to have this historical fill-in. The article on building small audio transformers was a bonus. However, the greatest satisfaction was the return of Gordon Holt to print. He and I had mutual friends in the 1950's and I found him very honest and fair.

I would be happy to swap information on disc recording which is a hobby of mine and not a profession.

A. R. JOURDAN  
Meriden, Conn.



Whether they liked it or not, the Editors appreciated the time that several hundred readers took to write us about the "New Look." Some readers sorely missed the old monthly departments, but most were willing to wait and see what POPULAR ELECTRONICS looked like in the months to come. The majority of letters and postcards (and telephone calls) were in favor of the changes and improvements.



Boy, I sure hope they bring some more of these on their next trip up here!

November, 1970

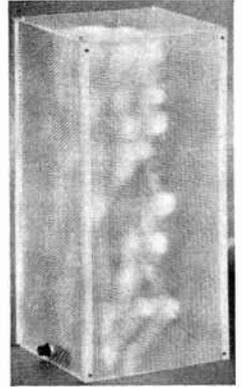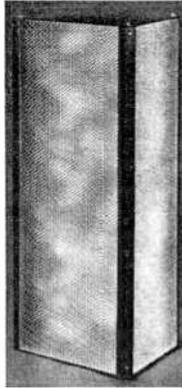M-25 \$19.95 **COLOR ORGAN KITS** M-27 \$24.95



Two channel, perform with brilliant ever-changing colored light patterns, which rise & fall with the tone & intensity of the music: used with AM-FM radio, tape decks, Stereo, musical instruments, etc.

M-25 HEIGHT 24"  
WIDTH 12" ALL SIDES  
TWO DIFFERENT  
PRISM PLATES  
FOR 3D EFFECT  
4 SQUARE FEET  
OF VIEWING  
SURFACE

M-27 HEIGHT 24"  
WIDTH 12" ALL SIDES  
FOUR DIFFERENT  
PRISM PLATES  
TOP & BOTTOM ARE  
PRISM PLATES  
MAY BE PLACED ON SIDE  
10 SQUARE FEET  
OF SURFACE

Usually Sold in Pairs—Send Check or Money Order to

**ELECTRONIC LIGHT CO.**

BOX 413 LAGUNA BEACH, CA. 92652  
CIRCLE NO. 12 ON READER SERVICE PAGE

CAN YOU QUALIFY  
*income*  
FOR MORE RESPONSIBILITY  
AS A **CIRCUIT DESIGNER?**



If you have a degree in engineering or formal training in electronics and work in the electronics industry, the Center for Technical Development's DIGITAL DESIGN PROGRAM (DDP-1) can make you more valuable as a trained circuit designer. DDP-1 is a new concept in practical home study courses designed to give you useable know-how fast. YOU CAN'T AFFORD TO WAIT ANOTHER DAY . . . WRITE FOR FULL DETAILS NOW!

We'll also send you information on our IC Logic and Power Supply courses.

Write Director, Dept. PE-110

THE CENTER FOR TECHNICAL DEVELOPMENT, INC.  
517 East Main Street • Louisville, Ohio 44641

CIRCLE NO. 35 ON READER SERVICE PAGE

95



# FREE!

## Lafayette's 1971 Golden Jubilee Catalog



Your 1st Guide To  
Everything in Electronics

- Stereo/Hi-Fi Components
  - Musical Instruments and Amplifiers
  - Photography Equipment
  - Ham and CB Gear
  - Public Address Systems
  - Tools and Test Equipment
  - Educational and Optical Equipment
  - Black and White/Color Televisions
  - Police and Fire Monitor Receivers
  - Books and Parts
- Plus Thousands of Additional Items

Lafayette Radio Electronics Dept. 35110  
P. O. Box 10, Syosset, L. I., N. Y. 11791

Send Me the Free Lafayette Golden Jubilee 1971 Catalog 710 35110

Name .....

Address .....

City .....

State ..... Zip .....


(Please include your zip code)

CIRCLE NO. 18 ON READER SERVICE PAGE



# avanti

EVERYTHING IS COMING UP ASTRO PLANES

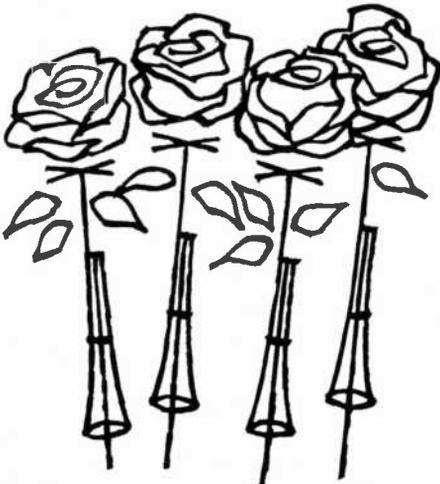

33-35 WEST FULLERTON AVENUE,  
ADDISON, ILLINOIS 60101

AVANTI RESEARCH & DEVELOPMENT, INC.  
THE PACESETTER IN HIGH PERFORMANCE ANTENNAS

CIRCLE NO. 2 ON READER SERVICE PAGE

## MEASUREMENTS LAB

(Continued from page 63)

units be assembled on printed circuit boards. If you want to make your own boards, you can do so with the aid of the etching guides given in Fig. 7.

Mount the components on their respective circuit boards (see Fig. 8), paying careful attention to the orientations of the IC's, transistors, diodes, and electrolytic capacitors. When you finish soldering, examine the foil sides of the boards, comparing them against the guides in Fig. 7, to determine if any solder bridges exist between the closely spaced foil conductors. If you locate a solder bridge, re-heat the connection adjacent to it and remove the excess solder.

Now, referring to Fig. 9, wire up range selector switch *S1*, and make all necessary connections between *S1*, the two circuit boards, and the 15-contact plug. (Note: Make absolutely certain that the wiring to the plug conforms with the wiring to the socket in the main frame. Use stranded hookup wire to and from the socket.) Then mount the circuit boards, TRIGGER LEVEL control, range switch, and input binding posts on the L bracket chassis as shown in Fig. 10. Before tightening the hex nut on *S1* (in the module) position it so that lugs 1 and 11 point upward; this way the index on the control knob will conform with the dial markings. Wire the TRIGGER LEVEL control and binding posts into the circuit. Then neatly lace together the wiring and put the control knobs on the shafts of the two controls.

**Testing the Counter Module.** Connect the plug on the module to the socket in the main frame and turn on the power by rotating the range switch to the 1000-Hz position. Rotate the DISPLAY RATE control on the main frame to its fully clockwise position and observe the readout display. With no input signal to the module, the readout tubes should reset to "0" as soon as the reset pulse occurs. Now, apply an input signal of 0.1 volt or more to the binding post input on the module and again observe the readout display. After a discrete interval, determined by the setting of the DISPLAY RATE control, the readout system

## THEORY OF COUNTER DESIGN

The 20-MHz Frequency Counter Module is divided into two basic sections—the Time Base circuit shown in Fig. 5, and the Scaler circuit in Fig. 6. The Time Base circuit employs a high-impedance source-follower FET input stage (*Q1*) to minimize loading the circuit under test. The signal, fed first through *Q1*, is direct-coupled to *Q2* where it is amplified to a level sufficient to drive the *Q3-Q4* Schmitt trigger. The driving signal level to the *Q3-Q4* circuit is primarily a function of the TRIGGER LEVEL control *R3*.

The purpose of the Schmitt trigger is to condition the signal, giving it fast rise and fall times. This is necessary to prevent false counts on low-frequency signals. Although the TTL gates and flip-flops in *IC1*, *IC2*, and *IC4* will operate at almost any frequency, the gates can produce multiple counts if the signal passes through the trigger point too slowly. The Schmitt trigger, as a result of shaping the signal, eliminates the possibility of multiple counts.

Every time the input signal at the base of *Q3* fires the Schmitt trigger, the output at the collector of *Q4* changes state, producing a series of square waves. After this, the square-wave pulses are amplified by *Q5* and fed to the sync circuits.

To obtain a readout in Hertz, the signal must be gated into the counter for a specific period of time. This is accomplished with the time base made up of *IC3* and half of *IC4*. The time base network is a divide-by-six circuit that counts down from the 60-Hz power frequency (applied at point R and obtained from one side of the 12.6-volt secondary winding in the power supply) to provide at point B a series of pulses that occur every 0.1 second. Diode *D1* clips the negative alternations of the 6.3-volt input, and capacitor *C3* filters out any high-frequency noise that might be present on the ac line.

The output at point B can be directly coupled into the sync circuit at point C to provide a single counting range of 1000 Hz. Or, it can be coupled through the Scaler subassembly (see Fig. 6) through *S1* for further divisions to provide the 10-kHz, 100-kHz, 1-MHz, and 10-MHz ranges. The signal can now be applied to point C in the sync circuit.

In the sync circuit, the input and timing signals are synchronized in such a manner that the count always starts at the same point in the input cycle to avoid any "one count" ambiguities in the reading. The "one and only one" circuit formed by *IC1*, when armed with a pulse, allows only one timing cycle to occur.

The display time setting of *R20* determines the firing rate of unijunction transistor *Q6*. When *Q6* fires, a sharp pulse appears across *R13*. After amplification through *Q7*, this pulse is applied to the S input of the R-S flip-flop in *IC1*, causing the Q output to go to "high". The high signal is next applied to the J input of the JK flip-flop in *IC1*, setting the flip-flop to change state with the next clock pulse from the time base network.

The first clock pulse that occurs after the display time circuit is fired switches the JK flip-flop. The Q output goes to high and is fed into the K input of the same flip-flop. This will result in the flip-flop going back to its original state on next clock pulse. The not  $\bar{Q}$  output goes to low (0 volt) on the first clock pulse, since it is the Q output's complement, and resets the S-R flip-flop and sets the sync switch of *IC4* to switch with the next clock pulse. The clocking pulse in this case is the input signal.

Now, the following occurs: On the first negative-going pulse that occurs in the input signal, *IC4* switches so that the Q output goes to low and opens the gate in *IC2* for signals to pass into the counter. The negative-going pulse that switched the flip-flop is inverted before being applied to the gate so that it becomes a positive-going pulse that does not pass through the gate to the counter.

The first count occurs on the next negative pulse of the input signal. When the "one and only one" circuit receives the second clock pulse from the time base, it switches back to its standby state to await another display generator pulse. This causes the sync switch to close on the first negative-going input pulse that occurs after the inputs change state. The leading edge of the pulse that opens the synchronizing circuit is applied to the inverter through *C5* to the reset buss in the counter, resetting the counter just before the next pulse train to be counted is applied to point A.

## FREE McIntosh CATALOG and FM DIRECTORY

Get all the newest and latest information on the new McIntosh Solid State equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.



**MX 114**

FM/FM STEREO TUNER  
and STEREO PREAMPLIFIER

### SEND TODAY!

McIntosh Laboratory Inc.  
2 Chambers St., Dept. PT-1170  
Binghamton, N.Y. 13903

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

CIRCLE NO. 24 ON READER SERVICE PAGE

**Olson**  
ELECTRONICS

**FREE**  
Catalog

Fill in coupon for a FREE One Year Subscription to OLSON ELECTRONICS' Fantastic Value Packed Catalog — Unheard of LOW, LOW PRICES on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, and other Values. Credit plan available.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_  
GIVE ZIP CODE \_\_\_\_\_

If you have a friend interested in electronics send his name and address for a FREE subscription also.

**OLSON ELECTRONICS**

DEPT. IK, 260 S. FORGE STREET, AKRON, OHIO 44308

CIRCLE NO. 26 ON READER SERVICE PAGE

**DISCOVER HIDDEN TREASURE**  
WITH A JETCO ELECTRONIC METAL DETECTOR



A powerfully sensitive instrument — detects gold, silver, coins, relics, etc. Fully tested — transistorized — guaranteed.

Send for Free Catalog

**\$29.95**  
up

JETCO, P.O. Box 132 PEM, Huntsville, Texas 77340

**1¢ SALE**  
GUARANTEED  
10 YEARS



The knife for hunting, fishing and all around use. Mirror polished, imported stainless steel blade honed to a razor's edge. Rugged. Opens with flick of finger. Locks into position. Blade will not close when in use. Press button in handle to close. Safety finger guard. Sure-grip handle. Balanced for target throwing. **IF BROKEN WITHIN 10 YEARS WE WILL REPLACE AT NO CHARGE!** Use 30 days. Money back if not pleased. Special 1¢ Sale. REG. PRICE \$1.98. Send \$1.99 & receive 2 knives. Add 49¢ postage, handling. **Limit TOTAL \$2.48 for 2 knives.** ORDER NOW! Midwest Knife Co., 9043 S. Western Ave., Dept. LDD-2, Chicago, Ill. 60620. Est. 1936.

GET INTO **ELECTRONICS**

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar, automation. Basic & advanced courses. Electronic Engineering Technology and Electronic Technology curricula both available. Associate degree in 29 months. B.S. curricula. C.I. approved. Start September, February, Dorms. campus. High school graduate or equivalent. Catalog.

**VALPARAISO TECHNICAL INSTITUTE**  
DEPARTMENT PE, VALPARAISO, INDIANA 46383



should display the frequency of the applied signal. Let the instrument reset itself several times and if the numerical indication remains the same for two of the three significant figures, this range is operating properly.

Test each of the remaining ranges individually as described, using an appropriate frequency signal to produce a readout display. Then, on any of the ranges, feed in a signal that exceeds the range capability by more than 100 percent and check to see that the over-range indicator lamp glows.

Finally, set the range switch to the TEST position and observe the readout display. You should obtain a 60-Hz reading every time the instrument automatically resets itself. If everything checks out, you can start using your frequency counter on the job. **—50—**

## OPTICOM

(Continued from page 50)

the active elements at each other. Turn on the transmitter and measure the voltage across *R11*. Adjust *R9* until this voltage is  $\frac{1}{2}$  volt. With both units operating, depress the transmitter pushbutton *S1* and move the receiver slightly until a loud tone is heard in the earphone. If no tone is heard, test the receiver by aiming it at a 117-volt 60-Hz light. If the receiver is operating properly, you should hear a distinct 60- or 120-Hz hum. If you do not, troubleshoot the receiver. Once it is working, and you still get no signal from the transmitter, troubleshoot it.

With both units working, mount the lenses using a commercially available sealant. Mount them on the inside of the chassis so that they cover the holes and their centers are in line with the light-sensitive semiconductor elements on the PC boards.

**Optical Alignment.** Hold each unit in the beam path of a relatively distant light source. DON'T use the sun for this step—a common light bulb about 10 feet away will do. Align the chassis so that the light falls on the window of the active optical element. Move the PC board back and forth until the light comes to a sharp focus on the element window. Once this position has been located, lock the mount-

ing screws; and, though it is not necessary, place a spot of cement on the screws to insure permanence. Once both units have been aligned optically, check that the batteries are firmly mounted and assemble the chassis covers.

**Range Testing.** Place the transmitter on a level mount and point it along a path unimpeded by obstacles for at least several hundred feet. With the Test pushbutton (S1) either depressed or temporarily shorted, walk about 10 or 15 feet away from the front of the transmitter carrying the receiver. Turn on the receiver and point it toward the transmitter, varying the aim until you hear the tone. You will notice the extreme directionality of the system. This is what makes it so private—you must be on the beam to get the signal. In daylight, the range will not be as great, but it can be improved by switching the receiver Day-Night switch (S2) to the Night position. If you find the tight beam too constraining, you can de-focus the receiver by moving the PC board slightly in toward the lens. One side effect of doing this is a reduction in range.

Of course, if two systems have been built for two-way communication, do not exceed the range of the worst pair.

**Operation.** If you are using a pair of communicators as a network, the transmitter at one end should be aimed at the receiver of the other end and the transmitter Test button pushed to tone-modulate the transmitter. Both ends should be positioned until the tone at each end is heard loud and clear. Once the link has been established, the pushbutton is released and the microphone is used for speech communication. Manipulation of the receiver Day-Night switch (S2) will affect the range and volume.

**Modifications.** There are numerous modifications and variations that can be used with the Opticom. Telescopes or binoculars at either, or both, ends greatly increase the range. Even low-cost plastic Fresnel lenses may be used. Since the light collecting area of a circular lens is proportional to the square of the diameter, a small increase in diameter results in a significant increase in the effective area. For example, a lens three inches in diameter has more than twice the light collecting area of a two-inch lens.

Since a diverging beam of light follows an inverse square law and produces a light energy density dependent on the square of the distance from the light source, doubling the lens light area will, in theory, double the range of the Opticom. Of course, operation in daylight or over paths having varied thermal conditions will limit the range. Longest ranges can be obtained on clear, cool nights, with a telescope at each end.

The Opticom system may also be used as a short-distance rangefinder. Mount a bicycle reflector on the target and aim the tone-modulated transmitter at it. From a short distance away from the transmitter, aim the receiver at the reflector until the transmitter tone can be heard. The transmitter, target and receiver should form a triangle. Once the tone has been heard, simple geometry can be used to solve the triangle and calculate the distance.

Daylight range can be improved if the interior of the receiver chassis is painted flat black. Also, a long focal plane lens can be used to narrow the field of view and reduce background illumination. This tightens the beam and makes more accurate alignment necessary. Also consider the use of a black interior tube or shield protruding from the lens to reduce ambient light to the phototransistor.

-50-

ADDED MOBILE POWER WHEN YOU NEED ADDITIONAL COVERAGE FOR CLEAR COMMUNICATIONS



170 WATT INPUT

Complete with remote power switch and indicator control panel plus mounting brackets.

FCC TYPE ACCEPTED  
Parts 89, 91, 93

\$129.95  
12 VDC

SMALL PACKAGED MOBILE POWER

## LINEAR R.F. POWER AMPLIFIER

Covers greater distances with increased transmit power. Can be used with SONAR BR20, FM40 or any similar FCC approved equipment with 1-15 watt output. Designed with top performance and dependable service when you need it. Automatic standby/transmit switching • Covers 25-50MHz range • transistorized power supply—negative ground • Used on amateur 28MHz for FM-AM-SSB. Small, compact, rugged design. Size: 2"H x 6"W x 3"D. Wt. 3 lbs. 12 VDC

SONAR RADIO CORP., 73 Wortman Avenue, Bklyn, N.Y. 11207  
Please send information on Model BR 2906 Linear Amplifier.

Dept. 110

Name   
Address   
City  State  Zip

CIRCLE NO. 28 ON READER SERVICE PAGE

# BUILD YOUR OWN LASER.

Ride into the future on a beam of coherent light! Our HeNe gas laser kits are lab-quality, easy to put together, and use in holography, interferometry, laser optics, communication, many others.

Metrologic Instrument, Inc.  
143 Harding Avenue, Bellmawr, N.J. 08030



Dear laser-makers,  
The whole idea of a light that turns me on is fascinating. And I'd like to get started on building my own. Please send me the things I've checked below.

### Basic Laser-Building Equipment

- Complete laser kit contains laser tube, power supply and housing ..... \$79.50
- 60-203 Transceiver Kit.\* Use your laser for communications. Transmit-receive ..... \$74.25
- 60-708 Laser Optics Experiment Kit.\* Lenses, prisms, mirrors, diffraction gratings, polarizers, beam splitters, interferometer, lab manual ..... \$40.00
- 60-625 Laser Holograph Kit.\* Contains all critical optics, film, and chemicals ..... \$34.75  
Laser not included.
- Information only. Complete catalog and prices.
- Please enclose check or money order for the total amount.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE NO. 20 ON READER SERVICE PAGE

## MISSILE BATTERY

THE ONLY LIFETIME BATTERY

**SURPLUS—NI-CAD PLASTIC SINTERED-PLATE BATTERY CELLS AT APPROX. 10% OF GOVERNMENT COST**



Connect these 1.2 V. cells in series to make batteries of any voltage. (Example: 10 cells = 12 V. Batt.), or size to replace storage batteries on autos, motorcycles, boats, radio, etc. All the good characteristics not possessed by lead-acid and other alkaline batteries such as: Lifetime service, lighter wgt., constant voltage, high discharge rate (approx. 10 times AH cap.), operate at 100% cap. in temp. range -65° to +165°F., not harmed by storage, discharge, overcharge, or freezing. May be charged thousands of times with the only maintenance of adding distilled water and keeping clean. Select cell sizes to fit your application below.

ESSE TYPE	AMP HR	DIMENSIONS INCHES			WGT. OZ.	COST
		HIGH	WIDTH	DEEP		
AH4	4	6	2	1/2	6	1.49
AH4	4	6	2	1/2	6	2.95 New
AH6S	6	4	2-1/2	1 1/8	8	1.79
AH6	6	4-5/8	2-5/8	3/4	8	1.79
AH6R	6	4-1/2	2-5/8	1 1/8	8	2.95 New
AH10	10	4-3/4	2-3/4	1-1/8	16	2.29
AH10	10	4-3/4	2-3/4	1-1/8	16	4.95 New
AH12	12	5-3/4	2-1/8	1-1/8	18	2.79
AH34	34	9-1/4	3-1/2	1-3/8	52	4.95
AH60	60	11-1/4	5	1-3/8	104	5.95

### SPECIAL CLOSE OUT!

Metal cased Ni-Cad cells, ideal for motor starting.  
30AHM—30 AH, 8-7/8 x 3 x 1-1/4, Wgt. 3-1/2 lbs. .... \$2.00  
52AHM—52AH, 9 x 3 x 1-1/2, Wgt. 4-1/2 lbs. .... \$3.50

Send for complete list including made-up batteries. All cells guaranteed for satisfaction or money back. All cells not marked new are used but serviceable. Include postage on parcel post shipments.

## ESSE RADIO COMPANY

Dept. PE-11 368 S. Meridian St.  
Indianapolis, Ind. 46225

CIRCLE NO. 13 ON READER SERVICE PAGE

## STEREO SCENE

(Continued from page 71)

as symphonic music, with a high degree of "sharing" between channels and a lot of random-phase content may confuse the decoder for I had the impression that the stereo localization of instruments between the front speakers was rather less definite from the Scheiber playback than from the original tape, and that the rear ambience, although definitely coming from behind, lacked some of the spaciousness of the four-channel original. If there are indeed some weaknesses in the Scheiber system, only time will tell whether they are inherent or can be "worked out."

As for compatibility, it is evident from Fig. 4 that the modulation axes for the rear-left and rear-right signals are not far removed from the vertical axis, which means those signals would virtually disappear in monophonic playback. A two-channel reproduction would place them out of phase at both side speakers, but because each axis is displaced from the vertical toward one side channel, its sound would be reproduced toward one side or the other, and the misphasing would not be conspicuous. More serious, though, is the loss of effective left-right separation, which would be reduced to a maximum of 75% (only 8 dB).

The cost to the consumer of a Scheiber decoder is something that seems rather indefinite at the moment. A spokesman for Advent Corporation, which is licensed to convert the basic Scheiber system into "marketable consumer products," said that the decoder could be "very inexpensive or quite costly," depending on its effectiveness! The intimation was that several versions would be made available; and, as far as performance was concerned, the buyer would get what he paid for. It seems reasonable to assume that the demonstration was conducted with the best version that could then be made and that cheaper versions would exhibit more or less the characteristics of a Hafler playback.

In view of the similarity between the two systems, it will be interesting to see how mutually compatible they are. Will a Scheiber-encoded recording play back on a Hafler "decoder" and vice versa, with the apparent sound sources appearing midway between the speakers? Could a Scheiber control amplifier allow the Hafler system to produce single-source ping-pong effects? I will have some of the answers at a later date.

—30—

# Let your uncle send you through school.

Thousands of young men today are getting top-notch training in rewarding career fields.

And they have an uncle footing the bill.

The Army is giving these young men a valuable education in work ranging from aircraft maintenance to radar to communications because it needs skilled soldiers.

If you're a high school graduate who qualifies, you can have your choice of hundreds of job-training courses with your selection guaranteed in writing before you enlist.

If you're not a high school graduate, you can earn a high school equivalency certificate while you're in the Army which will qualify you for further education at the Army's expense.

Find out more. Talk to an Army Recruiter.

Use the coupon or write to Army Opportunities, Department 200A, Hampton, Virginia 23369.

See what your uncle can do for a nephew.

Your future, your decision. Choose ARMY.



Army Opportunities Date \_\_\_\_\_  
Dept. 200, Hampton, Va. 23369

I'd like to know more about my educational opportunities in the Army. Please send me your free book.

Name \_\_\_\_\_ Date of Birth \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ County \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_ Phone \_\_\_\_\_

Education \_\_\_\_\_

2PE 11-70

# NEW Short-Wave Listening VERTICAL ANTENNA Model SWV-7

For 11,13,16,19,25,31 and 49 meter bands Cramped quarters keeping you from installing an SWL antenna? Your problem is solved! Model SWV-7 mounts easily on the roof or on the ground and stands just 13 ft., 3-5/8 in. tall.

Extensive field testing confirms that this antenna measures up to Mosley's high standards of performance. Construction is of the finest material to bring you years of trouble free listening pleasure. Complete with installation instructions.

Get the facts from your Mosley dealer, or write factory direct, for detailed brochure.

Dept. 202  
**Mosley Electronics, Inc.**

4610 N. LINDBERGH BLVD., BRIDGETON, MD. 63044



## COMMUNICATIONS

(Continued from page 81)

to take a hard, second look at its windshield radio antenna. Technically a fine-wire dipole imbedded in the windshield glass, the new antenna apparently has all of the advantages and drawbacks to be expected from an FM dipole—no gain and directionality. Although motorists acknowledge that the imbedded antenna curbs vandalism, both AM and FM reception are significantly deteriorated and broadcasters claim that the imbedded dipole cuts the FM reception area by two thirds! Some motorists claim that reception is worse during rain and snow storms whenever it becomes necessary to use the wipers; they say that signals bounce up and down in strength following the motion of the wipers.

### AMATEUR RADIO

**'Tain't Necessarily So**—Contrary to a notice in a summer ARRL Director's Letter, the FCC has not altered its amateur radio Rules and Regulations—nor is there a disagreement between Chairman Burch and the FCC staff. With a little double-checking, interested parties would have discovered that someone is crying "wolf." Obviously, the FCC could not condone the "student takeover" or the solicitation of funds during spring upheavals at various universities. Nor could it grant ham licenses to fraternal organizations for the purposes of establishing communications networks. Both actions violate Part 95.39 of the Rules. There is no reason to suspect that the FCC was "clamping down" on voluntary communications for events such as parades, sports car rallies, the Eye Bank Network, and so forth.

CIRCLE NO. 21 ON READER SERVICE PAGE

Hey!

Hams, Engineers, Hobbyists

# MARK LIKE

# MAGIC



Any surface \*  
can be marked with  
**DATAK'S**  
**DRY TRANSFER**  
titles and symbols.

The results are  
professional,  
it looks like the  
finest printing!



Write for your **FREE**  
**SAMPLE** and Catalog,  
listing hundreds of  
letter sheets and  
symbol sets.

Order from your distributor or directly from:

**THE DATAK CORPORATION**

\* From #K-64 1/4" letters and numerals... \$1.50  
Also available #9581 professional title set for electronic equipment... \$5.95

85 Highland Ave. / Passaic, New Jersey 07055

CIRCLE NO. 8 ON READER SERVICE PAGE

## OUT OF TUNE

"An Improved Four-Way Flasher" (August 1970). In the diagram on page 80 the unit specified for the flasher is a Tung-Sol type 535. This is a 3-terminal, 6-volt unit which will not work in this circuit. Instead, use Tung-Sol type 552, a heavy-duty 12-volt, two-terminal flasher.

# ELECTRONICS MARKET PLACE

**COMMERCIAL RATE:** For firms or individuals offering commercial products or services. \$1.25 per word (including name and address). Minimum order \$12.50. Payment must accompany copy except when ads are placed by accredited advertising agencies. Frequency discount: 5% for 6 months; 10% for 12 months paid in advance. **READER RATE:** For individuals with a personal item to buy or sell. 80c per word (including name and address). No Minimum! Payment must accompany copy.

## FOR SALE

**FREE!** Giant bargain catalog on transistors, diodes, rectifiers, SCR's, zeners, parts. Poly Paks, P.O. Box 942, Lynnfield, Mass. 09140.

**GOVERNMENT** Surplus Receivers, Transmitters, Snooperscopes, Radios, Parts, Picture Catalog 25¢. Meshna, Nahant, Mass. 01908.

**ROCKETS:** Ideal for miniature transmitter tests. New illustrated catalog. 25¢. Single and multistage kits, cones, engines, launchers, trackers, rocket aerial cameras, technical information. Fast service. Estes Industries, Dept. 18-L, Penrose, Colorado 81240.

**LOWEST Prices** Electronic Parts. Confidential Catalog Free. **KNAPP**, 3174 8th Ave. S.W., Largo, Fla. 33540.

**EUROPEAN** and Japanese bargains catalogs. \$1 each. Dee, 10639E Riverside, North Hollywood, Calif. 91602.

**WE SELL CONSTRUCTION PLANS.** TELEPHONE: Answering Machine, Speakerphone, Carphone, Phonevision, Legal Connector, Auto Dialer, Central Dial System. TELEVISION: \$35.00 Color Converter, Tape Recorder, 3DTV. \$25.00 Camera. DETECTIVE: Infinity Transmitter, Tail Transmitter, Police Radar Detector. HOBBYIST: Electron Microscope, 96 Hour Tape Music System, Ultrasonic Dishwasher, Radar-Oven, Electronic Tranquilizer. Plans \$4.95 each. COURSES: Telephone Engineering \$39.50, Detective Electronics \$22.50, Anti-Detective Electronics \$27.50. **NEW SUPER HOBBY CATALOG AIRMAILED \$1.00.** Don Britton Enterprises, 6200 Wilshire Blvd., Los Angeles, Calif. 90048.

**WEBBER LAB'S.** Police & Fire Converters. Catalog 25¢. 72 Cottage Street, Lynn, Mass. 01905.

**INVESTIGATORS, LATEST ELECTRONICS AIDS. FREE LITERATURE.** CLIFTON, 11500-L NW 7th AVE., MIAMI, FLORIDA 33168.

**LINEAR AMPLIFIERS:** "Hawk"—25 watts output—\$59.95; "Hornet"—50 watts—\$98.50; "Raider"—100 watts—\$139.95; "Maverick-250"—250 watts—\$244.95; AM/SSB. "Scorpion" 50 watt 12 volt mobile—\$99.95; "Bandit II" 100 watt mobile—\$169.95. 20-35 megacycles. (Illegal Class D 11 Meters.) Dealer inquiries invited, D & A Manufacturing Co., 1217 Avenue C, Scottsbluff, Nebraska 69361.

**ELECTRONIC PARTS, semiconductors, kits. FREE FLYER.** Large catalog \$1.00 deposit. **BIGELOW ELECTRONICS**, Bluffton, Ohio 45817.

**RADIO—T.V. Tubes—33¢ each.** Send for free catalog. Cornell, 4213 University, San Diego, Calif. 92105.

**ULTRA-SENSITIVE AND POWERFUL METAL DETECTORS—**join the many who are finding buried coins, minerals, relics and artifacts. Don't buy till you see our **FREE** catalog of new models. Write Jetco, Box 132-PE, Huntsville, Texas 77340.

**LASER** parts catalog 60¢. Moynihan, 107 North Brighton, Atlantic City, New Jersey 08401.

**PSYCHEDELIC** catalog. Posters, lighting, etc. Send 50¢ for handling to Hole In The Wall, 6055PE Lankershim, North Hollywood, Calif. 91606.

**THE ART OF DE-BUGGING—\$5.95.** TRON-X PUBLICATIONS, P.O. BOX 38155, HOLLYWOOD, CALIFORNIA 90038.

**CONSTRUCTION PLANS: LASER . . . \$2.00.** Listening Devices—two F.M. Mike Transmitters . . . \$1.00. Tail Transmitter . . . \$1.00. Sound Telescope . . . \$2.00. Infinity Transmitter . . . \$2.00. Equipment and kits available. Howard, 20174 Ward, Detroit, Michigan 48235.

**CLEARANCE SALE** rectifiers, transistors, 1000's other items. Catalog 15¢. General Sales Company, 254 Main, Clute, Texas 77531.

**SEMICONDUCTORS** and parts catalogue free over 100 pages. J. & J. Electronics, Box 1437, Winnipeg, Manitoba, Canada. U.S. Trade directed.

**GENERAL INFORMATION:** First word in all ads set in bold caps at no extra charge. All copy subject to publisher's approval. Closing Date: 1st of the 2nd month preceding cover date (for example, March issue closes January 1st). Send order and remittance to: Hal Cymes, POPULAR ELECTRONICS, One Park Avenue, New York, New York 10016.

**MECHANICAL, ELECTRONIC** devices catalog 10¢. Greatest Values—Lowest Prices. Fertik's, 5249 "D", Philadelphia, Pa. 19120.

**MUSIC LOVERS, CONTINUOUS, UNINTERRUPTED BACKGROUND MUSIC FROM YOUR FM RADIO, USING NEW INEXPENSIVE ADAPTOR. FREE LITERATURE.** ELECTRONICS, 11500-Z NW 7th AVE., MIAMI, FLORIDA 33168.

**SPACE-AGE TV CAMERA KIT!** Terrific for Experimenters, Industry, Education. Solid-state. Only \$116.95! Starter kits: \$18.95 up. Plans 25¢ up. Catalog FREE. Phone: 402-987-3771. Write: **ATV RESEARCH**, 1301 Broadway, Dakota City, Nebr. 68731.

**BURGLAR ALARM SYSTEMS** and accessories. Controls, bells, sirens, hardware, etc. **OMNI-GUARD** radar intruder detection system, kit form or assembled. Write for free catalog. Microtech Associates, Inc., Box 10147, St. Petersburg, Florida 33733.

**PRINTED CIRCUITS.** Magazine projects and experimental. Free listing. Vico, Box 1590, Los Angeles, Calif. 90053.

**SCORE, B&K TEST EQUIPMENT UNBELIEVABLE PRICES. FREE CATALOG AND PRICE SHEET.** FORDHAM RADIO, 265 EAST 149TH STREET, BRONX, N.Y. 10451.

**AMATEUR SCIENTISTS,** Electronics Hobbyists, Experimenters, Students . . . Construction Plans—all complete, including drawings, schematics, parts lists with prices and sources . . . Radar—Build your own ultrasonic doppler radar. Detect motion of people, automobiles, even falling rain drops. Transistorized, uses 9 volt transistor battery—\$4.50 . . . Long-Range "Sound Telescope"—This amazing device can enable you to hear conversations, birds and animals, other sounds hundreds of feet away. Very directional. Transistorized, Uses 9V battery—\$3.70 . . . Robot Man—Moves hands and arms—\$3.50 . . . Or send 25¢ coin (no stamps) for complete catalog. Other items include Psychedelic strobes, light shows, lasers . . . 46 different projects. Technical Writers Group, Box 5994, State College Station, Raleigh, N.C. 27607.

**ANTI-GRAVITY, EXPERIMENT AND THEORY;** rushed—\$1.00. U.S. Inquiries. Intertech-7A3, Box 5373, Station-F, Ottawa, Canada.

**SWL'S, Ham's, CB'ers—Rotary QSL File CB-8.** MB Sales, 1917 Lowell, Chicago, Illinois 60639.

**RADIO CHASSIS'S NEW.** Postpaid with SCHEMATIC. AM/FM 10 TRANSISTOR \$5.20 each. AM 6 Transistor \$2.65 each. Information 15¢. Union Supply; Box 32; Niles, Illinois 60648.

**ELECTRONIC COMPONENTS—**Distributor prices, Free catalog. Box 2581. El Cajon, California 92021.

**STROBES,** color organs, the incredible Strobot. Electric Candles. Remote Switch, Touch Switch. All in KIT and ASSEMBLED forms. Send 25¢ for complete catalog. Teletronics, Box 1266, South Lake Tahoe, California 95705.

**CHEMICAL FORMULAS** and preparation instructions when possible. Send self-addressed stamped envelope and \$3.50 to Chemtronics, Box 1266, South Lake Tahoe, California 95705.

**JAPAN & HONG KONG DIRECTORY.** Electronics, all merchandise. World trade information. \$1.00 today. Ippano Kaisha Ltd., Box 6266. Spokane, Washington 99207.

**PLANS-PARTS-KITS** A wide range of the unusual for the experimenter, hobbyist and amateur scientist. Many psychedelic items; STROBES, color organs. **ELECTRIC CANDLES,** Touch Switches, **LIGHTNING GENERATORS.** Complete line of COMPONENTS. Air Mail Catalog 50¢. Teletronics, Box 1266, South Lake Tahoe, Calif. 95705.

**CITIZEN BAND Radios, SSB, AM, Swan CB, Amateur.** Accessories. Free Catalogue. Dealers send letterhead for factory prices. Call 714-894-7555. "Baggy's" Radio, 6391 Westminster Avenue, Westminster, Calif. 92683.

**CAPACITORS** 140mfd 450 WVDC Electrolytics Brand New, ten for \$9.50. Mehafeff, 6835 Sunnybrook Lane, N.E., Atlanta 30328.

**RESISTANCE** decade box, featuring power, precision, convenient size. Six decades, constructed with 5 watt 1% resistors in 4x6 1/4 case. Modestly priced. \$44.50. Request literature. Telectric Company, Box 264, Hicksville, N.Y. 11801.

**TIME BASE CRYSTAL OVEN.** Center temp. 75° C. Cycling .05° C. 115 VAC. 1 1/2" dia. x 3" tall. Octal base. Holds HC-6/U xtal. Made by Ovensaire. Replacement for Berkeley Counters. \$10.00 includes shipping. Never used. Guaranteed. Yellow Cab Radio Dept., POB 587, Kansas City, Mo. 64108.

**TV TUNER REPAIRS**—Complete Course Details, 12 Repair Tricks, Many Plans, Two Lessons, all for \$1. Refundable. Frank Bockel, Box 833, Redding, Calif. 96001.

**QUALITY PRINTED CIRCUIT:** Epoxy Glass! 295 drilled holes! Outlined for three 16 pin D.I.P., plus components. 2" x 8 1/2". Tinned for solderability. Send \$3.00. **DIVERSIFIED ELECTRONIC TECHNOLOGIES**, 1529 Buffalo Road, Rochester, New York 14624.

**ELECTRONIC CD Ignitions, RPM Limiters, Precision Timers.** Send \$ .50 for complete Christmas catalog. AREpe, P.O.B. 9562, San Jose, California 95117.

**DIAGRAMS**—Radios \$1.50, Television \$3.00. Give make and model. Diagram Service, Box 1151PE, Manchester, Conn. 06042.

**ELECTRONIC Ignition.** Various Types. Information 10¢. Anderson Engineering, Epsom, N.H. 03239.

**EXPERIMENTERS**—Use any transistor radio for simple Radio Control Experiments. Complete Plans \$2. Creative Electronics, Box 4943A, Austin, Texas 78751.

**ROUTER** bits 1/4" shank, hi-speed, used, excellent condition, \$2.50 dozen postpaid. Lillians, Box 17165PE, Chicago, Ill. 60617.

**RADIOACTIVITY** experiment, see light flashes. Material with instructions \$1.00. Hamels, Box 453, Lafayette, Ind. 47902.

**FOLLOW THAT CAR. ELECTRONIC TRAILING EQUIPMENT. FREE LITERATURE.** CLIFTON, BOX 220, MIAMI, FLORIDA 33168.

**AVAILABLE NOW . . .** Plans; Visible and infrared Solid State Lamps; Matching receiving Photodiodes . . . Investigate fascinating optoelectronics field. Build profitable secret communications, surveillance, alarm, control systems. Amazing possibilities! New 1971 Catalog, 25¢. Lundart, University Station 4008-E4, Tucson, Arizona 85711.

**BURGLAR and FIRE ALARM SYSTEMS** and supplies. **INSTALLATION MANUAL** and catalog \$1.00. Refunded first order. Electronic Sentry Systems, P.O. Box 8023A, Sacramento, California 95818.

**NEW! PHONE PATCH** with automatic switch. Now you can record those important conversations automatically. **ONLY \$19.95.** Chico Electronics, 11835 Wilshire Blvd., Los Angeles, Calif. 90025.

**BACKGROUND MUSIC,** continuous commercial-free. Solid-state MUSICON SCA ADAPTER plugs into any FM Tuner, Receiver. Line powered. 5 year guarantee! Only \$39. postpaid. K-Lab, Box 5722, South Norwalk, Conn. 06856.

**PACEMATE** CB 2-way radio 2 watts 3 channel \$39.95. Regularly \$99.95. Request information. American Comset, 1638 W. 135th Street, Gardena, Calif. 90249.

**NEW SEMICONDUCTOR LIGHT EMITTING DIODES**—bright red lights replace light bulbs. Typical life 100 years. Operate at 1.65 volts, 50 milliamps. Order 2 for \$2.98 NOW. Data sheet and instructions included. Monsanto Company, Hobby Section, 10131 Bubb Road, Cupertino, California 95014.

**RIK-TRONICS LITE ALERT** with its exciting new Electronic Sound starts beeping immediately when the ignition is turned off if the headlights remain on. Installs in 2 minutes. List \$11.95, you send \$9.95. Rik-Tronics, Box 625, Franklin Pk., Ill. 60131.

**COMPUTER** for sale. Best offer over \$150. Send stamped, self-addressed envelope. Jon Paul, 1 Bogardus Pl., New York, New York 10040.

## PLANS AND KITS

**FIBRE OP-KITS,** using the "magical optical fibers" that transmit light energy. **FREE CATALOG.** Scientific Devices, 211E Albion, Wakefield, Mass. 01880.

**FORTY** Transistor Projects, \$1.00. Sirens, treasure finders, more! EDI, 1918B, 49th Street East, Palmetto, Florida 33561.

**SCA music adapter** for commercial-free FM background music. Connects easily to any FM tuner. 6-transistor circuit uses standard components. Plans and 3 x 4 1/2" etched circuit board \$4.50. Component kits also available. Wallace Enterprise, Inc., 83-15 98th Street, Woodhaven, N.Y. 11421.

**BUILD** your own electronic **COMPUTER.** New book explains theory, practical details. \$2.25 postpaid. Cinnamon Press, Box 8453-A, Minneapolis, Minnesota 55408.

**KITS** \$2.99. Buy two, one free. Free information. Aline, 434 West 4th Street, West Islip, New York 11795.

**CONSTRUCTION DIAGRAMS,** include olive transmitter, infinity transmitter, telephone room bugs, tailing devices, debuggers, radar jammer. Send \$2.00. Matusak, 5115 S. Campbell, Chicago, Illinois 60632.

**PHOTOGRAPHY** sink, Plywood fiberglass. Plans, instructions \$5.00. G. Miller, 9307 St. Lo Road, Houston, Texas 77033.

**INTEGRATED CIRCUIT KITS: COMPUTER, OPTOELECTRONICS, AUDIO.** Catalog free. **KAYE ENGINEERING,** Box 3932-A, Long Beach, California 90803.

**COLOR Organ Kits** \$7.50. Power Supplies \$2.75. Catalog. Murphy, 204 Roslyn Ave., Carle Place, New York 11514.

**COLOR** converter for black and white television. New patented system. Do-it-yourself electronic kit, for hobbyists and experimenters. Write for free brochure. Bele Electronics Corp., P.O. Box 2469, Main Office. Miami, Fla. 33101.

## HIGH FIDELITY

**FREE!** Send for money saving stereo catalog # P11E, lowest quotations on your individual component, tape recorder, or system requirements. Electronic Values, Inc., 200 W. 20th St., New York, N.Y. 10011.

**LOW,** Low quotes: all components and recorders, HiFi, Roslyn, Penna. 19001.

**Hi-Fi** components. Tape Recorders, at guaranteed "We Will Not Be Undersold" prices. 15-day money-back guarantee. Two-year warranty. No Catalog. Quotations Free. Hi-Fidelity Center, 239 (P) East 149th Street, New York 10451.

**TAPE RECORDERS,** Hi-Fi, components, Sleep Learning Equipment, tapes. Unusual Values. Free Catalog. Dressner, 1523R, Jericho Turnpike, New Hyde Park, N.Y. 11040.

**DIAMOND NEELES AND STEREO CARTRIDGES** at low, low prices for Shure, Pickering, Stanton, Empire, Grado and ADC. Send for free catalog and price sheet. We will be happy to quote on any cartridge—Magnetic, Ceramic or Crystal. All merchandise brand new and shipped **PREPAID.** **LYLE CARTRIDGES,** Dept. P, 265 East 149 Street, Bronx, New York 10451.

**New BSR** record changers; \$13. McDonald 300-\$18; 400-\$20; 500-\$25. AM/FM component system-\$50. Davis, Dept. 2737 Third Ave., Bronx, New York 10451.

**STEREO** headphones—\$20—Discounts available. Write H & M, Box 474, Pt. Hueneme, Calif. 93041.

## WANTED

**CASH PAID!** Unused tubes, electronic equipment. Barry, 512 Broadway, NYC 10012.

**QUICKSILVER,** Platinum, Silver, Gold, Ores Analyzed. Free Circular. Mercury Terminal, Norwood, Mass. 02062.

## TUBES

**TUBES "Oldies",** latest. Lists free. Steinmetz, 7519 Maplewood, Hammond, Indiana 46324.

**RECEIVING & INDUSTRIAL TUBES, TRANSISTORS.** All Brands—Biggest Discounts. Technicians, Hobbyists, Experimenters—Request **FREE** Giant Catalog and **SAVE!** **ZALYTRON,** 469 Jericho Turnpike, Mineola, N.Y. 11501.

**THOUSANDS** and thousands of types of electronic parts, tubes, transistors, instruments, etc. Send for Free Catalog. Arcturus Electronics Corp., MPE, 502-22nd St., Union City, N.J. 07087.

**RADIO & T.V. Tubes**—33¢ each. Send for free list. Cornell, 4213 University, San Diego, Calif. 92105.

**TUBES**—Lowest prices. Foreign-American. Obsolete, receiving, special purpose, transmitting tubes. Send for tube, parts catalog. United Radio Company, 56-P Ferry St., Newark, N.J. 07105.

**TUBE** Headquarters of World! Send 10c for Catalog (tubes, electronic equipment) Barry, 512 Broadway, N.Y.C. 10012.

## TAPE AND RECORDERS

**BEFORE** Renting Stereo Tapes try us. Postpaid both ways—no deposit—immediate delivery. Quality—Dependability—Service—Satisfaction—prevail here. If you've been dissatisfied in the past, your initial order will prove this is no idle boast. Free Catalog. Gold Coast Tape Library, Box 2262, Palm Village Station, Hialeah, Fla. 33012.

**STEREO TAPES**, save 20.30% and more, postpaid anywhere U.S.A. We discount batteries, recorders, tape/cassettes, 80-page catalog 25¢. **SAXITONE TAPES**, 1776 Columbia Road, N.W., Washington, D.C. 20009.

**OLD** radio programs on tape, 6 hours for \$8.00. Catalog 50¢. Don Maris, 1926 Cherokee, Norman, Okla. 73069.

**CASSETTES**—Cash in on a tremendous All-year round market. Send for lowest pricing and details. Include \$1.00 for 2 cassette samples. **DICTATION PRODUCTS**, PO Box 87 DPM, Hallandale, Florida 33009.

**OLD RADIO PROGRAMS** on tape. Hundreds available. 2-hr. sample \$6.00, 4-hr. \$9.00. Hobby Catalog for collectors of radio tapes, old comics, movie serials, nostalgic items, only \$1.25 or free with sample tape. **NOSTALGIA**, 9875 SW 212 St., Miami, Fla. 33157.

**ELECTRONICALLY** Made Moogmusic 4 track stereo, Scotch Reels. Send \$2.50—3257 Menomonee Parkway, Milwaukee, Wisconsin 53222.

## REPAIRS AND SERVICES

**TV** Tuners rebuilt and aligned per manufacturers specification. Only \$9.50. Any make UHF or VHF Ninety day written guarantee. Ship complete with tubes or write for free mailing kit and dealer brochure. **JW Electronics**, Box 51C, Bloomington, Indiana 47401.

**TELEVISION** tuners, any make VHF or UHF, cleaned, repaired and realigned per manufacturer's specifications \$9.50. One year guarantee. Quality Tuner Repair, 526 West Busby Street, Lebanon, Indiana 46052.

## PERSONALS

**MAKE FRIENDS WORLDWIDE** through international correspondence. Illustrated brochure free. Hermes, Berlin 11, Germany.

**INVESTIGATORS. LATEST ELECTRONIC AIDS. FREE LITERATURE.** CLIFTON, 11500-K NW 7th AVE., MIAMI, FLORIDA 33168.

## INSTRUCTION

**LEARN ELECTRONIC ORGAN SERVICING** at home all makes including transistor. Experimental kit—trouble-shooting. Accredited NHSC. Free Booklet. **NILES BRYANT SCHOOL**, 3631 Stockton, Dept. A, Sacramento, Calif. 95820.

**FCC** First Class License in six weeks—approved for Veterans Training. Write Elkins Institute, 2603B Inwood Road, Dallas, Texas 75235.

**LEARN WHILE ASLEEP**, Hypnotize! Strange catalog free. Auto-suggestion, Box 24-ZD, Olympia, Washington 98501.

**DEGREE** in Electronics Engineering earned mostly by correspondence. Free brochure. Dept. G-9, Grantham School of Engineering, 1505 N. Western Ave., Hollywood, California 90027.

**HIGHLY** effective home study courses in Electronics Engineering Technology and Electronics Engineering Mathematics. Earn your Degree. Write for Free Descriptive Literature. Cook's Institute of Electronics Engineering, (Dept. 15), P.O. Box 10634, Jackson, Miss. 39209. (Established 1945).

**F.C.C. FIRST CLASS LICENSE** in three to four weeks. Write American Institute of Radio, 2622 Old Lebanon Road, Nashville, Tennessee 37214 or 3986 Beach Boulevard, Box 16652, Jacksonville, Florida.

**FCC FIRST CLASS LICENSE THROUGH TAPE RECORDED LESSONS.** Also **RADAR ENDORSEMENT**. Radio License Training, 10600 Duncan, Manhattan Beach, Calif. 90266.

**MORE** sales through proper training. Pacific Institute of Programmed Instruction. P.O. Box 1326, Seattle, Washington 98102.

**LEAP! LEAP! LEAP!** Into BIG Money; 150,000 Computer Programmers needed in 5 years. Diploma Home Study Course, Price Breakthrough: only \$9.95. Act Now. Money Back Guarantee. U.S. Inquiries, Intertech-7G3, Box 5373, Station-F, Ottawa, Canada.

**LEARN** code from tireless teacher. Wilkinson programmed course and LP player stays with beginners to license speed. \$9.45 postpaid. Florida residents \$9.83. Details free. Wilkinson Laboratories, Box 14196, Gainesville, Fla. 32601.

**WANT AN F.C.C. 1st CLASS LICENSE? WANT TO BECOME A DISC-JOCKEY?** REI has a school near you VA approved. Call toll free: 1-800-237-2251 or write REI, 1336 Main St., Sarasota, Florida 33577, Florida Residents call: 813-955-6922.

**AMATEUR RADIO**, Correspondence Sight-and-sound no-textbook courses for **GENERAL, ADVANCED** and **EXTRA CLASS** licenses—complete Code and Theory. These are **NOT** memory courses. **AMATEUR RADIO LICENSE SCHOOL**, 12217 Santa Monica Blvd., Los Angeles, Calif. 90025.

## INVENTIONS WANTED

**INVENTIONS** wanted. Patented; unpatented. Global Marketing Service. 2420-P 77th, Oakland, Calif. 94605.

**PATENT** Searches including Maximum speed, full airmail report and closest patent copies, \$6.00. Quality searches expertly administered. Complete secrecy guaranteed. Free Invention Protection forms and "Patent Information." Write Dept. 9, Washington Patent Office Search Bureau, 711 14th Street, N.W., Washington, D.C. 20005.

**INVENTORS!** Don't sell your invention, patented or unpatented, until you receive our offer. Eagle Development Company, Dept. 9, 79 Wall Street, N.Y., N.Y. 10005.

**FREE** "Directory of 500 Corporations Seeking New Products." For information regarding development, sale, licensing of your patented/unpatented invention. Write: Raymond Lee Organization, 230-GR Park Avenue, New York City 10017.

**INVENTORS:** Protect your ideas! Free "Recommended Procedure". Washington Inventors Service, 422T Washington Building, Washington, D.C. 20005.

**PATENT SEARCHES**, including copies of related United States Patents. Inventors, attorneys, manufacturers use our "World-Wide" Airmail service Free: "Invention Record" form and "Information Every Inventor Needs", Hayward Company, 1029HR Vermont, Washington, D.C. 20005.

**FREE PAMPHLET:** "Tips on Safeguarding Your Invention." Write: United States Inventors Service Company, 501-H Thirteenth Street N.W., Washington, D.C. 20004.

## GOVERNMENT SURPLUS

**GOVERNMENT** Surplus How and Where to Buy in Your Area. Send \$1.00 to: Surplus Information PE, Headquarters Building, Washington, D.C. 20036.

**JEEPS** Typically From \$53.90 . . . Trucks From \$78.40 . . . Boats, Typewriters, Airplanes, Multimeters, Oscilloscopes, Transceivers, Electronics Equipment. Wide Variety, Condition. 100,000 Bid Bargains Direct From Government Nationwide Complete Sales Directory and Surplus Catalog \$1.00. (Deductible First \$10.00 Order). Surplus Service, Box 820-J, Holland, Michigan 49423.

**DIFFERENT?** You bet. Industrial and Government Electronic Surplus. Get our latest list now. Startronics, Box 17127, Portland, Oregon 97217.

## BOOKS

**FREE** catalog aviation/electronic/space books. Aero Publishers, 329PE Aviation Road, Fallbrook, California 92028.

**"UNUSUAL"** Books! Catalog Free! International, Box 7798 (PE), Atlanta, Georgia 30309.

**FREE** book prophet Elijah coming before Christ. Wonderful bible evidence. Megiddo Mission, Dept. 64, 481 Thurston Rd., Rochester, N.Y. 14619.

**INFORMATION.** Amazing Book. Swimsuits, jewelry. Write: LYN, Box 1573, Waco, Texas 76710.

**PSYCHOELECTRONICS** Handbook, \$14.95. (Sample pages Electrosex, \$1.00) Box 46156, Seattle 98146.

## MAGAZINES

**JAPAN PUBLICATIONS GUIDE** Business, pleasure, education. \$5.00. INTERCONTINENTAL, CPO 1717, Tokyo 100-91.

**OVER 2,000,000 backdate magazines!** Specify needs. Midtown, Box 917-PE, Maywood, New Jersey 07607.

## AUTHORS' SERVICES

**AUTHORS!** Learn how to have your book published, promoted, distributed. FREE booklet "ZD," Vantage, 120 West 31 St., New York 10001.

## HYPNOTISM

**"MALE-FEMALE HYPNOTISM" EXPOSED, EXPLAINED! "SECRET METHOD"—THEY NEVER KNOW! \$2, RUSHED. GUARANTEED! ISABELLA HALL, SILVER SPRINGS, FLORIDA 32688.**

**SLEEP Learning.** Hypnotic method. 92% effective. Details free. ASR Foundation. Box 702leg HC Station, Lexington, Ky. 40502.

**HYPNOTIZE PERFECT STRANGERS—EITHER SEX—SUCCESSFULLY!** Secret Methods—they never know! Illustrated Course and 10 inch Hypnodisk \$2.00. **RESULTS ABSOLUTELY GUARANTEED!** Dr. H. Arthur Fowler, Box 4399, Woodbury, New Jersey 08096.

## MAGNETS

**MAGNETISM** (100) page script newly discovered magnetic principles (\$3.00). Jesse Costa, Box 26, Waquoit, Mass. 02536.

**MAGNETS.** All types. Special—20 disc magnets, or 2 stick magnets, or 10 small bar magnets, or 8 assorted magnets, \$1.00 Maryland Magnet Company, Box 192E, Randallstown, Maryland 21133.

## PHOTOGRAPHY—FILM, EQUIPMENT, SERVICES

**SCIENCE Bargains Request Free Giant Catalog "CJ"—148 pages—Astronomical Telescopes, Microscopes, Lenses, Binoculars, Kits, Parts. War surplus bargains. Edmund Scientific Co., 300 Edscorp Bldg., Barrington, New Jersey 08007.**

## RECORDS

**POPULAR organ albums factory direct.** Concert Recording, Lynwood, Calif. 90262.

**SPECIAL interest records available,** produced by the editors of the world's leading special interest magazines. Send for free catalog. Record Catalog-PE, Ziff-Davis Publishing Company, One Park Avenue, New York, N.Y. 10016.

## PRINTING

**OFFSET Printing.** Free catalog. Speedy Print, 1906 Swede, Norristown, Pa. 19401.

**QUALITY Printing—Both Letterpress and Offset.** Economically priced. Speedy service. Free samples on request. Charles McCalister, 1222 W. Sevier St., Clarksville, Arkansas 72830.

## EMPLOYMENT INFORMATION

**FOREIGN and USA job opportunities available now.** Construction, all trades. Earnings to \$3,000.00 monthly. Paid overtime, travel bonuses. Write: Universal Employment, Woodbridge, Conn. 06525.

**EXCITING OVERSEAS JOBS.** Directory \$1.00. Research Associates, Box 942-E, Belmont, California 94002.

**"HOW to get jobs overseas"—Worldwide Lists Hiring Organizations—143 pages inside information—\$2.98.** Refundable. Staydrype, Whitestone, New York 11357.

## BUSINESS OPPORTUNITIES

**I MADE \$40,000.00 Year by Mailorder!** Helped others make money! Start with \$10.00—Free Proof. Torrey, Box 318-N, Ypsilanti, Michigan 48197.

**FREE BOOK "999 Successful Little Known Businesses"** Work home, Plymouth 445-K, Brooklyn, N.Y. 11216.

**\$200.00 DAILY in Your Mailbox!** Your opportunity to do what mail-order experts do. Free details. Associates, Box 136-J, Holland, Michigan 49423.

## CLASSIFIED ADVERTISING ORDER FORM

Please refer to heading on first page of this section for complete data concerning terms, frequency discounts, closing dates, etc.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

Words { @ 80¢ (Reader Rate) }  
 @ \$1.25 (Commercial Rate) } \$

Insert \_\_\_\_\_ time(s) Total Enclosed \$

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Signature \_\_\_\_\_

**WORD COUNT:** Include name and address. Name of city (Des Moines) or of state (New York) counts as one word each. Zip Code numbers not counted. (Publisher reserves right to omit Zip Code if space does not permit.) Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols such as 35mm, COD, PO, AC, etc., count as one word. Hyphenated words count as two words.

PE-1170

**MAKE BIG MONEY** raising chinchillas, rabbits, guinea pigs for us. Catalog—25¢. Keeney Brothers, New Freedom, Pa. 17349.

**SPARE TIME CASH**—Sell advertising Book Matches—every business a prospect—no investment—no experience needed—build steady repeat business. Power house selling kit with new complete catalog FREE. Quick sales and big cash commissions. Dept. T-1170, Superior Match, 7530 S. Greenwood, Chicago 60619.

**FREE CATALOGS.** Repair air conditioning, refrigeration. Tools, supplies, full instructions. Doolin, 2016 Canton, Dallas, Texas 75201.

**PRODUCE Household Products.** Your trade name—our formulas. Details 50¢. Thinker/Tinker, Box 205PE, Riverside, Conn. 06878.

**FREE BOOK** "996 MILLIONAIRE Plans, Odd, Unusual, Little-Known Businesses" on request. Work home evenings & Saturdays. National-22, Kerrville, Texas 78028.

**SELL HERTEL BIBLES**—Part Time. Finest reference Bible available. Demonstrator and supplies furnished. Excellent commissions. Write International Book, Dept. PE, Box 118, Wichita, Kansas 67201.

**PIANO TUNING** learned quickly at home. Tremendous field! Musical knowledge unnecessary. GI Approved. Information Free. Empire School, Box 327, Miami, Florida 33145.

**MAILORDER!** Make big money working home. Free report reveals millionaire's trade secrets! Executive (1K11), 333 North Michigan, Chicago 60601.

**EASY** to make plastic fishing worms. Costs 3¢. Sell for up to \$1.00. Big profits. Details and formula \$2.00. Poco Plantation, Dept. 150, P.O. Box 5046, Augusta, Ga. 30906.

**MAKE MONEY** in spare time. Information write. Capitol, Box 9363, Austin, Texas 78757.

**\$2000.00 MONTHLY** possible. Details. Ropchan, Box 5341 X, Shermanoaks, California 91413.

## TREASURE FINDERS

**GOLD, SILVER, RELICS!** Located with powerful Detectron Metal Detectors. Free information. Terms. Detectron, Dept. PE-11, Box 243, San Gabriel, California 91778.

**TREASURE FINDER** locates buried gold, silver, coins, treasures. 5 powerful models. \$19.95 up. Free catalog. Relco-A33, Box 10839, Houston, Texas 77018.

**FREE TREASURE GUIDE!** Fact-filled collectors edition; send 50¢ for postage. Also request free literature on ultrasensitive, professional Fisher Detectors. FISHER RESEARCH, Dept. PE-11, Palo Alto, California 94303.

## MUSICAL INSTRUMENTS

**30% DISCOUNT** any name brand musical instrument. Free catalog. Freeport Music, 127-N Sunrise Highway, Freeport, N.Y. 11520.

## SHORTWAVE LISTENING

**CONFIDENTIAL** frequencies revealed! Over 450—spies, space, military. \$2.00. EDI, 1918B 49th Street East, Palmetto, Florida 33561.

## RUBBER STAMPS

**RUBBER ADDRESS STAMPS** \$2.00. SIGNATURE \$3.50. FREE CATALOG. JACKSON'S, BOX 443-G, FRANKLIN PARK, ILLINOIS 60131.

## REAL ESTATE

**FREE . . . 232-PAGE FALL-WINTER CATALOG!** Describes and pictures hundreds of farms, ranches, town and country homes, businesses coast to coast! Specify type property and location preferred. Zip Code, please. UNITED FARM AGENCY, 612-EP West 47th St., Kansas City, Mo. 64112.

## MISCELLANEOUS

**WINEMAKERS:** Free illustrated catalog of yeasts, equipment. Semplex, Box 12276, Minneapolis, Minn. 55412.

**DRIVER'S License, Birth Certificate, H.S. & College Diploma, Marriage & Divorce Certificates**—Blank Forms. Fill them in yourself. Highest quality you can buy! Confidential 3 day service! \$2.00 each; any four—\$5.00, post-paid. Formco, Box 834-EB, Warren, Mich. 48090.

## BAGGY'S RADIO

AM AND SSB CB RADIOS AND ACCESSORIES  
SEND FOR FREE BIG BONUS CATALOG

P.O. Box 778, 6391 Westminster Ave.  
Westminster, California 92683  
714-894-7555



**USE FOR:**  
**HOME**  
**BOAT**  
**BUSINESS**  
**CAMPER**  
**CAR**  
**TRUCK**

**STINGER ANTENNAS**  
**SWAN HAM RIGS**

**MAJOR BRANDS**  
**CB RADIOS &**  
**ACCESSORIES.**

**MONITORS**  
**POLICE**  
**FIRE**  
**WEATHER**

**METAL DETECTORS**  
**ADAPT-A-MOUNTS**


**VFO 11 METER**  
**SLIDER SCANNER**

**AND MUCH MORE!**

**DEALERS SEND LETTERHEAD**  
**FOR**  
**FACTORY DIRECT PRICES**

**CIRCLE NO. 5 ON READER SERVICE PAGE**

# FREE CATALOG & PRICE LIST

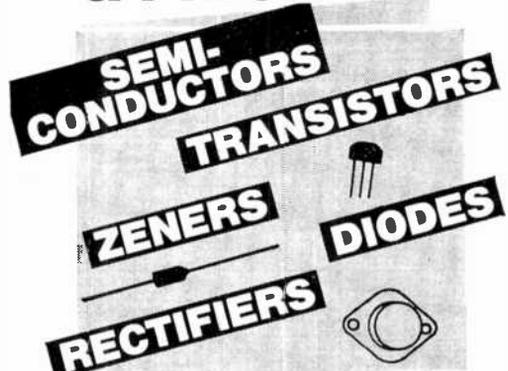

**SAVES BIG MONEY ON**  
**ALL YOUR PARTS NEEDS!**

Thousands of hand tested parts in open stock. 24-hour delivery on most items. Hard to find specialties? We have them! Order direct and save!


**SEMI-CONDUCTOR**  
**SUPPLY, INC.**

20 Commerce Street  
Springfield, N.J. 07081

**CIRCLE NO. 25 ON READER SERVICE PAGE**

1000's OF UNUSUAL SCIENTIFIC BARGAINS including...  
**SPECIAL UNIQUE PSYCHELIC LIGHTING**  
*for Fun, Profit, Effects!*


**3" ASTRONOMICAL TELESCOPE**

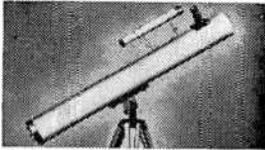

See moon shots, orbits-stars, phases of Venus, planets close up, 60 to 180X. New improved, aluminized & overcoated 3" diameter f/10 primary mirror, ventilated cell. Equatorial mount w/locks on both axes. 60X eyepiece, mounted Barlow. 3X finder telescope, hardwood tripod, Incl. FREE: "STAR CHART"; 272-P. "HANDBOOK"; Inst.

Stock No. 85,086AV ..... \$29.95 Ppd.  
 Stock No. 85,105 AV ..... \$41.50 Ppd.  
 Stock No. 85,086AV ..... \$199.50 P.O.B.

**CHROMATIC "MACHINE-GUN" STROBE**

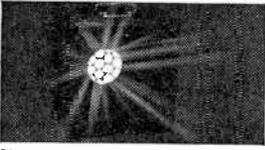

Red, Green, Blue & White light barrage the eyeballs every 6 seconds with this low-cost mechanical strobe that can run continuously without fear of burning up. Devasiating effects over 200 ft. sq. area. Created by rotating color wheel in front of 100W, 120V reflector flood lamp (Incl.)—elements seem to flash on & off as colors fluctuate. Turns store windows, posters, parties into flashing, pulsating productions. Convection cooled. Walnut cabinet. Brass handle. Reg. house current.

Stock No. 71,271AV ..... (9x10x6 1/4") ..... \$28.50 Ppd.


**PSYCHELIC LIGHTING HANDBOOK**



100 information packed pages! Fully explains latest in psychedelic lighting equipment, techniques, developments. Covers all facets of psychedelic light-show production including strobes, black lights, projectors, crystals, organic slides, mirrors, color organs, polarized colors, light boxes, MagicVision; etc. Shows how to "psychedelicate" parties, musical groups, shows or how to set up "electric trips" for private gatherings. 8 1/2" x 11" looseleaf paper for 3 rings.

Stock No. 9100AV ..... \$3.00 Ppd.

**LONG-WAVE BLACKLIGHT FIXTURE**

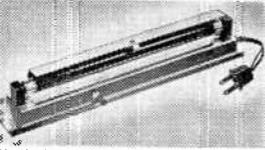

Extremely versatile, compactly designed, long wave (3200-4000 angstroms) black light (ultraviolet) fixture. Has 6-watt, 110-V lamp with built-in filter—eliminates harmful shorter wave ultraviolet rays. Use to identify minerals, fungi, bacteria—check for surface flaws, oil and gas leakage—perfect for displays with fluorescent paper, paints, chalk, crayons, trace powder, Incl. adjustable aluminum reflector. Mount vert., horiz., or on corner. 10" L., 1 1/4" W., 1 1/4" H.

Stock No. 70,364AV ..... \$12.50 Ppd.  
 Stock No. 60,124AV ..... REPLACEMENT BULB ..... \$4.75 Ppd.

**1st QUALITY OPAQUE UNDER \$200**



Terrific Buy! Top Quality! Projects brilliant, sharp 1/2 ft. sq. image from 8' using up to 8"x6" color, b&w illustrations. Retains all original colors, proportions. Enlarges drawings, coins, maps, etc. Revolutionary pscuut-size quartz halogen lamp (50 hr. life). 200mm anastigmatic lens (f3.5, 8" F.L.); unique internal reflecting system give maximum brightness, entire field focus. Can be used upside down. Turbo-cooled 0 1/2 cu. ft. .... 11 1/2 lbs) ..... \$89.75 Ppd.

Stock No. 71,272AV ..... (Wt. .... \$89.75 Ppd.

**MIRRORED BALLS BOUNCE LIGHT**



Yesterday's ballrooms echo in mirrored lights that ricochet to the beat of today's discotheque. Up to 1,000 lustrous, clear, handmade glass mirrors on each ball create fantastic lighting effects. Motorized—they cast reflections that blow the mind! Ideal for light shows, displays, restaurants, hotels, and modern stores.

Stock No. 71,066AV ..... (12" Diam.) ..... \$30.00 Ppd.  
 Stock No. 85,100AV ..... (16" Diam.) ..... \$75.00 Ppd.  
 Stock No. 71,065AV ..... (8" Diam.) ..... \$17.50 Ppd.

Order by Stock No.—Check or M.O.—Money-Back Guarantee  
 EDMUND SCIENTIFIC CO., 300 EDCORP BLDG., BARRINGTON, N.J. 08007

**WRITE FOR GIANT FREE CATALOG "AV"**



Completely new edition. New items, categories, illustrations, 148 easy-to-read pages packed with 4000 unusual items. Dozens of electrical and electromechanical parts, accessories. Enormous selection of Astronomical Telescopes, Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Lasers, Prisms. Many war surplus items for hobbyists, experimenters, workshops, factory. Write for catalog "AV."

**EDMUND SCIENTIFIC CO.** 300 EDCORP BLDG., BARRINGTON, NEW JERSEY 08007  
 ORDER BY STOCK NUMBER - SEND CHECK OR MONEY ORDER - MONEY-BACK GUARANTEE

CIRCLE NO. 11 ON READER SERVICE PAGE

**POPULAR ELECTRONICS**

**NOVEMBER 1970**

**ADVERTISERS INDEX**

READER SERVICE NO.	ADVERTISER	PAGE NO.
	Allied Radio Shack	85
	Audionics, Inc.	96
	Avanti Research & Development, Inc.	14
	Baggy's Radio	107
	CREI, Home Study Div., McGraw-Hill Book Co.	36, 37, 38, 39
	Cleveland Institute of Electronics	54, 55, 56, 57
	Center for Technical Development	95
	Courier Communications	87
	Datak Corp.	102
	Drake Company, R.L.	84
	Communications Div., DYNASCAN CORP.	9
	EICO Electronic Instrument Co., Inc.	
	FOURTH COVER	
11	Edmund Scientific Co.	108
12	Electronic Light Co.	95
13	Esse Radio	100
14	Finney Co.	11
15	GC Electronics (CALECTRO)	25
16	Heath Co.	88, 89, 90, 91, 92, 93
17	Jensen Mfg. Div., The Muter Co.	94
	Jetco	98
	Johnson Company, E.F.	THIRD COVER
18	Lafayette Radio Electronics	96
19	Mallory & Co., P.R.	23
20	Metrologic Instruments, Inc.	100
21	Mosley Electronics, Inc.	102
22	McGee Radio	86
23	McGraw-Hill Book Co., Electronic & Control Engineers Book Club	5
24	McIntosh Labs	97
	National Radio Institute	SECOND COVER, 1, 2, 3
	National Technical Schools	18, 19, 20, 21
25	New Jersey Semi-Conductors	107
26	New-Tronics	86
26	Olson Electronics	98
	RCA Electronic Components & Devices	26, 27, 28
	RCA Institutes, Inc.	72, 73, 74, 75
27	Sams, Howard W. & Co., Inc.	8
28	Sonar Radio Corp.	99
29	Sydmur Electronics	94
	Sylvania Electric	13
30	TDK Electronics Corp.	10
33	Turner Microphone Co., The	16
	U.S. Army	101
31	United Audio Products (DUAL)	6
	United Binocular	98
34	University Sound	17
32	Utah Electronics	12
	Valparaiso Technical Institute	98

CLASSIFIED ADVERTISING 103, 104, 105, 106, 107

Printed in U.S.A.

**check  
your CB rig's  
performance  
10 ways...**



Suggested list: **\$49.95**

## Johnson's new transceiver tester.

Does everything other testers do... and more! Reads power output in *actual watts*. Reads modulation *directly in percentage*. And lets you *hear* what your transmitted signal actually sounds like, with the headphone monitoring jack! Also can be installed to read received "S" units. Constantly monitors your rig while you're on-the-air. Flip a switch and you can make

tests using the built-in dummy load. There are built-in RF and audio generators, crystal activity checker, SWR meter, and more—so you can pinpoint problems like a professional. Battery operated and portable, it even has a field strength meter that's great for making comparative checks at jamborees. No serious CBer should be without it!

Other Johnson Accessories for the Advanced CBer...



CB MATCHBOX  
ANTENNA TUNER  
\$15.95



CB ANTENNA  
METER \$14.95

NEW



RECHARGER/BASE  
POWER SUPPLY FOR  
HAND-HELDS \$28.00

NEW



ANTENNA MATE  
TUNER AND SWR  
METER \$29.95

NEW



CB MOBILE  
SPEAKER \$13.00



**E. F. JOHNSON COMPANY**

WASECA, MINNESOTA 56093

CIRCLE NO. 3 ON READER SERVICE PAGE

# Be creative - and thrifty too!

Save up to 50% with EICO Kits and Wired Equipment.

## NEW "TREASURE HUNTER" KIT

Finds metals, pipes several inches underground. EICO TH-30 Solid State Treasure Hunter locates iron, steel, tin, gold, silver, copper etc. Beep pitch increases as you near object.

Battery operated. \$29.95.



## NEW "BULLHORN" KIT

Carries your voice up to 400 feet. EICO BH-16 Solid State Bullhorn. 2½ lbs. light, is perfect for all outdoors, camping, sports. Battery-operated. \$15.95.



## NEW EICOCRAFT

The electronic science project kits for beginners, sophisticates, educators. 42 kits to date.



FM Wireless Mike \$9.95.

## 8 NEW EICOCRAFT KITS

Automotive "LIGHTGUARD" • "VARIVOLT" DC Power Supply • "MOODLITE" Light Dimmer Control • "VARASPEED" Motor Speed Control • "LIGHTSHOW" Sound/Lite Translator • "ELECTRIC FIESTA" Audio Color Organ • "SUPER MOODLITE" Remote Control Light Dimmer • "ELECTROPLATER" From \$2.50 to \$14.95.

## NEW "FLEXI-CAB"

Build your own custom designed cabinet in minutes!

Give your EICOCRAFT and other projects that finished professional look with decorative FLEXI-CAB vinyl clad steel cabinets. Fast, easy, push-together assembly. 3-sizes from \$3.49.

## COLOR IMAGES

Electronic Art in Motion.

### "CHROMA-CUBE"

Classic white 18" Cube features a fantastic audio-responsive light display.



### "CELESTIAL LITES"

Constantly flowing color images move in rhythm to music. 24" x 24" x 6".



### "LIGHT FANTASTIC"

Translucent dome provides 3-dimensional world of ever changing light patterns in response to music. 38" high.



## NEW cortina2 STEREO KITS

The lowest priced component quality high fidelity!

EICO 3780 50-Watt Silicon Solid State FET AM-FM Stereo Receiver. Kit \$109.95, Wired \$169.95



EICO 3080 50-Watt Silicon Solid State Stereo Amplifier. Kit \$69.95, Wired \$109.95



EICO 3300 Silicon Solid State FET AM-FM Stereo Tuner. Kit \$69.95, Wired \$109.95

## NEW SOLID STATE TEST INSTRUMENTS

The first and only solid-state test equipment guaranteed for 5 years!



EICO 240 Solid State FET-TVM. Kit \$59.95, Wired \$79.95.  
EICO 379 Solid State Sine/Square Wave Generator. Kit \$69.95, Wired \$94.50.  
EICO 242 Solid State FET-TVOM. Kit \$69.95, Wired \$94.50.  
EICO 150 Solid State Signal Tracer. Kit \$49.95, Wired \$69.95.  
EICO 330 Solid State RF Signal Generator. Kit \$59.95, Wired \$84.50.



## FREE 1970 EICO CATALOG PE-11

Send me FREE catalog describing the full EICO line of 200 best buys, and name of nearest dealer.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_


EICO Electronic Instrument Co., Inc.  
283 Malta Street, Brooklyn, N.Y. 11207



NOW YOU CAN SEE THE MUSIC YOU HEAR.

## Sound n' Color

Color Organs, Translators, Strobes

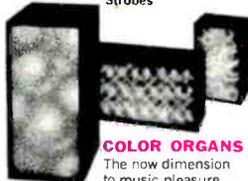

## COLOR ORGANS

The new dimension to music pleasure.

EICO all electronic solid-state Audio-Color Organs transform sound waves into moving synchronized color images.

MODEL 3450 Giant (30" x 12" x 10") 4-Channels. Kit \$79.95, Wired \$109.95.

MODEL 3445 (24" x 12" x 10") 4-Channels. Kit \$64.95, Wired \$99.95.

MODEL 3440 (10" x 15" x 16") 3-Channels. Kit \$49.95. Wired \$79.95. Other models to choose, from \$19.95 and up.

## TRANSLATORS

The electronics you need to create audio-stimulated light displays.



MODEL 3460 1 Channel. Kit \$24.95, Wired \$39.95.

MODEL 3465 3 Channel. Kit \$39.95, Wired \$69.95.

## STROBE LITES

Burst of white light flash in cadence of each beat of audio.

Model 3470 Adjustable Rate. Kit \$29.95, Wired \$39.95.

Model 3475 Audio Actuated. Kit \$39.95, Wired \$59.95.



## AUTOMOTIVE

EICO 889 Solid State Capacitive Ignition System.

Boost gas mileage up to 25%, life of points, plugs to 100,000 miles; Kit \$29.95, Wired, \$39.95.



EICO 888 Solid State Universal Engine Analyzer. Tunes and troubleshoots your car/boat engine, the totally professional way. Kit \$49.95, Wired \$69.95.