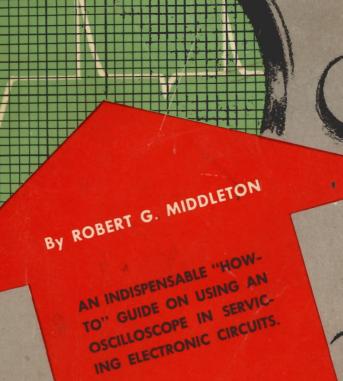


TROUBLESHOOTING with the OSCILLOSCOPE



TROUBLESHOOTING with the OSCILLOSCOPE

By ROBERT G. MIDDLETON



FIRST EDITION FIRST PRINTING — FEBRUARY, 1962 SECOND PRINTING — JUNE, 1962

TROUBLESHOOTING WITH THE OSCILLOSCOPE

Copyright © 1962 by Howard W. Sams & Co., Inc., Indianapolis 6, Indiana. Printed in the United States of America.

Reproduction or use, without express permission, of editorial or pictorial content, in any manner, is prohibited. No patent liability is assumed with respect to the use of the information contained herein.

Library of Congress Catalog Card Number: 62-12658

PREFACE

Troubleshooting modern electronic circuits literally demands the use of an oscilloscope, yet many service technicians experience difficulty in learning how to use this versatile instrument.

Of the numerous service technicians who have difficulty in employing an oscilloscope, many own or have used one, but really don't understand its functions well enough to set it up for proper waveform displays. On the other hand, technicians who fully understand the workings of a scope rate it among their most valuable instruments.

This book was planned and written with the full realization of the type of practical instructional help needed by service technicians. Its purpose is to help you obtain the maximum benefits from a scope, even if you have never used the instrument before.

Beginning with the first chapter, you'll learn the purpose and function of every oscilloscope operating control. Whether your unit is simple or elaborate, the mystery of how it operates is dispelled in this introductory chapter.

The next subject is the selection and application of probes, a very important consideration in obtaining proper waveform displays. Subsequent chapters are devoted to explaining how a scope is used in localizing TV troubles to specific receiver sections, and then to a particular stage. In several cases, you'll find it possible to use a scope to pinpoint the defective component itself.

Use of the scope is divided into two general categories—signal-tracing circuits supplied with external signals, and checking waveforms in signal-generating stages which operate independently of external signals. Since a scope can often give more information when particular types of external signals are utilized, material has been included to explain the advantages of using CW and modulated sine waves, video waves, FM sweep signals, and square waves.

While the major portion of this book concentrates on troubleshooting television circuits, chapters on servicing radio receivers and audio amplifiers have also been included to give you the thorough background needed to use the scope for checking practically any type of electronic circuit. To obtain the maximum value from the contents, I strongly suggest you actually work with your equipment as the various procedures are described. This "reinforced learning," gained at the workbench, will more than double the benefits you will derive from reading alone.

ROBERT G. MIDDLETON

January, 1962

TABLE OF CONTENTS

CHAPTER 1

Intensity-Control Adjustment — Centering-Control Adjustment — Focus-Control Adjustment — Setting the Horizontal-Amplitude and -Function Controls—Application of a 60-Cycle AC Test Voltage—Pattern Size Versus Intensity-Control Setting—Gain Controls—Frequency Control—Retrace Blanking—Horizontal Nonlinearity—Calibration and Peak-to-Peak Voltage Measurements—Complex Waveforms—Step Attenuators—DC Versus Peak-to-Peak Volts—Sync Function—Lissajous Patterns—Display of Narrow Pulses—Display of Square Waves—Fluctuating Line Voltage	•
CHAPTER 2	
Using Oscilloscope Probes	42
CHAPTER 3	
Signal Tracing in RF, IF, and Video Amplifiers Troubleshooting RF Amplifiers—Signal Tracing in the IF Section—Signal Tracing in the Video Amplifier	59
CHAPTER 4	
Signal Tracing in the Sync Section	77
CHAPTER 5	
Troubleshooting the AFC and Horizontal-Oscillator Section	87

CHAPTER 6

Waveform Tests in the Horizontal-Sweep Section	98
Sweep-Circuit Troubleshooting—Low Drive—Narrow Picture—High-Voltage Power Supply—Boost-Voltage Filtering—Keystoning	
CHAPTER 7	
Troubleshooting the Vertical-Sweep Section	108
Vertical Synchronization—Coupling Capacitor Checks—Feed-back Waveforms—Vertical-Output Transformer—Cathode Circuit—Vertical-Blanking Network	
CHAPTER 8	
Signal-Tracing the Sound and Audio Section Test Signal for the Intercarrier Section—Minimizing Circuit Loading—Limiter Characteristics	118
CHAPTER 9	
Troubleshooting Power Supplies	127
CHAPTER 10	
Radio-Receiver Troubleshooting	135
Scope Requirements—Gain Measurements—Type of Test Signal—Oscillator Defects—IF Stage Troubles—Audio Stage Tests—Hum Tracing	
CHARTER 11	
CHAPTER 11	
Testing Audio Amplifiers	145
Index	155