

PRACTICAL

August 1992 • £1.50

ELECTRONICS

SCIENCE AND TECHNOLOGY

HiFi On The Road

We take a look at in-car stereo systems


We are
giving away
**50 Sony
UX Turbo
Cassettes**



Is This The Future
Of The Personal
Organiser?

Plus

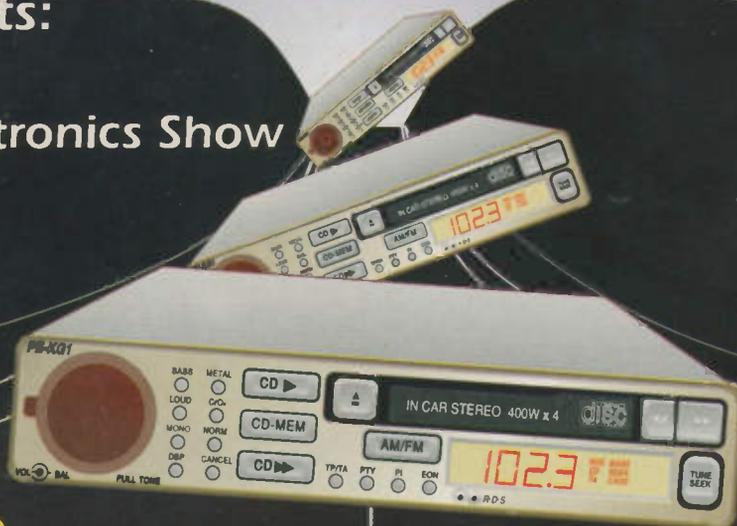Special Reports:
Multimedia 92
Consumer Electronics Show



Opinion

Barry Fox On Illegal Gadgets
Ian Burley On Multimedia



SURVEILLANCE PROFESSIONAL QUALITY KITS

No. 1 for Kits

Whether your requirement for surveillance equipment is amateur, professional or you are just fascinated by this unique area of electronics SUMA DESIGNS has a kit to fit the bill. We have been designing electronic surveillance equipment for over 12 years and you can be sure that all of our kits are very well tried, tested and proven and come complete with full instructions, circuit diagrams, assembly details and all high quality components including fibreglass PCB. Unless otherwise stated all transmitters are tuneable and can be received on an ordinary VHF FM radio.

UTX Ultra-miniature Room Transmitter

Smallest room transmitter kit in the world! Incredible 10mm x 20mm including mic. 3-12V operation. 500m range £16.45

MTX Micro-miniature Room Transmitter

Best-selling micro-miniature Room Transmitter
Just 17mm x 17mm including mic. 3-12V operation. 1000m range £13.45

STX High-performance Room Transmitter

Hi performance transmitter with a buffered output stage for greater stability and range. Measures 22mm x 22mm including mic. 6-12V operation, 1500m range £15.45

VT500 High-power Room Transmitter

Powerful 250mW output providing excellent range and performance. Size 20mm x 40mm. 9-12V operation. 3000m range £16.45

VXT Voice Activated Transmitter

Triggers only when sounds are detected. Very low standby current. Variable sensitivity and delay with LED indicator. Size 20mm x 67mm. 9V operation. 1000m range £19.45

HVX400 Mains Powered Room Transmitter

Connects directly to 240V AC supply for long-term monitoring. Size 30mm x 35mm. 500m range £19.45

SCRX Subcarrier Scrambled Room Transmitter

Scrambled output from this transmitter cannot be monitored without the SCDM decoder connected to the receiver. Size 20mm x 67mm. 9V operation. 1000m range £22.95

SCLX Subcarrier Telephone Transmitter

Connects to telephone line anywhere, requires no batteries. Output scrambled so requires SCDM connected to receiver. Size 32mm x 37mm. 1000m range £23.95

SCDM Subcarrier Decoder Unit for SCRX

Connects to receiver earphone socket and provides decoded audio output to headphones. Size 32mm x 70mm. 9-12V operation £22.95

ATR2 Micro Size Telephone Recording Interface

Connects between telephone line (anywhere) and cassette recorder. Switches tape automatically as phone is used. All conversations recorded. Size 16mm x 32mm. Powered from line £13.45

UTLX Ultra-miniature Telephone Transmitter

Smallest telephone transmitter kit available. Incredible size of 1mm x 20mm! Connects to line (anywhere) and switches on and off with phone use. All conversation transmitted. Powered from line. 500m range £15.95

TLX700 Micro-miniature Telephone Transmitter

Best-selling telephone transmitter. Being 20mm x 20mm it is easier to assemble than UTLX. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 1000m range £13.45

STLX High-performance Telephone Transmitter

High performance transmitter with buffered output stage providing excellent stability and performance. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. Size 22mm x 22mm. 1500m range £16.45

TKX900 Signalling/Tracking Transmitter

Transmits a continuous stream of audio pulses with variable tone and rate. Ideal for signalling or tracking purposes. High power output giving range up to 3000m. Size 25mm x 63mm. 9V operation £22.95

CD400 Pocket Bug Detector/Locator

LED and piezo bleeper pulse slowly, rate of pulse and pitch of tone increase as you approach signal. Gain control allows pinpointing of source. Size 45mm x 54mm. 9V operation £30.95

CD600 Professional Bug Detector/Locator

Multicolour readout of signal strength with variable rate bleeper and variable sensitivity used to detect and locate hidden transmitters. Switch to AUDIO CONFORM mode to distinguish between localised bug transmission and normal legitimate signals such as pagers, cellular, taxis etc. Size 70mm x 100mm. 9V operation £50.95

QTX180 Crystal Controlled Room Transmitter

Narrow band FM transmitter for the ultimate in privacy. Operates on 180 MHz and requires the use of a scanner receiver or our QRX180 kit (see catalogue). Size 20mm x 67mm. 9V operation. 1000m range £40.95

QLX180 Crystal Controlled Telephone Transmitter

As per QTX180 but connects to telephone line to monitor both sides of conversations. 20mm x 67mm. 9V operation. 1000m range £40.95

QSX180 Line Powered Crystal Controlled Phone Transmitter

As per QLX180 but draws power requirements from line. No batteries required. Size 32mm x 37mm. Range 500m £35.95

QRX180 Crystal Controlled FM Receiver

For monitoring any of the 'Q' range transmitters. High sensitivity unit. All RF section supplied as a pre-built and aligned module ready to connect on board so no difficulty setting up. Output to headphones. 60mm x 75mm. 9V operation £60.95

A build-up service is available on all our kits if required.

UK customers please send cheques, POs or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft and add £5.00 per order for shipment. Credit card orders welcomed on 0827 714476.

OUR LATEST CATALOGUE CONTAINING MANY MORE NEW SURVEILLANCE KITS NOW AVAILABLE. SEND TWO FIRST CLASS STAMPS OR OVERSEAS SEND TWO IRCS.

★★★ Specials ★★★

DLTX/DLRX Radio Control Switch

Remote control anything around your home or garden, outside lights, alarms, paging system etc. System consists of a small VHF transmitter with digital encoder and receiver unit with decoder and relay output, momentary or alternate, 8-way di1 switches on both boards set your own unique security code. TX size 45mm x 45mm. RX size 35mm x 90mm. Both 9V operation. Range up to 200m.

Complete System (2 kits) £50.95
Individual Transmitter DLTX £19.95
Individual Receiver DLRX £37.95

MBX-1 Hi-Fi Micro Broadcaster

Not technically a surveillance device but a great idea! Connects to the headphone output of your Hi-Fi, tape or CD and transmits Hi-Fi quality to a nearby radio. Listen to your favourite music anywhere around the house, garden, in the bath or in the garage and you don't have to put up with the DJ's choice and boring waffle. Size 27mm x 60mm. 9V operation. 250m range £20.95

**SUMA
DESIGNS**

THE WORKSHOPS, UNIT PE, 95 MAIN ROAD,
BAXTERLEY, NEAR AHERSTONE,
WARWICKSHIRE CV9 2LE
VISITORS BY APPOINTMENT ONLY



0827 714476

This month...

A slight change to the magazine this month as we take a stand with our new opinion pages. Industry pundits Barry Fox and Ian Burley make their views known on the subjects of advertising and multimedia.

Multimedia also features in one of our show reports as does the bi-annual US consumer electronics show. All of the electronics hardware that you can expect to appear in the shops was on display. In fact, there was so much of it, we've had to split our report in two.

I hope you fill in the reader survey on page 44 so that we can keep abreast of what it is you like (or possibly dislike) about the magazine. You may even get lucky and win one of Sony's special new cassettes.

Kenn Garroch, Editor



Electric cars on parade – page 10



A 20M hard disk in a matchbox – page 18

Next month...

Photography
Electronics in cameras and image
storage plus CES part 2.

Out On 6 August

Cover illustration and design: Kenn Garroch (with inspiration from Steven Spielberg)

Features

- Electronic Organiser**13
Apple's Personal Digital Assistant under scrutiny
- On Show In Chicago**14
DCC, widescreen TV, BOSS, watches and much more.
- HiFi Hits The Road**23
In-car stereo systems and RDS automatic tuning.
- Tapes For Cars**26
Sony's new UX Turbo in-car tapes under scrutiny
- Making Connections**.....30
How to get connected to the world wide computer network.
- Multimedia 92**.....34
A recent showing of Quicktime, Autodesk, touch screens and CD-I.
- One Transistor, One Junction**37
A full explanation of the uni-junction transistor.
- New Technology**41
New and cheaper solar cells, super amplifiers and clean ICs.
- The Future Of The Tuning Fork**.....48
Full details on constructing the latest in musical aids.
- Reader Survey 1992**44
We want to know what you think about PE and give away 50 of Sony's latest cassettes as well.



The Apple Newton – page 13



Sony's new tape – page 26

Regulars

- Wavelengths**.....4
Mosquitoes, meteor scatter and virtual reality in the letters page.
- Barry Fox**.....6
Does the CreditCall work or not?
- Ian Burley**.....7
Multimedia is no longer just a dream. It is here and now.
- Practical Computing**.....8
The latest news from the world of computer electronics.
- Innovations**10
Cooling the 486, the largest PCB in the world and electric cars.
- New Product Developments**..18
Includes the smallest hard disk ever, fractals and A5 notebooks.
- How It Works**30
A look inside a car engine management system.
- Techniques**.....53
How much work is really involved in electronic design?



DCC for sale – page 14



A5 portables – page 20

Editor: Kenn Garroch Advertisement Manager David Bonner Accounts Manager Martin Milner Production Manager: Richard Milner Additional photography by Carolyn Vaughn Publisher: Angelo Zgorelec • **Practical Electronics** Intra House 193 Uxbridge Road London W12 9RA Tel: 081-743 8888 Fax: 081-743 3062 Telecom Gold: 87: SQ0567 CIX Care of PROGNOW • Advertisements The Publishers of PE take reasonable precautions to ensure that advertisements published in the magazine are genuine, but cannot take any responsibility in respect of statements or claims made by advertisers. The Publishers also cannot accept any liability in respect of goods not being delivered or not working properly. • © Intra Press 1991. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. All material is accepted for publication on the express understanding that the contributor has the authority to permit us to do so. • Practical Electronics is typeset and reproduced at Intra Press on Macintosh computers using Quark Xpress, Scan Xpert scanner and Adobe Photoshop. Advertising reproduction by Circle Rule Ltd. Printing by Andover Press, St Ives plc. Distribution by Seymour Press • ISSN 0032-6372 •

Wavelengths

If you have any comments, suggestions, subjects you think should be aired, write to PE

Vista Address

Your review of the Vistapro virtual reality program in Practical Electronics June 92 was very interesting. The only thing missing was the name of a supplier. The comment "Vistapro is available from all good software suppliers" is of no help at all. Can you name your source?

P Wills
Northampton

The package is actually produced by a US company called Virtual Reality Laboratories Inc but a UK distributor is PCCConnections Tel 0706 222988

It may also interest you to know that a new version of Vistapro will soon be available with improved flying sequences and the VR Labs are hoping to get hold of the Magellan radar data from NASA to produce maps of the surface of Venus.

Photo-Video

I read with interest your features on Kodak's Photo-CD and would like to add a few comments. Firstly, I think that it is quite a nice idea but rather expensive and secondly, I can think of a cheaper and far more efficient way of doing the same thing.

Since the quality of the screen image is limited by the resolution of the TV, the best quality result can never be better than that of the TV screen. What I suggest is to use a video recorder and a camcorder. Photographs taken with the camcorder lasting up to 30 seconds can be stored in sequence on the video recorder. By using the still frame feature of the VCR, up to 1080 pictures can be stored on a 180 minute cassette tape if each is there for only 10 seconds. I would think that this is easily long enough to fast forward and freeze frame on the desired image.

A though that occurs at this

point is that the above technique has been possible for the past couple of years and since I have not seen it mentioned elsewhere, there are only three reasons why it is not used. It doesn't work, nobody has thought of it before or nobody wants to bother. The last possibility seems the most likely but it could be rather upsetting for Kodak who has spent umpteen thousands of pounds developing its Photo-CD system.

A Harshaw
Birmingham

Equipment Needed

The meteor scatter feature in the June issue of Practical Electronics was most interesting. Could you possibly tell me of any manufacturer of equipment that actually enables me to use this technique to send and receive information?

M Shannon
Swansea

I'm afraid that no one here at PE knows of a suitable company. Perhaps our readers can help?

Wanted: A cable

Why is it taking cable TV so long to be installed throughout the UK? I am very keen to get my hands on it. Apparently you can get all the satellite channels and other services such as phones, and there is no interference. I thought that the cables could be laid in existing gas or water pipes by little robots.

Henry Latham
Hayes
Middlesex

The trouble, as usual, appears to be a lack of cash. The cost of installing cable is quite high as roads have to be dug up to run it past houses. Until these houses take up the option of using

cable and it becomes a viable alternative to broadcast and satellite TV in the eyes of the public, the costs will remain quite high. Hopefully, within five to ten years, cable will take over completely.

Mosquito Killer

I have noticed a lot of high street chemists selling battery powered electronic mosquito killer devices. Can PE confirm if these gadgets actually work? And if they do, how do they operate. I would be interested to know because I am going on holiday to the Isle of Skye this year and have heard the midges there are terrible.

Congratulations on the new look of the magazine.

Toby Lynch
Streatham.

PS How about a mosquito killer project?

As far as we are aware mechanical mosquito killers are quite useless. The best deterrents are vapour blocks that are evaporated in special heaters or good smelly mosquito repellents.

On-line Service


I am thinking of getting a modem for my Atari ST, so I can access on-line services like CompuServe. Please can you explain the various different baud rates and protocols. Is it worth my while buying a 9600 baud unit? - these are about £600 each, which is more than I really want to spend.

Peter Zamit
Manchester

Taking the time savings due to the higher speed and the saving in telephone bills into account, a 9600 baud modem is generally worth the extra cost - it will probably pay for itself in the long run. Take a look at our feature on page 30 for more details. ■

EASY-PC, SCHEMATIC and PCB CAD

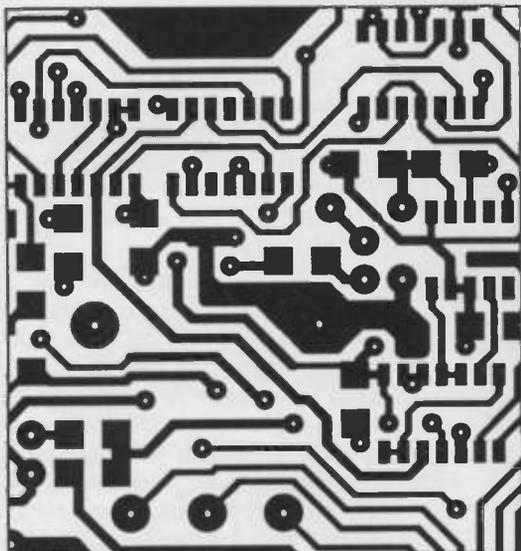
Over 12,000 Installations
in 70 Countries Worldwide!



- Runs on:- PC/XT/AT/286/386/486 with Hercules, CGA, EGA or VGA display and many DOS emulations.
- Design:- Single sided, Double sided and Multilayer (8) boards.
- Provides full Surface Mount support.
- Standard output includes Dot Matrix / Laser / Inkjet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Tech Support - free.
- Superbly easy to use.


**Still
Only
£98.00!**
Plus P&P+VAT

**BRITISH
DESIGN
AWARD
1989**

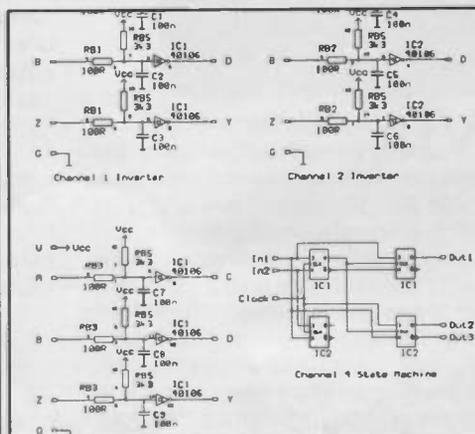


Options:-500 piece Surface Mount Symbol Library £48,
1000 piece Symbol Library £38, Gerber Import facility £98.

**DIGITAL
SIMULATION £195**

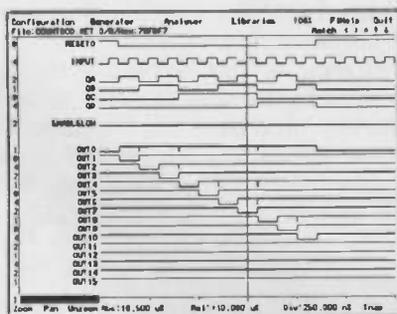


- At last! A full featured Digital Circuit Simulator for less than £1000!
- PULSAR allows you to test your designs without the need for expensive test equipment.
- Catch glitches down to a pico second per week!
- Includes 4000 Series CMOS and 74LS Libraries. 74HC/HCT libraries only £48.00 each.
- Runs on PC/XT/AT/286/386/486 with EGA or VGA.

**ANALOGUE
SIMULATION £195**

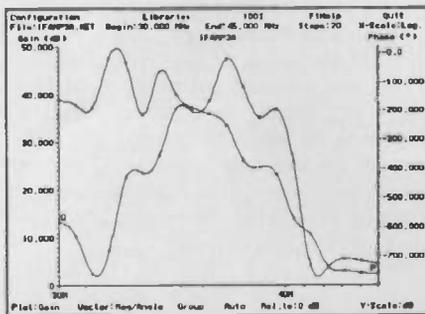

- NEW powerful ANALYSER III has full graphical output.
- Handles R's, L's, C's, Bipolar Transistors, FET's, OP-amp's, Tapped and Untapped Transformers, and Microstrip and Co-axial Transmission Lines.
- Plots Input / Output Impedance, Gain, Phase & Group Delay.
- Covers 0.001 Hz to > 10GHz
- For PC/XT/AT/286/386/486 with EGA or VGA.
- Very fast computation.

**SMITH CHART CAD
£195**

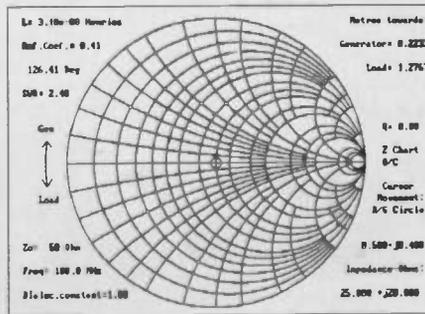

- Z-MATCH II simplifies RF matching and includes many more features than the standard Smith Chart.
- Handles transmission line transformers, stubs, discrete components, S Parameters etc.
- Supplied with many worked examples.
- Superbly easy to learn and use.
- Runs on IBM PC/XT/AT/386/486, CGA, EGA, VGA.
- Ideal for Education and Industry.

For full information, Write, Phone or Fax:-

Number One Systems Ltd. I

REF: PE, HARDING WAY, ST.IVES, HUNTINGDON, CAMBS, ENGLAND, PE17 4WR.

Telephone: 0480 61778 (7 lines) Fax: 0480 494042

International: +44 -480-61778, Fax: +44-480-494042 ACCESS, AMEX, MASTERCARD, VISA Welcome.

- TECHNICAL SUPPORT FREE FOR LIFE!
- PROGRAMS NOT COPY PROTECTED.
- SPECIAL PRICES FOR EDUCATION.



Barry Fox

Is it right to advertise something that doesn't work?

Magazines continually face a tricky dilemma. Should the advertising and editorial staff cooperate or work completely separately?

It is a no-win situation.

A science magazine campaigned against scaremongering advertisements for computer screen shields. The adverts played on the fears of pregnant women by suggesting that radiation from computers could harm unborn children. Because the magazine had a policy of independence, with no collusion between advertising and editorial staff, the magazine ran the scaremongering advert. Readers must have wondered what on earth was happening.

But readers will not trust a magazine if advertisements puffing a product "just happen" to appear on the next page from an article praising the product. This can happen if a journalist writes independent comment on a product which happens to be favourable, and the advertising staff see it the text in advance and use it as an opportunity to sell space for an advert.

As Practical Electronics has carried advertisements for a piece of equipment which is likely to make bad news, here is some independent comment and news, after the event.

"Slash your phone bills!!! 100% free dialling!!!" promises the advertiser, Top Secret Electronics of Malton in Yorkshire. "After months of legal battles we can now offer you the Creditcall from the inventors of the original Black Box".

The Black Box was a gadget developed by electronics buffs, known as "phone phreaks", twenty years ago in the US. It fooled the telephone system into giving subscribers free calls, by bleeping access codes into the handset.

"Simply plug the remarkable Creditcall into any authorised socket, then plug your telephone into the Creditcall. It works by blocking the metering pulses on the line and suppressing the charge signals" explains the advert. "Beware of inferior copies being sold in London for well over £200 - save a fortune for just £34.95

plus £2.50 postage and packing".

All these gadgets look like a modified two-way telephone adaptor (which lets two phones plug into one standard BT socket) and have a light emitting diode which glows red or green when the line is in use.

"These devices are completely, utterly useless" says BT. "They do not affect call metering in any way".

But subscribers who use them see the light glowing and make long distance calls round the world, thinking they will be free. Later they get the bill and discover they were not.

The subscriber cannot then complain to BT about the call charges because that would give BT the opportunity to prosecute on the two counts routinely used against anyone caught trying to get free calls, attempting to defraud BT and illegally using BT's electricity. The complainant would also be in trouble from admitting the use of a telephone accessory not certified by the British Approvals Board for Telecommunications.

The purchaser also cannot complain to the advertiser. Very small print at the end of the Top Secret advert warns that connection of the device is "strictly prohibited", that it must not be used "without the full consent of the telecommunications system provider" and that "the unauthorised obtaining of free telephone calls is a criminal offence".

Buried even further in the small print is a promise that money will be returned if purchasers are not "entirely delighted". The twist here is that the no-quibble, money-back guarantee carries the proviso that the gadget must be returned in "received condition". BT's engineers found that the gadget could only be used after a tag had been broken off.

Anyone applying to buy the gadget also has to sign a written declaration that they are "purchasing this unit as novelty only" and will not connect it to a telephone.

BT can recall only one previous case of comparable cheek. An entrepreneur offered subscribers a service called "Billbusters", for £7.50. It promised an end to all BT's telephone bills. Those who paid got back a letter telling them to cancel their account with BT. They would then get no more telephone bills.

Creditcall was also advertised by

leaflet with local newspapers in York and Scarborough. This led the North Yorkshire Trading Standards Officers to investigate, and see whether the adverts contravene the Trade Descriptions Acts and warrant prosecution. Other TSO's round UK are investigating other, similar, devices.

The TSO's have been working with a report produced by BT who X-rayed a Creditcall to see what was inside. BT's X-rays showed a 330Ω resistor in series with a diode (probably type 1N4001 with probable peak inverse voltage rating of around 100 volts), a capacitor of around 1μF value, and standard green LED. The LED lights only if the exchange line has incorrect polarity and the receiver is off the hook. Reverse polarity, does not necessarily cause a telephone to mis-operate.

BT's technical expert tested the device on a number of different exchange lines and found no effect on metering pulses and no effect on metered charges, either on incoming or outgoing calls.

I phoned Top Secret Electronics who insisted that that the device worked, and sent me explanatory notes. These claimed that the device blocks metering by converting BT's AC metering pulses into DC pulses. Perhaps significantly, the notes are marked "E&OE" at the bottom. They also confirm that the device is sold with a sticker tag which must be removed to use the device, and removal invalidates the guarantee.

At around the same time, the national press reported that two people in Wales had been jailed for up to eight months, and fined £6000, with costs. After just three weeks in business three hundred people had paid them £32,000 for meter-fooling sockets which did not work. The judge said that those who had bought the devices were "greedy and unprincipled, and no-one who had been fooled should be eligible for compensation".

So you have been warned. If something seems too good to be true, it probably is. There is no such thing as a free lunch. And always read the small print. ■

Ian Burley

Multimedia in no longer tomorrow's technology



I recently attended a multimedia exhibition, Multimedia '92 at Olympia, and was left with the dull realisation that the technology on show there really was going to revolutionise the way we all soak up information. I like to think I knew this was going to be the case all along, but for the first time I didn't have to imagine it. The products were there and prompting people in the industry to ask themselves how multimedia will impact on our everyday lives.

To me multimedia was, among other things, a loose collection of interesting infant CD ROM or laserdisc technologies you could hook onto your PC and amaze your friends with. You went to see multimedia at special sections of PC shows and it was fun to look at but the thought of spending some hard cash on multimedia hardware never entered one's mind.

It was tomorrow's technology.

However, this show was different; this was a show where multimedia itself dominated, not the PCs or peripheral hardware or the media formats, but the purpose and utility of the technology itself. Multimedia is no longer just a curiosity, an accessory or a fascinating hint at tomorrow's computing applications.

The emerging impact of multimedia even moved a group of information technology journalists to meet in a back room at the show to ask themselves the sobering question, does multimedia technology threaten the written word?

Multimedia is a modern day cliché, but what does it mean? The term multimedia – as has been oft-repeated – is many things to many people. For the sake of argument I define it as the ability to access large quantities of multi-format information interactively. By multi-format I mean pictures, sound, text and even motion video. Virtual reality would qualify under my definition and why not? There have been experiments with virtual reality garments like gloves which convey sensory touch. Nobody has cracked the olfactory senses yet, but I'm sure they're working on it. But I digress.

As for 'interactive' the gathered IT hacks spent a good deal of time debating what that term meant pre-

cisely, but for me it means having a degree of control over the flow of information you have access to, enabling one's responses to that information to dictate the process dynamically. This is what makes multimedia different to, say, television. TV has text, audio, pictures and motion video but it's unidirectional and certainly not interactive. But with the spread of modern interactive cable TV, multimedia will be piped straight into the home. Multimedia TV could offer real-time voting, instant selection of movies, interactive access to centralised multimedia libraries and more.

The most advanced form of multimedia I have experienced so far was a Northern Telecom telephone services demonstration. You could select which demonstration you wanted by choosing options on a touch screen monitor. One of these involved a demonstration of something similar to BT's Star Services. A video of a woman appears on the screen and she explains what is about to happen. A phone by the workstation rings, the same woman is now talking to you on the phone and she's telling you to push * and # buttons on the hand set and responding accordingly. It was surreal.

Another example is the Pandora multimedia communications project being developed jointly by Olivetti Research and the Cambridge Computer Laboratory. Pandora is an experimental video phone system using powerful workstation computers hooked into a very fast data network. You can record audio/visual messages for later viewing and editing, have one-to-one video phone conversations or conferences. You can also tune into broadcast TV, video or a CD-player, with full control over channels, track selection, stop, pause, etc. It would be a relatively trivial task to attach all sorts of multimedia information bases to Pandora.

The thrust of today's multimedia products lies in standards like CD ROM, CD-I, CDTV, Interactive Video and so on. CD ROM means at least 650 megabytes of data on a single 12cm disc. CD ROM versions of encyclopædias and other books one can loosely describe as 'educational' are obvious candidates for the multimedia

CD formats. Not only can you read the text and enjoy the pictures and diagrams you would normally find in conventional books, but you can hear things and watch them moving too. As one father who happens to be a director of a firm which makes multimedia add-ons for PCs said, multimedia technology is riveting for his kids. But so is TV – the difference is that the kids usually watch TV in a semi-stupor. Multimedia is a stimulating and educational but just as entertaining as TV.

Most important of all multimedia provides you with control. You can go back and repeat an animation sequence, the software may even be able to show the effect of some operation you can control, like the Time Life Photography CD-I disc which can show the effects of over and under exposure on a picture as you 'change' the camera settings, for example.

Instruction manuals for complex products like business software packages are now appearing in multimedia form. There's nothing more daunting than a six inch thick wad of books alongside a dozen floppy disks which need individual installation on your PC. A single CD ROM can replace all of this and by providing an interactive version of the manual on the disc a user can become proficient in his or her new software package far more quickly than before.

Given time, multimedia technology will evolve to provide us with gadgets which today's efforts can only hint at. Conventional books will seem quaint artefacts of yesterday's culture; cheap yet limited and even boring. We will be creating our own multimedia, not just buying it. Today's trends towards computer presentation graphics is just a start. Reports, letters and even children's scrapbooks could be ordered multimedia compilations.

The multimedia industry will remain confused for quite a while yet as different formats vie for superiority and the technology develops, but there's no looking back now. ■


Practical Computing

News from Anthony Robertson

Traditionally the Summer months are quiet ones for computer specific announcements. Times are changing though, the world recession has brought many computer companies to heel. Now it seems, manufactures no longer wait for computer shows to come around in order to launch new products.

Hypertec is one such company who have recently launched a booster card for IBM PS/2 users. A worthwhile power boost will prepare 80386DX based machines for a new generation of demanding software. Production versions of the new Hyperace 80486DX/33 upgrade board, can boost processing speeds by a factor of five!

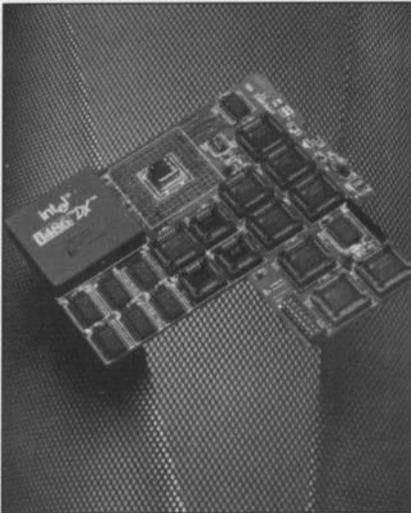In use, the unit simply plugs into the existing 80386DX



Upgrade from 80386DX to 80486DX painlessly

processor socket of PS/2 models 70 and 80. Processor replacement is actually preferable to adding a numerical co-processor to existing installations — the traditional numerical coprocessor route to increased processing speed is limited by the application in use. Replacing the 80386DX micro processor with the Hyperace 80486 based unit running at 33Mhz makes a lot more sense as the power boost will increase the performance of every software package run. This booster retails at £899. Further information can be obtained from Colin Lillywhite, Hypertec Europe Limited, on 0672-63936.

Dual Computer?

When is a laptop not a laptop? When its a desktop of course! Now before you think this columnist is going mad, let him tell you about the Cordata SX.

Many desktop owners shy away from laptop computers because of the obvious lack of expansion. If only a Laptop could remain portable and powerful for travel purposes, yet possess the facility for expansion to full desk top specifications. A pipe dream? No a reality with Cordata Technologies of Compton, California.




Two for the price of one?

The Cordata SX offers the best of both worlds being a pow-

erful 16 Mhz 80386SX portable on one hand. Yet able to integrate with a docking station to become a desktop equipped with plenty of space for expansion and additional storage.

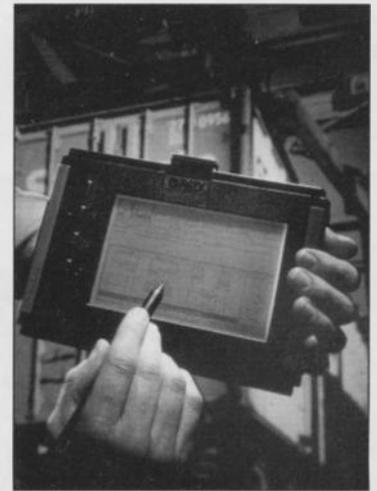Complete with a VGA LCD Screen and Super VGA graphics card, a full AT keyboard complete with detachable numeric key pad, 1Mb RAM plus 40Mb hard drive, and a 1.44Mb floppy. The Cordata SX costing £790 (exclusive of VAT) is now available in Great Britain, from UK Home Computers of Swindon, Tel: 0793-695034.



GRiD's PalmPAD wearable PC

Logitech Deal

Logitech has announced a deal with GRiD systems Corporation, a leading player in the pen-based computer market. GRiD has purchased a digitising tablet and wireless pen from Logitech to incorporate in the GRiD PalmPAD, billed as the world's first wearable PC.

The PalmPAD can be used in the hand or worn on the wrist. It can also be attached to the belt or carried on the shoulder in a durable case and is capable of withstanding three foot drops. For more information please contact Logitech on 0344-891313.

Datac's Award

Datac's new keypad for its DC Series hand-held computers has won a design award sponsored by the Membrane Switch Manufacturers Association. The keypad was entered by its manufacturers, Danielson Limited.

The Datac DC Series is specifically designed to perform



Pic 4 - caption could be - Dacom's award winner

data acquisition, storage and transmission in harsh environments, and the larger keys make it easier to operate with cold fingers or when wearing gloves. The 36 key alpha-numeric multi-function membrane has auto repeat, audio click and tactile mobile feedback, and custom designed options are available.

The DC Series comprises four models of hand-held computer, with two-or four line display with optional back-lighting and a wide range of memory sizes. For more information please contact Datac on: 061-941-2361. ■

Take the Sensible Route!

BoardMaker is a powerful software tool which provides a convenient and fast method of designing printed circuit boards. Engineers worldwide have discovered that it provides an unparalleled price performance advantage over other PC-based and dedicated design systems by integrating sophisticated graphical editors and CAM outputs at an affordable price.

NEW VERSION

In the new version V2.40, full consideration has been given to allow designers to continue using their existing schematic capture package as a front end to BoardMaker. Even powerful facilities such as Top Down Modification, Component renumber and Back Annotation have been accommodated to provide overall design integrity between your schematic package and BoardMaker. Equally, powerful features are included to ensure that users who do not have schematic capture software can still take full advantage of BoardMaker's net capabilities.

BoardMaker V2.40 is a remarkable £295.00 (ex. carriage & VAT) and includes 3 months FREE software updates and full telephone technical support.

AUTOROUTER

BoardRouter is a new integrated gridless autoroute module which overcomes the limitations normally associated with autorouting. **YOU** specify the track width, via size and design rules for individual nets, BoardRouter then routes the board based on these settings in the same way you would route it yourself manually.

This ability allows you to autoroute mixed technology designs (SMD, analogue, digital, power switching etc) in **ONE PASS** while respecting **ALL** design rules.

GRIDLESS ROUTING

No worrying about whether tracks will fit between pins. If the track widths and clearances allow, BoardRouter will automatically place 1, 2 or even 3 tracks between pins.

FULLY RE-ENTRANT

You can freely pre-route any tracks manually using BoardMaker prior to autorouting. Whilst autorouting you can pan and zoom to inspect the routes placed, interrupt it, manually modify the layout and resume autorouting.


BoardRouter is priced at £295.00, which includes 3 months FREE software updates and full telephone technical support. BoardMaker and BoardRouter can be bought together for only £495.00. (ex. carriage & VAT)




tsien

Tsien (UK) Limited
Cambridge Research Laboratories
181A Huntingdon Road
Cambridge CB3 0DJ UK
Tel 0223 277777
Fax 0223 277747

All trademarks acknowledged

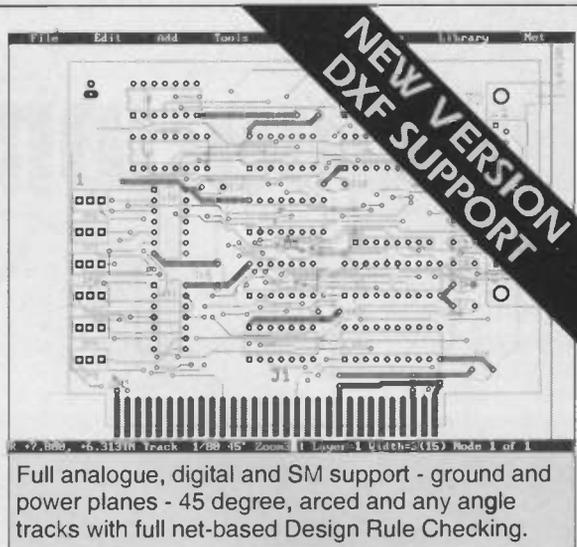

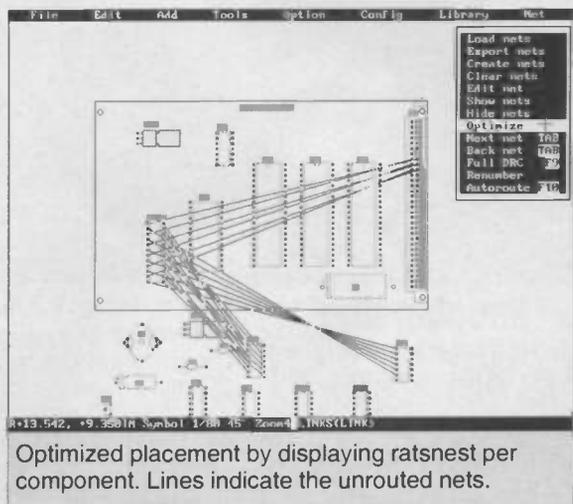Full analogue, digital and SM support - ground and power planes - 45 degree, arced and any angle tracks with full net-based Design Rule Checking.



Optimized placement by displaying ratsnest per component. Lines indicate the unrouted nets.

HIGHLIGHTS


- Net list import from OrCAD, Schema etc.
- Graphical and manual netlist entry
- Top down modification for ECOs
- Forward and back annotation
- Component renumber
- Effortless manual routing
- Fully re-entrant gridless autorouting
- Simultaneously routes up to eight layers
- Powerful component placement tools
- Copper fill
- Curved tracks
- Extensive Design Rule Checking
- Full complement of CAM outputs
- Support and update service
- Reports generator
- Gerber, PostScript & DXF output
- Full SMD support

Don't just take our word for it. Call us today for a FREE Evaluation Pack and judge for yourself.



Innovations

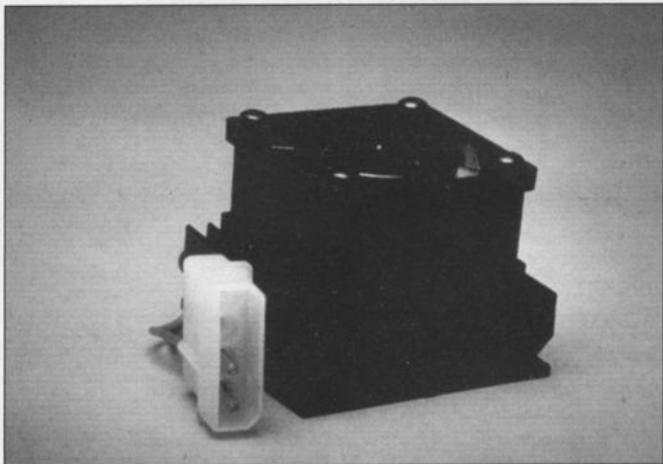A roundup of the latest happenings in the wide world of electronics, science and technology.



Keeping Kool


Installing an Intel 80486 microprocessor in a computer is not as simple a task as it might seem. Because of the chip's high speed, especially the 486-33 and the new DX2s, it is able to generate a lot of heat – a surface temperature of 76.8C was measured on one 486-33 after an hour of operation. Unless special precautions are taken the life of the processor can be reduced and the machine will throw up inexplicable errors and even crash unexpectedly.

The solution is to put in a more effective cooling system such as CPU Kooler from PCubid Computer Technology which keeps the surface temperature of the chip only 5.6C above the ambient temperature inside the computer's case. The device attaches to the top of the microprocessor and consists of a small fan and a finned heatsink. Power for the 12V motor is derived from a spare floppy disk drive connector available in most PCs. Alternatively, a 5V version is available for direct connection to the main board power supply.


The manufacturer of the

Kooler, PCubid, found that a number of requests for the device were from people who thought they had purchased new 50MHz 486DX50 machines. On removing the heatsinks from the microprocessor chips they discovered that, in fact, they were DX2-25/50. These run at 50MHz internally using Intel's speed doubling technology but the rest of the system, the bus, memory and so on, runs at 25MHz. Unfortunately, most PC speed test programs will say that such a system is indeed a 50MHz machine because the timing programs run within the on-chip cache memory and don't need to access the slower board memory. The lesson from this is that when buying a 50MHz 486 PC, make sure the whole thing is 50MHz and not just the insides of the microprocessor. ■

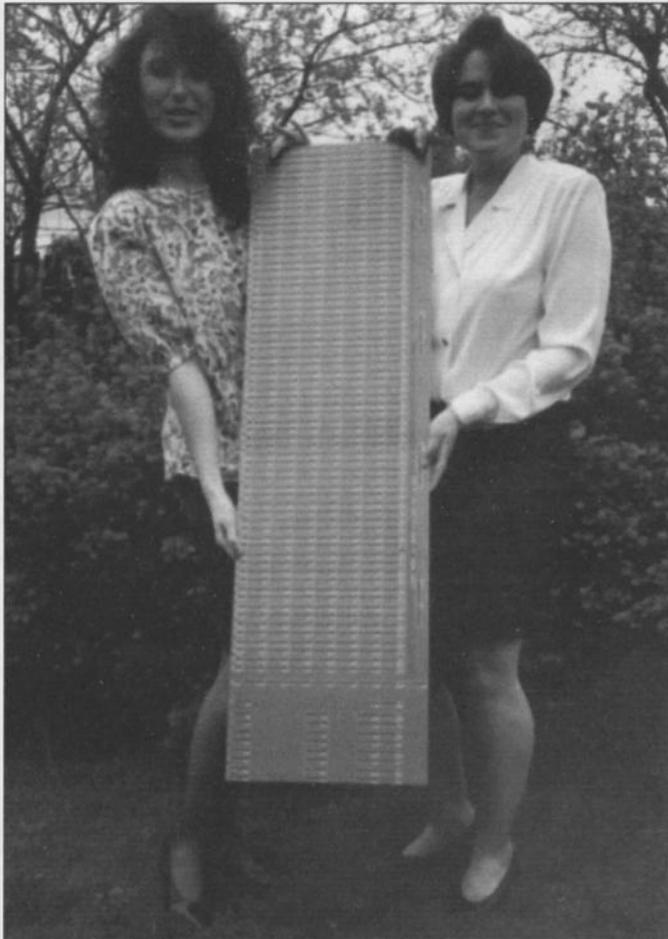The Cyrix Cx486SLC microprocessor announced in the June edition of *Practical Electronics* has found its way into the portable computer market already. The Wyse DecisionMate 486SLC costs £1555 with 4Mbytes of memory and an 80Mbyte hard disk drive. Wyse: 0734 342200 ▶



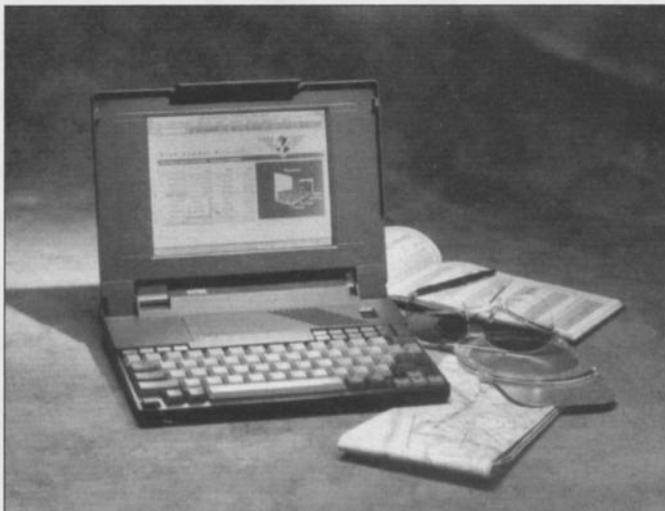▲ This plated through hole, double sided printed circuit board was produced by UK Electronics of Oldham. It measures 1219mm x 381mm x 3mm and has some 6000 connections and 100m of track. Used for a video surveillance systems, it must be among the largest PCBs ever made commercially.



In Brief


Pictures that used to be confined to PC monitors can now be displayed on a TV and recorded on video using the VGAPAL card from RDA - Tel. 0242 510760

Volunteers with some technical training who live in the London area are urgently needed by the Royal Institute for the Blind to help with the maintenance of its popular talking book service. If you can help, please contact David Finlay-Maxwell at RNIB 0484-450982 during the day, or 0484 604546 evenings.

Toshiba is to launch a new credit card sized modem for its T2200SX and T3300SL range of notebook PCs. They feature V21, V22 and V22bis as well as MNP4 and 5

Fujitsu Europe has extended its printer range with the introduction of the B100 bubble jet. Offering a resolution of 300dpi and a speed of 160cps, the machine costs £349. Contact Fujitsu Europe on 081 573 4444.

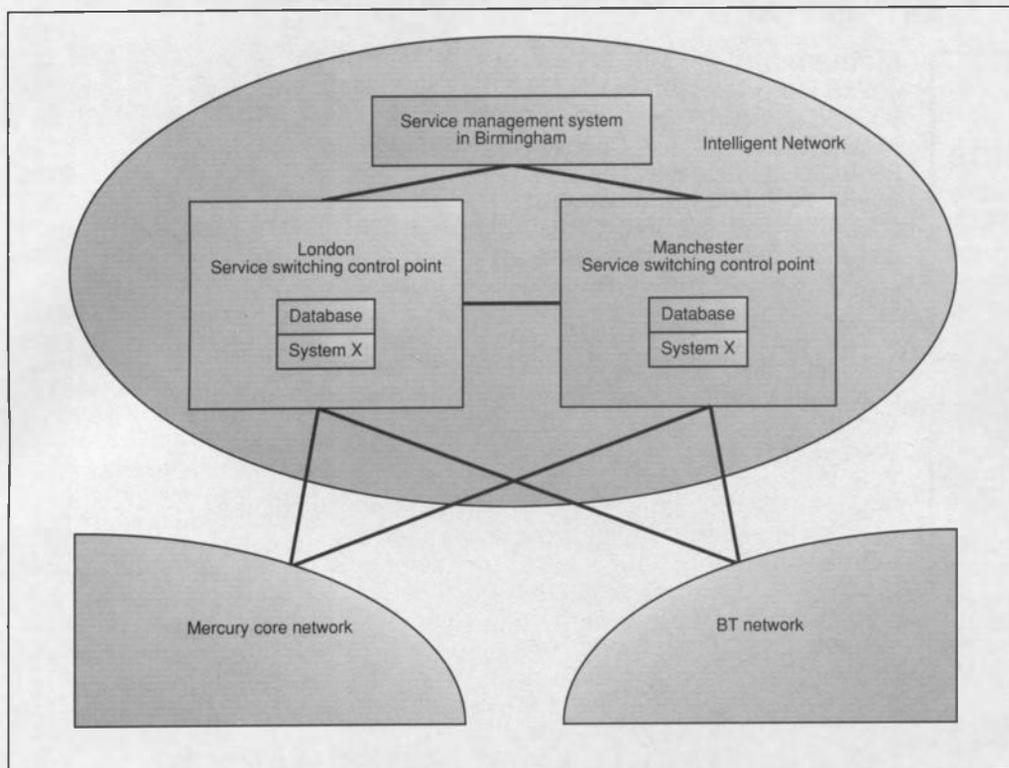Toshiba in Japan has announced reductions in the cost of its HDTV receivers. The 36in model will now cost ¥2.4 million (about £10,200) making it the cheapest in the market. Toshiba has also launched a new Hi-Vision 70in screen display unit at ¥10 million (£42,000). Since November 91, 8 hours of HDTV programming has been transmitted every day in Japan.



Mercury Communications has announced that from August, it will be using a twin computer system to control its exchanges. Used with 0500 toll free, 0645 local call and 0839, 0881 and 0660 premium rate services, the Intelligent Network automatically transfers calls to the correct number by means of a look up table.

In practice, two service

control points and central switching points are used, one based in Manchester and one in Birmingham. On receiving a premium rate, toll free or local call number, the intelligent network translates the number dialled via a pre-defined table to a "translate to" number which is where the call will eventually end up. The advantage of using tables in a computer is that their con-

tents can be changed at very short notice. They also offer facilities such as only routing calls to specific numbers at a certain time of day or day of the week, passing on the originating telephone number and making intelligent decisions on where to route calls depending upon the number of lines available at the receiving end.

The Mini EL pictured on the right is one of a number of vehicles that took part in the electric vehicle rally organised by Eastern Electricity in Ipswich. Also in the procession were one of the most modern electric cars, the LA 301 and one of the oldest, an electric lorry.

The LA 301 won a major competition in Los Angeles USA to find an electric vehicle that could be used in the city yet contribute no pollution. Designed as a petrol hybrid, the car is built along very aerodynamic lines and has a range of 150 miles.





Happy Memories

Now Available

The PC

Constructor's Choice

A new book which is the definitive guide to building your own PC. Includes chapters on choosing the best system; matching and sourcing the parts required; instructions on putting them all together including comprehensive trouble shooting and problem solving section; advice on upgrading existing machines and using second-hand parts. If you like to save money or just enjoy doing-it-yourself then this book will be an essential part of your toolkit. Only £19.95 + £2 p&p

Memories

1Meg x 9 SIMM 70ns 25.50

4Meg x 9 SIMM 70ns 109.95



Motherboards

80286 20MHz EMS on board , Up to 4Mb RAM	£72
80386SX 25MHz Up to 16Mb RAM	£99
80386DX 25MHz 32K Cache. Up to 32Mb RAM	£169
80386DX 33MHz 64K Cache	£195
80486SX 20MHz 256K Cache	£320
80486DX 33MHz 256K Cache	£475
80486DX 50MHz 256K Cache	£695

Diskdrives

5¼" 1.2Mb Floppy	£43	3.½" 1.4Mb Floppy	£36
40Mb 25Ms IDE 3½"	£149	104Mb 19Ms IDE 3½"	£229
IDE Controller for 16 bit bus. 2 x FDD & 2 x HDD	£14		
Ditto with 2 Serial, Parallel and games ports on board	£18		

Video

VGA card, 16 bit 256K RAM, upto 800 x 600 resolution	£25.00
VGA card, 16 bit 512K RAM, upto 1024 x 768	£45.00
VGA card, 16 bit 1Meg RAM, 1024 x 768 in 256 colours	£60.00
VGA paper white 14" inc. on-site warranty	£89.50
VGA colour monitor 1024 x 768 14" inc. 2 year on site warranty	£245

I/O, plug-ins, miscellaneous:

120Mb internal tape streamer (uses floppy controller)	£199
102 Key Tactile Keyboards	£24.50
MS compatible serial mouse, 9/25 pin adapter, software	£13.95
2 serial, 1 parallel & games port I/O card	£12.95
NE2000 compatible ethernet card	£75.00
Desktop or mini-tower case, power supply and all fittings	£75.00
Floor standing tower case, power supply and all fittings	£119.00
MS-DOS 5.0	£50
DR-DOS 6.0	£45.00

Carriage on Motherboards, Disk drives & Keyboards £5, Mice, Video & Controller cards, Software £3, Cases & Monitors £12 IC's free if over £20 nett, else add 75p. VAT to be added to the total. Full lists of IC's & computer parts on request.

Send orders to: HAPPY MEMORIES, FREEPOST, KINGTON, HEREFORDSHIRE HR5 3BR

TEL: (054 422) 618 FAX: (054 422) 628



New for 1992

★ New MOSFET Amplifiers

improved range of SMOS modules
30W, 30+30W, 60W, 120W

★ 20 watt Class A Amplifier

★ Low profile PCB Transformers

a range of encapsulated transformers
4VA, 6VA, 10VA, 18VA, 24VA, 30VA

Write or phone for data and prices...
which include details of standard range of toroidal transformers and audio modules.

No price increase for 1992

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL
Telephone: (0227) 375254. Fax: (0227) 365104

Service Manuals

We can supply Service Manuals for almost any type of equipment. Televisions, Video Recorders, Amateur Radio, Test Equipment, Vintage Valve, Any type of Audio Equipment, Military Surplus, etc. etc. *

All Makes and Models supplied, from the 1930s to the present.

Originals or photostats supplied as available.

FREE Repair and Data Guide with all orders or SAE for your copy.

Mauritron Services (PE)

8 Cherry Tree Road

Chinnor

Oxfordshire

OX9 4QY

Tel: (0844) 51694

Fax: (0844) 52554



Apple's Newton

Apple unveils its long rumoured Newton Personal Digital Assistant – Arthur King reports.

Apple Computer, better known for its friendly to use Macintosh alternative to the ubiquitous IBM-compatible PC, chose CES to finally own up to the consumer electronics industry's worst kept secret. Apple announced it is to use some core British technology and its computer know how to enter the consumer electronics market with an advanced pocket computer called a personal digital assistant or PDA. Apple has formed a new division called PIE (Personal Interactive Electronics) to develop PDAs and there is a formal link up with Japanese electronics giant Sharp.

Sharp will initially manufacture PDAs for Apple and also build its own versions for the Japanese market. PDA system know-how will be licensed to anybody interested enough – a departure from Apple's reluctance to open up the Macintosh computer standard.

In Apple's own words, "PDAs are digital devices which bridge the gap between personal computers and consumer electronics." The first of these PDAs is to be called Newton, an "intelligent" electronic notepad which is likely to start selling early next year according to Apple supremo, John Sculley. The target price for Newton is around \$800 (£450) or less. The notepad is designed to intelligently assist the user capture and organise information on the move. Apple is working on a number of projects which will form a family of devices all using core Newton operating technology. According to an Apple source if they don't sell millions of Newtons over the next few years the project will have been a failure.

The Newton shown at CES is a small device about the size of a filofax. It's a computer, but it doesn't have a keyboard and you can't run Macintosh or PC-compatible software on it. Instead Newton provides its user with a suite of utility programs using artificial intelligence managed



by a brand new multi-tasking operating system linked to an advanced character recognition user interface. Commands are entered by 'writing' onto the PDA's LCD screen using a stylus. The writing appears on the screen as it is written, warts and all, but as soon as Newton recognises the characters it replaces your scrawl with computer-generated translations. It's a validation system which lets the user edit mistakes immediately – if you write the name "Graham" and "Granam" is returned – you just replace the 'n' with an 'h' using the stylus.

Newton also features an intelligent natural language command parser. The example given was that if you scribble "lunch Jane Thursday" as a schedule the Newton system translates this into a command sequence which equates to a lunch appointment with somebody called Jane at noon on the following Thursday. It will then delve into its database and suggest a particular "Jane" and ask

you to verify the entry.

Character recognition is nothing new, but it is usually slow and cumbersome in operation, often because portable battery powered computers which offer the facility don't have enough processing horsepower to do the necessary computation.

This is where that British technology comes in. Newton uses a UK-developed RISC (reduced instruction set computer) microprocessor called ARM, which is short for Advanced RISC Machines. ARM Ltd is a spin-off company from Acorn Computers, which was originally responsible for the design of the BBC Micro. Apple and Acorn have an equal 46% share in Cambridge-based ARM Ltd, with the remainder owned by the US chip manufacturer, VLSI Technology.

The ARM processor used is the new 610 model

which comes from the same family of RISC processors originally designed in-house by Acorn to power the Archimedes workstation range. It's a 32-bit chip which delivers 15MIPs (million instructions per second) of processing power at a clock rate of 20MHz. This is significantly more powerful than an equivalent Intel 486 processor, which top-end PCs currently employ. Unlike the Intel chip, and other RISC chips for that matter, the ARM610 uses very little power – less than that used by a modest torch bulb according to Apple. Being small and relatively simple in design, ARM chips are very cheap too.

The tie-up with Apple is a coup for struggling Acorn which has not found it easy to sell its technically more advanced ARM-based workstations against industry standard PCs in its key education and hobbyist markets. Acorn's share price had rocketed by 500% by the time Newton was announced officially. ■

Summer CES In Chicago

The first of two reports from Ian Burley looks at the latest DCC, widescreen TV, digital watches that sense gravity and an LCD fish tank.

Practical Electronics regularly covers the consumer electronics scene in the States. This usually focuses on the twice-yearly Consumer Electronics Show (CES) which alternates between Las Vegas (winter) and Chicago (summer). Here is the first of a two part report on this year's Summer CES in Chicago.

Traditionally, CES is a trade-only event but to boost the declining summer event this year, the public was allowed in for the first time over the final two days. The audited figure for public attendance was over 90,000 in that period, a respectable figure but it didn't seem too busy.

The average punter was probably left feeling suitably dazzled by the exhibits, but the gaping holes this year's Summer CES line up certainly disappointed me. No less than JVC, Sony, Sanyo, Canon and Fuji, among others were missing from the main show floor. In fact



DCC gets the hard sell in Chicago.

Sony had a large number of new products (which we will cover next month) but was content to operate a mini-show out of its new downtown Chicago showrooms. A big surprise was the non-appearance of

Commodore and CDTV. The computer company's CDTV multimedia system was launched in Chicago in a blaze of publicity just two years ago. Commodore's absence combined with the accelerating prominence of Philips' rival CD-I must place a big question mark over the future of CDTV.

However, Panasonic/Technics, Toshiba, Sharp, Casio, Apple and most notably of all, Philips, were left to happily dominate. Philips probably deserved first prize for the biggest and most accessible stand with some of the most interesting leading edge technology on display- Digital Compact Cassette (DCC) and CD-I, including continuous demos of CD-I full motion video (FMV) (see PE last month for CD-I launch feature). However, Apple probably stole Philips' thunder with the out of show announcement of the Newton Personal Digital Assistant.

DCC was first shown at CES 18

Technics' RS-DC10 takes DCC cassettes.





RCA sports some wider screens.

months ago in Las Vegas. To recap, DCC is a digital audio tape format which Philips has developed from the ubiquitous analogue audio cassette which has been around for over twenty years. DCC decks can play both the new and old kinds of tape, a major advantage over Sony's failed DAT format. Philips' clever digital heir apparent to the compact audio cassette realm is just about ready to roll. DCC decks should appear in US stores in October. Initially these will be mainly high-end models from Philips and Technics. The former will sell for around \$600 (£335) while Technics fits in higher up at the sub \$1000 (£560) level. Philips subsidiary, Marantz, is will also introduce DCC decks this year.

The prices are disappointingly high, but we can probably expect price cutting near to Christmas. It's interesting to note that that Sony aims to launch its rival MiniDisc system at roughly the same time but is clearly targeting the lower cost portable/walkman market which Philips will turn its attention to later. Don't forget they have cross licensed their respective DCC and MiniDisc technologies. Philips demonstrated in car DCC players, a market DCC's designers took very seriously with tough high temperature cassette specifications, but in-car DCC won't be available until next year. Both BASF and Panasonic announced the imminent production of blank DCC cassettes.

16:9 aspect ration wide screen TVs were much in evidence this year. Panasonic, Toshiba, Philips

and Thomson RCA all showed wide screen models, though none of these are compatible with high definition TV (HDTV) broadcasts. US Federal authorities still have to choose a winner in the HDTV race and it's likely to be a couple of years yet before any serious HDTV broadcasting happens.

Instead the punters were being introduced to the delights of watching wide screen video versions of their favourite movies or footage from an increasing number of camcorders which offer a wide-screen recording option. Toshiba even featured a battery of its widescreen sets, each TV dedicated to a repeated showing of a full length wide screen version of a recent feature film. If that wasn't enough, the Batmobile from the recent Batman movie was parked conveniently close by.


Staying with televisions, Panasonic was showing off its new

SuperFlat tube which is claimed to be 30% less curved than first generation FST (flatter squarer tube) televisions. The new tubes have a claimed 46% improvement in contrast and an extra dark screen. A barium coated I-cathode electron gun is supposed to last longer and has improved edge focussing. Panasonic says its SuperFlat tubes can display resolutions up to 750 horizontal lines. This is in high resolution monitor territory and almost double the resolution of hi-band or S-VHS video. Some models have enhanced audio specifications which makes them more at home in a HiFi catalogue - dbx noise reduction and an onscreen graphic equaliser plus stereo surround sound decoding. Panasonic also offers twin-tuner sets which no longer need a video recorder tuner to feed the picture in picture facility. Then there's a fuzzy logic picture controller which continuously monitors the display and is capable of adjusting the contrast of one particular area of the screen.

Casio had one of the bigger stands at CES. The firm's two main attractions this time were its SF-R20 Executive BOSS personal organiser and a new divers' watch with electronic depth sensing. The SF-R20 BOSS is Casio's most ambitious personal organiser to date. 256K memory is supplied as standard and an

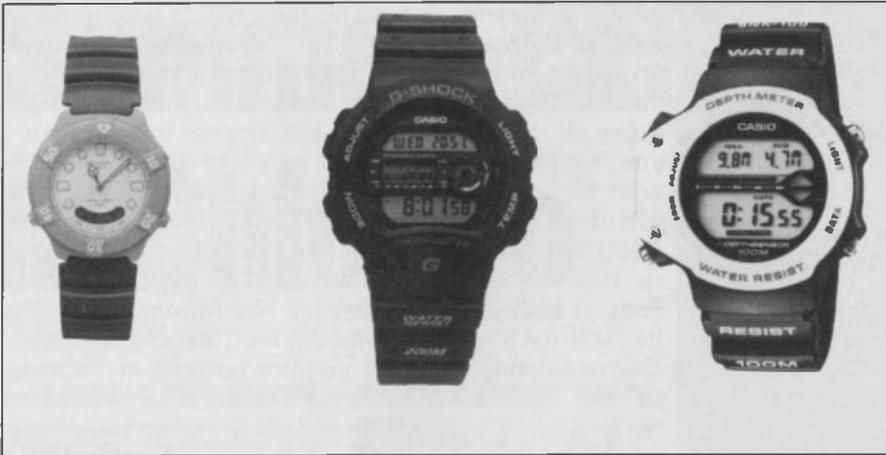Casio's 256Kbyte Business Organiser Scheduling System.





Also from Casio: left a ladies watch, centre the G-shock model and right, the diver special.


extra 256K can bring total capacity up to half a megabyte. A Lotus 1-2-3 compatible spreadsheet is built in and the various standard utility programs can be windowed on top of each other on the 40 character by 10 line LCD screen. The \$450 (£250) Casio is about as far as you can get without actually qualifying as a pocket PC. A link up kit to exchange data with a PC or Apple Mac is an optional extra. It's serious competition for Psion's Series III organiser which has had rave reviews in the States.

From the company which brought you the wristwatch heart and blood pressure monitor, or the wristwatch weather station, how about the 'Depth Meter' or 'G-Shock' watches? Casio describes its Depth Meter watch (model SNK-100-9V) as a dive computer on your wrist. A built in sensor can tell you how deep in the water you are and it can remember the deepest you went as well as the duration of your dive. The \$130 (£72) watch has a depth limit of 100 metres. If you want to go deeper, you may have to settle for Casio's G-Shock watch (model DW-6100-1V). This \$90 (£52) watch forsakes the depth sensor for water resistance to 200 metres and offers a simpler temperature sensor.

Sharp always offers an interesting pause during one's voyage through the the CES technology archipelago. Once again Sharp was showing its active matrix colour LCD prowess by feeding a scattered selection of wall-mounted screens with a stunning tropical aquarium view. I'm sure some of the visitors to Sharp's stand thought they were looking at the real thing. Less convincing was Sharp's colour LCD 'museum' display.

Hinting, perhaps, at what is to come with its recently announced collaboration with Apple on the Newton project, Sharp showed a much less ambitious yet impressive enough pen-sensitive personal organiser, the OZ-9600 Wizard (known as the IQ in the UK). The 9600 features a 320 by 200 pixel touch screen (up to 53 characters by 30 lines) but there's also a mini-QWERTY keyboard. The screen, which can sense fingertips as well as pens or styli, offers a multi-tasking and graphical user interface (GUI) complete with icons and windows. Unlike more advanced pen-input computers, the 9600 can accept scribbled input via the screen but there is no attempt to recognise written characters or diagrams.

Sharp's LCD fish tank.

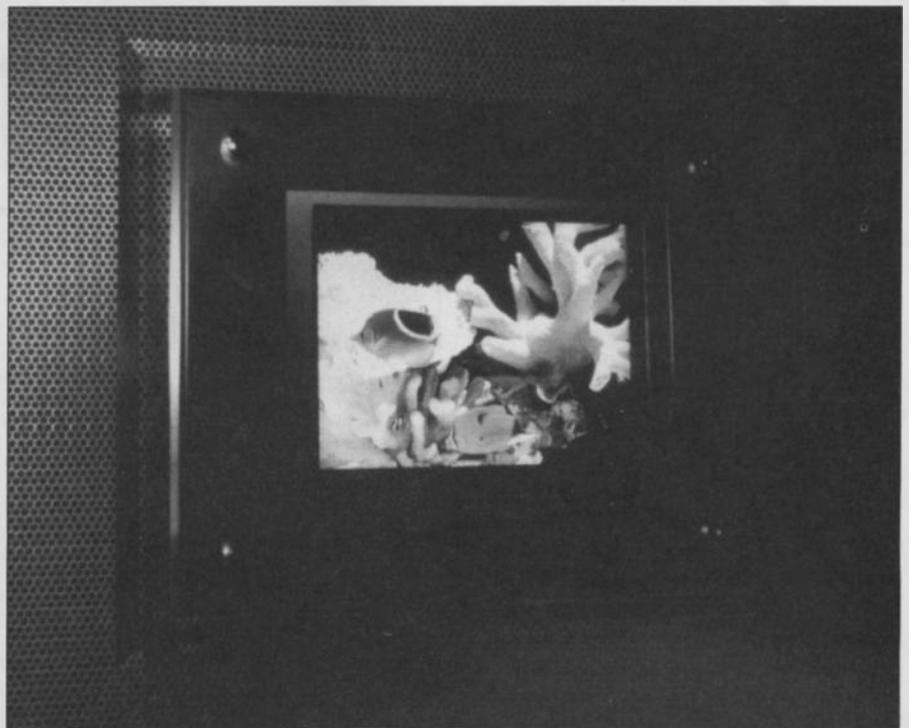

They are simply stored as graphical notes for later perusal by the user.



This has to be the simplest form of so-called electronic notepad. It's actually not-as useless as it sounds. By managing where the scribbled information is stored, you have the convenience of a notepad over a keyboard and the vestiges of a database system. Utility programs include a calendar, to do list, three phone directories, business card directory, word processor, scrapbook, outline processor, calculator and a world clock. 256K memory is built in, the contents of which can be backed up to a removable memory card in just five seconds. Another feature of the 9600 which mirrors the Apple Newton is wireless communications. Files can be exchanged with external computers via optional infra-red transmitter receivers. Terminal software is also provided for modem connections to electronic mail services. The OZ 9600 won't be on sale until the end of the year and Sharp wasn't speculating on prices at the show.

That's all we have space for from CES this month. Next month we complete our CES roundup with a glut of new products from Sony and AT&T, plus a look at the US videogame price war and moves at the show to publicise digital audio broadcasting and interactive cable TV. ■

CRICKLEWOOD

ELECTRONICS

1992 CATALOGUE

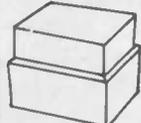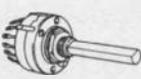 BOOKS	 BOXES & CASES	 CABLE & WIRE	 CAPACITORS
 CONNECTORS	 KITS	 RESISTORS	 SEMICONDUCTORS
 SPEAKERS	 VIDEO HEADS	 SWITCHES	 TOOLS & TEST GEAR



COMPONENT CATALOGUE.
ONE OF THE BEST
RANGES AVAILABLE

NAME

ADDRESS

.....

POSTCODE

CRICKLEWOOD ELECTRONICS LTD, 40 CRICKLEWOOD BROADWAY
LONDON NW2 3ET. TEL 081 450 0995, 081 452 0161 FAX 081 208 1441

Advertising Index

BK Electronics	IBC
Bull Electrical	36
Cricklewood	17
Greenbank Electronics	40
Happy Memories	12
International Correspondence School	40
Jaytee Electronics Services	12
Labcenter	27
M&B Electrical	43
Mauritron	12
Number One Systems	5
Oakleaf Technology	40
Seetrax	17
Silica Systems	OBC
Suma Designs	IFC
Tsien	9

LOW COST RANGER1 PCB DESIGN FROM SEETRAX

- Circuit Schematic
 - Circuit Capture
 - PCB Design
 - Host Of Outputs
- All-In-One Design System**

REDUCED PRICE!

£100

Fully Integrated Auto Router

£50

Ask Us About Trade-In Deals

Call Now For Demo Disk on 0705 591037

Seetrax CAE • Hinton Daubnay House

Broadway Lane • Lovedean • Hants • PO8 0SG

Tel: 0705 591037 • Fax: 0705 599036

What The Press Said About RANGER1

For most small users, Seetrax Ranger1 provides a sophisticated system at an affordable price. It is better than EasyPC or Tsien's Boardmaker since it provides a lot more automation and takes the design all the way from schematic to PCB - other packages separate designs for both, that is, no schematic capture. It is more expensive but the ability to draw in the circuit diagram and quickly turn it into a board design easily makes up for this.

**Source JUNE 1991
Practical Electronics**

Pay by Visa or Access



New Product Developments

Ian Burley looks at Sharp's latest IQ, Vortec and Olivetti's A5 computers, a new form of image enhancement and the world's smallest hard disk drive..



The World's smallest hard disk drive

Hard Disc In A Matchbox

Hewlett-Packard has announced Kittyhawk, the world's smallest yet hard disk drive mechanism – its glass platter is just 33mm in diameter and HP had to work with watch specialists Citizen in order to tackle the challenges of the unit's miniaturisation. US telecommunications and computer giant AT&T was also involved in the development of Kittyhawk.

Kittyhawk, which Hewlett-Packard describes as a Personal Storage Module (PSM), has a data storage capacity of just Over 20 megabytes yet the drive weighs less than a single ounce. Dimensions are 10.2mm high, 51mm deep and 36.6mm wide. HP expects that within a couple of years the capacity of future Kittyhawk versions could reach as much as 200

megabytes through the continued development of super-flat and rigid glass disk platters. Rival 1.8in hard disk drive technology which looked

so impressive when it was introduced last year now looks obsolete, though these larger drive formats (including 2.5in drives) could survive through lower cost. At this level the smaller you get the more it costs to make the mechanisms, initially at least.

There are several other benefits inherent with tiny dimensions. Kittyhawk can withstand comparatively large levels of physical shock because all the components are very low in mass. HP says a Kittyhawk will survive a drop of three feet and can withstand ten times more shock than 1.8in and 2.5in mechanisms. A specially developed chip prevents head crashes by sensing when one may be imminent and lifting the head clear. The drive only consumes 1.6 watts of power in typical operation, falling to 15 milliwatts in sleep mode. AT&T's contribution to the project was to reduce the 18 or so chip count of typical mini hard disks to just seven.

HP sees Kittyhawk drive tech-

Improved images





nology as a serious challenge to other compact solid state data storage mediums like flash memory. The latter remains relatively expensive in high capacity configurations at around \$50/megabyte while Kittyhawk will offer a cost of approximately \$12/megabyte. 33mm drives are ideal candidates for the next generation PCMCIA expansion card standard which is based on very slim credit card sized devices.

Fractal Enhancement

Following up its highly impressive hardware based Fractal Transform image compression system last year, Iterated Systems has now released a software-based compression system and unveiled a new Resolution Enhancement technology based on Fractal Transform techniques.

Fractal compression systems convert complex image components into compact mathematical formulae which take up very little space compared to the original data, typically as little as 1% of the original. Hardware acceleration was originally required to make the compression process fast enough for volume applications, but Iterated Systems has since produced a

The Comfax ad-on for the IQ.

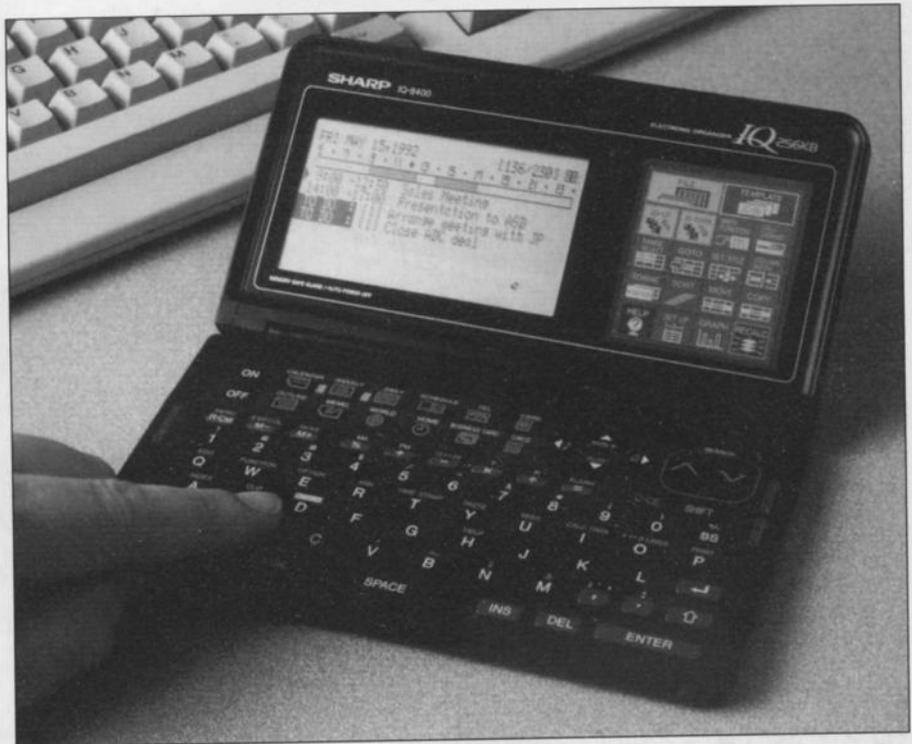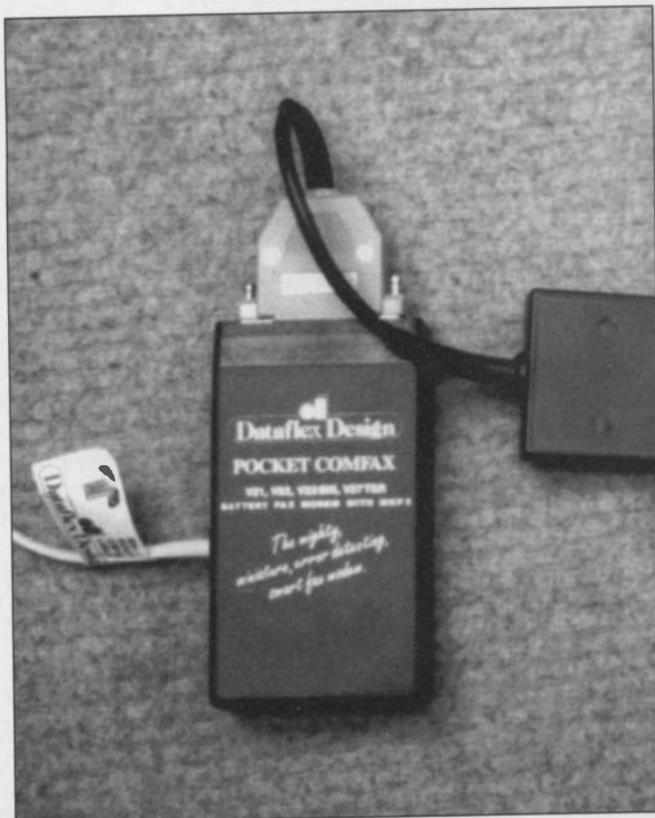

The Sharp IQ-8400

Microsoft Windows software-based compressor aimed at users who can't justify the cost of the PC card solution. Although compression is time consuming, decompression of FIF data (Fractal Image Format) is relatively fast and so doesn't require hardware acceleration.

A criticism of fractal compression by users who require very high quality images is that the compression process is not 'lossless' and side by side image comparisons before and after compression reveal tiny but visible discrepancies. Iterated's new Resolution Enhancement technology is a lossless system which improves the quality of displayed images considerably and is ideal, according to Iterated, for use with desktop publishing. Iterated Systems Ltd: Tel.0734 880 261.


Sharp Raises Its IQ

A new flagship model has been added to the Sharp IQ personal electronic organiser range. The new IQ-8400 has improved utility software and enhanced communication facilities. New 'To Do' and 'Daily Schedule' functions have been added along with a VT-100 scrolling text terminal facility for use as a terminal via a suitable comms device like a modem.

The 290g IQ-8400 has a 40x8 character LCD screen capable of displaying pixel graphics. 256K RAM is built in, with 234K available to the built-in applications which include a To Do reminder, Calendar, Scheduler, Telephone directory, Memo, Outline processor, Business Card database and world time clock. Facilities available via plug-in IC program cards are accessible by touching a labelled screen on the IC card window - which Sharp seems to think is a 'touch screen' feature.

A nice touch is that the scheduler has a bar chart function to indicate your plans for the next 24 hours. The chart is accessible from a two month calendar display which can itself indicate up to three planned activities against each date.

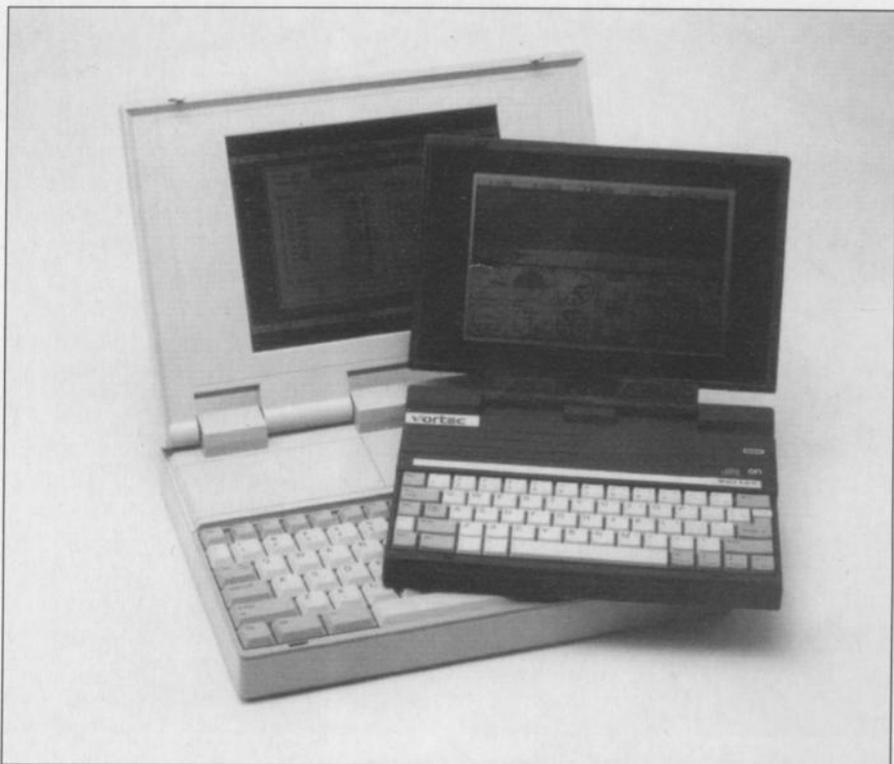You can connect your IQ-8400 to other IQ organisers via a special cable and transfer data between the two. Sharp also supplies an option-



The new A5 size Vortec.

al Dataflex Pocket Comfax pocket modem for fax transmission of prepared messages as well as data comms using the VT-100 terminal emulation. The IQ8400 can also be hooked up to an IBM PC compatible or an Apple Macintosh.

The Sharp IQ-8400 is priced £259 and looks set to give Psion's excel-

lent Series III Organiser a run for its money. Sharp UK: Tel.061 205 2335.

Half Pint Computing

So-called Notebook computers which took no more desk space than an A4 sheet of paper took the PC world by storm three years ago. A4 seems small, but if you've ever


used an A4 notebook you will probably agree they're far from pocketable and can be surprisingly bulky. So how about an A5 portable computer - half the size of the original A4? Two large corporations, Olivetti and Samsung/Vortec, recently unveiled their A5 PCs to kick off what could be a very lucrative market. PC compatibility and A5 dimensions may lump the Olivetti's Quaderno and Vortec' Booklet PC together, but in reality they offer quite different approaches.

The 1kg Quaderno is equipped with a relatively modest NEC V30HL processor. This puts it into the slower PC/XT class. The Quaderno is not designed for running processor hungry application like Microsoft Windows. However, you do get DOS 5.0 in ROM and a 20Mb hard drive, conveniently accessible personal management software applications and a voice memo recording function. Olivetti's marketing message is that the Quaderno has been designed to allow its owners the freedom to write, record, develop and transmit ideas, thoughts and decisions in any place at any time. In other words it's a grown up personal electronic organiser-come-dictaphone rather than a tiny desktop PC. A file transfer utility operating via the serial port is provided for exchanging files with another PC, like a desk-bound model.


The voice facility is an interesting feature which more PCs are now offering as standard - including the new entry-level PC range recently announced by Compaq. You can digitally record a message via a built in microphone and integrate voice files into text documents as voice annotations. The audio is recorded into files on the hard disk and can be manipulated using record, play, stop, pause and fast forward/rewind controls.

Up to eight hours of use can be squeezed from the rechargeable battery pack, which is exchangeable for six standard AA penlight batteries should you be caught short. There is also an optional car cigar lighter adaptor.

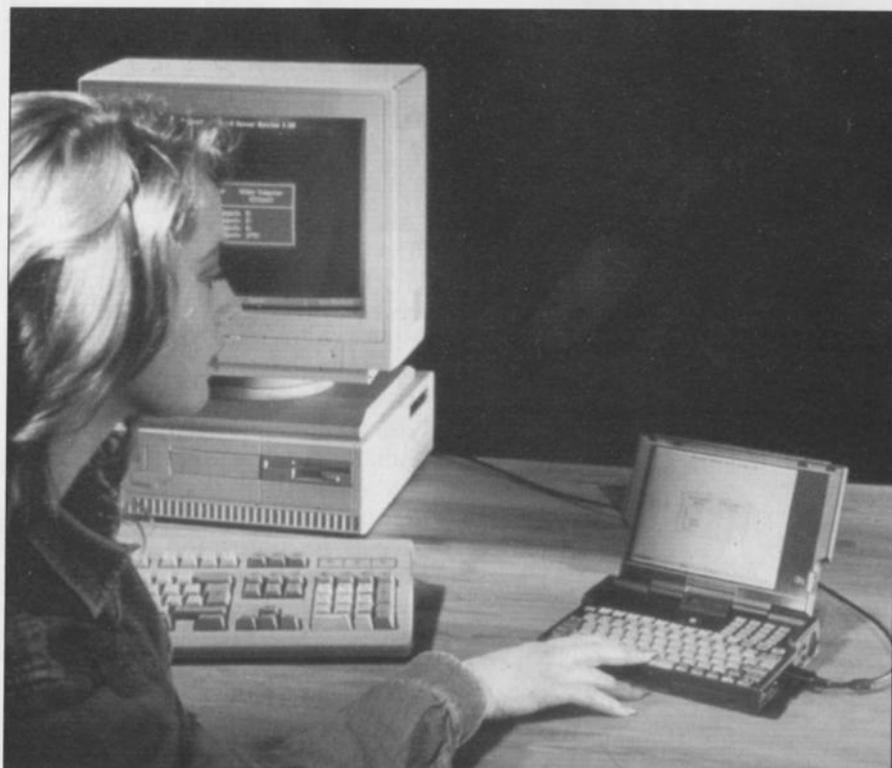1Mb RAM is standard and the DOS is stored in a 512K ROM. There is a single PCMCIA IC card expansion slot which can be used for solid state memory storage. There is no space for an integral



The Olivetti Quaderno.

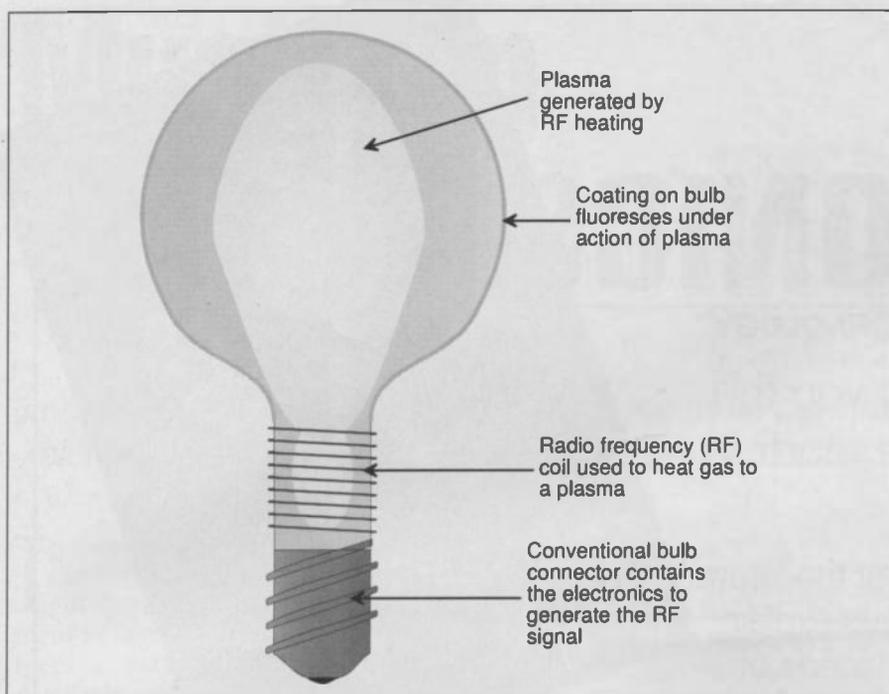

Artist's impression of the E-lamp.

3.5in floppy drive, but an external one is available. The screen used is a 7in LCD giving a 640x400 (EGA) resolution in 8 shades of grey.

In traditional Olivetti fashion, the Quaderno has had some decent industrial design applied to its case and the work of Mario Bellini has produced a stylish looking product. The Olivetti Quaderno is priced £699+VAT.

Vortec has taken another route entirely to its A5 PC solution. The Booklet PC, which also weighs 1kg, has a 16MHz lower power consumption version of the ubiquitous 286 processor. This means you can run Microsoft Windows on the Booklet without serious problems if you really must. A 40Mb hard drive (2.5in mechanism) is standard and options go up to 80Mb. 2Mb RAM is fitted. The screen is similar to the Quaderno's offering 640x400 resolution in 8 greyscales. All this extra power has to be paid for somewhere and with the added factor that the Booklet takes just five AA batteries (alkaline or rechargeable) compared to the Quaderno's six, it's not too surprising that battery life is just four hours compared to the Quaderno's claimed eight hours.

As with the Quaderno, you have to make do with an external floppy drive. A level II PCMCIA IC card slot is fitted to take memory cards or the latest miniature card modems or network adaptors. DR DOS 6.0 is stored along with the BIOS code in internal flash memory. Not only

does this free up hard disk space and reduce the number of power-hungry hard disk accesses required, but DOS or BIOS upgrades can be installed without physically removing any chips. Personal management software is provided with the Vortec Booklet PC, but there is no voice recording system. The Vortec Booklet PC starts at £1599+VAT.

What we have here with the Vortec is a valid attempt to squeeze the dimensions and functionality of a desktop PC into A5 dimensions while avoiding some of the limitations of true pocket PCs like Sharp's PC3000 or the Poqet PC – neither of which have hard disk drives, for example. The Quaderno on the other hand is more like a very advanced personal organiser which has assumed PC-like functions. The two products differ sharply in price and expected application – definitely a case of different horses for different courses.

Olivetti: Tel.081 785 6666

Vortec: Tel.081 862 9311

Tuning Into Light

When someone promises to revolutionise something as basic as the common light bulb, they're bound to generate a lot of excitement. The spotlight has been shining brightly recently on California-based Intersource Technologies which is claiming that it has perfected a viable and economical replacement

to the ageing and inefficient tungsten filament light bulb.

Intersource's new lighting device, dubbed the E-lamp, uses a high frequency radio signal to excite a gas enclosed in a glass globe. The gas becomes a plasma which makes a phosphorescent coating on the inside of the globe fluoresce and so emit light. Power consumption is about a quarter than of an equivalent brightness conventional light bulb and an E-lamp will never suddenly conk out. As it ages, an E-lamp will simply and gradually lose its brightness. An operating life fourteen times that of an ordinary light bulb is claimed too. That is supposed to equate to a typical life span of about 20 years. An E-lamp can be switched on and off instantly and can be dimmed – two key advantages over the currently available alternative efficient light sources which are compact fluorescent tubes. It's no surprise that an E-lamp is likely to be quite a bit more expensive to buy than an ordinary light bulb, but it should be cheaper than alternative fluorescent units which still usually cost over £10.

During the 1980s fluorescent replacements for conventional filament bulbs were also heralded as a major breakthrough, but the high purchase cost has deterred would-be buyers even though they are cheaper in the long run. The E-lamp is less bulky, works more like a conventional bulb and promises to be cheaper than a fluorescent replacement. Success must be guaranteed, or is it? The cynics, some of whom happen to be big producers of conventional light bulbs, say they are worried about the possibility of radio frequency interference (RFI) and there is still some anxiety that the price is still too high to woo buyers away from cheap and cheerful conventional light bulbs. Intersource is confident that it can answer its critics and has the multi-million dollar backing of Columbus, Ohio-based American Electric Power Co. which plans to be the first volume E-lamp manufacturer. We certainly haven't heard the last of the E-lamp. ■

Subscribe to

PRACTICAL **ELECTRONICS**

SCIENCE AND TECHNOLOGY

Every month we bring you the best coverage of the modern technical world.

Innovations has all the news of the latest developments, technical features explain the detail behind the glittering facade of technology, while writers such as Barry Fox, Technology Journalist of the Year and Ian Burley, Editor of BT's Prestel Micronet consumer section, analyse the growing role of electronics in everyday life. Finally, for those of you who want personal hands-on experience of design and construction, our projects offer entry level designs and advanced challenges.

A 12-month subscription is only £18 (UK), £22 (surface mail) or £39 (air mail). Concessionary rates also available. Order by credit card on 081 743 8888.

Subscribe today and book your place in the electronic future.



Send to:

Intra Press, Intra House, 193 Uxbridge Road, London W12 9RA.

Make cheques/postal orders payable to Intra Press in £ sterling.

Please subscribe me to Practical Electronics for 12 months, starting with the issue.

I enclose a cheque/postal order/banker's draft for £.....

Name

Address

Town

County

Post Code.....

Or: Please charge my VISA/Mastercard

Number

Expiry date.....

Subscription rates:

UK post - £18, Overseas surface mail - £22, overseas airmail - £39.

Discount rates:

UK BAEC/Educational concession- £16.20, Overseas BAEC/Educational concession - £19.80 (surface mail only available)

Please enclose proof of BAEC membership or educational status.

Music On The Move

In-car entertainment systems have now become an essential feature of the modern car. Kenn Garroch takes a look at some of the latest technology.

In these days of high speed, high comfort travelling on the road, a good quality in-car entertainment system is rapidly becoming a fixture rather than an extra. Available systems range from basic radios offering FM/AM tuning with output into a simple pair of stereo speakers, to high power CD/Radio/Cassettes with a whole bundle of added extras including digital signal processing and RDS – a system that tunes the radio automatically. Indeed, some in-car systems now rival the power, quality and price of home based systems and in many ways they are easier to use.

How easy it is to use a car accessory such as a cassette player is vital in a situation where all of the driver's attention should be on the road. Any unnecessary distractions such as having to turn over a cassette or tune in to the best radio channel are to be avoided. The latest in-car HiFi systems are almost completely automatic where possible and require only a simple button press for most functions – there is virtually never any need to take your eyes off the road.

Elements

There is a wide variety of in-car HiFi systems available, from a number of manufacturers. In general, they all offer the same basic functions but usually under a variety of different guises.

Cassette systems will usually have the ability to play both sides of the cassette (auto-reverse), one after the other. Rewind and fast forward (review and cue) are also generally available as is auto-stop. More advanced systems would also offer Dolby B and C noise reduction, auto programme search and blank skip, high quality cassette heads and metal/CRO₂/normal biases. In some ways, the cassette player is now the simplest unit in the system.

Unlike cassettes, car radio systems have become much more sophisticated over the past few years with the introduction of RDS (Radio Data System). In the bad old days, car radios had to be tuned by turning a knob until the desired program was found. More up-market systems had mechanical push-buttons that could be programmed to preselect stations.

The introduction of FM broadcasts on a European wide basis with increased quality of reception has led to the problem that only small areas defined by the 'line-of-sight' are able to receive a signal from any one transmitter. Neighbouring transmitters have to use different frequencies otherwise interference would ensue and reception would be impaired. For static receivers, this is not too much of a problem – once the programme has been tuned to a preset, it need never be changed. In a moving vehicle the radio must be re-tuned every so often to keep on listening to the same station.

RDS provides a solution to the problem of retuning by transmitting a data signal along with the regular programme. This can be used to tell the radio where the next frequency is for a particular service. The radio can then automatically tune to the next strongest signal when the current one gets too weak. Of course, RDS provides a number of other services as well.

In these days of heavily congested roads, it is important to keep track of any traffic information.



The Audioline 446 offers RDS for a mere £149.99

Radio Data Systems

Until quite recently tuning into your favourite radio programme could be a fiddly business – most receivers tended to be left on one station, day and night. With the invention of RDS or Radio Data Services in the late 1990s all this has changed. An inaudible signal transmitted along with the usual mono-stereo information allows suitable radios to behave in an almost intelligent fashion.

The RDS signal is transmitted alongside the usual FM station information as shown below. Mono receivers tune into the mono signal and their reduced bandwidth ignores anything above it. FM stereo receivers have access to the mono and stereo difference signals. By combining the mono Left plus Right with the difference Left minus Right, adding them together gives L+R+L-R or L and L+R-L-R or R. The RDS signal is transmitted at three times the frequency of the pilot tone and can be picked up by suitably equipped FM receivers.

One of the main features of RDS is auto-tuning. Each station transmits its own unique code and for


national stations the signals are transmitted on different frequencies depending upon the area. As a car and its radio moves from area to area, the radio automatically searches for the best reception of the particular station code. An additional feature is used in local radio where moving out of range would normally stop reception entirely. In this situation, RDS radios automatically tune to a related station, usually the area's local BBC radio transmission.

Another useful feature is used for receiving travel news. Stations which transmit travel information will also send out a TP (travel Programme) code over the RDS. When a travel announcement comes up a TA code causes the radio to tune into the relevant channel. When used with the enhanced other networks (EON) feature, this can be used to interrupt other stations, cassettes, CDs or even turn the radio on.

As with all "additional extras", not all radios offer all of the functions of RDS. A list of the functions and the standard codes is shown below.

PI	Programme Identification	Each station transmits a unique code that can be used in conjunction with the signal quality to obtain the best reception.
AF	Alternate Frequencies	A list of the station's frequencies tells the radio where to look for the best signal when moving between adjacent transmitter areas.
PSN	Programme Service Name	RDS equipped radios can use this to display the name of the radio station.
TP/TA	Travel Service	When stations transmit a travel news message, the radio will automatically change channels to receive it.
EON	Enhanced Other Networks	Cross reference information to other stations providing a similar service, for example other travel news.
CT	Clock Time And Date	Accurate calendar/clock which self-adjusts for time zone changes making sure that the radio's clock is always right.
PTY	Programme Type Selection	Allows the radio to select a type of listening rather than a particular station. There are 15 types of service classification: news, current affairs, information, sport, education, drama, science, cultures, varied speech (quizzes, comedy and so on), pop music, rock music, easy listening, light classical, serious classical, other music types.
PIN	Program Item Number	The radio can monitor what is being broadcast and switch itself fully on for specific listening or to record a show. This then makes allowances for changes in scheduling.
RT	Radiotext	Information such as a cast list or the title of the current piece of music can be displayed of suitably equipped radios.
DI	Decoder Information*	Various features of the radio can be turned on and off remotely with this feature.
MS	Music/Speech*	The relative volume levels of music and speech can sometimes be very different or some people might not like listening to the DJ. This feature can be used to select the volume level for speech or music.
TDC	Transparent Data Channel	Data transmitted on the RDS channel can be downloaded to the radio.

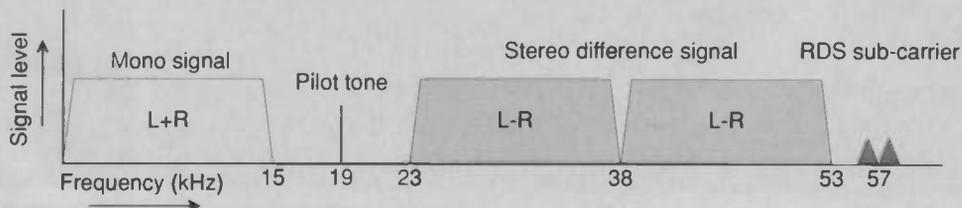RDS Features – * defines not in general use.





The Grundig WKC3880 offers RDS including full EON for £349.95

Radio stations that regularly transmit such material will also send out a TP or traffic programme code on RDS. The radio can then tune into the strongest such signal in the current area. An additional feature is the TA code which comes up when a traffic announcement is imminent. The radio can then retune, increase the volume and even switch from cassette or CD so that the announcement won't be missed. When used in conjunction with EON, the radio can tune into traffic announcements even when not listening to a TP station. RDS has totally revolutionised the way in which car radios can be used.

The other item in the car HiFi is the CD player. These can either be fitted on the dashboard and play discs in the usual way – shove them in and press go – or a multiple unit can be placed in the boot. This option adds to the security of the system as it cannot obviously be seen in the car. It also allows up to 12 discs to be stored in the player and any track from any disc played by remote control from the dashboard. The high quality and general overall ruggedness of CDs makes them ideal for in-car use. The only drawback is that should the car go missing (presumed stolen), a whole

twelve discs go with it, as well as the player.

Amplifiers

One thing that is unmistakable about car HiFi systems is that they are getting louder. Up to 400W of power is now easily available by means of a separate amplifier. Usually, this is spread between a number of speakers in the car which can be made up from small tweeters, mid-range, woofers and sub-woofers. Some systems also offer a centre channel speaker to give stable sound localisation and enhance the stereo imaging. To add to the overall quality and give the sound some 'environment' a digital sound processor can be used. This adds different amounts of delay to the various speakers to simulate stadiums, halls and even cathedrals. In addition, an automatic road noise controller listens to background noises made by the car and can boost various frequencies to compensate.

Protection

One of the biggest problems besetting car HiFi systems has been theft. Since most cars are relatively easy

to break into and the most valuable item in view is the HiFi a lot of work has gone into deterring thieves.

The most obvious solution has been to make the units removable. Simply lifting a handle and pulling removes the entire radio/cassette leaving an empty hole behind. The drawback with this is that every time the car is left anywhere, a bulky box must be carried off by the driver. If the HiFi is accidentally left in the car, it becomes even easier to steal.

Another solution to the theft problem is to provide individual code numbers for each system. Entering the right code allows the system to work, the wrong code disables it completely.

Yet another solution to the problem is a removable fascia plate. This is small enough to fit in a pocket but without it, the HiFi won't work. When used in conjunction with a code number, this technique can be quite effective.

Almost all modern HiFi systems offer some form of security feature. When considering the cost of the equipment and the high risk of losing it, it has become an essential feature. ■

The Panasonic CY-DA3000 digital signal processor offers complete surround sound.




Armour Plated In-car Cassettes

Arthur King checks out a new audio cassette from Sony that has been especially designed to withstand the rigours of being on the road.

If you drive a car and use an in-car cassette more than occasionally, you're bound to have suffered the inevitable tangled tape scenario. If you think about it, unless you happen to run a super smooth Roller with air-conditioning powerful enough to freeze a small town, a car dashboard must be one of the worst places imaginable to site a tape cassette mechanism. Heat attacks from all angles – the greenhouse effect of a car parked in hot sunlight with the windows closed, heat seeping in from the engine compartment, the heating system and even heat generated by the cassette player's own electric motor. But that's only half the story because vibration and shock coming from both the engine and the road, takes things from bad to worse. Then again it astonishes me how a cassette, and even the driver survive the megawatt blasting (mostly at ridiculously low resonant frequencies) which some people appear to enjoy enduring and spend literally thousands of pounds on in power amplifiers and woofers to achieve. I personally long ago abandoned the idea of trusting any car stereo with my best HiFi recordings. My car tapes are all backups of the originals and all eventually end up looking like an audiophile piranha has been at them.

Tape manufacturers, especially in the US where people spend a much larger proportions of their lives cocooned in a car, have become wise to the fact that the promise of a reliable cassette tape designed specially with car stereos in mind can be a much needed boost to flagging sales. Indeed Philips went to great lengths to stress how much research and development had gone into the formulating heat and vibration resistance specification targets for the new digital compact cassette (DCC) standard. Even if DCC, which HiFi buffs

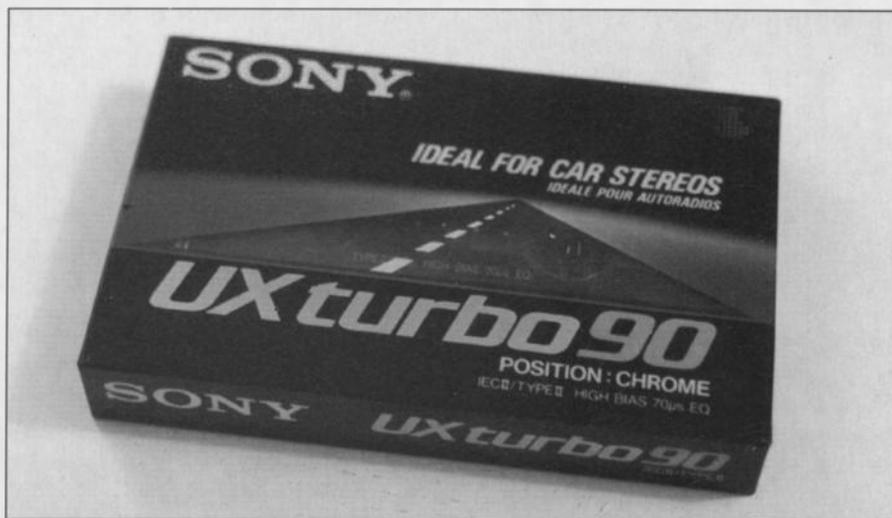

feel has a compromised sound quality, doesn't take off in the quality HiFi stakes it should remain popular for in-car systems. The comparatively noisy insides of even the most refined Roller means that DCC's admittedly good sound quality won't be judged 'not good enough' for a long while yet. DCC had to appeal to the car stereo manufacturers right from the word go and DCC's designed-in ability for its cassettes to withstand continuous 40C environments was one way of providing the required appeal.

Sony has produced such an armoured car-tape of the more conventional variety. The Super Chrome Position UX Turbo (sic) C90s we've been torturing have all survived intact. The cassette shells are identifiable by being unfashionably short on clear plastic window areas exposing the tape reels – opaque plastic is stronger than the transparent stuff. For extra rigidity the shell halves are welded together rather than bound by screws. Sony claims the plastic it uses can withstand 115 Celsius. Even the self-adhesive labels supplied are guaranteed not to peel off and migrate to the most delicate parts of

your car stereo's tape transport mechanism. Surprisingly Sony's attention to in-car requirements don't seem to have extended to the delicate stuff which does a good job of wrapping itself around capstan rollers. According to Sony specification sheets the tape itself is identical to ordinary UXS90 stock. This isn't half bad as Sony claims UXS has the least bias noise (-60.5dB) of any super chrome position tape. Other nice Sony touches include a non-slip grip for those changing-the-tape when one should be changing gears moments around multiple mini-roundabouts plus extra lumpy dimples for you to feel which side of the tape is which without taking your eyes off the road.

I could probably be tempted to spend the extra dosh on UX Turbo tapes, especially if the hot summers we've been getting in recent years are here to stay. ■


Sony UX Turbo 90 Tapes are available in twin packs at a recommended retail price of £3.99 per pack – note that some retailers may offer reductions on this.

INTRODUCTORY
PRICE JUST £179

SCHEMATIC DRAWING FOR WINDOWS

NEW

ISIS ILLUSTRATOR combines the high functionality of our DOS based ISIS products with the graphics capabilities of Windows 3. The result is the ability to create presentation quality schematics like you see in the magazines. **ILLUSTRATOR** gives you full control of line widths, fill styles, fonts, colours and much more. When the drawing is complete, transferring it your WP or DTP program is simply a matter of cutting and pasting through the Windows Clipboard.

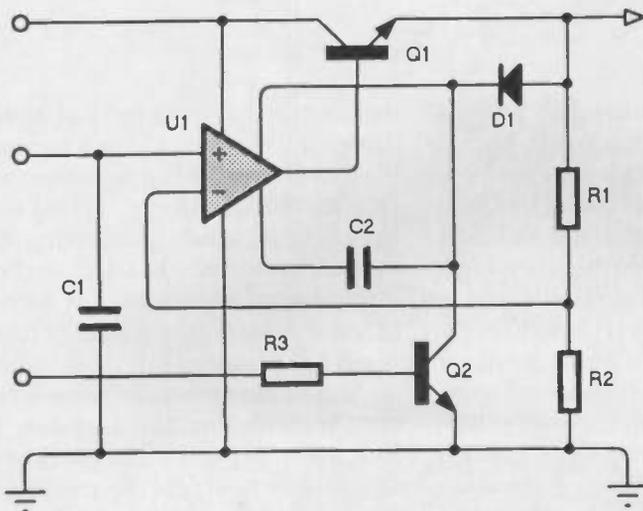

Features

- Runs under Windows 3.0 or 3.1.
- Full control of drawing appearance including line widths, fill styles, fonts, colours and more.
- Curved or angular wire corners.
- Automatic wire routing and dot placement.
- Fully automatic annotator
- Comes complete with component libraries; edit your own parts directly on the drawing.
- Full set of 2D drawing primitives + symbol library for logos etc.
- Output to Windows printer devices including POSTSCRIPT and colour printers.
- Loads ISIS SUPERSKETCH and DESIGNER files directly.

ISIS - Intelligent Schematics

ISIS SUPERSKETCH (from £69)

A superb entry level schematic drawing package offering all the editing features of ISIS DESIGNER but without the netlisting, bill of materials and electrical rules check features.

Extended device library available for an additional £30.

ISIS DESIGNER (£275)

Provides all you need to create and edit schematics prior to further processing with ARES or other EDA software. Through the provision of user definable menu options and a special script language, ISIS acts as a 'framework' from which you can control all your CAD software.

ISIS DESIGNER+ (£475)

This top of the range schematics package adds hierarchical design, automatic annotation/packaging, ASCII data import and Design Global Annotation to make it one of the most advanced schematics packages available for DOS.

ARES - Advanced Routing

PCB II (£69)

Our Graphical User Interface makes this PCB drafting package exceptionally easy to learn and use. Advanced features include Auto Track Necking, Gerber viewing, curved tracks, and DXF export.

ARES (£275)


This package offers multi-layer, netlist based PCB design together with Power Plane Generation, EMS memory support and back-annotation to ISIS DESIGNER+.

ARES AUTOROUTE (£475)

Adds a multi-strategy auto-router to ARES to provide the ultimate in design automation. Special strategy management features allow all design rules to be defined in ISIS so there is very little setting up to do.

Also available as **ARES 386** - a 32 bit version offering up to 400% faster operation, virtually unlimited design capacity and 1024x768 graphics support.

Labcenter
E l e c t r o n i c s

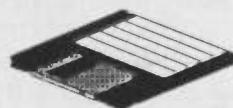

Call us today on 0274 542868 or
fax 0274 481078 for a demo pack.
Combination, multi-copy and educational
discounts available. Prices exc P&P and VAT.

14 Marriner's Drive, Bradford, BD9 4JT.

How it works

Engine Management

Derek Gooding opens the bonnet of his car to find out what is inside the black box that controls the engine.

Surely there is no comparison these days between the electronics under the bonnet and the very early days of the first petrol driven automobiles? Those 'Good ol' days when the roads were always clear, except for the herds of sheep or cattle. The open road. Next time you have the opportunity of a close look at an early vintage car, you will notice a number of levers around the driving position that we don't have to worry about today.

'Advance/Retard', 'Suction'. Such controls were fine for the enthusiasts willing to experiment and really learn how to drive, but more ordinary mortals would soon be in the driving seat.

Manufacturers have eventually developed engines that are so user-friendly, the owners seldom lift the bonnet to see that all is well and few would be able to understand the systems involved let alone be able to repair them.

Feedback

From the early days car engine designs have followed a pattern of complex mechanical feedback systems that produced a reasonable degree of engine protection and a smoother ride. Modern electronic systems also involve feedback; control of fuel/air mixtures; fuel injection; surge suppression; battery charging, and engine temperatures.

The drawing shows a Lucas Engine Management System unit with its transistor circuits, this is a replacement unit for a 1970's car, but at least we can see inside it. These days a 'black box' encapsu-

lated approach is used to protect the circuitry and it is worth knowing that to cut open a modern box, after it has ended its useful life, is to be avoided, especially if the unit has been subjected to very high temperatures. The resulting liquid is very damaging to ones health.

Full microprocessor control units are now in service as car management systems, these enable stepper motors to operate and control the carburettor setting; if the tick-over of the engine drops to the point where the battery charging ceases, the feedback automatically causes the engine to speed up to a point where charging recommences. Sometimes 'knock' begins in one cylinder and does the engine no good at all, but the feedback to some microprocessor car systems actually enables immediate reaction to the knock sensor's message and can retard just the one cylinder until the loading problem has passed.

Long term aims of the big manufacturers is to satisfy the demand for vehicles offering higher performance, better fuel economy, longer service intervals and lower emission levels. Even the humble spark plug is about to go back into the laboratory for a full reappraisal so the future is looking good for motorists.

Early Attempts

Many unfortunately remember the early days of electronic ignition systems where, without warning, the engine would just die. Some accidents may have happened because

the electronics 'gave up' just as the driver put their foot down to complete an overtaking manoeuvre. One journalist always carried two 'spare' units when test driving the new electronic box of tricks and on a number of occasions was forced to use them in replacement to finally get home again.

Maybe next time you see a veteran car rally, or the London to Brighton drive in November - where they celebrate the passing of the red flag safety walker who was forced by law to proceed any moving automobile - you will notice the fact that the driver is working much harder than any modern driver. But it's nice to know that in many ways the early drivers had it very easy indeed, for they only steered the vehicle.

In The Past

In the days of steam powered road transport the poor coal stoker at the back would control the power source for the driver. Coal dust experiments to ignite inside an engine cylinder proved difficult if not impossible but led to the development of the crude oil engine.

Soon petrol driven automobiles were on the road, making the stoker redundant. Owners found the fun of steering had gone and they were expected to learn the complexity of the many levers, adjusters and techniques of the 'new age' machines. Is it not to be expected that few continued to want to drive but instead re-deployed their stoker as driver. The French call their stokers: 'Chauffeurs'. ■

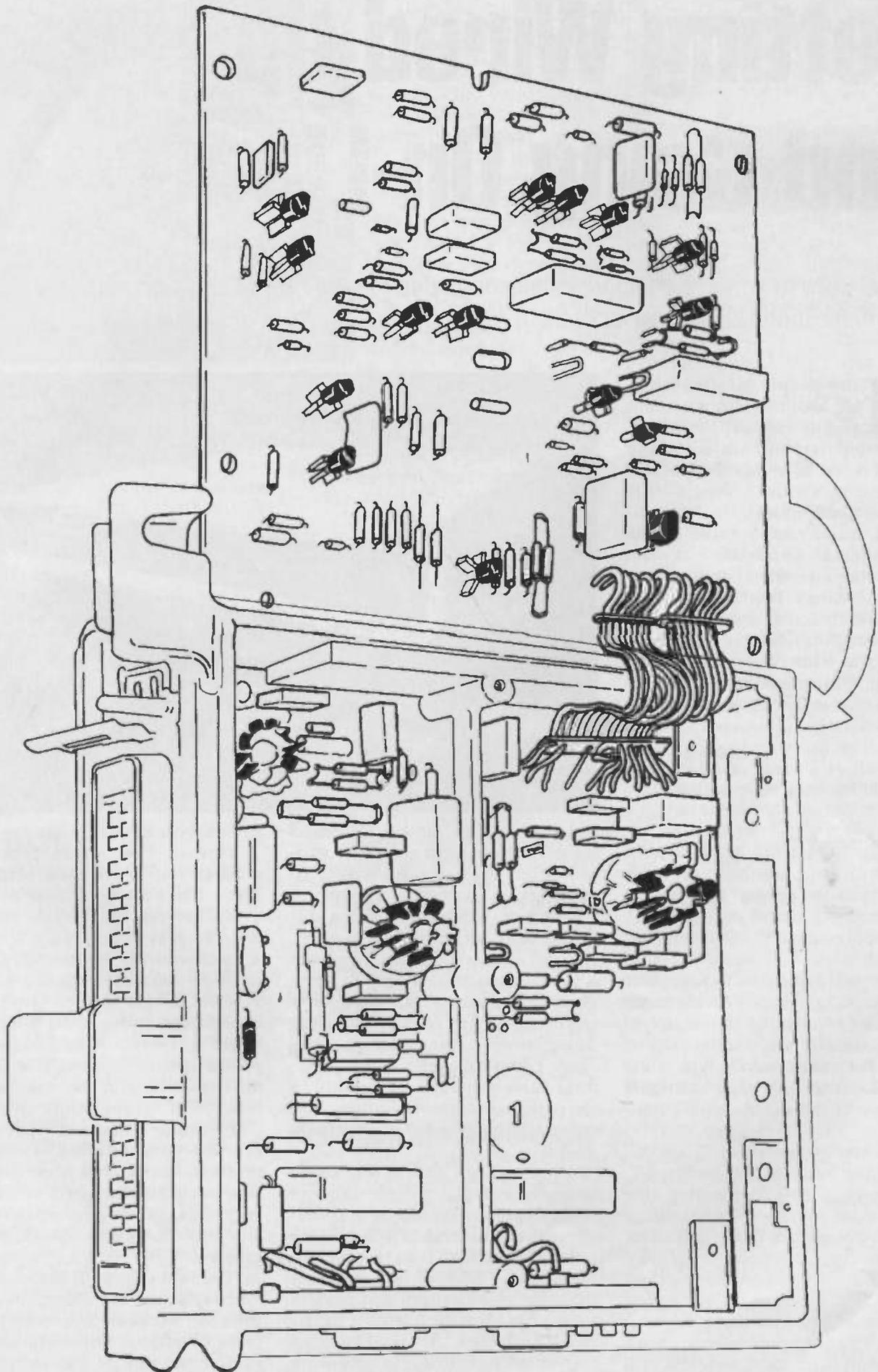


Illustration by Derek Gooding

Getting Wired Up And Going On-Line

All you need to know to go about connecting up to the wide world of Computer Communications with Steve Jackson.

Many people may be thinking about buying a modem and going on-line with their computers but are not really sure of what is involved. The following pages aim to shed a little light on communications for computers, and answer some of the more common questions.


Owning a modem opens a door to a new world. It enables a small computer to access a vast network of information which is quite literally world-wide. A modem brings the ability to connect to other computers to transfer programs, data, text files, news, exchange messages with other users and much much more, all at a press of a key. The possibilities are almost endless.

Equipment

To get on-line, various pieces of equipment are needed. In general, any items discussed in this article will apply to most types of computer system.

Obviously, the first requirement is a computer able to provide some means of connecting to a modem. This is usually via a serial port of which the most common type is the RS-232 – a widely used standard throughout the world. All PC compatible computers have a serial port, usually known as "COM1". Machines such as the Amiga, ST, Archimedes and Apple Mac also have serial ports which adhere to the same standard. Older machines, such as the Commodore 64, may require an interface of some kind maybe or, perhaps, a dedicated modem designed for that machine.

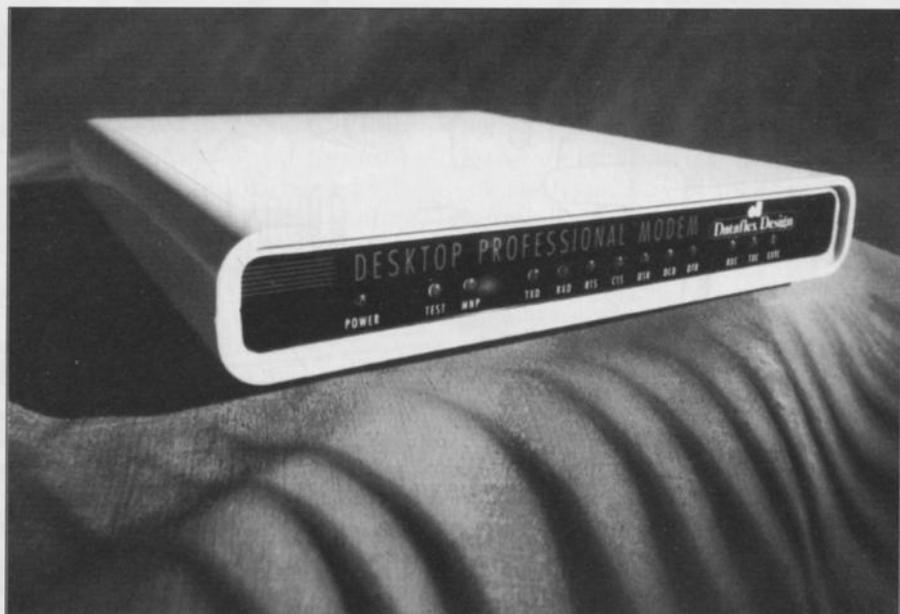Unless they are based on an expansion card, most modems will connect to your RS-232 port via a



serial cable. This can be purchased complete from most computer suppliers but they are quite easy to make up if you prefer – a couple of connectors, some cable and a soldering iron are all that are needed. In practice, serial cables using the RS-232 standard can vary in complexity. The most basic cable only requires use of three pins – transmit data, receive data and ground. More complex cables can include data flow control and signals to show if your communications and computer equipment are actually on-line.

At the other end of the cable from the computer is the modem itself. There are hundreds of different makes and models available; so much so that there is not room to go into them all here. Instead, a look at the main specifications and modem types plus a rough guide to the price of each – this is always an important factor of all computing topics, should give some idea of

what to bear in mind when buying.

One of the oldest types of modem is the acoustic coupler. There aren't many of these around today, but they can be seen used in films such as War Games. With an acoustic coupler devices telephone numbers are dialed manually with a normal telephone. Once the remote computer system can be heard answering the handset is placed into the coupler. This allows the computer and the remote system to exchange data. Unfortunately, acoustic couplers are not very reliable. They are prone to interference from the outside world and they only operate at very slow speeds – this makes them an option not worth considering in practice.

The next step up from an acoustic coupler are the older, but more reliable, manual modems. These come in various forms but use the same basic design and operation. Compared to more modern



modems they are a little dated but very cheap. These devices must be configured manually via switches and dials usually located on the front panel. Again, telephone numbers must be manually dialed but the difference is that the handset doesn't have to be placed into a coupler. The normal procedure is to simply flick a switch once the remote system replies and then put the handset down. Interference is not much of a problem but manual modems are limited in other ways. They can probably be picked up for under £50 second hand – it would be rare to find a new one nowadays. Speeds supported would be V21 and sometimes V23 (300/300 and 1200/75 baud respectively).

The Best

The best type of modem to look at is an automatic modem. The most common types are Hayes compatible and they all work in much the same way even though actual specifications may vary. Most of these modems can be controlled through software from the computer, although they often have manual switch settings available if you need them. Hayes compatible modems use commands that are issued via the keyboard of a computer or automatically by the communications software. This language allows you to completely configure the modem and use all its features. All have automatic dialling so there is no need to use a conventional telephone. The modem will also be able to autoanswer, so if there is an incoming call, the modem will pick up the line and carry out the connection by itself.

The most basic type of Hayes

compatible modem will offer V21 and V23 operation. Next up is V22 (1200 baud) and then comes V22bis (2400 baud). Most modems are downwardly compatible, that is, a V22bis modem will work with V22, V23 and V21. A V22bis modem will vary in price but it is possible to pick them up for under £100. This does depend on the manufacturer, whether it is new or not, and what features it has. The most widely used standard is probably V22bis. It offers

an acceptable transfer rate and is pretty much error free in most conditions.

Noise on the telephone lines can always be a problem when using a modem and a high transfer speed is sort after because it cuts down on the phone bill. The problem here is that the faster the modems talk to each other, the more prone they are to interference. This is where error correction and data compression come into play. Some modems are advertised with such options as MNP 5 and V42bis. Modems of this type, when connected to a modem which offers the same facilities, will provide completely error free communications. They will also compress the data so that a greater throughput is achieved. Unfortunately, this causes the price to start rising – over £100 in most cases. The thing to bear in mind is that the greater throughput the shorter the call time will be. This means a saving on phone bills, so in the long run it is worth while paying more for a faster modem.

Moving on to the top of the price range there are modems with very high speed capabilities such as V32 and V32bis modems. These offer

Systems To Go

01 For Amiga – BBS – 071 247 9240
 CIX – Commercial – 081 390 1255
 Compuserve – Commercial – 071 490 8881
 Computer Pages – Free Commercial – 081 751 1494
 Cyberspace – Commercial – 071 580 6433
 DTP – BBS – 081 656 5190
 MAX – Large BBS – 0905 52536
 PDSL – BBS – 0892 667091
 TUG 2 – BBS – 0905 775191
 Most BBS systems have a list available of other systems that you can dial up, these are just a selected few.

speeds of 9600 baud and 14400 baud and although the price of modems is falling all the time, a first class machine can easily cost over £400 pounds and, in some cases, over £1000. Again, this depends on whether the device is new and who manufactures it. Just about all of these modems have error correction and data compression built in. Some of the connection speeds which can be obtained are quite amazing. This sort of modem is especially useful for transferring large files that would otherwise take an unreasonably long time to carry out, using V22bis, or lower.

Software

To drive the serial port and modem a communications software package is needed – again there are plenty to choose from but all of them do much the same thing. As with most types of software there are both commercial products and packages which are available via Public Domain (PD) and shareware sources. It must be said that most of the commercial packages, save one or two, don't compare favourably to what is available through shareware and PD. People who are involved with communications are


Common Modem Standards

V21	300 baud, transfers data at 300 bps full duplex
V22	1200 baud, transfers data at 1200 bps full duplex
V23	1200/75 baud, receives data at 1200 bps and transmits at 75 bps full duplex
V22bis	2400 baud, transfers data at 2400 bps full duplex
V32	9600 baud, transfers data at 9600 bps
V32bis	14400 baud, transfers data at 14400 bps
V42	Error correcting protocol for modems. Packet based error detection and retransmission technique
V42bis	Data compression algorithm. Simple and compact technique giving up to three times the data throughput
MNP	Miracom Networking Protocol Error control in MNP 1 to 4 and data compression in MNP 5

often very devoted and this shows in the hobbyist software that is produced. Both shareware and PD programs can be freely distributed, often only costing the price of a disk and, in the case of shareware, a registration fee. A good PD library or a friend should be able to supply a reasonable program and once on-line it is possible download other communications programs without having to wait for the disk to arrive in the post. A good commercial package to look out for on the PC is Transend Professional and a decent Shareware/PD package, which is widely available, is PROCOMM.

Services

Once the computer, cable, modem and software are set-up a whole new world opens up. There are a variety of services available, some of which are free and some which have to be paid for. The most common type of communications system which can be contacted via modem is the bulletin board. 90% of these are run from the home by enthusiast as a hobby. There are hundreds in the UK alone and hundreds, if not thousands, around the world. On calling a bulletin board for the first time it will usually request details such as name, address, telephone number and so on. From there it will probably present some information about the system, what it has to offer and var-

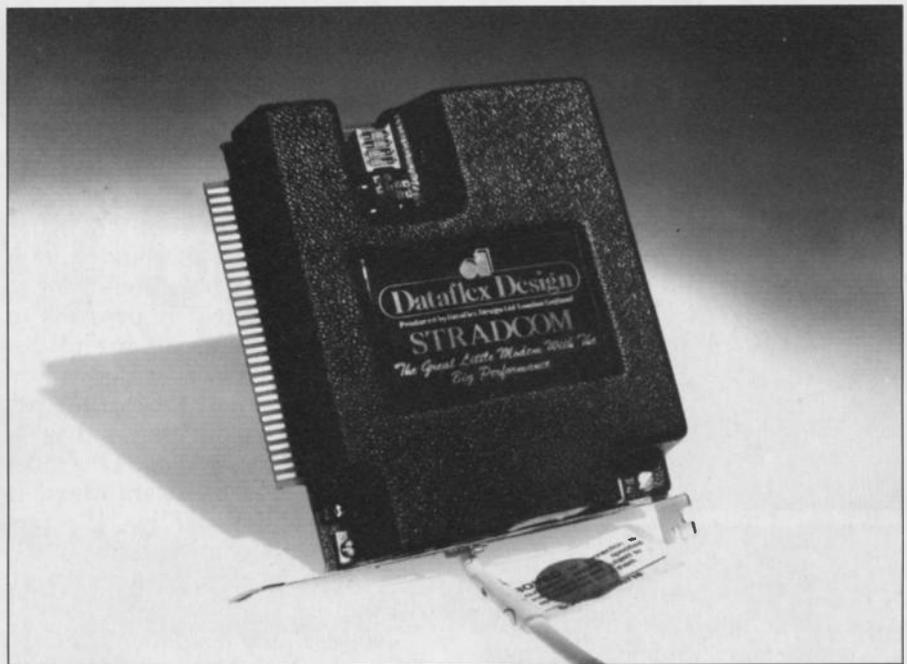

ious bits of the latest system news. It will then present a menu system which will allow the choice of various procedures and options. There are files which are available for download from the bulletin board or on-line service to your computer and messages from other users. Some systems even allow games to be played against other people who call the system, or in the case of multi-line systems play against someone in real-time. Most bulletin board systems are free to use, apart from the phone bill incurred when calling them. Some of the larger systems do ask for a small donation

and many have subscription fees.

There are also commercial on-line systems available which have to be paid for. This sort of system will offer a great deal of information, access to lots of other users and is often just a local phone call away. The subscription charges vary depending on what facilities you require and the service in question.

The world of communications is developing and expanding rapidly while the cost of accessing it is falling. All that is needed is to buy a cheap computer, cable, modem and software to start exploring it now. ■

Modem Glossary

ARQ – Automatic Repeat Request, a general term for error control

Asynchronous Transmission – Data transmission in which the length of time between transmitted characters may vary, applies to the sort of modem referred to in this article

Autoanswer – A feature in modems enabling them to answer incoming calls

Autodial – A feature in modems enabling them to dial phone numbers without the aid of a conventional telephone

Baud – The number of discrete signal events per second occurring on a communications channel. Although not completely correct, baud is often used to mean bit rate

Bits per Second – BPS for short, the number of bits transmitted per second via a communications channel

Carrier – A continuous frequency capable of being either modulated or impressed with another information carrying signal

CCITT – A international organisation that

defines standards for telephone equipment, for example, the modem standards

Data Compression – The modem compresses data received from the computer, transmits it to the remote modem, where it is then uncompressed and sent to the remote computer

DCE – Data Communication Equipment for example a modem

DTE – Data Terminal Equipment for example a computer

Download – The transfer of data from a remote to a local system

Duplex – Indicates a communications channel capable of carrying signals in either one direction at a time (half duplex) or in both directions (full duplex)

Error Control – various techniques which check the reliability of characters or blocks of data

Flow Control – A mechanism that compensates for differences in the flow of data input to and output on a modem

Local Echo – A modem feature that allows

the modem to send copies of keyboard commands and transmitted data to the screen

Local System – Usually refers to your computer

Modem – A device that transmits and receives computer data through a communications channel such as a telephone line: stands for modulator, demodulator

On-line – A connection is made between two modems for example

Remote Echo – A copy of the data received by the remote system

Remote System – A computer system located a distance away


Serial Transmission – The transfer of data characters one bit at a time

Synchronous Transmission – A form of transmission in which blocks of data are sent at strictly timed intervals

Upload – The transfer of data from the local to the remote system

Space Art

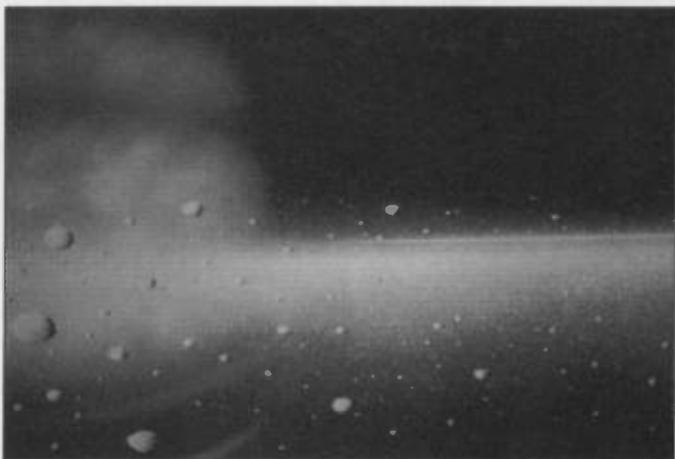Astronomy Now's Art Editor Paul Doherty is one of Britain's foremost space and astronomical illustrators. His pictures have featured in numerous books and regularly appear on *The Sky at Night*. Dr. Patrick Moore CBE said of Paul Doherty, "Paul's paintings are without doubt the most beautiful and technically accurate, which is why I select them to illustrate my books."



Astronomy Now Magazine is pleased to offer a special limited edition of four of Paul's most attractive paintings. Each picture is printed on heavy grade 200 gsm acid-free paper, to eliminate fading, and is available in a limited edition of only 300, individually signed and numbered by the artist. Select individual prints at £24.95 each, including P&P, or collect all four for only £89.95. The prints available are:

← **Inside the Rings of Saturn**, first published in

The Unfolding Universe (Rainbird in association with the Book Club Association) by Patrick Moore

← **Planetary System of Albireo**, first published in *Travellers in Space and Time* (St. Michael) by Patrick Moore

➔ **Planet close to a Globular Cluster**, first published in *Travellers in Space and Time* (St. Michael) by Patrick Moore



➔ **The Icy Surface of Pluto**, first published in the *George Philip Atlas of the Universe* by Mitchell Beasley

To order, please tick the box in the caption of the print(s) you require and send a copy of this page to Space Art (PD), Intra Press, Intra House, 193 Uxbridge Road, London W12 9RA. Please enclose payment in the form of a cheque or PO made out to Intra Press. Don't forget to include your name and address.



Orders will be processed on a first-come, first-served basis. Please allow 28 days for delivery.

Multimedia Comes Of Age

Rod Allen visits Multimedia 92 and finds a fascinating collection of interactive video, computers and software.


In the last two to three years the term multimedia has gone from being a buzz word for an idea to a buzz word for some real technology. The recent multimedia show at Olympia in London was a showcase for a wide variety of computer, video and sound systems.

Using computers to control video information and sound as well as their interaction with people is at the heart of multimedia technology. Some systems are complete in themselves – Philips CD-I and Commodore CDTV are good examples of this. Others are simple enabling technologies such as touch screens or video interfaces for computers. Still others are computer programs that allow current systems such as PCs and Mac to create and manipulate moving pictures and sound.

Interactive Entertainment

The two main competing systems for home multimedia market are Commodore's CDTV and the recently launched Philips' CD-I. Both had large stands at the show with a number of machines avail-

Apple's Quicktime in action.

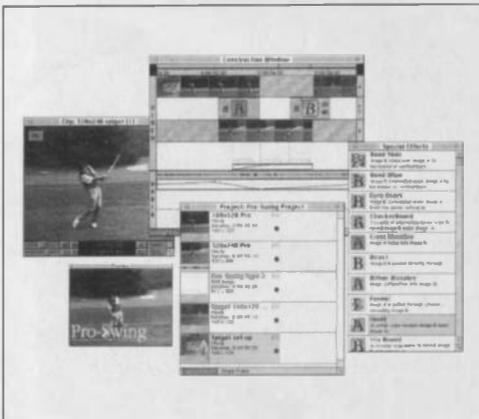

A picture drawn with Autodesk 3D Studio.

able to play with.

The Commodore system is based around its Amiga computer technology and is, in some ways, handicapped by this. The machines on show produced reasonable sound and pictures – about what you'd expect from a computer games machine. The CD-I system, on the other hand, had a much more professional look and feel. Time will tell which one wins out in the battle for the home multimedia market but my money is on CD-I.


Touching Technology

Evident at the show was a plethora of touch screens. These were being used on demos of everything: ATM machines, how to find your post-code using the Royal Mail's CD-

Post code system, a complete guide to the show with touch-screen maps of the exhibition and as a mouse replacement in general MS-Windows applications.

The technology of touch screens falls into three main categories, resistive, surface acoustic wave (SAW) and capacitive. Resolutions of up to 4000x4000 points are available and SAW systems are also pressure sensitive so that they not only sense the position of a finger on the screen, they also know how hard it is pushing. This can be used for dragging and clicking or in process control where things must be turned on and off.

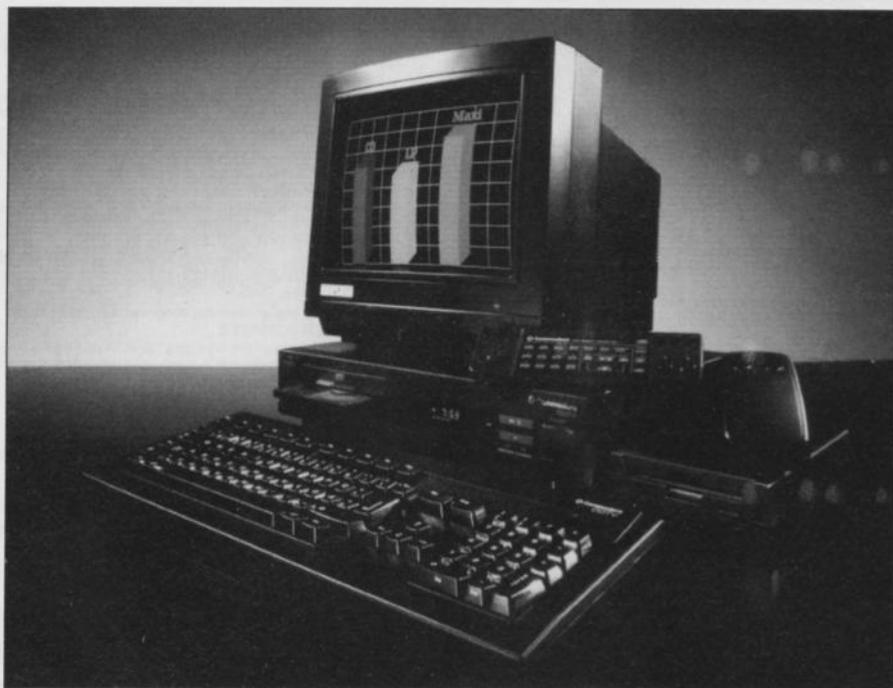The screens can be attached to almost any monitor – Ellinor reckon to make about eight or nine screens in each standard size to fit all of the



Commodore's stylishly black CDTV.

different makes and types of monitor. With an estimated life of about 1,000,000 touches for each point on the screen, they should last a lifetime and start appearing in the high street real soon now.

On-Screen

As display technology is important to multimedia, it was to be expected that there would be a large number of gadgets designed to improve picture quality and help interface to various sources of video information.

One of the drawbacks with the latest PCs and Macintosh computers is that they output their video information in a format that is totally incompatible with most VCRs. Among others, VideoLogic, Multimedia Italia and Magnifeye were providing solutions with cards or plug-ins that output PAL signals. Using these, the computer can be used to generate a sequence of images which can then be recorded on video tape to be spliced together with other sequences, resulting in a totally computer generated programme.

Software

Apart from the hardware, multimedia is intimately involved with computer software. In general this produces some impressive results – with the aid of some hefty process-

ing power. Two of the more impressive packages on show were Apple's Quicktime and Autodesk's 3D Studio.

Quicktime is an add-on to Apple's new System 7 operating system and allows the integration of video and sound into the Macintosh's graphical user interface (GUI). This is done in such a way as to allow video information to be passed from application to application without the need for any conversion or incompatibility problems. Able to run on all standard Macs, video sequences of between


10 and 24 frames per second can be viewed in a window on-screen. Images can be sourced from camcorders or VCRs via a plug in card and incorporated into presentations or learning packages. The big advantage of Quicktime is that the whole thing integrates seamlessly with the rest of the operating system.

When it comes to life-like images, Autodesk 3D studio is going to be hard to beat. Images are made up from a 3D wire frame model, each point of which can be easily position in 3D space. A rendering system then lays over this skeleton a perfect three dimensional rendition of any texture required using a predefined light source and viewing position. The texture can be a standard such as silver or wood grain, or can be scanned in to allow custom patterns to be used. The full colour results are so life-like that it is difficult to tell them from a photograph. Some of the main applications are in 3D modelling or the creation of mock-ups for design purposes.

Multimedia To Come

With applications in learning, training, point of sale, graphic design, communications, entertainment plus many others, multimedia has finally come of age. If the products on show at Multimedia 92 are anything to go by it will be appearing all over in the very near future. ■

Ellinor's touch screen system.

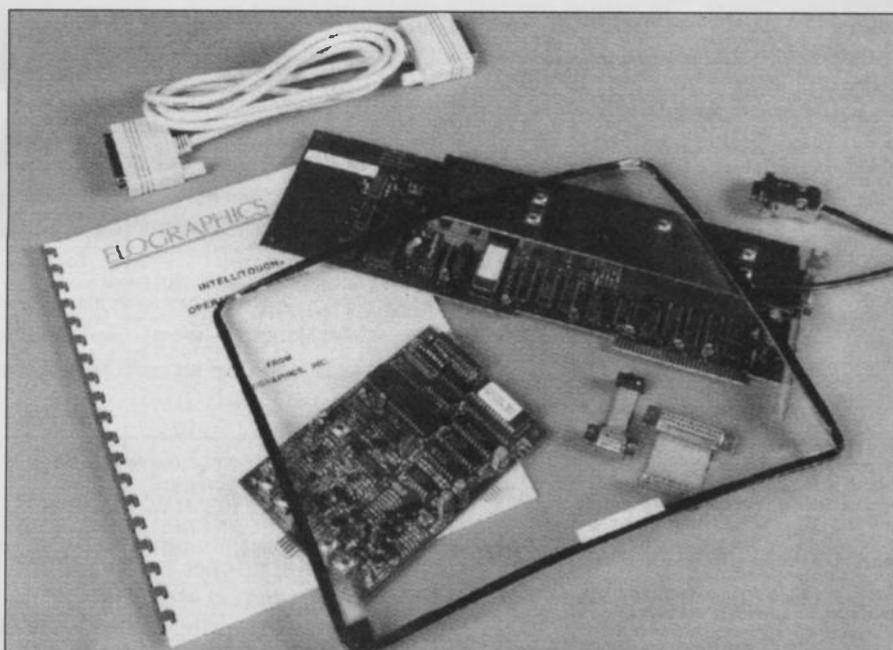



AMSTRAD PORTABLE PC'S FROM £149 (PPC1512SD), £179 (PPC1512DD), £179 (PPC1640SD), £209 (PPC1640DD). MODEMS £30 EXTRA. NO MANUALS OR PSU.

HIGH POWER CAR SPEAKERS. Stereo pair output 100w each. 4ohm impedance and consisting of 6 1/2" woofer 2" mid range and 1" tweeter. Ideal to work with the amplifier described above. Price per pair £30.00 Order ref 30P7R.

2KV 500 WATT TRANSFORMERS Suitable for high voltage experiments or as a spare for a microwave oven etc. 250v AC input. Now only £4.00 ref 4P157

MICROWAVE CONTROL PANEL. Mains operated, with touch switches. Complete with 4 digit display, digital clock, and 2 relay outputs one for power and one for pulsed power (programmable). Ideal for all sorts of precision timer applications etc. Now only £4.00 ref 4P151.

FIBRE OPTIC CABLE. Stranded optical fibres sheathed in black PVC. Five metre length £7.00 ref 7P29R

12V SOLAR CELL. 200mA output ideal for trickle charging etc. 300 mm square. Our price £15.00 ref 15P42R

PASSIVE INFRARED MOTION SENSOR. Complete with daylight sensor, adjustable lights on timer (8 secs -15 mins), 50' range with a 90 deg coverage. Manual override facility. Complete with wall brackets, bulb holders etc. Brand new and guaranteed. Now only £19.00 ref 19P29

Pack of two PAR38 bulbs for above unit £12.00 ref 12P43R

VIDEO SENDER UNIT Transmits both audio and video signals from either a video camera, video recorder or computer to any standard TV set within a 100' range (tune TV to a spare channel). 12v DC op. £15.00 ref 15P39R Suitable mains adaptor £5.00 ref 5P191R

FM TRANSMITTER housed in a standard working 13A adaptor (bug is mains driven). £26.00 ref 26P2R

MINIATURE RADIO TRANSCEIVERS A pair of walkie talkies with a range of up to 2 kilometres. Units measure 22x5x155mm. Complete with cases. £30.00 ref 30P12R

FM CORDLESS MICROPHONE. Small hand held unit with a 500' range 2 transmit power levels reqs PP3 battery. Tuneable to any FM receiver. Our price £15 ref 15P42AR

12 BAND COMMUNICATIONS RECEIVER. 9 short bands, FM, AM and LW DX/local switch, tuning 'eye' mains or battery. Complete with shoulder strap and mains lead **NOW ONLY £19.00!! REF 19P14R.**

CAR STEREO AND FM RADIO. Low cost stereo system giving 5 watts per channel. Signal to noise ratio better than wow and flutter less than .35%. Neg earth. £25.00 ref 25P21R

LOW COST WALKIE TALKIES. Pair of battery operated units with a range of about 200'. Our price £8.00 a pair ref 8P50R

7 CHANNEL GRAPHIC EQUALIZER plus a 60 watt power amp 20-21KHz 4-8R 12-14v DC negative earth. Cased. £25 ref 25P14R.

NICAD BATTERIES. Brand new top quality. 4 x AA's £4.00 ref 4P44R. 2 x C's £4.00 ref 4P73R. 4 x D's £9.00 ref 9P12R. 1 x PP3 £6.00 ref 6P35R

TOWERS INTERNATIONAL TRANSISTOR SELECTOR GUIDE. The ultimate equivalents book. Latest edition £20.00 ref 20P32R.

CABLE TIES. 142mm x 3.2mm white nylon pack of 100 £3.00 ref 3P104R. Bumper pack of 1,000 ties £14.00 ref 14P6R

1992 CATALOGUE AVAILABLE NOW IF YOU DO NOT HAVE A COPY PLEASE REQUEST ONE WHEN ORDERING OR SEND US A 6"X9" SAE FOR A FREE COPY.

GEIGER COUNTER KIT. Complete with tube, PCB and all components to build a battery operated geiger counter. £39.00 ref 39P1R

FM BUG KIT. New design with PCB embedded coil. Transmits to any FM range. 9v battery req'd. £5.00 ref 5P158R

FM BUG Built and tested superior 9v operation £14.00 ref 14P3R

COMPOSITE VIDEO KITS. These convert composite video into separate H sync, V sync and video. 12v DC. £8.00 ref 8P39R.

SINCLAIR C5 MOTORS 12v 29A (full load) 3300 rpm 6"x4" 1/4" O/P shaft. New. £20.00 ref 20P22R.

As above but with fitted 4 to 1 inline reduction box (800rpm) and threaded nylon belt drive cog £40.00 ref 40P8R.

SINCLAIR C5 WHEELS 13" or 16" dia including treaded tyre and inner tube. Wheels are black, spoked one piece poly carbonate. 13" wheel £6.00 ref 6P20R. 16" wheel £8.00 ref 6P21R.

ELECTRONIC SPEED CONTROL Kit for C5 motor. PCB and all components to build a speed controller (0-95% of speed). Uses pulse width modulation. £17.00 ref 17P3R.

SOLAR POWERED NICAD CHARGER. Charges 4 AA nicads in 8 hours. Brand new and cased £6.00 ref 6P3R.

12 VOLT BRUSHLESS FAN 1/2" square brand new ideal for boat, car, caravan etc. £5.00 ref 5P206.

ACORN DATA RECORDER ALF503 Made for BBC computer but suitable for others. Includes mains adaptor, leads and book. £15.00 ref 15P43R

VIDEO TAPES. Three hour superior quality tapes made under licence from the famous JVC company. Pack of 5 tapes New low price £8.00 ref 8P161

PHILIPS LASER. 2MW HELIUM NEON LASER TUBE. BRAND NEW FULL SPEC £40.00 REF 40P10R. MAINS POWER SUPPLY KIT £20.00 REF 20P33R READY BUILT AND TESTED LASER IN ONE CASE £75.00 REF 75P4R.

12 TO 220V INVERTER KITS as supplied it will handle up to about 15w at 220v but with a larger transformer it will handle 80 watts. Basic kit £12.00 ref 12P17R. Larger transformer £12.00 ref 12P41R.

VERO EASI WIRE PROTOTYPING SYSTEM Ideal for designing projects on etc. Complete with tools, wire and reusable board. New low bargain price only £2.00 ref B2P1

HIGH RESOLUTION 12" AMBER MONITOR 2v 1.5A Hercules compatible (TTL input) new and cased £22.00 ref 22P2R

VGA PAPER WHITE MONO monitors new and cased 240v AC. £59.00 ref 59P4R

25 WATT STEREO AMPLIFIER c. STK043. With the addition of a handful of components you can build a 25 watt amplifier. £4.00 ref 4P69R (Circuit dia included).

BARGAIN NICADS AAA SIZE 200MAH 1.2V PACK OF 10 £4.00 REF 4P92R, **PACK OF 100 £30.00 REF 30P16R**

FRESNEL MAGNIFYING LENS 83 x 52mm £1.00 ref BD827R.

ALARM TRANSMITTERS. No data available but nicely made complex radio transmitters 9v operation. £4.00 each ref 4P81R.

12V 19A TRANSFORMER. Ex equipment but otherwise ok. Our price £20.00

GX4000 COMPUTERS. Customer returned games machines complete with plug in game, joysticks and power supply. Retail price is almost £100. Ours is £12.00 ref B12P1

ULTRASONIC ALARM SYSTEM. Once again in stock these units consist of a detector that plugs into a 13A socket in the area to protect. The receiver plugs into a 13A socket anywhere else on the same supply. Ideal for protecting garages, sheds etc. Complete system £25.00 ref B25P1 additional detectors £11.00 ref B11P1

IBM XT KEYBOARDS. Brand new 86 key keyboards £5.00 ref 5P612

IBM AT KEYBOARDS Brand new 86 key keyboards £15.00 ref 15P612

386 MOTHER BOARDS. Customer returned units without a cpu fitted. £22.00 ref A22P1

COLOUR MONITORS

AMSTRAD CTM644

RGB INPUT

£75.00 REF A75P1

286 MOTHER BOARDS. Brand new but customer returns so may need attention. Complete with technical manual £20.00 ref A20P2

286 MOTHER BOARDS. Brand new and tested complete with technical manual. £49.00 ref A49P1

UNIVERSAL BATTERY CHARGER. Takes AA's, C's, D's and PP3 nicads. Holds up to 5 batteries at once. New and cased, mains operated. £6.00 ref 6P36R.

IN CAR POWER SUPPLY. Plugs into cigar socket and gives 3,4,5,6,7,5,9, and 12v outputs at 800mA. Complete with universal spider plug. £5.00 ref 5P167R.

RESISTOR PACK. 10 x 50 values (500 resistors) all 1/4 watt 2% metal film. £5.00 ref 5P170R.

CAPACITOR PACK. 10 x 50 values (500 capacitors) all 1/4 watt 2% metal film. £5.00 ref 5P170R.

MIRACOM WS4000 MODEMS

V21/23

AT COMAND SET

AUTODIAL/AUTOANSWER

FULL SOFTWARE CONTROL

PHONE AND PULSE DIALLING

£29

WASHING MACHINE PUMP. Mains operated new pump. Not self priming. £5.00 ref 5P18R.

IBM PRINTER LEAD. (D25 to centronics plug) 2 metre parallel. £5.00 ref 5P186R

COPPER CLAD STRIP BOARD 17" x 4" of .1" pitch "vero" board. £4.00 a sheet ref 4P62R or 2 sheets for £7.00 ref 7P22R.

STRIP BOARD CUTTING TOOL £2.00 ref 2P352R.

50 METRES OF MAINS CABLE £3.00 2 core black precut in convenient 2 m lengths. Ideal for repairs and projects. ref 3P91R

4 CORE SCREENED AUDIO CABLE 24 METRES £2.00 Precut into convenient 1.2 m lengths. Ref 2P365R

TWEETERS 2 1/4" DIA 8 ohm mounted on a smart metal plate for easy fixing £2.00 ref 2P366R

COMPUTER MICE Originally made for Future PC's but can be adapted for other machines. Swiss made £8.00 ref 8P57R. Atari ST conversion kit £2.00 ref 2P362R.

6 1/2" 20 WATT SPEAKER Built in tweeter 4 ohm £5.00 ref 5P205R

ADJUSTABLE SPEAKER BRACKETS Ideal for mounting speakers on internal or external corners, uneven surfaces etc. 2 for £5.00 ref 5P207R

WINDUP SOLAR POWERED RADIO FM/AM radio takes rechargeable batteries complete with hand charger and solar panel 14P200R

240 WATT RMS AMP KIT Stereo 30-0-30 psu required £40.00 ref 40P200R

300 WATT RMS MONO AMP KIT £55.00 Psu required ref 55P200

BULL ELECTRICAL
 250 PORTLAND ROAD HOVE SUSSEX
 BN3 5QT TELEPHONE 0273 203500
 MAIL ORDER TERMS: CASH PO OR CHEQUE
 WITH ORDER PLUS £3.00 POST PLUS VAT.
 PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY

NEXT DAY DELIVERY £8.00

FAX 0273 23077

ALARM PIR SENSORS Standard 12v alarm type sensor will interface to most alarm panels. £16.00 ref 16P200

ALARM PANELS 2 zone cased keypad entry, entry exit time delay etc. £18.00 ref 18P200

MODEMS FOR THREE POUNDS!! Fully cased UK modems designed for dial up system (PSTN) no data or info but only £3.00 ref 3P145R

TELEPHONE HANDSETS Bargain pack of 10 brand new handsets with mic and speaker only £3.00 ref 3P146R

BARGAIN STRIPPERS Computer keyboards. Loads of switches and components excellent value at £1.00 ref CD40R

DATA RECORDERS Customer returned mains battery units built in mic ideal for Computer or general purpose audio use. Price is £4.00 ref 4P100R

SPECTRUM JOYSTICK INTERFACE Plugs into 48K Spectrum to provide a standard Atari type joystick port. Our price £4.00 ref 4P101R

ATARI JOYSTICKS Ok for use with the above interface, our price £4.00 ref 4P102R

BENCH POWER SUPPLIES Superbly made fully cased (metal) giving 12v at 2A plus a 6V supply. Fused and short circuit protected. For sale at less than the cost of the case! Our price is £4.00 ref 4P103R

SPEAKER WIRE Brown twin core insulated cable 100 feet for £2.00 REF 2P79R

MAINS FANS Brand new 5" x 3" complete with mounting plate quite powerful and quite. Our price £1.00 ref CD41R

DISC DRIVES Customer returned units mixed capacities (up to 1.44M) We have not sorted these so you just get the next one on the shelf. Price is only £7.00 ref 7P19R (worth it even as a stripper)

HEX KEYBOARDS Brand new units approx 5" x 3" only £1.00 each ref CD42R

PROJECT BOX 5 1/2" x 3 1/2" x 1" black ABS with screw on lid. £1.00 ref CD43R

SCART TO SCART LEADS Bargain price leads at 2 for £3.00 ref 3P147R

SCART TO D TYPE LEADS Standard Scart on one end, Hi density D type on the other. Pack of ten leads only £7.00 ref 7P2R

OZONE FRIENDLY LATEX 250ml bottle of liquid rubber sets in 2 hours. Ideal for mounting PCB's fixing wires etc. £2.00 each ref 2P379R

QUICK SHOTS Standard Atari compatible hand controller (same as joysticks) our price is 2 for £2.00 ref 2P380R

VIEWDATA SYSTEMS Brand new units made by TANDATA complete with 1200/75 built in modem infra red remote controlled qwerty keyboard BT approved Prestel compatible, Centronics printer port RGB colour and composite output (works with ordinary television) complete with power supply and fully cased. Our price is only £20.00 ref 20P1R

AC STEPDOWN CONVERTOR Cased units that convert 240v to 110v 3" x 2" with mains input lead and 2 pin American output socket (suitable for resistive loads only) our price £2.00 ref 2P381R

SPECTRUM +3 LIGHT GUN PACK complete with software and instructions £8.00 ref 8P58R

CURLY CABLE Extends from 8" to 6 feet! D connector on one end, spade connectors on the other ideal for joysticks etc (6 core) £1.00 each ref CD44R

COMPUTER JOYSTICK BARGAIN Pack of 2 joysticks only £2.00 ref 2P382R

BUGGING TAPE RECORDER Small hand held cassette recorders that only operate when there is sound then turn off 6 seconds after so you could leave it in a room all day and just record any thing that was said. Price is £20.00 ref 20P3R

IEC MAINS LEADS Complete with 13A plug our price is only £3.00 for TWO! ref 3P148R

COMPUTER SOFTWARE BARGAIN 10 cassettes with games for Commodore 64, Spectrum etc. Our bargain price one pound! ref CD44R

NEW SOLAR ENERGY KIT Contains 8 solar cells, motor, tools, fan etc plus educational booklet. Ideal for the budding enthusiast! Price is £12.00 ref 12P2R

POTENTIOMETER PACK No 1 30 pots for £3.00! ideal for projects etc. Ref CD45R

286 AT PC 286 MOTHER BOARD WITH 640K RAM FULL SIZE METAL CASE, TECHNICAL MANUAL, KEYBOARD AND POWER SUPPLY £139 REF 139P1 (no i/o cards or drives included) Some metal work req'd phone for details.

35MM CAMERAS Customer returned units with built in flash and 28mm lens 2 for £8.00 ref 8P200

STEAM ENGINE Standard Mamod 1332 engine complete with boiler piston etc £30 ref 30P200

TALKING CLOCK LCD display, alarm, battery operated. Clock will announce the time at the push of a button and when the alarm is due. The alarm is switchable from voice to a cock crowing! £14.00 ref 14P200R

HANDHELD TONE DIALLERS Small units that are designed to hold over the mouth piece of a telephone to send MF dialling tones. Ideal for the remote control of answer machines. £5.00 ref 5P209R

COMMODORE 64 MICRODRIVE SYSTEM Complete cased brand new drives with cartridge and software 10 times faster than tape machines works with any Commodore 64 setup. The original price for these was £49.00 but we can offer them to you at only £25.00! Ref 25P1R

USED SCART PLUGS Pack of 10 plugs suitable for making up leads only £5.00 ref 5P209R

C CELL SOLAR CHARGER Same style as our 4 x AA charger but holds 2 C cells. Fully cased with flip top lid. Our price £6.00 Ref 6P79R



A Transistor At The Crossroads

The unijunction transistor is one of the simplest semiconductor devices, yet it can be used in oscillators, trigger circuits, and delay circuits. Samuel Dick reveals all.

The unijunction transistor, first investigated in the late 1940s, is a three terminal device just like a normal transistor. However, while transistors owe their operational characteristics to two semiconductor junctions, the UJT as its name implies, has only one. This earns the device its alternative name of 'double base diode'. The UJT's symbol is shown in Fig 1. The device has an emitter and two base connections. Looking at the silicon structure of the device, it is fabricated from a single silicon bar formed from N-type silicon with a single junction of P-type semiconductor formed on the bar (Fig 2). Fig 3 shows a simplified equivalent circuit.

If we ignore the emitter connection, the resistance across the bar is a few thousand ohms. In normal operation, the Base 2 connection is made positive and current flows down the bar. Since the bar behaves like a simple resistor, the voltage seen at the point where the emitter connection is made is some

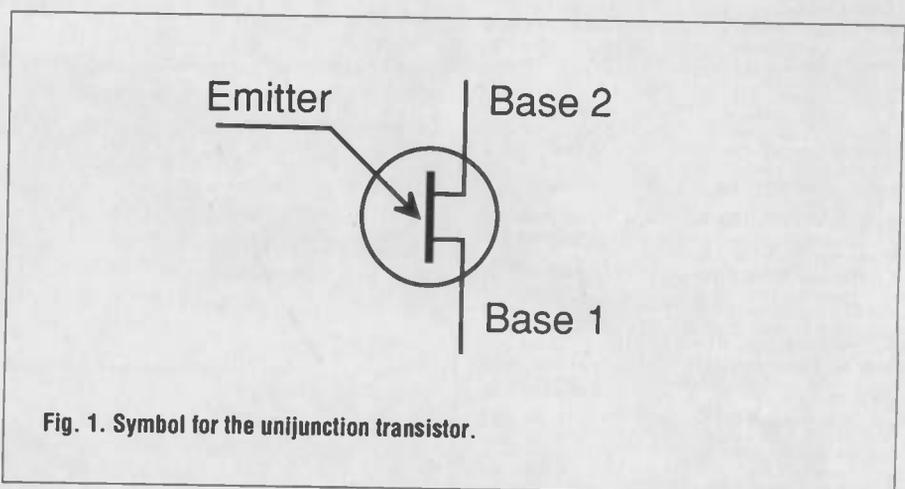


Fig. 1. Symbol for the unijunction transistor.

fraction of the supply voltage, the exact value depending on how far along the bar the emitter junction has been made. This fraction is known as the 'intrinsic stand-off ratio' and has the symbol η . The stand-off ratio typically has value from 0.4 to 0.8; the commonly available 2N2646 device has η between 0.56 and 0.75. The intrinsic stand-off ratio is an important characteristic of the UJT because it determines how the device works as a trigger.

In the equivalent circuit, the emitter is connected to the device via a diode: the voltage on the emitter terminal is less than that seen at the junction (that is, η times the supply voltage), only a small current will flow out of the device. Since this is the leakage current of the 'diode', its value is very small: currents of a few nano-amperes may be expected for normal operation con-

ditions. In this state, the current flow from Base 2 to Base 1 will also be small – only be a few hundred micro-amperes.

When the voltage on the emitter is increased so that the diode in the equivalent circuit is forward-biased – turned on – then current begins to flow in R_{B1} . This reduces the value of R_{B1} so the voltage difference across the diode is increased. This allows more current to flow from the emitter into the device, further reducing R_{B1} . This sets up a runaway condition during which the device can conduct quite heavily. The peak current for the emitter in a 2N2646 is 2 Amps! But note that the maximum Root Mean Squared (RMS) emitter current (the maximum average current) is only 50mA; the 2 Amp limit only allows for the rush of current when a capacitor is connected between the emitter and ground.

If the voltage supply on the emitter is such that it cannot be maintained above the value required to keep the junction conducting, the device will cease conducting and return to the 'off' state.

Fig. 2. Physical structure of the UJT


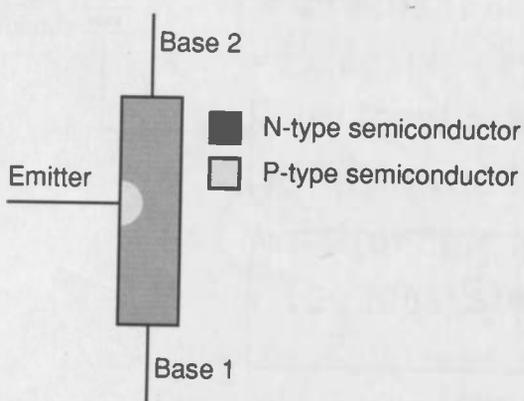



Fig. 3. Equivalent circuit for the UJT.

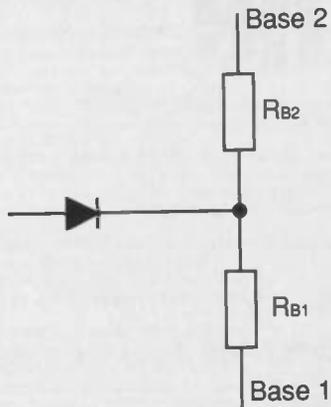

The UJT Oscillator

This is how the UJT is used as an oscillator. Fig 4 shows the circuit: R_2 and R_3 need not be considered for the moment. When power is first applied to the circuit, the capacitor, C_1 , is discharged and so V_e is zero. C_1 now charges up because of the current flowing through R_1 . Left undisturbed, the voltage across C_1 , V_c , would eventually equal the supply voltage, V_s . However, when V_c reaches the point at which the emitter is forward biased ($\eta V_s + 0.7$ Volts), the impedance seen through the emitter suddenly decreases and the UJT becomes a low resistance connected in parallel with C_1 . The result is that C_1 initially supplies a large current through the UJT. This flow of current discharges the capacitor and so lowers the voltage

Fig. 4. Simple oscillator circuit.

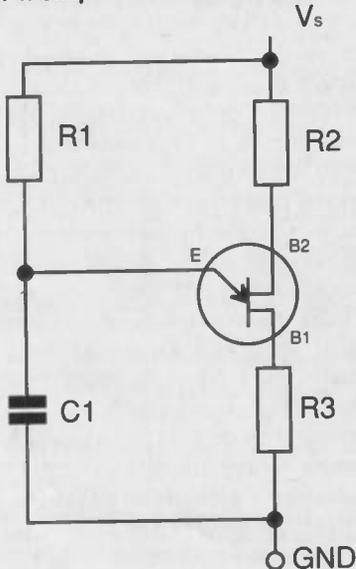

on the emitter. At some point, the voltage on C_1 is no longer sufficient to keep the junction forward biased and the UJT suddenly switches off. Now the voltage on C_1 will slowly rise again because of the charging current via R_1 - the UJT will only affect this process slightly since the leakage current through the reverse biased emitter will be very small ($<1\mu A$).

Hence, the whole cycle will repeat every time V_c reaches the trigger voltage, a pulse of current will flow through the UJT. The increased current causes the voltage across the two base resistors, R_2 and R_3 , to momentarily increase. Point A has a negative-going pulse while Point B has a positive-going pulse. The amplitudes of these pulses depend on the values of R_2 and R_3 .

The frequency of oscillation is controlled by how quickly C_1 can charge up again following a discharge pulse. By careful choice of R_1 and C_1 , frequencies from much less than 1Hz to near 1MHz may be obtained.

The pulse from the UJT may be used to drive a loudspeaker or piezo-sounder (Fig 5). It may also be used to trigger some other circuit.

Trigger

Another use for the UJT is as a simple trigger device. By connecting a resistor (R_c) in parallel with C_1 , a voltage divider is formed. The voltage fed to the emitter (with the UJT 'off') is $V_s R_1 / R_c$. While this voltage is below that required to trigger the UJT into conduction ($\eta V_s + 0.7$ Volts,

with $R_2 = R_3 = 100\Omega$), no current flows and so the voltage on Base 1 is $=0$. But when V_c exceeds the trigger voltage, the voltage at Base 1 increases to $=1$ Volt. This change could be used to trigger some other circuitry. But note that UJT's are made with a wide range of η so repeatability, from device to device, would not be very good - each circuit made would have to be set up individually.

Driving Thyristors

One of the most common uses of UJTs is as trigger devices for thyristors. The simplest application is a time delay circuit - either to turn a load on or off after a certain time,

In Fig 6, when power is first applied, the emitter of the UJT is at zero volts. The Base 1 is also nearly zero volts since only the ohmic leakage current of a few hundred microamperes is flowing through the UJT. The voltage on the capacitor will gradually rise and, at the trigger point, will turn the UJT on. The time taken for this to happen will depend on the time-constant of R and C ; with $1M\Omega$ and $2.2\mu F$ a delay of around 3s is realised. Once the UJT is triggered, the resulting pulse of current will create a voltage pulse across R_3 which will be seen by the gate of the thyristor and so turn it on. The UJT will continue to pulse but this does not matter since only the first pulse is required to turn on the power to the load - subsequent pulses are ignored.

The 'turn-off' circuit in Fig 7 is rather more complicated. Here, the thyristor which drives the load is

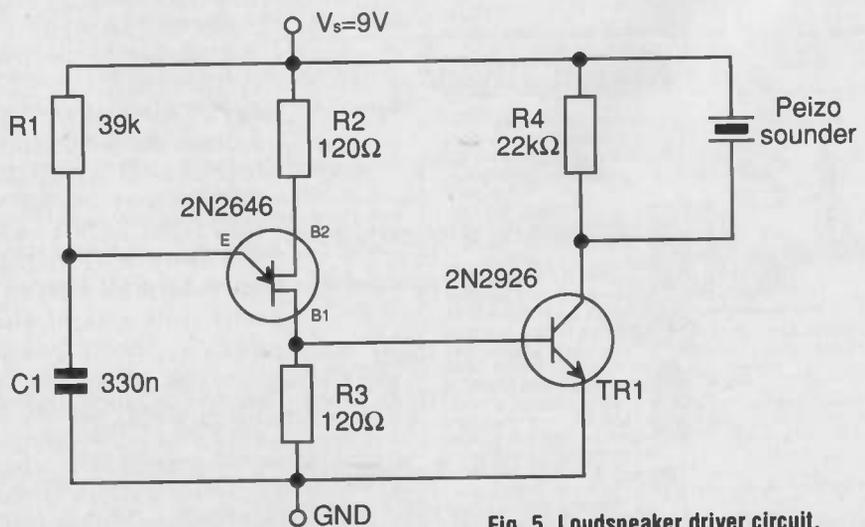


Fig. 5. Loudspeaker driver circuit.



Astronomy Now is Britain's leading amateur astronomy magazine.

It's topical and informative, keeping you up to date with the latest news in the astronomy world. It's extremely practical, telling you how to improve your observing and get maximum enjoyment from your hobby. Our contributors include the foremost names in the professional and amateur spheres.

- ★ Patrick Moore's Night Sky column ★
- ★ Features by and about the professionals ★
- ★ Practical advice from top amateurs ★
- ★ Extensive sky maps and finder charts ★
- ★ Entry level articles for complete novices ★
- ★ Advanced techniques for veterans ★
- ★ Astronomy and space science news ★
- ★ The most stunning astrophotography ★

Available from all good newsagents for £1.75 per month or by subscription from:

Astronomy Now, Subscription Department, Intra Press, FREEPOST, London W12 9BR

Annual rates £18 (UK), £21 (EC countries)

Payment by Visa, Access, cheque or postal order.

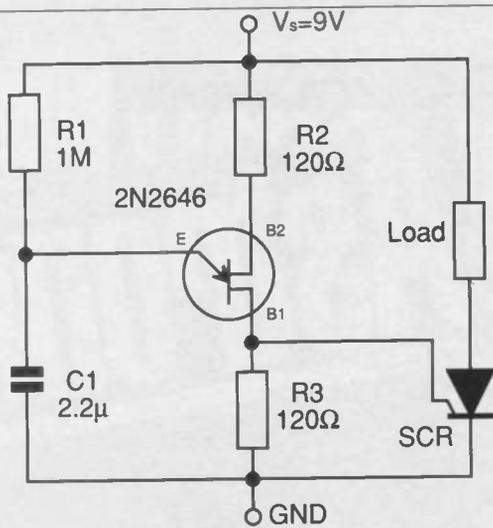


Fig. 6. Thyristor trigger circuit – delayed turn-on.

switched on immediately the power is applied, since its gate receives a pulse through C_1 . Once this initial pulse has turned on the thyristor, the gate is held low by R_4 ; power continues to be supplied to the load since thyristor is not latched on.

Once a thyristor has been triggered, it will stay on until the current flowing through decreases below the holding current. The value of the holding current depends on the current capacity of the thyristor; low power devices have holding currents of only a few milliamperes. Then the thyristor

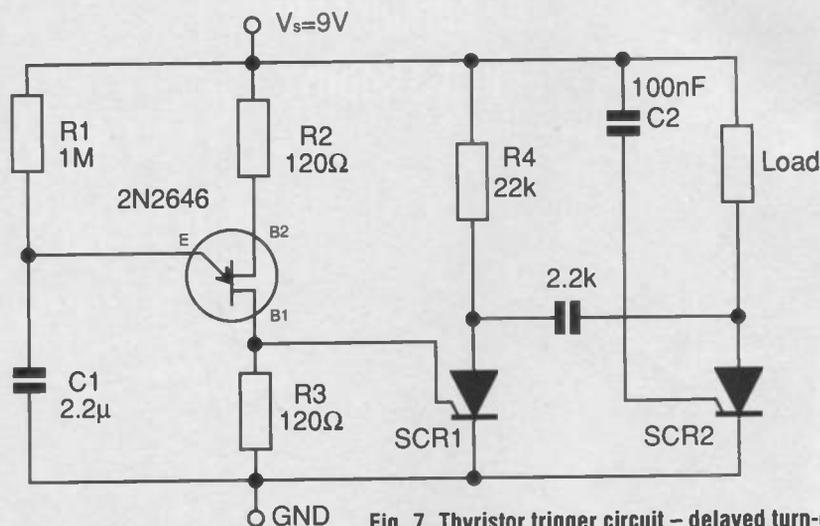


Fig. 7. Thyristor trigger circuit – delayed turn-off.

will switch off – and will stay off until another pulse is applied to its gate. The most obvious way of decreasing the current through the thyristor is to momentarily disconnect the load. A more subtle way is to divert the current into a capacitor for a short interval – only a few microseconds are required. This may be achieved by connecting a capacitor across the anodes of two thyristors as shown. By switching on the thyristor not connected to the load, the capacitor is grounded. The negative pulse fed to the load thyristor turns it off. By using the delay turn-on circuit of Fig 6 to fire the second thyristor, a delayed turn-off circuit is obtained. ■

MAKE YOUR INTERESTS PAY!

Over the past 100 years more than 10 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 100 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for **FREE INFORMATION** on the course of your choice. (Tick one box only!)

Electronics	<input type="checkbox"/>	TV, Video & Hi-Fi Servicing	<input type="checkbox"/>
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/>	Refrigeration & Air Conditioning	<input type="checkbox"/>
Electrical Engineering	<input type="checkbox"/>	Car Mechanics	<input type="checkbox"/>
Electrical Contracting/Installation	<input type="checkbox"/>	Computer Programming	<input type="checkbox"/>
GCSE/CCE/SCE over 40 examination subjects to choose from	<input type="checkbox"/>		

Name _____ Address _____
ICS International Correspondence Schools, Dept. EDS82
 312/314 High Street, Sutton, Surrey SM1 1PR. Or 041-221 7373 (24 hours).

Oakleaf Technology

Technical Authoring.
 PCB Design, Manufacture and Assembly.
 Electronic and Mechanical Engineering.

Ben Spencer
 100 Linsdale Street
 Swindon SN2 2BN
 England

Tel: +793 64 28 56

Send A5 SAE for technical procedures guide

Constructors!

GREL

SYSTEMS

PC Foundation Systems

(all including Motherboard, Case, 200W PSU; no RAM fitted)

Type 1 – 16 bit processor

16 MHz 296 (Desk Top Case)£139.50

Type 2 – 32 bit processor

25 MHz 386SX (Mini Tower Case)£199.50

Various accessories, (keyboards, monitors etc) available – please write or phone for more details.

Carriage, Terms

Add VAT to all prices. Carriage on Grel System components flat rate, regardless of order size: £4.50 (+ VAT)

Access and Visa accepted, no surcharge.

Greenbank Electronics, Dept PE08 460 New Chester Road,
 Rock Ferry, Birkenhead, Merseyside L42 2AE. Tel: 051-645 3391

New Technology Update

Ian Poole reports on new techniques in solar cell construction, wide bandwidth amplifiers and improvements in integrated circuit manufacturing.

Solar cells are seen by many as a very convenient and environmentally friendly source of power. However, to compete with more conventional forms it is estimated that their costs must fall by a factor of at least five. With existing semiconductor technology it is unlikely that this can ever be realised even if it is optimised to give the best performance. If solar cells are to provide a viable alternative source of power a totally new approach is required.

This may now be possible with a new technique developed in Germany. It involves a low cost technique for depositing a substance called cadmium telluride (CdTe). This enables efficient thin film CdTe solar cells to be made on inexpensive substrates including ordinary glass. By using this technique it is hoped to cut production costs to about a fifth of their current levels whilst still achieving efficiencies of just over 10%. It is also expected that by further development even higher efficiencies will be possible later.

Although a number of different materials can be used CdTe was chosen as the best. In tests it gave one of the highest conversion efficiencies. In addition to this it was rugged and provided a high degree of stability.

The new process is based around a specialised sublimation technique which produces polycrystalline CdTe films very rapidly on a variety of substrates. The process requires the use of a temperature of around 650C in a partially evacuated oven containing an inert gas. The CdTe source is located close to the substrate. At this temperature the material sublimates and

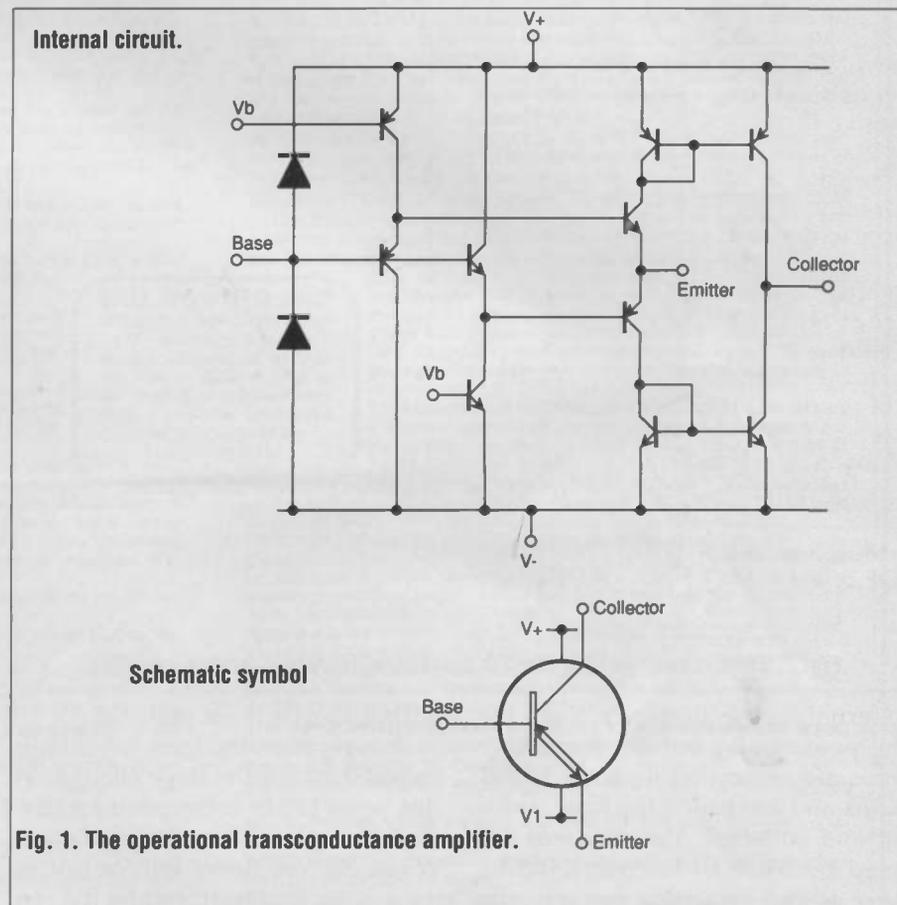


Fig. 1. The operational transconductance amplifier.

then "condenses" onto the substrate which is held at the lower temperature of 500C.


At the present time the process is still in its laboratory stages. However work is now progressing to develop a suitable production process. This is likely to take three years or more because this work needs to be undertaken very carefully to ensure that production costs are minimised.

Once the cells are in production it is estimated that there will be a large market in view of the growing demand for remote and sustainable energy sources. -

New For Wide Bandwidths

The quest for wider bandwidth analogue ICs has led Burr-Brown to develop a new type of circuit. Called the "diamond transistor" it functions as a voltage controlled current source or Operational Transconductance Amplifier (OTA). This new circuit has proved itself to be useful and versatile in a number of applications. It can be used as the basis for either a voltage or current feedback operational amplifier.

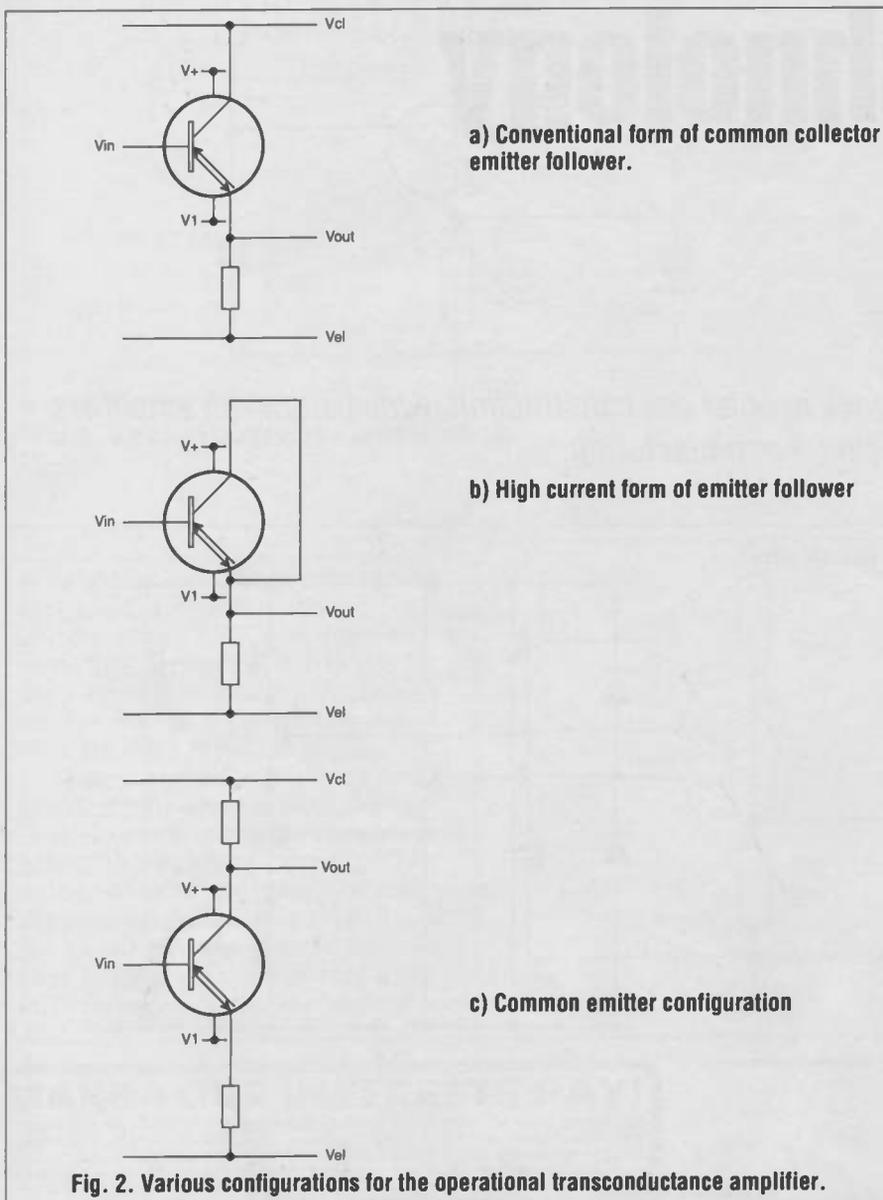The basic circuit consists of ten transistors and has a total of five



external connections. Two are for the power rails, but the remaining three are associated with the signal paths and are called the base, emitter and collector. These names are used because of the similarities have to the transistor ones. In the first instance the circuit can be used in the basic emitter follower configuration to give an impedance transformation and higher current capability. However there are some differences because it is possible to connect the collector to the emitter to increase its current capability.

The amplifier can also be used in a common emitter circuit. Again it shows many similarities. However it is found that there is a difference in the fact that the OTA does not give the standard 180° difference between input and output which is a characteristic of a true transistor circuit. Instead both the input and

output signals are in phase.

In operation the base has a high impedance. Any voltage changes at this point cause corresponding current changes in the emitter circuit. When current flows into or out of the emitter it is mirrored by the circuit for the collector. The ratio between the emitter and the collector is fixed by the internal parameters of the circuit making the circuit a complementary current source where the actual value of the current is determined by the voltage on the base.

To achieve a good high frequency response the circuit is fabricated using a complementary bipolar process with vertical transistors. These devices have very high transition frequencies, typically 3.5GHz for NPN transistors and 2.7GHz for PNP. This means that the whole amplifier is able to achieve a band-

width of 350MHz and a voltage gain of 4 when connected in an open loop configuration.

Although the circuit is used on its own the manufacturers expect its main use will be when it is incorporated within larger analogue ICs. As such it is only just beginning to see its full potential.

Improvements in ICs

Standards of cleanliness have to be exceedingly high in the production of semiconductor devices. ICs in particular demand very high standards. Poor cleanliness results in low yields and low long term reliability. This all means that if a manufacturer is to maintain his reputation, then cleanliness is of the utmost importance.

To improve standards Philips at Eindhoven has developed a new method for drying silicon wafers. Drying is often needed because the manufacture of a number of devices including ICs and liquid crystal displays often involves processes which use wet stages. These processes are usually followed by rinsing the wafer and then drying it. Once dried, traces of chemicals in the water are left on the surface of the semiconductor. These traces can greatly reduce yields and long term reliability.

Standard techniques involve rinsing the wafer and then spinning it to remove most of the water. This is not entirely satisfactory because some water still remains on the surface. In addition to this some stress damage can occur during the spinning.

To overcome these problems a vapour of a water soluble compound like iso-propyl alcohol is directed at the point where the wafers emerge from the rinsing bath. At this point the water absorbs the alcohol and as the wafer rises up out of the water a meniscus is formed. It is found that there is a larger concentration of alcohol at the top of the meniscus than at the bottom where it can be absorbed by the water more easily. In turn this causes a gradient in surface tension which encourages the water to flow off the wafer and back into the bath. This results in clean dry wafers emerging straight out of the bath without any need for spinning or drying. ■

BARGAINS - 10 New Ones This Month

SUPER MULTIMETER Ex British Telecom, this is a 10-range 20k o.p.v. top grade instrument, covers AC & DC voltages, current and resistance, very good condition, fully working and complete with leads £9.50, leather carrying case £2 extra (batteries not included but readily available).

MULTI-CORE CABLES all with 8A 230V cores so suitable for disco and other special lighting effects. With earthable woven screen and thick pvc outer. 3 core, 30p per metre, 16 core, 50p per metre, 18 core, 80p per metre, 25 core, £1 metre and 36 core, £1.50 per metre.

VARIAC an infinitely variable unit gives any voltage from 0-230 a.c. at 1/2A. Obviously an invaluable piece of equipment which should be in every workshop and probably would be except that the usual price for this is £36 plus VAT. Now is your chance to buy one, brand new, at £15 including VAT, Order Ref. 15P42B.

ULTRA THIN DRILLS Actually 0.3mm. To buy these regular costs a fortune. However, these are packed in half dozens and the price to you is £1 per pack, Order Ref. 797B.

YOU CAN STAND ON IT! Made to house GPO telephone equipment, this box is extremely tough and would be ideal for keeping your small tools. Internal size approx. 10 1/2" x 4 1/2" x 6" high. These are complete with snap closure lip and shoulder-length carrying strap. Taken from used equipment but in good condition, price £2, Order Ref. 2F283B.

BUILD YOUR OWN NIGHT LIGHT, battery charger or any other gadget that you want to enclose in a plastic case and be able to plug into a 13A socket. We have two cases, one 3 1/2" x 2 1/4" x 1 1/4" deep, £1 each, Order Ref. 845. The other one is 2 1/4" x 2 1/4" x 1 1/4" deep, 2 for £1, Order Ref. 565.

SAFETY LEADS curly coil so they contract but don't hang down. Could easily save a child from being scalded. 2 core, 5A, extends to 3m, £1, Order Ref. 846, 3 core, 13A, extends to 1m, £1 each, Order Ref. 847, 3 core, 13A, extends to 3m, £2 each, Order Ref. 2P260.

POWER SUPPLY WITH EXTRAS mains input is fused and filtered and the 12V dc output is voltage regulated. Intended for high class equipment, this is mounted on a PCB and, also mounted on the board but easily removed, are 2 12V relays and a Piezo sounder, £3, Order Ref. 3P80B.

5V 2.5A POWER SUPPLY UNIT £3, Order Ref. 5P186.

ULTRA SONIC TRANSDUCERS 2 metal cased units, one transmits, one receives. Built to operate around 40kHz. Price £1.50 the pair, Order Ref. 1.5P/4.

100W MAINS TRANSFORMER normal primaries 20-0-20 at 2.5A, or 30V at 3.5A, £4, Order Ref. 4P24. 40V at 2.5A, £4, Order Ref. 4P50. 50V at 2A, £4, Order Ref. 4P60.

PHILIPS 12" HIGH RESOLUTION MONITOR black & white in metal frame for easy mounting, brand new still in maker's packing, offered at less than price of tube alone, only £16, Order Ref. 15P1.

16 CHARACTER 2-LINE DISPLAY screen size 85mm x 36mm, Alpha-numeric LCD dot matrix module with integral micro processor made by Epson, their Ref. 16027AR, £8, Order Ref. 8P48.

INSULATION TESTER WITH MULTIMETER internally generates voltages which enable you to read insulation directly in megohms. The multimeter has four ranges, AC/DC volts, 3 ranges DC millamps, 3 ranges resistance and 5 amp range. These instruments are ex British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50 each, yours for only £7.50, with leads, carrying case £2 extra, Order Ref. 7.5P/4.

BRUSHLESS DC 12V FAN tiny, only 80mm square, good air mover but causes no interference, £8, Order Ref. 8P28.

MAINS 230V FAN best make "PAPST" 4 1/2" square, metal blades, £8, Order Ref. 8P8.

2MW LASER Helium neon by Philips, full spec. £30, Order Ref. 30P1. Power supply for this in kit form with case is £15, Order Ref. 15P16, or in larger case to house tube as well £18, Order Ref. 18P2. The larger unit, made up, tested and ready to use, complete with laser tube £68, Order Ref. 68P1.

1/3 HP 12V MOTOR - THE FAMOUS SINCLAIR C5 brand new, £15, Order Ref. 15P8.

SOLAR CHARGER holds 4 AA nicads and recharges these in 8 hours, in very neat plastic case, £6, Order Ref. 6P3.

FERRITE AERIAL ROD 8" Long x 1/4" diameter, made by Mullard. Complete with 2 coil forms. 2 for £1, Order Ref. 832B.

AIR SPACED TRIMMER CAPS 2-20 pf ideal for precision tuning UHF circuits, 4 for £1, Order Ref. 818B.

FIELD TELEPHONES 6 just right for building sites, rallies, horse shows, etc. Just join two by twin wire and you have two way calling and talking and you can join into regular phone lines if you want to. Ex British Telecom in very good condition, powered by batteries (not included) complete with shoulder slung carrying case, £9.50, Order Ref. 9.5P/2.

MAINS ISOLATION TRANSFORMER stops you getting "to earth" shocks. 230V in and 230V out. 150watt upright mounting, £7.50, Order Ref. 7.5P/5 and a 250W version is £10, Order Ref. 10P70.

LIMITED SUPPLY ITEMS

are only described in our newsletter. Over 50 appear in our current issue. If you order something this month you will receive this and the next three issues posted to you free of charge.

MINI MONO AMP on PCB. Size 4" x 2" with front panel holding volume control and with spare hole for switch or tone control. Output is 4 watt into 4 ohm speaker using 12V or 1 watt into 8 ohm using 9V. Brand new and perfect, only £1 each, Order Ref. 495.

SRPM MAINS DRIVEN This is a shaded pole motor, £5, Order Ref. 5P54.

POWER SUPPLY UNIT mains in, dc out, cased 4.5V 100mA, £1, Order Ref. 104, 6V 200mA £1, Order Ref. 103, 6V 700mA, £1, Order Ref. 103A, 9V 500mA, £2, Order Ref. 2P134, 24V 200mA, £2, Order Ref. 2P4, 12V 2A, £6, Order Ref. 6P23.

AMSTRAD POWER UNIT 13.5V at 1.9A encased and with leads and output plug, normal mains input £8, Order Ref. 6P23.

AMSTRAD 3.5 FLOPPY DRIVE brand new and cased, £35, Order Ref. 26P4.

ATARI 85XE at 85K this is quite powerful, so suitable for home or business, unused and in perfect order but less PSU, only £18.50, Order Ref. 18.5P/5B.

50W MAINS TRANSFORMER two available, good quality, both with normal primaries and upright mounting, one is 20V 4A, Order Ref. 3P106 the other 40V 2A, Order Ref. 3P107, only £3 each.

PROJECT BOX size approx 6" x 4" x 4 1/2" metal, sprayed grey, louvred ends for ventilation otherwise undrilled. Made for GPO so best quality, only £3 each, Order Ref. 3P74.

12V SOLENOID has good 1/2" pull or could push if modified, size approx 1 1/2" long x 1" square, £1, Order Ref. 252.

WATER VALVE 230V operated with hose connections, ideal for auto plant spray or would control air or gas into tanks etc., £1 each, Order Ref. 370.

10W ISOLATION TRANSFORMER if you want to isolate some small piece of equipment from earth this may be what you are looking for. You can use it either with a tapped input or a tapped output. It's upright mounting and well insulated. Price £1, Order Ref. 821.

BT POWER SUPPLY UNIT output 9.5V AC at 800mA, in black plastic case with 13A plugs to go straight into socket and approximately 3 metres of twin output lead. Price £1.50, Order Ref. 1.5P7.

BUILDING YOUR OWN PSU, battery charger, night light, or any other gadget that you want to enclose in a plastic case and be able to plug into a 13A socket? We have two cases, one 3 1/2" x 2 1/4" x 1 1/4" deep, £1 each, Order Ref. 845. The other one is 2 1/4" x 2 1/4" x 1 1/4" deep, 2 for £1, Order Ref. 565.

500V BRIDGE MEGGER developed for GPO technicians the Ohmster 12B is the modern equivalent of the bridge megger. 9V battery operated, it incorporates a 500V generator for insulation testing and a null balance bridge for very accurate resistance measurement. Ex B.T. in quite good condition with data & tested. Yours for a fraction of original cost, £45, Order Ref. 45P2.

EXPERIMENTING WITH VALVES don't spend a fortune on a mains transformer, we can supply one with standard mains input and secs. of 250-0-250V at 75mA and 6.3V at 3A, £5, Order Ref. 5P167.

15W 8 OHM 8" SPEAKER & 3" TWEETER made for a discontinued high quality music centre, gives real hi-fi, and only £4 per pair, Order Ref. 4P57.

FREE POWER! Can be yours if you use our solar cells - sturdily made modules with new system bubble magnifiers to concentrate the light and so eliminate the need for actual sunshine - they work just as well in bright light. Voltage output is .45 - you join in series to get desired voltage - and in parallel for more amps.

Module A gives 100mA Price £1 Order Ref. B0631

Module B gives 400mA Price £2 Order Ref. 2P199

Module D gives 700mA Price £3 Order Ref. 3P42

Module E gives 1A Price £3.50 Order Ref. 3.5P4

3V SOLAR PANEL price £3, Order Ref. 3P98B.

3 GANG 1000 MFD TUNING CONDENSER with slow motion drive. Beautifully made by Jackson Brothers and current flat price is probably around £20. Yours for £5, Order Ref. 5P186.

STEREO HEADPHONES extra lightweight with plug, £2 each, Order Ref. 2P261.

BT TELEPHONE LEAD 3m long and with B.T. flat plug ideal to make extension for phone, fax, etc. 2 for £1, Order Ref. 552.

WATER PUMP very powerful with twin outlets, an ideal shower controller, mains operated, £10, Order Ref. 10P74

STUDIO 100 by Amstrad, the ultimate disco control panel, has four separately controlled and metered channels, twin cassettes, AM/FM radio, stereo audio amplifier, phono & CD inputs, etc., regular price over £400, we have a few still in maker's packing, brand new and guaranteed, yours for £99, Order Ref. 99P1.

0-1MA FULL VISION PANEL METER 2 1/2" square, scaled 0-100 but scale easily removed for re-writing, £1 each, Order Ref. 750.

VU METER illuminate this from behind becomes on/off indicator as well, 1 1/2" square, 75p each, Order Ref. 368.

EDGE-WISE PANEL METER ideal when short of panel space only 40 x 14mm, also have built-in led, 500µA t.s.d, scaled 0-5, £1 each, Order Ref. 131.

PCB DRILLS 12 assorted sizes between .75 and 1.5mm, £1 this lot, Order Ref. 12B.

THIS MONTH'S SNIP

A £60 UNIT FOR LESS THAN £10 - switch mode power supply with outputs +12V at 4A, +5V at 16A and -12V at 1/2A. Enclosed in plated steel case, brand new, offered at a special price of £9.50 until July 31st, Order Ref. 8.5P1.

JUST ARRIVED


3 core 15A flex. Price is 10m for £2.50, Order Ref. 2.5P/3.

You can have this in longer lengths, multiples of 10m up to 100m. Also available: 3 Core 20A flex, 10m for £3, Order Ref. 3P109 and 2 core 20A flex, 15m for £3, Order Ref. 3P110.

DIGITAL FREQUENCY METER.

This is a hand-held instrument with an LCD display allowing 8 digits of frequency to be read, has internal nicad batteries, and a power supply which will recharge the batteries. Ideal for field and service work as well as general and industrial applications.

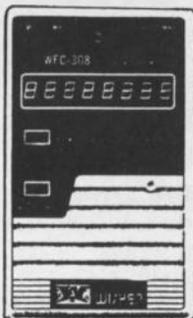Has high and low BNC inputs and a plug-in antenna which enables remote tests. It covers a very wide range of frequencies: switch position 'A' covers 10Hz to 20MHz and switch position 'B' covers 20MHz to 1200MHz. Price £99, but it compares very favourably with instruments selling at over £500 by our competitors. Order Ref. 99P2.



Prices include V.A.T. Send cheque/postal order or ring and quote credit card number. Add £3 post and packing. Orders over £25 post free.

M & B ELECTRICAL SUPPLIES LTD
12 Boundary Road, Hove, Sussex BN3 4EH
Telephone (0273) 430380
Fax or phone (0273) 410142

New Practical Electronics

1992 Readers' Survey

At Practical Electronics we care what our readers think of the magazine. We'd like you to help us produce the magazine you really want to read by filling in and returning this short questionnaire. If you'd like to take part, simply go through the questions ticking or writing in as appropriate, then send the completed form to PE 1992 Reader Survey, FREEPOST, London W12 9BR. It won't cost you a stamp unless you live outside the United Kingdom. Use a photocopy if you prefer not to damage your magazine.

As a special bonus, Sony Recording Media Company have provided 50 of their UX Turbo 90 minute Super Chrome Position car stereo cassettes which we'll give to the first 50 replies we pull out of the editorial hat on the 18th August.

Where did you obtain this copy of Practical Electronics?

- ...By subscription
 - ...Regular order with newsagent
 - ...Casual purchase from local newsagent
 - ...Casual purchase from high street newsagent
 - ...Casual purchase from station/travel point
 - ...Casual purchase from street news-stand
 - ...Other

In the past six months, how many issues of Practical Electronics have you bought?

- ...6 issues ...5 issues ...4 issues ...3 issues ...2 issues ...1 issue

How long have you been a regular reader of Practical Electronics?

- ...For up to six months
- ...One year
- ...Two to five years
- ...Over five years
- ...I am not a regular reader
- ...This is the first issue I have bought

Does anyone other than you read your copy of Practical Electronics?

- ...Yes ...No ...If yes, how many?

Practical Electronics regularly contains articles of the types listed below. Please indicate your degree of interest in each type of article

	Very interested	Moderately interested	Not very interested	Not interested
1 News				
2 Product reviews				
3 Comment (eg Barry Fox)				
4 General feature				
5 Show report				
6 Construction project				
7 Technical feature				

What do you like best about Practical Electronics?

Do you regularly read a newspaper?

If so, which newspaper?

Do you regularly read any news or lifestyle magazines?

If so, which ones?

Do you regularly read any of these other Electronics/Science/Technology magazines?

- ...Maplin Magazine
- ...Everyday Electronics
- ...Popular Electronics
- ...Computer Shopper
- ...Personal Computer World
- ...Nature
- ...Science Probe
- ...Scientific American
- ...New Scientist
- ...PC Direct
- ...Sound & Vision Shopper
- ...What Video
- ...What HiFi
- ...Byte
- ...PC Plus

Which of the following equipment do you own, or intend to buy or upgrade in the next year?

	Own.....	Buy	Upgrade
Video cassette recorder	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Computer (eg Atari ST, Commodore Amiga, PC)	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
CD-I/CD-TV	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Satellite dish and decoder	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Cable TV connection	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Fax machine/telephone answering machine	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
High Definition or Wide Screen TV	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Video Camera (8mm or C-VHS) and editing equipment	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Portable radio/cassette/CD/DCC	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Hi-Fi radio/cassette/CD/record deck	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Pocket TV/Pocket Hi-Fi (eg Sony Watchman or Diskman)	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Pocket electronic game (eg Nintendo GameBoy)	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
TV console electronic game (eg Super NES)	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Personal organiser or palmtop computer	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Musical equipment (effects, mixers, MIDI, synthesisers)	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

What age-group are you?

...Under 16 ...16-24 ...25-34 ...35-44 ...45-54 ...55-64 ...65+

Sex

...Male ...Female

Occupation

...Manual ... Office ...Unemployed or retired

Your income

Gross annual income

Up to £5,000 £5,001-£10,000 £10,001-£15,000 £15,001-£20,000 £20,001-£25,000 Over £25,000

Qualifications held

.....

Where do you live?

...City ...Large town ...Small town ...Rural/village

Please fill in your name and address, if you wish to enter the prize draw

Name

Address

Town/County

Postcode(Country).....

Prize draw entry rules: 1- The draw is open to anyone who returns this filled-in response form or a photocopy before the 18th August 1992. Completed forms must arrive by second post on the 17th August. We accept no responsibility for lost forms or delays in posting. 2- Only one entry per reader will be accepted 3- The first fifty names drawn at random will be prize winners. 4- The prize draw will take place on the 18th August 1992 and the winners will be informed by post by the 31st August 1992. 5- The draw is not open to employees of Intra Press. 6- The Publisher's decision will be final and no correspondence will be entered into regarding the outcome of the draw.

Test drive a Sony tape



Sony, the originator of the audio tape, has taken the first step towards simplifying the customer's choice by introducing a tape specifically designed for in-car stereo use.

The selection of optimum tape formulation and shell construction, combined with unique features, creates a product which offers enhanced use with In-Car Entertainment systems.

Sony UX Turbo tapes improve durability and functionality with these special features:

- Rigid welded shell reduces tape vibration
- 115° Centigrade heat resistant shell that stops it warping
- No-slip grip and raised marker on shell for ease-of-use
- Special adhesive labels that won't jam cassette players

Sony Turbo Super Chrome Position tapes have one of the lowest bias noise levels.

Sony is a registered trademark of Sony Corporation, Japan

Information given in your reply may be made available to other organisations for mailing and marketing purposes. Please tick this box if you do not wish to receive such information ...

Practical Electronics Classifieds

Reach thousands of serious electronics enthusiasts with your message. Take advantage of our free classified advertisements with the form on page 47. For commercial advertisements or semi-display (boxed advertisements), contact David Bonner on 081-743 8888. Send to *Practical Electronics Classifieds, Intra House, 193 Uxbridge Road, London W12 9RA*

Education

Start training now for the following courses.

- Telecomms Tech C&G 271
- Radio Amateur Licence C&G
- Microprocessor
- Introduction to Television

Send for our brochure - without obligation or telephone us on 06267 79398 (Ref: PE8/92)
Name.....

Radio & Telecommunications
Correspondence School,
12 Moor View Drive, Teignmouth,
Devon TQ14 9UN

Retailers

Project your retail image here!



Phone David Bonner
for details on
081-743-8888

LONDON N WEST

CRICKLEWOOD ELECTRONICS

One of the largest ranges of components in the UK!

40 Cricklewood Broadway,
LONDON NW2 3ET

Tel: 081-450 0995/452 0161

**Modernising your workshop?
Sell your old equipment
through PE Classifieds pages.**

FOR SALE

Practical Electronics
in Binders volumes one
(1965) to ten (1974) and
later loose copies. Offers
for lot (0905) 54318.

Computer Parts

CAMBRIDGE COMPUTER SCIENCE LIMITED

LCD modules,.....	16 char by 1: £4.00, 20 char by 2: £8.00, 40 char by 1: £8.00
5.25" Disk Drives, 80 Tk, DSD£25.00 each
5.25" Disk Drives, 80 Tk, DSDD Used, No Why£9.00 each
<small>(The £9.00 drives are sold on a 'as is' basis)</small>	
5.25" Disks, DSDD, 48dpi, boxes of 10 (free disk cleaner with 5 boxes)	£3.00/box
Digital multimeter, 14 ranges, inc leads & manual£10.00 each
Apricot Disk drive PSU 5V @ 2.5A, 12V @ 2A£10.00 each
Disk Drive Data lead BBC Micro to Disk Drive(s).....	Single £2.00 Dual £4.00 each
Disk Drive Power lead BBC Micro to Disk Drive(s) Single	£2.00 Dual £4.00 each
8088 CPU chips£2.00 each
Z80A CPU, CTC, PIO	£1.20 each; DMA £2.00
27128 EPROMS (Ex equipment)£1.20 each or £5.00/5
256K DRAM (Ex equipment)£0.40 each
1MBit-10 DRAM (Ex equipment)£1.40 each
256K Byte DRAM Modules, removed from equipment£6.00 each
16, 18 & 20 pin di low profile IC sockets 0.3" wide	£0.40/10
22 & 24 pin di low profile IC sockets 0.4" wide	£0.40/10
24, 28, 32, 40 & 48 pin di low profile IC sockets 0.6" wide	£0.40/10
Circuit tester, finds faults in TTL & CMOS logic circuits, inc leads£8.00 each
Metal project boxes drilled & painted but unused 28 x 32.5 cm£5.00 each
Used computer cards many useful components (large ones socketed)	
Flippy disk card (NEC FDC chip) £1.00	Wired controller (WD HDC chip) £1.00 each
CPU card (8088, Z80 & EPROMS)£3.00 each
Keyboards, full QWERTY, number pad and LCD£8.00 each
Desktop computer case with 200W mains PSU (used)£30.00 each

Prices include postage. Add 5% (plus VAT) to orders below £5.00
All items new unless stated. Add 17.5% VAT to all prices.
Send an SAE for our latest list or for more info.
Dept PE, 574 Milton Road, Cambridge, CB4 1SU
Tel: 0223 424062, 0831 430408 or 0831 430562 (Mail order only)

Components

CATALOGUE £1.00 + 25 P&P

LEDs 3mm or 5mm red/green6p each. Yellow 11p each,
High intensity red, green or yellow 5mm 30p each	
Cable ties 1p each	£5.95/1,000 £49.50 per 10,000
Stepping motor 4 phase 12V 7.5' step 50 ohms£8.95
SAAL027 stepping motor driver chip£3.95
FM Transmitter kit good quality sound£8.60
High quality photo resist copper clad epoxy glass boards	
Dimensions	single sided double sided
3x4 inches	£ 0.95 £1.07
4x8 inches	£ 2.40 £2.68
6x12 inches	£ 5.37 -
12x12 inches	£10.66

Special Offers

Computer Grade Capacitors with screw terminals 38000µf 20V£2.50
87,000µf 10V £1.95, 68,000µf 15V £2.95, 10,000µf 16V£1.50
7 segment Common anode led display 12mm£0.45
LM2931ATS.0 Low drop out 5V regulator T0220 package£0.85
BS250 P channel MOSFET £0.45, BC559 transistor£3.95 per 100
74LS05 hex inverter £10.00 per 100, used 8748 Microcontroller£3.50
TV Main switch 4A double pole with momentary contacts for remote control pack of 10	£3.95 box of 60 £19.95.
DC-DC converter Reliability model V12P5 12v in 5v 200ma out 300v input to output Isolation with data \$4.95 each or pack of 10£39.95
Hour counter (used) 7 digit mains 240V AC 50Hz£1.45
Resistor pack 2500 resistors 1/8-2W 50 different values£8.95
Qwerty keyboard 58 key good quality switches new£5.00
Qwerty keyboard with serial output, no data£5.00

Wide range of CMOS TTL 74HC 74F Linear transistors kits
Rechargeable batteries, capacitor tools etc always in stock.
Please add 95p towards P&P - VAT Included

JPG Electronics 276 - 278 Chatworth Road
Chesterfield S40 2BH

**Practical Electronics Classifieds
list the best sources for unusual or
back catalogue components**

Surplus

TURN YOUR SURPLUS

ICS transistors etc into cash, immediate settlement. WE welcome the opportunity to quote for complete factory clearance.

Contact:

COLES-HARDING & CO.,
103 South Brink, Wisbech, Cambs.
ESTABLISHED 15 YEARS
Tel: 0945 584188 - Fax: 0945 588844

Recycle your old projects and generate useful cash from spare components

Miscellaneous

Greenweld Newslines 0891 505 121

Calls charged at 36p/min cheap rate, 48p/min other times
For a weekly update on our latest surplus bargains – call now!! Our latest list FREE from GREENWELD, 27 Park Road, Southampton SO1 3TB

73 AMATEUR RADIO TODAY

Broaden your horizons.

Subscribe to the world's leading Radio Ham magazine. European rates for surface and air mail available on request from:

73 Amateur Radio Today
PO Box 50330
Boulder, CO.
80321-0330
USA

Study Electronics on the BBC Micro. An interactive approach to learning. Four program titles available. 'Introduction to Electronics Principles', 'Electronics Mathematics', 'Digital Techniques' and now 'Programming for Electronics'. Programs include theory, examples, self test questions, formulae, charts and circuit diagrams. User inputs and calculated outputs. £29.95 each + £2.00 P&P. Cheque or Postal Order to EPT Education Software, Pump House.

Components

SURPLUS/REDUNDANT ELECTRONICS COMPONENTS WANTED

ICs - Tuners - Transistors - Valves - Diodes etc - any quantity considered - immediate payment.

ADM ELECTRONICS SUPPLIES
Tel 0827 873311 Fax: 0827 874835



Cooke International

FOR SALE
Wide range of used test equipment also manual copy service available

Saturdays Only
Open our bargain store 10am-4pm
Cash items to clear

Contact: Cooke International, Unit Four Fordingbridge Site, Main Road, Barnham Bognor Regis, West Sussex PO22 0EB

Tel: 0243 545111 Fax: 0243 542457

Open
Mon-Fri 9am-4:30pm
Send SAE for lists

SOLAR PANELS

Special offer. 12V nominal (20V OC), 80 milliamps, 12 inch x 6 inch pre-wired amorphous silicon panel £4.50. Many other sizes, wind generators and other products. Orders to:

Robert Keyes, Gwlied, 4 Glanmor Crescent, Newport NP9 8AX
Catalogue 2 x 1st class stamps

Problems with your project?

Kit assembly, problem investigations, design work undertaken. Hourly rates or fixed prices available. Contact **SEDS, 205 London Road, Westcliff-on-Sea, Essex SS0 7BP**

Wanted: Set of Practical Electronics 1964 to approx 1980. Mr Bristow, 6 Finmere, Bracknell, Berkshire RG12 7WF, or 0344 425638 after 9PM.
PTFE

Surveillance

Suma Designs
sell top quality surveillance equipment in kit form or as ready built units.
See our full page display ad in this issue

Contact

HST for all your component needs. Send for your free catalogue and details of special offers.

**HST Ltd,
Technology House,
Prospect Road,
Carlton, Nottingham
NG4 6LA**
Tel: 0602-587225
Fax: 0602-484530

OMNI ELECTRONICS

stock a wide range of electronic components at
174 Dalkeith Road, Edinburgh EH16 5DX
Tel: 031 667 2611

Open Mon-Thu 9.15am-6.00pm
Fri 9.15am-5.00pm
Sat 9.30am-5.00pm

1990/91 catalogue costs £1.50
contains vouchers to use against purchases
Do you have your copy yet?

PTFE Low Friction material in 0.8mm sheet at 25p per square inch and 10mm thick blocks at £1.00 per square inch. SAE for details of Telescope Drive Systems and clocks. AWR Technology, 67 Thornbridge Road, Deal, Kent.

To book your free classified ad use this form or a photocopy and send it to David Bonner, PE Classifieds, Intra Press, Intra House, 193 Uxbridge Road, London W12 9RA. This scheme is for private individuals only. We cannot accept bookings by phone. Commercial advertisers may contact David Bonner on 081 743 8888 for rates and credit card bookings.

Build An Auto-Ranging Tuning Fork

This month's project is an all electronic way of tuning musical instruments to an accuracy of one eighth of a note. John Becker explains how to build it.

Players of acoustic and electronic music instruments can all benefit from this tuning aid. Consisting of a frequency counter and electronic look-up table, it analyses a musical input signal and displays data about its octave, note and tuning accuracy on three banks of LEDs (light emitting diodes). Data is split into 12 notes per octave, encompassing six octaves across the frequency range 54Hz to 2047Hz. Tuning accuracy is to within one eighth of a note. A reference tone generator is included as an optional extra. Acoustic instruments are monitored via a microphone input and variable gain preamp. Electronic instruments may be plugged in directly.

The block diagram for the complete tuner is shown in Fig.1. Fig.2 shows the main control and display circuit, excluding the reference tone generator.

Timing Control

Sampling of the musical input frequency is carried out at a rate of 1Hz. A master clock frequency of 32768Hz is generated by the crystal controlled circuit around IC1a. IC2, a 12-stage binary ripple counter, divides this frequency by 4096, producing an 8Hz output at its Q11 pin. One half of the dual 4-stage binary counter IC3 (IC3a) further divides the rate by eight. The positive-going edge of each 1Hz square wave pulse at IC3a's QA2 output triggers one half of the dual monostable IC4. The resulting anti-phase pulses at pins 6 and 7 of IC4 control the latching of the LED-driving control registers IC6 and IC9-IC11. R3 and C4 set the latch pulse duration to about 1 microsecond. When IC4 pin 7 reverts high at the end of the timed period, the positive-going transition triggers the second

monostable within IC4, resulting in a positive-going pulse from pin 10. This is the system's master reset pulse and its duration is set at about 1 microsecond by R4 and C5.

Toning Up

The principal input to the circuit is via the pre-amp stage around IC5a. Electronic instrument signals may be connected directly to this stage. Alternatively, a high-output microphone may be plugged in for monitoring acoustic instruments. VR1 is a panel-mounted control which sets the stage gain to between x1 and x100. The output from IC5a is fed to the comparator stage around IC5b which further amplifies and squares the amplitude of signals above the hysteresis threshold set by R8 and R11 in conjunction with the reference level set by R9 and R10.

Passing via S2, the outputs are

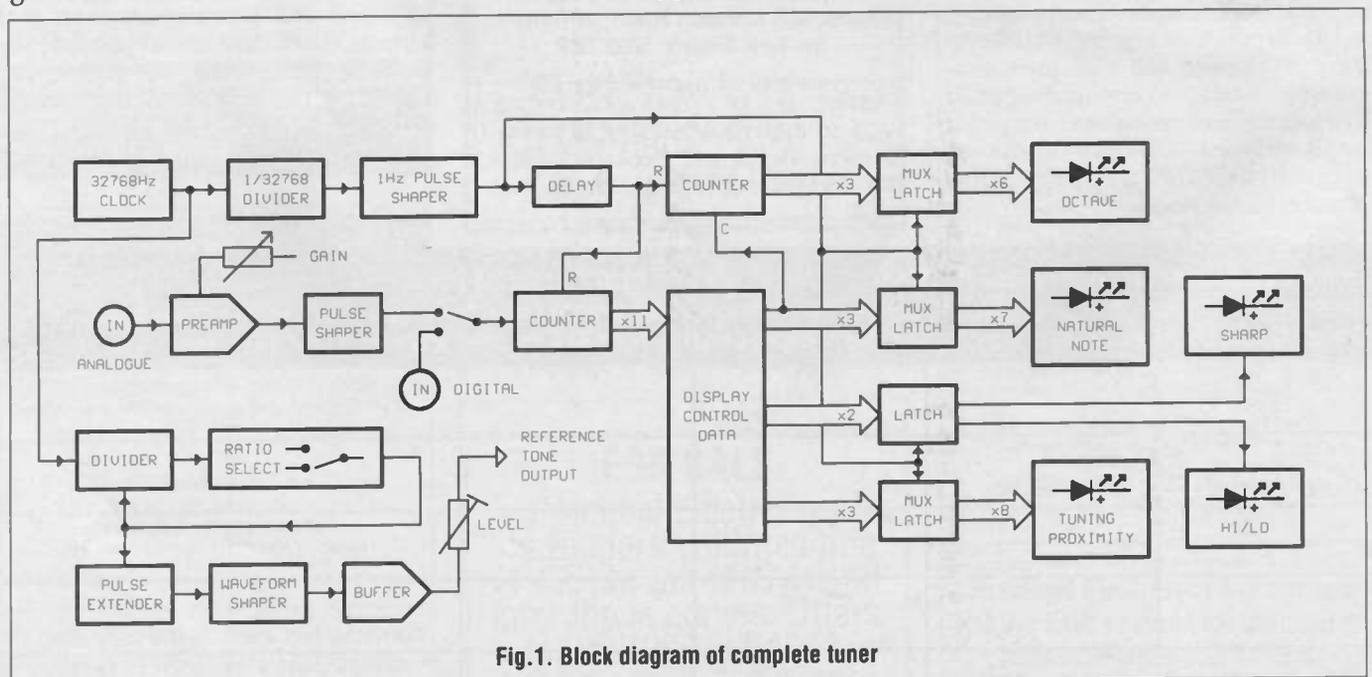


Fig.1. Block diagram of complete tuner

brought up to full line level by the Schmitt inverter IC1c and provide the clock pulses for the 12-stage binary counter IC7. Electronic musical instruments producing constant-amplitude pulses may be brought directly into IC1c via the second path of S2. The maximum amplitude may be between about 4V and 9V. The minimum amplitude should be less than 1V but not significantly lower than 0V.

IC7 counts the output pulses received from IC1c over a period of exactly one second and its outputs provide the address code to the look-up table held within the EEPROM (electrically erasable programmable read only memory) IC8. The memory holds data codes which provide information on how the sampled frequency relates to musical tones. The first three bits (D0-D2) of the 8-bit code hold the tone values as numbers between 0 and 7, representing notes A-G. Bit D3 indicates whether the note is a natural tone or a sharp. Bits D4-D6 provide information on how close the monitored frequency is to the precise frequency for a given note. Bit D6 indicates whether the monitored tone is above or below the optimum tuning pitch.

Outputs D0-D2 and D4-D6 are routed to inputs A0-A2 of the two latching multiplexers IC9 and IC11, providing the respective address codes which control their output lines. At the end of each one second counting period, pins 4 of IC9 and IC11 receive a negative-going pulse from IC4 pin 7 which transfers the data on the address inputs to an internal register. The address sets the corresponding output line high, providing current to a monitoring LED. LED7-LED13 monitor the note value lines and LED14-LED21 display the tuning accuracy value. Simultaneously, bits D4 and D7 are latched into the D-type register IC10 whose Q0 and Q1 outputs control LED22 and LED23. IC10's latching is triggered by the positive-going pulse on its pin 9 as supplied from IC4 pin 6.

Relative octave values are not directly set by memory output codes. Instead they are produced via a counter which responds to the transitions from note G to note A during IC7's count sequence. Memory bits D1 and D2 are Nanded by IC1b. When both lines

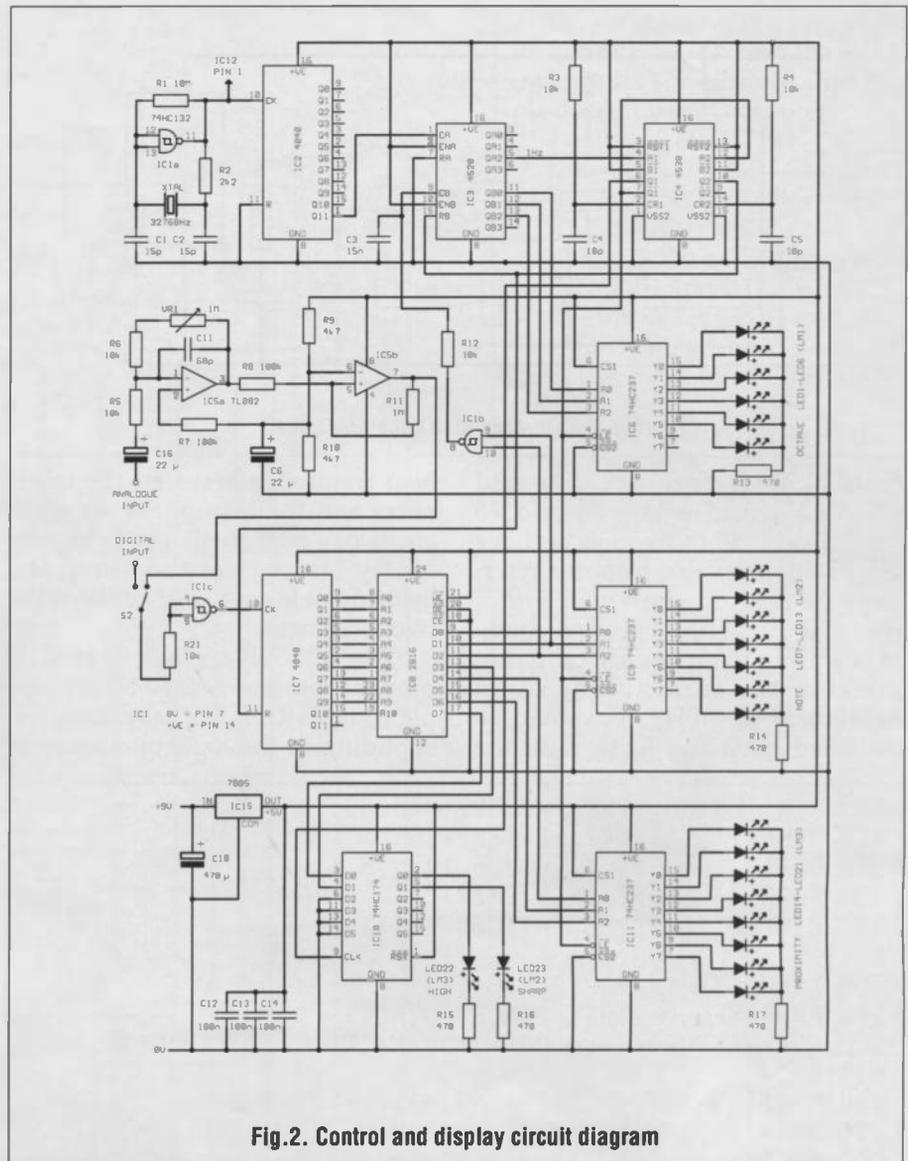


Fig.2. Control and display circuit diagram

are high, as they are for codes 6 and 7, IC1b pin 8 is set low. When the code changes from 7 to 0, IC1b pin 8 goes high, providing a clock pulse to the second 4-stage counter within IC3 (IC3b) whose QB0-QB2 outputs are fed as the address inputs to the multiplexing latch IC6. Latched by the same control pulse as IC9 and IC11, IC6 controls LED1-LED6 which display the corresponding octave count value. R12 and C3 are included to fractionally extend the clock pulse seen by IC3b's clock input.

At the end of each latch command, IC4 generates a pulse which resets IC7 and IC3b whereupon the signal input pulse counting sequence restarts. Since the LEDs are powered via the latching registers, they retain their display status until the next latching pulse is received.

Reference Tone

The circuit for the optional reference tone generator is shown in Fig.3. It is not necessary to build this part in order to use the main display facilities but, as most musicians will know, it is useful to also have an audio reference frequency when tuning instruments. Ideally, the reference tone should have been produced using a separate crystal controlled oscillator which would allow for the signal to be set at precisely 440Hz (Concert A). However, to keep this unit simple, it was decided to sub-divide the existing 32768Hz master frequency and to accept a slight compromise on the reference tone precision.

In order to obtain 440Hz from a 32768Hz master frequency a divisor of 74.472723 is required. However, a digital unit can only divide by integers, consequently the frequencies nearest to 440Hz obtainable

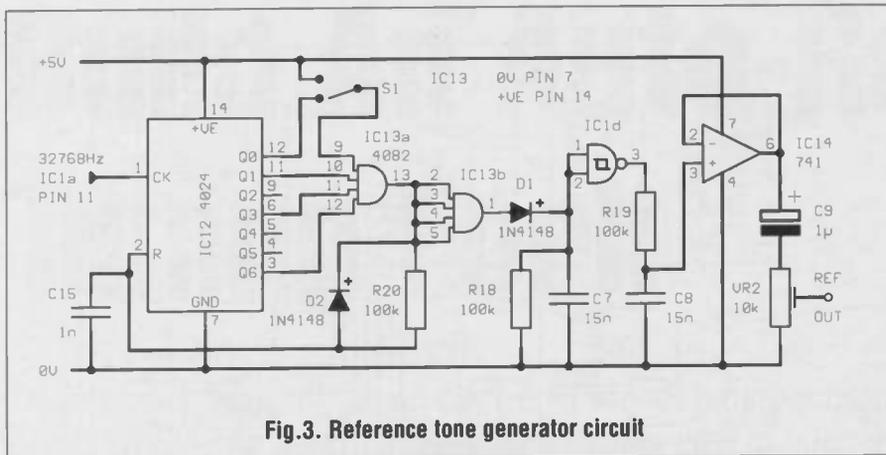


Fig.3. Reference tone generator circuit

from 32768Hz are 442.8Hz and 436.9Hz, dividing by 74 and 75 respectively. Both frequencies have been made available from the reference generator shown in Fig.3, using S1 to switch between them. When using the reference output to assist in the aural tuning of an instrument to 440Hz, S1 should be switched back and forth until the

beat frequency between the references and the instrument are similar. If one beat frequency is significantly faster than the other, the instrument is not tuned between the two references.

The 32768Hz clock signal is brought into the 7-stage binary ripple counter IC12. The outputs corresponding to the logic one states of

the binary codes for decimal 74 or 75, as partially selected by S1, are ANDed by IC13a which resets IC12 when the correct binary combination prevails. The reset pulse length is fractionally extended by the inclusion of C15, D2 and R20 to allow the buffering AND gate IC13b to also respond reliably to the pulse. From IC13b, the pulse is further extended by D1, R10 and C7 resulting in an output from the Schmitt inverter IC1d which closely approximates a square wave. R19 and C8 smooth the output to a rough triangular shape which is softer on the ear when fed via the buffering opamp IC14 and level setting preset VR2 to the user's own audio amplifier.

Software

Either an EEPROM or an EPROM with identical pinout functions may be used to hold the look-up table. Constructors must have access to a suitable programmer in order to load the chip with its data. The data codes should be calculated on a computer programmed with a suitable variant of the Basic software listing in Fig.4. The listing was written on a Commodore 3032 computer but is readily translatable for other machines. For constructors without a computer, a hex dump listing is available from the PE Editorial office at a charge of £2.

Full discussion of the software is beyond the scope of this article although the following points are pertinent to a basic understanding:

The frequency of musical octaves increases at a logarithmic rate, each octave having twice the frequency of the preceding one. Taking Concert A as 440Hz, note 'A' of the immediate octaves to either side has frequencies of 55Hz, 110Hz, 220Hz, 880Hz, 1760Hz, 3520Hz. The notes within each octave also increase in frequency by equal logarithmic steps. In essence, the software takes in turn each integer frequency between 54Hz and 2047Hz (the maximum memory size) and calculates its relationship to the ideal frequency of the nearest tone within a twelve tone scale. Numerical values are allocated to represent the natural notes A to G and a further bit is set to indicate a sharp. Although it is accepted that some musical purists may disagree with the notation, the twelve tone

```

100 REM TUNING FORK PROG322 04JUN91
110 DIMN(11),A(2047):R=0:N2=16
120 DATA2,10,3,11,4,5,13,6,14,0,8,1
130 FORB=0TO11:READN(B):NEXT
140 DV=LOG(2)/12:FORF=1TO20:IFEXP(DV*F)<1.71875THEN-
NEXT
150 X=LOG(1.71875)-(DV*(F-1))
160 FF=54:FORF=0TOFF-1:A(F)=0:NEXT
170 FORF=FFTO2047:L=LOG(F)/DV:K=INT(L/12)*12:W=(L-
K)*16+14
180 N=INT(W-2)/16-1:IFN-INT(N)>=.5THENN=N+1
190 N=INT(N):V=(K+N)*DV+X:S=EXP(V):IFN>11THENN=N-12
200 F=INT((F+.0051)*100)/100:S=INT((S+.0051)*100)/100
210 A(F)=N(N):IFF<>INT(S)THEN280
220 IFY=0THENJ=F:GOTO350
230 AA=1:BB=7:IFF-Y>BBTHENAA=BB/(F-Y)
240 FORJ-F TOYSTEP-1
250 MS=A(J)AND15:MT=INT(BB+.5):A(J)=MS+(16*MT) 260
PRINT"#"J;MS;MT,A(J):BB=BB-AA:IFBB<0THENBB=0 270
NEXT:J=F
280 IFN=N2THEN350
290 IFJ=0THENY=F:GOTO350
300 AA=1:BB=7:IFF-J>BBTHENAA=BB/(F-J)
310 FORY=JTOF
320 MS=A(Y)AND15:MT=INT(BB+.5):A(Y)=MS+(16*MT)+128 330
PRINT"*"Y;MS;MT,A(Y):BB=BB-AA:IFBB<0THENBB=0 340
NEXT:Y=F:N2=N
350 NEXT
360 REM DECIMAL TO HEX
370 W$="123456789ABCDEF"
380 FORB=0TO2047:IFB/8=INT(B/8)THENN=B:H=3:
PRINT:GOSUB400 390 H=1:N=A(B):GOSUB400:NEXT:PRINT:
PRINT"FINISHED":STOP
400 FORT=HTOOSTEP-1:A=16^T:REM 16 TO POWER OF T
410 IFN/A>=1THENW=INT(N/A):PRINTMID$(W$,W,1):N=N-
W*A:GOTO430 420 PRINT"0";
430 NEXT:PRINT" ":RETURN
    
```

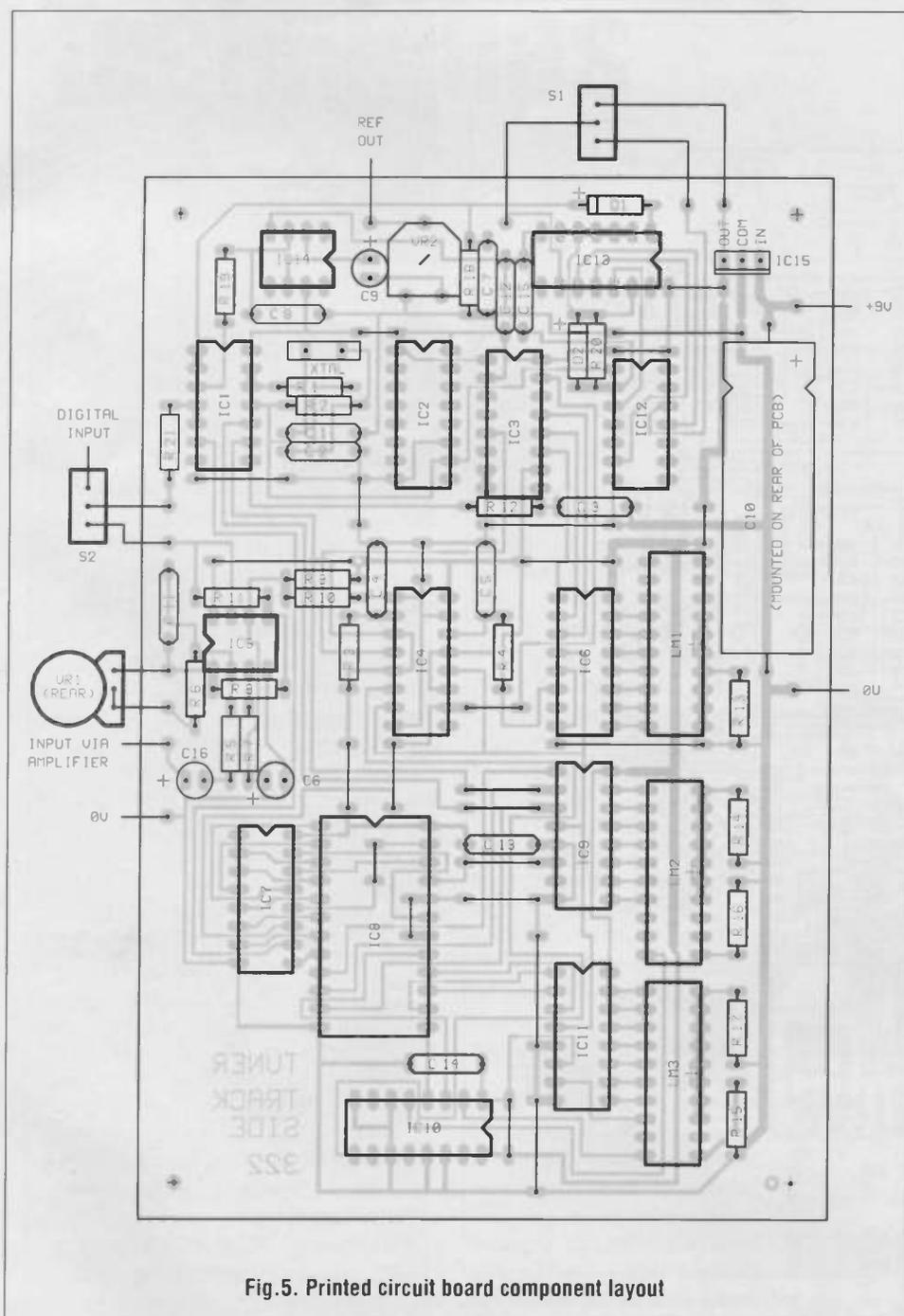


Fig.5. Printed circuit board component layout

scale has been taken as A, A#, B, C, C#, D, D#, E, F, F#, G, G#, A. Program line 120 gives the numerical values allocated to represent the 11 different notations, commencing with note C.

Lines 140 and 150 take 1.71875Hz (the frequency of the first sub-octave of note A above 1Hz) as a base from which a logarithmic value for an interval of one twelfth of a tone is calculated. During the subsequent looped processing, each time the loop integer is found to be the value closest to the ideal frequency for a tone, the frequency interval between this tone and the previous one is split into eight inte-

ger subdivisions which are retrospectively ANDed with earlier note data values stored in array variable A(.). Additional subroutines AND further data relating to whether the frequency is above or below the ideal. The print statements in lines 260 and 330 provide screen information on the progress of the main loop subroutines. On completion of the full calculation routine, the stored decimal data is coded into the hexadecimal (hex) format usually required by E(E)prom programmers, printing the data to screen. Users should include additional commands in this routine to send the data to printer or disc.

Before running the program in its entirety, check that the following results (or close to them) are produced by the computer:

$$\text{Log}(2) = 0.693147181$$

$$\text{DV} = 0.057762265$$

$$X = 0.0217368971$$

$$\text{EXP}(2) = 7.3890561$$

(DV and X may be displayed as 5.776226E-02 and 2.173692E-02.)

In the hex dump, addresses 0000 to 002A all hold zeros (00), then the next four lines should read:

```
0030 00 00 00 00 00 00 60 F0
0038 E0 68 F8 E8 61 F1 E1 D1
0040 62 F2 E2 5A 6A FA EA 53
0048 63 F3 E3 D3 6B FB EB DB
```

As a further programming guide, the following is a list of calculated frequencies in Hertz for the designated notes in the octave commencing with Concert A:

```
A 440.0
A# 466.163762
B 493.883302
C 523.251131
C# 554.365263
D 587.329536
D# 622.253968
E 659.255115
F 698.456464
F# 739.988846
G 783.990873
G# 830.609396
A 880.0
```

Tuning Up

The circuit has been designed to run from a 9V DC supply, such as a 9V battery eliminator (mains adaptor) regulated down to 5V by IC15.

Fig.5 shows the printed circuit board component layout and Fig.6 shows the tracking details. For compactness, 10-way DIL LED modules were used on the Author's model, ignoring the unused LED positions. Individual LEDs may be used instead if preferred. It is recommended that sockets should be used for all ICs and for the LED modules. Note that two of the link wires on the PCB go below IC8. C10 may be mounted below the PCB allowing the board to be mounted flush with the front panel of a suitable box in which slots are cut for viewing the LEDs.

Thoroughly check all soldered joints at the end of assembly, in particular making sure that solder bridging between close-run pads and tracks has not occurred. Before

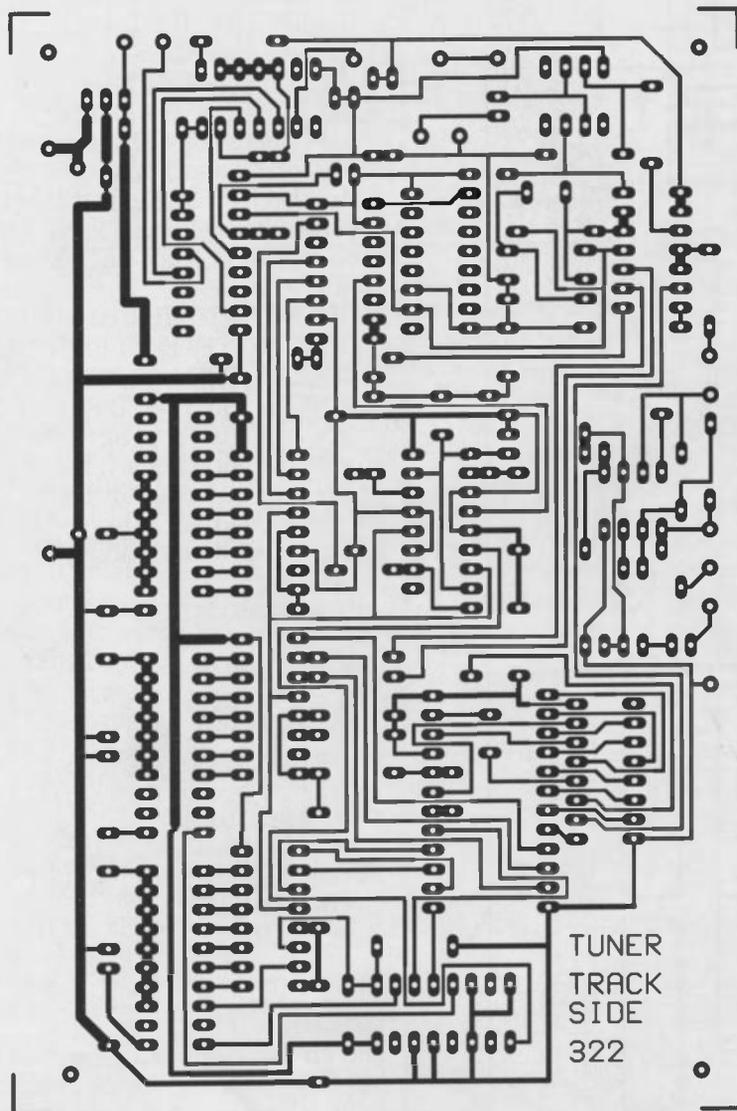


Fig.6. PCB track details

inserting any IC except IC15, check that with power applied to the board the output of IC15 delivers 5V. A voltage significantly below this could indicate a power line short. If the voltage is above 5V it is likely that IC15 is incorrectly inserted.

With all ICs on board, if the circuit fails to work first time switch off and recheck the assembly. No setting-up is required, just couple the unit to a variable frequency signal source, adjust VR1 to suit the input level and observe the LED responses. If the reference tone board has been built it may be used as the initial signal source, and may itself be checked by plugging it into any normal amplifier system.

A voltmeter can be used to check that a 1Hz signal is being produced at the output of IC3 pin 5. The meter can also be used to check the status of the later outputs of IC7 and of the memory outputs when an input signal is being fed in to the preamp. Should none of the LEDs appear to function, check that they are correctly oriented in their sockets.

When tuning an instrument, its note duration and amplitude should be sufficiently great to allow the tuner time to respond to several sampling cycles. The optimum tuning accuracy will be indicated by LED22 alternating fairly uniformly between on and off. ■

Components

Resistors

R1	10M
R2	2k2
R3-R6, R12, R21	10k
R7, R8, R18-R20	100k
R9, R10	4k7
R11	1M
R13-R17	470R
All 0.25W 5% or better	

Capacitors

C1, C2	15p polystyrene
C3, C7, C8	15n polyester
C4, C5	10p polystyrene
C6, C16	22 μ 16V electrolytic
C9	1 μ 16V electrolytic
C10	470 μ 16V electrolytic
C11	68p polystyrene
C12-C14	100n polyester
C15	1n polystyrene

Semiconductors

D1, D2	1N4148
IC1	74HC132
IC2, IC7	4040
IC3	4520
IC4	4538
IC5	TL082
IC6, IC9, IC11	74HC237
IC8	2816 EEPROM (see text)
IC10	74HC174
IC12	4024
IC13	4082
IC14	741
IC15	7805
LM1-LM3	10-way DIL LED modules

Potentiometers

VR1	1M lin rotary
VR2	10k min horiz preset

Switches

S1, S2	SPDT min toggle
--------	-----------------

DIL IC sockets

8-pin x 2, 14-pin x 3, 16-pin x 8, 20-pin x 3, 24-pin

Miscellaneous

32768Hz crystal, printed circuit board, PCB supports x 4, input and output sockets to suit, knob, box to suit.

Constructors note

The Author's semiconductors were purchased from RS/Electromail.

Techniques

Andrew Armstrong explains how to go about turning a project idea into a practical device.

A recent reader's letter to Techniques expressed the reader's dismay that, having written to several electronics suppliers requesting a circuit diagram for an application he wanted to build and a parts list and quotation for the necessary parts, he had received no joy from any of them. The application was of medium complexity and non-standard design.

If our reader had asked for, let us say, a circuit for a simple radio receiver using a standard radio IC, then it is quite likely that Maplin, Cirkit, or somebody else would have been able to locate a standard circuit and maybe have a PCB or complete kit available. Because the reader's requirement was not for a standard application, the supplier would have had to spend a minimum of several man-hours, and maybe several man-days, to design a suitable circuit for this project. He would have to do a thorough job, because the customer would have the expectation that it would work first time, and would no doubt expect him to make it work if there were any design errors.

Indeed, to design this particular application for industrial manufacture – which, to be fair, is not implied in the reader's request – I would probably have made a charge somewhere in the low thousands of pounds. And this is not expensive. Clearly, this is an over-large commitment for a components supplier to sell a few tens of pounds'-worth of parts!

Design Stages

How does one go about producing a design, whether as a magazine project or as a product to be manufactured?

To avoid giving away any current trade secrets, I will use as an example something which I designed some years ago.

This started with a friend who was tired of his car windscreen-

wipers scraping the glass in conditions of light drizzle (this was before the days when car manufacturers had developed the type of windscreen wiper which scrapes the glass even in conditions of heavy rain) asked me if it was possible to design an intermittent wiper which would accommodate itself to the weather conditions, rather than only being suitable for a narrow range of precipitation. I suggested a variable delay unit, but he didn't want to drill extra holes in his dashboard. No problem, said I, confidently. I can design a variable windscreen wiper delay unit which does not need any extra controls to be fitted to your car.

The method I chose was to detect operations of the windscreen wiper switch, to time the interval between two successive operations, and to automatically operate the windscreen wipers with a time delay equal to the measured time period.

The timing was carried out by charging a capacitor via a large resistor, after the first switch operation, and switching off the charge current using a bipolar transistor after the second switch operation. A relaxation oscillator using the same RC time constant was then used to control the wipers, with the charging switching point of the timer set by the stored charge on the first capacitor. I had been concerned about charge leakage, but the data book showed that the leakage through the transistor used to switch off the charging current was low enough not to change the timing by a significant amount over a period of half an hour. A CMOS op-amp

was used as the relaxation oscillator, so that charge leakage through this was also negligible. It only took me half a day to design, and another couple of hours to build a prototype which worked very well.

The next stage was to make several units for several different people's cars. The problems started to appear. What had worked well with the switch and motor on my car failed to respond to the switch operations on my friend's car, because I had applied slightly too much switch-bounce suppression. A reduction of the bounce-suppression to the minimum which would work on my car, caused multiple triggering in a vehicle owned by a third friend, and in the end I had to resort to multiple time-constants to

To design this particular application for industrial manufacture I would probably have made a charge somewhere in the low thousands of pounds.

cope with the range of switch-bounce and parking contact delay across a range of vehicles. The experimenting with, and correction of, the switch-bounce circuitry, took longer than the initial design.

Still, now we had a working product with the bugs carefully removed, so we could manufacture a number to sell.

The Veroboard prototypes were clearly unacceptable for sale, so we searched for a suitable box for which we could design a printed circuit. Because the unit would be housed under the bonnet and could be subjected to road spray it had to be sealed, and we found no suitable sealed case at a reasonable price. This was not seen as a problem and decided to use a good-quality potting compound intended for electronic products. We had a metal mould fabricated, designed the PCBs to fit, and made and potted some samples. The friend who had originally raised the question tried the first one on his car, and was upset to find that it became unreliable after a few weeks.

Considerable investigation eventually revealed that the potting compound, though properly cured, absorbed moisture from the atmosphere slowly, and eventually became faintly conductive. The conduction was just enough to leak away the charge on a $2.2\mu\text{F}$ capacitor over a period over about two minutes. We were now faced with the choice of redesigning the circuit to avoid the problem, or redesigning the housing – in which we had already invested effort and money.

An internal plastic cover over the sensitive part of the circuit proved ineffective, because the potting compound would flow in through the smallest gap, and sealed boxes were still quite unattractive, so we decided to modify the circuit.

My first approach was to try to increase the capacitance value far enough that the leakage would not matter, but the only way to do that

was to use an electrolytic, and no reasonably-priced electrolytic capacitor was specified to have a low enough internal leakage to hold its charge long enough regardless of any external leakage. In reality, most electrolytic capacitors will do the job when tested, but I wanted to avoid units failing subsequently due to ageing of the components or

In the end, I re-designed the unit from scratch using digital instead of analogue timing and this solved all the problems

to temperature variations.

In the end, I re-designed the unit from scratch using digital instead of analogue timing, and this solved all the problems and resulted in a product of which some samples are in service to this day. A cut-down embodiment of this was subsequently published as a magazine project, and the kit is still being marketed by Cirkit.

If the first prototype design had

been published as a magazine project, it would not have been good enough: some readers' units would have worked well, because the characteristics matched the wind-screen wiper circuitry in their cars, and others would not have worked, because of excessive switch bounce or switching delays. Unfortunately, some magazine projects do fall into

this category, because it is very difficult to predict all the problems which might arise on use in different situations, and it is normally uneconomic for the developer to make and test half a dozen or more prototypes to improve the design.

The design at the stage when the time constant problems had been solved, but before the unit had been redesigned as a digital circuit, would have been suitable for publication in a magazine, because it is not unreasonable to expect that electronics hobbyists can take care to mount their project away from direct road-spray, and that they could individually seal a plastic case once it has been installed. It is preferable to go one stage better than this for a magazine project, but it is very often not possible.

The third main stage of the design which was an acceptable product for manufacture, had taken a number of man-weeks to develop; a period of time totally out of proportion to the less than one day needed to make the first model work quite acceptably.

In summary, to design a product a good approach is first of all to decide upon the broad means by which the job is to be done, then to sort

out the details and try to predict future tolerance problems. Then several prototypes are normally desirable to show any snags which may have been overlooked. After this stage, minor or major redesign may be needed. In extreme cases the whole scheme may need to be changed. Attempts to short circuit this procedure leave a risk of a design which cannot be relied upon to work in all cases. ■



OMP MOS-FET POWER AMPLIFIERS
HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS
FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)
MXF600 (300W + 300W) MXF900 (450W + 450W)
ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★ Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV Inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19" x H3 1/2" (2U) x D11"
MXF400 W19" x H5 1/4" (3U) x D12"
MXF600 W19" x H5 1/4" (3U) x D13"
MXF900 W19" x H5 1/4" (3U) x D14 1/2"

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL. £12.50 EACH

OMP VARISPEED TURNTABLE CHASSIS



★ Manual arm ★ Steel chassis ★ Electronic speed control 33 & 45 R.P.M. ★ Vari pitch control ★ High torque servo driven DC motor ★ Transit screws ★ 12" die cast platter ★ Neon strobe ★ Calibrated balance weight ★ Removable head shell ★ 1/2" cartridge fixings ★ Cue lever ★ 220/240V 50/60Hz ★ 390x305mm ★ Supplied with mounting cut-out template.

PRICE £61.30 + £3.70 P&P

OPTIONAL MAGNETIC CARTRIDGES

STANTON AL500mkII GOLDRING G950
PRICE £16.95 + 50P P&P PRICE £7.15 + 50P P&P

STEREO DISCO MIXER DJ6500

★ WITH ECHO ★

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with tone control & talk-over switch, 7 Channels with individual faders plus cross fade, Cue Headphone Monitor, Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.



Price £134.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series. FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.

TYPE 'A' (KSN1D36A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
TYPE 'B' (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
TYPE 'C' (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
TYPE 'E' (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

OMP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE

Made especially to suit today's need for compactness with high output sound levels, finished in hard wearing black vinylite with protective corners, grille and carrying handle. Each unit incorporates a 12" driver plus high frequency horn for a full frequency range of 45Hz-20KHz. Both models are 8 Ohm Impedance. Size: H20" x W15" x D12".

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OMP 12-100WATTS (100dB) PRICE £163.50 PER PAIR
OMP 12-200WATTS (200dB) PRICE £214.55 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR



IN-CAR STEREO BOOSTER AMPS

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS

150 WATTS (75 + 75) Stereo, 150W Bridged Mono
250 WATTS (125 + 125) Stereo, 250W Bridged Mono
400 WATTS (200 + 200) Stereo, 400W Bridged Mono
ALL POWERS INTO 4 OHMS

Features:
★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection




PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH

OMP MOS-FET POWER AMPLIFIER MODULES SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

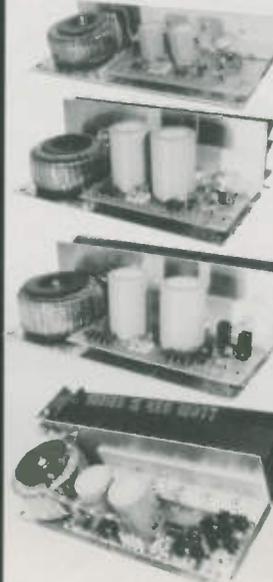THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P

OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £5.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz, PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D.s (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control for very fast rise and decay times. Tough moulded plastic case, with acrylic tinted front. Size 84 x 27 x 45mm.
PRICE £8.70 + 50p P&P

LOUDSPEAKERS

LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (50p STAMPED) FOR COMPLETE LIST.

From McKenzie Professional Series
From McKenzie Studio Series

McKENZIE:- INSTRUMENTS, P.A., DISCO, ETC

ALL MCKENZIE UNITS 8 OHMS IMPEDANCE
8" 100WATT C8-100GP GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £31.45 + £2.00 P&P
RES. FREQ. 80Hz, FREQ. RESP. TO 7KHz, SENS 96dB.
10" 100WATT C10-100GP GUITAR, VOICE, KEYBOARD, DISCO, EXCELLENT MID. PRICE £38.89 + £2.50 P&P
RES. FREQ. 72Hz, FREQ. RESP. TO 6KHz, SENS 97dB.
10" 200WATT C10-200GP GUITAR, KEYB'D, DISCO, EXCELLENT HIGH POWER MID. PRICE £53.21 + £2.50 P&P
RES. FREQ. 69Hz, FREQ. RESP. TO 5KHz, SENS 97dB.
12" 100WATT C12-100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. PRICE £71.91 + £3.50 P&P
RES. FREQ. 49Hz, FREQ. RESP. TO 7KHz, SENS 98dB.
12" 100WATT C12-100TC (TWIN CONE) HIGH POWER, WIDE RESPONSE, P.A., VOICE, DISCO. PRICE £41.39 + £3.50 P&P
RES. FREQ. 45Hz, FREQ. RESP. TO 12KHz, SENS 97dB.
12" 200WATT C12-200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. PRICE £59.05 + £4.00 P&P
RES. FREQ. 45Hz, FREQ. RESP. TO 5KHz, SENS 98dB.
12" 300WATT C12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARDS, DISCO ETC. PRICE £95.66 + £3.50 P&P
RES. FREQ. 49Hz, FREQ. RESP. TO 7KHz, SENS 100dB.
15" 100WATT P C15-100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO. PRICE £80.57 + £4.00 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 98dB.
15" 200WATT P C15-200BS VERY HIGH POWER BASS. PRICE £90.23 + £4.50 P&P
RES. FREQ. 39Hz, FREQ. RESP. TO 4KHz, SENS 99dB.
15" 400WATT C15-400BS VERY HIGH POWER, LOW FREQUENCY BASS. PRICE £105.46 + £4.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 4 KHz, SENS 100dB.
18" 500WATT C18-500BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS. PRICE £174.97 + £5.00 P&P
RES. FREQ. 27Hz, FREQ. RESP. TO 2KHz, SENS 98dB.

EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC

ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)
BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND
8" 50WATT EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £80.90 + £2.00 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB.
10" 50WATT EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £136.65 + £2.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB.
10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.
12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P
RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB.
FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
5 1/2" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P
RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.
6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P
RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB.
8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 89dB.
10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE. RANGE UP TO 3 MILES SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P
FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P



PHOTO: 3W FM TRANSMITTER

POSTAL CHARGES PER ORDER £1.00 MINIMUM, OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT, BODIES, P.L.Cs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.



B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHERN-ON-SEA, ESSEX, SS2 6TR.
Tel.: 0702 - 527572 Fax.: 0702 - 420243

CITIZEN

ALWAYS A GOOD IDEA

Silica presents some great offers on the award winning range of high quality matrix printers from Citizen. Each Citizen printer is built in the UK to exacting standards, ensuring superb reliability and output. Our confidence in Citizen's quality is such that we are pleased to include a 2 year guarantee with every printer. Plus, if you buy a Citizen printer from us, we will give you the Silica Systems Printer Starter Kit (worth £29.38), FREE OF CHARGE!

- FREE DELIVERY**
Next Day - Anywhere in the UK mainland
- FREE STARTER KIT**
Worth £29.38 - With every Citizen printer from Silica
- 2 YEAR WARRANTY**
Silica offer a 2 year warranty (including the printer head) with every Citizen printer from Silica.
- WINDOWS 3.0**
Free Windows 3.0 driver
Included with the Silica Starter Kit.
- FREE COLOUR KIT**
With every Swift 9 and Swift 24c printer.
- FREE HELPLINE**
Technical support helpline open during office hours.
- MADE IN THE UK**
Citizen printers are manufactured to high standards.

DOT MATRIX & NOTEBOOK PRINTERS



9 PIN PRINTER

144 CPS **80 COLUMN**

- Citizen 120D+ - 9 pin - 80 column
- 144cps Draft, 30cps NLO
- 4K Printer Buffer + 2 Fonts
- Parallel Interface as Standard
- Graphics Resolution: 240x240dpi
- Epson and IBM Emulation
- Pull tractor & bottom feed
- FREE Silica Printer Starter Kit

RRP:	£199
STARTER KIT	£25
TOTAL RRP:	£224
SAVING:	£95
SILICA PRICE:	£129

SERIAL INTERFACE OPTION
The 120D printer is available with a serial interface for £139+VAT. Ref: PRI 2125 - £163.33 inc VAT.

£129

+VAT=£151.58 ref: PRI 2120

9 PIN PRINTERS



192 CPS **80 COLUMN**

- Citizen Swift 9 - 9 pin - 80 column
- 192cps Draft, 48cps NLO
- 8K Printer Buffer + 3 Fonts
- Parallel Interface
- Graphics Resolution: 240x240dpi
- Epson and IBM Emulation
- FREE Colour Kit
- FREE Silica Printer Starter Kit

RRP:	£239
COLOUR KIT	£38
STARTER KIT	£25
TOTAL RRP:	£302
SAVING:	£123
SILICA PRICE:	£179

+VAT=£222.08 ref: PRI 2209



192 CPS **136 COLUMN**

- Citizen Swift 9x - 9 pin - 136 column
- 192cps Draft, 48cps NLO
- 8K Printer Buffer + 3 Fonts
- Parallel Interface
- Graphics Resolution: 240x240dpi
- Epson and IBM Emulation
- A3 landscape printing
- FREE Silica Printer Starter Kit

RRP:	£329
STARTER KIT	£25
TOTAL RRP:	£354
SAVING:	£105
SILICA PRICE:	£249

+VAT=£292.58 ref: PRI 2309

24 PIN PRINTERS



216 CPS **80 COLUMN**

- Citizen Swift 24c - 24 pin - 80 column
- 216cps Draft, 72cps LQ
- 8K Printer Buffer + 6 Fonts
- Parallel Interface
- Graphics Resolution: 360x360dpi
- Epson, IBM & NEC P6+ Emulation
- FREE Colour Kit
- FREE Silica Printer Starter Kit

RRP:	£365
COLOUR KIT	£38
STARTER KIT	£25
TOTAL RRP:	£428
SAVING:	£169
SILICA PRICE:	£259

+VAT=£304.33 ref: PRI 2534




192 CPS **80 COLUMN**

- Citizen 224 - 24 pin - 80 column
- 192cps Draft, 64cps LQ
- 8K Printer Buffer + 2 Fonts
- Parallel Interface
- Graphics Resolution: 360x360dpi
- Epson and IBM Emulation
- Colour Option Available
- FREE Silica Printer Starter Kit

RRP:	£299
STARTER KIT	£25
TOTAL RRP:	£324
SAVING:	£125
SILICA PRICE:	£199

+VAT=£233.83 ref: PRI 2484

NOTEBOOK PRINTER

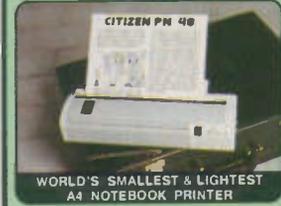

64 CPS **80 COLUMN**

- Citizen PN48 Notebook Printer
- Non-impact Printing On Plain Paper
- LASER QUALITY - 64cps
- 4K Printer Buffer + 2 Fonts
- Rear and Bottom Paper Loading
- Parallel Interface
- Graphics Resolution: 360x360dpi
- Epson, IBM, NEC P6 & Citizen Emulations
- Power: Mains, Battery or Car Adaptor
- FREE Silica Printer Starter Kit

RRP:	£325
STARTER KIT	£25
TOTAL RRP:	£350
SAVING:	£101
SILICA PRICE:	£249

+VAT=£292.58 ref: PRI 2100

24 PIN PRINTER



192 CPS **136 COLUMN**

- Citizen Swift 24x - 24 pin - 136 column
- 192cps Draft, 64cps LQ
- 8K Printer Buffer + 4 Fonts
- Parallel Interface
- Graphics Resolution: 360x360dpi
- Epson, IBM and NEC P6 Emulation
- A3 landscape printing - FREE Colour Kit
- FREE Silica Printer Starter Kit

RRP:	£489
STARTER KIT	£25
TOTAL RRP:	£514
SAVING:	£165
SILICA PRICE:	£349

+VAT=£410.08 ref: PRI 2574

24 PIN PRINTER



144 CPS **80 COLUMN**

- Citizen 124D - 24 pin - 80 col
- 144cps Draft, 48cps LQ
- 8K Printer Buffer + 2 Fonts
- Parallel Interface
- Graphics Res: 360x360dpi
- Epson and IBM Emulation
- FREE Silica Printer Starter Kit

RRP:	£249
STARTER KIT	£25
TOTAL RRP:	£274
SAVING:	£105
SILICA PRICE:	£169

+VAT=£198.58 ref: PRI 2534

ACCESSORIES STARTER KIT

FREE!
Worth: £25 +VAT=£29.38

To get you up and running with your new printer from Silica:

- 3 1/2" Disk - Amiga & ST Drivers
- 3 1/2" Disk - Drivers for Windows 3
- 2 Meire Parallel Printer Cable
- 100 Sheets of Continuous Paper
- 100 Continuous Address Labels
- 5 Continuous Envelopes

If you already own a printer, and would like to buy a kit, you may order one (ref. KIT 5500) for £24.95 - £5 off RRP!

SHEET FEEDERS

PRA 1200 120D	£71.38
PRA 1215 124D/224 Swift/24/24c	£88.70
PRA 1228 124D/224 Swift/24/24c	£42.00

SERIAL INTERFACES

PRA 1189 120D+	£56.45
PRA 1209 124D/224 Swift 9	£32.25
PRA 1709 Swift 24/24c	£26.38

32K MEMORY EXPN

PRA 1753 124D/224 Swift 24/24c	£13.10
--------------------------------	--------

PRINTER STAND

PRA 1242 124D/224 Swift	£24.03
PRA 1274 Swift 9/24c	£30.66

ORIGINAL RIBBONS

RIB 3520 120D/9pin Black	£2.91
RIB 3949 Swift 9x Black	£7.15
RIB 3924 124D/224 Swift/24/24c Black	£4.20
RIB 3936 Swift 9/24/24c Colour	£13.63
RIB 3248 P48 Single Strike	£3.61
RIB 3348 P48 Multi Strike	£3.61

COLOUR KITS

PRA 1236 Swift 9/24/24c	£35.25
PRA 1240 Swift 9/24c	£35.25

PN48 ACCESSORIES

PRA 1148 P48 Battery	£51.70
PRA 1155 P48 Cable Extn	£ TBC
PRA 1162 P48 Car Adaptor	£ TBC

All prices include VAT and Free delivery.

SILICA SYSTEMS OFFER YOU

- **FREE OVERNIGHT DELIVERY:** On all hardware orders shipped in the UK mainland.
 - **TECHNICAL SUPPORT HELPLINE:** Team of technical experts at your service.
 - **PRICE MATCH:** We normally match competitors on a "Same product - Same price" basis.
 - **ESTABLISHED 12 YEARS:** Proven track record in professional computer sales.
 - **BUSINESS + EDUCATION + GOVERNMENT:** Volume discounts available for large orders.
 - **SHOWROOMS:** Demonstration and training facilities at our London & Sidcup branches.
 - **THE FULL STOCK RANGE:** All of your requirements from one supplier.
 - **FREE CATALOGUES:** Will be mailed to you with offers and software/peripheral details.
 - **PAYMENT:** By cash, cheque and all major credit cards.
- Before you decide when to buy your new printer, we suggest you think very carefully about WHERE you buy it. Consider what it will be like a few months after you have made your purchase, when you may require additional peripherals or software, or help and advice. And, will the company you buy from contact you with details of new products? At Silica Systems, we ensure that you will have nothing to worry about. We have been established for over 12 years and, with our unrivalled experience and expertise, we can now claim to meet our customers requirements with an understanding which is second to none. But don't just take our word for it. Complete and return the coupon now for our latest Free literature and begin to experience the "Silica Systems Service".

MAIL ORDER: 1-4 The Mews, Hatherley Rd, Sidcup, Kent, DA14 4DX Tel: 081-309 1111
Order Lines Open: Mon-Sat 9.00am-6.00pm No Late Night Opening Fax No: 081-308 0608

LONDON SHOP: 52 Tottenham Court Road, London, W1P 0BA Tel: 071-580 4000
Opening Hours: Mon-Sat 9.30am-6.00pm No Late Night Opening Fax No: 071-323 4737

LONDON SHOP: Selfridges (1st Floor), Oxford Street, London, W1A 1AB Tel: 071-629 1234
Opening Hours: Mon-Sat 9.30am-6.00pm Late Night: Thursday until 9pm Extension: 3914

SIDCUP SHOP: 1-4 The Mews, Hatherley Rd, Sidcup, Kent, DA14 4DX Tel: 081-302 8611
Opening Hours: Mon-Sat 9.00am-5.30pm Late Night: Friday until 7pm Fax No: 081-309 0017

To: Silica Systems, Dept PRNOW-1291-55, 1-4 The Mews, Hatherley Rd, Sidcup, Kent, DA14 4DX

PLEASE SEND A CITIZEN COLOUR CATALOGUE

Mr/Mrs/Ms: Initials: Surname:

Address:

Postcode:

Tel (Home): Tel (Work):

Company Name (if applicable):

Which computer(s), if any, do you own?

55C

MAIL ORDER HOTLINE
081-309 1111

SILICA SYSTEMS

E.O.E. - Advertised prices and specifications may change - Please return the coupon for the latest information