

JANUARY 1984 90p

Australia \$1.50
New Zealand \$1.75
Malaysia \$4.95
IR £1.38 (inc. VAT)

Practical wireless


THE RADIO MAGAZINE

**HF
ANTENNA
SPECIAL**


*Two Band
Mini-X Beam*




The Vertical V Antenna

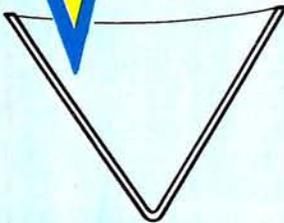

*Kite Antennas For
Top Band*

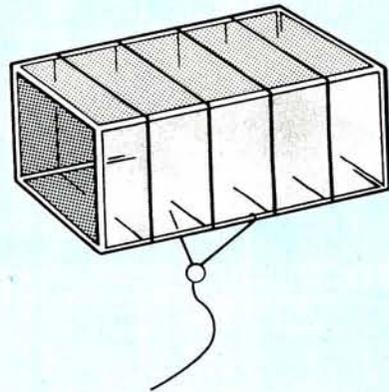

*Steerable
HF Antenna*

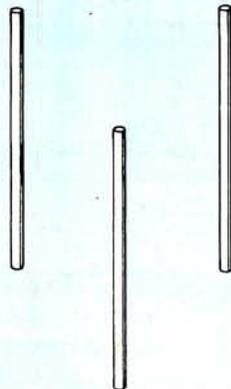

PLUS
**Receive Converter-
Top Band to 14MHz**

AUTHORISED DEALERS FOR ALL EQUIPMENT WE SELL



Bredhurst electronics

YAESU FRG7700 Gen Cov Receiver £335 inc VAT & Carriage



YAESU		£	c&p
FT1	H.F. Transceiver - Gen. Cov. Receive	1395.00	(-)
FT102	Amateur Band H.F. Transceiver	685.00	(-)
SP102	Matching speaker	49.00	(2.00)
FC102	Matching A.T.U. 1.2kW.PEP/AV	200.00	(2.00)
FC902	All Band A.T.U.	135.00	(1.50)
SP901	External Speaker	31.00	(1.50)
FT77	HF mobile transceiver 9 band	459.00	(-)
FP700	Power supply/speaker	110.00	(-)
FC700	A.T.U.	85.00	(1.00)
FT757GX	H.F. Amateur Bnd Tx Gen. Cov. Rx		POA
FC757AT	Automatic A.T.U.		POA
FP757GX	Power Supply		POA
FT726R(2)	Multimode multiband base station C/W 2M	675.00	(-)
FT230R	Transceiver 2M 25W F.M. mobile	239.00	(-)
FT290R	Transceiver 2M 2.5W Multimode portable	249.00	(-)
FT790R	Transceiver 70cm 1W Multimode portable	299.00	(-)
NC11C	Trickle Charger (240V ac)	9.20	(0.75)
MMB11	Mobile mount	24.90	(1.00)
CSC1A	Soft carrying case	3.85	(0.75)
FL2010	Linear Amp. 2M 10W	59.00	(1.20)
FT480R	2M Multimode mobile transceiver	399.00	(-)
FT780R	70cm Multimode mobile transceiver	311.00	(-)
FT208R	Handheld 2M F.M. transceiver	199.00	(-)
FT708R	Handheld 70cm F.M. transceiver	209.00	(-)
NC9C	Trickle charger (240V ac)	8.00	(0.75)
NC8C	Base Fast charger	50.00	(1.50)
PA3	Battery eliminator and charger (12V dc)	14.20	(1.00)
FRG7700	H.F. Receiver 0.15-30MHz all mode	335.00	(-)
FRG7700M	FRG7700 c/w 12 channel memory	389.00	(-)
MEMG7700	Memory Unit	98.00	(1.00)
FRT7700	Antenna tuner/switch	42.50	(1.00)
FRA7700	Active Antenna	38.70	(1.00)
YM34	Stand mic 500/50K 8 pin	23.40	(1.50)
YM38	Stand mic 500/50K 8 pin + SCAN	22.60	(1.50)
YD148A	Stand mic 600/50K 4 pin	27.20	(1.50)
MD1B8	Stand mic 600/50K 8 pin + SCAN	49.80	(1.50)
FF501DX	Low pass filter	25.70	(1.00)
FSP-1	Mobile speaker 8 ohm 6W	9.95	(0.75)
YH-55	Headphones 8 ohm	9.95	(0.75)
YH-77	Lightweight headphones	9.95	(0.75)
QTR24D	World time clock (quartz)	31.40	(1.00)

ICOM

IC-751	New H.F. Transceiver	969.00	(-)
IC 720A	H.F. Tx + Gen. Cov. Rx	949.00	(-)
IC PS20	P.S.U. for above with Speaker	155.00	(-)
IC PS15	P.S.U.	119.00	(-)
IC 2KL	H.F. Linear 500 Watts O/P	915.00	(-)
IC 2KLPS	P.S.U. for above	256.00	(-)
IC AT500	1.8-30MHz Auto A.T.U.	349.00	(-)
IC AT100	3.5-30MHz Auto A.T.U.	249.00	(-)
IC 271E NEW	2M Multimode Base Station	579.00	(-)
IC 290H	2M Multimode Mobile	433.00	(-)
IC 25E	2M FM Mobile 25W	269.00	(-)
IC 2E	2M Handheld	179.00	(-)
IC 4E	70cm Handheld	199.00	(-)
IC BC30	Base Charger	45.00	(1.50)
IC HM9	Speaker + Microphone	12.00	(1.00)
IC ML1	10 Watt 2M Booster IC2E	59.00	(1.00)
IC SM5	Desk Mic (8 pin for Icom only)	29.00	(1.00)
IC R70	General Cov. Receiver	499.00	(-)

F D K

Multi 725X	2M FM Mobile 25W	199.00	(-)
Multi 750XX	2M Multimode	299.00	(-)

BNOS LINEARS - Send for details

WELZ

		£	c&p
SP15M	SWR PWR Meter HF/ 200W	35.00	(1.00)
SP45M	SWR PWR Meter 2M/70cm 100W	51.00	(1.00)
SP200	SWR PWR Meter H.F./2M 1KW	69.95	(1.50)
SP300	SWR PWR Meter H.F./2M/70cm	97.00	(1.50)
SP400	SWR PWR Meter 2M/70cm 150W	69.95	(1.50)
SP600	SWR PWR Meter H.F./2M/20KW	97.00	(2.00)
SP10X	SWR PWR Meter H.F./2M	24.45	(0.75)
SP350	SWR PWR Meter H.F./2M/70 200W	59.95	(1.50)
AC38	A.T.U. 3.5 to 30MHz 400W PEP	65.00	(1.00)
CT15A	15/50W Dummy Load (PL259)	7.95	(0.75)
CT15N	15/50W Dummy Load (N type plug)	13.95	(0.75)
CT300	300/1kW Dummy Load 250MHz (SO239)	49.50	(2.00)

COAXIAL SWITCHES


-	2 Way Toggle Switch (H.F./2M)	6.00	(0.50)
SA450	2 Way Diecast - SO239 (500MHz)	10.00	(0.75)
SA450N	2 Way Diecast - N plugs (500MHz)	12.95	(0.75)
CH20A	2 Way WELZ - SO239 (900MHz)	17.95	(1.00)
CH20N	2 Way WELZ - N plugs (900MHz)	31.95	(1.00)
-	5 Way Western Rotary (H.F.)	15.95	(1.00)
-	3 Way LAR Rotary (H.F.)	19.95	(1.25)
DRAE	3-way rotary	£15.40	(0.75)

TRIO

TS930S	9 Band TX General Cov Rx	1216.00	(-)
TS930S	160-10m Transceiver 9 Bands	697.00	(-)
AT230	All Band ATU/Power Meter	135.00	(2.00)
SP230	External Speaker Unit	41.00	(1.50)
TS430S	160-10m Transceiver	736.00	(-)
PS430	Matching Power Supply	112.00	(3.00)
SP430	Matching Speaker	29.44	(1.50)
MB430	Mobile Mounting Bracket	11.27	(1.50)
FM430	FM Board for TS430	34.50	(1.00)
TS130S	8 Band 200W PEP Transceiver	559.00	(-)
TS130V	8 Band 20W PEP Transceiver	456.00	(-)
SP120	Base Station External Speaker	26.40	(1.50)
AT130	100W Antenna Tuner	93.00	(1.50)
PS20	AC Power Supply - TS130V	57.96	(2.50)
MC50	Dual Impedance Desk Microphone	30.80	(1.50)
MC35S	Fist Microphone 50K ohm IMP	14.70	(0.75)
MC30S	Fist Microphone 500 ohm IMP	14.70	(0.75)
LF30A	HF Low Pass Filter 1kW	21.00	(1.00)
TR9130	2M Multimode	433.00	(-)
TS9500	70cm Multimode	419.00	(-)
BO9A	Bass Plinth for TR9130	39.30	(0.50)
TW4000A	2M/70cm mobile	469.00	(-)
TM201A	2M 25W mobile	269.00	(-)
TR2300	FM Portable	152.00	(-)
VB2300	10W Amplifier for TR2300	36.50	(1.50)
MB2	Mobile Mount for TR2300	21.00	(1.50)
TR3500	70cm Handheld	250.00	(-)
TR2500	2M FM Synthesised Handheld	232.00	(-)
ST2	Base Stand	51.90	(1.50)
SC4	Soft Case	13.80	(0.50)
SMC25	Speaker Mike	16.10	(1.00)
PB25	Spare Battery Pack	25.00	(1.00)
MS1	Mobile Stand	31.90	(1.00)
R600	Gen. Cov. Receiver	257.00	(-)
R2000	Synthesiser 200KHz-30MHz Receiver	398.00	(-)
HC10	Digital Station World Time Clock	67.70	(1.50)
HS5	Deluxe Headphones	23.00	(1.00)
HS4	Economy Headphones	11.27	(1.00)
SP40	Mobile External Speaker	14.26	(1.00)

PLEASE PHONE ANTENNA ENQUIRIES

MINI- PRODUCTS HQ-1

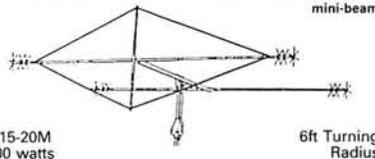

10-15-20M
1200 watts

6ft Turning Radius

£139 (£5 carriage)

MOBILE SAFETY MICROPHONES

ADONIS AM 202S Clip-on	24.50	(-)
ADONIS AM 202H Head Band +Up/Down Buttons	34.50	(-)
ADONIS AM 202F Swan Neck +Up/Down Buttons	37.00	(-)

DATONG

D70 MORSE TUTOR £56.35



DATONG PRODUCTS

		£	c&p
PC1	Gen. Coverage Converter HF to 2M	137.42	(-)
VLF	Very Low Frequency Converter	29.90	(-)
FL1	Frequency Agile Audio Filter	79.35	(-)
FL2	Multi-mode Audio Filter	89.70	(-)
FL3	FL2 + Auto Notch	129.37	(-)
ASP	Auto RF Speech Clipper (4pin plugs)	82.80	(-)
D75	Manually controlled RF Speech Clipper	56.35	(-)
RFC/M	RF Speech Clipper Module	29.90	(-)
D70	Morse Tutor	56.35	(-)
AD370	Outdoor Active Antenna	64.40	(-)
AD270	Indoor Active Antenna	47.15	(-)
MK	Keyboard Morse Sender	137.42	(-)
Codecall	Selective Calling Device	33.92	(-)
RFA	Wideband Preampifier	33.92	(-)
DC144/28	2M to 28MHz converter	39.67	(-)
MPU	Mains Power Unit	6.90	(-)
ANF	Auto notch filter (Audio)	67.85	(-)
SRBZ	Auto Woodpecker Blanker	86.25	(-)

MICROWAVE MODULES

MMT144/28	2M Transverter for HF Rig	109.95	(-)
MMT432/28S	70cm Transverter for HF Rig	159.95	(-)
MMT432/144R	70cm Transverter for 2M Rig	184.00	(-)
MMT70/28	4M Transverter for HF Rig	119.95	(-)
MMT70/144	4M Transverter for 2M Rig	119.95	(-)
MMT1296/144	23cm Transverter for 2M Rig	184.00	(-)
MML144/30	2M 30W Linear Amp	69.95	(-)
MML144/100S	2M 100W Linear Amp (10W I/P)	139.00	(-)
MML144/100LS	2M 100W Linear Amp (3W I/P)	159.00	(-)
MML432/30	70cm 30W Linear Amp (3W I/P)	99.00	(-)
MML432/50	70cm/50W Linear Amp	109.95	(-)
MML432/100	70cm 10/100W Linear Amp	228.64	(-)
MM2001	RTTY to TV Converter	189.00	(-)
MM4000	RTTY Transceiver	269.00	(-)
MMC50/28	6M Converter to HF Rig	29.90	(-)
MMC70/28	4M Converter to HF Rig	29.90	(-)
MMC144/28	2M Converter to HF Rig	29.90	(-)
MMC432/28S	70cm Converter to HF Rig	37.90	(-)
MMC432/144S	70cm Converter to 2M Rig	37.90	(-)
MMC435/600	70cm ATV Converter	27.90	(-)
MMK1296/144	23cm Converter to 2M Rig	69.95	(-)
MMD050/500	500MHz Dig. Frequency Meter	75.00	(-)
MMD600P	600MHz Prescaler	29.90	(-)
MMDP1	Frequency Counter Probe	14.90	(-)
MMA28	10M Preamp	16.95	(-)
MMA144V	2M RF Switched Preamp	34.90	(-)
MMF144	2M Band Pass Filter	11.90	(-)
MMF432	70cm Band Pass Filter	11.90	(-)
MMS1	The Morse Talker	115.00	(-)

TELEREADERS (CW & RTTY)

TONO 550	299.00	(-)
TONO 9000	669.00	(-)

POWER SUPPLIES

DRAE	4 AMP	30.75 (1.50)	12 AMP	74.00 (2.00)
	6 AMP	49.00 (2.00)	24 AMP	105.00 (3.00)
BNOS	6 AMP	48.00 (-)	25 AMP	125.00 (-)
	12 AMP	86.00 (-)	40 AMP	225.00 (-)

ROTATORS

Hirschman	RO250 VHF Rotor	45.00	(2.00)
9502B	Colorator (Med. VHF)	56.95	(2.00)
EMR400	Alinco	89.95	(2.50)
KR400RC	Kenpro - inc lower clamps	125.00	(2.50)
KR600RC	Kenpro - inc lower clamps	175.00	(3.00)

MORSE EQUIPMENT

HK708	Up/Down Key	11.95	(0.75)
MK704	Squeeze Paddle	11.95	(0.75)
HK703	Deluxe Key	25.70	(1.20)
EK150	Electronic Keyer	87.00	(-)

TEST EQUIPMENT

Drae VHF Wavemeter	130-450MHz	27.50	(-)
DM81	Trio Dip Meter	71.00	(0.75)
MMD50/500	Dig. Frequency meter (500MHz)	75.00	(-)



MAIL ORDER
Mon-Sat 9-12.30/1.30-5.30

All prices correct at time of going to press.

BREDHURST ELECTRONICS

Goods normally despatched within 24 hrs. **HIGH STREET, HANDCROSS, WEST SUSSEX. TEL. 0444 400786**

RETAIL
Mon-Sat. 9-12.30/1.30-5.30



E.&O.E.

Practical Wireless

FOR THE **Radio** ENTHUSIAST ...

JANUARY 1984 VOL. 60 NO. 1 ISSUE 922

Contents

Staff

- 19** 144MHz Repeaters in Ireland
- 20** Steerable HF Antenna
F. E. Wyer G8RY
- 21** Vertical "V" Antenna
E. J. Pestell G3BPB
- 25** Packet Radio—2
*Margaret Morrison KV7D, Dan Morrison KV7B
and Lyle Johnson WA7GXD*
- 36** PW "Dart" Converter
Rev. G. C. Dobbs G3RJV and Colin Turner G3VTT
- 41** PW Review
Datong ANF Filter
- 42** Two-Band Mini-X Beam
F. C. Smith GW2DDX
- 43** Kite Antennas for Top Band
P. Painting G3OUC
- 48** Adjustable Audio Filter
Tony Smith G4FAI
- 54** Domestic Aerials in the Good Old Days
Old Timer
- 60** Curing TVI to MF/HF Reception
A. J. Cawthorne G3TDJ
- 67** PW Review
Belcom LS20-XE Handheld
- 68** Maths for the RAE—2
Roger Lancaster

Regulars

- | | | |
|------------------|---------------|----------------------|
| 95 Advert Index | 46 Mods | 18 PW RUIS |
| 67 Benny | 22, 63 News | 17 Services |
| 17 Comment | 47 Next Month | 38, 59, 70 Swap Spot |
| 47 Did You Know? | 72 On the Air | |
| 33 Letters | 52 Products | |

EDITORIAL OFFICES

Practical Wireless
Westover House
West Quay Road
Poole, Dorset BH15 1JG
☎ Poole 671191

Geoff Arnold T.Eng(CEI) G3GSR
Editor

Dick Ganderton C.Eng., MIERE, G8VFH

Assistant Editor

Steve Hunt
Art Editor

John Fell G8MCP
Technical Editor

Alan Martin G8ZPW
News & Production Editor

Elaine Howard G4LFM
Technical Sub-Editor

Rob Mackie
Technical Artist

Keith Woodruff
Assistant Art Editor

Sylvia Barrett
Secretarial

ADVERTISEMENT OFFICES

Practical Wireless
King's Reach Tower
Stamford Street
London SE1 9LS
Telex: 915748 MAGDIV-G

Dennis Brough
Advertisement Manager
☎ 01-261 6636
☎ 01-261 6872

Roger Hall G4TNT (Sam)
Ad. Sales Executive
☎ 01-261 6807

Claire Gerrish
Secretary
☎ 01-261 6636

Barbara Blake
Classified Supervisor
☎ 01-261 5897

Ian Sweeney
Make-up & Copy
☎ 01-261 6570

COPYRIGHT © IPC Magazines Limited 1984 Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to our readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

Practical Wireless, January 1984

for the HF man, the **TS 430S**

£736.00 inc vat carriage £6.00



A new HF transceiver, taking into account the outstanding performance of the previous Trio rigs you could be forgiven for thinking that it would be impossible for them to improve on existing models and specifications. Alternatively of course, you might be of the opinion that engineers with the talents as displayed by the designers of such rigs as the TS830S, TS130V and TR2500 etc. would have no trouble in pushing forward the frontiers of transceiver technology as we know it today.

The new HF transceiver from Trio is the TS430S. Those who have seen it and the fortunate ones who have used it on the air are all agreed that here we have a major advance for the enthusiastic operator on today's busy bands. Not only does the transceiver have full amateur band coverage from 160 to 10 metres (including the three new bands) but it also incorporates a general coverage receiver (150 kHz to 30 MHz). The new transceiver features are many; USB, LSB, CW, and AM with FM available (optional FM430 board), compact size 270mm wide/96mm high/275mm deep, continuous tuning over the entire frequency range, two separate VFO's and an up/down scan mode using the optional MC42S microphone. Eight memories, each of which can be used as a separate VFO are provided and frequency scan is programmable between the two frequencies held in memory channels six and seven. Not only does the memory remember frequency but also the mode of operation, thus short wave DX and Broadcast stations can be stored alongside a SSB net channel and complete sense made as the frequencies are scanned. The by now normal Trio features are all included, IF shift, notch filter, speech processor and narrow/wide filter selection on CW, SSB and AM modes.

The TS430S, Trio's rig for today's operator.

and now **RTTY, ASCII and CW** using **TELEREADER** equipment.



I must confess that I was extremely sceptical regarding RTTY and the equipment already on the market. To realise that we were to market the Telereader range did not fill me with enthusiasm. That was the situation before Saturday 22nd October. Being the devoted company man that you all know, I decided to upset my tidy shack, remove TRIO TS700S and put in its place a TELEREADER CWR 685E complete with matching keyboard. The rig was taken home and connected to my shack power supply. After much study of the most comprehensive manual that I have seen, I made the necessary connections to the TS780. I must quickly point out that to connect any of the TELEREADER equipment to either a receiver or transceiver is simple. In the case of the top of the range CWR685E, three connections are required. These are, audio in from the external speaker socket of the TS780, transmit signal from the TELEREADER to the TS780 front panel microphone socket and finally a PTT line which again uses the front panel microphone socket. Simple! Having previously studied the two metre band plan I tuned the transceiver to 145.300, the RTTY afsk calling frequency (audio frequency shift keying) and waited. At this point I must confess I thought about half an hour would be enough, and then I could restore the TS700S to its rightful position. However, before 5 minutes had elapsed the TS780 burst into life but there was nothing on the screen. I quickly changed the baud rate, no success. Getting technical now! The information was arriving but I was still getting nowhere. To speed up matters I decided to throw caution to the wind and transmit, pressed control key + A and began to type. Result: nothing! the TELEREADER appeared to

work but not properly, when I stopped typing no idle tone could be heard, just a continuous carrier.

I must now mention G8FCQ who was the operator I was trying to copy. A more helpful chap I have yet to meet and quickly he put me right. Soon the CWR685E was idling away to itself and typing began. My problem was simple. TELEREADER have designed a beautiful machine, the 33 control commands put the keyboard in control of all functions and make operating a pleasure, but you have to know the commands. Not all of them but the basic ones. For example control key + key A pressed together change the rig from receive to transmit, control key + key Y + key establishes the idle mode and control key + key W sets the page on the monitor so that the five memories can be prewritten.

Why have memories and what is meant by "page"? Until you have experienced RTTY you will have no concept of the different and refreshing style of operating. By splitting the screen into two, you can receive at the top of the screen and at the same time be typing your reply at the bottom. When the other station has concluded his over and sends you "DE G8FCQ KKK" then you can quickly go to transmit (control key + A as you have already instructed the equipment to be in idle mode). The CWR685E begins transmitting what you have already typed at full speed. Soon you are caught up and from then on progress is at your typing speed which in my case is slow, hence the thoughtful inclusion by TELEREADER of memory. The memories are written prior to going on the air or loaded from tape storage and can be up to 5 blocks of information. For example; a CQ call complete with call sign, a response to someone else's call, a description of the station and in the final memory "73 DE G8GIY, THANKS FOR A FINE CONTACT BI BI". Having mastered the memories then you can prepare a sequence transmission. Again for example; memory 0 three times, station identification followed by a DE G8GIY KKK and, now for the sophistication, you can pre-instruct the TELEREADER to return to receive. Real armchair operation, key in control + key A and sit back to await a call. All the normal test transmissions are included and, don't forget, the rig also has ASCII and CW.

I must confess that I have used neither the CW or ASCII modes. My attention has been held by the number of contacts I have had on RTTY. Having said that, one RTTY contact has requested that I stand by with ASCII whilst he moves his terminal into the shack. I await his call.

It is most important that I convey the TELEREADER'S ability to receive under the most difficult conditions, the "fine" control on the front panel adjusts the tuning frequency of the space filter relative to a fixed mark frequency. So if the station you are trying to copy is not perfectly set up re. mark and space then you can make the necessary corrections yourself. This attention to detail is applied to all aspects of TELEREADER equipment and one doesn't have to use the equipment for long before concluding that a skilled electronic design team has been this way before. You may have discerned my enthusiasm, I've thrown my microphone away! after all, on that first weekend I worked on the TELEREADER, ON7XT, perhaps not the best DX but good enough for a beginner.

CWR685E RX/TX Unit
CWR670E RX Only
CWR610E RX Only

£730.99 inc vat
£335.00 inc vat
£175.00 inc vat

LOWE IN LONDON, Open monday to saturday, six days a week
lower sales floor, Hepworths, Pentonville Rd, London. telephone 01.837.6702
LOWE IN GLASGOW, Open tuesday to saturday
4,5 Queen Margarets Rd, Glasgow. telephone 041.945.2626



for the VHF operator, the **TR 7930** mobile transceiver

£305.21 inc vat carriage £6.00



Any amateur who has used or owns a Trio TR7800 has had the finest piece of 2 metre mobile technology at his fingertips. The TR7800 had simply everything that the keen mobile operator could ever want. Of course, there were a few points which customers said could be improved on and, I must admit, we, in the majority of cases, agreed. Trio, with the introduction of the new TR7930, have taken note of this feedback of information and the result, I am sure you will agree, is as close to perfection as you will find in a rig.

The improvements are, a green floodlit LCD readout which does not disappear in strong sunlight, additional memory channels, both timed and carrier scan hold on occupied channels, selectable memory channel for the priority frequency and automatically corrected mode selection (simplex or repeater) without having to instruct the rig. The most significant change is the liquid crystal frequency readout on a green illuminated background, but closely following this must be the ability to omit specific memory channels when scanning, and the programmable scan between user designated frequencies. This gives the rig the ability to scan simplex channels only, without holding on repeaters.

The Trio TR7930. The mobile 2 metre FM rig designed with ease of operation coupled to outstanding performance.

for the serious UHF and VHF operator, a DXing transceiver, the **TS 780**.

With the arrival of the TS780, the dual bander rig has come of age, giving the two band multimode facilities of the original concept, plus a wealth of additional operating facilities. Taking a trip across the front panel of the rig we have the repeater facilities, a non-locking tone switch, ideal now that most repeaters are tone accessed and carrier maintained. The tone, of course, only works whilst the rig is in the FM mode. Below the tone switch is the TX offset switch giving plus or minus 600 KHz or 1.6 MHz, depending on whether 2 metres or 70 cm is selected and last, but certainly not least, reverse repeater – to my way of thinking proof that the TS780 was designed for amateurs by amateurs.

The meter functions on receive as S. meter, ALC meter or as a centre meter, the functions being controlled from a panel switch. On transmit the meter reads relative RF output. Immediately above the digital frequency and memory/VFO indicator are indicating leds: "a busy" led indicating in FM mode whether the squelch is open thereby, assuming the squelch level is correctly set, that the other station is transmitting. A "frequency lock" led tells that the F lock switch is pressed and the VFO knob inoperative. The "on air" led indicates the rig is transmitting and the "offset" led reminds you that the TX offset switch is set to repeater.

The memory operation has been updated:

instead of having to progressively move through the memory content in sequence, by means of a rotary switch any of the ten memories (two more than the TS770's) can be selected at will. Entering frequencies into the memory is easier, as anyone who has a TS770 series will explain. Two priority frequencies are included: 9 and 10. Push buttons to the left of the VFO knob allow either of the two programmed frequencies to be quickly selected, immediately cancelling the previous instructions given to the rig. Just the thing for local net frequencies. SSB mic gain needs no explanation, as does the AF/RF gain control.

On the same control knob as the squelch level is a switch enabling the frequency width of scan to be determined. Briefly, when the rig is set to scan either in FM, FM step or SSB mode you can determine the amount of band to be covered.

The ranges are 0.5, 1, 3, 5 and 10 MHz, thus you can limit the rig to scan just the section of the band used by the mode you have selected. Example: scan width 0.5 MHz, VFO set at 144,000, coverage – 144,000 to 144,5 mode side band – result: free scanning of the SSB portion of the band. On FM the scan locks if a signal is present. On SSB the scan does not stop but you are made aware that there is activity on the band.

Another new control on the TS780 is the IF shift. Available for some time on HF equipment to cope with crowded band conditions, obviously the Trio design engineers have recognised that the 2 metre SSB end of the band can become crowded during contests or when there is "a bit of a lift on". At these times a rig that has the "IF shift" facility will certainly "score points".

The send/receive Vox/Man, meter function, NB, low/high power switches are all well known and have been found on previous generations of Trio base station equipment and again require no explanation. I could say the same thing about the mode switch but here you will notice alongside the standard FM position another marked FM CH. Put the mode switch in this position and instead of a free-running VFO you have a mechanical "click" step feel, the frequency now moving in either 12.5 KHz or 5 KHz steps. Of course the rig will also scan in these steps, controlled either by the scan switch or the up/down shift microphone. Again the Trio amateurs who design the equipment have here a major triumph.

By now you may be seeing why I am so enthusiastic about the TS780 but there is still more to come. How about a memory scan system that will scan either the 2 metre frequencies stored in the memory or the 70 cm ones or, if you wish, both. Well that's another feature of the TS780. Add to this list variable VFO steps of either 20 Hz or 200 Hz, a selectable braked feel to the VFO knob, rapid up and down MHz switching and you have the most comprehensive rig ever seen.

Too complicated some may say. Rubbish say I. Trio thrive on rigs designed to be simple to operate. Do you remember what John wrote in Radcom about the TR7500 and its competitors? And, finally, how about a rig that without resorting to a MHz switch will, by use of the VFO knob, tune from 144 to 146 MHz and from 430 to 440 MHz – only one rig –

£795.00 inc vat carriage £6.00



LOWE ELECTRONICS

Chesterfield Road, Matlock, Derbyshire. DE4 5LE.

Telephone 0629 2817, 2430, 4057, 4995. Telex 377482.

(Delivery of stock items normally by return of post)






South Midlands

* FREE FINANCE • 2 YEAR GUARANTEE
BRANCHES AT: SOUTHAMPTON, LEEDS, CHESTER

SMC WINTER SPECIAL OFFERS

FT902DM ~~£885~~ now only **£765 inc**

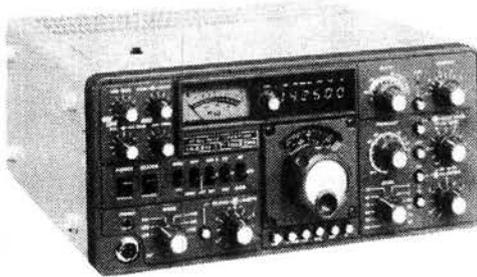

- * 160-10 metres including new allocations.
- * Variable IF bandwidth 2.4kHz down to 300Hz.
- * Audio Peak and independent notch controls.
- * AM, FSK, USB, LSB, CW, FM, (Tx and Rx).
- * Semi-break in, inbuilt Curtis IC Keyer.
- * Digital plus analogue frequency displays.
- * VOX built-in and adjustable.
- * Instant write in memory channel.
- * Tune up button (10 sec. of full power).
- * Switchable AGC and RF attenuator.
- * 350 or 600Hz CW, 6kHz, AM filters included.
- * Clarifier (RIT) switchable on Tx, Rx or both.
- * Plug in modular, computer style constructor.
- * Fully adjustable RF Speech processor.
- * Ergonomically designed with necessary LEDs.
- * Incredible range of matching accessories.
- * Universal power supply 110-234V AC and 12V DC.

FT780R MULTIMODE UHF TRANSCEIVER



~~£389~~
now only
£289 inc

FT780R + 1.6. version with S.M.C. 1.6mHz repeater shift and full reverse R.P.T. facility (for listen on input or continental R.P.T. use) **£299 inc.** N.B. 1.6 mHz shift modification is available only on sets bought from S.M.C. FP80A Matching AC P.S.U. **£55.00 inc.** An unrepeatable bargain not to be missed, and your passport to the D.X. on OSCAR 10 II.

YAESU's LINE-UP FOR '84 THE FT-757GX SYSTEM



FT757GX £625 inc
FP757GX £135 inc

FC757GX £210 inc

Frequency range 160-10m Tx, general coverage RX. 10 Hz VFO steps and 500 KHz band steps.
Modes, USB, LSB, CW, AM, FM all as standard.
Power output 100W SSB, CW, FM 25W carrier AM, 3rd order products -40dB at 100W on 14 MHz.
Dynamic range better than 100dB CW(N) at 14 MHz.
Frequency stability better than ± 10ppm after warm up.
Dual VFO's and 8 memories with VFO/memory transfer feature allowing more flexible split frequency operation.
Programmable memory scanning with scanstop threshold adjustable with the RF Gain control.
All accessories installed including AM, FM, Marker, Speech processor, shift filters, 600Hz CW filter and keyer.
New heatsink design and ducted cooling system allow 100W o/p at 100% transmitter duty cycle.
Selectable semi break-in or full break-in and built in iambic keyer with dot-dash memory.
Three microprocessors control most of the switching and adjusting functions normally done by hand and an optional CAT interface unit allow further operating flexibility with an external computer.

SMC STOCK CARRYING AGENTS WITH DEMONSTRATION FACILITIES

Neath John GW4FOI (0639) 52374 Day (0639) 2942 Eve Bangor John G13KDR (0247) 55162 Tandragee Mervyn G13WVY (0762) 840656 Stourbridge Andrew G4BJY (0384) 390916

SMC SERVICE

Free Securicor delivery on major equipment. Access and Barclaycard over the phone. Biggest branch agent and dealer network. Securicor 'B' Service contract at £4.49. Biggest stockists of amateur equipment. Same day despatch whenever possible.

FREE FINANCE

* On many regular priced items SMC offers. Free Finance (on invoice balance over £120). 20% down and the balance over 6 months or 50% down and the balance over a year. You pay no more than the cash price!! Further details and eligible items available on request. ● 2 year warranty on regular priced Yaesu products.

GUARANTEE

Importer warranty on Yaesu Musen products. Aply staffed and equipped Service Department. Daily contact with the Yaesu Musen factory. Tens of thousands of spares and test equipment. Twenty-five years of professional experience.

Communications Ltd.

SOLE, MAIN DISTRIBUTOR FACTORY BACKED
 WELLD, BUCKLEY, STOKE, GRIMSBY, JERSEY, EDINBURGH.



POWER METERS, MORSE KEYS, ANTENNAS, ROTATORS, LINEARS, PREAMPS ETC.



HANSEN		P&P
FS710H	1.8-60MHz 15/150/1500W Pep	£89.70 FOC
FS710V	50-150MHz 15/150W Pep	£88.70 FOC
FS50HP	1.8-80MHz 20/200/2000W Pep	£88.70 FOC
FS50VP	50-150MHz 20/300W Pep	£69.70 FOC
FS500H	1.8-80MHz 20/200/2000W Pep	£69.70 FOC
FS500V	50-150MHz 20/200W Pep	£69.70 FOC
FS300H	1.8-80MHz 20/200/1000	£46.40 FOC
FS300V	50-150MHz 20/200	£46.40 FOC
FS200	1.8-150MHz 20/200 Pep	£50.60 FOC
FS601M	1.8-30MHz 20/200W Pep	£51.35 FOC
FS601MH	1.8-30MHz 200/2000W Pep	£51.35 FOC
FS602M	50-150MHz 20/200W Pep	£51.35 FOC
FS603M	430-440MHz 5/20W Pep	£51.35 FOC
FS210	1.8-150MHz 20/200W Auto SWR	£55.20 FOC
FS301M	2-30MHz 20/200W	£36.65 FOC
FS301MH	2-30MHz 200/2000W	£36.65 FOC
FS302M	50-150MHz 20/200W	£36.65 FOC
FS711H	2-30MHz 20/200W Head	£36.80 FOC
FS711V	50-150MHz 20/200W Head	£36.80 FOC
FS711U	430-440MHz 5/20W Head	£36.80 FOC
HB1	FS711H Coupler	£23.75 FOC
VB1	FS711V Coupler	£23.75 FOC
UB1	FS711U Coupler	£23.75 FOC
FS5E	3.5-150MHz 20/200/1000W HF	£37.20 FOC
FS5S	1.8-150MHz 20/200/1000W HF	£37.95 FOC
FS7	145&432MHz 5/20/200 144	£41.00 FOC
SWR3E	3.5-150MHz 20/200/1000W HF	£25.00 FOC
SWR3S	3.5-150MHz F/S Meter ant.	£28.46 FOC
SWR508	3.5-150MHz Twin Meter	£26.45 FOC
FS20D	3-150MHz 5/20W	£37.95 FOC
FS800	1.8-150MHz 6/30/150W	£115.00 FOC
JD		
JD110	1.5-150MHz 10/100W	£13.80 FOC
MIRAGE		
MP2	50-150MHz 50/500/1500W Pep	£100.00 FOC
SMC		
S3-30L	Mini CB	£8.80 FOC
TS-170L	3.5-170MHz Relative	£14.95 FOC


MORSE KEYS		
BKU1	Squeeze Key	£30.30 £1.20
HK703	Straight Key	£25.70 £1.20
HK704	Straight Key	£17.65 £1.20
HK706	Straight Key	£14.60 £1.00
HK707	Straight Key	£13.75 £1.00
HK710	Straight Key	£36.40 £1.75
HK808	Straight Key	£45.60 £1.75
HK711	Key Mounting	£29.50 £1.50
BK100	Mechanical Bug	£22.25 £1.75
MK701	Single Lever Paddle	£25.25 £1.60
MK702	Single Lever Paddle	£26.45 £1.60
MK703	Squeeze Key	£25.96 £1.75
MK705	Squeeze Key	£22.60 £1.75
MK706	Squeeze Key	£19.50 £1.75
IKP60	Lambic	£9.95 FOC
SR1	Straight Key	£12.65 FOC

MORSE EQUIPMENT		
KP100	Squeeze CMOS 230 / 13.8V	£69.00 £2.00
KP200	Memory 4096 Multi Ch Mem Back Up 230 / 13.8V	£155.25 £2.50

DATONG Morse Tutor £56.35 FOC

PRICES INCLUDE VAT at 19%
 Mainland carriage where applicable

JAYBEAM		
4Y/4M	Yagi 4 element	7dB £29.90 £2.20
PW12/4M	Phasing harness 2-way	£16.10 £1.50
HO/2M	Halo head only	0dB £5.98 £1.20
HM/2M	Halo with 24" mast	0dB £6.55 £1.20
CS/2M	Colinear omnivert	4.8dB £54.62 £2.50
LW5/2M	Yagi 5 element	7.8dB £14.37 £2.50
LW8/2M	Yagi 8 element	9.5dB £17.82 £2.50
LW10/2M	Yagi 10 element	10.5dB £24.15 £2.50
LW16/2M	Yagi 16 element	13.4dB £35.07 £3.20
14Y/2M	Yagi 14 element	12.8dB £36.23 £3.20
PBM10/2M	10 ele Parabeam	11.7dB £44.85 £3.20
PBM14/2M	14 ele Parabeam	13.7dB £55.77 £3.20
Q4/2M	Quad 4 element	9.4dB £29.32 £2.50
Q6/2M	Quad 6 element	10.9dB £39.10 £2.50
Q8/2M	Quad 8 element	11.9dB £44.85 £2.50
D5/2M	Yagi 5 over 5 slot	10dB £25.30 £2.50
D8/2M	Yagi 8 over 8 slot	11.1dB £34.50 £2.50
5XY/2M	Yagi 5 ele crossed	7.8dB £28.17 £2.50
8XY/2M	Yagi 8 ele crossed	9.5dB £35.65 £2.50
10XY/2M	Yagi 10 ele crossed	£46.00 £2.50
PMH2/C	Harness cir polarisation	£9.77 £1.50
PMH2/2M	Harness 2-way 14MHz	£12.65 £1.50
PMH4/2M	Harness 4-way 14MHz	£28.75 £1.50
C8/70	Colinear Omni Vertical	6.1dB £62.10 £2.50
D8/70	Yagi 8 over 8 slot	12.3dB £25.87 £2.50
PBM18/70	18 ele Parabeam	13.5dB £32.20 £2.50
PBM24/70	24 ele Parabeam	15.1dB £42.55 £2.50
LW24/70	Yagi 24 element	14.8dB £27.02 £2.50
MBM28/70	28 ele Multibeam	11.5dB £21.27 £2.50
MBM48/70	48 ele Multibeam	14.0dB £35.65 £2.50
MBM88/70	88 ele Multibeam	16.3dB £48.87 £2.50
8XY/70	Yagi 8 ele crossed	10dB £42.55 £2.50
12XY/70	Yagi 12 ele crossed	12dB £52.90 £2.50
PMH2/70	Harness 2-way	£10.35 £1.50
PMH4/70	Harness 4-way	£22.42 £1.80
CR2/23CM	Corner reflector	13.5dB £40.25 £2.50
PMH2/23CM	Harness 2-way	£31.05 £1.50

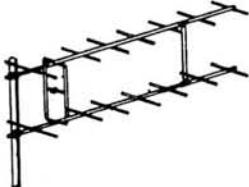

SMC-HS		
SMCGDX1	Discone 80-480MHz 3dB 33'	£40.25 £2.50
SMCGDX2	Discone 50-480MHz 3dB 62'	£49.45 £2.50
GDXA	Discone 100-440MHz 3dB	£33.75 £2.50
SMCVHFL	Discone 65-520MHz Rx only 50'	£15.70 £2.50
SMCGP23	Colinear 2M 3 x 1/2 wave 7.8dB 146'	£39.85 £2.50
SMCGP144W	Colinear 2M Multi 1/2 wave 6.5dB 102'	£27.60 £2.50
SMCGP2M	1/2 wave c/w ground plane 3.4dB 46'	£18.00 £2.50
SMCSQ144	2M Swiss Quad for vertical mounting	£57.60 £2.50
SMCGP432X	Colinear 70cm 3 x 1/2 wave 6.8dB 56'	£29.90 £2.50
SMC702V	Colinear 2.8dB 2M, 5.7dB 70cm 3.6'	£29.90 £2.50
SMC2HB6	6M HB9CV 2 Driven elements	£19.95 £2.50
SMCHS770	144/432 Duplexer 50W 30dB isolation	£15.35 £1.50

HY GAIN		
12AVQ	Vertical 10, 15, 20, 14.0'H	£50.60 £2.75
14AVQ/WB	Vertical 10, 15, 20, 40 18.0'H	£64.40 £2.75
18AVT/WB	Vertical 10, 15, 20, 40, 80M 25.0'H	£113.85 £2.75
14RMQ	Roof mounting Kit 12AVQ 14AVQ & 18AVT	£38.52 £2.75
18V	Vertical 10, 15, 20, 40, 80M 19.0'H	£36.22 £2.75
103BA	3 Ele Yagi 10 metres 17.0'LE 8.0'B	£67.85 £3.50
105BA	5 Ele Yagi 10 metres 18.5'LE 24.0'B	£155.25 £3.95
153BA	3 Ele Yagi 15 metres 23.0'LE 12.0'B	£90.85 £3.50
155BA	5 Ele Yagi 15 metres 24.5'LE 26.0'B	£236.90 £5.90
203BA	3 Ele Yagi 20 metres 35.0'LE 16.0'B	£178.25 £4.90
204BA	4 Ele Yagi 20 metres 36.5'LE 26.0'B	£286.35 £7.30
205BA	5 Ele Yagi 20 metres 36.5'LE 24.0'B	£386.75 £9.40
402BA	2 Ele Yagi 40 metres 43.0'LE 16.0'B	£247.75 £6.50
DB10/15A	3 Ele Yagi 10-15M 23.0'LE 13.0'B	£196.95 £4.80
TH3JNR	3 Ele Yagi 10-15-20M 24.2'LE 12.0'B	£202.40 £3.50
TH2MK3	3 Ele Yagi 10-15-20M 27.3'LE 6.0'B	£169.05 £3.50
TH3MK3	3 Ele Yagi 10-15-20M 27.0'LE 14.0'B	£274.85 £5.30
TH5DX	"Thunderbird" 5 Ele 31.0'LE 18.0'B	£419.75 £6.70
TH6DX	"Thunderbird" 6 Ele 31.1'LE 24.0'B	£396.75 £8.50
TH7DX	"Thunderbird" 7 Ele 31.0'LE 20.0'B	£511.75 £8.75
HYQUAD	2 Ele Quad 10, 15, 20M 13.5'TR 8.0'B	£354.20 £6.00



Type	Description	Price
RLD3	Bell	5 Core Light Duty £40.25
505	Bell	5 Core Light Duty £40.25
AR30	Offset	5 Core Light Duty £56.35
KP250	Bell	6 Core Lighter Duty £54.91
9502B	Offset	3 Core Lighter Duty £56.32
AR22	Bell	4 Core Medium Duty £67.85
9508	Offset	3 Core Medium Duty £80.21
AR40	Bell	5 Core Medium Duty £90.85
BT1	Bell	5 Core 4 Preset Medium £91.43
KR400	Bell	6 Core Medium matches K8500 £97.75
KR500	Thro	6 Core Elevation £112.12
AR50	Bell	5 Position Medium £113.85
KR400RC	Bell	6 Core Medium Duty £114.94
CD45	Bell	8 Core Heavy Duty £136.85
KR600RC	Bell	8 Core Heavy Duty £163.30
HAM IV	Bell	8 Core Heavy Duty £258.75
KR200RC	Bell	8 Core Heavy Duty £314.52
TXZ	Bell	8 Core Very Heavy Duty £327.75
H300	Bell	8 Core Digital Readout £493.35

LINEAR AMPLIFIERS

KLM	Description	Price
PA15/160BL	160W out 15W in	£195.50 FOC

Microwave Modules

MML28/100S	10M/10W in 100W	£129.95 FOC
MML70/50S	4M 10W in 50W out	£92.00 FOC
MML70/100S	4M 10W in 100W out	£149.95 FOC
MML144/30LS	2M 1/3W in 30W out	£69.95 FOC
MML144/50S	2M 10W in 50W out	£92.00 FOC
MML144/100S	2M 10W in 100W out	£149.95 FOC
MML144/100LS	2M 1/3W in 100W out	£169.95 FOC
MML432/30L	70cm 1/3W in 30W out	£129.95 FOC
MML432/50L	70cm 10W in 50W out	£129.95 FOC
MML432/100L	70cm 10W in 100W out	£245.00 FOC

TRANSVERTERS

Microwave Modules	Description	Price
MMT28/144	2M Down to 10M	£129.95 FOC
MMT70/28	10M Up to 4M	£129.95 FOC
MMT70/144	2M Down to 4M	£129.95 FOC
MMT144/28	10M Up to 2M	£109.95 FOC
MMT432/28S	10M Up to 70cm	£159.95 FOC
MMT432/144R	2M Up to 70cm	£184.00 FOC
MMT432/144S	2M Up to 70cm	£184.00 FOC
MMT1296/144	2M Up to 23cm 2W	£199.00 FOC
MTV435	70cm ATV 20W Transmitter	£149.00 FOC



CONVERTERS/PREAMPS

Microwave Modules	Description	Price
MMA28	10M Low Noise Preamp	£19.95 FOC
MMC28/144	10M Up to 2M	£29.90 FOC
MMC70/28	4M Down to 10M	£29.90 FOC
MMA144/V	2M RF Switching Preamp	£34.90 FOC
MMC144/28	2M Down to 10M	£29.90 FOC
MMC432/28S	70cm Down to 10M	£37.50 FOC
MMC432/144S	70cm Down to 2M	£37.50 FOC
MMC435/600	70cm ATV Up to UHF Ch 35	£29.90 FOC
MMA1296	23cm Low Noise Preamp	£34.90 FOC
MK1296/144	23cm Down to 2M	£79.95 FOC

MUTEK	Description	Price
SLNA144S	144MHz switched preamp	£37.10 £2.00
SLNA144u	144MHz unswitched preamp	£22.40 £2.00
SLNA144ub	Unboxed version of SLNA 144u	£13.70 £2.00
SLNA144sb	FT290R optimised preamp	£27.40 £2.00
SBLA144e	144MHz Mosfet Masthead	£79.90 £2.00
GFBA144e	144MHz Gasfet Masthead	£129.90 £2.00
TLNA432s	432MHz switched preamp	£74.90 £2.00
TLNA432u	Unswitched TLNA432s	£29.00 £2.00
TLNA432ub	Unboxed TLNA432u	£20.40 £2.00
GLNA432u	432MHz gasfet amplifier	£52.90 £2.00

HEAD OFFICE S.M. HOUSE, RUMBRIDGE STREET, TOTTEN, SOUTHAMPTON, SO4 4DP, ENGLAND,
 & MAIL ORDER Tel: Totton (0703) 867333, Telex: 477351 SMCOMM G, Telegram: "Aerial" Southampton

LEEDS	CHESTERFIELD	BUCKLEY	STOKE	GRIMSBY	JERSEY	EDINBURGH
SMC (Leeds) 257 Otley Road Leeds 16, Yorkshire Leeds (0532) 782326 9-5.30 Mon-Sat	SMC (Jack Twendy) Ltd 102 High Street New Whittington, Chesterfield Chesterfield (0246) 453340 9-5 Tues-Sat	SMC (TMP) Unit 27, Pinfold Lane Buckley, Chwyndy Buckley (0244) 549563 9.30-5.30 Tues-Sat	SMC (Stoke) 76 High Street Talks Pits, Stoke Kidsgrove (07816) 72644 9-5.30 Tues-Sat	SMC (Grimsby) 2474 Freeman Street Grimsby, Lincs Grimsby (0472) 59388 9.30-5.30 Mon-Sat	SMC (Jersey) 3 Belmont Gardens St. Helier, Jersey Jersey (0534) 77067 10-7 Mon-Sat	SMC Scotcomm 23 Morton Street Edinburgh EH15 2HN Tel: 031 657 2430 10-5 Tues Fri, 9-4 sat

WE DON'T BELIEVE IN MINCING WORDS. WE LEAVE ALL THAT TO OUR COMPETITORS.


ICOM FROM THANET IS QUITE SIMPLY, THE BEST.

**Something new
to celebrate!
IC-745 HF Transceiver £759.**



What's the celebration about?
The IC-745... a new all band HF transceiver with SSB, AM receive only, CW, RTTY, FM option, and 100KHz - 30MHz general coverage receiver. And...the IC-745 has a combination of features found on no other transceiver at such an incredibly low price. See the IC-745 at our shop and showroom at Herne Bay or contact your local authorised ICOM dealer for more information.

IC-R70, HF Receiver, £499.

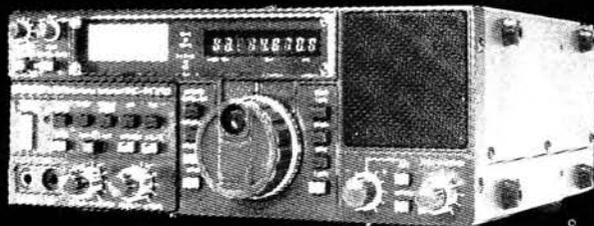

The R-70 covers all modes (when the FM option is included), and uses 2 CPU-driven VFO's for split frequency working, and has 3 IF frequencies: 70MHz, 9MHz and 455KHz, and a dynamic range of 100dB. It has a built-in mains supply.

**NEW! IC-271, £569. VHF
Multimode Base station**



Icom have made improvements to the IC-251 and brought it up to date. Power can be adjusted up to 25W on all modes SSB, CW and FM. Squelch works on all modes and a listen-input facility has been added for Repeater work. RIT shift is shown on the display. 10 Hz tuning facility. Options include a switchable front end pre-amp. Speech synthesizer announcing displayed frequency. 22 Channel memory extension - with scan facilities. Internal chopper PSU, SM5 desk mic. Why not call us for further details?

**NEW! IC-120, 1296 MHz FM
£419.**



Thinking of 1296? Then Icom IC-120 could be the answer.
Now you can have the sophistication of today's technology on this up and coming band-all built into a unit the same size as the IC-25E, very compact...

Thanet ICOM Thanet ICOM Thanet ICOM Thanet ICOM Thanet ICOM Thanet ICOM

IC-751, £969. HF Transceiver




Think about the IC-740. One of the most popular amateur bands transceivers, make a few improvements such as adding 36 memory channels, doing away with mechanical bandswitching and then add full HF receive capability (0.1-30 MHz) which is even an improvement on the famous R70 and you get a pretty good idea of what the IC-751 is like. It is fully compatible with Icom Auto units such as the AT-500 and IC-2KL and a further option for computer control can be added. There is also a digital speech synthesizer option which will be ideal for blind operators. For power supplies you have the option of the IC-PS740 (which fits inside) or the PS-15/PS20 range for external use.

RTTY, Morse & ASCII

Shortwave listeners and amateurs are able to take more interest in other modes of transmission than speech with the latest range of decoders and senders available. As well as amateur transmissions, there is an abundance of news and other interesting broadcasts which can be read using these space-age devices.

Some models in our range are the Tono 550, 9000E and the Telereader CWR-670, CWR-685E and CWR-610E. There is now available a professional version of the Tono 9000E, the PRO-1, which has a built-in scrambler. The Telereader CWR-670 is also available with a built-in VDU which can include a 40 column printer.

**TONO 9000E
Sender/Decoder
£669.**

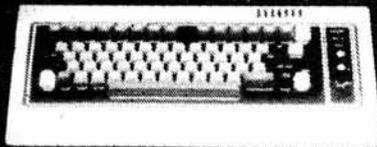

Code Master CW/RTTY

**CWR-610E, Decoder
£189.**

As U.K. importers of the renowned TONO and TELEREADER products, we can offer you a wide range, from a simple morse and RTTY reader which can be plugged into your TV, to a complete send and receive system with memories and built-in displays, or outputs for high-definition VDU.

As well as stocking the complete ICOM range of equipment suitable for European use, we also sell Yaesu, Jaybeam, Datong, Welz, G-Whip, Western, TAL, Bearcat, Versatower and RSGB publications from our shop and showroom at the address below.

IC-290D, VHF. £433. Multimode Mobile



The recently introduced IC-290H has proved so popular that we have decided to concentrate on this (25W) model 2m multimode. With its bright green display, 5 memories, scan facilities on either memories or the whole band, tone-call button on the microphone and instant listen input for repeaters, this little box really is a beauty. The 70cm version, the IC-490E has similar features (although the output is only 10W in this case).

**IC-2E, VHF/FM, £179.
IC-4E UHF, £199.**



Nearly everybody has an IC2E – the most popular amateur transceiver in the world – there is also the 70 cm version which is every bit as good and takes the same accessories.

**IC-25H/25E, £329/£369.
VHF, FM Mobiles**



The FM mobile choice has to be the Icom IC-25E. It is so small yet boasts a powerful 25 Watt voice and a sensitive receiver. The new 25H now available has a green display and 45 Watts output. There are five easily programmable memories, and facilities for changing the repeater shift from the default value of 600kHz.

Agent Please telephone first, anytime between 0900 – 2200 hrs.
Gordon Adams G3LEQ Tel: Knutsford (0565) 4040

**All prices shown include VAT.
Interest-free credit available
Securkor or post despatch free,
same day if possible.**

Thanet Electronics
143 Reculver Road, Herne Bay, Kent
Tel: (02273) 63859/63850
BANKCARD
VISA
Don't miss it



AMATEUR ELECTRONICS UK

SERVING YOU SINCE 1962!



THE SYMBOL OF TECHNICAL EXCELLENCE

Your number one source for **YAESU MUSEN**



Sincere Seasonal Greetings to all our friends

When you buy from Amateur Electronics UK you are dealing with the **FACTORY APPOINTED IMPORTER** with the largest stocks of equipment and spares in the country. Our delivery and after-sales-service is second to none and for your convenience we offer the following facilities ● Interest free finance (50% deposit - balance over 12 months) ● Free Securicor delivery on all major items ● **FACTORY BACKED EQUIPMENT** ● Extensive showroom/demonstration facilities ● Private large car park ● Now with **LOWER THAN EVER** prices - Your choice just has to be **YAESU** - write or phone for all details. Mail Order - All stock items same day service.

Mail Order - All stock items same day service


FT-757GX The latest all-mode HF rig from **YAESU**

How do they do it? - To get so much in so small a package - Just look at the features.

- All-mode operation SSB, CW, AM and FM are included as standard features. ● Full CW break-in. ● Dual VFO plus eight memories. ● Programmable memory scanning.
- 600Hz CW filter fitted. ● Iambic keyer with dot-dash memory.
- IF shift and width filters. ● TX coverage 160 thru 10 metres.
- High performance general coverage RX 500KHz - 29.999MHz.

Special Introductory Offer
Optional P.S.U.'s FP-757 (plinth type) FP-700

£ 625

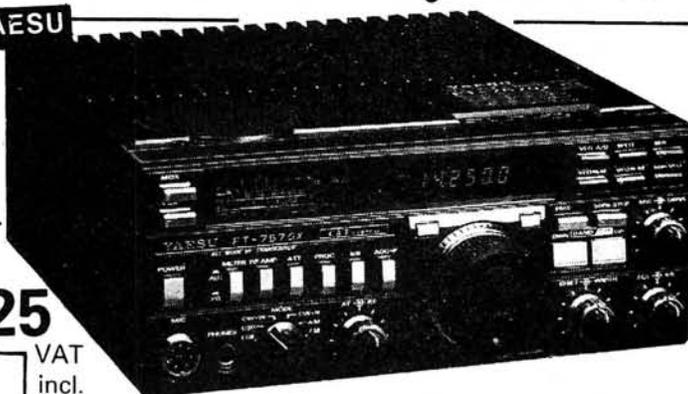

VAT incl.

FT-77 HF transceiver



Not just a mobile rig - with matching PSU and ATU this makes a first class budget station.

FT-77 - New low price **£ 459** VAT incl.
FT-77s - (10W version) **£ 399** VAT incl.

FT-102 HF transceiver



The superb 102 - Now the buy of a lifetime at **£ 685** VAT incl.

FT-107 HF transceiver



We are clearing out last stocks of this superb all solid-state rig at a very special price - Phone for details.

FT-980 All-mode HF transceiver



The ultimate HF rig - Superb all-mode operation plus full general coverage receiver. Rolls Royce performance at **£ 1,150** VAT incl.

NEW NORTHERN BRANCH!

We are pleased to announce that Harry Leeming G3LLL of Messrs Holdings, Blackburn, has now joined us and will be operating as Holdings (Amateur Electronics UK) from premises at 45 Johnston Street, Blackburn.

A full range of all our products including all Yaesu models will be in stock

Phone Harry on 0254 59595 for all the details

FT-726R VHF/UHF multi-mode



YAESU's latest VHF/UHF base station now comes to you at **£675** VAT incl. (70cm unit optionally extra).

FT-480R 2 metre multi-mode



Now back in town by popular demand! **£399** VAT incl.

FT-790R 70cm multi-mode portable

Your best buy at **£299** VAT incl.




FT-290R

2 metre multi-mode portable

This famous set now comes at **£249** VAT incl

FRG-7700 General coverage receiver

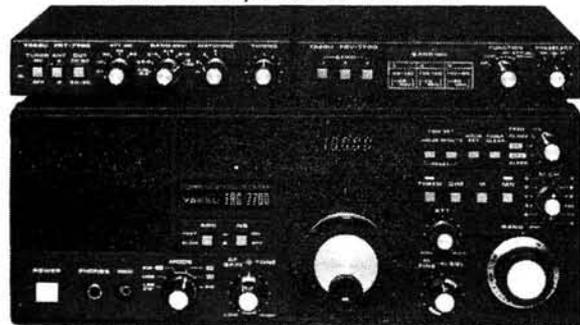With memory **£389** VAT incl.
Less memory **£335** VAT incl.



Attention FRG-7700 owners!

See us for your special requirements in converters and active antennas - complete range ex stock - Post free.

For full details of these new and exciting models, send today for our latest SHORT FORM CATALOGUE. All you need do to obtain the latest information about these exciting developments from the World's No.1 manufacturer of amateur radio equipment is to send 36p in stamps and as an added bonus you will get our credit voucher value £3.60-a 10 to 1 winner!

FT-230R 2 metre 25 watt FM mobile

A marvellous buy at only **£239** VAT incl.



FT-730R

70cm FM mobile

This is real value- for-money.

At the new price of **£259** VAT incl.

FT-780R 70cm multi-mode




Limited stocks only
but first come first served

at **£299** VAT incl.

FT-208R

FT-708R

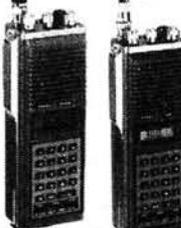

FT-208R 2 metre FM hand-held

The finest hand-held bar none at under **£200**. **£199** VAT incl.

FT-708R 70cm FM hand-held

New low price of **£209** VAT incl.

AGENTS

Wales & West - Ross Clare, GW3NWS, Gwent (0633) 880 146
East Anglia - Amateur Electronics UK, East Anglia, Dr. T. Thirst (TIM) G4CTT
Norwich 0603 667189
North East - North East Amateur Radio, Darlington 0325 55969
Shropshire - Syd Poole G3IMP, Newport, Salop 0952 814275

As factory appointed importers we offer you-
widest choice, largest stocks, quickest deal and
fast sure service right through-

504-516 Alum Rock Road - Birmingham 8 Telephone: 021-327 1497 or 021-327 6313
Telex: 334312 PERLECG Open: 9.30 to 5.30 Tues. to Sat. CLOSED all day Monday.


BI-PAK

BI-PAK SOLDER - DESOLDER KIT

Kit comprises: ORDER NO. VP80
 1 High Quality 25 watt General Purpose Lightweight Soldering Iron
 240v mains incl 3/16" (4.7mm) bit
 1 Quality Desoldering Pump
 High Suction with automatic ejection
 Knurled anti-corrosive casing and Teflon nozzle
 1.5 metres of De-Soldering braid on plastic dispenser
 2 yds (1.83m) Resin Cored Solder on Card
 1 Heat Shunt tool tweezer Type

Total Retail Value over £12.00

OUR SPECIAL KIT PRICE £9.95

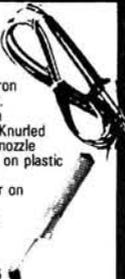

BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
 1 Expo Mini Drill 10,000RPM 12v DC incl 3 collets & 3 x Twist Bits
 1 Sheet PCB Transfers 210mm x 150mm
 1 Etch Resist Pen
 1 1/2lb pack FERRIC CHLORIDE crystals
 3 sheets copper clad board
 2 sheets Fibreglass copper clad board
 Full instructions for making your own PCB boards
 Retail Value over £15.00
 OUR BI-PAK SPECIAL KIT PRICE £9.95
 ORDER NO. VP81



DIGITAL VOLT METER MODULE

3 x 7 segment displays Basic Circuit. 0-2v± instructions provided to extend voltage & current ranges Operating voltage 9/12v Typ. Power Consumption 50mA

D/No. VP99 Once only price £9.95

SINGLE SIDED FIBREGLASS BOARD

Order No/Pieces	Size	Sq. Ins	Price
FB1 4	9 x 2 1/2"	100	£1.50
FB2 3	11 x 3"	100	£1.50
FB3 4	13 x 3"	156	£2.00

DOUBLE SIDED FIBREGLASS BOARD

FB4 2	14 x 4"	110	£2.00
-------	---------	-----	-------

"BCSBB"

BI-PAK COMPONENT & SEMICONDUCTOR BARGAIN BOX

This collection of Components & Semiconductors for the hobbyist is probably the most value packed selection ever offered, it consists of Resistors, carbon & wirewound of various values, Capacitors, All types sorts & sizes including electrolytics, Potentiometers, single, dual, slider & preset, Switches, Fuses, Heatsinks, Wire, P.C. Board, Plugs, Sockets, etc. PLUS a selection of Semiconductors for everyday use in popular Hobby Projects, these include: SCR's, Diodes, Rectifiers, Triacs & Bridges as well as a first class mix of Transistors & IC's.

In all we estimate the value of this BCSBB - in current retail catalogues to be over £25. So help yourself to a great surprise and order a Box today for just **£8.50 ONLY** at BI-PAK.

You can call us on 0920 3182/3412 and order it with your Barclaycard or Access Card - 24hr. Answerphone Service NOW. Order No. V.P. 85.

TRIACS - PLASTIC

4 AMP - 400v - T0202 - TAG 136G	100 OFF	50 OFF	100 OFF
40p	£3.75	£17.50	£30.00
8 AMP - 400v - T0220 - TAG 425	60p	£5.75	£27.50
			£50.00

MINIATURE FM TRANSMITTER

Freq: 95-106MHz. Range: 1 mile
 Size: 45 x 20mm Add: 9v batt. **ONLY £5.50**
 Not licenced in U.K.
 ideal for: 007-M15-FBI-CIA-KGB etc.

PROGRAMMABLE UNIJUNCTION TRANSISTOR

PUT case T0106 plastic MEU22 Similar to 2N6027/6028 PNP Silicon
 Price: 1-9 10-49 50-99 100+
 Each 20p 18p 15p 13p
 Normal Retail Price £0.35 each.

OPTO 7-Segment Displays

Brand new 1st Quality LITRONIX DL 707R 14-pin

Red 0.3" Common Anode Display 0-9 with right hand decimal point TTL compatible 5v DC Supply. Data supplied

5 pieces	£3	(60p each)
10 pieces	£5	(50p each)
50 pieces	£20	(40p each)
100 pieces	£35	(35p each)
1,000 pieces	£300	(30p each)

THE MORE YOU BUY - THE LESS YOU PAY

SEMICONDUCTORS FROM AROUND THE WORLD

100 A collection of Transistors, Diodes, Rectifiers & Bridges SCR's, Triacs, I.C.'s & Opto's all of which are current every-day useable devices. Guaranteed Value Over £10 Normal Retail Price. Data etc in every pack. Order No. VP56

Our Price £4.00



OUR GREAT NEW 1984 CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices. There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

We hold vast stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock. The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

To receive your NEW 1984 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-

Send your orders to Dept. PW1
 BI-PAK PO BOX 6, 3 BALDOCK ST.
 WARE, HERTS.



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your Total order. Postage add 75p per Total order.

Silver 70 ANTENNA

Superb 70cms band aerial still at only £31.95

For the discerning DX man who wants only maximum performance!

Tiger LY6 £12.95

Tiger LY8 £19.50

Tiger LY10 £32.95

Plus £4.50 Securicor delivery

Excellent range of two meter antennae



TIGER

GREAT VALUE FOR MONEY!
 Send cheque or money order TODAY

Ant Products

Trade enquiries invited

All Saints Industrial Estate Baghill Lane
 Pontefract West Yorkshire

Telephone: (0977) 700949

AUDIO FILTERS MODELS FL2, FL3, FL2/A

Model FL3 represents the ultimate in audio filters for SSB and CW.

Connected in series with the loudspeaker, it gives variable extra selectivity better than a whole bank of expensive crystal filters. In addition it contains an automatic notch filter which can remove a "tuner-upper" all by itself.

Model FL2 is exactly the same but without the auto-notch. Any existing or new FL2 can be up-graded to an FL3 by adding Model FL2/A conversion kit, which is a stand-alone auto-notch unit. Datong filters frequently allow continued copy when otherwise a QSO would have to be abandoned.

Prices: FL2 £89.70, FL3 £129.37, FL2/A £39.67

ACTIVE RECEIVING ANTENNAS

Datong active antennas are ideal for modern broadband communications receiver - especially where space is limited.

- highly sensitive (comparable to full-size dipoles).
- Broadband coverage (below 200 kHz to over 30 MHz).
- needs no tuning, matching or other adjustments.
- two versions AD270 for indoor mounting or AD370 (illustrated) for outdoor use
- very compact, only 3 metres overall length. • professional performance standards.

Prices: Model AD270 (indoor use only) £51.75 Both prices include mains power unit. Model AD370 (for outdoor use) £69.00

MORSE TUTOR

The uniquely effective method of improving and maintaining Morse Code proficiency. Effectiveness proven by thousands of users world-wide.

- Practise anywhere, anytime at your convenience.
- Generates a random stream of perfect Morse in five character groups.
- D70's unique "DELAY" control allows you to learn each character with its correct high speed sound. Start with a long delay between each character and as you improve reduce the delay. The speed within each character always remains as set on the independent "SPEED" control.
- Features: long life battery operation, compact size, built-in loudspeaker plus personal earpiece.

Price: £56.35

Our full catalogue plus further details of any product are available free on request. All prices include VAT and postage and packing. Goods normally despatched within 3 days subject to availability.

DATONG ELECTRONICS LIMITED

write to dept. PW1
 Spence Mills, Mill Lane
 Bramley, Leeds LS13 3HE
 England
 Tel (0532) 552461

THE CENTRE

LONDON'S NEWEST AND BRIGHTEST EMPORIUM

AND NOW IN THE MIDLANDS TOO!



ALWAYS A GOOD SELECTION OF USED EQUIPMENT AVAILABLE YAESU - TRIO - ICOM STANDARD - FDK ETC. ALL IN GOOD CONDITION, ALL GUARANTEED. PART-EXCHANGE WELCOME PLEASE RING

**XMAS OFFER
COMPLETE CW KIT**
HK707 MORSE KEY
CQ PRACTICE OSCILLATOR
(Variable Tone + Volume)
G4HXZ MORSE TAPE
PACKAGE DEAL

Inc. VAT **£28** Inc. P+P

WE ARE STILL AS ALWAYS KEEN TO PURCHASE YOUR SECOND HAND EQPT. WORKING OR NOT. WE PAY A FAIR PRICE ALSO PART EXCHANGE TRY US LAST WHEN YOU'RE SHOPPING AROUND

WE STOCK JAYBEAM TONNA MM WELZ DRAE DATONG ETC.

JUST ARRIVED
LATEST ISSUE OF THE CONFIDENTIAL FREQ. LIST INTERPOL - MILITARY - AERO SPACE COMMS. AND MANY OTHER INTERESTING FREQS. FULL FREQ COVERAGE 4MHZ to 30MHZ

£10.50
inc. P+P.

**ALINCO
LINEAR AMPS**
70 cms 1-3W in,
3-10W out
2 metres 1-3W in, 30W out
(now with Pre-Amp)
IDEAL FOR YOUR HAND PORTABLE

Inc. VAT **£60** Inc. P+P

NOW!
AT OUR B'HAM BRANCH ALL TYPES RF POWER TRANSISTORS AND POWER MODULES

A FULL RANGE OF ANTENNA LASHING KIT, POLES, BRACKETS, CLAMPS, ROTATORS, CABLES, PLUGS, SOCKETS, METERS, TUNERS.

BARCLAYCARD
ACCESS
CASH
EVEN



*BEST YULE TIDE WISHES
TO OUR MANY CUSTOMERS
FROM THE CQ STAFF*

Goods normally within 7 days


10 MERTON PARK PARADE
KINGSTON ROAD
(JUNCTION MERTON HALL RD.)
LONDON S.W.19
TEL: 01-543 5150/4212
MON-FRI 9.30-6.00, SAT 9.30-4.30



584 HAGLEY ROAD WEST
OLDBURY, BIRMINGHAM
B68 0BS

TEL: 021 421 8201
MON-FRI 9.30-6.00, SAT 9.30-4.30

AMPLIFIERS

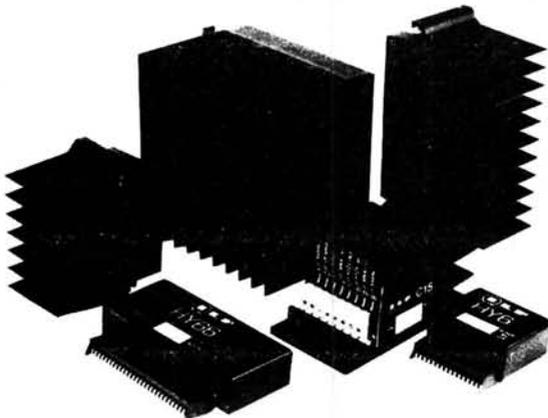

Over the last few years we have received feedback via the general public and industry that our products are from Taiwan, Singapore, Japan, etc... ILP are one of the few 'All British' electronics Companies manufacturing their own products in the United Kingdom. We have proved that we can compete in the world market during the past 12 years and currently export in excess of 60% of our production to over twenty different countries - including USA, Australia and Hong Kong. At the same time we are able to invest in research and development for the future, assuring security for the personnel, directly and indirectly, employed within the UK. We feel very proud of all this and hope you can reap some of our success.

I.L.Potts - Chairman



WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
HY30	15	4-8	0,015%	<0,006%	± 18	76 x 68 x 40	240	£8.40
HY60	30	4-8	0,015%	<0,006%	± 25	76 x 68 x 40	240	£9.55
HY6060	30 + 30	4-8	0,015%	<0,006%	± 25	120 x 78 x 40	420	£18.69
HY124	60	4	0,01%	<0,006%	± 26	120 x 78 x 40	410	£20.75
HY128	60	8	0,01%	<0,006%	± 35	120 x 78 x 40	410	£20.75
HY244	120	4	0,01%	<0,006%	± 35	120 x 78 x 50	520	£25.47
HY248	120	8	0,01%	<0,006%	± 50	120 x 78 x 50	520	£25.47
HY364	180	4	0,01%	<0,006%	± 45	120 x 78 x 100	1030	£38.41
HY368	180	8	0,01%	<0,006%	± 60	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15v/ μ s. Risetime: 5 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz >400.

PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT	Model Number	For Use With	Price inc. VAT	Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93	PSU 52X	2 x HY124	£17.07	PSU 72X	2 x HY248	£22.54
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83	PSU 53X	2 x MOS128	£17.86	PSU 73X	1 x HY364	£22.54
PSU 42X	1 x HY128	£15.90	PSU 54X	1 x HY248	£17.86	PSU 74X	1 x HY368	£24.70
PSU 43X	1 x MOS128	£16.70	PSU 55X	1 x MOS248	£19.52	PSU 75X	2 x MOS248, 1 x MOS368	£4.20
PSU 51X	2 x HY128, 1 x HY244	£17.07	PSU 71X	2 x HY244	£21.75			

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
MOS 128	60	4-8	<0,005%	<0,006%	± 45	120 x 78 x 40	420	£30.41
MOS 248	120	4-8	<0,005%	<0,006%	± 55	120 x 78 x 80	850	£39.86
MOS 364	180	4	<0,005%	<0,006%	± 55	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20v/ μ s. Rise time: 3 μ s. S/N ratio: 100db. Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms. Input impedance: 100K Ω . Damping factor: 100Hz >400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

£9.14 (inc. VAT)

Robust construction.

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz, T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 80dB, Load Impedance 3 Ω .

Input Sensitivity and Impedance (selectable) 700mV rms into 15K Ω . 3V rms into 8 Ω .

Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.



Post to: ILP Electronics Ltd., Dept. 1, Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP. Tel: (0227) 54778 Telex: 965780

YAESU

FT1 (Gen. coverage HF)
FT102 (AM bands HF)
FT77 (9 band HF mobile)
FT230R (2m 25W mobile)
FT290R (2m 2.5W Multimode)
FT480R (2m Multimode mobile)

FT780R (70cm Multimode mobile)
FT208R (2m handheld)
FRG7700 (0 15-30MHz receiver)
FRT7700 (Antenna tuner/switch)
FRA7700 (Active antenna)
QTR24D (Quartz world clock)

PHONE FOR LATEST PRICES ON YAESU EQUIPMENT

SPECIALS!

FT757GX (General coverage, HF) **£599**
FT790 **£249**
TS788DX (Koffeewarmer) 10m **£349**

We also carry a range of products from other manufacturers such as JAYBEAM, MICROWAVE MODULES, L.A.R., DATONG, CUSHCRAFT etc.

7 Day turnaround on all serving - full spares available for all our equipment

ALL PRICES MAY CHANGE OWING TO CURRENCY EXCHANGE FLUCTUATIONS.

All prices include VAT. HP terms available. Part Exchange. Access and Barclaycard welcome. Goods normally despatched by return of post.



*Merry Christmas and
Happy New Year*



GEMSCAN 70

- 70 CHANNELS MEMORY
- DIGITAL CLOCK
- 2 SCAN RATES
- AUTOMATIC AM/FM SWITCH
- LOCKOUT AND PRIORITY FACILITY
- AUTOMATIC SEARCH AND STORE
- DISPLAY SWITCHABLE
- COUNT FACILITY
- STORE FACILITY
- MEMORY BACKUP
- EPROM PROGRAMMABLE
- AUTOMATIC TAPE RECORDER CONTROL
- AC/DC 2-WAY POWER SUPPLY

Frequency Range:

60 - 89 MHz
108 - 138 MHz
140 - 144 MHz
144 - 148 MHz
148 - 179 MHz
380 - 470 MHz
470 - 519 MHz



102 DERBY STREET, BOLTON.
ROY G4GHE Tel: 0204-392226


Your official Sommerkamp Importer
We now stock a comprehensive range
of electronic components.



TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

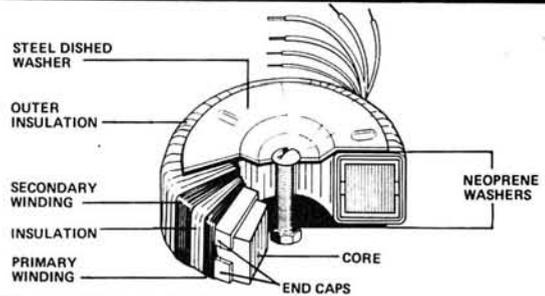Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



15 VA 62 x 34mm Regulation 19%	50 VA 80 x 35mm Regulation 13%	120 VA 90 x 40mm Regulation 11%	225 VA 110 x 45mm Regulation 7%	500 VA 140 x 60mm Regulation 4%																																																																																																																																																																								
<table border="1"> <tr><th>SERIES</th><th>SECONDARY</th><th>RMS</th></tr> <tr><th>No</th><th>Volts</th><th>Current</th></tr> <tr><td>0x010</td><td>6+6</td><td>1.25</td></tr> <tr><td>0x011</td><td>9+9</td><td>0.83</td></tr> <tr><td>0x012</td><td>12+12</td><td>0.63</td></tr> <tr><td>0x013</td><td>15+15</td><td>0.50</td></tr> <tr><td>0x014</td><td>18+18</td><td>0.42</td></tr> <tr><td>0x015</td><td>22+22</td><td>0.34</td></tr> <tr><td>0x016</td><td>25+25</td><td>0.30</td></tr> <tr><td>0x017</td><td>30+30</td><td>0.25</td></tr> </table>	SERIES	SECONDARY	RMS	No	Volts	Current	0x010	6+6	1.25	0x011	9+9	0.83	0x012	12+12	0.63	0x013	15+15	0.50	0x014	18+18	0.42	0x015	22+22	0.34	0x016	25+25	0.30	0x017	30+30	0.25	<table border="1"> <tr><td>2x010</td><td>6+6</td><td>4.16</td></tr> <tr><td>2x011</td><td>9+9</td><td>2.77</td></tr> <tr><td>2x012</td><td>12+12</td><td>2.08</td></tr> <tr><td>2x013</td><td>15+15</td><td>1.66</td></tr> <tr><td>2x014</td><td>18+18</td><td>1.38</td></tr> <tr><td>2x015</td><td>22+22</td><td>1.13</td></tr> <tr><td>2x016</td><td>25+25</td><td>1.00</td></tr> <tr><td>2x017</td><td>30+30</td><td>0.83</td></tr> <tr><td>2x028</td><td>110</td><td>0.45</td></tr> <tr><td>2x029</td><td>220</td><td>0.22</td></tr> <tr><td>2x030</td><td>240</td><td>0.20</td></tr> </table>	2x010	6+6	4.16	2x011	9+9	2.77	2x012	12+12	2.08	2x013	15+15	1.66	2x014	18+18	1.38	2x015	22+22	1.13	2x016	25+25	1.00	2x017	30+30	0.83	2x028	110	0.45	2x029	220	0.22	2x030	240	0.20	<table border="1"> <tr><td>4x010</td><td>6+6</td><td>10.00</td></tr> <tr><td>4x011</td><td>9+9</td><td>6.66</td></tr> <tr><td>4x012</td><td>12+12</td><td>5.00</td></tr> <tr><td>4x013</td><td>15+15</td><td>4.00</td></tr> <tr><td>4x014</td><td>18+18</td><td>3.33</td></tr> <tr><td>4x015</td><td>22+22</td><td>2.72</td></tr> <tr><td>4x016</td><td>25+25</td><td>2.40</td></tr> <tr><td>4x017</td><td>30+30</td><td>2.00</td></tr> <tr><td>4x018</td><td>35+35</td><td>1.71</td></tr> <tr><td>4x028</td><td>110</td><td>1.09</td></tr> <tr><td>4x029</td><td>220</td><td>0.54</td></tr> <tr><td>4x030</td><td>240</td><td>0.50</td></tr> </table>	4x010	6+6	10.00	4x011	9+9	6.66	4x012	12+12	5.00	4x013	15+15	4.00	4x014	18+18	3.33	4x015	22+22	2.72	4x016	25+25	2.40	4x017	30+30	2.00	4x018	35+35	1.71	4x028	110	1.09	4x029	220	0.54	4x030	240	0.50	<table border="1"> <tr><td>6x012</td><td>12+12</td><td>9.38</td></tr> <tr><td>6x013</td><td>15+15</td><td>7.50</td></tr> <tr><td>6x014</td><td>18+18</td><td>6.25</td></tr> <tr><td>6x015</td><td>22+22</td><td>5.11</td></tr> <tr><td>6x016</td><td>25+25</td><td>4.50</td></tr> <tr><td>6x017</td><td>30+30</td><td>3.75</td></tr> <tr><td>6x018</td><td>35+35</td><td>3.21</td></tr> <tr><td>6x026</td><td>40+40</td><td>2.81</td></tr> <tr><td>6x025</td><td>45+45</td><td>2.50</td></tr> <tr><td>6x033</td><td>50+50</td><td>2.25</td></tr> <tr><td>6x028</td><td>110</td><td>2.04</td></tr> <tr><td>6x029</td><td>220</td><td>1.02</td></tr> <tr><td>6x030</td><td>240</td><td>0.93</td></tr> </table>	6x012	12+12	9.38	6x013	15+15	7.50	6x014	18+18	6.25	6x015	22+22	5.11	6x016	25+25	4.50	6x017	30+30	3.75	6x018	35+35	3.21	6x026	40+40	2.81	6x025	45+45	2.50	6x033	50+50	2.25	6x028	110	2.04	6x029	220	1.02	6x030	240	0.93	<table border="1"> <tr><td>8x016</td><td>25+25</td><td>10.00</td></tr> <tr><td>8x017</td><td>30+30</td><td>8.33</td></tr> <tr><td>8x018</td><td>35+35</td><td>7.14</td></tr> <tr><td>8x026</td><td>40+40</td><td>6.25</td></tr> <tr><td>8x025</td><td>45+45</td><td>5.55</td></tr> <tr><td>8x033</td><td>50+50</td><td>5.00</td></tr> <tr><td>8x042</td><td>55+55</td><td>4.54</td></tr> <tr><td>8x028</td><td>110</td><td>4.54</td></tr> <tr><td>8x029</td><td>220</td><td>2.27</td></tr> <tr><td>8x030</td><td>240</td><td>2.08</td></tr> </table>	8x016	25+25	10.00	8x017	30+30	8.33	8x018	35+35	7.14	8x026	40+40	6.25	8x025	45+45	5.55	8x033	50+50	5.00	8x042	55+55	4.54	8x028	110	4.54	8x029	220	2.27	8x030	240	2.08
SERIES	SECONDARY	RMS																																																																																																																																																																										
No	Volts	Current																																																																																																																																																																										
0x010	6+6	1.25																																																																																																																																																																										
0x011	9+9	0.83																																																																																																																																																																										
0x012	12+12	0.63																																																																																																																																																																										
0x013	15+15	0.50																																																																																																																																																																										
0x014	18+18	0.42																																																																																																																																																																										
0x015	22+22	0.34																																																																																																																																																																										
0x016	25+25	0.30																																																																																																																																																																										
0x017	30+30	0.25																																																																																																																																																																										
2x010	6+6	4.16																																																																																																																																																																										
2x011	9+9	2.77																																																																																																																																																																										
2x012	12+12	2.08																																																																																																																																																																										
2x013	15+15	1.66																																																																																																																																																																										
2x014	18+18	1.38																																																																																																																																																																										
2x015	22+22	1.13																																																																																																																																																																										
2x016	25+25	1.00																																																																																																																																																																										
2x017	30+30	0.83																																																																																																																																																																										
2x028	110	0.45																																																																																																																																																																										
2x029	220	0.22																																																																																																																																																																										
2x030	240	0.20																																																																																																																																																																										
4x010	6+6	10.00																																																																																																																																																																										
4x011	9+9	6.66																																																																																																																																																																										
4x012	12+12	5.00																																																																																																																																																																										
4x013	15+15	4.00																																																																																																																																																																										
4x014	18+18	3.33																																																																																																																																																																										
4x015	22+22	2.72																																																																																																																																																																										
4x016	25+25	2.40																																																																																																																																																																										
4x017	30+30	2.00																																																																																																																																																																										
4x018	35+35	1.71																																																																																																																																																																										
4x028	110	1.09																																																																																																																																																																										
4x029	220	0.54																																																																																																																																																																										
4x030	240	0.50																																																																																																																																																																										
6x012	12+12	9.38																																																																																																																																																																										
6x013	15+15	7.50																																																																																																																																																																										
6x014	18+18	6.25																																																																																																																																																																										
6x015	22+22	5.11																																																																																																																																																																										
6x016	25+25	4.50																																																																																																																																																																										
6x017	30+30	3.75																																																																																																																																																																										
6x018	35+35	3.21																																																																																																																																																																										
6x026	40+40	2.81																																																																																																																																																																										
6x025	45+45	2.50																																																																																																																																																																										
6x033	50+50	2.25																																																																																																																																																																										
6x028	110	2.04																																																																																																																																																																										
6x029	220	1.02																																																																																																																																																																										
6x030	240	0.93																																																																																																																																																																										
8x016	25+25	10.00																																																																																																																																																																										
8x017	30+30	8.33																																																																																																																																																																										
8x018	35+35	7.14																																																																																																																																																																										
8x026	40+40	6.25																																																																																																																																																																										
8x025	45+45	5.55																																																																																																																																																																										
8x033	50+50	5.00																																																																																																																																																																										
8x042	55+55	4.54																																																																																																																																																																										
8x028	110	4.54																																																																																																																																																																										
8x029	220	2.27																																																																																																																																																																										
8x030	240	2.08																																																																																																																																																																										
<table border="1"> <tr><th>30 VA 70 x 30mm Regulation 18%</th> <th>80 VA 90 x 30mm Regulation 12%</th> <th>160 VA 110 x 40mm Regulation 8%</th> <th>300 VA 110 x 50mm Regulation 6%</th> <th>625 VA 140 x 75mm Regulation 4%</th> </tr> <tr> <td> <table border="1"> <tr><td>1x010</td><td>6+6</td><td>2.50</td></tr> <tr><td>1x011</td><td>9+9</td><td>1.66</td></tr> <tr><td>1x012</td><td>12+12</td><td>1.25</td></tr> <tr><td>1x013</td><td>15+15</td><td>1.00</td></tr> <tr><td>1x014</td><td>18+18</td><td>0.83</td></tr> <tr><td>1x015</td><td>22+22</td><td>0.68</td></tr> <tr><td>1x016</td><td>25+25</td><td>0.60</td></tr> <tr><td>1x017</td><td>30+30</td><td>0.50</td></tr> </table> </td> <td> <table border="1"> <tr><td>3x010</td><td>6+6</td><td>6.64</td></tr> <tr><td>3x011</td><td>9+9</td><td>4.44</td></tr> <tr><td>3x012</td><td>12+12</td><td>3.33</td></tr> <tr><td>3x013</td><td>15+15</td><td>2.66</td></tr> <tr><td>3x014</td><td>18+18</td><td>2.22</td></tr> <tr><td>3x015</td><td>22+22</td><td>1.81</td></tr> <tr><td>3x016</td><td>25+25</td><td>1.60</td></tr> <tr><td>3x017</td><td>30+30</td><td>1.33</td></tr> <tr><td>3x028</td><td>110</td><td>0.72</td></tr> <tr><td>3x029</td><td>220</td><td>0.36</td></tr> <tr><td>3x030</td><td>240</td><td>0.33</td></tr> </table> </td> <td> <table border="1"> <tr><td>5x011</td><td>9+9</td><td>8.89</td></tr> <tr><td>5x012</td><td>12+12</td><td>6.66</td></tr> <tr><td>5x013</td><td>15+15</td><td>5.33</td></tr> <tr><td>5x014</td><td>18+18</td><td>4.44</td></tr> <tr><td>5x015</td><td>22+22</td><td>3.63</td></tr> <tr><td>5x016</td><td>25+25</td><td>3.20</td></tr> <tr><td>5x017</td><td>30+30</td><td>2.66</td></tr> <tr><td>5x018</td><td>35+35</td><td>2.28</td></tr> <tr><td>5x026</td><td>40+40</td><td>2.00</td></tr> <tr><td>5x028</td><td>110</td><td>1.45</td></tr> <tr><td>5x029</td><td>220</td><td>0.72</td></tr> <tr><td>5x030</td><td>240</td><td>0.66</td></tr> </table> </td> <td> <table border="1"> <tr><td>7x013</td><td>15+15</td><td>10.00</td></tr> <tr><td>7x014</td><td>18+18</td><td>8.33</td></tr> <tr><td>7x015</td><td>22+22</td><td>6.82</td></tr> <tr><td>7x016</td><td>25+25</td><td>6.00</td></tr> <tr><td>7x017</td><td>30+30</td><td>5.00</td></tr> <tr><td>7x018</td><td>35+35</td><td>4.28</td></tr> <tr><td>7x026</td><td>40+40</td><td>3.75</td></tr> <tr><td>7x025</td><td>45+45</td><td>3.33</td></tr> <tr><td>7x033</td><td>50+50</td><td>3.00</td></tr> <tr><td>7x028</td><td>110</td><td>2.72</td></tr> <tr><td>7x029</td><td>220</td><td>1.36</td></tr> <tr><td>7x030</td><td>240</td><td>1.25</td></tr> </table> </td> <td> <table border="1"> <tr><td>9x017</td><td>30+30</td><td>10.41</td></tr> <tr><td>9x018</td><td>35+35</td><td>8.92</td></tr> <tr><td>9x026</td><td>40+40</td><td>7.81</td></tr> <tr><td>9x025</td><td>45+45</td><td>6.94</td></tr> <tr><td>9x033</td><td>50+50</td><td>6.25</td></tr> <tr><td>9x042</td><td>55+55</td><td>5.68</td></tr> <tr><td>9x028</td><td>110</td><td>5.68</td></tr> <tr><td>9x029</td><td>220</td><td>2.84</td></tr> <tr><td>9x030</td><td>240</td><td>2.60</td></tr> </table> </td> </tr> </table>	30 VA 70 x 30mm Regulation 18%	80 VA 90 x 30mm Regulation 12%	160 VA 110 x 40mm Regulation 8%	300 VA 110 x 50mm Regulation 6%	625 VA 140 x 75mm Regulation 4%	<table border="1"> <tr><td>1x010</td><td>6+6</td><td>2.50</td></tr> <tr><td>1x011</td><td>9+9</td><td>1.66</td></tr> <tr><td>1x012</td><td>12+12</td><td>1.25</td></tr> <tr><td>1x013</td><td>15+15</td><td>1.00</td></tr> <tr><td>1x014</td><td>18+18</td><td>0.83</td></tr> <tr><td>1x015</td><td>22+22</td><td>0.68</td></tr> <tr><td>1x016</td><td>25+25</td><td>0.60</td></tr> <tr><td>1x017</td><td>30+30</td><td>0.50</td></tr> </table>	1x010	6+6	2.50	1x011	9+9	1.66	1x012	12+12	1.25	1x013	15+15	1.00	1x014	18+18	0.83	1x015	22+22	0.68	1x016	25+25	0.60	1x017	30+30	0.50	<table border="1"> <tr><td>3x010</td><td>6+6</td><td>6.64</td></tr> <tr><td>3x011</td><td>9+9</td><td>4.44</td></tr> <tr><td>3x012</td><td>12+12</td><td>3.33</td></tr> <tr><td>3x013</td><td>15+15</td><td>2.66</td></tr> <tr><td>3x014</td><td>18+18</td><td>2.22</td></tr> <tr><td>3x015</td><td>22+22</td><td>1.81</td></tr> <tr><td>3x016</td><td>25+25</td><td>1.60</td></tr> <tr><td>3x017</td><td>30+30</td><td>1.33</td></tr> <tr><td>3x028</td><td>110</td><td>0.72</td></tr> <tr><td>3x029</td><td>220</td><td>0.36</td></tr> <tr><td>3x030</td><td>240</td><td>0.33</td></tr> </table>	3x010	6+6	6.64	3x011	9+9	4.44	3x012	12+12	3.33	3x013	15+15	2.66	3x014	18+18	2.22	3x015	22+22	1.81	3x016	25+25	1.60	3x017	30+30	1.33	3x028	110	0.72	3x029	220	0.36	3x030	240	0.33	<table border="1"> <tr><td>5x011</td><td>9+9</td><td>8.89</td></tr> <tr><td>5x012</td><td>12+12</td><td>6.66</td></tr> <tr><td>5x013</td><td>15+15</td><td>5.33</td></tr> <tr><td>5x014</td><td>18+18</td><td>4.44</td></tr> <tr><td>5x015</td><td>22+22</td><td>3.63</td></tr> <tr><td>5x016</td><td>25+25</td><td>3.20</td></tr> <tr><td>5x017</td><td>30+30</td><td>2.66</td></tr> <tr><td>5x018</td><td>35+35</td><td>2.28</td></tr> <tr><td>5x026</td><td>40+40</td><td>2.00</td></tr> <tr><td>5x028</td><td>110</td><td>1.45</td></tr> <tr><td>5x029</td><td>220</td><td>0.72</td></tr> <tr><td>5x030</td><td>240</td><td>0.66</td></tr> </table>	5x011	9+9	8.89	5x012	12+12	6.66	5x013	15+15	5.33	5x014	18+18	4.44	5x015	22+22	3.63	5x016	25+25	3.20	5x017	30+30	2.66	5x018	35+35	2.28	5x026	40+40	2.00	5x028	110	1.45	5x029	220	0.72	5x030	240	0.66	<table border="1"> <tr><td>7x013</td><td>15+15</td><td>10.00</td></tr> <tr><td>7x014</td><td>18+18</td><td>8.33</td></tr> <tr><td>7x015</td><td>22+22</td><td>6.82</td></tr> <tr><td>7x016</td><td>25+25</td><td>6.00</td></tr> <tr><td>7x017</td><td>30+30</td><td>5.00</td></tr> <tr><td>7x018</td><td>35+35</td><td>4.28</td></tr> <tr><td>7x026</td><td>40+40</td><td>3.75</td></tr> <tr><td>7x025</td><td>45+45</td><td>3.33</td></tr> <tr><td>7x033</td><td>50+50</td><td>3.00</td></tr> <tr><td>7x028</td><td>110</td><td>2.72</td></tr> <tr><td>7x029</td><td>220</td><td>1.36</td></tr> <tr><td>7x030</td><td>240</td><td>1.25</td></tr> </table>	7x013	15+15	10.00	7x014	18+18	8.33	7x015	22+22	6.82	7x016	25+25	6.00	7x017	30+30	5.00	7x018	35+35	4.28	7x026	40+40	3.75	7x025	45+45	3.33	7x033	50+50	3.00	7x028	110	2.72	7x029	220	1.36	7x030	240	1.25	<table border="1"> <tr><td>9x017</td><td>30+30</td><td>10.41</td></tr> <tr><td>9x018</td><td>35+35</td><td>8.92</td></tr> <tr><td>9x026</td><td>40+40</td><td>7.81</td></tr> <tr><td>9x025</td><td>45+45</td><td>6.94</td></tr> <tr><td>9x033</td><td>50+50</td><td>6.25</td></tr> <tr><td>9x042</td><td>55+55</td><td>5.68</td></tr> <tr><td>9x028</td><td>110</td><td>5.68</td></tr> <tr><td>9x029</td><td>220</td><td>2.84</td></tr> <tr><td>9x030</td><td>240</td><td>2.60</td></tr> </table>	9x017	30+30	10.41	9x018	35+35	8.92	9x026	40+40	7.81	9x025	45+45	6.94	9x033	50+50	6.25	9x042	55+55	5.68	9x028	110	5.68	9x029	220	2.84	9x030	240	2.60						
30 VA 70 x 30mm Regulation 18%	80 VA 90 x 30mm Regulation 12%	160 VA 110 x 40mm Regulation 8%	300 VA 110 x 50mm Regulation 6%	625 VA 140 x 75mm Regulation 4%																																																																																																																																																																								
<table border="1"> <tr><td>1x010</td><td>6+6</td><td>2.50</td></tr> <tr><td>1x011</td><td>9+9</td><td>1.66</td></tr> <tr><td>1x012</td><td>12+12</td><td>1.25</td></tr> <tr><td>1x013</td><td>15+15</td><td>1.00</td></tr> <tr><td>1x014</td><td>18+18</td><td>0.83</td></tr> <tr><td>1x015</td><td>22+22</td><td>0.68</td></tr> <tr><td>1x016</td><td>25+25</td><td>0.60</td></tr> <tr><td>1x017</td><td>30+30</td><td>0.50</td></tr> </table>	1x010	6+6	2.50	1x011	9+9	1.66	1x012	12+12	1.25	1x013	15+15	1.00	1x014	18+18	0.83	1x015	22+22	0.68	1x016	25+25	0.60	1x017	30+30	0.50	<table border="1"> <tr><td>3x010</td><td>6+6</td><td>6.64</td></tr> <tr><td>3x011</td><td>9+9</td><td>4.44</td></tr> <tr><td>3x012</td><td>12+12</td><td>3.33</td></tr> <tr><td>3x013</td><td>15+15</td><td>2.66</td></tr> <tr><td>3x014</td><td>18+18</td><td>2.22</td></tr> <tr><td>3x015</td><td>22+22</td><td>1.81</td></tr> <tr><td>3x016</td><td>25+25</td><td>1.60</td></tr> <tr><td>3x017</td><td>30+30</td><td>1.33</td></tr> <tr><td>3x028</td><td>110</td><td>0.72</td></tr> <tr><td>3x029</td><td>220</td><td>0.36</td></tr> <tr><td>3x030</td><td>240</td><td>0.33</td></tr> </table>	3x010	6+6	6.64	3x011	9+9	4.44	3x012	12+12	3.33	3x013	15+15	2.66	3x014	18+18	2.22	3x015	22+22	1.81	3x016	25+25	1.60	3x017	30+30	1.33	3x028	110	0.72	3x029	220	0.36	3x030	240	0.33	<table border="1"> <tr><td>5x011</td><td>9+9</td><td>8.89</td></tr> <tr><td>5x012</td><td>12+12</td><td>6.66</td></tr> <tr><td>5x013</td><td>15+15</td><td>5.33</td></tr> <tr><td>5x014</td><td>18+18</td><td>4.44</td></tr> <tr><td>5x015</td><td>22+22</td><td>3.63</td></tr> <tr><td>5x016</td><td>25+25</td><td>3.20</td></tr> <tr><td>5x017</td><td>30+30</td><td>2.66</td></tr> <tr><td>5x018</td><td>35+35</td><td>2.28</td></tr> <tr><td>5x026</td><td>40+40</td><td>2.00</td></tr> <tr><td>5x028</td><td>110</td><td>1.45</td></tr> <tr><td>5x029</td><td>220</td><td>0.72</td></tr> <tr><td>5x030</td><td>240</td><td>0.66</td></tr> </table>	5x011	9+9	8.89	5x012	12+12	6.66	5x013	15+15	5.33	5x014	18+18	4.44	5x015	22+22	3.63	5x016	25+25	3.20	5x017	30+30	2.66	5x018	35+35	2.28	5x026	40+40	2.00	5x028	110	1.45	5x029	220	0.72	5x030	240	0.66	<table border="1"> <tr><td>7x013</td><td>15+15</td><td>10.00</td></tr> <tr><td>7x014</td><td>18+18</td><td>8.33</td></tr> <tr><td>7x015</td><td>22+22</td><td>6.82</td></tr> <tr><td>7x016</td><td>25+25</td><td>6.00</td></tr> <tr><td>7x017</td><td>30+30</td><td>5.00</td></tr> <tr><td>7x018</td><td>35+35</td><td>4.28</td></tr> <tr><td>7x026</td><td>40+40</td><td>3.75</td></tr> <tr><td>7x025</td><td>45+45</td><td>3.33</td></tr> <tr><td>7x033</td><td>50+50</td><td>3.00</td></tr> <tr><td>7x028</td><td>110</td><td>2.72</td></tr> <tr><td>7x029</td><td>220</td><td>1.36</td></tr> <tr><td>7x030</td><td>240</td><td>1.25</td></tr> </table>	7x013	15+15	10.00	7x014	18+18	8.33	7x015	22+22	6.82	7x016	25+25	6.00	7x017	30+30	5.00	7x018	35+35	4.28	7x026	40+40	3.75	7x025	45+45	3.33	7x033	50+50	3.00	7x028	110	2.72	7x029	220	1.36	7x030	240	1.25	<table border="1"> <tr><td>9x017</td><td>30+30</td><td>10.41</td></tr> <tr><td>9x018</td><td>35+35</td><td>8.92</td></tr> <tr><td>9x026</td><td>40+40</td><td>7.81</td></tr> <tr><td>9x025</td><td>45+45</td><td>6.94</td></tr> <tr><td>9x033</td><td>50+50</td><td>6.25</td></tr> <tr><td>9x042</td><td>55+55</td><td>5.68</td></tr> <tr><td>9x028</td><td>110</td><td>5.68</td></tr> <tr><td>9x029</td><td>220</td><td>2.84</td></tr> <tr><td>9x030</td><td>240</td><td>2.60</td></tr> </table>	9x017	30+30	10.41	9x018	35+35	8.92	9x026	40+40	7.81	9x025	45+45	6.94	9x033	50+50	6.25	9x042	55+55	5.68	9x028	110	5.68	9x029	220	2.84	9x030	240	2.60												
1x010	6+6	2.50																																																																																																																																																																										
1x011	9+9	1.66																																																																																																																																																																										
1x012	12+12	1.25																																																																																																																																																																										
1x013	15+15	1.00																																																																																																																																																																										
1x014	18+18	0.83																																																																																																																																																																										
1x015	22+22	0.68																																																																																																																																																																										
1x016	25+25	0.60																																																																																																																																																																										
1x017	30+30	0.50																																																																																																																																																																										
3x010	6+6	6.64																																																																																																																																																																										
3x011	9+9	4.44																																																																																																																																																																										
3x012	12+12	3.33																																																																																																																																																																										
3x013	15+15	2.66																																																																																																																																																																										
3x014	18+18	2.22																																																																																																																																																																										
3x015	22+22	1.81																																																																																																																																																																										
3x016	25+25	1.60																																																																																																																																																																										
3x017	30+30	1.33																																																																																																																																																																										
3x028	110	0.72																																																																																																																																																																										
3x029	220	0.36																																																																																																																																																																										
3x030	240	0.33																																																																																																																																																																										
5x011	9+9	8.89																																																																																																																																																																										
5x012	12+12	6.66																																																																																																																																																																										
5x013	15+15	5.33																																																																																																																																																																										
5x014	18+18	4.44																																																																																																																																																																										
5x015	22+22	3.63																																																																																																																																																																										
5x016	25+25	3.20																																																																																																																																																																										
5x017	30+30	2.66																																																																																																																																																																										
5x018	35+35	2.28																																																																																																																																																																										
5x026	40+40	2.00																																																																																																																																																																										
5x028	110	1.45																																																																																																																																																																										
5x029	220	0.72																																																																																																																																																																										
5x030	240	0.66																																																																																																																																																																										
7x013	15+15	10.00																																																																																																																																																																										
7x014	18+18	8.33																																																																																																																																																																										
7x015	22+22	6.82																																																																																																																																																																										
7x016	25+25	6.00																																																																																																																																																																										
7x017	30+30	5.00																																																																																																																																																																										
7x018	35+35	4.28																																																																																																																																																																										
7x026	40+40	3.75																																																																																																																																																																										
7x025	45+45	3.33																																																																																																																																																																										
7x033	50+50	3.00																																																																																																																																																																										
7x028	110	2.72																																																																																																																																																																										
7x029	220	1.36																																																																																																																																																																										
7x030	240	1.25																																																																																																																																																																										
9x017	30+30	10.41																																																																																																																																																																										
9x018	35+35	8.92																																																																																																																																																																										
9x026	40+40	7.81																																																																																																																																																																										
9x025	45+45	6.94																																																																																																																																																																										
9x033	50+50	6.25																																																																																																																																																																										
9x042	55+55	5.68																																																																																																																																																																										
9x028	110	5.68																																																																																																																																																																										
9x029	220	2.84																																																																																																																																																																										
9x030	240	2.60																																																																																																																																																																										

- Why a Toroid?**
- * Smaller size & weight to meet modern 'slimline' requirements.
 - * Low electrically induced noise demanded by compact equipment.
 - * High efficiency enabling conservative rating whilst maintaining size advantages.
 - * Lower operating temperature.
- Why ILP?**
- * Ex-stock delivery for small quantities.
 - * Gold service available. 21 days manufacture for urgent deliveries.
 - * 5 year no quibble guarantee.
 - * Realistic delivery for volume orders.
 - * No price penalty for call off orders.

Prices including P&P and VAT

VA Size	£	VA Size	£
15 0	7.43	160 5	12.90
30 1	8.08	225 6	16.30
50 2	10.10	300 7	18.55
80 3	10.81	500 8	25.73
120 4	11.73	625 9	31.63

Mail Order - Please make your crossed cheques or postal orders payable to ILP Electronics Ltd.

Trade - We will open your credit account immediately upon receipt of your first order.

Post to: ILP Electronics Ltd., Dept. 1
Graham Bell House, Roper Close,
Canterbury, Kent. CT2 7EP
Tel: (0227) 54778 Telex: 965780



ILP ELECTRONICS LTD.

S.E.M. UNION MILLS, ISLE OF MAN

Tel: MAROWN (0624) 851277



NEW. S.E.M. IMABIC KEYSER. We have replaced its plastic box, with an attractive plated steel case. No better fully auto keyer anywhere. Uses Curtis chip. R.F. proof. £38. A first class twin paddle key £15.
BRAID BREAKER/HI PASS FILTER. Put in T.V. ant. lead to cure TVI. £6.50 Ex stock.

NEW. RF NOISE BRIDGE. Adjustable 0-1,000 ohms, 3" x 1 1/2" x 2" only. SO239s, 1-170MHz. Neat, accurate & economical. £29.50 Ex Stock.

S.E.M. TRANZMATCH
 The most VERSATILE Ant. Matching system. Will match from 15-5000 Ohms BALANCED or UNBALANCED at up to 1kW.. Link coupled balun means no connection to the equipment which can cure TV1 both ways. SO239 and 4mm connectors for co-ax or wire feed. 160-10 metres TRANZMATCH £75.50. 80-10 metres £67.50. EZITUNE built in for £24 extra. (See below for details of EZITUNE). All ex-stock. Note. We sell many more with EZITUNE fitted.

3 WAY ANTENNA SWITCH 1kW SO239s. Good to 2 metres. £15.00 Ex stock. Or 4th position to earth output £17.50 Ex stock.

S.E.M. 2 METRE TRANZMATCH. 5 1/2" x 2", 3" deep. SO239s. £24.90 Ex stock.

S.E.M. EZITUNE.

Because no similar unit is made, it's usefulness is not appreciated until you have used one.

Clean up the bands by tuning up without transmitting.

Connects in aerial lead, produces S9 + (1 - 170MHz) noise in receiver. Adjust A.T.U. or aerial for minimum noise. You have now put an exact 50 Ohms into your transceiver. Fully protected, you can transmit through it, save your P.A., and stop QRM. SO239s. £29.50 Ex stock. P.c.b. to fit any A.T.U. £24 Ex stock.

SENTINEL 2M LINEAR POWER/PRE-AMPLIFIERS
 Now feature either POWER AMP alone or PRE-AMP alone or both POWER AND PRE-AMP or STRAIGHT THROU when OFF. Plus a gain control on the PRE-AMP from 0 to 20dB. N.F. around 1dB with a neutralised strip line DUAL GATE MOSFET (BF981).

Ultra LINEAR for all modes and R.F. or P.T.T. switched. 13.8V nominal supply. SO239 sockets.

Three Models:

1. **SENTINEL 35** Twelve times power gain. 3W IN 36W OUT. 4 amps. Max. drive 5W. 6" x 2 1/2" front panel, 4 1/2" deep. £65 Ex stock.
2. **SENTINEL 50** Five times power gain. 10 W IN 50W OUT. Max drive 16W 6 amps. Same size as the Sentinel 35. £79.50 Ex stock.
3. **SENTINEL 100** Ten times power gain. 10W IN 100W OUT. Max. drive 16W. Size: 6 1/2" x 4" front panel, 3 1/2" deep. 12 amps. £115 Ex stock.

POWER SUPPLIES for our linears 6 amp £34. 12 amp £49.

SENTINEL AUTO 2 METRE or 4 METRE PRE-AMPLIFIER (R.F. Switched) 1dB N.F. and 20dB gain, (gain control adjusts down to unity) 400W P.E.P. power rating. Use on any mode. 12V 25mA. Sizes: 1 1/2" x 2 1/2" x 4". £28.00 * Ex stock.

PA5 Same specification as the Auto including 240V P.S.U. £33.00 *

SENTINEL STANDARD PRE-AMPLIFIER. No R.F. switch. £15.00 * Ex stock.

PA3. 1 cubic inch p.c.b. to fit inside your equipment. £10.00 Ex stock. 70cm versions of all these (except PA5) £4.00 extra. All ex stock.

S.E.M. AUDIO MULTIFILTER (A very good filter at a very good price). To improve ANY receiver on ANY mode. The most versatile filter available. Gives "passband" tuning, "variable selectivity" and one or two notches. Switched Hi-pass, Lo-pass, peak or notch. Selectivity from 2.5KHz to 20Hz. Tunable from 2.5KHz to 250Hz. PLUS another notch available in any of the four switch positions which covers 10KHz to 100Hz. 12V supply. Sizes: 6" x 2 1/2" front panel, 3 1/2" deep, all for only £57.00 Ex stock.

SENTINEL AUTO H.F. WIDEBAND PRE-AMPLIFIER 2-40MHz, 15dB gain. Straight through when OFF, 9-12V. 2 1/2" x 1 1/2" x 3". 200W through power. £19.55 * Ex stock.

SENTINEL STANDARD H.F. PRE-AMPLIFIER. No R.F. switching. £12.62 * Ex stock.

S.E.M. VISA 80 METRE RECEIVER

Already a great success. If you want an 80 metre (3.5-3.8MHz) Rx. Only 2 1/2" x 6" x 3". 12 volt operation. I.W. o/p. This is for you. £45.

FREQ. CONVERTERS from 10KHz to 2 metres in stock.

12 MONTHS COMPLETE GUARANTEE INCLUDING ALL TRANSISTORS.

Prices include VAT and delivery. C.W.O. or phone your credit card number for same day service. *Means Belling Lee sockets, add £1.90 for SO239s or BNC sockets. Ring or write for more information. Place orders or request information on our Ansaphone at cheap rate times.

Goods normally by return.

MASTER ELECTRONICS NOW!

The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY
THIS IS THE AGE OF ELECTRONICS!

the world's fastest growth industry...


Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer. All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state "chips"
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.

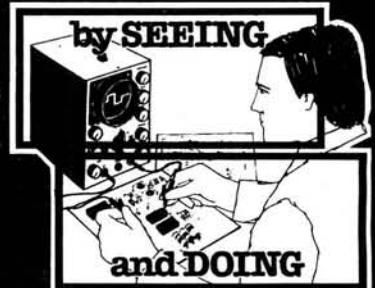

British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE!
 COLOUR
 BROCHURE

Please send your brochure without any obligation to

NAME _____
 ADDRESS _____

I am interested in:

- COURSE IN ELECTRONICS as described above
 RADIO AMATEUR LICENCE
 MICROPROCESSORS
 OTHER SUBJECTS please state below

Post now to:

British National Radio & Electronics School Reading, Berks. RG1 1BR

BLOCK CAPS PLEASE



OR TELEPHONE US
 0734 51515 OR
 TELEX 22758
 (24 HR SERVICE)

AMATEUR RADIO EXCHANGE



SEX BEFORE MARRIAGE

Even in this modern age where nearly anything goes, the vast majority of people still have doubts about the possible implications and complications that may result from such a relationship.

There are many who will argue that before they commit themselves to a lifelong union, they want to know whether or not they are compatible. Such arguments when applied to human relationships have little substance. However, when an amateur commits himself to a new rig, which he hopes to live with for years to come, to have and to cherish, the implications are quite different.

Of course you want to know all about it – to listen to it, to talk to it, to feel how the controls operate, check the specifications on the air against those which have been quoted – and that is exactly what we at Amateur Radio Exchange invite you to do. Both branches now have excellent demonstration facilities where all the popular models can be air tested, and that includes the rig which *you* may decide to buy.

By the time this magazine goes to press the long awaited FT 757GX should be available from stock, but at this moment in time very few people have seen this model let alone tested it. However, we did have an opportunity to operate the receive side at the Friedrichshafen exhibition last June, and undoubtedly the FT 757GX is going to be the world leader in HF transceivers for 1984 at a price of £625.00 including VAT.


For the many people who are interested in Scanning Receivers, there are three new models recently announced.

These are:-

the SX400 made by J.I.L. Japan who are, of course, well known for the very successful and popular SX200N. The new model will cover from 26 to 520 MHz with no gaps and will receive in FM and AM. Priced at over £500.00 this receiver is destined for the professional market.

FUNCTIONS (FRONT VIEW)

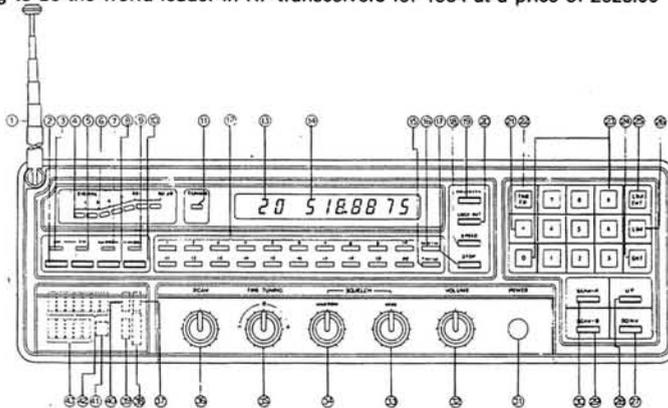1. Telescopic Antenna; 2. AM Switch; 3. AM Indicator Lamp; 4. FM Switch; 5. FM Indicator Lamp; 6. Signal Meter; 7. Narrow Indicator Lamp; 8. Narrow Switch; 9. Wide Indicator Lamp; 10. Wide Switch; 11. Tuning Meter; 12. 20 channel Memory Keys; 13. Memory Channel Display; 14. Frequency Display; 15. Scan Write, Minute Adjustment Key; 16. Memory Write, Hour Adjustment Key; 17. Stop Button; 18. Speed Change Key; 19. Priority Button; 20. Lock out Button; 21. Decimal Point Button; 22. Time & Frequency Selection Key; 23. Keyboard Frequency Selection Keys; 24. Frequency Entry Button; 25. Limit Entry Key; 26. Limit Key (ON/OFF); 27. Down Seek Key; 28. Up Seek Key; 29. Scan B Button; 30. Scan A Button; 31. Power Switch; 32. Volume Control; 33. Squelch Control of WIDE; 34. Squelch Control of NARROW; 35. Fine Tuning Control; 36. Scan Delay Control; 37. Auto Noise Limiter Switch; 38. Change Switch of Squelch Mode; 39. Carrier ON/OFF Switch; 40. Dimmer Control Switch; 41. Set Switch of Channel Space; 42. Change Switch of Channel Space (5 KHz/6.25 KHz); 43. Change Switch of Channel Space (10 KHz/12.5 KHz).



Then there is the new AOR2001. Information on this model has been available for some time – again general coverage between 25 and 555MHz and considered excellent for the amateur market at approximately £300.00.



Last but not least – a brilliant HF receiver from SONY. Most people will know of the SONY ICF2001 – but now they have excelled themselves with this new model, the ICF 7600D.


Size: Only 6" x 4" x 1" approximately.

Frequency coverage: 153KHz - 30MHz + FM, 87.6 - 108 MHz. Double conversion.

Keyboard entry of frequencies and memories.

SSB/CW/AM modes.

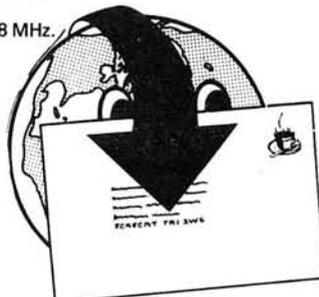Internal batteries and external antenna connections.



Yaesu	Bench
Trio/Kenwood	TET
Icom	Alinco
FDK	Drac
Tono	Bnos
Tasco	Datong
Weltz	Strumbeck
Mutek	Tonno
Adonis	J Beam
Diamond	Microwave Modules

We notice with some satisfaction a comment by another advertiser which refers to our mention of a well known quotation which we attributed to Winston Churchill. We have been corrected by several readers that this quotation was originally made by Phineas T. Barnum, and we have since proved this to be correct from reference books.



373 UXBRIDGE ROAD, ACTON, LONDON W3 9RH
Tel: 01-992 5765/6/7 Just 500 yards east of Ealing
*Common station on the District and Piccadilly Lines
 and 207 bus stops outside.*

Our thanks to Lowe Electronics for pointing out our error too – but Abe Lincoln never said it at all – *BUT* what is more important, however, is that **LOWE ELECTRONICS** read our advertisements.

38 BRIDGE STREET, EARLESTOWN, NEWTON-LE-WILLOWS, MERSEYSIDE (TELEPHONE: 092 52 29881)

Closed Wednesday at Acton and Monday at Earlestown, but use our 24-hour Ansafone service at either shop.



Amcomm

Wishes you a Merry Xmas
with prices to prove it



**YAESU FT980
GENERAL COVERAGE TRANSCEIVER**

Yaesu said the FT1 was an adventure in electronics and we agreed. The FT980 is something quite different... IT'S AN ACCOMPLISHMENT IN ELECTRONICS providing the operator with a brilliantly designed transceiver with a wealth of features. Every feature has been carefully designed in to ensure the operator has MAXIMUM BENEFIT without gimmicks while allowing INCREDIBLE EASE OF OPERATION. We'd need more than this page to do justice to the FT980 so we suggest you call in and try it for yourself or call 01-422 9585 for a beautifully illustrated leaflet with a full description... Yes it is expensive... the best usually is unless a way can be found to ease the pain... AMCOMM ARE EXPERTS AT THAT... TRY US.

THE FM MOBILES

There are many on the market these days and it must be difficult for the buyer to make a decision... DON'T LET IT WORRY YOU for we have exactly the same problem... We've searched the specs, tested the performance and analysed the reliability and our findings are simple... THEY ARE ALL GOOD... some have this and some have that, some are black, some are grey but they all have one thing in common... VALUE FOR MONEY. If you like it and it suits you then it's the one for you... It leaves only one problem... THE PRICE. Our Welsh friends are forever repeating our original copy "HELPING WHERE IT HURTS". We haven't changed, we're still easing the pain... Call 01-422 9585 and stop hurting.

ICOM ICR70 GENERAL COVERAGE RECEIVER

Our ads have said it all year "SILKY SMOOTH APPEARANCE WITH THE SILKY SMOOTH PERFORMANCE". What we did not mention was THE SILKY SMOOTH PRICE... We are still not going to but call 01-422 9585 and you will have yourself a merry christmas for sure at a price you will not refuse. Other receivers available FRG7700, KENWOOD 2000. Call for quote.



DATONG SRB2 and DATONG ANF

From the remarkable man in the north a pair of real SHOW STOPPERS... the SRB2 Auto Blanker for the nasty woodpecker... and it really works... the SRB2 locks on to the woodpecker as it appears and GETS RID OF IT just as fast, QRM GONE... OSO ON. The Automatic Notch Filter is really IMPRESSIVE... if you spend any time on the LF portion of 80mts you need to be a brave man to last the evening... with the ANF you'll lose a lot of sleep but your COUNTRIES SCORE WILL SOAR... You are sure to get one sometime why not now... Call 01-422 9585.

**YAESU 757GX
GENERAL COVERAGE RECEIVER**

The requests for leaflets of this unit has been incredible. Most of you have the information you need to make a decision, however there is one question left to ask, CAN MR. YAESU PRODUCE ENOUGH TO MEET THE DEMAND?... The competition are already in a state of depression... read on... this is the complete HF rig and includes as standard FULL BREAK IN, CW FILTER, KEYS, MARKER, IF/WIDTH SHIFT, NOISE BLANKER, SWITCHABLE AGC and RF PRE AMP... It also has AM and FM fitted. General coverage 150hz-29.999MHz plus TWIN VFO's... Call 01-422 9585 if you require more information and we will give you a Christmas surprise with the price.

Stop Press! Yaesu Lads on Nightshift.

THE HANDHELDS

The recent rise in popularity has kept us in short supply for most of the year, but we hope to have PLENTY IN TIME FOR CHRISTMAS. If you gift wrap it he (or she) will never guess its a transceiver. Imagine THE SHEER JOY on his (or her) face when he (or she) unwraps the neat little package. Whether a YAESU FT208 or FT708 or one of the Icom twins IC2E or IC4E our CHRISTMAS OFFER will delight you. Call 01-422 9585 for immediate despatch.




AMTECH 300B ANTENNA COUPLER

BRITISH MADE and MADE TO LAST... thousands in use throughout the world and priced to suit your pocket. Rated at 300 watts P.E.P. this coupler is suitable for coaxial feed antennas or random wires... just compare the price with anything else available and you'll understand why users say it's SUPER VALUE... at £49.95 including carriage. It really is our STAR BUY... Call 01-422 9585 for fast delivery.



ROTORS

HIRSCHMANN 250... There is no better buy on the market than this... A lightweight Rotor suitable for most VHF antennas... It's yours for £45... Carr and ins. £1.50.

SKYKING SU4000... An outstanding Rotor for large VHF arrays or light HF beams... A delightful illuminated compass readout... NICE ONE AT £85.00 CARR & INS. £1.50.

YAESU FT726R 2m/70cms/SAT

Without a doubt THE RIG OF THE YEAR and a clear indication of YAESU's view of the future of amateur radio (ring us and we will explain that)... It's a bit much to expect one to be in the shack on Christmas morning but we HOPE YOU ARE ONE OF THE LUCKY ONES, because we already have conspired with a few ladies (and one gentleman) to arrange special deliveries on Christmas morning... However, whether you are BUYING or HOPING, give us a nudge and we will ring THE CHRISTMAS BELL for you. 01-422 9585 for BUYERS A SUPER PRICE... for DREAMERS a chat and a leaflet with details.

**YAESU FT290RB 2m
ALL MODE TRANSCEIVER**

The world's BIGGEST AND FASTEST SELLING TRANSCEIVER EVER, still without a competitor in sight. This versatile rig is a REAL XMAS GIFT from AMCOMM to you at a price YOU'LL NEVER SEE AGAIN... You don't believe us? Call 01-422 9585 FOR YOUR XMAS SURPRISE.

N.B. Competitors please call after 6.00 p.m.

THE ICOM NEW ONES

ICOM have been busy little boys this year... THREE NEW ONES all announced at the same time... IC751 GENERAL COVERAGE TRANSCEIVER... IC745 ALSO A GENERAL COVERAGE TRANSCEIVER... The differences are shown in the full illustrated literature which is yours for a phone call... Replacing the IC251E is the NEW IC271, it ticks the part and our first buyers are saying it certainly lives up to the high standards everybody has come to expect from ICOM... 01-422 9585 FOR SUPER PRICE AND SUPER SERVICE.

UNION ELEC. WORLD TIME GLOBE

INSTANT TIME AT HOME AND ABROAD... simply turn the globe to the required country and it displays a red FLASHING LIGHT on that country... Beneath, IT DISPLAYS THE TIME IN THE UK AND THE COUNTRY OF YOUR CHOICE... Long life of batteries guaranteed by automatic switch off after 30 seconds... an IDEAL XMAS GIFT AT AN IDEAL PRICE £47.50 post paid... Call now 01-422 9585 FOR FAST DELIVERY.



YAESU FT102 9 BAND TRANSCEIVER

How does it go again? XMAS COMES BUT ONCE A YEAR AND WHEN IT COMES ITS VERY DEAR... DEFINITELY NOT TRUE THIS YEAR... ESPECIALLY WITH OUR YAESU FT102... DON'T WASTE TIME AND MONEY PHONING AROUND SIMPLY CALL AMCOMM ON 01-422 9585... WE'LL GIVE YOU YOUR BEST XMAS YET AND MANY HAPPY NEW YEARS WITH THIS SUPERB TRANSCEIVER... THE PRICE?... THAT WILL COST YOU A PHONE CALL.

OUR MAIL ORDER SERVICE

The words we hear most frequently are "I REALLY DIDN'T EXPECT IT UNTIL NEXT WEEK". THEY REFER TO OUR MAIL ORDER SERVICE and come both by telephone and letter. When we say "IT WILL GO TODAY" we really mean that, the same day via red label special Securicor or first class post. You have very little to do, refer to the list below, pick up the telephone, quote your credit card number and the product is on the way to you... or drop a cheque in the post and goods will be despatched on receipt. WE PROMISE YOU ONE THING, the very least you'll save is the cost of a telephone call... TET, HYGAIN, YAESU, ICOM, TRIO/KENWOOD, MICROWAVE MODULES, BNOS, DATONG, JAYBEAM, TONNA, MORSE KEYS including HI-MOUND and the SWEDISH BRASS, UNADILLA, SKYKING, HIRSCHMANN, TONO, TASC0, JVC PADDLE, VALVES, WELZ, MUTEK, HANSEN, DAIWA and many more. If you need it we probably have it. If you've got the time we've got the phone lines... We guarantee you'll save more than a phone call and not only at Xmas... All the year round call 01-422 9585 for fast quotes and fast delivery BACKED UP BY FIRST RATE AFTER SALES SERVICE.

E. & O.E.



194 NORTHOLT ROAD, SOUTH HARROW, MIDDX. HA2 0EN. ENGLAND. TEL: 01-864 1166; 01-422 9585. TELEX: 24263

Getting WISE

IT SEEMS THE FASHION that each new year is adopted by various organisations as a means of promoting some aspect of their operations or interests. You may already have noticed announcements about "Women into Science and Engineering" (WISE) year, a joint promotion by the Equal Opportunities Commission (EOC) and the Engineering Council which is to be launched in January and run throughout 1984.

Local education authorities and schools will already have received information packages about WISE, which will consist of a series of co-ordinated projects in schools and colleges throughout the UK, together with initiatives by employers, professional institutions and associations and public bodies. Both the EOC and the Engineering Council are concerned that so few women are employed as scientists and technologists, technicians or in craft occupations in the engineering industry. Currently 94% of all women who work in the industry are employed as operators, clerical staff and in unskilled grades.

The shift in emphasis from heavy to light engineering, much of it radio or electronics based, has undoubtedly helped to arouse a little more interest in engineering as a career for girls, but there is a long way to go. Many schools retain the attitude that it's not quite the done thing for girls to get involved in such things, and many men in the industry look on it as a threat to their future employment. The latter is an understandable reaction, but nevertheless times are

changing, the structure of society is no longer what it was. Without wishing to be caught in the crossfire between "male chauvinist pigs" and "militant feminists", my own feeling is that anyone, male or female, should have an equal opportunity to pursue their chosen interests.

The influx of YLs and XYLs into amateur radio in the last couple of years, though still very small in percentage terms, is evidence of increasing interest in "things technical" on the part of the ladies. Some old hands complain that meetings down at the radio club aren't the same any more, now that the YLs are there all the year round, rather than just for a Christmas social or a summer picnic. Again it's an understandable reaction—those of us who are getting a little longer in the tooth all have things we look back on with thoughts of "It was better in those days". But things change, and we must move with the times or disappear like the prehistoric animals.

Geoff Arnold

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the **Editor, "Practical Wireless", Westover House, West Quay Road, Poole, Dorset BH15 1JG**, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components for our projects are usually available from advertisers. For more difficult items, a source will be suggested in the "Buying Guide" box included in each constructional article.

PROJECT COST

The approximate cost quoted in each constructional article includes the box or case used for the prototype. For some projects the type of case may be critical; if so this will be mentioned in the Buying Guide.

INSURANCE

Turn to the following page for details of the PW Radio Users Insurance Scheme, exclusive to our readers.

CONSTRUCTION RATING

Each constructional project will in future be given a rating, to guide readers as to its complexity:

Beginner

A project that can be tackled by a beginner who is able to identify components and handle a soldering iron fairly competently. Generally this category will be used for simple projects, but sometimes for more complicated ones of wide appeal. In this case, construction and wiring will be dealt with in some detail.

Intermediate

A project likely to appeal to a wide range of constructors, and requiring only basic test equipment to complete any tests and adjustments. A fair degree of experience in building electronic or radio projects is assumed.

Advanced

A project likely to appeal to an experienced constructor, and often requiring access to workshop facilities and test equipment for construction, testing and alignment. Constructional information will generally be limited to the more critical aspects of the project. Definitely not recommended for a beginner to tackle on his own.

SUBSCRIPTIONS

Subscriptions are available at £13 per annum to UK addresses and £14 overseas, from "**Practical Wireless**" **Subscription Department, Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS**. Airmail rates for overseas subscriptions can be quoted on request.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at £1 each, including post and packing to addresses at home and overseas.

Binders are available (Price £5.50 to UK addresses, £5.75 overseas, including post and packing) each accommodating one volume of *PW*. Please state the year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF**. All prices include VAT where appropriate.

Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

PW RADIO USERS INSURANCE SCHEME



Practical Wireless Radio Users Insurance Scheme was devised by Registered Insurance Brokers B. A. LAYMOND & PARTNERS LIMITED following consultation with PRACTICAL WIRELESS to formulate an exclusive scheme designed to meet the needs and requirements of: Amateur Radio Enthusiasts ● CB Radio Users ● Taxi Companies and Fleet Users with Radio Telephones. A copy of the Policy can be inspected at the offices of B. A. Laymond & Partners Ltd., or of Practical Wireless in Poole.



SPECIAL FEATURES

- All Risks Cover ● "New Lamps for Old" Cover (as defined in policy) ● Index Linked Cover to combat inflation ● Includes Personal Liability cover against damages payments of up to £500000 to members of the public ● Licence protection—covers legal costs arising from any breach of your licence conditions ● Equipment covered anywhere in the UK, Channel Islands and Isle of Man, but not Northern Ireland and Eire ● Fixed Antennas (Aerials) covered ● Frequency, Power and SWR Meters and similar radio-related test equipment covered ● 30 days cover on Western Europe included Free of Charge ● Absolute Security as this scheme is underwritten by a leading member of the British Insurance Association on the London Insurance Market ● Practical Wireless radio receiver and transmitter projects covered (when stated in feature) ● Available to Clubs and Organisations† ● Available to Companies†

†Write directly to B. A. LAYMOND & PARTNERS LTD, for a special application form and full details enclosing the coupon below.

B. A. Laymond & Partners Ltd., Practical Wireless and the Underwriters wish to make it clear that it is an offence to instal or use a radio transmitter in the UK except under the authority of a licence granted by the Secretary of State and it is not their intention to provide cover for or to encourage or condone the illegal use of CB and/or other communications equipment.

Cover for property contained in vehicles is subject to a Limit of Liability of £250, increased to £750 where the vehicle is protected by a reputable audible alarm, correctly set and operational.

When the vehicle is unattended, mobile equipment secured so that tools or a key are required to remove it must be disguised or concealed from view. Portable and mobile equipment not so secured must be removed and placed in a locked boot or otherwise concealed from view, or removed from the vehicle entirely. Equipment not in a secure building or vehicle must not be left unattended.

How Much Will It Cost?

Claims will be settled after deduction of an excess in the following manner:

Sum to Insure	£1000	£3000	£5000
Annual Premium	£20	£35	£45

Type of Loss	Excess
From saloon cars and hatchbacks with fully concealed luggage compartments	15% of claim (minimum £25)
From estate cars, vans and hatchbacks without concealed luggage compartments	25% of claim (minimum £25)
All others:	Sums insured up to £3000 Sums insured up to £5000
	£25 £50

The premium is charged on sums insured in pre-selected bands. Thus equipment totalling £3750 would be in the band up to £5000, and the premium would be £45. Quotations for larger sums available on application.

How To Insure

Complete the application form below to obtain immediate insurance cover. Photocopies will not be accepted

APPLICATION FOR PRACTICAL WIRELESS RADIO USERS INSURANCE SCHEME						PW1/84
Name in full (State Mr, Mrs, Miss or Title)						
Address						
						Post Code
Occupation		Age		Phone No. (Home)		(Work)
I/We hereby apply to insure the equipment detailed below						
BLOCK LETTERS	Manufacturer's Name	Model	Serial No.	Description of equipment to be insured e.g. Base station; Mobile; CB; etc.	VALUE £	
	1					
	2					
	3	Antennas (Aerials), s.w.r. meters, etc.				
Please continue list of equipment on a separate sheet if necessary						TOTAL SUM TO INSURE £
<p>DECLARATION: I/We hereby declare that: 1. The sums insured represent the full replacement value of the equipment. 2. I/We have not* had insurance cancelled, declined, restricted, or other terms imposed in any way other than the normal Policy terms. 3. This proposal shall be the basis of the contract and that the contract will be on the Underwriters normal terms and conditions for All Risks and Legal Costs/Expenses cover unless otherwise agreed. 4. I/We have not* sustained any loss or damage to any radio communications equipment or been involved in litigation relating to use of radio equipment during the past three years, whether insured or not. 5. All the above statements made in connection with this proposal are true and no material information has been withheld. 6. I/We understand no liability shall attach until this proposal shall have been accepted by Laymond's and the premium paid in full and a Certificate issued.</p> <p style="text-align: right;">* If you have, please give details on a separate sheet.</p>						
Date		Signed			Rush us details of PW Club Insurance <input type="checkbox"/> PW Company Insurance <input type="checkbox"/>	
<p>DELAY IN ARRANGING COVER COULD COST YOU A GREAT DEAL OF MONEY. COMPLETE THIS APPLICATION AND POST WITH YOUR PREMIUM MADE PAYABLE TO "LAYMOND'S" NOW. ADDRESS TO: PRACTICAL WIRELESS (INSURANCE), B. A. LAYMOND & PARTNERS LTD., 562 NORTH CIRCULAR ROAD, LONDON NW2 7QZ. TELEPHONE: 01-452 6611.</p>						


144 MHz (2m) REPEATERS IN IRELAND

During the preparation of the 2m Datacard, which was published in the March 1983 edition of *PW*, it became apparent that significant v.h.f. repeater developments were under way in the Irish Republic. As the channel allocations were known to be under review full details were not published.

However, at a meeting of the EI Repeater Co-ordinating Group held on 2nd October 1983, revisions

were agreed to permit maximum coverage for mobile units from the relatively few experimental devices, at the same time minimising potential co-channel interference problems. The map produced here contains all known details and *should* represent the situation as of November 1983, both in EI and GI.

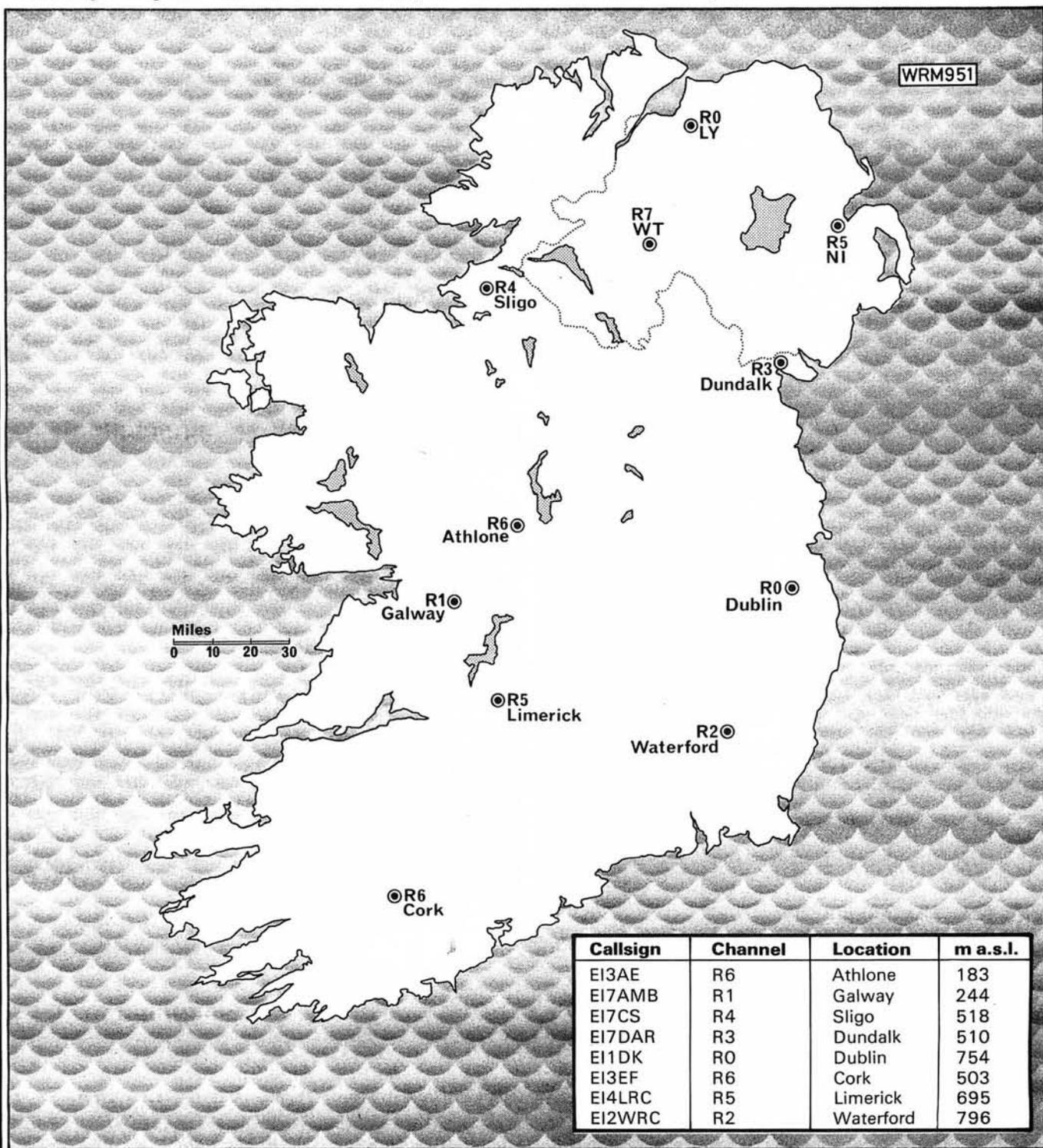Our thanks for the supply of this information go to Dr. T. S. Rea MRCGP, EI7AMB.



HF ANTENNA SPECIAL

Steerable HF Antenna

F. E. WYER G8RY

The antenna system to be described in this article could well be the solution for those unable to erect a steerable h.f. beam antenna and who, like the author, prefer working at ground level!

The basic principle of operation relies upon the phase effect obtained by the insertion of a $\lambda/4$ delay section between two radiating elements. By using three separate elements pitched in a triangle and arranging for the phase shifting element location to be varied from the operating position a six-way "end fire" directional beam effect is obtained.

In practice the antenna array consists of three identical $\lambda/4$ ground plane elements, which are individually gamma matched, feeding back via identical lengths of cable to a multi-pole wafer switch. The phasing section consists of an electrical $\lambda/4$ of feeder that is introduced between the appropriate selected pair of elements.

The cardinal lobe is approximately 60 degrees wide at the -3dB points therefore with three elements available it is possible to cover a full 360 degree sweep without the need for an expensive rotator system. Experimental measurements indicate a forward gain of 4.5dB over a single free space vertical. High attenuation of side and rear lobes is also evident.

To improve the system efficiency a network of buried wire radial elements are employed. This has the added incidental advantage of providing an excellent earthing arrangement. Because the bases of the $\lambda/4$ radiating elements are directly grounded this allows a substantial mechanical anchorage to be achieved together with ground level access for adjustments.

The schematic and constructional details provided in Figs. 1-3 indicate the general dimensions used by the author for operation on 21.3MHz (15m), however scaling of the $\lambda/4$ sections will allow systems to be developed for other h.f. bands such as 14MHz (20m).

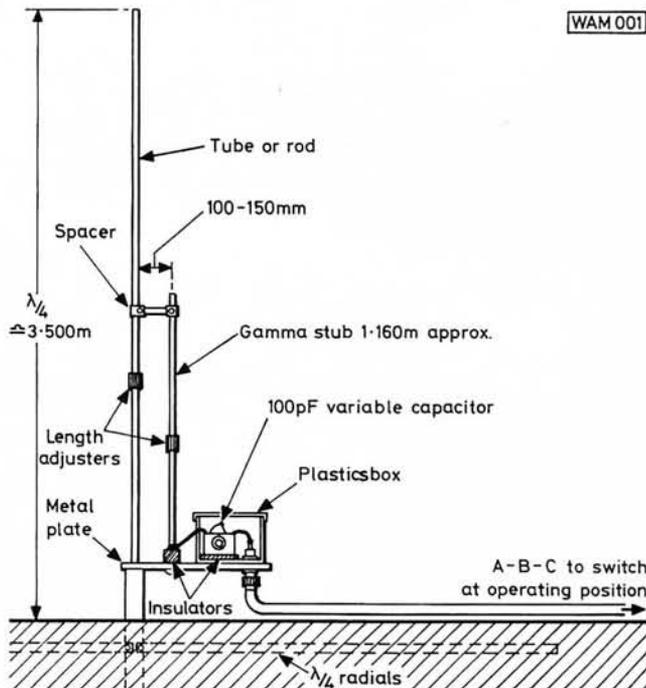
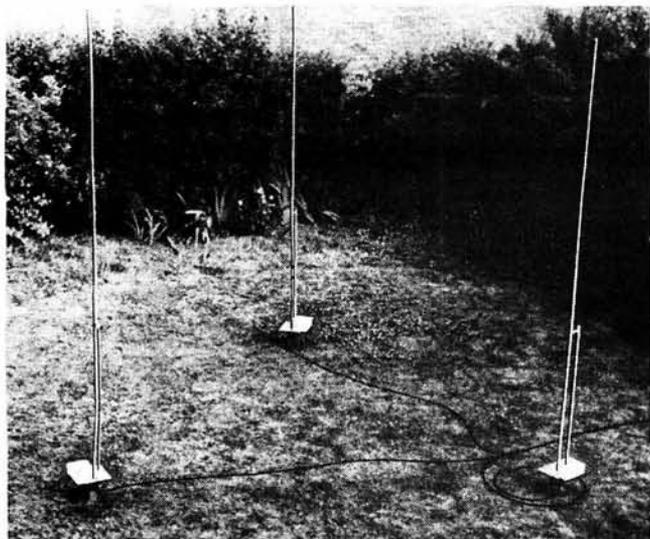


Fig. 1: Constructional details of the $\lambda/4$ gamma matched 21MHz radiating elements. The plastics box used by the author was a 2 litre ice cream container

When constructed the setting-up procedure consists of applying low power, at the frequency of interest, via an s.w.r. bridge to each individual radiating element. In the author's case 21.3MHz was selected and a long twin

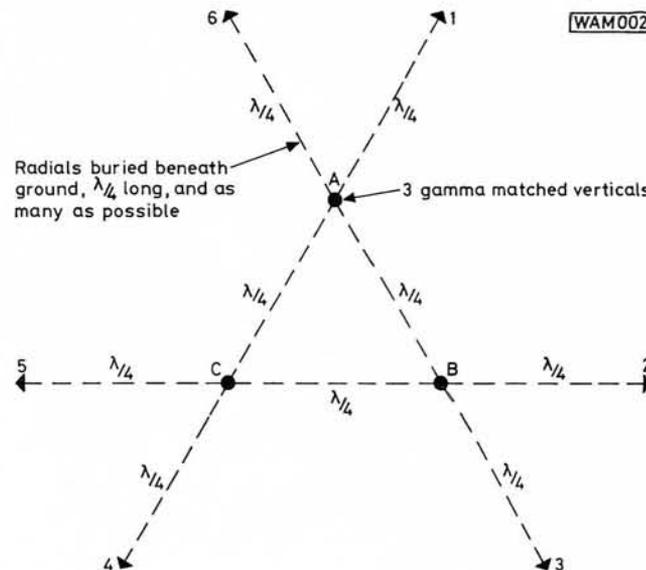


Fig. 2: Plan view of the system. The vertical elements are spaced $\lambda/4$ apart at the operating frequency

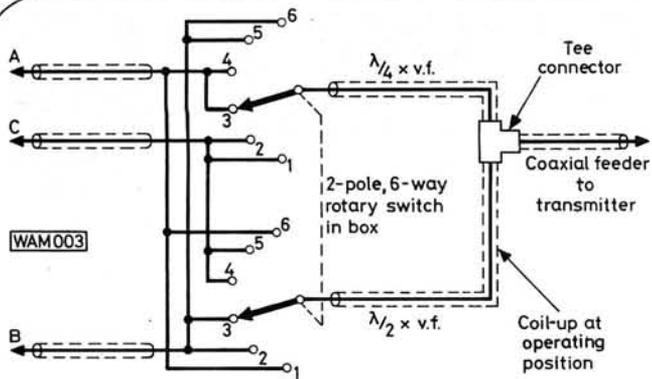


Fig. 3: Direction switching arrangements. Allowance must be made for cable velocity factor (v.f.)

feeder provided to connect a Morse key to the shack mounted transceiver. The s.w.r. bridge was located at the

base of the $\lambda/4$ element and resonance achieved by adjustments to the length of the gamma rod and capacitor element. Using this remotely keyed arrangement allows rapid tune up. Having set all three radiating elements a second check of matching should be made as there are some slight interaction effects.

The three feeders must be of equal length and ideally composed of an even number of $\lambda/4$ lengths, although this is not critical. At the shack end of the feeder runs a six-way wafer switch is used to select the desired beam heading. This switch can also be fitted with a further wafer section to provide a visual display indication of heading adjacent to the transceiver position. The transceiver should also be earthed (independently of the house mains supply earth) to a suitable earth stake, following normal practice.

The Vertical V Antenna

E. J. PESTELL G3BPB

Most amateurs are familiar with the properties of the inverted Vee h.f. antenna. The inverted Vee is simple and inexpensive to construct, provides a good match to 50 ohm coaxial cable and produces a quasi-omni directional

horizontally polarised radiation pattern when used at its fundamental frequency. An introductory chapter on antennas by Kraus¹ points out in a generic sense that a cylindrical vertical Vee can be expected to yield a broader

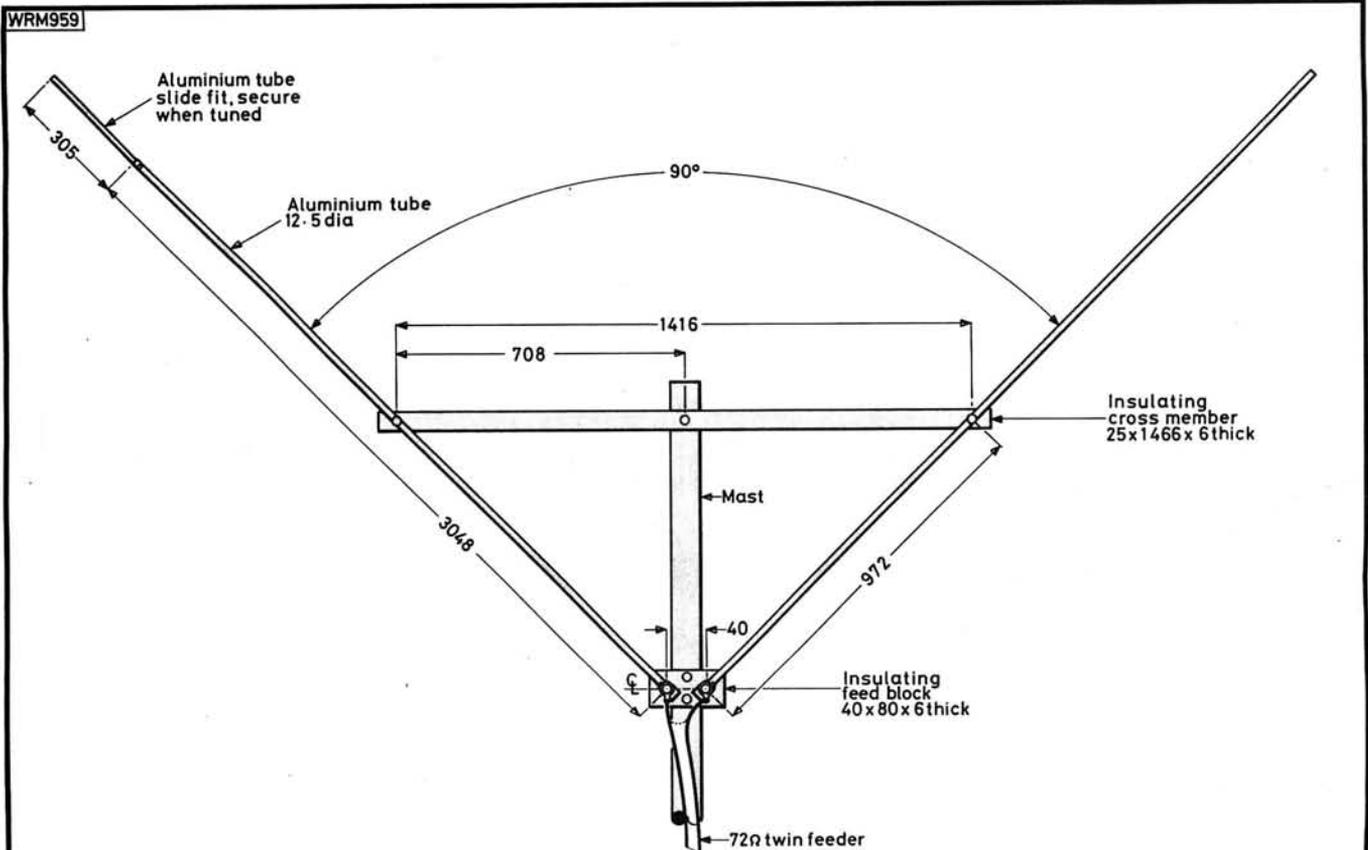


Fig. 1: Constructional details of the Vertical V antenna for 21MHz. Both radiating elements are provided with length adjustment and for best results a 1:1 balun should be fitted at the feedpoint when using 50 ohm coaxial cable. Note that this drawing is not to scale

usable bandwidth than the corresponding dipole. So it appears that a vertical Vee offers the potential for significantly improved performance over the common types of antennas. It is surprising that this type of radiator has not been described in the antenna manuals currently on sale.

The inverted Vee whilst providing excellent performance does suffer from deficiencies, such as ground effect and influence of feed point impedance if supported by a metal mast. Since the antenna is centre-fed the balanced currents may be induced on the transmission line even if a balun is used at the feed point. Finally, sloping the elements downwards to make the inverted Vee increases the likelihood of parasitic losses in nearby grounded objects. A vertical Vee would be much less affected by the above factors.

In addition a vertical Vee provides the further advantage of increased antenna height and simple construction as only one central support is required when self-supporting aluminium elements are used. It also has the capability of being rotated. Equipped with the above facts and informative constructional data supplied by VE3QE, the author decided to "have a go" at constructing such an antenna.

Time taken for construction was about 4 hours and the approximate cost was £8-£9. Tests were then arranged with VE3QE with the initial contact being made on

21MHz using a dipole orientated NW-SE. After communication was established the vertical Vee was substituted for the dipole and an identical report was received from Canada.

It should be noted that for this test the inverted Vee was at **ground level**. Half an hour later, after dismantling the dipole from a 4.5m mast and substituting the inverted Vee, putting it about 5m above ground, a further contact was made with the surprising report of two full "S" points increase in signal strength. Contacts were later established with RSARS members in Hong Kong, Sydney, Brisbane, Adelaide, Alice Springs, Norway, PA0, New York, Alberta, New Brunswick, plus other contacts with VE9, VK7, 8P6 and PY. Later tests, rotating the Vee, proved the antenna to have a fair degree of directional properties. Tests have now been carried out over a period of over 12 months with consistent reports. It is hoped that this short article will help readers to construct a cheap and reliable antenna. Tests have shown that feeding the antenna with 72 ohm twin feeder is better than using coaxial cable.

The author would like to thank VE3QE for the help and perseverance given during these tests. It is further hoped that our next project will be a trapped vertical Vee for the 28, 21 and 14MHz bands. ●

¹ *Antennas*. J.D. Kraus. McGraw-Hill USA

News

ARRA at Doncaster

The twelfth annual National Amateur Radio and Electronics Exhibition organised by the Amateur Radio Retailers Association (ARRA) was held in the Exhibition Centre at Doncaster Racecourse, from 6-8 October.



This is a new venue for the show, traditionally held at the Granby Halls in Leicester, and it proved to be very pleasant for visitors and exhibitors, with plenty of room to move about and good catering facilities. It was our pleasure on the *PW* stand (our first time at an ARRA event) to chat to many of our readers, and to show off some recent projects.

It is perhaps a sign of the times that attendance on the two weekdays, and particularly the Friday, was quite well



down. People with jobs can often get to exhibitions only at weekends; people who are unemployed probably can't afford to travel any great distance. So the organisers are in a dilemma as to the best days to hold the show. Let's hope next year will see an improvement in the economic situation for us all.

Scopex Instruments

Since a Receiver has been appointed for Scopex Instruments Ltd., readers who own one of their instruments may be interested to learn of a company offering to repair these products.

The company, Mendascope Ltd., have specialist knowledge of Scopex instruments and can provide a unique service which includes collection and a free estimate.

Lowe's Expanding

Lowe Electronics, the Matlock based Trio main agents, are soon to open yet another branch in Cardiff, Gwent.

The new shop will join their existing branches in London, Glasgow and Darlington.

For further information contact: *Lowe Electronics, Chesterfield Road, Matlock, Derbyshire DE4 5LE. Tel: (0629) 2817/2430/4057 and 4995.*

Armon Multimeters

Readers should note that prices quoted in Armon Electronics advertisements in recent issues of *PW* did not include VAT. Prices in this issue are VAT-inclusive.

Further details from: *Mendascope Ltd., Otter House, Weston Underwood, Olney, Bucks MK46 5JS. Tel: Bedford (0234) 712445.*

More on pages 63 & 64

Practical Wireless, January 1984

REG. WARD & CO. LTD.

AXMINSTER, DEVON

RODNEY G6LUJ

REG G2BSW

THE SOUTH-WEST'S LARGEST AMATEUR RADIO STOCKIST

YAESU		£	c&p	ICOM		£	c&p	STATION ACCESSORIES		£	c&p
FT1	HF Transceiver	P.O.A.	(-)	IC720	HF Transceiver	P.O.A.	(-)	POWER SUPPLIES			
FT980	HF Transceiver	P.O.A.	(-)	IC751	HF Transceiver	969.00	(-)	DRAE			
SP980	Speaker	54.80	(2.00)	IC745	HF Transceiver	769.00	(-)	4 amp 30.75 (2.00)			
FT102	HF Transceiver	685.00	(-)	IC730	Mobile HF Transceiver	P.O.A.	(-)	6 amp 49.00 (2.50)			
FC102	Tuner	200.00	(2.00)	PS15	P.S. Unit	119.00	(4.00)	12 amp 74.00 (3.00)			
FV102DM	VFO	230.00	(2.00)	IC290H	2m 25w M/Mode	433.00	(-)	24 amp 105.00 (4.00)			
SP102	Speaker	49.05	(2.00)	IC271E	2m 25w M/Mode Base Str.	569.00	(-)	BNOS			
AM/FM	Unit	46.00	(1.00)	IC25H	2m 45w FM	269.00	(-)	6 amp 48.30 (2.50)			
FT77	Mobile HF Transceiver	459.00	(-)	IC45E	70c 10w FM	289.00	(-)	12 amp 86.40 (3.00)			
FP700	PSU	110.00	(5.00)	ICBU1	B/U Supply for 25/45/290	20.00	(1.00)	24 amp 125.00 (4.00)			
FC700	Tuner	85.00	(2.00)	IC2E	2m H/Held	179.00	(-)	40 amp 225.00 (4.00)			
FT77s	10w. version	399.00	(-)	ML1	2m 10w Linear	64.00	(2.00)	DUMMY LOADS			
FMU77	FM Board for FT77	25.30	(1.00)	IC4E	70cm H/Held	199.00	(-)	TOYO			
FT757	HF Transceiver	P.O.A.	(-)	BC30	Base Charger	49.00	(-)	30w 6.61 (0.50)			
FT480	2m M/Mode Transceiver	399.00	(-)	HM9	Speaker mic	15.00	(0.75)	100w 20.12 (1.00)			
FL2050	Linear Amplifier	115.00	(2.00)	IC3	Carry Base	4.25	(0.75)	200w 31.36 (2.50)			
FT290	2m M/Mode Port/Transceiver	249.00	(-)	ICBP3	Std Battery Pack	23.00	(0.75)	WELZ			
FL2010	Linear Amplifier	59.00	(1.00)	BP5	High Power Battery Pack	44.00	(0.75)	300w 49.50 (2.00)			
FT790	70cm M/Mode Port/Transceiver	299.00	(-)	CP1	Car Charging Lead	4.49	(0.75)	CW/RTTY EQUIPMENT			
FL7010	Linear Amplifier	91.00	(1.00)	DC1	12v Adaptor	11.99	(0.75)	Tono 9000E Reader/Sender 669.00 (-)			
MMB11	Mobile Bracket	24.90	(1.00)	LINEAR AMPS				Telereader CWR610E 189.00 (2.00)			
NC11	Charger	9.20	(0.75)	TOKYO HY POWER				MICROWAVE MODULES			
CSC1	Carrying Case	3.85	(0.75)	HL 32V	2m 30W (1-5W drive)	53.50	(1.50)	MML144/30-LS inc preamp (1/3 w i/p) 69.95 (2.00)			
YHA15	2m Helical	5.00	(0.75)	HL 82V	2m inc preamp (2-12W in 35-85 + out)	144.50	(2.00)	MML144/50-S inc preamp, switchable 92.00 (2.00)			
YHA44D	70cm jwvave	8.25	(0.75)	HL 160V	2m inc preamp (1-10W in 160W + out)	242.40	(2.00)	ML144/100-S inc preamp (10w i/p) 149.95 (2.50)			
YM4A	Speaker Mike	16.85	(1.00)	HL 45U	70cm inc preamp (2-15W in 10-45W out)	119.75	(2.00)	MML144/100-HS inc preamp (25w i/p) 149.95 (2.50)			
FT230	2m 25w FM	239.00	(-)	B.N.O.S.				MML144/100-LS inc preamp (1/3w i/p) 169.95 (2.50)			
FT730	70cm 10w. FM	259.00	(-)	LPM 144/3-100	(3 watt input) inc preamp	172.50	(2.00)	MML432/30L inc preamp (1/3w i/p) 129.95 (2.00)			
MMB15	Mobile Bracket	11.90	(1.00)	LPM 144/10-100	(10 watt input) inc preamp	149.50	(2.00)	MML432/50 inc preamp (10w i/p) 129.95 (2.00)			
FT208	2m H/Held	199.00	(-)	LPM 144/125-100	(25 watt input) inc preamp	189.50	(2.00)	MML432/100 linear (10w i/p) 245.00 (2.50)			
FT708	70cm H/Held	209.00	(-)	TONO				SWR/PWR METERS			
MMB10	Mobile Bracket	6.90	(0.75)	MR 100	2m (10w in 90w out) inc preamp	129.00	(2.00)	HANSEN			
NC9C	Charger	8.00	(0.75)	MR 150	2m (10w in 120w out) inc preamp	169.00	(2.00)	FS200 1.8-150MHz 20/200 Pep 50.60 (1.00)			
NC8	Base/Station Charger	50.60	(2.00)	DATONG PRODUCTS				FS210 1.8-150MHz 20/200 Auto SWR 55.20 (1.00)			
PA3	Car Adaptor/Charger	14.20	(0.75)	PC1	Gen. Cov. Con.	137.40	(1.00)	FS5E 3.5-150MHz 20/200/1000W HF 37.20 (1.00)			
FNB2	Spare Battery Pack	19.95	(0.75)	VLF	Very low frequency conv.	29.90	(1.00)	FS500H 1.8-80MHz 20/200/2000W Pep 69.75 (1.00)			
YM24A	Speaker Mike	18.40	(1.00)	FL2	Multi-mode audio filter	89.70	(1.00)	FS7 145 & 432MHz 5/20/200 41.00 (1.00)			
FT276R	2m Base Station	675.00	(-)	FL3	Audio filter for receivers	129.00	(1.00)	FS710H 1.8-60MHz 15/150/1500W Pep 89.70 (1.00)			
430/726	70cm Module for above	230.00	(2.50)	ASP/B	r.f. speech clipper for Trio	82.80	(1.00)	FS711U 430-440MHz 5/20W Head 36.80 (1.00)			
FRG7700	HF Receiver 15-30MHz	335.00	(-)	ASP/A	r.f. speech clipper for Yaesu	82.80	(1.00)	PF711H 2-30MHz 20/200 W Head 36.80 (1.00)			
FRG7700M	As above with memory	385.00	(-)	ASP	As above with 8 pin conn	89.70	(1.00)	WELZ			
FRT7700	A.T.U. for above	42.55	(1.00)	D75	Manual RF speech clipper	56.35	(1.00)	SP15 1.8-160MHz PWR/SWR 37.00 (1.00)			
FRA7700	Active Aerial for above	38.70	(1.00)	D70	Morse Tutor	56.35	(1.00)	SP45 130-470MHz PWR/SWR 51.00 (1.00)			
FRV7700A	Converter 118-150MHz	78.95	(2.00)	MK	Keyboard morse sender	137.40	(1.00)	SP10X 1.8-150MHz PWR/SWR 24.45 (1.00)			
FRV7700B	Converter 50-60MHz & 118-150MHz	84.70	(2.00)	RFA	RF switched pre-amp	33.90	(1.00)	SP200 1.8-160MHz PWR/SWR 69.96 (1.00)			
FRV7700C	Converter 147-170MHz	74.75	(2.00)	AD270-MPU	Active dipole with mains p.s.u.	51.75	(2.00)	SP250 1.8-60MHz PWR/SWR 49.50 (1.00)			
FRV7700D	Converter 70-80MHz & 118-150MHz	80.90	(2.00)	AD370-MPU	Active dipole with mains p.s.u.	69.00	(2.00)	SP300 1.8-500MHz PWR/SWR 97.00 (1.00)			
MH188	Hand 600 8pin mic	13.80	(1.00)	MPU	Mains power unit	6.90	(1.00)	SP350 1.8-500MHz PWR/SWR 59.95 (1.00)			
MD188	Desk 600 8pin mic	49.85	(1.00)	DC144/28	2m converter	39.67	(1.00)	SP400 130-500MHz PWR/SWR 69.95 (1.00)			
FSP 1	8ohm Speaker	11.15	(1.00)	PTS1	Tone squelch unit	46.00	(1.00)	SP600 1.8-500MHz PWR/SWR 97.00 (1.00)			
YH77	Lightweight phones	9.95	(0.75)	ANF	Automatic notch filter	67.85	(1.00)	TOYO			
YH55	Padded phones	9.95	(0.75)	SRB2	Auto Woodpecker blanker	86.25	(1.00)	T430 144/432 120 W 35.00 (1.00)			
YH1	L/weight Mobile H/set-Boom mic	13.80	(0.75)	REG G2BSW				T435 144/432 200 W 39.10 (1.00)			
SB1	PTT Switch Box 208/708	14.95	(0.75)	GEORGE STREET, AXMINSTER, DEVON EX13 5DP				YAESU			
SB2	PTT Switch Box 290/790	12.65	(0.75)	Telephone (0297) 33163/34912				YS200 1.8 60MHz 52.90 (1.00)			
QTR24D	World Time Clock	31.45	(0.75)	OPEN MON-FRIDAY 9:00-5:30. SATURDAY 9:00-5:00. WED (9:00-1:00)				YS2000 1.8 60MHz 69.79 (1.00)			
FF501DX	Low Pass Filter	25.70	(0.75)	STOCK ITEMS NORMALLY DESPATCHED WITHIN 48 HOURS				STATION ACCESSORIES			
YP150	Wattmeter/Dummy Load 150w	92.00	(1.00)	ICOM				POWER SUPPLIES			
DATONG PRODUCTS											
AERIAL ROTATORS											
MUTEK PRODUCTS											
AERIALS BY JAYBEAM, HYGAIN, G. WHIP, TET, MINIBEAM USUALLY IN STOCK											
Mail/Telephone order by Cheque or Credit Card											
Instant credit also available											
Delivery prices shown in brackets.											



GEORGE STREET, AXMINSTER, DEVON EX13 5DP

Telephone (0297) 33163/34912

OPEN MON-FRIDAY 9:00-5:30. SATURDAY 9:00-5:00. WED (9:00-1:00)

STOCK ITEMS NORMALLY DESPATCHED WITHIN 48 HOURS



Delivery prices shown in brackets.



GAREX (G3ZV1)

RESISTOR KITS a top-selling line for many years. E12 series, 5% carbon film, 10Ω to 1M, 61 values, ratings 1/4W or 1/2W (state which).

Starter packs 5 each value (305 pieces) **£3.10**

Standard pack 10 each value (610 pieces) **£5.55**

Mixed pack, 5 each 1/4W + 1/2W (610 pieces) **£5.55**

Giant pack, 25 each value (1525 pieces) **£13.60**

SR-9 MONITOR RECEIVER 2m FM with 144-146MHz full coverage VFO + 11 xtal controlled channels; ideal for fixed/M/P use. 12V DC operation **£47.50**. Mains adaptor **£9.50**

CRYSTALS FOR NR-56, SR-9, SR-11, HF-12, TM-56B All 2m channels from 0 (145.00) to 33 (145.825) incl. also 144.80, 144.825, 144.85 Raynet at **£2.60** (+ 20p post per order). Over 40 popular marine channels for SR-9, etc at **£3.00** (+ 20p post).

PYE RADIOTELEPHONE SPARES (see full list). Ex. equip., fully guaranteed. **CAMBRIDGE AM10** 10.7MHz I.F. **£3.65**. 2nd mixer **£3**. 455KHz block filter 12½KHz **£9.40**. Ditto 25KHz **£3**. 455KHz AM I.F. **£4.95**. Audio bd. **£1.95**. Aerial relays **£1.50**.

WESTMINSTER W15/W30 AM RX RF 68-88MHz or 148/174MHz **£6.95**. 10.7MHz IF (inc. 12½KHz xtal filter) **£8.25**. 2nd Osc **£2.10**. 455KHz IF **£5.65**. 455KHz block filter (12½KHz) **£7.35**. Squeelch **£1.45**.

SCOOP PURCHASE
OF BRAND NEW PYE
WESTMINSTER & PF70
SERIES SPARES s.a.e. list

GARDEX FM DETECTOR & squelch conversion for Pye R/T equipment. Ready assembled, full instructions. Tailor-made, easy-fit design, replaces existing squelch board, with minimum of modifications. For AM Cambridge **£6.30**; for Vanguard AM25B (Valve RX) **£6.10**; for Transistor Vanguard AM25T **£6.95**.

★ REVCON ★

A superb quality 16-element, all British made, VHF/UHF broadband fixed station aerial from Revco. Ideally suited to SX200 and other VHF/UHF receivers. Covers 50 to 500 MHz. **PRICE £24.95 inc.**

MAIN DISTRIBUTOR OF REVCO PRODUCTS
PRICES INCLUDE UK POST & PACKING & 15% VAT.



GAREX ELECTRONICS

7 NORVIC ROAD, MARSWORTH, TRING, HERTS HP23 4LS.
Phone 0296 668684. Callers by appointment only.

Goods normally despatched by return



SX200-N THE SUPERIOR SCANNER



- ★ THE CHOICE OF THE PROFESSIONALS
- ★ MICROPROCESSOR CONTROLLED 32,000 CHANNELS
- ★ AM & FM ALL BANDS
- ★ WIDER COVERAGE: 26-58, 58-88, 108-180, 380-514MHz; includes 10m, 6m, 4m, 2m, & 70cm Amateur bands.
- ★ 5KHz & 12½KHz FREQUENCY INCREMENTS
- ★ 16 MEMORY CHANNELS WITH DIRECT ACCESS
- ★ SPECIALLY DESIGNED FOR EUROPEAN MARKET
- ★ 2 SPEED SCAN SCAN DELAY CONTROL
- ★ 2 SPEED SEARCH UP AND DOWN
- ★ SEARCH BETWEEN PRESET LIMITS UP AND DOWN
- ★ 3 SQUELCH MODES inc. CARRIER & AUDIO
- ★ RELAY OUTPUT FOR Aux. CONTROL
- ★ INTERNAL SPEAKER, ALSO EXTERNAL SPEAKER & TAPE OUTPUTS
- ★ LARGE GREEN DIGITRON DISPLAY BRIGHT/DIM
- ★ AM-PM CLOCK DISPLAY
- ★ 12V DC 230V AC OPERATION
- ★ FACTORY BACKED SPARES & SERVICE, 12 MONTH WARRANTY & THE ALL-IMPORTANT PRE-DELIVERY CHECK BY GAREX. THE MAIN SERVICE & SALES AGENTS.

£299 INC. VAT Delivered

EXCITING NEW RANGE
OF SCANNERS AVAILABLE
SOON INCLUDING THE SX-400
s.a.e. for details

THE ENFIELD EMPORIUM

WE STOCK

THE FULL RANGE OF

EQUIPMENT AND ACCESSORIES

ANTENNAS

ASSP · Jaybeam · Tonna
Cue Dee

ROTATORS

Kenpro · Diawa
Hirschmann

ADONIS

Boom microphones
available for
TR2500 - IC2E -
Yaesu 208/708

TONO

Linears - RTTY
Decoders - Morse
Decoders - Full
range available

Full range of

WELZ · YAESU · FDK

Secondhand Equipment

We always have a large selection of secondhand equipment in stock. Please phone for details.

PART EXCHANGES WELCOME

Slim Jim - Only £7.50 inc. p+p.

Stamped Addressed Envelope for brochure etc.

All prices include VAT. Goods normally despatched by return, but please allow up to 7 days.

281 HERTFORD ROAD, EDMONTON N9.

Telephone (01) 804 0128



Buses 249, 279 and 149 stop outside the door.

Opening hours: Mon-Thur 9-6; Fri 9-8; Sat 9-6 AND NOW Sun 9-1




ARMY AERIAL KITS comprising 10×3ft screw sections 1" dia plus adaptor to take 16ft whip aerial this give a 46ft vertical with insulator at base, supplied with ground spike, base insulator, 3×4 sets of guys with chain link insulators, ground pegs & spares, two 16ft whips 4 section are supplied in 4ft steel transit tube this also serves as a mast to take a 16ft whip with adaptor supplied, mast sections etc are supplied in canvas carrying case, new cond. **£46**, also Mast & fittings only **£32**. Whips & fittings **£16**. **CAR C.B. TYPE AERIALS** for use on 27/27.5Mc/s these use flex rubber aerial element with removable base loading coil, aerial approx 15" high, supplied with 11ft RG58 with plug, good quality unit, new unused **£4.50**, spare Ae section with coil **£1.50**. Also available VHF Car Aes see list. **F.M. TUNER HEAD** 88/108Mc/s reqs 12v 10.7Mc/s IF new **£4.75**. **MORSE KEYS** miniature for use with A510 new **£3.50**. **AERIAL FEEDERS** twin 75 ohm with dipole center approx 15mts new 2 for **£2.50**. **VALVE KITS** with CV types 6BA6×5, 6BE6×2, EF91×4, EB91×3, EL91 **£10**. **RADIOSONDE UNITS MK.II** works on 27Mc/s transmits in turn audio tones from 3 sensors, Press, Temp & RH with chart & circ reqs 90/2v new cond **£7.50**. **ARMY RADIO** No. 31 old manpack set covers 40/48Mc/s in 200Kc steps, Tx Rx FM reqs ext dry batts with book **£24.50**. **R.F. TUNING ASS** tunes 1.2 to 19Mc/s in 4 bands supplied with swt & 2 gang 350pf tuning conds, okay for Rx ATU **£7.50**. **ARMY RECT** No. 7 200/250v mains or 12v DC I/P gives 80v-0-80v 30Mz, 12v 300Ma DC etc, will also work off 12v DC to give 240v AC O/P about 40 watts in wood case size 7×9×7" with circ. **£8.50**. **CONTROL BOXES** aircraft radio/Nav types with meters, swts, pots etc. 3 different for **£6.50**. **AERIAL ROTATOR UNIT** aircraft radio compass drive for use on 24v DC approx ext size 7×6×6" shaft supplied with 360 Deg bearing lnd 3½" sq. **£28** the pair. **PORTABLE LIGHT UNIT** contained in case size 9×5×3" with hinged lid as two pen lights on 1 mt leads reqs 2× SP2 batts, with spare bulbs new **£4.50** ea, 2 for **£8**. **HEAD & MIKE SET** Modern style with boom mike and padded phones, finished in grey, nom imp 100 ohm phs & 600 ohms mike **£12.50**. **COAX CABLE** Type UR57 HD 75 ohm 10 mm osd new **£4.50** for 10 Mts 30p mt over this. **H.F. Rx Type R4187** provides up to 24 crystal controlled chan in range 2.8 to 18Mc/s (reqs Hc6/u crystals) supplied with control box, reqs 24/19v DC with book **£35**. **ARMY TYPE L556** HF SSB Tx 2/16 megs see list.

Above prices include carr/postage & VAT.

Allow 14 days for delivery, goods ex equipment unless stated new. SAE with enquiry or 2×16p stamps for List 32.

A. H. SUPPLIES

122, Handsworth Rd., SHEFFIELD S9 4AE
Tel. 444278 (0742)

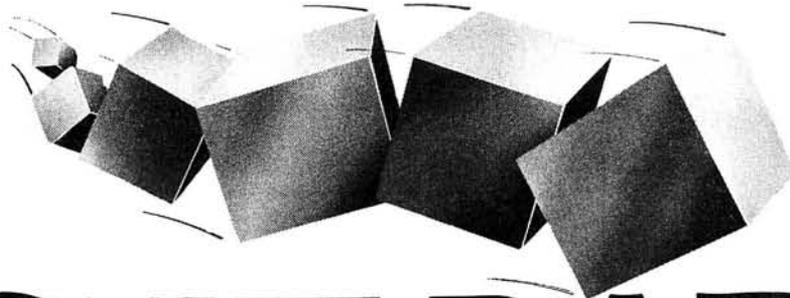

Part 2

PACKET RADIO

by Margaret Morrison KV7D, Dan Morrison KV7B and Lyle Johnson WA7GXD

This series is reprinted from Ham Radio Magazine by kind permission of the publishers, Communications Technology, Inc., of Greenville, New Hampshire, USA.

This article describes the inner workings of a terminal node controller (TNC), with emphasis on those aspects which are novel and useful to others interested in implementing digital radio systems. The discussion is based on the TNC designed by the Tucson Amateur Packet Radio Corporation (TAPR).¹

Understanding the TNC

As shown in Fig. 2.1, the TNC is essentially a special-purpose microcomputer. In many ways it is very much the same as any small computer system in that it contains a central processor, memory, and input/output (I/O) sections. The TNC differs from the average home computer in its I/O design, however, and we shall focus on these features.

The TAPR TNC uses a 6809 microprocessor, with 24K bytes of read-only memory (ROM) for program storage, and 6K bytes of read-write memory (RAM), for message buffers and other temporary data. The serial I/O port conforms to the EIA RS-232-C specification and is used to communicate through a terminal or with a computer. A dual 8-bit parallel I/O port is available for auxiliary use. A crystal-controlled clock provides system timing for various parts of the TNC.

The components of the TNC that make it a packet radio controller, and that could be added to a personal computer for a home-brew system, are the HDLC controller and the modulator/demodulator (MODEM). The HDLC controller is an l.s.i. circuit which provides a convenient means for implementing much of the level 1 and level 2 protocol discussed in part one of this series. It acts as a bidirectional digital port between the computer and the MODEM.

Equivalent to an RTTY terminal unit, the modem is a key part of the TNC, and contains the interface circuit that ties the computer to the station radio. It generates tones whose level can be adjusted for compatibility with the radio used, and its audio can be keyed to generate a Morse code station identification. The circuitry provides transmitter p.t.t. line keying and a fail-safe timer to prevent excessively long key-down. The demodulator can be easily configured to accept audio from different radios, and includes l.e.d. level indicators for adjusting the receiver volume.

Practical Wireless, January 1984

The versatile-interface adapter (VIA) block includes two 8-bit parallel I/O ports which communicate with the nonvolatile (RAM) semi-permanent storage, read user-settable switches, and control the modem. It also includes two counter-timers which provide interrupts for software timing and a programmable clock signal for the HDLC controller. The non-volatile RAM, a Xicor NOVROM which stores 32 bytes of information without battery or other standby power, represents a new technological achievement that should have wide application in Amateur Radio.²

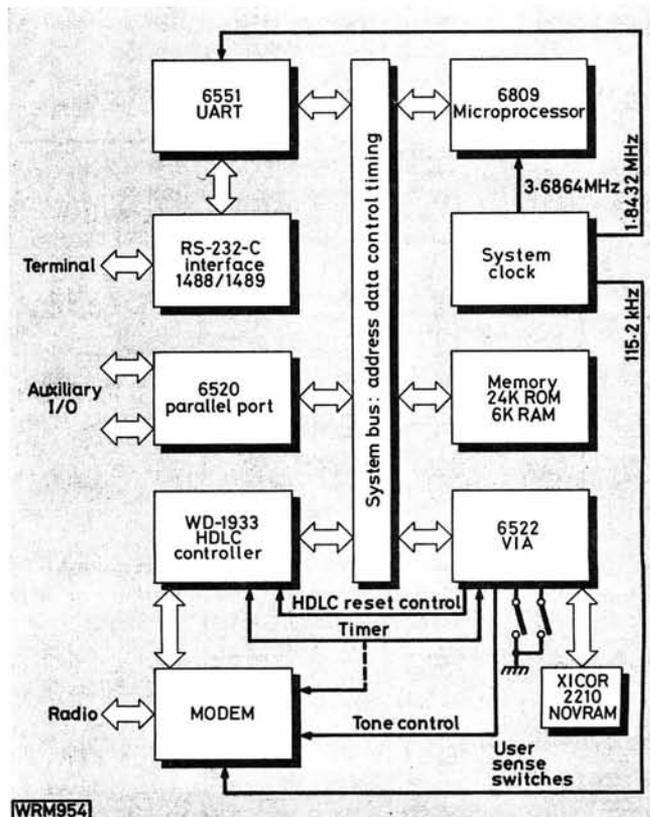


Fig. 2.1: Block diagram of the TAPR Beta TNC, showing system architecture

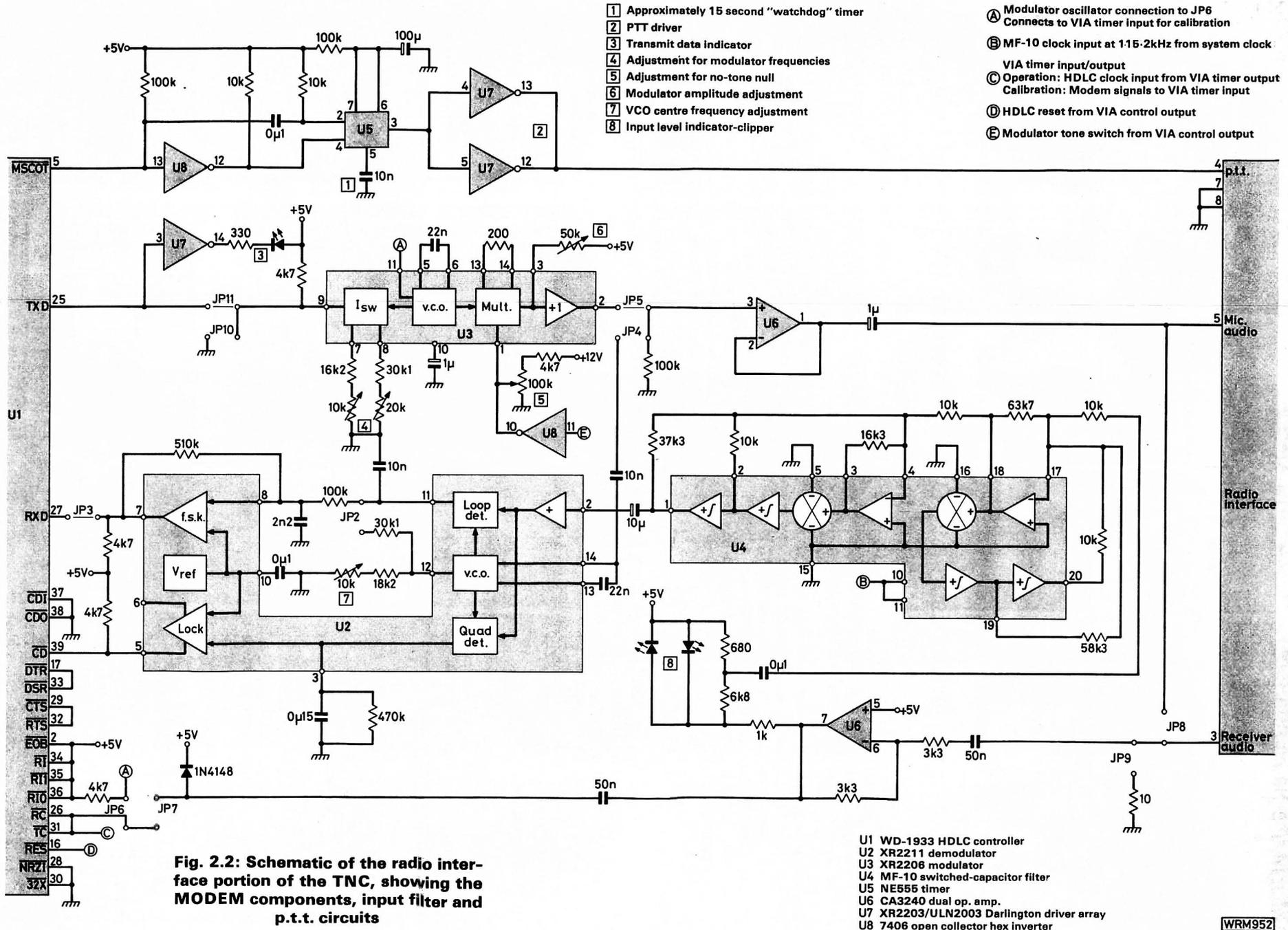


Fig. 2.2: Schematic of the radio interface portion of the TNC, showing the MODEM components, input filter and p.t.t. circuits

MODEM and Radio Interface


The radio and audio interface circuitry is shown in Fig. 2.2. Receiver audio output is buffered by one-half of U6 dual op. amp. Provision is made at jumper JP9 for attaching a load resistor in place of the speaker. The audio passes through an l.e.d. limiter/level-indicator to the MF-10 dual switched-capacitor audio input filter, which is configured as a high-pass section followed by a low-pass section. Both sections operate in Mode 3, as described by the manufacturer,³ with a clock input of 115.2kHz produced by the TNC system clock. The response of the filter is optimised for typical transceiver combinations using a computer-aided design procedure.⁴

The necessity for this filter is dictated by the audio spectrum of 1200Hz and 2200Hz NRZI data at 1200 baud. This spectrum, shown in Fig. 2.3, suggests that ideally the system should exhibit flat response from below 500Hz to above 2900Hz. In fact, the typical overall response measured using a pair of 144MHz f.m. transceivers is shown in Fig. 2.4 (a). Without proper filtering the roll-off shown prevents data from being demodulated much above 600 baud. The filter, U4 in Fig. 2.2, with the eight programming resistors shown (slightly different from those on the TAPR Beta TNC) restores the response to that shown in Fig. 2.4 (b), and seems a good compromise for a wide variety of f.m. rigs.

The filtered audio is demodulated by the XR2211, which is configured as recommended by Exar⁵ for demodulating 1200Hz and 2200Hz 1200 baud data, except for the lock-detect filter at pin 3. For better immunity to false lock indications this filter's time constant was increased. In addition to digital data from pin 7, the lock detect signal at pin 5 is required by the software to monitor channel activity.

The MF-10/XR2211 demodulator combination works well with a wide variety of f.m. transceivers. However, the lowest bit error rates for a given degree of receiver quieting will be achieved only by custom tailoring the input filter to produce the proper response for a specific transceiver pair. Normal experience is that data will be received perfectly under "full quieting" conditions, but deteriorates rapidly as the noise level goes up.

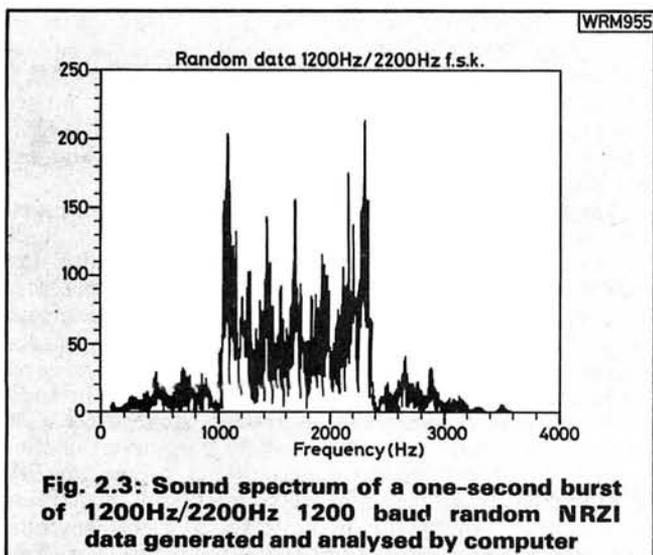Data originating on the TNC at the TXD output of the WD-1933 generates phase-continuous a.f.s.k. via the XR2206 modulator. As in the case of the demodulator, Exar's recommended values were used for loop compo-




nents.⁵ A control signal generated by the TNC's VIA under software control is used at point E to key the a.f.s.k. signal on and off. This permits the software to generate the c.w. identification and to eliminate modulator output except when actually sending packets. The modulator output is buffered by the second section of U6 before going to the microphone input of the transmitter.

The remaining circuitry of Fig. 2.2 grounds the radio's p.t.t. line to key the transmitter whenever the WD-1933 MSCOT output is brought low. To prevent channel lockup a NE555 one-shot "watchdog" times out after approximately 14 seconds, and MSCOT must be toggled high to restore p.t.t. operation. This simple circuit has proved invaluable.

Special Digital Hardware

The TAPR TNC includes digital circuitry that sets it apart from ordinary personal computers. Some details of these circuits will now be discussed; if you have a TNC, this information will help clarify some of its design considerations. Should you choose to home-brew a packet adapter for your computer, the discussion will serve as an example.

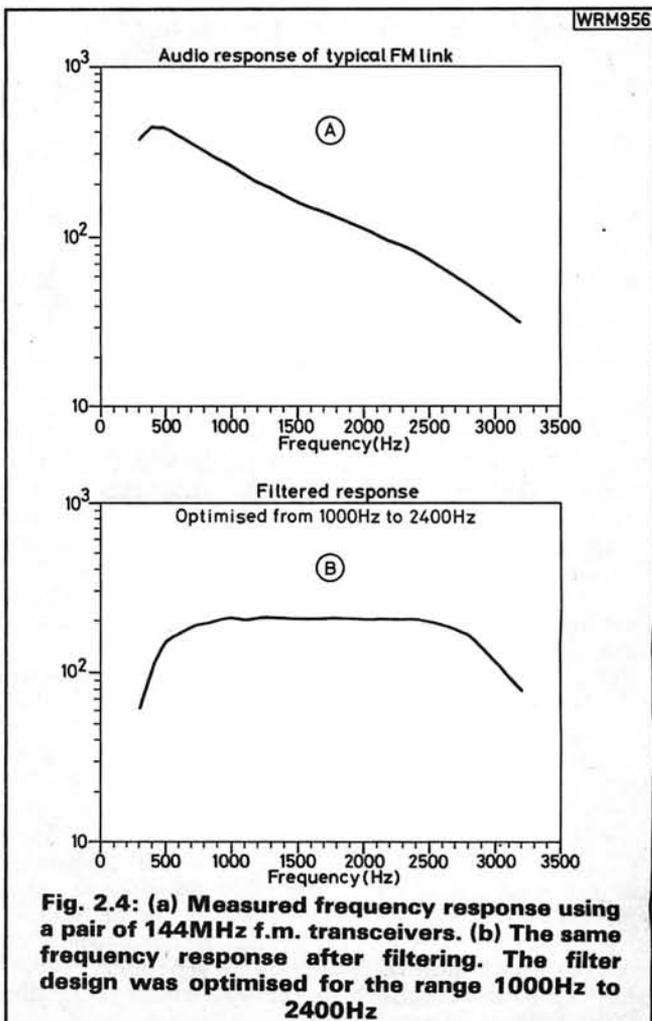The most important special chip on the TNC is the HDLC controller. There are several HDLC controller chips on the market today, and more are being introduced regularly. This is fortunate for the would-be TNC designer, because the HDLC chip relieves him of a fairly complex hardware design (typical 19 s.s.i. and m.s.i. i.c.s) or an equivalently complex software program (in assembly



language) to implement those parts of the HDLC protocol standard adopted by the overwhelming majority of packeteers.

As mentioned in the previous article, the most frequently used digital signalling technique employs Non-Return to Zero, Inverted (NRZI) encoding. This means that a digital 0 is encoded as a transition from a high to a low or vice-versa, while a 1 is passed as the absence of a transition. The result is this, along with "bit-stuffing" (in which a 0 is inserted by the sending station after five consecutive 1s and stripped out at the receiving end), is that the clock signal can be recovered from the data stream. A phase-locked clock is necessary to ensure proper recovery of the data in this synchronous data mode, since the data must be latched in the middle of a bit and not, for example, just as a transition occurs.

Clock recovery is fairly straightforward using a phase-locked loop (p.l.l.). Fortunately, the NRZI scheme is also widely used in the commercial world, so a few manufacturers have included a digital p.l.l. (d.p.l.l.) on their HDLC controller chips. In order to minimise the number of chips used in the TNC, both the VADCG and the TAPR designs incorporate these HDLC controllers.

Among single-channel devices, only the Intel 8273 and the Western Digital 193X series incorporate the d.p.l.l., and the TAPR TNC uses the WD-1933, as it is generally about half the price of the Intel device. Of course, nothing is free, and some special considerations apply when interfacing this chip to a microcomputer. The software must take account of the inverted data bus of the WD-1933 which treats 0s as 1s and vice-versa. In addition, the interrupt lines must be buffered and inverted prior to connection to the control bus. Furthermore, this chip requires a baud rate clock 32 times the data rate (for 1200 baud this means a 38.4kHz clock) to drive the d.p.l.l. when using the NRZI mode, and also requires a special reset signal to be applied after the baud rate clock has been applied.

In exchange for these interfacing considerations, the HDLC controller provides automatic generation of pre-frame and post-frame flag bytes for synchronisation, transparent bit-stuffing on transmit and unstuffing on receive, recovery of the clock signal from the incoming data stream, calculation of the Frame Check Sequence (FCS) used to validate data integrity on both transmit and receive, and automatic detection and reporting of errors in sending or receiving a frame. All in all, the usefulness of these l.s.i. devices more than compensates for any interface difficulties.

In order to supply the HDLC controller with the needed reset and clock signals, and to provide other services, the TAPR TNC incorporates a 6522 Versatile Interface Adapter (VIA). This unit contains a pair of 8-bit parallel ports, which can be set on a bit-by-bit basis for input or output. Two of the four handshaking lines provided are used as single-bit control outputs. A pair of 16-bit counter-timers are also provided.

One of the control lines is used to provide a software controlled reset to the HDLC chip, while the other is used to effect a tone on-off command to the MODEM. This allows generation of an easily-copied c.w. station identification, as well as enabling an operator to insert a voice signal over the channel without disconnecting the TNC from the radio.

Two lines of one of the 8-bit ports (port B) connect to the internal 16-bit counter-timers. One timer is used as a software-controllable baud rate generator for the HDLC chip. This not only allows the operator a simple means for control of the baud rate, it also allows generation of non-standard baud rates, such as the 400 baud used in the AMSAT Phase III satellite.

The other timer is used for calibrating the MODEM frequencies and for primary system timing. From this clock are derived all the various clocks that must be updated for proper operation of the packet station of which the TNC is an integral part.

Two lines on the VIA are used to test the settings of a pair of switches on the board. These switches may thus be read by the software and are presently being used to tell the TNC whether to use the default parameter settings found in the system EPROM or whether to take these parameters from NOVRAM.

The remaining lines from the VIA parallel port are used for the NOVRAM interface. This helps prevent accidental alteration of NOVRAM parameters, as well as easing system bus timing constraints. The NOVRAM is a nibble-oriented device, meaning that its data bus is only 4 bits wide, rather than the 8-bit bus width of the host microprocessor. It also has six address lines and four control inputs. The control lines allow for device selection, read/write control of data between the RAM portion of the chip and the data bus, recall of the contents of the Electrically Erasable Programmable Read Only Memory (EEPROM), and storing of data from RAM into EEPROM.²

The presence of the NOVRAM permits long-term storage of parameters peculiar to the station, such as the callsign and terminal characteristics. In addition, infrequently adjusted parameters, such as those associated with the timing of data retries and other link activity, may be stored. Without such a long-term storage function there are only two choices. Either the operator must enter all necessary information every time the unit is powered up (which is not too practical), or the various parameters must be "burned-in" at assembly time, meaning that the operator must have his EPROMs erased and re-programmed every time he wants to change baud rates, callsign, station ID, and so forth.

Controller Software

The software present on the TAPR TNC is organised on two levels. The High Level Routines (HLRs) implement the machine-independent logical processes associated with protocol decisions and response to user commands. These routines know nothing of the hardware details of the TNC and, in fact, are written in a transportable *high level* language (PASCAL). As the HLRs require data transfers or status information they call subroutines contained in the Low Level Routines package (LLRs), and leave the nitty-gritty details of interrupt service, terminal editing features, and timer maintenance to the LLRs. The LLRs, naturally, are written in 6809 assembly language, and are definitely not transportable. However, the logical organisation of the LLRs is universal and should serve as a model for other implementations of packet radio.

The HLRs can be divided roughly into two major parts. One implements the command protocol, allowing the user to request connect and disconnect packets, control the digital-relay function of the station, and perform other tasks as necessary. For the TAPR TNC, this section consists of a command parser which compares a string of characters from the terminal with a list of commands and takes appropriate action when a match is found. In addition to issuing connect and disconnect packets, the user can alter program parameters, save the parameters in non-volatile RAM, display current parameter values, identify in Morse code, change input mode, or enter a special service routine. For maximum flexibility in a test environment, the parser controls some sixty parameters, including

the operator's callsign, terminal attributes, input editing features, radio interface characteristics, packet baud rate, and timing parameters.⁶

The other part of the HLRs is a procedure which implements the packet radio protocol. This section assembles and disassembles packets, maintains information about the link status (for example, to whom you are connected), keeps track of unacknowledged outbound packets, acknowledges inbound packets, and sends supervisory packets as required by whatever protocol is implemented. This routine watches a clock to time retransmissions of unacknowledged packets, formulates input from the terminal into packets, and passes the contents of received packets to the terminal.

Both sections of the HLRs depend on the LLRs to maintain buffers and perform I/O under interrupt control. The LLRs also update clocks on receipt of timer interrupts and service the non-volatile RAM. When the program is required to transmit a message to the terminal or to send a packet, the information is actually loaded into a buffer to be sent when the peripheral component is ready. Similarly, the program reads incoming information not directly from the peripheral, but from a buffer. The presence of complete messages to be read is signalled by flags set by the low-level input routines. This makes it relatively easy to implement the protocol in a high-level programming language without direct access to the peripheral devices.⁷

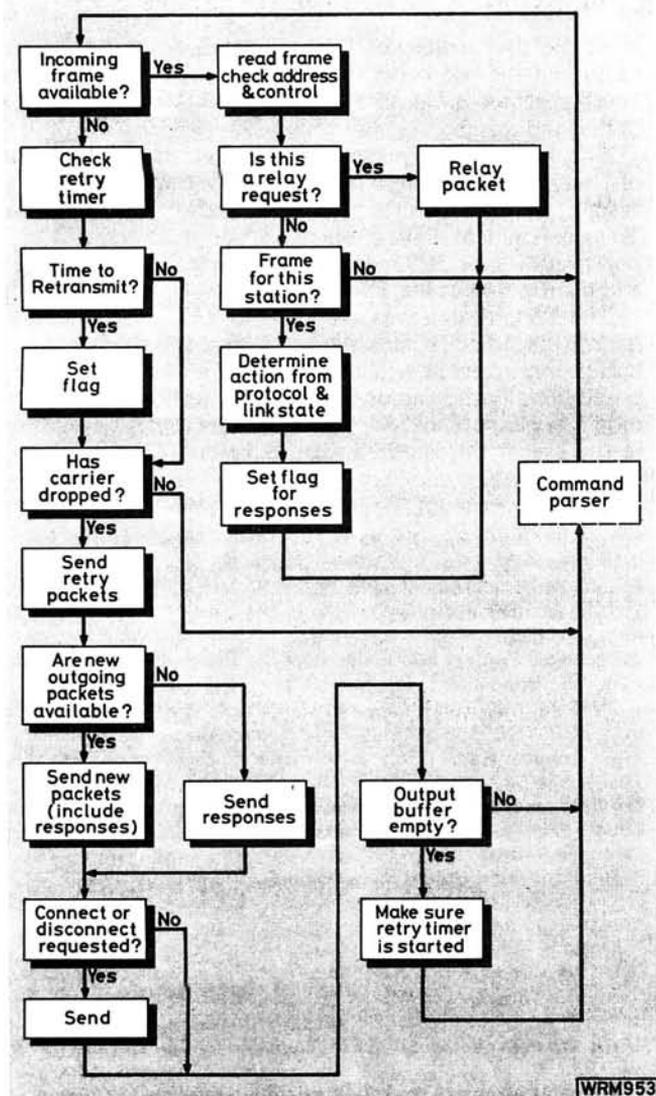


Fig. 2.5: Flowchart for operation of the packet protocol HLR routine

The utility of the HLR/LLR separation cannot be overemphasised. It allowed, for example, the two sections of the HLRs (command parser and packet protocol generator) as well as the LLRs to be developed independently by three people, in two different cities, on three different computers, prior to the final integration onto the TNC.

Program Structure

The structure of the packet protocol section of the HLR is shown in Fig. 2.5. This procedure is part of an infinite loop in which all routines alternately check for tasks to be done.

The first half of the procedure is concerned with reading incoming packets and determining the appropriate action to take. The action taken on receipt of a packet addressed to this station is determined by the protocol.^{1,8} Several possible link states are defined, which are stages in the communication sequence starting with a connect request and ending with a disconnect request. For each type of packet received (specified by the CONTROL field) there is a prescribed action depending on the link state. If the action involves sending a packet—say, an acknowledgment—a flag is set for the second half of the procedure. When all incoming packets have been read, the clock is checked to see if packets have been sent which should have been acknowledged by now.

The second half of the packet protocol procedure, which sends outgoing packets, is entered only if the frequency is clear, indicating that all packets of a group have been received. This is determined by monitoring the demodulator carrier detect signal. Outgoing packets are formulated with header information and moved to the outgoing packet buffer following any packets being retried. Acknowledgments are sent as part of the control information with these packets if possible; otherwise, a special acknowledgment packet is sent. Finally, any special supervisory packets requested either in the first section of the procedure or by the user are sent. When transmission is complete, the clock is started for packets which should be acknowledged.

I/O Management

The interrupt-driven I/O routines contained in the LLRs basically form a simple operating system for supporting the HLRs.⁹ In order to isolate the main program from the details of the hardware, all input and output is done through buffers. Since the HLRs do not examine incoming data until an entire line or packet has been received, terminal support such as character echoing, line-feed insertion, and response to character, line, and packet delete instructions (implemented by single editing characters) are managed by the low-level interrupt routines.

The structure of a typical buffer is shown in Fig. 2.6. There are four buffers, input and output buffers for terminal and radio data, each of which is accessed by an insertion pointer and a removal pointer. An input buffer, for example, has an insertion pointer which is advanced by an LLR interrupt routine as data is read from a peripheral device, and a removal pointer which is advanced by the HLR as it reads the data. All buffers are circular, meaning that when a pointer reaches the top of the buffer space it is moved back to the bottom. Input buffers require additional pointers to mark the beginning of a string which may be deleted by an editing command from the terminal, or in the case of a packet input buffer, by an error occurring during

receipt of a packet. Since a data string can be any length, the end of a packet or command line must be marked, either by a special character in the buffer or by a byte count at the beginning of the string.

Interrupt Handling

Only one hardware interrupt-request input of the 6809 microprocessor is used in the TAPR design—all interrupt lines are wire-ORed together. This means that when an interrupt occurs, each peripheral which could have generated it must be queried in turn, and an appropriate routine selected from a dispatch table when the cause of the interrupt is identified. Since more than one device could be in need of service at once, the order in which the devices are queried determines the interrupt priorities, which are as follows:

1. UART (terminal) input
2. UART output
3. VIA timer interrupt
4. HDLC (radio interface)
5. Parallel port input
6. Parallel port output

The serial input port is given highest priority, since if a character is not read before a new one is received, it is lost. The radio I/O interrupts are placed relatively low, since servicing the WD-1933 chip is complex and potentially time-consuming. Data lost in either direction due to slow service of this chip will be detected as an error, and the packet will be retransmitted. If the parallel port is used for user I/O, it should be serviced last, since full "handshaking" is used, and a sending device will not send new data until the old data has been read.

The timer interrupt is generated as the timer counts down past zero. By examining the count, the service routine can determine the actual elapsed time and compensate for any delay caused by conflict with other interrupts. For this reason, the priority for servicing the timer interrupt is arbitrary. Compensation must be made for the fact that the two count bytes are read at different times.

The timer interrupt service routine has a special function. After the software counters have been updated, a general housekeeping routine is entered. Time elapsed since a carrier drop is monitored and a packet transmission may be started from this routine. The c.w. station identification is also sent at appropriate intervals, and the timer routine toggles the audio signal on and off to produce dits and dahs.

The WD-1933 HDLC controller generates interrupts for the following seven conditions:

- Receive Interrupts (by priority)
 - Data received
 - Received message without errors
 - Received message with errors
 - Change in carrier detect state
- Transmit Interrupts (no priority)
 - Data requested
 - Transmitted message without errors
 - Transmitted message with errors
 - (Abort signal sent automatically)

Since they may potentially be present in any combination, and querying the chip resets most conditions, all conditions must be checked on each interrupt. The only difficulty results when logically inconsistent or out-of-place interrupts occur. For example, the presence of both "Received message without errors" and "Received message with errors," or a carrier-detect change while the transmitter is keyed, may occur. This is solved by ordering the receive interrupt priority as shown. Carrier detect can be ignored during transmission.

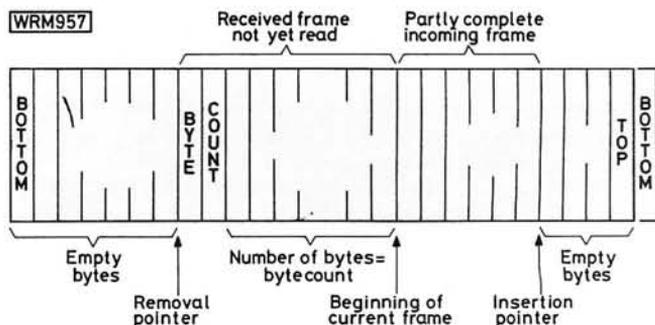


Fig. 2.6: A typical data buffer, showing pointers, and order of placement data. The buffer shown is the packet input buffer, and is similar to the other buffers

Transmit interrupts present a different sort of problem. The WD-1933 transmits HDLC frames automatically, but it must be commanded to send each section of the frame: flags, data and frame-check sequence. While the transmit function is active, it generates regular interrupts. These are "Data request" if the data function is commanded, and otherwise "Transmit end of message". These interrupts are treated as equivalent, and the interrupt service function is determined by the progress of the packet being transmitted.

Conclusion

In the first article of this series we described packet radio and the protocols in general use. In this article we have presented some details of the actual implementation of these concepts.

The TNC design presented represents the culmination of nearly two years of intensive effort by several Amateurs. These efforts resulted in both the formation of Tucson Amateur Packet Radio, a nonprofit R & D corporation of over 300 members worldwide, and the design and distribution of the TAPR TNC.

The TNC design was subjected to a Beta test with 172 boards placed at 19 sites. This test served to provide many useful improvements. Perhaps most importantly, it exposed literally thousands of Amateurs to this exciting new mode. We expect that soon there will be a rapid expansion in the use of this mode among Amateurs, and hope that you will join it.

References

1. Tucson Amateur Packet Radio Corporation Packet Radio System Beta Test (1983). (Available from TAPR, PO Box 22888, Tucson, Arizona 85734; \$15 post paid).
2. Lyle Johnson, WA7GXD, "Using the Xicor NOVRAM", *QEX*, August 1982, page 4.
3. Technical Product Information, *MF10*, National Semiconductor, 2900 Semiconductor Drive, Santa Clara, California 95051.
4. Margaret Morrison KV7D, and Dan Morrison KV7B, "Designing the TAPR TNC Audio Input Filter", *Proceedings of the Second ARRL Amateur Radio Computer Networking Conference March 19, 1983*, page 54.
5. *Phase-locked Loop Data Book*, Exar Applications Note AN-01, 1981, Exar Integrated Systems, PO Box 62229, Sunnyvale, California 94088.
6. Harold E Price, "Multi-use Design Considerations for the TAPR TNC", *Proceedings of the Second ARRL Amateur Radio Computer Networking Conference, March 19, 1983*, page 62.
7. David Henderson, "Design Decisions for the TAPR TNC Link Level," *Proceedings of the Second ARRL Amateur Radio Computer Networking Conference, March 19, 1983*, page 21.
8. Terry Fox, "AX.25 Level 2 Protocol", *Proceedings of the Second ARRL Amateur Radio Computer Networking Conference, March 19, 1983*.
9. Margaret Morrison, KV7D, "Real-Time Low-Level Software on the TAPR TNC", *Proceedings of the Second ARRL Amateur Radio Computer Networking Conference, March 19, 1983*, page 50.

BEST BUYS AT LEE'S



STANDARD C58 2M FM

STANDARD COMMUNICATIONS

C5800	The most advanced 2M multi-mode mobile yet with 25 watts output in all modes. Spare Mounting Bracket	359.00 9.95
C8900	New slim fully synthesized 2M 10W Mobile with 5 memories, scanning facilities and digital read-out etc.	219.00
C7900	New slim fully synthesized 70cm 10W mobile with 5 memories, scanning 10MHz coverage and digital read-out etc.	239.00
C58	Spare Mounting Brackets for above	7.95
C58	2M FM/USB/LSB and CW portable with 1W RF Power and tuning down to 100KHz	249.00
C78	Fully synthesized FM70cm 1W transportable	229.00
CMB8	Mobile mounting cradle for C58 and C78 with all the connections for antenna power etc. built in	21.51
CPB58	A 25W linear amplifier for C58 that bolts underneath the CMB8	82.50
CPB78	A 10W linear amplifier for C78 that bolts underneath the CMB8	69.43
CLC8	A carrying case for C58 and C78 with flap over top for added protection	6.95
C12/230	Charger for the C58 and C78 when Ni-Cads are used	7.75
CN10	Set of Ni-Cads for the C78/C58	9.00
C110	Synthesized 2M 2 watt hand held 144-148 MHz	139.95
CNB110	Heavy Duty Ni-Cad Pack	30.00
CSA110	Heavy Duty Base Ni-Cad Charger	30.00
CLC110	Leather Carry Case	6.75
CMC01	Car Power Adaptor	7.95
C10-230	Wall Type Charger with 6 Ni-Cads	12.50

TELECOMM

TOP QUALITY MOBILE ANTENNAE

TA301	Mobile 1/2 Wave 66-512 MHz snap-in mount	4.50
TA307	1/2 Wave Low Band 66-100 MHz	7.50
TA309	Mobile 5/8 Wave 144-172 MHz snap-in mount 3dB gain	9.95
TA144	Mobile 1/2 Wave 144-148 MHz snap-in mount 3dB gain	7.50
TA550	Mobile 1/2 Wave 138-180 MHz snap-in mount 3dB gain	14.66
TA330	Mobile 70cm co-linear 6dB snap-in mount	9.95
TA3MM	Magnetic mount with 5 mtrs coax PL259 fitted	9.75
TA309/MM	TA309 aerial and TA3MM Package	16.95
TA3GM	Solid gutter mount with 3/8 inch hole for all TA aerials	4.31
TAMSP	Folding Gutter mount, takes SO239 socket	7.50
TA3GC	Gutter Clip for all TA aerials 5 mtrs coax and PL259	10.35
TA5MM	PL259 Mag Mount with 5 mtrs of coax cable	9.95
MASPRO	7/8 Wave	17.95
TA285D	6dB Base Station co-linear 144-148 MHz with radials	32.50
TA485D	6dB Base Station co-linear 430-435 MHz with radials	32.50
DPLC22	6.5dB Mobile co-linear 144-146 MHz	29.95

HELICAL ANTENNAS

BNC	Type/PL259 Type/Screw thread long and short for Standard, Icom, Trio, Yaesu etc.	4.50
-----	--	------

YAESU MUSEN

THE LARGEST RANGE
IN LONDON
PHONE FOR PRICES!

POWER SUPPLIES


PX402	3A continuous 4A Max 13.8 VDC fully stabilized	19.95
PH500	5A continuous 7A Max 13.8 VDC fully stabilized	45.95
EP2510	25A continuous 30 Max 13.8 VDC fully stabilized	97.75
EP3010	As above but with meters	125.95
DRAE	13.8 12 AMPS	74.00

DUMMY LOADS

T-25	DC-500 MHz 30W with PL259 connection	6.00
T-100	DC-500 MHz 100W with SO239 socket	24.25
T-200	DC-500 MHz 200W with SO239 socket	34.50

LOW PASS FILTERS

TF30M	1Kw Low Pass Filters	19.95
-------	----------------------	-------

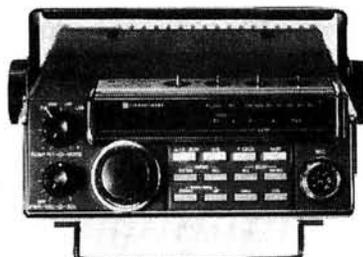

STANDARD C5800 2M

METRES

SWR15	Single meter SWR/Field strength 3.5-10 MHz	9.50
SWR25	Twin meter SWR/Power/Field strength 3.5-150 MHz	12.50
UH-74	Single meter SWR/Power 5/20/120W 144 and 432 MHz	16.95
SWR200B	Twin meter SWR/Power 3.5-150 MHz	40.25
TAL172	Single meter professional SWR/Power 5/25/100W 148-174 MHz optional mounting bracket available	37.95
T435	Twin meter 144/432 MHz SWR/Power 20W/120W	37.50
SWR150	Deluxe Twin SWR/Power meter 3.5-150 MHz	16.95

MORSE KEYS

HK707	Straight up/down keyer	13.00
BK100	Semi-automatic bug	20.00
HK702	Up/down keyer on marble base	26.50
MK702	Manipulator	26.50
MK705	Squeeze paddle	13.00
MK705	Squeeze paddle with marble base	26.50
MK1024	Automatic memory keyer	120.00
EK150	Semi automatic keyer	74.75
EMK1A	Morse code practice oscillator	7.50

LARGEST STOCKISTS
OF MICROWAVE
MODULES
PRODUCTS

COAX SWITCHES AND RELAYS

TS120	1 in 2 out slide switch with SO239 socket	6.04
CTS-1	1 in 2 out toggle switch with SO239	6.04
CTS-2	1 in 2 out toggle switch with 1 PL259/SO239s	6.04
SA450	New heavy duty 1 in 2 out switch DC-500 MHz 1KW power handling	10.24
CH-20A	1000W DC-1 GHz 1 in 2 Out	17.25
CX-600N	Heavy duty coax with N type connectors DC-500 MHz 600W/30 MHz	25.30
CX-230	300W DC-500 MHz (Max 1.5 GHz) fitted with 3 BNC sockets	20.99
CX-120A	150W DC-200 MHz (Max 1.5 GHz) for coax cable connectors	11.21

ADONIS MICROPHONES

AM803	Desk compressor mic with head and neck	59.00
AM503	Desk compressor mic as 803 with one output	42.25
AM303	Desk mic	32.78
202HD	Head set with control box and fet head	34.44
202FX	Swan-neck fet mic with control box	37.38
202S	Flexible neck clip mic with control box	23.00
HW7-TT	Head set boom mic for Trio	29.95
HW7-7I	Head set boom mic for Icom	29.95
HW7-7Y	Head set boom mic for Yaesu	29.95
MS10	Visor Speaker with Memory Pad	16.50



FULL RANGE IN STOCK


DATONG

PC1	Gen Coverage Converter HF on 2M	137.42
VLF	Very Low Frequency Converter	29.90
FL1	Frequency Agile Converter	79.35
FL2	Multi-mode Audio Filter	89.70
FL3	Audio Filter & Notch	129.37
ASP	Auto RF Speech Clipper (Trio or Yaesu Plug)	82.80
D75	Manually controlled RF Speech Clipper	56.35
RFC/M	RF Speech Clipper module	29.90
D70	Morse Tutor	56.35
AD270	Indoor Active Antenna (ex-PSU)	47.15
AD370	Outdoor Active Antenna (ex-PSU)	64.40
MK	Keyboard morse sender	137.42
Codecall	Selective Calling Device (Link Prog)	32.20
Codecall	Selective Calling Device (Switch Prog)	33.92
RFA	Wideband preamplifier	6.90
MPU	Mains Power Unit	6.90

AUDIO FILTERS

SRB2	*NEW* automatic Woodpecker Blanker	86.25
FL3	Deluxe multimode filter with automatic whistle remover	129.37
FL2	As FL3, but without automatic whistle remover	89.70
ANF	*NEW* advanced stand-alone automatic whistle removal filter for SSB, plus CW filter	67.85
FL2/A	Fully assembled module with hardware and instructions to convert FL2 to FL3	39.67

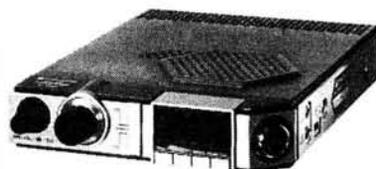A LARGE RANGE OF PLUGS
SOCKETS AND CONNECTORS
ARE AVAILABLE AT
COMPETITIVE PRICES



STANDARD C7900/C8900

All prices are inclusive of V.A.T. and are correct at time of going to press.
Carriage/Postage + Packing extra. New catalogue available now - 30p.

400 EDGWARE ROAD,
LONDON W2
01-723 5521 Tlx 298765




Normally 24hr despatch
but please allow up to 7
days for delivery.

NEAREST TUBE:
EDGWARE ROAD
PADDINGTON

OPENING TIMES:
9.30am-5.30pm Mon, Tues, Wed, Fri.
9.30am-1pm Thurs.
10am-4.30pm Sat.

Lee's Electronics Ltd

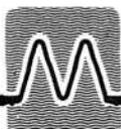

MICROWAVE MODULES LTD

MML144/30-LS MML144/100-LS
£69.95 (P&P £3) £169.95 (P&P £3.50)

These products have been specifically designed for the many low power multimode 2 metre transceivers, and have a switchable input for either 1 or 3 watt levels.

The MML144/30-LS provides 30 watts RF output power, whilst the MML144/100-LS will provide 100 watts. Both units require 13.8V DC and include an ultra low-noise receive preamp (3SK88), which can be controlled from the front panel.

An RF vox circuit is incorporated with switched delay times, suitable for FM or SSB, thus making the unit simple to operate.

When the DC supply voltage is removed, a straight through path is made so that the transceiver can be used barefoot, without disconnecting any leads.



MML144/30-LS



MMS 1

MML432/50 MML432/100
£129.95 (P&P £3.50) £245 (P&P £4.50)

These amplifiers are compatible with any 10 watt 70 cm multimode equipment, and can be supplied for ATV use at no extra charge.

The MML432/50 provides 50 watts RF output power whilst the MML432/100 will provide 100 watts.

Both units require a 13.8V DC supply and include an RF vox circuit, thus making operation simple. (The MML432/50 also includes a low-noise receive preamplifier).

Current drain is 8 amps for the 50 watt version and 18 amps for the 100 watt.



MMT432/144-R

MMS1
£115 (P&P £3)

MMS1 - The Morsetalker An ideal morse tutor, which sends random morse code in the range 2-20 w.p.m., and provides speech talkback of the morse so that the pupil may check his/her ability.

Letters and numbers can be selected and the alphabet is formatted in 4 sections to aid learning. Group lengths of 1, 5 and 50 characters can be selected, and the facility to send continuous morse without speech talkback is included. A 12 volt DC supply is all that is needed and the unit can be used in a vehicle from the standard battery.

MMS2
£169 (P&P £3)

MMS2 - Advanced Morse Space Trainer This unit is based on the MMS1, and boasts the same basic features, with the following additions:—

1. The pupil may key in his/her own morse code. In this way, sending proficiency can be perfected.
2. An uprated speed range: 6-32 w.p.m.

MMT432/28-S
£159.95 (P&P £3)

MMT432/28-S This transverter provides coverage of 432-436 MHz in two ranges, switch selectable, and is compatible with any 10 metre transceiver having a low-level output. (5-500mW).

The unit produces an output power of 10 watts and incorporates a low-noise receive converter, which together provide high performance in all respects.

MMT432/144-R Similar to the unit above, this transverter is compatible with 2 metre multimode transceivers, and incorporates a repeater shift of 1.6 MHz.

An attenuator is supplied to allow use with transceivers having an output power of 10 watts nominal. (An alternative attenuator allowing other levels is available to order).

MMT432/144-R
£184 (P&P £3)

MOVE UP TO THE PEACE AND QUIET ON 70 cm!
Goods normally despatched within 10 days

HOURS:
MONDAY TO FRIDAY
9-12.30, 1-5.00

OUR ENTIRE RANGE OF PRODUCTS WILL BE EXHIBITED AND ON SALE AT MOST OF THE 1984 MOBILE RALLIES BY OUR SALES TEAM. SEE YOU THERE...

MICROWAVE MODULES

BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN, ENGLAND
Telephone: 051-523 4011 Telex: 628608 MICRO G
CALLERS ARE WELCOME, PLEASE TELEPHONE FIRST

Ex-Gov. 27ft telescopic aerial close to 5ft. Good condition, complete with all base & fittings **£45**. P&P paid. Callers welcome **£25**.

Pye Pocketfone Nightcall for PF1/TX/RX. New boxed **£17.00**.

Whip aerial Ex-Gov. 4ft collapsible **£1.00**.

Aluminium masts 4ft x 2in dia poles. Height 50ft, push in, complete in bags. Ex-Gov. stakes, ropes, base. Good condition **£45.00**. Callers **£35.00**.

Crystals HC6U Ex. Equip. 5.000 mc/s, 7.000 mc/s, 8.000 I.M.C mc/s, 9.000 mc/s. Also Glass Crystal 100 Kc/s, to fit B7G base. All at **£2 p&p** paid.

Telephones - Type 706 good condition **£5 p&p** paid.

Small 230V fans, 4 in. x 2½ in. 2,500 r.p.m. **£4.50 p&p** paid.

Pye Pocketfone PF1, battery charger, 12 way with meter **£10 p&p** paid.

We have also for sale the following items which are too numerous to advertise. Callers only, valves, transformers, tuning units, receivers, bases, wave-guide, scopes, plugs, sockets, power units, capacitors, aerials, headsets, cable, signal generators, BC221.

Opening times:

Monday-Friday 8.30am-5.00pm, Saturday 8.30am-12am

Please allow 14 days for delivery.

A. H. THACKER & SONS LTD
HIGH STREET, CHESLYN HAY
NEAR WALSALL, STAFFS.

COMMUNICATION CENTRE OF THE NORTH

The largest range of communications equipment available in the North. Full range of receivers, transceivers, antennas, power supplies, meters. Ali tubing - wall brackets etc.

We are the only official TRIO stockists in the North West. Full range of equipment on display. Guaranteed after sales service.

RECEIVERS

TRIO R600 Solid State Receiver	£257.60
TRIO R2000 Solid State Receiver	£398.00
JRC NRD515 Receiver	£985.00
YAESU FRG7700 Receiver	£335.00
Diawa 2m FM Receiver	£46.00
CD600A Airband Receiver	£99.00
Wide Band Scanning Receiver AR2001, 25-550 MHz	£300.00
R532 Airband Receiver	£159.40

Please send SAE for full information and up-to-date prices as these fluctuate to change in sterling rates.

For the caller a wide range of Aluminium Tubing, Clamps, etc. at competitive prices, i.e. 12' x 2" Ali Tubing **£9.00**.

Part Exchanges welcome. Second hand lists daily.

Send S.A.E. for details of any equipment.

HP terms. Access/Barclaycard facilities.

Open 6 days a week. 24 Hour Mail Order Service.

Phone 0942-676790.

STEPHENS JAMES LTD.
47 WARRINGTON ROAD,
LEIGH, LANCs. WN7 3EA.

Letters

RAE—May 1983

Sir: I would be grateful if you will allow me a few lines in which to reply to the letter of Mr Rumbelow, published in your August issue, and the letters from other readers which supported his criticism.

It may be useful to some of your readers if I start with a brief outline of how multiple choice question papers are constructed. Every paper follows a standard specification which allocates a certain number of questions to each section of the syllabus. The present specification is given on Page 13 of the syllabus pamphlet and will only be changed to give more "weighting" to a particular section when the syllabus itself is revised.

Each paper is designed by a working party which selects items from a "bank" of questions, all of which have been validated in pre-test and many of which have been used in previous examinations. This bank is being continually reviewed and augmented. The validating procedures which include pre-testing give us a clear idea of how the particular item will "perform" (i.e. among other factors, how many candidates will get it right) and your readers may be surprised to learn that most items perform in the same way each time they are used. The "facility value" of an item (i.e. how easy or difficult it is) is therefore a known quantity but, obviously, varies from item to item. However, in constructing a paper, we can balance difficult items with easier ones and can predict accurately the "mean score" (average mark) for all candidates.

There was no departure from this system in the development of the May 1983 papers and certainly no change of policy. All items were taken from the bank and a number had already been used in earlier examinations. The syllabus was covered according to the specification. The overall results do not suggest that candidates found Paper 2 more difficult than in previous years: 19.2% failed Paper 2, compared with 24.9% last year and in the examination as a whole the pass rate of 70% (5305 out of 7533 candidates) compares favourably with 66.9% last year. I have been able to trace the results of 10 of the 16 candidates who wrote criticising Paper 2, and of these 3 obtained credits, 4 passed and 3 failed, two of the three also failing in Paper 1. It would seem that some of your readers have a very modest view of their own knowledge and ability.

I hope that this summary has been of interest and I should again point out that the ultimate objective of the RAE is to establish that the candidate is capable of operating an amateur station within the terms of the licence. The achievement of this objective can only be of benefit to all operators.

S. D. Allison

City and Guilds of London Institute

Sir: After reading the Letters in the October issue of *PW* I felt that as a Tutor I should reply.

Fifteen of my class took the May exam; 13 passed, 2 failed the second part and 1 failed the first part.

None of them complained about the questions and said that everything that I had taught them had come up. The two that failed the second part had not attended all the classes.

The RAE Manual does not cover everything and too many students rely on this book to pass the exam. Like Mr. E. W. Stannard, I have spent over £200 on books, most of this on the Heathkit Continuing Education Series. I don't expect my students to spend this much, but they get the benefit of them through my teachings. There are articles in your own

Practical Wireless, January 1984

publication *Passport to Amateur Radio* which are not in the RAE Manual. I have produced my own book which students can obtain at my classes to try and cover the "gaps".

Complaints of the phrasing of questions I find come from those who don't read the questions properly (it's happened in my classes). A lot of students accept the example questions as the ones they will get in the exam, what they should do is change the questions round as many times as they can and form new questions, for some of those wrong answers are right if a word or two is changed in the question, change "Input" to "Output", a $\frac{1}{4}\lambda$ or $\frac{1}{2}\lambda$ shorted line has a different impedance when it's an open line, etc.

Mr. R. W. Lannon complains of lack of mathematical problems, he was obviously expecting a lot. The syllabus states "Electrical Theory" 11 questions (Page 31, *How to Become a Radio Amateur*). There were 12 questions in the May exam. For those who complained about the syllabus take a look at pages 21-30 of the above publication. The exam covered all aspects of the syllabus. I have received complaints from students about the exam, from other teaching centres. Their main complaint was they were not taught the questions that came up, and they were bogged down with maths. This aspect lies squarely on the shoulders of the Tutors.

D. F. Jones GW3SSY
Blaenavon

Sir: With regard to the May RAE. I sat the examination and was successful; a credit on both papers. I first tried a correspondence course; although many people probably find this adequate I felt I needed more personal direction so I enrolled at the local Radio and Electronics Society. This proved, in my case, the correct move.

We were taught strictly to the syllabus by an excellent instructor who drilled us, I believe, to above pass-mark requirement.

Over 90 per cent of the class passed, many with credits, and at least two distinctions.

Until I received the result I was far from confident about passing Paper II. The questions seemed to call for wider concepts of radio than the sample questions in the *RAE Manual*. The examiners seemed to have moved in a maze-like fashion to arrive at some of the questions. So parrot learning of formulae would not have been enough to pass. A good grasp of English was also needed to arrive at some answers.

Maybe the powers that be, on monitoring 144MHz (as they must surely do), have decided that standards need to rise. My own impressions on listening on that band in the London area are that there is definitely room for improvement. Perhaps some people did obtain their licences too easily in the early years of the multiple-choice paper. It is indeed sad that the antics of the idiot few make it harder for the rest of us. It was ever thus.

The major criticism I would level at the RAE is the lack of a practical test. Radio and electronics societies and clubs could be entrusted with a short practical test dealing with operating procedures and interference at a practical level.

Thank you for the years of entertaining and instructive enjoyment your magazine has given me. Also my thanks to Alan Sammons and the Barking Radio & Electronics Society for their excellent course.

J. F. Page
Dagenham

Letters

Sir: Re. Comment RAE October copy.

It seems to me that all budding Radio Amateurs want "it on a plate". When I took my RAE in 1961 there was no RAE Manual, etc., and we all had to rely on our instructors' notes.

The comment by one writer, "as it bore no relation to previous papers", seems odd to me. Does he want all the papers with the same questions on them?

It is no good going into the exam "half cocked" and in my area there was I think nearly 100 per cent pass rate. I do not think that our question papers were different to other parts of the country.

I may be old fashioned in my comment so I would like to hear from other amateurs within my own call sign area.

R. W. Howe G3PLB
Basildon

Sir: I note in October 1983 the poor and blatant cries of how hard the RAE is in its multi-choice answers. I took this type exam and passed first go without current trends in education, but hastily add that I am not brilliant as I had a gap from the ham radio scene for 15 years. I put my name down at the local tech. and sat the exam without tuition. I also add that I took the RAE of the 1960s and failed; in those "good old" days one had to explain how things worked. I would like to see this type of exam reappear and bring ham radio back to ham radio, fully into the meaning of it and not CB amateur radio. A hard earned thing would then not be abused and used with care and consideration for others. This would then sort out the genuine ham operators from the time wasters who take the exam and pass then operate, only to disappear after a few months.

E. F. Powell G6RGH
Cannock

Sir: I pen these words in an "off-operating" period during s.s.b. h.f. Field Day having just read the letters in October PW.

All your correspondents speak with one voice but are, I suspect, equally guilty of not studying the information, such as it is, put out from C & G concerning the detailed syllabus, which contains much important detail. It should be realised that to always set a question on a particular topic, or topics, would defeat the purpose of any examination.

As an RAE instructor and having written the paper in question for a blind candidate I can state that while there were some tortuous and poorly-worded questions there were enough questions on the basics to obtain pass grades at least.

Much has been written, and spoken, about the RAE over a good number of years and there are three points which rarely, if ever, seem to be raised.

First, the quality of the instructors. Just what experience of teaching, syllabus analysis, topic preparation and interrelation does the average instructor have? From what I hear many are keen amateurs doing their best to give a service in providing instruction for a difficult form of examination. Do they give help on examination technique? Do they spend, as some do, many hours on practical work, which while interesting is really irrelevant as far as this examination goes. Some courses turn out almost skilled electronics engineers instead of concentrating on the object of the examination—to ensure a very basic knowledge of the fundamentals.

Secondly, that *RAE Manual*. As a professional lecturer in Technical Education (but in a non-technical subject) I can state that in 30 years of experience I have never seen such an atrocious, ill-written and disorganised collection of pages purporting to be a text book. A perusal of who wrote it

reveals a bunch of experienced experts and as such in difficulty in writing anything for the many students who start the RAE with no knowledge. Like the curate's egg the manual has its better parts. It should be bought and put away in a drawer until the final fortnight before the examination—i.e. use it for revision and not learning.

The suggested reading list published in the *Manual* and in the Home Office booklet are about the worst things for today's average student to learn from. If these leave much to be desired then what can be used in their place?

There are now available on the market a whole range of texts published for the Technician Education Council (TEC) in Electronics and Radio Systems which cover in a much more readable and understandable manner much of the RAE syllabus (other than the licensing conditions of course).

I would suggest intending students would find the Electronics (Level I and Level II) and Radio Systems (Level II and Level III) of much greater use than the *Manual*—though this will be needed to cover some topics towards the end of the course. A number of authors have written books for the above levels and enquiries at the local technical bookshop or library would produce authors, publishers etc. My particular favourites are those by D. C. Green published by Pitman. Another useful publication is the ARRL book *Understanding Amateur Radio*.

Finally, despite the criticism heaped on every new style RAE exam, with questions cancelled, questions withdrawn, questions without correct answers, questions with two correct answers, three questions on the same topic, the answer to one question given in the next question, etc., etc., I would suggest people save their breath, for C & G are notorious in many subjects for messing things up. They have done this for many years and leopards don't change their spots. By the way, what does the RSGB Education Committee do? What do the RSGB members of the moderation board of C & G think about the exam?

As a final final, let intending students be prepared in their examination for about half a dozen "odd" questions. Don't be put off by them and remember the questions you did do and not the ones you couldn't do.

R. G. Wilson G4NZU
Nottingham

Sir: I was somewhat perplexed to read the comments in the letters section of PW regarding the May '83 RAE. May I suggest with respect that these individuals turn their attentions to the May '83 RAE results!! May I also say that buying an RAE Manual, etc., does not automatically constitute an RAE Pass, nor does it infer one. Whilst on the subject of the RAE, why is it that so many wives of licensed amateurs are sitting the RAE? Are they subscribing to the philosophy if you can't beat them join them? Or is it so their husbands can more easily justify the expenditure of large amounts of money on the acquisition of the latest all-singing, all-dancing Far East "wonder box"?

R. J. Howes
Weymouth

Sir: Having read your letters on the recent RAE exam, I am writing to say my husband took this exam in May. He did not take the course, nor have an electronics background, only reading *Radio Exam Manual* and a *Guide to Amateur Radio*. He managed to pass with credit on both papers. Reading some of your letters prompted me to write mine.

Mrs. E. A. McLachlan
Glasgow

Letters

Sir: In reply to the letter published in August *PW* regarding the RAE exam, I would like to make the following comments. I agree with your reader that there was a virtual absence of many major items, most noticeable of which was the main reactance and resonance formulae. Surprisingly there seemed very little requirement for the use of a calculator and the ability to remember and use important formulae.

In defence of the RAE, however, I do feel that there really are far too few questions in the second paper to enable full coverage in the exam. There is, as I found myself, a tendency when studying with the limited number of sample papers to become conditioned to expect that the exam paper will be a convenient blend of the two sample papers in the RAE manual. In fact there are major items absent from the sample papers as well. As with most exams, the biggest disappointment is always the absence of questions on the parts you know well.

At the time of writing this letter, I have not yet got my result, but I think there is scope for making the exam more comprehensive. If it has to be multiple choice then the second paper should be longer.

A final word to your reader: If they don't ask you what the formulae are you can't get them wrong!

*J. S. Hind
Nottingham*

Sir: I was interested in the letters about the RAE. A friend of mine, a G3, was asked if he would take an RAE class at the local school. In the first two exams he had 100 per cent pass rate and in the last RAE 4 failed. In the May RAE 70.5 per cent passed, some 5307. The letter writers are not yet to the standard to become radio amateurs.

We are always in danger of losing our frequency bands, and unskilled operators would add to this. When I took the RAE in 1968 I was able to draw a circuit diagram of a transmitter, receiver and Xtal type wavemeter with component values as you would be asked to draw part of all three.

I don't wish this to return, but amateurs have more freedom of the airways than any other services. I would like to keep it that way.

*John Tye G4BYV
Norfolk*

Sir: It is rare for me to write to any magazine readers' letters page. However, the deluge of complaint letters you published has stung me into action on this occasion!

It is obvious to me that all published writers were not only suffering from the post-examination blues but had failed to appreciate the full City & Guilds syllabus. G. L. Benbow's *Radio Amateurs Examination Manual* clearly and explicitly indicates the range of subjects that the aspiring candidate must cover.

I cannot help thinking that your writers' misgivings are misdirected! Instead of griping about the "City & Guilds having changed the rules", I think they should be challenging their Technical Colleges and Correspondence Courses for failing to enlighten them fully. I feel qualified to make such statements to you because last winter I too went through the pain and anguish of evening classes, trying to absorb the requisite information. However, the difference is that we were schooled correctly and briefed fully about the possible pitfalls of ambiguity in the questions and the necessity to

Practical Wireless, January 1984

cover the full syllabus including fringe questions. Result?—Ten of us enrolled for this May's exam and ten of us now have City & Guilds pass certificates, many with credits, and incidentally none of us had any previous electronics experience.

So writers, there is nothing wrong with the system, it is how you have been taught that is your real bone of contention. How many of you were taught by an electronics lecturer and how many of you had a Radio Amateur who had himself sat the current multi-choice paper? How many of you, I wonder, spent the time between exam and results worrying and moaning about the so-called "unfairness" of Paper II, now find themselves not having to resit Paper II this December but Paper I!

*Tim Cattley G6YUW
Oswestry*

PW Mast Review

Sir: As a result of the *PW* March 1983 review of the Altron SM30 mast, several customers have queried the method of operating the winch when lowering the mast. I hope the following may clarify the situation.

As an added safety measure, the standard ratchet winch normally supplied with the Altron SM30 slimline mast is modified by Allweld in a unique way to enable the ratchet to function as a failsafe stop in the event of an accidental runaway, such as can occur if the handle of the winch is let go under certain load conditions. This can happen on any standard type of ratchet winch that is not auto-braked. As far as we know, Allweld are the only firm currently doing this simple but effective modification, which involves fitting a stop-screw to prevent the ratchet pawl latching in the "off" position.

As the modified ratchet must be held off during winch-down operations, a little inconvenience can be experienced during the first part of the tilt-over on a post-mounted SM30, when the mast has to be started moving. A simple solution, as mentioned in the review, is to wedge a short piece of wood between the post and the mast to form a kick-bar, leaving both hands safely free to operate the winch. We feel this small inconvenience is not a high price to pay for the additional safety in operation resulting from this Allweld idea. We could of course weld on a kick-bar, but this could result in more barked shins than it would be worth. However, we are working on the idea and hope we may come up with another Allweld innovation.


As an extra-cost option, we can supply auto-brake winches if required.

*A. Barraclough
Allweld Engineering*

Advice Wanted

Sir: I would like to hear from any reader who has purchased and operated scanner sets. All letters will be answered.

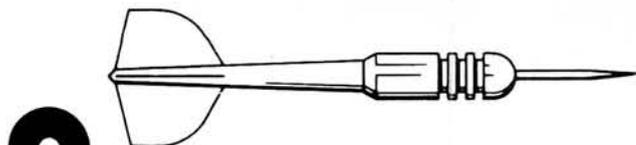
*Anthony Chaffe,
58 The Croft,
Halton Brow,
Runcorn,
Cheshire.*



PW DART

TOP BAND CONVERTER

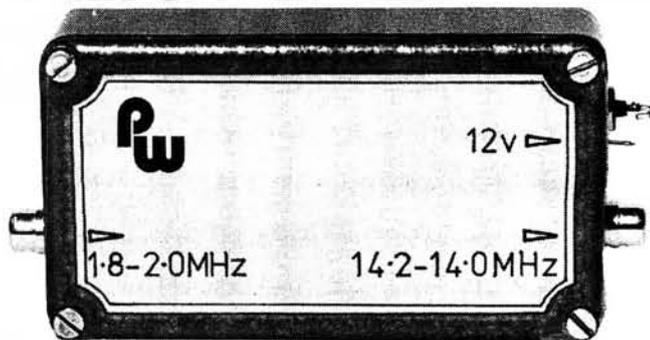by Rev G.C. Dobbs G3RJV & Colin Turner G3VTT



The *PW Dart* d.s.b.s.c./c.w. transmitter described in the November and December 1983 issues provides an ideal way to get onto the 1.81–2.0MHz amateur band at little cost. The circuit is perhaps most appealing to those who do not have facilities for that band. Many recent transceivers have omitted “Top Band” so the *PW Dart*, in conjunction with a suitable receiver, can fill in that gap.

It may be that if Top Band is missing from a station transceiver the station could have no receiving facilities for the band. An obvious way to overcome this problem is to build a receive converter to enable the band to be received on one of the more common amateur bands. What follows in this article is a simple up-converter design which can be bolted onto the back of the *PW Dart* transmitter to enable it to be used in conjunction with a transceiver or receiver which can tune 14MHz, to provide full transceiver facilities for the complete 1.8 to 2.0MHz band. The converter could be built as a small project in its own right to enable Top Band coverage to be added to any station receiver that tunes 14MHz.

Choice of IF

There are a few obvious problems in converting a signal from Top Band to another amateur band. For a start 1.8MHz is uncomfortably near to the medium wave a.m. broadcast band, with a variety of strong stations all waiting to break through on the input. Then there is the problem of breakthrough from existing signals on the amateur band selected as the conversion frequency.

On a dusty back shelf in my shack I have a converter from some years ago built to give me Top Band capability using the 7MHz band as the conversion band. A friendly little unit because if things are quiet on Top Band I can always listen to the local medium wave commercial station or to one of the broadcast stations encroaching into the 7MHz band in the evenings. Plainly a circuit to be avoided!

Another problem is finding a suitable crystal to form the local oscillator (l.o.) frequency for the conversion. Crystals can be etched to order on any suitable frequency but the cost is considerable and rather detracts from the inexpensive approach used in the *PW Dart* transmitter. A prototype was attempted using 27MHz radio control crystals, converting the band up to 29MHz. This works quite well but many receivers can be insensitive at these higher frequencies. The final conversion frequency was decided after noticing an advertisement in the back of *PW* from P. R. Golledge Electronics for “off the shelf” 16MHz fundamental crystals at £3.35 including VAT and postage.

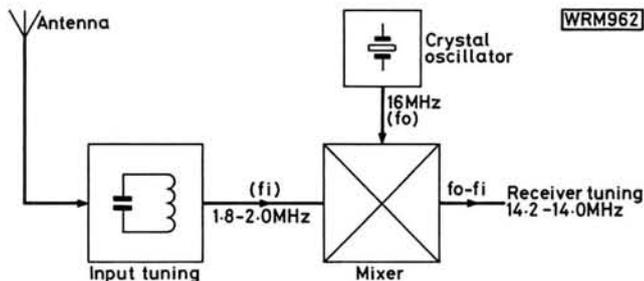


Fig. 1: Block schematic of the *PW Dart* 1.8MHz receive converter

Circuit Design

The approach adopted is shown in block form in Fig. 1. This is the classical simple receive conversion circuit. The required band (1.81 to 2.0MHz in Region 1) is tuned at the input and fed into a mixer stage. A 16MHz crystal provides the frequency for the local oscillator, which is also fed into the mixer. The frequency required at the output is the input frequency (fi) minus the oscillator frequency (fo). This produces the conversion from 1.8 to 2.0MHz as 14.2 to 14.0MHz—reverse tuned on the 14MHz amateur band. The s.s.b. stations on Top Band would normally use the opposite sideband to those on the 14MHz band so the reverse tuning is quite useful in that the sideband switch can be used in its “normal” (u.s.b.) position.

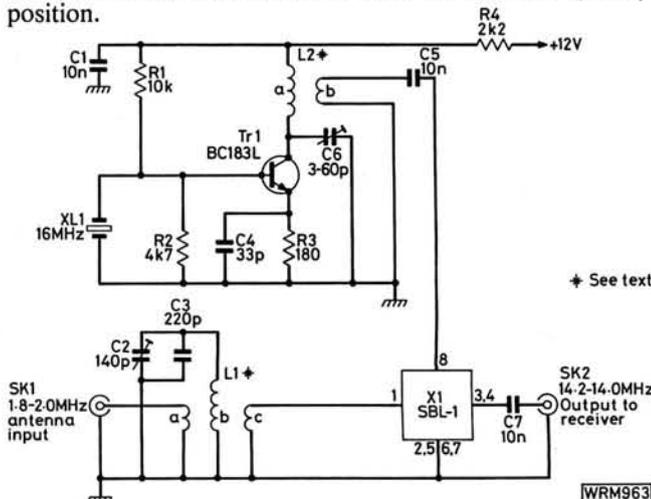


Fig. 2: Complete circuit diagram of the converter which will provide 1.8MHz band coverage when used in conjunction with a 14MHz receiver


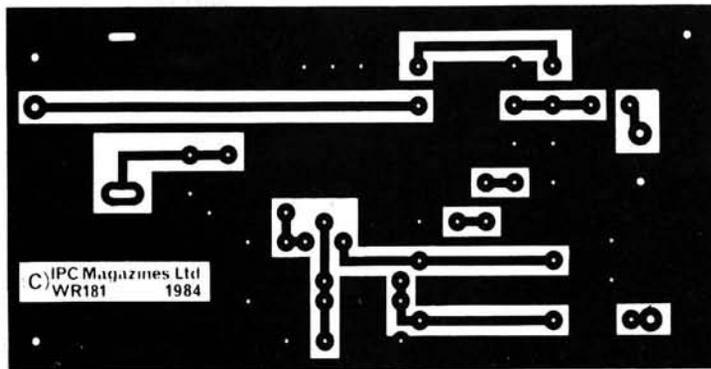


Fig. 3: Full size p.c.b. and component placement details. Pin 2 of the mixer X1 is located beneath the letter M of the part identification

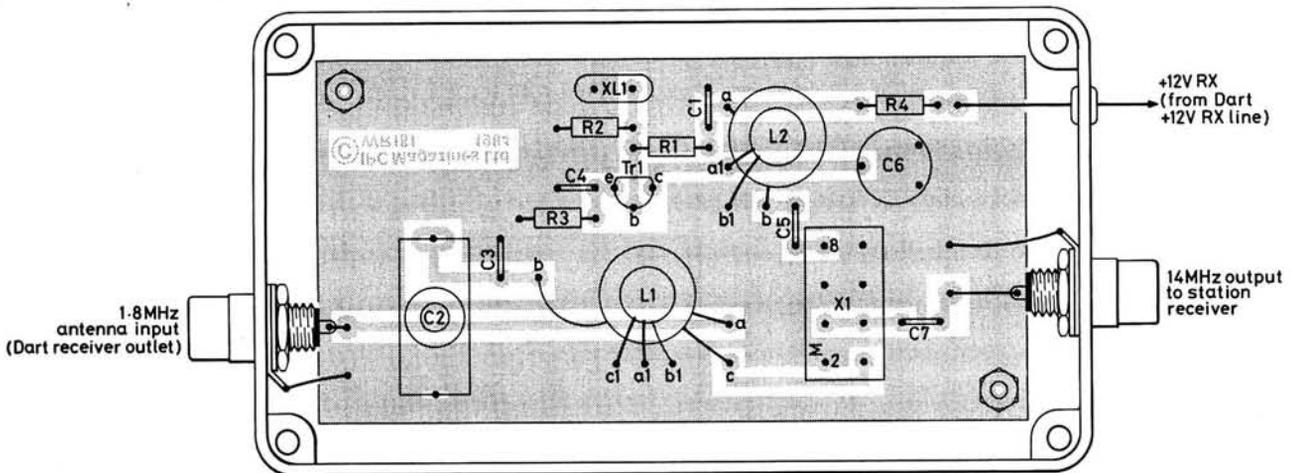

★ components

Resistors

Carbon film $\frac{1}{4}$ W 5%

180 Ω	1	R3
2.2k Ω	1	R4
4.7k Ω	1	R2
10k Ω	1	R1

Capacitors

Miniature Plate Ceramic

33pF	1	C4
220pF	1	C3
10nF	1	C5

Miniature Ceramic

10nF	2	C1,C7
------	---	-------

Compression Trimmer

140pF	1	C2
-------	---	----

Miniature Film Trimmer

3-60pF	1	C6
--------	---	----

Semiconductors

Transistors

BC183L	1	Tr1
--------	---	-----

Miscellaneous

SBL-1, double balanced mixer (1); 16MHz crystal HC18/U; phono sockets (2); feedthrough capacitor (see text); diecast aluminium box 110 x 60 x 30mm (see buying box); p.c.b.; T-50-2 toroid (1); T-50-6 toroid (1)

The full circuit diagram is shown in Fig. 2. Like the *PW* Dart, the circuitry is very simple. The mixing is done using a double balanced mixer type SBL-1. This is not a cheap device but it offers obvious advantages in this simple circuit. Being a high level mixer problems with cross modulation and adjacent channel interference are minimised. So much so that one preset tuned circuit ahead of the mixer was found to be sufficient against the ravages of the evening a.m. stations close to 1.8MHz. The balancing within the device is very "tight" and if adequate screening is used

BUYING GUIDE

Components for this project are readily available. An alternative housing is the Miniford A8 box. The prototype used a 16MHz HC18/U crystal from P.R. Golledge Electronics.

Approximate
Cost

£15

Construction
Rating

INTERMEDIATE

between the input and output ports and the i.o. the susceptibility to spurious signals is very low. Originally a tuned circuit or filter for the output was considered but in practice this made no difference. The output port is a well matched 50 ohms which can be fed directly, via C7, into the input of a receiver on 14MHz. The SBL-1 is a passive mixer so there is no conversion gain but on Top Band front end gain is of little importance. Who wants to amplify a lot of noise!

The input tuned circuit around L1 was found to be sufficient for the needs of the circuit. A two stage filter was considered, as was an externally adjustable input filter but this simple arrangement works well without problems of adjacent channel breakthrough. Setting C2 to peak signals in the centre of the band serves well for the whole band without need for retrimming. However, the fastidious could make C2 into a variable panel control if they so wish. The winding for L1b, which consists of 63 turns of 32 s.w.g. enamelled copper wire, occupies the whole of the T-50-2 toroid core. Inductors L1a and L1c, both comprising 5 turns of 26 s.w.g., are wound onto the grounded end of L1b. In practice the easiest way to do this is to take two lengths of wire and wind both L1a and L1c side by side onto the core in one action.

The oscillator circuit around Tr1 is very simple and should fire-up first time without problems. A whole range of transistors might be used for Tr1 but the BC183L is as cheap as most commonly available types. Inductor L2a tunes the 16MHz i.o. signal, in conjunction with C6, and L2b provides a low impedance output for the mixer. The two windings are mounted on a T-50-6 toroid, L2a being 16 turns and L2b 3 turns, both of 26 s.w.g. wire. When the oscillator stage is built it is best tested on its own before connection is made through capacitor C5 to the SBL-1.

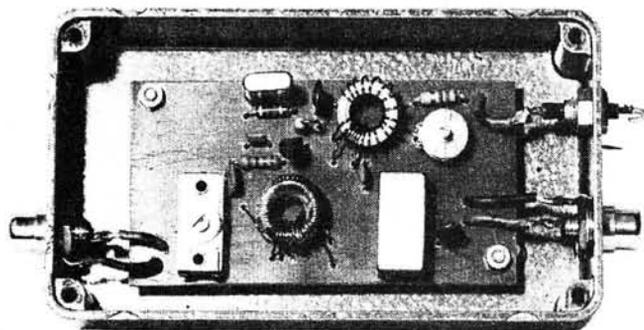


Fig. 4: A photograph of the author's prototype converter

A simple r.f. diode probe may be connected onto the output from L2a and a reading taken on a voltmeter. Passive mixers require quite a bit of drive—over half a volt is advised—so the output from L2a should read in the order of 1 to 1.5 volts (peak r.f.). This will be somewhat less when the output is loaded into the SBL-1. Crystal oscillators are perky little things and capable of much higher outputs than required here. If the output is too high, or under 0.5 volts, adjustment can be made to the value of R4.

A single printed circuit board accommodates the complete converter, as shown in Fig. 3. The board retains a large amount of copper to act as a screen mat which helps the isolation between the ports of the SBL-1. All components are standard types and easy to obtain. The assembled board was mounted into a diecast box measuring 110 x 60 x 30mm. This box happened to be to hand but a much cheaper alternative is the Minfordd A8 Box. Either will bolt directly onto the back of the *PW* Dart transmitter case. The input and output terminations are inexpensive phono sockets and a 1nF leadthrough capacitor takes the 12 volt d.c. supply into the box.

System Connection

The converter is a useful little unit to put ahead of any receiver that lacks Top Band but has 14MHz coverage. If it is to be used with the *PW* Dart, the method of connection is shown in Fig. 3. The Dart changeover board provides for a "receiver" output and a 12 volt d.c. line on receive (12VRX). The receiver line already comes out of the back of the case and can be fed into the converter input. The converter output goes to an existing station receiver on 14MHz. A leadthrough added to the back of the Dart case is probably the best way of getting the 12 volt line to the converter. The converter can now be used with the *PW* Dart and a receiver. Antenna changeover functions are provided within the Dart circuitry so once the converter has been peaked up using C2 it is merely left in place on the back of the transmitter case.

Armed with the *PW* Dart transmitter and this converter it is possible to get onto Top Band at little cost and with the added pleasure of making worthwhile contacts with homebuilt equipment. ●

Swap Spot

Have Harrier CBX radio, s.w.r./power meter, Sigma II antenna, halfbreed antennas. Would exchange for linear for Standard C-58 or w.h.y. Jeff Brown. Tel: 01-637 6270 T574

Have BSA Bantam D14 motorcycle (non-runner). Would exchange for any 144MHz or 28/29MHz gear, w.h.y. Tel: Basil G6VAN 0642 66869 (Cleveland). T577

Have 3½in screw cutting lathe with motor, some change wheels and accessories. Would exchange for 144MHz/432MHz hand held or base equipment, v.h.f. scanner or h.f. w.h.y. Tel: 051-645 5383 after 6.30pm (Birkenhead). T591

Have S registration Vee twin 350cc Morini motorcycle. Would exchange for h.f. receiver, FRG-7700, R1000 or w.h.y. Tony G3YSQ. Tel: West Hanney 386. T592

Have FT-290R mint condition. Would exchange for TS700G. Tel: G4TBM Lewes (Sussex) 6099. T598

Have FT-200 h.f. transceiver, 28MHz-3.5MHz with matching p.s.u.. Would exchange for TS700G. Tel: G8JDF Lewes (Sussex) 78080. T599

Have Spectrum 48K computer, plus ZX Printer and Sony cassette recorder. Also programmable joystick and interface and software worth £100. Total cost over £300. Would exchange for Yaesu FT-290R or Standard C-58 or similar. Tel: 041-637 0808 (Glasgow). T714

Have amusement arcade Space Invaders machine would exchange for h.f. receiver or FC-902 a.t.u. Karl. Tel: 01-575 0090 (Greenford, Middx.). T639

Have Quad f.m. 188MHz Tuner plus 3-waveband tuner all valve sets. Would exchange for w.h.y. J. F. Riley, 51 Leeswood, Ashurst, Skelmersdale. Tel: 33304. T637

Have Super 8-Sound Projector and Cine Camera. Would exchange for h.f. receiver 0-30MHz valve or solid state. Tel: 23638 (Coatbridge). T638

RADIO SHACK'S LATEST GOODIES



"The Oldest Name In Amateur Radio"

NEW



BRASS RACER IAMBIC

The newest addition to the Vibroplex family - the Brass Racer Iambic - A distinctive new design of Iambic paddle crafted from solid brass and mounted on a base of polished hardwood. No springs to fly off the middle of a contact. Superior Vibroplex quality. Always worth the difference and now a new Vibroplex look.



£66.50

NEW



BRASS RACER EK-1

An even more exciting step is the new Brass Racer EK-1, an electronic keyer built into the base of our new Brass Racer Iambic paddle. Using the Curtis 8044 chip, this self-contained keyer and paddle is fully Iambic with dot/dash insertion and adjustable speed control. Use on either tube or solid state rigs. The perfect unit for mobile, DXpedition, or just plain fun.



£98.98

THE IAMBIC

The distinctive look and quality of the Vibroplex Original is fashioned into the finest Iambic paddle anywhere. The dual paddles allows the operator to utilize automatic dot/dash insertion and other unique features of the modern electronic keyer. Vibroplex distinction for the modern operator.



Deluxe £62.18
Standard £49.19

THE VIBROKEYER

The Vibrokeyer is designed for "Bug" operators who want to move to electronic keyers without relearning keying. The single lever paddle initiates the automatic dots and dashes of the electronic keyer with the same motion used to operate the "Bug". For those who want to combine traditional skill with modern electronics.



Deluxe £62.18
Standard £49.19

THE ORIGINAL

In 1890 Horace Martin Searched for relief from the "glass arm" telegraph operators were getting from pounding the straight keys. His answer, the Vibroplex Original was an instant success. The vibrating lever bar automatically produces dots while dashes are made manually. Still popular today, the distinctive sound of the "Bug" can still be heard. It is the signature of the true C.W. expert.



Presentation £115.00
Deluxe £66.50
Standard £53.19

All of our keys are available in Standard and Deluxe models. The Original and the Iambic are also available in the Presentation models.

Standard Model: All Standard models come with a neat, crisp, textured, painted base with polished and chromed top parts. Attention to detail in the finishing process gives Vibroplex an unexcelled quality appearance. Highly conductive large coin-silver contacts provide a clear, sharp signal, and non-skid rubber feet keep the keyer in its place.

Deluxe Model: All Deluxe models feature a chromed base, buffed and polished to a mirror finish. As in fine watches and other precision instruments, their jewelled movement serves to prolong life, maintain smoother, easier operation and prevent binding.

Presentation Model: The Presentation model is the top of the line at the top. Available in the Original and Iambic, the Presentation features 24 carat gold-plated base top, engraved with name and call and makes a truly personal gift. The Original has the adjustable super speed control main spring for a wider range of sending speeds.

BEARCAT SCANNERS

BC-100FB £345.00

Hand held 16 channel programmable



BC-20/20FB
(with air band)



40 Channels
AM/FM
£258.75

COLLINS KWM-380 Transceiver



£2199


DRAKE R7A



General Coverage Receiver
£1069.50

BENCHER PADDLES

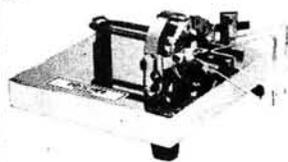- BY-1 Black Base £37.95
- BY-2 Chrome Base £48.30
- BY-3 Gold plated £92.00
- ZA-1A Balun £15.00
- ZA-2A Balun £17.25
- ZY-2 CW Audio Filter £57.50



TRIO - YAESU - ICOM
FDK - KDK - DATONG - HUSTLER
SHURE - ASTATIC - Hy-GAIN
TELEX - MICROWAVE MODULES
HAL - DAVTREND - AVANTI and
EVERYTHING ELSE IN AMATEUR RADIO



RADIO SHACK LTD

188 BROADHURST GARDENS,
LONDON NW6 3AY

(Just around the corner from West Hampstead Station on the Jubilee Line)

Giro Account No. 588 7151 Telephone 01-624 7174 Telex: 23718



Setting up a station?

AR2001



- * CONTINUOUS COVERAGE FROM 25-550MHz WITHOUT GAPS
- * 3 switchable modes - AM, FM wide & FM narrow
- * Lcd display shows frequency, mode & memory channel
- * Memory channels store frequency & mode
- * Full range of scan facilities
- * Typical sensitivity of 0.2µV for 12dB SINAD across the entire range

PROVISIONAL PRICE £298

Consult the professionals

You'll find all you need at Photo Acoustics. We can offer help and advice, the chance to try out the gear and financial facilities too. We offer Creditcharge Instant Finance and accept Access and Barclaycard. Part exchange welcome.

Four minutes from the M1 Exit Junc. 14. Head for the High St. Newport Pagnell. We're at No. 58. Parking at rear, opposite, or round the corner in Silver St.

We also stock a comprehensive range of rotators - Microwave Modules - BNOS - DRAE - Welz & Daiwa products

The Season's Greetings

Derek G3TGE-Roy G3TLE
Kerry G6IZF



TS 430S



A truly superb HF transceiver from Trio, incorporating a very sensitive general coverage receiver

£736

NOW IN STOCK

The matching auto - a.t.u. - the AT250

£273

Photo Acoustics Ltd.
OF NEWPORT PAGNELL



WE STOCK PARTS OTHER STORES CANNOT REACH!



We stock a vast selection of electronic components. Just take a look through our new illustrated catalogue and you'll see what we mean. Send for your copy today. Official orders welcome from Govt Depts, schools etc. Quantity discounts negotiable.

**CRICKLEWOOD
ELECTRONICS
LIMITED**

40 Cricklewood Broadway
NW2 3ET
Telephone: 01-452 0161 Telex: 914977

only
£1.00
inc. p & p

Please allow 28 days for delivery

AVCOMM LIMITED

25 Northold Street, Glastonbury, Somerset BA6 9HB.
Tel: 0458 33145 Shop open: 9.30am - 5.30pm, MON - SAT

- BF 981 Low noise MOSFET, 85p.
 - 3SK97 UHF GASFET, £3.
 - H.P. 5082.2800 Schottky diodes, 60p.
 - H.P. 5082.2396 Schottky diode mixers, £2.50.
 - 1N4148 Diodes, 3p each, 20p/10. £1/100.
 - BA182 PIN Diodes, 35p.
 - 7805 & 7812 Regulators, 45p.
 - 7905 & 7912 Regulators, 75p.
 - 741, 748, LM358 & MC1458CP op amps, 20p.
 - SN74LS374N, SN74123PC, 30p, SN75492AN, 40p.
 - TC5504AP-2 4096 x 1 Bit CMOS RAM, 85p.
 - AY-3-9400 Tone generator IC, £1.
 - 125µF 350V pcb mntg electrolytics, 50p or £4/10.
 - 60µF 450V Electrolytics, 50p or £4/10.
 - New pcb with Siemens DL1416 intelligent Alphanumeric displays, £1.
 - VARTA 4.8V 170mA pcb mntg nicads, £1.50.
 - Miniature ELECTRET mic inserts, 1.5V type, 8mm dia., 35p.
 - 1000pf & 2000pf 500V bolt in feedthroughs, 35p.
 - Miniature toggle switches: DPDT, 50p. SPDT, 45p. All 2A 250V AC types.
- Postage 40p on orders up to £10, over post free. Prices Exclude VAT @ 15%.
Our latest lists contain many bargains too numerous to advertise, to obtain a copy please send a large S.A.E. All goods sent by return.

Do you know what time it is!

When the globe of this digital clock is revolved, a red lamp indicating a major city in the world will blink, and the current time of that city will be displayed. At a glance know the current times of 24 different time zones. This mini-globe clock stands 195mm high and also has an alarm fitted. This useful device should stop you getting your Amateur friends, on the other side of the world, out of bed in the middle of the night.

Thanet Electronics 143 Reculver Road, Herne Bay, Kent
Tel: (02273) 63859/63850



£59

DW REVIEW

Datong Model ANF Auto-notch Filter

The Datong Model ANF is a compact, light-weight unit (150 x 90 x 42mm and 400g) which provides automatic or manual notching of interfering whistles and heterodynes, or manual peak filtering of c.w. signals.

It is simply connected to the external loudspeaker or headphone socket of a receiver using the lead provided, and has output sockets for a loudspeaker of 3Ω impedance or greater (a 2 watt audio amplifier is incorporated) or headphones.

The unit is controlled by four push-buttons and a manual tuning knob, and there is an i.e.d. indicator showing that the automatic notch filter is locked onto an interfering heterodyne, plus a bargraph i.e.d. display of notch or peak tuned frequency.

Operating the Model ANF is simplicity itself. The User Instruction sheets recommend that the unit is left permanently connected and operating in the auto-notch mode. In the absence of a steady interference note, the notch will sweep up and down the range 270-3500Hz, but will be quite inaudible because it is so narrow. As soon as a whistle or heterodyne appears, from an anti-social "tuner-upper" or whatever, the notch will lock onto the

offending signal, typically within one second, effectively removing it from the output of the unit.

The effectiveness of the unit can be checked by pressing NOTCH and PEAK buttons together, putting the filter into the "bypass" mode. The notch depth on the review unit was measured at better than 34dB across the whole range.

If more than one interfering tone is present at the same time, the filter will lock onto the first one it encounters in its sweep, and this may not be the most annoying one. In such cases, it is better to select the MANUAL mode and tune the notch using the manual tuning


knob. It is only necessary to get within 100Hz of the tone, a narrow-band a.f.c. system then takes over and fine-tunes the notch for maximum depth. This feature makes operation very easy.

For Morse code reception, the MANUAL PEAK mode turns the Model ANF into a high-quality c.w. filter, tunable to your favourite beat-note by means of the manual tuning knob, with operating frequency indicated by the bargraph i.e.d. display. The peak bandwidth on the review unit was measured at around 56Hz at -3dB points and 500Hz at -30dB points, with an ultimate rejection of better than 50dB.

Power requirements for the Model ANF are 11-18V d.c. with a measured consumption of 60mA at 13.2V. The supply need not be stabilised. The 4-page User Instructions give comprehensive operating advice, plus adjustment details for internal presets for Lock Threshold, Tuning Limits and Notch Depth. The unit is built on two p.c.b.s joined by ribbon-cable links, and constructed to the usual high Datong standard.

The Model ANF is priced at £67.85 including post, packing and VAT from **Datong Electronics Limited, Spence Mills, Mill Lane, Bramley, Leeds LS13 3HE, telephone 0532-552461**, to whom go our thanks for the loan of the review model, or from Datong dealers.

Geoff Arnold

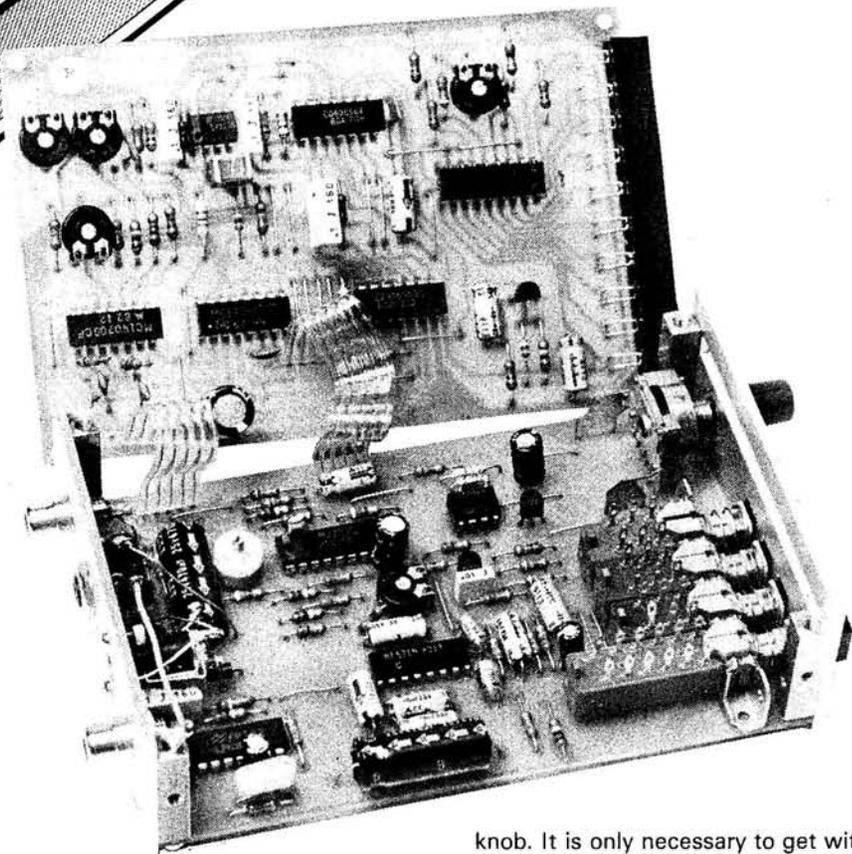

HF ANTENNA SPECIAL

Two Band Mini-X Beam

F. C. Smith GW2DDX

The mini "X" beam for 10 metres published in the March 1982 issue of *Practical Wireless* gave the author excellent results on the 28MHz band, even when used indoors.

It was to be regretted that good though this little beam was, it only covered the single band. Further thought was given as to how to make the excellent features of the "X" configuration into a more versatile dual-band antenna covering both 28 and 21MHz (15m), while still retaining its space saving utility. Accordingly, it was decided to make the "X" with 1.8m bamboo cane spreaders, thus making the external dimensions 2.438m x 2.438m, which still allows the antenna to be used indoors as well as outside. With the other simple modifications to the original design shown in Fig. 1, dual band operation is achieved.

Construction

As with the single band version, 300 ohm ribbon feeder is used for the elements, as this provides a broader bandwidth with the electrically shortened elements used on 21MHz (it will be noted that on 28MHz the elements are not shortened). Each section of the antenna is formed from 1.676m of ribbon feeder which is run along each cane and

then taped. The remaining outer section lengths of ribbon for both the driven element and reflector are folded over and held together with non-conductive cord.

The driven element is resonated at 28.2MHz with a grid dip oscillator (g.d.o.) and the reflector at five per cent lower in frequency, following conventional Yagi practice. That takes care of the 28MHz band requirements. The next procedure is to get the beam on to 21MHz.

After some thought it was decided that the best way to proceed would be to coil load the driven and reflector elements in a similar manner to the original "X" beam and insert $\lambda/4$ stubs to provide band switching.

Appropriate size coils are fitted to the centre of the elements and once again adjusted in conjunction with a g.d.o. to 21.3MHz, with the reflector a further five per cent lower in frequency. Care should be taken with these adjustments to ensure the best performance of the assembled beam. Two additional $\lambda/4$ pieces of 300 ohm ribbon feeder are then brought to resonance at 28.5MHz (these worked out at 1.625m in length on the author's prototype) and are then fitted across the coil sections. As these sections of cable are not part of the radiating system proper they can then be rolled up and secured to the centre board.

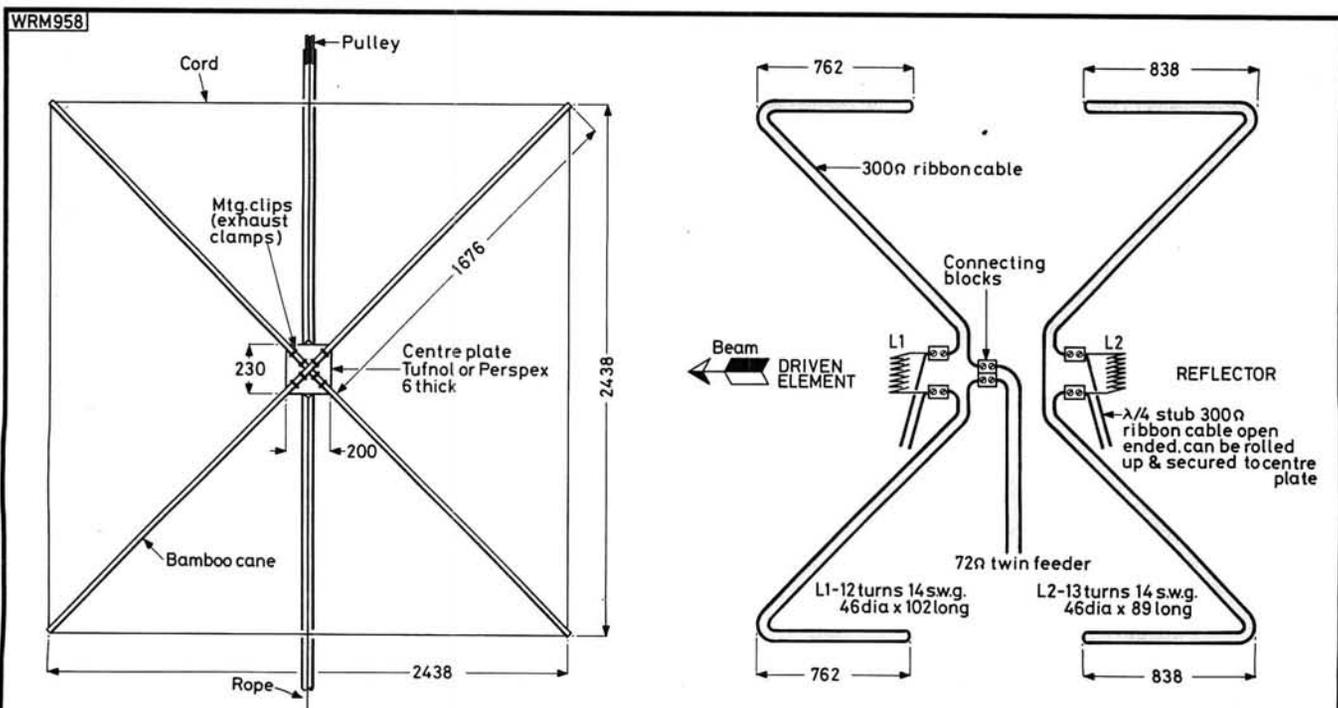


Fig. 1: Constructional details. The mechanical supporting structure is shown (above left) together with the associated element details. The folded-back ends of the 300 Ω ribbon can be drilled and held in alignment using non-conductive nylon cord. A 10m high mast is used by the author with the centre plate of the antenna retained by sliding rings. Beam heading can be changed from ground level by the addition of a rope tied off to the driven element. If used outdoors the loading coils and feeder connections must be weather proofed

The antenna now covers the two bands. When operating on 28MHz the $\lambda/4$ stubs short out the 21MHz coils, allowing the beam to be resonant on that band. This method is a quite effective and efficient means of automatically switching bands.

Since its construction the performance of the beam has given the author every satisfaction, on both 21 and 28MHz, and can be recommended to those who have little space for a full size beam. The total weight of the mini "X" beam is just over 1.5kg and it can be used in both the horizontal or vertical modes. Do not forget to treat the canes with a coat of paint or varnish to prevent weathering

effects. The estimated gain of the antenna should be approximately 5dB.

The 72 ohm twin feed line from the antenna driven element is connected to the transceiver via an a.t.u. having balanced input terminals and an output arrangement which is either balanced or coaxial as appropriate. In the author's case the a.t.u. is constructed from two 140pF variable capacitors, in series with the feeder conductors, connecting to each end of a six turn, 75mm diameter and 32mm long coil. The transceiver is coupled to this coil via a centrally placed two turn, 75mm diameter link coil which is 10mm long. ●

Kite Antennas For Top Band

P. Painting G3OUC

Of all the frequencies allocated to Radio Amateurs 1.8MHz (160m) is without doubt the best for the ease of construction of home built equipment. It is however unfortunately the case that for good results on "Top Band" considerable space is required on which an effective antenna system can be erected.

My garden is very small so I have constructed a 14m high centre loaded vertical antenna for this band. I have found that compared with a 40m long quarter wavelength antenna my own installation is inferior to some degree. Because of this situation, and having a fondness for 1.8MHz and the operators thereon, I frequently use the mobile or portable modes of operation using home constructed equipment, mostly amplitude modulated and simple in concept. Since my schooldays I have also had a keen interest in making and flying kites of all types so when I obtained my Amateur Radio licence in 1969 it was logical to combine the two hobbies and to use a kite as an antenna support on 1.8MHz.

Today with solid state equipment I am still getting a great deal of enjoyment, fresh air and plenty of interesting contacts whilst using the 20-year-old box kite to support a suitable length of wire. I have often been asked "over the air" to describe the equipment and antenna system; it is to those who wish to try this interesting and often effective method of stirring up activity on 1.8MHz that this article is dedicated.

Kite and Antenna Construction

You could say that I had a distinct advantage by using the ex-RAF air sea rescue type box kite and its associated antenna wire. It is possible that these excellent kites are still obtainable, however, I know of no source of supply.

This particular kite is perfect for portable use being both sturdy in construction and stable in a range of windspeeds from 30-70km per hour. Its design enables it to be dismantled and folded into a very small space. The struts are of duralumin and the sail material cotton. The antenna wire originally used with this kite was either stainless steel or phosphor bronze tinsel plaited with silk or nylon for strength and light weight. However, any stable kite capable of supporting the antenna wire will be suitable for the purpose, providing it falls within the specification laid out in the Air Traffic Control Regulations (see end of

article for kite flying regulations). The major consideration is that of lifting the antenna wire plus a suitable safety line, therefore the larger the kite the better, providing the weight does not exceed the legal limit of 2kg.

At this juncture may I point out that kites of the "stunter" or aerobic type are useless for antenna support. What is required is a steady stable system capable of flying whilst anchored down for as long as the operator wishes or whilst the wind blows favourably. Having to keep maintaining an eye on the kite or to rush about attending to things will not make you very popular whilst holding a QSO with a distant station—calling CQ only to have the kite descend as you receive a reply is no fun either! To ensure that all will be well when the great day comes it is important to get to know your kite and have a number of test flights in varying weather conditions so that the pitfalls previously mentioned do not occur.

The length of antenna wire I use is approximately 60m. This can be of 24 or 26 s.w.g. enamelled copper wire stripped from an old transformer, choke or solenoid. Aluminium alloy type wire sold by garden centres or horticultural stores is also very good. A further source suitable for large kites is electric fencing nylon/copper twisted cord obtainable from agricultural merchants;

WRM961

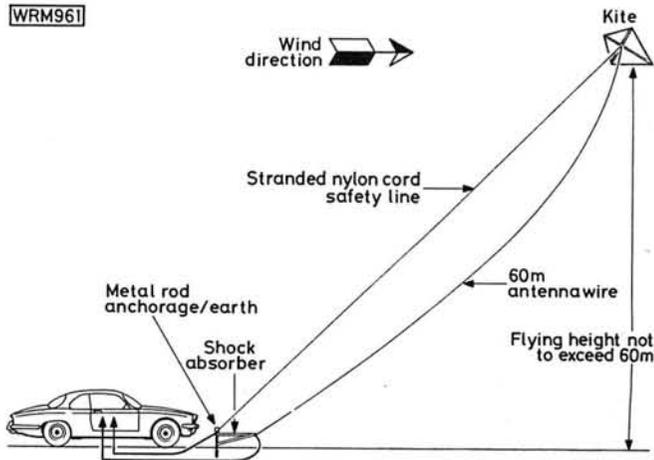


Fig. 1: The basic layout of the Kite supported antenna system discussed in the text

however, this cord is not cheap and for the one off portable foray the single strand enamelled wire will suffice. If more than a few flights a year are planned it is useful to have a winding reel to prevent the antenna wire being kinked or becoming a "bird's nest". If single strand wire is kinked or knotted it will eventually break so discard such damaged wire.


The antenna wire does not take the main pull of the kite. This can amount to several times the normal breaking strain of 26 s.w.g. copper wire. Even if the wire seems strong enough initially any slight kinks will eventually result in the wire snapping and/or prolonged use will stretch the wire to eventual failure. To prevent the antenna wire being broken, I use a safety line of nylon cord to take the strain. This should be capable of holding the kite in any "normal" wind. Further to this, if the antenna wire breaks the whole system can be brought down to terra firma safely on the main line. Although I use nylon stranded cord, any other strong rot-proof line will do provided it is not monofilament fishing line. The elasticity of such line precludes its use for this purpose.

At the ground end termination of the antenna and main support line it is wise to incorporate a rubber or elastic shock absorber to take up sudden stress due to wind variations etc. This shock absorber can be obtained from motor cycle shops where it is sold for holding equipment or panniers onto motor cycles, consisting of a length of rubber covered with fibre with two hooks, one at each end. Once the kite is flying at the required height it may be anchored by the hook end of the shock absorber to a secure point as close to the radio equipment as possible. A metal rod can be used for this support and it may also be used as an earth rod if required. Other anchor points may be convenient: trees, bushes, fence posts or large rocks, provided they are substantial enough to take the strain. Care should be taken not to cause damage when using such "natural" anchoring points.

Safety & Site Considerations

It may be opportune to raise a few points about safety at this juncture. Although my portable activities usually take place well away from built up areas, in fact the nearest buildings are about 5km away, there are always people, horses and sometimes vehicles in the vicinity, all of which can be a problem and should at all times be treated with due consideration.

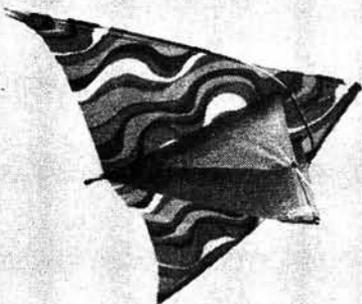It would be both foolhardy and extremely dangerous to set up a portable radio station using a kite supported antenna adjacent to power transmission lines or other types of overhead cables. If the kite broke free it could be carried by the wind across live conductors thereby energising the broken antenna wire.



The Twin Keeled Delta kite which is suitable for antenna support is available from Cochranes of Oxford Ltd., Leafield, Oxford OX8 5NT, Tel. 099 387 641

Other situations to avoid are damage to property and crops by using an ill-chosen site. Remember that the higher a kite flies, the further it will have to travel before it comes down. If the lines break, ensure that there is plenty of room for a safe descent, and that the kite can be retrieved without encroaching on private property.

During the summer months thunderstorms can build up quite rapidly. **On no account should the kite be used during such conditions.** Fortunately there are several indications of electrical storms long before they are within the area. As well as the daily weather forecast it is possible to obtain quite a good idea of suitable thunder-free conditions by listening on a medium wave broadcast band receiver. If electrical discharge interference can be heard this can indicate the presence of thunderstorms within 160km of the receiver. The 1.8MHz station receiver itself is also useful for this check; as the receiver frequency is raised towards 30MHz, the distance over which lightning discharge interference can be detected decreases. At 28MHz it seems to be approximately 30km on the author's mobile transceiver.

Visual indications of unsafe conditions are large dark clouds, flat at the base and towering to high altitudes, sometimes changing shape rapidly (cumulonimbus) together with hail or heavy rain squalls. Clouds such as these tinged with yellow are particularly good indications of bad conditions. On observing such approaching storm clouds or hearing static discharge interference (QRN) on the receiver it is prudent to discontinue operating and close down the portable station. It should be noted that thunderstorms can occur at any time of the year given the right conditions.

When vacating a portable site make sure that all rubbish, especially bits of wire or string, are removed as such things can be harmful to wildlife or livestock.

At this stage you may wonder if it is worthwhile proceeding further. I will just say that the previous information is a guide to proper portable field operating using a kite supported antenna. Provided care is taken there is no reason why you should not achieve success with safety.

Selection of Suitable Sites

At first site selection may seem a major problem; however, an Ordnance Survey map of the locality will often reveal open spaces where it is possible to set up a portable amateur radio station without causing annoyance to others. Most radio societies have known portable sites where field day operation takes place or where farmers/landowners are personal friends. Ridgeways and downland, wherever such places are open to the public, are also suitable. In fact in the South of England much v.h.f. portable work is carried out from such locations.

Common land which at first sight may seem ideal requires careful checking because under certain circumstances bylaws prohibit the use of vehicles thereon. Also such places attract large numbers of people when the weather is fine and this is not conducive to success or safety. Of course, if you live on a barren sea coast or are holidaying in Scotland or Wales where there is open country in abundance the problem is minimal; such sites would seem ideal.

High open country is particularly good for flying the kite because the winds are more reliable at such locations. I have found that at my home, which is about 90m above sea level, the wind can be barely noticeable. However, on Walbury Camp, a hill 297m above sea level where most of my portable work takes place, it can be strong enough to require very secure attachment of the line. A light breeze

early in the morning can by midday be blowing strongly enough for the equipment to be used for several hours.

A point which is not generally understood is that the wind does not blow at a continuous rate but in a series of gusts of varying intensity and time. Similarly the wind's direction may vary over the period of operating using the kite antenna. Light rain or drizzle though affording discomfort when operating need not prevent 1.8MHz portable operation, providing the wind is strong enough to keep the kite flying. Sometimes better results are obtained because of reduced atmospheric conditions in wet weather.

Antenna Length and Matching

As with all fixed station equipment, portable transmitting and receiving apparatus must be matched electrically to the antenna, for then and only then can the best results be obtained and of course possible damage to r.f. output transistors of solid state rigs be avoided. Modern transceivers have low impedance outputs in the 50 to 75 ohm range. To permit a random length of wire, which may be anything from 30 to 75m long, to be used as an antenna for such radio apparatus using coaxial input sockets, two important pieces of equipment are required. These are an antenna tuning unit (a.t.u.) and s.w.r. meter.

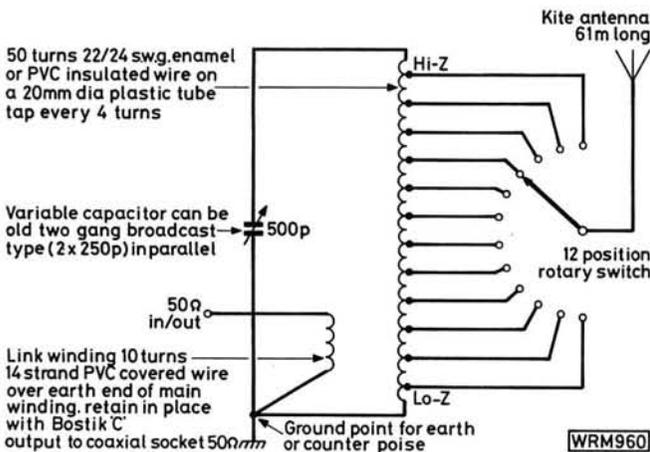


Fig. 2: Circuit details of the a.t.u. used by the author for operation on the 1.8MHz band

The a.t.u. matches the kite-borne antenna of unknown impedance to 50 or 75 ohms for connection via coaxial cable to the portable equipment. Several suitable designs of a.t.u. have been described in various radio magazines over the years. However, some of these can be complex and require careful adjustment, or will not adjust correctly with certain wire lengths.

Simplicity being the name of the game, I use a parallel tuned circuit with a 10 turn link coupling for 1.8MHz output (50 ohms) to the equipment, Fig. 2. The kite antenna is then tapped down the a.t.u. tuned circuit until a reasonable match between antenna and transmitter is obtained. The tuning capacitor of the a.t.u. is then carefully adjusted for final minimum reflected r.f. energy. By this method an extremely good transfer of r.f. energy to and from the transmitter/receiver is possible. Coupling of the a.t.u. to the rig is via coaxial cable of the correct impedance in series with an s.w.r. meter.

All initial adjustment of the a.t.u. should be done with reduced power and without delay, especially with solid state equipment, to avoid possible damage to unprotected r.f. output transistors under mismatch conditions. An indication of a near matched antenna is a rise in strength of

incoming signals when the a.t.u. tuning capacitor is adjusted whilst the equipment is on receive.

It is also unwise to operate solid state portable equipment whilst the kite is on or near ground level, which may occur if the wind abates. With transmitting equipment using valves, no p.a. damage of this nature will be possible (assuming 10 watts on 1.8MHz). During normal use moderate variation in height of the kite supported antenna does not have a serious effect on the s.w.r. In some locations the use of an earth rod may improve the matching of the equipment to the antenna. An improvement in noise reduction can also sometimes be obtained with a good earth or ground connection; failing this a counterpoise wire of the same length as the main kite antenna can be laid out on the ground to improve the effectiveness of the system. One end of the counterpoise is connected to the a.t.u. earth connection point or the transceiver chassis.

The terrain over which I use a kite antenna system is of chalk and flint which is much inferior to either clay or peaty acid soils, especially in dry weather conditions. Consequently I have never employed an earth or ground connection whilst using portable equipment in my locality.

The only other apparatus required is an s.w.r. meter which will show you how the system is working. Because of licence power restrictions on the 1.8MHz band and its low frequency, some commercial s.w.r. meters are somewhat insensitive. If frequent l.f. portable operation is contemplated it is wise to construct a more sensitive instrument. The use of low power or QRP transmitting apparatus will also require an s.w.r. meter of extra sensitivity.

Operating

All that is required now is a transceiver for a.m., c.w. or s.s.b. to complete the station, a suitable kite, oh and do not forget to park your car on a down gradient if you like to use the vehicle battery to power the rig!

One advantage of portable operation is that away from the built-up areas man-made interference from electrical equipment is very much less of a problem, so it is possible to work very weak stations which from the home station would be unreadable. With the equipment described, big signals are the order of the day. Due to the strength of the radiated signal it is diplomatic to avoid the frequencies shared by the maritime radio services. Listen on frequency before transmitting and be sure to maintain normal standards of operation at all times. Going portable is no excuse for sloppy operating.

This article is not meant to be a treatise on kite flying but a guide to a mode which has given the author enjoyment and fun for many years. May you go and do likewise.

Regulations for Use of Kites

Currently, Civil Aviation Legislation applicable to kite flying is contained in the Air Navigation Order 1980.

For kites of not more than 2kg in weight Articles 67 and 46 apply. Flying height is not to exceed 60m or be flown within 5km of an aerodrome at any height. Written permission from the Civil Aviation Authority for special circumstances can be obtained.

Article 46 of the Order requires that a person shall not recklessly or negligently cause or permit an aircraft to endanger any person or property (kites are classified as aircraft). It should also be noted that aerial advertising may not take place from kites.

For further information contact: General Aviation Section, Civil Aviation Authority, Aviation House, 129 Kingsway, London WC2B 6NN.

No. 27 Roger Hall G4TNT (Sam)

This month I have two mods for the Yaesu FT-480R 144MHz (2m) multimode. They were both sent in from Clapham by Robin, G8PVI, although the first one originated from Clive, G4PEB.

Low Power on Sideband

Robin enjoys QRP operation and although his FT-480R can be switched to low power on f.m. and c.w., he found that s.s.b. can only be used at full power. The following describes the mod he has built into his set to make the HI/LOW power switch work on s.s.b. as well.

First remove the bottom cover and locate the three coloured tags shown in Fig. 1. They are on the main board just to the right of Q61. To carry out the mod, just solder two 1N914 diodes across these tags as shown in the diagram. The circuit diagram Fig. 2 shows how they are incorporated into the circuit and when they are in place, the HI/LOW switch will be effective in all modes. All in all a very simple mod that should prove very useful for the QRP enthusiast.

Listen Input

Robin's second mod is also useful because it allows the user to check on the input of a repeater by pushing a button on the microphone.

The FT-480R has two pushbuttons for generating a toneburst, one on the front panel and one on the microphone. Robin has modified his set so that the button on the microphone now switches the receiver to the input of the repeater being used. The rear of the Satellite switch is shown in Fig. 3. There is a link between the two rear-most pins of the switch and this should be removed. When this is done, solder a 10kΩ resistor from the pin that has the blue wire soldered to it to the middle pin that has a violet wire running from it.

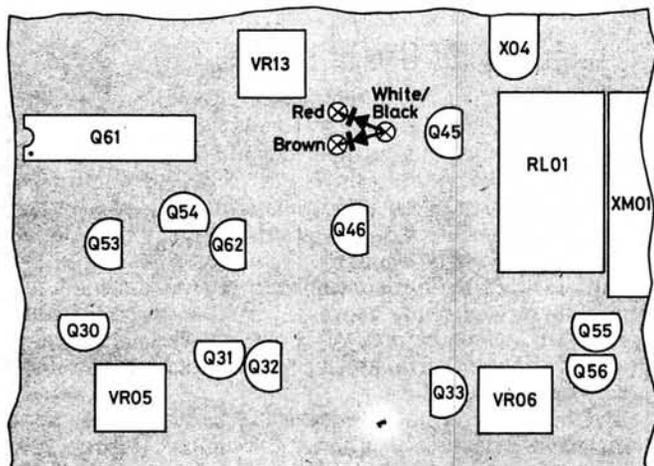


Fig. 1

IMPORTANT—The ideas presented here are suggestions only, and as they are untried by this magazine, we cannot accept responsibility for any resultant damage, however caused. Before alterations are attempted, care should be taken to ensure that any guarantee is not invalidated, and it should also be borne in mind that modifications usually have an adverse effect on resale prices. In cases where specialist skills or equipment are needed, most dealers will undertake the work for a reasonable fee.

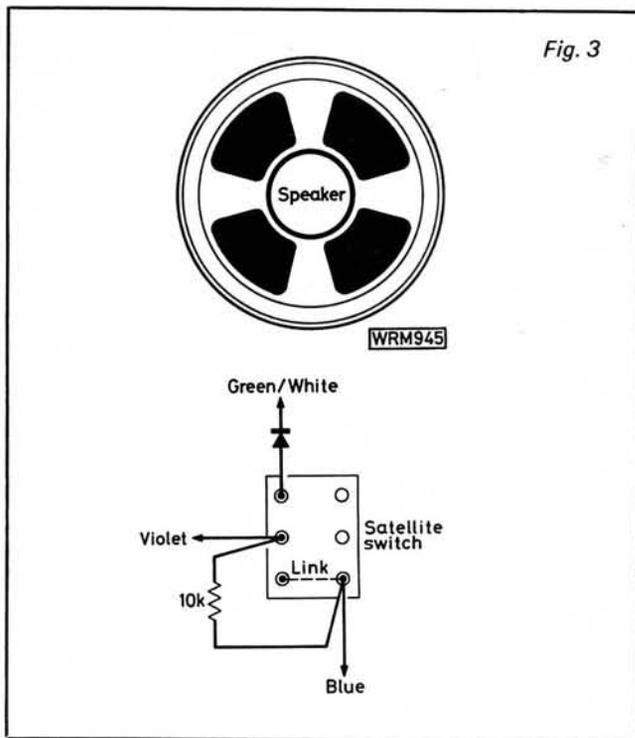


Fig. 3

Next, unsolder the green/white wire from the topmost pin and solder a diode (1N914) to that pin. Then solder the green/white wire to the other end of this new diode. Now, whenever you are listening to a repeater, pushing the toneburst button on the microphone will cause the receiver to switch to the input.

Thanks for two useful and easy mods Robin (and Clive).

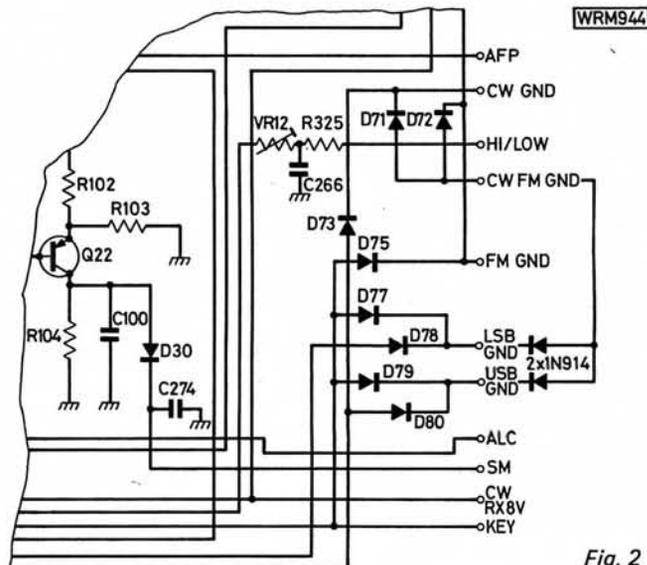


Fig. 2

Wanted

People are still writing in asking about extending the frequency range of the SX-200 scanner. As far as I know, this is not possible but I would be very pleased to hear from anyone who has had any success with this.

I have also received several requests from readers who are interested in joining a scanner club. Unfortunately I do not know of one in Britain, although there are several in America. Perhaps that is because these clubs are usually formed to allow members to swap frequencies and the legality of such a club in this country would be questionable. Of course there are lots of interesting transmissions that can be overheard with a scanner but that is illegal, so forming a British club to pass on the frequencies of these signals would certainly be frowned upon. Similarly, I cannot reply to those of you who have written to me asking for these frequencies, nor can I publish them as the legal position is not entirely clear. If there is a British scanner club that does not promote illegal listening, I would certainly like to know about it and I will publish the address(es) of any that care to contact me.

Pass it on...

If you have a mod that you would like to pass on or if you have a request for a mod that you would like to carry out, please write to me at this address: R. S. Hall, Practical Wireless, Room 204B, Hatfield House, Stamford Street, London SE1 9LS.

Did You Know...

That two famous professors demonstrated successful wireless apparatus before Marconi did, but were not interested in commercialising their systems?


In 1894, the English professor, Oliver Lodge demonstrated a complete wireless telegraphy installation comprising Hertz's generator with a Morse key for transmitting, and a combination of Hertz's resonator and an improved version of Branly's coherer for receiving. In addition, he connected the receiver to a Morse recorder, so that the dots and dashes were recorded as marks inked on paper. It worked well, but Lodge was a physicist and not interested in its practical application. The following year, a Russian, Professor Popov, used a somewhat similar receiving apparatus to record lightning flashes in thunderstorms, and increased its sensitivity by attaching it to an earth plate and a lightning conductor. He was thus the first to use an antenna but, like Lodge, was not concerned with the commercial use of his discovery.

Eric Westman


Next month in On Sale 6th Jan

VHF/UHF ANTENNA SPECIAL

Practical Yagi Design

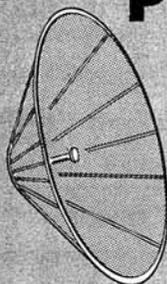

Microwave
Dish
Construction

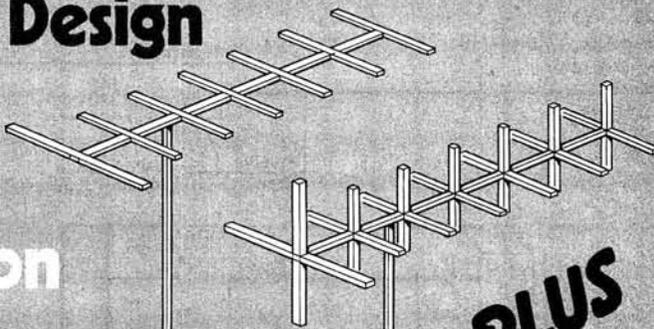

PLUS

Going Circular

PLUS

your favourite regulars in

FUSES - selection & use

**Practical
Wireless**



ADJUSTABLE AUDIO FILTER

by Tony Smith G4FAI

The device to be described in this article is a unit suitable for the aspiring radio amateur/s.w.l. beginning to listen to c.w. (Morse), or for the recently licensed operator anxious to use his newly mastered code, on the crowded amateur bands. At times conditions are such that it is quite difficult for an inexperienced operator to read the wanted signal in the midst of the cacophony of sound reaching his ears, and in these circumstances even a quite simple filter can be surprisingly effective.

The unit, which can be used for c.w. or speech, has adjustable bandwidth and centre frequencies; clipping, to reduce the audio level of powerful adjacent stations when used for telephony reception, and a headphone or built-in speaker output. An alternative, passive, filter for less demanding conditions together with a "straight-through" facility for connecting the 'phones or speaker directly to the receiver is provided and "finally" it can also be used as a Morse practice oscillator!

The Circuit

The heart of the circuit is Tr1. A twin "T" filter comprising R6/7, C6 and C4/5, R8/9, gives a narrow rejection notch at a frequency controlled by the setting of R9.

Connecting the filter between the output and input of Tr1 results in negative feedback reducing the gain of the transistor to a low level. At the notch frequency, however,

there is little feedback so at this frequency Tr1 exhibits practically full gain thus reversing the action of the notch filter. Any signal at the selected audio frequency is then boosted at the expense of all others making it very much easier to copy the wanted signal.

The centre of the range of R9 provides the frequency most usually required, about 750Hz, and adjustment of this front panel control enables this to be varied as desired.

Adjustment of R5 controls the overall gain of Tr1 and also the width of the passband of the audio signal. This gives, in effect, a variable Q control enabling the passband to be made sharper or broader as required. More sophisticated circuits would specify the range of centre and passband frequencies obtainable. This information is not available here but what can be said is that the filter can be adjusted by ear over a reasonable range of frequencies either side of 750Hz (which can be identified—see later), and the bandwidth can be varied from totally broad to a sharpness which results in the signal "ringing".

The two diodes D1, D2, provide clipping of the audio signal when receiving telephony signals. Any signal above 0.6V is conducted to earth by the back-to-back diodes whilst all lower voltage signals are unaffected. If the wanted signal is increased by the input control R1, until it is just below clipping level, any stronger signals or peaks will be clipped to the same level, effecting a considerable improvement in the readability of the wanted signal.

Transistors Tr2 and Tr3 form a two stage direct-

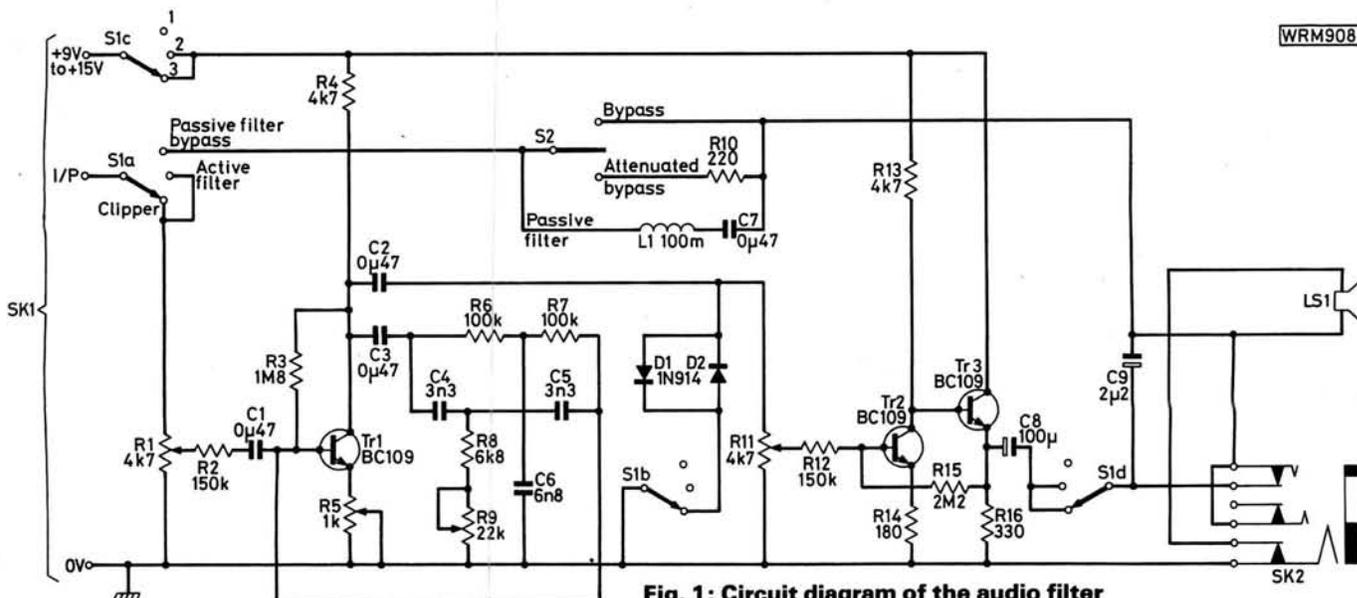


Fig. 1: Circuit diagram of the audio filter

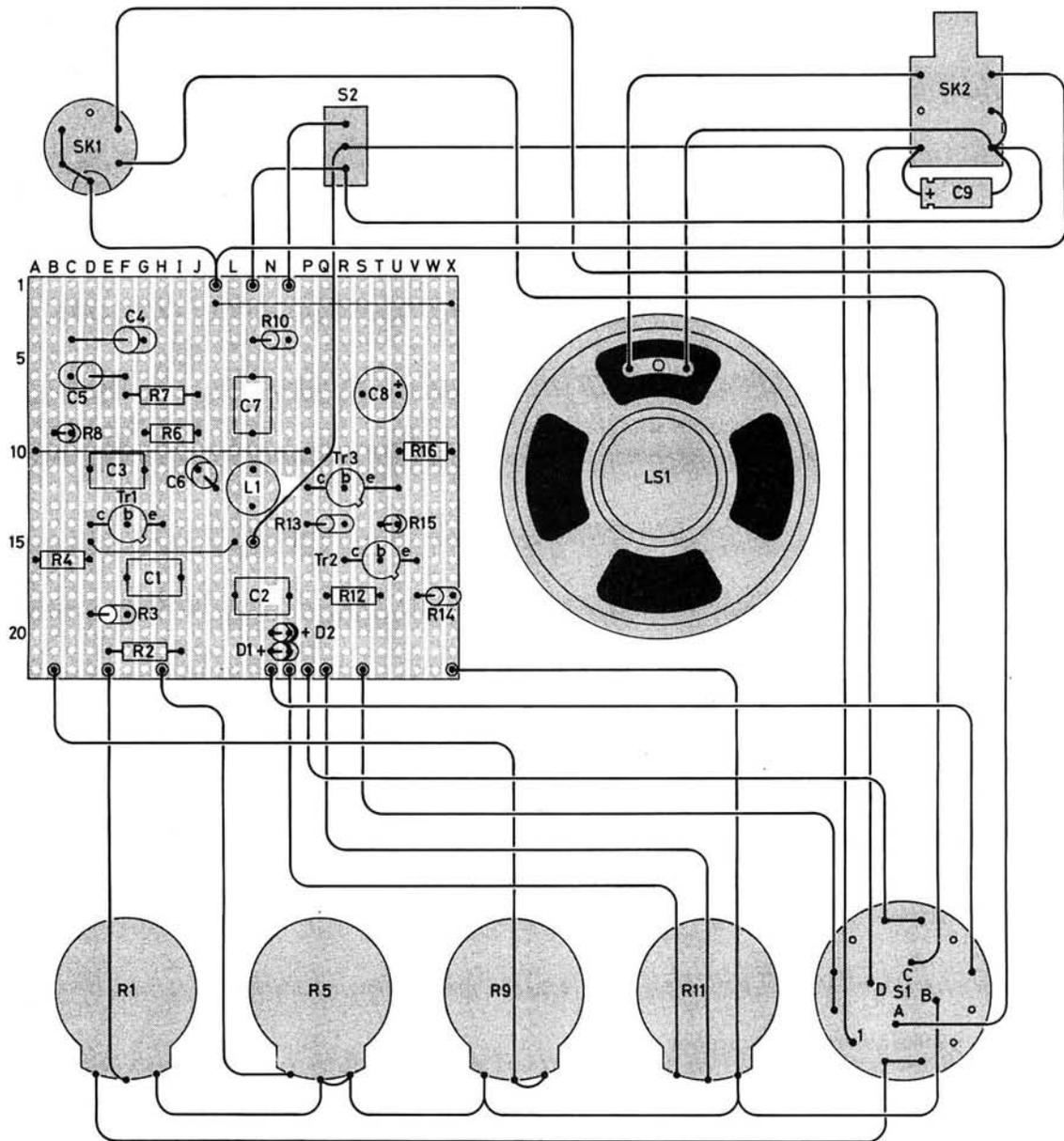


Fig. 2: Component placement and interconnection details. Veroboard track breaks occur at M7, M12, O12, E19 and N18

coupled amplifier with Tr2 in common emitter mode and its output matched by Tr3, an emitter follower, thus providing low impedance audio output.

With the speaker in use C8 is the output capacitor. Alternatively, when the 'phone jack is inserted in its socket C9 is automatically placed in series with C8, reducing the output capacitance to just over $2\mu\text{F}$. This attenuates the bass response whilst still giving adequate audio for headphone reception. Useful in cleaning up the signal when the filter is used within a wider passband.

Reasonable loudspeaker reception is obtained from stronger signals processed through the unit but the main purpose of the speaker is to provide "straight-through" reception when monitoring or tuning through the band. Serious operating should always be via headphones when the full effect of the filter can be realised. The 'phones used are unmodified standard 8Ω stereo types. High impedance 'phones ($4\text{k}\Omega$) can be fed directly from the filter in place of

the output control R11 and the audio amplifier would not then be required.

The inclusion of a passive filter, L1, C7, is an interesting feature which can be used on its own independently of the main unit. Traditionally, this type of filter has utilised heavy 88mH toroidal inductors and physically large capacitors. Here, modern miniature components have been used to provide, in the first instance, a simple filter quite suitable for dealing with modest interference to c.w. signals without requiring a power supply and secondly, a standard centre frequency against which the active filter can be set. With the values given a nominal frequency of 734Hz is obtained, which is as near as necessary to 750Hz . Other values can be used for other frequencies to suit particular receivers or the listening preference of the operator.

Switch S1, position one, disconnects the power supply and brings S2 into operation. The second position brings

in the active filter and the third position adds the clipping facility. Switch S2 offers three listening options—BYPASS, PASSIVE FILTER or ATTENUATED BYPASS via R10.

The circuit will also function as a Morse practice oscillator, with variable frequency and audio output, by simply breaking the connection between R9 and R8 and inserting a Morse key at that point.

Passive Filter Design Notes

The PASSIVE FILTER included in the circuit is a modest but useful c.w. filter in its own right which can cope reasonably well with all but the most difficult conditions. The inductor used is available in different values permitting a range of centre frequencies to be obtained with various capacitor values. It should be borne in mind that too great a variation from the receiver's normal beat frequency will necessitate use of a transceiver's r.i.t. or offset control since the transmit and receive frequencies will no longer coincide when the filter is in use.

The basic formula for the filter is:

$$f = \frac{1}{2\pi\sqrt{LC}}$$

where L = inductance in henries

f = frequency in hertz

C = capacitance in farads

The values used can be inserted directly into:


$$f = \frac{10^5}{6.32\pi\sqrt{LC}}$$

where L = inductance in mH

C = capacitance in μF

f = frequency in Hz

The result in either case is a nominal frequency because of the tolerance in the values of the components which need to be of 5 per cent tolerance or better.

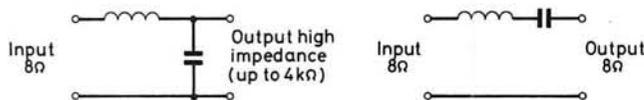

WRM909

Fig. 3: Passive filter basic configurations

Construction

This is quite straightforward. The Veroboard has only five breaks in its copper strips and is mounted as shown on three insulated pillars, which must be high enough to clear the board from any cover fixing screws. All drilling and wiring details are given in the diagrams. The loudspeaker can be fixed with "Super-glue". The combined audio input/power supply DIN socket is optional and different arrangements can be made to suit individual requirements. If the Morse practice facility is required an additional socket, with break contacts, can be fitted to the rear panel (see Fig. 4).

Cabinet feet should be fitted at the front to provide clearance for the speaker sound output. Smaller feet at the rear will result in the sound being projected forward.

Setting up

Connect the input lead of the filter to a low impedance output from the receiver. Connect the power lead to a d.c. supply of between 9 and 15V. A good arrangement is to take the power directly from the receiver or transceiver if this can be done, providing it is negative earth. Make sure

50

★ components

Resistors

Carbon film $\frac{1}{4}W$ 5%

180 Ω	1	R14
220 Ω	1	R10
330 Ω	1	R16
4.7k Ω	2	R4,13
6.8k Ω	1	R8
100k Ω	2	R6,7
150k Ω	2	R2,12
1.8M Ω	1	R3
2.2M Ω	1	R15

Potentiometers

$\frac{1}{4}$ inch spindle

1k Ω (lin)	1	R5
4.7k Ω (lin)	1	R1
4.7k Ω (log)	1	R11
22k Ω (lin)	1	R9

Capacitors

Polyester, 5%

0.47 μF	4	C1-3,7
--------------------	---	--------

Polystyrene

3.3nF	2	C4,5
6.8nF	1	C6

Electrolytic p.c.b. type

100 μF 25V	1	C8
-----------------------	---	----

Electrolytic double-ended

2.2 μF 50V	1	C9
-----------------------	---	----

Semiconductors

Diodes

1N914	2	D1,2
-------	---	------

Transistors

BC109	3	Tr1-3
-------	---	-------

Miscellaneous

TOKO 10RB, 100mH inductor (Ambit); 4 pole, 3 way rotary switch (S1); s.p.d.t. centre-off miniature toggle switch (S2); stereo jack socket; 5 pin DIN socket (see text); speaker 75mm, 8 Ω ; pointer knobs (5); Veroboard 0.1 inch matrix; Verobox 202-21038, 180 x 120 x 65mm; insulated pillars 6BA x 10mm; self-adhesive feet (4).

BUYING GUIDE

All components required for this project are readily available from normal sources

Approximate
Cost

£20

Construction
Rating

INTERMEDIATE

the earth side of the output from the receiver is connected to earth in the filter. Plug the headphones into the filter.

Next, set the input and output controls of the filter to approximately half-way and set the Q and Frequency controls at minimum. Switch the unit to BYPASS and select BYPASS also on S2 at the rear of the unit. Switch on the receiver and signals should be heard as if the 'phones were connected directly to the receiver. Now tune the receiver to a crystal marker tone, if this is available, otherwise find a steady heterodyne signal somewhere in an amateur band.

Select the PASSIVE FILTER with S2 and tune the receiver until the signal is peaked by the filter. It may be necessary to advance the audio output of the receiver to obtain the best peak as the filter attenuates the signal passing through it.

The receiver is now delivering an audio signal of approximately 734Hz, or whatever other frequency the filter has been designed for. If the ACTIVE FILTER is now switched in by S1 on the front panel, R9, the FREQUENCY control can be adjusted to peak the signal at the same frequency. A mark can then be made on the front panel to enable the frequency to be returned to whenever desired. Alternatively, the position of the knob on the shaft of the potentiometer can be adjusted so that the pointer coincides with the centre marking on the front panel.

During this operation it will be necessary to advance the Q control to a point just short of oscillation to obtain the best peak. At the same time it may be necessary to reduce the input to the unit by adjusting R1. The filter is now ready for use.

Operation


There is no need for the filter to be used at all if good clear c.w. signals are being received via the bypass line. A modest improvement can be obtained by listening via the attenuated bypass, which simply reduces the sensitivity of the 'phones, and a surprising improvement by using the passive filter. In this case a somewhat aggressive approach to the receiver's audio gain is sometimes necessary to get best results and the gain may have to be increased to just short of the point where distortion occurs on the wanted signal.

Remember not to switch back from passive filtering directly to ordinary by-pass as the result on the eardrums could be disastrous! The attenuated bypass is intended to match the two audio levels so that they can be switched from one to the other at about the same level.

If there is more interference than the passive circuit can cope with the active filter can be switched in by S1. If this is still set at the same frequency as before it should be possible to advance the Q control until much of the interference has been attenuated. Taking it to a point just short of oscillation will produce the sharpest filter effect. Back-

ing off from this point will "open up" the filter and the widest possible passband should be used consistent with good readability of the signal. The input level should be kept reasonably low to obtain best results and the optimum settings will become apparent with practice. If a high Q is used it may not always be possible to hear the transmitter side-tone satisfactorily and in this case the filter should be switched to ATTENUATED BYPASS when keying.

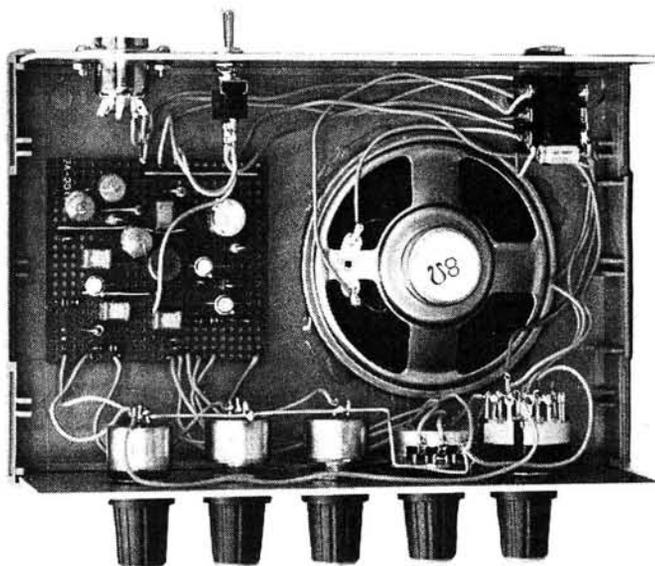Because this is an oscillatory circuit the adjustment of R5 between narrow and broad bandwidths is quite small. This does not cause any great difficulty in practice but a small improvement could be obtained by using a 500 Ω potentiometer instead of the 1k Ω specified.



One of the difficulties with using any sharp audio filter is the fact that not all transmitters, or receivers, are stable enough to permit the wanted signal to remain within the passband of the filter. If this problem is experienced with a transceiver there are three possible solutions depending on the band conditions and the amount of frequency shift involved. These are:


- 1) following the signal with the receiver incremental tuning;
- 2) adjusting the frequency of the filter;
- 3) reducing the Q to open up the passband.

If a separate receiver is used it is simply retuned to follow the frequency shift.

For use with telephony signals S1 should select the clipping circuit. The Q should be advanced until the wanted signal is readable when accurately tuned but distorted on either side if the tuning is shifted. For maximum effect the input to the filter (R1) should now be increased until the wanted signal falls just short of distortion by clipping. If necessary the receiver audio output can be increased to assist this. The output control (R11) should be reduced to provide a comfortable listening level.

If the optional Morse practice function is used R5 should be fully advanced to put the circuit into oscillation, R9 adjusted to provide the required frequency and R11 for output level.

This versatile little unit has a quite surprising performance. Expensive commercial units provide similar features with greater elegance and sophistication, but the question arises—how much sophistication is really needed? In the true amateur tradition here is a modest piece of home-built equipment which will give of its best in response to the acquired skill and enthusiasm of the operator using it.

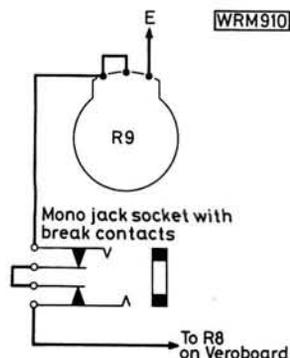

WRM910

Fig. 4: The modification needed to provide a Morse practice facility. The jack socket which should be a mono type, can be located on the rear panel of the filter housing

Products

VHF Band II Antenna

South West Aerial Systems, the Poole based antenna specialists, can supply a new antenna intended for the f.m. DX enthusiast and features a curved folded dipole, not unlike the familiar "Halo" commonly used in amateur circles.

Called the Triax Omni 1, it is tuned for use in the 88 to 104MHz portion of the spectrum (Band II v.h.f. broadcast band) and provides full 360° omnidirectional coverage, when mounted horizontally, without the need for a rotator.



Gain is claimed to be between -2 and -4dBd and the folded element is

constructed of $\frac{3}{8}$ in diameter seamless aluminium tube.

The quality of construction is to the usual high standard of Triax products, and within the connection box is a small ferrite balun converting the 300Ω balanced antenna element down to match standard 75Ω coaxial cable.

Priced at £10.90, which includes VAT and p&p, the Triax Omni 1 is obtainable from: *South West Aerial Systems, 11 Kent Road, Parkstone, Poole, Dorset BH12 2EH. Tel: (0202) 738232.*

Amateur Station Log Book

Ant Products, the Yorkshire based antenna manufacturers, now include in their product range an amateur radio station log book.

The A4 size log book is spiral bound and provides for over 2500 entries laid out to conform with UK licence requirements, also a European QRA locator map is printed on the inside front cover.

Priced at £3.50, which includes p&p, the log book also contains a voucher worth £2.00, redeemable against the purchase of one of their antennas (excepting the Super Slim Jim), and is obtainable direct from: *Ant Products, All Saints Industrial Estate, Baghill Lane, Pontefract, West Yorkshire. Tel: (0977) 700949.*

Latest on the SX-400 Scanner

We hear from Garex Electronics that the long-awaited SX-400 v.h.f./u.h.f. scanning receiver should be available early in the new year.

Based on the outstandingly successful SX-200, the SX-400 embodies many more features to appeal to the professional user.

Major features of the receiver include full coverage from 26MHz to 520MHz over 12 bands, programmable a.m. and f.m. throughout the range, switchable i.f. bandwidth, switchable channel spacing, 10.7MHz and 455kHz i.f. outputs, S-meter, computer handshaking for data recording and limitless memory capacity. An optional scaler (r.f. converter) enables the range to be extended down to 150kHz and up to 3.7GHz.

Priced in the region of £600, further details are available from: *Garex Electronics, 7 Norvic Road, Marsworth, Tring, Herts. HP23 4LS. Tel: Cheddington (0296) 668684.*

Hot News from Icom

Latest information from Icom reveals the launch of a new hand-held 144MHz transceiver onto the UK market early in 1984.

Entitled the IC-02E, it is intended to follow-on from the incredibly popular IC-2E and is housed in an almost identical case.

The IC-02E is microprocessor controlled and frequency selection is via a 16-button keyboard. A large digital l.c.d. readout displays frequency, relative signal strength, r.f. power and also identifies which of the 10 memory channels is being used.

Other main features include full


band scan, memory scan and scan between preset limits, plus a diecast aluminium back is incorporated to improve heat-sinking and the unit is fully compatible with all IC-2E accessories.

Nominally r.f. power out is 3W Hi with switchable 1W Lo but by using one of the two new battery packs the Hi figure can be lifted to 5W. Both new battery packs are fitted with a new locking arrangement to prevent accidental dislodging and also may be recharged direct from a separate 12V d.c. supply or car battery. Provision has also been made to power the transceiver direct from a 13.8V d.c. supply, such as the cigar lighter socket in a car.

Memory backup is provided by an internal lithium battery preventing the loss of frequencies stored in the memory when the main battery pack is removed. Other features include priority channel facility, frequency lock, and readout lamp on/off switch.

Finally, the v.c.o. is capable of covering the frequency range 50MHz to 1.1GHz, so we can probably look forward to other versions of this rig becoming available in the future, that will cover a variety of other amateur bands.

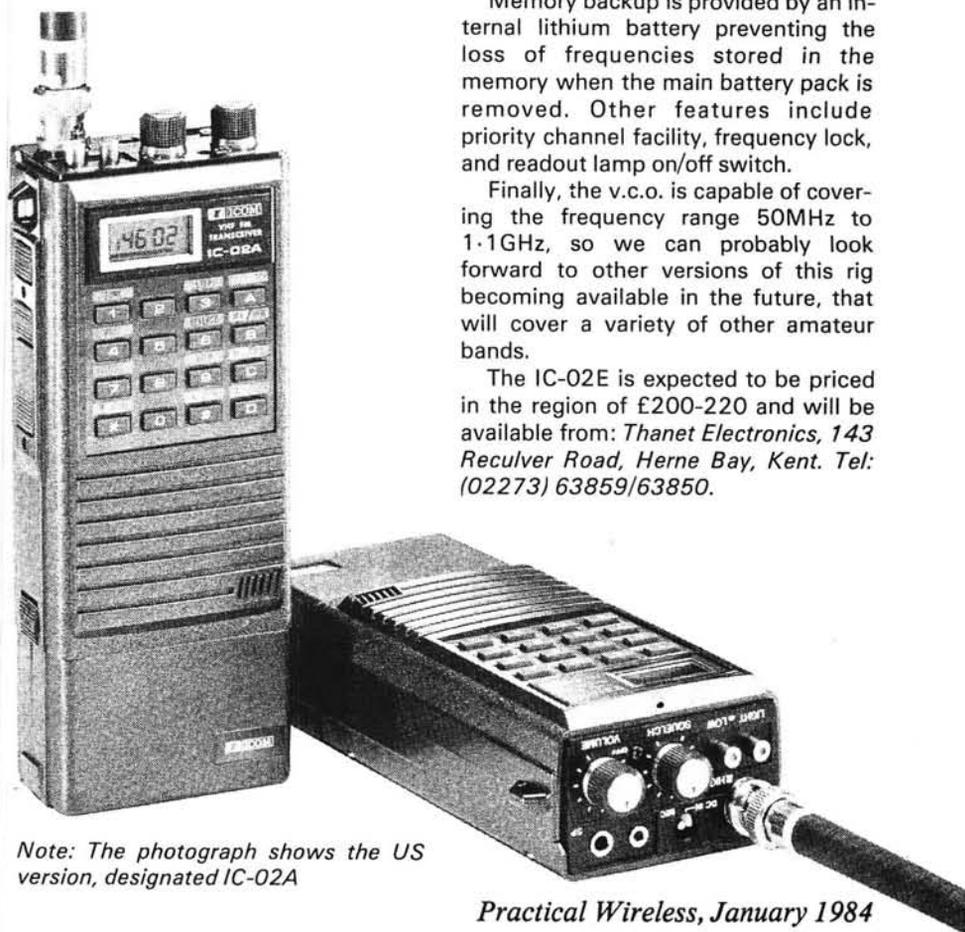The IC-02E is expected to be priced in the region of £200-220 and will be available from: *Thanet Electronics, 143 Reculver Road, Herne Bay, Kent. Tel: (02273) 63859/63850.*



Note: The photograph shows the US version, designated IC-02A

Products

Mobile Generators

An essential component in the running of an efficient portable station at contests or field days is a reliable and constant power source for the equipment. Unless the operator is prepared to manhandle a number of lead-acid batteries to the site, the obvious answer is a lightweight portable engine generator.

However, hiring a generator, for a number of events, can prove a most costly exercise, so, the special discount that Ray-Lift Ltd. are prepared to offer to *PW* readers could make the possession of a personal or club owned generator a reality.


The generators on offer are the MG series manufactured by Mitsubishi. Both models, the MG1801-D and MG2401-D, are compact and light in weight (40 and 49kg respectively), voltage stability is controlled by an automatic regulator which limits fluctuation to about five percent. Three

output voltages may be selected: 110V a.c., 220V a.c. and 12V d.c. at 8.3 amps. Maximum power output on a.c. is 1.5kVA for the MG1801-D and 2.0kVA for the MG2401-D.

Control devices such as control box, speed control lever and recoil starter are installed on one side for easy operation. Also a frequency meter and circuit breaker are supplied as standard.

Fuel tank capacities are four litres for the MG1801-D and five litres for the MG2401-D.

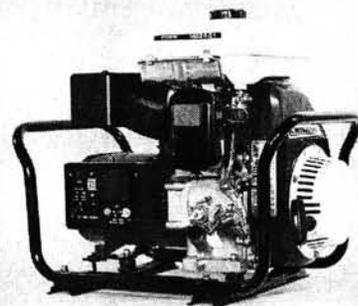List price for the MG1801-D is £390 plus VAT and £460 plus VAT for the MG2401-D. However, as mentioned previously, Ray-Lift Ltd. are prepared to offer a 30% discount to *PW* readers on orders received before the end of January 1984. Therefore, £283 plus VAT will buy the MG1801-D and £322 plus VAT will obtain the MG2401-D.



A Calor gas conversion kit is being produced, which will cost around £45 and will offer the advantages of cleaner burning, less dangerous exhaust fumes, quieter running, plus a 26lb bottle of gas will run the generator for approximately 26 hours.

Orders and further enquiries should be sent to: *Ray-Lift Ltd., 114 Kingston Avenue, Bilford Road, Worcester WR3 8PP. Tel: (0905) 56671.*

Another Winner for Sinclair and the UK

Following hard on the heels of the enormous success of the ZX series of home computers, comes the Sinclair 2in flat-screen TV, the first TV with a single i.c. chip for circuitry, which was introduced recently after a six year £4 million development programme.

About the size of an average paperback book this totally portable TV measures only 140 x 90 x 30mm, weighs 280g and will be priced at £79.95, which includes VAT and is approximately one third the cost of its nearest competitor.

Major features include, automatic standard switching for reception of most u.h.f. transmissions around the world (except France), high-quality video reception and extremely low power consumption with a special polaroid flat-battery providing 15 hours of reception time. Also the set is easy to operate having only two controls, on-off/volume and tune.

Key design elements in the new TV are Sinclair's revolutionary flat-screen c.r.t., and the single l.s.i. (integrated circuit) which performs the majority of signal processing functions within the set.

Simply described, the c.r.t. is assembled from just two sheets of glass, a flat front plate and a vacuum-formed backing plate. The phosphor screen is coated on the interior of the backing plate and is viewed through the front face from the same side that the electrons strike, resulting in up to three


times the brightness of a conventional c.r.t. with the same beam energy. The electron gun is set to one side of the screen with its axis parallel to the screen. Two sets of electrostatic deflection plates in the gun assembly provide horizontal and vertical scanning, and a third set between the phosphor screen and front face bends the electron beam toward the screen.

Regarding the single l.s.i., its special features include integrated sound selectivity, video innovations to eliminate image problems in the u.h.f. channel and an advanced synthesised scan generator to control the complex

waveforms needed to scan the flat c.r.t. It runs a check 50 times per second to ensure picture "hold".

UK retail and export sales are planned for the first half of 1984, and Sinclair is confident of selling up to one million sets per year worldwide, leading to the creation of hundreds of new UK jobs in component production and final assembly.

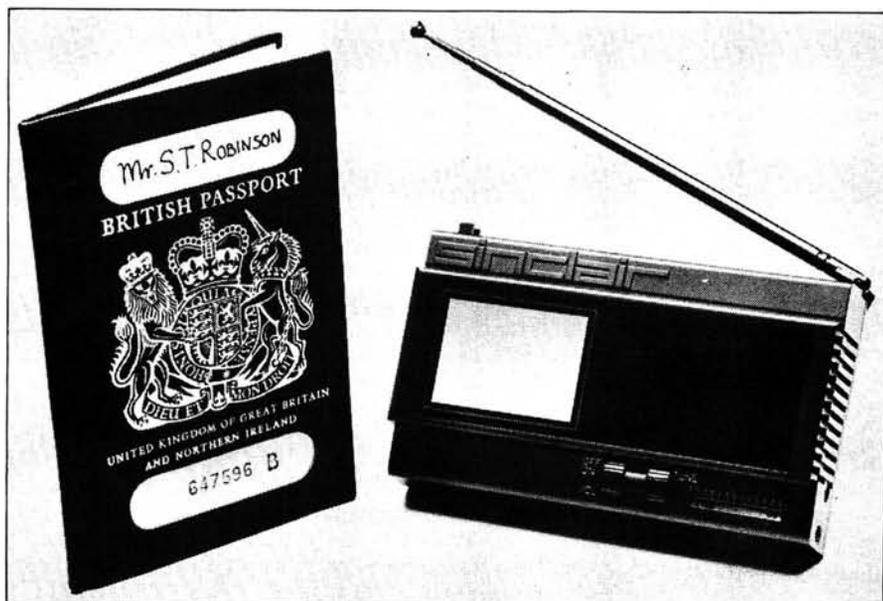Orders for the first available sets will be supplied strictly on a first-come, first-served basis and can be placed by contacting: *Sinclair Research Ltd. Stanhope Road, Camberley, Surrey GU15 3PS. Tel: (0276) 6211.*



Domestic Aerials



in the GOOD OLD DAYS

by 'Old Timer'

To those of us fortunate enough to have lived through the "Golden Age" of wireless, the 1920s and 1930s, the most abiding memory must surely be the forests of aerials that bristled over the towns and villages of Britain. Practically every home boasted one: the multiwire array that stretched from a centuries-old tree over spacious lawns to the roof of a stately home; the ubiquitous single wire strung from a bent pole at the bottom of the council house garden to a bedroom window; the cylindrical "birdcage" perched on a broom-handle above the top-floor flat. In those days there was a wonderment and excitement about the new miracle of communication; sadly the magic of wireless has now become commonplace, and the wonderment—like the aerials—is no more.

For the starry-eyed "listener-in" of the early 1920s, with his crystal set and headphones, the longer and higher he could make his aerial, the better. In fact, with a really lofty and lengthy array, the proud owner of a bright-emitter valve set could stand his headphones in a pudding basin to amplify the sound whilst admiring relations and neighbours thrilled at the resultant audible squeals and crackles. But since these primitive valve receivers often emitted oscillations and so became transmitters of interference, the length of aerials was limited by law to 30

metres, although there was no limit to the number of wires that could be connected in parallel. Incidentally, the correct form when assailed by oscillations from a neighbour's valve set was to turn your own reaction (feedback) knob as far as it would go and so return the compliment in the form of a multi-decibels blast—particularly effective if the offender was wearing headphones!

In the days before broadcasting began, a single strand of, say, 16 s.w.g. bare copper wire was used for an aerial. But by the mid-1920s the preference was for a multi-strand, insulated copper-wire aerial. Two configurations were popular: the "inverted L" in which the lead-in ran from the end nearer the house; and the "T" in which the lead-in descended from the centre of the aerial.

The aerial wire was insulated at both ends from its attachment to the pole and house by a porcelain "egg" insulator. To get the aerial into the house a "lead-in tube" was used. This was an ebonite tube 304mm long by 16mm diameter with a 2BA threaded brass rod running through it, the whole fitted through the wooden windowframe nearest the wireless receiver. The lead-in was attached to the exterior end by a knurled brass nut, while the receiver was similarly connected to the interior end.

If possible, the aerial was erected in alignment with the

transmitter it was most wanted to receive, which was often the only one that could be received. Sometimes it was erected broadside-on to the transmitter you didn't want to receive, usually a nearer or more powerful one that blotted-out the required station, or even a persistent offender's oscillating valve set.

Since it was popularly believed that several aerial wires connected in parallel increased the strength of the signal fed to the receiver, multiwire aerials became popular. A favourite arrangement was the "twin" comprising two horizontal wires hung parallel and up to six feet apart. They were often attached via egg insulators to a broom-handle "spreader" at each end. Another favourite was the "sausage" or "cage" aerial made up of six or more wires hung parallel to one another in a tubular configuration. The wires were attached at either end via the ubiquitous egg insulators to a wooden hoop about 610mm in diameter—ladies' embroidery hoops often served.

For people with no gardens, such as flat-dwellers, a popular type of aerial was the "birdcage". Mounted atop a pole fixed to a chimney, it consisted of two wooden hoops set horizontally one above the other about 610mm apart with a length of insulated wire zig-zagged up and down between them all the way round. This effectively concentrated a long aerial into a small space, and it was non-directional.

Those who could not manage any form of external aerial had to make-do with a "picture-rail" aerial, a length of flex strung along the wooden picture-rail all round the room. An aerial of this type was screened by the brick or stone walls surrounding it, and thus the strength of the signal reaching it was reduced.

Yet another collector of wireless waves for confined folk was the "loop" or "frame" aerial consisting of a circular, square or diamond-shaped wooden frame at least 610mm across, often 1.2 metres and in some cases 1.8m, when it would be mounted on the floor. Around the frame was wound wire, usually double-cotton covered and often of 20 s.w.g. The number of turns depended on the wavelength to be received and the size of the frame itself: the larger the frame, the fewer the turns. Although the signal it picked up was weaker than that from an outdoor aerial, it had two advantages: it could easily be aligned with any station it was wanted to receive, thus maximising the strength of the signal; and it could be turned broadside-on to an interfering station in order to minimise the interference.

The frame aerial usually took the place of the tuning coil in the receiver and was tuned, like the coil, by a variable condenser across the two ends of the winding. No earth was needed but reception could be badly affected by people moving about close to the frame. Indeed, some people became so adept at manipulating this property of the frame aerial that by setting their receiver at oscillating point and waving their hands to and fro near the frame they produced in their loudspeaker (and in other people's loudspeakers) mellifluous renditions of popular tunes of the moment. Music-hall performers used this principle to mystify their audiences with "magic music".


Still on the subject of frame aerials, a wireless magazine of the mid-1920s reported the case of a man living near the giant aerials of the new Daventry transmitting station who set up a large frame aerial, aligned it with Daventry, and obtained enough power to light a bulb in his shed. He was fined!

As wireless became more popular, all kinds of "monstrosities" were pressed into service as aerials. Sometimes the receiver was connected to a metal clothes-line running the length of the garden. With a height of only 2 metres compared with the normal 10 metres it was not very efficient; and not being insulated at each end, much of the signal would leak to earth. But the author remembers tuning-in Rome on a one-valve shortwaver in 1940, using a clothes-line aerial, and hearing Mussolini declare war on Britain.

Many people even swore that a tree would serve as an aerial if a nail were hammered into the trunk about two metres up and a lead-in connected to it, but most likely the length and the height of the lead-in caused the latter to function as an aerial on its own account. All the same, the United States army made a serious investigation of tree aerials in the First World War. It would be interesting to know how their 100 metres high Redwoods performed.

A good outdoor aerial system would have a 410mm bracket mounted on the outside wall near the lead-in tube, to hold the lead-in away from the wall and so prevent the signal from being damped. Without this bracket, the lead-in could be blown nearer or away from the wall thus varying the strength of the signal received and possibly upsetting all the painstaking adjustments of the receiver.

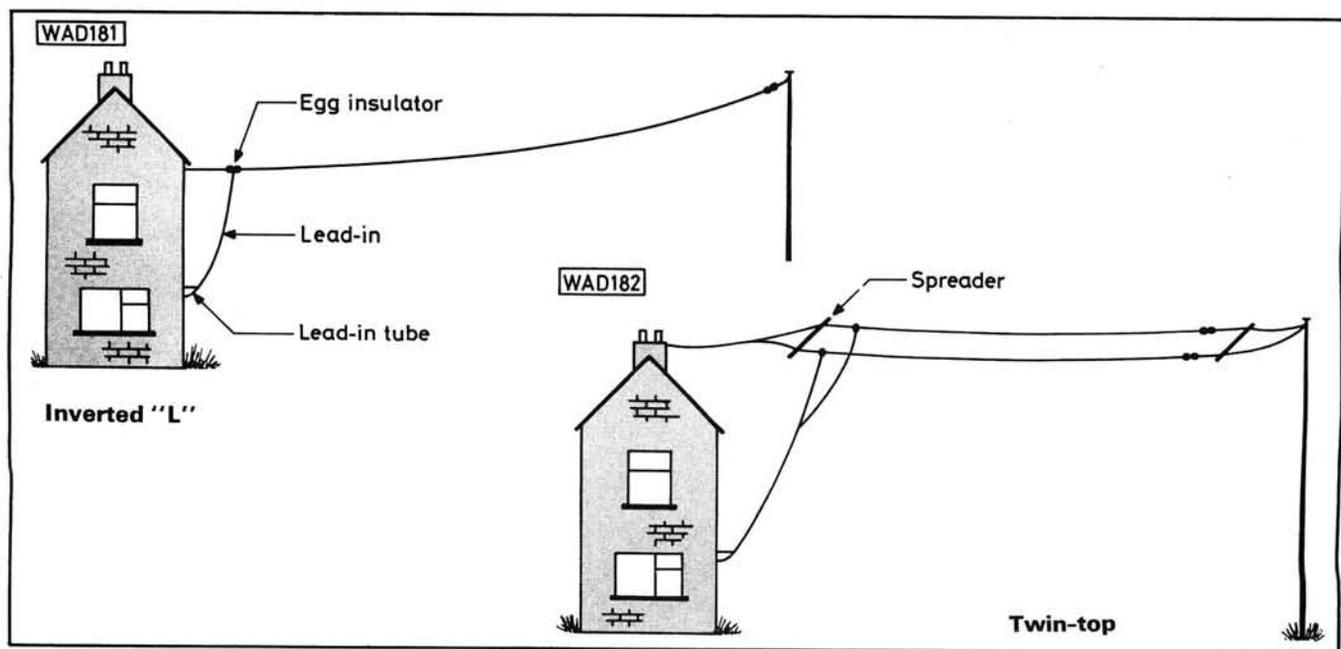Fear of lightning striking the aerial was very great, particularly in the 1920s. Cautious people disconnected the aerial wire from the receiver and stood the end in a jug of



water every night when going to bed, fondly believing that they had thereby earthed the aerial! One British manufacturer of insulated, stranded aerial wire profited by this fear and boosted sales when he gave a free £500 lightning insurance policy with every roll of his wire. This was enough to buy a new house, but the aerial manufacturer ran no risk—I never heard of a claim being made.

Many lead-ins incorporated a "lightning arrester" consisting of a brass spark gap with one of its electrodes connected to the aerial and the other to the earth. In the event of lightning striking the aerial, the charge would jump the spark gap and pass harmlessly to earth instead of damaging the receiver. A home-made version could be made from two short pieces of hacksaw blade mounted teeth to teeth with a 0.8mm gap between them. An even simpler method employed an old sparkplug connected between aerial and earth.

An alternative device was a knife-switch mounted on the outside wall to connect the aerial to earth in thundery weather. The author's late father—a village "wireless wizard" of the 1920s—used such a switch until the end of World War II and earthed his aerial every night before going to bed.


A cunning dodge employed by listeners-in who owned a telephone was to unscrew the lid of the telephone junction box and to connect the wireless set via a fixed capacitor to the external telephone wire which, with a length of many miles, made an excellent aerial. The author did this with an early crystal set and it operated a horn loudspeaker at fine volume. Some people believed that by tapping the appropriate terminals in the junction box they could obtain a

free 24-volt d.c. electricity supply with which to augment the expensive high-tension battery.

Whilst on the subject of telephone wires, an old countryman known to the author erected a long aerial running parallel with the telephone wires leading to a farm further down the lane. This aerial picked up by induction the currents in the telephone wires, and the old fellow enjoyed listening on his wireless set to conversations between the farmer's daughter and her boyfriends. This inductive effect was common and could be cured by re-erecting the aerial at right-angles to the telephone wires.

Many strange myths circulated during the 1920s and 1930s concerning the supposed properties of aerials, and each enthusiast had his pet beliefs. A Somerset villager recalls a widely held local belief that the static could be eliminated by wrapping cottonwool around the lead-in! And that a longer and higher aerial "took power" from a neighbour's inferior aerial, so that when his father installed his first Kolster-Brandes valve set, he also installed the highest and longest aerial in the neighbourhood.

Sadly, all the weird and wonderful contraptions that passed as aerials have gone; so, indeed, has the very name, for nowadays we speak of "antennas". A phenomenon that was an essential feature of British life for over a quarter of a century is now no more than a curiosity remembered by the older generation. And if anyone should today be imprudent enough to construct one in his garden—assuming his modern property to be big enough—he would almost certainly be charged with contravening some local planning regulation! ●

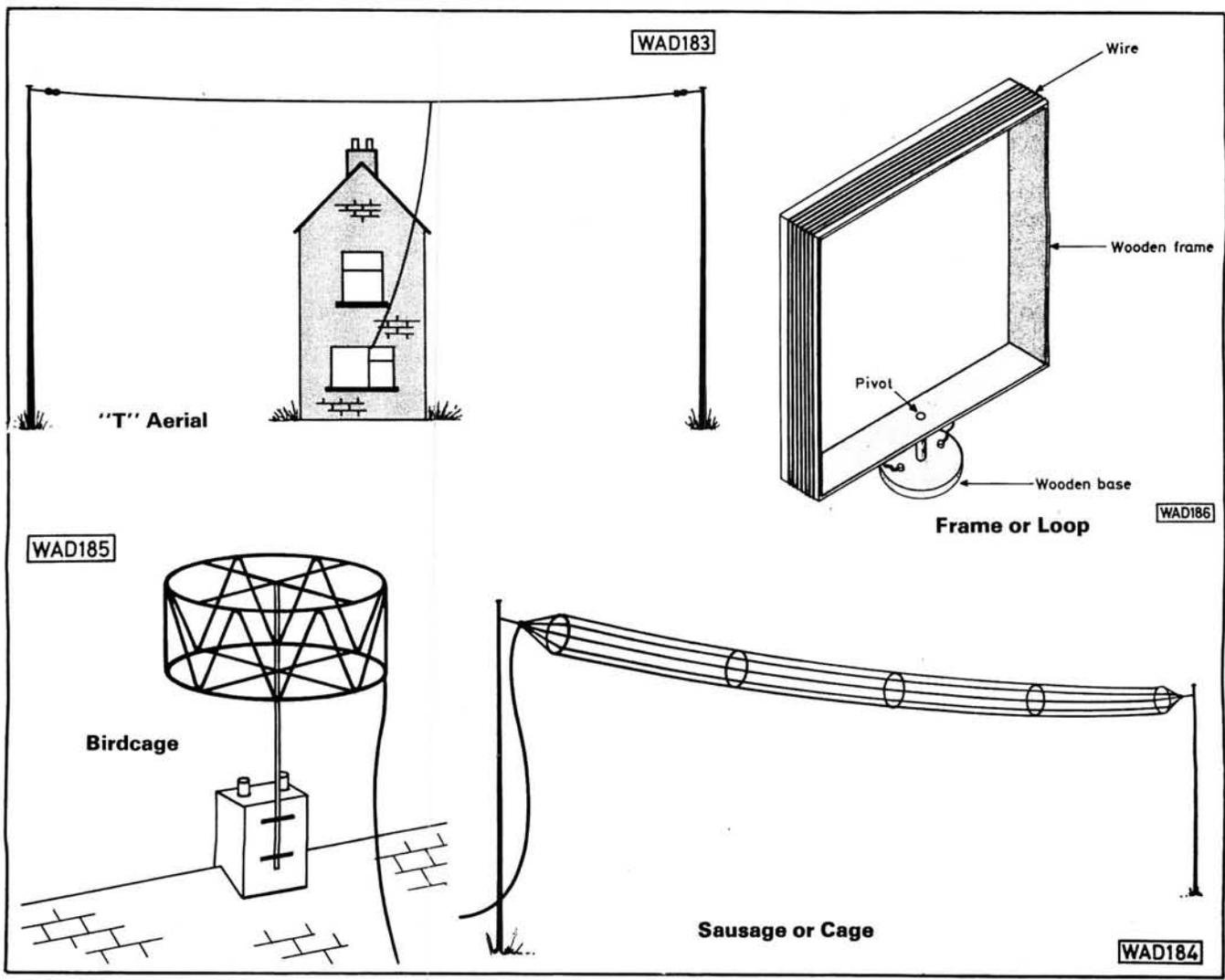

WATERS & STANTON ELECTRONICS

18/20 MAIN ROAD, HOCKLEY, ESSEX (0702) 206835
12 NORTH STREET, HORNCHURCH, ESSEX
TELEPHONE (04024) 44765

IF PRICES & SERVICE MATTER... GIVE US A CALL

OUR TWO BRANCHES STOCK VIRTUALLY EVERY
MAKE OF HAM RADIO EQUIPMENT.

TRIO - YAESU - ICOM - FDK - WELZ - AZDEN

FDK NEW M725X 2m FM



25w RF output
144 - 148 MHz
12½/25 KHz steps
Up/Down Mic Control
70cm Option
Mobile bracket/mic

**DISCOUNT
PRICE
£209!**

FDK NEW M750XX 2M FM/SSB/CW



20w RF output
144 - 148 MHz
5 KHz/100 Hz steps
Up/Down Mic Control
70cm Option
Mobile bracket/mic

**DISCOUNT
PRICE
£309!**

AZDEN PCS4000 2M FM



25w RF output
144 - 148 MHz
12½/25 KHz steps
16 memories/scanning
Up/Down Mic Control
Mobile bracket/mic


**SUPER
PRICE
£169**

JUST ARRIVED! "Super Snooper" RX40 Professional VHF monitor.

The RX40 is a new, highly sophisticated VHF monitor, packed into a remarkably small space. Built to professional standards, this unit will surely find application both commercially and for the enthusiast. It covers all VHF FM frequencies from 141.00 to 180MHz in 2.5kHz steps. This makes it suitable for all current channel spacings. Its comprehensive ranges include police, fire, ambulance, amateurs, marine, radio telephone, etc., etc. High sensitivity and complete portability enables the unit to be slipped into ones pocket and used as a "go anywhere" monitor. Frequency selection is by professional, thumbwheel selectors and power is via an internal ni-cad battery pack that provides up to 10 hours operation from a single charge (AC mains charger included). A detachable antenna is provided for. The built-in speaker provides good, clear audio with the facility of also using an earpiece and a squelch control enables the receiver to be muted when no signals are present.

FM
141-180 MHz

**PRICE SLASHED
THIS MONTH
£149
£119**

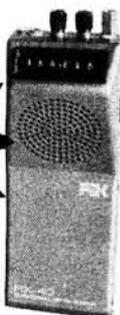

AIR BAND VERSION ATC720 £159

SEND SAE FOR
1983 CATALOGUE

ALL ITEMS IN STOCK
SENT BY RETURN

BARCLAYCARD ACCESS AND INSTANT CREDIT

E.&O.E.

MAIL ORDER SLIP to: Waters & Stanton Electronics, Main Road, Hockley, Essex.

Name.....

Goods required

Address.....

Please rush me the above. Cheque enclosed for £.....

Please charge to credit Card No.....

TRIO	TW4000	FM dual band mobile trans. 2m/70cm	469.00	2.50
	TS830S	160-10m trans./gen. cov. receiver	1,216.00	5.00
	AT930	Aut. ATU 80-10m ham bands	141.75	2.50
	TS430S	HF trans. 160-10m/gen. cov. receiver	736.00	5.00
	PS430	Mains PSU, built-in cooling fan	112.75	5.00
	SP430	Matching speaker for TS430S	29.50	1.50
	MB430	Mobile Mount bracket for TS430S	11.25	1.50
	FM430	FM option unit for TS430S	34.50	1.00
	TS830S	160-10m trans. with new bands	697.75	5.00
	VFO230	VFO with mem and digital readout	243.75	5.00
	AT230	All band ATU & power meter.	135.75	5.00
	SP230	Ex. speaker with switched filters	41.25	2.00
	YK88C	500Hz CW filter for TS430S	31.75	0.75
	YK88CN	270Hz CW filter for TS430S	37.25	0.75
	YG445CN	250Hz CW filter SPECIAL PRICE!	39.00	0.75
	TS530S	160-10m trans. with new bands	595.00	5.00
	AT130	100w aerial tuner - new bands	93.00	1.75
	TL922	160-10m 2kw linear. 3-500Z tubes inc	724.50	5.00
	MC50	Deluxe dual impedance desk mic.	30.75	1.75
	MC60A	Deluxe desk mic. with built in pre-amp	55.25	2.00
	MC35S	Fist mic. 50K impedance	14.75	1.25
	MC30S	Fist mic. 500ohm impedance	14.75	1.25
	MC40S	Up/down mic. for TR900/7800 etc.	14.75	1.25
	MC42S	Up/down hand mic. for TS930S	15.25	1.25
	LF30A	HF low pass filter, 1kw rating	21.25	1.25
	TS780	2m/70cm all mode transceiver	795.00	5.00
	TR9130	2m multi mode mobile/fixd station	433.50	2.50
	TR7800	2m FM syn. mobile/fixd station 25w	257.50	2.50
	TR7930	2m FM trans. with large LCD display	305.25	2.50
	TR2300	2m FM syn. portable trans.	152.00	2.50
	VB2300	10w amplifier for TR2300	65.75	1.50
	TR2500	2m FM syn. handheld	232.50	2.50
	VB2530	30w amplifier for TR2300	69.75	2.00
	SMC25	Speaker/microphone	16.00	1.00
	TR3500	70cm handheld trans. to match 2500	250.75	2.50
	TR9500	70cm syn. multimode mobile fixed.	395.00	5.00
	R600	Syn. Gen. Cov. receiver 150kHz-30MHz	257.00	5.00
	R1000	Syn. 200kHz-30MHz receiver	297.00	5.00
	R2000	Gen. Cov. Receiver	398.75	5.00
	VC10	VHF unit for R2000. 118MHz-174mH	113.00	1.50
	HC10	Digital station world time clock	67.50	1.50

YAESU	FT757GX	Gen. Cov. HF trans.	625.00	5.00
	FT980	New Gen. Cov. HF trans.	1,150.00	5.00
	SP980	Matching speaker	54.80	2.00
	FC902	9 band atu SWR/PWR meter.	135.00	5.00
	SP901	External speaker for 901 and 101	31.00	2.00
	FT101ZDFM	9 band HF trans. SSB-CW-FM	665.00	5.00
	FT480R	2M Multimode	395.00	
	FT102	9 band HF transceiver	685.00	5.00
	FC102	9 band matching atu	200.00	5.00
	SP102	External speaker plus AF filtering	49.05	2.00
	FM/AM	Unit for above	46.00	1.00
	FT77	SSB/CW 8 band 100w transceiver	459.00	5.00
	FM Unit		25.30	1.00
	FP700	PSU for FT77	110.00	5.00
	FC700	ATU for FT77	85.00	2.00
	FL2100Z	160-10m linear amplifier	475.00	5.00
	FT290R	2m multimode portable 2½ watts	249.00	2.50
	FT1790R	70cm multimode portable	299.00	2.50
	NC/WSE	2.2amp hour ni-cad pack for 290/790	22.00	2.00
	NC11C	230v AC charger for 290/790	9.20	1.00
	CSC1A	Soft carrying case for 290/790	3.85	0.75
	MMB11	Mobile mount for 290/790	24.90	1.75
	FL2010	Linear amp for 290R 2 watts o/p	59.00	2.00
	FT208	2m FM synthesised handheld 1 watt	199.00	2.00
	FT708	70cm FM synthesised handheld 2½ watts	209.00	2.00
	NC9C	slow charger	8.05	1.00
	PA3	Battery eliminator/charger 12v DC	14.20	0.75
	FT230R	2m 25 watt FM mobile transceiver	239.00	2.50
	FT730R	70cm 10 watt FM mobile transceiver	259.00	2.50
	FT726R	3 band all mode base station	699.00	5.00
	430T726	70cm module	230.00	2.50
	50T726	6 metre module	170.00	2.50
	SAT726	Full duplex cross band unit	90.00	2.00
	FRG7700	0.2-30MHz gen. cov. rec. digital display	335.00	5.00
	FRG7700M	As above but fitted memory unit	399.00	5.00
	MEMGR7700	Memory module option for above	98.90	1.50
	FRT7700	Antenna tuner unit for above	42.55	1.50
	FRA7700	Active Antenna	38.70	2.00
	YH55	VHF converters for FRG7700. Prices start from	74.00	1.50
		Padded 8ohm head phones	10.50	1.00



Tandy®

A 16-Channel Portable Scanner

£229⁹⁵

Now You Can Listen To Aircraft,
Hams and More - Wherever You Go
No Crystals To Buy!

Covers 68-88 MHz VHF-Lo, 144-148 MHz Ham,
108-136 MHz AM Aircraft, 138-144 MHz, 148-174 MHz VHF Hi,
380-450 MHz Ham, 450-470 MHz UHF-Lo, 470-512 MHz UHF-Hi

Direct-Access Keyboard Tuning of 22,884 Frequencies

Realistic PRO-30. A full-feature, microprocessor-controlled scanner with extended frequency coverage - in a compact size you can carry wherever you go! Scan up to 16 of your favourite channels continuously, or search a selected frequency range for new or unpublicised channels. Scan and Search in two speeds. Lockout feature temporarily bypasses unwanted channels. Big LCD display shows channels and frequencies being monitored or programmed as well as the status of the channels. Priority function monitors your favourite frequency while you listen to others. Frequency-tracking front end assures top sensitivity on all bands. Has jacks for external antenna and earphones. Requires six "AA" batteries or mains or DC adapter. Memory backup requires four silver-oxide batteries. 20-9131

NEW



NEW

... and A 60-Channel Programmable Scanner

£259⁹⁵

50 Public Service
and Aircraft
Channels
Plus 10 FM
Broadcast
Channels



Realistic PRO-2003. No crystals to buy - direct keyboard entry of 20,584 frequencies. Use the search circuit to find new channels. When you find one that sounds interesting, store it in memory! Has 2-speed scan and search, Scan Delay, individual channel-lockout, priority function and variable squelch control. Large easy-to-read display shows channel number, frequency, function and mode. Bands: VHF-Lo 68-87 MHz; FM Broadcast 88-107 MHz; VHF-Air AM 108-136 MHz; Ham 138-148 MHz; VHF-Hi 148-174 MHz; 410-450 MHz; UHF-Lo 450-470 MHz; UHF-Hi 470-512 MHz. Built-in speaker, telescopic antenna, plus jacks for headphone and external speaker. 3 1/8 x 11 1/4 x 9". With operating manual, mains operation or 12VDC negative ground. Memory backup requires 9V battery. 20-9117

All This
And More
At Your
Local

Tandy

Store

OVER 340 STORES AND DEALERSHIPS NATIONWIDE

Check your phone book for the Tandy Store or Dealer nearest you

Offers subject to availability Prices may vary at Dealers



Swap Spot

Have Philips N1700 long play video 8 hours of tapes—scratched, also Suzuki GT250 used daily up to last year. Would exchange either or both for h.f. transceiver plus cash if necessary, portable TV or w.h.y. Derek. Tel: 0621 828807 (Chelmsford). T658

Have 5m Fish Boat clinker hull/motor 6 h.p. L/S Johnson Oars etc., value £500. Would exchange for radio gear like SS105, KW Tentec FT-101 etc. Also have KW 2000 for motoret would split for acquisition of h.f. gear RX etc. G6RGH. Cannock, Staffordshire. Tel: Stafford 46306 (not QTHR). T667

Have £200 worth of Crest Hotel voucher valid to 1984. Would exchange for 144MHz (2m) transceiver. Tel: 0365 22014. T646

Have Cossor dual-beam blue screen 'scope, Heathkit AO-IU signal generator, Practical Electronics digital multimeter, Commodore programmable calculator, Realistic transistor tester. Would exchange for good airband/144MHz scanner, 144MHz handheld transceiver, good s.w. s.s.b. receiver. Andy. Tel: Macclesfield (0625) 614510. T647

Have Vic 20 Computer Cassette unit, joystick, four ROM cartridges. Under 6 months old, v.g.c. Would exchange for 144MHz handheld TX/RX. D. Gallagher. Tel: (0524) 811715. T693

Have Sony ICF 2001 s.w. scanner radio and manual. Also Realistic PRO-22 scanner with crystals, both as new. Would exchange for any good quality 144MHz multimode transceiver. A. Cocking, 31 Dryden Crescent, Stafford, ST17 9YH. T674

Have Datong Morse tutor, Morse cassettes and Homebru practice key. All v.g.c. Would exchange for good power/s.w.r. meter or ZX81 Computer. Alan. Tel: 0279 504728 evenings and weekends (Bishop's Stortford). T677

Have 40 ch f.m. hand held CB 4 watt Harvard 410T with NiCads and charger, also magmount antenna, rubber duck antenna. Want h.f. RX Drake 2B or similar or marine v.h.f. RX. W. H. Cross, 45 Rhiwlas Street, Liverpool L83 UA. T684

Have an Olympus Trip 35 camera, leather case, new. Plus a mobile 2 metre FDK multi-11 23 channel with 4 channel scan good condition. Wanted IC-2E or similar hand set. Phone Jim G6MJS. Tel: 01-556 4050 (Leyton, London). T686

Have Varicap v.h.f./u.h.f. RX, tunes 50MHz-470MHz, no gaps a.m./f.m. internal 240V p.s.u. very sensitive. Would exchange for any 6ch 144MHz handportable, pair of Pocketfones, PF5 etc., or w.h.y. similar. Tel: 02074 4342 evenings/weekends (Rowlands Gill). T700

Have Yaesu FR-50B amateur RX. Mint condition, 100kHz c.c. 1.8MHz-28MHz. (Mods: By Importer). Would exchange for synthesiser type, keyboard. Must have rhythm unit. Vic Stimpson G3SLU. 67 Alliance Avenue, Hull. Tel: 0482 55906. T713

Have Braun T1000CD communications receiver, 13 wavebands. Also have Audioline f.m. CB 40 channel, new in box. Would exchange for computer—Sharp MZ80K or w.h.y. Can deliver. Findley, 27 Keytes Lane, Barford, Warwick. T729

Have Midland 2001 CB new and boxed with crystal filter fitted. Would exchange for 144MHz pre-amplifier or w.h.y. for 144MHz. Tel: Cambridge 834263. T730

Have Cossor twin-beam 'scope, model 1049 MkIV. Would exchange for a 144MHz transceiver—any type considered. 35 Mill Road, Gillingham, Kent. Tel: 0634 54049. T731

Have Heathkit Mohican in excellent condition—modified to accept f.m., s.s.b., n.b.f.m. Would exchange for a four-track reel-to-reel or small synthesiser. M. Duddridge, 127 Rhode Lane, Bridgwater, Somerset. T733

Have following test equipment with manuals: Marconi Q-meter TF329G, Component Bridge B521, Capacitance Bridge Marconi TF1342, Inductance Bridge with Capacitance Attachment Sullivan AC100, Boonton Q-meter 100-A, Audio Tester Marconi TF894A. **FREE** to anyone who collects the lot. Tel: Ruislip 75769. T732

Have boxed 16K Video Genie computer with built-in cassette. Complete with much software and books, approximate value £200. Would exchange for 144MHz multimode portable such as FT-290R or similar. Steve. Tel: 0777 818427 (Retford, Notts). T735

Have ZX Spectrum + two cassettes (Planetoids and Space Raiders), Atari console + three cartridges (Space Invaders, Asteroids and Tank Battle), Yashica 8T2 standard 8mm movie camera (clockwork) and a Eumig standard 8mm projector. Would exchange for a 144MHz multimode mobile/fixed station. Will pay postage from me to you. J. D. Bolton, 10 Bownes Road, Coniston Park Estate, Timperley, Cheshire. T745

Have Katsumi EK121 electronic keyer plus EKM-12 monitor. Would exchange for ZX81 (16K RAM) with manual, 144MHz s.s.b. transceiver (non-working repairable accepted) or w.h.y. C. Ansell G6NBD. Tel: 0474 59929 (Gravesend). T746

Have Polaroid Instant Movie outfit, including zoom lens, viewer, filters and indoor lights. Value £70. Would exchange for 144MHz linear amplifier, beam or any 144MHz equipment considered. Bob Griggs G6ZGL. 8 Paradise Street, Accrington. Tel: 31081. T747

Have Realistic TRC1001 legal CB handheld with p.s.u., mic, rubber duck and mag-mount antennas. Would exchange for a good 144MHz transceiver. T. Jones, 53 Central Drive, Shotton, Deeside, Clwyd. T750

Have Microwave Modules MMS1 Morse Talker v.g.c. Would exchange for 432MHz f.m., 144MHz s.s.b., h.f. mini beam + rotator, printer for RTTY, anything considered. Richard G4SHD. Dudley, West Midlands. Tel: 235931. T762

Have 6m tower in two 3m sections, ideal for amateur, lack of planning permission forces swap. Would exchange for Realistic DX160 or 100 receiver or CB rig with base antenna. O. Haigh, 3 Brora Close, Lakes Estate, Bletchley, Milton Keynes, Bucks. T763

Have NEC CQ-P-2200E 12-channel 1/3W 144MHz f.m. portable/mobile transceiver. Would exchange for SX200N scanning receiver or similar. Also have Binatone five star 40 channel f.m. CB rig. Would exchange for air-band monitor CD-6000. J. L. Perez, Trent House, 24 Ormonde Gate, Chelsea, London SW3. Tel: 01-352 7847. T764

Have Yaesu FRG-7700M with 500kHz filter, immaculate condition. Would exchange for Trio R2000 in same condition. No cash, no offers, no deals, just a straight swap. Eddie. Tel: 01-624 2546 (evenings) or 01-257 5032 (office hours). T765

Have Yamaha A55 Electone organ, 12 auto rhythms, also Binatone 40 channel CB rig and power unit (both new). Would exchange for h.f. transceiver or w.h.y. Tel: 0753 653945 (Iver). T766

Have Olympus OM1, 50mm and 200mm lens, motorwinder, 2X converter, set of extension tubes, National flash with adjustable and zoom head and aluminium case. Would exchange for Icom R70. Tel: Nottingham 278912. T767

Have Yashicamat t.l.r. camera with leather case and tripod, both absolutely mint condition. Would exchange for decent a.t.u. e.g. KW Supermatch or SEM Tranzmatch 1.8-28MHz. F. S. Richards, 9 Dales Grove, Worsley, Manchester M28 5JW. Tel: 061 790 0866. T768

Curing **TW1** to MF/HF Reception

by **A. J. Cawthorne T.Eng(CEI) FSERT G3TDJ**

This article describes work done by the author to overcome annoying r.f.i. caused by line timebase radiation from the home television receiver. The work was prompted simply by the fact that, with the television on, many frequencies, particularly m.f., were unusable. Additionally severe r.f.i. caused by fluorescent lighting was cleared at the same time.

Essentially practically orientated there is no attempt at theoretical reconciliation. From the outset the writer was determined to solve or improve the r.f.i. problem on the communications receiver, a much modified FRG-7, without being "bogged down" or swayed by worries of correct impedance matching etc. In the writer's experience most modern communications receivers have more than adequate sensitivity and one need not be too concerned with receiver-antenna impedances, indeed how much input

attenuation seems to be the order of the day rather than the use of antenna tuners, pre-amplifiers and other expensive and often unnecessary "bolt-on goodies".

First thoughts on improving the r.f.i. problems were by use of an active antenna installed some distance from the "noisy" home environment, using the wide band matching to low impedance facility inherent in these devices and feeding the output signal via screened cable to the shack. It was difficult to justify the relatively high purchase cost of these admirable devices especially since it might not have cured the problem. A cheaper approach would have been to build an active array, but this faces the constructor with a tricky design problem if one is to avoid the pit-falls of low noise wideband amplification with suitable strong signal handling characteristics.

The writer had previously experienced considerable success with m.f. loop antenna fed to the receiver via a balanced screened transmission line and balun¹. It was decided therefore to extend this idea to the ubiquitous general purpose receiving antenna, in this case an 18.2m "T", and attempt to transfer the collected energy via wideband transformers and screened balanced transmission line through the "noisy" area to the shack.

Practical Applications

No originality is claimed for the principles involved. This article describes a cheap and simple practical application of ideas gleaned from books and articles^{2,3,4} which the writer would recommend as excellent further reading. Reference 2 provided the basic idea of an anti-interference antenna system, seemingly no longer available commercially. References 3 and 4 provide the details one requires to wind wideband transformers for amateur applications.

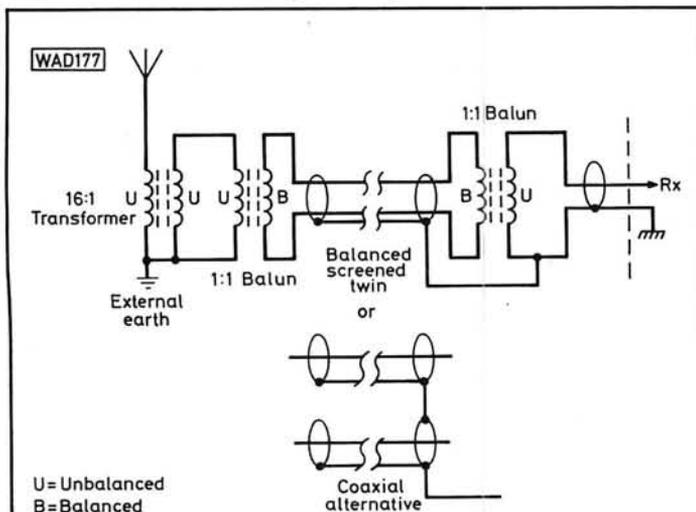


Fig. 1


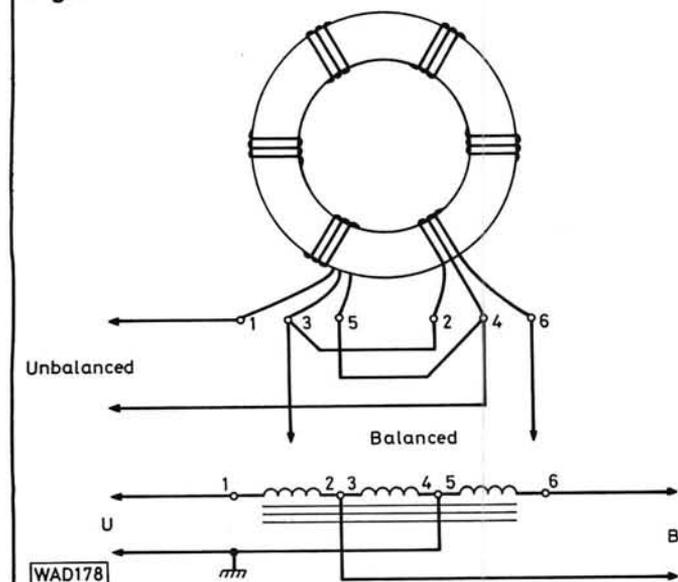


Fig. 2

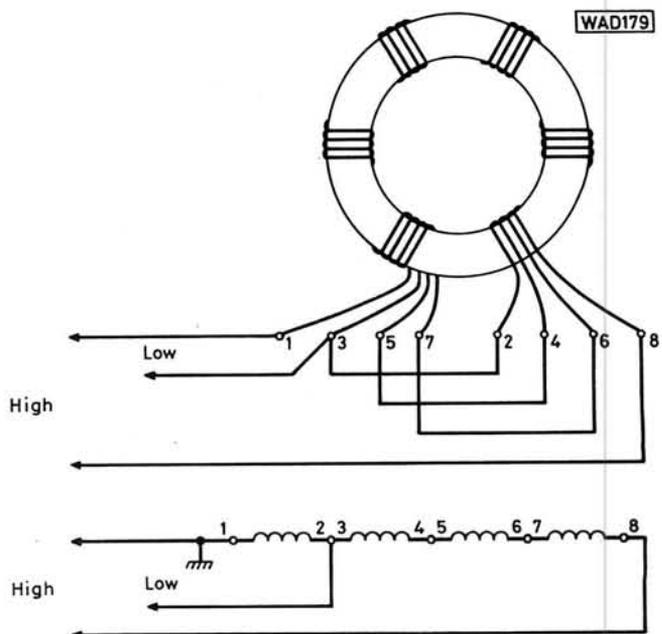

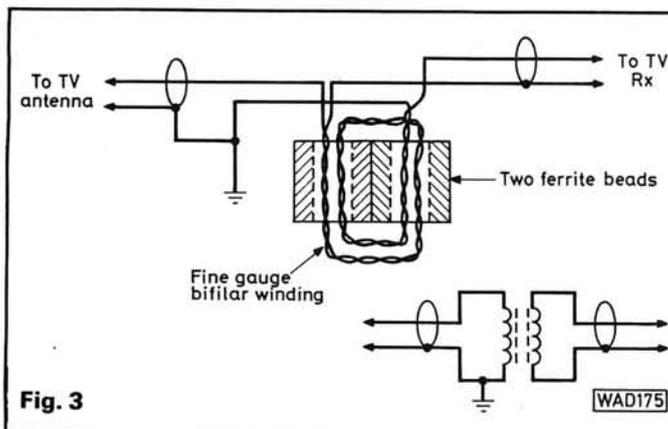


Fig. 3

Baluns

Fig. 1 shows the overall set up which is basically a balanced screened transmission line with 1 : 1 balun transformers at either end, at the receiver end the balun allows connection to the unbalanced receiver input, at the antenna end the balun allows connection to the unbalanced antenna system. A second, impedance step-up, wideband transformer is used at the antenna end to connect the antenna. Two transformers are used here simply to separate transformer functions and thus greatly simplify design. Reference 4 details several unbalanced to unbalanced step-up designs and the 16 : 1 version was chosen for this application.

Ideally the transmission line should be an r.f., screened, balanced twin feed. However, a most suitable alternative of course is two lengths of coaxial cable used "in parallel" the screens being joined together at the receiver end and grounded. In this application the FRG-7 receiver was converted to a single antenna input. Note that the ground connection to the antenna winding of the first transformer must be separate and not connected to the transmission line screen. As shown the transmission line outer screen must be left unterminated at the antenna end. This avoids a ground loop which will most certainly compromise the overall noise reduction available.

Wideband Transformers

Considering now the construction of the wideband transformers. At first this was thought to be a complex task but in fact can be done easily. Tests were carried out on various toroidal cores. Ferrite material was finally chosen to minimise the number of turns required. Several of the very cheap 38mm ferrite rings were to hand. These are currently widely advertised as interference aids against TVI. Initial tests to determine certain core characteristics were a little disappointing. The cores seemed far happier at hundreds of kilohertz rather than the megahertz required. However sufficient faith to "press on" was placed in Reference 4 which mentions that "it is common to find low frequency ferrite cores in h.f. applications since at high frequencies the core material tends to vanish electrically".

Two standard 1 : 1 baluns were wound for each end of the transmission line. These are trifilar wound, i.e. three wires wound on together. After a little experimentation a 12 turn design was adopted. The three windings are connected in series and the connections for balanced and unbalanced identified as in Fig. 2. The 16 : 1 unbalanced to unbalanced step-up transformer is wound on an identical core, 12 turns are again used but in quadrifilar fashion. Again the four windings are connected in series and the low impedance winding and high impedance antenna winding identified as in Fig. 2.

It does help to use wire with different coloured insula-

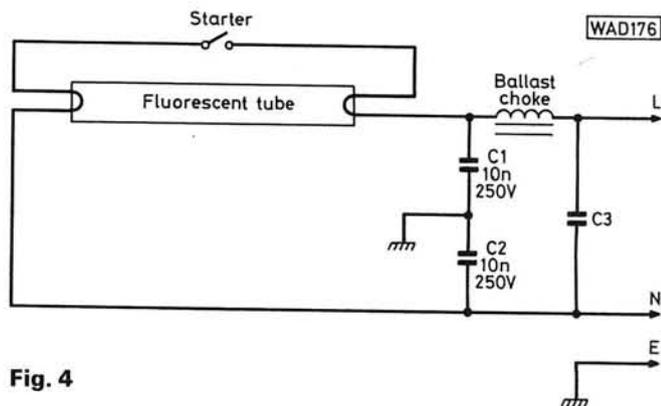


Fig. 4

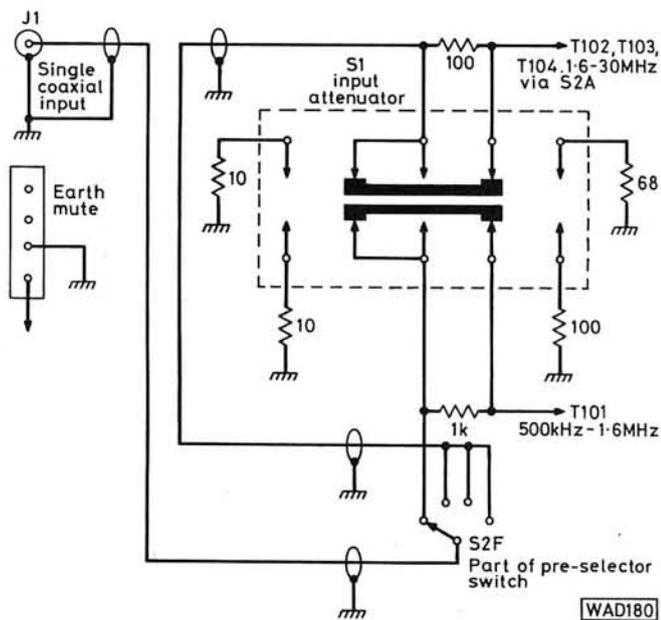


Fig. 5

tion for each winding. Single core insulated cable is used of about 20 s.w.g., but this is not critical.

In the writer's installation the antenna is fed into the loft through the eaves together with an external earth. This allows the two transformers at the antenna end to be inside. For external use suitable watertight housings should be used for the transformers.

Braid Breakers

One additional precaution was taken at this time, this was to install a simple braid breaker in the television receiver antenna feeder. Again no originality is claimed for this work, the writer using a braid breaker described in reference 5.

The braid breaker is shown in Fig. 3. It is constructed using two ferrite beads and bifilar winding two fine gauge wires as shown. Reference 5 recommends that the braid breaker be fitted 1 metre from the television set. In the writer's installation this was conveniently installed inside the wall mounted coaxial socket box. It was found very beneficial to ground the television antenna cable outer screen at the aerial side of the braid breaker. Note this grounding must be done at the antenna side of the braid breaker to avoid grounding the television receiver.

Considering now the results. To put the r.f.i. problem

into perspective at m.f. and low h.f. timebase interference registered a disgusting "S9 + 15dB" (whatever that might actually represent). Whilst as already stated the objective was to remove or reduce this interference level an overriding concern was that the transformers and transmission line would function as an unacceptably high value attenuator.

It would be a brave man indeed to claim that there was no degradation of incoming wanted signals, but over several months of intensive testing no noticeable reduction could be determined—much more to the point was the effect on interference levels. With the receiver tuned to 1.8MHz, normally a particularly noisy part of the spectrum, interference was reduced from the "S9 + 15dB" to not registering on the meter. Timebase noise was still audible above band noise but was sufficiently low to cause little or no hindrance.

As a further test, to clearly establish where the remaining interference pick-up was occurring, the antenna was disconnected from the first transformer and replaced by a 1000 ohm resistor. With this configuration no signals were audible but much more importantly no interference was audible either. Clearly then the system was now limited by timebase radiation directly into the antenna proper, this has proven to be relatively inconsequential and the television receiver now presents little barrier to m.f./h.f. reception.

Fluorescent Lights

As mentioned earlier fluorescent lighting within the house caused considerable r.f.i. This was much reduced with the system described in use but the writer was somewhat disappointed with the result. The suppression circuit detailed in Reference 2 was fitted with complete

success. This is reproduced here as Fig. 4 for those who suffer from similar problems. Capacitors used were 10nF 250V IS types from Maplin Electronics. The power factor correction capacitor is C3 and is left in circuit.

FRG-7 Modifications


Like so many receivers of its ilk the FRG-7 has separate antenna inputs for m.f. and h.f. This was considered to be a nuisance with the single low impedance antenna feed described. A simple modification shown in Fig. 5 allows single coaxial input to the FRG-7. This modification is easily implemented and easily reversible should the need arise.

A useful "spin-off" from the antenna system described has been the removal of the effect of a natural phenomenon. The writer was "plagued" with periodic rain static with conventional antenna systems. The d.c. path to ground provided by the first wideband transformer prevents any build up of static on the antenna.

The system described can of course be used with other types of antenna such as long wires and whips. The further the actual antenna from the source of the noise the better, within reason one need not be too concerned with losses on the transmission line.

References

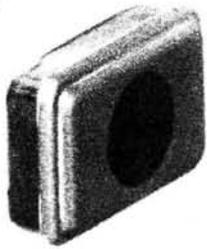- 1 *Practical Wireless* December 1981 page 70.
- 2 *The Practical Aerial Handbook*. Gordon King.
- 3 *Toroids in H.F. Applications*. N.W. Sedgwick G8WV. *Short Wave Magazine*, March 1979.
- 4 *The ARRL Handbook 1982*. Chapters 2 and 6.
- 5 *I.V.T. and Braid Breakers*. E. Margetts, GM4BOA. *Technical Topics. Radio Communication*. March 1976.




"... Have not yet heard an FT-101 sound any better than when used with The Key Element..." — Paul, G3AWP

"... I now have a comfortable feeling that my audio is better than the rig was originally capable of..." — Ken, W9UBS

"... Thank you for the fine report: all reports to date have been excellent..." — Lee, WISE

The Key Element

SSB clarity starts at the microphone...

Heil Sound, the company that pioneered proper audio equalization techniques for major performing groups and communicators, invites you to be part of one of the biggest advancements in Single Sideband transmission since the "Donald Duck" vs. AM days.

If you are not satisfied with the "sound of your station" — it's no wonder — most "communications" microphones used today were designed for "public address" use, not for sophisticated SSB techniques.

No one microphone can be all things to Hams, so this new

HC-3 element and HM-5 mic were developed *only* for maximum clarity on SSB transmissions. The response of this tiny ceramic element rolls off sharply under 350 Hz and above 3100 Hz with a peak at 2400 Hz for *high articulation* in the speech range. Hams who care about maximum results in getting over, around and through DX pile-ups now have another weapon in their arsenal... The Key Element!

You can easily install this small, advanced HC-3 element, with its broad-range impedance-matching characteristics, into virtually any microphone case you own, or purchase the custom HM-5 with HC-3 installed.

For those who desire the ultimate audio into and out of your transmitter/transceiver, consider the ideal combination of the Heil EQ-200 audio equalizer and HM-5 microphone.




All prices include VAT and Carriage, E. + OE.

For further information, or to order the HC-3 cartridge element at £17.99, the HM-5 SSB microphone at £49.95 or the EQ-200 at £45.95 contact our Sole European Distributor, Amcomm Services Ltd., 194 Northolt Road, South Harrow, Middlesex or Telephone 01-422 9585.



Hearing Is Believing...

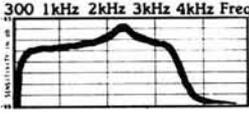

AR Station with a Difference

Probably the only amateur radio station established in a girls' school and run by licensed pupils is currently operating from Harrogate College, an independent girls' school with approximately 450 pupils, the majority of whom are boarders, whose ages range from 10½ to 18 years.

Amateur radio was first introduced to the school six years ago when David Andrews G4CWB joined the staff as Director of Music, and a year later was joined by Richard Horton G3XWH, appointed Head of Physics.

Shortly afterwards these two gentlemen ran a 24-hour exhibition station as part of the school's sports/open day. As a result, several girls expressed an interest in obtaining licenses and setting-up a school station. And that's how the bug, which most radio amateurs are so familiar with, was introduced into the "dorms" of Harrogate College.

Subsequently, David and Richard ran an RAE course, to be rewarded with five passes in the following May examination. During the course of the year a temporary "shack" was estab-



lished off the Physics Lab and with the loan of David's FT-101B the school station came on the air. Three more RAE successes were obtained the following year, and the 24-hour station became an annual open day event.

For the 1982 open day they were able to move into a purpose-built shack located in a section of their new Hobbies Centre, equipped with among other gear, their own TH3 Mk3 h.f. beam, 2m colinear and FT-208R transceiver.

During 1983 the school celebrated its 90th anniversary and the 5th year of operating GB2HC, the 24-hour special

event station. Additionally, they were most fortunate in marking this event with the delivery of a new h.f. rig, the Trio TS-430S.

The photograph shows three of the four licensed girls present in the school this year who are, left to right, Dione G4OOV (Richard's daughter), Sarah G6GGK and Danielle G6RHN (Head Girl), the fourth girl being Nora G6RHO.

Harrogate College's station, G4LYZ, is now very firmly established as one of the hobby activities within the school and the RAE course continues to attract a keen group of girls each year.

Amateurs in Space

To commemorate the operation of an amateur radio station from space by W5LFL aboard Space Shuttle "Columbia" STS9, a special philatelic cover (envelope) is to be issued in conjunction with the Solomon Islands Radio Society H44SI.

The cover will state "First Amateur Radio Operation from Earth Orbit" within the AMSAT logo.

A 45c Solomon Islands postage stamp featuring orbiter Columbia will be affixed to the cover and cancelled on the first day of operation.

The cover will be available from: PO Box 81, Honiara, Solomon Islands, at a cost US \$1.00 or equivalent (US \$1.00 or five IRCs) for direct mailing by air.



Covers can be supplied in mint condition within a sealed envelope, by air for an additional US \$1.00 for up to 10 covers, i.e. one cover addressed and mailed US \$1.00, one cover, mint, within envelope US \$2.00, five covers, mint, within envelope (5 + 1) US \$6.00.

At the time of going to press the final launch date and programme had not been confirmed.

RAF Halton Award

The RAF Halton Award is available to all licensed amateurs and listeners for contacts or confirmed reception reports with stations connected with RAF Halton Amateur Radio & Electronics Club, between 10 June 1983 and 30 June 1984 on all bands and modes.

A total of 25 points is required to qualify, and points will be awarded on the following basis: 10 points per QSO with Club Stations (G4SQC, G6WCR, GB2HAS and GB2HAR), and 5 points per QSO with Club Members.

Further information (sae please) or claims (£1 or 5 IRCs) to: G8BVJ, 6 Mansion Hill, Halton, Aylesbury, Bucks HP22 5NL.

PW QRP Contest Winners

Continuing with our policy of meeting as many of our readers as possible during the year Practical Wireless attended the Welsh Amateur Radio Convention held at Blackwood, Gwent. The event was a great success and well attended.

By coincidence the PW QRP 144MHz contest was won by a group of newly licensed amateurs all mem-

bers of the Blackwood & District ARS so the opportunity to present them with their trophy was not missed. The convention was opened by Don Baptiste, President of the RSGB, and he very kindly agreed to present the cup to the winning team.

Our photograph shows (left to right) GW8UCQ, GW6NEO, Don Baptiste, GW6TGW and GW6RPZ. The club callsign used by the winners is GW6GW.



Repeater News

GB3SF, the Sheffield University experimental s.s.b. unit, has now been licensed for a one-year period. It is expected to be some time before the unit becomes operational.

The RWG is now called the Repeater Management Group and as such is a new independent committee of the RSGB. We have been asked to emphasise that the primary function of the committee will remain that of a **working** group.

Following discussions between the RSGB and the DTI, an agreement has been reached allowing the RSGB to submit proposals for up to 12 repeaters (v.h.f./u.h.f.) in total, per annum. It is expected that this policy will be in force for the foreseeable future and will commence 1 January 1984. In practice, proposals will be sent every six months. These proposals will not apply to beacons or microwave repeaters.

Anyone wishing to propose a repeater installation should contact RSGB HQ prior to submitting details, whereupon a copy of the DTI specifications will be provided.

A 29MHz repeater may be licensed to provide information on the viability of such units within IARU Region 1. Details and observations will then be correlated and passed for discussion at a future conference.

The 1984 IARU Conference will, amongst other items, receive two papers from RMG chairman, Mike Dennison G3XDV, on the subject of u.h.f. repeater planning. A proposal to formally adopt the UK RB system for

Region 1 will be introduced. If this occurs, future bandplanning could allow the use of all 16 RB repeater channels.

Latest u.h.f. repeaters to become operational are GB3OH—Sterling on RB4 (reports please to GM4OMT, QTHR) and GB3TD—Swindon.

The v.h.f. repeater GB3WD—West Devon on R4 came on-air on 8 September. Reports suggest initial QRP operation. However, at the QTH of Technical Editor G8MCP, approximately 160km away, signals have been received just above noise, via a low-gain omni-directional vertical antenna, which confirms the effectiveness of the repeater's 630m a.s.l. site. Further reports please to G6IEP, QTHR.

The RSGB has agreed a site change for GB3LD on R3, the Lakeland v.h.f. repeater, to a local TV mast.

During the summer Mike Dennison G3XDV delivered a lecture to the second IEEE Conference of Radio Spectrum Conservation Techniques, based on the extensive UK 432MHz amateur repeater network. Reactions from the professional body were very encouraging with many delegates declaring their joint "amateur" status.

Information received from the Cambridgeshire Repeater Group, builders of the UK's first v.h.f. repeater GB3PI on R6, reveals that moves are under way to add relaying facilities, with message store and forward, to form an "electronic post-box", to the RTTY repeater GB3PT on R12 at Barkway. Should the proposals be accepted by the DTI/RSGB RMG, the standard CCITT telephone modem frequencies, at 300

baud, will be used. The explosion of home computer usage could make this a busy repeater soon. There is no truth in the rumour that successful access will only be obtained after zapping ten Klingons!

Also, GB3PS, the 1.3GHz f.m. voice repeater to be on RM3 at Barkway, is currently on soak test in Cambridge. In operation, following a successful access with toneburst, the device will switch from beacon to repeat mode, superimposing a 100Hz sub-audible tone onto the through audio. When the input carrier is dropped, it replies with a "K" unless the input signal is off-frequency or overdeviated, whereupon a National Semiconductor Digitaltalker takes over and gives the user a report to aid rig alignment. When installed at its final site the device will operate via a pair of slot antennas, fed with LDF 550 Heliax to give omni-directional coverage with horizontal polarisation.

After a period of nearly two years, the Central Kent 432MHz repeater, GB3CK on R80 has been completely rebuilt and restored to service.

Following many frustrating hours trying to obtain the necessary isolation between transmitter and receiver, with minimum insertion loss, the repeater group decided to seek expert advice.

Via the good offices of Mike Dennison G3XDV, RMG Secretary, the group were put in touch with Mike Senior G4EFO, an expert in this field, who spent a great deal of time setting up the cavity resonators.

The GB3CK repeater group through their Manager, Jeff Clark G3TIS, offer grateful thanks to all concerned.

Stolen Rig

A Yaesu FT-290R 144MHz multi-mode transceiver was stolen from a hotel room in Shaftesbury on Friday 7 October 1983.

The serial number is 3C26038 and the owner is offering cash rewards for its recovery.

If you have any information concerning this rig please contact the owner: *D. M. Cranvey G6XPV, tel: (0703) 613948 (home), (079 47) 382 (work) or Shaftesbury Police, tel: (0747) 2231.*

CB "Burners" at Petrol Filling Stations: A Warning

Following reports in the press and on radio recently about the use of high-powered amplifiers known as "burners" to disrupt the operation of petrol

pumps at filling stations, Mr. Alex Fletcher, Minister for corporate and consumer affairs in the Department of Trade and Industry, issued the following warning:

"All use of radio transmitters in petrol stations is potentially hazardous. The Code of Practice for Citizens' Band radio (available free at Post Offices) specifically draws attention to this. The use of high power transmitters such as a CB set coupled to an illegal 'burner' adds considerably to the risk of causing an electric spark close to the filling nozzle. An explosion could occur in some circumstances.

"The public are warned always to switch off transmitting equipment when entering a filling station forecourt and never to use CB 'burners' in a vehicle which is being filled with petrol.

"The use of a CB set with a burner is in any case illegal because of the interference it causes to domestic radio and

TV reception and to the emergency services; offenders may be imprisoned for up to three months and fined up to £1000. The sale and possession of 'burners' may be made illegal following the passage of the Telecommunications Bill at present before Parliament."

RAE Short Course

It is proposed to hold an RAE Course at the Barr Beacon Community Centre, Old Hall Lane, Pheasey, Walsall commencing on 19 January 1984 at 7.30pm.

The course will run for 10 weeks and the fee will be £7.50, however, school pupils and unemployed enthusiasts may join the course free of charge.

For further details contact the lecturer: *Frank Fear, 185 Longwood Road, Aldridge, Walsall, West Midlands WS9 0TB. Tel: (0922) 52706.*

Practical Wireless, January 1984

DRESSLER AMPLIFIERS

These are high power 240V linears using 4C x 150 or 4C x 250 or 4C x 350 Eimac Tubes NOT using the grounded Grid system. Fully protected, no thermal damage to PA finals possible.



DRESSLER AMPLIFIERS

D70 70cm 200wfm 400 PEP £700.00
 D200 2mtr 300wfm 600w PEP £595.00
 D200S 2mtr 400wfm 1KW PEP £695.00
 D200C 2mtr 100w. Few left at £275.00

GASFET DRESSLER PRE-AMPS

VV2 £44.00
 VV2GAAS 150W £75.00
 VV200GAAS 750W £85.00
 VV200GAAS 1KW £85.00
 VV2RPS S0259 Non switching £22.00
 VV2RPS N Type £24.00
 VV7RPS S0259 £22.00
 VV7RPS N Type £24.00
 New VV200 VOX £84.00 250w PEP VOX

Powered by the linear or with separate interface.
 0.7 - 0.9dB signal to noise
 0.2dB insertion loss

GASFET MASTHEAD PRE-AMPS

3SK97 GASFET Available separately £5.00



SPECIAL OFFERS

TRIO/KENWOOD
TR9130 25W
 2 MTR MULTIMODE
£395.00

FRG 7700



£275 without memory
 £340 with

FT 102 £625.00



FT 726



£625

INC. 70CMS + SATELITE
 £920.00

COMPUTERISED ROTATOR



PRICE SLASHED
~~£350~~

NOW £315.00

ICOM R70



P.O.A.

ICOM IC251



£469

ICOM

IC2E

P.O.A.



G4JDT
 HARVEY

EAST LONDON HAM STORE

H. LEXTON LIMITED

191 FRANCIS ROAD LEYTON E.10
 TEL 01-558 0854 TELEX 8953609 LEXTON G
 01-556 1415

YAESU

FT1 Gen. Coverage Tx/Rx £1200.00
 FT980 Gen. Cov. Cat System £1050.00
 FT757 Gen. Coverage £690.00
 FT102 150W 10m-160m £640.00
 FC102 A.T.U. £190.00
 FV102 V.F.O. £220.00
 SP102 Speaker £45.00
 FT77 — NEW — inc. M/C £425.00
 FP700 £95.00
 FC700 £85.00
 FTV700 D.M. £179.00
 FRG7700 Gen. Coverage Rx £265.00
 FRG7700 M £335.00
 FT790 FM/SSB £295.00
 FT290R with mods FM/SSB £249.00
 FT208 2mtr portable FM £199.00
 FT708 70cm portable FM £210.00
 FT230 2mtr FM mobile £220.00
 FT730 70cm FM mobile £259.00
 FT726 16-20-70 (X Band) £625.00
 FRV7700A 118-150 £60.00
 FRV7700B 50-60/118-150 £75.00
 FRV7700C 140-170 £65.00
 FRV7700D 70-80/118-150 £72.00
 FRT7700 Aerial Tuner £42.00
 FRA7700 Active Antenna £40.00
 FF5 Filter £9.95
 MMB11 FT290 Car Mount £24.00
 NC11C Charger £9.50
 NC8 Base Charger FT208/708 £45.00

DATONG

D70 Morse Tutor £56.35
 PC1 Gen. Coverage converter £137.00
 FL1 Agile filter £79.35
 FL2 Active filter £89.70
 FL3 Angle filter & notch £129.37
 ASP Auto clipper £82.80
 D75 Manual clipper £56.35
 RFC Speech clipper £29.90
 AD270 Indoor active ant. £47.15
 AD370 Outdoor active ant. £64.40
 RFA Wide band AMP £33.92
 ANF Auto notch & filter £67.85

DIAWA

CN620A. £57.00
 CN1001. Auto A.T.U. £150.00
 CNW419. 500W PEP. Gen. Coverage A.T.U. £130.00
 AF406. Active filter
 AF606 P.L.L. Active filter £60.00
 DR7500X £110.00
 DR7500R £120.00
 DR7600X £160.00
 DR7600R £170.00
 Kenpro KR400 inc lower clamps £110.00
 KR250 £45.00
 Hirshman Hitro 250 £55.00

TRIO/KENWOOD

TSS930 Gen. Coverage Rx/Tx £1150.00
 AT930 ATV £139.00
 TS530 H.F. P.O.A.
 R2000 £380.00
 TS430 H.F. £395.00
 TR9130 £690.00
 TR2500 2mtr portable £219.00
 AT230 ATU £135.00
 PS430 PSU £110.00
 R600 Receiver. AM/SSB £220.00
 TR3500 70cm portable £245.00

SMC 25 speaker mic £56.35
 PB 25 battery pack £137.00
 MSI Strand mobile £79.35
 R2000 Receiver £89.70
 VC10 - Converter £129.37
 R600 Receiver £82.80
 SWR 100A £56.35
 SWR 100B £29.90
 SWR 200 £47.15
 MC55 Mobile mic £44.15
 TW400 UHF/VHF £24.00
 VSI Voice synthesizer £259.00
 TM201A 2HTR P.O.A.
 FC10 Remote display P.O.A.

STANDARD

See the new Standard C5800 Multimode 25W £359.00
 SSB/FM/CW 2mtr £359.00
 C58 2mtr FM/SSB/CW £359.00
 C78 70cm portable £239.00
 C7900 70cm mobile £239.00
 C8900 2mtr mobile £219.00
 C5800 2mtr FM/SSB 25W £359.00
 C1100 2mtr portable £139.00
 Plus All Accessories

TONNA

50 5 ele £34.00
 144 4 ele £14.00
 144 9 ele £17.00
 144 9 ele cross £32.00
 144 9 ele portable £20.00
 144 13 ele portable £31.00
 432 21 ele £29.00
 435 21 ele ATV £29.00
 432 19 ele £20.00
 432 19 ele cross £34.00
 1296 23 ele £25.00
 144/432 9+19 ele cross £34.00
 Power splitters and portable masts in stock.

MORSE KEYS

Morse keys Swedish brass key £49.00
 HiMound HK707 £12.95
 HiMound MK705 £11.50
 HiMound HK702 £12.95
 Kenpro squeeze key KP100 electronic key £65.00
 Kenpro KR200 Memory keyer £149.00
 Daiwa DK210 Electronic £47.00

ICOM

IC751 HF P.O.A.
 IC745 HF P.O.A.
 IC271 2 HTR P.O.A.

IC251 Special £469.00
 ICR70 Receiver P.O.A.
 IC290E £369.00
 IC290M £415.00
 IC25E £259.00
 IC120 1296 £P.O.A.
 IC2E £165.00
 IC4E £185.00
 ICAT500 £329.00
 ICAT100 £249.00
 IC2KL Linear £900.00
 IC2KLPS £245.00
 SP3 Speaker £35.00
 HP1 Headphone £25.00
 SMS Base mic £29.00
 PS35 IC751 PSU £155.00
 Voice Box 751/271/471 £39.00
 IC DC1 DC Car, IC2E
 IC CP1 DL Lead
 All ICOM Accessories Stocked

TONO SPECIAL OFFER TASCOS TERMINALS

CWR 685E VDU TX/RX Keyboard
 RTTY 1 Morse £695.00
 CWR 675 As above reader £425.00
 CWR 670 Reader No VDU £285.00
 CWR 610 Basic model £160.00
 6550 RTTY/CW Terminal £285.00

SCANNING RECEIVERS

JIL SX200N £285.00
 CD6000 Air £90.00

JAYBEAM ANTENNA

All Jaybeam Antenna In Stock P.O.A.

ALL ACCESSORIES AVAILABLE - PLUGS SKTS CO-AX 2MTR COLINEAR £33.00 70CM COLINEAR £33.00



PRICES INCLUDE VAT AT THE PRESENT RATE OF 15%
 OPEN MON - FRIDAY 9.00 - 5.30. SATURDAY 10.00 - 3.00. INSTANT HP FACILITY AVAILABLE
 EASY ACCESS M2-M11-M1 NORTH CIRCULAR ROAD-EASY PARKING



IS SOFTWARE YOUR BASIC PROBLEM?

Are you bewildered by the choice of Software Programs on the market? Not sure what Program you really need, what it does or where to get it?

SOFTWARE INDEX

IS YOUR ANSWER

The most comprehensive magazine listing of Software programs for the eight leading Microcomputers.

**BBC
COMMODORE 64
DRAGON
ORIC**

**ATARI 400/800
SPECTRUM
VIC 20
ZX81**

Software Index takes the headache out of choosing the programs suited to your Micro.

For people involved in electronics and specialist programs, Software Index will provide the information you need and be a valuable time-saving guide. Games, education, business and personal management are also covered.



DON'T LET SOFTWARE GIVE YOU A HARD TIME—GET

SOFTWARE INDEX 1984 No 1

The problem solver— in your newsagent's now £1.50

DW REVIEW

144MHz Handheld Belcom LS20-XE

As handheld rigs go the Belcom LS20-XE must certainly rate as one of the smallest. Covering the full 144MHz amateur band in 5kHz steps it measures a mere 140 x 69 x 26mm and weighs in at only 260g complete. "Pocket radio" is the correct term as it slides easily into a coat pocket—or handbag!

Where a rig has been designed to fit into a pocket such controls as tone burst, repeater shift and power are concealed behind a cover on one side. The four AAA size cells are also in a neat compartment at the base of the transceiver behind another cover. Therefore the rig can be moved without fear of disturbing any of the settings and accidentally setting off the tone burst or losing your repeater shift.

The transmitter output is switchable (1W, 500mW and 100mW), giving the operator maximum efficiency from the

batteries. A very useful optional extra is the CP615 battery carrying pack, which will take four C size cells. This allowed the rig to be used for much longer before the batteries needed replacing. Reports on the transmitted audio were good using the built-in electret microphone, and only a slight difference noted when a speaker-microphone was used. Provision on the side of the rig is made for the connection of an external speaker-microphone and an external battery pack.



The 50Ω flexible antenna plugs into a BNC socket on the top panel where the volume/off switch, squelch and frequency selector switches are also located. Frequency selection is achieved with "thumb-wheel" switches and depending on the size of your fingers can be easy or difficult to operate.

As well as the electret microphone, the internal speaker is mounted behind the front panel. The audio from the speaker was very good—considering the size of the speaker, just 50mm. However a significant improvement came when the external speaker-mic was used.

The receiver section was found to be very sensitive and compared well with other handheld and portable 144MHz rigs. Its lack of size does not denote a lack of receiver performance. It has a 3SK114Y dual-gate MOSFET r.f. stage which provides excellent performance in such a small rig.


There are many optional extras available with the LS20-XE, the only ones tested during the review period being the battery pack and speaker-mic, both of which seem very useful extras. They enabled the user to get the best from the transceiver.

The LS20-XE costs £128 including VAT with a speaker-mic at £13.80 and the battery carrying pack £10.25. I would like to thank **Low Electronics, Chesterfield Road, Matlock, Derbyshire DE4 5LE, Tel. 0629 2817** for the loan of the review model.

Elaine Howard G4LFM

Benny



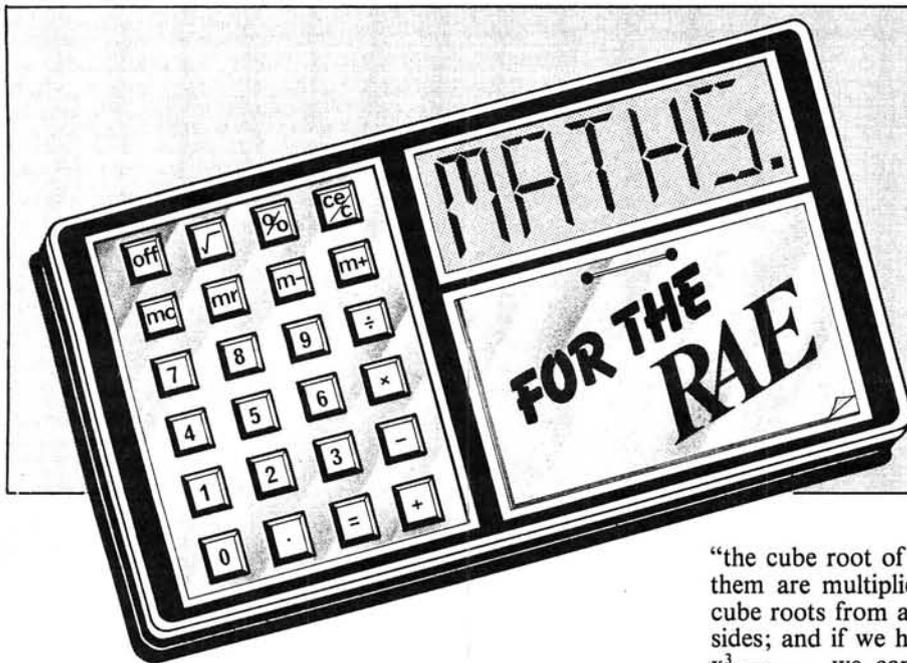

Part 2 by Roger Lancaster

Last month we dealt with the basic principles of changing the subject of a formula, so now we can look at the more complex forms of equation which might crop up in the examination.

It is sometimes necessary to **square** both sides of an equation. Suppose we want to express x in terms of a , b and c in the formula

$$3a = 4bc\sqrt{x}$$

We can cross-multiply to get

$$\sqrt{x} = \frac{3a}{4bc}$$

but we want x as the subject, not \sqrt{x} .

Multiplying a number by itself is called "squaring" and the reverse operation is "taking the square root". The term x^2 is read as "x squared" and is equal to x times x . The symbol \sqrt{x} is read as "the square root of x ". Thus, the square of the square root of a number is the number itself, i.e.

$$(\sqrt{x})^2 = \sqrt{x} \text{ times } \sqrt{x} = x$$

So, getting back to the example, we can get rid of all square root signs by squaring (the whole of both sides of the equation, of course) to produce

$$x = \left(\frac{3a}{4bc}\right)^2 \text{ or } \frac{9a^2}{16b^2c^2}$$

It is often easier to do the squaring before other operations, such as cross-multiplying. For example, if we want to make x the subject of

$$b = 4c\sqrt{xa}$$

This would become

$$b^2 = 16c^2xa \text{ and then, cross-multiplying}$$

$$x = \frac{b^2}{16c^2a}$$

The reverse operation may have to be used. To make x the subject of

$$3ax^2 = 4bc \text{ we first cross-multiply the } 3a \text{ to give}$$

$$x^2 = \frac{4bc}{3a} \text{ then take the square root of both sides i.e.}$$

$$x = \sqrt{\frac{4bc}{3a}} \text{ or } = 2 \cdot \sqrt{\frac{bc}{3a}}$$

since the square root of 4 is 2. Be sure again that the operation is always performed on the whole of both sides of the equation.

The same principles can be applied to powers and roots other than 2, of course. For example, x^3 , read as "x cubed", is equal to x times x times x , and $\sqrt[3]{x}$, read as

"the cube root of x ", is the number which, when **three** of them are multiplied together, will equal x . To get rid of cube roots from an equation, therefore, we can **cube** both sides; and if we have an equation whose left-hand side is $x^3 = \dots$ we can **take the cube root** of both sides. In general, x^n is "x to the power n" and $\sqrt[n]{x}$ is the "nth root of x " and we can take the nth root of both sides of an equation or raise both sides to the power n.

Here are some worked examples to clarify the foregoing. In each case, x is to be made the subject:

No. 1: $a(\sqrt[3]{x}) = 3bc$ becomes
 $a^3x = 27b^3c^3$ and then
 $x = \frac{27b^3c^3}{a^3}$

No. 2: $2ax^5 = 64bc$ becomes
 $x^5 = \frac{64bc}{2a}$
 $= \frac{32bc}{a}$ and then
 $x = \sqrt[5]{\frac{32bc}{a}}$
 $= 2\sqrt[5]{\frac{bc}{a}}$ (since $\sqrt[5]{32} = 2$)

No. 3: $a = \frac{1}{2\pi\sqrt{xb}}$ becomes
 $a^2 = \frac{1}{4\pi^2xb}$ and then
 $x = \frac{1}{4\pi^2a^2b}$

(see question No. 1 of the self-test in Part 1 of the series)

Now suppose the variable we wish to make the subject of the formula is itself a power, as in

$$a = bc^x \text{ where we want to make } x \text{ the subject.}$$

The right-hand side is the awkward one, so let us look at it more closely. Suppose b , c and x were real numbers, e.g.

$$(4.2) \text{ times } (7.48)^6.$$

How could we evaluate this without a calculator? We could multiply six lots of 7.48 together and multiply the result by 4.2—but this would be a laborious business. There is another way and that is to use logarithm (log) tables, which were popular before calculators made us even more lazy.

To multiply numbers together using log tables, you look up the log of each number and add these all together. This part is called "taking logs" and gives you the **log** of the answer to the original problem. You then look up the anti-logarithm (antilog) of this in the antilog tables to find the answer itself. (The idea behind log tables is that it is easier to add large numbers than to multiply them).

Thus, to evaluate $(7.48)^6$ for a start, we could look up the log of 7.48 (which is 0.8739), then add six of these together to get 5.2434, which is the log of the answer. The antilog of 5.2434 is 175 146, which is the result of multiplying six lots of 7.48 together. Of course, adding six lots of 0.8739 together is the same as multiplying 0.8739 by six, which is probably easier. To evaluate the (4.2) times $(7.48)^6$ we would add the log of 4.2 (which is 0.6232) to the 5.2434 prior to taking the antilog.

So what is all this leading up to? Well, if we write out the process of taking logs, we get

$$6 \cdot \log(7.48) + \log(4.2)$$

and we can see that the 6 is no longer a power. We can therefore use this process of taking logs (of the whole of both sides, of course) on the original formula ($a = bc^x$) to get

$$\log a = \log b + x \cdot \log c$$

Thence,

$$x \cdot \log c = \log a - \log b \quad \text{and}$$

$$x = \frac{\log a - \log b}{\log c}$$

To divide using logs, we take the log of the numerator and **subtract** the log of the denominator from it before taking the antilog. Thus to evaluate $7.48/4.2$, the **log** of the answer is $\log 7.48 - \log 4.2$ and the answer itself is the antilog of this result. The "taking logs" part is done prior to taking the antilog.

Therefore, if we have to make x the subject of

$$\frac{a}{b} = c^x \quad \text{taking logs gives us}$$

$$\log a - \log b = x \cdot \log c \quad \text{thence}$$

$$x = \frac{\log a - \log b}{\log c}$$

You will see that this example is merely a different form of the previous one and so yields the same answer for x .

Here is a worked example relating to the charging of a capacitor through a resistor: to make t the subject of the formula

$$v = Ve^{(-t/CR)}$$

Taking logs, we get

$$\log v = \log V + \left(\frac{-t}{CR}\right) \log e \quad \text{thence}$$

$$\frac{-t \cdot \log e}{CR} = \log v - \log V \quad \text{and then}$$

$$-t = \frac{CR(\log v - \log V)}{\log e} \quad \text{and finally}$$

$$t = \frac{-CR(\log v - \log V)}{\log e}$$

If we can take logs of an equation we can also take anti-logs, and this is sometimes necessary in examples where decibels (dB) are involved. Suppose we have to make x the subject of the formula

$$a = 10 \cdot \log x$$

in order to turn $\log x$ into x we simply take the antilog of $\log x$. So, if we cross-multiply the 10 first we get

$$\log x = \frac{a}{10} \quad \text{and then taking antilogs}$$

$$x = \text{antilog } \frac{a}{10}$$

Proportion

It is often useful to know what will happen to one variable in a formula if we change the value of another variable in the same formula. It is not always necessary to apply the formula in calculations in order to discover this. Often, with an understanding of **proportion** we can see straight away what the outcome will be.

Take the simple Ohm's Law relationship

$$I = \frac{E}{R}$$

Practical Wireless, January 1984

What will happen to I if we **double** E ? The right-hand side will become $2E/R$ and, to maintain the balance of the equation, the left-hand side must become $2I$. In other words, doubling E results in the doubling of I . In fact we could multiply E by any number and the result would be that I would be multiplied by the same number. We say that I and E vary in **direct proportion**, or that they are directly proportional (to each other).

But what will happen to I if we double R ? The right-hand side will become $E/2R$ and, to maintain the truth of the equation, the left-hand side must become $I/2$. So, doubling R results in the **halving** of I . If we multiply R by any number this will result in I being divided by the same number. We say that I and R vary in **inverse proportion**, or that they are inversely proportional (to each other).

There are forms of proportion more complex than direct and inverse proportion. Take the formula

$$P = I^2R$$

We cannot say that P and I are in direct proportion because doubling I will not **double** P , although any increase in I will certainly increase P . Doubling I will make the right-hand side $(2I)^2R$ and (since $2^2 = 4$) this is equal to $4I^2R$. So P is **quadrupled** when I is doubled. In this case, P is directly proportional to I^2 .

Another example is

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Here f is not strictly inversely proportional to L , since doubling L will not **halve** f , although an increase in L will certainly decrease f . Doubling L makes the right-hand side

$$\frac{1}{2\pi\sqrt{2LC}}$$

i.e. it has been divided by $\sqrt{2}$ (which is equal to 1.414), so this will result in f being divided by 1.414. In this case, f is inversely proportional to \sqrt{L} .

Let us look at the formula

$$R_t = R_1 + R_2$$

The term R_t is not directly proportional to R_1 because only in exceptional circumstances would the doubling of R_1 cause a doubling of R_t (i.e. when $R_2 = 0$). The doubling of R_1 would certainly cause an **increase** in R_t , but by how much would depend upon the relative values of R_1 and R_2 . In short, simple proportional relationships only exist between **factors** of each side of an equation. In the right-hand side of our example R_1 is not a factor (see Part 1 of this series).

Unless direct or inverse proportion is obvious, as in the $I = E/R$ examples, great care must be taken to determine exactly how a change in one variable will affect another variable. The general procedure is to establish what the given change in a variable has on its own side of the equation, then it follows that the same modification must be made to the other side of the equation.

Graphs

A graph is a pictorial method of showing the relationship between two variables.

Such a relationship between I and E in the purely resistive circuit is shown in Fig. 2.1. Previously we have seen this indicated by the formula $I = E/R$ and we saw that I and E were directly proportional to each other.

Every graph has two axes, each representing various possible values of a variable. In this case the vertical axis represents I in milliamps (mA) and the horizontal axis represents E in volts (V). **The axes should always be clearly labelled to show the variable represented and the units used.** The line of the graph shows the connection between the two variables.

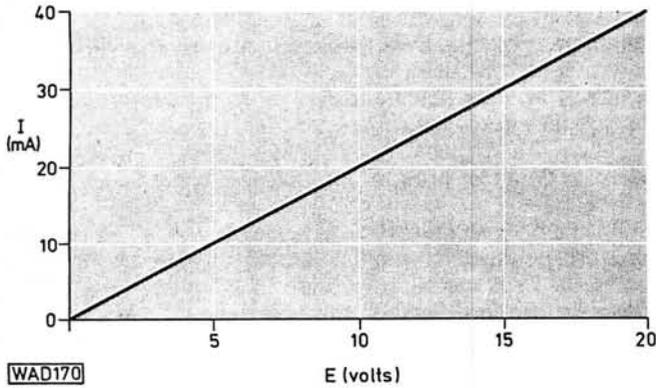
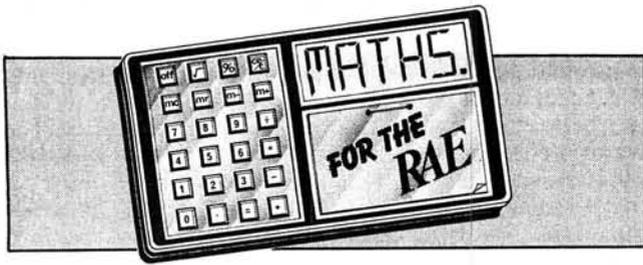


Fig. 2.1

If we want to see the effect of a certain value of E (say 15V) on I, we look vertically upwards from that value to the line of the graph, then from there horizontally across to the other axis to find the corresponding value of I (in this case 30mA). We could do the opposite, starting with a value of I (say 20mA) and ending with a corresponding value for E (10V). The graph shows at a glance all the values of I resulting from any value of E we care to choose, and vice versa, provided these values are not off the scale of the axes. All graphs can be used in this way.

It will be seen that doubling the voltage E (from 10V to 20V, for example) results in a doubling of the current I (from 20mA to 40mA). This shows direct proportion in the form of a straight line passing through the point where both variables are simultaneously zero.

The slope, or gradient, of the line shows the **rate of change** of one variable with respect to the other. In this case the slope is constant, i.e. the rate of change of I with respect to V does not vary, no matter which part of the graph (which range of values) is taken.

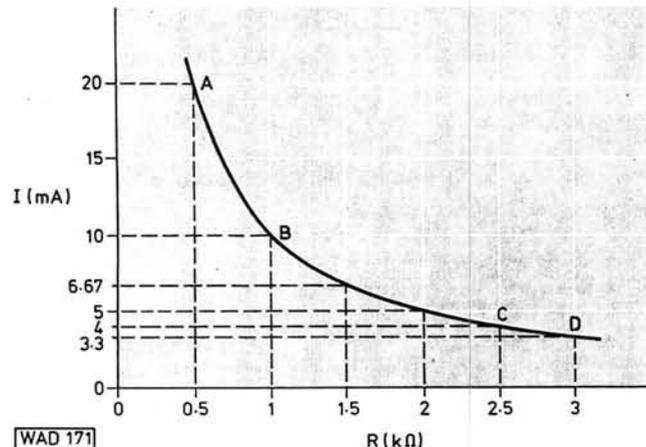


Fig. 2.2

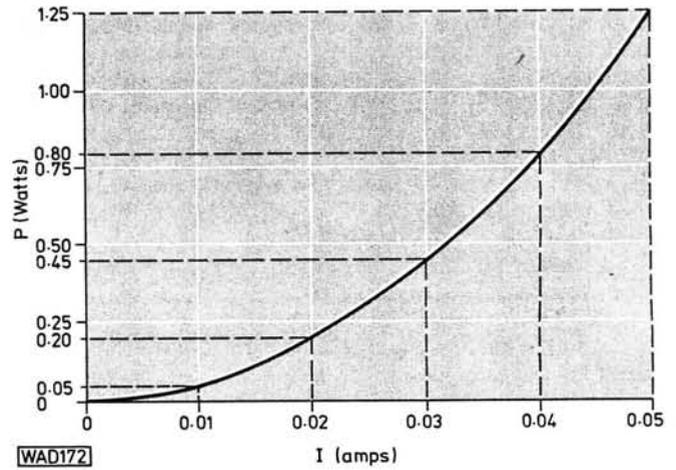


Fig. 2.3

If we keep E constant but vary R, we can see the effect on I for different values of R. This is shown in the graph of inverse proportion of Fig. 2.2. In this case, the graph is not a straight line but does follow a mathematical form governed by the formula. The slope varies, the rate of change of current with respect to resistance being high for low values of R (the steep slope between A and B) and low for higher values of R (the gradual slope between C and D).

The relationship between P and I in the resistive circuit ($P = I^2R$) when R is held constant is shown in Fig. 2.3.

Have Model Engineers equipment and tools, mostly new. Would exchange for a Yaesu FRV-7700 v.h.f. converter. Please write with s.a.e. for list stating requirements. 36 Hookfield, Epsom, Surrey. T492

Have UKW Technik 1296MHz transverter. Would exchange for good computer or ATV equipment. Terry G4HZN. Tel: 0405 813071. T493

Have Yaesu FT-7 h.f. transceiver, Ham HFC01 frequency counter, Protel AM601 compression mic. Would exchange for 144MHz mobile multi-mode, FDK, Trio, Yaesu. Roy. Tel: 0908 612707 (Milton Keynes). T506

Have tower unit (6m) in two 3 metre sections, value £40. Also Cortina Mk 3 1600 o.h.c. cylinder head, windscreen, back window, gearbox—value £35. Would exchange for Codar CR70A receiver, Satellit 1400 or any s.w. receiver in working order. 3 Brora Close, Lakes Estate, Bletchley, Milton Keynes. T508

Have Sony ICF2001. Would exchange for good frame tent and/or items of camping equipment. Tel: Droitwich 772501. T510

Have Yaesu 101ZD FM MkII, immaculate. Would exchange for FRG-7700, R1000, R2000 with cash adjustment, or would consider car. E. Wellington, 25 Fairlop Road, Ilford, Essex. Tel: 01-551 2169. T516

Have Wasp Deluxe Electronic Synthesiser; two v.c.o.s, two e.g.s, real keyboard, external instrument input, complete with p.s.u. and heavy duty flight case. Would exchange for good condition FRG-700 or for FRG-7 receiver with TX a.t.u. Jon Kempster. Tel: 04427 4175 (Berkhamstead). T522

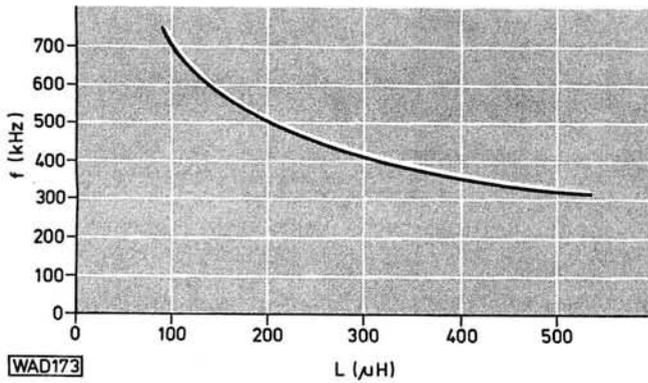


Fig. 2.4

The Fig. 2.4 shows the relationship between f and L in the tuned circuit.

$$f = \frac{1}{2\pi\sqrt{LC}} \quad \text{when } C \text{ is held constant.}$$

The relationship between I and E when a voltage E is applied to a certain non-linear component (one which does not obey Ohm's Law all the time) is shown in Fig. 2.5. This is just one example of a component's "characteristic", other components will be represented by quite different graphs of E and I . In this case, the graph is not linear and neither does it follow a simple mathematical law (formula) but it is just as easy to use as the others, reading from one axis to the other via the line of the graph.

Some of the peculiarities to be seen from this graph are:

(i) I changes rapidly as E increases between points A and B (steep slope)

- (ii) around points C and F, I changes only very slightly as E changes and at these points the slope is zero
- (iii) between C and F, I **decreases** as E increases and between F and G, I increases again, but the slope is less than between A and B
- (iv) the same value of I (40mA) can be achieved by applying any one of three values of E , namely 0.92V, 3.5V or 7.1V, although a value of 10mA is only achieved when E is 0.25V.
- (v) the maximum value of I (66mA) is achieved when E is 2.2V (at C).

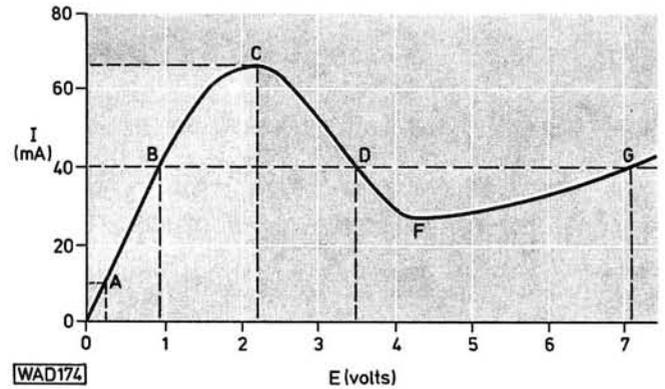


Fig. 2.5

Next month we will look at the graphs of the sine and cosine functions and also at vectors and phasors.

Swap Spot

Have Sinclair ZX81, full size keyboard, numeric pad built-in, p.s.u., 16K RAM, mother board, recorder, books, tapes plus Maxcom 4E CB rig (cost £190). Would exchange for Yaesu FT-290R or similar plus cash adjustment. G. Harris, 136 Centurion Way, Purfleet, Essex. T528

Have Quad II/202 with a.m. and f.m. tuners and decoder, plus Goldring Lenco with transcription arm. Would exchange for test equipment e.g. a.f. generator, lab. p.s.u., dual-beam 'scope, Avo 8 Mk 5. G. L. Mehan, 19 Alderson Crescent, Formby, Liverpool L37 3LY. T530

Have Kenpro KR-400RC antenna rotator, never used. Would exchange for MV5BH or any good multiband h.f. vertical. Tel: Folkestone 51259. T532

Have Amstrad radio receiver, battery or mains (l.w., m.w., s.w., f.m., air, marine, CB) also a Harrier CBX (new) mobile CB transceiver plus cash adjustment where necessary. Would exchange for Yaesu FC-902 a.t.u. or PDL II antenna. David Harrower, 39 Ravenswood, Forth, Lanark, Scotland ML11 8DW. T533

Have Icom IC-255E 144MHz transceiver plus 5-element XY Jay beam. Would exchange for h.f. transceiver, KW2000 w.h.y. Letters only to Jim GM6UHU, 30 Newlands Drive, Kilmarnock, Scotland KA3 2DW. T535

Have Sony ICF2001 a.m./f.m./s.s.b./c.w. receiver 150kHz-30MHz (worth £120). Would exchange for 144MHz or 432MHz mobile/portable. Tel: 01-521 9473 after 6pm G6YDY. T546

Have Sony 630 reel/reel, own amp, speakers and echo sound on sound. Would exchange for multi mode 144MHz rig. H. G. White, 5 Sandrock, June Lane, Midhurst, Sussex. Tel: 4427. T565

Have Oscilloscope—dual beam, 88 x 100 mm display, 4kV tube, timebase to 0.1μs per cm—good quality reliable instrument. Would exchange for 144MHz rig. Tel: Nottingham 819549 (evenings) T550

Have Scuba gear; two bottles, back-packs, fins, mask, weight belt, depth gauge and compass. Would exchange for h.f. equipment w.h.y. Tel: Kilmarnock 21997. T573

PW "SWAP SPOT"

Got a camera, want a receiver? Got a v.h.f. rig, want some h.f. gear to go with your new G4? In fact, have you got anything to trade radio-wise?

If so, why not advertise it FREE in our new feature SWAP SPOT. Send details, including what equipment you're looking for, to "SWAP SPOT", *Practical Wireless*, Westover House, West Quay Road, Poole, Dorset BH15 1JG, for inclusion in the first available issue of the magazine.

A FEW SIMPLE RULES: Your ad. should follow the format of those appearing above; it must be typed or written in block letters; it must be not more than 40 words long including name and address/telephone number. Swaps only—no items for sale—and one of the items MUST be radio related. Adverts for ILLEGAL CB equipment will not be accepted.

on the air

AMATEUR BANDS by Eric Dowdeswell G4AR

Reports to: Eric Dowdeswell G4AR, c/o 60 Blakes Lane, New Malden, Surrey KT3 6NX.

Logs by bands in alphabetical order.

The s.w. listener has a wonderful opportunity to experiment with antennas for the h.f. bands before an amateur transmitting licence is obtained, getting to know their characteristics and capabilities at various frequencies. Antennas used solely for receiving purposes do not need to have that care in construction paid to them which is essential when they are used to handle the r.f. power from a transmitter where proper insulation and fairly heavy copper wire or rigid elements are a necessity.

The s.w.l. can use odd pieces of plastic tube such as are obtainable from ball- or felt-tipped pens for insulators at the ends of wire elements, or as centre spacers supporting coaxial or open feeders, or as spacers for open wire feeders themselves. Ball-points are generally around 130mm long and can be cut in half to provide two spacers in the last application.

The actual gauge of wire used can be quite thin before it will stretch and break and need not be copper. Plastic covered iron wire as used in gardening is quite suitable and there are reels of aluminium wire sold for the same purpose which will do, although since it cannot be soldered, should be one continuous length when used as a long wire, without any breaks or joins.

Depending upon the layout of the space available for antennas it is a good idea to fix up pulleys and ropes at the highest points that can be reached so that

various antennas can be strung up very quickly with a minimum of bother each time. Where fixing points are in trees it is essential that a counterweight be fitted, either at the tree end or at the shack end, so that movement of the tree in the wind is taken up by the counterweight rather than the antenna wire itself.

It also saves a lot of time to have small marker pegs in the grass alongside the edge of a path, for instance, at 3m intervals so that lengths of wire can be measured off without having to drag out the tape measure each time. Don't forget to allow a few inches to the length of the wire for tying to insulators etc. After a while you will accumulate a number of wire elements that can be connected in all sorts of configurations and tried out quickly.

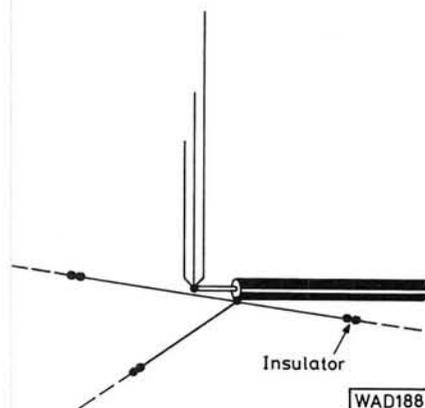


Fig. 2: If at all possible horizontal wires should be added as shown here, all soldered together and to the outer shield of the coaxial cable. The wires are the same length as those in the vertical elements, one for each band, but two or more per band are highly desirable

"Tried out quickly" is not quite the idea however because a new antenna needs to be used over a long period in order to evaluate it properly. Work out or look in the books for the likely polar diagram of a new antenna and see how the lobes apply to your particular location using a pocket compass in conjunction with a great circle map of the world.

Just because the signals from, say, North America, are down on a new antenna compared to a previous one it doesn't mean that it is any worse because it is probably much better in a quite dif-

ferent direction. If you are interested in receiving stations from a particular part of the world then one lobe of the polar diagram can be aimed in that direction.

Even single quad loops of about 5m a side can work very well on several bands, giving worthwhile gain on the higher frequencies. They can be suspended from the centre of a horizontal bamboo cane at the top and rotated from ground level with thin rope from the lower corners to anchor the loop in any direction. Such a loop should be fed with open or 300 ohm flat feeder, via an a.t.u., for all-band operation.

Where space is really restricted and only a vertical antenna can be accommodated then a modified ground plane design can give excellent results. In this, three wires, a quarter wave each for 14, 21 and 28MHz, are taped round a bamboo or other wooden pole, which only needs to be about 5m high, and the bottom ends soldered together and to the inner conductor of the coaxial feeder, the outer of which is earthed at the receiver. The cable may be 50 or 75 ohms impedance as available. This form of construction costs next to nothing and outperforms trapped verticals as there are no compromises in element lengths.

Ideally the true GP should also have horizontal elements from the outer conductor of the coaxial cable, one at least, a quarter wave long on each band. When used for transmitting purposes these wires can be sloped downwards to give a good match to the feeder cable. The GP antenna radiates/receives equally well all round, that is it is omni-directional, at a very low angle and is ideal for the real DX. However it does tend to pick up a lot of local electrical interference.

General

An appeal from Cliff Tooke, ISWL Awards Manager, and Sid Kerrison G3MFQ, for information on the present whereabouts of Bob Ford of AC4RF fame many years ago and author of "Captured in Tibet". C. E. Jefferies G5JF who was Bob's regular contact here would also be interested to know what has happened to Bob.

The last item one would think of abolishing as far as amateur radio is concerned is the log book yet this is what has happened in the United States. The reason given is "that there is no longer an official need for records of routine station activity" which doesn't convey very much. If such a step were taken here I

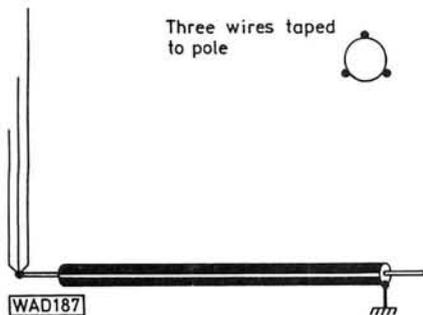


Fig. 1: Three pvc-insulated wires, 2-6m, 3-6m and 5-3m long respectively, are taped at intervals to a vertical wooden pole or bamboo cane. The bottom ends of the wires are soldered together to the inner conductor of the coaxial cable. The cable end should be sealed against the ingress of moisture. This antenna will cover the 28, 21 and 14MHz bands

doubt whether one in a hundred amateurs would drop their log-keeping except perhaps those who only operate regularly on established nets.

On the other hand it would make the pinning down of an amateur guilty of causing TVI or other interference very difficult indeed for the authorities. Personally, I am very pleased to have some of my old log books that I still treasure and which still make interesting reading.

Samuel Giles in Belfast wonders how he can copy amateur s.s.b. on his vintage Murphy TA160. The answer must be "with difficulty"! But really, although one can fit a b.f.o. module of some kind the selectivity and relative instability of the local oscillator would leave much to be desired and would hardly be worth the effort involved. If anyone wants to help Sam drop a line to 16 Fallswater Street, Falls Road, Belfast 12. Sam also wondered where to buy the Realistic series of receivers which, he says, he never sees advertised. They are retailed by the Tandy group through its nationwide chain of shops.

In the current issue of *Contact*, club mag of the Bangor & District ARS, sec **Stewart Mackay** GI4OCK wonders if the several club mobile rallies held during the year over there in N. Ireland could not be combined into an annual convention with the burden of the costs being spread among the organising clubs. A well-known personality could open the proceedings and there could be a much wider range of attractions for both the amateur and the families. Stewart says that at the moment the rallies are all much of a muchness being virtually static trade shows plus a secondhand stall which is usually the main attraction. He thinks that all aspects of electronics should be covered including computers, video equipment and radio-controlled equipment.

Stewart would also like actual demonstration facilities laid on by the retailers of AR gear so that prospective buyers can check it out for themselves. As Stewart so rightly says, who would buy a car without trying it out first? After all, some of today's rigs cost as much as a good secondhand car! Stewart would like to hear from other clubs who may like the idea of an annual convention in GI land.

I don't suppose that there is any point in hiding from you all that yours truly has now retired at the grand old age of 65 and can now get a cheap haircut! I am delighted to report that I shall continue to compile this feature every month as long as the Editor will have me so keep the letters etc coming to me direct.

Best wishes to you all for the forthcoming festive season and may Santa Claus be laden down with lots of black boxes from your dotting relatives!

On the Bands

A well-modified Trio 9R59DS receiver has enabled **Malcolm Tyrrell** of Moston, Manchester to pull in some good DX,

mainly on 21MHz. Writing in for the first time Malcolm has managed to get up a 28MHz ZL-Special, a delta loop for 21MHz in his loft space, and a wire antenna to a short mast in his 10m-deep garden. Wisely, all antennas are coupled to an a.t.u. On 21MHz Malcolm logged AP2P, C6AEY, H44DX, HL0U, J37AH, P29MF, YC4FW, ZL2RE, 6W8BG and 9Y4RT. The 28MHz was not so dead as some would make out, finding A4XIJ, CX4HS, J28DX, SV8RV, ZS6XB, 3B9FK, 9J2JN and 9K2EZ.

Regular writer **Dave Coggins** has good news for those who decry Top Band and the apparent lack of DX there. Listening between about 2000Z and midnight he caught EA8AAU, EA9KQ, SV1DT and UK9CAA on s.s.b. plus HZ1AB, UA9KBO and 4X4NJ on c.w. all between about 1825 and 1850kHz, on his FRG-7700 and a.t.u. plus W3EDP antenna. On 3-8MHz Dave didn't do too badly either with C30AAL (QSL F6EYS), FM0GA and ZL4AV on s.s.b. The 7MHz band produced EL7C, JY9RV, VK9NS on Norfolk Island and VK0GS thought to be on Macquarie Island. Only DX c.w. on our new 10MHz band was VK3BXN. On 28MHz it was CE8ABF, YC3CEV, VJ4RS who, Dave says, is a YL crossing the Atlantic in a small boat! Then came VP8ALD in the S. Orkneys, and 3B9FK. Dave's QTH is in Knutsford, Cheshire by the way.

Another newcomer to the column is **Paul Price** of Merthyr Tydfil, Mid-Glamorgan, who was a BC bands addict until he came across the amateur bands which he now checks regularly with his Sony ICF-2001 and its whip antenna. He has tried various lengths of wire as alternatives but inevitably ran into cross modulation and returned to the whip. On the 3-8MHz band he found C30AAN and 4X6DX with mostly Euros' on 7MHz. Of note on 14MHz were CR7OF, EA9LZ, J28ED in Djibouti (QSL W2TK), SV9JI on Crete, YC2OCN and 9V1VP. Of interest on 21MHz were J73HA on Dominica, SV8RX on Zante Island and VP8AEN (QSL GM3ITN).

In Felixstowe, Suffolk, our **Keith Ranger** has been having a lot of fun with his homebrew four-transistor portable t.r.f. receiver using an SK19 f.e.t. and three BC109's plus crystal earpiece and a short throw-out antenna, about 3m long, mostly at ground level. It is band-switched from 28 to 3-5MHz. Best DX so far he reckons is a ZL4 on 7MHz s.s.b. In detail, on c.w., K7GM/5N2, TR8JD, VU2RO and 3B8FK plus 7Q7LW on s.s.b. all on 28MHz. On 21MHz it was G3ZGC/J6 and 4K1GDW (Antarctica) on c.w. and TR8CR on s.s.b. 14MHz c.w. included CP2ARC, FG7CO, HB9AAX/ET3, HH2VP, JY5DT, UK0QAH, 8P6BW and 9J2LL with EL7C and YI1BTV on s.s.b. Of note on 7MHz c.w. was HK3YH and FM7WU with the ZL4BO on s.s.b. Among others on 3-5MHz c.w. was F0OV/P/FC. Rather puts some of the expensive black boxes to shame!

With his DX200, homebrew a.t.u., 10m dipole in the loft and a 20m-long wire **Dave Shapiro** in Prestwich, Manchester, has found the bands in pretty good shape of late so starting on Top Band it was EA8XS and 5B4EP both on s.s.b., with 3-8MHz providing OH0AC, OY8R and ZI4AP for a nice one. The St Paul Island DX-pedition came up on 7MHz in the shape of CY0SPI, then FK0AR, TR8GM, TU2NW, VP2KM, VS6DO, YS9EW and ZL1BOQ. For 14MHz there was TR8DX, VP8AEN, XT2BP, ZD7BW and 5T5RY with 21MHz giving up A22ME and IK0BZY, included because he was said to be using just 200mW, 3B9FK, 5R8AL, 7Q7LW and 9Q5JE. Finally on the 28MHz band Dave caught KG4DX, ST2SS, VS6DO, 3D6BP, 5Z4DE and 7P8CT, for a very fine log this month.

The h.f. bands have also been pretty well covered down in Callington, Cornwall, by **Viv Doidge** with his FRG-7700, a.t.u. and 40m-long wire. Starting with 3-5MHz the CY0SPI came up as did VK6HD and VK6DO, YS1GMV, ZF2OCZ and ZI4AP, and on to 7MHz and VS6DO, ZL2ANR and 5N8ARY. For 14MHz it was 3V8DC, 3Z0SOB (QSL SP9KZ), 4S7EA, 5T5RY, 5Z4TV, 9M2CK and 9X5CL. Up to 21MHz and FG7BZ, J37AH, WB7PSH/J73, S79WAW, ZD7BW, 5H3JR, 5R8AL ending with PJ3EK on Aruba.

D. R. Norton of London W6 has been s.w.l.ing since the beginning of the year with his FRDX500, FL21 audio filter, SST6 a.t.u. and 20m of wire and writes in for the first time, concentrating mainly on the 14MHz band where he logged 9N1MM for his best DX so far with the QSL already to hand. "D.R." also comments on those stations that still don't QSL even when an s.a.e. is provided. One can't do much more than that! Others on 14MHz were SV1TH, G3CNM/VE3, 5T5AA, VP2MO, VP8ANT, J73CB on Dominica, 9H4B on Gozo Island, 9V1VP, VU83BBJ, 5N6ATT, YB0ARA, CY0SPI and ZB2HG. C30AAN was the only item of interest on 3-8MHz but 21MHz did find AH2AN on Guam, YC5QZ and 4X4MS/P/5N0.

Studies for the RAE have occupied **David Price** down in Wellington, Somerset, but even so he has sent in a very impressive log from 28 to 3-5MHz using his FRG-7 fed from a 43m wire in the form of a delta loop which would account for the excellent DX on the 3-5MHz band, like JA6IEF, VK6LK and 5N8ARY, all between 2100 and 2300Z around 3-795kHz. On to 7MHz and ZL2BT, HK4FLT and VP8ANT (QSL POB 146 Cambridge) with 14MHz providing 8R1X, T77C, CY0SPI (QSL VE1ASJ), TR8DX, VS6DO and UN station 4U1VIC located in Vienna. The 21MHz band seems to have been the most prolific with VP8AQA, 6W8BG, VU2GO, YC4FS, 3B9FK, 5R8AL, FG7CC, 9L1DR, 4D9RG (QSL DU9RG) VP8ZV in Port Stanley and KC2CS/P/J6L on St Lucia.

Club Time

If you are not already a member of your local AR club or group why not make a resolution to do something about it right now and join in the fun of the forthcoming winter season and the pleasure and satisfaction of meeting other amateurs that perhaps you only know as distant voices on the bands.

Abergavenny & Nevill Hall ARC Note for December, the Christmas dinner on Friday the 9th at the Llanwenarth Arms on the A40, Aberg'y. Routine meetings at 7.30 every Thursday at the Pen-y-Fal Hospital, Aberg'y, above the Male Ward 2, with RAE classes at the Seminar Room, Nevill Hall Hospital, Brecon Road, Aberg'y at 7.15 on Tuesdays. Don't forget the club is an official RAE centre and applications for the March exam should be in by January 14. More from sec David Jones GW3SSY, 2 Dalwyn Houses, Llanover Road, Blaenavon, Gwent.

Acton, Brentford & Chiswick ARC G3IUU Tuesday, December 20 will see the club discussing antennas, at 7.30pm, at the Chiswick Town Hall, High Road, Chiswick, London W4 where new members and visitors alike will be made most welcome. So says sec W. G. Dyer G3GEH, 188 Gunnersbury Avenue, Acton, London W3.

Axe Vale ARC Meeting spot remains the Cavalier Inn, Axminster, on the first Friday at 7.30. The RAE course run by G8AOJ has a few vacancies and is held at the St Clare's Centre, Seaton. Peter Peach G3GOS, is the hon sec and resides at The Firs, Goldsmiths Lane, All Saints, Axminster, Devon or you can ring him on A'minster 34259.

Banbury ARS Members are asked to note a change in the meeting day, now the last Thursday of the month but still at the St Pauls Church Hall, Warwick Road, B'bury, with items like DF hunts, talks, junk sales and the like. Sec remains John Burrell G8OZH, 6 Blenheim Croft, Brackley, Northants, or ring (0280) 702900.

Bangor & District RS According to PRO Stewart Mackay G14OCK, 11 Dellmount Park, Bangor, Co Down, N. Ireland, the club is back in business for the winter season at the Sands Hotel, Bangor at 7.30 on the first Friday of the month.

Braintree & District ARS G4JXG G6BRH First of all the sec is none other than Pat Penny G6TAF and you've just got to believe that she comes from GW-land! Present QTH however is 13 Newnham Close, Braintree, Essex, or B'tree 26487. The club's mag *BARSCOM*, edited by G3PEN, is quite something and a really good read. Contact Pat for the latest information on club events.

Bromsgrove ARS G4TUI Formed last May the club specialises in outdoor demonstrations, special event stations to generally promote AR in the district, in addition to the normal run of club features. Second Tuesdays at Rigby Lane School, Bromsgrove at 8 with the 1984 programme being formulated. In the meantime try Alan Kelly G4LVK, 8 Green Slade Crescent, Bromsgrove, Worcs for up-dated info.

Bromsgrove & District ARC G3VGG Not to be confused with the other Bromsgrove group, this club meets on the second Friday at the Avoncroft Art Centre at 8pm with the December gathering encompassing the

Christmas Party, says sec Jim Calder G6EAM, available on Kingswinford 8580.

Bury RS The club's AGM is scheduled for Tuesday December 13 with wine and cheese afterwards, says Publicity Officer Malcolm Pritchard G3VNU, 56 Shelfield Lane, Norden, Rochdale, Lancs although the sec would be glad to hear from visitors or newcomers at 4 Colne Road, Burnley, Lancs (Burnley 24254) otherwise Brian Tyldsley G4TBT. Meetings every Tuesday at 8, at the Mosses Community Centre, Cecil Street, Bury.

Chichester & District ARC It's the annual Christmas Social on Thursday December 15, otherwise first and third Thursdays at the Green Room, Fernleigh Centre, 40 North Street, C'chester at 7.30, plus club net on S11 (145-275MHz) at 7pm on Wednesdays. The Bognor Adult Education Centre has courses for both the RAE and Morse code exams running currently. Hon sec is T. M. Allen G4ETU, 2 Hillside, West Stoke, C'chester, Sussex also obtainable on West Ashling 463.

Flight Refuelling ARS G4RFR G6SFR Sundays at the Sports and Social Club, Merley, Wimborne, Dorset. Following participation in the RSGB's 144MHz contest on December 4 the meeting at 7.45pm will be another of Nick's Rambles, otherwise G8MCQ, again by popular request. Incidentally the club is rather chuffed that Nick has been recruited to the RSGB's VHF Committee. On December 11 it's Paul G3MDH on "Another use for r.f." subtitled "who needs a laser" so work that one out! Another repeat performance, this time by PW's Elaine G4LFM on "CW Worldwide", on the 18th. Strangely, no meeting on the 25th but the club wishes members and guests a very Happy Christmas! Mike Owen G8VYF, Hamden, 3 Canford View Drive, Canford Bottom, Wimborne is also on (0202) 882271 if you want to contact the club secretary.

Fylde ARS At the Kite Club, Blackpool Airport, first and third Tuesdays at 7.45, with code classes beforehand for those interested. Date to note is December 6 when it's Christmas Party time. Your contact is H. Fenton G8GG, 5 Cromer Road, St Annes, Lytham St Annes, Lancs.

Halifax & District ARS PRO G4SDX says the club meets on the first and third Tuesdays at the Running Man, Pellon Lane, Halifax, and imagine 7.30 would be about right. XYLs and other members of the family will be welcome at the Christmas ragchew followed by a pie and peas supper on December 6. Note that on the 20th G6BPH will be giving a talk on domestic video recorders. The sec for further info is David Moss, Beechwood Lodge, Leeds Road, Lightcliffe, Halifax, W. Yorks otherwise (0422) 202306.

Hastings Electronics & Radio Club G6HH Consistently good club mag *Vital Spark* reveals membership up to 172 of which 21 are on the current RAE course, all due no doubt to the very wide spread of electronic interests. First, second, fourth and fifth Wednesdays at 8, at the Ashdown Farm Community Centre are Micro Nights, with main monthly meeting on third Wed at the West Hill CC. Tuesdays at 7.30 is code time with the RAE classes on Thursdays at 7.45. If you have a Friday evening to spare it's chat time. Highlight of December is the 21st and the Christmas Social for all the family. For info on a host of

these and other activities contact George North G2LL, 7 Fontwell Avenue, Little Common, Bexhill-on-Sea, or Cooden 4645.

Leighton Linslade RC You may get your *PW* in time to take note of the December 5 meeting, a Monday, when G4ASH talks on through-line power measurements while the 19th is devoted to the usual Christmas social and fun-making. All at the Vandyke Community College, Room A64, Vandyke Road, Leighton Buzzard, Beds, generally at 7 and lasting until around 10pm, first and third Mondays. Your contact at the club is Peter Brazier G6JFN, Kingsway Farm, Miletree Road, L'ton Buzzard, Beds, also available on Heath and Reach 270.

Lough Erne ARC Bill Ward G14NRE contributes the following bit of "useless information" that the club sits on the most westerly part of the UK! I'm sure a lot of us would like Lough Erne for a groundplane! Chairman Bill says the club meets at the Railway Hotel, Enniskillen, on the third Monday of the month, a new venue. Anyone with an interest in any branch of electronics is most welcome and should contact sec Joe G14UHA on Enniskillen 4905 for more info.

Macclesfield & District RS G4MWS Second and fourth Tuesdays at 8, the Fenman Club, Oxford Road, M'field, which is a new home for the club. A programme for the forthcoming season in the pipeline has a wide variety of attractions so contact Dave Lucas G6HLQ, 62 St Austell Avenue, M'field, Cheshire for latest news on events, or try M'field 28610.

Magherafelt ARS G14MFT A new one for this feature I think, meeting first Tuesdays at the club HQ at 12 Garden Street, M'felt, with a varied programme of events including code classes and an RAE course at the local tech on Monday evenings. New members are sought and visitors promised a warm welcome, says sec Jack Chapman G14LVC, 55 Greenvale Park, M'felt N.I. (0648) 32096.

Milton Keynes & District RS Ex-DX column correspondent Alan Date is now G1AZG and says the club meets the second Monday at 8pm, the Lovat Hall, Silver Street, Newport Pagnell, Bucks, with more detailed info from sec Dave White G3ZPA, Rose Cottage, Shenley, Brook End, Bucks.

Nene Valley RC G4NWZ G6GWZ December 7 is natter nite and closing date for the club's Construction Trophy entries while the 14th has a chat on the Cambridge Repeater Group from G8HVV. It's Christmas Buffet time on the 21st but note that the club will be closed on the 28th and January 4. Which makes it every Wednesday at 8pm, at the Dolben Arms, Finedon, near Wellingborough, N'hants, with Lionel Parker G4PLJ, 128 Northampton Road, Wellingborough, N'hants willing to answer your queries about the club.

North Bristol ARC G4GCT Plenty of interesting material in the second issue of the club's new mag *Q5* to suit all tastes, including fast scan TV, RTTY and contests. Every Friday at the Self-Help Enterprise, 7 Braemar Crescent, Northville, Bristol at 7. December 9 is dedicated to a junk sale and on the 30th are the annual Christmas/New Year festivities and party. Contact Ted Bidmead G4EUV, 4 Pine Grove, Northville, Bristol for latest info on club activities.


ANNOUNCING A NEW AMATEUR RADIO DISTRIBUTOR IN WALES WHOLESALE COMMUNICATIONS (VIEWFLINT LTD.)

We are pleased to announce that we have acquired the well-known amateur radio enterprise – South Wales Communications Ltd. and we will honour all service obligations on their behalf. We will continue to maintain their high standards.

WE CAN SUPPLY ANY OF THE FOLLOWING MAKES:—

TRIO — YAESU — ICOM

(and all the accessories you could want)

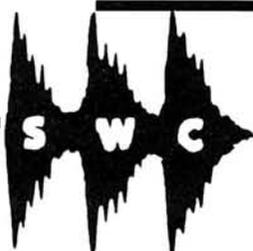

**CLUB:— WE WILL CONTINUE
TO SUPPLY S.W.C. CLUB MEMBERS
AT ADVANTAGEOUS PRICES AND
NEW MEMBERS ARE WELCOME.**

TRADE

IT IS OUR AIM TO SPECIALISE IN WHOLESALE SUPPLY – SO IF YOU ARE IN THE AMATEUR RADIO BUSINESS AND EXPERIENCING DIFFICULTIES IN OBTAINING SUPPLIES OF THE ABOVE EQUIPMENT, GIVE US A RING.

**111 LOWER DOCK STREET (Near the George St. Bridge)
NEWPORT GWENT (TEL: 0633 212455)**



There's an extra bonus for Householder's this month...


home plus

for home, car and garden winter '83

The new colour quarterly supplement will be carried in three of your favourite practical magazines. Amateur Gardening, Practical Householder and Motorist.

SPECIAL FEATURES

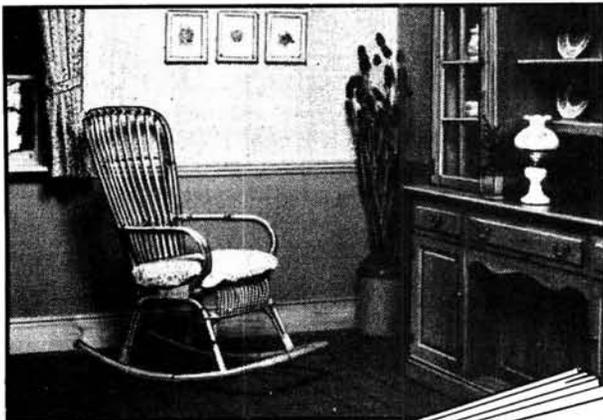- Getting the right tool for the job
- Home Help! Electrical Appliances Review
- Understanding Insurance



To get your copy of Home Plus buy...



**EXTRA!
EXTRA!**
home plus
for all Home Lovers,
Keen Gardeners
and Motoring
Enthusiasts



WHATEVER YOUR INTEREST, YOU'LL GET ADDED VALUE WITH THESE BUMPER ISSUES.

Plymouth RC Established meeting spot is the Penlee Secondary School, Somerset Place, Stoke, Plymouth, at 7.30 with December's dates being the Christmas Quiz on the 12th, a Monday, and Christmas Social on the 17th which is the following Saturday. More on club events from M. C. Newcombe G4FJZ, 56 Dolphin Square, Plymstock, Plymouth, Devon.

Radio Amateurs Technical Engineering Club (RATEC) The sole object of this club is to promote the constructional side of our hobby and as such should be given every support and encouragement. Apart from meetings every Monday at 8 at the British Legion Club, Moor Lane, Woodford, Cheshire, there is an excellent pocket sized magazine published every two months containing anything up to a dozen constructional projects and much more useful information, and is very well produced. Forthcoming projects include a 1296MHz transceiver inspired by the new 1296MHz repeater for the Manchester area, a frequency synthesiser, 24A power supply and lots more. *RATEC News* is posted direct to members at an inclusive fee of £6 a year. Sec is now Nigel Spear G4RWI, 58 Cheadle Road, Cheadle Hulme, Cheshire.

Rhyl & District ARC GW4ARC GWIARC I notice the club pounced on the GWIARC very quickly and very nice too! Hon sec is John McCann GW4PFC, 67 Ashley Court, St Asaph, Clwyd, and informs me that there has been a change in the club's meeting days, now first and third Mondays, at the 1st Rhyl Scouts Hut, Tynenydd Road, Rhyl, starting at 7.30. A programme of events is being formulated by the recently elected committee but contact John for the latest info.

Ripon & District ARS Every Thursday at 7, starting off with RAE and Morse code classes followed by a talk or film or demonstration of some kind, all in the St John Ambulance Hall in Ripon. More from sec Peter Fautley G6CUG, Parkside, Thornton-Le-Street, Thirsk or buzz Thirsk 24945.

Smiths Industries RS G4MEN Meeting at the Club House, Newlands, Bishops Cleeve, Cheltenham, Glos, the next occasion being on Thursday December 8 and then on January 12 and every other Thursday thereafter. More frequent gatherings result from the extensive alterations at the club house and better facilities for operating the club station. The club thinks it is high time that there was some kind of net for club stations and proposes to be on 3735kHz s.s.b. on club evenings from 9pm onwards. With clubs meeting on every day of the week this could be a daily feature for the exchange of information. More from Roger Hawkins G8UJG, c/o Sports & Social Club, Smiths Industries, Evesham Road, Bishops Cleeve, Cheltenham, Glos.



PW contributor Eric Dowdeswell G4AR, right, receives some retirement goodies from Keith Macdonald, MD of Business Press International, at a farewell party, like a Trio VF240 external v.f.o., an MC50 desk microphone and a low pass filter. Eric was technical editor on *Electrical & Radio Trading* prior to which he spent seven years on *PW*

Southdown ARS G3WQK Sec is T. Rawlance G4MVN, 18 Royal Sussex Crescent, Eastbourne and from the excellent club newsletter I learn that the AGM will be on December 5 with meetings generally on the first Monday at 7.30, at the Chaseley Home for Disabled Ex-Servicemen, Southcliff, Eastbourne, Sx. Activities include Raynet operation, DF hunts, contest operation on all bands plus lectures and talks.

Stockton & District AR Group A reminder of the new venue at the Billingham Community Centre, Stockton, every Wednesday at 7.30, all for a mere 50p membership fee and 20p whenever you visit. Not to mention guest speakers, RAE and Morse code classes and all the usual club attractions. It's John Walker G6NRY, 7 Widdrington Court, Stockton-on-Tees, Cleveland, or buzz (0642) 582578.

Stoke-on-Trent ARS G3GBU Every Thursday at 7.30, at the rear of the Cottage Inn, Oakhill, Stoke, with visitors cordially welcomed. The club will be celebrating its 60th anniversary next year and an appeal is made for any information, photographs etc of the past activities of the club, perhaps from those who have been members but have moved away from the area. Sec now is John Wiles G4TVA, 38 Northwood Lane, Newcastle-under-Lyme, Staffs, or try (0782) 625960.

Stourbridge & District ARS G6OI G6SRS The venue is the Garibaldi in Cross Street, Stourbridge, on the first and third Mondays the latter day being considered the main meeting of the month starting at 8 prompt. Amusing note in the *STARS Newsletter* is

that "the bar is deemed to be inaccessible during main meetings when the guest speaker has the floor"! Make a note now and do something about the annual construction contest to be judged on January 16. Hon sec is Malcolm Davies G8JTL, 25 Walker Avenue, Quarry Bank, Brierley Hill, or try Lye 4019.

Stratford-Upon-Avon & District RC G3PGU Meeting place remains at the Control Tower, Bearley Radio Station, Bearley, about three miles north of Stratford, on the second and fourth Mondays starting at 7.30. Home construction of gear is to be the theme for the winter season at the club where workshop facilities are being made available, with projects being lined up for members. PRO is Chris Ousbey G6DCL, Ormond Lodge, Newbold-on-Stour, Stratford-Upon-Avon, Warks, or try Ian Hopwood G6CWK on S'ford 68863 for a speedier contact.

Sunderland ARS G4LPK G6BXJ Sunday mornings at 10 plus Mondays and Thursdays at 7.30, at the Brewery, Westbourne Road, S'land are the meeting times for this group with code classes a feature. An FT-480R and TS-520S are available for use by licensed members. More from temp sec Colin Howe G4RTJ at the club address.

Sutton & Cheam RS The Christmas get-together takes place at the Downs Tennis Club, Holland Avenue, Cheam, Sy, on Friday December 23 starting at 7.30. More details of the club's activities can be got from acting sec Jack Korndorffer G2DMR, 19 Park Road, Banstead, Sy, or try Burgh Heath 58729.

Vale of White Horse ARS Canteen and Social Club, Milton Trading Estate, at 7.30pm the first Tuesday, usually formal, and third Tuesdays, but the main meeting in December will be given over to the inevitable Christmas Social so pass the word around. If you want to monitor the club nets Thursdays at 7.30pm on 28.750MHz and Sundays at 8pm on 145.2MHz. Club secretary is Ian White G3SEK, 52 Abingdon Road, Drayton, Abingdon, Oxon or (0235) 31559.

Wirral ARS G3NWR The Guide Hut, Westbourne Road, West Kirby, will find the club in session on the first and third Wednesdays from 7.45 onwards according to club mag *News & Views* which is a font of information on club activities. However for up-to-date gen on current events contact sec Cedric Cawthorne G4KPY, 40 Westbourne Road, West Kirby, also 625 7311.

Usual reminder to get your letters and copy to me by the 15th of the month and a note to club secs and PROs that at least six weeks' notice of specific events is required if they are to get into the appropriate issue of *PW*. Calendars of events are welcomed, saving a lot of unnecessary correspondence in both directions.

MEDIUM WAVE BROADCAST BAND DX by Charles Molloy G8BUS

Reports to: Charles Molloy G8BUS, 132 Segars Lane, Southport PR8 3JG.

"I always wanted to discover the medium wave band but never got around to it" is a phrase in a letter from Jeff Pascoe (G4ELZ) that has stuck in my mind since reading it. The medium waves, often called the oldest DX band, is quite different from any other band so one does

have to get the feel of it, to "discover" it, before getting the best out of it.


It was with something like this in mind that I started examining small segments of the band and we will continue along this path but first of all it might be useful, for the benefit of newcomers, to

emphasise a couple of items. You must have a path of darkness between the transmitter and receiver in order to hear DX. The medium waves is allocated to local broadcasting so one has to reach through a curtain of local QRM to pick up a distant station.

621kHz

Why exactly 621kHz? It is a European channel in a plan that has 9kHz separation between stations so all sorts of "odd" frequencies come up. 621kHz is dominated during the evening by a French speaking station whose transmitter is located at Wavre in Belgium but if you listen carefully you should be aware of a weaker companion. Even if you manage to reduce the strength of Wavre by using a loop and this is none too easy with short distance high power stations, you will still not be able to separate the two as they are roughly in the same direction. What do we do now? Wavre signs off for the night shortly after 2300 so if we listen then, we will find that as soon as the Wavre carrier is switched off, up pops the weaker companion. We are now listening to the Voice of the Arabs (Sowt el Arab) at Batra in Egypt.

Batra literally does pop up. Its strength increases quite dramatically on account of the action of the receiver's automatic gain control (a.g.c.). The a.g.c. adjusts the gain of the "front end" of the receiver. You could do this yourself by operating the r.f. gain control. Turn it down when listening to a strong station. Turn it up again when listening to a weak one. The a.g.c. works automatically to combat fading so when Wavre is on the air the receiver is desensitised. Once Wavre goes off then the gain is restored.

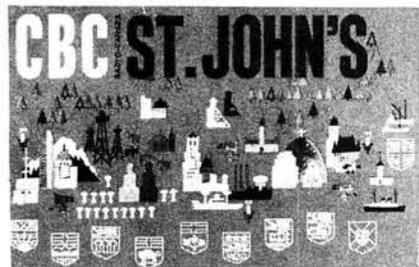

CBN in St John's

The Voice of the Arabs programme is in Arabic but if you want to try them with a reception report send it to Radio Cairo, PO Box 1186, Cairo, Egypt. The problem will be collecting suitable material for the report. News bulletins, time checks etc, are the sort of things to look for. There is another station on 621kHz which can be separated easily from Batra with a loop. This is the government owned outlet at Santa Cruz de Tenerife in the Canary Islands. Programming is in Spanish and even if you do not have a loop you can still listen to it, as the relative strength of the two stations is constantly changing owing to fading. The address for a QSL is Radio Nacional Espana, San Martin 1, Santa Cruz de Tenerife, Canary Islands.

There are other broadcasters on 621kHz. There is a medium power Portuguese station at Vila Real and a more powerful one at Makhachkala in the USSR which signs on at 0200. Perhaps readers will search for these themselves as we are now moving to Newfoundland.

Listen to Newfoundland


Although this Canadian province is no farther away than Egypt we are in a different ballgame altogether when DXing this part of the world. The great circle path across the North Atlantic, which is the route followed by radio waves, passes not too far from the magnetic north pole in Northern Canada. Consequently reception is less reliable than from Egypt. Sometimes strong signals are heard. On other occasions you will hear nothing.



Slow cyclic fading with a period of several minutes is very noticeable on this path so we have to stay on a channel for two or three minutes to make sure. Even a good solid signal can dip to inaudibility for a short period.

It should now be approaching midnight so tune carefully up the band from 621kHz to 640kHz and listen for CBN in St John's. If there is a heterodyne, a 1kHz whistle, then it is caused by interaction between the carriers of CBN and the Spanish stations on 639kHz. The latter can be nulled out with a loop. CBN is the key station of the Canadian Broadcasting Corporation (CBC) in Newfoundland. There are several slave stations that carry the same programme so we will have a look for one of them. Go back to 621kHz and tune down the band to 600kHz. Listen for CBNA in St Anthony. If successful then come back 10kHz to 610kHz and try for CKYQ at Grand Bank. This is a commercial broadcaster that belongs to the same network as CJYQ on 930kHz which is the key station. You may hear the call "Q Radio" instead of the more formal identification CKYQ. Finally return to 621kHz and tune down slightly to 620kHz. CKCM in Grand Falls can be found here when conditions are good.

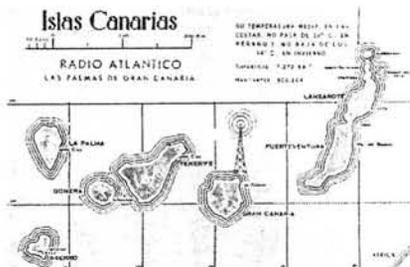These four stations are logged regularly by DXers in the UK and they do verify. Write to CBN and CBNA at PO Box 12010, Station A, Kenmount Rd, St John's, to CKYQ at Box 6130, St John's, to CKCM at Box 620, Grand Falls, all of course being in Newfoundland, Canada.



Radio Atlantico is in Las Palmas

Features of North American DX

Several things emerge from our quartet of Canadian stations. We have been DXing ITU Region 2 where station separation is 10kHz and frequencies are multiples of 10kHz i.e. the final digit is zero. Sometimes this works out to our advantage. CJYQ on 930kHz lies neatly between European channels 927kHz and 936kHz. In the part of the band we have been looking at, the situation is less favourable so we have to rely on a reduction of QRM late at night and on the ability of our loop antenna to reduce it.

Identification of North American station is usually easy as every station is allocated a callsign which is used frequently during the programme. Those in the USA have the prefix W if they are east of the Mississippi and K if to the west. In Canada the prefix is C except for a few stations in Newfoundland like VOXM on 590kHz, which retain the old colonial prefix V.

White's Radio Log

A copy of a new edition of this very comprehensive listing of North American medium wave stations is currently to hand. At one time the log was published in parts in an American radio magazine and I still have a slim volume which I bound myself, of sections from several issues. The log has been published in book form for some time now and the new 136 page edition is available for \$6.95 postpaid from Don Gabree, Worldwide Publications Inc, PO Box 5206, North Branch, N.J. 08876, USA.

The medium wave information is in two sections, one for the USA and the other for Canada. Each section has three lists, one by frequency order, one by call

letters, one by location. The new edition has been enlarged and describes itself as "an up-to-date directory of North American a.m., f.m. and TV stations including a special section on world-wide short wave stations". Not all of this information is of interest to us but the medium wave lists are a valuable source of reference for anyone interested in DXing North America.

News Items

A recent report from *Sweden Calling DXers* drew attention to Sud Radio Andorra which has resumed operations on 819kHz. It seems that this return to the air may only be temporary as the transmitter in Andorra is to be closed down when a new one in South West

France is operational. If you want a QSL from Andorra now would seem to be the time to get one. The address for reception reports is Sud Radio, BP7, Andorra-la-Vieille, Andorra.

Also from SWCDX is a note that Radio Finland is using 254kHz longwave to supplement its international service at 2100 which is suffering from "interference" on 963kHz.

SHORT WAVE BROADCAST BANDS by Charles Molloy G8BUS

Reports: as for Medium Wave DX, but please keep separate.

"Are there any English language stations in Latin America?" asks **Glenn Hocking** of Redruth in Cornwall who is having difficulty with the languages used in that area. Yes there are a few. Among local broadcasters the most prominent is Radio Spice Island on 15.095MHz which can be heard between 2000 and 2130, usually with quite a good signal. Others that may be picked up later on in the night are Georgetown in Guyana on 5.950MHz, Belize on 3.285MHz and Honduras on 4.820MHz.

Broadcasts to Europe

There are special broadcasts from Latin America beamed to Europe. Listen for Radio Bras in Brasil which, at the time of writing is on 15.280 at 1800; for RAE in Buenos Aires on 15.345 at 1930 and 2230, for Cuba on 11.690 at 2010 and again on 11.705 at 2200. The most prominent broadcast to us from Latin America is HCJB the Voice of the Andes in Ecuador. Its English broadcasts to Europe are generally well heard in this country. Listen at 1900 on 17.790MHz and 21.478MHz and at 2130 on these and the additional frequency of 15.295MHz. On Mondays and Saturdays the 2130 transmission, which lasts

for half an hour, is devoted to the well known *DX Party Line* presented by Clayton and Helen Howard.

Radio Propagation

Regular readers of this column will be aware of the ionospheric data broadcast at 18 minutes past the hour by WWV. Less well known but nearer home is a similar transmission by the Bureau de l'heure (BIH) in France. The data supplied by BIH is more comprehensive than from WWV, reception is more reliable but the transmission is in Morse code (A1A).

Four transmitters are involved. The first three, FTH42 on 7.428MHz, FTK77 on 10.775MHz and FTN87 on 13.873MHz are located near Paris while the fourth, FTA83 on 83.8kHz, is near Lyon. The ionospheric data is broadcast 4 times a day as follows:

1208UTC FTA83, FTK77; 1308 FTA83, FTN87; 2008 FTA83, FTK77, 2108 FTA83, FTH42.

Unlike WWV whose clock pulses are on the air continuously, BIH only has this at selected periods, none of which occur immediately before the ionospheric data, but listen for CQ DE (callsigns) which is repeated several times before the start. The information begins with MEUDON URSIGRAM followed by a number of sections. It is the first of these called GEOALERT or GEOSOL that is of interest to us.

The Geoalert consists of a number of five figure groups, the first four groups containing the date we want. The first digit of each group is a key number. Number 9 indicates hour and date of the period e.g. 91215=1200UTC on the 15th of the month. Key digit 1 indicates sunspot data, the following three digits giving the relative sunspot number and the last digit=number of new groups that have appeared during the period. Key digit 2 is for solar flux, next three digits are the SF number and the last digit is the number of important bursts during the period.

Key digit 3 is for magnetic activity. Following three digits give the Ak index, the last digit indicates important events where 0=no event, 1=end of magnetic storm, 2=storm in progress, 6=gradual storm commencement, 8=very pronoun-

ced storm commencement. Key digit 4 is for cosmic radiation while the remainder cover solar flares.

Thanks are due to Dr Paul Simon of the Meudon Observatory who supplied this data. He said he was glad we were interested in this kind of information and mentioned that the Sunday transmission repeated the Saturday message.



Radio SWA QSL sent in by Philip Hodgson

ADDX

Reader **Dietmar Jendreyzik** of Cologne writes to say that he is a member of the ADDX which is a DX club located in West Germany. It has about 4400 members in more than 30 countries and publishes a fortnightly bulletin, in German, called *Kurier*.

Since June of this year the club has had its own transmission in German, carrying matters of interest to broadcast band DXers. "It's possible for us to make a transmission in English language if there is a need," continues our reader who goes on to say that there will be one on the 14 December 1983 at 1800UTC on 3.770MHz and 14.277MHz +/- QRM with the call DF0AD. "If your readership is interested in this special transmission in their own language they should write to us a postcard to our address ADDXeV/DF0AD, PO Box 15 01 24, D-4000 Dusseldorf 1. FRG."

Glad to hear from you Dietmar and good luck to your club's new venture.


On the Bands

"I am using a Vega Spidola 250 with approx 5 metres of wire connected to the whip by means of a clip, and using a



Radio Beijing QSL sent in by Simon Lexton

mains adaptor" writes reader L. Lyon from Scarborough who says that the Voice of Vietnam comes in well, the English transmission being from 1800 to 1830 on 15-012MHz. A DX302 communications receiver with indoor antenna is in use by Marcus Walden of Harrogate who reports hearing SABC on 4-835MHz at 2100, ELWA Liberia on 4-765 MHz at 2050, RAE Argentina on 15-345 at 2240, Voice of Nigeria on 15-120 at 0945 and KYOI in Saipan on 15-990 at 1000 and again on 11-900 at 1130.

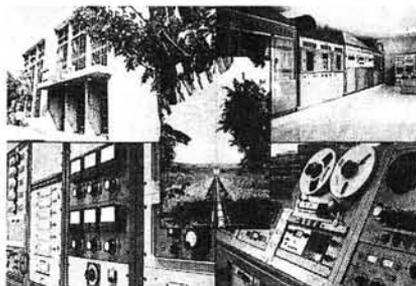

Radio Lara QSL sent in by Bill Pentland

referring to the short wave broadcast bands. Unlike the amateur bands, the international broadcast bands are not harmonically related to one another. Consequently you would need a separate beam for each band. Physical size is against it on the lower frequencies. A dipole for the 9MHz band (31m) would be roughly 15m in length. If it had a director and reflector of similar dimensions then you would end up with a formidable structure even if it were non-rotatable.

Simon Lexton (Cheam) has been DX-ing for two years. "I have logged around 40 countries—on a Vega Selena B212, showing what can be done on a low-budget. This should encourage any newcomer showing that he/she need not purchase an expensive black box to start with." It is worth remembering though that this type of receiver does not readily lend itself to modification or improvements nor does it usually perform well when connected to a good outdoor antenna. None-the-less this is an economical way to start out on the hobby.

Jeff Pascoe (G4ELZ) who has been a radio amateur for ten years still gets a lot of fun from our side of the hobby and he asked me to send him a list of DX clubs "so that I can follow up-to-the minute information on the subject". Readers may

be interested to learn that the European DX Council (EDXC) has recently produced a list of member clubs. Write to the EDXC, PO Box 4, St Ives, Huntingdon, PE17 4FE, for further information.

A note from Ray McLellan (G4TAA) mentioned that the final broadcast of the DX programme *Spectrum* was on the 9 October. The presenter Dick Speekman announced that the replacement is *Talk Back*, introduced by Barry Feeba, covering communications developments, DX news and listeners' tips. Ray heard



Radio Thailand QSL sent in by Philip Hodgson

"For anyone who enjoys a very strong signal, here are some stations that beam into the UK" says Paul Price of Merthyr Tydfil who uses a Sony ICF 2001 with telescopic antenna. For the benefit of newcomers, this list includes the Voice of Turkey on 11-755 at 2200, Korea on 15-575 at 1900, Cairo on 9-805 at 2200, Dubai on 21-655 at 1600 and Greece on 11-645 at 1820.

Readers' Letters

"Is it feasible to use a beam antenna for this type of listening" writes Ed Harrison from Victoria in Canada who is



Doha, Qatar QSL sent in by Bill Pentland

Spectrum on Radio Australia's transmission on 9-570 at 0612, 21-720 at 0810 (not reliable) and on 7-205 at 1612. A cry for help comes from 14 year old Stuart Gough who lives at 33 Cranwell Drive, Wideopen, Newcastle upon Tyne, NE13 6AS. "I have just received a letter from Radio Berlin International that says my reception report was read out over the air on 29 August 1983. I would be very grateful if any *PW* reader who recorded this programme could let me have a copy—expenses will of course be refunded." Good luck with your request Stuart.

VHF BANDS by Ron Ham BRS15744

Reports to: Ron Ham BRS15744, Faraday, Greyfriars, Storrington, West Sussex RH20 4HE.

What a time we all had! Openings from 28MHz to 432MHz, plenty of DX from around the world, a fair share of RTTY and a question, have you heard or worked the "ROBOT"? If so do drop me a line and tell me about the gear and antennas you use.

Solar

Both Cmdr Henry Hatfield, Sevenoaks and I recorded a radio noise storm on September 28 and 29 at 136 and 143MHz respectively and our technical editor, John Fell G8MCP, heard very strong radio noise, when he swept his 144MHz beam across the rising sun at 0750 on the 28th. Individual bursts of radio noise, lasting 4 minutes and 7 minutes, were recorded at midday on Oc-

tober 9 and 17 respectively and a mild noise storm occurred on the 15th.

While using his optical equipment, Ted Waring, Bristol, observed 9 spots on the sun's disc on September 23, 20 and some active areas on the 28th which accounted for the radio noise on that day, 10 on October 1, 12 on the 5th and 24 on the 10th. During the morning of the 17th, Henry, with his spectrohelioscope, observed one medium sized sunspot group containing about 10 spots, one double spot and a single and writes, "Things look very quiet indeed".


The 50MHz (6m) Band

Graham Rogers VK6RO, spent his holiday from August 25 to September 6, at Carnarvon, Dampier, Port Hedland

and worked 150 JAs on 50MHz, all from his car with an IC505. On the 30th, he heard the Japanese beacon JA2IGY and says "I have now worked 953 JAs while on four holidays, 1980-83 inclusive, in the north-west of VK6, all with between 10 and 20W output and a quarter wave whip antenna on the car roof". This time, Graham used 50 instead of 52MHz and writes, "The difference the 2MHz made is staggering, the m.u.f. did not get much above 50MHz on most days". We often find that here Graham, DXTV on 48-25MHz but nothing on 49-75MHz.

The 28MHz (10m) Band

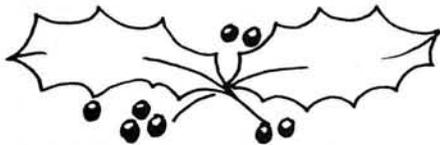"The main feature of the period was the gradual opening up of 28MHz during the last week of September and the



British Technology & Innovation

B.N.O.S. ELECTRONICS

British Designed & Manufactured



“I’m dreaming of 2 metre Linear Amplifiers — nothing like the ones I used to know”

Over 40 years of design experience has gone into what is fast becoming acclaimed as the biggest break-through in linear technology. Performance and reliability have been designed in, which gives us the confidence to offer a free 5-year warranty. Why not take a closer look at our products and see where value for money really counts.

The LPM144 Range

This sophisticated, but simple to use, range of amplifiers have performance characteristics and extra features previously not available in the UK. The pre-amplifier uses the highly regarded BF981 MOSFET, and an LED bargraph power meter is provided, to highlight only two of the amazing number of features.


The L144 Range

To complement the LPM range, we have introduced the L series linear-only versions for the amateur who may already be equipped with a good pre-amplifier and power meter. The excellent linear performance is maintained and both RF Vox and hard-wired changeover are standard.



- Linear all mode operation
- Continuous rated RF output power (RMS)
- RF & HARD switched changeover with selectable delay
- Trouble-free RF switching at low drive levels
- Straight-through mode when switched off
- Unique over-drive protection circuit
- Mobile mount on all 100 Watt models

LPM144-1-100	£172.50
LPM144-3-100	£172.50
LPM144-10-100	£149.50
LPM144-25-160	£189.50
LPM144-3-180	£215.50
LPM144-10-180	£212.50

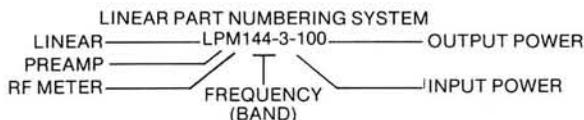

L144-1-100	£138.00
L144-3-100	£138.00
L144-10-100	£115.00
L144-25-160	£155.00
L144-3-180	£181.00
L144-10-180	£178.00

BNOS 'A' Series Power Supplies

12/6A £48.30

- 13.8V, 6A continuous output
- 7A maximum output current
- 10A current meter
- 10A output terminals
- LED shut down indicator
- Fully protected




12/12A £86.40

- 13.8V, 12A continuous output
- 15A maximum output current
- Large 20A current meter
- 15A output terminals
- LED shut down indicator
- Fully protected

12/25A £125.45

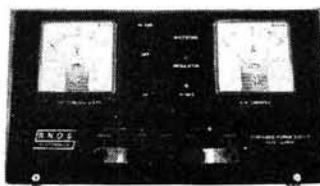- 13.8V, 25A continuous output
- 30A maximum output current
- Large 30A current meter
- 30A output terminals
- LED shut down indicator
- Fully protected



12/40A £225.40

- 13.8V, 40A continuous output
- 50A maximum output current
- Large 50A current meter
- Large output meter
- LED shut down indicator
- LED out of regulation indicator
- Output sensing terminals
- Fully protected

Our Guarantee Our aim is to provide you with high quality products at realistic prices, to give you the best value for your money.

All products that carry our logo are designed and built by our engineers in the UK and carry a full 12-month guarantee, which includes all parts and labour.

We are so confident that our linears are simply the best that we offer to repair your unit at component cost for up to 5 years from date of purchase. That means we will repair, calibrate and return to you free of charge.

All other products sold by us carry our standard 12-month guarantee.

Available direct or from one of our many UK agents — or come and see us at most rallies and exhibitions



BNOS Electronics (Dept PW) Greenarbour, Dutton Hill, Great Dunmow, Essex, CM6 3PT
Telephone (0371 84) 767 SAE for further details

All prices include VAT. Postage free on all Mainland UK orders, goods normally despatched by return.

DEWSBURY ELECTRONICS



West Midlands only autorised TRIO dealer
WE WISH ALL OUR FRIENDS AND
CUSTOMERS A MERRY CHRISTMAS
AND A PROSPEROUS NEW YEAR

AR2001

CONTINUOUS COVERAGE FROM 25-550MHz WITH NO GAPS



FEATURES: 25-550MHz continuous coverage - Switchable modes (AM, FM narrow or FM wide) - Liquid Crystal display - memory channels that store frequency and mode - a full range of scan facilities - Definitely not deaf, on FM (n) the typical sensitivity is 0.2 μ V for 12dB SINAD across the entire range.

PROVISIONAL PRICE £298

Also stockists of DAIWA-WELTZ-DAVTREND-TASCO TELEREADERS
MICROWAVE MODULES-ICS AMTOR-AEA PRODUCTS
DRAE-BNOS-JRC

Dewsbury Electronics, 176 Lower High Street,
Stourbridge, West Midlands.

Telephone: Stourbridge (0384) 390063.

After Hours: Kidderminster (0562) 851255.



30 WATT 2 METER LINEAR AMPLIFIER KIT designed for the TF290R or any transceiver up to 3 $\frac{1}{2}$ watts output, 2 $\frac{1}{2}$ watts in will give 25 watts output, suitable for FM or SSB. Rx pre-amp is switched in when required this gives up to 20db gain or can be made variable by adding a potentiometer, kit consists of ready drilled PCB & all components but less case & heat sink, all assembly instructions included **ONLY £29.50**, suitable die cast box & heat sink £6.00, if ordered with kit **£5.50**.

80 WATT 2 METER LINEAR AMPLIFIER ready built requires 2 $\frac{1}{2}$ -3 $\frac{1}{2}$ watts drive for full output designed for the FT290R, size 112x80x210mm power required 13.8v DC @ 14 amps. (no receive pre-amp) **£98.00**.

HF BAND DIPOLES made by famous radiotelephone manufacturer consists of 1-1 balun in waterproofed die cast box, 230ft 7/029 aerial wire 15mtrs 50 ohm UR67 down lead, 60ft halyard & pulley & insulators, as new & unused can be cut for any frequency from 2 to 30MHz **BARGAIN ONLY £26.00**.

432MHz POWER AMPLIFIER UNITS as used in Pye UHF Westminster radiotelephones this is believed to be the latest designed PA for this radio which uses a BLX68 in the output stage giving a minimum of 7 watts out. Requires 250 m/w drive @ 145 MHz for full output ready tuned for 432 MHz band. With circuit as new & unused **ONLY £16.00**

VHF FM RADIO TUNERS 88-108MHz (could be modified for 2 meters) dual gate mosfet RF stage plus mixer & separate oscillator, 7 gang tuning capacitor 4 tuned circuits @ VHF, plus 3 gangs of 365pf for an AM tuner section, as new & unused **BARGAIN ONLY £4.00**.

JOHNSON VALVE BASES cat. No. 124-0110-001 for the 4CX250B type valves, bases only sorry no chimney's new & boxed **ONLY £15.00**.

AERIAL CHANGE-OVER RELAY'S as used in VHF Pye Westminsters etc, made by Magnetic Devices type 354. OK up to 50 watts @ 200MHz 12 volt coil, new unused **ONLY £1.00** each or box of two for **£1.75**.

CRYSTAL FILTERS

10.7 MHz Cathodeon type BP4113 \pm 15KHz @ 3db, imp. 2k ohm unused **£5.00**.

10.7 MHz Cathodeon type BP4133 SSB LSB only imp. 200 ohm unused **£5.00**.

10.7 MHz ITT type 024BC \pm 7 $\frac{1}{2}$ KHz @ 3db imp. 910 ohm OK FM 2mtrs **£6.00**.

10.7 MHz HY-Q type DF10728 for SSB w/ 1sb no carrier xtals **£12.00**.

23.455 MHz Cathodeon type BP4143 \pm 14KHz imp. 1k ohm min. type **£4.00**.

Many more send for list.

PTFE feedthrough insulators

Solder in feedthrough capacitors 1000pf 500vw

Bolt-in feedthrough capacitors 1000pf 500vw

Glass feedthrough insulators 4mm dia.

Leadless disc ceramic capacitors 1000pf 500vw

RF POWER TRANSISTORS

2N3866 1 watt @ 400MHz 10db 28v 75p.

PT4236A 1 watt @ 175MHz 9db gain 12v 75p.

BLY 4 watt @ 175MHz 7db 12v **£4.00**.

BLY 87A 10 watt @ 175MHz 9db gain 12v **£6.00**.

PT4236B 11 watt @ 88MHz 10db 12v **£4.00**.

PT4236C 35 watt @ 88MHz 6db gain 12v **£5.50**.

PT4555 25 watt @ 145MHz 7db gain 12v **£6.00**.

PT8711 40 watt @ 145MHz 7db gain 12v **£10.00**.

PT4577 no info except FT1200MHz, 15v, collector current jump **£1.50**.

FETS/MOSFETS - 3SK88 90p, 3SK87 **£1.00**, 3SK60 75p, 3SK51 70p, 3SK45 65p, BFR84 50p, TIS88A

40p, BP256 35p, 2N4381 (P chan.) 45p.

AH ELECTRONICS

20, Barby Lane, Hillmorton, Rugby,

Warwickshire. Tel: Rugby (0788) 76473

25 for £1.00
50p per 10
40p each
60p per 100
50p per 10

Terms of business cash/cheque with order, education orders accepted on 30 day basis, full money back guarantee, prices include VAT, please add 60p for postage, callers by appointment only.

YOUR RADIO AMATEURS EXAM SUCCESS

Study at home - pass first time with
RRC's Complete Home Tuition Service

- Self-contained courses, regularly updated for The City & Guilds Radio Amateurs Exam
- Fully inclusive fees
- No costly, time consuming text books to buy
- Everything you need in booklet lecture form
- Regular tests ensure you are fully prepared
- Enrol at any time
- Timetable to suit you
- Continued tuition at no extra cost if you don't pass first time

FREE PROSPECTUS & ADVISORY SERVICE

Write or phone today for full details, and a FREE copy of our prospectus, without obligation to:



THE RAPID RESULTS COLLEGE
Dept. JX11, Tuition House, London SW19 4DS
Tel: 01-947 7272 (9am-5pm) - or use our 24-hour Recordacal Service:
01-946 1102 quoting Dept. JX11



Name _____
(BLOCK CAPITALS PLEASE)

Address _____

Postcode _____

My interest is _____



THE RAPID RESULTS COLLEGE

SELECTRONIC

RADIO, TV AND RADIO COMMUNICATION

SPECIALISTS

★ **934MHz UHF** ★
RADIO EQUIPMENT

We have in stock the full range of Reftec equipment, i.e. Mobile Transceiver MTR 934J2 plus full range of aerials and fittings, etc. Hand held model now available. S.A.E. for full details.

AUTHORISED REFTEC SERVICE DEALER

An easily installed radio system, with uses for small businesses, from home to small boats and a useful home to car two-way private radio system. Ranges of over 200 miles are being obtained by present users.

- ★ STOCKISTS OF AMATEUR RADIO EQUIPMENT: Yaesu, Trio, F.D.K. Tonna, Jaybeam, Revco etc.
- ★ REPAIRS & MODIFICATIONS BY EXPERIENCED & QUALIFIED STAFF.
- ★ CREDIT TERMS AVAILABLE.
- ★ TANDY MODEL 100 PORTABLE COMPUTER NOW IN STOCK.

For further information please ring:

Mike Machin on (0268) 691481.



203, HIGH STREET,
CANVEY ISLAND




highlight was on the days October 7 to 10, with east coast and mid-west United States stations simply pouring in", writes **Norman Hyde G2AIH**, Epsom Downs. "Wall to wall Ws and VEs" writes **Fred Pallant G3RNM**, Storrington, for October 8 and 9 and adds, "at 1830 on the 9th, conditions changed, the Ws and VEs went down in strength and LUs and PYs began to appear". Fred also heard signals from EA, CT3, CX7, I, PY1 and 9J2 between September 20 and 25 and from Canada, Europe, Scandinavia and both Americas during the early evenings of October 2, 4 and 6. "28MHz is open, first time this month, I think", writes **Bill Kelly**, Belfast, who logged stations from South Africa and South America and on October 7 I heard many Ws commenting about the good conditions and the "fine opening to Europe". **Peter Lincoln BRS42979**, Aldershot, reports hearing CX7AR, H5AE, JY5ZM, ZP5CF, ZS1GL, 3D6AN and 7P8CM during this active period. **John Coulter**, Winchester, heard Canadian, European and United States stations in QSO on October 1 and 2 and says, "7Q7LW was causing a bit of a pile up on the 8th". Throughout the period I found that a Morse code reader greatly increased my enjoyment of the event especially when there were so many stations active at both ends of the band.

28MHz Satellites

Stan Williams G3LQI is very keen on c.w. and is an active member of the "First Class Operators Club", the Worthing and District Amateur Radio Club and also AMSAT-UK. At his home in Lancing, Stan uses a FT-101, 144MHz transverter and 8-element Yagi for transmitting to the OSCAR or RS satellites and a TS-120S and 3-element Tribander beam to receive the signals back, around 29-350MHz. Stan, who has worked all of Europe and many stations in Canada, the USA and the USSR via RS5, 6, 7 and 8, has also worked the "ROBOT" on RS5 and 7 and explained. "You transmit to RS5 or RS7 on 144MHz sending "RS5 DE G3LQI AR" and the satellite replies, "G3LQI DE . . ." giving a serial number and the words "op ROBOT". The details of this QSO are stored by the satellite and later transmitted to the control station for their records. Robots for RS5 can be

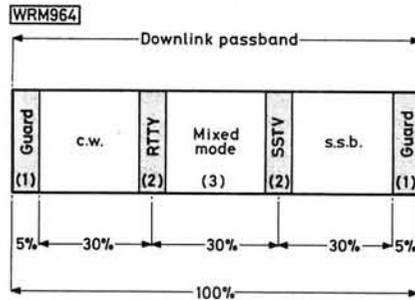heard on 29.331MHz and for RS7 on 29.341MHz, c.w. only.



- (1) Guard area to avoid interference to beacons. These frequencies are available for emergency and bulletin stations.
- (2) RTTY and SSTV are placed at the edge of the c.w. and s.s.b. passbands, conforming to their usage at h.f. where RTTY is present within the c.w. space and SSTV is transmitted in the s.s.b. sub-band.
- (3) Mixed mode area. This is recommended for crystal controlled stations, or by DXpedition stations, or anyone wishing to work both c.w. and s.s.b. stations.

Bill Kelly heard signals from stations in France, Germany, Italy, Switzerland and the USA at 1617 on September 24 on 29.345MHz, possibly from RS3 and on the same day John Coulter heard "V CQ welcome contest via RS on IOKT 2100 to 2OKT 2100Z log Moscow Box 88 til 30 Nov AR" and it continued for 3 days. I logged the same message at 0830 on the 25th and very strong signals from a satellite on 29.331MHz giving information about RS7 at 0755 on October 1.

Readers wishing to know more about amateur satellite communications and membership of AMSAT-UK, should send an s.a.e. to Ron Broadbent G3AAJ, AMSAT-UK, London, E12 5EQ.

28MHz Beacons

John Coulter, Winchester, received signals from the beacon modes of KA1YE/B on October 9 and 10,

W2NZH/B on the 8th and 9th and from the Canadian beacon VE3TEN on the 12th. Among the beacon signals heard by **Ted Owen**, Malden, were ZS5VHF on September 29 and LU1UG on the 30th and Ted Waring logged the South African beacon ZS1CTB on October 7 and 10. Ted Waring, with his 3-transistor, home-brew, receiver and long wire antenna has forty 28MHz beacons to his credit and the information in his log and the logs from John Coulter, Norman Hyde, Henry Hatfield, Bill Kelly, Ted Owen and me, provided the material to complete our monthly beacon chart, Fig. 1. Between October 11 and 15, Henry noticed that the tone of the South African beacon Z21ANB, was "funny" almost auroral and at 1815 on the 18th, two German beacons DLOIGI and DK0TE, were both 599 during one of those short lived, out of season, sporadic-E disturbances.

RTTY

In our October issue, I published one of the RTTY callsign patterns, received by Peter Lincoln, from EA3CJF and now, **Norman Jennings**, Rye, has copied another of these, Fig. 2. He tells me that his camera was 0.6m away from his monitor screen and set at f5.6 at 0.5 seconds. During the four weeks prior to October 12, Norman, using a Telereader CWR670E terminal unit, received RTTY signals from 52 countries including CY0SPI, the St. Paul Island Expedition, who was very strong on 21MHz, EL2AT and HC1JX on 28MHz, then on several occasions RTTY signals from the ARRL HQ station W1AW, Fig. 3.

To stimulate interest in the 3.5MHz band RTTY, **Geoff Dalton G4GZK**, Wolverhampton, **Eddy G5YM**, Twyford, **Frank Wyr G8RY**, Wolverhampton and **Noel Lapper GW2DUR**, Llanelly have started a Monday through Friday net, between 0730 and 0830, around 3588kHz. Frank and Geoff use Creed 444 machines and Eddy and Geoff have both built BARTG terminal units. Frank has a Spacemark SRD-1 terminal unit and Noel uses Microdot gear. "Callers in are welcome" writes Frank, who recently installed quarter wave, gamma matched, phased verticals for 14MHz and finds this antenna most effective for DX QSOs.

Although Peter Lincoln did not spend a great deal of time on RTTY during the month preceding October 13, he did log signals from Asia and the Far East and at 2200 on September 27 he added HP2SM to his new countries list.

I noted a marked increase in RTTY activity on the h.f. bands and between September 21 and October 19, I copied signals from 23 countries, CT, EA, F, G, GM, HA, I, IT9, LA, OE, OH, OK, ON, OZ, SM, SP, SV, UK, VE, VK, W, YO and 9H1 on 14MHz, 11 countries, EA, CT, I, IT9, JA, J28, KA, UK, W, YU and 5Z4 on 21MHz and a W on 28MHz.

At 1947 on October 10, I copied IOAOF, a regular on 14MHz RTTY, operating with the special callsign IOAOF for 1983 Holy Year.

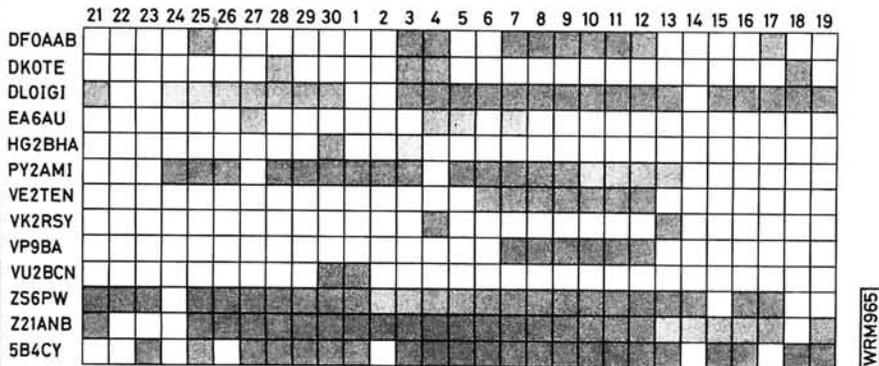


Fig. 1: Distribution of beacon signals

Congratulations to **Ted Double G8CDW**, contests and awards manager of the British Amateur Radio Teleprinter Group, on achieving The Scandinavian WSRV Award at the highest level, the Gold Rosette. "Not only is he the first G station to do so, he is the only s.w.l. to do it at all" writes G3GJW, the BARTG chairman, in their Autumn newsletter. He adds "It took 4 years of patient effort with simple equipment: an indoor 14MHz dipole and one of the last valve receivers, a FRDX400. The BARTG newsletter is always full of gen and readers wishing to join the organisation should send an s.a.e. to their membership secretary, Mrs T. Crane, Greta Woods, Bromley Rd, Ardleigh, Colchester CO7 7SF.

One of the interesting results from an extensive survey taken among BARTG members is that the first 3 places in the league table of bands used for RTTY are 144MHz, 14MHz and 3.5MHz.

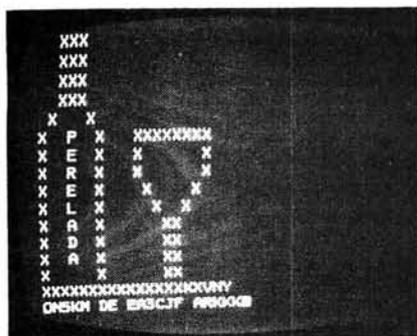


Fig. 2: Signal from EA3CJF

Norman Jennings

Tropospheric

Following a sharp drop to 29.7in (1005mb) at 1800 on September 21, the atmospheric pressure, measured at my QTH, rose to 30.2 (1022) by midday on the 22nd, giving good v.h.f. conditions which continued to improve as the pressure reached 30.4 (1029) at 1100 on the 25th and gradually fell back to 30.0 (1015) by midnight on the 29th. Apart from watching his barometer, **Harold Brodribb** followed the path of this high pressure system on the weather maps published in his daily newspaper. By noon on October 1, the pressure was up again to 30.1 (1019) where it hovered until midnight on the 12th, when it began to fall rapidly reaching 29.4 (995) at 0600 on the 16th and then began to rise again slowly as a bad weather system passed by.

"The period September 23 to 29 produced exceedingly good 144 and 432MHz tropo DX into all parts of Europe from Denmark and Scotland, Ireland to south of France, Austria, Spain and Switzerland", writes John Fell G8MCP, who added that most of the stations he worked in Germany and Holland commented on the high level of sunshine. John noted an extensive opening, lasting all day, into Europe with strong signals from 144MHz stations in Austria and

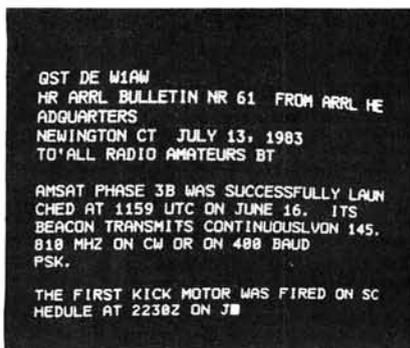


Fig. 3: ARRL station

Norman Jennings

Czechoslovakia on the 23rd. On the 24th and 25th, John worked stations in France, Germany and Holland and was pleased with his QSOs with DL5BBL at 770km and PA3DBJ/P who was using only 2.5 watts to a hand-held HB9CV antenna at sea level. During the period, John had contacts with stations having the prefix letters, DF, DG, DL, DJ, EA, EB, EI, F, GD, GI, GJ, GM, GW, ON, PA, PE, PI and TO. He also heard signals from the 144MHz beacons in England GB3CTC 144.915MHz and GB3VHF 144.925MHz, France FX-0THF 144.895MHz and FX8VHF 144.955MHz, Scotland GB3ANG 144.975MHz, Spain EA1VHF 144.867MHz and Switzerland HB9HB 144.865MHz. When John heard the Spanish beacon at 0742 on the 28th, he also heard signals from EA1TA and during the evening heard many EA and EB stations being worked on both the 144 and 432MHz bands. John concluded the evening and I would think a very satisfactory week, by working G14OMK, G18EWM and G14GVS crossband 144/432MHz and received a 59 plus 40dB signal from EI9Q on 432MHz. A fine effort John, you have shown how rewarding amateur radio can be during a tropospheric opening as did **Mike Joy G4MUB**, Lychett Matravers, when he heard LX1JA in QSO with a French station on S20 f.m.

Simon Hamer heard Dutch stations working through the 144MHz repeater in Birmingham GB3BM R5 on the 23rd, signals through the repeaters in Leicester GB3CF R0 and Wells GB3WR R0 on the 25th, Enfield GB3NL R7, Hertfordshire GB3PI R6, Bournemouth GB3SC R1 and Stoke-on-Trent GB3VT



Fig. 4: QSL card from Eric Sandever

R1 on the 27th and EI1DK R0 on the 29th. At 0900 on the 23rd, I heard an ON working through a repeater on R5, around 0200 on the 24th three PD0s were working G stations through a repeater, possibly GB3KN, on R4, strong signals through GB3BM on the 25th and at 0200 on the 28th I logged a QSO through the Malvern Hills repeater GB3MH R3, between ON1OY in Ohey and a GW4 in Abergavenny.

Band II

John Berridge, who uses a National Panasonic or a Pioneer receiver when he is in South Wales and a Sanyo portable, which has travelled the world with him, when he is in London, finds that Band II provides both "curiosity and interest". While John was in Algiers he listened to a classical concert from Madrid, around 85MHz, at 1930 on Sundays and during the early part of the September opening he heard a French station, in Cherbourg, around 103MHz, about 500km from his QTH in Wales.



Fig. 5: QSL card from Fred Southwell

I counted at least 17 foreign stations between 87 and 104MHz at 0900 on September 23rd and at 1030 **Ian Davidson**, Carmarthen, received 10 French stations around 94MHz on his Sanyo G1005 music centre fed by a 6-element Yagi. At midday on the 25th and around 0700 on the 26th, **Denis Parkes**, Brighton, received the ILR station Signal Radio and many Belgian and French stations some in good stereo, between 100 and 104MHz. On the 27th, Denis heard BBC Radios Devon and Cornwall. Not too far from Denis, at St. Leonards-on-Sea, Harold Brodribb logged between 10 and 20 French stations each day from September 23 to 30, Dutch stations on the 26th, 27th and 28th and Radio Gwent on the 23rd, 24th and 27th.

"I heard so many Belgian, Dutch, French and German stations, mostly in good stereo, but could not identify all of them" writes **Steve Green**, who, like Simon Hamer also heard the BFBS from Bielefeld on 101.5MHz. In addition to the abundance of continentals in Band II, Simon heard *The Breakfast Show* on ILR Southern Sound and identified other locals: Capital Radio, LBC, Piccadilly Radio, Thames Valley, Hereward Radio and Radio Trent.

TELEVISION

by Ron Ham BRS15744

Reports: as for VHF Bands, but please keep separate.

LA4TG learned about G3WW's SSTV activity through reading *PW*, Peter Lincoln logs two SSTVs chatting about our magazine, Fig. 1, and the end of September tropospheric opening are among the main talking points this time.

Amateur Television

Alan Cross G6NQE, Bristol, using a *PW* converter and 48-element multibeam on August 17, received amateur television pictures from **Ken Stevens** G4BVK, Figs. 2 and 3, and **R. Worth** G8ZQF, Fig. 4, both in Bristol. Alan tells me that two of the receive only stations G6ASP and G8YCL are also using *PW* converters and G6SPA has a converted television receiver.

Sporadic-E

Sheffield reader **Tony Palfreyman** began TVDXing on July 29 when he installed a 2-element beam for Band I, which he made from the drawings in Roger Bunney's book, *Long Distance Television*. Between then and the end of the 1983 sporadic-E season Tony received pictures from Czechoslovakia, Scandinavia, Spain, the USSR and Yugoslavia and during a disturbance on October 4 he added Hungary MTV-1 Budapest on Chs. R1 49.75MHz and R2 59.25MHz and Romania TVR Bucuresti on Ch. R2. Around 1600 on October 3, I received a strong test card from Yugoslavia scribed RTV JRT LJNA on Ch. E3 55.25MHz and **Simon Hamer**, New Radnor, reports a disturbance around Chs. E3 and R2 during the evening of October 10.

Although we are some 5 months away from the 1984 sporadic-E season it is well worth taking a look at Band I for these short-lived openings which often occur during the winter months and can be very rewarding. Weak pictures were seen on Chs. R1 and E4, during such an event around 1815 on October 18.

SSTV

During the evening of September 27, **Richard Thurlow** G3WW, March, had a two-way colour slow-scan QSO with **H. Mitchell** G4DYB in Sheffield and with **John Stace** G3CCH in Scunthorpe. G4DYB was using a Robot 400 with a recently-fitted VE3EGO Colorscan 403 kit of three memories and automatic rotating colour filters in front of his mono TV camera, and John was using his home-brew SSTV equipment. "Both were transmitting beautiful colour pictures in the 8 seconds 3x3x3 mode", writes Richard, who tells me that the Essex f.m. SSTV net on 144.5MHz continues every Wednesday evening and following a

meeting between himself and G3LUI at the Colchester Mobile Rally, they later exchanged both 24 seconds and normal time-frame colour pictures.

Richard met up with G3CCH, G4DYB and G4NJI at the Doncaster show and they were impressed by the new Volker Wrasse SC-1 SSTV/FAX converter. During a lull in the second part of the DL SSTV contest, Richard had a 2-way QSO with **Martin Hyde** G4IHZ, Barnsley, who was using the SC422A he purchased at Doncaster the previous day. On October 8, G4NJI used his new SC-1 Volker Wrasse converter to send 24 seconds single-frame, three-colour, 256x256-lines, 64-shades, pictures to G3CCH on 144.230MHz. John Stace taped the pictures and transmitted one, Fig. 3, to Richard, who received it under marginal conditions with his SC422A at 0900 on the 9th. Richard recorded the picture with a 20-year-old Polaroid camera and was pleased with the results all around.

Among the recent newcomers to 2-way SSTV operations are DL5GR, DL8GG, EA3AO, I1CEL, I5TSC, LA5VB, OE5RI, VE3DX 50 miles within the Arctic Circle, WA1VIA, WA3SRU, WB4IQB, WB4ONI, WB4UFP and WD8OHA on 144MHz and G6OHM on 144MHz f.m. At 1616 on October 10, Richard had a QSO with VK6SP giving Richard his 1929th first-time 2-way SSTV QSO, believed to be a world record.

"There have been a few openings to north-America on 14MHz", writes **Peter Lincoln**, Aldershot, who, on October 11, copied a CQ from WA1ZMJ, Fig. 10 and watched a QSO between DJ0GF, Fig. 1 and G4GOZ who were talking about the SSTV pictures which have appeared in this column. Peter, who sent me one of the pictures under discussion, has sent a copy to DJ0GF and we look forward to hearing more about it. I am always pleased to hear about the activities of SSTV stations at home and overseas, so, don't forget lads and lasses, drop me a line and I will use what I can.

Tropospheric

The atmospheric pressure, see *VHF Bands*, did all the right things to give us that tropospheric opening which began on September 23 and ended on the 30th. "And what an opening it was" writes **Mike Bennett**, Datchet, who, on the 23rd saw the Belgian station RTBF 1 on Ch. E3 and the Dutch station NED-1 on Ch. E4 62.25MHz. Around 1950 the NED-1 test card was followed by a clock and for about 3 hours Mike saw adverts for after-shave, a bank, biscuits, an appeal for the disabled, Scotch Whisky and the *Willy*

Ross Lotto Show followed by the news. Mike tells me that the word VARA is a programme company name and that this Dutch station was so strong that no other signal could break through. At 1239 on the 23rd, while using my Plustron TVR5D with its own rod antenna near the Kent/Sussex border, I received strong test cards labelled SW1-HGR on Ch. E9, RTL with a digital clock showing 1339 and Wendelstein around Ch. E10, any ideas? I also noted strong, negative, pictures from French TV transmitters on about 10 spots between Chs. 21 and 69. I tried again at 1452 and received test cards from Belgium BRT TV1 and BRT TV2 on Chs. 43 and 45. About an hour later I was at Sissinghurst Castle and identified the French captions FR3 and TF1 between Chs. 21 and 27 and during a final check at 1821, situated above the Bewlbridge reservoir some 100m a.s.l., I found a very strong Dutch station giving a programme schedule on Ch. E10 and the u.h.f. band was full of French stations. During that evening, **Adrian Butcher**, Washington, watched an American film, *Not With My Wife*, with Belgian sub-titles on BRT-1 and saw their clock, programme line-up and the news with a YL presenter. On August 21, Tony Palfreyman installed a pair of Triax BB Grids, and a Triax combiner and amplifier for u.h.f. to feed his Grundig 6400T receiver and was rewarded with DX from Holland on Chs. 39 and 45 on the 25th and Germany ARD ZDF on the 28th and 30th Figs. 7 and 5. Among the pictures Tony received during the September opening were again from Holland and Germany on Chs. 39 and 45, Figs. 6 and 8 and a mystery test card, Fig. 9, on Ch. 55, any ideas?

"I do not have any u.h.f. DX gear but today I had a chance to use some while a lift was in progress" writes **Paul Hardy**, Reading, on September 24, when, between 1036 and 1330 he received test cards from Belgium RTBF-1, BRT TV1, France FR3, TF1, TDF, Antenne 2 and Holland PTT-NED 1 and PTT-NED 2. Paul also saw *Clash of the Titans* and *Dukes of Hazzard* from France and Teletext from Holland. A fine effort Paul, you picked a good day to give it a try. During the event, **Harold Brodribb**, St Leonards-on-Sea, received pictures from Belgium, France and Holland between Chs. 21 and 69. Simon Hamer also looked around the UK for DX and received Anglia TV from Sandy Heath on Ch. 24, Sudbury Ch. 41 and Tacolneston Ch. 59, Central TV from Oxford Ch. 60 and Waltham Ch. 61, London Weekend TV from Crystal Palace Ch. 23 and Guildford Ch. 43 TVS from Dover Ch. 66, Hannington Ch. 42 and Midhurst Ch. 58 and Tyne Tees from Bisdale on Ch. 29. Simon also watched such



Fig. 1: SSTV picture Peter Lincoln



Fig. 2: Test card G6NQE



Fig. 3: SSTV picture Richard Thurlow



Fig. 4: ATV test card G6NQE



Fig. 5: German TV Tony Palfreyman



Fig. 6: Dutch TV Tony Palfreyman



Fig. 7: German TV Tony Palfreyman



Fig. 8: German TV Tony Palfreyman

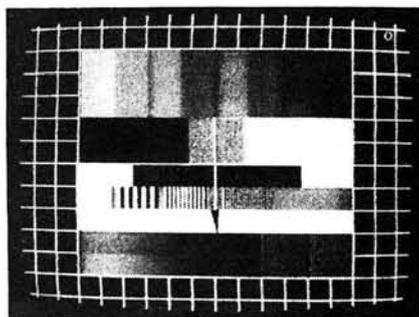


Fig. 9: Mystery test card Tony Palfreyman



Fig. 10: SSTV CQ Peter Lincoln

programmes as *Coast to Coast* on TVS, *South Today* on BBC 1 and *Thames News* from Thames Television.

At 1344 on the 27th, from a site 300m a.s.l., I received test cards from FR3 and TDF on 9 spots between Chs. 21 and 69 and at 1650, at another location some 80m a.s.l., I logged very strong test cards from Belgium, BRT TV2 on Ch. 25 and Warve Canal 28 Tele 2 on Ch. 28 and BRT-II Teletext on Ch. E10.

Between the 23rd and 28th, Steve Green, Malvern, concentrated his efforts on Band III and logged stations from Belgium on Chs. E8, 9 and 10, France E11, Germany E6, 9, 10 and 11 and Holland E5 and 6. Most of the signals Steve received were in good colour and he was pleased to see BRT showing a *Popeye* cartoon with sub-titles.


My thanks to TV DXer Ian Moody, Sutton, for the information that BF272 transistors are manufactured by SGS-ATES (UK) Ltd., Planar House, Walton Street, Aylesbury, Bucks.

Very often specific technical points or statements are made, especially in magazine articles and specialised books, which require further explanation to the reader and this is where I find a glossary of technical terms or a good questions and answers book, dedicated to the subject, is invaluable. Newnes Technical Books have published the third edition of *Q and A Colour Television* by Eugene Trundle (ISBN 0 408 01305 2), and with more than 120 pages of sensible questions and easy-to-read concise answers, in my view, it is well worth a student engineer or TVDXER sporting £2.50 for it.

PARTS FOR RADIO COMMUNICATION...

Have you got a copy of Ambit's latest component catalogue? It's packed with a unique range of components for radio, communications and only 80p from your newsagent or direct. (Includes 3x£1 discount vouchers)

Helical Filters

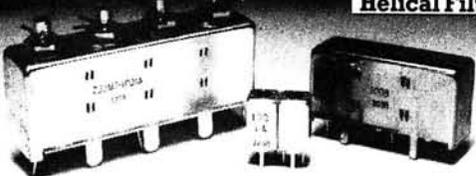


HRQ **7HW** **CBT**

Selected from the Ranges 130-170MHz 400-500MHz

Type Number	Centre	3dB BW	Stock No.	Price	Type
252MT1001A	435MHz	18MHz	17-10011	1.85	7HW
232MT1001A	435MHz	10MHz	17-10010	7.90	HRQ
272MT1008	145MHz	1.2MHz	17-10083	3.15	CBT

* All above 50Ω in/out impedance

Crystal Filters

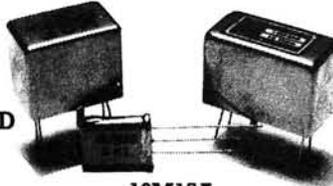

10M08D **10M15A** **10M22D**

Type	10.7MHz	Stock No.	Price
10M15A	2 Pole 15KHz BW	29-10152	0.99
10M22D	8 Pole 2.4KHz BW	20-10028	17.20
10M08D	8 Pole 7.5KHz BW	20-10088	15.50

Plenty more types in the catalogue + ceramic blocks etc.

Coax Relays + Schotky Mixers



CX520D **SBL1** **CX120P**

Type	Ratings		Stock No.	Price
CX120P	150W at 500MHz	PC Mounting	46-90120	11.96
CX520D	300W at 16Hz	N Connectors	46-90520	26.98
SBL1	+7dBm	Double Bal. Mixer	12-00003	4.68

RF Semiconductors

FET's/MosFets

Type	Stock No.	Price
J176	59-02176	0.65
2SK55	59-01055	0.32
2SK168	59-01168	0.37
3SK45	60-04045	0.49
3SK51	60-04051	0.54
3SK60	60-04060	0.58
3SK81	60-04081	1.32
3SK88	60-04088	0.99
40823	60-03823	0.65
3SK112	60-04112	4.60
BF960	60-06960	0.99
BF981	60-06981	1.20
J310	59-02310	0.80

RF Power


Type	Stock No.	Price
MRF237	58-14237	3.20
MRF238	58-14238	16.50
MRF245	58-14245	40.00
MRF475	58-14475	4.60
PT8811	58-18811	9.50
2SC1945	58-01945	2.60
2SC1971	58-01971	2.49
2SC2053	58-02053	0.63
2SC2097	58-02071	14.75
TP2320	58-12320	10.24
VN66AF	60-02066	0.95
ZTX3866	58-03866	0.45
2N3866	58-13866	1.20

PROJECT PACKS

MkII 2m Converter

2m to 10m Converter with 3 chamber Helical filter


40-14401 £14.60

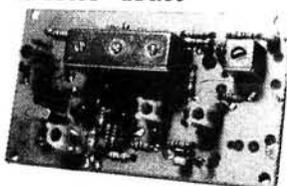

Auto Modulation Meter

This unit will scan 20-175MHz, automatically lock into a NBFM signal and read the deviation.


40-20175 £34.06

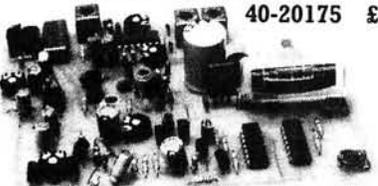

2m Monitor (UOSAT etc)

Complete 2m/UOSAT VHF NBFM receiver system. With mains PSU and high spec ceramic filter.

40-14006 £33.84

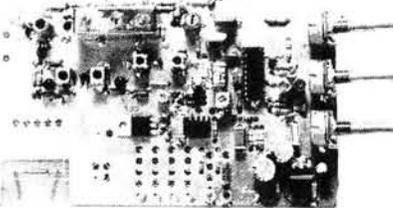

CW Filter

Two stage band pass filter and phase-locked loop to regenerate CW from noisy signals

41-00205 £8.54



UHF converter

70cm to 2m and 70cm to UHF TV Band


40-00170 £24.67



2m Preamp

18dB gain, noise figure less than 1.5dB, impedance 50Ω

40-14400 £3.35

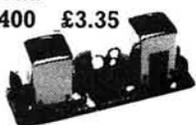

REMEMBER TO ADD P&P 60p — AND VAT!

In stock items despatched within 48 hrs

ambit INTERNATIONAL

200, North Service Road,
Brentwood, Essex CM14 4SG.
Telephone: (0277) 230909

WOOD & DOUGLAS

Our new manufacturing facility in Berkshire will provide an even better service for our extensive range. Credit card orders can also now be taken, ring for details.

PRICE LIST - JUNE 1983-NOVEMBER 1983

New Package Offers		Kit
1. 500mW TV Transmit	(70FM05T4 + TVM1 + BPF433)	30.00
2. 500mW Transceiver	(As 1 above plus TVUP2 + PSI 433)	50.00
3. 10W TV Transmit	(As 1 above plus 70FM10 + BDX35)	50.00
4. 10W TV Transceiver	(As 2 above plus 70FM10 + BDX35)	70.00
5. 70cms 500mW FM Transceiver	(70T4 + 70R5 + SSR1)	70.00
6. 70cms 10W FM Transceiver	(As 5 above plus 70FM10)	90.00
7. Linear/Pre-amp 10W	(144PA4/S + 144LIN10B)	36.00
8. Linear/Pre-amp 25W	(144PA4/S + 144LIN25B)	40.00
9. 70cms Synthesised 10W Trans.	(R5+SY+AX+MOD+SSR+70FM10)	120.00
10. 2M Synthesised 10W Trans.	(R5+SY+SY2T-SSR+144FM10)	100.00

70cms EQUIPMENT

Transceiver Kits and Accessories	Code	Assembled	Kit
FM Transmitter (0.5W)	70FM05T4	38.10	24.95
FM Receiver	70FM05R5	68.25	48.25
Transmitter 6 Channel Adaptor	70MC06T	19.85	11.95
Receiver 6 Channel Adaptor	70MC06R	27.15	19.95
Synthesiser (2 PCB's)	70SY25B	84.95	60.25
Synthesiser Transmitter Amp	A-X3U-06F	27.60	17.40
Synthesiser Modulator	MOD 1	8.10	4.75
Bandpass Filter	BPF 433	6.10	3.25
PIN RF Switch	PSI 433	7.10	5.95
Converter (2M or 10M i.f.)	70RX2/2	27.10	20.10

TV Products	Code	Assembled	Kit
Receiver Converter (Ch 36)	TVUP2	26.95	19.60
Pattern Generator	TVM1	39.93	32.53
TV Modulator	TVM1	8.10	5.30
Ch 36 Modulator	TVMOD1	10.15	6.95
3W Transmitter (Boxed)	ATV-1	87.00	—
3W Transceiver (Boxed)	ATV-2	119.00	—

Power Amplifiers (FM/CW Use)	Code	Assembled	Kit
50mW to 500mW	70FM1	14.65	8.85
500mW to 3W	70FM3	19.65	13.25
500mW to 10W	70FM10	30.70	22.10
3W to 10W	70FM3/10	19.75	14.20
10W to 40W	70FM40	58.75	45.20
Combined Power Amp/Pre-Amp	70PA/FM10	48.70	34.65

Linears	Code	Assembled	Kit
500mW to 3W	70LIN3/LT	25.75	18.60
3W to 10W (Compatible ATV1/2)	70LIN3/10E	39.10	28.95

Pre-Amplifiers	Code	Assembled	Kit
Bipolar Miniature (13dB)	70PA2	7.90	5.95
MOSFET Miniature (14dB)	70PA3	8.25	6.80
RF Switched (30W)	70PA2/S	21.10	14.75
GaAs FET (16dB)	70PA5	19.40	12.65

2M EQUIPMENT

Transceiver Kits and Accessories	Code	Assembled	Kit
FM Transmitter (1.5W)	144FM2T	36.40	22.25
FM Receiver	144FM2R	64.35	45.76
Synthesiser (2 PCB's)	144SY25B	78.25	59.95
Synthesiser Multi/Amp (1.5W O/P)	SY2T	26.85	19.40
Bandpass Filter	BPF 144	6.10	3.25
PIN RF Switch	PSI 144	9.10	7.75

Power Amplifiers/Linears	Code	Assembled	Kit
1.5W to 10W (FM) (No Changeover)	144FM10A	18.95	13.95
1.5W to 10W (FM) (Auto-Changeover)	144FM10B	33.35	25.95
1.5W to 10W (SSB/FM) (Auto-Changeover)	144LIN10B	35.60	26.95
2.5W to 25W (SSB/FM) (Auto-Changeover)	144LIN25B	40.25	29.95
1.0W to 25W (SSB/FM) (Auto-Changeover)	144LIN25C	44.25	32.95

Pre-Amplifiers	Code	Assembled	Kit
Low Noise, Miniature	144PA3	8.10	6.95
Low Noise, Improved Performance	144PA4	10.95	7.95
Low Noise, RF Switched	144PA4/S	18.95	14.40

GENERAL ACCESSORIES

Toneburst	TB2	6.20	3.85
Piptone	PT3	6.90	3.95
Kaytone	PTK3	8.20	5.95
Relayed Kaytone	PTK4R	9.95	7.75
Regulator	REG1	6.80	4.25
Solid State Supply Switch	SSR1	5.80	3.60
Microphone Pre-Amplifier	MPA2	5.95	3.45
Reflectometer	SWR1	6.35	5.35
CW Filter	CWF1	6.40	4.72
TVI Filter (Boxed)	HPF1	5.95	4.75

6M EQUIPMENT

Converter (2M i.f.)	6RX2	27.60	19.95
---------------------	------	-------	-------

Prices include VAT at the current rate. Please add 75 pence for postage and handling to the total order. ATV-1 and ATV-2 orders should include £3.00 for postage and insurance. Goods in stock - allow 7 days.

MAIN AGENTS

J. BIRKETT (0522) 20767 DARWEN ELECTRONICS (0254) 771497

When you purchase one of our products you are guaranteed success because we offer full back up and servicing on any item no matter how small. The confidence we have in the products is reflected in the range available and the low service return rate incurred.

Why not try a kit today? We accept credit cards or written orders direct to our industrial premises or at rallies and exhibitions throughout the season. Enjoy your hobby more by building your next rig or accessory.

Unit 13, Yours Development
Aldermaston, Reading RG7 4PQ
Tel 07356 5324. Telex 848702



ELECTROVALUE

THE P.W. ENTHUSIAST'S

A-Z

BUYING GUIDE

It's amazing what you'll find in the pages of our current autumn price list, be you beginner, expert or professional. The list below gives some idea of the enormous stocks we carry, and our service is just about as good as meticulous care and nearly twenty years of specialised experience can make it. WRITE, PHONE OR CALL FOR OUR AUTUMN PRICE LIST NOW!

IT'S FREE!

Good Bargains
Good Service
Good Choice



- | | | | |
|--------------------|---------------|------------------|-----------------|
| Access facilities | Connectors | Lamps | Semi-conductors |
| Aerosols | Discounts | Meters | Switches |
| Batteries | Electrolytics | Opto-electronics | Solder tools |
| Boxes | Ferrites | Potentiometers | Tools |
| Breadboards | Grommets | Pot Cores | Transformers |
| Computers & Eqpmnt | Hardware | Quantity prices | Vero products |
| Capacitors | I.Cs | Resistors | Visa facilities |
| | Knobs | Relays | Zener diodes |

ELECTROVALUE LTD., 28 St Jude's Road, Englefield Green, Egham, Surrey TW20 0HB, (0784) 33603. Telex 264475: Northern Shop (Callers only) 680 Burnage Lane M/c M19 1NA. (061-432 4955) EV Computing Shop, 700 Burnage Lane, Manchester (061-431 4866).

ALL VALVES & TRANSISTORS

Call or phone for a most courteous quotation
01-749 3934

We are one of the largest stockists of valves etc. in the U.K.

Open Monday to Friday 9-1 pm, 2.00-5.30 pm.

TRADE & EXPORT 01-743 0899

Delivery by return of post

COLOMOR ELECTRONICS LTD. (01-907 3530 LONDON)
170 GOLDHAWK ROAD, LONDON W12

SPECTRUM COMMUNICATIONS

RECEIVE PRE-AMPS. General purpose variable gain 0-20dB. Low noise 1dB typical. Types RP2S, RP4S, RP6S, RP10S. Box kit **£11.78**. Boxed built **£19.50**.

RECEIVE CONVERTERS. 2 metre, 4 metre or 6 metre, low noise <1.5dB. Gain 26dB 10 metre IF, LO output, type RC2-10, RC4-10. Unboxed kit **£14.30**. Boxed built **£27.30**.

TRANSMIT CONVERTER. 2 metre, 4 metre or 6 metre, 0.5W output, 0.1-1W 10 metre I/P and low level LO I/P, types TC10-2, TC10-4, TC10-6. Unboxed kit **£15.00**. Built **£23.50**.

TRANSMIT AMPLIFIER. 2 metre linear, 1-5W I/P, 10-25W O/P, unswitched, type TA2. Kit **£13.54**. Built **£19.54**.

FREQUENCY MODULATOR-DEMODULATOR. 455KHz. IF, NBFM add-on for CBAM transceivers Type FM455. Unboxed kit **£5.98**. Unboxed built **£7.98**.

Delivery within 7 days subject to availability
Vat inc. prices, add 35p for P&P. Send SAE for product price list.

UNIT B6, MARABOUT INDUSTRIAL ESTATE, DORCHESTER, DORSET. TEL 0305 62250



SCARAB SYSTEMS

39, Stafford Street, Gillingham, Kent ME7 5EN.
(0634-570441)

141, Nelson Road, Gillingham, Kent ME7 4LT.
(0634-575778)

AMATEUR RADIO PROGRAMS

RTTY

	ZX.81	SPECTRUM
Cassette & PCB	£13.45	£15.00
Complete package	£25.10	£29.55
Assembled & Tested	£30.00	£35.00

Please note these RTTY programmes do need a decoder/encoder.

BBC-B £9.20	VIC-20 £9.00
PET £7.50	Dragon 32 P.O.A.
MPTU-1 RTTY/AMTOR terminal unit for use with all computer based systems. £69.70.	

Morse Tutor programs all at £5.00 each for:-
BBC-B* DRAGON 32* TRS-80* SPECTRUM*.

MORE BBC. PROGRAMS.

CW.QSO. Complete Rx/Tx program	£7.50
MULTIFILE. A versatile filing system	£10.25
TELLTEX. 21-page VIDEO MAGAZINE	£15.00

All prices include VAT & postage. Please allow 14 days delivery.

Write for further details of these and other programs.

WANTED Amateur Radio, Technical & Business software for all popular home micro's.



NEW! SBLA 144e

Masthead 144 MHz Preamp



- ☆ 250W pep through-power handling
- ☆ 1dB typical noise figure
- ☆ variable gain
- ☆ unique balanced pair of BF981's for excellent dynamic performance
- ☆ superb filtering (of course!)
- ☆ rf or hard switching facilities
- ☆ £79.90 + 2.50 p&p inc. vat

Want to know more? Then please ring or write for details.
If in stock, items usually delivered within seven days.

muTek limited the rf technology company



Dept PW, Bradworthy Holworthy Devon EX22 7TU.
Telephone: 0409 24-543



FREE CAREER BOOKLET

Train for success in Electronics Engineering, T.V. Servicing, Electrical Engineering—or running your own business!

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the fields of electronics, T.V., electrical engineering—now it can be your turn. Whether you are a newcomer to the field or already working in these industries, ICS can provide you with the specialised training so essential to success.

Personal Tuition and 80 Years of Success

The expert and personal guidance by fully qualified tutors, backed by the long ICS record of success, is the key to our outstanding performance in the technical field. You study at the time and pace that suits you best and in your own home.

You study the subjects you enjoy, receive a formal Diploma, and you're ready for that better job, better pay.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

ELECTRONICS ENGINEERING

A Diploma Course, recognised by the Institute of Engineers & Technicians as meeting all academic standards for application as an Associate.



T.V. & AUDIO SERVICING

A Diploma Course, training you in all aspects of installing, maintaining and repairing T.V. and Audio equipment, domestic and industrial.




ELECTRICAL ENGINEERING

A further Diploma Course recognised by the Institute of Engineers & Technicians, also covering business aspects of electrical contracting.



RUNNING YOUR OWN BUSINESS

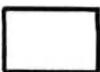If running your own electronics, T.V. servicing or electrical business appeals, then this Diploma Course trains you in the vital business knowledge and techniques you'll need.



Name

Address

ICS

ICS
Dept Q276
160 Stewarts Road,
London SW8 4UJ.



01-622 9911
(all hours)

HENRY'S AUDIO ELECTRONICS

COMPUTERS • COMMUNICATIONS • TEST EQUIPMENT • COMPONENTS

VISIT OR PHONE • OPEN 6 DAYS A WEEK • ALL PRICES INC VAT



NEARLY 1/2 PRICE

COMPLETE WITH FULL HANDBOOK, 3 ROLLS PAPER £99.95 inc. VAT. (UK post etc. £1.05) (List approx. £187) £86.91 - VAT. Full 96 CH ASC II = 40 CPL = 280 Data Bell Auto-underline = 50 Graphic Symbols = Back Space = Self Test = VU/HOR TABS = 7 x 10 Matrix = 4.4" Wide Paper Bidirectional = 220/240 V AC = Size Approx. 9.8 x 2.8 x 7.2" SUITABLE FOR: TANDY • BBC • ORIC • NASCOM • GEMINI • ACORN • NEW BRAIN • DRAGON • etc. etc. (Your enquiries invited). (Interface unit with leads £15 - estate model).

PRESTEL ADAPTOR 3 card set with data etc (P/S -/- 12V and -5V) £69.95 inc. VAT

CHERRY ADD-ON KEYPAD 16 button pad non-encoded £5.95

MODEM CARD 6T approved ready assembled unit with data and accessories. £39.95 inc. VAT




SANYO DM21 12 HIGH RESOLUTION MONITOR 12" green display. Composite video. 1280 characters. Over 15 MHz B/W. 240V AC 34 w. 16" x 11 1/2" x 12 1/2". Alphanumeric and Graphic display. Usually £89.95 - £99.95 incl VAT. Price £69.95 (UK C/P & ins £2.05)



I.T.T. 2020 CABINET Complete PROFESSIONAL Case beautifully constructed with cut out for one 'CHERRY' keyboard, plus ample room to house a COMPLETE SYSTEM and power supply. Complete with fittings. (Case top detachable) Unit is silver grey in colour. Robust construction. Sliding front with side ventilation. Ideal for NASCOM, ACORN, TANGIERNE or your own system. Size 16" x 15" x 4" (front sloped). £27.50 inc. VAT (UK C/P £2.50)



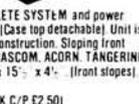
LOGIC PROBES LP10 10 MHz £26.95 DLP50 50 MHz with carry case and accessories £49.95




HIGH VOLTAGE METER Direct reading 0/40 KV. 20K/Volt. £23.00 (UK C/P £5p)



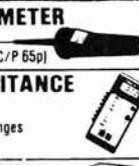DIGITAL CAPACITANCE METER (UK C/P £5p) 0.1 pf to 2000 mfd LCD 8 ranges DM6013 £52.75



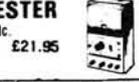TRANSISTOR TESTER Direct reading PNP, NPN, etc. TC1 (UK C/P £5p) £21.95



VARIABLE POWER SUPPLIES (UK C/P £1.00) PP241 0/12/24V, 0/1A £35.00 PP243 3 amp version £59.95 PS1307S 8/15V 7 amp twin meter £24.95



FREQUENCY COUNTERS PFM200A 200 MHz hand held pocket 8 digit LED £77.60 MET1008 digit LED bench 2 ranges 100 MHz £102.35 MET6008 digit LED bench 3 ranges 600 MHz £132.25 MET1000 8 digit LED 3 ranges 1 GHz £182.85 TF40 8 digit LCD 40 MHz, Thandar £126.50 TF200 3 digit LCD 200 MHz, Thandar £166.75



DIGITAL MULTIMETERS

with case (rotary switches) + Side button - case £2.95
K025C 13 range 0.2A DC £23.50
2 meg ohm £23.50
K0305 16 range 10A DC £26.95
2 meg ohm £26.95
K030C 26 range 1A AC/DC 20 meg ohm £29.50
Nemes 3000 30 range 10A AC/DC £33.50
20 meg ohm £33.50
6010 - 28 range 10A AC/DC 20 meg ohm £34.40
7030 4 - AS6010 high acc. 0.1% basic £41.30
K0615 16 range 10A DC 2 meg plus Hfe tester £39.95
SIFAM 2200B 21 range 2A AC/DC 20 meg Bench Models £29.95
TM355 29 range LED 10A AC/DC 20 meg Thandar £86.25
TM356 26 range LCD 10A AC/DC 20 meg Thandar (Replaces TM353) £97.75
TM351 29 range LCD 10A AC/DC 20 meg Thandar £120.75
SIFAM 2500 24 range LCD 2A AC/DC 20 meg £79.95
ALSO IN STOCK: Thurbly, Matrix and Beckman. Professional series incl. True RMS, etc.

MULTIMETERS (UK C/P 65p)

C7081 50 K/Volt range doubler, 10A DC. Total 36 ranges. Special Offer £12.50
HM102BZ 20K/V/10A DC 22 range & cont. buzzer £13.50
TMK500 23 ranges 30K/V. 12A DC plus cont. buzzer £23.95
MH56R 20K/V. 22 range pocket £10.95
830A 26 range 30K/V. 10A AC/DC overload protection, etc. £23.95
360TR 23 range 100K/V. Large scale 10A AC/DC plus Hfe £39.95
AT2100 31 range 100K/V deluxe. 12A AC/DC £33.50
AT1020 18 range 20K/V. Deluxe plus Hfe tester £18.95
YN360TR 19 range 20K/V plus Hfe tester £15.95



SIGNAL GENERATORS (220/240V AC)

FUNCTION: All sine/square/triangle/TTL etc.
TG101 0.02HZ-200KHZ £113.85
TG102 0.2HZ-2 MHz £166.75
PULSE
TG105 Various facilities 5 Hz-5 MHz £97.75
AUDIO: Multiband Sine/Square
LA627 10 Hz to 1 MHz £90.85
AG202A 20 Hz to 200 KHZ (list £94.50) £83.50
LAG 120A 10 Hz-1MHz Low Distortion £159.85
RF
SG402 100 KHZ to 30 MHz (list £79.50) £69.50
LS617 100 KHZ to 150 MHz £79.35

OSCILLOSCOPES

Full specification any model on request. SAE by post.
'HM' Series NAMEG: 'SC' THANDAR: 'CS' TRIO: '3' CROTECH: 'V' HITACHI
SINGLE TRACE UK C/P £3.00
3030 15 MHz 5mV, 95mm tube plus component tester £177.10
SC110A Miniature 10 MHz battery portable £171.00
Post free
Optional carry case £6.84 AC adaptor £6.69 Nicads £12.50
HM103 15 MHz 2mV 6 x 7 display plus component tester C/P £3.00 £181.70
DUAL TRACE (UK C/P £4.00)
HM203/4 Dual 20 MHz plus component tester £303.60
CS1562A Dual 10 MHz (List £321.00) £269.50
3131 Dual 15 MHz - component tester £276.00
CS1566A Dual 20 MHz All facilities (List £401.35) £349.50
HM204 Dual 20 MHz plus component tester £419.75
sweep delay £419.75
HM705 Dual 70 MHz sweep delay £676.00
V212 Dual 20 MHz £399.25
V222 Dual 20 MHz plus extra facilities £391.00
V422 Dual 40 MHz portable £586.50
V203F Dual Trace 20 MHz sweep delay £408.25
V134 Dual Trace 10 MHz storage £1092.50
All HITACHI, CROTECH & TRIO • With probes MODELS AVAILABLE
OPTIONAL PROBE KITS
X1 £7.95 X10 £9.45 X1 - X10 £10.50
Huge stocks of semiconductors, components, tools, etc. Large range of CB equipment and telephones in stock.



RST

MAIL ORDER CO.
Langrex Supplies Ltd.,
Climax House,
159 Fallsbrook Road, Streatham, SW16 6ED.
SPECIAL EXPRESS MAIL ORDER SERVICE

A231	£p	EM87	2.50	PY81	1.50	6AN8A	3.50	6SA7	3.00
CL33	2.75	EN91	7.05	PY82	1.50	6AQ5	2.25	6SC7	2.75
DY867/7	4.00	EY51	2.75	PY83	1.25	6AR5	3.50	6S17	3.25
DY802	1.50	EY86	1.75	PY88	2.00	6AS6	8.56	6SK7	3.50
EB8CC	7.46	EY500A	3.00	PY800A	4.00	6AS7GA	8.75	6SL7GT	3.00
E180F	9.90	EZ80	1.50	PY801	1.50	6AT6	1.25	6SN7GT	3.00
E801F	21.26	EZ81	1.50	QV02-6	16.50	6AU6	5.00	6S7	2.75
EABC80	1.25	GY501	3.00	QV03-10	14.10	6AW8A	3.75	6S7M	2.50
EB91	1.50	GZ32	4.00	QV03-20A	48.38	6B7	3.25	6V6GT	2.25
EBF80	1.50	GZ33	4.75	QV06-40A	48.38	6B8	3.25	6X5GT	1.75
EBF89	1.50	GZ34	3.00	QV03-12	6.80	6BA6	1.50	7C1	4.50
EC91	8.00	GZ37	4.75	R18	9.24	6BA7	5.00	7C1A	4.50
ECC33	4.50	KT61	5.00	R19	2.50	6BE6	1.50	7C2	4.45
ECC35	4.50	KT66	8.00	SP41	6.00	6BH6	2.50	90C1	6.00
ECC81	1.75	KT77	8.00	SP61	4.00	6B16	2.25	150B2	6.50
ECC82	1.75	KT88	11.00	SP61	4.00	6B16	2.25	150C2	3.25
ECC83	1.75	N78	15.00	SP61	4.00	6B16	2.25	150C4	6.00
ECC85	1.75	OA2	3.25	SP61	4.00	6B16	2.25	12AX7	1.75
ECC88	2.10	OB2	4.35	U19	13.75	6B8A	3.50	12BA6	2.50
EC91	8.83	OC3	2.50	U25	2.50	6BS7	6.00	12BE6	2.50
ECF80	1.55	OD3	2.50	U26	2.50	6BW6	6.00	12BY7A	3.00
ECH35	3.00	PC86	2.50	U37	12.00	6BW7	1.50	12HG7	4.50
ECH42	3.50	PC88	2.50	UABC80	1.25	6BZ5	2.75	30FL1/2	1.38
ECH81	3.00	PC92	1.75	UBF89	1.50	6C4	1.25	30P4	2.50
ECL80	1.50	PC97	1.75	UCH42	2.50	6C6	1.75	30P19	2.50
ECL82	1.50	PC900	1.75	UCH81	2.50	6C8BA	2.50	30PL13	1.80
ECL83	3.00	PCF80	2.00	UCL82	1.75	6CDEGA	5.00	30PL14	1.80
ECL86	1.75	PCF82	1.50	UCL83	2.75	6CDE	3.75	75C1	4.50
EF37A	5.00	PCF86	2.50	UF89	2.00	6CH6	13.00	85A2	4.45
EF89	2.75	PCF84	2.00	UL41	3.50	6CW4	8.00	90C1	6.00
EF41	3.50	PCF802	2.50	UL84	1.75	6D6	1.75	150B2	6.50
EF42	4.50	PCF85	1.70	UY41	2.25	6D05	6.00	150C2	3.25
EF50	2.50	PCF808	1.70	UY85	2.25	6E8A	3.00	150C4	6.00
EF54	5.00	PCH200	3.00	VR105330	2.50	6E85	1.85	57B2	30.00
EF55	3.50	PCL82	2.00	VR15030	2.50	6F6	3.00	805	45.00
EF80	1.75	PCL83	3.00	Z755	25.00	6G6	2.75	807	3.75
EF86	1.75	PCF84	2.00	Z803U	19.00	6H6	3.00	811A	18.33
EF91	2.95	PCL85	2.50	Z021	3.25	6H56	3.77	812A	18.33
EF92	6.37	PCL86	2.50	3B28	40.00	6J5	4.50	813	125.86
EF183	2.00	PCL805	2.50	4CX250B	40.00	6J6	8.83	866A	20.03
EF184	2.00	PD500	6.00	5R4GY	3.50	6J7	4.75	872A	20.00
EH90	1.75	PF200	2.50	5U4G	3.00	6J8A	5.00	931A	18.50
EL32	2.50	PL36	2.50	5V4G	2.50	6J58C	6.00	2050	7.00
EL33	4.00	PL81	1.75	5Y3GT	2.50	6K4N	2.50	5763	4.50
ELK34	3.00	PL82	1.50	5Z3	4.00	6K6GT	2.75	5814A	4.00
EL36	2.50	PL83	2.50	5Z4GT	2.50	6K7	3.00	5842	12.00
EL81	5.25	PL84	2.00	6/30L2	1.75	6K8	3.00	6080	14.00
EL84	2.25	PL504	2.50	6AB7	3.00	6K8D	7.00	6146A	8.25
EL85	2.75	PL508	2.50	6AH6	5.00	6L6	3.00	6146B	8.25
EL91	9.69	PL509	6.00	6AK5	5.99	6L6GC	3.00	6883B	8.25
EL95	2.00	PL519	6.00	6AL5	1.50	6L7	2.50	6973	4.00
EL360	8.50	PL802	6.00	6AM6	6.02	6B06	7.50	7360	10.00
EM81	2.50	PY33	2.50	6AN5	4.75	607	3.75	7586	12.00

Open daily to callers: Mon-Fri 9 a.m.-5p.m.
Valves, Tubes and Transistors - Closed Saturday
Terms W.O.O. only, allow 7 days for delivery. Tel: 01-677 2424/7.
Prices excluding VAT add 15%
Quotations for any types not listed S.A.E.
Post and packing 50p per order
Telex 946708
Prices correct when going to press

ANTENNES TONNA (F9FT)

50MHZ 144MHz 15 element + £34.30(a)
4 element £14.95(a)
9 element fixed £17.71(a)
9 element portable £20.00(a)
9 element crossed + £32.43(a)
13 element portable + £31.05(a)
NEW 17 element fixed £37.66(a)
435MHZ 19 element £20.70(a)
19 element crossed + £34.27(a)
21 element 432MHz £29.67(a)
21 element ATV £29.67(a)
144/435MHZ Oscar Special £34.27(a)
9 & 19 element +

YOUR NUMBER ONE CHOICE FOR 6m, 2m, 70, 24 & 23cm ANTENNAS 1250MHz OR 1296MHz £25.90(b)
23 element + £140.00(a)
4 x 23 el antennas - power splitter - stacking frame £140.00(a)
Telescopic Portable Masts 4 x 1m £18.68(a) 3 x 2m £21.85(a)
4 x 2m £33.20(a)
ANDREW HELIX LDF-50 COAXIAL CABLE Attenuation per 100ft. 144MHz-0.8dB 435MHz-1.6dB. 1296MHz-2.9dB
£3.20 per metre (a). 'N' Type connectors for LDF4-50 male or female £10.35.
MICROWAVE MODULES - ROTATORS - COAXIAL CABLES ETC.
POWER SPLITTERS AVAILABLE FOR 2 OR 4 ANTENNAS

+Denotes 50Ω ONLY - all others 50Ω or 75Ω impedance
PLEASE ADD CARRIAGE AS SHOWN (a) £4.00. (b) £1.80. ALL PRICES INCLUDE VAT AT 15%
Terms: Cash with order, ACCESS - VISA - telephone your card number.
FOR FULL SPECIFICATION OF OUR RANGE SEND 30p FOR CATALOGUE
Callers welcome, but by telephone appointment only please. Goods by return.
RANDAM ELECTRONICS (P)
12 Conduit Road, Abingdon, Oxon OX14 1DB. Tel: (0235) 23080 (24 hours)

Northampton Communications

PHONELINK

A separate unit that enables any radio system to have a direct link to the telephone network.

Phone for further details:
Northampton Communications Limited
Communications House
76 Earl Street, Northampton. NN1 3AX.
Telephone: (0604) 33936 or 3820

THE AMATEURS PROFESSIONAL SUPPLIER

TRIO / ICOM / LAR PRODUCTS / AERIALS



TRIO R2000

General Coverage

All Mode Receiver

PRICE £398 INC VAT CARR £5



TRIO TR7930

2 Meter FM Transceiver

Memory - Auto Scanning

PRICE £305 INC VAT CARR £5



TRIO 130V

Mobile HF Transceiver

SSB-CW All Amateur Bands

PRICE £456 INC VAT CARR £5



TRIO TS430S

Base HF Transceiver

General Coverage Receiver

All Mode FM Optional

PRICE £736 INC VAT CARR £5

LEEDS AMATEUR RADIO

Please send for our Catalogue and/or Antenna Catalogue

60p EACH or £1.00 FOR BOTH PLUS PRICE LIST

Goods By Return Subject To Availability

SALES/SERVICE/MAIL ORDER



27 COOKRIDGE ST. LEEDS LS2 3AG

34 NEW BRIGGATE LEEDS LS1 6NU

LEEDS 452657 the PROFESSIONALS!



QUARTZ CRYSTALS

STOCK CRYSTALS		CRYSTALS FOR 2 METRES	
TX CRYSTALS	RX CRYSTALS	£1.96 FOR ONE CRYSTAL	£1.74 WHEN 2 OR MORE PURCHASED CHANNELS IN STOCK
HC6/U 4 & 8 MHz 30PF	44 MHz SERIES RES		
HC25/U 12 MHz 30 & 40PF	44 MHz SERIES RES		
HC25/U 18 MHz 25 & 20PF	14/15 MHz 20 & 30PF		
4 METRE CRYSTALS FOR 70.26 in HC6/U AT £2.25 each			
TX B.78250 RX 29.7800 6.74666			
70CM CRYSTALS £5.00/pr or £2.50 each			
For Pve PFI PFI2 & PFI3 series. Wood & Douglas and FDK Multi U11			
SUB (433.2) RB0 RB2 RB4 RB6 RB10 RB11 RB13 RB14 RB15.			
CONVERTER CRYSTALS IN HC18/U AT £2.85 each			
22,000, 38,666, 70,000, 96,000, 101,500, 116,000			
FREQUENCY STANDARDS £2.75 each			
HC6/U	200kHz	455kHz	1000kHz
HC18/U	1000kHz	7.00MHz	3.50MHz
			5.00MHz
			10.00MHz
			100.00MHz
TONEBURST, I.F. & MPU CRYSTALS IN HC18 £2.25 EACH			
7.168 MHz (for 1750 kHz Tone) 10.245 MHz (for 10.71 F.)			
3.2769 4.000 5.03288			
YAESU CRYSTALS FOR FT101's FT901, etc. £4.00 each			
Many available ex stock. (A list is available on request please send S.A.E.)			
A stamped addressed envelope with ALL enquiries please.			

FUNDAMENTALS		MADE TO ORDER CRYSTALS	
FREQUENCY RANGE	PRICE	FREQUENCY RANGE	PRICE
6 TO 30kHz	£23.00	3rd OVT	21.00 TO 65.00MHz
30 TO 80kHz	£15.00	5th OVT	60.00 TO 110.00MHz
80 TO 150kHz	£10.50	5th OVT	110.00 TO 125.00MHz
160 TO 999kHz	£7.00	5th, 7th &	125.00 TO 150.00MHz
1 TO 1.5MHz	£10.75	9th OVT	150.00 TO 250.00MHz
1.5 TO 2.5MHz	£5.00		
2.5 TO 4.0MHz	£4.75		
4 TO 21MHz	£4.55		
21 TO 25MHz	£6.50		
25 TO 30MHz	£8.50		

Unless otherwise requested fundamentals will be supplied for 30pf load capacitance and overtones for series resonant operation.

HOLDERS: PLEASE SPECIFY WHEN ORDERING - else HC25/U supplied for XTLS above 3MHz HC13U 6-200kHz HC6/U & HC33U 170kHz-170MHz HC18/U & HC25/U 2-250MHz.

DISCOUNTS: Price on application for 10+ units to same frequency/spec. or bulk purchases of mixed frequencies. We supply xtals for use in U.K. repeaters.

COMMERCIAL CRYSTALS: Available on fast delivery and at competitive prices. Please send for list stating interests.

EMERGENCY SERVICE: for XTALS 1 to 125MHz. Add the surcharge for each XTAL. Days refer to working days. 4 days + £12. 6 days + £7. 8 days + £5. 13 days + £3.

CRYSTAL SOCKETS HC6 & HC25 £0.20 each. MINIMUM ORDER CHARGE £1.50.

TERMS: Cash with order post Inc. to U.K. & Ireland. Cheques & P.O.'s to QSL LTD.



QuartzLab

MARKETING LTD

P.O. Box 19
Erith
Kent DA8 1LH

Telephone: 01-690 4889 24hr Ansafone: Erith (03224) 30630
Telex: 8813271 GECOMS - G (Attention QUARTSLAB)

DRAE VHF WAVEMETER



Designed for VHF operation **£27.50**



VARIABLE BENCH PSU

3-30 volts, 10 amps, twin meters
switched-mode **P.O.A.**

PRICES OF THE COMPLETE RANGE

VHF Wavemeter	£27.50
4 Amp 13.8V PSU	£30.75 + £1.50 carr.
6 Amp 13.8V PSU	£49.00 + £2.50 carr.
12 Amp 13.8V PSU	£74.00 + £2.50 carr.
24 Amp 13.8V PSU	£105.00 + £3.50 carr.
Morse Tutor	£49.00 + £1.00 carr.
3-way VHF Switch	£15.40 + £0.50 carr.
SSTV Receiver	£189.00

(Please Check Availability)

COMMERCIAL UNITS -
Please enquire for details

- ★ DC-DC Converters
- ★ Switched Mode PSU's
- ★ Regulated Battery Chargers
- ★ Uninterruptable Power Supplies
- ★ Custom Built PSU's

ALL PRICES INCLUDE VAT

Davtrend Limited



The Sanderson Centre, Lees Lane, Gosport PO 123UL Gosport 20141

Delivery normally from stock but please allow up to 28 days for delivery.

SMALL ADS

The prepaid rate for classified advertisements is 36 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £12.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Dept., Practical Wireless, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St, London, SE1 9LS. (Telephone 01-261 5785).

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Software

ELECTRON, ORIC, BBC programs: Morse Tutor £4.50, Locator £4.50, BBC RTTY (requires TU) £5. SAE details: T. Tugwell, 11 The Dell, Stevenage, Herts.

COLOUR GENIE RTTY/CW, machine code, numerous facilities, details: 0742 882913 G4PHL/G8UEB.

TRS-80 programs for CW, data file, QRA, etc. etc. SAE to STUDIO DEEJAY, 7 Fitzwilliam Place, Billingham, Lincoln LN4 4EU.

Aerials

50M (165ft) AERIAL WIRE. Strong PVC covered copper - £4.80 inc. Post. W. H. WESTLAKE, Clawton, Holsworthy, Devon.

AERIAL WIRE. Hard drawn copper 140ft 14swg £6.90, 50 meters 16swg £5.90 including postage. S. M. TATHAM, 1 Orchard Way, Fontwell, Arundel, W. Sussex.

AERIAL BOOSTERS

Next to the set fitting

B45H/G-UHF TV, gain about 20dbs, Tunable over the complete UHF TV band. PRICE £8.70.
BII-VHF/FM RADIO, gain about 14dbs, when on the off position connects the aerial direct to the radio. £7.70.
 All Boosters we make work off a PP3/006P/8F22 type battery or 8v to 18v DC. P&P 30p PER ORDER.
ELECTRONIC MAILORDER LTD, 62 Bridge St, Ramsbottom, Lancs B0 9AG. Tel (070682) 3036
 Access/Visa Cards Welcome SAE Leaflets

G2VF H.F. long and medium wave frame antennas. S.A.E. for details: MR. RYLAND, 39 Parkside Avenue, Millbrook, Southampton.

G2DYM AERIALS KILL THAT INTERFERENCE ANTI-TVI ANTI-QRN

Data sheets, Large 23p SAE.
Aerial Guide 75p.

Callers for Appointment Tel. 03986-215
G2DYM, Uplowman, Tiverton, Devon.

DX - TV's

PLUSTRON TVR50 5" dual band, 825 line VHF/UHF, 5.5/6MHz Sound switching + Radio (AM/FM) £91.05
COLOUR-PAL/SECAM TV's, 4 standards! (UK, France, W. European, M. East) Systems PAL I (For UK), PAL B & G (For Europe), SECAM L (For France), SECAM B (For Middle East) 14" Screen, Brand new £298.50
 Both prices inclusive of VAT and Securicor delivery, both very limited stocks. We are DX specialists, our Catalogue of Aerials, filters and associated hardware costs 54p. SAE all enquiries please. ACCESS/BARCLAYCARD welcome.

SOUTH WEST AERIALS (PW)
 11 Kent Road, Parkstone, Poole, Dorset, BH12 2EH.
 Tel. 0202-738232

NOTICE TO READERS

Whilst prices of goods shown in advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

Receivers and Components

MICRO-TRANSMITTERS VHF/FM, complete kit, and microphone £5.00. Assembled £10.00. Electro-Kit (Mr T. Owens), 62 Candlish Street, Westoe, South Shields, NE33 3JP.

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. FORRESTERS (National Radio Supplies) late Holdenhurst Rd. now at 36, Ashley Rd., Boscombe. Tel. 302204. Closed Weds.

G3LL HAS MOVED. Yaesu Sales & Service, 15 mins. Jun. 31 M6. Free parking. Holdings Ltd., 45 Johnston Street, Blackburn. BB2 1EF. Tel. (0254) 59595.

RADIO CANADA

RADIO PEKING, RADIO AUSTRALIA, VOICE OF AMERICA

A Vega 206 (6 xSW/MW/LW) pulls these and dozens more. £23.45.
 Year's guarantee. Return despatch.
Corrigan-Radiowatch, Building 109, Prestwick Airport, KA9 2RT.



TELEVISION VALVES Ecc82-EF85/183/184-DY86/802-PCF80/802-PCL82/84/85/86, PC86/88/92/97-PY88/800-PL36/504. All 35p Each, P&P 50p. ELECTRONIC MAILORDER, Ramsbottom, Lancashire, BLO 9AG.

VHF CONVERTERS. 140-150MHz, 118-136MHz, 146-174MHz. All mechanically tuned, 10.7MHz IF output. Mosfet RF stage. High sensitivity. £9.75 each. SAE Data, lists: H. COCKS, Cripps Corner, Robertsbridge, Sussex. Tel. 058083-317.

NOW OPEN IN NEWCASTLE

For the best in Electronic Components, Test Equipment and Accessories.
MARLBOROUGH ELECTRONIC COMPONENTS
 15 Waterloo Street, Newcastle NE1 4DE
 Tel. 618377
 Open 9am-6pm Mon-Sat - Easy Parking
 Stockists of:
 Transistors, Resistors, Capacitors, I.C. Diodes, Electronic Books, Etc.

COMPUTER RTTY

Use your micro to transmit and receive RTTY
PL1-PLL RTTY Terminal unit 170Hz Shift . . .
 Transmit & receive, also handles ASCII . . .
 TTL in/out.

Kit 13.50 Built 17.50
FP1-Two channel active filter & PSU for PL1.
 Requires 15/0/15v AC.
Kit 7.25 Built 10.75
 Suitable transformer for above 2.45

Software for the DRAGON 32
RTTY send-receive programme by G4BMK
 Split screen receive-Type ahead buffer OSO review & many other features.
Cassette 12.00 ROM Cartridge 21.00

MORSE transceiver programme up to 150 wpm! Hardware interface also available.
Post and Packing 50p per order.

Other hardware available for the DRAGON 32
 For further details and full price list please send **LARGE S.A.E. to:**
PNP COMMUNICATIONS,
 62 Lawes Avenue, Newhaven,
 East Sussex, BN9 9SB.
P. Simmons G3XUS Tel. (0273) 514465
Callers by appointment only.

BARGAINS GALORE!! Component Packs. Over 100 Special Offers. Silly Prices. FREE list. Write Now. Dept PW1, Fullers Supplies, 22 Verder Grove, Heronridge, Nottingham NG5 9BH.

CRYSTALS Brand new high-precision. You benefit from very large stocks held for industrial supplies. All normal freq standards, baud rates, MPU, and all magazine projects inc: HC33/U: 1.0. £3.75. 2.5625 MHz. £3.50. HC18/U: 4.0. 5.0. 6.0. 7.0. 8.0. 9.0. 10.0. 10.7. 12.0. 15.0. 16.0. 18.0. 20.0. 38.6667 MHz. £3.35. Selected freqs stocked in Glider, Marine and 27 MHz bands. Any freq made to order in 8 weeks from £4.50, 2-3 week service available.
CB Beat "Bleed-Over" with our special 10.695 MHz, 7 kHz BW. HC 18/U Filters £4.00 each. Quantity discounts. Many crystals stocked for CB conversions.
 Prices inc. VAT and UK post. SAE lists.

P. R. GOLLEGE ELECTRONICS
 G3F JW, Merriott, Somersat, TA16 5NS.
 Tel: 0460 73718

ELECTRONIC BARGAIN SUPPLIES

MINIATURE TRANSISTORISED BFO UNIT.

Enables you to receive C.W. and S.S.B. transmission. Fully transistorised (tunable). Very compact. Fits anywhere. Single hole fixing. Brand new with fitting instructions. £6.95. PP 50p.
LIGHTWEIGHT HEADSETS (Govt. release). Brand new 600 ohms impedance. A bargain at £3.50. PP £1.50. 2 pairs for £7.50 post free.

THE GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK

Gives detailed information and circuit diagrams for British and American Government Surplus Receivers, Transmitters and Test Equipment etc. Also suggested modification details and improvements for surplus equipment. Incorporated is a Surplus/Commercial cross reference valve and transistors guide. The standard reference work in this field. Only £7.50 p.p. £1.50. No VAT on books.

HALF-PRICE TRANSFORMER SALE. TYPE 1. Midget clamped type. Input 200/250v. 50 c/s. Output 250-0-250v. 60ma. 6.3v at 2 amps. Price £2.50. P&P £1.50. 2 for £7.00 post free.
 TYPE 2. Upright mounting, fully shrouded. 425-0-425v. 200ma. 6.3v. at 4a. C.T. plus 6.3v at 4a. Plus 5v at 3a. Should be £25.00 each. OUR PRICE £7.50. P&P £2.50. Ideal for valve amplifiers incl. RSC and Linear. TYPE 3. 450-0-450v. 200ma. 6.3v at 4a. C.T. 5v at 3a. Should be £25.00. OUR PRICE £8.00. P&P £2.50. Ideal for group valve amplifiers and also for transmitters. ALL ABOVE TRANSFORMERS HAVE MAINS INPUT, ARE BRAND NEW AND FULLY GUARANTEED. Trade enquiries welcome.

GENUINE AFV TANK HEADSETS AND MIKE £3.50 per pair, p.p. £1.50. 2 pairs £7.50 post free. All headphones fitted with ex-ministry plug. Standard jack plugs available 25p each. 2 for 40p. Headphone extension sockets available at 25p each. 2 for 40p. Impedance 600 ohms. All headphones in good condition.

PYE POCKET PHONE PFI DATA AND INSTRUCTIONS. Contains circuits, layouts, operating and modification details for amateur use etc. £1.50 post free.

CAPACITOR BARGAIN PACKS. Bulk purchase enables us to offer a pack containing 500 new standard polyester capacitors. 0.01 (MFD-0.47MFD). 100 to 600v working. PRICE £8 per 500 lot. PP. £1. 1000 lot £16.50 post free. Trade enquiries invited.

MINIATURE MAINS TRANSFORMER. Mains input. Output G-0-6V. 250MA. 90p. P&P 35p. 2 for £2. Post free. 10 for £8.75. Post free.

FERRITE RODS. 4" long. 5/16ths diameter. Packs of 10 £1.35. P.P. 50p. 10 packs (100 rods) £10. Carr. £2.50.

BULK BARGAIN TRANSISTOR RADIO/CASSETTE SERVICE PACK. Contains at least £25 worth of new transistor radio and cassette spares. Loads of those hard to obtain components and spares including hardware. Ideal for the radio service engineer. **ONLY £6.50.** P.P. £1.50. Double Pack £12.75 carr. free.

GENUINE EX-GOVT COLLAPSIBLE AERIALS. A fully adjustable highly efficient whip aerial in 5 sections. Length 1 1/2 metres. Closed 300 mm. Copper plated sections. As used on Ex Govt Manpacks. Brand new in makers boxes. £2.50 each, p.p. 75p. 2 for £5 post free. Aerial bases for same, £2.75, P&P £1.25.

HAVE YOU SEEN THE GREEN CAT? 1000's of new components, radio, electronic, audio at unbelievably low prices. Send 60p for catalogue.

GOVT SURPLUS LIST 60p.
VALVE LIST. Valves from 1925 to 1980. Many obsolete types. Modern TV, radio and transmitting valves. Send 60p. Or £1 (Refundable on purchase) for all three.

WE SELL VALVES OF ALL TYPES. Please send SAE for your requirements.

Try a **JUMBO PACK.** Contains transistors, resistors, caps, pots, switches, radio and electronic devices. **OVER £50 WORTH FOR £11.00.** Carriage and packing £2.50.

Please add 15% VAT to all orders including carriage and PP.

Myers Electronic Devices

Dept. PW7, 12/14 Harper Street, Leeds LS2 7EA. Tel: (0532) 452045. Retail premises at above address (opposite Corals). 9 to 5 Mon to Sat. Sunday 10 to 1 by appointment. **GOVT. SURPLUS ITEMS ALWAYS IN STOCK.**

Security

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
- HIGHEST QUALITY EQUIPMENT
- FREE DIY DESIGN GUIDE
- FULLY ILLUSTRATED
- MICROCHIP CIRCUITRY
- QUICK DESPATCH SERVICE
- FULL INSTRUCTIONS

SEND SAE OR PHONE

C-TEC SECURITY, Dept PW
60 Market St, Wigan WN1 1HX.
Telephone (0942) 42444



Veteran & Vintage

OVER 200 RADIO'S 1920's-1950's. SAE for list. Valve Radio's etc. Repaired - restored. RADIO VINTAGE, 250 Seabrook Road, Seabrook, Hythe, Kent. CT21 5RQ. Phone (0303) 30693. Anytime.

VINTAGE VALVE WIRELESS RECEIVERS plus repairs, service information, spares, valves. S.a.e. information MR M. SMALL, 8 Cherrytree Road, Chinnor, Oxfordshire, OX9 4QY.

Books and Publications

CONFIDENTIAL FREQUENCY LIST lists 10,000 CW, aero, coastal, fax, etc., frequencies £8.25 + 60p P&P. Guide to RTTY frequencies lists 4500 commercial, aero, UN, coastal, etc., frequencies £7.35 + 50p P&P. World Press Services Frequencies news RTTY services listing GMT, and country plus more £4.55 + 50p P&P. 2+ books P&P free. INTERPRODUCT LTD., PW2, Stanley, Perth: tel. 073882-575.

INTERNATIONAL LISTENING GUIDE. Complete Directory of External Services in English & Frequency Survey of Short-wave Broadcasting Stations. Free Sample: DXLS, Merianstrasse, D-3588 Homburg, West-Germany.

SHORTLISTS SECONDHAND BOOKS SALE. Wireless, Television, others. State interest. SAE: GOSLING, 19 Moor-side Road, Westmoors, Dorset.

DIAL-SEARCH

3rd edition (1984)

Much enlarged (48 pages). Up-to-date checklists Europe MW, LW; U.K. MW, VHF; indexed. U.K. map & large Europe map for easy bearings. Signature tunes; SW selection; music survey; etc., etc. Price £2.75 (abroad 15 IRCs) includes postage.

Direct from George Wilcox (PW1),
9 Thurrock Close, Eastbourne,
East Sussex BN20 9NF.

AIRCRAFT COMMUNICATIONS HANDBOOK (Europe), including spot MF, HF, VHF, UHF, frequencies. Military & Civil Airports, Air Traffic Control Centres, Long Range Stations, Broadcast Times, Navigation Beacons, Co-Ordinates, Callsigns, Maps, etc. £5.50 P/P £1. PLH Electronics, 70 Vallis Road, Frome, Somerset, BA11 3EJ.

CALLING ALL DX-ERS

The 1984 International Edition of the Finnish DX Diary is now available from the sole UK agents. Packed with information for SW enthusiasts this Diary is invaluable for DX-ing in 1984 and will make an ideal gift.

We can also supply SWL cassettes, log report books and reception confirmation forms plus the complete range of Babani technical books and publications on DX-TV. Send 16p in stamps (or 2 IRC's) for our latest catalogue to:

HS PUBLICATIONS

Dept. W(Y), 7 Epping Close, Derby DE3 4HR.

Educational

COURSE FOR CITY & GUILDS, Radio Amateurs Examination. Pass this important examination and obtain your licence, with an RRC Home Study Course. For details of this and other courses (GCE, Career and professional examinations, etc.) write or phone: THE RAPID RESULTS COLLEGE, Dept JX7, Tuition House, London, SW19 4DS. Tel. 01-947 7272 (9am-5pm) or use our 24hr Recordacall Service: 01-946 1102 quoting Dept JX7.

Courses

CONQUER THE CHIP... Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. C1, Reading, Berks RG1 1BR.

NEW!! Scientifically prepared courses to get you through the R.A.E. examinations. 01-346 8597 for free booklets.

Service Sheets

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc., £1.50 plus SAE. Service Manuals on Colour TV and Video Recorders, prices on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

TECHNICAL INFO SERVICES

76 Church St - Larkhall - Lanarks

FULL SIZE SERVICE SHEETS

£2 and I.s.a.e.

CTVs/MusC £3 & I.s.a.e.

Worlds largest collection service manuals 30's - date from £4.50-£35 each

Repair data/circuits almost any named TV/VCR £9.50

S.a.e. brings any quotation!
FREE 50p mag. inc. service sheet!
Pricelists unique elect. publications

FOR FAST QUOTES
RING 0698 883334

For Sale

DATA DYNAMICS 390 teletype with integral tape punch and reader. Working order £50. 19 rolls tape £10. 11 rolls printer paper £10. Gestetner FB12 photocopier and 1000 sheets copier paper £200. Murphy V20155 BW TV 20". Good picture all channels. £15. Enquiries to 0202-874496.

ADVERTISING USED EQUIPMENT is fast and easy with List-A-Rig. Send £1 for every 40 words or less for immediate entry. For a copy of the latest list send 2 first class stamps. G3RCQ, 65 Cecil Avenue, Hornchurch, Essex.

SPECIAL! 39 off Hammond A100 30/50 valve amplifiers. New still in box mounted on wooden plinth, with volume and tone control. £39.00 each plus VAT plus £2.00 P&P. Tel. 0704 822433.

CALL SIGN BADGES professionally engraved by return of post. £1.50 cash with order. (State name and call sign). AYLMEYER-KELLY (P), 2 Pickwick Road, Corsham, Wilts. SN12 9BJ.

FREQUENCY COUNTER ACCESSORIES. Having trouble measuring low frequencies? Low pass filter, eliminates false readings. Boxed, BNC connectors £10. Advanced P.L.L. frequency multiplier allows any counter to measure down to 1Hz. Unboxed £11, boxed BNC Connectors £17. P&P free. D. KIRKBY, 54 Ringwood Road, London E.17.

FDK MULTI 700EX 20 watts F.M. beautiful audio as new £135.00. DAVID HARROP G6NWP, 4 Astbury Close, Altrincham, Cheshire WA15 8JA.

YAESU 980 as new £900. AZDEEN 4000 two metre transceiver £160.00. ICOM 25E £180.00. Phone 01-592 7800.

CORNWALL CALLING DE-G3EKK. Good stock receivers, TX's, Scanners, CO-AX, components. Established 1952. Part exchanges. 0872-862575.

"JAY BEAM" BAND II Masthead Amplifiers £5.50. 12 volt P.S.U.'s £9.00 post free. Cheque/PO to BATES, Unit 85, Storforth Lane Trading Estate, Chesterfield, Derby.

YAESU FRG7 RECEIVER as new, £130. Tel. 021-353 8436.

UNIQUE 24 VOLT to 12 volt Voltage Reducer. Either Polarity Battery Connection. Overvolts Protection on outputs. Suit all 24 volt vehicles. SAE to Electrotech, 41 Windermere Road, Manchester M24 3QT.

For Sale - Cont.

AMATEUR EQUIPMENT bought and sold. Cash waiting. Contact: G3RCQ, Hornchurch 55733 evenings.

TRIO R600 RECEIVER and Yaesu A.T.U. £200 o.n.o. Stoke on Trent 88916.

Miscellaneous

BURGLAR ALARM EQUIPMENT. Ring Bradford (0274) 308920 for our catalogue or call at our large showrooms opposite Odsal Stadium.

WAVEGUIDE, FLANGES & DISHES. All standard sizes & alloys (new material only) from stock. Special sizes to order. Call EARTH STATIONS, 01-228 7876. 22 Howie Street, London SW11 4AR.

PRACTICAL WIRELESS PCB's 1.5mm G.F.

ALL TO PRACTICAL WIRELESS SUPPLIED MASTERS

June 83	PW7. WR165 £1.90,	WR166 £3.33
	RTTY with ZX81,	WR167 £3.98
July 83	PW7. WR168 £1.72,	WR169 £1.97
	Marchwood	WR161 £2.06
Oct 83	Dig. cal. WR173 £2.62, Cap M WR174 £2.09	
Nov 83	Sig. gen WR175 £3.79, Dart WR176 £2.38	
VAT included Postage 35p UK. 70p Europe Please send SAE for complete list.		

PROTO DESIGN

14 Downham Road, Ramsden Heath,
Billericay, Essex CM11 1PU. Tel. 0268-710722

MINIATURE TRANSMITTER, professional - with hyper-sensitive pick-up-with hi-fi quality reception on domestic VHF/FM air band radio, using sub-Miniature components for exceptional transmission stability and range, tunable 70-150MHz, size 2" x 1", complete kit, includes all components, ultra-sensitive microphone, illustrated plans etc, only £9.95 post paid. Send cash/cheque/PO to MODULEX (Mr M. Banks), P.O. Box 102, 180 Shepherds Lane, Dartford, Kent, DA1 2PW.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from PVC. Faced steel. Vast range. Competitive prices start at a low £1.50. Punching facilities at very competitive prices. Suppliers only to Industry and the Trade. BAZELLI, (Dept. No. 25), St. Wilfrid's Foundry Lane, Halton, Lancaster LA2 6LT.

QSL CARDS, printed to your own design on white or coloured gloss card. Send for samples. The Nutley Press, 21 Holmehorpe Avenue, Redhill, Surrey RH1 2NB.

MORSE CODE PREPARATION

RECEIVING

Cassette A: 1-12 wpm for amateur radio examination. Cassette B: 12-25 wpm for professional examination preparation. Each cassette is type C90. Price each cassette (including booklets) £4.75.

SENDING

Morse key with separate battery (PP3) - driven solid-state oscillator and sound transducer produces clear tone for sending practice; optional light (solid state) signal included. Price of key with electronic unit £9.95.

Price includes postage etc. Europe only.

MH ELECTRONICS (Dept PW)

12 Longshore Way, Milton,
Portsmouth PO4 8LS.

RARE DX

UNDER QRM? DIG it OUT with a Tunable Audio Notch Filter, between your receiver and speaker, BOOST your DX/QRM ratio, 40dB notch, hear WEAK DX. £16.40.

V.L.F.? EXPLORE 10-150KHz. Receiver £21.20. LOSING DX? Get SPOT-ON with a Crystal Calibrator, between your antenna and receiver, switched 2MHz, 200, 50KHz markets to vhf, £28.20.

Each fun-to-build kit (ask for full list) includes all parts, printed circuit, case, instructions, by-return postage etc, money back assurance, SEND away NOW.

CAMBRIDGE KITS

45 (PA) Old School Lane, Milton, Cambridge.

SELLING OR BUYING

A Classified Advertisement could solve your problem at very little cost.

Ring Laraine on
01-261 5785



PM COMPONENTS LTD. VALVE & COMPONENT SPECIALISTS

SELECTRON HOUSE, WROTHAM ROAD, MEOPHAM GREEN, MEOPHAM, KENT
PHONE 0474 813225. TELEX 966371 PM COMP



NEW BRANDED VALVES				INTEGRATED CIRCUITS				SEMICONDUCTORS				OTHER COMPONENTS																																					
A2087 11.50	ECC83 Philips	EL821 8.50	EL822 12.95	PL84 0.65	GAS5 1.50	12A7 0.85	12A7WA 2.50	AN2140 2.50	AC127 0.20	BC107B 0.15	BF199 0.14	BF200 0.40	TIP32C 0.42	BF258 0.28	BF259 0.28	TIP41 0.45	TIP42C 0.47	TIP47 0.65	TIP146 2.75	TIP295 0.80	TIP305 0.55	TIS91 0.20	2N3054 0.59	2N3055 0.52	2N3702 0.12	2N3704 0.12	2N3705 0.12	2N3707 0.12	2N3708 0.12	2N3737 1.95	2N5294 0.42	2N5296 0.48	2N5496 0.65	2SA715 0.95	2SC496 0.80	2SC1173 1.15	2SC1306 1.00	2SC1449 0.80	2SC1678 1.25	2SC1945 2.10	2SC1953 0.95	2SC1957 0.80	2SC1969 1.95	2SC2028 1.15	2SC2029 1.45	2SC2078 1.95	2SC2314 0.80	2SC2316 1.95	3SD234 0.50
A2134 14.95	ECC85 0.60	EM80 0.70	EM81 0.70	PL500 0.95	GAS7G 7.50	12A7 0.85	12A7WA 2.50	AN240 2.80	AC128 0.28	BC171 0.09	BF259 0.28	BF259 0.28	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42	
A2300 11.50	ECC88 0.85	EM81 0.70	EM82 0.70	PL802 5.95	6A7 0.75	12A6 1.50	12A6V 0.80	LA4400 2.15	AC176 0.22	BC173B 0.10	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
C1148A 115.00	ECC91 2.00	EM84 1.65	EM85 1.10	PY800 0.79	6A7 0.75	12A6 1.50	12A6V 0.80	LA4422 2.15	AC176K 0.31	BC182 0.10	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DAF91 0.45	ECC804 0.60	EM85 1.10	EM87 2.50	PY800 0.79	6A7 0.75	12A6 1.50	12A6V 0.80	LA4422 2.15	AC187 0.25	BC183 0.10	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DAF96 0.65	ECC807 2.50	EM87 2.50	EM87 2.50	PY800 0.79	6A7 0.75	12A6 1.50	12A6V 0.80	LA4422 2.15	AC187K 0.28	BC184 0.10	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DEF22 2.80	ECC807 2.50	EM87 2.50	EM87 2.50	PY800 0.79	6A7 0.75	12A6 1.50	12A6V 0.80	LA4422 2.15	AC188 0.25	BC212 0.09	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DEF22 2.80	ECC807 2.50	EM87 2.50	EM87 2.50	PY800 0.79	6A7 0.75	12A6 1.50	12A6V 0.80	LA4422 2.15	AD142 0.79	BC212L 0.09	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DET23 39.00	ECC82 0.85	EN91 1.10	EN92 4.50	QV003-10 5.50	6B6E 0.72	12B6A 1.50	12B6B 1.50	MC1330P 2.00	AD161 0.39	BC213 0.09	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DET24 35.00	ECC86 0.85	EN91 1.10	EN92 4.50	QV003-10 5.50	6B6E 0.72	12B6A 1.50	12B6B 1.50	MC1330P 2.00	AD161 0.39	BC213 0.09	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DF92 0.60	ECH35 1.60	EY88 0.55	EY88 0.55	QV003-20A 3.95	6B6E 0.72	12B6A 1.50	12B6B 1.50	MC1330P 2.00	AD161 0.39	BC213 0.09	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DF96 0.65	ECH42 1.00	EZ80 0.60	EZ81 0.60	QV006-40A 18.50	6B6E 0.72	12B6A 1.50	12B6B 1.50	MC1330P 2.00	AD161 0.39	BC213 0.09	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DK91 1.90	ECH81 0.58	EZ81 0.60	EZ81 0.60	QV006-40A 18.50	6B6E 0.72	12B6A 1.50	12B6B 1.50	MC1330P 2.00	AD161 0.39	BC213 0.09	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DK92 1.20	ECH84 0.69	EZ90 0.96	EZ90 0.96	QV006-40A 18.50	6B6E 0.72	12B6A 1.50	12B6B 1.50	MC1330P 2.00	AD161 0.39	BC213 0.09	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DK96 2.50	ECL80 0.60	GZ22 1.00	GZ22 1.00	QV006-40A 18.50	6B6E 0.72	12B6A 1.50	12B6B 1.50	MC1330P 2.00	AD161 0.39	BC213 0.09	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DL92 0.60	ECL82 0.65	GZ33 4.50	GZ33 4.50	QV006-40A 18.50	6B6E 0.72	12B6A 1.50	12B6B 1.50	MC1330P 2.00	AD161 0.39	BC213 0.09	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25	BU126 1.60	BU205 1.30	BU208 1.39	BU208A 1.50	BU326A 1.52	MRF450 12.50	MRF453 17.50	MRF454 23.50	MRF475 10.00	MRF477 25.00	OC71 0.40	R2008B 1.70	R2010B 1.70	R2540 2.48	TIP29 2.48	TIP29C 0.42	TIP30C 0.42	TIP31C 0.42			
DL96 2.50	ECL84 0.74	GZ34 2.15	GZ34 2.15	QV006-40A 18.50	6B6E 0.72	12B6A 1.50	12B6B 1.50	MC1330P 2.00	AD161 0.39	BC213 0.09	BF336 0.34	BFX29 0.30	BFX84 0.26	BFX85 0.32	BFX86 0.30	BFX87 0.30	BFX88 0.25	BFX89 0.25	BFY50 0.21	BFY51 0.21	BFY52 0.25	BFY53 0.25	BT106 1.77	BT108 1.49	BT116 1.20	BT105 1.22	BU108 1.69	BU124 1.25																					

INDEX TO ADVERTISERS

A.H. Supplies	24
A.J.H. Electronics	82
Amateur Electronics UK	8, 9
Amateur Radio Exchange	15
Ambit International	87
Amcomm Services	16, 62
Amtron	94
Antex	Cover 3
Ant Products	10
Armon Products	96
Audio Electronics	90
Avcomm	40
Bi-Pak	10
Birkett, J.	96
B.N.O.S. Electronics	81
Bredhurst	Cover 2
British National Radio & Electronics School	14
C-Tec Security	93
C.M. Howes	94
C.Q. Centre	11, 95
Cambridge Kits	93
Colomor Electronics	88
Corrigan Radio Watch	92
Cricklewood	40
Datong Electronics	10
Davtrend	91
Dewsbury Electronics	82
Electronics Mail Order	92
Electrovalue	88
Enfield Emporium	24
Garex Electronics	24
George Wilcox	93
G2DYM Aerial	92
Gemini Communications	13
G.T. Technical Services	93
Greens Telecom	96
H.A.C. Shortwave Products	95
H.S. Publications	93
I.C.S. Intertext	89
I.L.P. Electronics	12, 13
Lee Electronics	31
Leeds Amateur Radio	91
Lexton, H.	65
Lowe Electronics	2, 3
Maplin Electronics	Cover 4
Marlborough Electronics	92
M.H. Electronics	93
Microwave Modules	32
Mutek	89
Myers Electronics	92
Northampton Communications	90
P.M. Components	94
Photo Acoustics	40
P.N.P. Communications	92
P.R. Gollidge	92
Proto Design	93
Quartzlab	91
Rapid Results College	82
R.S.T. Valve	90
Radio Component Specialists	95
Radio Shack Ltd.	39
Randam Electronics	90
Scarab Systems	89
Selectronic	82
S.E.M.	14
South Midlands Communications	4, 5
South West Aerials	92
Spectrum	88
Stephens-James Ltd	32
Tandy	58
Thacker, A.H.	32
Thanet Electronics	6, 7, 40
Ward, Reg	23
Waters & Stanton	57
Wholesale Communications	75
Wireless World	96
Wood & Douglas	88

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

TRIPLE-T

TRANSISTOR RECEIVER

for use with headphones
or small speaker.

Construct your own
SHORTWAVE RECEIVER

for only

£29.00

for the complete kit

All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

"H.A.C."

SHORT-WAVE PRODUCTS

P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, West
Sussex RH19 3SZ.

BAKER LOUDSPEAKERS

Make	Model	Size	Watts	Ohms	Price
Baker Hi-Fi	Major	12in	30	4/8/16	£16.00
Baker Hi-Fi	Superb	12in	30	8/16	£26.00
Baker Hi-Fi	Group 45	12in	45	4/8/16	£16.00
Baker Hi-Fi	Auditorium	12in	45	8/16	£24.00
Baker Hi-Fi	Auditorium	15in	60	8/16	£27.00
Baker P.A.	DG75	12in	75	4/8/16	£20.00
Baker P.A.	Group 100	12in	100	8/16	£26.00
Baker P.A.	Disco 100	12in	100	8/16	£26.00
Baker P.A.	Group 100	15in	100	8/16	£35.00
Baker P.A.	Disco 100	15in	100	8/16	£35.00
Baker Disco	twin turntables, twin speakers, Headphones, Microphones, Slide Controls, 150W	£300, 300W	£399	car. £30	

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p, 500mF 12V, 15p; 25V 30p; 50V 40p; 100mF 12V, 20p; 25V, 35p; 40V, 50p; 100V £1.20;

LOW VOLTAGE CAPACITORS

1200mF/76V, 80p, 2000mF 63V 25p; 25V, 42p; 40V, 60p; 2000mF/100V, £1.50, 2500mF 50V, 70p; 3000mF 50V, 85p, 3300mF 63V, £1.50; 1500mF 100V, £1.20, 4700mF 40V, £1.00; 63V £1.80

HIGH VOLTAGE ELECTROLYTICS

8/450V	45p	16+16/450V	85p	32+32+32/325V	50p
16/450V	45p	32+32/350V	85p	32+32+32/450V	95p
32/350V	75p	32+32/500V	£2.00	100+100/275V	50p
8+8/500V	£1.00	50+50/300V	50p	150+200/275V	50p
8+16/450V	75p	32+32+16/350V	85p	125/500V	£2

VERNIER DIALS

0-100, 30mm, £3.00, 50mm, £2.50.

NEON PANEL INDICATORS, 250V Red 11 x 1.45p.

RESISTORS, 1W, 1W, 1p, 2W, 10p, HIGH STABILITY, 1W 2p, 5p.

LOW OHM, 1 watt 10p. WIRE-WOUND, 5 watt, 10 watt, 20p.

BLANK ALUMINIUM CHASSIS, 6 x 4, £1.75; 8 x 6, £2.20; 10 x 7, £2.75; 12 x 8, £3.20; 14 x 9, £3.60; 16 x 6, £3;

16 x 10, £3.80. All 25in, 18 swg. ANGLE ALI, 6 x 1 x 1in, 30p.

ALUMINIUM PANELS, 18 swg, 6 x 4, 55p; 8 x 6, 90p; 14 x 3, 90p; 10 x 7, £1.15; 12 x 8, £1.30; 12 x 5, 90p; 16 x 6, £1.30;

14 x 9, £1.75; 12 x 12, £1.80; 16 x 10, £2.10.

BLACK PLASTIC box with aluminium face, 61 x 31 x 2in, £1.50.

ALUMINIUM BOXES WITH LIDS, 3 x 2 x 1, £1; 4 x 2 x 2, £1.20; 4 x 4 x 1, £1.20; 6 x 4 x 2, £1.90; 7 x 5 x 3, £2.90; 8 x 6 x 3, £3; 10 x 7 x 3, £3.60; 12 x 5 x 3, £3.60; 12 x 8 x 3, £4.30.

MAINS TRANSFORMERS

250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A £6.00 £2

350-0-350V 250mA, 6.3V 6A CT £12.00 £2

220V 25mA 6V lamp £3.00 220V 45mA 6V 2Amp £4.00 £1

Tapped outputs available

2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V £6.00 £2

1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £6.00 £2

ditto 2 amp £10.50, 3 amp £12.50, 5 amp £16.

5-9-10-16V, 1A £2.50 £1 15-0-15V 1A £4.00 £1

6V, 1A £2.00 £1 15-0-15V 2A £4.50 £1

6-0-6V, 1A £3.50 £1 20V 1A £4.00 £1

9V 250ma £1.50 £1 20-0-20V 1A £4.50 £1

9V 3A £4.50 £1 20-40-60V 1A £4.50 £2

9-0-9V 50ma £1.50 £1 25-0-25V 2A £4.50 £2

9-0-9V 1A £3.50 £1 28V 1A Twice £5.00 £2

10-0-10V 2A £4.00 £1 30V 1A £4.50 £1

10-30-40V 2A £4.50 £1 30V 5A and £4.50 £1

12V 100ma £1.50 £1 17-0-17V 2A £5.50 £2

12V 750ma £2.50 £1 35V 2A £4.50 £1

12V 3A £4.50 £1 TOROIDAL 30-0-30V 4a £4.50 £1

10-0-12V 2A £4.50 £1 and 20-0-20V 1A £8.50 £2

RADIO COMPONENT SPECIALISTS

Dept 2, 337 WHITEHORSE ROAD, CROYDON, SURREY, U.K. TEL: 01-684 1665

Post 65p Minimum

Closed Wed. Same day despatch. (Callers Welcome. Lists 32p.)



SPECIALS

JUST ARRIVED!

24cms A.T.V. CONVERTOR
(Plugs into domestic T.V.) £29.50

HB9-CV ANTENNA
(2 METRE 2 EL BEAM) £8.50

AS ABOVE 70cms
(BOTH INC. MOUNTING CLAMP)
£8.50

Extra Special - Slim Jim £7.00 (inc. p+p)
EDDYSTONE RE1 MARINE GEN. COV. RECEIVER - FEW ONLY £450
Delivery normally within 7 days.

MORSE PRACTISE OSCILLATOR
£13.50 (inc. p+p)
(with key £28.50)

MORSE TUTOR TAPE
(INC. SIMULATED TESTS) £6.50

FT290R ANTENNA EXTENSION
CONVERTS TELESCOPIC AERIAL
TO 3/8 WHIP £10.50

30 FOOT TELESCOPIC MAST
(Not Mail Order) £28.50




See main ad
on page 11



The other side of the micro.

ELECTRONICS & Wireless world

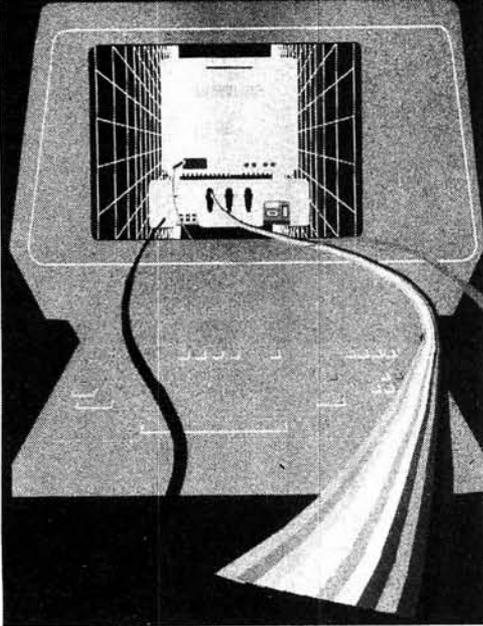

Another first from Wireless World.

This month's Wireless World won't be telling you what a micro does, instead we'll tell you how to choose the micro that's most relevant to your technical needs.

This is possibly the most detailed guide to microcomputer facilities yet to be offered in a monthly publication in the UK.

December's Wireless World lists the available micros, their characteristics and facilities for connecting peripherals.

This is a survey for engineers and experimenters, who need to know how individual computers can be used in their work—the emphasis is on the interfacing capabilities of the machines described.

We were the first with the inside stories of television and video, in the December issue we're first again.

Out now.

PUBLISHED BY
ELECTRICAL-ELECTRONIC PRESS

J. BIRKETT 13 The Strait,
Lincoln, LN2 1JD. Phone 20767

JACKSON SOLID DIELECTRIC VARIABLE CAPACITORS 100p.f. @ £1.15.
MINIATURE AIR SPACED VARIABLE CAPACITOR 10 +10 +20p.f. @ £1.15.
EDDYSTONE TRANSMITTING VARIABLE 30 +30p.f. (60p.f.) @ £2.30.
VMOS POWER TRANSISTORS VN10KM @ 50p, VN90AA @ 80p.
5 MEDIUM POWER VHF TRANSMIT-RECEIVE PIN DIODES for 60p.
5 MEDIUM POWER UHF TRANSMIT-RECEIVE PIN DIODES for 75p.
20 ASSORTED TANTALUM CAPACITORS for 85p.
R.T. TRANSMIT BUTTERFLY PRE-SET VARIABLE CAPACITORS 25 x25p.f. @ 50p.
PNP POWER TRANSISTORS 2N 3789 @ 50p, OC36 @ 50p, AL103 @ 75p.
TANTALUM BEAD CAPACITORS .1u.f. 35vw, .22u.f. 35vw, .33u.f. 35vw, .47u.f. 35vw, 1u.f. 35vw, 2.2u.f. 25vw, 3.3u.f. 16vw, 4.7 u.f. 25vw, 6.8u.f. 25vw, 10u.f. 25vw, 15u.f. 25vw, all at 10p each. 22u.f. 25vw at 15p, 33u.f. 10vw at 15p, 47u.f. 10vw at 20p, 68u.f. 25vw at 20p, 100u.f. 20vw at 40p.
FERRITE BEADS FX 1115 @ 15p doz, 1/2" long type 6 for 10p.
20 WAY LUCAR TAG CONNECTING BLOCK @ 60p.
2 AMP 12 WAY BARRIER STRIPS. 5 for £1.
WIRE ENDED ELECTROLYTICS 1000u.f. 16vw @ 15p, 5000u.f. 15vw @ 20p.
GLASS REED SWITCHES. 10 for £1.
A.T.E.S. GERMANIUM TRANSISTORS AC 138 at 5 for 60p.
2N 3866 R.F. TRANSISTORS unmarked Good at 3 for 75p.
VHF FETS J304 @ 6 for £1, J230 at 25p each.
VHF POWER TRANSISTORS 2N 5590. 10 watt 175MHz 12 Volt @ £4.95.
WOOD AND DOUGLAS KITS available to callers.
Please add 30p for post and packing, order over £3 post free. Goods normally by return.

TELECOM

6 NEW ST, BARNESLEY
TEL 0226 5031

ICOM	YAESU/ SOKA	MICROWAVE MODULES	ALSO L.A.R. MODULES
IC720A	FT102	MML30LS	J BEAM
IC45	FT77	MML50S	CUSHCRAFT
IC740	FT790	MML100S	REVCO
IC290H	FT290R	MML100LS	DATONG
IC25E	FT707	MM2001	SUN
IC2E	FRG7700	MMC14A/28	SUN
IC4E		MMA144V	TONO
R70			

RING US FOR PRICES
BARCLAYCARD/ACCESS/HP FACILITIES

Accurate Digital Multimeters at Exceptional Prices

SPECIFICATION MODELS 6010 & 7030

- ★ 10 amp AC/DC
 - ★ Battery: Single 9V drycell. Life: 200 hrs.
 - ★ Dimensions: 170 x 89 x 38mm.
 - ★ Weight: 400g inc. battery.
 - ★ Mode Select: Push Button.
 - ★ AC DC Current: 200µA to 10A
 - ★ AC Voltage: 200mV to 750V
 - ★ DC Voltage: 200mV to 1000V
 - ★ Resistance: 200Ω to 20MΩ
 - ★ Input Impedance: 10MΩ
 - ★ Display: 3 1/2 Digit 13mm LCD
 - ★ O/load Protection: All ranges
- 28 RANGES, EACH WITH FULL OVERLOAD PROTECTION



NEW ANALOGUE HM 102 BZ SPECIFICATION

With continuity
buzzer and
battery scale

- ★ DC Voltage: 0-25, 1, 2.5, 10, 25, 100, 250, 1000 volts 20,000 ohms/volt.
- ★ AC Voltage: 0-10, 25, 100, 250, 1000 volts, 10,000 ohms/volt.
- ★ Decibels: -20 to +22dB
- ★ DC Current: 0-50, 500µA, 0-5, 50, 500mA, 10A
- ★ Ohmmeter: 0-6 Megohms in 4 ranges. 30 ohms Centre Scale.
- ★ Power Supply: One 1.5 V size 'A' battery (incl)
- ★ Size & Weight: 135 x 91 x 39mm, 280gr.

ARMON ELECTRONICS LTD.

Cottrell House, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH, England

Add 15% to your order for V.A.T. P&P is free of charge.
Quantity discount for trade on application.

Please allow 15 days for delivery.



Telephone 01-902 4321 (3 lines) TELEX No. 923985



Published on approximately the 7th of each month by IPC Magazines Limited, Westover House, West Quay Road, Poole, Dorset BH15 1JG. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon and Gotch (Asia) Ltd.; South Africa - Central News Agency Ltd. Subscriptions INLAND £13 and OVERSEAS £14 payable to IPC Magazines Ltd., "Practical Wireless" Subscription Department, Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

THE NEW ANTEX TCSU-D

temperature control digital soldering unit

has joined the Antex range

advancing the science of soldering

With the New Antex TCSU-D High-Value high-performance unit. Its simple design incorporates an LED display and a unique ULA integrated circuit.

Tight temperature control can be maintained by setting the station — then removing the knob, preventing any further alteration, for laboratory, for workshop, for production-line. Joins the most sophisticated range of soldering equipment. Irons, bit, kits, stands, units and accessories — each at the fore front of soldering technology. It's just one more advance from Antex.

For the very latest in the science of soldering send for a catalogue now.

Please send literature and price list to: Made in England.

Name _____ Our products are

Address _____ widely distributed by

_____ wholesalers and

_____ retailers throughout


Telephone _____ the U.K. Please try

_____ your local dealer.

Excluding V.A.T. (15%) and PW1

Postage & Packing

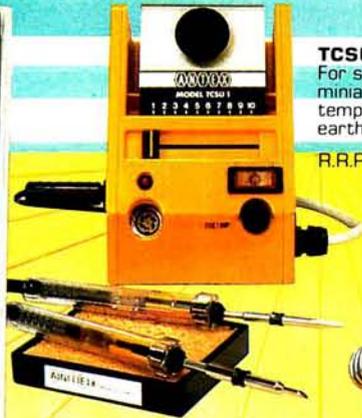and keep up to date with the science of soldering from ANTEX




TCSU1 Soldering Station
For safe 24 volt temperature-controlled miniature soldering iron, variable tip temperature 65-430°C, antistatic earth connection, with XSTC or CSTC iron.

R.R.P. £55.00


ST4 Stand
R.R.P. £1.75



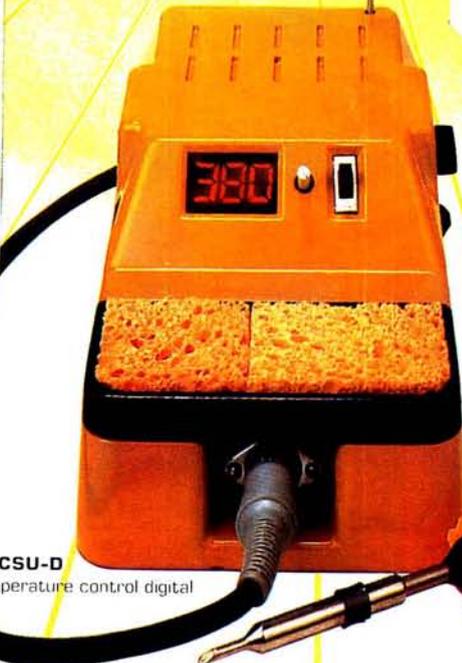Model C
— 15 Watts
Stainless steel shaft only,
240 and 115 volts
R.R.P. £5.20
50 and 24 volts
R.R.P. £5.40



TCSU-D
temperature control digital

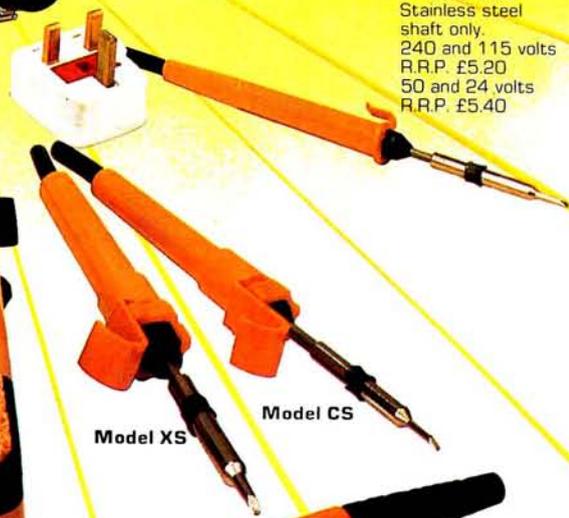

Model XS

Model CS

Model XS
— 25 Watts
Available for 240 and 115 volts
R.R.P. £5.40
50, 24 and 12 volts
R.R.P. £5.60

Model XS-BP
— 25 Watts
Fitted with safety plug 240 volts
R.R.P. £6.20

Model CS
— 17 Watts
Available for 240 and 115 volts
R.R.P. £5.20
50, 24 and 12 volts
R.R.P. £5.40

Model CS-BP
— 17 Watts
Fitted with safety plug 240 volts
R.R.P. £6.00

SK5 Soldering Kit
Contains model CS230 iron and the ST4 stand
R.R.P. £7.00

SK6 Soldering Kit
Contains model XS230 iron and the ST4 stand
R.R.P. £7.25

SK5-BP and SK6-BP Soldering Kits
Fitted with safety plugs.
SK5-BP kit R.R.P. £7.80
SK6-BP kit R.R.P. £8.00

TCSU-D temperature control digital soldering unit.
● Temperature range — ambient to 495°C. ● Bit temperature maintained to ± 5°C. ● Zero crossing switching ● Detachable sponge-tray and includes the world-famous ANTEX Iron. R.R.P. £67.50



ANTEX (Electronics) Ltd.,

Mayflower House, Plymouth, Devon. Telephone: 0752 667377 Telex: 45296

THE NEW MAPLIN CATALOGUE FOR 84!

NOW WITH PRICES ON THE PAGE


More data, more circuits, more pictures, in the brand new 480 page Maplin catalogue. Take a look at the completely revised Semiconductor section or the new Heathkit section with descriptions and pictures of dozens of kits and educational products from digital clocks to 16-bit business computers. The much expanded computer section itself, gives details of hundreds of pieces of software for Atari, BBC, Commodore 64, Dragon, Spectrum and VIC20. In addition to all this you'll find hundreds of fascinating new items spread through the rest of the catalogue.

As always, the Maplin catalogue is tremendous value for money and now has prices on the page!


Pick up a copy at any branch of W.H. Smith or in one of our shops for just £1.35 or send £1.65 including postage to our Rayleigh address. On sale from 1st Nov 1983.

PROJECTS FOR THE HOME CONSTRUCTOR

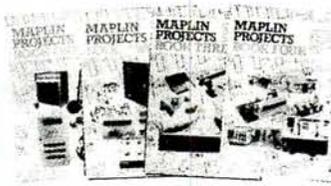Choose from our huge range of value-for-money projects. Projects like our Modem, Mosfet Stereo Amplifier, Home Security System, Frequency Counter and Home Computer add-on kits.



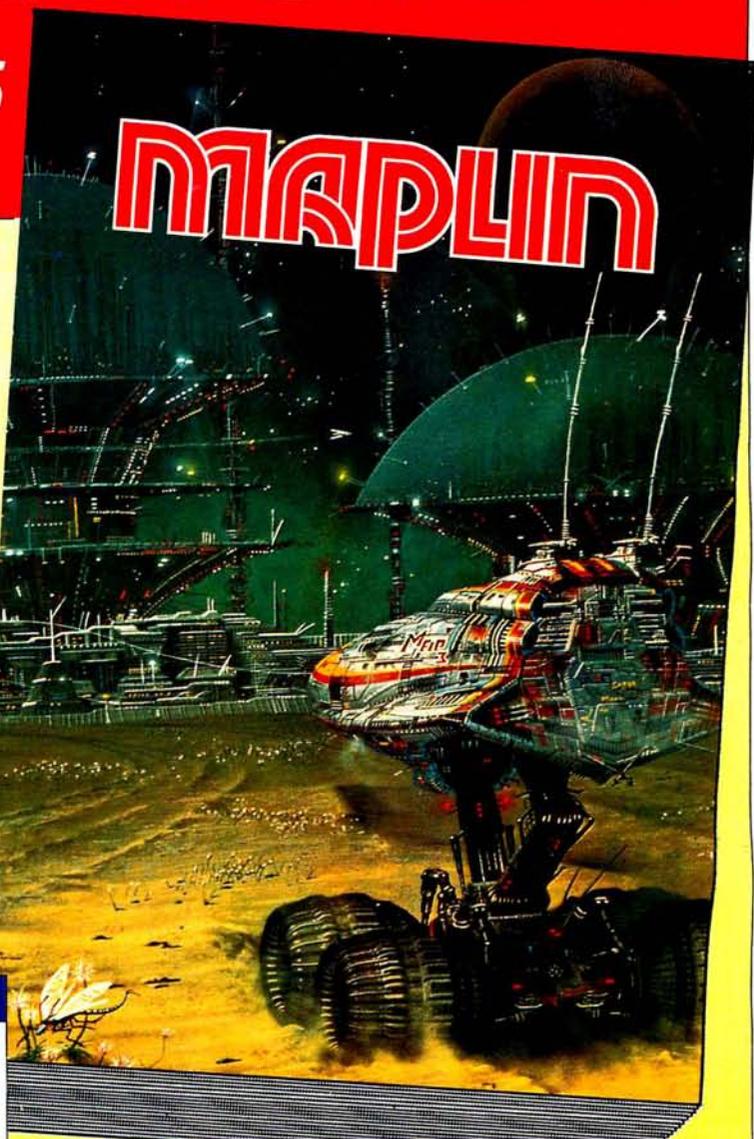Full construction details in our Project Books and brief specifications in our new catalogue. Dozens of fascinating new projects coming soon including a Keyboard for the ZX Spectrum with electronics to make all shifts, single-key operations. Full details in Project Book 9 on sale 11th November 1983. Order As XA09K. Price 70p.



MAPLIN

NEW MAPLIN STORE IN SOUTHAMPTON

Opening on 1st November 1983, our new south coast store is at 46-48 Bevois Valley Road, Southampton (Tel: 0703 25831). You will find our full range of components, projects and computers on sale. We are within easy reach of the city centre with good parking close by. Call in and see us soon.



Post this coupon now for your copy of the 1984 catalogue. Price £1.35 + 30p post and packing. If you live outside the U.K. send £2.20 or 11 International Reply Coupons. I enclose £1.65.

Name

Address

PW1/84

MAPLIN ELECTRONIC SUPPLIES LTD

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 ● Shops at: 159-161 King Street, Hammersmith, London W6. Tel: 01-748-0926 ● 8 Oxford Road, Manchester. Tel: 061-236-0281 ● Lynton Square, Perry Barr, Birmingham. Tel: 021-356-7292 ● 282-284 London Road, Westcliff-on-Sea Essex. Tel: 0702 554000 ● *46-48 Bevois Valley Road, Southampton. Tel: 0703 25831.
*Opens 1st November 1983. All shops closed Mondays. All prices include VAT and carriage. Please add 50p handling charge to orders under £5 total value (except catalogue).

Despatch by return of post where goods available