

HI-SPEC FROM HIGHTECH



Have you ever been in the situation of working rare DX when a short skip signal comes in on the back of your beam and wipes out your QSO? Most beam antennae commonly available today rarely better an F:B ratio of 30dBd. With the **MBFr80** an F:B ratio of 43dBd is easily attainable. **MBFr80** is not a traditional parasitic array but uses absorption techniques to achieve this 'quantum leap' in performance. Over 3 years of research work has been put into development of this type of antenna and extensive proving trials have shown us that in many cases the quoted specifications will be exceeded.

MBFr80 presents an input impedance of 50Ω (unbalanced) yet does not require a conventional balun due to methods of capacitive coupling used within the driven elements.

Due to the use of linear frequency decoupling conventional traps (i.e. coil and capacitor) are not required, hence reducing losses to a very low level. This means that **MBFr80** can sustain a maximum power input of 2kW (100% duty cycle) and 5kW peak at reduced duty cycles.

Unlike conventional 'trapped' antennae, this array has a much greater bandwidth. The plots above speak for themselves — solid state transmitters do not normally require an ATU with **MBFr80**. A conventional three element tri-band beam often has as many as 12 separate traps, leading to excessive losses, narrow bandwidth and limited power handling capabilities.

Using aircraft grade (fatigue tested) aluminium and high quality poltruded GRP, our antennae exhibit extreme durability, corrosion resistance and strength.

The **MBFr80** is exceptional value for money at £189.95 inc. VAT and P&P and is expandable through upgrade kits which will shortly become available for 2M (interlace) and HF (extra parasitic element). For users who demand maximum performance on a restricted budget, **MBFr80** only requires a lightweight mount and with careful siting may be used on a chimney mount without significant deoradation in performance.

TECHNICAL SPECIFICATIONS

| Input impedance | 50 Ω (unbalanced) |
|-----------------------------|--|
| Max. power input | 2kW (100% duty cycle) 5kW peak (reduced duty) |
| Forward gain | Better than 4.5dBd |
| F:B ratio | Better than 43dBd |
| Max. boom length | 4m |
| Max. element length | 2.3m |
| Boom diameter | 40mm |
| Turning circle | 3m |
| Netweight | 8kg |
| Max. wind survival velocity | 100mph |

HIGHTECH

 Antennae (Scotland) Ltd.

 To: HTA (Scotland) Ltd., 24 Gremista Ind. Est., Lerwick, Shetland Is. ZE2 OPX

 Please Supply
 MBFr80 Antenna(e)

 @ £189.95 incl. VAT & P & P

 Name (please print)
 @

 Address (please print)
 Postcode

 I enclose a cheque/PO payable to HTA (Scotland) Ltd value £
 P

 or debit my Access Card No.
 P

 Cardholder Signature
 Cardholder Signature

 Credit Card Hotline 0595 - 5949
 Pease allow 28 days for delivery. Offer valid UK only

FOR THE Radio ENTHUSIAST ...

Free with this issue, Computing in Radio magazine

NOVEMBER 1984 **VOL. 60**

NO. 11 ontents

ISSUE 932

The September 10 Schedule Revision 18

24 Introduction to Antennas—3 Gordon J. King G4VFV

actical

- 28 **Kindly Note** Simple Top-Band Receiver—June 1984
- 31 **Battery State Indicator** J. P. Talbot G4AYV
- Modifying the FRG-7—3 36 Peter D. Rouse GU1DKD
- PW "Teme" Modular Transceiver—1 40 Rev. G. C. Dobbs G3RJV
- Stable Toneburst 48 D. I. Shaw G8ESN
- PW QRP Contest Results 50 Neill Taylor G4HLX
- **Multiple Choice** 54 Practice Questions for the RAE

We are sorry that Part 5 of Practical LC Filter Design has had to be held over to make space for details of the new licence schedule



- 79 Advert Index
- 21 Benny
- 17 Comment 22 News
- 33 Next Month 55 On the Air 34 Products

Services

17

39.46.49 47 Uncle Ed

Swap Spot

EDITORIAL OFFICES Practical Wireless Westover House West Quay Road Poole, Dorset BH15 1JG

Geoff Arnold T.Eng(CEI) G3GSR Editor

Dick Ganderton C.Eng., MIERE, **G8VFH** Assistant Editor

Steve Hunt Art Editor

C Poole 671191

John Fell G8MCP **Technical Editor**

Alan Martin G8ZPW **News & Production Editor**

Elaine Howard G4LFM **Technical Sub-Editor**

Rob Mackie Technical Artist

Kathy Moore Secretary

ADVERTISEMENT OFFICES

Practical Wireless King's Reach Tower Stamford Street London SE1 9LS Telex: 915748 MAGDIV-G

Dennis Brough Advertisement Manager \$ 01-261 6636 \$ 01-261 6872

Roger Hall G4TNT (Sam) Ad. Sales Executive \$ 01-261 6807

Claire Gerrish Secretary € 01-261 6636

Barbara Blake Classified Supervisor \$ 01-261 5897

Ian Sweeney Make-up & Copy \$ 01-261 6570

COPYRIGHT © IPC Magazines Limited 1984 Copyright in all drawings, photographs and articles published in Practical Wireless is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by Practical Wireless to ensure that the advice and data given to our readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

LOWE SHOPS

Whenever you enter a LOWE ELECTRONICS' shop, be it Glasgow, Darlington, Cambridge, Cardiff, London or here at Matlock, then you can be certain that, along with a courteous welcome, you will receive straightforward advice. Advice given, not with the intention of "making" a sale, but the sort which is given freely by one radio amateur to another. Of course, if you decide to purchase then you have the knowledge that LOWE ELECTRONICS are the company that see the standard for amateur radio after-sales service. The shops are open Tuesday to Saturday and close for lunch 12.30 till 1.30pm.

In Glasgow the LOWE ELECTRONICS' shop (tele-phone 041-945 2626) is managed by Sim GM3SAN. Its address is 4/5 Queen Margaret's Road, off Queen Margaret's Drive. That's the right turn off Great Western Road at the Botanical Gardens' traffic lights. Street parking is available outside the shop and afterwards the Botanical gardens are well worth a visit . .

In the North East the LOWE ELECTRONICS' shop is found in the delightful market town of Darling-ton (telephone 0325 486121) and is managed by Don G3GEA. The shop's address is 56 North Road, Darlington. That is on the A167 Durham road out of town. A huge free car park across the road, a large supermarket and bistro restaurant combine to make a visit to Darlington a pleasure for the whole family.

Cambridge, not only a University town but the location of a LOWE ELECTRONICS' shop managed by Tony G4NBS. The address is 162 High Street, Chesterton, Cambridge (telephone 0223 311230). From the A45 just to the north of Cambridge turn off into the town on the A1039, past the science park and turn left at the first roundabout. After passing a children's playground on your left turn left again into High Street. Easy and free street parking is available outside the shop.

Cardiff now has its own LOWE ELECTRONICS' shop. Managed by Richard GW4NAD, who hails from Penarth, the shop (our telephone number is 0222 464154) is located within the premises (on the first floor) of South Wales Carpets, Clifton Street, Cardiff. Clifton Street is easily found, being a left turn off Newport Road just before the infirmary. Once in Clifton Street, South Wales Carpets is the modern brick building at the end of the street on the right hand side. Enter the shop, follow the arrows past the carpets, up the stairs and the "Emporium" awaits you. Free street parking is available outside the shop.

MOVING . . . MOVING . . . MOVING . . From the 13th September 1984 the LOWE ELECTRONICS' London shop will be located at 223/225 Field End Road, Eastcote, Middlesex (the new telephone number is 01-429 3256). The new shop, managed by Andy G4DHQ is easily found, being part of Eastcote tube station buildings. Immediately behind the shop is a large car park where you can currently park for the day for 20p. There is also free street parking outside the shop.

Finally, here in Matlock, David G4KFN is in charge. Located in an area of scenic beauty a visit to the shop can combine amateur radio with an outing for the whole family. May I suggest a meal in one of the town's inexpensive restaurants or a picnic on the hill tops followed by a spell of portable operation.

I have been using the TRIO TS711E VHF 2 metre base station for some time now. The transceiver has, as standard, a digital code squelch facility which when used in conjunction with our other TS711E operated by my colleague David, G4KFN, has proved most useful.

It was with considerable interest, therefore, that I greeted the news that TRIO were going to introduce a higher specification version of the current TR2500 that would incorporate this new call facility. As the TS711E can also be programmed to send your callsign digitally at the beginning and end of each transmission, I wondered whether TRIO would include this useful facility on the new rig.

The answer is yes! The new TR2600E has digital code squelch and will also send your callsign automatically. The digital code squelch and callsign ability are not the only new features to be incorporated into the new TS2600E. Each memory will store both frequency and whether or not the rig was set with simplex or repeater shift: Most useful on today's FM scene when a contact made by repeater quickly becomes a simplex one. Two modes of memory scan are available, the rig looking for either a clear or a busy frequency. Having locked on a signal, scanning resumes after a timed period or when the carrier drops (in open channel scan, when a carrier appears). Programmable scan is as the TR2500, lower and upper scan limits are entered into memories 8 and 9, any multiple of 5 kHz (10, 15, 20, 25 kHz) being programmable. The TR2600E also has a priority channel and



the ability to omit selected channels from the scan pattern. Anyone who has used a TR2500 will know that occasionally one or two fre-quencies entered in memory become superfluous. To remove these frequencies without removing everything would be most useful. A definite advantage is that the time taken for memory scan is shortened. The new higher specification TR2600E has this facility. The

TR-3600E frequency readout is improved, the full 145.500 digits being displayed and to stop the operator having to continually give 5 by 9 reports the TR2600E has an S meter as part of the top panel which doubles as a battery state indicator.

For the UHF enthusiast there is also a 70 centimetre version of the TR2600E, the TR3600E.

Until now, the TRIO TR2500 and TR3500 were "the" hand held transceivers for 2 meters and 70 centimetres - the TR2600E and the TR3600E, with their higher specification, provide the only alternative. TR2600F

| THEOUL | with DCS | £269.88 inc VAT. carr £6.00 |
|---------|------------------------------------|-----------------------------|
| TR3600E | 70 centimetre handheld with DCS | |
| BC2 | AC Charger | |
| DC26 | DC/DC converter | £19.47 inc VAT. carr £1.00 |
| EB3 | External battery case | £14.45 inc VAT. carr £0.75 |
| HMC1 | Headset with VOX | £25.00 inc VAT. carr £1.00 |
| PB26 | Nicad battery pack | £30.50 inc VAT. carr £1.00 |
| SC9 | Soft case | £18.50 inc VAT. carr £0.75 |
| SMC30 | | £21.58 inc VAT. carr £1.00 |

SN In trying to describe the new 2 metre FM transceiver from TRIO, I am faced with a major difficulty. The TH21E is small, 2.24 inches wide, 4.72 inches high and only 1.1 inches deep but size alone is not the rig's fascination. Only by holding the transceiver can one begin to appreciate the attention that has been place on its ergonomics. The way in which the **TRIO TH21E**, once picked up, seems impossible to put down. Its ability to slip into the inside pocket and for you to forget you have it. So far no one who has seen a TH21E has been able to resist picking it up, it's as simple as that.

There is also a 70 centimetre version of the TH21E available, the TH41E.

Operating the TH21E could not be easier. Thumbwheel switches being used to set the frequency, the last digit being set by a simple top panel switch. Power output is 1 watt (HI) and 150 milliwatts (LOW). I have used the rig over the past few days and have been really amazed at the distance that can be covered on 1 watt. Both transceivers have repeater shift, the tone burst switch is on the top panel. Microphone and earphone sockets are also located on the top panel enabling both the conventional speaker/microphone and the NEW TRIO HMC1 headset to be used. A clever



feature of the headset is that it has, incorporated in its connecting cable, a minute vox unit. The transceiver comes complete with aerial, nicad battery pack and charger.





I am pleased that I can claim one of the rigs to use at home prior to writing the advertising and let the rest of the company fall out about who is having the other one. Never before can I remember two handhelds that have had such fascination.

| TH21E | 2 metre transceiver | £175.00 | inc VAT. carr £6.00 |
|-------|-----------------------|---------|---------------------|
| 1H41E | 70 centimetre version | £198.00 | inc VAT. carr £6.00 |
| SMC30 | speaker/microphone | £21.50 | inc VAT. carr £1.00 |
| HMC1 | headset with VOX | £25.00 | inc VAT. carr £1.00 |
| DC21 | DC power supply | £18.98 | inc VAT. carr £1.00 |
| PB21 | Nicad battery pack | | |
| BT2 | Dry battery case | £9.00 | inc VAT. carr £0.75 |
| SC8 | Soft case | | |
| EB2 | External battery case | £14.58 | inc VAT. carr £1.00 |

Ever since the demise of the TRIO 700 series of equipment, we, here at LOWE ELECTRONICS have been campaigning for the introduction of a new "true base station" transceiver. Those who have used a TRIO TS700S or G will know what I mean. There is that certain feel which a base station transceiver has which the mobile or portable rig, when taken out of the car or used in the shack, definitely has not. I am pleased to say that TRIO have introduced a new 2 metre base station, it is called the **TS711E**. I have been fortunate enough to have used the transceiver over the past couple of weeks and again I am lost for words. Certainly there will be a TRIO **TS711E** in my shack, I have even prepared a space for it!

Having used the rig let me explain some of its features. In size, weight and appearance the **TS711E** is similar to the TS430S HF transceiver but unlike the TS430S it has its own internal power supply. It also has an inbuilt speech processor and IF shift, both ideal features for today's active 2 metre band. Power output is 25 watts but the rig I have been using produces 32. Typical TRIO! The **TS711E** has two VFOs and, wait for it, forty memory channels. Yes, I too wondered how one could use so many memories.

Initially I started to use the rig as I had my dual band TRIO TS780. One VFO left on 144.300 and the other on 145.500. Since the rig remembers both frequency and mode there was no problem operating SSB on one VFO and with the electronic click step engaged, FM on the other. Electronic click step? ... the **TS711E** has been designed so that as a multi-mode rig you can have a free running VFO on SSB and CW and when operating FM, a VFO with 5 or 12.5 kHz click steps. I refer to the click step as electronic because a touch switch instantly changes the VFO function. Of course, I need not tell you that the memories remember which VFO operation has been selected or for that matter whether repeater shift was required. On SSB and CW the **TS711E's** synthesized VFO tunes in 10 Hz steps.

After using the rig for some time without the 40 memories I concluded that since it was possible to move a frequency from memory to VFO it would make sense to program the memories logically and then use them as a basis for operating. Result, the rig is a dream to use. With the **TS711E's** memory carrying a sequence of calling channels, beacon, simplex and repeater frequencies a swift rotation of the VFO (which also serves to change memory channels) and the entire band can be looked at in seconds. To check on OSCAR 10, dial up the correct memory holding say the satellite beacon frequency, if that's audible then move the beacon frequency to the VFO by pushing the appropriate switch and there you are, tuning the correct part of the band, in the right mode and with the VFO running free. The same can be applied to the CW end of the band and with the VFO set to click stop, FM channels also.

There are facilities to put both VFOs on the same frequency, to operate split using one VFO for receive and the other for transmit. A priority call channel is available as is the ability to go back to a predetermined frequency. The **TS711E** will scan the band or the memories holding for a brief period on an occupied frequency. It will also scan the memories looking at only those frequencies entered in a particular mode. Programmable scan is also included, memory channels 39 and 40 setting the limits. The now standard full repeater facilities are included.

For the blind operator the **TS711E** is a dream come true. Full voice announcement of frequency and whether the rig is set to repeater shift comes by fitting the optional VS1 board. A push button, conveniently located on the bottom corner of the front panel, activates the voice. The careful location of this control shows TRIO's attention to detail. How difficult would the switch have been to find for the blind operator had it been located in the middle of the panel. Mode of operation is indicated by switches which when pushed instead of a general beeping, send the morse code letter F for FM, U for USB, C for CW, L for LSB and A for auto. Auto, what's auto?... With auto switched on, as you tune across the band the **TS711E** selects the correct mode for the appropriate frequency. You can over-ride this function and as I have said elsewhere, you too can transmit FM on the SSB part of the band.

Enough I hear you say. Sorry, one more feature. DIGITAL CODE SQUELCH! The transceiver has as standard an inbuilt selective tone call system incorporating a call alarm. So if you are not in the shack then you will know you have been called. The transceiver will also send up to 6 letters or numbers as part of the selective call. I am sure it will not be long before TRIO introduce a **TS711E** accessory (I am told it is called the CD-10 call sign display) which will decode the information. Then will you not only know that you have been called but who has called you, the 6 letters or digits making up the callsign.

What more can I say, what a rig! For the operator who wants the finest two metre base station transceiver TRIO have produced the TS711E. For the UHF operator there is the TRIO TS811E, the 70 centimetre version. Both ideal ways of getting on to the VHF/UHF bands.

TS711E 2 metre base station

transceiver with DCS £758.00 inc VAT. carr £6.00 TS811E 70 centimetre base

station transceiver with DCS . £878.00 inc VAT. carr £6.00 CD10 Callsign display unit£105.40 inc VAT. carr £6.00 SP430 Matching speaker£30.99 inc VAT. carr £2.50



The new DCS system has also been applied to the popular compact mobiles, the TM201A and TM401A. The NEW transceivers are the TM211E for two metres and for 70 centimetres, the TM411E. The two rigs also have front panels whose viewing angle can be adjusted. So what was an easy to accommodate rig becomes much more so. The tight space which would accommodate a rig but where you could not see its front panel is a thing of the past. Add the convenience of a digital code squelch system, 25 watts output on the 70 centimetre TM411E and the two new rigs from TRIO provide the only alternatives to the TR201A and TR401A.

TM211E Mobile 2 metre transceiver £360.00 inc VAT. carr £6.00 TM411E Mobile 70 centimetre













The R70 covers all modes (when the FM option is included), and uses 2CPU-driven VFOs for split frequency working, and has 3 IF frequencies. 70MHz, 9MHz and 455KHz, and a 100dB dynamic range. It has a built-in mains supply. Other features include input switchability through a pre-amplifier, direct or via an attenuator, selectable tuning steps of 1KHz, 100Hz or 10Hz, adjustable IF bandwidth in 3 steps (455KHz). Noise limiter, switchable AGC, tunable notch filter, squelch on all modes, RIT, tone control. Tuning LED for FM (discriminator centre indicator). Recorder output, dimmer control.

15.710.0



The R-70 also has separate antenna sockets for LW-MW with automatic switching, and a large, front-mounted loudspeaker with 5.8W output. The frequency stability for the 1st hour is \pm 50Hz, sensitivity – SSB/CW/RTTY better than 0.32 uv for 12dB (S + N) \div N, Am – 0.5 uv. FM better than 0.32 for 12dB Sinad. DC is optional.

Ever since its introduction the IC-R70 has proved to be a popular and reliable HF receiver making your listening hours a pleasure. Please contact us for further details on this excellent set.



For those who like the easy life, the R71E has the option of an infra-red remote control unit, making it a very sophisticated rig indeed, here are some details.

100 KHz – 30 MHz all mode (with FM option). Quadruple conversion superhet. IF frequencies 70MHz,9MHz and 455KHz with continuous bandpass tuning and notch filter. Virtually immune from adjacent channel interference with 100db dynamic range. Adjustable AGC, noise blanker and switchable pre-amplifier. Direct keyboard into twin VFO's with 32 programmable memories. 5 year lithium memory backup cell. Memory and band scan with auto-stop. Tuning rates 10Hz, 50Hz and 1 KHz with 6 digit readout. AC mains operation. Auto squelch tape record function.

OPTIONS:- Synthesized voice readout, infra-red remote controller, 12 V DC kit, mobile mounting bracket, two CW filters 500 and 250 Hz, FM unit, computer interface, headphones.

You can get what you want just by picking up the telephone. Our mail-order dept. offers you: free, same-day despatch whenever possible, instal . credit, interest-free H.P., telephone Barclaycard and Access facility and a 24 hour answering service. Please note that we now have a new retail branch at 95, Mortimer Street, Herne Bay, Kent. Give it a visit, BCNU.



Practical Wireless, November 1984

ICOM TONO COMPUTERS

Tono 5000E, £829.

From the famous TONO stable comes the new THETA – 5000E now ready to send and receive AMTOR as well as CW, RTTY, and ASCII.

Features include:- 5" high resolution monitor displaying 400chr. x 16 lines x 2 pages, ARQ/FEC, time clock, Selcal (Selective calling), high speed RTTY demodulator – up to 300 bauds (600 baud using TTL level); 3 shifts (170,425 and 850 Hz) and two tones (2125 and 1275 Hz); manual or automatic Tx/Rx; Battery back-up memory (72 chars x 7 channels and 24 chars x 5 channels); type ahead correctable buffer memory; Morse code 5 – 100 wpm (variable weights) + autotrack on receive; CW practice feature with random generator; Automatic CR/LF with wrap around display; Automatic letters code insertion; Printer interface; Bargraph LED meter for tuning; TOR A, B and L – the list goes on and on..... Power requirements by the way are AC mains or 13.8v DC.





Please note that we now have a new retail branch at 95, Mortimer Street, Herne Bay, Kent. Give it a visit, BCNU.

Fono 9100E, £729.

The famous TONO THETA 9000E has had AMTOR modes A, B and L added to its functions providing transmit and receive facilities with selective calling on AMTOR, RTTY (with 3 selective shifts and 2 tone pairs), CW with built in practice function and random generator, and ASCII with full Duplex facility. The 9000E requires an external VDU. The battery backed memory covers 256 characters x 7 channels with Channel 6 which is divided into 16 subsections of 16 characters each and Channel 7 into 8 subsections of 32 characters. Any of the subsections may be used individually and messages can be repeated 1 – 9 times from a keyboard command.

Agent: Gordon G3LEQ, or telephone Knutsford (0565) 4040. Please telephone first, anytime between 0900 – 2200 hrs.





LEICESTER SHOW S

Bernie – At these prices you may have made a few boobs!

SUPERB 2 METRE BASE STATION



ICOM IC271E

2m base station for the eighties, 25w O/P, 32 memories, scanning, 10/100Hz auto shift tuning rates + (as options) voice frequency synthesiser, internal 12V psu, GaAS FET preamp.

£629 WITH **ICSM6 ELECTRET BASE STATION MIC** 0R

AG20 INTERNAL **GaAS FET ICOM** PREAMP

HOW LOW CAN WE GO!



YAESU FT790R Portable microprocessor controlled UHF 70cm multimode. Fast becoming as popular as its 2m brother the FT290R-the FT790R has the same major features. Power output is 1 watt, but includes a speech processor.

£249 INC. NICADS AND CHARGER

RCLAYCARD + WRITTEN DETAILS ON REQUEST

PRICES CORRECT AT TIME OF GOING TO PRESS ALL OFFERS SUBJECT TO AVAILABILITY

VISA

PERFECT TIMING



ICOM ICR71

The latest superior grade receiver, with keyboard entry, 32 tunable memories, three rates of tuning + (as options) infra red remote, F.M., voice frequency synthesiser, additional filters.

£625 WITH AT 1000 **AERIAL TUNING UNIT**

REACH FOR THE SKY & CATCH A SATELLITE



YAESU FT726R Multiband base station transceiver. Just compare the following features:

£739 INCL MUTEK PRE-AMP

| FEATURES | FT 726R | TS780 |
|--------------------|-----------|--------|
| Choice of bands | yes | no |
| 450 MHz capability | yes | no |
| IF Shift | yes | yes |
| IF Width | yes | no |
| CW Filter | option | no |
| X-band Full Duplex | option | no |
| Squeich | all modes | FMonly |
| Memory Channels | 11 | 10 |

| FEATURES | FT 726R | TS780 |
|-------------------|------------|---------|
| Limited Band Scan | yes | yes |
| Mode Memory | yes | no |
| Memory Backup | lithium | AA cell |
| RX Tone Control | yes | no |
| RF PWR Control | continuous | Hi/Low |
| Speech Processor | AF | none |
| VOX | no | yes |
| CW Semi break-in | yes | yes |

EXTRA-SPECIAL OFFER FT726R WITH 70cm CARD FITTED £1,053 - WITH DUPLEXER/SATELLITE MODULE WORTH £100!

ALL PRICES INCLUDE V.A.T.





| Provide • FACTORY APPOINTED IMPORTER • FREE SECURICOR DELIVERY ON ALL MAJOR ITEMS • FACTORY APPOINTED IMPORTER • FACTORY APPOINTED IMPORTER • FAUL • HE ransceiver with gencoverage RX • Second and the second appoint of the second appoint appoint appoint appoint appoint appoint appoint appoint appoint | • | AKD • | BNOS . DATONG . MUT | EK 🔹 | MICROWAN | /E MODULES • TONNA | HÍ MOUND |
|---|----------|--|--|--------|-------------------|---|----------------|
| VACESU Standard charger (FNB-3) 9:20 FMU.11 DC lad MH-102AB Standard charger (FNB-3) 9:20 FMU.11 DC lad MH-102AB Standard charger (FNB-3) 9:20 FMU.11 DC lad MH-102AB Mubile mount 5:00 Kufnon Crists Kayer 1:20 Codaptor 1:600 Kufnon Crists Kayer 1:935 FNB-3 1:0-8V bitst pack 3:350 XF-8 9KC CW filter (500 Hz) anrow 1:935 FNB-4 1:2V bitst pack 3:350 YF-7600 HF transceiver with gen coverage RX 1:22:00 FT-2308 maynth handia thumbwheel tuning + FNB-3 1:760 FF-800 External spaster with audio filter 6:560 FT-2308 maynth handia thumbwheel tuning + FNB-3 1:500 FF-800 Computer interface Apple I 1:560 FT-2308 maynth handia thumbwheel tuning + FNB-3 1:500 FF-800 Computer interface Apple I 1:560 FT-2308 maynth handia thumbwheel tuning + FNB-3 1:570 FF-800 Computer interface Apple I <td< th=""><th></th><th>Access</th><th></th><th></th><th>CAUTHORISED -</th><th></th><th></th></td<> | | Access | | | CAUTHORISED - | | |
| VACESU Standard charger (FNB-3) 9:20 FMU.11 DC lad MH-102AB Standard charger (FNB-3) 9:20 FMU.11 DC lad MH-102AB Standard charger (FNB-3) 9:20 FMU.11 DC lad MH-102AB Mubile mount 5:00 Kufnon Crists Kayer 1:20 Codaptor 1:600 Kufnon Crists Kayer 1:935 FNB-3 1:0-8V bitst pack 3:350 XF-8 9KC CW filter (500 Hz) anrow 1:935 FNB-4 1:2V bitst pack 3:350 YF-7600 HF transceiver with gen coverage RX 1:22:00 FT-2308 maynth handia thumbwheel tuning + FNB-3 1:760 FF-800 External spaster with audio filter 6:560 FT-2308 maynth handia thumbwheel tuning + FNB-3 1:500 FF-800 Computer interface Apple I 1:560 FT-2308 maynth handia thumbwheel tuning + FNB-3 1:500 FF-800 Computer interface Apple I 1:560 FT-2308 maynth handia thumbwheel tuning + FNB-3 1:570 FF-800 Computer interface Apple I <td< th=""><th>μ.</th><th></th><th>• FACTORY APPOINTED IMP</th><th>ORTER</th><th></th><th></th><th>A 4</th></td<> | μ. | | • FACTORY APPOINTED IMP | ORTER | | | A 4 |
| VACESU Standard charger (FNB-3) 9:20 FMU.11 DC lead 10:89:00 NC-3C Standard charger (FNB-3) 9:20 FMU.11 DC lead 10:89 NM-12/28 Standard charger (FNB-3) 9:20 FMU.11 DC lead NE-40 10:89 NM-12/28 Standard charger (FNB-3) 9:20 FMU.12 DC lead NE-40 10:89 NM-12/28 Standard charger (FNB-3) 9:20 FMU.12 DC lead NM-12/28 Standard charger (FNB-3) 9:20 16:40 Kufnom Crist Keyr 19:35 FNB-4 12:Vastrpack 33:50 YK-9 SKC CW filter (600 Hz) 17:46 FR-203R 2m synth handia thumbwheel tuning + FNB-3 17:60 FFF-800 HF transceiver with gen coverage RX FC-203R Tm synth handia thumbwheel tuning + FNB-3 17:60 FFF-800 Computer interface Apple I 3:60 NC-11C Charger (FF-203R) Accessories as for FF-203R) Acces | | | | | | | |
| VACESU Standard charger (FNB-3) 9:20 FMU.11 DC lead 10:89:00 NC-3C Standard charger (FNB-3) 9:20 FMU.11 DC lead 10:89 NM-12/28 Standard charger (FNB-3) 9:20 FMU.11 DC lead NE-40 10:89 NM-12/28 Standard charger (FNB-3) 9:20 FMU.12 DC lead NE-40 10:89 NM-12/28 Standard charger (FNB-3) 9:20 FMU.12 DC lead NM-12/28 Standard charger (FNB-3) 9:20 16:40 Kufnom Crist Keyr 19:35 FNB-4 12:Vastrpack 33:50 YK-9 SKC CW filter (600 Hz) 17:46 FR-203R 2m synth handia thumbwheel tuning + FNB-3 17:60 FFF-800 HF transceiver with gen coverage RX FC-203R Tm synth handia thumbwheel tuning + FNB-3 17:60 FFF-800 Computer interface Apple I 3:60 NC-11C Charger (FF-203R) Accessories as for FF-203R) Acces | 1 | Contraction of the local division of the loc | | | VAESI | | |
| FT.AB. HF transceiver with gen coverage RX TSB00 Standard charger (FNB-3) 9 20 DCL-1 DCLead 1044 MMB-21 Formation 1748 DCL-1 DCLead 1044 MMB-21 Headset tric 1449 Kuthon Curis Kaye 2850 Formation 1449 Formation 1449 Kuthon Curis Kaye 2850 Formation 1449 Formation 1449 XFL 07XC CWFISK (800Hz) Trad 1740 Formation 1850 YFL 07XC CWFISK (800Hz) Trad 1740 FFA3 277 Formation 187 YFL 07XC CWFISK (800Hz) Trad FFA3 277 Formation 187 | | VISA | ALL MAJOR ITEMS | | | | |
| Prove HF transceiver with gen coverage RX 156-90 NC-3C Standard charger (FNB-3) 9-20 PMU-1 DC La DC lead MM-1022B Spkrmic 17-69 RAM.B Non-volatil MEM 14-69 MM-122B Mobile mount 800 RAM.B Non-volatil MEM 14-69 MM-122B Mobile mount 800 RAM.B Non-volatil MEM 14-69 MM-122B Mobile mount 800 XF-8 9RC. CW filter (300 kl) anrow 1935 FN8-4 12V batt pack 3825 XF-8 9RC. CW filter (300 kl) anrow 1746 FR-50 Batt case for AA dry cell 655 SP-80 Computer interface Abole 1 15200 FT-303R maynth hardin thumbwheel luning + FN8-1 17400 RF-230C Computer interface Abole 1 15400 MM-11 Mobile mount 28900 FF-6 Computer interface Abole 1 25400 FT-303R Fmaynth andia thumbwheel luning + FN8-1 15400 FF-80 Computer interface Abole 1 25400 Mobile mount 28900 | • | | | VAR | | | |
| Product FMU-1 < | | | | | | | 0.00 |
| • xF - BirCk, CW Tiller (300 Hz) arrow 19:35 FIN-4 12/bat pack 38:25 • XF - 10:7K, CW FSK (300 Hz) 17:49 FRA-5 FF-303R Zm synth handle thumbwheel tuning + FNB-3 17:5:00 • SP 940. External speaker with (cAT system) 129:45 FF-303R Zm synth handle thumbwheel tuning + FNB-3 17:5:00 • SP 940. External speaker with (cAT system) 129:45 FF-303R Zm synth handle thumbwheel tuning + FNB-3 17:5:00 • FF-323C Computer interface Apple I 54:00 FF-737R Alccessories and FF-203PI Alccessories and FF-203PI Alccessories and FF-203PI FF-33 • FF-323C Computer interface Apple I 54:00 NMB-11 25:00 NML-44 Worker helicial antenna 7:00 • FF-35/RC CW filter (ceramic) 45:00 NH-44 Worker helicial antenna 7:00 • FF-75/RC HF ransecure gen coverage all moords 15:00 NH-44 Worker helicial antenna 7:00 • FF-75/RC HF ranse def S-23:2 Signo M-1 | G | | | | | | |
| • xF - 8 - 9KC, CW TSK (SOUH-) 174 bit stresser, CW TSK (SOUH-) 174 bit | | | | | | | |
| • xF - BirCk, CW Tiller (300 Hz) arrow 19:35 FIN-4 12/bat pack 38:25 • XF - 10:7K, CW FSK (300 Hz) 17:49 FRA-5 FF-303R Zm synth handle thumbwheel tuning + FNB-3 17:5:00 • SP 940. External speaker with (cAT system) 129:45 FF-303R Zm synth handle thumbwheel tuning + FNB-3 17:5:00 • SP 940. External speaker with (cAT system) 129:45 FF-303R Zm synth handle thumbwheel tuning + FNB-3 17:5:00 • FF-323C Computer interface Apple I 54:00 FF-737R Alccessories and FF-203PI Alccessories and FF-203PI Alccessories and FF-203PI FF-33 • FF-323C Computer interface Apple I 54:00 NMB-11 25:00 NML-44 Worker helicial antenna 7:00 • FF-35/RC CW filter (ceramic) 45:00 NH-44 Worker helicial antenna 7:00 • FF-75/RC HF ransecure gen coverage all moords 15:00 NH-44 Worker helicial antenna 7:00 • FF-75/RC HF ranse def S-23:2 Signo M-1 | Ĕ | | | | | | 1201212 |
| • xF - BirCk, CW Tiller (300 Hz) arrow 19:35 FIN-4 12/bat pack 38:25 • XF - 10:7K, CW FSK (300 Hz) 17:49 FRA-5 FF-303R Zm synth handle thumbwheel tuning + FNB-3 17:5:00 • SP 940. External speaker with (cAT system) 129:45 FF-303R Zm synth handle thumbwheel tuning + FNB-3 17:5:00 • SP 940. External speaker with (cAT system) 129:45 FF-303R Zm synth handle thumbwheel tuning + FNB-3 17:5:00 • FF-323C Computer interface Apple I 54:00 FF-737R Alccessories and FF-203PI Alccessories and FF-203PI Alccessories and FF-203PI FF-33 • FF-323C Computer interface Apple I 54:00 NMB-11 25:00 NML-44 Worker helicial antenna 7:00 • FF-35/RC CW filter (ceramic) 45:00 NH-44 Worker helicial antenna 7:00 • FF-75/RC HF ransecure gen coverage all moords 15:00 NH-44 Worker helicial antenna 7:00 • FF-75/RC HF ranse def S-23:2 Signo M-1 | 4 | | | | | | 16.00 |
| V 71-07XC CV FSR (800H-H) 17-49 FRA-5 Bart case for 6A dry cell 645 V 71-98C HF transceiver with gen coverage RX FT-203R Zm synth handle thumbwheel tuning + FRA-5 155:00 V 72-98C HF transceiver with gen coverage RX FT-203R Zm synth handle thumbwheel tuning + FRA-5 155:00 V 72-07XC Automatic anterna tune 25:00 FT-203R Zm synth handle thumbwheel tuning + FRA-5 155:00 V 72-07XC Automatic anterna tune 25:00 FT-203R Zm synth handle thumbwheel tuning + FRA-5 155:00 V 74-580HC Computer interface N.E.C. 105:00 NC-11C Charger 10-35 V FA 980HC CW filter (800 H2) 23:50 YR-444 Wave helical anterna 700 V FA 980HC CW filter (800 H2) 23:50 YH-44 Wave helical anterna 17:50 V FA 980HC CW filter (800 H2) 23:50 YH-44 Wave helical anterna 17:50 V FA 980HC CW filter (800 H2) 23:50 YH-44 Wave helical anterna 17:50 V FA 980HC CW filter (800 | | | | 19.35 | FNB-3 | | 33.20 |
| B Fr.980 HF transceiver with gen coverage RX (CAT system) FT.203R Zm synth handle thumbwheel uning + FNB-3 T75 op T75 op T7203R SP -880 External speaker with aufoil filter (F1-203R) T7200R Zm synth handle thumbwheel uning + FNB-3 T55 op T75 op T7203R Zm synth handle thumbwheel uning + FNB-3 T55 op T75 op T700m protein aufoil filter (Accessorise as for FT-203R) Zm synth handle thumbwheel uning + FNB-3 T55 op T75 op T700m protein aufoil filter (Accessorise as for FT-203R) SF 580 Computer interface RS-212 SP 600 FT FT-203R Zm synth handle thumbwheel uning + FNB-3 T55 op T700m protein aufoil filter (Accessorise as for FT-203R) SF 580 Computer interface RS-212 SP 600 FT FT-800 FT-730R | | XF-8-9KCN | CW filter (300 Hz) narrow | | | | |
| FT -980 HF transceiver with gen coverage RX FT -233R Zm synth handle thumbwheel tuning + FNA-3 T75 00 C/C 750 AT Atternal speaker with audio filter 6150 FT -233R Zm synth handle thumbwheel tuning + FNA-5 T55 00 FC -757A Automatic antenna tuner 254 00 Computer interface Apple 1 544 00 FF -252C Computer interface Apple 1 544 00 MCB-1 Mobile mount 239 00 FF -252C Computer interface Apple 1 544 00 MCB-1 Mobile mount 239 00 FF -252R Computer interface Apple 1 545 00 MCB-1 Mobile mount 293 00 FF -257K Computer interface Apple 1 545 00 MCB-1 B52 50 MCB-2 Spk mic 193 55 FF -257K Computer interface Apple 0 FF -303 M Mobile boom mic 184 55 FF -757A Automatic antenna surver 2560 MA-14 Wave helical antenna 700 FF -757A Automatic antenna surver 7450 M MA-14 Masove helical antenna 700 FF -757A Automatic antenna surv | | | | | FBA-5 | Batt case for 6 AA dry cell | 6.82 |
| FIF:232 Computer interface RS-232 S900 FT-790R 70cm portable/mobile/base multimode 259.00 FIF:28 Computer interface RS-232 S900 FT-790R 70cm portable/mobile/base multimode 259.00 FIF:28 Computer interface RS-232 S900 FT-790R Mobile mount 28.90 FIF:28 Computer interface RS-232 S900 FT-790R Mobile mount 29.91 FIF:28 Computer interface RS-232 S900 FT-790R Mobile mount 19.25 FIF:280 CM filter (450 h2) 29.50 YHA-44 Vave we helical antenna 700 FIF:2757 Switched mode FSU-50% duty 14900 S8-2 Switching unit 14.50 FIF:257 Switched mode FSU-50% duty 14500 MF-1A38 Mobile boom mic 19.95 FIF:65 Computer interface RS-22 9500 FT-708R 70cm synth handle 19.95 FIF:65 Computer interface RS-22 9500 MF-1A38 Mobile boom mic 19.95 FIF:77 Hit mount 18.50 NC-30 <td< th=""><th>щ</th><th></th><th></th><th>19.35</th><th></th><th></th><th></th></td<> | щ | | | 19.35 | | | |
| FIF:232 Computer interface RS-232 Second Se | | FT-980 | | | | 2m synth handle thumbwheel tuning + 1 | FNB-3 175.00 |
| FIF:232 Computer interface RS-232 Second Se | 4 | 00.000 | | | | | |
| Fir:232C Computer interface APJeII 59:00 FT-790R 70cm portable/mobile/base multimode 259:00 Fir:50 Computer interface APJeII 105:00 NC-11C Charger 1035 XF-8.9HC CW filter (450 Hz) 29:50 CSC-1A Case 445 XF-8.9HC CW filter (450 Hz) 29:50 YH-44 ½ were whicial anterna 70cm XF-458MC CW filter (ceramic) 49:00 SB2 Switching unit 19:57 XF-458MC CW filter (ceramic) 49:00 NF-1A30 Mobile boom micle 19:25 YF-757DX Hir transceiver gen coverage all modes 719:00 MF-1A38 Mobile boom micle 19:25 FF-757DD Hawy dury FSU - 100% dury 19:500 MF-1A38 Mobile boom micle 19:25 FF-650. Computer interface NE-322 19:500 MF-1A38 Mobile boom micle 19:50 FF-777 Hir transceiver 8 ban mobile/basi 100W 103:44 YM-240 Syntrmic 19:50 FF-77 Hir transceiver 8 band mobile/basi 100W 103:34 YM- | U | | | | F1-203h | | BA-5 155.00 |
| FIF-85 Computer interface Apple II 54:00 MMB-11 Mobile mount 28:19 FIF-86 Computer interface Apple II 29:50 CSC-14 Case 4-45 XF-8-9HC Wifter (600 Hz) 29:50 CSC-14 Case 4-45 XF-8-9HCN Wifter (600 Hz) 29:50 YHA-44 Vavare helical antenna 700 XF-455MCN Wifter (600 Hz) 29:50 YHA-44 Vavare helical antenna 700 YF-455MCN Wifter (ceramic) 49:00 YH-14 Hedset mic 19:57 FT-757KT Automatic antenna tuner 24:500 FT-720R 70cm 10W FM mobile 23:90 FP-757HD Heavy duty FSU - 100% duty 15:60 FT-720R 70cm synth handle 19:95 FR-53 Computer interface RS-232 59:00 FT-708R 70cm synth handle 19:95 FR-700 Matching gower supply 14:500 NC-7 Base stn. charger algoto 56:75 FR-700 Matching gower supply 14:500 NC-9 Stat charger 9:20 | | | | | FT-790B | 70cm portable/mobile/base multimode | 259.00 |
| Files Computer interface N.E.C. 105:00 NC-11C Charger 10:35 XF-89HC CW filter (450 Hz) 2950 CSC:1A Case 445 XF-89HC CW filter (450 Hz) 2950 YM-43 Spkr mic 19:25 XF-89HCM CW filter (ceramic) 4900 SB:2 Switching unit 14:46 XF-45SMC CW filter (ceramic) 4900 SB:2 Switching unit 14:50 XF-45SMC CW filter (ceramic) 4900 SB:2 Switching unit 14:50 FC-757A Automatic anterna turner 28:400 FF-720 Winthed mode FS1 56:75 FF-650 Computer interface NE:C. 105:00 MF-13:38 Mobile boom mic 19:95 FF-757 Computer interface NE:C. 105:00 MF-13:38 Mobile boom mic 19:95 FF-757 Mit transceiver 8 band mobile/bas 100W NC:7 Base stn. charger 39:465 57:5 FF-700 Matching anterna unit 103:44 YM-240 YD Cgrounded anterna 9:50 FF-700 </th <th></th> <th></th> <th></th> <th></th> <th></th> <th></th> <th></th> | | | | | | | |
| FF-767 Switched mode PSU = 50% duty 179:00 YM-1 Headset mic 172:22 FF-757HD Heavy duty PSU = 100% duty 179:00 SB-2 Switching unit 145:00 FF-85 Computer interface Apple II 54:00 SB-2 Switching unit 145:00 FF-85 Computer interface RS-232 59:00 FF-700R 70cm synth handle 189:00 FAS-14R Remote antenna selector 49:00 NC-8A Base stn. charger 34:65 FF-70 Matching power supply 145:00 YM-44 YD-22 Standard charger 32:00 FC-700 Matching antenna unit 103:44 YM-24A Spkr mic 22:50 FV-700 Transverter frame only 12:500 MMB-10 Mobile mount 8:45 FTV-2M Zm module 24:100 FRA-2703R 70cm handie thumbwheel tuning + FNB-3 TBA FTV-24R Multimode transceiver 2m fitted 774:99 FR-7703R 70cm handie thumbwheel tuning + FNB-3 TBA FV-724R Multimode transceiver 2m fitted 774:99 FR-7703R <td< th=""><th>S</th><th></th><th></th><th></th><th></th><th>1024</th><th>10.35</th></td<> | S | | | | | 1024 | 10.35 |
| FF-767 Switched mode PSU = 50% duty 179:00 YM-1 Headset mic 172:22 FF-757HD Heavy duty PSU = 100% duty 179:00 SB-2 Switching unit 145:00 FF-85 Computer interface Apple II 54:00 SB-2 Switching unit 145:00 FF-85 Computer interface RS-232 59:00 FF-700R 70cm synth handle 189:00 FAS-14R Remote antenna selector 49:00 NC-8A Base stn. charger 34:65 FF-70 Matching power supply 145:00 YM-44 YD-22 Standard charger 32:00 FC-700 Matching antenna unit 103:44 YM-24A Spkr mic 22:50 FV-700 Transverter frame only 12:500 MMB-10 Mobile mount 8:45 FTV-2M Zm module 24:100 FRA-2703R 70cm handie thumbwheel tuning + FNB-3 TBA FTV-24R Multimode transceiver 2m fitted 774:99 FR-7703R 70cm handie thumbwheel tuning + FNB-3 TBA FV-724R Multimode transceiver 2m fitted 774:99 FR-7703R <td< th=""><th>E</th><th></th><th></th><th></th><th></th><th></th><th>4.45</th></td<> | E | | | | | | 4.45 |
| FF-767 Switched mode PSU = 50% duty 179:00 YM-1 Headset mic 172:22 FF-757HD Heavy duty PSU = 100% duty 179:00 SB-2 Switching unit 145:00 FF-85 Computer interface Apple II 54:00 SB-2 Switching unit 145:00 FF-85 Computer interface RS-232 59:00 FF-700R 70cm synth handle 189:00 FAS-14R Remote antenna selector 49:00 NC-8A Base stn. charger 34:65 FF-70 Matching power supply 145:00 YM-44 YD-22 Standard charger 32:00 FC-700 Matching antenna unit 103:44 YM-24A Spkr mic 22:50 FV-700 Transverter frame only 12:500 MMB-10 Mobile mount 8:45 FTV-2M Zm module 24:100 FRA-2703R 70cm handie thumbwheel tuning + FNB-3 TBA FTV-24R Multimode transceiver 2m fitted 774:99 FR-7703R 70cm handie thumbwheel tuning + FNB-3 TBA FV-724R Multimode transceiver 2m fitted 774:99 FR-7703R <td< th=""><th>Ĕ</th><th>XF-8-9HCM</th><th>CW filter (450 Hz)</th><th></th><th></th><th></th><th></th></td<> | Ĕ | XF-8-9HCM | CW filter (450 Hz) | | | | |
| FF-767 Switched mode PSU = 50% duty 179:00 YM-1 Headset mic 172:22 FF-757HD Heavy duty PSU = 100% duty 179:00 SB-2 Switching unit 145:00 FF-85 Computer interface Apple II 54:00 SB-2 Switching unit 145:00 FF-85 Computer interface RS-232 59:00 FF-700R 70cm synth handle 189:00 FAS-14R Remote antenna selector 49:00 NC-8A Base stn. charger 34:65 FF-70 Matching power supply 145:00 YM-44 YD-22 Standard charger 32:00 FC-700 Matching antenna unit 103:44 YM-24A Spkr mic 22:50 FV-700 Transverter frame only 12:500 MMB-10 Mobile mount 8:45 FTV-2M Zm module 24:100 FRA-2703R 70cm handie thumbwheel tuning + FNB-3 TBA FTV-24R Multimode transceiver 2m fitted 774:99 FR-7703R 70cm handie thumbwheel tuning + FNB-3 TBA FV-724R Multimode transceiver 2m fitted 774:99 FR-7703R <td< th=""><th>U</th><th></th><th></th><th></th><th></th><th></th><th></th></td<> | U | | | | | | |
| FF-767 Switched mode PSU = 50% duty 179:00 YM-1 Headset mic 172:22 FF-757HD Heavy duty PSU = 100% duty 179:00 SB-2 Switching unit 145:00 FF-85 Computer interface Apple II 54:00 SB-2 Switching unit 145:00 FF-85 Computer interface RS-232 59:00 FF-700R 70cm synth handle 189:00 FAS-14R Remote antenna selector 49:00 NC-8A Base stn. charger 34:65 FF-70 Matching power supply 145:00 YM-44 YD-22 Standard charger 32:00 FC-700 Matching antenna unit 103:44 YM-24A Spkr mic 22:50 FV-700 Transverter frame only 12:500 MMB-10 Mobile mount 8:45 FTV-2M Zm module 24:100 FRA-2703R 70cm handie thumbwheel tuning + FNB-3 TBA FTV-24R Multimode transceiver 2m fitted 774:99 FR-7703R 70cm handie thumbwheel tuning + FNB-3 TBA FV-724R Multimode transceiver 2m fitted 774:99 FR-7703R <td< th=""><th>1</th><th></th><th></th><th></th><th></th><th></th><th></th></td<> | 1 | | | | | | |
| FF-767 Switched mode PSU = 50% duty 179:00 YM-1 Headset mic 172:22 FF-757HD Heavy duty PSU = 100% duty 179:00 SB-2 Switching unit 145:00 FF-85 Computer interface Apple II 54:00 SB-2 Switching unit 145:00 FF-85 Computer interface RS-232 59:00 FF-700R 70cm synth handle 189:00 FAS-14R Remote antenna selector 49:00 NC-8A Base stn. charger 34:65 FF-70 Matching power supply 145:00 YM-44 YD-22 Standard charger 32:00 FC-700 Matching antenna unit 103:44 YM-24A Spkr mic 22:50 FV-700 Transverter frame only 12:500 MMB-10 Mobile mount 8:45 FTV-2M Zm module 24:100 FRA-2703R 70cm handie thumbwheel tuning + FNB-3 TBA FTV-24R Multimode transceiver 2m fitted 774:99 FR-7703R 70cm handie thumbwheel tuning + FNB-3 TBA FV-724R Multimode transceiver 2m fitted 774:99 FR-7703R <td< th=""><th>Ż</th><th></th><th></th><th></th><th></th><th></th><th></th></td<> | Ż | | | | | | |
| FF-767 Switched mode PSU = 50% duty 179:00 YM-1 Headset mic 172:22 FF-757HD Heavy duty PSU = 100% duty 179:00 SB-2 Switching unit 145:00 FF-85 Computer interface Apple II 54:00 SB-2 Switching unit 145:00 FF-85 Computer interface RS-232 59:00 FF-700R 70cm synth handle 189:00 FAS-14R Remote antenna selector 49:00 NC-8A Base stn. charger 34:65 FF-70 Matching power supply 145:00 YM-44 YD-22 Standard charger 32:00 FC-700 Matching antenna unit 103:44 YM-24A Spkr mic 22:50 FV-700 Transverter frame only 12:500 MMB-10 Mobile mount 8:45 FTV-2M Zm module 24:100 FRA-2703R 70cm handie thumbwheel tuning + FNB-3 TBA FTV-24R Multimode transceiver 2m fitted 774:99 FR-7703R 70cm handie thumbwheel tuning + FNB-3 TBA FV-724R Multimode transceiver 2m fitted 774:99 FR-7703R <td< th=""><th>ō</th><th></th><th></th><th></th><th></th><th></th><th></th></td<> | ō | | | | | | |
| • FP-757HD Heavy dury FSU-100% dury 179:00 YM-1 Headset mic 1575 • FP-757HD Heavy dury FSU-100% dury 179:00 YM-1 Headset mic 189:00 • FP-752 Computer interface N.E.C. 105:00 NK-1A3B Mobile boom mic 189:00 • FR-7232C Computer interface N.E.C. 105:00 NK-1A3B Mobile boom mic 189:00 • FR-7232C Computer interface NE-522 59:00 NC-5A Base stn. charger interface NE-522 36:00 • FR-720 Matching power supply 103:44 YM-24A Base stn. charger interface NE-522 59:00 • FT-70 Matching antenna unit 103:44 YM-24A Do 20:00 DA:3 DC adaptor 16:00 FT-720 Matching antenna unit 119:00 FN2-2 Battery pack adaptor (NCBA-NC-7) 365 FTV-4M Am module 56:00 FT-703R 70cm handie thumbwheel tuning + FNB-3 TBA MU-770 form module 24:10 19:35 FRG-7700/R | C | | | | | | |
| FIF-65 Computer interface AppleII 54:00 SB-2 Switching unit 14:50 FIF-63 Computer interface RS-232 59:00 M5-17.08R Mobile boom mic 18:95 FIF-73 AR Remote antenna selector 49:00 MC-7A Base stn. charger/adator 56:75 MMB-20 Mobile mount 18:50 NC-7 Base stn. charger 34:65 FF-77 Hf transceiver 8 band mobile/base 100W 507:55 NC-9C Standard charger 9:20 FF-77 Matching anterna unit 10:84 YM-24A Spkrminic 2:250 FV-700 Matching anterna unit 10:84 YM-24A Spkrminic 2:250 FV-700 Transverterfame only 12:600 MMB-10 Mobile mount 8:45 FTV-70 Torm module 241:00 FN-2 Battery pack 70:70 FV-70 Torm module 29:00 FT-703R Torm handie thumbwheel tuning + FNB-3 TBA MU-77 Marker unit 10:94 FT-703R Torm handie thumbwheel tuning + FNB-3 | | | | | | | |
| B FIF-80 Computer interface N.E.C. 105-00 MF-1A3B Mobile boom mic 18-95 FF-732C Computer interface NS-323 59-00 FT-708 70cm synth handie 18-95 MMB-20 Mobile mount 18-95 70cm synth handie 18-96 FF-700 Matching power supply 103-84 YM-44D ½D Cgrounded antenna 950 FV-700 Matching antenna unit 103-84 YM-24A Spkrmic 22-50 FV-700 Matching antenna unit 103-84 YM-24A Spkrmic 22-50 FV-700 Matching antenna unit 10-90 FNB-2 Battery pack adaptor (NCBA-NC-7) 3-65 FTV-700 Transverter frame only 125-00 FR-703R 70cm handie thumbwheel tuning + FNB-3 TBA FTV-4M 4m module 95-00 FR-7703R 70cm handie thumbwheel tuning + FNB-3 TBA MULTIP Multimode transceiver 2m fitted 77-93 FRG-7700/M General coverage receiver 38-50 FT-726R Multimode transceiver 2m fitted 95-00 FRV-7700/M </th <th></th> <th></th> <th></th> <th></th> <th></th> <th></th> <th></th> | | | | | | | |
| MMB-20 Mobile mount 19-50 NC-7 Base str. charger 34-65 FF-700 Hartning power supply 145-00 YHA-44D ½ DC grounded antenna 9-50 FF-700 Matching power supply 103-80 YM-44D ½ DC grounded antenna 9-50 FV-700 Matching antenna unit 209-00 DA-3 DC adaptor 16-00 FV-700DM Digital VFO 209-00 DA-3 DC adaptor 8-45 FV-700 Transverter frame only 125-00 MAB-10 MAB-10 Mobile mount 8-45 FV-700 Tom module 19-00 FF-703R 70cm handie thumbwheel tuning + FNB-4 TBA MU-77 Marker unit 10-84 FF-703R 70cm handie thumbwheel tuning + FNB-4 TBA XF-8 9KC CW filter (600 Hz) 19-35 FRG-7700 General coverage receiver 385-00 FT-728R Multmode transceiver 2m fitted 774-93 FRG-7700/M General coverage receiver + 12CH memory 455-00 FV-726R Multmode transceiver 2m fitted 79-00 | 8 | FIF-80 | | | MF-1A3B | | |
| MMB-20 Mobile mount 19-50 NC-7 Base str. charger 34-65 FF-700 Hartning power supply 145-00 YHA-44D ½ DC grounded antenna 9-50 FF-700 Matching power supply 103-80 YM-44D ½ DC grounded antenna 9-50 FV-700 Matching antenna unit 209-00 DA-3 DC adaptor 16-00 FV-700DM Digital VFO 209-00 DA-3 DC adaptor 8-45 FV-700 Transverter frame only 125-00 MAB-10 MAB-10 Mobile mount 8-45 FV-700 Tom module 19-00 FF-703R 70cm handie thumbwheel tuning + FNB-4 TBA MU-77 Marker unit 10-84 FF-703R 70cm handie thumbwheel tuning + FNB-4 TBA XF-8 9KC CW filter (600 Hz) 19-35 FRG-7700 General coverage receiver 385-00 FT-728R Multmode transceiver 2m fitted 774-93 FRG-7700/M General coverage receiver + 12CH memory 455-00 FV-726R Multmode transceiver 2m fitted 79-00 | S S | | | | FT-708R | | |
| FT-77 HF transceiver 8 band mobile/base 100W 507-55 NC-9C Standard charger 9 20 PF.700 Matching antenna unit 145:00 YHA.44D ½D C grounded antenna 9 50 FC-700 Matching antenna unit 128:00 MKB-10 DC adaptor 16:00 FV-700 Transverter frame only 125:00 MKB-10 Mobile mount 8:45 FTV-70 Tormondule 21:00 FNB-2 Battery pack 23:00 FTV-70 Tormondule 21:00 FNB-2 Battery pack daptor (NC8A-NC-7) 3:65 FTV-72M Arm module 95:00 FT-703R 70cm handie thumbwheel tuning + FNB-3 TBA XF-8:9KC CW filter (600 Hz) 19:35 FRG-7700 G General coverage receiver 38:50 FT-726 Multimode transceiver 2m fitted 70:99 FGC-7700/M General coverage receiver + 12CH memory 45:50 50/726 Gm module 25:900 FRV-7700/A VHF converter 9:425 50/726 Gm module 29:90 FRV-7700/C VHF converter 9:425 50/726 Gm module 9:90 <th>ž</th> <th></th> <th></th> <th></th> <th></th> <th></th> <th></th> | ž | | | | | | |
| PP.700 Matching power supply 145:00 WD.444D ½ DC grounded antenna 9:50 PC.700 Matching antenna unit 103:84 YM-24A Spkr mic 22:50 PV.700DM Digital VFO 2090 DA-3 DC adaptor 16:00 FV.700 Transverter frame only 12:00 MMB-10 Mobile mount 8:45 FTV-70 Transverter frame only 12:00 FBA-2 Battery pack 23:00 FTV-70 Torm module 24:100 FBA-2 Battery pack adaptor (NC8A-NC-7) 3:65 FTV-70 Torm module 9:50 FT-703R 70cm handie thumbwheel tuning + FNB-3 TBA KF8-8%C Wifter (600 Hz) 19:35 FRG-7700 General coverage receiver 38:500 FT-726R Multimode transceiver 2m fitted 77:99 FRG-7700M General coverage receiver 38:500 F1-726R Multimode transceiver 2m fitted 79:99 FRV-7700/A VHF converter 39:50 50/726 6m module 29:90 FRV-7700/A VHF converter <td< th=""><th></th><th></th><th>1.5 States of the second states of the second states and the second states are set.</th><th></th><th></th><th></th><th></th></td<> | | | 1.5 States of the second states of the second states and the second states are set. | | | | |
| PC 700 Matching antenna unit 103:84 YM-24A Spkr mic 22:50 PV-700D Digital VFO 209:00 DA:3 DC adaptor 16:00 FTV-700 Transverter frame only 125:00 MMB-10 Mobile mount 8:45 FTV-700 Transverter frame only 125:00 MMB-10 Mobile mount 8:45 FTV-700 Transverter frame only 126:00 FNB-2 Battery pack 23:00 FTV-707 70cm module 24:100 FBA-2 Battery pack adaptor (NC8A-NC-7) 3:65 FTV-707 70cm module 95:00 FT-703R 70cm handie thumbwh.el tuning + FNB-3 TBA FTV-726 Wittimode transceiver 2m fitted 774:99 FRG-7700M General coverage receiver + 12CH memory 455:00 21/24/28 HF module 299:00 FRV-7700/M VHF converter 99:95 50/726 form module 299:00 FRV-7700/M VHF converter 90:75 430/726 70cm module 299:00 FRV-7700/M VHF converter 94:25 | | | | | | | |
| FTV-700 Transverter frame biny 12.50 MMB-10 MODE 10 36.50 FTV-70 Tocm module 21100 FBA-2 Battery pack adaptor (NC8A-NC-7) 365 FTV-70 Tocm module 9500 FBA-2 Battery pack adaptor (NC8A-NC-7) 365 MU-77 Marker unit 10.84 FT-703R Tocm handie thumbwhel tuning + FNB-4 TBA KF8-9KCN W filter (300 Hz) 19.35 FRG-7700 General coverage receiver 385.00 FT-728R Mutimode transceiver 2m fitted 77499 FRG-7700/M General coverage receiver + 12CH memory 455.00 50/726 6m module 19500 FRV-7700/A WHF converter 89.95 50/726 70cm module 255.00 FRV-7700/A VHF converter 90.75 50/726 70cm module 259.00 FRV-7700/C VHF converter 91.74 50/726 70cm bile/mobile/base multimode 1950 FRV-7700/C VHF converter 94.25 50/726 70cm bandie transceiver 44 1950 FRV-7700/C VHF converter 94.25 50/726 70cm bale mount 279.00 | | | Matching power supply | | | | |
| FTV-700 Transverter frame biny 12.50 MMB-10 MODE 10 36.50 FTV-70 Tocm module 21100 FBA-2 Battery pack adaptor (NC8A-NC-7) 365 FTV-70 Tocm module 9500 FBA-2 Battery pack adaptor (NC8A-NC-7) 365 MU-77 Marker unit 10.84 FT-703R Tocm handie thumbwhel tuning + FNB-4 TBA KF8-9KCN W filter (300 Hz) 19.35 FRG-7700 General coverage receiver 385.00 FT-728R Mutimode transceiver 2m fitted 77499 FRG-7700/M General coverage receiver + 12CH memory 455.00 50/726 6m module 19500 FRV-7700/A WHF converter 89.95 50/726 70cm module 255.00 FRV-7700/A VHF converter 90.75 50/726 70cm module 259.00 FRV-7700/C VHF converter 91.74 50/726 70cm bile/mobile/base multimode 1950 FRV-7700/C VHF converter 94.25 50/726 70cm bandie transceiver 44 1950 FRV-7700/C VHF converter 94.25 50/726 70cm bale mount 279.00 | A | | | | | | |
| FTV-2M 2m module 119:00 FNB-2 Battery pack 23:00 FTV-70 70cm module 241:00 FBA-2 Battery pack adaptor (NC8A-NC-7) 3:65 FTV-4M 4m module 10:84 FT-703R 70cm handie thumbwheel tuning + FNB-3 TBA MU-77 Marker unit 10:84 FT-703R 70cm handie thumbwheel tuning + FNB-4 TBA XF-8-9KCN Wiltimode transceiver 2m fitted 19:35 FRG-7700 General coverage receiver 385:00 712/24/28 HF module 209:00 FRV-7700/A VHF converter 89:95 50/726 6m module 29:900 FRV-7700/A VHF converter 89:95 50/726 70cm module 29:900 FRV-7700/C VHF converter 84:50 SAT-726 Duplex module 29:90 FRV-7700/C VHF converter 94:25 SAT-726 Duplex module 29:90 FRV-7700/C VHF converter 94:25 SAT-726 Duplex module 29:90 FRV-7700/C VHF converter 94:25 | | | | | | | |
| FTV-70 70cm module 24100 FBA-703R 70cm handie thumbwheel tuning + FNB-3 TBA MU-77 Marker unit 1084 FT-703R 70cm handie thumbwheel tuning + FNB-3 TBA XF-8-9KC CW filter (600 Hz) 1935 70cm handie thumbwheel tuning + FNB-4 TBA XF-8-9KC CW filter (600 Hz) 1935 FRG-7703R 70cm handie thumbwheel tuning + FNB-3 TBA YF-728 Multimode transceiver 2m fitted 1935 FRG-7700M General coverage receiver 385:00 21/24/28 HF module 209:00 FRV-7700/A VHF converter 89:95 430/726 70cm module 299:00 FRV-7700/A VHF converter 90:75 430/726 70cm module 299:00 FRV-7700/C VHF converter 94:25 YF-455MC 300 HZ CW filter (ceramic) 49:00 FRV-7700/F VHF converter 94:25 YF-455MC 300 HZ CW filter (ceramic) 49:00 FRV-7700/F VHF converter 94:25 YF-455MC 300 HZ CW filter (beramic) 49:00 FRV-7700/F | • | | | | | Battery pack | 23.00 |
| W XF-8-9KC CW filter (600 Hz) 19:35 (Accessories as for FT-209 – FT-203R) YF-8-9KCN CW filter (300 Hz) 19:35 (Accessories as for FT-209 – FT-203R) YF-726R Multimode transceiver 2m fitted 19:35 (FG-7700) General coverage receiver + 12CH memory 455:50 21/24/28 HF module 209:00 FR-7700/M General coverage receiver + 12CH memory 455:50 50/726 6m module 19:500 FRV-7700/M VHF converter 90:75 50/726 70cm module 299:90 FRV-7700/C VHF converter 91:74 SAT-726 Duplex module 99:95 FRV-7700/C VHF converter 94:25 SAT-726 Duplex module 29:90 FRV-7700/F VHF converter 94:25 FT-290R 2m Portable/mobile/base multimode 279:00 FRV-7700/F VHF converter 94:25 FT-2010 10W linear for above 66:55 FRA-770 Active antenna 43:95 CSC-1A Case 44:15 FILe 11:25 YHA-15 Helical antenna 5:65 RSL-43:6GP 70:50 vore %k ground plane <td< th=""><th></th><th></th><th></th><th></th><th></th><th>Battery pack adaptor (NC8A-NC-7)</th><th></th></td<> | | | | | | Battery pack adaptor (NC8A-NC-7) | |
| W XF-8-9KC CW filter (600 Hz) 19:35 (Accessories as for FT-209 – FT-203R) YF-8-9KCN CW filter (300 Hz) 19:35 (Accessories as for FT-209 – FT-203R) YF-726R Multimode transceiver 2m fitted 19:35 (FG-7700) General coverage receiver + 12CH memory 455:50 21/24/28 HF module 209:00 FR-7700/M General coverage receiver + 12CH memory 455:50 50/726 6m module 19:500 FRV-7700/M VHF converter 90:75 50/726 70cm module 299:90 FRV-7700/C VHF converter 91:74 SAT-726 Duplex module 99:95 FRV-7700/C VHF converter 94:25 SAT-726 Duplex module 29:90 FRV-7700/F VHF converter 94:25 FT-290R 2m Portable/mobile/base multimode 279:00 FRV-7700/F VHF converter 94:25 FT-2010 10W linear for above 66:55 FRA-770 Active antenna 43:95 CSC-1A Case 44:15 FILe 11:25 YHA-15 Helical antenna 5:65 RSL-43:6GP 70:50 vore %k ground plane <td< th=""><th>Σ</th><th></th><th></th><th></th><th></th><th></th><th></th></td<> | Σ | | | | | | |
| XF-8-9KCN CW filter (300 Hz) 19-35 FRG-7700 General coverage receiver 385-00 YF-726R Multimode transceiver 2m fitted 774-99 FRG-7700/M General coverage receiver + 12CH memory 455-00 21/24/28 HF module 209-00 FRV-7700/M General coverage receiver + 12CH memory 455-00 430/726 fm module 19-50 FRV-7700/B VHF converter 90-75 430/726 70cm module 29-90 FRV-7700/C VHF converter 91-74 SAT-726 Duplex module 99-95 FRV-7700/C VHF converter 91-74 SAT-726 Duplex module 99-96 FRV-7700/E VHF converter 94-25 SAT-726 Duplex module 99-96 FRV-7700/E VHF converter 94-25 SAT-726 Duplex module 19-90 FRV-7700/F VHF converter 94-25 FT-290R 2m Portable/mobile/base multimode 279-00 Antenna tuning unit 48-25 FL-2010 10W linear for above 66-55 FRA-770 Active antenna 43-95 CSC-1A Case 445 FS-5 < | | | | | FT-703R | | B-4 TBA |
| 50/726 6m module 195:00 FRV-7700/B VHF converter 90:75 430/726 70cm module 259:00 FRV-7700/C VHF converter 84:50 50/726 70cm module 99:95 FRV-7700/C VHF converter 91:74 50/726 600 Hz CW filter (ceramic) 49:00 FRV-7700/C VHF converter 94:25 50/726 600 Hz CW filter (ceramic) 49:00 FRV-7700/F VHF converter 94:25 50/726 70 motable/mobile/base multimode 279:00 FRV-7700/F VHF converter 94:25 FT-290R 2m Portable/mobile/base multimode 279:00 FRV-7700/F VHF converter 94:25 FL-2010 10W linear for above 66:55 FRA-7700 Antenna tuning unit 43:95 NC11C Charger 10:35 Base station YAESU antennas 11:25 VM-49 Spkr mic 19:25 RSL-145GP 20 % 4 ground plane 24:75 YH-1 Headset mic 15:75 RSL-35 80m mobile whip 13:85 SB-2 Switching unit 14:50 RSL-14 5GP 20m mobile whip </th <th>8</th> <th></th> <th></th> <th></th> <th></th> <th></th> <th></th> | 8 | | | | | | |
| 50/726 6m module 195:00 FRV-7700/B VHF converter 90:75 430/726 70cm module 259:00 FRV-7700/C VHF converter 84:50 50/726 70cm module 99:95 FRV-7700/C VHF converter 91:74 50/726 600 Hz CW filter (ceramic) 49:00 FRV-7700/C VHF converter 94:25 50/726 600 Hz CW filter (ceramic) 49:00 FRV-7700/F VHF converter 94:25 50/726 70 motable/mobile/base multimode 279:00 FRV-7700/F VHF converter 94:25 FT-290R 2m Portable/mobile/base multimode 279:00 FRV-7700/F VHF converter 94:25 FL-2010 10W linear for above 66:55 FRA-7700 Antenna tuning unit 43:95 NC11C Charger 10:35 Base station YAESU antennas 11:25 VM-49 Spkr mic 19:25 RSL-145GP 20 % 4 ground plane 24:75 YH-1 Headset mic 15:75 RSL-35 80m mobile whip 13:85 SB-2 Switching unit 14:50 RSL-14 5GP 20m mobile whip </th <th>×</th> <th></th> <th></th> <th></th> <th></th> <th></th> <th></th> | × | | | | | | |
| 50/726 6m module 195:00 FRV-7700/B VHF converter 90:75 430/726 70cm module 259:00 FRV-7700/C VHF converter 84:50 50/726 70cm module 99:95 FRV-7700/C VHF converter 91:74 50/726 600 Hz CW filter (ceramic) 49:00 FRV-7700/C VHF converter 94:25 50/726 600 Hz CW filter (ceramic) 49:00 FRV-7700/F VHF converter 94:25 50/726 70 motable/mobile/base multimode 279:00 FRV-7700/F VHF converter 94:25 FT-290R 2m Portable/mobile/base multimode 279:00 FRV-7700/F VHF converter 94:25 FL-2010 10W linear for above 66:55 FRA-7700 Antenna tuning unit 43:95 NC11C Charger 10:35 Base station YAESU antennas 11:25 VM-49 Spkr mic 19:25 RSL-145GP 20 % 4 ground plane 24:75 YH-1 Headset mic 15:75 RSL-35 80m mobile whip 13:85 SB-2 Switching unit 14:50 RSL-14 5GP 20m mobile whip </th <th></th> <th></th> <th></th> <th></th> <th></th> <th></th> <th></th> | | | | | | | |
| 430/726 70cm module 259:00 FRV-7700/C VHF converter 84:50 SAT-726 Duplex module 99:95 FRV-7700/C VHF converter 91:74 Lu XF-455MC 300 HZ CW filter (ceramic) 49:00 FRV-7700/E VHF converter 94:25 FT-290R 2m Portable/mobile/base multimode 279:00 FRV-7700/F VHF converter 94:25 FL-2010 10W linear for above 66:55 FRA-7700 Antenna tuning unit 48:25 NC11C Charger 10:35 FRA-7700 Active antenna 43:95 CSC-1A Case 45:66 RSL-145GP 70cm % over %A ground plane 26:25 YM-49 Spkr mic 19:25 Mobile Stub mast RSE-2A 4:95 YH-1 Headset mic 18:95 RSL-35 80m mobile whip 13:850 SB-2 Switching unit 14:50 RSL-34 40m mobile whip 12:99 YH-1 Headset mic 19:25 RSL-34 10m mobile whip 12:99 YH-1 Headset mic 18:95 RSL-14 20m mobile whip 12:99 | | | | | | | |
| SAT-726 Duplex module 99-95 FRV-7700/D VHF converter 91-74 XF-455MC 600 Hz CW filter (ceramic) 49-00 FRV-7700/E VHF converter 94-25 YF-455MCN 300 Hz CW filter (ceramic) 49-00 FRV-7700/F VHF converter 94-25 YF-455MCN 300 Hz CW filter (ceramic) 49-00 FRV-7700/F VHF converter 94-25 YF-455MCN 300 Hz CW filter (ceramic) 49-00 FRV-7700/F VHF converter 94-25 YF-455MCN 300 Hz CW filter (ceramic) 49-00 FRV-7700/F VHF converter 94-25 YF-4510 10/Winear for above 66-55 FRA-7700 Active antenna tuning unit 48-25 NC11C Charger 10-35 Base station YAESU antennas 70 YHA-15 Helical antenna 5-66 RSL-435GP 70cm % over % A ground plane 36-25 YM-49 Spkr mic 19-25 Mobile Stub mast RSE-2A 495 SB-2 Switching unit 14-50 RSL-74 40m mobile whip 13-50 YM-49 Spkr mic 19-25 RSL-14 | • | | | | | | |
| XF-455MC 600 Hz CW filter (ceramic) 49-00 FRV-7700/E VHF converter 94-25 XF-455MCN 300 HZ CW filter (ceramic) 49-00 FRV-7700/F VHF converter 94-25 FT-290R 2m Portable/mobile/base multimode 279-00 FRT-7700 Antenna tuning unit 48-25 FT-290R 2m Portable/mobile/base multimode 28-19 FRA-7700 Antenna tuning unit 48-25 MMB-11 Mobile mount 28-19 FR-5 Filter 11-25 NC11C Charger 10-35 Base station YAESU antennas CSC-1A Case 4-45 RSL-145GP 2m %A ground plane 24-75 YM-49 Spkr mic 19-25 Mobile Stub mast RSE-2A 4-95 YH-1 Headset mic 15-76 RSL-3-5 80m mobile whip 13-85 SB-2 Switching unit 14-50 RSL-7A 40m mobile whip 12-99 YM-49 Spkr mic 18-95 RSL-14 20m mobile whip 12-99 YM-49 Spkr mic 19-25 RSL-28 10m mobile whip 12-99 YM-49< | | | Duplex module | | | | |
| FT-290R 2m Portable/mobile/base multimode 279-00 FRT-7700 Antenna tuning unit 48-25 FL-2010 10W linear for above 66-55 FRA-7700 Active antenna 43-95 MMB-11 Mobile mount 28-19 FF-5 Filter 11:25 NC11C Charger 10:35 Base station YAESU antennas 24-75 YHA-15 Helical antenna 5-66 RSL-145GP 2m % d ground plane 24-75 YM-49 Spkr mic 19-25 Mobile Stub mast RSE-2A 4-95 YH-1 Headset mic 15-75 RSL-35 80m mobile whip 13-85 SB-2 Switching unit 14-50 RSL-7A 40m mobile whip 12-99 FT-230R 2m mobile 25W FM 269-00 RSL-21 15m mobile whip 12-75 YM-49 Spkr mic 19-25 RSL-22 0m mobile whip 12-75 FT-230R 2m mobile 25W FM 269-00 RSL-14 20m mobile whip 12-75 YM-49 Spkr mic 19-2 | Ш | | | | FRV-7700/E | | |
| FL-2010 10W linear for above 66-55 FRA-7700 Active antenna 43-95 MMB-11 Mobile mount 28-19 FF-5 Filter 11-25 NC11C Charger 10-35 Base station YAESU antennas 24-75 CSC-1A Case 445 RSL-145GP 2m % & ground plane 24-75 YHA-15 Helical antenna 5-65 RSL-35GP 70cm % over % & ground plane 36-25 YH-1 Headset mic 15-75 RSL-35GP 70cm % over % & ground plane 36-25 SB-2 Switching unit 14-50 RSL-7A 40m mobile whip 13-85 SB-2 Switching unit 14-50 RSL-7A 40m mobile whip 12-99 FT-230R 2m mobile 25W FM 269-00 RSL-21 15m mobile whip 12-75 YM-49 Spkr mic 19-25 RSL-28 10m mobile whip 12-45 YM-49 Spkr mic 19-25 RSL-28 10m mobile whip 12-45 YM-49 Spkr mic 19-25 RSL-28 10m mobile whip 12-45 SB-2 Switching un | | 2000 00 / 2000 00 00 00 00 00 00 00 00 00 00 00 0 | · 이상에 가지 않는 것 같아? 이 가지 않는 것 같아? 이상이 있는 것 이 가지 않는 것 같아? 이상에 있는 것 같아? 이상에 있는 것 같아? 이상이 있는 것 같아? 이상이 있는 것 같아? 이상이 가 있는 것 같아? 이상이 있 않는 것 같아? 이상이 있는 것 같아? 이상이 있 | | | | |
| OCN MMB-11 Mobile mount 28:19 FF-5 Filter 11:25 NC11C Charger 10:35 Base station YAESU antennas 24:75 CSC-1A Case 4:45 RSL-145GP 70cm % over % / ground plane 24:75 YHA-15 Helical antenna 5:65 RSL-435GP 70cm % over % / ground plane 36:25 YH-1 Headset mic 15:75 RSL-35 80m mobile whip 13:85 SB-2 Switching unit 14:50 RSL-7A 40m mobile whip 13:85 MF-1A3B Mobile mic 18:95 RSL-7A 40m mobile whip 12:99 FT-230R 2m mobile 25W FM 269:00 RSL-21 15m mobile whip 12:99 YM-49 Spkr mic 19:25 RSL-28 10m mobile whip 12:99 YM-49 Spkr mic 19:25 RSL-21 15m obile whip 12:99 FT-209R 2m synth FM handie 350mw/3W 239:00 RSL-145S 2m % / whip 10:50 FT-209R 2m synth FM handie 500mw/5W 259:00 RSL-150SS 2m % / whip 4:25 | • | | | | | | |
| NC11C Charger 10:35 Base station YAESU antennas CSC-1A Case 4:45 Base station YAESU antennas 24:75 YHA-15 Helical antenna 5:65 RSL-145GP 2m %/ ground plane 36:25 YM-49 Spkr mic 19:25 Mobile Stub mast RSE-2A 4:95 YH-1 Headset mic 15:75 RSL-3:5 80m mobile whip 13:85 SB-2 Switching unit 14:50 RSL-7A 40m mobile whip 13:50 MF-1A3B Mobile mic 18:95 RSL-14 20m mobile whip 12:75 YM-49 Spkr mic 19:25 RSL-21 15m mobile whip 12:75 YM-49 Spkr mic 19:25 RSL-21 15m mobile whip 12:75 YM-49 Spkr mic 19:25 RSL-28 10m mobile whip 12:45 MF-1A3B Mobile boom mic 18:95 RSM-2 Gutter clip for above 12:45 SB-2 Switching unit 14:50 RSL-145S 2m %/ whip 10:50 FT-209R 2m synth FM handie 350mw/3W 239:00 | | | | | | | |
| YH-1 Headset mic 15-75 RSL-35 80m mobile whip 13:85 SB-2 Switching unit 14:50 RSL-7A 40m mobile whip 13:50 MF-1A3B Mobile mic 18:95 RSL-7A 40m mobile whip 12:99 FT-230R 2m mobile 25W FM 269:00 RSL-21 15m mobile whip 12:99 YM-49 Spkr mic 19:25 RSL-28 10m mobile whip 12:45 MF-1A3B Mobile boom mic 18:95 RSM-2 Gutter clip for above 12:45 SB-2 Switching unit 14:50 RSL-145S 2m %/ whip 10:50 FT-209R 2m synth FM handie 350mw/3W 239:00 RSL-150SS 2m ¼/ whip 4:25 FT-209RH 2m synth FM handie 500mw/5W 259:00 RSL-435S 70cm % over %/ whip 17:74 NC-15 Base stn charger/adaptor 49:94 RSM-3R Gutter clip for above 9:25 NC-18 Standard charger (FNB-4) 10:35 RSM-4M Mag mount for above 15:00 | N. | | | | - 12.12.12.12.12. | | 1125 |
| YH-1 Headset mic 15.75 RSL-35 80m mobile whip 13.85 SB-2 Switching unit 14.50 RSL-7A 40m mobile whip 13.50 MF-1A3B Mobile mic 18.95 RSL-7A 40m mobile whip 12.99 FT-230R 2m mobile 25W FM 269:00 RSL-21 15m mobile whip 12.75 YM-49 Spkr mic 19:25 RSL-28 10m mobile whip 12.45 MF-1A3B Mobile boom mic 18:95 RSM-2 Gutter clip for above 12.45 SB-2 Switching unit 14:50 RSL-145S 2m %/ whip 10:50 FT-209R 2m synth FM handie 350mw/3W 239:00 RSL-150SS 2m ¼/ whip 4:25 FT-209RH 2m synth FM handie 500mw/5W 259:00 RSL-435S 70cm % over %/ whip 17:74 NC-15 Base stn charger/adaptor 49:94 RSM-3R Gutter clip for above 9:25 NC-18 Standard charger (FNB-4) 10:35 RSM-4M Mag mount for above 15:00 | N | | | 4.45 | | | 24.75 |
| YH-1 Headset mic 15.75 RSL-35 80m mobile whip 13.85 SB-2 Switching unit 14.50 RSL-7A 40m mobile whip 13.50 MF-1A3B Mobile mic 18.95 RSL-7A 40m mobile whip 12.99 FT-230R 2m mobile 25W FM 269:00 RSL-21 15m mobile whip 12.75 YM-49 Spkr mic 19:25 RSL-28 10m mobile whip 12.45 MF-1A3B Mobile boom mic 18:95 RSM-2 Gutter clip for above 12.45 SB-2 Switching unit 14:50 RSL-145S 2m %/ whip 10:50 FT-209R 2m synth FM handie 350mw/3W 239:00 RSL-150SS 2m ¼/ whip 4:25 FT-209RH 2m synth FM handie 500mw/5W 259:00 RSL-435S 70cm % over %/ whip 17:74 NC-15 Base stn charger/adaptor 49:94 RSM-3R Gutter clip for above 9:25 NC-18 Standard charger (FNB-4) 10:35 RSM-4M Mag mount for above 15:00 | | ····································· | Helical antenna | | | | |
| YH-1 Headset mic 15'75 RSL-3:5 80m mobile whip 13:85 SB-2 Switching unit 14:50 RSL-7A 40m mobile whip 13:50 MF-1A3B Mobile mic 18:95 RSL-14 20m mobile whip 12:99 FT-230R 2m mobile 25W FM 269:00 RSL-21 15m mobile whip 12:75 YM-49 Spkr mic 19:25 RSL-28 10m mobile whip 12:45 MF-1A3B Mobile boom mic 18:95 RSM-2 Gutter clip for above 12:45 SB-2 Switching unit 14:50 RSL-145S 2m %/ whip 10:50 FT-209R 2m synth FM handie 350mw/3W 239:00 RSL-150SS 2m ¼ / whip 4:25 FT-209RH 2m synth FM handie 500mw/5W 259:00 RSL-435S 70cm % over %/ whip 17:74 NC-15 Base stn charger/adaptor 49:94 RSM-3R Gutter clip for above 9:25 NC-18 Standard charger (FNB-4) 10:35 RSM-4M Mag mount for above 15:00 | A | | Spkrmic | | | | 4.95 |
| SB-2 Switching unit 14'50 RSL-7A 40m mobile whip 13'50 MF-1A3B Mobile mic 18'95 RSL-14 20m mobile whip 12'99 FT-230R 2m mobile 25W FM 269'00 RSL-21 15m mobile whip 12'75 YM-49 Spkr mic 19'25 RSL-28 10m mobile whip 12'45 MF-1A3B Mobile boom mic 18'95 RSM-2 Gutter clip for above 12'45 SB-2 Switching unit 14'50 RSL-145S 2m %/ whip 10'50 FT-209R 2m synth FM handie 350mw/3W 239:00 RSL-150SS 2m ¼/ whip 4'25 FT-209RH 2m synth FM handie 500mw/5W 259:00 RSL-435S 70cm %/ over %/ whip 17'74 NC-15 Base stn charger/adaptor 49:94 RSM-3R Gutter clip for above 9'25 NC-18 Standard charger (FNB-4) 10'35 RSM-4M Mag mount for above 15:00 | | | 그는 것은 것 같아요. 것은 것은 것은 것은 것을 알고 있다. | | | | |
| FT-230R 2m mobile 25W FM 269:00 RSL-14 20m mobile whip 12:39 YM-49 Spkr mic 19:25 RSL-21 15m mobile whip 12:45 MF-1A3B Mobile boom mic 18:95 RSL-28 10m mobile whip 12:45 SB-2 Switching unit 14:50 RSL-145S 2m % / whip 10:50 FT-209R 2m synth FM handie 350mw/3W 239:00 RSL-150SS 2m ¼ / whip 4:25 FT-209RH 2m synth FM handie 500mw/5W 259:00 RSL-435S 70cm % over % / whip 17:74 NC-15 Base stn charger/adaptor 49:94 RSM-3R Gutter clip for above 9:25 NC-18 Standard charger (FNB-4) 10:35 RSM-4M Mag mount for above 15:00 | | | | | RSL-7A | | |
| Nin-1ASB Mobile boommile 10-53 RSM-2 Gutter clip for above 12/45 SB-2 Switching unit 14-50 RSL-145S 2m % / whip 10-50 FT-209R 2m synth FM handie 350mw/3W 239:00 RSL-150SS 2m ¼ / whip 4:25 FT-209RH 2m synth FM handie 500mw/5W 259:00 RSL-435S 70cm % over % / whip 17:74 NC-15 Base stn charger/adaptor 49:94 RSM-3R Gutter clip for above 9:25 NC-18 Standard charger (FNB-4) 10:35 RSM-4M Mag mount for above 15:00 | | | | | | 이번 방법 방법 방법 가슴다. 것 같은 것 같 | |
| Nin-1ASB Mobile boommile 10-53 RSM-2 Gutter clip for above 12/45 SB-2 Switching unit 14-50 RSL-145S 2m % / whip 10-50 FT-209R 2m synth FM handie 350mw/3W 239:00 RSL-150SS 2m ¼ / whip 4:25 FT-209RH 2m synth FM handie 500mw/5W 259:00 RSL-435S 70cm % over % / whip 17:74 NC-15 Base stn charger/adaptor 49:94 RSM-3R Gutter clip for above 9:25 NC-18 Standard charger (FNB-4) 10:35 RSM-4M Mag mount for above 15:00 | A | | | | | | |
| SB-2 Switching unit 14-50 RSL-145S 2m % / whip 10-50 FT-209R 2m synth FM handie 350mw/3W 239-00 RSL-145S 2m % / whip 4-25 FT-209RH 2m synth FM handie 500mw/5W 259-00 RSL-435S 70cm % over % / whip 17-74 PC-15 Base stn charger/adaptor 49-94 RSM-3R Gutter clip for above 9-25 NC-18 Standard charger (FNB-4) 10-35 RSM-4M Mag mount for above 15-00 | | | | | | | |
| FT-209R 2m synth FM handie 350mw/3W 239:00 RSL-150SS 2m ¼ / whip 4:25 FT-209RH 2m synth FM handie 500mw/5W 259:00 RSL-150SS 2m ¼ / whip 17:74 NC-15 Base stn charger/adaptor 49:94 RSM-3R Gutter clip for above 9:25 NC-18 Standard charger (FNB-4) 10:35 RSM-4M Mag mount for above 15:00 | • | Second and a second state of the second s | | | | | |
| FT-209RH NC-152m synth FM handie 500mw/5W Base stn charger/adaptor NC-18259:00 Base stn charger/adaptor Standard charger (FNB-4)RSL-435S 49:9470cm % over % / whip Gutter clip for above Mag mount for above17-74 9:25MC-18Standard charger (FNB-4)10:35RSM-4MMag mount for above9:25 | 100 | FT-209R | | 239.00 | | | |
| | E | The second s | | | | | 17.74 |
| | 2 | NC-15 | Base stn charger/adaptor | | RSM-3R | Gutter clip for above | |
| | | NC-18 | Standard charger (FNB-4) | 10.35 | RSM-4M | Mag mount for above | 15.00 |
| | 1.000 | AKD • | BNOS . DATONG . MUT | EK • | MICROWA | VE MODULES . TONNA | HI MOUND |

| essories Frequency counter Frequency counter Dummy load wattmeter Mobile ext spkr Leather case FT-208/708 DC lead FT-0NE DC lead FT-480R | YA 189·75 270·00 103·95 16·50 32·57 10·84 | ESU DCL-230/73 FF-501DX LB QTR-24D YH-55 | Low pass filter Log book World clock | /730 | 2.5 |
|---|---|---|---|---|---|
| Frequency counter Frequency counter Dummy load wattmeter Mobile ext spkr Leather case FT-208/708 DC lead FT-0NE | 270.00 103.95 16.50 32.57 | FF-501DX LB QTR-24D | Low pass filter Log book World clock | /730 | 28·9 2·5 |
| Frequency counter Dummy load wattmeter Mobile ext spkr Leather case FT-208/708 DC lead FT-0NE | 270.00 103.95 16.50 32.57 | FF-501DX LB QTR-24D | Low pass filter Log book World clock | | 28·9 2·5 |
| Dummy load wattmeter Mobile ext spkr Leather case FT-208/708 DC lead FT-0NE | 103·95 16·50 32·57 | LB QTR-24D | Log book World clock | | 2.5 |
| Leather case FT-208/708 DC lead FT-0NE | 32.57 | | World clock | | 24.0 |
| DC lead FT-0NE | | YH-55 | | | 34.9 |
| | | | Headphones | - h to | 12.5 |
| | 6.55 | YH-77 MU-7700 | Headphones (I Memory unit fo | | 12·5 75·0 |
| T. | E.T. a | ntennas | • | | |
| 2 element tri-band beam 10, 15, 20m | 172.50 | | Vertical antenna 1 | | 98-99 |
| 3 element tri-band beam 10, 15, 20m | 231.50 | MV3BHR | Vertical antenna 1 | 0, 15, 20m + trapped r | adials 78.00 |
| | | | | | |
| | | | | | 1 58·99 45·79 |
| Vertical antenna 10, 15, 20, 40m | | | | | 45·74 52·74 |
| Το | kyo H | ly Power | r | | |
| HF bands ATU 200W PEP | 82.95 | Pre-amps | | | |
| HF bands ATU 350W PEP | 149.00 | HRA-2 | | | |
| HE DANGS AT U ZKW PEP | IBA | HKA-/ | /ucm mast head | pre-amp 103-30 | |
| 30W 2m linear 0.5-3W input | 39.99 | | | | |
| 85W 2m linear 10W input | 144.50 | | | | 3-00-6 |
| 110W 2m linear | 179.95 | | EWALD | licro-7 | |
| 160W 2m linear 10W input | 244.52 | | | | |
| 160W 2m linear 25W input | 209.73 | Joh 70 | and handle 4 | ah fitted | |
| 20W 70cm linear | 77.00 | | | ch. fitted | |
| | | 200mw | FM | A A A A | - |
| 90W 70cm linear 10W input | 268.59 | Pairs of crys | stals 10.00 | £99.00 | |
| | | | | | |
| | 13.67 | Baluns | 0.1.50 | 10.1 | |
| | | 2 20 PE 11 2 2 3 5 2 | | | 14.90 |
| | | BLOOK | | i balun 4 kw (pep) | 18.65 |
| orse key, A.B.S. base, dust cover | 18.97 | SAMEON | | itch (N/ connectors | |
| orse key, marble base, dust cover | 29.65 | | | | s 12.6 |
| orse key, heavy marble base and dust cover | 39.00 | RF2000 | | | 5 12·6 |
| | | 5M | PL259-PL259 pat | ch lead 50 cm | 2.24 |
| | | 8M | 물건 영감은 승규가 바람이 잘 해야 하는 것이 가지 않는 것이 것. | | 2.3 |
| ode oscillator for practice | 7.99 | 5MM | | ch lead 3·8 m | 2.9 |
| | | | | lator | 0.40 eac |
| | | AE/DOG | | | 0.60 eac |
| | | | | 5 100 0 V | |
| | | | | Amateur Electro | onics Ltd. |
| 00 watt 3·5–500 MHZ dummy load | 42.26 | | | FREEPOST | |
| 45/430 MHZ R.F. Thru-line watt meter, 200W | 49-35 | ENC | | Birmingham B8 | 1BR |
| | 2 element tri-band beam (mini) 10, 15, 20m 3 element tri-band beam (mini) 10, 15, 20m Vertical antenna 10, 15, 20m Vertical antenna 10, 15, 20m Vertical antenna 10, 15, 20m Vertical antenna 10, 15, 20m To HF bands ATU 200W PEP HF bands ATU 250W PEP HF bands ATU 2Kw PEP 30W 2m linear 0-5–3W input 85W 2m linear 10W input 110W 2m linear 160W 2m linear 10W input 160W 2m linear 25W input 20W 70cm linear 45W 70cm linear 10W input 90W 70cm linear 10W input and morse key with A.B.S. base and morse key with A.B.S. base and dust cover orse key, A.B.S. base, dust cover orse key, marble base, dust cover orse key, marble base, dust cover orse key, narble base, dust cover orse key, narble base, dust cover orse key, narble base and dust cover orse key, narble base and dust cover orse key on a heavy marble base base code oscillator for practice 5–150 MHZ 120 watt SWR/PWR meter 45/430 MHZ R.F. Thru-line watt meter, 120W 0 watt 3-5–500 MHZ dummy load 20 watt 3-5–500 MHZ Rumy load 20 watt 3-5–500 MHZ Rumy load | 2 element tri-band beam (mini) 10, 15, 20m 3 element tri-band beam (mini) 10, 15, 20m Vertical antenna 10, 15, 20m Vertical antenna 10, 15, 20m 49:95 Vertical antenna 10, 15, 20, 40m169:50 230:00 49:95 Vertical antenna 10, 15, 20, 40mTokyo HHF bands ATU 200W PEP HF bands ATU 250W PEP HF bands ATU 2Kw PEP82:95 149:00 HF bands ATU 2Kw PEP30W 2m linear 0.5–3W input 10W 2m linear 110W 2m linear 110W 2m linear 10W input 45W 70cm linear 10W input 244:52 160W 2m linear 10W input 25W 70cm linear 10W input 268:5920W 70cm linear 10W rocm linear 10W input 268:59and morse key with A.B.S. base and morse key with A.B.S. base and dust cover orse key, has. base, dust cover orse key, marble base, dust cover orse key, marble base, dust cover olished brass key with weighted wooden base queeze key heavy base required queeze key heavy marble base pobe oscillator for practice18:80 42:76 7:995–150 MHZ 120 watt SWR/PWR meter 45/430 MHZ R.F. Thru-line watt meter, 120W 0 watt 3:5–500 MHZ dummy load 00 watt 3:5–500 MHZ dummy load | 2 element tri-band beam (mini) 10, 15, 20m 3 element tri-band beam (mini) 10, 15, 20m Vertical antenna 10, 15, 20m Vertical antenna 10, 15, 20m Vertical antenna 10, 15, 20, 40m169-50 230-00 49-95 SQY06 SQY08MV4BHR SQ22 SQY06 SQY08Tokyo Hy Power HF bands ATU 200W PEP HF bands ATU 2Kw PEP82-95 149-00 HF bands ATU 2Kw PEPPre-amps HRA-2 HRA-2 HRA-730W 2m linear 0.5–3W input 100W 2m linear 10W input 100W 2m linear 10W input 200 71339-99 144-50 179-95 200 70cm linear 10W input 152-77 20W 70cm linear 10W input 45W 70cm linear 10W input 90W 70cm linear 10W input 268-593ch. 70 200 mw Pairs of crys 3ch. 70 200 mw Pairs of crysand morse key with A.B.S. base and morse key with A.B.S. base and dust cover orse key, A.B.S. base, dust cover orse key, heavy marble base, dust cover orse key, heavy marble base, dust cover orse key, heavy marble base, dust cover orse key heavy marble base and dust cover orse key heavy marble base and dust cover orse key heavy marble base and dust cover orse key on a heavy marble base dueeze key heavy base required queeze key heavy base required 45/430 MHZ R.F. Thru-line watt meter, 120W 0 watt 3:5–500 MHZ dummy load 44/30 MHZ R.F. Thru-line watt meter, 200WBaluns BAU <b< td=""><td>2 element tri-band beam (mini) 10, 15, 20m 169-50 MV4BHR Vertical antenna 10 3 element tri-band beam (mini) 10, 15, 20m 230-00 SQ22 Double quad 144 Vertical antenna 10, 15, 20m 49-95 SQY06 Swiss quad/yagi 1 Vertical antenna 10, 15, 20, 40m 59-49 SQY06 Swiss quad/yagi 1 Vertical antenna 10, 15, 20, 40m 59-49 SQY06 Swiss quad/yagi 1 Flephands ATU 200W PEP 82-95 Pre-amps HF bands ATU 200W PEP 149-00 HRA-2 2m mast head pre- 10W 2m linear 0-5-3W input 39-99 144-50 Tokyo Wer 10W 2m linear 10W input 144-50 110W 2m linear 10W input 209-73 20W 70cm linear 10W input 152-77 3ch. 70cm handie 1 90W 70cm linear 10W input 152-77 3ch. 70cm handie 1 and morse key with A.B.S. base 13-67 Blauns and morse key with A.B.S. base 14-60 50 ohm-50 ohm 1 Dished brask key with weighted wooden base 2000 2 kw (cw) SA450N 2 way antenna sw 5M Suble brask key, haavy marble base and dust cover 18-60 5M</td><td>2 element tri-band beam (mini) 10, 15, 20m 169-50 3 element tri-band beam (mini) 10, 15, 20m 230-00 3 element tri-band beam (mini) 10, 15, 20m 230-00 Vertical antenna 10, 15, 20, 40m 49-95 Vertical antenna 10, 15, 20, 40m 49-95 SQY06 Swiss quad/yagi 144 mhz 6 element Wata Aru 200W PEP 82-95 HF bands ATU 200W PEP 82-95 HF bands ATU 200W PEP 144-50 HF bands ATU 200W PEP 144-50 HF bands ATU 200W PEP 144-50 100W 2m linear 10W input 144-52 100W 2m linear 10W input 144-52 100W 2m linear 10W input 144-52 100W 2m linear 10W input 152-77 20W 70cm linear 77-99 90W 70cm linear 10W input 156-77 90W 70cm linear 10</td></b<> | 2 element tri-band beam (mini) 10, 15, 20m 169-50 MV4BHR Vertical antenna 10 3 element tri-band beam (mini) 10, 15, 20m 230-00 SQ22 Double quad 144 Vertical antenna 10, 15, 20m 49-95 SQY06 Swiss quad/yagi 1 Vertical antenna 10, 15, 20, 40m 59-49 SQY06 Swiss quad/yagi 1 Vertical antenna 10, 15, 20, 40m 59-49 SQY06 Swiss quad/yagi 1 Flephands ATU 200W PEP 82-95 Pre-amps HF bands ATU 200W PEP 149-00 HRA-2 2m mast head pre- 10W 2m linear 0-5-3W input 39-99 144-50 Tokyo Wer 10W 2m linear 10W input 144-50 110W 2m linear 10W input 209-73 20W 70cm linear 10W input 152-77 3ch. 70cm handie 1 90W 70cm linear 10W input 152-77 3ch. 70cm handie 1 and morse key with A.B.S. base 13-67 Blauns and morse key with A.B.S. base 14-60 50 ohm-50 ohm 1 Dished brask key with weighted wooden base 2000 2 kw (cw) SA450N 2 way antenna sw 5M Suble brask key, haavy marble base and dust cover 18-60 5M | 2 element tri-band beam (mini) 10, 15, 20m 169-50 3 element tri-band beam (mini) 10, 15, 20m 230-00 3 element tri-band beam (mini) 10, 15, 20m 230-00 Vertical antenna 10, 15, 20, 40m 49-95 Vertical antenna 10, 15, 20, 40m 49-95 SQY06 Swiss quad/yagi 144 mhz 6 element Wata Aru 200W PEP 82-95 HF bands ATU 200W PEP 82-95 HF bands ATU 200W PEP 144-50 HF bands ATU 200W PEP 144-50 HF bands ATU 200W PEP 144-50 100W 2m linear 10W input 144-52 100W 2m linear 10W input 144-52 100W 2m linear 10W input 144-52 100W 2m linear 10W input 152-77 20W 70cm linear 77-99 90W 70cm linear 10W input 156-77 90W 70cm linear 10 |





STEP ELECTRONICS

FRG7 OWNERS ARE GOING — DIGITAL AND SIDEWAYS

And you can join them by using our custom designed DFC70 digital frequency counter. The DFC70 is specifically designed for the FRG7 and gives rock steady read out on all bands with 100Hz resolution. Signal frequency is computed and displayed unambiguously on a state of art LCD display specially made for us in Japan. It is not necessary to drill any holes and only one wire has to be connected to a well marked test point in the receiver.

With our new FM7 adaptor module, you will be able to receive sideways modulation (FM as it is otherwise known). Our superb state of art FM detector uses the very latest 3359 chip from Motorola, and has a built in IF filter and a variable squelch control for noise free monitoring. Although specially designed with the FRG7 in mind, it will happily work with other receivers or transceivers with a 455kHz IF amplifier. The FM7 will add a whole new dimension to your listening activities. You will of course be able to follow legal CB contacts but you will also hear the exciting DX being worked by amateurs on 10 metre FM. Used in conjunction with our DFC7 counter, you can accurately tune to a specific CB or amateur channel and so be sure that you will not miss whatever goes on. **Kit Price £9.95 Tested Module £14.95** P&P £1.00 (VAT inc.)

DFC70 Kit £19.95 Built and tested module £24.95 Kit Price

Will also work with the Lowe SRX30 and Drake SSR/1.

KIt Price £9.95 Tested Module £14.95 P&P £1.00 (VAT inc.) For FM reception on receivers with any IF up to 50mHz, the FM 42 is the answer to all your problems. *Please state frequency required when ordering*. KIt Price £14.00 Tested Module £19.00 p&p £1.00 (VAT inc.)

TIMOTHY EDWARDS MK2 144 MHz PRE-AMP HEAR IT LIKE YOU NEVER HEARD IT BEFORE

We are proud to announce that the well known RF consultant Timothy Edwards has given us the exclusive marketing rights to his new 2 metre pre-amp. Timothy Edwards RF designs are used by British Telecom amongst others and so you can be sure that this pre-amp will perform to perfection. It employs the incomparable BF981 which has a better noise figure at 2M than the often used 3SK88. Spec. Size (tiny) 34mm x 9mm x 15mm (same as Mk1) Noise figure 1.0db Gain 26db Kit Price £4.95 (inc VAT & P&P).

| TRANSISTOR 2 N6456 ^{mHz} 30 | PoutW Pin W Volts . Pri 60 1.25 13.8 £5 (i | | | |
|---|---|---|--|--|
| short wave receivers using common | nters that will cover up IFs. Similar to the FC1 Inge won't do what yo data. | COUNTERSto 200mHz and give 1KHz resolution to 39MHz. Ideal for most77 but cheaper! Supply voltage 5-15V dc. Will operate on 26u want probably nothing will. Works with all of Tony BaileyHz £18.50 kitDFC42 0-200MHz £21.95 kit | | |
| LWA144. OUR ace RF designer Timothy Edwards has done it again! In line 144MHz RF switched pre amp which needs no modification to any rig. Just put it in the co-ax feed, supply 12V and your deaf rx will have ear ache. Uses the BF981 with a total of 4 tuned circuits for the best out of band rejection. The relays are 500hm gas filled with earthed metal cans and are good to over 800MHz. This was originally designed for 'British Telecom Satellite Division' hence the provision for gold 14GHz SMC connectors. 1dB noise figure and 18dB gain is guaranteed to improve all standard rigs on 144-146MHz. Will fit in standard diecast box (not supplied). Try one in the car under a wing mounted aerial and be surprised. LNA144 kit £14.95. Built and tested module £24.95. | | | | |
| 70cm POWER AMPLIFIER At last a c power module by TRW the world lea Only 150mW input for a full 15 watt ou 430 to 440 MHz. Use with an attenuate or build a simple TV Transmitter with TRW MX15 £12.75 | ders in RF modules. tput all the way from or for your handheld | TOP BAND CONVERTER Listen to the other local nets and DX on 160m with any 2m SSB receiver. Does not need a large aerial and will comfortably out perform most commercial receivers. UC160 Kit £9.95 UC160 built and tested £16.50 | | |
| 2M MONITOR RECEIVER. A super crystal and ceramic filters coupled w BF981 results in an almost bomb pr channel with squelch and 500mW aud to wind and little alignment requi crystals from 'PM Electronics'. MON: and tested module £29.95. For p 18-200mHz built and tested module crystal. | vith the MC3359 and oof monitor. Single to amplifier. No coils red. Uses standard 2M Kit £19.95 Built rofessional use on | WHO IS TIMOTHY EDWARDS? He's 32, licenced for 14 years, was a senior design engineer at Pye Telecomm and now works full-time for Timestep. He's also responsible at Timestep for designing the synthesizers and down convertors for British Telecom used on the current ECS satellite system. He also specified and uses our new Spectrum analiser and signal generators costing over £40,000. Now you can see why our amateur modules always work properly and have full meaningful specifications | | |
| | | | | |

GAS FILLED RF RELAY

New Japanese 50 ohm low loss gas filled RF relay. Only 0.3dB loss at 430 MHz with 35 watts input. Ideal for switching pre-amps and the TRW MX15. BSWR 1.5:1 at 1gHz. 12 volt coil. **DR12V £4.75**

All prices include postage and VAT. Send 35p for individual data on any of the above. Mail order only. Please allow up to 28 days for delivery. TIMESTEP ELECTRONICS LTD, WICKHAMBROOK, NEWMARKET, SUFFOLK. TELEPHONE NO 0440 820040 TELEX 817015 TIMST G

UNION MILLS, ISLE OF MAN S.E.M. Tel: MAROWN (0624) 851277



S.E.M. FACT 9. If you 'phone your order with your credit card number, we can dispatch it the same day.

S.E.M. TRANZMATCH. The most VERSATILE Aerial Matching (Tuning) Unit available. Matches 15-5,000 ohms BALANCED or UNBALANCED feeders up to 1 KW. Air coupled BALUN (no toroids) means no connection to equipment, which can cure TV1 both ways. An SO239 and screw terminals for CO-AX, END FED or TWIN FEEDERS. Size Bit × 4* × 7½*, 3.5-30MHz £74, 1.8-30MHz £83. The highly acclaimed EZITUNE built in (see below) £29.50 extra. 90% we sell have the EZITUNE option. All Ex-stock.

NEW S.E.M. WAVEMETER. Have you read your licence? Have you got a wavemeter? Produced following so many requests. 1.5-30MHz in 3 switched bands with a very nice meter. Only £29.50.

S.E.M. IMABIC KEYER. No better fully auto keyer anywhere. Uses Curtis chip. R.F. proof. Sidetone etc. £38. A first class twin paddle key £17.50 Ex stock.

BRAID BREAKER/HI PASS FILTER. Stop TVI at TV. £6.50 Ex stock.

RF NOISE BRIDGE. Adjustable 0-1,000 ohms, $3^{"} \times 1^{J"} \times 2^{"}$ only. S0239s, 1-170MHz. Neat, accurate & economical. £34.50 Ex Stock.

3 WAY ANTENNA SWITCH IKw SO239s. Good to 2 metres. £17.50 Ex stock. Or 4th position to earth output £19.80 Ex stock.

S.E.M. 2 METRE TRANZMATCH. 51 × 2", 3" deep. SO239s. £24.90 Ex stock. S.E.M. EZITUNE. New circuit. Gives MORE noise & bomb proof operation.

Because no similar unit is made, it's usefulness is not appreciated until you have used one. Eliminates need for S.W.R. bridge.

Clean up the bands, increase your P.A. life by many times, by tuning up without transmitting.

Connects in aerial lead, produces S9 + (1 – 170MHz) noise in receiver. Adjust A.T.U, or aerial for minimum noise. You have now put an exact 50 Ohms into your transceiver. Fully protected, you can transmit through it, save your P.A. and stop ORM. SO239s. $3^{*} \times 1_{2}^{*} \times 2^{*}$ **£34.50 Ex stock.** P.c.b. + fixing + instructions to fit in TRANZMATCH or any ATU £29.50 Ex Stock.

SENTINEL 2M LINEAR POWER/PRE-AMPLIFIERS Feature either POWER AMP alone or PRE-AMP alone or both POWER AND PRE-AMP or STRAIGHT THROU when OFF. Plus a gain control on the PRE-AMP from 0 to 20dB. N.F. around 1dB with a neutralised strip line BF981.

Ultra LINEAR for all modes and R.F. or P.T.T. switched. 13.8V. SO239s.

Three Models: SENTINEL 35 Twelve times power gain. E.g. 3W IN 36W OUT. 4 amps. Max. drive 5W. 6" x 21" front panel, 41" deep. £65 Ex stock. SENTINEL 50 Five times power gain. E.g. 10W IN 50W OUT. Max drive 16W 6 amps. Same size as the Sentinel 35. £79.50 Ex stock. SENTINEL 100 Ten times power gain. E.g. 10W IN 100W OUT. Max. drive 16W. Size: 61" x 4" front panel, 31" deep. 12 amps. £115 Ex stock.

POWER SUPPLIES for our linears 6 amp £34. 12 amp £49.

SENTINEL AUTO 2 METRE or 4 METRE PRE-AMPLIFIER (R.F. Switched) 1dB N.F. and 20dB gain, (gain control adjusts down to unity) 400W P.E.P. power rating. Use on any mode. 12V 25mA. Sizes: 1¹/₂ × 2¹/₄ × 4⁴. **£29.50 • Ex stock**.

PA5 Same specification as the Auto including 240V P.S.U. £33.00 • Ex stock. SENTINEL 2 METRE PRE-AMPLIFIER. No R.F. switch. £15.00* Ex stock.

S.E.M. AUDIO MULTIFILTER (A very good filter at a very good price). The most versatile filter available. Gives "passband" tuning, "variable selectivity" and one or two notches. Switched Hi-pass, Lo-pass, peak or notch. Selectivity from 2.5KHz to 20Hz. Tunable from 2.5KHz to 250Hz. PLUS another notch available in any of the four switch positions which covers 10KHz to 100Hz. 12V supply. Sizes: 6" × 2]" front panel, 3]" deep, all for only £57.00 Ex stock.

SENTINEL AUTO H.F. WIDEBAND PRE-AMPLIFIER 2-40MHz, 15dB gain. Straight through when OFF, 9-12V. 24 × 14 × 3". 200W through power. £19.55* Ex stock.

SENTINEL STANDARD H.F. PRE-AMP. No R.F. switching. £12.62 * Ex stock.

S.E.M. VISA 80 METRE RECEIVER

A 1st class performance (3.5-3.8MHz) Rx. Only 2]" \times 6" \times 3". 12 volt operation. I.W. o/p. This is for you. £45 Ex stock.

12 MONTHS COMPLETE GUARANTEE INCLUDING ALL TRANSISTORS.

Prices include VAT and delivery. C.W.O. or phone your credit card number for same day service. *Means Belling Lee sockets, add £1.90 for S0239s or BNC sockets. Ring or write for more information. Place orders or request information on our Ansaphone at cheap rate times.

Goods normally by return.



DEALER ENQUIRIES INVITED

WOOD & DOUGLAS ~D

★ NEW Product ★ * 24 cms * ★ FM TV Downconverter ★

From reviews received already, from independent test sources this product is likely to become a market leader ... read on

1250 DC50

The 1250 DC50 is a completely self-contained 24 cms downconverter compatible with our 50 MHz video intermediate frequency processor demodulator. The module has facilities for remote tuning and AFC input. The full 24 cms TV allocation is covered with minimal loss in gain.

SPECIFICATION:

SPECIFICATION: Input frequency range: 1240-1325 MHz Intermediate frequency: 50 MHz nominal Local oscillator injection: 1190-1325 MHz Conversion gain: >25 dB; 30 dB typical First RF stage: MGF 1100 Ga As FET Mixer type: Discrete Schottky ring

Post mixer processing: SL560c amplifier Operating voltage: 11.5-14.0 Volts Operating current: 80 mA nominal Internal stabilisation: 8.5V; 5.5V rails External connections: AFC input Supply input Tuning voltage input 8.5V rail output

RF connections: BNC

Unlike the majority of our extensive product range this unit will not be available as a kit. The complexity of the circuitry demands a high level of instrumentation to allow correct alignment. Minor variations in assembly technique could also not be tolerated at such a high frequency. For these reasons we have reluctantly decided to modify our policy but would point out that the VIDIF for use with the above is available in either kit or assembled form.

Inclusive Price: £69.96

Place your order now for the 1250 DC50 or any of our product range by mail order or credit card. While our staff strive to give a return of post service please allow 28 days for any possible delay particularly on assembled modules. Our current catelogue is available by return of post on receipt of an A5 stamped addressed envelope. Please add 75p to your total order for postage and handling.

ANYONE CAN SELL A KIT... REPUTATION SELLS OURS UNIT 13, YOUNGS INDUSTRIAL ESTATE ALDERMASTON, READING RG7 4PQ TEL: (073 56) 71444 TX: 848702



| \star \star \star THE LEICESTER \star \star | * |
|---|--------|
| AMATEUR RADIO | |
| SHOW COMMITTEE | |
| $\star \star \star \star$ | |
| EXTEND AN INVITATION TO THE | |
| NATIONAL AMATEUR RADIO AND ELECTRONICS | |
| EXHIBITION | |
| AT THE | |
| GRANBY HALLS | 3 |
| LEICESTER | |
| ON | |
| FRIDAY & SATURDAY | S T |
| остовек 26тн & 27тн | A R |
| G 1984 | R A |
| ^{&} 10.00 ам – 6.00 рм | F F |
| U Y ENQUIRIES TO FRANK G4PDZ on 0533 553293 ★ ★ ★ ★ | L E |



Plain Language

THE FIRST STEP towards making the UK Amateur Radio Licence easier to understand was taken on September 10 when a new Schedule was published by the Department of Trade and Industry (see page 18 in this issue).

The new Schedule is not intended to change the basic licence conditions in any way, but simply to state clearly, and without the constant need to refer to numbered footnotes, what powers and modes may be used in each amateur band. It also aims to clear up several misunderstandings and anomalies, some of long standing, but mostly resulting from the revised emission codes adopted at the 1979 World Administrative Radio Conference.

We have not yet had time to study the new Schedule in depth, but a quick scan revealed the following points:

1. Footnote A clears up the question: "Can Class B Licenceholders send Morse using an automatic sender such as a keyboard?".

2. Footnote I, Note (b) should be useful for answering the occasional "Smart-Aleck" who enjoys asking questions like "What emission mode do I put in my log when I'm sending my callsign in speech at the end of a TV transmission?"

Although the WARC'79 emission code table gave the answer, the summary of those codes included in the Amateur Licence did not.

We understand that discussions between the DTI and the RSGB are continuing with a view to issuing a totally revised amateur licence, hopefully some time in 1985. The present licence, rather like Topsy, "just growed". The incorporation of the mobile licence and then the amateur TV licence into the main licence over the years has involved piecemeal alterations which mean that very, very careful reading of the licence as a whole is required for a full understanding of all the rules we amateurs should be obeying. The review now under way should clear up most of this confusion.

One point I hope they'll sort out is the difference between "telegraphy" as defined by the Radio Regulations (see the new Schedule) and "telegraphy" as in the Wireless Telegraphy Acts. The latter definition occupies almost a page in the 1949 WTA, but the important part is that it includes any wireless communication which "serves for the conveying of messages, sound or visual images" (Part III, 19. — (1) (a)). People who argue that the Wireless Telegraphy Acts don't apply to them when they're transmitting telephony (speech) had better try to think up a new excuse!

Whilst on the topic of definitions, the abbreviation ISM in the Schedule stands for "Industrial, Scientific and Medical", meaning the many uses which can be made of radio-frequency electromagnetic energy apart from radio communication and control. There are a number of frequency bands set aside internationally for the purpose, and other users of the same bands have to accept the limited-range interference generated by ISM equipment.

ervices=

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, "Practical Wireless", Westover House, West Quay Road, Poole, Dorset BH15 1JG, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components for our projects are usually available from advertisers. For more difficult items, a source will be suggested in the "Buying Guide" box included in each constructional article.

PROJECT COST

The approximate cost quoted in each constructional article includes the box or case used for the prototype. For some projects the type of case may be critical; if so this will be mentioned in the Buying Guide.

INSURANCE

Turn to the "News" pages for details of the PW Radio Users Insurance Scheme, exclusive to our readers.

CONSTRUCTION RATING

Each constructional project will in future be given a rating, to guide readers as to its complexity:

Beginner

A project that can be tackled by a beginner who is able to identify components and handle a soldering iron fairly competently. Generally this category will be used for simple projects, but sometimes for more complicated ones of wide appeal. In this case, construction and wiring will be dealt with in some detail.

Intermediate

A project likely to appeal to a wide range of constructors, and requiring only basic test equipment to complete any tests and adjustments. A fair degree of experience in building electronic or radio projects is assumed.

Advanced

A project likely to appeal to an experienced constructor, and often requiring access to workshop facilities and test equipment for construction, testing and alignment. Constructional information will generally be limited to the more critical aspects of the project. Definitely not recommended for a beginner to tackle on his own.

SUBSCRIPTIONS

Subscriptions are available at £13 per annum to UK addresses and £14 overseas, from "Practical Wireless" Subscription Department, Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. Airmail rates for overseas subscriptions can be quoted on request.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at £1 each, including post and packing to addresses at home and overseas.

Binders are available (Price £5.50 to UK addresses, £5.75 overseas, including post and packing) each accommodating one volume of *PW*. Please state the year and volume number for which the binder is required.

Send your orders to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 OPF. All prices include VAT where appropriate.

Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

The September 10 Schedule Revision

A new schedule to the amateur radio licence was introduced on 10 September 1984. This is the result of joint discussions between the Department of Trade and Industry and the Radio Society of Great Britain.

The new single-format schedule (the technical supplement to the licence which lists the frequencies amateurs may use, etc.) covers amateur radio operations of both Class A and Class B licensees. It has been designed with the needs of the user in mind and also clears up areas of misunderstanding. Operators will in future be able to see at a glance the frequencies they may use and their status (i.e. primary/secondary), the maximum power and the type of transmission permitted.

Two minor changes to the amateur licence are also being made. The first is to reflect the transfer of functions of the Radio Interference Service from British Telecom to the Department of Trade and Industry. In Clause 1(1)(a)(iii), reference to the "General Manager of the British Telecom Telephone Area" is deleted and replaced by "Manager of the Radio Investigation Service District".

The second change removes old Clause 1(2)(e) referring to Radio Teleprinter (RTTY) transmissions since this is now superseded by the new schedule. Old clause 1(2)(f), referring to the prohibition of offensive or indecent messages, becomes new Clause 1(2)(e).

THE SCHEDULE

For the sake of convenience, this schedule appears in an identical format in both the Class A and Class B licences.

| Frequency bands in MHz | Status of allocations in the UK to: The Amateur Service | The Amateur Satellite Service | Maximum power Carrier PEP | Permitted types of transmission |
|---------------------------|--|-------------------------------|------------------------------|--|
| 1.810–1.850 | Available to amateurs on a basis | | 9dBW 15dBW | Morse Telephony RTTY Data Facsimile SSTV Morse Telephony Data Facsimile SSTV |
| 1.850–2.000 | of non-interference to other services. | No allocation. | | |
| 3.500-3.800 | Primary. Shared with other Primary services. | No allocation. | | Morse |
| 7.000-7.100 | Primary. | Primary. | | Telephony RTTY Data Facsimile SSTV |
| 10.100-10.150 | Secondary. | No allocation. | 20dBW 26dBW | |
| 14.000-14.250 | Deleteren | Primary. | | |
| 14.250-14.350 | Primary. | No allocation. | | |
| 18.068–18.168 | Available to amateurs on a basis of non interference to other services. Antennas limited to horizontal polarisation, maximum gain OdB with respect to a half-wave dipole. | No allocation. | 10dBW — | Morse, A1A only |
| 21.000–21.450 | Primary. | Primary. | 20dBW 26dBW | Morse Telephony RTTY Data Facsimile SSTV |
| 24.890–24.990 | Available to amateurs on a basis of non interference to other services. Antennas limited to horizontal polarisation, maximum gain OdB with respect to a half-wave dipole. | No allocation. | 10dBW — | Morse, A1A only |
| 28.000-29.700 | Primary. | Primary. | 20dBW 26dBW | 1 |
| 70.025–70.500 | Secondary basis until further notice. Subject to not causing interference to other services. Use of any frequency shall cease immediately upon demand of a government official. | No allocation. | 16dBW 22dBW | Morse Telephony RTTY Data Facsimile SSTV |
| 144.0-146.0* | Primary. | Primary. | 20dBW 26dBW | |

(*See Footnote A opposite.)

continued ► Practical Wireless, November 1984

| Frequency bands in MHz | Status of allocations in the UK to: The Amateur Service | The Amateur Satellite Service | Maximum power Carrier PEP | Permitted types of transmission |
|---------------------------|--|---|------------------------------|---|
| 430431.0 | Secondary. This band is not available for use within the area bounded by: 53N 02E, 55N 02E, 53N 03W and 55N 03W. | | | |
| 431.0-432.0 | Secondary. This band is not available for use: a) Within the area bounded by: 53N 02E, 55N 02E, 53N 03W and 55N 03W b) Within a 100km radius of Charing Cross, 51° 30' 30"N 00° 07' 24"W. | No allocation. | 10dBW 16dBW e.r.p. e.r.p. | Morse Telephony RTTY Data Facsimile SSTV Television |
| 432.0-435.0 | | No allocation. | | |
| 435.0-438.0 | Secondary. | Secondary. | 20dBW 26dBW | |
| 438.0-440.0 | - | No allocation. | | |
| 1240-1260 | | No allocation. | | |
| 1260-1270 | | Secondary. | | |
| 1270-1325 | Secondary. | Earth to Space only. | | |
| 2310-2400 | | No allocation. | | |
| 2400-2450 | Secondary. Users must accept interference from the ISM allocations in this band. | Secondary. Users must accept interference from the ISM allocations in this band. | | |
| 3400-3475 | | No allocation. | | |
| 5650-5670 | Secondary. Secondary. Earth to Space | Secondary. Earth to Space only. | | |
| 5670-5680 | | | | |
| 5755-5765 | _ | No allocation. | | |
| 5820-5830 | | | | Morse |
| 5830-5850 | Secondary. Users must accept interference from the ISM allocations in this band. | Secondary. Users must accept interference from the ISM allocations in this band. Space to Earth only. | 20dBW 26dBW | Telephony RTTY Data Facsimile SSTV Television |
| 10000-10450 | Secondary. | No allocation. | 1 | Television |
| 10450-10500 | occontary. | Secondary. | | |
| 24000–24050 | Primary. Users must accept interference from the ISM allocations in this band. | Primary. Users must accept interference from the ISM allocations in this band. | | |
| 24050–24250 | Secondary. This band may only be used with the written consent of the Secretary of State. Users must accept interference from the ISM allocations in this band. | No allocation. | | |
| 47000-47200 | | | | |
| 75500-76000 | Priman | Primary. | | |
| 142000-144000 | Primary. | r mildiy. | | |
| 248000-250000 | | | | |

FOOTNOTES

A. Except in accordance with clause 1 (2) (c) (ii) holders of the Amateur Radio Licence (B) are not permitted to use frequencies below 144MHz nor may they use the type of transmission known as morse (whether sent manually or automatically).

Practical Wireless, November 1984

B. Definition of types of transmission and classes of emission permitted:

Under the ITU classification (see section I) emissions are designated by groups of three characters. The types of transmissions defined here are grouped according to the third character, that is the type of information being used. 1. **Morse:** Morse telegraphy intended for aural reception using any classes of emission ending in A, i.e. ******A.

Telephony: Telephony using any classes of emission ending in E, i.e. ******E.

Television: Television using any classes of emission ending in F, i.e. ******F.

This may only be used where indicated on bands above 430MHz and the station's callsign must be sent periodically using either morse telegraphy or telephony on the centre frequency of the video channel, as required by this licence.

 When using any of the following types of transmission the station's callsign must be sent periodically on the same frequency using either morse telegraphy or telephony.

Radio Teleprinter (RTTY): Automatic telegraphy using any classes of emission ending in B, i.e. ******B. This includes teleprinters using any CCITT recognised codes, and morse telegraphy intended for automatic reception.

Data: Data using any classes of emission ending in D, i.e. **D. The Radio Regulations require that transmissions between amateur stations in different countries shall be in plain language. Transmissions between UK amateur stations and those in different countries shall be restricted to using CCITT recognised codes (in plain language); this requirement also applies to transmission between UK amateur stations in all bands allocated to the Amateur Service on a secondary basis.

Facsimile: Facsimile using any classes of emission ending in C, i.e. ******C.

Slow Scan Televsion (SSTV): Television operating in a reduced bandwidth using any classes of emission ending in F, i.e. **F.

Simultaneous use of combinations of any of the preceding types of transmissions, e.g. Telephony and Data, are described as classes of emission ending in W, i.e. **W.

N.B. The symbol "*" when used in emission designators represents any appropriate symbol as defined in section I.

C. Maximum power levels refer to the rf power supplied to the antenna. These levels will be specified by carrier power. For emissions having a suppressed, variable or reduced carrier, the power shall be determined by the peak envelope power (p.e.p.) under linear conditions. For pulse emissions (P**) the mean power shall not exceed the p.e.p. specified on that band.

D. For frequency bands above 1GHz, since high intensities of rf radiation may be harmful, the following safety precautions must be taken: in locations to which people have access, the power flux density on transmit must not exceed the limits recommended by the competent authorities. (Currently, this limit is 10mW per square centimetre.)

E. The bands allocated to the amateur service at 3.5, 7.0, 10.1, 14.0, 18.068, 21.0, 24.890 and 144MHz may, in the event of a natural disaster, be used by non-amateur stations to meet the needs of international disaster communications in the disaster area in accordance with the Radio Regulations.

F. The bandwidths of emissions shall be such as to ensure the most efficient utilisation of the spectrum; in general this requires that bandwidths be kept at the lowest values which technology and the nature of the service permit.

Where bandwidth-expansion techniques are used, the minimum spectral power density consistent with efficient spectrum utilisation shall be employed.

However, whatever class of emission is in use, the bandwidth occupied by the intended emission shall be such that not more than 1% of the mean power of the transmis-

sion shall fall outside of the authorised bands. This 1% does not include the power contained in harmonic and spurious emissions.

G. The class of emissions, type P**, may only be used on bands above 1GHz.

H. **Primary, permitted and secondary services:** For the purpose of this licence, bands are allocated to the Amateur Service and the Amateur Satellite Service on a primary basis on the understanding that they cannot claim protection from harmful interference from any other authorised services. This applies equally to bands allocated on a secondary basis where stations of the Amateur Service and the Amateur Satellite Service are also required not to cause harmful interference to stations of a primary or permitted service to which frequencies are already assigned or to which frequencies may be assigned at a later date.

I. Designation of emissions:

The symbols used to designate the classes of emission have the meaning assigned to them in the Radio Regulations, International Telecommunication Union (Geneva 1982). The classification is specified by three symbols. The first denotes the type of modulation of the main carrier, the second the nature of the modulating signal(s), and the third the nature of the information to be transmitted.

FIRST SYMBOL

| TINGTSTINDOL | |
|--|-------|
| Type of modulation of main carrier. | |
| Emission of unmodulated carrier: | N |
| 2. Emission in which the main carrier is ampli | |
| modulated, including cases where sub-carriers angle modulated. | are |
| Double sideband: | Α |
| Single sideband, full carrier | н |
| Single sideband, reduced or variable carrier: | R |
| Single sideband, suppressed carrier: | J |
| Independent sideband: | В |
| Vestigial sideband: | С |
| 3. Emission in which the main carrier is angle modulat | ted. |
| Frequency modulation: | F |
| Phase modulation: | G |
| 4. Emission in which the main carrier is amplitud | le or |
| angle modulated either simultaneously or in a | pre- |
| arranged sequence: | D |
| 5. Emission of pulses. | |
| Unmodulated sequence of pulses: | Ρ |
| A sequence of pulses | |
| (a) modulated in amplitude: | К |
| (b) modulated in width/duration: | L |
| (c) modulated in position/phase: | M |
| (d) in which the carrier is angle modulated during | the |
| period of the pulse: | Q |
| (e) which is a combination of the foregoing of | or is |
| produced by other means: | V |
| 6. Cases not covered above, in which an emission con | sists |
| of the main carrier modulated, either simultaneously | |
| a pre-established sequence, in a combination of tw | vo or |
| more of the following types of transmission-ampli- | tude, |
| angle, pulse: | W |
| 7. Cases not otherwise covered: | Х |
| Note: Emissions where the main carrier is dir | ectly |
| modulated by a signal which has been coded into c | uan- |
| tized form (e.g. pulse code modulation) should | |

modulated by a signal which has been coded into quantized form (e.g. pulse code modulation) should be designated under 2 or 3. SECOND SYMBOL

Nature of signal(s) modulating main carrier

1. No modulating signal:

2. A single channel containing quantized or digital information without the use of a modulating subcarrier (excluding time-division multiplex):

0

3. A single channel containing quantized or digital information with the use of a modulating subcarrier (excluding time-division multiplex): 2

4. A single channel containing analogue information: 3
5. Two or more channels containing quantized or digital information: 7

6. Two or more channels containing analogue information: 8

7. Composite system with one or more channels containing quantized or digital information, together with one or more channels containing analogue information: 9 8. Cases not otherwise covered: X THIRD SYMBOL Type of information to be transmitted 1. No information transmitted: N

 2. Telegraphy—for aural reception:
 A

 3. Telegraphy—for automatic reception:
 B

 4. Facsimile:
 C

 5. Data transmission, telemetry, telecommand:
 D

 6. Telephony (including sound broadcasting):
 E

 7. Television (video):
 F

 8. Combination of the above:
 W

9. Cases not otherwise covered: X

a) In this context the word "information" does not include information of a constant, unvarying nature such as provided by standard frequency emissions, continuous wave and pulse radars etc.

b) For the purposes of this licence, modulation used only for short periods and for incidental purposes, such as identification or calling, may be ignored when calculating the emission designator.

c) For the purposes of this licence, Double Sideband emissions with reduced or suppressed carrier are included in the designation A**.

J. Interpretation:

Gain of an Antenna: The ratio, usually expressed in decibels, of the power required at the input of a loss free reference antenna to the power supplied to the input of the given antenna to produce, in a given direction, the same field strength or the same power flux-density at the same distance. When not specified otherwise, the gain refers to the direction of maximum radiation. The gain may be considered

-Benny

for a specified polarisation. The reference antenna is usually either an isotropic antenna or a half-wave dipole. The gains may be referred to as decibels relative to an isotropic antenna (dBi) or as decibels relative to a half-wave dipole (dBd).

Equivalent Isotropically Radiated Power (e.i.r.p.): The product of the power supplied to the antenna and the antenna gain in a given direction relative to an isotropic antenna.

Effective Radiated Power (e.r.p.) (in a given direction): The product of the power supplied to the antenna and its gain relative to a half-wave dipole in a given direction. By convention, e.r.p. is used below 1GHz, and e.i.r.p. above 1GHz: e.i.r.p. is $2 \cdot 1dB$ greater than e.r.p.

Mean Power (of a radio transmitter): The average power supplied to the antenna by a transmitter during an interval of time sufficiently long compared with the lowest frequency encountered in the modulation taken under normal operating conditions.

Carrier Power (of a radio transmitter): The average power supplied to the antenna by a transmitter during one radio frequency cycle taken under the condition of no modulation.

Peak Envelope Power (p.e.p.) (of a radio transmitter): The average power supplied to the antenna by a transmitter during one radio frequency cycle at the crest of the modulation envelope taken under normal operating conditions.

Telegraphy: A form of telecommunication which is concerned in any process providing transmission and reproduction at a distance of documentary matter, such as written or printed matter or fixed images, or the reproduction at a distance of any kind of information in such a form.

For the purposes of the Radio Regulations, unless otherwise specified therein, telegraphy shall mean a form of telecommunication for the transmission of written matter by the use of a signal code.

Telephony: A form of telecommunication primarily intended for the exchange of information in the form of speech.

Television: A form of telecommunication for the transmission of transient images of fixed or moving objects.

Facsimile: A form of telegraphy for the transmission of fixed images, with or without half-tones, with a view to the reproduction in a permanent form.

These licence conditions represent the situation in the UK. Frequency allocations may differ from the international allocations given in Article 8 of the Radio Regulations.



Practical Wireless, November 1984



A new four-day exhibition, tailored specifically for the electronics enthusiast, is to be held at the Royal Horticultural Hall, Victoria, London, between 8 and 11 November 1984.

Called "Leisuretronics", the event is being sponsored by *Practical Wireless*, *Practical Electronics*, *Everyday Electronics*, *Software Index* and *Electronics* & *Wireless World*.

In addition to stands devoted to amateur radio and associated equipment, other attractions will include:

DBS IF Recommendations

The May edition of *PW* carried an Editorial Comment on the choice of Direct Broadcast Satellite i.f. frequencies (see Ifs and Buts—p.17 *PW* May) and concluded that the then known choices of 950–1350MHz (first i.f.) and 134MHz (second i.f.) could well lead to interference problems from and to amateur band operations.

A recently received paper from BREMA (British Radio Equipment Manufacturers Association) recognises that extremely high power radar systems operate throughout Europe on approximately 1300MHz. The BREMA Interference Sub-Committee has therefore recommended that UK DBS setmakers avoid the use of frequencies below 1410MHz for the first i.f. in domestic products. However this statement is qualified by acknowledging that some products will use the lower "half-band" 950-1350MHz as components for the higher frequencies may not be readily available at the start of production.

On the choice of the second i.f. the sub-committee considered two questions

1) Is the use of 134-26MHz practicable in the presence of 144-146MHz amateur transmissions? 2) If the answer to this question is no, what alternative frequencies can be considered?

The worst hypothetical case considered was a 400W p.e.p. station, located 10m from a domestic DBS system (12GHz input signal from the Satellite down-converted to 1GHz at the antenna and feeding via coaxial home computers; satellite signalling equipment; radio control; robotics; video; electronic kits; audio; electronic music; tools and components etc., in fact just about everything to interest the electronics hobbyists.

On the Practical Wireless stand, we are hoping to run a special event station and display both past and future projects. Our technical staff will be manning the stand and we will also have available recent issues of the magazine, computer program tapes, copies of the popular *PW* publications and *PW* parabolic dishes.

Admission to "Leisuretronics" will be £1.50, and further details are available from the organisers; *Trident International Exhibitions Ltd., 21 Plymouth Road, Tavistock, Devon PL19 8AU. Tel: (0822) 4671.*

cable to an indoor second i.f. and demodulator unit).

The use of 134.26MHz for the second i.f. was confirmed to be suitable, assuming the wanted carrier power is at -57dBm at the input to the indoor unit; the unit is contained within a totally enclosed metal screening box. Further, the coaxial cable between the antenna/first i.f. converter and the indoor unit must be correctly terminated at both ends (using N type connectors or better-no compromise is possible) to reduce the vulnerability to spurious fields. The quality of this cable is critical and must provide immunity to 145MHz interference of at least 50dB (Likely to be achieved by using closeweave braid or tape/braid construction).

With regard to the second i.f. unit its input rejection of signals breaking through onto the down-lead cable must be at least 70dB at 145MHz relative to the first i.f.

What these recommendations amount to is the need for a very well engineered system, using high quality components, with attendant cost. Let's hope that the industry responds because if they do not, or imported equipment, using mass-produced ineffectively screened components, become established, the prospects for mutual interference on both 144MHz and 1296MHz look decidedly grim.

Insurance

Readers who are interested in applying to the *PW Radio Users Insurance Scheme* are advised to use the coupon published on page 18 of a previous issue.

Repeater News

Latest Proposals-soon to go to the DTI for consideration. 144MHz: GB3GD (R1), location Snae Fell, Isle of Man. As previously reported this unit could have initiated the implementation of 12.5kHz channel spacings for UK repeaters. However, following negotiations between the RMG and the Anglo-Scottish Repeater Group it has been decided that GB3AS will change channel to RO, leaving GB3GD to occupy the vacated channel, thus avoiding potentially widespread cochannel problems, a fine example of inter-group co-operation which should benefit all users in the North West. If the callsian rings bells with you don't worry because until now GB3GD had been allocated to the up and coming Data repeater at Leicester. However, it was agreed by all that the relevance of the Callsign was too good to miss and so the Leicester unit will operate under the Callsign GB3RY.

432MHz: Six proposals for u.h.f. repeaters will soon be passed to the DTI including: GB3AN—Anglesey (RB4); GB3DC—Sunderland (RB11); GB3LF—South Lakeland (RB14); GB3LR—Lewes, East Sussex (RB11); GB3NW—Hendon, North West London; GB3OV—Huntingdon. Final channel details of the last two devices are yet to be determined.

In addition to the above, two 1-3GHz f.m. repeaters will also be proposed.

Boost for SETI

During the next two years NASA's SETI (Search for Extraterrestrial Intelligence) programme will receive a great boost when a system capable of scanning millions of channels simultaneously is brought on line. There are so many frequencies and so many directions from which any intelligent beings could try to send signals to us that the task of picking them out seems almost impossible. There have been about 45 searches for extraterrestrial signals from beings in outer space during the past 20 to 30 years, but no convincing evidence has vet been found.

Paul Horowitz, a Harvard physicist, is conducting one of the most extensive searches using a radio telescope 26 metres in diameter, but says he can scan 'only' 128 000 different channels at any one time and that this is a very small fraction of the many millions of possible channels where one might expect to find signals from the cosmos.

BD

Catalogues

The new 160 page Toolmail catalogue has been expanded and contains an even larger range than ever before. A really comprehensive selection of over 3500 items all fully illustrated in colour with technical details. Also included is a large range of products for electrical and electronic work.

Toolmail's policy is to sell only top quality tools and most items in the catalogue come from established and reliable British and European manufacturers.

Most of the items are held in stock, allowing Toolmail to dispatch orders, usually within 48 hours of receipt. There is no charge for p&p on orders over £30 and a no quibble guarantee is offered on all items.

The catalogue costs £1.50, including postage, and on orders over £20 a £5 discount voucher can be used. To obtain a copy, apply to: *Toolmail (1982) Ltd., 7 London Road,*

Will Flat Antennas Replace Dishes?

The well-known parabolic dish antennas are almost universal for concentrating the signals received from satellites; like the mirror of an astronomical telescope, the dishshaped reflector concentrates the high frequency waves into a microwave horn near the centre of the dish.

However, work at the Weizmann Institute could make the conventional dish antenna a thing of the past. The research team there has used electromagnetic theory to analyse the operation of flat microwave antennas printed on dielectric surfaces. They expect their flat, wafer-thin antennas will replace many of the dish antennas and horns in current use for communica-



Sevenoaks, Kent TN13 1AH. Tel: (0732) 455252 and 452020.

Cricklewood Electronics Ltd., the telephone and mail order component specialists, have their latest catalogue available.

This useful 32 page catalogue lists all the products stocked by Cricklewood, and is obtainable for 40p plus an s.a.e., from: *Cricklewood Electronics Ltd., 40 Cricklewood Broadway, London NW2 3ET. Tel: 01-452 0161 and 01-450 0995.*

tions with satellites and aircraft as well as for television reception.

The Weizmann group believe that the compactness and low cost of the flat antennas together with their low weight will make them attractive for many communications purposes. They claim a further advantage is the ability to mount these antennas on curved surfaces.

The work is currently involving the development of complex mathematical models for forecasting the antenna properties for flat and for cylindrical shaped surfaces. This approach is expected to lead to considerable simplification in the design of the optimum conductor surface in the thin flat antennas.

Can You Help?

A reader has a "Koyo—11 Band" portable communications receiver that has developed a fault and he would dearly like to obtain a circuit/service manual for it.

Unfortunately, we at PW have no knowledge of the receiver, which covers l.w., m.w., s.w.(\times 5) and four v.h.f. bands.

If you can help, please contact: David Townsend, Staff House 2, Grange OPH, Staverton Road, Daventry, Northants.

9L1FTN 28MHz Beacon

The summer edition of Hamster, the journal of the Cheshunt & District Amateur Radio Club, contains a report of the successful construction by members of the group of a new 28MHz beacon now active from Sierra Leone.

Located 400 m.a.s. at Kortright, Mount Aureol, Freetown (08°30'N, 13°2'W) the beacon is in an area frequently subjected to thunderstorms and much effort went into the provision of "spike" protection, valuable help being provided by the M.O. Valve Co (GEC) in terms of advice and gas-filled surge arrestors. The beacon, whose callsign 9L1FTN can be heard on 28-27250MHz, employs a vertical $\lambda/2$ antenna and F1A keying at 12 w.p.m. with a 20-second interval. Due to the intermittent nature of the local mains power, the unit will automatically revert to 12 V d.c. indicating this state by sending up to 8 "dits" before the callsign (corresponding to battery charge state).

Reports which will be acknowledged by special QSL card are welcomed by the group and should be addressed to Roger Frisby G4OAA (QTHR) or G4ECT via the QSL bureau.

TRANSCANADA EXPEDITION

2¹/₂ year crossing of Canada via Hudson Bay and the North-West Territories needs volunteers to run U.K. and Canada communications stations. Must have full Radio Operator's Licence. The purpose of the Expedition will be to travel between the Indian tribes and the Innuit (Eskimo) people, studying local culture, habitat and wild life. This will be recorded in a unique photographic documentary, in stills and film, to broaden man's understanding of his natural world and to aid education and science.

Applicants apply to:

Stewart Holmes, TransCanada Expedition, 'The Studio', 41 Moorhouse Road, London W2 5DH. Telephone: 01-727 7220.



Part 3 by Gordon J. King T.Eng(CEI), AMIERE, G4VFV

Without delving too much into the mathematics of the progression and bringing in the component of radiation resistance (see later), a useful formula for determining the signal voltage across a loaded antenna in a given signal field is:

$$V_{a} = \sqrt{\left(\frac{R_{a}G_{a}G_{d}}{120}\right)\frac{\lambda}{\pi}\frac{Z_{L}}{Z_{a}+Z_{L}}E}$$

where V_a is the loaded antenna signal voltage, R_a the antenna's radiation resistance, G_a the gain of the antenna relative to a dipole, G_d the gain of a dipole relative to an isotropic radiator, λ the signal wavelength, Z_a the feed impedance of the antenna, Z_L the impedance of the load and E the signal field in V/m.

Let's take R_a as 73 ohms (which is close to the centre feed impedance of a half-wave dipole), G_a as unity, G_d as our previously established 1.635, the frequency as 98MHz, Z_a and Z_L both as 73 ohms (assuming correct matching from antenna to load) and E as 100μ V/m, and use a pocket calculator to secure the answer. I came up with 48.57 μ V. I expect you got close to this, too, provided you didn't forget to convert 98MHz to 3.06m! Now, let's suppose that the antenna is coupled to the receiver through 24m of coaxial cable whose attenuation at 98MHz is 5dB per 30m.

The signal is thus reduced by a factor of 0.63 (5 \times 24 \div 30 = 4dB corresponding to a voltage ratio of 0.63), so the receiver signal would be

$$48.57 \times 0.63 = 30.6 \mu V$$

You would obtain a similar answer from the basic formula of:

$$V_a = \frac{G_a A_f}{2} E$$

which assumes that both the receiver load and the antenna have impedances of 73 ohms and where in this case G_a is the voltage gain of the antenna and A_f the voltage attenuation of the feeder, both in direct ratios (not dB). The first formula, however, is the more versatile as it lends itself to greater scope of calculation.

Improving Receiver Signal

The result is a miserable signal, so what can be done to give the receiver more signal? You could, of course, shift the antenna into a stronger signal field, or, indeed, raise its height since, as will be recalled from Part 2, the spacewave field increases proportionally with antenna height. Not possible? Okay so gain an extra 2dB by using lowloss coaxial cable. You have done that? Well, the only other possible thing is to use an antenna of higher gain. You will remember that the calculation was based on an antenna of unity gain relative to a dipole. If you use a directional antenna of 6dB gain you will double your signal voltage at the receiver.

We are now getting down to the nitty gritty of antennas, but right now I would like to show you one or two important things about antenna couplings and radiation resistance. The fundamental type of resonant antenna is the half-wave dipole whose voltage/current distribution is shown in Fig. 3.1(a) and whose equivalent circuit is shown in (b).

The Dipole and its Couplings

The voltage/current distribution alters at frequencies above and below resonance, and that shown is at resonance where the current along the antenna can be regarded as sinusoidal. As revealed at (b), the antenna constitutes a distributed tuned circuit, containing inductance, capacitance and resistance, which makes it more like a transmission line than an ordinary kind of "lumped" tuned circuit. It is tuned to the signal by adjusting its length; but because the effective capacitance per unit length is greater at the edges a dipole appears to be electrically longer than its physical length.





Let us suppose that we wish to tune the antenna to 100MHz, which is 3m. The half wavelength is thus 1.5m but the physical length for resonance is around 5 per cent shorter than this-the precise length is influenced by the length/diameter ratio of the conductor-making it close to 1.425m. Velocity factor can thus be regarded as 0.95 which holds when the length/diameter ratio is around 200. You can now cut your own f.m. dipole at a frequency in the middle of Band II and it would be broad-band enough not to deviate too much from resonance at band extremes. Bandwidth increases as the length/diameter ratio falls.

Fig. 3.1(a) shows maximum current and least voltage at the centre and maximum voltage and least current at the ends. This means that the impedance is lowest at the centre of the antenna, the value being nominally 73 ohms, though this can vary above or below depending upon height. It can be as high as 98 ohms at 1m above a perfectly reflecting earth. Anyway, the centre impedance corresponds favourably to the characteristic impedance of f.m. and TV coaxial cable. We can thus achieve a relatively low-loss coupling by cutting the antenna at the centre and connecting the coaxial cable across the two points, usually aided by an insulator as shown in Fig. 3.2. Although the centre feed point of a dipole is symmetrical (balanced) and coaxial asymmetrical (unbalanced) a reasonable coupling is still attained, though for optimum results balanced feeder or, better, a balun (short for balanced-tounbalanced) at the coupling point can be used.

Transmission Lines

I must now show you the secrets of the transmission line and its behaviour at high frequencies. Consider an infinite length of line into which a short pulse is launched. The pulse will travel along the line and, under certain conditions, retain its shape. Now, if you put a short across the line the pulse will be reflected back from the short to the launching point. If instead of a short the line is terminated with a resistor the pulse will be absorbed and there will be no reflection when the value of the resistor is the same as the characteristic impedance of the line. The characteristic impedance is determined by the spacing of the conductors, their dimensions and shape, but is independent of frequency. When any practical length of line (i.e. less than infinite) is terminated by a resistance corresponding to the line's characteristic impedance (Z_o) then the line's input impedance also corresponds to Zo. This is what you aim to do when coupling your receiver through the feeder to the antenna-the antenna's impedance is close to Zo as also is the antenna input of the receiver. The correctly matched condition is then obtained.

A feeder (transmission line) possesses distributed inductance along its length and distributed capacitance between its conductors along with the inevitable resistance of the conductors and the leakage resistance between them. For a finite line without losses the characteristic impedance is given by:

$$Z_o = \sqrt{\frac{L}{C}}$$

where L is the inductance in henrys and C the capacitance in farads.

If a short line is not correctly terminated-end shorted or open-circuit-the input impedance swings, over wide limits, as a function of the frequency of signal and the



length of line. $\lambda/4$ is commonly used for impedance matching and balancing, about which more will be told later when we deal with antenna phasing and so forth. For the time being Fig. 3.3 gives you an idea of the effects of a $\lambda/4$ line (a) when the end is shorted, (b) open-circuit and (c) when correctly matched, while Fig. 3.4 shows the voltage and current distribution and the standing waves which result from non-matching.

Radiation Resistance

At resonance the dipole current and voltage are phase coincident and the centre impedance is equivalent to 73 ohms of pure resistance, which is the radiation resistance (R₁). When shorter than resonance the centre feed-point swings capacitive with the resistive component falling below 73 ohms.



When longer than resonance the centre feed-point swings inductive and the resistive component becomes larger than 73 ohms. These effects are illustrated in Fig. 3.5. For optimum operation the reactive component of the impedance must be minimal and R_r shoud be as high as possible.

Indeed R_r determines the amount of signal an antenna can receive, and as we shall see for a "long wire" m.f. antenna which is shorter than resonance by its very nature, it needs to be as long as feasible to retain a viable value of R_r and endow it with reasonable efficiency.



Fig. 3.5

When resonant and coupled to the receiver through coaxial cable of the correct Z_o which also corresponds to the antenna input impedance, a dipole is an efficient collector of signal in its own right. We may require more gain by adding extra elements but we shall see about that later, along with directionality. Under ideal matching conditions the losses are essentially those in the coaxial cable itself, these increasing with frequency.

VSWR and the Bugs of Mismatching

We must now see what happens if the antenna system is not correctly terminated and matched. Let's suppose that the antenna is off-tune or the receiver's antenna input different from Z_0 . If the mismatch exists at the receiver the signal will be reflected back up the cable to the antenna. A mismatch at the antenna will cause some loss (albeit small) of signal coupling to the feeder, while a mismatch both ends will cause the signal returned up the cable to be reflected back again so as to arrive a small fraction of a second after the main signal at the receiver. This can affect the quality of stereo f.m., something like multipath, depending on the length of feeder and its intrinsic attenuation factor.

A mismatch thus evokes standing waves on the feeder (see Fig. 3.4). The ratio of maximum to minimum voltage along the cable is called the Voltage Standing Wave Ratio (v.s.w.r.). The Reflection Coefficient (p) is expressed:

$$p = \frac{v.s.w.r. - 1}{v.s.w.r. + 1}$$
(direct ratio)

while the Return Loss is:

$$r.l. = 20 \log (dB)$$

From these, therefore, we can discover the Power Loss (p.l.) from any v.s.w.r. using the formula:

p.l. = 1 -
$$\left[\left(\frac{1}{10} \right)_{antilog} \right] (dB)$$

This may appear to be a bit complicated but it is a useful formula for it can tell you how much signal power you will lose when there is a mismatch.



As an example, suppose that the mismatch results in 1.5:1 v.s.w.r., p would work out to 0.2, r.l. to 13.98dB and p.l. to a mere 0.177dB, which means that the power loss is only 4 per cent, the system thus working at 96 per cent efficiency. Even with a v.s.w.r. of 3:1 the p.l. is only 1.249dB, so I think people do tend to get unduly hot under the collar about a small v.s.w.r. due to a minor mismatch at the receiver or antenna. Some CBers and even amateurs go almost crazy if they find their v.s.w.r. around 2:1. It is virtually impossible to secure a perfect match, anyway, and the matching will alter with frequency—but, of course, you should always aim for the best possible match. To save you the toil of arithmetic the graph in Fig. 3.6 expresses the p.l. over a wide range of v.s.w.r.

MF and HF Antennas

A modest length of wire or rod will respond to the radio signals around us and yield a very small signal voltage as the result of the flow of signal current. On the long and medium wavebands the antenna will almost certainly be shorter than resonance. This means that its R_r will be low and its efficiency poor. The R_r of this type of antenna can be expressed as:

$$R_r = 80\pi^2 \left(\frac{1}{\lambda}\right)^2$$

where 1 is the effective length of the wire or rod and λ the wavelength of the signal being tuned. Let's say, then, that



Practical Wireless, November 1984



we are working at 1MHz (300m) and that the antenna is a vertical 4.57m conductor with the termination point at its lower end. Doing another little sum with your calculator you will find that R_r comes out to a mere 0.1832 ohm.

It is also possible to find the reactive component of the impedance which, of course, is capacitive (see Fig. 3.5) and works out, in fact, to -12.9×10^3 and thus corresponds to 2.900 ohms. One way of coupling the signal to the receiver and a good one to boot, is by loading the bottom of the antenna with an inductor having a value which cancels the capacitive reactance, leaving essentially Rr. In principle, this is what happens when a simple antenna is connected to a certain type of m.w. receiver, its internal antenna coupling taking the place of the inductor. To achieve resonance the antenna's capacitive reactance (X_c) needs to equal the inductive reactance (X_L) , we are then left with R_r plus inductor and conductor losses. In this case X_c would be close to 55pF and X_L close to 460 μ H. If you work out the resonance of these two you will find it falls close to 1MHz! Frequency at resonance (f_o), incidentally, is equal to:

$\frac{1}{2\pi\sqrt{LC}}$

where fo is in Hz, L in henrys and C in farads.

You would find out what the antenna signal would be in a given signal field by using the full formula in the section under Antenna Voltage, but this G_d is 1.5 (gain relative to an isotropic radiator). This is because in this case the antenna length is much shorter than the wavelength. The basic coupling is shown in Fig. 3.7.

CB Antennas

A similar loading arrangement is required by law for CB antennas. Maximum length of the radiating element is 1.65m while the wavelength of Channel 20 is 10.794m (27.79125MHz). Clearly, the antenna is significantly less than $\lambda/2$ and about 1m short of $\lambda/4$. It thus needs to be loaded by bottom inductance to combat the capacitance of the shortened monopole, as shown in Fig. 3.8. The recently revised specification for CB antennas allows the length to be up to 1.65m and the diameter to be 55mm, both dimensions to include any loading coils which can be placed anywhere along the antenna. Ground planes are excluded from these dimensions.

Actually, the antenna is resonated to correspond to a shortened $\lambda/4$ monopole with the earth plane making up the missing $\lambda/4$ part of a dipole (see Fig. 3.8). Design is based on $Z_0 = 50$ ohms, this impedance value being applicable to the feed point of the antenna, the coaxial cable and the antenna input/output of the transceiver. The antenna is named after Marconi as distinct from the dipole which is named after Hertz. Fig. 3.9 shows the basic principle where the earth effectively mirrors the missing $\lambda/4$ section. The Marconi antenna resonates in its own right, but when shortened for CB use requires a loading coil to counter the feed point capacitive component of the impedance. For CB the loading coil also serves as a low-pass filter, thereby helping to attenuate the radiation of harmonics which might otherwise cause interference to radio, TV and other services.

CBers are permitted to use a maximum r.f. input to the antenna of 4W (average carrier power). The e.r.p. is -



generally below this owing to the antenna limiting requirements of the Home Office. Nevertheless, with a competently designed antenna 2W e.r.p. can be achieved. Radiated power can be expressed as:

$$\frac{R_r \times W_1}{R_r + R_d + R_e} \text{ (watts)}$$

where R_r is the radiation resistance, W_1 watts of r.f. from the transmitter, R_d the r.f. resistance of the loading coil and R_e earth plane resistance and other losses. Taking R_1 as 7.6 ohms, R_d as 3 ohms and R_e as 4 ohms, then with 4W r.f. input the radiated power would be around 2.1W, giving an input/output efficiency of about 52 per cent. It is possible to achieve even greater efficiency while still keeping in the legal requirements as witnessed by tests I have made when the ground plane is more elaborate and less "lossy" and the loading coil is well designed.

Car Antennas

Car antennas for broadcast reception on the l.w./m.w. bands constitute a short rod. They are closer to resonance at v.h.f. f.m. where the metal body of the car can help with loading. Coupling is shown in Fig. 3.10 where nonterminated coaxial cable is used. Resistive loading would greatly impair the signal, so the capacitance of the cable is included as part of the input circuit of the receiver. There is also usually a trimmer in the radio to peak the antenna tuning at the top of the m.w. band.



27



Car CB antennas are the same as already described but the ground plane consists of the metal body of the car, and good results are possible from a well fitted mobile CB system.

Home MF and HF Antennas

For long and medium wave reception the ferrite rod antenna is now mostly used; but sometimes there is merit in employing the old type of "long wire" antenna consisting of a horizontal span (say 9m) and a vertical down-feed (say 4.5m). Current is induced in both sections, but the horizontal section certainly enhances the signal collection. A wall-mounted vertical rod can also be relatively efficient if mounted high on a chimney stack clear of electrical interference.

Such an antenna, however, is often best fed into suitably ratioed transformers with balanced screened cable between as shown in Fig. 3.11. This prevents the pickup of interference on the downlead.

For h.f. work a tuned antenna becomes possible, such as a centre or end-fed dipole, and this is much the best way to secure good reception on short waves. There are hosts of different antennas which can be used but, sadly, there is just insufficient space here to investigate them. Design, however, is based on the tuning of antennas as already detailed.

Ferrite Rod Antenna

This type of antenna is a development of the loop antenna which many years ago was commonly used in socalled portable radios. The loop, however, is still used for certain applications. With a ferrite rod the air within the loop is complemented by a core of ferrite of very high permeability with respect to that of air, which is unity. Core material for the l.w./m.w. bands is commonly a nickel-zinc ferrite of permeability ranging between 200 and 500 and the design is such that at these frequencies eddy current losses are remarkably small. Because of the high permeability and low losses the loop (which is now a coil) can be of small diameter, allowing the antenna to be mounted -



Fig. 3.14 ►

Max response WRM215

easily at the rear of the tuner or inside the cabinet of a small radio.

The antenna works by concentrating the magnetic field of the radio wave along the ferrite rod and hence through the coil as shown in Fig. 3.12 and the coil is tuned and coupled to the first stages of the receiver as shown in Fig. 3.13. Compare this with Fig. 3.7.

Although one or two arrangements have been mooted for v.h.f. f.m. ferrite rod reception, no receivers that I know of have yet been marketed with a v.h.f. ferrite rod antenna. The permeability falls off and the losses increase at frequencies much above 10MHz, though a special material which works up to about 100MHz has been developed, so perhaps we shall see f.m. tuners with inbuilt ferrite rod antennas one day.

Because it is sensitive only to the magnetic component of the radio wave, the ferrite rod antenna is directional, having deep nulls when the ends are pointing to the station and maximum pick up when broadside on. This makes it possible to adjust the position to minimise interference, the polar pattern being figure-of-eight, as shown in Fig. 3.14, the same as a horizontal dipole.

This leads us to the reason why we use a horizontal dipole for v.h.f. f.m. reception. At one time the urban skyline was cluttered by vertical TV antennas in numerous configurations. Now, of course, our TV antennas are that much smaller because they are tuned to the shorter wavelength of the u.h.f. channels, but instead of being vertical their elements are horizontal, as those of v.h.f. f.m. antennas. Why, then, are some antennas vertical and others horizontal? You will have to wait until Part 4 to find the answer.

-Kindly Note

Simple Top-Band Receiver—June 1984

The p.c.b. track pattern and component overlay contained two errors in the region of the LM380 amplifier (IC2). An amended track pattern and overlay for the affected area is shown below. If you have a p.c.b. with the wrong track pattern it can still be used simply by adding a wire link between IC2 pin 14 and R22 (+12V) and another between IC2 pins 2 and 3. It is not necessary to modify the connection to pin 13 as this is already disconnected internally.



Practical Wireless, November 1984

TERS

18/20 MAIN ROAD, HOCKLEY, ESSEX. Tel: (0702) 206835 12 NORTH STREET, HORNCHURCH, ESSEX. Tel: (040 24) 44765

| TRIO | |
|--------------------------------|---------|
| | |
| TS930S HF Tcvr | |
| AT930 ATU | |
| SP930 Speaker | |
| TS430S HF Tcvr | |
| PS430 AC psu SP430 Speaker | |
| AT250 ATU | |
| MB430 Mobile Unit | |
| FM430 FM mod | |
| TS830S HF Tcvr. | E7E9 00 |
| VF0230 VF0 | |
| AT230 ATU | |
| SP230 Speaker | |
| TS530SP HF Tcvr. | 6669.00 |
| VEO240 VFO | |
| TS130S HF Tcvr | £576.00 |
| TL120 200w 1in | |
| MB100A Mobile mount . | £19.50 |
| SP120 Speaker | £29.00 |
| SP140 speaker | £14.90 |
| AT130 ATU | £98.00 |
| PS20 PSU | |
| TL922 2kw | £950.00 |
| TS780 2m/70cm | £850.00 |
| TR9130 2m Tcvr | £458.00 |
| BO9A base | £49.50 |
| TR7930 2m Tcvr | |
| TW4000A 2m/70cm | |
| TR2500 2m h/held | |
| VB2530 30w amp | |
| ST2 charger | |
| SC4 Case | |
| MS1 | £33.90 |
| SMC25 Speaker/Mic | |
| PB25 nicad | |
| LH2 case | |
| BT1 AA case | |
| DC25 12v TR3500 70cm h/held | £17.00 |
| TM401A 70cm | |
| TM201A 2m | |
| SP40 speaker | |
| R600 Rx. | £272 00 |
| R2000 Rx | |
| VC10 VHF conv. | £117.00 |
| YK88C 500Hz | £35.47 |
| YK88CN 270Hz | £39.50 |
| YK88SN 1.8kHz | £33.35 |
| MC50 mic | £32.90 |
| MC60/S6 mic | £59.50 |
| MC80 mic | £39.00 |
| MC42S mic. | £16.00 |
| MC55 Mobile Mic | £39.95 |
| LF30A LPF | £22.49 |
| HC10 Clock | |
| DM81 GDO | £75.40 |
| | |

TRIO

YAESU

| FT1 HF Tx/Rx | .£1,569.00 |
|-------------------|------------|
| FT980 HF Tx/Rx | |
| SP980 Speaker | £61.50 |
| FT102 HF Tx/Rx | |
| FC102 ATU | £185.00 |
| SP102 Speaker | £55.00 |
| FM/AM | |
| FT77 HF Tx/Rx | £479.00 |
| MRKT77 marker | £10.85 |
| FP700 PSU | £145.00 |
| FC700 ATU | £103.85 |
| MMB16 Mount | £14.49 |
| FT757GX HF Tx/Rx | £719.00 |
| FC757AT ATU | |
| FP757GX PSU | £145.00 |
| FP757HD PSU | £179.00 |
| FL2100Z amp | £599.00 |
| FT290R 2m Tx/Rx | |
| FT790R 70cm Tx/Rx | £259.00 |
| | |

| NC11 charger | £10.55 |
|---------------------|---------|
| NC nicads | |
| CSC1A case | |
| YHA/5 Ant. | |
| MMB11 Mount | |
| FL2010 amp | |
| FT208 2m h/held | |
| FT708 70cm h/held . | |
| NC9C charger | |
| FNB2 pack | |
| PA3 12v | |
| MMB10 | |
| FT203R 2m h/held | |
| MH-12A2B mic | |
| MMB21 bracket | £8.00 |
| FT230R 2m 25w | £269.00 |
| FT730R 70cms 10w . | £239.00 |
| FT726R 2m | £775.00 |
| 430/726 | £259.00 |
| 144/726 | £165.00 |
| 50/726 | £195.00 |
| SAT726 | £99.95 |
| FRG7700 Rx | £385.00 |
| FRG7700M Rx | £455.00 |
| MEMO | £75.00 |
| FRT7700 | £48.25 |
| FRA Ant. | £43.95 |
| FF5 LPF | £11.25 |
| FRV7700E | £94.25 |
| YM24A mic | £22.50 |
| MH-1B8 | £15.70 |
| YD148A mic | £25.25 |
| | |

ICOM

| IC751 HF Tx/Rx | |
|----------------------------------|-----------|
| ICPS35 PSU | £149.00 |
| IC745 HF Tx/Rx | £839.00 |
| IC730 HF Tx/Rx | £659.00 |
| PS15 PSU | £119.00 |
| ICR70 Rx | |
| ICR71 Rx | |
| FL45 filter | £45.00 |
| FL63 filter | |
| IC2KL 1kw | £1,349.00 |
| IC271E 2m base | |
| IC271H 2m 100w | |
| ICPS25 PSU | |
| IC290D 2m 25w | |
| IC471E 70cm base | |
| IC490E 70cm | |
| ICO2 2m h/held | |
| | |
| ICO4 70cm h/held HM9 spkr/mic | £16 50 |
| LC3 case | |
| LC11 Case | |
| BP3 nicad | |
| BP4 AA | |
| BP5 | |
| DC1 12v | |
| | |

| £39.90 |
|-------------|
| £22.40 |
| £13.70 |
| £27.40 |
| |
| E State Sta |
| |

| PM144-1-100 | £172.50 |
|--------------|---------|
| PM144-3-100 | £172.50 |
| PM144-10-100 | £149.40 |
| PM144-25-160 | £207.00 |
| PM144-3-180 | £235.75 |
| PM144-10-180 | £235.75 |
| 2/25A PSU | £138.00 |
| 2/40A PSU | £276.00 |
| | |

| | | | / |
|----------------------------|----------------|---------|-----|
| | FDK | | |
| 1725X 2m 2 | 5w | £239 | .00 |
| 4750XX 2m | | | |
| XP430 70cm | | | |
| almcomm I | ll 2m h/he | ld £135 | .00 |
| ATC720 AM | | | |
| RX40 FM Rx | | £142 | .00 |
| | WELZ | | |
| | VVELZ | | - |
| SP200 1kw | | | |
| SP300 1kw | | | |
| SP400 150w | | | |
| SP10X 200w | | £28 | .75 |
| SP15M 200w | | | |
| SP45M 100w | | | |
| P250 2kw | | | |
| SP350 200w | | | |
| AC38 ATU | | | |
| CA-35A prote | ector | £12 | .75 |
| T15A 50 wa | att | | .95 |
| CT150 400 w | | | |
| T300 1kw | | | |
| H20A switc | | | |
| H20N switc | | | |
| OF72C duple | | | |
| RS455 4a PS RS655 6a PS | | | |
| S1100 11a | | | |
| RS1150D 11a | | | |
| RH2B whip . | | | |
| RH200B whip | | | |
| RH702B whi | | | |
| M285 whip . | P | E 10 | 05 |
| M287 whip . | | | |
| wild will . | ************** | E 1/ | .50 |

....£19.95

£17.50

£32.50

£35.75

£10.75

..£2.95

£15.25

£9.95

£23.95

£43.50

£38.00

£49.00

£95.00

£133.00

£69.00

£89.00

TONNA

EL770E whip ... B285 2m base ..

GH22 2m base

SPM Magnetic

EL80 HF whip ..

EL40 HF whip

CP3 vertical

CP4 vertical

CP5 vertical

KB101 vertical

KB105 vertical

GLS gutter . GLP SO239

TRB.

LOR

GH72 70cm base

| 20505 50mHz | £33.15 |
|---------------|--------|
| 20104 144mHz | £14.95 |
| 20109 144mHz | £17.70 |
| 20209 144mHz | £20.00 |
| 0118 144mHz | £32.40 |
| 20113 144mHz | £31.00 |
| 20117 144mHz | £37.60 |
| 20419 430mHz | |
| 20438 430mHz | £34.00 |
| 20421 430mHz | |
| 0422 435mHz | |
| 20199 Oscar | £34.20 |
| 20623 1296mHz | £25.90 |
| | |
| | |

ROTATORS

| AR200XL VHF | £47.50 |
|-----------------|---------|
| CDEAR40 HF/VHF | £105.00 |
| 9502B VHF | £59.50 |
| 9523 bearing | £19.75 |
| KR400RC HF | £121.50 |
| KC038 clamps | £12.65 |
| KS065 bearing | £21.50 |
| KR500 elevation | £131.85 |





H I I I I

Spend £25 or more with us during October (exhibitions, shop or mail order) and we'll refund your entrance fee on production of ticket stub.

> Un-interrupted coverage from 26MHz to 520MHz AM & FM. This is the most so-Un-interrupted phisticated monitor we have grammable steps, superb image rejection, etc. etc. 12v DC operation. Optional mains power supply.

AOR 2001_MONITOR 26MHz-550MHz

The diminutive AOR 2001 is the ideal portable or base station monitor. Small enough to fit in a vehicle, it provides no gap coverage from 26MHz to 550MHz. The 69

usual scanning and memory facilities are included and power requirements are 12v DC or 230v AC with the mains adaptor module (included in price).

EB

Take one of these fine Philips AM/FM porta-bles (MW + 88-140MHz) free with every order for SX400 or AOR 2001, Ofextends throughout October.





ATC 720 **RX40** FDK M.750XX 2M SSB-CW-FM 42000 £349

-

The M.750XX must be one of the best buys in VHF amateur radiol its highly sophisticated circuitry and low price represent extraordinary value that many hundreds of customers have already taken advantage of. Full coverage from 144 to 148MHz. FM-SSE-CW makes this ideal for base or mobile use. Its power 20 watts output matches its highly sensitive receiver so that for DX work it's superb. Equally effective for cross town chats, the extra sharp FM filters ensure minimum adjacent channel inter-ference whilst providing good clean transmitted audio. And if CW happens to be your choice, there is a built-in monitor. Add to this the 70cms expander option and you'll see that the M.750 provides remarkable value.

(All orders despatched MAIL ORDER SLIP same day)

To:- Waters & Stanton 18-20 Main Road, Hockley, Essex. Name

Address

Items required

Carriage:- Items under £10-£1.00; Over £10-£1.50; Larger aerials £6; Securicor £6.

| A Control of the second | abile 488.00 Trio R2000 310.00 Trio VC-10 VHF conv. 279.00 Yaesu FRG 7700M with 265.00 Yaesu FRG 7700 with 246.00 Yaesu FRG 7700 antien 279.00 Yaesu FRG 7700 with 246.00 Yaesu FRG 7700 antien | v. Rx. 1195.00 v. Rx. 779.00 758.00 669.00 576.00 719.00 576.00 719.00 576.00 719.00 649.00 649.00 565.00 479.00 117.00 for R2000 117.00 for R2000 for R | ANTENNA BITS Hi-Q Balun 1:1 5kW PEP WAU Unadilla 4:1 Balun 7.1742/128 MHz Unadilla traps - pair Self amalgamating Tape 10m × 25mm 50 Mtrs 16 swg hand drawn copper wird 7-piece Polyprop. Dipole centre Polyprop Strain insulators 8 mall ceramic egg insulators 9 ohm Twin Feeder - Jern metre UR76 50 ohm coax per metre UR76 50 ohm coax per metre UR76 50 ohm coax per metre MATO ohm coax per metre MATO 10 ohm coax per | 1.50 (0.40) 0.55 (0.10) 0.75 (0.10) 0.75 (0.10) 0.75 (0.10) 0.41 (0.04) 0.65 (0.20) 0.25 (0.05) 0.30 (0.05) metre 0.16 (0.04) £ C&P 134.00 (1.50) 75.00 (0.75) 24.95 (−) HMOUND - AKD |
|--|---|--|---|---|
| R.W TRANSCEIVERS RECEIVERS | We are authorised Yaesu agents £279 (RWC listen input mod in also agents for Icom, FDK and F | s and we can supply the <i>fu</i> cluded), <i>FT757</i> £719 , <i>F</i> | ·清·《书·································· | F7290 D. We are |
| ANTENNAS | AS We are agents for Jaybeam – Tonna – Revco – Bantex – A.R.M. plus our own well established range of HB9CVs for 2m, 10m and 70cm from £5.99 . Tonnas from £17 . Jaybeam from £5.98 and the Revco discone from £29.95 . We carry a large stock of antennas both base and mobile. | | | |
| ACCESSORIES | As we are authorised agents for Yaesu, Icom, FDK and Revco, we can supply the <i>full</i> range of matching accessories for all these products. E.g. atus, psus, swr meters, dummy loads, antenna switches, rotators etc. Ask about our free accessories with new transceivers. | | | |
| EXCLUSIVE OFFERS | Revco RS 2000 scanner – 3 versions a tinuous coverage 1. Standard model 2. 60–179MHz & 380–520MHz 3. 60-520MHz continuous (post, packing and insurance | £259 New LCL/I £271.50 Modified a £299 with repea | IVERSIONS omplete with instructions for LCL/DNT £12 NT unmodified rigs nd complete | £33 £47.50 |
| SERVICE FACILITIES | your disposal. For instance, are you sure the Tx power output. Harmonic content, spectre | hat your radio is working correctly? T ral purity, Frequency, FM deviation (o 50. We will also undertake to do sin | e in excess of £20,000 worth of test equipmore o find out just bring it along to us and we vor or AM modulation), Receiver Sensitivity (SIN aple jobs on the spot but please telephone er Modules direct from Japan. | will check the NAD) etc, etc. |
| Lombard Tricity Finance | MON, SAT 8:30–5:30 LATE NIGHT T Secondhand lists available/part excl STOCK ITEMS NORMALLY DELIVER Overseas customers welcome, we s Telex: 334303 TXAGWM/G | hanges welcome ED WITHIN 7 DAYS | DAD WEST, OLDBURY, WARLEY (QUINTON, BIRMI Fel: 021-421 8201/2 (24 HR ANSW S.A.E. with all enquir | INGHAM) ERPHONE) |
| C Designed and manufactured in Brit | Black × Star | Sine, Square, Triangloutput Typically 0.02Hz - 7 7 switched ranges wit coarse and fine frequency controls ± 30V output capab JUPITER 500 Colour leaflet with the start to (Den) | range 700kHz * Variable DC off th * External A.M. f jency * External sweep * Short circuit pr | ally 1% of fset facility facility otection Ex-stock 28.80 Delivery from: yes. |

BATTERY STATE INDICATOR by J. Talbot G4AYV

The author owns several pieces of battery operated equipment and because no visual indication exists that the supply is on, quite often, it would be forgotten at the cost of what are, these days, expensive batteries.

The Battery State Indicator serves not only to provide the user with an indication when the battery needs replacement within a particular piece of equipment, but acts as a low power pilot light, drawing only about six to nine hundred microamps when set up correctly.

The unit comprises an 8211 micro power sensor i.c. which, when driving an l.e.d. direct, would consume 7mA from its own internal constant current source. Of course for many batteries, this consumption when added to that of the equipment would soon exhaust them. One way to overcome this problem is to pulse the l.e.d. as this is the item that draws practically most of the current, the quiescent state being about 60μ A. Even when pulsed at a slow rate the indication is as outstanding, if not more so, than a continuous light emission. Using this principle with the values given, a consumption of about 600μ A average was achieved with reasonable brightness. It should be pointed out that high brightness l.e.d.s consume more than ordinary types so are less suitable for this type of application.

Circuit

The pulser itself is formed by two inverters, gates c and d of IC2 wired as an astable, R3 and C2 governing the pulse rate. Each pulse acts as an enable signal to gates b and c of IC3. The 8211 contains an accurate voltage



Fig. 1: Circuit diagram Practical Wireless, November 1984 reference comparator as well as a pair of output buffers and as mentioned provides 7mA current limited output. Originally a Schmitt trigger was used to detect the voltage threshold but hysteresis proved a problem so the idea was given up in favour of the 8211 which does not have this problem, the transition being very sharp. The output of this device changes state when the sensed voltage reaches a level pre-determined by R2. In the high state IC1 turns on gate b of IC3 whilst in the low state gate c is turned on through an inversion at gate a of IC3.

For different voltages the current limiting resistor R5 had been made variable and should be adjusted for acceptable brightness commensurate with low current consumption.

It should be stressed that all unused gates should be tied to ground as is good practice, otherwise instability and higher current consumption will occur.

Construction

A printed circuit board layout is shown in Fig. 2 although the design could be built on Veroboard if required. A maximum voltage of 18 volts should not be exceeded without modification otherwise damage to the c.m.o.s. devices will occur.

***** components

| Resistors | | |
|------------------------|--------|---------------|
| 1 W 5% carbon film | | |
| 470Ω | 1 | R6 |
| 47kΩ | 1 | R1 |
| 1MΩ | 1 | R4 |
| 22MΩ | 1 | R3 |
| Miniature horizontal p | re-set | in the second |
| 10kΩ | 1 | R5 |
| 470kΩ | 1.5 | R2 |
| Capacitors | | |
| Polyester | | |
| 10nF | 1 | C3 |
| 0·1µF | 1 | C1 |
| Polycarbonate | | |
| 0-47µF | 1 | C2 |
| Semiconductors | | |
| Diodes | | |
| Red 0.2in I.e.d. | 1 | D2 |
| Green 0.2in I.e.d. | 1 | D1 |
| Integrated Circuits | | |
| 4011 | 2 | IC2, |
| 8211 | 1 | IC1 |
| | | |

Miscellaneous

Printed circuit board; Sockets for i.c.s.





Fig. 2: Full-size p.c.b. layout and copper track pattern for the battery state indicator. The unit is wired across the battery after the on-off switch, so acting as a pilot lamp as well

Construction of the board is straightforward, but note that IC2 and 3 are c.m.o.s. devices, and that the appropriate handling precautions must therefore be taken. Sockets should be used for both devices; they should be left in their anti-static packaging until they are to be fitted onto the board; they should be handled as little as posssible; they should not be fitted onto the board until it is complete in all other respects. Make sure that all the integrated circuits are fitted onto the board the right way round, and don't forget the link adjacent to R6.

To set up the circuit, simply connect a variable voltage to supply wires and adjust to the voltage at which transition from green to red is required. Now adjust R2 until this just happens. The unit is now set and ready for use.

Without switching off, the circuit has run now for several weeks on a 6-F22 (PP3) battery—the threshold having been set to 7.5V.



BEGINNER





New 934MHz Equipment

Telecomms of Portsmouth have recently introduced a comprehensive series of 934MHz CB accessories from the Nevada Communications range. Four different vertical colinear antennas are listed, all with 7dBi gain, and configured for base station, mobile, mag mount and mobile gutter mounting.

The base station PA7-E is less than 1.5m long but incorporates an array of $5\lambda/8$ radiating elements to achieve good gain with attendant low angle radiation. Construction is of chromed steel with the radiating elements fully shrouded in glassfibre. An N-type r.f. socket is built into the base.

The HPS-900 Power/s.w.r. meter has a low insertion loss and is therefore suitable for continuous in-line monitoring (N-type connectors are fitted). The meter movement incorporates twin needles to continuously indicate the outgoing power level and system s.w.r. Internal illumination is provided by a 12V lamp and the unit is robustly constructed within a metallic case.

For increased receive capability the HRA-900 GaAs-f.e.t. masthead preamplifier should provide very effective results. Quoted specifications include a gain of 15dB (minimum) and a noise figure of 0.8dB (maximum). The device is supplied within a plastics/stainless steel enclosure with N-type socket connectors and a remote switched d.c. supply lead. (Supply requirements 13.8V at 200mA.) Two coaxial relays are incorporated, permitting the unit to handle up to 50W of r.f.



The photograph above shows most of the Nevada range of products and below is the Cybernet 934MHz CB transceiver

In the near future Telecomms will be marketing an all-new Cybernet 934MHz transceiver which has been developed in Japan. The basic transceiver has been designed to allow variants to be compatible with several other 900MHz CB and PMR systems, now becoming available throughout the world. We hope to have a review of this interesting equipment in a future issue. The UK version has 20 channel capability and will be readily expandable to 40 channel operation (when available).

As a guide to pricing of these products (all include VAT), the PA.7 base colinear version costs £59.00 and the mobile variations all cost £39.95. The HPS-900 power/s.w.r. meter costs £89.95 and the HRA-900 masthead pre-amp £149.95. As for the Cybernet 934MHz transceiver, the rig should be available in quantity shortly after this issue is published and will be priced at £325, once again including VAT.

For further details, contact: Telecomms, 189 London Road, Portsmouth. Tel: (0705) 662145.



Preset ATU for 144MHz

Traditionally radio amateurs have relied on the antenna pruning method to improve the v.s.w.r. of 144MHz mobile antennas. However, Davtrend Ltd., of Gosport, have come up with a new solution—the Drae preset antenna tuning unit, which when placed between antenna and transceiver, gives optimum performance for any given situation.



Terminated in U.H.F. sockets, type SO-239, the 30 watt, 50 ohm unit is priced at £11.80, which includes VAT and p&p. Full technical details and tuning instructions are included.

The Preset ATU is obtainable from: Davtrend Ltd., Sanderson Centre, Lees Lane, Gosport, Hampshire PO12 3UL. Tel: (070 17) 20141.

Microwave Dish Feed

Mike Walters, G3JVL is now producing a 10GHz waveguide feed designed to be fitted to the PW Exe 450mm parabolic dish. The feed is based on the original concept of G4ALN but has an additional 3 point spider support assembly. A standard waveguide 16 flange is fitted to directly connect to microwave systems. If required the feed can be supplied ready fitted to the dish. Also available are a range of interdigital and waveguide filters and versions of the image recovery mixer for both 5.7 and 10GHz. Further details: stamped addressed envelope to: *JVL Electronics, 26 Fernhurst Close, Hayling Island, Hants PO11 ODT or Tel:* 07016-4482.

If you please

Please mention this column when applying to manufacturers or suppliers featured on this page.


Low Cost Function Generator

One of the latest products from the Black Star stable is a British-made low cost function generator with 30V output.

Entitled the Jupiter 500, it is a rugged mains operated instrument that offers features unique in its price range, such as full programmability of both amplitude and frequency by external voltage, plus exceptionally high output voltage of up to 30V peak-to-peak.

The frequency range covered is 0.1Hz to 500kHz via seven switched decade ranges with fine frequency control. Sine, square, triangle and t.t.l. (30 loads) waveforms are selectable, and an adjustable d.c. offset up to 15V can



be applied to the output.

Supplied with a comprehensive instruction manual and spare fuse, the Jupiter 500 sells in the UK at £110.00 plus VAT, and is available from: *Black Star Ltd., 9A Crown Street, St. Ives, Huntingdon, Cambridgeshire PE17 4EB. Tel: (0480) 62440.*

Talking Frequency Meter

WPO Communications announce the re-introduction of the Talking Frequency Meter for the visually handicapped amateur radio enthusiast.

Designed specifically to assist blind radio operators in determining their transmit frequency, the unit may also be used for any of the applications a visually displayed frequency counter could be put to.

The unit covers the frequency range 500kHz to 150MHz (minimum) in two ranges, with resolution of 100Hz between 500kHz and 40MHz, and 1kHz

between 20MHz and 150MHz.

Via the built-in speaker, the speech quality is claimed to be good, and the meter also features either manual or automatic repeat operation, with selectable two, four or six digit groups of figures spoken. Additionally, the new unit has improved sensitivity at h.f., reverse polarity plus input protection. The Talking Frequency Meter requires an external 12V d.c. power source and is supplied ready-built and tested.

Priced at £179, which includes VAT and carriage, the Talking Frequency



Meter is available from: WPO Communications, 20 Farnham Avenue, West Sussex BN6 8NS. Tel: (079 18) 6149.

Versatile Cleaner

The abrasive properties of the ends of a tightly packed bundle of glass fibre strands are surprising. Gunson's Speedplate Glass Fibre Cleaning Pencil utilises this considerable cleaning power in a neat, propelling pencil type holder.

For the electronics enthusiast this cleaning aid will prove most useful preparing metal surfaces, component leads and p.c.b. tracks prior to soldering, particularly where space is restricted as the tip of the pencil can get into nooks and crannies that other abrasives cannot reach and be efficient without causing damage to surrounding components.

As an additional bonus, the pencil's other uses are almost endless: removing rust spots on painted metal; clearing out screw threads or typewriter keys; buffing up small metal parts—in fact, hundreds of small

Practical Wireless, November 1984



cleaning and polishing jobs.

The Speedplate Glass Fibre Cleaning Pencil costs around £1.75, comes complete with two refills and full instructions for use, and is available from the d.i.y. departments of major stores, and from motorist accessory shops like Halfords.

Please Note!

A number of our advertisers have asked us to advise readers that the prices of imported products are likely to change from month to month.

The reason behind these changes is fluctuating international exchange rates. So, readers are therefore advised that they would do well to check prices with suppliers prior to sending off orders.

Modifying The FRG-7



by Peter D. Rouse GU1DKD Part 3

The next constructional project in this series based around the FRG-7 receiver is for an f.m. adaptor and all-mode squelch. Although the two circuits were specially designed for the FRG-7, certain allowances have been made so that they should happily marry-up to other receivers. The printed circuit board layout has been configured in such a way that it will fit on to the stand-off panel described in the previous part for the switched filter unit.

Before going any further it is perhaps worth mentioning why it is desirable to fit the f.m. facility. Quite simply there is now an increasing amount of f.m. traffic on the shortwaves particularly at the h.f. end of the spectrum. In addition to the UK CB service between 27.6 and 28MHz there is now an increasing amount of f.m. use in the 28MHz amateur band. Readers familiar with f.m. operation will know that background noise under no-signal conditions, is very high and so it is essential to have some kind of muting or squelch control to turn off the audio when no signal is present. However, such a control is also a useful feature with a.m. operation as well and it was with this in mind that the two circuits were adopted rather than the more familiar method of a separate f.m./i.f. stage with its own squelch limited to f.m. use only.

Design Considerations

At this stage it is also worth mentioning why a separate f.m./i.f. was not considered as many will argue that a properly designed limiting i.f. amplifier would have given better performance. Indeed, two such circuits have been tried using Motorola and Plessey communication f.m. i.c.s and they have worked very well. However, they have also been far costlier and more complex than the circuit presented here. The biggest problem has been designing stable layouts to cope with the high gain and wide bandwidth of such i.c.s, they have had to have their own filters and buffers to prevent loading of the low level signal at the final conversion mixer.

Comparisons made between these circuits and the one finally chosen have shown only a very marginal difference in performance. The likely explanation for this would seem to be that when using the FRG-7 at a fixed location with a reasonably good antenna system the conditions are nowhere near as demanding as when operating mobile with problems such as flutter. In the latter instance the separate i.f. stage would possibly offer superior performance. The same argument applies to some extent to the choice of carrier operated squelch instead of deviation muting. Whilst this may not be ideal for f.m., it is simple, it works and its operation can be extended to other modes, in particular a.m. and f.s.k.

Circuit Operation

The f.m. stage is centred around YIC1 and just a few other components. It uses the TA7130 which is not an i.f. stage but merely an active demodulator. Although the i.c. is rarely seen in constructional projects, it is often found in equipment made in the Far East and appears extensively in CB equipment. It is inexpensive and readily available from a number of suppliers including advertisers in *PW*.

Signal for this stage is picked-off the FRG-7 final i.f. transformer, T405 at its junction with C427, C428, Q406 and R404. The signal is then fed via YC2 to pin 1 of the TA7130(YIC1). Transformer YT1 is the quadrature coil and can be almost any 455kHz i.f. transformer but preferably a low-Q first stage one. With some transformers that have a higher-Q it will be necessary to dampen the coil by fitting resistor Ry. Provision has not been made on the p.c.b. for this resistor but it can easily be soldered directly to the pins of YT1 on the underside of the board. The value of the resistor can be determined by trial and error but will probably be somewhere between $10k\Omega$ and $39k\Omega$, whichever gives the best audio.

Demodulated audio appears at YC8 via YR9 from pin 7 of YIC1. The squelch stage is a fairly standard and familiar one often seen in communications equipment. It consists of an untuned i.f. amplifier, detector stage, Schmitt trigger and switched audio amplifier. The common emitter transistor, YTr1, the diode detector stage YD1, YD2 via YC3. The very high gain of this stage ensures that the d.c. that appears at the junction of YD1, YR5, swings as high as 7 volts on a strong signal and this gives the squelch a high degree of sensitivity.

Transistors YTr2 and YTr3 form a conventional Schmitt trigger which, because of the shared emitter resistor, exhibits a very positive toggling action. Resistor YR5 together with YR7 form the biasing network for YTr2 and under no-signal conditions, YR5 is set so that YTr2 is turned off which turns YTr3 on. When YTr3 is on, the audio amplifier YTr4 is turned off via YR13 and so will not amplify the audio signal appearing via YR17/YC10.



However, an incoming signal will cause more current to appear at the base of YTr2, it will start to turn on and in doing so will start to switch YTr3 off, continuing until the Schmitt action causes a definite switching. As a result, YTr4 is turned on and the audio signal is amplified and fed back to the FRG-7 volume control via YC12.

Several other points should be noted about the circuitry. Resistor YR5 is a log control operated in reverse and the value of YR6 ensures that best use is made of the log taper. If you have carried out the previous modifications then the old volume control will be ideal for this application. If not, note that a linear control can be used although the value of YR6 will have to be adjusted to bring the nosignal turn-off point to about 30 per cent of the track. Another feature concerns the capacitor YC9. Although the Schmitt trigger has sufficient hysteresis to stop it from chattering on marginal signals, this capacitor has been included to slug the switching rate of YTr4 and so soften the switching thump associated with this type of circuit.

The final point concerns the divider network YR12/17 which determines the amount of audio fed to YTr4. The values shown are optimised for the FRG-7 but if the unit is to be fitted to a receiver that needs extra audio gain, these values can be adjusted accordingly by increasing YR12 and reducing YR17.

Construction and Fitting

A p.c.b. layout is given in Fig. 3.2, and this board matches the earlier one for the switched filter unit and fits the same stand-off panel. There is however no reason why other methods should not be adopted. Circuit layouts are not critical and the only point to watch is that there should be fairly short leads around YIC1. There is also, of course, no reason why only one of the circuits should be built. Assuming the circuit board is being fitted to the FRG-7, the logical way to switch f.m. will be to include it on the mode switch in the position occupied by the automatic noise limiter (a.n.l.). In the author's view the a.n.l. is not very effective anyway. The a.n.l. connection is on the outer wafer of the mode switch and it is only necessary to break one bridging link between two tags and connect the f.m. audio as shown in Fig. 3.3.

Once the tap-off point for the i.f. has been located, connection to the board should be made with a short piece of miniature coaxial cable.

Refer again to Fig. 3.3 and locate the audio coaxial cable which runs from the mode switch to the volume control. Disconnect this at the volume control and connect it to the a.f. input of the squelch. Use another piece of coaxial cable to connect the squelch output back to the volume control.

The problem now arises as to where to fit the squelch control. If you are using the old volume control then the easiest way round this is to remove the RECORD socket, widen the hole slightly and fit the control here. The RECORD socket leads can be extended and this facility resited on the back panel next to the loudspeaker socket.

Should you need to buy a potentiometer then a suitable miniature one is available from the Alps range stocked by Cirkit (formerly Ambit International) who also have control knobs to fit the 6mm shafts of these components.

Finally it only remains for the circuit to be connected to the 10 volt stabilised supply available in the FRG-7.

Setting-up and Testing

Assuming all connections have been checked, switch on the receiver and select f.m. Transformer YT1 must now be



| * | co | m | p | or | e | nt | S |
|---|----|---|---|----|---|----|---|
| - | | | | | | | - |

Resistors

| W 5% Carb | on film | |
|-----------|---------|----------------|
| 100Ω | 1 | YR1 |
| 390Ω | 1 | YR10 |
| 1kΩ | 4 | YR3, 6, 12, 16 |
| 2.2kΩ | 2 | YR4, 9 |
| 5.6kΩ | 1 | YR15 |
| 10kΩ | 3 | YR8, 11, 17 |
| 15kΩ | 1 | YR14 |
| 22Ω | 1 | YR7 |
| 100kΩ | 2 | YR2, 13 |

Logarithmic potentiometer (reverse) 10kΩ 1 YR5

Capacitors

| 100pF | 1 | YC2 |
|-------|---|-----------|
| 270pF | 1 | YC1 |
| 10nF | 3 | YC3, 6, 7 |
| 47nF | 1 | YC4 |

| 1µF | 3 | YC8, 10, 12 |
|-----------|--------|-------------|
| 10µF | 1 | YC5 |
| 22µF | 2 | YC9, 11 |
| 100µF | 1 | YC13 |
| Semicondu | ictors | |

| Diodes | | |
|---------------|---------|--------|
| 1N4148 | 2 | YD1, 2 |
| Transistors | | |
| BC109 | 4 | YTr1-4 |
| Integrated Ci | ircuits | |
| TA7130 | 1 | YIC1 |

Miscellaneous

Printed circuit board; i.f. transformer YRCS11098AC; miniature coaxial cable.



Fig. 3.3: Connection details for the new board to the FRG-7

peaked and the easiest way to do this is to find an f.m. transmission and trim it for the loudest and clearest audio output. In most areas a good source of f.m. transmissions is the UK CB service. Find a relatively weak signal and adjust YT1 for the best signal to noise ratio. Do not be surprised if some of the signals sound distorted, in the author's experience many CBers use badly adjusted accessories such as power microphones and echo boxes. However, if distortion is a persistent problem then refer to the section dealing with resistor Ry.

If all is well with the f.m. stage now test the squelch. There should be a definite switch-off point with no signal and it should be found that with the squelch set to just off, even a signal that does not register on the S-meter should open the squelch "gate". If problems are encountered, check with a voltmeter that there is a definite voltage

swing at the "hot" end of YR5 when tuning through stations. The i.f. signal level at the last transformer of the FRG-7 is sufficiently high that the squelch/demodulator circuit has no noticeable loading effects. It should therefore not be necessary to re-trim T405 but if any effects are noticed it might be worthwhile adjusting the core and seeing if this cures the problem. With other receivers it may be necessary to make such adjustments and indeed if loading effects are marked it may be necessary to reduce the values of YC1/YC2, although this will de-sensitise both the f.m. and squelch circuits.

Once all is working, it only remains for the controls to be suitably marked. The neatest solution is to use white 3mm rub-down lettering on small strips of grey card and lightly stick these over the words AM/ANL and RECORD.

Operating

Several of these demodulator/squelch boards have been built by the author and all are working well. The only operating points worth noting concern the squelch. This should be set carefully to the switch-off point as going beyond that will make the receiver deaf to all but the strongest signals.

There is no reason why the squelch should not be used on virtually any of the short wave bands although on the lower frequencies it will be found that QRM and QRN spikes are likely to trigger it.

One useful area where the squelch can be used to good advantage is when receiving RTTY, the control can be set so that the audio blocks at the end of the transmission so stopping the terminal from clattering on background hash.



Have 1937 HMV model 540AC cabinet radiogram, 1953 Marconi T19A table radio, both in good order. Also have Celestion UL8 40W speakers. Would exchange for Olympus OM10, Fuji STX, Minolta SRT 100 or Rotel/Akai stereo deck. Schomburgk, 2 Duchess Close, Whitchurch, Reading RG8 7EN. Tel: Pangbourne 3181. V999

Have Yaesu FRG-7 complete with Amtech 200 a.t.u. and 144MHz converter, also Codar AT5 60-180 metre TX with p.s.u. All in v.g.c. Would exchange for 144MHz transceiver. Jeff G6ZGU. Tel: 01-439 6512 (day) 01-803 5235 (evenings). Note NOT QTHR. *WO01*

Have Microwave Modules RTTY to TV converter and IC-2E with charger, ICBP3, BP4, DC1, HM9, LC3. Would exchange for FT-290R/MuTek, Sinclair 48K Spectrum. Tel: 0277 354378 (Essex). W002

Have Pentax K1000 camera, 50mm, 28mm, 135mm Pentax series M lenses, DOI 7-element 2x converter. All immaculate boxed condition plus cases. Would exchange for R1000, R600, FRG7700 or similar direct readout receiver. Tel: 01-309 1295. W012

Have SBE Opti/scan model 12SM, Eddystone 358, Grundig 3400, Daiwa SR-9 (144MHz). Would exchange for pair Quad Bronze els's, SME pick up arm, Myford machine tools/equipment, Bolex 16mm cine equipment, Stuart Turner steam models/fittings. Tel: 0296 622725 (Bucks). W013

Have Yaesu FRG-7 receiver fitted 4kHz filter, Tandy Patrolman 50 receiver, Plustron TVR5 TV/radio, BSR-McDonald MP60 record deck. Would exchange for Telereader CWR610E, MuTek BBA500U wideband pre-amp, good discone. Graeme. Tel: 0642 318451 evenings (Middlesbrough). *W023*

Have Fidelity 3 waveband radio. Would exchange for service info, circuit diagram of Magneta public address transistor amplifier PA100. Martin, 18 High Street, Dover. Tel: 206048. W024

Have Edgcumbe 500V Metrohm appliance, earth continuity, etc., testmeter, with case and leads. Used value over £100. Would exchange for anything useful radiowise, not necessarily same value. Home-brew equipment acceptable. Dave. Tel: Stoke-on-Trent 721904. W035

Have complete TV station for 430MHz TV—TX plus camera plus lens plus TV monitor. Would exchange for good condition FT-290. G4GIQ QTHR. Tel: Northwich 45584. W054

Have Daiwa Auto ATU CN1001, as new. Also have TR2500 144MHz hand-held with speaker mic, soft case, d.c. power lead, all boxed. Would exchange for h.f. beam, 430MHz gear, h.f. linear, or w.h.y. Dave G4WBB. Tel: 0709 67471 (Rotherham). W055

Practical Wireless, November 1984

Have Trio 2400 hand-held, home charger, car charger, leather case, speaker mic, Welz SP15M s.w.r. meter, 9 amp p.s.u., Welz 2-way antenna switch and Drae v.h.f. wavemeter. Would exchange for good computer—not Sinclair. Brian. Tel: 051-264 9860 (Liverpool). W057

Have Honda 90cc motorcycle "S" registration plus Casio 602 electronic organ as new. Would exchange for 934MHz transcéiver. Rowe, 7 Arrowcroft Road, Guilden Sutton, Chester. W068

Have FRG-7700, 10hrs use. Cost £365. Would exchange for best computer system offered. Elvin. 214 Horninglow Road, Firth Park, Sheffield S5 6SG. W071

Have Sony IC2001 h.f. receiver, all mode, memory, etc. New £180. Also have Olympus OM30 camera f:1.8 s.l.r., OM winder, OM in focus trigger cord, Ozyeck 2× multiplier and straps, holdall, etc. All in v.g.c. Would exchange for any h.f. transceiver. Martin. Tel: Northampton 719233. *W089*

Have Waltham Music Centre, tuner and amplifier in good working order, tape and record decks in need of slight repair. Would exchange for general coverage receiver (FRG-7 or similar) or 144MHz beam and rotator or w.h.y. Tel: 0926 57234 (Kenilworth). W111

PW "SWAP SPOT"

Got a camera, want a receiver? Got a v.h.f. rig, want some h.f. gear to go with your new G4? In fact, have you got anything to trade radio-wise?

If so, why not advertise it FREE in our new feature SWAP SPOT. Send details, including what equipment you're looking for, to "SWAP SPOT", *Practical Wireless*, Westover House, West Quay Road, Poole, Dorset BH15 1JG, for inclusion in the first available issue of the magazine.

A FEW SIMPLE RULES: Your ad. should follow the format of those appearing above; it must be typed or written in block letters; it must be not more than 40 words long including name and address/telephone number. Swaps only—no items for sale—and one of the items MUST be radio related. Adverts for ILLEGAL CB equipment will not be accepted.

PW`TEME Modular QRP Transceiver Part 1 by Rev. George Dobbs G3R.



Dobbs G3RJV

In the twenty or so years that I have held an amateur radio licence the ethos of the hobby has changed completely. I actually recall when radio amateurs boasted about how cheap their station was and now, so often, the reverse is true. Recently I was answering questions from a group of RAE Candidates and found that they really only had two questions to ask, "What should I buy?" and "How much is it going to cost me?" Yet in spite of the current trends in the hobby it is possible to participate fully and have a lot of enjoyment from the use of relatively simple low-power, home-made equipment. Hundreds of pounds and hundreds of watts are not required on the h.f. bands. As William of Occam (1290-1350) said,

> "It is vain to do with more, what can be done with less."

This series of articles will describe a progressive h.f. c.w. amateur radio station for the popular 7 and 14MHz bands which can be built by the average constructor at low cost using easily obtainable components. The project takes the form of a series of add-on modules. It begins with a basic transmitter, which can be used in its own right, then further modules are added to build up to a reasonably sophisticated and highly usable amateur radio station. So right from the beginning, with the construction of the first module, the constructor has something which can be used. It is then up to the individual to add modules according to taste, ability or pocket. Each module is housed in an identical smart case. The cases are stackable, as the station grows, and smart enough to grace any room in even the most fastidious home.

The Modules

The make-up of the final station when all the modules are completed is shown in Fig. 1.1. The basic unit is a transmitter for the 7 and 14MHz bands (with a 10.1MHz option, if required). The transmitter module also contains the changeover (transmit/receive) control circuitry which produces a number of switched power lines for controlling sections of the other modules. These lines are distributed to the various modules via a standard 5-pin DIN plug and socket on each box. The transmitter is low powered (ORP) having a drive control which can give an r.f. output from nothing to 3 watts. That might seem very low but some avid QRP operators would regard 3 watts output as being too much for them!

The basic transmitter is a variable crystal oscillator (VXO) circuit which only allows limited frequency coverage, so the second module provides a variable frequency oscillator (v.f.o.) to enable the c.w. portion of the bands to be covered. The v.f.o. is on 7MHz, and a doubler on the same board allows for a 14MHz output. These two modules together give a very useful transmitter for two amateur bands and, used in conjunction with an existing receiver, could make up a viable station. This would provide a lot of satisfaction from making contacts with a home-made transmitter. But why stop there? Confound the opposition by adding the receiver module and operate a completely home-made station. The existing v.f.o. and doubler are used, together with a direct conversion receiver board to provide full transceiver facilities. The common selectivity problems usually associated with direct conversion receivers are minimised by good front end tuning and a built-in, two-position audio filter.

The station may be completed by adding a stabilised 12 volt power supply unit to save the inconvenience of battery supplies. The supply is made compact by using a toroidal mains transformer. It is well smoothed to overcome the hum problems sometimes apparent when using a direct conversion receiver on a mains operated power supply. The final module contains a standing wave ratio (s.w.r.) meter for tuning up the transmitter and an antenna tuning unit (a.t.u.) to enable a wide range of antennas to be used with the transceiver. The a.t.u. assumes the use of an endfed piece of wire as an antenna but alternative circuits (that will fit the case) are discussed for other configurations.

The whole project is easy to build, costs very little—in fact the cost is spread out because of the modular approach. NO SPECIALISED TEST EQUIPMENT IS RE-QUIRED to build any of the modules. The constructor only requires a reasonable bench multimeter, in the 20 000 ohms per volt class, an existing amateur bands receiver to identify the signals in the early stages of construction, and a simple diode probe, which is built as part of the project. If a newcomer is thinking of buying a multimeter for this project, all that is required is a medium priced analogue meter (one with a needle scale) rather than a digital meter. As with a lot of amateur construction work, we will be using the meter to measure changes and peaks, rather than exact finite readings, and such changes are better seen in the swing of a needle.

The Transmitter Circuit (Module 1)

The circuit for the transmit module is shown in Fig. 1.2. The amateur radio literature is full of circuits for, and myths about, little crystal-controlled transmitters. Many are much simpler than this circuit but practice shows that over-simplified transmitter circuits can be prone to all manner of problems. The power amplification section (1Tr2 and 1Tr3) comes from a conversation I had with Wes Hayward W7ZOI, the doyen of QRP circuit design, when we met in Houston at the ARRL Convention in 1983. This broadband amplifier circuit uses negative feedback in both stages, is very stable and easily reproducible without problems. The DRIVE control, 1R5 allows for a power range of zero to 3 watts of r.f. output using the sturdy BLY33 transistor in 1Tr3.

The oscillator stage, 1Tr1, is a simple crystal oscillator using a fundamental frequency crystal, for the 7 or 14MHz bands, as a feedback element. The series variable capacitor 1C2 allows some frequency shift in the oscillator. The amount of frequency offset available from 1C2 will vary according to the band and specific crystals. A tuned circuit, 1L1 and 1C3, tunes out the 7 or 14MHz signal according to the band in use and link winding 1L2



Fig. 1.1: The PW "Teme" modular transceiver system interconnection arrangements

To avoid confusion between the several modules making up the PW "Teme" project, each has been numbered as follows:

| undered as follows. | |
|---------------------|----------|
| Transmitter | Module 1 |
| VFO/Doubler | Module 2 |
| Receiver | Module 3 |
| ATU and SWR Bridge | Module 4 |
| Power Supply | Module 5 |
| Digital Clock | Module 6 |
| | |

Each drawing and components list will state which module number it refers to. In the text, component references will be prefixed by the module number. For example, resistor R9 in the Transmitter Module would be called 1R9, while R9 in the Receiver Module would be 3R9.

feeds the DRIVE control, 1R5, a $1k\Omega$ linear carbon potentiometer.

The driver stage, 1Tr2, is coupled via a wideband matching transformer, 1L3, into the power amplifier (p.a.) stage, 1Tr3, which requires a heatsink of the "star type" designed for a TO-5 transistor case. The collector load, 1L4, is a small r.f. choke wound from a few turns on a small ferrite bead. Capacitor 1C10 then couples the output





into switchable low-pass filters. A double-pole change-over switch, 1S1 selects either the 7 or 14MHz filter.

The low-pass filters are seven-segment, standard value capacitor filters of the type popularised by Ed Wetherhold W3NQN. Simpler methods can be used to tune the output of a QRP transmitter but harmonic suppression is important even in low power transmitters. These filters, based upon the computer standardised values of W3NQN, are compact, inexpensive and provide high harmonic rejection with little attenuation of the output. The values required are listed in the chart of Fig. 1.4. The correct toroid cores and good quality silvered mica or polystyrene capacitors must be used for these filters.

Two d.c. switching transistors, 1Tr4 and 1Tr5, provide the keying and change-over control circuits for the module. Note that 1Tr4 and 1Tr5 are *pnp* transistors. The key operates both 1Tr4 and 1Tr5 through 1D1 or 1D2. When the key is down, +12 volts is switched onto the collector of 1Tr4 which keys the transmitter through the driver stage 1Tr2. A little shaping to improve the keying characteristics is provided by 1C12, 1R14 and 1C11. Also when the key is down 1Tr5 conducts and energises the d.p.c.o. relay 1RLA/2. The electrolytic capacitor 1C14 holds the contacts of 1RLA in the energised position for a small interval of time. The changover from transmit to receive is controlled by 1RLA, a form of semi-automatic break-in is the result.

When keying begins the circuits switch to the transmit condition and will not release from this condition until the key has been released. The delay caused by 1C14 allows the transmit condition to prevail during normal keying speeds so that the relay does not clatter in and out with every action of the key. The delay speed can be adjusted by changing the value of 1C14. The relay changes the antenna over from the receiver to the transmitter. It also switches a 12 volt line to provide a 12 volt receive (12 RX) or a 12 volt transmit (12 TX) control voltage. These lines are used in later modules as is the 12 volt keyed (12 KEY) line taken from the collector of 1Tr4. The 12 TX and 12 RX lines are also used to switch two small l.e.d.s, 1D4 and 1D5, which give a front panel indication of the status of the transmit module.

Construction

The transmit module is built on one printed circuit board. The layout is shown in Fig. 1.3. The transmit board is best built a section at a time beginning with the oscillator stage, 1Tr1, so that each stage can be tested in turn. The only test equipment required is a multimeter with a simple r.f. probe and perhaps a station receiver. The circuit for the r.f. probe is shown in Fig. 1.2(b). This probe is used in conjunction with a multimeter. The probe tip is placed upon a part of the circuit and the ground clip is connected to the ground end of the circuit or the transmitter case. The r.f. signal is converted into a d.c. voltage by 1D6 and 1D7. This represents a peak-to-peak reading of the r.f. voltage present at the probe and can be used for checking the presence and progress of the r.f. signal. The prototype r.f. probe was made on an offcut of printed circuit board material, the simple track pattern being cut with a lino cutter blade. A small piece of Veroboard could be used instead. The leads to the multimeter must be screened to

| * components MODULE 1 TRANSMITTER | | Semiconductor Transistors | Semiconductors Transistors | | | amic nla | te | | |
|---|---------|------------------------------|-------------------------------|-----------------------|---|--------------------------------|------------------------------------|------------------|--|
| | | BC107 BLY33 2N2905A | 2 1 2 | Tr1,2 Tr3 Tr4,5 | Miniature cera 10pF 10nF 0·1μF | 1 10 3 | C15 C4,6–11,13,24,25 C1,5,12 | | |
| Resistors | | San Television | in an engine and engine | | ALL SECTION OF | Polystyrene of | r silverer | d mica | |
| 1W 5% carbo | on film | 12 36 36.7 | Diodes | | | 180pF | 2 | C20.23 | |
| 4.7Ω | 2 | R12,13 | 1N914 | 4 | D1,2,6,7 | 270pF | 2 | C16,19 | |
| 22Ω | 1 | R8 | 1N4001 | 1 | D3 | 390pF | 2 | C10,19 C21,22 | |
| 33Ω | 1 | R17 | 3mm l.e.d.s | 2 | D4,5 | 680pF | 2 | C17,18 | |
| 100Ω | 2 | R3,4 | | | | | Ref. 29 Tel | In State of the | |
| 150Ω | 1 | R10 | Industan | | | Electrolytic, 16V double-ended | | | |
| 330Ω | 1 | R6 | Inductors | | | 10µF | 1 | C14 | |
| 560Ω | 1 | R16 | L1-10 See t | .ext a | and Fig. 1.4 | Variable | | | |
| 680Ω | 1 | R11 | the summer search the summer | | | 350pF (see | toyt) | 1 C3 | |
| 1kΩ | 1 | R15 | A side of the bell and | | | | e text) 1 | 1 C2 | |
| 1.2kΩ | 1 | R9 | | | | 0001 (500 | lext/ | 2 | |
| 2·2kΩ | 2 | R7,14 | | | | 11、10、12、12、13、13 | | 副语 法主部的 | |
| 4.7kΩ | 1 | R2 | Miscellaneous | | | | | | |

Miscellaneous

Phono sockets (4); 2-pole ¹/₄in jack; 5-pin DIN socket; Crystal holder, HC25U; Relay d.p.c.o., 12V 185Ω coil, "Continental" type (Maplin FX27E or similar); Switch d.p.c.o. min. toggle; Heatsink, push-fit TO-5 for Tr3; Printed circuit board; Case, see text and Buying Guide; Feet, knobs (3), etc.

Potentiometer, carbon track $1k\Omega$ (lin) 1 B5

22kΩ



R1

Crystals: Amateur Band crystals for the transmitter may be obtained from P. R. Golledge Electronics, Merriott, Somerset for 7030 and 14060kHz (QRP Calling Frequencies) and 14030, 14040 and 14 050kHz. These are HC25U crystals priced at £4.00 each (£3.50 each for a G-QRP Club Member) including VAT and postage.

Toroid Cores: All the toroid cores for the transmitter can be obtained from SMC(TMP) Unit 27, Pinfold Workshops, Pinfold Lane, Buckley, Clwyd CH7 3PL, (0244) 549563, or from Cirkit. Please note, with the exception of L3, the toroids are iron powder, not ferrite cores. Most unmarked surplus toroid cores are ferrite.

Cases: The J6 Instrument Case is available from Minffordd Engineering, Sun Street, Ffestiniog, Gwynedd L141 4NE. (076676) 2572.

P. A. Transistors: The BLY33 is available from BCD Electronic Services, 200 Hessle Road, Hull, (0482) 225437, or Heller Electronics Ltd., 49 Blossom Waye, Hounslow, Middlesex TW5 9HB. Other similar transistors could be substituted.

Front Panel Legends: Water slide transfers (in white only) of amateur radio legends are available from John Kaine, 74 Campden Mews, London N1 9BX for £1.25 a sheet, inc postage.



Practical Wireless, November 1984

prevent stray r.f. pick-up. All the measurements for the prototype were made with this probe and an inexpensive 20 000 ohm per volt multimeter.

The variable capacitor required for the oscillator frequency shift control vxo has a value of some 3-60pF and that used in the prototype was made from a semiairspaced trimmer, being a much cheaper alternative than an airspaced variable capacitor. (Note: Some of these semi-airspaced trimmers tend to have a very short life if moved frequently-Editor). The trimmer is mounted onto an offcut of Veroboard and a short piece of 6mm $(\frac{1}{4}in)$ diameter shafting (in the prototype, excess from the potentiometer 1R5) is counter-bored and glued onto the screwdriver control of the trimmer. This is shown in Fig. 1.5. The crystal, 1XL1 is held in an HC25U crystal holder on the front panel. Coils 1L1 and 1L2 are wound onto a single T37-6 toroid core as shown in Fig. 1.4. The main winding, 1L1 should occupy some 80 per cent of the core, each time the wire passes through the centre of the core counts as one turn.

The output tuning capacitor for 1Tr1, 1C3, covers the 7 and 14MHz bands with 1L1. This variable capacitor is a polycon semi-airspaced type of the sort used in cheap Far Eastern a.m. radios. This could be culled from such a radio but ensure there is enough control shaft to take a knob. A suitable variable capacitor can be bought from Cirkit (type CY2-3217Z). Usually such capacitors have two sections of some 350pF and may have smaller sections for f.m. tuning. Using an ohmmeter, identify the connection which is common with the shaft and join that tag to ground. Inspect the capacitor to identify a tag that goes to the fixed vanes of a large tuning section and connect that tag to 1L1.

Build the first stage as far as 1R5 and test that the oscillator works. Set the r.f. probe up with a multimeter on a low voltage scale (say 10 volts). Insert a 7MHz band fundamental crystal in the crystal socket and apply 12 volts to the top of 1R3. Attach the probe to the top end of 1R5 and adjust 1C3 until the voltmeter indicates a peak reading, which will probably be in the order of 3.5 volts. The signal can also be located on a receiver capable of tuning the frequency of the crystal. The same test can be tried with a 14MHz band fundamental crystal. Again it should be possible to obtain an output peak using 1C3.



Fig. 1.3: Full-size printed circuit track pattern and component layout and wiring diagram for Module 1, the Transmitter

The driver stage may now be constructed as far as 1R10. The transformer 1L3 is wound on a ferrite core with a bifilar winding. The T37-43 core is ideal but almost any surplus small ferrite core would serve in this position.

A bifilar coil is wound by making two windings side by side over the small core. Take enough wire to wind two windings of 10 turns around the core. Place the wires side by side and twist them together, making roughly 8 twists per inch. The 10 turns are then wound onto the core. The start and finish of both windings must be identified using the ohms range on a multimeter and connected as shown in Fig. 1.2. With the oscillator working and peaked for



7-ELEMENT LOW-PASS FILTER COMPONENTS



| ELEMENT | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
|----------|-----|-------|-----|-------|-----|-------|-----|
| 7MHz | 270 | 21 | 680 | 24 | 680 | 21 | 270 |
| | pF | turns | pF | turns | pF | turns | pF |
| | C16 | L5 | C17 | L6 | C18 | L7 | C19 |
| 14MHz | 180 | 16 | 390 | 17 | 390 | 16 | 180 |
| | pF | turns | pF | turns | pF | turns | pF |
| | C20 | L8 | C21 | L9 | C22 | L10 | C23 |
| Optional | 270 | 19 | 560 | 20 | 560 | 19 | 270 |
| 10-1MHz | pF | turns | pF | turns | pF | turns | pF |

Fig. 1.4: Inductor and filter details for Module 1, the Transmitter

maximum output, 12 volts are applied to the top of 1L3 and the r.f. probe is connected to the top of 1R10. The output should be in the order of 10 to 11 volts.

The power amplifier stage is added with the r.f. choke being wound on a small ferrite bead as shown in Fig. 1.4. The output of the whole transmit board may now be checked with the r.f. probe. Transisitors 1Tr1 and 1Tr3 take a common 12 volt line and 12 volts must be applied to 1Tr2 at the top of 1L3, as it will be when the transmitter is keyed. The p.a. stage requires a dummy load for the test, in fact the transmitter should not be operated without a load for the sake of the health of 1Tr3! A suitable load can be made from a non-inductive resistance of around 50 ohms. Two 100 ohm, 2 watt, carbon resistors in parallel would be suitable. Connect the r.f. probe across the dummy load to check the output of the p.a. The output will depend upon the DRIVE control, and could be in excess of 3 watts output with high drive. Rough equivalent readings to r.f. output in watts are: 3 watts output about 21 volts, 2 watts output about 17 volts, 1 watt output about 12.5 volts.

The low-pass filters are constructed from the chart in Fig. 1.4. The basic transmit board requires a filter for 7MHz and 14MHz. These are selected by a double-pole, change-over, miniature toggle switch, 1S1. The connections between the p.a., the switches and filters must be made with screened leads. The transmit board is capable of use on the 10.1MHz band with a suitable crystal and setting of 1C3. Although this band will not be used in the final project, values for the 10.1MHz band are given in the chart in Fig. 1.4 should the constructor wish to use the basic transmit module on this band.

The change-over and control circuit around 1Tr4 and 1Tr5 is best built and tested with a voltmeter before being used to control the transmitter. The relay, 1RLA/2, is a small 12 volt, 2-pole, change-over, relay with coil resistance around 185 ohms. When the circuitry around 1Tr4 and 1Tr5 has been completed and power applied, operating the key should cause the relay to come in when keying begins. The relay should remain closed until keying is stopped. Using the stated value for 1C14, the relay still remains closed at keying speeds as low as 8 words per

G-Q.RP Club

A specialist group for users and builders of Low Power Equipment. Details from: Fred Garrett G4HOM, 47 Tilshead Close, Druids Heath, Birmingham B14 5LT.



text)

5.140



minute. Also check that as the key is operated 12 volts appears at the collector of 1Tr4 in sympathy with the keying action. The interconnections for the control system can now be added. The antenna change-over section must be wired with screened leads and the 12 volt lines, +12V, 12 RX, 12 TX and 12 KEY are connected to a 5-pin DIN Socket, as shown in Fig. 1.1, for control lines in future modules. The transmit/receive indication l.e.d.s are mounted in small holes in the front panel.

When the receiver module is added, it requires oscillator injection from the transmitter board. If this module is to be built later it is best to add the oscillator output socket when building the transmit module. The circuitry required is shown in Fig. 1.2(a). The oscillator output is taken from the top of 1R5 via a 10pF capacitor and screened lead to an output socket. All the signals leads in the PW "Teme" use the small standard phono plugs and sockets which are cheap and more than adequate for the purpose.

The photographs show the module layout. One standard case is used to house each module through the whole project, this being the inexpensive J6 Instrument Case sold by Minffordd Engineering. This case measures 152 × 102 \times 51mm (6 \times 4 \times 2in) has an aluminium base and front/back panels with a pvc coated lid. The type I used had a rich deep brown pvc coated lid. I therefore used a lighter tone brown for the front panel. The front panel is made in the manner I have used for many years to give an attractive finish. When the front panel has been drilled to hold the controls, these are then removed. A piece of suitable thin card (pale brown in my example) is cut to fit the front panel. The positions of the holes are marked on the reverse of the card and cut out with a small pair of pointed scissors or modelling knife. The lettering is added with rub-down letter transfers and the card is lightly attached to the metal panel with "Pritt" glue. The whole front panel is then covered with a layer of transparent sticky-backed plastics film, of the sort used to cover books. This provides a durable, attractive finish and protects the lettering. A sharp knife removes the surplus plastics film from the holes and the controls are replaced. Care must be taken when tightening up control mounting screws not to bear down too tightly upon the plastics film and cause unsightly wrinkles. The whole effect is smart and durable and far superior to the usual amateur application of car aerosol paint and lettering. Constructors using dark coloured, or black, front panels could use the excellent water slide transfers of amateur radio legends which are now available for front panels.

Using the Transmit Module

The transmitter may be used as a viable QRP rig in conjunction with an existing receiver. The receiver interconnects with the transmitter via the change-over circuitry for antenna, transmitter and receiver. The receiver may require some form of internal muting, although at these power levels just changing over the antenna and turning down the gain controls may be enough. In fact this method



allows the receiver to monitor the keying of the transmission. One problem is that in the circuit shown in Fig. 1.2 the oscillator stage is on the whole time and may be heard on the receiver during reception. This can be solved by making use of the link in the printed circuit board between the top of 1R3 and the +12 volt line. Remove this link and connect the top of 1R3 to the 12 TX line. This will mean that the oscillator is only switched on when the transmitter is in the transmit mode. This connection must be restored to the original circuit arrangement when the transmitter is used in conjunction with the later modules.

Operating a low-powered transmitter on the amateur bands can be great fun. Added to the challenge is the satisfaction that the transmitter is home-made. Although the signal is likely to be some two S-units down on the average UK amateur signal, the user will soon be surprised what can be worked at these power levels. The transmitter is designed for a 50 ohm termination and like most modern transmitters must be used into an antenna with a characteristic impedance of 50 ohms, such as dipole or beam, or matched to the antenna with an antenna tuning unit (a.t.u.). The vxo control should give enough frequency offset to allow stations slightly off the fundamental frequency of the crystal to be called. QRP operation can be very addictive as the 2000-plus members of the G-QRP Club will confirm. For the low outlay, this little transmitter module should provide a lot of enjoyment.

NEXT MONTH

The Variable Frequency Oscillator



Have Icom IC2E, hardly used. Would exchange for Realistic DX302 or R–600 communications receiver. Tel: 02576 2126. W218

Have 2 Hitachi colour video cameras, zoom lens, etc. One v.g.c. other for parts. Would exchange for Epson printer, FRG-7, 144-430MHz transverter or w.h.y. Tel: 031-660 4180 (days). W245

Have Vic 20 CPU, C2N Datasette unit, p.s.u. and all cables, Introduction to BASIC Pt. 1 and 16K RAM pack, cartridges and cassettes. Value over £300 when new. Would exchange for FRG-7700 or w.h.y. Tony. Tel: 0478 2548—RAE student. *W246*

Have CR2021 portable Uniden 0.15—29.999MHz plus f.m., 2 months old. Would exchange for a similar receiver non-portable. Must be suitable for RTTY, cash adjustment as required. G. Dutton, 40 Grafton Road, Harwich, Essex CO12 3BD. W260

Have WW–II Navy receivers, B.29 and B.41, also have Specto 16mm film projector, 2-speed, 16 & 2 f.p.s. and still. Would exchange for vintage wireless items, crystal set or components. Tel: Brighton 737076. W261

Have Super 8mm Sound Cine outfit, camera f:1.2 5x zoom, projector, screen, tripod, editor/splicer. Would exchange for automatica.t.u. G3AAH. Tel: 021-451 3369 (Birmingham).W280

Have Chinon CM3 camera and various accessories including large powerful flash unit. Also have Realistic PRO-47 scanner with 6 crystals fitted. Would exchange for 144MHz transceiver, would prefer multimode as just passed RAE. Don. 9 St. Annes Park Road, Bristol BS4 4DT. Tel: 773390. W297



PROTECTION—2

Last month I talked about how to protect receiver input circuits from damage caused by r.f. energy picked up on the receive antenna from an associated transmitter.

The arrangements I showed in the drawings in Part 1 all rely on a relay coil being energised when the transmitter is keyed. A better way is to have the relay contacts connected up so that the receiver is protected when the relay is deenergised, and works normally when the relay is energised. The circuit of Fig. 7 shows how this can be done, using the "back" contact of a Morse key or the "rest" contact of a changeover press-to-talk (p.t.t.) switch. The supply marked +V comes from the receiver power unit, so when the receiver is switched off and the supply disappears the receiver is protected.

So, we have protected the receiver input, but connecting and disconnecting the antenna with the receiver operating at normal gain levels will cause loud "crashing" noises in the loudspeaker or headphones. What is needed is a way of reducing the receiver gain each time the transmitter operates. To stop the crashing noises, the gain must be reduced just before the antenna is disconnected from the receiver, and not restored to normal until after the antenna has been reconnected. The time intervals I'm talking about are only a few thousandths of a second (milliseconds).

This process of reducing the receiver's gain whilst a transmitter is operating is called desensitising. Exactly how it is done will depend on the receiver design. A favourite arrangement in valved communications receivers was to key the r.f. gain control circuitry (Fig. 8) so that the cathode bias of the controlled stages was increased (reducing the gain) whilst transmitting. Alternatively, a keyed voltage was superimposed on the receiver's automatic gain control (a.g.c.) line. Whereas the a.g.c. voltage would have a fast attack but a slow decay, the desensitising voltage must have a fast attack and a fast decay. The circuit of Fig. 9 shows the outline of the idea. The values of C1 and R1 are chosen to give a longer time constant for the a.g.c., compared with C2/R2 in the desense line. The two diodes isolate the two time-constant circuits from each other.

In transistorised receivers, basically similar gain adjustment techniques can be used, but often variable shunt attenuators are favoured instead (Fig. 10). A control voltage is applied via isolating resistor R1 to forward-bias the diode, making it conduct and shunting some of the signal away to

Practical Wireless, November 1984

earth. The greater the forward bias, the more heavily the diode conducts, and the more of the signal is leaked away to earth. The diode in this arrangement is a conventional small signal diode. A single attenuator of this type gives a fairly limited range of attenuation, and normally several will be used at different places in the r.f./i.f. amplifier chain.

-Uncle Ed-

The techniques I have described, with suitable choice of time constants for attack and decay, and with the appropriate timing of antenna switching and desensitising, will allow you to "listen through" your own Morse code transmissions for signals from the distant station, or give instant send/receive switching when using telephony. You can, of course, keep the circuitry simpler but make your operating life more complicated by manually switching the receiver to "standby" each time you transmit, or by physically turning down the receiver gain control. Adding a little automation to the system can work wonders though, so if you're using separate receiver and transmitter, rather than a transceiver where the switching is all done for you, it's worth the trouble of wiring up a system for the protection it gives your receiver, and the easier routine it brings to operating.



Stable TONEBURST

by D. I. Shaw G8ESN

Repeater access toneburst circuit designs, both simple and complex, have been published many times over the last few years. If your demand is for the ultimate in frequency accuracy and stability the natural choice would be to use a crystal controlled oscillator—the fact that the toneburst circuit could well cost more to construct than the ex p.m.r. handheld it's destined to be fitted to is one of those odd quirks of technology! Cheaper free running oscillators can of course be built but these invariably exhibit considerable frequency dependence on both supply voltage and ambient temperature variations.

With these considerations in mind the following design was evolved which is not only very cheap in terms of component cost but it will actually fit into a u.h.f. Pye PF1 Pocketphone without drastic surgical effort and at the same time remain very close to the required 1750Hz.

Circuit Description

The circuit shown in Fig. 1 was designed to operate without a potentiometer for frequency adjustment. This can be justified by a potentiometer's poor stability with time and temperature. Metal oxide resistors have been used to give improved temperature stability.

Operation of the oscillator is as follows: Gates IC1a, b and c form a 3-gate oscillator. Resistors R5, R6 and R7 are chosen to restrict the voltage swing on the input of IC1c to within the voltage rails. This prevents conduction of the internal protection diodes improving the stability of the oscillator.

Components R8, R9 and C2 are the burst duration elements of the circuit. Resistor R8 may need to be varied because of the large tolerance of electrolytic values. Gate IC1a, which supplies part of the bias for the oscillator, is on for slightly longer than the duration of the toneburst—this is for two reasons. In the first instance, the stability of the toneburst is ensured until the end of the burst and secondly the inactive current consumption of the circuit is less than 1μ A.

The current consumption of the toneburst is approximately 2mA when active. The temperature stability of the oscillator is good and only drifts 2–3Hz for 10°C temperature change. Frequency stability with supply voltage is excellent, only drifting approximately 5Hz over a 5V to 20V supply variation and therefore this unit does not need a regulated supply.

As previously stated there is no provision for a potentiometer in this circuit for stability reasons so the frequency should be set on the bench by adjusting the value of R2 to bring the toneburst frequency to $1750Hz \pm 5Hz$. The oscillator can be kept on by shorting C2 thus facilitating the use of a frequency counter, connected to pin 3 of IC1, for setting up. It has been noticed that with some transmitters it was necessary to couple the toneburst circuit with an electrolytic capacitor in series with R4.

The printed circuit board and component layout is shown in Fig. 3. The order of component insertion is critical otherwise you will not be able to solder leads to pads. The two through-board links are first soldered in place ensuring that the i.c. socket still fits flush to the board. This socket is fitted next. A strip of thin card 10mm wide by 24mm long is placed under the resistors on the opposite side of the p.c.b. to the i.c. to prevent the resistor leads shorting onto the soldered joints of the i.c. socket. All pins and wires must be cropped as short as possible. The usual handling/static discharge precautions should be followed, leaving the insertion of IC1 until last. For those with access to an oscilloscope Fig. 2 is provided to indicate circuit conditions during operation.



Practical Wireless, November 1984





Have rack mounting 150 watt amplifier, excellently made, inclusive power unit 1000V, panel metallic sea green. Ideal conversion linear amplifier. Also have power unit 400V 200mA. Would exchange for 430MHz or 144MHz transmitter. Cash adjustment. Must collect Birmingham. Tel: 021-743 5068 after 6pm. W113

Have Pye u.h.f. portable (the "Professionals" style) in mint condition with base charger and NiCads on the 430MHz band. Would exchange for Burndept u.h.f. portable (police style) in similar condition. Allan. Tel: 0782 612868. W137

Have Datong Morse Tutor, CCTV camera, 430MHz TV upconverter W & D, all in working order. Would exchange for h.f. receiver in working order. Tony G6RBK. Tel: 0923 673765 (St. Albans, Herts). W145

Have ZX Spectrum 48K computer, 6 months old, plus £70 worth of programs and magazines. Would exchange for Telereader *Practical Wireless, November 1984*

CWR610E or MM2001 RTTY converter or w.h.y. S. Rake, 80 Cripps Ave., Tredegar, Gwent NP2 3PB. W146

Have 12V Sceptre push-button car radio. Would exchange for Pye Bantam transceiver. Tel: 0788 822508 (Northants) W154

Have early model thermionic press-button band-change radiogram. Would exchange for mains/battery commercial receiver—Sony or similar. Tel: Caterham 49851. W155

Have TRS-80 16K, level 2 micro, covers, green screen, cassette, thermal printer and interface, £250 + software and books. Would exchange for v.h.f. multimode transceiver worth £250 +, e.g. FT-290, C58, etc. Andy. Tel: 0625 614510 (Macclesfield). *W180*

Have Atari TV game plus 6 different cartridges, cost £280, all in v.g.c. Would exchange for 144MHz hand-held transmitter. Tel: Ebbw Vale 301078. W203

Have Casio MT800 stereo electronic organ, plus Yaesu FT–208R hand-held. Would exchange for IC–251 or FT–77. Would separate Casio MT800 for FT–290R or C58. Mr Keen, 30 Bath Road, Chiswick, London. Tel: 01-995 7339. W208

RESULTS RESULTS RESULTS



by Neill Taylor G4HLX

A staggering 234 entries were received for this year's QRP contest, held on June 17, seemingly making it the best-supported v.h.f. contest ever held in the UK. Entrants shared a common enthusiasm, although stations ranged from one-man home fixed stations to highly organised mountain-topping groups. Locations used varied between the two extremes of sea-level sites and the summit of Ben Nevis.

The Welsh hill-tops proved the most successful sites again, the leading three stations in both multi- and single-operator category taking advantage of the superb take-off available. The overall winners by an impressive margin were a group comprising GW4TTU, G8TFI, G4VXE and GW5NF, collectively known as the "Bug Bashers Contest Group". They gain the winners' cup for their operation as GW4TTU/P from Mynydd Maen, a stone's throw from the Blackwood ARS, last year's winners, now beaten into second place.

Roger Dyke, GW4NVA/P, leads the single operators from a site near Wrexham. Last year's leading single operator, Chris Otley, G4CYA, in Sheffield, this year takes the top fixed station position instead. The overall runners-up in 1983, Martyn Wright and Neil Underwood, are still the leading station in England, this year under the callsign G4RLF/P from the same Wiltshire site of Win Green. In Scotland, David Taylor and Peter Robertson, as GM4RZW/P, take the lead, and also manage 6th place overall, which is very commendable from their site on Broad Law, south of Edinburgh. Robert Loftus E17DG/P tops the EI/GI entries from Three Rock Mountain near Dublin.

The table summarises the ten certificate winners, and shows details of the leading ten multi- and single-operator stations. A detailed list of all the entrants is available on receipt of a large s.a.e. at the Poole Offices. Those entrants who have already submitted envelopes will receive the results shortly.

The map shows how the 234 stations were distributed around the OTH squares, and also lists the leading stations in each square. The other figure in each square is the average number of QTH squares worked by the entrants in it, which may destroy a few myths about where the most favourable positions are.

Where The Points Were Lost

Apart from the sheer bulk of 234 logs to cross-check, adjudication was a little easier this year due to an apparent general improvement in the standard of log-keeping (computerisation of the records helped, too), although a few stations will persist in presenting entries in their own format instead of that required by the rules. A handful of logs were almost illegible, too, and as a contact can't be verified if it can't be read, points have been lost. One station sent a scruffy log, containing many errors, on non-standard sized paper with the columns in the wrong order and some of the covering information missing. A pity, as the group put in much effort during the event, and the claimed score would have put them 16th.

About 50 per cent of entrants lost some points for general logging errors, only a few really losing a substantial amount. The most common error again was omitting a /P suffix from a callsign, and it seems certain that in most cases it hasn't been sent by the portable stations. Several entrants commented on this, for example G4WCK/P: "A number of /P stations did not send /P during an entire QSO, but were heard to send it in an earlier or later QSO. This was most annoying." More than one portable station even omitted the suffix on the entry sheet!

The only general lowering of log-keeping standard was with regard to unmarked duplicate contacts, which were found in even computerised logs. A few stations seem to have been operating without check-logs, relying on a quick check after the contest which has been insufficient to spot all duplicates.

From Sunburn to Frostbite

To portable stations, weather conditions can be more important than propagation conditions, particularly if they reach extremes, which they certainly did during this event. The reports from "an absolute scorcher"—G6VAT/P, to "awful!"—GM6VDN/P. Many parts of the UK enjoyed unbroken sunshine, "the temperature 26 degrees in the shade"-GJ8RVT/P, and at the other extreme,

GM4TJL/P "reached a patch of snow" on the way to the site, atop Ben Nevis, where he found "my hands were so cold I could hardly hold the nuts and bolts that

hold the elements on the boom". At GW8FUM/P, "we were engulfed in a dense cloud which condensed on the antenna and steadily dripped on us", and G6ZME/P found that "the sun-lounger was not needed". Meanwhile, at G4CAR/P, "T-shirts and shorts were the order of the day", while GM6VDN/P "certainly needed the heavy anoraks we took".

The biggest feature of the weather, however, was thunderstorms. Violent storms raged in the south-east most of the day, and as G6WBP notes, these "effectively closed down the eastern half of ZL square, AL square and AK square . . . only the stalwarts were on the air." Many operators wondered where all the stations had gone in these squares-now you know. Even those away from the centre of the storms found that "at times nothing was heard except S-9+ static crashes"-G6NAD.

It was not only the south-east that experienced thunderstorms, and in many places portable stations closed and dismantled, for example at G4NVM/P: "discretion being the finer part of valour I unplugged everything, lowered the mast and disappeared". Some didn't even wait that long; at GW4MKF/P "I realised that I was the highest thing around", and after a lightning strike 1 kilometre away, "jumped in the car and abandoned station".

To Malta on 3 Watts

For most of the day, tropospheric propagation was unexceptional; although a few stations reported heavy QSB at times, no real openings developed. However, this mediocrity was broken in several areas by spells of good sporadic-E paths to Italy and Malta. The areas most favoured were the far south-east and parts of Northern England and Scotland. Several stations completed contacts using QRP and were highly delighted at the achievement. "The highlight of the day" at G3YMD/P "was to work our first sporadic-E . . . 9H1GB in HV square". For a few, it happened at the wrong time; "after setting up the station . . . the first

PW 1984 QRP Contest

| Pos. Callsign | Score | Pos. Callsign | Score | Pos. Callsign | Score | Pos. Callsign | Score | Pos. Callsign | Score | Pos. Callsign | Score |
|---------------|--------|---------------|-------|---------------|-------|---------------|-------|---------------|-------|-------------------------|-------|
| I GW4TTU/P | 19 270 | 40 G1DXY/P | 4431 | 79 G6RAF | 2928 | 118 G6HFW | 1566 | (GM4PGV/P | 1040 | 195 G4XAT | 520 |
| 2 GW6GW/P | 10 956 | 41 G4RNL/P | 4410 | 80 G8DDY/P | 2880 | 119 G6UXT | 1560 | 156 G6FEX | 1040 | 197 G6DVO | 510 |
| 3 GW6KQC/P | 10 850 | 42 GW6PKK/P | 4400 | 81 G6MAN/P | 2862 | 120 G6ZMO/P | 1520 | G4PUZ/P | 1040 | 198 G14OWA/P | 494 |
| 4 G4RLF/P | 9517 | 43 G6HIE/P | 4389 | 82 G4SJK/P | 2839 | 121 G4XSC/P | 1512 | 160 G1FRJ/P | 1022 | 199 G6NUZ/P | 462 |
| 5 G4WET/P | 8596 | 44 G4RAQ/A | 4368 | 83 G6HQT/P | 2760 | 122 G6SVX/A | 1484 | 161 G4XXG/P | 1020 | 200 GW2OP | 451 |
| 6 GM4RZW/P | 8343 | 45 G6OYL/P | 4255 | 84 G6PRR/P | 2678 | 123 G8CYW/P | 1445 | 162 G1BHU | 1008 | 200 G6LUE | 451 |
| 7 GW6GS/P | 7776 | 46 GW6DTD/P | 4248 | 85 G4RVR/P | 2660 | 124 GM4MYL/P | 1444 | 163 G4UIF | 994 | EI4ALE/P | 450 |
| 8 GW4NVA/P | 7616 | 47 GW4ARC/P | 4212 | 86 G4RVJ/P | 2610 | 125 G4SJM/P | 1440 | 164 G6PSH | 990 | 202 G6PBW | 450 |
| of GW6MKR/P | 7560 | 48 G4ARI/P | 4080 | 87 G3BPK/P | 2574 | 126 G6FWT/P | 1422 | 165 GM4RGC/P | 966 | GIBOQ | 450 |
| G6ZME/P | 7560 | 49 G1BIV/P | 4063 | 88 G3YLE/P | 2565 | 120 (G4WCK/P | 1422 | 166 G6HXU | 952 | 205 G4SZI | 424 |
| 11 G4EFE/P | 7279 | 50 G6PHF/P | 4025 | 89 G4PNB/P | 2506 | 128 G4TTT/P | 1416 | 167 G6PZT | 948 | 206 GIDWQ | 420 |
| 12 G6LJO/P | 7226 | 51 GW4WVB/P | 3990 | 90 G3SVC/P | 2457 | 129 EI4FO/P | 1411 | 168 G1EKK | 944 | 207 G8VEL | 418 |
| 13 G4XPS/P | 7150 | 52 GW4XGA/P | 3933 | 91 G4PIQ | 2451 | 130 G6WKK | 1392 | 169 G4WXX | 928 | 208 G4PFY | 390 |
| 14 G6KNF/P | 7020 | 53 G6XYL/P | 3850 | 92 GJ8RVT/P | 2414 | 131 G4DRV/P | 1391 | 170 G6YSQ | 924 | 209 G8SSL | 378 |
| 15 G6YNL/P | 6939 | 54 GM6WIX/P | 3840 | 93 G8SDS/P | 2413 | 132 G4WRW/P | 1350 | 171 GIACY | 918 | 210 GONNA | 360 |
| 16 G41L1/P | 6500 | 55 G6LKB/P | 3818 | 94 G6LCL/P | 2394 | 133 G6SXE | 1335 | 172 GIBRS | 913 | 210 GOUKX | 360 |
| 17 G3BRS/P | 6240 | 56 G4VRY/P | 3780 | 95 G8SKM/P | 2340 | 134 G6EPN/P | 1320 | 173 G4UUH/P | 910 | 212 GIAMX | 342 |
| 18 G6TW/P | 6175 | 57 G4CAR/P | 3759 | 96 G4XYU/A | 2322 | 135 G6VAT/P | 1302 | 174 G4VFG/P | 882 | 213 G6NAD | 336 |
| 19 G4MWC/P | 5976 | 58 G4VWH/P | 3654 | 97 G6ZPN | 2200 | 136 G4LWG/P | 1296 | 175 G4TTF/P | 871 | 214 G6XDZ | 328 |
| 20 G3UFB/P | 5940 | 59 G3IZD/P | 3586 | 98 G8TWH/P | 2142 | 137 G6CSY/P | 1284 | 176 G4WZV | 870 | CCCVD/D | 320 |
| 21 G4WWD/P | 5902 | 60 G4JBR/P | 3565 | 99 G8PRF/P | 2109 | 138 G6SSH/P | 1280 | 177 G4WGE/A | 860 | 215 GM4RIV/P | 320 |
| 22 GM4PPT/P | 5871 | 61 G4LCQ/P | 3564 | 100 G4HMB/P | 2090 | 139 G8TNK/A | 1246 | 178 GW3POM | 840 | 217 G6NZQ/P | 312 |
| 23 G4SVK/P | 5798 | 62 GW4VIX/P | 3540 | 101 G6PUS/P | 2052 | 140 G6VMK/P | 1241 | 179 G6IAZ/P | 832 | 218 GICFE/P | 300 |
| 24 GW4MKF/P | 5778 | 63 G4OKY/P | 3528 | 102 G6YPH/P | 2034 | 141 G6TPE | 1235 | 180 GW4REI/P | 810 | 219 G6IXS | 270 |
| 25 GW8FUM/P | 5592 | 64 G6IKU/P | 3496 | 103 GIAWD | 2016 | 142 G1DVI | 1232 | 181 G6NDQ/P | 800 | 220 G6YTR/P | 250 |
| 26 G4CYA | 5525 | 65 G4PPM/P | 3408 | 103 G4MDP/P | 2016 | 143 G6WOI | 1204 | 182 GM6WAZ/P | 799 | 221 G1F10 | 240 |
| 27 G6EKR/P | 5481 | 66 G4SKG/P | 3381 | 105 G6XYI/P | 1989 | 144 GIAAJ/P | 1200 | 183 GIFVR | 756 | (G6OLK/A | 210 |
| 28 GIFKN/A | 5162 | 67 G6HNB/P | 3366 | 106 G4VYX/P | 1980 | 145 G6TEP | 1184 | 184 G4SKA | 686 | 222 {G60LK/A G6UDE | 210 |
| 29 GM4SUC/P | 5100 | 68 EI7DG/P | 3350 | 107 G6WZI/P | 1938 | 145 GM6VDN/P | | 185 G4TSW/P | 660 | 224 G6YZR | 198 |
| 30 G4LRP/P | 4840 | 69 G4VIM/P | 3344 | 108 G61EK/P | 1900 | 147 G6ORM/P | 1176 | 186 G4CDD/P | 651 | 225 G4GFY | 190 |
| 31 G3YMD/P | 4752 | 70 G4RPO/P | 3297 | 109 G4UXY/P | 1875 | 148 G6ICI | 1173 | 187 GIDUR/P | 640 | 226 GM4TLJ/P | 189 |
| 32 G4NVF/P | 4693 | 71 G4WJS/P | 3280 | 110 G4VMM/P | 1872 | 149 G6SBR/P | 1156 | | 630 | 227 GM4BAE/P | 152 |
| 33 G6XWM/P | 4692 | 72 G4NCJ/P | 3240 | 111 G8ETD | 1818 | 150 G4LVK/P | 1148 | 188 G4WBR | 630 | 228 G4UZB | 110 |
| 34 G4NZV/P | 4641 | 73 G4XPE/P | 3222 | 112 GW1FOF/P | | 151 G4LGK/P | 1140 | 190 G6IJV/P | 627 | 229 G6RAH | 68 |
| 35 G4WIK/P | 4598 | 74 G4ROB | 3192 | 113 G4WOR/P | 1750 | 151 G6YCY | 1140 | 191 G6XUV/P | 585 | 230 G6BJR | 64 |
| 36 G6VGI/P | 4560 | 75 G6YEA/P | 3160 | 114 G4ETW/A | 1728 | 153 G6HYZ | 1110 | 192 G6NLZ | 572 | 231 G6RZZ | 57 |
| 37 G4SHC | 4550 | 76 G4TKU/P | 3024 | 115 G4NVM/P | 1700 | 154 GM6ZGV/P | 1105 | 193 GM6RJP/P | 546 | 232 GI4XSF | 42 |
| 38 G4URT/P | 4498 | 77 GIDVA/P | 2983 | 116 G6ZYL/P | 1664 | 155 GW4VPX/P | 1088 | 194 GIGGZ/A | 525 | 233 G4TVH | 32 |
| 39 G8JAG/P | 4473 | 78 G6WBP | 2980 | 117 G6EDB/P | 1638 | 156 GI4KKK/P | 1040 | 195 EI2AG/P | 520 | 234 G2DHV | 18 |

Bold type indicates a certificate winner

Certificate Winners

| Overall Winners | Bug Bashers Contest Group | GW4TTU/P |
|--------------------------|--------------------------------|----------|
| Runners-Up | Blackwood Amateur Radio Soc. | GW6GW/P |
| 3rd Place | Glamorgan Contest Group | GW6KQC/P |
| Leading Single Op. | Roger Dyke | GW4NVA/P |
| Runner-Up Single Op. | Christopher Foster | GW6MKR/P |
| 3rd Placed Single Op. | Dr. Malcolm Franks | GW4MKF/P |
| Leading English Station | Martyn Wright & Neil Underwood | G4RLF/P |
| Leading Scottish Station | David Taylor & Peter Robertson | GM4RZW/P |
| Leading Irish Station | Robert Loftus | E17DG/P |
| Leading Fixed Station | Chris Otley | G4CYA |

signal we heard was 9H1BT, who when called returned with a 5/7 report on 2.5 watts! Great, but what a pity only 0825GMT."—G4RVR/P.

At some stations the sporadic-E was less welcome. G6EKR/P was one of several groups who "could have done without the sporadic-E opening which meant that the local stations not taking part in the contest wound up their power and gave us considerable QRM".

A further report on this opening will be prepared when the information in the logs has been more carefully analysed.

All Over The Band

Many entrants again comment on how few bad signals there were. "QRP resulted in clean signals and a relatively *Practical Wireless, November 1984* splatter-free band"—G6YPH/P, was a typical comment, "congratulations go to all stations heard" says G4XPS/P, "as there were no poor quality signals noted". Not everyone would agree, as a few found, like GW6PKK/P, "a good deal of splatter across the band; it was ever present from start to finish".

The adjudicators' two monitoring stations, one in the north of England and one in the south, listened carefully for broad signals and found nothing really exceptional. We agree with GW6PKK/P (and others), however, that "some stations were using some forms of speech processing which gave rise to signals which were quite wide and the audio quality left a lot to be desired". Some, in fact, were so heavily compressed as to be almost unintelligible. Some of the "odd sounding stations" were assumed by G6EPN/P to be "due to weird and wonderful ways of obtaining 3 watts". G3UFB/P points out that some rigs which "deliver 3 clean watts of s.s.b. into a 50Ω load in the shack" may "flattop at the 2.2 watt level with a load v.s.w.r. of 1.5:1", leading to splatter.

The other side of the coin, of course, is that of the receiver's ability to handle strong signals. Some operators seem to think that there shouldn't be any strong signals in a QRP contest, but this is manifestly untrue. With so much activity from good sites and exceptional antennas, in some locations the number of strong signals at the RX front end could actually exceed those in "open" contests. It has been stated many times that a high gain pre-amplifier is a contest operator's worst enemy unless tamed by plenty of attenuation after it. "Our pre-amp was a waste of time", say GM6RJP/P, who were on one of the several sites where two or more stations operated in close proximity. "Splatter from co-sited stations was ±50kHz with the pre-amp in; once switched off the splatter went down to ±10kHz." Moral: If you feel you must use a pre-amp, make sure you can switch it off when needed.

However, the vast majority of entrants were untroubled by bad signals. Those who were, might like to spare a thought for G4WGE/A, operating at the University of Surrey, who twice had to close down while experiencing "desensitising due to the attitude control commands for UOSAT which were about 8kW e.r.p. at a distance of about 5 metres from the shack!"

Equipment Used

A similar selection of transceivers were in use as last year, with the FT-290R again the favourite. Only one station used a homebrew transceiver, the Newcastle West Contest Group G8CYW/P, though many had home-constructed accessories.

Emphasis this year seems to have been on antenna systems, so important in a QRP station. The leading three stations all used arrays of four Yagis which paid dividends. "The antennas took some getting up" at GW4TTU/P, "but worked very well indeed". A number of stations put up pairs of Yagis, and even some of the single operators managed this.

Contests always put pieces of equipment through fairly rigorous use, but GW8FUM/P took this to extremes; "the ubiquitous FT-290R showed its ability to stand rough treatment when one of our group dropped it 60m down the mountain and, although dented, it still functioned".

Three one-man portable stations, GW4XGA/P, G4ARI/P and GM4TJL/P each carried their entire stations on their back and reached their sites by walking and climbing. The most remarkable of these was John Hebborn GM4TJL/P, who reached the top of Ben Nevis. "The 11km ascent is a hard enough walk without transceivers, antennas, a portable mast and enough food and warm waterproofs to sustain life for eight hours", he says. "The top 300m of the mountain was in thick cloud . . . eventually visibility increased and I discovered I was close to the sheer drop of Observatory Gully, much nearer the summit than intended."

Superlatives

GM4TJL/P rightly claims to have had the highest altitude of any station competing, but there are some other biggest

| | TH square Ing station in square | 16 | 21 - in -6 - A | lo, of entrai n square werage no. quares wor | of |
|----------|---------------------------------------|----------|-------------------|---|--------------------------------------|
| | : 34 | | | | |
| | p* *** | XQ 1 | YQ 4 | | |
| | 10 | 7.0 | 16.0 | | |
| | | GM4TJL/P | GM4MYL/P | | |
| | 市会 | XP 1 | YP 4 | ZP 2 | |
| | 1 | 16.0 | 21.7 | 12.0 | |
| . di | the States | GM4PGV/P | GM4RZW/P | G4VYX/P | |
| 100 | WO 2 | XO 5 | YO 8 | ZO 7 | |
| me dia | 13.0 | 10.8 | 20.8 | 13-8 | |
| | GI4KKK/P | GM4PPT/P | G8JAG/P | GAVRY/P | |
| VN 1 | WN 2 | XN 2 | | | AN 3 |
| 9.0 | 19.0 | 23.5 | 19.1 | 17.1 | 24.5 |
| E14ALE/P | | GW8FUM/P | GW4NVA/P | G4XPS/P | G4SKG/P |
| | WM 1 | XM 1 | YM 18 | ZM 21 | AM 2 |
| | 17.0 | 16-0 | 16.6 | 16.6 | 12-0 |
| | EI4FO/P | | G6ZME/P | and the second se | contracted in the state of the state |
| | | | | Sector Acher | AL 18 |
| 10×10* | | 17.0 | 21.6 | 14.5 | 14.0 |
| | | | GW4TTU/P | | |
| | | 100 | | COLLEGA ALL DESCRIPTION OF | AK S |
| | | 19.2 | 17.0 | 17.5 | 21.2 |
| | | G6XYL/P | G4RLF/P | G3UFB/P | G1FKN/A |
| | | | 1 LY | | |
| | | | 17.0 | | |
| | | | GJ8RVT/P | | |

Leading Single-Operator Stations

| Pos. | Name | Callsign | Score | QSOs | Squs. | QTH | antenna | a.s.l. (m) | TX/RX |
|------|--------------------|----------|-------|------|-------|-------|----------------|---------------|----------|
| 8 | Roger Dyke | GW4NVA/P | 7616 | 272 | 28 | YN74d | 13Y | 559 | FT-225RD |
| 9 | Christopher Foster | GW6MKR/P | 7560 | 270 | 28 | YL05j | $2 \times 10Q$ | 800 | FT-290R |
| 24 | Dr. Malcolm Franks | GW4MKF/P | 5778 | 214 | 27 | YM55f | $2 \times 17Y$ | 640 | FT-290R |
| 26 | Chris Otley | G4CYA | 5525 | 221 | 25 | ZN43e | $2 \times 12Z$ | 200 | IC-202E |
| 36 | Peter Appleyard | G6VGI/P | 4560 | 190 | 24 | ZN31j | $2 \times 14Y$ | 500 | FT-290R |
| 38 | Peter Hutchinson | G4URT/P | 4498 | 173 | 26 | AK02b | 11Y | 210 | IC-251E |
| 42 | Dave Flanagan | GW6PKK/P | 4400 | 200 | 22 | YN65h | 9Y | 290 | FT-290R |
| 46 | Michael Ryder | GW6DTD/P | 4248 | 236 | 18 | YM05j | 13Y | 386 | FT-290R |
| 48 | Tim Raven | G4ARI/P | 4080 | 170 | 24 | YM65e | 8Y | 486 | IC-202S |
| 52 | David Iles | GW4XGA/P | 3933 | 171 | 23 | XN80b | 5Y | 999 | FT-290R |

80 single-operator entries

Leading Multi-Operator Stations

| Pos. | Name | Callsign | Score | QSOs | Squs. | QTH | antenna | a.s.l. (m) | TX/RX |
|------|--------------------------------|----------|--------|------|-------|-------|----------------|---------------|----------|
| 1 | Bug Bashers Contest Group | GW4TTU/P | 19 270 | 470 | 41 | YL25j | $4 \times 9Y$ | 472 | FT-290R |
| 2 | Blackwood ARS | GW6GW/P | 10 956 | 332 | 33 | YL06d | $4 \times 9Y$ | 430 | FT-726R |
| 3 | Glamorgan Contest Group | GW6KQC/P | 10 850 | 350 | 31 | YL23h | $4 \times 14Y$ | 610 | FT-290R |
| 4 | Martyn Wright & Neil Underwood | G4RLF/P | 9517 | 307 | 31 | YK10a | 6Q | 280 | TS-770 |
| 5 | Triple B Contest Group | G4WET/P | 8596 | 307 | 28 | ZM71d | $2 \times 14Y$ | 300 | IC-271E |
| 6 | David Taylor & Peter Robertson | GM4RZW/P | 8343 | 309 | 27 | YP44f | $2 \times 9Y$ | 840 | IC-251E |
| 7 | Guildford & District RS | GW6GS/P | 7776 | 288 | 27 | YL05c | 9Y | 552 | IC-271 |
| 9 | Telford & District ARS | G6ZME/P | 7560 | 315 | 24 | YM35c | $2 \times 13Y$ | 490 | FT-225RD |
| 11 | Martin Peters & Others | G4EFE/P | 7279 | 251 | 29 | ZL53b | 16Y | 297 | IC-202 |
| 12 | S. Cheshire & N. Staffordshire | G6LJO/P | 7228 | 278 | 26 | YN70f | 14Y | 270 | IC-290H |

154 multi-operator entries





















































- 1: G6YNL/P on Lowbury Hill in Oxfordshire
- 2: G3UFB/P near Lewes in East Sussex
- 3: G4ARI/P Tim Raven's back-packing station, 9th placed single op.
- 4: GW8FUM/P Manchester University ARS on Pen-Yr-Ole-Wen, Snowdonia
- 5: G1AMX William Wilson's station at Cramlington, Northumberland
- 6: G4WOR/P Worthing & District ARC on Chanctonbury Hill, Worthing
- 7: G6YEA/P The "World Domination" RC! Located on Winter Hill
- 8: G4HMB/P North East Radio & Communications Club in the Cheviot Hills
- 9: G60YL/P in its exotic location on top of a colliery slag heap!
- 10: GW4TTU/P The Cup Winners, "Bug Bashers Contest Group" nr Blackwood
- 11: GJ8RVT/P Jersey ARS, at Les Landes Racecourse, St. Ouen
- 12: G4WIK/P Devizes & District ARC on Milk Hill
- 13: EI7DG/P on Three Rock Mountain, south of Dublin. Leading Irish station
- 14: G8DDY/P with G4WNZ (right) complete with broken leg and crutches
- 15: GM4RIV/P one of the three stations of the Wigtownshire ARC 16: G4CDD/P Denby Dale & District ARS with 16-element broadside
- array known as the "Flying Bedstead", fixed in a SE direction
- 17: GW6MKR/P Christopher Foster, runner-up single op., in the Black Mountains
- 18: G4SVK/P husband & wife team on Ditchling Beacon in Sussex
- 19: GM4RZW/P David Taylor & Peter Robertson, the leading Scottish station and 6th overall
- 20: G4WWD/P Petersfield Area Contest Team (PACT) nr Hindhead, Surrey
- 21: G8CYW/P Newcastle West Contest Group on Stanhope Moor, Co. Durham

and best claims, too. "How about a prize for the longest name?", asks GW4WVB/P, the Rhosllanerchrugog Group. There also seems to be a competition on for the oddest group name, some of the contenders being "The Laugh-a-Minute Contest Group"— G4ILI/P, "The Carrot Crunchers"— G4SKA, "The World Domination Radio Club"—G6YEA/P, "The Bearded Wonders"—GW4VIX/P and "The Lincolnshire Yellow Bellies"—G4VIM/P, to name but a few.

G4PIQ claims to have used the oddest equipment, a KW Viceroy TX, Trio R600 RX and sundry bits of transverter, mainly home-made. The most unusual location must surely be that of G6OYL/P, on top of a colliery slag heap at Maltby, near Doncaster.

Several entrants bemoaned the general lack of c.w. activity (although it was up on last year), so well worth a mention are two stations who used c.w. exclusively: GM4BAE/P, who made 20 contacts and G4TVH who made 18, although 8 of these were cross-mode with s.s.b. stations.

Let's Do It Again!

So many positive comments were received about the use of low power. Here is a selection: "QRP contests are an ex-



Another aspect commented on was the "marvellous spirit throughout"— G1DWQ; "very courteous spirit"— G4WBR. "A pleasant surprise was the friendliness of many operators"— G1BEK. So many entrants remarked on how enjoyable the event was, even though they knew they weren't too near the top of the results table. "Not a winning entry", said G8SSL, "but one that reflects enjoyment".

Next year's QRP contest is eagerly awaited by most of this year's entrants. It will be on **Sunday**, 16 June 1985, 0900–1700GMT. The rules will be much the same as this year, although comments sent in with logs are being carefully considered.

We have shown the leading single operators separately this year in response to some of these comments. "I don't know how the single-operator stations manage to keep going for eight hours"— G6YEA/P. "It takes a fair bit of effort... doing the check log, turning the mast, keeping the log all by yourself"— G4JBR/P. However, we resist two separate sections, as that would discourage one form pooling resources with a friend. Likewise a fixed station section would remove the incentive to go portable, which is essential to get the best out of QRP.

In conclusion, congratulations to the cup winners, certificate winners and all who put such an effort into their entries. Thanks to all those who sent entries and comments, including those (many) who could not be included in this summary, and thanks to those non-participating stations who sent checklogs; G1AZJ, G2HIF/P and G8RZO. Finally, good luck in the next *Practical Wireless* 144MHz QRP Contest, 16 June 1985.





If you are an aspiring RAE candidate or just feel like testing your knowledge of amateur radio these multiple choice style questions will fill your needs. The questions are typical of those appearing in both the RAE papers; but they are not taken from these papers. For the answers, together with explanatory notes to help you, please turn to page 70.

Paper 2 Section 3. Solid State Devices-amplifiers

Question 2–1

The gain of this audio stage can be increased by putting a large capacitor across



Paper 1 Section 1. Licensing Conditions-log /M and /P

Question 2–2 When operating /M or /P you should fill in the log

- a. within 24 hours of the commencement of operating
- **b.** as soon as possible after the end of a journey
- **c.** at the time of operating
- d. immediately at the end of a journey

Paper 2 Section 2. Electrical Theory

Question 2–3 What current will flow through a 24Ω resistor connected across a 12 volt battery?

| 🗌 a. | 0.5 amps |
|------|----------|
| □ b. | 5 amps |
| 🗆 c. | 12 amps |
| 🗌 d. | 24 amps |

Paper 1 Section 1. Licensing Conditions-special recordings

Question 2–4

Which of the following special recordings may be transmitted?

a. a triangular wave with a constant frequency
 b. two sine waves both with frequencies varying within the audio spectrum
 c. a rectangular wave with a pulse repetition frequency within the audio spectrum
 d. a sine wave with a constant ultrasonic frequency

Practical Wireless, November 1984

0+12V



Reports to: Eric Dowdeswell G4AR, 57 The Kingsway, Ewell Village, Epsom, Surrey, KT17 1NA. Logs by bands in alphabetical order.

The direct conversion type of receiver (d.c.r.) is very popular and is often the first constructional effort of the tyro s.w.l. It is cheap to make and needs virtually no alignment and will often work the first time it is switched on. A block diagram of the simple d.c.r. is shown in Fig. 1 and since there is a local oscillator and a mixer stage it is often thought to be essentially a superheterodyne receiver. It is! But because the local oscillator is on the same frequency as the incoming signal the intermediate frequency (i.f.) is zero! There are no i.f. amplifying stages, the output going through an audio filter to the audio amplifier.

In a conventional superhet the overall selectivity is provided by a filter following the mixer stage and may be a mechanical, crystal or ceramic in its design. In the d.c.r. this selectivity is provided in the audio filter only, any r.f. tuned circuits providing little in the way of desirable selectivity. Unfortunately many d.c.r. designs treat the filter as just another audio filter without realising its importance in the overall design.

I found the filter circuit Fig. 2 in my notebook. The original source is unknown but obviously I must have thought it worthy of note at the time. It is fairly easy to make it up on a piece of circuit board and to use it to replace the existing filter and in this way either filter can be tried out by simply changing over the input lead to one filter or the other. The inductors L2 and L3 are made from the familiar 88mH toroids used in RTTY terminal units, which are advertised in PW and elsewhere, except that the existing winding should be increased by about 50 turns of 28s.w.g. enamelled copper wire. The capacitors of 0.053µF can be made up with a $0.05\mu F$ and a $0.003\mu F$ in parallel while the $0.08\mu F$ is formed from 0.05µF and 0.03µF in parallel.

The frequency response of this filter should be something like that shown in Fig. 3. The input capacitor provides cutoff at the lower frequencies. The other capacitors should be of the Mylar type or something similar, and ± 10 per cent is suitable. The inductors L1 and L4 are "standard" r.f. chokes comprising three windings in series on a 6mm ($\frac{1}{4}$ in) diameter former.

On an entirely different matter, a common complaint from s.w.l.s, and licensed operators come to that, is the "gabbling" of callsigns, to the extent that the call is not understandable even with a strong signal. While foreign amateurs can be excused if they cannot get their calls over in



WAD241 L1-4 see text

English there is always the international phonetic code which should solve the problem. Even the sometimes hilarious phonetics like "jolly, jumpin dog" for the JJD suffix, is acceptable if it does the trick. I have come across this problem myself, principally on the 144MHz (2m) v.h.f. band, and it has to be said that the "gabbler" is all too often an ex-CBer.

One would think that the ex-CBer would drop the CB jargon and habits and learn the accepted amateur procedures. Stations operating mobile seem the worst offenders perhaps because of the exhilaration of speeding along a motorway but this is just the time when extra care should be taken. You should always remember that an amateur callsign is unique to the owner and one's habits, language and procedures on the air are a reflection of the operator.

There is little doubt in my mind that the best amateur operators are those who have "come up through the ranks", as it were, having spent some time listening on the bands making themselves conversant with normal amateur procedures, as well as by reading the various magazines that deal with amateur radio such as PW, SW Magazine and Radio Communication, better known as RadCom, the official journal of the RSGB. The Society's publication Amateur Radio Operating Manual is a must for the beginner and experienced operator alike and well deserves to be known as the "bible" of amateur radio. It is also a mine of information for the s.w.l.

1kHz

5kHz

10kHz

General

100Hz

Stephen Beare's monthly contribution would normally appear in the DX section but unfortunately he is now unemployed and has had to sell his Trio 9R59DS receiver, so no log this month. However the good news is that Stephen, down in Feoch, Truro, Cornwall, has passed his RAE "without even trying" as he puts it, but I admit he did say beforehand that he was entering the exam just to gain experience. He is worried at the number of CBers who can pass the RAE without any previous s.w.l. experience and "wreak havoc on the v.h.f. and u.h.f. bands."

Stephen intends to make a QRP rig and in the meantime neighbour G4KNY is helping with the code practice. In the interim let us hope that one of the interviews Stephen has organised will have come up trumps by the time this appears in print. Incidentally, Stephen raised a point in this column a while back concerning Beverage antennas and was delighted to receive some copies of QST articles on the subject from Stein Isaksen LA7CF.

I seem to be losing my regulars right, left and centre! Now DXer Paul Martin of Poole, Dorset, says he has passed his RAE and is anxiously awaiting his callsign. He can't make up his mind about going on with the code practice and getting an "A" ticket. So I have ordered him to get on with it, which is always my advice! I know how much he wants to get cracking, working everyone he can find on 144MHz, but there are slow Morse stations around the country in the RSGB's Slow Morse service and Paul should take advantage of this while on 144MHz as he is almost certain to need to operate on the h.f. bands at some time in the future. He is very interested in RTTY and the 430MHz band at the moment.

If any of you out there who are practising for the Morse test feel that you are having a hard time a story in the latest issue of the RAIBC's journal Radial may stop your grumbling! The story came to light on the death of Arthur Byrnes G6AB. Dick Boydell, now G3VOA, told the RAIBC about his severe disability which meant that the Morse code could only be sent using his feet. "The next thing I knew was a knock on the door and there was Arthur G6AB!" He took an outline of one foot and not long after came back with an electronic bug foot key using side-operated switches, and a speaker. "After a year's hard work I was able to pass the code test, since when the el-bug has been hooked up to my transmitter"

Later G6AB was able to fix Dick up with a c.w. reader since he is unable to write anything and previously had to remember it all in his head. Information on the workings of the RAIBC can be got from Francis Woolley G3LWY, 9 Rannoch Court, Adelaide Road, Surbiton, Surrey.

Anent my bit on the headphones/speaker switching unit in the August issue Brett Lanoish G4NZK of Rednal, Birmingham, mentions a friend, G2FXJ, who through continued use of headphones found that he was starting to rely upon them, using the speaker less and less. He also developed a "ringing" in his ears. The point Brett makes is that one should only use headphones for the weaker signals and not let them become a habit. Personally, I have used headphones all my life and have that singing in the ears but I blame it on the fact that I spent some 8000 hours as a radio op in Dakota aircraft where the RO sits right alongside the port propeller with an unbelievable high ambient noise level!

QRP Corner

G. E. Slingsby of Bury St Edmunds, Suffolk, has passed his RAE, congratulations, but admits he is unable to afford the prices of commercial transceivers so is hard at it on the Morse code in order to get his "A" ticket right away and have a go at constructing a QRP outfit, and wonders where he can get some circuits and other useful information. The G-QRP Club's *Circuit Book* ought to fill the bill, obtainable from the club or the RSGB Publications department for $\pounds4.19$ p&p, for non-members. In passing it should be noted that one does not have to be a member of the RSGB in order to buy its publications.

_____ on the air 📼

Membership of the G-QRP Club is really a must for the QRP operator anyway. Possibly the most economical way of getting on the air with QRP is the direct conversion receiver in which the local oscillator, which works at the signal frequency, more or less, can be switched to act as the transmitter or as a driver for a QRP p.a. stage, mentioned earlier. (See the PW "Teme" series, beginning in this issue—Editor).

Dave Dhuglas GM4ELV up in Glasgow continues the good work with his QRP Ten-Tec Argonaut 509 and a trapped dipole multi-band antenna at 15m and an a.s.l. of 155m, but he reckons the bands have been pretty poor of late, reflected in his short log this month. On 21MHz he managed a QSO with RJ6R in the Pamir mountains, with cards to UJ8JJ, and SPOPBT a special event station with QSLs to SP1PBT, this on 14MHz. On 7MHz he managed EI4JDX with cards via the Irish bureau. All these contacts were on s.s.b., by the way. It is worth mentioning that Dave came first in the G. Marconi QRP contest (s.s.b.-all bands) with a total of 43968 points but it seems that the contest may not be held again as the Italian ORP club is now defunct, according to IOOAY. Dave says cards for the ON5NT/HBO operation should go to ON4FK while JW5NM can be QSLed through LA6NM.

Phil Dykes G4XYX continues to go from strength to strength with his QRP converted CB f.m. rig and a wire dipole for the 28MHz band. A bout of 'flu kept him home for a while (oh dear, what a shame!) and found the band open most days working 207 stations in 27 countries, often able to sustain a OSO for half an hour or so. He worked LU1HCO and LU7HEA, CE3HFI, with many contacts around Europe. Of interest were W3ZNB/HB0 with cards to DA2AA, and I2DMK/IL7, QSLs to I2MQP. Phil is starting to build the PW Severn QRP rig for the 7MHz band to open up an entirely different aspect of amateur operating, namely c.w. on a band famed for the QRM.

Don't overlook the QRP Convention being run by the Yeovil club on Sunday October 14 at Preston School, Monks Dale, Yeovil, with talk-in starting at 9am, the convention opening at 9.30. There are five lectures on AR topics, the show ending at 5pm. Light refreshments available and a pub not far away. Club stations G3CMH and G8YEO will be active and there will be a display of equipment and a junk stall. Further info from Eric Godfrey G3GC on (0935) 75533.

Bill Stevenson G4KKI is still going

strong in the QRP mode with his latest success, a Trans-Atlantic c.w. QSO on the 7MHz band with W3GM. His normal power output is 750mW (0.75W) to a 27m wire which he tries to keep aloft with a Delta kite! Otherwise it's been round Europe on the 3.5MHz band. He has had problems with static build-up on the antennas but as I pointed out to Bill he should always have an r.f. choke between the wire and earth to provide a d.c. path for the static voltages without affecting the signal voltages. Bill is about to acquire a caravanette and hopes to have a lot of fun next year going portable. Current project is a direct conversion receiver covering the 21, 14 and 7MHz bands.

DX Bands

Regular writer David Price of Wellington, Somerset, is yet another to announce his success in the May RAE so congrats all round and good luck on the bands. He's going to get his "B" licence but is swotting madly for the code exam. Good lad! He'll be too busy working the stuff soon to be able to send logs in future so this could be the last report from David. Only DX of note on 21MHz was 9J2BO but on 14MHz it was YS1RT, RJ6R (QSL UJ8JJ), VU2CVP, FY7AN, HL9SP. OD5NT, and VQ9AC on Chagos Island with cards to KA3EDN. Catch on 7MHz was VU2CVP again, and on 3.8MHz an excellent catch for this time of the year in VK2AVA at 2100Z.

I'm told that there were 8000 successful candidates in the last RAE and I think it must have included all my regular correspondents! Very few ordinary DX logs this month so far. Michael Newell of Kenilworth, Warks, says he has passed the RAE and is now G1HGO so I suppose we must congratulate him also. He is busy on 144MHz now with an FT-290R and a whip antenna and seems to have got into all the local repeaters. I have told him that I expect him to get on with the code and pass the test. He seems a bit reluctant to try s.s.b. on 144MHz but, contrary to his expectations, he may work a lot more DX on s.s.b. than he ever will on f.m.

Reception logs from s.w.l.s are welcomed and should be with me by the 15th of the month. For those who can write in regularly I can send them a few



Surbiton, Surrey KT6 4TE.

Practical Wireless, November 1984



In July, members of the Bury RS visited the IBA TV transmitters at Emley Moor, West Yorkshire, if only to drool at the 275m concrete mast supporting a further 56m of mast and antennas! This mast replaces an earlier one which collapsed in March 1969 due to severe icing-up. The 432MHz and 10GHz beacons GB3MLY and GB3MLE are housed in the microwave link room at the 275m level

(Photograph courtesy of the Bury RS PRO G3VNQ)

Club News

Club AGMs are starting to occupy clubs and I would remind secs that if they send me the club's winter programme then there is no need to write every month unless there are any significant changes, plus details of meeting place and days and time. May I also suggest that clubs that only meet once a month should consider meeting more often in order to maintain interest and to give members a wider choice of dates.

308 ARC Another reminder of the bringand-buy junk sale on Tuesday October 9 at St Marks Church Hall, Church Hill Road, Surbiton, Surrey. Cheques accepted and coffee and tea dispensed. It is suggested that this is a good opportunity to please the XYL by getting rid of the junk in the bedroom! More details from sec Dave Davis G6YQD, 13 Maple Road, Surbiton, Surrey.

Acton, Brentford & Chiswick ARC G3IIU The 430MHz band will be the subject for G6BLT on Tuesday October 16, at 7.30 at the Chiswick Town Hall, High Street, Chiswick, London W4, with new members and visitors most welcome, says club sec W. G. Dyer G3GEH. 188 Gunnersbury Avenue, Acton, London W3.

Axe Vale ARC First Fridays at The Cavalier, West Street, Axminster, at 7.30. Principal event in December is the annual dinner on Friday December 7. No further details available unless you contact the sec Roger Jones G3MYK, 10 Oak Tree Close, Upottery, Honiton, Devon.

Banbury ARS Last Thursday of the month at St Paul's Church Hall, Banbury, with latest





Two interesting QSL cards received by Denis Norton of London W6, 9N1MM seems to have been around the bands from the year dot. He is seen here with a group of Nepalese children. The other card is from a rare DX spot, Clipperton Island, activated by F6EAY as FB8WJ

details from J. Burrell G8OZH, 6 Blenheim Croft, Brackley, Northants, otherwise (0280) 702900.

Braintree & District ARS G6BRH First and third Mondays at the Braintree Community Centre, Victoria Street, Braintree, with doors open from 7.30, with the odd bit of bartering of gear allowed up to formal start time of 8pm. Your local net is G6BRH on 145.375MHz (S15) on non-meeting Mondays at 8pm. More info on meetings and events contact sec Pat Penny G6TAF, 13 Newnham Close, Braintree or buzz (0376) 26487.

Basingstoke ARC G3TCR G8JYN Second Tuesday at 7.30, the Swan Inn, Sherbourne St John, near Basingstoke, with the AGM scheduled for October 9. November's offering on the 13th is to be a constructor's contest so get cracking. Advance notice of the club's Christmas Social, on December 11. Your sec is Eddie Thompson G4SQZ, 21 Wigmore Road, Tadley, Basingstoke, Hants.

Biggin Hill ARC G4RQT G6TBH It's construction contest time again, Tuesday October 16 in St Mark's Church Hall, Church Road, Biggin Hill, Kent, at 8.30pm, so bring along your best bit of homebrew equipment for judging. Hon sec is Ian Mitchell G4NSD, Greenway Cottage, Tatsfield, Westerham, Kent or try (09598) 376.

Bridgend & District ARC Third Friday of the month with the first Friday being a natter night, plus on-the-air sessions, all at the YMCA, Bridgend, in Angel Street. October's main meeting will be devoted to the AGM, while in November a homebrew contest is planned. Your contact is Trevor Morgan GW4SML, 4 Rhiw Tremaen, Brackla, log sheets on receipt of an s.a.s.e. Copies of logs are not necessary, just a selection of perhaps a dozen of the best DX heard, with QSL information if copied.

It might be as well to outline what constitutes "best" DX. It is not necessarily the furthest stations heard, like the VK's which can be copied most mornings on 14MHz and are therefore commonplace, but DXpeditions to spots seldom activated by amateurs, unusual prefixes, or reception of a station at an unusual time of day or night due usually to exceptional propagation conditions.

Most s.w.l.s are anxious to log signals from as many different countries as possible or vie for the greatest number of prefixes heard so information in this feature can be very helpful as a guide to which band such stations may be found. Although the 14MHz band is the one which most DX can be found it is a good idea to monitor the other bands. The 21MHz band can prove an eye-opener at times. Although the sunspot cycle is now on the downward trend 28MHz should not be ignored, generally during daylight hours, with principal reception on a north/south path.

The 3.5MHz band can still bring surprises during hours of darkness as witness one reader with a VK2 recently. Most receivers used by s.w.l.s have coverage from the 1.8MHz to 28MHz bands so why not make maximum use of these facilities.

Bridgend, Mid-Glam.

North Bristol ARC G4GCT Friday evenings at 7pm, the Self-Help Enterprise, 7 Braemar Crescent, Northville, Bristol. Much more info from Ted Bidmead, 4 Pine Grove, Northville, Bristol.

South Bristol ARC G4WAW Wednesdays at the Whitchurch Folk House, East Dundry Road, Whitchurch, Bristol, at 7.30. On October 10 the club's winter project will be formulated and on the 17th it's computer activity time under the auspices of G4WOD. October 24 will be spent discussing the 1985 events calendar, leading on to a bring-and-buy evening on the 31st. If you need to know more try Len Baker G4RZY, 62 Court Farm Road, Whitchurch, Bristol, or 'fone (0272) 834282.

British Railways ARS The society has some 80 members garnered from the railways and associated companies and their AGM will be held at 1pm on Saturday October 20 at Stanier House, Birmingham. This is close to New Street Station and off Stephenson Street and all members are urged to attend. More on the society from G. Sims G4GNQ, 85 Surrey Street, Glossop, Derbys.

Bury RS A construction contest will be judged on Tuesday October 9 this being the second Tuesday of the month which are considered main meetings, with other Tuesdays being more informal. So, Tuesdays it is, at the Mosses Community Centre, Cecil Street, Bury, at 8pm. Newcomers are invited to contact hon sec Brian Tyldsley G4TBT, 4 Colne Road, Burnley or try Burnley 24254, for more gen on club matters and meetings.

Cheltenham ARA G5BK Friday October 5 sees a combined meeting with other local societies, otherwise it is first and third Fridays at the Stanton Room, Charlton Kings Library, Cheltenham. More on the club from Mrs G. Harmsworth G6COH, 42 Leckhampton Road, Cheltenham or ring Cheltenham 525162.

Cheshunt & District ARC G4ECT G6CRC Every Wednesday at 8pm, the Church Room, Church Lane, Wormley. October 10 has a film show run by G3TIK and on the 24th G6BTQ holds forth on coaxial cables. Otherwise it's natter nights. Don't forget that the club can put you on to local RAE and Morse code classes. AGM time is November 21 so don't say you haven't been warned. Try Jim Sleight G3OJI, 18 Coltsfoot Road, Ware, Herts for more info or buzz (0902) 4316.

Chester & District RS G3GIZ G8GIZ Tuesdays, except the first, at 8pm the Chester RU Football Club, Hare Lane, Vicars Cross, Chester, with code practice for half an hour beforehand, courtesy of G4MOU. October 4 is a night out with a visit to the local IBA radio "Marcher Sound" while on October 16 it's RTTY Telereader time with G3LEQ officiating. G4UXD and G4EWZ expound on the latest equipment on the 23rd and G8AWS deals with amateur satellites on the 30th. Your club PRO is Dave Hewitt G8ZRE, 31 Broadmead, Vicars Cross, Chester or (0244) 316673.

Civil Service ARS G3CSR/A First and third Mondays at 12.30pm in the CS Recreation Centre. Monck Street, Westminster, London SW1 with an operational rig to hand. Net time is 7.30pm on Tuesdays on 144-575 (S23) and at 8pm on 3.720MHz. More from George Costin on 01-632 3875 who is the club sec.

Coulsdon ATS G4FUR Second Monday at St Swithun's Church Hall, Grovelands Road, Purley, Surrey, at 8, plus the last Thursday same time and place, when Morse code practice seems to be the order of the day. Ring Richard Goring G6VYT, the club's PRO, on Downland 54319.

Dartford Heath DF Club Needless to say frequent DF hunts are laid on and the organiser is Pete G8DYF to be found on Greenhithe 844467. Pre-hunt gatherings are held at the Horse & Groom, Leyton Cross, Dartford Heath, Dartford, Kent, after 9pm.

SE Derbyshire ARS Tuesdays during term time at the SE Derbyshire College, Ilkeston Road, Heanor, at 7.30pm with talks or other attractions laid on. Sec is W. F. Peck G4VNB of 2 Sandfield Avenue, Ravenshead, Nottingham.

Dudley ARC G4DAR The Allied Centre, Greenman Alley, which is off Tower Street, Dudley, first, second and fourth Mondays according to letter received but could conceivably be every Monday. Note the AGM is on October 22. Note for the future, the demo by the Microwave Society on November 19. Meeting time is 7.45pm. Cheryl Wilding G4SQP. the sec, can be found on Codsall 5636.

Dunstable Downs RC G4ARD G4DCC G8DCC Two films on October 12, *The Electric Wave and Opportunity at Sizewell* while on the 26th there is a talk on h.f. antennas. Meetings every Friday at 8pm, the Chews House, High Street South, Dunstable, Beds. Sec P. G. Deaford G8XTW, will be glad to hear from visitors or potential members on. (0525) 384419. **On the air** Edgware & District RS G3ASR Second and fourth Thursdays at 8, 145 Orange Hill Road, Burnt Oak, Edgware, Middx, with a talk likely on October 11 plus an on-the-air session. November 8 is an "Emmet" key evening with dummy loads and power meters to the fore. Will it descend to touching the ends of two pieces together, I ask myself! Try sec John Cobley G4RMD on Hatfield 64342 for more gen on the club and it's activities.

Fylde ARS Still going strong at the Kite Club, Blackpool Airport, first and third Tuesdays at 7.45. Outings and visits to interesting venues are frequent. Make a note of the junk sale on November 13. Sec. H. Fenton G8GG of 5 Cromer Road, Lytham St Annes, is also on L-St-A 725717.

Gloucester ARS St John Ambulance HQ, Heathville Road, Gloucester, every Wednesday starting around 7.30, plus frequent outdoor activities. Visitors most welcome at any meeting. Tony Martin of 12 Redwood Close, Podsmead, Gloucester, is club sec.

Hastings Electronics & RC G6HH G1HHH Third Wednesdays at 7.45pm, West Hill Community Centre, Croft Road, Hastings, for main meetings and the clubroom at Ashdown Farm Community Centre, off Harrow Lane on Fridays at 8pm. On October 17 there is a junk sale and make a note of the Christmas Social on December 19. Sec Dave Shirley G4NVQ lives at 93 Alfred Road, Hastings and I'd like to ask him to note my correct change of QTH as in spite of a letter from me the club mag still goes to my old QTH.

Hornsea ARC G4EKT G6EKT Coming up! Hamfest on Sunday October 21 at the Floral Hall, Hornsea, with special event station in action, junk plus bring-and-buy stalls. The show will cover radio, computers and electronics generally. Normal venue is the Mill, Mill House, Atwick Road, Hornsea, with weekly meetings at 7.30 on Wednesdays, with a lecture to start off preceded by a code class. Secretary Norman Bedford G4NJP can be found on (0262) 73635.

Harrow RS Every Friday night at 8pm the Harrow Arts Centre, High Road, Harrow Weald, Middx with a constructional contest taking place on October 12 and G4UBB dealing with counterpoise design on the 19th. Other Fridays are informal with a practical aspect, together with a Morse code class. The PRO is Dave Atkins G8XBZ, 25 Maxwell Close, Rickmansworth, Herts or Rickmansworth 779942.

Inverness ARC GM1DZU GM4TPF Thursdays at 7.30 at the Cameron Youth Club, Planefield Road, Inverness. The Gaelic Mod in Inverness will be the occasion to have a special event station operating on the h.f. and 144MHz bands, GB2MOD, from October 12 to 19 with Gaelic-speaking ops in attendance. Needless to say the special QSL card will be worth having. Lots more details from sec David Jones GM4SXD, Beachan, Farr, Inverness also on (08083) 240.

Ipswich RC G4IRC Second and last Wednesdays at 8 in the club room of the Rose & Crown, 77 Norwich Road, Ipswich. This is a detached room and it is not necessary to go through the pub to reach it. Thought I'd just mention that point. A night on the air with the club station is planned for October 10 with a bring-and-buy sale on the 31st but note that this will take place at the Barrack Corner Church Hall. The annual social get-together is planned for November 21 but before that G4BJO will talk about weather fronts and radio propagation on the 14th. More details from this very active club from Jack Tootill G4IFF, 76 Fircroft Road, Ipswich, Suffolk or buzz him on (0473) 44047.

East Lancs ARC A new one for the column I think. Meets first Tuesdays for a lecture, demonstration or suchlike, and on the last Tuesdays of the month for an informal gettogether, at the Conservative Club, Cliffe Street, Rishton, at 7.30. For more details on the club drop a line to the PRO Stuart Westall G6LXU, 430 Blackburn Road, Accrington, Lancs where also resides Accrington 393457.

Leith Nautical College AR & EC GM4AXG Meetings start again in October, every Monday at 6pm in the T2-4 electronics lab of the college, a wide range of test equipment and facilities being available for use. Lucky lads! The club station sports an FT-101E and FT-221R. Students and past students and evening class students are most welcome as are s.w.l.s and members of the general public. Further info from sec/treasurer Susan Beech GM4SGB who can be contacted via the college.

Lincoln SWC G5FZ G6COL Second and fourth Wednesdays at the City Engineers Club, Central Depot, Waterside South, Lincoln at 8. Intervening Wednesdays are c.w. and RAE evenings with instruction on both. October 10 has a slide show on the western USA and Canada, with an activity night-cumnight on the air on the 24th. The Christmas family get-together is scheduled for December 12 this year. More info on the club from Pam Rose G4STO at the club QTH.

Manchester University ARS G3VUM G8FUM Every Wednesday afternoon during term time at the radio shack which is located on the first floor of the Students' Union building, next to the Main Debating Hall, with visitors always most welcome. Sec is Khee Chan G5MUR MUARS, Students' Union, Oxford Road, Manchester M13 9PR.

Mansfield ARS First Friday and third Tuesday of the month, Victoria Social Club, Princes Street, Mansfield, Notts, with a lecture on satellites down for October 5, by G4CUO, and the 16th being a natter night. On November 2 G4AFJ of the RSGB's Repeater Committee will be talking on that subject. This year's Buffet Disco is down for December 7. Hon sec is Keith Lawson G4AAH, 223 Southwell Road West, Mansfield, Notts.

Newark & District ARC Still going strong with gatherings first Thursdays at the Palace Theatre, Appletongate, Newark, at 7.30. A special meeting was held recently to bring together new and existing members and those who had lost touch with the club of late. The winter programme will cover lectures on satellites, RAYNET activities and code practice evenings. There is also an informal meeting around the middle of the month at a local pub where YLs, XYL's of OM's are welcome, and vice versa of course! Club net is on 144.525MHz f.m. Monday at 8pm with more info from sec Michael Gayler G4SDZ, 58 Fosse Road, Farndon, Newark, Notts or (0636) 702076.

ARC of Nottingham G3EKW G6CW G8IUT Every Thursday, 7.30, the Sherwood Community Centre, Mansfield Road, Nottingham, with G4NJH speaking on his trip to



MICROWAVE MODULES LIFO

AS IF DIDN'T ALREADY KNOW. YOU

Microwave Modules Ltd. Is a full time professional organisation, established over 15 years ago in 1969, and currently employs over 30 full time, on site staff based in our two modern, purpose built factories. In addition, a similar number of 'Outworkers' are involved in assembly and mechanical operations.

OUR EXTENSIVE RANGE . . .

Our product range now exceeds 50 Individual items in total and is the widest range available from any one manufacturing company. Our technical resources have enabled us to not only become the largest and most successful designer and manufacturer of R F Products, such as Linear Amplifiers and transverters, but also designers and manufacturers of innovative microprocessor and digital products such as The Morsetalker, MMSI, and the RTTY to TV decoder, MM2001.

.L British . . .

Every product in our range is designed and manufactured in the UK by our own employees, and wherever possible British Components are utilised.

GUARANTEED . .

All Microwave Modules Products are Fully Guaranteed for 12 months. This includes all semi-conductors and PA Transistors. We have built our reputation around our customer service and back-up which is second to none.

OUR RANGE OF LINEAR AMPLIFIERS . . .









MMI 144/30-LS

MML144/50-S

MML144/100-LS

MML144/200-S

| | INPUT | OUTPUT | MODES OF | PRE AMPLIFIER | | POWER | RF• | | | | | | | |
|---------------|-------------------|--------|-----------|---------------|-------------|--------------|------------------|---------------------|-------------|--------------|---------------------|---------------|--------------|---------------------|
| PRODUCT | POWER | POWER | OPERATION | GAIN | NF | REQUIREMENTS | vox | PRICE INC VAT | | | | | | |
| MML144/30-LS | 1 or 3W | 30W | SSB. | | | 13.8V @ 4A | \checkmark | £75 (p&p inc £3) | | | | | | |
| MML144/50-S | 10W | 50W | FM. | | | 13.8V @ 6A | V | £92 (p&p £3) | | | | | | |
| MML144/100-S | 10W | 100W | | FM. | FM. | FM. | 12dB | <1.5dB | 13.8V @ 12A | \checkmark | £149.95 (p&p £3.50) | | | |
| MML144/100-HS | 25W | 100W | AM. | (1550 | | | | | | | | 13.8V @ 12A √ | \checkmark | £149.95 (p&p £3.50) |
| MML144/100-LS | 1 or 3W | 100W | cw. | | | 13.8V @ 14A | V | £169.95 (p&p £3.50) | | | | | | |
| MML144/200-S | 3, 10 or 25W 200W | CVV. | CVV. | | 13.8V @ 30A | \checkmark | £245 (p&p £4.50) | | | | | | | |





| | INPUT | OUTPUT | MODES OF | PRE AN | IPLIFIER | POWER | RF• | |
|-------------|---------|--------|-----------------|--------|----------|--------------|--------------|---------------------|
| PRODUCT | POWER | POWER | OPERATION | GAIN | NF | REQUIREMENTS | vox | PRICE INC VAT |
| MML432/30-L | 1 or 3W | 30W | SSB. | 12dB | 2dB | 13.8V @ 6A | V | £139.95 (p&p £3.50) |
| MML432/50 | 10W | 50W | FM, AM, ATV. | 12dB | 2dB | 13.8V @ 8A | \checkmark | £129.95 (p&p £3.50) |
| MML432/100 | 10W | 100W | CW. | _ | - | 13.8V @ 20A | V | £245 (p&p £4.50) |

CONNECTORS . . .

144MHz Products — Our standard connector on these products is SO239. We use a high quality PTFE socket of superior quality, but we are able to supply the choice of BNC or 'N' type at no extra charge. Please specify.

432MHz Products - The MML432/30-L is fitted with BNC connectors, 'N' type available, please specify. The MML432/50 and MML432/100 both have BNC input sockets and 'N' type output sockets. If this is not to your preference please specify when ordering.

DATA SHEETS

A full printed data sheet is available on each product, and is free on request.

CATALOGUE ...

A copy of our latest catalogue can be obtained by sending a large SAE (23p) or by sending 40p in stamps to the address below

RALLIES & EXHIBITIONS ... Our entire range of products will be exhibited and on sale at the Leicester Show.

Come and take a closer look.

AVAILABILITY Our products are normally available from stock, either direct from ourselves or any of our 75 UK outlets.



MICROWAVE AODULES BROOKFIELD DRIVE, AINTREF, LIVERPOOL L9 7AN, ENGLAND Telephone: 051-523 4011. Telex: 628608 MICRO G.

CALLERS ARE WELCOME. PLEASE TELEPHONE FIRS

HOURS: MONDAY-FRIDAY 9-12.30, 1-5.00 E&O.E.

RADIO AND TELEVISION SERVICING

1983-84 MODELS

Editor: R. N. Wainwright, T. Eng (CEI), F.S.E.R.T.

This volume, like its predecessors, continues to provide the only comprehensive reference source for a large range of domestic entertainment products currently available from retail outlets.

The first part of this volume contains manufacturer's circuits and service information for the main classes in a wide selection of colour and monochrome receivers. The second section presents a selection from the numerous available types of audio equipment, including portable and clock radios, in-car units, cassette recorders, personal-portables and unit audio systems. The usual addendum gives cross-references to relevant information detailed in earlier volumes, together with supplementary servicing information abstracted from the technical bulletins issued by the manufacturers during the year.

Price: £24.25 On sale now

Previous volumes are still available. Enquiries to the Sales Department, Macdonald & Co.

From booksellers, or in case of difficulty, please use the coupon below:-

To: Cash Sales Dept. Macdonald & Co., Maxwell House, Worship Street, London, EC2A 2EN.

Please send me.....copy(ies) of RADIO AND TELEVISION SERVICING 1983-84 MODELS.

I enclose a cheque/PO made out to Macdonald & Co (Publishers) Ltd for Please allow 28 days for delivery.

I prefer to pay by Barclaycard Access American Express Diners Club My card number is

| SignatureDate | |
|---------------|----|
| Name | |
| Address | |
| | |
| | PW |

a BPCC PLC company

| GAREX | THE SCANNER SPECIALIS WITH 4 GREAT PRODUCTS | |
|--|---|---|
| J.I.L. SX-200-N – THE SU * The choice of the profe * AM + FM all bands * Wide coverage: 26-88, * 16 memories * Positi * Proven reliability * 13 * S-meter & 96-108MHz | ssionals 108-180, 380-514MHz ive action keyboard 2v DC & 230v AC | £299 |
| REVCO RS-2000-E - THE * 70 memories * AM * Cover: 60-180, 380-5201 * Search & store of active * All the usual search & s * 12c DC & 230v AC oper * Counts activity of select | + FM all bands MHz e channels scan functions ration | £259 |
| REVCO RS-160 – FM POC * Incredible 160 memorie * Positive action keyboar * Covers 26-32, 68-88, 13 * Scans, searches & store * With nicads, charger & | es (4 banks of 40) d 8-176, 380-512MHz es active frequencies | £249 |
| Computer interfacing for control & data logging Switchable channel spather I.F. output terminals (10 Specifications set by the | gaps) comatic or programmable) or limitless memory, remote acing & I.F. bandwidths 0.7MHz & 455KHz) e professionals | £598 |
| A superb quality 16 el broadband fixed station to all scanners ar Covers 50-50 | r for SX-400 REVCONE ★ ement, all British made VHF/L n aerial from Revco. Ideally sui od other VHF/UHF Receivers 10MHz PRICE £24.95 inc ECONDHAND SCANNER BARG | JHF ited |
| ★ SP CENTURY 21D comm CW, USB, LSB, AM & I an external speaker ar former for only | ECIAL OFFER ★ unications receiver. 0.5 to 30M FM. Digital readout. Provisions nd headphones. An excellent p £ | for per- |
| RESISTOR KITS a top set 5% carbon film, 10Ω to 1m or $\frac{1}{2}$ W (state which). Starter pack 5 each value Standard pack 10 each value Standard pack, 25 each $\frac{1}{2}$ W + Giant pack, 25 each value DC/DC TRANSISTORISEI rectified and fully smooth This unit is a chassis set tidied, fully wired & teste cabinet. 24v version – sar | Ilue (610 pieces) W (610 pieces) (1525 pieces) D INVERTERS 12V input, 400V ied output ction cut from used R/T equi ed. Free-standing but no luxur | t £3.00 k. series, ting ¹ W .£3.10 .£5.55 £13.60 200mA .£9.50 pment ies like |
| WESTMIN also Cambridge, Vang | OR PYE RADIOTELEPHONES ISTER & PF70 SERIES uard etc. SAE for free extensive | |
| Ready Assembled, full instr places existing squelch board Cambridge £6.30; for Vangue Vanguard AM25T £6.95. MAIN DISTRIBL | squelch conversion for Pye R/T eq ructions. Tailor-made, easy-fit des d, with minimum of modifications. ard AM25B (Valve RX) £6.10; for Tr JTOR OF REVCO PRODUCTS UDE UK P&P and 15% VAT | For AN |
| GAREX E | LECTRONIC D, MARSWORTH, TRI | SNG, |

Phone 0296 668684. Callers by appointment only Goods normally despatched by return VK-land, on October 11, an activity night on the 25th. Further details from Jim Towle G4PJZ, 63 Digby Avenue, Mapperley, Nottingham or try Nottingham 624764.

Oldham ARC Reminder of the new venue for the club in the Bunker, Wheatsheaf Hotel, Derker Street, Oldham, on Monday evenings at 8.30pm, with visitors and new members most welcome. Further info from Fiona Butterworth G4SPX on 061-652 8862.

Salop ARS G3SRT AGM on October 11 takes pride of place but there will be a talk on AR by G6AKE on the 25th. Thursday evenings at 8, the Albert, Smithfield Road, Shrewsbury. Note November 8 and a talk on a very important subject, planning permission, by G4HFX. Club details from yet another lady sec Diane Parslow G4XBI, 1 Willington Close, Little Harlescott Lane, Shrewsbury.

Southend & District RS Brian Wood G4RDS says the club meets every Friday at the Council Offices, Rayleigh, at 7.30. Details of meetings from Brian, who is the club's Liaison Officer, at 27 Fernlea Road, Benfleet, Essex or ring (03745) 50494.

Southgate ARC Regular meetings second Thursday of the month, St Thomas' Church Hall, Prince George Avenue, Oakwood, London N14. On October 11 it's G6GOS dealing with audio matters. More from PRO R. F. Snary G4OBE, 12 Borden Avenue, Enfield, Middx.

Spalding & District ARS G4DSP I'd love to get along to the White Hart Hotel, Spalding, at 8pm on Friday October 19 when the expert Geoffrey Perry late of the Kettering Grammar School will deal with satellite reception. Straight from the horse's mouth, so to speak! Meetings second Friday of the month at above venue, and get ready for the construction contest to be decided on November 9. Christmas social and junk sale is slated for December 14. Betty Whitley G6YBL is sec, on (0775) 2781.

Stanford-Le-Hope & District ARC Keen to attract new members the club meets every Monday at 8pm at St Joseph's Parish Rooms, Scratton Road, S-Le-H, Essex. Sec Jim Thompson G4OVG is on the S-Le-H 642312 and ready to supply any details of the club's activities.

Stowmarket & District ARS First Mondays by the look of it at the Maltings Entertainment Complex which is opposite the railway station in Stowmarket. November meeting has G3ZQU telling how to get started on the 1.3 and 2.3GHz bands, a popular subject just now. The Christmas social takes place on December 3. Sec is G8SCB J. Lowe, "Bulan", 35 Barking Road, Needham Market, Suffolk or alternatively G3ZQU on Stowmarket 676288.

Stratford-Upon-Avon & District RC G3PGU Second and fourth Mondays starting at 7.30 at the Control Tower, Bearley Radio Station, about five kilometres north of the town. Construction is the main theme of the club with members encouraged to bring in their own projects, either to get help or to encourage others. Chris Ousby G6DCL is PRO at Ormond Lodge, Newbold-on-Stour, Stratford-Upon-Avon, Warks, or try Ian Hopwood G6CWK on Stratford 68863.

on the air 🛛

Street & District ARS Meets first Tuesday at the Strode College says sec Colin Webber G4SCD of 3 Orchard Road, Street, Somerset. Like many other clubs this one will be active in the Scouts Jamboree-on-the-Air Sat/Sun October 20/21, using the call GB0SSG. The speaker on November 6 will be G6HTI on the subject of DXTV reception.

Thames Valley ARTS First Tuesday of the month at 8pm, the Thames Ditton Library, Watts Road, Thames Ditton, Surrey. While the title of the club is "Transmitters Society" in fact s.w.l.s are most welcome and you don't have to have a ticket! David Foster G3KQR of 56 Elmbridge Avenue, Tolworth, Surrey, is the sec also to be found on 01-399 1289.

Vange ARS G3YCW Thursday evenings at 8, the Barstable Community Centre, Basildon, Essex, with a junk sale at least once a month. Talks by members are supplemented by outside lecturers. Sec Mrs D. Thompson can be found on (0268) 552606 with lots of info on the club's activities.

Verulam ARC RAFA HQ, New Kent Road, off Marlborough Road, St Albans, second and fourth Tuesdays of the month. G8MQT will talk about Larkspur ex-military equipment on October 23. Your enquiries to Hilary Claytonsmith G4JKS, 115 Marshalswick Lane, St Albans, also St Albans 59318.

Wakefield & District RS G3WRS "Alternate Tuesdays" translated means October 16 when G8UCH deals with p.c.b.s, with a tape and slide lecture "The Human machine as a radio operator" on the 30th. Go along to Holmfield House, Denby Dale Road, Wakefield, around 8pm, with code practice sessions starting half an hour beforehand. Club sec Walter Parkin G8PBE can be located on Wakefield 378727.

North Wakefield RC Carr Gate WMC every Thursday at 8 with a junk sale laid on for October 4. More details from sec Steve Thompson G4RCH, 2 Alder Close, Morley or Morley 536633.

Welland Valley ARS G4WVR Mondays at 7.15 at Welland Park College, says Judith Day G60FZ the Publicity Officer of this new club. She can be contacted at 11 Warwick Close, Market Harborough, Leics. New members will be made most welcome as will any visitors. You can also try sec Dave Lunn G3LSL on M.H. 880746.

Wessex ARC Recently formed, the club will welcome prospective members and visitors at the Cricketers, Wimborne, Dorset. Meeting "every fortnight" seems to make it October 16 and 30, Tuesdays, but hope the arrangements will be made a bit more definite 'ere long. In the meantime try sec Wendy Stacey, Spinney House, 16 Crane Drive, Verwood, Wimborne, Dorset.

West Bromwich Central RC G4WBC Sunday evenings at 8, the Victoria in Lyng Lane, West Bromwich. Everyone welcome with classes to help those taking the code test or the RAE. More from sec John Bates G6ZLW on 021-553 0531.

Westmorland Radio Society New sec is Gordon Chapman G11IE, who can be found on 0539 28491. He tells me that future events are: October 9 a Photographic Audio-Visual Evening with G3UEC, November 13 is a St John First Aid Talk and December 11 a talk on 10 metres (28MHz) by G3IZD. That makes it the second Tuesday at 8pm in the Strickland Arms, Sizergh, near Kendal.

Wimbledon & District RS Meets at the St John Ambulance HQ second and last Fridays, the HQ being at 124 Kingston Road, Wimbledon, London SW19. October 12 is AGM time with a very special occasion on the 26th when a social evening to celebrate the 21st anniversary of the re-formation of the club will be held. The special call GB0WIM was issued to the club and used to the full with operation on all bands h.f. to u.h.f. at a long weekend camp near Chessington Zoo. Club sec Geoff Mellett G4MVS resides at 26 Paget Drive, Sutton, Surrey, and will be glad to hear from potential members. He can also be found on 01-644 8249.

Winchester ARC The Log Cabin, Stockbridge Road, Winchester starting at 7.30, with a junk sale on Saturday October 20, otherwise the third Saturday of the month. December 15 is Christmas social time again. Brian Epps G3SHQ is sec and can be contacted on Twyford 713003.

Wirral ARS G3NWR First and third Wednesdays, the Parish Hall, Heswall, said to be off the Milner Road, behind the church, at 7.45. This is a change of venue and a talk-in service is on the cards. Club net is on 144-725MHz every evening 7.30pm, with Sunday at noon on 7050kHz. Main item in October is the AGM on the 17th. Details from Cedric Cawthorne G4KPY, on 051-625 7311.

Wirral & District ARC G4MGR G8WDC Second and fourth Wednesdays at the Irby Cricket C¹ub, Irby, Wirral with new members most welcome, as well as visitors. Sec is Gerry Scott G8TRY, on 051-630 1393.

Yet another appeal to club secs, do ensure the programme information sent to me includes the place, time and day/s of meetings. It is surprising how often the meeting place is omitted!

MEDIUM WAVE BROADCAST BAND DX by Charles Molloy GBBUS

Reports to: Charles Molloy G8BUS, 132 Segars Lane, Southport PR8 3JG.

"What is the best way of matching a loop antenna into a receiver" asks reader **Peter Cutts** of Birmingham. Well there is a problem but the method used to overcome it with the standard medium wave loop is to use a single-turn coupling winding. See my article in *Out of Thin Air*. The main winding, which picks up the signal and is resonated by the loop's tuning capacitor, consists of seven turns. The coupling winding, which is not connected to the main winding but picks up signal from it by induction, is led off to the receiver. It should be connected to a dipole input if one is available or alter-

natively to the A and E terminals. The main and coupling windings between them form a 7 to 1 step-down transformer which provides an approximate match to the receiver. It is the best that can be done as you must have a complete number of turns on each winding or the loop will not work properly. Fractions of a turn are out!

Differential Matching Amplifier

Why not do without a coupling winding and connect the receiver directly to the main winding? If you do this then the input impedance of the receiver will be shunted across the loop which will then be detuned and damped. Damping will broaden the tuning of the loop and weaken the signal picked up by it.

Much the best way of matching a loop to a receiver is to use an isolating or buffer matching amplifier. This will have a high input impedance which can be connected directly across the loop's main winding with little adverse effect. The low output impedance of the amplifier goes to the receiver's antenna input. This usually has a low impedance, so a good match with maximum signal transfer is obtained. The coupling winding is not used and need not be fitted to a loop intended for use with a matching amplifier.

DXers use a special amplifier called a differential matching amplifier (d.m.a.) which helps to maintain the accuracy of the loop's directional effects. A useful feature if you are interested in direction finding. For most practical DXing though, the standard one metre square loop with coupling winding is adequate. It is a good compromise as it gives good results with a minimum of complications and it is a passive device, i.e. it does not require a power supply. Improved results can be obtained by the experimenter who will find details of a d.m.a. in the February 1983 issue of Practical Wireless.

North American DXing

Last month we saw how to pick up Newfoundland, the nearest part of North America so far as the DXer is concerned. Now that the long nights of winter are nearly upon us, it is worth searching for DX from more distant locations. The eastern coast of Canada, the United States and the Caribbean can all be picked up in the UK when conditions are favourable. While a communications receiver and medium wave loop antenna are desirable they are not essential. A table receiver connected to a short outdoor antenna, preferably via an antenna tuning unit (a.t.u.) should pull in some DX but it really is asking a lot to expect a small portable with internal antenna to be up to this sort of DXing.

Before we start, it is worth noting that every broadcasting station in Canada and the United States will have a callsign, just FOR LONDON & THE SOUTH-EAST LBC IS NEWS LOCAL NATIONAL AND INTERNATIONAL 24 HOURS A DAY



like a Radio Amateur. The station is obliged to identify itself by its callsign and many of them do so frequently. This makes station identification very easy. Callsigns consist of either three or four letters. In Canada the first letter is a C while in the US it can be either a W or a K. Most of the stations we are likely to pick up will have call letters starting with a W. In the Caribbean, call letters are less frequently used except on American territory like Puerto Rico.

It is best to wait until 2300 before looking for DX. By this time the path will be in darkness and a number of European stations will have closed down for the night, reducing QRM. Check first of all for CJYQ in St John's, Newfoundland on 930kHz. This will show if the DX path across the North Atlantic is open. If you cannot pick up CJYO then it is unlikely that you will hear anything else. Tune now to 1510kHz, 2kHz below the European channel 1512kHz. The Belgian on 1512 should have closed down by now and the weaker occupants in Saudi Arabia and the USSR should not give much trouble.

Listen on 1510kHz for WMRE which is located in Boston. This station is often the first to fade in from the United States. It is of course commercially operated so there will be adverts, frequent/station identification either spoken or sung (jingles). Try now on 1210kHz for WCAU in Philadelphia. Remember the slow fading which is characteristic of DX signals on the medium waves. The fading cycle may be spread over two or three minutes so once you have located a channel, stay tuned to it for a few minutes just to see what comes up out of the noise. Other stations to search for are WQXR on 1560, WHN on 1050, WNEW on 1130, all with studios in New York city.

Mainland Canada, strangely, is more difficult to pick up than the United States but try 940kHz for CBM in Montreal, 1410 for CIGO Port Hawkesbury, Nova Scotia and 1570 for CKLM Montreal on 1570 CKLM which is in the province of Ouebec, has programming in French.



Caribbean DX

There are several broadcasts in the Caribbean that come in regularly in the UK. The easiest to locate is the out-ofband Caribbean Beacon in Anguilla on 1610kHz. Programming is often religious and in English. Move down to 1580kHz and listen for the Voice of American relay, in English on 1580kHz. It comes from Antigua. Now try 1210kHz for Radio Caraibes in Dominica in French. You can often hear it, mixed with WCAU and if the fading cycles are favourable one may fade down as the other fades up.

Radio Cayman on 1555kHz put in a good signal early in the night on several occasions last winter. Listen to Radio Malta on 1557kHz as it goes off at 2330. Then tune down 2kHz and listen for R. Cayman. Programmes are in English with a pronounced Caribbean flavour. Other DX to listen for is Radio Paradise in St Kitts on 825kHz, Radio Antilles in Montserrat on 930kHz, ZDK Antigua 1100. Next time we will have a look at DX from South America and how to send reception reports to distant medium wave stations.

Local Radio DXing

Two interesting items picked up recently at my QTH were Festival Radio on 1530kHz broadcasting from the International Garden Festival in Liverpool and BBC Radio Wigan testing on 1296kHz. The latter is an experimental community radio outlet broadcast from a radio vehicle.

Daytime DX from my own log in-cludes BBC Radio Solway (Dumfries) on 585kHz, Radio 4 in Newcastle on 603, York on 666, Cumbria 756, Ulster (Londonderry) 792, Furness (Barrow) 837, Ulster (Enniskillen) 873, Norfolk (King's Lynn) 873, Devon 990, Derby 1116,

Cambridgeshire 1449, Nottingham 1521 and 1584, Kent 1602. Commercially owned outlets heard were Radio Aire in Leeds on 828kHz, Radio Wyvern 990, the new Viking Radio in Hull 1161, Hereward Radio in Peterborough 1332, Manx Radio, Isle of Man 1386, Radio Tay in Perth on 1584. All stations were picked up with a DX160 and 20 metre random wire antenna plus an a.t.u. Daytime reception is by the ground wave and some of the stations heard are quite low power, such as Cambridge on 1449kHz which is only 100 watts. Radio Tay on 1584kHz was an interesting catch. During the day it

on the air

was a weak companion to Nottingham but as sunset approached and sky wave reception became possible, the relative strengths of the two stations changed. Radio Tay peaked up and was easily identified. The period before sunset, and sunrise too, is a good time for medium wave DXing.

SHORT WAVE BROADCAST BANDS by Charles Molloy GBBUS

Reports: as for Medium Wave DX, but please keep separate.

The identification of broadcasting stations on the long and medium waves is seldom a problem for the average listener. Stations are well spaced on the dial, so it is easy to locate the one of your choice. On the short waves the situation is rather different. Broadcasting is confined to quite small segments, each crammed with stations, making it impossible with a general coverage receiver to set it even approximately to the station of one's choice.

Set designers have attempted to combat the problem using multiband sets where each s.w. band occupies the whole length of the scale and there are still a number of these sets available. Broadcasters too tried to help by using interval signals and signature tunes before the start of a transmission, so that the listener could home in on them, as it were.

Interval Signals

Something of a misnomer, carried forward from the early days of short wave broadcasting, interval signals are widely used on the short waves today. Perhaps the most famous was the letter "V" in Morse used by the BBC during the last war as an identification of its broadcasts to occupied Europe. Today, interval signals are of infinite variety ranging from a few bars of music to bird calls, the Kookaburra bird of Australia for example, or even recordings of farmyard animals as used by Botswana. The talking drums from Tahiti are also well known to DXers.

Recordings of intervals signals are both interesting and useful. Currently, a cassette of recent signals is available from the European DX Council. Send a s.a.e. to the EDXC, PO Box 4, St Ives, Huntingdon, Cambs. PE17 4FE for details. The twice weekly DX Party Line from HCJB in Ecuador has been playing recordings of interval signals for some time now. Each is played several times and the listener is invited to identify it before this is revealed.

Once digital readout becomes commonplace then the need for interval or identification signals will disappear, as the listener will be able to set his receiver to the desired channel with certainty. Whether they will actually vanish is a matter for conjecture. Personally I hope not, as they add a little character to short wave broadcasting and enable stations to project an image, if they so wish.

The High Frequency Bands

The two bands designated 21MHz (13 metres) extending from 21.450MHz to 21.750MHz and 17MHz (16m) covering 17.700 to 17.900 are similar and can be treated together so far as the s.w.l. and DXer is concerned. These are long distance, daytime only bands. Reception demands a path of darkness between transmitter and receiver, so at sunset 21MHz and 17MHz appear dead or nearly so. Newcomers to the short waves sometimes think there is something wrong with their receiver when the h.f. end of the spectrum is quiet, but it is only a demonstration by the ionosphere, that we are totally dependent on it for long distance reception on the short waves.

Sunrise in the UK opens a path of daylight to the east and with it the two bands open up for the day. Typical of what can be heard is Japan on 17.755, 17.785 and 17.870MHz, Australia on 21.720, 21.525, 17.715, Pakistan on 21.775,17.645, Dubai on 21.605, Saudi Arabia 21.495, Baghdad 17.720. No need for a sensitive receiver and long outdoor antenna. Signals on 21MHz and 17MHz come roaring in and can be picked up easily with a table receiver and whip antenna.

There are still a few stations on these bands after dark. These are from the west or south-west where the track or most of it is still in daylight. Listen on 17.790 for HCJB in Ouito, Ecuador, on 21.470 for the Voice of America in the USA, on 17.820 for Radio Canada International, on 17.605 and 21.685 for the Radio Netherlands relay in Bonaire. Reception deteriorates gradually as the evening progresses and more and more of the path goes into darkness. It is a pity that many short wave receivers do not tune above 15MHz or even 12MHz. Such sets are to be avoided as their users miss a lot of interesting listening and DX.

On the Bands

The following regular broadcasts will be of interest to newcomers to short wave listening. All times are UTC (GMT).

Austrian State Radio (ORF) has a programme for Europe at 0830 daily (0900 Sundays) on 6.155MHz (49m band) 7.170MHz (41m band) and 9.770MHz (31m band); at 1230 on 6.155 and 9.770; at 1830 (1805 Sundays) on 6.155 and at 2130 on 5.945 (49m band). ORF is easily located as the interval signal is the first few notes of the Blue Danube waltz. Austrian Short Wave Panorama is carried on the 0900 and 1805 transmissions on a Sunday and contains items of general interest to the short wave listener. The address for listeners' letters and a schedule is Austrian Radio (ORF), Short Wave Service, A-1136 Vienna, Austria.

The Pacific Service of Radio Australia on 6.035MHz comes in well in the UK during the afternoon and evening until sign off at 2000. Interesting to listen to programmes intended for reception on the far side of the world at breakfast time the following morning. Radio Sweden International has a daily half-hour broadcast in English which can be heard at 1100 on 9.630 and at 1830 on 6.065. Programmes cover a wide variety of topics while on a Tuesday the well known Sweden Calling DXers, hosted by George Wood, is on the air. Norway broadcasts in English once a week on a Sunday only, with a half-hour transmission that is repeated several times during the day. Listen at 1000 on 6.015, at 1300 on 9.590, 1400/1600/1700 on 6.015 and at 1900 on 9.590. Other frequencies used from time to time are 9.600 and 15.175.

From the United States the Armed Forces Radio and TV Service (AFRTS) beams to US Forces in the Atlantic area daily from 1100 to 0100 on 15.420MHz (19m band). Programmes are taken mainly from domestic networks and carry a large amount of sports and commentaries as well as feature programmes and news, interesting to the onlooker and providing a useful service to US residents or travellers abroad in addition to its military audience. Address for further information is AFRTS, 1016 North McCadden Place, Los Angeles, Calif 90038, USA.

From South America, Brazil is represented by Radiobras daily at 1800 on 15.279MHz (19m band). The programme lasts for an hour and usually comes in well in the UK. The way of life, music and viewpoints from a part of the world different to our own comes over well from Radiobras, with features such as History of Carnival, Samba, Brazilian Culinary Arts. In contrast Kuwait, rather surprisingly, provides a largely western style of programming to its foreign audience. You are more likely to hear



Radio Cairo

rock music than Koran from Radio Kuwait. Listen on 11.675MHz (25m band) at 1800 for its daily programme which lasts until 2100 and is usually a strong signal in the UK.

VHF BANDS by Ron Ham BRS15744

Reports to: Ron Ham BRS15744, Faraday, Greyfriars, Storrington, West Sussex RH20 4HE.

Fig. 1

1 2 3 4 5 6 7 8

Although the seasonal sporadic-E is predominant in almost all subjects in this episode of v.h.f. activity, there are reports about awards to RTTY operators, limited tropospheric openings, readers at the Chalks Pits museum, a couple of super QSOs and a request for help.

Solar

WAD239

MONTH

DATE

DKOTE DLOIGI EA6AU GB3SX LA5TEN LU1UG PY2AMI ZD9GI ZS1CTB ZS5VHF ZS6PW Z21ANB 3B8MS 5B4CY

On July 19, **Cmdr Henry Hatfield**, Sevenoaks, using his spectrohelioscope, located a very small sunspot and 6 filaments, then one spot and 4 filaments on the 28th. "Very quiet," and "even

JULY

16 17 18 19 20 21 22 23 24 25 26 27 28 29 30 31

quieter," remarked Henry about the sun on those two days; similar reports came from Patrick Moore, Selsey, and Ted Waring, Bristol. Although Ron Livesey, Glasgow, auroral co-ordinator for the British Astronomical Association, said, on August 6, "no positive sightings of auroral activity have reached me so far for July," his magnetometer was very active on the 13th and 31st and fairly active on the 15th, 16th and 19th. There was a slight increase in solar activity during the first half of August, Patrick sent a series of sunspot drawings showing what looks like a double group around central meridian on the 10th and while Ted counted

AUGUST

9 10 11 12 13 14 15

_____ on the air ____

AMERICAN FORCES RADIO AND TELEVISION SERVICE AFRTS-W SHORTWAVE VERIFICATION CARD

Bert Carter of Romford refers to the

piece I wrote in the July issue about the

Radio Japan relay in Gabon and goes on

to say "I thought you might like to know

I sent a report on the 21.695 transmis-

sion off to Tokyo on June 25 and received the special Gabon relay QSL on

July 10. That's the fastest return I've had

in nearly 40 years of QSLing . . . congratulations to Radio Japan." Shows

what can happen when a station is look-

Readers' Letters

ing for reception reports.

11 sunspots on that day, I recorded a few small bursts of solar radio noise at 143MHz on the 9th and 11th. The first radio noise I had recorded from the sun since June 24.

Sporadic-E

ter teretter

"I had been watching Band I TV all day on June 30 and thought the prevailing sporadic-E might climb to the 144MHz band and, sure enough, it did," writes **Phil Hodson** G8RBY, Melton Mowbray. He took advantage of the situation and made s.s.b. contacts with stations in VB, YY, WW and WX squares with 5/9 reports both ways. One of Phil's near neighbours, **Tim Fern** G4LOH, worked two stations in Portugal and four in Spain using just two watts to a 16-element Tonna array. "Gerrard Boot PD0MHO, Fig 2, is a very active amateur on 144MHz horizontal f.m.," writes **Tony Gould** G4UAM, Norwich.



Another satisfied reader is A. M. C.

Austrian Radio

Trickey who purchased a Vega 206 portable. "One can receive dozens of stations—definitely identified are Israel, Syria, Hanoi, Australia, South Korea, Pakistan, Dubai, Afghanistan. It really seems this set will get anything if one is prepared to wait for station identification, the strength of reception is phenominal. I might say I am 80 and am like a kid with a new toy." Yes it really is remarkable what a modern receiver with whip antenna will pull in. Technology has advanced a long way since I started listening with my home-made one-valver. Good listening OM.

EW DRAE SLOW SCAN TELEVISION RECEIVER

Provides an affordable entry to the exciting world of SSTV

£189 (Inc VAT)
for a complete receive unit
Simple upgrade to full

transceive with plug in TX Module (available soon) • Latest design all on a single PTH Glass Fibre PCB. • Receives European and US standard transmissions Add a new dimension to your H.F. receiver with a DRAE Slow Scan Television Receiver. Simply connect between any receiver and a standard television or video monitor to watch slow scan pictures from all over the world. Previously the preserve of a devoted few the DRAE SSTV receiver brings Slow Scan within the reach of the average amateur. Available from

PRECISION REGULATED POWER SUPPLIES

Supply

Excellent Proven Reliability

Totally Protected

ORAE Slow Scan

- Excellent value for money
- Well proven design
- 4, 6, 12 and 24 Amp units available
- High surge rating

In 1980 Davtrend introduced the DRAE range of power supplies. These set new standards for regulation ripple and protection for amateur equipment. Three and a half years and several thousand PSU's later their reliability has been proven running professional equipment in countries from Hong Kong to Nigeria as well as amateurs in the UK. There are no better equipments for powering your station but there are more expensive alternatives.

| Prices | |
|--|--------------------------|
| VHF WAVEMETER | £27.50 |
| MORSE TUTOR | £52.00 |
| 3 WAY VHF SWITCH (SO239) | £15.40 |
| 3 WAY UHF SWITCH (N Type) | £19.90 |
| 2 Metre Preset ATU | £11.80 |
| SSTV Receiver | £189.00 |
| 24 A Power Supply | £110.00 |
| 12 A Power Supply | £79.50 |
| 6 A Power Supply | £53.50 |
| 4 A Power Supply | £34.00 |
| Prices and Details of Commerce Supplies+DC/ DC Converters | cial Power on request |

A REFERENCE

Stock at time of going to Press.

MORSE TUTOR Why settle for a Class B Licence?

Loudandclear1KHztone • Code practice oscillator

• Single, Groups of 5 or • Repeat key Continuous Morse • Built in Power Supply. There is only one way to pass the morse test, PRACTICE. With the DRAE Morse Tutor you can practice receiving and sending morse code. The unique repeat facility and the two variable speed controls simplify learning each of the characters. Once you know the characters you can increase your speed with groups of five or even a continuous stream of random morse. Finally using the built in practice oscillator and the invaluable repeat key you can train yourself to send morse correctly.

All DRAE products are designed and manufactured by DAVTREND LIMITED in the U.K. and carry a full one year guarantee.

Delivery of stock items despached within 24 hrs





DAVTREND LTD. Sanderson Centre, Lees Lane, Gosport, Hampshire PO I2 3UL Telephone 0705 52014



He told me that between 0245 and 0250 on August 6, Gerrard worked 17JNE on 144MHz, a distance of some 1516km from his home in Gouda. Gerrard is an active s.w.l. on 430MHz ATV and can usually be found on 145-350MHz or S20, using horizontal f.m., and is pleased to give reports and take part in tests. Congratulations, Gerrard, let's hope we hear more from you.

At 1720 on July 23, Harold Brodribb, St. Leonards, logged 9 Eastern European f.m. broadcast stations between 66 and 73MHz, 49 at 1015 on the 24th, 10 at 0935 on the 31st, and 14 on August 1. During similar sporadic-E conditions I counted 9 at 1230 on July 21, 19 at 0755 and 32 at 1900 on the 24th, 28 at 1930 on the 27th, 38 at 1030 and 26 at 1915 on the 31st, 23 at 1015 on August 1, 32 at 0830 and 45 at 1217 on the 4th, 21 at 0755 and 32 at 1850 on the 5th, 51 at 1326 and 15 at 2004 on the 6th. At such times the signals from these stations are exceptionally strong. Unfortunately, they disrupt the 70MHz amateur band, but their numbers do give a general idea about the extent and intensity of the prevailing disturbance.

Signals from the users of the 27MHz Citizens Band, located in Northern Ireland, Scotland and Wales, poured into southern England during such conditions on August 4, 5 and 11, and at 0955 on the 5th one was maritime mobile off the north coast of Scotland.

The 50MHz (6m) Band

During July, Dave Coggins, Knutsford, heard G3BAO, 'COJ, 'LTF, 'NOX, 'TCU, 'UGF, 'ZIG, G4CUT, G5KW, G6XM, GM3WOJ, GM3ZBE, GM4FZH, GW3LDH, GW3MHW and the beacon GB3SIX in the 50MHz band. 18-year-old Roland Jeffery G6DSA, Winsford, has been active listening on 50MHz since January after a very infor-mative QSO with GW3LDH in Wrexham. Roland used his father's (G8SIG) FT-225RD and wire dipole before he purchased his TS-700G and made his own dipole. "Now I can listen on 50MHz and the 144MHz talk-back frequency, says Roland, who is also very pleased with the Wood and Douglas 50RX144 converter and already has 7 countries in his 50MHz log. During May, June and July, he often received signals from GB3SIX and the Gibraltar beacon ZB2VHF, by meteor scatter and sporadic-E.

The 28MHz (10m) Band

"It has been a busy time on 28MHz with the sporadic-E booming through, many European countries logged and some at ridiculous strengths," writes Dave Coggins. He has recently added a Lowe SRX30D receiver to his station equipment. "28MHz never seemed to open up for DX working, only short

Practical Wireless, November 1984

_____ on the air ____

European skip, at least at my QTH," says Bill Kelly, Belfast, using a NRD 515 communications receiver and a 22m longwire antenna. I logged Italian and Spanish s.s.b. stations at 1300 on July 26; EA, HB9, I, OK, SM and SP on August 4 and at 2044 on the 4th there was a lot of short skip on the band, mainly from Sweden. In fact, the 28MHz band throughout the weekend of 4th and 5th was dominated by short skip conditions. An ideal time for the variety of Morse reading machines to identify the c.w. stations at the bottom end of the band. My Tono Theta 550 certainly earned its keep that weekend. In Cork City, John Desmond, heard many Danish stations working into the UK on August 8 and during the short skip activity on the 11th, he heard CX9AU, a lone South American, working a station in Sweden.

28MHz Beacons

"DK0TE became DK0TEN on August 1," writes Ted Waring. This change was also mentioned in the letters I received from John Coulter, Winchester, and Ted Owen, Maldon, who said on August 18 that the past month had been very interesting. Dave Coggins heard the beacon DF0THD on July 27, and one morning at 0345 he switched on his rig and found very strong signals from the German beacons DF0AAB, DK0TE and DL0IGI. Typical sporadic-E, Dave. "Besides sporadic-E, I noticed that every night at some time I could hear DL0IGI via meteor scatter," writes John Desmond, who uses a Yaesu FRG-7 receiver and Hy-Gain 3-element Yagi on 28MHz. He adds, "The sporadic-E opening on the 11th was quite extensive. All German beacons were strong and for a while I could hear the Sussex beacon GB3SX. which is relatively close for me." On July 15, Chris van den Berg, The Hague, heard EA4CGN in beacon mode on 28.210MHz and reports that he often receives very strong signals from the Palma beacon EA6AU. "The Palma beacon was very strong at 2359 on August 1," writes Henry Hatfield, whose log, along with those of Chris van den Berg, Dave Coggins, Bert Glass, John Coulter, John Desmond, Norman Hyde G2AIH, Epsom Downs, Bill Kelly, Ted Owen, Ted Waring and my own, were used to complete the monthly beacon's analysis chart, Fig.1.

My thanks to Fred De Witte NL7357, for the gen about the new experimental beacon PA0ETE, due to start transmission on 28·302MHz, with an output of 470mW, on August 10. In fact, Bert Glass BRS32693, Plymouth, reports hearing this on test on August 1.

28MHz Satellites

"Among the successful users of the RS-transponders, being active almost every possible orbit are F9EA, OK3AU, I5YT, G3EMU, SM7BYU and SP9DH,"

writes Chris van den Berg. Both Chris and John Coulter logged signals from G3DDG on August 5 and Chris reported receiving 5-digit groups, plus the word "AMSAT" from OSCAR-9. Over in Belfast, Bill Kelly logged European stations and orbital data from the Russian satellites around 1830 on July 8 and 1245 on the 10th and in his letter, John Coulter said, "Plenty of QSOs on the RS satellites, mostly European except for K2AGJ, VE2LI, W0CA, W8MMC and W9YCV." John also received and translated such messages as, "Wishing success to the Pioneer's Ether 84 Com-petition," from RS3A on July 17, and "Greetings to participants in the Pioneer's Ether 84 Competition,' from the same electronic bird at 1057 on August 12.

Tropospheric

The atmospheric pressure, measured at my OTH, began this period at 30.15in (1020mb) on July 16 and remained consistent at this level until midnight on the 25th when it took off, peaking around 30.35 (1028) at 1400 on the 27th, then, by 2000 on the 31st it had slowly fallen to a low of 29.7 (1005). From midnight on August 1 to 1800 on the 5th, the pressure hovered around 30.0 (1015), rose slowly to 30.3 (1026) by midnight on the 9th and from 1400 on the 10th it gradually fell back, reaching 30.1 (1019) at 0600 on the 13th, where it stayed to the end of this report, on the 15th. "The long spell of fine weather brought some pleasant listening," writes Bill Kelly, having heard plenty of amateurs from England, Scotland and Wales working through the Northern Ireland repeater, GB3NI on R5. Bill also heard signals through the repeaters at Caernarfon GB3AR on R4, Caldbeck GB3AS on R1 and Ayr GB3AY on R2.

"Our new 144MHz repeater GB3BB, Brecon Beacons, on R4, is operational, and both Bert Mills GW3LJP and I can hear it well," writes **Simon Hamer** from New Radnor. Around 1720 on August 11, **Kenneth Begg**, Dundee, heard a GM4 working mobile through the Scottish Borders repeater GB3SB on R2, a distance of about 155km.

At 1840 on July 4, **David Last** G6LEU, Truro, using an FT-290R, 25watt kit-built linear and 8-element Quagi antenna on 144MHz, worked, 5/9 both ways, EA8XS at about 2700km. The QSO was joined by G8ZDS, who then completed a QSO with the Spanish station on the 430MHz band. David worked the EA again on 144MHz at 2140 on the 5th and says that he also heard him working other stations on both the 144 and 430MHz bands.

Band II

Andrew Hill, Walsall, is normally a short wave bands enthusiast, but for several days in July he heard Viking Radio on 102.7MHz with a strong signal and decided to send a report, which earned him a QSL card, Fig. 3, from the station in Hull. Andrew's interest in radio began 5 years ago when he was 12 and had the chance to occasionally tune the short wave band of an old Grundig radiogram. Later he had his own Hitachi radio/recorder and now uses an ex-Admiralty B40 and long-wire antenna for his h.f. listening. On July 29, Andrew Guy, Newport, received BBC Radio London, LBC, France Cultur and Frequence Nord between 94 and 100MHz. In addition to the Crown SHC6300 Andrew uses for Band II DXing, he now has a Sony ICF-7600D communications receiver which he is pleased with, and writes, "The v.h.f. section is very good, not only sensitive but selective, too.

I logged 14 continental stations between 87 and 100MHz at 0945 on the 28th and early in August. When **Damien Read**, Newport, took his receiver on holiday with him to Humberside to see what Band II was like there, he logged BBC Radios Cleveland, Leeds and Sheffield and ILRs Aire, Hallam, Tees and Viking.

I used the radio section of my Plustron TVR5D while portable in East Sussex on July 27 and, with its own telescopic antenna, I counted 10 French stations in the band.



Fig. 3

During the sporadic-E disturbance on August 6, John Williams, Harpenden, was surprised to hear Russian speech around 90MHz, at 1400, on his Auritone clock radio with its one metre of wire antenna strung among the kitchen utensils. He then fired up his Ferranti 045 and heard a variety of East European stations between 1400 and 1415 and at 1430 a voice announced Radio Bruno, that's good DX, John. Early on the 8th, Harold Brodribb logged Belgian, Dutch and a good number of French stations between 88 and 100MHz.

_____ on the air ____

RTTY

In the BARTG Spring VHF/UHF RTTY Contest, the winner and runner-up in the 144MHz single operator section were G6CZV and GU6JST. The multioperator section was won by G4PDY/P and G8MWU with G3WOR/P and G6LUT the runners-up. G5MUR and G3KUE/P were the No. 1 stations in the 432MHz single and multi sections, and BRS28198 and NL4483 were the leading s.w.l.s.

NL4483 and OZ-DR2135 lead a field of 15 receiving stations and ON4UN, YU7AM and UT5RP and LZ1KDP, VE1ASJ and OK3KJF lead the respective transmitting sections in the h.f. event.

Congratulations also to **Phil Hodson** G8RBY for earning the first ever 10 countries/40 squares RSGB award for RTTY QSOs on 144MHz, and he especially thanks Ray Lowes G4NJW and Kevin Coleman G6SSX for their help in taking equipment to rare DX places to give him the opportunity to work them. "What other mates would ring and ask, 'Where do you want me to go on holiday next week?' Thanks to Kevin and Ray I obtained 144MHz RTTY QSOs in AN, XM, XN, XJ and ZR squares," said Phil.

For the contest minded, the BARTG are holding their Autumn VHF Contest between 1800GMT on October 13 and 1100 on the 14th, with a compulsory rest period of 4 hours during the event. The contest is limited to the 144MHz band and is open to licensed amateurs who are permitted to use RTTY in CQ DX Zones 14 and 15. Listener reports are very welcome and will be scored separately. The 1984 Winter 144/432MHz Cumulative RTTY Contests will take place between 2000 and 2200GMT on November 5, 12, 19 and 26 and December 3. Contacts via repeaters or satellites are not valid in either competition. All details from the BARTG contest manager, 464 Whippendell Road, Wat-ford, Herts WD1 7PT.

Between July 16 and August 15, I copied RTTY signals from 36 international prefixes, CE, CN, DJ, DK, EA, EI, F, G, GI, GM, HA, HB9, I, IT9, KP4, LA, LX, QE, QD, QH, QK, ON, OZ, SM, SV, TR, UO, UZ, VK, Ws 1, 4, 6 and 9, YO, YU and 9H4 around 14.090MHz, then seven prefixes EA, DF, DL, GI, I, OE and W1 on around 21.090MHz and a German station dur-

ing a sporadic-E event around 28.090MHz. In addition to the usual European RTTY stations, Peter Lincoln received signals from A7IAD, CE3BBW, EA9JE, FG7XC, HK3PJ, JR6FC, PZ1DZ, VP2MD, VU2AIG, YB3BHP and 9M2GV.

Tailpiece

While talking to father and son, John and Andrew Coulstock G6TXY and G6TXZ, from Tunbridge Wells and Northants respectively, I learned that they both use a Totosuko TR2100M on 144MHz while John uses a FT-208 and Andrew a FT-790 on 430MHz. For 144 at their respective shacks John has a home-brew Slim Jim and a 5-element Yagi and Andrew an 8-element Jaybeam.

On August 5, I had the pleasure of showing Paul Essery G3KFE, editor of *Short Wave Magazine*, Norman Field G4LQF, Bob Fowler G3IQF, Fred Garratt G4HOM, Colin Turner G3VTT, Ted Trowell G2HKU and Adrian Weiss W0RSP, all members of the QRP Club, around the radio building at the Chalk Pits museum, along with their host, Chris Page G4BUE. Bob Fowler is a founder member of the club and at home in South Dakota, Adrian uses mainly home-brew gear for QRP operation.

Andrew Humphries BRS 34368, is looking for a circuit or any information on the vintage receiver Chakophone model 1B, built by Eagle Engineering in Warwick. Andrew has been interested in radio since he was 9 and is now a member of the British Vintage Wireless Society, RSGB and the RAFARS using AR88 and Eddystone 680X receivers and long-wire antenna on the h.f. bands and a FDK TM56B receiver and loft Halo antenna for 144MHz. If anyone can help, please write to Adrian at 21 Gould Road, Hampton Magna, Warwick CV35 8TU.

While in Italy last year, Fraser Lees took pictures of the antennas at Monte Penice, the site can be seen in TV bands in this issue.

Did you "spot" the mistake?

Our sunspot pictures on page 64 of the October issue didn't convey much, did they? Unfortunately, between the time that we ok'd the page proofs and the actual printing of the magazine, all the sunspots disappeared. Apologies to Patrick Moore, Ron Ham and our readers.

TELEVISION by Ron Ham BRS15744

Reports: as for VHF Bands, but please keep separate.

"It has been great for me logging, making graphs and plotting the map of Europe," remarked **Owen Jones**, Stoke-on-Trent, when, like many other readers, he enjoyed seeing the wide variety of captions, clocks, programmes and test cards which poured into the UK, enhanced by sporadic-E, from television stations in Eastern Europe, the Mediterranean coasts, Scandinavia and the USSR between July 16 and August 15.

Sporadic-E

When I had the pleasure of analysing the comprehensive letters and logs of the TVDXers named in Fig. 1, I noted that TV clocks from Germany, Hungary, Italy, Norway, Spain, Sweden and the USSR were seen showing times which varied between 1 and 4 hours ahead of GMT. The time differences shown by such clocks can help the TVDXer to decide the likely origin of the broadcast. Among the test cards logged were Austria OFR-FS1, Belgium RTBF,

Czechoslovakia RS-KH and SR1 TV Bratislava, Denmark DR, Finland YLE-TV1, Germany DDR-1 and Grunten, Holland PTT-NED 1, Hungary MTV-1 Budapest, Iceland RUV, Italy RAI-1 (Fig. 2), Norway Bremanger, Gamlen, Gulen, Hemnes Melhus, NRK and Steigen, Poland, Portugal RTP, Rumania, Bucharesti, Spain TVE-1, Aitana 3 (Fig. 3) and Andalucia, Sweden SR and TV1 and 2, Switzerland +PTT-SRG 1, USSR and Yugoslavia JRT BGRO and RTV Ljubljana.

Among the captions mentioned were ARD, Azimut, Beograd, BPEMR, CCP, CNOPT, COMPNTE, CST, Deutsches Fernsehen, dt, EESTI, Granada, Heute, HOBOCTN, HIREK, Le Transmissioni Riprenderanno Alle Ore 1100, NPOR-PAMMA, PRAHA, RAI UNO, SZUNET, TACC-COObWAET, TALLINN, Telejournal, TP, TVP, TV Reklam, Vortagsprogramm, ZDF and ZPRAVY, which, to my way of thinking, was pretty good, especially when we know that pictures often ride over each other and the words are not easy to read.

At 1850 on July 21, Simon Hamer watched a vintage film about Hitler and his generals on Danish TV and the presenter talked about the D-Day landings. Also this month Harold Brodribb saw an episode of the series To The Manor Born with Italian sound on Ch. Ia at 1625 on July 19.

Tropospheric

Although there were no spectacular tropospheric openings between July 16 and August 15, I am sure that readers sorted out what was going, for example, at 1335 on July 26, Walter Haller received a good colour weather report, Fig. 4, from Anglia TV at Sandy Heath on Ch. 24. Around the same time on the 27th, I used my Plustron TVR5D in the car park at Herstmonceux Castle and with its own telescopic antenna I received the French TDF/FR3 test card on four channels between 25 and 60. Then from home on the 30th I watched boxing, a BRT TV1 test card and Olympic swimm-

_____ on the air 📼

Fig. 1

David Appleyard—(Eastbourne) Mike Bennett—(Slough) Harold Brodribb—(St Leonards on Sea) Adrian Butcher—(Washington) Paul Drinkwater—(Sutton Coldfield) Walter Haller—(Bicester) Simon Hamer—(New Radnor) Chris Howles—(Lichfield) Philip Hodgson—(Stamford) Owen Jones—(Stoke on Trent) Fraser Lees—(Ringmer) Tony Palfreyman—(Sheffield) Keith Chaplin—(Leicester) Ron Ham—(Storrington)



ing in Band III between Chs. E8 and 10. Harold Brodribb logged test cards from Belgium RTBF-1 Ch. E8 and BRT TV1 on E10 early on the 22nd and about 4 French stations in the u.h.f. band at 0830 on August 9. Later on the 9th Tony Palfreyman received Nederlands 1 and 2 on Chs. 39 and 45. At 1800 on the 11th, Kenneth Begg, Dundee, saw the start of the Nederlands 1 programmes followed by their news, Nos Journaal. Kenneth also saw the news, *Heute*, from Ger-many's ZDF with an Olympic report and on the 12th he watched various programmes throughout the day from ARD/ZDF and Nederlands 1 and 2 and then Belgium's RTBF 2 in the late evening. Ken could still receive the German stations in good colour on the 13th, which all fits nicely with the slight fall in atmospheric pressure which began around midday on the 10th and seen by Harold on the weather charts in his daily newspaper.

"SSTV has been quite good with signals from West Germany and Italy the most common," reports **Peter Lincoln**, Aldershot, for the month prior to August 14. Peter also received pictures from call areas F, PA, HA, HB9, LA, OH, OK, SP and YU as well as North America, Fig. 5, in the late evenings and LU5NA and ZP5CCG from South America. Peter has written a computer test programme for generating a grey scale for SSTV equipment, I am not surprised because computers, RTTY and SSTV are his special interests as some readers know who have spoken to him on the 'phone.

Between July 31 and August 9, Richard Thurlow G3WW, March, had first time 2-way QSOs with CT1BK, DF0ND, DK7UD, DL1MY, DL2DV, DL4SAW, HA3MQ, PA3BUR and 4X6LM, bringing his total first timers to 2031. Richard also copied pictures from, or exchanged them with, A92NH, DA2ZE, DF3ST, DJ0GF, DL5GR, I5CYN, LU5NA, LX1DT, ZS6OZ and ZS6BTD. At 0730 on August 14, Richard got into the European SSTV Net and exchanged 8 seconds monochrome pictures with DJISS, DLIMY, DLIKBP and OZ3WP and 24 seconds single frame colour pictures for over half an hour with DJ1SS who was using the Volker Wrasse SG-1 converter and the latest KB-1 keyboard. "PAOLAM/EA put in a beautiful SSTV picture on 14.230MHz at



Practical Wireless, November 1984

----- on the air ------



0812 on the 13th, using normal 8 seconds, black and white, frame speed and received my 32 seconds mono pictures well," said Richard. He has been demonstrating his latest SSTV 12 seconds colour equipment to John Holmes G3UEU, one of the early slow scan television enthusiasts.

Station Reports

While in Italy last year, Fraser Lees photographed the TV antenna at Monte Penice, Fig. 10 and took another shot of the masts, Fig. 11, carrying the v.h.f. radio and TV antennas, looking north toward the Alps. At the time Fraser G6JIO, was taking part in a v.h.f./u.h.f./



Fig. 11



Fig. 12



Fig. 13

s.h.f. contest with his good friends I2CNC and IW2BNA.

Kenneth Begg, Dundee, is now using a Triax Unix 92 and twin BB grid system, mounted on a Hirschmann rotator on a mast some 6m above his chimneys, for u.h.f. and a loft mounted Antiference MH473, feeding a Labgear up-converter for Bands I and III. On July 7 he logged pictures from Germany and Holland and at 2330 on the 8th he received a Philips 5544 test card showing BFBS Colour.

"The month of May was fairly good for sporadic-E DX," writes **Major Rana Roy** from India and adds, "the main station available was Russian with Dubai a regular coming up every day between 1930 and 2130. Rana saw Indian labourers dancing and singing on an American documentary film from Dubai,

in Band I, during the evening of the 10th and a Russian test card at 1430 on the 12th. An Arabic station, Fig. 6, appeared at 1930 on the 13th and a Russian station being overlapped by a Russian test card at 1500 on the 14th. We often see this overlapping of signals here Rana es pecially during an intense disturbance. At 1735 on the 15th, a Russian news caster, Fig. 7, was seen on Ch. 3 and a football match, Figs. 8, 9 and 13 from Dubai, Ch. 2 on the 19th, with an Arabic song and dance programme, Fig. 12, at half time. On June 29, Rana received test cards from China and the USSR and Russian news with male and YL presenters on the 30th. At 1710 on July 1 he saw a girl playing a guitar on an Arabic station and a test card from Dubai TV at 1500 on the 2nd.



Are you cheating? If you are reading this page before page 54 then you are. Please turn to page 54 for the questions.

Question 2–1. Answer-d.

A large value electrolytic capacitor across R4, the emitter resistor, keeps the d.c. bias on the transistor unchanged but at the same time prevents the emitter voltage varying with the audio, which would produce negative feedback. So the efficiency of the stage is increased; in other words, it gives higher gain.

Question 2–2. Answer-b.

Clause 6 (1) (g) of the Licence relates to the log

"Entries made in respect of calls made when operating from a vehicle or vessel, or as a pedestrian should be made as soon as possible after the end of the journey and must consist of date, geographical area of operation, frequency band(s) used and time of commencement and end of journey."

Question 2-3. Answer-a.

We need Ohm's law for this question. Using the diagram below as a memory aid, cover up the thing we want to find out—in this case the current. Voltage



Although you are allowed to take calculators into the exam room (so long as they are silent and not of the programmable type), all the calculations will contain only simple numbers which you can do mentally.

Question 2–4. Answer-b.

"Modulation is prohibited by means of recordings of any kind other than special recordings of sinusoidal tone or tones within the audio frequency spectrum which may be either constant or steadily changing in frequency." (Clause 8 (2) of the Amateur Licence).

PLEASE MENTION PRACTICAL WIRELESS WHEN REPLYING TO ADVERTISERS


| Telephone: | (0376) | 27117 | (24-Hour | Ansaphone Servicei | |
|------------|--------|-------|----------|--------------------|--|
| | (0376) | 42494 | | | |



Hay Lane. Braintree Essex CM7 65



| Telex. | 9 | 87911 | | | | | | | | | | Lasex | 0 | 0.54 | | 101 11000 | |
|----------------|-------|----------------------|---------------------|------------------------|--------------|----------------|--------------|---------------------|-------|----------------------|-----------|---------------------|-------|----------------------|--|------------------------------------|-------|
| | | Nationa | | VALVES Mullard, RC/ | A, ITT | | | | | | | | | NSISTORS | | | |
| DA42 E80CC | | EL803S | 9.95 | | 4 50 | 6GF5 6GH8A | 210 | 2N3375 2N3553 | | 2SC1209D 2SC1213A | 0.64 | 25C2283 25C2287 | 9.00 | MRF475 MRF475 | 200 SD1077 225 SD1078 | 160 SD1220-1 | 9.50 |
| BOF | | EM84 | 2 00 | | 1.30 | -GJ5A | 3.00 | 2N3632 | | 2SC1213A 2SC1213C | 0.40 | 2502289 | 12.50 | MRF475 MRF477 | 1250 SD1080 | 26.50 SD1222-5 1.55 SD1222-STUD | 1100 |
| BOL | | EN32 | 16.25 | 6AWBA | 265 | 5GJ7 | 185 | 2N3733 | | 25C1239 | 2.50 | 2SC2290 | 27.50 | MRF492 | 27.50 SD1080-6 | 7 50 SD1224-2 | 13.00 |
| E81CC | | EN91 | 2.80 | | 3.80 | 9GK6 | 1.95 | 2N3866 | | 2SC1241 | 15.00 | 2SC2347 | 0.30 | MRF497 | 18.50 SD1080-7 | 7 50 SD1229-F1 | 109 |
| EBBCC | | EN92 | 3.30 | | 1 60 | 6GW8 | 1.70 | | | 2SC1251 | 10.00 | 2SC2369 | 2.00 | MRF515 | 390 SD1088 | 26.00 SD1229-STUD | |
| E89F E90CC | 9.25 | EZ35 EZ41 | 1.85 2.45 | | 2.75 | 6GX6 6GY6 | 3.00 | 2N3927 2N4416 | | 2SC1260 2SC1303 | 1 11 5 00 | 2SC2370A 2SC2379 | 18.00 | MRF517 MRF620 | 3.50 SD1089 18.00 SD1089 | 28.50 SD1244-6 | 12.75 |
| E92CC | 6.50 | E280 | 1.95 | | 2.00 | 6H6 | 3.00 | 2N4427 | | 2501303 | 1.00 | 2SC2395 | 15:00 | MRF644 | 18:00 SD1089 27:50 SD1115-2 | 4010 SD1256 7.50 SD1262 | 6.95 |
| E130L | 23.50 | EZ81 | 1.65 | | 185 | SHAG | 3.05 | 2N5090 | | 25C1307 | 1.50 | 2SC2407 | 1 00 | MRF646 | 2800 SD1115-7 | 210 501270 | 3.75 |
| E180F | 8.50 | EZ90 | 2.00 | | 415 | SHB6 | 3.05 | 2N5109 | 2.00 | 2SC1311 | 0.40 | 2SC2420 | 18:00 | MRF648 | 3300 SD1127 | 2 50 SD1272 | 10.95 |
| E188CC | 7.50 | PCL805 | 1.85 | | 68.50 | SHE5 | 4.00 | 2N5160 | 4.80 | 2SC1311E | 0 32 | 2SC2494 | 16.00 | MRF750 | 650 SD1131 | 3.25 SD1272-2 | 1095 |
| E5070 | 27 50 | PL509 | 5 50 | | 3.80 | GHF5 | 385 | 2N5190 | | 2SC1314 | 25.00 | 25C2509 | 6.00 | MRF846 | 46 00 SD1133 | 950 SD1278 | 1375 |
| EB91 | 1.95 | PL519 QQVQ2-6 | 575 | | 145 | 6HG5 6HG8 | 1.95 | 2N5589 2N5590 | | 2SC1318 2SC1368B | 0 40 | 2SC2531 2SC2538 | 1 30 | MRF901 MRF904 | 275 SD1133-1 | 1000 SD1278-1 | 1375 |
| EBC91 EBF89 | 1.50 | QQV02-6 | | | 1 50 | 5H56 | 3.95 | 2N5591 | | 2SC13688 | 0.50 | | 15.00 | MRF911 | 2 95 SD1134-1 2 50 SD1134-2 | 2 50 SD1285 10 00 SD1300 | 1275 |
| EC90 | 1.85 | QQV07-50 | 12.00 | | 245 | 6HZ6 | 275 | 2N5643 | 13.00 | 25C1424 | 1.35 | 2SC2540 | 24.95 | MRF5175 | 22.50 SD1134-8 | 10.00 SD1300 10.00 SD1303 | 2.50 |
| ECC32 | 2.50 | QVO3-12 | 4.50 | | 160 | 1J5 | 3.15 | 2N5913 | 2 50 | 2SC1509 | 6.00 | 2SC2545E | 0.29 | MRF5176 | 3000 SD1134-STUD | 7.60 SD1316 | 2 10 |
| ECC40 | 2.95 | 4CX250B | (EIM/AMP) | 6BR8A | 2.95 | GJSGT | 2.95 | 2N5945 | 8.95 | 2SC1546 | 0.45 | MRF208 | 12.00 | MRF5177 | 43.00 SD1135 | 10.25 SD1317 | 8 00 |
| ECC70 | 3.70 | | 49 00 | | 1.35 | 616 | 2.20 | 2N5946 | 15.63 | 2SC1568 | 0.45 | MRF212 | 12.00 | MRF8004 | 200 SD1135-3 | 12:00 SD1405 | 21.00 |
| ECC81 | 1.60 | | NAT) 3950 | | | ABL | 3.00 | 2N6080 | 6.00 | 2\$C1589 | 5.00 | MRF221 | 12.05 | SD1005 | 8 20 SD1136 | 12 50 SD1407 | 27 50 |
| ECC82 | 1.60 | | EIM) 70.00 | 6C4 | 1.85 | GJB5 | 4.00 | 2N6081 | 8.75 | 2501622 | 0.33 | MRF229 | 3.50 | SD1006 | 210 SD1143 | 9.45 SD1407MP | 55.00 |
| ECC83 ECC85 | 1.60 | 4CX350A (4CX350F | AMP) 68.00 72.00 | | 1 65 3 50 | GJB6A GJC6A | 4 20 3 50 | 2N6082 2N6083 | 12 00 | 2SC1623 2SC1688 | 1980 | MRF231 MRF232 | 12 36 | SD1012-3 SD1012-4 | 1000 SD1143-1 1050 SD1144-1 | 10:00 SD1410 2:50 SD1410-1 | 21.06 |
| ECC88 | | 4CX1500A | 440.00 | | 1 90 | GJEGC | 4.95 | 2N6084 | 13 20 | 2SC1674 | 0 25 | MRF233 | 14.30 | | 10 00 SD1144-1 | 2.50 SD1410-1 7.95 SD1410-3 | 21 00 |
| ECC91 | 3.00 | 4CX1500B | 370.00 | | 1.90 | 6JG6A | 385 | 2N6094 | 8.00 | 2SC1675 | 0 20 | MRF234 | 16.00 | SD1014-6 | 1050 SD1201 | 7.35 SD1412 | 36.00 |
| ECC189 | 210 | 4CX100000 | | | 2.25 | GJHB | 3 25 | 2N6095 | 8.50 | 2SC1678 | 1 25 | MRF237 | 310 | SD1015 | 17 50 SD1202 | 7.50 SD1412-3 | 24.00 |
| ECF80 | 145 | 4D21 | 57.00 | 6CH6 | 9.95 | GJK6 | 2.20 | 2N6255 | 3.45 | 2SC1729 | 18:00 | MRF238 | 12.60 | SD1018-6 | 1300 SD1212-4 | 6 00 SD1413 | 18.00 |
| ECF86 | 2.50 | 4D32 | 64.75 | | 2.30 | 6JM6 | 3 9 5 | 2SC730 | 4.10 | 2SC1730 | 0.25 | MRF239 | 20.00 | SD1019 | 2470 SD1212-7 | 400 501414 | 36.00 |
| ECF801 | 1.85 | 4PR60C | 250.00 | | 1095 | 6JS6C | 3.95 | 250731 | . 395 | 25C1740Q | 0.20 | MRF240 | 24.50 | | 2470 SD1214 | 870 SD1416 | 33.00 |
| ECH81 ECL82 | | 4X150A 5-500A | 42.50 225.00 | | 5.00 3.30 | SKEGT | 2.75 | | 0.25 | | 7 75 | MRF243 MRF245 | 35.00 | SD1020 SD1074 | 1.50 SD1216 16.10 SD1219 | 11.00 SD1418 | 30.00 |
| ECL83 | | 54R4 | 3 50 | | 2 30 | 2AT7 | 1 60 | | 6.60 | | 0.20 | MRF247 | | SD1076 | 18.50 SD1219-4 | 18:00 SD1421 18:00 SD1428 | 36.0 |
| ECL86 | 1.70 | 5AS4A | 2.50 | | 4.95 | 2AU6 | 2.00 | | 0 30 | | 0.30 | MRF260 | 5.00 | 001010 | 10.30 3012194 | S01429 | 15.9 |
| EF40 | 8.50 | 58254M | 24.00 | | 2.20 | 2AU7A | 1.60 | 2SC829B | 0.25 | 2SC1945 | 3.50 | MRF264 | 11.00 | | | 301423 | 13.8 |
| EF80 | 1.35 | 5C22 | 128.00 | 6CW4 | 6.50 | 2AV6 | 2.00 | 25C890 | 8.50 | 2SC1946 | 1975 | MRF309 | 42 00 | | ALSO AVAIL | ABLE | |
| EF85 | 1.65 | 5CX1500A | 535.00 | | 1.95 | *2AX7 | 1 60 | 2SC891 | 18.00 | 2SC1946A | 16.50 | MRF316 | 55.00 | | ALSO ATAIL | ADEL. | |
| EF86 | | 5022 | 76.00 | | 3.80 | 2AX7WA | 4.80 | 2SC900 | 018 | 2SC1947 | 9.88 | MRF317 | 73.00 | A replace | ment guide to dozen | s of Motorola Trans | istor |
| EF89 | 2.30 | 584 | 6.00 | | 3.00 | 2B4A | 2.90 | 2SC900F | 0.19 | 2SC1955 | 7 20 | MRF321 | 35 00 | part numb | | | |
| EF91 EF92 | 2.95 | 5R4GYA/B 5R4WGB | 375 | | 3 15 2 30 | 12BA6 12BA7 | 2.00 | 2SC908 2SC911A | 4.50 | 2SC1966 2SC1967 | 11.00 | MRF323 MRF326 | 35.00 | | original RF Devices f | rom such manufactu | urers |
| EF93 | 1.60 | 55R6 | 6 00 | | 2.45 | 2BE6 | 1.90 | 2SC945 | 0.21 | 25C1968 | 17.50 | MRF327 | 70.00 | 35 | | | |
| EF94 | 1.80 | 5U4GB | 2 50 | 6008 | 1.50 | 128M7A | 2.50 | 2SC945R | 0.21 | 2SC1968A | 22.00 | MRF329 | 58.06 | MOTORO | LA, RCA, GE, TRW, M | ISC ACRIAN TOSH | IRA |
| EF95 | 3.90 | 5UPI | 40.00 | | 1.70 | 128Y7A | 2.65 | 2SC952 | 0.60 | 2SC1969 | 3 50 | MRF412 | 18.51 | | J. NEC. MITSUBUSH | | |
| EF183 | | 5V4GA | 2.75 | | 3.95 | 12BZ6 | 3.70 | 25C982 | 0.30 | 2SC1970 | 1 50 | MRF421 | 36.85 | | and oth | | |
| EF184 | | 5Z4GT | 1.90 | | 2.30 | | 42.00 | 2SC994 | 2.50 | 25C1971 | 4 00 | MRF422 | 42.00 | | | | |
| EFL200 | | 6AH6 | 3.50 | | 2.30 | | 2.90 | 2SC998 2SC1001 | 3.90 | 2SC1972 2SC1978 | 7 50 | MRF426 MRF427A | 23.00 | | POWER TUBE AC | ESSORIES | |
| EK90 EL34 | 1.90 | 6AJ8 6AK5 | 2.50 | | 4 20 2.45 | EIU A | 50.00 | 2SC1001 | 15:00 | 2SC2001 | 0.45 | MRF427A | 57.00 | | | | |
| EL36 | 2 30 | 6AKSW | 2.90 | | 1.65 | | 19.90 | 2SC1070 | 1.15 | 2502026 | 075 | | 75 00 | CHIMNEYS | CONNECTORS F | INGER STOCK SOCI | KETS |
| EL38 | 4.95 | 6AK6 | 195 | | 200 | | | 2SC1096L | 0.90 | | 080 | MRF433 | 16.21 | | | | |
| EL81 | 10.95 | 6AL5 | 1.95 | | 2.00 | H13 (RC | A) 65.00 | 2SC1096M | 0.90 | 2SC2097 | ·36 00 | | 14.95 | ENQUIRIE | S: Quotation for any typ | es not listed SAE | |
| EL83 | 6.00 | BALSW | 1.80 | | | £29B | 17.20 | 2SC1117 | 1.50 | 2SC2099 | 15 00 | | 11.90 | TERMS | | r Cheque with order | - |
| ELB4 | 1.60 | 6AM5 | 9.10 | | 2.10 | | 61.50 | 2SC1120 | 12.50 | 2SC2100 | 24.00 | | 14.00 | 1000000000 | | | |
| EL86 | 1.95 | 6AM6 | 2.95 | | 2.85 | | 10.00 | 2SC1121 | 24.00 | 25C2103 | | MRF453A | 14.00 | CREDIT | | ubject to approved referen | nces |
| EL91 | 9.10 | 6AN8A | 2.70 | | 1.50 | 145 1578 | 48.30 708.00 | 2SC1122 2SC11628 | 18.00 | 2SC2105 | | MRF454 | 21.00 | POSTAGE | Add £1.00 to order u | nder £50 value | |
| EL360 EL500 | 7.95 | 6AQ5A 6AQ5W | 1.95 | | 2.00 | | 15.50 | 2SC11628 | 6.95 | 2SC2116 2SC2118 | 1.60 | MRF454A MRF455 | 24.00 | VAT | All prices are exclud | ing VAT, please add 15% | to |
| EL503 | 39.00 | 6AQ8 | 2.20 | | 2.25 | | 24.00 | 2SC1169 | 4.85 | 25C2221 | 5.50 | MRF455A | 21.00 | 1000 | order and postage | | |
| | 6.00 | 6AR5 | 2.85 | | | E72A | - 19.00 | 2SC1176 | 14.00 | 2502233 | 0.90 | MRF458 | 19.95 | GUARANTEE | Proprieta a construction of the second s | cification and sold with | |
| | | | | | | | | | | | | | | | | | |
| EL505 EL519 | 6.75 | 6AS6 | 5.50 | 6GB5 | 2.80 | 922 | 12.50 | 2SC1177 | 17.25 | 25C2237 | 16.00 | MRF466 | 24.50 | Gordanie | manufacturers warra | | |



SOLARTRON BENCH SCOPES Type CT386 general purpose single beam with 4" PDA CRT with 4Kv for use on 240v. General spec. Y Amp 30 gain settings from 1 Mill/V Cm to at 100Kc to 10v Cm at 10Mc/s, DC 30 gain settings from 1 Mill/V Cm to at 100Kc to 10v Cm at 10MK/s, DC coupled from 1v/Cm T.B. 0.1 Us Cm to 1 Sec/Cm in 7 ranges, X amp up to ×5 expansion, int free run or trig T.B. with provision for ext sync & T.B. out. Approx ext size 16×10" depth 23" supplied in good cond tested with handbook. **£95. ARMY AERIAL KITS** comprise 30ft 1" mast in 10 screw sections plus 2× 16ft 4 section whip aerials, with guys, stakes, base insul, carrying bag etc can be used as 30ft mast or 46ft Ae good cond. **£46. CRYSTAL CAL** type CT432 for 240v, provides O/Ps at 100Kc 1Mc/s & 10Mc/s from 3 int crystals, unit can also be swt to operate from various types of ext crystals also as int mixer amp with O/ operate from various types of ext crystals also as int mixer amp with O/ P for phones, neat unit tested with info. **£28. SIGNAL GENERATORS** Marconi type TF995/A2. for 240v freq 1.5 to 220Mc/s in 5 bands, AM or FM Mod with meter indication, fine & coarse atten in case size 17×12×9" tested with handbook. **£100.** Also TF144G large bench unit 85Kc to 25Mc/s in 8 bands, O/P var 1 Uv to 1 volt, int AM at 400c/s, RF 8 Mod depth meter, late series units tested with circ etc. **£65.** VIDEO RECORDERS Philips N1500/1/2 series units, colour, int Receiver sup-plied with 2 cassettes & circs. **£65. AUDIO OSC** old type BFO 20c/s to 20Kc, var O/P into 600 ohm, O/P meter for 240v in table case, with spare valve kit. **£18. TAPE RECORDERS** Ferrograph series 6 for use on 240v single chap 1 track units with provision for fitting stores hard high \$k\$ single chan 1/2 track units with provision for fitting stereo head, high & low level I/Ps, int speaker with ext speaker O/P of 15 ohm 2.5w, will take al⁴ spools, three speeds 7½/3½/1⅔, in grey leather o/P of 15 ohm 2.5w, will take sl⁴ spools, three speeds 7½/3½/1⅔, in grey leatheret type table case size 18×18×10⁴ in very good cond with handbook. **£85**. **MARCONI TF1041B** VTVM for 240v meas DC volts 300 Mill/V to 1Kv in 8 ranges I/P res 100 Megs, AC volts 300 Mill/V to 300v in 7 ranges, as RF probe to 1500Mc/s, Ohms 50 ohms to 500Megs FSD in 8 ranges, as DC/Ohms & AC/RF probes, size 11×8×7" tested with handbook. **£48. WATT**-METER. Type CT87 for use 100/156 Mc/s 50 ohm max reading 10 watts, meter range can be extended, in case size 6×5½×4". £14.50. ROTARY CONV I/P 24v DC 10 amps O/P 230v AC 50c/s 100 watts in case. £45. Or Rotary only £27. C.B. CAR AERIALS with base loading coil flexible element approx 15" with 13ft RG58 & plug new. £4.50. INDICATOR UNIT with DH7-78 CRT 3" PDA flat face P31 trace, unit as two PCBs with Transis etc, regs 115v 400c/s complete in case size 5×7×15" CRT connec supplied. £25. SERVICES Type CT219 Deviation meters 2.5 to 100Mc/s meas dev 0 to 75 Kc/s in 3 ranges meter indication for 240v with book. £55. S.S.B. COMPONENTS PCBs removed from Tx units, all 455Kc inc LSB mech filter, Bal Mod 455Kc crystal, Audio amp brd, Bal mod for VFO with circs. £18. also 400c/s mech BPF 455Kc. £8.50. Above prices inc carr/postage & VAT, goods ex equipment unless stated new, allow 14/28 days for delivery. SAE with enquiry or 2 × 16p stamps for List 34. A. H. SUPPLIES 122 Handsworth Rd., SHEFFIELD S9 4AE 1 Tel. 444278 (0742)



Practical Wireless, November 1984

C. M. HOWES COMMUNICATIONS FUN TO BUILD KITS BY MAIL ORDER

Building your own radio equipment is one of the most rewarding aspects of amateur radio. We help make construction a pleasure. All our kits come with a clear and full set of instructions, detailed parts list and circuit diagram. The kits include all board mounted components and a good quality glass-fibre printed circuit board. The board has the component locations screen printed on it for easy assembly. It printed circuit coard. The board has the component locations screen printed on it for easy assembly. It has been said that one of the best things about our kits is what we don't include! We leave you to provide your own case and external parts so that you can add your own individual touch. Many customers can make their own cases, or obtain them cheaply at railies so saving money. If you have trouble obtaining these items, we can always supply them, simply phone or write for a quote. We have done the difficult technical bit for you, but you can still build up a piece of equipment with a good deal of your own contribution to the finished item. All kits are also available ready assembled. Choose an interaction excited from express. ng project from our range

Interesting project from our range:-DerX DIRECT CONVERSION COMMUNICATIONS RECEIVER The DcRx is a single band communications receiver that has been designed with the beginner in mind. It is straightforward to build and works amazingly well. Although this is a simple design, a lot of thought and development went into this kit and it is capable of receiving most of the signals that can be heard on very much more expensive equipment. We find that sales of the DcRx split roughly in half between beginners and experienced operators who are looking for an interesting alternative to their expensive rigs. The DcRx is a lot more fun to use than a sophisticated factory built radio, it brings back some of the challenge and satisfaction to amateur radio. You expect an expensive radio to pick up signals from all over the world, when you hear far-off lands on a simple set you built yourself. I find that a little bit of magic is put back into the hobby. We do two versions of this receiver at the moment, one covering either 20 or 30 metres and one for 80

Imagic is but back into the houpy.
We do two versions of this receiver at the moment, one covering either 20 or 30 metres and one for 80 metres. An experienced constructor could easily modify these for other bands. We will be producing a Top-Band (160M) version of this kit, it may be available by the time you read this. If you would fike to see what others think of the DcRx, G3RJV wrote an article on it in the May issue of Shortwave Magazine. Whilst I have been typing this advert out, I have had a phone call from a customer in Holland saying that he is very pleased with his DcRx kit and that a number of his friends want them too, as he is visiting the UK and tweek compter and locate the double of the double. UK next week can be call round and collect half-a-dozen? They must be good! The only external parts you need to go with the kit (apart from a case and the knobs etc.) is a couple of tuning capacitors of about 50pF. If you do not have these in your junk box, we can supply suitable items at £1.50 each whilst stocks last **Brief Details**

- Details: Power required: 12 to 14V DC @ 30@ quiescent ideal for battery use. Audio output: Approx. IW into 8 ohm 'speaker or headphones. Modes: SSB and CW. Bands: 20, 30, or 80 metre versions available. PCB size: Approx. 3 inches (75mm) square.

DcRx Kit £14.80, assembled PCB module £19.90.

ST2 CW SIDE-TONE/PRACTICE OSCILLATOR

ST2 CW SIDE-TONE/PRACTICE OSCILLATOR The ST2 is a very simple to build item, but gives a much nicer sounding note than most of the various Morse code oscillators on the market. The ST2 gives up to 1W output into 8 ohms at approx 800Hz sinewave. The unit will work from a Morse key (electronic or straight) or from the output of a transmitter by RF sensing. This is a very versatile unit, you could use one as a practice oscillator while learning the code, and then later use it with your TX when you have your class A licence. Most practice aids are of no further use after the Morse test, not so with the ST2. It will work with as little as 1W RF on the HF bands, so it is ideal for the QRP operator.

ST2 Kit £7.30, assembled PCB module £10.80.

139 HIGHVIEW, VIGO, MEOPHAM, KENT, DA13 OUT. FAIRSEAT (0732) 823129

COMING SOON!

CUMING SUCUM! We have a couple of new kits that are up and running in prototype form as I write. They may well be available by the time this advert is published. One is a QRP CW TX for 80 metres. This will produce about 5W maximum output, the power level being adjustable. The basic TX is crystal controlled, but provision is made for adding a VFO. We will be producing a VFO kit, and another module that will enable the transmitter to be used with the DcRx as a full transceive setup. Versions for other bends will be along in a while. The basic 80M TX kit will include a crystal and the price will probably be a little cheaper than the mpanion DcRx receiver.

companion DcRx receiver. The other prototype that is working nicely on the bench at the moment is a desk mic kit. This includes a microphone capsule and a Plessey VOGAD compressor/preamp. This is a very nice sounding unit that is getting super reports on FM, both on 2M and CB. The kit is going to be priced at a very keen rate at about £10. I think you will have a hard job to beat this for value in desk mics, especially as reports over the air indicate that the audio quality is as good as some of the most expensive items on the market. If you would like more details and an accurate price on these items, send us an SAE. I will try and make sure we have an information sheet on these ready by the time this appears in print.

XM1 mk2 CRYSTAL FREQUENCY MARKER



A must for any shack, the XM1 is a very useful piece of test equipment, as well as helping keep you "legal". This is a very comprehensive calibrator, having a built in voltage regulator and EIGHT marker output frequencies. See the picture above and read the review of the mark one version in the June issue of "Amateur Radio"

Marker outputs: 10, 2.5 & 1 MHz, 250, 100, 25, 10 & 2.5 kHz. These are useable from LF up to UHF.
 Power required: Any voltage from 8 to 24V DC @ approx. 40mA.

XM1 mk2 Kit £16.80, assembled PCB module £21.30.

AP3 AUTOMATIC SPEECH PROCESSOR The AP3 has sold over 1000 units since my article in the September '83 issue of "Ham Radio Today". This excellent processor really can make the difference between working a station and failing to get through. The AP3 uses a Plessey V0GAD chip for automatic level control and has four selectable dipping levels in approx 6dB steps. The unit has a built in voltage stabiliser, active filtering, and turns itself on and off automatically. There is only one adjustment to make to set the output level, so the AP3 is really easy to get going.

PAZ/15 10dB gain 15W 2M linear amplifier PAZ/30 30W 8dB gain 2M linear amplifier CO1 RF or PTT operated switching unit for above amps The PA series amplifiers are suitable for FM, CW and SSB.

Kit £18.90, assembled £23.90 Kit £22.90, assembled £27.90 Kit £9.80, Built £13.80

If you would like further information on any product, simply drop us a line, enclosing an SAE. We have an information sheet on each item. We aim to keep everything in stock and delivery within 7 days. Please add 60p P&P to your total order value. 73, Dave, G4KQH Technical Manager

| COMN | Λυνια | CATIO | N CE | NTRE |
|------|-------|-------|------------|------|
| | - | IE NO | 1 101112 0 | |

The largest range of communications equipment available in the North. Full range of receivers, transceivers, antennas, power supplies, meters. Ali tubing – wall brackets etc.

We are the original amateur radio suppliers in the North West with 20 years experience in all types of equipment.

We are the only official TRIO stockists in the North West. Full range of equipment on display. Guaranteed after sales service.

RECEIVERS

| TDIO DOOD Calid Ctata Dessiver | £272.00 |
|---|----------------|
| TRIO R600 Solid State Receiver | |
| TRIO R2000 Solid State Receiver | £436.00 |
| JRC NRD515 Receiver | £965.00 |
| YAESU FRG7700 Receiver | £385.00 |
| Wide Band Scanning Receiver AR2001, | |
| 25-550 MHz | £345.00 |
| R532 Airband Receiver | £175.00 |
| Please send SAE for full information a | nd up-to-date |
| prices as these fluctuate to change in ste | erling rates. |
| For the caller a wide range of Aluminium T | ubing, Clamps, |
| etc. at competitive prices, i.e. 12' × 2" Ali Tub | ing £9.00. |
| Full range of RSGB and ARRL publication | ns in stock. |
| Part Exchanges welcome. Second hand | lists daily. |
| Send S.A.E. for details of any equip | ment. |
| HP terms. Access/Barclaycard facil | |
| Open 6 days a week. 24 Hour Mail Orde | er Service. |

Phone 0942-676790.

STEPHENS JAMES LTD. 47 WARRINGTON ROAD, LEIGH, LANCS. WN7 3EA.

| R | S | Γ | | 159 I SPECIAL | Fallsbroo | MAIL ORDE angrex Supp Climax Ho ok Road, Str RESS MA | lies Ltd., ouse, eatham, | SW16 6ED | VICE |
|----------------|------------|----------------|------------|---------------------|-----------|--|--------------------------------|----------|--------|
| | | EM81 | 2.50 | PL509 | 6.00 | 6AK5 | 5.99 | 61.6G | 3.00 |
| AZ31 | £p 2.75 | EM87 | 2.50 | PL519 | 6.00 | 6AL5 | 1.50 | 6L6GC | 3.50 |
| CL33 | 4.00 | EN91 | 6.50 | PL802 | 6.00 | 6AM6 | 6.02 | 6L7 | 2.50 |
| DY86/7 | 1.50 | EY51 | 2.75 | PY33 | 2.50 | 6AN5 | 4.75 | 6LQ6 | 7.50 |
| DY802 | 1.50 | EY86 | 1.75 | PY81 | 1.50 | 6ANBA | 3.50 | 607 | 3.75 |
| EBSCC | 8.42 | EY88 | 1.75 | PY82 | 1.50 | 6AQ5 | 2.25 | 6SA7 | 3.00 |
| E180F | 10.20 | EY500A | 3.00 | PY83 | 1.25 | 6AR5 | 3.50 | 6SC7 | 2.75 |
| E810F | 35.48 | EZ80 | 1.50 | PY88 | 2.00 | 6AS6 | 8.66 | 6SJ7 | 3.25 |
| EABC80 | 1.25 | EZ81 | 1.50 | PY500A | 4.00 | 6AS7G | 8.75 | 6SK7 | 3.50 |
| EB91 | 1.50 | GY501 | 300 | PY800 | 1.50 | 6AT6 | 1.25 | 6SL7GT | 3.00 |
| EBF80 | 1.50 | GZ32 | 4.00 | PY801 | 1.50 | 6AU5GT | 5.00 | 6SN7GT | 3.00 |
| EBF89 | 1.50 | GZ33 | 4.75 | QQV02-6 QQV03-10 | 31.80 | 6AU6 6AW8A | 2.50 | 6SS7 | 2.75 |
| EC91 | 8.00 | GZ34 | 3.00 | | | 6B7 | 3.75 | 6SG7M | 2.50 |
| ECC33 | 4.50 | GZ37 | 4.75 | QQV03-20/ | 48.38 | 688 | 3.25 | 6UBA | 2.25 |
| ECC35 | 4.50 | KT61 | 5.00 | QQV06-40 | | 6BA6 | 1.50 | 6V6GT | 2.25 |
| ECC81 | 1.75 | KT66 | 12.00 | 00000-407 | 75.00 | 68A7 | 5.00 | 6X4 | 2.00 |
| ECC82 | 1.75 | KT77 | 9.00 | QV03-12 | 6.80 | 6BE6 | 1.50 | 6X5GT | 1.75 |
| ECC83 | 1.75 | KT88 | 15.00 | R18 | 3.00 | 6BH6 | 2.50 | | |
| ECC85 | 1.75 | N78 | 15.00 | B19 | 9.24 | 68.16 | 2.25 | 12AX7 | 1.75 |
| ECC88 ECC91 | 2.10 | OA2 | 3.25 | SP41 | 6.00 | 6BN6 | 2.00 | 12BA6 | 2.50 |
| ECF80 | 1.50 | OB2 | 4.35 | SP61 | 4.00 | 6BQ7A | 3.50 | 12BE6 | 2.50 |
| ECH35 | 3.00 | OC3 | 2.50 | U19 | 13.75 | 6BR7 | 6.00 | 128Y7A | 3.00 |
| ECH42 | 3.50 | OD3 | 2.50 | U25 | 2.50 | 6BR8A | 3.50 | 12HG7 | 4.50 |
| ECH81 | 3.00 | PC86 PC88 | 2.50 | U26 | 2.50 | 6BS7 | 6.00 | 30FL1/2 | 1.38 |
| ECL80 | 1.50 | PC88 PC92 | 1.75 | U37 | 12.00 | 6BW6 | 6.00 | 30P4 | 2.50 |
| ECL82 | 1.50 | PC92 PC97 | 1.75 | UABC80 UBF89 | 1.25 | 6BW7 6BZ6 | 1.50 2.75 | 30P19 | 2.50 |
| ECL83 | 3.00 | PC900 | 1.75 | UCH42 | 2.50 | 6020 | 1.25 | 30PL13 | 1.8 |
| ECL86 EF37A | 1.75 | PCFB0 | 2.00 | UCH81 | 2.50 | 6C6 | 1.75 | 30PL14 | 1.80 |
| EF37A EF39 | 2.75 | PCF82 | 1.50 | UCL82 | 1.75 | 6CB6A | 2.50 | 5728 | 30.00 |
| EF41 | 3.50 | PCF86 | 2.50 | UCL83 | 2.75 | 6CD6GA | 5.00 | 805 | 45.0 |
| EF42 | 4.50 | PCF801 | 2.50 | UF89 | 2.00 | 6CL6 | 3.75 | 807 | 3.7 |
| EF50 | 2.50 | PCF802 | 2.50 | UL41 | 5.00 | 6CH6 | 13.00 | 811A | 18.3 |
| EF54 | 5.00 | PCF805 | 1.70 | UL84 | 1.75 | 6CW4 6D6 | 8.00 | 812A | 29.5 |
| EF55 | 3.50 | PCF808 | 1.70 | UY41 UY85 | 2.25 | 6005 | 6.00 | 813 | 125.8 |
| EF80 EF86 | 1.75 | PCH200 | 3.00 | VR105/30 | 2.50 | 6EA8 | 3.00 | 866A | 20.03 |
| EF91 | 2.95 | PCL82 | 2.00 | VR150/30 | 2.50 | 6EH5 | 1.85 | 872A | 20.0 |
| EF92 | 6.37 | PCL83 | 3.00 | Z759 | 25.00 | 6F6 | 3.00 | 931A | 18.5 |
| EF183 | 2.00 | PCL84 PCL85 | 2.00 | Z803U | 19.00 | 6Gk6 | 2.75 | 2050 | 7.0 |
| EF184 | 2.00 | PCL85 PCL86 | 2.50 | 2D21 | 3.25 | 6H6 | 3.00 | 5763 | 4.5 |
| EH90 | 1.75 | PCL805 | 2.50 | 3B28 | 40.00 | 6HS6 | 3.77 | 5814A | 4.0 |
| EL32 | 2.50 | PD500 | 6.00 | 4CX250B | 45.00 | 6J5 | 4.50 | 5842 | 12.0 |
| EL33 | 4.00 | PFL200 | 2.50 | 5R4GY 5U4G | 3.50 3.00 | 6J6 6J7 | 4.75 | 6080 | 14.0 |
| EL34 EL36 | 4.00 | PL36 | 2.50 | 5V4G | 2.50 | 6JB6A | 5.00 | 6146A | 8.2 |
| EL36 EL81 | 5.25 | PL81 | 1.75 | 5Y3GT | 2.50 | 6JS6C | 6.00 | 6146B | 8.2 |
| EL84 | 2.25 | PL82 | 1.50 | 523 | 4.00 | 6K4N | 2.50 | 6883B | 8.2 |
| EL86 | 2.75 | PL83 | 2.50 | 5Z4GT | 2.50 | 6K6GT | 2.75 | 6973 | 4.0 |
| EL91 | 9.69 | PL84 | 2.00 | 6/30L2 | 1.75 | 6K7 | 3.00 | 7360 | 10.0 |
| EL95 | 2.00 | PL504 | 2.50 | 6AB7 | 3.00 | 6K8 | 3.00 | 7586 | 12.0 |
| EL360 | 8.50 | PL508 | 2.50 | 6AH6 | 5.00 | 6KD6 | 7.00 | 7587 | 18.5 |
| | | Open daily | to callers | : Mon-Fri 9 | a.m5p.r | n. | | Prices | orrect |
| | | | | sistors - Clo | | I-677 2424/7. | | when | |
| | lerms L.V | y.u. only, al | iow / day | /s for deliver | v. rel. U | -0// 2424/1. | in a successful | | ress |

Practical Wireless, November 1984



Practical Wireless, November 1984



Receivers and Components

COMPONENTS AT BARGAIN PRICES. All full spec. devices. S.A.E. for current list. Box No. PW187.

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. FORRESTERS (National Radio Supplies) late Holdenhurst Rd. now at 36, Ashley Rd.. Boscombe. Tel. 302204. Closed Weds.

CRYSTALS Made to order for any purpose and large stocks of standard frequencies for computers, modems, etc. Amateur CW (QRP) freqs £4.00 and CB conversion crystals at £4.50. PROGRAMMABLE OSCILLATORS (PXO) for baud rates, MPU, and freq markers £12.50.

FILTERS Crystal, monolithic, mechanical and ceramic for all standard IF's. Special 10.695MHz for big improvement to most CB rigs at £4.50 each.

S.A.E. FOR USTS. PRICES INCLUDE VAT AND POST P. R. GOLLEDGE ELECTRONICS G3EDW, Merriott, Somerset, TA16 5NS Tel. 0460 73718

UNAVAILABLE COMPONENTS IN WEEKS! RICKMAN, South Ronaldsay, Orkney KW17 2TW. Or Phone 085683-430.

RADIO CANADA, Peking, Australia, Voice of America. A Vega 206 (6× SW/MW/LW) pulls these and dozens more. £23.95. Year's guarantee. Return despatch. CORRIGAN-RADIOWATCH, Building 109, Prestwick Airport, KA9 2RT.

Educational

COURSE FOR CITY & GUILDS, Radio Amateurs Examination. Pass this important examination and obtain your licence. with an RRC Home Study Course. For details of this and other courses (GCE, Career and professional examinations, etc.,) write or phone: THE RAPID RESULTS COLLEGE, Dept JX15, Tuition House, London, SW19 4DS. Tel. 01-947 7272 (9am-5pm) or use our 24hr Recordacall Service: 01-946 1102 quoting Dept JX15.

SMALL ADS

The prepaid rate for classified advertisements is 36 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £12.00 per single column centimetre (minimum 2-5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Dept., Practical Wireless, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St, London, SE1 9LS. (Telephone 01-261 5785).

NOTICE TO READERS

Whilst prices of goods shown in advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

Aerials

AERIAL BOOSTERS Next to the set fitting B45H/G-UHF TV, gain about 20dbs, Tunable over the complete UHF TV band. PRICE 68.70. AMPLIFIED SET TOP AERIALS for UHF TV, trebles the gain. PRICE £9.70.

 FILE 15.7U.

 All Boosters we make work off a PP3/006p/6F22 type battery or 8v to 18v DC. P&P 30p PER ORDER.

 ELECTRONIC MAIL ORDER, 62 Bridge Street, Ramsbottom, Lance SILO 346, Tel. (070682) 3036.

 Access/Visa Cards Welcome
 SAE Leaflets

G2VF D.I.Y. H.F. long and medium wave frame antennas, S.A.E. for details; F. RYLANDS, 39 Parkside Avenue, Millbrook, Southampton.

WORLD RECORD JOYSTICK ANTENNA: 2ft. long successor now available. Details s.a.e. PARTRIDGE G3CED, 17 Ethel Road, Broadstairs, Kent. Tel. 0843 62839.

G2DYM AERIALS **KILL THAT INTERFERENCE** ANTI-TVI ANTI-QRN

Data sheets, Large 23p SAE. Aerial Guide **75p**. Callers for Appointment Tel. 03986-215 G2DYM, Uplowman, Tiverton, Devon.

G5RV TYPE AERIALS half size £13.00, full size £14.95. NEW HARD DRAWN COPPER AERIAL WIRE. 140ft 14swg £7.90. 50 metres 16swg £6.90. All items postage paid. S. M. TATHAM, 1 Orchard Way, Fontwell, Arundel, West Sussex.

50M (165ft) AERIAL WIRE. Strong PVC covered copper -£4.80 inc. Post. W. H. WESTLAKE, Clawton, Holsworthy, Devon

Service Sheets

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc., £1.50 plus SAE. Service Manuals on Colour TV and Video Recorders, prices on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

TECHNICAL INFO SERVICES 76 Church St - Larkhall - Lanarks

FULL SIZE SERVICE SHEETS Any radio, audio £2.50 + I.s.a.e. CTVs/MusC £3.50 + I.s.a.e. complete set

> Worlds largest collection service manuals 30's - date from £4.50-£35 each.

Comprehensive T.V. Repair Course Complete Radio Service & Repair Course ONLY £9.50 EACH

Repair data/circuits almost any named TV/Video for £10.50

S.a.e. brings any quotation FREE 50p mag. inc. service sheet! Pricelists unique elect. publications

FOR FAST QUOTES **BING 0698 883334**

Shows

MET ANTENNAS look forward to seeing old and new friends at the forthcoming Leicester Show on October 26th and 27th on stand 34

Books and Publications

SHORTLISTS SECONDHAND BOOKS SALE, Wireless, Television, others, State interest, SAE: GOSLING, 19 Moorside Road, Westmoors, Dorset.

RADIO & RTTY BOOKS GUIDE TO RTTY FREQUENCIES Lists 4,500 Commercial Aero, U.N., Coastal, etc., frequencies. £7.85 + 50p P&P. WORLD PRESS SERVICES FREQUENCIES News RTTY Ser-vices listing GMT and Country, plus more £5.55 + 50p P&P. RTTY TODAY, Beginners RTTY Guide £4.90 + 50p P&P. CLANDSTINE CONFIDENTIAL Rebel Radio £5.55 + 50p P&P. 2 + Books P&P Free.

INTERPRODUCT LTD. PW12, Stanley, Perth, PH1 4QQ. Tel: 073882-575

| Cheques and Postal | Orders should be cross | ed Lloyds Bank Ltd. and | made payable to Practical | Wireless) |
|--------------------|------------------------|-------------------------|---------------------------|-------------------------------------|
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | DDAOTIOAL | ed Advertisement Dept., WIRELESS |
| LAME | | | Classified Adver | |

Software

MORSE READING PROGS. Work on clean signals without hardware interface. ZX81 1K Unexpanded Memory. Translated code with word and line spaces for easy reading. Automatic scroll action. £7 incl. Spectrum 16/48K. Scroll action with 10-page scrolling memory, instantly accessible page by page. £8 incl. All types variable speeds. Feed signal direct into Ear socket. PINEHURST DATA STUDIOS, 69 Pinehurst Park, West Moors, Wimborne, Dorset. BH22 0BP.

SPECTRUM 16/48K, ZX81 1/16K RTTY. Features such as split screen type ahead, auto TX/RX, 26 programmable memories plus many more. For more details of programs, PCB's, Kits, and ready made units send s.a.e. to G4MJC/ G4FDW, 3 Aylesbury Avenue, Eastbourne BN23 6AB.

"DIDI-DIDA" New Morse Tutor for CBM64 is the best yet and its many features will improve your receiving and sending ability. Cassette £7.00. Disc £9.00. MORAY MICRO COM-PUTING, Enzie Slackhead, Buckie, Moray. AB52BR.

MORSE READER for Spectrum, Dragon, any Vic 20. Self tracking approx. 8/30 wpm. Spectrum needs no interface, others use simple one transistor interface. Full instructions and cassette, £6.00. Spectrum Morse Tutor, variable speed and spacing, £4.50. J. E. PRICE, 4 Housman Walk, Kidderminster.

For Sale

COSSOR TWIN WAVE OSCILLOSCOPE for sale £95 o.n.o. 061-494 1487 MR. FENLON.

NEW AND USED Amateur Radio Equipment, supplied, bought and exchanged. Sae for list. CALBRESCO LTD., 258 Fratton Road, Portsmouth, Hants. Telephone: 0705 735003.

AMATEUR EQUIPMENT BOUGHT, Sold, Exchanged. Telephone Dave, 040 24 57722: or send SAE for current list. Equipment also sold on a commission basis. G3RCQ ELECTRONICS, 132 Albany Road, Hornchurch, Essex.

| ANTENNES TONN | A (FOFT) | 1296MHz OR 1269MHz OSCAR UPLINK |
|----------------------|------------------|---|
| | | 23 element £25.90(b) |
| 50MHz | CO4 00/-1 | 4×23 element – power splitter |
| 5 element | £34.30(a) | - stacking frame £140.00(a) |
| 144MHz | | ALSO AVAILABLE FOR 1250MHz |
| 4 element | £14.95(a) | •denotes available for 50 Ω or 75 Ω |
| 5 element crossed | £26.30(a) | all others 50 Ω ONLY. |
| 9* element fixed | £17.71(a) | PORTABLE ALUMINIUM TELESCOPIC MASTS |
| 9* element portable | £20.00(a) | 4×1m £20.70(a) 3×2m £24.15(a) |
| 9° element crossed | £32.43(a) | 4×2m £36.66(a) |
| 13 element portable | £31.05(a) | GALVANISED STEEL TELESCOPIC MASTS |
| 17* element fixed | £37.66(a) | |
| 435MHz | | 2×3m £30.48(a) 3×3m £54.77(a) |
| 9 element | £16.10(a) | 4×3m £88.41(a) 5×3m £119.60(a) |
| 19* element | £20.70(a) | STACKING FRAME KITS FOR 4 ANTENNAS |
| 19* element crossed | £34.27(a) | POWER SPLITTERS FOR 2 AND 4 ANTENNAS |
| 21* element 432MHz | £29.67(a) | |
| 21* element ATV | E. (5.3751650) | ANDREW LDF4-50 HELIAX COAXIAL CABLE |
| 144/435MHz | | ROTATORS - COAXIAL CABLE-CONNECTORS |
| 9 & 19 element Oscar | £34.27(a) | |
| | | . (b) £1.95. ALL PRICES INCLUDE VAT AT 15% |
| | | none your card number for immediate despatch. |
| | | SEND 40p FOR CATALOGUE |
| | | |
| | | ointment only please. Goods by return. |
| | | CTRONICS (P) |
| 12 Conduit Road, | Abingdon, Oxon O | X14 1DB. Tel: (0235) 23080 (24 hours) |



For Sale Cont:

FOR DISPOSAL: Douglas Progressive Wave Winder & Transformer Winder, both motor driven. Wire enamelled, Litz, Silk, Rayon. Avos. Marconi. Cossor. Equipment. Requests with stamp please to 4 Bengyes Road, Necton, Swaffham, Norfolk,

AR2001 SCANNER 25-500MHz. New condition, original packing, £320 o.n.o. G41JF/G5CCI, Tel. (0206) 396610.

PRACTICAL WIRELESS VOL. 1. 1-15, individual copies two blueprints. Good condition. Offers. Tel. 0865 (Oxford) 241054, daytime.

SHORTWAVE RECEIVERS. Racal RA117E. AR88D. Yaesu FRG7, Century Digital (New), Advance Signal Gener-ator. Lots of other equipment. Part exchanges. G3EKX. S.S.B. PRODUCTS, Tel. 0872-862575 (Cornwall).

Miscellaneous

SUPERB INSTRUMENT CASES by BAZELLI, manufactured from PVC, Faced steel. Vast range. Competitive prices start at a low £1.50. Punching facilities at very competitive prices. Suppliers only to Industry and the Trade. BAZELLI, (Dept No. 25), St. Wilfrid's, Foundary Lane, Halton, Lancaster LA2 6LT.

FREE! PARCEL OF COMPONENTS worth £10. Send only 80p postage!. D. HORSLEY, 113 Clare Road, Braintree, Essex

NEW AND SURPLUS components and equipment now in stock. Also amateur, F.M. and T.V. aerials and a complete range of burglar alarm equipment. Write or phone for price list. SPECTRUM RADIO AND ELECTRONICS LTD., 36 Slater Street, Liverpool L1 4BX. Tel. 051 709 4628.

RIGONDA. Complete range of spares for all models Rigonda radiograms, record players, televisions. Also reconditioned complete chassis, speakers, record players. Repairs undertaken. Write for information: RIGONDA SUPPLIES, c/o 332 Cann Hall Road, London E11.

QSL CARDS, printed to your own design on white or coloured gloss card. SAE for samples to: THE NUTLEY PRESS, 21 Holmethorpe Avenue, Redhill, Surrey RH1 2NB.

MORSE CODE PREPARATION

Cassette A: 1-12 wpm for amateur. Cassette B: 12-25 wpm for professional examination preparation.

preparation. Price of each cassete (including booklets) **£4.75**. Morse key with separate battery (PP3) – driven solid-state oscillator and sound transducer produces clear tone for sending practice. Price of key with electronic unit **£8.50**. Price includes postage etc Europe only.

MH ELECTRONICS (Dept PW) 12 Longshore Way, Milton. Portsmo

QSL CARDS. Gloss or tinted cards. SAE for samples to TWROG PRESS, Dept PW, Penybont, Gellilydan, Blaenau Ffestiniog, Gwynedd.

WAVEGUIDE, FLANGES & DISHES. All standard sizes & Alloys (new material only) from stock. Special sizes to order. Call EARTH STATIONS 01-228 7876. 22 Howie Street, London SW11 4AR.

BURGLAR ALARM EQUIPMENT. Ring Bradford (0274) 308920 for our catalogue or call at our large showrooms opposite Odsal Stadium.

HEATHKIT. UK Spares and Service Centre. CEDAR ELECTRONICS, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. (0684) 73127.



- RARE DX UNDER ORM? DIG it OUT with a Tunable Audio Notch Filter, between your
- receiver and speaker, BOOST your DX/QRM ratio, £17.40, hear WEAK DX. LONG WIRE ANT? Outside or INDOOR, boost DX with a 0.1-30MHz Antenna Tuner, adapts to absorption wavemeter etc, 10W tx, £25.20, ideal for FRG7700 etc.

Each fun-to-build kit includes ALL parts, instructions, case etc, by-return postage, list of other kits.

CAMBRIDGE KITS 45 (PL) Old School Lane, Milton, Cambridge.

| | the local sector is a sector of the |
|--------|-------------------------------------|
| LINEAR | IFIFDC |
| | |
| | |

| | D.C. Supply | Power In | Power Out | Preamp Incl. | Kit | Ready Built & Tested |
|---------------|---|---|---------------------------|------------------------|-------------|-------------------------|
| 2 METRES | 13.8v | 1.5w | 15w | No | £24.50 | £36.50 |
| | 13.8v | 2.5w | 25w | No | £29.50 | £39.50 |
| | 13.8v | 10/15w | 40/50w | Yes | £29.50 | £43.50 |
| | 13.8v | 2.5w | 50w | Yes | £44.50 | £57.50 |
| | 13.8v | 2.5w | 100w | Yes | £89,50 | £109.50 |
| | 13.8v | 10w | 100w | Yes | £69.95 | £89.50 |
| | 13.8v | 25w | 100w | Yes | £59.85 | £78.95 |
| | Mains Operated | | 150w | Yes | | £159.50 |
| | Mains Operated | | 150w | Yes | | £169.95 |
| 70 cms | 13.8v | 1.5w | 10w | No | £26.95 | £39.95 |
| | 073715 | 1.5w | 40w | No | £59.95 | £71.95 |
| | | 10w | 40w | No | £52.00 | £64.50 |
| connectors. | e pre-drilled cas Pre-amp gain -2 | 22dB, <n.f< td=""><td>sink and a . 1.5dB, Au</td><td>all parts to Switch</td><td>except RF</td><td>Input/Outpu eover.</td></n.f<> | sink and a . 1.5dB, Au | all parts to Switch | except RF | Input/Outpu eover. |
| SUPPLIES | BREMI 13.8v 10a TARREN 13.8v 5 RFD 13.8v 20a Re | -7a Regula | ted P.S.U. | | | £19.9 |
| 4 | have a limited num All goods sold gua | aranteed for | or 12 mont | ths incl. P | A. Transist | tors. |
| | Post & Packing £0 | | | | v 21 days f | or aenvery. |
| S.A.E. for fu | urther info: | R.F. | DEVIC | ES | | |

49 Roxholme Terrace, Leeds LS7 4JH. Telephone (0532) 680410

ICOM IC:271H,£819 The IC-271H is the most advanced 2 meter transceiver available today, it covers the spectrum from 144-146 MHz with FM, SSB, or CW using the most advanced 10Hz PLL system. The IC-271H is suitable for simplex, repeater operation, moonbounce or satellite work, and has features found on no other transceiver.

Some standard features include 32 tunable memories, a high visibility fluorescent display, RIT readout, scanning, 12V DC operation with optional AC power supply.

The 271H has a speech synthesizer that announces the displayed frequency, ideal for blind operators, this is an optional extra along with the SM6 desk microphone and 22 channel memory extension with scan facilities.

Practical Wireless, November 1984



easier, it contains all the necessary addid and in processing to turn a good quality intruder alarm module (e.g. Solfan type) into a 10GHz WBFM system – just add an antenna (why not the PW dish?), microphone, loudspeaker and a few controls, and you're well on your way to all the fun of one of amateur radio's fastest growing interests!

The GDIF 107ub comes as a ready assembled, aligned and tested printed circuit board with very full instructions and helpful hints on how to get the whole system together. For further information please ring or write. Thanks.



Practical Wireless, November 1984

£3.00

£2.75

£2.00

£3.00

£1.75

£2.75

£3.50

£3.75

£2.75

£4.00

£5.00

£4.00

£4.30

£3.25

Access

(each)

July 1983

July 1983

July 1983

July 1983

July 1983

Oct 1983

Oct 1983

May 1984

May 1984

June 1984

Barclaycard Visa

Marchwood Power Unit

PW Capacitance meter

PW Digital calibrator

Transceiver Box Unit

PW IF Signal Generator

Top Direction Receiver

Suppliers of R.S. Components.

Please send Cash with Order

C. BOWES ELECTRONICS LTD Unit 7, Kenwood Road, Reddish, Stockport, Cheshire SK5 6PH. Tel: 061 432 9434 Goods by Return

Top Band Receiver

Auto Notch Filter

PW Seven

PW Seven

PW Dart

Bridport

PW Prescaler

PW Prescaler

WR161

WR169

WR168

WR171

WR174

WR173

WR182

WR179

WR175

WR183

WR184

WR185

WR176/177/178

WR172A

INDEX TO ADVERTISERS

| A.J.H. Electronics | 79 |
|-------------------------------------|------|
| A.H. Supplies | 72 |
| Allweld Engineering | 66 |
| Alyntronics | 12 |
| Amateur Electronics U.K. | , 11 |
| Amateur Radio Exchange | 8, 9 |
| Birkett, J. | 80 |
| Blackstar | 30 |
| Bredhurst | 30 |
| Cambridge Kits | 77 |
| C. Bowes | 78 |
| C.Q. Centre | 12 |
| Colomor Electronics | 80 |
| Datong Electronics | 12 |
| Davtrend | 65 |
| Dressler (U.K.) Ltd | 15 |
| Electronic Mail Order | 76 |
| Electro-Tech Ltd | 66 |
| Electrovalue | 80 |
| G2DYM Aerials | 76 |
| Garex Electronics | 60 |
| Golledge Electronics | 76 |
| Greatech Electronics | 72 |
| G.W. Morse Keys | 80 |
| Hightech Antennae (Scotland) LtdCov | er 2 |
| Howes, C.M., Comms | 74 |
| I.C.S. Intertext | 72 |
| Interproduct Ltd | 76 |

| Lecmar Electronics Leicester Amateur Radio Show Leisuretronics Lee Electronics Low Electronics 2 | 14 16 73 66 , 3 |
|--|-----------------------------|
| Maplin SuppliesCove M.H. Electronics | r 4 77 |
| Microwave Modules Mutek | 59 78 |
| Dedia & T.V. Candida | 60 |
| Radio & T.V. Servicing Randam Electronics | 77 |
| R.A.S. Nottingham | 79 |
| R.E.G. Petri | 79 |
| R.F. Devices | 77 |
| R.S.T. Valve | 74 |
| R. Withers Comms | 30 |
| S.E.M. | 14 |
| South Midlands Comms | |
| South-West Aerials | 66 |
| Stephens-James, Ltd | 74 |
| | - |
| Technical Info Services | 76 |
| Thanet Electronics | 13 |
| Timestep TransCanada Expedition | 23 |
| | |
| Ward & Co., RegCove | r 3 |
| Waters & Stanton | 29 |
| Weirmead Ltd. | 80 |
| Wood & Douglas | 14 |



AJH ELECTRONICS

Practical Wireless, November 1984



79

| J. BIRKETT 25 THE STRAIT, LINCOLN LN2 1JF. TEL 20767 | |
|--|--|
| | |
| MULLARD I.F. AMPLIFIER MODULE LP1165 470KHz plus 10.7MHz, No Details @ £1.50. | |
| MULLARD CRYSTAL FILTER LP1175 470KHz @ 95p. | |
| MULLARD VARIABLE AIR SPACED CAPACITOR 500+170p.f. @ £1.50. | |
| CRYSTALS 10XAJ Type 500KHz, 600KHz, 1MHz, 6MHz @ £1.50 each. Glass B7G Type 100KHz @ | |
| £1.50, Wire ended glass 28KHz, 28.5KHz @ 60p, T05 CAN 10MHz @ £1.50. | |
| X BAND GUNN DIODES with Data @ £1.65. | |
| TAPE ENDED S BAND 3GHz DETECTOR DIODES DC1509 @ £1.95. | |
| X BAND TUNING VARACTOR DIODES 2p.f. or 4p.f. @ £1.65 each. | |
| X BAND DETECTOR DIODES similar to S1M2 @ 25p. | |
| PASSIVE LIMITED PIN DIODE Range 1 to 12GHz Handling 100WATT @ £1.65. | |
| AERIAL SWITCHING PIN DIODES VHF Type @ 40p, UHF Type @ 60p. | |
| CRYSTAL FILTERS ITT538ACB 1.4MHz BW 3KHz @ £5. | |
| S.E.I. QC1112V 1.4MHz BW 32KHz @ £5, QC1112Z 1.4MHz 32KHz @ £5. ITT 10.7MHz BW 6KHz @ | |
| £5, ITT 10.7MHz BW 3.7KHz @ £5. ITT 21.4MHz BW 7.5KHz @ £3.50, ITT 68.6MHz Type 237 @ £3.50. | |
| VERNITRON CERAMIC 10.7MHz FILTERS @ 6 for £1. | |
| LOW PROFILE 12VOLT SPCO RELAYS suitable for aerial switching @ 60p. | |
| AIR SPACED TRIMMERS 15p.f. @ 15p, Differential Type 10×10p.f. @ 18p. | |
| VMOS POWER TRANSISTORS VK10KM @ 50p, VN90AA @ 80p, WM211 @ 40p. | |
| LEADLESS DISCS 4.7p.f., 220p.f., 1000p.f. ali @ 20p Doz. | |
| 50 ASSORTED INSULATED STAND-OFFS @ 45p, 50 assorted metal spacers @ 35p. | |
| 2GHz STRIPLINE NPN TRANSISTORS 18VOLT @ 3 for £1.15. | |
| VHF FETS like 2N3819, J304 @ 6 for £1. | |
| ACCESS AND BARCLAYS CARDS ACCEPTED. Post and package 50p under £5. OVER FREE. | |
| WOOD AND DOUGLAS KITS available by post and for callers. | |
| Goods normally by return. | |
| | |

VALVES VAT VALVES Minimum Special Order £1 Quality 0.60 0.95 0.65 0.65 0.60 0.60 0.80 0.95 12AU7 **UF8G** 0.85 FY51 OV03-12 4.20 584GY 1.80 FCC83 UV03-12 SP61 TT21 TT22 UABC80 UAF42 UBF80 ECC84 ECC85 ECC88 ECC88 ECC189 EY81 EY86/87 EY88 EZ80 EZ80 0.75 0.75 0.95 1.50 0.75 1.80 5U4G 6F12 6F14 1.50 12AV6 12AX7 0.65 32.20 29.50 0.75 220 5V46 9.50 5Y3GT 0.75 5Z3 1.20 5Z4G 0.70 5Z4GT 1.30 3.20 0.75 1.75 0.90 1.25 3.00 18.95 0.95 6F15 1.50 6F17 0.75 6F23 1.05 6F24 0.90 6F33 0.70 6FH8 1.15 6GA8 0.60 6GH8 1.15 6H6 0.65 6H6 6F15 128A6 128E6 128H7 12E1
 ECC804
 0.90

 ECF80
 0.85

 ECF80
 0.85

 ECF81
 0.85

 ECF82
 0.85

 ECF81
 1.05

 ECH414
 2.26

 ECH414
 2.26

 ECH414
 2.26

 ECH414
 0.80

 ECH414
 0.80

 ECH41
 0.70

 ECH41
 0.70

 ECH41
 0.70

 ECH41
 0.77

 ECH42
 0.77

 ECH43
 0.77

 ECH43
 0.77

 ECH43
 0.80

 EF33
 0.80

 EF33
 1.50

 EF80
 0.60

 EF95
 0.65

 EF80
 0.80

 EF94
 1.60

 EF95
 0.65

 EF32
 1.50

 EF33
 0.80

 EF184
 0.80

 EF184
 0.80

 EF184
 0.80

 EF184
 0.80
 EZ81 GM4 0.70 0.70 5246T 0.70 6730L2 0.85 6A87 0.70 6AC7 1.30 6AC5 1.30 6AC5 1.30 6AK5 0.95 6AK5 0.95 6AK5 0.95 6AK5 0.95 6AK5 0.95 6AK5 0.95 6AM5 0.95 6AM5 0.90 6AM5 0.90 6AM5 0.90 6A05 0.9 5.90 GY501 GZ32 GZ33 GZ34 GZ37 1.30 1.05 4.20 2.75 3.95 10.95 UBF89 10.50 12J5GT 12K7GT 0.55 0.70 UCC84 UCC85 UCF80 12.50 6GA8 6GH8A 6H6 1.95 1.95 1.60 12K8GT 12Q7GT 12SC7 12SC7 0.80 0.60 0.65 UCH42 1.15 6H6 0.65 6JU6 0.60 6J4 0.60 6J4 0.85 6J5 4.20 6J5GT 1.50 5J6 2.50 6J6W 3.40 5FH8 1.00 5K7 KT66 KT88 UCH81 5.85 10.95 UCH81 18.40 UCL82 2.80 UF41 2.80 UF80 9.90 UF85 0.70 UL84 0.80 UM180 0.95 UM84 0.95 UM84 0.96 UY82 1.35 2.00 2.30 0.90 0.65 0.90 17.80 0.80 4.85 4.85 12SJ7 0,70 ML4 ML6 N78 OA2 OB2 12507 1.45 0.85 4.20 1.50 2.50 3.40 1.00 1.80 1.15 12S07GT 12Y4 0.85 0.70 2.80 0.90 0.85 11.50 8.50 39.55 13D3 13D5 19AQ5 PCL82 PCL84 SK7 SJE6C SJS6C 18G3 PCL84 0.90 PCL86 0.75 PCL805/85 0.95 PD500/510 4.30 PFL200 1.10 0.85 1.25 1.35 0.95 1.70 UY85 VR105/30 19G6 19H5 85 0.95 VR105/30 10 4.30 VR150/30 1.10 X66 2.80 X61M 1.10 Z759 0.85 Z749 0.70 Z800U 0.60 Z801U 0.95 Z803U 1.00 Z803U 6AS6 6AU6 6AV6 6AX4GT 6AX5GT 6BA6 0.90 6KD6 6L6GC 6L6GT 4.50 2.80 2001 0.80 2001 2001 20091 25L6GT 25Z4G 35W4 1.30 0.65 0.95 0.75 0.80 3.70 PL36 PL36 PL81 PL82 PL83 PL84 PL504 PL508 PL509 PL509 PL509 PL519 PL502(SE) PY80 PY81/800 19.00 1.30 1.80 0.75 3.45 3.75 6L18 6LD20 0.70 0.70 1.30 1.80 1.50 1.50 1.40 0.65 2749 0.70 Z800U 0.60 Z801U 0.95 Z803U 1.00 Z900T 2.40 1A3 807G 6SA7 6SG7 6SJ7 1 40 0 70/1 20 + 85A2 6BE60.60/1.20 + 6BG6G 1.60 16.00 255 * 807 813 2.55 * 1.60/2.40 * 19.32 69.50 * 2.45 6BG6 1.40 6BJ6 1.60 2.40 0.50 6807A 0.80 68R7 0.45 68W6 0.45 68W6 0.45 68W6 0.45 66W7 0.45 6C4 0.80 6C5 0.70 6CW4 2.40 6CX8 2.50 6CL6 0.70 6CW4 2.40 6CX8 19.50 6F6 19.00 6F6GB 0.60 6F7 18.25 6F48 0.50 6BO7A 0.85 6SK7 1L4 1R5 1S4 1S5 1T4 1U4 5.80 5.80 2.95 0.70 4.80 6.20 1.80 0.50 0.55 6SR7 6SL7GT 6SN7GT 6SQ7 6V6G 4.60 0.85 0.80 0.95 1.50 0.95 0.95 8298 24 00 832A 866A 86SE 931A 954 8.90 3.80 6.25 19.80 1.20 1.20 1.20 1.20 1.20 5.30 5.80 6.80 0.65 1T4 0.65 1U4 0.60 1X2B 2.10 2X2A 3.20 3A4 7.50 3AT2 3B28 PY81/800 EL86 EL90 EL91 EL95 EL504 EL509 EL509 EL519 EL821 0.95 1.00 PY82 PY88 8.20 6V6GT 6.50 8.20 6V6G1 2.75 6X4 8.50 6X5GT 3.80 6Y6G 1.15 6Z4 0.70 9D6 1.60 11E2 1.10 12A6 2.80 12ATE 0.80 1.70 3.95 PY500A 955 955 956 5763 6060 6080 6146 6146B 6380 21.50 00V03/10 7.50* 00V03-20A 21.50 0.55 0.65 0.90 0.70 2.90 19.50 1.00 6.90 8.20 9D6 11E2 12A6 12AT6 00V03-25A 300 36.50 3E29 354 EL822 ELL80(SE) 9.95 280 0.85 00V06/40A 2.80 0.70 6360 2.85 EM87 19.50/36.50* 4B32 18.25 6FH8 17.80 12AT7 0.85 6550 8.05 VALVES AND TRANSISTORS Telephone enquiries for valves, transistors, etc. Retail 7493934, trade and export 743 0899. PRICES MAY VARY. POSTAGE: £1-£3 45p; £3-£5 55p; £5-£10 60p; £10-£15 80p; £15-£20 100p. Same day despatch.

COLOMOR (ELECTRONICS LTD.) 170 Goldhawk Rd, London W12 Tel: 01-743 0899 or 01-749 3934. Open Monday to Friday 9 a.m.5.30 p.m.

SPECIAL PRICES ON SURPLUS EQUIPMENT

Racal RA17 receivers, high grade communications receivers, 500kHz/ 30MHz in 30 effective bands from £175.00. Eddystone receiver 730/4, 500kHz/30MHz in 5 bands £145.00. All in excellent condition. Carriage £15.00. Sanyo RP8880 9 bands portable communications receivers £125.00. Pye Westminster W15 low band AM £30.00, p&p £2.50. 27ft telescopic mast with guys, insulator etc £25.00 collected. High Impedence headphones with book mic, new £7.50. Avo valve testers £35.00, p&p £4.00. New 28 range digital multimeters £40.25. PCR receivers, LW/MW/ SW, untested less PSU £20.00, p&p £5.00. 10ft whip aerials £4.00, p&p £1.50. Creed teleprinters £25.00. Various single and double beam oscilloscopes, signal generators, valve testers, output meters etc always in stock. Surplus circuit book containing circuits and notes on many surplus receivers, transceivers etc £7.50. Send 50p for illustrated catalogue, includes £1 voucher. Over 500 sets in stock. Avo's amateur rigs wanted for cash. New shop open at 218 St Albans Rd. Come and see the bargains!

WEIRMEAD LTD, 218 St Albans Road, Watford, Herts. 0923 49456 Access/Visa Welcome

G W MORSE KEYS 4 Owen Close, Rhyl, Clwyd, Wales LL18 2LQ THE GW MORSE KEY A joy to use and to look at, this key is made from solid brass polished and mounted on a slate base, here in GW land (not JA) Mounting the key on slate stops all movement of the key when in use. £34.50 pp £2.00 each. 24 HR LCD CLOCK Clear ¹/₂ high lcd readout repeat alarm clock, battery powered (2 AA pencells). No R/F problems known. Complete with batteries £9.50 pp £0.50 each. **GW HIP PRODUCTS** The full range of Gwhips always in stock for quick and prompt delivery or collection.

| MEW | NEW BASE STATION ANTENNA FROM | NEW |
|-----|-------------------------------|-----|
| NEW | GWHIP PRODUCTS | NEW |
| NEW | NOW AVAILABLE | NEW |

For full information and price list please send SAE BRASS CALL PLATE

Your callsign engraved on a brass plate for fixing to the GW morse key or any of your radio equipment. £1.00 only. NO POST & PACKING CHARGE FOR ORDERS OVER £50.00



MENTION PRACTICAL WIRELESS WHEN REPLYING TO ADVERTISEMENTS

Published on approximately the 7th of each month by IPC Magazines Limited, Westover House, West Quay Road, Poole, Dorset BH15 1JG. Printed in England by Chapel River Press, Andover, Hants, Sole Agents for Australia and New Zealand – Gordon and Gotch (Asia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions INLAND £13 and OVERSEAS £14 payable to IPC Magazines Ltd., "Practical Wireless" Subscription Department, Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

PW

EG. WARD & CO. LTD. WESTERN PARADE, WEST STREET, AXMINSTER, DEVON, EX13 5NY.

THE SOUTH-WEST'S LARGEST

| ×. | — Trio — | |
|--------------------------------|--|--------------------------------|
| T\$930\$ | 9 Band TX General Cov RX | 1195.00 () |
| | 160-10m Transceiver 9 Bands | 758.00 () |
| | All Band ATU/Power Meter | 143.91 (2.00) |
| | External Speaker Unit 160m-10m Transceiver | 42.09 (1.50) 669.61 () |
| | 160m-10m Transceiver | 669.61 () 779.55 () |
| | Matching Power Supply | 119.43 (3.00) |
| | Matching Speaker | 30.99 (1.50) |
| | Mobile Mounting Bracket | 12.00 (1.50) |
| | FM Board for TS430 8 Band 200W Pep Transceiver | 36.48 (1.00) 576.66 () |
| | Base Station External Speaker | 576.66 () 27.99 (1.50) |
| | 100W Antenna Tuner | 98.95 (1.50) |
| MC50 | Dual Impedance Desk Microphone | 32.98 (1.50) |
| | Fist Microphone 50K ohm IMP | 15.49 (0.75) |
| | HF Low Pass Filter 1kW | 22.49 (1.00) |
| | 2M FM Mobile 2M Multimode | 323.30 () 458.72 () |
| | 2M/70cm mobile | 458.72 (—) 488.70 (—) |
| | 2M 25W mobile | 279.00 () |
| | 7cms FM 12W | 310.32 () |
| | 2M FM Synthesised Handheld | 243.36 () |
| | 70cm Handheld | 265.85 () |
| TR2600 | New 2M FM Synthesised Handheld | P.O.A. () |
| ST2 SC4 | Base Stand Soft Case | 54.98 (1.50) |
| | Son Case Speaker Mike | 14.49 (0.50) 17.00 (1.00) |
| | Spare Battery Pack | 26.50 (1.00) |
| MS1 | Mobile Stand | 33.91 (1.00) |
| R600 | Gen. Cov. Receiver | 272.83 () |
| | Synthesiser 200KHz-30MHz Receiver | 436.75 () |
| HC10 | Digital Station World Time Clock | 71.96 (1.50) |
| HS5 | Deluxe Headphones Mobile External Speaker | 24.48 (1.00) |
| SP40 | | 14.98 (1.00) |
| - | - Linear Amps — | |
| TONO (G serie | s) | |
| 2M40G 2m, | I-3 W in, 20-35W out, preamp | 79,00 (2.00) |
| | I0-15W in, 70-90W out, preamp | 115.00 (2.00) |
| | 10-15W in, 110-130W out, preamp | 159.00 (2.50) |
| 4M70G 70 cr | ns, 3-15W in, 40-60W out, preamp | 179.00 (2.00) |
| MICROWAVE | MODULES | |
| MML144/30-LS | | 75.00 (2.00) |
| MML144/50-S | inc preamp, switchable | 92.00 (2.00) |
| ML144/100-S | inc preamp (10w i/p) | 149.95 (2.50) |
| MML144/100-H | | 149.95 (2.50) |
| MML144/100-L MML432/30L | | 169.95 (2.50) 139.95 (2.00) |
| MML432/50 | inc preamp (1/3w i/p) inc preamp (10w i/p) | 129.95 (2.00) |
| MML432/100 | linear (10w i/p) | 245.00 (2.50) |
| B.N.O.S. | | |
| LPM 144-1-100 | 2m, 1W in, 100W out, preamp | 172.50 (2.50) |
| LPM 144-3-100 | 2m, 3W in, 100W out, preamp | 172.50 (2.50) |
| LPM 144-10-100 | 2m, 10W in, 100W out, preamp | 149.50 (2.50) |
| LPM 144-25-160 | | 207.00 (2.50) |
| LPM 144-3-180 | 2m, 3W in, 180W out, preamp | 235.75 (2.50) |
| LPM 144-10-180 LPM 432-1-50 | | 235.75 (2.50) |
| LPM 432-1-50 LPM 432-3-50 | 70cm, 1W in, 50W out, preamp 70cm, 3W in, 50W out, preamp | 184.00 (2.50) 184.00 (2.50) |
| LPM 432-10-50 | 70cm, 10W in, 50W out, preamp | 155.25 (2.50) |
| | WR/PWR Meters | s — |
| HANSEN | | |
| FS200 | 1.8-150MHz 20/200 Pep | 55.95 (1.00) |
| FS210 | 1.8-150MHz 20/200 Auto SWR | 59.80 (1.00) |
| FS5E FS500H | 3.5-150MHz 20/200/1000W HF | 41.00 (1.00) |
| FS710H | 1.8-80MHz 20/200/2000W Pep 1.8-60MHz 15/150/1500W Pep | 77.80 (1.00) |
| WELZ | | 97.75 (1.00) |
| SP15 | 1.8-160MHz PWR/SWR | 41.00 (1.00) |
| SP45 | 130-470MHz PWR/SWR | 59.75 (1.00) |
| SP10X | 1.8-150MHz PWR/SWR | 28.75 (1.00) |
| SP200 | 1.8-160MHz PWR/SWR | 82.00 (1.00) |
| SP250 SP300 | 1.8-60MHz PWR/SWR | 57.75 (1.00) |
| SP300 SP350 | 1.8-500MHz PWR/SWR 1.8-500MHz PWR/SWR | 115.00 (1.00) 69.95 (1.00) |
| SP400 | 130-500MHz PWR/SWR | 82.00 (1.00) |
| SP600 | 1.8-500MHz PWR/SWR | 106.00 (1.00) |
| τογο | | |
| T430 | 144 /422 120 14/ | 44 EE (1 00) |

144/432 120 W

144/432 200 W

HQ1 MINI BEAM 10 - 15 - 20

ONLY £169.00 (4.00)

1.8 60MHz

1.8 60MHz

T430 T435

YAESU

YS200 YS2000

| VUN | , EA IS SINT. | |
|------------------------|---|--|
| AMATEL | JR RADIO STOCKIST | |
| _ | - Icom Products - | |
| IC751 | HF Transceiver | 1099.00 () |
| IC745 | HF Transceiver | 839.00 () |
| IC730 | Mobile HF Transceiver P.S. Unit | 659.00 () 119.00 (4.00) |
| PS15 PS30 | Systems p.s.u. 25A | 229.00 () |
| SM6 | Base microphone for 751/745 | 34.50 (1.00) |
| IC290D | 2m 25w M/Mode | 499.00 () |
| IC271E | 2m 25w M/Mode Base Stn. | 649.00 () |
| IC271H | 100W version of above | P.O.A. () 359.00 () |
| IC25H IC27E | 2m 45w FM 25W FM mobile | 359.00 () 319.00 () |
| IC45E | 70c 10w FM | 345.00 () |
| ICBU1 | B/U Supply for 25/45/290 | 24.50 (1.00) |
| ICR70 | General Coverage Receiver | 565.00 () |
| ICR71 | General Coverage Receiver | 649.00 () |
| IC02E | 2m H/Held | 239.00 () |
| IC2E ML1 | 2m H/Held 2m 10w Linear | 179.00 () 69.00 (2.00) |
| IC4E | 70cm H/Held | 229.00 () |
| BC30 | Base Charger | 56.35 () |
| HM9 | Speaker mic | 16.50 (0.75) |
| IC3 | Carry Case | 5.00 (0.75) |
| ICBP3 | Std Battery Pack | 25.00 (0.75) |
| BP5 CP1 | High Power Battery Pack Car Charging Lead | 48.00 (0.75) 4.95 (0.75) |
| DC1 | 12v Adaptor | 12.50 (0.75) |
| | - Mutek Products | |
| SLNA 50 | 50MHz Switched preamp | 44.90 (1.20) |
| SLNA 144s | 144MHz Low noise switched preamp | |
| SLNA 145sb | Preamp intended for 290 | 27.40 (1.20) |
| GLNA 432e | 70cm Mast head preamp | 149.90 (2.50) |
| RPCB 144ub | Front end FT221/225 | 74.90 (1.20) |
| RPCB 251ub | Front end IC251/211 | 79.90 (1.20) |
| BBA 500u GFBA 144e | 20-5000MHz Preamp 2m Mast head preamp | 32.90 (1.20) 139.90 (2.50) |
| SBLA 144e | 2m Mast head preamp | 89.90 (2.50) |
| RPCB 271ub | | 89.90 (1.20) |
| TVHF 230c | 2M-FM Transverter | 334.90 (5.00) |
| 2 | Datong Products | |
| PC1 | Gen. Cov. Con. | 137.40 (1.00) |
| VLF | Very low frequency conv. | 29.90 (1.00) |
| FL2 FL3 | Multi-mode audio filter Audio filter for receivers | 89.70 (1.00) 129.00 (1.00) |
| ASP/B | r.f. speech clipper for Trio | 82.80 (1.00) |
| ASP/A | r.f. speech clipper for Yaesu | 82.80 (1.00) |
| ASP | As above with 8 pin conn | 89.70 (1.00) |
| D75 | Manual RF speech clipper | 56.35 (1.00) |
| D70 MK | Morse Tutor Keyboard morse sender | 56.35 (1.00) 137.40 (1.00) |
| REA | RF switched pre-amp | 33.90 (1.00) |
| AD270-MPU | Active dipole with mains p.s.u. | 51.75 (2.00) |
| AD370-MPU | Active dipole with mains p.s.u. | 69.00 (2.00) |
| MPU | Mains power unit | 6.90 (1.00) |
| DC144/28 PTS1 | 2m converter Tone squelch unit | 39.67 (1.00) 46.00 (1.00) |
| ANF | Automatic notch filter | 67.85 (1.00) |
| SRB2 | Auto Woodpecker blanker | 86.25 (1.00) |
| <u> </u> | W/RTTY Equipme | nt — |
| Tono 9000E Tono 550 | Reader/Sender Reader | P.O.A. () 299.00 (2.50) |
| MICROWAVE | | |
| MM2001 | RTTY to TV converter | 189.00 (1.25) |
| MM4001 | RTTY terminal | 269.00 (1.25) |
| MM4001KB | RTTY term with keyboard | 299.00 (2.00) |
| HI-MOUND N | | |
| HK702 | Up down keyer marble base | 27.00 (1.00) |
| HK703 HK704 | Up down keyer Up down keyer | 28.15 (1.00) 19.25 (1.00) |
| HK705 | Up down keyer | 13.57 (1.00) |
| HK706 | Up down keyer | 15.90 (1.00) |
| HK708 | Up down keyer | 13.00 (1.00) |
| HK802 | Up down solid brass | 82.85 (1.00) |
| HK808 MK704 | Up down keyer Twin paddle keyer | 39.95 (1.00) 12.00 (1.00) |
| MK705 | Twin paddle keyer marble base | 24.65 (1.00) |
| KENIDDO | | C129002000000000000000000000000000000000 |

Yaesu . FT1 HE Transc P.O.A (-) 1329.00 (--) 61.55 (2.00) HF Transceiver FT980 SP980 Speaker 719.00 (--) 185.00 (2.00) FT102 HF Transceive FC102 Tuner FV102DM VEO 239 00 (2 00) 55.00 (2.00) SP102 Speaker AM/FM Linit 49.00 (1.00) Mobile HF Transceiver FT77 479.00 145.00 (5.00) FP700 PSU FC700 Tuner 103.85 (2.00) FT77s 10w. version 449.00 (-) FMU77 FM Board for FT77 28.55 (1.00) FT757 **HF** Transceiver 719.00 (--) 245.00 (2.00) FC757 Auto A.T.U. Heavy Duty PSU Switched Mode PSU FP757HD 179.00 (2.00) FP757GX 145.00 (2.00) FT480 2m M/Mode Transceiver 399.00 (--) Linear Amplifier 2m M/Mode Port/Transceiver FL2050 119.00 (2.00) 279.00 FT290 (-) (-) FT290 With Mutek front end fitted 309 00 FL2010 66.55 (1.00) Linear Amplifier 70cm M/Mode Port/Transceiver FT790 259.00 4 MMB11 Mobile Bracket 28.19 (1.00) 10.55 (0.75) NC11 Charger CSC1 YHA15 Carrying Case 2m Helical 4.45 (0.75) 5.65 (0.75) YHA44D YM49 70cm Jwave 9.00 (0.75) Speaker Mike 19.25 (1.00) FT230 2m 25w FM 269.00 (--) 239.00 FT730 70cm 10w. FM 14.65 (1.00) P.O.A. (--) P.O.A. (--) MMB15 Mobile Bracket FT203 NEW 2m H/Held FT209 NEW 2m H/Held FT208 2m H/Held 209.00 (--) (--) FT708 70cm H/Held 189.00 8.45 (0.75) MMB10 Mobile Bracket NC9C Charger 9.20 (0.75) NC8 PA3 56.75 (2.00) 16.00 (0.75) Base/station Charger Car Adaptor/Charger FNB2 Spare Battery Pack 23.00 (0.75) YM24A Speaker Mike 22.50 (1.00) FT7268 2m Base Station 775.00 1-1 430/726 70cm Module for above 259.00 (2.50) (-) FRG7700 HF Receiver 15-30MHz 385.00 455.00 FRG7700M As above with memory FRT7700 A.T.U. for above 48.25 (1.00) MH1B8 Hand 600 8pin mic 15.70 (1.00) MD1B8 Desk 600 8pin mic 56.00 (1.00) MF1A3B 18.95 (1.00) Boom mobile mic YH77 Lightweight phones 12.50 (0.75) Padded phones L/weight Mobile H/set-Boom mic YH55 12.50 (0.75) YH1 15.75 (0.75) SB1 PTT Switch Box 208/708 17 00 (0 75) PTT Switch Box 290/790 14.50 (0.75) SR QTR24D 35.00 (0.75) World Time Clock FF501DX Low Pass Filter 28.99 (0.75) YP150 Wattmeter/Dummy Load 150w 99.00 (1.00) Power Supplies -BNOS DRAE 52.90 (2%0) 95.45 (3.00) 138.00 (4.00) 4 amp 6 amp 34.00 (2.00) 6 amp 53.50 (2.50) 79.50 (3.00) 12 amp 12 amp 25 amp 24 amp 110.00 (4.00) 40 amp 276.00 (4.00) Aerial Rotators -57.50 (2.00) 98.90 (2.00) 99.94 (2.50) 3 core Lighter Duty 5 core Medium Duty 9502B **AR40** KR400 Med/H Duty KR500 KR400RC 6 core Elevation 6 core Medium Duty 126.50 (2.50) 118.45 (2.50) **CD45** 8 core Heavy Duty 149.50 (2.50) KR600RC HAM1V 8 core Heavy Duty 167.90 (3.00) 264.50 (4.00) 8 core Heavier Duty 8 core Very Heavy Duty T2X 332.35 (4.00) - Switches -Sigma 2 way SO239 11.50 (0.75) Sigma Welz 2 way 'n' Skts 2 way SO239 15.50 (0.75) 20.75 (0.75) Welz 2 way 'n' Skts 37.00 (0.75) Drae way SO239 15.40 (0.75) Miscellaneous DRÁE 27.50 (1.00) Wavemeter 30W Dummy load 100W Dummy load 200W Dummy load 7.10 (0.50) 28.00 (1.00) 41.40 (1.50) 58.00 (2.00) T30 T100 T200 CT300 300W Dummy load 2m Pre-set A.T.V. Altai Dip Meter DRAE 11.80 (1.50) 49.00 (1.00) AERIALS BY:- JAYBEAM -HYGAIN - G. WHIP - TET -MINIBEAM - USUALLY IN STOCK (Tel: 0297-34918) FDK OPEN MON-FRIDAY 9:00-5:30. SATURDAY 9:00-5:00 WED. 9:00-1:00 (closed for lunch 1:00-2:00) STOCK ITEMS NORMALLY DESPATCHED WITHIN 48 HOURS **RODNEY G6LUJ**

-

Delivery prices shown in brackets

Squeeze CMOS 230/13.8v

....

Memory 4096 Multi Channel

ICOM

79.50 (2.00)

Mail/Telephone order by Cheque or Credit Card. Cheques cleared before goods despatched.

169.50 (2.50

KENPRO

REG G2BSW

Instant credit

KP 100

KP200

44.65 (1.00)

49.35 (1.00)

52.90 (1.00)

69.79 (1.00)

IUNDREDS OF NEW LINES

The amazing Maplin Catalogue is here again! The new edition is packed with hundreds and hundreds of new electronic components to bring you right up to date with all the latest developments. As all home constructors agree (and a good many professionals too) the Maplin Catalogue is the one essential piece of equipment they really need. And now with all our **prices on the page** the Maplin Catalogue is better value than ever.

On Sale From 10th November 1984.

Pick up a copy as soon as it's published at any branch of W.H. Smith or in one of our shops. The price is still just £1.35, or £1.75 by post from our Rayleigh address (quote CA02C).

Post this coupon now for your copy of the 1985 catalogue. Price $\pounds 1.35 + 40p$ post and packing. If you live outside the U.K. send $\pounds 2.40$ or 11 International Reply Coupons. I enclose $\pounds 1.75$.

Name

Address

... PW11/84



Maplin Electronic Supplies Ltd. Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911. •Shops at:159-161 King Street, Hammersmith, London W6. Tel: 01-748 0926. •8 Oxford Road, Manchester. Tel: 061-236 0281. •Lynton Square, Perry Barr, Birmingham. Tel: 021-356 7292. •282-284 London Road, Westcliff-on-Sea, Essex. Tel: 0702-554000. •46-48 Bevois Valley Road, Southampton. Tel: 0703-25831. All shops closed all day Monday.

presented FREE with Willeless

AUT 84



comment

A Healthy Interest

Apologies for keeping you on tenterhooks for the second issue of Computing in Radio. An industrial dispute within IPC Magazines made it impossible to meet the schedule necessary for inclusion inside the October issue of Practical Wireless. Still it does mean that the next issue of CiR will come that much quicker, as you will now only

have to wait until the January issue of PW.

There can be no doubt that you like the format of CiR from the favourable comments we have received. The almost embarrassing flow of programs for review or publication indicates a healthy interest in this side of amateur radio. If you have written a program which you think could be of

interest to other radio amateurs, please let us know. We are also interested in what the smaller manufacturers and professional software writers are doing-remember, if you don't tell us of your latest product or program, we cannot tell our readers. Better still, send a sample, kit or program for review-don't wait to be asked. G8VFH



The British Amateur Radio Teleprinter Group (BARTG) have produced a version of the ST5 RTTY terminal unit especially for use with computers. Previously, the amateur wanting to use an ST5 t.u. with his computer had to drastically modify the p.c.b. to remove a lot of unwanted components, and then add the necessary t.t.l. drivers. Now, the transmit and receive sides are on the one p.c.b. and the power supply required is just +5V. Complete kits are available at £74.50 for non-members. Members save £7 on this price, so even if you are not yet a member of BARTG you could join before you buy a kit and still be £2 in pocket! For membership, just send £5, together with your name, address and callsign, if you are licensed, to John Beedie G6MOK, 161 Tudor Road, Hayes, Middlesex UB3 2Q.G.

In the Software reviews in the Summer issue of CiR we managed to get the wrong address for Softricks. To order or find out more about the Softricks Morse Tutor program for the 48K Spectrum, contact R. Gierelo, 1 Rowan Place, Dundee DD3 0PH. Tel: Dundee 88232.

Scarab Systems are now marketing a SSTV system, receive only, for the popular 48K Spectrum. Audio from your receiver are input into the Spectrum's EAR socket and the computer decodes them to display the final SSTV picture on the TV connected to the computer.

The program, on cassette, costs £15 inclusive of postage and VAT and is available from Scarab Systems, 39 Stafford Street, Gillingham, Kent, ME7 5EN who will be only too pleased to provide you with details of this and other programs.

The next issue of Computing in Radio will be presented free with the January 1985 issue of Practical Wireless on sale the first Friday in December 1984. To ensure your copy why not place a regular order with your local newsagent or take out a subscription.

Following on from the news in the Summer issue of CiR we have now received a printed price list of programs, accessories and spares for the Jupiter ACE computer. Of most interest to the radio amateur is the fact that as well as a wide range of hardware most spare parts can be obtained including partly built and bare circuit boards and the ACE FORTH ROM chip. An s.a.e. to Boldfield Limited Computing, Sussex House, Hobson Street, Cambridge, CB1 1NJ will bring you full details. Boldfield have promised for the future a controller for $5\frac{1}{4}$ inch disk drives, a colour card and printer interfaces, as well as some interesting software.

Richard Wilmott GW3RRI is now selling his computer software under the Technical Software label. His address is still Fron, Upper Llandwrog, Caernarfon, Gwynedd LL54 7RF. Tel: 0286 881886.

The rumours currently going the rounds that Sinclair have stopped production of the ZX81 are completely without foundation. We contacted Sinclair Research who told us that the ZX81 was still going strong and selling well particularly in overseas markets where computing was just getting going.

We also asked about the supposed differences between Issue 3 Spectrums and previous models regarding the loading of programs from tape. As far as they know there are no differences in loading any model of Spectrum from cassette.

COPYRIGHT C IPC Magazines 1984. Copyright in all drawings and articles published in Computing in Radio is fully protected and reproduction in whole or in part is ex-pressly forbidden. All reasonable precautions are taken by Computing in Radio to ensure that the advice and data given to our readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

Advertisement

Advertisemen

No. 1 in Bromley

As official Acorn Dealers we have high standards to maintain. We offer friendly, professional advice and service, and stock a full range of hardware and software.

> For the best service in Bromley come to the



GROSVENOR SOFTWARE (G4BMK)

AMTOR Dragon 32/64. Superb stand-alone program. FEC ARQ and Listen Modes. Type ahead, QSO review etc. Requires conventional RTTY terminal unit plus a clock/PTT board (see below). Cartridge £49. Addition to RTTY/CW Cart £44. Tape £39. Receive only £24.

RTTY Superb split screen type ahead programs for VIC20, CBM64, ATOM, DRAGON. Any band rate, saveable memories, QSO review etc.

MORSE and BASICODE converters for Dragon.

PNP COMMUNICATIONS — QUALITY TERMINAL UNITS RTTY: Dual filters + PLL: Kit £32.50, Assembled £41.50, Boxed £63.25. MORSE INTERFACE: KIT £13.20, ASSEMBLED £20.12. AMTOR CLOCK/PTT switching unit: Boxed £22.40, available assembled without box.

SAE for details. State computer and call sign (if any) 22 GROSVENOR ROAD, SEAFORD, EAST SUSSEX. Tel: (0323) 893378

hardware

Power Cleaning Plug

The mains supply is a constant source of worry for the computer user. Spikes and other noise on the mains may cause the computer to crash. The B&R Power Cleaner is a 13A mains plug with built-in filtering to clean up the supply. Recommended retail price is £13.46 inc. VAT. B&R Relays Ltd., South Road, Temple Fields, Harlow,





Adva

RTTY and CW TRANSCEIVE with NO TERMINAL UNIT

This fantastic program interfaces direct with your rig. Split screen, type ahead, 26 memories and much, much more. Tape and components for the very simple interface for only £17.50. For CBM64. BBC-B and VIC20 versions coming. CW-only version for SPECTRUM £10.

And three very popular programs for CBM64, VIC20, BBC-B, SPECTRUM, ZX81-16k RAE MATHS TUTOR This program gives you all the practice and testing you need to become perfect in this vital part of the RAE. Tape and comprehensive reference sheet detailing all you need to know for only £8. VIC20 needs expansion. Don't let maths make you fail. PASS with this program.

MORSE TUTOR Britain's best. Learn fast in easy stages from absolute beginner to over 40 wpm. Join the hundreds who have succeeded with this program. Tape and full learning guide for only £6.

LOCATOR Enter QTH or Universal (Maidenhead) locator or lat & long of anywhere in the world and get distance, beam and return headings, long path details, VHF contest points and totals. Converts between locator and lat & long. Not available for ZX81.

All programs are menu-driven, very easy to use, and come with full instructions. Prices include p&p 1st Class by return. Add £1 per tape if outside UK or Ireland.

technical software

Fron, Upper Llandwrog, Caernarfon, Gwynedd LL54 7RF. Tel. 0286 881886

DRAGON, BBC, SPECTRUM DEALERS

| BBC B Computer 1.2.O.S £399.00 | R.T.T.Y. Circuit Board including |
|--|---|
| 1.2 ROM£8.00 | instructions£7.00 |
| Graphics Rom£33.00 | R.T.T.Y. Eprom Version£20.00 |
| Microvitec Monitor £228.00 | BBC/Slow Scan Program & Board £17.50 |
| Sanyo Green Monitors£97.00 | Computer Dust Covers£3.00 |
| Disc Drives from £150.00 | Cannon 1080A Printer (inc. Cable) £350.00 |
| Joysticks (Pair)£17.90 | CP80 Printer (inc. Cable) £230.00 |
| Wordwise Word Processor£39.00 | Printer Cable (BBC or Dragon 32) .£12.90 |
| Acorn Electron £199.00 | Dragon 32 Disc Drive |
| All connectors, plugs and sockets for BBC, | (inc. Controller) £275.00 |
| ribbon cable, discs C.20, C.15, C.12, | Joysticks (pair)£14.90 |
| cassettes etc. in stock. | ZX Spectrum 48K £129.00 |
| Centronics Printer Cable (BBC & | Memotech 512 £325.00 |
| Dragon)£12.90 | New tatung einsten computer. Send for |
| R.T.T.Y. Program for BBC.B£7.50 | leaflet£4.99 |
| | |

R.T.T.Y. Program for BBC.B£7.50 leaflet

DRAGON SERVICE CENTRE

Full service and repair facility – spare parts in stock Wide range of software for BBC, Dragon 32, ZX Spectrum etc. Please send SAE for full list. Post and package on small items £4. All available mail order. Access and Visa. 24 hour phone. All prices (include VAT at 15%). Goods in stock by return of post.

S P ELECTRONICS 48 Linby Road, Hucknall, Notts NG15 7TS. TEL: Notts (0602) 640377.

SSTV on the BBC-B



Believed to be the first SSTV program for the BBC-B, G3LIV and G8UEE are producing a package enabling the SSTV enthusiast or newcomer to display SSTV signals on a TV or monitor using the BBC.

If the sample photographs of a TV display sent to us with the review kit are anything to go by, then when we have completed tests on this piece of equipment, we should be well pleased. A full review will follow in a future issue of Computing in Radio.

Program, p.c.b. and full construction details cost £17.50 inclusive, while a complete and tested terminal ready to use with program will set you back £95.

For full technical details send an s.a.e. to J. Melvin G3LIV, 2 Salters Court, Gosforth, Newcastle, Tyne and Wear. Tel: 0632 843028.



Sure! More than 10 tasks simultaneously and, in some cases, up to 300 times faster! That's what replacing the basic ROM with the new FORTH does for the ZX81-and more!

The brains behind the breakthrough belong to David Husband, and he's building Skywave Software on the strength of it. Already orders are flooding in and it's easy to see why

The ZX81-FORTH ROM gives you a totally new system. In addition to multi-tasking and split screen window capability, you can also edit a program while three or four others are executing, schedule tasks to run from 50 times a second to once a year, and with a further modification switch between FORTH and BASIC

Return of post subject to availability.

The ZX81-FORTH ROM gives you a normal keyboard with a 64 character buffer and repeat, it supports the 16k, 32k, 64k RAM packs, it is fig-FORTH compatible and it supports the ZX printer.

The price, too, is almost unbelievable. As a "fit it yourself Eprom", complete with manual, it's just £25+VAT.

Add £2 p&p UK (£5 Europe, £10 outside Europe) and send your order to the address below



73 Curzon Road, Bournemouth, BH1 4PW, ENGLAND. Tel: (0202) 302385 International +44 202 302385.

Amstrad CPC 464 64K Colour Computer

Computers come and go at an alarming rate these days, each one claiming to be the best thing since sliced bread.

reviewy

When, over 12 months ago, we were told that a well-known company was going to launch into the home computer market with a computer that would see off every other model available, we politely said that we would be interested when it was a reality. So when Amstrad announced that it was launching its range of computers it came as little surprise, other than the name of the company. Amstrad are well known for their radio products, but the computer market is totally new to them. Even more surprising is the speed with which the range has been developed-well under the year, including a complete re-think and redesign internally. Still, isn't that just how Sinclair started!

The run-of-the-mill computer magazines will undoubtedly review the CPC 464 range with benchmark tests, comparing the speed of its BASIC with that of other competitors, etc. We, on the other hand, will tell you what it is like as far as the radio amateur is concerned.

The CPC 464 comes in four different packages, and these are so different from any other home computer that it makes comparisons very difficult. The two obvious differences are that the machine has a built-in cassette recorder with no provision for the connection of another recorder. The second is that the monitor comes with the computer and houses the power supply.

Options

The four options centre around the monitor-two models, green screen or colour-and disk drive or no disk drive. The first choice-the monitor-is where the difficulties will lie. If you pick the green screen model to keep the initial buying price as low as possible you save £100 over the colour monitor. Unfortunately, the monitors are not available separately-yet-so that it is not possible to up-grade to a colour monitor. We found, however, that our "monitor," a home-modified Ferguson TX 14 portable colour TV, worked without any changes so if you already have a colour monitor it should plug straight into the CPC 464 video socket. You will have to provide a separate power supply.

The computer itself is well presented and pleasant to use. The keyboard is not quite so sensitive as the BBC's, requiring a distinct smart key depression rather than a light touch, but this does prevent you making entries just by brushing against a key always a bit of a nuisance with the BBC. We particularly liked the enormous ENTER key, it made life so much easier when punching in programs. A secondary number key pad with its own small ENTER key is provided to the right of the main keyboard, with the datacorder on the right of that. The cassette recorder was easy to use and worked every time, although it is not fast by any means—it seemed to be comparable with a Spectrum in terms of loading time. We would have liked to see the cassette inputs and outputs brought out so that two recorders could be used—very useful when developing a long program.

Expansion is catered for by two edge connectors along the rear of the computer. One of the connectors gives access to the built-in parallel printer interface which we used to drive our Tandy CGP-115 Colour Graphic Printer. Here we found a slight problem in that the computer instruction manual tells you to connect the edge connector pin-for-pin with the printer connector. Unfortunately, this is not so in this case, even though the Tandy printer uses a standard connector. Having sat down and worked out, from the information given in the manual, just what the correct connections should be, the Tandy printer worked very well indeed, and offers a low-cost means of obtaining hard-copy both alphanumeric and graphics. It would have been much better if the edge connectors had been scrapped at the start and standard IDC-style connectors fitted.

The second edge connector is used for the disk system which uses the Digital Research CP/M operating system. The version we had for review was not fitted with a disk drive, so we have no experience of this.

In the limited time allowed for the trials with the CPC 464 we tried translating some of our *PW Radio Programs* as well as some of the newer programs. To show some of the differences, the listing for the Crosshatch Generator program is reproduced here. It differs from the BBC-B version (p6) in having a circle generator.

QRM

One of the biggest headaches for the amateur is the QRM generated by most home computers. Not all computers generate worrying amounts of interference and not all models from the same maker exhibit the same interference footprint. We have tried to equate the noise output radiated from the CPC 464 and displayed on our Marconi Spectrum Analyser with possible problems on the amateur bands. We obviously need to develop this idea further for it to be of use, but the tests performed to date would indicate that there should be little problems at 144MHz with most interference being between 30MHz and 90MHz peaking around 54MHz.

The manual provided with the computer was good but omitted a couple of important points. The first is that there is an abbreviation for PRINT. The keyword PRINT can be input by using ?, a useful feature as this is probably the most used keyword. There are no other abbreviated keywords however. The other more serious omission concerns the Trigonometric functions or rather lack of them. For some inexplicable reason TAN. SIN and COS are available but only ATN (Arctan) in the reverse direction. Now I know that the omission of Arccos and Arcsin can be overcome by using some horrendous formulae but it is of no help if these formulae are not readily available. In our case we have a VIC 20 which also suffers from the same deficiencies in trig functions and as the VIC 20 manual's one redeeming point is the listing of the tricks needed to overcome the problem, we referred to this. Just why the designers of a computer imagine that letting you calculate trig functions in one direction only is sufficient I cannot understand.

To sum up then, will the CPC 464 satisfy the needs of the radio amateur? We think it will—it is well made, nice to use with a good display on the colour monitor. The use of edge connectors is penny pinching, particularly in the light of experience with other computers using edge connectors and their general lack of long-term reliability. The computer and monitor stood up to being left switched on for several days without a break and only got warm.

The pricing structure is realistic for what you get—£229 for the bottom of the range system with green screen monitor and £329 with the colour monitor. A disk drive on either system adds a further £200. The difficulties arise when trying to decide whether to spend £329 or whether to spend a little bit more for a BBC–B even though you don't get a colour monitor and a cassette recorder with BBC. In a lot of ways the Amstrad is nicer to actually use than the BBC but the BBC is very well catered for in terms of software specifically written for the radio amateur. *G8VFH*

```
10 REM CROSS HATCH GENERATOR - CPC 464
12 CLS PRINT PRINT PRINT PRINT PRINT
15 PRINT
              CROSS HATCH AND CIRCLE GENE
RATOR PRINT PRINT
16 PRINT
                    by 1.M. Terreli G4JX2
 PRINT PRINT
17 PRINT 'translated for Amstrad CPC464
DV GBUFH
18 PRINT PRINT PRINT PRINT PRINT PRINT.
PRINT
          copyr ght IPC Magazines Ltd. 1
984
19 FOR 1 - 1 TO 2000 NEXT 1-CLS
20 MODE 1
30 LET 11-0
40 FOR 1-1 TO 15
50 MOVE M.O
68 DRAU M. 1827
70 LET M-M-45.6
80 NEXT I
90 LET N=0
100 FOR 1=1 TO 13
110 MOVE 0.N
120 DRAW 1280, N
130 LET N=N+33.2
140 NEXT 1
150 ORIGIN 320,200
160 FOR angle = 1 10 360 STEP 0.25
170 xpoint = 190*COSfangle)
180 ypoint = 190*SIN(angle)
190 PLOT xpoint,vpoint
200 NEKT
210 FOR 2 - 1 TO 1000000 -NEKT 2
220 END
```

Piggy-backing" your ZX81 FORTH ROM

In order to make the most of the series by David Husband on FORTH for the radio amateur you will need to be able to try the various programs and ideas on a computer that will run FORTH. There are several FORTH programs available for different computers and the Jupiter Ace has recently become available again at a greatly reduced price.

Feature

However none of these options will support multi-tasking, the usefulness of which will become obvious as David's series progresses. The simplest and most costeffective way of getting into multi-tasking FORTH is to convert your ZX81 into a two language machine using the ZX81-FORTH ROM as supplied by Skywave Software. The manual which is supplied with the ROM explains how to substitute the ZX81-FORTH ROM for the Sinclair BASIC ROM but this has the disadvantage of only allowing the machine to operate in ZX81-FORTH. By "piggy-backing" the Sinclair BASIC ROM onto the ZX81-FORTH ROM and using a small switch it is possible to select either BASIC or multi-tasking ZX81-FORTH as desired.



A study of the circuit diagram of any piece of computer hardware will reveal that many of the i.c.s used have all but one or two of their pins connected together, the chip required being selected by some form of switching of the appropriate pins. It should be obvious that any number of similar i.c.s such as ROMs can be "piggybacked" with their leads permanently soldered together and only the chip select pins brought out to the switching system.

The drawing (Fig. 1) shows one way of 'piggy-backing" the Sinclair BASIC ROM onto the ZX81-FORTH ROM using a 24 pin d.i.l. socket soldered onto the ZX81-FORTH ROM. This way round saves you from having to solder your Sinclair ROM as it is plugged into the socket. If you do not mind soldering onto the Sinclair ROM you can "piggy-back" the ZX81-FORTH ROM onto the Sinclair ROM and you may need to do this if the ZX81-FORTH ROM is supplied mounted onto a carrier.

Make sure that you use the correct set of pins or sockets on the ZX81 board and on

> Fig. 1: One suggested method of "piggybacking" the two ROMs. The socket can be omitted if you are prepared to solder the two ROMs together

> > Fig. 2: Outline circuit diagram of the 'piggy-backed' ROMs. Note that R28 is already on the p.c.b. and only the pins actually needing connections are shown.

the two ROMs. Skywave Software should be producing a small p.c.b. which will carry both ROMs and plug into the ZX81 board and you may prefer to use this instead.

The chip select pins (20 on the Sinclair ROM and the pin directly under it on the ZX81-FORTH chip) are taken via insulated wires to a small slide switch. Resistor R28 on the ZX81 p.c.b. is lifted from the p.c.b. at the end nearest IC2 and connected via another wire to the centre pin of the slide switch. As the ZX81 will have to be RESET each time you change from FORTH to BASIC, or back again, it pays to fit a RESET button. This can take the form of a push-to-make push-button switch connected between 21A and 4B on the ZX81 edge connector. Pushing the button connects the RESET line to OV, thus resetting the computer without having to resort to pulling out the power plug.

Now you should be able to select either BASIC or FORTH using the slide switch and reset the computer simply by using the push-button switch.



DC

Morse Code Tutor

Technical Software, Fron, Upper Llandwrog, Caernarfon, Gwynedd LL54 7RF. Tel: 0286 881886

Spectrum, ZX81+16K, VIC 20, Commodore 64, Dragon **Black and White** Cassette

The menu gives you 6 choices.

- 1. 7 characters (EISHTMO). All groups will consist of only these characters.
- 2.15 characters (EISHTMOAUVNDBWJ).
- 3. 26 characters-the complete alphabet.
- 4. 10 figures.

5. 36 Mixed. This gives groups of mixed letters and numbers-but no punctuation.

6. Send Entered Text. You input a portion of text e.g. plain language or code groups and the computer will send your text.

At speeds below 12 w.p.m. if you ask for 10 characters to be sent then they are sent by the computer with no spacing after 5 letters i.e. the normal code group length. Above 12 w.p.m. the computer asks how many "words" you would like, the "words" are made up from the number of letters you have chosen and will be of varying length. For example, if you opted for 7 characters (EISHTMO) at 12 w.p.m. with 3 words this could be: SEI MTEEI SHTM

After the computer has sent the required groups of letters you type back in the answer and the computer checks it for you. By pressing ENTER you can have the answer displayed immediately.

Advertisement

PANTLING ELECTRONICS, 77 LEIGHTON ROAD, WING,

LEIGHTON BUZZARD, BEDS. (tel 0296 68 406)

| RI | IY INTERFACES FOR THE COMMODURE COMPUTERS |
|----------|---|
| MODULE 1 | 5v TTL to/from a terminal unit |
| MODULE 2 | With Decoder & Audio Board [Optimised for 1445/1275 mark/ |

| BAUD RATES | space. 170Hz shift] 45,45,50 (75, 110, 135, 150) [higher baud rates only provided for experimentation] |
|------------|---|
| | |

experimentation] CHARACTER CODE CCITT NO. 2 PROGRAM Machine code in ROM (no loading!) FACILITIES FROM THE KEYBOARD INCLUDE: * Baud Rate Change * Automatic Control of the PTT Line * Split Screen Operation (type in your answer whilst still receiving) * Manual change of letters/numbers shift on receive * 26 Pre-Programmed messages (eg by QBF RST QRA Location Equipment etc) * 8 Type Ahead Buffers * Printer routines for CBM printers [not Printer Plotters] * SElective CALling using Printer or Cassette Recorder using Echo Routine * Morse Ident for Class A * DX/Normal letters shift on space * Real Time Clock * Fully Compatable Transmissions to Mechanical Printers * Word Unwrap on Receive

VIC & 64 MODULE 1 TTL £79.95 (BARTG MEMBERS £69.95)

VIC & 64 MODULE 2 £109,95 (BARTG MEMBERS £99.95) ALL UNITS ARE BUILT TO ORDER, DELIVERY AROUND 14/21 DAYS. CASH WITH ORDER PLEASE. SPECIAL "RAYNET" VERSIONS AVAILABLE ON REQUEST.

<u>program</u>

Polar Plotting by B. P. Hainey and Tom Lawless

The usual way of finding out the radiation pattern of an antenna is to construct a scale model which is rotated at about 60 r.p.m. and the signal received from a nearby u.h.f. transmitter displayed on an oscilloscope, after suitable processing.

Using this short program together with your BBC-B computer and a simple interface you can plot the polar diagram of your full-size antenna with the added bonus of also showing up the effects of any nearby objects such as the roof, mast, trees etc.

Interface

The simple d.c. amplifier shown in Fig. 1 is the only additional interfacing needed between your receiver output and the computer. Construction should present no problems—Veroboard can be used here and power supplied by two 6-F22 (PP3) batteries. Set R1 and R3 to mid-position short the input to the amplifier and adjust R1 for OV across C1. Remove the short across the input and connect the input to the S-meter of your receiver and the output of the amplifier to the analogue input of the BBC computer. The OV line of the amplifier is connected to Pin 8 and the output to Pin 12.

The Other Station

Load the program into the computer. It will ask you for the rotation time in seconds of your rotator which you will have to find by actually timing the rotator from one end stop to the other.

You will need another amateur some 4km away to transmit a constant carrier for the time that the antenna is rotating 360 degrees. Adjust the gain of the amplifier (R3) and the power output of the transmiter to obtain the best pattern on the screen. If the transmitted signal is too weak you will not see anything other than the main lobe while too strong a signal will swamp the antenna.

If you have a disk drive or tape recorder then several plots can be made and stored so that comparisons can be made after adjusting the antenna.

Disk or Tape

The set-up can be used in reverse to plot the polar diagram of the other station. Enter the rotation time of the other stations antenna, ask for the antenna to be rotated and start the program. Your antenna should

```
10 REM DISABLE ESCAPE
   20 *FX229,1
   30 *FX4,1
   40 REM DISABLE COPY & EDIT
   50 MODE 1
  60 COLOUR 2
  70 PRINT TAB(13,7) "POLAR PLOTTER"
  80 PRINT TAB(18,10) "by"
  90 PRINT TAB(14,14) "B.P.HAINEY"
  100 PRINT TAB(18,16) "&"
  110 PRINT TAB(14,18) "Tom LAWLESS"
  120 PRINT TAB(4,22) "Copyright 1984 IP
C Magazines Ltd"
  130 PRINT TAB(6,30) "PRESS SPACE BAR T
O CONTINUE"
  140 LET Q$=INKEY$(100)
  150 IF Q$=" " GOTO 170
  160 GOTO 140
  170 CLS:CLG
  180 DIM A(510)
  190 VDL 28,0,2,20,0
  200 CLS
  210 PRINT "INPUT ROTATION"
  220 PRINT "TIME IN SECONDS"
  230 INPUT T
  240 CLS
  250 REM CALC OF DELAY LOOP CONSTANT
  260 W=(T-37.96)/0.3429
  270 PRINT "PRESS RETURN "
  280 PRINT "TO START TEST"
  290 LET Q$=INKEY$(100)
  300 IF Q$=CHR$(&0D) GOTO 320
  310 GOTO 290
  320 REM TAKE IN DATA ROUTINE
  330 CLS:CLG
  340 GCOL0,2
  350 MOUE 640,0:DRAW 640,1024
  360 MOVE 0,510:DRAW 1280,510
  370 GCOL0,2
  380 MOVE 640,510
  390 FOR A=0 TO (2*PI) STEP(2*PI)/504
  400 LET R=ADUAL(3)
```

```
410 R=R*(400/65520)
420 GOSUB 550
430 LET A(INT(A*80))=R
440 NEXT A
450 REM PLOT DEGREE LINES
460 GCOL0,3
470 FOR A=0 TO (2*PI) STEP (2*PI)/36
480 LET R=A(INT(A*80))
490 LET X=R*SIN(A)
500 LET Y=R*COS(A)
510 MOVE 640,510
520 DRAW (X+640), (Y+510)
530 NEXT A
540 GOTO 270
550 REM PLOT DURING INPUT SUBROUTINE
560 LET X=R*SIN(A)
570 LET Y=R*COS(A)
580 FOR D=0 TO W STEP 1:NEXT D
590 DRAW (X+640), (Y+510)
600 RETURN
```

Cross Hatch Generator

by I. M. Terrell

10 REM CROSS HATCH GENERATOR - BBC B 15 REM by I.M. Terrell G4JX2 18 REM copyright IPC Magazines Ltd 1984 19 FOR Y = 1 TO 5000 :NEXT Y:CLS 20 MODE 2 30 LET M=0 40 FOR I=1 TO 15 50 MOVE M,0 60 DRAW M, 1027 70 LET M=M+91 80 NEXT I 90 LET N=0 100 FOR 1=1 TO 13 110 MOVE 0, N 120 DRAW 1280,N 130 LET N=N+85 140 NEXT 1 150 END

point directly at the other station.

A modified program listing can be supplied to allow the tests to be stored on disk or tape. Send an s.a.e. marked "BBC Polar Plotter" to Computing in Radio, Westover House, West Quay Road, Poole, Dorset, **BH15 1JG**

We would like to thank Paisley College of Technology, Electrical and Electronic Engineering Dept for their help and the use of their equipment.

Fig. 1: The circuit of the simple interface amplifier for use with the Polar Plotting program. Construction is simple and can be on Veroboard. The input is taken from the receiver's S-meter while the output is connected to the Analogue Input socket (SK6) of the BBC-B as shown. The positive and negative 9V supplies can be provided by suitable batteries



Morsen Electronics RTTY Terminal Unit

The ZX81 has become a popular computer for starting in RTTY. The reasons for this are not hard to find-the machine is cheap, especially secondhand or in kit form, and lends itself to use as a component rather than a computer.

CDICC

There are several programs available for the ZX81 and in this review we will look at the hardware supplied by Morsen Electronics for use with the G4IDE RTTY programs.

The G4IDE programs are held in EPROM and are either RITTY 2 for the 1K machine or RITTY 3 for the 16K version. Morsen recommend RITTY 3 if you have a 16K ZX81 and I would add that if you only have 1K of memory on your ZX81 then it would pay to add a RAMpack so as to allow you to run RITTY 3 and get the advantages of the 26 programmable stores and the other useful features such as split screen.

The program uses "time-sharing" techniques to allow you to type in your next transmission while still receiving the other station. A split screen format keeps transmission material separate from received copy and you can copy the reception screen onto a printer whenever required.

Stores

Up to 26 programmable stores, each holding a maximum of 600 characters, are available and these can be transmitted as desired by typing shifted s followed by the appropriate letter for the store required (A to z). Store 1 sends 16 RYs while Store 2 sends a CQ call with your callsign in it.

The instructions on using RITTY 3 are clear and easily understood and should therefore present no problems to the user.

To be able to use RITTY 3 with your 16K ZX81 you will need the Morsen ZX-10 which is available in either kit form or ready built from Morsen Electronics. I have built the kit for both the Interface and the Terminal Unit and in this part of the review I

will cover the constructional side, leaving the performance and operational side until the next issue.

The Interface is built on a double sided epoxy-glass p.c.b. which can be used for either RTTY or Morse but not both. This dual use carries through to the Terminal Unit board and can cause problems if you are not looking far enough ahead during construction. The instruction sheets state that components for the c.w. circuits are not included with the kit so that I assumed that all the components in the bag should be used. Unfortunately this turned out to be a false assumption and I ended up with a board carrying a lot of redundant sockets and resistors. No circuit diagram is provided for this board, instead a set of connection tables are given and bearing in mind the repetitious nature of computer circuits this is a reasonable approach. However there are four small circuit diagrams given with no explanation of what they do or how they are to be connected, or even whether you need them. I would like to see some explanation given in the instructions-not every builder is an RTTY expert!

The p.c.b. when completed can be fitted either into the Morsen metal keyboard case or inside the terminal unit box which is supplied with the t.u. kit. If it is inside the ZX81 metal keyboard case then I would recommend that you hardwire both the RAMpack and the Interface unit to the ZX81 p.c.b. to give improved reliability.

Terminal Unit

The terminal unit kit is supplied complete with mains power supply and metal case with a screen printed front panel. Again it is a dual-purpose piece of equipment covering both RTTY and c.w. and, unlike the Interface, can be simply switched from one mode to the other. Basic construction is simple so long as you work methodically and carefully to ensure that you do not insert components into the wrong holes. Here

the component placement drawing is not the clearest.

Based on the G4IDE design the t.u. can be used with any computer having a TTL compatible I/O port. The circuit uses active filters based around 741 op.amps. for the receive section while the transmit side uses a 567 p.l.l. chip as the a.f.s.k. generator using only the free-running oscillator and not the complete phase-locked loop. To help in setting up the board a frequency counter is included and the t.u. is isolated from the Interface board by opto-isolators.

In the next issue of Computing in Radio I will continue with the performance and operation of the completed system, but in the meantime further details and prices are available from Morsen Electronics, 3 Aylesbury Avenue, Eastbourne, BN23 6AB. Tel: Eastbourne 31620.

Just as we were going to press Morsen Electronics informed us that they have improved the kit for the t.u. making it RTTY only and screen-printing the p.c.b. to make assembly easier. More on this in the next issue.

G8VFH



G3WHO split-screen program available on Cassette, Disk or Eprom. Type-ahead while receiving, 6 memo-ries, Clock. Generates AFSK tones. Up to 100 baud.

Disk or Epron. ries. Clock. Generates Aron Amtor program available soon. P. J. Harris, Great Aine, Alcester, Tel. 078981 377.

G3LIV Terminal units. Ideal for above program. Inter-face directly with BBC micro but will work with other computers. PC boards or ready built. Slow Scan T.V., P.C.B.'s and Built units with Software to Interface with BBC Computer.

J. Melvin, 2 Salters Court, Gosforth, Newcastle, Tyne and Wear. Tel. 0<u>91 284</u> 3028.

Excellent reviews of both products. SAE to either address for full details.



Kantronics UTU Universal Terminal Unit The Kantronics Universal Terminal Unit (UTU for short) gives any computer with an RS232 port and a terminal program the ability to interface with any transceiver. The need for additional programs has been eliminated with the inclusion of a microcom-puter in UTU. The internal programming of UTU allows reception and transmission of Morse code, Radioteletype, ASCII, and Amtor.

KANTRONICS

| The Interface RTTY/CW (Software required) | £139.95 |
|--|---------|
| Interface II RTTY/AMTOR/CW (Software required) | |
| UTU Universal Terminal Unit (No software needed) | |
| Software | |
| Hamsoft Vic-20 Cartridge | |
| Hamsoft Apple II Disk | 29.95 |
| Hamsoft TI-99 Cartridge | .99.95 |
| Hamsoft TRS-80 Colour Cartridge | |
| Hamtext Vic-20 Cartridge | |
| Hamtext Com-64 Cartidge | |
| Hamtext Disc Apple II, IE | |
| Amtorsoft Vic-20 Cartridge | |
| Amtorsoft Com-64 Cartridge | |
| Apple Hamtext/Amtorsoft Disk | |
| Supertap Vic-20 Cartridge | |
| Supertap Com-64 | |



Mains Adapter£6.99 DC Adapter£4.49 £229.95



AMATEUR RADIO

PRO-30 Hand-held Scanner

Covers 68-88 MHz VHF-Lo, 144-148 MHz Ham, 108-136 MHz AM Aircraft, 138-144 MHz,

RADIO SHACK LTD

LONDON NW6 3AY

(Just around the corner from West Hampstead Station on the Jubilee Line) Giro Account No. 588 7151 Telephone 01-624 7174 Telex: 23718

rom Scarab Systems

From the UK's leading Radio Software House, come two new exciting professionally produced items.

SSTV for 48K SPECTRUM. This slow scan TV program cassette enables you to receive photographs or diagrams without additional hardware. It provides the facility of syncing and the ability to change the grey scale. Images may be transferred to a printer if required. £15.00 inc. VAT.

ZX81-RTTY on EPROM. This features an encased 'Motherboard' with several input/output connectors, offering an expandable system which is easily connected and allows the ZX expansion RAM Pack to be incorporated. Variable Baud Rates can be selected and the chip is installed on the interface board, allowing



for added expansion. It also enables the storage of memories on tape and has the ability to 'hard-switch' external circuitry directly. Motherboard £21.95, EPROM program board £15.95 Communications interface board (TTL) £24.95 inc. VAT.

188 BROADHURST GARDENS.

MODEM ORDERING SYSTEM

Please send me

le

You can now scan our stock list and order your Scarab System Equipment direct using this exciting new method. Send off the coupon for details



Scarab Systems produce many other top-quality programs and equipment for the Radio Amateur. Use the coupon now for details.

VISA

| SSTV for 48K SPECTRUM £15.00 | Details of Modern Ordering System |
|--|---|
| *Motherboard £21.95 *EPROM program board £15.95 *Communications interface board (TTL) £24.95 * Delete where necessary. | Free details of other equipment and programs |
| close a cheque/postal order for | |

| I wish to use my Access/Visa Card No | 5. | | | | |
|---------------------------------------|----------|------------|----|---|-------|
| Name | ** | | | - | |
| Address | | | | | |
| | | | | | www.r |
| Tel. No. | **** | ******* | | | |
| Signature | | | | | **** |
| · · · · · · · · · · · · · · · · · · · | 123 1223 | 2012/02/11 | 11 | | |

I understand that, if I am not fully satisfied. I can re the equipment with full reimbursement. 14 days delivery