VOL. XXII

NOVEMBER, 1964

NUMBER 9

K. W. ELECTRONICS for all your Amateur Radio Requirements

Consult us at K.W. for all your equipment - we may have it in stock

NEW! CDR Rotor and Coll. TRIIA £13. Also in stock CDR Rotor and Control Unit models AR22, TR44 and "HAM-M."

WE STOCK :

KEYS-Vibroplex Semi-auto-G.P.O. type, matic and C HKIB keyer,

VFO'S-Geloso, Miniphase. TOWERS-G3BXI and S.V.S. PHASE-SHIFT NETWORKS -B and W.

ROTATORS—CDR TRIIA, AR22, "HAM-M," & TR44. BEAMS—Mosley, Hy-G 11HC 2 metre curtain. Hy-Gain.

AERIALS-K.W. & Mosley, G3FIF & Webster Bandspanner (mobile).

MIC'S-Geloso, Shure, Acos. FILTERS SSB-McCoy Crystal and Kokusai Mechanical.

FILTERS-High Pass and Low

"WALKIE-TALKIE" Transceiver on 28.5 mc/s. New 200 mW. model.

AIRDUX COILS. Co range ½" to 2" dia. Complete RELAYS-Dow Key Co-axial

type. SIG. GENERATOR - Nom-

brex Transistorized. CABLE-Co-ax 75 and 52 ohm, 15 s.w.g. enamelled

POLYTHENE CORD-280 lb. and 350 lb. strain. SWR INDICATOR - KW

Match 75 or 52 ohm. CONVERTER - Front-end KW. Geloso.

PLUGS. SOCKETS, PI COILS. R.F. CHOKES, etc.

COLLINS 'S' LINE 32S3 & 75S3



The KW77 Receiver

K.W. TRANSMITTERS

KW "Viceroy" S.S.B. Transmitter MK. IV with built-in Power Supply £156 (Additional \(\frac{1}{2}\) lattice filter, £9 extra)

KW500 Linear Amp. 500 watts p.e.p., £78 10s.

KW "Vanguard" A.M. and C.W. 10-80m. £69.6.0 10-160m. £73.10.0 Kits also available. KW160. Top band transmitter with a punch, £30.10.0

Send for details. Carriage extra

Awarded Silver Plaque, Radio Communications Exhibition. Seymour Hall, London, 1963 KW2000 SSB TRANSCEIVER AND A.C. POWER SUPPLY 10-160 metres, Mobile and Fixed Station

Easy Terms Available

NEW! 50/- each 6146B tubes 2/6 postage & packing

Importers of U.S.A. Equipment

KW MODELS FOR 1965

KW 2000. SSB Transceiver KW 600. Linear Amp.

KW 2000A. SSB Transceiver (180 watts)

KW 2000C. Commercial 4-chan. Tcvr.

KW 77. Receiver-Trip. Conversion

KW 707. Receiver-Mech. Filter KW "Vespa." SSB Transmitter

KW "Viceroy." SSB Transmitter


KW 200. Transverter, 2 metres KW "Vanguard." AM/CW Tx

... and more to come . . .



ELECTRONICS LTD Vanguard Works

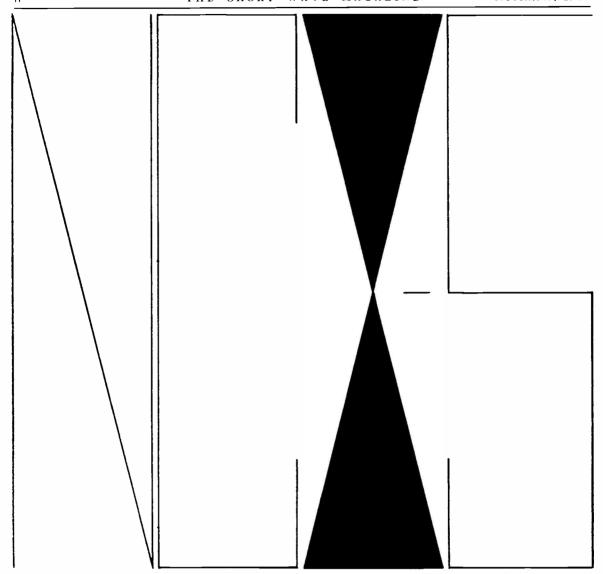I HEATH STREET, DARTFORD, KENT Cables: KAYDUBLEW, Dartford Phone: DARTFORD 25574



NEW NATIONAL NCX-5 All Band TRANSCEIVER

The NCX-5 is far superior in features and performance than any of the finest equipment previously available. Designed as a total amateur station for the 80-10 metre bands, without compromise for either mobile or fixed station operation. For use with the NCX-3 power supply.

Sole distributors:

Ad. Auriema Ltd.,

125, Gunnersbury Lane, London, W.3

Telephone: ACOrn 8762





FOR DEMONSTRATION, TERMS, PART EXCHANGE, ETC., YOUR NEAREST STOCKIST IS CENTRAL LONDON, New Max Electronics Ltd., 220, Edgware Road, W.2. SOUTHERN ENGLAND, Green & Davis, 104, Hornsey Road, N.7. MIDLANDS, Chas. H. Young Ltd., 170-172, Corporation Street, Birmingham 4. YORKSHIRE AND THE NORTH, Peter Seymour Ltd., 410, Beverley Road, Hull.

Z & I AERO SERVICES LTD.

Head Office: 44a, WESTBOURNE GROVE, LONDON, W.2. Tel: PARk 5641-2-3
Retail Branch: 85, TOTTENHAM COURT ROAD, LONDON, W.I. Tel: LANgham 8403

Please send all correspondence and Mail orders to the Head Office. When ordering by Mail please include 2/6 in £ for packing and postage.

Regret no C.O.D. orders accepted

VALVES FOR RADIO, T.V. AND AUDIO APPLICATIONS

VAL	VALVES FOR RADIO, T.V. AND AUDIO APPLICATIONS								
OA2 6/-16AT6	. 4/-i10D1	. 7/-135Z4G	4 / IEBF83	7/6;EL81	. 8 /6(PCC85	7/-ITP25 5/	TRANSISTORS		
OB2 6/-6AU6	. 6/- IOFI	. 14/-35Z5GT	6 /- EBF89	6/9 EL84	. 5 / PCC88	10/6 TP2620 7/	A QC23 8/- QC43 8/- QC// 8/-		
OB3 6/-6AV6	. 6/- 10F3	. 8/-50B5	7 /- EC80	8 /- EL85 12 /- EL86	. 8/PCC89	10/-TT21 32/	T 0036 (E) 0071 E) 00170 E)		
OC3 6/-6BE6 OD3 5/-6BH6	7/-110F9	. 10 /- 50C5 . 9 /- 50CD6G	6 /6 EC88	2/6/EL86	. 7/6 PCC189 6/-IPCF80	10/- 025 11/	OC42 8/- OC72 8/- OC171 9/-		
IA5GT 5/-6BJ6	. 8/-lioLi	. 7/6/50L6GT	6/6/FCC91	5/-EM31		6/- U26 / 7/- U191 /	OC44 6/- OC76 6/- OC204 10/6		
IA7GT 8/-6BK4	. 20/- 10LD11	10/- 757	16/-IECC84	6/6EM34		8/-10251 12/	Matched pair of OC81 with one OC81D 12/6		
1B3GT 7/-6BK7A	8/IOP13		30 /- ECC85	6/6 EM80		8/- U281 13/	_ N.C.A. 2N410 (OC45); 2N412 (OC44)		
IH5GT 7/-6BN6	· 7/-110P14	12 /6 807 GT 5 /- 829B		10/-EM81		10/- U282 14/	TIRCA set of two ONIVID and and		
	11/6/12AH8		60 /- ECF80 20 /- ECF82	7 /6 EM84 7 /6 EM85		10/- U301 12/- 13/- U403 7/-	7 2N4IO 8/		
105GT 8/-16BR8		7/- 954	5 /- ECF86	11 /- EM87		9/- U801 18/-	G.E.T.115 7/- G.E.T.573 20/-		
IR4 6/-6B\$7	. 16/-112AT6	5/- 955	3 /- ECH21	10/-EN31	. 10/- PCL82	6/6 U4020 7/	Platched pair of G.E. .5/3 35 /-		
IR5 5/-6BW6	9/- 12AT7	4/- 956	2/-ECH35	12 /- EN32	. 10 /- PCL83	8/3 UABC80 5/			
IS4 5/-6BW7	9/- 12AU6 . 12/- 12AU7	6/- 957 5/- 958	5/-ECH42	8/- EY5!	7 /- PCL84	7/UAF42 8/-	Philes TI166		
IT4 3/-6CB6	. 5/-112AX7	5 /- 958 6 /- 959A	4/-ECH81 8/-ECH83	6/- EY81 7/6 EY83	. 8 /- PCL85 9 /6 PCL86	9/- UBC41 6/6 9/- UBC81 7/	9		
ITSGT 6/-6CD6G		6/-12050	12/6 ECL80	6/6 EY86	6/-PEN45	6/6/UBF80 6/6	21 JEIN-CONDOCION		
1U4 5/-6CH6	. 6/- 12BE6	5/- 5654	8 /- ECL82	7 /6 EZ80	5 /6/PEN45DI		POWER RECTIFIERS		
1U5 6/-6CL6			10 /- ECL83	9/-EZ81	4/6	12 /- UBL21 11 /-	Silicon :		
1X2A 7/-6CW4	12/- 12Q7G 15/- 19AQ5		25 /- ECL86 27 /6 EF36	9/- GZ32 4/6 GZ34	10/~PEN46 10/~PEN220A	61-JUCC84 91 71-JUCC85 61			
2C51 2/-16F8G	5/-20F2	. 15 /- AZI	9 /- EF37A	8/- GZ37	9/- PEN348	12/-IUCF80 9/6			
2CW4 12/-6F11	. 6/-20LI	14/- AZ31	8 /- EF39	5/- HL2	3 /- PEN453C	D UCHZI 8/	BYZ10, 800 p.i.v., 5 amps 7/6		
2D21 6/-6F13		14/-AZ41	6/6/EF40	9/HL2K	3 /	10/6 UCH42 7/4	Germanium:		
3A4 4/- 6F17 3A5 7/- 6F23			9/-EF41 6/6 EF42		6/-PL36	8/6 UCH81 7/-	- GJ3M, 200 p.i.v., 400/800 mA 3/6		
3D6 4/-16F24		12/- DAF91	4/6 EF54	6/- HL23DI	15/-IPL81	16/UCL82 8/- 7/UCL83 10/-			
3Q4 6/6/6F28		5/- DAF92	6 /- EF55	8 / HR7	15/-PL82	5/6 UF41 7/6	GJ7M, 80 p.i.v., 500/1,000 mA 3/6		
3Q5GT 6/6 6F33	. 6 /– 25L6G1	8 /- DAF96	6 /- EF80	5 /- KT8C	20/- PL83	6/- UF42 7/6			
3\$4 5/-6K8GT		7 /- DF96	6/-EF83	10/-KT41	7 /6 PL84	6/6 UF80 6/6			
3V4 5/6/6LI 5R4GY 9/-6LI8		7 /6 DK96	7 /6 EF85 6 /- EF86	6/- KT44 6/6 KT61	5/- PL500 12/6 PX25	15 /~ UF85 7 /- 10 /~ UF86 10 /-			
5U4GB 6/6/6N7		7 /-IDM70	5/-EF94	6/-IKT63	6/-IPY31	10/- UF86 10/- 7/- UF89 6/-			
5V4G 8/-6U4GT	10 /6 30C15	10/-DY80	7/- EF95	5 /- KT66	15 / PY33	9/-IUL41 7/6			
5Y3GT 5/-6U8		12 /- DY86		10 /- KT88		5/6 UL84 6/-	- internal 100 kc/s. crystal up to 25 mc/s.		
5Z4GT 8/-6V6 6/30L2 10/-6X4	. 9/- 30F5 . 4/- 30FLI	9 /- E88CC	14/-EF183	8/- N78	15 /- PY82	5/-\UM4 10/-	at I mc/s. intervals. Power supplies required		
6AB4 6/6.6X5GT	5/6/30L17	11 /- E180F 13 /- EABC80	15 /- EF184 6 /- EFP60	8/- NR88		6/- UM80 7/- 8/6UY2I 8/-			
6AF4 11/-16Y6G	6/-30P12	10/-EAF42		12 /6 ORP12	12/- PY800	8/6 UY41 5/6			
6AG7 6/- 7D8	7/-30P19	14/- EB4I		10/- ORP60	10/- QQV03-1	UY85 5/-			
6AH6 10/-19BW6	7/-30PLI	11/6 EBC33		17 /6 PC86	12 /- QQ VU3-1	35 /_ W8IM 6/-			
6AM6 4/-9D7	7/-35A5				12/- TH41	10/- X65 5/-			
6AO5 6/-10C1	10/-35L6GT	7 /- EBC81		7 /- PC97			NEW PRICE LIST OF VALVES AND TUBES		
6AS7G 22/6 10C2		5 /- EBF80	6/6 EL42			7/- X79 18/-			
						<u>.</u>	<u>- </u>		



21 VICTORIA ROAD SURBITON, SURREY

Tel.: Elmbridge 2833 and Lower Hook 2000

100 yards from Surbiton station — Opposite Victor Value

WE HAVE A COMPREHENSIVE RANGE OF AMATEUR COMMUNICATIONS EQUIPMENT

NATIONAL NC77X £28.14.1, NC121 £53.6.11, NC190X £89.18.2, NCX3 £148.8.4, NCX5 £235.0.0, LAFAYETTE HA63 £27.10.0, HE30 £35.0.0, HE-40 £19.19.0, SECOND-HAND 640, 740, 750, 840A, 680, 888A, EC10, G209, KW Viceroy, KW160, Minimitter Top 2-7, Drake 2B, Redifon R50M, AR88, CR100, SX28, HRO, RG-1, BC221, LM14, RA-1B, etc., etc. JOYSTICK antenna and ATU, and many more items too numerous to list.

SEND US YOUR REQUIREMENTS — HIRE PURCHASE — PART EXCHANGE
JUST WRITE OR PHONE FOR FURTHER DETAILS

Brian J. Ayres & co.

- 9



THREE MODELS

Mosley El Toro aërials are available in three models, TW-3X, NS-3 and TW-3X Jt., designed to give outstanding performance.


THREE BAND OFERATION

Mosley TW-3X and TW-3X In gerials operate on 20, 40 and 75/80 meters. Mosley NS-3 (Novice Special) operates on 15, 40 and 80 meters. All Mosley pertols feature previoued, compact design and excellent broad band characteristics.

TWO POWER RATINGS

Moster TW-3X has on AM rating of 1000 watts input to the final amplifier and a CW/SSB rating of 2000 watts P.E.P. Mosley TW-3X Jr. and NS-3 (Novice Special) have ratings of 300 watts on AM and 500 watts CW or 1000 watts P.E.P. on SSB.

 Masley El. Toro gerials are trap type grounded quarter wave derials using a unique method of tuning and a single 52 ohm coax line Aerial 1s. 58 ft. long and can be mounted to fir most any location. No radials are needed when mounted at ground level, Aerials come pretuned, in his form analogue be easily adjusted to resonate at any portion of the rated bands.



13

Model V.4.6

SWR with response exceptionally flat across full width of each band. Weather proof traps are of Hi-Q design wound on groved polystyrene forms. Will maintain resonant points under wide variations of temperature and humidity. Rated to 1 KW. Rugged, lightwei ht aluminum rubing telescopes to height of 20. Pre-drilled and color coded for fast, easy assembly. Supplied with ot 20° Pre-drilled and color coded for fast, easy assembly. Supplied with heavy duty base mannt that is made of malded "Cycolac" and incorporates a scoax fitting and ground strap. Polyethylene guy rope, hardware and detailed instructions are also furnished. Normal ground installations required 4 radials 33' each: Shipping weight, 12 pounds.

Model D4 BC A

Beautifully constructed base loading coil petmits operation of V-4-6 Vertical Aeriol. on 75 and 80 meter bands. Rated to handle a full kitowatt (AM), coil is space wound. Mounts quickly and easily on base section of vertical. With silver plated coax connector. Shipping weight, 3 paunds.



Cammando II, incorporates many features which make it the Durstanding Transmitter Buy Today! Only reliable "air-tested." circuitry is used. Power Supply Is the latest cool-running Silicon Recfifier, suse protected and conservatively rated. Power Amplifier ampleys two 6146 Tetrodes operating at 750 Volts Class ABI kinger Amplifier Service to give Maxaring of 750 Volts Class ABI kinger Amplifier Service to give Maximum I.C.A.S. rating at 180 warts P.P. The Pl. Tank circuit bands witching 80 thrus 10 Meters gives efficient loading into low impedance coaxial lines. Sideband generation at 435 kcs. with half-lattice crystal filter for 45 db. sideband/carrier rejection. Sideband switch in "normal" position is correct for band in use, but, an "inversion" switch gives choice "inversion" switch gives choice of alternate sideband.

Masky Electronics Itd. 40, Valley Road, New Costessey, Norwich, Norfolk.

FOR PEAK PERFORMANCE AT LOW COST — PICK







Advanced design and craftsmanship plus an unequalled reputation proved by the many hundreds of testimonials received from CODAR users is your guarantee of complete satisfaction. Only the best is good enough for CODAR—Mullard, Brimar Jackson, Denco, Electroniques, Thorn, A.E.I. are just some of the famous names built into CODAR equipment. Illustrated leaflets available on request.

For or the beginner and S.W. listener CODAR CR66 Communication RECEIVER

The finest superhet kit ever offered.

CR66 KIT £19. 10. 0. (Ready Built £22 10 0) CR66 'S' METER

MODEL KIT £21. 10. 0. (Ready Built £24 10 0) Carr. 7/6 on all models (H.P. Terms available)

CODAR R.F. PRESELECTOR Will considerably improve the performance of any superher receiver. "Results are amazing." "Well worth the money." Model P.R.30. Uses EF183 Frame Grid tuned R.F. Amplifier and provides up to 20 dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12 M/a H.T. 53 volts 3 amp. L.T. Size: 84" x 5" x 4". Ready built, complete with cables, plugs and instructions, £4.17.6, carr. 3/-. Model P.R.30X. Self-powered version for 200-250v. A.C. and also provides 25 M/a. at 200v. H.T. and 6.3v. I amp. L.T. for other accessories, £7.2.0, carr. 3/-.

CODAR "Q" MULTIPLIER | CODAR A.T.5, 12 WATT | Model R.Q.10. For use with any | 2 BAND TRANSMITTER. CODAR "Q" MULTIPLIER Model R.Q.10. For use with any superhet receiver with an I.F. between 450 and 470 kc/s. Provides considerable increase in selectivity for either peaking or rejecting a signal on AM, CW or SSB. Both PEAK and NULL functions tunable over receiver I.F. passband. B.F.O. facility included. Size: 8½" × 5" × 4". Power requirements 180-250v. H.T. at 5 M/a. 6.3v. 3 amp. LT. Ready built, complete with cables, plugs and instructions, £6.15.0, carr. 3/-.

The newest, most compact transmitter for fixed or mobile use on 160/80 metres. "The tiny TX with the BIG voice." Size only 8½" x 5" x 4" (Base area is less than 2/3rds of this page).

Illictions tunable over receiver I.F. passband. B.F.O. facility included. Size: 8½" x 5" x 4". High stability new type calipole of the power of the

A.T.S. POWER SUPPLY UNITS.

Type 250/S. For 200/250v. A.C. with Standby/ Net/Transmit and aerial changeover switching, stabilised V.F.O. supply, neon standby / transmit indicator, £8.0.0, carr. 5/-.

Type 12/MS 12v. Transistor power supply unit available shortly.

CODAR-QOILS SPACED INDUCTORS.

SPACED INDUCTORS.
A complete range of low loss air-spaced inductors developed by CODAR and suitable for all types of circuit application. Over 40 different sizes from 4" to 3" diameter suitable for all types of circuit application including V.F.O. P.A. Tank, Pinetwork, A.T.U., aerial loading, etc. Full data and prices on request.

Codar-Qoil

U.K. Distributors :

ELECTRONIQUES Ltd. Penfold Road, Felixstowe, Suffolk.

CODAR RADIO COMPANY

BANK HOUSE, SOUTHWICK SQUARE, Southwick, Sussex. Tel. 3149

NEW from Labgear THE ONE SIXTY SERIES

FOR MOBILE AND FIXED INSTALLATIONS





The One Sixty Topband Mobile/Fixed Transmitter

- Full 10 watts 1.8–2.0 Mc/s.
- High level modulation for punch.
- Build-in aerial c/o relay.
- Netting c.w.— Remote switching facilities.

Price £15.15.0

Mobile Power Supply Unit

- I2v. D.C. input.
- 300v. I50 mA D.C. output.

Price £8.0.0

Fixed Station Power Supply Unit

- 200–250v. 50 c/s. A.C. input.
- 6.3 or 12.6v. A.C. output.
- 300v. I50 mA D.C. input.

Price £7.7.0

The One Sixty Topband Mobile Converter

- Connects to any car radio.
- Covers 1.8-2.0 Mc/s.
- I.F. output in MW band.
- Crystal controlled.

Price to be announced


HIQIF' QOILMAX STABQOIL'

ELECTRONIQUES

'QOILPAX' 'PATHFINDER'

HIGHLIGHTS of the 1964 I.R.C. EXHIBITION

AIR-WOUND "CODAR-QOILS"

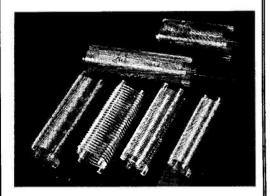

THE PERFECT COILS FOR ANY TX DESIGN

A complete range of over 40 different sizes from 3" D. to 3" D. Beautifully engineered. High 'O' and low losses. Ideal for Pi Tank Circuits, Aerial Tuning Units, Loading Coils, etc.


EXCLUSIVE U.K. DISTRIBUTORS

PATHFINDER WORKS. PENFOLD ROAD, FELIXSTOWE, SUFFOLK.

"QOILPAX"

Our famous "QOILPAX" now FULLY TRANSISTORISED!

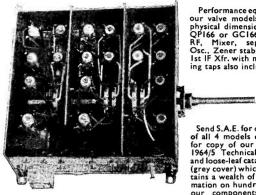MODEL HB166/T 6 BANDSPREAD HAM BANDS MODEL GC166/T 6 GENERAL COVERAGE BANDS



Performance equal to our valve models. All physical dimensions as QP166 or GC166. RF, Mixer, separate Osc., Zener stabilised. Ist IF Xfr. with matching taps also included.

Send S.A.E. for details of all 4 models or 2/6 for copy of our latest 1964/5 Technical Data and loose-leaf catalogue (grey cover) which contains a wealth of infor-

mation on hundreds of components and complete data on our special kits for such famous designs as the G2DAF Mk. II RX and SSB TX, the G3BDQ RX and SSB TX, the G3RKK prize winning RX and 50 watt AM/CW TX, the G3KWG RX, etc., etc.

Phone: 4500

SIDEBAND ENGINEERS TRANSISTORISED

SSB GEAR

Built-in Power Supply and Loudspeaker. 18 Transistors, 18 diodes and 1 zener diode.

Low current drain. Collins mechanical filter. The only tubes used are two, rugged PL-500.

FL-300. Bandswitch and tuning capacitor are interlocked by Geneva movement making it impossible to tune to a spurious frequency. Size: (Overall) 5½" H., 12" W., 10" D. Weight: 15 lbs.

THERE'S A I KW SBE LINEAR TOO!

HORNSEY ROAD, LONDON, N.7.

Tel.: NORth 6871

S.B.E.

SB33, 4 Band Transceiver, £163.16.0 · SB2DCP, Mobile Power Supply, £33.9.0 · SB1LA, I KW Linear Amplifier, £117.11.0 · SB3DCP, Mobile Supply for SB1LA, £109.3.0 · SB1MP, Mobile Mounting Bracket, £5.5.0 · SB1VOX, Add on Vox for Sp33, £16.15.0 · SB1MIC, Microphone with P.T.T., £6.2.0.

GREEN & DAVIS EQUIPMENTS

GREEN & DAVIS EQUIPMENTS
P.G.L.A.1., ½ KW Linear Amplifier, £87.10.0 .
2M1000, 150 watt 2 metre Transmitter, 96 gns. .
2M15-20A 20 watt fixed/mobile 2 metre Transmitter, 48 gns. . MKI11, 2 or 4 metre Nuvistor Converter, £8.19.6 . MKI17, 2 or 4 metre Nuvistor Converter, £14.14.0 . SN70, 70 centimetre Nuvistor Converter, £16.16.0 . CTX-2, 20 watt fixed/mobile 2 metre Transmitter, £14.14.0 . CTR70, 8 watt Tripler/Amplifier for 70 cm., £20.0.0 .
70CM1000, 90 watt Tripler/Amplifier for 70 cm., £30.0.0 . £65.0.0.

1965 EQUIPMENTS

T160-2, Top band and two metre Transmitter. 15 watts Input. Transistor Modulator, 48 gns. TVR-2, Top band and two metre Transceiver extensively transistorised. 10 watts input. 20-2, Transverter from 14 mc/s. SSB to 144 mc/s. SSB for use with Transceiver or separate TX/RX.

NATIONAL EQUIPMENT

NC77X, Receiver, £28.14.1 NC121, Receiver, £53.6.11 NC190X, Receiver, £89.18.2 NTS3B, Matching Speaker for 190X, £7.8.1 XCU, Crystal Calibrator, £7.15.7 NCX-5, SSB 3 Band Transceiver, £148.8.4 NCX-5, SSB 5 Band Transceiver, £235.0.0 NCX-A, AC P.S.U. for NCX3-NCX5, £46.7.1 NCX-D, DC P.S.U. for NCX3-NCX5, £50.8.11 NCL-2000, 2 KW Linear Amplifier, £735.0.0 Amplifier, £235.0.0.

COMMUNICATIONS FOUIPMENT SPECIALISTS

PETER SEYMOUR LTD

				COMMONICATIONS EQUILINEIN SEE		LIS	113
A = 0.0 - 1.	£	s.	d.			s.	
AR88LF/E. 75-550 Kc., 1.5-30 Mc/s., fitted with "S"				MARCONI CRI00 with noise limiter, 100-240 AC	-	3.	u.
meter. Less cabinet (P/P £1)	35	0	0	17 DUE 60 KC 30 MC (D/D CI)	15	^	
Rewired with p.v.c. 100/240 AC input. With cabinet				NATIONAL NCI88. 540 Kc30 Mc/s., separate	13	U	U
(P/P fl)	40	0	0	80-10 metrs. bandspread (P/P 15/-)	24		
AR88D. 540 Kc32 Mc/s. Rewired with p.v.c. (P/P £1)	65	ň	ŏ	HALLICRAFTERS HT40 TRANSMITTER, 80-10	30	U	U
AR88D. New, less accessories (P/P £1)	65	ň	ŏ	MALLICAATIERS HI40 IRANSHII IER, 80-10			
CRISO in first class condition. 2-60 Mc/s. less power	03	•	٠	metrs., xtal controlled with provision for separate			
unit (P/P £1)	25	•	۸	V.F.O., 75 AM/CW. As brand new (P/P 10/-)	30	0	0
HAMMARLUND SP600JX. 540 Kc54 Mc/s. 100-	13	U	U	SX 140. 80-10 metrs., amateur bands only. Variable			
245 AC input, double conversion. 20 tubes, 2 RF				selectivity, "S" meter, etc. In stock new or second-			
		_	_	hand (P/P 10/-) respectively 54 0 0	25	0	0
Stages, etc.	150	0	0	All new Hallicrafters equipment can not be supplied			
MURPHY API00335 RECEIVERS. 60-550 Kc. and				catalogues free on request. Other new items in stock			
1.5-30 Mc/s. Miniature valves, 2 Rf, Mix, sep osc.,				include, Green and Davis Mk.42 met. Converter.			
3 IF, variable selectivity, BFO, etc. Less power unit.				G3EKX SSB Tx. 160-80-20 metrs. Will drive the			
Required 6.3 AC and 200-250 DC. In original packing				largest linear. 240 AC input	75	n	0
cases (P/P £1)	28	0	0	THE NEW NATIONAL NUX 3 and 5. NC171 Millen			
EX ADMIRALTY TUNING OSCILLOSCOPES.				GDO with coils 1.5–300 Mc/s	25	•	
240 AC input would make FB modulation monitor				ELECTRONIC BUG KEYS:	23	U	U
with no modification. 3" tube. Small size. (P/P 10/-)	4	10	0		17		
LABGEAR LG300. RF section only 80-10 metrs.			•		16		
to clear (P/P fl)	25	0	0	Hammarlund HKI Transistor switching	!5	Ō	Ū
HALLICRAFTERS S76. Double conversion 50 Kc.		•	•	Hammarlund HKI. Transistor, battery operated	1/	.0	ò
second I.F. 240 AC input. 550 Kc30 Mc/s., separate				SEMI AUTOMATIC BUG. Japanese. "Superspeed"	4		
bandspread, "S" meter, variable selectivity (P/P 15/-)	35	0	٨	MATCHED FOURS SSB diodes pack		5	
HALLICRAFTERS S107. 55-1.6, 2.5-30 Mc., 47-54	"	٠	٠	DUVIDAL CM21. Crystal microphones, new (P/P 9d.)		9	6
Mc. Built-in speaker (P/P 10/)	20	0	0	MULTIRANGE METERS. 1000 opv. 0-15, 150, 1000v.			
Mc. Built-in speaker (P/P 10/-) HALLICRAFTERS S38E. 540 Kc30 Mc/s. with	20	U	v	AC/DC, 0-100K, 0-150Ma (P/P 1/6)	2	0	0
bandspread (P/P 10/-)				RIO9A. 1.97-12 Mc/s. 6v. DC input, built-in speaker,			
HALLICRAFTERS SING Name 540 Kg 22 Mg/	20	0	U	BrO, etc (P/P 10/-)	2	10	0
HALLICRAFTERS SIOS. New. 540 Kc32 Mc/s.				FIELD STRENGTH INDICATORS. 1-250 Mc/s			
separate calibration dial, 80-10 metrs. Noise limiter,		_		built-in meter, antenna, etc	2	14	6
BFO, etc (P/P 10/-)	53	0	0	4 AMP. BATTERY CHARGERS. New, British made			•
COLLINS T.C.S. 1.5-12 Mc/s. with power unit and				(P/P 5/-)	2	10	n
speaker (P/P In/a)	ш	10	0	4X250B. Complete with special base, brand new	-		٠
EDDYSTONE 940. As new, 480 Kc30 Mc/s. product				(P/P 3/6) Each	6	0	•
detector, 2 RF, etc	95	0	0	BY100's. Brand new (P/P 6d.)	٠	5	
						3	U
PROFILE VEGOIVED EDDAZIONE RECEIVERS 640	, 88	8, 8	88A	AND MODERN SSB EQUIPMENT. PLEASE STATE YOU	R P	RIC	E
MUST HA	AVE	NO	MA	AJOR MODIFICATIONS		•	
EXPORTE	נח.	, ,	ALL I	PARTS OF THE WORLD			

410 BEVERLEY ROAD - HULL - YORKSHIRE Telephone HULL 41938 (43353 after 7.30 p.m.)

TECHNICAL PUBLICATIONS — Available from Stock

LATEST ISSUES

CALL BOOK (Autumn Edition)

"DX Listings," 27s. post free. "US Listings," 45s. post free The two together, covering the World, 65s. post free

AMATEUR RADIO HANDBOOK

(by R.S.G.B.), 550 pp., 36s. 6d.

RADIO AMATEUR'S HANDBOOK

by A.R.R.L. (41st Edition) 37s. 6d. post free (Library Binding) 47s. 6d. post free

MAGAZINES BY SUBSCRIPTION

One Year
CQ, RADIO AMATEUR'S JOURNAL 44s. 0d.
QST, ARRL 48s. 0d.
Post free, ordinary mail only

EASIBINDERS for Short Wave Magazines, hold 12 issues (One Volume) 16s.

LOG BOOKS, spiral bound, by ARRL, 7s. 6d.

LOG BOOKS, by Webbs Radio, GPO Approved, 6s. 3d. post free

RADIO HANDBOOK—Sixteenth Edition 86s, post free

DX ZONE MAP (With Amendment List to Oct. 1963) (Great Circle, centred U.K., size 25ins. by 35ins. A "must every DX operator and SWL) Linen Backed (de luxe) 11s. 0d. post free

AMATEUR RADIO MAP OF WORLD

Mercator Projection — Much DX Information — In Colour, 8s. 6d. post free Second Edition

WORLD SHORT WAVE RADIO MAP

(General SWL and BC coverage, with handbook) 8s. 6d. post free

RADIO AMATEUR MAP OF THE U.S.A.

State boundaries and prefixes, size 16ins. by 36ins., paper. 4s. 3d. post free

AMATEUR'S WORLD ATLAS RADIO

In booklet form, Mercator projection, for desk use. Gives
Zones and Prefixes 8s. 3d. post free

SHORT WAVE MAGAZINE

PUBLICATIONS DEPARTMENT · 55 VICTORIA ST · LONDON S.W.I · ABBEY 5341

TECHNICAL PUBLICATIONS — Available from Stock

Latest Issues

	Post 3	Free		Post	Free
AMATEUR SINGLE SIDEBAND (Collins)	30s.	0d.	NOVICE HANDBOOK, Tx and Rx, 150	00-	C A
ANTENNA ROUND UP (by CQ)	25s.	0d.	OPERATING AN AMATEUR RADIO	23s.	oa.
ANTENNA HANDBOOK (A.R.R.L., 9th	10-	0.3	STATION (A.R.R.L.)	2s.	8d.
Edition)	195.	0d.	PORTABLE TRANSISTOR RECEIVER	3s.	0d.
BASIC MATHEMATICS FOR RADIO AND ELECTRONICS	18s.	3d.	QUAD ANTENNA	23s.	0d.
BEAM ANTENNA HANDBOOK, New			RADIO AMATEUR EXAMINATION		
Edition	28s.	0d.	MANUAL	5s.	6 d .
BETTER SHORT WAVE RECEPTION		0d.	RADIO AMATEUR OPERATOR'S HAND- BOOK (Data Publications)	5e	0d.
CALL BOOK (U.K. only), 1965 Edition	5s.	6d.	RADIO CONTROL MANUAL	25s.	
CHART OF INTERNATIONAL FRE- QUENCY ALLOCATIONS — GENEVA,			RADIO CONTROL FOR MODELS (F. C.	×05.	٠
1960 (Official), 10 Kc. to 40 Gc., 51"	_		Judd)	16s.	0d.
x 34", wall mounting		3d.	RADIO DATA CHARTS (Iliffe)	11s.	3d.
COMMUNICATION RECEIVERS		0d.	RADIO DATA REFERENCE BOOK	14s.	0 d .
CQ ANTHOLOGY (1952 — 59)	25s.	0 d .	RADIO INTERFERENCE SUPPRESSION	11s,	3d.
COURSE IN RADIO FUNDAMENTALS (A.R.R.L.)	10s.	6d.	RADIO VALVE DATA 4,800 types listed	8s.	3d.
ELECTRONIC CIRCUITS HANDBOOK	24s.		S9 SIGNALS	8s.	6d.
FOUNDATIONS OF WIRELESS	22s.	3d.	SHORT WAVE RECEIVERS For the Beginner (Data Pubs.)	6s.	6 d .
GETTING STARTED WITH TRANSISTORS (GERNSBACK)	28s.	6d.	SHORT WAVE RADIO AND THE IONO- SPHERE (Iliffe)	11s.	9d.
GUIDE TO AMATEUR RADIO	4s.	. 0d .	SINGLE SIDEBAND FOR THE RADIO	10	e a
GUIDE TO BROADCASTING STATIONS	Ĕ.	6d.	AMATEUR (A.R.R.L.) (3rd Edition) STEREO HANDBOOK	18s. 11s.	
(Hiffe)		6d.	SURPLUS SCHEMATICS (Published by	115.	TU.
HAMS INTERPRETER (4th Edition)			CQ)	21s.	0d.
HINTS AND KINKS Vol. 6	115.	0d.	SURPLUS HANDBOOK (Editors and		
HOW TO BECOME A RADIO AMATEUR (A.R.R.L.)	10s.	0d.	Engineers)	24s.	0d.
HOW TO IMPROVE YOUR SHORT WAVE			SURPLUS CONVERSION MANUAL Vols. I, II and III, each	24g	0d.
RECEPTION	14s.	9d.	TELEVISION EXPLAINED (Iliffe)	13s.	
HOW TO LISTEN TO THE WORLD,	4 =	0.3	TRANSISTORS: THEORY AND PRAC-	TOS.	ou.
1963/64	I5s.	. 0d.	TICE (Published by Gernsback)	23s.	. 0d.
INTERNATIONAL TRANSISTOR DATA MANUAL (AVO)	360	. 3d.	TRANSISTOR THEORY AND PRACTICE		
•			(Published by World Radio Handbook)	9s.	6d.
LEARNING MORSE	15.	. 9 d .	TRANSISTOR TECHNIQUES (Gernsback)	12s.	6 d .
LEARNING THE RADIO TELEGRAPH CODE (A.R.R.L.)	4s.	. 6d.	TRANSISTOR RADIO HANDBOOK		
MOBILE HANDBOOK (Published by CQ)		. 0d.	(Editors and Engineers)	45s.	0d.
MOBILE MANUAL (Published by	₩ ±3.	. vu.	UNDERSTANDING AMATEUR RADIO	19s.	. 6 d .
A.R.R.L.)	24s	. 6 d .	VALVE DATA MANUAL (AVO)		. 3d.
NEWS FROM AROUND THE WORLD \dots	11s.	. 6d.	VHF HANDBOOK (Orr W6SAI)	24s.	. 0d.
NEW RTTY HANDBOOK	32s	. 0d.	VHF FOR THE RADIO AMATEUR (CQ)	28s.	. 0d.
NEW SIDEBAND HANDBOOK (by CQ)	25s.	. 6d.	WORLD RADIO HANDBOOK (1964)	22s.	. 6 d .

SHORT WAVE MAGAZINE

Publications Department · 55 Victoria St · London S.W.I · Abbey 5341

Nº1 OUT NOW

For all Electronics Enthusiasts





Code Calculator for





INSIDE

ELECTRONIC DATA PULL-OUT BOOKLET

CONTENTS INCLUDE

CONSTRUCTIONAL PROJECTS: Full details for building:- 5 watt Integrated Amplifier. Simple Geiger-Muller Ratemeter and other TRANSISTORISED UNITS

SPECIAL FEATURES: Semiconductors for Automobiles, Electronic Developments in Industry and other fields. New Components and Equipment.

Practical Electronics

PLACE A REGULAR ORDER-2'6 November

YUKAN Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Available in Grey Hammer at 14/11 at our Care Hammer at 14/11 a

Get this Air Drying Grev **HAMMER FINISH**

IT'S SUPERB

THE PUSHBUTTON WAY!

Dept. SHW, YUKAN, 307a EDGWARE ROAD, LONDON, W.2. (Closed Thurs. afternoons, open all day Sats.—Annual closing Dec. 10 to Jan. 1) Choice of 13 selfspray plain colours and primer (Motor car quality)

NORCOL LTD

Suitable to fit car radio pocket; also MW (Luxembourg, Caroline, West Home Service).

De Band Transmitter Mit Top Band Receiver Kit Top Band Transmitter Kit (SHORTLY AVAILABLE) HRO Receiver-Several, good condition £IO (plus £1 each for coils) £30 Good battery Jap Tape Recorder (New)... £18 Small Jap Tape Recorders £R RECORD YOUR QSO's

Components, Cheap Prices, S.A.E. Lists

147, LONDON ROAD, YORKTOWN, CAMBERLEY. SURREY

Telephone: Camberley 3743

TWEEDY G3ZY IACK

Electronic Supplies, Communication Equipment, Eddystone Stockist, Heathkit Authorised Dealer, KW Electronics, Codar, Green & Davis, Mosley and other equipment supplied.

NEW: Eddystone EC10, £48; EA12, £185; Eagle RX80, £45; G. & D. NEW: Eddystone ECIO, E46; EAIZ, E163; E2816 NAOV, E43; S. G. D. VHF converters and transmitters, Codar-Qoils, PR30 preselectors, RQ10 "Q" Multipliers, CR66 Rxs. and "S" meter kits, Miniphase vios, Vibroplex keys. Full range of Eagle equipment and accessories. USED: Tiger 300X completely overhauled, smart appearance, £70; Minimitter de-luxe AM/FM/CW, £50; Minimitter Top-2-7, £25; Minimitter 3 band mobile with control box and transistorised psu, £18; MR37 Rx., £26; Eddystone \$750, £37/10/-; \$X28, £28; New Sig. Gen. Type 106 (.55 to 55 mc/s.), £6/15/- including carriage.

Please send S.A.E. for details, H.P. terms available. Trade-ins accepted

21 Birkin Lane, Grassmoor, Nr. Chesterfield, Derbyshire Tel. HOLMEWOOD 506

YOU OWN A GOOD TAPE RECORDER

So insist on obtaining the best sound reproduction from it, and to do this is by getting a Lustraphone Microphone.

A wide range of models both ribbon and dynamic is available.

For full details contact

LUSTRAPHONE LIMITED (Dept. S.W.II) St. George's Works, Regent's Park Road, London, N.W.I

Telephone: PRImrose 8844/5/6

INDEX TO ADVERTISERS

	PAGE
B. J. Ayres & Co	513
Ad. Auriema, Ltd	cover ii
Anglin	568
Anglin Bradfærd, Ltd	575
British National Rac	io
School	566
Busfield's Astro-Marine	568
Charles H. Young	cover iii
	515
Daystrom	cover iv
Electroniques, Ltd.	517
Finnigan Speciality Pair	nts 568
G. D. Components	
G3HSC (Morse Record	
Green & Davis	517
G.W.M. Radio	574
Henry's Radio	573
Home Radio	572
J.T. Supply	576
J. Tweedy	520
K.W. Electronics	520
front cover of	& cover iii
	516
J. B. Lowe, Ltd	576
Lustraphone, Ltd	520
Minimitter	573
Mosley Electronics	514
Multicore	574
Norcol Ltd	520
Norcol, Ltd Olympic Works	572
Partridge Electronics, L	td
570	0, 575, 576
Peter Seymour	518
Practical Electronics	520
Practical Wireless	571
Royal Naval Reserve	522
R.S.C. (Derby) Ltd.	568
Service Trading Co.	575
Short Wave (Hull)	
Short Wave (Hull) Small Advertisements	567-575
Smith & Co. Ltd	569
S.S.B. Products	566
Smith & Co., Ltd S.S.B. Products S.W.M. Publications 518	8, 519, 567
Withers	566
Withers Yukan Z. & I. Aero Service	520
Z. & I. Aero Service	æs,
Ltd	513

SHORT WAVE MAGAZINE

(GB3SWM)

Vol. XXII	NOVEMI	BER, 1	964			No	253
	CONT	ENTS					
							Page
Editorial		•••			•••	•••	523
Receiver Pre-Selecto	r Unit, by M. A. S	Sandys	(G3BC	3J)	•••		524
Screening the TV Re	ceiver, by E. Carr	(G3SI	DE)		• • •		525
Realities of Beam Ac	erial Gain, by B. S	ykes (G2HC	G)			526
Latching Relay Cha							529
Do You Know That	· · · · · · · · · · · · · · · · · · ·				•••		529
LF-Band Phone Tra	nsmitter, by W. S	tephen	(GM3	IVZ)			530
Amplifier-Clipper-Fil		dulatio	on,	•••	•••		532
Heavy Mast Erection by C. R. Plant,	on, A.M.Inst.E., Assoc	c.I.E.E	. (G5C	P)	•••		535
"SWL" - Listen	er Feature						537
Calibrating the G	rid-Dip Oscillatorson, A.M.I.E.E.)	•••		•••	540
Small-Current Meas	urements, by G. A	. W. P.	artridg	e	•••		542
Communication and	DX News, by L. H.	I. Thor	nas, M	.B.E. (G6QB)		544
Notes on Mobile Aer	rials, by W. Farra	r, B.Sc	. (G3E	SP/M)			550
VHF Bands, by A.	J. Devon			•••			553
The Month with Th	e Clubs-From Re	eports					556
Identification Letters	s, Alphabetically, f	or Clu	bs in N	MCC			561
The Other Man's S	Station—G3JDK	•••		•••			563
New QTH'S .							564

Managing Editor: AUSTIN FORSYTH, o.B.E. (G6FO/G3SWM)

Advertising: MARIA GREENWOOD

Published on the first Friday of each month at 55 Victoria Street, London, S.W.1. Telephone: Abbey 5341/2 Annual Subscription: Home and Overseas 42s. (\$6.00 U.S.) post paid

© Short Wave Magazine Ltd.

AUTHORS' MSS

Articles submitted for Editorial consideration must be typed double-spaced with wide margins on one side only of quarto or foolscap sheets, with diagrams shown separately. Photographs should be clearly identified on the back. Payment is made for all material used, and it is a condition of acceptance that full copyright passes to the Short Wave Magazine, Ltd., on publication. E.&O.E.

Come and join the

ROYAL NAVAL RESERVE COMMUNICATION BRANCH

and make the most of your spare time



Bribling traces as a second se

Men between 16 and 26 and women between 17 and 40 may join. Those with previous experience of this branch of the Royal Navy may by accepted up to the age of 45. Training takes place 2 or 3 evenings a week with opportunities for occasional visits abroad.

You will not be out of pocket

as Pay, allowances, bounty and uniform are provided.

Besides professional training there is ample opportunity for social and sporting activity giving you the chance to meet people with the same interests in a friendly atmosphere. There are numerous Wireless Training Centres throughout the United Kingdom.



Write for full details of this interesting service to:-

ADMIRAL COMMANDING RESERVES, MINISTRY OF DEFENCE, LONDON

or ask at your nearest Royal Naval Careers Office.

EDITORIAL

Miniaturisation

This is one of those words which, even if it is ugly and un-English, is very expressive and does not require to be explained to any radio man. Except perhaps in one particular sense.

Aus his both,

For it does not only mean equipment designs made physically small simply by bunching everything together, to a greater degree than has been accepted practice in the past. It means making full and proper use of modern parts, and especially transistors, so that much less space is taken up without troubles such as interaction and over-heating. In the field of miniaturisation, we are well served for most components—not only an excellent range of valves, but also condensers, resistors, coil packs and mountings and fittings such as jacks, knobs, dials and switches. The only exception seems to be power supply components; it is still necessary to provide a good deal of space for even a modest HT unit if it is to be kept within its ratings.

However, in spite of the potentialities of miniaturisation, in Amateur Radio circles full advantage has not yet been taken of all the possibilities. One still sees a great deal of homeconstructed equipment, larger and heavier by far than it need be, which could have been scaled down to something much neater, lighter and more compact with no loss of efficiency.

Some of the latest commercial designs, on the other hand, are excellent in these respects. and show what can be done by the proper use of modern components and constructional techniques.

While among radio amateurs there are some superb craftsmen, capable of turning out handbuilt work up to the highest standards of electrical and mechanical design, the majority of us have not yet really got down to this business of miniaturisation in the way it should be tackled for our particular requirements.

Here, indeed, is food for thought and an interesting field for constructional activity during the months of semi-darkness now before us.

WORLD-WIDE COMMUNICATION

RECEIVER PRE-SELECTOR UNIT

COUPLED THROUGH
TRANSMITTER TANK CIRCUIT
—INTERESTING
CONTINUOUS-COVERAGE
TUNER

M. A. SANDYS (G3BGJ)

THE simple double superhet described by the writer in the March, 1964, Short Wave Magazine was unusual in that it utilised the transmitter pi-network as the first RF tuned circuit. This fed, via a cathode follower, the grounded-grid RF stage of the receiver. The arrangement worked admirably but suffered from some minor shortcomings which were attributed mainly to a lack of front-end selectivity. The circuit, therefore, was modified to include an extra signal tuned circuit. In its new form, as a pre-selector which is an integral part of the transmitter, it may appeal to the home constructor as a simpler method of improving the front of his receiver than building a separate unit.

The Pre-selector

Fig. 1 shows the circuit of the pre-selector and the relevant portions of the transmitter and receiver.

One half of an ECF82 acts as a pentode RF amplifier and the other half as a cathode follower to feed into the receiver. A neutralised triode or grounded grid stage was originally considered for V1A but ease of modification dictated the choice of the noisier pentode. Its use does not appear to have impaired the performance of the receiver on the higher frequencies. The extra gain, however, caused some cross-modulation effects to appear. To reduce these the original 100 $\mu\mu$ F coupling capacitor from the pi circuit was replaced by a 30 µµF Philips trimmer (C1) and the capacity reduced until interference of this type was indiscernible. A beneficial side effect of this was to cure an annoying defect of the original circuit, namely that on the higher frequencies the tuning of the pi circuit for transmission did not quite correspond to the setting for optimum reception. The pi circuit is coupled to the pentode grid by relay contact A1, this contact earthing the grid when transmitting. The relay coil is in the anode circuit of the driver and operates when the Tx HT is switched. The complete circuit of the transmitter itself was described

Table of Values

Fig. 1. Circuit of the Pre-selector by G3BGJ

```
15,000 ohms
100,000 ohms
Osmor QO4
Osmor QO2 (link
        C1 = 30 \mu \mu F Philips
                                                                      R6
                     trimmer
        C4
C5
                   .01 μF
300
                                                                      1.2 =
                                                                                 removed)
250v. 50
                    300 \mu\muF two-
gang (see text)
16 \muF, 350v. elect.
                                                                  MR1
                                                                                                50
C6, C7
R1
R2
                                                                                  rectifier
6.3v. 1.5A heater
transformer
                   1 megohm
47,000 ohms
270 ohms
47 ohms
              =
                                                                                 ECF82
```

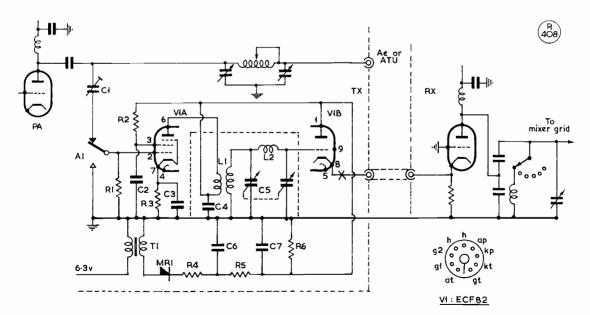


Fig. 1. The pre-selector designed by G3BGJ to work between the transmitter tank circuit and the receiver which, in his case, has a grounded-grid RF stage. The circuit could, however, be used with any receiver having a low-impedance input. The circuit elements L1, L2, C5 constitute an all-band tuner (see text) covering from 3.5 to 28 mc without any coil change being involved. The sketch at Fig. 2 shows how the bands appear on the tuning dial. This circuit configuration is used in commercial practice to obtain all-band coverage.

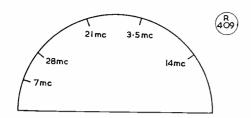


Fig. 2. This sketch shows the sequence in which the amateur bands come up on the all-band tuner L1, L2, C5 shown in Fig. 1. The only precaution to be observed when setting up the tuner is to ensure that no two bands can appear at the same setting.

in the October, 1962, SHORT WAVE MAGAZINE.

All-Band Tuned Circuit

The pentode anode is coupled to an all-band tuned circuit via the link on the low-frequency coil L1. For those unacquainted with this double-coil arrangement (now much used in commercial gear), the coil L2 constitutes a short circuit at low frequencies and L1 is tuned by the two sections of the ganged condenser in parallel. On the high frequencies L1 may be regarded as an RF choke and L2 is tuned by the two sections in series. By suitably choosing L1 and L2 all amateur bands from 3.5 mc to 28 mc can be covered by one sweep of the tuning capacitor. The cores of L1 and L2 were adjusted to tune the amateur bands in the sequence shown in Fig. 2. The procedure is to set C5 to near minimum, peak L1 for maximum signal on 7 mc, then rotate C5 through about 20 degrees and peak L2 for maximum on 28

mc, repeating these operations several times. The other bands may then be tuned in to ensure that no two appear at the same setting. A two-gang condenser of 300 $\mu\mu$ F per section was available at the time of building and was used for C5, but one of 200 $\mu\mu$ F per section should suffice. A slow-motion drive is desirable for ease of tuning. The all-band tuned circuit is connected to the grid of the triode section, the cathode of which feeds directly to the grounded-grid stage of the receiver.

Power Unit

The original power supply, a half-wave rectifier fed from a heater transformer placed back to front, was found to be adequate providing about 90v. for the valve anodes. For receivers with little frontend gain higher voltages could be used on the anode and screen of the pentode. Replacing R5 by a smoothing choke would increase the HT to about 250v. An RF gain control might then be beneficial.

This pre-selector, whilst being a decided improvement on the original circuit, could be used to even greater advantage with some of the older receivers. When connected to the writer's R.1155 it transformed an almost dead 14 mc band into one full of readable signals. If used to feed the aerial link coupling of a conventional receiver, a small resistor and RF by-pass condenser in parallel should be inserted at point X. In some receivers, such as the R.1155, the aerial link may not go direct to chassis; an alternative in this case is to connect a 300-ohm resistor between V1B cathode and earth, the output being taken from the cathode via a 001 µF capacitor.

SCREENING THE TV RECEIVER


AGAINST TRANSMITTER
INTERFERENCE — USING THE
FARADAY LINK

E. CARR (G3SDE)

UPON acquiring a compact self-contained transmitter of a popular commercial make, the writer found himself bedevilled by TVI. This just would not respond to the usual treatment of low-pass, high-pass and mains filters, and became a problem for much discussion and head scratching.

The TV interference manifested itself in the form of break-through on Sound, and line breaking with patterning on the local ITV Ch. 10 whenever the

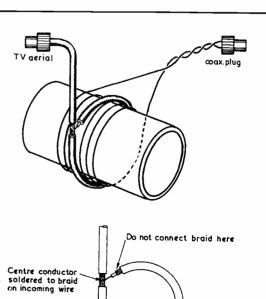This sketch illustrates the discussion by G3SDE, showing how a Faraday screen can be applied to the input of a TV receiver to minimise, if not eliminate, TVI. As this circuit is so easy to put together, it is worth trying, though the coil value may call for a little experiment, and a good deal depends on the level of signal at the TV aerial.



12

Tx was radiating on any of the three amateur bands 160, 80 and 40 metres.

The ITA station is only 15 miles away from the writer's QTH and the signal is exceptionally strong. Indeed, it was found that a short piece of wire plugged into the TV receiver gave very good results on Ch. 10 during QSO's but replacing the correct aerial and coax lead reintroduced the interference pattern. At this point it should be mentioned that BBC/TV on Ch. 2 did not appear to suffer. Consultations with the manufacturers of the TV and the transmitter did not give any clue to the cause of the bother.

Considerable investigations were carried out into the possibilities of how 10 watts on 1.9 mc could possibly give harmonics or other responses on the 199 mc band (Ch. 10) and attempts to overcome the difficulty included moving the TV aerial around, also the Tx aerial. Many different types of aerial couplers were tried without any improvement.

Solution

It was eventually discovered that by disconnecting the braid of the TV aerial the interference pattern was cleared—but of course the TV picture had a "ringing" effect, i.e. black outlines following white, and vice versa. This suggested that some better means of coupling into the TV Rx should be sought.

The coil unit shown here was found very effective in coupling the aerial to the TV set while isolating the Tx interference from the braiding. Although an old TV receiver is in use, the cure has been found effective and details are passed forward for the benefit of anyone who may have tried all the usual filter systems without success.

Naturally, it is not guaranteed to cure every case,

and of course the usual procedures should be adopted in tracing TVI—but it is offered as another weapon in the amateur's armoury for TVI difficulties.

The device consists of 5 turns of 22g. copper wire, polythene insulated, wound on a 2in. o.d. former and spaced about \$\frac{1}{2}\$ in. between turns; the ends are twisted together to form a "flex" and are terminated in a coax plug, one lead to the centre and the other to the shell, and taken to the TV/Rx input—see p.525.

Around the centre of this winding and over it is made one Faraday Link turn; this consists of a length of TV coax cable with the centre conductor soldered to the outer braiding of the incoming line at the point where the link completes one turn—see sketch. The loose end is fitted with a coax termination in the usual way to take the TV aerial.

It may be necessary to reverse the connections to the 5-turn winding and even to fit the Faraday Link in the opposite direction to that originally on the coil. Some experimentation with turns direction and coupling may be required to arrive at the condition which gives a clear picture. Incorrect phasing of the coil assembly results in the TV picture showing the "ringing effect" and the negative images which are characteristic of mismatch and standing waves on the aerial feed line.

The unit should be mounted in an insulating box—a metal container is not recommended as the metal work tends to permit the interfering signal to by-pass the isolator. Orientate the RF coil to avoid pick-up from the scan coils around the tube base, or the TV screen may exhibit a vertical white line along the left-hand side. Keep the twisted leads from the coil as short as practicable and mount the assembly as close as you can to the aerial socket on the Rx.

REALITIES OF BEAM AERIAL GAIN

WITH PARTICULAR REFERENCE
TO THE E-M-E PATH

B. SYKES (G2HCG) (J-Beam Aerials, Ltd.)

THE advent of Moonbounce is a reality for the amateur rather than a dream has only been brought about by recent improvements in the performance of equipment. The Moonbounce path is completely unforgiving in terms of performance—unlike the early amateur short-wave experiments when the results exceeded the apparent realms of possibility. The earth-moon-earth path is nearly half a million miles, and the attenuation over this distance is a constant, and is accurately known. The reflection co-efficient of the moon is also

accurately known, and there are thus no short cuts to the performance required. Transmitter power is limited by regulations, and is accurately known. Adequate receiver performance is relatively easy to obtain and the limitation here is cosmic noise rather than performance capability. The remaining requirement is adequate aerial gain, and this inevitably works out to a figure in excess of 20 dB over a half-wave dipole. The gain of an aerial is very often an unknown quantity taken on trust! Anyone who has studied aerial theory is able to form his own conclusions as to the possible gain of a given aerial, but many people have to rely upon published information with no means of checking the figure claimed.

There is one basic rule with aerial gain figures, namely that to double the gain of an aerial, *i.e.* to add 3 dB, it is necessary to double the size of the aerial. This basic rule applies in almost every case. For instance, stacking two identical aerials increases the gain by 3 dB, or doubling the length of a Yagi increases its gain by 3 dB, while adding reflectors to a stack of dipoles also increases the gain by 3 dB. This provides a very simple rule-

of-thumb method of checking up on published gain figures.

Some Facts

Commonest of beam aerials is the Yagi and the gain of a Yagi is governed by its physical length, rather than by the number of elements used. This is a most important point to remember. A typical example is the use of the long-Yagi technique, with directors spaced at 4λ . Using this technique 13 dB of gain over a half-wave dipole can be obtained from ten elements on a boom length of some two wavelengths. An aerial using 20 elements could be manufactured on this same boom length of two wavelengths, but its performance would not exceed the 13 dB obtainable from 10 wide-spaced Bandwidth would perhaps be made greater with the additional number of elements, but overall gain is basically limited by the length of boom.

Basic fact is, therefore, that every additional 3 dB of gain means doubling the size of an antenna. This very rapidly results in the "law of diminishing returns" when beam design is considered for an earth-moon-earth project for a gain in excess of 20 dB. That 20 dB may well necessitate a system measuring 12ft. x 12ft. x 12ft.; increasing the number of elements in this 12ft. cube will not increase the gain, and there is no way around the fact that to get 23 dB will mean an aerial measuring 24ft. x 12ft. x 12ft.

Finally to measure the gain of a large E-M-E aerial array is very difficult indeed. It will normally be made up of a large number of units, and if the gain of each of these units is accurately known, the gain of the whole array can be calculated. A useful basic aerial for a 2-metre moonbounce array is the 10-element Long Yagi, having a gain of 13 dB over a half-wave dipole. Utilising the fact that each 3 dB of additional gain means doubling the size, two 10-elements will give 16 dB, four will give 19 dB, and eight will give 22 dB—which is about the minimum to ensure results on the earthmoon-earth path.

Stacking and Aperture

The next basic fact that has to be swallowed is that there is a *minimum stacking distance* between two aerials, and this may perhaps be understood


Our contributor is, of course, a recognised authority on VHF beam design in the protessional with the context, knowledge. experience and resources to carry his ideas through to practical effect. Recently, some most improbable (not to say improper) claims have been made in the literature on the subject of beam gain. This article discusses the basic facts from which there can be no escape, and also explains the practical difficulties involved in measuring the gain of full-sized systems. -Editor.

when the aperture of an aerial is considered. Aperture is directly proportional to gain, meaning the greater the gain the larger the aperture. This can be quite literally represented by imagining an infinite sheet of metal between transmitter and receiver with the gain of an aerial represented by a hole in the sheet. The greater the gain the larger will be the hole, and obviously if it is required to increase the gain by the use of two holes then it would not pay to allow them to overlap—thus, the optimum distance is that which just allows the apertures to touch, and in the case of the 13 dB 10-element Yagi this is 11ft. The E-M-E array, made up for convenience as nine Yagis in three rows of three, will therefore be 22ft. square to the centre of each cross boom—quite an erection!

Returning to the basic aerial for a moonbounce array it is of vital importance that the efficiency of this unit be high in terms of the ratio of gain to amount of material used. Any inefficiencies here will be multiplied by the number of aerials used, resulting in a larger array than is really necessary—and as we have seen even a fully efficient E-M-E array is quite a mighty pigeon perch.

Gain Factor

The gain of an aerial is normally expressed in dB over a half-wave dipole. The very term dB is an expression of ratio, and any figures published without this qualification of gain over a half-wave dipole should be treated with extreme suspicion since the figure is thereby meaningless. The figure of gain over a half-wave dipole is obtained simply by substituting for the aerial under test a half-wave dipole and noting the difference in gain. This sounds very simple, but when a number of tests are under-

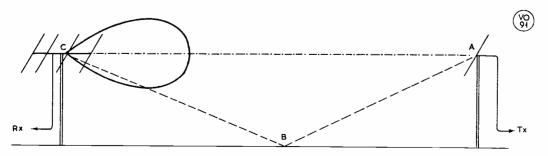

Sketch to show the confusion that can arise, due to multi-path interference (ABC), when attempting to evaluate the gain of a VHF beam system. In fact, there are considerable practical difficulties in setting up a VHF testing range—see text for discussion.

taken on the same aerial in different locations results are found to differ wildly.

There are many sources of inaccuracy in aerial gain measurement, probably the greatest being the difference in propagation characteristics of the aerial under test, and the dipole which is to be substituted for it. The dipole may be receiving not only the direct signal but also a reflected signal from the ground which could be out of phase, causing cancellation and an apparent reduction in dipole performance. On p.527 is illustrated a typical test set up with the shape of the radiation pattern of the test aerial superimposed. It will be seen that in addition to the direct signal path between the two aerials AC there is a reflected signal path ABC. The phase relationship of these signals will be a function of path length or frequency and the reflected signal may augment or diminish the signal received. In this case, however, the sharpness of the radiation pattern of the aerial under test will result in a considerable reduction in intensity of the reflected signal, which will thus have little effect. When, however, in an attempt to measure gain a dipole is substituted for the test aerial, there will be little or no attenuation of the reflected signal, and an entirely misleading reading of the dipole will be obtained.

Test Problems

Hence, the problem is not so much that of measuring the performance of the test aerial, but of measuring the performance of the dipole with which to provide comparison.

The amount of space required for an accurate testing range is quite large and measurements made using normal dipole substitution methods on inadequate ranges only result in misleading results. The main requirement is that there should be no reflections or if reflections do occur the path length shall be similar to that of the direct path. Similar path lengths can only be achieved by spacing the aerials quite a large distance apart, and keeping them reasonably low down. A simple formula for this spacing is: $R=4D^2/W$, where R is the spacing and D is the largest physical dimension of one aerial and W is the wavelength in use.

Pursuing the fact that the most difficult part of the measurement is that of the dipole itself it is very advantageous to use an aerial of known gain for substitution instead of the dipole. Considerable effort can be expended on measuring the gain of this known aerial, which typically could be a 6-clement Yagi with a gain of 9 dB over a half-wave dipole; 9 dB is approaching the theoretical maximum for six elements, and any test results or published gain figures in excess of this should be ignored.

There are of course other methods of measuring gain which minimise the problems mentioned here. A very well-known one is the measurement of beam width from which gain can be calculated. This should, however, be treated with a considerable amount of reserve, since no allowance is made

for losses in the aerial itself and these can be quite considerable at VHF and UHF. As a matter of interest, and bearing on this problem, a method employing two identical test aerials has been developed by the writer's Company, and enables the actual substituted dipole performance to be computed, thus providing an accurate source of comparison. This method is beyond the scope of this article, which is intended to bring out the problems involved and to explain the facts.

THE AMATEUR LICENCE FIGURES

We are informed by the Post Office that by September 30, there were 10,899 amateur "A licences in issue in the U.K.-these are the full all-band radiating permits that most of us hold. In addition there were 114 "B" licences, which are in the G8AAA sequence and for UHF phone only (obtainable by R.A.E. without benefit of Morse test), making a nett total of 11,013 U.K. amateurs licensed to be on the air. Included in this figure are the 1,721 amateurs who hold "A" permits to work mobile—surely a most remarkable increase in the /M interest. There are also 168 licences out for ATV (likewise UHF only), for which callsigns are (or will be) in the G6AAA/T sequence. Looking at the basic figure of 10,899 "A" licences, the nett increase in the four months since May 31 is only 216. Where do all these chaps who pass the R.A.E. go? Is Subject No. 55 simply an educational stepping-stone or an intellectual objective? In point of fact, the answer is of no consequence-because obviously so many individuals must be taking, and passing, the exam. for the simple reason that they have a practical interest in radio communication. Which is a good thing for its own sake.



The Hammarlund HQ170A-VHF is a new general-coverage receiver which takes in all amateur bands from two metres to 160m., including the 6m. band. The VHF ranges are covered on separate nuvistor front-ends, designed to ensure sharp front-end sensitivity, the figures for 2m. and 6m. being 0.3 µV for a 10 dB signal-noise ratio, with an IF rejection at 145 mc of better than 70 dB. The dial arrangement gives expanded vernier tuning on VHF and the Rx will take AM, CW or SSB signals.

LATCHING RELAY CHANGE-OVER SYSTEM

INTERESTING CIRCUIT USING NORMAL RELAYS

R. A. BUTTERWORTH (G8BI)

S/Ldr., R.A.F. (retd.)


HERE is a circuit which could possibly be of interest and use to many readers, for a variety of purposes. The writer came across it when a requirement arose for a quick change-over from "Main T/R" to "Std./By." There are Latching Relays available, but there were two snags—price and insufficient contacts on one relay. At least eight were needed at G8BI.

The basic circuit is shown in the diagram. This was hooked up using two 12v. relays, RLA and RLB, having 4 + 4 c/o, and one 12v. 2 + 2 c/o RLC, with one pressel switch Sw1. It never failed to operate and all who saw it were fascinated and would have played with it for hours!

Operation is as follows: When Sw1 is pressed RLA operates, RLA-1 closes; RLB cannot function at this moment since positive voltage is applied to it. Immediately Sw1 is released, however, it does go over and changes RLB-1 over to bring into circuit RLC—but not into operation since no volts are applied.

At the next pressing of the switch, RLC is energized, closing RLC-1 to earth and bringing the whole circuit back to normal.

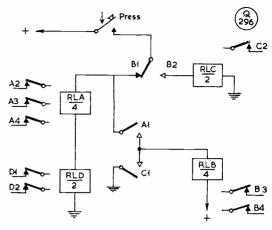Eight circuit change-overs were wanted, and two,



Relays RLA-RLD all 2500a

The relay layout devised by G8BI and explained in his article. Operation of the pressel switch is all that is required for change-over. Each of the relays is of 2500 ohms DC resistance.

RLA-1 and RLB-1 having been used, another relay RLD was put in series with RLA and the voltage increased a bit. Thus was obtained change-over of two microphone lines, two audio lines, three operational lines and one lamp indicator, to show which equipment was in use.

No doubt those who work with relays will recognise the circuit as a counting relay system, as used in landline circuits. To the best of the writer's knowledge it is not well known to amateurs, so is offered in the hope that it may be of use to those with a complicated change-over problem. Anyway, it is worth spending a few minutes hooking it up and trying to make it mis-fire!

Do You Know That-

— Small brass paper fasteners pushed through the holes in peg-board (or ordinary hardboard), with the prongs opened out, make very good tag-panels, or mountings for transistor equipment. For better insulation where required use Paxolin strip with holes drilled. (G3KIA).

—— Beams and outdoor aerial assemblies generally can be protected against the weather by giving them liberal treatment with rubberised car under-coating. This is flexible to a certain extent and can be peeled off when necessary. (G3KPO).

— The brass valence rail as sold by Woolworth's at about 1s. 2d. a foot is well suited to making handles for equipment. The edges are ready rounded, and it is strong enough for most applications. Bends should be formed round dowelling of suitable diameter, and the brass then painted over with a clear plastic varnish. Valence rail of this type is also ideal for making small aerials, such as a halo for two metres. (G3TFR).

When winding coils that are required to be specially rigid (such as for VFO's) it is a good idea to put the former in the refrigerator and the wire in the oven before making the coil. As the materials attain normal room temperature, the windings tighten, producing a "stay-put" job where it is most wanted. (GM3BN).

The improved absorption wavemeter indicator (M. H. Judd, p.472, October) can be made even more sensitive by connecting a DC supply in series with the miniature neon. If this is set at just less than the striking voltage, only a little RF is needed to produce a glow, with a further improvement in sensitivity. (G4LU).

— Aluminium tubing of 17g. is a sliding fit in the $\frac{1}{8}$ in. sizes—for instance $\frac{3}{8}$ in. diameter tubing will be a sliding fit into $\frac{1}{2}$ in. tube, and all $\frac{1}{8}$ in. differences can be used similarly. This is very useful for beam aerial adjustment and the construction of telescopic masts. (G3JEQ).

A small reward of 10s. 6d. is paid for any item we can print under the D-Y-K-T heading.—Editor.

LF-BAND PHONE TRANSMITTER

PRACTICAL DESIGN FOR

/A, /M OPERATION

W. STEPHEN (GM3IVZ)

AFTER acquiring a BC-454 Receiver (3.5-6 mc) and completing the necessary modifications to get it operational, the writer decided to construct a transmitter of similar dimensions to operate /A.

A look through the junk box produced an RF-24 case and a chassis and front panel were fabricated to suit this case. The SHORT WAVE MAGAZINES accumulated over the years were scrutinised and the circuit by F. G. Rayer, G3OGR, in the October 1963 issue was selected.

The alternatives mentioned in his article were adopted, viz. an RF choke in the anode of the buffer when operating on Top Band; an EF91 used as the buffer-doubler; the variable resistance in the screen supply to the buffer-doubler was omitted. For metering the PA current, a 100 mA meter is plugged into the cathode.

It was planned, and has been so wired, that an OA2 regulator valve would be used for stabilization of the oscillator HT, but this has so far not been found necessary.

A centre-tapped speaker transformer is used as a choke in the modulator and the valves are ECC83 for speech amplifier, and EL84 for modulator. The

Table of Values

Circuit of the Choke-Control Phone Tx


```
27,000 ohms
100,000 ohms
22,000 ohms
                         25 μμF, VFO tune
75 μμF, VFO set
                                                                                  R9
   C8, C10
C5, C6,
C13
                                                                                                5,600 ohms, 2w.
2.2 megohm
47,000 ohms
                          .01 μF
                                                                               R14
R15
R16
R17
R18
                                                                     R12,
R13,
C7, C9
C11, C12
C14
                          100 μμF
.002 μF
                                                                                                100,000 ohms
1,500 ohms
                          ^{.002} \mu F

^{250} \mu \mu F


^{500} + ^{500} \mu \mu F,

BC gang type
                                                                                                1 megohm
220,000 ohms
                                                                                                1,200 ohms
10,000 ohms
2.5 mH RF choke
       C16,
C16A
, C18
C19
                          16 μF, 450v.
.005 μF
                                                                                R 20
                                                                              ŔŦĊ
                          .005 μF
50 μF, 12v.
68,000 ohms
33,000 ohms
                                                                                                (see text)
EF91
                                                                           V1, V2
    R1
R2, R6
                                                                                  V3
V4
                                                                                                5763
ECC83
                                                                                          =
                          2,200 ohms
    R3, R8
```

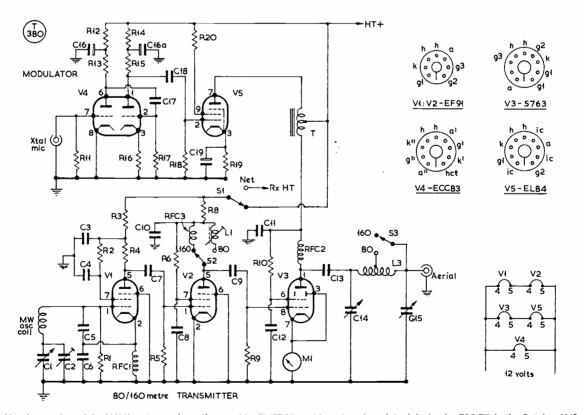Notes: The modulating choke is a centre-tapped speaker transformer primary, such as the Radiospares EL84 output type. Metering is in PA cathode, with a test point in the EL84 mod. cathode, using an 0-100 mA meter. The RF choke could be substituted by a tuned circuit if drive is insufficient.



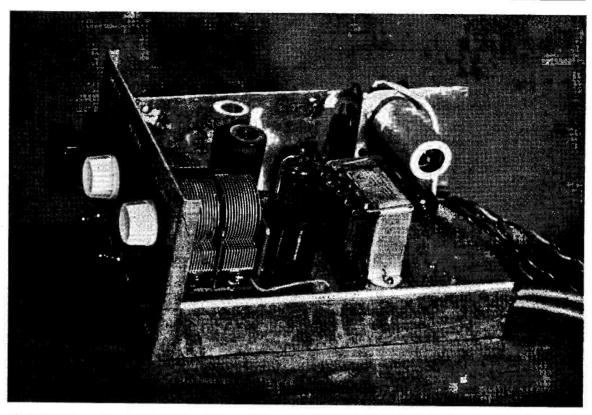Circuit complete of the 80/160m. transmitter discussed by GM3IVZ, and based on the original design by G3OGR in the October 1963 issue of "Short Wave Magazine." It can be built up in a very compact form and, as shown here, is giving very good results on both LF bands. The photograph suggests some constructional details.



The LF-band transmitter described in the article by GM3IVZ. This view is on the PA side of the chassis, showing the tank coil, output loading condenser, and the modulating choke (actually the primary of a speaker transformer), with the 5763 PA valve and buffer-doubler stage V2 alongside. The modulator is on the sub-chassis and the VFO behind the screen.

valve heaters are wired in series-parallel to work with a 12-volt supply, thus: two EF91's in series, EL84 and 5763 in series, and the ECC83 takes 12 volts.

When operating from AC mains, a silicon rectifier is wired into the power lead to the ex-19 Set relay with a 100 μ F 25-volt working capacitor to chassis. The 12 volts for the heaters is obtained by using 6·3 volt and 5 volt in series, which gives it near enough.

For /A or /M operation, a coil former for a centre-loaded whip was made from a 3in. o.d. plastic bottle with a 1in. dia. perspex rod through the neck and out via a hole in the base, and then held in position with Evo-Stick. The ends of the 1in. dia. rod were drilled and reamed to take the ends of the whip sections.

Coils used in the transmitter were a medium-wave type oscillator coil for the VFO, and for L1, a \(\frac{3}{3}\)in. dia. cored Aladdin former filled complete length with 30g. enamelled wire. The PA coil L2 was 70 turns of 26g. enamelled on a 1\(\frac{1}{4}\)in. dia. former, tapped about the centre for 80 metres.

This transmitter has worked very well for the writer on 80 metres from fixed and portable sites, running 12 watts input with 1½ mA of grid drive. Reports have given good quality with plenty of modulation. No traces of frequency modulation

have been reported. Operation on Top Band has proved equally successful, using a transistor converter for 160m. reception. The general set-up is shown in the photograph above.

DECEMBER R.A.E. SITTING

At certain centres, a sitting for the Radio Amateur's Examination—Subject No. 55 in the City & Guilds of London Examination syllabus—is being held on December 10. Those taking it should by now have their applications in. We wish them luck and hope to see many more new callsigns come through as a result. The main examination will be in May next year, for which a large number of candidates are preparing.

SOLD BEFORE HE SAW HIS COPY!

A reader with a Small Advertisement in the September issue of Short Wave Magazine—Flt./Lt. Pain, whose adv. was on p.445 of that issue—writes to say that he disposed of the gear before he had even seen his advertisement in print! We do not suggest that this is what always happens, but it does show that if you have something worth offering at a reasonable price, you are pretty sure of disposing of it quickly and easily through our Readers' Small. Advertisement section.

AMPLIFIER-CLIPPER-FILTER FOR BETTER MODULATION

TRANSISTORISED UNIT FOR GOOD AM PHONE

C. E. DEAMER (G3NDC)

IT is well known that the only useful power radiated by a transmitter is that contained in the sidebands, and that the sideband power is determined by the modulation percentage. Also it is generally recognised that a 100-watt transmitter modulated 100 per cent is equal, in communication effectiveness, to a 400-watt transmitter modulated 50 per cent and causes less heterodyne interference. In these days of crowded amateur bands these facts are of considerable importance and have led to a great increase in the use of single sideband, with the improvement it offers in communication efficiency.

There are, however, still a large number of amateurs who prefer AM for 'Phone working and for this reason numerous articles have appeared dealing with circuit techniques for increasing mean modulation percentage. These invariably describe systems which, if employed with an existing transmitter, reduce the overall modulator gain and since in the writer's case there was very little gain in hand it became apparent that any system employed must introduce no less and should preferably increase the available overall gain.

The transmitter at present in use at G3NDC is a K.W. Valiant which has given very good service for a number of years. It was felt that, rather than modify its existing circuitry, a general-purpose unit should be developed which could be connected externally, between microphone and modulator, with this and any other transmitter. This required that the unit should be small, so attention was turned to the possibility of employing transistor circuitry.

The amplifier-clipper-filter described here was produced for use with a crystal microphone and in addition to increasing mean modulation percentage gives an overall gain which is variable and, of course, dependent on input level since the clipping circuit limits the output to approximately 300 mV maximum.

Description of Circuit

The circuit diagram Fig. 1 shows the unit as now in use at G3NDC and although it is not essential that the same type of transistors be used, some care should be taken when selecting that to be employed in the first stage TR1 (OC201) since it is of primary importance that this stage should introduce as little noise as possible. The input impedance of a common-emitter amplifier stage is normally too low to be used with a crystal microphone but by the use of negative feedback the input impedance of the first stage has been raised to a suitable level. In this first stage the OC201 ensures a low noise factor.

Two stages of amplification TR2, TR3, follow and the gain of the first is made variable by feedback control on the OC44. It was found necessary to

Table of Values

Fig. 1. Circuit of the Transistorised Amplifier-Clipper-Filter

```
0.1 \muF

2 \muF

50 \muF, 6v.

1 \muF, 50v.

10 \muF, 15v.

100 \muF, 25v.

0.25 \muF, 15v.

0.20 \muF, 005 \muF

0.04 \muF

100,000 ohms

220,000 ohms
                                                                              820 ohms
                                                        R11 =
R12 =
R13, R15 =
R16, R20 =
R17 =
R18 =
                                                                              56,000 ohms
10,000 ohms
3,300 ohms
500-ohm, var.
 C2
C3, C9
C4, C6,
C5, C10
               _
        C7
C8
                                                                              270 ohms, ½-w.
8,200 ohms
                                                                  R 19
      C14 = C12 =
                                                                              950 mH, Mullard
                                                                   core
L2 = 167 mH. Mullard
        R1
R2
                                                                              core
63 mH, Mullard
                                                                   1.3
        R3 == R4 =
                     33,000 ohms
                                                                                core
                    68,000 ohms
4,700 ohms
2,200 ohms
                                                                  Tr1 = OC201, Mullard
R5 = R6, R21 =
                                                                  Tr2 = OC44, Mullard
                                                                  Tr3 = GET-103, G.E.C.
        R7
                     1,000-ohm, var.
R9, R14 = R8 =
                                                                  Tr4 = OC77, Mullard
                    1,000 ohms
22,000 ohms
                                                         D1, D2, D3 = OA6, Mullard
                    15,000 ohms
       R10
```

Notes: Resistors can be rated quarter-watt, except as stated. Inductors L1, L2, L3 are wound on Vinkors LA-2303 cores. Any equivalent transistors may be used for Tr1-Tr4 and for diodes D1-D3, but the *Mullard* OC201 is recommended for Tr1.

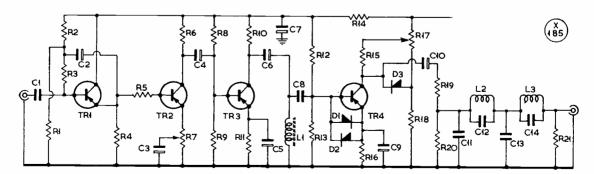


Fig. 1. Circuit of the unit described by G3NDC, performance curves of which are shown in Fig. 2. It can be made quite small (see photograph) and is intended to insert between the microphone and the first stage of any existing speech amplifier. An essential requirement is that the unit should be sufficiently well boxed in to prevent any RF pick-up from the transmitter with which it is being

employ two stages in order to get the signal level high enough to obtain satisfactory clipping.

The amplified signal is then clipped by the following stage TR4 which can be adjusted to give symmetrical clipping by means of the balance potentiometer R17, Fig. 1.

The filter C11, L2/C12, C13, L3/C14 which follows the clipper removes unwanted harmonics and also limits the overall response to that shown. It will be seen from Fig. 2 that the low-frequency response of the filter does not fall off very rapidly but that of the complete unit overall does. This is brought about by the supplementary effect of the low values used for C4 and C6, together with L1 and C8.

The unit was constructed on a piece of *Veroboard* and housed in an aluminium box 4in. x 5in. x 1½in.


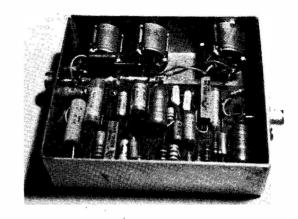


Fig. 2. Curves derived from the circuit of Fig. 1. At (A) is the response of the filter section alone (see text), while (B) represents the response overall. These curves are in good agreement, and the unit covers an adequate audio pass-band for speech—see text.

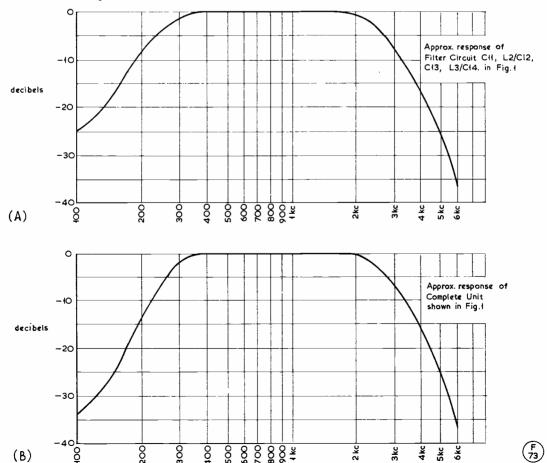The amplifier-clipper-filter unit as described and constructed by G3NDC. The circuit is shown in Fig. 1, and measured performance curves in Fig. 2.



and the general layout is as shown in the photograph. The filter inductances L1, L2, L3 were wound on Mullard Vinkors type LA-2303 to reduce the size and to allow them to fit in the available space.

Any form of construction may be used and the layout presents no real problems since the overall gain is quite small. Care should be taken, however, to ensure that RF cannot get into the box as this will cause feedback, positive variety.

Setting Up

When completed and connected to any existing AM transmitter it will be found necessary to reduce the gain of the modulator from that normally employed. A signal should be applied to the input of the unit at approximately 1000 cycles—either by using an audio frequency oscillator or by whistling into the microphone—and the gain control R7 adjusted until the modulation does not exceed 100 per cent regardless of the level of the input signal.

Symmetrical clipping is most easily set up by using an oscilloscope, but a fair approximation can

be reached by monitoring the radiated signal—preferably at a distance and with the help of a co-operative local amateur—and adjusting the balance control R17 for best quality, in conjunction with the gain of the modulator itself. The setting is quite easily found and will not normally require readjustment even with a change of microphone, although in this case it may be necessary to re-set the unit gain control, R7.

Power Supply

The power supply need only provide 15 mA at 12 vols, or any other conveniently available voltage up to a maximum of 20 volts although some adjustment of R18 may be necessary to obtain symmetrical clipping. The power supply at present in use at G3NDC is a battery which is connected only during "transmit" periods. If the unit were built into a transmitter a power supply would probably be more conveniently derived from a rectifier fed from a low-voltage transformer winding, provided the output was well smoothed, using 500 µF condensers.



The Green & Davis 70CM100 is a tripler-amplifier for the 430 mc band, rated at up to 90w. input, depending upon what PA valve is fitted (to customer requirement). Both tripler and amplifier stages are blown, and all 70-cm. circuits are formed by parallel lines, screened for better efficiency and mini: aum radiation. Both stages are metered, a heavy-duty coax relay is fitted for aerial change-over, and all metai-work relevant to the output frequency is heavily silver-plated. Construction is on a copper chassis. The 70CM100 is intended to be driven from any suitable two-metre transmitter.


HEAVY MAST ERECTION

USING A LEVER-BOOM FOR
A 55-FOOT STICK

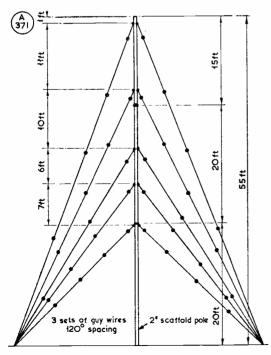
C. R. PLANT, A.M.Inst.E., Assoc.I.E.E. (G5CP)

IT is a fallacy to assume that an aerial mast some fifty feet in length, complete with a three element tri-band beam and a five element 144 mc Yagi and associated drive mechanism, can be easily built and as easily erected. However, with careful planning and preparation, the assistance of local club members and a great deal of hard work, it can be done. Such a mast was recently installed at G3ZY, near Chesterfield, Derbyshire.

Two pieces of wood 12ft. 6in. x 7in. x 2in. were fastened together, spaced at 6in. by 2in. diameter tube, using ½in. galvanised bolts 1ft. long. This tabernacle was buried 5ft. in the ground to form a rigid base; the heavy clay obviated the necessity for concrete filling. The lowest section of the mast is made of 2in. diameter mild-steel tube and the remainder is in similar section standard aluminium scaffold pole; all the fittings for joining the lengths together and securing the mast in the



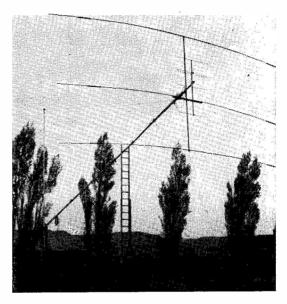Mast dimensions and guying system in the G3ZY layout, as described in his article by G5CP—and see photographs.



Hanging between earth and heaven—the G3ZY beam assembly on its 55-foot mast, just before hoisting. This was done by using the lever-boom technique, hauled on by block-andtackle for the heavy work.

final position are standard scaffold erecting items. The sketch shows a general layout of the mast and the points of connection for the guy wires; these are all $\frac{1}{8}$ in. diameter semi-stiff galvanised wire, similar to that used by local Electricity Authorities for small-pole tensioning. All the guy wires were cut to length, insulated and fixed to the mast prior to the aerials being fitted.


The mast hinge is simple and effective—a 5in. length of 1in, steel tube is slipped over the top \(\frac{1}{2} \) in. bolt of the base structure and over this a similar length of 2in. tube. The latter is clamped solidly with the vertical tube which forms the mast in the same fitting, thus allowing the whole to hinge freely on the inner tube and bolt.

Raising


A boom 20ft. long, of 2in. scaffold pole, was next mounted at right angles to the mast 8ft. from the base using a standard scaffold fitting and to the remote end a complete set of guy wires was tensioned—a temporary guy was also taken from this point to the base of the mast (this being removed after the mast had been raised into position). A flexible steel rope was also taken to the end of the boom and firmly fixed and then passed through a block and tackle, the latter being secured to a convenient tree located immediately behind the mast position 5ft. above ground level. With the remaining guy wires loosely fastened to their respective anehorages and with a man positioned at each point, the mast was raised to a height of 8ft. and rested on a tripod

support. The aerials and ancillary equipment were then fitted and all was ready for the big lift! An extendable ladder was pushed under the mast and with some effort the remote end was raised to a height of 15ft.—at this point four men commenced pulling the cable attached to the block and tackle, thus taking the strain. allowing the ladder to be extended and the lift increased. After several lifts and repositioning of the ladder, the boom haulage was able to take full control and the mast was pulled into a vertical position where it was secured.

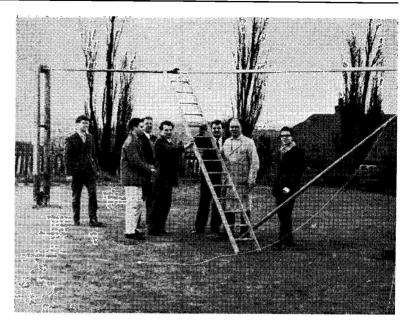During the whole of the lifting process the guy wires at 60° and 300° were manually tensioned, progressively, to keep the mast straight; the importance of this cannot be over-emphasised. At the first attempt one of the top guy wires slipped and the mast came down to the ground—fortunately the boom tension controlled the fall and little damage resulted and (after the fright) a second attempt was



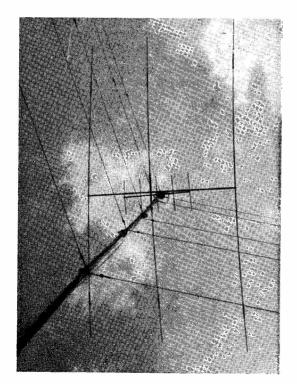The ground-crew standing by to start the erection of the G3ZY mast—see article. The lever-boom method, with block and tackle, was used for hoisting. This is very effective and perfectly safe provided that all materials are strong enough for the job, the hoisting guys are correctly measured off—and all concerned know exactly what they have to do.



The G3ZY system in the vertical, and before final adjustments had been made to the guy-wire turnbuckles. The diagram shows the guy-wire layout—more than adequate for the job.

completely successful.

Results obtained by G3ZY on 14 and 21 mc fully justify the work put into this project—and it has also been used as a vertical radiator on Top Band, tuned by a variometer at the base, with outstanding success. The Chesterfield Amateur Radio Society provided the necessary man-power for the raising operation and the total cost to G3ZY, excluding aerials, was £34.

GET THE OTH RIGHT

Most every day in every month we tussle with addresses that can only be read by guess and signatures that are totally illegible. In this office, hours are wasted checking through gazetteers to establish whether your name could be Bossock in Chagford or Bostock in Chalfont. And if in the end we get it wrong, it is entirely your own fault! So, when writing in to SHORT WAVE MAGAZINE, about anything at all, please scribe your name and address clearly—and if you have a callsign, put it in plain capital letters (so that, if necessary, we can check in the Call Book). And speaking for the Post Office, the correct address for all amateur licence matters is: Radio Services Dept., Radio Branch, Amateur Licensing Section, G.P.O. Headquarters Building, St. Martin's-le-Grand, London, E.C.1.

5 W L • • • • •

"ESCALATION"—NEWCOMERS—JOYS OF CW
— HOW THEY STARTED — THE COMING
SEASON—HPX LADDER MOVEMENTS

ONE of the factors that makes such a feature as this rather difficult to compile is the constant "escalation" of its readers. (That rather horrid word is the only one to describe the situation briefly.) They join us at the bottom of the stairs, so to speak, and gradually improve their own standing until they reach the roof and leave us, cheerfully waving a QSL card with their newly-acquired callsign as they depart.

Those who are keen on the competitive side of things also join us at the bottom of the "HPX Ladder" and are usually a goodly way up by the time they leave it. Some—bless them !—don't leave at all, but become dyed-in-the-wool listeners with no intention of going for a transmitting licence.

The point is this—how does the compiler of a feature like "SWL" cope with the technical side of things? A couple of years back we dealt pretty exhaustively with many of the things an SWL wants to know: Aerials, tuning units, receiver frontends, converters, the conception of a modern receiver, Q-Multipliers, How to QSL and all that. And now we have a bunch of new readers who need the same all over again; and at the same time we have the old hands who know the basic stuff inside out and want something more advanced. This, of course, they can get from other articles in the MAGAZINE.

Fortunately there are many who are quite content to see "SWL" as a bi-monthly summary of what goes on, and what the SWL's are doing. One, this month, is kind enough to write "I am pleased to see that 'SWL' improves in content and interest with every issue" (and thank you kindly, John Fitzgerald of Great Missenden!) And certainly the volume of mail is such that there is no difficulty in filling the allotted space by merely using the more useful comments from readers' letters . . . which, it appears, is what the majority like to see, anyway.

So we will continue doing just that, leavening it where possible with technical gen., and referring back to some of the earlier numbers for details. (New readers can obtain several of the back numbers still.)

Newcomers

This month sees more new faces, so to speak, than ever before, and a lot of unfamiliar names appear at the lower end of the HPX Ladder (and even some a good way up).

R. de Buis (Felixstowe) joins the CW Ladder, and reports that he mastered CW by the very

method we recommended—"switch on that receiver and listen to everything." He now finds that he can read callsigns at 35-40 w.p.m., although his full copying speed is much lower. Pet aversions—those signals from Eastern Europe that sound like something from a bird sanctuary, and those who call very long CQ's and get blotted out when they come to the more important part — their own callsign. (SWL de Buis queries the TJ8 prefix, but it is quite in order—Republic of Cameroon).

Chris Freeman (Nuthall) has been held up by GCE QRM, but is now out to get the prefixes, and joins at the bottom of the ladder. He uses an 870A and an R.107, with a Joystick and ATU, also an outside wire for the LF bands. He asks if /P and 5M stations count for HPX—they don't!)

Another "joiner" is W. J. Angerson (Leeds), 14-year-old owner of a home-brew TRF four-valver; he can copy SSB on it by using regeneration, after a little practice... and it must be tricky, too. He asks if "YA6ZA" is genuine, but we don't think so—was it YU?

Victor Rix (Swindon) writes in for the first time, although he has been with us since Vol. 1 No. 1 (in 1938). He regrets the old days of the 'thirties, when quite primitive gear would bring in the VK's... whereas now, with all the advanced technique, better components and all, we find ourselves listening to a load of QRM... for which one can only blame "progress" and the increase in population. And he believes in improving the signal where it matters most—so he uses a good aerial.

David Griffiths (Ilford) joins with an HPX figure of 155, all on an ordinary 7-transistor radio using an untuned long wire; quite a bit of DX in his list, too.

N. Roberts (Cambridge) says he has been listening hard for seven months, "punctuated, though not interrupted, by A-level Exams." He has a 52 Set and copes with both phone and CW, but hopes for something more selective and going higher than 15 mc in due course. R.A.E. coming up in December!

Iain Mackay (Dingwall) shifted his interest from philately to listening to commercial stations on an old pre-war BC set. Duly infected, he bought an HE-30 and set about things in earnest, now covering six amateur bands. He queries the HPX rules for stations like VE1AJR/SU... and that is simply an SU; /MM's count separately, provided that their prefixes are all different; and OHØ is not only a different prefix, but a different country—Aland Is.

David Richmond (Alloway) comes in with a score of 239, collected on six bands AM and SSB with a Hallicrafters S.38, a 132-ft. wire with ATU, and a ground-plane using the ex-Government kit, as described in the June, 1964, SHORT WAVE MAGAZINE. He is $15\frac{1}{2}$, and started eighteen months ago with an old BC receiver.

D. H. Foster (Rainham) is 13 years old and runs an R.107, with a 132-ft, wire for the LF bands and a ground-plane for Twenty. He is keen on CW, because he finds that exotic prefixes can be winkled

out when the Phone portion of the band is virtually dead—and that's a pretty good reason.

Christopher Pedder (Preston) has an unmodified R.1155L, connected to a 14-mc dipole with coax. He was justifiably surprised, therefore, when he casually tuned Eighty one evening and logged W1 and W2 (W1FRR was 5-and-7). SWL Pedder became interested about eighteen months ago, and three weeks after becoming thus infected, he put his name down for the R.A.E. (on the last day!). Yes—he passed. He now queries a "doubtful" FK8BC, speaking French on Twenty SSB, 0800; we should say this one was genuine . . . why not?

D. W. Chappell (Axminster) sends in a list, but it proves to be of callsigns, not prefixes! (Imagine 119 prefixes on One-Sixty—gave us quite a start!) Prefixes, Don, are the bits that go before the callsign—the letters and figures. Thus all G3's count the same; but G4's are different, and so are GM3's or GC3's, and so on . . . we hope you have got it now.

Douglas Watts (Staines), listening on a 4-valve portable covering Medium and Long, hears stations on both Top Band and Eighty if he puts a biggish aerial on the thing. "Images," of course, and, we presume, from pretty strong and quite local stations. But when it comes to identifying two "tone" signals on the 10-metre band, we give up ... there seem to be masses of them if the band is open.

All the foregoing correspondence came from readers who wrote in for the first time, many of them quite new to these columns. We like to see it.

The Regulars

J. E. Hart (Leeds) asks two queries, both of which have been answered in foregoing replies . . . and he adds that he is now awaiting a CR-100 and a Codar preselector.

John P. Fitzgerald (Great Missenden) fills a long letter with many points. One of them is that the lack of sunspots is barely noticeable—a little selective and intelligent listening brings in all sorts of DX. One of the happy hunting-grounds is the section around 14100-14120 kc, where, almost any night around 2230, you will find some quite rare prefixes (he also heard PJ3, HC1, HP1 and T15, higher up the band, all in a few minutes). As soon as Ten opens up, SWL Fitzgerald proposes to buy, or build, some new gear; at present he can only copy AM, and if one thing is pretty certain it is going to be that Ten will be the happiest hunting-ground of them all for SSB.

Terry Popham (Exeter) added 46 prefixes recently, despite a stay in OE-land on holiday. He comments on the excellent openings for SSB on Fifteen—especially to the Caribbean and Central American area.

More Points about CW

This hoary old CW-versus-Phone argument (it has been rumbling round for the last 40 years) usually ends up in a slanging-match, but it is

interesting to see new points of view. An unusual one comes from R. Hunter (Kenton), who says "CW does have the disadvantage of not indicating a person's nationality by his accent, as on Phone. For example, an early-morning watery note could be an out-of-skip G or West European station, or it might come from Hawaii."

Pete Cayless (Exeter) cracks back at those who have insisted that CW will get through when other modes fail, by saying that it is therefore less of an achievement to log DX stations on CW...one can find them in profusion when the identification of a weak AM phone is quite difficult.

Yet again, there are those who look on this extra ease of logging DX (or, later on, of working it) as a just reward for their perseverance in mastering the Code in the first place. And it is a remarkable fact that nearly all those who dislike, or decry, CW are those who can't read it and don't look as if they particularly want to try.

Briefs

"Many days the 20-metre CW band is jammed by all the USSR 'WSEM' boys furiously swapping numbers at 35 w.p.m. Maybe they enjoy sending numbers, but from a listening point of view . . ." (R. Hunter, Kenton). "Just because you have passed an exam. and can bash out 12 w.p.m., it doesn't necessarily mean that you have the ability, experience and sense to track down an elusive one. A few years with receiver-only can't hurt anybody, and I'm quite sure that any licensed amateur who has been an SWL for some length of time will agree that the experience and knowledge is useful" (Pete Cayless, Exeter).

"My CW prefixes are steadily mounting up, but I am not trying to notch up the 150 in as little time as possible; instead, I try to copy as much of the QSO as I can—this makes for better practice and speed" (Phil Holliday, Nottingham). "At the time of writing, the 80-metre band on SSB is beginning to look interesting. W1's were audible here at 0001 GMT during August, and VE1WI was also coming in . . . 5 & 7, or even 8. The Central New England Net is held on 3842 kc at either 1800 or 0930 GMT every day." (Derek Rogers, Wrexham).

"I think I owe my high score (600) to my good QTH here—I am situated at the top of a high hill, and even though I have a poor aerial, I hear a lot of DX. (Also, it is a great help having the gear at the bedside—you can listen at very odd hours!)" (Ray Williams, Birmingham).

"I get most of the more exotic DX stations when I listen to the G's calling them—sometimes they come back" (R. S. Finley, Kenton). "Anyone with no outdoor space should not hesitate to erect an indoor aerial. I have found mine really no handicap as an all-band aerial, provided that there is correct matching to the receiver. On this 100-ft. long wire, ZL's are being heard on 80-metre SSB during the early morning sessions; but most of my time is spent on Forty, and just about all the stuff

worked by the U.K. group has been heard." (J. R. Daws, Leeds).

Interesting note from one of our most experienced SWL's: Roy Patrick (Derby) reports the appearance of JPIAH and JPIKAE, both active on 14 mc CW from Mongolia, their QSL address being Box 60039, Ulan Bator. This is in the difficult Zone 23 area, and will be of great interest to many DX operators and listeners.

Barry Curnow (Plymouth) says "I was overjoyed to see that I had at last fulfilled a lifelong ambition in reaching the top of the HPX Ladder on CW." And he is now in the double-DXCC category, having passed the 200-countries confirmed mark. During the summer, Barry and two SWL friends did a 2,000-mile tour through the Lake District and GM, meeting scores of amateurs who had been heard on CW and phone; a most successful trip, by all accounts. And he adds, modestly, "Even my O-Level results turned out very well, so with major exams. over for a couple of years, and more time for DX, I certainly have nothing to complain about just now"! And he's still at the top of that CW listing.

A. Pardoe (Stourbridge) has started at London University, so will not be able to do any more

HPX LADDER

(Starting January 1, 1960)

Qualifying Score-150

Quantying Scote—130							
SWL PREI	TIXES	SWL	PREFI	XES			
PHONE ONLY		P	HONE ONLY				
A. W. Nielson (Glasgow)	657		er (Westcliff)	255			
R. J. C. Coats (Cowie)	637	J. P. Fitz	gerald				
R. Hunter (Kenton)	609		Great Missenden)	254			
R. Williams (Birmingham)			ting (Birmingham)				
L. Margolis (Ilford)	579	I. A. Mac	kay (Dingwall)	240			
T. R. Popham (Exeter)	547		hmond (Alloway)	239			
S. Foster (Lincoln)	536		e (Gainsborough)	239			
B. Curnow (Plymouth)	511		ephens (Hove)	233			
P. Etheridge (Hull)	470		rmee (Reading)	220			
D. A. Whitaker (Clitheroe		J. E. Har		212			
A. H. Pardoe (Stourbridge			ley (Harrow)	208			
D. A. Pickup (Preston)	456	H. Wolto:					
C. N. Rafarel (Poole)	448		(Cambridge)	204			
K. C. Staddon (Stroud)	447		r (Morden)	196			
P. A. Cayless (Exeter)	447		(Chesham)	190			
M. Vincent (Cheltenham)	441		(Morden)	188			
P. Baxter (Winchester)	428		iday (Nottingham)				
M. Healey (Horsham)	391		er (Spalding)	171			
M. Woellin (Leeds)	381		(Wrexham)	170			
C. Crisp (Maidstone)	355	C. Dillon		164			
M. English (Yeovil)	348	D. Griffitl		155			
M. J. Summers		N. Robso	n (Corbridge)	154			
(Market Harborough)			gerson (Leeds)	154			
C. Pedder (Preston)	326	C. Freema	an (Nuthall)	150			
A. Stone (Kidderminster)	325		CW ONLY				
J. R. Daws (Leeds)	298						
C. Whaley (Cambridge)	292		w (Plymouth)	547			
A. F. Roberts			(Kenton)	538			
(Kidderminste			liams (Winchester)				
D. C. Parker (Redditch)	285	V. Lindgr		356			
J. L. Pearce (Basingstoke)	279		nt (Cheltenham)	339			
B. G. Hamilton (Belfast)	276		(Horsham)	286			
M. Shaw (Bromley)	271		s (Felixstowe)	195			
R. Turlington (Braunstone		P. Etherid	ge (Hull)	188			
D. H. Foster (Rainham)	255	M. Wooll	in (Leeas)	150			

(NOTE: Listings include only recent claims. Failure to report for two consecutive issues of "SWL" will entail removal from the table. Next list, January, 1965 issue—deadline, NOVEMBER 27.)

SWL

continued

serious listening till the Christmas vacation comes round. But he hopes to "keep in touch with the bands" in the meantime.

Potted Histories

Most SWL's seem to start up in the same way. Here's a very new one, still only 14, who says his first efforts were on local stations with the BC receiver; then an H.A.C. One-valver; then a two-valve mains set; and now a CR-100 . . . and after this, what? (This is C. Dillon, Bath).

And then comes Lawrence Carter (Spalding), first triggered off by his friend Ian Buffham (who has now left us to try his luck on the bands with his own call). The start was a crystal set "which looked hideous and relied for insulation on Elastoplast" but which brought in Radio Moscow, Sofia and others on a moderate aerial. Then to a Philips domestic receiver, covering 13-50 metres, and then a new front-end to bring in 80 and 160 metres. And, more recently, an R.107 which, with a 70-ft. wire produces reasonable DX. (Still more recently, the R.A.E. passed, and the Morse Test awaited . . . a complete and typical "pilgrim's progress"!)

Mike English (Yeovil) used to be on the Ladder a long time back; he dropped out because of QRM from finals, but has now come back on again, with a better QTH and more room for aerials . . . but they will be used for other purposes, no doubt, as he passed the R.A.E. in May.

Laurie Margolis (Ilford) — one of the fortunate ones with an active amateur for a father — has set next May as his target, and hopes to get a ticket before his 15th birthday. He says that Fifteen is wide open to Central America, W4 and the like at 2230; the rig is now a Heathkit SB-300, with a Quad at 44ft. G3NMR intends to add the SB-400 (the matching Tx) to complete the station, but he has just acquired a Creed 7B page-printer, so RTTY is about to invade the household . . . It's all go and progress!

QRM Troubles

R. S. Finley (Kenton) has to pipe down during peak TV hours, since the oscillator of his Rx produces a harmonic that causes TVI. (He doesn't tell us what the receiver is, but some old HRO's with an acceptor circuit and a low-pass filter and says "anyone would think it was a Tx, not an Rx!"

In reverse, don't some TV sets radiate? We know of several cases in which interference from the harmonic of the line timebase generator produces patches of QRM every 10 kc, especially

Next appearance of this feature— January 1965. All correspondence and photographs (of SWL stations and equipment) by November 27, addressed "SWL," c/o The Editor, Short Wave Magazine, 55 Victoria Street, London, S.W.1.

on Top Band. In crowded areas this has become quite a problem, and, of course, a re-diffusion system doesn't help—if anything it makes it worse, because the noise can be re-radiated by the distribution cables.

Miscellaneous

SWL's who really want to make the best of their hobby are reminded that this is yet another winter for peak DX on the LF bands. One-Sixty, in particular, should be about as good as it has ever been—but the DX won't be of much interest to the "Phone-Only" men. CW from exotic parts may well be heard, even in the evenings . . . and the W's and VE's will be there most mornings between 0500 and 0800. Many SWL's will agree that there is a particular thrill about logging

American stations on this band. It's a challenge, anyway.

The DX season for Eighty is also upon us—and the "magic spot" is around 3800 kc, which is the boundary between the two worlds, so to speak. The W's are not allowed to use phone below 3800 kc, and we are not allowed to use anything above it! So most QSO's between the U.S.A. and Europe take place "across the wall"; the VE's are not so handicapped, and can work in our part of the band.

Contests — Top-Banders should look at the Club Notes for the gen. on MCC, which takes place on November 14-15. This is a case where SWL's can really be of help by putting in check logs (but, again, it's a CW event). And the CW half of the CQ Worldwide DX Contest will be on over the weekend of November 28-29 (the Phone half was in October).

The next instalment of "SWL" will appear in the January, 1965, issue, and the deadline for letters will be first post on *Friday*, *November 27*, addressed "SWL," c/o The Editor, SHORT WAVE MAGAZINE, 55 Victoria Street, London, S.W.1. Make a note of it, don't miss it—and we hope you all have many interesting happenings to report by then. Good Listening!

CALIBRATING THE GRID DIP OSCILLATOR

BY EXTRAPOLATION METHODS

G. P. ANDERSON, A.M.I.E.E. (G2QY)

MUCH has been written on that useful piece of equipment, the Grid Dip Oscillator, and the calibration is usually dismissed with some such phrase as "by comparison with a suitable receiver." But supposing no suitable receiver is available? For instance, a GDO may have been built as a means of adjusting 70 or 144 mc receiving equipment, and one is faced with the difficulty of "finding the band"; there are a few markers in these regions to use as guides.

The method to be described makes use of a general-coverage short-wave receiver, such as is to be found in the average amateur station, accurately calibrated over at least one of the ranges to be covered by the GDO. The only other equipment, apart from the oscillator itself and its coils—which must have overlapping ranges, a usual feature—is a separate tuned circuit, which may consist simply of a variable capacitor and a coil or coils; as will be seen later this is to be used as a reference during the calibration process, and need not be elaborate. As a guide, the coil for each range will be approximately the same size as the corresponding one in the GDO and hence one coil may be used, and the turns

reduced as calibration reaches higher frequencies; this will become clearer as the description proceeds.

For convenience, the frequencies to be referred to as examples will be those applying to the particular model used to prove the method, and they will not of course apply to any other unit.

First, it is necessary accurately to calibrate one of the lower frequency ranges of the GDO—for example, 8·8-15·3 mc. It is very convenient if this can be marked on the oscillator dial, but if it has only a 0-100 or 0-180 division scale it may be necessary to note the scale reading corresponding to say, every 100 kc step, and to draw a calibration graph. If possible calibrate the next range in a similar way. Again using the prototype as the example, this covers 14·2-24·7 mc; this step is not essential but serves as a useful check on the method. In fact calibration of one range only is required.

The next range commences at 22.7 mc, and its higher frequency limit will be in the same ratio to this as are the maximum and minimum frequencies of the other ranges; thus if x represents the highest frequency covered by the coil, and referring to

the accurately calibrated range, then $\frac{15.3}{8.8} = \frac{x}{22.7}$

(and incidentally $=\frac{24.7}{14.2}$) from which by simple arithmetic:

$$x = \frac{15.3 \times 22.7}{8.8} = 39.5 \text{ mc}$$

This coil therefore tunes from 22.7 to 39.5 mc, and calibration of intermediate points on the scale can be carried out by a similar calculation of proportions. For instance, to mark the 25 mc point we have to find the corresponding frequency on the 8.8-15.3 mc range; let this be represented by y, then

$$\frac{25}{22.7} = \frac{y}{8.8} \text{ or } y = \frac{8.8 \times 25}{22.7} = 9.67$$

Therefore, if we set the GDO dial to the 9.67 mc mark, we can draw a line on the appropriate scale to indicate 25 mc, or alternatively note the dial reading corresponding to this frequency. Similar calculations may be carried out for other frequencies to complete the calibration of the range.

Reference Circuit

Assuming that it is not possible to continue the calibration by comparison with a receiver, the next problem is to find the lower limit of the next coil, and it is here that we bring the separate coilcondenser circuit into use. With the next higher frequency coil inserted in the GDO, and its condenser all-in, i.e. set to the lowest frequency, adjust the separate circuit to resonance, observing the usual precautions exercised with Grid Dip Oscillators, namely to use only sufficient coupling between the circuits to obtain a dip indication on the meter. Replace the coil in the GDO by the next lower frequency—in our case 22.7 to 39.5 mc—and use the GDO to find the resonant frequency of the reference tuned circuit. It is obviously essential that the adjustment of the latter must not be disturbed during this operation, but again the degree of coupling should be only just enough to give a meter indication. In the prototype this frequency proved to be 36.4 mc, and applying the ratio calculation as before this gives a range of 36·4-63·5 mc for this coil. Calibration of other points in this range are carried out as described above, after which the lower frequency limit of the next coil may be ascertained by bringing the reference circuit into play again.

The Grid Dip Oscillator is inherently a rather approximate method of frequency measurement—in fact it is really more correct to refer to it as a means of frequency indication. But within these limitations, the method of calibration described does enable one to obtain at least a rough idea of frequencies in ranges otherwise not perhaps readily available by other means.

Use of Slide Rule

The calculations can be made easier if a slide rule is available, and a brief note is appended for the benefit of those not familiar with its use.

The simplest form of slide rule has four scales, two on the body of the rule and a corresponding pair on the slider; for convenience, these are usually referred to as the A, B, C and D scales, A and B being the upper pair and C and D on the lower half of the rule. There may be several other scales as well, but for our purpose we can ignore all but the C

and D ranges. The slide rule will also have a transparent cursor with a fine line drawn across it, and this is useful in setting up and reading off some of the figures.

In order to simplify the explanation of the procedure it is proposed to use the calibration of the 14.2 to 24.7 mc range in order to mark out the 22.7 mc "plus" coil. First set the cursor so that its hair line is on top of the 22.7 mark on the D-scale -that on the upper edge of the lower half of the slide rule—then move the slide so that 14.2 on the C-scale lies under the line on the cursor; that is, we now have 14.2 on the C-scale opposite 22.7 on the D. Examination of the D-scale opposite 24.7 on the C will show that the corresponding frequency, the highest frequency of this range, will be 39.5. Thus we see that while the C-scale represents the 14.2 to 24.7 mc range, frequencies on the coil range 22.7 to 39.5 mc lie in the D-scale, and the corresponding ones may be read off from it.

A slight complication occurs if we use the range 8.8 to 15.3 mc as the standard, owing to the C-D scales only encompassing one decade, *i.e.* 1-10. Having set the cursor to D 8.8, set C 22.7 beneath the line as before; the frequency corresponding to 25 mc may now be read off (9.67), but above about 25.8 we run off the D-scale. It is therefore necessary to transfer to the other end of the D-scale, by setting the cursor opposite 1 on the C-scale, and moving the slider so that C 10 falls under the cursor line, when the other points may be obtained; it will be seen that D 15.3 is opposite C 39.5. An alternative way is to use the A and B scales, which are marked as 1-100 with 10 at mid-point (or occasionally, especially on smaller rules, as two similar decades).



The PACO G.32 Sweep Generator is an FM Sig. Gen. with a basic frequency range of 3-213 mc in 5 bands overlapped, and the sweep width is adjustable over 0-30 mc at the VHF end. The application of the instrument (which is available in kit form) is in the alignment of wide-band amplifiers, and a marker-adder facility is provided to avoid misleading results.

SMALL-CURRENT MEASUREMENTS

ALLOWING FOR METER RESISTANCE — METHOD FOR AC READINGS

G. A. W. PARTRIDGE

VOLTAGE testing on most radio apparatus is usually quite simple. It is just a question of connecting a suitable voltmeter across the circuit and reading off the result. Current measurement has the disadvantage of having to break the circuit in order to insert a milliammeter. However, such work is carried out from time to time, especially in valve and transistor testing. Some of these currents are very small and therefore require far more sensitive equipment than the usual ammeter.

Fortunately in most radio work it is only small DC currents that need to be determined. Milliammeters and microammeters are moving coil instruments which are admirable for the purpose. Their scales are easy to read and for such sensitivity the prices are reasonable. Milliammeters cost about 27s. 6d. while the far more sensitive microammeters are approximately £2. Of course, these prices vary, especially on the surplus and second-hand markets, but this is a rough indication.

Multimeters are constructed around millior microammeter movements, so they can be used successfully for testing small currents.

Here again, there is a wide variety on the market. It is advisable to purchase the more expensive meters (not less than 5,000 ohms per volt DC) which have reliable milli- and microampere scales. The cost of such instruments could be from about £5 to £24.

Fig. 1 illustrates how a current meter is connected to a circuit. The internal resistance is very low so no appreciable loading of the circuit takes place under most circumstances. The following gives the approximate internal resistances of some current meters.

If, however, it is desired to know what difference the internal resistance makes to a circuit the procedure illustrated in Fig. 2 can be applied. The current meter is connected into the circuit in the cusual way and the voltage E measured at the point indicated with a high resistance voltmeter. Now the total resistance, that is the resistance of the load and the internal resistance of the meter, is found from:

$$R_{\rm t} = \frac{E}{I}$$
 where $R_{\rm t} = Total$ resistance;

E = Voltage, and I = Current in Amp_{δ} .

We now subtract the meter internal resistance and find the actual current that would flow in the circuit without the meter from:—

$$I = \frac{E}{R_1}$$
, where $R_1 = Load$ resistance.

Here is an example:

The current taken by a particular circuit was found to be 5 mA when 12 volts was applied to it. The resistance of the milliammeter used was 4 ohms.

The total resistance

$$R_{\rm t} = \frac{E}{I} = \frac{12}{5/1000} = 2400$$
 ohms.

The resistance of the circuit without the milliaammeter is 2400-4 = 2396 ohms.

The current that would flow when the milliammeter is out of circuit will be:

$$1 = \frac{E}{R_1} = \frac{12}{2396} = .00501 \text{ Amp.} = 5.101 \text{ mA}.$$

It will now be seen that the internal resistance of the milliammeter has very little effect upon the circuit. In fact it is small enough to be ignored. Therefore the reading on the milli- or microammeter can be taken as correct.

AC Current Measurement

The measurement of small AC currents does not often occur but there is the possibility that a small AC heater current may need to be checked or the

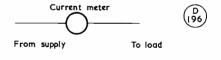


Fig. I. A simple current test

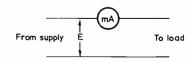


Fig. 2. Testing for Rm effect

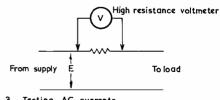


Fig. 3. Testing AC currents

Circuits to explain the points made in the text in connection with the measurement of very small currents.

current flow through an inductance or capacitance determined under AC working conditions. There are very few AC milliammeters available and most multimeters have no AC milliamp. scale. However, the problem can be overcome by inserting a noninductive resistance into the circuit and measuring the voltage across it (Fig. 3). A low-reading high-resistance voltmeter (not less than 1000 ohms per volt AC) must be used. The resistance value should be high enough to give a clear reading on the voltmeter. The current is calculated from:

$$I = \frac{E}{R}$$
 where $I = Current$ in Amps.; $E =$

Voltage across resistor; and R = Value of resistor.

An example: A voltmeter indicates 1.2 volts AC across a 30-ohm resistor. What is the current?

$$I = \frac{E}{R} = \frac{1.2}{30} = .04$$
 Amp., or 40 mA.

In order to find the current that would flow without the 30-ohm resistor R, first measure the voltage across the load at the point shown in Fig. 3. Suppose this reading to be 12.

Then the total resistance will be:


$$R_t = \frac{E}{I} = \frac{12}{40/1000} = 300 \text{ ohms.}$$

The load resistance R_1 will be R_t -R, which is 300-30=270 ohms.

The actual current that will flow without R will then be:

$$I = \frac{E}{R_1} = \frac{12}{270} = .044 \text{ Amp.} = 44 \text{ mA.}$$

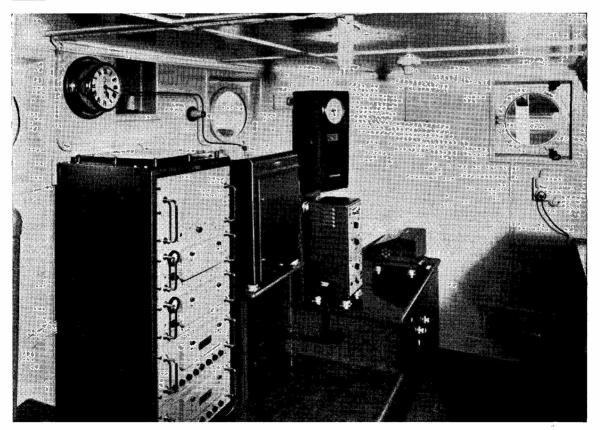These simple measurements will cover most current tests. A good valve voltmeter will enable small AF currents to be determined quite accurately in the same way.



In addition to their normal function of marking shoal water and dangerous channels by lights and sound signals, the lightships of Trinity House will in future also put out a radio beacon signal in the MF band, as a navigational aid. This is a typical installation, manufactured and installed by Redifon, Ltd. The transmitters are their Type G.142, giving 80w. output, designed for automatic unattended operation, controlled by a callsign sender and chronometer, and incorporating an immediate-alarm system in the case of failure of any of the units. The installation shown here will be in the ship on the East Goodwins, a notorious hazard on what is probably the most congested shipping lane in the world.

COMMUNICATION and DX NEWS

— L. H. Thomas, M.B.E. (G6QB)

AT the time of writing, Twenty is full of W6's, all S9 or more; W7's, VE7's and some WØ's are equally strong, and there is no European QRM whatever. Just a few Europeans are coming in, but weak and watery, and, for once, they all seem to have quite good notes. No lids, no chirpers or creepers.

Up in the phone band, too, there are only a few Europeans. Some of them, on SSB, are nice signals and easy to copy—but all the outstanding signals seem to be from W6 and 7. What has happened to the band? Have we reached the happy day at last, when the DX rolls in and the local QRM has vanished? Unfortunately, no . . . only one thing has changed. Your conductor happens to be writing this in Los Angeles.

To be precise, in W6EBG's "front yard," with a 3-el. beam 50 feet above his head and a blue swimming-pool alongside; and with 6,000 amateurs in the same city, within a radius of some thirty miles. Many of them are capable of punching holes in all that European QRM that we know and love so well (?). and a short drive around the hilly region to the North of the city reveals a few dozen beams, some of them real monsters.

Many of the local TV receiving aerials are just about as big as the average amateur beam in the U.K. -imagine clusters of TV aerials on top of a 60-feet steel lattice tower! But there they are. and a few of them must be 100 feet up. if the owners happen to be in a low-lying spot. The real amateur beams seem to grow everywhere, even in the centre of the city, and few small towns were passed through on our various trips pretty without seeing some ambitious ones.

Internal QRM in California? Well, worse than anything we have to suffer in Europe, but such

nice quality! No T6's, no bad chirps or clicks (unless a real local comes up, and then the whole band seems to tilt over, although very often the station being worked can still be copied).

If all our Eastern European friends were to be dumped in, say, W9 or WØ land instead of the stations who cause the present QRM, our W6 friends would probably not appreciate the change.

The sheer number of amateurs on the West Coast is incredible to the visitor from afar: About 6,000 in Los Angeles, and probably almost the same number in the San Francisco area; 3,000 or thereabouts in San Diego; nearly 1,000 estimated by W6AM to be in Long Beach (which is a smallish place, by Californian standards).

Although the really red-hot DX men constitute only about 1 per cent of the total (as they seem to do the whole world over), that gives quite enough tremendous signals to fit into one pile-up... and they do not use 150 watts (except in the exciter units)!

Among the top scorers the height race and the element-race is continuous. Beams seem to go up from 50 feet to 80, from 80 to 100, possibly having an extra element or two added in the process. Competition is of an intense nature that the average G simply wouldn't understand; even owners of 50ft, beams and full kilowatts look on themselves as small fry compared with the boys who put in those really fantastic signals when a "new one" is around . . . and anyone with an average G outfit-150 watts and a dipole or "piece of wire" would never even be heard when the pack is in full cry.

The DX Clubs (the writer had the pleasure of attending the meetings of three of them) include among their members many of the top DX'ers in the world. Any hint

of a DX-pedition or a new one and the whole place hums like a dynamo. VHF links come into operation, landlines buzz, tips are passed around—and at the meeting after all this activity, everyone reports on his luck. (And most of them, of course, worked the quarry before he escaped.) The sheer enthusiasm for DX for its own sake is terrific, and the results justify it. We came away with the impression that California is one vast DX-hunting machine of a most efficient type, and that the only fly in the ointment is that these types have mostly worked everything that's going, and require another DX-pedition every so often to bring them to the boil

Regarding our own signals . . . having listened to Europe on many consecutive days from W6-land, it can most definitely be said that it takes a really exceptional station ever to put in a signal there which compares in any degree with the W6's coming in the reverse direction. On the whole, the G's are rare; just a handful of them seem to come up with a good signal now and then, but mostly they are just plain weak, compared with DL's, OK's, OE's, UB5's and others. A question frequently met with is "Why don't we hear you guys?"

On some days it only takes a moment to decide that conditions to Europe are hopeless; on others a weak DL or two will alert an operator who, if he stays around, may work quite a few European countries before the band folds. (Most of these remarks apply to 1500 GMT or thereabouts—the morning session at 8 a.m., clock time, in Los Angeles, when the vast majority of W6's will have gone to work.)

Other quick impressions—the pleasure of seeing a familiar W6 call on the number-plate of a car in front of you; the amazement at

seeing W6AM's world-famous Rhombic Farm, bigger in actuality than one could imagine; W6YY's remote - controlled station on Mount Wilson, only reached after a 19-mile drive, naturally uphill all the way . . . and then a 6-element Telrex beam on a big, big pole at the top of the mountain; and, of course, the overwhelming kindness and hospitality with which a visitor is treated.

More of this later, we hope—there is much more to say about life in W6-land. But there is so much correspondence in hand for this month that we must come back to earth and deal with it. Meanwhile, just a heartfelt vote of thanks to the W6 gang, and especially to Gene, W6EBG, for the most enjoyable (and strenuous) holiday of a lifetime. Your conductor will never be quite the same again!

Top Band Topics

Time Marches On! Once more, a clarion call from W1BB on behalf of the traditional Trans-Atlantic Tests on One-Sixty. These have now expanded into World-Wide Tests, but to many they are still the original Trans-Atlantics, started in 1932 and continuing without a break except for the war years.

Dates: December 6 and 20; January 3 and 17; February 7 and 21. Set your clocks accurately, so that W/VE stations can call on the hour and every ten minutes thereafter, with the DX responding at 5, 15, 25 and so on past the hour.

The North American stations will use 1800-1825 kc (East Coast), 1975-2000 kc (West Coast). Europeans 1825 kc upwards, ZL 1875-1900 kc, VK 1800-1860 kc, and stray DX will crop up, as always, anywhere from 1800 kc.

Remember that these are Tests, not contests, and send your reports either to G6QB or to W1BB (preferably the former for all U.K. stations). Also be alert for unusual DX openings almost anywhere, as long as most of the path is in darkness.

Apart from such organised tests as these, there will be lots of DX forays to and from various places; but we have a feeling that the amount of DX worked will vary in direct proportion to the amount of sleep lost.

G3RFS (East Barnet) says he has been completely off the bands for some time, but now has a new Top Band aerial—a quarter-wave with a 60ft. vertical section, four quarter-wave radials and three shorter ones. He already has skeds lined up with ZS1, ZL, W6 and JA... last season he worked 32 W/VE stations, 22 countries and had SWL reports from EP, 5N2, VS1 and VS6, all on an aerial rather inferior to the new one.

G3SVW (Manchester) already has 10 countries to his credit, including W1BB, who was worked on September 6 (with a 132ft. wire only 25ft. high).

G3PAI (Ongar), who operated from Sark during the CQ 160-metre Contest this year, tells us that he intends to repeat the trip for the 1965 event.

GM3KLA (Haroldswick)— the "farthest North station in the U.K."—joins the select band at the top of the WABC Ladder with 98/98. He is the third GM to do so (GM3OM and GM3COV were the previous ones) and he points out that no GI, GW, GC or GD has

ever made it. It's interesting, too, to note that his WABC (60 counties) was achieved during his first year on the air, with a battery-powered rig—before the mains reached the island! Finally, 54 out of the 98 contacts were over distances of more than 500 miles . . . and Bill wants to thank all the stations, including many /P types, who made his final score possible.

G3PLQ (Salisbury) is probably off on his West Africa run again by now. During his leave he worked VE2UQ (September 13) and was delighted to have personal visits from G3GRL, 3PPU, 8AX, 3TSJ and 3JWH. He reports that ZB2AE will soon be active; that 9L1HX is already on, and that 9G1DV should be there by January. (The "OZ's" and "LA's" worked by G3PLQ and others were phoneys, and now it seems that G3PU landed a YU—almost certainly of the same ilk.)

A later letter from G3PLQ tells us that he is now aboard m.s. Kumba and bound for Takoradi and Lagos. Listening for G's at 2100-0001 GMT Mondays to Fridays, 2100 Saturdays and 0400-2100 Sundays.

ZONE-BAND TABLE

Station		Total Zones					
	28 mc	21 mc	14 mc	7 mc	3.5 mc	1.8 mc	Zones
G2DC	40	40	40	36	25	5	186
W6AM	36	39	40	37	23	9	184
G6QB	38	40	40	34	20	7	179
G3DO	39	40	40	28	24	2	173
G3IGW	36	38	38	32	18	11	173
G3HZL	27	39	39	28	14	2	149
OH3NY	32	30	40	25	10	7	144
G3NOF	34	38	39	10	8	1	130
G3PEK	2	21	35	30	17	4	109
G3RDC	3	14	38	11	3	1	71
G3IDG	20	23	17	3	2	2	67
G3OLN	2	7	11	16	3	4	42
G3PLQ	1	8	7	3	3	5	29

(Entries for this new table are invited; scores are postwar, i.e. starting from any time back to January 1946.)

Super-Pirate!

6Y5XG (formerly 6YAXG) had a couple of months in England and is now back in Jamaica, looking forward to a first-class season on Top Band. He was amazed when a pile of OK listeners' cards for 6YAXG turned up; at first very pleased, but when he found that none of them checked, very annoyed! As Peter says: "Someone actually had the audacity to use my call on Ton Band-should not be so touchy if he had kept it to the HF bands, but this is a bit much." He will be spending more time on 7 and 3.5 mc than on the HF bands, from now on. Look for him after 2300 GMT, around 3520-3525, 7010 kc (and on Top Band, 1800-1820). ORN has been high up to now, but the local thunderstorms should end in a few weeks.

The Cyprus Affair

Most DX-chasers will know by now that the old ZC4 prefix has reappeared. Apparently all the 5B4's outside the Sovereign Base Areas on Cyprus were closed down and had their gear confiscated (as reported last month), but from September 18 those within the S.B.A.'s reverted to their old ZC4 prefixes and kept the flag flying.

Unfortunately many people think they are pirates, and realise their mistake only when they hear others. ZC4GT says he understands that ZC4 now counts as a separate country, but we have no confirmation. G3HAL (Winslow) writes to say that he worked G3HHT using a ZC4 call, and he told him precisely the same. And G3NWT (Stapleford) says he heard SV5GB who, he thinks, must have been 5B4GB "on the threshold of an enforced QRT." He remarks on it as possibly "the world's first example of a reversion from a shocking numeral prefix to a sane and old-fashioned one." These ZC4's-who are, of course, all British Service personnel-have now clinched the deal-good luck to them.

Note from VS6

Rather strangely, our next letter is from VS6FO, who used to be a ZC4, but has never been a 5B4.

He is G3ICH, ex-DL2SU and ZC4PN, and now finds himself with "the poorest location on the island" for working the U.K. Being surrounded by hills up to 1,800 feet high, Pete has no great hopes for his DX-40, crystal frequencies and AR88, but he intends to try, starting with a dipole and progressing as circumstances dictate. We hope to hear and work him soon.

VU2GW, current.y very active on Twenty CW, writes with a few queries and tells us that he uses a Geloso VFO driving a pair of 807's with 100 watts input. He finds conditions rather poor and not helped by lots of the old DC fans, which his neighbours continue to use with metal rectifiers! Twenty is open to Europe almost daily, 1330-1600 GMT, and when the Quad, which is "taking shape" is finally in action, Ranga expects even more luck with the G's.

5Z4JD, Awards Manager for the Radio Society of East Africa, writes to say that the independence of Northern Rhodesia (Zambia) has been marked by a temporary increase in points value. From October 24 until December 12 (Zambia's Independence Day and Kenya's Republic Day respectively), cards from Kenya will count for two points, Zambia for eight.

Since Zambia is the sixth "ex-VQ" area to change prefix during recent years, a new award will be produced to replace the "Worked All VQ Areas" certificate; details will be issued as soon as it is finalised, but applications for the "WAVQ" will still be processed for some time.

Odd Notes

Interesting technique, reported by G3SVW:—"One of those long-drawn-out CQ calls the other day from a G3T - -. And he ended it with 'VA dit—dit.' No reply!" Perhaps he simply didn't want one?

G3IDG under fire from

G3SEN:—"I am always interested in the comments of G3IDG, but surely some are a little unnecessary? Is ours a hobby in which we please ourselves how we operate (up to a point), what mode we use, what band, and so on, or not? We are not in some sort of Secret Service in which all transmissions must be cut to the bare essentials, and 'the,' 'RST,' 'ur' considered irrelevant."

As for recent strictures on "BK," SWL Steve Gall (Old Coulsdon) surely has the last word. He sends a newspaper cutting with the headline "Break-In Method Kept Secret," which goes on to say that prosecuting counsel admitted "Even the police had never heard of it, but a carpenter would find it very simple." Actually the perpetrator was a carpenter, and he was put on probation for three years for "five break-in offences." Just watch it, some of you breakers . . .

G3OHX (Ashford, Middx) sends the following, with the permission of the amateur who made the comment: "Just come back from two glorious weeks in Devon and Cornwall with the YL, and it's nice to get back to the rig." G3OHX says this sentiment surely represents the ultimate in loyalty to Amateur Radio, but adds "The poor chap must be mad."

And G3JDK sends a story from behind the Iron Curtain (one of those "whispered-from-person-toperson" affairs): A Russian peasant, working in a forest, found a wire strung between two trees, and on the strength of his discovery he claimed the invention of the telegraph. About the same time, a peasant in Red China was planting rice and did not find any wires, so the Red China government claimed the invention of wireless. Oh, well . . . !

Around the Bands

And so to some DX! G2DC thinks the conditions are holding up remarkably well, and finds no

Reporting the HF Bands


difficulty in raising good DX at reasonable hours on at least three bands—7, 14 and 21 mc. The Far East has been really good on 14 mc during the afternoons, with 21 mc wide open to those parts in the mornings (0800-1000), for Africa and North America in the afternoons, and for South America in the evenings. Oceania has been bagged on 7 mc as early as 1730 and also from 0700-0830.

Jack has been overhauling transmitter and aerial for Top Band, too, and has been listening in order to get the swim of things on One-Sixty. (How nice if a few others would do this, too, instead of barging in without knowing what really ticks!) He was distressed to hear of a G using a pair of 813's in his PA for this band, which presages some acid comments flying around—not to mention some QRM.

G3HZL (Isleworth), who was QRT until last August, now has up a 33ft. vertical and uses it on all bands—to the tune of 55 countries in 22 Zones in five weeks. He says it is exceptionally good on Top Band, with eight countries and a 579 from OHØ. On the strength of this, he joins the Zone-Band Table, in what he calls his "usual middling position"!

GM3JDR (Golspie) has moved to 21 mc for most of his operations, and finds Africa most consistent but very hard to get, as they seem to have a permanent pipeline to the U.S.A. On SSB he raised a pile of ZS's, 7Q7, 9Q5, 9G1, 5H3, 5Z4 and the like, as well as quite a longish list on CW. On 14 mc CW he collected the Cambodia DX-pedition, W9WNV/XU, but never managed to hear him on SSB.

G3NOF (Yeovil) reports several openings to Africa on Ten, but says it's often necessary to listen for long hours to catch one of them. Fifteen, though, has been opening to the U.S.A. many afternoons around 1500, and on October 18 from 1200-1800. Things are definitely looking up! Twenty has been good for all areas, and Don quotes a few "specimen OSO's" with HS1I, DUIAP, W9WNV/XU, YAIAN, 4W1F, ZL1ABZ and such, as a

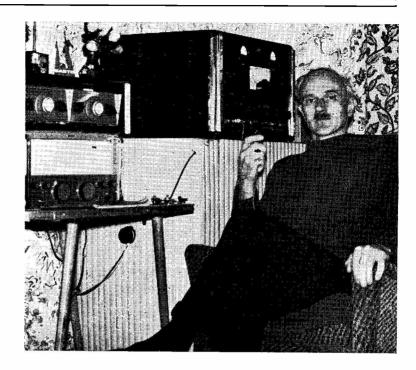

Now of 34 Birch Avenue, Romiley, Cheshire, G4HU was first licensed pre-war under the AA call 2DDM. After a varied experience, on the air and off it, he is now settled on 14 mc for CW and 3.5 mc for phone, operating after midnight because the local TV receiver time-base radiation blots out his Rx—TVI in reverse, in fact! The Tx is a PR-120V and the receiver an Eddystone 840C with a Codar PR-30X preselector and a Q-multiplier. For the HF bands the aerial is Mosley trapped dipole, with "a bit of wire" for 80m. G4HU's other hobby is fencing and, taking part in tournaments about the country, he travels | M.

measure of the conditions (all SSB, as ever). His most consistent signal has been VS9MG. And on Forty the VK's have been heard around 2000 most evenings, and VS9MG was also worked there.

Some more brief reports on Ten Metres: G3IDG heard VQ2DT, ZS6ADY and 5A3TL (all AM and round about 1700); G3OAD (Dudley) lost his 3-ele. rotary in a recent gale, but before that had worked CX's, LU's, PY's as well hearing 9G1, 6W8, South Americans and several Europeans: and **SWL** W. H. Gundill (Dewsbury) heard VQ2DT, LU4DM and CX1AAM.

A suggestion has been put up that, in order to promote more activity on Ten, interested operators should call CQ on the hour, 1600-2200 GMT, in the 28600-28650 kc region. (The same might go for the CW types, say 28000-28050 kc.) Excellent idea—please adopt it,

Contests and Suchlike

Coming events: November 28-29, CQ Worldwide DX (CW Half). Rules as usual, but remember that it now starts and ends at midnight, not 0200.

January 30-31: *CQ* Worldwide 160-metre Contest. As before, but fuller details will be given in the next two issues.

Results of the CQ (1964) SSB Contest will appear in full in our December issue, but a preliminary flash gives DL3LL as the outright winner in the All-Band category, with G4CP also in the Top Ten—the only G and the only other European to make it.

The 1965 French Contest, celebrating the 40th anniversary of the R.E.F., will be held on January 30-31, 1400-2100 GMT (CW half) and February 27-28, 1400-2100 GMT (Phone half). Three points per QSO with French and French-Colonial stations; multiplier the sum of French Departments and

DUF countries for each band. All stations sending in a log for a score of over 1,000 points will receive a special certificate for this Anniversary event.

Top scorers in the 1964 French Contest (all with over 20,000 points) were DJ5BV, UB5FG, YO4WU and YU1BCD. Topscoring G (out of only three entries) was G3EYN with 13,851. Longest entry lists came from UA, UB, OH, OK, SM and DL.

For the IOTA (Islands On the Air) Award, the following continental committee members have been appointed: Europe G3AWZ; Asia 4X4DK; Africa 5Z4ERR; North America W2BXA and

TOP	BAND	COUNTIES		
	LAD	DER		
Station	<u>Cc</u>	nfirmed	Work	

Station	Confirmed	Worked			
	Phone and CW				
G2NJ G3GGS G3NPB G3REA G5JM G6VC GM3KLA	98 98 98 98 98 98	98 98 98 98 98 98			
G3LWQ	96	96			
G3PLQ	92	95			
GM3IKD	86	90			
G3RHM	73	78			
G3NOW	72	81			
G3NLR	67	67			
G3PPE	60	72			
G3OJE	55	56			
G3IDG	51	56			
G3SWH	38	58			
G3SNU	37	59			
G3SJJ	36	71			
GW3ITZ	35	61			
G3SXW	23	45			
G3SVW	19	59			
	Phone only				
G3NPB	88	88			
G5JM	72	74			
G3RHM	69	70			
G3PLQ	55	58			
G2NJ	54	54			
G3REA	53	66			

(Failure to report for three months entails removal from this Table. New claims can be made at any time.) VE3CFG; South America CX2CO. (About as hot a "WAC" of DX'ers as you will ever find grouped under one heading!) The preparation of the Directory of Islands is now in progress, and the whole scheme will open on January 1.

It is some time since we mentioned the "Top People" in the DXCC Listings in QST; so it is nice to be able to record that G4CP and G3AAM are both in the very top bracket, with 311 current credits, and 335 including the "deleted" countries. Other G's very near the top are G2PL with 309/322, and G3FKM with 309/326. FB!

DX News from Everywhere

W9WNV/XU, during his brief stay in Cambodia, made 7,100 QSO's. His QSL's will count for DXCC, and of course the big thing (for the W's) about this DX-pedition was that the FCC legalised contacts with Cambodia, since the operator was a W with full permission to carry out the whole project. Don then proceeded to Vietnam (3W8) on the same basis, and fired up on October 20 with good signals into Europe at 1330.

Other imminent DX-peditions include one by G3NIR, who will be on from VR2, VR5, YJ1 and FK8. This was due to start on October 28, but should still be on by the time you read this.

K2HWL will be in Tahiti for some days when he goes there at the end of October . . . callsign FO8JL. VU2NR begins his trip to the Andaman Is., whence he will sign VU2NRA, around November 18. He will take his home-brew gear, and use a 3-ele. beam on a 100-ft. mast which is already in position on the island.

5H3KC, on 14 mc SSB, is DL9HF, who will be on as DL9HF/ZE in November. Thereafter he is liable to show up from at least a dozen African countries, possibly including Rio de Oro and Ifni, operating a transceiver on 14 SSB.

Norfolk Island: VK3TL will be signing VK9TL from this spot during January... Lots of activity from New Guinea, especially from VK9GC (14 mc CW). Also VK9BW (14275 kc SSB), VK9CJ and 9MM (7 mc CW) and VK9NT (14105 kc SSB).

Easter Island (CEØ): Activation promised by W4QVJ and W6UF, around December 1; CW at LF end of 80, 40, 20 and 15, SSB in various places on 40, 20 and 15. Film and tape recordings will be made, also a TV film.

For the WPX-chasers, some unusual ones: DU5DM, a Field Day station; YA3TNC, YS1HUKE (the year's most improbable callsign), and, of course, the first operation from Zambia (exNorthern Rhodesia) for which the new prefix is not known at the time of writing.

Aerial Gen.

Each month we receive quite a good selection of letters saying that the writers approve of the new format of this feature. Mostly they say that the news about what people are using, or doing, or just thinking, is more interesting to them than lists of Calls Worked, which tell one so little in these times.

So—it is felt that the time has come for a little research into aerial systems. How do the various types match up with the results that their owners are getting? What are the latest brainwaves being thought out, tried out-even thrown out? Did that freak thing that old G3 --- mentioned six months ago ever work? Why has the Top Band signal from so-andso suddenly increased by about 20 dB? Has he gone mad and installed a pair of 813's, or has he really found an aerial that does things for him?

Please let us know about all this, even if you are merely using a home-made Quad which only stays up there if the wind is less than five knots. This is one thing about which everyone talks, on the air, and it might well be extended into these columns.

As an example we have a "Late Flash" letter from G3NPB (Hexham) telling us that he, too, now claims the top score of 98/98 on the WABC Ladder — and we should like to know what kind of a wire he did it on . . . and the next letter is from G3PPE (Wallasey), who says that he and G3TKN

are experimenting with loaded "L" aerials for Top Band, with the object of obtaining both long-wire and whip characteristics from the one wire so as to work locals, GDX and "real DX" with equal efficiency.

Reverting for a moment to W6-land... the word seems to be getting around in the States that nothing is so good for DX as a Quad. After all, many of these "QRP" G's who beat the big DX'ers at their own game are using them. But—we didn't see a single Quad in California; just Yagi's, bigger, better and higher.

Yet a recent analysis of the DX-Kings' antennae, in one of the American publications, established that the Quad was without doubt the top scorer overall. What would results of a similar survey in the U.K. reveal? We would hazard a guess that there may possibly be more Quads than Yagis over here. (Meanwhile we find on returning that our own "piece of wire" is at zero-height at the far end, owing to the ravages of a gale which struck a week or so back . . . but it seems to work just as well in this position. But the look of the thing is so bad that the missing halyard must be replaced as soon as possible, just to soothe the nerves.)

More DX Shorts

Recent gleanings on *Top Band*: K4KYV, VE3AGX, W1BB, W2EQS, W2IU, W2KQT, K2GAL... all logged around 0430-0500. Known to be QRX—VK5KO, 1832 kc, 2000; VQ2W, every Monday, 2030-2115.

And on Eighty: CW—VK5NO (2000), VQ2DT (2000), ZL1AXB, 2AUA and 3OX (0615). SSB—Evenings, OX3WX, OY7ML, VP9BN, 5Z4AA, PJ2ME, VO, VE and W1. Early mornings, ZL2BCG, 3BG, 4LM, YV5ANS and 5BPJ, W5, W9 and WØ.

Forty: Evenings, MP4TBJ, VE1AJR/SU, VP2SC, VP8HU, 5Z4IV, 9Q5AB, BY1PK, OR4VN. Mornings, KC4USK, VK9RB, ZL4JF, W6's, VK3ZR, 6W8AJ. SSB: Evenings, JA2BTV, MP4BBW, VK's, 5Z4AA, 9M4LX, EP3HS. ZS1XX. Mornings, VK, ZL, T12SS.

All the above have been either



In August issue we showed a picture of G3PLQ in his sea-going capacity. Here he is in his own station at 32 Campbell Road, Salisbury. A very keen Top Band man, he worked a good deal of GDX on 160m. while home on leave during September. By the time this appears, he will be away at sea once more—and will be listening at DX for G's on Top Band. The Tx shown here is K.W.-160 (middle left), and the Rx an HRO Senior with bandspread, using a Codar PR-30X preselector.

heard or worked from the U.K. during the three weeks or so before writing.

Gus Browning should really be on his way to AC3/5 by now, probably having passed through London en route... Trinidade Is. (PYØ) operation is hinted at for the first week in November by PY2PE/Ø... YA1A, YA4A and DJ4EK/YA are all reported active, mostly 21 mc... Hammarlund are working on an operator to go to Heard Island (VKØ), late October or early November... HZ2AMS is back in Saudi Arabia and further DX-peditions to the Neutral Zones are expected soon.

The Tables

Note the new look of that Top Band Counties Ladder, with seven callsigns sharing the Top Spot of 98/98. Others have made it in the past, of course, and have "retired," but never before have there been more than three or four displayed in the top bracket. Where do they go from there?

A few recruits to the Zone-Band Table seem to appear every month; we hope this one will become more popular as DX conditions on all bands show an upward tendency.

And now—at last—for the new table: Ten-Metre Counties and

Countries Worked. We should like to start this one next month, with just the three columns: (a) Callsign; (b) U.K. Counties Worked; (c) Countries Worked, commencing date October 1, 1964. This will give some encouragement towards ground-wave and tropospheric working, we hope, rather than making it exclusively a DX list. If anyone ever achieves 98 British Counties on Ten, we shall be very surprised indeed! So send in your entries by next month's deadline.

Sign-Off

So much, then, for a pretty interesting month, despite a lowish level of conditions on the HF bands. Things will liven up from now onwards, especially on Top Band and Eighty; let us hear of all your activities by first post on November 16. Without long lists of Calls Worked, we should like to hear briefly of your doings and chief successes on each band; something about the Quads, Yagis and bits of wire responsible for them; and any general chat you may have. Address everything, by that deadline, to "Communication and DX News." Short Wave Magazine, 55 Victoria Street, London, S.W.1. The more the merrier; and, until then, Good Hunting, 73 and-BCNU.

NOTES ON MOBILE AERIALS

FOR TOP BAND—CONSTRUCTION, FITTING AND TUNING

W. FARRAR, B.Sc. (G3ESP/M)

IT has been said often enough that a transmitting station is only as good as its aerial, and this certainly applies to mobile operation. The whip used for the popular 160-metre band suffers especially due to its shortness compared to a normal quarter-wave wire, so to get other than mediocre results it is essential to get its efficiency as high as possible. There is a distinct lack of published information on the subject, and what has been published (mainly in the U.S.A.) seems to be based more on theoretical than practical considerations. (The outstanding exception is the well-known article "Resonant-Whip for Mobile Working on Top Band," in the June 1956 issue of SHORT WAVE MAGAZINE, this being still the standard reference on practical design and construction. -Editor.) The following notes are offered as a result of a few years of trial and error.

What is an essential requirement of any radiating system? Obviously, it must resonate at the frequency fed into it, and here many a mobile aerial falls short. There are those who get two or three whip sections, stick a coil in series and hook it to the transmitter, and are delighted to get an R4-S5 report from ten miles away. Others may buy a commercial model with similar results. But, to get only that report from that distance is by no means good, assuming that the car is not hemmed in by buildings. It is easy enough to build a suitable compact mobile transmitter (such as the Minitopper, described in SHORT WAVE MAGAZINE for August 1962)—but the most difficult part of a Top Band mobile installation is the making of an aerial which is truly resonant.

Whip Design

What is a loaded whip? It is effectively a tuned circuit, which should resonate at the operating frequency. The loading coil provides the inductance, and the rod above the coil the capacity to ground. Because a base-loaded aerial has a longer top section than a centre-loaded system of the same overall length, the capacity is greater, and so the coil can be smaller. Whether one uses base or centre loading is a matter of choice. It is generally conceded that a centre-loaded system is better than a base-loaded one, though some people get excellent results with the latter. It depends a lot on how it is mounted and fed. G3ESP/M uses an approximately centre-loaded whip, and a brief description of this follows, along with points of design which could apply to any other mobile aerial.

The mobile handbooks stress the absolute necessity of having a large diameter air-spaced loading coil. The difference between this inconvenient and bulky device, and a smaller, neater and probably stronger coil is not noticeable in practice. Thus one can use very satisfactorily a good quality coil former and a close-spaced winding. It can be long and narrow, and therefore less obtrusive than a large diameter type.

The writer's aerial consists of a bottom section of solid dural (ex-TV aerial) about 3ft, 6in, long, and a top section of about 4ft. 6in., being the upper and part of the middle section of a British tank aerial. The coil is wound on a hollow perspex former 7in. long by $1\frac{1}{2}$ in. in diameter, with perspex end plugs. The winding consists of 236 turns of 23g. enamelled copper wire, close wound, the winding length being 6½ in. The top section is permanently fixed into the end of the former, and one end of the coil soldered to it. The other end of the coil is soldered to a \frac{5}{8}-in. diameter threaded plug, which screws into a corresponding threaded socket fixed on top of the bottom whip section, making good electrical and mechanical connection. Thus most of the aerial can be removed (essential for garaging!) and carried in the car.

One should not now go away and make a Chinese copy to these measurements, because most likely it would not resonate at the required frequency. A noticeable change in resonant frequency can occur if the top section is changed slightly in length, or replaced by a rod of different diameter, or if the coil is altered in any way. The frequency is dependent also on the design of the car body and the mounting position, as well as proximity to buildings, trees, lamp posts, etc. Obviously no cut-and-dried formula can be used. Instead, it must be a case of cut-and-try.

Mounting Methods

Before dealing with the job of trimming the aerial, the mounting of it must be considered, as the final tuning must be done with the aerial on the car in the permanent operation position. The G3ESP/M aerial is mounted where car receiving aerials used to be—just in front of the windscreen, on one side. It goes through a hole in the bodywork,




G3HXN/M (Glos.) runs an MG fitted with 160m. gear, for which the Rx, PSU and modulator are all-transistor. The Tx (VFO, BA, PA) is valved, with a 5B/254M in the output stage — at Woburn on September 13.

A G3GMN print

suitably insulated, and down a few inches behind the dashboard. To ensure that it goes where it should, it is advisable to drill a small pilot hole from inside the car, and complete the job from outside (you can't replace the hole if you put it in the wrong place). For years this insulation consisted of a synthetic rubber grommet. Now it consists of a rubber grommet with a polythene sleeve around the rod where it goes through. The bottom of the rod is fixed to a bracket, insulated from it, of course. The small Ford cars from 1953 to 1959, and the "Popular" from 1959, have a parcels tray; this makes an excellent insulated anchor for the bottom of the rod. Super insulation is not required, as the RF voltages at the bottom of the

whip are low (and anyway the power limit is ten watts). With an overall length of about 8ft. 9in., the top of the whip is less than 12 feet from the ground, which clears all normal obsructions like bridges and trees. Even in difficult territory, the springy top section just bends out of the way. The coil is well above the car roof level, and it works remarkably well. A bumper-mounted whip could be longer, of course, but might tend to sway, unless stayed in some way.

Front fitting has much to recommend it. The feed impedance of such an aerial is very low, and normal coaxial cable will not match this. Therefore a minimum length of such cable is desirable. Further, some form of tuner is required, so that the aerial can be resonated at various frequencies over the band. One commercial model uses a capacity hat in the form of a small springy cross, which can be slid up the top section to alter its capacity to ground. The disadvantage here is that it could perhaps be dragged off if the aerial fouled a tree. Also, it seems that a ladder might be needed for extreme adjustment. A telescopic top section is another solution. The disadvantage of such external tuning systems is that the operator has to get out of the car to adjust them. An internal adjuster, conveniently to hand, is much better. With an aerial mounted at the front, as described, this is a simple matter. In the writer's case, a coil of some 20 µH is put in series with the aerial, inside the car. The coil has tapping points every few turns over most of the length, and every turn for the last ten turns. These tappings are connected to rotary switches, giving coarse and fine adjustment. This extra base loading enables the aerial to be resonated anywhere in the 160-metre band. The free end of the coil is connected by a short

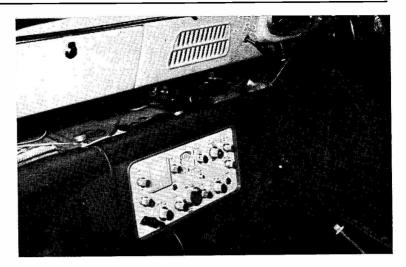

The KW-2000 Transceiver owned by G3FZW/M is fitted in his Austin A.40, the aerial system used being the Webster Band Spanner, which is an all-band design for mobile. A G3GMN print

length of coax to the change-over relay, which in turn is connected to link windings on the transmitter and receiver.

Making The Whip


Let us now consider how to make a whip successfully. Having got a suitable former and rods, wind the coil bigger than necessary. Then assemble the rods and coil in the operating position, and connect up to the transmitter. The resonant frequency will be lower than desired. An approximate idea of the frequency of the aerial can be determined before connection to the transmitter, by putting a two-turn coil between the bottom of the aerial and the car frame, and linking this to a grid dip meter. On tuning this, it will show a dip at the resonant frequency. This will at least show that the aerial is at a lower frequency than required. If not, add more wire. Next, set the transmitter to the lowest operating frequency, and take wire off the loading coil two or three turns at a time, until it is resonating in the band. Then proceed very carefully pruning the coil, finally removing one turn at a time, until the aerial is resonant just below 2000 kc. Before reaching this stage, it could be that there is an inch or two of former to spare, where wire has been removed. This can be cut down before finally pruning the coil.

Having got the aerial resonant at the highest usable frequency, it can then be tuned to lower frequencies by the aerial tuning coil already described. Even if one is a single-crystal operator, the aerial still needs some tuning device, as nearby buildings and trees can throw it off resonance when working from a static location.

Now for a few final hints, to ensure a satisfactory

job. In joining tank aerial sections, one should not rely merely on the push fit. These tubes are of steel and, though copper-plated, can rust in time. Clean down to the steel on either side of the joint, wind thin wire over the joint, then flood the lot with solder (a large hot iron is useful here). When everything is connected up, the sections can be given a beautifying and protective coat of aluminium paint.

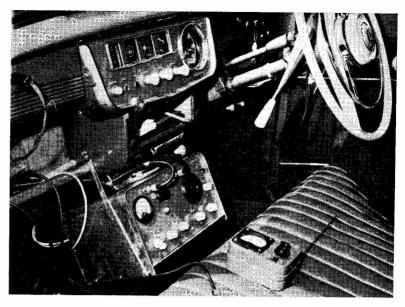It must be emphasised again that precise tuning of the aerial is essential for maximum efficiency. In the writer's station, a change of one turn on the internal aerial tuning unit can cause a change of about 2 mA in the PA anode current, which runs about 30 mA normally. This is a change of about 6 per cent, or a change in input power of about half a watt. Why waste this? Every little helps.



A Hillman Minx fitted mobile for Top Band. The installation is home-constructed and is operated by G3PPP/M, of Northampton.

A G3GMN print

First Impressions of The Show

At the moment of writing, the Exhibition at Seymour Hall is in full swing. So far, attendances have been good, and record totals all round are expected by the time the Show closes.

The opening, by Mr. E. D. Whitehead, lately Director of Electrical Inspection, Ministry of Aviation—in the presence of a much larger crowd than usual—was attended by a distinguished gathering from the world of Electronics and Communication—and Amateur Radio.

It was then announced that the annual Manufacturer's Prize had been awarded to the firm of T. Withers (Electronics) of which the principal is Tom Withers, G3HGE, the equipment selected being his new range of TW Communicators. These are single-band transceivers for two metres, four metres and Top Band, their main features being: Small size, internal aerial change-over; push-to-talk, and the CW facility; an all-transistor Rx in each case; a 15-watt transmitter complete with modulator; a transistorised PSU; and full metering.

The size and general design of these units make them very suitable for portable or mobile use, or for QRP operation in a fixed station. Finish and workmanship are, of course, up to the usual high standards expected from this stable.

It is not the intention, nor is there the space, here to discuss all that there was to say and do at this year's Exhibition—suffice it to say that the general impression, as gathered from visitors round the stands, was that it was the best Show yet, in terms of new equipment to be seen and people to meet. The whole atmosphere of Seymour Hall as this is being written is one of buoyancy and enthusiasm.

A fuller report, with more detailed information about new products, will appear in the next issue.

WHI BANDS

A. J. DEVON

ONDITIONS, like the weather, slumped during the middle part of October. Having been good up to about the 5th, there was then an abrupt fall-off until the 18th—during which quite a lot of GDX was noted—and again a slump till towards the end of the period, when things started to pick up again.

GB3LER (Shetland beacon, and your A.J.D. apologises for having put him on the wrong frequency last time; it should, of course, be 145.995 mc, nominal) was again being heard in Southern England on October 3/4, exciting because one would expect shoals of GM's to be there under such conditions. But the fact is that many reports say that this is just what does not happen — GB3LER may be coming through quite well with not a GM signal to be found on the band.

Since we all know that the GM"s are as alert for openings as anyone else, this rather unexpected phenomenon suggests that there may be a pronounced ducting effect over the route, carrying the beacon signal right over GM and Northern England

—which may sound improbable, but it does tie in with those occasions (very few, it must be admitted) when GM's inaudible in England have been working F's and PA's.

Whatever the explanation, the fact remains that the presence of the GB3LER signal in the London area does not necessarily mean that there are GM's about, and workable. What we would now like to know is when, and how, the Glasgow and Edinburgh boys find GB3LER? Is he a consistent signal, does he tie up with GDX conditions, or what?

G3EDD (Cambridge) is one of those who have noticed the peculiar timing sequence on GB3LER — he says "they must have a little man winding the handle" and that it is necessary to sit on the frequency for not less than nine minutes before deciding whether or not it is audible. He also mentions the paucity of GM's when the beacon signal is there—though GM3HLH was worked on October 3 and GI3GXP on October 4, with nothing much else on the band in the way of GDX.

Sideband and Channel

On quite another topic: Now comes up the matter of the SSB band. Inspired (and your A.J.D. thinks that is probably the correct term) by G3BA (Sutton Coldfield), about twenty or so Sideband types have settled in the frequency-area ± 25 kc of 145 mc. Being VFO-controlled, they are able to clear the CC boys, and can enjoy the pleasures of single-channel working under Vox conditions, with the minimum of searching and calling CQ. As all this is obviously contra the Zone Plan, it is not popular in all quarters, and the question now is: What should be done? So far as we are concerned, the answer is nothing until the matter has been more fully discussed, and all the implications examined. As G3BA points out, with the coming of transverters, commercial and otherwise, there will be a lot more people in a position to operate VFO-wise on two metres (even if they are not using SSB),

and Tom's idea is that the 145 mc region is the right band area for this because (a) It is midband and easily remembered; (b) For most people the desirable EDX/GDX is at the LF or HF ends: and (c) The readily available crystals can be for translation from either 14 or 28 mc. He also says that the 145 mc channel is in the largest zone, and that 95 per cent of VHF operators look for DX in other parts of the two-metre band. These ideas may not find favour with everybody, but at least it can be said that "something is being done"-and that it is now for protagonists of opposite view to have their say.

New Record Notes

G5ZT (Plymouth) has worked GC2FZC (Guernsey) on 430 mc

TWO METRES

COUNTIES WORKED SINCE SEPTEMBER 1, 1964 Starting Figure, 14 From Home OTH only

Worked	Station
50	G3EDD
46	G3SAR
42	G3HRH
38	G3CO
34	G3FNM, G3GWL
32	G3AHB
29	G2CDX
27	G3PSL
25	G3KWH
23	G2BJY, G3LAS
19	G3FIJ
18	G3PTM
17	G2AXI
16	G8VN
14	G3KQF

This annual Counties Worked Table will run till August 31, 1965. All two-metre operators who work 14 or more Counties on the band are eligible for entry. QSL cards or other proofs are not required. After the first 14 worked, simply claim from time to time with counties as they accrue, giving callsign and date for the county worked. To keep the Table up-to-date, claims should be made at frequent intervals. Operators new to VHF are particularly invited to join Annual Counties.

for a "first"—this was on September 23, with good signals both ways. GC2FZC has a QQV03-20A as a tripler final, into a 6/6 slot-fed, and a transistorised converter with an HRO; the gear at G5ZT consists of a 4CX250A in a coax line as PA, with a pair of 8/8 slots in stack, and his Rx is an A.2521 pre-amp. into a CC converter, the main Rx being a BC-454.

Harry, EI2W, is also knocking up more "firsts." On September 27 he made it with GD3FOC/M

TWO METRES COUNTRIES WORKED Starting Figure, 8 Starting Figure, 8
26 ON4FG (DL. EA, EI, F, G, GC, GI, GM, GW, HB, HG, LA, LX, LZ, OE, OH, OK, ON, OZ, PA, SM, SP, UA, UP, UR, YU)
24 G3LTF (DL. EI, F, G, GC, GD, GI, GM, GW, HB, HG, LA, LX, LZ, OE, OH, OK, ON, OZ, PA, SM, SP, UA, UR)
22 G5YV (DL, EI, F, G, GC, GD, GI, GM, GW, HB, HG, LA, LX, OE, OH, OK, ON, OZ, PA, SM, SP, YU)
21 G3HBW G3HBW G3CCH 19 G2JF, G6NB, ON4BZ, OK2WCG 18 G3BA, G3BLP, G3CO, G3GHO, G3KEQ, G5MA, G6RH, G6XM, PAØFB G2CIW, G2XV, G3AYC, G3DKF, G3EDD, G3FZL, G3HRH, G3RMB, G4MW, GM3EGW GSRMB, G4MW, GMSEGW

14 G2FR, G2HDZ, G3AOX, G3FAN, G3HAZ, G3IOO, G3JWQ, G3KPT, G3LAS, G3NUE, G3PBV, G3SAR, G3WS, G4LU, G5BD, G5DS, G6LI, G8OU, 13 G2HIF, G2HOP, G3DMU, G3DVK, G3GPT, G3GWL, G3LHA, G3NNG, G6XX, G8VZ G3AOS. G3EHY G3IIT G3OHD. 12 EI2A, EI2W, F8MX, G2BJY, G2CDX, G3BNC, G3GFD, G3GHI, G3JAM, G3JLA, G3JXN, G3OBD, G3PSL, G3WW, G5CP, G5JU, G5ML, G8DR, GW2HIY 11 G2AJ, G2AXI, G2CZS, G3ABA, G3BDQ, G3BOC, G3GSO, G3IUD, G3JHM/A, G3JYP, G3JZN, G3KUH, G3PTM, G4RO, G4SA, G5UD, G6XA, GC2FZC, OKIVR, PAØVDZ GC2F2C, GRIVK, PAGVDZ

10 G2AHP, G2FQP, G3BK, G3DLU,
G3FIJ, G3GSE, G3KQF,
G3LAR, G3LRP, G3LTN,
G3MED, G3OSA, G3OXD/A,
G5MR, G5TN, G5UM, G8IC,
GW3ATM, GW3MFY, GW5MQ

A CARRELLY CADMY. C2BHN, G2DHV, G2DVD, G2FCL, G3BOC, G3BVY, G3FUR, G3OJY, G4LX, G8CP, GC3EBK, GI3ONF, GM3DIQ, GM3LDU G2BHN. 8 G2BDX, G2DDD, G2XC, G3AEP, G3AGS, G3AHB, G3CCA, G3EKX, G3GBO, G3HCU, G3HWJ, G3KHA, G3PKT, G3AUS, G3EKX, G3GBU, G3HWJ, G3KHA, G3PN1, G3MPS, G3VM. G5BM, G5BY, G3MPS, G3VM. G5BM, G5BY,

on 4 metres, this giving him all G call areas on 70 mc, and 48C. on that band. Also noteworthy is Harry's two-metre QSO with GI3KYP/P on October 10—he says he has been waiting for 15 years to work Fermanagh, this putting him up to 96C. in the All-Time.

Two-Metre Talk

After an interval of five years, G5MA from Gt. Bookham has been out portable again, using the old 10w. rig with a pair of 6C4's in the PA. From the site on the South Downs, near Storrington, a 214-mile QSO was obtained with F1FK (the F1's are the French VHF phone-only boys) and G3IOE was worked at 290 miles. This was on October 3; on the 4th Bob was at home listening to GB3LER and wondering why the GM's were not coming through.

G3CO (Hartley, Kent) missed G3IOE during the October 3 session but was compensated by a contact with GM3HLH. Another nice QSO for him was with G3BDS/P for Hereford.

From Sale, Ches., G3FNM makes a first claim for the Annual, remarking that he has now been on two metres for 12 months, with a 40w, PA and a slot-fed 5/5 at 30ft. He is glad to notice an increase in CW operation and (like others) suggests that it would be very helpful if people would give their locations when calling CQ - yes, agreed, and it is a procedure that we have consistently advocated. G3FNM was also hearing GM3HLH on October 4.

G8VN (Leicester) has got up to 16C in the Annual on his indoor beam, and mentions a number of new stations worked on two metres in the Midlands district.

G3AHB (Slough) found nice conditions on October 20 for GDX across to the south-west, and had a very good first-time contact with G3XC for Cornwall. G3FIJ (Colchester) reports again, for the current tables, after a long absence, and G3SAR (Sevenoaks), who was there for some of the DX openings, reports an

extraordinary occurrence: GI3SLI calling GW2HIY to tell the latter that G3SAR wanted him. DX the hard way, one might say!

G3PQR (Thorpe, Essex) writes in with a first report and says he's having a "whale of a time" after a few weeks on the band; with QRP and small beam he has worked 55S in three countries—but he is disappointed with his QSL return. Very few cards have

FOUR METRES

ALL-TIME COUNTIES WORKED

Starting Figure, 8
From Home QTH Only

Worked	Station
49	G3IUD
48	EI2W, G3OHH (187)
43	G3EHY
37	G3PJK
34	G3JHM/A
33	G2OI, G5JU
32	G3NUE, G5FK
31	G3OWA (195)
30	GM3EGW
28	G3PMJ
26	G3LQR
25	G2BJY, G3AYT
24	G3LZN
23	G3BOC
21	GI3HXV
20	G2AXI
19	G3BNL
16	G3BJR, G3FDW, G3HWR
14	G3OKJ
12	G5CP, G5DS
11	G3LHA, G3OJE, G3SNA, G5UM
10	G2BDX, G3ICO
9	G3EKP, GC3OBM
8	G3NNO, G3PRQ

This Table records Counties Worked on Four Metres, on an all-time basis. Claims can be made as for the other Tables, e.g. a list of counties with the stations worked for them, added to from time to time as more counties accrue. QSL cards or other confirmations are not required. Totals in excess of 100 different stations worked can be claimed and will be shown in brackets after the call.

come back for all those sent direct.

Also reporting with claims are G3PSL, G3KWH, G2CDX and G2DHV.

Alfred Gay, G6NF

We were very sorry to hear of the recent death of Alfred Gay, who as G6NF was a keen and consistent VHF man, with a particular interest in the 430 mc band. An old timer, and of the old school, he would have been well known to many who will see these lines.

Some Four-Metre Items

G3OHH (Macclesfield) has now worked no less than 187 stations on 4 metres, and the all-time for this band shows some striking movements. G3RDC (Hastings) writes to say that he has got going on 70.2 mc, with 13w. AM phone and 17w. CW, and would like to find others to work during the evenings—he has a neighbour in G3RZC (Bexhill), who is running a B.44 with a 4-ele beam.

An interesting 4-metre claim from Fraser, GM3EGW (Dunfermline) who has accounted for 30 counties in five countries — which, from where he is, represents pretty good going. He has always been a well-known VHF operator, and has good totals on two metres and 70 cm. as well.

GI3HXV (Belfast) gained another one from the Co. Fermanagh boys and says that 4m. continues to hold the interest of the GI's—helped in no little way by the appearance of GD3FOC /M (who made it a very good mobile expedition for himself).

Other 4m. correspondents this time are G3LZN (Rowington, Warks.), G3OJE (London, S.E.20) and G3OWA (Old Coulsdon, Sy.), with claims. We were also glad to see a movement from GC3OBM (Guernsey), now at 10C in the table by reason of a QSO with G3ICO for Somerset. For those remote from the centres of activity, it is hard going on a band like 4 metres — however, with GC3ROP on Sark, GC3OBM can claim the GC/GC "first."

G3JHM/A, who has a "favourable location" near Worthing, is an active three-band man, and he has worked a lot of GDX on 4 metres recently-his best heard was G3FDW/P in Cumberland. In the Sussex-Surrey area there is a great deal-and "great deal" is the term-of mobile operation on four metres; indeed, G3JHM lists more than 20 stations who use 70.26 mc (as distinct from the Guildford chaps, who are netted on 70.65 mc) and on his Portsmouth - Worthing regular journey each night, he can get two or three mobile QSO's. An interesting fact is that G3PUR of Worthing has now worked 100 stations under strictly /M conditions. And for those who would like to know more about all this. there is a get-together arranged for November 23 by the Worthing group-see p.560 this issue for all the details.


And to Conclude-

By the time you see this, the Exhibition will be over, and there will have been much discussion about this and that connected with VHF. This is, of course, being written under what might be called extreme Exhibition-pressure, and your A.J.D. can only say that he hopes no important point has been missed. For the next offering, it is hoped and intended to get the Two-Metre All-Time out again, also if possible to show one or two other Tables we are not able to include very often.

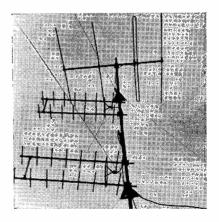Please let us have all your VHF gen. for the December issue by Friday, November 20, addressed: A. J. Devon, "VHF Bands," Short Wave Magazine, 55 Victoria Street, London, S.W.1—with you again on December 4 (all being well, and Allah being with us). 73 de A.J.D.







Some pictures taken by G3OUF on the GB2GC expedition to Alderney, C.I., during September 3-7. Top, the two-metre station, looking N-E; the blockhouse is a relic of the German war-time occupation. Next down is the gear used on 4 metres. Below is the 4m./70 cm. aerial array. The two-metre beam was a separate installation, and 61S were worked off it. The contest produced 24S raised on 4 metres. But 70-cm. results were disappointing—this, the boys admit, was largely due to certain inadequacies in the 430 mc gear. But they did try, and had very difficult conditions to contend with, as regards both the Wx and radio-wise. For the trip, every single thing needed had to be taken over—food, tents, camp-beds, the lot. One of the most teasing practical problems was getting 3/12v. accs. across in strict accordance with the air safety regulations The team consisted of G3OUF, G3PSH, G3RRU and G3SHK—and they reckon they were taking more risks for VHF than any other team in the DX-pedition business!

THE MONTH WITH THE CLUBS

By "Club Secretary"

(Deadline for December Issue: November 13)

(Address all reports for this feature to "Club Secretary")

If the number of additional requests for Club identification letters is anything to go by, it looks like being the hottest MCC yet. Several Clubs are putting in two stations, and a few are even contemplating a third—which is, of course, all to the good, since our annual Top Band Club Contest has for long been recognised as first-class training for potential contest operators of all ages. It is of no consequence if a particular Club fails to gain a high place due to the inexperience of its operators, so long as the ops. themselves learn something by taking part in the Contest.

Certainly, for any Club to win MCC nowadays—or even to get a high place in the event—means that it must be very well tee'd up, with first-rate gear and an effective aerial, an operating team well trained in the technique of fast CW working, with a good supporting group of log-keepers, monitor-receiver operators, and tea-makers! There are not many Clubs in a position to meet all these desiderata—and some even leave it to a couple of their ace-operators to handle the whole project. More than a few dummy-runs will be staged between now and November 14 to make sure that all is in order. And on the day there will be some local-Derbys, too!

But those who do not aspire to striking sparks and hope simply for a creditable place in the Table of Results—or at least to see an improvement on their last year's performance—gain just as much enjoyment from "MCC," and of course it is their participation that helps to make it all worth while.

The final list, arranged alphabetically for convenience in checking off, appears on p.561 and was complete at the time of going to press. Read the footnotes, and delegate somebody to prepare the fair log we hope to have from you before November 27. Good luck to all who are having a go, and we look forward to an interesting and successful event.

CLUB REPORTS

With a stand-in "Club Secretary" in charge and a larger-than-usual compilation this time—only to be expected, as we are now well into the busiest time of the year in the Amateur Radio context—we look first at proposed new club formations.

At **Bedford**, accommodation has been secured, a first meeting has been held, and it is hoped that all licensed amateurs and SWL's in the district will give their support to G3OWQ, who is acting hon.

secretary—which means that he is doing a lot of hard work to get things going.

The British Aircraft Corporation Amateur Radio Club has already been formed, at Hurn, where they have excellent facilities for radio construction and operation—and a very nice QSL card, featuring the BAC-One Eleven, is available for members. The idea is to get in any licensed member of the Vickers-Armstrong group of companies, with a view to forming a register and arranging skeds. G2DBF is handling matters (QTH as panel, p.558).

G3NXP writes that a club is proposed for the Aldridge, Brownhills and Walsall district, and anyone interested (AT op. or SWL) should get in touch with him, at 32 Mob Lane, High Heath, Pelsall, Nr. Walsall.

One of the most active Clubs in East Anglia is **Peterborough**, where they have an energetic secretary in G3KPO; he reports that their AGM is to be held on November 6, at the Technical College; that club-nights are each Friday; and that their new Hq. is in Old Mill (back of the Peacock Inn), in London Road.

An interesting note from **Ipswich** remarks "we decided not to recess this summer and were rewarded with practically normal attendances"—good! Their meeting place is the Civic College, last Wednesday in the month, and they have a programme to suit all members, "DC to UHF," as the report puts it.

Midlands and North

One of the oldest Amateur Radio clubs in the country (if not in the world) is **Barnsley**, with fortnightly meetings, at the King George, Peel Street, and a varied programme—such as their traditional Pie Supper, held a fortnight ago. Next meetings are on November 6 and 20, and G4JJ is the new hon. secretary.

An established society with a new name is Loughborough, now known as the Loughborough Amateur Radio Club. They also have new premises,

" MCC " — NOVEMBER 14/15

Rules and scoring, pp.498-499, October. Final Club Identification List, p.561 this issue. Take an accurate GMT time check before 1700 on Saturday 14th. Make sure your log-keepers have read Rule 7, p.498, October. Logs with us by Friday 27th latest, or earlier if possible.

at Beach Yard, Wards End, L'boro', where they get together every Friday at 8 p.m.—except when they are off on a trip somewhere, as on November 29, when they visit Rugby Radio, GBR, the famous GPO station capable of world-wide coverage (When, and if, we ever had the time, a lot of interesting research could be done on the subjects of famous GPO stations and amateur clubs with a long history—such as Loughborough and Barnsley.)

Blackpool and Fylde will have a home-built CC converter demonstrated to them by G6DN on November 9; on the 16th, the lecture is on Elements of Radio Valve Theory and Manufacture. G8JU will talk on Aeronautical Electronics (what the Americans now call "Avionics") on the 23rd; and the 30th is booked for a junk sale (and come prepared to tidy up afterwards!) The Liverpool programme also includes a junk sale, on November 10, and on the 17th the talk will be by G3GST.

The group known as Northern Heights is very active in the Halifax district. Having arranged an R.A.E. course at the Percival Whitley College, they laid on a demonstration station during the enrolment week. Next event is a visit to the Mullard Film Show at Kings Hall, Bradford, on November 10, and on the 11th there will be a most important occasion—three of their youngest SWL's will Lecture on Listening, one of the speakers being recently-licensed G3TQA, who, though only 14½, has had much experience of SWL'ing. On November 25, they will get back to such matters as Transmitter Alignment, by (we suspect) a professional. And this is the sort of thing that makes the pattern of Amateur Radio.

An interesting visit is scheduled for Spen Valley on November 12 — they go to the Home Office Wireless Dept., QTH The Common, Kippax (that's what it says!). In fact, authorities such as the Ambulance Service, the Fire Brigade, the Police, and the Post Office are only too glad to show off their stations and communication systems to intelligent visitors if the right approach is made to the proper authority—and we would say that there are few Clubs, anywhere in the country, not within reach of some such official radio station well worth a visit.

Going much further north, to Edinburgh, a report from the Lothians Radio Society says that they have started the winter session, the big event to come being the Hobbies Exhibition arranged by Edinburgh Rotary Club during November 7-14, in the Waverley Market, when the Club will be represented. Next meeting will be on November 26, their visitors' night, when members of any neighbouring GM Club will be most welcome.

It may be remembered that in the September issue of Short Wave Magazine we mentioned one Sid Warren, a protégé of South Birmingham Radio Society, who was being helped through considerable difficulties to obtain his licence. He is now G3TPC, on the air in his own right, and doing well, thanks to the local lads. Their next meetings are on November 19 and December 17, 7.30 p.m., at Friends Institute, Moseley Road, Birmingham.

At Coventry they have a new hon, secretary,

G3TKO, and next on the clip is a report from Mid-Warwickshire, where membership continues to grow, with meetings on alternate Mondays at 7.30 p.m. in the C.D. Training School, Harrington House, Newbold Terrace, Leamington Spa. The local College of Further Education is now an R.A.E. centre, and five members are expected to take the next examination.

The Chester group have meetings fixed for November 17 and 24, 8 p.m. at the Y.M.C.A., and at **Dudley**—a club from which we do not often hear—they have had their third AGM, at which the officials elected were G2DTQ, G3PWJ (hon. secretary), G3OSP and G3SIO, with two SWL's as committee members; meetings are normally in the Art Gallery, Dudley, but on November 7 they "go outside" for the annual dinner.

Next get-together for Melton Mowbray will be on November 26, 7.30 p.m., at the St. John Ambulance Hall, Asfordby Hill, when the time will be devoted to construction; here, members can keep in touch either by joining in on or listening to a twice-weekly Top Band net. The Leicester Radio Society has got through its AGM; meetings take place on Sunday mornings and Monday evenings, and participation in various competitive events is planned. Derby send in a programme taking them through to August of next year! In the meantime, they meet weekly on Wednesdays, 7.30 p.m., in Room 4, 119 Green Lane, the next on November 11 being devoted to a Demonstration of Communications Receivers—could be very interesting.

From the October issue of their Newsletter, we get it that for Midland the big days are November 17, when they have a demonstration of the Eddystone EA-12, and December 15, which will be the occasion of their annual Christmas party. Included with this issue of the Newsletter is the financial statement, which shows M.A.R.S. to be in its usual good position. Though there was again a loss on the annual dinner, the Trentham Rally showed them a profit of £43, and there was an excess of income over expenditure for the year. Their realisable cash assets now stand at over £400.

The neighbouring **Sutton Coldfield** Club hold their AGM on November 18 when, no doubt, finance will be up for discussion.

West and South-West

At their recent (and first) AGM Bristol were given a very good report; of the 42 members present, 18 held full licences, no less than ten of these having been gained in the year. New premises have been made available to them at the Bristol University Settlement, 43 Ducie Road, Barton Hill, and a strong body of officials includes five callsigns.

For Torbay, the next meeting will be on November 7, at the Hq. in Bath Lane, Torquay. Plymouth continue very active, with gatherings each Tuesday, 7.30 p.m., at Virginia House, Bretonside. Their new station G3PRC was officially opened by Mrs. Western, G3NQD, of the Torbay A.R.S., on October 13, which was also the occasion of the return quiz-contest between the two Clubs—handsomely won this time

by the home team. The evening was a great success (and not only for this reason!) as they had a capacity attendance, including members of the Kingsbridge group.

Many of the Clubs reporting this time mention their intended participation in MCC-but only Yeovil have already booked a date, November 18, for their post mortem on it! We can only hope that the findings will satisfy the coroner! Another activity during the month will be the re-building of the Club's 160m. Tx (the two themes seem to be connected. somehow!) for operation from their Hq. at Park Lodge, The Park, where they meet every Wednesday at 7.30 p.m. Cornish report that at every meeting, held on the first Thursday of each month at the S.W.E.B. Recreation Room, Pool, Camborne, "we find new faces appearing and becoming members." On October 8, no less than 32 members were present -which is pretty good for a district rather underpopulated in the amateur sense.

The next Southampton group meeting will be on November 14, when a visiting American officer will talk on—Espionage! The Group takes in the Wessex A.R.C. and the R.N.A.R.S. and they issue a joint

newsletter, called QUA, each month, covering the activities of all.

In Somerset, the **Burnham-on-Sea** Club get together on the second Tuesday of each month at The Hall, Berrow Road, the premises also being open on Sunday mornings and "at other times when needed." On November 10 G3NUK will give Part II of his talk on Fifty Years of Fun with Morse, and it is said that those who heard Part I will not want to miss this. Another speaker scheduled for a future occasion is Ken Randall, G3RFH/VP8HF, on his wanderings in the Antarctic.

Also from Somerset, the R.A.F. Amateur Radio Society, Locking reports, but rather a dolorous state of affairs. Though the financial statement shows an excess of income over expenditure, and a good liquid asset position, this has only been achieved by cutting down drastically on QRV, the Society's periodical (which still makes a loss). And the absence of RAF-ARS from the recent Exhibition, for the first time in years, was due to the unfortunate fact that Ministry financial support has been withdrawn. (That magnificent stand we used to see every year was provided by the Service public relations department,

LOUGHTON: A. W. Sheppard, 11 Barfields, Loughton (LOU

Names and Addresses of Club Secretaries reporting in this issue:

ACTON, BRENTFORD & CHISWICK: W. G. Dyer, G3GEH, 188 Gunnersbury Avenue, London, W.3.

A.E.R.E. (HARWELL): C. Sharpe, G2HIF, Building 347.3, A.E.R.E., Harwell, Berks. (Abingdon 1220, Ex. 3026).

A.R.M.S.: N.A.S. Fitch, G3FPK, 79 Murchison Road, London, E.10 (LEYtonstone 6700).

BARNSLEY: J. A. Ward, G4JJ, 44 Northgate, Barnsley, Yorks. BASILDON. C. Roberson, Milestone Cottage, London Road, Wickford (2462), Essex.

BEDFORD: J. R. Clarke, G3OWQ, 12 Robin Hill, Brickhill, Bedford.

BLACKPOOL & FYLDE: J. Boulter, G3OCX, 175 West Drive, Cleveleys.

BRISTOL: E. Davis, G3SXY, 72 Northview, Westbury Park, Bristol, 6.

BRITISH A/C Corpn., HURN: J. F. Squires, M.B.E., G2DBF, 18 Wakefield Avenue, Northbourne, Bournemouth, Hants. BURNHAM: D. W. Birt, G3GIW, 99 Stoddens Road, Burnhamon-Sea, Somerset.

CEYLON: D. S. Ratnadurai, 4S7SR, 17 Jayakunta Lane, Kiriulla Road, Timbirigasyaya, Ceylon.

CHESTER: P. J. Holland, 19 Kingsley Road, Gt. Boughton, Chester.

CORNISH: W. J. Gilbert, 7 Poltair Road, Penryn, Cornwall. COVENTRY: E. E. Snow, G3TKO, 11 Lupton Avenue, Styvechale, Coventry.

CRAWLEY: R. G. B. Vaughan, G3FRV, 9 Hawkins Road, Tilgate, Crawley (23359), Sussex.

CRAY VALLEY: S. W. H. Harrison, G3KYV, 30 Plaistow Grove, Bromley, Kent.

CRYSTAL PALACE: G. M. C. Stone, G3FZL, 10 Liphook Crescent, London, S.E.23 (FOR 6940).

DERBY: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

DORKING: R. Catles, 4 Dawnay Road, Great Bookham (3291), Leatherhead, Surrey.

DORKING: R. Catles, 4 Dawnay Road, Great Bookham (3291), Leatherhead, Surrey.

DORKING: R. Catles, 4 Dawnay Road, Great Bookham (3291). Leatherhead, Surrey.

HALOW: G. O'Donald, G3TLJ, Great East, Roydon Road, Roydon, Harlow, Essex.

HOUNSLOW: D. F. J. Walmsley, G3HZL, 153 Worple Road, Isleworth, Middlesex (POP 3239).

PSWICH: R. J. Wells, 43 Clench Road, Holbrook, Ipswich. LEICESTER: J. R. Dowson, 384 Hinckley Road, Leicester. LIVERPOOL: H. James, G3MCN, 448 East Prescot Road, Liverpool, 14.

LOTHIANS (Edinburgh): T. Spears, GM3OWI, 24 Priestfield Road, Edinburgh,

4296), Essex.

MELTON MOWBRAY: D. W. Lilley, G3FDF, 23 Melton Road, Asfordby Hill, Melton Mowbray, Leics. (Asfordby 373).

MIDLAND: C. J. Haycock, G3JDJ, 29A Wellington Road, Handsworth, Birmingham, 20.

MID-WARWICKSHIRE: H. C. Loxley, 51 Guy Street, Warwick. NEWBURY: R. A. Fuller, 6 Pleasant Hill, Tadley, Basingstoke, Hants.

NORTHERN HEIGHTS: A. Robinson, G3MDW, Candy Cabin, Ogden, Halifax.

NORTH KENT: B. Dawson, G3RMI, 16 Derwent Close, Dartford, Kent.

PETERBOROUGH: D. Byrne, G3KPO, Jersey House, Eye, Peterborough, Northants.

PLYMOUTH: R. Hooper, 2 Chestbut Road, Peverill, Plymouth. R.A.F. A.R.S.: Hon. Secretary, R.A.F. Amateur Radio Society, R.A.F. Station, Locking, Somerset.

R.A.I.B.C: Mrs. F. Woolley, G3LWY, 10 Sturton Road, Saxilby, Lincoln.

READING: R. G. Nash, G3EJA, 9 Holybrook Road, Reading. REIGATE: F. D. Thom, G3NKT, 12 Willow Road, Redhill, Surrey.

SCOTLAND (Radio Club of): A. Barnes, GM3LTB, 7 Southpark Terrace, Glasgow, W.2 (WEStern 4080).

SOUTH BIRMINGHAM: A. E. Bishop, Jr., 40 Cecil Road, Birmingham, 29.

SOUTHGATE: R. Wilkinson, 33 Amberley Road, Palmers Green, London, N.13.

SPEN VALLEY: N. Pride, 100 Raikes Lane, Birstall, Leeds.

STEVENAGE: G. R. Henderson, G3RTJ, 76 Austen Paths, Stevenage, Herts.

SURREY (Croydon): S. A. Morley, G3FWR, 22 Old Farleigh Road, Selsdon, South Croydon.

SUTTON & CHEAM: F. J. Harris, G3BOF, 143 Collingwood Road, Sutton, Surrey.

SUTTON COLDFIELD: K. H. Varney, G3DMV, 149 Whitehouse Common Road, Sutton Coldfield, Warks.

TORBAY: Mrs. G. Western, G3NQD, 118 Salisbury Avenue, Barton, Torquay.

UXBRIDGE: F. J. P. Offord, 43 Greys Road, R.A.F. Uxbridge, Middlesex.

WEST KENT: H. F. Richards, 17 Reynolds Lane, Tunbridge Wells.

WIMBLEDON: E. N. Hurle, G3RZN, 156 Monkleigh Road, Morden, Surrey.

WORTHING: R. J. Tarr, G3PUR, 245 South Farm Road,

YEOVIL: D. L. McLean, G3NOF, 9 Cedar Grove, Yeovil, Som.

Worthing, Sussex.

not by the Society.) It seems that unless a recruiting return is forthcoming, the Ministry will not put up the cash. And the authorities must now be scratching their heads a bit about the enormous cost of providing tied lines for the RAF-ARS stand at the Earls Court Radio Show — whoever thought of this!

London & Home Counties

The majority of Clubs are, of course, in this part of the country, and we have a corresponding number of reports. Uxbridge fill their three November meetings with a series of talks on SSB, by G3NDU, who gives Parts II and III on November 16 and 30. On December 7 they have a jollification, their bangers-and-mash supper.

Valley, covering the

Cray

December 18.

Eltham, Sideup and Orpington districts, have been hearing about the good old days (and they were good, for radio amateurs) from G2MI; the current issue of their newsletter QUA has a screed from G2HP about the Goyder Lock method of CO-PA drive-which worked well if you could get it to work. Indeed, this issue of QUA has a number of interesting items. West Kent also produce a neatly printed single-sheet news!etter, called QLF, listing their fortnightly meetings at Culverden House, Culverden Park Road, Tunbridge Wells, next being on November 13 (Talk on Components) and November 27 (Dual Standard TV Circuitry); their Christmas Party is slated for

Dorking took part in three contests this year, "with average success," the report says. Their chairman, G3LHC, as a member of a recent overseas trade delegation, was able to show the September meeting some interesting colour slides of China and Japan. On November 10 the gathering will be at the Wheatsheaf, and on November 24 at the Star & Garter—visitors always welcome.

The Southgate, Finchley & District group will be at Atlasta Lodge, Tottenhall Road, Palmers Green, N.13, on November 12 for the G6QM trophy competition, and on November 26 for talks with and for SWL's.

For **Guildford**, the November 13 meeting will be devoted to a discussion on the Racal RA-17 receiver, by G3NR, and on the 27th they have a talk on the Decca Navigator. The big night is December 11, when their president will discuss The Operation of Practical Equipment, 1900-1922; this lecture is being specially recorded, and should be of considerable interest. (*Note* 1900-1922!)

Reigate decided that, for this year's VHF field day, they would "get well away from the London ORM" — so they went down to a site near East-



For the Harlow & District Radio Society's Rally on September 27 last, the talk-in station on Top Band was G3PRN—and here it is being operated by Robert Frost, G3SZF, who is Harlow's youngest member; he is just bobbing on the ripe age of 15 years.

bourne, and 17 members were in camp, under canvas; in spite of the weather, they were not deterred, and similar forays are planned for the future. On November 21, at the George and Dragon, Redhill, G8RW will be talking on UHF. The latest call in the Reigate group is G3TQY.

A talk started by G3MFB on Radar Techniques, for **Wimbledon**, proved so interesting that time overran, and the second part is to be given on November 13. Their AGM is fixed for December 11. Acton, **Brentford and Chiswick** will be meeting on November 10 to hear G3IGM on Radio Test Gear, 7.30 p.m., at Club Hq., 66 High Road, Chiswick.

Harlow report a very successful Mobile Rally on September 27, with 180 cars in the park, of which 60 were fitted /M; some had come over 100 miles to be at Magdalen Laver for the event. More than 50 donated prizes were handed out by Harlow's president, G6UT, and from the Rally proceeds it was possible to make a substantial donation to the very-deserving R.A.I.B.C. The Club has arranged R.A.E. and Morse classes locally, under G3GRQ and G3K.FG, about which information can be obtained from the hon. secretary.

Also reporting a very good Rally are Reading, one of their visitors being an SWL from Coventry — on a scooter! On November 28, the evening at Palmer Hall, West Street, will be devoted to the Conversion and Use of Government Surplus, a pretty broad subject of perennial interest; the December meeting will be on the 19th, same QTH. Sutton and Cheam get together monthly at the Harrow, High Street, Cheam, and November 18 will be the occasion for a Junk Sale. North Kent run a lively Newsletter, though the latest issue to reach us gives no forward information about November meetings — but the sequence

looks like fortnightly Thursdays (12th and 26th) at the Congregational Church Hall, Clock Tower, Bexleyheath.

Worthing have an interesting event scheduled for November 23 — a 4-metre gathering, to be held at the Royal Oak, Hooksway, 6 miles from Chichester, just off the B.2141. (The hostelry itself is described as old, isolated, interesting and without mains!). G3PUR on 70·26 mc will be well sited for talking-in 4-metre mobiles, the time is from 8 p.m., and all interested would be very welcome. The Worthing club itself now has over 30 members, meetings are held monthly on the second Monday at the Adult Education Centre, Worthing, and visitors are always expected. On November 9 the discussion will be on the Use and Construction of Simple Test Equipment.

During November 14-21, Loughton will be cooperating in a large-scale experimental closed circuit TV presentation on behalf of the Television Viewers' Council, to be put on at Loughton Hall; localinterest programmes representing the activities of cultural groups in the district are to be professionally produced and viewed by judging panels, to decide whether such a service would be of community interest. Much of the gear is being supplied by the British Amatur Television Club, under G3MJZ/T, this group having had much experience of practical closed-circuit TV work. Loughton's regular meetings are on alternate Fridays, 7.30 p.m., at Loughton Hall, Rectory Lane, and on November 6 they will be hearing, from a BBC speaker, about the Corporation's broadcasting techniques on short-wave.

Basildon will entertain Peter Blair, G3LTF, for his lecture on VHF/UHF, at the Bullseye, Southernhay, Town Centre, Basildon, on December 9 at 8 p.m. As this talk will be of special interest, many visitors are expected, and they are informed that admittance is free, with ample car parking.

The October issue of QAV, for Harwell (A.E.R.E.) is again a good one, with much meaty practical gen, about Club activities. Their meetings are held on the third Tuesday of each month, at the Social Club, A.E.R.E., at 7.30, and visitors are always welcome. The talk on October 20 was by G3CBU on Noise Measurement, with special reference to parametric amplifiers at 144 mc.

Crawley maintain a high level of activity, and have decided to "celebrate another successful year" by a dinner — on March 19, 1965! The next meeting here is on November 25, with a welcome for everybody. The SRCC Monthly News, from Surrey, gives November 10 for the next meeting — at the Blacksmiths Arms, South End, Croydon — when G5DJ will talk about Cables.

The Stevenage Beam is a well-presented newsletter, for the Stevenage and District A.R.C., and reports some very useful lectures at recent meetings; another event during the month was a visit to the Shefford A.R.C., in their new Hq., which proved to be a very enjoyable evening. The Stevenage AGM is on November 19 when, as usual, all members are asked to make a special effort to be present, and on time!

Next date for **Newbury** is November 27, when the Rev. Paul Sollom, G3BGL, will give a talk entitled A Little Flutter on VHF — as he is good at VHF, this should be interesting. The QTH is, as usual, Ellott's Canteen, West Street, at 7 p.m. Visitors are invited, and a p.c. to the hon. secretary will bring any information required.

Hounslow have got the Club station G3TDD going on two metres, attendances are improving, and a successful season is anticipated. November 16 is marked as "special meeting," and the 23rd as "Transmitting night on 144 mc — G3TDD on the air." On November 30 Audio Techniques will be considered

One of the stronger Clubs in the London area is Crystal Palace, of which Geoff. Stone, G3FZL, has been hon. secretary for many years. He produces a regular one-sheet newsletter which shows that a variety of interests are covered — including hi-fi, D/F, stereo, RTTY, VHF and the ordinary business of working DX on the HF bands — what more could you want!

Special-Activity Clubs

Under this heading come the organisations which. by their nature, have a specialist appeal outside and beyond any particular district or area. the R.A.I.B.C. ("Radio Amateur Invalid & Bedfast Club") devoted to the needs and interests of those who, by reason of disablement or infirmity, cannot get about; their only contact with the outside world can be over the air. The members of R.A.I.B.C. are kept together by their monthly compilation Radial, which in turn is kept going by the devoted and painstaking work of Mrs. Frances Woolley, G3LWY, who regularly turns out a well-written, newsy and nicely produced 8-page bulletin, full of personalia. We make no apology for suggesting that anyone with charitable instincts in the Amateur Radio context might consider getting in touch with G3LWY—but, remember, she is a busy housewife, with domestic responsibilities of her own. So keep it short, enclose an s.a.e., and make it clear whether you would like to help with gear (in working order), radio periodicals-or cash. (And while writing this, it occurs to your stand-in "Club Secretary" that there might well be scope for local visiting of bedfast types, taking out for drives, and so on. But only G3LWY is competent to advise.)

Now we come to the Amateur Radio Mobile Society, also a specialist organisation, but in quite a different context. They, too, produce a monthly journal, likewise well-written and nicely duplicated, and involving a great deal of production effort, all in an honorary capacity. After nearly six years of hard trying, they can show about £260 of nett assets disposable among fewer than 400 members—vet there are at this moment more than 1.700 amateurs licensed mobile in the U.K. alone (the appeal of A.R.M.S. is claimed to be "world-wide"). Well might they ask, in their September issue, "Where Do We Go From Here?"—though, to be fair, this is out of context, because the quote is taken from the September leader comment about their

IDENTIFICATION LETTERS FOR CLUBS IN "MCC"

Full Alphabetical List

	_		
AB Aberdeen	CT* Crawley, Sussex,	LP 42nd Sig. Regt.	RP R. Sigs. A.R.S.,
AC Acton, Brentfo	rd & No. 3	Liverpool	Catterick
Chiswick	CU* 65th Sig. Regt.	LS Leeds Univ.	RR R.A.FA.R.S.,
AG Ash Green (St	irrey) (Scot.)	LV Liverpool	Locking
AI Ainsdale (Land		LY Leeswood	RS Radio Club of
AL Aldershot	CW Cotswold RCC	E1 Eccswood	Scotland
AQ Aquila (Kent)	CX Crawley, Sussex,	MA Macclesfield	RV Ravensbourne
AR Aborfield (Berl		MD Medway	
AT A.T.C. Sqdn.	CY Chorley and	MF* Moray Firth	(London) RY Rugby
(Staffs.)	Leyland, Lancs.	MC* Magnus CS	
AW Albright & V	/ilson CZ Clifton (London).	MG* Magnus G.S.	RZ R.A.F., Sealand
(Dirmingham	/ilson CZ Clifton (London),	(Newark)	
(Birmingham	No. 2	MH Mitcham	SA Salisbury
		MO Morecambe	SB St. Benedict's,
BA Barnet	DA Dalriada (Scot.)	MP* Marconi	London
BB BBC, Lime Gr	ove DB Danbury, Essex	Apprentices,	SC Scunthorpe
BC Buchan (Fife)	DH Dollis Hill, GPO	Chelmsford	SD Sheffield, No. 1
BD BBC, Evesham	DL Deal	MR Midland RCC	SF* Sunderland Tech.
BG Bradford G.S.	DR Derby	MS Midland ARS	Coll.
BH BBC, Bush Ho		MY Maidstone YMCA	SG Stroud
BI Bristol	20 24:5:0)	MZ Manchester	SH Shefford
BJ Bath	EC Farles Lance		
BL BBC, Langhar	EC Eccles, Lancs.	NK Newark	
Place	LD Lugwait	NL* Northampton	SK Sole Bay
BM Blackwood, M	EK East Kent	College, London	SL South London
	LL Last Works.	NN North Notts	Mobile
	EW East Cheam	NO North Kent	SM South Manchester
BO Bagshot	EX Exeter	NP* Northern Poly-	SO South Birmingham
BP Blackpool	1	technic, London	SP Stockport
BQ* Burnham Beec	ones, GD Guildford	NR Norfolk	SQ* Silverthorn, London
Bucks.	GE G.E.C. Research	NT Nottingham	SR Scarborough
BR Barnsley	CF Groonford	NU Newcastle Univ.	SS South Shields
BS Burnham-on-S	GN Grafton	NW Norwich	ST S.T.C., Harlow
Som, No. 1	CP Grayecond		SU Stourbridge
BT British Timker	GS^* G.E.C. Apprentices,	NY Newbury	SV Stevenage
Coventry	Coventry	OV Overstone	SW* South-West Essex
BU Bangor Univ.	CV Colonalisa		Tech. Coll.
BV* Burnham-on-S	ea, Of Gillisoy	(Northants.)	SX Stoke-on-Trent
Som. No. 2		OX Oxford	SY Surrey (Croydon)
BW Brentwood, M	liddx. HA Halifax	PD Paddington	SZ Sutton and Cheam
BX Burslem, Staffs	HL Hallamshire (Yorks.)		DE DUCTOR UNA CREAM
BY Bury	HR Harlow	PL Plymouth	THE THE
BZ Basingstoke	HS* Hounslow	PN Painton (Northants.)	TH Thanet
· ·	HT Hartlepools	PO Port Talbot,	TY Torbay
CA Cheltenham	HW Harrow	South Wales	TITE II : C II 1
CB City of Belfas	HX Harwell (A.E.R.E.)	PR Preston	UK Univ. of Keele
CC* Cannock Chas	No. 1	PT Petersfield	UX* Uxbridge
CD* Cambridge	HY^* Harwell (A.E.R.E.)	PY Purley	
	No. 2		VR Verulam (St. Albans)
CE Chester		RA Reigate, No. 1	VS Vickers, Hurn
CF Cray Valley	IL* Isle of Man	RB Reigate, No. 2	
CG City & Guilds	,	RC Reigate, No. 3	WD Wanstead and
London	KN Kingston	RD Reading	Woodford
CH Chiltern, Buck	77777 77 777 77 11 01 1	RF 92nd Sig. Regt.,	WK Wakefield
CL Clifton (Londo	on), KW K.W. Radio Club	Forfar	WL Wellingborough
No. 1		RG* No. 1 MHU A.R.C.,	WO Wolverhampton
CN* Conway Valle		Middlesex	WR Wirral
CO Cornish	LD Loughton (Essex)	RH Rhondda Valley	WS Wimbledon
CR Crawley, Susse	ex, LF Leven (Fife)	RL R.A.F. Little	WT Worcester
No. 1	LH Loughborough	Rissington	WV Wolverton, Bucks.
CS Civil Service,	LM Lymington	RN Royal Naval A.R.S.	,
London	LO Lossiemouth	RO Rotherham	YV Yeovil
			

NOTES: (1) Clubs marked* are those who have applied for identification letters since the October issue appeared.

(2) It does not necessarily follow that every Club named here will enter the Contest.

(3) The listing is complete at time of going to press. Later applicants will be allotted identification letters but cannot now be listed.

(4) Rules, with scoring and operating examples, appeared on pp.498-499 of the October issue.

(5) It is essential to have all logs in by the due date, November 27, made out as laid down in Rule 7, p.498, October.

(6) The judges reserve the right to refuse adjudication of logs not conforming to the rules.

alleged success in wiping everyone else's eye in the matter of Reciprocal Licensing. This is one of those concepts which is of far less importance than it is made out to be, and it is much to be regretted that exaggerated language has always to be used "for and on behalf of" a small organisation which —as the figures show—has only a limited appeal. However, this is not to say that the Amateur Radio Mobile Society has not done—and has the potential for doing-a good and useful job. It is just that the language should be moderated a bit and some attention paid to increasing membership among U.K. mobiles—and the fact is that even if A.R.M.S. succeeded in doubling its U.K./M membership, it would still have only a bare half of the G's licensed mobile! The hon. editress of Mobile News does an excellent job journalistically—she has a most engaging style.

In another category again is the 4S7 Bulletin of the Rad o Society of Ceylon. Also a duplicated effort, it is produced by Ian Wollen, 4S7IW, who talks entirely in the Amateur Radio context. Though his Bulletin represents one of the smaller Commonwealth societies, with quite a small membership (less than 100 members), it has nevertheless achieved the distinction of IARU recognition. The aim is to publish six times a year, giving a journal of about 20 pages a time—no mean effort, and 4S7IW draws attention to the difficulties of any honorary editor in getting suitable material from a small group of members.

And one could say that the GM Magazine, the monthly offering for the Radio Club of Scotland, produced by GM3AXX with the assistance of GM3OLG, is in yet another category. The September issue runs to 45 duplicated pages of which seven are devoted to tape recording interests and 15 pages to summarised information on M-O valve types. This leaves about 23 pages for the coverage of Amateur Radio activity in Scotland—and here again. the hon, editor has to issue an urgent appeal for more support in the way of technical articles, lecture

NOTE FOR SECRETARIES


These pages are available for reports from any Club caring to make use of the space. It is essential that we have reports by the due date, given each month at the head of article, with the Club hon. secretary's name, c/s (if any) and full address for inclusion in the Secretaries' QTH Panel. Reports received late cannot be written in. Address all items for this feature to: "Club Secretary," Short Wave Magazine, 55 Victoria Street, London, S.W.1.

material and assistance from members for Club projects generally.

For Consideration

Truth of the matter is that for any worth-while periodical to survive with the support of fewer than about 500 members, paying quite a high subscription (not less than 15s.), means that there must be a great deal of sustained and selfless honorary effort. This is always forthcoming—for a time. But sooner or later, the crunch must come and it is then that serious difficulties arise—as we have already seen in the case of the R.A.F. Amateur Radio Society, which can claim a membership in this bracket and at one time enjoyed considerable backing, official and unofficial, to say nothing of trade support.

For next "Month With The Clubs," your standin Club Secretary (who always follows this feature with the closest interest) will be handing back to our regular contributor—so don't blame him for any errors, omissions, expressions of opinion, misunderstandings or failures to comprehend in this month's offering! He will want to hear from all honorary secretaries in good time for the December issue—so note the date at the top of p.556. And remember that MCC logs, strictly in accordance with Rule 7, p.498 October Short Wave Magazine, must be in on time—Friday, November 27.

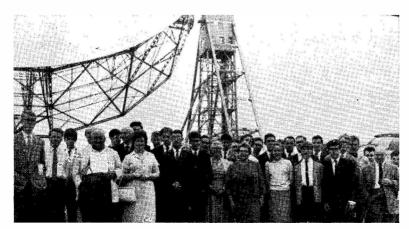

Group photograph taken on the occasion of the Northern Heights Amateur Radio Society's visit to the Radio Astronomy Laboratory at Jodrell Bank, Cheshire. The party consisted of over 40 members and friends, and heard a lecture by Sir Bernard Lovell, the director of the Laboratory. They were much impressed by what they saw and heard.

LOOK AT THE BOOK LIST

Here and there in this issue are the list of books available through our Publications Department, which aims to give a byreturn service, because everything we advertise is from stock. The titles shown on p.567 are all new ones, carefully selected from the wide range of new books coming on to the Amateur Radio market from Britain and the U.S.A. And with Christmas coming, what better present could there be for a radio amateur than a book on some aspect of the subject in which he is particularly interested -such as Sideband, VHF, RTTY, Mobile of even DX.

THE OTHER MAN'S STATION

G3JDK

H. N. Kirk, of 54 Allendale Road, Rotherham, Yorkshire, was licensed as G3JDK in 1953, and the picture here represents the third of his amateur-band installations since that date. And with the exception of the Hallicrafters SX-110 and the HT40K transmitter, the whole of the rest of the gear, including the console, is home-built—and not, G3JDK adds, from kits!

From left to right, we see the first main unit, a CW/Phone transmitter for Top Band (832 PA, 10w. input), incorporating a small CRT for modulation monitoring. This Tx has made WABC and has also given many EDX contacts, using a 134ft. wire and the Z-match unit standing above it. Next on the bench line come a modified Heathkit VFO, re-housed in a G3JDK cabinet above which stands the electronic keyer for CW operation. Across the corner comes the HF-band Tx, running 120w. to a TT21, which is self-contained for power, and is plate-and-screen modulated by a pair of 5B254M's giving 45 watts of audio, with a separate, external 600v./200 mA PSU. These items are contained in the narrow-panel units standing on the Tx.

To the right is the station main Rx, the SX-110, with an HF-band Z-match unit above it. Further to the right, behind the microphone, is a 75-watt standby Tx for emergency use.

At lower left, below desk level, is the station control panel, for selecting units and bringing on their power supplies; the main switch on this panel is an automatic circuit-breaker, which "fails safe" if any mains circuit fault develops. This panel also incorporates a mag-slip driven direction indicator for the 15m. rotary beam. Radiation on all other bands



is off the 134ft. aerial, through the Z-match unit—which, says G3JDK, is "worth its weight in gold."

Beside the control panel are cupboards for storage of tools and spares. The operating console may be of some interest because, basically, it is of standard metallised material, with die-cast corner fittings and edging, as obtainable from the local D-I-Y supplier. Cost for main members is in the region of 1s. 6d. per foot run. A sliding writing-top, seen under the right-hand desk level, accommodates the Call Book, the station log and note pads.

It will be observed that this is a very neat installation in the sense of layout. That is only partly because it is in the G3JDK dining-room and so must have the critical acceptance of the XYL! The other reason is that G3JDK has a particular flair for doing his own cabinet work, which is why all these units look "together" and so professionally finished—readers may remember an article by him in the September 1963 issue of Short Wave Magazine, from which the style can be recognised.

G3JDK operates on all bands from 160m. to 10m., CW and phone, DX or local as opportunity offers, and divides his AT activity between building and operating in the ratio 60:40. This means that much equipment is always on the drawing board (including a new SSB Tx) or is in hand for a written-up description in the *Magazine*.

NEW QTH's

This space is available for the publication of the addresses of all holders of new U.K. callsigns, as issued, or changes of address of transmitters already licensed. All addresses published here are reprinted in the U.K. section of the "RADIO AMATEUR CALL BOOK" in preparation. QTH's are inserted as they are received, up to the limit of the space allowance each month. Please write clearly and address on a separate slip to QTH Section.

- G2FUX/A, F. W. Fletcher, 53 St. Ives Park, Ringwood, Hants.
- G3BYX, D. Dowson, 23 Langley Road, Newton Aycliffe, Darlington, Co. Durham. (Tel. Newton Aycliffe 356.) (Re-issue.)
- G3SKO, P. M. Wingfield, Rothelstone House, Bell Street, Swanage, Dorset.
- GI3SLI, 1938291 SAC Osborne, Hut 6, Site 4, R.A.F. Bishops Court, Downpatrick, Co. Down. G3SXZ, W. D. Sargent, 17 Truro
- Road, Gravesend, Kent.
- G3TGQ, P. Taylor, 72 The Course, Eltham, London, S.E.9.
- G3THW, P. J. Walters, 112 Windsor Avenue, Penn, Wolverhampton, Staffs.
- G3TIP, F. H. Gibbons, 11 Gold Street, Barnsley, Yorkshire.
- G3TIS, J. A. Clarke, 40 Morland Avenue, Dartford, Kent.
- G3TJB, D. J. Norman, 98 Hamilton Road, Feltham, Middlesex.
- G3TJG, H. E. Plant, 171 High Street, Chasetown, Walsall, Staffs.
- G3TJK, R. Everitt, Ferndale, Colchester Road, Ardleigh, Colchester, Essex.
- G3TJN, R. W. Pattullo, Hill Cottage, Kirk Merrington, Spennymoor, Co. Durham. (Tel. Spennymoor 2207.)
- G3TJO, E. Box, 15 Blankney Crescent, Lincoln. (Tel. Lincoln 25685.)
- G3TJY, D. R. H. Jolly, D.S.C., 30 York Road, Broadstone, Dorset.
- G3TKB, J. B. Foster, 21 Leechmere Road, Grangetown, Sunderland. Co. Durham. (Tel. Sunderland 71529.)
- G3TKI, D. Bradshaw, The Bungalow, Moorgate, Chorley Old Road, Horwich, Bolton, Lancs. (Tel. Horwich 938.)
- G3TKO, E. E. Snow (ex-9G1DS/ZD1S), 11 Lupton Avenue, Styvechale, Coventry, Warks.
- G3TKQ, G. T. Barrell, Floral Dene, Park Lane, Langham, Colchester, Essex.
- GW3TKZ, W. J. Palmer, 42
 Bloomfield Road, Blackwood,
 Mon.

- G3TLC, A. Marcantonio, 24 St. Laurence Avenue, Brundall, Norwich, Norfolk. NOR.86.Z. (Tel. Brundall 2118.)
- G3TLH, I. D. Brown, 10 Langdale Drive, Flanshaw Estate, Wakefield, Yorkshire.
- G3TLS, B. C. Little, 28 Fitzgerald Road, St. John's Lane, Bristol,
- GI3TLT, H. Irvine, Fernrock, Ballyree, Bangor, Co. Down.
- G3TLU, J. H. Serlin, 25 Parkside Drive, Edgware, Middlesex. (Tel. Stonegrove 7405.)
- G3TLV, G. C. Wynes, 14 Brook Road, East Twerton, Bath, Somerset.
- GW3TLW, T. G. Davies, The Malt House, Llantrisant, Pontyclun, Glam.
- G3TMA, I. Buffham, 99 Pennygate, Spalding, Lincs.
- G3TMI, E. Wood, 18 Dover Street, Canterbury, Kent.
- GW3TMJ, A. Taylor, 24 Emroch Street, Goytre, Port Talbot, Glam.
- GM3TMK, I. M. Ross, 11 St. Duthus Street, Tain, Ross and Cromarty. (Tel. Tain 174.)
- **GW3TMP**, J. H. Jones, 3 Bryn Clyd, Leeswood, Mold, Flintshire.
- G3TMQ, R. J. Harrison, 28 Carmalt Gardens, Putney, London, S.W.15. (Tel. PUTney 9107.)
- G3TMX, Mrs. Sheila Bennett, 73 Guildhall Street, Bury St. Edmunds, Suffolk.
- G3TMY, T. C. Bennett, 73 Guildhall Street, Bury St. Edmunds, Suffolk.
- G3TMZ, D. Greaves, 46 Grosvenor Drive, Walkden, Manchester
- G3TNI, J. F. Clingan, 12A Marlbrook Lane, Bromsgrove, Worcs. (Tel. Hillside 2922.)
- GI3TNK, S. Dornan, 67 Earlswood Road, Belfast, 4.
- G3TNL, P. W. Tynan, 111 Cheam Common Road, Worcester Park, Surrey.
- G3TNZ, K. Drummond, Midholme, Barmoor Lane, Ryton, Co. Durham.

- G8ACK, M. Sugit, 5 Worsley Road, Hampstead, London, N.W.3.
- G8ACZ, P. J. Cox, 51 Bicester Road, Richmond, Surrey.
- G8ADD, B. A. Carter, 57 Gravelly Hill, Erdington, Birmingham, 23
- G8ADU, G. P. Shirville, Tansor Court, Tansor, Oundle, Northants. (Tel. Cotterstock 224.)
- G8ADU/A, G. P. Shirville, No. 2 The College, Malvern, Worcs.
- G8KI, P. C. Mortimore, O.B.E., Pinelands, Beechwood Avenue, Weybridge, Surrey. (Tel. Weybridge 46140.) (Re-issue.)

CHANGE OF ADDRESS

- G2TP, C. W. Andrews, M.C., Tobermory, Grove Road, Beacon Hill, Hindhead, Surrey.
- G3ANW, C. Paxton, 116 Preston Lane, Tadworth, Surrey.
- G3DQW, Peterborough and District Amateur Radio Society, c/o D. Byrne, Jersey House, Eye, Peterborough, Northants. (Tel. Eye 351.)
- G3EHM, K. H. Parkes, 41 Golborn Avenue, Meir Heath, Stoke-on-Trent, Staffs.
- G3FCB, E. D. Melville, R.E.M.E. Inspectorate, B.F.P.O. 34, B.A.O.R.
- GW3GWX, L. P. Jones, Noddfa, Vicarage Road, Llandudno, Caerns.
- G3HDQ, W. Baker, 148 Redditch Road, Alvechurch, Birmingham.
- G3HGD, V. S. Best, 2 Eden Avenue, Dewsbury Road, Wakefield, Yorkshire. (Tel. Wakefield 6429.)
- G3HGJ, D. M. Foster, 31 Glamis Crescent, Rowlands Gill, Co. Durham.
- G3IEX, D. J. Roper (ex-G131EX), c/o 78 Bush Road, Cuxton, Rochester, Kent.
- G3IGL, C. J. Lovelock, 29 Pendell Avenue, Harlington, Hayes, Middlesex.
- G3III, G. P. Lovelock, 6 Compton Bassett, Calne, Wilts. (Tel. Calne 2298.)

- G3JFC, B. M. Stone (ex-VSIGN | VS4BD | VS5BS | VR3L | ZC5GN/5A2CW), 18 Glenluce Road, Blackheath, London, S.E.3.
- G3JMH, V. Callaghan, 18 Dean Close, High Wycombe, Bucks.
- G3JQL, J. S. Haggart (ex-GM3JQL), 22 Alnwick Road, Framwellgate Moor, Durham City.
- G3JRJ, F. Buckley, 18 Sherwood Court, Harrowby Street, London, W.1.
- G3JUC, R. G. Timms, 14 Woodlands Road, Neston, Wirral, Cheshire.
- G3KCB, B. N. Green, 44 Mansfield Road, Flixton, Manchester.
- G3KTZ, C. Lindsay (ex-GM3KTZ), 43 Witherington Road, Holloway, London, N.5.
- GW3KUA, J. Rae (ex-G3KUA | GM3KUA), 64 Coryton Rise, Whitehurch, Cardiff, Glam.
- G3MKV, C. Curtis, 8 Compton Bassett, Calne, Wilts. (Tel. Calne 3010.)
- G3MPN, D. E. Johnson, 3 Folly Gardens, Folly Road, Wymondham, Norfolk. (Tel. Wymondham 3382.)

- GW3MXC, Rev. D. J. Whelan, 27 Elizabeth Avenue, Colcot, Barry, Glam.
- G3NEA, L. J. Saunders, 5 Henleaze Terrace, Westbury-on-Trym, Bristol.
- G30CM, D. A. Hills, South Holt, Danbury, Chelmsford, Essex.
- G30GZ, M. S. Beer, Braizedale Close, Larchfield, Leadhall Lane, Harrogate, Yorkshire.
- GM3ORX, A. G. Rumbold (ex-G3ORX), Valhalla, Tullichewan Road, Balloch, Dunbartonshire.
- G30ZS, D. J. Marrage, South Holt, Danbury, Chelmsford, Essex.
- G3PDM, P. G. Martin, 2 Dence Park, Herne Bay, Kent. (Tel. Herne Bay 391.) G3PFL, W. J. Perkins, Shepherds
- G3PFL, W. J. Perkins, Shepherds Hey, Browns End Road, Broxted, Dunmow, Essex.
- GW3PMR, A. H. Jubb (ex-G3PMR), 1 Friars Terrace, Bangor, Caerns.
- G3PMY, M. J. Harwood, 93 Pine Hill, Epsom, Surrey.
- G3PQE, J. Thorn, 6 Plumtree Close, Sandford Road, Winscombe. Somerset.
- G3PRP, R. G. Poole, 50 Peterfield Road, Whitwick, Coalville, Leics.

- G3PTC, Peterborough Technical College, c/o D. Byrne, Jersey House, Eye, Peterborough, Northants. (Tel. Eye 351.)
- G3RBG, A. L. Gray, 6 Hillingdon Road, Whitefield, Manchester, Lancs.
- G3RBR, F. B. S. Rogerson, 14 Vicarage Road, Winslow, Bucks.
- G3RFH, K. J. Randall (ex-VP8HF), 5 Blakes Crescent, Worston Lane, Highbridge, Somerset.
- G3RKL, A. J. T. Whitaker, 7 Sea View Park, Whitburn, Sunderland, Co. Durham. (Tel. Whitburn 2174.)
- G3RLK, J. H. Longhorn, A.M.I.E.E., 9 Foxlands Avenue, Wolverhampton, Staffs. (Tel. Wolverhampton 35289.)
- G3RUZ, D. H. Martin, 2 Dence Park, Herne Bay, Kent.
- G3SJC, G. J. Perry (ex-VP2SZ), 171 London Road, Horndean, Hants.
- G3SXK, B. J. Doel, South Holt, Danbury, Chelmsford, Essex.
- G4DK, W. H. Morehouse, Flat 6, Damery Court, Fir Road, Bramhall, Cheshire. (Tel. Hillbrook 425.)
- **G8AAP**, G. Toulalan, 9 Shavington Avenue, Hoole, Chester.



The new Heathkit Sideband Transmitter, Model SB-400, is a very interesting piece of equipment, now making its debut. It is a five-band Tx, covering 3.5-30 mc in the amateur ranges, and giving 100w. RF output over 15-80m. and 80w. on 10m., into a 50-ohm load. The SSB rating is 180w. p.e.p. and 170w. on CW, adapted for break-in, using grid-block keying. Sidebands are selectable, and the specification shows a very high order of frequency stability. The PA is a pair of 6146's, and the PSU, using silicon diodes, is self-contained.

RADIO AMATEURS LICENCE

We supply a special course of home study prepared specifically for the Radio Amateurs sound and TV Licence as issued by the G.P.O. It covers every aspect of the syllabus-starting right from the beginning-so that no previous knowledge is necessary. The fullest details of the licence requirements, itself, are included and the method of sitting the examination and applying for the licence is fully described. At the end of the Course, a complete series of specimen exam, questions with fully worked model solutions are provided-giving invaluable revision before students take the exam. We also provide full training for the Morse Code-including morse key, transistor audio oscillator and 12 in. L.P. practice record. This latter equipment is available separately from the Course if required. Our record of successes by our students for the Exam. is unsurpassed by any other institute. Established 23 years. COURSES ALSO AVAILABLE for all subjects in Radio, TV and Electronics and for the City & Guilds Technicians Certificates, etc. Write NOW for full details without any obligation, to :-

DEPT. 20

BRITISH NATIONAL RADIO SCHOOL

Radio House, Russell Street, Reading, Berks.

FIXED OR MOBILE GET WITH IT!

● 70 cms	.A2521 TROUGH LINE CONVERTER. 6D54 nuvistor G.G. mixer, 6BQ7A cascode I.F. 12-16 mc/s. or to order. 6J6 xtal osc. 6D54 multiplier.	£18
● 2 m.	TW-2 10w. TX. Complete with modulator. TW NUVISTOR CONVERTER (6DS4)	_
	any I.F. (With built-in mains supply £15). TW TWOMOBILE. All transistor RX. 144-146 mc/s. Self-contained. TW TRANSISTOR CONVERTER. 1" x 3". Philo transistors. I.F.s 4-6, 14-16, 24-26 mc/s. Suits any RX.	£30
● 4 m.	TW NUVISTOR CONVERTER. Any I.F. Same price as 2m. models. TW4 10w. TX. Complete with modulator. Same price as 2m. model. TW TRANSISTOR CONVERTER. ["x	•
	1" × 3". 1-820-2-020 m/cs.	9 gns.
■ 160 m.	TW TOPBANDER. 10w. TX. Complete with modulator. High stability V.F.O. TW TOPMOBILE. All transistor RX. 1-8-2-0 mc/s.	£23

Mains and Mobile P.S.U.s for the above transmitters, complete with aerial switching, £15

NEW! The TW "Minihalo," only 6" dia. £2 17 6 For full details, write to:-

T. WITHERS (Electronics)

156 GILBERT STREET, ENFIELD, MIDDX.

G3HGE Tel. Waltham Cross 26638

THE SPHINX TX.

Size:— $14\frac{1}{2} \times 6''$ panel. $11\frac{1}{2}''$ deep.

SSB-AM-CW - 160-80-20m. Plus 40m. AM-CW.

PRICE £75 Carr. paid

160M.—£48

160/80M.-£62

For brief specification—please refer to July, Aug., Sept. S.W.M. The latest more powerful Sphinx, 40-70w. P.E.P. now contains II valves, contact cooled bias rect. and 4 xtals. We must emphasize that all these are individually tested for max. emission and activity before they are placed in any of our transmitters. Every transmitter is rigorously tested and aligned before despatch. There are now an ever increasing number of these Tx's on the air. Listen to them and hear the Natural speech quality they put out. No Robot-like sounds. We suppress the carrier not the quality. By now many amateurs will have seen our products at the Rad. Comm. Exhibition. How well made and solid value they are. The Pyramid Linear and Sphinx Rx. prototypes were on display and both will be in production as soon as possible. The Sphinx Tx. is available in 6 different coloured cabinet and panel combinations. We pack them extremely well and they are Ex. Stock. H.P. Terms Part Exchanges

S.S.B. PRODUCTS

7A EDWARD ST. **DERBY 42909**

J. BIRKETT-G3EKX

SHORT WAVE (HULL)

Second-hand Receivers	£	s.	d.
EDDYSTONE 670. Marine HALLICRAFTERS SX! 10. 550 kcs. to 34 mcs.	17	10	0
Amateur bandspread BRT 400. 150 kcs. to 33 mcs. Immaculate	49	0	0
condition	70	0	0
Second-hand Transmitters			
MINIMITTER 2-7 TX. Little used. 24 watts	25	0	0
FALCON 2 METRE TX. 12 volt type	26		0
KW 160 TX. Immaculate	24	0	0
New Equipment			
SPHINX SSB TX. Ex stock	75	0	0
HALLICRAFTERS SXIII. Amateur bands	120	ŏ	ŏ
EDDYSTONE 870A	34	5	8
EDDYSTONE 840C	62	ō	ŏ
EDDYSTONE 940	125	ŏ	ŏ
EDDYSTONE EC 10. New transistor receiver			
Ex stock	48	0	0
EDDYSTONE EA 12. New Amateur bands			
receiver, ex stock	185		0
TELREX 4 element w/s beam for 15 metres	18	0	0
Carriage extra on all the above			
£65 allowed on your Eddystone 888A against a new EA 12			

24a NEWLAND AVENUE, HULL Telephone: 408953

Wanted - your modern receivers, SSB gear, etc.

NEW TITLES-AVAILABLE FROM STOCK

AMATEUR RADIO ANTENNA HANDBOOK. 157 pages, 24s. (by H. D. Hooton, W6YTH)

AMATEUR RADIO, 31s. 6d. (by F. G. Rayer, G3OGR)

BEGINNER'S GUIDE TO ELECTRONICS, 15s. 6d. (Newnes)

BEGINNER'S GUIDE TO RADIO, 9s. (Newnes)

DICTIONARY OF ELECTRONICS, 8s. (Penguin Books)

ELECTRICAL HOBBIES, 5s. 6d. (Collins)

PROJECTS. 157 pages, 24s. (Sams)

RADIO ASTRONOMY FOR AMATEURS. 220 pages, 31s. 6d. (by Frank Hyde)

RCA TRANSISTOR MANUAL, 17s.

RCA TUNNEL DIODES, 16s. (d.

RADIO & ELECTRONIC HOBBIES, 22s. (by F. C. Judd, G2BCX)

SHORT WAVE AMATEUR RADIO, 22s. (by PAØHH, Philips Technical Library)

SINGLE SIDEBAND COMMUNICATIONS HANDBOOK. 285 pages, 56s. (by H. D. Hooton, W6YTH)

SHOP & SHACK SHORTCUTS, 32s. (by D. L. Stoner, W6TNS. Latest "CQ" publication)

SHORT WAVE MAGAZINE

PUBLICATIONS DEPARTMENT · 55 VICTORIA STREET · LONDON, S.W.I · ABBEY 5341/2

SMALL ADVERTISEMENTS

(" SITUATIONS " AND " TRADE ")

9d. per word, minimum charge 12/-. No series discount. All charges payable with order. Insertions of radio interest only accepted. Add 25% for Bold Face (Heavy Type). No responsibility accepted for errors. Replies to Box Numbers should be addressed to The Short Wave Magazine. 55 Victoria Street, London, S.W.1.

SITUATIONS VACANT

TECHNICAL CIVIL SERVICE: Home Office Communications Branch invites applications for Wireless Technician posts at Regional Wireless Depots in England and Wales for installation and maintenance work on VHF and UHF communications systems for Police, Fire and Civil Defence services. Salary: £792 at age 21, rising to £929 at age 25 (this being the highest payable rate on entry), increasing to a maximum of £1,067 by annual increments. Qualifications and Experience: Applicants, who must be natural-born British subjects between 21 and 40, should have a sound and up-to-date knowledge of radio theory and practice, preferably supported by relevant Ordinary National or City and Guilds Certificates. Experience of VHF or UHF equipment would be an advantage. Prospects: All appointments will be in an unestablished capacity in the first place but there are reasonable prospects of establishment and promotion to Senior Wireless Technician (£1,091—£1,285) and Chief Wireless Technician (£1,244—£1,539). Opportunities for further technical education will normally be available.—Further particulars and application forms are obtainable up to 27th November, 1964, from Communications Branch, Home Office, Whitehall, London, S.W.1. Interviews will be in London.

TELEPRINTER Mechanic required with experience of Teletype equipment. Interesting post for RTTY enthusiast. Commencing pay approximately £21 per week exclusive of overtime.—Box No. 4020, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

TRADE

ROTARY converter in silence cabinets. Smoothing, etc., 240v. DC to 240v. AC, 120 watts, £10 each. Carriage £1. WANTED: Hammarlund HQ-170 or EA-12; consider exchange for AR88.—G. Hill, 19 Station Road, Tadcaster, Yorks. (Phone 2253.)

METAL Supplies. Aluminium, Brass, Copper, Steel —in sheets, tubes, rods and sections. Write for free price list.—Senmor Metals, Dept. R/5, 35 St. John's Road, Isleworth, Middlesex. (Tel. ISLeworth 6017)

OSL CARDS AND LOG BOOKS, G.P.O. APPROVED. CHEAPEST, BEST, PROMPT DELIVERY, SAMPLES.—ATKINSON BROS. PRINTERS, LOOE, CORNWALL.

WEBB'S LOG BOOK for recording signals heard and worked; 112 pages $9\frac{1}{4}$ in. x 8in. approved format, semi-stiff covers. Excellent value; 7s. 6d. post free, or callers, 5s. 4d.—Webb's Radio, 14 Soho Street, London, W.1.

OSL CARDS: Buff, blue, pink, green, 100, 15s.; 250, 25s.; 500, 40s.; 1,000, 75s.—Samples (s.a.e.); Reilly, Panxworth, Norwich, 56.Z.

FOR SALE: AR88 medium size knobs, 8 for 14s. or 2s. each. Mail order only.—J. A. Baker, 8 Goldwell House, Quorn Road, London, S.E.22.

R.S.C. (DERBY) LTD. The SPOT, 26, Osmaston Rd., Derby (Tel. 41361)

LAFAYETTE HE.40. SHORT WAVE BROADCAST RECEIVER (3 Band and B.F.O.). Bandspread Tuning and "S" Meter. Only £24/15/- (carr. paid). LAFAYETTE HE.40.

COLLINS TRANSMITTER 310B/1. 5 Band. 6146 in the P.A., £35 only (carr. £1).

2 METRE. 5 element Yagi and Super Mast bracket, 39/6; 8 Element, 59/-; add on 3 elements, makes 5 into 8, 19/6, all plus 5/6 carr. each.

S.S.B. COMPONENTS. 500 ohm, IK and 2K lab carbon linear controls, 6/- each. P. and P. 6d.

I" S.F.6. FERRITE RINGS, 3/9 each. P. and P. 6d. MATCHED PAIR OA79 DIODES, 6/-. P. and P. 6d. EDDYSTONE RECEIVERS and spares.

2" CAST MAST COUPLERS, 9/- each. P. and P. 2/6.

Now a BRUSHING HAMMER FINISH

The modern finish for electronics. (Not crackle finish). JUST BRUSH IT ON, no stoving. It dries as fast as cellulose but is not as inflammable.

Looks fabulous on chassis, cases, panels etc. As supplied to schools, laboratories, and manufacturers throughout the country.

Can also be sprayed using cellulose thinners. In blue or pewter $2\frac{1}{2}$ oz. tins 3/6, $\frac{1}{2}$ pint 7/6, I pint 15/-, post 6d. on any order

From radio and model shops

Trade supplied

FINNIGAN SPECIALITY PAINTS, (SW), Mickley Square, Stocksfield, Northumberland

G4GZ's BARGAINS

VALVES: EA50, EF50, 12SC7M, 1/6 each, 6K7G, 2X2, 6B8G, 6C4, E132, EB91, 6AM6, EF91, 6l6, 2/- each, 18/- doz. 12A6, ARP12, AR8, 1626, TT11, VP23, 2/6 each, 24/- doz. 6J7G, 12K7G, 2C97G, 35X-6G, 959, EF85, EF89, EF80, EZ40, 6X4, 6SL7GT, 80, 12C8M, 12AU6, 12AU7, 12AT7, 42, 6AU6, 6BH6, 6BH6, 6X5, 1R5, 1S5, 6K8G, PCC85, PV83, EZ80, PV82, UABC80, UY41, 4/6 each, 48/- doz. 3A5, 446A, EM80, PU82, EZ81, EABC80, UY41, 4/6 each, 48/- doz. 3A5, 446A, EM80, UAF42, DAF96, DK96, EF89, 50L6GT, 6/- each, 54/- doz. 6L7M, 6L6M, UCH81, ECH42, ECG55, 787, 7C5, 7/6 each, 5R4GY, G232, 9/6, 4E27, 40/-. Post/packing 6d, per valve (1/- min.). Free over 63. Skirted B9A Valveholders, moulded 57, doz. 62, cors. Misclay

40/-- Post/packing 6d. per valve (I/- min.). Pree over £3.

Skirted B9A Valveholders, moulded, 5/-- doz., £2 gross. Micalex ditto 6/6 doz., 55/- gross. Cans 5/- doz. extra.

ET4336 Trans. 190-250v. input, 2½v. 10A CT twice, 10v. 10A CT., 35/-- plus 7/6 carr.

Gunfire Electric Time Switches. 200-250v. A.C. 20A. contacts, offered brand new and boxed. Unrepeatable at only 47/6, plus 2/6 P/P.

IOHN ANGLIN

385, CLEETHORPE ROAD, GRIMSBY, LINCS. Tel. 56315

BUSFIELD'S ASTRO-MARINE

	FOR NEW EDDISTONE RECEIVERS	5			
870A. EC 10. 840C. 940. EA 12.	150 Kc/s-380 Kc/s.; 510 Kc/s24 Mc/s Transistor, 550-1500 Kc/s.; 1,5-30 Mc/s 480 Kc/s1150 Kc/s.; 1,12 Mc/s30 Mc/s 480 Kc/s1030 Kc/s.: 1,03 Mc/s30 Mc/s Amateur Bands, Double Conversion	£34 £48 £62 £125 £185	80000	90000	
LAFAY 550 K	Also ETTE "HE.30" A.C. MAINS RECEIVER. c/s, to 30 Mc/s. Bandspread "Q" Multiplier.	2.00	Ĭ	Ů	

S.S.B. Noise Limiter, "S" Meter. NEW. Price £35 0 0 DIRECTION FINDER AMERICAN MODEL
"NAV. M" 200 to 400 Kc/s, and 500 to 1,500 Kc/s, ex-Govt. surplus. Complete with loop, 2-6 volt power units. Price

Carriage extra at 10/- each

Manual wanted for D.S.T. 100 H.P. - PART EXCHANGE - WANTED GOOD RECEIVERS

45/47 Eastborough, Scarborough, Yorks.

SMALL ADVERTISEMENTS, TRADE-continued

MARCONI Transmitter Power Meter, £5; No. 10 Crystal Calibrators, 37s. 6d.; 40w. power meters, £2 10s.; s.a.e. list.—Worthing Radio, 245 South Farm Road, Worthing.

READERS' ADVERTISEMENTS

3d. per word, min. charge 5/-, payable with order. Add 25% for Bold Face (Heavy Type). Please write clearly, using full punctuation and recognised abbreviations. No responsibility accepted for transcription errors. Box Numbers 1/6 Extra. Replies to Box Numbers should be addressed to The Short Wave Magazine, 55 Victoria Street, London, S.W.1.

FOR SALE: HRO Senior, completely modernised throughout, 6BA6's etc., panel RF trimmer control, noise limiter, crystal marker fitted; with PSU, complete range of nine general coverage coils, 50 kc-30 mc, £20 o.n.o.? Bandspread coils, including 21 mc, £2 each; manual, 10s. Carriage extra (Midlands).—Box No. 4002, Short Wave Magazine, Ltd., 55 Victoria Street London SW1 55 Victoria Street, London, S.W.1.

SALE: R.206, first-class condition, 55 kc-30 mc, front end 50-600 kc, power unit, S-meter. Deliver 30 miles; manual, bargain, £15.—R. Smith,

50 Calfridus Way, Bracknell, Berks.

URGENTLY REQUIRED: Mains transformer for Cossor Oscilloscope type 339A.—Walters, G3THW, 112 Windsor Avenue, Penn, Wolverhampton, Staffs.

2-METRE T.W. T.R. converter, £5 10s. Bargain, Heathkit Rx RG-1, almost new, factory built, £32.—Worthington, 43 Mount Road, Penn, Wolverhampton

EXCHANGE: Compact 8 zoom Projector, new; Volks Ciné 8 zoom Movie Camera, F2.8 Zeika lens, pistol grip, case, both perfect, value approximately £65, FOR best Hammarlund or similar Receiver offered.—Kavanagh, 27 Sandringham Road,

Swindon, Wilts. (Tel. 6885, evenings.)

FOR SALE: Eddystone 640, good condition, unmodified, complete with 3in. external S-meter, £20 o.n.o.? AVO Valve Tester, £3. Small Oscilloscope, £3 10s. Buyer collects.—G3OSK, 77 Southampton Road, Cosham, Portsmouth.

SALE: Eddystone 840C, £46 o.n.o.? VFO controlled CW Tx, 10-metre 10w. C/W int. PSU, £8.

—Marriott, 100 The Crescent, Andover, Hants.

WANTED: Marconi No. 52 Receiver (mains and 12v. operation) must be electrically 100%;

cannot collect but will pay £1 of carriage.—Details to Wilkinson, Craig-y-Don, Conway Road, Penmaenmawr, North Wales.

SALE: Receiver HRO5T, complete with nine coils, matching speaker, power unit and handbook, VGC, £15; Transmitter DX-40U, VFO type VF-1U and 20-metre Quad Antenna, £28; GDO, £4; G.E.C. 36-range Multimeter, £6; BC-221, £12. Prefer buyers collect from Bucks, otherwise carriage extra. WANTED: Electronic Keyer.—Box No. 4003. Short Wave Magazine, Ltd., 55 Victoria Street, London, S W.1

WANTED: Codar PR.30 in fair condition; also Eddystone S.640 manual/data.—Condition and price to S. Richards, Bancroft's School, Woodford, Essex.

WANTED: All knobs for CR-100 Rx; also crystals of 9.000, 11.500, 11.750, 12,000 kc.—G3SJX, Hart, 42 Gravel Hill, Addington, Croydon,

SMALL ADVERTISEMENTS, READERS-continued

NEW and slightly used 4X150A valves, holders, chimneys, what offers? 144 mc Transceiver, mobile, over 700 stations worked on this compact rig, £20; AC power unit for shack use, £4; 70 mc Transceiver, mobile, first-class performance, £20; 70 mc QRO PA unit for QQV06-40A, £10; 70 cm Converter, 6AM4's, £9; 144 mc Nuvistor Converter, 12-volt, £8; 144 mc Nuvistor Pre-Amp, with power unit, £3; Command Rx 3-6 mc, all mods., FB, £5. Load of VHF/UHF equipment available.—State requirements to Box No. 4004, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

DXCC'er has above average S.640 (one owner) for sale, £24. WANTED: 888A.—Box No. 4005, Short Wave Magazine, Ltd., 55 Victoria Street,

London, S.W.1.

SALE: KW-2000 with DC power supply, August 1964 model, £180.—J. H. Winnard, Mount Severn, First Raleigh, Bideford, N. Devon.

WANTED: G8KW Multiband dipole with 97ft. W coax. State price.—G3NAK, 145 Huddersfield Road, Meltham, Huddersfield.

FOR SALE: TCS Rx with PSU and LS, £11 10s.;

Joystick aerial 35c. Procedure Williams

Joystick aerial, 35s.; Practical Wireless, April 1 Joystick aerial, 35s.; Practical Wireless, April 1957 to March 1963, offers? "Natterbox" components (Short Wave Magazine, June 1961), crystals, transformers, etc., 45s., all post extra.—L. Arnold, 24 Albert Road, Stechford, Birmingham, 33.

ALE: Test Card C Monoscope tube; Videcon; Power units 400v. 200 mA, metered; 50-250v. variable output: 250v. stabilised; all with heavy-duty.

variable output; 250v. stabilised; all with heavy-duty heaters, all items £2 each.—G6AAL/T, 127 Horton

Road, Datchet, Bucks.

R.A.F. Halton Apprentices seek 10-80 metre gear for Club station, offers?—G3TFG-ZBIFG, R.A.F. Halton, Aylesbury, Bucks. (Wendover 2242, Ex. 227.)

SALE: Hartley 13A double-beam Oscilloscope complete with leads, manual and graticule, £25 o.n.o.? Heathkit V7A-U.K. Valve Voltmeter with HF probe, £9. Both very good condition. WANTED: Prop Pitch Motor, Hy-Gain 7 mc or 7/14 mc beam HT-18.—G3FPQ, Markham Oak, Bucks Horn Oak, Farnham, Surrey.

FOR SALE: BC-342 Rx, 1:5-18 mc, £7 10s.;

Advance Sig. Generator, 100 1-70

Advance Sig. Generator 100 kc-60 mc, £10; 100 yards high grade twin coax cable, £2 10s.—Crossan, 9 Palace Street, London, S.W.1 (VIC 0252/SPR

6645.1

WANTED: HF-Band Radiogoniometer, ex-D/F apparatus (Adcock station, etc.), with data. Good price paid for instrument in clean condition and working order. Can collect.—Renly Box No. 4010, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

ALLERS ONLY: Valves, Z-Match condensers, Command Rx's, Mains and LP filters, vibrator 12v. etc. Evenings. Lots of junk.—Smith, 54 Fresh-

field Road. Formby, Lancs.

ANTED: Outer main tuning knob for R.107, also antenna terminals; set less above, £9.

Cree, 20 Longwood Lane, Amersham, Bucks.

HAMMARLUND Super-Pro 200v. 0.55-20 mc, rack type with cabinet and 240v. PSU, GC plus BS, £15. Also 10-15m. self-powered CC converter, £10. Also Hammarlund Super-Pro 400X, 1·3-40 mc table model, BC-794B, 110v. PSU, GC plus BS, £15. R.109A Rx, as new. 1.8-3.5-7.0 mc bands, works from only 6v. DC, £3. Will deliver reasonable distance, or buver collects.—G5IC, Oakville, Longden Common, Longden, Shrewsbury.



A SUPERB RECEIVER FOR ONLY £27/10/0 Carriage 10/-

NEW LAFAYETTE COMMUNICATION RECEIVER

MODEL HA-63 7 VALVES Plus Selenium Rectifier 4 BANDS

Covering 55 kc/s.-31 mc/s.

Illuminated "S" Meter. 1.5 microvolt sensitivity. Electrical bandspread. Aerial trimmer. Noise limiter. B.F.O. R.F. stage. Big slide rule dial. Output for headphones or 4/89-speaker. Modern steel cabinet size: 13" x 7 4/5" x 10". Operation 220/240 volt A.C. Supplied Brand New and Guaranteed with instruction Manual. Matching speaker in Cabinet, 55 /-. S.A.E. for full details.

FULL RANGE OF OTHER LAFAYETTE RECEIVERS IN STOCK MODEL HE-40 4 Bands, 550 kc/s,-30 mc/s. £35 MODEL HE-30 9 Valves, 4 Bands, 550 kc/s.-30 mc/s.

Each receiver supplied brand new and fully guaranteed complete with manual. Carriage 101-. All models for operation on 220/240 volt A.C. S.A.E. for illustrated leaflet — generous part exchange allowances.



TM-59'er "S" METER

Signal strength meter using VTVM principles Calibrated in S units. Sensitivity and zero adjustments. For any superhet receiver with AVC. Requires 150/200 volt and 6 or 12 volt. Complete with valve and full instructions. 82 /6. Post and packing 2/6.

CLEAR PLASTIC PANEL METERS

First grade quality, Moving Coil panel meters, available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows Type MR. 38P. I 21/32" square fronts.



32/6 1-0-1mA22/6 150mA 22/6 3v DC 22/6 500v DC 22/6 1004A 29/6 ImA 22/6 200mA 22/6 10v DC 22/6 750v DC 22/6 200μA 27 /6 2mA 22/6 300mA 22/6 20v DC 22/6 15v AC 22/6 500µA 25/- 5mA 22/6 500mA 22/6 50v DC 22/6 50v AC 22/6 50-0-50µA 29/6 10mA 22/6 750mA 22/6 100v DC 22/6 150v AC 22/6 100-0-100µA27/6 50mA 22/6 IA DC 22/6 150v DC 22/6 300v AC 22/6 500-0-500µA22/6 100mA 22/6 5A DC 22/6 300v DC 22/6 500v AC 22/6

Larger sizes available — send for lists

ILLUMINATED ''S' METER. 1 21/32" sa. front. Cal. in S units,
6v. lamp, 29/6, P.P. 1/-; 2 5/16" square, 39/6, P.P. 1/-.

SILICON RECTIFIERS

250v, P.I.V, 750mA 3/- 400v, P.I.V, 500mA 3/6 400v, P.I.V, 3A ... 7/6 200v, P.I.V, 200mA 3/-200v, P.I.V, 6A ... 5/6 95v, P.I.V, 3A ... 5/6 1000v, P.I.V, 650mA7/6 70v, P.I.V, 1A ... 3/6 800v. P.I.V. 500mA 5/6 150v. P.I.V. 1A ... 1/-Discounts for quantities. Post extra

MS-435 SEMI-AUTOMATIC 'BUG'

Super speed morse key. Seven adjustments for speed and comfort. Speed adjustable 10 wpm to as high as desired, weight scale for reproducible speed settings. Precision tooled, anti-rust nickel plated brass and stainless steel operating parts. Size: 6½° × 3° × 2½°. Brand new £4/12/6, post paid.

AR88 LF RECEIVERS

New release. 75-550 kc/s. and 1.5-30.5 mc/s. on 6 bands. 110/230v. A.C. operation. Available in excellent condition, fully tested and checked £35 each, carr. 30/-. A few AR88D model receivers available in as new condition, £65 each, carr. 30/-.

TRANSISTORISED FIELD STRENGTH METER



3 bands 2.5 to 57 mc/s., permits easy tune up for max, transmitter output. Earphone jack to monitor audio. 200µA meter cal. 0-10. Supplied complete with battery, telescopic aerial, £1/7/each. P.P. 2/6.

350 MA R.F. METERS

2" round. Plug-in type, 8/6. P.P. 1/6

LONDON STOCKISTS OF CODAR EQUIPMENT

G.W.SMITH & CO. (RADIO) LTD. 3-34 LISLE STREET, LONDON, W.C.2

ne: GERRARD 8204/9155 Cables: SMITHEX LESQUARE OPEN 9 a.m.-6 p.m. EVERY DAY MONDAY TO SATURDAY

Send 1/- P.O. for full catalague and lists

G. D. COMPONENTS

RETURN OF POST

DELIVERY ON THE FOLLOWING:

- New OC29 Power Transistors, 7/6 each.
- Heat Sink for mounting 2 of the above or similar types, 3/6 each.
- Silicon Rectifiers, 800v. P.I.V. 4 amp., 6/- each.
- Plug in Relays. Double Pole Changeover, Octal Based. 6.3v. A.C. or 12v. D.C. Ideal for mobile or antenna switching, 25/- each.
- Co-Axial Relays, brand new and boxed, 450 mc/s. max. At 50 watts of R.F. 6.3v. A.C. or 12v. D.C., 75/- each.
- Modulation Transformers. For 30 watt P.A. Primary IOKs. centre tapped to a 5.5Ks. secondary. Small size and brand new, 30/- each.
- Cooling Fans. Silent running on 230v. A.C. Ideal for P.A.'s, Linears, etc. Chassis mounting brand new at 23/-.
- Field Strength, Meter type, R.F.40. 1-250 mc/s. Brand new and boxed, 55/-.
- Linear Amplifier Plate Chokes. IKW. 80 to 10 metres, £1.
- A.C. to D.C. Power Module. 1250-0-1250 A.C. Input 1700y. D.C. at 500 m/A. Output. Compact size, £12.
- 300 mfd. at 500 volt Electrolytics. $4\frac{1}{2}$ " x $1\frac{3}{4}$ ". 35/- each.
- D.C.—D.C. Converters. 12v. D.C. Input at 6 amps. 300v. D.C. Output 175 m/A, £7/19/6.
- Nuvistors, type 6CW4, with base R.C.A. Boxed.

PLEASE ADD POST AND PACKING TO ORDERS

DEPT. S., G. D. COMPONENTS. 104 HORNSEY ROAD, LONDON, N.7.

'JOY' NEWS No. 3

For TRANSMITTING AMATEURS & S.W.Ls.

Whatever your favourite band — 160, 80, 40, 20, 15 or 10, the "JOYSTICK" will put you among the QSO's. Whether you live in a bungalow or ground floor room with no garden, you can trust the "JOYSTICK" to pull in the DX and fire a potent signal in all directions.

1,500 delighted customers bear constant witness.

"Worked GW on CW with 'JOYSTICK' standing on the ground (160 metre band). My sigs. were 579. Compare with his report 589 using 500ft. wire!!!"-M. Turner, G3LYE.

Never was 6 band mobile operating made so easy, and at such low cost. No more coil changing, or external adjustments, 25 /- from stock, plus Standard "JOYSTICK."

The mobile version of the "JOYMAST"—guys hook under car wings - puts out a terrific signal from your selected vantage point, £2/15/- from stock, less standard "JOYSTICK."

FULL MONEY-BACK GUARANTEE!

PARTRIDGE ELECTRONICS LTD.

7, Sowell Street, Broadstairs, Kent

SMALL ADVERTISEMENTS, READERS—continued

RADIOVISION Commander, double superhet, 1.7-31 mc plus full-scale calibrated bandspread, partly miniaturised, EF183 RF, etc., handbook, £16. Olympic 75w. de luxe Z-Match (loaded), £6. DA-1 electronic keyer (new), cost £16 10s., accept £12 10s. o.n.o.? Surplus Conversion Manuals, set of 3, 10s. each. Modified Command modulator (mains), xtal mic. pre-amp., £1. 160m. VFO, 10s. Prefer buyer collects or carriage extra.—G3JFC, 18 Glenluce Road, Blackheath, London, S.E.3.

TRANSISTOR Bargains: OC16, 10s.; OC22, 12s.

TRANSISTOR Bargains: OC10, 108.; OC22, 128. 6d.; OC23, 158.; OC24, 158.; OC36, 128. 6d.; OC71, 38.; OC77, 48. 6d.; GET573, 108.; GJ5 diode 300v. p.i.v., 1 Amp., 28. 6d.; p. & p. extra, s.a.e. list, other types Orders over £2 post free. numerous other types. Orders over £2 post free.

Tynan, 29 Elm Walk, Stevenage, Herts.

QAOA working order, £18; buyer collects,

840A, working older, 210, out of handbook, Essex. Hallicrafters SR-150 handbook, Magazine Ltd. 15s.—Box No. 4006, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

RTTY TELEPRINTER SCOOP: 43 Type 7B page printers for sale. Also two wavemeter/sighal generators 140-255 mc, xtal check, with instruction manual and mains PSU, £2 10s. TF517 Signal Generator 10-300 mc, £3 10s. 25w. CW transmitter, Geloso VFO, mains PSU, £10. Carriage extra; s.a.e. details and price of T/P's.—G3LMR, 112

Groby Road, Glenfield, Leicester.

FOR SALE: AR88D, excellent condition, £40—or
HRO with bandspread coils, covering 80m., 40m., and 10m., and general coverage, haggle around £25.

—F. Nurse, 31 Woodfield Avenue, Colindale,

London, N.W.9 (COL 4791.)

R-100 Receiver. Loan or purchase of the manual for this receiver required by B. Gordon, 72 Coldshott, Holland, Oxted, Surrey

WANTED: Mod. xformer UM-1 or similar, also Eddystone 898 dial.—Maxwell, 367 Gower Road, Killay, Swansea (Tel. 22909.)

HRO coils 3.5.7.3 mc, 50-100 kc, 10s. each, post 2s. 6d. each. New valves: ECF80, ECH81, EF80, EF85, EF89, EBF89, EABG80, EBC81, EL84, EF80, EF81, ECC81, ECC82, ECC85, EM80, EM81 EZ80, EZ81, ECC81, ECC82, ECC85, EM80, EM81, EM84, 4s. each: p. & p.—J. Cooper, Churchfield Road. Outwell, Wisbech, Cambs.

R88LF, S-Meter, £30; Mullard Bridge, £3; Cossor A Pattern Generator Type 1320, £7, all with manuals. TBS, Tx and Rx, 60-80 mc, £2 10s. each. Buyer must collect.—G3RZD/T, 9 Park Lane,

Southwick. Sussex.

R.107, good condition, £10 o.n.o.? Buyer inspects, but will deliver London area. M/c Milliammeters, 2in. flush round, 0-50, 0-100, 0-200, 7s. 6d. plus 2s. Two 813's with bases, £1 each plus 2s. Maintenance manual for Creed 7B T/P, 4 µF 1.500v. capacitors, 3s. plus 2s. New Muirhead S/M drives with vernier blocks, etc., 10s. plus 2s.—Box No. 4007, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

BC-221, complete, £15. Panda Cub and mannual, £35. HRO modified with B7G valves and product detector; five bandspread coils, 80, 40, 20, 15, 10, PSU, manual, £25.—G3HDA, 98a Lea Green Lane,

Wythall. nr. Birmingham (Wythall 3338.)

W/ANTED: Viceroy Mk. IV. SALE: Olympic 250w. loaded Z-Match; HRO coils 10-15-80m. BS with one 80m. GC; MC-70 studio crystal mike. Offers?—Box No. 4009, Short Wave Magazine, Ltd., 55 Victoria Street. London, S.W.1.

WANTED: BC-453.—Fabricant, 5 Benscliffe Drive, Loughborough, Leics. (5118 after six.)

SMALL ADVERTISEMENTS, READERS-continued

EDDYSTONE S.640, in very good condition, complete with matching loudspeaker and manual, £19; AIR Inverter, input 110v. DC, output 110v. AC, 60 c/s, 350w. continuous, almost as new, £22 o.n.o.? Eico 720 90w. CW Tx, 115v. AC input, electrically OK, although exterior marked, £22. All above buyer please collect. Joystick, new, 35s.; Type 5 Joymatch, 10s.; HRO bandspread coils 80, 40, 15 metres, very good condition, 50s. each. (Oxford).—Box No. 4008, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

OR SALE owing to bereavement: Viceroy Trans-FOR SALE owing to bereavement: Viceroy Transmitter Mk. III with filter; AR88 Receiver (rewired), other items. Send for list.—Aram, 23 Elmshurst Gardens, Tonbridge, Kent (Tel. Tonbridge)

2969.)

SALE: Type 3 Teleprinter with spares and power pack, £15; 35 reels paper tape, 35s. Marconi T.F. 428A Valve Voltmeter, £4. Post Office rack with swing doors, £5. No. 9 Rx with power pack, £5. Terminal unit C.F.S. ZA-39384, £5. Tape perforator, £2. ATU for 52 Set, 15s. Collins ATU, new, £1. De large Loyetick, with all-conner RF elements, £3 5s. luxe Joystick with all-copper RF elements, £3 5s. Acos mic. 39, £1. Angle-iron rack, £1. Minimitter converter, Amateur and Commercial, £15, as new.—B. Davies, 16 Mulkern Road, Holloway, London,

FOR SALE: Eddystone S.640 with Eddystone speaker and Smeter, £20.—G3KTL, 30 Sudbury Drive, Cheadle, Cheshire.

A UTO TRANSMITTER 6S5, AC mains, hammer-grey finish, £50; no offers, worth £80.—Box No. 4011, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

WANTED: Miniature Tx/Rx type RT-159B/ URC-4; also 30s. offered for manual for the above. Will pay good price for all types of manuals, handbooks, etc. relating to suitcase-sets, used by Forces.—Gee, 11 Whitehorse

Resistance Forces.—Gee, 11 Whitehorse Lane, Stepney, E.1.

SALE: Minimitter mobile whip Antenna, 160-metre, mounted on one section of Skirack for metre. attachment to roof of car; together with 80-metre coil and top section, £7 10s.—G3RDC, QTHR,

Speedwell 8831.

A R88D, as new, manual and tools, £50. TA-33 Sr. traps etc., £10. Sterns Mullard 5/10 Amplifier, £9. Two-valve pre-amp/equaliser for above, £5. Pair QY3/125's with bases, £4. 2C39A, £3. FM tuner, £5. New bug-key, £3. Crystal calibrator, £1. FT241 crystals for G2DAF Rx filter, £2. WANTED: BC-348 Rx in good condition.—Ring G3LAS, Berkhamsted 1186 (QTHR).

hamsted 1186 (QTHR). TIGER TR.60B in excellent condition, with Tiger Z-Match and Minimitter LPF, £55 o.n.o.? Carriage paid. Minimitter Top 2-7, 24w. excellent, £21 (10s. carriage). HRO-MX, 9 coils and power supply, £21 (£1 carriage); Jackson C.804 capacitors 15 and 30 $\mu\mu$ F, brand new, suitable tuning B.44, 3s. 6d. each, post 6d.; A.M. Morse keys, 12s. 6d., (2s. 6d. postage), few only. Meters, components, many new items; s.a.e. for enquiries.—G3MOE, Westbury Road Cheltenham Glos. (24217.) Road, Cheltenham, Glos. (24217.)

WANTED: Junk AR88D at junk price for spares; also VTVM and 'scope for fair price.—G3AAJ, $O^THR.$

FOR SALE: Minimitter MR.44 Receiver, £25; Brenell MR.5 Tane Recorder, £25; BC-221 Freq. Meter with mains PSU, £15. All excellent working order. Delivery reasonable distance.—FIN 7262 evenings or weekends, not Tuesdays or Thursdays.

FREE BLUEPRINT

TO BUILD BEGINNERS'

SHORT-WAVE **SUPERHET**

and simple **Alignment Oscillator**

- * Coverage 1.67—31.5 Mc/s
- * Plug-in coils
- * 5-valve circuit using 1.6 Mc/s intermediate frequency
- * Separate power pack
- * Panel aerial trimmer

Plus constructional details for Oscillator to align this and other receivers.



DECEMBER ISSUE OUT NOW GO FOR YOUR COPY TODAY - 2/-

FLAT DWELLERS, THE

Olympic 'Loaded Z-Match'

Solves Your Aerial Problems

NO MORE UNSIGHTLY . . . **INDOOR AERIAL CONTRAPTIONS**

We Guarantee as good Results on just 33ft. of Insulated Wire completely hidden behind picture rail and coupled to TX via our new Coupler.

(The XYL WILL be pleased!!!)

Well over 300 already sold

Send 4" x 9" SAE for leaflets to

OLYMPIC WORKS

136a Markham Road, Bournemouth, Hants.

SHORT WAVE AERIALS IN STOCK

AERIALITE SPOXO 80 £3.19.0 An 8-element 2 metre array. Carr. 7/6 MOSLEY MODEL RD.5 £8.0.0 Dipole antenna kit for 10-80 metres. P. & P. 1/6 MOSLEY MODEL SWL-7 £7.0.0 Dipole Kit. For II-49 metres.

STOP PRESS!! We now have in stock the famous Eddystone Transistor H.F. Communications Receiver. Price £48. Full details free on request.

NEW CATALOGUE

Our new Catalogue, price 5/-, is bigger and better than ever. On the first page are 5 coupons, each worth 1/-. For each complete £1 of your order enclose a coupon and deduct 1/- from the money you send. If you buy £5 worth of components-even though spread over several years—your catalogue will have cost you nothing! Send a P.O. for 6/- (5/- plus 1/postage) right away.

HOME RADIO LTD

Dept. SW, 187 London Rd., Mitcham, Surrey

SMALL ADVERTISEMENTS, READERS-continued

CALE: Two Parmeko 'C'-core potted trans-SALE: Two Parmeko 'C'-core potted transformers, rated 500-0-500v. at 250 mA and four separate LT windings, £2 each; also five 8 μF at 1,000v. DC paper capacitors, 7s. each. All plus postage.—G3SWH, 66 Pettigrove Road, Kingswood,

R-100 with S-meter, manual, £17; CR-300 with manual, £14; Scott Marine Rx, 1.9-22 mc with manual, £8; Marconi Oceanspan Tx with manual, £5; Marconi Auto-Alarm with manual, £3. Also other gear.—G3IGG, 26 Hooton Way, Hooton,

Wirral, Cheshire (Hooton 2009.)

SB Transmitter etc. required for The Norfolk
Amateur Radio Club Station, Will collect 100

miles.—Secretary, 140 Oak Street, Norwich.

FOR SALE: Canadian No. 52 Set with all parts,
£16; 62 Set, £4 10s.; Creed 3x Printer and PSU, £6; TV, £2; 10-line exchange, 30s.; 19 Set PSU, £1; B2 Rx, 10s. More oddments. Buyer collects.—Taylor, Hollydene, Beckenham Lane, Bromley, Kent (RAV 8776.)

SALE: Collins TCS Tx Modulator preamp. on crystal platform, otherwise unmodified, £9. Collins TCS Rx, noise-limiter model, 3-ohm output transformer, otherwise unmodified, £9; Heathkit 465 kc Q-Multiplier, assembled and as new, £7 10s.; 10s.—G3PTD, 185 Bispham Road, 1/813, £1 Blackpool.

IST of Tape Library addresses free, 2½d, stamp appreciated.—D. French, 136 Tollington Park,

Stroud Green, London N.4.

SALE: Complete SSB station: KW-77, K.W.
Viceroy Mk. III, mike, RME DB-23 preselector, Dow Key Ant. relay, two years old, cost over £300, mint; no serious offer refused.—G3FWB, Hunt, 10 Weston Way, Weston Favell, Northampton (Tel. 36258 day, 35876 evening.)

TOP BAND CW transmitter, VFO control, £5; Radiocraft Type 46 transmitter, crystal control, phone (CW 80/10 metres 55—Reth 4 Compdense)

phone/CW, 80/10 metres, £5.—Roth, 4 Camden

Road, Somerton, Somerset.

FOR SALE: DX-100U, perfect, with manual, £50 o.n.o.?—G3OMY, 191 Dudley Road, Springfield,

Dudley, Worcs.

FOR SALE: K.W. converter, 10-80m., brand new condition, £15.—GW3TMP, 3 Bryn Clyd, Lees-

DISABLED SWL has for sale Transistor Signal Generator, 150 kc to 300 mc, new, cost £9 10s., sell £6 10s. or EXCHANGE S.38 Receiver or any receiver. Crystals 100 kc, 500 kc, 7s. 6d. each.—Box No. 4012, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

MARCONI CR-100, 6SG7, RF's, S-meter, hand-book, good condition, £17.—GW3PPQ, 25 Fouracres, Llantwit Major, Glamorgan.

FOR SALE: AR88D, new condensers and aligned, f22. Buyer arranges collection.—Peers, 3 Monks Brook Close, Eastleigh, Hants.

FOR SALE: CT.84 miniature 'scope, instructions, circuit, leads, case, transformer, £14. Nombrex Sig. Generator, new, £6 10s, 38 Set complete, £1. Transformers, valves, etc., £1, or EXCHANGE lot for good general receiver. No dealers (London).-Box No. 4013, Short Wave Magazine, Ltd., 55 Victoria Street London, S.W.1.

EDDYSTONE S.640 fitted RF EF85, ECH81 and crystal calibrator, mint condition, £21. Reslo ribbon mic., type R.V., £3 5s.—Box No. 4015, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

SMALL ADVERTISEMENTS, READERS-continued

SALE: Modified Redifon RTTY T/U ZA39384, 465 or 735 kc input, built-in mains PSU, £10 o.n.o.? Carriage extra.—G3NPF, 130 Ashingdon Road, Rochford, Essex.

Road, Rochford, Essex.

SPACE REQUIRED: Hammarlund SP600/JX6, Cabinet table model, new and almost mint condition, complete with full U.S.A. technical maintenance manual, £165 o.n.o.? Tiger TR2M 2-metre Tx, 75w. 'phone, brand new (list £85), £55. Tiger 2-metre Cascode Nuvistor converter, IF 28-30 mc, new, £8 10s. K.W.-160 Mk. II, brand new, £20. Marconi UHF Sig. Generator TF.762/A, 400-600 mc, brand new, complete with manual, £15. TF.912 Tx output meter, 0-25w., £6 10s. BTH UHF Wavemeter, 250-850 mc, uses 4in. 50 μA meter, £5 10s. Mobile 2-metre Tx complete (PTC-115) QQV03-20 PA, excellent condition, with manual, £8. Command Rx 28-41 mc, £3; 1-5-3 mc model, new in carton, £9. BC-453, same condition, £7 10s. Browns Type "F" phones, new, 25s. Special quality U.S. Air Force, 21s. RF-26B, brand new, 25s. All plus carriage costs. WANTED: R.216, preferably complete with PSU, also first-class Oscilloscope, single or D-Beam, Cossor, Solartron, Heathkit, etc.; also GD-1U. Any of these requirements accepted in PART EXCHANGE for the above equipment; cash adjustment either way.—Box No. 4014, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

CR-100/8, brand new with manual, £29 or exchange for best 35mm. magazine loaded slide projector with screen.—Arends, 18 Granada Road, Denton, Lancs. (DEN. 4937.)

WANTED: Valiant Tx 10-160 metres, will pay up to £40 for late good clean model and collect up to 50 miles.—G3GQ, phone Hatfield Woodhouse 230.

MK. I 32ft. Vertical Aerials (see June Short Wave Magazine), £3. K.W. all-band dipole (new), £4 2s. Tx cabinet 19in. x 12in. x 18in., grey, £2 15s.

Call—11 St. Edwards Road, Birmingham, 29.

FOR SALE: BC-221 Frequency Meter with internal mains power pack (stabilised), £15.—Good, Rose Cottage, Steeple Morden, nr. Royston, Herts.

Cottage, Steeple Morden, nr. Royston, Herts.

FOR SALE: 40w. 6-band Mobile Station comprising K.W. Valiant Tx, K.W.76 double conversion Rx and Aveley 425v. Transistor PSU, £65. Will not separate. Withers 2-metre transistor converter, IF 4-6 mc, £6 10s.—G3KNB (QTHR.)

FOR SALE: CR-100/8 mod., with Codar PR30X, splendid performance, £16.—Phone TOT 6632, 189 The Avenue, Tottenham, London, N.17.

TWO APG5 12 cm. Transmitter/Receivers, £6 each.

Pye Television Monitor, as new, £12. Vitavox

B.50 mobile hand mic., unused, 35s. (cost £6). Many

Valves, Crystals and components very cheap, e.g.
6J5G, 1s.; U18, 2s.; s.a.e. list. Post extra.—Liv 8489,
after 7.30 p.m. V. Cedar, 2A Convent Hill, London,
SE 19

WANTED: HRO-5T in mint condition, with bandspread coils.—Fletcher, 43 Park Lane, Whitefield Manchester (Tel. WHI 5165.)

WANTED: A Novice Band in the British Isles.— C. Forrister, 368 Rush Green Road, Romford, Essex.

WANTED: SSB Tx and Rx, such as Hallicrafters, Collins or similar, also Vanguard. Cash.—Box No. 3073, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1


Street. London, S.W.1.

FOR SALE: DX-100U, in good condition, £40.

Delivery free 30 miles.—Wickham, 56 Kings Road,
Walton-on-Thames, Surrey.




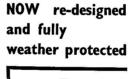HENRY'S RADIO Ltd. PAD 1008/9 Mon.-Sat. 9-6 p.m.
303 EDGWARE ROAD, LONDON, W.2 Thurs. 9-1 p.m.



The MINIMITTER BIRDCAGE F.M. AERIAL

Mk. 2

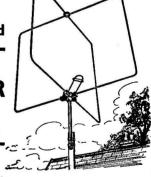

- Suitable for 88-108 Mc/s.
- High Gain (+9.5dB) with high Front to Back (-35dB) and Front to Side (-30dB) ratios.
- Full wavelength elements reduce interference.
- Elimination of vertically polarised signals gives freedom from aeroplane "flutter."
- Tuning facility incorporated to enable the cable to be accurately matched to the aerial.
- Suitable for loft or outside erection.

Retail price £5 (+ 4/6 post and packing)

Trade Enquiries Invited

Order direct from

MINIMITTER (1964) Ltd. Albion Mews, Kilburn High Road, London, N.W.6 (MAlda Vale 5588)

Manufacturers of Specialist Aerials and Aerial Equipment for the Entertainment and Communication Industries.



The world-famous copper loaded alloy containing 5 cores of non-corrosive flux, that saves the soldering iron bit. Ersin Multicore Solder is also available in high tin quality alloys. 60/40 in 22 s.w.g. for printed circuits, transistors, etc.

THE HANDY DISPENSER



Easy to find in the tool box-simple to use. Virtually a third hand for tricky soldering jobs. 12 feet 5core 18 s.w.a ERSIN MULTICORE

SAVBIT alloy in a continuous coil used direct from freestanding dispenser.

2/6 each

SAVBIT ALLOY saves wear on soldering iron bits

BIR RECORDING TAPE SPLICER

Gives a professional touch-A handy precision tool allows quick and accurate editingno wastage or post-editing clicks. Can be mounted direct on the tape deck. It uses all your odd lengths of tape. 18/6 each



BIB WIRE STRIPPER AND CUTTER

Strips insulation without nickina wire, cuts wire cleanly, adjust-able to most thicknesses. Splits extruded plastic twin flex. 3/6 each



MULTICORE SOLDERS LTD.

MULTICORE WORKS . HEMEL HEMPSTEAD . HERTS. (BOXMOOR 3636)

CMMS 448

G. W. M. RADIO LTD.

RECEIVERS

CRI00/B28. 60 kc/s. to 30 mc/s., crystal filter, B.F.O., two R.F. and two I.F. stages. 6V6 output, 230 volts A.C. power pack built in, only needs speaker and aerial. Good condition and working order.

R.1132. Tunable 100 to 125 mc/s., easily altered for other frequencies, in good condition, £5, carriage 15/-

P104 (R1392). Crystal controlled 100 to 150 mc/s. 13 valves, A.G.C., B.F.O., R.F. and L.F. gains. Tuning meter. In good condition complete with simple instructions for conversion to tunable

POWER UNIT, TYPE 3, 230 volts A.C. Supplies 250 volts 100 MA. and 6.3 volts 4 amps. to suit above R1132 and P104, £2/5/-, carriage 10/-. A few available with damage externally to handles, switches, etc. But good working order at 35/-, carriage 10/-.

TRANSCEIVERS. 6 volts D.C. input. Ex-motor cycle installation, approximately 120 mc/s., less crystals. Complete with control box and handset, £4/10/-, carriage paid.

230 VOLTS A.C. POWER UNITS FOR SCR522 TX/RX. Dry and clean, 50/-, carriage paid as they come.

METERS. 2" round 500 microamp, scaled 0-15, 0-600 volts, or 0-500 microamps, ex-equipment, tested. Either type 8/6, post 1/6. 2½" round 0-100 MA., 8/6, post 1/6.

VALVES 807. Ex-equipment, 3/6, post 6d.

RELAYS. Ex-equipment, 12 volt coil, single make 50 amp., silver contacts, 3/6, post 1/6. New 1000 ohm. high speed single pole changeover. Ideal for remote keying, 7/6, post 1/6.

AERIAL TUNING UNITS. Made for Collins TCS12, I to 12 mc/s. Good condition, 12/6, post paid.

FIELD STRENGTH METERS. 100 to 150 mc/s. Telescopic chrome aerial. 2" round 0-1 MA. meter. 155 valve needs 90 and 1.5v. batteries or can easily be replaced by crystal diode, 35/-, post paid.

All equipment offered is complete but not tested unless otherwise stated. Carriage charges quoted are for England and Wales only.

Terms: Cash with order. Early closing Wednesday.

40-42 PORTLAND RD., WORTHING, SUSSEX

SMALL ADVERTISEMENTS, READERS-continued

STEEL Tower, 32ft., in two sections, with rotator and TA-32Jr. Beam. Also Hallicrafters Top-Band Portable Tx/Rx. Offers? — Scarr, Treeton Road,

Howden, E. Yorks.

MINIMITTER Top 2-7, excellent condition, £20.—

Road, Howden, E. Yorks.

MINIMITTER Top 2-7, excellent condition, £20.—

EXCHANGE: 500 Bun pennies, 150 H and KN pennies, plus mint 10 x 50 binoculars with case, plus cash, for best Radio Receiver offered. Also WANTED: outside aerial for general coverage Receiver.—Coldwell, 154 Bradway Road, Sheffield. 750% or 850v. 250 mA power supplies; also give 6.3v. 7A. 300v. 100 mA, Bias 200v. with two FW4/500, 5Z4 small size, 90s.; buyers collect. Transformers, Admiralty rated, from above, £3, including post. Marconi Sig. Generator TF-390G, 16-250 mc, as new, £10, crated, including charts, spares. WAN1ED: Eddystone Smeter.—B. L. Cedar, 2a Convent Hill, London, S.E.19. (Tel. Livingstone 8489,

evenings.) HRO, six coils with HRO PSU and preselector collects. WANTED: Eddystone 640.—GW3LSB, Holcombe, Vicarage Avenue, Llandudno, Caerns.

ZC-1 Mk. II, 160 and 80 metres, pi-output, mains powered, but complete with vibrator unit removed from Set, £8. Buyer collects or carriage extra.

G30ZA, 9 Erneston View, Corsham, Wilts.

POR SALE: K.W.-77, £70. London area.—Box No.
4016, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

R. 107, excellent condition, £10; Mohican, £14, or PART EXCHANGE general coverage Receiver, AR88, etc.—Westwood, 114 Pettits Lane, Romford.

(Romford 47577.) QRT SALE: DX-40U, VF-1U, Olympic loaded Z-match, LP filter, co-ax relay, £30; Eddystone S.640, Codar preselector, £25; Top Band CW/phone TX, £10.—Box No. 4017, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

62 Short Wave Magazines, 1957-1963, mint condition, indexes, 25s. Buyer collects.—Bennett, 130 Avenue Road Acton London, W.3.

130 Avenue Road, Acton, London, W.3.

MINIMITTER MR-44/II Receiver, new condition, £35, or EXCHANGE Eddystone S.750 or similar general coverage receiver. Two Command Receivers less valves, 30s., unmodified. Berks.—Box No. 4018, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

SALE: SX-101A Receiver, ideal SSB, immaculate condition, £95; or EXCHANGE for Eddystone 770R or similar VHF Receiver.—King, G3ACB,

OTHR or Sanderstead 3943 after 7 p.m.

PANDA PR-120V, 5-band 150w. Tx, £45. Excellent condition. Buyer to inspect and collect, please.— G3NLY, 20 Bridge Cross Road, Chase Terrace, Walsall, Staffs.

OR SALE: DX-40 with VFO, £25. Wavemeter FOR SALE: DA-40 with And Charts, £8 o.n.o.?-Sgt. Akehurst, Royal Signals Camp, Newton Abbot, Devon

KW-77 Receiver with matching speaker, manual, also Hy-Gain 14 AVS vertical antenna with LC.80 loading coil, very little used. £85 complete.-W. Sneedie. Barnbeth, Bridge-of-Weir, Renfrewshire. SALE: Short Wave Magazines, August 1956 to February 1964, £5: R.S.G.B. Bulletins, November 1957 to December 1963, £4: 1958 ARRL Handbook, 12s. 6d.; Antenna Book. 7s. 6d.; Multimeter, £1; TCS loading coil, 10s.: \(\frac{1}{2}\)in. coax. etc. for callers.— 118 College Hill Road, Harrow Weald, Middx.

SMALL ADVERTISEMENTS, READERS-continued

MANTED: ZC-1 RX/Tx for 160-80 metres. All letters answered.—Box No. 4019, Short Wave

Magazine, Ltd., 55 Victoria Street, London, S.W.1.

WANTED: Crystal Calibrator Mk.10 or similar.
State full details including range, condition, price.—1 Homemead Avenue, Leicester.

FOR SALE: BC-453, £5 10s.; RF.26B, 35s.; R.216
Power Unit, £12 10s.; AVO All-wave Signal
Generator, £10. All new, unused. Marconi TF-340 output meter, £10. SX-28A Mains Transformer, £3; CR-100 Manual, 35s.—A. J. Reynolds, 139 Waller Road, New Cross, London, S.E.14. (Tel. New Cross 1443 after 7.30 p.m.)

G73 Wavemeter with xtal calibrator, good condi-tion, £10 o.n.o.?—Barr, 21 Whitecross Road,

Lydney, Glos.

K.W. built, 10-16m., The Crescent, Donnington, Wellington, Shrops.

R.107 Handbook, S-meter, coax, input, spare valves, vibrator, rebuilt, professionally realigned, FB condition, £12.—Macdonald, Gracie Hall, Wake Green Road, Birmingham, 13.

WANTED: Transformers (1) Ex-SCR.522 mod. or DT-1; (2) Woden UM-2; (3) Parmeko type 620, 550, 375v. outputs.—Harkess, GM3THI, 8 Ailsa Street, Prestwick, Ayrshire.


MADE MORSE EASY

The famous RHYTHM RECORDED COURSE cuts practice time down to an absolute minimum!

One student, aged 20, took only 13 DAYS, and another, aged 71, took 6 WEEKS to obtain a G.P.O. pass certificate. If you wish to read Morse easily and naturally, enclose 6d. stamp for full explanatory booklet to:

G3HSC, THE MORSE CENTRE (UPLANDS 2896) 45 GREEN LANE, PURLEY, SURREY

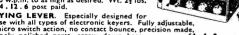SEMI-AUTOMATIC "BUG" SUPER-SPEED MORSE KEY. Seven adjust-ments, precision tooled, speed adjustable 10 wp.m. to as high as desired. Wt. 2½ lbs. £4.12.6 post paid.



£4.12.6 post paid.

KEYING LEYER. Especially designed for use with all types of electronic keyers. Fully adjustable, micro switch action, no contact bounce, precision made, finely polished parts, screw down base.

TRANSISTORISED FULLY AUTOMATIC ELECTRONIC KEYER. (illustrated) 230v. AC or battery operated. Incorporates built-in monitor oscillator, speaker, and keying lever. Adjustable speeds, giving either auto, semi-auto or hold. 7 transistors, 4 diodes. Price £16.10. + 4/6 p. and p.

semi-auto or hold. 7 transistors, 4 diodes. Price EID. 10. T 700 p. and p. TRANSISTORISED MORSE OSCILLATOR. Fitted 24" moving coil speaker. Uses type PP3 or equiv. 9v. battery. Complete with morse key. 22/6 + 1/6 p. and p. All mail orders, also callers to:-

SERVICE TRADING COMPANY

47, HIGH STREET, KINGSTON-ON-THAMES, SURREY Personal callers only at KIN 9450 9, Little Newport Street, London, W.C.2 **GER 0576**

Vertical Aerial or Light Mast Kits

10 x 3' sections x \(\frac{1}{6}\)" dia. tubular steel, with 14' Whip Aerial, total height approximately 45'. Insulated base, adjustable rope guys, pegs, hammer and reamer. All complete in canvas carrying bag. New surplus.

Price: £3 15s. per KIT, Carriage paid

H. H. BRADFORD LTD. RAMSEY, NEAR HARWICH, ESSEX



A life time of experience and aerial "know-how" A little time of experience and aerial "know-how" has gone into the development of this revolutionary principle of a Variable Frequency Antenna on which World Patents are now pending. Possessing the unique property of an even performance over all frequencies between 1.5 and once, the Joystick's special matching facilities and associated A.T.U. ensures efficiency on any frequency. requency. Peak performance for transmission and maximum voltage for reception—the Joystick is a major break-through for ardent SWLs and all licensed stations. Over 1,500 stations all over the world are already equipped with the logistick. lovstick.

SIZE 7'6" VERTICAL 2:3 METRES

"Have heard your V.F.A. both mobile and in attics on 75m. S.S.B. and they sound F.B. Mobiles sound like fixed stations. No fading whatsoever!"

WA4NPL, Alabama.

A poor QTH is now no excuse for a weak signal - act . . .

ORDER	YOUR	JOYSTICK	NOW
-------	------	----------	-----

Full "money-back" GUARANTEE if you're not completely satisfied. Not convinced? Still complete the coupon below for a detailed brochure and showers of testimonials!

PARTRIDGE ELECTRONICS LTD., 7, Sowell Street, Broadstairs, Kent Thanet 62535

Please supply "JOYSTICK" (tick appropriate box)


Standard Model, £3 10s.
De luxe Model (all copper RF elements), £4 10s.
"JOYMATCH" Type 3 for Receiving, £2 1s.
"JOYMATCH" Type 5 for Transmitting, £1 2s.

Enclosed is cheque/M.O./P.O. value £

Please send brochures and testimonialsCallsign NAME.

ADDRESS.....

GET ABOVE THE QRN WITH THE NEW

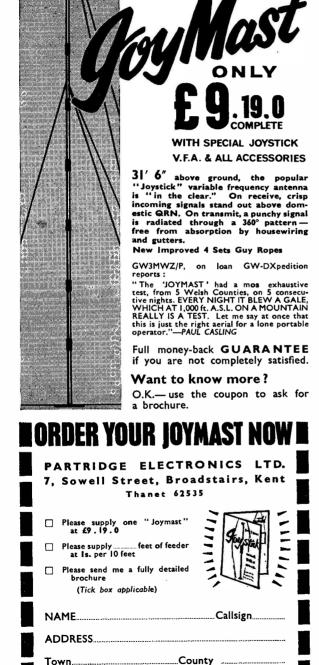

AERIAL MATCHING TUNING UNITS

LATEST AMERICAN RELEASE BULK PURCHASE OF 3000 These well made tuning units, made for the American using a large precision calibrated scale, are an essential piece of equipment for the serious Tx or Rx operator. This unit will match an unsured wise a William Co. piece of equipment for the serious Ix or fix operator. This unit will match an untuned wire or Whip Aerial to almost any Short Wave Receiver or Transmitter, exceptionally good for Mobile Top Band use. This American version being well noted as far superior to any other. GUARANTEED BRAND NEW, only 20/post 7/6. Instructions supplied.

PYE or INVICTA LOUDSPEAKER UNITS

Enclosed in a brown wooden cabinet with carrying handle, using a silver speaker mesh. Complete with 40' of lead and jack plug. A 10" heavy duty 3 ohm speaker is used, being very useful for Groups, Halls, P.A. work, etc. (made for Army entertainment use). BRAND NEW and BOXED, ONLY £2/15/-, Carr. 5/-. A fraction of cost.

88 Tx-Rx POWER UNIT

12v. input to 90v., 7.5v., 1.4v. stabilised output. Also contains L.F. amplifier. These are sold BRAND NEW with four B.7.G valves, only 50/-. P.P. 5/-.

T. SUPPLY (Dept. H.) 38 MEADOW LANE, LEEDS II

BRAND NEW SURPLUS

Post Free by Return

ANTENNA RELAYS—Coax. and 300 ohm, from 7/DIRECTIONAL COUPLERS. 50 ohm, £1
DUMMY LOADS. 20W. £3; 50W. £4; 500W. £8
JONES "MICROMATCH" POWER AND S.W.R. METER (used but good), £6

Capacitors Mica .00187 mF 4Kv., 2/6 R.F. Chokes, transmitting type, 2/6 Miniature pots. 50K linear, 3/6 S.P.D.T. knife switches, 3/–

Practice Buzzers, 4/-Morse keys, 3/-Micro switches, 3/-Rotary switches, many types from 2/-

FOR THAT QRO LINEAR

Capacitors 5mfd. 5000v., 67/6; 4mfd. 4000v., 52/6; 2mfd. 4000v., 35/-; 6mfd. 3000v., 45/-; 8mfd. 1500v., 12/6 Chokes from 16H 120ma. at 7/6 to 8H 800ma. at £1 plus

Chokes from 16H 120ma. at 7/6 to 8H 800ma. at £1 plus (sorry!) carriage.

Swinging Chokes . Power Resistors . Fuses . Panel lights Transformers all the way from 5/- up to a monumental 3360-0-3360 at 850ma. at £8, plus carriage.

Coils, 4° plated tubing 3° dia. x 2½° long x 5½ turns — 3½° dia. x 3° long x 7 turns both at 7/6 each.

Relays, Plugs, Sockets, Meters, Switches — micro, thermal, roller, etc. Right angle drives 2:1 reduction, 5/-. Shaft couplings (universal), 3/-. 15A standard flush fitting sockets with switch, 3/-

TERMINAL BOARDS. All sizes, all very useful, I/- each, 10 for 5/-, 50 for 22/6, 100 for £2. A must for any construction project.

IS OLATING TRANSFORMERS. 230:230 or 115, 250 watt, 22/6 MODULATION TRANSFORMERS up to 200 (oh boy!) watts

TRIPLER to 40 mc 5736-5736-2E26-815 fully metered, 19" rack mounting; a little beauty for the price of the meters, £5 (no p.s.u.)

Many additional assemblies, odds and ends, valves, coils, hardware, etc. for callers to whom, incidentally, we knock the cost of postage off the above prices.

DISCOUNTS FOR QUANTITIES OVER 6. I will do my level best to give you the best deal in the business.

WANTED--Good test gear, receivers, SSB Tx's-try me for new equipment, I can give you an excellent trade-in deal.

A S.A.E. will get you my latest price list.

J. B. LOWE (ex VE8DP)

115 CAVENDISH ROAD, MATLOCK, DERBYSHIRE



MIDLAND AGENTS FOR

- * EDDYSTONE RECEIVERS & COMPONENTS
- * NATIONAL RECEIVERS & TRANSCEIVERS
- * GREEN & DAVIS CONVERTERS
- * KW EQUIPMENT
- * MOSLEY AERIALS
- * WITHERS
- H.P. FACILITIES AVAILABLE
- PART EXCHANGES

AERIAL EQUIPMENT

TWIN FEEDER. 300 ohm twin ribbon feeder similar K25 6d. per yard. K358 Telecon (round) 1/6 per yard. 75 ohm twin feeder 6d. per yard. Post on above feeders and cable, 1/6 any length.

COPPER WIRE, 14G, H/D, 140 ft., 22/6; 70 ft., 11/6, post and packing 2/6. Other lengths pro rata.

FEEDER SPREADERS. 6" Ceramic type F.S., 10d. each. Postage 1/6 up to 12.

CERAMIC CENTRE PIECE for dipoles, Type AT, I /6 each. P. & P. I/-.

2 METRE BEAM, 5 ELEMENT W.S. YAGI. Complete in box with 1" to 2½" masthead bracket. Price 49/-, P. & P. 3/6.

SUPER AERAXIAL, 70/80 ohm coax, 300 watt very low loss, 1/8 per yard. P. & P. 2/-.

TOUGH POLYTHENE LINE, type ML1 (100 ibs.), 2d. per yd. or 12/6 per 100 yds. Type ML2 (220 ibs.), 4d. per yd. or 25/- per 100 yds., ML4 (400 ibs.), 6d. per yd., post free. Ideal for Guys, L.W. Supports, Halyards, etc.

ABSORPTION WAVEMETERS. 3.00 to 35.00 Mc/s. in 3 Switched Bands. 3.5, 7, 14, 21 and 28 Mc/s. Ham Bands marked on scale. Complete with indicator bulb. A MUST for any Ham Shack. ONLY 22/6 EACH. Post free.

BANDCHECKER MONITOR, 3.00-35.00 Mc/s. in 3 switched Bands. 0-1 mA Indicator. Monitor Socket. Very sensitive. £3.13.6, P. & P. 2/6.

VARIABLE CONDENSERS. All brass with ceramic end plates and ball race bearings. 50pf, 5/9, 100-6/6. 160, 7/6, 240, 8/6 and 300pf, 9/6. Extension for ganging, P. & P. I/-.

RACK MOUNTING PANELS: 19" x 5½", 7", 8½", or 10½", black crackle finish, 5/9, 6/6, 7/6, 9/-respectively. P. & P. 2/-.

GELOSO VFO UNITS. 4/102 with new dial and escutcheon. Outputs on 80, 40, 20, 15 and 10. For 2-807 or 6146 Tubes. Only £8 15 0. 3 valves to suit, 24/-. ALL POST FREE.

SHADED POLE MOTORS, 230 v. or 110 v. operation, ideal for fans, blowers or models. Single Unit 12/6 plus 2/- P. & P. or Pair £1 plus 2/6 P. & P.

PARMEKO TRANS. 200/200 40 mA. 6.3v., 3A. New, not ex W.D. Only 12/6. P. & P. 2/6.

(Established 1910)

CHAS. H. YOUNG LTD.

170-172 Corporation St., Birmingham 4.

Please print your address. No C.O.D. under £1. 'phone CEN 1635

HAMMARLUND

A Member of the Gianinni Scientific Group of Companies



THE HX-50 SSB TRANSMITTER (as used on many DX-peditions) 130 watts p.e.p. AM/CW £175



THE HXL-I LINEAR AMPLIFIER
Two 752A tubes in the final. Max. 1500 watts p.e.p. 1200 watts CW
Can be driven by HX-50, Viceroy, KW 2000, etc. £165

Other models include: HQ170A: Triple conversion super. Amateur bands only. HQ180A: Triple Conversion, general coverage and bandspread. HQ145X: Double Conversion, Amateur bands only. HQ100A: General coverage and bandspread, "Q" Multiplier. HK1B: Keyer Unit. SP600 JX: Professional Receiver 0.54-54 mc/s.

Sole U.K. Distributors

Easy terms available

KW

ELECTRONICS LTD Vanguard Works

I HEATH STREET, DARTFORD, KENT Cables: KAYDUBLEW, Dartford Phone: DARTFORD 25574



Save money building any Heathkit model

A wide range of British and American models to choose from

Radio-Amateur Equipment - Test Instruments - Hi-Fi Equipment

(All British models are available in kit form or assembled. Deferred terms available U.K. over £10)

HIGH SENSITIVITY GENERAL COVERAGE RECEIVER, Model RG-I. A high performance, low-cost receiver for the discriminating Short-wave listener. Frequency coverage from 600 Kc/s. to 1.5 Mc/s. and 1.7 Mc/s. to 32 Mc/s. Send for details. £39.16.0 Kit £53.0.0 Assembled

"MOHICAN" GENERAL COVERAGE RECEIVER, Model GC-IU. In the forefront of design with 4 piezo-electric transfilters, 10 transistors, variable tuned B.F.O. and Zener diode stabiliser.

£37. 17.6 Kit
£45. 17.6 Assembled
Suitable Battery Eliminator. Model UBE-1.
£2.17.6 Kit

AMATEUR TRANSMITTER, Model DX-100U. Covers all the amateur bands from 160-10 metres, 150 watts D.C. Input. Own power supply. £79.10.0 Kit £104.15.0 Assembled

SINGLE SIDEBAND ADAPTOR, Model SB-10U. For use with most A.M. transmitters. Less than 3 W. R.F. input power required for 10 W. output. Operation on 80, 40, 20, 15 and 10m. on U.S.B., L.B.S. or D.S.B. £39. 5.0 Kit £54.18.0 Assembled

AMATEUR BANDS RECEIVER, Model RA-I. Covers all amateur bands 10-160 metres. Half-lattice crystal filter at 1.6 Mc/s. I.F. Provision for fixed, portable or mobile uses. Switched USB and LSB for SSB. £39.6.6 Kit £52.10.0 Assembled

Q MULTIPLIER, Model QPM-1. May be used with receivers having 450-470 Kc/s. I.F. Provides either additional selectivity or signal rejection. Self powered. Model QPM-16 for I.6 Mc/s. I.F.

Either model £8.10.0 Kit £12.14.0 Assembled

AMATEUR TRANSMITTER, Model DX-40U. From 80-10m. Power input 75 W. CW., 60 W. peak, C.C. phone. Output 40 W. to aerial. £33.19.0 Kit £45.8.0 Assembled

VARIABLE FREQ. OSCILLATOR, Model VF-IU. Calibrated 160-10m. fund. outputs on 160 and 40m. Ideal for our DX-40U and similar TX. £10.17.6 Kit £15.19.6 Assembled

GRID-DIP METER, Model GD-IU. Continuous coverage 1.8 to 250 Mc/s. Self-contained. £10.19.6 Kit £13.19.6 Assembled









RG-I

DX-100U

AMERICAN HEATHKIT SINGLE SIDE BAND EQUIPMENT

As stocks in UK are limited, order as early as possible to avoid disappointment









SB-300E

HO-10E

HW-12

3" MONITOR 'SCOPE, Model HO-10E. A must for the SSB station. Gives at-a-glance, visual indication of your transmitted signal and the incoming signal, displaying envelope patterns. Built-in two-tone generator ensures a clean output signal. Power Req.: 115/230v. A.C. 50/60 c/s. £34.10.0 Kit

FILTER-TYPE SSB TRANSCEIVER, Models. For the 80, 40, or 20 metre bands. 200 W. P.E.P. input TX. I µV sensitivity RX. Employs easy-to-build printed board techniques, with pre-aligned circuits. Power Req.: 800v. D.C. at 250 mA., 250v. D.C. at 100 mA., 125v. D.C. at 5 mA., 12v. A.C. or D.C. at 3.75A.

Model HW-12. 80m. HW-22. 40m. HW-32. 20m.

£60 . 1 . 0 each. Kit

GH-12. Push-Talk Microphone £3.13.0 Assembled

SEND FOR THE COMPREHENSIVE ILLUSTRATED AMERICAN HEATHKIT CATALOGUE

Sent for only 1/- post paid

SHOWING RANGE

Please send me FREE BRITISH CATALOGUE (Yes/No) AMERICAN HEATHKIT CATALOGUE 1/-. Full details of model(s)...

NAME (BLOCK CAPITALS)

SWII

SB-300E AMATEUR 80-10m. BANDS RECEIVER. de-luxe receiver offers unsurpassed value to the Radio Amateur.

Of advanced concept, employing up-to-date design and construction techniques its ultimate specification ensures unparalleled performance. Full specification and details on request. Weight 22lb. Power Req.: 115/230v. A.C. 50-60 c/s. 50 watt. Size: 14\frac{1}{8}" \times 6\frac{5}{8}" \times 13\frac{3}{8}". \frac{1}{8} 14.0 \times 0 \times

A fitting companion for this receiver is the SB-400E Transmitter which is designed for "lock-in" facility with the SB-300E. A self-powered filter type Tx covering the "Amateur" bands, 80 to 10m. with a P.E.P. of 180 watts. Weight 331b. Power Req.: 115/230v. A.C. 50-60 c/s. Size: 14½" x 6½" x 13½". £165.4.0 Kit Full specification and details on request

"CANTENNA" TRANSMITTER DUMMY LOAD, Model

REFLECTED POWER METER. Model HM-II. Indicates Antenna/Transmitter match.

MANY OTHER BRITISH MODELS

Covering a wide range of equipment, including models for the discerning Radio Amateur, instruments for laboratory, service, test and workshop, presents for the youngsters, Hi-Fi equipment, and models for home and office.

DEPT. SWII, GLOUCESTER, ENGLAND

THE BRITISH HOME OF HEATHKIT MODELS