

The SHORT WAVE Magazine

3/6

VOL. XXV

JANUARY, 1968

NUMBER 11

KW Equipment PRICE and Quality NOT devalued



KW 201 Amateur Bands Communications Receiver

The KW201 is now being manufactured with 2 detectors (i) product detector for SSB and CW (ii) diode detector for AM. The KW201 has been specifically designed for optimum performance on SSB. 11 ranges give coverage 1.8 mc/s. to 30 mc/s. A mechanical filter gives an IF selectivity of 3.1 kc/s. at 6 dB, and 6 kc/s. at 60 dB. A "Q" multiplier is available giving a variable range of 3.1 kc/s. to 200 cycles selectivity.


£105

BASIC PRICE

additional extras if required

100 kc/s Crystal Calibrator £6. 0.0

'Q' Multiplier £8.10.0

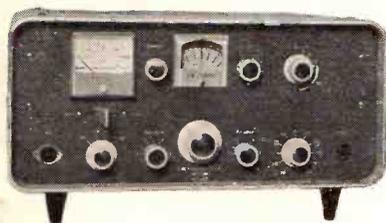

KW Vespa MkII

TRANSMITTER

£128

Transmitter for all H.F. Bands. 220 watts PEP, SSB, AM, CW. Now in full production, complete with psu.

We also stock imported equipment. Exclusive U.K. agents for DAVCO, Hammarlund, Hy-gain, Drake, CDR and Kokusai.

Agents for Collins, Sommerkamp, Swan, Mosley, National, Galaxy, etc. Microphones, coaxial cable and all your amateur radio equipment.



KW1000

LINEAR AMPLIFIER

£128

1200 watts PEP complete with built-in psu and SWR indicator.



KW2000A

Deliveries from stock.

inclusive **£220**

SSB TRANSCEIVER or £182 (transceiver only)

The finest value available, with no extras to buy. 180 watt PEP operation on all amateur bands 10-160 metres, complete with AC psu, VOX control, crystal calibrator, independent receiver tuning, Upper/lower sideband tuning, Top band included, Automatic linearity control or transmit. Special attention to TVI proofing.

KW
ELECTRONICS
LIMITED

KW ELECTRONICS LTD.

1 HEATH STREET, DARTFORD, KENT. Telephone: Dartford 25574
Cables: KAYDUBLEW Dartford.

11 licensed amateurs on our staff are waiting to serve you.

KW
ELECTRONICS
LIMITED

Eddystone EC10

ALL TRANSISTOR COMMUNICATIONS RECEIVER



Covering the 1.5 to 3.0 MHz maritime band and providing the maximum listening pleasure from medium-wave programmes, the fully tropicalized EC10 gives reliable reception, in any part of the world, of shortwave broadcasting, amateur, aeronautical and other services in the range of 550 kHz to 30 MHz. The 9-inch tuning scale has a calibration accuracy better than 1% while the logging scale and auxiliary vernier enables station settings to be recorded.

PRIMARY FEATURES:

- Sensitivity better than $5\mu\text{V}$ for a 15 dB signal-to-noise ratio.
- Independent r.f, a.f and b.f.o controls.
- Powered by U2, car, or boat batteries with optional a.c mains unit available.
- Light, rugged and housed in two-tone steel cabinet for use under adverse conditions. List price **£53**.

Comprehensive information from your Eddystone distributor or: Eddystone Radio Limited, Eddystone Works, Alvechurch Road, Birmingham 31. Telephone: Priory 2231. Telex: 33708

Radio Shack Ltd

London's Amateur Radio
Stockists

Just around the corner from West Hampstead Underground Station

A Tiger on 20 metres Hy-Gains Model 204BA

9.2db Forward Gain ● Up to 25db Front-to-Back Ratio ● SWR less than 1.5:1

The Model 204BA is a high performance DX beam for 20 meters that is light enough to mount on a lightweight tower . . . rotate with a standard Ham rotator . . . yet rugged enough to insure maximum mechanical and electrical reliability. Four full spaced elements on 26ft. boom . . . feeds with 52 ohm coax . . . Beta Matched for optimum gain. Seamless aluminium construction with taper-swaged elements . . . rugged machine formed aluminium boom to mast and element to boom brackets . . . iridite treated hardware insures maximum durability. 2in. OD boom is 26ft. long; longest element, 36ft. 6in. Wind load at 80 MPH, 100 lbs. Maximum power input, 1 kw, AM. Mast diameter, 1 1/2in. Shpg. Wt. 55 lbs. Model 204BA.

HY-GAIN ANTENNAS

We can now offer you the full range of Hy-Gain antennas, including the 50ft. Hy-Tower and 40 metre beams, from stock. Should you require 6 metre or the DX "Long Johns," then we'll get them rapidly for you.

DRAKE

2-C

RECEIVER

£99

FEATURES

- * Covers ham bands 80, 40, 20, 15 meters completely and 28.5 to 29.0 MHz of 10 meters with crystals furnished.
- * Or tunes any 500 kHz range between 3.0 and 30 MHz with an accessory crystal.
- * Three Bandwidths of selectivity (equivalent to 3 filters) are furnished: .4 kHz, 2.4 kHz and 4.8 kHz.
- * Solid State Audio with 1.8 watts output.



- * Solid State AVC with fast attack and slow release for SSB or fast release for high break-in CW. Also AVC may be switched off.
- * Receives SSB, AM, CW, and RTTY with full RF gain, complete AVC action and accurate S-meter indication.
- * Product Detector for SSB/CW—diode detector for AM.
- * Excellent overload and cross modulation characteristics; insensitive to operation of nearby transmitters.

● COAX SWITCHES

Four position Coax selector switch.
Silver plated contacts.
Power handling capacity 1,000 watts.
Insertion loss negligible up to 160 Mc.
VSWR approx. 1.2 at 160 Mc.
Mounting is single hole panel mount.
The switch as supplied is complete for in-cable or operating cable use as well as in panel mounting.
Mounting hardware supplied.
Switch comes with write-on escutcheon plate with provision for erasing.
Multi-mount nameplates are available separately for use when panel mounting the switches in equipment.
£3 . 7 . 6.

THE MARK PRODUCTS HELIWHIP

is a full range of mobile antennas we are stocking.

We also specialise in—

DRAKE

and hold stocks of every model.

SWAN

transceivers are always on show with all the accessories.

TRIO

receivers, 2-metre transceiver, in stock and the 5-band SSB transceiver together with transmitters will be available shortly.

The rest of our shelves carry New—

KW Equipment SOMMERKAMP
HALLICRAFTERS SHURE Microphones
and of course the Trade-ins.

RADIO SHACK LTD.

182 BROADHURST GARDENS, LONDON, N.W.6.


Just around the corner from West Hampstead Underground Station

Telephone: 01-624 7174

You can depend on Shure quality MICROPHONES For amateur radio communications


Shure Model 444 Controlled Magnetic Microphone

Specially designed for radio communications, giving optimum performance from single sideband transmitters as well as AM and FM units. Response cuts off sharply below 300 c/s and above 3,000 c/s, with a rising characteristic to 3,000 c/s. This results in optimum speech intelligibility and audio punch to cut through noise interference. High impedance. Dependable under all operating conditions. Complete with switch for instantaneous press-to-talk or VOX operation; finger-tip control bar; long-life switch; adjustable microphone height; sturdy, high-impact base and case; 7 ft. two-conductor shielded cable.

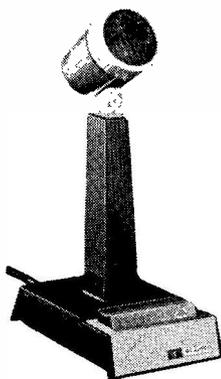

Shure Model 201 Diaphragm Type Ceramic Microphone

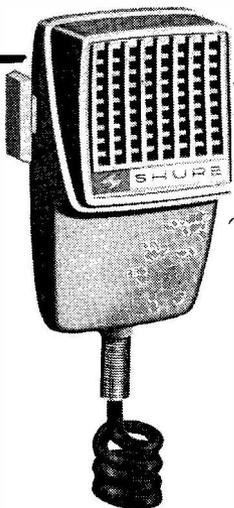- *Provides clear, crisp, natural voice reproduction of high intelligibility
- *High impedance *Ideal voice response and omni-directional polar pickup characteristics
- *No humidity or temperature problems
- *Light, strong and compact
- *Heavy duty push-to-talk (non-locking) switch
- *Frequency response: 200 to 4,000 c/s
- *3-conductor retractable cable.



SHURE

Setting the
world's standard
in sound

SHURE ELECTRONICS LTD.
84 Blackfriars Road, London, S.E.1. Tel.: 01-928 6361

GEORGE FRANCIS

G3TWV

FRANCIS for EDDYSTONE			
EB35	£60 6 3
EB36	£54 0 0
EC10	£53 0 0
EA12	£185 0 0
All in stock including full range of dials.			

FRANCIS for K.W.			
KW2000A	£220 0 0
KW VESPA	£128 0 0
KW201	£105 0 0
KW1000 Lin	£128 0 0

Full range of L.P. and H.P. Filters,
Q Multiplier, Dummy Loads,
PEP Meter, EZ-Match.
All in stock.

FRANCIS for SWAN			
SWAN 500 and A.C. P.S.U.	£283 0 0
Remote VFO Adaptor	£57 0 0
Extension Speaker	£1 15 0
All in stock.			

FRANCIS For TRIO and LAFAYETTE			
9J-59DE Rx	35 gns.
JR500E Rx	59 gns.
HA500 Rx	42 gns.
All in stock.			

FRANCIS for JOYSTICK			
JOYSTICK De Luxe	£5 19 6
3A Tuner	£3 12 6
4A Tuner	£6 6 0

FRANCIS for HALSON (FIF)			
Whips and Coils. All in stock.			

FRANCIS for CDR ROTATORS			
AR22	£21 0 0
All others, one week delivery.			

FRANCIS for TOWERS, ANTENNAS and CABLES, etc.			
--	--	--	--

**BXI TOWERS AVAILABLE
HIGH GAIN ANTENNAS AVAILABLE**
75 Ω Ordinary, 7d. per yd.; 75 Ω Low Loss, 1/6 per yd.; 52 Ω Ordinary, 1/4 per yd.; 52 Ω Low Loss, 2/- per yd.; 300 Ω Flat Twin, 6d. per yd.; 75 Ω Flat Twin, 6d. per yd.; Coax Plugs, 1/6 each; Coax Sockets, 1/6 each; Coax Couplers, 1/3 each; PL259 Plugs (American), 7/6; PL259 Sockets, 8/-; PL259 Angled Couplers, 1/6; Egg Insulators, 6d. each. All in stock.

FRANCIS for MICROPHONES			
SHURE 201	£4 10 0
SHURE 444	£9 10 0
Crystal Hand Mics	15 0
Crystal Lapel Mics	4 0
BM3	£1 15 0
BM3 and stand	£2 5 0
Acos metal	£1 2 6
Acos plastic	£1 0 0
This is just a selection we have over 24 different mics. in stock.			

FRANCIS for TRANSISTORS and VALVES			
OC44 2/1, OC45 2/-, OC71 2/1, OC72 2/3, OC81 2/3, OC83 2/2, OC170 3/-, OC171 4/-, OC26 7/6, OC35 14/3, AC126 2/1, AC128 3/1, AF114 4/-, AF116 2/6, AF117 2/6, AD140 11/-, BSY26 3/-, BSY28 3/-, BSY65 3/-, BSY95A 3/-, BSY18 3/-, OAB1 1/6, BY100 Silicons 5/- or 5 for £1, 6146B 50/-, 6HF5 33/-, 6EW6 15/-, 7360 35/-.			



FRANCIS for RESISTORS, CAPACITORS, CHASSIS, VALVE HOLDERS, etc., etc.			
--	--	--	--

FRANCIS for SECOND-HAND GEAR			
KW2000 + A.C./P.S.U. as new, £155, KW600 Lin £80, KW2000 D.C./P.S.U. £25, Pyramid Lin £40, Eddystone EB36 as new £45.			

NO ORDER TOO SMALL PART EXCHANGES
GOODS DISPATCHED RETURN OF POST POSTAGE EXTRA

93 BALDERTON GATE, NEWARK, NOTTS.
Tel. 4733; after 6 p.m. 2578

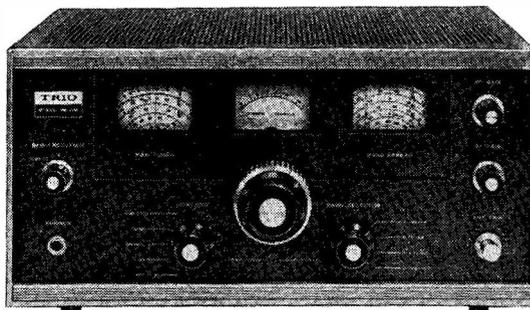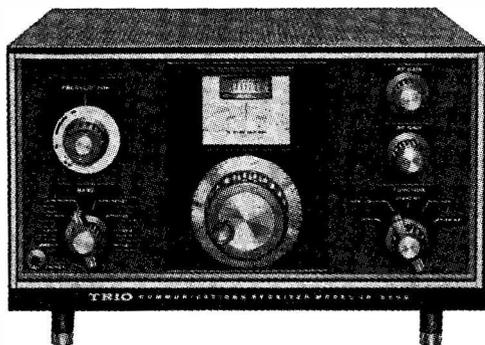♣ Technically Proven For Exacting Performance



Model JR-500SE CRYSTAL CONTROL TYPE DOUBLE CONVERSION COMMUNICATION RECEIVER

- * Superior stability performance is obtained by the use of a crystal controlled first local oscillator and also, a VFO type 2nd oscillator.
- * Frequency Range: 3.5 MHz-29.7 MHz (7 Bands)
- * Hi-Sensitivity: 1.5 μ V for 10 dB S/N Ratio (at 14 MHz)
- * Hi-Selectivity: ± 2 KHz at -6 dB ± 6 KHz at -60 dB
- * Dimensions: Width 13", Height 7", Depth 10".

Model 9R-59DE BUILT IN MECHANICAL FILTER 8 TUBES COMMUNICATION RECEIVER

- * Continuous coverage from 550 KHz to 30 MHz and direct reading dial on amateur bands.
- * A mechanical filter enabling superb selectivity with ordinary IF transformers.
- * Frequency Range: 550 KHz to 30 MHz (4 Bands)
- * Sensitivity: 2 μ V for 10 dB S/N Ratio (at 10 MHz)
- * Selectivity: ± 5 KHz at -60dB (± 1.3 KHz at -6dB) When use the Mechanical Filter
- * Dimensions: Width 15", Height 7", Depth 10".

TRIO

manufactured by TRIO Corporation, Tokyo, Japan.

Sole Agent for the U.K.

B.H. MORRIS & CO., (RADIO) LTD
84/88, Nelson Street, London E.1, Phone : 01-790 4824


TO : B.H. Morris & Co., (Radio) Ltd. SW
84/88, Nelson Street, London E.1.
Send me information on TRIO COMMUNICATION
RECEIVERS & name of nearest TRIO retailer.

NAME :


ADDRESS :

HEATHKIT — The World's Largest


THE FAMOUS HEATHKIT SB-SERIES

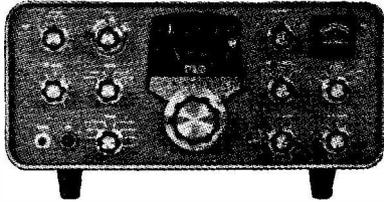

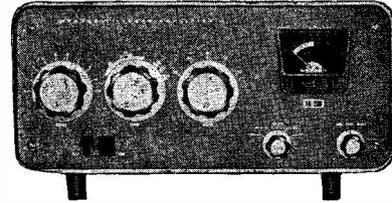SB-101 80 Through 10 Meter SSB Transceiver . . . 180 watts PEP SSB, 170 watts CW (the practical power level for fixed/mobile operation). Features USB/LSB on all bands, PTT & VOX. CW sidetone, and more. Unmatched engineering and design.
Kit SB-101, 23 lbs., £185 . 12 . 0 Assembled £225 . 12 . 0




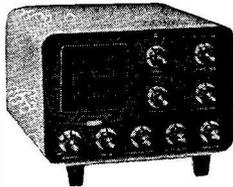SB-200 KW SSB Linear Amplifier . . . 1200 watts PEP input SSB, 1000 watts CW on 80 through 10 metres. Built-in antenna relay, SWR meter, and power supply. Can be driven by most popular SSB transmitters (100 watts nominal output).
Kit SB-200, 41 lbs., £120 . 18 . 0 Assembled £145 . 18 . 0




SB-610E Signal Monitor Scope . . . operates with transmitters on 160 through 6 meters at power levels from 15 watts through 1 kw. Shows transmitted envelope. Operates with receiver IF's up to 6 Mc/s. showing received signal waveforms. Spots over-modulation, etc.
Kit SB-610E, 14 lbs., £41 . 14 . 0 Assembled £51 . 14 . 0

New !

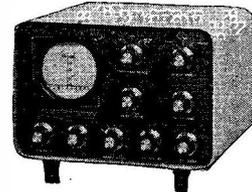

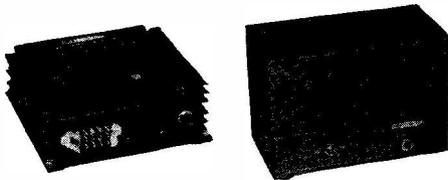SB-620 "SCANALYZER" Radio Spectrum Monitor and Analyzer New narrow sweep widths with crystal filter for single channel analysis. 10 Kc/s., 50 Kc/s. Variable width to 500 Kc/s. Styled as SB series.
Kit SB-620 £64 . 13 . 0 Assembled £77 . 3 . 0




HP-13 Mobile and HP-23 Fixed Power Supplies . . . For the "Single Banders" and SB-100. Provide all necessary operating voltages with excellent dynamic regulation.
Kit HP-13, 7 lbs., £37 . 2 . 0 (+ earth available) Assembled £44 . 2 . 0
Kit HP-23E, 19 lbs., £30 . 18 . 0 Assembled £36 . 8 . 0

MODELS
HW-12A
 (80m.)




HW-32A
 (20m.)

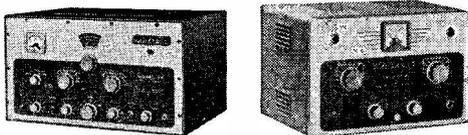HW-12A and HW-32A Filter-Type SSB Transceivers . . . 200 watts PEP input TX. 1 μ V sensitivity RX. PC Board. Pre-aligned circuits. Power required : 800v. D.C. at 250 mA., 250v. D.C. at 100 mA. —125v. D.C. at 5 mA. 12v. A.C. or D.C. at 3-75A.
Kit, either model, £60 . 3 . 0 Assembled £74 . 13 . 0
GH-12 Push Talk Microphone Assembled £4 . 3 . 0



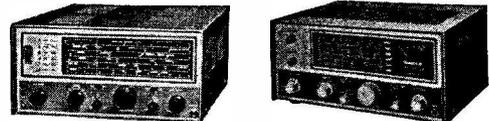DX-100U Transmitter . . . 120 watts CW, 100 watts Phone. Built-in VFO and all power supplies. Band coverage : 160, 80, 40, 20, 15 and 10 metres.
Kit DX-100U £81 . 10 . 0 Assembled £106 . 15 . 0
DX-40U Low-priced Transmitter . . . 75 watts CW, 60 watts peak. Controlled carrier Phone, 80-10 metres.
Kit DX-40U £29 . 19 . 0 Assembled £41 . 8 . 0




RG-1 High Sensitivity General Coverage Receiver . . . High performance at lowest cost. Covers 600 Kc/s. to 1.5 Mc/s., 1.7 Mc/s. to 32 Mc/s. Full specifications available.
Kit RG-1, 18 lbs., £39 . 16 . 0 Assembled £53
RA-1 Amateur Bands Receiver . . . Covers 10-160m. Half-lattice crystal filter at 1.6 Mc/s. Switched USB and LSB for SSB. Provision for fixed, portable or mobile uses.
Kit RA-1 £39 . 6 . 6 Assembled £52 . 10 . 0


SEE HEATHKIT MODELS IN LONDON - 233 Tottenham Court Road, W.1. Telephone: 01-636 7349

Selection of Amateur Radio Equipment


THE ULTIMATE IN VALUE AND PERFORMANCE

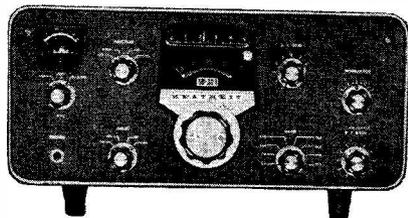

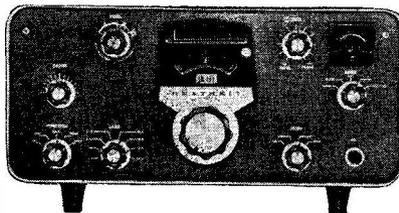SB-301E Amateur Band Receiver . . . SSB, AM, CW and RTTY reception on 80 through 10 metres + 15 MHz WWV reception. Tunes 2 metres with SBA-300-4 plug-in converter.
Kit SB-301E, 23 lbs. (less speaker) £140 . 12 . 0 Assembled £170 . 12 . 0




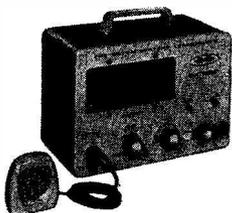SB-401E Amateur Band SSB Transmitter . . . 180 watts PEP SSB, 170 watts CW on 80 through 10 metres. Operates "Transceive" with SB-301—requires SBA-401-1 crystal pack for independent operation.
Kit SB-401E, 34 lbs., £157 . 10 . 0 Assembled £192 . 10 . 0
SBA-401-1 crystal pack, 1 lb., £17 . 3 . 0



HW-30 2 Meter Transceiver . . . For fixed, portable, or mobile. Ideal for local and RAEN purposes. Input 5 watt. CC. Tunable regenerative RX. Size 9½" w. x 8" h. x 6" deep. (For 230v. operation if required).
Kit HW-30, 6½ lbs., £26 . 8 . 0 Assembled £36 . 8 . 0
Kit GP-11 (Power supply 6 or 12v. D.C.) £10 . 13 Assembled £13 . 13

New !


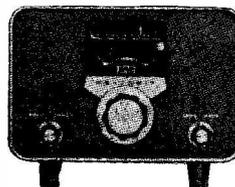


SB-640 External LMO for SB-101 . . . Provides Linear Master Oscillator frequency control or either of two crystal controlled frequencies for a total of five frequency control options. Power supplied from SB-101 Trans.
Kit SB-640, 9 lbs., £51 . 6 . 0 Assembled £56 . 6 . 0




HA-14 The World's Smallest Kilowatt Linear . . . 80-10m. Only 3⅝" x 12⅝" x 10" deep.
Kit HA-14 £55 . 13 . 0 Assembled £67 . 13 . 0

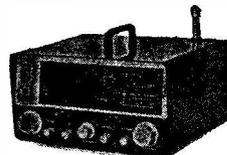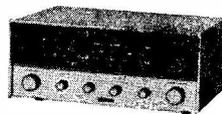HD-10 All Solid-State Electronic Keyer . . . 15 to 60 w.p.m. with 10 to 20 w.p.m. slow speed option.
Kit HD-10, 6 lbs., £23 . 12 . 0 Assembled £30 . 12 . 0



GR-64E Short Wave Receiver . . . Covers 1 Mc to 30 Mc/s., plus 550 Kc/s. to 1620 Kc/s. AM band. Many special features for such a modest price. For 115, 230v. 50/60 c/s. A.C. mains operation.
Kit GR-64E £22 . 9 . 0 Assembled £29 . 9 . 0
GC-1U "Mohican" General Coverage Receiver . . . 10 transistors, 5 diode circuit. Tunes 580-1550 Kc/s. and 1.69-30 Mc/s. in 5 bands. 6" x 4" speaker.
Kit GC-1U £37 . 17 . 6 Assembled £45 . 17 . 6

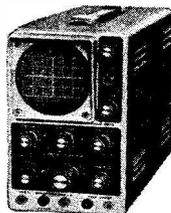

A complete line of Test Instruments for the Amateur Radio Station. The V-7A VVM and RF probe. The MM-1U Mutimeter. The OS-2 Portable Oscilloscope and many more instruments are fully described in the latest Heathkit catalogue.

HEATHKIT

DAYSTROM LTD., Dept. SW-1, GLOUCESTER

Enclosed is £..... post paid U.K.

Please send model(s)

Please send FREE Heathkit Catalogue.

NAME

ADDRESS

Prices and specifications subject to changes without notice.

JOYSTICK

VFA ONLY 7' 6" LONG!



ZL-G DX!

WHY STRUGGLE IN THE RAT-RACE?

DO IT THE EASY WAY—WITH A


JOYSTICK V.F.A.!!

Like ZL1TB (ask to see a copy of his really exotic DX log)

or

ZL4GA who works G-DX on 80m. with an INDOOR

JOYSTICK V.F.A.!!!

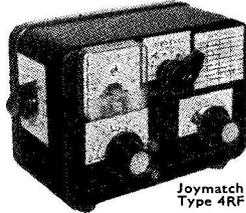

Joymatch Type 4RF

Heavy duty improved tuner for transmission and reception 160 thru 10 metres. Built-in RF meter ensures peak efficiency.

Your Joystick V.F.A. stockists:

- Bath : Ryland Huntley, 15 Old Bond St.
- Birmingham : Chas. H. Young Ltd., 170-172 Corporation St.
R.S.C. Hi-Fi Centres Ltd., Gt. Western Arcade.
- Bradford : R.S.C. Hi-Fi Centres Ltd., 10 North Parade.
- Bradford 1 : Radio Ham Shack, 75 Godwin St.
- Brighton : Technical Trading Co., Park Crescent Place.
- Bristol : R.S.C. Hi-Fi Centres Ltd., 14 Lower Castle St., Bristol 1.
- Burnley : Trafalgar Supplies, Standish St.
- Cardiff : Wesak Radio, 54 Daniel St., Cathays.
- Cheltenham : Spa Radio, 335-337 High St.
- Chesterfield : J. & A. Tweedy (Electronic Supplies) Ltd., 64 Lordsmill St.
- Coventry : Swanco Products Ltd., 247 Humber Ave.
- Darlington : R.S.C. Hi-Fi Centres Ltd., 13 Post House Wynd.
- Derby : R.S.C. Hi-Fi Centres Ltd., 26 Osmaston Road, The Spot.
- Doncaster : B. Page, Tape Recorder Centre, 18-19 Wood St.
- Edinburgh : R.S.C. Hi-Fi Centres Ltd., 133 Leith St.
- Folkestone : John Golding, Tontine St.
- Glasgow : R.S.C. Hi-Fi Centres Ltd., 326 Argyle St.
R.S.C. Hi-Fi Centres Ltd., 403 Sauchiehall St.
- Halifax : Albert Hind Ltd., 16-18 Waterhouse St.
- Newcastle-under-Lyme : Sidney T. Chadwick, "Ham Radio," 53 George St.
Richley & Freeman Ltd., 100 Percy St.
- Newcastle-upon-Tyne : R.S.C. Hi-Fi Centres Ltd., 41 Blackett St.
- Newport, Mon.: K. F. Paull Ltd., 14 Doek St.
- Nottingham : Pete's Electronics Ltd., 165 Arkwright St.
- Portsmouth : Technical Trading Co., 350-352 Fratton Rd.
- Purley (Croydon) : G3HSC, 45 Green Lane (for demonstration phone 660 2896).
- Scarborough : Derwent Radio Ltd., 28 Hillcrest Ave.
- Sheffield : R.S.C. Hi-Fi Centres Ltd., 13 Exchange St.,
Castle Market Buildings.
- Southampton : Technical Trading Co., 72 East St.
- South Shields : J. T. Gough Electronics, 87 Imeary St.
- St. Helens : Harold Stott, 18 Westfield St.
- Stoke-on-Trent: See Sidney T. Chadwick, Newcastle-un.-L.
- Sunderland : The Red Radio Shop, 31 Crowtree Rd.
- Walsall : Normal Service Ltd., 113 Lichfield St.
- Worcester : Jack Porter Radio Ltd., 40-42 College St.
- Worthing : G.V.M. Radio Ltd., 40-42 Portland Rd.
Technical Trading Co., Montague St.

- Hartlepool : The Radio Shop, 58 Park Rd.
- Huddersfield : Radio Craft (Hudd) Ltd., 38 King St.
- Hull : R.S.C. Hi-Fi Centres Ltd., 91 Paragon St.
Short Wave (Hull), 24A Newland Ave.
- Ilford : Radio Developments Ltd., 298 Clayhall Ave.,
Barkingside.
- Leeds : R.S.C. Hi-Fi Centres Ltd., County (Mecca) Arcade,
Briggate.
- Leicester : R.S.C. Hi-Fi Centres Ltd., 32 High St.
S. May Ltd., 12-14 Church Gate.
- Liverpool : R.S.C. Hi-Fi Centres Ltd., 73 Dale St., Liverpool 2.
Stephens-James Ltd., 70 Priory Rd.
- London : G.W. Smith & Co. (Radio) Ltd., 3 & 34 Lisle St., W.C.2.
Lasky's Radio Ltd., 118 Edgware Rd., W.2.
Lasky's Radio Ltd., 297 Edgware Rd., W.2.
Lasky's Radio Ltd., 33 Tottenham Court Rd., W.1.
Lasky's Radio Ltd., 42 Tottenham Court Rd., W.1.
Lasky's Radio Ltd., 152-3 Fleece St., E.C.4.
RT & I Electronics Ltd., Ashville Old Hall, Ashville Rd., E.11.
Alfred Imhof Ltd., 112-116 New Cross St., W.C.2.
Daystrom Ltd., 233 Tottenham Court Rd., W.1.
- Loughboro' : Taurus Electrical Services, 26 Nottingham Rd.
- Luton : Coventry Radio Ltd., 189-191 Dunstable Rd.
- Manchester : R.S.C. Hi-Fi Centres Ltd., 60A Oldham St.
- Middlesboro' : R.S.C. Hi-Fi Centres Ltd., 106 Newport Rd.
- Newark : George Francis (G3TWV), 93 Balderton Gate.

By the time this list appears in print it will be incomplete—so please write to us for your local stockist, or order direct from:

PARTRIDGE ELECTRONICS LIMITED (Dept. SWA)

CAISTER HOUSE, PROSPECT ROAD, BROADSTAIRS, KENT

Telephone 0843 62535

UK Pat. No. 1,045,481
and world patents granted or pending

This brochure gives you the facts and only the facts!

SEND TODAY

PARTRIDGE ELECTRONICS LIMITED
CAISTER HOUSE, PROSPECT ROAD, BROADSTAIRS, KENT

NAME CALL/BRS No.

ADDRESS




SWA

THE MOST RELIABLE SERIES OF TRANSCEIVERS EVER OFFERED

SWAN

ASK THE AMATEUR WHO OWNS ONE

Transmitter power : 480 watts SSB PEP input, 360 watts CW input, 125 watts AM input • Two 6HF5 P.A. tubes • Frequency range : 3.6-4.0 mc, 7.0-7.5 mc, 13.85-14.35 mc, 21.0-21.5 mc, 28.0-29.7 mc • Extended frequency coverage provides for operation with external crystal oscillator • High frequency crystal lattice filter common to transmit and receive circuits : 2.7 kc bandwidth • Overall audio bandpass essentially flat from 300 to 3000 cycles • Sideband suppression : 50 dB • Carrier suppression 60 dB • Third order distortion : 30 dB • Selectable upper and lower sideband • Output circuit : wide range Pi coupler, coarse and fine adjustment • Transmitter ALC with audio compression • Grid block CW keying, offset frequency •

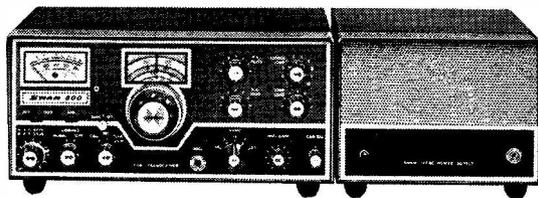

**5 BANDS — 480 WATTS
HOME STATION — PORTABLE — MOBILE**

Transistorised VFO, Temperature and voltage stabilized • Precision dual-ratio tuning • Receiver sensitivity better than 5 µv for 10 dB signal-plus-noise to noise ratio • Amplified AGC system. S-meter functions automatically when receiving • Automatic noise limiter • 100 kc crystal calibrator • External VFO available for separate frequency control • Factory installed accessory socket for addition of model 410 external VFO • Panel controls : receiver A.F. gain, receiver R.F. gain, function switch, ANL switch, PTT-VOX selector, mic, jack, band selector, mic, gain, carrier balance, P.A. plate, P.A. grid, P.A. load, coarse and fine. • Dial set • 5 1/2 in. high, 13 in. wide, 1 1/2 in. deep, 15 lbs. weight. £283 complete with power unit.

LATEST BROCHURES ON REQUEST SEE THEM AT YOUR

Appointed Stockists

Main Agent — PETER SEYMOUR LTD.
410, Beverley Road, Hull.

LONDON and the S.E.

RADIO SHACK
182, Broadhurst Gardens, London, N.W.6.

Midland Area

GEORGE FRANCIS
93 Baldertongate, Newark.

S.W. Area

SWANCO PRODUCTS
247 Humber Avenue, Coventry.

Scotland

L. HARDIE
542 George Street, Aberdeen.

ALL ITEMS IN STOCK AT THE TIME OF GOING TO PRESS

	£	s.	d.		£	s.	d.
LAFAYETTE HA55A. 108-136 mc/s.	19	17	6	LAFAYETTE HA500. 80-6 metres. Amateur bands only. Dual conversion, etc. New	44	2	0
RACAL RA17. Mint condition	265	0	0	HA-700. 550 kc/s. to 30 mc/s., mechanical filter, product detector "S" meter, etc. New	37	16	0
HALLICRAFTERS SX146 with additional CVW filter and calibrator. As new	130	0	0	NATIONAL NC183D. 540 kc/s. to 31 mc/s., plus separate calibrated dial 80-10 metres, a de-luxe 5WL receiver ...	85	0	0
TRIO 9R59DE. 550 kc/s.-30 mc/s. Immediate delivery ...	36	15	0	EDDYSTONE 888A. As new	75	0	0
NATIONAL NC109. 550 kc/s.-40 mc/s. Product detector, crystal calibrator, etc.	55	0	0	NATIONAL NCX3 with non-commercial p.s.u. 200w, P.E.P. 200w, CVW 125w, AM 80, 40, 20. First class condition throughout	110	0	0
EDDYSTONE "S" METER. Suitable for 750, 640, 740, 888, etc.	5	0	0	SOMMERKAMP FR100B New	105	0	0
AR88LF. Re-wired with PVC	40	0	0	SOMMERKAMP FL200B Tx. 240w, P.E.P.	130	0	0
WINDSOR 170A. VTVM	7	10	0	EDDYSTONE 680X. 480 kc/s.-30 mc/s. As new	75	0	0
HUNTS C/R BRIDGE. Mains operated	5	0	0	HALLICRAFTERS SX111. Amateur bands only, 80-10	85	0	0
MULTI BAND DIPOLE TRAP SETS with full instructions fully encapsulated per pair	2	10	0	EDDYSTONE 770U/2. 150-500 mc/s. AM/FM, works reconditioned at a cost of £90. Brand new condition ...	175	0	0
EAGLE. Fully transistorised G.D.O.'s. 435 kc/s.-220 mc/s.	12	10	0	GONSET G77. Mobile/mains Tx with mains/battery p.s.u. 75w, input 80-10	38	0	0
EDDYSTONE 750. The latest type made, 480 kc/s.-32 mc/s. with mounting blocks "S" meter and speaker	55	0	0	THE NEW DRAKE 2C and TR4 is in stock along with the fabulous SWAN 500 and is available for your inspection.			
TRIO JR-500 SE crystal controlled Osc., tunable IF system, full coverage 80-10 metres. Amateur bands only. Two mechanical filters, transistorised VFO, etc. ... New	61	19	0	EAGLE DE-LUXE SWR INDICATORS reads forward and reflected power directly calibrated in SWR up to 10-1 plus direct reading RF wattmeter 0-15w, FSD, 2-200 mc/s.	9	19	6

FULL H.P. FACILITIES ON EQUIPMENT OVER £35


25% DEPOSIT, UP TO 24 MONTHS TO PAY. LET US KNOW YOUR REQUIREMENTS

PETER SEYMOUR LIMITED

410 BEVERLEY ROAD, HULL, YORKSHIRE

Telephone : 41938 (43353 after 7.30)

GO MOSLEY BRITISH AND BEST

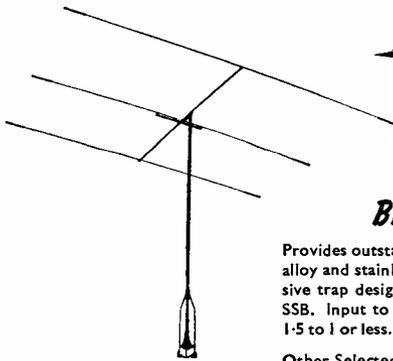

ELAN



V-3 Jr.

THE ELAN FROM MOSLEY OF ENGLAND BRITISH MADE FROM BRITISH MATERIALS

Provides outstanding performance on 10 and 15 metres, coupled with light weight (17 lbs.). All aluminium alloy and stainless steel construction, exceptional broad band characteristics, over full Ham bands, exclusive trap design, single co-ax 52 ohm feed point. Power ratings : 300 watts AM/CW, 600 watts, p.e.p. SSB. Input to final. Forward gain up to 8dB. Front to back ratio 20dB or better. Standing wave ratio 1.5 to 1 or less. Maximum Element length 20ft. 3in. Boom length 12ft. Turning radius 12ft. £23 (ex works)

Other Selected Prices :	TA-33JR	£27 5 0
	V-4-6	£15 10 0
	RV-4	£16 10 0
	CLASSIC-33	£50 0 0
	MP-33	£32 17 0

FOR ALL ANTENNA DETAILS :
Send for complete Catalogue, containing full details of Antennas and other technical information. 28 pages 1/6.

We sell direct or through our distributors :
Southern Area : K.W. Electronics Ltd.
Midland Area : Swanco Products Ltd.

Carriage and Insurance Extra


Telephone: Costessey 2861, orders only

Mosley Electronics Ltd. 40, Valley Road, New Costessey, Norwich, Norfolk. Nor. 26K

HOME RADIO (Mitcham) LTD. 187 London Rd., Mitcham CR4 2YQ, Surrey. Phone 01-648 3282

Magnificent ONCE ONLY Offer

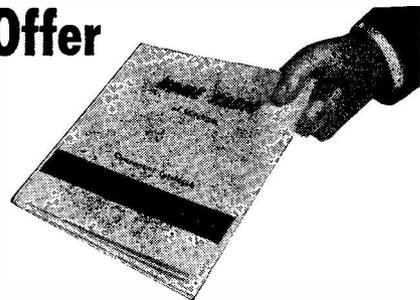Exclusive to readers of Short Wave Magazine and R.S.G.B. Bulletin !!



An opportunity to acquire one of the famous Home Radio Catalogues for ONLY 3/6 post paid (normal price 9/6 post paid), showing a saving of 6/- !!

It sometimes happens that when we are ready to launch a new Edition of our Catalogue we have a few copies of the current one left. These are still excellent, useful catalogues and containing as they do the latest supplement are superior to many catalogues offered at twice the price !

Please hurry; when we say 'Once only' we mean 'Once only.'
Send your P.O. or cheque for 3/6 TODAY.


And in spite of its modest price we are still giving away with each Catalogue 3 vouchers each worth 1/- if used as directed, a voucher worth 5/- if used to purchase a Weller Soldering Iron, our unique Bargain List, a useful Book Mark, an order form and an addressed envelope !!!

Please write name and address in block capitals

NAME

ADDRESS

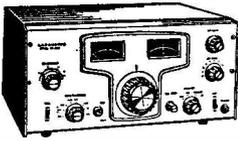HOME RADIO (Mitcham) LTD., DEPT. SW, 187 LONDON ROAD,
MITCHAM, CR4 2YQ



SPECIAL OFFER!
LAFAYETTE HA-350
10-80 METRE
AMATEUR RECEIVER


- Mechanical Filter for Exception Selectivity.
- 12 Valves Dual Conversion.
- Automatic Noise Limiter.
- Product Detector for Selectable Upper and Lower Sideband Reception
- Complete with Crystals for 80, 40, 20, 15 and 10 Metres.
- 100 kc/s. Crystal Calibrator and Crystal BFO.
- "S" Meter-Calibrated in "S" Units 1-9 and to +40 dB.

A limited quantity of these fabulous receivers are available which were made for 115 volt A.C. only. Offered Brand New and guaranteed at a much reduced price.

ONLY
£67.10.0

Suitable 115/230 volt transformer 24/-.

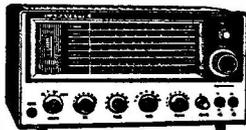
LAFAYETTE MODEL HA-500 SSB/AM/CW
80 THROUGH 6 METRE RECEIVER



New outstanding Ham Bands only receiver covering the 80/40/20/15/10/6 metre bands. Incorporates 10 valves, product detector, two mechanical filters, S Meter, dual conversion on all bands, crystal calibrator, B.F.O. noise limiter, aerial trimmer, I.F.s. 2,608 Mc/s and 455 Kc/s. Output 8 ohms and 500 ohms. Operating 220/240 volt A.C. Supplied brand new and guaranteed with handbook, 42 gns. Carr. 10/-, 100 Kc/s. crystal, 35/-.


NEW LAFAYETTE MODEL HA700 AM/CW/SSB AMATEUR COMMUNICATION RECEIVER

Eight valves, 5 bands incorporating 2 MECHANICAL FILTERS for exceptional selectivity and sensitivity. Frequency coverage on 5 bands 150-400 Kc/s., 550-1,600 Kc/s., 1-4-0 Mc/s., 4-8-14.5 Mc/s., 10-5-30 Mc/s. Circuit incorporates RF stage, aerial trimmer, noise limiter, B.F.O. product detector, electrical bandspread, S meter, slide rule dial. Output for phones, low to 2KΩ or speaker 4 or 8 ohms. Operation 220/240 volt A.C. Size 7 7/16 in. x 15 in. x 10 in. Supplied brand new and guaranteed with handbook, 36 gns. Carr. 10/-, S.A.E. for leaflet.

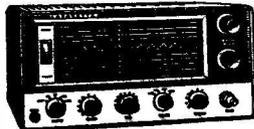


HAM-1. 4 BAND COMMUNICATION RECEIVER

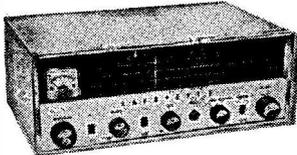Four wavebands covering 535 Kc/s.-30 Mc/s. Five valve superhet circuit. Incorporates S meter, B.F.O., BANDSPREAD TUNING, BUILT-IN 4" SPEAKER, FERRITE AERIAL AND EXTERNAL TELESCOPIC AERIAL. Operation 220/240v. A.C. Supplied brand new with handbook, £17/17/-, carr. 10/-.




TRIO JR-500SE AMATEUR RECEIVER

Covers all the amateur bands in 7 separate ranges between 3.5 and 29.7 Mc/s. 7 valves, 2 transistors and 5 diodes plus 8 crystals; output 8 and 500 ohm and 5000 ohm phone jack. Crystal controlled oscillator. Variable BFO. VFO. AVC. ANL. S meter. SSB-CW. Stand-by switch. special double gear dial drive with direct reading down to 1 kHz. Remote control socket for connection to a transmitter. Audio output 1 watt. 115/250v. A.C. Mains. Superb modern styling. Size 7 x 13 x 10 in. with instruction manual and service data, £59. Carriage 12/6.

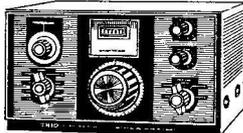

TRIO 9R-59DE

Brief spec: 4 band receiver covering 550 Kc/s. to 30 Mc/s. continuous and electrical bandspread on 10, 15, 20, 40, and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW. ANL. Variable BFO. S meter. Sep. bandspread dial. IF frequency 455 Kc/s. audio output 1.5w. Variable RF and AF gain controls 115/250v. A.C. Mains. Beautifully designed. Size: 7 x 15 x 10 in. with instruction manual and service data. £35. Carriage 12/6.

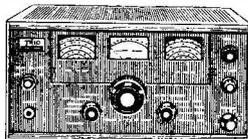


JOYSTICK AERIALS

Revolutionary variable frequency aerials with a variety of different matching units suitable for receiving or transmitting and covering medium and short waves.

STANDARD JOYSTICK, £4/15/-, DE LUXE JOYSTICK, £5/19/6

TUNING UNITS

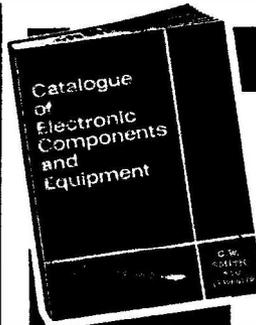Type 2A £3/15/- Type 3 £2/15/- Type 3A £3/12/6 Type 4 £4/ 4/- Type 4R £6/ 6/- Type 4H £3/10/6 Type 4H/RF £6/ 6/- Type 6RF £3/19/6



CATALOGUE


- ★ ELECTRONIC COMPONENTS
- ★ TEST EQUIPMENT
- ★ COMMUNICATION EQUIPMENT
- ★ HI-FI EQUIPMENT

We are proud to introduce our first comprehensive catalogue of Electronic Components and equipment. Over 150 pages, fully illustrated, listing thousands of items many at bargain prices. Free discount coupons with every catalogue. Everyone in electronics should have a copy, 5/-, P. & P. 1/-.

Send today
5/- P&P 1/-


ADMIRALTY B.40 RECEIVERS

Just released by the Ministry. High quality 10 valve receiver manufactured by Murphy. Five bands 650 Kc/s.-30 Mc/s. 1/2". 500 Kc/s. Incorporates 2 R.F. and 3 I.F. stages, bandpass filter, noise limiter, crystal controlled B.F.O. calibrator, I.F. output, etc. Built-in speaker, output for phones. Operation 150/230 volt A.C. Size 19 1/2 in. x 13 1/2 in. x 16 in. Weight 114 lbs. Offered in good working condition, £22/10/-, Carr. 30/-, With circuit diagrams. Also available B41 L.F. version of above. 15 Kc/s.-700 Kc/s., £17/10/-, Carr. 30/-.

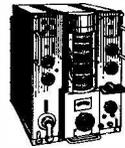


COLLINS TCS TRANSMITTERS

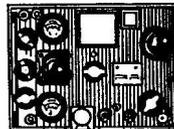Frequency range 1.5-12 Mc/s., in 3 bands. Employ 7 valves, 2 of 1625 PA, 1625 Buffer, 1625 Mod, 3 x 12 A6 Osc. R.T. or C.W. V.F.O. or provision for Xtals. Incorporate plate and aerial-current meters. Require ext. P.S.U. Offered in excellent condition, £8/19/6. Carr. 15/-.



CLEAR PLASTIC PANEL METERS

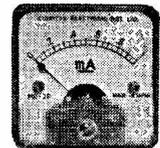First grade quality, Moving Coil panel meters, available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows.



Type MR. 38P. 1 21/32 in. square fronts.	50µA	22/6	5mA	22/6	1A	DC	22/6		
	100µA	29/6	10mA	22/6	2A	DC	22/6		
	200µA	27/6	20mA	22/6	5A	DC	22/6		
	500µA	25/-	50mA	22/6	3V	DC	22/6	500v	DC 22/6
	50-0-50µA	29/6	100mA	22/6	10V	DC	22/6	750v	DC 22/6
	100-0-100µA	27/6	150mA	22/6	20V	DC	22/6	15v	AC 22/6
	500-0-500µA	22/6	200mA	22/6	50V	DC	22/6	50v	AC 22/6
	1-0-1mA	22/6	300mA	22/6	100V	DC	22/6	50v	AC 22/6
	1mA	22/6	500mA	22/6	150V	DC	22/6		
	2mA	22/6	750mA	22/6	300v	DC	22/6		

Larger sizes available—send for lists


R.C.A. AR88 SPEAKERS

Eight-inch, 3 ohm speakers in metal case. Black crackle finish to match our 88 receivers. Brand new and boxed with leads, 59/6. Carr. 7/6.

GRID DIP METERS

KYORITSU, 360 Kc/s.— £ s. d.
220 Mc/s. Mains operated ... 12 10 0
Lafayette Nuvistor 1.7-180 Mc/s. Mains operated ... 12 10 0
TE.15 Transistorised. 440 Kc/s.-270 Mc/s. ... 11 11 0

CODAR EQUIPMENT

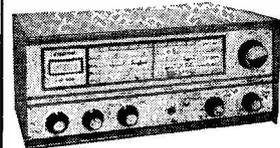

EX-AM CONTROL BOX

with two Londex 7026 24v. D.C. Aerial Change-over Relsys. New, 39/6. Carr. 5/-.

BUG KEYS £3 19 6

ELECTRONIC KEYS £16 10 0

ELECTRONIQUE COIL PACKS

GC.166. QP.166 £13 13 0
GC.166T. HB.166T £16 16 0
I.F. strips also in stock.

CR.70 Receiver	£	s. d.
CR.45 Receiver	11	7 0
CR.45 Kit	9	10 0
PR.30 Preselector	5	10 0
PR.30X (Built in P.S.U.)	7	4 0
RQ.10 Q Multiplier	6	15 0
RQ.10X (Built in P.S.U.)	8	8 0
CC.40 Control Unit	6	10 0
AT.5 Transmitter	16	10 0
T.28 Receiver	15	10 0
12/MS Mobile P.S.U.	11	5 0
12/RC Control Unit	2	7 6
AT5 Mains P.S.U.	8	0 0
Mini Clipper Kit	1	19 6

OPEN
9 a.m.—6 p.m.
EVERY DAY
MON. TO SAT.

G. W. SMITH & CO. (RADIO) LTD.

3-34 LISLE STREET, LONDON, W.C.2

Phone: GERRARD 8204/9155

PART
EXCHANGES
WELCOME

J. B. LOWE

51 Wellington Street, Matlock, Derbyshire

Tel.: Matlock 2817 (2430 after 6)

HAPPY NEW YEAR

Sorry, lads, no pretty pictures this month as I've got to make room for a whole load of stuff I want to flog.

First of all, a word on devaluation—I'm afraid it is bound to increase prices on the vast majority of the stuff I flog. Sorry and all that, but it can't be helped. Incidentally, as anyone with a slide rule can tell you, a devaluation of 14% does not mean that the import price goes up 14%. No sirree! It goes up darn' nearly 17%! If you don't believe me, figure it out !!

Still, there's one good thing about devaluation—it gives British industry a better chance. Let's hope to goodness they take it and stop messing about. Damn it, after all I am reasonably patriotic—I don't like having my shelves full of imported gear—I'd much rather sell British. If Management smarten up and Labour does a little work, the whole world would be selling British. Then you'd all be stinking rich like Bill Lowe !

Who does this Bill Lowe think he is ! He can talk ! The only work he ever does is carry a suitcase of cheques to the bank !

Enough of this nonsense—I have my own troubles—John is threatening to go on strike 'cos his screwdriver's too heavy. He'll be wanting extra pay for working 12 hours a day 7 days a week next ! Fortunately he thinks overtime means drinking after hours.

NEW STUFF :

You know darn' well that I have a very wide selection of new stuff. Rx's, Tx's, test gear and bits and bobs, so I won't waste space pushing it. I would, however, like to mention the new Sommerkamp equipment :—

FR-500 : A new Rx similar in design to the FR-100-B, but with the following additional features : (1) Top band. (2) 500 cycle mechanical filter. (3) Notch filter.

FL-500 : A new Tx, again similar in design to the FL-200-B, but featuring 500W p.e.p.

FT-500 : The new transceiver with 500W p.e.p.

By the time you read this I should have had deliveries of the Rx (probably sold 'em all, too !!) and the Tx and transceiver should be on their way. I'm got going to go hog wild on advertising—you know the reputation of Sommerkamp, so all I'll say is—if you're smart, you'll get on the waiting list right now.

SECOND-HAND :

RX's : HA350, £60 ; 940, £90 ; SX110, £40 ; AR88D, £30 ; EA12, £120 ; 75A2, £120 ; HRO, £27 10s. ; APR4, £50 ; AR77E, £30 ; EC10, £38 ; HR22, £80 ; KT340, £20 ; 640, £20 ; SX101A, £80 ; HT32, £80 ; R388, £110 ; SP600, £85.

TX's : DX40U, £20 ; Matching VFO, £5 ; LG50, £25 ; LG300 r.f. section, £20 ; Top-2-7, £18 ; Viceroy 3, £90 ; Labgear topbander, £18 ; DX100 and SB10, £60. Geloso Miniphase with VFO and o.s.u., £40 ; B2 Spy Tx/Rx, £12 ; KW600 linear, £70 ; Panda Cub, £25.

SUNDRIES : 10 metre walkie-talkies on 28.5 mc/s., £12 10s. per pair, post free ; Shure 401A mikes, £5 10s. ; Darronics 'scope, £20 ; Codar mobile p.s.u., £8 ; Codar preselector, £5 ; BC453 "Q fiver," £5 ; R.F. output meters, £2 10s. (the meter alone is worth this !) ; 339 'scope, £15 ; Power Units 234A for 1132 or 1392 sets. Ideal bench supply giving 300v. D.C. or 250v. D.C. and 6.3v. A.C. Absolute gift, 30/- carriage paid ; RF Units 24B. These are the popular things for a 20, 15 and 10 converter. 7 mc/s. out, 20/- carriage paid ; Tuning Unit 4218 containing coil formers, ceramic trimmers and no less than 3 rotary inductors (priceless !!) for 30/- carriage paid.

COMPONENTS :

NEW : Tubular trimmers either ½-5pF or 3-15pF, 1/- each. 10/- a doz. ; Feedthroughs 1000pF screw type, 1/- each, 10/- a doz. ; Disc ceramics .001, 3/6 a doz. ; .01, 5/- doz. ; Standard coax sockets, 1/- each ; Standard coax plugs, 1/4 each ; PL259 plugs, 5/- each ; Alligator clips, 6d. each ; Plugs (Octal, B7G, B9A), 2/6 each ; 2pF and 3pF ceramics, 3d. each, 2/6 a doz. ; Electrolytics—brand spanking new can types, complete with mounting clips. 10mF 350v., 1/8 ; 20mF 350v., 2/3 ; 20mF 450v., 2/9 ; 100mF 350v., 5/6 ; 100-100mF 350v., 6/8 ; 100mF 450v., 7/2 ; 40-40mF 500v., 7/3 ; 100mF 500v., 7/9 ; 100-100mF 450v., 13/2 ; Silicon rectifiers—Current manufacture, NOT surplus, NOT seconds. You can rely on these. SE-05 1000piv 500mA, 4/6 ; IS1066 1000piv 750mA, 8/-.

New Surplus : Resistors, most values from 2d. each. I can make up a batch of 100 useful values for 10/-. Capacitors from 2pF to

150mF from 2d. each. Again I can make up a very useful lot of 200 for 25/-. Mica trimmers 1000pF, 1/- ; 2,800pF solid dielectric variables—ideal top band loading, 1/- . Oil filled 8mF at 750v. D.C., 2/- . Pots—from 5 ohms to 1 meg, 6d. each. I can make up a useful bunch of 25 for 10/-. The guts of the 19 set variometer, 5/- post free.

TRANSFORMERS—All new :

	Primary	Secondary
Tapped	110, 120, 200-250,	325-0-325 200mA 5v. at 3A, 30/-
"	180-250	300-0-300 150mA 6.3 at 6A, 2.5-0-2.5 at 3A, 30/-
"	105-250	250-0-250 120mA, 0-4-5 at 2.5A, 0-4-6.3 at 5A, 30/-
"	180-250	300-0-300 50mA, 2-0-2 at 2.5A, 6.3 at 1.5A, 20/-
"	240	250-0-250, 5v., 6.3v., 20/-
"	220	0-1860 at 4mA (5Kv. insulation), 20/-
"	105-250	325-0-325 at 10mA, 6.3 at .6A, 6.3 at .3A, 15/-
"	200-250	5Kv.-0-5Kv. at 120mA, £10
"	220-250	400-0-400 at 400mA, 80-0-80 at 10mA, 63-0-63 at 6A, £6 10s.

Autotransformers 0-110-150-190-230 at 1.6 KVA, £3 10s.

SPECIAL OFFER :

In order to clear up stocks of stuff which I can't advertise (because I haven't many of each and if I did advertise, they'd soon go and I'd spend the rest of the month returning cheques, P.O.'s, etc., with a letter of apology !) I can send you a very sound junk box if you'll send me £1. A mixed bunch of resistors, capacitors, trimmers, pots, etc., carriage paid, which I guarantee to be good value. I can promise that they won't be the usual horrible surplus. Usually these bargain offers involve chucking 90% of it away, but in this case you'll only chuck 89% away ! Seriously—a good buy.

Service Department : Sorry, lads, we're full up for the present.

Postage : Except where items are marked "carriage paid," postage is extra. Please remember the days of the penny black are over and something weighing 2 lbs. 1 oz. costs 4/6. Don't be frightened of sending too much, I'll return any excess.

A s.a.e. will get you my latest blurb.

H.P. certainly. The Credit Co., have such long faces as they count their devalued millions. 'Tis heart-breaking, Jim lad !

73,

The Bandit,
VE8DP/G3UBO.

INDEX TO
ADVERTISERS

	PAGE
Aeronautical Instrumentation, Ltd.	723
A.J.H. Electronics	723
Amateur Electronics (G3FIK)	727
Baginton Electronics	726
D. J. Bean	719
Charles H. Young	cover iii
Coventry Communication Equipment	715
D. Cursons	728
Daystrom	668, 669
Derwent Radio	719
Eddystone Radio	cover ii
Eley Electronics	728
Finnigan Speciality Paints	718
George Francis	666
G3HSC (Morse Records)	725
Globe Scientific, Ltd.	726
G.W.M. Radio	722
Hangear Electronics	728
Henry's Radio	718
Home Radio	672
A. Imhof, Ltd.	725
Jack Tweedy, Ltd.	717
J. B. Lowe	674
John's Radio	676, 717
JXX Converters	725
K.W. Electronics	front cover
Lasky's Radio	676
Marlison Electronics	719
Minitenna Products	718
Mosley Electronics	672
Multicore	728
N.W. Electrics	724
Partridge Electronics, Ltd.	670
Peter Seymour, Ltd.	671
Proops, Bros., Ltd.	719
Radio Shack, Ltd.	665
Rex Radio	722
R.T. & I. Electronics	726
Shure Microphones	666
Small Advertisements	719-726
Smith & Co., Ltd.	673
Space Research	718
Spacemark, Ltd.	718
S.S.B. Products	717
Stephens-James, Ltd.	727
Swanco Products, Ltd.	720, 721
S.W.M. Publications cover iii and iv, 716, 727, 728	
Taurus Electrical Services	726
Telltime, Ltd.	716
Trio Corporation	667

SHORT WAVE MAGAZINE

(GB3SWM)

Vol. XXV

JANUARY, 1968

No. 291

CONTENTS

	Page
Editorial	677
An HF-Band Transverter , by B. A. Watling, G3RNL	678
Useful Double-HT PSU Circuit	683
Going Sideband on VHF , by T. P. Douglas, M.B.E. (G3BA)	684
Communication and DX News , by E. P. Essery, G3KFE	690
"SWL"—Listener Feature	697
An Eddystone Occasion	702
The Other Man's Station—G3WYS	704
The Twenty-Second MCC—Report and Results	705
New QTH's	713
Three-Band Aerial System	714

Managing Editor: AUSTIN FORSYTH, O.B.E. (G6FO/G3SWM)

Advertising: Maria Greenwood

Published at 55 Victoria Street, London, S.W.1, on the last Friday of the month, dated the month following. Telephone: ABBey 5341/2 (STD 01-222-5341)

Annual Subscription: Home and Overseas 42s. (\$6.00 U.S.) post paid

Editorial Address: Short Wave Magazine, BUCKINGHAM, England

AUTHORS' MSS

Articles submitted for Editorial consideration must be typed double-spaced with wide margins on one side only of quarto or foolscap sheets, with diagrams shown separately. Photographs should be clearly identified on the back. Payment is made for all material used, and it is a condition of acceptance that full copyright passes to the Short Wave Magazine, Ltd., on publication.

© Short Wave Magazine Ltd.

Lasky's Radio

NOW AVAILABLE FOR THE FIRST TIME IN GREAT BRITAIN TWO NEW TRIO COMMUNICATIONS RECEIVERS

These receivers offer the Ham enthusiast high quality and the latest design developments at a realistic price

MODEL JR-500SE



This high performance receiver is made especially to cover the amateur bands and utilises a crystal controlled double heterodyne circuit for extra sensitivity and stability. **Brief spec.:** Covers all the amateur bands in 7 separate ranges between 3.5 and 29.7 Mc/s. Circuit uses 7 valves, 2 transistors and 5 diodes plus 8 crystals; output 8 and 500 ohm and 500 ohm phone jack. **Special features:** Crystal controlled oscillator ● Variable BFO ● VFO ● AVC ● ANL ● S meter ● SSB-CW ● Stand-by switch ● special double gear dial drive with direct reading down to 1 kHz ● Remote control socket for connection to a transmitter. Audio output 1 watt. For use on 115/250 V A.C. Mains. Superb modern styling and control layout—finished in dark grey. Cabinet size 7 x 13 x 10in. Weight 18 lbs. Fully guaranteed, comp. with instruction manual and service data.

LASKY'S PRICE 59 Gns. Carriage and Packing 12/6.

MODEL 9R-59DE

Brief spec.: 4 band receiver covering 550 Kc/s to 30 Mc/s continuous and electrical band spread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. **Special features:** SSB-CW ● ANL ● Variable BFO ● S meter ● Sep. band spread dial ● IF frequency 455 Kc/s ● audio output 1.5 W ● Variable RF and AF gain controls. For use on 115/250 V A.C. Mains. Beautifully designed control layout finished in light grey with dark grey case, size: 7 x 15 x 10in. Weight 19 lbs. Fully guaranteed, comp. with instruction manual and service data.

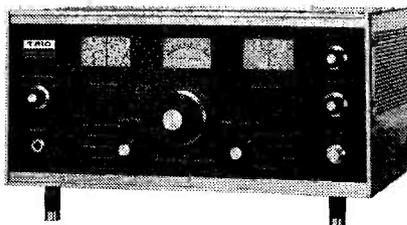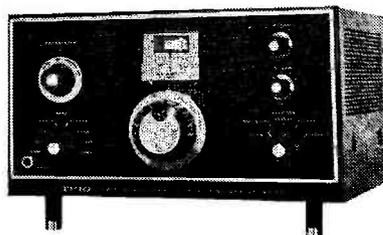
LASKY'S PRICE 35 Gns. Carriage and Packing 12/6.



207 EDGWARE ROAD, LONDON, W.2 Tel. 01-723 3271
33 TOTTENHAM CT. RD., LONDON, W.1 Tel. 01-636 2605
The above branches open all day Saturday. Early closing Thursday.

152/3 FLEET STREET, LONDON, E.C.4 Tel. FLE 2833
Open all day Thursday. Early closing Saturday.

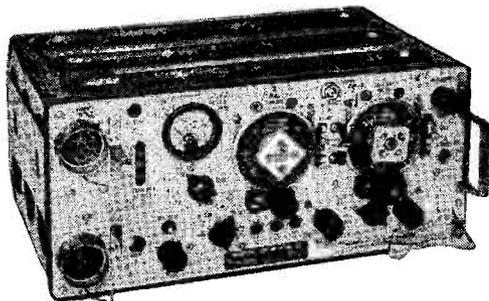Mail Orders and correspondence to 3-15 Cavell Street, Tower Hamlets, London, E.1. Tel. 01-790 4821/2



FAMOUS ARMY SHORT-WAVE TRANSRECEIVER MK.III

This set is made up of three separate units (1) a two valve amplifier using a 6V6 output valve; (2) (some only, not built in the very latest models) a V.H.F. transreceiver covering 229-241 Mc/s. using 4 valves; (3) the main shortwave transmitter/receiver covering, in two switched bands, just below 2 Mc/s.—4 Mc/s., and 4½ Mc/s.—8 Mc/s. (approx. 160-37.5 metres) using 9 valves. For R.T., C.W., and M.C.W. The receiver is superheterodyne having 1 R.F. stage, frequency changer, 2 I.F. (465 Kc/s.) signal detector, A.V.C. and output stage. A B.F.O. included for C.W. or single side-band reception. T.X. output valve 807 other valves octal bases. Many extras, e.g. netting switch, quick flick dial settings, squelch, etc. Power requirements LT 12 volts, HT receiver 275 volts D.C., HT transmitter 500 volts D.C., size approx. 17½ x 7½ x 11 ins. Every set supplied in new or as new condition in carton with book including circuits, only £4 10s. 0d., or Grade 2 slightly used 50s., carriage both 15s. A KIT of brand new attachments for this set including all connectors, control box, headphones and mike, co-axial lead, etc. at only 40s., carriage 5s. 12 VOLT D.C. power unit with all connectors to set and battery, 30s., carriage 5s. WE MAKE A MAINS 200/250 VOLT POWER UNIT in louvred metal case to plug direct into set power socket to run (1) receiver, 70s., post 5s.; (2) TX and RX, £6 10s. 0d., post 7s. 6d. A charge of 10s. to unpack and test the receiver of these sets is made only if requested.

FEW ONLY LEFT

WALKIE-TALKIE MK III and CRYSTAL CALIBRATOR No. 9

This set is housed in a waterproof diecast aluminium case made by Murphy Radio for the Govt. having only reliability and quality in mind. Range 7.3—9 Mc/s. also on side of set is crystal calibrator No. 9 which gives pips on marks provided on the tuning dial. Set uses a total of 5 valves; power required L.T. 4 volts D.C. H.T. 100-175 volts D.C. Sets supplied in NEW or as new condition, boxed, only 37/6, carriage 7/6.

V.H.F. TRANSRECEIVER MK.1/1


This is a modern self contained tunable V.H.F. low powered frequency modulated transceiver for R.T. communication up to 8-10 miles. Made for the Ministry of Supply at an extremely high cost by well known British makers, using 15 midjet B.G. 7 valves, receiver incorporating R.F. amplifier, Double superhet and A.F.C. Slow motion tuning with the dial calibrated in 41 channels each 200 Kc/s. apart. The frequency covered is 39 Mc/s.—48 Mc/s. Also has built-in crystal calibrator which gives pips to coincide with marks on the tuning dial. Power required L.T. 4½ volts, H.T. 150 volts, tapped at 90 volts for receiver. Every set supplied complete with valves and crystals. New in carton, complete with adjustable whip aerial, and circuit. Price £4 10s. 0d. carriage 10s. Headset or hand telephone 30s.

JOHN'S RADIO

(Dept. F)

OLD CO-OP, WHITEHALL ROAD,
DRIGHLINGTON, BRADFORD

Telephone: DRIGHLINGTON 732

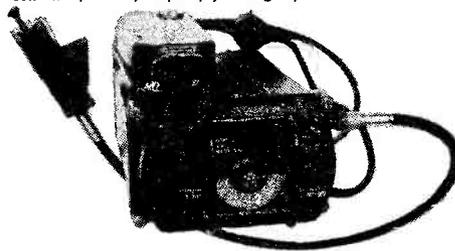

FOR THE RADIO AMATEUR AND AMATEUR RADIO

The
SHORT-WAVE
Magazine

**To All Our Readers, a Very Happy
New Year, with Prosperity and
Good Health in 1968**

It is again the season for Sound Advice and Good Resolutions—and it hardly needs saying here that in our world of Amateur Radio much useful advice could be given and a long list of excellent resolutions could be catalogued.

It is widely held that nowadays radio amateurs use more commercial equipment than gear they design and build themselves. Certainly, whereas 30 years ago it was essential to home-construct much of one's apparatus, today there is no need to build anything at all—it can all be bought off the shelf, ready to go on the air. There is nothing wrong with this; indeed in many ways it is a very good thing that such an approach to Amateur Radio is possible.

But as always, amateurs will remain individualists who pursue a great hobby as the spirit moves them—they are not really much concerned about what others may be doing, thinking or building.

So instead of offering advice for the New Year to those who may glance over this page, we would simply say that we wish all our readers, all over the world, the best of luck, happiness and good fortune for the coming year, and success in whatever direction their amateur activities may lead them.

*Austin Foshk,
G6FO.*

WORLD-WIDE COMMUNICATION

AN HF BAND TRANSVERTER

CIRCUIT DESIGN— AND A PRACTICAL EXAMPLE

B. A. WATLING (G3RNL)

Our well-known contributor now offers a solution to the familiar problem of working SSB on other bands when an existing Sideband transmitter or transceiver only gives restricted coverage. The principle of signal mixing at the proper frequencies to get SSB output on some different band or bands is well enough known—but there can be design difficulties if the amateur constructor is starting from scratch. All these are ironed out in the G3RNL HF-Band Transverter described and illustrated here.

—Editor.

STATIONS running commercial or even home-built rigs with only limited band coverage soon get to the stage of wondering how best to get going on the other bands. With improving conditions on the HF bands, 10-15 metres appear as a very attractive proposition. Several possibilities are considered. Either the purchase of an all-band rig, or constructing a small transmitter or transceiver for these two bands. The first alternative is a problem because of the cost, while the second alternative has most of the frustrations of building multi-band equipment. The answer then is to construct some form of converter. The existing rig can be plugged into this new unit which then converts the output signal into the required bands.

For owners of transceivers, a transverter is called for. This will not only mix the transmitter output to the other bands, but also act as a crystal controlled front-end converter on the receiver side. It was mainly for the owners of transceivers such as the NCX-3, HW-12 or M. & G. three-bander that the G3RNL transverter was devised. Even if separate transmitters and receivers are available, this same unit can still be utilised as a transverter. Alternatively, it can be run as a transmitter-converter only, by leaving out one of the five valves.

General Considerations

The transverter to be described was built specifically for use with the transceiver at G3LAT, which gives three bands—160, 80 and 20 metres. The other three bands, 10-15-40m., are provided by the transverter.

The size of the unit was designed to fit the available components, but with a little careful shopping round for certain items and lowering the PA valve through the chassis, the height could be reduced and made compatible in appearance with an existing transceiver. The PA valve in the transverter is the same as that in the transceiver, a 6146 in this case. This enabled the existing PSU, which had some capacity in hand, to be used. If the power supply is already running at or near its limit then, of course, a separate power supply for the transverter will have to be provided. The power requirements, using a 6146 in the PA, are: +750v. at 120 mA peak,

+250v. at 40 mA, +210v. stabilised at 15mA, —100v. at 15 mA and 6.3v. AC at 3 amps.

Circuit Plan


Fig. 1 is a block diagram of the transverter. V1, a 12AT7, operates as the conversion unit on the "transmit" side and is a simple balanced mixer. This is necessary in order to help suppress the straight feed-through of the 80m. signal or its harmonics, preventing these from reaching the aerial. Following the mixer is V2, a 6CH6 driver, which doubles as an RF amplifier on "receive." Gain control is effected on this stage for both transmit and receive. The relevant potentiometer is connected into the cathode circuit as part of the transmit/receive switching. The driver is followed by a Class-AB1 PA, a 6146 in the prototype. On the "receive" side the aerial is switched to the input of V2, which then functions as an RF amplifier. The output of V2 feeds V5, the receiver mixer. This form of mixer was chosen for its low-noise characteristics, as well as the good isolation it gives between the conversion oscillator input and the signal path. If the oscillator injection were to be to the cathode of this mixer, then a positive feedback loop would occur on "transmit."

Switching is also provided in the design so that the transverter can be left permanently connected to the transceiver. When switched to "Thro," the transceiver operates normally with the supplies to the relay, receiver mixer and conversion oscillator taken off. The PA is normally biased back anyway, leaving only the driver/RF amplifier conducting. An additional switch could be included in the PSU or on the transverter itself, to cut the heaters of the transverter for sustained non-use.

Circuit Details

The transmitter mixer, V1 of Fig. 2, is a simple balanced mixer that requires no adjustment. The incoming signal appears on the cathode of the first half of the triode and is coupled *via* C2 to the grid of the second triode. The two anodes are strapped together so that the components of the incoming 80-metre signal appearing at these anodes cancel (due to the fact that they are in phase opposition). The incoming signal is mixed with the output of the conversion oscillator (V4). This signal appears on the grid of the first triode of V1. The incoming 80m. drive must be of low level to prevent overloading of the mixer and is, therefore, coupled to the cathode of the mixer *via* C1, while R1 is selected to match the output impedance of the transceiver (50-ohm or 75-ohm). The drive requirement is only a matter of 2-3 watts maximum. Any more will drive the mixer towards cut-off and, therefore, reduce the output and would, of course, produce a very distorted output. If any difficulty is experienced in reducing the output of the transceiver to a suitably low level then C1 can be cut down to just a few pico-farads. This means, however, that the resistor R1 will need to have an increased power rating to soak up the unwanted output of the transceiver. In the prototype, however (using an M. & G. transceiver) the drive could be reduced to manageable proportions. If, on other types, it is found that the only way the drive can be reduced is by turning down the transmitted audio gain, then this will not be very satisfactory—because if only the audio is reduced

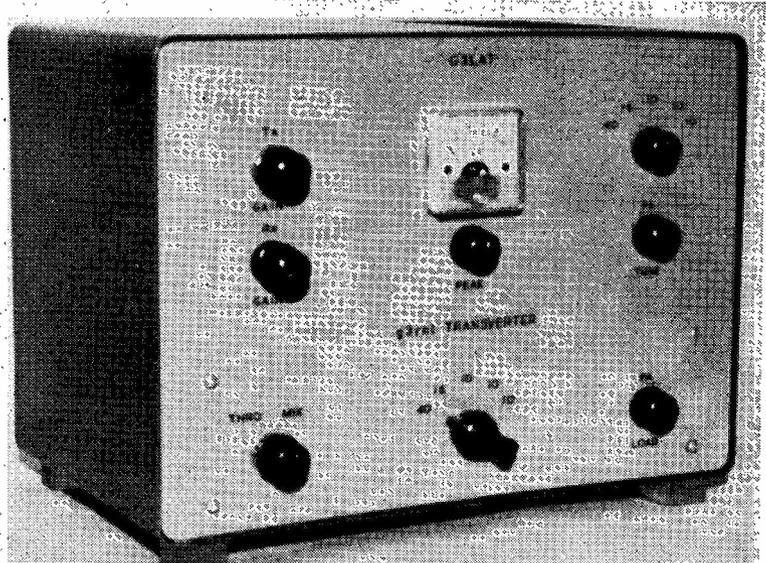Front panel view of the completed Transverter, this model actually being built for G3LAT—see text.



the "suppressed" carrier stays at the same level; this means that the ratio of carrier to peak output will be such that the output from the transverter will be approaching AM! If there is no gain control in one of the RF stages of the transceiver the only answer is to use a small coupling capacitor for C1 so that the audio gain on the transceiver can be kept at a reasonable level.

The driver stage is conventional Class-A with the cathode switched on change-over to the relevant potentiometer. These provide "Transmit" and "Receive" gain facilities. The PA, in Class-AB1 has π -tank output coupling and is neutralised by NC. In the prototype NC needed only to be a matter of a few pico-farads. It can be made up by two pieces of substantial insulated wire, about 2 inches long, twisted together. If this does not provide enough capacity for neutralising then the driver tuned circuit decoupling capacitor (C14) can be reduced to as little as 300 $\mu\mu\text{F}$.

Coil Points

In order to simplify the switching the anode coils of the transmitter mixer (V1) are arranged such that the 40-metre coil is in circuit all the time and the other coils are switched to be in parallel. This allows the aerial input to be permanently wired to the link on the 40-metre coil with no switching required.

In the prototype, switched coils were used as the conversion oscillator anode load. This was found most convenient due to the large frequency differences involved. If only 15 and 10 metres be required (as would be the case if used with an NCX-3) then only one coil would be needed as the anode load, with condensers switched across to change its resonant frequency. New wire-ended crystals were used in the prototype. However, surplus FT-243 crystal should prove satisfactory. For 40-metre operation a 3.3 mc fundamental crystal was used, while for 10-15 metres the second harmonic of a


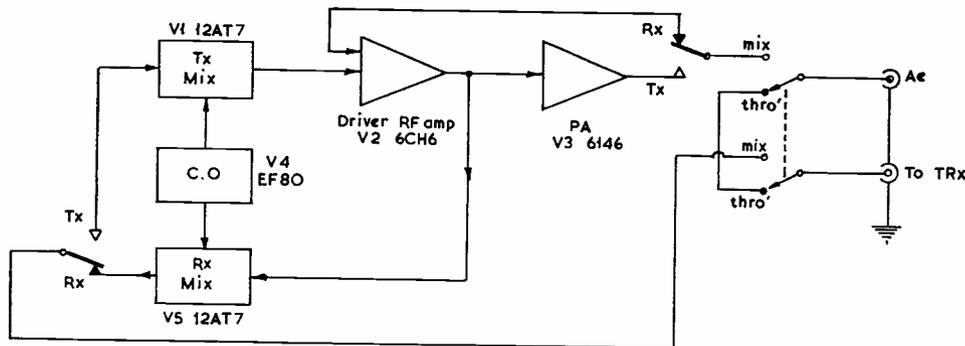


Fig. 1

Fig. 1. Schematic diagram of the Transverter

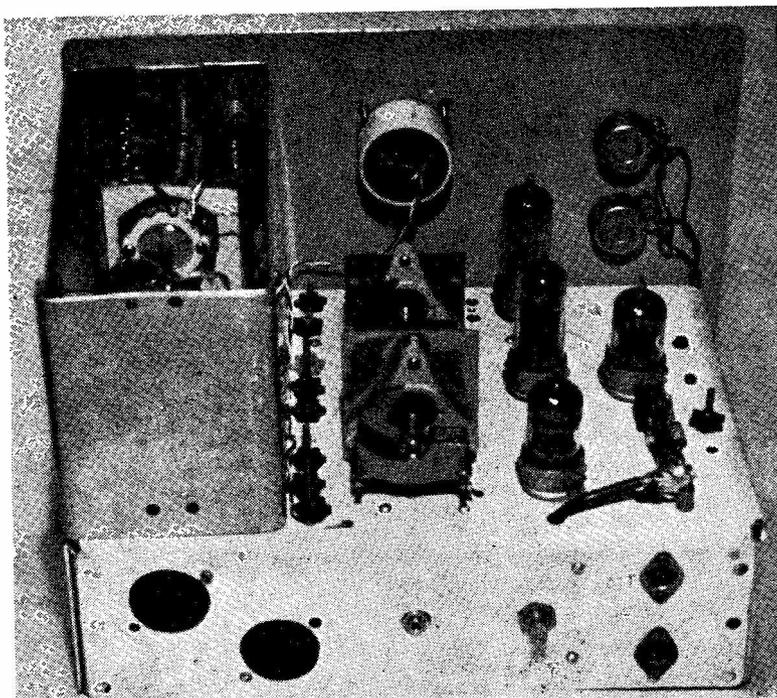

Inside view of the top-chassis layout of the G3RNL Transverter.

12.5 mc crystal and the fourth harmonic of crystals around 8 mc respectively were selected.

Layout

Construction of the prototype was on a four-sided chassis measuring 10in. by 7in. by 3in. deep. The front panel is 10½in. by 7½in. Each stage in the prototype was screened, but this amount of screening probably was not necessary. The valve layout, as seen in the illustrations is, from the front panel, crystal oscillator V4, driver V2, transmitter mixer V1. To right of these is the receiver mixer V5 and to the left is the PA compartment including V3 and the π -tank coil and PA tuning capacitor. The change-over relay is mounted under the chassis near the receiver mixer V5 and the Mix/Thro switch.

Operation

With the Mix/Thro switch set to "Mix," the "Peak" control should first be peaked up on a received signal. This will set it near enough for transmission. On "transmit" a small amount of carrier can be inserted to give a slight rise in cathode current above the no-signal level (25 mA). The peak control can now be set for maximum reading on the cathode current meter. With about 50 mA indicated, the PA tune should be adjusted for maximum output (or dip if the PA is neutralised correctly). The carrier can now be increased until the point is reached where further carrier does not increase the cathode current. The PA should then be loaded for a maximum cathode current of 135 mA. The tune-up procedure must be done fairly quickly to prevent

Table of Values

Fig. 2. Main Circuit, G3RNL Transverter

C1 = 50 $\mu\mu\text{F}$ (see text)	R4 = 2,200 ohms
C2, C21 = .001 μF	R6 = 1,500 ohms
C3, C7,	R7 = 470 ohms
C8, C11,	R8 = 15,000 ohms
C12, C14,	R10, R12 = 47 ohms
C16, C17,	R11 = Meter shunt (to
C20, C22,	150 mA f.s.d.)
C25, C27 = .01 μF	R14, R15 = 27,000 ohms
C4, C9,	R16, R17 = 4,700 ohms
C26, C29 = 47 $\mu\mu\text{F}$	R19 = 1,000 ohms
C5, C10 = 300 $\mu\mu\text{F}$	R21 = As for relay
C6, C13,	R22 = 10,000 ohms
C16, C23,	RV1,
C24 = 100 $\mu\mu\text{F}$	RV2,
C18 = .001 μF , 4kV	RV3 = 20,000-ohm pot.
C19 = .01 μF , 1kV	RFC1,
VC1 = 50 $\mu\mu\text{F}$, two-gang	RFC2 = 2.5 mH RF choke
VC2 = 365 $\mu\mu\text{F}$, wide-spaced	X1 = 3,300 kc
VC3 = 365 $\mu\mu\text{F}$, two-gang	X2 = 12,500 kc
R1 = To match o/p, 50/75 ohms	X3 = 8,000 kc
R2, R5,	X4 = 8,125 kc
R19, R13,	X5 = 8,250 kc
R18, R20 = 100,000 ohms	V1, V5 = 12AT7
R3 = 100 ohms	V2 = 6CH6
	V3 = 6146
	V4 = EF80

TABLE OF COIL DATA

- L1, L4: Denco Range 4 "blue."
 L2, L3, L5, L6, L10, L11, L12, L13: Denco Range 5 "blue."
 L7: Six turns 20g. wound on R12.
 L8: 21 turns 18g., one-inch diam., tapped at 5t. and 7t. from VC2 end.
 L9, L14: Denco Range 3 "blue."

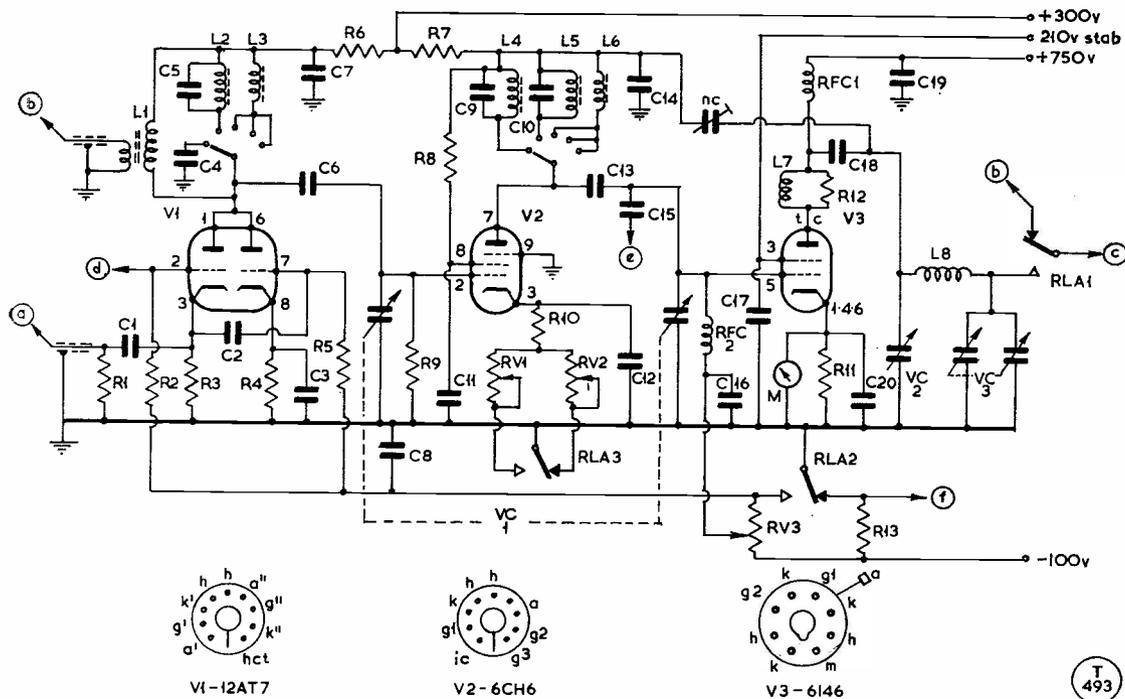


Fig. 2A "TRANSMIT" PATH

Fig. 2(A). "Transmit" path circuit diagram — and see below.

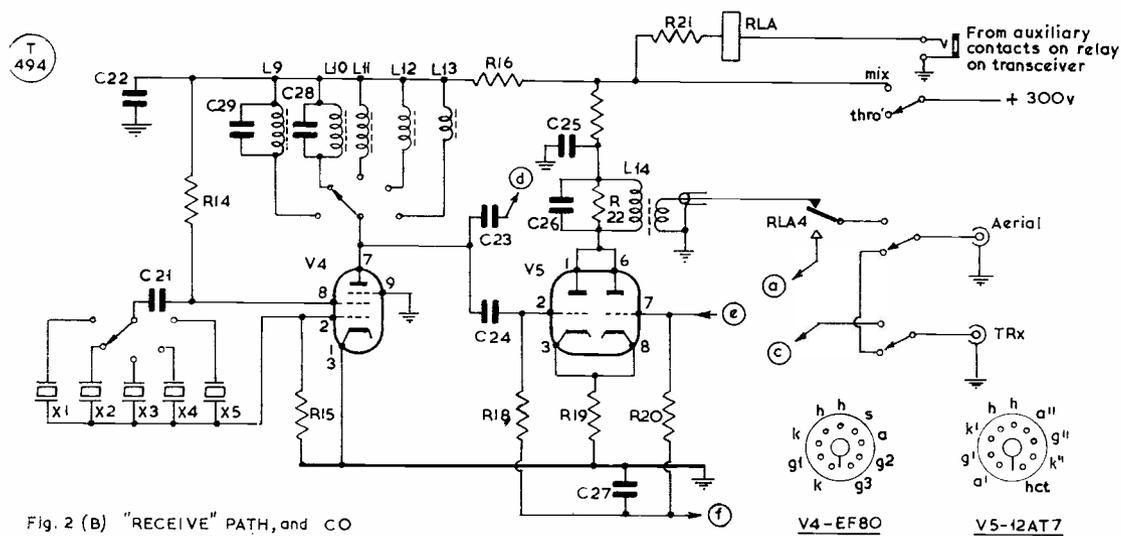


Fig. 2 (B) "RECEIVE" PATH, and CO

Fig. 2(B). The "receive" path and CO circuit for the G3RNL transverter. Points (a), (b), (c) etc. inter-connect with Fig. 2(A). Note that the unmarked resistor between C25 and R21 is R17.

exceeding the anode dissipation of the PA for too long. It is advised that full input only be used for about 2-3 seconds at a time. On voice modulation the cathode current should peak up to only *half* that indicated with full carrier.

Alternative Arrangements

In the case where a separate transmitter and receiver are used this same transverter can be employed. The 80-metre band on the receiver then becomes a tunable IF. No modifications are required to the unit for this form of operation. The aerial input to the transmitter, having its own aerial change-over facilities, should be connected to the input socket of the transverter. If only a transmitter-converter is required then V5 can be left out of the circuit altogether and the aerial change-over switching altered so that the aerial is switched to the transverter input socket on "receive."

If different bands are required, e.g. 20 metres, as may be the case if an HW-12 transceiver were used, then the conversion oscillator frequency must be 18 mc. This can be accommodated using a 9 mc crystal and doubling.

The conversion oscillator frequencies chosen for the transverter give full band coverage only if the original rig covers the full 500 kc of 3.5 mc to 4.0 mc. The dial readings relative to the 80-metre calibrations will then be as shown in Fig. 3.

Alignment

The following alignment procedure is intended as a guide to getting the transverter into a working state following its construction. The transceiver should first be set up on 80 metres and the PA tuned and loaded into a dummy load (or the aerial) before commencing the transverter alignment. The initial alignment can be done on any of the bands covered by the transverter and initially should have the PA anode and screen supplies disconnected. Ensure that the crystal oscillator (V4) is oscillating and then peak the anode load coils to resonate at the desired harmonic frequency. Resonate V1 and V2 and V5 (if used) anode loads on "receive" with the peak control set to mid position.

Adjust PA bias control for -50v. on the wiper with the equipment in the "transmit" position. Turn Tx gain fully up and insert carrier on the transceiver to a few watts driving the transverter. Monitor the output of the transverter and tune PA (with *no* HT on screen or anode) for maximum output. Adjust NC for minimum ensuring that PA is tuned for maximum output each time NC is adjusted. When complete connect PA supplies and equipment is ready to operate. Slight adjustment of the coils may be found necessary on transmit to ensure maximum drive.

Conclusions

One final thought on the subject of transverters is that the arrangement shown could be utilised to provide 160-metre operation, preferably mixing from 7 mc. This may be of interest to owners of transceivers covering 80 metres to 10 metres only. Conversion from 7 mc requires a conversion oscillator frequency of 5.2 mc. Another possibility is a transverter for 2-metre operation, mixing from either 20 metres or 10 metres. This would necessitate a slightly different arrangement than that

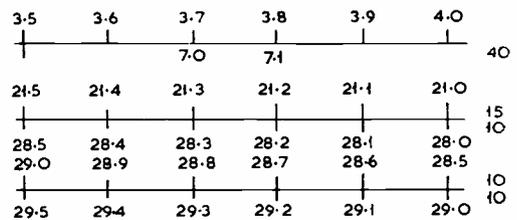


Fig. 3

T
495

Fig. 3. The dial calibration to be expected when using the G3RNL transverter from 80 metres, and crystal frequencies specified.

used in the G3RNL HF band transverter, but it can be done. One does hear, on the air, several views on the dissipating or wasting of power into a dummy load when using a transverter. The author's view on this is that if it is necessary—as in the case of rigs with only an audio gain control—it can still be more convenient, and cheaper, than building a separate SSB rig for the required bands!

COLOUR TV AT THE SCIENCE MUSEUM

If you want to see what Colour TV looks like—received in a high signal-level area—go to the Radio Demonstration Room at the Science Museum, South Kensington, London, S.W.7, any week-day between 1030 and 1100 or 1400-1530, or on Saturdays 1030-1200 and 1400-1600, clock times. If the colour TV is not on, they give you high-quality VHF radio, or DX communication on the amateur bands over the Science Museum's own station signing GB2SM.



"... Having a bit of trouble here with an intermittent—signal may have gone down..."

USEFUL DOUBLE-HT PSU CIRCUIT

GIVING TWO DC VOLTAGES FROM
ONE TRANSFORMER

THERE is a sufficiency of cheap rectifier valves and multi-wound HT transformers still available to make the circuit shown here an attractive proposition for an HT/PSU giving two output voltages.

The arrangement shown in Fig. 1 is somewhat unusual in that one set of rectifier valves and one HT transformer are connected to provide two DC voltages, one of which is twice the value of the other.

It is evident that this circuit offers certain advantages over the conventional HT power pack arrangement, as regards both initial cost and component space required. The rectifiers are not equally loaded, but by using U19's this is no disadvantage, since the maximum rating for four U19's, in this type of circuit, is 500 mA at 4000v. DC.

Operation of the circuit is shown more clearly in Fig. 2. Two of the U19's and the components dotted in take no part in supplying the low voltage HT so that the arrangement resolves itself into a two-valve full-wave connection with the rectifiers inverted. The HV side utilises the four U19's but Ch. 2, Ch. 3, C5-C6 and C7-C8 (which are series connected condensers) take no part in the operation of supplying the high-voltage HT.

For C1, C2, C3 and C5-C6 with C7-C8, series-connected electrolytic condensers are recommended. With proper choice of values, the necessary working capacities are easily achieved. On the LV side, the input choke Ch. 2 must not be omitted.

Operating Notes

In a Sideband amplifier, for which this particular power pack was designed, a very large variation of anode current is called for as the drive (input) signal changes. The swing may be anything from 50 to 300 mA.

Since the internal impedance of the power unit produces some interaction between the 1000v. and 500v. supplies (in the circuit of Fig. 1) a sudden demand for maximum current would cause a reaction on the 500v. output if conventional condenser capacities were used for C1, C2, C3. The solution is to use three 450v. working 160 μ F condensers in series, to give an effective 50-60 μ F at 1350v. working. Resistors R1, R2, R3

Table of Values

Circuits of Fig. 1, Fig. 2 and Fig. 3

C1, C2, C3, C5, C6, C7, C8 = 160 μ F, 450v. wkng. electrolytic	C10, C11, C12 = Rate for circuit
C4 = .01 μ F, 1,500v. wkng. paper	R1, R2, R3, R4, R5, R6, R7 = 100,000 ohms, 1- watt
C9 = .01 μ F, rated for voltage used	R8, R9 = 10,000 ohms, 1- watt

Note: Chokes Ch.1-Ch.6 can be 5-20 Hy swinging type, rated for maximum required current.

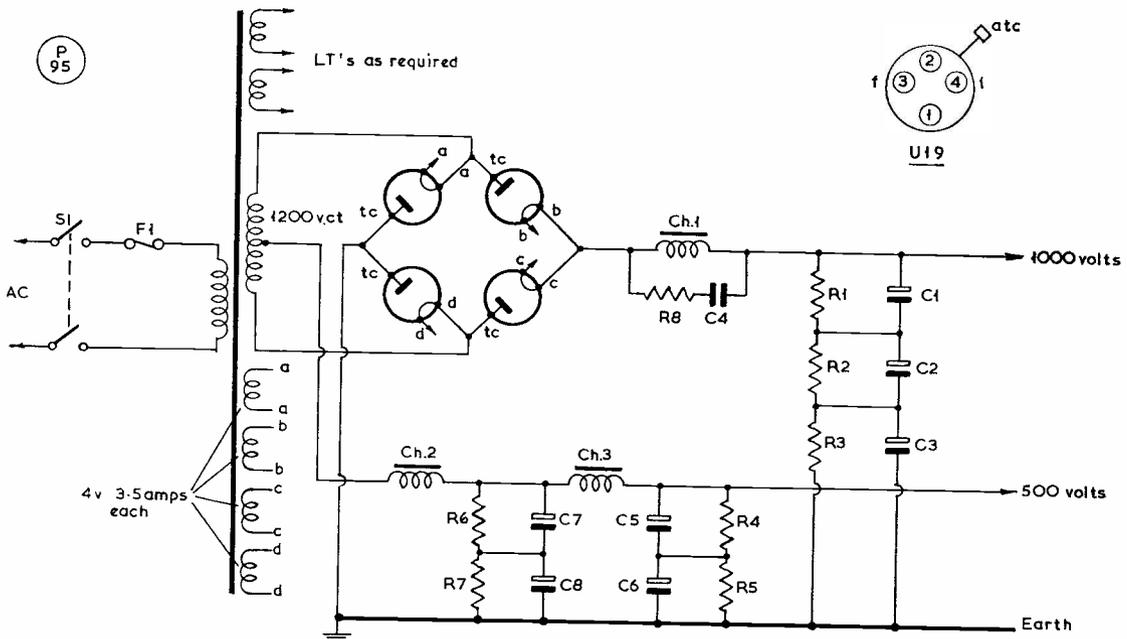


Fig. 1. HT supply circuit for two-voltage output.

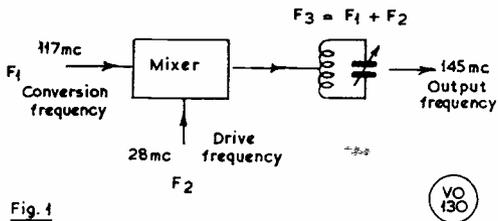


Fig. 1

Fig. 1. Basic frequency converter for two metres.

with cries of “there is no activity” or “only some of these SSB types quacking away.”

VHF at the best of times is an area of endeavour where a “piece of string” and a couple of watts never really bring in dozens of QSO’s. Beam aerials and quite good equipment are required to beat poor signal-to-noise over the longer distances. How often have we had to struggle to identify some weak carrier with low mod. whereas had the station been using CW or SSB it would have been quite easy. The long-distance skeds operated on both 4m. and 2m. have shown the difference when using SSB compared with AM. Recent Continental openings have been a give-away for the SSB group over here as they only had to tune over a few channels at the most and immediate contacts were gained by net-frequency operation, Vox or p-t-t control, and all with much less QRM than had the stations been on AM. True, the AM people had their fun, but it was so much harder having to wait your turn whilst the DX started at one end of the band and worked its way up to your crystal frequency! What was really startling about the November opening, however, was the number of EU stations which were now using Sideband. The SSB channels were just full of stations, many of them G, but mostly DL’s or PAØ’s. Comments on the air afterwards were generally to the effect that “you SSB boys certainly had a ball” or “it was all right for you SSB chaps, we had to wait our

turn.” The old adage of “if you cannot beat them, join them” seems to fit here, and it was with this in mind that set out here are one or two practical ideas, to show that VHF SSB is really very easy—and in many cases can be achieved by just a simple modification to existing gear which is perhaps not being used to its fullest capabilities.

For the doubters or those who imagine that going on VHF SSB is a “difficult thing” and requires lots of wasted time spent on building equipment, let it be said that it is quite simple. Apart from the fact that there are one or two excellent Transverters on the market which will give instant results without pain or strain, this article is really aimed at the man who wants to do something on his own.

Transverter Principles

Most amateurs are aware of the fact that in a multi-band SSB transmitter the sideband is developed at a relatively low frequency and this is then mixed with some crystal controlled RF source to produce the band required. To extend this to VHF is, in essence, exactly the same. So we can see that a transverter is not some complicated thing, but just another mixer stage with a few variations.

If we take for example a frequency of 117 mc and mix it with 28 mc in a frequency converter, we can obtain 145 mc by just adding the two frequencies. (Fig. 1.) To be more specific, if the 28 mc is actually 28.41 mc and the drive is exactly 117 mc, we get 145.41 mc at the converter output. If the 28.41 mc is a USB signal then this will produce a small SSB drive, also on upper sideband, on 145.41 mc. Now, the internationally agreed Sideband frequency sector on two metres is centred on 145.41 mc—so that in principle getting on 2-metre SSB is fundamentally straightforward. Obviously, there is much more to it than just getting a 117 mc crystal and beating it up with some 28 mc SSB, but let’s not get frustrated with complications, and see how we can expand on the principle.

[over

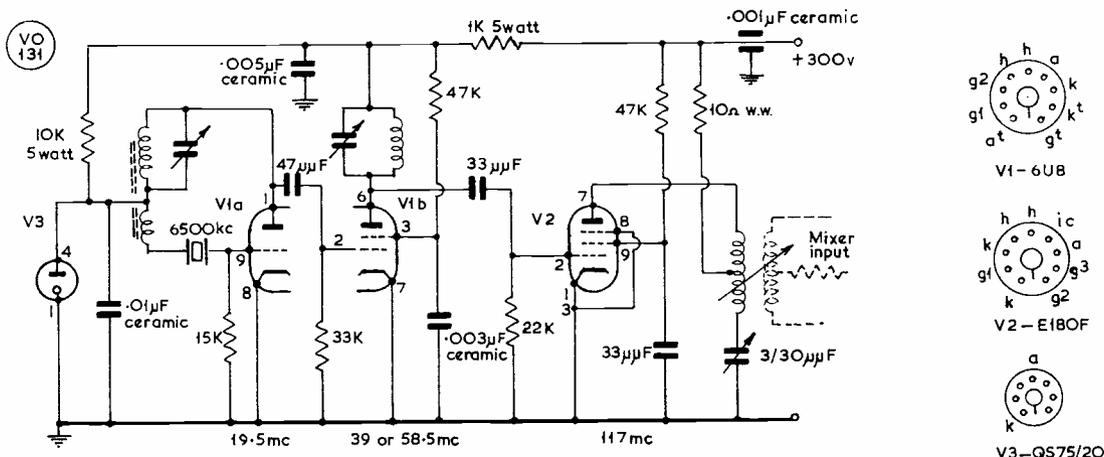


Figure 2.

Fig. 2. Conversion frequency stages for 117 mc output. The tuned circuits are proportioned to resonate for channels as indicated.

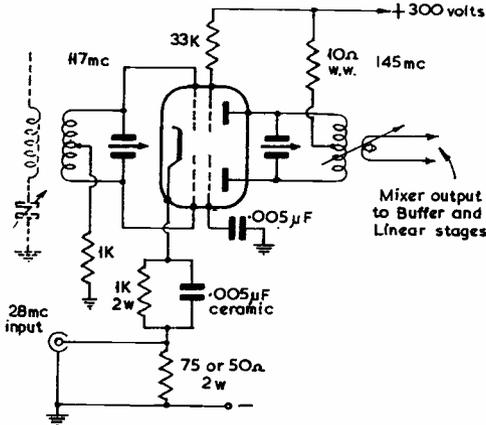


Fig. 3

VO 132

Fig. 3. A balanced mixer stage, the recommended arrangement.

Producing the Conversion Frequency

An actual crystal of 117 mc is not easy to obtain at present and in any case it is most unlikely that it would be capable of providing much power output with any real degree of stability. HC6/U crystals of 39 mc are available and these could be tripled to 117 mc, but this is not to be recommended as the HC6/U types, while being ideal in transistor circuits, abhor having a lot of power taken out of them or having their working state disturbed in any way by switching surges or the like. The FT-243 crystal of 6,500 kc operated in third overtone is hard to beat for ruggedness and will function very well indeed provided it is clean and undamaged. This then means that we have to generate 19.5 mc first of all and this can best be done in the triode section of a 6U8/ECF82—See Fig. 2. The pentode can then double the 19.5 mc to 39 mc or triple it to 58.5 mc; it is preferable to do the latter except possibly in Ch. 4 TV areas of very low field strength when the doubler would be advisable for obvious reasons. Next, to get the 117 mc out—this can probably best be achieved by using an E180F as a frequency doubler (or tripler) and there will be ample drive for what we want. Two valves total for the Conversion Frequency stage and that is all there is for this section. (Fig. 2, p.685.)

Type of Mixer

The mixer is perhaps the most important part of the whole transverter unit. A single-ended mixer could, of course, be used. However, it is very undesirable that this kind of circuit be adopted as, unless considerable filtering is embarked upon, the result will be full of spurious frequency responses. The Balanced Mixer is the arrangement to look at as this configuration can be used to reduce considerably one of the mixing frequencies. The problem is, which way round should we connect this mixer? Should we run the 28 mc in push-pull on the grids with the 117 mc in parallel, or *vice versa*? On the face of it, there might be a good case for the former

layout because the 117 mc could be so well attenuated that it could not possibly appear at the mixer anode. True enough, but it is not very difficult to use selective circuits to do this if need be, so let us look a little closer at the mixer circuit before making the final decision. If we have the grids and anodes in push-pull, then any frequency presented to the grids at any reasonable power level will become multiplied in the anode and passed on to subsequent stages. With a comparatively low frequency, such as 28-30 mc, as the SSB source it is not difficult to see that the 5th harmonic of 28 mc is 140 mc and of 30 mc is 150 mc—so that whichever frequency we use as SSB drive will come out either in or near the band as a horrid-sounding spurious of enormous proportions! But if we do things the other way round then all of the output frequencies from the SSB exciter will be suppressed in the mixer and the aforementioned tuned circuits will take more than adequate care of the 117 mc component as it goes through the subsequent stages. So recapping again: The 117 mc is push-pull connected on the balanced mixer grids, the 28.41 mc SSB drive is applied to the grid (or cathode) in parallel and the sum product is taken from the anode in push-pull. (Fig. 3.)

After the Mixer

Having got our 2-metre SSB drive in the right sense, *i.e.*, USB, the power at this stage is not more than about a watt or two p.e.p. output, thus amplification is called for in the usual way to boost it up to whatever power is desired. It is good practice to follow a mixer with a buffer in Class-A and a suitable valve for this is the QQV03-10 which, incidentally, is the type recommended for use as the balanced mixer. The final output stage could well be a QQV06/40A or similar, and this will take a good 120 watts input to produce 70 watts p.e.p. output, RF.

The circuit diagrams herewith should be fairly self-explanatory and need not be gone over in detail. If we take a look at the block diagram Fig. 1 of what stages we have in the transverter and compare them with those in any low-power transmitter used with crystal control on either 2 or 4 metres, it will be seen that both are well-nigh identical in arrangement. What this really means is that if you already have a QRP transmitter available, here you have the transverter all made up and ready to go after only a few minutes' work with a soldering iron and some resistors and condensers! The reasoning is

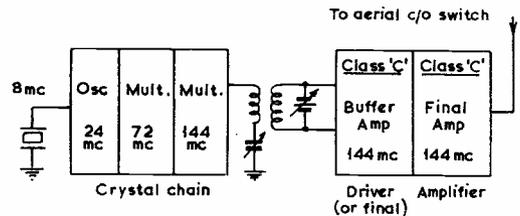


Fig. 4

VO 133

Fig. 4. Typical two-metre RF arrangement for a transmitter using crystal control.

thus: The usual VHF transmitter has a crystal oscillator/multiplier chain which is adequate to drive its power amplifier into enough grid current for Class-C operation. Compare it with the conversion frequency chain on the Transverter—surprise! It's the same (give or take small changes in circuit arrangement) so cunningly we throw away the 8 mc xtal for two metres and pop in the 6.5 mc FT-243 crystal already mentioned and tune it all up on 117 mc instead of 145 mc. This should be easy enough, as this frequency is lower than before, so circuits only need a bit more C to resonate.

Now look at the input of the QV03-10 or 832 or what-have-you in your old first amplifier—yes, it's in push-pull too! It only needs to be peaked on 117 mc and we are nearly on the band! Where's the SSB fed in? Well, that is where the soldering iron comes in. You will most likely find that the cathode circuit of what was your buffer or PA was grounded to earth by a strap or wire. Unsolder this lead and pop in a bias resistor (1K, 2w.) with a .005 μ F by-pass capacitor across it and then connect the earthy ends of these two components down to ground *via* an unby-passed 50 to 70 ohm non-inductive resistor of 2w. rating. Put about one watt p.e.p. RF at 28.41 mc across this small resistor and you can take off about 2 watts or so p.e.p. from the anode on two metres. If you have a following amplifier stage this is sheer bliss, as all you have to do is to fix its potentials for Class-AB1 operation and you are ready to go on the air. If you have not got an RF amplifier, you will have to make one up to the circuit in the sketch for this stage. (Fig. 6, p.688.)

What has been said for two metres goes also for four metres. There is as yet no fixed SSB channel on the 70 mc band but most SSB adherents are on 70.35 mc or slightly lower. Crystal frequencies for the 4-metre band can be worked out, taking 14 mc from the SSB exciter.

Some operators will be asking whether 14 mc could be used likewise for the 2-metre rig. Though the answer is Yes, there is a warning to be heeded—take the two-metre SSB output from the mixer into a buffer first of all and then *via* a tuned circuit inductively coupled to the linear grids to give sufficient tuning selectivity to ensure that the 131 mc component is eliminated from the transmitter output. In fact, it is good practice to put this simple tuned filter circuit into *any* SSB rig, as it deals very effectively with out-of-band spurious radiations, without complication.

SSB Driving Requirements

It may have been noted that only one watt of SSB excitation is needed for the mixer circuit described. But most SSB exciters have power outputs of 50 or 100 watts RF peak and this has to be attenuated in some way. You could take off a low-power drive from an early stage of the HF transmitter, but this may be inconvenient. By far the easiest way is to feed the HF Sideband Tx into its dummy load and run it as it was designed to work in the first place. This ensures that the signal out to suppressed carrier ratio is correct and that all transmitter noise is in the right proportion to the SSB output. Attenuate the voltage developed across the load down to the 7 volts peak or so required by a simple series capacitor variable from 5-100 μ F connected

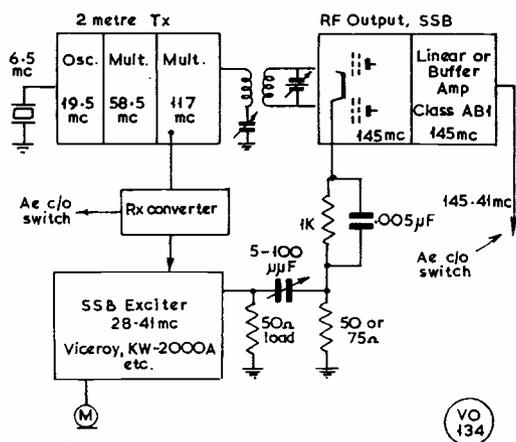


Fig. 5

Fig. 5. Transverter linear circuitry, for final SSB output on VHF. Auxiliary contacts on c/o switch or relay open the screen HT feed to mixer and following stages on "receive."

from the hot end of the load to the inner conductor of the coaxial cable which terminates on the 75- or 50-ohm unby-passed resistor in the mixer cathode.

Setting up the Mixer

It is necessary to set up the mixer in order to get it working cleanly and well within its capabilities. To do this we must measure the anode current of the mixer valve. If the crystal oscillator drive on 117 mc is cut and no SSB signal is being fed to the cathode, then the mixer valve will be running static. In this condition, with a 1K resistor in the cathode, the anode current with a 300v. supply rail will be about 15 mA or so. Switch on the 117 mc and drive the anode current up as high as it will go with all oscillator circuits and the mixer input tuned "on the nose." Now slack back the coupling from the last doubler to the mixer input until the anode current drops to about 30 mA. This is the right drive condition for the conversion frequency and no further adjustment is required. Put in SSB tone to drive the cathode with one-watt SSB RF when the anode current may rise ever so slightly. Reduce the 28 mc RF a little on the attenuator capacitor until only a 1 mA rise, at the most, is noticed in the mixer anode current. Do not exceed this setting from now on. Connecting the buffer (if any) and the linear, adjust for maximum drive all the way through. If the PA goes into grid current then reduce the SSB drive on the attenuator control only until it just tips grid current on voice peaks. Load up the PA for a shallow anode current dip for best linearity. The text books give all the appropriate information on how linear stages are adjusted—See 1967 ARRL Handbook, or Single Sideband (ARRL.)

Operating Conditions on VHF

To someone who has only operated on the HF bands the conditions which prevail on VHF may be a little bewildering. Those who find VHF operation the most rewarding will be operators who are situated well

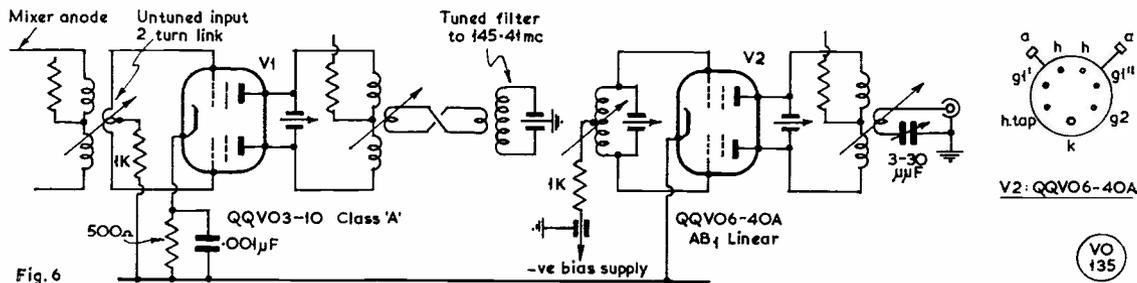


Fig. 6. Basic circuitry for typical buffer and linear amplifier stages, showing essential values.

a.s.l., with a clear unobstructed take-off in most directions towards the population densities from their location. Those who are screened into a valley, with high hills all round, will find it difficult to do well. For them, it is imperative that a properly mounted, rotatable, outside VHF beam system be erected, clear of other aerials and obstructions. It is best to go in for a thoroughly proved commercial aerial, designed for the band, and the best coaxial cable you can manage. The VHF population is much lower than on any HF band, so it is most unrewarding to come on, except by arrangement, outside the evening hours or at week ends. Of the total British VHF population, only a relative few have SSB gear and this is why we want more to come on to swell the ranks. The communications of the future will be *via* satellite of the synchronous type and it is certain that only SSB will be used for telephony work. Amateur satellites have been and are being sent into orbit and will use our VHF bands. The amateur with VHF/SSB equipment has this exciting new field before him. But in the meantime, on the everyday level VHF/SSB gives reliable communication over distances and from difficult locations where otherwise only CW could make the grade.

Every Monday from 2000z is Activity Evening on SSB, so the newcomer is advised to come on first during this period so that he can have the benefit of the help, which will be readily forthcoming, from the goodly number of stations on the air at this time. Remember

it is only necessary to be able to call CQ over the 145.4 to 145.5 mc spectrum for SSB, as normally there will be no Sideband stations on any other channel. If four metres is the interest, then Monday evenings same time around 70.35 mc will be where to look for QSO's, although current activity is somewhat less on this band than on two metres.

Reception of SSB on VHF

Nothing has been mentioned so far about receiving SSB on VHF. Any normal 2-metre or 4-metre converter can obtain its crystal drive from a little RF taken off the transmitter converter frequency chain instead of from its local oscillator chain, and then the IF can be modified to 28 or 14 mc as required. Transceivers will use the receiver side for their "receive" input and it will then be just like working on any of the bands for which the set was originally designed.

For those who have no converter and do not wish to build one, *JXK Converters* offer a unit which will function with any normal transverter crystal drive, either for transceive or split-unit working.

When you get on VHF/SSB you will find the natives are really very friendly and all are keen to help any newcomer. Sideband communication is the future method for most VHF voice work and it behoves us as amateurs to be in the forefront of such progress and to demonstrate this by our operating skills and equipment.

TO BE FAIR . . .


With reference to that picture of the Racal RA.1218 on p.617 of the December issue, we ought to make it clear that the sensitivity should have been given as "one *microvolt* for 15 dB S/N on CW/SSB"—and the stability as "50 cycles over 8 hours." It was just that in the printing the symbol μ got misplaced.

"MOBILE FOR TOP BAND"

For his article in the December issue, G3SFV now informs us that in the legend for Fig. 2 (p.626), C1, C7 should have been shown as 220 $\mu\mu\text{F}$ (C6 remains as .001 μF), and the Denco coils are "blue, 3T," while in Fig. 3 terminal 8 the transformer T1 is left floating. The transistor IF strips mentioned are obtainable as advertised by A.J.H. Electronics (G8AQN), on p.591 of the November issue.



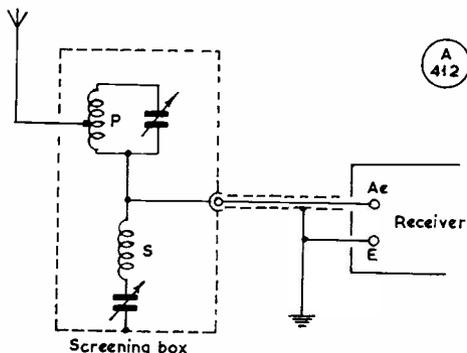"... Hope you can still follow—know I've got a mike somewhere..."



"THE BREAK-THROUGH PROBLEM"

Further to this article in the December issue of SHORT WAVE MAGAZINE, it is suggested by G51C (Shrewsbury) that the circuit shown above would give an even better result as regards rejection of an unwanted break-through signal at the receiver IF. The aerial is tapped down the parallel tuned circuit P, and S is series tuned. By making sure that P and S are well screened (in an earthed box, as indicated), and keeping the coax lead short, it should be possible to deal with almost any interfering signal by adjustment of P, S and the Ae tapping point, without affecting the general tuning of the receiver. What it comes to is that this is a useful and interesting experimental approach, which ought to give better results than that shown on p.641, December.

CHANGE-OVER SYSTEM FOR TWO TRANSMITTERS

At right is an arrangement suggested by G3OHK (Seaton, Cumbs.) where more than one transmitter is in use but only one aerial. The switching works very well, two wafers being used, each a single-pole three-way, with the central connection left open. The switch assembly itself should be of good quality (preferably ceramic), especially if full-power Tx's are being used. The rod through the switch wafers is made of Tufnol, or some other hard insulating material, and is carefully filed with two flats to engage with the wafers. For a tidy job, the switch-box (which need not be screened) could have coax sockets mounted on it, for the various leads.



MAST FOR VHF PORTABLE

GI8AYZ (Ballymena, Co. Antrim) describes a mast he uses for his 70-cm. beam when out /P. Three 7ft. lengths of 2in. dia. aluminium tube (sold as rain-water piping) are joined by using 15in. sleeves made by slitting pieces of the same material length-wise, opening the sleeve out a little along the slit and making a force fit of the joint, which is then secured by tightening up with Jubilee clips (the sort of screw-up clips used for car water-hose connections, and many similar purposes, obtainable in various sizes at most repair garages). The butt of the mast fits over a ground-spike driven in

close beside the car, with another support at the top of the door pillar, nylon guys being taken out from the second joint. The result is a cheap, light mast, easily and quickly erected, which knocks down to short sections convenient for transport. In GI8AYZ's case, the aerial for 70 cm. is a J-Beam "Parabeam," which goes up to 21ft. when operating portable with the mast described.

"VHF BANDS"

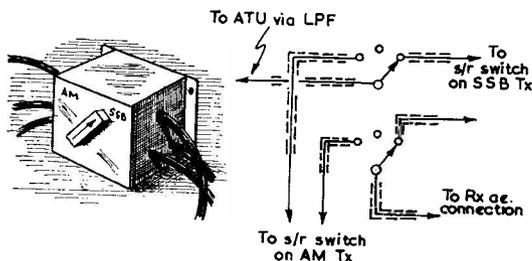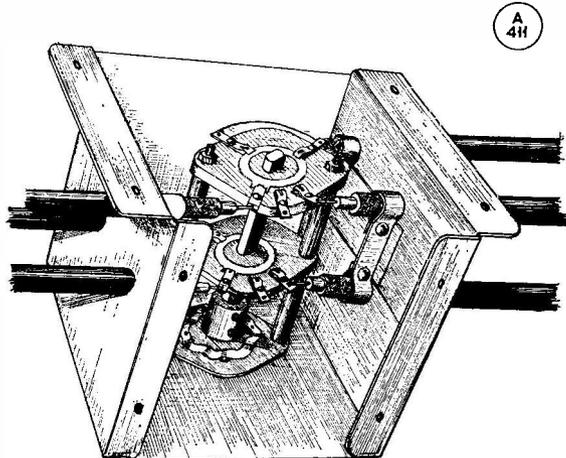For those who have written about "VHF Bands"—and made kind enquiries about A.J.D.—we had hoped before now to have been able to make an announcement regarding the re-appearance of the feature. Though it has not yet been possible to finalise arrangements we expect to be able to resume the feature very shortly.



COMMUNICATION and DX NEWS

E. P. Essery, G3KFE

JANUARY is traditionally the time for the making of Good Resolutions—and of breaking them as soon as possible! However this New Year pans out—and from this point in time it looks as though it will be one stage worse than 1940—there are quite a few things where the effect of a New Year resolution, carried out over the whole year, can improve our lot in the Amateur Radio context. Improvements in equipment performance; the installation of break-in facilities; a determined attempt to ensure that the outgoing signal is above reproach; adequate split-frequency facilities for those chasing DX with a transceiver—all these can be of great help. Above all, though, a change of heart on the operating side. Over the past year or so there has been an alarming slide in the standard of operating, and a lack of tolerance on the bands, which reflects itself in liddery and bad tempers, and even in downright contravention of the terms of the licence. As a tree is known by its fruit, so also is an op. by his fist and his behaviour—and none of us *wants* to be branded as lids!

Top Band DX Tests

Spinning the dial rapidly away from the voice of discontent, and tuning the bands, the first port of call is Top Band. Here the boot is on the other foot—your poor old scribe hangs his head in shame—because he forgot to mention the important matter of the Trans-Atlantic Tests. The times, as ever, are 0500 to 0730 GMT, and the dates December 31, January 14, February 4 and 18; the “First-Timers” sessions are January 7, February 4, and March 3. The W/VE stations will call “CQ DX Test” during the first five minutes of the hour, and alternate five-minute periods after that, listening during the intervening periods. The “even” five-minute periods (when the W’s are listening) the Europeans will be calling. This

routine should be adhered to *at all times unless a QSO is actually in progress*, and reverted to when the contact is completed. As for frequencies, the East Coast W’s will be in the 1800-1825 kc segment, and the Western ones 1975-2000 kc. VK5KO is understood to be coming on 1802 kc, Africans in the area from 1800 to 1830 kc, and everyone (note this) will be listening for the European stations between 1823 and 1830 kc. During the FT’sers sessions, it is particularly asked that those who have already “done the trick” will hold off and let the first-timers have a clear run, the only exception being the case where something rare and juicy which has not yet been booked in appears. In the latter case, the ploy is to get in, work him, and get off again with as little disruption of the first-timers’ activities as may be.

The CQ WW Top Band Contest occurs over the weekend January 27/28, from 0001 Saturday to 1500 GMT on the Sunday—the extra three hours being to give the West Coast W’s a chance. CW only is the rule, with no cross-mode or cross-band contacts allowed. Score 2 points for each station in one’s own country, five points for QSO’s with other countries, and 10 points for every W/VE/VO contact. A multiplier of one for every country (outside one’s own) W state, or Canadian Province, is allowed, and the total score is the QSO points *times* the multiplier. The Contest exchange will be the usual RST plus serial number, starting at 001, and followed, for the W’s, by their State or Province. Incidentally, Hawaii and Alaska will count as separate *countries*; and there are three Provinces prefixed VE1, and two signing VE8. Disqualification may be imposed for breaking the rules of the Contest, unsporting conduct, or taking credit for duplicate contacts in excess of 3 per cent. A whisper from a little bird says that there are going to be all sorts

of interesting things going on—so get the logs off in good time. Mailing deadline is February 29, and they go to: CQ 160 Contest, 14 Vanderventer Avenue, Port Washington, L. I., N.Y., 11050, U.S.A.

From Cyprus, another letter from ZC4GM (R.A.F., Episkopi), who indicates that already the weather has done its worst to his aerial; however, at the time of writing, Gordon was moving into different quarters, and had hopes of the necessary copper wire to erect a 360-footer emerging from the bottom of his kit. Gordon has hard things to say about the EU QRM—haven’t we all!—and their strange S9 babblings of “First QSO” and “QSL certain,” while ZC4GM is working someone else. An operating point, that is rather against the usual run, is that owing to the malign intelligence of the local thundercrashes, even an S9 signal needs to repeat each of the essential parameters of the contact—RST, name, QTH, and so on, several times if the contact is to be R5. Gordon’s own opinion is that at least *five* times is none too many. All the operational stations in ZC4 have extremely good receivers, but the constant static, regardless of the season, is the problem.

On now to G3BDQ (St. Leonards-on-Sea), who came on with his KW2000 and AR-8516L receiver between 2300 and midnight on the evening of November 25, staying on a frequency of 1820 kc, and worked OE5XXL, HB9NL, OF2KH, DL5YZ, EI9J, and ZC4RB—not bad for one hour of operation!

Another one to ring the bell quite hard on 160m. was G3VPS (Hailsham), who hooked 9H1AG on his second CQ with the Panda Cub which now decorates the shack, using a 175-foot end-fed wire hooked straight in to the Tx.

G3VMW writes to bring his table entry up to date, and mentions that he has been a participant in most of the Contests; Steve moves

up to 95 Counties/19 Countries, and worked a hatful of interesting stuff in the process, including VO1FB, ZC4RB, OF6UW, OE3PWW, HB9QA, HB9TT, HB9NL, OE5XXL, OF2KH, OE1KU, OE5KE, OE2JG, DJ6TR, DL1CF, DLØKF, DJ9IJ, DJ2TI, PAØPN, PAØGMU, EI9J, EI5AJ and of course many OK/OF stations.

Quite a long time since last we heard from G3UJS (Snettisham) who seems to be firing on all cylinders again after his back injury. Dave has put in a good deal of time elsewhere, but his main news is that he has a thousand cards to dispose of before he leaves U.K. for Australia; so anyone wanting one for Norfolk should work G3UJS if they have not already done so, and he will QSL 100 per cent by way of the bureau. The same applies to anyone who wants a card for a contact already made.

After a period of relative inactivity due to work pressures, G3SED is back on the band from Portsmouth. GW8CW was raised, but Mike understands that although many stations called him, Jan had considerable difficulty with the QRN, and just did not hear many of the callers. During the month of December, Mike prognosticates activity from 5Z4, VQ9 and EP2, and so will be about on the band, but in the New Year he intends to give the other allocations a whirl.

G3TNO (Horsham) used a home-built transmitter based on the 2DAF design, albeit with many modifications, and also a home-spun receiver to operate all bands from 160 to two metres. As far as the 1.8 mc activities are concerned, the aerial is the weak link, being a much-bent halfwave at a maximum height of 35 feet; it has produced OK, PA, DL, and ZB2BC whose card arrived *via* Bureau after Malcolm had mentally written him off as a pirate because the incoming signal was so strong.

Mike of G3VYF (N. London) bewails his "contact" with the supposed "VP8JD" which we discussed in this column last time; after replaying to himself the tape he made of the signal, G3VYF has to remark that it had all the right attributes of a DX signal, even if it was a phoney—but of course it may indeed have come from DX

somewhere or other.

More news of piracy, this time from G2HKU, who remarks on a character heard at 339 working OE2JG, and giving callsign as ZL1AJU, name Brian, and QTH Auckland, on 1824 kc. This one has to be dud for various reasons—in the first place the North Island ZL's have 1875-2000 kc as their allocation, secondly the real owner of the call lives over 40 miles from Auckland—so be warned! Ted has been activating the Isle of Sheppey pretty hard to judge by his list of QSO's, out of which we must mention a rather comic one: Seems G13NPP was hooked for Tyrone, but lost after exchanging reports; fifteen minutes later Ted was telling the sad story to G13OQR, who came back with "Yes, Ron is my brother and sitting here with me—we share the same shack!"

The delights of the new transmitter

have been somewhat curtailed for G3VWC (Bishops Stortford) partly through the need for revision and preparation for examinations, and partly because of time spent assisting with a local production of "Tom Jones"; three more counties were booked in, though, in G3NTI (Cheshire), G4LV for Northumberland and G3EKW, Notts.

Studies for A-level have also restricted things for GW3VPL (Porthcawl), who also mentions a rise of three counties; however, Steve has hopes that the pressure will be a little easier after Christmas and hence the score will rise.

A third one to suffer a lack of activity from the home station is G3WIT (Newport, I.O.W.) who spent more of his time contest-operating with the local group and also has a nice shiny new job on the go. He was at home for the recent 1.8 mc Contest, and heard lots of



Hector Cole, G3OHK, 25 Causeway Road, Seaton, Workington, Cumberland, runs a home-built SSB Tx (left), with a kit-constructed K.W. Victor (extreme right) and has a variety of auxiliary items, including gear for two metres. The HF-band aerial is a 135ft. wire. The receiver at centre is also a home-built job for all-band coverage.

the Northern stations on just before the "off"—alas, the most Northerly station worked was G3RPJ in Warwickshire.

ZB2AP came back to a CQ from G3TLX (Edgware), which must have shaken Ron to the core. However, he recovered from the shock enough to book in OF2KH, OK/OL's, DL/DJ's, and a PA0.

Contact with 6W8CW was missed by G3UBW, who is now at Cambridge, although we gather that his operating is done from home when he is on vacation—and so a wrong date meant that he went home on the wrong weekend. Meantime, thoughts are being turned to the key to all DX success on Top Band, namely improvements to the earthing system.

Since last writing, G2DC (Ringwood) has been sniffing around Top Band as well as his more usual stamping-grounds higher in the spectrum. Jack is firmly convinced that most of the *élite* on the band must either live on the tops of mountains or have dud PA meters, judging by the way in which juicy bits of DX pop up, work these chaps, and then disappear. During the period under review, with a genuine 10 watts and no mountain in sight, G2DC traded reports with thirteen countries.

G3PQF (Farnborough) is another call not often heard among the Top Band lists, but Dave tuned up forty-metre vertical with another leading coil which made it resonate on the band, and proceeded to work GM3SVK, GI6TK, and DJ4SS for his first contact with the Continent on 160 metres—all this using SSB.

A new reporter is GI3WSS (Holywood, Co. Down) who had been a medium-wave BC/DX addict for years before deciding to join the technical class locally and ending up by passing the R.A.E. and getting on the air. Cyril started off on Top Band, and his second QSO was GM3SVK, which must have pleased him no end. Eight watts to a bent hundred-footer wound into the garden has so far secured contacts with 56 counties and 7 countries—of which only three are GI, and one of those not regularly operational on Top Band. What it boils down to is

that just about every QSO that Cyril has is at DX.

Eighty Metres

Quite a crop of reports this time on the band; the first on the heap being that from G3VMW, who ran his standby rig at 60 watts to a 6146. This raised 5A1TP, 4X4CA, VE1ART on Prince Edward Island, W8GKX, K1LHK and an assortment of EU's.

The Royal Naval Amateur Radio Society wish it to be known that their code-practice runs, curtailed since 1965, are back in operation again; the first Tuesday in each month, and a start being made at 2000z on 3520 kc. Speeds will be 15, 20, 25, 30, and 35 w.p.m. and 100 per cent copy is required to qualify for one of the certificates they issue. Entries, with five three-penny stamps, should go to: QRQ Manager, RNARS, 27 Oxted Rise, Oadby, Leicestershire.

Talking about CW, G3TNO has an axe to grind. Malcolm is firmly of the opinion that *every* operator should be able to take the stuff down at 12's at least. The G3TNO aerial for 3.5 mc is the "5RV" type which had to be wangled over the top of the house carefully to get the length in; it has paid off with W, VE, all the usual EU calls and some of the rarer varieties of U-derivation.

Conditions on the LF bands have shown an improvement in the last month, and have helped G3TLX to work all W call areas apart from the sixes and sevens, VE, VO, CT, I, EA, ZL's and PY's, UL7GW, UA9's assorted, 5A1TP, UD6DF and CX8CZ. Point taken!

G3PQF has been playing around with "one of the old faithfuls" in the G3KFE thing on aeriels, and finds it gets the current node up in the air OK, but it is not as good as the loaded vertical—oh well! On the other hand, G2DC has been driving his existing skywire to no mean effect during the few hours he spent on 80 metres, the reward being 31 countries in six Zones.

Forty-Metre News

Still with G2DC, we find that Jack has been running a sked with

VQ9JW, which had not, at the time of writing, succeeded, although the G2DC signals had been heard. Up to around midnight 40m. seemed pretty hopeless, but through the night, after the rude noises have retired, all continents were workable. The best of the crop were EA8BF, EP2BK, KZ5TW, PY5BLR, PY7VON, TA2BK, UF6QB, UI8AI, VK7SM, W6HJT, W6IBD and ZL4IE.

The band still has great potential in the view of G3UJS, who has allowed it to monopolise his time, although Dave does not say in detail exactly what he found; however, your scribe would agree

TOP BAND LADDER		
(G3U-- and G3V-- stations only)		
Starting date, January 1, 1966		
Station	Counties	Countries
G3UTS	96	15
G3VMW	95	19
G3UBW	94	18
G3VGR	94	16
GM3UWL	93	13
G3VYF	83	17
G3VLT	80	16
GW3VPL	78	16
G3UXP	74	11
G3VMQ	73	15
G3UGF	71	11
G3VMK	70	11
G3UVT	68	12
GW3UUZ	66	15
G3VES	63	16
G3VOK	61	15
G3UJS	51	12
G3USE	51	12
G3VSL	51	9
G3VLX	50	8
G3VTY	49	9
G3UGK	43	13
G3UMK	39	7
G3UCS	36	?
G3VWC	34	7
G3VSI	19	4

that even during the evening period it is far from impossible to find a way through the crannies to the DX. On one evening the G3KFE receiver lighted upon a 4Z4 and a KP4, the former weakish but the latter a good signal, calling CQ—and little or no interest being shown in either of them.

G3TLX is the only other correspondent to make serious mention of 40 metres, and he winked out all W call areas, VE's, VE5VD, VE7BQF, KL7PI, LX, TF5TP, KP4UW, 9H1's, UM8BA, UL7, UI8, CX3BH, VK's and ZL's, ZB2, ZD3G, FP8DJ, HK4EX, PY 'LU, 4S7FJ, YV5BPJ, TA2BK and OX3ZO. In the intervals he "cleaned up" on the other bands and built a Heathkit DX-40U transmitter!

Using the mast for the aerials at G3TNO, as he has only permission for one pole—so he has devised a rapid system whereby, when he wants to change bands, he changes aerials over in about ten minutes; also he uses the stick as a GP aerial, in addition to the dipole, with the aid of pre-tuned ATU's for each, which also makes for speed. The ground-plane has not been properly tried out over a period as yet, but so far every evening session when it has been used has yielded at least one U.S. contact. One of the droppable aerials, as has already been mentioned elsewhere, is a "5RV," and Malcolm finds this inferior to the dipole, the latter yielding much better reports.

The HF Bands

For this time, with winter conditions well and truly upon us—and not just in the Amateur Radio context—it may be interesting to lump together the reports on the three HF bands and see how folk compare them.

Taking the letter from G2DC first, Jack seems to have been fairly active on all three; in terms of countries and Zones, Twenty has yielded 52/19, Fifteen 40/17, and Ten 67/32. On Twenty, good all-round DX under the QRM and the intruders, with the morning period probably the best, with CE2DI, PJ3CC, VQ9JW, KZ5TW and TA1AV outstanding. The 21 mc band has been doing it's stuff from



Station of G3GIQ, Henry Lewis, of 271 Popes Lane, Ealing, London, W.5, features a KW-2000A, with a Heathkit SB-200 linear amplifier and SB-610 'scope, as well as an AR88D as second receiver. Outside is a Mosley TA-33Jr. (traps of which are thought to have burnt out!) and though the main activity has therefore been confined to 10 metres, normally all HF/DX bands are worked, and Henry is also active on two metres. His first station appeared in "Short Wave Magazine" eleven years ago (December '56)—but since then there have been many changes.

around 0700 until 2000, with annoying fluctuations in the MUF at about the latter time, causing a station to disappear, and then suddenly return at good strength. On both these bands the JA's have been numerous during the morning period, so that DX is buried under them, but at least, as Jack says, they are possessed of good clean signals and do not smear the whole band. Turning to Ten, G2DC found it opening as early as 0700 to the South, with the West coming in around 1100, so that by noon it is possible to work all continents. CE3ZK, CX8CZ, ET3FMA, HPIIE, HP1HXG, OA4PF, PJ3CC, PZ1AH, several VK6's, VK8UG, VQ9JW and ZD8J add up to a good month at the CW ends of the bands.


G8DI (Liverpool) details the nature of the QRM from which he suffers—School rebuilding, rehearsals for a nativity play, and carol concerts!—which resulted in only two contacts of note. VP8JD(S, Orkney) was followed by a QSL direct from G2RF, which enabled Bert to apply for a "squiggle" certificate which he has wanted to

achieve for a long time; pity he was so excited your old scribe cannot decipher the squiggle! The other one, also found on 14 mc, was HZ1AB.

Apart from the Top Band activity discussed elsewhere, G3WIT preferred Ten and Fifteen, partly due to the loan to him of an AR88D. CW/SSB was used for a contact with VE3IT, who gave him 579 for his first VE on Ten, this one lasting for half-an-hour or more till the band started to fold up. Another one on Ten was LZ1CW, also for a new country, at 599 both ways. Fifteen also stumped up with a new country in the guise of EA7MG who came back to a CQ.

The Sphinx on the operating table and the sphinx behind the controls at G3VWC seem to be settling down happily together, and in the very limited time at their joint disposal another new one has been collected in the form of ZB2AP.

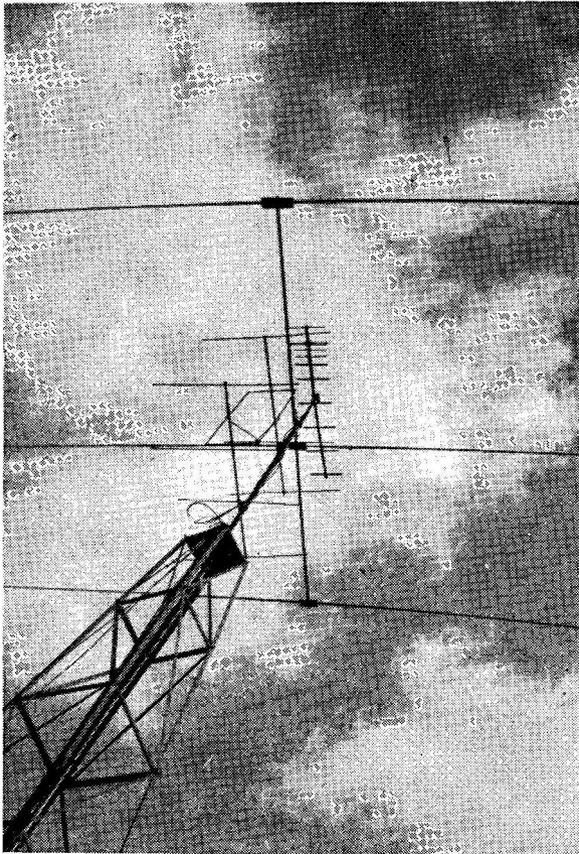G2HKU worked only VK7RX and his regular sked with ZL2KP on Twenty SSB, but heard in addition KG6AAY, OA4UZ KC4USD, and WA6YMT/MM bound for



Paul Smith, recently licensed as G3WPB at 76 Southfield Road, Hinckley, Leicestershire, has a very fine composite aerial array. Operation is on all bands 10 to 160 metres, as well as on VHF, and the lower assembly seen here is a 3-ele Yagi for 15 metres.

Christchurch and then on to McMurdo Sound, where he is to remain as KC4USG. CW on Twenty—listening only—gave F8TT/FC, VP8JG, XE1WS, FB8YY, PY7AHO, PY2DEH, YJ8BW (the latter being G3JWW, QSL via W4NJJ). Turning to the CW end of 21 mc, Ted heard UJ8AH, UL7KAA, ET3FMA, PY7NJ, JA6ELV, JA2JGC and EA8FJ.

Part of a note from ZB2BG mentions the activities in Gibraltar at the time of writing; the R.A.F. boys are still at it, mainly on Fifteen and Twenty. ZB2W is in the throes of building a Tx for Twenty Phone only, with an SSB rig for the same

band to follow; as he is located at the Europa lighthouse he gets out quite well. ZB2BG himself is nicely shielded by about 600 feet of Rock to the Eastwards and surrounded by high flats to boot, so that he can only expect his dipole on the roof to stump up in the Westward direction and has to take pot luck elsewhere. Also connected with Gib., although not there at the time of writing, G3RFH writes in to say that all the cards for his ZB2BA doings have now been sent. Ken has occupied the time during his two-year tour on his present ship by building a receiver, and a wobulator with which to align it, so that

now he is angling for a chance to get into one of the ship's receivers with the wobulator "just for a practice!"

After a three month's trial of his new QTH in a stone cottage 300 years old, set in a valley with 500-foot hills all around, G5CP (Ashover) finds his signals are really getting out to some effect. A dual-band 10/15 metre Quad two-element beam and a doublet of 300-ohm ribbon have been put up, and so far VK/ZL, most W districts, KL and ZS have all been worked, together with UV3BC/MM in the Antarctic—Twenty CW—and DI2LE/MM on his forty-foot catamaran *World Cat* by the same method.

Snapshooting is the best description of the tactics of G3VDL (Chalfont St. Giles) during the last month, due to a shortage of time and heavy commitments. These short, snappy sessions resulted in QSO's—all on CW with 60 watts to dipoles—with YV, JA, TF2WKS, and KZ5TW on 14 mc. Then 21 mc yielded OY6FRA, VK, PJ3CC, 4L3A(?), IS1, 5Z4KX, ET3FMA, HZ1AB, 5R8BA and 9G1HM, while the ten-metre stunts gave SV0WEE, KZ5GN, 4L3A, PJ3CC, ZS, 5R8BA, 9J2, 7Q7LZ, TJ1QQ and TA1AB. Since OY, PJ3, 5R8, and TJ1 were all new ones to give a lift to the score, it was quite effective shooting!

It seems quite strange to be compiling a column without the aid of a letter from GM3SVK, who by the time this is in print, will once more be just plain G3SVK—but our Far North still has a representative in the shape of GM3JDR (Golspie) who once again stuck to 14 and 21 mc, mainly the latter. Twenty CW accounted for PJ3CC, TY2KG, YV5BUA, 9H1AG and 9J2MX. On Fifteen, both CW and SSB were brought to bear, the former producing contacts with EA8, EL2D, ET3FMA, JA0AUF, KP4, PJ3CC, PY7ABY, TA's, TG0AA, TY2KG, assorted rarer U-varieties, VK/ZL, 4L3A, 5R8BA, 5H3KJ, 5VIKG and 6W8DW, while the talking-type stuff gave F9UC/FC, HP1AD, lots of JA's, MP4BBA, UA9KDL, UA0SK and ZC4AK. This, mark you in a month when the man complains that the band is closed for him by 1700! Whatever would he do if the band were open through

the 24 hours?

Enfield College of Technology have well and truly fired up G3VZN, and G3LAS, who is the chief driver, finds it all very exciting after those boring VHF bands where he has been holidaying these ten years past. However, the DX touch has not entirely deserted him, and on 14 mc HL9KR, KL7AHB, KR6CR, PZ1CE, TF2WKT, VE8ML and VE8RCS (both on Ellesmere Island) UAØNM, 3C1ASJ, together with hordes of VK's and ZL's, gave them a good start. On 21 mc, a gotaway was TJ1AR, but contacts were completed with CR4, DU1FH, KG6's, KV4, KZ5, VS6DO, VU2DKZ, YA1DAN, ZD7KH, 9G1FL, VK/ZL and all W call areas. As for 28 mc, the openings at times when G3VZN was on were mostly to Africa and U.S.A., so the log highlights the following: CE6EZ, CR6, EL8J, KV4, VE, VP2VM, XE's, ZD7DI, ZP5JB, 7Q7LZ, VK's, ZL's and all W call areas including K7ZFX/M in the streets of Phoenix, Arizona. An interesting contact was one with GB5QM/MM, the *Queen Mary*, the first indeed that has come to the notice of either this column or that of the SWL's, this occurring when she was west of Mexico.

Among the one-band merchants is G3SML (Earl Shilton) who spent his time on 21 mc. Roy mentions a round dozen VK/ZL contacts, plus KØILI/P/KG6, VU2DKZ, JA's by the canful, 5H3KJ and 9N1MM. Roy reckons that one of the most consistent signals is ZL2ANF, who he works regularly on a sked contact. As for the strongest signal, this prize goes to ZL2BE, who is probably firing at U.K. with one of his rhombics.

G3TLX with his DX-40U is now active on the HF bands. All W call areas, VE, YV, PY, LU, JA, and VK/ZL were worked on 14 mc, while a burst on 21 mc brought back CM1AR, and an assortment of W and VE signals, nothing being done as yet on Ten.

G3TNO has TVI severely on 14/21 mc, as he is in a Ch.1 super-fringe area, although by running QRP and paying extreme care to matching and feeder balancing it is possible to get on Twenty; as for Ten, Malcolm has had the idea of

Reporting the HF Bands

using a "ZL Special" firing at right-angles to the two-metre beam supported on the structure of the Skybeam. By making the ZL Special a bit "inverted-Vee-ish" it fits nicely across the ten-element VHF array.

The Tabular Matter

This is the time of year when we make the changes to bring things up to date. Next month will be the first time out for G3V-- and G3W-- calls to go into competition, and for the G3U-- calls to drop out of this particular table. Thus this month is the last time for the Table to be shown in its present form. The other Top Band ladder will remain as at present, for the time being, anyway.

Turning to the HF Bands, the "New Cycle" Five-Bander will be replaced by a similar, but "All-time Post-War," one, the order of precedence being varied from month to month against a score on a specified band, or total countries worked. As far as the Zones Table is concerned, it is proposed to run a ladder showing total number of prefixes worked and number of Zones scored, starting from January 1, 1968, over all *six* HF bands. Just total up the prefixes for all bands—each one counting only once, of course (no matter how many bands it is worked on) and do the same with the Zones, so that your entry next month would just read, for instance, "G3ZZZ 100 prefixes, 10 Zones" and keep it topped up each month. This one will be of additional interest to the readers of the "SWL" feature in that they will be able to check the rate of working 'em against their rate of hearing, as shown in their own HPX Table.

Here and There

By way of G3SRZ, we are advised that the address for QSL cards for

KG6FAE or WAØKKR/KG6 is either: CMR Box 53, APO San Francisco, California, 96334, U.S.A., or D. L. Haasager, RFD No. 3, Beresford, South Dakota, 57004, U.S.A.

G3PLQ/MM writes in to quote his new address, which will appear in due course in the "New QTH" column; here it is of interest to notice that G3PLQ/MM has now been allocated to John personally, rather than to the combination of John-plus-ship, which was the earlier procedure. This means that G3PLQ/MM does not have to go through the whole rigmarole each time he has a change of ship, providing the GPO inspector passes the station each time a change of ship occurs.

Still on the tack of addresses, but in a slightly different context, we hear from GI6TK that all claims for the W.A.G.I. award should be forwarded to Frank Robb, GI6TK, 125 Downshire Road, Holywood, Co. Down, Northern Ireland.

Reverting back to that preamble last month, when the question of shack heating was touched upon, G3VLX takes up the whole question on the argument that turning the heat off when the place is not in use lets the condensation bug loose in the place; but, although this is a fair comment, what your scribe was driving at when he mentioned G3JLA's method was merely the preservation of the gear itself. Deryck attacks things—probably better—by lining his shack with a layer, 1½ inches thick, of expanded polystyrene, insulating it to such a degree that a mere 100 watts left permanently on would be sufficient to keep the temperature as high as 50°F. It will be interesting indeed to see how the G3VLX plot, which should be working by the time this is in print, makes out.

G3MOJ, G8AFH, and G3VPS betook themselves to the Welsh Mountains for the CQ WW Contest (*Brrrr!*), and had a whale of a time.

We understand from G3VPS that all three survived the weather, but on his return he was so cold that he forgot to tell us how they got on!

All being well, March 1968, should see G3RFH posted from his present ship, which at the moment is in a far sunnier clime than the U.K., and he hopes that his new location will not be too far from Sunny Somerset so that he will be able to fire up the Viceroy (and let the local TV owners know he is back!).

G3WET (Sutton Coldfield), the chap who, not so long ago, worked W2DRY, recently had successive QSO's with HBØLL and HV3SJ at 59's. The point of interest here is in the fact that these two prefixes muster a total of—we believe—four amateurs, and, more to the point possibly, they were worked, using the KW2000A, on a trap dipole just nine feet in the air. As a result, G3WET is now thinking of coiling up the 8KW aerial and burying it. However, in order to work the same sort of DX, it would seem likely he would have to go over to CW!

The Late Mail

Thanks to the vagaries of the mail at this time of the year, generating a bonanza for the Christmas-card printers while slowing down everything else, several letters came in too late to be embodied in the text, and so we just mention them here.

A catastrophe in the power department resulted from G3UXP (Birmingham) trying to tune for maximum smoke—he got it! However, it is to be hoped that a repair can be effected to get Ron back on by the time this is printed.

The other late bird was GM3SVK (Unst), who wrote on December 4 with a long and most interesting final report from Shetland before packing up traps and returning to the South. Anyone still lacking a card for his Shetland QSO with Fred may write direct to G3SVK, 144 Chandos Road, London, E.15.



“... Tonight we are going to hear what conditions are like in VP8...”

He ended up with a score of 207 All-Time from Unst, and 201 in 1967, which indicates how much the interest in Amateur Radio helped in keeping him amused during his tour in Unst. As a final note GM3SVK would wish his thanks to be passed on to all the SWL's who sent him reports, to the stations he worked and made friends with, and particularly to GM3KLA, who not only spurred him on but also helped in keeping him on the air when the gales demolished his aerial farm.

Contests—Pro and Cons

In his letter this month, G3IDG (Basingstoke) points out that while Contests may be regarded by some as a nuisance there is no doubt that, given that one has a reasonable interest in the odd new country, one can find them more easily in the contests. Allan cites the *CQ WW* affair, in which he was on for only a short period, but came out with three new prefixes, a new country and two new stations towards the fourth sticker on his “Tops Century Certificate.” On the other side of the coin, Allan is surprised at the number of stations on in contests

who seem always to give reports of 599—is it true, or is it just easier to send 5NN? Skimming round the band during these battles it is very noticeable that it is usually the weaker brethren who go to the trouble of sending varied reports. Certain it is that the report of “four and one” mentioned in last month's piece is more credible than 59 from a DX station, even if it is perhaps going too far in the opposite direction!

Sign-Out

And there you have the story for this month. Before we give the deadline for next time, it is for your E.P.E. to thank all the many correspondents for their support in the past twelve months, and also specially to thank all those, too many to answer individually, who have sent their Christmas and New Year Greetings. Let us hope the New Year brings more fun, more DX, and, from us, all you wish yourselves in the Coming Year.

The deadline for the next issue is first post on **Monday, January 8**, addressed “CDXN,” *SHORT WAVE MAGAZINE*, BUCKINGHAM. Till then, 73 es bcnu.

• • • SWL • • •

SHORT WAVE LISTENER
FEATURE

MORE ABOUT THE R.A.E.—TALK ON TECHNICALITIES — COMMENTS OF GENERAL INTEREST—DX ON THE TV CHANNELS—ON CONTESTS, SLP's AND THE HPX LADDER

By Justin Cooper

THOSE first paragraphs about the R.A.E. in the last "SWL" raised the odd comment in the mail this time; and in particular from *A. P. Ashton (Stowmarket)*. Writing a farewell letter, now that he has become G3XAP—what a wonderful way to start the New Year—Phil says that it has all been hard work. The reason for it being hard work is fairly obvious—to judge from his handwriting, Phil is, as our American friends would have it, no chicken—and he has had to do the lot, both R.A.E. and Morse, unaided, which has made the call all the more valued now he has got it. As he says, it is hardly an unfair requirement to be asked to prove one's interest by passing a stipulated test. In any case, the question of fairness hardly comes into it, as the rules and regulations are laid down and one has the choice of either obeying them or not getting a ticket.

The other side of the coin comes, by implication if not directly, from *W. L. Rees (Llandudno)*, who regards himself as a non-practical type, and, indeed has been struggling unsuccessfully with the recipe for the "Justin Cooper Five-Minute ATU" for some time now, just to prove the truth of his statement—fair enough, but that does not mean, as Bill believes, that he cannot pass the R.A.E. Far from it, as a glance inside the Development Lab. where your J.C. does his daily stint will show any time that there are many ideas that come to nought for each one that is good. Indeed, in the case of an SWL who has little or no connection with the practical side, it is mainly from one's failures that theory is wedded eventually to practice.

A certain licensed amateur of the writer's acquaintance who took up Amateur Radio in his late fifties had all his life been connected with the business of bricks and mortar; after passing the R.A.E. and Morse (at no small sacrifice of midnight oil) during the following year set to work to build his first Tx. Mark One was a birdsnest to end 'em all, but with help, it was persuaded to put out a decent signal—and then, *but not before*, George set-to and made Mark Two to the same circuit, which went almost at the first puff. Mark Three was a "Princess" which was duly modified in the course of time to the SSB version; and Mark Four was the linear to end all linears, which he designed himself and built from scratch with enough confidence to order the front panel cut and engraved to his requirements. Each one has provided more wisdom, and each one has

proved the wisdom of his thinking out and understanding why things went wrong and what had to be done to put them right.

The New Year's resolution that ends the sermon is quite simple: Even if you don't think you have a chance, have a go—and if you fail first time, sit back and think a bit at each stage in the next course, to see where understanding was lost the previous time—it'll be twice as much fun when you do get on the air!

Technical Topics

Again a hark-back to the November "SWL" in which we discussed the use of an ordinary transformer with centre-tapped secondary, say 250-0-250 volts, in conjunction with a bridge rectifier to obtain 500 volts. *P. T. A. Watson (Horley)* points out that the fact of the peak voltage between either end of the winding and frame being able to rise as high as 706 volts (or twice the value when used normally) may mean that the transformer insulation, on a cheap-and-cheerful specimen, could give up even though from the VA point of view the thing is able to do the job. A fair comment, and one that was not emphasised enough last month. One can go further, and point out that the peak-inverse-voltage rating of the rectifier in this application is not unimportant; the figure of 1.57 times the DC volts quoted "in the book" does not make adequate allowance for variations of mains voltage at times, and the use of a pair in series in each leg of the bridge, each rated at 800 volts p.i.v. is far from pointless, to allow for the occasional surge. All this indicates that Peter is quite a knowledgeable type—and so he is, as he is putting off taking the R.A.E. until he has made his way through his IEE exams. When he has done so, he will be that rare bird in the Electronics industry—the chap who knows how to do it in practice and why it can't work in theory! Strange how these two attributes so rarely appear in the same individual, and how much it costs the industry each year—but that is another story on which we could expound for too long!

Arising from the recent activities with the value of the pound—cash, not weight—*G. T. Theasby (Keighley)* asks why so many amateurs buy a rig of American origin when there are perfectly good equipments of British origin on the market. This is a difficult one to answer, but probably stems from

Gordon Allis, of 117 Chessington Road, West Ewell, Surrey, is by calling a TV service engineer. He has been interested in Amateur Radio for the last three years, during which he has steadily built up a very nice Rx station. He now has an AR88D, a Geloso 209R and various home-built items. His antennae consist of a multi-band vertical dipole and a Quad. With a Countries score of 227 in 39 Zones confirmed, Gordon is now setting about getting his ticket.



unusual area—rather like logging a G9, in fact!

Since his last entry, *J. Edwards (Penge)* has managed to acquire an SX-24 receiver. This one was one of the line of communications receivers made by Hallicrafters in prewar years which culminated in the SX-28. The "X" in the model number indicated the presence of a crystal gate. Reader Edwards is also compiling a list for the CW table, which he hopes to enter next time out.

D. Sapsworth (East Ham) is quite elated at having found all forty Zones, the last one to be booked in being in the form of a VS6 in Hong Kong. This, and 24 other prefixes added to his total, mainly arose from the activity on 28 mc.

HPX is having to take a back seat at the QTH of *I. Cooper (Alnwick)* who is dividing his time between examination studies and R.A.E. with a little Morse thrown in.

GB5QM/MM has been somewhat elusive, to say the least; in fact at the time of writing no hard news of either hearings or contacts have come to hand, in spite of band openings in the desired directions. *D. Rollitt (Navenby)* has been trying hard in other directions, and the TA33 beam has helped in these also, the prefix total taking a large upward leap by 54 to 850.

First entry for the HPX table from *R. Geary (Leicester)* who uses a R.1475 receiver with sundry outboard bits, to a long-wire fed through a 19 Set variometer; however, he is handicapped by the presence nearby of a mains sub-station, which generates a fair amount of noise. SWL Geary queries the status of 4L7A, which was a special callsign from Russia; 4M5A (on for their contest from YV-land), and finally a "5K4RCA," which your conductor suspects to be a misreading of something else.

TV/DX News

On this front, we have a long letter from *F. Smales (Pontefract)* who while laid up has been putting some good work in on the test cards, particularly during that admirable opening over the middle of November. UHF was "forthcoming" on November 18, which started off with a colour test-card from Lille and for the next five hours several French and Dutch stations were solid copy. After going with Bruce Thomas to Ripon, where they met Denis Boniface, Frank came home and was able to resolve Tele-Luxembourg on 819 lines, always a difficult one due to QRM from the 625-line transmission from Markelo on the same E7 channel. Frank seems to be home-bound for quite a spell yet, and is planning to use the time to get his Bush TV receivers up to scratch, and also to modify one of them to give a complete 625 vision-plus-FM sound strip with tuners switched for all bands. Incidentally, on that evening of November 18, Frank logged signals from no less than nineteen different stations (other than the local channels) all but five being UHF outlets.

Bruce Thomas (Castleford), in addition to meeting Frank and Dennis, has been pushing away at the HPX, although at a slower rate than previously, due to the interfering influences of work and TV/DX; his total has gone up to sixteen countries seen on TV channels, and it is hoped to put it higher still when a new mast goes up *chez* Thomas in a few months' time.

A good reason for being off the air for anyone is being Hon. Sec. of a Club—this fate has befallen *J. A. Ennis (Saltash)*, who is probably finding the seat hotter even than his worst fears. Your old scribe *knows*—he's had some!

Quite a long band report from *D. Henry (North*

Berwick) who has recently had the pleasure of obtaining a CR-70A receiver. This has been used to some effect on most of the bands; Eighty has produced W's in the morning and VS6 in the late evening, the latter being the cause of the first pile-up SWL Henry has heard on 80m. For the rest, Ten has been good during the daylight hours, the mornings particularly, with Fifteen in a similar state. Twenty, as is to be expected this time of year, has been pretty dead in the evening hours, except for the odd opening to PY and occasional ZS's, CR6 and so on.

An echo to that discussion about gear and the operators behind it comes from *M. Watson (Williton, Som.)*, who recently had the use of a NCX-5 and TA33 beam on which to listen. In spite of what Malcolm describes as "this fantastic piece of equipment" he was bitterly disappointed at the poor total he was able to show. However, as he so rightly says, this proves the point that it is the operator that matters, and he himself has gained a lot of know-how in the process. As a side-issue, Malcolm has a few things to say about small—seventy-five milliwatt—transistor transmitters on Top Band, which he claims to have a range of a few yards. Seems only a few weeks ago that various people were reporting 589 signals from OL4AFI all over the U.K. when Jarda was running a similar power level on the same band—and it's not so many years since your aged J.C. had ears capable of making a one-watt WAC on Forty, admittedly as a result of more than a little burning of the candle at both ends and the middle!

John Dutton (Ilkeston) has been spending less time at the controls of his receiver due to the needs of his A-Level syllabus, although quite a few of the missing "uncommon EU" type of prefixes have been winkled out to swell the total.

A good way of gaining new prefixes, or countries for that matter, is to come on during the Contests. *E. Parker (Hove)* did just that, and by sitting through the entire 36 hours of the recent 21/28 mc event profited handsomely. Ernie took his part in the 7 mc shindig as well, and contrasts the behaviour of the U.S. amateurs in the 21/28 mc band queueing up to give the boys a point, while the G's on Forty were most reluctant to swap numbers, so that the going became very heavy, and things seemed virtually wrapped-up three or four hours before the end for lack of stations to work. This is one of the interesting things about the 40m. band, and it seems that those who are quite content to work the same round of EU stations stay on Forty and almost resent the presence of DX. A few evenings ago, J.C. tucked his beard inside his jacket, put on the cans, and listened round the band, about 2130z, and was amazed to find KG6 at 579 and a 559 signal from 4Z4 calling CQ and finding no takers—both as near in the clear as they could ever be on Forty, and certainly 100 per cent readable CW signals on his Eddystone 888. Eventually both got a contact, but nothing remotely like a string of them resulted.

The PCR-3 receiver used by H. N. Plumridge

(*Bishopstoke*) has now been fitted with a BFO, and so can resolve SSB signals, although we gather it can only be done on 14 mc and then with difficulty. It rather sounds as though the BFO is not being set correctly, as stations below 10 mc use lower sideband and those above 10 mc—such as Twenty, for instance—use the upper sideband. K. Plumridge writes from the same address to say that he has added another thirty feet to the aerial and feels it is giving a slight improvement.

K. Jeeves (Huddersfield) had his finger crossed at the time he wrote his letter—uncomfortable?—as he was waiting the result of the December R.A.E. On the question of QSL returns, Keith says that he sends a good report, encloses an IRC, and covers it by a clearly-typed letter on headed notepaper—and has a return to date of around 75%.

Nice to hear again from *B. Macklin*, who is now in digs at *Farnborough*, and spending most of his spare time studying. The old CR-100 has been pensioned off and Barry has only his transistor set to play with—but an HA-500 is "in the pipeline" and will soon be set to useful work with the CW, which is now the only obstacle to a licence, R.A.E. having been passed last May.

Controversial?

From *D. Whitaker (Harrogate)* comes a plea that we should run a new HPX Table starting from January 1st, and also an SWL contest. Taking the first point, one feels this is somewhat unfair to the present leaders, who, if they took part in any such a ladder, would almost certainly go straight to the top again, but at a lower score. As for the second, while SWL contests are mildly popular, the logs are far from being self-checking—as the transmitting events are automatically, to a great degree, in that the contestants mainly work each other. Thus it means not only that an SWL contest needs quite a lot of organising, but also a fair number of invigilators on the band if any sort of fair check is to be made on logs sent in. No, the Set Listening Period is far more attractive—and we must see about another one!

Another graduate from the SWL ranks is *A. P. Legg (Sutton, Surrey)*, who now has G8BCS, and operates the Club station G3UCL on occasions; we rather gather that progress is being made in the general direction of a G3-plus-3 call. Meanwhile, Anthony has a SR-600 on the HF bands and an Eddystone EC-10 for the lower ones, which have netted him an HPX total so far of 474.

Up 50 in the Table is *M. A. Lount (Leicester)*, who, apart from having various troubles with the receiver, which were fairly easily cured, has been under the weather himself, and so has had to type rather than write his letter, and that with one hand—we can imagine the language!

In spite of pressure of work, *S. Foster (Lincoln)* found time for the odd hour or two on the bands, and as a result Stewart manages to rise a little further in the lists, with a new total of 914. *Stuart Swain (Hayling Island)* refers to the 5LA2 and 5LA8 prefixes, and points out that they were Liberian

Field Day stations—a fact that your scribe knew but completely failed to remember. *Mea culpa!*

Last time out the score in the Table was not up-to-date—but after all, if you don't send it in, we cannot claim any reliable results by telepathy! Seriously, though, the complaint of *A. Hydes (Enfield)* resulted from the non-enclosure of his list, as a glance at the file here showed! The majority of "misses" are, in fact, *because they miss the deadline*—but the Editor expects to have this piece ready for getting into the *Magazine* on time. What it all boils down to is that your J.C. has just one week, less postal delays each way, to write the script if we are to come out on time—and *SHORT WAVE MAGAZINE* is *never* late out of our hands. Getting back to Alan, he mentions that he has tacked a Codar PR-30X preselector on the front of his receiver, to the good of his score. However, it should always be borne in mind that the extra gain may result in increased cross-modulation, and so more care is needed in keeping the "front-end" gain as low as can be.

A 19 Set was recently acquired by *I. Poole (Leeds)* which came in handy when the rectifier in the converter went west—he was able to take the one out of the CR-45 and get back on the air by using the converter ahead of the 19 Set. Improvements have been made in the shack, and some early morning listening tried on Eighty, which yielded W's and ZL's at good strength.

Quite a large rise in the score is recorded by *J. P. Scragg (Stockport)*, who nevertheless failed to make his target of 500-up, because the receiver decided to go on the blink, at an inopportune moment. However, it is well said that it is better to travel hopefully than to arrive, and no doubt the next entry will turn the trick.

While cutting wood *J. Singleton (Hull)* managed to investigate the sharp part of the saw too closely; the piece has been stuck back on, and John hopes to see it again by the time this gets into print, although it may take longer before he has it as new! Very nasty. John has a few pertinent comments on the question of passing the R.A.E., and feels that a lot of the protestations are the result of an attempt to save face at the Club—or with one's self—rather than admit one was not adequately prepared! A good point, this.

Using an RA-1 built by father GC3WDX, *R. Allisett (Guernsey)* has been putting in about 24 hours listening each week; the combination of ability to listen to the HF bands with time spent has resulted in a thumping rise in Dick's score, from 226 to 406 in a couple of weeks.

A newcomer to this piece is *P. L. Spindler (Ilford)*, who is of but 13½ years and seems to have been severely bitten by this Amateur Radio business. Paul is able to put in a first entry in the Table, thanks to a spot of hard listening on the SR-150 to make the last few up. In addition, he is up to the point of 10 w.p.m. on CW, and pressing on to try to get over the hump.

Where have all the GM SWL's gone, wonders *D. Douglas (Dundee)*, who now has broken the

"150 countries confirmed" barrier. David has a gripe about a number of amateur stations who receive cards direct, including IRC's or return postage, but neither stump up with the card nor even a reply stating it is not the policy to QSL (using the postage sent).

That comment by G3WUD about "not being an SWL any longer" was bound to make someone rise to the bait—and it is none other than Allan, G3IDG, who points out that the licensed type is *more* of an SWL than the SWL, in that most HPX hunters tend to identify the call and then pass on to pastures new, while the transmitting amateur in QSO has to get the whole contact from end to end. This being so, the licensed listener will always tend to be more careful in his scanning of the band, so as to sort out for himself the stations calling in whom he is interested — whether for DX value, quality of their fist, signal strength or whatever.

C. P. Davis (Leicester) has dabbled in the SWL hobby for years—he built his first 0-V-1 receiver way back in 1931—but has at last decided to get down to things a bit more seriously. Pete uses a R.1475 which he has realigned and generally done up. Although a crystal-controlled converter for 21/28 mc is completed it has not seen much use yet due to interest being concentrated on Twenty. A query heard on this band is "AC5DC," claiming to be in Zone 22; although there are a couple of AC5's in the call-book this one sounds to be rather Ungood—has anyone any news?

P. D. G. Milloy is now at University, and so finds his operating time rather short, though some good openings on Ten during the year have made it all worth while. Peter is involved with the *University of Manchester ARC* and forecasts a lot of activity from them in the way of DX-peditions.

Finally, to a couple of old-timers—old friend *A. W. Nielsen (Glasgow)* has been with "SWL" almost from the first and has been listening to the *CQ Contest* since 1959. A resumé of his loggings during this Contest over the years is most interesting, bringing out as it does the variation in the sunspot cycle and its effects on DX results. Another interesting point is that although A.W.N. does not listen much during the summer, since January 1st, 1967, he has logged 551 prefixes—which is the same total as he took thirty-three months to collect up to September of 1962. It just goes to show that it is experience that counts! *Charles Harrington (Maidenhead)* spent a lot of time on the same contest, and as a result goes up to 380 from the present QTH, all on a TV array as an aerial. To judge by his card, Charles has been at the SWL game since before the War, and is strictly a CW man, using an HQ-170A receiver.

Deadline

So there you have it. Remains only for your J.C. to wish you each and every one, what you hope for yourself in the coming Year, and to give you the deadline for the next "SWL." This is rather short—first post **January 19, 1968**, addressed to "SWL," *SHORT WAVE MAGAZINE*, BUCKINGHAM. Till then, 73 es DX.

An Eddystone Occasion

Presentation of EA-12 Receiver to Bruce Taylor, GM3NZI

IT will be remembered that early in the year—as announced in the April, 1967, issue of *SHORT WAVE MAGAZINE*—Eddystone Radio Limited offered an Open Essay Competition, under four subject headings to choice, for which the judges were to be Prof. R. Jennison, B.Sc., Ph.D., F.R.A.S., F.Inst.P.; T. P. Douglas, M.B.E. (G3BA); and H. A. Bartlett (G5QA). The point of particular interest here is that 20 years ago the then Roger Jennison, G2AJV, was himself the winner of the Eddystone Competition, his prize being an S.640—which, incidentally, he still possesses, and uses. He is now Director of the Electronics Laboratory, University of Kent, Canterbury, and accepted the firm's invitation to present this year's prize, an Eddystone EA-12, to the winner.


This turned out to be Bruce Taylor, GM3NZI, a 25-year old student at the University of Edinburgh. He chose as his essay subject a new approach to receiver design to meet the stringent requirements of international Amateur Radio as we know them today. He turned in a masterly treatise (later to be published in these pages) on the subject, his basic conception being a main chassis engineered to accept plug-in modules to meet a wide variety of amateur-band operating requirements—from HF to UHF, and in all modes—enabling the receiver always to be in step both with immediate needs and foreseeable development.

The judges agreed unanimously that of all the contributions received, this was the most useful and imaginative. Accordingly, at a very pleasant ceremony at the Hq. of Eddystone Radio Limited, on November 27 last, GM3NZI received his EA-12 (priced at £185 in the current Eddystone list) from Prof. Jennison. In addition to Eddystone senior staff, the judges and press representatives, one of those present was Austin Forsyth, O.B.E. (G6FO), Managing Editor of *SHORT WAVE MAGAZINE*, who had himself been one of the three competition judges when Roger Jennison was awarded the prize 20 years earlier.

In the course of the proceedings, Mr. W. Cooke, chief engineer, Eddystone Radio, discussed the EA-12—an amateur-band Rx of the highest grade—in detail, and also disclosed many of the technical features of the new Eddystone 990R solid-state VHF receiver.

Following the presentation and the hospitality of Eddystone Radio Limited—of which the managing director is Arthur Edwards, G6XJ, and himself a keen CW/DX operator—the party toured the Eddystone Radio works, to see the various production lines and manufacturing departments; the test and development rooms; and the drawing office.

From all of which not only can it be said that GM3NZI is the fortunate possessor of a very fine amateur-band Rx, but also that anyone who “buys Eddystone” invests in first-class equipment, backed by years of know-how (they started in the business about 1926), up-to-the-minute design and engineering, careful pre-sale test and efficient servicing. Had it been otherwise, Eddystone Radio Limited would not be where they are today, with up to 60 per cent of their output going for export.

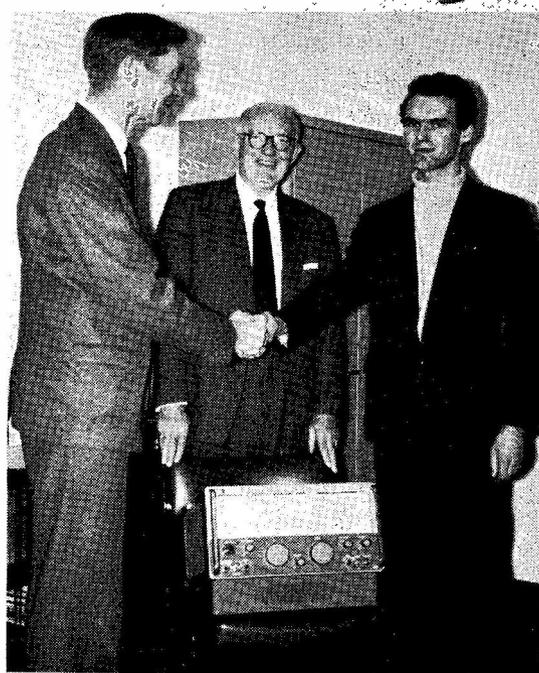

The presentation, on November 27, of the EA-12 receiver to Bruce Taylor, GM3NZI (of Edinburgh University), winner of the Eddystone Essay Competition. On left, Prof. R. Jennison, with GM3NZI on the right. At centre is Arthur Edwards, G6XJ, managing director of Eddystone Radio, Ltd., and himself a confirmed CW/DX operator on the HF bands. In the foreground is the prize, an Eddystone EA-12 receiver, which is one of the more ideal types for amateur-band reception.



A general view inside the Birmingham works of Eddystone Radio Limited. Prof. Jennison is examining the chassis of one of the new Eddystone receivers, with Mr. Cooke, chief engineer of Eddystone Radio, on his immediate right. At left is GM3NZI, who was probably quite surprised to find out not only what is involved in the design, manufacture and pre-sale testing of his EA-12 (see story) but also that something like 60 per cent of Eddystone's receiver output—covering the whole range of specialised design for the marine, commercial communication, Service and amateur requirement—goes for export. The firm of Eddystone Radio, Ltd., has been in the short-wave receiver manufacturing business for the best part of 40 years.

“IT'S AN ILL WIND . . .”

To quote from a recent letter: “Whoever said it's an ill wind that blows nobody any good certainly knew what he was talking about. Having recently been laid up for four months, I was persuaded by amateur friends to learn Morse—which I did. I took and passed the Test a short time ago and am now the proud possessor of my call sign and can join the rest on the New QTH page.” (C. F. Withall, G3XBW, 8 Sumpter Pathway, Hoole, Chester.)

“QUEEN MARY,” W6PMO, LONG BEACH, CALIFORNIA

If you hear, or can work, W6PMO any time from now on, it will be the Long Beach Amateur Radio Club station aboard the ship we used to know as R.M.S. *Queen Mary*. In spite of all the ballyhoo, like many another great ship of bygone years, eventually she will rot at her moorings. Too big to keep clean and too expensive to maintain below the water-line, the mayor

of Long Beach will come to wish that his municipality had never taken on the commitment. The awful thought is that ex-GB5QM/MM will be pointed out to sightseers as another of Britain's white elephants. Who wants a ship that can never again sail out under her own power.

USAFE/UK BID SALE, R.A.F. MOLESWORTH

With reference to the notes on p.569, November, and p.372, August, we are now informed by the U.S. authorities that the next bid sale for American surplus radio and electronic equipment has been fixed for Tuesday, January 16, at R.A.F. Molesworth, Huntingdon. The surplus being offered is valued at something like *three million dollars*, all subject to bid and covering a very wide range of radio-electronic apparatus. Apply for Sale Catalogue to: Sales Support Section, USAFE/UK Redistribution & Marketing Centre, R.A.F. Station, Molesworth, Huntingdon. (Tel. *Bythorn 371*.) And whatever you buy, make sure you get the handbook that should go with it.



THE OTHER MAN'S STATION

G3WYS

SOME 18 months ago, members of the Silverthorn Radio Club found a 12-year old radio enthusiast awaiting their arrival on a meeting night. He was allowed to remain and, with some misgivings because of his age, was a little later admitted to full membership.

Philip Routledge (36 Oak Hill Close, Woodford Green, Essex) amply proved that the principle of "catching them young" paid dividends. Not without some opposition from the Local Authority, he was accepted into the forthcoming R.A.E. class, together with others under age, largely as an experiment. His instructor's faith was fully justified, and starting from the bottom rung of the ladder, he passed the Exam. first time. And before the R.A.E. results were out, he also took and passed the Morse Test and so had the frustrating wait until his 14th birthday.

As a concession, the Post Office allowed him his Amateur Radio certificate, thus enabling operation under supervision. At last *the* day arrived with the call G3WYS, *plus* a birthday card from the Post Office—a very nice touch!

Time spent in studying, and experience on the air, inevitably limited construction, and although a CR-100

was acquired, the transmitter was not ready. Philip's *début* on Top Band was therefore made with an A.T.5 loaned by a local amateur. His own transmitter is now well under way, and should be air-borne before long.

A refreshing feature of Philip's approach to Amateur Radio is his love of the key—all too often neglected nowadays—and 20-30 w.p.m. holds no terrors for him. The writer feels rather humble when he hears G3WYS paddling a bug with all the aplomb in the world! The station is housed in a garage, and although aerial size is limited by a small garden, a potent signal is put out.

In the photograph, the A.T.5 is shown on top of the CR-100. On the left there is a home-built HF rig, covering 10-80m., CW and 'Phone, running around 50 watts. On these bands the CR-100 and R.208, also on the bench, are linked for double conversion. Under the CR-100 can be seen the Top Band transmitter nearing completion. The associated modulator, on top of the HF-band rig, was built when Philip was 12, and worked first time when tested by a near-by amateur. The future of Amateur Radio is bright indeed when one so young makes such a promising start.

G2HR

THE TWENTY-SECOND MCC

The Magazine Top-Band Club Contest November 11-12, 1967

WITH an actual entry of 94 logs—one more than last time—this year's MCC has demonstrated how resistant the average amateur is to change; in 1964 everyone said the new Rules were "impossible," but in 1967 only one Club even commented on them. Perhaps this was partly due to the extra effort expended this year, because of the rather poor band conditions on both sessions, which, of course, progressively increased its effects on the scoring, right down the Table.

Thus, we find the winner this year, **Burslem**, made 641 points, almost the lowest winning score since the present Rules came into force—so for them to raise their total of last year by nearly 100 points is a fine effort, on which they are to be congratulated. Runners-up **Moray Firth** "A" made 598 this year as against the 675 which took them to third place in 1966. Third slot this time goes to last year's winners, **Kirkcaldy**, who managed 530 points for 1967. At the other end of the Table, a similar trend is noticeable, the wooden spoon going to a score of 46, as against 98 in 1966.

What it all adds up to is just that the band was somewhat down as compared with last year, which is rather as one would have expected—but the 127 Clubs who played, and the non-Club stations who came on to give a point, still enjoyed themselves immensely.

It is, of course, much to be regretted that no less than 33 of the known participants failed to put in logs—some at least would have found themselves in a good position in the Final Table had they done so! But this particular phenomenon is with us every year.

MCC has always had a "training" aspect, in that many groups like the idea of using it as a means of teaching the newer members the tricks of contest working, while the experts either stand behind and criticise, or go away and demonstrate how they do things from another site. To this end, it behoves us to make sure that it is not only a pleasant entertainment but also a little more difficult than usual. And so we changed the coding system—which also made it easier to check the logs—and required the QTH of the Non-Club stations to be recorded. Seems this was a little difficult . . . G3BMY was noted as being at Craven, Craven Arms, Cradley, Chester and Crewe in various logs . . . Otley were sending, quite correctly, 001, but half the stations he worked were foxed by his code and only claimed one point for him! . . . No. 235 Squadron, ATC had 702 for a code, and *ninety per cent* of their contacts could not get it first time of trying—quite a lot required it *spelling out* to them!

Naturally, as a result of all this, most of the claimed scores have taken a beating in one direction or another, as the Table shows. Apart from one competitor near the top, everyone did their arithmetic in accordance with

the rules, and the standard of presentation of some of them was a delight, although far fewer than usual were typed. One in particular (a first entry in this or any contest) by Hemel Hempstead, was a model of all it should be. There were, thank heaven, no really bad ones this year.

Gear Used

On the equipment side, the winners, **Burslem**, used a KW-2000 for transmitting, and a Drake R4A receiver, together with a half-wave dipole at 70ft. firing North/South and an end-fed half-wave at the same height covering East/West, used in conjunction with an ATU. The runner-up, **Moray Firth**, gave no details of their equipment, but the third-placed group, **Kirkcaldy**, used an Eddystone 750 and a Geloso/5763 PA into a dipole at 40ft.; their change-over system went on the blink for half-an-hour on the Saturday, which may have been enough to deny them second place. Among the rest, transceivers were prominent, along with a lot of homebrew rigs, Codar A.T.5's and a few Vespas and Cannonballs. Receiving was sometimes done on the transceivers, but quite a number of these were used in conjunction with other receivers; **Kings Norton** had a brace of Project 66 transceivers cross-coupled so that both were listening together, both were muted when transmitting, and either could be radiating. The Drake R4A already mentioned was only one of many types, from an old Hammarlund SP-200, through several varieties of HRO, AR88's, a Sommerkamp used in conjunction with a transverter, Heathkit RA-1's, BC-348, to a Racal RA-17—the latter with a Top Band preselector in front!

The invigilation of the whole affair is done each year by several experienced operators, each with blue pencil at the alert. This year there was, as always, the admirable



check log from SWL D. Law (Leicester) and also check logs from G3UKC, the University of Kent group in Canterbury, and G3REI (Reigate "A"), who were aware they had poor signal quality, particularly on the Sunday evening, and so sportingly closed down early.

By and large, the netting was pretty good this year, although there were one or two who seemed consistently to be listening on the "wrong side of the crystal." Usually, the trouble with Morse is in the receiving of it—but there was one station, fairly well up the list, who, to judge from his logging, *receives* far better than he sends—a couple of S-points of extra outgoing signal punch is no good for radiating "Martian Morse!" One or two others lost their grip on the paddle of the bugkey at times, with strange results in the logs. Calling was, at times of stress, a little overdone, as when two stations called CQ on top of each other for three minutes, and then proceeded to a QSO well larded with "BK" during which each gave t'other a 599 report.

Some Comments

"The multiplier greatly overestimates our difficulty of scoring (*no* quotes or locals and colleagues will lynch me!)" . . . "Hoping for some further addition to the traffic to be sent from one station to another—how about the frequency of this last contact together with the registration letters of his car?" (*Kings Norton*) . . . "The only side-effect was hearing CQ MCC at 30 w.p.m. during sleep on Sunday night" (*Wakefield*) . . . "Roll on next November" (*Manchester University*) . . . "CW operating procedure was shocking—many stations could not receive at 20 w.p.m., which one would think to be the minimum requirement for a contest" (*Nottingham*) . . . "And so—back to the drawing-board once more!" (*South Manchester*) . . . "Our first attempt at Top Band contests; aerial was a half-wave dipole at 200ft. which gave good results" (*University College of North Wales, Bangor*) . . . "Why, oh why, must some people not only key with their left foot, but also be proud of it?"

(*Marconi Apprentices*) . . . "Thank you for organising a most enjoyable contest" (*Henley-in-Arden*) . . . "A1 signals with 6 kc bandwidths" (*Lowland Royal Signals*) . . . "Scoring rate drastically reduced this year by heavy QRN—from a local power station?—so we apologise to those we did not work" (*R.A.F. Sealand*) . . . "One station caused serious blocking—either a wizard aerial or an 813" (*Southgate*) . . . "Site ten feet a.s.l., fifty yards from a creek, and surrounded on three sides by hills" (*Isle of Wight*) . . . "The new ident. codes were very successful" (*Chester*) . . . "We like the code system" (*Mid-Herts*) . . . "Showers of dots without a home now and again—very FB! . . . Least said, soonest mended!" (*Ampfield*) . . . "We heard quite a few going at Mach 2!" (*Ballymena*) . . . "It would neither load, match, nor radiate" (*Maidenhead*) . . . "Only trouble was the ident. system!" (*South Birmingham*) . . . "Don't go much on scoring system" (*Grimsby*).

Technical Points

In previous years *Verulam* have used the same site, and the same aerial—this year they make no mention of their tradition of hauling the earth-plate out of the moat for the annual MCC burnishing—and they are a hundred points down. Just proves tradition is useful!

Chesham, for once, had no bothers with the gear, which was an all-band all-transistor job built by G3HBW, using *three* frequency synthesizers, and an overlay transistor in the PA; on the aerial side, they had a pair of half-wave inverted-Vees, with the centres held up to 110 feet, at right angles to one another. The point of interest here is that these antennae were fed in the balanced mode by using, on each aerial, a pair of cables with the sheath commoned, as a screened twin-balanced feeder, which *must* have done something for the noise-level.

Another G3HBW transceiver design was in use by the *Harrow* crowd; this one has a pair of BUY11 transistors in the PA and, apart from the usual facilities, had a bandwidth variable from 6 kc down to one cycle (!).

Making a first entry in MCC, the I.o.M. group signing GD3TNS worked themselves into 39th place. Here we see, on the key, GD3FXN (right) with GD3EGF, and standing (left) GD3HQR (who did that little cartoon on p.705), with GD3TNS. They ran a KW-2000, with a KW Ezee Match and an HA-350 Rx, the aerial being a half-wave.





The winners of the 22nd MCC, with their winning smiles—Burslem Amateur Radio Society, G3VNR, who sailed away from the GM's to bring First Place back into the Midlands—see graph p.712. On the key, G4OD with his son G3VNR logging. Left to right, standing, are G8IX, G3SAJ, G3COY, G3USF and SWL Wild (hon. secretary, Burslem A.R.S.). The gear they used was a KW-2000, a Drake R4A receiver and an electronic keyer, with choice of two good aerials—an east-west dipole and a 300ft. wire at an offset angle, both at a height of 70ft. Throughout the Contest, G3VNR was an outstanding signal and very well operated.

This, according to the Harrow operators, was the last word and their only other problem was cross-modulation. To cure this, someone thought of a 6 dB pad in the aerial feeder on "receive"—but then the receiver front end took off. They put in a cracking score. Incidentally, they got a T8 report or two on the Sunday, which puzzled them a bit, as locals said the note was quite OK and T9x.

This resurgence of home-brewing, in the sense that there were several other transceivers and receivers, as well as the usual run of transmitters is, of course, gratifying to the old-timer, but is nonetheless rather puzzling. One possible explanation could be that many operators are finding how useful real BK is from personal experience on a transceiver, and are then setting to work to make one without the shortcomings of some of the commercial devices.

Among the Non-Club stations, there were several who seem to have a connection running out over many years with MCC. G2YS, who appeared in one or two logs, is the only call to have been noted as winner of

MCC from two different places—Coventry and Chester—while G3BMY took Stourbridge to the heights on several occasions—see graph. Two mobiles were worked by Clubs, one of whom was suspected of keying with his change-over switch! Other personal stations which appeared in various logs were G3TLX, GW3FSP (a winner in earlier years), GM3SVK, G3RSO, G3SWM, G6HD, OK2BJJ, PA0PN and G2MJ.

Time and Frequency

Dealing with last things first, quite a few of the entrants still had not adjusted the old alarm-clock (borrowed from Auntie) which we complained of last year. Nonetheless, between them, the invigilators made a note of most of the optimists, and points were docked if the QSO started after the closure—but we really will have to think up a stiffer penalty for the stations calling "CQ MCC" several minutes before and after time.

On a slightly different aspect of the *Time* question, one or two stations have called for a reduction in hours compensated for by a later start and a third session on

Sunday morning. This is a little difficult to comment on, but there seem to be two things to take into account: In the first one there is the undoubted fact that a Top Band contest on a Sunday morning would probably not be popular with the usual inhabitants of the band at that time—and they have a right to enjoy it without too many contests to ruffle things up. The second is that it would be very difficult to retain a balance which would give the GM's, for example, a sporting chance. The present sessions are chosen so that a Southern station can collect a hatful of contacts, while not giving the lads with the big multipliers too much scope for high scoring.

Another factor as regards timing of the sessions is that many Clubs who use their own Hq. station already have enough trouble in getting their premises opened for weekend use.

On the point of *Frequency*, all we or anyone else (who monitored the event) can say is that there was a lot of wasted space due to the main concentrations of activity being between about 1805 and 1865 kc. Instead of attempting to spread out, most operators simple piled in where the activity seemed highest, thereby merely increasing the congestion. A thoughtful few tried to attract activity up to 1900 kc, but found no takers.

But here again, it is what happens every year, and why there are Club signals that are simply never heard in some parts of the country! Careful analysis of the logs reveals this as a fact.

Looking now at the *Operating*, to anyone monitoring some of it was pretty extraordinary—chaps put on bug keys that obviously were set too fast for them, producing a plethora of dots . . . the numeral "3," occurring in practically every callsign, but so often sent as "SM" . . . the procedure signal BK frequently heard when it was clear the sending operator was not listening through . . . scrappy or indefinite signing-off or acknowledging . . . weakness in dealing with non-Club stations, either because the Club op. had not been briefed, or hadn't read the rules . . . a general tendency for over-fast sending . . . and, at some stations, the marked change in operating efficiency as a new hand took over the key (though this in itself is no bad thing, as it showed that somebody else was getting a turn).

However, in spite of these mild criticisms and strictures, the general standard of operating was pretty high, and from some stations outstandingly good, with clear, steady sending, correct procedure and quick, but not hurried or scrambled, clearing of QSO's. If the invigilators were pressed, they might mention G3VNR,



GM3FXM/A notched up 580 points to make third place for Kirkcaldy Radio Club in the 1967 MCC. Seated, left, GM3PFQ, with GM3FXM on the key. Standing, left to right, SWL's George, Donaldson and Givens, who backed up all through. Their Tx ran 10 watts to a 5763 PA, the receiver was an Eddystone S.750, and the aerial a half-wave.

TABLE I
Positions and Scores, Twenty-Second MCC

PLACE	CLUB	REGION	POINTS	PLACE	CLUB	REGION	POINTS
1	Burslem (G3VNR)	M	641				
2	Moray Firth "A" (GM3KHH)	GM	598	49	Cheshunt (G3TZZ)	S	245
3	Kirkcaldy (GM3FXM/A)	GM	580		Northern Heights (G2SU/A)	N	245
4	Newcastle University (G3OWM)	N	561		Southgate (G3SFG/A)	S	245
5	East Barnet (G3RPB)	S	557	52	Brunel University (G3UBR)	S	244
6	Spenn Valley (G3SVC)	N	552	53	STC, Harlow (G3NIS)	S	241
7	Harrow (G3EFX)	S	524		Stroud (G3SDR)	S	240
8	Kings Norton (G3GVA)	M	523	54	Acton, Brentford & Chiswick (G3IIU)	S	240
9	Wakefield (G3VMW)	N	520	56	Crawley "B" (G3TNO)	S	234
10	Leyland Hundred "A" (G3GGS)	N	504	57	Isle of Wight (G3SKY)	S	232
11	Government Comms. (G3SSO)	S	500	58	Silverthorn (G3SRA)	S	230
12	Surrey (G3SRC)	S	485	59	Nuneaton (G2HAO/A)	M	229
13	Manchester University (G3VUM)	N	482	60	East Cheam (G3OJE)	S	227
14	Nottingham (G3EKW)	M	470	61	Bury St. Edmunds (G3PHW)	M	226
15	Stourbridge (G6OI/A)	M	463	62	Speedbird (G3NAF)	S	223
16	Albright & Wilson (G3OXD)	M	399	63	Southampton University (G3KMI)	S	222
17	South Manchester (G3FVA/A)	N	395	64	Chester (G3GIZ/A)	M	217
18	Hereford (G3HVX/A)	M	387	65	235 Squadron ATC, Stoke (G3IGE/A)	M	213
19	Echelford "A" (G3UES)	S	386	66	Plessey (West Leigh) (G3WLE/A)	S	212
20	Ealing (G3UUP)	S	384		Mid-Herts (G3WGC)	S	204
21	University of N. Wales (GW3UCB)	GW	374	67	Southdown (G3WQK)	S	204
22	Marconi Apprentices (G3JTW)	S	373	69	Clifton (G3GHN)	S	201
23	Chesham (G3MDG/A)	S	372	70	Leyland Hundred "B" (G3VAL)	N	195
25	Painton (G3PHC)	M	372		Chippenham (G3VRE)	S	195
26	Moray Firth "B" (GM3TKV)	GM	356	72	Southampton Group (G3SOU)	S	194
28	Hemel Hempstead (G3WIH/A)	S	356	73	South Shields (G3DDI)	N	192
29	Guildford (G3TLM/A)	S	355	74	Ampfield (G3JFY)	S	166
29	Verulam (G3VER)	S	351	75	Ballymena (G3FFF)	GI	161
30	South Bucks (G3KGV)	S	341	76	Macclesfield (G3MKR)	M	160
31	Crawley (G3WSC)	S	339	77	Addiscombe "A" (G3UFY)	S	159
	Hillingdon (G3PWY)	S	339	78	Echelford (G3SAZ)	S	157
33	Cardiff (GW3SQX)	GW	332	79	Worthing (G3WOR)	S	156
34	Henley-in-Arden (G3SIA)	M	319	80	Nailsworth (G3VVV)	S	150
35	Salop (G3SRT/A)	M	312	81	Mid-Sussex (G3BZO)	S	129
36	Crystal Palace (G3VCP)	S	305	82	Gosport (G3RQK)	S	129
37	Cray Valley (G3RCV)	S	304	83	Bishops Stortford (G3RGA)	S	125
38	Leyland Hundred "C" (G3JMZ)	N	295	84	Brighton Tech. College (G3TCB/A)	S	124
39	Isle of Man (GD3TNS)	GI/GD	290	85	South Birmingham (G3OHM)	M	123
40	Lowland R. Sigs. (GM3TLR)	GM	286	86	Sussex University (G3SIX/A)	S	108
41	Stevenage (G3SAD)	S	283	87	Maidenhead (G3WXX/A)	S	102
42	Midland (G3MAR)	M	281	88	Addiscombe "B" (G3VYI)	S	93
43	Reigate "B" (G3OVL)	S	280	89	Bromsgrove (G3VGG)	M	85
44	Bristol (G3TAD)	S	277	90	Grimsby (G3VIP)	M	76
45	Salisbury (G3FKF)	S	273	91	Mansfield (G3GQC)	M	74
46	R.A.F. Sealand (GW3ITZ)	GW	262	92	Dover and Deal (G3UWQ)	S	66
47	Wirral (G3NWR)	M	257	93	Swindon (G3VBQ)	S	60
48	Loughton (G8AB)	S	246	94	Haverfordwest (GW3KGD/A)	GW	46

G3SSO and G2HAO/A as among the best *operated* stations heard. And this is not to say that there were no others.

It should be remembered that, apart from trying to give Clubs an interesting competitive event, another objective of MCC is that it should be an exercise in CW-expertise—which does not just mean extra high-speed key manipulation.

Potted History

Many people imagine that MCC has been, in essentials, the same sort of event from time out of mind—this is just not so, and perhaps now would be a good

time at which to put the record straight. A look at the graph, first, which shows how MCC has gone from strength to strength over the years—as, indeed, has Amateur Radio itself.

Back in 1946, the battle was spread over *nine days*, out of which one could take a maximum of twenty hours, to work all takers, and with a multiplier based on the number of call areas covered. G2YS (*Coventry*) made 209 contacts in the time with a multiplier of six. Actually the "possible" was nine—G, GC, GI, GM, GW, DL, LA, OK and OZ.

Year 1947 saw the number of hours upped to thirty, and this time G2JL, *West Cornwall*, replaced *Coventry* in the top spot, with 179 contacts and a multiplier of



One of the sides to field a second station for this year's MCC was the Echelford Amateur Radio Society (Zone South). The operating team consisted of (left to right), G3WVJ, SWL Adams, G3SAZ (foreground), G3WPK, G3UIJ and G3UNV (who took the picture). They knocked up 157 points for their 78th position in a field of 94 Club stations entering.

seven; "possible" this time was ten, with GD added to the list.

In GC, GI, GM and GW they seemed to have found the going a little tough, so for 1948, it was decided to make a QSO outside one's own Zone worth two points. For the GW stations this was just dandy, and GW3FFE (*Rhigos*) hit the jackpot, with seven prefixes, a victory repeated in 1949 with a multiplier of eight, while for 1950, he did the hat-trick with a multiplier of no less than eleven, these being G, GC, GD, GI, GM, GW, DL, EI, HA, OK and OZ—but it has to be said that even if the earlier rule of one point per QSO had been kept to, GW3FFE would have still been very near the top.

Clearly a change was due, and so 1951 saw the first real inter-Club affair. Nine days coverage still, Club contacts only, and each Club could be worked once each day. *Coventry* came first once again, this time signing G2LU.

A further change the following year saw eight periods from 1830 to 2230, and was spectacular in that G2YS, now representing *Chester*, and GW3EOP (*Neath*) dead-heated for first place. From 1953 to 1958 the rules were the same, but the operating period was progressively reduced, and times varied. Afternoons were taken in '53, and GW3EOP (*Neath and Port Talbot*) thrived on them, as they did again in 1954. Then 1430-1630 was replaced by 1500-1900, which enabled G3BFP, battling for *Surrey*, to break the GW stranglehold but not, be it noted, before the second hat-trick had been brought off, by GW3EOP over the years '52 to '54.

A further reduction, this time to twelve hours, by was of four sessions 1600-1900, and G3BMY put *Stourbridge* on top, as he also did the following year with an increased score. G3BMY nearly made another hat-

trick in 1958 but just missed it by coming joint second with *Coventry* to the winners, *Crystal Palace*. The 1959 MCC featured later hours, 1700-2000, and the dropping of the exchange of QRA/QTH in favour of a scheme of Club identifying numbers, very similar to the one used this year, with which system *Stourbridge* again brought home the bacon with the help of G3BMY; under the same conditions he won yet again in 1960, this time very narrowly from *Aldershot*, who were also

TABLE II
Top Scorers in the Regions

<i>Southern</i>				
1	East Barnet (G3RPB)	557
2	Harrow (G3EFX)	524
3	Govt. Communications (G3SSO)	500
<i>Northern</i>				
1	Newcastle University (G3OWM)	561
2	Spenn Valley (G3FVC)	552
3	Wakefield (G3VMW)	520
<i>Scotland</i>				
1	Moray Firth "A" (GM3KHH)	598
2	Kirkcaldy (GM3FXM/A)	580
3	Moray Firth "B" (GM3TKV)	356
<i>Midland</i>				
1	Burslem (G3VNR)	641
2	Kings Norton (G3GVA)	523
3	Nottingham (G3EKW)	470
<i>Wales</i>				
1	University of N. Wales (GW3UCB)	374
2	Cardiff (G3SQX)	332
3	RAF Sealand (GW3ITZ)	262
<i>GI/GD</i>				
1	Isle of Man (GD3TNS)	290
2	Ballymena (GI3FFF)	161

second the previous year, albeit by a much wider margin.

A new system, by which contacts were loaded by different points-value for each region, attracted a large entry—in fact a record up to then—and also a first Northern winner in *Hallamshire* (G3JHC). Talk there was of the absence of GI/GD stations of the previous years, and of allowing ten points per contact to the GM stations to give them a sporting chance! Indeed, in 1962, the GM stations *were* getting ten points per QSO—but apart from GM6RI, who was third, the order seems to have been determined solely by the number of Club QSO's made. Among the might-have-beens is the case of the Southern group who dismissed GM6RI as "not worth waiting for," as they thought he was "only a one-pointer"—but the 10 pts. would have brought him up a place and improved an already good position! Already, SWL D. Law had started his series of check-logs which have made him an institution in MCC, his first one appearing in 1961. *Gravesend* won this one.

As in 1962, the 1963 MCC was run off over one weekend, but with four hours instead of three in each of two sessions, GW3FSP winning on this occasion for *Port Talbot*. By this time the idea of MCC as a Contest

"MONTH WITH THE CLUBS"

With next month's issue, dated February and due out on January 26, the Club feature will revert to normal—for which reports should be with us by Friday, January 5, addressed: "Club Secretary," Short Wave Magazine, Buckingham.


wherein stations competed with one another on a regional basis, as well as for the absolute win, was well established. 1964 saw the first Contest under the present rules, using a two-letter code group instead of the earlier letter-plus-number system, and G3IGW took the plum, with *Oxford* (G3RBP) following *Halifax* into second place. Came 1965, and *Racal* (G3RAC) made a first stab at MCC—and won! They were followed home by *Maidstone* YMCA, with *Sheffield* "B" taking third place.

Just to show we really had a well-balanced formula at last, 1966 gave the first three as *Kirkcaldy*, *Newcastle University* and *Moray Firth*, in that order.

And so to this year, when no changes were made other than to revert back to a letter/number identification,



This time, Verulam Amateur Radio Club, at 29th position, scored 351 points, their team being G3LXP (finger on paddle), SWL Fisher (logging), G2AIA checking the October issue of "Short Wave Magazine" to make sure they'd read the rules right, and SWL's Wells and Goldsmith. The gear consisted of a modified Sommerkamp Rx with an out-board Tx unit using the receiver VFO to give full transceive facilities, with BK, side-tone monitoring and low-current keying. To ensure accurate netting, a 7 mc "rubber crystal" circuit was used in the Tx mixer, this being combined with the 5 mc VFO to produce transverted output drive for the PA on Top Band.

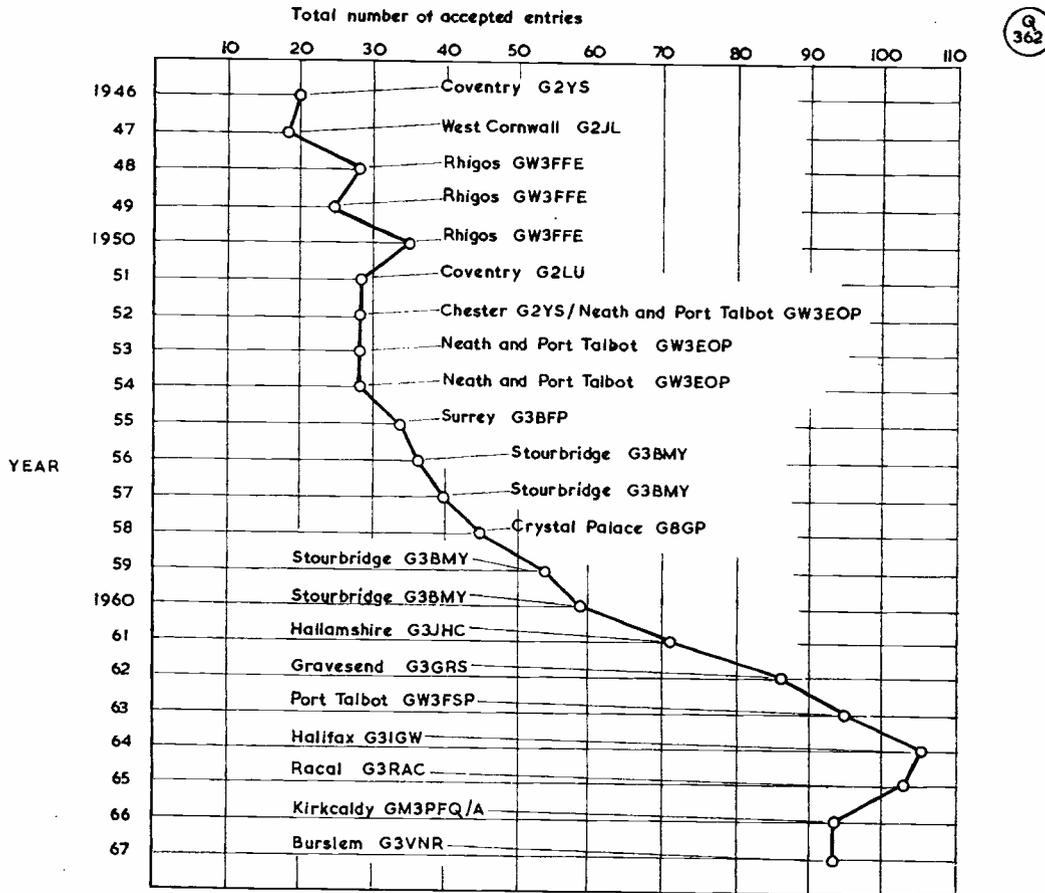

Graph showing MCC development and progress since the inception of the Contest in 1946. Points of interest are discussed in the text.

albeit this time in a standard form which made the length of the group about the same for everyone; however, there is no doubt that the ball *did* run ill for the lads with the 702 code—it should have been printed as Z02!

Over the years, MCC has been notably a sporting Contest, and the fact that so many of the same calls that were prominent in yesteryear are still to be heard, one way or another, is a fine thing.

Changing tack a little, it is interesting to note how few "Works" groups enter. Really, this is not surprising, as there are few of us who are so dedicated as to want to play on the same premises where we work—but it is noticeable that, over the years, those who have found the enthusiasm have usually done well. One thinks of *Racal*, of *Plessey* (West Leigh) and, of course, of *Painton*, who this year put in an entry which took them to 23rd place with 372 points. The gear was the Club's KW-2000A, used in conjunction with SWR bridge and ATU to energise a half-wave end-fed aerial at 30 feet. The Painton operators were G3KAN, G3WJY, G3WJZ and G3RVM, all members of the firm.

Again, looking at the picture over a period of years, it seems to your scribe that there is a tendency for the groups operating in true Club fashion—that is, using the Club gear in their own premises—to score a little lower than those groups who put in a determined entry from the station of a member. But it doesn't seem to matter tuppence to the lads if there are snags, or whether the shack is warm or cold, so long as the Contest is played out—and that's how we on the *Magazine* like it, too!

So there you have it. One of the friendliest, and yet keenest, Contests on Top Band, and as much pleasure, we sincerely believe, to those who operate and log, as it is to us of *SHORT WAVE MAGAZINE* to lay it on, invigilate, assess the logs, and to read all the wise, witty—and otherwise!—comments.

Next month, it is back to normal for "The Month with The Clubs" and your reports, covering in particular forthcoming events, should be in to us by first post January 5, for inclusion in the February issue. Address them, as always, to "Club Secretary," *SHORT WAVE MAGAZINE*, BUCKINGHAM. Meanwhile, a Happy and Prosperous New Year to you all.

NEW QTH's

This space is available for the publication of the addresses of all holders of new U.K. call signs, as issued, or changes of address of transmitters already licensed. All addresses published here are reprinted in the U.K. section of the "RADIO AMATEUR CALL BOOK" in preparation. QTH's are inserted as they are received, up to the limit of the space allowance each month. Please write clearly and address on a separate slip to QTH Section.

EI7BS, P. J. McGorman, McCurtain Street, Clones, Co. Monaghan. (Tel. Clones 97.)

GM3RAO, P. S. Hayes, 3 Sydenham Road, Glasgow, W.2.

G3VRB, J. D. Nias, 49 St. Margarets Road, Bishopstoke, Eastleigh, Hants. SO5 6DG. (Tel. Eastleigh 3782.)

G3WLT, D. Firth, 3 School Lane, Shaldon, Teignmouth, Devon.

G3WLW, R. Millar, 17 Brooklands, Bradley, Huddersfield, Yorkshire.

G3WPH, M. J. Chamberlain, 148 Calve Croft Road, Peel Hall, Manchester, 22. (Tel. Mercury 2665.)

G3WRA, S. Powell, 7 Commercial Road, Hereford. (Tel. Hereford 3415.)

G3WRD, R. J. Richardson, 32 Elliott Road, Chiswick, London, W.4.

G3WSJ, A. Evans, 1 Spital Lane, Cricklade, Swindon, Wilts. (Tel. Cricklade 479.)

G3WSZ, P. Gilson, 22 Carr Manor Place, Leeds, 17.

G3WTR, D. T. Wright, 8 Nolton Place, Edgware, Middlesex. (Tel. 01-952 7342.)

G3WWX, P. C. Swann (ex-MD5PS), 56 Church Street, Old Glossop, Derbyshire. (Tel. Glossop 2650.)

G3WXG, I. D. Habens, 367 Ditchling Road, Brighton 6, Sussex. (Tel. Brighton 53150.)

G3WXJ, G. Sanby, 25 Norton Park Drive, Norton, Sheffield. S8 8GP.

G3WYH, R. R. T. Hutton, 118 Ruskin Avenue, Sawley, Long Eaton, Notts. (Tel. Long Eaton 4885.)

G3WYY, J. R. Smith, Manor House Farm, Eccleston, Chorley, Lancs. (Tel. Eccleston 373.)

G3WZF, A. Butt, 15 Brownberrie Crescent, Horsforth, Leeds, Yorkshire.

G3WZI, K. A. Reeves, 15 Chadley Close, Solihull, Warks. (Tel. SOLihull 0450.)

G3WZJ, A. Dudley-Watt, 67 Glenhurst Avenue, Bexley, Kent. (Tel. Crayford 22564.)

G3WZM, G. A. Suckling, Station House, Railway Road, Downham Market, Norfolk.

G3WZP, G. A. Budden, 102 Frost Road, Kinson, Bournemouth, Hants.

G3WZS, H. Williams (ex-9L1HW), 4 Meadowbank Road, Fareham, Hants.

GM3WZU, J. Brown, 10 West Doura Avenue, Saltcoats, Ayrshire.

G3XAA, D. J. Howe, 7 Mayfair, Pedmore, Stourbridge, Worcs.

G3XAB, D. Whittaker, 6 Lynthorpe Road, Nelson, Lancs.

G3XAC, C. J. Whitehead, 68 Hollingreave Road, Burnley, Lancs.

G3XAD, A. Southwell, 12 Brockenhurst Street, Burnley, Lancs. (Tel. Burnley 26037.)

G3XAE, B. W. Hodkinson, 33 Brook Street, Macclesfield, Cheshire.

G3XAI, J. E. Temple, 4 Coquetdale Place, Bedlington, Northumberland.

G8BBG, S. Garrity, 11 Town Field Villas, Doncaster, Yorkshire.

G8BBP, K. F. Ballinger, 125 Astwood Road, Rainbow Hill, Worcester.

G8BBY, C. Hayward, Toll House Filling Station, Watling Street, Watford, Rugby, Warks. (Tel. Long Buckby 200.)

G8BCS, A. P. Legg, 12 Orchard Way, Sutton, Surrey.

G18BDR, N. E. Evans, Killyberry, Castledawson, Co. Derry.

GM8BDX, A. J. Scott, Manderston Stables, Duns, Berwickshire.

G8BEA, R. I. Harcourt, 50 Pleydell Road, Swindon, Wilts.

G8BFJ, M. J. Brindle, 24 Mount Pleasant, Ruislip, Middlesex.

CHANGE OF ADDRESS

G2CIW, J. F. Moseley, 69 Brandwood Road, Kings Heath, Birmingham 14. (Tel. HIGbury 1053.)

G3BIK, E. Chicken, 21 Townsend Crescent, Kirkhill, Morpeth, Northumberland.

G3BNI, D. L. K. Coppendale, 27 Lismore Road, Homefarm, Highworth, Swindon, Wilts.

G3CCU, G. Phillips (ex-GW3CCU), c/o 7 Harbour Street, Broadstairs, Kent.

G3CIV, J. M. F. Sweet, 31 Gredtale Avenue, St. Annes, Lancs.

G3JMJ, D. E. Nunn, Fircroft, Station Road, Edenbridge, Kent. (Tel. Edenbridge 3467.)

G3LRS, Leicester Radio Society, Gilroes Cottage, Groby Road, Leicester. LE3 9QJ.

G3MFV, A. S. Frank, 8 Kennedy Avenue, Fixby, Huddersfield, Yorkshire. (Tel. Huddersfield 23534.)

GM3MHG, J. Enderby, 2 Muirhead Road, Troon, Ayrshire.

GW3NJW, C. Whelan, 24 Severn Road, Canton, Cardiff.

GW3PEX, L. France, 8 Conway Drive, Pant Farm Estate, Cwm-bach, Aberdare, Glam.

G3PGX, D. G. Murgatroyd (ex-9H1AI), 14 Raleigh Road, Padstow, Cornwall.

G3SZC, I. G. West, 110 Wife of Bath Hill, Canterbury, Kent.

G3TRA, A. Wilkinson, 25 St. Helens Drive, Leicester. LE4 OGS.

G3TXH, B. G. Levett (ex-VS9ABL), 36 Lymescote Gardens, Sutton, Surrey.

GM3VVF, A. C. Ross, 42 Granton Place, Edinburgh 5.

G3VYE, J. Doswell, 42 Woodford Road, Poynton, Stockport, Cheshire.

G4AL, G. R. Cox, 98 Whatton Road, Kegworth, Derby.

G6KD, K. M. Dunsford, 51 Albany Road, St. Leonards-on-Sea, Sussex. (Tel. Hastings 3690.)

G6RJ, A. Robinson, Purdis Rise, Bucklesham Road, Ipswich, Suffolk. (Tel. Ipswich 78748.)

THREE-BAND AERIAL SYSTEM

FOR 40-20-10 METRES,
WITH STUB MATCHING

WHERE only one transmitting aerial can be erected, the amateur with limited ground space at his disposal is faced with a problem in making this aerial operate efficiently on all bands. The problem is complicated if the line of the aerial cannot be orientated in a direction favourable to propagation along the general DX paths.

The aerial described here has proved to be very satisfactory for multi-band operation, and its performance on DX has been outstanding. Local conditions of terrain, height and obstructions play a big part in aerial performance, and it is not suggested that this one is necessarily the best for a particular situation. But whatever the conditions, it might be worth trying, as the construction is simple. The height is about 30ft. only. The mast end is on a halyard, so that the aerial can be raised and lowered easily.

Ability to bring the centre of the "flat-top" to within reach is an essential feature, as will be seen later.

Multi-Band Requirements

Use for Top Band dictates that the aerial be as long as possible, since the lengths of 50 to 100ft. generally feasible in most situations only represent a fraction of the wavelength, and anything less is not of much use except for local contacts. Much the same considerations apply to the 80-metre band. No appreciable control of directivity can be achieved on either of these bands, and the usual practice is employed of tying the feeder ends together at the transmitter end, and working the whole thing against ground. On 7 and 14 mc, however, dipole horizontal tops become practicable, and even the 66-ft. top requisite for a 7 mc dipole can be achieved at most locations.

Unless a dipole can be erected approximately N-to-S it is not the best form of aerial for the DX bands 14 to 28 mc. On the contrary, some form of long-wire aerial is desirable at these frequencies, in order to bring lobes to bear in the required directions.


As the LF section of 7 mc is becoming useful again as a DX band, a dipole top cut for Forty will be worth having for general operation on it, irrespective of aerial direction.

Assuming, then, that a 66-ft. top is erected, its operation on 14 and 28 mc as a full-wave and two-full-wave aerial respectively will provide a more desirable lobe distribution, whilst operation on 1.7 and 3.5 mc with the feeders tied and operated against ground will give reasonable efficiency for local working.

The problem therefore resolves itself into one of feeding the aerial efficiently on the three HF bands.

Feeding and Matching

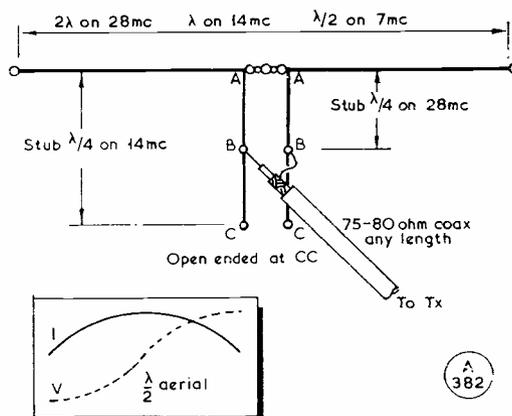The use of tuned feeders has always been viewed with distaste because at HF it is difficult to avoid losses, and to maintain balance—particularly with end-fed aerials



General layout and coupling system for the three-band aerial discussed in the text. It can also be used on the LF bands with "feeders tied". As explained in the article, the aerial must be erected in such a way that one end at least can be conveniently lowered.

and aerial coupling coils and tuning condensers—becomes difficult for multi-band operation. Also, at full p.e.p. output the tendency to condenser flash-over is a nuisance, necessitating wide spacing and bulk in the ATU.

Current feed, using a simple untuned link to the PA tank and a coaxial feeder, connecting into a current loop point on the aerial, is modern, simple and efficient.

Consideration of the application of this method to an all-band system led to the conclusion that a compromise was necessary, either in respect of efficiency or convenience. It was decided to maintain efficiency, and the sacrifice lies in the fact that in order to change the working band it is necessary to go outside and shift the position of the aerial end of the coax feeder.

Design of the Feeder

Above is shown a 66-ft. 7 mc dipole and the current distribution along its length. A current loop at the centre enables the feeder to be attached at that point, using low-impedance (75-ohm) coaxial cable.

The same top used on 14 or 28 mc has a current distribution such that the centre becomes a current node (voltage loop) and the low-impedance feeder cannot be attached at this point. If it is, the PA refuses to load up, because of the violent mis-match. Obviously the coax can be applied if the point of feed can be moved a quarter-wavelength (at the frequency to be used) away from the centre.

This can be accomplished by inserting a stub a quarter-wavelength long at the centre of the aerial, connecting the feeder to the other end. The effect is the same as adding another half wave into the aerial, except that since it is folded, the added portion will be non-radiating. However, two different stub-lengths are necessary for the 14 and 28 mc bands, the length of the former being approximately twice that for the latter. This led to trying out the idea shown in here, in which the open-ended stub is about a quarter-wavelength long on 14 mc and hangs vertically from the top portion.

For 7 mc operation the stub is not required, and the

coaxial feeder is attached at points AA.

For 28 mc the point of attachment is BB (quarter-wave at 28 mc below the centre) whilst for 14 mc the whole stub length is required and the feeder connects at CC.

The presence of the unused portion of the open stub at 7 and 28 mc has no effect on the functioning of the system. The stub comprises an open-wire twin-line of 16-gauge wire spaced to 3in.

The top or dipole section of the aerial was designed for 28,500 kc because it is best to cut the roof to the length necessary for the *highest* frequency band.

Since on 10 metres the top is two wavelengths long, the actual physical length is somewhat shorter than four times the length for a dipole at this frequency, owing to end effect.

The length may be calculated from the usual formula:

$$L \text{ (ft.)} = \frac{492 (N - 0.05)}{\text{Freq. (mc)}}$$

Where N=the number of half-waves in the top (4 for 28 mc). The stub length is given by:

$$L \text{ (ft.)} = \frac{234}{\text{Freq. (mc)}}$$


The stub length is actually made 17ft., so that on 14 mc the feeder taps on a few inches above the bottom end.

Adjustment and Operation

Begin with 28 mc. Attach the coax feed line to a point roughly half-way down the stub, inserting an RF ammeter in series with one side of the coax at this point.

The clips are now moved above and below this position about 2in. at a time until maximum current is indicated. At each setting the coupling of the PA tank circuit link is adjusted for constant power input to the PA. The stub wires are marked when the correct position of attachment is found. The same process is employed to determine the position for 14 mc with the feeder clipped on near the bottom.

INTRODUCING THE STAR-LINE SSB EQUIPMENT

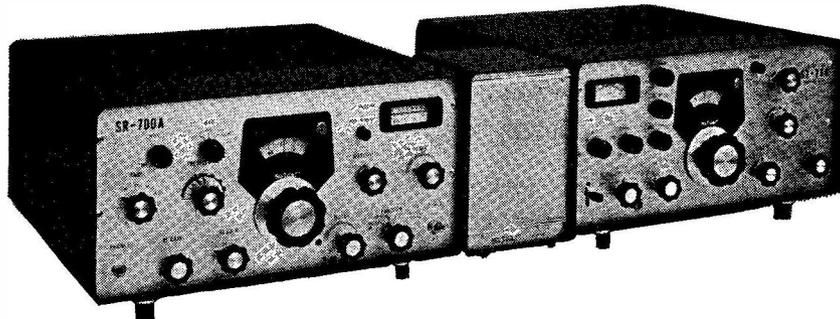

STAR S.R.700A TRIPLE CONVERSION HAM BAND RECEIVER

Xtal controlled 1st Osc.
100 kc/s. calibrator.
1-6 mc/s. and 55 kc/s. IFs.
Switched USB and LSB with xtal controlled osc.
Selectivity 0.5-1.2-2.5-4 kc/s. (6 dB bandwidth).
Bands : 600 kc/s. of all Ham bands 80m.-15m. with 28-29.7 mc/s. of 10m. band.
Gear driven dial gives direct read out to 1 kc.
Product detector for SSB-CW. Diode for AM.
Variable noise limiter.
Fast and slow AVC.
Notch filter variable in both frequency and depth.
BFO variable for CW acts as a receiver offset control in transceiver operation with ST700.

STAR TX. S.T.700 £128.0.0

STAR RX. S.R.700A £110.12.0

STAR SPK. SP7 £4.17.0

Also the S.R.550 AMATEUR BAND RECEIVER £52.10.0

DL5YP G6ABH/T G3WCQ

COVENTRY COMMUNICATION EQUIPMENT

43, EARLSDON AVENUE SOUTH, COVENTRY, WARWICKSHIRE


Telephone 0203-73641

Special for British and American Forces in Germany—

S.T.700 and S.R.700A—2,100 DM. or equivalent per pair ex Freeport Hamburg.

STAR ST 700 200 WATT P.E.P. AMATEUR TRANSMITTER

Selection of PTT or VOX with variable delay and antivox on SSB and AM. Full BK with sidetone monitor on CW.
Upper and lower SSB on all bands with 2.2 kc/s. mechanical filter (6 dB points).
Frequency read out to 1 kc by gear driven dial.
Full Transceiver facilities with matching S.R.700A Receiver.
Meter switchable for final grid—final anode—power out.
Facilitated for low power tune up.
Final uses pp 6146s, extremely well screened and filtered for low harmonic output.
A.L.C. control of final amplifier for high talk power with low T.V.I. T.V.I. extremely low as all stages conservatively run in linear mode. Built in p.s.u. for 220-240 volt mains.

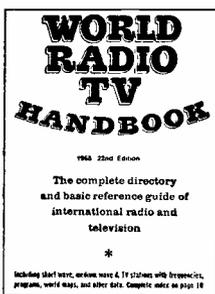

Special pre-publication offer of
1968 World Radio TV Handbook
 The world's only complete reference guide
 to International Radio and Television

Normal Price 2 gns.

*Copies ordered before January 15 — 35s.

Unsurpassed reader usefulness.

WORLD RADIO TV HANDBOOK is a must for short wave listeners, hams, DXers, station executives, engineering staffs, marketing and advertising specialists, broadcast organisations, or, in fact, anyone who needs a complete and accurate information on international radio or TV. Whether your interest is business or pleasure, **WORLD RADIO TV HANDBOOK** is the one reference book you should not be without. Don't miss owning your own copy of the new 1968 edition.

***Order from:**

Telltime Limited, 7 Welbeck St., London, W.1.

Name

Address

B5

Tell a friend about World Radio TV Handbook


Please send descriptive information without obligation to:

Name

Address

B5

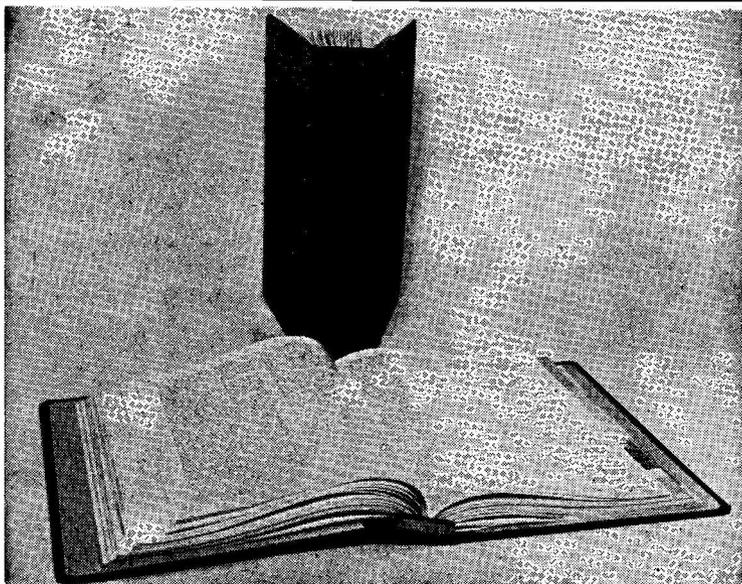Advertising in "Short Wave Magazine" guarantees the largest and most effective coverage of the U.K. radio amateur interest



CREATE YOUR OWN REFERENCE LIBRARY

by binding copies of Short Wave Magazine in the "EASIBINDER."


The "EASIBINDER" is designed to bind 12 copies of the Magazine as you receive them month by month, eventually providing a handsomely bound volume for the bookshelf.

No need to wait until twelve copies are assembled. As each copy is received, it is quickly and simply inserted into the binder. Whether partially or completely filled, the binder is equally effective, giving the appearance of a book, with each page opening flat.

Strongly made with stiff covers and attractively bound in maroon Leathercloth and Milskin, the binders have only the title gold blocked on the spine.

Price 14s. 0d. post free.

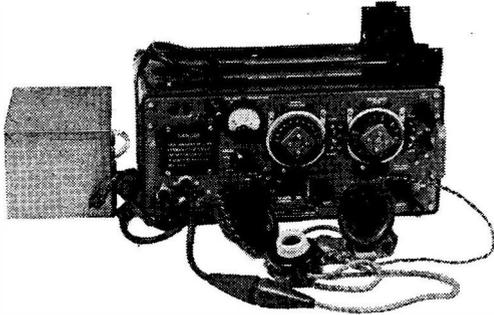**PUBLICATIONS DEPARTMENT
 SHORT WAVE MAGAZINE
 55 VICTORIA STREET
 LONDON, S.W.1**




TRANS/RECEIVER TWO TWO

This is one of the latest releases by the govt. of an extremely recent R/T set covering 2-8 Mc/s. in two switched bands, containing 13 valves (3 EL32s in Tx output) which can be used for Morse, CW or R/T. Also has netting trimmer, BFO, RF and AF controls, switched meter for checking all parts of set, size 17" x 8" x 12". Power required LT 12 volts D.C., HT 325 volts D.C. **Supplied Brand New** and boxed with **Headphones and Mike** also **Two Spare Valves** and circuit of set. **Few Only at £5/10/-**, carr. 30/- . New plug-in power supply made by us for either 12 volts D.C. input, £3/10/- or 200/250 volts A.C., £3/17/6.

LARGE QUANTITY OF SARAH V.H.F. TRANS/RECEIVERS

AVAILABLE FOR IMMEDIATE EXPORT

General Information. This set is normally carried in the life jacket of Airmen, it is a complete miniature lightweight radio Trans/Receiver, which is used to give a Beacon plus two-way speech communication in the event of finding themselves in the sea. It comprises a Transmitter-Receiver, a speech unit, a coding unit and a power supply either Battery or Transistor. These three items are permanently interconnected and all units are completely sealed and water tight using a combined speaker/mike, press to talk or listen buttons, fold-up aerial, a total of three valves is used, power required 6-3 volts LT 90 volts and 435 volts D.C. HT. Frequency 243 Mc/s. Transmitter output pulse power—Beacon 15 watts, Talk 3 watts. **Supplied in maker's boxes** in Grade 1 condition, singly at 45/-, post 5/- with circuit. New batteries if available, 7/6 each.

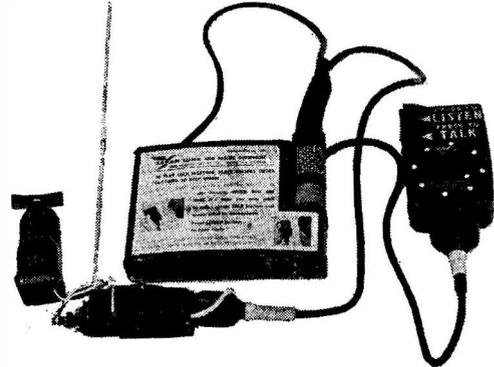

JOHN'S RADIO

OLD CO-OP, WHITEHALL ROAD, DRIGHLINGTON, BRADFORD
Telephone: DRIGHLINGTON 732

S.S.B. PRODUCTS

A good idea for 1968 — BUY BRITISH
HAPPY NEW YEAR TO ALL. 73—NORMAN BIRKETT—G3EKX

"SPHINX" Mk. II TX. S.S.B./A.M./C.W. 80 watts. 160m., 80m. (40m.), 20m. Built-in power unit. Still the best quality. Attractive cabinets. Easy to resolve pleasant sigs. All complete ready to plug-in, £84. (Reconditioned ones, £65.)

"PYRAMID" 800 watt LINEAR. 80-10m. Built-in power unit. All parts including cabinet and metalwork, £49/15/- (25/-).

"CANONBALL" TX. S.S.B./A.M./C.W. covers 1-8 to 2 mc. only 8 x 6 x 6 ins. (3-5 to 4 mc and 12v. versions), £38 (7/6).

"DELTA" Co-ax Relay. A.C. 1/1P, £7/5/- (6/-).

"NAPOLEON" SWR Bridge. Only 5 gns. (4/6).

"SCARAB" Xtal Filters, £8/7/6 (2/-) } includes carr. Xtal.

"SCARAB" Kits, £6/19/6 (2/-) }
All SCARAB Filters are complete with Cct. and easy to build in, instructions. No test gear needed. You cannot get on S.S.B. with good quality any easier. Imported filters as good as this, cost twice the price. Build a Tx yourself and learn a lot.

SPECIAL OFFER. SEND your CLASS D wavemeter for conversion to 240v. A.C. i/p. re-spray case, re-smooth, re-calibrate. (Xtal must be O.K.) Cost only, £5/10/- (8/6). Wanted to buy:—Class D wavemeters. Any condition. Any quantity. Fair Price.

SPECIAL OFFER CABINETS. 15 x 6 in., panel 12 in. deep with plain All' panel and blank chassis. Any colour. All 3 for only, 99/6 (8/6). These are the rounded corner modern design.

HA350 Receivers. 240v. 160-10m., £84 (6 band). We will convert your HA350 to 160m. Convert it to 240v. i/p. (fit special transformer). Improve the A.M. Specialists on this Rx. Write please (S.A.E.) and say what you want doing. Professional.

SILPLUG units. 500v., 30/-, 750v., 40/- (2/-).

D.A.I. electronic keyers in stock, £16/10/- (6/-).

KY.102 bug keys in stock, £4/10/- (4/6).

R.F.45. FIELD STRENGTH meters, only 45/- (2/-).

DM16HL dynamic mic. and cable stand, only 92/6 (4/6).

6146. BRAND NEW AND BOXED, only 30/- (2/3 each, P. & P.).

6HF5. 32/- each (2/3 each Post), bases 4/- each (6d.).

BM3 Mic's. Few left at 32/- each (4/6).

SPARE VALVES FOR CLASS D, Only 2-10/- (1/6).

TRIO. 9R-59, 35 gns. TRIO, JR500, 59 gns. or 160-10m., 64 gns.

7A EDWARD STREET DERBY
42909 42961

G3ZY

G3ZY

J. & A. TWEEDY (Electronic Supplies) Ltd.

Appointed Dealer and Stockist for

EDDYSTONE, K.W., ELECTRONIQUES, CODAR, SOMMERKAMP

New Equipment

EDDYSTONE : EC10 £53 ; 940 £133, 840C £66, EA12 £185.

KW ELECTRONICS : Full range in stock. KW2000A (inclusive £220). KW201 £105 (basic).

CODAR : AT5 £16/10/-, PSU's A.C. £8, D.C. £11/5/- ; RQ10X £8/8/- ; RQ10 £6/15/- ; PR30X £7/4/- ; PR30 £5/10/- ; T28 £15/10/-, CC40 control units £6/10/-.

SOMMERKAMP : Fully guaranteed FL200B £130, FR100B £112, FL1000 £90, FT100 Transceiver £180.

LAFAYETTE : HA500 £44/2/-, HA700 £37/16/-.

PARTRIDGE ELECTRONICS : Joystick Std. £4/15/- ; de luxe £5/19/6. Tuners : type 3 £2/15/- ; 3A £3/12/6 ; 4 £4/4/- ; 4RF £6/6/-.

"TAVASU" Whip Aerials for mobile. Full set of 5 coils and 8ft. 6in. adjustable whip complete £12/10/- per set. W.A.C. mobile first week-end test. British made.

Used Equipment

HA350 as new, £57/10/-, Heathkit DX100 with SB10U SSB Adaptor as new, £80. Panda PR120V, £35. National NCX5 with A.C. p.s.u., £165. LG50, £27/10/-, Geloiso G209, 160-10, £35. Geloiso G209, 80-10, £33. SX140, £18. HRO with 8 coils and matching p.s.u. as new, £20. NC101X (110v.), £20.

G3L GK 70 cm. Converters with p.s.u. £8/5/-.

H.P. TERMS AVAILABLE

TRADE-INS ACCEPTED.

64 Lordsmill Street, Chesterfield, Derbyshire

Tel.: Chesterfield 4982 or Holmewood 506 (evenings)

SCIENCE RESEARCH COUNCIL RADIO & SPACE RESEARCH STATION Ditton Park, Slough, Bucks.

MALE ASSISTANT EXPERIMENTAL OFFICERS are required for a three-year tour of duty at Stanley, Falkland Islands, for operating and maintaining advanced apparatus for recording scientific information transmitted by telemetry from satellites. (Shift work). Married staff live in rent-free accommodation in modern well-furnished bungalows.

QUALIFICATIONS :

University or C.N.A.A. degree, H.N.C. or equivalent qualification. If under age 22, five G.C.E. passes including two science or mathematical subjects at "A" level (or equivalent).

SALARY :

Salary whilst overseas on scale £690 per annum rising to £1,318 ; starting salary at age 21 years £809 ; at age 26 years or over, £1,092. Additional overseas allowances and shift pay.

Apply :— The Secretary, S.R.C. Radio and Space Research Station, Ditton Park, Slough, Bucks.

HAMMERITE HAMMER PATTERN BRUSH PAINT FOR PANELS, METALWORK, ETC.

TRIAL TIN (covers 5 sq. ft.) only 3/9 + post 9d.

COLOURS : blue, silver, black, or bronze.
2½oz. tins, 3/9. ½ pint, 8/-. 1 pint, 16/-. Very special prices for larger sizes. Carr. up to 5/-. 9d., up to 10/-. 1/9, over 10/-. 3/-.
HAMMERITE produces the cellular pattern known as hammer finish. Just brush on. It air dries in 20 minutes to a smooth, dust repellent tough finish. Withstands 150 C, oil, water, etc. Adheres to practically anything without a primer. Ideal for metalwork. One coat on hardboard makes fabulous panels. (No primer needed). Government tested. Amazing results, just try it!

RETURN OF POST SERVICE, Monday to Friday.

Fireproof spray thinners, tinters, panel transfers, etc. List Free.

FINNIGAN SPECIALITY PAINTS (SW)
MICKLEY SQUARE, STOCKSFIELD, NORTHUMBERLAND
Tel.: Stocksfield 2280

The Mini-Ten

Two element beam for 10 metres

Work the D.X. with this small beam which can be erected anywhere single handed.

Sold only direct to the Radio Amateur which means lower prices.

Overall length only 10ft. 8in., weight only 8½lbs.

The Mini-Ten is of all dural construction and necessary parts cadmium plated.

Send S.A.E. (9 x 4) for fully illustrated leaflet, to

MINITENNA BEAM PRODUCTS

(J. Sharratt)

EDLESBOROUGH DUNSTABLE, BEDS.

Tel. Eaton Bray 297.

NEW 1967

24 page illustrated list of
Valves - Transistors, SCR's, Zeners, Tunnel Diodes, F.E.T.'s, Photo Devices, Quartz Crystals, 1/-.

Completely New Edition
2,000 listed Devices
Have you sent for your copy!

1967 CATALOGUE

Completely New Edition 200

Packed Pages Fully illustrated

10/- DISCOUNT VOUCHERS enclosed with every copy.

Price 8/6
Post paid.



HENRYS RADIO Ltd. PAD 1008/9
303 EDGWARE ROAD, LONDON, W.2 Mon.-Sat. 9-6 p.m.
Thurs. 9-1 p.m.

PRINTSET

KITS FROM
WEST GERMANY

Easy to Build — Printed Circuits — LOW priced!

VHF : 2M Superhet Receiver (Transistors)
2M Transmitter { " }
2M Modulator { " }
2M Converter (Valves)
2M Transmitter { " }
2M PA and Modulator { " }

SSB : 9MHz SSB Generator, and Mixer-Oscillator for Amateur Bands.

CW : Electronic Morse Keys (Transistors)

RTTY : DL6EQ Demodulator (TU), Bandpass and Tuned, 2125/2975, 1050/1900 Hz Filters, C/R Tuning Unit, FS Keyer, AFSK Oscillators, 88mhz Toroids, T/P Motor Strobe Forks.

If you want to know more — Ask for leaflet SP4.

SPACEMARK Ltd.

14 PICCADILLY,
MANCHESTER 1
(Tel: 061-237 0817)

UP TO THE MINUTE INFORMATION

LOOK! Greatly Reduced Prices of TRANSISTORS

2N1302/3	3/11	2N706	3/6	2G302	5/5
2N1304/5	5/3	2N699	12/2	2G301	3/10
2N2926	4/-	2G371	3/6	2N3703	4/9
2N3706	3/11	2G374	4/5	GM290A	17/2
2N3707	5/9	2N1613	7/-	2N3711	4/6

OUR REPUTATION IS FOR NEW, QUALITY DEVICES
P. & P. Is. 6d. Revised price list 4d. stamp. Catalogue 2s.

MARLISON
Electronics

J.W.E. Ltd., Dept. S2,
176 Hagley Road, Halesowen,
Worcestershire.
Tel. 021-550-3210.


SCA 63982 **DERWENT RADIO** S.A.E. LISTS

We stock:—KW, Sommerkamp, Swan, Drake, TW, Eddystone, Hallcrafters, Codar, Lafayette, etc.

KW Viceroy II and p.s.u.	£80	Lafayette Precon	... £12
Hallcrafters SX111	... £80	HRO/p.s.u./8 coils	... £16
LG50 transmitter	... £26	National NC 183D	... £65
HRO bandspread coils	30/-	Star SR550	... £35

Cash or a good trade-in for your used equipment. Carriage extra.
28 HILLCREST AVENUE, SCARBOROUGH, YORKSHIRE

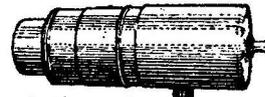A new delivery of the famous COWL GILL MOTOR



● Ideal for beam rotation, etc.

Magnificent fully enclosed motor. Incorporates 600 to 1 epicyclic gearbox, final speed 11 r.p.m. on 12v., 15 r.p.m. on 24v. Limit switches can be removed to provide continuous running in either direction. 12in. x 3½in. x 1½in. dia. splined drive shaft x 3/4in. long. 4A at 12v. D.C. Instructions supplied for running on A.C. voltages. As new.

55/-
Carr. 7/6

PROOPS BROTHERS LTD.,
52 TOTTENHAM COURT ROAD, LONDON, W.1
Telephone: LANgham 0141

MORSE TAPE SERVICE

Individual morse lessons to AMATEUR LICENCE standard. Each tape at the speed you require. No repetition of text, avoiding familiarity. Deposit 7/6 (refundable) for first tape, then 2/6 per tape.

For details of this unique service, S.A.E. to:—

D. J. BEAN, G3TJQ
51 HEATHFIELD SQUARE, LONDON, S.W.18

SMALL ADVERTISEMENTS

(“SITUATIONS” AND “TRADE”)

9d. per word. minimum charge 12/-. No series discount. All charges payable with order. Insertions of radio interest only accepted. Add 25% for Bold Face (Heavy Type). No responsibility accepted for errors. Replies to Box Numbers should be addressed to The Short Wave Magazine, 55 Victoria Street, London, S.W.1.

TRADE

QSL CARDS: Attractive two-colour designs, 25s. per 100. Send s.a.e. for samples.—G3OYI, 16 Banks, Honley, Huddersfield, Yorkshire.

HUNDRED-PAGE Illustrated Catalogue No. 17 of Government and Manufacturers' electronic and mechanical surplus, including a completely new section covering the latest semiconductors and miniature components, with a credit voucher worth 2s. 6d. Send for your copy now, price 3s. post free. The reading alone is worth the money!—Arthur Sallis (Radio Control), Ltd., 93 North Road, Brighton, Sussex.

QSL Cards and Log Books, GPO approved, cheapest and best. Prompt delivery.—Samples from Atkinson Bros., Printers, Looe, Cornwall.

QSL Cards: Two-colour, attractive design, variable features, from £3 3s. per 1,000 (inclusive). Send foolscap s.a.e. for samples.—ARA Press, 46 Moat Avenue, Green Lane, Coventry.

Introducing the new G-Whip fibreglass helical antenna for mobile or portable working. This aerial features compactness, a matching impedance of 50 ohms, shows an SWR of better than 1.5:1 and is rated to the full 400 watts p.e.p. limit. Send s.a.e. for further details.—**Roberts Radio Service, 82 Duke Street, Southport, Lancs. (Tel. 3990).**

WANTED Urgently: BC-221 and LM Series Frequency Meters; also BC-312, BC-342 and BC-348 Receivers TCS transmitters and receivers; all types of Oscilloscopes and Test Gear. Also RCA 8516L and Hammarlund SP-600 receivers. Write, call, or phone.—**Amateur Electronics, 518-520 Alum Rock Road, Alum Rock, Birmingham, 8. (Tel. East 1497).**

Valve Voltmeters, No.2, 70s. Xtal Calibrator No.7, 70s. HRO PSU's, 50s. Capacity Bridges, range 50 mmF to 50 mF, 80s. Lo-Band 25-watt Rangers, 85s. Wooden masts, 20ft., 1½in. diameter, 12s. 6d. Codar A.T.5 Tx and PSU, new, £23. A.T.5 Tx, new, £15. Coils, 30 and 50 turns 1½in. diam. on ceramic formers, 1s. each. Also meters, two-metre J-Beams and other items. Add postage.—J. M. Fish, G4MH, 18 Town End, Golear, Huddersfield (52653), Yorkshire. (Open Sundays).****

JOB OPPORTUNITY

Radio Mechanic Required, for maintenance of MF/VHF equipment and Electronic Apparatus at Lighthouses and on board Light Vessels. Age range 25-45 years, average salary £1,350 plus liberal subsistence allowances, with two weeks' paid holiday, sick pay, etc.—Applications to: **Workshops Superintendent, Trinity House Workshops, Orchard Place, Blackwall, London, E.14. (Tel. EASt 5864/7).**


READERS ADVERTISEMENTS

3d. per word, minimum charge 5/-, payable with order. Add 25% for Bold Face (Heavy Type). Please write clearly, using full punctuation and recognised abbreviations. No responsibility accepted for transcription errors. Box Numbers 1/6 Extra. Replies to Box Numbers should be addressed to The Short Wave Magazine, 55 Victoria Street, London, S.W.1.


SALE: Pye Ranger Type PTC-2002V, 12-volt input pos. or neg., complete and unmodified, with circuitry, hand microphone and crystals for 70·26 mc, price £10, plus carriage (Surrey area).—Box No. 4578, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

FOR SALE: Volumes “Short Wave Magazine” 1947-56, 1958-59 and 1962-67, 15s. per volume, or near offer. Also RF units 24 and 26, at 7s. 6d. each.—**Smith, 40 Harrow Road, Carshalton, Surrey. (Tel. 01-642 0207).**

F-SERIES SSB EQUIPMENT

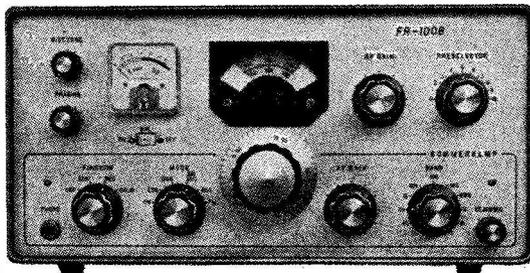

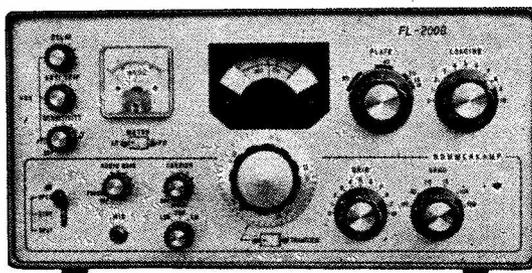FR-100B double conversion superheterodyne with crystal controlled first mixer, 80-10 metres
£112 0 0



FL-200B SSB/AM/CW transmitter, 240 watts PEP. Complete with built-in power supply and antenna relay
£130 0 0

also available

FL-1000 Linear Amplifier 960 watts PEP with built-in PSU £90 0 0

Full range (in stock) listed on facing page.

SAE Illustrated Brochure or

Hours: Monday-Saturday 9.0 a.m.—6.0 p.m.

SEE THEM IN STOCK AT

SWANCO PRODUCTS LTD.

247 Humber Avenue, COVENTRY

Telephone: Coventry 22714 Evenings: G3NAP Tile Hill 64279 G3PQQ Keresley 3456

SMALL ADVERTISEMENTS, READERS—continued

SELLING: As new, KW-600 Linear Amplifier, at £90. SBE-34 Transceiver in mint condition, £145. AVO Minor Mk.IV, unused, £6.—Barry, 15 Fairlawn Court, London, W.4.

SALE: One 70-centimetre tripler/PA, complete with 2/C39A's, blower, etc., £10. One 23-centimetre tripler, with 2C39, blower, etc., £8. Also two-metre/four-metre receiver, consisting two CC converters into Command Rx, tunable IF, switched bands, all on one chassis, price £10. All units ready to go. Take £25 for The Lot.—Russell, G8AWS, QTHR, or ring 051 ELL 2085, STD.

ENTHUSIAST Wanted to complete triple-conversion receiver project based on all-wave converter, R.1155 and BC-453. All the spade work has been done. Equipment complete plus full gen. and relevant magazine articles, asking £20 only.—Matthews, 31 Braemore Road, Hove, Sussex. (Tel. Brighton 730984).

SALE: Receivers BC-639A, coverage 100 to 156 mc, £12; R.1155 at £6. Also Marconi Type TF-428B/1 valve voltmeter, £8.—Bloom, 4 Langsett Avenue, Sheffield 6, Yorkshire.

WANTED: National HRO Senior receiver, with BS coil packs for amateur bands. PSU not essential. State price and condition. (Angus, Scotland).—Box No. 4579, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

OFFERS? Receivers AR88D and AR88LF, cleaned and with new valves, plus spares. Also Avometer Mk.VII and Nombrex Signal Generator. Best offers secure. — Clarke, Rosebank, Canon Pyon (374), Hereford.

WANTED: Several QQV02-6 valves at a reasonable price. Details, pse.—Grigg, G3PRX, 72 Elmstone Road, Rainham, Kent.

COMPLETE Mobile Station: Codar A.T.5 Tx, £12. T.28 Rx, £11. PSU, 12v., £8. R/C unit, 12v., 30s. Halsion whip and coils for 80/160m., £8 10s. Xtal microphone, 30s. Speaker 2½-in. by 8¼-in. Carriage extra, or complete rig £40, carriage paid.—Livermore, 15 Angel Hill, Bury St. Edmunds, Suffolk.

WANTED: By a novice-SWL, good amateur-band receiver, or any such Rx capable giving satisfactory SSB reception and any other interesting listening. Up to £75 available, but price must include delivery.—Coan, 140 Wroxham Road, Norwich, Norfolk.

WANTED: R.216 receiver with its PSU. Must be in perfect condition.—Davidson, 19 Cavendish Avenue, Finchley, London, N.3. (Tel. FINchley 4353).

BARGAINS For Quick Sale: Heathkit DX-100U Tx, £50. National NCX-3 with NCX-A PSU and suitable auto-transformer, £100. Star SR.550 receiver, amateur bands only, double-conversion with product detector for SSB, £45. All items in perfect condition and carriage paid.—Hargan, G12DHB, 3 Epworth Street, Londonderry, Northern Ireland.

FOR SALE: K.W. Vanguard transmitter, covering 10 to 160 metres, 50 watts AM/CW, £40 or near offer? Home-built Rx to the G3RKK design, with Electroniques QPP-166 front end, two-converter, £25 or offer. Also Collins mechanical filter, 500 c/s 455 kc, offers?—Arscott, G3VSL, 5 Copswood Road, Ashurst, Nr. Southampton, Hants.

SELLING: Latest model Swan 350 Transceiver with SAC/PSU, both in as-new condition. Have made WAS/WAC with this rig using indoor dipoles! Price £190. Going VHF/UHF, (Lancs. area).—Box No. 4580, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

WANTED: KW-2000A or Swan Transceiver.—Cafferty, 190 Victoria Avenue, Hull, Yorkshire.

SMALL ADVERTISEMENTS, READERS—continued

SALE: Lafayette HA-350 fitted 100 kc crystal calibrator, condition as new, £55. National HRO-5T, with nine coil-packs, condition as new and unmodified, £25. Codar PR-30X preselector, 65s. Joystick de luxe with Type 3 tuner, 70s.—Gillham, 260 Summerhouse Drive, Wilmington, Kent. (Tel. Swanley 3968).

SALE: Heathkit Mohican GC-1U receiver, in excellent condition and recently checked and aligned by Daystrom, Ltd., price £25.—Burke, 28 Gloucester Avenue, Hurstead, Rochdale, Lancs.

WANTED: Bandsread coil-packs for HRO-5T, covering 3.5 mc, 7 mc, 14 and 28 mc. Good price offered.—Oates, 3 Canadian Avenue, Hoole, Chester.

SALE: Converted Stratton (Eddystone Radio) transmitter, covering 20-40-80m. bands, running 90-200 watts, 813 PA, high-level modulated, VFO and with robust power supplies, any test, price £20.—Rayer, G3OGR, Reddings, Longden Heath, Upton-on-Severn, Worcs.

FOR SALE: Stabilised power supply units; five-inch and 14-inch oscilloscope displays; UHF wobblers; wideband 30 mc amplifiers; chassis and cabinets. Buyers to inspect and collect. No reasonable offer refused.—Wiltshire, G8AKA, 12 Leslie Road, Winton, Bournemouth, Hants.

EXCHANGE or Sell: Pye Base Station for 60-100 mc band; ideal for four metres, comprising Type PTC-330N Tx and PTC-3002N Rx, in modern blue cabinet, crystal-controlled with oven, 20 watts output, with manual, in excellent condition but requires new meter, price £20 complete plus 20s. post/packing; manual sent on 10s. deposit — or Exchange Phone Tx for 10-30m., home-built rig considered but must be TVI-proof. What Have You? All letters answered.—Lambert, No. 35 A.M.Q., R.A.F. West Raynham, Fakenham, Norfolk.

SALE: Hallicrafters HT-40 transmitter (circuit similar to DX-40), price £18 or near offer. Also new and unused KW low-pass filter for Ch.II, 75-ohm, 70s.—Brown, G3TLH, QTHR.

SALE: Eddystone EC-10, 12 months old, price £38.—Whitham, 25 Chatburn Park Drive, Clitheroe (2276), Lancs.

EXCHANGE or Sell: Eddystone S.640 Rx, modified and in excellent condition, with Candler Morse Course and practice buzzer, price £15—or Exchange for Model Railway, W.H.Y.?—Watson, Bartlow Road, Castle Camps, Cambridgeshire.

SELLING: Lafayette HE-30 receiver, £20. Also "Short Wave Magazine," years 1952-'64, from 15s. per volume.—Pillej, G3HLW, 27 Oxted Rise, Oadby, Leicester, LE2 5WG.

SALE: Collins TCS-12 receiver, in immaculate condition, with PSU, £8 10s. R.1475 Rx, with built in amplifier, £7 10s. Buyer pays carriage.—Smith, 50B Aldershot Road, Guildford, Surrey.

FOR SALE: For 70 mc band, Pye PTC-108D radio-telephone, £5 10s. Type RT34/APS-13 UHF Tx/Rx, 70s. All valved. Tuning Units TU5B, TU6B, TU7B, 50s. each. All carriage paid.—Austen, 1 Valebridge Road, Burgess Hill Sussex.

WANTED: For my R.1155, the IF transformers to suit, also any information about fitting a half-lattice filter, postage refunded. (London area).—Box No. 4581, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

OFFERING: Due Arrival Expensive Junior Op., my superbly-constructed 2DAF receiver, in a Philpotts cabinet, with new QCC xtals, Electronics coils and transformers, complete except for its valves and not aligned, cost of parts over £100, snip for you at £45 (or a reasonable offer?). Also Electronics coils and IF transformers for the 2DAF Tx £10 or offer? All carriage paid.—Sykes, G3OYW, 1 Smallacombe Road, Bakers Hill, Tiverton (3466), Devon.

WANTED: A National NCX-5, Mk. II. (Midlands). Box No. 4584, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

SWANCO PRODUCTS

LIMITED

G3NAP AMATEUR RADIO SPECIALIST G3PQQ

NEW EQUIPMENT

£ s. d.

Sommerkamp F-Series Equipment		
FR-100B double conversion superheterodyne with crystal-controlled first mixer, 80-10 metres	...	112 0 0
FL-200B SSB/AM/CW transmitter, 240 watts PEP, complete with built-in power supply and antenna relay	...	130 0 0
FL-1000 linear amplifier, 960 watts PEP	...	90 0 0
Sommerkamp FT-150 transceiver, 80-10 metres	...	190 0 0

Swan Line Equipment :		
Swan 500 BB transceiver	...	238 0 0
Swan 230-XC power supply/speaker	...	45 0 0
Swan 410 V.F.O. and adapter	...	57 0 0

Hallicrafters Equipment :		
SX-130 Communications receiver	...	79 0 0
SX-122 Communications receiver	...	135 0 0
SX-146 SSB receiver, 80-10 metres	...	125 0 0
HT-146 SSB transmitter, 80-10 metres	...	175 0 0
SR-2000 Hurricane transceiver	...	495 0 0
P-2000 power supply	...	195 0 0
HA-1 electronic keyer	...	39 0 0

Eddystone Radio Ltd.:		
Eddystone EA12, Amateur bands receiver, 160m.-10m.	...	185 0 0
Eddystone 940, Communications receiver	...	133 0 0
Eddystone 840C receiver	...	66 0 0
Eddystone EB35 receiver	...	60 6 3
Eddystone EC10 receiver	...	53 0 0

Trio Communications Receivers :		
Trio JR-60, 14 tubes amateur communications receiver, 540 kc/s.-30 mc/s., plus 142-148 mc/s.	...	61 19 6
Trio 9R-59, 9 tube communications receiver	...	34 13 0
Trio 9R-59DE, 8 tube receiver	...	36 15 0
Trio JR-500SE, Crystal controlled double superhet	...	61 19 0

Lafayette Receivers :		
HA-500, Amateur bands receiver	...	44 2 0
HA-700, Communications receiver	...	37 16 0
HA-350, Amateur bands receiver	...	78 15 0

K.W. Electronics Ltd.:		
K.W.201, Amateur bands communications receiver, 160-10m.	...	125 0 0
K.W. "Vespa," Mk. II with P.S.U.	...	108 0 0
K.W.2000A and P.S.U.	...	220 0 0

Full range of K.W. Equipment now in stock.

Full range of Drake Equipment available.

Full range of Heathkit Equipment available.

Swanco/CSE Equipment :		
Swanco/CSE 2A10 solid state transmitter	...	43 7 0
Swanco/CSE 2AE solid state receiver	...	44 0 0
Swanco/CSE, Type II A.T.M.A. mobile/fixd/portable antenna	...	9 15 0
Swanco/CSE microphone, type MM2	...	2 17 11
Halson, Mobile antenna, new all weather all bands system	...	6 17 6
Extra coils (when more than one band required)	...	3 17 6
Swanco Quad Spiders (per pair)	...	6 10 0

Mosley Electronics (Beams)		
TA-33Jr, Triband three element beam	...	27 5 0
TA-32Jr, Triband two element beam	...	19 5 0
TA-31Jr, Triband dipole	...	11 11 0
V-3Jr, Triband vertical	...	8 5 0
TD-3Jr, Wire trap Dipole kit	...	6 15 0

Echelford Communications 4 metre Equipment :		
Echelford B1/4 transmitter	...	30 0 0
Echelford M1/4 transmitter (mains or mobile)	...	40 0 0
Echelford C1/4 converter	...	10 10 0

Codar Radio Company					
CR.70A receiver	£ s. d.		CR.45RB	£ s. d.	
PR.30	19 10 0		ATS	11 7 0	
PR.30X	5 10 0		250 volt PSU	16 10 0	
R.G.10	7 4 0		12/MS PSU	8 0 0	
R.G.10X	6 15 0		12/RC	11 5 0	
CC.40	8 8 0		T28	2 7 6	
CR.45K	6 10 0		Mini-Clipper	15 10 0	
	9 10 0			1 19 6	

Partridge Electronics			Shure Microphones		
Joystick std.	£ s. d.		Shure 201	£ s. d.	
Joystick de-luxe	4 15 0		Shure 202	4 10 0	
Type 3 tuner	5 19 6		Shure 444	5 0 0	
Type 3A tuner	2 15 0		Shure 401A	10 12 6	
Type 4 tuner	3 12 6		Shure 272SK	5 10 0	
Type 4RF tuner	4 4 0			4 2 6	
	6 6 0				

SECOND-HAND EQUIPMENT

Many items in stock including: LG-300, K.W. "Viceroy," K.W. "Vanguard," Geloso 212, LG-50, Minimitter, SX-101A, AR8BD's, AR8BLF's, RA-1, Mohican, B-44MKII's, Heathkit Two-er, LA-600, EC-10, etc. Your enquiries please.

Full H.P. facilities (credit sale on small items).

Full Service facilities—receivers realigned, transmitters serviced, etc.

Illustrated Catalogue 7/6 post paid

SWANCO PRODUCTS LIMITED

247 Humber Avenue, COVENTRY

Telephone : Evenings : G3NAP Tile Hill 64279
Coventry 22714 G3PQQ Keresley 3456

G5JV REX RADIO G3JVM

NEW

TRIO JR500SE. Amateur band receiver. Latest model.	59 gns.
TRIO 9R59DE. General coverage, with mechanical filters.	35 gns.
LAFAYETTE HE30. Quite a fair receiver at the price, listed 35 gns.	20 0 0
FANTAVOX HE50. Built-in speaker	12 10 0
CODAR "Q" Multiplier	6 0 0
REVOX G37 tape recorder with twelve 10½" tapes, cost nearly £200	100 0 0
TRUVOX transistor F.M. tuner, listed £32	25 0 0
GRUNDIG I4L tape recorder in sealed carton, listed £38/17/-	30 0 0
GRUNDIG TK18 de-luxe, listed £41/19/-	32 10 0
B. & O. 2000DL tape recorder, listed £131/5/-	100 0 0

SECONDHAND

R.C.A. 4336 transmitter with valves, and spare 805 and 813	15 0 0
HAMMARLUND HX50/160 and HXL/1 linear and set new spare valves, cost over £400	200 0 0
HALLICRAFTERS SX71 double conversion receiver with matching speaker	35 0 0
PAMPHONIC F.M. tuner, self powered	10 0 0
JASON F.M. tuner, self powered	7 10 0
Pair of PAMPHONIC column speakers	10 0 0
LEAK stereo 30 transistor amplifier, listed 49 gns.	35 0 0
R.C.A. 813s. New and boxed	2 0 0

329 Kilburn Lane, London, W.9

Telephone Ladbroke 1770

SHOWROOMS AT 301 KILBURN LANE W.9

G. W. M. RADIO LTD.

RECEIVERS

ADMIRALTY B40. 640 Kc/s. to 30.5 Mc/s. 14 valves. Speaker, A.C. power unit built in. Bandwidth switched 1, 3 and 8 Kc/s. Crystal calibrator. Large vertical calibrated illuminated dial. Circuit diagram, £22/10/-. Also B41 low frequency version, 15 Kc/s. to 700 Kc/s., £10. Also B2B covers only: 150 to 300 Kc/s., 560 Kc/s. to 1.5 Mc/s., 3.9 to 10 Mc/s., 9.5 to 18.5 Mc/s., 17.6 to 30.5 Mc/s., £12/10/-, carriage 30/- per set.

B44 Mk. 3 complete with installation kits comprising aeriels, connecting cables, headphones/mike, £7/15/-, carriage paid.

HEADSETS for 19 or 22 set with mike, used 10/-, new 15/- post paid. Control boxes 8/6, post paid.

R1475. 2-20 Mc/s. Large slow motion dial, etc., with original power unit for 12 volts D.C. or 230 volts A.C. Less connecting cable, all connections marked, £10/10/-, carriage £1.

R209. 11 valves 1 to 20 Mc/s. 6 volt or 12 volt models available, £15, carriage £1.

10X TYPE CRYSTALS, 100 or 1000 Kc/s., 12/6, either post paid.

ACCUMULATORS, 6 volt 40 ampour, 35/-, carriage paid, new, 813 valve bases, new 6/-, used 5/-, post paid. 19 set rotary power unit, 12 volt D.C., 30/-, carriage paid.

METERS. 2½" round flush, D.C. 0-100 volts, 0-500 volts, 12/6 each; 0-50 Mic/amps, 25-0-25 Mic/amps, 0-500 Mic/amps, 17/6 each 0-1 Ma. in desk case, 17/6, 3½" flush round, 0-100 Mic/amps, 30/-, Ex-equipment 0-500 Mic/amps calibrated 0-15, 0-600 volts, 8/6, post 1/6 per meter.

MARCONI B2B/CR100, 100 Kc/s. to 30 Mc/s., £18/10/-, carriage £1.

R.F. UNITS type 136 (RF27) Tunable. Ideal for 4 metre conversion, 35/-, post 5/-.

BSR L050 Audio Oscillator, £5, carriage £1.

PARMEKO Speech Amplifiers, A.C. mains, Pair KT66, 15 watts output, £4/5/-, carriage paid. Admiralty 50 watt Amplifiers, A.C. mains, Four KT66, £6, carriage paid.

TX/RX 31. Complete with headset and aerial, £4/10/-, carriage paid. 88 set with headset and aerial, £4, post paid. Wavemeter/Crystal Calibrator No. 10, 45/-, post paid. Mains Transformers, standard tapped input, 340-240-0-240-340 volts at 75 mA., 0-4-5-6-3 volts 2 amps, 25/-, also 240-0-240 volts at 133 mA, 5v. 2a, 6-3v. 2a, 6-3v. 2a, 6-3v. 5a, 35/-, both post paid.

All equipment offered is complete but not tested unless otherwise stated. Carriage charges quoted are for England and Wales only.

Telephone 9097

Terms: Cash with order. Early closing Wednesday.

40-42 PORTLAND RD., WORTHING, SUSSEX

SMALL ADVERTISEMENTS, READERS—continued

WANTED: Heater transformer for an 813. An Eddystone 2½-in. ceramic coil former. And a Mosley TA-32Jr. Beam assembly.—Bowen, G3GCO, 31 The Crescent, Donnington, Wellington, Shropshire.

SELLING: Frequency Meter BC-221T, with internal voltage stabiliser, PSU and spares, £30. Solartron Type SRS-152 stabilised PSU, output variable 0-500v. DC at 200 mA, 6.3v. AC, metered and with overload relays, brand new with manual (listed £100), bargain at £30. Marconi TF-1073 precision attenuator, coverage 1-250 mc, 75-ohm, with manual and leads, brand new in carton, £15. New spares for the AR88D: mains xformer, 85s.; full set IF's, 70s.; xtal 455 kc, 20s.; AR88LF o/p xformer, 35s. Xtal for BC-221, 50s. All items plus postage. Also the official manuals for CT.45, CT.218, Type 13A 'Scope and others, s.a.e. for list. (Lancs. area).—Box No. 4582, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

COULD you Let Me Have a copy of the October and November 1965 issues of "Short Wave Magazine"? Have for Sale an R.A.E. postal course (cost me £13), at bargain price £7. (South Wales).—Box No. 4585, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

SWL's to Note! Monarch HM-1 receiver, with Codar PR-30 preselector, in excellent condition, £16. Also battery-operated MW/LW valve type portable Rx, at 30s. Cost includes carriage.—Skelcher, 52 Victoria Road, Wilton, Salisbury, Wilts.

ACCOMMODATION: In the Isle of Wight, bed-breakfast and evening meal, large TV lounge. Also a 4-berth caravan, with electricity and flush toilet.—Berden, G3RND, Bridgecourt Farmhouse, Godshill (606), Isle of Wight.

SALE: Cossor Type 1035 Mk.1 double-beam oscilloscope, in very good condition and fully working, case resprayed like new, as offered elsewhere at £35, my price £21 only, and will haggle! A bargain for someone with more space. Command Rx, coverage 6.0-9.1 mc, free with 'scope, or going separately for 30s.—Street, G3TJA, 117 Parkway, London N.W.1. (Tel: 01-387 2158).

WANTED: An R.216 receiver, with its matching PSU and instruction manual. All letters answered.—Box No. 4583, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

SELLING: K.W. Viceroy Mk.IIIA SSB/CW transmitter, with extra filter, consistently reported as having exceptional speech quality, price £100. AR88D, up to full specification, £35. Special quality 2.7 kc Kokusai mechanical filter. 1.85 shave factor, new, at £10. Carriage extra.—Edson, G3NYQ, 24 Wrenbeck Avenue, Otley (3814), Yorkshire.

SALE: National HRO, with nine coil-packs, Type 234 PSU, and manual, in good condition, price £25 or offers? Also an unmodified SCR-522 Tx/Rx, in mint condition and unmodified, offers?—Romans, 50 Lamsdown Road, Gloucester.

SALE: R.206 Rx, with PSU and Adaptor, together covering 50 kc to 30 mc continuous tuning, also Minimitter converter, comprising together receiving station in excellent working order, no mods. and as good as 10 years ago, still a bargain at £30. —Whitehead, 91 Blackpool Road, Ansdell, Latham, Lancs.

WANTED: By old-fashioned Old Timer, a CW-only Transceiver or combined transmitter/receiver, mains operated, for /A QTH. Must cover normal HF bands and have first-rate stability, with Tx QRI. AM or SSB of no interest whatever. Offers welcomed. (Birmingham area). —Box No. 4587, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

FOR SALE: K.W. Viceroy CW/SSB Tx, 10-160m., in excellent condition and complete with LP filter, aerial relav. PSU's and manual, £75 or near offer?—Firth, G3MFJ, QTHR (Tel. Bradford 43953).

SMALL ADVERTISEMENTS, READERS—continued

WANTED: Valve-voltmeter (VTVM), also an amateur-band receiver; home-built with circuit details, or 2DAF-type would do. Full information and price, pse; could collect. (Staffs. area).—Box No. 4586, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

EXCHANGE: Seven-valve Top Band Tx, VFO, pi-output, input xtal mic., PSU stabilised for VFO, metered for grid and cathode, with one meter on PSU; also receiver AR88D, in FB condition, with manual; also Xtal Calibrator, with PSU and manual, giving 10/100/1000 kc points; also SWR Bridge, with 0-500 micro-ammeter; also unmodified R.1132A receiver, with Type 3A PSU and meters; also Marconi UHF Wavemeter Type TF-643A, coverage 26 to 350 mc, complete with manual and charts. All this lot in EXCHANGE for SP-600JX or R.C.A. AR-85162 or Hammarlund HQ-170, or similar Rx in mint condition with manual, plus Avo Model 8 or 9, or good Valve Voltmeter. Disposing following valves, new and boxed: TZ40, 40s.; 807, 9s.; EBC35, 10s.; KT61, 9s.; EBC33, 6s.; 25SN7, 10s.; OS-108/10, 8s.; 6X4, 5s. 1d.; S6F17, 14s. 1d.; 6443, 14s. 1d.; 6067, 14s. 1d.; CV-4065, 15s. 1d.; F/6060, 5s. 1d.; 5899, 12s. 6d.; 3B22, 20s.; Z759, 23s. 1d.; 6ASW, 14s. 1d.; 6CL6, 8s. 1d.; 15B, 10s. 1d.; GL2D2, 19s. 1d.; OB2, 5s. 1d.; 6AU6B, 6s. 1d. Also, equipment: G1/371K, 10s. 1d.; 6AM6, 2s. 6d.; 6064, 4s. 1d.; EF92, 2s. 1d.; 12A77 2s. 1d.; 6021, 3s. 1d. Plus many others, pse enquire. Postage 6d. per valve.—Carey, 89 Pevensley Road, Bognor Regis, Sussex.

SELLING: Eddystone 940 receiver, in mint condition, with plinth speaker, £98. Light alloy rotatable 30 ft. aerial mast, with wall bracket, stay wires and p.t.f.e. bearings, £26. Shorrock Mk.V receiver, VHF/AM, aircraft band 110-144 mc, battery portable, as new, £18. Joystick de-luxe, with matching unit, £8. Buyers collect. — Ring Hunt, Walton-on-Thames 21842, after 7.30 p.m.

FOR SALE: R.C.A. AR88LF, cabinet resprayed metallic blue, RF alignment spot-on, price £21. Suitable transistorised Q-multiplier, 20s. Matching R.C.A. speaker unit, 25s. Buyer collects or pays half-carriage.—Jones, 14 Shakespeare Drive, Caldicot, Newport, Mon.

WANTED: An Eddystone bug key, in perfect condition; would consider Vibroplex, but no Japs. — Barnard, G3VSZ, Lulworth, Rushmoor Avenue, Hazlemere, High Wycombe, Bucks.

SALE: Hallioncrafters HT-40 transmitter, in mint condition, with 250-110v. auto transformer, £25. —Nicholson, 6 Craigmount Place, Edinburgh, 12. (Tel. 031-334 5126).

SINGLE-Copy Orders for February issue (4s. post paid), due out on January 26, to reach us by Wednesday 24th—despatch Thursday 25th guaranteed. — Circulation Dept., Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

FOR SALE: K.W. pi-tank, covering 10-160m., with tuning and loading condensers, plate choke and pair 6146's, 75s. the lot. Potted transformers: 504-0-504v. 240mA, plus heaters, 22s.; 6-3v. 2 amps (four times), 12s. 6d.; small plastic meters, under 2-in. square, 0-500 microamp. and 0-1 amp, 14s. each. Steel cabinet, grey hammer finish, with hinged lid, inside dimensions 15in. x 7½in. x 12in., price 25s. All carriage extra.—Edwards, G3KGN, 126 Danescroft Drive, Leigh-on-Sea, Essex.

REQUIRED: Complete 70-centimetre station; price and full details, pse.—Batten, 31A Whitton Road, Hounslow, Middlesex. (Phone 01-570 3154).

SWL, aged 20, intending to work his way round the world, seeks travelling companion, both paying own expenses. Genuine enquiries, pse.—Brown, 17 Stanley Street, Galashiels, Selkirkshire, Scotland.

SALE: Geloso converter, coverage 10 to 80m., complete with internal PSU and in good condition, price £12. — Woodhouse, G2AHY, Fellswood, The Avenue, Crowthorne, Berks.

Transistor Double Tuned I.F. Transformer, set of three (no details), 7/6.

Transistor Audio Transformers, Driver with split sec. for transformerless output, 3/-. Output and Driver to suit OCB1s, etc., 3/- each or 5/6 pair.

Epicyclic drives with dial flange ratio 6-1, new, 2/-.

Transistors, OC23, 4/6; GT45B (OC71), 1/6, 15/- doz.; matched pair, OC19s, 8/-; OC84, 2/6; P346A, 600 mc/s., 900 milliwatts, T05 case, 4/-.

Diodes, BY100, 800 P.I.V. at 550 M/A, 4/-, 35/- doz.; SX638, 3/-; ZR11, ZR12, 1S115, 3/-.

Zener Diodes, OAZ224, 3/6; OAZ247, 2/3; 1S7051A, 1S705A, 3/6.

SCRs 400 P.I.V. at 5A, 11/6. Transistor and Diodes are new, not rejects.

Paper Capacitors, 2,200 pf 400 V.W., 47,000 pf 125 V.W., .005 mfd. 500 V.W., .004 mfd. 750 V.W., .04 mfd. 250 V.W., 3d. each, 2/6 doz.

Tubular Ceramics, 470, 1,000, 2,000 pf, 3d. each, 2/6 doz.

Transistor Capacitors, .1 mfd. 50 V.W., 4 for 1/-, 12 for 2/6, 100 for 15/-.

Disc Ceramics, .01 mfd. 12 V.W., 2/6 doz.

Transistor Electrolytics, 4 mfd. 64 V.W., 50 mfd. 6 V.W., 100 mfd. 6 V.W., 350 mfd. 9 V.W., all at 6d. each, 5/- doz.; 150 mfd. 12 V.W., 9d., 7/6 doz.; 200 mfd. 25 V.W., 400 mfd. 15 V.W., 1/-, 9/- doz.

Double Gang Potentiometers, 1MΩ log, 500K lin., 100K log, 2/6 each; QGV03-10, as new, 7/6.

Printed Circuit Board, 5" x 2", 4d.; 5" x 4", 9d.; 5" x 5", 1/-; 5" x 8", 1/9 single and double sided.

Tuning Capacitors with 6-1 reduction gear 324pf + 388pf, 4/6.

Polystyrene Capacitors, 30 V.W., 20, 60, 1000, 5000pf, 5%, 3d. each, 2/9 doz., £1 100. Other voltages and values in stock.

Ferrite Rod, 5/16" dia. x 3½" long, 6d. each.

Stabilised Double Power Supplies, variable 200-300 volts D.C. at 180 M/A twice or 450 volts at 250 M/A twice (unstabilised), 6.3 volts A.C. at 6A four times, 250 volts A.C. input, fully metered black crackle case, size 15" x 8" x 12". Some single power supplies, 425-625 volts at 300 M/A. Buyer to arrange collection. A bargain at £7, used, good condition (postal service only). Please add postage. S.A.E. for lists.

A. J. H. ELECTRONICS (G8AQN)
59 Waverley Road, The Kent, Rugby, Works.

AERONAUTICAL & COMMERCIAL INSTRUMENTATION LTD.

	£	s.	d.
HRO RECEIVERS suitable for spares or rebuild Carriage £1	5	0	0
PCR RECEIVERS —similar Carriage £1	2	10	0
Resistance and Capacity Bridges (110 volt)	7	0	0
Cossor Ganging Oscillator	5	0	0
Portable Teleprinter in transit case (German origin) Carriage £1/10	15	0	0
Assorted Package Resistors Package	5	0	
Trimmers Pt. No. CX999 for AR88			6
		Each	
Ceramic Coil Formers	} Price on application		
High Voltage Capacitors	}		

Please send S.A.E. for lists.

AERONAUTICAL & COMMERCIAL INSTRUMENTATION LTD.

SPRINGFIELD ROAD, CHESHAM, BUCKS

Telephone: CHESHAM 6161/2

N. W. ELECTRICS

52 GT. ANCOATS STREET
MANCHESTER 4

CEN 6276

G3MAX

Business hours : 9 a.m.-6 p.m. Tuesday-Saturday
CLOSED ALL DAY MONDAY

THE NORTH'S
LEADING STOCKISTS

OF

EDDYSTONE RECEIVERS &
COMPONENTS

T.W. COMMUNICATORS

HALSON MOBILE AERIALS

DENCO COMPONENTS

'Q' MAX CHASSIS CUTTERS

NEW STYLE CABINETS

Removable Front and Back
16 swg. ALI. PANEL

Made to fit our standard range of Chassis
S.A.E. for list

We have tremendous stock of small components
for Valve and Transistor Circuits, Meters, Test
Equipment, G.D.O's. Field strength Meters.

Specialists in repair, alignment of all types of
communication receivers.

Stamped addressed envelope please, for any
inquiries.

Coaxial Relay, Londex Type 7026. 24 volts D.C.
19/6 each, 2/6 postage. Plugs to suit 1/- each. Ex-
equipment, postage 3 for 1/-.

Low Resistance Headphones. 100oh ms, D.C.
Brand new, boxed, 7/6. Postage 3/-.

R.A.F. Modulator Ex. TRI986 VHF Trans-
mitter. EF92-EL91-P.P.6C4. Circuit supplied,
15/-, post 4/6.

New Morse Keys, Army Pattern. With cover,
lead and Jack plug, 5/-, post 2/6.

G3SMI

G8SB

SMALL ADVERTISEMENTS, READERS—continued

SALE: KW-77 receiver, having full pre-sale service by K.W. Electronics. Little used, as 2nd string to KW-2000A, in first-class condition electrically, mechanically and appearance-wise, price £70, no offers.—Sharpe, G3UXU, QTHR. (Hemel Hempstead 54413).

MUST sacrifice Hi-Fi Gear in EXCHANGE for proven all-band Tx. Offering immaculate Heathkit LW/MW/SW AM/FM tuner and 12-watt amplifier, with preamp/gram motor supplies, 3/15 ohm output. Slight cash adjustment as necessary.—Bates, G8BBJ, 88 Penhill Road, Lancing (3338), Sussex.

FOR SALE: Woden Transformers: 500-0-500v. 150 mA, 6-3v. 4A, 5v. 3A; 320-0-320v. 150 mA, 6-3v. 3A, 5v. 2A, ex-equipment, 30s.; modulation xformer, 75w., p/p 807's into 6,000 ohms RF, two off, 20s. each; driver xformers, 6J5-p/p grids, two at 10s. each. Partridge hi-fi 30w. Type WWOFB/O/1-7, 40s.; modulation xformer, 300w., 10,000-ohm push-pull into 6,000-ohm RF, 50s. Prefer buyers collect or carriage extra. Also available Instruction Manuals: SX-28, 11s.; AR88D, 16s.; AR60T/R/S, 11s.; ET-4336B, 6s.; ET-4332B, 11s. Limited quantities, post free.—Cook, G5XB, QTHR (Tel. Kidmore End 2195).

FOR SALE: R.C.A. AR88 communications receiver, plus 6-volt battery PSU M.18319A, with spares and instructions, price £25. Valve tester and data, £5. Transformer 500-0-500v. plus LT's. 40s. (Bucks.)—Box No. 4588, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

WANTED: Faulty receiver, such as CR-100, R.107, R.1155, or what-have-you, any condition acceptable, state price, collection arranged anywhere.—Briscoe, 335 Eton Road, Ilford, Essex. (Tel. 01478 8141).

WANTED: Original handbook for the R.C.A. AR88LF receiver.—Moss, 18 Whalley Road, Wiltshire, Blackburn, Lancs.

SELLING: BC-221 in first-class condition, with professionally built-in stabilised PSU and charts, price £20. Battery-operated RQ.105s two-speed tape recorder, with all accessories, brand new, £15.—Simpson, 58 Dale Avenue, Hassocks (2394), Sussex.

WANTED: Manual for the Canadian Reception Set R.103, Mk.I, 30s. offered. Also manuals or instruction books on British, American and German Army, Navy and Air Force radio equipment.—Gee, 11 Whitehorse Lane, Steppney, London, E.1.

WANTED: Thermo-couple 0.5 amp meter, also 200 micro-amp moving coil meter.—Lewis, GW8BDV, 37 Edwin Road, St. Thomas, Exeter, Devon.

FOR SALE: General coverage receiver, NC-77X, 550 kc to 30 mc, price £12. Codar PR-30X pre-selector, 70s. Codar RQ-10, 60s. All in mint condition, buyers to collect.—Pepler, 26 Springfield, Bushey Heath, Herts.

WANTED: Several Pye High-Band Mobile Radio-telephones, suitable conversion to two metres, modified or not. Your price paid for units in good condition.—Phillips, 40 Castle Drive, Cimla, Neath (4998), Glam., South Wales.

FOR SALE: Transistor portable, VHF/MW/LW, 12in. by 6in. by 3in., in black padded leather, £8. R.C.A. AR88 Rx, in excellent condition, will deliver to 50 miles, £37. Also two new 31 Set transceivers, with headsets, £6 each. **WANTED:** Modern wobulator, valve voltmeter and signal generator covering 85 kc to 80 mc approximately; also a DC/PSU for the KW-2000A.—Lord, G3PHN, Newfield House, Moira, Burton-on-Trent, Staffs. (Tel. Swadlincote 7537).

COLLECTOR'S Items! Eleven bound volumes "Wireless World," 1922-1929, in excellent condition. Will Exchange for Collins TCS equipment or W.H.Y?—Dotchin, G3WEP/VE3CXG, 34 Princes Street, Peterborough.

SMALL ADVERTISEMENTS, READERS—continued

EXCHANGE: Hallicrafters SX-101A receiver, 15-valve dual conversion, coverage 10 to 80m., selectable sidebands, with notch filter and xtal calibrator FOR an Eddystone 940 or Hammarlund SP-600.—Woloff, 7 St. Mary's Avenue, Humberstone, Leicester.

WANTED: R.C.A. S-meter, in mint condition, for the AR88.—Hervey, 259 Lutterworth Road, Nuneaton, Warwickshire. (Tel. ONU2 4804).

SALE: K.W. Vanguard Tx and AR88D receiver, priced at £65 together, or £34 each. Can be seen and tried.—Hogan G3PUZ, 101 Radbourne Road, London, S.W.12. (Tel. 01-673 2061).

FOR SALE: Eddystone S.840A general coverage receiver, range 480 kc to 30 mc in four bands, with internal speaker, BFO and suitable for 110v. or 200-250v. AC/DC, recently realigned, electrical condition and appearance very good, price £25, with free delivery to 100 miles.—Smith, G3PZZ, 38 Leasway, Wickford (2791), Essex.

SELLING: R.C.A. AR88D, in good condition, with manual, speaker and headphones, price £27 10s. or near offer. Transport arranged in London area.—Claxton, 36 Priory Road, London, N.W.6. (Tel. GLAdstone 0209, day time).

SALE: Lafayette KT-340 (similar HE-30), twelve months old and in very good condition, price £17 or near offer?—Adkins, 72 Courtenay Avenue, Harrow Weald, Middlesex.

SELLING: Brand-new and unused Nombrex Signal Generators: Type AF-30 at £14 10s.; RF-31 at £9 10s. Also Avominor, £6, and an "Advance" valve millivoltmeter, range .001 to 300v., 4.5 mc, in mint condition (list £49), price £20. (London area).—Box No. 4590, Short Wave Magazine, Ltd., 55 Victoria Stdeet, London, S.W.1.

WANTED: Sideband Equipment in immaculate condition, such as Collins, KW-2000A, Heathkit, Sommerkamp, or similar. Also beam rotator; CSE-2A10 160m. Tx, CSE-2AR Rx, or Top Band SSB Tx, such as Cannonball. Prices and full details, pse.—Baylis, Holt Farm, Fair Oak Road, Bishopstoke, Hants. (Tel. Fair Oak 470).

WANTED: R.216 receiver, price and details.—Vink, 7 Hayes Gardens, Hayes, Bromley, Kent. (Ring 01-462 2005, weekends or evenings; HOLborn 6989 working hours).

BARGAIN! T.W. Communicator two-metre transceiver, perfect, very little used, with J-Beam halo and 4-over-4 slot-fed. All as new. Having moved QTH, activity now low. Bargain all-in at £68.—Lewis, G2BTY, 10 Agar Meadows, Caron Downs, Nr. Truro, Cornwall. (Tel. Perranarworthal 198).

STILL Available, Heathkit SB-10U Sideband Adaptor, as advertised November. Must sell, reasonable offers around £25.—Hoban, G3EGC, 96 Ashworth Lane, Astley Bridge, Bolton (51502), Lancs.

OFFERING £25-£28 for a recent Eddystone EC-10 or EB-35 (FM) receiver. (Essex).—Box No. 4589, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

SALE: Brand new unopened Trio 9R5-9DE, first reasonable offer? Also new de luxe Joystick, with 3A tuner, offers?—Parker, 43 Trafalgar Court, Tividale, Warley, Worcs.

MORSE MADE !!!
EASY !!!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2896 or send 8d. stamp for explanatory booklet to:
G3HSC/F, 45 GREEN LANE, PURLEY, SURREY.

EDDYSTONE SHOWROOM



Visit the Eddystone Showroom at Imhofs and see all the popular models on permanent side by side demonstration. You can hear and compare the models that interest you and obtain the most expert advice about this range of superb communication receivers and accessories. Same day despatch to any part of the world, tax free for export and free delivery in the U.K. After sales service second to none.


- EB35 — £60. 6. 3.
- EB36 — £54. 5. 7.
- EC10 — £53. 0. 0.
- 840C — £66. 0. 0.
- EA12 — £185. 0. 0.
- 940 — £133. 0. 0.
- 830/7 — £276. 0. 0.

Send today for full details

AT IMHOFS

Main Eddystone Retail Distributors for the London Area
Alfred Imhof Limited, Dept.11/1,
112-116 New Oxford Street, London WC1. 01-636 7878
R46

JXK CONVERTERS

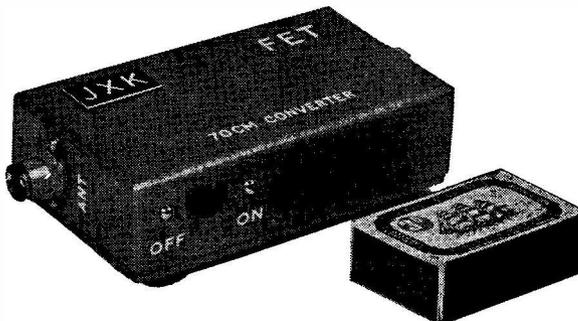

THE VERY LATEST IN TRANSISTOR VHF EQUIPMENT

- 70 Cm. CONVERTER. AF239 front-end. NF 3.5 dB. TIS34 FET mixer. IFs 28-30, 24-26, 18-20, 12-14 Mc. ... £20
- 70 Cm. PREAMPLIFIER. AF239 front-end. NF 3.5 dB. Gain 30 dB ... £10
- 2 METRE FET CONVERTER. TIS34 cascode RF. NF 1.8 dB. 2N3819 mixer. IFs 28-30, 24-26, 20-22, 18-20, 4-6, 1.8-3.8 Mc. ... £14
- 2 METRE FET PREAMPLIFIER. TIS34 cascode RF. NF 1.8 dB ... £10
- 4 METRE FET CONVERTER. TIM12 cascode RF. NF 1.8 dB. TIM12 mixer. IFs 29.1-29.7, 18.1-18.7, 2.1-2.7 Mc. ... £14
- 4 METRE FET PREAMPLIFIER. TIM12 cascode RF. NF 1.8 dB ... £10
- 10 METRE FET CONVERTER. TIM12 cascode RF. IF 2-4 Mc. ... £14
- 10 METRE FET PREAMPLIFIER. TIM12 cascode RF. ... £10
- SSB TRANSVERTER CONVERTERS. High Q breaks incorporated. 2 metre 28 Mc. IF (116 Mc. injection) 14 Mc. IF (130 Mc injection) 70 cm. 14 Mc. IF (60 Mc. and 360 Mc. injection) ... £12
- SATELLITE BAND CONVERTERS. 136-137 Mc. IF 20-21 Mc. ... £20

Post and packing 3/9 per item
2N3819 25/-, TIS34 32/-, TIM12 15/-, GM290A 15/-.

JXK CONVERTERS

Peel House, Porters Lane, Osprings, Faversham, Kent

R. T. & I. ELECTRONICS LTD.

where equipment is fully overhauled

Hammarlund SP-600-JX, 540 kc/s.-54 mc/s.	£125 (30/-)
Hammarlund HQ-170, bandspread receiver	£120 (30/-)
National HRO-50T-1, complete with tuning coils ...	£105 (30/-)
Hammarlund HQ-110-A, bandspread receiver ...	£95 (30/-)
KW Electronics KW77, bandspread receiver ...	£85 (30/-)
Eddystone 888A, bandspread receiver ...	£85 (25/-)
Star SR-600, bandspread receiver ...	£72 (30/-)
G.E.C. BRT-402-E, 150-385 ck/s. and 510 kc/s.-30 mc/s., Xtal Cal.	£70 (35/-)
R.C.A. AR88D, 540 kc/s.-32 mc/s.	£65 (40/-)
Eddystone 680/2, 480 kc/s.-30 mc/s.	£60 (30/-)
Star SR-550, bandspread receiver ...	£50 (25/-)
R.C.A. AR88LF, 75-550 kc/s. and 1.5-30 mc/s.	£42 (40/-)
Eddystone EC10, 550 kc/s.-30 mc/s., transistorised ...	£40 (20/-)
Heathkit RA-1, bandspread receiver ...	£35 (20/-)
Heathkit "Mohican" GC-1U Mk. 2, transistorised ...	£35 (20/-)
Heathkit RG-1, 600 kc/s.-32 mc/s.	£33 (20/-)
Marconi CR100, 60-420 kc/s. and 500 kc/s.-30 mc/s. ...	£30 (30/-)
Eddystone 870A, 150-380 kc/s. and 510 kc/s.-24 mc/s. ...	£20 (15/-)
Lafayette HA-63, 550 kc/s.-31 mc/s.	£20 (20/-)
LM14 Frequency Meter, complete with mains p.s.u.	£25 (20/-)
Geloso Converter ...	£15 (10/-)
Heathkit Grid Dip Oscillator, complete with coils ...	£10 (7/-)
Hallicrafters HT-37 Transmitter, SSB/AM/CW ...	£105 (50/-)
Hallicrafters SX-111 Receiver ...	£95 (30/-)
or both the HT-37 and the SX-111, for only ...	£185 (60/-)

ANY MAKE OF NEW EQUIPMENT SUPPLIED—a few examples, which are mainly in stock being:

AVOMETERS, Model 7, Mk. 2, £22/5/-; Model 40, Mk. 2, £22/5/-; Model 8, Mk. 3, £24; Model 9, Mk. 2, £24; Multiminor, Mk. 4, £9/10/-; BROWN'S HEADPHONES, Type "F", 120 ohms, 2,000 ohms, 4,000 ohms, £37/6 (3/6). Type 3C/1100, noise excluding, high quality, electrodynamic, low impedance, £6/6/- (3/6).

KW EQUIPMENT, Vespa Mk. 2 with A.C. p.s.u., £128; KV2000A, with A.C. p.s.u., £220; KV201 receiver, £105; KW1000 linear, £128.

GREEN EQUIPMENT, TMR-25 receiver, £35; Mark 5, 2-metre converters, £12.

CODAR, ATS, £16/10/-; 250/S, £8; T28, £15/10/-; PR30X, £7/4/-, etc. PARTRIDGE "Joysticks" and "Joymatch." Lists and details on request.

TRIO EQUIPMENT, Receivers JR-60-U, 540 kc/s.-30 mc/s. and 2 metres, £61/19/- (25/-). JR-500SE, bandspread, £61/19/- (10/-). 9R-59DE, 540 kc/s.-30 mc/s., £36/15/- (10/-). 9R-59, 54 kc/s.-30 mc/s., £34/13 (15/-).

Our latest list of over 50 receivers, and many other interesting items sent free upon receipt of your s.a.e.

CARRIAGE for England, Scotland and Wales shown in brackets.
TERMS: C.W.O., Approved Monthly Accounts, Hire Purchase and Part Exchange.

R. T. & I. ELECTRONICS LTD.


Ashville Old Hall, Ashville Road, London, E11 Tel: 01-539 4986

TAURUS ELECTRICAL SERVICES

Prop.: G3TED

Transistor Panels Ex New Equipment.
OC35 on Heat Sink, 8/9, post paid.
OC36 on Heat Sink, 9/3, post paid.
Mixed Transistors on Panels with Diodes, etc. Types: BCY30, 2N1500, 2N1499A, MDS31, GET882, 2S103, GET104, OC203, 12 and 15v. Zeners, etc. All guaranteed panels with at least 20 transistors, plus various components. All new Bargains at 20/-, post paid.
Tantalum 22, mid 25v, short ends, 5/- each.
Silicon Planar Transistors by Fairchild P346 N.P.N. 550 Mc/s. working, 7/6 each, post paid.
Specialist: 600Ω Amplifiers. 19" rack mounted. Mains supply. Snip, £3, post paid.
Lightweight headsets. 600Ω imp., 9/6, post paid.
12v.-24v. Fans. Bargain, 17/6, post paid.
Test Set Type 261. 175-305 Mc/s., £1/10/- delivered.
Rotary Converters, 12v. in., 250v. D.C. out., 12/6 each; 12v. in., 490v. D.C. out., 8/- each. Postage on either type 4/6.
Transistors, A.F., 3/9 dozen, post paid.
New Ferrite Pot Cores, 1/6 each or 15/- dozen, post paid.
Transistorised Morse Oscillators will drive speaker or phones, inc. battery, 18/9, post paid.
ECC81, 1/9; ECC82, 2/-; ECC83, 3/-; 6BA6, 5/-; 6AO5, 5/-, All post paid.
Magnetic Microphones. Ex-Govt., 5/-, post paid.
Sound Powered Inserts. Ideal intercom., 3/6, post paid.
New and Bored Mains Relays, 2 pole 2-way octal base, 17/6, post paid.
New OA90 or OA200 Diodes, 1/- each. Post paid.
New Nylon Jack Plugs, 2/6; Jack Sockets, 2/9 or 5/- pair, post paid.
New TTC Visconal, 500v. .05 Mfd., 4/- dozen, post paid.
Miniature Motors, 2 1/2" x 1 1/2", 12v., 6/-, post paid.
Tank Aerials. Three 4' sections making 12', 8/6. P. & P. 5/- any number. Bases, 4/6. P. & P. 2/-.
Breast Sets. Safe for Mobile Operation, 10/-, post paid.
Xtal Insets to fit above Breast Sets, 7/6. P. & P. 9d.
Creed 7B Teleprinters. Used, £15. P. & P. 30/-.
Creed 7B Teleprinters. New, £30. P. & P. 30/-.
All spare parts for Creed 7B Teleprinters in stock.
Head Sets. 19 set type or type DLR, 11/-, post paid.
Small Stand-off Insulators by Eddystone, 1/- each.
Roller Inductors (SILVER Conductors), 50/-, post paid.
46H2 Meter Rectifiers, NEV, 1/-, post paid.
Standard Army Type Morse Keys, New 5/-, P. & P. 1/6.
Dry Battery Packs, 72 and 11; and 11; 4/6 each. P. & P. any number 3/-.
New Key Switches. Less knobs 2/6. P. & P. any number 1/-.
Buzzers, 4 1/8v. D.C. or A.C., 5/6, post paid.
New Small Condensators, Not Junk. 200 for 25/-, post paid.
Multi-Test Meters, 1000Ω/V., 37/6.
Multi-Test Meters, 20,000Ω/V., £3/5/-.
Xtal Label Mikes. Complete, 6/6.
26/28 NOTTINGHAM ROAD, LOUGHBOROUGH, LEICS.
Telephone 5131

TX/RX MOBILE POWER SUPPLY UNITS

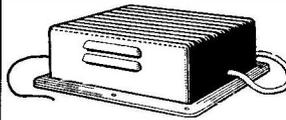

This brand new specially designed unit is ideal for powering your mobile rig. A 12 volt battery input gives an independent supply of 250 volts D.C. up to 150 watts. Also an independent supply of 500 volts D.C. at 75 watts. Designed for all mobile communication equipment. Contained in a compact louvered steel case. Full connecting leads. Also ideal for A.C./D.C. equipment, drills, and T.V. List price over £30. Our price whilst stocks last, 8 gns., carr. free.

COLLAPSIBLE AERIAL A fully adjustable highly efficient Whip aerial made to exacting specifications. Copper plated sections. Brass base. An ideal aerial for Tx/Rx use. Easily adaptable for cars, scooters, walkie-talkies. Brand new in makers boxes. Only 17/6 each, p. and p. 2/6. Two aerials for 30/-, post 2/6.

IN 5 SECTIONS
CLOSED 13'
OPEN 5'-6"

← BASE

Aerial Tuner units for Tx/Rx use. Will load almost anything. Calibrated control dial. Housed in compact steel case. Ideal for all radio amateurs and S.W.Ls, 25/- p. and p. 7/6.

We wish to buy Communication equipment. Send details for a top cash offer.

New walk-around store open at this address. Callers welcome

GLOBE SCIENTIFIC LTD Dept. No. S.W.6.
24 CAWOODS YARD, MILL STREET, MARSH LANE, LEEDS 9

BAGINTON ELECTRONICS

G3TFC (SALES) Ex ZC4JC

MARCONI AD108D RECEIVERS. Bands 2-4.2, 4.2-8.8, 8.8-18.5 mHz and 260-510 kHz. A modern type aircraft single superhet, superseded the R155 in civil aircraft, not Government Surplus. 600 kHz IF, xtal filter and tunable BFO. Valve line up: RF EP92, MIX EP91, LO EP91, 1st IF EP92, 2nd IF EP92, DET/AGC EB91, BFO EP92, LF EP92, OP EL91. Controls: Tuning, RF Gain, LF Gain, BFO Tune, AGC, Band Change, Bandwidth (1 or 4 kHz) and BFO. Size: 8 x 4 x 14 inches, weight 9 lbs. Black crackle finish, modified for 6-3 heaters, needs 250 HT, tested, in good condition, with connection data £11
A few in poor condition, untested £5

TRIO 9R59. Good condition £25

MURPHY AP10035 RX. 60-550 kHz, 1.5-30 mHz, xtal BFO, lattice filter, 2 RF, fitted S meter, speaker, resprayed £45

COMMAND RX's. Various £4

MARCONI ATU's. L or Pi £4

MARCONI P.A. UNITS. 3829B's, blower, meter £5

XTAL CONTROL UNITS. 34 xtals £3

XTALS: 2654, 2658, 2660, 2662, 2665, 2667, 2669, 2677, 2680, 2684, 2688, 2695, 2699, 2702, 2716, 2727, 2730, 2727, 2749, HC6/U, 8/- each, post free. Many others. List 1/-.

Enquiries S.A.E. Carriage extra, send £1 we will return change.

BAGINTON ELECTRONICS (Sales)

MARKET CORNER, BAGINTON, WARKS. (200 yrd. Airport)
Tel. TOLL BAR 3688 (OCO.331 3688)

Short Wave Magazine Advertising gives

WORLD-WIDE COVERAGE IN THE AMATEUR RADIO FIELD

For Space Rates apply:

ADVERTISEMENT MANAGER,
SHORT WAVE MAGAZINE, LTD.,
55 Victoria Street, London, S.W.1.
(Tel.: Abbey 5341)

MORE TITLES AVAILABLE FROM STOCK

Amateur Radio	31/-
(by F. G. Rayer)	
ABC's of Antennas	16/9
(Foulsham)	
Amateur Radio Construction Projects	21/-
Beginner's Guide to Radio	9/-
(Newnes)	
Beginner's Guide to Colour Television	15/8
(Newnes)	
Beginner's Guide to Electronics	15/6
Dictionary of Electronics	8/6
(Penguin)	
Electronic Transistor Circuits	25/9
(Foulsham)	
Elements of Radio Engineering	15/10
(Clever-Hume)	
Q. & A. On { Audio	10/-
(Newnes) { Electronics	10/-
{ Transistors	10/-
Handbook of Transistor Circuits.	36/-
(Foulsham)	
Introduction to Valves	9/4
(Liffe's)	
Radio Astronomy for Amateurs (220pp)	31/-
(by Frank Hyde)	
Remote Control by Radio	10/9
(Philips)	
Radio and Electronic Hobbies	22/-
(by F. C. Judd, G2BCX)	
RCA Silicon Power Circuits Manual	27/-
RCA Transistor Manual	27/-
RCA Transmitting Tubes	20/6
Shop and Shack Shortcuts	32/-
(by W6TNS)	
Short Wave Amateur Radio	22/-
(by PAØHH, Philips Technical Library)	
Short Wave Listening	13/2
(by J. Vastenhoud)	
Short Wave Listener's Guide	13/6
(Foulsham)	
Transistor Transmitters for the Amateur	22/-
(Foulsham)	

All prices inclusive of postage and packing

SHORT WAVE MAGAZINE
55 VICTORIA STREET : LONDON, S.W.1
PUBLICATIONS DEPARTMENT

G3LRB G3MGN
STEPHENS-JAMES LTD.

Equipment supplied by KW Electronics, Sommerkamp, Hy-Gain, Codar, Joystick, Hallcrafters, TW Electronics, National, Drake, Collins, Electroniques, Lafayette, Eagle, Heathkit.

KW2000A, £220 ; KW Vespa, £128 ; KW Linear, £128.
HY-GAIN range of Verticals, Tri-bander and mono-bander beams.
SOMMERKAMP "F" Line. FR100B, £125 ; FL2000B, £145 ; FL1000, £100.

Receivers and Transmitters by **DRAKE** and **HALLCRAFTERS**.
New **PAROS** 80-40-20m. Transceivers, complete, £125.

BXI Towers. 2 sections, 50ft., £120 ; 3 sections, 60ft., £155 delivered.

TW ELECTRONICS 2 and 4 metre transmitters and converters. Communicators and transverters.

LA FAYETTE and **TRIO** receivers. **CDR** antenna rotators. **SHURE** microphones 201 and 444. Crystal mics, 15/- . **H.P.** filters, 18/6. Cabinets, chassis, diecast boxes, panel meters, co-ax cable.

EDDYSTONE EC10, £40. **EAGLE** RX60N, £12/10/- . **KW77** Rx., £70. **EDDYSTONE** 888A "S" meter and mounting blocks, £70. **KW** Viceroy Mk. 3, £90. **KW** SWR meter, £6. **NCX3** + A.C. P.S.U., £110.

NEW ! G-WHIP. Single and duo-bander mobile antennas. Lower price than any other on market. Amazing results. **GW3DZJ/M** worked : VS6DO, 5/6 ; VK6XX, 5/7 ; IA3LVA, 5/8 on 10m. Lightweight design. Tri-Bander for 10-15-20m.

Send S.A.E. for full details.

H.P. and Credit terms. Part exchanges. Carriage and post extra all items. S.A.E. enquiries please. Delivery and installations arranged.

After sales service. Half day Wednesday.

70 Priory Road, Anfield, Liverpool, 4

Telephone : 051-ANF-7829

No parking problems. We are approximately 1/2 mile from the Liverpool and Everton Football grounds.

AMATEUR ELECTRONICS

G3FIK

	£	s.	d.
AR88D RECEIVERS. We have excellent stocks of these, graded according to physical condition, but in all cases in fully aligned and operational order. <i>from</i>	45	0	0
AR88LF RECEIVERS. As above <i>from</i>	35	0	0
BC221 complete with charts and internal power supply <i>carriage paid</i>	21	0	0
LABGEAR TOPBANDER. Excellent and unmarked <i>carriage paid</i>	16	0	0
TW COMMUNICATOR 160. First class order and appearance <i>carriage paid</i>	45	0	0
DX100 TRANSMITTER COMPLETE WITH SB10-U SSB ADAPTOR <i>carriage paid</i>	75	0	0
BC-1031A PANORAMIC ADAPTOR. 455 Kc. input, 200 Kc/s. sweep absolutely unmarked and mint <i>carriage paid</i>	26	0	0
HARTLEY 13A OSCILLOSCOPES. Tested and complete	25	0	0
FL8 FILTER UNITS <i>carriage paid</i>	12	6	
COLLINS EQUIPMENT SUPPLIED TO ORDER SOMMERKAMP FROM STOCK. All models in the Sommerkamp F line available at current prices.			
TRIO JR-500SE. AMATEUR BAND RECEIVERS	59	gns.	
TRIO 9R-59DE. GENERAL COVERAGE RECEIVERS	35	gns.	
Please note that these excellent value and interesting receivers are available from stock at the pre-devaluation price.			
R209 RECEIVERS. A few to clear, at ... <i>carriage paid</i>	9	10	0
BC312 RECEIVER. Complete with separate power supply and Eddystone speaker unit	15	0	0
CT52 MINIATURE OSCILLOSCOPES <i>carriage paid</i>	22	10	0

The above is a representative selection from our large and growing stock of quality equipment and components. When in the Midlands we shall be pleased to see you at our showrooms which we feel sure you will find are well worth a visit.

S.A.E. please with enquiries.

Hire Purchase available.

518-520 Alum Rock Rd., Alum Rock, Birmingham 8

Telephone: EAST 1497.

"DX ZONE MAP"

In four colours, on durable paper for wall mounting, 35in. wide by 25in. deep. Giving essential DX information—bearing and distance of all parts of the world relative to the U.K. The 40 Zone areas into which the world is divided for Amateur Radio purposes, with major prefixes listed separately. Distance scale in miles and kilometres. Time scale in GMT. Marking of Lat./Long. close enough for accurate plotting. About 1,000 place names, mainly the unusual ones, and most of the rare islands.

Revised to October 1966

Immediate delivery from stock

Price 14s. 9d.

including postage and special packing in postal tube to avoid damage in transit.

Publications Dept.

Short Wave Magazine Ltd., 55 Victoria Street,
London, S.W.1. (01-222 5341/2.)

CURSONS TRANSISTORS

ALL GUARANTEED

- 1/- each. BAY31, BAY50, DK10, OA70, OA81.
2/- each. XA101, XA102, OC71, OC72, OC81, OC81D, OC44, OC45, GET16, FST3/1, ACY22.
3/- each. OC139, OC140, 2N706, 2N708, 2N2894, BY100, RAS310AF, 2N914, BSY26, BSY27, BSY95A, AFZ12, BFY18, BFY19, BFY26.
7/6 each. RAS508AF, CRS3/40, BLY10, BLY11, BUY10, BUY11, ADY22, ADY23, ADY24, OC26.

ZENER DIODES

- 3.9v. to 26v., 1/2w., 3/- each. 1.5w., 4/-, 7w., 5/- each.

D. Cursons

78 BROAD STREET, CANTERBURY, KENT
S.A.E. LATEST NEW LIST

WE BUY

Surplus Components, Equipment, Transistors, etc.
ANY QUANTITY—PROMPT PAYMENT

Especially Required: Tubular Relays, G.E.C. Relays, Notched Relay Contacts, in any condition. S.A.E. details.

Special Offer: 3 valve RF24 Converters. Covering 15 and 10 metres (20 to 30 Mc/s.). Five preset frequencies, 7 Mc/s. I.F., 6/- each plus 6/- postage.

ELEY ELECTRONICS
112 Groby Road, Glenfield, Leicester

CURSONS TRANSISTORS

ALL GUARANTEED

- 1/- each. BAY31, BAY50, DK10, OA70, OA81.
2/- each. XA101, XA102, OC71, OC72, OC81, OC81D, OC44, OC45, GET16, FST3/1, ACY22.
3/- each. OC139, OC140, 2N706, 2N708, 2N2894, BY100, RAS310AF, 2N914, BSY26, BSY27, BSY95A, AFZ12, BFY18, BFY19, BFY26.
7/6 each. RAS508AF, CRS3/40, BLY10, BLY11, BUY10, BUY11, ADY22, ADY23, ADY24, OC26.


ZENER DIODES

- 3.9v. to 26v., 1/2w., 3/- each. 1.5w., 4/-, 7w., 5/- each.

D. Cursons

78 BROAD STREET, CANTERBURY, KENT
S.A.E. LATEST NEW LIST

NEW 1968 PRICES

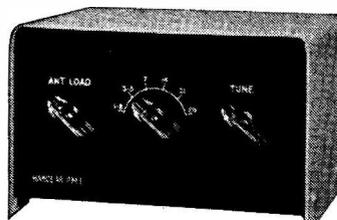

PRESELECTOR

This unit is a pentode pre-amp covering 1.6 to 32 Mc/s. completely with a built in Pi tank antenna tuner. P/Pack incorporated, complete and ready to use.

£5.18.0.

Also supplied with a built-in xtal Calibrator giving 1 Mc/s. points over the entire range covered.

£9.18.0.

HAMGEAR ELECTRONICS
29 CARLYLE ROAD, NORWICH

Send for four-page illustrated leaflet on this equipment.

"CALLBOOK"

WINTER EDITION

Now Available

Limited Quantity Only

Known the world over as the CALLBOOK, this comprehensive reference lists about 260,000 licensed radio amateurs in the United States Directory and 140,000 or more in the rest of the world (contained in the "DX Section"). The listings grow with every issue! In the new U.S. Section, licence classifications are now being shown. Each issue is an entirely new book with revised listings of new licences, names and addresses. The CALLBOOK also includes much incidental DX information. Every amateur operator and SWL needs the latest CALLBOOK to get the most out of Amateur Radio.

DX Listings 42/6 US Listings 64/6

The two together, covering the World, £5/2/6

Available only from

Publications Dept.,

SHORT WAVE MAGAZINE

55 Victoria Street, London, S.W.1

01-222 5341

ERSIN

Multicore
5 CORE SOLDER

for quick,
easy, reliable
soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required. Ersin Multicore Savbit Alloy also reduces wear of copper soldering iron bits.



SIZE 5 HANDY SOLDER DISPENSER

Contains 12 ft. coil of 18 s.w.g. Ersin Multicore Savbit Alloy. 2/6 each.



SIZE 15 SOLDER DISPENSER

Contains 21 ft. coil of 60/40 Alloy, 22 s.w.g. Ideal for small components, transistors, diodes, etc. 3/- each.



SIZE 12

Ideal for home constructors. Contains 102 ft. of 18 s.w.g. Ersin Multicore Savbit Alloy on a plastic reel. 15/- each.



BIB MODEL 8 WIRE STRIPPER AND CUTTER

Strips insulation cleanly and quickly, fitted with unique 8 gauge wire selector. Plastic handles. 9/6 each.

From Electrical and Hardware shops. If unobtainable, write to:
Multicore Solders Ltd., Hemel Hempstead, Herts.

Fast Mail Order for the Amateur Radio Enthusiast!

AERIAL EQUIPMENT

TWIN FEEDER. 300 ohm twin ribbon feeder similar K25, 8d. per yard. 75 ohm twin feeder, 6d. per yard. Post on above feeders, 2/- any length.

COPPER WIRE, 14G, H/D, 140ft., 30/-; 70ft., 16/-, Post and packing 3/3. Other lengths pro rata.

FEEDER SPREADERS. 6" Ceramic type F.S., 10d. each. Postage 2/6 up to 12.

CERAMIC CENTRE PIECE for dipoles Type AT, 1/6 each. P. & P. 1/-.

2 METRE BEAM, 5 ELEMENT W.S. YAGI. Complete in box with 1" to 2 1/2" masthead bracket. Price 56/-, P. & P. 4/-

SUPER AERAXIAL, 70/80 ohm coax, 300 watt very low loss, 2/3 per yard. 50 ohm 300 watt, 2/6 per yard. P. & P. 2/6.

TOUGH POLYTHENE LINE, type ML1 (100lb.), 2d. per yd. or 12/6 per 100 yds. Type ML2 (220 lb.), 4d. per yd. or 25/- per 100 yds., ML4 (400 lb.), 6d. per yd. Ideal for Guys, L.W. Supports, Halyards, etc. Postage 1/6 on all line.

MIDLAND AGENTS FOR EDDYSTONE

Receivers & Components

Transmitters, Receivers and Sundry Equipment by

- KW ELECTRONICS
- HALSON
- T.W. ELECTRONICS
- CODAR RADIO
- PARTRIDGE

NEW BOXED VALVES. 3/6 each, 4 for 10/-, P. & P 2/-.

Types 6N7GT, 6AB7, 6AC7, 6SK7, 6SF7, 6SH7, 6F7, 956, U10, MSP4, 6G6G.

ABSORPTION WAVEMETERS. 3-00 to 35-00 Mc/s. in 3 Switched Bands. 3-5, 7, 14, 21 and 28 Mc/s. Ham Bands marked on scale. Complete with indicator bulb. A MUST for any Ham Shack. ONLY 25/- EACH. Post free.

SHORT WAVE KITS. One valve only, 45/-, phones, ant, and datts, 40/- extra if required. Ideal for Junior op.

VARIABLE CONDENSERS. All brass with ceramic end plates and ball race bearings. 50pF, 5/9; 100, 6/6; 160, 7/6; 240, 8/6. Extension for ganging. P. & P. 2/-.

SEALED RELAYS, 12v. 105Ω Coil. Type A, 4 Pole, C.O. 15/-, Type B, 2 Pole, C.O. + 2 Pole Norm. on, 12/6. P. & P. 1/6.



The Widest Range in the Midlands

★ HIRE PURCHASE

★ PART EXCHANGE

CHAS. H. **YOUNG** LTD.

At your service G2AK, G3LAY, G3VFX

Please print your address. No C.O.D. under £1.

'phone 021-236-1635

170-172 Corporation Street,

Birmingham 4

MAPS

AMATEUR RADIO MAP OF WORLD

Mercator Projection — Much DX Information — In Colour. Second Edition, 8s. 9d.

GREAT CIRCLE MAP

(Black and White only) 5s. 6d. (See S.W.M. page 661, Jan. '67)

DX ZONE MAP

(Revised to October 1966) 14s. 9d. (See S.W.M. page 643, Jan. '67)

RADIO AMATEUR MAP OF THE U.S.A. AND NORTH AMERICA

State boundaries and prefixes, size 24in. by 30in., paper. 7s. 3d.

RADIO AMATEUR'S WORLD ATLAS

In booklet form, Mercator projection, for desk use. Gives Zones and Prefixes, 11s. 0d.

CALL BOOKS

"G's" only 6s. 7d.

WINTER EDITION

"DX Listings," £2/2/6. "U.S. Listings," £3/4/6. The two together, covering the World, £5/2/6.

All prices inclusive of postage and packing

LOG BOOKS

A.R.R.L.

(Spiral bound), 9s. 6d.

A.R.R.L.

(Minilog) 4in. by 6in., 5s. 6d.

R.S.G.B.

Listeners and Observers 7s. 0d. Standard 7s. 0d.

MORSE COURSES

G3HSC Rhythm Method of Morse Tuition

Complete Course with three 3 speed L.P. records with books 84/-

Beginner's Course with two 3 speed L.P. records with book 60/6

Single, 12" L.P. Beginner's with book 50/-

Single, 12" L.P. Advanced with book 50/-

Three speed simulated GPO test. 7in. d.s. E.P. record 15/-

Available from **SHORT WAVE MAGAZINE**

Publications Dept., 55 Victoria Street, London S.W.1 . 01-222 5341

(Nearest Tube Station, St. James's Park)

TECHNICAL PUBLICATIONS LATEST ISSUES

	Post Free
AMATEUR RADIO (by F. G. Rayer)	31s. 0d.
AMATEUR RADIO ANTENNA HANDBOOK. 157 pages (by H. D. Hooton, W6YTH) ..	25s. 0d.
ANTENNA HANDBOOK Vol. 1, by K7GCO (Cowan Publication).....	30s. 0d.
ANTENNA ROUND-UP (by CQ).....	25s. 0d.
ANTENNA ROUND-UP (Vol. 2).....	30s. 0d.
ANTENNA HANDBOOK (A.R.R.L., 10th Edition).....	19s. 6d.
BASIC MATHEMATICS FOR RADIO AND ELECTRONICS.....	18s. 3d.
BEAM ANTENNA HANDBOOK, 3rd Edition	30s. 0d.
BETTER SHORT WAVE RECEPTION.....	24s. 0d.
CHART OF INTERNATIONAL FREQUENCY ALLOCATION—GENEVA (Official 10 Kc to 40 Gc), New Edition. 24in. x 16in. wide folding pages	31s. 6d.
COMMUNICATION RECEIVERS.....	3s. 5d.
CQ ANTHOLOGY 45-52.....	16s. 9d.
CQ ANTHOLOGY (1952-1959).....	25s. 0d.
COURSE IN RADIO FUNDAMENTALS (A.R.R.L.)	10s. 6d.
ELECTRONIC CIRCUITS HANDBOOK Vol. I.....	24s. 0d.
ELECTRONIC CIRCUITS HANDBOOK Vol. II (Tom Kneitel).....	24s. 0d.
FOUNDATIONS OF WIRELESS.....	22s. 6d.
GUIDE TO AMATEUR RADIO.....	5s. 9d.
GUIDE TO BROADCASTING STATIONS.....	6s. 9d.
HAMS INTERPRETER.....	8s. 6d.
HANDBOOK OF HAM RADIO CIRCUITS (by W9CGA).....	25s. 0d.
HINTS AND KINKS Vol. 6.....	11s. 6d.
HOW TO BECOME A RADIO AMATEUR (A.R.R.L.).....	10s. 0d.
HOW TO IMPROVE SHORT WAVE RECEPTION.....	20s. 0d.
"HOW TO LISTEN TO THE WORLD".....	27s. 3d.
LEARNING MORSE (Iliffe).....	2s. 3d.
THE MORSE CODE FOR RADIO AMATEURS by G3ACC.....	1s. 9d.
LEARNING THE RADIO TELEGRAPH (A.R.R.L.).....	4s. 6d.
MOBILE HANDBOOK (Published by CQ).....	24s. 0d.
MOBILE MANUAL (Published by A.R.R.L.).....	24s. 6d.
NEW RTTY HANDBOOK.....	32s. 0d.
NEWS FROM AROUND THE WORLD 1967.....	15s. 6d.
NEW SIDEBAND HANDBOOK (by CQ).....	25s. 6d.
NOVICE HANDBOOK, Tx and Rx, 150 pages.....	23s. 6d.
OPERATING AN AMATEUR RADIO STATION (A.R.R.L.).....	2s. 8d.
PORTABLE TRANSISTOR RECEIVER.....	3s. 0d.
QUAD ANTENNA.....	23s. 0d.
RADIO AMATEUR EXAMINATION MANUAL.....	5s. 9d.
RADIO AMATEUR HANDBOOK (A.R.R.L.), 1967.....	Paper Edition 44s. 0d. Buckram Edition 54s. 0d.
RADIO AMATEUR OPERATOR'S HANDBOOK (Data Publications).....	5s. 6d.
RADIO AMATEUR CALL BOOK (U.K. only, 1967).....	6s. 7d.
RADIO CONTROL FOR MODELS (F. C. Judd).....	16s. 0d.
RADIO DATA REFERENCE BOOK.....	14s. 0d.
RADIO HANDBOOK (Wm. I. Orr) (17th Edition).....	88s. 6d.
RADIO VALVE DATA (Iliffe), Eighth Edition.....	10s. 7d.
SERVICE VALVE AND SEMI-CONDUCTOR EQUIVALENTS (R.S.G.B.).....	5s. 6d.
SSB EQUIPMENT.....	3s. 3d.
S9 SIGNALS.....	8s. 6d.
SHORT WAVE LISTENING.....	13s. 2d.
SHORT WAVE RECEIVERS FOR THE BEGINNER (Data Pubs.).....	6s. 6d.
SHORT WAVE RADIO AND THE IONOSPHERE (Iliffe).....	11s. 9d.
SINGLE SIDEBAND FOR THE RADIO AMATEUR (A.R.R.L.) (4th Edition).....	22s. 6d.
SURPLUS CONVERSION MANUAL Vols. 1, 2 and 3.....	each 24s. 6d.
SURPLUS HANDBOOK (E. & E.).....	24s. 6d.
SURPLUS SCHEMATICS (Published by CQ).....	21s. 0d.
SURPLUS CONVERSION HANDBOOK (including "Command Sets").....	24s. 0d.
TECHNICAL TOPICS FOR THE RADIO AMATEUR.....	10s. 8d.
TELEVISION EXPLAINED (Iliffe).....	13s. 6d.
TRANSISTOR RADIO HANDBOOK (Editors and Engineers).....	45s. 0d.
UNDERSTANDING AMATEUR RADIO.....	19s. 6d.
VHF HANDBOOK (Orr W6SAI).....	24s. 0d.
VHF MANUAL by A.R.R.L.....	21s. 6d.
VHF FOR THE RADIO AMATEUR (CQ).....	28s. 0d.
WORLD RADIO AND TV HANDBOOK, 1967.....	33s. 0d.

Available from **SHORT WAVE MAGAZINE**
 Publications Dept., 55 Victoria St., London S.W.1 • 01-222 5341
 (Counter Service, 9.30-5.15, Mon. to Fri.) (Nearest Tube Station: St. James's Park)